

SEPTEMBER 1973

electronics today

INTERNATIONAL

20p

SPECIAL OFFER:

BUILD THIS PROJECT
FOR UNDER £6!



FULL DETAILS ON OUR
**Electronic
Transistorised
Ignition**



THE
SOLAR SOLUTION

— IS IT THE ANSWER
TO THE ENERGY
CRISIS?

PLUS:

CALCULATORS—THE INSIDE STORY
DIGITAL ALARM CLOCK PROJECT

HI-FI... CONSTRUCTION... COMMUNICATIONS... DEVELOPMENTS

Awaken to the sound of Teleton



Join the procession
in Aida.
Smell 1812 gunsmoke.
Shiver
on Bare Mountain.
*Awaken to the
sound of Teleton.*

There's a new world of high fidelity in a Teleton sound system; with the GA-202 amplifier at its heart to bring you new standards of purity, new heights of quality in the faithful reproduction of the world's greatest music.

The Teleton GA-202 combines all the latest advances in hi-fi technology—calibrated slider controls for bass, treble and channel volume, hi-cut filter, loudness contour, headphones socket, tape and auxiliary inputs, to give you 15 watts per channel (RMS) at under one per cent distortion, 30–30,000 Hz—the soaring choruses and the whispers of a cathedral inside an elegant walnut and brushed aluminium cabinet.

Listen to the Teleton GA-202—your ears have been asleep. Price £49.94 inc VAT, recommended retail. Teleton Electro (U.K.) Co. Ltd., Teleton House, Waterhouse Lane, Chelmsford CM1 3DW. Tel: Chelmsford 62442.

Teleton
Sound Sense

electronics

TODAY INTERNATIONAL

SEPTEMBER 1973

Vol 2 No.9

main features

THE WATERGATE BUGGING	27
<i>Scoop report tells how it was done and with what equipment</i>	
SETTING UP PA SPEAKERS	30
<i>Complete guide to choosing, installing and connecting PA speakers</i>	
THE SOLAR SOLUTION	44
<i>ETI investigation looks into one solution for the energy crisis</i>	
PERSONAL CALCULATORS	54
<i>The inside story and how they work</i>	
TRANSDUCERS IN MEASUREMENT AND CONTROL	60
<i>Final part discusses measurement of force and related topics</i>	

projects

TIMTRONIC	16
<i>Digital Alarm/Calendar Clock uses a single chip</i>	
ETI ELECTRONIC TRANSISTORISED IGNITION	36
<i>A lot of benefits from a small outlay</i>	


news & information

EDITORIAL -5; NEWS DIGEST -7; INPUT GATE -34;
PREVIEW OF NEXT MONTH'S ETI -43; ELECTRONICS
TOMORROW -69; COMPONENTS NEWS -71; EQUIPMENT
NEWS -73; AUDIO NEWS -75; DX MONITOR -81;
TECH-TIPS -82.


Cover: The ETI Electronic Ignition System has been fully tested to check out the performance. The photograph shows one of the tests on a rolling-road which was made on the prototype.



Page 16

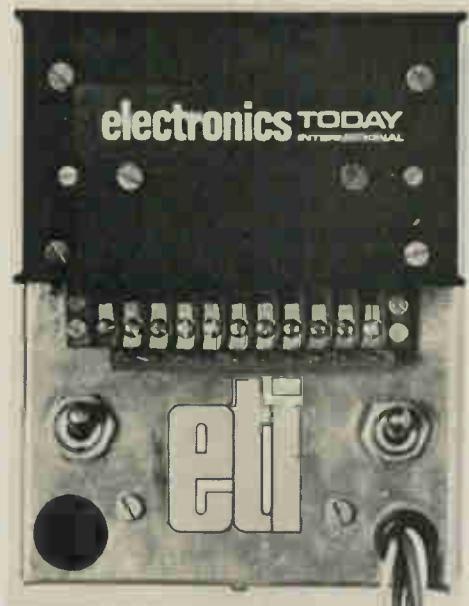

Page 36

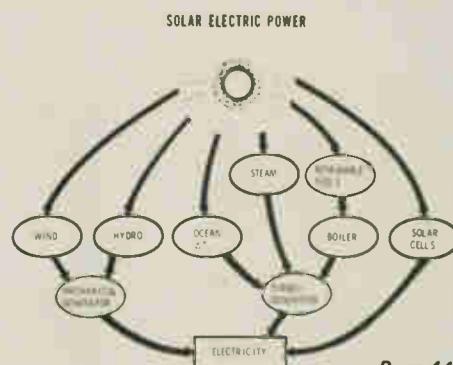

Page 44

EDITORIAL & ADVERTISEMENT OFFICES
36 Ebury Street, London SW1W 0LW

Phone: 01-730 2136/9

Published by WHITEHALL PRESS LTD

Printed in England by: Alabaster Passmore & Sons Ltd, London & Maidstone

INTERNATIONAL ASSOCIATES: Modern Magazines (Holdings) Ltd, 21-23 Bathurst Street, Sydney 2000. Phones: 26-2296 22-6129. ACP, Room 401, 1501 Broadway New York, USA. Bancho Media Service, 15 Sanyecho, Shinjuku-Ku Tokyo, Japan. Distributed by: Argus Press Ltd

© Copyright Worldwide

Subscription rates per year: Home-£3.60 Overseas-£4.00.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY £1.05

POST & PACKING 4s EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes 1000 PIV lamp plastic	55p
B81	10	Reed Switches 1 long High speed P.O. type	55p
B99	200	Mixed Capacitors - Approx. quantity counted by weight Post and packing 15p	55p
H4	250	Mixed Resistors Approx. quantity counted by weight Post and packing 15p	55p
H7	40	Mixed Resistor Mixed types and values	55p
H9	2	OCP71 Light Sensitive Photo Transistor	55p
H28	20	OC200 1 2 3 PNP Silicon uncoated TO 5 case	55p
H30	20	1 Watt Zener Diodes Mixed Voltages 6.8-43V	55p
H35	100	Mixed Diodes Germ. Gold bonded etc Marke and Unmarked	55p
H38	30	Short Lead Transistors NPN Silicon Planar types	55p
H39	6	Integrated Circuits 4 Gates BMC 962 2 Flip Flops BMC 945	55p
H40	20	BFY50 2 2N696 2N1613 NPN Silicon uncoated TO-5	55p
H41	2	Si Power transistors comp pair BD131 132	55p
UNMARKED UNTESTED PAKS			
B1	50	Germanium Transistors PNP AF and RF	55p
B66	150	Germanium Diodes Min. 150 type	55p
B83	200	Trans. manufacturers' rejects all types NPN PNP Sil. and Germ.	55p
B84	100	Silicon Diodes DO 7 equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub min IN914 and IN916 types	55p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	55p
H15	20	Top Hit Silicon Rectifiers 750mA Mixed volts	55p
H16	30	Experimenters' Pak of Integrated Circuits Data Supply	55p
H17	15	3 Amp. Silicon Stud Rectifiers mixed volts	55p
H20	20	BY126 7 Type Silicon Rectifiers 1 amp plastic Mixed volts	55p
H34	15	Power Transistors PNP, Germ. NPN, Silicon TO-3 Can	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each

BI-PRE-PAK LTD

Co. Reg No. 820919

OVER
1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Silicon planar plastic transistors

Unmarked, untested, factory clearance. A random sampling showed these to be of remarkable high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8, BC168/9 etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44 P. & P. 11p/1.00.

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-S can.

TYPE "B" PNP Silicon, plastic encapsulation.

TYPE "E" PNP Germanium AF or RF.

TYPE "F" NPN Silicon plastic encapsulation.

TYPE "G" NPN silicon similar ZTX 300 range.

TYPE "H" PNP silicon similar ZTX 500 range.

8 RELAYS FOR VARIOUS TYPES £1.10
P & P 27½

Our famous PI Pack is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P.I. Only 55p. 11p P & P on this Pak.

A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

ELECTRONIC TRANSISTOR IGNITION

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features:

Transistor and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility.

This project is a "star" feature in this issue.

Our kit is recommended by the ETI magazine.

Complete kit including p&p £7.92

Ready built and tested unit £3.02 extra

FREE

CATALOGUE
FOR
TRANSISTORS,
RECTIFIERS,
DIODES,
INTEGRATED
CIRCUITS,
FULL PRE-PAK
LISTS

PLASTIC POWER TRANSISTORS

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.
1-12 13-25 26-50
40 Watt 22p 20p 18p
90 Watt 26p 24p 22p

Range 2. VCE. Min 40. HFE Min 40.
1-12 13-25 26-50
40 Watt 33p 31p 29p
90 Watt 38p 36p 33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of ICs at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each. Now new low 16 pin type at 18p each profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes: 40p

This includes many thousands of British, U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor Data Book 9th Edition; p. & p. 23½p. Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. 75p

Send for lists of publications


N.B. Books are void of VAT

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

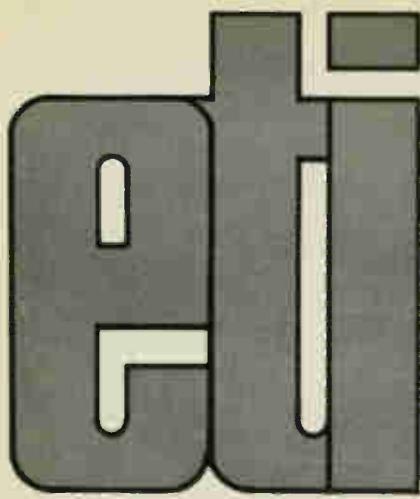**ALL PRICES INCLUDE 10% VAT
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 11p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE.**



HALVOR MOORSHEAD

Editor

ALEX MELLON

Advertisement Manager

SID GLADWIN

Production Manager

Electronics Today International

36 Ebury Street

London SW1W 0LW

01-730 2136

International Editions

COLLYN RIVERS

Editorial Director

Australia

BRIAN CHAPMAN

Technical Editor

WENDY ROY

Assistant Editor (Hi-Fi)

BARRY WILKINSON

Engineering Manager

Electronics Today International

Ryrie House, 15 Boundary Street

Rushcutters Bay 2011

Sydney, Australia

France

DENIS JACOB

Editor-in-chief

CHRISTIAN DARTEVELLE

Editor

Electronique Pour Vous

International

17 Rue de Buci

Paris, France

SOLAR SOLUTION

The feature 'Solar Solution — is it the answer to the energy crisis' — is one that we have been working on for two months. During this time there have been a number of articles and TV programmes covering the same subject but our research has been very extensive and the article includes many unpublicised activities.

To obtain the necessary material we have literally made contacts all over the world: Britain, U.S.A., Australia, France, Japan, India, Israel, Soviet Union, Egypt and South Africa. We have also interviewed a number of researchers in this field.

What has struck us has been the enormous activity that has been going on, most of it initiated within the last two years. However, one point stands out: much of the work has been conducted in isolation. Many of the researchers we spoke to were unaware of the activities of almost identical work being pursued elsewhere in the world.

Interest in harnessing the sun's energy is growing and, to say the least, it seems a pity that co-operation is, as yet, on a limited scale. Our technology has reached the stage when any research into a new field is extremely expensive and this is surely an ideal field for international co-operation. Harnessing the sun's energy must be one of the few fields where there can be no military applications (we can think of none anyway) and it is also one which could help the underdeveloped nations. These nearly all lie in the equatorial regions which are best suited to harnessing solar energy. Similarly, these underdeveloped nations do not have vast plants and capital tied up to produce their electricity from fossil fuels and, starting from scratch, they would seem to be ideal areas to develop.

We have been careful in our presentation of this subject to avoid overstating the case for solar energy—that is our reason for having the question mark in the sub-title. We have drawn attention to the problems as well as to the benefits. Nevertheless, it is certainly a field worth pursuing and one in which international co-operation is needed. Let us hope that this can be achieved before too long. —H.W.M.

J. T. EDEN ELECTRONICS

TRANSISTORS

DIODES AND RECTIFIERS

DIODES AND RECTIFIERS

INTEGRATED CIRCUITS

ZENER DIODES

All preferred voltages from 20 to 330
5% Tolerance 400 MW (ISO 7) 12p 15%
W (ISO 16) 20p 10W (ISO 10) 20p

RESISTORS

RESISTORS

L C SOCKETS

14 pin, 14p.
16 pin, 16p.

Please send your remittance with order: cheques, P.O.'s, M.O.'s should be made payable to J. T. EDEN ELECTRONICS and crossed. Cash should be sent by registered post. Add 12p. for post and packing charge: orders are despatched by first class post. If an item is temporarily out of stock and is not expected in from our supplier for more than a week, a credit note is issued for the value and should be included with your next order. We can also despatch the item to you when it arrives and not charge you for the post and packing. If you would prefer, we can also refund the amount to you. Please let us know what you would like us to do.

As V.A.T. is chargeable, please add 10% of the total value (that includes the 12p. post and packing charge). In order to try and keep prices down we have decided to charge only 5% to orders of £5 and over, so if you just include 5p. in the pound, we will pay the rest in the form of a discount to you.

Finally, if you think there are any significant omissions or lines you like us to stock, we will try to include them in our new catalogue which will include capacitors, potentiometers, meters, kits and more semi-conductors.

kits and more semi-conductors.

ORDERS TO

J. T. EDEN ELECTRONICS, P.O. Box 5, LANCASTER LA1 3HZ.

neuws digest


A NEW TRANSISTOR FOR 3W AND 3GHz

The photo shows a UHF broadband power transistor for 3GHz and 3W mounted on a film-type circuit measuring 0.6 x 0.6mm. The two wires are used to connect emitter and base of the component. The transistor design made visible in the photo is typical for microwave technology: close spacing and strip widths in the um range ensure a favourable emitter edge length to collector-base capacitance ratio. The resistors arranged on the left in front of each emitter strip are used to keep the current load uniform and in this way to achieve a good overall HF quality factor. The high frequencies — research has shown that a value of 4GHz is at present possible — and a drive current of up to 0.1A are obtained by extremely shallow surface diffusion of boron and phosphorus ions and by multilayer metallization on a gold base, which also results in high reliability. The silicon planar system is protected against the effects of humidity by nitride passivation.



The new transistor was photographed by the "Autoscan" sampling electron microscope, which has a greater depth of field and a resolution several powers of ten higher than an optical microscope. In this way very favourable methods of assessing new semiconductor components present themselves, in which conventional electric measurements can be supplemented by an electron-optical check of the fine structure.

"INTELLIGENT" SATELLITES

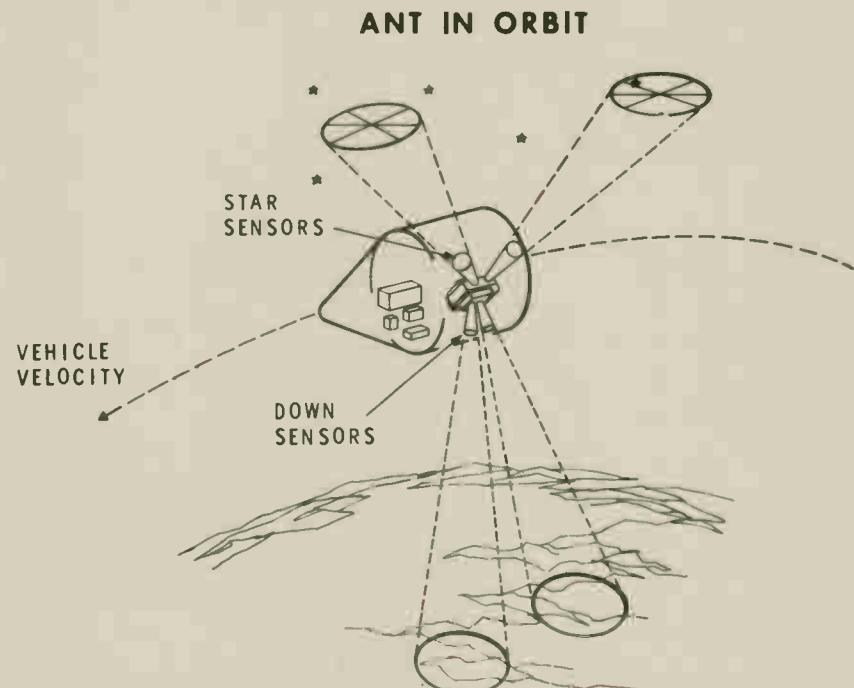

A technique for enabling satellites to find their own way around the earth without having to rely on ground tracking stations is being designed at Honeywell's Aerospace Division under contract from the U.S. Air Force Space and Missile Systems Organisation.

The technique — called Autonomous Navigation Technology (ANT) — will enable a satellite to identify its position even before it completes one full orbit of the earth. This particular solution to satellite self-navigation, along with two others being developed by other companies, will be considered by the U.S. Air Force for possible equipment development.

The ANT concept calls for use of a gravitational model of the earth, stored in a satellite's computer memory, which will be continually refined by data provided by optically sensing various earth landmarks. A major part of the Honeywell effort will be to develop a laboratory prototype of the landmark sensing device, called a Down Sensor Assembly (DSA).

The DSA is a telescope that looks vertically at the earth, and receives

reflected or radiated energy from features of the earth on its photodetector. For maximum accuracy two such telescopes strapped to the satellite body are required. An image viewed on the first detector will be "seen" by the second detector an instant later. The time lag between the two sightings is the basic measurement used to update the satellite's position and speed.

Horizon sensors and star sensors used to align the satellite after orbit is achieved have already been developed and most of the ANT testing will be accomplished through computer stimulation of these devices.

FASTER REHABILITATION WITH COMPUTER SUPPORTED EDUCATION

Believed to be one of the largest and most complex rehabilitation centres in the whole of Europe, The Heidelberg Centre in the Federal Republic of Germany provides retraining facilities for physically handicapped adult students unable to practise their own

THE TAPE SPECIALISTS

ALL ORDERS POST FREE*

BASF	Tape length	Cash Price (not inc. Price VAT)	Tape length	Cash Price (not inc. Price VAT)	Tape length	Cash Price (not inc. Price VAT)					
5" SP	600'	£1.48	£0.82	SCOTCH HIGH ENERGY COBALT	5" LP	900'					
5" LP	900'	£1.95	£1.08	C60	5" DP	1200'					
5" DP	1200'	£2.25	£1.24	C90	5" TP	1800'					
5" TP	1800'	£3.26	£1.81	SCOTCH HI-FI TAPE	5½" LP	1200'					
5½" SP	900'	£1.95	£1.08	5" SP	5½" DP	1800'					
5½" LP	1200'	£2.25	£1.24	5" LP	5½" TP	2400'					
5½" DP	1800'	£3.26	£1.81	5" DP	7" LP	1800'					
5½" TP	2400'	£4.03	£2.23	5" TP	7" DP	2400'					
7" SP	1200'	£2.25	£1.24	5½" SP	7" TP	3600'					
7" LP	1800'	£3.26	£1.81	5½" LP	10½" LP	4200'					
7" DP	2400'	£4.03	£2.23	5½" DP	8" SP	1200'					
7" TP	3600'	£5.04	£2.78	5½" TP	8" LP	1800'					
PHILIPS HIGH FIDELITY LOW NOISE TAPES											
5" SP	600'	£1.29	£0.80	7" SP	1200'	£2.32	£1.44	C60	£0.79	£0.48	
5" LP	900'	£1.44	£0.85	7" LP	1800'	£2.95	£1.84	C90	£1.07	£0.68	
5" DP	1200'	£1.94	£1.15	7" DP	2400'	£4.03	£2.49	C120	£1.57	£0.98	
5½" SP	900'	£1.70	£1.05	5½" SP	3600'	£4.86	£2.99	8" SP	£0.71	£0.39	
5½" LP	1200'	£1.80	£1.10	5½" LP	4200'	£3.93	£2.47	8" LP	£0.99	£0.59	
5½" DP	1800'	£2.83	£1.70	5½" DP	10½" LPNA8	£6.25	£3.90	C60	£1.49	£0.84	
7" SP	1200'	£1.97	£1.19	SCOTCH LOW NOISE 8 TRACK BLANK	7" SP	1200'	£2.32	£1.44	C90	£0.80	£0.49
7" LP	1800'	£2.57	£1.54	CARTRIDGES	7" LP	1800'	£2.95	£1.84	C120	£1.11	£0.69
7" DP	2400'	£3.97	£2.44	40 min.	7" DP	2400'	£4.03	£2.49	10½" LPNA8	£1.51	£0.94
10½" LP	3,600'	£5.50	£3.30	80 min.	7" TP	3600'	£6.25	£3.90	C60	£0.71	£0.39
PHILIPS LOW NOISE CASSETTES											
C60		£0.71	£0.39	5" SP	600'	£1.34	£0.92	8" SP	£1.34	£0.84	
C90		£0.99	£0.59	5" LP	900'	£1.89	£1.17	8" LP	£1.74	£1.14	
C120		£1.49	£0.84	5" DP	1200'	£2.26	£1.47	8" TP	£2.24	£1.44	
SCOTCH DYNARANGE CASSETTES											
C60		£0.77	£0.35	7" SP	1200'	£3.21	£1.95	10½" SPNA8	£0.71	£0.34	
C90		£1.07	£0.50	7" LP	1800'	£4.01	£2.45	10½" LPNA8	£0.99	£0.49	
C120		£1.62	£0.80	7" DP	2400'	£5.00	£3.45	C60	£1.49	£0.74	
MEMOREX LOW NOISE HIGH OUTPUT TAPES											
				10½" SPNA8	2500'	£6.00	£3.90	C90	£1.05	£0.54	
				10½" LPNA8	3600'			C120	£1.25	£0.64	
MEMOREX LOW NOISE HIGH OUTPUT CASSETTES											
				C60	40 min.	£0.76	£0.39	C90	£1.70	£0.84	
				C90	64 min.	£1.00	£0.59	C120	£1.55	£0.90	
				C120	80 min.	£1.50	£0.84	40 min.	£1.70	£1.00	
MEMOREX CHROMIUM DIOXIDE CRO₂ SM CASSETTES											
				C60	40 min.	£1.35	£0.84	64 min.	£1.85	£1.10	
				C90	64 min.	£1.75	£1.14	80 min.			
MALLORY LNF DURATAPE CASSETTES											
				C60	40 min.	£0.76	£0.39	40 min.	£0.76	£0.39	
				C90	64 min.	£1.00	£0.59	64 min.	£1.00	£0.59	
				C120	80 min.	£1.50	£0.84	80 min.	£1.50	£0.84	
MALLORY COBALT ENERGISED CASSETTES											
				C30	40 min.	£0.76	£0.39	40 min.	£0.76	£0.39	
				C60	64 min.	£1.00	£0.59	64 min.	£1.00	£0.59	
				C90	80 min.	£1.50	£0.84	80 min.	£1.50	£0.84	
MEMOREX HIGH FIDELITY 8 TRACK CARTRIDGES											
				C60	40 min.	£1.35	£0.84	40 min.	£1.35	£0.84	
				C90	64 min.	£1.75	£1.14	64 min.	£1.75	£1.14	

ALL TAPES BRAND NEW AND GUARANTEED. SUPPLIED IN MANUFACTURERS' SEALED LIBRARY CASES

QUANTITY DISCOUNT

Order 10 or more tapes and deduct £0.05 per reel.

Order 10 or more cartridges and deduct £0.03 per cartridge.

Order 10 or more cassettes and deduct £0.01 per cassette.

*U.K. Only

Please supply me with:-

ORDER FORM

TAPES at each =

TAPES at each =

TAPES at each =

*PLUS VAT @ 10% =

enclose Cheque/PO for total of £

NAME

ADDRESS

ET11

INTER-PHONICS
MILL HOUSE-BROMHAM-BEDFORD Tel. OAKLEY 3389

profession.

Computer supported education is among a wide variety of teaching techniques employed at this centre. At the heart of the Centre is a computer complex containing two IBM and two Siemens digital computers. One computer, in addition to helping to control a host of administrative functions, stores hundreds of programmed lessons on subjects ranging from electronics engineering to business administration. The computer records, analyses and corrects students answers, assisting and guiding them to the correct solutions. Because students use CRT terminals to communicate with the computer, they can continue their studies even from a hospital bed.

From a maximum of thirty students, each with a CRT terminal, in a building approximately 3Km from the main computer, data is fed along a link to the computer. Normally each terminal would require a telephone link of its own, but using Racal-Milgo multiplexing equipment only one data link is required, thus reducing line rental costs.

EMI-SCANNER, WINS QUEEN'S AWARD


The Central Research Laboratories of EMI Limited have won a 1973 Queen's Award to Industry in "recognition of their outstanding achievement in technological innovation". The award

is for the EMI-Scanner — the company's revolutionary computerised X-ray system for the diagnosis of brain disorders which was described in ETI of June 1972.

Fully proven in clinical trials, the machine can build up a highly detailed picture of a patient's brain with much greater sensitivity and clarity than conventional X-ray equipment. The

development will enable brain diseases and defects to be diagnosed and located quickly with less discomfort and exposure to X-rays for the patient.

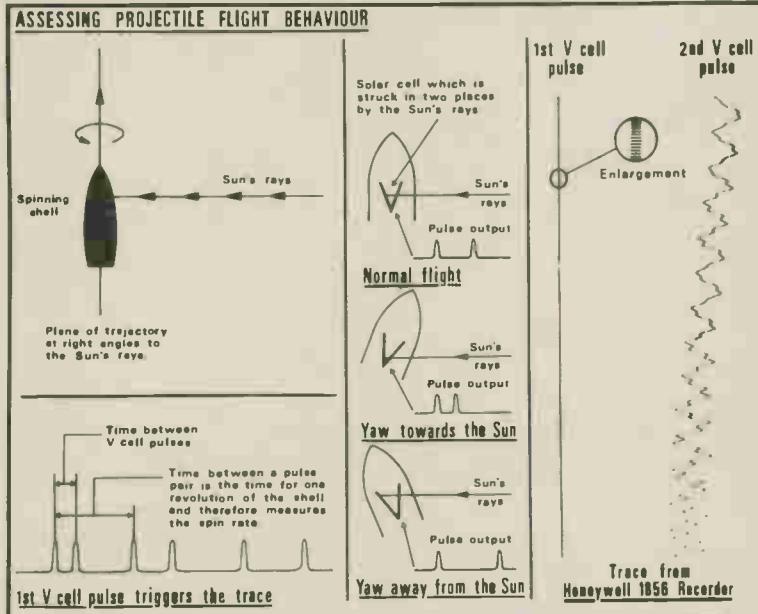In November last year, the system won Britain's equivalent of the Nobel Prize, the MacRobert Award of £25,000 and a gold medal for Godfrey Hounsfield and EMI.



A method of assessing the flight behaviour of various projectiles is currently being used by the Directorate of Proof and Experimental Establishments, Ministry of Defence. The method uses the sun and a photovoltaic V-shaped attitude sensor carried on board the projectile.

The attitude data is telemetered from the projectile to ground receiving stations. The data consists of pulse pairs generated from the sensor, which

when processed result in a record of the projectile's attitude with respect to the sun.

The pulse pairs are transmitted at the projectile's spin frequency of several hundred revolutions per second. These are demodulated from the receiver and displayed on a Honeywell Line Scan FO-CRT Type 1856 in parallel with being recorded on magnetic tape.

Dynachem

New Dimensions in Chemistry

GIRL BY INSTALMENTS!

Electronics manufacturers throughout Europe are receiving a series of unusual sales leaflets from a manufacturer of specialist chemicals used in the making of

printed circuit boards.

Dynachem are sending out four leaflets spaced at regular intervals. On the front of each will be printed a tantalising part of the company's DYNAGIRL, an exquisite young lady well worth a second look. By keeping

the leaflets, the recipient will be able to build up a complete picture.

On the reverse sides will be information about the company's range of photo-resists, plating solutions, brighteners, cleaners and ancillary chemicals.

CONTROL DRILL SPEEDS

DRILL CONTROLLER

New 1kW model. Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger tip control. Kit includes all parts, case, everything and full instructions £1.65, plus 13p post and insurance. Made up model also available £2.45 plus 13p p. & p.

MIGHTY MIDGET

Probably the finest possible radio, as described in Practical Wireless, January 73. All electronic parts £2.20 post paid.

1 CHIP RADIO

Ferranti's latest device ZN414—gives results better than superhet. Supplied complete with technical notes and circuits £1.38 each. £0 for £1.11.

HI-Q TUNER COMPONENTS

For experimenting with the ZN414 Kit No. 1 Plessey Miniature Tuning Condenser with built-in 1V switch and 3in. ferrit slab and litz wound MW coil 72p.

Kit No. 2 Air spaced tuning condenser 6in. ferrit rod litz wound MW and LW coils. And wave change switch 94p.

Kit No. 3 Air spaced TC with slow motion drive 8in. ferrit rod with litz wound LW and MW coils. And wave change switch £1.10.

KIT No. 4 Permeability tuner with fast and slow motion drive and LW loading coils. And wave change switch 50p.



12 VOLT 1.5 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd smoothing. Price £2.20, plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6.33 plus 65p post.

MICRO SWITCH

5 amp changeover contacts, 11p each. 10 for 99p. 15 amp. S.P. Model 15p, changeover 17p each.



MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1 in. pull—approx. size 1 1/2 x 1 1/2 x 1 1/2 in., 66p. Model 4001—1 in. pull. Size 2 1/2 x 2 1/4 in. 83p. Model TT1—1 in. pull. Size 3 x 2 1/2 x 2 in. £1.98 plus 20p post and insurance.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (Class B wiring). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10 plus 20p postage.



TIME SWITCH

Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bill, etc. £2.25.

EDUCATIONAL KITS—all with pictorial instructions



THIS BALANCE KIT FREE

Eagle educational kits. Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits £4.45 each post paid. Special price for all 7 kits £3.00 with free balancing kit.

KA2 Lens Kit. Eleven parts, including candle, one concave lens, one convex lens, stage and slit frame, etc. Watch light rays bend as they pass through different lenses.

KA3 Water Pump Kit. Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working.

Three types of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle.

KA4 Buzzer Kit. Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.

KA7 Electro Magnet Kit. Fifteen parts, includes compass. Makes two electro magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.

KA8 Current and Resistance Kit. Twenty nine parts, including bench top light bulb. Conduct interesting and educational projects to learn the application of "OHMS LAW" and see the difference in current and resistance with different types and lengths of wire.

KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.

KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate.



THIS MONTH'S SNIP

GOOD COMPANION I.C. MODEL

We can now offer this fine receiver that is I.C. integrated, using Ferranti ZN414 and Mullard AF Modules 1172. Cabinet size approx 11in wide x 8in high x 3in deep. Complete with excellent 2 turn cabinet with assembly instructions £5.75.



THYRISTOR LIGHT DIMMER

For any lamp up to 250 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £3.35. Industrial model 5A £3.30.

10 AMP DIMMER CONTROL

For the control of lighting on stage or in a studio or for control of portable equipment in workshops, etc. This has two 13 amp socket outlets each is controlled by a 5 amp solid state regulator. The overall length is 17in., width 3 1/4in. and depth 1 1/2in. In the end is fitted master On/Off switch indicator, lamp and fuse. Price £8.25.

STANDARD WAFER SWITCHES

Standard size 1 1/2in. wafer—silver plated 5 amp. contact, standard 1/4in. spindle 2in. long with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	44p	44p							
2 poles	44p	44p							
3 poles	44p	44p	44p	44p	77p	77p	1£.04	1£.04	1£.32
4 poles	44p	44p	44p	77p	77p	77p	1£.32	1£.32	1£.32
5 poles	44p	44p	44p	77p	77p	1£.04	1£.04	1£.60	1£.60
6 poles	44p	77p	77p	77p	77p	1£.04	1£.04	1£.87	1£.87
7 poles	77p	77p	77p	77p	77p	1£.32	1£.32	2£.15	2£.15
8 poles	77p	77p	77p	77p	77p	1£.32	1£.32	2£.42	2£.42
9 poles	77p	77p	77p	77p	77p	1£.60	1£.60	2£.70	2£.70
10 poles	77p	77p	77p	77p	77p	1£.60	1£.60	3£.00	3£.00
11 poles	77p	1£.04	1£.04	1£.04	1£.04	1£.87	1£.87	3£.25	3£.25
12 poles	77p	1£.04	1£.04	1£.04	1£.04	1£.87	1£.87	3£.52	3£.52

DISTRIBUTION PANELS


Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plug and on/off switch with neon warning light. Supplied complete with 6 feet of heavy cable. Wired up ready to work. £2.48 plus 25 p. & p.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless* June). Price £5.55 plus 30p post. When ordering please state whether for positive or negative systems. Also available ready made ignition systems for 6v. vehicle. £5.78 plus 20p.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods, powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size of blower is approx. 4 1/2" x 4" x 4". When mounted by its flange air is blown into the equipment but to suck air out mount it from the centre using a clamp, ideal for cooling electrical equipment, or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc. etc. A real bargain at £2.04.

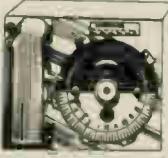

ELECTRIC TIME SWITCH

Made by Smiths these are A.C. mains operated. NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into a box with 13A socket. 2 completely adjustable time periods per 24 hours. Lamp changeover contacts will switch circuit on or off during these periods. £2.73 post and ins. £2.3p. Additional time contacts 55p pair.

SPECIAL SUMMER OFFER

Mullard Unilux at Pre V.A.T. price. You want a good stereo system—well here's an offer you should not miss! The four Mullard modules all in original manufacturers cartons and with original makers guarantee. £3 for the lot. Control unit with name plate and 4 spun aluminium faced control knobs £3. Total £10 post and VAT paid. 2 Goodmans Speakers £3.00

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied.

Model 1153 500mW power output 72p.

Model 1172 750mW power output 94p.

Model EP9000 4 watt power output £1.60.

EP9001 twin channel or stereo pre amp. £1.99.

10% discount if 10 or more ordered.



WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make. £2.48.

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could

programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	Continuously
5	Continuously	Continuously

Suitable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling, taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3in. x 2in. x 2in. deep. Price £3.85 as illustrated but less case.

TAPE PLAYBACK UNITS

Mains operated. Made by Rediente the famous "music in background people." These are complete units ready to work and we understand that they are in good going order. We have not tested them but would exchange any that do not work properly. These have a superior motor driven fly-wheel to control the tape through the capstan and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Two models offered, good as new £6.50 and some £10 miles extra.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p S.A.E. with enquiries please.

NEW ITEMS THIS MONTH

LABORATORY INSTRUMENTS

Used but believed in good order—one only of each—on offer to highest bidder. Emi Parotronic wave analyser.

2 Beckman Universal Epti. Timer Model 7360 c

Furst Electronics Wav. Meter 115RA

Manson Proportional Oven and Xtal Osc RD140

Airmec Millivolt Meter type 264

Marconi Magnification Meter TF 329G

Airmec Frequency Meter Type 726

Soarion Laboratory Amplifier 15 c/s—350Kcs Aws 51a

GEC Quartz Ntality Activity Test Set 2—20 mc/s

Muirhead Phasemeter D729 BM

Muirhead Phasemeter B729 BS

Heath Kit—C Bridge C34

RCA Flutter Indicator.

Metrix Standard Sig Generator 50m/cs. 50m/cs to 50 mc

50 mc to 500 mc

500 mc to 5000 mc

5000 mc to 50000 mc

50000 mc to 500000 mc

500000 mc to 5000000 mc

5000000 mc to 50000000 mc

50000000 mc to 500000000 mc

500000000 mc to 5000000000 mc

5000000000 mc to 50000000000 mc

50000000000 mc to 500000000000 mc

500000000000 mc to 5000000000000 mc

5000000000000 mc to 50000000000000 mc

50000000000000 mc to 500000000000000 mc

500000000000000 mc to 5000000000000000 mc

5000000000000000 mc to 50000000000000000 mc

50000000000000000 mc to 500000000000000000 mc

500000000000000000 mc to 5000000000000000000 mc

5000000000000000000 mc to 50000000000000000000 mc

50000000000000000000 mc to 500000000000000000000 mc

500000000000000000000 mc to 5000000000000000000000 mc

5000000000000000000000 mc to 50000000000000000000000 mc

50000000000000000000000 mc to 500000000000000000000000 mc

500000000000000000000000 mc to 5000000000000000000000000 mc

5000000000000000000000000 mc to 50000000000000000000000000 mc

50000000000000000000000000 mc to 500000000000000000000000000 mc

500000000000000000000000000 mc to 5000000000000000000000000000 mc

5000000000000000000000000000 mc to 50000000000000000000000000000 mc

500000000000000000000000000000 mc to 5000000000000000000000000000000 mc

50000000000000000000000000000000 mc to 500000000000000000000000000000000 mc

5000000000000000000000000000000000 mc to 50000000000000000000000000000000000 mc

500000000000000000000000000000000000 mc to 5000000000000000000000000000000000000 mc

50000000000000000000000000000000000000 mc to 500000000000000000000000000000000000000 mc

5000000000000000000000000000000000000000 mc to 50000000000000000000000000000000000000000 mc

500000000000000000000000000000000000000000 mc to 5000000000000000000000000000000000000000000 mc

50000000000000000000000000000000000000000000 mc to 500000000000000000000000000000000000000000000 mc

5000000000000000000000000000000000000000000000 mc to 50000000000000000000000000000000000000000000000 mc

500000000000000000000000000000000000000000000000 mc to 5000000000000000000000000000000000000000000000000 mc

50000000000000000000000000000000000000000000000000 mc to 500000000000000000000000000000000000000000000000000 mc

5000000000000000000000000000000000000000000000000000 mc to 50000000000000000000000000000000000000000000000000000 mc

500000000000000000000000000000000000000000000000000000 mc to 5000000000000000000000000000000000000000000000000000000 mc

500000

SOLID STATE VALVE

Co-operation in the field of high-voltage direct current was established between ASEA and the two Scandinavian power utilities, ELSAM and NVE, in order to bring about the installation of a new type of thyristor valve in the Danish station of the Konti-Skan DC transmission link between Denmark and Sweden. This new ASEA generation of thyristor valves has been developed to meet future demands on HVDC power and voltage levels. The valve, which is replacing one of the permanent mercury-arc valves, is planned to run commercially for a couple of years in order to gain service experience.



The thyristor valve for HVDC has been developed within a very short period. In 1967 ASEA introduced the thyristor technique to HVDC through the installation of a thyristor valve for a test period in the DC transmission link between Gotland and the mainland of Sweden. The research and development carried on since then have resulted in a new type of thyristor valve with a design principle prepared to meet any voltage and power levels expected for HVDC transmission schemes to come. The new valve has 125MW output (125kV at 1000A).

The thyristor valve is built up from modular units, each comprising six thyristors. Each unit has its separate cooling system, valve damping circuits and control equipment. By means of series connection of the modular units the voltage can be adapted to the optimum voltage level determined by the DC line.

Air is used for both cooling and

insulation. The control unit for each thyristor obtains its auxiliary power supply directly from the thyristor voltage.

COMPUTER SYSTEM FOR CRIMINAL INVESTIGATIONS

A major breakthrough in the fight against crime has been achieved in the United States by the introduction of a low-cost computerised investigation system. Developed by the Oakland Police Department's Research and Development Division, the system is based on a Hewlett-Packard mini-computer.

The computerised system performs a number of investigative functions by utilising the often fragmentary descriptions supplied by witnesses to a crime. It helps identify criminals by comparing known physical characteristics and methods of committing crimes with information already contained in police files.


As well as identifying a vehicle (and hence the driver) involved in a crime, it can also match fingerprints found at the scene of a crime with those on file. A fingerprint file search that formerly took four or five hours can now be completed in fifteen to twenty minutes.

The computer is interfaced with two microfiche viewers. One displays photographs so that witnesses can identify offenders, while the other contains classified fingerprints which can be compared with prints taken from the scene of crimes.

In the first few weeks of testing the system, with only a partial data base, eight burglars were identified and arrested as the result of computer-directed fingerprint searches. At least six robbery suspects were identified from photographs and another suspect was identified solely on his nickname.

Data formerly on fingerprint cards, police records and photographs are now stored on files in the computer system or on microfilm. The system is capable of storing information on more than 25,000 people and on 31,000 vehicles.

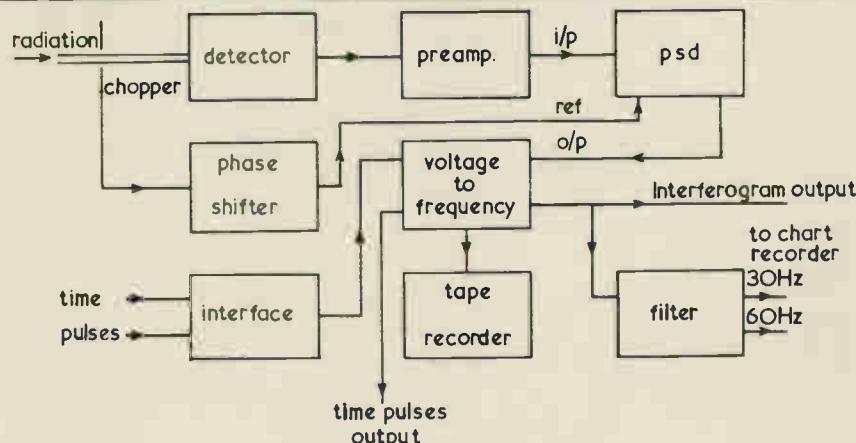Criminals' photographs are maintained in a microfilm viewer which is interfaced with the minicomputer. The computer file contains nicknames, first names and up to 25 physical characteristics of each subject (sex, race, height, weight, hair colour, complexion, fingerprint data etc.). The police records can be searched on any one, or a combination of these characteristics.



Block diagram of experiment

CONCORDE 001 FOLLOWING THE SUN

On the 30th June 1973 Concorde 001 flew astrophysicists from Queen Mary College, London, to study Pnehomogenities (electron temperature and density as functions of height and position above the photosphere) on a scale of a thousand Kilometres in the sun's chromosphere during the eclipse by the moon. Concorde flew into the shadow of the eclipse and followed it to obtain about 80 minutes of total eclipse.

The diagram shows the experiment which was conducted. Radiation (infra-red) from the sun was chopped and fed into a Michelson Interferometer

which was repeatedly scanning, to take in the wave-lengths of interest.

Radiation from the interferometer was then focused onto a Rollin detector — an indium antimonide crystal cooled by liquid helium. The output from the detector was amplified and fed into a phase sensitive detector, the output of which was voltage to frequency converted and stored on a magnetic tape for subsequent analysis.

SKYLAB CREW WELDS WITH AN ELECTRON BEAM

Welding was one of the experiments conducted in the Skylab mission to see how molten metal behaves in a weightless environment. Since welding will

INSTANT CLOCKS

Choose your combination from the tables below.
If you need any help, please feel free to phone us.

CLOCK CHIP	12/24 HOUR	4/6 DIGIT	BCD OUTPUT	7-Seg output	MUXED	1 Hz OUTPUT	AM/PM IND	ALARM	DATE	SNOOZE	SLEEP	PIN COUNT	DISPLAY INTERFACE					Drive volts	Drive current mA		UNIT PRICE	
												DL34	TIL360	DL707	DL62	DG12	SP151	LIQ.CRYS				
MM5311	✓	✓	✓	✓	✓							28	✓	✓	✓	✓	✓		11-19	8		£11.50
MM5314	✓	✓		✓	✓							24	✓	✓	✓	✓	✓	✓	11-19	8		£11.00
MM5316	✓	4	✓	✓	✓	✓	✓	✓	✓	✓	✓	40				✓	✓	✓	8-29	4		£16.00
5017AA	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	24	?	?		✓	✓		5-24	8		£14.00
5017BB	✓	✓	✓	✓					✓			24	?	?		✓	✓		5-24	8		£14.00
5017AN	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	28	?	?		✓	✓		5-24	8		£15.50

DISPLAY CODE	TYPE	PACK	DIGITS	HEIGHT (INS)		DECIMAL POINTS	COLON	AM/PM	Drive Voltage	REMARKS			COST PER DIGIT	UNIT PRICE
				DIG	PACK									
DL34	LED	14 PIN	4	0.1	0.2	4			2v	CALCULATOR TYPE			£2.50	£10.00
TIL360	LED	16 PIN	6	0.1	0.2	6			2v	CALCULATOR TYPE			£2.50	£15.00
DL707	LED	14 PIN	1	0.3	0.7	1			2v	SIM TO MAN 7 TIL302			£2.00	£2.00
DL62	LED	16 PIN	1	0.6	0.9	1			2v				£6.50	£6.50
DG12H	PH-DIODE	TUBE	1	0.3	1.0	1			15v				£2.00	£2.00
SP151	SPERRY	FLAT	3½	0.5	1.2		✓		160v	SPECIAL SKT AVAIL.			£2.00	£7.50
TA8055	LIQ.CRYS	EDGE	4	0.6	1.3		✓	✓	60v AC	Reflective/Transmission			£3.25	£13.00
D.I.Y.	LED	VERO BOARD	1	3"	3"				2v	21 LED LAMPS			£5.00	£5.00

SOCKETS — 24 or 28 pin £1.15, 40 pin £1.35

CASES — WE ARE HOPING TO HAVE CLOCK CASES SOON, PLEASE PHONE BEFORE ORDERING.

KITS — 5017AA + PCB + SKT + 4 DG12s + INSTRUCTIONS. £24 — AVAILABLE NOW

5017BB + PCB + SKT + 4 DG12s + INSTRUCTIONS. £24 — AVAILABLE NOW

MM5316 + PCB + SKT + TA8055R + INSTRUCTIONS. £31 — AVAILABLE SEP/OCT

MM5316 + PCB + SKT + SP151 + INSTRUCTIONS. £26 — AVAILABLE OCT/NOV

CLOCK DATA SHEETS — SAE. ADVICE — PHONE 0442-62757

POST & PACKING — 10p. OVERSEAS (AIRMAIL) 50p. VAT — ALL PRICES EXCLUDE VAT.

PAYMENT C.W.O. OR ACCOUNT. ACCESS. ORDERS & PAYMENT BY PHONE ACCEPTED.

QUANTITY DISCOUNTS ON MOST ITEMS — STATE REQUIREMENTS FOR QUOTATION.

BYWOOD ELECTRONICS
181 EBBERNS ROAD
HEMEL HEMPSTEAD
HERTS. TEL.0442-62757.
24 HOUR ANSAPHONE ON-LINE.

news digest

be necessary in future space missions, Skylab's crewmen tested an electron beam welder developed for the space agency's Marshall Space Flight Centre by Westinghouse Electric Corporation's Astronuclear Laboratory.

Electron-beam welding is one of the newest techniques for metal joining and, in many respects, possibly the most desirable. One advantage is that welding is so rapid that the heat in the weld has no chance to spread to the surrounding metal to make it brittle and susceptible to cracking. The process produces exceptionally deep, strong, uniform welds and it can be applied to a variety of metals and alloys including all those likely to be used in space.

A unique feature of the new Westinghouse welder is that it is a completely self-contained unit. It measures 36in long by 13in in diameter. Without the battery it weighs 77 pounds, the battery weighs 43 pounds. Earth-bound counterparts are powered by large external power supplies. The battery produces 100A at 28V for about 10 minutes.


A tungsten filament generates a 20kV, 100mA, tightly focused electron beam that does the welding. The electron gun is attached to a work chamber which during the experiments is vented to space, producing a vacuum. This has two important advantages. One is that the better the vacuum, the better the electron beam welds. The other advantage is that the absence of air and particles means there are no contaminants to affect the quality of the weld.

£30M TRANSATLANTIC PHONE LINK

The cableship Mercury has started to lay a £30 million telephone cable linking Britain and Canada. Handling more than 1,800 telephone conversations simultaneously the cable, Cantat-2, will be the biggest single telephone cable across the Atlantic, carrying more telephone calls than all the existing transatlantic cables combined. The cable system will be used for communication between the UK and mainland Europe, and Canada and the USA.

Being financed and operated jointly by the British Post Office and the Canadian Overseas Telecommunications Corporation, the 3,000-mile cable is being provided to meet the massive growth in telecommunications between Britain and North America. In ten years' phone calls between Britain and Canada have risen eightfold from 135,000 calls a year

TRANSATLANTIC TELEPHONE CABLES

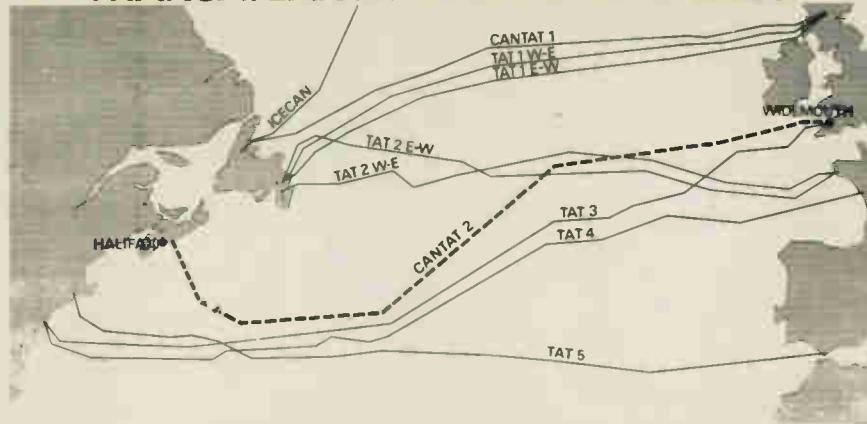

in 1962 to their present level of more than a million a year. This will rise again to nearly 6 million a year by 1980. Growth in calls between the UK and the USA has risen from half-a-million in 1962 to more than 4½ million in a year in 1972, and by 1980 this will have reached 24 million a year.

Cantat-2 will have 473 repeaters. The task of the repeaters is to amplify telephone signals on their undersea journey. In the deepest parts of the Atlantic repeaters will be under a pressure of three tons to the square inch, and are protected by deep-sea pressure housings.

2,800 transistors will be used in the amplifiers in Cantat-2, each with a design life of at least 25 years.

Cantat-2 will also have 31 equalisers, spaced at approximately 90-mile intervals in the cable and placed in pressure housings similar to a repeater. Equalisers are electrical circuits designed to compensate for variations in the match between repeater gain and cable loss. The electrical characteristics of the cable are altered when it is placed in the sea, and equalisation compensates for the difference between the predicted and actual change.

Equalising these differences ensures that the performance of telephone circuit over the whole of Cantat-2's frequency range will be virtually identical. The equaliser is initially assembled at the cable works and finally completed at sea during the course of laying operations.

Cantat-2's 1,840 circuits are arranged as 23 supergroups, transmitting in the frequency band 312.6, 012kHz in the UK-Canada direction and 8,000-13,700kHz in the Canada-UK direction. In addition four speaker circuits of nominally 3kHz bandwidth each, use the frequency bands 6,024-6,036kHz in the UK-Canada direction and 7,976-7,798kHz in the Canada-UK direction, for system and circuit maintenance.

The cable itself is predominantly of lightweight design and will weigh no more than five tons a mile. Less than two inches in diameter for most of its length the cable has an outer conductor of aluminium. Its strength is centred in a steel rope inside an inner copper conductor. External armour will be used to protect the cable at the UK shore end.

LASER FOR CLOUD HEIGHT MEASUREMENT

ASEA, Sweden, have developed a new low-power cloud ceilometer, QL 1210, as complementary equipment to the high-power type introduced some years ago. This smaller unit is intended for use at airfields, meteorological stations etc., for the continuous recording of cloudbase height up to 1000m (3300ft).



An injection laser transmitter is employed, using a gallium arsenide diode. The light intensity is well below the limit for non-injurious radiation, so it is not necessary to take any special precautions in use or during servicing. A 2-core telephone line connects the transceiver to a pen recorder, set up indoors.

The control unit sets the recorder pen off on its sweep at the same time as a light pulse is transmitted. When an echo pulse is received the pen begins to write, having reached a position on the scale corresponding to the height of the cloud.

NEW VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT
ONE ELEVENTH

74 Series TTL

INTERNATIONALLY
KNOWN BRANDS
1st. GRADE DEVICES AT NEW
ROCK BOTTOM PRICES

16p	40p
16p	40p
18p	50p
17p	44p
30p	69p
16p	74p
99p	74p

PRICE BARRIER SLASHED

LED READOUTS


14 pin DIL



Ref LED 1

£1.99 + 20p VAT = £2.19

BRIDGE RECTIFIERS

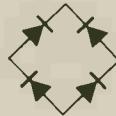

P.I.V.	1 AMP	R.M.S.	2 AMP
20p		35p	
22p		40p	
25p		45p	
38p		50p	

RECTIFIERS

P.I.V.	1 AMP	3 AMP
6p	15p	
7p	16p	
9p	17p	
9P	22p	
11p	26p	
13p	30p	
16p	33p	
16p	23p	
22p	55p	
16p	£1.65	
16p	£1.65	
16p	25p	

OR
FILAMENT INDICATOR
MINITRON 3015F & G



a1 **BREAKTHROUGH
PRICE £1.49**

Cheapest Opto yet GaAsP LED's



LED 2 0.125" 26p
LED 3 0.175" 17p
LED 4 0.125" 69p
LED 5 0.175" 75p

Remember Vat Inclusive Prices

Veroboard

Copperclad 0.1" 0.15" Plain 0.15"

6½p 6½p 11p 13½p

22p 18p 11p 13p

26½p 23p 13p

30p 30p 19p

74p 55p 41p 10p

99p 77p 57½p 10p

Dip Breadboard 4.15" x 6.15" 110p

Verostrip 8.5" x 1.5" 26p

Spot Feed Cutter 40p

Pin Insertion Tool (state 0.1" or 0.15") 52p

Terminal Pins (packs of 36) state size 20p

I.C. SOCKETS



DUAL IN LINE
13½p 17½p 39p
15½p 26½p 44p

HEAT SINKS

TV2 for TO 66 15p. 5F for TO 5
TV3 for TO 3 16p 18F for TO 18



5½p.

DIP10 2 for
SL403D

DIP14 5 for
EA1.000



35p



46p

DIGITAL CLOCK



on
a
chip

just imagine, one MOS
LSI I.C. eliminating 15
MSI I.C.s & numerous
other components. Either

12 or 24 hour, 4 or 6 digit
50 or 60Hz operation
leading zero suppression
single voltage supply
similar to DIGITRONIC in
P.W. March 1973.

Only £6.99

With 4 LED's £15.59

With 6 LED's £19.75

CHROMASONIC electronics

RESISTORS

RATING	TYPE	TOLERANCE	RANGE	PRICE EACH
1.16 Watt		± 5%	51Ω	100K1 5p
1.8 Watt		± 5%	5.1Ω	330K1 1p
1/2 Watt		± 2%	10Ω	1M1 4p
1/2 Watt		± 2%	56Ω	150K1 0p
1/2 Watt		± 5%	10Ω	10Ω 1p
1/2 Watt		± 0.5%	2.2Ω 2.7Ω 3.3Ω 3.9Ω 4.7Ω 5Ω	4Ω 4p
1 Watt		± 10%	5.6Ω 6.8Ω 8.2Ω	5Ω 5p
1 Watt		± 5%	10Ω	10Ω 3p
2 Watts		± 5%	10Ω	10Ω 6p
2 Watts		± 10%	0.22Ω 0.47Ω	10p 10p
2½ Watts		± 5%	1Ω	270Ω 10p
5 Watts		± 5%	0.5Ω	6.8Ω 11p
10 Watts		± 5%	0.5Ω	6.8Ω 11p
10 Watts		± 5%	10KΩ 15KΩ 20KΩ 25KΩ	17p 17p
15 Watts		± 5%	10Ω 6.8KΩ	13p
DISCOUNTS	10%		25%	

Postage & Packing Extra 8p per quantity


CAPACITORS

MULLARD C333 629 & 630 Series Ceramic	5½p
CERAMIC DISC - Low Voltage	5½p
5½p	6½p
FOLY TYRENE 160V	5½p
MYLAR PLATE 400V	2½p
2½p	3½p
ULLARD C220 250V Polyester	3½p
3½p	5½p
ULLARD C281 400V Polycarbonate	6p
6p	8p

ALL VARIOUS TYPES TANTALUM PULSE
CERAMICS & MONOLITHIC CERAMICS ARE
ALL DETAILED IN LEAFLET ND 13

**new
stabilised**
POWER PACK CONVERTER

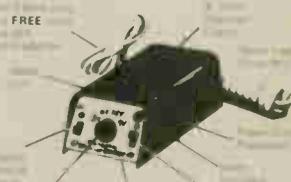Switched 3, 6, 7, or 9 Volts
Up to 400 mA Output



Our Price £3.99 + p & p 16p

Unfinished Version of above £2.99

Other Electronics (unfinished)	
5 Volt	10A £1.65
9 Volt	10A £1.65
9 Volts (immediate)	10A £2.09
6.16	10mA £2.75
9.9	30mA £2.75
7½ Volts	12.5mA £2.20
3.4 - 6.7 - 9.12 Volts up to 1A	1A 10mA £3.70
With Standard On Off Control	
With switched on/off by 7-9 Volts	
p & p on all models 16p	£3.99

ZENERS

All 5% tolerance	
BZY88	11p
1ZS	18p
BZX70	27p

The basic circuits for a TTL digital clock are well known and usually require from 20-25 i.c.s. These designs however, apart from their complexity, are subject to spurious mains pulses which frequently mean that the clock will gain a few seconds each day. In addition, the power requirements are not insignificant and a current drain of 0.5A is typical. These problems have resulted in true electronic digital clocks being very expensive and no company has produced these in quantity.

Commercial digital clocks usually use flip-over digits or 'Nixie' tubes switched by rotary switches. Both these types use a synchronous electric motor. A true electronic clock has no moving parts (except for the setting switches) and will not wear out. In fact, a true electronic clock could still be running when electricity goes out of fashion!

For this reason an electronic clock could be regarded as a pretty good investment but how about one that makes full use of the accuracy of a electronic technique and operates as an alarm or displays time and date alternately?

Using TTL techniques the complexity would present serious problems — thirty or more i.c.s would be required and the current drain would

be about 1A. The associated switching would also be highly complex.

Wouldn't it be wonderful if the technology which produces calculator chips could be applied to clocks... well, it has! Mostek, who produce a calculator chip found in many machines have recently introduced a range of clock chips. The range is known as the MK5017 and there are three variations: the AA which has an alarm circuit, the AN with alarm and sleep circuitry and the BB which has a calendar facility. The AA and BB are very similar and with a few modifications a clock built with the MK5017AA will accept the

BB chip.

In this feature we shall describe the AA, digital alarm clock version but the modifications to incorporate the BB will also be given.

MOSTEK 5017AA ALARM CLOCK CHIP

The MK5017AA is designed to drive 7-segment luminescent-anode display tubes directly without interface circuitry. Either four or six digits can be accommodated and the clock will work from 50 or 60Hz mains frequency. The clock always works in the 24 hour mode for alarm setting reasons but

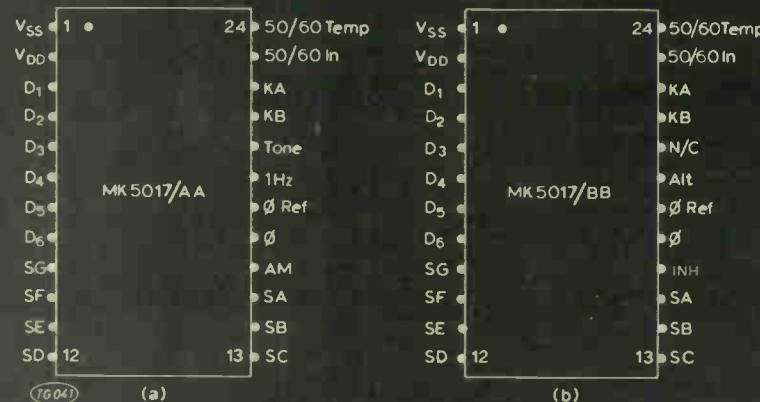


Fig. 1. The pins connections for the a) MK 5017/AA (alarm clock) and b) MK5017/BB (calendar clock).

TIMTRONIC

BY JOHN MILLER-KIRKPATRICK

A digital alarm
calendar clock



either 12 or 24 hour display can be selected, if the 12 hour display is selected, the AM/PM output can be used to show which part of the day the time refers to. Time setting is simplified since separate controls of the hours, tens of minutes and minutes is provided. The alarm time is set in a similar way to the time of day, and then stored in a RAM (Random Access Memory) and continuously compared to the current time; when co-incidence is detected, the alarm circuit is switched on. The alarm is a 700Hz signal modulated at 1Hz which may be fed via a simple transistor amplifier to a loudspeaker. The display output is a multiplexed 7-segment output on 6 digit drives, the multiplex frequency is decided by a CR network external to the chip. Supply voltage is 11-18V D.C. (unregulated) at 16mA. The pin configuration is shown in Fig. 1a.

tional and has two separate secondary windings. One of these goes to the heaters of the display tubes via a dropping resistor. This is only necessary to enable a widely available transformer to be used. The heaters of course operate from a.c.

The 50/60 TEMP point is for a useful feature; if there is a short interruption of the mains frequency and a DEAC rechargeable cell is incorporated, the chip will continue to work, the 50Hz being provided artificially by the network R1, C1.

On the right hand side of the circuit it will be seen that the decimal of the second display can be arranged in three ways. It can either be on permanent, flashing at 1Hz or only be shining during a.m. if the clock operates on a 12 hour display.

The ϕ REF and ϕ points connect to a preset pot which controls the

flicker rate of the displays.

The tone output is the alarm signal which gives 700Hz switched on and off at 1Hz. The switching associated with outputs D1-D6 is rather more complex than shown in the circuit but is amplified in Fig. 3. There are optional links for 60Hz operation and for 12 hour operation.

CONSTRUCTION

The basis of the Timtronic is an extremely complex I.C. which, although physically very small, contains thousands of transistors. It is far from cheap and should be handled with care. It is supplied protected by a piece of black plastic material which prevents static building up with possibly disastrous results. Do not remove this material until the last minute. It is essential that the I.C. is mounted in a socket so that

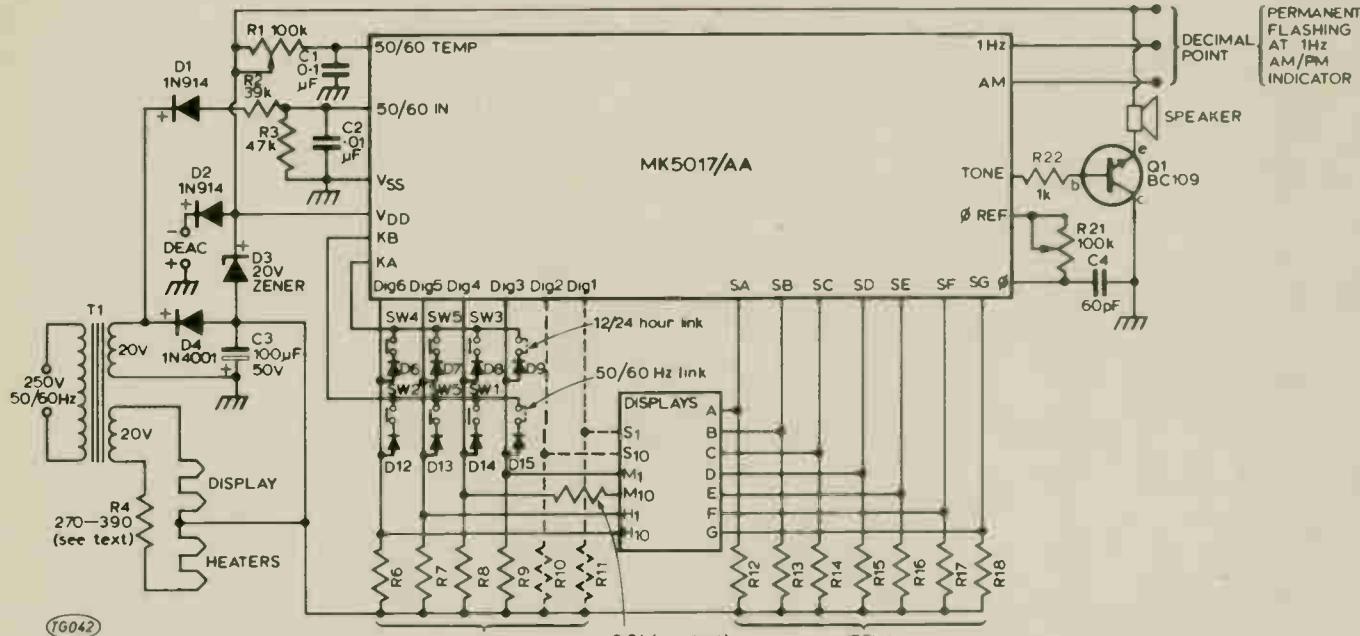


Fig. 2. The complete circuit of the alarm clock. See the text for the differences for the calendar clock. D6-D9 and D12-D15 are all 1N914 diodes.

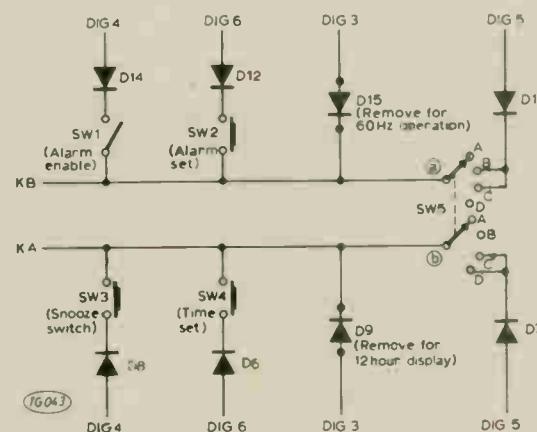


Fig. 3. The controlling switch circuitry.

CIRCUIT OPERATION

The circuit, as far as the constructor is concerned, is extremely simple and is shown in Fig. 2. As you will see, there are a mere handful of components in addition to the chip itself.

The power supply is fairly conven-

handling, etc., can be kept to a minimum.

The printed circuit board pattern is shown in Fig. 4. As can be seen, this is far from a simple pattern with very

TIMTRONIC

close tracks. For those readers who want to purchase a p.c. board, ready etched, drilled and with the component siting printed on top, these are available — see the components list.

The p.c. board has been designed as small as possible and this means that the tracks are very close together. For this reason care must be taken to avoid 'bridging' with solder.

The instructions which follow describe the method of construction of the Timtronic 5017AA Digital Alarm Clock. Construction for the Timtronic 5017BB Digital Clock-Calendar is identical in nearly all respects. Where differences occur, they are clearly noted in the text.

CONSTRUCTION OF DISPLAY SECTION

The recommended display tubes for the clock are either DG-10A or DG-12C. The latter have a slightly larger digit size. Wire lead-out diagrams for each are shown in Fig. 5.

The two heater leads are easily identified by the red sleeving which is on them. It will be seen that there are either 6 leads to the front of the tube between the heater wires (DG-10A), or 5 leads to the front between the heater wires (DG-12C). You should now identify the grid wire on each of the tubes you are using. It is one of the leads to the front, and location is a simple matter using Fig. 5. When you have located each grid wire, mark it in the same way as the heater by slipping a short piece of insulation on to it.

Now locate the decimal point (DP) lead on each tube, and remove it on all but one of the tubes by snipping it off as close to the tube as possible. The tube on which you leave the decimal point lead will become the hours units' indicator, or DIG 2. Finally, if you are using DG-10A tubes, remove the two leads marked 'N/C' (not connected).

Start building up the display section by inserting DIG 2. This is the tube on which you left the decimal point wire. Solder it into position between one-eighth and one-quarter of an inch above the printed circuit board. This will give the tube a certain amount of flexibility for final positioning, when you come to align all four tubes.

Do not solder in either the heater wires, or the grid lead on DIG 2 for the moment. Work on these will follow after the other tubes have been soldered into position.

After you have soldered DIG 2 into

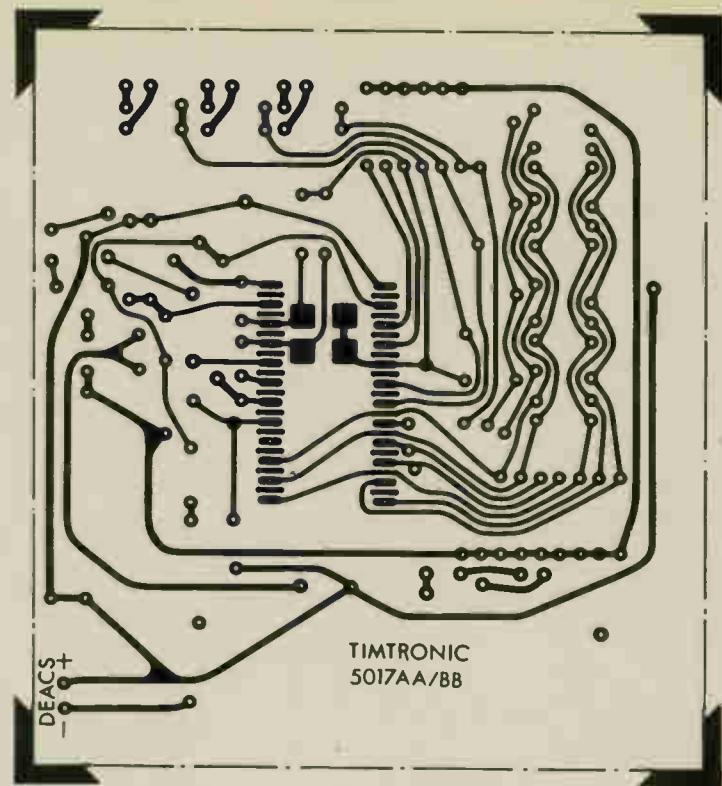


Fig. 4. The PCB pattern shown full size.

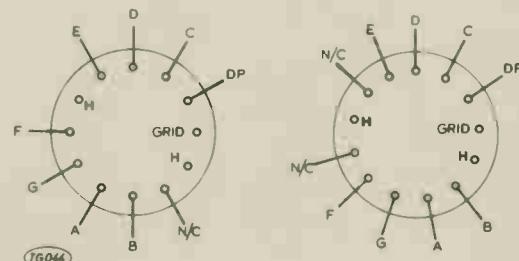


Fig. 5. The pin connections for the alternative tubes. The DG-12C is shown on the left, the DG-10A on the right.

position, insert DIG 1, and then DIG 3 and DIG 4 in exactly the same way. Try for as good alignment as possible as you insert each tube, paying especial attention to the relative heights of the actual digits in the tubes. You may find that the outer glass body of the tubes varies slightly in height, and it is therefore wise to check that the digits themselves are in line horizontally with each other.

The printed circuit board has been basically designed for DG-10A tubes. If you are using DG-12C tubes, you will find their slight extra width makes fitting a little more difficult, but they will fit satisfactorily if care is taken.

When all four tubes are in position, twist together and solder the heater leads between DIG 1 and DIG 2. Make the twist as close in to the tubes as possible, removing the red sleeving to assist in this, then snip off the surplus wire. Repeat this on the two heater leads between DIG 2 and DIG 3, and between DIG 3 and DIG 4.

This process will effectively have connected the heater leads in series. Now the heater lead on the left-hand side (looking at the tubes from the front) of DIG 1 should be extended with a short piece of wire, and soldered into the point marked HTR 2 on the printed circuit board. Now connect the heater lead from the right-hand side of DIG 4 to HTR 1 on the PCB.

Finally solder a wire, which should be insulated, to the twisted join in the heater wires between DIG 2 and DIG 3. Solder the other end of this wire to the point marked HTR 3 on the PCB.

TESTING THE DISPLAY

All connections in this section are temporary. First, connect between 2 and 3V across the points HTR 1 and HTR 2. The polarity is not important. When this is done, you will probably be able to see the heater filaments glowing very faintly. Do not worry at this stage if you cannot, however, and certainly do not increase the voltage!

PARTS LIST

R1	Preset Resistor	100k miniature skeleton type
R2	Resistor	39k 5% 1/8 W or 1/4W
R3	"	47k "
R4	"	270-390ohms 1W — see text
R6	"	68k 5% 1/8 W or 1/4W
R7	"	68k "
R8	"	68k "
R9	"	68k "
R10	"	68k "
R11	"	68k "
R12	"	150k"
R13	"	150k"
R14	"	150k"
R15	"	150k"
R16	"	150k"
R17	"	150k"
R18	"	150k"
R21	Preset Resistor	100k miniature skeleton type
R22	Resistor	1k 5% 1/8 W or 1/4W
C1	Capacitor	0.1uF Mylar, polyester, ceramic etc.
C2	"	0.1uF
C3	"	100uF 50V electrolytic
C4	"	60pF ceramic, polystyrene etc.
Integrated Circuit		MK 5017-AA or MK5017-BB
D1	Diode	1N914
D2	"	1N914
D3	Zener Diode	20V 250mW min.
D4	Diode	1N4001
D6	"	1N914
D7	"	1N914
D8	"	1N914
D9	"	1N914
D12	"	1N914
D13	"	1N914
D14	"	1N914
D15	"	1N914
Q1	Transistor	BC109

DISPLAY TUBES

Four DG-10A or four DG-12C luminescent anode seven segment display tubes.

TRANSFORMER

240 volt primary, 0-20, 0-20 volt secondary (R.S. Components Miniature 20V type)

LOUDSPEAKER

75-80 ohm miniature type, or GPO telephone earpiece

SWITCHES

SW1.....single-pole on-off miniature switch
 SW2.....single-pole push-to-make push button
 SW3.....single-pole push-to-make push button
 SW4.....single-pole push-to-make push button
 SW5.....two-pole four-way rotary wafer

MISCELLANEOUS

Case, solder, fine gauge insulated wire in several colours, 24-pin socket for integrated circuit, transistor socket if desired, transformer mounting screws, 3 volt and 9 volt batteries for initial testing of displays, etc.

SYMBOLS NOT USED—R5, R19, R20, D5, D10 and D11.

A kit of the PCB, socket, four display tubes and IC is available from: BYWOOD ELECTRONICS, 181 Ebberns Road, Hemel Hempstead, Herts for £24 plus VAT (inc. postage)

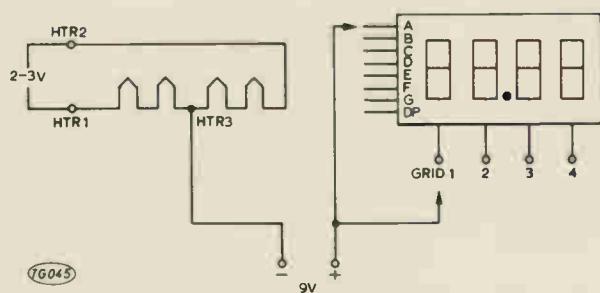


Fig. 6. Test circuit for testing the displays.

Now connect the negative side of a 9V source to HTR 3, and the positive side of the same source to the grid lead of DIG 1, and also to any one of the segment wires of DIG 1.

When the 9V positive is applied to one of the segment wires of DIG 1, one and only one, of the DIG 1 segments should light. If no segment lights, measure the voltage across each heater. It should be approximately 0.75V. If this figure is obtained, then check all connections. If more than one segment lights, check for solder bridges across the 'runs' on the underside of the PCB, or for short-circuits between the leads of the tubes.

When one segment lights successfully in DIG 1, repeat the test for the remainder of the segments in DIG 1, and then carry out an identical check on DIG 2, DIG 3 and DIG 4. This is a total of 29 checks, including the decimal point in DIG 2.

Do not proceed further with construction until these checks have been successfully carried out. When they have, disconnect the voltage sources and leads used for the testing.

FINISHING THE DISPLAY SECTION CONSTRUCTION

Solder the grid lead of DIG 1 to the point on the printed circuit board marked SC1. The grid lead will probably be sticking out to the front of the tube, and so you will have to carefully bend it down and feed it to the rear of the tube, passing it under the two soldered heater wires. Make sure the insulation of the grid lead prevents it shorting against any other wires.

Repeat this process for DIG 2, soldering the grid lead to the point marked SC2. In the same way, solder the grid leads for DIG 3 and DIG 4 to the points marked SC3 and SC4 on the PCB. Finally insert and solder into position the plain wire links L1, L2 and L3. These may be uninsulated wire, since there is little likelihood of any shorts occurring.

This concludes the construction of the display section.

CONSTRUCTION OF THE MAIN CLOCK CIRCUIT

First, insert the 24 pin i.c. socket into the holes on the p.c.b. The socket may be either way round. Insertion must be done with great care and may require some patience! You may find that a small screwdriver will help to align the pins of the socket to the holes in the board, and it will certainly be worthwhile taking a few moments before you begin insertion to straighten any pins which may have become slightly misaligned.

After the socket is firmly in position, solder all 24 pins on the underside of the PCB. Again, take your time over

TIMTRONIC

this as this is one point at which the space between the pins is very small, and it will be easy to accidentally bridge the gaps with solder. When you have finished, examine the soldering carefully to make sure no bridges have occurred.

Under no circumstances insert the clock integrated circuit at this stage.

Most of the rest of the components can now be inserted and soldered into position.

The first of the differences between the Alarm Clock and the Clock Calendar must now be mentioned. Diode D9 is *not* inserted for the Clock Calendar. This will provide a conventional 12-hour clock display, but the clock chip will nevertheless operate in 24-hour mode. It is necessary to operate the Clock Calendar with a 12-hour display to ensure that the months indication is correct when the clock switches to calendar display. If diode D9 is inserted then the clock display will be 24-hour, but the calendar months will only run up to '11' for November, '0' for December, and then revert to '1' for January. This is because of the integrated circuit design.

Constructors of the Alarm Clock may also omit diode D9 if they prefer a 12-hour, rather than 24-hour display. There will be no side-effects from doing this.

Should either clock be intended for operation on 60Hz mains frequency, diode D15 should also be omitted.

The penultimate items to be added are the two links L4 and L5, and the transistor. The short link L5 poses no problems and need not be insulated, but link L4 should both be of insulated wire and also somewhat slack. The slackness is required to allow the link to fit round one side of the transformer which is, as you will see, mounted quite close to L4.

The resistor R4 should be left until last and the value should lie between 330 ohms and 390 ohms if DG-10A tubes are being used, or 220 ohms and 270 ohms if DG-12C tubes are being used. We suggest you use the larger value initially, as it is very easy to apply too much voltage to the heaters, which will over-run them and immediately destroy the displays!

The aim is to secure the optimum heater voltage without actually getting the heater wire glowing visibly. You may therefore find that you will have to experiment with slightly different values of resistor for R4 to achieve this state.

There is a second reason for making R4 the last component to go into


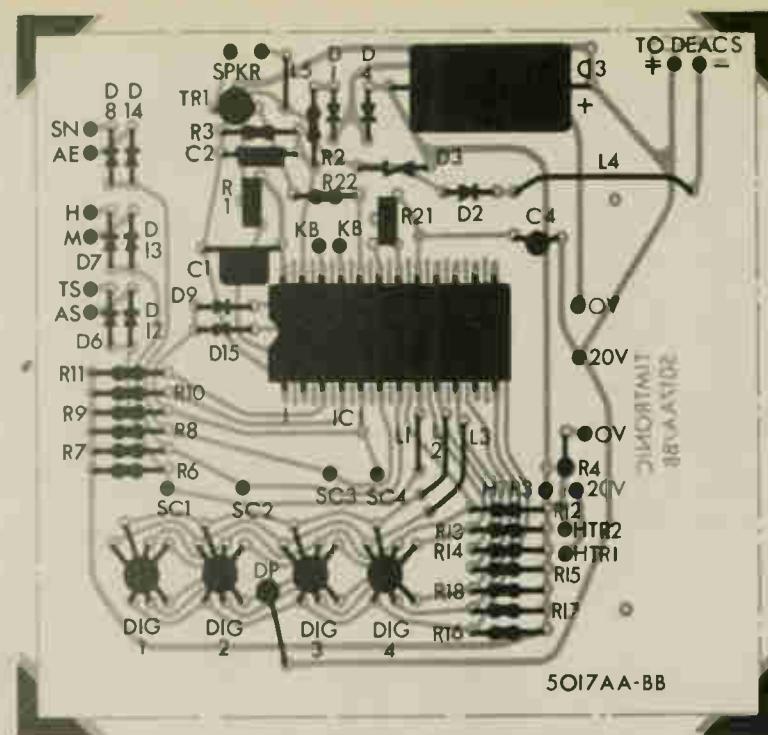


Fig. 7. The component layout on the PCB.

Fig. 8. The back panel wiring.

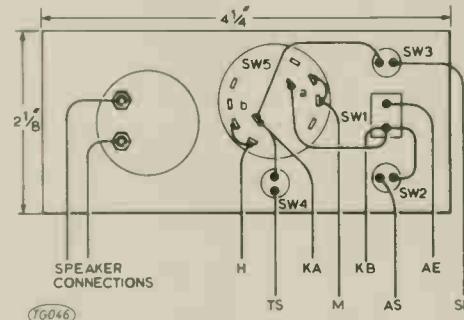

position — it must be fitted in such a way as not to touch any other component. Since it is dropping most of the 20V output from one of the transformer secondaries, it gets very hot.

The best position is lying across links L1, L2 and L3 but not in contact with them. You should also note that part of R4 will lie under part of the transformer windings.

WIRING THE CONTROL BUTTONS AND SWITCHES

The basic wiring for the control buttons and switches is as shown in Fig. 3, but the purpose of some of them differs, according to whether the Alarm Clock or the Clock Calendar is being constructed.

SWITCH SW1: 'ALARM ENABLE' ONLY

Alarm Clock: To enable the alarm, the switch is closed; to disable the alarm, it is opened. After the alarm is disabled it may be re-enabled immediately without causing the alarm to continue sounding. The alarm will now sound again 24 hours later. In this way, the

24-hour alarm capability of the clock is fully utilised.

Clock Calendar: Switch SW1 is not used in the Clock Calendar.

SWITCH SW2: 'ALARM SET' OR 'CALENDAR SET'

Alarm Clock: This is the alarm set switch. When the switch is closed, the display will show the content of the alarm counter — in other words, the time for which the alarm is set. This will not disturb the clock timing operation, and when the switch is released the display will revert to showing time. The switch is also used when actually setting the alarm time, in a way which will be described under 'Switch SW5' later.

Clock Calendar: This is the Calendar Set switch. The normal operation of the Clock Calendar is to display the time for 8 seconds and then to display the date for 2 seconds, switching from one to the other occurring automatically. When the Calendar Set switch is closed, the display will show the calendar only. This switch is used when the calendar is set initially, and when it is reset at the end of months containing less than 31 days. This process will be

described under 'Switch SW5' later.

SWITCH SW3: 'SNOOZE' ONLY

Alarm Clock: This switch temporarily resets the alarm when it begins sounding to allow a short period for an extra snooze! Hence the name 'Snooze Switch'. The reset period is a timed 7 minutes before the alarm sounds again. At this point the switch can be reactivated for a further 7 minutes. The maximum number of reactivations is 8, as the alarm automatically disables after 60 minutes, if it is not disabled with Switch SW1 before that time.

Clock Calendar: Switch SW3 is not used in the Clock Calendar.

SWITCH SW4: 'TIME SET' ON BOTH CLOCKS WITH SMALL DIFFERENCES

Alarm Clock: Setting the time is accomplished with the clock circuit counting or temporarily stopped, and is done via SW5 (described next). However it is desirable for accuracy to set the time with the clock stopped, subsequently releasing the clock against a known time reference source (the telephone time clock, for example). Switch SW4 allows this to be done. When the switch is closed, the internal seconds counter resets to '00' and the clock operation stops until the switch is released.

Clock Calendar: As noted, the clock calendar alternates between a time display for 8 seconds, and a calendar display for 2 seconds. If Switch SW4 is closed, time will be displayed continuously. It has already been seen that

SWITCH SW5: HOURS, TENS OF MINUTES AND MINUTES TIME SET

Alarm Clock: Assuming your wiring is as shown in Fig. 3, and you are therefore using a 2-pole, 4-way switch, the first position allows normal clock operation. The second position will cause the minutes to count from '0' to '9' at two counts per second. No other digit will be affected. The third position will cause the tens of minutes to count from '0' to '5' again without affecting any other digit. The fourth position will cause the hours and tens of hours to count from '00' to '23' if you have constructed a 24-hour clock, or from '1' to '12' if you have constructed a 12-hour clock. In the latter case, the tens of hours digit will not at any time show a '0' but will remain off until '10' is reached, when it will then show the '1'. All of the foregoing is equally true when the 'Alarm Set' switch SW2 is closed, and the display is showing the contents of the alarm counter; incrementing of the alarm counter is done in an identical way to incrementing of the main time display.

Clock Calendar: The preceding details regarding setting the time display on the Alarm Clock are equally true for the time display on the Clock Calendar. When the Calendar Set switch SW2 is closed, the date will be displayed and may be set. Special note: the first two figures of the display are the month, and the second two are the day. This is in accord with common practice in many Continental countries and in the USA. When the setting is done, DIG 4

FINAL WIRING OF THE SWITCHES

The final wiring of the switches may now be done, following the wiring diagram given in Fig. 8.


We suggest you wire the switches 'loose' first of all, rather than mounting them into the case. This will allow reasonably long lengths of wire to be used for the wiring: any circuit 'bugs' which might occur to be traced easily; and the final wiring into the case to be done with much shorter lengths of wire for neatness and appearance.

TESTING THE CIRCUIT

Before commencing testing, the transformer must be connected to the mains and to the p.c.b. Do not mount the transformer on the board at this stage.

After you have connected the mains lead to the transformer, and before you do anything further, we strongly urge you to cover the mains tags of the transformer with two short lengths of insulating tape, both at the top and, if your transformer also has tags on the mains side at the bottom, over those also. As testing proceeds, it is all too easy to become deeply interested and unwittingly lay one's hand, wrist or arm on the mains point.

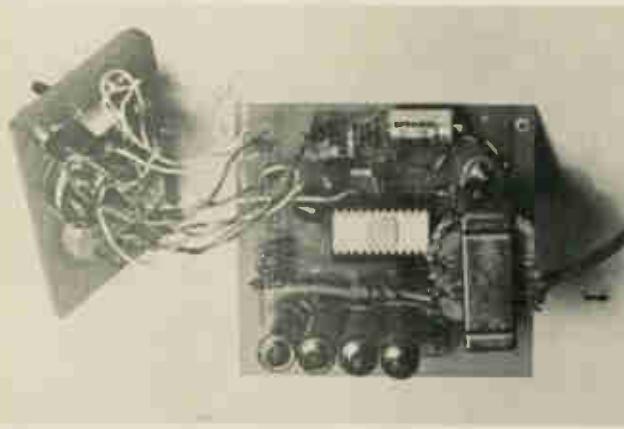Connect one of the 20V outputs from the transformer to the points near R4 marked '0' and '20'. Switch the mains on and check the heater filaments in the display. If you have followed the instructions carefully, and chosen the value of R4 correctly, you may just be able to see the faintest possible glow from the heaters in a



Inside view of the prototype.

SW2 causes the calendar to be displayed as long as the switch is closed, but it should be further noted that both switches should not be closed together; if they are, incorrect display conditions will result. Switch SW4 is thus used when time is being set initially via SW5 (described next). However, the clock circuit will continue counting, even though SW4 is closed — counting will actually occur on digits less significant than the digit being set.

will run from '0' to '9'; DIG 3 from '0' to '3'; and DIG 1 with DIG 2 from '01' to '12'. As before, the setting of any one digit will not affect the setting of the others, with the obvious exception of DIG 1 and DIG 2 which set in conjunction with each other. When the calendar is set, the clock time display will reset to the AM portion of the day automatically. This means that calendar setting should always be done before setting the time, or considerable frustration is likely to ensue!



Rear view showing the switches and speaker.

totally darkened room! If you can see nothing, do not worry — this is highly desirable, and you know from your early testing of the heaters and segments that all is probably well.

Transformers do, however, vary in their output voltages, and you may have a perceptible glow from the heaters. Should this occur, you will need to switch the mains off and change R4 for a slightly higher value. Don't forget that R4 will be very hot by this time.

TIMTRONIC

When you are happy with the heaters switch off again, and connect the other 20V output from the transformer to the two remaining points marked '0' and '20'. Switch on again, and check the voltage across C3, and the voltage between the positive end of C3 and pin 2 of the socket. The voltage across C3 should lie between 30V and 40V while the voltage between C3 and pin 2 should be between 15V and 20V.

If your voltages do not correspond with these, check the power supply components. Look particularly at the polarity of capacitor C3, and the polarity of the diodes D1, D3 and D4. If the polarities are right, check the functioning of these components, their positioning on the PCB, the adequacy of the soldering, and so on.

When the correct voltage ranges are obtained, switch off the mains again. Now check on the two preset potentiometers. The wiper of each one should be set to approximately mid-position.

The integrated circuit can now be inserted into the socket. Take the greatest care at all stages of this operation, because this is an expensive component deserving respect!

Handle it by the ends, keeping your fingers away from the pins. Take care not to short the pins out, even with your fingers, and do not short the pins to any component on the board. Make especially sure that, when you start to insert the component into the socket, it is the right way round. Pin 1 on the component is identified with an arrow, while Pin 1 for the socket is clearly marked on the board and in Fig. 7. Seat the component firmly into the socket before proceeding further.

The mains can now be switched on again. The display should then light up and show '88.88'. This particular display of four '8's is the standard indication that power has failed and then been restored. If the display appears to be flickering or pulsing, make a small adjustment in either direction to the preset R21 until the flicker disappears.

Now close the 'Time Set' control SW4 and then open it again. The display should immediately change to '00.00' in the case of 24-hour clocks, or '12.00' in the case of 12-hour clocks. Counting will also begin, but this will only become obvious quickly on the Clock-Calendar, when the display will switch from time to calendar after 8 seconds; hold the calendar display for 2 seconds; and then switch back to time. It will become clear that the Alarm Clock is counting satisfactorily after 1 minute, when DIG 4 will change to '1'.

CONCLUDING THE CONSTRUCTION

All that remains now is to mount the transformer permanently and to place the clock in whatever case you have decided to use, setting the switches into their final positions.

The transformer will need to be mounted on the p.c.b. if you are planning to use the plastic case designed for the clock.

It is highly likely that the tags on the secondary winding of the transformer not only protrude above the top of the secondary, but also below. If this is the case, you will have to bend those below either backwards or forwards, to clear resistor R4.

Before you finally mount the transformer, there is one more point to note. We suggest you place a small piece of insulating material — black vinyl insulating tape, for example — between the base of the transformer and the PCB. Make the insulation a little larger than the transformer base and, if you use insulating tape, bend it up slightly on each side of the transformer, so that it runs along the windings. This will avoid any last possibility of shorts occurring between the transformer and any other item on the PCB.

Actually mounting the transformer and reconnecting the secondaries to the board is straightforward, and requires no comment beyond a suggestion that the connecting wires should be as short as possible, and neatly twisted together.

ALARM CLOCKS: SETTING THE TIME

1. For ease of explanation, let's assume the time, when you come to set the clock is 10.13 p.m.

With one hand, close the 'Time Set' switch SW4. With the other hand, move Switch SW5 to its 4th position. The hours will now start to count forward at the rate of 2 digits per second. This isn't nearly as fast as it sounds, as you'll see. If you have built a 24-hour clock, you should be ready to move SW5 to its 3rd position when the hours figure reaches '22'. If you have built a 12-hour clock, be ready to move SW5 when the hours reach '10'.

3. When you move SW5 to its third position, the hours will stop counting and remain set on either '22' or '10' while the tens of minutes begin counting. Again, be ready to change SW5 to its 2nd position when the tens of minutes reaches '1'.

4. When SW5 is changed to its second position, tens of minutes will stop counting and remain on '1', while the minutes units will begin counting. Again, you should be ready to change SW5 back to its 1st position when the units figure — and this is

important, if you want accuracy — reaches either '4' or '5'.

5. When SW5 is turned back to its 1st position, the time showing on the display will either be '10.14' or '10.15'. Throughout this process you will have kept the 'Time Set' switch SW4 closed, and you should continue to keep it closed to prevent the clock starting to count before you are ready.
6. On the assumption you have a phone and it's close at hand, you can now dial the 'speaking clock'. As it announces that the time is precisely 10.14 or 10.15 release the 'Time Set' switch.
7. The telephone clock will continue to announce the time for about 90 seconds and we suggest you stay on the line until the next precise minute arrives. Your morale will be enormously boosted to see your clock change in precise synchronism with the speaking clock!

CLOCK CALENDARS: SETTING THE TIME

1. The basic instructions for setting the time for the Clock Calendar are exactly as given for the Alarm Clock.

2. Remember, however, that less significant digits than those actually being set continue to count, even though the 'Time Set' switch is held closed. This means that minutes and seconds are counting while the hours are being set, and seconds are counting while the minutes are being set.

3. If near-perfect accuracy is wanted, it is therefore necessary to slightly change the setting order. We then use the fact that less significant figures to those being set continue to count in the Clock Calendar, while more significant figures are disconnected from the counting chain. The only constraint is that the setting must be done at any time before 12 noon, because we shall be setting the calendar after the clock, and when the calendar is set, the clock reverts to the AM part of the day.

4. First, switch the mains off completely, and then on again. This will produce the standard 'power failure' indication of '88.88'. Now move SW5 to its 4th position, and then obtain a standard reference time source, such as the speaking clock. Stand by with your finger on 'Time Set' switch SW4 and, when an exact minute is reached by the time source close 'Time Set' and hold it closed.

5. The display will now switch to '00.00', seconds will start to count internally, and the hours display will start to count visibly.

6. When the correct hours indication appears, move SW5 to its 3rd position to begin incrementing the tens of

Henry's

Your Complete Audio-Electronic Stores

BUILD THE TEXAN

20 + 20 WATT INTEGRATED
I.C. STEREO AMPLIFIER

* FREE TEAK CABINET with complete kits!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardner low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES -DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc. (Parts list Ref. 20 on request). Constructional details (ref no 21) 30p.

SPECIAL KIT PRICE £28.50 P & P 45p




PW Tricolour
as per April 1973
1973 Parts list on
request (52A)

COMPLETE WITH FREE TEAK CABINET
Designer approved kits distributed by Henry's Radio Ltd.

* SLIM DESIGN WITH SILVER TRIM
Overall chassis size
145" x 6" x 2" high

VAT ALL PRICES ARE EXCLUSIVE OF 10% VAT WHICH MUST BE ADDED TO ALL ORDERS INC. CARR/PACKING.
(NOTE: CATALOGUE IS NOT SUBJECT TO VAT).

INTEGRATED CIRCUITS

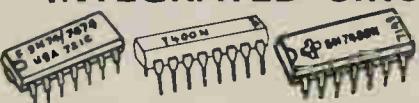

Why buy
alternative
when you can
buy the genuine
item direct from us
at competitive
prices from stock?

BRANDED FROM TEXAS I.T.T. FAIRCHILD

Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
BN7400	20p	18p	18p	BN7451	20p	18p	18p
BN7401	20p	18p	18p	BN7453	20p	18p	18p
BN7402	20p	18p	18p	BN7454	20p	18p	18p
BN7403	20p	18p	18p	BN7460	20p	18p	18p
BN7404	20p	18p	18p	BN7470	20p	18p	18p
BN7405	20p	18p	18p	BN7472	20p	18p	18p
BN7406	20p	18p	18p	BN7473	20p	18p	18p
BN7407	20p	18p	18p	BN7474	40p	38p	38p
BN7408	20p	18p	18p	BN7475	40p	38p	38p
BN7409	40p	38p	38p	BN7476	48p	42p	38p
BN7410	20p	18p	18p	BN7478	40p	38p	38p
BN7411	20p	18p	18p	BN7480	78p	67p	67p
BN7412	42p	38p	38p	BN7481	81-25	81-15	81-10
BN7413	30p	27p	25p	BN7482	87p	80p	70p
BN7414	30p	27p	25p	BN7483	£1.00	90p	80p
BN7415	30p	27p	25p	BN7484	90p	85p	80p
BN7416	30p	27p	25p	BN7485	90p	85p	80p
BN7417	30p	27p	25p	BN7486	41p	38p	38p
BN7418	20p	18p	18p	BN7487	78p	70p	67p
BN7419	20p	18p	18p	BN7488	78p	70p	67p
BN7420	48p	40p	40p	BN7489	78p	70p	67p
BN7421	48p	40p	40p	BN7490	78p	70p	67p
BN7422	48p	40p	40p	BN7491	78p	70p	67p
BN7423	48p	40p	40p	BN7492	78p	70p	67p
BN7424	48p	40p	40p	BN7493	78p	70p	67p
BN7425	48p	40p	40p	BN7494	80p	78p	70p
BN7426	48p	40p	40p	BN7495	80p	78p	70p
BN7427	48p	40p	40p	BN7496	£1.00	97p	95p
BN7428	60p	48p	42p	BN7497	82p	80p	70p
BN7429	20p	18p	18p	BN7498	82p	80p	70p
BN7430	20p	18p	18p	BN7499	82p	80p	70p
BN7431	48p	40p	40p	BN7500	82p	80p	70p
BN7432	48p	40p	40p	BN7501	82p	80p	70p
BN7433	70p	61p	44p	BN7502	82p	80p	70p
BN7434	65p	60p	50p	BN7503	82p	80p	70p
BN7435	65p	60p	50p	BN7504	81-48	81-38	81-30
BN7436	65p	60p	50p	BN7505	81-48	81-38	81-30
BN7437	65p	60p	50p	BN7506	81-48	81-38	81-30
BN7438	65p	60p	50p	BN7507	81-48	81-38	81-30
BN7439	20p	18p	18p	BN7508	81-48	81-38	81-30
BN7440	20p	18p	18p	BN7509	81-48	81-38	81-30
BN7441	78p	78p	78p	BN7510	80p	78p	70p
BN7442	78p	78p	78p	BN7511	81-48	81-38	81-30
BN7443	£1.00	98p	90p	BN7512	81-48	81-38	81-30
BN7444	£2.00	£1.75	£1.50	BN7513	80p	78p	70p
BN7445	£2.00	£1.75	£1.50	BN7514	80p	78p	70p
BN7446	£2.00	£1.75	£1.50	BN7515	81-25	81-20	81-15
BN7447	£1.75	£1.50	£1.45	BN7516	82-55	82-47	81-38
BN7448	£1.75	£1.50	£1.45	BN7517	81-50	81-40	81-30
BN7450	20p	18p	18p	BN7518	81-50	81-40	81-30
IC SOCKETS 16 lead 17p 14 lead 15p 8 lead 15p				BN7519	84-60	83-70	83-85

Prices of 7400 series are calculated on the total number ordered regardless of mix. Larger quantity prices phone 01 402 4891

TEST EQUIPMENT

SE250B Pocket Pencil Signal Injector £1.00

SE500B Pocket Pencil Signal Tracer £1.50

THL33D 2KVA/50Hz £4.55

TE15 Grid Dip Meter 440 KHz-280 mHz £13.65

500 30 KV Multimeter £8.25

With leather case £10.50

200H 20 KV Multimeter £4.20

With case £9.50

AF105 50 KV Multimeter £8.50

With case £9.50

U4341 AC/DC Multimeter with transistor tester. Steel case £16.50

RF Generator 120KHz-500MHz £15.05

TE20D Audio Generator 20Hz-200KHz £17.50

Carr. 25p

C-1 3" Pulse Scope, 10Hz-10mHz £30.00

Carr. 50p

TE65 Valve Voltmeter 28 ranges £17.50

Carr. 40p

ALL NOMBREX MODELS IN STOCK

"BANDSPREAD" PORTABLE

MW/LW TUNER

MI 3 - Superhet

MW/LW radio

Tuner to build

S.M. Tuning

Mullard Module

etc. ALL PARTS

£4.85. P. & P. 15p

7 SEG & MIXIE TUBES
(Post 15p for 1 to 6)
XN3, XN13, GN6 0-9 side view
with data, 85p.

GNP-7, GNP-8 0-9 side view
with decimal points and data,
85p.

3015F 7 seg. £2 each, £7 per 4
with data.

Ref. No. 31 15p.

ULTRASONIC TRANSDUCERS
Operate at 40kc/s up to 100
yds. Ideal remote switching
and signalling. Complete with
data and circuits.

PRICE PER PAIR £9.00. Post 10p.

BN7441

BN7442

BN7443

BN7444

BN7445

BN7446

BN7447

BN7448

BN7449

BN7450

SILICON RECTIFIERS
WIRE ENDED PLASTIC

Type P.I.V. 1-11
1 Amp miniature

IN4001 50 6p

IN4002 100 8p

IN4003 200 8p

IN4004 400 10p

IN4005 600 10p

IN4006 800 12p

IN4007 1000 15p

1.5 amp miniature

IN4001 50 8p

PL4002 100 8p

PL4003 200 10p

PL4004 400 10p

PL4005 600 12p

PL4006 800 15p

PL4007 1000 16p

SL4030D PLESSEY
3 WATT R.M.S. I.C.
Complete with 8 page Data
Booklet and Circuits £1.50.
(P.C. Board Stereo 6p; Heat
Sink 14p).

Also Sinclair IC12 £1.00.

TH9013P-20 watt Power Amp
Module £4.57.

TH9014P-IC Preamp £1.50.

Data/Circuits for above
No. 42-120.

ZN414 Rug IC £1.20.

LINAR (O/P AMPS)

702C TOS 75p

709C TOS9 35p

709C D.I.L. 35p

723C TOS9 1.00

725C (TOS) £4.50

741C D.I.L. 55p

741C TOS9 55p

741C D.I.L. 55p

747C TOS9 £1.10

747C D.I.L. £1.10

747C D.I.L. 60p

7274P D.I.L. 10p

7274P D.I.L. 10p

TRANSISTORS, IC's,
DIODES, TRIACS,
BRIDGES, SCR'S, ZENERS,
LDR'S.

This advert. contains just a
small selection of the thou-
sands of devices kept in stock.

Send for Stock List Today!

Quantity prices Phone:

01-402 4891.

Fully guaranteed

£3.50 (post 15p)

ALL stores within 200 yards - call in and see for yourself

404-406 Electronic Components and Equipment 01-402 8381

354-356 High Fidelity and Tape Equipment 01-402 5854

309 PA-Disco-Lighting High Power Sound 01-723 6963


303 Special offers and bargains store

All mail to 303 Edgware Road, London W2 1BW

(As featured in "Practical Wireless"
May to August 1972)

CATALOGUE

IN ELECTRONICS?
THIS IS A MUST!

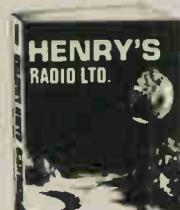

LATEST EDITION!
Fully detailed and illustrated covering every aspect of Electronics—New data—New Information. 10,000 Stock Lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid
(40p FOR CALLERS)

PLUS! FIVE 10p VOUCHERS

For use with purchases


Send to this address—HENRY'S RADIO LTD. (Dept WW)
3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail to '303' and callers to '404' see below.

3 Amp

</div



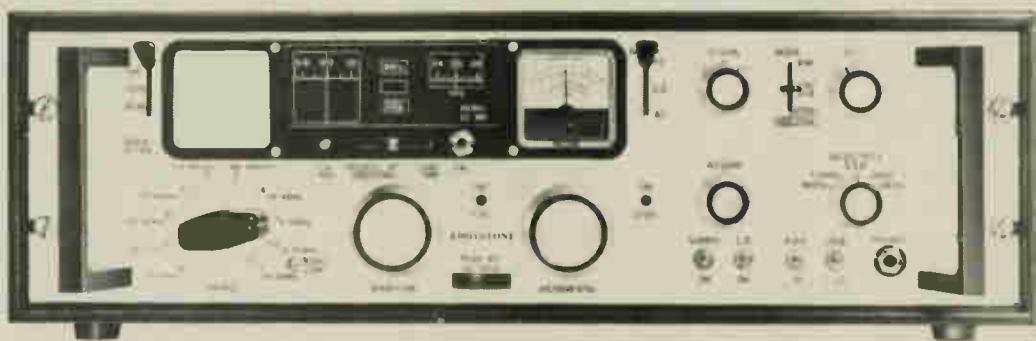EC958 series of receivers 10kHz to 30MHz In world-wide use



Simplicity

Reliability

Economy

Professional high-stability receiver series for a wide variety of applications. The standard version can be used as a self-contained F.S.K. terminal, or as a dual-diversity terminal with common oscillator control. Variants are available for Lincompex terminal use, for specialized network monitoring surveillance and for marine applications.

Please send for an illustrated brochure to:

Eddystone Radio Limited

Alvechurch Road, Birmingham B31 3PP Telephone: 021-475 2231 Telex: 337081

A member of Marconi Communication Systems Limited.

LTD/ED99

TIMTRONIC



minutes. Again, when the right digit appears, move SW5 to its 2nd position.

7. This will increment the units of minutes, and SW5 should be moved back to its original 1st position when the correct minutes unit appears. Providing you have completed the process within one minute from obtaining the reference time, this will be the minutes unit figure of the reference time.
8. Only after you have the correct time indication, and switch SW5 is back in its first position, should you release 'Time Set' switch SW4.

ALARM CLOCKS: SETTING THE ALARM

1. Setting the alarm is a very simple matter, and is done exactly the same way that the time was set, excepting that the 'Alarm Set' switch SW2 should be held closed throughout the process, and not 'Time Set' switch SW4. The time will remain undisturbed throughout the process but remember not to open the 'Alarm Set' switch until switch SW5 is back in its 1st position.
2. To test the alarm operation, set an alarm time one or two minutes ahead of the time display on the main clock, and close the 'Alarm Enable' switch SW1. When the main clock reaches the time set on the alarm, a quiet but insistent 'beep... beep... beep' sound will be heard from the loudspeaker.
3. If the 'Snooze' switch SW3 is momentarily closed, the alarm note will cease immediately, and resume after 7 minutes have elapsed.
4. If 'Alarm Enable' switch SW1 is opened, the alarm note will also cease immediately. The 'Alarm Enable' switch may then be closed again, as the alarm will have automatically reset and will not come on again for another 24 hours.
5. If you have constructed a 12-hour version of the Alarm Clock, there is one further point which you will need to note. The display is 12-hour but the clock operation remains 24-hour, as does the alarm operation also. It is therefore possible to set the alarm to a certain time, and for that time to be reached on the main clock display without the alarm sounding. This is because the alarm will have been set into the other 12-hour segment of the 24-hour clock. You should therefore check, if you are operating a 12-hour clock function, that this is not likely to occur, by testing the alarm function. We

would not like you to hold us responsible if you arrive at work 12 hours late!

6. When you first test the alarm function after construction, it may be that the alarm will only produce one quick 'beep', or not sound at all. Should this happen, place a 3.9K resistor in series with the grid of DIG 3. This should cure the problem. If the brightness of DIG 3 is slightly affected by the resistor, place a similar resistor in series with the other three grids to restore even brilliance.

CLOCK CALENDARS: SETTING THE CALENDAR

1. Calendar setting is achieved very simply by pressing 'Calendar Set' switch SW2 and then moving SW5 to its 4th position.
2. This will cause the months to increment but remember that the calendar display shows the months *first* and the day-date *second*.
3. When the right month figure is shown move SW5 to its 2nd position to increment days.
4. When the calendar setting is correct, move back to its 1st position and release 'Calendar Set' switch SW2.

EXTRA DATA ON THE CLOCK INTEGRATED CIRCUITS

Experienced constructors may be interested in some extra information. We suggest, however, that great care is exercised if any circuit modifications or additions are attempted.

THE ALARM CLOCK AM OUTPUT

Pin 16 of the chip carries an AM output which is near V_{ss} for an AM indication and is open-circuit for a PM indication. It can be used to convert a seven-segment 'P' to an 'A' for example, or to advance an external calendar. The transition occurs at 12 hour intervals.

1Hz OUTPUT

Pin 19 of the chip carries a 1 Hertz square-wave. Blinking of an external a.m./p.m. or seconds indicator is possible. The 1Hz output is modulated to maintain the relative intensity at the same level as the time display.

TEMPORARY AC POWER FAILURE

Temporary power failure can be tolerated if a battery back-up is provided. Pin 24 oscillates at a frequency determined by R1 and C1, and continues to provide an approximate line frequency provided that a V_{dd} is maintained within the chip's operating range. With the display tubes used, power is not required to operate them, since the filaments are a.c. driven. A small rechargeable battery is required, however to power the chip, and this must supply at least 18V. However, the cost of rechargeable cells for this facility is so high that many readers will think this facility something of an extravagance.

THE CLOCK CALENDAR ALT OUTPUT

Pin 19 of the chip carries an ALT output, which indicates whether the time or the date is being displayed. During the time display, the output will be near V_{ss}. The indication occurs when neither 'Time Set' nor 'Calendar Set' are closed. The output can be used to select either a colon or a dash, as required, or used to select the 24-hour display during the time display period, if 24-hour display conditions are preferred.


FULL SIX-DIGIT DISPLAY

A full six-digit display is possible, basing the necessary wiring on that demonstrated by the printed circuit board supplied. A modification to the value of R4 will be needed, and this should be calculated with great care, using data and voltage indications provided elsewhere in these instructions. It will probably be possible to contain the extra two digits on the PCB, if the transformer can be mounted elsewhere. Alternatively, a new display section can be constructed, using Veroboard or a similar material, and running leads from the main PCB to appropriate points on it. Pins 3 to 8 or the chips provide the digit drives for the display, while pins 9 to 15 are the seven-segment decoded segment drives. Pin 1 is V_{ss} and pin 2 is V_{dd}, which should be 0V and between 11V and 18V respectively.

Expensive Equipment

Then why not have the aerial it deserves ??

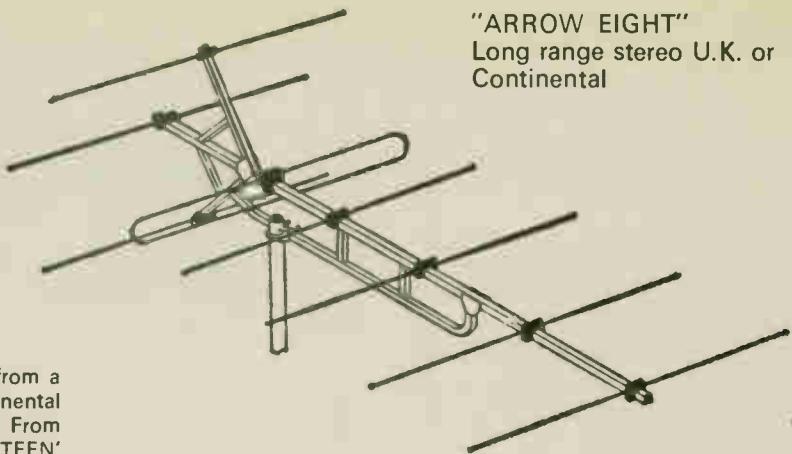Whether your requirement is simply clean Stereo from a local transmitter, or good recording from Continental stations, our extensive range meets the demand. From the basic 'H' to the superlative 'ARROW SIXTEEN' strict quality control, and design expertise, give specifications to meet every need.



SPECIFICATIONS:	Standard			Economy Arrow			Main Arrow Range			
	H	3EI	4EI	5	6	7	Six	Seven	Eight	"16"
Model	H	3EI	4EI	5	6	7	Six	Seven	Eight	"16"
Gain @ 93Mhz.	2.5	4	5	6.8	7.6	8.8	9.7	10.8	12.3	14.8
F. to B. dB	9.2	13.7	15.9	18	20	22	22.8	23.9	26.5	29
A. Ang. Degrees	78	68	67	66	63	59	58	56	45	38
Length-inches	32	42	72	42	72	102	84	114	162	222
Height "	—	—	—	21	21	21	40	40	58	65
W/load @ 100mph	12lb	16lb	20lb	24lb	27lb	30lb	32lb	38lb	55lb	90lb
PRICE Including V.A.T. & Carr.	£ 2.75	£ 3.85	£ 4.95	£ 7.15	£ 8.80	£ 10.45	£ 12.10	£ 13.20	£ 21.45	£ 40.70

NEW ZODIAC ELEVEN MODELS 16 to 142 ELEMENT

- *High Forward Gain
- *Narrow Acceptance Angle
- *Excellent Back Rejection
- *Flat Response
- *Minimal Side Lobes


U.H.F. STANDARD RANGE

- *Good Basic Design
- *Low Weight
- *10, 15, 20 & 30 Elements

AERIAL ROTATORS

We stock Stolle Auto and Memo models.
For heavy duty work we have the C.D.R. A.R.22.

TRADE SUPPLIED
DETAILS ON REQUEST

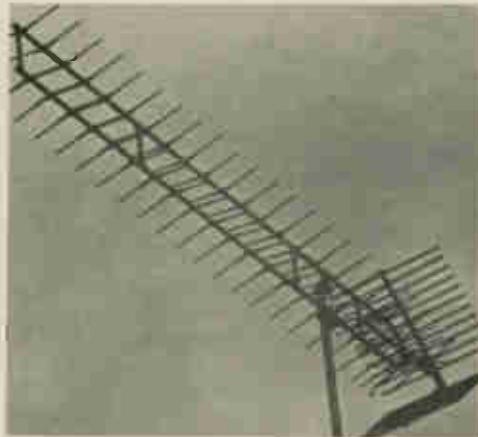

ZODIAC TWENTY-FIVE
WIDEBAND - GAIN - 15 to 19 dB
F. to B. 28-34 dB. A. An. Min. 14°.

INSTALLATION SERVICE

- *Fully skilled rigging teams.
- *Field strength meter alignment.
- *Special ladders for roof work.
- *Percussion masonry drills.
- *Full insurance cover—all risks.
- *Five years' guarantee parts and labour.
- RANGE—up to 100 miles from LUTON.
Booking—write or phone for details.

ARROW RANGE FEATURES

- *New reflector design giving high gain and good front to back ratio.
- *Narrow acceptance angles and minimal side lobes.
- *Ideal for rotator operation.
- *Suitable for Continental and difficult U.K. areas.
- *Deep support boom for rigid mounting.

LONG RANGE U.H.F. COLOUR GROUP "A" or WIDEBAND

- *British made by Specialists
- *Low Weight and Windloading
- *Twin & Quadruple Booms.
- *Businesslike Appearance
- *Ideal for Rotor Operation

U.H.F. "ARROW" RANGE

- *Efficient Reflector Design
- *Five Models Groups A, B & C.
- *High Performance — Low Cost

ACCESSORIES

Complete range of masts, brackets etc. Send for catalogue of all products.

MAIL ORDER SERVICE

Fast service — goods despatched promptly on receipt of cash or cheque with order. Advice free by post or telephone.

R SMITH AERIALS

T.V.

F.M.

Designers & Manufacturers of Radio and Television Aerials of all Types.

98 ASH ROAD, LUTON, LU2 9AX Telephone: LUTON 36561

For catalogue or information 0582-36561

9.0 to 6.0 Monday to Saturday—callers welcome—5 mins from exits 10 & 11 M.1. motorway

THE WATERGATE BUGGING

— how it was done, Collyn Rivers reports.

SOMETIME during the second week in June 1972, two men, James McCord and Howard Hunt, entered the Watergate headquarters of the US Democratic Party and installed a number of bugging devices in selected areas.

The two conspirators were subsequently spotted by an alert security guard — and their subsequent trial and indictment triggered off a scandal that has made the late and unlovely President Harding's escapades of the 1920's seem by comparison to be mere peccadilloes.

The main bugs consisted of so-called 'infinity transmitters' and were installed inside each of four telephones inside the Democratic Party's headquarters.

The Watergate infinity bugs were adaptations of the 'conventional' infinity transmitters described in our article on bugging in June, 1972.

These bugs enabled all sound within the bugged rooms to be picked up and transmitted to the conspirators' listening station in the Howard Johnson Hotel — just across the road from the Watergate building.

HOW THEY WORKED

A block schematic drawing of these bugs is shown (in simplified form) in Fig. 1. The section that was installed inside each telephone is shown in

dotted lines. This section consists of a frequency sensitive decoder that actuates a miniature multi-pole relay. The conspirators used a resonant reed encoder that was switched onto the telephone line *immediately* after the bugged telephone's number had been dialled. This encoder generated a tone (probably 500 Hz) that was detected by the decoder concealed within the bugged telephone. This caused the relay to be actuated which in turn open-circuited the bell ringing circuit and connected the handset's microphone to an inbuilt audio amplifier the output of which was connected to the telephone line.

Thus the bugs, once actuated by the conspirators, picked up all sound within the room and transmitted it to the bugging headquarters — even though the handsets were still on the rests: if a third party tried to ring the number whilst the bug was in use he would receive a normal 'busy' tone.

The conspirators also installed a small microphone and low-power FM transmitter inside a fire alarm smoke detector that was conveniently fitted to the ceiling of the Democratic headquarters. The low-power signals from this unit were received just outside the Watergate building and then relayed by a more powerful

transmitter to the bugging headquarters across the road.

The relatively sophisticated bugs described above appeared to be mass-produced. They carried no manufacturer's name — but this lack of identification is normal practice. Certainly, even outside the USA, it is not too difficult to purchase this type of equipment if one is sufficiently determined and can pay the high prices involved. But surprisingly — at least to those who are not aware of the extraordinary amount of surveillance equipment commercially available — most of the electronic bugging equipment used by McCord and Hunt was purchased on the open market. For example the conspirators bought a considerable quantity of communications equipment — transmitters, receivers, microphones, etc. from the Kelcom Division of Bell & Howell. Invoices and shipping documents from that firm show that the equipment was shipped to McCord and his associates on May 26 — about three weeks before the bugs were installed.

Bell & Howell state that the equipment sold to McCord was normal off-the-shelf communications gear. The company does in fact make surveillance equipment but this they stress is sold only to 'bona-fide law enforcement agencies'. They emphasize that they did not make any of the actual bugging units used in the Watergate conspiracy.

Another firm that supplied equipment to McCord was the CEI Division of Watkins-Johnson.

This division specializes in the manufacture of military electronic countermeasure receivers — it is believed that the sale to McCord and his associates was for a type RS 11 wideband receiver. This receiver is a standard commercial item — produced as an offshoot of the company's military equipment — and is available to anyone who wishes to buy one.

The Watergate inquiry is not yet over and it is quite probable that evidence may yet be given which will highlight the ever increasing use of surveillance equipment — not only by industrial saboteurs — but by the FBI, the CIA, the Secret Service, and now it seems at the highest levels of government itself. ●

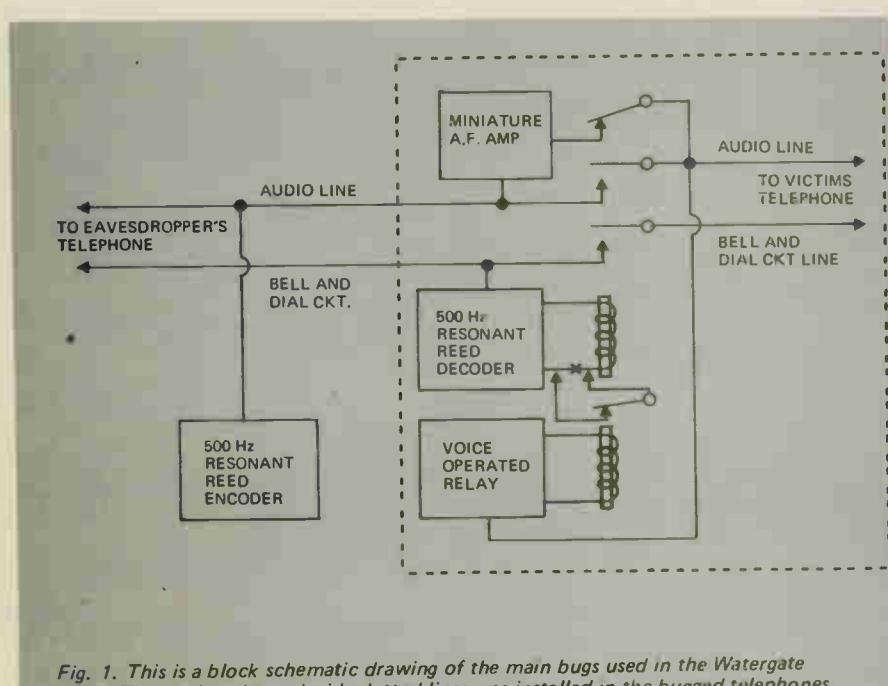


Fig. 1. This is a block schematic drawing of the main bugs used in the Watergate affair. The section shown inside dotted lines was installed in the bugged telephones.

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

VOLTAGE RANGE											
AC107	0.60	AD162	0.33	BC148	0.10	BD137	0.45	BF188	0.40	OC19	✓ 25
AC113	0.20	AD161 &	BC149	0.50	BD138	0.50	BF194	0.18	OC20	✓ 0.63	
AC115	0.23	AD162 (MP)	BC150	0.18	BD139	0.40	BF195	0.14	OC22	✓ 0.63	
AC117*	0.20		BC161	0.20	BD140	0.45	BF196	0.14	OC23	✓ 0.63	
AC122	0.12	ADT140	0.60	BC152	0.17	BD153	0.80	BF197	0.14	OC24	✓ 0.65
AC123	0.17	ADT141	0.24	BC153	0.23	BD175	0.70	BF200	0.45	OC25	✓ 0.65
AC126	0.17	ADT15	0.24	BC154	0.30	BD176	0.80	BF222	0.95	OC46	✓ 0.25
AC127	0.17	ADT16	0.24	BC157	0.18	BD177	0.64	BF257	0.45	OC48	✓ 0.60
AC128	0.17	ADT17	0.24	BC158	0.12	BD178	0.68	BF258	0.60	OC59	✓ 0.60
AC132*	0.14	ADT18	0.38	BC159	0.12	BD179	0.70	BF259	0.65	OC35	✓ 0.62
AC134	0.14	ADT19	0.38	BC160	0.45	BD180	0.70	BF262	0.58	OC36	✓ 0.60
AC137	0.23	ADT19	0.60	BC161	0.50	BD181	0.68	BF263	0.55	OC41	✓ 0.20
AC141	0.14	ADT20	0.26	BC167	0.18	BD182	0.45	BF270	0.25	OC42	✓ 0.24
AC141K	0.17	ADT21	0.28	BC168	0.18	BD187	0.70	BF271	0.25	OC44	✓ 0.18
AC142	0.14	ADT22	0.30	BC169	0.18	BD188	0.70	BF272	0.25	OC45	✓ 0.12
AC142K	0.17	ADT23	0.50	BC170	0.60	BD189	0.75	BF273	0.25	OC70	✓ 0.10
AC151	0.18	ADT24	0.60	BC171	0.14	BD190	0.75	BF274	0.25	OC71	✓ 0.10
AC154	0.20	ADT25	0.50	BC172	0.14	BD195	0.85	BF279	0.60	OC72	✓ 0.14
AC155	0.20	ADT26	0.45	BC173	0.14	BD196	0.85	BF280	0.27	OC74	✓ 0.14
AC156	0.20	ADT26	0.45	BC174	0.14	BD197	0.90	BF284	0.22	OC75	✓ 0.15
AC157	0.24	ADT27	0.38	BC175	0.32	BD198	0.90	BF285	0.20	OC76	✓ 0.15
AC163	0.20	ADT27	0.38	BC176	0.19	BD199	0.90	BF286	0.22	OC77	✓ 0.25
AC166	0.20	ADT28	0.38	BC177	0.19	BD200	0.90	BF287	0.24	OC78	✓ 0.14
AC167	0.20	ADT29	0.38	BC178	0.19	BD201	0.90	BF288	0.24	OC79	✓ 0.14
AC168	0.24	ADT29	0.38	BC179	0.19	BD205	0.90	BF289	0.24	OC80	✓ 0.18
AC169	0.24	ADT29	0.38	BC180	0.24	BD206	0.90	BF290	0.20	OC82	✓ 0.15
AC175	0.24	ADT29	0.38	BC181	0.24	BD207	0.90	BF291	0.20	OC82D	✓ 0.15
AC176	0.24	ADT29	0.38	BC182	0.24	BD208	0.90	BF292	0.20	OC83	✓ 0.20
AC177	0.24	ADT29	0.38	BC182L	0.10	BD209	0.90	BF293	0.17	OC84	✓ 0.20
AC178	0.24	ADT29	0.38	BC183	0.10	BD210	0.90	BF294	0.17	OC85	✓ 0.20
AC179	0.24	ADT29	0.38	BC183L	0.10	BD211	0.47	BF295	0.20	OC86	✓ 0.20
AC180	0.17	ADT29	0.38	BC184	0.10	BD212	0.47	BF296	0.20	OC87	✓ 0.20
AC180K	0.20	ADT29	0.38	BC184L	0.10	BD213	0.70	BF297	0.25	OC88	✓ 0.20
AC181	0.17	ADT29	0.38	BC185	0.28	BD214	0.45	BF298	0.25	OC89	✓ 0.20
AC181K	0.20	ADT29	0.38	BC186	0.28	BD215	0.45	BF299	0.25	OC90	✓ 0.20
AC187	0.24	ADT29	0.38	BC187	0.28	BD216	0.45	BF300	0.25	OC91	✓ 0.20
AC187K	0.24	ADT29	0.38	BC188	0.28	BD217	0.45	BF301	0.25	OC92	✓ 0.20
AC188	0.24	ADT29	0.38	BC189	0.28	BD218	0.45	BF302	0.25	OC93	✓ 0.20
AC189	0.24	ADT29	0.38	BC190	0.28	BD219	0.45	BF303	0.25	OC94	✓ 0.20
AC190	0.24	ADT29	0.38	BC191	0.28	BD220	0.45	BF304	0.25	OC95	✓ 0.20
AC191	0.24	ADT29	0.38	BC192	0.28	BD221	0.45	BF305	0.25	OC96	✓ 0.20
AC192	0.24	ADT29	0.38	BC193	0.28	BD222	0.45	BF306	0.25	OC97	✓ 0.20
AC193	0.24	ADT29	0.38	BC194	0.28	BD223	0.45	BF307	0.25	OC98	✓ 0.20
AC194	0.24	ADT29	0.38	BC195	0.28	BD224	0.45	BF308	0.25	OC99	✓ 0.20
AC195	0.24	ADT29	0.38	BC196	0.28	BD225	0.45	BF309	0.25	OC100	✓ 0.20
AC196	0.24	ADT29	0.38	BC197	0.28	BD226	0.45	BF310	0.25	OC101	✓ 0.20
AC197	0.24	ADT29	0.38	BC198	0.28	BD227	0.45	BF311	0.25	OC102	✓ 0.20
AC198	0.24	ADT29	0.38	BC199	0.28	BD228	0.45	BF312	0.25	OC103	✓ 0.20
AC199	0.24	ADT29	0.38	BC200	0.28	BD229	0.45	BF313	0.25	OC104	✓ 0.20
AC200	0.24	ADT29	0.38	BC201	0.28	BD230	0.45	BF314	0.25	OC105	✓ 0.20
AC201	0.24	ADT29	0.38	BC202	0.28	BD231	0.45	BF315	0.25	OC106	✓ 0.20
AC202	0.24	ADT29	0.38	BC203	0.28	BD232	0.45	BF316	0.25	OC107	✓ 0.20
AC203	0.24	ADT29	0.38	BC204	0.28	BD233	0.45	BF317	0.25	OC108	✓ 0.20
AC204	0.24	ADT29	0.38	BC205	0.28	BD234	0.45	BF318	0.25	OC109	✓ 0.20
AC205	0.24	ADT29	0.38	BC206	0.28	BD235	0.45	BF319	0.25	OC110	✓ 0.20
AC206	0.24	ADT29	0.38	BC207	0.11	BD236	0.45	BF320	0.25	OC111	✓ 0.20
AC207	0.24	ADT29	0.38	BC208	0.11	BD237	0.50	BF321	0.15	OC112	✓ 0.20
AC208	0.24	ADT29	0.38	BC209	0.12	BD238	0.50	BF322	0.15	OC113	✓ 0.20
AC210K	0.20	ADT29	0.38	BC212L	0.11	BD239	0.50	BF323	0.15	OC114	✓ 0.20
AC211	0.24	ADT29	0.38	BC213L	0.11	BD240	0.50	BF324	0.15	OC115	✓ 0.20
AC212	0.24	ADT29	0.38	BC214L	0.11	BD241	0.50	BF325	0.15	OC116	✓ 0.20
AC213	0.24	ADT29	0.38	BC215L	0.11	BD242	0.50	BF326	0.15	OC117	✓ 0.20
AC214	0.24	ADT29	0.38	BC216L	0.11	BD243	0.50	BF327	0.15	OC118	✓ 0.20
AC215	0.24	ADT29	0.38	BC217L	0.11	BD244	0.50	BF328	0.15	OC119	✓ 0.20
AC216	0.24	ADT29	0.38	BC218L	0.11	BD245	0.50	BF329	0.15	OC120	✓ 0.20
AC217	0.24	ADT29	0.38	BC219L	0.11	BD246	0.50	BF330	0.15	OC121	✓ 0.20
AC218	0.24	ADT29	0.38	BC220L	0.11	BD247	0.50	BF331	0.15	OC122	✓ 0.20
AC219	0.24	ADT29	0.38	BC221L	0.11	BD248	0.50	BF332	0.15	OC123	✓ 0.20
AC220	0.24	ADT29	0.38	BC222L	0.11	BD249	0.50	BF333	0.15	OC124	✓ 0.20
AC221	0.24	ADT29	0.38	BC223L	0.11	BD250	0.50	BF334	0.15	OC125	✓ 0.20
AC222	0.24	ADT29	0.38	BC224L	0.11	BD251	0.50	BF335	0.15	OC126	✓ 0.20
AC223	0.24	ADT29	0.38	BC225L	0.11	BD252	0.50	BF336	0.15	OC127	✓ 0.20
AC224	0.24	ADT29	0.38	BC226L	0.11	BD253	0.50	BF337	0.15	OC128	✓ 0.20
AC225	0.24	ADT29	0.38	BC227L	0.11	BD254	0.50	BF338	0.15	OC129	✓ 0.20
AC226	0.24	ADT29	0.38	BC228L	0.11	BD255	0.50	BF339	0.15	OC130	✓ 0.20
AC227	0.24	ADT29	0.38	BC229L	0.11	BD256	0.50	BF340	0.15	OC131	✓ 0.20
AC228	0.24	ADT29	0.38	BC230L	0.11	BD257	0.50	BF341	0.15	OC132	✓ 0.20
AC229	0.24	ADT29	0.38	BC231L	0.11	BD258	0.50	BF342	0.15	OC133	✓ 0.20
AC230	0.24	ADT29	0.38	BC232L	0.11	BD259	0.50	BF343	0.15	OC134	✓ 0.20
AC231	0.24	ADT29	0.38	BC233L	0.11	BD260	0.50	BF344	0.15	OC135	✓ 0.20
AC232	0.24	ADT29	0.38	BC234L	0.11	BD261	0.50	BF345	0.15	OC136	✓ 0.20
AC233	0.24	ADT29	0.38	BC235L	0.11	BD262	0.50	BF346	0.15	OC137	✓ 0.20
AC234	0.24	ADT29	0.38	BC236L	0.11	BD263	0.50	BF347	0.15	OC138	✓ 0.20
AC235	0.24	ADT29	0.38	BC237L	0.11	BD264	0.50	BF348	0.15	OC139	✓ 0.20
AC236	0.24	ADT29	0.38	BC238L	0.11	BD265	0.50	BF349	0.15	OC140	✓ 0.20
AC237	0.24	ADT29	0.38	BC239L	0.11	BD266	0.50	BF350	0.15	OC141	✓ 0.20
AC238	0.24	ADT29	0.38	BC240L	0.11	BD267	0.50	BF351	0.15	OC142	✓ 0.20
AC239	0.24	ADT29	0.38	BC241L	0.11	BD268	0.50	BF352	0.15	OC143	✓ 0.20
AC240	0.24	ADT29	0.38	BC242L	0.11	BD269	0.50	BF353	0.15	OC144	✓ 0.20
AC241	0.24	ADT29	0.38	BC243L	0.11	BD270	0.50	BF354	0.15	OC145	✓ 0.20
AC242	0.24	ADT29	0.38	BC244L	0.11	BD271	0.50	BF355	0.15	OC146	✓ 0.20
AC243	0.24	ADT29	0.38	BC245L	0.11	BD272	0.50	BF356	0.15	OC147	✓ 0.20
AC244	0.24	ADT29	0.38	BC246L	0.11	BD273	0.50	BF357	0.15	OC148	✓ 0.20
AC245	0.24	ADT29	0.38	BC247L	0.11	BD274	0.50	BF358	0.15	OC149	✓ 0.20
AC246	0.24	ADT29	0.38	BC248L	0.11	BD275	0.50	BF359	0.15	OC150	✓ 0.20
AC247	0.24	ADT29	0.38	BC249L	0.11	BD276	0.50	BF360	0.15	OC151	✓ 0.20
AC248	0.24	ADT29	0.38	BC250L	0.11	BD277	0.50	BF361	0.15	OC152	✓ 0.20
AC249	0.24	ADT29	0.38	BC251L	0.11	BD278	0.50	BF362	0.15	OC153	✓ 0.20
AC250	0.24	ADT29	0.38	BC252L	0.11	BD279	0.50	BF363	0.15	OC154	✓ 0.20
AC251	0.24	ADT29	0.38	BC253L	0.11	BD280	0.50	BF364	0.15	OC155	✓ 0.20
AC252	0.24	ADT29	0.38	BC254L	0.11	BD281	0.50	BF365	0.15	OC156	✓ 0.20
AC253	0.24	ADT29	0.38	BC255L	0.11	BD282	0.50	BF366	0.15	OC157	✓ 0.20
AC254	0.24	ADT29	0.38	BC256L	0.11	BD283	0.50	BF367	0.15	OC158	✓ 0.20
AC255	0.24	ADT29	0.38	BC257L	0.11	BD284	0.50	BF368	0.15	OC159	✓ 0.20
AC256	0.24	ADT29	0.38	BC258L	0.11	BD285	0.50	BF369	0.15	OC160	✓ 0.20
AC257	0.24	ADT29	0.38	BC259L	0.11	BD286	0.5				

KING OF THE PAKS **Unequalled Value and Quality**
SUPER PAKS **NEW BI-PAK UNTESTED SEMICONDUCTORS**

SUMITOMO SEMICONDUCTOR

Satisfaction GUARANTEED in Every Pak, or money back.			
Pak No.	Description	Price	
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.50	
U 2	60 Mixed Germanium Transistors AF/RP	0.50	
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.50	
U 4	40 Germanium Transistor like OC81, AC128	0.50	
U 5	60 200mA Sub-Min. Silicon Diodes	0.50	
U 6	30 RU. Planar Trans. NPN like BY50A. 2N706	0.50	
U 7	16 RU. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000-5000	0.50	
U 8	50 RU. Planar Diodes DO-7 Glass 250mA like OA200 202	0.50	
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.50	
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0.50	
U 11	25 PNP SU. Planar Trans. TO-5 like 2N1132, 2N2904	0.50	
U 12	12 Silicon Rectifiers Epoxy 300mA up to 500 PIV	0.50	
U 13	30 PNP-NPN SU. Transistors OC200 & 2N104	0.50	
U 14	150 Mixed Silicon and Germanium Diodes	0.60	
U 15	25 NPN SU. Planar Trans. TO-5 like BFY51, 2N697	0.50	
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.50	
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.50	
U 18	8 6 Amp Silicon Rectifiers BY213 Type up to 600 PIV	0.50	
U 19	25 Silicon NPN Transistors like BC108	0.50	
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.50	
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0.50	
U 22	30 MADD's like JH1 Series PNP Transistors	0.50	
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 500 PIV	0.50	
U 25	25 500 MHz NPN Silicon Transistors 2N708, BY27	0.50	
U 26	20 Fast Switching Silicon Diodes like IN514 Micro-Min.	0.50	
U 27	120 Germanium AF Transistors TO-1 like AC127	0.50	
U 29	10 1 Amp MUR's TO-5 can, up to 600V CR81/23-600	1.00	
U 30	13 Plastic Silicon Planar Trans. NPN 2N2926	0.50	
U 31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0.50	
U 32	25 Zener Diodes 400mV DO-7 case 1/3-watt mixed	0.50	
U 33	18 Plastic Case 1 Amp Silicon Rectifiers in 4000 Series	0.50	
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY28 2N2002	0.50	
U 35	25 Silicon Planar Transistor PNP TO-18 2N2906	0.50	
U 36	25 Silicon Planar NPN Transistors TO-3 BY90 51.52	0.50	
U 37	30 Silicon Alloy Transistors 80-2 PNP Octo. 2N3522	0.50	
U 38	20 Fast Switching Silicon Trans. NPN MHz 2N3011	0.50	
U 39	30 KF. Germ. PNP Transistors 2N1303 5 TO-5	0.50	
U 40	10 Dual Transistor 6 lead TO-3 2N2058	0.50	
U 41	25 Germanium Transistor TO-5, OC45, NKNT72	0.50	
U 42	10 VHF Germanium PNP Transistor TO-1 NK5767, AP117	0.50	
U 43	25 RU. Trans. Plastic TO-18 AF. BC113 114	0.50	
U 44	20 RU. Trans. Plastic TO-5 HU113 NPN	0.50	
U 45	7 3A MUR. TO66 up to 600PIV	1.00	

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

A LARGE RANGE OF TECHNICAL
AND DATA BOOKS ARE NOW
AVAILABLE EX. STOCK
SEND FOR FREE LIST

**BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE
RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT
COMPETITIVE PRICES—**

ELECTRONIC SLIDE-RULERS

The MK Slide Rule is designed to simplify Electronic calculations featuring the following scales:—Conversion of Frequency and Wavelength; Calculation of L , C and F of Tuned Circuits; Reactance and Inductance; Area of Circles; Volume of Cylinders; Resistances of Conductors; Weight of Conductors; Decibel Calculations; Angle Functions; Natural Log and Exponential Functions; Multiplication and Division; Square Roots and Square Roots; Conversion of kW and HP; A must for every electronic engineer or enthusiast. Size: 2 1/2" x 4" cm., complete with case, instructions, etc.

<http://www.usc.edu>

1

18 BALDOCK STREET (A10), WARE, HERTS
TEL. (STD 0920) 61593.

OPEN MON.-SAT. 9:15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.

WARE, HERTS.

卷之三

CLOSED UNTIL 8 P.M.

卷之三

卷之三

REF ID: A672

BER 1973



SETTING UP P.A. SPEAKER SYSTEMS

by Bogen Division of
Lear Siegler Inc.,
Paramus, New Jersey.

THERE are four primary considerations when using cone or horn speakers as a part of a PA system. These are the power available to the speakers, the number of speakers, the type of speakers, and the placement and connection of speakers.

The first step is to survey the proposed installation and carefully determine how many and what type of speakers are needed. The following table may be of aid in this respect.

AMPLIFIER POWER	SPEAKERS NEEDED FOR INDOOR INSTALLATION	SPEAKERS NEEDED FOR OUTDOOR INSTALLATION
6 to 8 W	Two 8-in. speakers	One 12-in. speaker
15 to 18 W	Two 12-in. speakers	One trumpet
25 to 30 W	Four 12-in. speakers	Two trumpets
45 to 50 W	Six 12-in. speakers	Three trumpets
60 to 70 W	Eight 12-in. speakers	Four trumpets

There are several types of speakers available, and the choice of speakers depends upon five main factors:

1. Geometry and acoustical characteristics of the area to be covered.
2. Ambient sound level in which the speakers must operate.
3. Fundamental use of the system (i.e. — speech or music reproduction.)
4. Fidelity and intelligibility requirements.
5. Economic factors.

SPEAKER PLACEMENT

The most complex step in speaker installation is their placement and hookup. Conditions under which each system must operate vary so widely with each installation, that only the primary steps are given when considering speaker placement. For indoor systems, two kinds of placements can be used. The speakers may be positioned flat against the

considerations are direction of sound and the area to be covered. Here brute-force is generally used by employing highly-directive trumpets. Bear in mind that subjective loudness drops approximately 45% to 55% below the previous level each time the distance from the speaker is doubled. Also, directivity (amount of power concentrated along the speaker axis) increases with the size of the speaker horn.

SPEAKER CONNECTIONS

When connecting the speakers together, impedance matching and phase relation must be considered.

Efficient transfer of power from the amplifier to the speakers is the prime consideration in a sound system. The two methods of transfer of power are connection from the amplifier directly to the speaker voice coils, and connection from the amplifier to the speaker voice coils through a transformer. The first method is used when short runs of wire not over 200 feet in length and simple speaker arrangements involving low impedances are used.

The second method is used when the wire runs are over 200 feet, when there are complex speaker arrangements, and when it is desired to have less than 15% power loss in the transmission lines. The use of transformers also simplifies impedance

walls, and the axis of the speakers rotated so that they radiate energy at an angle from the wall. The speakers may also be positioned in the corners of a room. Variations from these two arrangements must be considered where there are alcoves, balconies, booths, dividing walls, and side rooms. In such cases, extra speakers must be set up to prevent dead spots resulting from unusual reverberations or blanking by obstacles.

For outdoor systems, the main

calculations and facilitates changes in complex speaker arrangements.

IMPEDANCE MATCHING WITHOUT TRANSFORMERS

For the most efficient transfer of power, it is important that the total speaker impedances match the output impedance of the amplifier. Single speakers should be matched as shown in Fig. 1.

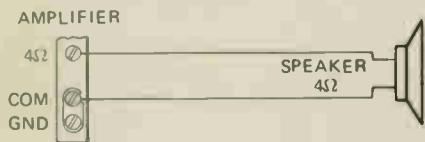


FIG. 1—SINGLE PA SPEAKER is connected like this. Just match the two impedances.

When there is more than one speaker in a sound system, calculations of total speaker impedance are based upon two formulas:

(a) For series connection of speakers, add the individual speaker impedances together to obtain the total matching impedance (see Fig. 2).

$$Z_T = Z_1 + Z_2 + \dots + Z_n$$

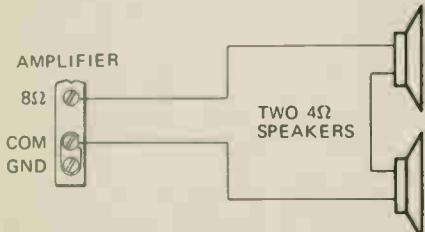


FIG. 2—SERIES SPEAKERS are selected so the sum of Impedances matches amplifier.

(b) For parallel connection, add the reciprocal of the individual speaker impedances together to obtain the reciprocal of the total matching impedance (see Fig. 3).

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$

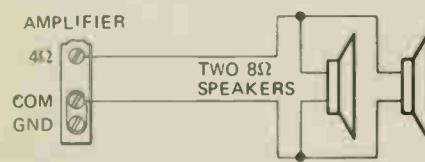


FIG. 3—PARALLEL SPEAKER connections tend to cause excessive line losses.

It is generally not advisable to use more than two speakers in parallel. Operation with less than 4 ohms impedance will result in excessive line losses.

(c) For series/parallel connections, combine the two formulae as the speaker connections indicate. For example, in Fig. 4, apply the series formula for A and B, then for C and

D. Take the results of this and apply the parallel formula to obtain the final matching impedance:

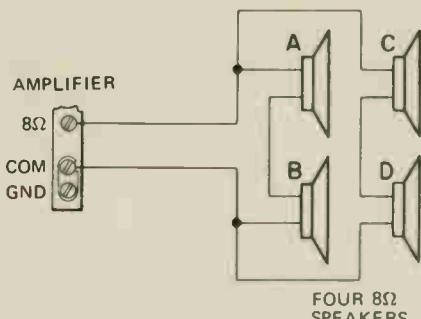


FIG. 4—SERIES-PARALLEL connections may be used to gain desired power distribution.

$$A + B = X \quad (1)$$

$$C + D = Y \quad (2)$$

$$\frac{1}{Z_T} = \frac{1}{X} + \frac{1}{Y} \quad (3)$$

$$Z_T = \frac{XY}{X+Y} \quad (4)$$

POWER DISTRIBUTION WITH TRANSFORMERS

In a series system of speakers, all with the same voice coil impedances, equal power distribution will occur. However, if one speaker has 4 ohms impedance and another 8 ohms, the power consumed by the 4 ohm speaker will be twice that of the 8 ohm speaker.

In parallel systems of speakers, all with the same voice coil impedances, equal power consumption will result. When speakers of different impedances are connected in parallel, the smaller impedance speaker will receive the greater power. If one speaker is 8 ohms and one is 16 ohms, the 8-ohm speaker will consume twice as much power as the 16-ohm speaker.

When operating speakers on voice coil impedance (without transformer), use as heavy a wire as possible. Speaker cable runs of 100 feet or over should be at least 16 s.w.g. wire. Runs from 50-100 feet should be 18 s.w.g. wire or larger.

IMPEDANCE MATCHING WITH TRANSFORMERS

The proper use of transformers with speakers far from the amplifier prevents comparatively large power losses in the transmission lines. In complex installations having large numbers of speakers, the use of transformers simplifies power distribution.

Constant-voltage transformers are most commonly used for this purpose, though impedance-matching transformers may be used in some sound installations. The constant-voltage transformer has its secondary tapped for different values

of power (watts) for the speaker. The primary matches the constant voltage line, which is either 25 volts or 70 volts.

CONSTANT VOLTAGE SYSTEM

The constant-voltage system was developed particularly for use in large multi-speaker installations, but that does not prevent smaller installations from enjoying its advantages.

The constant-voltage method greatly reduces the amount of computation necessary to determine the proper transformer taps when varying sound levels are required. It also permits the addition to, or changing of, an existing system without recalculation of the total impedances and the power required.

A favourable load condition exists if the total power consumed by the loudspeakers is always less than or equal to the amplifier rating.

When the constant voltage transformer taps are marked in watts:

1. Choose the transformer with a matching secondary (8-ohm secondary for an 8-ohm speaker).

2. Select the power tap desired, and connect to speaker.

3. Connect the constant-voltage line to the primary.

If the transformer is marked in impedances, the required power can be determined by applying the formula:

$$Z = E^2 / P$$

Where Z = Required transformer impedance in ohms, E = Amplifier output voltage (25 or 70 volts) and P = desired power at the speaker in watts.

MISMATCHING SPEAKER TO AMPLIFIER

Mismatching upward (connecting an 8-ohm speaker to the 4-ohm output of an amplifier) will decrease the power delivered to the speaker. Power loss will be about proportional to the upward impedance mismatch (50% when connecting an 8-ohm speaker to a 4-ohm amplifier tap). Mismatching cannot ordinarily damage a well-designed amplifier.

As a general rule, no serious frequency response deficiency will be noted if upward mismatches up to about five-to-one ratio are used.

Downward mismatching (connecting a 4-ohm speaker to an 8-ohm amplifier tap) should be avoided. It will reduce the amplifier power output and overload the output tubes or transistors, seriously affecting their life and performance.

PHASING SPEAKERS

When more than one speaker is used in a sound system installation, it is advisable to phase the speakers to reduce the cancellation effect. Speakers out of phase lose up to

SETTING UP P.A. SPEAKER SYSTEMS

one-half of their normal volume and operate with degraded tone quality and increased distortion.

For speakers facing in the same general direction, the speakers are in phase when their respective diaphragms move outward and inward at the same time. With two speakers facing each other, proper phasing is achieved when the diaphragm of one speaker moves outward as the diaphragm of the other speaker moves inward.

Phasing is done by checking the polarity of the speaker terminals with respect to the movement of the speaker diaphragm, and connecting the speakers to produce the diaphragm movement or phasing desired. With loudspeakers of the same make and model, the respective diaphragms should move in the same direction when the terminals are connected in the same manner, but it is safer to check the polarity.

Where different speakers are used, carry out the following procedure to determine the diaphragm movement with respect to the speaker terminals for speakers connected in parallel:

1. Connect one lead from a 1.5-volt dry-cell to one voice coil terminal of the speaker.

2. Momentarily touch the other lead from the dry cell to the other speaker terminal.

3. Observe direction of cone or diaphragm movement (either inward or outward) when the circuit is closed.

4. Note this direction of the movement on a slip of paper.

5. Mark the terminal connected to the positive pole of the dry cell if the movement is outward, mark the terminal connected to the negative pole if the movement is inward.

6. Repeat steps 1 through 5 for other speaker or speakers to be checked.

7. Connect the marked and unmarked terminals according to the manner of electrical arrangement shown in Fig. 5 if the speakers are facing in the same direction. If the speakers face each other, make connections as shown in Fig. 6.

In simple sound systems, it may be easier to check phasing by listening to a low audio frequency while alternating the speaker leads. The human ear can usually detect when the low frequency sound is at the higher volume, indicating that the speakers are properly phased.

BALANCED LINE CONNECTIONS

In most sound installations, unbalanced speaker lines will provide satisfactory performance. A typical

unbalanced line installation for a 25-volt system is shown in Fig. 7. Two-conductor unshielded cable is normally employed in such installations. One conductor is connected to the 25-volt terminal on the amplifier output strip. The other wire goes to the common terminal, which is then connected to ground.

However, in more elaborate systems where input lines are run in close proximity to the speaker lines for extended distances, currents in the speaker lines may be picked up by the

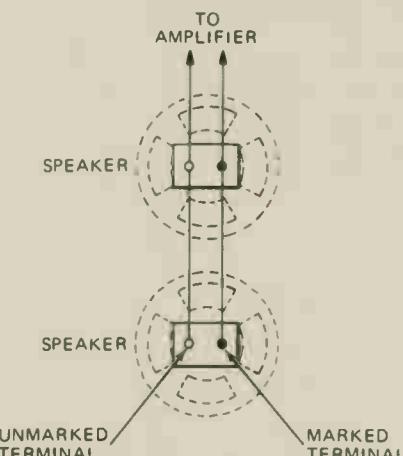


FIG. 5—PA SPEAKERS facing same way are phased with like terminals wired together.

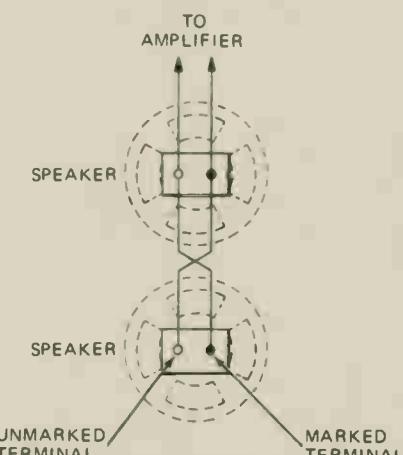


FIG. 6—SPEAKERS FACING EACH OTHER have line transposed for In-phase operation.

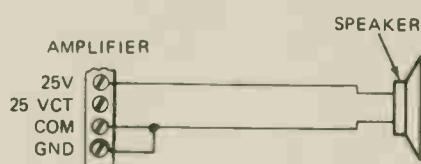


FIG. 7—A 25-VOLT UNBALANCED line is typical. Balanced lines are for special cases.

input lines. When these stray currents are fed back to the amplifier, hum and crosstalk will be introduced into the system, or the amplifier may oscillate.

For this reason, balanced line connections are recommended for installations in which long input and speaker lines are run close together. A balanced line is obtained by

under-grounding the common terminal, leaving the outputs floating. In a balanced line, any current which is developed in one side of the line is offset by an equal and opposite current in the other side. This greatly reduces the possibility of inducing stray currents in nearby input lines.

In some balanced line installations, it may also be necessary to connect the appropriate centre-tap terminal to ground, and to ground the amplifier chassis.

If hum or other pickup is encountered with a balanced line as described above, it may be necessary to run a shielded two-conductor cable to the speakers and to ground the shielded two-conductor cable to the speakers and to ground the shield at the amplifier end.

SOUND COLUMN SPEAKERS

Sound columns are designed for sound reinforcement in theatres, auditoriums and arenas where it is necessary to cover a large area with a minimum number of speakers. A sound column consists of six or more cone loudspeakers enclosed in a rectangular cabinet lined with acoustic material. Depending on the size and type of cone speakers employed, the output rating of a sound column may range from 25 to 200 watts. The terminal strip and sometimes a plate for mounting a line-matching transformer are located on the rear panel.

The arrangement of the speakers in the column is such that their acoustic output adds up in the forward direction, so that the effective throw of the sound column far exceeds that of the individual cone speakers. The effective throw or maximum distance at which sound from the column is distinctly audible is usually between 100 and 200 feet.

Because of its configuration, the sound column produces a highly directional beam pattern, which permits the sound to be aimed over a well-defined area of the installation site. Since about 90% of the acoustic output of the column is confined to this pattern, there is virtually no random sound available to cause reverberation or reflection. Consequently, a sound column can be properly directed to cover a hall or section of a hall most effectively and to keep harmful reflections away from the floor and ceiling.

In addition, the geometrical configuration of the speakers in the column produces a sound dispersion pattern which is quite broad in the horizontal plane but much narrower in the vertical plane. In a typical sound column, the horizontal dispersion pattern is 120°, which is a great deal more than that of the individual

BUILD THE

TREASURE TRACER MK III



METAL LOCATOR

- Incorporates varicap tuning for extra stability
- Weighs only 22oz and has perfect balance
- Loudspeaker or earphone operation (both included)
- Handle knocks down to only 16in for transport
- Ministry approved design
- Excellent sensitivity and stability
- Kit can be built using only soldering iron, screwdriver, pliers and wire snips
- Drilled, tinned, fibreglass p.c. board with component siting printed on
- Incorporates Faraday screen

Send for s.a.e. for leaflet

Complete kit with pre-built search coil £9.80
Plus 35p Post (inc. VAT)

Built, tested and Guaranteed £13.75
Plus 35p Post (inc. VAT)

MINIKITS ELECTRONICS,
35d Langley Drive, Wanstead,
LONDON E11 2LN
(Mail order only)

SETTING UP P.A. SPEAKER SYSTEMS

speakers. However, the cumulative effect of the in-line speakers produces a vertical dispersion pattern of approximately 25° as shown in Fig. 8.

PLACING SOUND COLUMNS

A typical sound column installation is shown in Fig. 9. The sound column is placed in the general vicinity of the original sound source (singer, speaker), as close as practicable to the source. Having the loudspeaker sound originate near the original source provides a more natural effect for the audience, and avoids confusing the performer.

The column is placed so that the microphone is below and slightly behind the sound column, to minimize feedback. The sound column is oriented so that its vertical distribution will deliver nearly equal minimized feedback. The sound column is oriented so that its vertical distribution will deliver nearly equal loudness to all listeners, from front to back, except those who are within the effective range of the speaker's voice.

A sound column can be aimed quite accurately at this point by the light reflection method. Attach a small mirror to the face of the column centre. Standing at the aiming point with a light directed at the sound column, have the column adjusted for maximum light reflection from the mirror.

CONNECTING SOUND COLUMNS

One or more sound columns may be connected to an amplifier in a sound system. The columns are normally

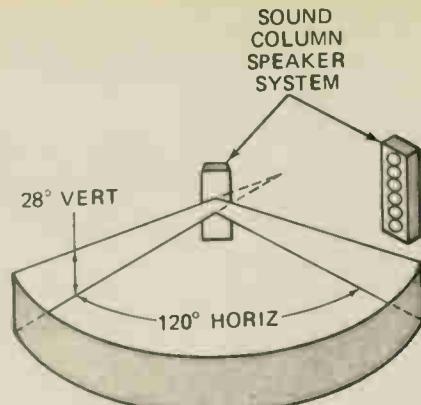


FIG. 8—RADIATION PATTERN from a vertically oriented sound column is horizontal.

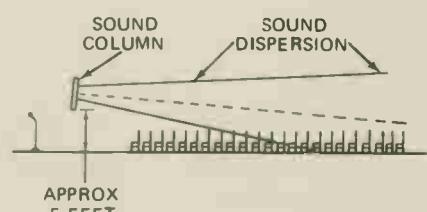


FIG. 9—HOW SOUND COLUMN IS PLACED for most effective coverage of an audience.

connected in parallel as shown in Fig. 10.

Sound columns normally have an impedance rating of 16 ohms. If only one sound column is used, connect the amplifier leads to the 16-ohm output terminal. For two sound columns in parallel, connect the leads to the 8-ohm terminal.

There you have it, a quick guide to PA speaker installation — use it to simplify your next PA job.

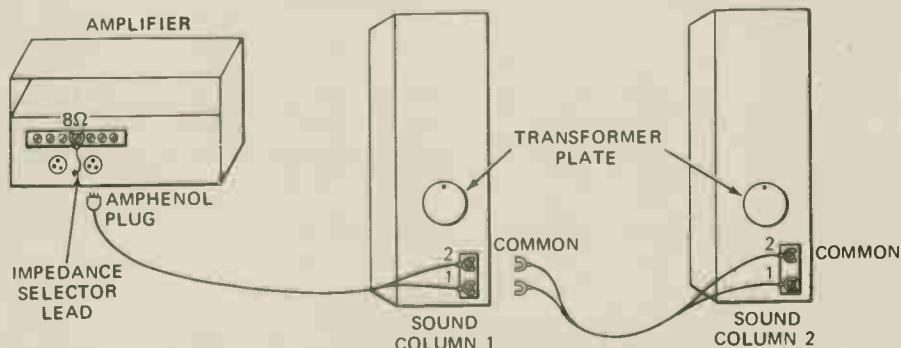


FIG. 10—ONE WAY to connect sound columns to PA amplifier system. Here two 16-ohm columns are in parallel across the amplifier output adjusted for an 8-ohm load impedance.

"Reprinted from May 1973 Radio Electronics, copyright Gernsback Publications 1973"

ELECTRONIC TENNIS

I was recently invited to play "tennis" in a West End pub by some friends of mine who had discovered an electronic game there. The game looked like a big, old fashioned, TV set. On the screen a white dot bounced diagonally up and down, backwards and forwards. Beneath the screen there were two knobs—one for each player.

The game was quickly explained to me—the rules were like those of tennis, but the "ball" (represented by the moving dot) was allowed to bounce off the "side walls" (the top and bottom of the screen as the players see it). A dotted line indicated the position of the "net".

On insertion of a coin, two "men" (represented by vertical 15mm lines) appeared on the screen. By use of the control a player can move his "man" across the court (seen by the viewer as a vertical movement).

A skillful player will move his "man" into the path of the "ball", which will bounce the ball back to his opponent. If a player fails to return the ball, his opponent scores a point and this is registered on the score display projected onto the screen.

Variation is introduced when the "ball" doesn't bounce cleanly off the "man". Sometimes it will reverse along its incident path, sometimes bounce back at a different angle. Clever features of the game include the "serve" facility—where the "ball" appears to come out of the "net" on service, cutting down the time available to prepare the return shot—and the realistic "ping" sound which accompanies the successful return.

I was absolutely fascinated by the game and soon got the hang of the play (although I seemed to deteriorate after I had won my first pint!) Trying to work out the electronics has kept me occupied for days—it must be something simple.

It is good to see electronics coming into the amusements field and I hope to see more such games around (I have quite a few ideas myself).

—R.P. London, W.1.

We managed to contact the owners of this particular game and they say

it is the only one of its kind in the country. It was brought over specially from the United States where games like this have been in use since the late 60's.

Production is soon to start in England too, but only on this one model. In the US there are already 5-a-side football games, squash and doubles games, based on the TV screen idea. The electronics are pretty intricate and a special I.C. board, with over fifty circuits, will be imported from the States for use in the British model. The rest of the circuitry is as in a standard TV set.

COMPONENT PROBLEMS

Through your columns I would like to draw attention to the bad service that everyone I know seems to be getting from mail-order component suppliers lately.

They seem to be getting worse and worse with part-orders being delivered more often than not. Isn't it time that these companies pulled their socks up?

I am sure many of your readers have had the same experience and I wonder if you, as a magazine, can draw attention to this situation in the hope that these companies will not like the adverse publicity.

—K.T.Eye, Suffolk.

We have had a number of comments similar to the above. If we knew of any company dragging its heels, we would be the first to criticise.

However, the current situation is almost certainly not the fault of the component suppliers as there is a serious world wide shortage of almost all electronic components. This is made worse in the U.K. because of our current boom which has added to the problems.

We are in touch with several component suppliers and to a man they are in serious trouble with obtaining supplies. Even mundane components such as resistors are becoming harder and harder to obtain. You could answer that the distributors should keep higher stocks but even those who had massive stocks have had these exhausted.

One small electronic company we know wanted several thousand each of 8 resistor values. His usual suppliers could only help him with one or two values and it took 30 'phone calls and five different suppliers to fulfil his requirements. These resistors were not unusual either, being standard $\frac{1}{4}W$ types in the E12 series.

The delivery times being quoted by the makers normally now run into six months or more. If a manufacturer can't get hold of stock, you can imagine what it is like for the retailer.

We can only suggest to readers that they show a little patience until this chronic shortage is overcome and take it easy on your retailer—his problems are much worse than yours.

BRITISH AMATEUR TREASURE HUNTING CLUB

May I offer the following background information on amateur treasure hunting which may be of interest to readers who construct the "COIN COLLECTOR" metal detector featured in your July issue.

There are 30,000 amateur treasure hunters in Britain and our activities are governed by a strict CODE OF CONDUCT which was written with the help of the Department of the Environment at a time when our hobby was under severe attack from professional archaeologists. It is absolutely essential that anyone who uses a detector should abide by this code; any reader who wishes to obtain a copy may do so by sending a stamped addressed envelope to me.

The British Amateur Treasure Hunting Club welcomes the publication of do-it-yourself metal detector circuits. The Club is currently campaigning in its magazine, "TRUE TREASURE MONTHLY", for a reduction in the retail prices of many detectors now on the market which are far too costly and which do not do what their manufacturers claim. You would do us a great service if you made do-it-yourself detector circuits a regular feature of your magazine.


Edward Fletcher, Editor, TRUE TREASURE MONTHLY, 24-9 Trellick Tower, 5 Goldborne Road, London W10.



A Executive

STOP PRESS

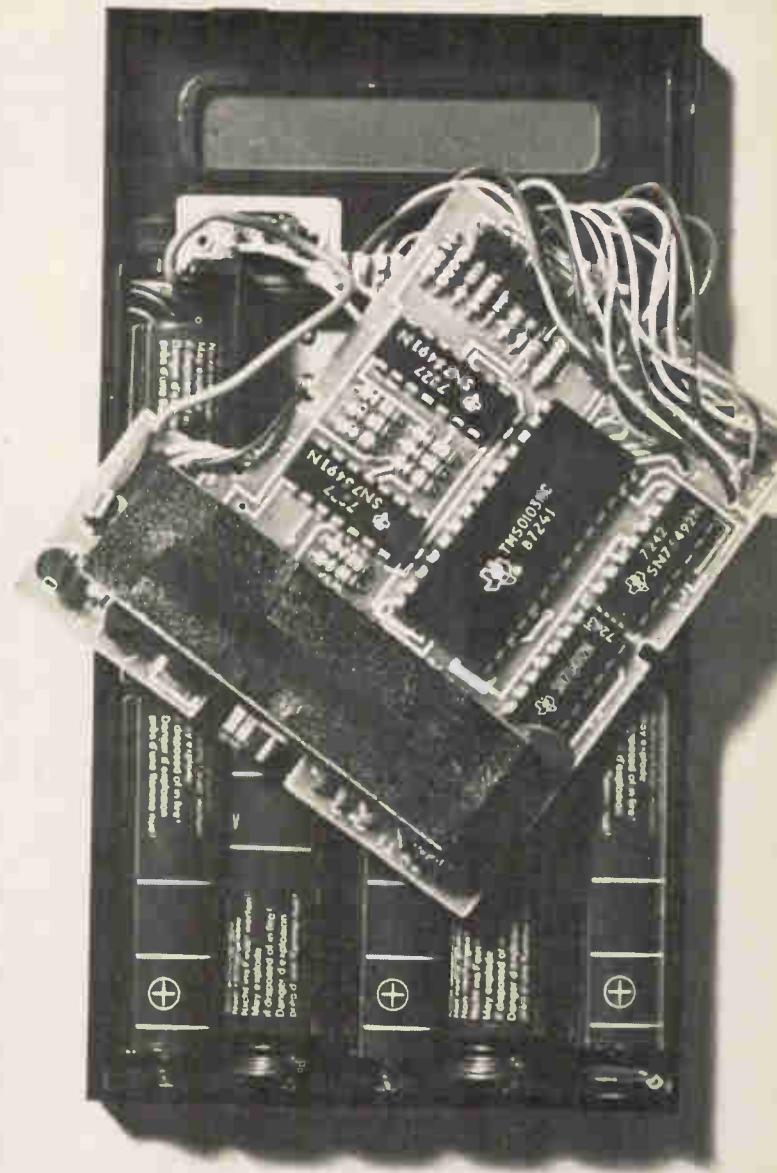Coming soon, in [REDACTED] we shall be offering a kit version of this calculator for less than £30!



Not just a pretty face.

The Advance mini Executive is a beautiful hand-held calculator.

Some, almost as good looking, are as fragile as a butterfly's wings. Ours isn't.

Some are so small you keep mis-punching and get the wrong answers. Ours isn't.

Some aren't made by specialists in electronics but merely imported from goodness knows where. Ours is made right here in Britain by Advance Electronics Limited.

Finally, if you think it's about time you had your very own pocket calculator, ours costs only £52.50.

It's guaranteed for a year.

Has a battery life of 15 hours.

And to remind you, it's called the mini Executive. The coupon will get you literature.

Go on, spoil yourself.

Because at £52.50 (plus VAT) it's the finest pocket calculator in the world.



Name _____

Address _____

Advance Calculators,
Raynham Road, Bishops Stortford, Herts.
Telephone 0279 55155. Telex: 81510.

A close-up, high-angle photograph of a car engine's distributor and ignition coil assembly. The engine block is visible in the background, showing various mechanical components like hoses and bolts. In the foreground, a black metal box labeled "electronics TODAY INTERNATIONAL" is mounted on the engine. A red plastic connector is attached to the side of the box. A yellow wire is connected to the connector, which then splits into two wires: one goes to the distributor cap, and the other goes to the coil. The coil itself is a large, cylindrical component with a red and silver finish.

electronics
TODAY
INTERNATIONAL

THE GO Electronic Transistorized Ignition

By Caleb Bradley, B.Sc.

TRANSISTOR IGNITION will be standard equipment on tomorrow's cars but today you can easily fit the ETI Electronic Transistor Ignition to your present car, old or new. It will give the proved advantages of smoother engine running, greatly extended life from spark plugs and contact breaker, freedom from plug fouling, plus worthwhile improvements in miles-per-gallon, performance and pollution . . . all this plus a burglar foiling facility!

STANDARD IGNITION

The simple ignition circuit which is still used in virtually all mass-produced cars is shown in Fig. 1. Incredibly it was designed 60 years ago by Charles Kettering as an improvement on early magneto ignition. The way it works and the reasons why it is no longer adequate for today's highly developed petrol engine are as follows.

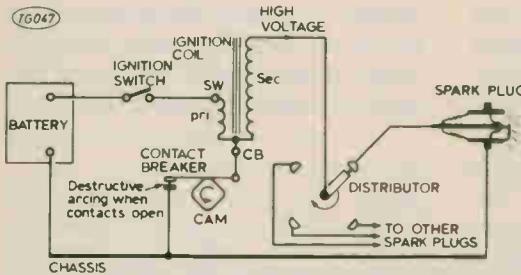


Fig. 1 (Above) The standard (Kettering) ignition circuit as fitted to virtually all mass produced cars for 60 years.

Fig. 2 (Right) After the contact breaker closes, current in the coil primary builds up at an exponential rate. Dotted lines show the times when the contact breaker opens for different sizes of engine at high speed. This graph assumes the contact breaker is in good condition and is driven with 50/50 mark/space ratio.

The contact breaker (or 'points') in Fig. 1 is driven by a cam to break the current in the ignition coil primary every time a spark is required to ignite the petrol vapour in a cylinder. Consider when the contact breaker has just closed. The battery is then connected across the primary, via the ignition switch and, since the primary has inductance, the current increases at a slow exponential rate as shown in Fig. 2. With typical primary inductance and resistance values of 10 millihenries and 3 ohms the circuit's time constant (the time for the current to reach 63% of its final value) is about 3.3 millisecond, though there is considerable variation between coils. If the engine is not running (so the cam is not turning) the primary current will settle at its maximum value of 4A or more which is set only by the battery voltage and


the primary resistance. This high current tends to overheat the coil and run down the battery if a car's ignition switch is left on with the engine stationary.

Primary current causes magnetic flux in the coil, representing stored energy of value $\frac{1}{2}LI^2$ joules. When a spark is required, the contact breaker opens and the primary current is broken. As the previously created flux collapses it induces voltages in the coil windings, proportional to their numbers of turns. The peak voltage induced in the primary is about 300V but, since the secondary has about a hundred times as many turns, the secondary voltage is about 30,000V. This is sufficient to ionise the air gaps in the distributor (between the rotor arm tip and whichever terminal connected to a spark plug is nearest) and at the selected spark plug, so a spark occurs. Actually the spark plug is not firing in air but in a gas com-

miles driving the first signs of pitting become visible — see the photograph. Pitting creates sharp edges on the contact faces which worsen arcing; the available spark voltage is reduced since arcing limits the voltage achieved in the primary. Also pitted contacts have significant resistance when closed so that optimum current (energy) is no longer built up in the primary. Eventually the loss of engine performance becomes so serious that the contacts have to be replaced.

THE 'CONDENSER'

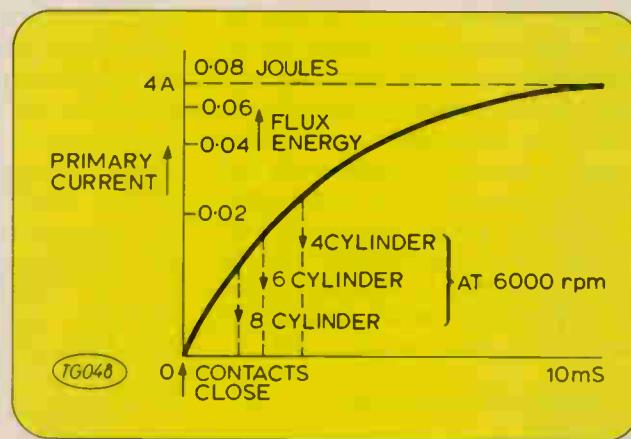This is a small capacitor which is connected across the contact breaker to reduce pitting and improve the spark slightly. When the contacts open, this capacitor is in effect connected across the coil primary and slows down the voltage transient so the contacts have a better chance of breaking the primary current cleanly. It is only a partial improvement, sufficient to make



pressed to 200 lbs per square inch or more which requires a higher voltage to ionise it.

The weak link in the Kettering circuit is the contact breaker. This is a simple mechanical device which must be driven relatively slowly compared with rise of voltage in the primary; this is dictated by practical factors such as the return spring strength, the weight of the moving contact and the allowable force on the distributor cam. The unavoidable result is that the primary voltage transient rises faster than the breakdown potential of the newly opening air gap in the contact breaker and therefore arcing occurs in the early stages of contact breaking. Besides wasting some of the energy stored in the coil, this arcing detaches metal from one contact face and deposits it on the other and after only a few

the Kettering circuit barely useable, and the capacitor must not be too large or the spark voltage will suffer.

DESIGN LIMITATIONS

Two situations stretch conventional ignition to its limit. These are:

- Starting on a wintry morning when the starter motor loading reduces the battery voltage and hence the primary flux so only a feeble spark is available to ignite a cold mixture, and
- High speed running when the time between sparks does not allow adequate flux to build up.

Most drivers are well aware of shortcoming a) but it is not well known that most cars with conventional ignition suffer from misfiring at high speeds, though there is a definite loss in m.p.g. and smoothness. The reason for spark deterioration at high speeds

Electronic Transistorised Ignition

A surprising feature of the inverter circuit is that it continues to function weakly if one of the transistors is removed or goes open circuit. This might suffice to get you home at 30 m.p.h.!

In most previously published designs the inverter is allowed to 'see' a short circuit (via the bridge rectifier), for example at switch-on when C1 is not charged, and every time the S.C.R. fires. Although this does no damage it causes the inverter to run briefly in a high-frequency low-efficiency mode since the only inductance loading the transistors is the leakage inductance of the transformer. An alternative is to design the inverter to stop oscillating when shorted but this presents starting delay problems. For this design it was thought preferable to keep the inverter running continuously in the proper audio-frequency high-efficiency mode. A simple way of achieving this is by having a resistor in series with the secondary winding. The inverter now continues to run audibly even if the bridge output is shorted. If a milliammeter is used to do this a short-circuit current of 30 - 40mA can be measured indicating the circuit has excellent 'pick up' after each spark. Note that T1 and the secondary resistor normally run warm but get quite hot if the bridge output is shorted continuously. No difficulty has been found in relying on the backswing from the ignition coil to turn off the S.C.R. specified in this circuit, in spite of the high charge current.

OVERSHOTS

The inverter provides adequate output voltage to start the engine at reduced battery voltage of 8V or less yet will not exceed 400V with a fresh battery, so no attempt has been made to use the inverter waveform overshoots for output regulation. As can be seen on the waveforms in Fig. 7 the overshoots are small, partly because the primary of T1 is bifilar wound for low leakage inductance and partly because most of the overshoot power is taken by the neon indicator.

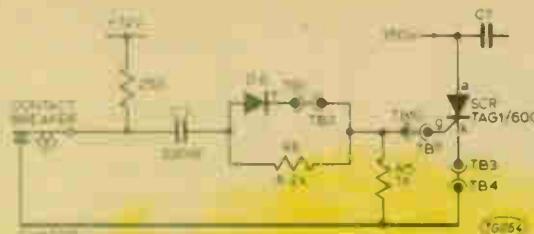


Fig. 8. Trigger circuit for negative chassis vehicles.

NEON LAMP

A neon lamp with series resistor is connected across C1 so that illumination indicates that the inverter is working. C1 is a highly stressed component; it is not short circuit and that the ignition coil primary connections are intact. To avoid taking excessive power from the circuit the neon is not driven very brightly but should be clearly visible in the shade of the engine compartment.

S.C.R. TRIGGERING

The S.C.R. must be triggered by means of a positive pulse at its gate relative to its cathode every time a spark is required. i.e. every time the contact breaker opens. Different means of triggering are used for negative- and positive-chassis vehicles as shown in Fig. 8 and Fig. 9. Viewing Fig. 8, 0.5A is passed through the contact breaker when closed by the 25 ohm resistor. The purpose of this current is to keep the contacts clean by burning off any minute deposits; contact breakers switching smaller currents can be very troublesome due to a fine film of oil and dirt building up on the contact faces. Since the contact breaker has approximately 50/50 open-shut period, the mean current drain of this arrangement is negligible at 250mA.

When the contact breaker opens, the 25 ohm resistor pulls one side of C3 from OV to 12V. D6 conducts and a positive pulse, differentiated by C3 and R6, is fed to the S.C.R. gate causing it to fire and discharge the 350V on C1. It is not possible

for another trigger pulse to be produced until C1 discharges. D6 blocks the discharge current which cannot flow until the contact breaker closes and must then flow through the comparatively high value resistor R6 and R5. Thus a new trigger pulse cannot be produced until the contact breaker has been closed long enough to discharge C3. This arrangement effectively makes the system immune to false triggering caused by contact breaker bounce. The component values are chosen to suit the trigger characteristics of the S.C.R. specified and may not suit other types.

The trigger circuit for positive chassis in Fig. 9 works similarly with the difference that the trigger is a negative pulse which is passed by D5 to the S.C.R. cathode. Since the gate is connected to chassis this gives the correct trigger conditions. When the S.C.R. fires the discharge current flows through D7.

FULL CIRCUIT

The full circuit is shown in Fig. 10 and has the features of easy switch-over from transistor to conventional ignition by means of toggle switches S1, S2, and convertibility for positive or negative chassis by mounting a link strip in alternate positions on a miniature terminal block. The main elements of the circuit have been described; the connections to the terminal block are rather complex but can be understood by reference to Figs. 8 and 9. When S1 and S2 are both switched to conventional the transistor circuit is isolated (though

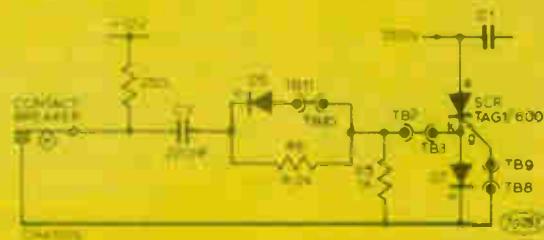


Fig. 9. Trigger circuit for positive chassis vehicles.

the inverter still receives power) and the normal connections for Kettering ignition are remade i.e. coil primary connected to ignition switch and contact breaker. This switchover facility can be used while the engine is running for comparison purposes.

COMPONENTS AND CONSTRUCTION

For obvious reasons the unit must be dependable while driving. To this end all the components specified are of high quality and in many cases of higher than necessary ratings. Construction must be equally sound. Component substitutions are not recommended e.g. slide switches should *not* be used in place of the toggle switches because of the inductive circuit switched, nor is it a good idea to remote these switches to the dashboard.

The components are mounted on the lid of a standard Norman AB10 aluminium box for easy access. The layout is shown in Fig. 11 and in the photograph. Drilling details are given for the box in Fig. 13 together with

PARTS LIST


R1	Resistor	220ohm 5W wirewound
R2	"	220ohm "
R3	"	7.5k "
R4	"	25-39ohm 10W "
R5	"	1k 1/2W 5%
R6	"	8.2k "
R7	"	330k "
C1	Capacitor	0.47uF or 0.5uF 440V a.c. tubular (MFD type TSAC)
C2	"	3500uF 25V electrolytic
C3	"	220nF (0.22uF)
D1-D4	Diodes	1N4006 or 1N4007
D5-D9	"	1N4001 (or -2, -3 etc.)
SCR	Thyristor	TAG 1/600
Q1-Q2	Transistor	NPN silicon plastic power type with min Vce of 50V and min gain at 500mA of 40.
T1	Inverter Transformer (Bi-Pre-Pak)	
S1, S2	Switches	Heavy duty DPDT toggle switches
PS		5A 1 1/2in fuse with holder
TB		11 way miniature terminal block with screws and solder tags (Carr)

Miscellaneous

Norman AB10 chassis with lid; Heatsink; Neon bulb; 2 x 10 way tag strips; Transistor mounting hardware; Grommets; Coloured wire; Nuts and bolts etc.

A complete kit including predrilled chassis is available to readers at the special price of £5.92. A built, tested and guaranteed unit is also available at reduced cost. These offers are limited to ETI readers using the coupons on page 77. Offer ends September 30th 1973.

VEHICLE CONNECTIONS

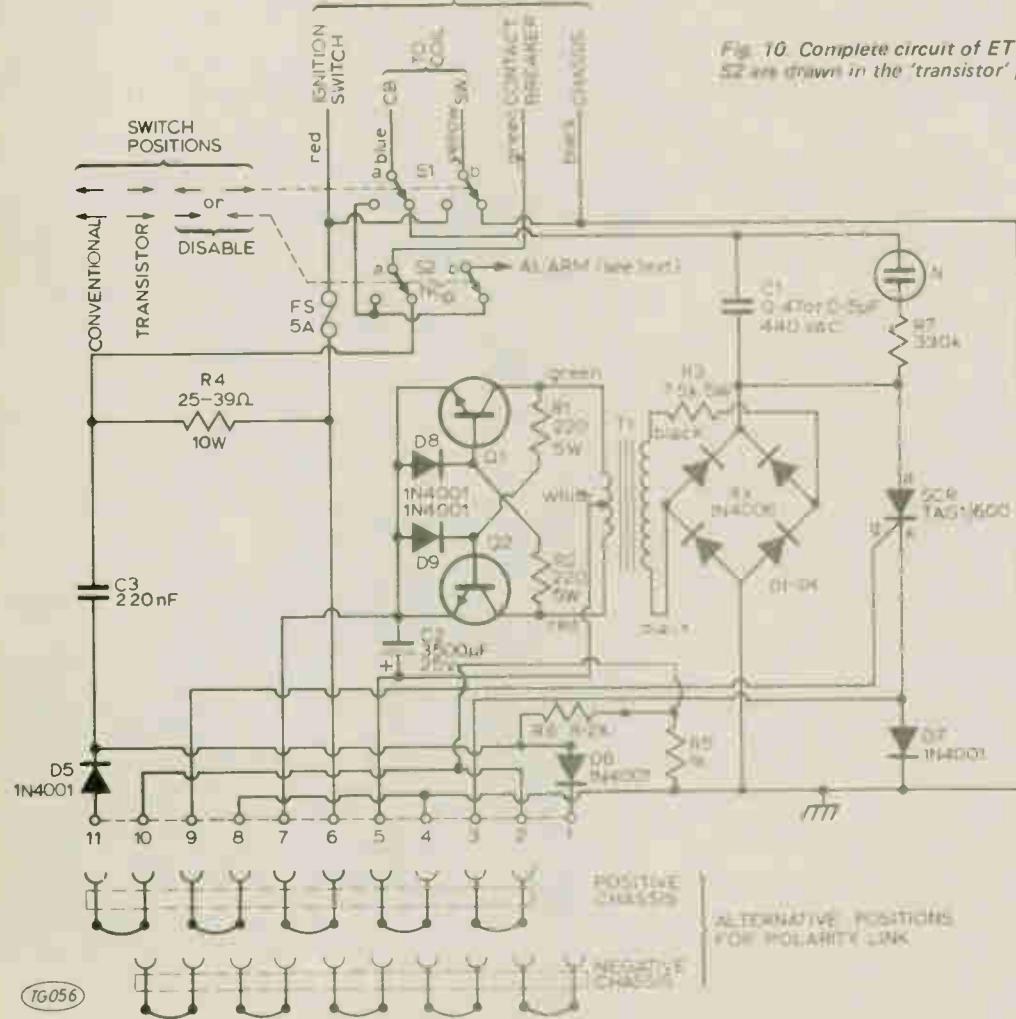

LEAD IDENTIFICATION



Electronic Transistorised Ignition

an aluminium heatsink for the transistors and inverter transformer but the kit is supplied with a predrilled chassis and will not in this case be necessary.

It is convenient to mount as many components as possible on the tagstrips before mounting the tagstrips in the box. Pass the tagstrip mounting bolts through both the lid and the heatsink. Then mount the plastic power transistors using the mica washers and insulating bushes supplied to isolate the metal part of the transistor (collector) from the box — see Fig. 12. The transistor mounting bolts are live to the collectors.

Mount the toggle switches, transformer, fuseholder and terminal block. The wiring can now be completed. Take special care to make robust connections to the transistor leads, using sleeving to prevent shorts. Wrap component wires round tags before soldering to give strength to the joint. Be careful with connections to the small tags on the terminal block, this is mounted with pin 1 on the right when viewing the unit from the out-



An excellent example of pitting on a contact breaker. Due to the very much lower current switched for an electronic ignition system such problems are eliminated.

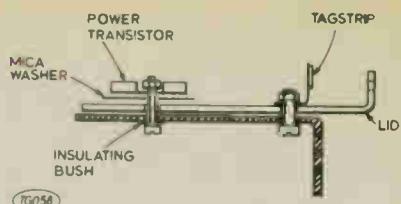


Fig. 12. Method of mounting power transistors. The shaded part is the heatsink.

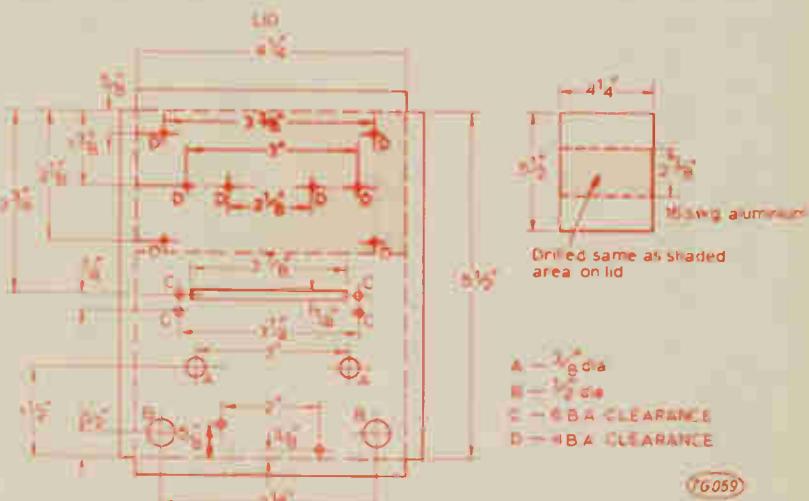


Fig. 13. The chassis drilling details. The three-eighth inch holes may have to be larger with some toggle switches.

Continued on Page 76


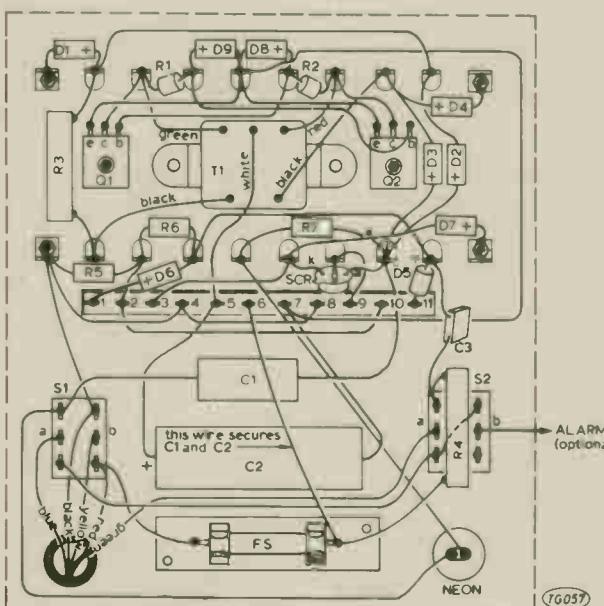



Fig. 11. ETI Transistor Ignition Component layout. (Prototype has Q1, Q2 in slightly different positions, also has an unused position 12 on the tag block).

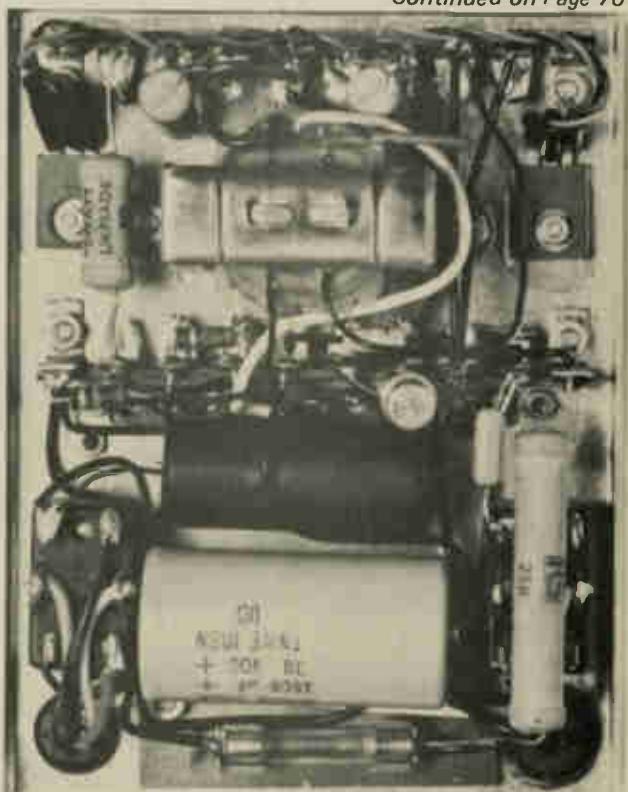

An internal view of the unit. This is one of several prototypes and uses the components supplied in the special kit.

et*i*

WHAT TO LOOK FOR IN OCTOBER...

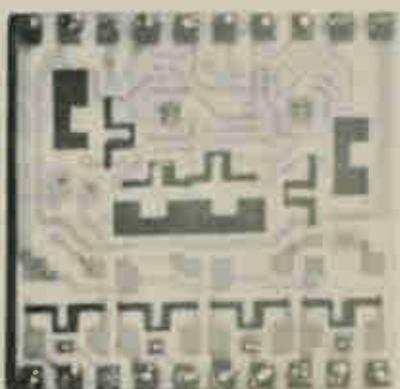

et*i* AUDIO WATTMETER

Our direct reading Audio Wattmeter gives instant power readings in r.m.s. watts and level differences in decibels. It operates at any frequency within the audio range and is specifically designed for Hi-Fi amplifiers with output impedances of 4, 8 or 15 ohms. Three ranges are provided—up to 500mW, to 5W and to 50W.

Next month full details of circuit boards, calibration and metal work will be provided for this project, enabling you to make yourself an instrument invaluable in the checking of amplifier performance.



MAGNETIC LEVITATION

Repulsive or attractive? This is just one of the debates going on amongst researchers into magnetic levitation/suspension. The latest interest of researchers is in using principles of magnetism in the support of high speed trains. A recent contender in the field of train levitation is the principle used by Bachelet in 1912 but discarded as impractical. This utilises eddy currents, induced in a thick aluminium plate by a fluctuating magnetic field, to provide the repulsive force to lift the vehicle. Recent developments in cryogenics and superconductivity now make this form of transport a practical possibility.

ON SALE MID-SEPTEMBER—20p

ETI TAKES A PRIDE IN BEING REALLY UP-TO-DATE, SO WE OURSELVES DO NOT ALWAYS KNOW WHAT WILL BE IN THE NEXT ISSUE SO THE FEATURES MENTIONED ON THIS PAGE ARE ONLY SOME OF THOSE THAT WILL BE INCLUDED.

electronics
today INTERNATIONAL

THE SOLAR SOLUTION

IS IT THE ANSWER TO THE ENERGY CRI

"... We are facing a vitally important energy challenge. If recent trends continue unchecked, we could face a genuine energy crisis. But that crisis can and should be averted, for we have the capacity and resources to meet our energy needs if only we take the proper steps and take them now."

President Nixon, 18th April, 1973.

SIX MONTHS AGO, if someone had used the term 'Energy Crisis', the chances are that it would have required a lengthy explanation. Today it is such a common talking point that it is running the danger of being overstated. What are the facts?

In the United States, which consumes a third of the world's energy, a number of independent filling stations have had their supplies stopped by the oil giants because they no longer have a surplus. That is all that has happened; why then are we getting concerned? The answer is that although this is only a beginning it has focused attention on a potentially very serious situation. Every TV station, every newspaper, every centre of higher learning has taken out the crystal ball and is gazing into the future... most of the time the forecasts are gloomy.

We, *Homo sapiens*, have increased our standard of living so enormously in the last 100 years that we are beginning to effect our environment; in addition to increasing our standard of living we are also multiplying our numbers very rapidly, adding to the problems.

In the developed countries we are surrounded by machines: motor cars, combine harvesters, air conditioners,

central heating plants and so on. The definition of man used to be the *tool-maker* (though this is now falling from favour) and as we have progressed we have harnessed a variety of energy forms to operate these tools to make our lives more comfortable.

For thousands of years we harnessed the energy of the ox and later the horse. Then we harnessed the wind for sailing ships and windmills, then the waterwheel.


The industrial revolution required large resources of energy and coal was the answer. It is no coincidence that the industrial revolution started in Britain, on an island that has been called a 'floating coal mine'.

As we progressed we found that oil was more convenient, especially for transport, and if we call the last century the 'age of coal' we must refer to the last 30 years as the 'age of oil'.

Oil is a marvellous resource. It is cheap (at the moment), easily transported and stored, it is stable and, until now, has been abundant. We have continued to use a large variety of other energy forms but oil is dominant. The trouble is that oil is a limited resource and is being used up at a staggering rate.

Production of oil in the United

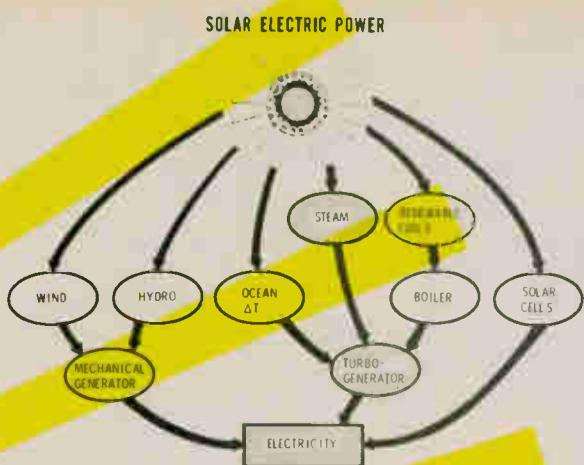*Methods of harnessing the sun's power.
This diagram illustrates that there are
a variety of approaches that can be
taken.*



RISI

SPECIAL REPORT BY
HALVOR MOORSHEAD

States has reached its peak and will start to decline before the decade is out. To fill the gap between supply and demand the Americans are now beginning to buy on the world market in a big way and the pressure is on.

What of the Alaskan and North Sea oil fields, surely these are going to save the day and what of the continual discoveries still being made? The predictions have taken account of future discoveries: we are without doubt now consuming oil faster than new fields are being discovered. There are still substantial reserves but our appetite is so great that nearly all the experts agree that if we continue to use oil at the same rate we will not have a drop left in twenty years time. Many of the cars being turned off the production lines today will still be around then and it will be within the lifetimes of most of us.

In fact things will not happen this way. As the reserves are exhausted, the price will soar upwards and other energy forms will be found, leaving oil for specialised uses.

One danger we run into in an article of this type is that we cannot predict the future with any certainty, for technology is moving at a remarkable rate. We could fall into the 'Malthusian Trap'* of predicting too far ahead, while assuming that conditions will not alter. However, we are looking into the foreseeable future and we can safely say that alternative energy sources must be found and found pretty quickly. The alternatives must be operative and on a vast scale within twenty years. What are the alternatives?

*Thomas Malthus (1766-1834) in his gloomy essay 'The Principle of Population' foresaw the maximum world population as a fraction of what it is now and a declining standard of living. He calculated what the population would be but did not foresee the huge improvement in agriculture or technology. He said that technology could not increase as there was not enough grazing land for the horses necessary to provide the motive power!

COAL

There is still plenty of coal, even bearing in mind our appetites. The known reserves of coal, in energy terms, are at least 15 times greater than for oil and this is despite the fact that modern technology has not been applied (to any great extent) to finding new reserves.

Coal has its disadvantages. The un-worked seams are deeper and deeper and more costly to mine; there is the problem of subsidence and there are social problems. In addition, most coal produces SO₂ when burnt and it is not easy to transport.

Even so, coal may well gain in importance and help to fill the gap before another energy source is found but, like oil, it is a diminishing, non-replaceable source and it is not the long term answer.

NATURAL GAS

Natural gas and oil are closely allied; if anything the gas will run out before the oil. Gas is very important in certain parts of the world, notably North America and Britain, where in the last few years it has become a major energy source.

Despite there being substantial remaining reserves, gas, like coal, is certainly not a long term answer.

NUCLEAR ENERGY

If we are forced to look into the future it seems likely that our needs will be met by nuclear energy, but this is some way off. The conversion of matter into energy makes a very attractive formula. A few pounds of matter, when converted into energy, is enough to satisfy a person's energy requirements for life. We are a long way from this, however, and at present we are confined to using a limited number of elements, such as uranium, for this.

THE SOLAR SOLUTION

Despite the fact that, in terms of weight, we need very small quantities of uranium, there are not vast reserves and the processing requires a substantial back-up industry.

There is also the political question: are we prepared for nuclear power stations, as used in the developed world, to be installed in less stable countries? Once you have a nuclear power station and access to uranium it is not too difficult to make your own nuclear bombs!

There are also the problems of radioactive waste which are very serious. A variety of methods are used to dispose of this but none are truly safe. These problems will no doubt be overcome but an answer has been sought for the last 20 years and still the problem remains.

Nuclear fusion uses deuterium which is abundant (enough to last us 10^9 years!) but, despite intensive research, this is more theory than practice at the moment. We know it works but we have a long way to go and this still poses the problem of waste disposal.

GEOTHERMAL

We all know that the inside of the earth is very hot. In certain parts of the globe, where ground water comes into contact with hot rock, high pressure steam is produced which can be harnessed. Italy, France, New Zealand, USA, Japan and the USSR already harness this energy but the natural occurrence of this phenomenon is rare.

It has been suggested that we could create these conditions artificially but this has yet to be tried and there are not suitable conditions in many parts of the world.

OTHER ENERGY SOURCES

We have been very ingenious at harnessing various energy sources. Hydroelectric stations are in use all over the world and produce cheap electricity but there are few remaining sites which can be used. The great dam building days of the 1930's and the 1950's are over and every available site in Western Europe and the USA has been used.

Tidal power is used in France. By damming suitable estuaries, the rise and fall of the tide can be harnessed

to drive turbines. The French scheme has had severe problems but is now operative. But once again the potential and the number of sites make this a curiosity rather than an answer.

For centuries the wind was the sole motive power for ships and the major energy source for grinding corn; even today in remote locations it is used to generate electricity. However, the capital investment and inconsistency of wind does not make it anything more than a curiosity.

The temperature gradients in the ocean could provide staggering quantities of energy but, as yet, no commercial plant has been built. This, however, holds out great promise. The difference between the temperature at the surface and at the depths of the oceans can be as much as 20°C , and energy can be harnessed from any potential heat difference. This is, of course, one aspect of harnessing the sun's energy. This suggestion is not new, having been proposed by J. D'Arsonval in 1881. The chief advocate now is C. Zener of the Carnegie-Mellon University, U.S.A. In 1966 a cost analysis of this project indicated that it would compare with a conventional power station.

The disadvantages are the physical size of such a plant. Water would have to be pumped 1000 metres through a 12 metre diameter tube. Various methods could be used to convert a 20°C heat difference into a higher potential difference.

This scheme appears fairly attractive but very little work has been done on it and the scheme remains on the drawing board with a number of problems remaining.

THERMAL POLLUTION

We do not wish to 'write-off' any of the above but vast research remains to be done on those which appear promising. All may be used as our



"I think the gods are warning us about an impending energy crisis" (from the Daily Telegraph at the time of the recent Solar Eclipse).

demands increase but we have to take an overall view of our world and the effect we are having on it. The American astronauts, returning from the moon, could only make out one unnatural feature on the surface of the earth—the massive smoke plume from the Four Corners power station in the south western U.S.A.—one of the largest power plants in the world.

We have become acutely conscious of pollution even to the extent of overstatement, as with most good causes, but we normally think in terms of industrial waste and effluent. If we think in terms of pollution we must also think in terms of heat pollution.

A speeded up radar view of south-east England in the winter shows vast flocks of birds leaving London every morning to feed on the surrounding countryside. At dusk the process is reversed. Why? Because the temperature at the centre of London is about 2°C higher than that of the surrounding countryside and this in turn is due to the quantity of energy consumed in the city and suburbs.

At present this effect is localised and of little importance but it can be calculated that in 50 years the world temperature will rise by 1°C and in 100 years by 5°C . There are two schools of thought as to the consequences of this. The good news is that plant life will take up the excess and become more prolific... the bad news is that it will start the melting of the polar icecaps with the low lying parts of the world being flooded. Even if we accept the optimistic view, there is obviously a limit to the ability of plant life to absorb the extra heat.

This warming up of the environment will happen with most of the energy sources mentioned in our survey of possibilities but it does not apply to one which we shall now investigate—Solar Power.

THE SUN

The sun has been worshipped by most races at one time or another as a god. When one realises the potential and power of it, a cynic could well suggest that perhaps we should never have stopped.

The statistics are easy to come by but the scale is almost outside our imagination. The sun is 865,000 miles across and is a vast nuclear fusion bomb, gobbling up matter at a phenomenal rate and releasing it as energy. At the centre the temperature is calculated to be 13 million degrees centigrade (a coal fire is under 1000°C).

At this temperature atoms are split into separate nuclei and electrons—in such a state this is called plasma. The atomic nuclei frequently collide with each other at great speeds and reactions occur between them. This process converts hydrogen, of which the sun is chiefly composed, into helium and releases enormous quantities of energy in the form of electromagnetic radiation.

Although the sun is on average 93 million miles away, the energy falling onto the surface of the earth is sufficient to sustain life for thousands of millions of years to come.

This energy has been stored on the earth by natural phenomena in a number of ways. The organic life of more than 100 million years ago has become coal and oil and this is due to the sun. The temperature gradients in the ocean, wind and hydroelectric power are also a result of the sun's power. (Geothermal and nuclear power are not a direct result of the sun's energy, however).

We are rapidly using up this stored energy in the form of fossil fuels while the other forms do not at present seem easy to harness with present technology.

On a normal day the energy falling on the surface of the earth is equivalent to over 1kW per square metre—and taken over the whole earth this is about the nearest we can get to an unlimited reserve.

AVAILABLE POWER

Enough energy falls on the earth in a 15 minute period to supply our requirements for a whole year. Looking at it practically, worldwide energy requirements until the year 2000 could be derived from the energy falling onto 250 miles square.

This energy is virtually limitless, pollution free, available anywhere in the world and it would not upset the temperature balance of the earth. The surface temperature would fall where collection takes place and this would be channelled to population

centres where it is released; these would cancel exactly.

One query may arise. As the sun has been feeding this energy onto the surface of the earth for about 4,000 million years, why is the earth not heating up naturally? The reply is that the earth itself is in balance and almost exactly the same quantity of heat is reradiated as we receive, maintaining an equilibrium. We can channel this to new areas and concentrate that energy without upsetting the overall balance.


LIMITATIONS

It is tempting to propose the sun as the obvious answer and to take the 'why-didn't-we-think-of-it-before' attitude. It is also tempting to regard the sun's energy as free... it is not.

A lot of rubbish has been talked about new energy forms, for instance, that atomic power would reduce the cost of electricity to virtually nothing. Electricity is cheap but even if the fuel was free the price would drop by only 20 per cent. In most of the world 80 per cent of the cost of electricity is accounted for by the capital equipment, the power lines, the personnel, etc., and only one fifth by the fuel cost. This has been the problem with nuclear power stations. The electricity from these costs about twice as much as from coal or oil despite the fact that they use only a few pounds weight of fuel each year because the capital cost is so very much greater than for conventional power stations.

This formula applies to solar energy. Whatever methods are used to harness it, it will have a massive capital cost and this has to be paid for by the user. Most of the realistic protagonists of solar power estimate that the cost will be at least twice that of conventional methods but this still makes it competitive with nuclear energy. Cost, however, must take a back seat; new energy sources must be found. On the other hand, these estimates do not take account of major technical breakthroughs, though this is an unwise argument. We have no right to assume, or even guess, that there will be technical breakthroughs in this field while assuming there will not be breakthroughs in completely new sources of energy.

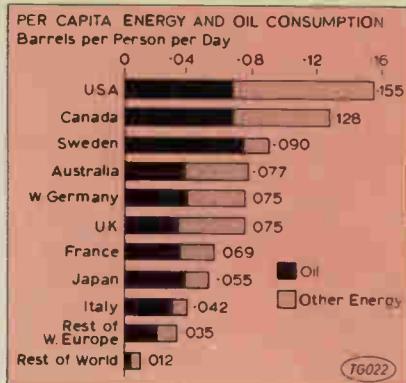Another temptation is to advocate the sun's energy because the technology is easily understood. A 15-year-old schoolboy can understand the technology necessary for many of the sun power schemes while very few understand the processes and problems of nuclear fusion for instance. We have mentioned these qualifications before explaining the various methods



proposed in order that we keep the whole thing in perspective.

Not everyone is enthusiastic about the idea: a Committee of the U.S. National Academy of Sciences only last year reported that sun power was unlikely to be of much importance for future energy needs and we cannot dismiss such an august body of gentlemen. However, research is not only continuing but is expanding in all parts of the world. The U.S. Government has increased the budget for research in this field ten-fold, from \$1.2 million in 1972 to \$12 million for the coming year. Considerable research is also going on in France, Australia, India and Israel. It has been suggested that a number of the Arab states are prepared to back research from their oil revenues as their countries will be ideal collection areas; this could give them something to fall back on when the oil wells dry up.

Research in Britain appears to be on a very minute scale at present. This is probably due to the fact that, as far as the energy crisis is concerned, Britain is one of the best placed countries in the world. The Table of Per Capita Energy and Oil Consumption for the world (1970 Data) shows that Britain is rather less dependent on oil than most countries due to the considerable use of coal and nuclear energy (Britain easily leads the world in this). The natural gas and oil deposits in the North Sea will shortly be brought into production. On the other side the climate in the United Kingdom does not exactly encourage research into sun power!

HARNESSING THE ENERGY

Harnessing the sun's power is not a new idea and from 1860-1920 a large number of solar engines were built. Some of these were remarkably ingenious but the technology of the time was not able to provide the precision necessary for viable mass production. In the 1920's oil started to grow in importance and the in-

THE SOLAR SOLUTION

centive for continuing the research disappeared. One photograph shows a solar collector in use beside the Nile River in 1913.

The main disadvantage with harnessing the sun's energy is the low density. Although the energy is equivalent to over 1kW per square metre, the conversion efficiency is likely to be considerably less than 100 per cent: most researchers will be happy with 25 per cent efficiency. From the table of energy consumption it will be seen that Australia, West Germany and the U.K. have very similar figures, each person using a little less than 0.08 barrels of oil per day equivalent; converted to electricity equivalent this is 12kWh per day per head. If we assume a 25 per cent conversion rate, this will necessitate about 4 sq. metres of collection area each (the 1kW applies only in daylight of course) or 20 sq. metres per household—and this does not allow for the rapid growth which is taking place. Even if individual solar collectors were cheap, this area is rather large for many houses and would be impractical in a city.

There are two main methods of collecting this energy—high concentration and low concentration.

HIGH CONCENTRATION METHODS —THE ODEILLO FURNACE

Five thousand feet up in the French

A solar collector built in 1913 and used beside the Nile River.



Pyrenees, near the village of Odeillo, is the world's largest solar furnace which is the inspiration of Professor Felix Trombe, Director of the Solar Energy Research Laboratory. This is a massive concave mirror which concentrates the energy from other mirrors feeding into it. This enables the sun's energy to be concentrated 16,000 times and is equivalent to 1000kW and a temperature of 3,800°C.

This furnace has been designed primarily for research but is already in limited industrial use where super-high, super-pure heating is required, such as in the fusion of silicas.

The furnace sounds a simple conception but is considerably more complex than it appears. The 'feeder mirrors' have to track the sun across the sky very accurately and these feeder mirrors total 325 sq. yards.

This research project is by far the most advanced in the world and is at least working but it is very unlikely to be the model for a major power plant. The siting of the Odeillo project was carefully chosen; in the high Pyrenees there are few overcast days and at this height the water vapour, which cuts off much of the energy at lower altitudes, is very low. The size of the furnace is considerable

and though 1000kW sounds a lot, it is only sufficient for about 500 homes.

TRough COLLECTORS

The University of Minnesota and Honeywell Inc. are co-operating in the research of trough collectors and have been given a substantial grant by the U.S. National Science Foundation to pursue this.

Unlike many of the research projects being undertaken, this one is aimed at finding a solution for large scale energy needs and to the mass production of collectors. Most of the work so far has been theoretical and at the time of writing a prototype has not been built. Nevertheless a considerable amount of research has already been devoted to this by Roger Schmidt of Honeywell and, since the design is based on current technology, it looks promising.

The basis of this method is the trough-shaped collector which would concentrate the energy onto a 'heat-pipe'. This, in effect, would raise the temperature to about 1000°F and feed it to one end of the pipe where a heat exchanger would produce high pressure steam to be fed to a conventional generator. The heat exchanger would also incorporate an eutectic material, that is, one that will store heat and act as a reservoir during the night. The problem of storage has not yet been dealt with but it is of course vital. We shall not be able to use the sun as an energy source unless we have a reasonably constant energy supply. Electricity is not easily stored, batteries can be used but show only a tiny capacity and are prohibitively expensive. In Britain the Central Electricity Generating Board has a scheme where at night, when there is an excess of electricity, water is pumped to a high reservoir and during the day this is fed down again to provide hydroelectric power, but this is not very efficient and the number of suitable sites is limited.

On the other hand, heat can be



The Odeillo solar furnace high in the French Pyrenees.

stored fairly easily. The University of Minnesota/Honeywell method is to melt salt in periods of excess heat and rely on the latent heat released during the cooling process to keep the cycle fairly constant.

The size of the trough is somewhat arbitrary but for efficiency, ease of transport and repair, etc., the best size would seem to be 40ft. x 10ft., but larger or smaller units may prove to be better once the research has been done. The cross-section of the trough is a parabola but surprisingly the design of this proved to be rather complex and a massive computer program had to be drawn up to design it. This parabola concentrates the sun's energy by a factor of 20 onto the heatpipe. Various reflective surfaces are being tried. The heat pipe itself has to be coated to provide high acceptance for the wavelengths received from the sun but low emittance at infra-red. This is necessary to prevent the heat being reradiated. A suitable coating has been developed and tested at the necessary high temperatures; this consists of alternating layers of alumina and molybdenum. The heat pipe is surrounded by a glass tube and the space evacuated to reduce convective losses.


HEAT PIPE

The heat pipe is a sealed hollow-bored tube containing a fluid which changes phase—from liquid to vapour and vice versa. The pipe operates by absorbing energy along its whole length, which causes the fluid to vaporise and release energy at one end by condensing the vapour back to liquid. This then runs back down the tube to repeat the cycle.


Heat pipes act like a diode—heat can only travel one way and the process is not reversible. They are also amazingly efficient, being a thousand times better conductors of heat than a solid copper rod.

A variety of liquids show promise, especially water, but this has the disadvantage that at high temperatures steam is rather corrosive and has a maximum operating temperature of 325°C. Other materials are being investigated, such as potassium and Dowtherm, but water seems the most promising.


The heat pipe feeds into a heat exchanger where it will convert steam for feeding the generators. The heat can either be stored at each collector, or centrally at the generating station. A material that stores heat in melting and releases it in freezing has the advantage that the temperature stays nearly constant. Some eutectic salt mixtures have been developed for this purpose. The Philips Research Lab-

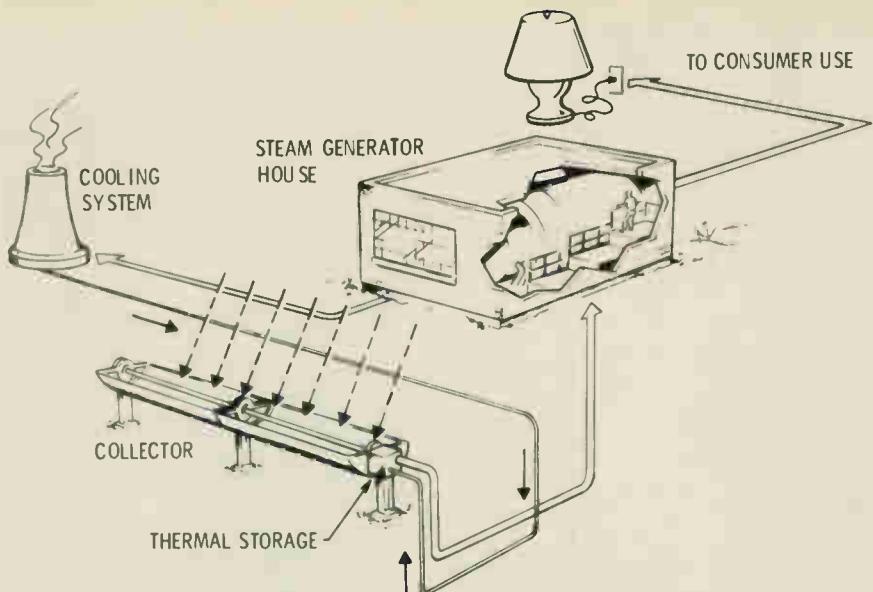

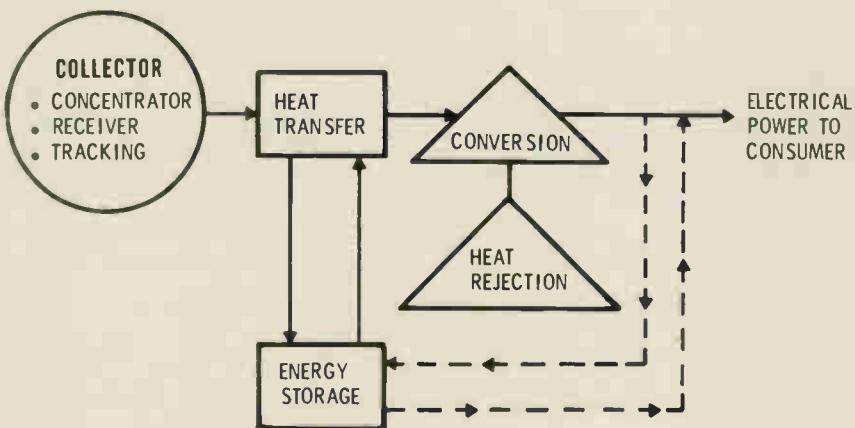The University of Minnesota/Honeywell suggested method for producing electricity from the sun's rays.



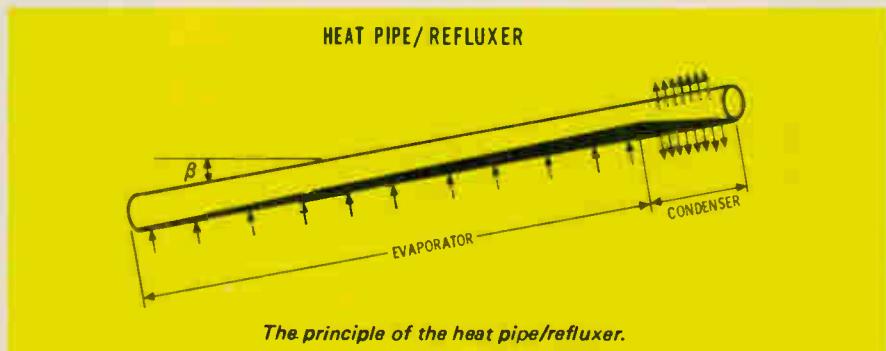Basic elements of the parabolic solar collection system.



The principle of the heat pipe/refluxer.

oratory at Aachen in West Germany has demonstrated the suitability of a mixture $\text{NaF}_2\text{--CaF}_2$. This stores 350kWh per cubic metre but at a rather high temperature of 745°C, rather too high for use with water. The search is on for a suitable material which stores heat around 300°C. As little research has yet been conducted in this field it is not regarded as a serious problem.

Another method of storage would be to bubble the high pressure steam

into a pressurised water tank. The temperature inside would rise but, due to the pressure, the water would not be converted to steam. When the steam is required the pressure is reduced and flash vaporisation occurs. This method of energy storage is already to use and allows about 100kWh per cubic metre to be stored.

Each of the associated solar collectors would provide 2kW averaged over a 24 hour period but the range would be enormous, from a 25kW peak to

THE SOLAR SOLUTION

nil for periods of darkness.

The parabola would have to track the sun across the sky to achieve maximum efficiency.

Costs have already been worked out and such a collector produced in reasonable quantities would work out at £600. A complete generating station would need 500,000 of these units to produce 1,000 Megawatts. With the connecting pipes, storage and generating plant the cost would work out at £400 investment per kilowatt as opposed to present conventional systems which cost about £80 per kilowatt. As we have mentioned before, on a purely cost basis solar power does not stand up well.

The solar farms, the name already coined for these collecting areas, could serve a dual purpose. They would almost certainly be sited in desert areas and would provide a considerable amount of shade which would encourage fertility in the soil.

The collectors would have to be washed regularly to retain the efficiency and this waste water could be used for irrigation of these dry areas ... a minor point but an additional benefit.

Anyone who doubts the benefit of this shading should consider one of the rare benefits of pollution. The smoke haze surrounding Salt Lake City in Utah, U.S.A., has cut down the sunlight to such an extent that the desert is becoming fertile again!

The Honeywell/University of Minnesota scheme is not the only one based on the trough type collector and other people are working along the same lines, notably Aden and Marjorie Meinel of the University of Arizona who have a prototype collector in operation.

Individual collectors could be used, siting these on the roof of a house but this would require individual generators. Simpler versions without storage and with no generators could find a market. In the areas of the world where these collectors could be used, one of the main uses of electricity is for the powering of air conditioning plants - which are only required during daylight when the sun is strong. More than one expert has forecast that sun-powered air conditioning plants will be available before the end of the decade.



Sunshine catchers like these may be the answer to the power shortage. This artist's impression shows a solar farm in the desert, with sun collectors providing shade for grass to grow.


Surprisingly a solar collector will have a slightly higher efficiency during the winter than in the summer. The shorter daylight hours and lower air temperature are more than compensated for by the lower concentration of water vapour in the atmosphere which allows more sunlight to reach the collector.

SATELLITE SOLAR POWER STATION

The most ambitious plan for harnessing the sun's energy must be the

idea of Peter E. Glaser of the U.S. company Arthur D. Little. This has attracted the support of some major companies and N.A.S.A.

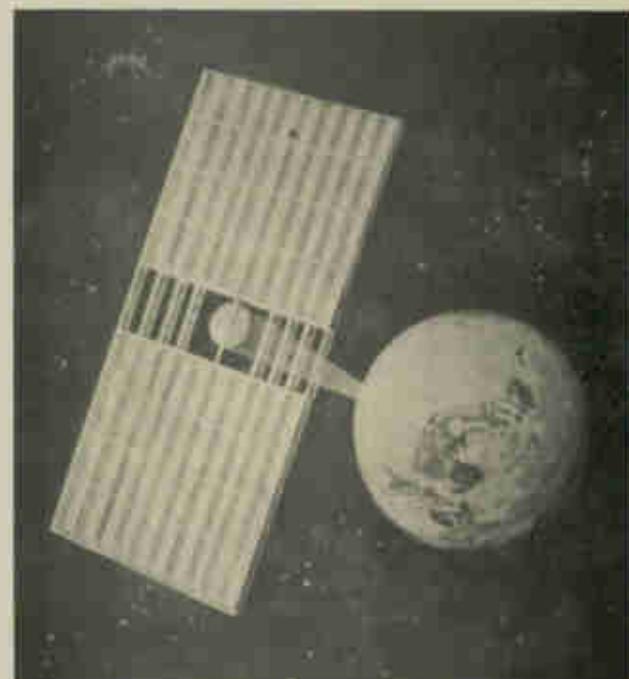This scheme would utilise a massive artificial satellite in synchronous orbit around the earth. This would comprise a massive bank of solar cells about 18 sq. miles in area. The current generated would be fed to a microwave transmitter (a frequency of 3.3GHz has been proposed) and beamed down to an earth receiving station, 3 miles in diameter. This would comprise a vast array of half-wave dipoles



Peter Glaser's satellite scheme could provide enough energy for the largest of the world's cities using a satellite with a collector area of about 18 sq. miles.

which would connect to solid state rectifiers. Schottky barrier diodes at present have an 80 per cent microwave rectification efficiency at 5 watts and a figure of 90 per cent is envisaged.

This scheme would generate 5,000MW, enough to keep the world's largest cities going. Being in space there would be far more energy collected by the cells as the attenuation of the atmosphere would not be present and the satellite would always be operating providing a source of energy 24 hours a day. It is thought that there would be no harmful effects if a bird or plane flew into the microwave path though this requires investigation.

Precise alignment of the beam would be necessary and this could be achieved by transmitting a beacon from the ground station back along the same path.

There are disadvantages and they are major ones. This scheme assumes a technological breakthrough in several areas—especially in the price reduction of solar cells which would have to cost about one thousand times less than at present. It would also require several hundred space shuttle flights and this is not yet in operation.

This scheme is certainly imaginative and should not be condemned for that reason, but it is certainly a very long way off. Even the protagonists of this scheme do not expect a prototype before 1990 even if the go-ahead was given now. Optimistic cost forecasts give a figure of £400 per kilowatt, similar to the solar farms and, incidentally, both are again similar to the capital costs for a nuclear power station. However, the satellite solar power station costs assume cost reductions on a massive scale; solar farms and nuclear power do not.


SOLAR CELLS ON EARTH?

If the solar cell is a possibility for a satellite, why not on earth? Despite truly extensive research we have not come across anyone seriously proposing this. It would assume an even greater cost reduction than the SSPS and would give no power at night and considerably reduced power in cloudy conditions. Storage would involve conversion from electricity to some other medium, probably heat, and this would reduce efficiency.


It is tempting to suggest that house roofs could be made from a bank of solar cells but although it is simple in its conception, it lies a long way behind the other schemes for cost and practicality.

FLAT PLATE COLLECTORS

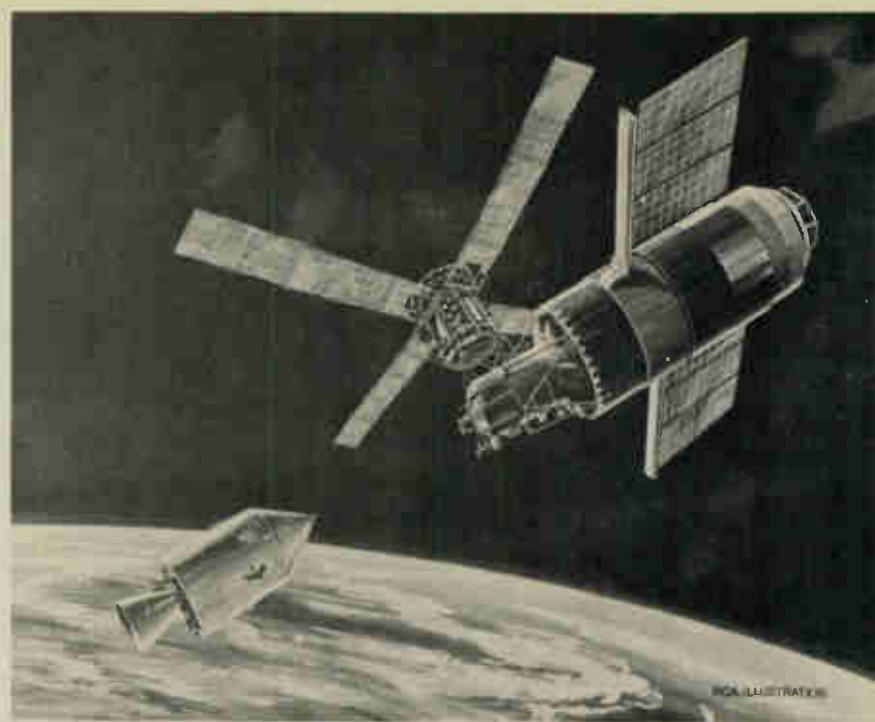
Solar farms require reliable weather conditions and are unlikely to be of



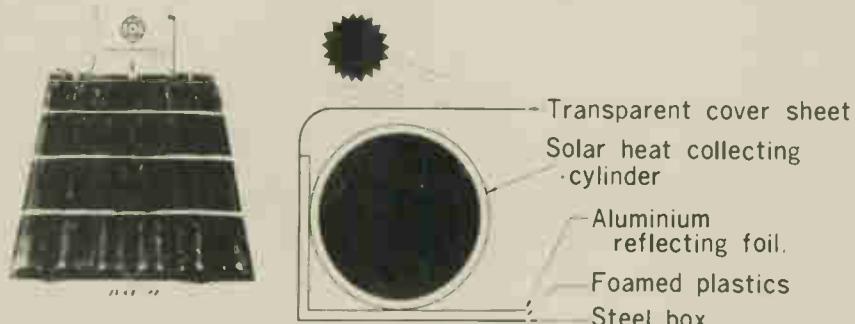Solar power is already harnessed for many space projects including Skylab. Unfortunately, one of the solar collector plates failed to open and is causing some of the current problems of this project.



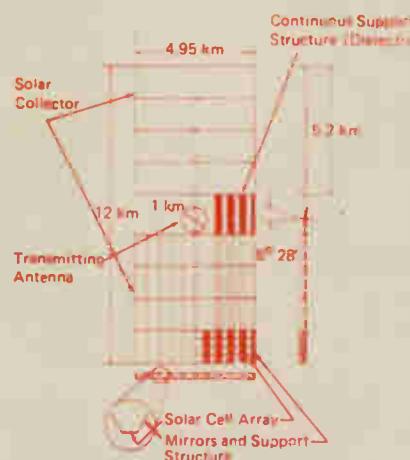Photograph and cut-away drawing of a Japanese water heater operating as a solar flat-plate collector.



Dimensions of the SSPS.

use in latitudes of 40° or more but diffused light can be harnessed anywhere for low temperature uses.

We suggest you try a simple experiment. Get hold of a glass bottle, paint it matt black, fill it with water and put it outside. After an hour or two, measure the air and water temperatures

with a thermometer. We set up this experiment which demonstrates perfectly the principle of the flat plate collector.

With an air temperature of 72°F, after an hour the water temperature was over 100°F. We also put water in an unpainted bottle and this had risen only to 85°F.

With a properly designed system, it is quite possible to achieve temperatures of 140°F, rather warmer than is comfortable to the touch. About 12-15 per cent of the energy consumption in the industrialised nations is used for heating water up to this sort of temperature.

Water heaters of this type, which usually look like a modern central heating radiator, were popular in Australia and the U.S.A. in the 1930's and over a million homes in Japan today use roof mounted flat plate collectors as the source of warm and hot water. Surprisingly, these are becoming less common, especially in Japan where they are associated with

THE SOLAR SOLUTION

a low standard of living.

Flat plate collectors are best built into the original structure of the house and this need not make the building unattractive as the architects' drawings for a house in Atlanta, U.S.A. show.

Atlanta is in a sunny area of the world but plans are well advanced for the construction of such a house in the North of England. This is being designed by a team led by S.V. Szokolay of the Central London Polytechnic.


Flat plate collectors are only considered to be a very basic system which must be used with a conventional heating system, but the saving in fuel bills can be quite dramatic.

A number of swimming pools in Britain are heated by solar power: the photograph shows one such installation for a 50,000 gallon pool at East Grinstead. You can buy one of these flat plate collectors and the cost is less than £60 for a 25 sq. foot unit and a few houses have these fitted already. Including installation, the cost should be less than £100 and this can show a dramatic saving in fuel costs with the cost being recovered in a few years. Sun Trap units, the proprietary name, are made by Solar Heat Ltd., 99 Middleton Hall Road, Kings Norton, Birmingham 20.

USING THE ELECTRICITY

All the methods of harnessing the sun's power have been designed to produce electricity or direct heat. Electricity can be fed easily to remote locations. Already power lines cross international boundaries. The peak current periods in Britain and France are different and a power line laid under the English Channel feeds current to France during their peak and the process is reversed during the British peak. The huge Cabo Bassa dam on the Zambesi in Mozambique will provide electricity for several countries in southern Africa, so there are already precedents for transmitting electricity large distances. Northern Europe could take electricity from the Sahara for instance, either using conventional power lines or via superconductors.

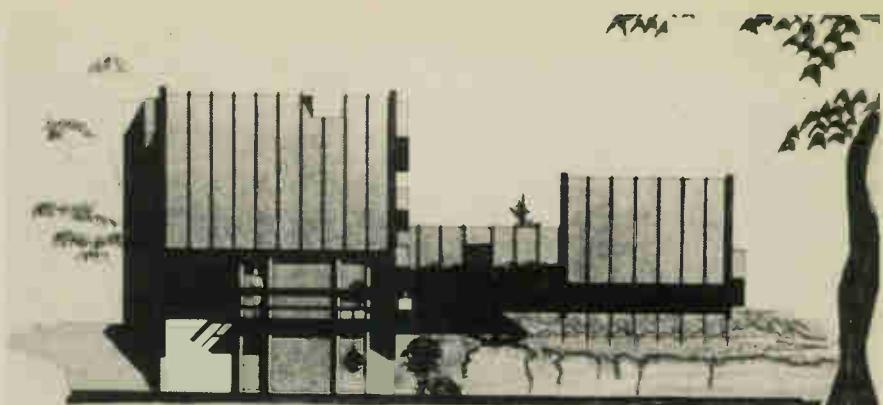Electricity, however, is not the most convenient energy source for all uses—especially in the field of transport.



Architect's drawing for a house in Atlanta, Georgia, U.S.A., which has been specifically designed to incorporate flat-plate solar collectors.


The electric car has been dreamed about for a long while and we are continually hearing that it is 'just around the corner'. The facts are that electric cars have been produced and Enfield Automotive, Isle of Wight, expect to make 500 before the end of the year. Even so, mass production is some way off. Most of the prototypes use lead-acid batteries but there is probably not enough lead available for true mass production of cars based on this. Energy cells are lighter but much more research is required to improve the efficiency.

Petrol is such an ideal material with regard to the power in each gallon that artificial production may be the answer. Towards the end of the last war, after the Germans lost the Rumanian oil wells, they were able

to continue the war by distilling petrol from Lignite which is low grade brown coal. Production was on a substantial scale but the cost was such that it was discontinued after the war.

A whole range of hydrocarbons, including petrol, are produced in South Africa by Sasol. These are produced by the gasification of coal and catalytic synthesis of hydrocarbons using the Fischer-Tropsch process. Over 10 per cent of South Africa's petrol is produced in this way and is sold under the 'Blue Pump' brand name. The South Africans are the world leaders in this field. As a temporary measure coal could well be converted to hydrocarbons but, as we have mentioned, it is a limited resource.

The artificial production of petrol

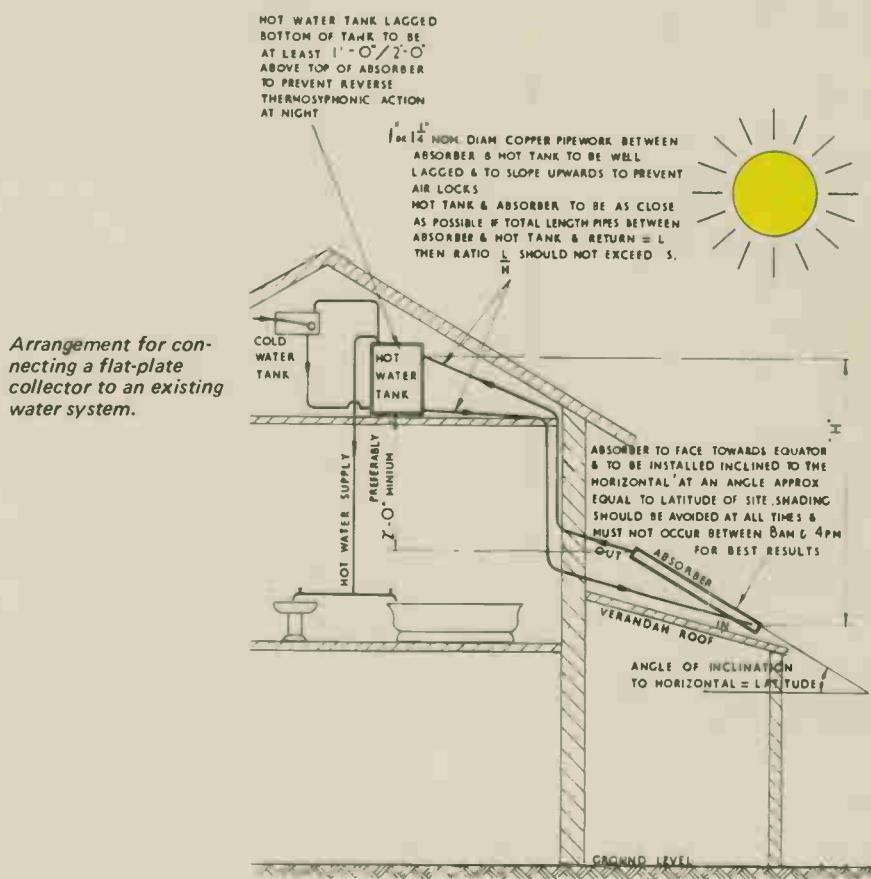

is possible; after all, the elements are carbon and hydrogen, both of which are very plentiful. Hydrogen can be derived from water while carbon can be obtained from CO_2 in the air or from limestone and chalk—both of which are plentiful. Enormous quantities of energy however are needed for this production.

There are a number of advocates for Hydrogen Power, especially in the United States. Rather than combining the hydrogen with carbon to form petrol, it can be used directly. There is plenty of water and using electricity it can readily be broken up into hydrogen and oxygen. A hydrogen car is actually running, it has been developed by the University of California, and only the simplest modifications are necessary to a standard motor car to enable it to run off hydrogen. It is of course pollution free and it is claimed you can drink the exhaust! The hydrogen is carried at high pressure and the storage space is comparable to a conventional petrol tank.

WHAT IS THE ANSWER?

In this article we have described various research work going on all over the world, but the subject is so vast that we have only been able to give a very general outline of the subject. We have not even mentioned some schemes and have concentrated only on the most interesting or those which we consider most practical. We have commented but have avoided judgment.


Let us look into the future and guess at the developments in the next few decades.

1975-1980

Oil goes up considerably in price due to an anticipated shortage, but production continues at a high level due to intensified searching for new fields and the working of previously uneconomic sources (e.g. the Tar Sands and oil-shale in North America). New power stations are either coal burning or nuclear, but environmental arguments oppose these.

1980-1990

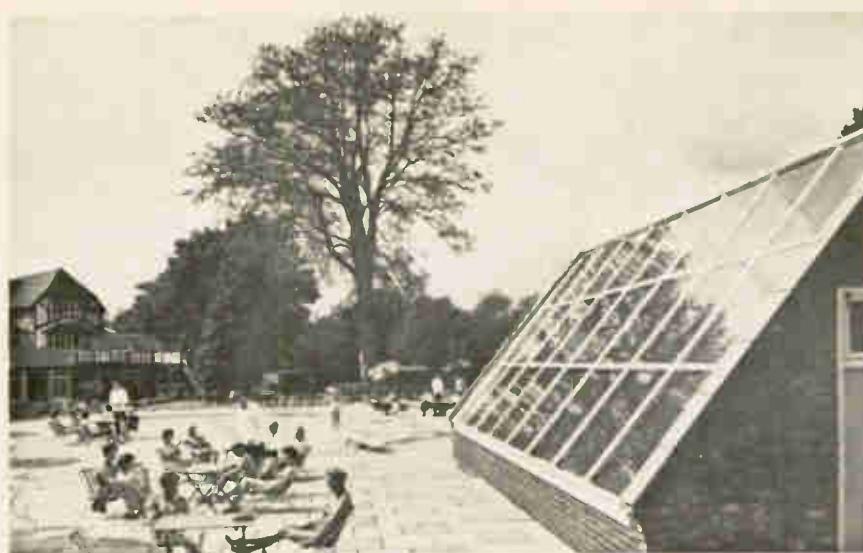Intensive investigation to replace oil takes place and also a massive investment in solving the nuclear power problems, but also in solar research. Oil continues to rise in price and hydrogen becomes an important source of energy, especially in transport and towards the end of the decade surpasses oil in importance. Hydrocarbons are produced from coal on a very large scale.



Solar collector used for heating a 50,000 gallon swimming pool in East Grinstead.



Apart from the technical problems, the use of solar power could well necessitate some changes in the law: what will be your rights with regard to shadows cast by other people's property for instance.

1990-2000

Solar power used on a large scale, either using solar farms or by harnessing ocean temperature gradients. Hydrogen power supreme for transport but petrol and oil still important. Nuclear power gaining in importance as the problems are solved.

2000-2010

Nuclear power dominant in the industrialised world, solar power elsewhere. Hydrogen universal for personal transport.

2010-2020

Nuclear power and hydrogen are dominant though existing solar power stations continue.

Predictions in the past have almost invariably been wrong and so this time scale may be wildly out. What we can say with certainty is that a new energy source must be found, and found fast, to take over from oil.

Various problems beset nuclear power at present and until solutions are found we are going to have to find an alternative. Solar power has its own problems, especially with regard to cost, and it may not be the answer, but it is certainly worthwhile investigating. . . and time is running out.

ETI would like to thank the following for their help in compiling this article and for their permission to use drawings and photographs:

Roger Schmidt, Honeywell Inc., Minneapolis, Minn., U.S.A., and Michael Young of the U.K. office.

Peter Glaser, Arthur D. Little Inc., Cambridge, Mass., U.S.A.


William H. Woodward, N.A.S.A., Washington D.C., U.S.A.

S.V. Szokolay, The Polytechnic of Central London.

Solar Heat Limited, 99 Middleton Hall Road, Kings Norton, Birmingham 30. International Solar Energy Society, Australia and New Zealand Section.

U.S. Treasury; CNRS, Paris, France; Daily Telegraph; H.M.S.O.; Shell Oil; Sasol; Helen Gimpel, Researcher.

PERSONAL

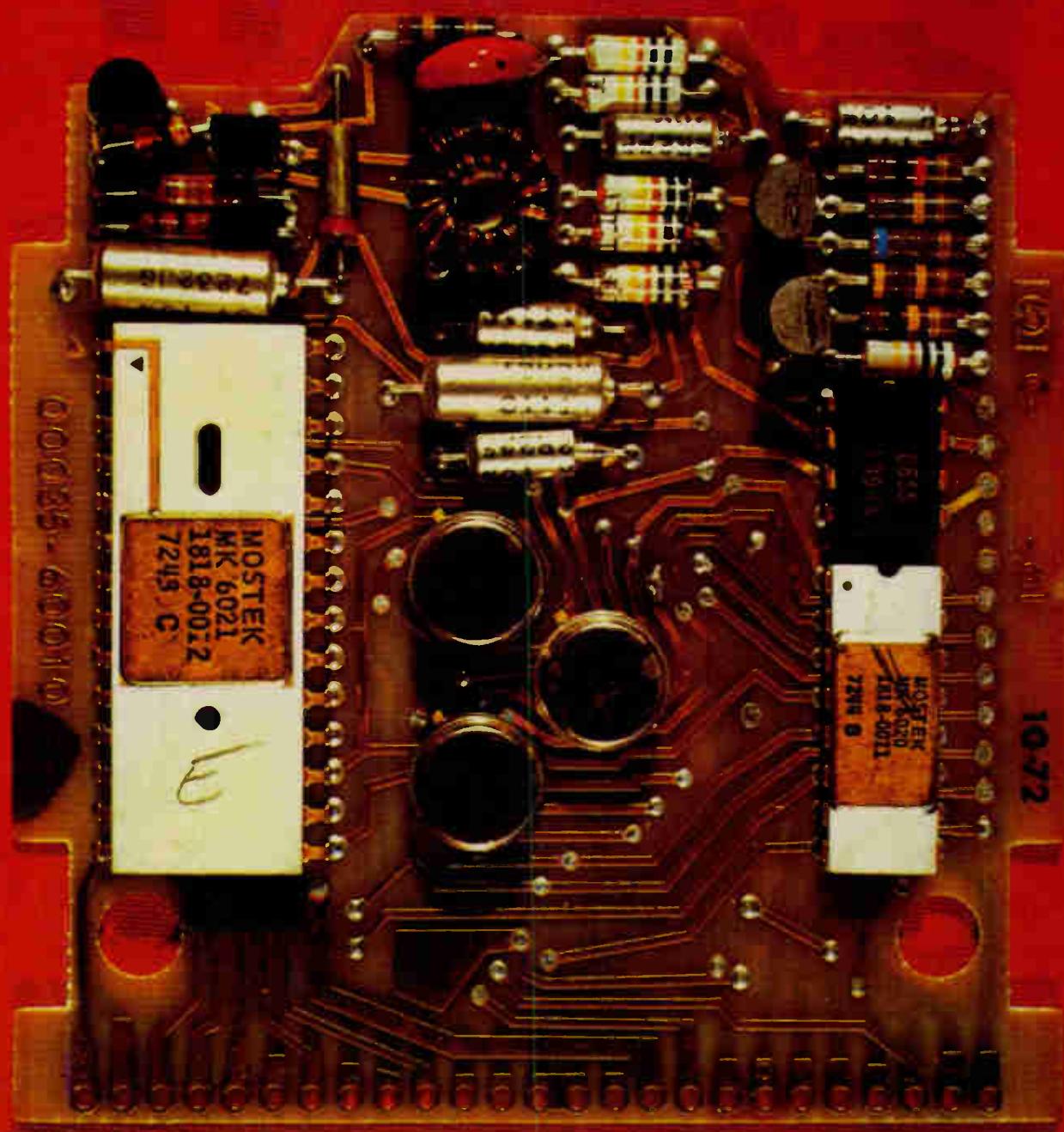

Logic board of Hewlett Packard HP-35 calculator

CALCULUS

Had you been late for an appointment with Julius Caesar, you would no doubt have hailed a passing hire chariot and galloped hastily on your way through the cobblestoned streets of ancient Rome.

As you progressed you would have heard a periodic clunk coming from a device mounted on one of the wheels. This device was called a "hodometer"

— or road measurer. Every time the wheel rotated one turn, a pebble would pass from one container to another via a small hole. At the destination the driver would simply count the number of pebbles to calculate the charge.

The Latin word for pebble is "calculus" — and so we see how our English word "calculate" had its beginning.

JUST what does make a calculator tick? It is not possible to answer this question fully in a short article such as this because even the simplest of four-function calculators is based on one or more integrated circuits containing at least 5000 transistors. These are arranged in a logic array which would have astounded the computer engineer of 20 years ago — in fact it's still amazing! So we will not get involved too much in the 'innards' of the integrated circuits themselves but will describe the way they are used in currently available machines.

The small electronic calculator can add, subtract, multiply and divide.

CALCULATORS -the inside story

How they work, and how to choose one.

Most models can handle the decimal point, either by presetting it or by using floating point arithmetic. The number of displayed digits varies between six and 16, depending on the model, with negative results (so called credit balances in the business world) clearly indicated as such.

Operations are done nearly instantaneously, and the machines are silent, small, light, and in most cases service-free. Some personal calculators are capable of remembering a constant for repeated multiplication or division, and some have a completely separate memory which may totalise numbers for recall whenever required. Still others, to be described later, can solve functions such as logarithms, trigonometric identities and such like. One recent model is even capable of solving accounting equations (such as compound interest) at a single keystroke — and all this for a selling price of around £200.

With such features as these, and with the virtual assurance that prices will continue to fall dramatically, (we hazard a guess at £20 per 8 digit, four-function calculator by the end of the year) it seems most likely mum will be checking the grocery bill on her pocket four-function calculator, and the kids in a few years time will all have their personal, electronic slide-rule to remove the unnecessary drudgery from mathematics.

The electronic calculator, although it looks simple enough, is really the most complicated machine available to the consumer today. In a way it may be said to be a scaled down version of a digital computer with some important differences. The computer is designed for flexibility and hence it needs to be continually reprogrammed for each problem of a different kind. It must also be capable of performing many different functions with the computed data — It may drive a teletype, control a process automatically, or print out the data at high speed. It may also produce a range of answers to a problem from a string of input variables. Thus we say that the computer is not dedicated to any one

job. But it suffers for this by having complicated input and output structures. Thus to add two and two by computer you must first program the machine to perform arithmetic and instruct it what to do with the results — a time consuming process for one calculation to say the least!

The personal calculator on the other hand, is a dedicated machine. It solves mathematical problems in accordance with a program that is built into the integrated circuits. It accepts data from a manual keyboard only, and presents its output almost invariably direct to a display. Some other types of calculator approach the computer more closely by having external program capability, but they are still calculators *not* computers because they are dedicated to solving individual mathematical problems. The computer on the other hand may solve thousands of such problems in less than a second in order to perform its programmed function. Nowadays the two machine capabilities overlap to some extent and it is sometimes

difficult to differentiate between a programmable calculator and a mini-computer, but that is another story.

The calculator revolution moved into full swing when Texas Instruments (the inventors of integrated circuits in the late 50's) began mass producing a single-chip, MOS/LSI calculator-logic device in late 1971. Bowmar and Eldorado Electrodata were the first to use these devices to manufacture small calculators which retailed in the US for around \$200.

30 000 TRANSISTORS IN YOUR POCKET

It is interesting at this point to compare these LSI (Large Scale Integration) calculators with the first electronic computer ENIAC. This machine, built in 1946, used 18 000 vacuum tubes and occupied 1800 feet of floor space. The LSI calculator contains up to 30 000 transistors, in integrated form, and can be carried in your pocket.

Typical of the latest four-function and memory calculators is the ELS1-811A from Sharp.



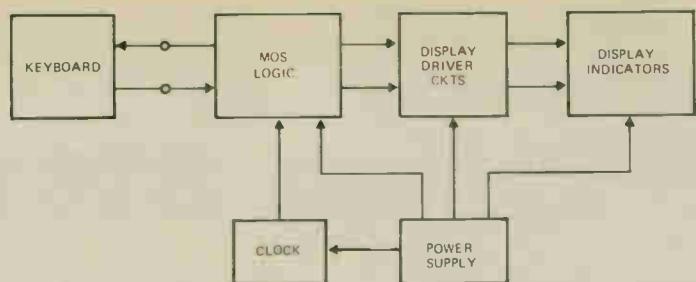


Fig. 1. Simplified block diagram of a calculator showing interconnection of the major component blocks.

This degree of miniaturization was made possible by the progress in MOS (Metal Oxide Semiconductor) technology. Where, for example, an RTL (Resistor Transistor Logic) or TTL (Transistor Transistor Logic) integrated circuit contains on average 10 transistors per silicon chip the integrated circuits fabricated with the MOS technology can typically accommodate 1000 to 5000 transistors per chip.

This increase by a factor of at least 100 in the number of transistors per chip opened the way for using integrated circuits as memory elements, where 1000 or more bits of information can be stored in one integrated circuit. In fact, single chip devices capable of storing 8192 bits of information are now available.

Another advantage of MOS integrated circuits, in addition to miniaturization, is their small power consumption. Typically the power consumed by an MOS integrated circuit is 10 microwatts per transistor, compared to 10 milliwatts per transistor in an RTL circuit. Nothing being perfect in this world, MOS integrated circuits have also certain drawbacks. One of them is their relative slowness (microseconds switching times rather than the nanoseconds required by modern computers). Another drawback has been the relatively high cost, in particular when compared to a large magnetic core memory. But MOS prices have fallen such that they are now challenging even core as a storage medium. A third drawback is that early MOS circuits could easily be damaged during handling through static electricity discharges. Therefore special precautions, like grounding of all tools, have to be taken during production, assembly, and testing of such circuits. Most modern MOS devices incorporate protection circuitry against this eventuality, and some later families such as CMOS may be handled without fear of such damage.

Considering the advantages and drawbacks of the MOS technology, it can be seen that it is ideally suited for personal calculators where speed is not too important and a division lasting

100 milliseconds is still considered pretty fast.

A typical personal calculator contains from one to six MOS LSI integrated circuits with a total of 5000 to 30 000 transistors and perhaps a dozen or more discrete transistors and a few non-MOS integrated circuits to interface with displays. Chips are now coming on the market which include all circuits except power supply, display and keyboard. Typical of these newer systems is the Philips EDC200/210 set (see Fig. 1).

In a typical calculator, MOS integrated circuits perform the arithmetic and memory functions, direct the flow of logic, and store the instructions and results. The discrete transistors provide the interface between low power, low voltage MOS integrated circuits and high power, high voltage displays (e.g. Nixie tubes). Discrete transistors are also used for clock signal generation and for voltage regulation. Standard TTL or RTL ICs are used for interface between MOS ICs and medium-power, low-voltage displays like LEDs (Light Emitting Diodes). Standard ICs are also used for translation of numbers from the form in which they are handled by the calculator into appropriate display form (either numbers 0-9 in Nixie tubes or the proper segments in multiple segment displays).

The main blocks of an electronic calculator are the power supply, keyboard, display circuitry, clock generator, input scanner, registers, arithmetic control unit, the ROM (Read Only Memory) for instruction storage, and the output control. We will not describe the power supply or the keyboard as these are entirely conventional.

CLOCK GENERATOR

The clock generator provides a series of pulses at a rate between 20 kilohertz and 500 kilohertz, depending on the calculator model. These pulses synchronize the flow of information between various calculator blocks and step the logic through the program steps contained in its ROM (Read Only Memory).

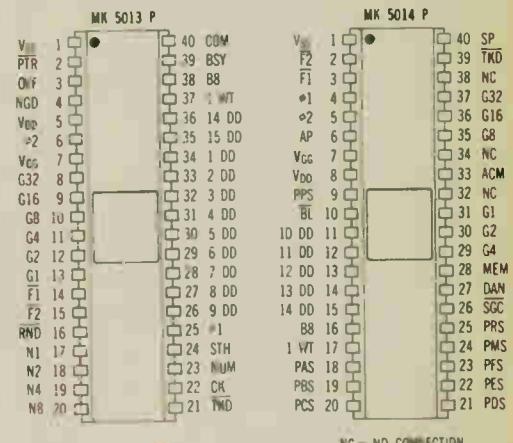
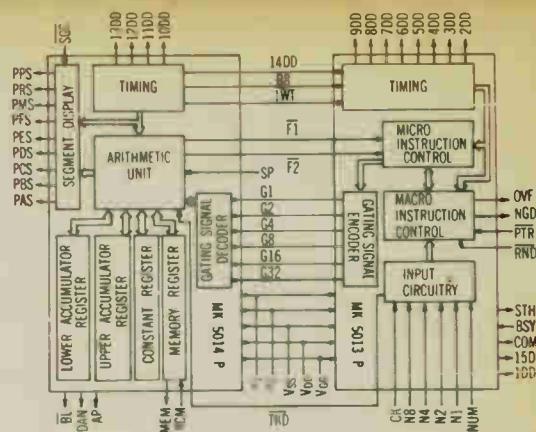


Fig. 2(a)

INPUT SCANNER

The input scanner continuously scans the keyboard so that it can detect which key has been depressed. The numbers from the keyboard are entered into the input register and the selection function ($-$, $+$, \times , \div) is translated into an initial address to the ROM. The input scanner is then disabled until that key is released and the control ROM has completed its function. This prevents erroneous entries.

REGISTERS

Every calculator has at least two or three shift registers. Firstly there is an input register which stores the number entered by the keyboard one digit at a time in BCD (Binary Coded Decimal), each digit requiring four bits of storage. Thus the number 1973 would be stored as:—

1 9 7 3
0001 1001 0111 0011
(8421 weighting)

A 12 digit calculator would therefore require 48 bits of storage capacity in each shift register.

Each number as it is stored in the input register is decoded and appears on the output display.

When an add, subtract, multiply, or divide command is entered, the command is stored and the contents of the input register are transferred into a register known as the 'Accumulator', freeing the input register to accept a

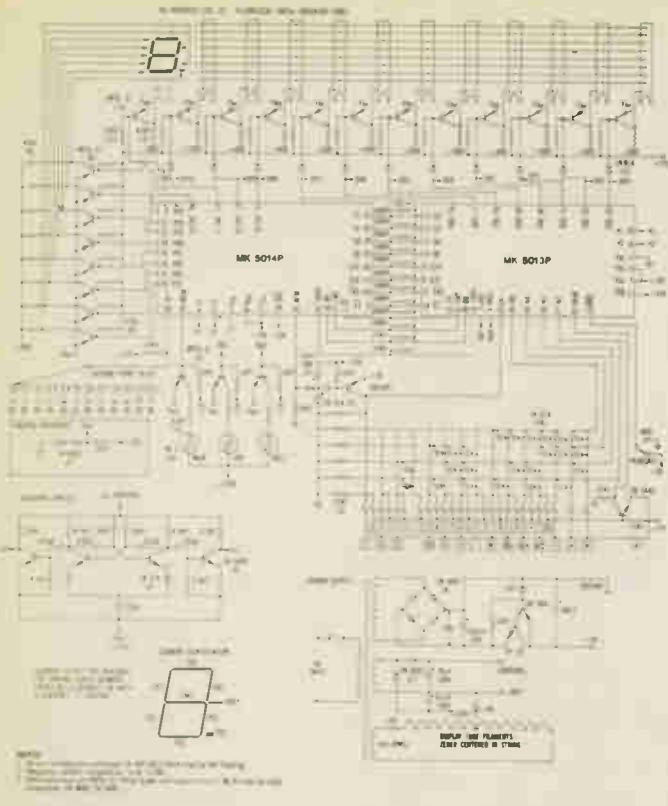


Fig. 2(b)

Fig. 2(a) Block diagram and (b) circuit diagram of Mostek, two chip, 12 digit calculator with constant and memory. The display is multiplexed, and transistors are used to interface the output of the chips to the high voltage requirements of a Panaplex display.

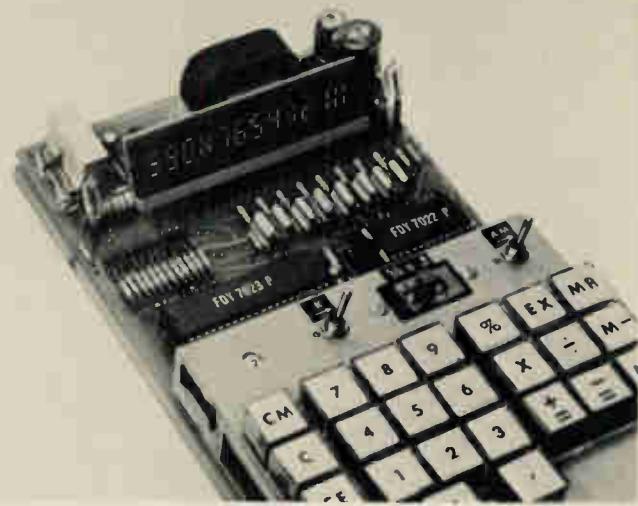


Fig. 3(a) Prototype calculator using the Philips EDC200, two chip set and the Philips Pandicon display type ZM1500/12. It has 12 digit capability, full memory, percentage floating or fixed point operation, and round-up or round down.

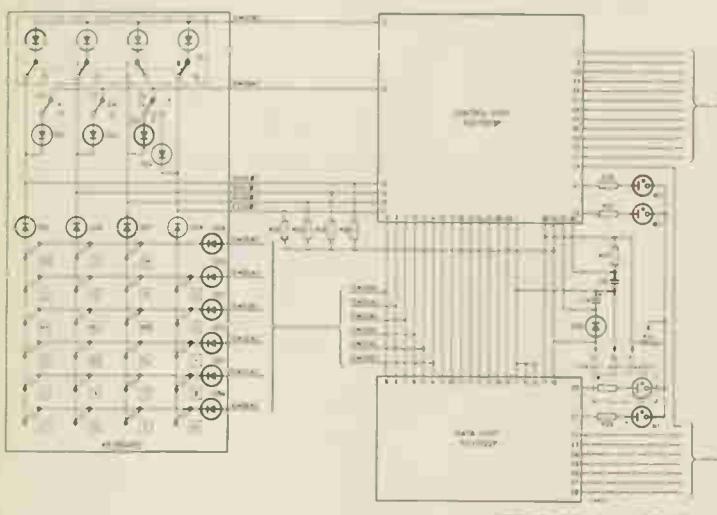


Fig. 3(b) Circuit diagram of Philips EDC200 shown in Fig. 3(a)

new number. When the first key is selected for the new number the input register is cleared, and the new digits are stored and displayed as the keys are pressed. The calculator now awaits a new command. If the 'equals' key is pressed, the command is carried out (for the two stored numbers) by the arithmetic and control logic, and the result displayed.

For multiplication or division a third register is used to shift the digits left or right and store intermediate results. This register is therefore sometimes known as a multi-quotient register.

Those calculators which have a 'Constant' facility have a switch that prevents the number initially

transferred onto the accumulator from being cleared. Successive operations may therefore be performed without continually re-entering the constant.

A further register may be used as a 'memory' in which totals can be accumulated. The contents of this register can ideally be separately cleared or recalled to the input register for further processing as required without destroying the contents of the memory. This facility adds considerable power to the calculator.

ARITHMETIC CONTROL UNIT

The arithmetic control unit provides logic for performing additions and subtractions. Multiplication is

performed by repetitive addition and shifting of digits in the multi-quotient register in association with the ROM. In the same register, division is performed by subtraction and shifting. Most calculators, depending on the circuitry, will either truncate (cut short) the results, or round them to the next digit. For example, a simple calculator will show $2 \div 3 = 0.6666$, a more elaborate one would show the result as 0.6667. Because all numbers are stored and operated upon one digit at a time, the calculators are true decimal machines. Therefore, the results are exact as long as they can be represented with the number of digits available for display.

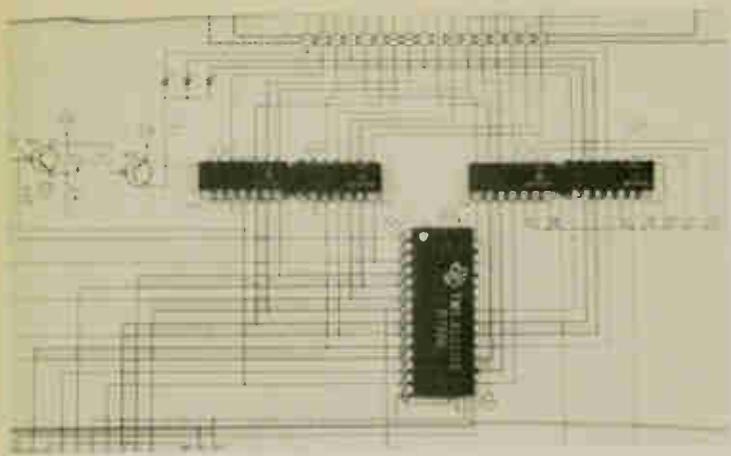


Fig. 4. This Texas Instruments' chip set is for an eight digit floating-point calculator with constant facility. The 28 pin pack, TMS003, is MOS/LSI and performs the calculator logic. The other four chips decode the outputs to drive a seven segment LED display.

READ ONLY MEMORY

The Read Only Memory provides instructions to the arithmetic unit and to the registers in order to perform the required arithmetic operations. Part of each instruction is the address of the next instruction in the ROM. Both multiplication and division require approximately 50 instructions each. The keyboard operation entry leads to the address of the first instruction corresponding to a particular arithmetic operation. The control is then transferred to the second instruction using its address attached to the first instruction and so on until the complete operation is performed.

OUTPUT CONTROL

Output control transfers the number stored in the output register to the display indicators. To save on BCD-to-decimal translators, the display indicators are generally operated in time-shared mode. Digits are scanned and transferred one at a time and the display is repeated every few milliseconds. At this fast rate, it appears to the eye that the display is continuous.

Other functions of the calculator are imbedded within previously described major blocks. These are control of the decimal point, storing of constants for multiplication or division, checking for negative results and activation of the negative sign, checking for overflow etc.

DISPLAYS

In personal calculators, particularly those designed for battery powered operation, the display poses a problem in terms of both power dissipation and cost. Older calculators almost invariably used single neon-indicator tubes for each digit. But with this type of display a high voltage power supply is required as well as drivers capable of high voltage operation. Neon indicator


prices cannot be reduced much below about £1.00 per digit, and this coupled with extra mounting and driver costs has ruled them out for new designs. In fact one of the pioneers of neon indicator tubes is phasing them out of production completely except for replacement quantities.

Those displays which are at present enjoying the most favour are multi-digit units constructed using gas discharge, light-emitting-diode or liquid-crystal technologies.

Gas discharge displays such as the Panaplex or Pandicon are favoured where large digit size (1/4" or more) is required. Up until recently LEDs (light emitting diodes) have enjoyed almost exclusive use in calculators employing digit heights of around 1/8". However they are still too expensive to be used for the larger digit sizes. More recently liquid crystal displays (LCDs) are being used as 'life' problems and ac drive requirements of these displays have been largely overcome.

The tendency now in the 'pocket'

Fig. 5. Circuit diagram of the Heathkit IC-2009 calculator kit which uses Texas Instruments MOS/LSI chips.

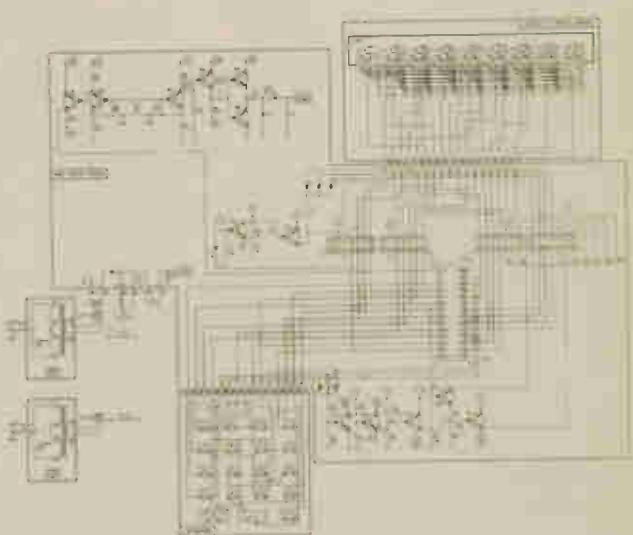

calculator field is to integrate all the display drive circuitry into the one chip together with the rest of the logic. Thus true one-chip calculators are beginning to become available.

THE SCIENTIFIC CALCULATOR

The four-function calculator, although extremely useful, has limited mathematical capability. It cannot handle very large or very small numbers, nor can it handle transcendental functions (that is, trigonometric, logarithmic, exponential etc) or in most cases even square root. Thus they are a long way from replacing the ubiquitous slide-rule.

A new class of personal calculator is now appearing, members of this family being known as scientific calculators. Typical examples are the Hewlett Packard HP35 and HP80, the MITS 7400 and the shortly to be released Texas Instruments SR10.

The block diagram of an HP35 can be seen in Fig. 7. The essential differences between this and the four-function system is the inclusion of more registers, four of which are arranged in an operational stack, much more extensive ROM to perform the transcendental function calculation, and a re-orientation of the display so that numbers may be represented in scientific notation. The 15 digit display is capable of registering and operating on numbers between 10^{-99} and $9.99999999 \times 10^{99}$, the last two digits of the display being used to represent the exponent.

Calculators of this class can be said to truly replace the slide rule. They provide an accuracy which had previously been unattainable even with seven place logarithm and trigonometric tables.

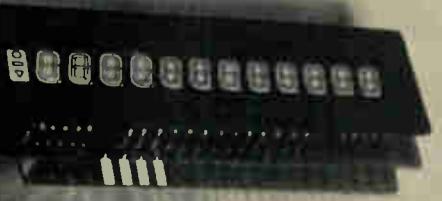


Fig. 6. Typical 12 digit calculator, the Sanyo ICC3101 uses two chip logic and a seven-segment, fluorescent display panel.

WHAT OF THE FUTURE?

In the future, we see the four function calculator remaining as a very cheap (£15 and non repairable) unit for the consumer market, and a memory will probably become a standard feature.

The pocket scientific calculator will have more models dedicated to specific branches of engineering. For example — as the HP80 is dedicated to accounting problems, we will see others dedicated to surveying, navigation, electronics etc.

No doubt for the desk range we will also see the incorporation of a cheaper printer, and plug-in programmers will also become available, at reasonable prices, which will give the calculator a capability approaching the mini-computer. Already one company has plans to introduce such a programmer for its under £250 scientific calculator. The question now arises — Now that we have all this calculating power what are we going to do with it?

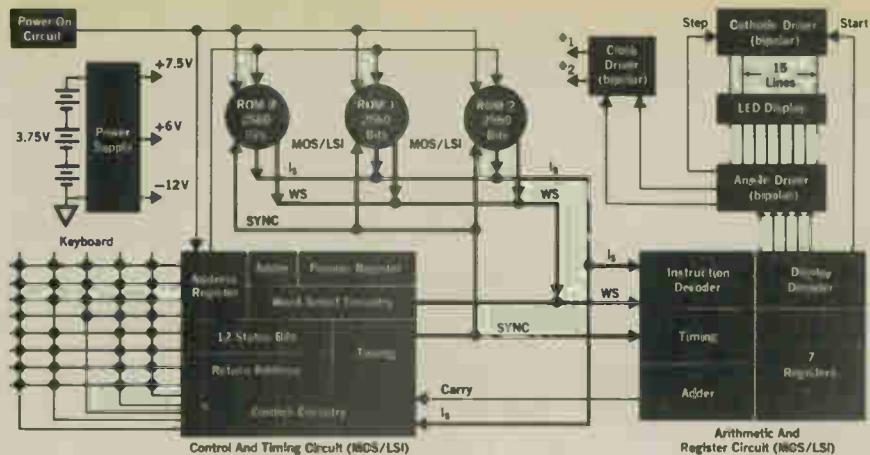


Fig. 7. Block diagram of the HP35 calculator.

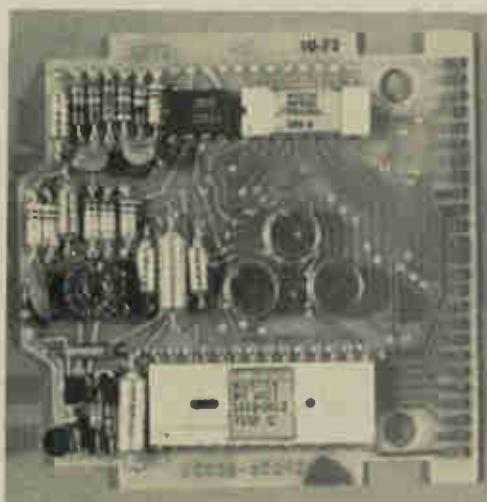


Fig. 8. Logic card of the HP35 calculator is deceptively uncomplicated in the light of the calculator's capabilities.

Fig. 9. Gold-plated keyboard contacts, display decoders and the three display chips (each with five characters) of the HP35.

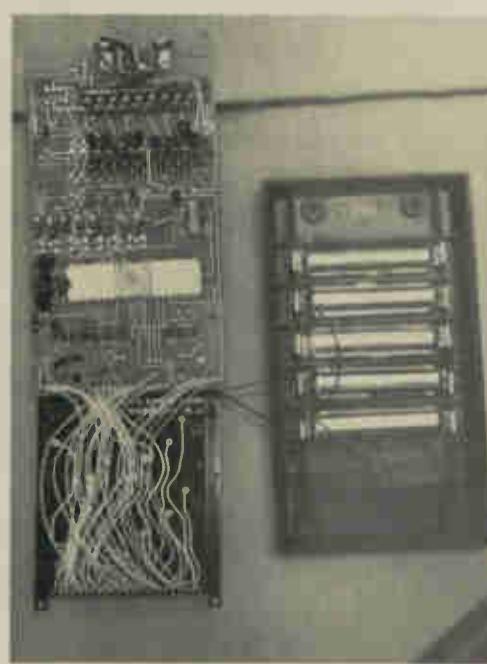


Fig. 10. (left) The Mini-Executive 8-digit calculator from Advance uses one-chip logic for fixed or floating point operation with constant facility.



Fig. 11. An alternative for those who wish to build a calculator into other equipment is this MAPS 14 digit system from National Semiconductor which has two memories, percentage and constant as well as floating or selectable fixed point operation. A version using scientific notation will shortly be available.

Transducers in measurement and control

Dr Sydenham discusses the measurement of force and related topics in this, the final part of this series.

Physical objects have a property of mass as well as size. This is a fixed value for an object (provided time has no influence). It is the magnitude of the gravitational attractions upon it that decides its weight (weight = mass gravity). An object exerts a force upon its support due to the gravitational attractions. When zero gravity exists there is no such force — articles float in outer space because the gravitational pull of the heavenly bodies is negligible. A force can also be exerted by an accelerating mass (as Newton realised with his force = mass x acceleration equation) in the absence of gravity. Gravity is but one form of acceleration. A force can also be created by devices such as springs or magnetic attractions which do not rely on acceleration or gravity.

Basically then, the weight of an object is decided by our knowledge of the gravitational pull acting on it. Fortunately, variations in gravity with time and place (on the Earth at least) are small compared with the precision needed in most commercial applications and a fixed value, or even a total disregard for it, suffices. (For example the roughly 12 hr period gravity variations due to the effect of the changing orbit of the Moon are roughly one part in 10^7 .) The standard value of gravitational acceleration is 9.80665 m/s^2 .

Units of mass, weight and force in existence are varied. The Imperial systems' pound and slug (an engineering term used for mass as opposed to weight) have been confusing to the uninitiated. The distinction between mass and weight is often not made.

Metrication now dictates the use of the kilogram kg as the mass unit and the Newton N as the force unit. As force and weight are often synonymous it has been usual practice to qualify force by the use of the letter f as in lbf but now only Newtons N and kilonewtons KN are to be used for force with the gram g, kilogram kg and tonne t being reserved for mass.

Not always is it the total force of a system that is of interest. Instead it

may be a derived quantity. Pressure is the force exerted by a distributed force on a unit area of surface. Torque is variable acting about a pivot joint that is created by a force effectively acting at the end of a lever arm.

Common Imperial pressure units are pounds per square inch, psi, or inches of mercury Hg or water H₂O. (A column of liquid exerts an absolute pressure at the bottom depending on its density and the height of the column). In the new metric system the unit of pressure is the pascal Pa (Pa = N.m⁻²). Older units were kilograms per square centimetre or metre and centimetre height of water or mercury. In meteorological measurements of atmospheric pressure the millibar mb is commonly used — weather charts express pressures of highs and lows in hundreds of millibars mb. A standard atmosphere is now exactly defined as 101.325 kPa, but millibar units will still be used in weather records. A pound per square inch equals 6.89kPa.

To further confuse the issue, vacuum pressures (those less than atmospheric in general) often use a unit 'torr' that is the pressure exerted by 1 mm of Hg at 0°C. In this range it is also acceptable to use mm Hg and uHg units. Specific mention is made of vacuum gauges for they measure low pressures by quite different methods to the above atmospheric pressure devices.

To conclude this brief resume of units there are three forms of pressure definition. Firstly it can be expressed in an absolute sense, pure vacuum being zero pressure. In absolute terms atmospheric pressure is the familiar 14.7 psia or the 101 KPa mentioned above. (Note the use of 'a' to denote absolute). Secondly, a gauge pressure can be used, psig for instance, where atmospheric pressure is used as a reference datum of zero pressure. Thirdly, pressure might be the difference between the unknown and a convenient datum pressure other than atmosphere. This is the differential pressure — psid is how it is denoted. If the pressure is stated in the column height form it could be designated as in.wg (water gauge) or inH₂O

measuring inches of water.

Torque is now correctly expressed as newton metres N·m but the many older units such as pounds force-inches, ounce-inches, dyne-centimetres, kilogram-metres and others will be in use for a considerable time to come. They should not, however, be used in newly-prepared documents describing new products.


THE STANDARD OF MASS AND CALIBRATION OF FORCE

As force, weight, pressure and torque depend on mass it is appropriate to discuss the means by which the unit of mass is standardised.

Like all standards, that of mass is man-made — there is nothing about our everyday experience of nature that is regular enough to suggest its use as a standard. The aim, therefore, has been to provide commerce and science with a certain piece of substance that is the sole mass standard. The earliest mass standard seems to be the *beqa* used by the Egyptians around 3 800 BC. It was a cylindrical object with rounded ends (perhaps to ensure no corners could be knocked off?) that weighed around 0.2 kg. It is said our Troy weight system developed from this. As civilisations flourished independently in those times there were also other standards. Today the standard is universal and is a lump of platinum-iridium that is held by the International Bureau of Weights and Measures (BIPM) in Paris. This object defines the prototype kilogram — all others are substandards and are calibrated by comparison with this.

Many modern standards are now based on atomic phenomena (a verbal definition of an apparatus enables any group to construct its own standard to the same precision without need to actually inter-compare the two — atomic phenomena give excellent results) but to date it is not possible to relate the prototype kilo with the fundamental mass unit ($1.66 \cdot 10^{-27}$ kg) to a precision equal to the current arrangements of merely weighing the unknown and the standard. Even a comparatively simple beam-balance can be used to compare similar masses to within parts in 10^9 when used with adequate precautions. If the masses are of different material the task is not so simple. Firstly, the buoyancy of each in a fluid will be different due to their different volumes, and secondly they each will have a different quantity of absorbed gas. The use of vacuum weighing to avoid the buoyancy problem only introduces a problem by removing the absorbed gas that is regained when the vacuum is released. The practical solution (standards must be a practically useful arrangement) is to compare different masses in a

Fig. 1. Calibration of force transducers (a) dead weight device; (b) balance method.

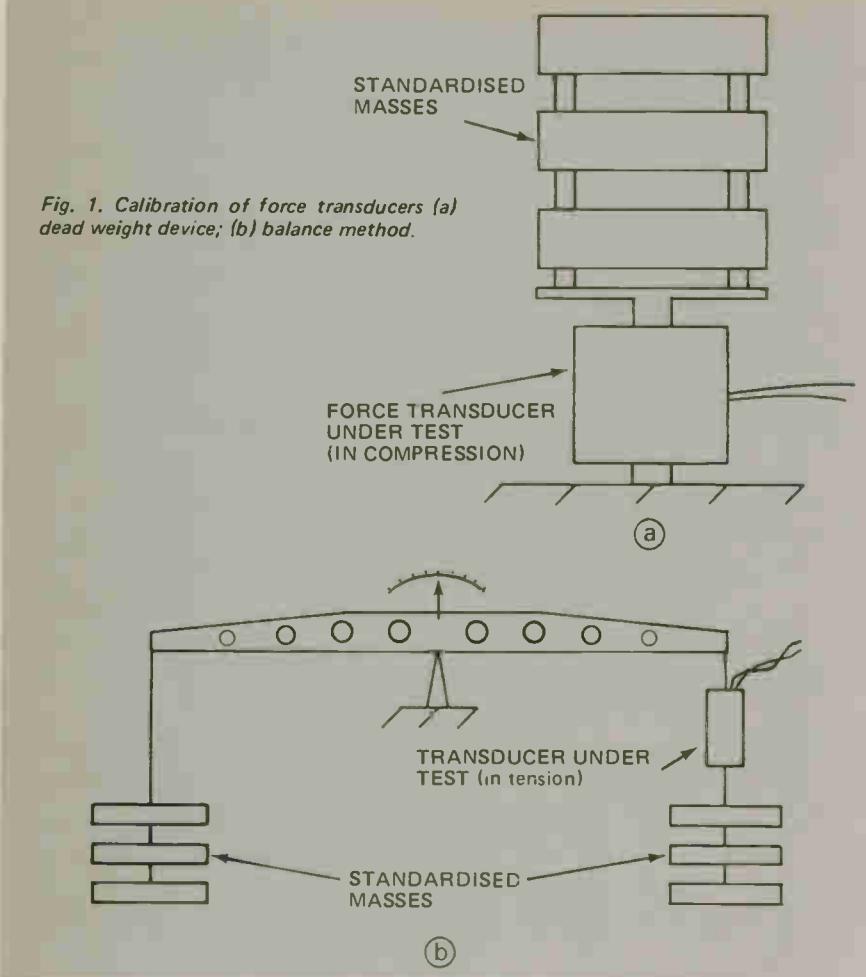

standard air pressure.

In use, a standardised mass will exert a defined force due to gravity. Force transducers are therefore calibrated by putting them in series in a force loop. The two ways of doing this are shown in Fig. 1. Deadweight testing rigs go as high in capability as 100 000 000 N. Balances usually are used to calibrate to 10 000 N.

FORCE TRANSDUCERS

The need to determine the force acting in a mechanical loop arises in the calibration of pressure transducers, in the testing of civil structures where stress levels must be known, for weighing both static and moving loads, in the testing of automatic machine-tool structures, as the basis of accurate electric current determination and in force-balance devices mentioned earlier.

Unlike other variables there are comparatively few forms of force measuring transducer. The main principle employed makes use of an elastic mechanical member that deforms proportionately with loading. A secondary output transducer monitors the resultant displacement.

The design-aims for the elastic member are to achieve a linear

movement of adequate magnitude that suits the available microdisplacement sensors. It must also have low mechanical hysteresis, a long fatigue life and be minimally influenced by environmental factors such as temperature. A few of the force sensing elements in common use are shown in Fig. 2. In each arrangement the sensor is usually placed at the position of maximum stress. Resistive strain gauges, inductive and capacitive sensors are generally used. The complete device is termed a load-cell. In some designs a solid-block is machined out to produce areas of considerably high stress to enhance the sensitivity. In the measurement of dynamic force systems a compromise must be made between the load cell spring rate (a more elastic cell gives a larger strain signal) and the sensitivity obtained (a less elastic cell results in higher resonant frequencies but gives a smaller output signal).

Piezo-electric ceramics provide an electrical output directly from the application of force across the device. During the initial period of force variation, charge will flow to balance the energy but as there is only a fixed amount of energy available for a given force distance product the

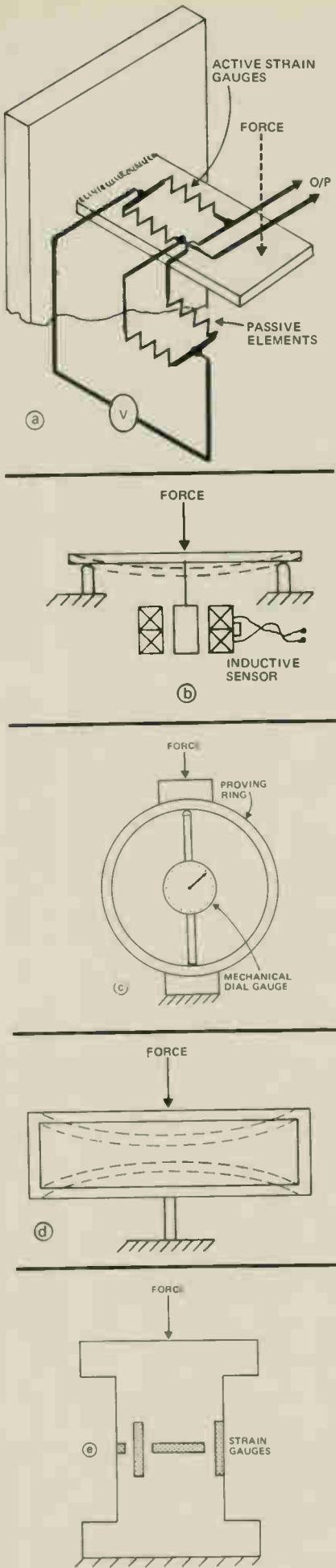


Fig. 2. Elastic elements used in force transducers. (a) cantilever; (b) simply supported beam; (c) proving ring; (d) disk cell; (e) solid or tube column.

signal eventually drops to zero. To extend the duration of the signals (to give the piezo device quasi-static performance) an extremely low-leakage amplifier is used to read the charge flow. When measuring rapidly varying alternating forces, as for instance in machine-tool vibration analysis, there is a continual energy supply and the high input impedance amplifier is not as vital. The force transducers are extremely stiff so little deflection occurs across them.

Many instruments rely on springs to provide a calibrated balancing force that can be used to measure an unknown force. There is a basic difference between such dynamic devices and force assessment by the use of weights.

The weight of an object determined by the absolute method using a beam-balance will be the same regardless of the value of gravity for both masses are equally attracted. A spring devised determination, however, will vary with gravitational changes, for the spring provides a constant force-distance relationship. (This is the basis of many sensitive gravity-meters).

CHEMICAL BALANCES

Beam balances have been in use since the earliest times and even a crude arrangement can be used to compare weights to high precision. In the 18th century the rise of research interest in

chemistry created a continual need for better balances. Joseph Black reported results of a chemical weighing to the nearest grain (0.065 gm). By the 19th century Handolt was weighing 500 gm loads to several micrograms.

The simple beam balance has been continually developed to reduce the errors in knowledge of the length of the arms, to increase the sensitivity by reducing frictional errors and to simplify the balance adjustment and reading arrangement. Modern balances often make allowance for buoyancy effects and are quite different in appearance from the traditional beam balance. Counterbalancing loads are sometimes applied by front mounted knobs and this provides for simple use and direct readout of value.

Microbalances measure small loads to micrograms resolution, (they are, however, not often small in size). Most make use of a fine torsion-fibre or ribbon suspension that is twisted by the load. To determine the exact load, a counter-torque is applied to rezero the beam. Figure 3 is schematic of a commercial electro-balance. The sample is placed in one pan and a roughly equal weight in the other. To achieve balance the current in the coil is varied until the photocell displacement detector receives a standard illumination level. The process is easily automated to follow changing weights. A recently developed microbalance makes use of a magnetic field suspension system to support the load without mechanical restraint. The field-coil current needed to establish position balance is a measure of load. Modern microbalances can resolve weights of less than a microgram.

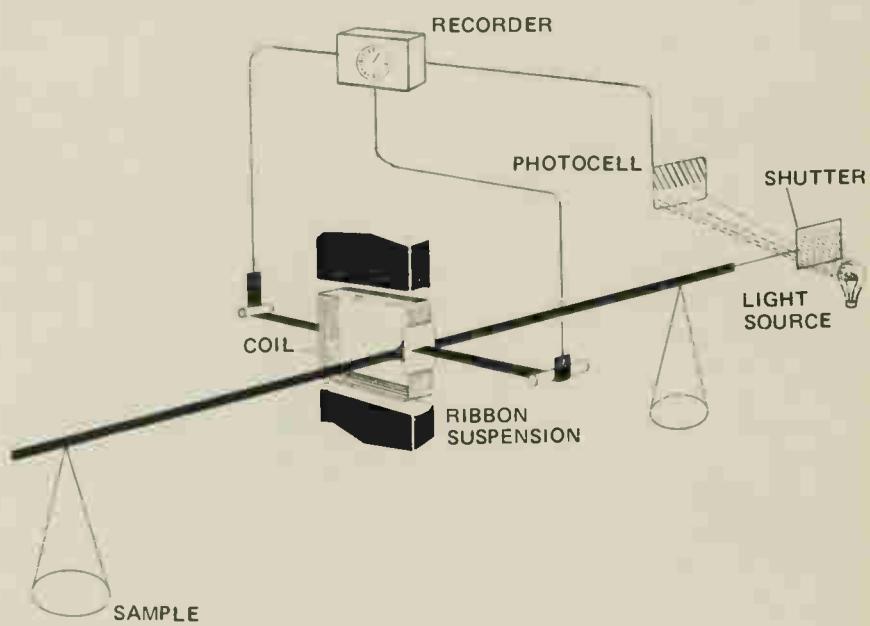


Fig. 3. Schematic of the Cahn electro-balance.

Transducers in measurement and control

DYNAMIC WEIGHING

An automatic readout weighing machine consists of a platform operating on effectively frictionless pivots that bears down upon a load-cell. Details of a commercial unit are shown in Fig. 4. If the load is stationary, the reading is reliable, but a moving load, such as an animal or a travelling string of goods wagons on a railway or material on a conveyor belt, will produce a more complex signal such as that shown in Fig. 5. Averaging the value eliminates the fluctuations about the true mean but to obtain a fast response more sophisticated adaptable filtering is used. The power of such methods is shown by stating that a simple R-C low pass filter gives 200 times greater error than a weighted averaging method (patented by Avery) when used in an equal, short-time period.

PRESSURE SENSORS

The range of pressures that exist is vast and ranges from tens of megabars (10^8 atmospheres) down to inter-stellar space pressure (10^{-19} atmospheres). Consequently many techniques are used to suit the range.

As with force transducers the commonest procedure uses a mechanical elastic element coupled to a microdisplacement transducer. The main difference is that pressure transducers usually do not need the stiffness essential in force sensors.

Commonly used sensing elements are shown in Fig. 6. The limiting factor is usually the magnitude of mechanical hysteresis and perhaps bearing friction in the simpler devices.

The most general need for accurate pressure measurement around an atmosphere is for weather mapping and for elevation determination (barometric levelling). The aneroid barometer uses a stack of bellows to drive a pen or transducer. The best resolution instruments are termed microbarometers. The schematic of an advanced instrument is given in Fig. 7. Note the quartz helical bourdon tube that is used because of the excellence of its stability and spring-rate. Microbarometers have been used to detect the pressure surges caused by nuclear test explosions on the opposite side of the globe.

Pressure sensors using an elastic element are not absolute and must be calibrated against those using a head of liquid as a reference, or by the use of dead weights driving a piston filled with liquid.

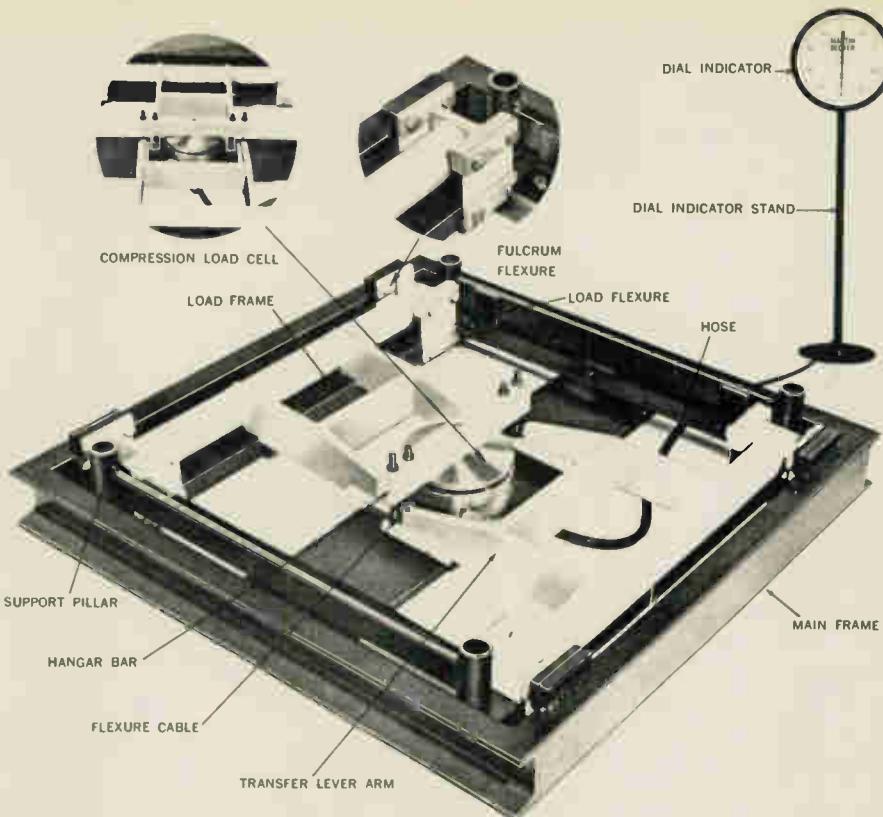


Fig. 4. Inside details of a Martin Decker deck scale.

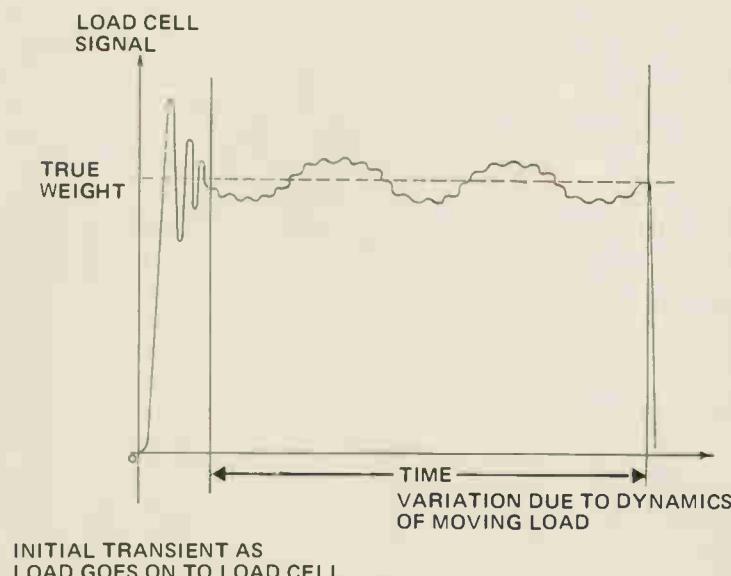


Fig. 5. Typical weighing signal produced by rolling stock passing over a battery of load cells.

The standard mercurial barometers, of the Kew or Fortin pattern, are devices in which the height of a mercury column is measured against a mounted scale. If the column is coupled to the pressure within a closed system via a pipe it is termed a manometer. These are used in abundance in hydraulic research as readouts for pressure difference flow meters and in aerofoil section investigation. Chemical reactions often must be monitored under precisely known pressure conditions.

Manometers used in this work are often made more precise by electrically sensing the position of the top surface of the column. Auto tracking inductive sensors, such as that given in Fig. 8, and capacitive or optical sensing have been employed to resolve to micrometers. One micromanometer measures the surface height with an optical interferometer that looks at the mercury surface from above.

An analog output signal may be undesirable from a pressure sensor. A

Transducers in measurement and control

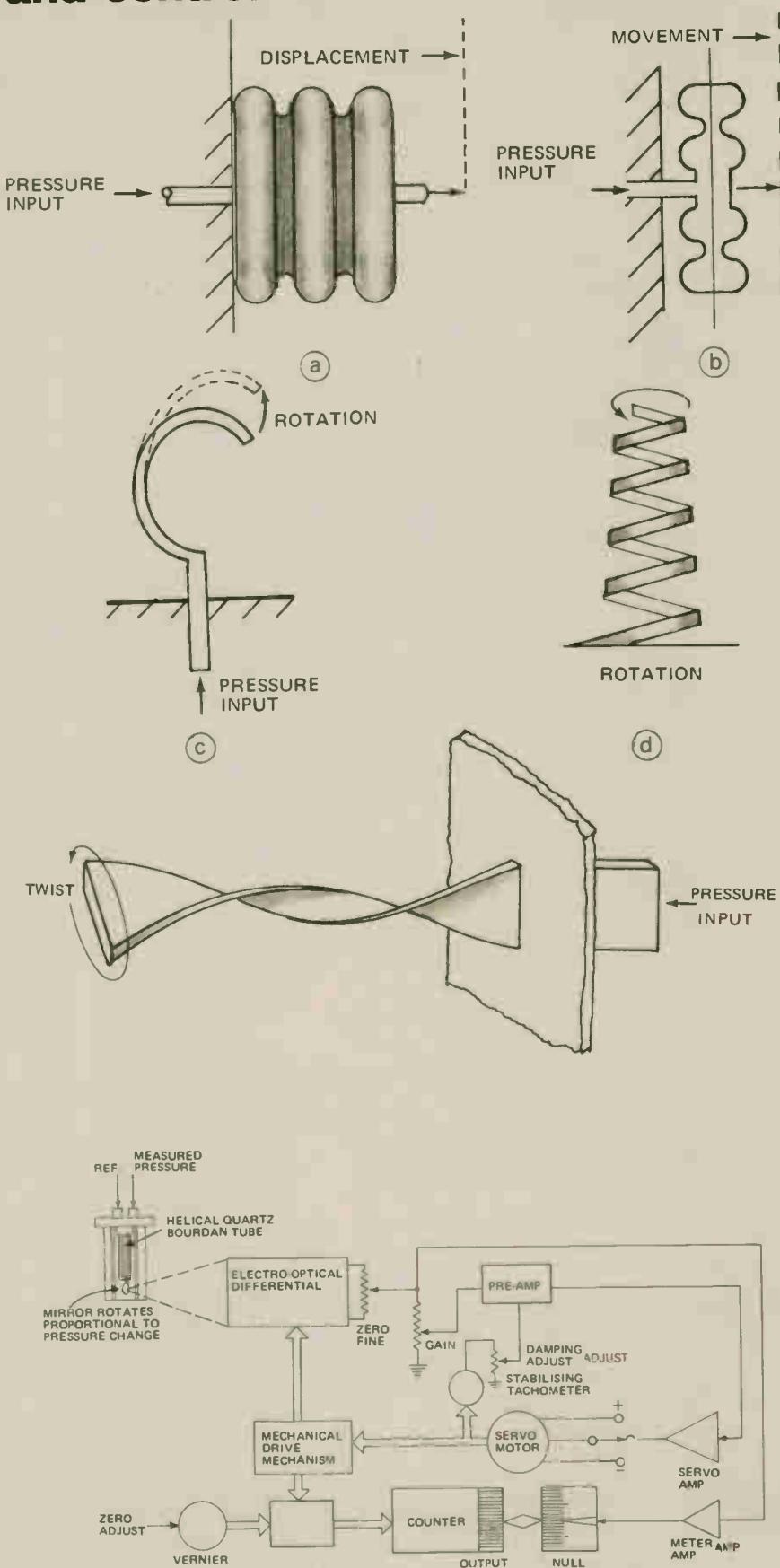


Fig. 7. Block diagram of the Mensor helical quartz pressure sensor having digital readout to 0.0005% of full scale.

sensor developed at the Royal Aircraft Establishment uses the force-balance technique in an oscillatory mode. From the schematic of Fig. 9 it can be seen that the driving coil forces the diaphragm against the pressure, opening the contact. This in turn de-energises the electrodrive, setting the system into vibration. The average duration of the contact dwell is the measure of pressure. This form of transducer can provide a time-duration modulated signal that is easy to transmit due to its binary nature.

Another transducer derives a frequency modulated output by monitoring the natural resonance of the sensing diaphragm. An electromagnetic excites the diaphragm. A capacitive sensor monitoring the displacement is coupled to the excitation driver and the two oscillate at the resonant frequency. As pressure changes so does the frequency.

VACUUM PRESSURES

From 1 mm Hg (1 torr) to an atmosphere is low vacuum, from 10^{-3} mm to 1 mm is medium vacuum. High vacuum extends from here down to

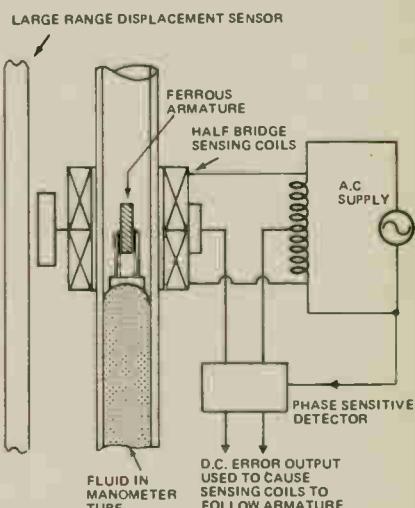


Fig. 8. The height of the liquid column is measured by slaving the detecting coils to follow the armature in this servo-manometer.

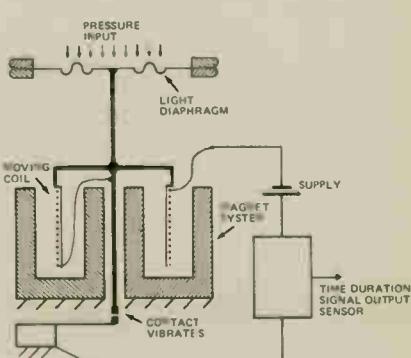


Fig. 9. Schematic of the RAE vibrating-contact pressure transducer.

10^{-6} mm, very high from 10^{-9} to 10^{-6} mm. Ultra-high vacuum is a pressure less than 10^{-9} mm of Hg. Mechanical pressure gauges are often capable of measuring to 10^{-3} mm Hg but for better than low vacuum it has been necessary to employ quite different methods.

For the pressures of 10^{-4} mm Hg upward, the simplest vacuum gauge is the thermo-conductivity unit. The heat transfer from a heated sensor depends upon the mass of gas thermally coupling it to the container heat sink. The lower the vacuum the less the transfer. Earlier designs used a purely resistive sensor connected to a Wheatstone bridge to monitor its temperature via its resistance change — see Fig. 10, and this is commonly called the Pirani gauge. Another variation uses a thermocouple to measure the temperature. The most recently introduced models make use of a thermistor sensor instead. In this range the McLeod gauge — a type of manometer, provides an absolute method.

Below 10^{-3} torr, ionization gauges are used that rely on the ionization of the gas molecules to determine pressure. In the hot filament kind a heated cathode provides electrons that are accelerated by a grid to make impact on an anode, providing ions in the process. (The design is similar to a triode valve.) Positive ions are collected by an electrode and the ratio of ion to electron current is a measure of gas pressure. The Bayard-Alpert configuration, shown in Fig. 11a, has a small collector to reduce errors from unwanted soft X-ray generation. The anode collector can be replaced by an electron multiplier and versions using this can detect 10^{-18} torr pressure changes.

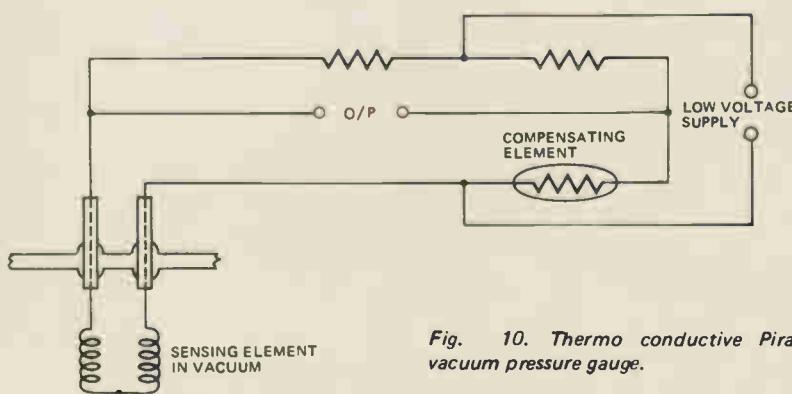


Fig. 10. Thermo conductive Pirani vacuum pressure gauge.

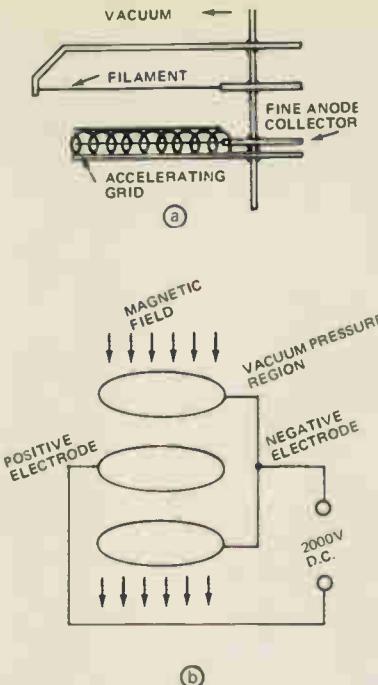


Fig. 11. Ionization gauges used to determine vacuum pressures. (a) This Bayard-Alpert sensor uses a hot filament; (b) In the Penning gauge a cold cathode is used.

The Penning, or Philips gauge, shown in Fig. 11b, is a cold-cathode, magnetic field, ionization pressure sensor. A discharge current is established by the application of 2000 Vdc between the anode and cathodes. The purpose of the magnetic field is considerably to lengthen the electron path (it makes them travel in a helical locus) enhancing the chance to form ions. The current drawn is the sum of electron and ion currents and is, therefore, not a linear measure of pressure. These are useful in the range 10^{-7} to 10^{-3} torr. The cold cathode is often preferred, for an unintentional vacuum loss will not destroy the cathode as would the heated version.

For pressures below 10^{-7} torr there are other methods. The Redhead gauge is also a cold cathode, magnetic, instrument but the internal layout is

different being based upon the Magnetron. It has the advantage of giving a linear ion-current to pressure relationship down to at least 10^{-10} torr.

The Knudsen radiometer gauge is occasionally used and is the only absolute method for the range 10^{-8} to 10^{-2} torr. A small mirror is suspended in the vacuum by a torsional filament that also supports a moving paddle-vane. Fixed close to the moving vane ends are two others that are heated. The momentum of the gas molecules passing near the heated plates causes them to bombard the unheated vane deflecting it in proportion to the gas mass present. The mirror forms part of an optical level readout.

SOUND MEASUREMENTS

Acoustic propagation involves pressure wave travel. The above mentioned pressure gauges are of little value for sound pressure measurement due to the high frequency low pressure characteristics of sound waves. The detector, therefore, (the microphone) is designed to have a bandpass response including the frequencies of interest. Generally microphones have to couple an air medium so a comparatively compliant diaphragm is used to obtain an efficient acoustic match. Motion is transduced with a displacement sensor. Microphones in use use piezo-electric crystal, capacitance and moving-coil principles.

When making sound-level

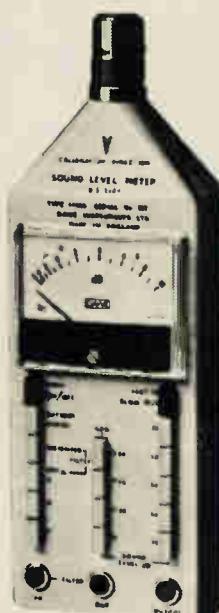


Fig. 12. The Dawe Sound level meter.

measurements it is necessary to use specially designed meters, Fig. 12. In these a stable characteristic microphone produces a basic pressure

Transducers in measurement and control

signal. This is processed to allow for the random-like nature of sounds and for the frequency characteristics of the human ear.

By definition a sound level pressure (SPL) of 0dB is 0.0002 ubar this being the lowest discernible level for the ear (the pressure is 10^{-9} psi!). The compensated noise-level (that makes allowance for the frequency response of the ear) is expressed as the effective perceived noise level EPNL. The threshold of pain occurs at 144dB. At 4 km. Concorde 002 produced 120 EPNdB. The loudest noise produced is probably that generated by the NASA 50ft steel and concrete horn - 210dB which is 400 000 acoustic watts! (Don't tell any pop groups! - Ed).

TRANSDUCING TORQUE

Torque is the product of a force acting at a distance, so for static shaft measurements a torque transducer is little more than a load cell driven via an arm (as shown in Fig. 13a). As the shaft is constrained it is not of any value for measuring rotating shaft torques.

A simple way to monitor the rotating shaft is to fix a strain rosette at 45 degrees to the axis (for this is the maximum stress direction) and connect the gauge to the bridge via slip rings as shown in Fig. 13b. Mercury-wetted rings have been used for extreme rotational rates; monitoring at 30,000 r.p.m. is quite feasible. A more sophisticated arrangement is shown in Fig. 14. Power to excite the bridge is induced by magnetic means, thus avoiding the problems associated with sliprings. A similar approach is to mount the power supply on the shaft along with the circuits and radio-telemeter the output. This has the advantage that the sending receiver and transducer needs no rigid position tolerance. It has been used in the measurement of tail-shaft torque in automobile research.

When the rotation is constrained, as with bearings at each end, a phase difference method can be employed. Detectable 'marks' (for inductive, capacitive or optical sensing) are mounted around the shaft at two points as shown in Fig. 15. Fixed proximity sensors generate two alternating waveforms which will have the same frequency but a varying phase-difference depending upon the amount of twist in the shaft. (This

method is similar to a shaft encoder principle described in the earlier discussion on angle transducers). The major disadvantages are that there is no output when the shaft is stationary and that the frequency at which the phase comparison must be made varies with speed.

FURTHER READING

"Handbook of Transducers for

Electronic Measuring Systems" H.N. Norton, Prentice Hall, 1969.

"Measurement Systems: Application and Design" E.O. Doeblin, McGraw Hill, 1966.

"Weighing Vehicles in Motion" A.C. Ferguson, Trans Inst. M.C. 1969, 2, 12, 214-222.

"Development of the Chemical Balance" J. T. Stock, Her Majesty's Stationery Office, 1969.

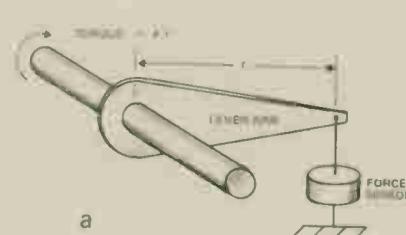


Fig. 13. Torque measurement. (a) Load cell and lever suffices if rotation is not needed; (b) Slip-rings enable the shaft to turn whilst monitoring torque.


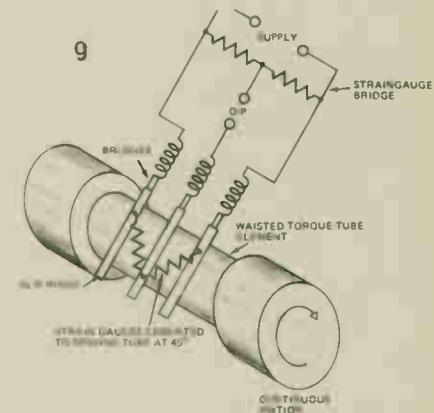


Fig. 14. This Philips torque transducer supplies power and monitors the output of a strain gauge bridge via a new contact inductive coupling head.

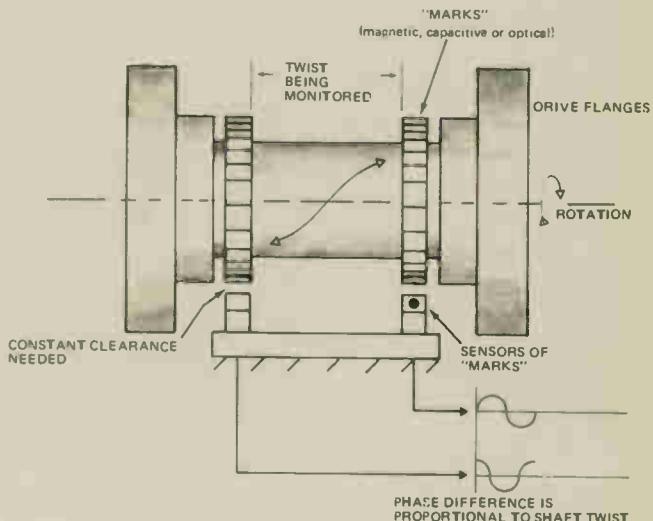

Fig. 15. Measuring the torque of a rotating shaft by the phase difference method.



ESSENTIAL BOOKS

THE MODERN DICTIONARY OF ELECTRONICS. Contains concise definitions of more than 18,000 terms in electronics, communications, micro-electrics, fibre optics, semi-conductors, computers, medical electronics. Fully illustrated. Essential to any collection of electronics reference books. Ideal for workshop and laboratory. £6.50 post free.

HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION. Only 40p. p.p. 10p.

HANDBOOK OF BASIC ELECTRONIC EQUIPMENT. Gives specific details of the components and equipment used in Radio, Television, Tape-Recording, Record Playing, Short Wave Listening, Amateur Radio. Enables you to choose the best components and accessories and use them economically and safely. Illustrated. £1.75 post free.

RADIO HANDBOOK. Latest impression. 974 pages. W.I. Orr. 19th edition. A comprehensive communications handbook written especially for the radio enthusiast and electronics engineer. Includes every aspect of radio likely to be of interest to the constructor and amateur. Contains the latest designs and developments. £7.50 post free.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuits data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. With modifications to sets and test equipment. Latest impression £3.25 including postage.

DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS. Gives details of surplus wireless equipment stores and dealers including addresses, plus equipment and spares that they are likely to have available. A valuable book only 40p. p.p. 10p. Allow 28 days for delivery as directory is being brought up to date.

99 WAYS TO IMPROVE YOUR SHORTWAVE LISTENING. Essential to all SWLs. £1.90 post free.

PERSONAL CALLERS WELCOME AT OUR NEW SHOWROOM & TRADE COUNTER. Hartleys Yard, Off Town Street, ARMLEY, LEEDS 12. Just past The White Horse Inn. The North's largest selection of Radio and Electronics Books plus thousands of books on all subjects at discount prices.

PROBLEMS IN ELECTRONICS WITH SOLUTIONS. A must for student, technician, and electronics engineer. Contains 349 problems, answers and how they were arrived at. Includes all aspects of electronics, amplifiers, power supplies, computers, aerials, waveguides, transmission lines. 307 pages. Only 90p. p.p. 10p.

COSMIC RADIO WAVES. Start a new hobby - RADIO ASTRONOMY. This big book of 444 pages is an ideal handbook for the beginner and established enthusiast. Numerous photographs and illustrations. Published by Oxford University Press. Price £2.50. p.p. 25p.

THE SCATTERING AND DIFFRACTION OF WAVES. A goldmine of information for the experimenter, amateur and scientist. Profusely illustrated. Published by Oxford University Press. Price £1.60 post free.

TRANSISTOR SUBSTITUTION HANDBOOK. Gives the substitutes for thousands of European, American and Japanese transistors. Where no substitute is available shows how to select a replacement. Includes over 10,000 types. £1.40 post free.

HANDBOOK OF SATELLITES AND SPACE VEHICLES. A comprehensive working handbook that provides important data both tabular and graphical enabling space scientists, technicians and telecommunication engineers to acquire a greater working knowledge of satellite and space vehicle design, launching, orbiting etc. Includes a detailed coverage of COMMUNICATIONS IN SPACE. An imposing book of 457 pages. Published at £8.20. Available at the trade price of £6.50 post free.

All mail order to: Dept. ET2, GERALD MYERS (Book-seller & Publisher), 18 SHAFTESBURY STREET, LEEDS LS12 3BT. Callers welcome to new showroom address shown in advert.

THE HIGHEST PERFORMANCE DIGITAL FREQUENCY COUNTERS AT THE PRICE IN THE WORLD
EVERYBODY BUYS THEM



301 5 DIGIT 32 MHz
STABILITY 3 parts in 10⁸
SENSITIVITY 50mV

£75



401 6 DIGIT 32 MHz
STABILITY 1 part in 10⁸
SENSITIVITY 10mV

£110




501 8 DIGIT 32 MHz
STABILITY 3 parts in 10⁸
(crystal oven)
SENSITIVITY 10mV

£160



701 8 DIGIT 50 MHz
STABILITY 3 parts in 10⁸
SENSITIVITY 10mV

£170

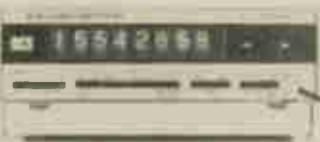

801A 8 DIGIT 300 MHz
STABILITY 3 parts in 10⁸
SENSITIVITY 10mV

£260

PRICES EXCLUSIVE OF VAT
ELECTRONIC START/STOP version PLUS £10
MEMORY version PLUS £25
DIRECTLY COUPLED INPUT AND SPECIALS TO ORDER

Write for illustrated leaflet.

*Supplied to and acclaimed by professional engineers everywhere
who have purchased our electronic instruments for the
past 10 years.*

Norwegian Agent: ELECTRO-TRADE, TRONDHEIM, NORWAY.



R. C. S. ELECTRONICS
NATIONAL WORKS, BATH ROAD,
HOUNSLAW, MIDDX. TW4 7EE
Telephone: 01-572 0933/4

electronics tomorrow

Are you reading this magazine whilst you are lazing in a deckchair with the sun blazing down on you? Perhaps you are reading it in a hot crowded train or bus on your way to or from work, or even at work? In any case it is a bit difficult to imagine the darker evenings to come in only a couple of months, those beautiful evenings spent over a hot soldering iron and birds-nest wiring. Perhaps we can help you plan those evenings with some of the products we have this month. As the first Electronics Tomorrow article has not been published whilst this is being written, we are a little short of response from manufacturers, etc. on new products but we have enough for this month so lets get on with it.

LSI TIMER CIRCUIT


Many of you may have seen this on *Tomorrow's World* in May, set up to demonstrate its ability to run the house whilst you are away by switching on lights, air-conditioning, etc., to deter burglars. It was also mentioned in the July ETI but we have chased up a bit more data for this column. It is the LR171E made by Ferranti for Eremco for long or short term accurate timing pulses. Eremco are in the timer business already and have made their name with mechanical timers, the introduction of a solid state timer is an obvious move from which the amateur might benefit.

An integral operational amplifier is used to form a relaxation oscillator with an externally adjustable timing period. These pulses are passed to a counter chain capable of dividing by 4096, this means that a pulse width of, say, one second produced by $1\mu F$ can be converted to a pulse width of just over one hour, the alternative method of using $5000\mu F$ in the original CR network would be bulky and also unreliable in temperature and humidity changes. A digital-to-analogue converter on the chip may be used with a meter to show how much of the timing period has elapsed... just think of the applications for that alone. A total of five driving outputs are supplied A and \bar{A} at 4096, Q_{12} at 2048, Q_{11} at 1024 and Q_{10} at 512 input pulses, these can be combined to give eight switching periods each one eighth of the main period.


One of the most interesting parts of the data sheet on this device is the supply current at typically $5mA$ for battery operation or, if you want to run it off the mains, do so: the supply voltage reads min. $6V$, typical $12V$, max (this is not a printing error) $450V$ d.c.! Just think of the hours spent getting $5V$ d.c. ripple-free and stabilised a $5V$ for other ICs, one of my pet moans is transformer sizes but perhaps they won't be needed in future? Data and devices (1).

$$555 + 555 = 555$$

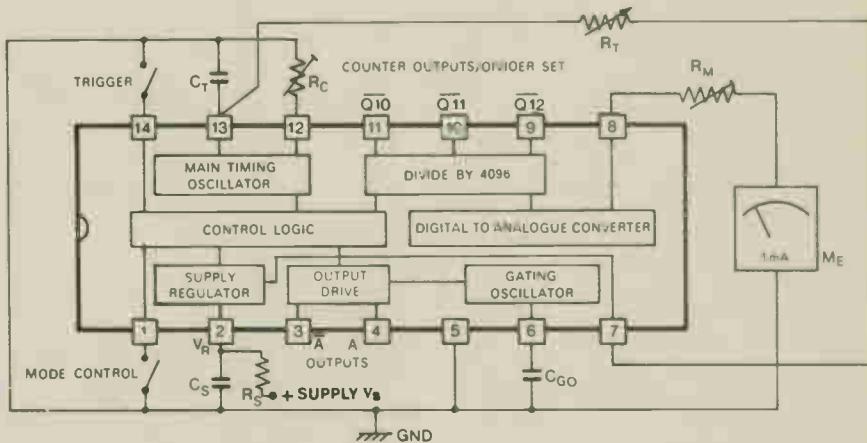Or to put it another way two 555's are now a 556. The Signetics 556 is a fourteen-pin IC containing two 555 timers, no data or prices



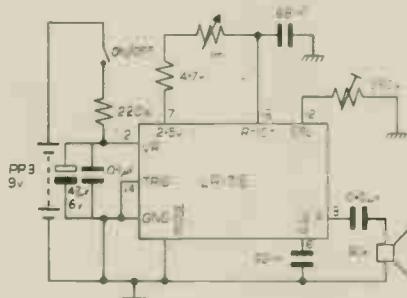Internal arrangement of the LR171E made by Ferranti for Eremco



Battery-operated general purpose timer, 2 seconds - 5 minutes. The gating oscillator is used as a drive for a speaker which sounds at the end of the timing.

were available from Signetics at the time of writing as the device is not scheduled for release until October. Similarly no prices have been set at present but it seems unlikely that the 556 is going to be twice the price of the 555. If you haven't yet become familiar with the 555 type of timer it would be a good idea to do so, these devices are going to be as popular as BC109s in circuits in a few months.

The 555 timer can function as the heart of an automatic battery charger. The circuit is intended to maintain full charge on a standby battery supply for an instrument that is not always connected to mains supply. These kinds of instruments usually use NiCD batteries or similar, the battery charger is typically for calculators, DMMs, etc. The zener diode provides a reference voltage for the two on-chip comparators through the timers internal resistive divider network. Calibration is done with known voltages across the battery terminals and OFFadjusted

to the high (ie stop charging) voltage and the ON to the low voltage, with NiCD cells these are typically $1.2V$ and $1.4V$ per cell. The timer output in this circuit switches between 0 and $10V$ d.c. R_1 is used to limit the current and D_2 blocks the batteries discharging through the 555.

In the second circuit two 555's or one 556 are used to produce an inexpensive burglar alarm for the car or home. The first 555 produces a time delay of, say, five to ten seconds to allow entering and leaving; turning off the ignition causes $12V$ to be connected to the timer, opening the driver's door (or similar microswitch) connects the timer trigger to ground and thus starts the delay timing. The second timer is able to trigger as soon as the delay is complete, the trigger of the second 555 is held high until one of the sensing microswitches is closed, these could be under the driving seat or connected to one of the car functions. The output from timer two could be fed via a relay to the car horn or lights. Two alarm enable switches are shown although only one is required, the one on the ignition is for the lazy owner who forgets that his car is "alarmed" and works on the principle that if the car alarm goes off the last thing a thief is likely to do is switch on the ignition. Anyway they are two new circuit ideas to play with, if you have any more let us at ETI know, they might be worth publishing.

555, 556 Data: 2, 555 chips: 3.

WILLIAM TELLS ALL!

Having mentioned our William we could either go on to apples or arrows, it happens to be Arrow's catalogue. Arrow Electronics Ltd is a mail order firm working from Brentwood, Essex, their catalogue arrived recently and it proved to be quite interesting as catalogues go. The first few pages list

semiconductors and prices; all popular transistors and IC's are stocked. Similarly, several pages are devoted to capacitors, knobs, other hardware, rectifiers, resistors, diodes, and switches. Some of the more interesting products stocked are RCA COS-MOS logic circuits, IC mounting pins (DIY sockets), Motorola IC's (MC1303, 1310), some thick film circuits, opto devices and ultrasonic transducers. One of the thick film devices, the NMC457, is a 75db gain amplifier requiring only a 9V supply, microphone and 300ohms headphones. It is stated as being suitable for hearing aids, null detection process amplifiers and sensing applications. The price is £3 (plus VAT), quite reasonable.

Catalogue: 4.

NUMBER CRUNCHER

This is the name given to the Texas TMS0117 LSI chip announced recently. Basically it can be imagined as a ten-digit calculator chip but, instead of keyboard inputs and seven-segment outputs, data are entered and extracted in BCD format allowing interface with other ICs and thus enabling the TMS0117 to become the heart of a complex device. In addition to the formal calculator operations this will add 1, add 1 until overflow, subtract 1 to zero, shift left, shift right and exchange operands. The rather vague data received so far states that the chip can be used so that "special purpose, dedicated, processing systems can be constructed at ridiculously low cost." Unfortunately the low cost would need to start with the £26.50 required for the one-off price of the chip. It would seem reasonable that manufacturers of these kind of chips would make a limited number available to schools, clubs, etc, one day it might pay off with genius designs/designers in the future. In the meantime: Data from : 5,6, Chips from 5.




The Texas TMS 0117; it feeds on numbers but at which end?

Whilst on the subject of Texas Instruments and data on their devices some readers may be interested to know that they run a subscription service enabling you to receive data sheets, books, etc, as they become available. The author joined this service about a year ago for £6 and has received about 9 data books, 20 booklets and numerous data sheets but is, however, still waiting for the TMS0117 data booklet. For details of the service write to: 'Subscription Service' at 6.

MORE TIMERS

In addition to second sourcing the Signetics timer with the LM555, National Semiconductors have another timer the LM322. This is a precision timer that offers great versatility with high accuracy, operating voltages are 4.5V to 40V unregulated. The output of the timer is a floating transistor with built in current limiting. It can drive ground referred or supply referred loads up to 40V and 50mA. The floating nature of this output makes it suitable for interfacing, lamp or relay driving, and signal conditioning where an open col-

Simple Slot Together Method of Assembly

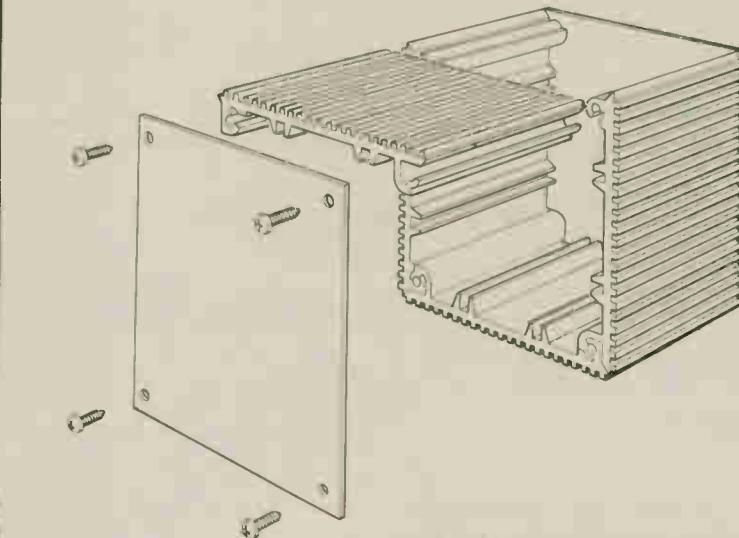

No: 4 self tapping pozidriv screw.

Construction and assembly of the clever new Veroboxes

lector or emitter is required. The trigger input has a threshold of 1.6V independent of supply voltage but is fully protected against inputs as high as plus or minus 40V, even when using a 5V supply. An internal 3.15V regulator is included in the timer to reject supply voltage changes and to provide the user with a convenient reference for applications other than a basic timer. External loads up to 5mA can be driven by the regulator. An internal 2V divider between the reference and ground sets the timing period of 1 R/C. The timing period can be voltage controlled by driving this divider with an external source through the Vadj pin, timing ratios of 50:1 can be achieved.

The data sheet received on this device is beautiful, for a start it contains full data, electrical characteristics, performance graphs (12 of them), schematic diagram, definition of terms and 14 application examples.

Price of the LM322 is £2.50.

Data: 7, Devices: 3, 8.

BUILD IT YOURSELF BOXES

As mentioned earlier, one of my pet moans is transformer sizes, another is casing. The aluminium boxes, plastic boxes and die-cast boxes available are all very well as long as they are not to be seen. So far no manufacturer has taken a production case for a clock or calculator or even anything non-electronic and made it available to the public and thus if you need to house something attractively there is no alternative but to make your own metal, plastic or wooden case which, if your handiwork is anything like mine, finishes as a mess if it finishes at all. Now Vero have introduced a range of plastic cases and a range of extruded aluminium cases, the latter are called Veroboxes. These Veroboxes are based on a finned aluminium unit 50mm wide and in units of 25mm deep from 25mm to 200mm. The units slot together and screw to an end plate to give an attractive range of boxes that can be left in the raw or sprayed with paint (matt black is very effective) or anodised, etc. Two types of extrusion are used, a corner joint and an extension joint, thus a 50mm cube would use four 50mm deep corner jointed extrusions and two 50mm high, 100mm wide

and 75mm deep would use 75mm deep extrusions, four corner joined and two extension jointed plus two 50mm by 100mm end plates. The boxes come in a plastic wallet with extrusions, end plates and screws, they are ordered by quoting the end plate dimensions and then the depth, thus our two examples are a 50-50/50 and a 50-100/75.

Out of eighty standard Verobox kits available to industry, Vero have released only six kits for retail, a telephone call to Vero confirmed that they are quite willing to deal with direct orders for any of the other 74 kits at industrial prices. They also said that they might extend the retail range if the demand is large enough, so here's your chance to affect future product availability. The kits available and their prices (exclusive VAT) are listed below, the first six are the retail kits and the rest are examples of the industrial kits.

50-50/50	49p	50-50/25	40p
50-100/50	73p	100-100/50	98p
100-100/75	117p	100-150/50	125p
50-100/100	91p	100-100/125	140p
50-150/200	187p	200-200/200	401p

If ordering direct from Vero don't forget to add VAT and about 5% for carriage and packing charges. Data and cases: 9. It is also worth asking about the range of plastic cases.

REFERENCES

- 1 Electrical Remote Control Co. Ltd. P.O. Box 10, Bush Fair, Harlow, Essex CM186LZ
 - 2 Signetics International, Yeoman House, Croydon Rd, London SE20
 - 3 Bywood Electronics, 181 Ebbens Rd, Hemel Hempstead, Herts.
 - 4 Arrow Electronics Ltd. 7 Coptfold Rd, Brentwood, Essex.
 - 5 SDS Components Ltd. Hilsea Trading Estate, Portsmouth, Hants PO3 SJW
 - 6 Texas Instruments Ltd. Manton Lane, Bedford, Beds.
 - 7 National Semiconductors (UK) Ltd. The Precinct, Broxbourne, Herts.
 - 8 Atlantic Components Ltd. 143 Loughborough Rd, Leicester LE4 5LR
 - 9 Vero Electronics Ltd. Industrial Estate, Chandler Ford, Hants SO5 3ZR
- NB. Please note that all prices exclude VAT and carriage.

From ITT.

A completely new kind of changeover relay.

**Don't let its size
fool you.**

We've recently developed a changeover relay quite unlike any other on the market. It's called a diaphragm relay and offers almost exactly the same performance as a mercury-wetted relay yet is smaller in size. And a lot smaller in price!



Distributor quantities available
from ITT Electronic Services, Harlow 26777

Take a look at these outstanding features.

- ★ Hermetically-sealed precious metal contacts.
- ★ Switching capability of 30W.
- ★ Max. current and voltage contact ratings are 500mA and 150V. a.c./d.c. respectively.
- ★ Coil voltages (d.c.) 6, 12, 24 and 48V.
- ★ Withstands high levels of shock and vibration. From 50Hz to 5kHz and acceleration of 100g.
- ★ Pins provided for direct-mounting onto 0.1 in. module printed circuit boards.
- ★ Dimensions:
26.25mm x 12.5mm x 11.5mm.
Phone Harlow 26811 Ext. 642 now for more information.

ITT Components Group Europe,
Electro-Mechanical Product Division,
Edinburgh Way, Harlow, Essex. CM20 2AQ.
Telex : 81146.

Components **ITT**

J-BEAM F.M. 6S THE OUTSTANDING BRITISH ENGINEERED F.M. AERIAL STILL UNRIVALLED IN ★ PERFORMANCE ★ QUALITY ★ AND PRICE ★



20 Miles Radius
Professional Installation Service

We also stock the new broadband J-Beam F.M. 4S, 1, 2, 3, element F.M. arrays high performance A.M. vertical rod aerials, all U.H.F. T.V. aerials, Stolle Memomatic and Automatic aerial rotators, balanced twin feeder, coaxial cables, masts, fixings, amplifiers, baluns, and a host of other accessories. Please send large S.A.E. for catalogue to:

APOLLO AERIALS, STATION FORECOURT, GUILDFORD STREET, CHERTSEY, SURREY
TEL CHERTSEY 60320 and BYFLEET 43151

FASTEST IC FET OP AMP

National Semiconductor now claim to make the industry's first really fast - and really easy to use - IC FET-input operational amplifier. The new LH0062/LH00620 is an order of magnitude faster than conventional IC FET amplifiers, yet it plugs directly into standard monolithic amplifier sockets to solve system performance problems immediately.


The circuit contains a monolithic dual JFET chip and a specially designed bipolar op amp similar to the LM118. National's interdigitated dual JFET design assures tight input matching. Typical offsets are 2mV and 1pA.

No external components are required for operation, since the amplifier is internally compensated, compensation and balancing can be added, if desired. Speed ratings with normal compensation are 15MHz bandwidth 70V/ μ s slew rate, and 1/ μ s settling time to 0.1%. Feedforward compensation almost doubles the speed, while an extra capacitor lowers settling time.

Gain is 100V/mV and noise currents less than 0.1pA rms. Other characteristics are similar to those of quality monolithic amplifiers. The supply range is $\pm 5V$ to $\pm 20V$. The LH0062 is specified over the full military temperature range.

Both are available in 8-pin TO-5 and 14-pin dual in-line packages. The TO-5 version is pin-compatible with most monolithic op amps.

National Semiconductor (UK) Ltd. The Precinct, Broxbourne, Herts.

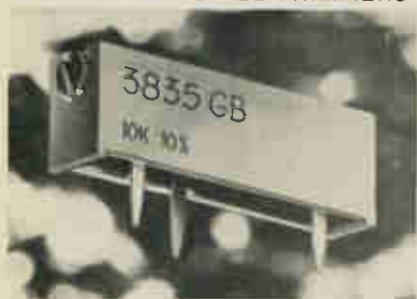ULTRA-LOW PROFILE TRIMMERS

High performance low profile cermet trimmers designated 3835 GB Series are now available from Amphenol. In a standard length of 19.2mm and measuring only 5.8 mm high and 4.3mm wide, these devices are very well suited to applications requiring high packing density or with limited space available for discrete components. Resistance values range from 100 Ω to 2M Ω .

Amphenol Limited, Thanet Way, Whitstable, Kent CT5 3JF.

NEW QUICK-HEAT TUBE

A new 12in monochrome picture tube that

warms up so rapidly it can present a clear picture within five seconds of being connected to a heater supply has been introduced by Mullards. Type A31-410W, it has a deflection angle of 110° and operates with an anode voltage of 12kW. It requires a heater supply of 11V at 140mA.

Mullard Ltd, Mullard House, Torrington Place, London W.C.1.

FERRANTI CUT LED DICE COSTS

The Special Components Department of Ferranti Limited at Gem Mill have announced reductions in the price of red and green LED dice of up to 50%.

Ferranti, who were the world's first manufacturers of LEDs, are now opening up an entirely new area of this rapidly expanding market. The availability of these dice, which can be mounted and bonded by techniques identical to those used in silicon technology, will enable traditional device manufacturers to enter the LED field without committing effort to the development of growth and processing techniques for the complex III-V compounds. In addition, it will enable hybrid houses and existing LED manufacturers to produce green emitting lamps and displays at highly competitive prices, as semiconductor dice are now being offered at 6p each in medium quantities, falling to 4p for larger orders.

The devices, which are manufactured from gallium phosphide for green emission and gallium arsenide phosphide for red emission, are available as dice for producing individual lamps or matrices, bars for hybrid seven segment arrays or full monolithic seven segment devices 1.25mm and 2.5mm high. *Ferranti Limited, Special Components Dept. Gem Mill, Chadderton, Oldham, Lancashire OL9 8NP.*

PRECISION POTENTIOMETERS

High precision 10-turn potentiometers specially developed to satisfy the design requirements in industrial electronic equipment are now available from Sasco.



The 47130 Series of Micropots with wire-wound elements offers a wide range of standard resistance values from 10 Ω to 200 k Ω \pm 5% with linearity tolerances \pm 0.25% (100 Ω – 100k Ω) not exceeding \pm 0.5% at

the highest and lowest resistance values.

The components have a power dissipation of 2W (+40°C), an insulation resistance of 1,000M Ω minimum and a noise figure of 1000 E.N.R. max. Rotational life is 2×10^6 revolutions.

Two versions of gold-plated Beryllium Copper terminals give the option of solder connection to wired circuits or plug-in to printed circuit assemblies.


The tough polyamid housing is resistant to most solvent and cleansing agents and there is high resistance to shock, vibration, humidity and other environmental characteristics.

These compact 10-turn potentiometers have an overall length of less than 3cm.

Sasco Ltd, PO Box 2000, Gatwick Road, Crawley, Sussex, RH10 2RU.

V-F ANNOUNCE SMALLEST PANEL LAMPDRIVER

What is claimed to be the smallest hybrid display panel lampdriver currently available has been introduced by V-F Instruments Limited of Gloucester. The new LD401 Series Hybrid Lampdriver announced by the Company consists of six 60mA drivers in one flatpack measuring 0.375in x 0.375in x 0.075in thickness, or approximately one-half the volume required for the next smallest available unit. Unlike the larger DIP packaged lampdrivers which provide only four drivers, the new hybrid package is a hermetically-sealed, all-metal type.

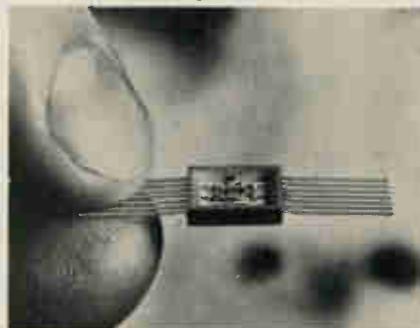


Capable of driving a wide variety of lamps from different lamp voltages up to 20V d.c. the LD401 Series offers complete flexibility for a broad range of special driver requirements. Principal applications, in addition to its use in lampdrivers, are as relay drivers, power drivers and hex inverters. Input is TTL and TTL compatible.

Another important feature of the hybrid lampdriver is extremely low power consumption, typically 50mW from the 5V power supply. "On" voltage is typically less than 0.2V, and remains so over the unit's operating temperature ranges from -55°C to $+125^{\circ}\text{C}$.

V-F Instruments Ltd, Northgate Mansions, 110 Northgate Street, Gloucester GL1 1SL.

DIGITAL PANEL METER

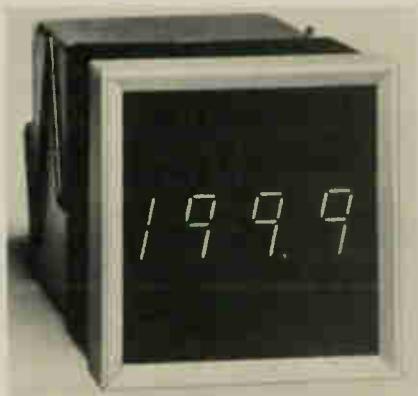48 x 48mm . . . less than 4 square inches, is all the panel space required by Schlumberger's new miniature 3½ digit DPM, the 6520.




The 6520 features a floating input, auto polarity, 0.1% precision, a ± 1999 display using 7 segment tubes with a polarised green filter and a range from 2 to 200V. The decimal point can be preset by the user.

Easy to install, the 6520 requires only 5V d.c. + 10% (1.5W) and allows direct replacement of existing analog meters at low cost.

*Schlumberger Instruments et Systèmes,
12 place des Etats-Unis, Montrouge, France.*

PLANAR DIFFUSED PHOTO DIODE

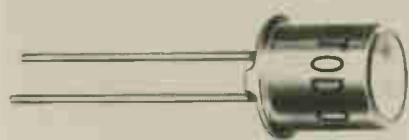

A planar diffused photo-diode which, when reversed biased has a leakage current proportional to the incident light, has been introduced by RS Components. With the fast linear response it is ideal for photometer circuits and many applications, for instance, batch counting, punch card reading, intruder alarms etc. The diode is housed in a two lead TO18 case with end window. It costs 85p and is available from RS Components Ltd, PO Box 427, 13/17 Epworth Street, London EC2P 2HA.

CMOS IN PLASTIC PACKAGES

Motorola Semiconductors have just announced that 39 devices from their standard CMOS logic family are now available in plastic packages. In the past, ceramic packages have been used for all CMOS devices manufactured

by this company.

The new devices, all in 14 or 16 pin dual-in-line plastic packages, have the same electrical specifications as the standard ceramic packaged components with type numbers suffixed CL. They will operate over the extended commercial temperature range of -40 to +80°C and are roughly 10% cheaper than their ceramic packaged counterparts.

Motorola Semiconductors Ltd, York House Empire Way, Wembley, Middx.

NARROW ANGLE HIGH INTENSITY LED LAMP


A new GaAsp solid state high intensity LED lamp - the NSL5027 - has been introduced by National Semiconductor.

The new lamp has a very high intensity at 10mA and is intended for front panel pilot lights, optical coupling and back panel lighting.

It has a forward current of 70mA, a reverse voltage of 3V and a power dissipation of 140mW.

NEW PC MOUNTING MICROSWITCH

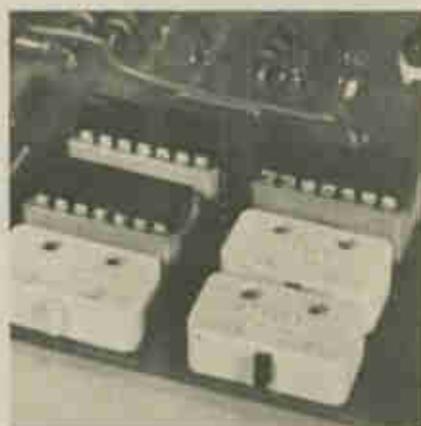Feltec Components Ltd have announced the availability of a new microswitch, Type 9201, for printed circuit mounting. The switch has a SPDT action and a 14 lead DIL package area - using pin positions 1, 6, 7 and 14.



The switch has a minimum life expectancy of 10⁶ operations, and has contact ratings of 3A at 24V a.c. or 1A at 250V a.c. Insulation resistance of the standard type is better than 100MΩ. Alternative case and contact materials are available for applications requiring lower contact resistance or higher insulation resistance.

Feltec Components Ltd, Weydown Road, Haslemere, Surrey.

SAMPLE/HOLD CIRCUITS

Guest International Ltd have available the S/H725 and S/H725WB sample/hold circuit which are suitable for insertion into 16-pin DIL sockets.

Both units are packaged in a small, compact, completely self-contained module measuring just 1.4 x 0.6 x 0.48in and offer a linearity of better than 0.01%. Sample-to-



hold offset error is under 2mV and the devices will operate with signals in the ± 10V range. They have an aperture time of under 100nS and aperture uncertainty time of 10nS.

Both units are powered by + 15V at 10mA and operate over the 0 to 70°C temperature range. They use high reliability components and should find applications in such areas as the holding of a signal for an A/D converter and as cascading sample/hold.

Guest International Ltd, Redlands, Coulsdon, Surrey, CR3 2HT.

NEW TRANSISTORS

New transistors from Mullards for use in high-power, high-quality audio amplifiers are families of complementary pairs that can give outputs of up to 100W. For example, in applications where an output of 6 to 15W is required, pairs from the transistor family BD433 to BD438 are suitable. (Odd numbers are NPN types, and even PNP.) These have a maximum V_{CEO} rating of 22 to 45V and a total dissipation of 36W.

Silicon power transistors type BD266 and BD267 form a complementary pair that can give a high-quality, audio output of 25W; they are also suitable for use in general purpose amplifiers and switching applications. Both are monolithic epitaxial-base Darlington transistors. Consequently, with a collector current of 3.0A and a collector-to-emitter voltage of 3.0V, each has a typical h_{FE} of 1500, a high value that enables a simple drive circuit to be used with them.

The BD266 is a PNP device with a maximum V_{CEO} rating of 60V, and the BD267 an NPN type with a maximum V_{CEO} of 80. The maximum I_{CM} rating is 12A, and with a mounting base temperature not greater than 25°C a total dissipation of 55W is permissible.

Other new Darlington devices to be shown are types BDX62 to BDX67, which are power transistors with TO-3 encapsulations. Complementary pairs selected from these for use in audio amplifiers will give outputs of 25 to 100W. Typical h_{FE} values are 1500, and peak collector current ratings are 12, 16 or 20A. Total power dissipations vary from 90 to 150W, and the devices have a transition frequency ranging from 2.5 to 7MHz which makes them particularly suitable for use in high-quality amplifiers.

Mullard Ltd, Mullard House, Torrington Place, London WC1.

DIGITAL MULTIMETER



Fluke International claims that its new systems oriented instrument offers unusual capability in a 5½ digit multimeter. The standard configuration combines high accuracy measurement of d.c. volts, true r.m.s. a.c. volts and a broad resistance range plus a unique self-test feature for rapid checkout of all measurement functions. Many systems options, available for both factory and field installation, are also offered.

Basically, the instrument offers 5½ digits, autoranging and autopolarity, functional self-test, 5 ranges of d.c. volts to measure from 1µV to 1100V, 4 ranges of true r.m.s.

a.c. volts measuring from 10µV to 1100V and 7 ranges of resistance to measure from 100Ω to 12MΩ.

Other features include switched four-pole filter with true broadband noise rejection, variable sample-rate control, push-button selection of range and function with complete interlocks, 100V guarding and 1500V overload protection.

Options include data output, remote control and real time ratio for four terminal d.c./d.c. ratio measurement.

Fluke International Corporation, Garnett Close, Watford WD2 4TT.

LOW COST POWER UNIT



A new, low cost, regulated d.c. power supply — made by Zauie Industries Ltd — is available from PBRA Ltd.

Designated Type 2005, the unit has an output range of 0–20V d.c. at 0 to 0.5A. Both line and load regulation is within 0.01% + 1mV. Ripple and noise at full load is less than 1mV peak-to-peak and resolution is


within 50mV. The unit has a 20µS transient recovery time and a total drift figure of less than 0.1% + 4mV over an eight hour period.

Measuring only 3in x 6in x 8in, the 2005 has its own voltmeter and separate ammeter built in, and is priced at £25.00.

PBRA Ltd, 33 Holmethorpe Avenue, Holmethorpe Trading Estate, Redhill, Surrey.

NEW STROBES

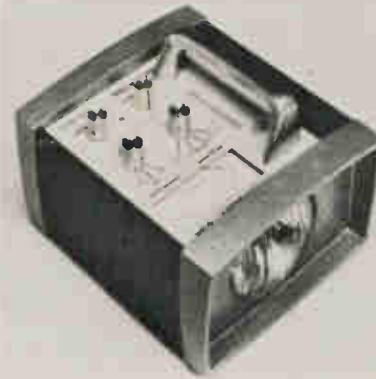We have information from two companies manufacturing stroboscopic equipment. Electroplan Ltd have a new *Strobe Automation* range of instruments and accessories on the market. There is a low cost torch, covering the speed range 3 to 100 flashes per second, and the 15K stroboscope, with a speed range of 4 to 250 flashes per second.



The 15K stroboscope from Electroplan

The 5K model is an intermediary instrument, suitable for demonstrating the principles of the stroboscope by analysing the movement of rotating parts. The prices range from £30 to £110.

S.E. Labs Limited have developed an instrument (*Type EM6*) with an extended range, from 5 to 1,000 flashes per second. By



The S.E. Labs EM6

illuminating once every revolution, machinery moving between 300 and 60,000 r.p.m., can be observed. (Up to 120,000 r.p.m. if every second cycle is observed).

See over

A 6in scale meter indicates the rate in flashes per second and the corresponding shaft speed in r.p.m. The flashing can be controlled in one of five ways - (1) using the internal continuously variable oscillator, (2) by an external mechanically operated switch (3) applying external sine or squarewave pulses, (4) introducing the supplied photoelectric transducer, or (5) locking to multiples or sub-multiples of the mains supply frequency.

The lamp reflector can be operated, by using the extension lead, separately from the control unit. An output pulse is supplied at half the flash rate, facilitating the driving of ancillary equipment or digital counting.

Electroplan Ltd., P.O. Box 19, Orchard Road, Royston, Herts.

5 DIGIT, 32MHz COUNTER

We have news of a portable (225.8mm x 177.8mm x 92mm, 3½lbs), easy to operate piece of equipment from RCS Electronics.




The RCS 301 Counter is a straight frequency counter based on a new design with leading zero suppression, automatic level control and decimal point. The instrument will measure from 0-32MHz in two ranges with 1Hz resolution. A low voltage 5 digit 7 segment display is employed so a d.c. supply of 10 to 15V may be used, instead of mains operation using the internal fully stabilized P.S.U.

RCS Electronics, National Works, Bath Road, Hounslow, Middlesex.

ELECTRONIC THERMOMETERS

Electroplan have been appointed as the distributors for a range of new Comark electronic thermometers. There are five in the range covering -120°C to $+1100^{\circ}\text{C}$. The instruments are easy to use and are calibrated for direct reading in $^{\circ}\text{C}$. Cold junction errors and problems from the resistance of thermocouple and lead length are eliminated. Four of the thermometers are calibrated for Chromel/Alumel thermocouples, the fifth is calibrated for Copper/Constantan.

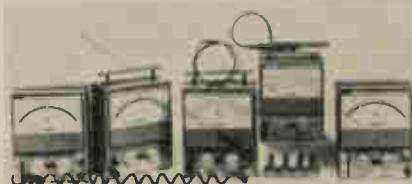

The 1601 and 1621 models are 2% RSD units for general purpose use with varying resolution depending on the range. The 1602 has a 1°C resolution with suppressed zero. For measurement in 10°C steps the 1604 and

1605 types have a resolution of 0.1°C at an accuracy of $\pm 0.5^{\circ}\text{C}$. These thermometers are claimed to be ideal for a wide range of research and practical laboratory applications in agricultural, process industries and academic environments.

Electroplan Limited, PO Box 19, Orchard Road, Royston, Herts. SG8 5HH.

A TORCH THAT TESTS FUSES

Every electrician carries two basic tools - a torch and a fuse tester. Now Flument Electric have combined them in one simple instrument that slips into the pocket. The Flument FuseTester looks like an ordinary hand torch, taking two U2 batteries. It comes in two models - the standard in metal, the heavy duty encased in rubber.



The instrument functions as a conventional torch and, without change, as a tester for circuits and fuses. It must never be used, of course, on live circuits, sockets or switches. Each model is fitted with a pair of leads which, when applied to each end of a fuse or section of a circuit, make the torch bulb light if the circuit is complete. One lead is arm length, making it particularly useful for reaching inaccessible corners. Sockets on the body neatly show and protect the leads when the instrument is not in use. Recommended prices (without batteries) are - standard £1.20, heavy duty £1.80, from electrical wholesalers or direct from the manufacturers.

Flument Electric Ltd., Newton Avenue, Longsight, Manchester.

ALUMINIUM SOLDER

Multicore Solderers Ltd., have announced that their 'Alu-Sol' - believed to be the first cored solder that readily joins aluminium and many of its alloys - is now available to the amateur constructor. This does not mean, however, that one can now solder aluminium using a standard soldering iron.

The specific heat of aluminium is high (about 2½ times that of copper) and its thermal conductivity is good. To bring the

job to the required temperature range (280 - 370°C) a larger capacity of heat is needed compared to that necessary in most soldering jobs. These thermal characteristics, however, mean it is easier to heat the assembly evenly.

Unless the amateur is prepared to buy a large capacity soldering iron (with the recommended tip temperature) another method will have to be devised, using a hot plate for instance. Care must be taken to keep the finished joint dry, possibly by painting with a protective coating, because aluminium is subject to a greater degree of oxidation and electrochemical corrosion than most metals.

DIGITAL SIGNAL GENERATOR

Radiometer A/S of Copenhagen, have announced a new digital signal generator, the MS30. This is an AM-FM instrument which covers the frequency range 50kHz to 520 MHz, indicated on an 8 digit display with a 10Hz resolution. A coarse frequency setting employs electronic tuning in steps of 10MHz and 100MHz and a fine tuning control covers the entire range continuously. In combination with a 3 digit selector and a frequency lock capability this provides very precise and very easy frequency selection. Both accuracy and stability are $\pm 10\text{Hz}$.

Output level is also digitally displayed on a 3 digit indicator in μV , mV or dBm and the output can be adjusted within the range +10dBm to -126dBm by means of an electronically controlled 1 and 10 step attenuator and a varier. The r.f. output includes an on/off facility and is protected against unwanted signals up to 20W.




A third 3 digit display indicates the mode frequency and AM% or FM deviation of either of two modulation generators. One generator has 6 fixed frequencies of 150, 300, 400, 1000, 3000 and 6000Hz with an accuracy of $\pm 1\%$ and the other has continuously variable frequency from 300Hz to 3kHz with an accuracy of ± 1 digit.

Another feature includes facilities for phase locking the internal 10MHz reference signal to an external reference so that when required the MS30 can be frequency locked with another MS30.

The RF frequency and the output level of the MS30 can be programmed via an interface unit and several versions of this unit are available to cover the requirements of most OEM and automatic test systems.

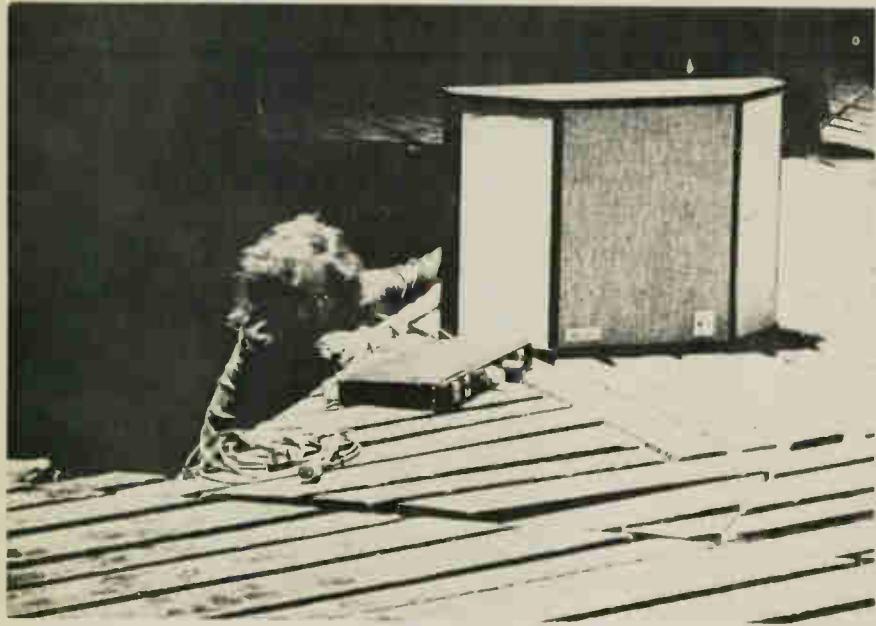Marketed through International Instruments Ltd., Cross Lances Road, Hounslow, Middlesex.



In the recent production of *Don Giovanni*, at Covent Garden, the voice of the Commendatore's statue reached the audience through an AR-LST speaker system concealed beneath the stage grillwork. The real singer was singing into a microphone off-stage. Many people have been listening to a loudspeaker and thinking it to be 'live' music.

The photo shows a Covent Garden technician removing the AR-LST from its concealed position after a dress rehearsal of *Don Giovanni*.

VACUUM RECORD CLEANER

The manufacturers, R.I. Audio, claim that their new "Groovac" record cleaner is the only unit available which removes dust from records by vacuum cleaning. It has long been recognised that vacuum cleaning is the best way to remove dust, especially fine dust. Now the suction method is available for the effective removal of the fine dust particles which collect inside record grooves and which are responsible for record and stylus wear.

A tracking force of only 0.7 gram has been achieved by using a lightweight design with lubricated-for-life bearings throughout. This is considerably below the 3 to 6 grams force of simple brush cleaners. Low tracking force allows fine hairs to be incorporated in the Groovac cleaning nozzle which ensure efficient removal of dust from the bottom of record grooves — most brush cleaners have hairs with a diameter which is larger than the width of the record grooves. Low tracking force also means an almost immeasurable reduction in turntable speed, a reduction which is at least three times less

The Royal Opera House owns 5 AR-LST's, which have been used a number of times this season. The offstage brass band in *Aida* was actually a pair of these speakers, painted black and placed near the end of the proscenium.

The AR-LST is the professional version of Acoustic Research's basic acoustic suspension speaker system.

Acoustic Research International, High Street, Houghton Regis, Dunstable, Bedfordshire LL15 5QJ

than that caused by brush cleaners.



The Groovac consists of a precision lightweight arm, and a suction unit which is acoustically isolated in a special enclosure. The suction unit has been designed to be inaudible at a distance of 2 metres; it has a mains switch and indicator, and is attractively finished in teak. The arm takes less space than brush cleaners — the counterweight projects less and the arm occupies less height. It mounts by means of a convenient magnetic base, and its height is adjustable to suit different turntables. When not in use it is simply rotated outwards and

lowered onto its integral rest. The price is £6.90 plus VAT and is available from hi-fi retailers or direct from the makers.

R.I. Audio, Kernick Road, Penryn, Cornwall.

MINIATURE CASSETTE RECORDER

Here is a pocket-sized, (6½in x 4in x 17/8in, 1.6lbs without batteries) Cassette Recorder with all the features you would normally find only on larger machines.

JVC's model CP-1646 has an unusual built-in Condenser Microphone which operates in two ways. Retracted into the record casing it behaves as an omni-directional microphone recording all the surrounding sounds. When pulled out from the casing it becomes a unidirectional microphone picking up only those sounds at which it is aimed. Furthermore JVC have fitted an Automatic Level Control circuit.



Control of the CP-1646 cassette-drive mechanism is simple: the one-touch recording button is interlocked to the playback button so that recordings can be made with just one finger. Autostop, automatically disengages the mechanism thus switching off the whole electrical circuit, and the power is switched off to conserve the batteries. A pause button is also fitted, and the normal Fast/Forward/Rewind switch and Eject button are provided.

Other features are a combined recording and battery level meter. An earphone can be fitted for monitoring purposes, and an external microphone can be plugged in if required. In addition, a remote control socket is fitted which allows all the recorder's functions in either the record or playback mode to be controlled externally. Power is normally obtained from 4 built-in cells, but it can be run off the a.c. mains or a car battery if necessary.

CASSETTES AND AMSTRAD AMPLIFIERS

A.M.S. Trading (Amstrad) Ltd. have now set up facilities in their new enlarged Service Department to give advice on the use of Cassette/Tape Decks with Amstrad Amplifiers. Should the Cassette/Tape Decks owned by any Amstrad customer prove non compatible, the Service Department can modify the Amplifier as necessary at a cost of £3.00. All arrangements should be made through Simon Angel — Service Manager.

A.M.S. Trading (Amstrad) Ltd., 89 Ridley Road, Dalston, London E8.

Electronic Transistorised Ignition

Continued from Page 42

side with the heatsink uppermost. Check these tags cannot foul the edges of their rectangular cutout. Use insulating sleeving on all exposed wires. The neon is held in a black rubber grommet to improve visibility and give physical protection. All connections to the vehicle are by means of heavy gauge colour-coded cables which pass out of the unit through a grommet. Note that C1 and C2 are held secure by the wire from the fuseholder to TB6 being passed over them. R4 is mounted flat against the bottom of S2. Check that there are no shorts to the box when the two halves are screwed together. Solder the five links on the link strip and screw it to the terminal block in the correct position:

LEFT (heatsink uppermost) for positive chassis;
RIGHT for negative chassis.


INSTALLATION AND USE

With the ignition switched off, disconnect the existing leads to your car's ignition coil. Mount the unit by means of two screws passed through the base of the box in a convenient part of the engine compartment, less than 30in from the ignition coil and in a position well away from the hot exhaust manifold and reasonably well ventilated. DO NOT mount unit on engine. A good position is on a flat surface such as the main bulkhead since this helps heatsinking. Recheck the polarity setting, then connect the colour coded leads as follows:

RED: To ignition switch. Normally the lead just disconnected from the ignition coil SW terminal can be used but there must be no ballast resistor in series with the supply to the unit. Beware of ballast resistors incorporated in the SW lead.

BLACK: To chassis. This lead can be anchored under a nearby bolt to ensure a low resistance connection. It may seem anomalous that on positive chassis vehicles, red goes to battery negative and black goes to positive!

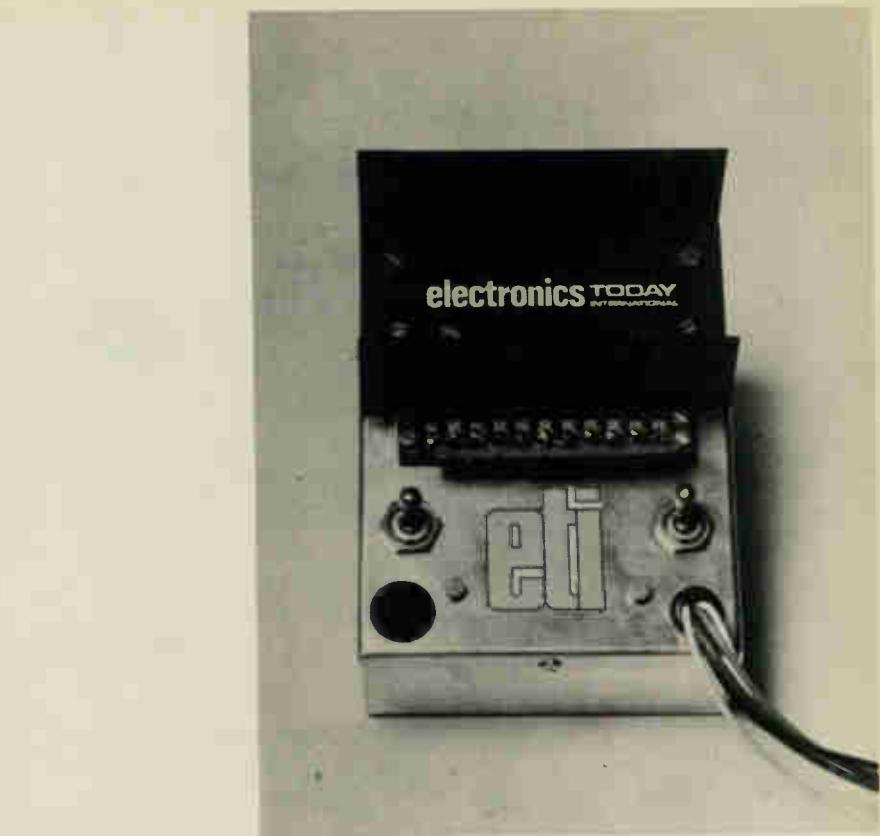GREEN: To the contact breaker in the distributor. It can be connected to the free end of the lead previously disconnected from the CB terminal of the ignition coil.



The completed unit. The heatsink should be sprayed matt-black.

BLUE and YELLOW: To the CB and SW terminals of the ignition coil. Remove any suppressor capacitor on the coil.

Check that all connections are secure (especially those to the coil) and taped to prevent shorts. Dress all wiring neatly and clear of hot or moving engine parts.

Put both toggle switches towards the heatsink and switch on the ignition. The neon should light and a whistle come from the unit showing the inverter is working. Start the car and observe the neon while revving up; it should not dim greatly. Treat your car to a new contact breaker, a plug gap check and a garage tune-up since these will not have to be repeated for a long time. If the garage is suspicious of transistor ignition, switch back to conventional. Resistive (suppressor) plug leads in poor condition should be replaced as they deteriorate faster with transistor ignition.

BURGLAR FOILING

If the toggle switches are put in alternate positions (one up, one down) neither transistor nor conventional ignition circuits are complete and the engine will not start. This feature can be used to immobilise the car

when parked. Most car thieves will give up at this but a stronger deterrent can be arranged for more persistent thieves. A wire can be taken from the unused pole (b) of S2 (see circuit and layout) to the coil of the horn relay (if fitted) or to an extra hidden relay which when energised operates the horn or other alarm. Then if the ignition is disabled by putting S1 down and S2 up, any unauthorised use of the ignition switch will energise the relay and sound the alarm. Since the alarm supply at S2b comes via the ignition coil primary it may not be able to operate the horn directly although this may be possible with some horns if they are sufficiently sensitive. Horns that are switched in their chassis returns cannot be used without a relay.

SPARK POLARITY

At speed the tip of a spark plug runs at high temperature and some cathode emission, as in a radio valve, occurs. This means that the breakdown voltage is slightly lower for a negative spark pulse (with respect to chassis) than a positive one. The effect is usually ignored and is fairly academic with transistor ignition where adequate spark voltage is always available. However some claims are made that reversing the leads from

Electronic Transistorised Ignition

the unit to the ignition coil (blue and yellow) improves performance and there is no harm in experimenting.

To increase the spark energy another 0.47uF or 0.5uF capacitor can be added across C1 but the unit is then suitable only for fairly low-revving engines with 4 cylinders or less.

Please note that this project is only suitable for 12V cars and we are unable to provide modifications details for 6V models.

SPECIAL OFFER FOR ETI READERS

Use the coupons below to order either the kit or a built, tested and guaranteed version of the ETI Electronic Transistorised Ignition, in both cases at £2 less than the normal price.

USE THIS COUPON FOR THE BUILT VERSION

To: DOLPHIN DESIGNS, New Farm House, North Shoebury Rd., Shoeburyness, Essex.

Please find enclosed a cheque/PO for a built version of the ETI Electronic Transistorised Ignition at the special price of £8.91 which includes postage, packing and VAT.

Name

Address

.....

This offer applies only to orders postmarked before September 30th 1973 after which the normal resale price of £11.00 applies. Please allow 28 days for delivery. Orders at the special price will not be accepted unless accompanied by this coupon.

USE THIS COUPON FOR THE KIT

To: BI-PRE-PAK LTD., 222 West Road, Westcliff-on-Sea, Essex SSO 9DF

Please find enclosed a cheque/P.O. for a complete kit of the Electronic Transistorised Ignition at the special price of £5.92 which includes postage, packing and VAT.

Name

Address

.....

This offer applies only to orders postmarked before September 30th 1973 after which the normal resale price of £7.92 applies. Please allow 28 days for delivery. Orders at the special price will not be accepted unless accompanied by this coupon.

P. C. BORED?

— not with the

DECON—

DALO 33PC



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

**NO MESS—
NO MASKING**

A perfect circuit every time !

The Decon-Dalo 33 PC marker is now available in France, Germany, Italy, Switzerland, Austria and all Scandinavian countries. Send for details of local supplier.

Please send me further details on the 33PC:

Name

Address

Post to: **DECON LABORATORIES LTD.**

FREEPOST

PORTSLADE, BRIGHTON

(No Stamp Needed)

Electronic Brokers Ltd.

PORTABLE AC/DC RECORDING VOLTAMMETER

Fitted with separate zero-marking pen. Accuracy 1.5% DC, 2.5% AC. Measurement ranges — AC and DC 5 15 150 250 500mA 1.5 5 Amps 5 15 50 150 250-500V DC only. Frequency range 45 to 1000 c/s. Chart width 100mm. Chart speeds 20-60-180-600 1800 5400 mm/hour. Weight 2.2 lbs. Price complete with accessories £78.00

WHEATSTONE BRIDGE AND CABLE FAULT LOCATOR

Measurement of resistance in the range of 0.005 to 1 megohm. Location of cable faults using Varley loop method. Location of cable faults using Murray loop method. Measurement of asymmetry of wires. Use of four-decade section as a resistance box. The bridge consists of four decade switches giving a range from 1 to 9999 ohms in 1 ohm steps. Accuracy from 1 to 99.99 ohms 0.5%. From 0.1 to 9.999 ohms 1.5%. From 100s to 1 megohm 5.0% from 0.005 to 0.0999 ohms 5.0%. Dimensions 300x230x150 mm. Weight Approx 12 lbs. Price complete with connecting leads £41.00

AC/DC MULTIMETER

With four band suspension movement. Sensitivity 20,000 ohms per volt on DC and 4,000 ohms per volt on AC. Technical Data: 0.06-0.6-6-60 600mA 3 Amps DC 0.3-3-30-300mA 3 Amps AC 0.6-1.2-3-12-30-60-120-600 DC 1200 Volts 3.6-15-60-150-1300-600-900 Volts 45 to 20,000 Hz 500Ω 5-50 500kΩ resistance Decibel range -10 to +12dB Accuracy 1% of FSD. — DC and resistance measurements. 2.5 Price with test leads and storage case £8.00

3" SINGLE BEAM PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. Vertical amplifier Bandwidth 10 MHz. Sensitivity at 100 kHz V RMS 1.25 Horizontal Amplifier Bandwidth 500 kHz. Sensitivity at 100 kHz V RMS/mm sec. Free running 20-200,000 Hz in 3.25 Preset stepped sweep 1-3000μ sec ranges. Calibrated pips. Dimensions 220x360x430 mm. Weight 40 lbs. 115-230V AC operation £39.00

DOUBLE BEAM OSCILLOSCOPE

Designed for investigation and measurement of pulsed and periodic waveforms. The use of two independent vertical deflection amplifiers permits the display and analysis of two different waveforms simultaneously. Display area 35x90 mm. Repetition rates of investigated waveforms 50 Hz to 1 MHz. Range of pulse length 0.35μ sec to 1 sec. Range of amplitudes 0.04 to 400V. Maximum amplitude without external attenuator 100V. Characteristics of vertical amplifiers. Amplifier passband at 1dB DC to 1 MHz. Amplifier passband at 3dB DC to 5 MHz. Sensitivity at medium frequencies at broad passband 500mV/mm. Size of undistorted pulse display 40mm. Input Impedance 0.5 - 0.1 Megohms shunted by 45pF. Input Impedance with external attenuator 5 Megohms shunted by 13pF. Voltage attenuation ratios of the built-in attenuator 1:1 1:10 1:100. 1:1000. Time Base Preset calibrated sweep durations microseconds per cm 0.2 0.5 1 2 5 10 20 50 100 Milliseconds per cm 0.2 0.5 1 2 5 10 20 50 100. Free-running time base frequency range 50 Hz to 1 mHz. Sweep sync voltage and trigger voltage 0.5V. Maximum trigger pulse repetition rate 10 kHz. Built in amplitude calibrator. Amplitude of test pulses with duration of 0.35μ sec or longer 0.04-100V. Fundamental error of the calibrator 10%. Frequency of quartz crystal calibrator 100 kHz. Overshoot of pulse top for pulses with rise time not below 0.1μ sec 10%. Instrument warm up time 30 min. Power inputs 220-250 - 50 Hz. Overall dimensions 260x550x376 mm. Weight 55 lbs. £87.00

4-RANGE GENERAL PURPOSE TEMPERATURE RECORDER Type 01

Specially designed compact self-contained instrument for recording temperatures up to 500°C. The main design objectives were for an easy to use robust instrument suitable for use in the laboratory and the field. The four ranges are 10°C 50°C 100°C and 500°C. These are selected by the 3 wide chart. Two chart speeds 1 and 6 per hour are provided by the 240v 50Hz synchronous chart drive.

The 3 basic accuracy of the instrument which is adequate for most applications has been achieved without introducing stability problems in the d.c. amplifier making the recorder ideal for use in schools, colleges and universities and by unskilled personnel. The recorder is complete with NiCr/NiAl thermo couple and mains lead. This product is brand new and manufactured in our own laboratories with three month guarantee.

£95.00 plus £5.00 packing and carriage

THREE CHANNEL HIGH SPEED RECORDER

Strip Chart Recorder. Chart length 175ft. Footage indicator. Width of recording channel 80mm. Chart speeds selected by pushbuttons 1, 2, 12, 30, 60, 120, 300, 600, 3000 mm per minute. Full deflection current 8mA. Internal impedance 210 ohms. External impedance 800 ohms. Dimensions 510x345x175mm. Weight 44 lbs. Price complete with accessories £90.00

10 CHANNEL EVENT RECORDER

Designed for recording sequences of up to ten different operations e.g. sequence of machine tool operation switching silences etc. Record is presented in the form of square pulses. When energised pen moves by approximately 4mm to the right of zero line. Response time 100 milliseconds. Chart width 110mm. Chart length 50m. Inv capacity 72 hours. Chart speeds 20, 60, 180, 600, 1800, 5400 mm/hour. Size 180x160x255mm. Weight 9 lbs. Price complete with accessories £52.00

AC CLAMP VOLTAMMETER

Clamp-on voltmeter is used for measurement of AC voltages and currents without breaking circuits. Specification: Measurement ranges -- Current 10-25-100-250-500 Amps. Voltage 300-600 V. Accuracy 4%. Scale length 60mm. Overall dimensions 283x94x36mm. Weight 1.5 lbs. £10.50

MULTIMETER

0.1 1 10 100 1000mA 2.5-10-20-250 500 1000V AC/DC. Sensitivity AC and DC all ranges except 10V-10 000 Ohm V. Dimensions 212x118x75 mm. Weight 2.9 lbs. Price complete with steel carrying case and test leads £4.95

NEW AMPERTEST 690 — A NEW CLAMP TYPE AMMETER

Electronic Brokers Limited announce the introduction of a new clamp type ammeter having 6 current ranges plus 2 voltage ranges for use on 50 to 60 alternating current supplies. Known as the AMPERTEST 690, the new instrument is manufactured in Italy by Industrie Costruzioni Elettromeccaniche, one of Europe's largest manufacturers of electrical measuring instruments.

The Ampertest 690 uses the familiar clamp or 'pincer' system to measure the current flowing in a conductor without breaking the circuit. The meter, which is designed to be used with one hand, has 8 current ranges from 3 to 600 amps. It is supplied with the first division at 100 mA. The current ranges may be extended by use of a 10 to 1 current transformer which is supplied with the instrument providing ranges from 300 mA to 60000 amperes. In addition there are two a.c. voltage ranges, 250V and 600V a.c. The connections for voltage measurements are made by two leads and probes which plug into the base of the instrument.

The range to be used is selected by rotating a small serrated thumbwheel on the side of the instrument. This action brings the appropriate scale under the meter needle removing the possibility of reading the wrong scale. When not in use the meter movement is clamped by the ON-OFF switch to prevent damage during transit.

The Ampertest 690 is supplied complete with voltage measuring leads and probes and combined twin wire adaptor/current transformer in a solid leather carrying case. A belt fitting pouch is available as an extra.

£37.50



This instrument basically consists of a transistorized amplifier voltmeter which measures the voltage across a specified load. It is provided with 40 load values ranging from 2.50m to 20kohm. As the loads are purely resistive, their value keeps constant with varying frequency. A special negative feedback loop allows a nearly linear scale to be obtained. No damages to the instrument result from errors in presetting the load values or the power ranges.

Power measuring range (in 4 ranges) from 1mW to 10 W. Level measuring range Ref 1mW Frequency range from -3 dB to +40 dB. Within 0.5 dB. Accuracy 40 Values better than 5% R.M.S. Instrument Calibration £89

ELECTRONIC TIME DELAY SWITCH.

Specification:
Delay period 1-25 minutes adjustable load 1000 watts maximum. Operating Voltage 180-250V a.c. 50Hz. Size 3½ x 3½ x 1½ Standard Ivory Surface mounting Box Trade Price £8.80

Fantastic value in Test Equipment



MODEL 300 LOGIC PROBE

A compact, easy to operate logic probe. As a light-emitting diode is used the unit activates with low power. It does not affect the circuit under test because of high input impedance. Up to as high a frequency as 12 MHz.

£5.50

plus 75p packing and carriage



TV SWEEP MARKER GENERATOR Type VU 167

Suitable for alignment of tuned circuits in television sets. Incorporates a sweep generator, a marker generator and a crystal-controlled oscillator operating at 5.5 MHz. Sweep frequency range 1.30 MHz - 170-260 MHz. Fund. 470-780 MHz. Harmonic Marker Frequency range 2.286 MHz, 480-800 MHz.

£195.00



PORTABLE WHEATSTONE BRIDGE

Designed for measurements of DC resistances in the range of 10^{-3} to 10^4 Megohms. Basic accuracy 0.01 ohms to 10⁴ ohms is 0.2%. Dimensions 300x230x150 mm. Weight approx 13 lbs.


£59.00



MINIATURE PEN RECORDER

Provides permanent record of DC currents up to 1mA. Emminently suitable for use where space is limited. Separate time marker pen provided. Chart width 80mm. Chart length 40ft. Chart speeds: Slow 20-60-180 mm/hour. Fast 600-1800-5400 mm/hour. Dimensions 120x120x255mm. Weight 7.7 lbs (3.5 kg). Price complete with accessories

£39.00

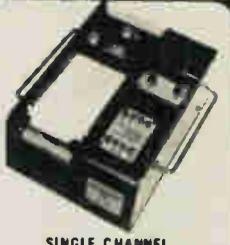

SINGLE CHANNEL HIGH SPEED RECORDER

Chart length 175ft. Footage indicator. Width of recording channel 80mm. Chart speeds (selected by push buttons) 1.2-6-12-30-60-120-300-600-3000 mm per minute. Full deflection current 8mA. Internal impedance 210 ohms. External impedance 800 ohms. Dimensions 320x340x175mm. Weight 35 lbs. Price complete with accessories

£55.00

Supertester 680R.

Buy it for what it is. Or buy it for what it can be. ACCESSORIES TO CONVERT THE SUPERTESTER 680R TO THE FOLLOWING:

Amperclamp



For measuring a.c. currents from 250mA to 500 amps £11.95

Gauss Meter

For measuring magnetic field strengths £11.95

Phase Sequence Indicator

To indicate the phase sequence of a 3 phase supply £8.95

Signal Injector

Producing 1KHz and 500 KHz signals for circuit testing £8.95

Temperature Probe

Covering the range -30 to +200°C etc.

Electronic Voltmeter

Input resistance of 1Mohm for d.c. and 1.6Mohms shunted by 10pF for a.c. £18.00

Transistor Tester

For transistors and diodes £11.00

£18.50

Complete with case & probes

SUPER TESTER 680R

SPECIFICATION

13. D.C. ranges

from 0.1 to 12

Ranges from

500A to 20,000A

Accuracy 1%

11. A.C. ranges

250A to 4,000.0V Accuracy

Resistance: 8 ranges from 0.5Ω to

100MΩ Reactance: 1 range of

0-10MΩ Frequency: 2 ranges of 0.5-

and 0.5000 Hz Output Voltage: 9

-24 to +70dB Capacitance: 10 ranges from

20 to 20,000 pF from internal battery and

2 ranges from 50,000 to 500,000pF using mains

Ranges from 10 to 20,000V DC/Delta: 10 ranges from

24 to +70dB Capacitance: 8 ranges, 4 ranges

from 50,000 to 500,000pF using mains

Ranges from 10 to 20,000V DC/Delta: 10 ranges from

24 to +70dB Capacitance: 8 ranges, 4 ranges

from 50,000 to 500,000pF using mains

Ranges from 10 to 20,000V DC/Delta: 10 ranges from

24 to +70dB Capacitance: 8 ranges, 4 ranges

from 50,000 to 500,000pF using mains

Ranges from 10 to 20,000V DC/Delta: 10 ranges from

24 to +70dB Capacitance: 8 ranges, 4 ranges

from 50,000 to 500,000pF using mains

Ranges from 10 to 20,000V DC/Delta: 10 ranges from



ARROW


CT series subminatures low cost... high standard

In subminiature switching, low cost needn't mean low quality! That's the message that British-made Arrow CT series carries round the world—gaining ready acceptance wherever it goes. Those rugged little lever switches pack maximum performance into minimum size and weight. Single and double pole versions with 2 or 3 way action, give a choice of levers in bright chrome or seven colours. They meet ratings up to 2A at 250V ac, and with their C.S.A. and U.L. approvals they'll help you show the flag.

Get the full data on hardy,
home-grown Arrow CT sub-mins.

ARROW-HART (EUROPE) LTD.
PLYMBRIDGE ROAD, ESTOVER,
PLYMOUTH PL6 7PN, ENGLAND.
TEL 0752 701155 Telex 45340 Cables ARROWHART PLYMOUTH

Arrow switches right across the panel

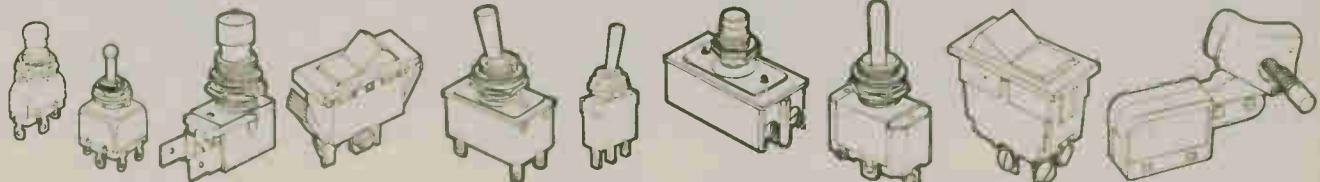

Scottish Office
13 MURRAY PLACE, STIRLING FK8 1DQ
Telephone: 0786 3823

U. K. Distributors ITT ELECTRONIC SERVICES HARLOW - 027-96 26777 RENFREWSHIRE -
Johnstone 23457 LEIGH - Leigh 5211/2/3 SUTTON COLDFIELD - 021-355 4511 BRISTOL - 0272 290125
C.E.S. LTD. CROYDON - 01-686 0505 COMWAY ELECTRONICS BRACKNELL - 0344 24765
S.A.S.C.O. LTD. CRAWLEY - 0293 28700 GLASGOW - 041-221 6152 3
JERMYN INDUSTRIES. SEVENOAKS - 51174

Overseas Agents in Arabian Gulf, Belgium, Ceylon, Denmark, East Africa, Eire, Finland, France, Greece, Holland, Hong Kong, India, Israel, Italy, Kuwait, Federation of Malaysia, Norway, Philippines, Portugal, Singapore, South Africa, Spain, Sweden, Switzerland, Trinidad and Western Germany.

DX MONITOR

Compiled by Alan Thompson



GEAR - that's the subject of this month's compilation: a subject of which DXers never tire! Numerous letters indicate that many of you are intrigued by some of the gear which appeared in the picture at the head of the first DX MONITOR so let me take you on a conducted tour of my shack adding, as we go, some notes that I hope will be of interest and use to fellow DXers.

AERIAL

There are two basics in any receiving installation - the receivers and the aerials. Currently, I'm using five separate aerials in the search for those elusive DX signals. The first is the easiest to describe - it is the "Aerialite" Mastatic vertical aerial, all 18ft. of which rises slimly from a rear chimney. This aerial may not have any terrific 'gain' - the manufacturers make no claims in that regard - but if you live in a noisy location it can certainly be recommended for the way in which an ingenious feeder set-up eliminates a lot of the noise-blanket of electrical interference which exists around any house in an urban location. The second one is also a vertical which was erected experimentally about 3 years back and has never been taken down because - despite all theoretical considerations - it does give an astonishing amount of pick-up, even though it has a feeder of about 80ft. between aerial base and receiver terminals.

Third comes the aerial which brings in most of the low-powered African stations that form my real favourite hunting ground. Erected so that it runs in an east-west direction it is an inverted-L, about 50ft. long including the vertical portion, and is only 20ft. high at best, falling to about 15ft. at the receiver end. Aerials 4 and 5 really go together - basically, they are derived from a long-wire about 130ft. long, mounted some 45ft. high. This is centre-tapped to form a 'T' and is also tapped at one-third of its length, which you will recognise as forming a 'Windom'. In practice, the two feeders off the same aerial cause no problems at all, and the aerial switching is so arranged that both feeders can be fed to a receiver at the same time, if required, which gives an improvement of an S-point or more on some signals. Comparison with separate aerials of 'T' and 'Windom' construction show no appreciable difference between them and the 'composite' system I am using. Each aerial is fed to a DPDT switch so that when it is not in use it is connected direct to earth - useful in thundery conditions and a good way of avoiding interaction between aerials. DPDT switches are used in preference to SPDT types since some of the aerials are fed by coaxial cable and others by single wire feeder: the use of DPDT switches means that it is easy to accommodate changes in the system (something that is always going on). The selected aerial is fed to a home-brew pi-network coupler, concealed in the space behind the control panel under the receivers, and from there can be easily switched to either of the two main receivers, or to any other receiver that may be on test.

RECEIVER

That brings us to the receiver department and the main receiver is the "Racal" RA1 7K (right centre of picture), a professional

Communication Receiver covering from about 500kHz to 30MHz without any break at all. This 23-valve job is for me the ultimate in receivers for DXing for two reasons - firstly, its stability is such that one can tune to a frequency and be sure that the receiver will still be 'spot-on' however long the DX session lasts, and, secondly, the degree of bandspread is astonishing, spreading each MHz band over 5ft. so that the total medium- and short-wave spectrum occupies something like 150ft. with each kilohertz clearly marked on the superb dial. As you might guess, RA17's don't come cheap! New you wouldn't have a lot of change from £1,000 and a second-hand one in good condition is likely to separate one from about £300: I'm sure, though, that anyone who has used one will agree that it is money very well spent as the mechanical and electrical construction is superb.

The other receiver (the one under my left hand in the 'photo') is not at all well-known and my example has been somewhat modified as it needed some pretty extensive re-furbishing when I acquired it. It is an ex-Royal Navy receiver, the "Rees-Mace Marine" model CAT, sometimes known as the A.P.100339, and it is another general coverage receiver spanning about 50kHz to 31MHz in 8 calibrated wavebands, and using 12 valves as well as requiring a separate power-pack (not visible in the picture). This is not the world's best receiver above about 10MHz but its performance on the lower frequencies is excellent and I find it ideal for medium-wave DXing.

PRESELECTOR

Sitting atop the "CAT", we find a "Hamgear" P.M. 1IBX pre-selector and this is a mains-powered solid state device covering frequencies above about 1.5MHz. The pre-selector is claimed to give between 20 and 25db gain in that frequency range and has proved to be really excellent when used with the "Racal". A switching arrangement allows it to be taken in or out of circuit as needed. For years, there has been much speculation as to whether a good Communication Receiver requires a pre-selector, and it has even been suggested that there is something amiss with the receiver if one is needed! To me, this seems to be one of those hoary chestnuts which remains in circulation for ever and a day - if not, perhaps, someone can explain why "Racal" do (or did?) make a pre-selector of their own for use with the RA17-series, which are generally acknowledged as being the best receiver ever made using valves. DXers are concerned with achieving the best possible signal-to-noise ratio they can, so one starts with getting as much signal as possible to the aerial terminal of the receiver, reducing, in the process, the noise pick-up as much as possible. Now, the early stages of a receiver add their own noise to the signal and, thereafter, both signal and noise get amplified in the various stages of the receiver. If one can insert, between the aerial and the receiver, a device which has a low noise level of its own then it is axiomatic that the signal-to-noise ratio at the receiver's aerial terminal will be better than would be the case without the use of such a device. This pre-selector, using an F.E.T. front-end, certainly does improve the signal-to-noise ratio and makes otherwise useless signals into fair DX-copy.

DX MONITOR

AUDIO PROCESSING

The audio side of the set-up is uncomplicated: the "Racal" has only a small panel speaker for monitoring purposes, whilst the "CAT" has no loudspeaker of any kind - both, of course, are provided with a variety of outlets for taping and other purposes and these are brought out to suitable sockets on my control panel. The main audio feeds from each are switchable to an old "Tripletone" amplifier (top left) which has the valuable asset of providing control over bass, treble and middle-range audio frequencies - a great asset in eliminating a lot of background 'mush' from a signal. The small box-of-tricks on the top-right of the picture (surmounted by an S-meter connected to the "Racal") is another device for 'cleaning-up' the audio delivered by the receiver and is to a design of ETI's Editor, Halvor Moorshead, when he was associated with "Practical Wireless": briefly, this "Audio Processing Unit" helps to eliminate heterodynes by selective attenuation of some of the audio frequencies.

Some readers suggested - perish the thought! - that our picture was posed, as the pair of headphones I was wearing were not connected to a receiver. Sorry to disappoint you but for reasons of convenience I prefer to use stereo 'phones - they are much more comfortable for late-night listening - so I've duplicated the 'phone output of the "Racal" and the "CAT" on the control panel. In the picture, the "Racal" 'phone socket is feeding directly into the "A.F. Processing Unit" and I am monitoring the resulting signal from the socket on the control panel. One mark for me!

CONTROL PANEL


You can not see the complete Control Panel in the picture but it really consists of a hardboard drawer which slides into the racking on which all this gear is mounted, and has a plywood front panel. However often it is said "Electricity is dangerous" so a large red neon glows when any mains-operated equipment circuit is 'live' even if the equipment is switched off. Everyone in the house knows that in an emergency knocking off that red neon-cum-switch puts everything out of action! These DPST plus neon switches are not cheap but their price could be the price of a human life so they are worth fitting even though they may never be needed. Each piece of equipment is switched on-and-off by means of a small push-button switch and has its associated neon indicating that the circuit is 'live'.

The remainder of the panel is taken up with the controls for the "pi-network coupler", mentioned earlier: switches for the routing of aerials to the receivers; switches for routing the audio to the amplifier and to tape-recorder sockets and so on. The aim has been to make DXing as easy as possible and to avoid having to stop operating to connect in a tape-recorder or some other gadget. It is a custom-built job and I would recommend anyone embarking on such a project to spend a lot of time in the design stage so as to get something that really suits their needs. Such a panel is expensive to build both in money terms and in time spent on the work and is not easy to modify at a later stage: this is my third essay in this field and 18 months after it was built I can already see that next Winter is likely to have me building Version No. 4 to accommodate various ideas that have since sprung to mind. Some prospect!

That then is my shack, or, at least, part of it. I've not mentioned the lazy DXers best friend - a time switch which allows you to check a channel whilst you are tucked up snug in bed! - nor the tape-recorders, nor the reference works that one needs nor..... But those are all subjects that must wait until next time we talk about shacks. See you next month, but for the present "So long" and Good DXing! Reports as usual should be sent to me at 16 Ena Avenue, Neath, Glamorgan SA11 3AD and if you want a reply enclose an s.a.e.

ETI TECH-TIPS


BASIC TRANSISTOR TESTER

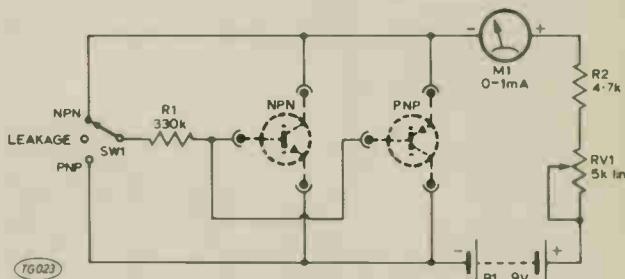

There are a number of parameters which determine a transistor's performance but the main ones for low voltage use are leakage and gain. The circuit shown above will indicate both. Two transistor sockets are required, one for NPN devices, the other for PNP; this simplifies switching. With the switch SW1 set on leakage the current passing through the device is indicated on the meter: modern transistors, even germanium types should show only the tiniest reading if any at all. For gain R1 is applied between base and collector. RV1 should be adjusted so that short-circuiting the emitter-collector contacts just registers full scale deflection.

Gain can be directly calibrated onto the scale but this is best done by noting deflections given by inserting transistors of known quality.

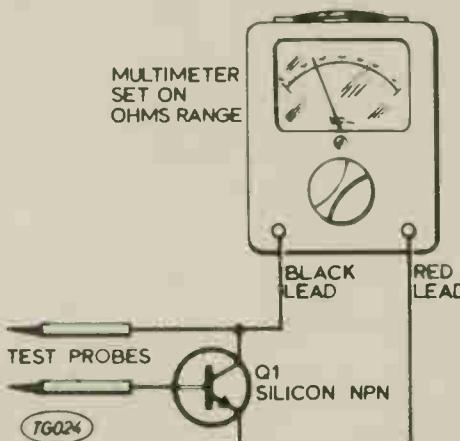MEASURING HIGH RESISTANCE ON LOW SENSITIVITY METERS



Many inexpensive multimeters are unable to give useful readings on the ohms range much above 47k. However, by using almost any silicon NPN transistor (BC107 for example) in the arrangement shown will give considerable deflections for quite high values. The meter's scale will not apply but by noting the readings from high tolerance, high value resistors and some interpolation, fairly accurate measurements can be made. Note that on a multimeter the Black (negative) lead connects to the battery positive on the ohms range.

TAPE NOW, PLAY LATER

with the

JONAN "FAB"



A new radio-clock recorder, the JONAN "FAB" ensures that listeners never miss im-

portant radio programmes. ITS SECRET is a remarkable clock which is preset to start its built-in cassette recorder at any hour.

If you find a programme scheduled inconveniently you merely set the clock and leave JONAN "FAB" to its job and return to hear the recorded version whenever you wish. JONAN "FAB" can also be used as an ordinary radio, cassette-recorder or clock radio.

Two simple controls preset the recorder; one dial selects the time, a second dial sets programme length. Sixty minutes can be recorded on one cassette. JONAN "FAB" receives medium wave and FM on battery or mains and is fitted with automatic level control, socket for external speakers, microphone (of course, there's one built-in as well) or telephone pick-up.

I enclose 3p stamp for illustrated leaflet

NAME _____

ADDRESS _____

JONAN

Send 3p for leaflets to:
275 West End Lane,
London N.W.6
01-794 9611

GETTING BORED WITH ELECTRONICS?

Some things are repetitive, once you have built an astable multivibrator, they tend to get boring—try a 555 timer? It works in mono or astable modes for long or short pulses (95p). How about building a radio tuner for your record player, the ZN414 chip makes this simple (£1.10). LEDs? We have a fantastic choice—LED lamps—TIL209 or HP4480, 4 for £1.50, 50 for £10; large lamps (HP4480), 35p each, 50 for £15, RED and GREEN LEDs £1 per pair. LED displays—TIL302 (or similar) £2.50 each, TIL312 (similar to MAN4) £2 each—limited quantity. TIL360 6 digit package £18, DL34 four digit package £15, DL62 (3") £6.50. Phosphor diode displays DG12 £2 each.

CLOCKS CLOCKS CLOCKS CLOCKS Bywood is now foremost in the LSI clock chip market (who else has four different clock chips in stock with two more on order?) MM5311—the original—£11.50, MK5017AN with alarm or radio controls £15.50. MK5017AA with alarm or MK5017BB with calendar, either of these two is offered with a PCB, socket and suitable displays (4DG12s) at £24.

Don't get bored, if none of the above fascinate you how about liquid crystal displays, DVM chips etc? This technology is here to stay. Bywood have got it or can get it—give us a try.

VAT. All prices above EXCLUDE VAT, add 10%. P. & P. Please add 10p post and packing.

You can have clock data sheets for a S.A.E. or our 1973 catalogue (2nd issue) for 15p. (And we haven't even mentioned our calculators yet—but they are in the catalogue.)

You may phone us for help on 0442 62757 and you can use your ACCESS card for phone or personal purchases—Service from Bywood!

BYWOOD

ELECTRONICS, 181 EBBURNS ROAD, HEMEL HEMPSTEAD, HERTS. 0442 62757

DISCOUNT COLOUR!

Perfect working order. Repolished cabinets. 30 DAY GUARANTEE!

19" DECCA £77

19" GEC £88

22" PHILIPS/DECCA £132

25" DECCA/BUSH/GEC/BRC 2000/PYE £110

CASH AND COLLECT PRICES, V.A.T. included.

3 or over less 10% discount

BRAND NEW 26" COLOUR TV CABINETS

Slight seconds without backs. All with doors in Dark Teak. Delivered for £10 cwo

MONO UHF TV'S

Sold complete but unserviced with tube tested. Good cabinets. Valve tuner type inc.—

BUSH 128, SOBELL 1000, GEC 2000, THORN 900. Singles £5 each (add £2 delivery). 6 for £25. Delivery extra.

Transistorised tuner type makes inc.: THORN 950, BUSH 141, GEC 2010 to 2038. Philips style 70. Singles £10 each (add £2 delivery). 6 for £50 delivery extra.

TRANSISTORS FOR BRC 3000

R2008 (Line) R2010 (Chopper)
Singles £1 each. Any twelve £10 inclusive. Send cwo.

Send SAE for list of UHF tuners, valves, tubes, washing machines etc. Open 6 days every week.

TRADE DISPOSALS

1043 Leeds Road, Bradford 3.

Tel Bradford (0274) 665670

and

Peacock Cross Industrial Estate,
Burnbank Road, Hamilton.

Tel Hamilton (06982) 29511

HARDWARE


Screws, nuts washers etc.

Sheet aluminium cut to size or in standard packs, plain or punched/drilled to spec.

Printed circuit boards for published designs or individual requirements, one-off or small runs.

Fascia panels, dials, nameplates etc in etched aluminium. 6p for details.

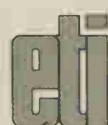Ramar Constructor Services,
29 Shelbourne Road,
Stratford on Avon, Warwickshire.



MINI-ADS

SPECIFICALLY
DESIGNED
FOR THE
SMALL
ADVERTISER

*See page 84 for
details on how
to book space*

THIS SPACE COSTS
£20 PER MONTH
FOR A MINIMUM
OF 3 MONTHS = £60.

THIS SPACE COSTS
£10 PER MONTH FOR
A MINIMUM OF
3 MONTHS = £30.

 **MINI-ADS**
SPECIFICALLY DESIGNED
FOR THE SMALLEST
ADVERTISER WHO WANTS
RESPONSE. MINI-ADS ARE
CHEAPER THAN THE
STANDARD RATE BUT MUST BE
BOOKED FOR AT LEAST 3
MONTHS.

THIS SPACE
COSTS £30 PER
MONTH, FOR 3
MONTHS = £90.

team up with the
new look 

IS YOUR BUSINESS SELLING ELECTRONIC EQUIPMENT?
IS YOUR BUSINESS SELLING QUALITY AUDIO EQUIPMENT?
ARE YOU LOOKING FOR EXPERIENCED STAFF?

THEN

TAKE ADVANTAGE OF OUR NEW CLASSIFIED SECTION
THIS SPACE COULD BE YOURS FOR ONLY £20 PER MONTH
FOR FULL DETAILS OF THE REALISTIC INTRODUCTORY RATES

CONTACT

ALEX G MELLON, ADVERTISEMENT MANAGER
ON 01-730 2136/7/8/9

OR WRITE TO: ELECTRONICS TODAY INTERNATIONAL
36 EBUARY STREET LONDON SW1W 0LW

FM TUNER

NELSON-JONES

Approved parts for this outstanding design (W.W. April 1971/2).

Featuring 0.75 µV sensitivity. Mosfet front end.
Ceramic I.F. strip. Triple gang tuning, 3V r.m.s.
output level, suitable for phase locked decoder,
as below. Designer's own P.C.B.

FURTHER PRICE REDUCTIONS

Basic Tuner Parts with Screening Box.
NOW LESS THAN £11.50. Please send S.A.E. lists.

NEW ALIGNMENT SERVICE

Details on request.

SOLID STATE TUNING INDICATOR

(W.W. April '72). Tuning is indicated by the balance of two light emitting diodes. The kit includes, LED's, high gain transistors, P.C.B., resistors, mounting kit and instruction booklet. Order T041. Price £1.72 plus P. & P. 10p, with two LED's (or £1.90 with extra LED for "stereo" lamp see decoder).

DIAL CHASSIS KIT

Now available—includes all dial drive components, dial plate, decoder mounting bracket, tuning scales, decoder-tuner tagstrips, etc., 4-way 2/3 pole rotary switch and instruction booklet. Price £2.15 plus P. & P. 17p (Note: may be purchased without dial drive components.)

PHASE-LOCKED STEREO DECODER KIT

Now with free LED "stereo on" light—complementing this superb decoder (W.W. Sept. '70). Suitable for wide variety of tuners including the NELSON-JONES TUNER.

Complete kit ONLY £7.50. P. & P. 16p.

NEW IC Stabilised PSU. S/C, overload protected, low ripple. £3.55. P. & P. 10p.

LIGHT EMITTING DIODES (Red)

Improved efficiency type, mech. identical to HP LED, panel or PCB mounting with free mounting clip—clear or black—please state. Order LED1A. Please add postage.

Monsanto miniature PCB mounting with radial leads. Order LED2. Please add postage.

NOW ONLY 35p each with connection data.

Note. Tuner metalwork and case now matches TEXAN

TEXAN AMP.

Please enquire about delivery.

AERIALS—3 ELEMENT VHF/FM (Outdoor)

A good aerial is essential for optimum Stereo Radio reception.

ONLY £2.00. P. & P. 40p.

Coax 5p/metre. (Masts and Fixing kits available).

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW

Phone Repton (028389) 3580

FREQUENCY COUNTER

If you want a frequency counter, either 10MHz or 40MHz guaranteed, you should consider our modules. Our crystal timebase has been supplied to Industry, Government research and Universities—now we can supply everything for measuring frequency.

COUNTER GATE: This unit converts TTL decade displays into a frequency counter, using only a reference and power supply. It provides the rest 'O' pulse and has display 'hold' facility, 10MHz guaranteed, 7-pin package, with data £9.90 each.

TIMEBASE I. Our popular G8 timebase gives 13 simultaneous TTL frequencies (10Hz to 10MHz) with good stability (0.005%) normally from stock, £23.00 each.

TIMEBASE II. Electronically switched version, covers 1Hz to 100kHz with outputs at 1MHz and 10MHz. Ideal for counters or ATE, £24.00 fibreglass pcb.

Ditto, but larger pcb to take our counter-gate package £24.50

DISPLAYS. Our LED displays at £12.00 each will be announced this month. They will be built and 10MHz tested. Supplied on fibreglass pcb. All normal counter facilities.

PRESCALERS and **PREAMPLIFIERS** will be available next month.

LOGIC DETECTOR for TTL, a LED shows Logical 1. Operation to 12MHz, input 150k Ω with protection to mains voltage. These units do not have to be hand-held. Supplied boxed, with leads and clips £6.50 each. Quantity discounts 10-up.

Send for further details (private enquiries: 3p stamp, please).

Our module catalogue available at 25p + 5p P & P.

All goods sold subject to our Terms and Conditions.

SPOTRON (U.K.) LTD.

P.O. BOX 81, WALLINGTON, SURREY

Telephone (normal office hours) 01-669 0571

7 SEGMENT LED Displays.

Lowest cost.

0.325" characters. Continuous segments (*not dotted*)

GaP high efficiency Red Light Emission
TTL compatible.

Common anode and common cathode
types available.

LOW COST

Prices:

Common anode type £2.46 each

£1.97 25+


Common cathode £2.33 each

£1.83 25+

½ dig. common anode £2.33 each

7447 decoder driver (for C.A.) £1.30 each

All devices available from stock.

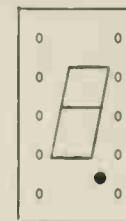

V.A.T.

FROM APRIL 1st ADD V.A.T. AT 10%
TO ALL PRICES

SPECIAL OFFER

4 function 8 digit display calculator with CONSTANT KEY, fixed or FLOATING DECIMAL, clear last entry key.

Complete with BUILT IN RECHARGEABLE CELLS, mains charging unit, AND carrying case. Full 12 months guarantee.

ONLY £45.00 p. & p. 50p.

M.Sc. Course in Electrical Engineering

with specialisation in any one of the following:

Electrical Machines,

Power Systems,

Communication Systems,

Electronic Instrumentation Systems,

Control Engineering and Digital

Electronic Systems,

Design of Pulse and Digital Circuits

and Systems,

The Course, which commences in October 1973, may be taken on a Full Time, Part Time, sandwich or Block Release basis, and is open to applicants who will have graduated in Engineering or Science, or who will hold equivalent qualifications, by that date. The Science Research Council has accepted the Course as suitable for the tenure of its Advanced Course Studentships.

Research in Electrical Engineering

Applications are also invited from similarly qualified persons who wish to pursue a course of research leading to the Degree of M.Phil. or Ph.D. in any of the above subjects.

Application forms and further particulars from the Head of the Department of Electrical Engineering (Ref: M.Sc. 8), The University of Aston in Birmingham, BIRMINGHAM B4 7PB.



**THE UNIVERSITY
OF ASTON
IN BIRMINGHAM**

INDEX TO ADVERTISERS

Advance Calculators	35
Appollo Aerials	70
Arrow Hart	80
BIET	Cover iii
Bi-Pak	28, 29
Bi-Pre-Pak	4
Bywood Electronics	12
Chromasonic Electronics	14, 15
Classified Ads	83, 84, 85
Decon	77
Eddystone	24
Electronic Brokers	78, 79
Gerald Myers	67
Henry's Radio	23
Interphonic	8
ITT	70
J Bull Electrical	10
J T Eden	6
Minikits Electronics	33
RCS Electronics	67
R Smith Aerials	26
Sansui	Cover iv
Teleton	Cover ii

NEWSAGENT:

Please deliver ELECTRONICS TODAY INTERNATIONAL for 12 months, starting with the issue:

NAME

ADDRESS

GIVE THIS COUPON TO YOUR LOCAL NEWSAGENT

USE
THIS COUPON



**costs
no
more
delivered
to your
door ...**

...by your local newsagent

For only £2.40 a year (12 issues at 20p each) you ensure that every copy of ELECTRONICS TODAY INTERNATIONAL will arrive on your doorstep as soon as it is published — and that you'll never miss out on it if an issue happens to sell out.

electronics
TODAY
INTERNATIONAL

FREE!

Over 150 ways to engineer a better future



**find out how
in just 2 minutes**

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BEI08 Aldermaston Court, Reading RG7 4PF.



Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know

about **Radio & Electronics**

maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

MECHANICAL

- A.M.S.E. (Mech.)
- Boiler Inspect.
- & Operation
- C & G Eng. Crafts
- C & G Fabricat.
- Diesel Eng.
- Eng. Inspection
- Eng. Metallurgy
- Inst. Eng. & Tech.
- Inst. Motor Ind.
- Mainten. Eng.
- Mechanical Eng.
- Sheet Metal Work
- Welding

ELECTRICAL & ELECTRONIC

- A.M.S.E. (Elec.)
- C & G Elec. Eng.
- C & G Elec. Inst.
- C & G Elec. Tech.
- Computer Elect.
- Elec. Maths
- Elec. Science
- Electronic Eng.
- Electrical Eng.
- Install. & Wiring
- Meters
- & Measuring Instruments

MANAGEMENT & PRODUCTION

- Auto. Control
- Computer Prog.
- Electronic Data Processing
- Estimating
- Foremanship
- Inst. Cost & Man.
- Accountants
- Inst. Marketing
- Management
- Metrication
- Motor/Trade Man.
- Network Plan.
- Numerical Cont.
- Operational Research
- Personnel Man.
- Planning Eng.
- Production Eng.

AUTO & AERO

- Aero Eng.
- A.M.I.M.I.
- A.E.C. Cert.
- Auto Engineer.
- Auto Repair
- C & G Auto. Eng.
- Garage
- Management
- MAA/IMI Dipl.
- Motor Vehicle Mechanics

CONSTRUCTIONAL

- A.M.S.E. (Civil)
- Architecture

Coaching for many major exams.
including ONC, C & G, etc.

Constructional-cont.

- Building
- Building Drawing
- Build. Foreman
- Carpentry & Join.
- Civil & Municipal Works
- Engineering
- Constructional Engineering
- Construction Surveyors
- Institute
- Clerk of Works
- Council Eng.
- Geology
- Health Eng.
- Heat & Vent.
- Hydraulics
- Inst. of Builders
- Inst. Works & Highway Sup.
- Painting & Dec.
- Public Hygiene
- Road Engineer.
- Structural Eng.
- Surveying

GENERAL

- Agricultural Eng.
- Council of Eng. Inst.
- Farm Science
- General Educat.
- Gen. Plastics
- Pract. Maths
- Pract. Slide Rule
- Pure & Applied Maths
- Refrigeration
- Rubber Tech.
- Sales Engineers
- Tech. Report Writing
- Timber Trade
- University Ent.

G.C.E.

- 58 'O' & 'A' LEVELS SUBJECTS
- Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BEI08
Aldermaston Court, Reading RG7 4PF

ON BEI08

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____


AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Harry Saunders

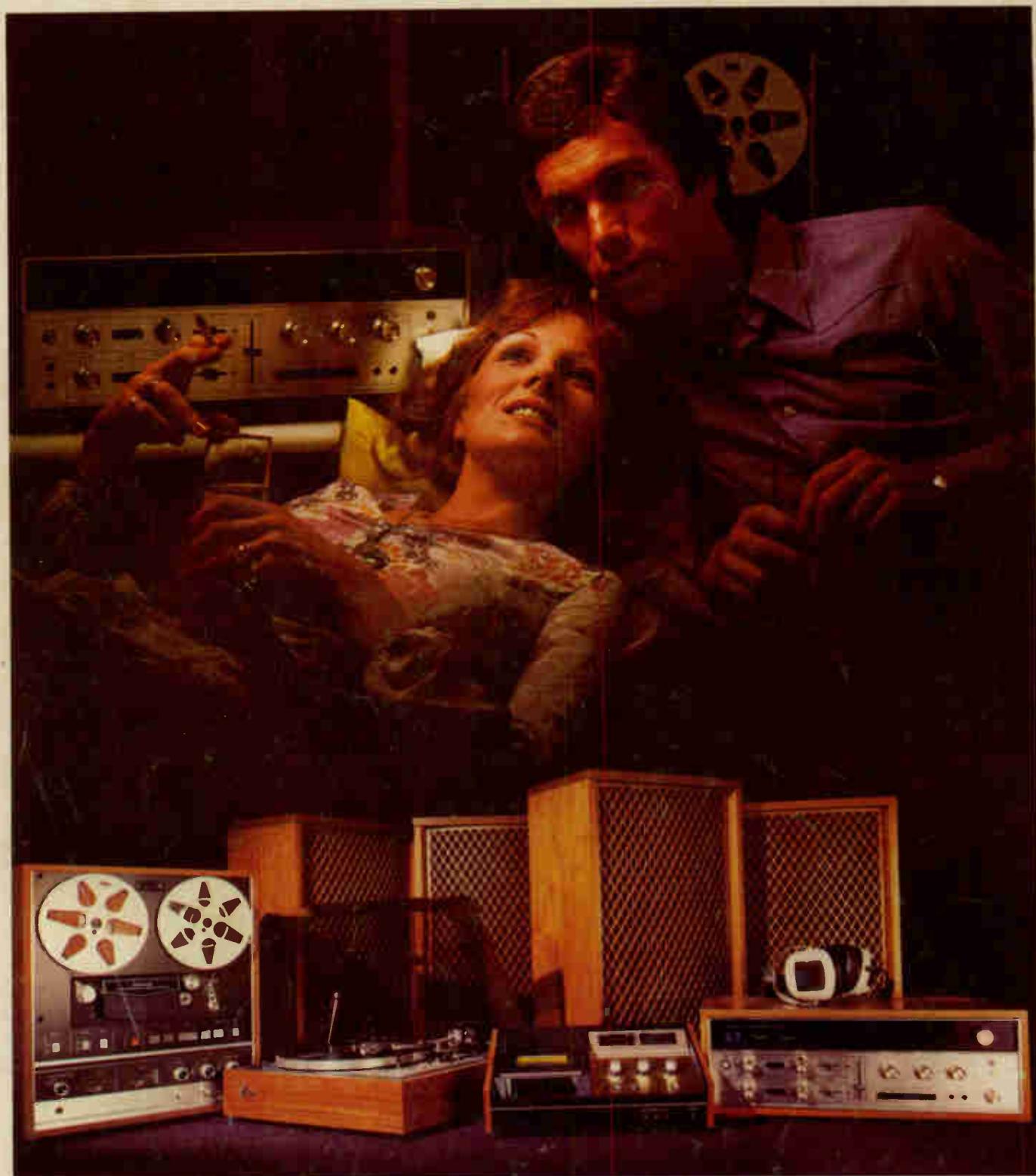The entrancing world of SANSUI's quadraphonic 4-channel stereo.



The complete range of Sansui's sophisticated
4-channel equipment at your dealer's now!



4-CHANNEL STEREO

England : VERNITRON(UK)LTD. Thornhill Southampton SO9 5QF Tel : Southampton 44811

SANSUI AUDIO EUROPE S.A. Diocesi di Bruxelles, Avenue Louise 38/66, 1050 Antwerpen, Belgio
SANSUI ELECTRIC CO., LTD. 14-1 Ichinomiya-cho, Nakahara-ku, Yokohama, Japan

SANSUI ELECTRONICS CORPORATION 32-17 61st Street, Woodside, New York 11377, U.S.A.