

# electronics today international

JULY 1977

35p

## NERVOUS TENSION?

LEARN TO RELAX  
WITH OUR  
GSR MONITOR

8-PAGE  
**DATA**  
SUPPLEMENT

TV GAMES RIFLE  
ACTIVE FILTERS

TACHOMETER

MICROAMP

MPU CALCULATOR REVIEW



WIRING PEN OFFER

# WATFORD ELECTRONICS

33 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 37774

ALL DESIGN & BRAND NAME COMPONENTS AVAILABLE FOR THE FOLLOWING CATEGORIES  
DISPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH ON DELIVERY  
P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL  
INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY  
WELCOME. P&P ADD 25p. To ALL ORDERS UNDER £10.00 OVERSEAS ORDERS  
POSTAGE AT COST. AIR SURFACE SEND S.A.E. FOR OUR FREE LIST

**VAT** (Value Added Tax) Applicable to U.K. Customers only. Unless stated otherwise we add 8% VAT to the price of all goods. VAT is shown in parentheses in the list. VAT is not charged on exports outside the U.K.

We stock many more items than listed. Send S.A.E. for our full list. It lists 5000+ items. We are a member of the British Electronic Equipment Council. Registered under paragraph 28 of the Electronic Equipment Council Regulations. Registered under paragraph 28 of the Electronic Equipment Council Regulations. Registered under paragraph 28 of the Electronic Equipment Council Regulations.

Sales tax: Sample Free Car Parking space available

**POLYESTER CAPACITORS** 50p 150V 22p 250V 45p 500V 100p

**QUINER 1000V** 150V 22p 250V 45p 500V 100p

**POLYESTER RADIAL LEAD** 150V 22p 250V 45p 500V 100p

**FEED THROUGH CAPACITORS** 150V 22p 250V 45p 500V 100p

**ELECTROLYTIC CAPACITORS** 150V 22p 250V 45p 500V 100p

**150V 22p 250V 45p 500V 100p**

**150V 22p 250V 45p 500V 100p**

**150V 22p 250V 45p 500V 100p**

**150V 22p 250V 45p 500V 100p**

TTL 74s

|    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |     |
|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|-----|
| 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 | 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 | 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 | 91 | 92 | 93 | 94 | 95 | 96 | 97 | 98 | 99 | 100 |
| 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 | 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 | 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 | 91 | 92 | 93 | 94 | 95 | 96 | 97 | 98 | 99 | 100 |

|   |   |   |   |   |   |   |   |   |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |     |
|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|-----|
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 | 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 | 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 | 91 | 92 | 93 | 94 | 95 | 96 | 97 | 98 | 99 | 100 |
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 | 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 | 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 | 91 | 92 | 93 | 94 | 95 | 96 | 97 | 98 | 99 | 100 |

|   |   |   |   |   |   |   |   |   |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |     |
|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|-----|
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 | 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 | 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 | 91 | 92 | 93 | 94 | 95 | 96 | 97 | 98 | 99 | 100 |
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 | 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 | 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 | 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 | 91 | 92 | 93 | 94 | 95 | 96 | 97 | 98 | 99 | 100 |

It's Here!

TV GAMES

## The "Olympic" Games Kit

The "Olympic" Games Kit is a complete set of electronic components for building a TV game. It includes a detailed circuit diagram, a parts list, and a step-by-step assembly guide. The kit is suitable for beginners and experienced hobbyists alike. It contains all the components you need to build a fun and challenging TV game. The components are of high quality and are guaranteed to last. The kit is a great value for money and is a must-have for anyone interested in electronics. The kit is available in a convenient box and is easy to store. It is a great gift for anyone who loves electronics. The kit is a great way to learn about electronics and to have fun at the same time. It is a great way to spend your spare time and to learn something new. The kit is a great way to improve your skills and to challenge yourself. It is a great way to learn about the world of electronics and to have fun at the same time. The kit is a great way to spend your spare time and to learn something new. It is a great way to improve your skills and to challenge yourself. It is a great way to learn about the world of electronics and to have fun at the same time.

SPECIAL OFFER TO ETI READERS  
£27.85

£34.50

AY-3-8500 (E55)

1950

**electronics today**  
international

2002年 第10期

## Features

|                                                                                               |    |
|-----------------------------------------------------------------------------------------------|----|
| <b>SPECIAL COMPANILE PROGRAMMABLE PERIPHERALS</b><br>A System of Interconnecting Peripherals  | 10 |
| <b>SOFTWARE TECHNIQUES FOR HARDWARE TEST</b><br>An Introduction to Programming Test Equipment | 18 |
| <b>ACTIVE FILTERS - PART I</b><br>Four Methods for Designing Active Filters                   | 23 |
| <b>VALUE BOARD - ON THE HORIZON</b><br>Aboard the Value Board, a New and Exciting Product     | 34 |
| <b>BYPASS DATA SUPPLY BOARD</b><br>A New Data Supply Board for the IBM 7090                   | 39 |
| <b>GREYSCALE</b><br>A New Color System for the IBM 7090                                       | 49 |
| <b>COMPONENTS</b><br>A New Component for the IBM 7090                                         | 55 |
| <b>ELECTRONICS - IT'S BACK - PART II</b><br>A New Component for the IBM 7090                  | 61 |
| <b>TECH TIPS</b><br>A New Component for the IBM 7090                                          | 66 |

## Data Sheet

|                              |    |
|------------------------------|----|
| CLUSTER = WAVEFORM GENERATOR | 00 |
| COM TYPE = STRACTION COMP    | 00 |

## News

### Information

|                                |     |
|--------------------------------|-----|
| Training, Management Selection | 4   |
| Recruitment                    | 10  |
| Flow of New Members into       | 10  |
| Organizational                 | 4-7 |
| Structure                      | 1-3 |
| Process                        | 10  |
| Training                       | 10  |
| Organizational                 | 10  |

### Special offer

EDITORIAL AND ADVERTISING OFFICES

HALVOR W. MOORSHEAD

ADD 21274 1004

**JIM PERRY**

TONY ALSTON  
Brentwood, Tenn.

### Preparation

**SANDRA ZAMMIT MARRARA**

**Admission: \$125.00**

KIM HAMILTON

of *Aspergillus* spores

[illegible]

## INTERNATIONAL EDITIONS

1998  
 1999  
 2000  
 2001  
 2451  
 2452

1. **Introduction**  
 2. **Methodology**  
 3. **Results**  
 4. **Discussion**  
 5. **Conclusion**  
 6. **References**  
 7. **Appendix**  
 8. **Index**  
 9. **Table of Contents**  
 10. **Figure 1**  
 11. **Figure 2**  
 12. **Figure 3**  
 216. **Figure 207**  
 217. **Figure 208**

[illegible]

© 2004 Blackwell Publishing Ltd, *Journal of Internal Medicine* 255: 103–110

**INTERVIEW OF**

2000-2001  
2001-2002

understanding of the importance of social networks and the support they can provide. It is important to note that the study was limited to a specific population and the results may not be generalizable to other groups. Further research is needed to explore the long-term effects of the intervention and to identify the factors that influence its effectiveness.



# BI-PAK

High quality modules for stereo, mono and other audio equipment.



NEW

PUSH-BUTTON

## STEREO FM TUNER

OUR PRICE ONLY

£20.45

Fitted with Phase Lock-loop Decoder

STEREO 30 MMS 1 PS12 7530

Typical Specifications  
Sensitivity 3 volts  
Dynamic range 20db  
Supply required 20-30v or  
50 Hz a.c.

## MPA 30



£2.85

VAT  
ADD  
12 1/2%

POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for small. Min £1.00

## STEREO PRE-AMPLIFIER

## PA 100

OUR PRICE  
£13.75

## NEW AL30A

10w R.M.S. AUDIO  
AMPLIFIER MODULE

## STEREO 30

COMPLETE AUDIO

3 x 7 WATTS  
R.M.S.

£16.25

MR. 60 AUDIO KIT  
PRICE £20.55  
TEAM 60 AUDIO KIT



ONLY £3.60

- Input Imp. 10k
- Gain 20 to 30 db
- Low distortion < 1%
- Low impedance 16
- Sensitivity 100 mV
- Two outputs, Stereo
- Frequency 20 Hz to 20 kHz
- 10w R.M.S. 100 Hz
- 100 Hz to 10 kHz
- 100 Hz to 10 kHz



## AL 60

25 Watts [RMS]

- Max. Max. Amp. 100V
- Frequency response 20Hz to 100kHz
- Distortion better than 0.1% at 1kHz
- Supply voltage 18-24V
- Thermal Protection
- Design Improvements
- Load 3.6, 8 or 16 ohms
- Signal to noise ratio 80db
- Overall size 63mm x 105mm x 13mm

£4.35

## NEW PA12

## PA12

12Watts [RMS]

£6.70

Module 12watts 100Hz to 100kHz  
Supply voltage 18-24V  
Thermal Protection  
Design Improvements  
Load 3.6, 8 or 16 ohms  
Signal to noise ratio 80db  
Overall size 63mm x 105mm x 13mm

## PS12

12Watts [RMS]

£1.30

## Stabilised Power Supply Type SPM80

Transformer 5MT80  
£2.60 + 12p postage

£3.75

# BI-PAK

SHOP AT 18 BALDUCK ST WARE HERTS  
OPEN 9.15-5.30 Mon-Sat

P.O. BOX 6, WARE, HERTS.

# news digest

## HANDY METER



Teleonic, Altair UK, announced the new M22 Digital Multimeter from Data Tech at this year's All Electronics Show in London last month. The M22 has five full functions, 0.1% accuracy, handheld portability, 200 hours battery life, ac or dc current to 20 A.

It measures dc volts from 100mV to 1 kV, ac volts from 100mV to 750V, resistance from 0.1 ohm to 20 megohms, and dc or ac current from 100 nanoamps to 20 A.

The Model 22 can be carried by hand, used on a bench stand or worn like a wrist watch for two handed probing and bug-wrested people. The reading hold feature should be used when measuring difficult to reach points. The reflective liquid crystal display gives clear, concise information and is easily readable from wide viewing angles. Teleonic, Altair UK, 2 Castle Hill Terrace, Maidenhead Berks, SL6 4JR.

## BIRTHDAY PRIZEWINNERS

Well, we said it wasn't easy! Our April competition attracted hundreds and hundreds of entries. Unfortunately just less than 10% were correct! Having thus insulted nine tenths of our reader's here are the CORRECT answers: A) Skeleton project pot B) Solderless IC sockets C) Compression transistor D) Fuse holder E) Photo plug F) Fuse holder cap and fuse G) Potted bridge rectifier (R/S) H) Slider control knob

The five stalwarts who emerged as winners were R. H. Hearn, 10 Speedwell Close, Polesfield, Lowestoft, Suffolk NR3 1TD. T. Davis, 2 Northcotes Square, Exeter, Devon EX4 4ES. A. P. Thomas, 40 Rowley Road, Tottenham, London N15 4R. Strickland, 18 Rupert Road, Newbury, Berks. R. P. Midford, 95 Elm Close, Bristol BS12 4RS. To all those who entered and failed, thank you for entering, better luck next time.

## VOLUNTEERS NEEDED

Deal Fax is a research group making and distributing Tele-text decoders to the deaf and the hard of hearing to enable them to pick up CeeFax and Oracle. The units are rented out to the people for a nominal sum. Deal Fax have applied for charitable status, and make not a bent penny from the exercise.

However, someone has to build the units in the first place, and that's where you come in. If you're feeling like helping someone and are in need of something challenging to put together, contact the Secretary, Mrs Sheena Carter at 99 Wentage Road, Wallingford, Oxford.

## GRAPHICALLY CHEAP

Compelec Electronics have available a circuit board called the VTI which provides all the electronics to turn a television receiver or monitor into a VDU. In addition, the card provides an 8-bit parallel port for interface to a standard ASCII keyboard.

The card is designed to plug into any microcomputer system employing the S-100 bus structure. The microcomputer board looks like 512 (1024 as an option) memory locations. Data can be stored in or retrieved from this block of display memory by the microcomputer just like standard RAM. The character generator ROM contains the full ASCII upper and lower case alphabet, the Greek alphabet, a set of graphics characters and various symbols and punctuation marks.

In kit form the VTI with 1024 bytes of RAM providing a display of 16 lines of 64 characters, costs £210 plus VAT from Compelec Electronics, 310 Kilburn High Road, London NW6 5BB.

## DEE TO ENT

Precision Monolithics have introduced a new series of 2-dig BCD monolithic multiplying D/A converters with fast settling time, complementary high impedance current outputs and universal logic inputs. Direct interfacing with MOS TTL, DTL, ECL and HTL is provided by an optional logic threshold adjustment. The DAC-30 is the first BCD DAC to interface directly with the high impedance NMOS and PMOS outputs of microprocessors. RAMs, Buena (Trumpet) Limited, Holford House, 17/27 High Street, Haverstock, Herts.

## I'M SORRY I'LL PRINT THAT AGAIN!

System 68, May 77. Link between common pin of Reg 3 and earth omitted on PCB layout.

## SINTEL ATING NEWS?

A 4th special ad appears on page 74 this month. Whilst not an actual E.T.I. Reader Offer it will be of great interest to most readers. SinTel have chosen E.T.I. through which to make a whole list of specially priced components available. You won't find these in any other electronics magazine should you be foolish enough to read an

## CRAFTY VIDEO?

VideoCraft have released a Teletext decoder that costs less than half that of comparable decoders presently available. It is supplied as a complete kit comprising an (assembled and fully tested) Texas Tifax Teletext decoding module, power supply, interface module (supplied as a kit), an assembled and tested cable connected remote control and complete instructions for installation in most (common) television receivers. Due to the compact nature of the Tifax module and interface module installation within most receiver cabinets is no problem.

Facilities include seven colours, upper and lower case characters, graphics, time coded display and newflash and subtitle inserts in the TV picture. To enable them to supply the correct interface module and instructions they must know your television set make model and it possible chassis type. The kit costs £180 + 8% VAT. (Advertcraft, Assets House, Fiverton Street, London SE11P 2QR)

## I.T.T. v. THE REST

It may interest you to know that ordering a "4xx Series TTL chip is not as simple as it might at first seem. It has come to our notice that at certain numbers in this series can refer to chips with completely different logic functions (nasty).

Although for most of the range it does not matter from which manufacturer the devices come the table below shows that for a few chips I.T.T. have gone it alone in the allocation of numbers.


### I.T.T.

- \*4 5 Quad 2 I/P NAND Schmitt
- \*4 1 B Quad 2 I/P OR power driver (10 A, 100 m A)
- \*4 130 Quad 2 I/P OR power driver (1.5 A, 100 m A)

### THE REST

- \*4 5 Quad 1 A OR NOR gate
- \*4 30 3 to 8 line decoder/demultiplexer
- \*4 130 Dual 2 to 4 line decoder/demultiplexer

## WHAT A CHARACTER!

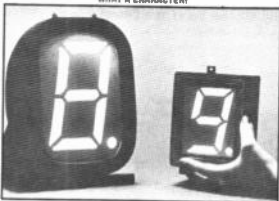


The English Electric Valve Company has developed a high brightness character display tube which operates on a different principle to the more usual CRT. The display can be manufactured in sizes up to about 25 inches diagonal and can display special characters.

The tube operates in a manner similar to a cathode ray tube: a front face plate carries a high luminance, high-efficiency phosphor overpiped by a flood beam of electrons from the

cathode. Placed between the cathode and the faceplate is a seven-segment mask with a lead from each of the segments brought out separately so they can be switched at high speeds using a control voltage of 5 V at 10 MΩ input resistance.

The supply voltage is 12 V dc. The power consumption is 2 W total for the 4-inch (E727) and 3 W total for the 8-inch tube (F728) P.E.V., Chelmsford, Essex, CM1 2QU.

## GENERATES FUNCTIONING BRITAINS?

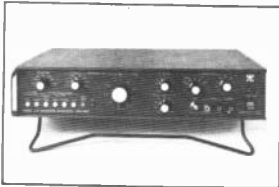

The Pro-Sci Scientific Instruments 1211 Function Generator. Sine, square, triangle, ramp, and variable duty cycle pulses. Frequency range 0.04 Hz to 5 MHz. And most important it's 100% British! A versatile unit with full sweep facility, and all the other bits and bobs these things are supposed to have. It is designed to compete with the likes of the HP 3310A, but at a cost of £425 is considerably cheaper. PSI Ltd, Lady Lane Industrial Estate, Hatfield, Herts AL9 6DQ.

# Metac SPRING BARGAINS

## THE METAC DIGITAL CLOCKS

• COMPLETE KIT •



- Pleasant green display 24 Hour readout
- Extra Simultaneous Accuracy Fully automatic
- Pulsating alarm Push button setting
- Bunking time in Attractive alarm tone
- Easy to follow instructions Size 6 x 4 x 2
- Heavily shielded PCB acc apt components

A professional product for the home constructor has been designed by engineers using the most modern techniques and components will support both the well-used hobbyist and the more sophisticated user for future expansion - he is considering everything except a major loan for any loans required are a small following over solder screened ver and a 100 uF capacitor.

**KIT PRICE £9 60**

• 70p VAT FRP incl

## ALARM CLOCK KIT

by alarm plus

- 24 Hour Alarm
- Minute Register
- Memory Save

**KIT PRICE £11 60**

• 62p VAT

## BRITAIN'S TOP SELLING CLOCK

**3 YEAR GUARANTEE** **ALARM CLOCK** **THOUSANDS SOLD**  
 Fully built in version. Super-quiet • WITH SLEEP-OVER FEATURE



- Bright single Hour Display
- Built-in 24 Hour Display
- 4 Hour Alarm
- Minute Register
- Alarm Set Indicator
- Accurate Silent Timekeeping
- Inexpensive Designed and Built in Britain

Push-over reset

**COMPLETE CLOCK**

**£13.43**

• £1 97 VAT

## THE 'METAC' DIGITAL WATCHES

### THE GREEN EXECUTIVE AMERICAN MADE LCD

Continuous 8 digit display with back-light




Hours, Min, Sec, Date  
 Solid heavy metal case  
 A superb men's watch

**£32.41**

• £2 90 VAT
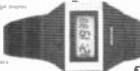
### THE BLACK WATCH by BULER SWISS PRECISION MADE LCD

Continuous 8 digit display with back-light



Hours, Min, Sec  
 Month, Date  
 Auto 4 year calendar  
 Green-Med epoxy back cover

**£30.55**

• £2 46 VAT

### THE TIMESAND by FAIRCHILD AMERICAN-MADE LCD

Continuous 8 digits with back-light



Hours, Min, Sec  
 Month, Date  
 Auto 4 year calendar  
 Superb metal bracelet

**£26.95**

• £2 16 VAT

### THE SILVER BAND by TIME-MICRO BRITISH-MADE LED

Continuous 8 digits



Hours, Min, Sec  
 Month, Date  
 Auto 4 year calendar  
 Quality metal bracelet

**£17.95**

• £1 43 VAT

## SAME DAY DISPATCH

Orders received before 4pm are posted same day. Cash Cheque Postal Order Visa Amex. Access orders quote name address and post number

## Metac-Electronics and Time Centre

### GIVE YOURSELF A TREAT

Gifts that give you a well-earned rest for yourself and your family. All top quality electronic clocks, digital watches, electronic games and battery powered toys.

### DAVENTRY

57 HIGH STREET  
 DAVENTRY  
 NORTHANTS  
 TEL (032 72) 70645

### SEND YOUR ORDER TO

### UXBRIDGE

3 THE NEW ARCADE  
 HIGH ST., UXBRIDGE  
 MIDDLESEX  
 TEL. 0345 600000  
 (0000) 50001



SEE OUR COMPONENTS ADVERT ON PAGE 38

SHOWROOMS OPEN 9.30 DAILY




## UPDATE 1: 3,4000 more Transistor Substitutes

The most  
comprehensive,  
low-cost,  
single volume  
coverage  
of transistors  
you can buy.
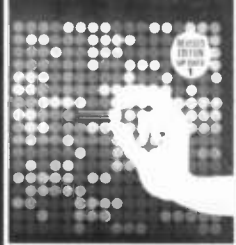
### Towers' International Transistor Selector

T.D. Towers, MBE, MSc, BSc, CEng, MInstP

Over 10000 transistor, diode, thyristor and triac types with  
domestic and international specifications, manufacturers and pinout diagrams



# We've got the new one!

COMPLETELY REVISED. 30% MORE COVERAGE. ONLY £5.00 INC. P & P.

When the first edition of this excellent book was published in 1975 ETI was the first to offer it.

We are doing it again!

UPDATE 1 increases the coverage of transistors by about 30% on the first edition.

European Protection Standard devices increase by 1500 and now ensure a very comprehensive coverage of Philips, Siemens, Telefunken and Texas Instruments in Europe.

The Japanese 2S Standard Devices coverage has been increased from 1850 to 3400 and a further 800 American 2N devices have been updated.

The original 10,000 entries have been fully edited and this new production has been clearly printed from new computer setting.

Your order will be processed on the day of receipt.

To: ETI BOOK SERVICE  
PO BOX 79, MAIDENHEAD, BERKS SL6 2EG

Please send me: \_\_\_\_\_ copies of  
Towers' International Transistor Selector  
Revised Edition (1st Date) at £5.00 each plus order

which I will enclose under £4.00  
made payable to ETI BOOK SERVICE

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_



**Gaps?**



**Gaps?**



**Gaps?**



**Gaps?**



It can be a nuisance, can't it, going from magazine to magazine? "Sorry guys, don't have it" isn't one should be out soon." Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the magazine's going to be sure to put his order for the next issue - but we're glad to say it doesn't happen very often.

Do yourself, your magazine and us a favour. Place a regular order for ETI: your magazine will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember - we'll do it for you.

For a subscription, send us £5.00 (£7.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

ETI Subscription Service  
Electronics Today International,  
26-27 Oxford Street, London W1R 1RF



**ETI PROJECT**

**LEARN TO REDUCE TENSION WITH ETI's**

# GSR MONITOR

**This galvanic skin response monitor provides a means of measuring the minute variations in skin resistance which research has linked to the emotional state of a person**

THE BEST WAY to start experimenting with biofeedback is to use a galvanic skin response monitor, a device which measures changes in skin resistance. In March 1977, we published an article which covered the background and theory of biofeedback, and we discussed the various types of biofeedback instruments which are available. The GSR monitor is the most simple to use; the electrodes can be simply attached to the fingers with straps and the technique of using the machine can be quickly learned.

Skin resistance changes with changes of emotional state. When tension increases, the skin resistance falls; when tension decreases, there is an increase in skin resistance. (Some biofeedback instruction manuals speak in terms of conductivity rather than resistance and state measurements in mhos, and the meter we use gives a positive deflection for decreasing resistance.)

The connection between skin resistance and tension is not fully understood. Tension affects sweat glands and is in the changes in the sweat glands there is a change in the membrane permeability of the skin and this change in permeability is the major cause of changes in electrical activity.

A more than a century ago, a scientist named W. Ch. Fere discovered that the resistance of the skin to a small electric current changed in response to aroused emotions. This information has since been used in various ways; one obvious example is the polygraph, or lie detector, which responds to the tension generated when a person is lying.

It was not until 1967 that Dr. J. Kamiya was able to conduct a series of



# GSR MONITOR


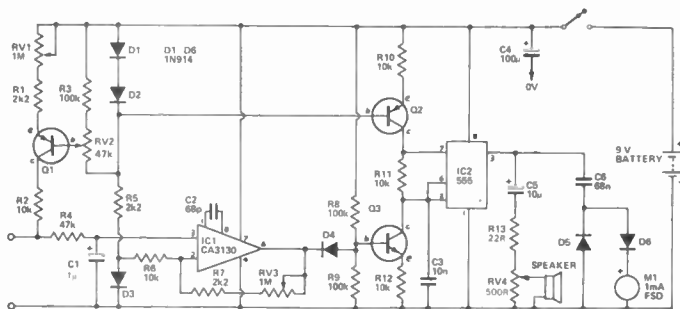


Fig. 1. Circuit diagram of the GSR monitor.

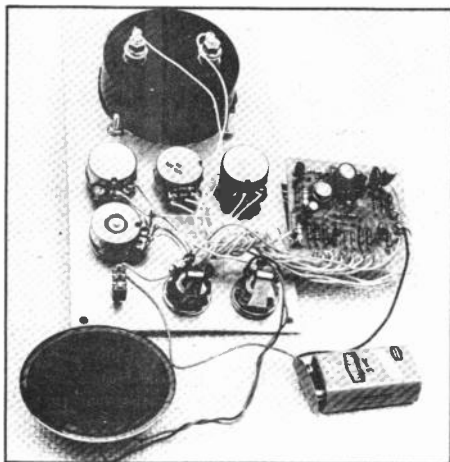**WARNING: THE GSR MONITOR SHOULD NOT BE USED WITH A MAINS POWER SUPPLY.**



The picture above shows the internal layout of the GSR monitor. The wiring from the PCB to the front panel, loudspeaker and meter is clearly shown.

## HOW IT WORKS

Transistor Q1 acts as a constant current source - the actual value can be varied over a large range by RV1 and over a limited range by RV2. These act as the coarse and fine level controls. This current is passed via R2 to the probes. The voltage developed across the probes is proportional to the skin resistance and is fed to the input of IC1. This amplifies the signal with reference to 0.6 V (drop across D3) and the gain is variable by RV3.

The second IC is an NE555 oscillator where Q2 provides a constant current (about 60 uA) to the capacitor C3. When the voltage on C3 reaches 6 V the IC detects this and shorts pin 7 to ground, discharging C3 via R11. This continues until the voltage reaches 3 V at which point the short on pin 7 is released, allowing C3 to recharge. The output of the oscillator is connected to a speaker via the volume potentiometer RV4 and the meter via C6 and the diodes D5 - 6. The meter operates in reverse sense i.e. usual, a low resistance gives full scale (or high tone) and high resistance gives zero (or low tone).

We vary the frequency of the oscillator and the meter reading by robbing some of the current supplied by Q2 into Q3. In this way the frequency can be lowered and actually stopped. Transistor Q3 is controlled by IC1 completing the connection between the probes and the output.

### Getting hold of components

Nothing here to trouble the constructor

### Cost of construction

Should be about £5.00 excluding boxing and meter.

experiments with brain waves, found that with feedback his subjects developed the ability to produce 'Alpha waves' at will.

Dr. Kamiya's experiments created considerable interest and started investigations into whether other bodily functions could be brought under conscious control. Since that time it has been demonstrated that with feedback it is possible for people to control heart beat, blood pressure and temperature — all previously considered to be automatic bodily functions mostly beyond conscious control.

Of course it should be stated that various mystics and yogis have previously demonstrated this type of ability but the fascination of biofeedback is the speed and ease with which this type of control can be learned.

Biofeedback has exciting medical possibilities. GSR machines are being used by therapists for the treatment of many disorders related to tension. The average person will find a GSR machine mainly useful for relaxation training. With the GSR machine it is possible to recognise tension and learn how to decrease tension levels. This type of training is so effective that the machine quickly becomes unnecessary.

However not everyone suffers from tension. The biofeedback machine can be a fascinating toy to play with. Discovering that you can bring an internal bodily function under conscious control with the same ease that you can twitch your nose is most interesting. And of course you can then perfect this ability just as you perfect your ability at a game like tennis. For many people this is reason enough to build this machine.

### What you do with it once you have built it

The ET1 GSR monitor has an on/off switch, a sensitivity control and fine and coarse level controls. The machine also has a connection for headphones.

To start relaxation training, you'll need a comfortable chair, low lighting and no distractions. Taking any type of drug can interfere with your ability to relax. This applies to alcohol and cigarettes. Attach the electrodes to the fleshy part of the first two fingers on one hand — firm but not too tight (the non-dominant hand is recommended). Set the sensitivity control to minimum and the fine level control to mid-range. Turn the volume control to minimum. Now you have to set the level with the

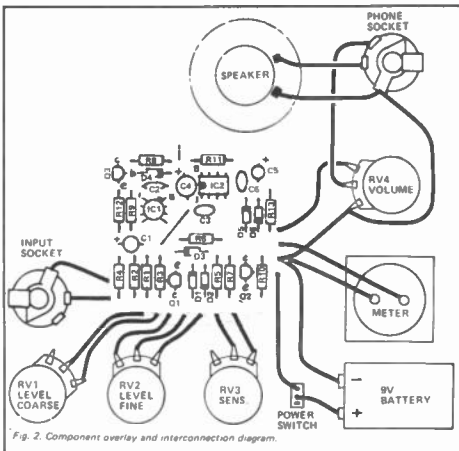


Fig. 2. Component overlay and interconnection diagram.

## PARTS LIST

### RESISTORS (all 1/2 W 5%)

R1 2k2  
R2 10 k  
R3 100 k  
R4 47 k  
R5 2k2  
R6 10 k  
R7 2k2  
R8,9 100 k  
R10-12 10 k  
R13 22 R

### POTENTIOMETERS

RV1 1 M log  
RV2 47 k lin  
RV3 1 M log  
RV4 500 R lin

### CAPACITORS

C1 1 u 16 V electrolytic  
C2 68 p ceramic

C3 10 n polyester  
C4 100 u 16 V electrolytic  
C5 10 u 16 V electrolytic  
C6 68 n polyester

### SEMICONDUCTORS

D1,6 1N914  
Q1,2 8C559 or 8C179  
Q3 8C549 or 8C109  
IC1 CA3130  
IC2 NE555

### MISCELLANEOUS

PC board ET1 546  
Meter 1 mA FSD  
Box 196 x 113 x 60 mm  
Two phone jacks  
Four knobs  
Small speaker  
PP3 or 9 V battery + holder  
Pickup probes

'coarse' level control (when the sensitivity is set low the 'fine' level control need not be used). Start with the 'coarse' control at full anticlockwise and turn it up until the meter needle starts to move. Carefully set the needle to mid range. Now the instrument is set up in its minimum sensitivity position.

Having mastered setting up with minimum sensitivity try to set the GSR monitor with the sensitivity set halfway. It will require delicate adjustment of the 'coarse' level control. Now the effect of the 'fine' level control can be seen. This control enables you to set the level on a high sensitivity setting.



# The

# Sinclair

# Cambridge

# Programmable



**THIS NEW MPU CALCULATOR  
IS AMAZINGLY LOW PRICED  
BUT HOW GOOD IS IT? RON  
HARRIS INVESTIGATES**

PROGRAMMABLE CALCULATORS have always had their market where ever a task must be repeated over and over with different data. Examples in electronics would include filter design, optimising component values for given allowed parameter variations, calculation of resistor networks for attenuators or to achieve a given R using paralleled units and perhaps even Fourier Analysis.

There are two types of calculator with this ability to remember a sequence of keystrokes, card programmables epitomised by the HP87 reviewed in ETI last month and keyboard programmables of which the CBM PR 100 is a good example. Price has up until now been a fairly high hurdle between the mass of potential users and the machines.

Until now

The Sinclair Cambridge Programmable could well be the step ladder to solve that problem! Selling at around £15 discount including mains unit its 38 step program memory becomes accessible to even the most inpericious student.

## Stepping into the limelight

Housed in the same case almost as its predecessor the Programmable is outwardly little different. Only the 'GT style' bulge on the battery compartment (to accept a PP3) and the actual word 'programmable' coyly added to the front panel artwork alert to the vital difference!

As a normal scientific the new Cambridge has more functions on the

keys than its Daddy. Nearly all the buttons are three function in fact making a double shift key necessary. The advantage of the small case size wages a fierce war on keyboard convenience and display visibility which means the Cambridge is fiddly to use in this generation as the last.

But this is not a normal scientific far from it. This is a 38 step programmable calculator with conditional branching and step facilities altogether a different animal.

## The nature of the beast

Along with the machine comes a desk stand, instruction manual and sample program booklet. Full back up is provided by Sinclair in the form of a 4 volume program library containing almost 300 programs. This is available at £4.95 complete.

Sinclair's library gives the basics of the calculation required and then lists the program in a three column table giving step number, keystroke and check code.

Scattered within the library pages are blank program sheets to enter your own creations for storage. We have a suggestion to make to Sinclair about that!

It seems to us that large number of

potential users will be putting the machine to work 'in the field' as it were, and these people will like as not be unwilling or unable to hump around a book the size of a program library volume for reference to program listings. Why not a book of blank program sheets the same size as the calculator which could then fit within the carrying case supplied?

Within the case are just three components: MPU chip, display driver and a capacitor! Both chips are from National Semi as is the display. The MPU is the 4bit MMS799. The on chip memory of this MPU has made it possible for Sinclair to hold the price as low as they have. The mask program was written in America, where Sinclair concentrate their software expertise. According to them they only just made it all go into the space available, which means that they don't give anyone else a prayer of getting near the price for a long time.

It will be interesting to see how soon anybody does begin to compete or indeed if anyone bothers!

Using a Mallory PP3 gives around 30 hours use less if you keep the machine in program mode. With that desk stand under its body, the Cambridge is not at all bad for use

# Cambridge Programmable

as a desk machine, although naturally its size doesn't help any!

Putting it in the  
ground is easy

Using the Cambridge as a program machine takes perhaps an hour or so to get used to, aided by the excellent manual and examples provided. Simply the best method to learn to program this calculator is to play with it! Once familiar with its little ways and means (i.e. the four key sequence to get into program mode, and a further two to get it to listen to what you're telling it!) entering sequences is no problem at all.

We doubt that anyone short of Dr Who could simply pick up the little white box and get it to run programs, but within half an hour all should be well. This is a complex instrument of course, and it would be unreasonable to expect otherwise.

Once entered, a program is checked by 'stepping' through and comparing a list of 'check codes' with the displayed characters. The codes are written on the keyboard too, just so you can be sure.

The greatest advantage of such an instrument is perhaps the fact that once programmed up operation is by use of a single 'RUN' key. This means that untrained operators can use it to good advantage. As an example we did out a short program to calculate an invoice amount, in which a certain number of magazines are sold at a discount of say 30%.

The calculations needed for each unit are thus (nos of magazines)  $\times$  (price), 30% of this and then total less 30%. On an normal calculator this could involve the following sequence

```

enter number) * 35 = (total amount)
+ 30 100 (discount amount) and
then (total amount) (discount
amount) = invoice total

```

This would be shortened with memory or percentage key functions we realise, and 30% could be calculated as 0.3 more easily but bear with us we're only trying to make things clear!

## in good voice

Now if only one invoice is to be made up, then no advantage is gained by use of the program. However,

most businesses use this kind of invoice procedure many times in any given period, and once the number exceeds three the program will save the time it takes to enter it.

Our programme is listed out below, with the check codes next to it. Each step is simply the button to operate at that point in the sequence.

To use this listing to work out invoices for you you would simply go through the sequence, check it, and then clear the display.

Enter the number of magazines to be sold on the first invoice. Press **RUN**. Displayed now is the first total to be typed in. Press **RUN** again. The display now gives you the 30% discount on the previous total. Type this and then give **RUN** a third job. The number now sitting there is the final total.

On 20 such invoices, using the Programmable is shorter by over 600 keystrokes, thus removing 600 possible errors, and making a tedious task far less time consuming.

**Come for a few  
reservations**

We found the Sinclair an excellent introduction to programmable calculators. As an ordinary scientific we have reservations, but surely

few people would use it as such. The key spacing is quite tight, and the display does have a limited viewing angle to it.

One beautiful aspect to the business of running programs is the fact that you can get the machine to play games with you! Sinclair gave three games programs in the library, including a decent version of moon-landing. The four arithmetic function, keys all do something different if operated twice and this can be used to advantage within a program. For example the sequence  $x \pm x$  will square a number.

If you intend to buy a Cambridge, don't begrudge the £495 for the program library, it is worth far more and extends the usefulness of the machine immeasurably.

**Go to conclusion!**

All in all then an amazing presentation for the money, and a machine which will probably create its own market. (We suspect Sinclair themselves will be surprised at the reaction this calculator may elicit).

For our part we can recommend it enthusiastically despite the reservations expressed earlier. It is worth its asking price for the games it's capable of playing!

| CODE | STEP   |
|------|--------|
| 3    | x      |
| 3    | a      |
| 3    | s      |
| 5    | t      |
| 7    | sto    |
| 8    | viny   |
| 5    | ad     |
| 3    | n      |
| 3    | e      |
| 3    | s      |
| 8    | r      |
| 3    | d      |
| 6    | +<br>1 |
| 1    | i<br>0 |
| 8    | o      |
| -    | o      |
| 8    | stop   |
| 8    | *      |
| 5    | rdl    |
| 8    | prg    |
| 6    |        |
| 2    | go to  |
| 0    | 0      |
| 0    | 0      |

**INVOICE**

---

N    Magazines at 35¢ each  
      Less 30% discount

---

Total Due \$ 1.70

The example program referred to in text is shown on the left and the type of invoice it would put on a screen above. The CODE column shows what appears on the display at each step of where the program.

Using this check code enables the program being to be checked before running.



□ □ □ □ □ □ □ □ □ □ □ □ □ □ □ □

**FREE** in AUGUST

# EDITORIAL

## A CONSIDERATION OF THE METHODS USED TO APPLY DIGITAL CIRCUIT

THE WEALTH OF EXPERIENCE possessed by engineers and technicians involved with digital hardware can be enormously valuable to them in their transition to microprocessor based designs. The thought of programming may distress the hardware man however to write efficient assembly language programs demands an intimate familiarity with the hardware structure of the particular microcomputer being used.

The flowchart forms the basis of program writing by ensuring that the logical sequence of events has been crystallised. Consider as an example a process control situation depicted in Fig 1. After a controlled start system initialisation can commence by processing the input data to check given interlock requirements. Satisfactory results allow the process to begin otherwise the interlock failure is announced and a system stop ordered.

As the process continues towards a designated goal periodic status checks of the system are required so that control action can be implemented. To ensure that actuators operate correctly the response to an action command is fed back for the system to monitor. This outline scheme typifies the use of flowcharts. Of course each block could be examined further resulting in a more detailed diagram.

### Program Power

The real power of programs is their ability to make decisions. Examples of assembly language conditional instructions are

JUMP and

INCREMENT SKIP IF ZERO

Jump instructions can either be mandatory thus directing the program to an address which is accessed in all cases or jumps can be conditional as illustrated by the following examples.

JZ could mean Jump if accumulator=0

JC could mean Jump if accumulator carry=1

JCN could mean Jump if a given CPU pin=1

The number and type of jump instructions provided depends upon the particular microprocessor in use. The Increment Skip if Zero (ISZ) is

useful for decision making because it can distinguish between zero and non-zero contents of index registers. A designated path can be followed in each case.

### Interesting Routine

A program sector which is frequently used during a process forms a prime candidate for a SUBROUTINE. In Fig 1, the block performing

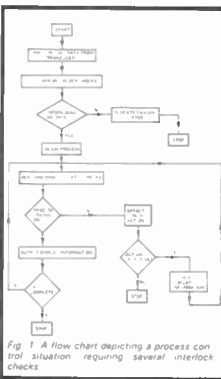


Fig 1 A flow chart depicting a process control situation requiring several interlock checks

process status checks would clearly be used repeatedly. Two of the three paths leading to this block are the result of decisions made during the on-going process. The subroutine would therefore be called into action by an instruction such as JMS 70 (Jump to subroutine at address 70).

To perform process status checks, data has to be input from transducers stored and then a number of successive decisions made based upon the data. These requirements can be met by using NESTED SUBROUTINES. A number of subroutines are written each one called by a preceeding member of the set. Fig 2 shows subroutines nested to a depth of three.

After servicing a subroutine the micro processor needs to know the

re-entry point in the program. This information is normally provided by a section of memory store known as a push-down stack. As each further level is entered in a nested subroutine system the latest return address is placed at the top of the stack thus causing previously entered return addresses to be pushed-down.

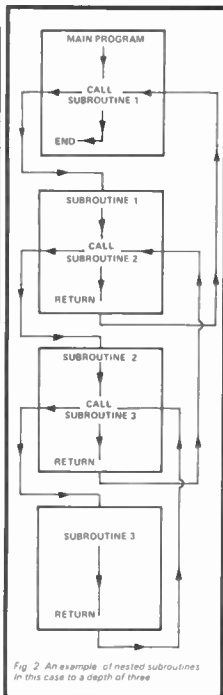


Fig 2 An example of nested subroutines in this case to a depth of three

## DESIGN TECHNIQUES TO SOFTWARE ROUTINES BY R. WILSON MSC

### Displaying Versatility

A main application area of microprocessor systems is in replacing hard-wired logic by a stored program. A multiplexed seven-segment LED system for numeric display is usually implemented by interconnecting integrated circuits. The function of some of the circuits can be duplicated by a sequence of assembly language instructions.

### Flowing Charts

A flowchart for a subroutine which controls the indications of four BCD digits by seven-segment displays is shown in Fig. 3. When this subroutine is called, a four-bit index register which acts as a loop counter is set to 1100 in binary (12 in decimal). By using the ISZ instruction the decision can be programmed simply. The loop counter is incremented each time this instruction is executed. After three loops the index register would contain binary 1111 (15 in decimal). When incremented this becomes 0000 ensuring that after four loops the alternative path is selected by the "skip if zero" part of ISZ.

### Routine Subs

The subroutine multiplexes the four displays by successively sending 0001 0010 0100 and 1000 as digit drive data during the progression of the program from the first to the fourth loop. The BCD digits represented as segment drive data are thus automatically routed to the correct display from a common highway.

Each BCD digit was stored by four bits of random access memory (RAM). The read/write facility was essential as variable data was being processed. When programming for dynamically changing data the locations of the various data sets in RAM must be constantly reviewed. A RAM map (Fig. 4) is a straightforward visual aid which makes this task easier. A diagram is drawn showing the empty memory locations then as the instructions are written the space in RAM can be thoughtfully allocated, modified and updated as necessary.

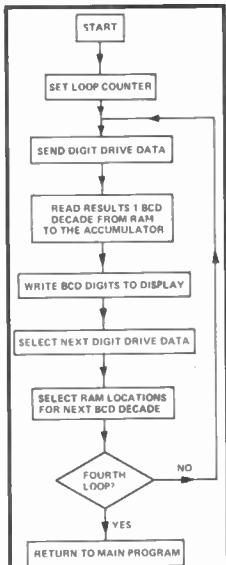


Fig. 3 This subroutine is to run four seven segment displays multiplexed and with each digit stored in RAM

### Finding Bugs

Engineers know that the phrase "nothing ever works first time" usually applies to hardwired designs. It also applies to software designs. When a comprehensive program has been written it will contain errors therefore a means of examining the program operation is required. The main sections of a microcomputer hardware structure: the CPU, memory, I/O and clock can be simulated either by software in the form of a computer package or by

special purpose hardware. Software simulators are available through various commercial time share networks whereas hardware simulators can be obtained direct from microprocessor distributors.

The source program written in mnemonics needs to be translated into numeric patterns. The resulting data called object code is generated from the source code by using an assembler. Again hardware and software assemblers are available. The object code version of the program can then be presented to the simulator for testing.

Program testing is not a simple task but the following suggestions might be helpful. If possible assemble the whole program from the outset, or at least assemble substantial segments such as subroutines. This ensures that the actual program is examined rather than a simplified version. By mentally working through the selected program segment using chosen test data the expected outcome can be predicted before beginning a test-run. The RAM map is often useful during this procedure. If a teletype is used to communicate with the simulator during a program test-run a printed record of the test process can be preserved for analysis later. As each section is tested, modified and eventually verified as correct further segments can be processed. The aim is to commit the whole of the validated program to PROM.

The hardware man can be comforted in his venture into software by remembering that a microcomputer is after all an engineer's computer.

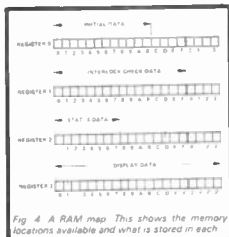


Fig. 4 A RAM map. This shows the memory locations available and what is stored in each

## BE A CATHODE RAY COWBOY WITH OUR

# TV GAMES RIFLE

FROM CIRCUIT AND TEXT BY WATFORD ELECTRONICS

THE TV GAMES UNIT featured in our May 77 issue has provision for the addition of two rifle games. In both games a target appears on the TV screen and the object is to hit this with the TV rifle. When the trigger of the rifle is pulled a shot counter is incremented by one and if the rifle is on target the hit counter is incremented a hit noise produced and the target blanked for a while.

The difference between the two game options is that in one the target moves randomly about the screen and in the second the target traverses the screen from left to right under the control of the manual serve button.

Unlike the other games the score does not appear on the screen during the game since this might confuse the player instead the score appears after 15 shots. The score is displayed with the number of shots (i.e. 15) on the left and the number of hits on the right.

### Seeing the light

The rifle uses a photodarlington to detect the target on the TV screen but relies on careful construction of the optics involved to ensure adequate sensitivity is obtained from the unit. We also arranged for the rifle to ignore any sources of light other than the target on the TV screen.

Though we called this project a TV rifle game we finally settled on what might more accurately be described as a pistol. The general method of construction used in the pistol is shown in Fig. 1.

### Getting started

The butt is made from a fairly hard wood and after being fashioned to the shape shown in

the drawing, the top was dished with half round file to accommodate the barrel. The next step is to drill a hole vertically through the butt to take the connecting cable between the pistol and games unit. The trigger switch is mounted by drilling two holes, one above the other and chiselling out the remaining wood to form an oblong hole. A small aluminium plate was then drilled to accept the switch and two small wood screws used to secure the plate to the butt.

### Roll out the barrel

The barrel is made from 28mm dia metal tube  $8\frac{1}{2}$ in. in length. To fit it to the butt two holes were drilled at one end, and two further holes drilled diametrically opposite the first pair. By passing a screwdriver through the top holes the barrel may be secured to the butt.

The lens used in the pistol had a focal length of  $2\frac{1}{2}$ in. and came from an old jeweller's eye glass.

this was mounted in a B9A valve screening can. The photodarlington should be carefully positioned at the focal point of the lens. We mounted the photodarlington on a piece of veroboard which enabled us to slide it back and forth until its position was correct.

The assembly may then be mounted in the barrel.

### End in sight

The front sight was formed from a 4BA bolt which was filed to provide a sight tip. The rear sight is formed from a  $\frac{3}{8}$ in. wide strip of aluminium about  $2\frac{1}{2}$ in. long. One end is bent up and a V slot filed with a needle file.

At this stage the p.c.b. may be assembled. The only thing to note about the components used is that they must be as small as possible we used tantalum beads for C3, C5 and sub miniature electrolytic types.

When the board has been assembled wire it to



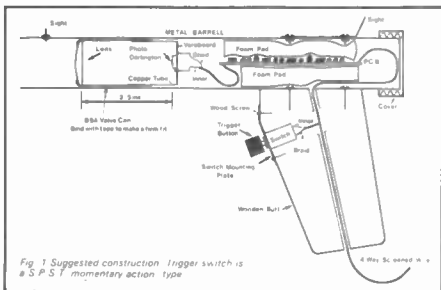


Fig. 1 Suggested construction. Trigger switch is a S.P.S.T. momentary action type.

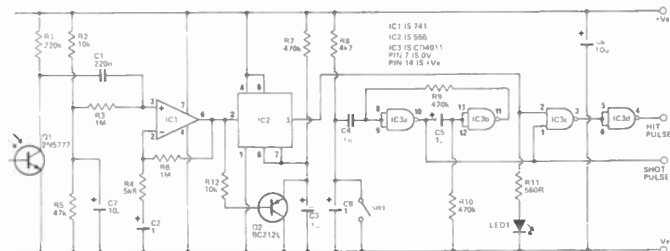

# TV GAMES RIFLE

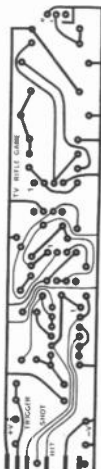

the trigger switch and to the connecting cable. It may then be mounted at the rear of the barrel by gluing it to a foam pad which may in turn be stuck to the barrel.

The connecting wire we used was four core screened cable and should be connected to the games unit as follows: (via DIN plug)

|            |          |
|------------|----------|
| 0V         | to pin 5 |
| 6V         | to pin 3 |
| Hit pulse  | to pin 1 |
| Shot pulse | to pin 4 |

## Testing

The games unit should now be connected to your TV and the brilliance control of the TV adjusted until the target is bright and the background just visible. If the rifle is now aimed at the target, at close range initially the On Target LED should glow and a blip should be heard from the speaker when the trigger is pressed.

To adjust the sights use the score display which appears at the end of the game. Block off all the screen except one digit of the score

The sight may then be adjusted so that the hit LED is on when the pistol is aimed at the score

## To play

Select the rifle option required with SW2 and press the reset and serve buttons. The target should appear on the screen and bounce around the screen until hit.



The PCB layout is shown full size on the left. Above is a picture showing the games rifle.

## Big saving, good looking, fast checking NEW Doram DIGITAL MULTIMETER—BUILD IT YOURSELF AND SAVE UP TO £40!



### KEY DATA

Varia DC 200mV, 2V, 20V  
200V 1000V input  
resistance 2MΩ Max current  
not over 100mA  
Varia AC 200mV, 2V, 20V  
200V 500V input impedance  
2MΩ Max current impedance  
100kV  
Current AC DC 20mA, 2mA, 2mA  
200mA, 2A  
Resistance 200Ω, 2kΩ, 20kΩ, 200kΩ, 2MΩ

A clear, functional multimeter, featuring extremely accurate digital display in superbly styled shatterproof carry-case. It could cost £100! But the complete Doram kit with case, printed circuit board, leads and all components is yours for just £54.50 plus £4.36 VAT.

Based on Ferranti technology with accuracy  $\pm 0.6\%$  the new Doram Multimeter is an indispensable tool at a terrific saving. Measurement is indicated by a 3 1/2 digit display updated twice per second—display flashes to indicate overload.

And it saves you money before it's even built!

## DEPEND ON DORAM

Thousands of a million do for top value and modern technology.  
Doram Electronics Ltd PO Box 718, The Designer Road, Indus Valley, Walsingham, Norfolk, NR25 7JH.  
Registered in England No. 1155866 Directors: A. Miller, D. Sump, C. Cline.

## Yes, I want to save up to £40

Please send this coupon to: Doram Electronics Ltd, Dept 1, PO Box 718, Indus Valley, Walsingham, Norfolk, NR25 7JH. I am interested in the Doram Digital Multimeter at £54.50 + £4.36 VAT and I would like to receive the unprinted edition 7 days and claim my money back 14 days. I understand I can return the unprinted edition 7 days and claim my money back 14 days. I understand I can return the unprinted edition 7 days and claim my money back 14 days. I understand I can return the unprinted edition 7 days and claim my money back 14 days.

Please send me: complete DORAM KIT CATALOGUE showing an additional 28 kits at 25p each.

I enclose cheque/PO return  
NAME AND ADDRESS  
ADDRESS  
TOWN  
COUNTRY

POST TO: DORAM ELECTRONICS LTD, DEPT 1, PO BOX 718, INDUS VALLEY, WALSINGHAM, NORFOLK, NR25 7JH.



# Wilmslow Audio

## THE firm for speakers!

Send 10p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossovers, etc., and discount price list

ACT • AUDAX • BAKER • BOWERS & WILKINS  
• CASTLE • CELESTION • CHARTWELL •  
COLES • DALESFORD • DECCA • EMI • EAGLE  
• ELAC • FANE • GAUSS • GOODMANS •  
HELM • I M F • ISOPHON • JR • JORDAN  
WATTS • KEF • LEAK • LOWTHER •  
MCKENZIE • MONITOR AUDIO • PEEFLESS •  
RADFORD • RAM • RICHARD ALLAN • SEAS •  
TANNOY • VIDEOTONE • WHARFEDALE

## WILMSLOW AUDIO Dept. ETI

SWAN WORKS, BANK SQUARE, WILMSLOW,  
CHESHIRE, SK9 1HF  
Discount HiFi, etc., at 5 Swan Street and 10 Swan Street

TEL: WILMSLOW 29599 FOR SPEAKERS  
WILMSLOW 26213 FOR HiFi

# DESIGNING & USING ACTIVE FILTERS

## PART 1

A SHORT SERIES BY TIM ORR WHICH WILL ENABLE THE HOME CONSTRUCTOR TO UTILISE CIRCUITS OF HIGH COMPLEXITY AS EASILY AS PLUGGING IN A RESISTOR!

THERE IS NO DOUBT that active filters are very useful devices. Also, there is no shortage of literature on the subject. This would seem to suggest that designing active filters is a fairly straightforward business. Well, it is and it isn't. It is if you read *this* article. It isn't if you read the aforementioned literature. Most of the books on this subject have filled our heads with terms such as poles and zeros, Laplace transforms, transfer functions etc. which haven't actually helped us to design anything!

### Some basic theory

It is advisable quickly to run through some basic terms and expressions. Firstly, consider a simple low pass filter. Fig 1a. The frequency response (Fig 1b) is

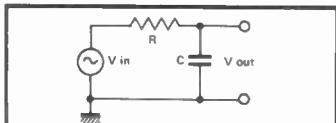


Fig 1a Simple low pass filter

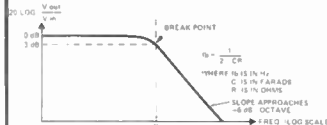


Fig 1b Frequency response of above

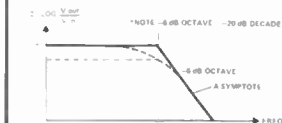


Fig 1c Asymptote at 0 dB to response

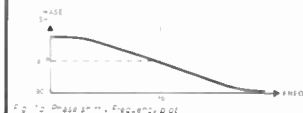


Fig 1d Phase response of above

nearly flat until the break point denoted by  $f_b$ . After this point the response rolls off at 6dB/octave: that is signals above this frequency are increasingly attenuated. The break point is defined as being the frequency where the resistance equals the capacitive reactance. When this occurs the output is attenuated to 0.707 (-3dB) of the input. Although the resistance equals the capacitive reactance, the output is *not* half of the input. (This is because it is the vector sum of the two and hence equals 0.707 of the input!)

As the frequency response is a rather complex curve it is very useful to use a straight line approximation to it. These lines are called asymptotes (Fig 1c). Note that the frequency response graph uses the convention of logarithmic scales, octaves or decades along the frequency axis and dBs along the vertical axis representing output voltage divided by input voltage.

Phase shift with respect to frequency is also often plotted as in Fig 1d. These two (the phase and frequency response plots) are known as Bode diagrams and are generally considered the most useful way of representing a filter's performance.

You will note that for the lowpass filter of Fig 1a, the phase shift starts at 0° is 45° at  $f_b$  and then approaches 90° as the frequency approaches infinity. This is not an active filter: it is composed entirely of passive components which means that its output cannot be effectively loaded without changing its performance.

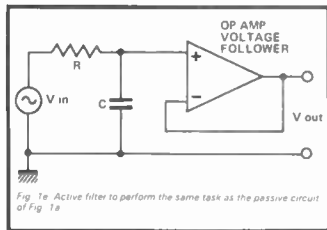


Fig 1e Active filter to perform the same task as the passive circuit of Fig 1a

Fig 1e shows the same filter but in its active form, the op amp being used as a voltage follower serving only to isolate the filter's output. This type of filter is known as a First Order filter — a measure of the roll off slope.

When a more rapid slope is required, a higher order filter structure (one with more reactive elements) must be used. This is dealt with later.

# ACTIVE FILTERS

Summary of low pass filter of Fig. 1

|                   |                                        |
|-------------------|----------------------------------------|
| Filter type       | Low pass                               |
| Filter order      | First order                            |
| Roll off slope    | -6dB/octave or -20dB/decade (the same) |
| Breakpoint fb     | $f_b = 1/2\pi CR$ Hz                   |
| Phase shift at fb | 45                                     |

TABLE 1

## Passing highs

Next, let us consider the simple high pass filter of Fig. 2a. It is the complement of the low pass filter, the elements having been interchanged. Therefore it is not

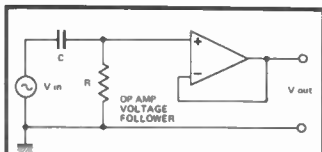


Fig. 2a Simple high-pass active filter

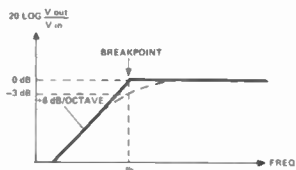


Fig. 2b Frequency response of the high pass filter

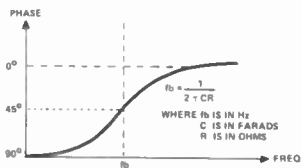


Fig. 2c Phase v frequency plot of the same filter

difficult to accept the complementary phase and frequency response curves of Fig. 2b. Note that the break point is the same and so is the roll off slope

Summary of the high pass filter of Fig. 2

|                   |                             |
|-------------------|-----------------------------|
| Filter type       | High pass                   |
| Filter order      | First order                 |
| Roll off slope    | +6dB/octave or +20dB/decade |
| Break point fb    | $f_b = 1/2\pi CR$ Hz        |
| Phase shift at fb | 45                          |

TABLE 2

## Passing bands

The next type to be considered is a simple band pass filter shown in Fig. 3a. Although it uses an inductor it is only to illustrate the bandpass theory. Later on in this series, inductors will be replaced by their active equivalents.

The frequency response (Fig. 3b) shows that this circuit is symmetrical, having roll off slopes of 6dB/octave on either side of its RESONANT peak. This

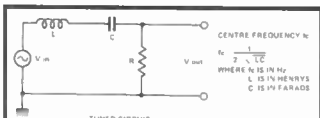


Fig. 3a Simple band-pass filter

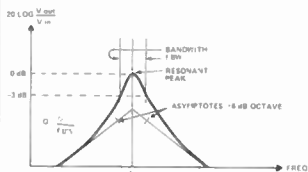


Fig. 3b Band-pass frequency response

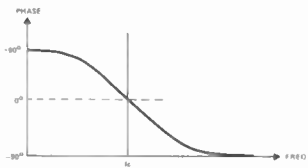


Fig. 3c Band-pass phase response

filter is known as a second order filter because it has two reactive sections, the L and the C. The C is responsible for the +6dB/octave portion of the slope, the L for the -6dB/octave portion. But where these two slopes should meet the response of the filter peaks and the slopes become much larger (Reson-



ance). The sharpness of this peak is described as the Quality of the filter the Q factor. Resonance occurs at a frequency known as the Centre frequency denoted by  $f_c$ .

The bandpass filter is so called because it only passes signals within a certain bandwidth, which is defined as being the frequency range contained between the two points that are 3dB below the resonant peak. There is a fixed relationship between Centre frequency ( $f_c$ ) bandwidth (fbw) and Q factor given by  $Q = f_c / \text{fbw}$ .

The centre frequency is given by  $f_c \approx 1 / 2\pi \sqrt{LC}$  Hz. This is only approximate, as it assumes that the value of R is relatively low. As R decreases the Q factor increases. Thus R has the effect of damping the resonances and so as it approaches zero ohms Q approaches infinity.

The phase shift is shown in Fig. 3c. As this filter is a second order structure then the total phase movement will be twice that for a first order structure, i.e. 180°. Fig. 3d shows the phase and frequency responses for different values of Q. Note that a high Q has a very rapid rate of change of phase, a low Q has only a slow rate of change.

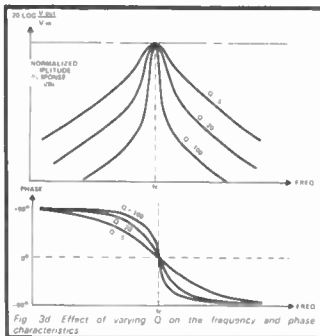


Fig 3d Effect of varying Q on the frequency and phase characteristics

## Time phase

Bandpass filters also have a time response as opposed to their frequency response. When an impulse is applied to a bandpass filter it rings (Fig. 3e). The filter oscillates at the centre frequency  $f_c$ , the amplitude of the oscillations decaying exponentially in time. The ringing time  $T_r$  is the time taken for the oscillations to decay to 37% of their initial value. Ringing time is related to the Q and  $f_c$  by the following equation:

$$T_r = Q / 2\pi f_c$$

When a high Q filter has been constructed it may prove difficult to measure its Q factor accurately due to the narrowness of its bandwidth. However, if the filter is made to ring, a reasonably accurate measurement of the Q can be obtained by measuring  $T_r$  and  $f_c$ .

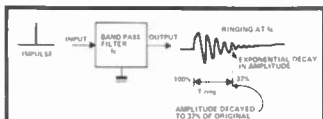


Fig 3e Ringing in a band pass filter

|                        |                                                   |
|------------------------|---------------------------------------------------|
| Filter type            | Band pass                                         |
| Filter order           | Second order                                      |
| Roll off slopes        | + and -6dB/octave greater near to resonance       |
| Centre frequency $f_c$ | $f_c \approx 1 / 2\pi \sqrt{LC}$                  |
| Phase shift at $f_c$   | 0                                                 |
| Q factor               | $f_c / \text{fbw}$ where fbw is the 3dB bandwidth |
| 3dB bandwidth fbw      | $f_c / Q$                                         |
| Ringing time $T_r$     | $Q / 2\pi f_c$                                    |

TABLE 3 Summary of band pass filter

## Failed band

Another common filter structure is the band reject or notch filter. There are many ways of realising this filter, one of which is shown in Fig. 4. The input signal is subtracted from the bandpass output. By adjusting  $R_a$  with respect to R complete cancellation can be obtained at  $f_c$ .

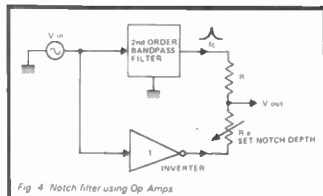


Fig 4 Notch filter using Op Amps

Thus the centre frequency of the bandpass filter is the centre frequency of the notch, whose depth can be varied by altering  $R_a$ .

Very deep notches are possible. 50dB is easily obtained. As the Q of the bandpass filter is increased, so is the Q of the notch filter. However,  $R_a$  will have to be reset for each value of Q.


## Filter Order

Consider the ideal low pass filter shown in Fig. 5a. Its response is flat right up until the break frequency to frequencies above  $f_b$  are attenuated to nothing! You won't be surprised to learn that filters like this don't exist. However, it is a common requirement to produce filters with very steep roll off slopes and this is achieved by designing filters with lots of sections to increase the
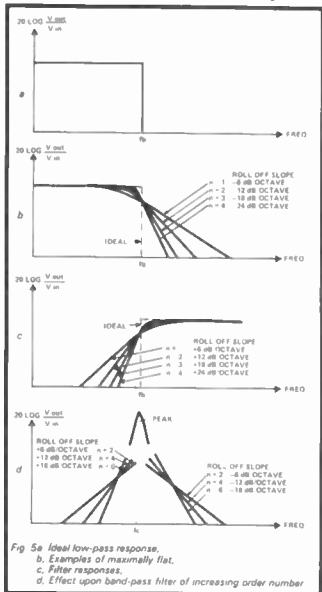
# ACTIVE FILTERS

filter order. Each reactive element in the filter increases the filter order by one, therefore a low pass active filter with three capacitors is known as a third order filter and will have an ultimate roll off of three times 6dB/octave which is 18dB/octave.

However, designing a third order lowpass filter is not just a simple case of sticking three first order RC circuits in a line. What you get when you do this is a very soggy curve indeed! The filter should be flat in the pass band, then it should turn over and rapidly assume its ultimate roll off slope. Examples of this type of Maximally flat filter are shown in Figs 5b and c. The effect of order number upon a bandpass filter is shown in Fig. 5d.



Later on in this series the circuit diagrams and design charts are given for various filter types and order numbers. It would seem that to get a filter to approach its ideal response, all that is needed is to increase the order number. This is in fact true but there are certain tolerance problems (When 8th order filters are designed, component tolerances of about 1% are required!)

## Which filter shape?

The type of filter that is chosen to do a particular job will depend on what parameters are thought to be important. There are three basic characteristics to be considered (lowpass and highpass filters only):


1. Good transient response
2. Maximum flatness of the filter within its passband
3. Maximum rolloff slope outside the passband

The type of filter used should be chosen to fit the job that they are being designed for. The filters have been categorised into three basic types for the purpose of simplicity.

**Filter number 1** is known as a Bessel filter. Its phase changes almost linearly with frequency. It is useful for systems where a good transient response is required such as joining the dots up on the output of a digital to analogue converter. It has a very poor initial roll off slope.

**Filter number 2** is known as a Butterworth filter. It has the flattest pass band possible. Its other two parameters are a compromise. That is it has a reasonable overshoot and a fairly fast initial roll off.

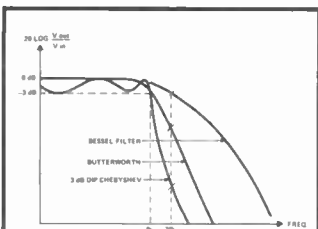**Filter number 3** is known as a Chebyshev filter. It has some ripple in its pass band although this is small and a very fast initial roll off and a poor transient response.



ATTENUATION AT FIRST OCTAVE (2 fb)

|                 |    |    |    |    |    |    |
|-----------------|----|----|----|----|----|----|
| *3 dB CHEBYSHEV | 17 | 28 | 39 | 51 | 62 | 75 |
| BUTTERWORTH     | 12 | 18 | 24 | 30 | 36 | 42 |
| n/FILTER ORDER  | 2  | 3  | 4  | 5  | 6  | 7  |

\*NOTE THE IMPROVED ATTENUATION

Fig. 6 Response of all three types of filter discussed, with table showing variation in attenuation between them.

**Next Month: Full design charts and circuits for three types of Active Filter.**

|                                                                                                                                      |                                                                           |                                                                                                           |                                                                                                |
|--------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------|
| <b>MARCONI T9075P WIDE RANGE PULSE GENERATOR</b><br>4 ranges 100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V<br>100V to 1000V | <b>ROYAL INVERTERS</b><br>100V to 1000V<br>100V to 1000V<br>100V to 1000V | <b>MARCONI NOISE GENERATOR T9077/1</b><br>4 ranges 100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>AVO TRANSISTOR ANALYSER CT448</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V |
|--------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------|

|                                                                                   |                                                                                            |                                                                                            |
|-----------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|
| <b>FOR THE VIBRATOR</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>WE ARE BREAKING COMPUTERS</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>EDWARDS HIGH VACUUM PUMPS</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V |
|-----------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|

|                                                                               |                                                                                                     |
|-------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------|
| <b>Single phase</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>UNIVAC MAGNETIC TAPE UNITS</b><br>Complete with heads and 10 reels 1 tape<br>£77.50 Cabbage paid |
|-------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------|

|                                                                               |                                                                         |                                                                         |                                                                         |
|-------------------------------------------------------------------------------|-------------------------------------------------------------------------|-------------------------------------------------------------------------|-------------------------------------------------------------------------|
| <b>TRANSFORMERS</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>DIODES</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>DIODES</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>DIODES</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V |
|-------------------------------------------------------------------------------|-------------------------------------------------------------------------|-------------------------------------------------------------------------|-------------------------------------------------------------------------|

|                                                                                                                                                |  |  |  |
|------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|
| <b>PICK-A-PACK — 50 PENCE A POUND</b><br>FROM OUR PICK-A-PACK AREA WEIGH UP YOUR OWN INDIVIDUAL COMPONENTS<br>NO RESTRICTIONS ON WHAT YOU TAKE |  |  |  |
|------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|

|                                                                            |                                                                |                                                                              |
|----------------------------------------------------------------------------|----------------------------------------------------------------|------------------------------------------------------------------------------|
| <b>MINIATURE</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>1/2" MAG TAPE</b><br>Approx 2 000 ft<br>NOW 25p each P&P £1 | <b>Quantity of</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V |
|----------------------------------------------------------------------------|----------------------------------------------------------------|------------------------------------------------------------------------------|

|                                                                   |  |  |  |
|-------------------------------------------------------------------|--|--|--|
| <b>PICK-A-PIECE — 50 PENCE EACH</b><br>FROM OUR PICK-A-PIECE AREA |  |  |  |
|-------------------------------------------------------------------|--|--|--|

|                                                                                                           |                                                                                          |
|-----------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------|
| <b>SUPPLIES — BRAND NEW — REPLACEMENT TUBES</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V | <b>DATA LOGGERS BY DYNACOR</b><br>100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V |
|-----------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------|

|                                                                                  |  |  |  |
|----------------------------------------------------------------------------------|--|--|--|
| <b>PICK-A-METER — £1 EACH</b><br>A LARGE SELECTION OF BRAND NEW AND EX EQ METERS |  |  |  |
|----------------------------------------------------------------------------------|--|--|--|

|                                                                                                              |  |  |  |
|--------------------------------------------------------------------------------------------------------------|--|--|--|
| <b>CHILTMHEAD LTD</b><br>7/9 ARTHUR ROAD, READING, BERKS (near Tech College, King's Road) Tel Reading 882806 |  |  |  |
|--------------------------------------------------------------------------------------------------------------|--|--|--|

|                                                        |  |  |  |
|--------------------------------------------------------|--|--|--|
| 100V to 1000V<br>Output 100V to 1000V<br>100V to 1000V |  |  |  |
|--------------------------------------------------------|--|--|--|



# SHORT CIRCUITS

KEEP THIEVES AWAY — WITH OUR INVALUABLE

## ALARM ALARM

ONE PROBLEM WITH BURGLAR alarms is that they don't 'go off' until the burglar has broken in, but here is a project which can be installed in a car to warn thieves that a burglar alarm is operating. It should warn a thief to go and find a car which is not owned by an ETI reader! Even if there is actually no burglar alarm, the 'alarm alarm' can still be used. It's what the car thief believes that counts — and he's not going to investigate to see whether there really is an alarm.

The unit is simply a box containing two lamps which flash slowly on and off, together, and shine through a Perspex panel to illuminate the words **ALARM ACTIVE**. It uses a 555 timer IC, which is used as an astable multivibrator.

As the circuitry is isolated from the box this alarm can be used with any car having a 12 volt battery — whether the positive or negative terminal is connected to the chassis. Take care to see that the unit is correctly connected.

### Installation

The unit can be permanently mounted in a car near one corner of the windscreen and the wiring neatly run to a switch below the dashboard. Alternatively it may simply be placed in position when required, and plugged in to the cigarette lighter socket. To work effectively it should be prominent day or night.

### Construction


We mounted the components on an 'L' shaped bracket which is ideal for fitting to the dashboard. Lamps 1 and 2 are push fitted into two rubber grommets mounted on an aluminium bracket, and arranged to illuminate the perspex panel as shown. We used Letraset for the panel lettering.

The components are assembled onto the small PCB according to the component overlay, taking care that the 555 and C1 are correctly orientated.

We fitted an On/Off switch but if the car actually has a burglar alarm,



Fig 1 Circuit diagram of the Alarm Alarm

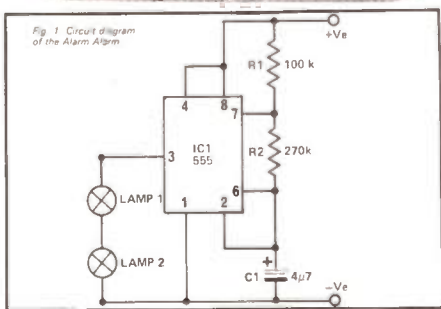

### HOW IT WORKS

The 555 IC is used as an astable (i.e. not stable) multivibrator. As soon as it is connected to the supply it starts to oscillate (slowly in this case) and the output voltage at pin 3 changes regularly and suddenly from high to low and low to high as the capacitor is charged and discharged.

The charge time (during which the output is high and the lamps are on) is given by the formula:

$$T_c = 0.69 (R1 + R2) \times C \text{ and is in seconds when } R1 \text{ and } R2 \text{ are in megohms and } C \text{ is in microfarads. So}$$
$$T_c = 0.69 (0.1 + 0.27) \times 4.7 = 1.2 \text{ seconds}$$

The discharge time (during which the output is low and the lamps are off) is given by the formula:

$$T_d = 0.69 \times R2 \times C$$
$$= 0.69 \times 0.27 \times 4.7 = 0.88 \text{ seconds}$$

Total time of one oscillation =  $T_c + T_d = 2.08$  seconds. So, we have a flasher which is on for about 1 second in 2. The exact timing depends on the actual capacitance of the capacitor C, and this may differ from its rated value by as much as -20% and +50%.

The rate of flashing may be changed by changing the values of R1 and R2. Higher values cause slower flashing.


# Short Circuits

then this device should be connected so that it is activated as the burglar alarm is energised.


The parts list specifies two 6 volt lamps of 60 mA rating which are connected in series. The current consumption is so low that the unit could be left operating for many hours without any danger of running down a car battery.

The IC is actually capable of switching up to 200 mA through pin 3, so there is no reason why two or even three slave units (with lamps only) should not be run in parallel with the lamps in the master unit. This could provide warnings at all vulnerable points in a car.

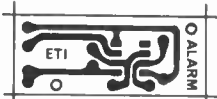This same device can be used in windows of homes as a discouragement to house burglars. In this case it could be operated from a simple power supply running from the mains.



Foil pattern shown full size

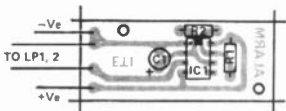

Component overlay of Alarm Alarm. Because of the small size, miniature components should be used.

## PARTS LIST

### RESISTORS (all 1/4 W 5%)

- R1 100 k  
R2 270 k

### CAPACITOR

- C1 4u7 15 V tantalum

### SEMICONDUCTOR

- IC1 555 timer

### LAMPS

- LP1,2 6 V .06 A MES type

### SWITCH

- See text

### MISCELLANEOUS


- Nuts, bolts, spacers, etc.  
Aluminium for front panel and bracket  
Grommets, flex, red translucent perspex  
PCB as pattern.

## GETTING HOLD OF COMPONENTS

All the components used in this project should be available from most component suppliers.
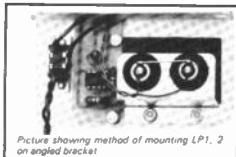
## COST OF CONSTRUCTION

The total cost of this project should be about £2.00.




Picture showing method of mounting LP1, 2 on angled bracket.

# microAMP

THERE IS OFTEN A NEED for a piece of equipment which can give a reliable answer as to another unit's state of being. In audio, for instance, a repaired amplifier might need to be tried without risking a pair of expensive monitor loudspeakers, or even headphones (which are worth a few bob themselves these days!).

Our micro-amp is designed to be a portable stereo test amp, capable of betraying any faults or distortions inherent in the suspect unit. The transducers utilised are low-cost crystal earpieces, for which the design has been optimised. Although there are only a handful of components in the design, the amp gives exceptionally good sound quality suitable, say, in checking whether that cassette deck in 'Rip-Off Hi-Fi' has 1% or 100% distortion.

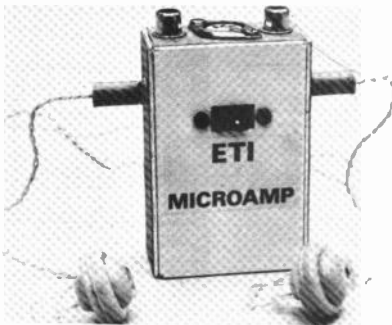Quality is ultimately limited by the earpieces, but they are capable of doing better than the two-transistor 'Super-Squark' portable radios to which they are more usually mated.




View of completed Micro amp  
In and Out and In ...

In the prototype, sockets were provided for a 'tape input' type of signal, i.e. from a cassette recorder at the DIN socket pins 3 and 5. If a signal is to be input from a tuner or amplifier, either use the phono sockets

or pins 1 and 4 so that you keep things standard.

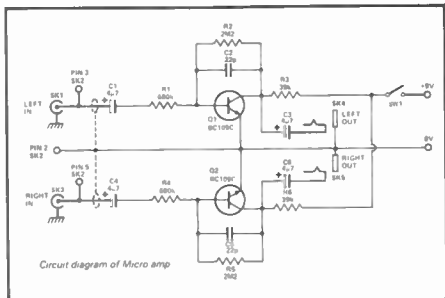Input level is ideally around 100 mV; if vastly different to this, R1 can be juggled in value to compensate. Increase if the level is higher.



## HOW IT WORKS

Q1 and Q2 are base biased single stage amplifiers. The feedback capacitors C2 and C5 are there to provide high frequency correction, and experimentation with the value will change the resultant sound quite noticeably.

C1 and C4 decouple the input from preceding circuits, and the resistors R1 and R4 will set the level seen by the amplifier, and hence by the earpieces. No volume controls are provided, as none proved to be necessary with the prototype. C3 and C6 serve to decouple output from dc. Crystal earpieces only are recommended.

As seems to be usual for us now-a-days, space within the box is very restricted, but it will go into the case if you take some care over the layout. Perhaps our photographs will help.

## Power and Construction

A PP3 is all that will fit into our box and is all that is needed. Current drain is around 300  $\mu$ A (hence the name!) and so even this will have a life-span approaching that which it would have enjoyed had you left it sitting merrily on a shelf.

The PCB is smaller than most, so take care when soldering it up: too long with the iron in one place, and the track will become emotionally attached to the bit, and not wish to leave it!


BC109Cs must be used to give a high enough output from the specified input. Surplus transistors will obviously work, but don't blame us if the sound is bad!

## GETTING HOLD OF COMPONENTS

Most components should be readily available from a number of suppliers. We have listed Doram part numbers for the phono sockets and Norman's reference for the box we used in our microamp.
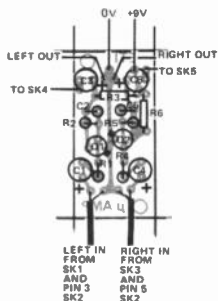
## COST OF CONSTRUCTION

The total cost of this project should be about £3.50 inc VAT.



## PARTS LIST

### RESISTORS (all $\frac{1}{2}$ W 5%)

R1,4 680 k  
R2,5 2M2  
R3,6 39 k

### CAPACITORS

C1,3,4,6 4u7 tantalum  
C2,5 22 p polystyrene

### SEMICONDUCTORS

Q1,2 BC109 C - see text

### SWITCH

SW1 On-off rocker, or slide type

### SOCKETS


SK1,3 Chassis phono sockets.  
(Doram: 478 093 red, or:  
477 B48 black)  
SK2 Chassis 5 pin DIN 180° socket  
SK4,5 3.5 mm chassis jack socket

### CASE

Norman type AB12 or similar (3 x 2 x 1")
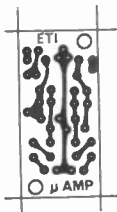
### MISCELLANEOUS

PP3 battery, clip to suit,  
Miniature screened wire flex  
Nuts, bolts, spacers etc.  
PCB as pattern  
2 off crystal earpieces with 3.5 mm jack plug,



Foil pattern of PCB is shown full size



# — SHORT CIRCUITS —

CONVERT ANY 1mA METER MOVEMENT INTO AN ACCURATE  
TACHO FOR YOUR CAR WITH OUR

## TACHOMETER

This design uses a single integrated circuit to provide an easily calibrated unit that will provide rpm indications of a wide range of engine speeds. It is suitable for 4 or 6 cylinder engines.

UNTIL TEN OR SO YEARS AGO, car tachos were cumbersome mechanical devices usually driven via a flexible cable from gearing attached to the shaft of the vehicle's dynamo — or sometimes via the distributor shaft.

The advent of transistor technology changed all this and since then almost all car tachos are electronically operated.

The basic principle is much the same for all electronic tachos: an electrical signal taken from the low tension side of the distributor is converted into a voltage proportional to engine rpm and this voltage is displayed on a meter calibrated accordingly.


Most car tachos are complex and expensive devices — but here's one with a difference! It is simple yet extremely effective. Its simplicity is due to our using one single integrated circuit rather than the more conventional multiplicity of individual transistors.

The unit will operate on both positive and negative earth vehicles and will also operate successfully and without modification with most types of electronic ignition systems as well as the more common electro-mechanical systems.
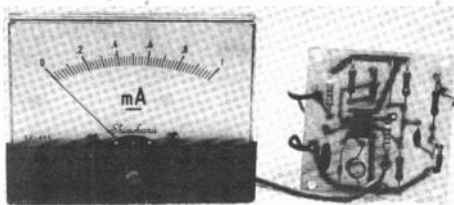
### Construction

As there are so few components, construction is very simple and straightforward. Do make sure though that the 555 IC is soldered in the right way round — ditto the two diodes. Compare your work against our layout drawing as a final check.

Any type of meter that has one milliamp full scale deflection can be used. This is a very common type of instrument and you should be able to obtain



Photograph showing a view of the completed pcb connected to a 1mA meter with 120 movement. The compact layout of our single integrated circuit design is apparent from this picture.

one new or secondhand with no difficulty. Ideally you should choose one that has 180° or 280° movement but these tend to be rather expensive. The meter size should be chosen to suit your proposed housing.

When the meter has been assembled connect it to the vehicle's battery and connect the input to the contact breaker side of the coil.

### Calibration

We can think of three ways to calibrate this unit. The easiest method is to borrow an already calibrated tachometer which can be temporarily connected to your car. RV2 may then be adjusted until the two readings agree over a range of engine speeds.

The unit may also be calibrated by the use of a signal generator by recognising that with a four cylinder engine there are two sparks per engine


revolution. To calibrate the unit, take the output from a signal generator to the tachometer (via an amplifier if necessary) and adjust RV2 until the reading on M1 satisfies the relationship:  $f = 2M$  where  $f$  = frequency in Hz, and  $M$  = meter reading in r.p.m.

Our final method is to calculate the vehicle speed per 1000 r.p.m. in top gear and adjust RV2 accordingly. Needless to say, this is a two person operation.

If the adjustment of RV2 is found to be too coarse its value may be reduced to 25k or lower. If this is done it will be necessary to increase the value of R4 accordingly.

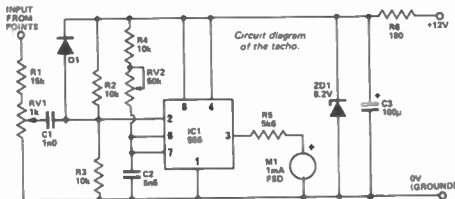Before making final calibration, adjust RV1 to eliminate any false triggering - check at all engine speeds. This unit may be used with either +Ve or -Ve earth vehicles - simply connect the battery leads as shown.





## PARTS LIST

# VALVE SOUND on the rebound?

GEORGE CHKANTZ  
AND  
RICHARD ELEN

**TWO PROFESSIONAL SOUND ENGINEERS HAVE A NEW AND HIGHLY CONTROVERSIAL THEORY TO ADD TO THE CONTINUING DEBATE AROUND THE SUPPOSED SUPERIORITY OF VALVE AMPLIFIERS**

IMAGINE YOU ARE SITTING in front of a pair of monitor speakers listening to some master tapes. The first track you hear is a very good high quality mix, such as one could find on a fair proportion of modern albums. But the second one is something else.

It too is of very high quality, but in addition it seems to possess an undefinable something. Could one call it clarity? Rightness? It's hard to put into words, but there is something about that mix which makes it stand out from the rest — an unknown factor which is nonetheless sufficiently noticeable for you to be able to tell the difference every time. Yet you know that the two recordings were made in the same studio, on the same desk, the same tape machines — every link in the chain from microphone to master tape was duplicated. But with one subtle change. The first mix was monitored on a pair of loudspeakers driven by a modern, high-power transistor amplifier with a rated output of 300 W.

The second, on the other hand, was reproduced using a pair of old glowing valve amps running a mere 50 W — and unaccountably sounding just as loud.

Why the difference?

## Valves versus Transistors

It is important to state at the outset that this is intended to be a qualitative analysis of points that we have found to be significant over the past few years during our work as

sound recording engineers. Some of the points we are raising are nowadays being discussed, but not all. One reason for this is that several of them are not easily measured — rather, they are experienced.

Until a couple of years ago, the standard answer you would get from any audio engineer worth his salt when asked the question "Why do valve amps sound better than transistors?" would have been "Well, valves produce more even-harmonic distortion, and you like the distortion, which is more musical" than the distortion produced by a transistor amp. And after all, transistors are more distortion-free than valves ever were. He would not give the same answer today, unless he spent all his time listening to test instruments instead of real signals.

A big question that needs to be discussed is "Is distortion just a variable you can measure with test equipment or is high fidelity, in the words of a well-respected manufacturer, 'the closest approach to the original sound'?" What does it mean to have 0.0001% distortion when it still doesn't sound like the original (and when the speakers are adding a further 2%)?

## Distorted assumption

The tacit assumption in the design of so-called valve sound musical instrument amplifiers is "Musicians like the sound of a valve amp. Valve amps may have more distortion. Therefore musicians like the distortion."

Manufacturers thus have produced special boxes which may introduce up to 25% second harmonic distortion and come up with a valve-sound, which some musicians like, but many describe as sounding more like a fuzz box than an AC30.

This seems to suggest that maybe we aren't just talking about distortion. And when we come on to studio monitoring amplifiers, we find that there is little significant difference in distortion figures between solid state and thermionic equipment. It must be remembered, however, that we are not suggesting that all valve amps are nice, or that all transistor amps are nasty. The major problems inherent in transistor amplifier design are the direct result of developments made on valve circuits. Also, these problems, as will be seen, do not necessarily apply to low-power transistor amplifiers as usually encountered in Hi-Fi systems. For example, the problems seem to arise in the method and amount of negative feedback application.

## Feedback and its Misuse

There are two major ways of applying negative feedback to an amplifier, in the form of an overall feedback loop from one end of the amp to the other, or by the application of an individual feedback path per stage. Valve amplifiers like the Leak triple loop feedback series primarily use the latter method with little additional overall feedback (typically about 10dB). Certain other valve amps relied mainly on a high



# VALVE SOUND

degree of overall feedback producing sound much closer to that of transistor amps. The main reason for the choice of overall feedback was obviously economic: a glance at the handful of components underneath a certain well-respected Hi-Fi amplifier will indicate how cheap they must have been to produce. But it appears that the amps which used a feedback loop on each individual stage that produce the oft-mentioned valve sound.

OK, you may well ask what's so bad about high levels of overall feedback. Well, there are three main reasons: one well-known, the others totally unheard of.

## T.I.D.

Almost everyone has heard of manufacturers' recent efforts to eliminate the newly-discovered menace of Transient Intermodulation Distortion, but, case you missed the (sub)story may be broadly described as the type of distortion produced when the rising edge of a waveform applied to the amplifier is rising faster than the total transit time of the time taken for a signal to pass through the amplifier. This may result in a spike of pure 100% distortion whose output power may well be limited only by the peak handling capacity of the PSU.

There are two ways of dealing with this. Either the initial stages of the amplifier must be capable of taking the maximum level of applied signal with no feedback applied, or the rising edges must be slowed down to avoid the effect. The latter solution is the one generally used today and is equivalent to placing a low-pass filter on the input to the

frequency response to something below the level of flat from DC to Light.

TID was not so prevalent in certain valve amplifiers because of a) locally applied feedback on the stage itself thus reducing the transit time (and perhaps electrons crawl more slowly across semiconductors than they travel in vacuum) and b) because the linear portion of the valve transfer curve is longer than the corresponding area of transistor characteristics.

## The Ricochet Effect

A point often not considered in amplifier design is that as negative feedback across the amp is increased the back-to-front impedance (ie the impedance from the output looking back up the feedback loop towards the input) is reduced. Some high-power transistor amps have loops with an impedance of only a few ohms. This is because transistors are generally low impedance devices.

But how does this affect the sound produced? Let us remember that amplifiers are most often used to drive loudspeakers which are placed in fortunately-not normally anechoic rooms. A loudspeaker can also be considered as a microphone and as such it is evident that whilst sound is being projected into the room it is also being picked up after multiple bouncing around by reflection and reconverted into voltages which will appear at the amplifier input. (The back-to-front impedance is sufficient to allow another way of looking at this would be to say that the loudspeaker is loaded by standing and other pressure-waves in a non-linear manner with respect to frequency. The total effect is that the same source amplifier-speaker system will sound different in various locations

whilst a system without this effect will vary only slightly according to room acoustics. We noticed this whilst working in a studio fitted with Tannoy Monitor Reeds in Lockwood cabinets, overdriven by well-known 300 W transistor power amps. The act of penning a signal from left to right changed its sound dramatically, far more than one would expect in an acoustically treated studio environment. Replacing the studio amps with our venerable bottles however removed the effect almost entirely, most other factors (including subjective SPL) remaining equal. The transistor amps of course had a high level of overall feedback, unlike the valve system.

## Frequency Response


One problem with evaluating the Ricochet Effect and to some extent TID is that they are very hard to measure objectively. You should be able to pick them out by listening critically, but using normal test procedures it will often be found that there is little discernible difference between nice and nasty sounding amps on the test bench. However, one point of comparison has emerged. It was found that a number of nasty sounding amplifiers had a very limited frequency response with the feedback loop removed (one specimen managed 3 dB points at 250 Hz and 8 kHz approx, with 40 Hz and 15 kHz over 10 dB down), whereas our nicest amplifier was found to be nearly flat under similar conditions (3 dB points at 40 Hz and 15 kHz approx). However, this point required further investigation and removing a feedback loop is not always as easy as one would wish.

As far as the Ricochet effect is concerned we have so far found no other satisfactory explanation for the phenomenon, try it and see!
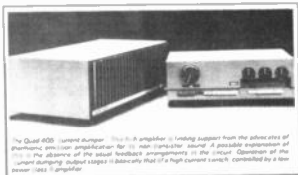
## Conclusions

The result of a few years of subjective listening tests has indicated very firmly to us that the second harmonic distortion explanation for the valve sound IS **LARGELY A FALLACY**. And after all, we were always taught at college that push-pull output stages cancelled out even harmonic distortion. Where is it all coming from?

We feel that the major reason for certain valve amps sounding better than certain transistor amps is largely the result of the use of smaller amounts of overall feedback, the former resulting in less TID and the reduction of what we have termed the hypothetical Ricochet Effect.



The Quad 405 current source. The 6N6 amplifier. The push-pull support from the previous stage of the harmonic distortion amplifier for the 6N6 push-pull sound. A possible explanation of the absence of the usual feedback components in the circuit. Operation of the current source. Output stage is identical to that of a high current source controlled by a low current source.



# CBM Calculators Special Spring Offer

**£5 OFF SHOP PRICE** Commodore 4190 The outstanding scientific rechargeable calculator for today and tomorrow's needs.

**£2 OFF SHOP PRICE** Commodore 4148 The very popular AB single key rechargeable scientific calculator.

**£1 OFF SHOP PRICE** Commodore 1800 The everyday scientific calculator featuring big green display and unique 3-way power system.

Voucher valid at participating Commodore retailers ONLY  
TILL 20 JUNE 77

Scissors icon

British-made Commodore calculators outsell all others. It's not surprising. Because Commodore's advanced technology gives you all you want in a calculator now - plus all you're likely to need.



**commodore**

More than a calculator • a sensible investment

Commodore Business Machines Ltd, 148-149 East Point, Troop, Bexley SE18 3SD

## ETI READER OFFER

# ZARTRONIX

### WIRE THREADING INTROKIT

USUAL PRICE **£5.95** ETI OFFER PRICE **£4.50** inc



#### KIT INCLUDES

- 1/16" Distribution Panel
- Spare wire spool
- Circuit Board
- IC tag deframer
- WD Rings (press 5 glue fit)
- Full instructions

ETI has arranged it's offer to introduce readers to the best scientific principle IC tag deframer. Please send request for this offer to: ETI, 115 Lion Lane, Haslemere, Surrey GU27 1JL

The Zartronix IC tag deframer is a simple yet powerful tool. It is made of plastic and has a 1/16" distribution panel. The distribution panel has 16 pins. The IC tag deframer is a simple yet powerful tool. It is made of plastic and has a 1/16" distribution panel. The distribution panel has 16 pins.

Offer expires July 31st 1977

To: ETI Reader offer  
**ZARTRONIX**  
115 Lion Lane, Haslemere, Surrey GU27 1JL

Please send ... Zartronix Wire Threading Introkit for which I enclose (at £4.50 each)

Name .....  
Address .....  
.....

ACL 50 CAGS 10

Signature



# electronics today

What to look for in the August issue: On sale July 1st

## SOIL MOISTURE INDICATOR

HOW TO KEEP YOUR HORTICULTURE HAPPY

"THE ANSWER lies in the soil." Used to be a statistic joke but its true especially if household plants.

Soil tests have long been used to measure the nutrient content and to ensure the right mix of salts and get optimum results. The answer does lie in the soil, and for house-planters.

In these days of nitrogen, phosphorus, potassium, etc., dosing your finger with the water of a soil plant is not only tedious, it is also unnecessary. There is a simple device that is easy to use and does not cost a lot of money. It is the Soil Moisture Indicator.

And it works. It tells you when the soil is dry, when it is too wet, and when it is just right. It is a simple device that is easy to use and does not cost a lot of money. It is the Soil Moisture Indicator.



## SWEEP GENERATOR

A FULLY automatic sweep generator with a range of frequencies from 100 to 10,000 Hz. It is a simple device that is easy to use and does not cost a lot of money. It is the Sweep Generator.

## 3-TRANSISTOR RADIO

The first of the new 3-transistor radios is the 3-Transistor Radio. It is a simple device that is easy to use and does not cost a lot of money. It is the 3-Transistor Radio.

## PICKUP PRINCIPLES



THIS IS how the pickup works. The first principle is the magnet. The second is the coil. The third is the damper. The fourth is the pole piece. The fifth is the cantilever. The sixth is the stylus.

The first of the new 3-transistor radios is the 3-Transistor Radio. It is a simple device that is easy to use and does not cost a lot of money. It is the 3-Transistor Radio.

## ETI'S COVER PRICE

ETI'S COVER PRICE is the price of the magazine. It is a simple device that is easy to use and does not cost a lot of money. It is the ETI's Cover Price.

## FREE INSIDE THE AUGUST ISSUE MARSHALLS CATALOGUE

The August issue of the magazine is the Marshall's Catalogue. It is a simple device that is easy to use and does not cost a lot of money. It is the Marshall's Catalogue.

The first of the new 3-transistor radios is the 3-Transistor Radio. It is a simple device that is easy to use and does not cost a lot of money. It is the 3-Transistor Radio.

The first of the new 3-transistor radios is the 3-Transistor Radio. It is a simple device that is easy to use and does not cost a lot of money. It is the 3-Transistor Radio.

The first of the new 3-transistor radios is the 3-Transistor Radio. It is a simple device that is easy to use and does not cost a lot of money. It is the 3-Transistor Radio.

# ETI DATA SUPPLEMENT

PRESENTED FREE WITH ELECTRONICS TODAY INTERNATIONAL JULY 1977

Hexadecimal and Binary conversion  
Tables  
Logic family comparisons  
Logic symbols and Truth tables  
Logic of Boolean algebra  
Transistor and FET characteristics

Resistor and Diode characteristics  
Component codes  
TTL to CMOS functional equivalents  
Standard 40 Amp circuits  
Standard Power supply configurations  
Microprocessor Glossary

# HEXADECIMAL AND DECIMAL INTEGER CONVERSION TABLE

| 8   |               | 7   |             | 6   |            | 5   |         | 4   |         | 3   |         | 2   |         | 1   |         |
|-----|---------------|-----|-------------|-----|------------|-----|---------|-----|---------|-----|---------|-----|---------|-----|---------|
| Hex | Decimal       | Hex | Decimal     | Hex | Decimal    | Hex | Decimal | Hex | Decimal | Hex | Decimal | Hex | Decimal | Hex | Decimal |
| 0   | 0             | 0   | 0           | 0   | 0          | 0   | 0       | 0   | 0       | 0   | 0       | 0   | 0       | 0   | 0       |
| 1   | 258 435 456   | 1   | 16 777 216  | 1   | 1 048 576  | 1   | 65 536  | 1   | 4 096   | 1   | 256     | 1   | 16      | 1   | 1       |
| 2   | 536 870 912   | 2   | 33 554 432  | 2   | 2 097 152  | 2   | 131 072 | 2   | 8 192   | 2   | 512     | 2   | 32      | 2   | 2       |
| 3   | 805 306 368   | 3   | 50 331 648  | 3   | 3 145 728  | 3   | 196 808 | 3   | 12 288  | 3   | 768     | 3   | 48      | 3   | 3       |
| 4   | 1 073 741 824 | 4   | 67 108 864  | 4   | 4 194 304  | 4   | 262 144 | 4   | 16 384  | 4   | 1 024   | 4   | 64      | 4   | 4       |
| 5   | 1 342 177 280 | 5   | 83 886 080  | 5   | 5 242 880  | 5   | 327 880 | 5   | 20 480  | 5   | 1 280   | 5   | 80      | 5   | 5       |
| 6   | 1 610 612 736 | 6   | 100 663 296 | 6   | 6 291 456  | 6   | 393 216 | 6   | 24 576  | 6   | 1 536   | 6   | 96      | 6   | 6       |
| 7   | 1 879 048 192 | 7   | 117 440 512 | 7   | 7 340 032  | 7   | 458 112 | 7   | 28 672  | 7   | 1 792   | 7   | 112     | 7   | 7       |
| 8   | 2 147 483 648 | 8   | 134 217 728 | 8   | 8 388 608  | 8   | 524 288 | 8   | 32 768  | 8   | 2 048   | 8   | 128     | 8   | 8       |
| 9   | 2 415 919 104 | 9   | 150 994 944 | 9   | 9 437 184  | 9   | 589 624 | 9   | 36 864  | 9   | 2 304   | 9   | 144     | 9   | 9       |
| A   | 2 684 354 560 | A   | 167 772 160 | A   | 10 485 760 | A   | 655 360 | A   | 40 960  | A   | 2 560   | A   | 160     | A   | 10      |
| B   | 2 952 790 016 | B   | 184 549 376 | B   | 11 534 336 | B   | 720 896 | B   | 45 056  | B   | 2 816   | B   | 176     | B   | 11      |
| C   | 3 221 225 472 | C   | 201 326 592 | C   | 12 582 912 | C   | 786 432 | C   | 49 152  | C   | 3 072   | C   | 192     | C   | 12      |
| D   | 3 489 660 928 | D   | 218 103 808 | D   | 13 631 488 | D   | 851 968 | D   | 53 248  | D   | 3 328   | D   | 208     | D   | 13      |
| E   | 3 758 096 384 | E   | 234 881 024 | E   | 14 680 064 | E   | 917 504 | E   | 57 344  | E   | 3 584   | E   | 224     | E   | 14      |
| F   | 4 026 531 840 | F   | 251 658 240 | F   | 15 728 640 | F   | 983 040 | F   | 61 440  | F   | 3 840   | F   | 240     | F   | 15      |
| B   |               | 7   |             | 6   |            | 5   |         | 4   |         | 3   |         | 2   |         | 1   |         |

## TO CONVERT HEXADECIMAL TO DECIMAL

1. Locate column of decimal numbers corresponding to left-most digit or letter of hexadecimal number from this column and record number that corresponds to position of hexadecimal digit or letter.
2. Repeat step 1 for next second from left position.
3. Repeat step 1 for units (third from left position).
4. Add numbers selected from table to form decimal number.

## TO CONVERT DECIMAL TO HEXADECIMAL

1. A. Select from table highest decimal number that is equal to or less than number to be converted.  
B. Record hexadecimal of column containing selected number.  
C. Subtract selected decimal from number to be converted.
2. Using remainder from step 1 (C) repeat all of step 1 to develop second position of hexadecimal (and remainder).
3. Using remainder from step 2 repeat all of step 1 to develop units position of hexadecimal.
4. Combine terms to form hexadecimal number.

# COMPARISON OF STANDARD LOGIC FAMILIES

| Logic family | Noise Immunity Volts | Prop. delay nS | Fan Out | Max. Toggle Speed MHZ | Supply Voltage<br>Nominal Min. Max. V V V |      |      | Power Diss. per package mW (typ) | Decoupling and other requirements                                                                            |
|--------------|----------------------|----------------|---------|-----------------------|-------------------------------------------|------|------|----------------------------------|--------------------------------------------------------------------------------------------------------------|
| 74 Series    | 0.4                  | 9              | 10      | 15                    | 5.0                                       | 4.75 | 5.25 | 40                               | 0.1 uF Ceramic capacitor for every 8 packages to eliminate switching current spike<br>No special precautions |
| 74H Series   | 0.4                  | 6              | 10      | 40                    | 5.0                                       | 4.75 | 5.25 | 60                               |                                                                                                              |
| 74S Series   | 0.3                  | 3              | 10      | 125                   | 5.0                                       | 4.75 | 5.25 | 40                               |                                                                                                              |
| 74LS Series  | 0.3                  | 9              | 10      | 25                    | 5.0                                       | 4.75 | 5.25 | 8                                |                                                                                                              |
| CMOS         | 4.5                  | 30             | >50     | 10                    | —                                         | 3.0  | 18.0 | 0.01                             |                                                                                                              |

### TTL BIPOLAR LOGIC

The 74 Series of transistor-transistor logic is a medium speed family of saturating integrated circuit logic designed for general digital logic application requiring clock frequencies to 30MHz and switching speeds in the 7-11 nS range under moderate capacitive loading.

The circuits are identified by a multiple emitter input transistor and an active "pull up" in the upper output network. Clamp diodes are provided at each input to limit the undershoot that occurs in typical system applications such as driving long interconnect wiring. The active pull-up output configuration provides low output impedance in the high output state. The resulting low impedances in both output states ensures excellent a.c. noise immunity and allows a high-speed operation with capacitive loads.

### COMPLEMENTARY MOS (CMOS)

Complementary MOS is the newest of the general purpose logic families.

The following are primary design features of the whole of the COS/MOS and McMOS ranges.

- Double diode protection on all inputs.
- Noise immunity typically 45% of VDD, 30% of VDD minimum.
- Buffered output compatible with MHTL and Low Power TTL.
- Low quiescent power dissipation: 25mW typ. per package.
- Wide power supply voltage: 3-18 Volt dependent on type.
- Single supply operation.
- High fanout: greater than 50.
- High input impedance: 10 ohms typ.
- Low input capacitance: 5pf typ.



# BASIC LOGIC SYMBOLS AND TRUTH TABLES

**BUFFER**

INPUT OUTPUT



| A | C |
|---|---|
| 0 | 0 |
| 1 | 1 |

**INVERTER**

INPUT OUTPUT



| A | C |
|---|---|
| 0 | 1 |
| 1 | 0 |

**AND GATE**



| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

**AND GATE**



| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

**OR GATE**



| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

**XOR GATE**



| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 0 |

**EXCLUSIVE  
OR GATE**



| A | B | C |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

**EXCLUSIVE  
NOR GATE**



| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

## LAWS OF BOOLEAN ALGEBRA

$$\begin{aligned}
 A + 0 &= A & A \cdot A &= A \\
 A + 1 &= 1 & A \cdot \bar{A} &= 0 \\
 A + \bar{A} &= 1 & A \cdot A &= A \\
 A + A &= A & A \cdot 1 &= A \\
 A \cdot B &= A \cdot B \cdot C \\
 A \cdot B \cdot C &= A \cdot B \cdot C \\
 A \cdot B \cdot C &= A \cdot B \cdot C
 \end{aligned}$$

**J K Flip Flop**



| INPUTS |     | OUTPUTS |   |        |             |
|--------|-----|---------|---|--------|-------------|
| CLR    | CLK | J       | K | Q      | $\bar{Q}$   |
| 0      | X   | X       | X | 0      | 1           |
| 1      | ⌋   | 0       | 0 | $Q_0$  | $\bar{Q}_0$ |
| 1      | ⌋   | 1       | 0 | 1      | 0           |
| 1      | ⌋   | 0       | 1 | 0      | 1           |
| 1      | ⌋   | 1       | 1 | TOGGLE | TOGGLE      |

⌋

HIGH LEVEL PULSE DATA IS TRANSFERRED ON FALL OF PULSE

$Q_0$

THE LEVEL OF Q BEFORE INDICATED INPUT COMBINATION WHEN STABLE

TOGGLE

EACH OUTPUT CHANGES TO ITS COMPLEMENT ON EACH ACTIVE TRANSIENT PULSE OF CLOCK



## ND FET CHARACTERISTICS

[illegible]

[illegible]

| DIODES        | CASE  | V <sub>B</sub> | I <sub>F</sub> (mA) | C <sub>tr</sub> (pF) | V <sub>R</sub> | $\phi$ | I <sub>R</sub> (mA) | I <sub>RR</sub> (A) | V <sub>RR</sub> | T <sub>j</sub> (°C) | USE                       | COMPARABLE TYPES |
|---------------|-------|----------------|---------------------|----------------------|----------------|--------|---------------------|---------------------|-----------------|---------------------|---------------------------|------------------|
| <b>Signal</b> |       |                |                     |                      |                |        |                     |                     |                 |                     |                           |                  |
| 1N4148        | DO-35 | 75             | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4149        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4150        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4151        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4152        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4153        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4154        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4155        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4156        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4157        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4158        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4159        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4160        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4161        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4162        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4163        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4164        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4165        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4166        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4167        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4168        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4169        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4170        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4171        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4172        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4173        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4174        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4175        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4176        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4177        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4178        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4179        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4180        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |
| 1N4181        | DO-35 | 100            | 10                  | 5                    | 0.5            | 0.7    | 100                 | 0.01                | 100             | 75                  | General purpose switching | 1N4148           |

RESISTOR VALUES WILL BE REPRESENTED THUS:

|               |                  |      |               |                  |       |
|---------------|------------------|------|---------------|------------------|-------|
| 0.47 $\Omega$ | will be shown as | R 47 | 100 $\Omega$  | will be shown as | 100 R |
| 1 $\Omega$    | will be shown as | 1R   | 1 k $\Omega$  | will be shown as | 1k    |
| 4.7 $\Omega$  | will be shown as | 4R7  | 10 k $\Omega$ | will be shown as | 10 k  |
| 47 $\Omega$   | will be shown as | 47 R | 10 M $\Omega$ | will be shown as | 10 M  |


CAPACITOR VALUES WILL BE REPRESENTED THUS:

|         |                  |       |
|---------|------------------|-------|
| 10 pF   | will be shown as | 10 p  |
| 1000 pF | will be shown as | 1n    |
| 1 uF    | will be shown as | 1u    |
| 4.7 uF  | will be shown as | 4u7   |
| 100 uF  | will be shown as | 100 u |

[illegible]

# STANDARD OPERATIONAL AMPLIFIER CIRCUITS

Non-Inverting Buffer

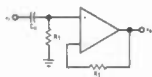


$$A_v = 1$$

$$R_{in} = R_1$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

Definitions:  
 $A_v$  = Closed Loop AC Gain  
 $R_{in}$  = Input Resistance (Load Included)  
 $f_c$  = Cutoff Frequency

Non-Inverting AC Amplifier

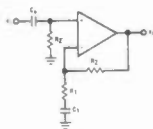


$$A_v = 1 + \frac{R_2}{R_1}$$

$$R_{in} = R_1$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

Difference Amplifier

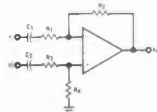


$$A_v = \frac{R_2}{R_1} \left( \frac{R_1 + R_2}{R_1} \right)$$

$$R_{in} = R_1 + R_2$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

Inverting Buffer

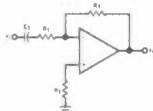


$$A_v = -1$$

$$R_{in} = R_1$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

Inverting AC Amplifier

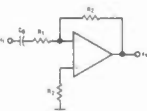


$$A_v = -\frac{R_2}{R_1}$$

$$R_{in} = R_1$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

Inverting Summing Amplifier

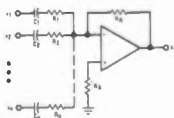

$$A_v = -\left( \frac{R_2}{R_1} + \frac{R_2}{R_2} + \frac{R_2}{R_3} + \frac{R_2}{R_4} \right)$$

$$R_{in} = R_1 + R_2 + R_3 + R_4$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

THE SUPPLY CONNECTIONS HAVE BEEN OMITTED IN THE ABOVE CONFIGURATIONS FOR THE SAKE OF CLARITY.

# STANDARD POWER SUPPLY CONFIGURATIONS

FULL-WAVE BRIDGE - CAPACITIVE INPUT FILTER



$$V_{dc} = 0.95 V_{sec}$$

$$I_{dc} = 0.82 I_{ac}$$

FULL-WAVE BRIDGE - RESISTIVE LOAD



$$V_{dc} = 0.90 V_{sec}$$

$$I_{dc} = 0.90 I_{ac}$$

HALF-WAVE - CAPACITIVE INPUT FILTER



$$V_{dc} = 0.45 V_{sec}$$

$$I_{dc} = 0.28 I_{ac}$$

FULL-WAVE - CAPACITIVE INPUT FILTER



$$V_{dc} = 0.95 V_{sec}$$

$$I_{dc} = 0.82 I_{ac}$$

FULL-WAVE - RESISTIVE LOAD



$$V_{dc} = 0.90 V_{sec}$$

$$I_{dc} = 0.90 I_{ac}$$

HALF-WAVE - RESISTIVE LOAD



$$V_{dc} = 0.45 V_{sec}$$

$$I_{dc} = 0.28 I_{ac}$$



# FROM ETI TECHNICAL BOOKS FROM

## TECHNICAL BOOKS FROM ETI TECHNICAL BOOKS

### CALCULATIONS

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### COMMUNICATIONS

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### COMPUTER AND MICROPROCESSORS

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### TELEVISION AND AUDIO

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### TEST EQUIPMENT AND OSCILLOSCOPES

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### TELEVISION AND AUDIO

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### TEST EQUIPMENT AND OSCILLOSCOPES

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

### TELEVISION AND AUDIO

**ADVANCED ELECTRIC CIRCUIT CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**DIFFERENTIAL CALCULATIONS**  
By A. C. Smith  
117 pp.  
\$1.75

**WAVE THEORY OF LIGHT**  
By A. C. Smith  
117 pp.  
\$1.75

# TECHNICAL BOOKS FROM ETI

## ETI TECHNICAL BOOKS FROM ETI TECHNICAL

# MICROFILE

**Gary Evans, ETI's resident microprocessor man, powers up microfile to report on a new personal computing system and Europe's first conference for home computer builders.**

THE HOMEBREW COMPUTER market in this country seems about to 'take off'. With sales of manufacturer's development kits on the increase, and signs that many firms are beginning to move into the hardware/software supply field, it seems that this sector of the hobby electronics market will be one of the major growth areas over the next few years.

This month we report on two recent events which reflect this growing interest in the home computing field. The interest ranges from the large manufacturers ready to sell complete systems, to the smaller supplier specialising in the provision of hardware and software for the D.I.Y. market.

## Household Pet

First off we look at CBM's announcement that they intend to launch their PET Model 2001 towards the end of this year. PET (Personal Electronics Transaction) is a compact and very versatile home computer system, complete with display screen, cassette interface and a calculator style keyboard.

The basic unit's display screen is a nine-inch CRT capable of a 1000 character display arranged as 40 columns x 25 lines. The display has a standard 64 character ASCII set as well as 64 graphics related characters.

Input to PET is via a calculator style keyboard which allows the basic 64 characters to be entered without shift, while the shift control allows the graphics characters to be entered. Various screen editing and control functions are also available from the keyboard.

Model 2001 provides a cassette interface which uses standard audio cassette tapes to provide program and data storage for the system. The cassette storage system has a number of facilities which allow easy editing and management of user programs.

PET is based on the MOS Technology's (not MOSTEK!) MOS 6502 microprocessor. This micro is popular in the States but has not been seen very much over here, although with the recent announcement that Rockwell are to second source this chip, the situation might change.



*Our astronaut is soon landing her LHM with the help of PET's moon landing program. A wide variety of software is available for PET, covering applications, the home, for example, storing records, its programs for small industrial users. The PET CRT with graphics handling capability, the calculator style keyboard, and cassette interface, all in one - see pic over.*

The system memory is provided by 12 K of ROM and 4 K of RAM (expandable to 32 K). The ROM is divided into two blocks. The first block of 4 K provides the operating system. This will allow Machine language accessibility and is capable of supporting multiple languages.

The resident high level language is BASIC, and is provided by an interpreter occupying the remaining 8 K of system ROM. CBM claim that this BASIC interpreter is 20% faster than other 8 K BASICs. The interpreter provides facilities for handling strings, integer and multiple dimension arrays as well as providing a random number generator.

CBM hope to provide a large range of cassette based software for the system. The programs will cover such areas as video games, list management and inventory control. As well as CBM's software, there is a vast amount of material already available in BASIC language.

There are plans to produce peripherals that will extend the scope of PET's activities, floppy disks, printers and a MODEM are at present under development.

PET will even tell you when it is sick. A self-diagnostic trouble light will tell the operator if any of the boards are not working properly.

The unit should be in production during the summer with a target production figure of 1 000 (yes one thousand) per day. The price in this country is expected to be 'wait for it' £800.

At this price, not much more than a teletext decoder or a large colour-TV set, CBM see a vast potential in the home and small industrial markets. They are reducing their commitments to electronic calculators and plan to devote much of their energies to the manufacture and supply of PET.

About the only thing this PET will not do is come when you call it, and CBM may well be working on that.





# ETI DATA SHEET

ICL 8038 WAVEFORM GENERATOR/V.C.O.

INTERSIL

The 8038 has been around for about 5 years — which is a long time in electronics. In fact it has reached the position of becoming an Industry Standard on a par with the 741. An inherently versatile device it has its drawbacks like most chips — but overall has a lot going for it. Intersil even produced a very honest application bulletin AD131 called 'Everything you always wanted to know about the 8038' which explained how to get the best out of this device and admitted its defects — an uncommon event with most manufacturers! Some of the data from AD131 has been included in this data sheet but for fuller information ask Rapid Recall for AD13 AD12 and the latest information sheet (strangely referenceless but brown in colour!)

## Description

The 8038 Waveform Generator is a monolithic integrated circuit capable of producing sine square triangular sawtooth and pulse waveforms of high accuracy. The frequency or repetition rate can be selected externally over a range of less than 1 1000 Hz to more than 1 MHz and is highly stable over a wide temperature and supply voltage range. Frequency modulation and sweeping can be accomplished with an external voltage and the frequency can be programmed digitally through the use of either resistors or capacitors. The Waveform Generator utilizes advanced monolithic technology such as thin film resistors and Schottky barrier diodes.

## Theory of operation

A block diagram of the waveform generator is shown in Figure 1. An external capacitor C is charged and discharged by two current sources. Current source #2 is switched on and off by a flip-flop while current source #1 is on continuously. Assuming that the flip-flop is in a state such that current source #2 is off, then the capacitor is charged with a current I. Thus the voltage across the capacitor rises linearly with time. When this voltage reaches the level of comparator #1 set at 2/3 of the supply voltage, the flip-flop is triggered, changes states and releases current source #2. This current source normally carries a current 2I, thus the capacitor is discharged with a net-current I and the voltage across it drops linearly with time. When it has reached the level of comparator #2 set at 1/3 of the supply voltage, the flip-flop is triggered into its original state and the cycle starts anew.

Four waveforms are readily obtainable from this basic generator circuit. With the current sources set at 1I and 2I respectively the charge and discharge times are equal.

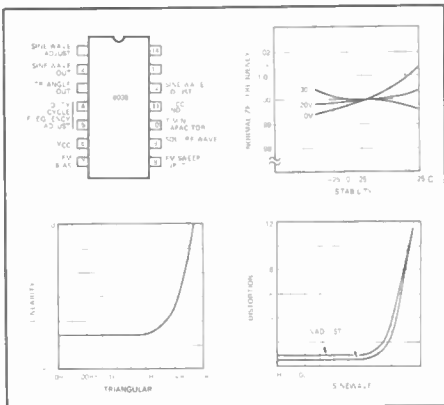


Fig 1. BLOCK DIAGRAM OF WAVEFORM GENERATOR

Thus a triangle waveform is created across the capacitor and the flip-flop produces a square-wave. Both waveforms are fed to buffer stages and are available at pins 3 and 8.

The levels of the current source can however be selected over a wide range with two external resistors. Therefore, with the two currents set at values different from 1 and 2, an asymmetrical waveform appears at terminal 3 and pulses with a duty cycle from less than 1% to greater than 99% are available at terminal 8.


The sine-wave is created by feeding the triangle-wave into a non-linear network (see component). This network provides a generating function equivalent to the integral of the triangle, making the two extremes.

## Power Supply

The waveform generator can be operated either from a single power supply, 10 to 30 Vdc, or a dual power supply,  $\pm 5$  to  $\pm 15$  Vdc. With a single power supply the average levels of the triangle and sine wave are at exactly one-half of the supply voltage, while the square wave alternates between  $+V$  and ground. A split power supply has the advantage that all waveforms move symmetrically about ground.

Also notice that the square wave output is not inverted. The load resistor can be connected to a different power supply, as long as the applied voltage remains within the breakdown capability of the waveform generator (20 V). In this case, the square-wave output is made 7% compared to the resistor connected to  $+5$  volts, while the waveform generator itself is powered from a much higher voltage.

## Purity

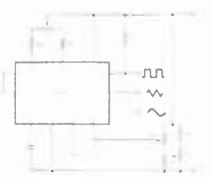

The symmetry of all waveforms can be adjusted with the external timing resistors. To minimize skew-when observed, the capacitors between pins 11 and 12 are best made variable ones. With this arrangement, portions of less than 1% is achievable. To adjust this even further, new potentiometers can be connected as shown. This configuration can allow a reduction of skewness distortion, close to 0.5%.

Both the sine-wave and triangular output are pins used up to about 20kHz at a relatively pure signal is required. A proof of this points will show only.


## Strobe



With a dual supply voltage  $\geq 15V$ , the external capacitor pin 10, can be shorted to ground so that the sine wave and triangle wave always begin at a zero crossing point. Random switching has a 50/50 chance of starting on a positive or negative slope. A simple AND gate using pin 9 will allow the choice to start on one slope or the other.


Using only a single supply, the capacitor pin 10 can be switched either to  $+V$  or ground to force the capacitor to start in either the charge or discharge mode. The disadvantage of this technique is that the beginning time of the next burst will be 30% longer than the normal cycle.

## F.M. and Sweeping

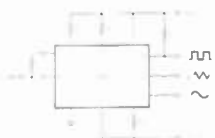

The frequency of the waveform generator is a direct function of the DC voltage at terminal 8 measured from  $+VCC$ . Thus by varying this voltage, frequency modulation is achieved.

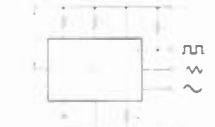For small deviations (i.e.,  $\pm 10\%$ ) the modulating signal can be applied directly to pin 8, merely providing its decoupling with a capacitor. An external resistor between pins 7 and 8 is not necessary, but it can be used to improve input impedance. Without a 1k resistor, 7 and 8 connected together, the input impedance is 8k. With it, this impedance increases to  $8k \times Bk$ .



For larger FM deviations or for frequency sweeping, the modulating signal is applied between the positive supply voltage and pin 8. In this way the entire bias for the current source is changed by the modulating signal and a very large (e.g., 1000:1) sweep range is obtained (i.e.,  $V_{CC} \approx 0$ ). Care must be taken, however, to regulate the supply voltage; in this configuration the change

current is no longer a function of the supply voltage, yet the trigger thresholds still exist and thus the frequency becomes dependent on the supply voltage. The potential on pin 8 may be swept from  $V_{CC}$  to about  $2/3 V_{CC}$ .

## Buffering



The sine wave output has a relatively high output impedance (1k Typ). The circuit provides buffering, gain, and amplitude adjustment. A simple op amp buffer circuit can be used.

If the oscillator outputs are all fed through a buffer, extra resistors can be inserted in series with the signal before a switch. Values of 47k square wave, 15k triangular and 10k sine wave will ensure equal amplitude signals.

## Audio Oscillator



To obtain a 1000:1 Sweep Range in the audio voltage across external resistors RA and RB must decrease to nearly zero. This requires that the highest voltage on terminal Pin 8 exceed the voltage at the top of RA and RB by a few hundred millivolts.

The circuit achieves this by using a diode to lower the effective supply voltage on the B038. The large resistor on pin 5 helps reduce duty cycle variations with sweep. The range of the circuit is 20kHz to 20 kHz output buffer can be added to make a general purpose bench unit.

## Points to Note!

The B038 runs hot to touch; this is minimal, and is due to the relative nature of the sensitive shaping network.

The optimum supply voltage for minimum temperature drift is 30V; this can be seen in the supply graph.


The B038 is available from **Rapid Recall Ltd., 9 Batterton Street, Drury Lane, London WC2H 9BS.** Price for 1 off is **£4.08 inclusive**.

The Intersil ICM 7205 is a relatively new device, main points of interest are: on chip display drivers, fully protected against static - no special handling precautions required, average current of only 10 mA when in operation (including display!)

The ICM 7205 is a fully integrated CMOS six digit stop watch circuit. The circuit interfaces directly with a six digit/ seven segment common cathode LED display. The low battery indicator can be connected to the decimal point anode or to a separate LED lamp. The only components required for a complete stopwatch besides the display are: three SPST switches, a 3.2768 MHz crystal, a trimming capacitor, three AA batteries, and an on-off switch. For a two function stopwatch one additional switch would be required.

The circuit divides the oscillator frequency by  $2^{15}$  to obtain 100 Hz which is fed to the fractional seconds, seconds and minutes counters. An intermediate frequency is used to obtain the 1/6 duty cycle 1.07 kHz multiplex waveforms. The blanking logic provides leading zero blanking for seconds and minutes independently of the clock. The ICM7205 is packaged in a 24 lead plastic DIP.

#### Stopwatch Circuit

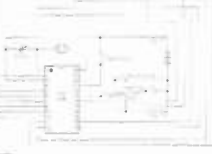

#### Switch Characteristics

The ICM7205 is designed for use with SPST switches throughout. On the display unlock and reset inputs the characteristics of the switches are unimportant, since the circuit responds to a logic level held for any length of time, however short. Switch bounce on these inputs does not need to be specified. The Start/Stop input however responds to an edge and it requires a switch with less than 15 ms of switch bounce. The bounce protection circuitry has been specifically designed to let the circuit respond to the first edge of the signal, so as to preserve the full accuracy of the system.

#### Low Battery Indicator

The on-chip low battery indicator is intended for use with a small LED lamp or with the decimal points on a standard LED display. The output is the drain of a P-channel transistor of approximately half the size of one of the segment drivers. The LBI circuitry is designed always to provide a voltage difference between the LBI trigger voltage and the minimum operating voltage, i.e. the lower the LBI trigger voltage the lower the minimum operating voltage. In this way a stopwatch using three AA batteries will provide at least 15 minutes of accurate timekeeping after the LBI comes on.

#### Functional Operation

Turning on the stopwatch will bring up the reset state where the fractional seconds are on displaying 00 and the other digits are blanked. This display always indicates that the stopwatch is ready to go.

#### Start/Stop



The Start/Stop modes can be used for a single event timing with the Split/Taylor input in either state. The illustration indicates the operations and the results. To time another event the reset switch must be used prior to the start of the event. Seconds will be displayed after one second, minutes after one minute. The range of the stopwatch is 59 minutes 59.99 seconds. If an event exceeds one hour, the number of hours must be remembered by the user. Leading zeros are not blanked after one hour.

#### Taylor



When the Split/Taylor input is left open circuit or is connected to Vss, the stopwatch can be used in the Taylor or sequential mode. As depicted graphically above, each split time is measured from zero in the Taylor mode, i.e. after stopping the watch, the counters reset to zero momentarily and start counting the next interval. The time displayed is the time elapsed since the last activation of Start/Stop. The display is stationary after the first interval unless the display unlock is used to show the running clock. Reset can be used at any time.

#### Split



When the Split/Taylor input is connected to VDD, the stopwatch is in the Split mode. The Split mode differs from the Taylor in that the lap times are cumulative in the Split mode. The counters do not reset or stop after the first start until reset is activated. Any time displayed is the cumulative time elapsed since the first start after reset. Display unlock can be used to let the display 'catch up' with the clock. Reset can be used at any time.

#### Points to Note

Absolute maximum supply voltage is 5V5. Never short outputs to earth or low impedance power supply as this will destroy the device.

The ICM 7205 is available from: Rapid Recall Ltd., 9, Betterton Street, Drury Lane, London WC2H 9BS. Price for one off is £12.60 inclusive.

# SPECIALS FROM ETI



## TOP PROJECTS No. 1 + No. 2

Projects 1-2000  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £2.50

£2.50 + 20p P&P



## TOP PROJECTS No. 3

Projects 201-400  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.00

£1.00 + 20p P&P



## TOP PROJECTS No. 4

Projects 401-600  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.00

£1.00 + 20p P&P



## TOP PROJECTS No. 5

Projects 601-800  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.00

£1.00 + 20p P&P



## ETI CIRCUITS No. 1

Projects 1-100  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.50

£1.50 + 20p P&P



## ELECTRONICS — IT'S EASY

Projects 801-1000  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.20

£1.20 + 20p P&P



## ETI 4600 SYNTHESIZER

Projects 1001-1200  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.50

£1.50 + 20p P&P



## HOW TO ORDER

Projects 1201-1400  
Circuit diagrams  
Parts lists  
Construction hints  
Troubleshooting tips  
Safety notes  
Index  
Price: £1.00



Described by John Miller-Kirkpatrick

LAST MONTH WE LEFT YOU with board A completed and checked by temporarily connecting the address generator outputs to the data inputs. All of these temporary connections are now removed and a ribbon cable connected to the points marked. The reason for using ribbon cable is for neatness and sanity for connection of about 9 in. of 20-way cable is needed.

### Assembly Board B

As with PCB A the first thing to do is insert all of the through hole links solder and test for continuity. Sockets can then be installed in all IC locations and if required in all keyboard input connector. The 31 way connector should be installed at this stage and mounted on to the PCB with nuts and bolts through the holes provided.

The ribbon cable from PCB A is wired to connect the addresses from board A to B, the data from B to A and a power supply from B to A. A second cable carries the video signal, the video invert signal and ground to the front panel. With all of the soldering completed the ICs can be inserted and power applied to PCB B and thus also to A).


### How it works and why it doesn't

When the power is applied the sync oscillator may be out of alignment and need adjustment but leave the unit for about


30 seconds before making any adjustment as the oscRb for seems to need a warm up time. With the sync locked the display will probably show the same character in all locations on the screen. If you think about this it seems very unlikely that all of the locations of an 8Kbit RAM will turn on in the same state, the reason is quite simply that the screen is only getting one byte of data from the RAM. Although the address counters from board A are physically connected to the RAM they are directed via the 74C157s and the select lines of these hps are currently open circuit. A logical 1 at pin one of the 74C157s or at pin 15 of the 31 way connector will cause the selectors to use the PCB A addresses to access the RAM. With an MPU connected to the VDU this is the state that the selectors are normally in if the MPU wishes to

access the RAM it will signal that it wishes to do so by taking the VDU select line to logical 0.

As each RAM location is addressed by board A so the data for that location becomes available on the data bus. One problem here is that the time difference between asking for and getting the data is typically 650ns. This is approximately the same time as it takes to display a character width. Thus a sequence from the first character is presented to the RAM when the count enable line goes high as the counters have been reset for some time the RAM has had time to retrieve the data and present it to the character generator, thus if the first characters were ABCDE then an A will be displayed first. At the end of the first character time the address 0000000001 is given to the RAM but during the 650ns before

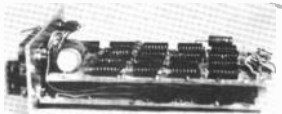

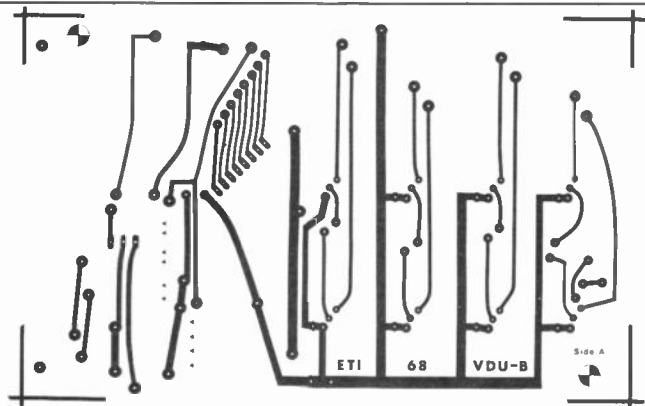View of the A and B boards ready for insertion into mainframe



VDU board B component side foil pattern shown full size

the data for 'B' is available at the character generator the generator has data for an A and thus the display now shows 'AA'. At some time near the end of the second character time the data for 'B' will become available at the character generator but as the RAMs can react at different times different bits become true at different times thus making the second half of the second character change to a B. Similarly the third character will become a B C the fourth a C/D and so on up to the end of a character row. At the end of the line the display enable turns off the character display, but the characters keep going until the count enable halts the count. The data for the last character is not available until just before the display is disabled but it is available for nearly 650ns after the display has been disabled.

### Problems

There are thus two problems: the first to latch the data bits at a specific time during each character to stop the ragged change from one displayed character to another; the second problem is then to lose the double first character and retrieve the last.


The DM8678 has an internal latch and can thus handle the latching for six data bits if an 8679

is used in tandem then seven bits will be latched leaving the extra data bits (if used) to be latched with the 7475. This latching was not shown in the circuit for PCB A but no additional ICs are required. Pin 4 of the DM8678 is connected to the inverse of the load signal on pin 10. Ideally the store signal should occur one bit time before the load but in practise it was found that the inverse of the load could be used. This is available at the output of IC11c.

To solve the second problem it would be useful if the whole display


enable area could be moved one position to the right. A simple way to do this is to break the signal from IC7 to IC12 and process this via the 7475 latch. As this latch is operated at the same time as the DM8678 Load and Store it means that the display enable signal is delayed by about one character time. This means that the enable is now turned on at the start of the second character and off at the start of character time after the last character in the row.

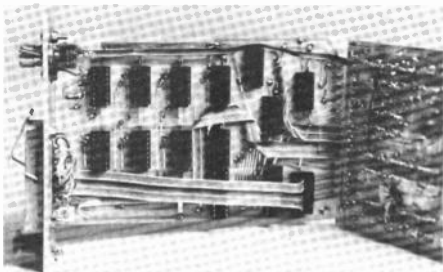If at this time the display is not nearly perfect then it is best to



The two boards opened out to give general idea of cable layout

# VIDEO DISPLAY UNIT

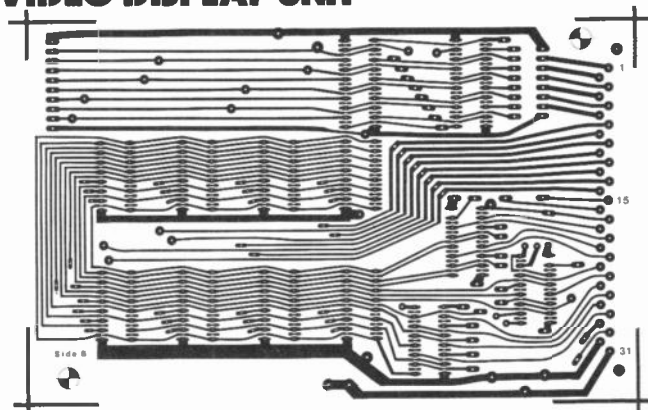

VDU board B underside foil pattern shown full size

## PARTS LIST

### INTEGRATED CIRCUITS

IC 18 20 74C157  
IC 21 28 MM2102-2  
IC 29-28 DM81L595

### MISCELLANEOUS

SW1 SPDT 316.709;  
D1 1N4148


### HARDWARE

16 pin d1 plug 401-841;  
IC socket strips 401-902) + holders  
401-920)  
ETI 68VDU board B (Croftan)  
Terminal pins 433 860)


Omitted from last month's parts list

Doram RS) numbers in brackets

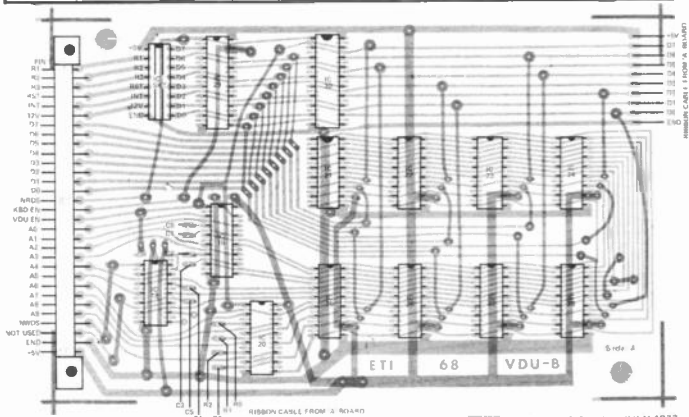A complete kit of all parts, including pcbs) is available from Bywood Electronics





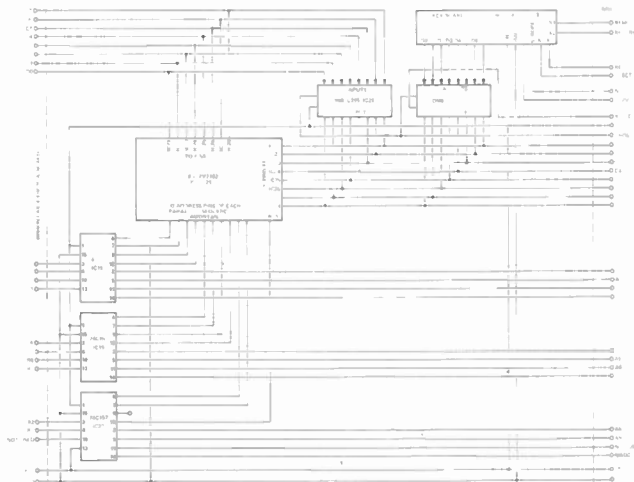

Full circuit diagram of the B board, in conjunction with last month's A board forms complete VDU module

assume race conditions in the ICs to be a problem. CMOS will not work much above 1MHz at 5v so check that there are no 74C series where there should be 74 series and vice-versa. It is also advisable to check for solder runs as we found a couple causing problems in the prototype. Problems with this type of equipment can be very difficult to cure without a very fast scope or a lot of thinking. Thinking is usually cheaper than scopes so use the circuit to narrow down faults and they soon become apparent.

### Keyboard Interface

In addition to the VDU interface this PCB also allows an ASCII keyboard to be connected into the system. As VDUs and keyboards go together in most applications it makes sense to have them on one interface board. If you are not using the System 68 case you may prefer to connect

the keyboard into the PCB using a standard 16-pin socket and pin header/plug. With the System 68 case we use a 2 in front panel module to carry the Video output socket, video invert switch and keyboard connector. We have used professional 25-way plugs and sockets wherever required as these tend to be an industry standard on this type of equipment. As the keyboard can be disconnected at the front panel the front panel connector can be wired into the 16-pin socket holes.

Whichever way you do it this connector carries 16 signals to - from the keyboard. We have allowed eight bit ASCII whereas a lot of keyboards have only six or seven bit output. The unused inputs can be connected to ground or to the keyboard strobe signal. Most keyboards feed on a diet of +5v, GND and -12v and so we


have provided for these lines to be keyboard. The other line we have to have is a strobe signal which should be negative going ie it is normally logic 1 unless a key is pressed in which case it goes to logic 0 until the key is released. We have four of our 16 leads unconnected. These are reserved for additional I/O signals to/from the keyboard. Such signals could be switches to the interrupt and/or reset pins of the MPU or could be status LEDs mounted on the keyboard.

### Checking out

Checking out is very tedious without an MPU because you have to simulate the control signals and that involves a lot of logic state changing and testing. It's worth doing at this stage because you then know that the VDU element works. A check sequence is given.
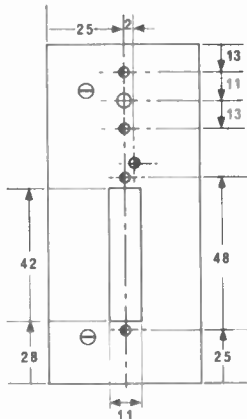
# VIDEO DISPLAY UNIT

Alternative positioning of sockets on front panel




## Folding up

Now is the time to fold up the two boards and check that they will fit in the case. Note that only PCB B is screwed to the front panel. A is held parallel to B by the card guides in the case; they should fit 1/2 in. apart and thus fit into adjacent card guides. If you have fitted your keyboard connector slightly off centre then you may find that the boards fit better 1 in. apart either is acceptable. Slide the unit into the case in the correct location and mark the position of the 31 way connector; slide the unit out; fit the 31-way socket; slide the unit home and feel that satisfying click as it locks into place.
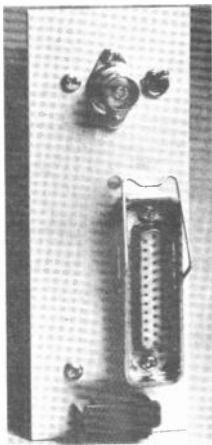
## Next month

How to use the VDU with an MPU, data and address buffers and things.

- DRILL 1 HOLE 28A
- DRILL 1 HOLE 48A
- DRILL 4 HOLES 68A



## System 68 VDU Checkout

This checkout routine involves a couple of subroutines called TEST BUS; this involves checking each bit of the appropriate data bus, unless you wish to do the FULLCHECK. (It is only necessary to convince yourself that no data bit is affecting another (odd bridge) and that all are connected at the appropriate points (open circuit, broken track)).

|                                                | KBD | EN | VDU | EN | MMDS | NRDS |                                |
|------------------------------------------------|-----|----|-----|----|------|------|--------------------------------|
| START                                          | 1   | 1  | 1   | 1  | 1    | 1    | TEST BUS AT VDU = BUS AT RAM   |
| WRITE TO VDU                                   | 1   | 0  | 0   | 1  | 0    | 1    | TEST BUS AT RAM = BUS AT INPUT |
| READ FROM VDU                                  | 1   | 0  | 1   | 0  | 1    | 0    | Ditto                          |
| READ FROM KBD                                  | 0   | 1  | 1   | 0  | 1    | 0    | TEST BUS KBD = BUS AT INPUT    |
| FULLCHECK                                      | 1   | 0  | 0   | 0  | 1    | 1    | ADDR AT INPUT = 00000000       |
| LOOP 1                                         |     |    |     |    |      |      | DATA AT INPUT = 10101010       |
| READ                                           | 1   | 0  | 1   | 0  | 1    | 0    | DATA AT RAM = 01010101         |
| WRITE                                          | 1   | 0  | 0   | 0  | 1    | 1    | DATA AT INPUT = 01010101       |
| READ 2                                         | 1   | 0  | 1   | 0  | 1    | 0    | DATA AT RAM = 01010101         |
| GOTO LOOP 1 after incrementing INPUT ADDR by 1 |     |    |     |    |      |      |                                |

## INTERESTED IN BONDAGE?

We've got something to interest you if you're that way inclined. Sorry, it's got nothing to do with kinkiness if that's what you thought, but if you want your old copies of ETI under bondage, we've got the perfect binder for you.

Beautiful quality as well, this binder. No messing with string, either: it has concealed rivets and gold lettering, and made specially for us in black simulated leather to take twelve issues of ETI.

P.S. Just in case, binders are sent under plain cover.

Send £2.50 (which includes VAT and postage) to:  
ETI Binders,  
25-27 Oxford Street,  
London W1R 1RF.

# RESISTOR CODES PART 11

## An explanation of the colour codings on all types of resistors

THE VALUE AND TOLERANCE, and other pertinent characteristics, of resistors may be marked on the body of the component in one of three ways. Viz:

(1) By marking directly on the body.  
(2) By using a standard colour code — coloured bands or dots, etc, read in sequence.

(3) By using an appropriate typographic code, consisting of letters and numerals arranged according to a convention.

Which method is used depends on the type and physical size of the component to a large extent and also according to the manufacturer's preference. The larger components, such as power resistors (particularly wire-wound types), usually have the value, tolerance and wattage rating marked directly on the body. Most common low power resistors, from 0.05 W to 2 W, use the standard resistor colour code. Some manufacturers use a typographic code on their resistors, physical size allowing (usually radial-lead types having wattage ratings between 0.25 W and 10 W). The special resistors (PTC, NTC thermistors and Varistors) also may be marked with a colour code or typographic code to indicate their value and characteristics.

### The Standard Colour Code and Markings

The common axial-lead, composition and film-type resistors are marked with a series of coloured bands, as shown in Figure 1, which are read according to the standard colour code table in Table 1. The standard E24 (5%), E12 (10%) and E6 (20%) series components are marked with either three or four bands. Components below 10 ohms in the E6 series may have only two bands indicating the value. Resistor values in the E48 (2%) and E96 (1%) series are marked with five bands.

The bands are located on the component towards one end. If the resistor is oriented with that end towards the left, the bands are read from left to right as shown. The extreme left (or first) band colour indicates the value of the first digit of the component value; the next, or second, band indicates the

second digit of the value and so on. If the bands are not clearly oriented towards one end of the resistor it is best sorted out by trying to locate the tolerance band first. As the most commonly used resistors these days are either E12 or E24 series, the tolerance band is either silver or gold respectively. If still in doubt — resort to an ohmmeter.

The body colour of modern resistors is also used to indicate the resistor type. Carbon film resistors have a very light tan body, and carbon composition resistors have a medium tan body — somewhat darker than the carbon film body colour. Metal film resistors have a brown body colour — quite distinguishable from composition resistors and metal glazed film resistors have a light blue body colour.

High stability resistors (E48, E96, E192 series) are distinguished by salmon-pink 5th band or body colour. For those who have difficulty remembering the resistor colour code, Table 2 lists the most commonly used values in the E12 series, between 4R7 and 2M2.

### Old-Style Resistors

Prior to the standardisation of the banded system of resistor marking, resistors were colour coded with their value and tolerance by either one of two systems. These were the "Body-End-Dot" and the "Body-End-Band" systems, which are illustrated in Figure 2 (a) and (b) respectively. The body colour represents the first digit of the resistor value, the end colour the second digit, the dot or band colour, the multiplier. The tolerance was indicated

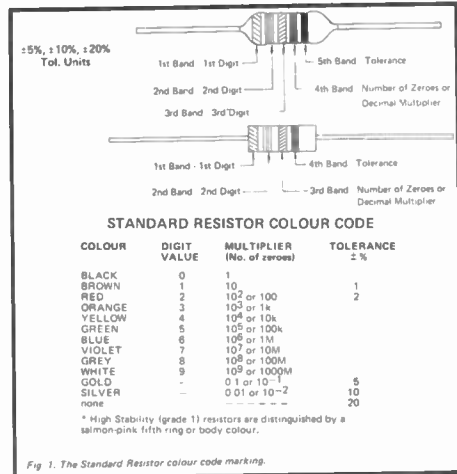


Fig. 1. The Standard Resistor colour code marking.

# RESISTOR CODES

by a coloured spot which partially covered the end of the resistor opposite the 'end' colour or a band much narrower than the 'end' colour. In the body-end-dot system, the dot was generally located midway along the body. In the body-end-band system the band was generally located closer to the 'end' colour. Omission of the tolerance colour indicated a tolerance of  $\pm 20\%$ .

Some other manufacturers indicate the component value and tolerance by a series of dots or small bands which do not completely encircle the resistor body. This system of marking is commonly used on radial-lead and upright mounting styles of resistor from some manufacturers (particularly Erie Co., and some Japanese firms); these are illustrated in Fig. 2c. With the upright mounting style of resistor, the colour code is located towards the upper end of the body. The colour closest to the upper end indicates the first digit of the value, the next colour down, the second digit and so on.

## Typographic Codes and Markings

Resistors may be marked with a combination of letters and figures to indicate the value, and tolerance. Alternatively a combination of direct marking and typographic code may be employed.

The typographic codes used are illustrated in Figure 4. A series of three letters, R, k, M, are used to indicate multipliers of  $\times 1$ ,  $\times 1000$  and  $\times 1000000$ . The significant figures of the value are indicated directly with figures, the position of the multiplier indicating the decimal point. For example:—

|      |                      |
|------|----------------------|
| 4R7  | = 4.7 ohms           |
| 330R | = 330 ohms           |
| 5k6  | = 5.6k (5600 ohms)   |
| 68K  | = 68k (68,000 ohms)  |
| 1M8  | = 1.8M (1.8 megohms) |
| 22M  | = 22M (22 megohms)   |

The tolerance is indicated by one of five letters (see Figure 4) which immediately follow the value code on com-


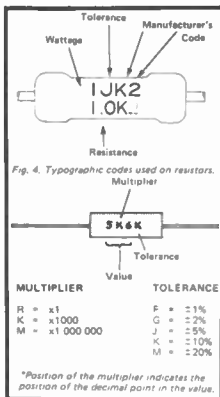


Fig. 2 Other styles of resistor colour code markings

- A 1st Digit
- B 2nd Digit
- C Multiplier
- D Tolerance (use Table 1)

(a) The "Body End Dot" system of resistor marking common on many older resistors.

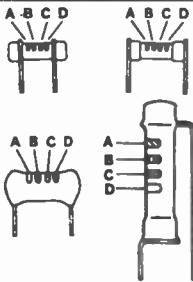(b) The "Body End-Band" system also used on many older resistors



(c) Markings on radial lead and upright mounting resistor styles

## Direct Marking

This style of marking a resistor is commonly used on power resistors (usually from 2 W), wirewound and precision resistors. It usually includes a manufacturer's code indicating the type of resistor perhaps including a date code indicating when the component was manufactured. Figure 3 illustrates a 1 k,  $\pm 5\%$ , 2 W resistor.

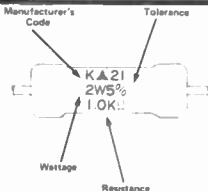


Fig. 3. Resistor with characteristics and value marked directly on the body.

ponents which are marked completely with a typographic code. Some examples of the complete code are as follows:

|       |                       |
|-------|-----------------------|
| 2k2F  | = 2.2k, $\pm 1\%$     |
| 120kG | = 120k, $\pm 2\%$     |
| 2M2J  | = 2.2M, $\pm 5\%$     |
| 150KR | = 150 ohm, $\pm 10\%$ |
| 6R8M  | = 6.8 ohm, $\pm 20\%$ |


## THERMISTOR MARKING CODES

Thermistors may be marked with a colour code or a typographic code, or may have no markings at all! The manner in which they are marked depends largely on their construction and the preference of the manufacturer. NTC thermistors may be marked with either a colour code or typographic code (or not at all) but PTC thermistors are marked with a typographic code only — when they are marked!

Whatever marking is employed, the resistance value at  $25^\circ\text{C}$  ( $R_{25}$ ), and its tolerance at that temperature (if included) are generally the basic characteristics indicated. Other parameters (such as the B value) may be indicated when a typographic code is employed. The manufacturer's data should be consulted for the complete thermistor characteristics.
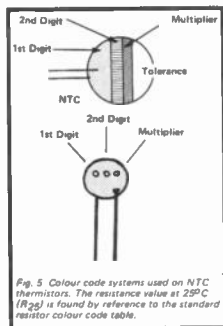
## Colour Coded NTC Thermistors

Two basic methods of colour coding NTC thermistors are used, illustrated in Figure 5. The value of  $R_{25}$  is found by reference to the standard resistor colour



code table. The tolerance is sometimes omitted. The marking method illustrated on the left in Figure 5 distinguishes NTC thermistors from varistors (see Figure 8).

### Typographic Coded NTC Thermistors

The typographic code occasionally employed on NTC thermistors is illustrated in Figure 6. This code is from the American EIA system of component designation. The tolerance range of NTC thermistors extends from  $\pm 5\%$  to  $\pm 40\%$  and two extra letters are added to the standard typographic tolerance code. The temperature constant B, is also indicated with the typographic code and reference to the manufacturer's data for the basic parameters is not necessary. However, if the dissipation, wattage rating, etc. are needed then the manufacturer's data will need to be consulted.

The typographic code consists of a prefix which may be 'ERT' to indicate and NTC thermistor or simply NTC. The value and characteristics may follow immediately or a manufacturer's code may precede it (usually indicating component type). However, the characteristics are always the last group.

#### TOLERANCE CONSTANT(B), °K (at 25°C)

|                |                |
|----------------|----------------|
| J = $\pm 5\%$  | A = up to 1000 |
| K = $\pm 10\%$ | B = 1000-1500  |
| L = $\pm 15\%$ | C = 1501-2000  |
| M = $\pm 25\%$ | E = 2501-3000  |
| R = $\pm 40\%$ | F = 3001-3500  |
|                | G = 3501-4000  |
|                | H = 4001-4500  |
|                | I = 4501-5000  |
|                | J = 5001-5500  |
|                | K = 5501-6000  |
|                | L = over 6001  |

### PTC Thermistor Marking Codes

The typographic code that may be used on PTC thermistors is from the EIA system code, illustrated in Figure 7. The prefix ERP indicates that the component is a PTC thermistor. The suffix is divided into three portions. The first consists of a letter and a numeral indicating the prime characteristic of the component. If it is an A-type PTC thermistor the temperature coefficient is indicated, as shown in the accompanying table. If it is a B type, which changes resistance abruptly at a specified temperature (the 'switching' temperature), then the switching temperature is indicated as shown in the Table.

The tolerance and the resistance at 25°C ( $R_{25}$ ) follow, and are read off in the same way as for NTC thermistors — see Figure 6.

PTC thermistors are often not marked, but their packaging may contain the above typographic code along with a manufacturer's component code.

### Varistor Marking Codes

Both colour and typographic codes are used to mark varistors. As they are voltage dependent devices, the voltage value and its tolerance are given. The colour code that is used on ZNR and SiC varistors is illustrated in Figure 8. The value and tolerance is found from the standard colour code table (see section on Component Marking Codes). The tolerance is the first band on these components when held with the colour bands at the left as illustrated. Just to confuse matters, some manufacturers use the 1st, 2nd and 3rd digit bands to indicate the last three digits of their type number!

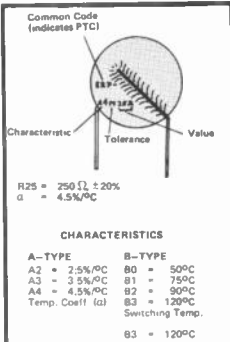
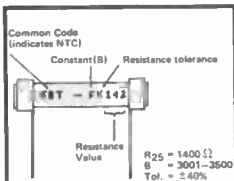


Fig. 7 Typographic code used on PTC thermistors (from EIA system standard). The value and tolerance are read off as for the typographic code used on NTC thermistors.

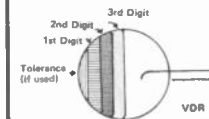


Fig. 8 Colour code used on some varistors. The tolerance refers to the voltage tolerance, and is found from the standard colour code table. The 1st and 2nd digits indicate the two significant figures of the voltage, the third digit indicating the number of following zeros (i.e. the multiplier); the values being read from the standard colour code table. Some manufacturers indicate the last three digits of their type number. Very confusing!

### Ceramic Diode (Varistite) Varistors

These devices have an asymmetric voltage characteristic and it is the value of the forward voltage that is of interest. They are generally made to a specified forward voltage and a colour code is used to indicate the value as illustrated in Figure 9. A single colour spot is used, and it is applied to the cathode side of the device.

# RESISTOR CODES

## ZNR Varistor Typographic Code

The typographic code used on ZNR varistors is usually arranged in one of two ways, as indicated in Figure 10. The disc-shaped varistors are generally marked in the manner illustrated, the ZNR marking directly indicating the type of component. This is followed by a single letter indicating the voltage tolerance followed by the voltage value. A 220 V,  $\pm 15\%$  varistor is illustrated.

The cylindrical body style of varistor is generally marked according to the EIA system standard, as illustrated on the right in Figure 10. This code gives a more complete specification of the component's characteristics. The wattage rating and shape may sometimes be omitted. Reading this sort of code on any component can be confusing — it is best to first identify the component by the prefix and then read the code groups commencing from the right. The voltage value is always indicated last — but watch it again... the manufacturer may attach a suffix for his own purpose! It is usually a single letter and thus the voltage value group is easily recognised.

## Silicon Carbide (SiC) Varistor Marking

These varistors are also generally marked using the EIA system code, in a similar manner to ZNR varistors. The two basic marking styles are illustrated in Figure 11. The common code signifying a SiC varistor, ERV, prefix is in variably marked on both disc and cylindrical shaped components, the disc-shaped varistors generally having an abbreviated code indicating only the voltage value and measuring current. The cylindrical-shaped varistors have the more complete code marked on the component body, as illustrated on the right in Figure 10. The wattage rating, measuring current, voltage value and voltage tolerance are the characteristics indicated. Note that the wattage rating code differs from that for ZNR varistors in that only a single figure is used to indicate components having a wattage rating of 1 W and 2 W respectively.

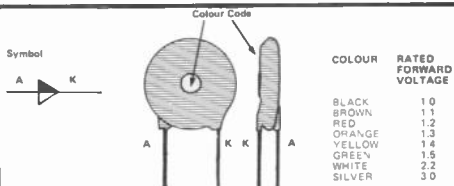


Fig. 9. Colour code used on Ceramic Diode (varistors). These have an asymmetric voltage characteristic and the colour code, indicating the rated forward voltage, is marked on the cathode.

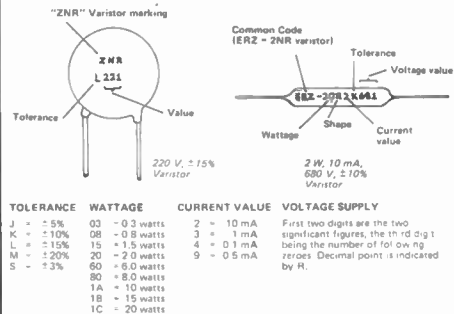


Fig. 10. Typographic code combinations used on common (ZNR) varistors. The more complete form is shown on the right. It may be abbreviated however as indicated on the left. The current value is sometimes included as well, the wattage rating is usually only included where the more complete form of the EIA code is used.

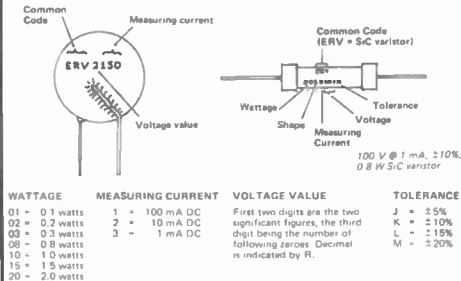


Fig. 11. Typographic code combinations used on Silicon Carbide (SiC) varistors. The complete form of the code is illustrated on the right. It is also used in an abbreviated form, as illustrated on the left, only the voltage value and current being indicated, although the tolerance is sometimes also included.



# ELECTRONICS —it's easy!

## PART 41

### Oscilloscopes; The refinements

MANY MEASUREMENTS in electronics can be handled by the relatively unsophisticated oscilloscopes described in the last part of this series. More capability can be provided at greater cost and this can be valuable if the user understands how to make the most of it. This part describes refinements that will be encountered on more advanced oscilloscopes.

#### IMAGE STORAGE

**Screen persistence.** Repetitive signals such as a sine-wave signal can be made to repeat on the screen overlapping the previous trace produced. If the time base frequency is sufficiently high from thirty or forty hertz upward the screen provides an apparently stationary signal of constant and adequate intensity. This is primarily because the eye cannot detect individual scans (as in motion pictures and television) and secondly because the phosphor at frequencies above a few hundred hertz is re-energized before its light emission due to the previous scan has decayed away.

Phosphors with large time constants are available (such as P2 which takes one second to reduce to 10% of original brightness and P7 which takes three seconds) and oscilloscopes have been manufactured which use these to enable signals of less than one hertz to be studied. This feature, however, largely restricts the use of the instrument to low frequency work because medium and high frequency signals that are not well synchronized will produce separate traces which remain and add up with time to produce an unclear picture. This method of studying slow transient phenomena has not been developed to any great degree because of this and other factors (such as poor resistance to burning) in addition the retained image times are still inadequate for many applications.

#### CAMERAS

Storage requirements fall into two classes — those where the transient is unique and therefore needs to be recorded only long enough to allow the trace to be studied and those where a permanent record is needed.

The oscilloscope fulfills both these

needs. Until the advent of the Polaroid-Land process this involved a time-consuming development process before the operator was certain of having even recorded the trace. Most oscilloscope makers now offer specially built trace-recording cameras that fasten onto the large bracket surrounding the screen.

Such cameras use a Polaroid Land film pack of some kind and often incorporate a 35 mm roll film facility also. A Dumont unit is shown in Fig 1. The user sets the CRO controls until satisfied that the trace will be as needed. This is done using the viewing aperture which reflects the screen image to the observer's eye and it is essential that the camera has the correct focal distance set for the CRO concerned so in general cameras relate to specific units. Some models incorporate adjustable object image (as a few are fixed ratio). With experience it is even possible to capture multiple trace events (by multiple exposure) for comparison purposes.

A considerable amount of film and patience can be consumed trying to record once-only events. Cameras can be quite expensive — several hundred pounds — but they do provide a

permanent record for reports which no other storage system can provide and the price of a camera is not as great as the extra cost of the variable persistence storage units to be discussed later.

#### STORAGE OSCILLOSCOPE

Most of the objections of the above storage methods with the exception of permanent photographic reproduction are overcome by using an advanced form of the basic CRO tube. It is called a variable persistence storage tube and is a development of early 1950's storage tubes which the waveform could only be held at a constant intensity without the feature of gradual fade-out. In fact variable persistence is a feature of tube operating with, not the tube itself.

The construction of a typical storage tube is given in Fig 2. The phosphor viewing screen having 0.1 s persistence time from P31 material and the writing electron gun shown are similar to those used in the simple cathode ray tube. Additional components are the focusing electron gun system, a storage mesh which is coated

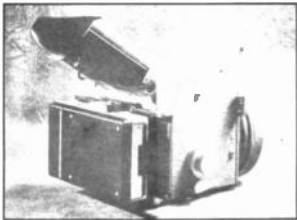


Fig 1. Recording camera using Polaroid Land film pack.



## ELECTRONICS—it's easy!

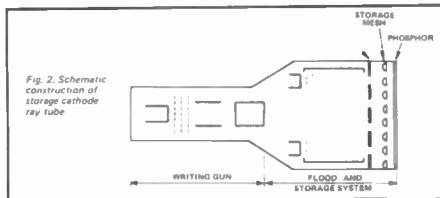


Fig. 2. Schematic construction of storage cathode ray tube

with a non-conducting, highly-resistive material such as magnesium fluoride, and a collector mesh which is held at a positive potential.

To store a trace the writing gun is scanned over the storage surface. Where the beam strikes the storage mesh electrons are knocked loose leaving a positive-charge pattern. The high-resistivity of the surface prevents the charges moving toward a neutral state; the scan is thus stored — and can be held for at least an hour (one maker offers four hours) in a reduced intensity mode.

To make the trace visible, low velocity electrons are sprayed by the flood guns onto the entire mesh surface. These electrons are allowed to pass through to the phosphor in proportion to the amount of positive charge at each aperture of the storage mesh. The positive field pulls many electrons through causing them to pass on to hit the phosphor.

The collector mesh is provided to help accelerate the flood electrons, to repel the positive ions generated by the flood guns; (which would otherwise write the whole screen bright)

and to absorb the emitted secondary emission electrons produced whilst writing is in operation. It is not possible to store the trace in the view mode for as long as in the store mode. One to ten minutes of viewing time are typical for various makers' designs.

Erasure is done by applying a large positive voltage to the storage mesh which charges capacitively to the same value. The mesh voltage is then brought back to a small positive value whereupon the flood guns reduce the voltage to zero. A small sudden negative excursion is finally applied to the mesh making it ready to write. (This procedure is automatically initiated at the single action of a switch.)

Variable persistence is incorporated by changing the time taken to erase the picture. In the Hewlett Packard unit, shown in Fig.3, this is achieved by using a variable-width pulse generator that applies erase voltage pulses to the storage mesh. The positive-ions created by the flood guns limit this mode to a maximum of 10 minutes persistence.

Storage oscilloscopes can be used as conventional units by applying about 30 volts to the storage and collector meshes. Long persistence has many virtues — it enables successive traces resulting from adjustments to a system response to be overlaid together for comparison purposes. It also allows us to see very low-frequency scans, and to plot scans of spectrum analysers. Long persistence also finds use in time-domain reflectometry where the time between send and receive pulse needs measuring.

By stacking sweeps on top of each other a long persistence time can be used to integrate or average a set of traces. Variable-persistence storage oscilloscopes are extremely versatile but the high price restricts their use to large laboratory groups.

### STORAGE USING DIGITAL MEMORY

Figure 4 shows a unit marketed around 1972. The transient recorder unit accepts the analogue signal, converts it to a digital equivalent with respect to time and stores the values in digital registers. Readout can be obtained by using digital to-analogue conversion of the stored increments which are scanned sequentially, the resultant analogue voltage being fed to an oscilloscope or chart recorder. Digital print-out is taken direct from the scanned store locations.

This method is less common than the storage oscilloscope alternative but the ever-reducing cost of digital methods may put this technique into a competitive price region.

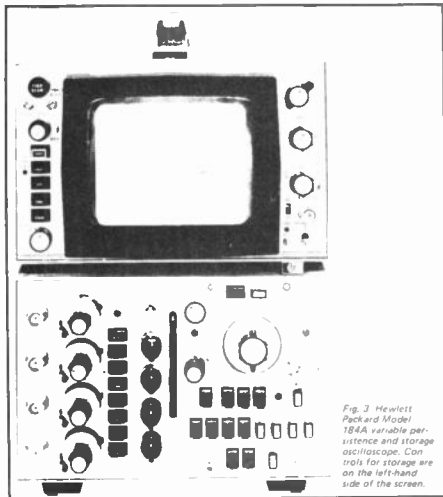


Fig. 3. Hewlett Packard Model 184A variable persistence and storage oscilloscope. Controls for storage are on the left-hand side of the screen.

Another method of capturing difficult to see, once-only transient signals, and very slowly changing waveforms is to record the level of the signal, increment by increment, as the signal occurs, using a digital memory. The concept is simple and the method offers certain advantages. These include ability to speed up or slow down the timescale of the original event, ease of providing a permanent numerical printout and the facility to process the signal before display.

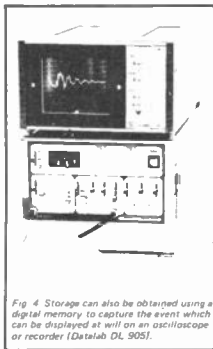


Fig. 4 Storage can also be obtained using a digital memory to capture the event which can be displayed at will on an oscilloscope or recorder (DataLab DL 905).

## SAMPLING OSCILLOSCOPES

How to capture a very fast repetitive event, say near to the GHz region where scan times of 0.1 ns/division are needed, is a problem because the electron beam cannot transfer enough energy into the phosphor to obtain a useable trace brilliance. Further it

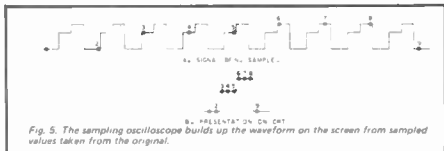


Fig. 5. The sampling oscilloscope builds up the waveform on the screen from sampled values taken from the original.

becomes increasingly difficult to deflect the beam at such speeds. The sampling oscilloscope offers a solution to these problems.

The sampling oscilloscope makes use of the stroboscope concept to look at a waveform, which must therefore

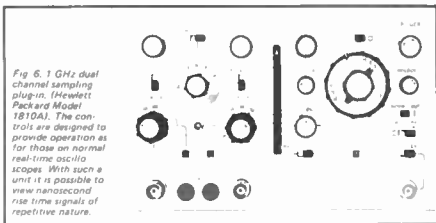


Fig. 6. 1 GHz dual channel sampling plug-in (Hewlett Packard Model 1810A). The controls are designed to provide operation as for those on a normal real-time oscilloscope. With such a unit it is possible to view nanosecond rise time signals of repetitive nature.

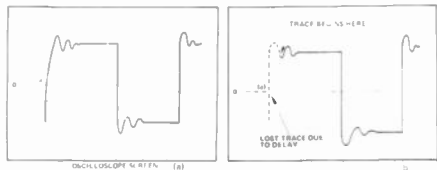


Fig. 7 Inherent trigger delay, if not compensated for, will lose the leading edge of a waveform.

be repetitive (as shown in Fig. 5). The beam is set to illuminate the screen at point 1 in the diagram, waiting there until the next cycle where it moves to point 2 — and so on. The trace therefore gradually works its way through the complete cyclic waveform and because the scan speed is slower than with a conventional sweep system the cathode-ray tube system can operate with a lower bandwidth than the signal. The waveform produced is an average of many so the display is not only sharper but more uniform. (This may be a disadvantage in some applications for the sampling unit is effectively smoothing the unknown true original signal) Sample and hold

## DELAY FACILITIES

Often one needs to study a certain part of a repetitive waveform — the very beginning, for instance. An example is the ringing of a non-dead square wave shown in Fig. 7a. The trace is triggered, to begin the sweep, by a fast-going edge. Due to circuit response times, the trace does not begin to sweep at exactly that time but begins a little later. The result is loss of the leading edge region of the wave as shown in Fig. 7b. The following waveform may provide the information sought but attempts to widen the waveform in the horizontal direction lead to the second front disappearing. The simplest solution to this problem is to incorporate an appropriate fixed delay into the triggering circuits and this is often provided within the circuits. A slightly better method is to provide an adjustable delay control on the trigger panel.

A more difficult problem is capturing a point on the signal train that is remote from the triggering transient. Consider the signal shown in Fig. 8(a), where the problem is to investigate the spike transient on the pedestals of the square wave. Triggering is best achieved by using the edge (a). But this means that scale expansion puts the spike off scale when the horizontal expansion scale is great enough to provide information about the spike structure.

methods were discussed in the previous part discussing D-A and A-D conversion.

In practice a sampling oscilloscope is a normal high quality scope which can accept a sampling plug-in Fig. 6 is the panel of a dual sampling unit.

# ELECTRONICS—it's easy!

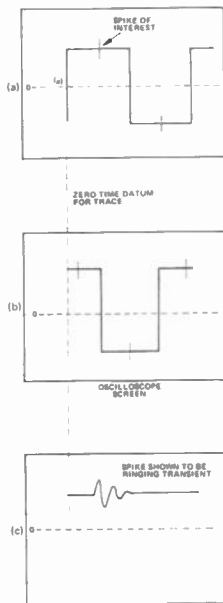


Fig. 8 Use of introduced delay in triggering to enable an event away from trigger transient to be investigated.

- (a) Original spike on pedestal of square wave  
 (b) Delay introduced to bring spike back to time origin  
 (c) Scale expanded to reveal true nature of spike.

Variable delayed sweep is the answer. The trigger circuit is set by the (a) edge but trace scan does not begin until after a period, as in 8(b). Thus the trace captures the spike at the left hand side of the screen and scale expansion will now be possible as in 8(c).

To make this workable in practice the operator must know just where triggering occurs for there may be

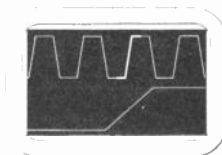


Fig. 9 Trace brightening is used to show which part of the waveform is to be expanded. In this display the expanded portion is also displayed on the second trace of the CRO

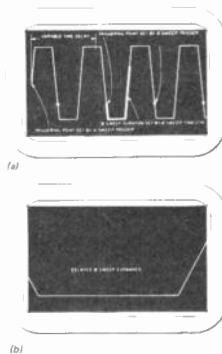


Fig. 10 Use of dual delayed triggering point (a) original (b) expanded

several somewhat similar events along the trace. It is vital to know which one is being viewed. A refinement provided in variable delay circuits is to brighten the original display from the point where triggering will begin. Taking the idea one step further leads to a second delay that effectively decides where the trace stops. Fig. 9 shows the waveform brightened to show the portion that will be expanded and the second trace of the dual-beam unit is used to show the expanded part. Another useful feature is to be able to use a trigger point not on the origin of the first trace set up — as in Fig. 10. Here a marker dot is provided to help the operator.

## PROBES

Passive probes for voltage measurement. In Nos from May 77 the importance of providing the right matching conditions between two electronic systems was stressed. This is also important when connecting an oscilloscope to a circuit for each putput and input has certain resistive and reactive conditions which must be properly combined to get realistic signal transfer.

The oscilloscope can be represented as an ideal termination shunted by a large R and an adequately small C value — or at least they appear this way at first sight. Fig. 11 is the most common approximate equivalent circuit — others used include 50 ohms with negligible reactance in certain applications. Referring to the chart in Fig. 12 it can be seen that with 20pF at 10 MHz the circuit being measured must have the equivalent output resistance of no more than 8 ohms!

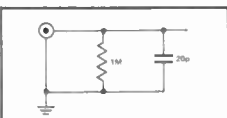


Fig. 11. Most oscilloscopes have this input equivalent circuit. Although the values seem insignificant, at high frequencies they become dominant requiring the use of special probes.

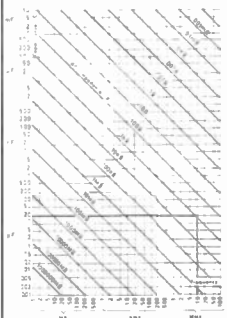


Fig. 12 Chart for obtaining reactance of capacitors at various frequencies of operation.

For high frequencies, those above 100 kHz say, we therefore need a better connection method. To further compound the problem the oscilloscope input leads can easily increase the equivalent C value to 100 pF — leads for 1:1 connection must therefore be carefully designed to ensure known loading conditions which can be allowed for in signal measurement corrections. It is very bad practice to use any piece of coaxial cable and connector for frequencies beyond 100 kHz.

The first improvement is to use a probe which has 10:1 attenuation built in, for these are designed to have a lower effective cable capacitance — see Fig 13 a). Still better is a special correction arrangement that balances the shunt against series capacitance to provide a wider bandwidth — see Fig 13 b). By the use of inductive tuning a further improvement in bandwidth can be obtained — Fig 13 c). Probes with division ratio of 100:1 also are manufactured — these can provide equivalent termination conditions of 5K/0.7 pF, 10M/1.8 pF, 1M/1 pF. The reason for different pair combinations arises from the need to alter the trade offs between rise time and signal loss in high frequency and very fast transient measurements.

There is no easy answer to the question of which attenuator probe to use. These guides are the start. For amplitude measurements select a minimum-impedance source point to measure from. The best probe to use here is one with the highest impedance at the frequency of interest. Capacitance is less important here than resistance for it alters edge shapes, not amplitude.

For fast risetime measurements again select a low impedance source point and use a probe with lowest effective capacitance — signal attenuation is less important than transient edge shape changes.

## ACTIVE PROBES FOR VOLTAGE MEASUREMENT

The above probes make use of passive matching arrangements. But for the extremes of frequency and/or risetime measurements the values of components required in passive probes become impractical. However active amplifiers interposed between the circuit and the oscilloscope can be used to improve performance by increasing input resistance and lowering capacitance (short loads). FET probes are marketed to meet this.

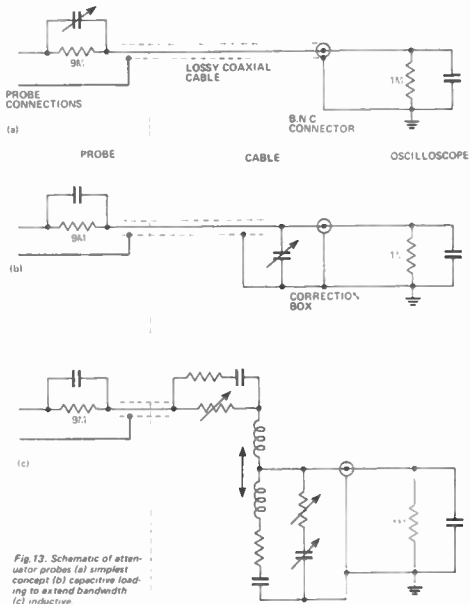


Fig. 13. Schematic of attenuator probes (a) simplest concept (b) capacitive loading to extend bandwidth (c) inductive.

## OTHER PROBES

Voltage measurements are by far the most frequent measurements made but in some instances it may not be possible to determine voltages, and current measurement is used instead. An example is the current flowing in a direct-coupled Darlington pair configuration where no significant resistance exists over which a voltage can be

developed. DC current probes (see Fig 14) clip over the wire in question coupling the dc magnetic field created by the current flowing in the wire into a Hall effect transducer which generates a voltage equivalent to the current flowing. These will also measure ac currents. The maker specifies the conversion constant — typically 1 mV/mA. AC only, current

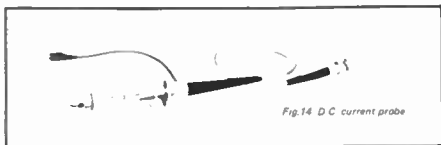


Fig. 14 DC current probe

## ELECTRONICS—it's easy!

Probes are also made using a current transformer principle.


Probes for use in digital circuits are also available. These may incorporate a logic gate that combines the outputs from up to 8 circuit points as shown in Fig. 15. Power for the gate is obtained from the circuit under test.

### SPECIAL PLUG-INS

The oscilloscope, due to its extensive flexibility can form a major part of many test systems thereby reducing the overall price of advanced measurement systems where a suitable CRO already is available. Special plug-ins are offered to suit certain main

cost is concerned) is the CAT itself for frames) that will convert an oscilloscope into a spectrum analyzer or into a semiconductor characteristic-curve tracer. Another plug-in is offered that converts the CRO into a four trace unit.

A basic need in manual measurement is the provision of output form that best suits the operator. In many tasks a visual output in the form of a picture or graph is better than having to view many traces of a time sequence taken over the whole system. Already we have logic analysers which it is just about the last remnant of thermionic device technology remain-

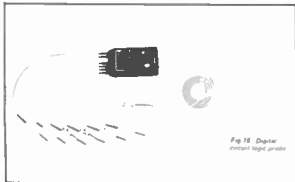

**Fig. 18 Digital  
control block diagram**

display space plans information on the CRO screen multi-meter CRO units that enter digital values on the screen and units that provide assist information on screen graphs. With the reducing cost of advanced processing it will not be long before the micro-processor and memory (already in use in very sophisticated units) are introduced into quite moderately priced oscilloscopes for converting the information taken from the circuit into better forms of display. Display monitors are already available with many display forms. The next stage must be the marrying of the basic CRO unit to such capability via a wider range of sophisticated plug-ins. The colour oscilloscope will also soon be with us extending the information rate at which the operator can be informed about a system via a CRO.

The only weak link in present systems (as far as robustness is and

ing in general use. This too will soon be replaced by a solid state equivalent. Perhaps this will take the form of a matrix of three colour LEDs in a flat display making maximum use of the low cost production advantages of LSI techniques.

*Continued next month*

### FURTHER READING

Due to the versatility of the oscilloscope most books on electronic instrumentation include basic descriptions of how oscilloscopes work and how to perform basic measurements with them. Many books are devoted entirely to the oscilloscope.

General considerations are discussed in Test and measuring instruments 1974 Catalogue (Philips) Tektronix, Hewlett Packard, Dumont and Marconi outlets also provide basic articles on the selection and use of oscilloscopes. ●



### EDITORS

Suitable for all sizes and to large, medium and small plants specify which! Yellow with black lettering. Send £2.00 (which includes VAT and postage) to:

## ETI T-SHIRTS

25-27 Oxford Street  
London W1A 1BP



### 6 FUNCTION LCD AND

## STOPWATCH

**£34.95**

www.elsevier.com/locate/jmb

At last a really thin but functional LCD at 11.4mm (slender and elegant) glass that is scratch resistant to 150H pencil, proof and dustproof.

AND IT'S A STOPWATCH  
AS WELL

**THE NOW FAMOUS  
CASIO C01**



© 2006 The Authors  
Journal compilation © 2006 Blackwell Publishing Ltd

**Executive Pocket Dictionary**  
Size 9 1/2" x 6 1/2" 50 x 250-00

Figure 1. *Staphylococcus aureus* strains used in the study.

KRAMER &amp; CO

© 2000 Blackwell Publishers Ltd. *Journal of Internal Medicine* 247: 395–401

Received: 2014-01-20; Accepted: 2014-02-10



# ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

## Standardisation et al.

I WAS READING IN an American magazine how programs written for SVT6800 don't work on an Alta 6800 8080 programs not running on a different mainframe and therefore non-standardisation. What that means if you're not quite a bit MPU-jargonist is that a program written in machine code for one manufacturer's MPU will not work in another manufacturer's version of the same MPU kit. Existing programs may involve careful checking of the code to ensure that any subroutines required are available and in the correct locations. As different manufacturers of microcomputer systems use different decoding techniques for device addresses they have a different MONITOR or DEBUG program.

The monitor program is a program which is operated upon after Power up or Reset has been signalled to the MPU. The Monitor sets pass variables or pointer registers and then branches to an I/O routine for a command from the operator. This command is a programming code which instructs the Monitor to perform a set of tasks which will result in the required operation. Examples of such commands are Print Memory, Alter Memory, Execute Program, Store and Read.

The monitor program must reside in a fixed location memory (HICORE for 6800 8080 LOCORE for SCMP etc) and is usually sold in the form of PROM. On some machines the basic monitor program is simply a BOOTSTRAP. This is a program entered via data and address switches. The program is usually on a 40 or so bytes and it causes data to be read into RAM and then that program data to be executed. The program data read is in the usual form of monitor described earlier.

Because the Monitor program executes in a fixed location its I/O routines these sub-routines must also be in a fixed location in memory and thus they are usually stored in the same PROM. These subroutines are useful and convenient because they are probably the first MPU programs you will get to know and convenient because any programs that you write can use the same sub-routines for I/O. Here lies the biggest problem you

are likely to come across in MPU's. Any programs you write may not work on another MPU system based on the same chip. Conversely any programs you require from a library must have been written with your system in mind. Hardware standardisation is much simpler; you either go for one of the big systems with 100 or more parallel connectors or a minibus with just the bare essentials paralleled. Standardisation of hardware is being discussed variously at present, whether it be bus structure or pin and signal compatibility between MPUs. Interface and communication standardisation is supported by 20mA loops, CUTS, ASCII, etc.

Software standardisation seems to be based solely on the idea of using the 50 or so characters on a keyboard in whatever sequence seems right at the time. I have been guilty of doing this myself but I have now seen the light and feel that I should pass on the message to all concerned.

Instead of basing everything on a fixed location monitor use a fixed location STACK or Working Storage RAM. You still need your basic monitor or a switch entry system at reset but once set up the system no longer needs that program. Any parameters such as data or addresses to be passed to from subroutines or I/O devices are stored in this WS RAM. The Monitor stores for instance the address of the I/O routines in the PROM at fixed locations in the WS RAM. In order to branch to a routine it must first load the data from the WS RAM into a branching register and then jump to that address.

Any programs you write can use the same I/O routines by simply following the address load and branch sequence. Any subroutines you write use the same technique of somehow storing their location at a fixed location in WS RAM. If the subroutine happens to be an I/O routine then its address could replace the address of the PROM I/O routine in WS RAM. Any reference by a program to the PROM I/O routine will now use your routine instead of something gone wrong in your routine hit Reset and you are back with the standard I/O.

Perhaps you are an old hand at MPU's or computers and you think in terms of a programming language such as BASIC, FORTRAN, COBOL or PL. At least one English language compiler is available for most MPUs and some have several optional compilers. Some compilers end up with a machine code program while others work as interpreters of the stored program text. Back the bad old days of IBM 360s 1400s System 4s etc, manufactured by large international companies 1400 COBOL didn't work on 360s. IBM FORTRAN had to be modified for ICL or whoever. The mainframe boys made a bad start in software standardisation so please let's have some sense with MPU software.

## Time on my hands

After my appeal for information on DCF77 I have received several letters with copies of articles on DCF77, some code receivers, all in German. My thanks to all of those who sent in this data and to those who indirectly assumed my knowledge of German and offered translations.

One point about DCF77 which I feel that should point out to any prospective user is that the annual licence fee of 2 000 DM but prescribes that this is only payable for reception in Germany. ■

# tech-tips

## TTL KEYS


This device can be used to send perfectly spaced Morse at very high speeds - up to twice as fast as with an ordinary Morse key. It uses six integrated circuits, and also requires two special switches, SW1 and SW2, which are described later.

To describe the operation of the circuit fully would take over a page of ETI, and so a simplified explanation is given here. IC1 is a 555 timer connected as an astable multivibrator, whose frequency is varied by RV1. The output is fed to IC2a, a D flip-flop, which divides the input frequency by 2, producing a square-wave with a 1:1 mark-space ratio (dots).

If SW1 and SW2 are both open, the D inputs of IC2b and IC6a are both at logic 0, so that the dots from IC2a are inverted by IC3a, but blocked by IC5a. IC5b output is a 0, and so the audio oscillator made up of Q1 and Q2 and the associated components is disabled and no tone is fed to the speaker.

If SW2 is closed, IC6a's D input becomes logic 1. However IC6a's output can only change state on the rising edge of a clock pulse (i.e. the beginning of a dot). Hence if a dot has already started when SW2 is closed, it will not get through to the speaker, but the next dot will, because it will make IC6a's Q output to go to 1. Hence the dots now get through to the oscillator and successively enable and disable it, causing dots to be heard coming from the speaker. When SW2 is opened, if a dot is in progress it will continue until it has finished, and then at the beginning of the next dot, IC5a output will go low and no more dots will be heard. There is a short delay between the beginning of the dot and the Q output going low, which does cause a short 'blip' at IC5b output, but the blip is too fast to be heard.


If SW2 is closed, but SW1 open, IC4c output goes to 1 and IC2b's Q output is effectively shorted to its D input. This causes IC2b to divide the string of dots from IC2a by two. The outputs of IC2a and IC2b are combined by IC3a to produce a waveform with a 3:1 mark-space ratio (dashes). These are passed on to the audio oscillator just as before. The dashes, like the dots, are self-completing. Notice that IC4c output determines whether dots or dashes are produced.

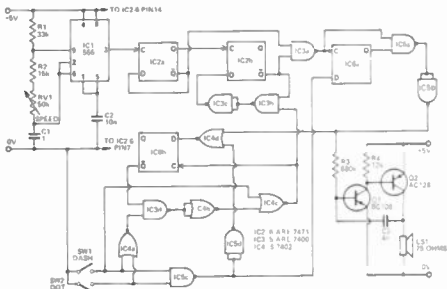

While SW1 or SW2 is closed, IC6b's D input is fed from IC4c output and clock pulses come from IC5b. If SW1 and SW2 are both operated together, IC4a allows the output of IC6b to pass to IC4c, and IC4d inverts IC4c output again, so that IC6b's Q output is shorted to its D input. Thus IC6b changes state every time a dot or dash begins at the output, and causes alternate dots and dashes to be produced. This is useful when sending a letter like C (dash-dot-dash-dot), as the switches SW1 and SW2 each need to be closed and opened just once.

It was found after the unit had been built, that it was difficult to send a letter like A (dot-dash) at high speed because SW1 had to be closed a fraction of a second after SW2, which was difficult to achieve at the first attempt. Hence IC5d and IC4d were added. When both switches are released, IC6b input becomes 0. A clock pulse is then applied to IC6b by the 'blip' described earlier. This makes the output go high, and if now SW1 and SW2 are closed simultaneously, the first thing to be heard in the speaker will be a dot.

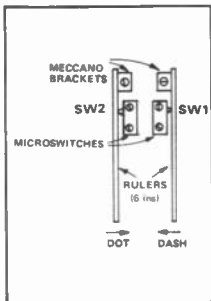SW1 and SW2 are push-button microswitches, and these are operated by means of a lever arrangement as shown in the diagram. Plastic rulers were used on the unit built because they are flexible.



The component values shown around IC1 give a speed range of 11-30 words per minute. The upper limit can be raised by decreasing R2. I have so far reached a speed of 20 wpm on the unit, after only a week or so of using it. As it stands it is a Morse practise unit, but if IC5b output is taken to a transistor driving a relay, the relay contacts could be used in place of an ordinary Morse key in a C.W. transmitter.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI, TCM-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.





# SINTEL BARGAINS OFFER OPEN UNTIL 31st JULY, 1977

**SINTEL SPECIAL OFFER — CONDITIONS**  
OPEN UNTIL 31st JULY 1977 INCLUSIVE — WHILE SPECIAL OFFER STOCKS LAST

SINTEL SPECIAL OFFER

ACK

£2.80  
**£24.80**

## BARGAIN KIT PRICES

**£3**

OFF ACK AND CCK

CCK

**£39.00**

**£2**

OFF THESE KITS

## SIX JUMBO DISPLAYS

FOR ONLY **£6**



FRD500x6  
£6.00

## TAKE 10% OFF ALL CMOS

|      |      |      |
|------|------|------|
| 7400 | 1.00 | 0.90 |
| 7401 | 1.00 | 0.90 |
| 7402 | 1.00 | 0.90 |
| 7499 | 1.00 | 0.90 |

TAKE 10% OFF  
THREE CMOS  
PACKS

## SPECIAL OFFER

FROM £6.70

RCA CMOS AND  
LINEAR IC  
DATABASE

Only **£4.95**

## SINTEL chooses the ZILOG Z80

COMING IN A FEW MONTHS  
A COMPUTER USING THE Z80

We think it's well-worth waiting for

## SPECIAL OFFER PRICES FOR SINTEL INDUSTRIAL MODULE KITS

FOR THE FOLLOWING KITS SEE LIST OF SPECIAL OFFER PRICES

| Kit No. | Kit Name                           | Kit Price | Special Offer Price |
|---------|------------------------------------|-----------|---------------------|
| 1       | 16K 8080/8085                      | £45.00    | £40.50              |
| 2       | 16K 8080/8085 + 8255               | £65.00    | £58.50              |
| 3       | 16K 8080/8085 + 8255 + 8279        | £85.00    | £76.50              |
| 4       | 16K 8080/8085 + 8255 + 8279 + 8280 | £105.00   | £94.50              |

## TAKE 10% OFF PRICES OF ALL

SINTEL INDUSTRIAL MODULE KITS

| Kit No. | Kit Name                           | Kit Price | Special Offer Price |
|---------|------------------------------------|-----------|---------------------|
| 1       | 16K 8080/8085                      | £45.00    | £40.50              |
| 2       | 16K 8080/8085 + 8255               | £65.00    | £58.50              |
| 3       | 16K 8080/8085 + 8255 + 8279        | £85.00    | £76.50              |
| 4       | 16K 8080/8085 + 8255 + 8279 + 8280 | £105.00   | £94.50              |

## ON SPECIAL OFFER FROM SINTEL

Z80/ 8080/8085  
700-443000

£29.50

**£28.00**

Simple Z80 Replacement

NOTE: SINTEL has limited the Z80/8085/8086 to the 700-443000 price. Other Z80/8085/8086 kits are available at their normal prices. Please refer to the Z80/8085/8086 price list for details.

© 1977 SINTEL LTD



SINTEL LTD OFFER  
PO BOX 754, OXFORD  
Tel 0185 49751

## LOW COST SOLDERCON IC SOCKETS

These sockets are a Low Cost Socket for 16K 8080/8085/8086. They are made of high quality dielectric material and are available in two sizes.

1000  
for £4.00  
**£3.00**

SINTEL  
4.51  
SINTEL  
GIVE

COUPON

VAL 8  
SINTEL  
754  
JULY  
1977  
END

# tech-tips


## SIMPLE STEREO SWITCH

A device to switch the audio from a stereo tuner only when a stereo signal is being received.

Two CMOS NAND gates and two transistors are employed. One of the inputs from each gate is connected together and to the indicator output of the decoder IC.

The other gate inputs are connected to the emitter's of Q1 and Q2 respectively, by means of the feedback resistors R2 and R4. On reception of a stereo signal the indicator output of the decoder goes high and the feedback resistors bias the gates into the linear region passing the signal. On reception of a mono signal or interstation noise no signals pass through the gates the circuit providing a mute function.

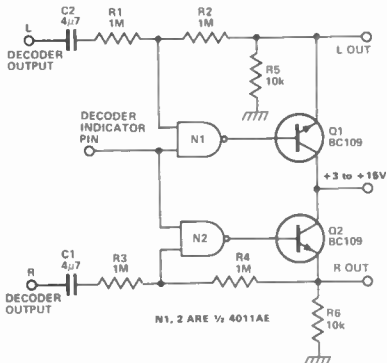N.B. Some CMOS will not function in the linear mode. CMOS that will not work include R.S., Doran, Signetics, CMOS that will work include N.S., R.C.A., Motorola. All unused inputs should be connected to ground.




## VOLTAGE AND FREQUENCY CALIBRATOR

This circuit provides simultaneous voltage and frequency calibrations by generation of a precision squarewave.

The 555 timer IC is used in a slightly unusual configuration, having the advantage that an exact 50:50 mark/space ratio may be attained by trimming R1. The frequency of oscillation may be set between 10 kHz and 1 kHz by switching timing capacitors C1-4. C5 decouples the internal reference potential-divider of the 555 from supply-transients.

The squarewave output from pin 3 of the IC, while stable in frequency, is not stable in peak-to-peak voltage as this depends on the supply voltage. This is used to switch on and off a temperature-compensated constant-current source Q1. R2 ensures that the current-source turns off completely when pin 3 goes high. The current-source output, trimmed by R3 to be exactly 1 mA, drives a resistor ladder network so that a series of precise squarewave voltages are generated. The advantage of current drive rather

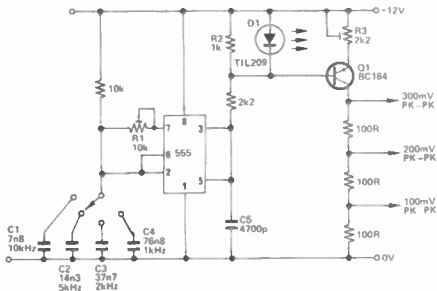

than voltage drive for this sort of network is that calibration is much easier. A simple ladder network is shown by way of example and more complex ones may simply be constructed to give a wider variety of output voltages.

The non-standard component values used were obtained by paralleling standard values. For the timing capacitors several in parallel had to be used, and only the resultant value is shown on the diagram.

[illegible]

## JUNE ISSUE INCLUDES

# RADIO & ELECTRONICS

## CONSTRUCTOR

## IMPORTANT PROJECT...

## SIMPLE QUADRAPHONIC AMPLIFIER — Part 1

A 3-part article, this quadraphonic amplifier incorporates comprehensive tone and balance controls and takes advantage of the Motorola SQ decoder, i.e. type MC1312.



**SPECIAL SHORT SERIES . . .**

## BLOB-A-JOB

### No. 1 Voltage Stabilizer

This voltage stabilizer can be built to provide outputs at 3, 5, 6 or 9 volts, according to the zener diode chosen.

**EASY CONSTRUCTION** using Blob Board

**ON SALE NOW**

**PRICE 40p**


# tech-tips

## BEAM SPLITTER FOR OSCILLOSCOPE

The basis of the beam splitter is a 555 timer connected as an astable multi-vibrator, components R1, R2 and C1 being selected to give approximately equal high/low pulses of about 3 kHz.

Resistor R3 couples the output of the oscillator to the npn/pnp pair Q1 and Q2. When the output of the oscillator is low, resistors R10 and R11 allow Q2 to be on so that any signal applied to input 2 is effectively short-circuited via resistor R8 to the common line of the power supply. At the same time, the npn transistor Q1 is off, so that any signal at input 1, plus a positive voltage provided by RV1a and R4, appears at the output via R7.

Conversely, when the output of the oscillator is high, Q1 is biased on whilst Q2 is off. A signal at input 2 plus a negative voltage via RV1b and R5 appears at the output via R9. Thus signals at the two inputs are alternately displayed on the oscilloscope with a clear separation between them. The separation is controlled by the tandem potentiometer RV1a/b which also varies the amplitude of the traces.

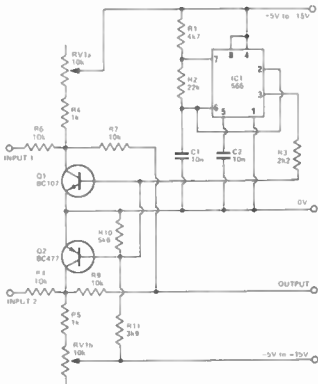

## A SIMPLE V.C.D.


This circuit generates sawtooth and triangle waveforms at a frequency set by an external control voltage.

Current source Q1 draws a current I from timing capacitor C. Simultaneously current source Q2 draws the same current from current mirror Q3, Q4; this is set up (by R1 and R2) to deliver (from the collector of Q4) twice the current leaving Q2.

Hence C receives a current 2I from the top rail, at the same time delivering I to the bottom rail, the net effect being that the capacitor is charged by a constant current I, its voltage rising linearly until the 555's upper trigger point (at  $2/3V_{cc}$ ) is reached.

The output (pin 3) then goes low, as does the open-collector discharge output at pin 7. The latter shunts the output of the current mirror to earth, D1 becoming reverse-biased and isolating C.

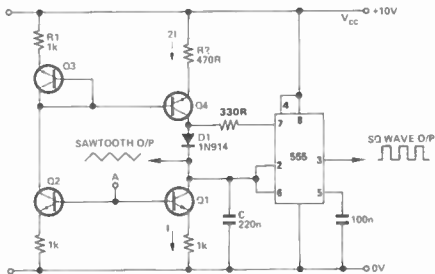Now only current source Q1 is connected to the timing capacitor which is now linearly discharged by current I. In this way C is alternately charged and discharged. When the voltage on C falls to the 555's lower trigger point at  $1/3V_{cc}$ , the output and discharge pins go high, and the



cycle recommences; the repetition frequency is determined by the magnitude of I, which is set by the voltage applied at the input point A.

With the component values shown, the frequency range is from approx.

2.5 kHz to less than 10 Hz, as the control voltage varies from +10 V to zero; the frequency is directly proportional to the control voltage. Other ranges may be obtained by altering the value of C.

# 15 — 240 Watts!

## HY5

Preamplifier

FEATURES  
APPLICATIONS  
SPECIFICATIONS

Power 15 W + 40 W AT P & P Mode

## HY30

15 Watts into 8 $\Omega$

FEATURES  
APPLICATIONS  
SPECIFICATIONS

Power 15 W + 40 W AT P & P Mode

## HY50

25 Watts into 8 $\Omega$

FEATURES  
APPLICATIONS  
SPECIFICATIONS

Power 25 W + 50 W AT P & P Mode

## HY120

60 Watts into 8 $\Omega$

FEATURES  
APPLICATIONS  
SPECIFICATIONS

Power 60 W + 120 W AT P & P Mode

## HY200

120 Watts into 8 $\Omega$

FEATURES  
APPLICATIONS  
SPECIFICATIONS

Power 120 W + 240 W AT P & P Mode

## HY400

240 Watts into 4 $\Omega$

FEATURES  
APPLICATIONS  
SPECIFICATIONS

Power 240 W + 480 W AT P & P Mode

## POWER SUPPLIES

ILP Electronics Ltd  
Crossland House  
Neckington, Canterbury  
Kent CT4 7AD  
Tel (0227) 63218

Power Supplies  
Full Range of Power Supplies  
100W to 480W  
Power 240W to 480W  
Power 240W to 480W  
Power 240W to 480W  
Power 240W to 480W



## COMPONENTS &amp; KITS

## Catronics

PARTS SYSTEM  
FOR VERO CABINET

we stock the full range of 19" cord frame parts

|                    |          |        |
|--------------------|----------|--------|
| Card Frame: Cased  | 71-3841L | £20.91 |
| Grid Plates (pair) | 71-3842A | 50p    |
| 8" Module          | 71-3843A | £4.64  |
| 4" Module          | 71-3844C | £3.08  |
| Veroboard          | 06-5579A | £1.27  |
| 2" Square Panel    | 71-3845B | £1.03  |
| 1" Square Panel    | 71-3846A | 90p    |
| Veroboard          | 06-10349 | £3.21  |
| Power Board        | 06-1040J | 81p    |
| O.P.P. Board       | 58-1041J | £3.28  |
| 21-way plug        | 17-4267H | 80p    |
| 31-way socket      | 17-4268C | £1.87  |

**KEYBOARDS** - We hope to have available a keyboard in module form for home construction - a PCB to hold up to 60 switches and wipers - in groups of 6 allowing 36, 48, 54 and 60 station keyboards to be assembled. Please send S.A.E. for details.

LOW  
COST  
V.D.U.

in standard  
lead, DEPT OC1  
10000

All items available for this project.  
Complete kit at special price £60.00 + 75p p.h.  
Components also available separately - PC6 set, £8.85  
2112.2, £6.50 2512, £9.25, 565, 47p



2 METER  
POWER  
AMP  
as described  
SEPTEMBER  
1980E  
Page 149

2 METER  
POWER AMPLIFIER

Complete kit to build this 60 watt power amplifier - £18.25

Send S.A.E. for full price list in 20p plus air po 74p S.A.E. for price copy of our Data Catalogue. All prices include VAT at current rates. Please note our maximum order value is £1000.00. All orders accepted where indicated is 20p. 1 x POST ORDER is welcomed. - Write for Price & Parts List.

COMMUNICATIONS HOUSE,

DEPT. 757 20 WALLINGTON SQUARE,

WALLINGTON, SURREY, SM6 8RG

Tel. 01-469 8700 (3 a.m. to 9 p.m., 7 p.m. Sat.)

Detectknow-  
ledgey

Detectknowledgey? No, we haven't forgotten how to spell a number of you thought we had during our 'Technoknowledgey' ad service last year. It is simply an expression of Ambit's specialist logic for Summer 1977 Metal Detectors. In other words, we want you to know that we know about them and just telling them last time they work and why. It is surprising how few people can explain the theory and application of best principles to metal locators. Things like why a bunch of keys can sometimes fail to register whilst a Zip pack indicates at 6' 10" or why a lump of iron reacts at 1' 1" were so far out. See our new publication on the subject, a concise reference work that sets out to explain from first principles the various phenomena you will encounter. £1.00 inc PP.

## PW SEEKIT COMPLETE KIT

Spreading of technology, that is, the application of scientific discovery to practical situations and every day equipment, the PW Seekit can claim to have used a few scientific features only achievable with detectors that we have been largely unsuccessful in producing, so it is not surprising we are able to offer complete kits, and all parts for this exciting project. The complete Seekit kit costs £20.00 including PP AND VAT. This contains all electronic and plastic components (untested) for things like gas, fuel etc. which you are sure that likely to have passed the tests for SAE and being you are sure that likely to have passed the tests for SAE. Please note our own early detector service testing on complete kits purchased from us.

## BIONIC FERRET 4000

Not an electronically rugged or robust outfit but AMBIT's own VCO metal locator system. The BIONIC FERRET is a spring of approx. £25.00 on the human system. Please complete the kit and include parts. The complete kit costs £20.00 including PP AND VAT at 8. A few days of metal Detectknowledgey with all kits.

Wireless COMPLETE TUNER KITS  
MODULES COMPONENTS etc.

|           |      |         |      |           |       |       |       |
|-----------|------|---------|------|-----------|-------|-------|-------|
| CA1300L   | 1.80 | 7000A/C | 1.50 | 40072     | 0.57  | 7752  | 20.50 |
| MC1310P   | 2.20 | 70013   | 1.20 | 9000000   | 0.70  | 7752  | 20.50 |
| YBA120    | 0.75 | 8001412 | 1.20 | 80108     | 0.20  | 7020  | 6.50  |
| uA701     | 1.80 | 70151   | 1.50 | Veroboard | 70.00 | 50.00 |       |
| HA1137P   | 2.50 | 701620  | 1.20 | BA121     | 0.20  | 90270 | 12.90 |
| CA3080A/C | 3.75 | 70024   | 1.20 | BA121     | 0.20  | 90270 | 6.95  |
| HA1700    | 4.30 | uA772C  | 0.80 | 80104     | 0.65  | 7701  | 26.50 |
| uA770     | 1.40 | 700500  | 0.80 | 80108     | 0.32  | 7710  | 11.25 |
| CA3123C   | 1.40 | 6020C   | 4.50 | 80108     | 1.50  | 80108 | 1.50  |
| HA1167    | 1.40 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| TS4001    | 1.01 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| LM3004    | 1.00 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| LM301N    | 1.01 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| LM3000    | 0.75 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| TS4002    | 2.00 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| TS4003    | 1.00 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |
| TC4000    | 1.00 | 80108   | 0.70 | 80108     | 1.50  | 80108 | 1.50  |

VAT extra 12.5% + 8% PP 27p per order unless otherwise stated. Full catalogue (much more stuff) sent 75p 80p SAE for free AS or at 375 High Street (Overhead) Essex CM14 4AH 0273 716679

ambit  
international











# MAPLIN



## ELECTRONIC ORGAN

For the home or office, the electronic organ is a versatile and popular instrument. It is available in a wide range of styles and prices, from a simple electronic organ to a more sophisticated electronic organ with a built-in amplifier and speaker.



## GRAPHIC EQUALISER



The graphic equaliser is a device which allows you to adjust the frequency response of your audio system. It is available in a wide range of styles and prices, from a simple graphic equaliser to a more sophisticated graphic equaliser with a built-in amplifier and speaker.



## TOOLS



The tools section of our catalogue contains a wide range of tools, from a simple screwdriver to a more sophisticated power tool. It is available in a wide range of styles and prices, from a simple tool to a more sophisticated tool with a built-in amplifier and speaker.

## PEDAL UNIT



The pedal unit is a device which allows you to control the volume of your audio system. It is available in a wide range of styles and prices, from a simple pedal unit to a more sophisticated pedal unit with a built-in amplifier and speaker.

## T.V. GAME



The T.V. game is a device which allows you to play a game on your television set. It is available in a wide range of styles and prices, from a simple T.V. game to a more sophisticated T.V. game with a built-in amplifier and speaker.



## IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8 1/2") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller! **DON'T MISS OUT! SEND 60p NOW!**

Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers (they save you pounds!) - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

## MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715115

Shop 284, London Road, Westcliff-on-Sea, Essex

London Office: Telephone: 01-581 4111

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE  
PRICE 60p

Please fill in this coupon and send it to the address below. We will send you a copy of our catalogue free of charge. If you prefer to receive our newsletter, please tick the appropriate box and send it to the address below. Your name and address will be kept confidential.

Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
City: \_\_\_\_\_  
Postcode: \_\_\_\_\_

