

electronics today

DECEMBER 1979

INTERNATIONAL

50p




PROJECTS

VFET Applications

Chess Machines

Coral MC 81

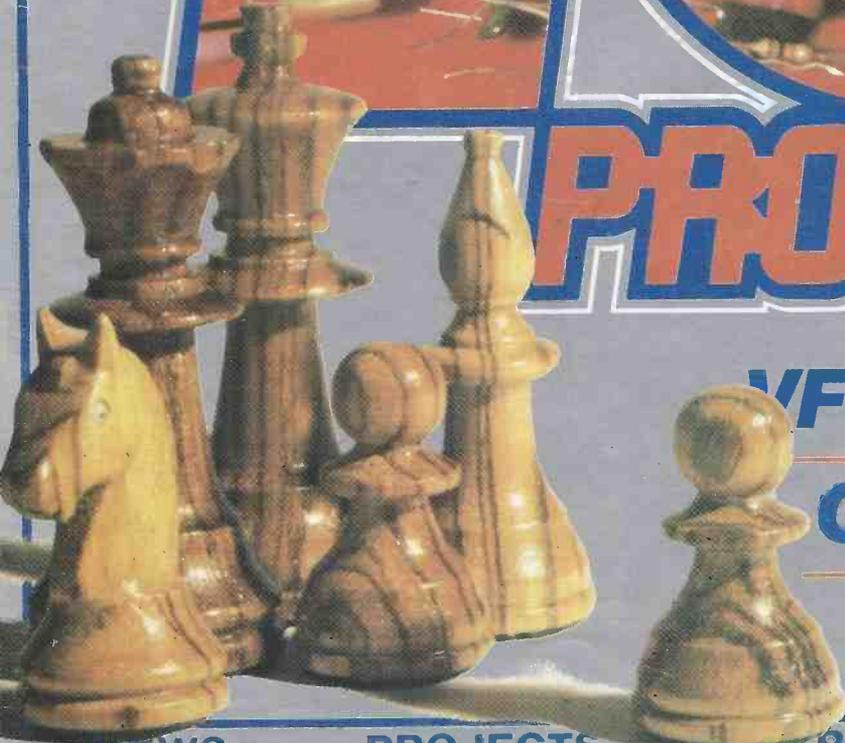


TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an effective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features. The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal trim!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for between £500 and £700!

**COMPLETE KIT
ONLY
£172.00 + VAT!**

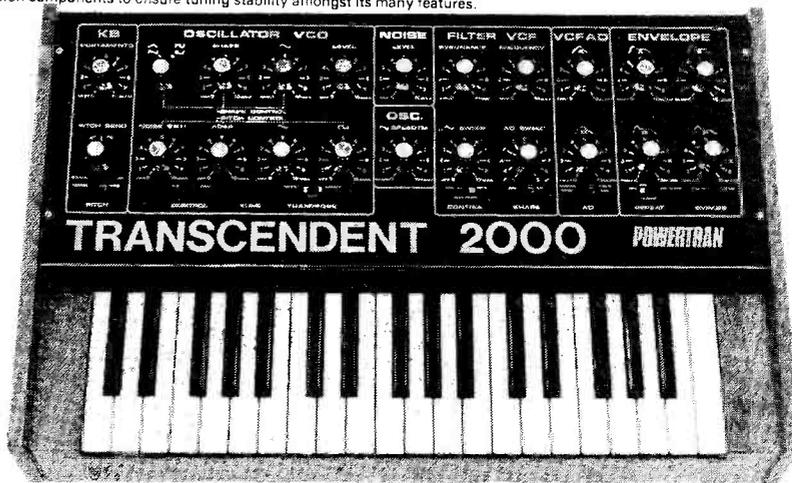Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

AS FEATURED IN AUGUST-NOVEMBER '79
Another superb design by synthesizer expert Tim Orr!

NEW! TRANSCENDENT DPX

DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

COMPLETE KIT ONLY £365.00 + VAT!

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either string or mid effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without a pitch or key change, computer composing etc., etc.) and an interface socket (25 way D type) is provided for this purpose.

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide, nuts, bolts, etc. even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1,200!

POWERTRAN

**ORDERING INFORMATION
AND MORE KITS ON PAGE 8**

All kits also available as separate packs (e.g. P.C.B., component sets, hardware sets, etc.). Prices in FREE CATALOGUE.



electronics today

DECEMBER 1979 VOL 8 NO 12 INTERNATIONAL


FEATURES

DIGEST	9	Find it first here
VFET APPLICATIONS	25	VMOS — how good and why
AUDIOPHILE	39	Music to your ears from Coral
RAVEN ON	52	News views and dictionary
CHESS MACHINES	61	Find your ideal mate
MICROFILE	71	Home computers awaken
DESIGNERS NOTEBOOK	81	The circuits circuit
TECH TIPS	107	Your ideas and your work

Square sines and triangles p.20



Electronic playmates p.61

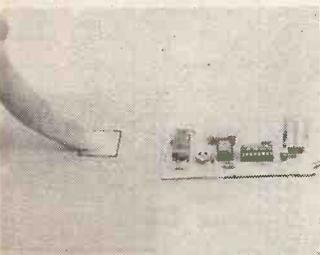

Touching project p.93

PROJECTS

FUNCTION GENERATOR	20	Sine on here
DICE	32	Let it roll
RAIN ALARM	35	Don't be a drip
HUM FILTER	46	Sound device
LONG PERIOD TIMER	55	Wait a minute . . . or an hour . . .
RANDOM NOISE SOURCE	67	Have a row
AIR BAND CONVERTER	76	Ear to the air
THE BEAST Pt 2	86	Remotely interesting
TOUCH SWITCH	93	Do it by feel
FLASH TRIGGER	97	Out with the bulbs
LOGIC PROBE	101	Bit useful

INFORMATION

ETI NEXT TIME	31	Advance warning
MARKETPLACE	44	A new watch offer
SPECIALS	51	One offs from ETI
SUBSCRIPTIONS	80	Why do it any other way?
BOOK SERVICE	85	Fine print
HE FOR THEE	72	Don't be left out

EDITORIAL AND ADVERTISEMENT OFFICE 145 Charing Cross Road, London WC2H 8DEE. Telephone 01 437 1002/3/4/5	
INTERNATIONAL EDITIONS AUSTRALIA Collyn Rivers Publisher Roger Harrison Acting Editor HOLLAND Anton Kriegsmen Editor-in-Chief CANADA Graham Wideman Editor GERMANY Udo Wittig Editor	Ron Harris, B.Sc Editor Ian Graham B.Sc Editorial Assistant Diego M. Rincon Art Director Dee Camilleri Production Paul Edwards, Tony Strakas Technical Illustrators Joanne Barseghian Ray Marston Project Editor Keith Brindley, John Fitzgerald Project Engineer Steve Ramsahdeo Project Development Margaret Hawitt Administration Lorraine Stout Editorial Secretary Christopher Surgenor (Manager) Advertising Sandie Neville Ad. Production Steve Rowe Ad. Representative Halvor Moorshead Editorial Director
	PUBLISHED BY Modmags Ltd., 145 Charing Cross Road DISTRIBUTED BY Argus Distribution Ltd. (British Isles) Gordon & Gotch Ltd. (Overseas) PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

Send your orders to: —
DEPT ETI 12, PO BOX 6, WARE, HERTS. Tel 0920-3182
 Visit our NEW shop: **3 BALDOCK ST., WARE HERTS. Telex: 817861**

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	£0.50
BP14	2nd Book Transistor Equivs & Subs	£1.10
BP24	52 Projects Using IC741 (or Equiv)	£0.95
BP26	Radio Antennas Book Long Distance Reception & Transmission	£0.85
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	£0.60
BP32	Build Metal & Treasure Locators	£1.00
BP35	Handbook of IC Audio Preampifiers & Power Amplifier Construction	£1.25
BP36	50 Circuits use Germ/S11/Zener Diodes	£0.75
BP39	50 Field Effect Trans Projects	£1.25
BP40	Digital IC Equivs & Pin Connection	£2.50
BP41	Linear IC Equivs & Pin Connection	£2.75
BP42	50 Simple LED Circuits	£0.75
BP43	How to make Walkie-Talkies	£1.25
BP45	Projects on Opto-electronics	£1.25
BP46	Radio Circuits Using ICs	£1.35
BP47	Mobile Discotheque Handbook	£1.35
BP48	Electronics Projects for Beginners	£1.35
BP49	Popular Electronic Projects	£1.45
BP50	IC LM3900 Projects	£1.45
BP55	Radio Stations Guide	£1.45
BP160	Coil Design & Construction Manual	£0.75
BP202	Handbook of Integrated Circuits Equivalent & Substitutes	£1.00
BP205	1st Book Hi-Fi Speaker Enclosures	£0.75
BP213	Circuits for Model Railways	£1.00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	£0.85
BP217	Solid State Power Supply Handbook	£0.85
BP221	28 Tested Transistor Projects	£1.25
BP222	Short-wave Receivers for Beginners	£0.95
BP223	50 Projects using IC CA3130	£0.95
BP224	50 CMOS IC Projects	£0.95
BP225	A Practical Intro to Digital ICs	£0.95
BP226	Build Advanced Short-wave Receivers	£1.20
BP227	Beginners Guide to Building Electronic Projects	£1.25

NEWNES BOOKS

216	Transistors 3rd Ed	£1.00
217	Integrated Circuits	£1.00
218	Radio & Television Electronics	£1.25
219	Electronics	£1.15
220	Colour TV 2nd Ed.	£1.15
221	Hi-Fi	£1.15
222	20 Solid State Proj. for Car	£1.95
223	20 Solid State Proj. for Home	£1.95
224	110 Int. Circ. Proj. for Home	£2.95
225	110 Thyristor Projects	£2.50
226	Operational Amp. Proj. for Home	£2.50
228	Electricity	£1.15
229	Beginners Guide to Electronics	£0.48
230	Beginners Guide to Television	£2.25
231	Beginners Guide to Transistors	£2.25
232	Beginners Guide to Electric Wiring	£2.25
233	Beginners Guide to Radio	£2.75
234	Guide to Colour TV	£2.25
235	Electronic Diagrams	£1.80
236	Electronic Components	£1.80
237	Printed Circuit Assembly	£1.80
238	Transistor Pocket Book	£3.90
239	50 Photoelectric Circuits	£1.80
240	Semiconductor Handbook Part 1	£5.25
241	Semiconductor Handbook Part 2	£4.28
242	Electronics Pocket Book	£3.90
244	Beginners Guide to Integrated Circuits	£2.75
209	BI-PAK TTL Data Book	50p
	BI-PAK CMOS Data Book	50p

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.16
DPDT standard slide	1974	£0.17
Toggle switch SPST 1/2 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on-off mains switch	1977	£0.58
Push switch — Push to make	1978	£0.16
Push switch — Push to break	1979	£0.21

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST — moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.35
	BLACK	1981	£0.35
	WHITE	1982	£0.35
	BLUE	1983	£0.35
	YELLOW	1984	£0.35
	LUMINOUS	1985	£0.35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.81
Miniature SPST toggle 2 amp 250V ac	1959	£0.86
Miniature DPDT toggle 2 amp 250V ac	1960	£0.91
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.07
Push-button SPST 2 amp 250V ac	1962	£1.04
Push-button SPST 2 amp 250V ac	1963	£1.09
Push-button DPDT 2 amp 250V ac	1964	£1.34

MIDGET WAFER SWITCHES
 Single bank wafer type — suitable for switching at 250V ac 100mA or 150V dc in non-reactive loads make-before-break contacts. These switches have a spindle 0.25 in dia and 30 indexing.

Description	No.	Price
1 pole 12 way	1965	£0.55
2 pole 6 way	1966	£0.55
3 pole 4 way	1967	£0.55
4 pole 3 way	1968	£0.55

MICRO SWITCHES	No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac	1970	£0.29

OPTOELECTRONICS

NEW INCREASED RANGE — ALL 1ST QUALITY LEDs (diffused)

O/no.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (125)	RED	£0.12
1502	MIL3232 (TIL211)	3mm (125)	GREEN	£0.22
1503	MIL3331 (DP212A)	3mm (125)	YELLOW	£0.22
1504	ARL4850 (FLV117)	5mm (2)	RED	£0.12
1505	MIL5251 (TIL222)	5mm (2)	GREEN	£0.22
1506	MIL5351 (MV5353)	5mm (2)	YELLOW	£0.22
1509	'HL-BR11'	5mm (2)	CLEAR (Hl. Red)	£0.13

SUPER 'HI-BRITE' TYPE

No.	Type	Size	Colour	Price
1521	MIL32	3mm (125)	RED	£0.12
1522	MIL52	5mm (2)	RED	£0.12
1514	ORP12 Light dependent resistor		RED	£0.63
1520	OCF71 Photo transistor		RED	£0.40

LED CLIPS

No.	Description	Price
150B/125	pack of 5 125 clips	£0.17
150B/2	pack of 5 2 clips	£0.21

DISPLAYS:

No.	Description	Common Anode	Price
DL703	7 segment D.P. left (30" height)	o/no. 1523	£0.85
DL707	7 segment D.P. left (30" height)	Common Anode	£0.82
DL708	7 segment D.P. left (30" height)	Common Anode	£0.82
DL709	7 segment D.P. left (30" height)	Common Anode	£0.82
DL727	7 segment D.P. right (510" height)	Common Anode	£2.07
DL747	7 segment D.P. left (630" height)	Common Anode	£1.73

OPTO-ISOLATORS
 Isolation Breakdown — Voltage 1500 — continuous fwd current 100mA

No.	Description	Price
CL74	Single-Channel 8 pin DIP standard type — optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor	o/no. 1497 £0.61
CLD74	Multi-Channel 8 pin DIP Two Isolated Channels	o/no. 1498 £1.22
CLQ74	Multi-Channel 16 pin DIP Four Isolated Channels	o/no. 1499 £2.69

MEL 11 (TIL81) NPN LIGHT DETECTOR
 Silicon Photo Darlington Amplifier — V_{CEO} 30v V_{ECO} 10v I_c 100mA Ptot. 300mW Hl Min 0.5 Typ. 2mA ID 100mA nA o/no. 1496 £0.29

NUTS AND BOLTS

BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50

Type	No.	Price	Type	No.	Price
1in OBA	839	£1.38	1/2in 4BA	846	£0.37
1/2in OBA	840	£0.86	1/4in 4BA	847	£0.25
1/4in 2BA	842	£0.75	1/8in 6BA	848	£0.48
1/8in 2BA	843	£0.52	1/16in 6BA	849	£0.24
1/16in 2BA	844	£0.60	1/32in 6BA	850	£0.29
1in 4BA	845	£0.51			

BA NUTS — packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	859	£0.16	4BA	861	£0.14
2BA	860	£0.14	6BA	862	£0.14

SOLDER TAGS — Hot tinned supplied in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	851	£0.46	4BA	853	£0.25
2BA	852	£0.32	6BA	854	£0.25

AUDIO LEADS

No.	Type	Price
107	FM Indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	£0.86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m	£0.98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead. Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios. 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.21
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£1.04
120	Car stereo connector. Variable geometry plug to fit most car cassettes, 8 track cartridge and combination units. Supplied with inflated fuse power lead and instructions	£0.69
123	6.6m Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£1.72
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.85
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.85
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.85
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.49
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5. Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m	£0.86

AUDIO LEADS

134	5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm	£0.78
136	Coiled stereo headphone extension lead. Black, length 6m	£2.01
178	AC mains lead for calculators, etc	£0.52

TRANSFORMERS

MINIATURE MAINS Primary 240V

No.	Secondary	Price
2021	6V-0.6V 100mA	£1.04
2022	9V-0.9V 100mA	£1.04
2023	12V-0.12V 100mA	£1.29

MINIATURE MAINS Primary 240V
 with two independent secondary windings

No.	Type	Price
2024	MT280-0.6V-0.6V RMS	£1.84
2025	MT150-0.12V-0.12V RMS	£1.84

1 AMP MAINS Primary 240V

No.	Secondary	Price	P & P
2026	6V-0.6V 1 amp	£2.88	45p
2027	9V-0.9V 1 amp	£2.30	45p
2028	12V-0.12V 1 amp	£2.99	55p
2029	15V-0.15V 1 amp	£3.16	66p
2030	30V-0.30V 1 amp	£3.97	86p

STANDARD MAINS Primary 240V
 Multi-tapped secondary mains transformers available in 1/2 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50V. Voltages available by use of taps.

No.	Rating	Price	P & P
2031	1/2 amp	£3.91	86p
2032	1 amp	£5.06	86p
2033	2 amp	£6.27	£1

2035 240V Primary 0.55V @ 2A Secondary £7.30 P & P £1

SPECIAL OFFER

2042 240V Primary 0.20V @ 2A Secondary. By removing 5 turns for each volt from the secondary winding any voltage up to 20V @ 2A is easily obtainable. Ideal for the experimenter.
 £1.50 P & P 86p

CASES AND BOXES

INSTRUMENT CASES. In two sections, vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.73
156	11in	6in	3in	£2.92
157	6in	4 3/4in	1 3/4in	£1.79
158	9in	5 1/4in	2 1/2in	£2.43

ALUMINIUM BOXES. Made from bright anodized construction each box complete with half-inch-deep lid and screws

No.	Length	Width	Height	Price
159	5 1/4in	2 1/4in	1 1/2in	£0.85
160	4in	4in	1 1/2in	£0.85
161	4in	2 1/4in	1 1/2in	£0.85
162	5 1/4in	4in	1 1/2in	£0.87
163	4in	2 1/4in	2in	£0.87
164	3in	2in	1in	£0.60
165	7in	5in	2 1/2in	£1.43
166	8in	6in	3in	£1.82
167	6in	4in	2in	£1.18

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front — strong construction easily accessible

169	2 1/4in	5 1/4in	2 1/4in	1 1/2in	8in	£5.45
168	1 5/8in	7 1/4in	4in	1 1/2in	1 1/2in	£8.31

VERO plastic case box. These boxes consist of top and bottom sections which include fixing points for horizontal mounting PC boards & chassis plates, the two sections are held together by four screws which enter through the base and are concealed by plastic feet

No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4.35
171	140mm	75mm	205mm	£4.85
172	140mm	110mm	205mm	£6.30

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0.18
1 1/4in x 1/4in chassis mounting	507	£0.14
1 1/4in car inline type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1 1/4in	510	£0.37

QUICK BLOW 20mm

Type	No.	Type	No.	Type	No.
150mA	611	7p	1A	615	6p
250mA	612	6p	1.5A	616	7p
550mA	613	6p	2A	617	6p
800mA	614	6p	2.5A	618	7p

ANTI-SURGE 20mm

Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK-BLOW 1 1/4in


Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634

All 6p each

Type	No.	Type	No.	Type	No.
1A	635	2.5A	638</		

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

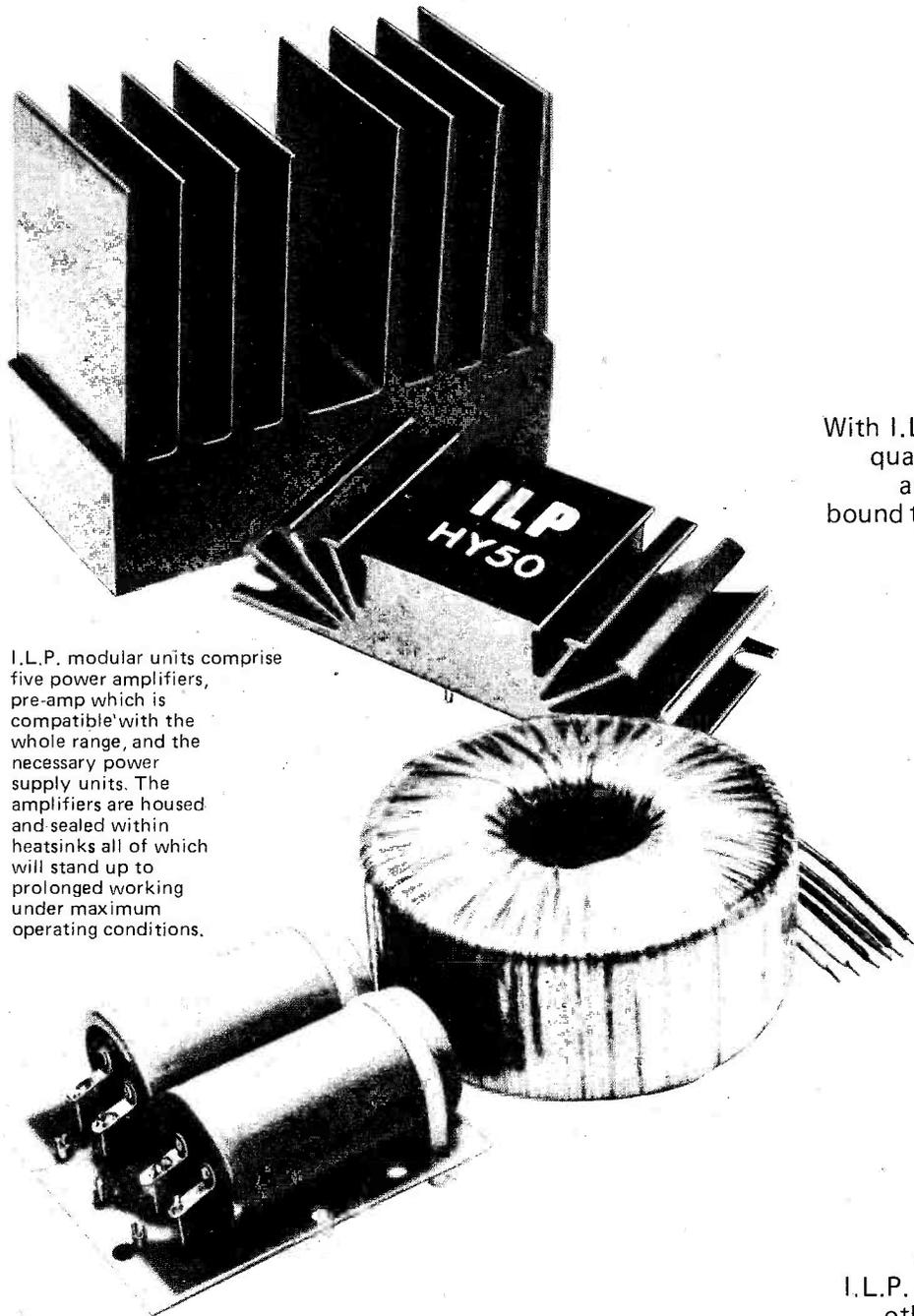

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.



With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance — and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain — the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

and staying there

PERFORMANCE MODULAR UNITS


HY5 PRE-AMPLIFIER

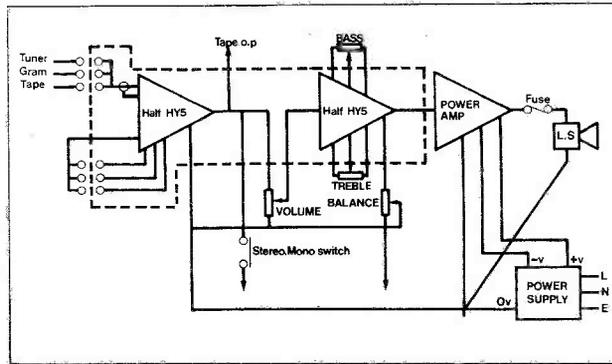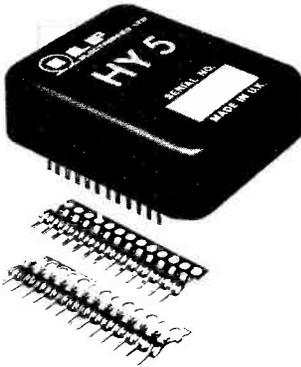

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.


£4.64 + 74p VAT

THE POWER AMPLIFIERS

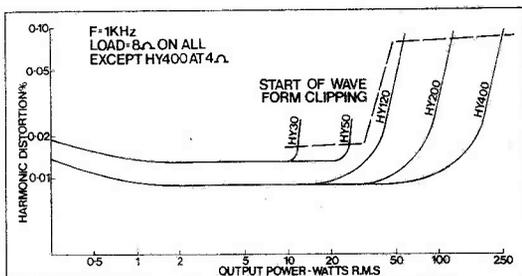


Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

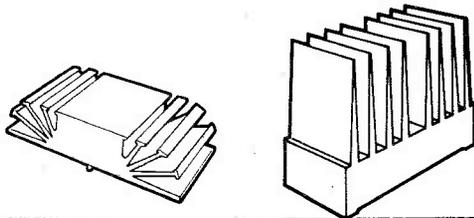Load impedance — all models 4 - 16 Ω
 Input sensitivity — all models 500 mV
 Input impedance—all models 100 KΩ
 Frequency response — all models 10Hz - 45KHz - 3dB



THE POWER SUPPLY UNITS

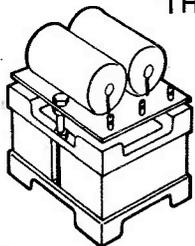

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled transformer the other with toroidal transformer half weight and height of conventional laminated types.


- PSU 30** ± 15V at 10ma to drive up to five HY5 pre-amps £4.50 + 68p VAT
- PSU 36** for 1 or 2 HY30's £8.10 + £1.22 VAT
- PSU 50** for 1 or 2 HY50's £8.10 + £1.22 VAT
- PSU 70** with toroidal transformer for 1 or 2 HY120's £13.61 + £2.04 VAT
- PSU 90** with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT
- PSU180** with toroidal transformer for 1 HY400 or 2 x HY200 Ma £23.02 + £3.45 VAT

**NO QUIBBLE
 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BUILT-IN PROTECTIVE CIRCUITRY
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE
 — see below**

ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

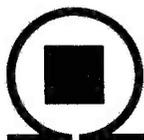Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



ELECTRONICS LTD.
 FREEPOST, 4 Graham Bell House, Roper Close
 Canterbury, Kent CT2 7EP
 Telephone (0227) 54778 Telex 965780

Please supply Total purchase price £

I enclose Cheque Postal Orders International Money Order


Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

CHROMATHEQUE 5000

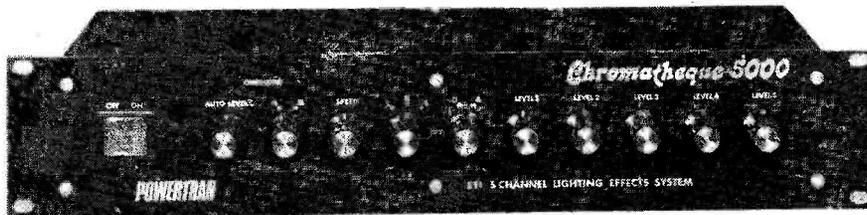

Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

POWERTRAN

5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT

ONLY

£49.50 + VAT!


MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

COMPLETE KIT

ONLY


£49.90 + VAT!

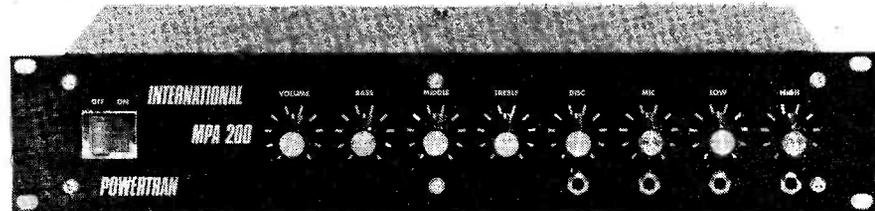**MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!**




Panel size 19.0" x 3.5". Depth 7.3"

Featured as a constructional article in *ETI*, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 2000 is simplicity itself with minimal wiring needed making construction very straightforward. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

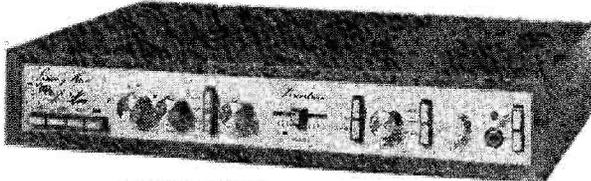


DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in *H-Fi News and Record Review* and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

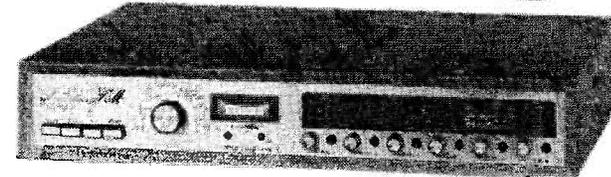

WIRELESS WORLD FM TUNER £70.20 + VAT

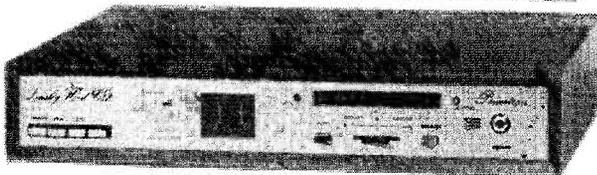A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder, incorporating active filters for "birdy" suppression.



LINSLEY-HOOD CASSETTE DECK £79.60 + VAT

This design, published in *Wireless World*, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control.

T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in *Practical Wireless*, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for **£38.40 + VAT**.

MATCHING TUNERS — SEE OUR FREE CATALOGUE!

COMPLETE KITS: Our complete kits really are complete. All of the projects shown on this page are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet (first 4 kits on this page), or professional quality rack mounting cabinet (first 2 kits on this page), cables, nuts, bolts, etc., and full instructions — in fact everything!

All of the kits shown on this page are available as separate packs for those customers who wish to spread their purchase or perhaps make their own cabinets or metalwork. Prices are given in our **FREE CATALOGUE**.

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until January 31st, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m.-4.30 p.m. Monday-Thursday.

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!


POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455



DIGEST

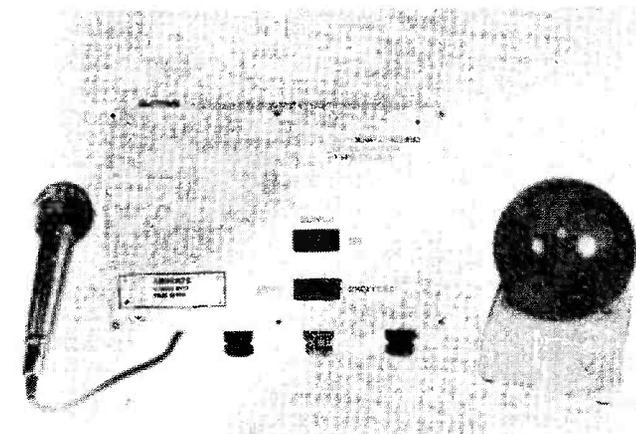

Silence Is Golden

It's also ball-shaped. (I'm not going to be rude, honest). The Golden Ball is a new, automatic sound level controller for discos and dance halls. Made by Ardent of Windsor, well-known for their work in noise control, this unit is designed to help club owners avoid complaints, keep neighbours happy and reduce health risks to audiences.

A sensitive directional mike detects harmful noise levels, a golden, ball-shaped light switches on when the sound is too loud and a control box shuts off amplifier power if the warning is ignored.

The mechanically accepted

figure at which sound becomes a danger to health is 90dB, so the system automatically cuts out noise in excess of this figure. Below that, users can set their own particular comfortable maximum noise level.

So what happens when the maximum is exceeded? Well, the ball lights up to warn everyone that the limit has been reached. Five seconds then elapses in which the sound level can be reduced voluntarily. If this isn't done, there's an embarrassing five seconds of silence until the system resets itself.

Full details of the Golden Ball are available from the Anti-Noise Pollution Division, Ardent Ltd, Thames Avenue, Windsor, Berkshire.

Air-Porters

If you've had to lug cases miles around an airport, from terminal to bus station or car park, you're well aware of the need for transport within an airport complex. Gatwick are going in for a luxury system — unmanned vehicles.

However, these won't be the sort of unmanned buses that sit stationary by the kerbside defying all timetables and raising the blood pressure. Built by Westinghouse (couldn't a British firm do it?) the system will comprise two fully automatic buses, each operating on its own track connecting the main terminal to the new satellite building.

Each bus will carry 80 passengers, mainly standing, although some seats will be provided for the elderly, infirm or panic-stricken. Doors will open and shut automatically and pre-recorded message will advise passengers to mind the doors and hold tight. No passenger should have to wait more than 90 seconds for a lift.

Although it's an American system, 45% of the work will be done by UK industry. Work has already begun on the new satellite project, which is due for completion in 1982.


Sitting Comfy?

How do you rate the ride comfort of your daily commuter train? Perhaps the number of coffee spills per mile or the number of times you're woken from pleasant slumbers.

Well, the ride comfort on the new Advanced Passenger Train should be improved, thanks to the Jacobmeter. This interesting little instrument (named after the BR engineer who developed the concept) measures vertical and horizontal accelerations separately and displays calculated root mean square values according to criteria in ride comfort curves derived from the ISO and motion sickness data. The integration period can be set to either 10 or 60 seconds.

The Jacobmeter is currently being used in commissioning trials on the prototype Advanced Passenger Train. It may later be used as a tool for general use throughout British Rail. So, fellow commuters, it looks like chuff-chuff comfort may be a bit better by the time we take out a mortgage on our next season ticket.

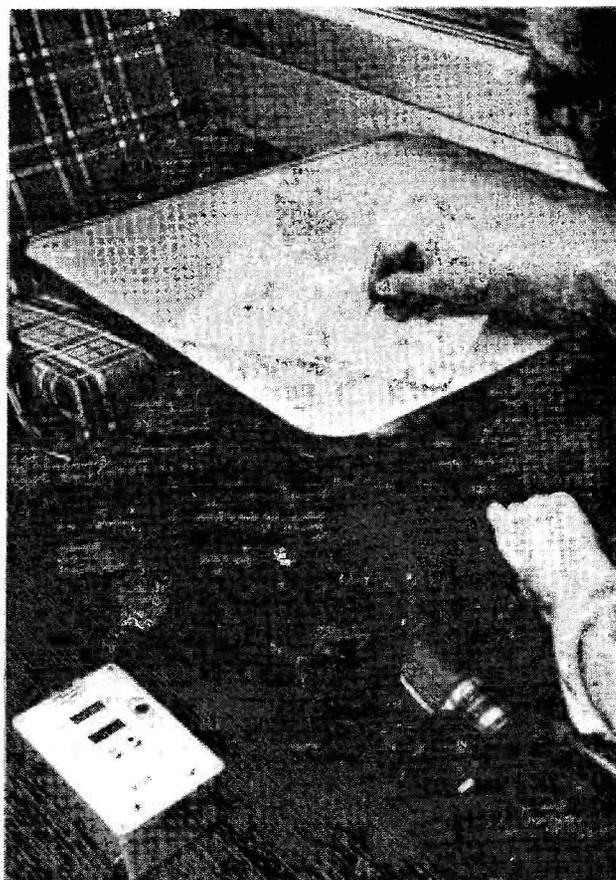The Jacobmeter is made to a BR design by Kemo Ltd, 9-12 Goodwood Parade, Elmers End, Beckenham, Kent BR3 3QZ.



Romane Electronics

LOW POWER SCHOTTKY TTL EX STOCK

We are holding substantial stocks of the Devices listed below. All orders, large and small, will be dealt with in strict rotation. Please add 15% V.A.T. to all orders plus 30p for P&P. Export orders no VAT but postage at cost air/surface. Prompt delivery on all orders.

Device	Price	74LS38	39p	74LS132	70p	74LS197	120p
74LS00	13p	74LS40	23p	74LS136	45p	74LS221	110p
74LS01	14p	74LS47	80p	74LS138	75p	74LS244	250p
74LS02	13p	74LS48	130p	74LS139	80p	74LS245	260p
74LS03	14p	74LS49	130p	74LS151	65p	74LS247	150p
74LS04	15p	74LS73	40p	74LS153	65p	74LS248	150p
74LS05	25p	74LS74	40p	74LS155	96p	74LS249	90p
74LS08	30p	74LS75	38p	74LS156	96p	74LS251	100p
74LS09	30p	74LS76	38p	74LS157	65p	74LS273	200p
74LS10	16p	74LS78	43p	74LS158	83p	74LS279	85p
74LS11	23p	74LS83	120p	74LS160	118p	74LS283	92p
74LS12	25p	74LS85	120p	74LS161	100p	74LS290	92p
74LS13	36p	74LS86	40p	74LS162	130p	74LS293	100p
74LS14	75p	74LS90	50p	74LS163	130p	74LS298	100p
74LS15	25p	74LS93	90p	74LS164	100p	74LS352	170p
74LS20	17p	74LS95	110p	74LS173	90p	74LS353	170p
74LS21	24p	74LS107	40p	74LS174	90p	74LS365	95p
74LS22	25p	74LS109	50p	74LS175	92p	74LS366	95p
74LS26	35p	74LS112	50p	74LS190	120p	74LS367	95p
74LS27	25p	74LS113	50p	74LS191	120p	74LS368	95p
74LS28	40p	74LS114	50p	74LS192	120p	74LS374	160p
74LS30	19p	74LS123	80p	74LS193	110p	74LS386	50p
74LS32	27p	74LS125	40p	74LS195	110p	74LS670	200p
74LS37	32p	74LS126	40p	74LS196	100p		

LOW PROFILE DIL SOCKETS BY TEXAS

8 Pin	13p	18 Pin	25p	24 Pin	33p
14 Pin	14p	20 Pin	27p	28 Pin	43p
16 Pin	16p	22 Pin	28p	40 Pin	53p

I.C. TEST CLIPS 10% Discount for 25+ clips, 15% Discount for 100+.
 8 Pin **£4.50** 14 Pin **£2.73** 16 Pin **£2.88** 18 Pin **£6.06**
 20 Pin **£7.00** 22 Pin **£7.43** 24 Pin **£8.41** 28 Pin **£9.24**
 36 Pin **£12.09** 40 Pin **£12.73**

SUPERSTRIP BREADBOARDS 840 solderless plug-in tie points. Accommodates up to nine 14 Pin DIPs. Price £10.07 with 10% Discount for 10+ superstrips and 15% Discount for 25+.

POWERACE PROTOTYPING LABS Two Superstrip Breadboards plus power supplies

- POWERACE 101** 5-15VDC supply @ 600mA plus 0-15V meter. Price £68.55.
- POWERACE 102** +5VDC supply @ 1A plus 3 logic indicators and pulse detector, 2 logic switches, 4 data switches, clock generator and one-shot. Price £92.75.
- POWERACE 103** +5VDC supply @ 750mA plus +15VDC @ 250mA and -15VDC @ 250mA. Also meter (15.0-15V), 2 logic indicators, 2 logic switches and 2 data switches. Price £99.80.

VERO PRODUCTS

Vero Wiring Pen	276p
2xSpare Spools	95p
Spot Face Cutters	93p
VeroBread Bread boards	325p

VEROBOARD PCBs

2.5"x5"	62p
2.5"x3'75"	53p
2.5"x1'7"	186p
3.75"x5"	69p
3.75"x1'7"	240p

MEMORIES

- 2114 **500p**
- TMS 2516 2K EPROM. Single 5V Supply **£27.00**
- 76477 Sound generator drip **210p**


LIGHT EMITTING DIODES

	0.122"	Price		0.2"	Price
RED	TIL209	13p	RED	TIL220	15p
YELLOW	TIL212	22p	YELLOW	TIL224-1	20p
GREEN	TIL232	20p	GREEN	TIL243-1	20p

All orders, large and small, will be dealt with IN STRICT ROTATION. Please add 15% V.A.T. to all orders plus 30p for P&P (£1 P&P for Poweraces). Export orders no V.A.T. but postage at cost air/surface. Prompt delivery on all orders. A full range of Breadboards, I.C. test clips, ribbon cable assemblies available (mostly ex-stock). Please send large S.A.E. for catalogue and price lists.

ROMANE ELECTRONICS

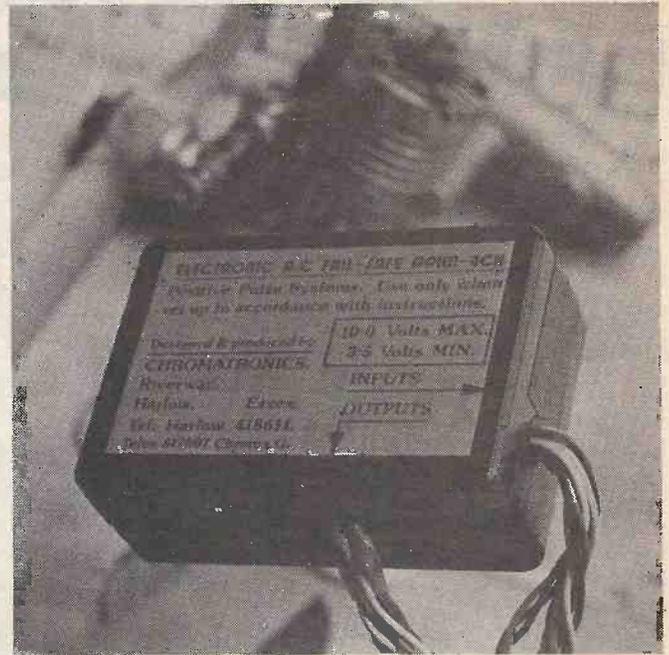64 Newlyn Drive, Sale, Cheshire. M33 3LE
 Tel. 061-962 2606



SOS (Save Our Servos)

Radio-control fans — remember that sinking feeling in your stomach as you watched your R/C model fall out of the sky, unable to do anything about it. Bet it was a shock, especially if your model was a yacht.

Chromatronics have just announced the introduction of an electronic fail-safe for radio modellers to minimise the danger of a model going out of control in the event of interference or loss of signal. Interference from what? Who said Citizen's Band (or is it Banned)?

The system will cope with co-channel interference from another R/C transmitter or CB (I promise I won't mention it again), total or partial transmitter or receiver failure and the model moving out of range. If your model tips the scales at 5kg or more, a fail-safe device is obligatory under CAA regulations.

Unlike earlier simple devices, the PP1M-4CH works by two level threshold detection on all four receiver outputs. So, all primary control functions can be protected from severe

glitches from whatever source. The unit is used to set up to four control servos in preset safe positions during a catastrophe. So, if the world should end, your Sopwith or Starfighter will still be zooming around the blue yonder until it runs out of four star, thanks to Chromatronics.

The unit works with any three wire positive pulse servo and has individual preset controls for each servo and variable fault detection thresholds. Cut-in time is only 0.1 seconds. The PP1M-4CH is connected between the receiver and servos and works with either AM or FM systems on the 27MHz UHF band or any other operational frequencies. It is small (62x42x23mm) and lightweight, packed in a robust plastic capsule. It comes with four input leads and four output leads already fitted, but you have to fit the appropriate plugs and sockets for your equipment.

For only £14.95 (including VAT), this electronic fail-safe device sounds like remarkably good value, considering the cost of replacing a crashed model. The PP1M-4CH is available from Chromatronics, Coachworks House, River Way, Harlow, Essex.

New Neosid

Neosid, a name well known in professional and consumer electronics, has recently established a new outlet for the amateur constructor and small user.

The new Small Order Catalogue covers a broad cross section of the company's products — ferrite beads, screw cores, rods, E, I and U cores and coil assemblies, plastic formers and trimming tools.

Send a stamped, addressed envelope for the Small Orders Catalogue to Neosid Small Orders, PO Box 86, Welwyn Garden City, Herts AL7 1AS.

Just a little bit more...

NASCOM-2


Compare its features:

- Z-80A 4MHZ. CPU:** The most powerful 8-bit processor on the market.
- 8K Basic:** resident on board, MICROSOFT Basic, the industry standard, with extensions for on-screen editing, graphics, machine code interfacing. Optimised for speed (see benchmarks below).
- Full 57 Key Licon solid state keyboard:** switch mechanisms are contactless, high reliability professional units for long trouble free life. Keyboard is mounted separately to avoid straining main P.C.B.
- Total of 20K on-board memory:** 2K monitor (Nas-Sys 1), 1K Video RAM, 1K Work space RAM, 8K Microsoft Basic, 8K user RAM.
- Kansas City cassette interface:** for reliable storage of programs and data at 300 or 1200 baud, with full checksum error detection.
- Nas-sys monitor:** A powerful 2K machine code monitor provides an ideal environment for learning about and developing machine code programs. Nas-sys uses a blinking non-destructive cursor, with 22 commands. ASCII terminals are fully supported via the serial interface; users can add their own I/O drivers via the system I/O vector table to support other devices.

Nas-sys commands are:

- | | |
|-------------------------------------|-----------------------------|
| A—Hex arithmetic | N—return to normal |
| B—set breakpoint | O—Output to P.I.O. |
| C—Copy | Q—Query input port |
| E—Execute | R—Read tape |
| G—Generate | S—Single step |
| H—Operate as half duplex, terminal. | T—Tabulate memory |
| I—Intelligent copy | U—activate user I/O drivers |
| J—Execute at FFA | V—Verify tape |
| K—set keyboard options | W—Write tape |
| L—load from tape | X—set external device |
| M—Memory modify | Z—execute at FFD |

- On board P.I.O. — An uncommitted P.I.O. (MK 3881) giving 16 programmable I/O lines with handshake.**
- On board RS-232C Will interface directly into any standard teletype — allowing use of BASIC or Nas-sys from the teletype.**
- Full on-screen editing:** a complete screen editor with cursor movement (UP, DOWN, LEFT, RIGHT), insert and delete, backspace etc.
- Screen display of 16 lines x 48 characters:** Stable, clear display to British television standards. Full 128 ASCII character set; option for further 128 graphics characters.
- Fully buffered NASBUS compatible:** Well defined bus structure with a range of expansion cards; including (shortly) a floppy disc system with CP/M — the industry standard operating system.

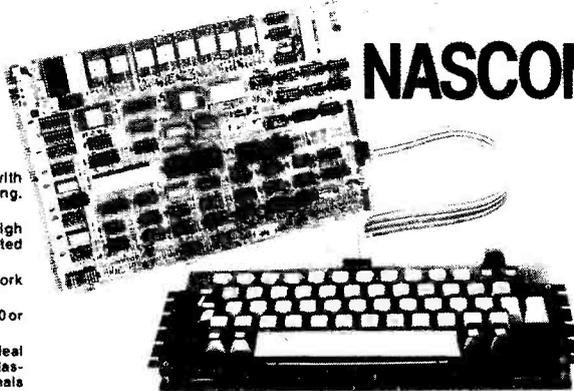

	Nett	Vat	Total
Nascom-2	295.00	44.25	339.25
Power supply	24.50	3.68	28.18
10 C15 cassettes	4.44	0.66	5.10
Z-80 Programming manual (Mostek)			4.50
Z-80 Microcomputer handbook			6.95
Practical microcomputer programming the Z-80			20.00
Sargon-8K Z-80 Chess program (book)			9.50

PERSONAL COMPUTER WORLD BENCHMARK TESTS

	APPLE II	RM. 380Z	PET
BM 1	1.5	1.1	1.7
BM 2	3.2	5.4	9.9
BM 3	7.3	11.1	18.4
BM 4	7.2	11.6	20.4
BM 5	8.9	12.6	21.7
BM 6	18.6	19.3	32.5
BM 7	28.2	27.6	50.9
BM 8		5.2	6.2



MICRODIGITAL

25 Brunswick Street, Liverpool L2 0BJ
Tel: 051-236 0707 (Mail Order) 051-227 2535 (All other Depts)

- | | |
|--|----------|
| TEK scope 545A with H plug-in | £125 ea. |
| TEK scope 545A with CA plug-in | £175 ea. |
| H.P. scope 175A 50MHZ Dual trace Single Trae | £175 ea. |
| WAYNE KERR Universal Bridge CT375 | £75 ea. |
| MARCONI Wave Analyser TF2330 | £500 ea. |
| MARCONI Audio Oscillator TF1101 20HZ-200KHZ | £45. ea. |
| MARCONI Valve Voltmeter TF1041C | £30 ea. |
| NOISE GENERATOR CT410 — covers audio to VHF | £8 ea. |
| TEK Transistor Curve Tracer | £225 |
| NAGARD Pulse Generator 5002C | £50 ea. |
| MARCONI Wave Analyser type TF455E | £50 ea. |
| SOLARTRON DVM LM1420 with AC unit LM1477 | £40 ea. |
| HONEYWELL 1920 character Upper Case ASCII VDU with edit and block mode transmission. Limited quantity. With data | £260 ea. |
| CALCOMP Drum Plotter type 564 | £1,500 |
| MARCONI GEN FT995 (CT402) | £170 |
| MARCONI Bridge TF868B | £120 |
| RANK Fluter Meters | £50 ea. |
| HEWLETT PACKARD Signal Gen. 608D | £240 |
| AVO Signal Generator HF135 | £120 ea. |
| MARCONI Magnification Meter TF1245 with TF1246 | £175 |
| MARCONI Magnification Meter TF1245 with TF1247 | £175 |
| VARIACS — Ex-Equipment. Good condition. 8 Amps | £25 ea. |
| 20 Amps | £35 ea. |
| Some 3 phase available. Please enquire. Carriage all units £4 ea. | |

CRYSTALS 19.2KHZ
FLAT METAL CASE. BRAND NEW
50p EACH

- 10-Way Multi-Colour Ribbon Cable.** New. 40p per metre. P&P 50p.
- SPEAKERS** 2 1/2in. 50 ohm 0.2W. New 40p each. P&P 50p.
- STEPPING MOTORS** 6 1/2 position with additional where the rotor is coils. Device can be used as a tach. Diagram supplied. Will actually work on 5 volts. 12/24 recommended. £1.50 each. P&P 75p. Reduction for quantity.
- RAPID DISCHARGE capacitors** 8mfid 4kV. £5 each. P&P £1.50.
- GEC UHF 4 button tuner.** £2.50 each. P&P 85p.
- BIG INCH MOTOR** 110V AC 3rpm 50 cycle — very small. 50p each. P&P 50p.
- CENTAUR 115V FANS.** Brand New 4.5x4x1.5in. £4.50 each. P&P 75p.
- Ex-Used Equipment** — tested. 60p each. P&P 75p.
- POTTER & BRUMFIELD TIMER RELAY.** 115V AC Heavy duty 2 pole c/o with 2 second delay. Change R & C for different timing. 50p each. P&P 85p.
- CONTACTORS.** Heavy Duty 24V DC 5 make. £1 each. P&P 85p.
- GEC UHF/VHF 6 button tuner.** £4.50 each. P&P £1.
- DIGITAL 24 HOUR CLOCK** with built-in alarm as used in Braun Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 6 1/2 x 2 1/4 x 2 1/4. ONLY £3.75 each. P&P 50p.
- 931A PHOTOMULTIPLIER** in stainless steel container with window and built in resistor network. £2 each. P&P £1.
- SLIDER CONTROL 500K.** Log Single track. Complete with knob. Length 3 1/2in. 25p each. P&P 25p.
- RANCO 250V 16A THERMOSTATS** with Control Knobs calibrated 50-200degree F. £2.50 each. P&P £1.
- SOLID STATE UHF TUNERS.** 3B mcs. £1 each. P&P 75p.
- BRAND REX blue wire wraps.** 30 metres for £1. P&P 25p.
- 5in. SOLID RUBBER RINGS** (1in. dia. rubber). Keep the kids (or dog) happy. 4 for £1. P&P £1.25.

- TRANSFORMERS**
- AUTO 240V** input 115V. 1 Amp output. £1.25 each. P&P £1.25.
- 240V** input Sec 6V. Size 2 1/2 x 2 x 2in. Good quality. £1.50 each. P&P £1.
- 240V** input Sec 12V 0.92A. Size 2 1/2 x 2 x 2in. Good quality. £1.50 each. P&P £1.
- 240V** input Sec 12V 100MA. Size 60 x 40 x 42mm. 50p each. P&P 75p.
- 240V** input Sec 12.0-12V 50MA. Size 53 x 45 x 40mm. £1 each. P&P 75p.
- 115V** input Sec 5V 250MA. Size 1 1/2 x 1 1/2 x 1 1/2in. 2 for 50p. P&P 75p.

SEMICONDUCTORS

- At 2p each.
- 1N3063, 1S44.
- At 5p each.
- BC147; BC148B; BC157; BC158; BC 237; BF197; OA90; OA91; BA154; BA243.
- At 25p each.
- TIP31, TIP41A; 2N5296; AF139; ZTX341.
- BY127 10p; BF181 20p; BD239 40p; BD241 40p; MJE340AT 40p; BD222 50p.
- BD235 & BD234 Comp pair 25W — 80p per pair or 50p each.
- Regulator TBA335 8 to 20V in — 5V out 100MA. T08. Can. 50p each.
- BF256C — 20p.
- FND10 7 segment display 0.15in. 40p each.
- TV AMPLIFIER TBA120. 20p each.

Integrated Circuits

7453	5p	709	15p	75325	£1
7451	5p	74H74	12p	SN15882	4p
7401	5p	74H51	7p	MC4028	60p
7402	12p	74S38	10p	7417	14p
7476	20p	74S02	12p	7441	40p
7495	35p	74154	70p		

- MOTOROLA DUAL** in Line 6 pin Opto Coupler 30p each. Gold plate tester version. 50p each.

- AM9140-4K RAMS** STATIC 5 Volt ceramic. £4 each.

- TELEPHONES.** 706 style. Black or Grey £5.50 each. 746 style B or Grey £7.50 each. Older style Black £2.50 each. Postage £1 each.
- HONEYWELL** Humidity Controllers 50p each. P&P 40p.

- THYRISTOR TIMERS.** Solid State. 15secs adjustable (pre-set) in plastic relay case. Standard 7 pin base. Series delay 50p each. P&P 85p.
- MINIATURE PC MOUNT SLIDE SWITCH.** Single pole 5-wire. 10p each.

- DIGITAL to ANALOGUE CONVERTOR.** 8-bit will fit standard socket. With data. £2.50 each. P&P 25p.
- VARIACS:** 2 amp Standard 240 Volts £10 each. P&P £1.50.
- ELECTROSTATIC VOLTMETERS.** 7.5KV £6 each. P&P £1.50.
- Other ranges available — please enquire.
- TRIMMERS.** Sub min 0.25 to 1.25p; 1 to 4 5p; 5 to 20p; All at 6p each.

Minimum order £3 value of goods. P&P or Carriage and VAT at 15% on total must be added to all orders

CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5 pm Monday to Saturday incl. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMHEAD LTD

NORWOOD ROAD, READING TEL NO. READING 669656

(2nd left passed Reading Tech College in Kings Road then first right — Look on right for door with spoked wheel)

LOGIC PROBE

If you're into TTL or CMOS, you could use a logic probe.

Good quality commercial probes don't come cheap.

Our probe features high and low indication

and detects pulse trains to over 1MHz, for less than a fiver.

Interest in digital electronics has grown rapidly in the past few years with the advent of microprocessors and large scale integration. The most essential test instrument for experimenting with digital circuitry is a logic probe.

In its most basic form this should provide an indication of the logic level at any point in a circuit without overloading the section being tested. Other desirable features are the ability to follow high frequency pulse trains (preferably over 1 MHz) and to detect isolated, narrow pulses less than 1 μ S in width. Finally, the instrument should be compatible with both TTL and CMOS ICs and be able to operate from a wide range of supply voltages (say five to 15 volts).

Commercial logic probes that satisfy all these requirements are available, but they invariably cost over £30. The probe design described here offers comparable performance for less than £4, combined with an excuse to enjoy a good cigar — a cigar tube is used for the case!


Indication is by means of three LEDs. Two red LEDs indicate either a HIGH or a LOW condition on the point under test, a green LED is used to indicate that a pulse train is occurring.

The circuit uses a single CMOS IC and a handful of resistors and capacitors. The components are mounted on a small board and housed in a tubular case such as an aluminium cigar tube or a length of plastic conduit. The power is supplied from the actual circuit under test and the performance characteristics of the prototype are described in the specification listed here.

Construction

A printed circuit board is recommended for this project to provide consistent performance characteristics.

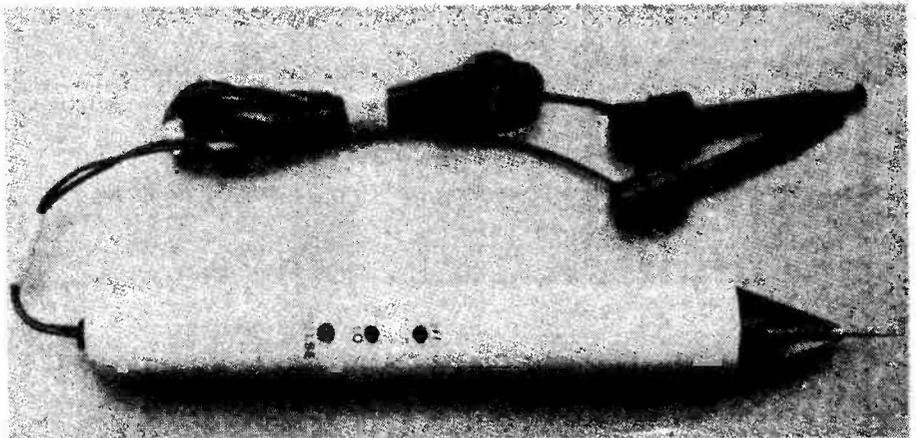Before attempting to mount the components on the printed circuit



The logic probe in a cigar tube, showing the Hi, Lo and Pulse indication LEDs.

board check to see that it fits easily into the case. The board must be a loose enough fit to allow it to be moved up and down within the case over a range of at least 5 mm. (Refer to the diagram).

Mount the wire links, the resistors and the capacitors on the board, keeping all components as close to the board as possible. Note that C3 is mounted on the underside of the board. Next, install the three LEDs. The height of the LEDs above the board must be such that the assembly will slide into the case with the board pushed down against the bottom of the case (see diagram). For a 20 mm diameter case this height should be about 12 mm. If the LEDs are not high enough, then it will not be possible to push the assembled board up into a position where the LEDs project through the holes in the case.

Next, add the power leads (without clips or E-Z hooks at this stage) and the 10 cm wire to the probe tip. Last of all solder IC1 into position, observing all

the usual precautions — shorted pins, heat sink, earthed soldering iron, pins 8 and 16 soldered first.

Drill the 3 mm holes for the LEDs at 10 mm intervals, starting 75 mm from the front of the case. The hole for the supply leads is drilled in the back of the case and fitted with a small rubber grommet (or plastic LED housing) to prevent the case rubbing through the insulation on the leads.

Before mounting the assembled board in the case check the circuit for dry joints, solder bridges, incorrectly mounted components, etc. Then test the device as follows. Connect to a five volt supply and observe the three LEDs. None should light with the probe tip isolated. If the LOW LED (LED 2) comes on or flashes, then R2 is too small and must be replaced by a slightly larger resistor (say 820k). Touching the probe tip with the fingers may cause LED 2 to light, but this should go off when the tip is isolated. Touching the probe tip to either supply rail should ▶

HOW IT WORKS

Three of the six inverter/buffers in IC1 are used in the high/low detection circuit. IC1c is connected to the probe tip via R9. When the input goes HIGH (logic 1), IC1c output goes low and illuminates LED 2 through R5. Similarly when the input goes LOW (logic 0), the series pair IC1e and f illuminate LED 1 through R4. The resistor network R1, R2 and R3 ensure that the outputs of both IC1c and IC1f remain high when the input is 'floating'. C1 is connected across R2 as a 'speed-up capacitor' to maintain a sharp pulse shape into IC1e and so improve the ability to follow high frequency pulse trains (over 1MHz).

The two inverters IC1a and b form a monostable circuit that stretches short pulses (less than 500 nsec) out to 15 msec (0.7RC) using C3 and R8. The input of the monostable comes from the DC level of the output of IC1c and is isolated from the DC level by C2. The combination of R7 and D1 normally holds IC1b through C2, the output goes high, forcing IC1a to go low and illuminate LED 3. Diode D1 ensures that the input to IC1b is kept low (0V7 above zero) so long as the output of IC1a remains low. This prevents subsequent pulses from re-triggering IC1b until the monostable itself re-triggers via discharge of C3 to earth through R8, and allows IC1a output to go high, switching off LED 3.

Capacitors C4 and C5 (optional) confer immunity to spikes or pulses in the supply lines, which are taken from the circuit being tested.


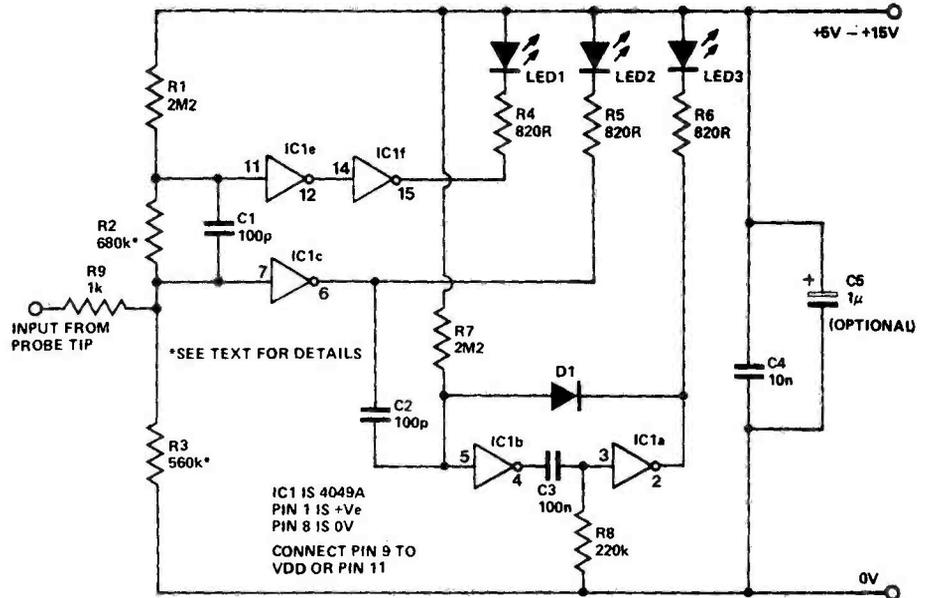


Fig.1. Circuit diagram. Note the polarity of LEDs 1, 2 and 3.

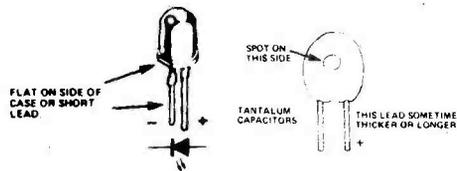

NOTE
C5 IF USED IS MOUNTED ACROSS C4 (OBSERVE POLARITY)

CONNECT RESPECTIVE LETTERS TOGETHER A TO A B TO B etc.

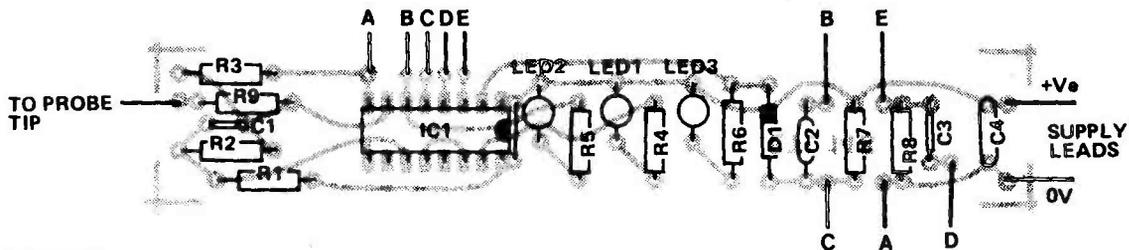


Fig.2. Component overlay.

PARTS LIST

Resistors all 1/4W, 5%

R1,7	2M2
R2	680k*
R3	560k*
R4,5,6	820R
R8	220k
R9	1k

Capacitors

C1,2	100p Ceramic
C3	100n Polyester
C4	10n Polyester
C5	1u (Optional)

Semiconductors

IC1	4049A
-----	-------

LED 1,2	3mm red
LED 3	3mm green
D1	1N4148 (or equivalent)

Miscellaneous

PCB; red and black leads with alligator clips or E-Z hooks; cigar case (or equivalent) — minimum dimensions 20mm ID, 140mm long; probe tip housing.

* Resistors R2 and R3 may have to be altered slightly (in the range 470k to 820k) to suit the transfer characteristics of IC1 — see text.

BUYLINES

Once again, components should be readily available from most suppliers. Make sure the components you buy will fit into the container you choose. If you're not a cigar smoker, plastic piping from your local hardware store will do just as well.



The long thin PCB should look like this when it's finished.

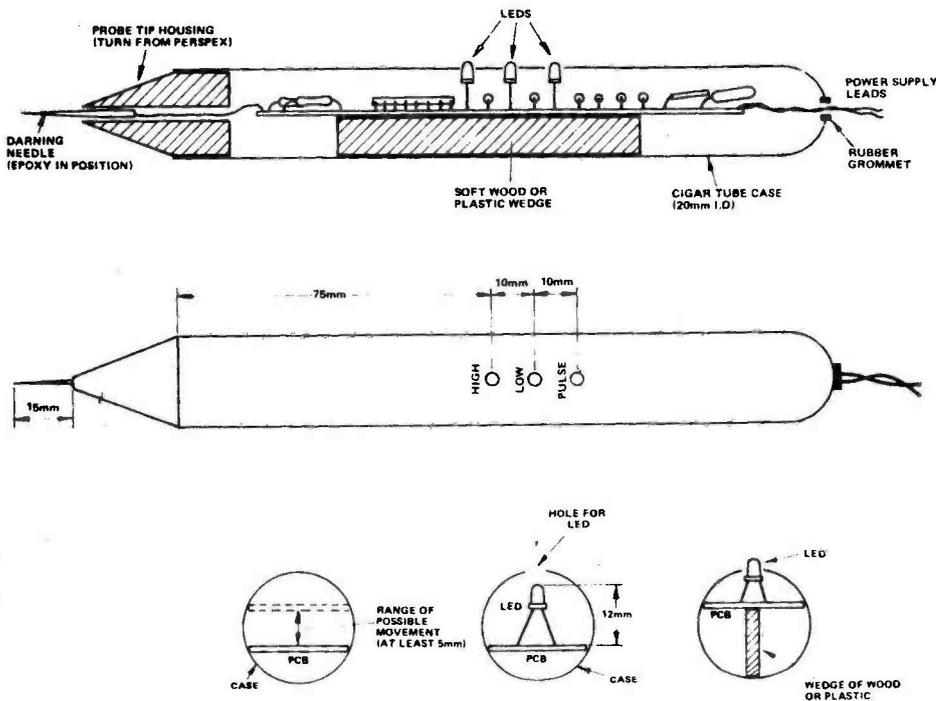


Fig.3. The PCB slides into the cigar tube and rests on a piece of wood or plastic.

light the appropriate LED, with the PULSE LED flashing when the tip first touches the positive rail. If the LOW LED does not light when the probe is connected to 0V, then R2 is too large. Change R2 to 560k and repeat the sequence above.

Now try a 15 volt supply. Again, all LEDs should be extinguished when the probe tip is isolated. The HIGH LED (LED 1) may glow very faintly. If this glow is too strong, reduce the value of R3 to say 470k. However, if R3 has to be altered it will be necessary to recheck the circuit at 5V to see that the low voltage performance is still satisfactory. At 15 volts repeat the process of touching the probe tip to the two supply rails. The results should be the same as in the case of the 5 volt supply, but the LEDs will be considerably brighter. **ETI**



GRANDSTAND

VIDEO ENTERTAINMENT COMPUTER

SIMPLY PLUGS INTO YOUR TV

Beautifully simple to link to any 625-line UHF Television. Connects to the mains and just plugs into the TV aerial socket and ... you're off! Plays in colour on colour TVs and gives a sparkling black and white picture with B & W televisions, and broadcasts realistic sound effects to add to the excitement.

Space-age computer technology brings an amazing variety of games which you play in the comfort of your own armchair stadium at home. Get in with the action without getting out! Fun for all the family, it plays the generation game with live TV action to suit all ages. Once you've been in control of the TV, normal service might never be resumed again!

It's so excitingly different ... great for parties and to make the evening when visitors call.

CARTRIDGES AVAILABLE AT £11.99

Videocart-1: 1-player games — "Noughts and Crosses," "Shooting Gallery," "Doodle" and "Quadroodle"

Videocart-2: 2-player "Desert Fox" and 1-player "Shooting Gallery"

Videocart-3: 1 and 2-player "Video Blackjack"

Videocart-4: 1 and 2-player "Spitfire"

Videocart-5: 2-player "Space War"

Videocart-6: 1-player "Math Quiz 1" (addition-subtraction)

Videocart-8: 1-player "Mind Reader"

Videocart-9: 2-player "Drag Strip"

Videocart-10: 1 and 2-player "Maze" and "Cat & Mouse"

Videocart-11: 2-player "Backgammon" and "Acey-Ducey"

Videocart-12: 2-player "Baseball"

Videocart-13: 1 and 2-player "Torpedo Alley" and "Robot War"

Videocart-14: 1 and 2-player "Sonar Search"

Videocart-15: 1 and 2-player "Memory Match"

Videocart-16: 1 and 2-player "Dodge It"

Videocart-17: 1 and 2-player "Pinball Challenge"

Videocart-18: 1 and 2-player "Hangman"

Videocart-20: 1 and 2-player "Video Whizball"

Videocart-21: 1 and 2-player "Bowling"



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CARD or AMERICAN EXPRESS number.

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G

Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN · 10 am · 7 pm — Monday to Saturday

★NOW OPEN ALL DAY SUNDAY — For Shop Sales Only★

Close to New Barnet BR Station — Moorgate Line.



(Part of the Compshop Ltd. Group)

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Electrolytic Radial Leads				Order Code				Miniature Low Value				Polyester Radial Leads															
Electrolytic Axial Leads				-10% to +50% Tol.				-10% to +50% Tol.				Cap 034 + μ F + Volts				Cap 424															
μ F	V.d.c.	16	25	40	63	μ F	V.d.c.	6.3	10	16	25	35	40	50	63	pF	424	632	630	nF	424	629	Cap 632	Cap 630	Cap 629	μ F	352	360	μ F	352	360
1.0	1.5					47	68									1.2	100	18	7	10	27	8				0.01	7	1	7	9	
2.2	3.3					1.0	1.5									1.5	120	18	9	12	29				0.02	6	7	15	8	10	
4.7	6.8					2.2	3.3									2.2	150	18	9	15	29				0.033	6	7	33	11	11	
10	15					4.7	6.8									3.3	180	18	9	18	31				0.047	6	7	47	14	14	
22	33					10	15									4.7	220	18	9	22	31				0.068	6	7	68	17	17	
47	68					22	33									6.8	300	18	9	33	42				0.1	6	8	1.0	20	24	
100	150					33	47									10	350	18	9	39	50				0.15	6	8	1.5	30	35	
220	330					47	68									15	470	20	9	27	42				0.22	6	8	2.2	35	35	
470	680					68	100									20	630	20	9	33	45				0.33	6	8	3.3	45	45	
1000	1500					100	150									25	820	20	9	39	50				0.47	6	8	4.7	50	50	
2200						150	220									33	1000	20	9	39	50				0.68	7	8	6.8	60	60	

Trimmers				Order Code				Electrolytic Can Type				Order Code				Tantalum Bead				Order Code											
250V D.C. Wkg. Film Dielectric, Miniature				Cap 808 A				High Ripple, IEC Grade 1, Low E.S.R. Cap MR + μ F + Volts				Supplied complete with Vertical Fixing Clip				20% Tol.				Cap PR + μ F + Volts											
1.4 - 4.1pF	20	20	22	22	22	22	22	10000 μ F	16V	Repple 5.8A @ 85°C	8.1A @ 50°C	238	22000 μ F	16V	8.8A	13.7A	370	0.1	V.d.c.	10	16	25	35	0.22	0.47	1	2.2	4.7	22	47	
2 - 20pF	20	20	22	22	22	22	22	22000 μ F	25V	4.8A	6.4A	215	4700 μ F	25V	6.0A	11.2A	282	2.2													
5.5 - 59.5pF	31	31	31	31	31	31	31	4700 μ F	40V	5.6A	7.8A	248	10000 μ F	40V	9.2A	12.8A	393	13													
								4700 μ F	70V	7.5A	10.5A	403							18												

INTEGRATED CIRCUITS				7400 T.T.L.				OPTO ELECTRONICS				SWITCHES				SEMICONDUCTORS																																		
4000 Buffered C-MOS - High Speed				7400 T.T.L.				Light Emitting Diodes, Individual				Miniature Toggle - Honeywell				In914																																		
HEF4000	HEF4001	HEF4002	HEF4003	HEF4004	HEF4005	HEF4006	HEF4007	HEF4008	HEF4009	HEF4010	HEF4011	HEF4012	HEF4013	HEF4014	HEF4015	HEF4016	HEF4017	HEF4018	HEF4019	HEF4020	HEF4021	HEF4022	HEF4023	HEF4024	HEF4025	HEF4026	HEF4027	HEF4028	HEF4029	HEF4030	HEF4031	HEF4032	HEF4033	HEF4034	HEF4035	HEF4036	HEF4037	HEF4038	HEF4039	HEF4040	HEF4041	HEF4042	HEF4043	HEF4044	HEF4045	HEF4046	HEF4047	HEF4048	HEF4049	HEF4050
HEF4001	HEF4002	HEF4003	HEF4004	HEF4005	HEF4006	HEF4007	HEF4008	HEF4009	HEF4010	HEF4011	HEF4012	HEF4013	HEF4014	HEF4015	HEF4016	HEF4017	HEF4018	HEF4019	HEF4020	HEF4021	HEF4022	HEF4023	HEF4024	HEF4025	HEF4026	HEF4027	HEF4028	HEF4029	HEF4030	HEF4031	HEF4032	HEF4033	HEF4034	HEF4035	HEF4036	HEF4037	HEF4038	HEF4039	HEF4040	HEF4041	HEF4042	HEF4043	HEF4044	HEF4045	HEF4046	HEF4047	HEF4048	HEF4049	HEF4050	

RESISTORS				VERO ELECTRONICS PRODUCTS				SKELETON PRESETS, Miniature				SKELETON PRESETS, Standard				POTENTIOMETER, Rotary				POTENTIOMETER, Slider			
Carbon Film, Fixed				2.5" x 5" 1" pitch Veroboard				0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting				0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting				0.5W, E3 Values, 1K1-2M2 Lin.				0.5W, E3 Values, 2K2-470K Lin.			
0.25W, E24 Values, 10R-10M, 5% Tol.	2 each	100/100 (Multi 10/Value)	Res RD%	3.75" x 5" 1" pitch Veroboard	71	200-21069J	71	200-21069J	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8	Mn. Preset H	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11	Sid. Preset H	0.5W, E3 Values, 1K1-2M2 Lin.	39	Ro Pot Lin	0.5W, E3 Values, 2K2-470K Lin.	45	Si Pot Lin			
0.5W, E12 Values, 10R-4M7, 10% Tol.	3 each	150/100 (Multi 10/Value)	Res RD% + Value	2.5" x 5" 1" pitch Veroboard (5)	85/Pack	200-21076B	85/Pack	200-21076B	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
0.5W, E24 Values, 10R-10M, 5% Tol.	8 each	400/100 (Multi 10/Value)	Res MR30	3.75" x 5" 1" pitch Plain Board	65	200-21018A	65	200-21018A	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
0.5W, E12 Values, 10R-10M, 10% Tol.	16 each	800/100 (Multi 10/Value)	Res PR52 + Value	5.82" x 2.9" 1" pitch V-Q DIP Board	107	200-21013A	107	200-21013A	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				Spot Face Cutters	107	200-21013A	107	200-21013A	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				Pin Insertion Tool for .040 type pin	147	200-21015F	147	200-21015F	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				DS Pins .040 (100)	40/Pack	200-21017B	40/Pack	200-21017B	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				55 Pins .040 (100)	44/Pack	200-21017B	44/Pack	200-21017B	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				Verovore Kit (1 pen, 2 wire, 25-comb)	454/Kit	200-21341D	454/Kit	200-21341D	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				Verovore Combs (25)	109/Pack	200-21339F	109/Pack	200-21339F	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			
				Verovore Wire (2)	109/Pack	200-21340G	109/Pack	200-21340G	0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting	8 <td>Mn. Preset H + Value</td> <td>0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting</td> <td>11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td></td>	Mn. Preset H + Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting	11 <td>Sid. Preset H + Value</td> <td>0.5W, E3 Values, 1K1-2M2 Lin.</td> <td>39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td></td>	Sid. Preset H + Value	0.5W, E3 Values, 1K1-2M2 Lin.	39 <td>Ro Pot Log</td> <td>0.5W, E3 Values, 2K2-470K Lin.</td> <td>45 <td>Si Pot Log</td> </td>	Ro Pot Log	0.5W, E3 Values, 2K2-470K Lin.	45 <td>Si Pot Log</td>	Si Pot Log			

GMT
ELECTRONICS

**Freepost
Birmingham
B19 1BR
021-233-2400**


- ACCESS
- VISA
- CASH
- CHEQUE

See
us
at

**EXHIBIT
BOARD
1979**

4th - 8th
December
Royal Horticultural
Halls, London

FULL SPEC KIT TELETEXT DECODER

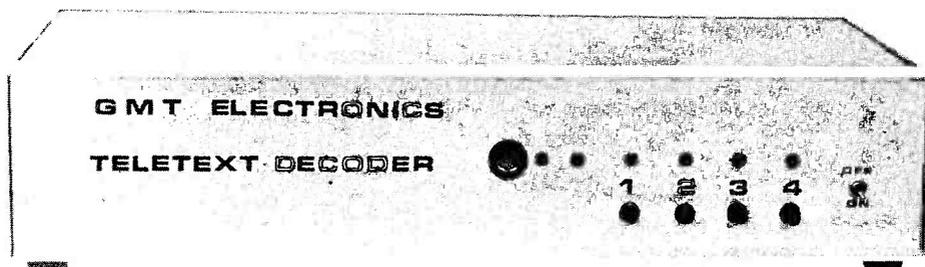

- STATE OF THE ART L.S.I. CIRCUITS
- DOUBLE HEIGHT CHARACTER SELECTABLE FOR LEGIBILITY
- CHARACTER ROUNDING - EFFECTIVELY DOUBLES DEFINITION
- ULTRASONIC REMOTE CONTROL
- HIGH QUALITY THROUGH PLATED P.C.B.
- ALL I.C. MOUNTED ON SOCKETS
- PREALIGNED UHF/IF MODULES
- NEEDS NO INTERNAL CONNECTION TO THE TELEVISION SET
- SIZE 430mm x 90mm x 220mm
- SUPPLY 240v 50Hz 35w
- *NEW *TOUCH-CONTROL KEYPAD* NEW*


INCLUDES TUNER, P.S.U., DECODER, REMOTE KEYBOARD, P.A.L. ENCODER, U.H.F. MODULATOR CASE WITH SCREENED AND PUNCHED FRONT PANEL.

— £189.90 inc VAT. P & P £3.00.

FULL TELETEXT MANUAL IF BOUGHT SEPARATELY — £2.50 P & P £0.50.


P.C.B.'S AND L.S.I. I.C.'S NOT SOLD SEPARATE FROM KITS.

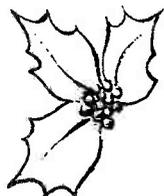P & P INCLUDES CARRIAGE, PACKING AND INSURANCE



GMT HAS

Ideas for Christmas

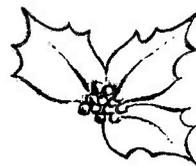

SEND FOR OUR FREE LEAFLET

Enclosing an S.A.E.

* KITS, TOOLS & OTHER GOODIES *

BREADBOARD

Royal Horticultural Halls Elverton Street
Westminster London SW1

December 4-8th 1979 Admission £1 (students 70p)

1979



There's a lot going on at Breadboard!

Seventy exhibitors showing and selling everything that the hobby electronics enthusiast could want! Demonstrations of electronic organs — computer kits — audio gear.

Radio Station S22 broadcasting throughout the show. See your voiceprint! Get your own weather details direct from Tiros M! Test your reactions — and your strength.

Careers in Electronics — get the advice and information that could start you off on a rewarding and interesting career.

It's worth going to Breadboard!

Please add 25p for p&p.

DELTA TECH & CO.

62 NAYLOR ROAD, LONDON, N20 0HN
All prices VAT inclusive

RESISTORS (1/4W E12) 10 ohm to 10 Mohm	1.5p
PRESETS (1/4W Horizontal) 100 ohms to 2 Mohms	8p
POTENTIOMETERS (Carbon) LOG AND LINEAR	
1 Kohm to 2 Mohms	28p
VEROBOARDS (0.1" Copper) 2.5" x 5"	52p
3.75" x 5"	62p
ZENER DIODES (400mW) 2.7V to 33V	8p
TRANSFORMERS (240V) 9.0-9V, 100mA	90p
0.15V, 0.15V, 200mA	100p
CERAMIC CAP (50V) 22pF to 50nF	2p
POLYSTYRENE CAP (160V) 10pF to 1,000pF	4p
POLYESTER CAP (100V) 1nF to 100nF	4p
15, 22, 33, 39uF	5p
47, 68uF	9p
1uF: 12p	2.2uF: 20p
3.3uF: 26p	4.7uF: 30p
ELECTROLYTIC CAP (uF/V) 1/25V to 50V/25V	5p
68/50V, 100/25V	6p
150/40V, 220/12V	7p
220/25V	8p
330/12V, 500/30V	12p
1,000/10V	13p
1,500/25V	24p
2,200/6.3V	20p

BRIDGE RECTIFIERS 0.75/200V	25p
0.75/600V	30p
1A/50V	22p
1A/100V	27p
1A/200V	32p
1A/400V	34p
2A/50V	40p
2A/100V	42p
2A/200V	48p
2A/400V	55p

VOLTAGE REGULATORS 320H-05	40p
320H-24	40p
7805	70p
7812	70p
7815	70p
7818	70p
7824	70p
7905	90p
7912	90p
7915	90p
7918	90p
7924	90p

OPTO/DISPLAY 2N5777	55p
OCP71	65p
ORP12	60p
MAN72	110p
MAN74	110p
1.25" & 2"	
LEDs:—	
Red	10p
Green	14p
Yellow	14p
1.25" clip	3p
.2" clip	4p
DIODES BY127	10p
OA47	8p
OA91	8p
OA200	6p
OA202	9p
1N916	5p
1N4148	4p
1N4001	4p
1N4002	4p
1N4003	5p
1N4004	6p
1N4005	6p
1N4006	8p
1N4007	8p
1N5400	13p
1N5401	14p
1N5402	15p
1N5404	16p

DIL SOCKETS 8 pin	11p
14 pin	13p
16 pin	14p
18 pin	18p
22 pin	22p
24 pin	24p
28 pin	28p
40 pin	40p

LINEAR CIRCUITS 709	40p
710-14	33p
747-14	48p
748-8	44p
CA3018	70p
CA3028A	85p

CA3046	70p
CA3054	90p
CA3080	75p
CA3130	90p
CA3140	45p
LF351N	65p
LF356N	75p
LM301AN	32p
LM308N	60p
LM318N	200p
LM324N	74p
LM339N	60p
LM348N	90p
LM377N	175p
LM380N	75p
LM381N	140p
LM382N	130p
LM1310N	150p
LM3900N	55p
LM3909N	70p
MC1496P	85p
NE531	105p
NE555	25p
NE556	60p
NE566	140p
TBA641A	200p
TBA641B	200p
TBA800	75p
TBA810S	110p
ZN414	100p
ZN1034	200p

4030	48p
4035	107p
4041	78p
4042	58p
4043	83p
4044	90p
4047	90p
4048	55p
4049	30p
4050	30p
4066	38p
4069	15p
4070	15p
4071	15p
4072	15p
4073	15p
4081	15p
4082	15p
4086	66p
4510	73p
4511	99p
4516	95p
4518	72p
4520	69p
4528	99p
TTL 7400	11p
7401	11p
7402	11p
7403	11p
7404	13p
7405	13p
7406	15p
7407	20p
7408	13p
7409	13p
7410	13p
7411	17p
7412	15p
7413	27p
7414	48p
7416	25p
7417	25p
7420	13p
7421	21p
7422	16p
7427	25p
7428	28p
7430	13p
7432	18p
7433	30p
7437	15p
7438	15p
7440	10p
7441	56p
7442	43p
7443	35p
7444	78p

7445	60p
7446	65p
7447	53p
7448	62p
7450	10p
7451	12p
7453	12p
7454	12p
7460	12p
7470	17p
7472	21p
7473	24p
7474	24p
7475	30p
7476	26p
7480	25p
7485	66p
7486	22p
7490	32p
7491	28p
7492	17p
7493	32p
7494	30p
7495	30p
7496	42p
7497	200p
74100	60p
74105	43p
74107	20p
74109	25p
74110	40p
74118	88p
74121	26p
74122	22p
74123	40p
74125	34p
74126	34p
74132	48p
74141	45p
74142	200p
74145	55p
74150	69p
74151	48p
74153	52p
74154	89p
74155	54p
74156	30p
74157	52p
74160	64p
74161	66p
74162	66p
74163	66p
74164	66p
74165	45p
74166	85p
74173	70p
74174	50p
74175	60p
74176	64p


74177	53p
74180	50p
74181	99p
74182	30p
74190	75p
74191	70p
74192	50p
74193	64p
74194	68p
74195	65p
74196	80p
74197	40p
74198	107p
74199	80p
TRANSISTORS AC126/7	20p
AC128	20p
AC128/176	
Mt. pr.	40p
AC176	20p
AC187/8	21p
AD149	60p
AD161/2	40p
AF116	35p
AF117	35p
AF124	34p
AF139	35p
AF239	45p
BC107	10p
BC108/9	10p
BC147	8p
BC148	10p
BC149	9p
BC157	10p
BC158/9	10p
BC167	13p
BC169C	13p
BC173	6p
BC177/8	16p
BC179B	18p
BC182/3	10p
BC184	10p
BC209	11p
BC212/3	11p
BC214	14p
BC261B	14p
BC461	34p
BC477	23p
BC478/9	23p
BC547/8	12p
BC549	13p
BC557/8	13p
BC559	15p
BCY70	16p
BCY71	19p
BCY72	18p
BD115	40p

BD131/2	38p
BD135/6	35p
BD137/8	35p
BD139	35p
BD140	35p
BF180	24p
BF181	8p
BF184	21p
BF185	25p
BF194/5	10p
BF196/7	10p
BF244B	35p
BF259	25p
BFR39	32p
BFR79	32p
BFX29	25p
BFX87	22p
BFX88	27p
BFY50/1	22p
BFY52	18p
BRV39	22p
BSX20	140p
BU205	200p
BU208	200p
MJ2955	110p
MJE340	70p
MJE2955	104p
MJE3055	85p
MPF102	40p
MPF103	40p
MPF104	40p
MPF105	40p
MPF106	46p
MPSA06	26p
MPSA56	26p
MPSU06	61p
OC35	86p
TIP29	35p
TIP29B	35p
TIP30	35p
TIP30B	35p
TIP31	35p
TIP32	35p
TIP33	40p
TIP33C	60p
TIP34A	55p
TIP35A	200p
TIP36A	220p
TIP41A	60p
TIP42A	60p
TIP2955	70p
TIP3055	55p
ZTX107	13p
ZTX108	13p
ZTX109	13p
ZTX300	16p
ZTX301	18p
ZTX302	20p

ZTX303	24p
ZTX304	27p
ZTX311	19p
ZTX341	22p
ZTX500	16p
ZTX501	16p
ZTX502	21p
ZTX503	17p
ZTX504	28p
2N696	33p
2N697	13p
2N698	30p
2N706	14p
2N914	34p
2N918	33p
2N1131	20p
2N1302	28p
2N1303	60p
2N1304	55p
2N1613	25p
2N2222A	21p
2N2369	17p
2N2484	30p
2N2646	50p
2N2904	23p
2N2905	23p
2N2906	11p
2N2907	23p
2N2908	11p
2N3053	22p
2N3054	50p
2N3055	50p
2N3442	150p
2N3702	
2N37	11p
2N3722	180p
2N3772	330p
2N3819	21p
2N3820	55p
2N3821	70p
2N3822	60p
2N3903	10p
2N3904	10p
2N3905	10p
2N3906	10p
2N4030	33p
2N4059	12p
2N4067	14p
2N4068	35p
2N4069	35p
2N4070	35p
2N6027	45p



TECH TIPS

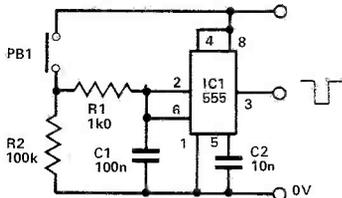

555 Micro Input Reset

P. Davidson

When dealing with a microprocessor system, there are several features which place requirements on the duration of their input leg reset. These


signals are usually negative (in the author's experience) and so, with the use of a 555, these requirements can be filled reliably (as opposed to the normal flip-flop debounce circuit). The circuit saves on logic used to invert the normal 555 monostable action.

LED Audio Power Indicators

M. P. Downes

The circuit diagram shows the input circuitry from the loudspeaker terminals. For simplicity only two of the monostable and LED driver circuits are shown. Six of these circuits can be constructed using three 4001s and one 4049 CMOS ICs. The circuit is based on the fact that CMOS has an input threshold of approximately half the supply voltage (actually 0.45 — 0.55 supply volts). IC1a and IC1b are dual input NOR gates connected in a monostable configuration with timing components R1 and C1. When the input to IC1a exceeds the threshold voltage, the monostable's output goes high for a period determined by R1 and C1 (with values shown approximately 200 mS). This output is inverted and buffered to drive a LED for this period. The input to trigger the monostable comes from the speaker terminals where it is full wave rectified and appears across RV1. R3 is a safety resistor in case of bridge failure. IN4005 diodes have the desired voltage and frequency characteristics for the bridge. R2 is to limit the current flowing into IC1a's internal protection diodes under large signal conditions and the value of RV1 depends on the desired input triggering voltage.

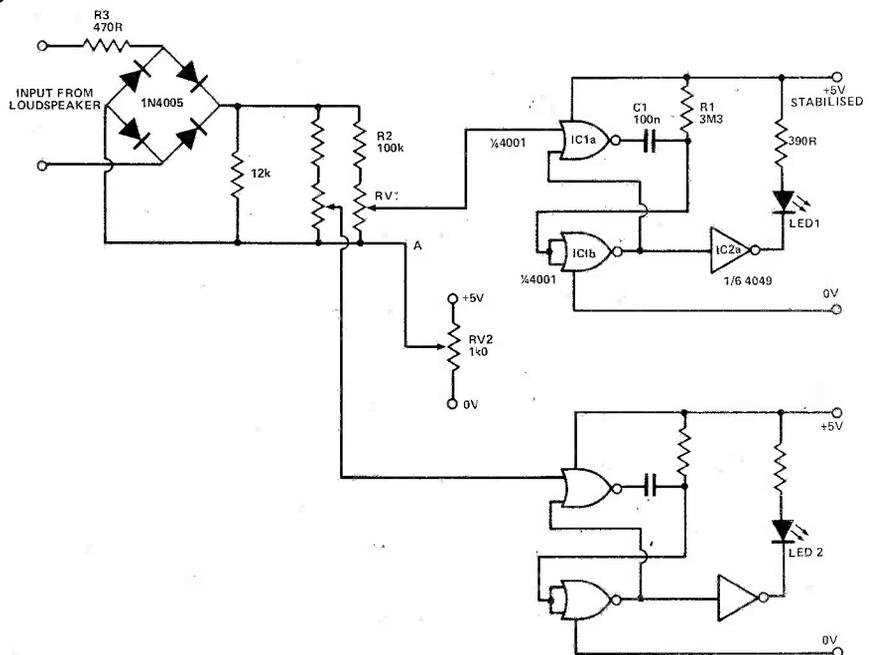The lowest input voltage that can trigger the monostable is limited by the voltage drop across the bridge (0V8) and the threshold voltage of IC1a (approximately 2V5). The



threshold limit is largely overcome by using RV2 to bias point A to just below the threshold voltage. In practice, the circuit operates on an input frequency of from less than 5 Hz to more than 50 kHz sine wave and at an input voltage of from approximately 1V4 RMS (0.25 W into 8R) to more than 90 V RMS (1 kW into 8R). A single positive or negative 4 μS wide pulse will also operate the circuit.

The +5 V supply must be stabilised to ensure stable threshold levels and the usual decoupling of ICs and supply is advisable. If two units are

required for stereo use, two completely separate +5 V power supplies are essential to prevent partial shorting out of the input bridge, due to a possible common loudspeaker terminal in the amplifier. Greater input sensitivity can be achieved by using OA91 diodes in the input bridge, but with slight loss in high frequency response and a lower maximum input voltage. If there is a variation in the threshold voltage of individual ICs then the lower threshold ICs should be used in the most sensitive positions of the circuit, i.e. 0.25W.

CHIPTESTER FOR NASCOM 1

Brand new fantastic product for Nascom 1 owners. Use your Nascom to test all those surplus and suspect ICs and sort out the good ones from the duff ones.

Just clip the IC in to the test clip provided and use the Nascom to examine the logic levels on each input and output. A graphical representation of the chip showing all pins and their logic levels is shown on the screen.

Tests all 5V TTL ICs up to 16 pins. Includes commands for automatic and manual testing of logic levels of all inputs and outputs simultaneously.

All inputs may be changed under keyboard or program control including continuous test mode.

Propagation delays may be calculated using an oscilloscope.

Routines to test ICs may be stored on cassette for later use.

Uses 2 ports on minimum Nascom system. No expansion whatever required.

Comes complete with all parts, full comprehensive instruction book, cassette with program and sample programs for popular ICs.

Send s.a.e. for free descriptive leaflet.

Price inclusive of VAT and postage

£19.50

Orders will be dealt with by return of post subject to availability of stock.

Stockists of Apple Micro Processor and Peripherals

Access and Barclaycard welcome

STRATHAND

44 St. Andrew's Square, Glasgow G1 5PL

Tel: 041-552 6731 or 2.

Telex: 777268 (24 hours service)

LINES FROM OUR VAST STOCKS — IMMEDIATE DELIVERY

NEW STOCKS BELOW MANUFACTURERS' PRICES.

Postage & packing add 50p per order.

CALCULATOR CHIPS General instrument GIMT4 on anti-static foam 24 pin D.I.L. socket for use with Bowmar display £1.50 ea. Pack of 25 chips £25, 100 for £80, 500 for £350.

BOWMAR 9 DIGIT CALCULATOR DISPLAY with PC connector 0.2 digits. Common cathode with bezel £1.25 ea. 10 for £10.

ORP12 light dependent resistance (Eq = RPY30). 2 for £1, 10 for £4.50, 100 for £40.

TBA 120A TV I.C. amplifier. Siemens 55p, 10 for £5, 100 for £50, 1,000 for £350.

BECKMAN 500 kcs Triggerable clocking oscillator for use with calculator chips 5v supply with circuit £1, 10 for £8, 100 for £65.

BURROUGHS 9 DIGIT Panaplex calculator display 7 segment 0.25" digits. Neon type with red bezel socket and data. £1.95 ea. 10 for £17, 100 for £140.

HONEYWELL PROXIMITY DETECTOR integral amplifier 8v D.C. £3.50 ea. 10 for £30.

MULLARD TBA800 I.C. audio amplifier. £1 each. 10 for £8, 100 for £70, 500 for £300.

RCA CA3069 F.M. IF £1.50, 10 for £12.

RCA CA3090A F.M. decoder £2.50, 10 for £20.

SU 206 MULLARD £1.50 ea. 10 for £12, 100 for £100.

2N2069 30v version T03 power. 10 for £3.50, 100 for £28, 500 for £125, 1,000 for £200.

DL707 by Hewlett-Packard. 1st grade 95p, 6 for £5, 50 for £35, 200 for £125.

C. Anode half-inch display in manufacturer's cartons.

MULLARD AD181-AD182 Matched pairs 1 pair 80p, 10 pairs £8, 100 pairs £50.

Cartons of 600 pairs £250 EX-STOCK.

RADIATION DETECTORS Quartz Fibre Dosimeters. Pen type with clip with lens and scale 0-50R. Originally over £5. **OUR PRICE 95p EACH**, 10 for £8, 100 for £80, 1,000 for £500.

CLOCKING OSCILLATOR (Phys-Dynamics). thick film 1MHz supply 5v 19x25x8mm 85p, 10 for £7, 100 for £60, 500 for £250.

TV TUNERS by Mullard. U.H.F. 38 mcs size 3 1/2 x 2 1/2 x 1 1/4 £2.50 ea. 10 for £20, 100 for £175, 500 for £750, 1,000 for £1,250.

MULLARD TUNER MODULES with data. LP1171 combined AM/FM IF strip £3.50.

LP1179 FM front end with AM tuning gang, used with LP1171 £3.50. LP1171 and 79 pair £5.75, 10 pairs for £50, 100 pairs for £400.

CAS885 RCA POSITIVE VARIABLE REG. Switch 100m amp variable 1.8 2 1/2v 55p ea. 10 for £5, 100 for £35, 1,000 for £300.

MULLARD LP1157 AM tuner modules with circuit £2.50 ea. 10 for £20, 100 for £175.

LUSTRAPHONE RIBBON MIKE £1.50, pre amp on chassis 3x2x1in. 10 for £12.50.

5 WATT GOULD-ADVANCE AMPLIFIER (built) 500kc into 2K input 4-8 ohms with data £3 ea.

AVO-8 METER MOVEMENTS for military version. Precision 37.5 micro-amp (50µa with integral shunt) movement £10.50.

TV SOUND

High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. £8.50 (UK P&P 50p).
As reviewed by "Popular Hi-Fi", July '79.

PHOTO CONDUCTIVE CELL £1.25. High power Cds cell 600 mw for control circuits. Resistance 800 ohm to 4K. Max volts 240. Size 1 1/2 x 1/2 in. 10 for £11, 100 for £100.

DYNAMIC MICROPHONE. Low imp. Foster insert. £1.45, 10 for £11, 100 for £100.

UHF TUNER BY GEC. 38mc/s with slow motion tuning. Size 5x3x2in. £3 ea. 10 for £25, 100 for £220, 500 for £1,000.

TWO GANG MINIATURE VARICAP TUNER 500pf with tuning knob. size 3x1 1/2 x 1 1/2 in. £1.25 ea. 10 for £10, 100 for £85.

ATES U1452 AUDIO I.C. AMPLIFIER 14 PIN D.I.L. 300 m. watts 55p each. 10 for £4.50, 100 for £35.

GENERAL ELECTRIC 2+2 watt I.C. stereo audio chips with circuit & data £1.95 each.

RCA CD4028AE 16 pin D.I.L. presettable up-down counter 85p each. 25 for £15, 100 for £50, 1000 for £355 (in anti static tubes of 25).

U.H.F. TV TUNER (preamp) with BF180 55p each. Built on P.C. board 2 x 2 in (sold without data) 10 for £4.50, 100 for £35, 1,000 for £250.

MARCONI I.C. Oscillator Data (T099 can) 30p each. 10 for £2, 100 for £15, 1,000 for £125.

PLESSEY SL432A I.C. IF amplifier (T099 can) 65p each. 10 for £6, 100 for £38, 500 for £190.

V.H.F. MODULATORS for tv games 85p each. 2 transistor — on built P.C. sizes 2 x 2 x 1 1/4 in. 10 for £8, 100 for £35, 500 for £150.

R.F. Filters for above modulators 20p each. Components and coils on built P. circuit. size 2 x 2 x 1 1/4 in. 10 for £3.50, 100 for £30, 500 for £125.

HIGH VOLTAGE TV TRIPLER DIODES BY I.T.T. stick type per 10 £1.50, per 100 £18, per 1000 £85.

TBA625 ATEs voltage regulators 85p each. 5 volts 100 m/amps (T099) per 10 £4.50, per 100 £39, per 1000 £280. 12v TBA625A, 15v TBA625C at same price.

MAINS LEADS 2 core 3 metres lengths (grey) per 10 £2.50, per 100 £20, per 1000 £165.

IN914 TYPE DIODES tested, uncooked in boxes of 1,000-£10, 10,000 for £75, 100,000 for £500.

ULTRASONIC TRANSDUCERS. 40KCs, pair £2.95, 10 pairs £29, 100 pairs £220.




Henry's

All mail to:
404 Edgware Road
London W2 England
Phone 01-723 1008



EXPORT ORDERS add ten per cent for carriage and packing. Payment in Sterling.


A Range of Performance from... ...HAMEG

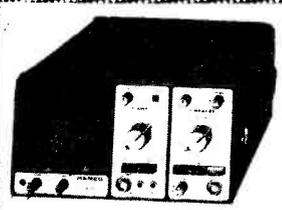

PERFORMANCE AND RELIABILITY
ARE THE SEALS FIRMLY STAMPED
ON THE COMPLETE HAMEG RANGE
AND IT IS A COMPLETE RANGE

- | | |
|--|------|
| HM307 Single Trace DC-10MHz Plus Built-in Component Tester | £149 |
| HM312 Dual Trace DC-20MHz, 5mV/cm, Full X-Y, 30MHz Trigger, Plus TV Trigger | 250 |
| HM412 Dual Trace DC-20MHz, 2mV/cm, X-Y, 40MHz Trigger, Plus Sweep Delay | 350 |
| HM512 Dual Trace DC-50MHz, 5mV/cm, X-Y, 70MHz Trigger Sweep Delay, Plus Single Shot, Sweep Delay and After Delay Trigger | 580 |
| HM812 Dual Trace as per HM512. Plus Storage, Automatic Storage and Variable Persistence | 1325 |

Prices UK List ex VAT

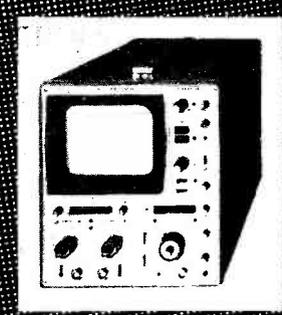

For FULL DETAILS and DISTRIBUTOR LIST Contact


Hameg Ltd.,
74-78 Collingdon St.,
Luton,
Beds.
LU1 1RX.

Tel: (0582) 413 174

Autowah Without Tears

S. N. Goodwin

The main disadvantage of a simple wah-wah circuit is that it requires a manual trigger for the effect, usually provided by a foot-pedal, which needs solid (and often expensive) mechanical construction and also prevents the guitarist from moving freely about the stage. After a couple of hand-made pedal systems collapsed in use, the standard wah-wah circuit was modified as follows: A light dependent resistor was mounted on the soundboard of the guitar about 2 cms from the highest string, pointing out about 1 cm from the front of the instrument. The shadow of the player's hand moving across the guitar triggers the effect — the more light

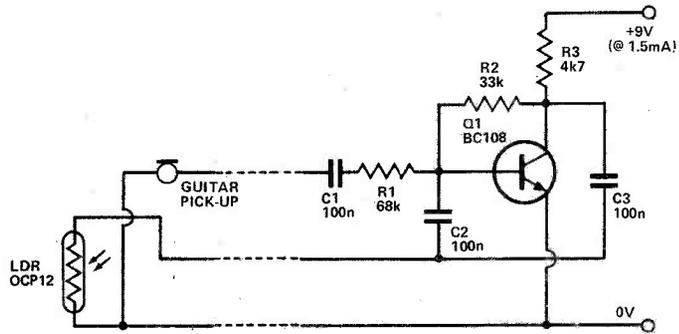

shining on the LDR, the higher the frequency-range boosted by the circuit.

It is tolerant of quite a wide range of light levels and if the range is found to be incorrect this can be rectified in two ways. Lenses or filters can be put across the LDR, or resistors can be connected in series/parallel with it.

Fluorescent lights could give problems with mains hum, but, under normal incandescent lighting, none were experienced. The wire to the LDR should ideally be screened, but over short distances this is not vital. Avoid bending its leads close to the body, as they can be snapped off very easily.

A Simple Sequencer

P. Hill

A simple sequencer can be constructed using shift registers.

A logic 1 is shifted down the shift registers (IC4, 5) outputs, otherwise at logic 0, at each clock pulse. This places a voltage across the variable


resistors RV1 — 16 in turn. A preset DC voltage is thus available at the output, after being buffered by R1 - 16 and IC6 for each clock pulse. A sequence of control voltages can be set up and used to drive a voltage controlled oscillator.

The sequencer is reset by S1. The switch is debounced by IC1a and

IC1b. Resetting zeros all shift register outputs and results in a logic 1 appearing at the input of IC4.

When a clock is applied a positive going edge at pin 8 of IC4 and 5 corresponds to a negative-going edge at pin 1 of IC2, due to inverters IC1c and IC1d. The first positive going edge at pin 8 of IC4 and 5 causes the logic 1 at pin 1 and 2 of IC4 to be transferred to pin 3. Since IC2 is positive edge triggered it's output remains at logic 0, allowing the logic 1 to be transferred to pin 3. On the following negative edge the logic 0 appears at pin 1 and 2 of IC4. For subsequent positive edges the logic 1 is shifted down the shift register outputs and is replaced by the logic 0 at the input.

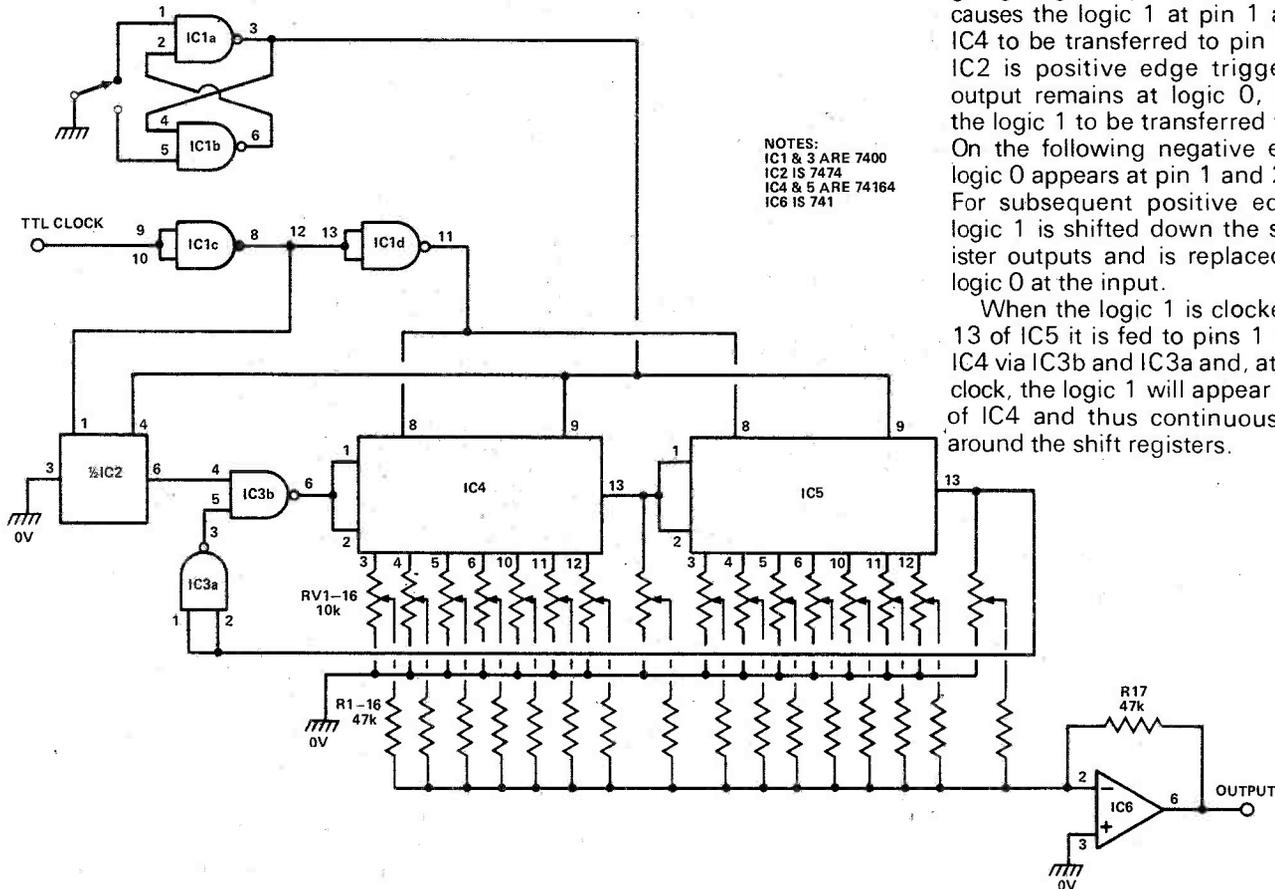When the logic 1 is clocked to pin 13 of IC5 it is fed to pins 1 and 2 of IC4 via IC3b and IC3a and, at the next clock, the logic 1 will appear on pin 3 of IC4 and thus continuously cycle around the shift registers.



NOTES:
IC1 & 3 ARE 7400
IC2 IS 7474
IC4 & 5 ARE 74164
IC6 IS 741

TTLs by TEXAS 7400 11p 74251 140p 4018 85p 7401 13p 74252 250p 4019 45p 7402 14p 74278 290p 4020 100p 7403 12p 74279 110p 4021 110p 7404 12p 74283 160p 4022 100p 7405 14p 74290 190p 4023 22p 7406 14p 74293 160p 4024 55p 7407 14p 74298 200p 4025 160p 7408 14p 74365 100p 4026 130p 7409 15p 74366 100p 4027 50p 7410 15p 74367 100p 4028 80p 7411 21p 74368 100p 4029 80p 7412 21p 74369 100p 4030 80p 7413 30p 74370 200p 4031 200p 7414 30p 74371 200p 4032 200p 7415 30p 74372 200p 4033 200p 7416 27p 74373 200p 4034 200p 7417 27p 74374 200p 4035 200p 7418 27p 74375 200p 4036 200p 7419 27p 74376 200p 4037 110p 7420 17p 74377 200p 4038 125p 7421 17p 74378 200p 4039 250p 7422 22p 74379 200p 4040 100p 7423 22p 74380 200p 4041 80p 7424 30p 74381 40p 4042 90p 7425 30p 74382 40p 4043 90p 7426 30p 74383 40p 4044 90p 7427 34p 74384 40p 4045 110p 7428 367430 74385 40p 4046 110p 7429 74386 40p 4047 100p 7430 74387 40p 4048 95p 7431 74388 40p 4049 95p 7432 74389 40p 4050 45p 7433 74390 40p 4051 80p 7434 74391 40p 4052 80p 7435 74392 40p 4053 80p 7436 74393 40p 4054 150p 7437 74394 40p 4055 150p 7438 74395 40p 4056 135p 7439 74396 40p 4057 600p 7440 74397 40p 4058 115p 7441 74398 40p 4059 115p 7442 74399 40p 4060 115p 7443 74400 40p 4061 115p 7444 74401 40p 4062 115p 7445 74402 40p 4063 115p 7446 74403 40p 4064 115p 7447 74404 40p 4065 115p 7448 74405 40p 4066 115p 7449 74406 40p 4067 115p 7450 74407 40p 4068 115p 7451 74408 40p 4069 20p 7452 74409 40p 4070 20p 7453 74410 40p 4071 22p 7454 74411 40p 4072 22p 7455 74412 40p 4073 22p 7456 74413 40p 4074 22p 7457 74414 40p 4075 22p 7458 74415 40p 4076 107p 7459 74416 40p 4077 107p 7460 74417 40p 4078 107p 7461 74418 40p 4079 107p 7462 74419 40p 4080 107p 7463 74420 40p 4081 22p 7464 74421 40p 4082 22p 7465 74422 40p 4083 125p 7466 74423 40p 4084 125p 7467 74424 40p 4085 125p 7468 74425 40p 4086 125p 7469 74426 40p 4087 125p 7470 74427 40p 4088 125p 7471 74428 40p 4089 125p 7472 74429 40p 4090 125p 7473 74430 40p 4091 125p 7474 74431 40p 4092 125p 7475 74432 40p 4093 125p 7476 74433 40p 4094 250p 7477 74434 40p 4095 250p 7478 74435 40p 4096 250p 7549 74506 40p 4167 250p 7550 74507 40p 4168 250p 			93 SERIES 9301 160p 9302 175p 9308 175p 9310 275p 9311 275p 9312 275p 9314 185p 9316 225p 9321 225p 9322 225p 9334 360p 9335 200p 9370 200p 9374 200p 			VERBOARDS 0.1 0.15 2.5x3.75" (copper clad) 45p 2.5x5" 57p 3.75x3.75" 57p 3.75x5" 64p 3.75x17" 22p 4.75x17" 29p Up to 100 pins Spot face current 85p Pin insertion tool 110p Vero Wiring Pen + 2 wire spools + combs 370p Combs 7p 			TRANSISTORS AC126 25p AC127 25p AC176 25p AC187 25p AF116 25p AD149 70p AU107 200p BC107 11p BC109 11p BC117 11p BC147 8p BC157 8p BC159 11p BC169C 12p BC172 12p BC173 12p BC178 17p BC182/3 10p BC184 11p BC187 30p BC212/3 11p BC214 12p BC227 70p BC337 16p BC338 16p BC481 36p BC487 36p BC547 78p BC547A 78p BC547B 78p BC547C 78p BC547D 78p BC547E 78p BC547F 78p BC547G 78p BC547H 78p BC547I 78p BC547J 78p BC547K 78p BC547L 78p BC547M 78p BC547N 78p BC547O 78p BC547P 78p BC547Q 78p BC547R 78p BC547S 78p BC547T 78p BC547U 78p BC547V 78p BC547W 78p BC547X 78p BC547Y 78p BC547Z 78p 			TRANSISTORS BF259 36p BF399 25p BF440 25p BF441 25p BF442 25p BF443 25p BF444 25p BF445 25p BF446 25p BF447 25p BF448 25p BF449 25p BF450 25p BF451 25p BF452 25p BF453 25p BF454 25p BF455 25p BF456 25p BF457 25p BF458 25p BF459 25p BF460 25p BF461 25p BF462 25p BF463 25p BF464 25p BF465 25p BF466 25p BF467 25p BF468 25p BF469 25p BF470 25p BF471 25p BF472 25p BF473 25p BF474 25p BF475 25p BF476 25p BF477 25p BF478 25p BF479 25p BF480 25p BF481 25p BF482 25p BF483 25p BF484 25p BF485 25p BF486 25p BF487 25p BF488 25p BF489 25p BF490 25p BF491 25p BF492 25p BF493 25p BF494 25p BF495 25p BF496 25p BF497 25p BF498 25p BF499 25p BF500 25p 			TRANSISTORS TIP29C 55p TIP30A 55p TIP30C 55p TIP31A 55p TIP31C 55p TIP32A 55p TIP32C 55p TIP33A 55p TIP33C 55p TIP34A 55p TIP34C 55p TIP35A 55p TIP35C 55p TIP36A 55p TIP36C 55p TIP37A 55p TIP37C 55p TIP38A 55p TIP38C 55p TIP39A 55p TIP39C 55p TIP40A 55p TIP40C 55p TIP41A 55p TIP41C 55p TIP42A 55p TIP42C 55p TIP43A 55p TIP43C 55p TIP44A 55p TIP44C 55p TIP45A 55p TIP45C 55p TIP46A 55p TIP46C 55p TIP47A 55p TIP47C 55p TIP48A 55p TIP48C 55p TIP49A 55p TIP49C 55p TIP50A 55p TIP50C 55p TIP51A 55p TIP51C 55p TIP52A 55p TIP52C 55p TIP53A 55p TIP53C 55p TIP54A 55p TIP54C 55p TIP55A 55p TIP55C 55p TIP56A 55p TIP56C 55p TIP57A 55p TIP57C 55p TIP58A 55p TIP58C 55p TIP59A 55p TIP59C 55p TIP60A 55p TIP60C 55p 			TRANSISTORS 2N3054 65p 2N3055 65p 2N3442 140p 2N3553 240p 2N3565 200p 2N3573 200p 2N3634/4 48p 2N3702/3 12p 2N3704/5 12p 2N3706/7 12p 2N3708/9 12p 2N3713 300p 2N3819 25p 2N3820 25p 2N3823 25p 2N3826 25p 2N3827 25p 2N3830/3 4 18p 2N3905/6 20p 2N4037 65p 2N4058/9 12p 2N4060 12p 2N4061/2 18p 2N4123/4 27p 2N4125/6 27p 2N4130/3 27p 2N4227 90p 2N4271 90p 2N4272 90p 2N4273 90p 2N4400 90p 			TRANSISTORS 2N4000 90p 2N4001 90p 2N4002 90p 2N4268 90p 2N4269 90p 		
--	--	--	--	--	--	---	--	--	--	--	--	---	--	--	--	--	--	---	--	--	--	--	--

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all...

Our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, ICs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100's of prices out of our popular lines including ICs, Transistors, Resistors and many more.


If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-482 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2GD. Tel: 041-332 4173. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

<p>MOTORS. 1.5V Model motors 22P, Sub. min. 3/16 inch 115vdc 3 rpm motor 32p. 12vdc 5 pole model motor 37p. Replacement 6 track 12vdc motors 55p. Gearred motor motors 24 rpm. 7p. 115vdc 4 rpm motor 35p. Cassette motor 5-8vdc ex. equip. 70p. 9VDC Cassette Motor 95p.</p>	<p>RECORDING TAPE. Low noise mylar, unspliced unassd. 7" 1200' £1.00. 7" 1800' £1.45. 10" 3600' £5.00. BLANK CASSETTES. C60 10 for £2.75. C90 10 for £3.85. TAPE HEAD DEMAGNETISER. 240vac curbed probe £2.65. LOW COST 1/4" tape splicer £1.95.</p>	<p>AMPHENOL CONNECTORS (PL259) PLUGS 47p. Sockets 42p. Elbow 90p. Reducers 13p. DUMMY LOADS (PL259) 52ohms 1 watt with indicator bulb 97p.</p>	<p>MULTIMETERS. NH55 2,000 opv., IKV AC/DC, 100MA DC CURRENT, 2 resistance ranges to 1Meg £5.95. HANSEN AT210. 100,000opv., 1.2KV AC/DC, 12 amps AC/DC current, resistance to 200Meg in 4 ranges, capacitance range 200pf-0.2Mfd., 1000ohm, dB range, internal safety fuse, dimensions 160X65X50MM, a good quality meter. £34.50p.</p>	<p>TRANSFORMERS. All 240vac primary (postage per transformer is shown in brackets after price). MINIATURE RANGE 6-0-6v 100ma., 9-0-9v 75ma., 12-0-12 50ma all 70p each (15p). 12-0-12 100ma 99p (15p) 0-6-0 290ma £1.20 (20p). 0-4-6-9v 200ma these have no fixing bracket 70p (15p). 12v 500ma 99p (22p) 12v2A £2.35 (45p) 12v4A £2.85 (45p) 15-0-15v 1A £2.25 (45p) 30-0-30v 1s £2.85 (54p), 20-0-20v 2A £3.65 (54p). 0-12-15-20-50V 2 amp £4.75 (54p) 20v 2.5a £2.35 (54p).</p>	<p>ALUMINIUM PROJECT BOXES. 10 S.W.B. with fitted lid and screws. A81 3/8x2 1/2x1 1/2. A82 4x3x1.5. A83 3x2x1 1/2. A84 6x4x2 1/2. A85 6x4x3 1/2. A86 8x6x4x2 1/2. A87 8x6x3 1/2. £1.25.</p>
<p>BUZZERS. Miniature solid state type. 33x17x15mm. 70db at 3 feet. 15ma drain. 4 types. 6-9-12 or 24v 80p. LOUD 12 volt buzzer 50x30mm 63p. 6PD type adjustable buzzer 6-12 volts 27p. 12VDC SIREN, all metal rotary type, high pitched wail. £8.50.</p>	<p>TOOLS. SOLDER Sucker, good suction, applied unassd. £4.95. Side cutter. £1.45. Pliers 5" £1.45. NEON DRIVER 8" LONG 43p. NHYAMA 16 pin IC test clip £1.85. 6 PIECE precision screwdriver sets, individual handles. £1.05. JUMPER TEST LEAD SETS 10 pairs of leads with insulated cross each and 50p.</p>	<p>19-PIECE PRECISION TOOL KIT. In plastic hinged case. Consists of 5 spanners, 4x2/3mm 5 nut drivers, 30mm, 3 small screwdrivers, 2 Philips drivers, 1awl, 3 Alan Keys. £3.35.</p>	<p>MICRO SWITCHES. Standard button operated 28x25x8mm make or break new 15p each, roller operated version of the latter new 20p each. Light action micro switch. 3 mm make or break 35x20x7mm 12p each. Cherry plunger operated micro switch. 2 norm. open and 2 norm. closed, plunger 20mm long (40x30x18mm) 25p each.</p>	<p>TRIAC XENON PULSE TRANSFORMERS. 11 (6PD style) 32p. 11 plus 1 sub. min. pcb mounting 65p.</p>	<p>DIODES. IN4005 10 for 45p. BY255 10 for 85p.</p> <p>BRIDGE RECTIFIERS. 500V 600ma Ex equp. 12p each. 100V 3 amp stud mounting (new) 35p.</p> <p>ZENER DIODE. 24V 400mw 10 for 35p.</p>
<p>SPECIAL OFFER SEMICONDUCTORS. 2N5062 SCR's 18p. 8X504 opto isolator 25p. CA3130 95p. 78A800 50p. C1060 (400V) SCR 20p. 741 22p. 723 35p. NE555 24p. IM3400 40p. AD161/2 70p pair. 2N5055 36p. IM4005 10 for 35p. 8023B 29p. 8040B 29p. 7413 35p. 2N414 75p. TL305 alpha numeric display £2.50. MANSA 3mm LED displays 45p. Min. LDR's 30p. LEDs 0.2" CLEAR 15p. GREEN 12p. RED 10p.</p>	<p>MICROPHONES. Min. Tin pln. Oni. uses dual ad battery (supplied) £4.95. Low cost condenser ECM105 50ml. 600ohms on/off switch standard jack plug £2.95. EM507 Condenser. unit. 600ohms. 30-18KHz. highly polished metal body. £7.95. DYNAMIC stick microphones dual imp., 600ohms or 20k. 70-15KHz. attractive black metal body. £7.75. EM506 Condenser. cardiod. unit. 500ohms or 50k. heavy chromed copper case. £12.95. DYNAMIC P.A. Mike, mobile radio etc. Hmb switch 50k imp. £3.75. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT crystal replacement 35x10mm 40p. GRUNDIG Electret insert, with built in FEY preamp 3-6vdc. £1.00.</p>	<p>TAPE HEADS. Mono cassette, £1.75. Stereo cassette £3.90. Standard 6 track stereo £1.95. BSH MM 1330 4 track 50p. BSR SRP90 4 track £2.10. TD10 dust head assembly 2 heads both 1/2 track R/P with built in erase £1.25.</p>	<p>ROCKER SWITCHES. 2 amp SPST single hole fixing, various colours (red, black, yellow, green, white) 19p each. 250vac 6 amp white rocker. 21x15x13mm 17p each.</p>	<p>PROJECT BOXES. Heavy ABS black plastic boxes with brass inserts and lid. 75x50x35mm 54p. 95x70x35mm 65p. 115x9x37mm 75p.</p> <p>VERO HAND HELD BOX. White ABS. 24in x 3.7 in tapered, with screws 68p each.</p> <p>VERO POTTING PLASTIC. Boxes with lid and screws 70x50x20mm. White or black. 43p each.</p>	<p>RANK ARENA stereo cartridge pre-amplifier modules, suitable for Magnetic cartridges, new, supplied with connective details. £1.95.</p>
<p>NEW STOCK ITEM — We are now stocking Expo mini hand held drills, these are a precision British made tool, ideal for P.C. board drilling, model makers etc. They operate on 12V DC. Drill kit supplied in plastic hinged case, with drill and 21 accessories, drills, sanders, reamers, buffers, etc. complete kit only £14.25</p>	<p>SEND G.S. ETCHING KIT SYSTEM. Unique idea for etching P.C. boards, off done in a sealed bag, supplied with everything needed for etching P.C. boards, will etch approximately 1600cm of copper board. £2.10.</p>	<p>SWITCHES. Sub. Min. Toggle. SPST 8x5x7mm, 52p. DPDT (8x7x7) 62p. DPDT Centre off (12x11x9mm) 77p.</p> <p>PUSH SWITCHES (16x6mm) red top, push in make 15p each, push on break version black wavy 17p each.</p> <p>SLIDE SWITCHES all DPDT 15x8x12mm 13p. 16x11x9mm 13p. 22x13x8mm 13p. 22x13x6 centre off 14p. Multipole slider double wctch (12 tag) 29x9x11mm 25p.</p>	<p>RELAYS. Encapsulated reed relay 1,000 coil, 9-12vdc, single make, 0.1 matrix mounting 35p. Moisture encapsulated reed relay, 0.1 matrix mounting, single make operated on 12vdc 50p. Continental series, sealed plastic case type. 24vdc, 3 pole c/c 5 amp contacts, new 65p. 230vac Sealed Relay, 3 pole 5 amp contacts, ex. equipment, 11 pin base. 60p each. Metal Cased relay 50x45x17mm has 4 heavy duty make reed inserts, operates on 12vdc 35p each.</p>	<p>CLIFF CLUCKTEST. 13 amp mains connector, ideal for workshop, etc., provides rapid and safe mains connection, tough moulded case and lid with some indicator and fuse £5.15.</p> <p>PUSH BUTTON T.V. TUNERS (not varicap) transistorised U.F. new £2.25.</p>	<p>FINNED HEATSINKS. Supplied anodised 4mm thick. 27mm high. 75x124mm 60p. 150x124mm 95p. Smaller version 2.7mm thick. 75x108mm 48p. TRANSISTOR SOCKETS, T05 or T018 9p each.</p> <p>MURATA SEMICONDUCTORS, REC. SENDER. MA401L 40KHz £3.50 pair.</p>
<p>Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for new illustrated lists.</p>		<p>PROGRESSIVE RADIO 31 CHEAPSIDE, LIVERPOOL L2 3JD ALL ORDERS DESPATCHED BY RETURN POST</p>			

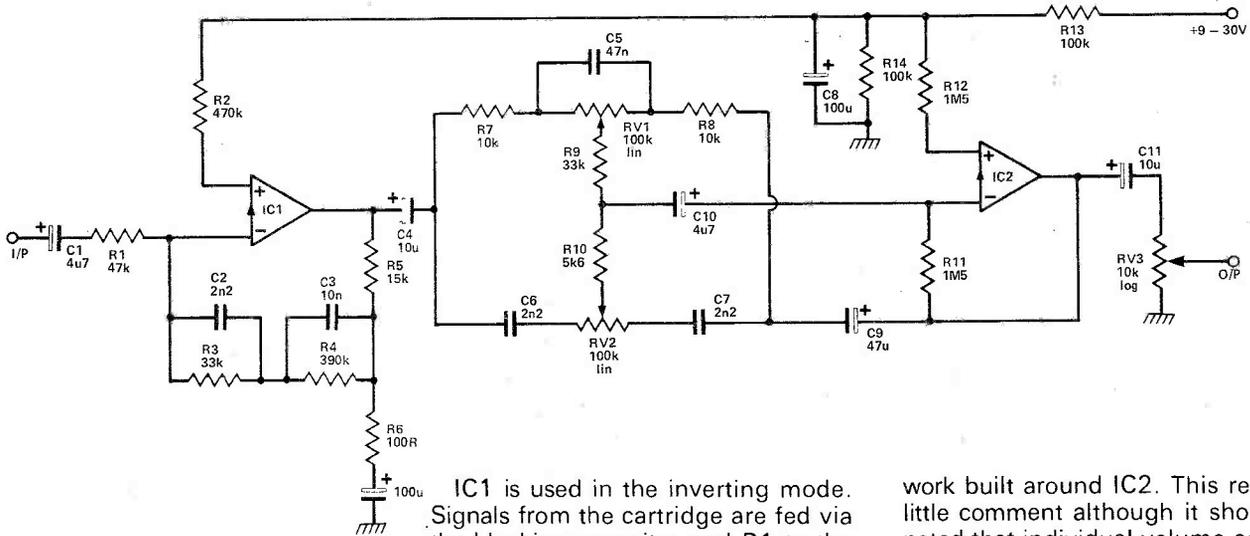

One Chip Preamplifier

J. P. Macaulay

The circuit shown utilises the four Norton op amps contained within an LM3900 to produce a high quality stereo preamp, catering for magnetic cartridges.

IC1 is used in the inverting mode. Signals from the cartridge are fed via the blocking capacitor and R1 to the inverting input. R1 defines the input impedance and provides the right damping for the cartridge.

R5 and R6 define the midband gain of the stage whilst the network R3, R4, C2 and C3 provide the required RIAA equalisation. From here the equalised signal is fed to a standard Baxendall tone control net-

work built around IC2. This required little comment although it should be noted that individual volume controls are employed for each channel. This not only reduces crosstalk between channels but also works out cheaper in that only two single gang potentiometers are used.


Performance is good with overall distortion below 0.1% and a S/N ratio of -67db unweighted, ref 500 mV out.

2 Chip Electronic Dice

P. Adams

This electronic dice produces a true dice display using only two IC's — a 74132 and a 7495. The 7495 is a 4-bit parallel-access shift register. It can either operate as a shift-register or be parallel (broadside) loaded at inputs A-D. Control over these two functions is by a mode control input. When the mode is high data is loaded into Qa — Qd from inputs A - D on the next negative-going clock edge. When the mode is low data is shifted on Qa — Qd on the next negative-going clock edge.

By connecting the mode control to Qa so that the register alternates between load and shift and making the input word a function of the existing output word, with some simple logic, the register can be made to execute a count that will drive LEDs in a dice display. Note LEDs are lit when outputs are low. IC1a is connected as a conventional Schmitt oscillator providing clock pulses to the register. SW1 stops the oscillator and halts the count. On switch-on the register may start on an invalid count, but in a couple of clock cycles it will produce a valid count and then remain in that sequence.



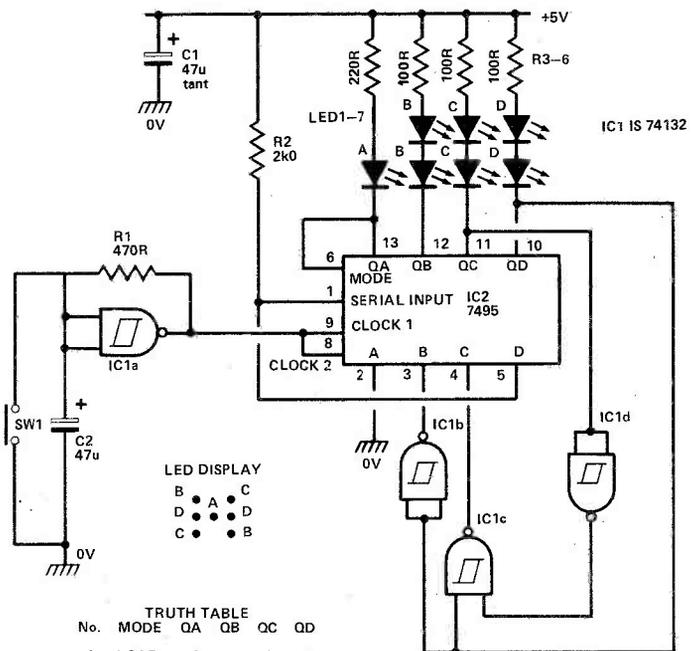






LED DISPLAY
 B • A • C
 D • • • D
 C • • • B

TRUTH TABLE					
No.	MODE	QA	QB	QC	QD
1	LOAD	0	1	1	1
2	SHIFT	1	0	1	1
3	LOAD	0	0	1	1
4	SHIFT	1	0	0	1
5	LOAD	0	0	0	1
6	SHIFT	1	0	0	0
1	LOAD	0	1	1	1
ETC					

PCB FOIL PATTERNS

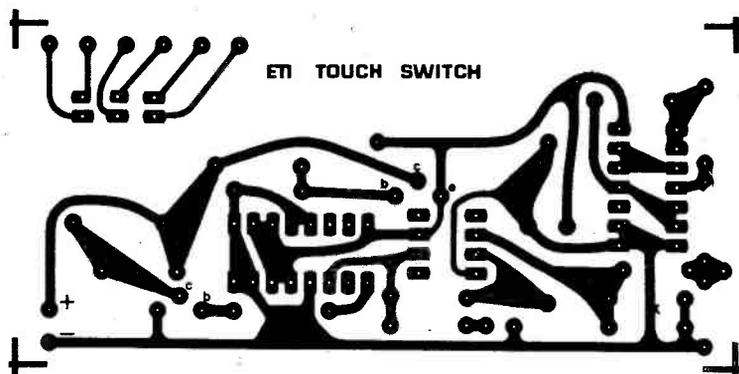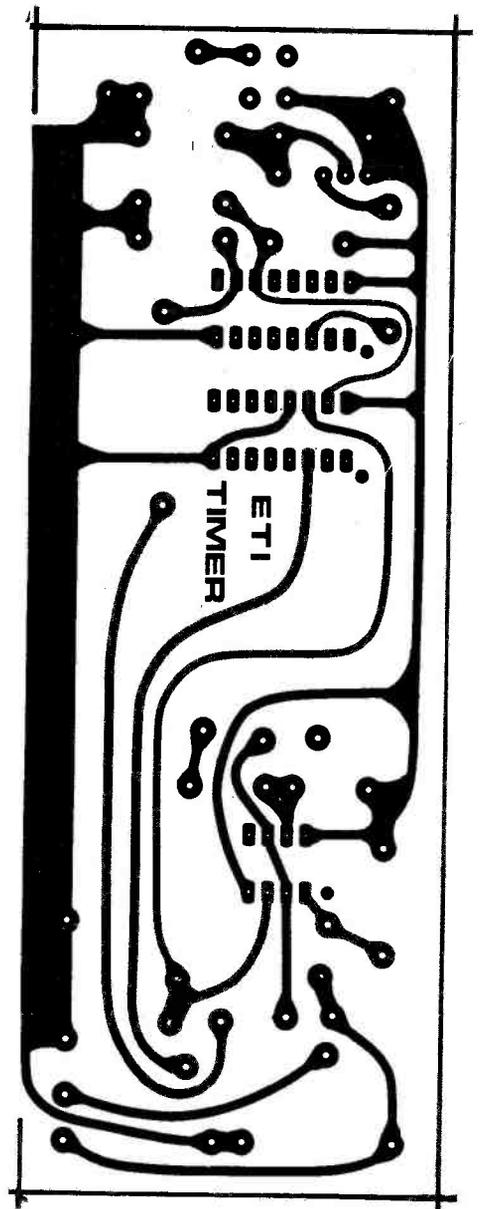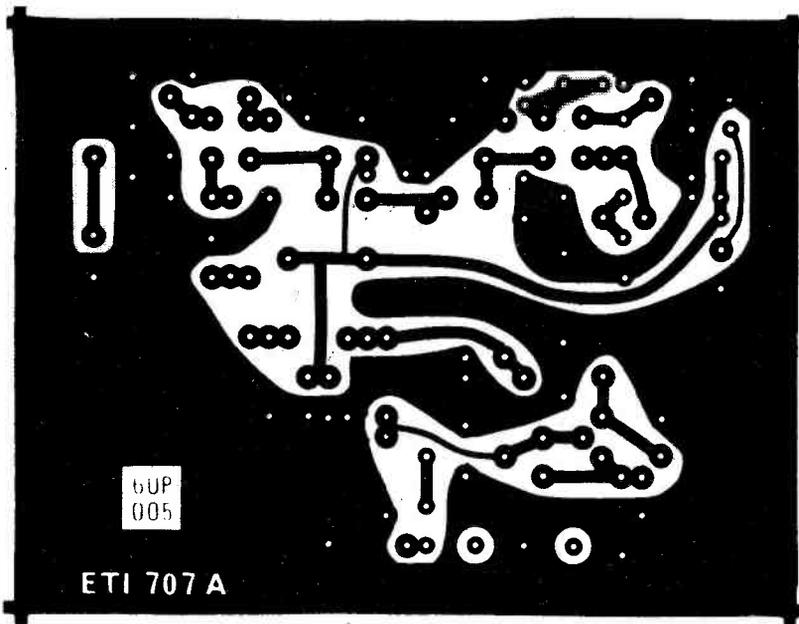We didn't have room in this issue to pack in all the foil patterns. Never fear, if you're anxious to get started on your PCBs, send us a large sae and they'll be on their way to you. If you can bear to wait until next month's issue, we'll find a little space somewhere for them. Rest assured, they will all appear on Etiprints.



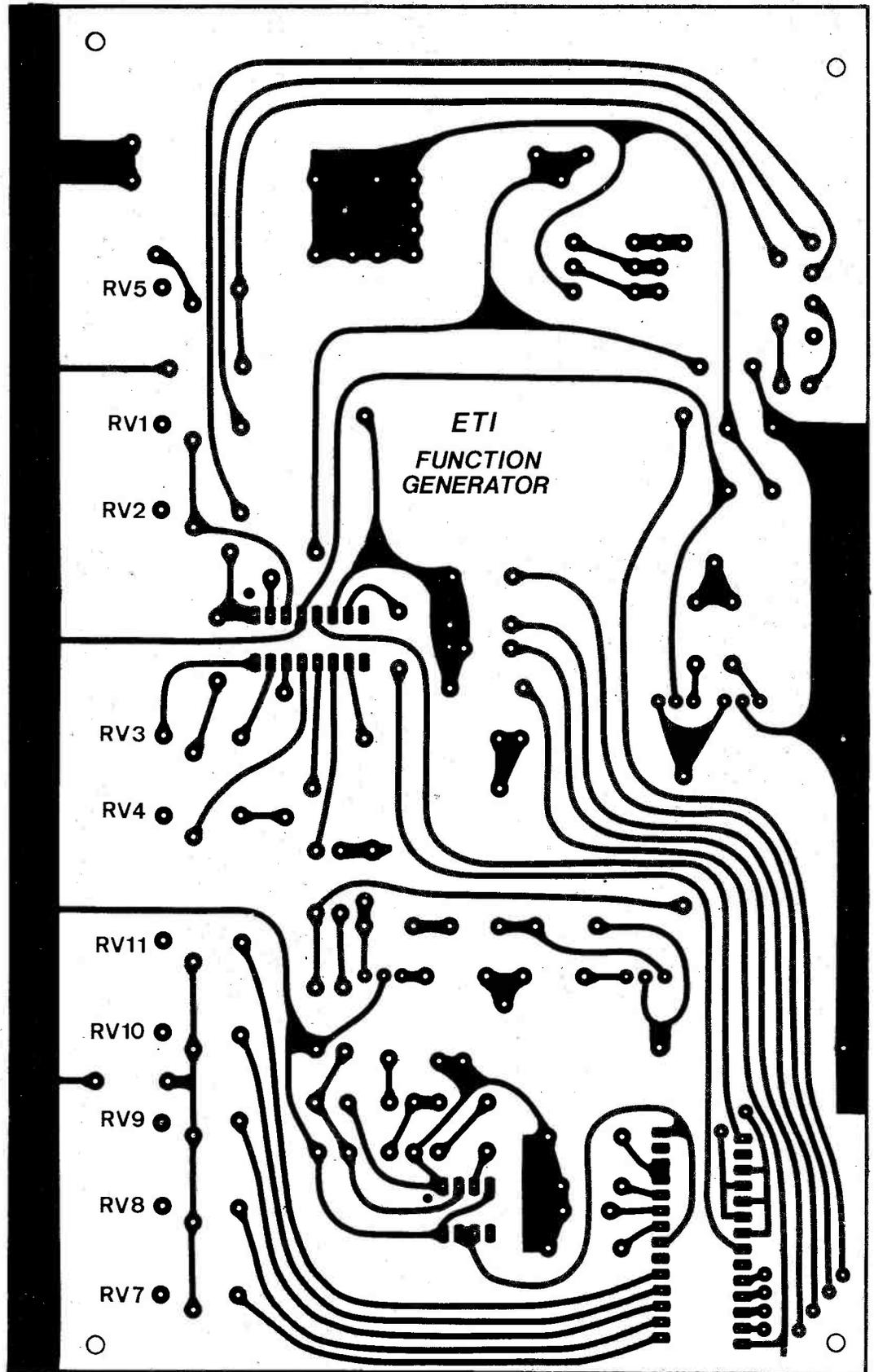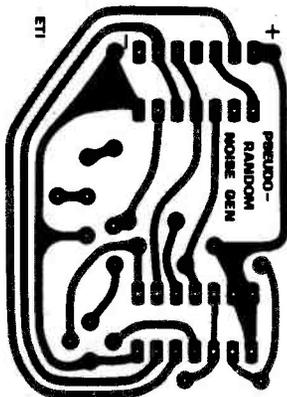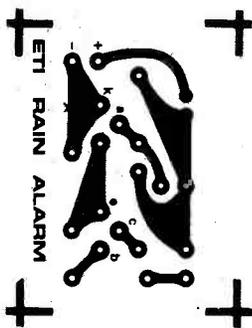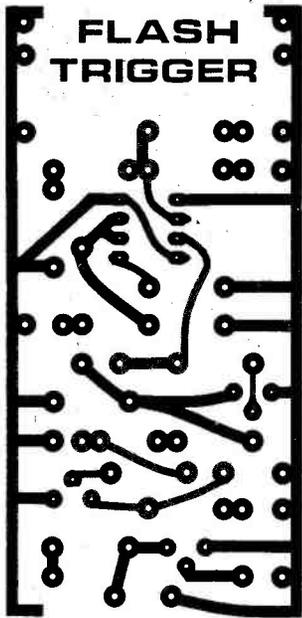

Here's why you should buy an I.C.E. instead of just any multimeter

- * Best Value for money.
- * Used by professional engineers, D.I.Y. enthusiasts, hobbyists, service engineers.
- * World-wide proven reliability.
- * Low servicing costs.
- * 20K/volt sensitivity and high accuracy.
- * Large mirror scale meter.
- * Fully protected against overload.
- * Large range of inexpensive accessories.
- * 12 month warranty, backed by a full after sales service at E. B. Sole U.K. Distributors.

Prices from £16.60 —
£32.00 + VAT



I.C.E.

ELECTRONIC BROKERS LIMITED
49-53 Pancras Road, London NW1 2QB.
Tel: 01-837 7781. Telex: 298694.

Please send me full colour leaflet and prices on whole ICE range including accessories.

Name

Address

ETI



Microcomputers are coming - ride the wave! Learn to program

Millions of jobs are threatened, but millions more will be created through the microcomputer revolution. Will YOU sink or swim? Be one of the people who welcomes computers and the end of boring jobs.

Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency - all you need to start with is a knowledge of simple arithmetic and the use of decimals. And you don't need a computer.

This unique course comes as four A4 books, written by three authors well-known in the fields of microcomputing, self-instruction and writing clear English. In 60 straightforward lessons you learn the five essentials: problem definition, flowcharting, coding the program, debugging, and preparing clear documentation.

Every lesson has thought-provoking questions and we never ask for mindless drudgery. You will know that you are mastering the material and feel a rare satisfaction. Harder problems are provided with a series of graded hints, a unique and really helpful approach. So you never sit glassy-eyed with your mind a blank. First time through, you may need to read most of the hints, but you will soon learn to tackle tough programming tasks - such as writing programs for computer games, preparing graphs on an output printer, calculating compound interest tables and estimating costs.

COMPUTER PROGRAMMING IN BASIC £7.50

Book 1 Computers and what they do well; READ, DATA, PRINT; powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT; RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

FORTRAN COLORING BOOK £5.40

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

A.N.S. COBOL £4.40

Covers the most widely used computer language in business today. It teaches how to write a COBOL program and compile it effectively, paying proper attention to spelling, punctuation, and format.

THE ALGORITHM WRITER'S GUIDE £3.40

FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

The Algorithm Writer's Guide

explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

Cambridge Learning Enterprises

Understand Digital Electronics

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £6.50

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

- Book 1 Binary, octal and decimal number systems; conversion between number systems.
- Book 2 AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables.
- Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates.
- Book 4 R-S and J-K flip flops; binary counters, shift registers and half adders.

DESIGN OF DIGITAL SYSTEMS £10.50


Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

- Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2 OR and AND functions; logic gates; NOT, exclusive-OR NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

O-LEVEL ENGLISH LANGUAGE £6.50

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on COMPREHENSION, Book 2 covers SUMMARY, PUNCTUATION & SPELLING, and Book 3 coaches you in the principles of COMPOSITION. Size: 3 A4 volumes totalling 250 pages.

SELF-INSTRUCTION COURSES

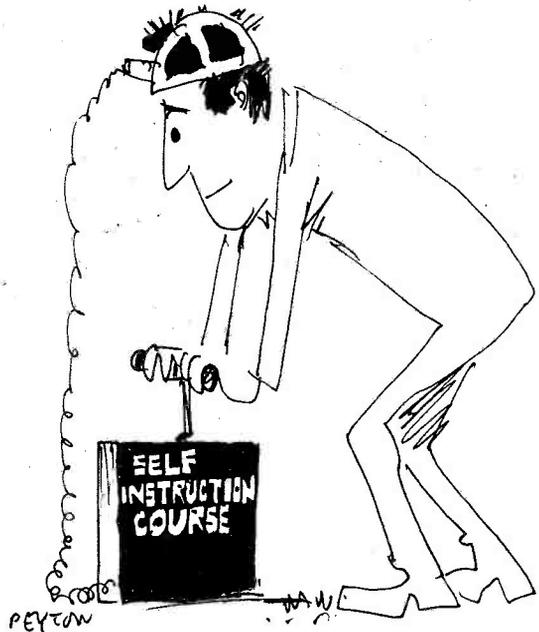

CAMBRIDGE LEARNING ENTERPRISES, UNIT 14
RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON,
CAMBS PE17 4BR, ENGLAND.
TELEPHONE: ST. IVES (0480) 67446

All prices include worldwide postage (airmail extra)
If order comes to £15 or more, deduct £2
Please allow 21 days for delivery

GUARANTEE No risk to you.

If you are not completely satisfied your money will be refunded.

Please send me the following books:

- Computer Programming in BASIC (4 books) at £7.50
- The BASIC Handbook at £11.50
- FORTRAN Coloring Book at £5.40
- A.N.S. COBOL at £4.40
- Algorithm Writer's Guide at £3.40
- Digital Computer Logic & Electronics (4 books) at £6.50
- Design of Digital Systems (6 books) at £10.50
- O-Level English Language (3 books) at £6.50

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my

*Access/Barclaycard/Visa/Eurocard/Mastercharge/Trustcard
account no. (*delete where applicable)


Signature.....

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers (inc. Eire) should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

Name

Address

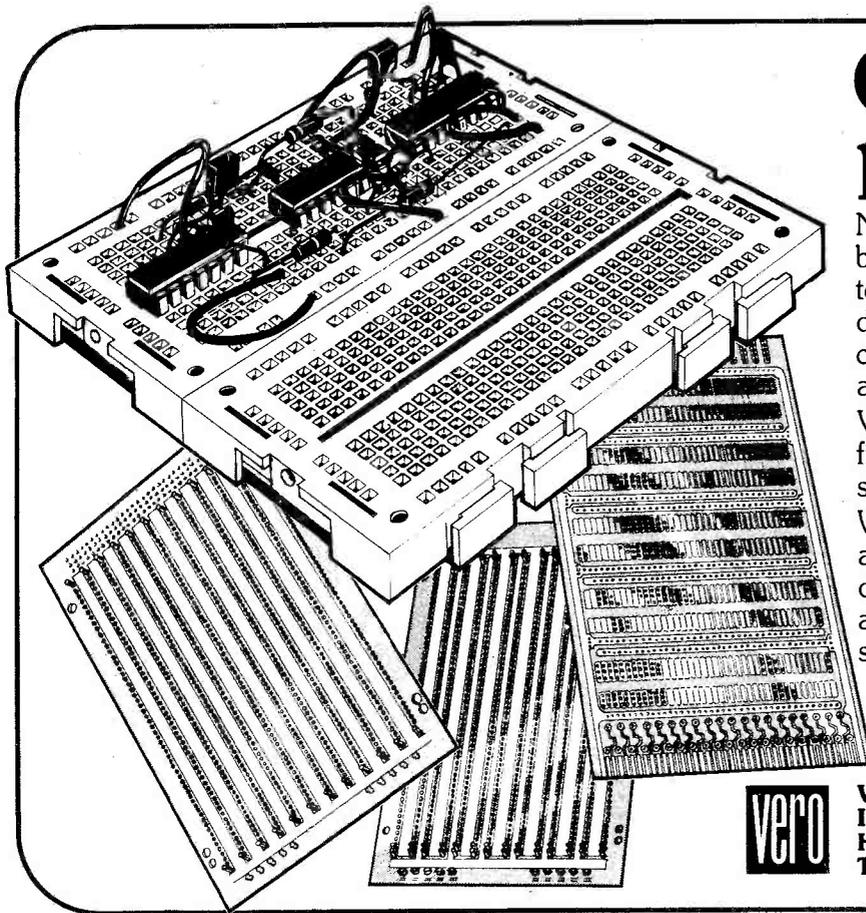Cambridge Learning Enterprises, Unit 14, Rivermill Site,
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England.



Circuit prototyping

Now you can get a prototyping block from Vero for building and testing circuits. It is designed to dovetail together to form a continuous 2,54 pitch so you can put any size of IC on it.

Verobloc is supplied singly but if you fit three together it gives a Eurocard size area for your circuits.

When you've designed your circuit and it comes to building the project don't forget Veroboards are available in a range of sizes and styles to suit every application.



VERO ELECTRONICS LTD RETAIL DEPT.
 Industrial Estate, Chandler's Ford,
 Hampshire SO5 3ZR
 Tel: (04215) 62829



IT'S A DOGS LIFE!

Mighty mongrel strikes again!

Stop your powerful pooch carving up your carefully collected ETIs with his canine choppers and live in hardback harmony with a profusion of precious project books by armour-plating your archives.

Invest in an ETI binder. You know it makes sense.

You can have any colour you like as long as it's black.

Send a mere £3.20 to:
 ETI Binder
 145 Charing Cross Road
 London WC2H 0EE

8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

KANSAS CITY

low error rate tape interface.



2 MICROPROCESSORS

Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10⁻⁹⁹ to 9 x 19⁹⁹ to 8 figures plus 2 exponent digits.

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

resident in EPROM.

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.

COMPLETE KIT

**ONLY
£275.00
+VAT**

Kit also available as separate packs: e.g. PCB, Keyboards, Cabinet, etc.

Cabinet size 19.0" x 15.7" x 3.3". Television by courtesy of Rumblelows Ltd., price £58.62

POWERTRAN

PSI Comp 80. Z80 Based powerful scientific computer
Design as published in *Wireless World*, April-September, 1979.

The kit for this outstandingly practical design by John Adams being published in a series of articles in *Wireless World* really is complete!

Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer, 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.

PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion socket is made via a ribbon cable.

Mother board:	Fibre glass double sided plated through hole P.C.B. 8.7" x 3.0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug	£39.90
8K Static RAM board	Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" Set of components including IC sockets, plug and socket but excluding RAMs	£12.50 £11.20
	2114L RAM (16 required)	£5.00
	Complete set of board, components, 16 RAMs	£89.50
8K ROM board	Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" Set of components including IC sockets, plug and socket but excluding ROMs	£12.40 £10.70
	2708 ROM (8 required)	£8.00
	Complete set of board, components, 8 ROMs	£78.50

Floppy Disk, PROM programmer and printer interface coming shortly!


Value Added Tax not included in prices

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until January 31st, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subsequent to 15% surcharge for VAT. No charge is made for carriage. *Or current rate if changed.

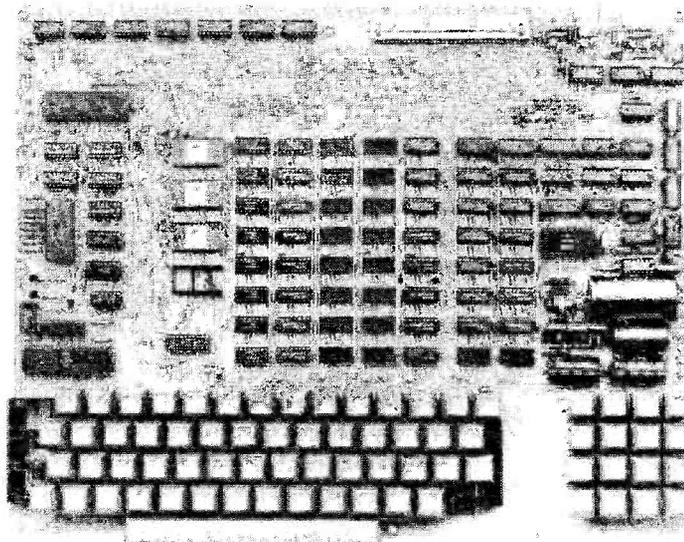SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.



UK Carriage FREE

POWERTRAN COMPUTERS

(a division of POWERTRAN ELECTRONICS)

PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NM

ANDOVER
(0264) 64455

WE STOCK THE PRODUCTS OF

EAGLE **KNIPEX** **NEWNES**
WELLER **SERVISOL** **JAYBEAM**
DRAPER **BARNARD'S** **LIDEN PLASTICS**
SPIRALUX **& BABANI** **GREENPAR**

B. BAMBER ELECTRONICS

5 STATION ROAD
 LITTLEPORT, CAMBS.
 PHONE: (0353) 860185

1980 Electronics Catalogue now available price 75p + 20p postage. If you send £1.55 you will receive our Catalogue plus six bi-monthly Short-form Catalogues to keep you up to date with prices and special offers.

B.K. ELECTRONICS

AM/FM Stereo Tuner Amplifier chassis (originally designed for installation into a music centre) Ready built, comprising of a tuner/pre-amp. board, and separate power supply/power-amp. board.

Note: Interconnection wiring diagram supplied.

Rotary Controls: Tuning, on/off volume, balance, treble, bass.

Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), LW, MW, SW.

Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.

Frequency Response: 60Hz-20KHz within ± 3 dB.

Tape Sensitivity: Output — typically 150 mv. input — 300 mv for rated output.

Disc Sensitivity: 100 mv (ceramic cartridge)

Radio: FM (VHF) 87.5MHz-108MHz.

Long Wave 145KHz-265KHz.


Medium Wave 520KHz-1620KHz.

Short Wave 5.8MHz-16MHz.

Size: Tuner — 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. x 7 $\frac{1}{2}$ in. Approx. Power Amp — 2in. x 7 $\frac{1}{2}$ in. x 4 $\frac{1}{2}$ in. Approx.

240 volt AC operation. Complete with circuit diagram.

Price — £22.00 + £2.50 P&P.

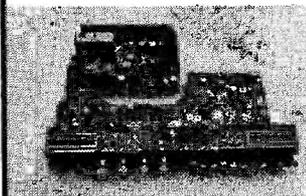

Stereo Cassette Tape Deck Assembly.

Comprising of a moulded top panel assembly and tape deck mechanism coupled to a record/play back printed board assembly, for installation into cabinet of own choice (separate power amplifier required).

Specification: Pause control, solenoid assisted auto stop, 3 digit tape counter, DC motor with electronic speed control, twin Vu meters, normal/chrome tape switch, twin Mic input sockets, AC erase system.

Tape Speed: 4.8 cms/sec.

Input Sensitivity: For 0dB ref. level 0.25mv \pm 3dB

Input Impedance: 2.2K Ohms.

Output Level: To both left and right hand channels 160 mv \pm 2dB.

Output Impedance: <6.8K Ohms.

Signal/Noise ratio: 45 dB (Nominal).

Harmonic Distortion: 2% (Nominal).


Note: Power supply requirements 9 volt AC and 24 volt AC transformer *not* supplied.

Size: Tape Mechanism 4 $\frac{1}{2}$ in x 6 $\frac{1}{4}$ in x 1 $\frac{1}{4}$ in.

Approx. Top Panel 13 $\frac{1}{4}$ in. x 9 $\frac{1}{4}$ in. Approx.

Price — £25.00 + £2.50 P&P.

Mail Order Only

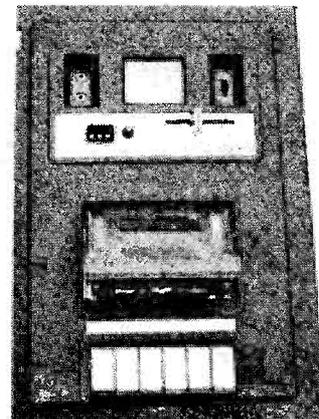

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex

A new edition from Newnes Technical Books

Questions and Answers Integrated Circuits

Second Edition

R. G. Hibberd

Covers in easy-to-follow Q & A format, all main types of integrated circuits. A new chapter on microprocessors and their application has been added for this new edition.

1979

108 pages

£1.55

(US \$3.50)

In the same series

Q & A Electronics, Clement Brown

Q & A Hi-Fi, Clement Brown

Q & A Radio Repair, Les Lawry-Johns

Q & A Radio and Television — Fourth

Edition, H. W. Hellyer and I. R. Sinclair

£1.55 each (US \$3.50)


For further information please send for a free colour brochure describing these and many other publications.



Newnes-Butterworths

Borough Green, Sevenoaks, Kent TN15 8PH Tel: (0732) 884567

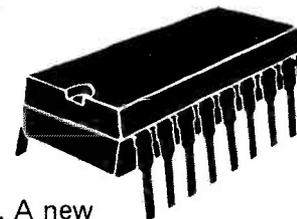Butterworths have companies in Australia, Canada, New Zealand, South Africa and the USA, where local prices apply



CLASSIFIED INFORMATION

Semi-Display:—

1-3 insertions — £6.00 per single column centimetre
 4-11 insertions — £5.50 per s.c.c.
 12 insertions — £5.00 per s.c.c.

Classified:—

23 pence per word (minimum 25 words)
 Box number £1.00 extra

ALL ADVERTISEMENTS IN THIS SECTION MUST BE PRE-PAID

Closing date: 1st Friday in month preceding publication.


Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

Cheques and postal orders should be crossed and made payable to 'Electronics Today International.'

CLASSIFIED ADS, E.T.I., 145 CHARING CROSS ROAD, LONDON WC2H 0EE. (TEL: 01-437 1002).

STOP PRESS: Superboard Compatible!

COLOUR YOUR NASCOM!

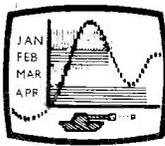

DAZZLING COLOUR GRAPHICS FOR NASCOM 1

Genuine bit-addressable "pixe" system for straight-forward programming of pictorial or mathematical functions.

8 Colour display plus 8 colour independent background facility. Full documentation with FREE SOFTWARE: powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems — send us diagrams etc of your b & w video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.

NOW AVAILABLE FOR LIMITED PERIOD AT **£45** Inclusive of VAT and postage.


WILLIAM STUART SYSTEMS LTD

Dover House, Billerica Road, Herongate, Brentwood, Essex CM13 3SD
 Telephone: Brentwood (0277) 810244

MICROBITS MEMORY OFFER. Special purchase of fully tested and guaranteed 2708s, £6.90 each + VAT (while stocks last), including postage/packing. Phone your order to Camberley (0276) 34044, or write: 34B London Road, Blackwater, Camberley, Surrey.

PRECISION SHEET METAL work chassis, panels, etc. Steel, stainless or aluminium, long/short runs, good deliveries. E.E.S. Limited, Clifford Road, off Monks Road, Exeter 36489. Telex: 42401.

ORGANISE YOUR COMPONENTS!

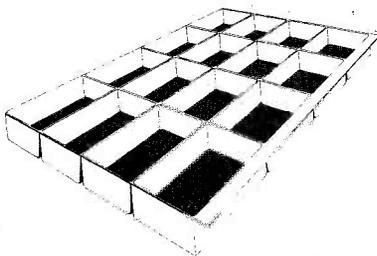

COMTRAYS

Store resistors, capacitors, IC's, screws, etc. Ideal for organising your project components — saves all that searching around while constructing. Plastic trays with 16 compartments, each compartment 3/4 x 2 1/4 x 1 1/2 ins. deep.

£1.90 each, including p.p. and VAT
 Four for £6.95 (64 compartments)
 Eight for £12.60 (126 compartments)

Cheque or P.O. to:

HELISTAR SYSTEMS LTD.
 150 WESTON ROAD
 ASTON CLINTON
 AYLESBURY, BUCKS HP22 5EP
 Tel. Aylesbury 630364

50Hz SUPERBOARDS BRITISH MODEL

from **£190** + VAT
 Fully built, set up and tested

AUTHORISED dealer back-up

C.T.S., 1 Higher Calderbrook
 Littleborough, Lancs.
 Tel. Littleborough 79332 any time

SOUTH WALES

FOR

**TTL, CMOS, LINEARS
 DISCRETES, PASSIVES
 HARDWARE, TOOLS
 CASES, TRANSFORMERS,
 ETC.**

**CLOCKS
 LEKTROKIT
 BREADBOARDING AND
 VERO DEALERS**

Mail and Official Orders accepted

Come to:

**STEVE'S ELECTRONICS
 15/17 THE BALCONY
 CASTLE ARCADE
 CARDIFF CF1 2BU
 TEL: (0222) 41905**



INTRODUCTION TO MICROPROCESSORS AND COMPUTING.

50 pages of diagrams and explanation to get you started. Price £2.30 + 45p postage.

EDUCATIONAL DATA AND TECHNICAL SERVICES

59 Station Road, Cogenhoe, Northampton NN7 1LU

A QUALITY STEREO POWER AMPLIFIER offer for Christmas.

Stab'd PSU 2N3055 output — stereo 60w; RMS, IC Preamp. Case inc., controls vol., select, etc., din output / inputs for mag. p.u. / mike (3 Mv) + tuner + aux., 26 trans — 2 i.c. Screened xformer; 240v. A.C. mains lead. New + data £19.95. KLIFCO ELECTRONICS, 1 Regent Road, Ilkley, W. Yorks. LS29 9EA.



READING: 15.7 nF!!

DCM 1pF-2µF in 5 ranges. On-board switch, precision resistor network and 0.8" leds give direct readout in pF, nF and µF. Basic acc. 0.5%. Assembled and tested. ONLY £21.95 inclusive. Case available separately. Precision Measurements P.O. Box 70, St Stephens Ct., Canterbury CT1 2UU. (Callers by appointment only).

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.


Selected range of popular components Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices P.C. Boards to individual designs Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Alfac range of etch resist transfers, and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
 MASON'S ROAD
 STRATFORD-ON-AVON
 WARWICKS. Tel. 4879

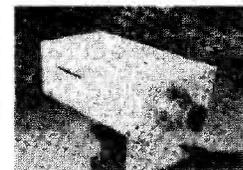TGS GAS SENSORS 812 & 813. Send addressed envelope 6 1/2" x 9" for Tech. Data and Prices. Design service also available. Asti Supplies Ltd., Shannon, Co. Clare, Ireland.



CCTV CAMERA

£114.99 + P/P £3.45
 Optional extra manual £6. Total £124.44.

**BEST OFFER EVER
 Camera Kit, Lens,
 Vidicon & Modulator**

CROFTON

Tel: 01-891 1923 For full details

VIDEO MUSIC



Videograph II links to the aerial socket of your tv and provides a full colour **GIANT** oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. **Plus** — full details for testing your audio system for transient distortion, crosstalk etc.

Complete Kit only £26.95 **Luxury cabinet and controls. £12.95**

READY BUILT UNIT £49.95 + £1.00 P&P

WILLIAM STUART SYSTEMS LTD
 Dower House, Billericay Road, Horngate, Brentwood, Essex CM13 3SD
 Telephone: Brentwood (0277) 810244

LOGEX ELECTRONICS / RECRUITMENT SERVICE

If you are considering a new career for the 1980s utilising your digital/analogue/RF qualifications and experience, you should be looking now. You are invited to register with us to take advantage of the wide range of jobs becoming available. We specialise in Field Service, Commissioning and Installation in such industries as Computers (commercial and industrial applications), Communications, NC/CNC, CCTV, etc. Write or telephone for details of our free service. **Logex 309, High Road, Loughton, Essex. 01-502 1589 and 01-464 7714, ext. 502** (24 hr. Readycall secretarial service).

CIRCUIT DESIGN, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems: Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

ETI P.C.B.'s

Buy it with Access

Available for most ETI projects from day one of ETI, phone your order.

SPECIAL OFFER—Single-sided Pax PCB mat, four off, 4 3/4" x 6 1/2", 99p all up

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM MIDDLESEX TW1 4AD · Tel: 01-891 1923

INTENSIVE WEEKEND COURSES IN BASIC

including hands-on mini computer operation.

This short intensive course is intended to instruct from minimal knowledge to an operational capability of computer programming in BASIC high level language. The course is fully residential from Friday evening to Sunday afternoon. Option of non-residential weekend, week-day evening and weekday courses available if required.

For further details of dates available, fees, etc.:

Phone (0401) 43139, or write to:
 Dept. ETI
CLEVELAND BUSINESS SERVICES
 Cleveland House, ROUTH
 Beverley, North Humberside

COLOUR MODULATOR

Kit **£9.95** FOR ALL TV GRAPHICS!
 Red, Green, Blue inputs (can be mixed). Available now: Nescom Colour Kit. £45.00 inc. Graphics Software.

WILLIAM STUART SYSTEMS
 Dower House, Billericay Road, Horngate, Brentwood, Essex CM13 3SD Tel: (0277) 810244
 Barclaycard / Access welcome

Electronic kits for the thrifty!

Build 50 interesting Projects on a P.C. Chassis with surplus components from your "Spares-Box."

EXPERIMENTER'S PRINTED CIRCUIT KIT

Contents: 4 small boards to suit the enclosed designs. Etching Powder, Resist Paint, Solvent, Degreaser and Etching Instructions; also 50 Circuit diagrams, Chassis Plans and Layouts for simple Crystal Sets, Transistor Radios, Transmitters, Amplifiers, Intercoms., Radio Control, Metal Detector, Photoelectric and Ultrasonic Alarms, "Perpetual Motions", Light-Beam Telephone Instruments, Testers, Gadgets, etc., you can build at negligible cost with "Surplus" or reclaimed parts and transistors you already have.
 Price: £1.70. Postage and Packing 30p.

PHOTOELECTRIC KIT

A kit of basic parts to build a simple I.R.-sensitive Photoelectric Switch. Contents: Phototransistor, Transistors, Diode, Resistors, Connector, Latching Relay, Chassis Board, Case, Screws and full instructions.
 Price: £4.50. Postage and Packing 50p.

OPTICAL KIT

A kit of parts to build an I.R. folded-beam Projector and Receiver to suit the above kit. Contents: 2 Lenses, 2 Mirrors, 2 45-deg. blocks, Infra-Red Filter, Lampholder, Building Plans. Price: £3.70. Postage and Packing 30p. Both kits together make an Invisible-Beam Alarm.

EXPERIMENTAL ELECTRONICS
 335 Battersea Park Road, London SW11 4SL
 Send SAE for full details of all kits and circuits

MSF CLOCK

NEW! Shows Date, Hours, Minutes, Seconds. 8 digit LED — larger digits for Hours and Minutes, also parallel BCD output, auto-reset after power failure, auto GMT/BST and leap year. 5x8x15cm, built-in antenna, TIME SIGNAL accuracy. **£48.80.**

60KHz MSF Receiver, serial data output. **£13.70.**
V.I.F.? EXPLORE 10-150KHz Receiver **£10.70.**

MAKE UP YOUR OWN TUNES on a Programmable Chime — new carol each day? **£23.50** less speaker.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc. money back assurance so SEND off NOW.

CAMBRIDGE KITS
 45 (TZ) Old School Lane, Milton, Cambridge

ELECTRONIC TECHNICIANS Grades 3 and 4 required to assist in the construction, modification and maintenance of electronic equipment for use in teaching and research carried out in the Psychology Dept. of U.C.L. The work is varied and interesting and covers a wide range of analogue and digital techniques. ONC, C&G or equivalent required. The Grade 3 technician could have an electrical/mechanical background. Salary in range Grade 4: £3432-£3950; Grade 3: £3122-£3553, plus £524 London Weighting (under review). Application form from Personnel Officer (technical Staff CK3), University College London, Gower Street, London WC1E 6BT.


TOP QUALITY 1N4148 specification diodes: 150, 500, 1000 for £1, £3, £5. **RESISTORS** (5% C.F.) 20p per packet of 50. Following values only 270R, 1k, 3k9, 15k, 20k, 27k, 100k, 470k. Post free from D Johnston, 12 Balgillo Road, Dundee DD5 3LU.

URGENTLY WANTED. ETIs April, May, November 1972. Good price paid. T. Sheridan, 19 Maze Green, Bishop's Stortford, Herts. Tel: (0279) 54675 or 01-242 1055.

FLASHING RED L.E.D.s 89p. Small Reed Switches, 10p. Magnets 7p. Large 6V DC Electronic Buzzers 99p. Postage 18p. Grimsby Electronics, Lambert Road, Grimsby, Humberside (Retail Shop).

BARGAINS FOR THE ELECTRONIC HANDYMAN

BRANDED LED DIGITAL ALARM CLOCKS

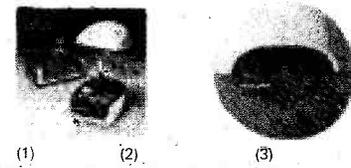

Returned to Service Department within guarantee period.

- (1) With alarm repeat — S.R.S.P. of £17.00 offered at **£3.95** inc. VAT.
- (2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at **£7.95** inc. V.A.T.
- (3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues S.R.S.P. of £32.00—offered at **£7.45** inc. V.A.T.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases

PRESCOTT CLOCK AND WATCH COMPANY LIMITED
 Prescott House, Humber Road, London NW2 6ER

PLEASE MENTION
ETI
 WHEN REPLYING
 TO ADVERTS

SITUATION VACANT

ELECTRONIC ENGINEERS

We are looking for a number of engineers (male/female) to work with electronic equipment at our premises in the London Area and for small numbers of vacancies in Belfast and Bristol. Initial Salary

£5170 to £5620 in London
£4720 to £5170 elsewhere

Plus additional payments for shift or irregular hour working.

Applicants should have a Degree, HND or HNC in Electronic or Electrical Engineering or Applied Physics
OR

A City & Guilds Full Technological Certificate in Telecommunications (Course 271).

All our engineering staff receive comprehensive training, so experience is not essential.

Write for further information and application form to: **The Engineering Recruitment Officer, BBC, Broadcasting House, London W1A 1AA,** Quoting Ref: 79.E.4119/ET.



CLASSIFIED

ADVERTISEMENTS

CONTACT

KATE SMITH

ETI

145 CHARING

CROSS ROAD

LONDON,

WC2H 0EE

**FOR RATES
SEE PAGE 119**

AD INDEX

AJD DIRECT SUPPLIES	24	ELECTROVALUE	79	E. R. NICHOLLS	84
AMBIT INTERNATIONAL	14	GREENBANK	69	NIC MODELS	58
AUDIO ELECTRONICS	58	GREENWELD	65	T. POWELL	45
B. BAMBER	118	GR INTERNATIONAL	53	POWERTRAN COMPUTERS ..	117
BAYDIS	65	GMT ELECTRONICS ...	104 & 105	POWERTRAN ELECTRONICS	2 & 8
BBC	121	HAMEG LTD.	108	PROGRESSIVE RADIO	110
BI-PAK	4 & 5	HARVELEC	53	PROTON ELECTRONICS	53
BK ELECTRONICS	118	HENRY'S	50, 73 & 108	J. W. RIMMER	53
B.N.R.S.	65	ILP ELECTRONICS	6 & 7	ROGER SQUIRE'S DISCO CENTRE	96
S. & R. BREWSTER	37	INTEGRATED CIRCUITS	34	ROMANE ELECTRONICS	10
BUTTERWORTHS	118	LASCAR ELECTRONICS	95	R.T.V.C.	92
CALCULATOR SALES AND		LB ELECTRONICS	74	SERVICE TRADING	70
SERVICE	84	L & B ELECTRONICS	95	STEVENSON	42
CAMBRIDGE LEARNING	114 & 115	LEYTRONICS	36	STRATHAND	50 & 108
CHILTMead	100	LOTUS SOUND	96	SURETRON	50
CHROMASONICS	95	MAGNUM AUDIO	37	SWANLEY	45
CHROMATRONICS	37	MAPLIN	124	TANDY	66
CLEF PRODUCTS	58	MARSHALLS	110	TECHNOMATIC	11
CODESPEED	96	MENOCREST	30	TELERADIO	24
COMP, COMP, COMP	103, 122 & 123	METAC	16, 17, 18 & 19	TEMPUS	74 & 75
CRIMSON ELEKTRIK	57	MICRO CIRCUITS	15	TK ELECTRONICS	24
CROFTON ELECTRONICS	73	MICRODIGITAL	41 & 100	TRANSAM	54
C.S.C.	49	MINIKITS	84	TRIDENT EXHIBITIONS	106
DELTA TECH & CO	106	MONOLITH	73	VERO ELECTRONICS	116
E.D.A.	73	MOUNTAINDENE	84	VIDEOTIME PRODUCTS	38
ELECTRONIC BROKERS	114	NASCOM	43 & 59	WATFORD ELECTRONICS	12 & 13
		NEWBEAR	60	WILMSLOW AUDIO	45

PET COSTS LESS AT COMP and it's a pedigree


8K — Comes complete with integral cassette deck

Full manuals supplied. Powerful 8K Microsoft Basic in ROM. Masses of software available — £499 + VAT

16K — Same as above but with new improved keyboard and cassette supplied as extra. Machine code monitor on board so you can program in 6502 machine code — £590 + VAT

32K — for a little extra get 32K memory providing greater storage capacity for programs or data — £690 + VAT

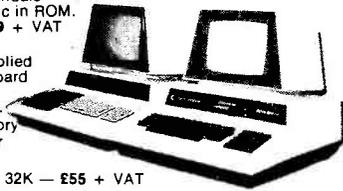External Cassette deck for 8K, 16K or 32K — £55 + VAT complete with cable and connector.



EXTENDED WARRANTY BY COMPUTARE

THE TRS80 (Special Scoop) Low Priced, Ready to Go!

£399 + VAT



EXTENDED WARRANTY BY COMPUTARE

PLUGS INTO YOUR OWN TV Use your own cassette

LEVEL II BASIC WITH 16K USER RAM provides you with possibly the most powerful micro around. All our TRS80s are fully converted to English Television Standard and include a U.K. Power Supply, Cassette Leads, Sample Tape, Level I & Level II programming manuals, and special lead that enables you to connect direct into your own television.

Special features of Level II Basic enable you to:-

- Set or reset any point on the screen — Test for the presence of a point on the screen (these features enable easy animation) — Save or load data from cassette under program control — File handling capabilities on cassette using named files. — Graphics blocks as standard — design your own pictures and many many more features for only £399 + VAT

FULL RANGE OF PETSOFT SOFTWARE NOW AVAILABLE

SORCERER SPEAKS YOUR LANGUAGE

For personal or business use. The best value for money around.

- ★ 512 by 256 point screen resolution ★ 16K or 32K

User RAM ★ Centronics Parallel Port ★ RS232C Serial Port ★ Composite TV peak to peak video output T.V. output supplied as extra. ★ 64 programmable graphics + 64 standard PET graphics ★ 79 key keyboard including 16 key numeric keypad. ★ Expansion bus for connection to S100 Expansion Box.

16K Sorcerer — £690.00 + VAT
32K Sorcerer — £790.00 + VAT
S100 Expansion Box — £210 + VAT

Word Processing Pac and Development Pac now available.

Word Processing Pac — £70 + VAT Development Pac — £70 + VAT



EXTENDED WARRANTY BY COMPUTARE

FULL RANGE OF TRS80 SOFTWARE NOW AVAILABLE

ANADIX DP8000


ONLY £540 + VAT
PET Connector — £49



The DP 8000 prints the 96-character ASCII set in single or double width at 84 lines per minute. ● The unit operates bidirectionally to print a 9 x 7 matrix on multiple copy, pin-feed plain paper. ● This model accepts RS-232C or current loop serial data at baud rates switchable from 110 to 9600 and Parallel Bit data input at over 1000 characters per second.

- Standard storage capacity of 256 characters ● Other features include Out of Paper Detector, Top of Form Programming and Skip Over Perforation Control.

THE NEW ITT APPLE (2020)

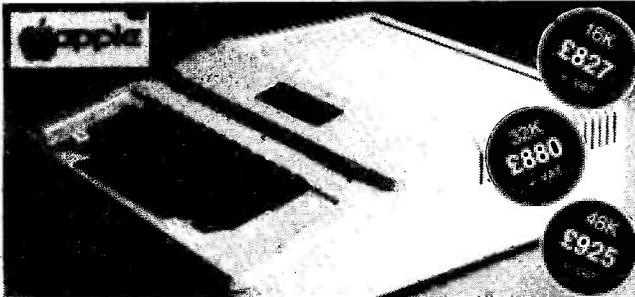

16K
£827


32K
£880

48K
£925

- ★ Full colour — UHF output ★ Audio cassette tape interface ★ Up to 48K RAM on board ★ BASIC in ROM (graphics commands include COLOUR = VLIN, HLIN, PLOT and SCRIN) ★ Built in loudspeaker ★ Buckets of software available ★ Disk System (110K byte per drive — includes controller) only £425 + VAT **EX-STOCK**

COMP PRO Mixer

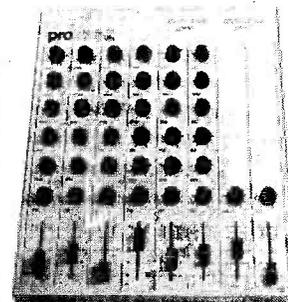Professional audio mixer that you can build yourself and save over £100.



6 into 2 with full equalization and echo, cve and pan controls.

All you need for your own recording studio is a stereo tape or cassette recorder.

This superb mixer kit has slider faders, level meters and additional auxiliary inputs.


Only £99.90 plus VAT for complete kit Plus FREE power supply valued at £25.00

Ideal for

DISCOS STAGE MIXING HOME STUDIOS AND MANY OTHER APPLICATIONS

video 100

12" BLACK & WHITE LOW COST VIDEO MONITOR

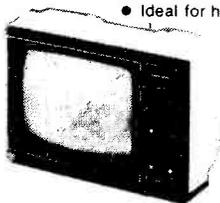

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

Only £79 + VAT

MODULATORS UHF Channel 36

Standard 6 meg band width £2.25

High Quality 8 meg band width £4.90 **EX-STOCK**

SHORT C12 CASSETTES FOR COMPUTER PROGRAMMES 10 for £4.00

HIRE PURCHASE AVAILABLE THROUGH HODGE FINANCE.

SEND S.A.E. FOR APPLICATION FORM.

JUST COMPARE OUR CASH AND CARRY PRICES!

SEND LARGE S.A.E. FOR OUR FREE '79 CATALOGUE

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER —
JUST CHECK THE SPEC'S.

AS SEEN IN
P.E. AUGUST, SEPTEMBER
OCTOBER 1979


COMPUKIT UK101

SAMPLE TAPE
WITH EXTENDED
MACHINE CODE MONITOR
AND DISSASSEMBLER
INCLUDED FREE

LOW COST SUPERBOARD IN KIT FORM

The CompuKit UK101 has everything a one board 'superboard' should have.

- * Uses ultra-powerful 6502 microprocessor.
- * 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- * 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs
- * Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen
- * Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF
- * Fully stabilised 5V power supply including transformer on board
- * Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder
- * 4K user RAM expandable to 8K on board £49 extra
- * 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible).
- * 6502 machine code accessible through powerful 2K machine code monitor on board.
- * High quality thru plated P.C.B. with all IC's mounted on sockets.
- * Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software

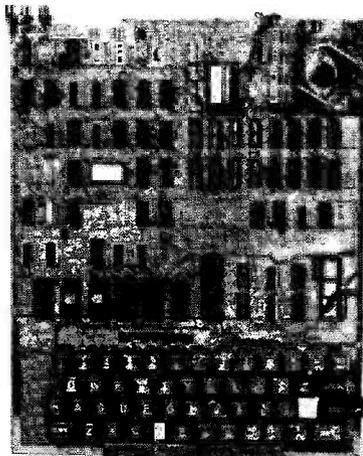

Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

KIT ONLY **£219** + VAT including RF Modulator & Power supply. Absolutely no extras.

Available ready assembled and tested, ready to go for **£269** + VAT

*8K Microsoft Basic means conversion to and from Pet, Apple and Sorcerer easy. Many compatible programs already in print.

SPECIAL CHARACTERS

@ Erases line being typed, then provides carriage return, line feed.
Erases last character typed.

CR Carriage Return — must be at the end of each line.
: Separates statements on a line.

CONTROL/C Execution or printing of a list is interrupted at the end of a line. "BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.

CONTROL/O No outputs occur until return made to command mode. If an input statement is encountered, either another CONTROL/O is typed, or an error occurs.

? Equivalent to PRINT

FUNCTIONS

ABS(X)	ATN(X)	COS(X)	EXP(X)
LOG(X)	PEEK(I)	POS(I)	RND(X)
SPC(I)	SQR(X)	TAB(I)	TAN(X)
FRE(X)	INT(X)		
SGN(X)	SIN(X)		
USR(I)			

STRING FUNCTIONS

ASC(X)	CHR\$(I)	FRE\$(X)	LEFT\$(X\$,I)
RIGHT\$(X\$,I)		STR\$(X)	
LEN(X\$)	MID\$(X\$,I,J)		
VAL(X\$)			

COMMANDS

CONT LIST	NEW	NULL	RUN		
STATEMENTS					
CLEAR DATA	DEF	DIM	END	FOR	
GOTO GOSUB	IF GOTO	IF THEN	INPUT	LET	
NEXT ON GOTO	ON GOSUB	POKE	PRINT	READ	
REM	RESTORE	RETURN	STOP		

EXPRESSIONS

OPERATORS
+ * ^ NOT AND OR >> << > < = <= >= RANGE 10³² to 10⁺³²

VARIABLES

A B C ... Z and two letter variables
The above can all be subscripted when used in an array. String variables use above names plus \$ e.g. A\$.
\$# = array number

COLOUR ADD-ON CARD AVAILABLE SOON

Enables you to choose your foreground the background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form.

THE ATARI VIDEO COMPUTER SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges! Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous.

You'll have thrill after thrill, whether you're in the thick of a dogfight, screeching around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright color (on color TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available in stock:

- Basic Maths — Hunt & Score* — Space War — Video Olympics — Outlaw — Surround — Sky Diver
- Basket Ball — Air Sea Battle — Black Jack — Breakout
- *Codebreaker — Miniature Golf.
- Extra Paddle Controllers — £14.90 + VAT
- *Keyboard Controllers — £16.90 + VAT

£138
+ VAT

£13.90 each.
+ VAT

SPECIAL OFFER WHILE STOCKS LAST:

Free extra cartridge of your choice please state 1st 2nd and 3rd preference.



SAVE £30



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CARD or AMERICAN EXPRESS number. CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G
Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday
NOW OPEN ALL DAY SUNDAY — For Shop Sales Only
Close to New Barnet BR Station — Moorgate Line.

COMP COMPUTER COMPONENTS
(Part of the Compshop Ltd. Group)



MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.




Our catalogue even includes some popular car accessories at marvellous prices.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.

Breadboard 1979 is even bigger and better than last year. It's the one show no one should miss!

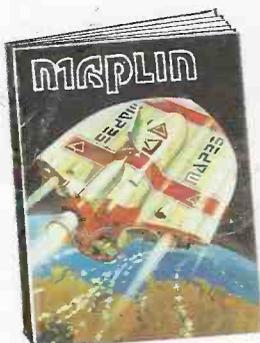These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £15.92 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

MAPLIN

ELECTRONIC SUPPLIES LTD

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____

ETI 12/79



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.

Maplin will be there in force with all our projects on permanent demonstration. There will be plenty to see and many of our interesting lines will be on sale.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.

WATFORD ELECTRONICS

ILP MODULES 15-240 WATTS

We are now stockists for these world famous fully guaranteed (2 years guarantee on all modules) Pre amps, Amplifiers & Power Supplies.

HY5 Preamp. 500mV RMS £4.75; HY120 Power Amp. 60W RMS/8Q £15.40;
 HY30 Amplifier. 15W RMS/8Q £4.95; HY200 Power Amp. 120W RMS/8Q £18.50;
 HY50 Amplifier. 25W RMS/8Q £7.25; HY400 Power Amp. 240W RMS/4Q £27.50.



POWER SUPPLIES
 PSU36 — Drives 2 x HY30s £6.38
 PSU50 — Drives 2 x HY50s £8.18
 PSU70 — Drives 2 x H120s £13.70
 PSU90 one HY200 £13.70
 PSU180 2 x HY200 or one HY400 £22.99

OHIO SUPERBOARD II

Only £188.00

Yes, we are now selling this popular single board microcomputer at the giveaway price of £188.00. Due to the recent devaluation of the US Dollar against £ Sterling, we have been able to purchase Superboards at lower prices. Naturally, we wish to pass this price advantage on to our customers. Buy now to avoid disappointment should Mrs. Thatcher & Co. decide to devalue the Pound. Superboard II is supplied fully assembled and tested to British TV specification. Also included at no extra cost 4 manuals and a Cassette with programmes. Requires +5V at 3A and a Video Monitor or TV with RF Converter to be up and running. (Data sheet supplied. We can also supply the RF Converter and Power Supply in Kit form or ready-built).
 80K Microsoft BASIC in ROM 4K Static RAM — on BOARD expandable to 8K. Full 53 Key Keyboard with Upper/Lower Case & User programmability and a lot more. See it for yourself. Continuous demonstration on at our retail shop.
 Specially designed attractive fibreglass case (VDU Unit can be mounted on it).
 Power Supply Kit with RF Modulator £21.75
 Extra 4K of RAM £38.50

SWITCHES

TOGGLE 2A, 250V 28p
 SPST 28p
 DPST 34p
 DPDT 34p
 4 pole on/off 54p

SUB-MIN TOGGLE

SP changeover 59p
 SPST on/off 54p
 SPST based 85p
 DPDT 6 tags 70p
 DPDT centre off 70p
 DPDT Biased 115p

ROTARY: Make your own multiway Switch.

Adjustable Stop Shafting Assembly. Accommodate up to 6 Wafers 75p
 Mains Switch DPST to fit 34p
 Break Before Make Wafers. 1 pole/12 way. 2p/6 way. 3p/4 way. 4p/3 way. 5p/2 way 47p

Spacer and Screen

ROTARY: (Adjustable Stop) 1 pole/2 to 12 way. 2p/2 to 6 way. 3 pole/2 to 4 way. 4 pole/2 to 3 way 41p
 ROTARY: Mains 250V AC. 4 Amp 45p

SLIDE 250V:

1A DPDT 14p
 1A DPDT c/over 15p
 1/2A DPDT 13p
 4 pole 2-way 24p

PUSH BUTTON

Spring loaded 80p
 SPST on/off 65p
 DPDT 6 Tag 85p

MINIATURE

Non Locking 15p
 Push to Make 25p
 Push Break 15p

CRYSTALS

100KHz	385
455KHz	383
1MHz	323
1.008M	393
1.28MHz	392
1.6MHz	323
1.8MHz	323
1.8432MHz	362
2.4576MHz	362
3.2768M	323
3.57954M	195
4.032MHz	323
4.433619M	135
5.0MHz	355
5.195M	323
5.555M	323
6.800M	323
8.86723M	323
9.375M	323
10.0MHz	323
10.7MHz	323
12MHz	323
14.3181MHz	300
18MHz	323
18.432M	323
20.0MHz	323
27.848M	323
48.0MHz	323
100.00MHz	323

TRANSFORMERS (Mains Prim. 220-240V)

6-0-6V: 9-0-9V: 12-0-12V 100mA	95p
8V: 6V-5A: 9V-5A: 9V-4A: 9V-4A: 12V-3A	195p
12V: 4.5V-1.3A: 4.5V-1.3A: 6V-1.2A: 6V-1.2A	195p
12V-5A: 12V-5A: 15V-4A: 15V-4A: 20V-3A	220p (20p p&p)
20V-3A	220p (20p p&p)
24VA: 6V-1.5A: 6V-1.5A: 9V-1.3A: 9V-1.3A:	45p (45p p&p)
12V-1A: 12V-1A: 15V-8A: 15V-8A: 20V-6A	45p (45p p&p)
20V-6A	45p (45p p&p)
50VA: 6V-4A: 6V-4A: 9V-2.5A: 9V-2.5A: 12V-2A:	55p (55p p&p)
12V-2A: 15V-1.5A: 15V-1.5A: 20V-1.2A: 20V-1.2A:	350p (50p p&p)
1.2A: 25V-1A: 25V-1A: 30V-8A: 30V-8A	650p (60p p&p)
100VA: 28V-0.28V-2A	650p (60p p&p)
100VA: 12V-4A: 12V-4A: 15V-3A: 15V-3A:	650p (60p p&p)
20V-2.5A: 20V-2.5A: 30V-1.5A: 30V-1.5A:	650p (60p p&p)
40V-1.25A: 40V-1.25A: 50V-1A: 50V-1A	650p (60p p&p)

ALUM. BOXES*

3x2x1"	54
2 1/2x5 1/2x1 1/2"	72
4x4 1 1/2"	70
4x2 1/2x1 1/2"	72
4x5 1/2x1 1/2"	78
4x2 1/2x2"	88
5x4 2"	98
6x4 2"	98
7x5 1/2"	145
8x6 3"	185
10x7 3"	210
10x4 1/2x3"	175
12x5 3"	215
12x8 3"	265

PANEL METERS*

FSD 60x46x	54
35mm	54
0-50uA	70
0-100uA	70
0-500uA	70
0-1mA	78
0-10mA	98
0-50mA	98
0-100mA	115
0-500mA	115
0-1A	120
0-2A	120
0-5V	175
0-50V AC	175
0-300V AC	175
"S"	175
"VU"	175
475p each	

ETI Projects:

Parts available for: Click Eliminator; Ambush; Guitar Effect Unit; Audio Display; DM900, Audio-ophile Amp; 60W Amplifier System; Train Controller. Send SAE plus 5p for list.

VOLTAGE REGULATORS

1A TO203	7905	7905	220p
5V TO75	7812	7812	220p
12V TO15	7815	7815	220p
15V TO18	7818	7818	220p
18V TO24	7824	7824	220p
100mA TO92 Plastic Casing			
5V TO75	65p	7905	75p
5V TO75	65p	7912	75p
12V TO15	65p	7915	75p
15V TO18	65p	7918	75p
18V TO24	65p	7924	75p
100mA TO92 Plastic Casing			
5V TO75	30p	7905	65p
6V TO62	30p		
8V TO82	30p		
12V TO12	30p	7912	65p
15V TO15	30p	7915	65p
LM300H	170p	LM327	270p
LM305H	140p	LM723	38p
LM309K	135p	TAA550	50p
LM317K	350p	TBA625B	95p
LM323K	550p	TDA1412	150p
LM325N	240p	78H05 + 5/5A	595p
LM326N	240p	78H5 + 5 to +24	650p

OPTO ELECTRONICS

LEDs with Clips			
TIL209 Red	13		
TIL211 Grn.	17		
TIL212 Yel.	18		
TIL220 2" Red	14		
2" Green, Yellow or Amber	18		
7 Segment Displays			
Red, TIL307	675		
CA, TIL312 3"	105		
CA, TIL313 3"	105		
CC, TIL321 5"	115		
CC, TIL322 5"	115		
CC, TIL323 5"	115		
CC, TIL324 5"	99		
CC, TIL325 5"	99		
CC, TIL326 5"	99		
CC, TIL400 5"	99		

ISOLATORS


IL74	48		
TIL111/2	85		
TIL114	95		
TIL117	110		

293	128	3006	68	4045	145	4097	372	4515	259	4549	375
295	185	4007	14	4046	66	4098	99	4516	52	4553	398
298	168	4008	55	4047	87	4099	145	4517	382	4554	150
324	240	4009	30	4048	58	4180	78	4518	58	4555	46
325	290	4010	27	4049	25	4181	78	4519	55	4556	44
326	294	4011	18	4050	33	4182	78	4520	55	4557	365
327	286	4012	14	4051	45	4183	78	4521	228	4558	105
347	148	4013	35	4052	45	4174	82	4522	149	4559	375
348	186	4014	55	4053	45	4175	78	4526	65	4560	210
352	228	4015	63	4054	110	4184	90	4527	152	4561	65
353	228	4016	25	4055	99	4408	670	4528	55	4562	375
365	65	4017	60	4056	110	4409	670	4529	145	4566	155
366	65	4018	60	4057	1650	4410	670	4530	85	4569	280
367	65	4019	32	4059	480	4411	795	4531	135	4572	26
368	66	4020	70	4060	90	4412F	1250	4532	67	4580	595
373	180	4021	52	4061	1200	4412V	1050	4534	675	4581	297
374	180	4022	50	4062	995	4415F	520	4536	365	4582	130
375	160	4023	14	4063	110	4415V	390	4538	142	4583	75
377	212	4024	40	4066	30	4419	280	4539	105	4584	63
378	184	4025	14	4067	280	4422	426	4541	135	4585	105
379	215	4026	100	4068	14	4433	780	4543	155		
384	86	4027	35	4069	14	4435	540				
390	230	4028	50	4070	14	4440	1275				
393	230	4029	54	4071	14	4450	260				
395	218	4030	50	4072	14	4451	220				
396	215	4031	150	4073	14	4452					
398	276	4032	80	4075	14	4490F	310				
399	230	4033	95	4076	57	4490	240				
445	150	4034	1.99	4077	14	4501	16				
447	144	4035	80	4078	14	4502	57				
490	180	4036	E3.25	4081	14	4503	42				
668	182	4037	100	4082	14	4506	46				
669	182	4038	108	4085	52	4507	35				
670	248	4039	320	4086	52	45					

Tecknowledgedgy for sale.

The Mark III FM Tuner

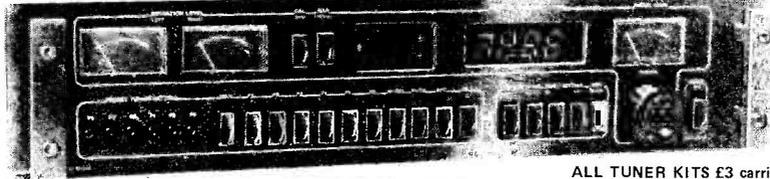DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically and visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £22.35 VAT With Hyperfi Series modules £185.00 + £27.75 VAT



ALL TUNER KITS £3 carriage

Features of the system:

- * Precision construction & design of all parts
- * Time/frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gap) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.95 VAT
Complete with digital frequency readout/clock/timer hardware £99.00 + £14.85 VAT
Complete with MA1023 clock/timer module with dial scale £66.00 + £9.90 VAT

*Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW/MW/FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RFI - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV. Complete kit £19.50 + £2.93 VAT, built and tested module £27.00 + £4.05VAT



Ambit stocks and distributes a wide range of frequency counter LSI for all types of DFM - part two of the catalogue contains details of the MS5523/4/5/6 range, and the versatile MS12318 divide by ten or hundred prescaler IC. The DFM1 combined counter for AM, FM SW and direct/clock/stopwatch/timers - details available, but SAE please!

PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00+£5.55vat

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design but using standard (fundX9) crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + £4.68 vat

MICROMARKET

OSTS over/low:					
6800P	650p	8212	230p	2102	170p
6820P	600p	8216	195p	2112	340p
6850P	275p	8224	350p	2513	754p
6810	400p	8228	478p	4027	578p
6852	365p	8251	625p	2114	1000p
8080	630p	8255	540p		+15% VAT

RADIO and AUDIO MODULES: Consistently the most advanced

FOR FM
EF5801-3-4 series: 6 stage varicap tuning, all with oscillator output
5801 Dual gate MOSFET RF stages, bipolar mixer £17.45 + 2.61VAT
5803 Dual gate RF/mixer stages, amplified LO out £19.75 + 2.96VAT
5804 'Hyperfi' series, with internal PIN diode a/c, and ultra wide range tuning system £24.95 + 3.74VAT

EF5402 4 stage varicap tuner with TDA1062 and LO output. Uses FET/IC input. PIN a/c £10.75 + 1.61VAT

FOR 30-200MHz

The EF series are available on special order to cover bands (usually approx 20% of the centre frequency) in the range described. Details in our price list.

FOR RF IFs at 10.7MHz

7030 single 6 pole linear phase filter 1F with HA1137£10.95 + 1.64VAT
7130 two 6 pole linear phase filter 1F with CA3189E £16.25 + 2.44VAT
7230 Hyperfi IF, switched bandwidth, AGC IF preamp, linear phase ceramic filters with diode switched narrow filter £24.95 + 3.74VAT

DECODERS for MPX (STEREO)

Various types, guaranteed the world's biggest and best ranges

LARSHOLT FM TUNERS

7252 MOSFET front end combined with CA3089 IF £26.50 + 3.97VAT
7252 JFET front end, combined with IF and decoder £26.50 + 3.97VAT

FM/AM tuning synthesiser, see details elsewhere in this advertisement

COMPONENTS FOR RADIO/COMMUNICATIONS/AUDIO/TV etc.

As usual, Ambit brings you the latest and best, a small selection of which is shown in this advertisement. The Ambit stocks contain information on most of the devices mentioned here - and an order for the new part three will ensure you stay up with latest developments. Data photocopying service described in pricelist info.

RADIO ICs for FM vat

SL1600 series	Audio preamps	vat
CA3089E 1.94 29	LM381N 1.81 27	
CA3189E 2.45 37	LM382N 1.65 25	
HA1137VW 2.20 33	K84436 2.53 38	
HA11225 2.20 33	K84438 2.22 33	
SN7660N 0.75 11	TD102P 3.50 53	
SL1620 2.17 33	TD102S 3.50 53	
SL1621 2.17 33	TD107A 3.75 56	
SL1623 2.44 37		
SL1624 2.17 33		
SL624 3.28 49		
SL1625 2.17 33		
SL1626 2.44 37		
SL1630 1.62 24		
SL1640 1.69 28		
SL1641 1.89 28		
SL6640 2.75 41		
SL6690 3.20 48		
MC3357 3.12 47		
MC1496 1.25 19		
NE544 1.70 25		

IF AMPLIFIERS

KB4406 0.50 07
MC1350 1.20 18
SL1640 1.69 28
SL1641 1.89 28
SL6640 2.75 41
SL6690 3.20 48
MC3357 3.12 47
MC1496 1.25 19
NE544 1.70 25

COMMUNICATIONS

K84412 2.55 38
K84413 2.75 41
MC1496 1.25 19
NE544 1.70 25

OSTS: Remember all OSTS stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

TTL Standard AND LP Schottky

VOLTAGE REGS:		MISCS Counter/timer, scalar devices.....	
7400	13 20	74142	265
7401	13 20	74143	312
7402	14 20	74144	312
7403	14 20	74145	65 97
7404	14 20	74146	175
7405	18 26	74147	109 191
7406	38	74148	99
7409	17 24	74149	64 84
7410	15 24	74150	64 54
7411	20 24	74151	64 54
7412	17	74152	64 110
7413	30	74153	64 110
7414	51	74154	65 75
7415	24	74155	60
7416	30	74156	210
7417	30	74157	82 130
7418	30	74158	82 130
7419	30	74159	130
7420	30	74160	130
7421	29	74161	130
7422	27	74162	92 78
7423	27	74163	92 78
7424	27	74164	104 130
7425	27	74165	105
7426	27	74166	105
7427	27	74167	20
7428	35 32	74168	200
7430	17 24	74169	230 200
7432	25 24	74170	625 130
7434	24	74171	625 130
7436	33 24	74172	87 120
7438	33 24	74173	87 120
7440	17 24	74174	75
7441	74	74175	78
7442	70 99	74176	78
7443	115	74177	350
7444	112	74178	210
7445	94	74179	135
7446	94	74180	135
7447	82 89	74181	165 350
7448	56 99	74182	165 350
7449	99	74183	165 350
7451	17 24	74184	135
7453	17 24	74185	135
7454	17 24	74186	135
7455	35 24	74187	274
7460	17	74188	135
7463	124	74189	92
7470	28	74190	105 180
		74191	105 180
		74192	105 180
		74193	105 180
		74194	105
		74195	99 110
		74196	99 110
		74197	105
		74198	150
		74199	160
		74200	90
		74201	105
		74202	105

IMPORTANT: ALL PRICES SHOWN EXCLUDE VAT WHICH MUST BE ADDED AT 15% OVERALL. PLEASE NOTE THE REDUCED CMOS/LPSN TTL RANGES DUE TO CURRENT SUPPLY SHORTAGE.

CD4000

4000	17	4522	149
4001	17	4528	102
4002	17	4529	141
4006	109	4532	125
4007	18	4538	150
4008	58	4539	110
4009	58	4543	176
4010	58	4549	399
4011	17	4554	153
4012	17	4558	117
4013	55	4560	218
4014	95	4562	530
4017	80	4566	159
4018	60	4568	281
4019	60	4572	25
4020	93	4584	63
4021	82	4585	100
4022	90		
4023	17		
4024	76		
4025	17		
4026	180		
4027	55		
4028	72		
4029	100		
4030	100		
4031	120		
4032	83		
4033	64		
4034	85		
4035	65		
4036	130		
4037	65		
4038	55		
4039	55		
4040	65		
4041	65		
4042	65		
4043	65		
4044	80		
4045	130		
4046	60		
4047	65		
4048	65		
4049	65		
4050	55		
4051	65		
4052	65		
4053	65		
4054	135		
4055	563		
4056	115		
4057	115		
4058	109		
4059	120		
4060	53		
4061	25		
4062	20		
4063	20		
4064	20		
4065	20		
4066	20		
4067	20		
4068	20		
4069	20		
4070	20		
4071	20		
4072	20		
4073	20		
4074	20		
4075	20		
4076	20		

MORE FROM THE GENERAL AMBIT CATALOGUE RANGES:

Varicap tuning diodes for AM/FM/TV: 1.9v AM tuning (IC 15-1) from TOKO - KV121 double matched 17.5p 20p vat KV120 triple matched 24.5p 37p vat KV121S triple snap-apart 24.5p 37p vat MVAM115 single 15v 105p 16p vat MVAM125 single 25v 105p 16p vat MVAM2 double 25v 148p 22p vat BB204/104 double FM 40p 6p vat BA102 single AFC etc 30p 4p vat BA121/TT210 single afc 30p 4p vat BB105B single UHF 40p 6p vat PIN DIODES, BANDSWITCH types BA479 PIN attenuator 35p 5p vat TDA1061 Pi-form anten. 95p 14p vat BA182 Bandwitch 21p 3p vat All RF semiconductors stocked in depth. Please ask for quantity pricing details.

TOP GRADE LEDs by AEG: PRICES ARE EXC VAT (add 15%)

SIZE Red Green Yellow Orange QUANTITY discounts for LEDs: 5mm 14p 16p 15p 20p 10 per type - less 10%; 3mm 13p 15p 18p 19p 100 per type - less 30%; 2x5x5 17p 20p 20p 24p 100 mix in 10s - less 25%

FUTABA FLUORESCENT VACUUM DISPLAYS for CLOCKS etc

5LT02 clock display (static drive) with AM/PM flags £9 + 1.35
5LT03 DFM display for MS5525 LSI counter £9.45 + 1.42 vat
6LT06 5 digit DFM display (GI AY58100) mpccc £9.75 + 1.46 vat

TOKO COILS, FILTERS, CHOKES etc for AM/FM/TV comms.....

TYPE Size: 5mm 7mm 10mm (please add VAT @ 15%)
AM IF 5mm 33p 30p Various for ICs, transistor etc.
FM IF 5p 33p 33p Various for ICs, transistor etc.
SW coils 5p 33p 33p Two impedance series
OSC coils 5p 33p 33p For L, MW, SW
TV vif/af 35p

Various coils in the range 20kHz to 300MHz - see TOKO catalogue

CERAMIC and MECHANICAL FILTERS (inc MURATA TYPES)

CFT455B/CFT455C 60p; CFX014 120p; CFU455C 85p
CFT470C 60p; CFU470C 65p
MURATA CFU455H and CFU455F ceramic block filters 1.95ea
MURATA CFM455 series ladder filters D, E, F, G, H bandwidths available now (20, 16, 12.8, 6.4kHz) £8.35 ea (metal encapsulated)
SFD455B, SFD470B, SFD472B 85p ea
CFM2 series mechanical elements types A, B, C, D (4-10kHz bandwidth) - 65p ea. As used in RCMC feature)

MULTIPLEX/PILOT TONE FILTERS, FM IF FILTERS (see cat and)

CFSE10.7/SFE10.7 stereo FM IF ceramic filters (slim FM4 etc) 50p
CFRB10.7/SFE10.7MJ mono bandwidth ceramic FM IF filters 50p
SFE10.7ML ultra linear phase ceramic IF filters 70p
CDA10.7 - 10.7MHz ceramic discriminator for CA3089 etc) 70p

Current news: A PCB for the Mullard DC tone and volume control system is now available £3 + 0.45 VAT. HMOS PA modules for 60-100W - kit £14 + £2.10VAT, heatsink £4.10+0.61. FM radio control system crystals £3.75 pair inc VAT (Sept on). MK50366N: static drive clock/timer IC £3.78 + 0.57 VAT. 12kHz channel spacing 8 pole 10.7MHz XTAL filter by TOYO type H4402 £15.50 + £2.32VAT. A further updated pricelist is now available, and we would like to remind you that enquiries can only be answered if accompanied either by an official business letterhead, or an SAE. STOP PRESS: TOKO's new split-apart triple AM tuning diodes are in stock £2.45 + 37p VAT, (KV121S). SBL1 diode DBM 1.500MHz - £4.25+0.64p.

Terms: CWO please. Account facilities for commercial customers OA. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access £15 for credit purchases. Catalogues: Ambit: Part 1 45p. Part 2 50p. 90p pair. TOKO Euro shortform 20p. Micrometals toroid cores 40p. All inc PP etc. Full data service described in pricelist supplements. Hours/phone: We are open from 9am - 7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm (not Saturdays). Saturday service 10am to 6pm.

ambit international (R) AMBIT catalogues are guaranteed to contain the most up-to-date and best informed comment on modern developments and advances in the field of radio and audio. There is no competitive publication that even approaches the broad range of parts/information on modern techniques.

2 Gresham Road, Brentwood, Essex. (0277) 227050

CMOS SALE

Compare our make, quality and prices. All items subject to prior sale.

	Make	Price
CD4015BE	RCA	57p
CD4027BE	RCA	36p
CD4028BE	RCA	57p
CD4053BE	RCA	60p
CD4098BE	RCA	75p

TRANSISTOR SALE

2N 3819	TEXAS	17p
2N 3820	TEXAS	27p

DISPLAY LEDs AT LOWEST PRICES

DL 704/DL 707	90p
FND 500/FND 510	75p

NOW THE CHIPS ARE DOWN

Due to bulk purchase, we are able to offer unbeatable prices on INTERSIL chips. Compare our prices and see how much you save.

	1-24	25+	100+
ICL7106CPL	6.50	6.25	5.95
ICL7107CPL	6.25	5.95	5.75
ICL8038CCPD			
	3.00	2.75	2.15
ICM7216AJI			
	18.75	17.75	14.75
ICM7216BPI			
	16.75	14.75	12.25

LINEAR ICs

LM324N Quad Op. Amp	40p
NE555N-8 Timer	18p
LM555N-14 Dual Timer	50p
LM723CN Voltage Regulator	33p
LM747CN-14 Dual Op Amp	40p

VOLTAGE REGS

SG780 5CP/SG781 2CP	55p
SG7905CP/SG791 2CP	70p

POWER CONVERTER FC-5

Now you can operate 120 Volts. American equipment from 240 Volts! Only **£9.95** complete with British type plug.

LED BAR GRAPH AND ANALOG METER DRIVER.

New from National LM3914. Drives 10 LED directly for making bar graphs, audio power meters, analog meters, LED Oscilloscopes, etc. Units can be stacked for more LEDs. A super versatile and truly remarkable IC. Just out! Special price: Only **£1.99** inc. 12 page spec. sheet.

FAIRCHILD RED LED LAMPS

*FLV5057 Medium Size Clear Case RED EMITTING. These are not retested off-spec. units as sold by some of our competitors. These are factory prime, first quality, new units.



VERY LIMITED STOCK!!
8p EACH 100 077
6p EACH 1,000 077
5p EACH 2,000 077

Texas Instruments Low Profile Sockets



Contacts	Price
8 PIN	.08
14 PIN	.12
16 PIN	.14
18 PIN	.18
20 PIN	.20
22 PIN	.22
24 PIN	.24
28 PIN	.28
40 PIN	.40

"THE COLOSSUS"

FAIRCHILD SUPER JUMBO LED READOUT

A full .80 inch character. The biggest readout we have ever sold! Super efficient.

YOUR CHOICE
FND 847 Common Anode
£2 each

FND 850 Common Cathode
£1.50 each. 100 off

THE MOST VERSATILE LIQUID CRYSTAL DISPLAY

1.24	25+	100+
LCD106	6.45	5.50 5.25

.5" Field effect LCD display featuring 3½ digits, colon, plus/minus sign, 3 decimal points and "LO BAT" indicator. Ideal for DMMs, DPMs, digital thermometers, AM/FM radio readouts. Just look at the features. Ultra low power consumption, high contrast ratio-wide viewing angle-rapid response-proven sealing techniques-superior MTBF-reflective aluminium foil. Over 300,000 already sold! Compare our price at below distributors!

MICROPROCESSOR MADNESS

Compare our prices before you buy elsewhere.

CPUs	MEMORIES
B080A 4.95	2102 1.00
6800 7.00	2114 low power 2.14
Z-80 8.50	300 NS 4.75
Z-80A 10.50	5101 4.95

EPROMS	UARTS
1702A 4.00	AY-5-1013A 3.50
2708 7.00	AY-3-1015 4.00
2516 24.50	

CHARACTER GENERATOR

RO-3-2513	5.50
-----------	-------------

ELECTRONIC YAP BOX—3 DISCREET SOUNDS

- Laser Gun
 - Siren
 - Ray Gun
 - Plus many others.
- Use on car PA system, bicycle horn, or protection against would-be attackers. Invent your own sound effects, make believe you are the police or firemen. Must for DJs, pop groups and recording studios. Only **£9.95** inc.

We apologise to our customers for the delay in completing orders during July/August as a result of our move. We are now back to normal.


Ordering information: For orders under £50 add 50p p.&p. Add 15% VAT to total. All items are subject to prior sale and therefore subject to availability. Prices are subject to change without notice.

All orders to:



NOTE OUR NEW ADDRESS

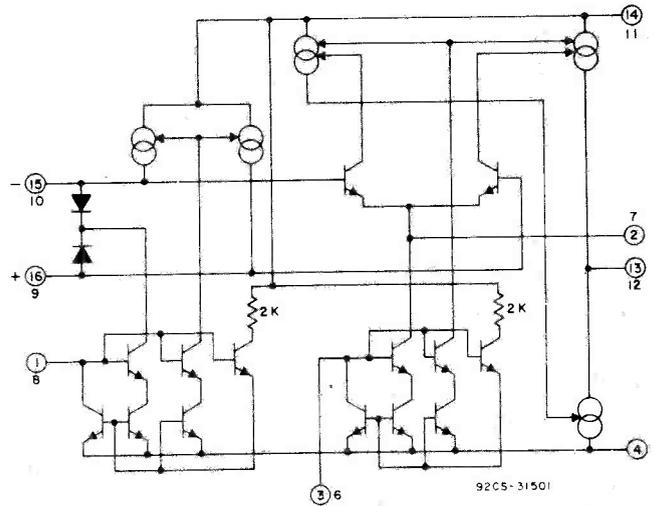Please note new address:
4 Meeting Street
Appledore, Nr. Bideford
North Devon EX39 1RY
Telex 8953084 Maclin G
All enquiries to our London office,
01-278 7369




Happy Families

The latest offspring of RCA Solid State is a new family of dual variable operation amplifiers. The CA3280G Series combines two operational transconductance amplifiers in a single package.

The two amps are independent, differential input types and the output is a current proportional to the differential input voltage and the transconductance, which is programmable via a separate input terminal.

All characteristics of the two amplifiers are matched to within 5%. Peak output current can be as high as 650 uA at a bias current of 500 uA and operating bandwidth is 9MHz at a bias current of 1mA.

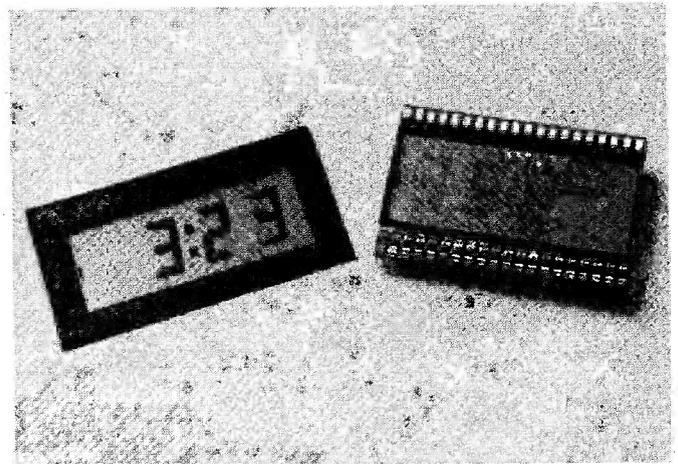Applications include voltage-controlled amplifiers, voltage controlled filters, voltage controlled oscillators, function generators, etc. The devices are supplied in 16 lead DIL plastic packages and are available with operating temperature ranges of -55 to +125°C (CA3280 AG) and 0 to +70°C (CA3280) from RCA Solid State — Europe, Sunbury on Thames, Middlesex TW16 7HW.



Display Giants

New from Fairchild are a range of large area liquid crystal displays, suitable for clock and digital panel meter purposes.

There are two versions — 3½ digit (FLB 3513) and 4 digit (FLB 4013), both featuring 0.5 inch digits. The inclusion of a colon allows the displays to be

used in timekeeping applications. Decimal point and polarity signs are included for digital panel meter use.

Power requirements? — 5V typical with a maximum drive current requirement, at 3V with all segments on, of 5uA.

You can find out more about these LCDs from Fairchild Camera & Instrument (UK) Ltd, 230 High Street, Potters Bar, Herts EN6 5BU.

Quartz Melody Multi-Alarm Chrono For 1980 Try this 34 Function

for only £26.95

Count-down Timer



Can be used for a host of applications from boiling an egg to warning you your parking meter is expired. The timer is presettable to 23 hours 59 mins. 00 secs. in 1 min. steps and counts down in 1 sec. steps. It operates quite independently of the other counters and the watch can be in any other mode whilst it is being used.


At the preset time the musical tone will sound for 1 minute.

Alarm



The alarm can be set at 1 minute intervals to any time within the 24 hour period. A clear firm musical tone sounds for 1 minute at the appointed time. An automatic roll-over to the normal time is a feature after the alarm has been read. A clear indicator displays whether the alarm is set or not.

Time Zone

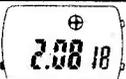

The time zone enables you to tell the time in two places at once. It can be useful on holiday or business trips. Just programme the second time zone and it will be permanently recorded for your easy reference.

Chronograph



This watch incorporates a sophisticated and very accurate stop/start counter which has many applications in sporting events and timing for recordings etc.

Mode 1: Is the normal stop-watch mode. Stop-Start-Zero.


Mode 2: The lap timer enables first and second past the post times to be recorded. The display is frozen but the counter continues to count.

Mode 3: Longer timing intervals, such as journey times, can be recorded whilst the watch is reading its normal time, or the count-down is being used. The counter counts to 1 hour in 1/100 sec. steps in all its modes.



MODEL M30

Display Format (NORMAL TIME DISPLAY)

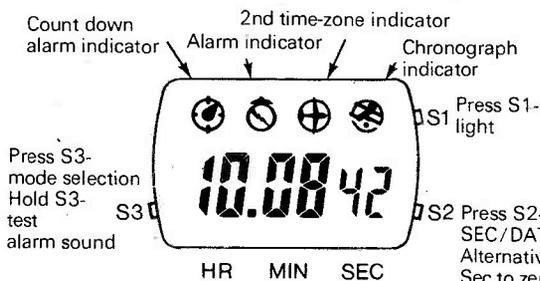

5 independent working modes

- i) Normal watch
- ii) Count down alarm
- iii) Alarm
- iv) Dual time zone
- v) 1/100 sec. chronograph

Display indicators (not all shown)

A very impressive new watch at a superbly low price from Metac. This super slim watch is only 7mm thick (that's thinner than most mechanical tick-tocks), but its micro-processor heart packs 34 different features.

In addition to those listed on the left the watch can display the day of the week in French or German or English (just select the one that suits you).

It has fast and slow setting rates for the counter and the alarm as well as the normal time setting.

There are 7 display indicators, 6 digits and a back light for night viewing. The 5 working modes are independent of each other, and the watch can be operated in all 5 modes at once.

FOR ORDERING INFORMATION PLEASE SEE OVER

Metac

**ELECTRONICS
& TIME CENTRES**

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

**QUARTZ LCD
5 Function**

Hours, mins, secs, month, date, auto calendar, back light, fully adjustable bracelet to fit all wrists.

£6.65

Guaranteed same day despatch.

Very slim, only 6mm thick.



M1

**SOLAR QUARTZ LCD
5 Function**

Genuine solar panel with battery back-up. Hours, mins, secs. Day/date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

**QUARTZ LCD
11 Function** SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold!

Guaranteed same day despatch



M3

**QUARTZ LCD
ALARM 7 Function**

Alarm. Hours, mins., secs. Month, date, day. 6 digits. 3 flags plus continuous display of day and date and seconds. Back-light. Only 9mm thick

£12.65

Guaranteed same day despatch



M4

**MULTI ALARM
6 Digits
10 Functions**

- ★ Hours, mins., secs.
- ★ Month, date, day
- ★ Basic alarm.
- ★ Memory date alarm
- ★ Timer alarm with dual time and 5 country zone.
- ★ Back light.
- ★ 8mm thick.

£18.65



M5

**FRONT-BUTTON ALARM
Chrono Dual Time**

6 digits, 5 flags, 22 functions. Constant display of hours and mins. plus optional seconds or date display. AM/PM indication. Month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light.

£22.65 Guaranteed same day despatch

Fully adjustable open bracelet.



M6

**SOLAR QUARTZ LCD
Chronograph with Alarm
Dual Time Zone Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£27.95



M7

**ALARM CHRONO
with 9 World
Time Zones**

- ★ 6 digits, 5 flags.
- ★ 6 basic functions.
- ★ 8 further time zones.
- ★ Count-down alarm.
- ★ Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps
- ★ Split and lap timing modes
- ★ Alarm.
- ★ 9mm thick.
- ★ Back-light.
- ★ Fully adjustable bracelet.

£29.65



M8

**SOLAR QUARTZ LCD
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th secs. 10X secs., mins. Split and lap modes. Back light. Auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65 Guaranteed same day despatch.



M9

**LADIES DAY WATCH
QUARTZ LCD**

Ladies Day Watch only 25 x 20mm and 6mm thick. Hours, minutes, seconds, day, date, backlight and auto calendar. Elegant metal bracelet in silver or gold fully adjustable to suit very slim wrists. State colour preference.

£9.95 Guaranteed same day despatch



M15

**LADIES FASHION WATCH
QUARTZ LCD**

Lady's Fashion Watch. Elegant bracelet in bronze/gold finish or silver colour. Hours, minutes, seconds, day, date, backlight and auto calendar. Adjustable for the slimmest of wrists. State colour preference.

£14.95 Guaranteed same day despatch



M17

**LADIES COCKTAIL WATCH
QUARTZ LCD**

Lady's Cocktail Watch. Highly functional watch which also suits those special occasions. Beautifully designed with a very thin bracelet which retains strength as well as elegance. Hours, mins, secs., day, date, backlight and autocalendar. Bracelet fully adjustable to suit slim wrists. State gold or silver finish.


£19.95

Guaranteed same day despatch



M18

**HANIMEX
Electronic
LED Alarm Clock**

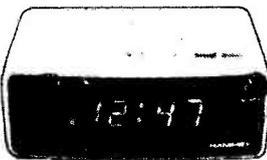

Features and Specifications:
Hour, minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).

£10.20 Thousands sold!
Mains operated.

Guaranteed same day despatch.

M13

**EXECUTIVE
ALARM WATCH**

6 functions plus alarm: Conference signal, 5 minute snooze alarm. Conference signal sounds 4 secs. before main alarm to give advance warning and option to cancel. Snooze sounds 5 mins. after main alarm and is always preceded by the conference signal.

£14.95



M60

**MACY QUARTZ
ANALOGUE**

Automatic calendar day and date, infinite bracelet. This man's watch has elegance as well as the robust appearance provided by a watch with traditional features. Accuracy is provided by a quartz crystal powered by a long life miniature battery.

£24.95



M21

Metac price break-through for an Alarm Chronograph with Dual Time

Only **£16.95**



OUTSTANDING FEATURES

- ★ **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing
- ★ **CALENDAR FUNCTIONS** include the date and day in each time zone.
- ★ **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes and 59.9 seconds. On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- ★ **ALARM** can be set to any time within a 24-hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

Metac Wholesale:
Trade enquiries — send for a complete list of prices for all the goods advertised plus many more not shown, also minimum order details.
Telephone orders: Credit card customers can telephone orders direct to Daventry (03272) 76545 or Edgware Road 01-723 4753 24 hours a day.

Service Enquiries: 03272-77659
CALLERS WELCOME. Shops open 9.30am-6.00pm.




Metac ELECTRONICS & TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

SEIKO MEMORY BANK

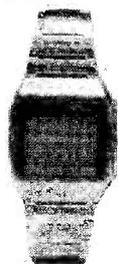Calendar watch M354
Hours, mins., secs.
Month, day, date in
12 or 24 hour format
all indicated continuously.
Monthly calendar display
month, year and all dates
or any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advance.
2 year battery life.
Water resistant.



Metac Price **£79.50** **M11**

SEIKO ALARM CHRONOGRAPH

With WEEKLY Alarm.
Hours, mins, Secs.
month, date, day,
am/pm.
Weekly alarm — can
be set for every day at
designated time, e.g.
6.30am on Mon.,
Wed. and Friday.
Alarm set time
displayed above time
of day.
Full stopwatch
functions, laptime,
split, etc.



Price **£89.95** **M10**

SEIKO MELODY ALARM CHRONOGRAPH

Chiming Alarm, plus
chrono. Hours, mins,
secs, date, day,
24-hour alarm, 12
hour chronograph,
1/10th secs, laptime,
back light, stainless
steel, mineral glass.

Metac Price **£92.95** **M19**

SEIKO CALCULATOR WATCH

Full specification
calculator with
memory, plus multi
function watch.
Hours, mins, secs,
day, date, backlight.
Automatic calendar.
Long-life battery.



Price **£96.20** **M27**

CASIO CHRONO 95QS-3LB

Stainless steel case,
water resistant to 66
feet. Hours, mins, secs,
am/pm, year, month,
date, day. Auto-calendar
pre-programmed until
year 2029. 12/24 hour
stopwatch function.
Range 7 hours, 1/100
sec. (Mode). Net
time/lap-time/1st-2nd
place times. Dual time
function. Accuracy
15secs. per month.
Battery life approx. 4
years.



Price **£22.95** **M22**

CASIO LADIES 86CL-23B-1

Elegant slim line stainless
steel bracelet, fully
adjustable. Hours, mins,
10 sec. symbol second by
flash, am/pm. Month,
date, day. Auto-calendar
pre-programmed for 28th
day in Feb. Accuracy per
month 15 secs., battery life
approx. 15 months.



Price **£29.95** **M23**

CASIO F-200 SPORTS CHRONO

Attractive man's watch
in black resin with
mineral glass. Hours,
mins, secs, am/pm.
Month, date,
alpha-numeric day.
Auto-calendar set 28th
Feb. Stopwatch
working range 1 hour
units 1/100 sec.
Mode, Net time/lap
time/1st-2nd place
times. Accuracy
approx. 15 secs per
month. Battery 12
months.



Price **£14.95** **M24**

CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs,
day, and also day,
month and year
perpetual automatic
calendar. 100th sec
chronograph to 7
hours. Net time/lap
time/1st and 2nd
place times. User
optional 12/24 hr.
display. 24 Alarm.
User optional, hourly
chime. Backlight,
mineral glass, stainless
steel. Water resistant to
100ft. Battery life
approx. 4 years.



Price **£34.95** **M25**

BELTIME CHRONOGRAPH

9 Functions
Hours, mins, secs,
day, date, month,
interchange feature,
automatic calendar,
backlight, net time/lap
time. Stainless steel
bracelet. Battery life 1
year.



Price **£14.95** **M34**

BELTIME MULTI ALARM

29 Functions
Hours, mins, secs,
date, day. Alarm,
chronograph, light.
Watch 8 functions,
Alarm 4 functions,
chronograph 17
functions. Stainless
steel bracelet.



Price **£29.95** **M35**

CASIO F-8C

3 Year Battery Life


Hours, mins, secs,
am/pm, date, day
Auto calendar set
28th Feb. Stopwatch
function. Accuracy 15
secs. per month.
Battery life approx. 3
years.



Price **£9.95** **M36**

CASIO CALENDAR 200

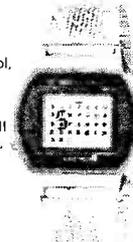47CS-23B-1Black
Stainless steel. Hours,
mins, 10 second symbol,
second (by flash),
am/pm. Month, day,
date. Auto calendar set
from 1901 to 2009. Full
month calendar display,
dual time function.
Accuracy 10 secs. per
month. Battery life
approx. 15 months.



Price **£59.95** **M37**

MELODY MULTI-ALARM CHRONOGRAPH



Hours, mins, secs, day, date, countdown
alarm, dual time zone, 1/100th sec.
stopwatch. Lap/split time, 1st and 2nd
place times. Melody test function.

Price **£26.95** **M30**

DUAL TIME-ALARM CHRONOGRAPH



Incorporating module of world-famous
Japanese watch manufacture. Hours,
mins, secs, day of week, month, day and
date, 24 hour alarm, 12 hour chrono-
graph, 1/10th secs, lap time, backlight,
stainless steel case and bracelet, mineral
glass, battery hatch, long life battery.

Price **£35.00** **M12**

PICOQUARTZ MICROPROCESSOR ALARM CHRONOGRAPH



Multi-language — day of the week can be
set to English, French, German, Italian or
Spanish. Chime — every full hour com-
bined with a response signal, beeping at
every pressing of the functions. Can be
switched off. 12-24 hour format, back-
light, Chrono — 1 full-scale chrono with
lap, counting hours, up to 24 hours.
Minutes, secs, 1/100th secs. Two Alarm
systems. Two time zones.

Price **£37.95** **M32**

SEIKO CHRONOGRAPH



Hours, mins, secs and day of the week,
Month, date and day of the week. Stop-
watch display. Hours, mins, secs up to 12
hours. Minutes, secs 1/100 sec up to
20 minutes. Lap timing, continuous time
measurement of two competitors. Stain-
less steel, mineral glass.

Price **£56.00** **M33**

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

**DIGITAL
CLOCK RADIO**



Mains. AM/FM/LW radio. Green digital display. Snooze alarm. Auto switch off. Clock dimmer. External FM Aerial.

£19.95

plus £1.30 Post & Packing

M40

**Portable LCD
Clock Radio**




- ★ Back-light.
- ★ Batteries supplied free.
- ★ Quartz crystal controlled.

£17.95

M41

**DIGITAL CLOCK LCD
Travel**

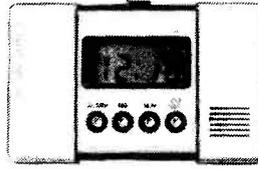


Hours, mins. 24 hour time and Alarm. Snooze timer. Large 12.5mm display. Night light. Size: 120mm x 74mm x 19mm. Weight: 120 grams.

£17.65

M42

**QUARTZ ANALOGUE
CLOCK TRAVEL**

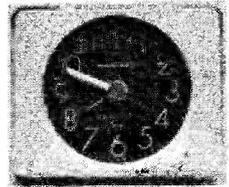


Mini Quartz Alarm clock. Complete with travel pouch. Features loud alarm and operates from 1½ volt battery.

£9.95

M43

LCD Calculator

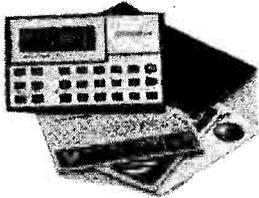


Credit Card size Memory % ect plus auto power off.

£7.95

M44

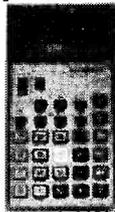**Digital Clock/Alarm/
Calculator/
Stopwatch**




Calculator with % and memory. Continuous clock with hours, mins., secs., day, month, day of week. Alarm, Stopwatch, split-time. 1 year battery. Leatherette wallet.

£17.95

M45

**LCD CALCULATOR
SCIENTIFIC**

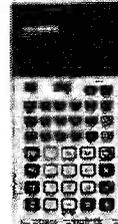

8-digit mantissa, 2-digit exponent electronic calculator on one single chip.


Functions-SIN, COS, TAN, SIN-1, COS-1, Tan-1, SINH, COSH, TANH, e^x, 10^x, Ln, Log, Y^x, 1/x.

Statistical functions

£16.95

M46

**LCD CALCULATOR
CASIO MELODY 80**

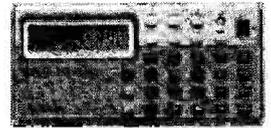

Full calculator spec 3 independent musical alarms time, stop-watch, countdown timer

£23.95

M47

TV GAMES



Black & White or Colour. 4 game. 2 ball speed, 2 ball angles, 2 battery sizes. Tennis, Hockey, Football, Handball, Practice.


£11.95 Colour

£8.95 B/W

plus 54p Post & Packing

M48

TV GAME WITH GUN

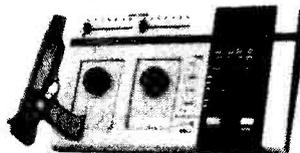


Colour. 6 games. Moving target. Football, Target, Tennis, Squash, Practice. Battery or main.

£17.95

plus £1.25 Post & Packing.

M49

**AIR FRESHENER
Electronic**

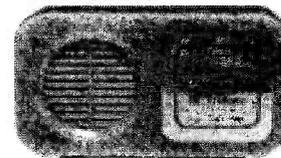

Timer can be set to emit nice smells when required or running permanently to remove really bad smells. Battery operated.

Price £4.95

M50

**DIGITAL
CLOCK**

LED Display. Features Hours/mins. Display Alarm with snooze. Mains operated excellent value for money. Compact size only 6 1/2 in x 2 1/2 in x 3 in.

£6.95

M51

**RADIO/CASSETTE
3-Band/LW-MW-FM**



Auto stop. DC6V, AC Power 220V. Built-in condenser microphone. High power output

M52

**RADIO/CASSETTE
1-Band/MW**




Condenser microphone. Battery or AC. Pushbutton key operation. Auto level control. Retractable handle. Eject equipment.

£17.95

plus £2.00 Post & Packing

M53

**MAINS/BATTERY
Portable Radio**

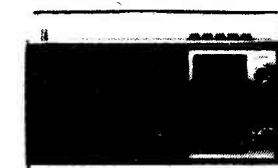


4 Bands, LW/MW/SW/FM. Teak finish case.

£19.95

plus 85p Post & Packing

M54

AIRCRAFT RADIO

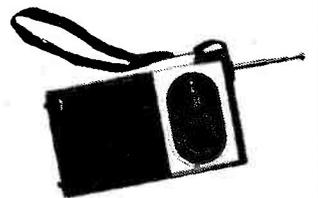

AM/FM. Receives Police/Aircraft frequencies. Battery operation. Retractable aerial.

£9.95

M55

**RADIO
CONTROLLED
CAR**

Formula One Racer. 4 function, forward, reverse, steering left to right. No wires, remote control.

£19.95

M56

**MODEL CAR
RADIO**

Scale model car incorporating single band radio. Excellent quality sound with clever design of controls incorporated in the car components.

£5.95

M57

**ELECTRIC
CAR AERIAL**

Sonix automatic motor antenna. 5 sections. One meter in length. Excellent value at

£10.95

M58

**CAR RADIO/
CASSETTE**

2 band car radio/stereo cassette player. Long and Medium waveband coverage. Rotary controls for on-off/volume, tone, balance and tuning. Push-button control for cassette eject and fast forward wind. Output 2x3 Watts (music) 12 volts.

£34.95

M59

Metac

**ELECTRONICS
& TIME CENTRES**

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

FUNCTION GENERATOR

A wide range (1 Hz - 100 kHz) sine/triangle and square wave generator with built-in analogue frequency meter.

A really nice piece of test gear from ETI.



The main characteristic of a function generator is that it produces a basic fixed-amplitude waveform other than a sine wave, from which a fixed-amplitude sine wave is then synthesised. The main advantage of this technique is that the resulting output waveforms of the generator are immune to amplitude 'bounce' when they are swept through their frequency ranges, thus enabling amplifier or filter gain/frequency tests, etc. to be carried out very rapidly. The only disadvantage of the technique is that the resulting sine wave has an inherently higher degree of distortion than is obtainable from good 'Wien bridge' and similar 'tuned' oscillator circuits.

The ETI function generator produces three output waveforms (sine, triangle and square) and covers the frequency range 1 Hz to 100 kHz in five decade ranges. The sine wave output typically produces a THD (total

harmonic distortion) value of only 0.5%, has a maximum amplitude of 2 volts rms, and is ideal for general purpose testing. The triangle output has a typical linearity of 1%, a maximum peak-to-peak amplitude of 5V6 and is ideal for cross-over distortion testing of class-AB amplifiers, etc. The square wave output is positive-going, has a maximum peak amplitude of 8 volts, has typical rise and fall times of less than 200 nS and is ideal for testing digital circuits. All output waveforms of the generator are DC coupled, with the sine and triangle waveforms swinging symmetrically about the zero volts line.

Our function generator incorporates a number of additional, very attractive features. It has a built-in analogue frequency meter, for ease of calibration. It has two output terminals, each with its own attenuator network. A sine or triangle waveform is available from one output and a

PARTS LIST

RESISTORS All 1/4W, 5%

R1,2,14	10k
R3,17	1k0
R4,5,10	2k2
R6,7,9	22k
R8	470R
R11,18	100R
R12,13,15,	47R
16	
R19	11R

POTENTIOMETERS

RV1,2	47k cermet multiturn (3/4")
RV3	22k cermet multiturn (3/4")
RV4	470R cermet multiturn (3/4")
RV5	4k7 cermet multiturn (3/4")
RV6	100k lin. dual gang
RV7-10	10k
RV11	100k cermet multiturn (3/4")
RV12,13	1k0 lin

CAPACITORS

C1,2	100u 25V electrolytic
C3,9	50p polystyrene
C4,13	10n polyester
C5,10,14,11	100n polyester
C6,15	1u0 polycarbonate
C7,8	10u 25V electrolytic
C12	1n0 polystyrene

SEMICONDUCTORS

IC1	XR2206CP
IC2	NE555
Q1,3	BC182L
Q2,4	BC212L
D1-3	1N4148
ZD1	BZY885V6

MISCELLANEOUS

SW1	DPDT (PCB type) toggle.
SW2	4 pole 5 way wafer switch assembly and 2 PCB wafers (2 pole 6 way)
SW3	DPDT toggle
SW4	1 pole 3 way rotary switch


2 BNC connectors, 2 PP7 batteries, case to suit, PCB.

square wave is available from the other. The square wave output is available at all times, is synchronous with the sine/triangle waveform and can thus be used to provide synchronisation signals to an oscilloscope timebase during sine wave testing, etc. The unit is battery powered, for maximum user convenience.

A fine unusual feature is that the frequency ranges are alternately contra-connected, so that to increase frequency you turn the 'fine' control clockwise on one range, anticlockwise on the next range and clockwise on the next range, etc. This facility enables the frequency to be swept through several decades very rapidly when testing the frequency response of amplifiers and filters, etc. As we said in the introduction, this is a really nice piece of test gear.


Construction

Most of the circuit is built up on a single large PCB. Various points should be noted before starting construction. First, note that 4-pole 5-way range switch SW1 is mounted directly on the PCB and in fact is a 6-way PCB type (see Buylines) with one of the 'ways' unused. The next point to note is that the C6 (1u0) and C7 (10u) main timing capacitors are non-electrolytic types. We obtained ours from Electrovalue.

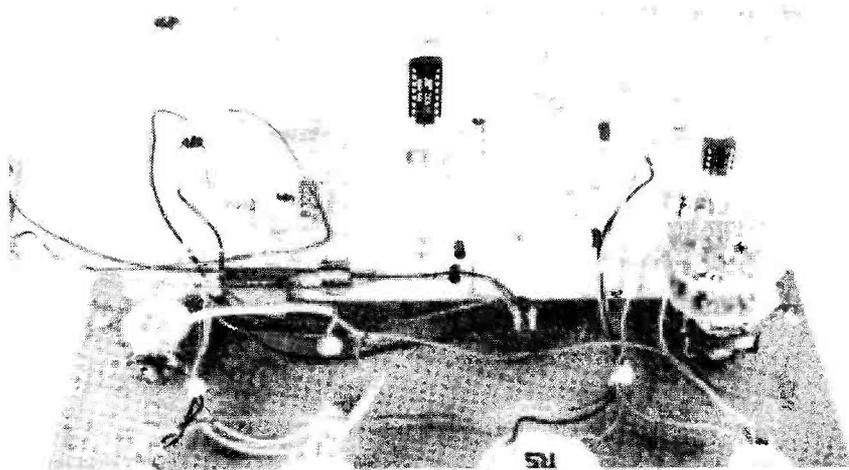

SPECIFICATION

Frequency range	1 Hz to 100 kHz in 5 decade ranges.
Output waveforms:	
Sine: distortion (typical)	0.5% at 1 kHz.
Triangle: linearity (typical)	1% at 1 kHz.
Square: rise/fall times (typical)	less than 200 nS.
Waveform stability (typical)	.002% per °C.
	.01%/V supply sensitivity.
Maximum output levels (with 9-0-9 V supply).	Sine = 2 V rms.
	Triangle = 5V6 pk-pk.
	Square = 8 V peak.
	Two 9 V batteries.
	30 mA typical.
Supply	
Total current consumption	

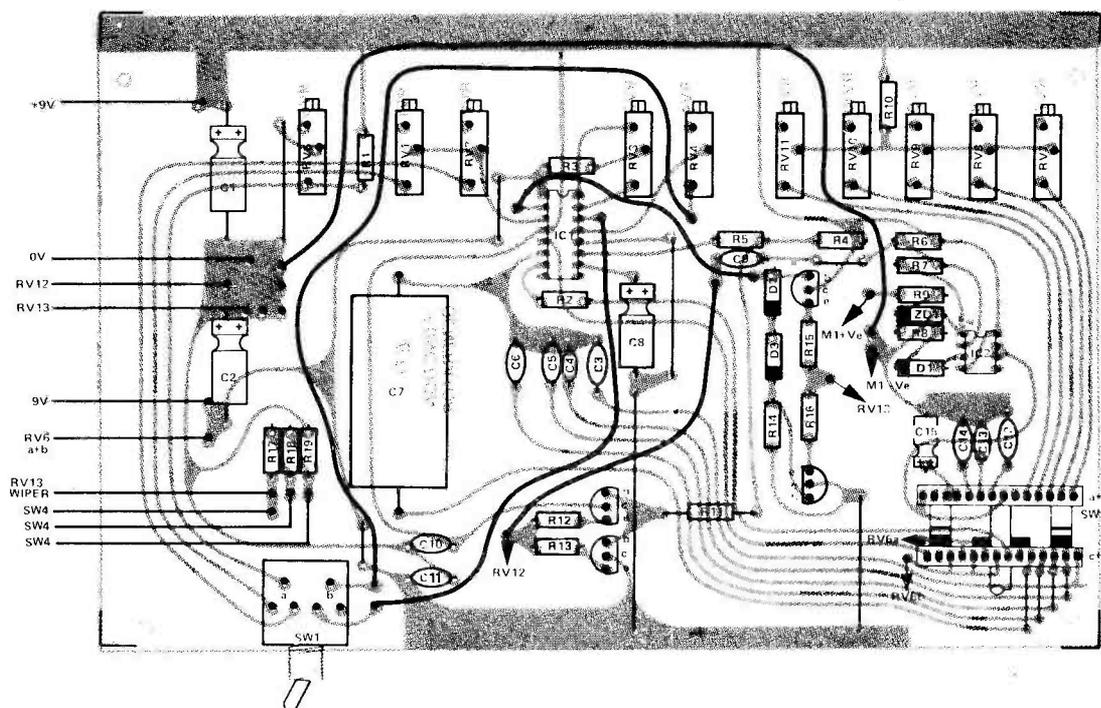

At this stage access to a distortion meter is desirable, so that RV3 and RV4 can be trimmed for minimum distortion. With care, a third figure of 0.5% can be obtained. In the absence of a distortion meter, the simple twin-T 1 kHz filter of Fig. 2 can be used in conjunction with the oscilloscope or with a millivoltmeter to set the generator for minimum distortion at 1 kHz. The procedure is to apply the sine wave output of the generator to the input of the filter at about 1 volt rms at approximately 1 kHz and take the output of the filter to the input of the scope or millivoltmeter. Next, adjust the generator frequency and R4 of the filter to give minimum output indication and, finally, adjust RV3 and RV4 of the generator to reduce the output indication of the filter to the minimum possible value. At final balance, the output of the filter corresponds to approximately 0.1% thd per mV rms of indicated reading, ie if the indicator shows a reading of 5 mV rms, the thd of the generator approximates 0.5%. Now retrim OFFSET control RV5. The sine wave calibration procedure is then complete.

(3). Set the unit to TRIANGLE mode. Monitor the waveform on the scope and adjust RV2 for a pk-pk amplitude of 5V6.

(4). Check that the unit is functional on all ranges, in all waveform modes.

(5). Switch the unit to its top frequency range, set the output frequency to 100 kHz and adjust RV7 for full scale deflection. If necessary, slightly reduce the value of C3 so that 100 kHz can be obtained.

(6). Repeat the frequency calibration procedure on all ranges, using the

appropriate pre-set (RV8 to RV11), noting that a very 'jerky' reading will be obtained on the lowest (1 Hz to 10 Hz) range. The calibration procedure is then complete, and the unit is ready for use.

A final point to note is that we used 10-turn cermet for all pre-sets on our prototype unit. A slight touch of luxury, this. You can get away with ordinary presets, if you prefer, but in this case you'll have to make slight modifications to the PCB.


Actual construction on the PCB is fairly straightforward, but take extra care to observe the polarities of all electrolytics and all semiconductor devices. When construction is complete, fit the board into a suitable case and complete the interwiring to the remaining switches, pots and to the moving coil meter. The unit is then ready for testing and calibration.

CALIBRATION

Calibration of the unit is fairly tricky and requires access to an oscilloscope and some kind of frequency reference (you can use the scope timebase as a reference if it is known to be reasonably accurate). The calibration procedure is as follows:

(1). Set the unit to the SINE mode. Set the attenuator controls for maximum output. Set the frequency controls for approximately 1 kHz on the 1-10 kHz range. Set all pre-sets at mid value. Switch the unit on, and use a scope to check that some kind of waveform is available (the waveform may be pretty awful at this stage). Check that the frequency is variable via RV6.

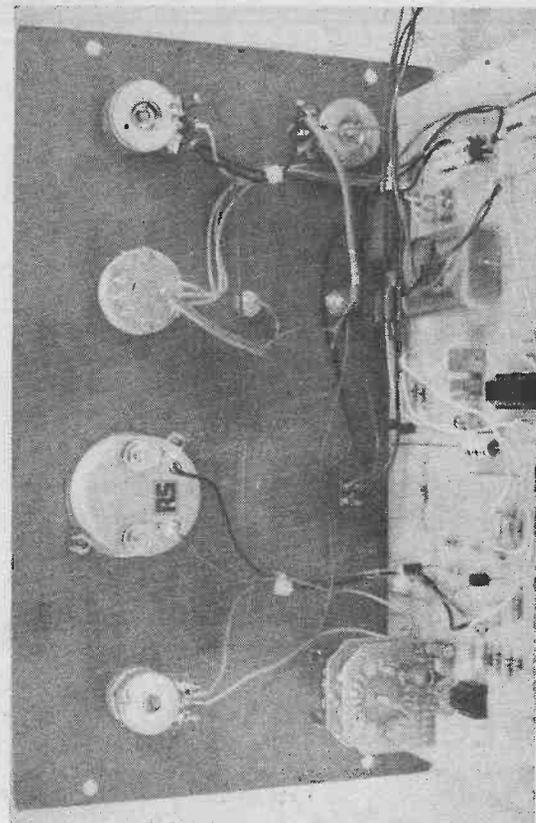(2). Reset RV6 for a 1 kHz output and adjust RV1 for a pk-pk amplitude of about 5V6. Adjust RV4 for a 'passable' sine wave, and then readjust RV1 for 5V6. Now alternately adjust RV4 for MINIMUM DISTOR-



Rear view of the front panel controls.

HOW IT WORKS

There is not an enormous amount we can say here, since most of the work of the circuit is carried out inside IC1, which is a special function generator chip that produces a square wave output from pin 11 and a sine or triangle wave from pin 2. The purity of the sine wave can be trimmed via RV3 and RV4 and the maximum amplitude can be pre-set via RV1. The maximum triangle amplitude can be pre-set via RV2 and both waveforms can be offset via RV5. The sine/triangle waveforms are made available to the outside world via buffer amplifier Q3-Q4 and the associated attenuator network. The square wave is made available, in positive-going form only, via the Q1-Q2 buffer and RV12.

The operating frequency of the generator is variable via timing capacitors C3 to C7 and via resistor network R2-RV6. The frequency is monitored on a simple analogue frequency meter that is designed around 555 timer IC2, which is triggered via the square wave output of the Q1-Q2 buffer amplifier.

The entire circuit is powered from two 9 volt batteries, and the circuit consumes a typical total current of about 30 mA.

and RV3 for best SYMMETRY, occasionally readjusting RV1 for 5V6 pk-pk until a good sine wave is produced. Adjust RV5 for zero offset (so that the output waveform swings symmetrically about the zero volts level) and retrim RV3 and RV4 for a good sine wave.

BUYLINES

The 10µ (C7) capacitor can be purchased from Electrovalue Ltd. All other components used in the function generator should be readily available from major mail order companies that advertise in this issue.

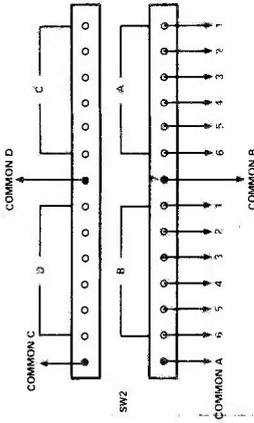


Fig 3 Range switch wafer pin-out.

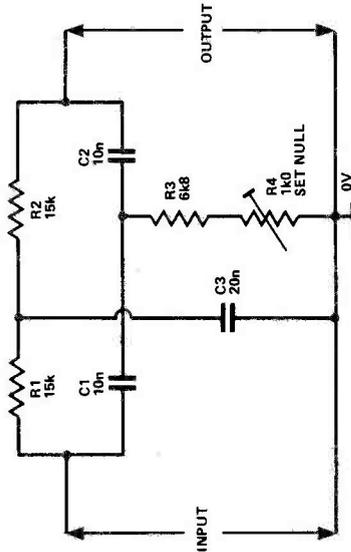


Fig 2 This simple twin-T filter can be used to set the generator for minimum distortion.

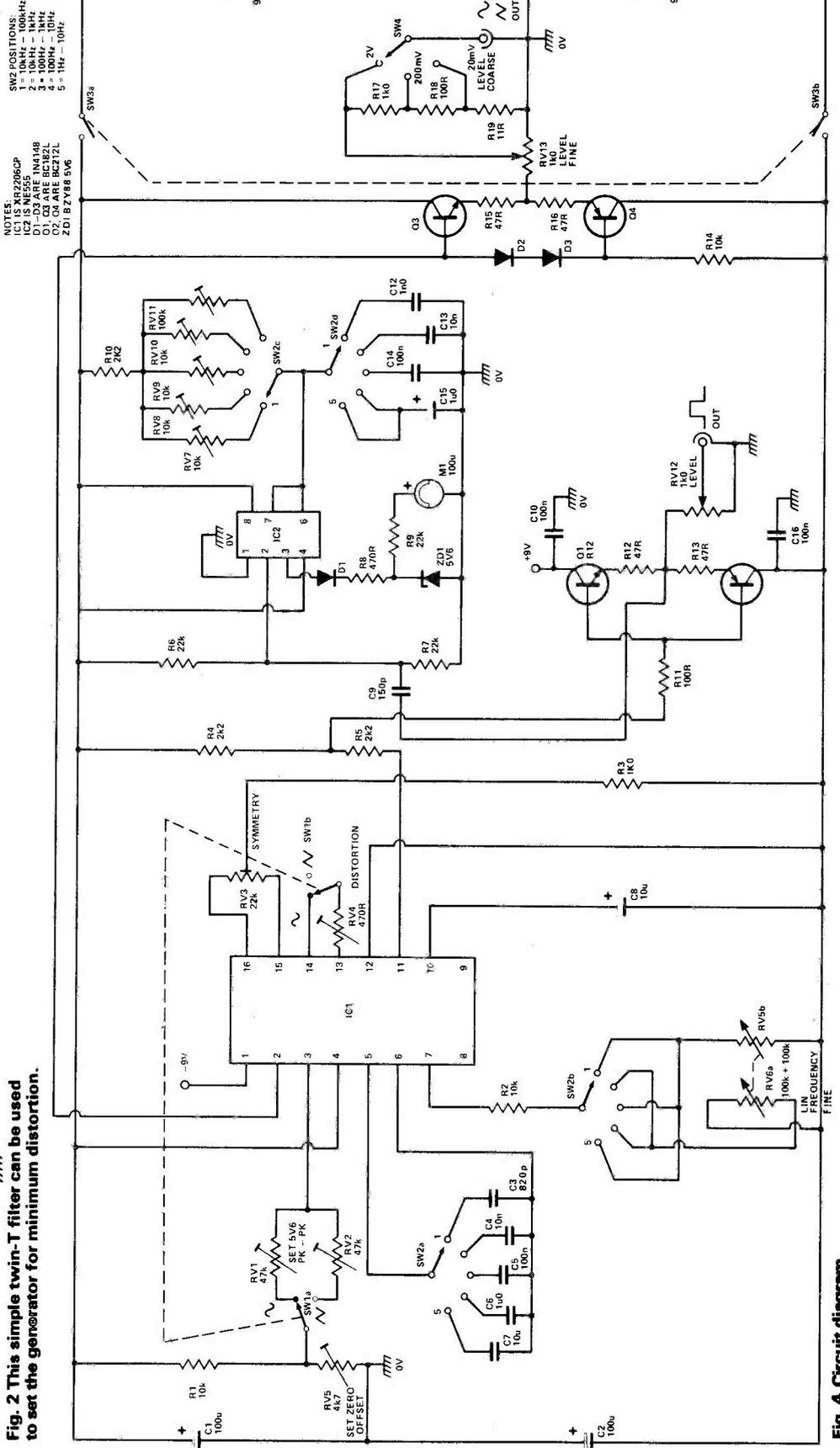


Fig 4 Circuit diagram.

- NOTES:
- IC1 IS XR2206P
 - D1, D2 ARE 1N4148
 - D3 ARE BC182L
 - Q1, Q3 ARE BC182L
 - Q2, Q4 ARE BC212L
 - ZD1 BZ788 5V6
- RANGE POSITIONS:
- 1 - 10kHz - 100kHz
 - 2 - 10kHz - 1kHz
 - 3 - 100Hz - 1kHz
 - 4 - 10Hz - 10kHz
 - 5 - 1Hz - 10Hz

24 TUNE DOOR CHIMES

DOOR TUNES £17.13 + VAT

Waddington's Videomaster announce a doorbell that doesn't go Brrringo, Ding-Dong or Bzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



T.V. GAMES

PROGRAMMABLE £28.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At last long a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES:

ROAD RACE - £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises SUPER WIPEOUT - £8.17 + VAT.

10 different games of blasting obstacles off the screen.

STUNT RIDER - £12.16 + VAT.

Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.

NON PROGRAMMABLE TV GAMES

6 Game - COLOURSCORE II - £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS

STAR CHESS - £86.00 + VAT.

PLAY CHESS AGAINST YOUR PARTNER.

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 - £26.85 + VAT.

PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.



ELECTRONIC CHESS BOARD TUTOR

£17.17 + VAT

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.

OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

CHESS CHAMPION - 6 LEVELS £47.39 + VAT.

CHESS CHALLENGER - 10 LEVELS - £139.70 + VAT.

BONIS - MULTI-LEVEL TALKING DISPLAY £162.94 + VAT.

DRAUGHTS COMPUTERS

CHECKER CHALLENGER 2 LEVELS £43.00 + VAT

4 LEVELS £78.00 + VAT

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling - demonstrations daily - open from 9am to 5pm Mon Sat (9am to 4pm Wed)

To order by telephone please quote your name, address and Access/Barcode number

Postage and Packing FREE

AJD DIRECT SUPPLIES LIMITED, Dept. ET 12 102 Bellegrove Road, Welling, Kent DA16 3DD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

DL1000K

This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.60



DLZ1000K

A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00
Optional Opto Input (DLA1) 60p



MINI KITS

These KITS form useful subsystems which may be incorporated into larger designs or used alone. KITS include PCB, short instructions and all components

TEMPERATURE CONTROLLER / THERMOSTAT. Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 500W £3.20 1KW £3.50

SOLID STATE RELAY. Ideal for switching motors, lights, heaters, etc. from logic. Opto isolated with zero voltage switching. Supplied WITHOUT triac. Select the required triac from our range. £2.60

BAR/DOT DISPLAY. Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

RESISTORS

1/4W 22 ohm-10M E12 Series 10p
Pack of 10 (one value) 80p
10 Packs

DIGITAL VOLTMETER / THERMOMETER KIT



Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display.

Components are also included to enable the basic DV kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V Supply (PP3 battery). £20.75

LEDS DISPLAYS

0.1" Red	DL727 D 5"	
0.2" 9p	2-digit CA	£1.00
Red 9p	DL304 (pin compatible with DL704) 0.3" CC. Red	70p
Green 12p	DL847/OL850 (pin compatible with DL747/750) 0.8" CA/CC	£1.80
Yellow 12p		
Square Red	LIQUID CRYSTAL DISPLAY	
5x2.5x9mm 20p	pin dip 40	1234
	pin dip	£8.10
SPECIAL OFFER		
25 off 0.2"		
Red	★ SPECIAL ★ IL74 Opto Isolat	45p
Green	tor	
Yellow		£2.00

TRIACS

400V Plastic Case (Texas)			
3A	48p	15A	90p
6A	62p	20A	185p
12A	70p	25A	190p
6A with trigger			80p
8A isolated tab			82p
Diac			18p


INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	18p
AY-5-1224 Clock	£2.60
AY-5-1230 Clock/Timer	£4.50
AY-5-1232 Clock/Timer	£4.60
ICL7106 D.V.M. (LCD Drive)	£7.00
TDA1024 Zero Voltage Switch	£1.20
LM10C Op Amp	£2.99
LM3911 Thermometer	£1.20

ALL COMPONENTS ARE BRAND NEW AND TO MANUFACTURERS SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 30p P&P. MAIL ORDER - CALLERS WELCOME BY APPOINTMENT.

TK Electronics

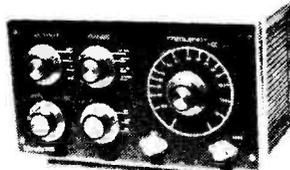(E1) 106 STUDLEY GRANGE ROAD LONDON, W7 2LX TEL. 01-579 9794



LOW COST AUDIO SIGNAL GENERATORS

(Sine & Square Waves)
10Hz-100kHz
Very low distortion (-0015%)
£36 (or in kit form £31)
+ Tax 15%

Model 146

Low cost version, A0113 (0.2% dist), £27.50 (Kit £23). Other instruments include: Millivoltmeter, Tachometer, Noise level meter, Distortion Analyser, F.M. Sig. Gen. Crystal Frequency Standard. KEF Speaker Units. Send S.A.E. for lists. VAT extra 15%. Post/Pkg. £1.75.

TELERADIO ELECTRONICS

325 Fore Street, Edmonton, N.9. 01-807 3719

Closed all day Thursday

ADVERTISERS PLEASE NOTE

DUE TO CHRISTMAS AND NEW YEAR WOULD ADVERTISERS PLEASE NOTE THAT THE COPY DEADLINE FOR THE FEBRUARY ISSUE HAS BEEN BROUGHT FORWARD ONE WEEK TO NOVEMBER 30TH

VFET APPLICATIONS

Is the VMOS power FET a really important device, or a mere flash-in-the-pan? In the next few pages

Project Editor Ray Marston appraises the device.

IMAGINE a power transistor that has virtually infinite input impedance, 'beta', and power gain which has a bandwidth extending from DC to 600 MHz and which can switch 1 A on or off in a mere four nanoseconds. Imagine also that this device is immune to secondary breakdown and has a negative temperature coefficient that minimises thermal runaway problems and enables devices to be directly paralleled for increased power handling capability.

The above 'miracle' device already exists, and is readily available at fairly low cost. It is known as a VMOS Power FET. VMOS Power FETs were first introduced by Siliconix in 1976. At that time they were hailed as "the most revolutionary semiconductor in decades — likely to eliminate bipolars within five years". Now, three years on, VMOS still hasn't made a great impact on the industrial or consumer market.

What Is It?

The term 'VMOS power FET' stands for 'Vertical structured Metal-Oxide Silicon power Field-Effect Transistor'. Conventional MOSFETs use the form of construction shown in Figure 1, in which current flows *Horizontally* from source to drain through the channel, which is induced on the top surface of the silicon substrate. This form of structure results in low current densities, poor heat dissipation capabilities, very limited power handling capacity and relatively large chip capacitance.

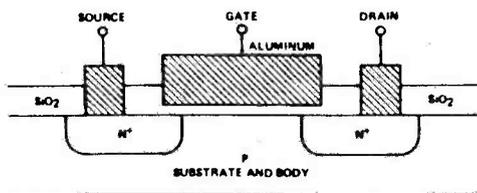


Fig 1. Cross Section of a conventional FET.

VMOS power FETs, on the other hand, use the form of structure shown in Figure 2, in which current flows *vertically* from source to drain. This structure results in high current densities, low saturation resistance, excellent heat dissipation and power handling capabilities, low chip capacitance and excellent wide band performance.

VMOS power FET technology has been pioneered by Siliconix, who currently produce a variety of such devices

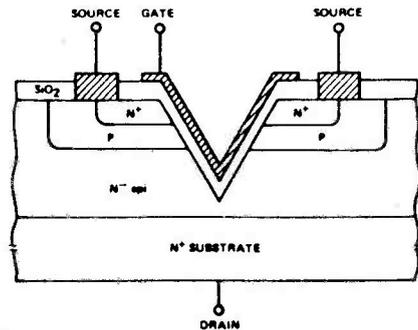


Fig 2. Cross Section of a VMOS power FET.

with maximum continuous drain current ratings ranging from a modest 500 mA up to a hefty 12A5, and with maximum drain-to-source voltage ratings ranging from 35 to 90V. All the products in their present VMOS range are n-channel enhancement-mode devices, in which the source-to-drain path is normally closed but can be opened by applying a positive gate voltage. The gate has a near-infinite input impedance.

A major defect of the existing VMOS technology is that it is not readily compatible with the production of p-channel devices. This factor greatly reduces the devices' attractions in audio power amplifier applications, where class-AB output stages are currently in vogue.

A more detailed account of VMOS construction and operation theory is given in the July '78 edition of ETI.

Characteristics

Figure 3 shows typical output and saturation characteristics of the type VN67AF VMOS power FET. Note the following points:

1 The device passes negligible drain current until the gate voltage reaches a threshold value of approximately 1 volt. The drain current then increases non-linearly as the gate is varied up to approximately 4 volts, at which point the drain current has a value of about 400 mA. The device, in fact, has square law transfer characteristics below 400mA.

2 The device has a highly linear transfer characteristic above 400mA (4V on the gate) and thus offers great potential as a low-distortion class-A power amplifier.

3 The drain current is controlled almost entirely by the gate voltage and is almost independent of the drain voltage so long as the device is not saturated. A point not shown in the diagram is that, for a given value of gate voltage, the

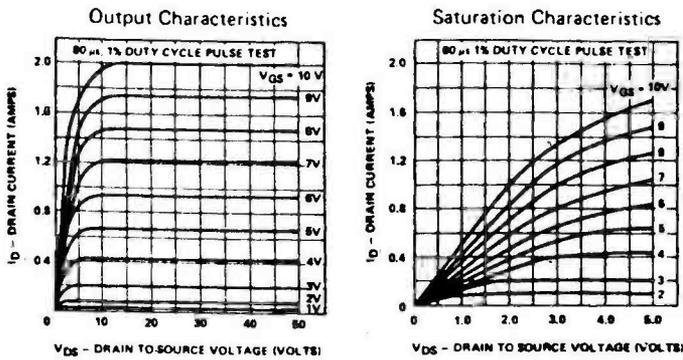


Fig 3. Output and saturation characteristics of the VN67AF VMOS power FET.

drain current has a negative temperature coefficient of about 0.7% per °C so that the drain current decreases as temperature rises. This characteristic gives a fair degree of protection against thermal runaway.

4 When the device is saturated (switched fully on) the drain-to-source path acts as an almost pure resistance with a value controlled by the gate voltage. The resistance value is typically 2R_O when 10 volts are on the gate, and 10R when 2 volts are on the gate. The off resistance of the device is in the order of megohms. These characteristics make the device highly suitable for use as a low-distortion high-speed analogue power switch.

Figure 4 shows the circuit symbol and the case outline of the VN67AF, which incorporates a 15V input-protection

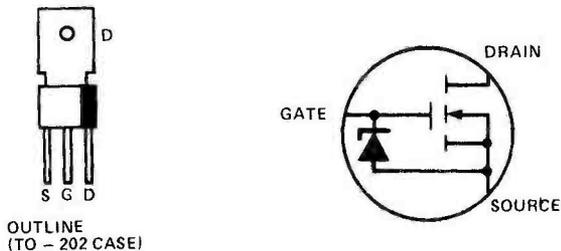


Fig 4. Symbol and outline of the VN67AF.

Zener and Fig. 5 summarises the static and dynamic characteristics of the device. Points to note here are that the input (gate-to-source) signal must not be allowed to exceed the 15V Zenering of the device and that the device has a typical dynamic input capacitance of only 50 p: this capacitance dictates the dynamic input impedance of the device. The static input impedance is of the order of a million megohms.

Digital Circuits


VMOS is delightfully easy to use in digital switching and amplifier applications. Figure 6 shows the basic connections. The load is wired between the drain and the positive supply rail and the digital input signal is fed directly to the gate. Switch-off occurs when the input goes below the gate threshold value (typically 1V₂). The drain on current is determined by the peak amplitude of the gate signal, as shown in Figure 3, unless saturation occurs. In most digital applications the on current should be chosen to ensure saturation.

STATIC	Maximum Drain-Source Voltage	60V
	Maximum Drain-Gate Voltage	60V
	Maximum Continuous Drain Current	2.0 A
	Maximum Pulsed Drain Current	3.0 A
	Maximum Continuous Forward Gate Current	2 mA
	Maximum Pulsed Forward Gate Current	100 mA
	Maximum Continuous Reverse Gate Current	100 mA
	Maximum Forward Gate-Source (Zener) Voltage	15V
	Maximum Reverse Gate-Source Voltage	-0.3V
	Maximum Dissipation at 25°C Case Temperature	15W
	Temperature Operating and Storage Range	-40 to +150°C
	Gate Threshold Voltage	0.8V min, 1.2V typical
	Zero Gate Voltage Drain Current	10uA Max at 25°C
	ON-state Drain Current at V _{GS} = 10V	1.0A min, 2.0A typical
	Forward Transconductance	250 millimhos typical
DYNAMIC	Input Capacitance	50pF typical
	Reverse Transfer Capacitance	10pF typical
	Common-Source Output Capacitance	50pF typical
	Typical switching times, 25 volt supply 23R load, 0-10V gate drive from a 50R source	Turn-ON Delay 2 nS Rise Time 2 nS Turn-OFF Delay 2 nS Fall Time 2 nS

Fig 5. Summary of the static and dynamic characteristics of the VN67AF.

The static input impedance of VMOS is virtually infinite, so zero drive power is required to maintain the VN67AF in the on or off state. Drive power is, however, required to switch the device from one state to the other. This power is absorbed in charging or discharging the 50p input capacitance of the VN67AF.

Fig 6. Basic VMOS digital switch or amplifier.

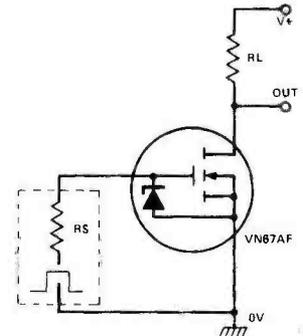

The rise and fall times of the output of the circuit are determined by the source impedance of the input signal, the input capacitance and forward transconductance of the VMOS device and the value of R_L. If R_L is large compared to R_S the VN67AF gives rise and fall times of roughly 0.11 nS per ohm of R_S resistance. Thus, a 100R source impedance gives an 11 nS rise or fall time.

If R_L is not large compared to R_S these times may be considerably changed. A point to note when driving the VN67AF is that its input Zener forward and reverse ratings must never be exceeded. Also, because of the very high frequency response of VMOS, the device is prone to unwanted oscillations if circuitry is improperly designed. Gate leads should be kept short, or be protected with a ferrite bead or small resistor in series with the gate.

VMOS can be interfaced directly with the output of CMOS, as shown in Figure 7. Rise and fall times of about 60 nS can be expected, due to the limited output currents available from a single CMOS gate. Rise and fall times can be reduced by driving the VMOS from a number of CMOS gates in parallel, as shown in Figure 8, or by using a special high-current driver.

VMOS can be interfaced with TTL (either standard or LS type) by using a pull-up resistor on the TTL output, as shown in Figure 9. The 5 volt TTL output of this circuit is

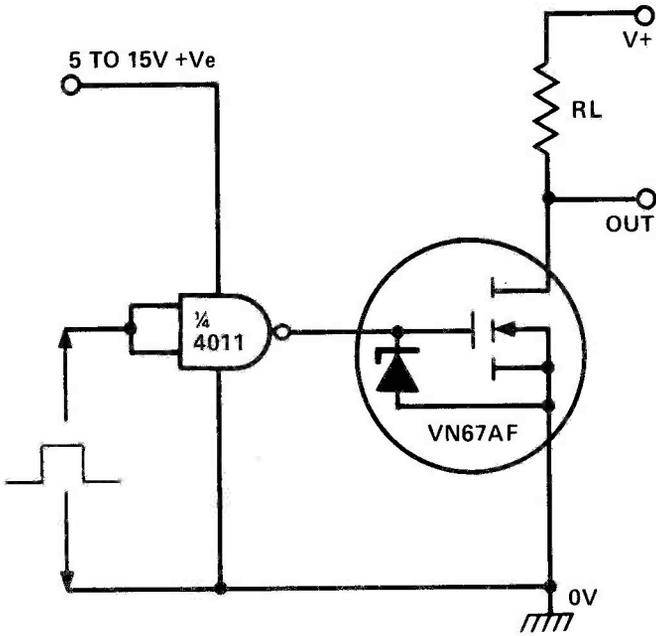


Fig 7. Method of interfacing VMOS with CMOS!

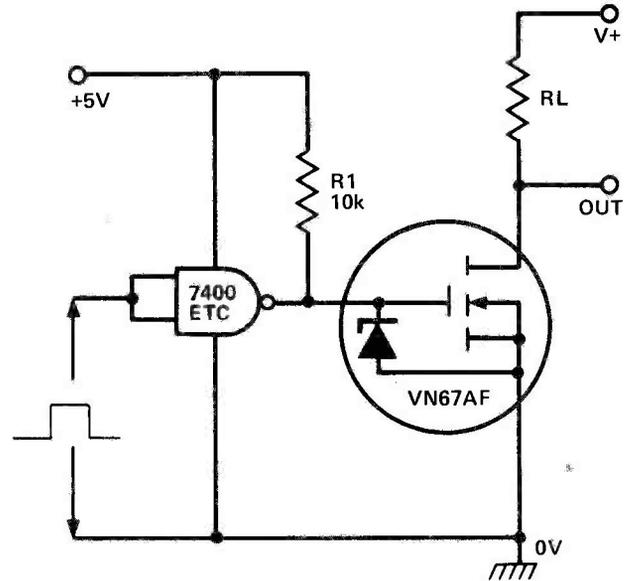


Fig 9. VMOS can be driven from the output of TTL if a pull-up resistor (R1) is used.

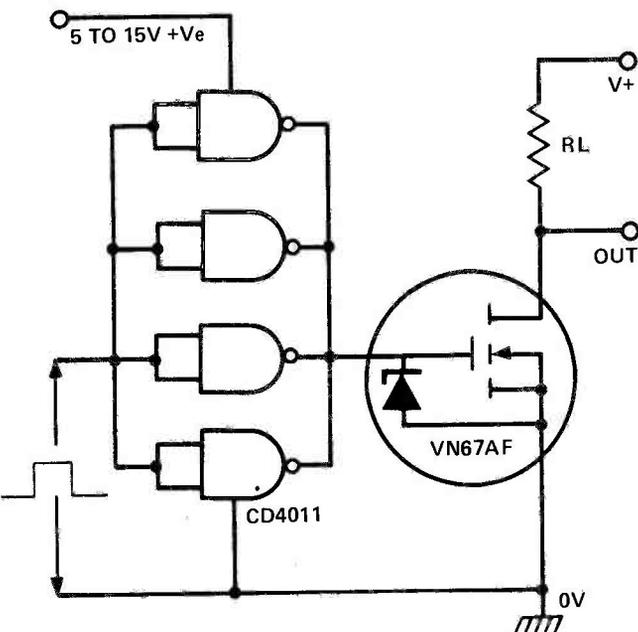


Fig 8. VMOS switching times can be reduced by driving with a number of gates in parallel. Typical $R_T = 25 \text{ nS}$.

sufficient to drive 600 mA through a single VN67AF. Higher currents can be obtained either by wiring a level shifter between the TTL output and the VN67AF input, or by wiring a number of VN67AFs in parallel as shown in Figure 10.

Analogue Circuits

VMOS power FETs can be used with relative ease in either the common source or common drain (voltage follower) modes. The voltage gain in the common source mode is equal to the product of R_L and the device's g_m or forward transconductance. In the case of the VN67AF, the device gives a voltage gain of 0.25 per ohm of R_L value, i.e., a gain of 4.0 with 16R load, or a gain of 25 with a 100R load. The voltage gain in the common drain mode is slightly less than unity.

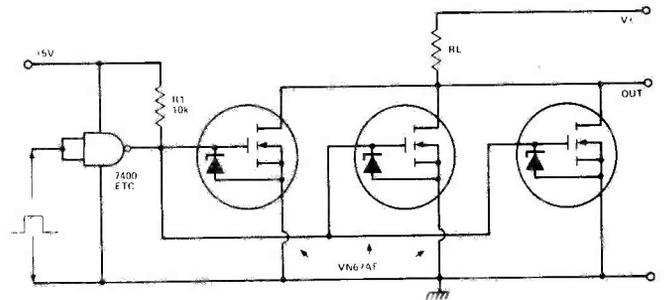


Fig 10. Boosting the output of Fig 9 by driving three VN67AF in parallel.

Fig. 11 shows three alternative basic ways of biasing the VMOS power FET for common source operation. In most practical applications, the device will be biased into the linear mode, with the drain at a quiescent value of approximately $V_{\text{supply}}/2$, so that maximal signal swings can be accommodated between the cut-off and saturation clipping levels.

In Fig 11a the gate is biased at a supposedly fixed level by potential divider R1-R2. The input impedance of the circuit is (at low frequencies) equal to the parallel values of R1 and R2. Defects of this simple biasing arrangement are that the voltage biasing level varies with the supply voltage, and the drain current biasing level depends on the characteristics of the individual VN67AF that is used in the circuit. An advantage of the circuit is that the quiescent drain voltage can be biased below that of the gate.

The alternative circuits of Figs. 11b and 11c can be used in cases where the quiescent drain voltage is greater than that of the gate. In Fig 11b, potential divider R1-R2 is fed from the drain of the VN67AF, and DC negative feedback makes the quiescent drain current substantially independent of variations in supply voltage and device characteristics. AC negative feedback also occurs, and reduces the effective input impedance to a value approximating the parallel values of R1 and R2 divided by the voltage gain ($g_m \times R_L$) of the circuit.

Figure 11c is a simple modification of the Fig 11b circuit, and results in increased input impedance. R3 is wired

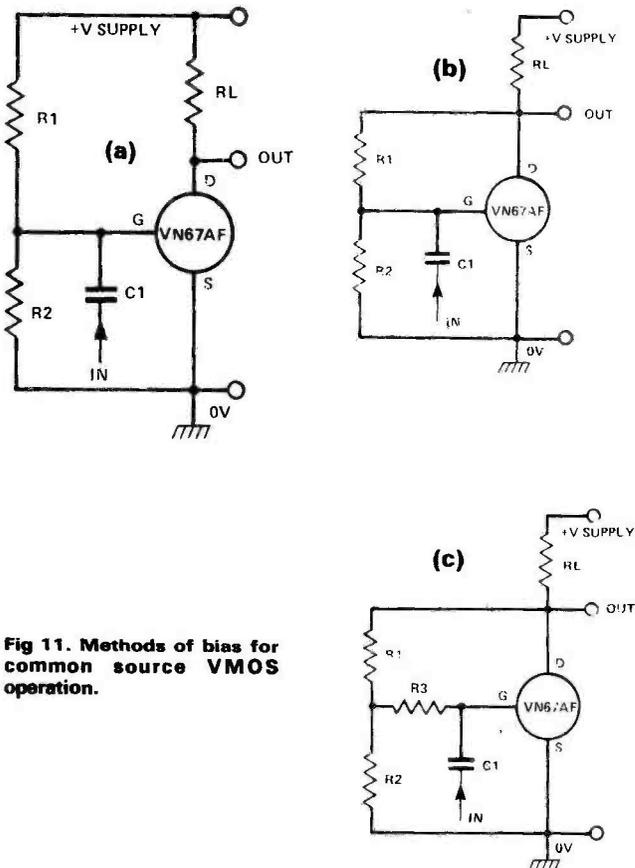


Fig 11. Methods of bias for common source VMOS operation.

between the gate of the VN67AF and the junction of R1-R2. R3 does not effect the biasing of the circuit, but if its value is large relative to that of R1 and R2 it raises the input impedance to a value approximating that of R3. If the source impedance of the input signal is low relative to R3, the AC negative feedback effects of the circuit are virtually eliminated and the input impedance is further increased. If, in the Fig 11c circuit, the drain is likely to swing below the desired gate bias level under active conditions, a capacitor can be wired across R2 to preserve stable biasing conditions.

Fig. 2 shows methods of biasing VMOS power FETs for common drain operation. In Fig. 12a the circuit is biased by a simple potential divider (R1-R2), and the source takes up a value a few volts below that of the gate. Because of the inherently high level of negative feedback of this configuration, the resulting bias (quiescent) source/drain current of the circuit is substantially independent of the characteristics of the individual VN67AF that is used. The input impedance of this circuit is equal to the parallel values of R1 and R2.

Figures 12b and 12c show how the input impedance of the basic Fig 12a circuit can be increased. In Fig 12b, R3 is given a value that is large relative to R1 and R2, thereby raising the input impedance to a value approximating that of R3 without effecting the biasing of the circuit. In Fig 12c the value of R3, and thus the input impedance, is effectively increased by a factor of $1/(1 - A_v)$ via bootstrap capacitor C2. Thus, if R3 is 10M and A_v is 0.95, the input impedance is raised to 20M. If R3 is 1M and A_v is 0.99, the input impedance is raised to 100M. C2 must have the

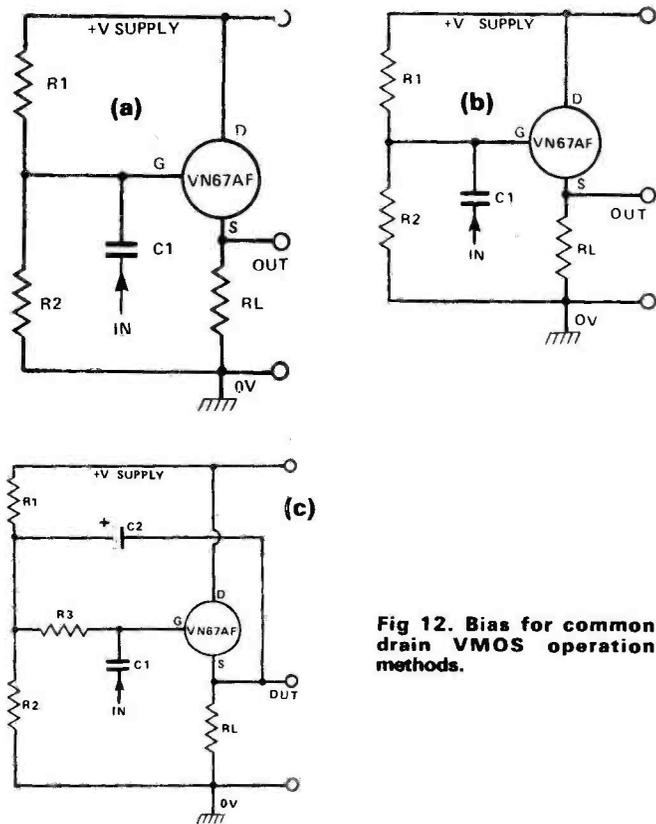


Fig 12. Bias for common drain VMOS operation methods.

impedance that is low relative to R1 and R2 over the required bandwidth of the amplifier.

Practical Circuits

The best way to get to know VMOS power FETs is to experiment with them in a few practical circuits. With this in mind, Figs. 13 and 22 show a few simple designs that you can play with. All of these circuits are based on the VN67AF, which typically costs less than a pound in one-off quantities.

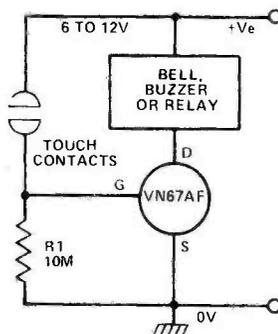


Fig 13. Touch switch.

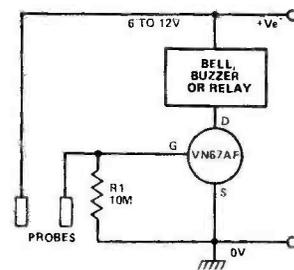


Fig 14. Water switch.

Figs. 13 and 14 couldn't be simpler. When the contacts/probes are open, zero volts are on the gate of the VN67AF and the device passes zero current. When a resistance (zero to tens of megohms) is placed across the contact/probes (by contrast with skin resistance, water, etc), a substantial gate voltage is developed by potential divider action and the VN67AF passes a high drain current.

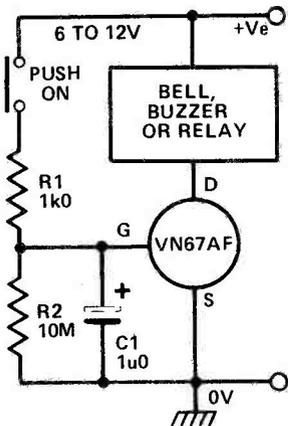


Fig 15. Delay turn off switch.

In the Fig. 15 circuit, C1 charges rapidly via R1 when S1 is closed and discharges slowly via R2 when S1 is open. Thus, the load activates as soon as S1 is closed, but does not deactivate until some tens of seconds after S1 is released.

Figs. 16 to 18 are lamp control circuits. In Fig. 16 the drain current and lamp brightness is controlled via RV1. In

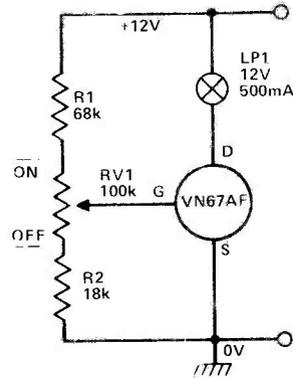


Fig 16. DC lamp dimmer.

Fig 17. Soft-start analogue lamp switch.

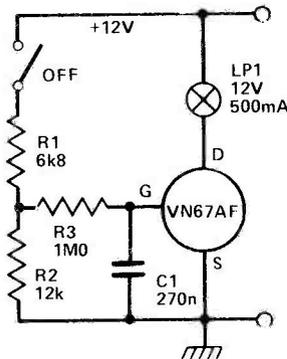


Fig. 17 the lamp turns on slowly when the switch is closed as C1 charges up via R3, and turns off slowly when the switch is opened as C1 discharges via R3.

The Fig. 18 circuit is a highly efficient 'digital' lamp dimmer. The two 4011 gates are connected as an astable

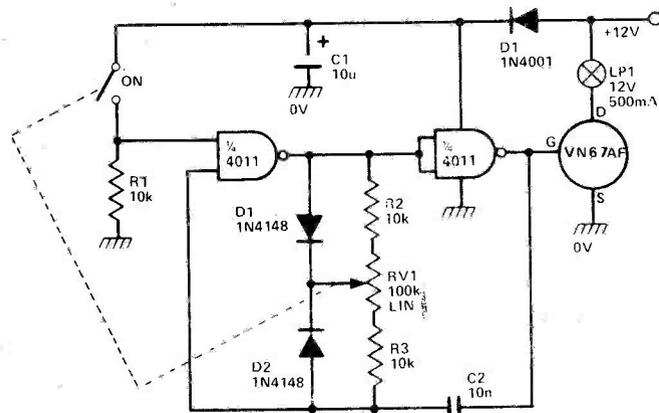


Fig 18. Digital DC lamp dimmer.

multivibrator that has a mark/space ratio that is variable from 10:1 to 1:10 via RV1, and has its output fed to the gate of the VN67AF, thereby enabling the 'mean' lamp

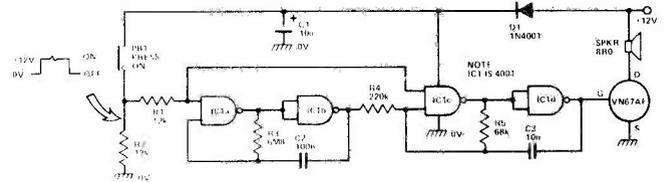


Fig 19. Warble-tone alarm (2 tone output).

brightness to be varied from virtually full-off to full-on.

Fig. 19 is an inexpensive but very impressive alarm-cell generator circuit that produces a police-like 'dee-dah' sound. The alarm can be turned on by closing PB1 or by feeding a 'high' voltage to the R1-R2 junction. The circuit is used with an 8Ω speaker, and generates roughly 6 watts of output power.

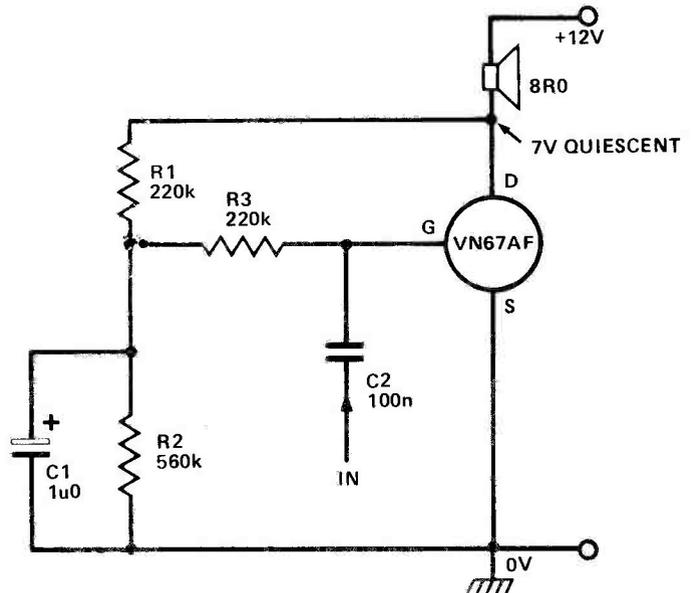


Fig 20. Super simple class-A amplifier.

The Fig. 20 class-A power amplifier gives an incredibly impressive performance, but is very inefficient. The VN67AF must be mounted on a decent heat sink. Since the amplifier is used in the class-A mode, it produces a valve sound output. Because of the excellent linearity of the VN67AF, the apparent distortion of the amplifier is remarkably low. When used with 8Ω resistive load, the amplifier has a bandwidth that extends up to 10 MHz.

The Appraisal

VMOS is undoubtedly a remarkable technology with many great advantages over conventional bipolar technology. Latest reports indicate that at least five major semiconductor companies other than Siliconix are now actively researching into or actually manufacturing VMOS power FETs, so that technology is clearly not just a 'flash in the pan'. Each of these companies is apparently developing its own particular version of the technology and preliminary reports indicate that the Siliconix technology is still way ahead of the competition in most areas (switching speeds, device linearity, high voltage rating, etc.).

Siliconix are expected to announce a 400 volt 8 amp device, which can switch 8 amps in less than 100 nanoseconds, within the next few months. They already have a 65 volt 8 amp 100 watt device on the stocks that can give a 10 dB gain at 175 MHz.

FEATURE: VFET Applications

The simple circuit of Fig. 21 makes an excellent radio control or CW transmitter output stage. The L1-C2 and L2-C3 values must be chosen to suit the required operating frequency.

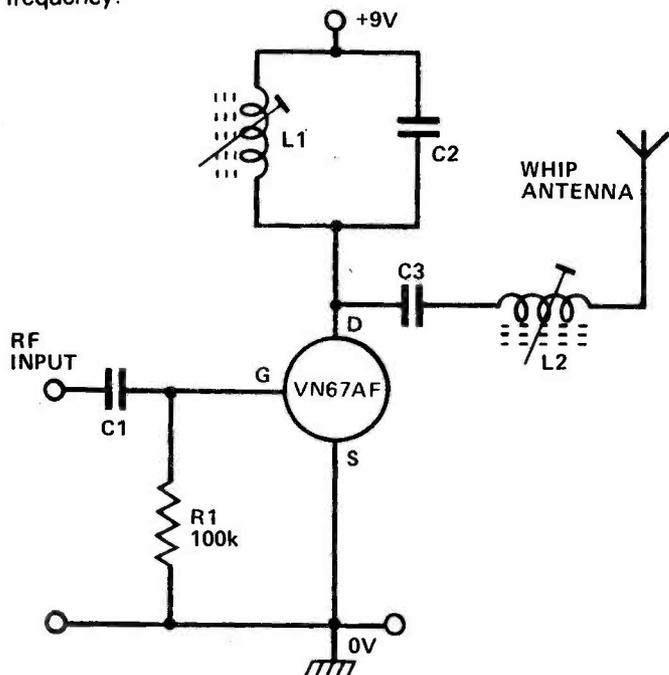


Fig 21. 60mW R/C or CW transmitter L1-C2 is tank circuit, C3-L2 is the antenna circuit.

Finally, Fig. 22 shows the basic circuit of a 20-watt class-D audio power amplifier using a pair of VN67AF's. We hope to publish a practical version of this circuit in ETI in the near future, so keep your eyes open.

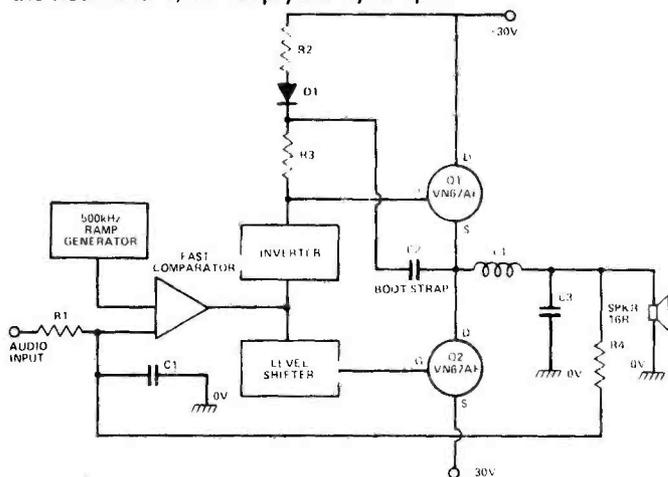


Fig 22. Basic circuit of a 20W class-D switched-mode audio power amplifier. An ideal application for VMOS.

The only criticism that we've been able to make against the Siliconix VMOS power FET technology concerns the present total lack of p-channel devices. Our spies tell us, however, that Siliconix are already working on that problem, and will have it beaten within a year. If that is so, we reckon that the 1976 prediction that "VMOS may eliminate bipolars within five years" could still come true.

In the meantime, we at ETI are already 'sold' on VMOS, and plan to use a good deal of it in the coming year. We reckon that once you've started using it, you'll like it as much as we do.


ETI

Random Electronic


EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete
or
Kit

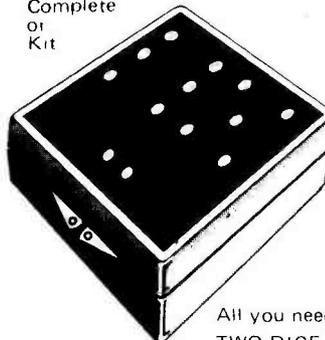

PCB
Layout

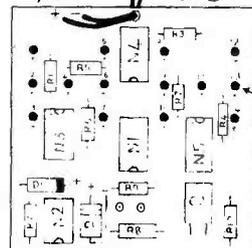

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice £3.95
- b *Ready built Dice £4.75 (INCL. P+P)

Order now from **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk (0473 210151)

Amount enclosed £

Name

Address







please state amount required in appropriate box a b

D'YA WANNA BE IN PICTURES?



Afraid of the dark? If so this is no job for you. Modmags' photographer will spend half his time in our darkroom, printing pictures and working our graphics camera.

When let loose on the real world he will be working under the direction of our editorial and art departments: taking photos for Electronics Today, Hobby Electronics and Computing Today. So if you think you can make pictures as good as (or probably better than) those in this magazine if you're not afraid of the darkroom and £3400 salary sounds right, write now to Diego Rincon, Art Director, Modmags Ltd., 145 Charing Cross Road, London, WC2H 0EE.

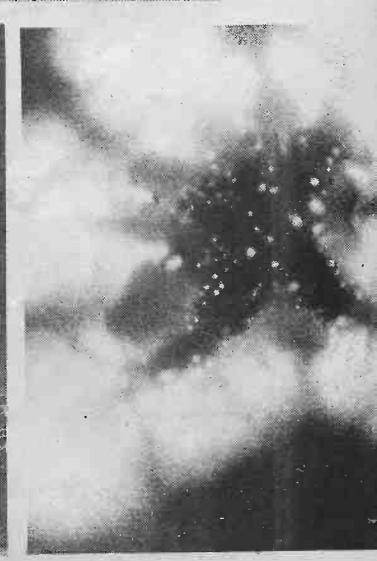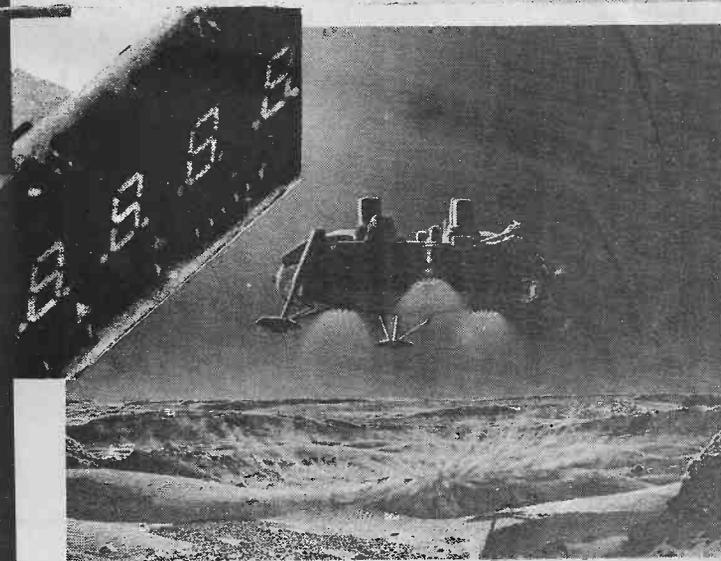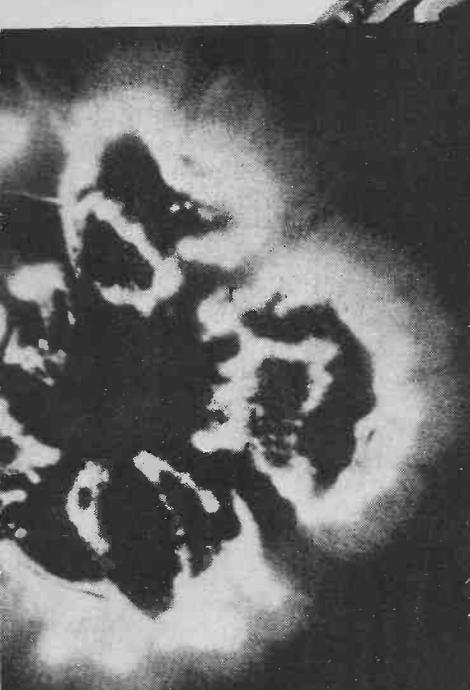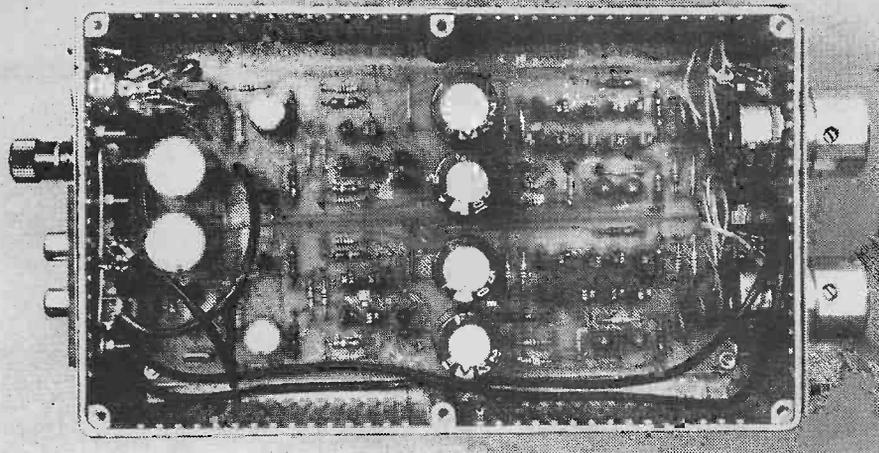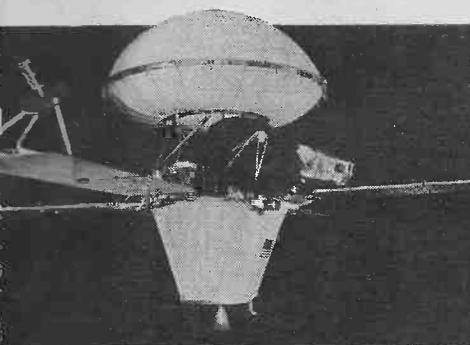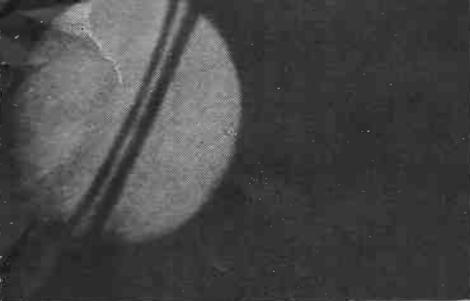

electronics today *international*


January issue on sale December 7th

Containing constructional details of five projects including a superb DIGITAL FREQUENCY METER and a very hi-fi MOVING COIL PREAMP. Amongst the usual array of brilliant features you will find KIRLIAN PHOTOGRAPHY full explained and DEEP SPACE PROBES beautifully detailed. Miss a single page and you will weep long into the cold winter nights.



DIE

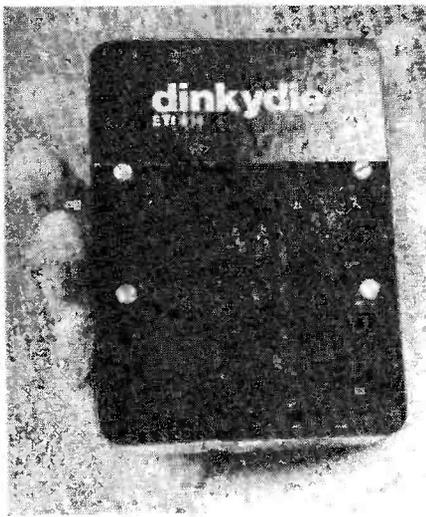Liven up your Ludo with the ETI Dinkydie. Throw away that Block of wood with dots on and bring your board games into the twentieth century.



Fed up with shaking rattling and rolling that boring set of wooden dice? Need something to brighten up that game of which the kids have grown tired?

We've spent some time designing this little project — an example of just how difficult it can sometimes be to get something 'just right': As few components as possible, all the desirable features, no obscure parts and nice low price for the constructor.

Operation couldn't be simpler: To 'throw' the dice, touch two fingers across one set of screw heads seen either side of the front panel in the picture here. Your 'throw' then appears in a dice pattern on the LEDs behind the perspex.

To throw again, touch the pair of screw heads once more.

If you leave the dice 'un-thrown' for a few seconds, the display fades and the circuit switches itself off, drawing only a miniscule current in its quiescent

state.

Mount all the components on the board, placing the LEDs last. These should be spaced off the board by about 3 mm so to ensure that they are the highest components. If the bolts are level no spacers are needed as they can be tightened just enough to hold the LEDs hard against the perspex. If you wish, a piece of block cardboard may be cut to cover the other components to obscure the board.

Once the board is assembled the battery clip and battery may be connected and the device tested. Once bolted in the nuts on the underside of the board should be quickly soldered to the pads to ensure good contact. To complete the assembly the bottom of the case can be screwed in, and the battery jammed in place with a small piece of foam rubber or styrofoam. (Use the bit the CMOS IC's came in perhaps). Finally, if you fear for the coffee table top, four adhesive rubber feet on the bottom would be a good idea?

ETI

BUYLINES

All the components used in the Dinkydie should be readily available from your favourite mail order supplier.



An LED sandwich — make sure the LED's are the highest components on the PCB.

PARTS LIST

Resistors all 1/4W, 5%

R1	2M7
R2,7	10k
R3	100k
4	56k
R5	4k7
R6	70k
R9-R11	270R
R12	330R

Capacitors

C1,C2	33u 10V tantalum
C3	10n polyester

Semiconductors

D1	1N914
LED1-LED7	Red LEDs, TIL220R
Q1,Q2	BC558
Q3-Q6	BC548
IC1	4011B
IC2	4029B

Miscellaneous

Case 9V battery clip, glue, four 6BA nuts and 20 mm bolts. PCB.

DIODES/ZENERS			
QTY.	1N914	100v	10mA .05
	1N4005	600v	1A .08
	1N4007	1000v	1A .15
	1N4148	75v	10mA .05
	1N4733	5.1v	1 W Zener .25
	1N4749	24v	1W .25
	1N753A	6.2v	500 mW Zener .25
	1N758A	10v	" .25
	1N759A	12v	" .25
	1N5243	13v	" .25
	1N5244B	14v	" .25
	1N5245B	15v	" .25
	1N5349	12v	3W .25

SOCKETS/BRIDGES			
QTY.	8-pin	pcb	.16 ww .35
	14-pin	pcb	.20 ww .40
	16-pin	pcb	.25 ww .45
	18-pin	pcb	.30 ww .95
	20-pin	pcb	.35 ww 1.05
	22-pin	pcb	.40 ww 1.15
	24-pin	pcb	.45 ww 1.25
	28-pin	pcb	.50 ww 1.35
	40-pin	pcb	.55 ww 1.45
	Molex pins	.01 To-3 Sockets	.35
	2 Amp Bridge	100-prv	.95
	25 Amp Bridge	200-prv	1.50

TRANSISTORS, LEADS, etc.			
QTY.	2N2222M	(2N2222 Plastic .10)	.15
	2N2222A		.19
	2N2907A	PNP	.19
	2N3906	PNP (Plastic)	.19
	2N3904	NPN (Plastic)	.19
	2N3054	NPN	.55
	2N3055	NPN 15A 60v	.60
	T1P125	PNP Darlington	1.95
	LED Green, Red, Clear, Yellow		.19
	D.L.747	7 seg 5/8" High com-anode	1.95
	MAN72	7 seg com-anode (Red)	1.25
	MAN3610	7 seg com-anode (Orange)	1.25
	MAN82A	7 seg com-anode (Yellow)	1.25
	MAN74	7 seg com-cathode (Red)	1.50
	FND359	7 seg com-cathode (Red)	1.25

9000 SERIES			
QTY.	9301	.85	9322 .65
	9309	.50	9601 .30
			9602 .45

C MOS								
QTY.	4000	.15	QTY.	4017	.75	QTY.	4034	2.45
	4001	.20	4018	.75	4035	.75	4071	.25
	4002	.25	4019	.35	4037	1.80	4081	.30
	4004	3.95	4020	.85	4040	.75	4082	.30
	4006	.95	4021	.75	4041	.69	4507	.95
	4007	.25	4022	.75	4042	.65	4511	.95
	4008	.75	4023	.25	4043	.50	4512	1.50
	4009	.35	4024	.75	4044	.65	4515	2.95
	4010	.35	4025	.25	4046	1.25	4519	.85
	4011	.30	4026	1.95	4047	2.50	4522	1.10
	4012	.25	4027	.35	4048	1.25	4526	.95
	4013	.40	4028	.75	4049	.65	4528	1.10
	4014	.75	4029	1.15	4050	.45	4529	.95
	4015	.75	4030	.30	4052	.75	MC14409	14.50
	4016	.35	4033	1.50	4053	.95	MC14419	4.85
					4066	.75	74C151	2.50

MICRO's, RAMS, CPU's, E-PROMS		
QTY.	8T13	2.50
	8T23	2.50
	8T24	3.00
	8T97	1.75
	74S188	3.00
	1488	1.25
	1489	1.25
	1702A	4.50
	AM 9050	4.00
	ICM 7207	6.95
	ICM 7208	13.95
	MPS 6520	10.00
	MM 5314	4.00
	MM 5316	4.50
	MM 5387	3.50
	MM 5369	2.95
	TR 1602B	3.95
	UPD 414	4.95
	Z 80 A	22.50
	Z 80	17.50
	Z 80 P10	10.50
	2102	1.45
	2102L	1.75
	2107B-4	4.95
	2114	9.50
	2513	6.25
	2708	11.50
	2716 D.S.	34.00
	2716 (5v)	69.00
	2758 (5v)	26.95
	3242	10.50
	4116	11.50
	6800	13.95
	6850	7.95
	8080	7.50
	8085	22.50
	8212	2.75
	8214	4.95
	8216	3.50
	8224	4.25
	8228	6.00
	8251	7.50
	8253	18.50
	8255	8.50
	TMS 4044	9.95

- T T L -						
QTY.	7400	.20	QTY.	7492	.45	
	7401	.20	7493	.35	74H20	.25
	7402	.20	7494	.75	74H21	.25
	7403	.20	7495	.60	74H22	.40
	7404	.20	7496	.80	74H30	.30
	7405	.35	7497	1.15	74H40	.35
	7406	.25	74100	1.15	74H50	.30
	7407	.55	74107	.35	74H51	.30
	7408	.20	74121	.35	74H52	.20
	7409	.25	74122	.55	74H53	.25
	7410	.20	74123	.55	74H55	.25
	7411	.25	74125	.45	74H72	.35
	7412	.25	74126	.45	74H74	.35
	7413	.45	74132	.75	74H101	.95
	7414	.75	74141	.90	74H103	.55
	7416	.25	74150	.85	74H106	1.15
	7417	.40	74151	.95	74L00	.30
	7420	.25	74153	.95	74L02	.30
	7426	.25	74154	1.15	74L03	.35
	7427	.25	74156	.70	74L04	.40
	7430	.20	74157	.65	74L10	.30
	7432	.30	74161/9316	.75	74L20	.45
	7437	.20	74163	.85	74L30	.55
	7438	.30	74164	.75	74L47	1.95
	7440	.20	74165	1.10	74L51	.65
	7441	1.15	74166	1.75	74L55	.85
	7442	.55	74175	.90	74L72	.65
	7443	.45	74176	.95	74L73	.70
	7444	.45	74177	1.10	74L74	.75
	7445	.75	74180	.95	74L75	1.05
	7446	.70	74181	2.25	74L85	2.00
	7447	.70	74182	.75	74L93	.75
	7448	.50	74187	1.25	74L123	1.95
	7450	.25	74190	.75	74L00	.40
	7451	.25	74191	1.25	74L01	.40
	7453	.20	74192	.75	74L02	.45
	7454	.25	74193	.85	74L03	.45
	7460	.40	74194	.95	74L04	.45
	7470	.45	74195	.95	74L05	.45
	7472	.40	74196	.95	74L06	.45
	7473	.25	74197	.95	74L07	.45
	7474	.30	74198	1.45	74L08	.45
	7475	.35	74199	1.50	74L09	.45
	7476	.40	74201	1.50	74L10	.45
	7480	.75	74202	1.50	74L11	.45
	7481	.85	74203	1.50	74L12	.45
	7482	.95	74204	1.50	74L13	.45
	7483	.95	74205	1.50	74L14	.45
	7485	.75	74206	1.50	74L15	.45
	7486	.55	74207	1.50	74L16	.45
	7489	1.05	74208	1.50	74L17	.45
	7490	.55	74209	1.50	74L18	.45
	7491	.70	74210	1.50	74L19	.45
			74211	1.50	74L20	.45
			74212	1.50	74L21	.45
			74213	1.50	74L22	.45
			74214	1.50	74L23	.45
			74215	1.50	74L24	.45
			74216	1.50	74L25	.45
			74217	1.50	74L26	.45
			74218	1.50	74L27	.45
			74219	1.50	74L28	.45
			74220	1.50	74L29	.45
			74221	1.50	74L30	.45
			74222	1.50	74L31	.45
			74223	1.50	74L32	.45
			74224	1.50	74L33	.45
			74225	1.50	74L34	.45
			74226	1.50	74L35	.45
			74227	1.50	74L36	.45
			74228	1.50	74L37	.45
			74229	1.50	74L38	.45
			74230	1.50	74L39	.45
			74231	1.50	74L40	.45
			74232	1.50	74L41	.45
			74233	1.50	74L42	.45
			74234	1.50	74L43	.45
			74235	1.50	74L44	.45
			74236	1.50	74L45	.45
			74237	1.50	74L46	.45
			74238	1.50	74L47	.45
			74239	1.50	74L48	.45
			74240	1.50	74L49	.45
			74241	1.50	74L50	.45
			74242	1.50	74L51	.45
			74243	1.50	74L52	.45
			74244	1.50	74L53	.45
			74245	1.50	74L54	.45
			74246	1.50	74L55	.45
			74247	1.50	74L56	.45
			74248	1.50	74L57	.45
			74249	1.50	74L58	.45
			74250	1.50	74L59	.45
			74251	1.50	74L60	.45
			74252	1.50	74L61	.45
			74253	1.50	74L62	.45
			74254	1.50	74L63	.45
			74255	1.50	74L64	.45
			74256	1.50	74L65	.45
			74257	1.50	74L66	.45
			74258	1.50	74L67	.45
			74259	1.50	74L68	.45
			74260	1.50	74L69	.45
			74261	1.50	74L70	.45
			74262	1.50	74L71	.45
			74263	1.50	74L72	.45
			74264	1.50	74L73	.45
			74265	1.50	74L74	.45
			74266	1.50	74L75	.45

RAIN ALARM

Don't get wet feet, don your wellies and come and see the Rain in Spain fall
Mainly on the ETI Rain Alarm. - By George, we've got it!

Have you ever been tied up with other jobs, such as polishing the furniture, doing the washing up, etc while your washing is out drying on the line? Then, just as you are finishing your present chore you look out of the window and see that the heavens have opened on your nearly dry washing. Well, this happens virtually every Monday (being washing day) to the ETI Project Team and we were just about getting fed up with it

. . . .so we had a conference!

It became apparent, after we had looked in the piggybank and found we didn't have enough for a second-hand tumble dryer, that we should do something constructive (for a change). We decided that even we couldn't design a machine to stop it raining on Mondays (though officially we won't admit it) so the alternative was the ETI Rain Alarm, which, at the vaguest hint of rain, will ring out loud and clear so that the pots and pans can be dropped while we run outside and fetch in the washing from the line. ▶

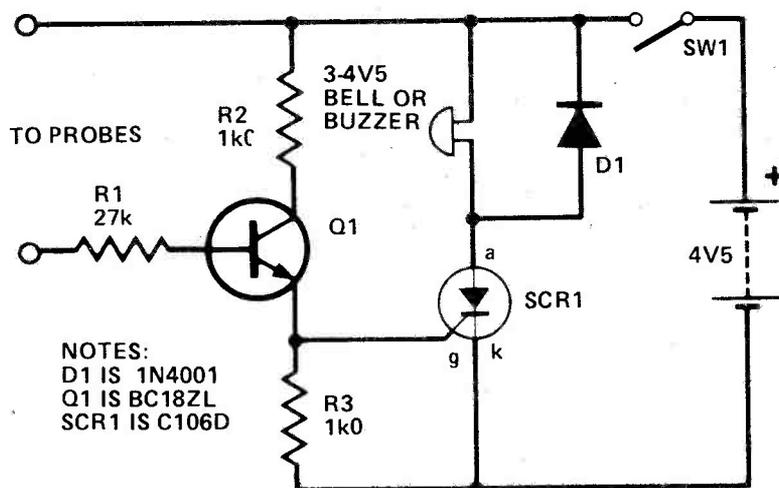
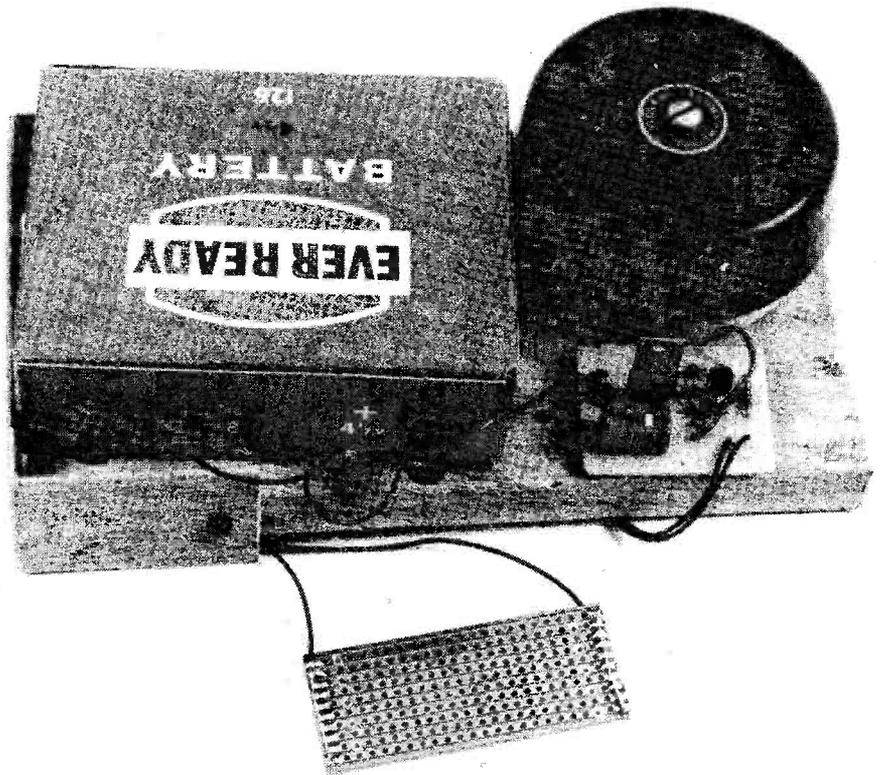


Fig. 1. Circuit diagram.

HOW IT WORKS

The heart of the rain alarm lies around the thyristor SCR 1 which switches the bell or buzzer on. Normally, in D.C. mode a thyristor is switched on by a small gate current. It will not switch off however, until the voltage applied across the whole device reduces to near zero, at which point it will remain off until the voltage at the gate increases enough to switch it on again.

When used with a make and break device such as a bell or buzzer the applied voltage momentarily decreases to zero at whatever frequency the bell or buzzer is operating at. This will in turn, switch off the SCR. This gives us a non-latching D.C. switch, operated by applying a small D.C. voltage to its gate.

Q1 provides switching action in that as the resistance across the probes decreases from infinity to a comparatively low value (i.e. as rain falls on them) then the voltage across R3 increases from near zero to above the threshold voltage necessary to switch SCR1 on.

PARTS LIST

BUYLINES

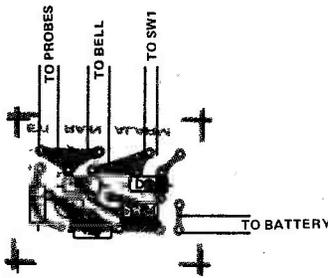


Fig. 2. Component overlay.

Of course detecting rain to keep your washing dry needn't be its only function. Anywhere a device to detect the presence of water is required, then the Rain Alarm will do it. It takes only minimal current when in standby mode so can quite happily be left on for long periods without significantly battery wastage.

Construction

As the whole rain alarm only contains

RESISTORS All ¼W, 5%

R1 27k
R2,3 1k0

SEMICONDUCTORS

Q1 BC182L
D1 1N4001
SCR1 C106D

MISCELLANEOUS

SW1 SPST switch
3-4½V Bell or buzzer 4½ volt battery
Small piece of stripboard.

seven components, including the on/off switch, it fits very neatly onto a small PCB only about 1 inch by 1½ inches (or 25 mm by 40 mm if you have already been metricated by the vet). In fact, the 4½ volt bell battery is by far the biggest item in the project.

The construction of the circuit on our PC layout will present no difficulties — just take care that the semiconductors are inserted cor-

All parts should be easily obtainable from your local stockists. However, any of the mail order firms advertising in ETI should be able to help, if you are stuck.

rectly. Use a printed circuit mounting switch for SW1 if you can obtain one — it makes a neater job, but if not, any SPST switch will do.

The probes in our prototype were constructed from a small piece of commercially available stripboard, the two leads soldered to alternate copperstrips, providing an interleaving of the copper. Any small drop of water landing on the copper side of the stripboard will automatically bridge at least two of the strips, therefore operating the alarm.

And, now that you have finished the ETI Rain Alarm, you can go — in the words of the immortal and legendary Gene Kelly (Ray's hero) — Ringing in the Rain.

ETI


 <p>MEN'S FIVE FUNCTION QUARTZ LCD Hours, mins., secs., month, date, auto. calendar. Quality metal bracelet. £6.95</p>	 <p>LADY'S 7-FUNCTION ALARM Ladies' 7-function Alarm. Min., sec., hr. Day, date, month, backlight. £14.95</p>	 <p>LADY'S 5-FUNCTION WATCH Gold/silver colour finish. £12.95</p>	 <p>LADY'S 5-FUNCTION WATCH Hours, mins., secs., day, month, date, backlight. £9.95</p>
 <p>MEN'S DUAL TIME ALARM CHRONO £35.00</p> <p>OUTSTANDING FEATURES: DUAL TIME: Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing. CALENDAR FUNCTIONS include the date and day in each time zone. CHRONOGRAPH/STOPWATCH displays up to 12 hours, 59 minutes, 59.9 seconds.</p> <p>On command stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation. ALARM can be set to any time within a 24-hr. period. At the design time, a pleasant effective buzzer sound... remind or awaken you!</p>	 <p>MEN'S 7-FUNCTION ALARM WATCH Alarm. Hours, mins., secs. Month, date, day, 6 digits, 3 flags, plus continuous display of day and date or seconds. Back-light. £11.95</p>	 <p>MEN'S ALARM CHRONO Hr., min., sec., day, date, 1/10 chronograph, lap time, alarm, 6 digits plus day, 12/24 hour option. Month date/date month option. £18.95</p>	 <p>MEN'S 11-FUNCTION ALARM 6 digit, 11 functions. Hours, mins. secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Backlight, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. £10.95</p>

LEYTRONICS LTD
12 Little Newport Street
London WC2 7JJ

Payment can be made by sending cheque or postal order. Write your name and address and order details clearly. All products carry one year guarantee and full money back 10-day reassurance. Battery fitting service is available at our shops. All goods are sent by first-class post.
Shop open 7 days per week, 12 noon to 8 p.m.

MAGNUM

at

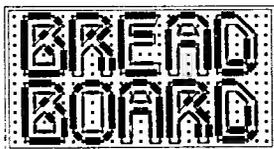

Meet us on **Stand C3** where our NEW CATALOGUE will be on distribution, itemising:

MAGNUM AUDIO MODULES
MAGNUM ENERGY CONSERVATION MODULES
FUTABA VF DISPLAYS combined with
OKI L.S.I.
DELPK KEYBOARDS
DELPK POWER SUPPLIES

If you can't make the exhibition but would like a copy of our **New Catalogue**, send large S.A.E. to:

MAGNUM AUDIO Ltd.

DEPT. ET112
 13 HAZELBURY CRESCENT
 LUTON LU1 1DF
 TEL. 0582 28887

S. & R. BREWSTER LIMITED

WHY PAY MORE?

for Miniature Soldering Irons & Accessories

	PRICE EACH	P. & P Extra EACH
S.R.B. 18 watt Soldering Iron available in 12, 110 & 240 Volts, fitted with No. 20 bit	£4.43	+ 24p
SPARE BITS No. 19 size 1.5mm or No. 20 size 3mm or No. 21 size 4.5mm or No. 22 size 6mm	52p	—
No. 78. I.C. Desoldering Bit	£1.04	+10p
No. 1920L Long Life Bit	£1.12	10p
SAFETY STAND	£4.23	+ 70p
SOLDER Savbit 20'	61p	+ 9p
Savbit 10'	32p	+ 5p
Lowmelt 10'	76p	+10p

INDUSTRIAL/RETAIL ENQUIRIES WELCOME FOR THE ABOVE

We also Offer & Recommend for Mail Order & Personal Callers Only

	PRICES EACH including V.A.T. and P. & P.
Oxy 50 Temperature Controlled Soldering Iron	£11.75
Spare tips for above	£1.39
Isotip quick charge rechargeable Soldering Iron	£24.80
Spare tips for above	£3.42
Cable 7/0.2 11 Colours 100 meter reel	£2.40
0.1 Veroboard 3/4" X 11 1/2"	£2.00
0.1 Veroboard 4/4" X 18"	£4.50
Copper Clad board single sided	75p
Watchmakers Side Cutters	£5.85
Watchmakers Pliers	£4.75
Transformer 100VA 2 X 12V 4.1A	£11.20

OTHER ITEMS ALSO AVAILABLE ASK FOR LIST S.A.E.

MAIL ORDER DEPT.
 86-88 Union Street, Plymouth
 PL1 3HG Tel:(0752) 65011




Please Quote your Number when ordering



TUNE IN!

Build the World Famous CHROMA-CHIME

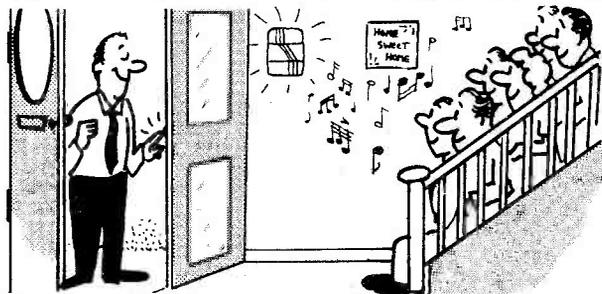

Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed



* Save pounds on normal retail price by building yourself

TMS 1000N - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.




New low price only **£4.95 inc. p&p**

R/C MODELLERS - LISTEN FOR THE C.B. MENACE GET A 27MHZ MONITOR

- * Audibly confirm your channel's clear.
- * Tunes over whole 27mhz model band.(CB)
- * Receives normal broadcast AM/FM bands as well.
- * Sensitive with telescopic aerial.
- * Totally portable.
- * Runs on standard batteries.

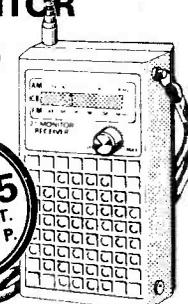This neat three band Superhet receiver not only provides an invaluable service, checking your channel and TX, but gives normal broadcast reception when you need it as well. Costing less than a decent Servo, you'll find it cheap and reassuring insurance!



ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:
 TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____
 ADDRESS _____

I enclose cheque/PO value £ _____
 or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS



MUSICAL ALARM

Chrono-plays melody on alarm 6 digit 11 functions countdown alarm, Dual time zone, 1/100th sec chrono, 2 piece s/s bracelet

£25.95

inc. VAT p&P

VT20 8mm thick

GREEN DISPLAY MAINS ALARM CLOCK RADIO

3 wavebands, LW, MW, FM Snooze alarm, dimmer control



220x150x60mm

ONLY £19.95

(inc. VAT, P&P)

ALARM CHRONO

with 9 World Time Zones



6 digits, 5 flags. 6 basic functions. 8 further time zones. Count-down alarm. Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

ONLY £29.95

(inc. VAT, P&P)

VT17

SEIKO MEMORY BANK VT21

Calendar watch M354 Hours, mins., secs. Month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display month, year and all dates for any selected month over 80 year period. Memory ban function. Any desired dates up to 11 can be stored in advance, 2 year battery life. Water resistant. Same as ETI offer

ONLY £74.95 inc. VAT P&P

Low cost 5 function 4 digit — **£7.95** inc.

LADIES COCKTAIL WATCHES £12.95 inc.



LCD SNOOZE ALARM

24-hr. alarm Hours, Mins., Secs., date, month, back-light, auto. calendar. Adjustable stainless steel bracelet, 12-month guarantee.

ONLY £12.95

(inc. VAT, P&P)

VT10 Same day despatch

ATARI VCS System

— Most popular top range micro-video game

Current cartridges — Air Sea Battle (27), Space War (17), Outlaw (16), Video Olympics (50), Breakout (12), Basketball (2), Surround (14), Blackjack (7), Basic Maths (8), Codebreaker (20) Hunt & Score (8), Miniature Golf (2), Skydiver (5), Street Racer (27), Chess (8) Levels Backgammon (8), Brain Games, Bowling.

VCS Unit — £159.95 inc. Cartridges mostly — £14.95 inc. CHESS (8 levels) — £45.00 inc. BACKGAMMON — £34.50 inc. SUPERMAN — £23.25 inc.

details on request. Same day despatch.



SOLAR LCD ALARM CHRONO

- ★ WATER RESISTANT (no vents)
- ★ MINERAL GLASS
- ★ ALL STAINLESS STEEL
- ★ ONLY 7mm THICK



24-hr. alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility. Night light.

ONLY £29.95 (inc. VAT, P&P)

Same day despatch

VT16

BELTIME CHRONOGRAPH

9 Functions Hours, mins, secs, day, date, month, interchange feature, automatic calendar, backlight, net time/lap time. Stainless steel bracelet, 8mm thick




£12.95 (inc. VAT P&P)

VT07 Same day despatch

TELENG TELEVISION COMPUTER SYSTEM — low cost micro-video game — British made

Details on request

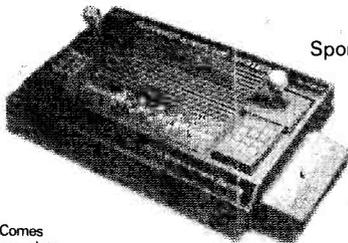

Comes complete with Sportsworld

Sportsworld, Combat, Horse Racing, Maze Maths Two, Far in Raw, Mastermind, Air-Sea Battle, Boxing, Black Jack, Sporting Shotgun, Motor Racing, Maths One Circus

Console — **£89.95** inc. Cartridges — **£12.95** inc.

LCD ALARM CHRONOGRAPH

All usual features. Perpetual calendar, day, date. 24-hr. alarm with on/off indication. 1/10 second chronograph measuring set, lap and first and second place times. Dual time zone facility. Night light. 12-month guarantee.

ONLY £17.95 (inc. VAT, P&P)



Same day despatch Same as ETI offer

VT06

BELTIME MICROPROCESSOR

VT18

- ★ 2 alarms
- ★ 2 chronos
- ★ Hourly chime
- ★ Mineral glass

Hours (program 12 or 24), minutes, seconds, day (multi-language program). Date, 1/100th sec. chrono 24 hrs., countdown chrono with alarm, backlight.



ONLY £37.95


(inc. VAT P&P) Same as HE offer

PHILIPS G7000 — HOME VIDEO COMPUTER GAME

— a new dimension to video games 11 exciting VIDEOPACS

PAC 1 — Motor Race, Spin-out, Cryptogram, PAC 2 — Paris, Space Rendezvous, Logic, PAC 3 — American Football, PAC 4 — Air-Sea and Tank Battle, PAC 5 — Blackjack, PAC 6 — Ten Pin Bowling, Basketball, PAC 7 — Maths, Echo, PAC 8 — Baseball, PAC 9 — Computer (Assembler and Machine code), PAC 10 — Golf, PAC 11 — Space Conflict.

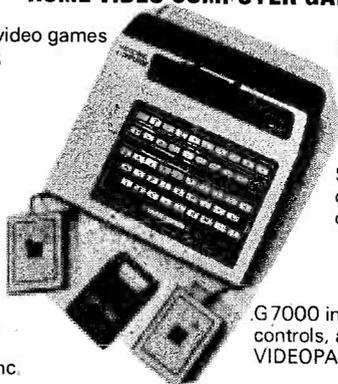G 7000 — **£149.95** inc. VIDEOPACS most each — **£12.95** inc.



full details on request

Same day despatch

G7000 includes controls, adaptor, VIDEOPAC 1

SOLAR LCD ALARM CHRONOGRAPH

24-hr. alarm with on/off indication 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility. Night light.

ONLY £19.95 (inc. VAT, P&P)



Same day despatch VT12

12-month guarantee. 15% VAT included. Cheques or P.O.s or telephone Card No. to Allow 7 days delivery unless specified

VIDEOTIME PRODUCTS, 56 QUEENS ROAD

BASINGSTOKE, HANTS RG21 1REC. Tel: (0256) 56417 or 26620 TLX: 858747

FACTORY AGENTS WANTED MONEY BACK GUARANTEE OFFERS SUBJECT TO AVAILABILITY. TRADE ENQUIRIES WELCOME





AUDIOPHILE

Having spent a month coiled up with a lump of Coral (well each to his own) Ron Harris presents a review of the new MC81 pick up.

It has been a month of musical evenings. The television has remained off, the soldering iron cold, the wargames unplayed and the books unopened. Meanwhile the power amp glows red in the night and my neighbours have taken to wearing ear defenders and shaking their fists at my approach.

Ah, the fools, they know not the delights they scorn. . . .

You see. I have been playing a lot of records this month, all due to this MC81 device I mentioned when last you read Audiophile. They should put a warning on the side of the box — "This cartridge can seriously damage your social life."

At first glance it is a most unimpressive blob of black plastic, but that in itself brought to mind something someone once told me about not covering judges with books — or something like that anyway.

Book Covers

Being of the moving coil strain, the Coral MC81 needs a head amp, or pre-pre-amp as some people with stutters persist in calling them, to increase the voltage level to around 3mV in order that a normal RIAA input can process the signal.

The unit designed to work with the MC81 in this manner is the H300, which possesses a few unusual points itself. There *are* head amps on the market which will work with the majority of cartridges, but none are totally satisfactory with all. The best of these is possibly the Sony HA55, (which is mains powered). The H300 has a variable input impedance facility which suggests that it too is aimed this way and it will be interesting to see if it gains acceptance on the end of cantilevers other than the MC81. I confess I did not audition it any other way myself, but I will get around to that. . . .

Back to the cartridge. It weighs a puny 5g, but is surprisingly large for this weight as you can see from the photos. Set up in the SME III the Coral tracked most material happily at 1.8g, and took everything (just!) at 2.0g. The damping option on the SME should be exercised, although the fluid may need thinning for best results.

One good point about the cartridge body itself is that the top is sensibly large and flat — allowing for a large contact area with the headshell and thus good mechanical coupling between the two. At least it *would* do if the SME headshell was long enough!



Coiled Up

Initially I had the MC81 operating through a HA55, while the H300 was getting over its birth pains and into this cruel world. In this configuration the cartridge worked well, but I was less than happy with the lowest bass registers. The mid-range, however, came as a revelation. It was crystal clear and sharp and 'opened out' relative to the other cartridges I was comparing with it (Coral's own 777EX and the Entré 1). Treble quality was all I'd hoped for, being both accurate and extended without either emphasising surface noise or wielding that steel edge with which some moving coils cut through the music. I was impressed!

I was further beguiled once I had the MC81 and H300 operating together, a combination which went a long way to taking the ground from under my objections to the bass. It was never that the unit lacked bass at all, but that I had a feeling that the level was down upon what I would have expected.

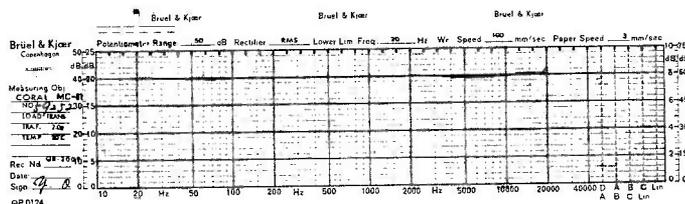


Fig. 1. Frequency response of the MC81. If you can't see it that's because it's so straight it's hidden behind the graph paper. What happened to all those nice dips and peaks reviewers could have such fun commenting on?

Bass *quality* was immaculate. Each instrument, bass guitar, drum, double bass or whatever was clearly and precisely identified and distinguishable. If you think that's easy, try it with your own cartridge — now — can you absolutely distinguish the different notes from a bass guitar for instance? Is the bass drum in full possession of its transients?

As regards this aspect the Coral has the *best* bass I've heard and I'm not prepared to trade that quality back in for a bit more quantity of a less than equal pedigree.

Timely Decision

Running through an evening of the best recorded LPs I had soon convinced me that any initial unease I had experienced was groundless. Direct comparison between the V15 IV, the Entré an FR1 and the MC 91 led to others being employed in ever shorter bursts and, before the day was through, left alone.

In each comparison there were differences. The FR1 had a 'sweeter' mid-range but *not* the incredible detail. The Shure had for more bass signal present but *not* the attack and the Entré just didn't measure up at all — with either or any head amp.

In fact it was probably the V15 IV's slight bass emphasis that had led me up the garden path in the first place.

Talking Of Heads

Consider the H300 for a moment. The input of this device has variable gain and variable capacitance facility. Loading can be switched from 5000p to 20000p in steps of 5n. Gain can be switched up from 23-30dB.

Both these are controlled by DIL switch banks on the front of the PCB, but can only be accessed by removing the front panel entirely. That same panel contains the power switch and 'charge' light.

The H300 takes its electrons from a Ni-Cad source, and when switched off the batteries go on trickle charge. It takes (say Videotone) twelve hours to deplete the storage — I didn't fancy staying awake long enough to get an accurate figure — and forty eight hours to replace the power once used up. The charge light (LED) comes on when the box is switched off, a changeover relay diverts the input from a separate mains adaptor to the charger. This same relay operates as a switch-on delay system to prevent a 'thump' which is potentially dangerous to amp, ears and cones.

Unfortunately this relay doesn't seem to work on switch off and I got a loud 'whoop' if I did things in the wrong order! It could all lead to a flat cell and no music tonight, Josephine.

All in all, even weighing the advantages of reduced hum and lower source resistance (hence less RF interference etc), I think I prefer a plain mains supply with the extra costs that infers.

Still the H300 system works, and works well. The head amp sounds very fine indeed, and on audition proved indistinguishable from the Sony HA55 at a fraction of that unit's cost.

Full marks for circuit design and final performance Videotone but the grumble on supply you'll have to live with — it's an odd solution albeit one that works.

System Round-Up

Taken together the MC81/H300 system is an impressive and exciting new pickup system. The cartridge is well-nigh excellent and does not entail a second mortgage on the



Above: the H300 sat sitting between the MC81 in SME, dressing and an ACI it fed. Small is it not?

mortgage to afford it, like some Oriental Offerings I could name (It costs about £90 in the shops).

The H300 sounds very healthy indeed, but has that quirky PSU arrangement. This should give no trouble but does not make life as "thought-free" as it could. (Cost circa £60).

I would heartily recommend anyone interested in a new cartridge to head for an MC81 with open ear, and try and get a good listen.

If Felicity Kendal was interested, I'm sure I could find SOMEONE willing to extend the hospitality of his hi-fi for an evening or two (thousand!).

A Gold Ring To It?


The point on the right has a point to it. A very strange shaped point—but a point nonetheless, a Van den Hul point in fact. After many months of trial and tribulation Goldring have fitted said sharp bit to a cantilever for their new G900IGC pick-up cartridge.

To all things under heaven there is a season, eh?


Welcome to the pickup season. After the Coral cometh the IGC and lo, music was bountiful upon the ears of Man and he heard that it was good.

The new G900 is claimed to exhibit greatly reduced distortion when compared to either a conventional elliptical point or the Shibata variation upon the theme. This is claimed to be due to the straight line of contact between stylus and groove and the smaller minor radius of the Van den Hul design.

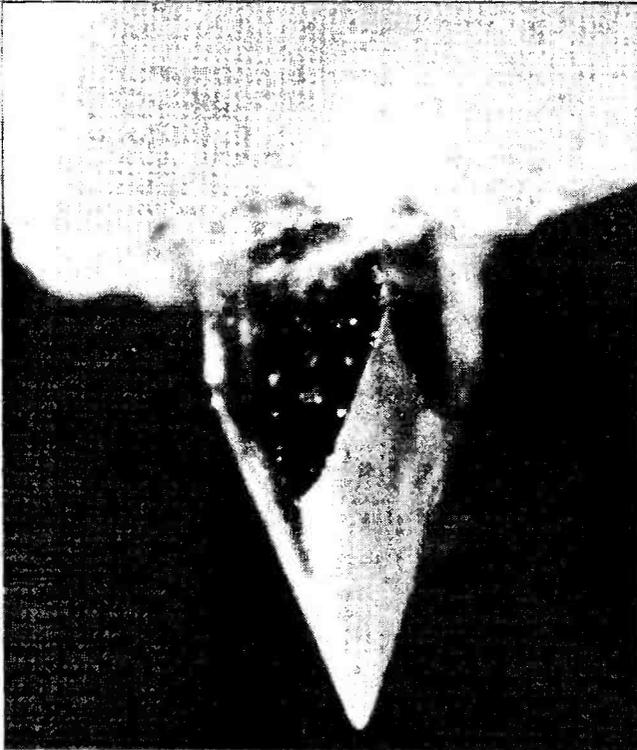The finish and presentation of the cartridge is superb, but up to now I haven't had a chance to listen to my sample at all. So once again its next month folks . . .



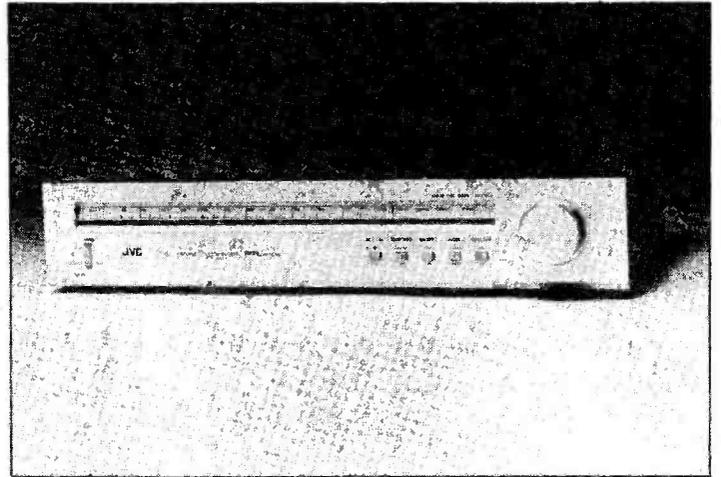Above: the point of Goldring's new G9001GC is easily seen.



Tuning In JVC

Interesting looking new tuner from JVC, the TX5, features their award winning Phase Tracking Loop detector stage. Naturally PTL is claimed to improve everything from AM objection to sliced bread — and judging by the details I've seen could be Wonderloaf are in for a hard time.


The TX5 also has two patented ideas incorporated — a 'quieting slope' control which acts as a sort of signal sensitive noise reducer, and a new tuning system. The price is around £250.

ETI

New for Nascom 1 from Microdigital

Put your Nascom to work with the new Microdigital Relay Board.

- * 16 Reed Relays, totally isolated 200 mA, 50 V.D.C. 5 W max each. Operate and release time 1 ms (including bounce).
- * Single sided, glass fibre board, with gold plated edge connectors and silk screened component layout.
- * Plugs directly into Nasbus, does not interfere with normal Nascom operation, all Interrupt and D.M.A. Daisy Chain Links carried on. Draws only 250 mA from each of the +5 and +12V Rails.
- * All components supplied, all IC's socketed, easy to build, and easy to program in Basic or Machine Code.
- * Occupies 2 consecutive ports, link selectable — several boards can be used on one Nascom System.
- * Output is via front edge connector on 0.1" centres. Uses standard edge connectors for connection to controlled devices.
- * Complete manual with sample software.

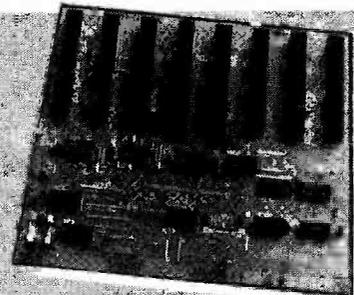

- * Light displays
- * Industrial process control.
- * Model Railway Control.
- * Pre programmed music generation.
- * Robots, Central Heating Systems.
- * Stepping Motors.
- * ?

PRICE £49.95 plus V.A.T. (Total Cost £57.44)
Access, Barclaycard, Mail Order.



MICRODIGITAL

25 Brunswick Street, Liverpool L2 0BJ
Tel: 051-236 0707 (24 hour Mail Order)
051-227 2535 (All other Depts.)

Mail orders to: MICRODIGITAL LIMITED,
FREEPOST (No Stamp Required)
Liverpool L2 2AB.



CMOS			
4020	50p	4050	25p
4022	50p	4060	80p
4023	13p	4066	30p
4024	40p	4068	13p
4025	13p	4069	13p
4026	90p	4070	13p
4027	28p	4071	13p
4028	45p	4072	13p
4029	50p	4081	13p
4030	55p	4093	36p
4031	28p	4041	55p
4032	50p	4042	55p
4033	55p	4043	55p
4034	55p	4044	55p
4035	55p	4045	55p
4036	55p	4046	55p
4037	47p	4047	90p
4038	55p	4048	25p
4039	55p	4049	25p


FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	74141	55p
7401	10p	74145	55p
7402	10p	74148	90p
7403	10p	74150	55p
7404	12p	74151	40p
7405	22p	74152	40p
7406	22p	74153	40p
7407	12p	74154	55p
7408	12p	74155	55p
7409	10p	74156	55p
7410	10p	74157	55p
7411	22p	74158	100p
7412	39p	74159	55p
7413	12p	74160	55p
7414	39p	74161	55p
7415	12p	74162	55p
7416	20p	74163	55p
7417	20p	74164	55p
7418	12p	74165	55p
7419	12p	74166	55p
7420	12p	74167	55p
7421	20p	74168	55p
7422	12p	74169	55p
7423	12p	74170	100p
7424	12p	74171	100p
7425	12p	74172	100p
7426	12p	74173	100p
7427	12p	74174	100p
7428	12p	74175	100p
7429	12p	74176	100p
7430	12p	74177	100p
7431	12p	74178	100p
7432	12p	74179	100p
7433	12p	74180	100p
7434	12p	74181	100p
7435	12p	74182	100p
7436	12p	74183	100p
7437	12p	74184	100p
7438	12p	74185	100p
7439	12p	74186	100p
7440	12p	74187	100p
7441	12p	74188	100p
7442	12p	74189	100p
7443	12p	74190	100p
7444	12p	74191	100p
7445	12p	74192	100p
7446	12p	74193	100p
7447	12p	74194	100p
7448	12p	74195	100p
7449	12p	74196	100p
7450	12p	74197	100p
7451	12p	74198	100p
7452	12p	74199	100p

OPTO			
LED's	0.125in.	0.2in.	each 100+
Red	TIL209	TIL220	9p 7.5p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	

DISPLAYS			
DL704	0.3 in	CC	130p 120p
DL707	0.3 in	CA	130p 120p
FND500	0.5 in	CC	100p 80p

SKTS

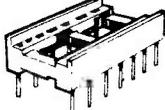

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

3 lead T018 or T05 socket. 10p each
Soldercon pins. 100:50p 1000:370p

PCBS

VEROBOARD			
Size in.	0.1in.	0.15in.	Vero
2.5 x 1	14p	14p	Cutter 80p.
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	

Single sided pins per 100 40p 40p
Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each
'Dato' pens 75p each
Five mixed sheets of Alfac 145p per pack

RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix each 100+ 1000+

0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability, low noise: rated at 1/4W. 1% Available from 51ohms to 330k in E24 series. Any mix.

0.25W	each 4p	100+ 3.5p	1000+ 3.2p
-------	---------	-----------	------------

LINEAR

THIS IS ONLY A SELECTION!

709	35p	LM339	45p	NE531	98p
741	16p	LM378	230p	NE555	23p
747	45p	LM379S	410p	NE566	60p
748	30p	LM380	75p	NE567	100p
7106	850p	LM3900	50p	RC4136	100p
7107	900p	LM3909	65p	SN76477	230p
CA3046	55p	LM3911	100p	TBA800	70p
CA3080	70p	MC1458	32p	TBA810S	100p
CA3130	90p	MM57160	590p	TDA1022	620p
				TL081	45p
				TL084	125p
				ZN414	80p
				ZN425E	390p
				ZN1034E	200p

TRANSISTORS

AC127	17p.	BCY72	14p	ZTX500	16p
AC128	16p	BD131	35p	2N697	12p
AC176	18p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BD140	35p	2N3055	50p
BC107	8p	BFY50	15p	2N3442	35p
BC108	8p	BFY51	15p	2N3702	8p
BC108C	10p	BFY52	15p	2N3703	8p
BC109	8p	MJ2955	98p	2N3705	9p
BC109C	10p	MPSA06	20p	2N3706	9p
BC147	7p	MPSA56	20p	2N3707	9p
BC148	7p	TIP29C	60p	2N3708	8p
BC177	14p	TIP30C	70p	2N3819	15p
BC178	14p	TIP31C	65p	2N3820	44p
BC179	14p	TIP32C	80p	2N3904	8p
BC182	10p	TIP2955	65p	2N3905	8p
BC182L	10p	TIP3055	55p	2N3906	8p
BC184	10p	ZTX107	14p	2N4058	12p
BC184L	10p	ZTX108	14p	2N4547	32p
BC212	10p	ZTX300	16p	2N5459	32p
BC212L	10p			2N5777	50p
BC214	10p				
BC214L	10p				
BC477	19p	1N914	3p	1N4006	6p
BC478	19p	1N4001	4p	1N5401	13p
BC548	10p	1N4002	4p	BZY88 ser.	8p
BCY70	14p	ITT Full spec. product.			
BCY71	14p	1N4148	£1.40/100 £11/1000		

DIODES

1N914	3p	1N4006	6p
1N4001	4p	1N5401	13p
1N4002	4p	BZY88 ser.	8p
ITT Full spec. product.			
1N4148	£1.40/100 £11/1000		

CAPACITORS

TANTALUM BEAD

0.1, 0.15, 0.22, C.33, 0.47, 0.68, 1 & 2.2uF @ 35V	each 8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1	3p
0.068, 0.1	4p

POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22	5p
0.33, 0.47	7p
0.68	10p
1.0uF	14p
	17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
						7p
						13p
						20p
25V	10	22	33	47		5p
						8p
						10p
						15p
						23p

CONNECTORS

JACK PLUGS AND SOCKETS

2.5mm	screened 9p	unscreened 13p	socket 7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

2pin	7p	chassis socket 7p	line socket 7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits. Red & black. Plugs 6p each. Sockets 7p each

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs 11p each. Sockets 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

STEVENSON

Electronic Components

SOLDERING IRONS

ANTEX X25 (25W) or ANTEX CX (17W) 390p each
Reel of solder (39.6M) 240p each


LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p

Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
Crystal earpiece including 3.5mm plug. 30p each

SWITCHES

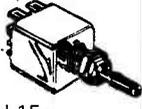Subminiature toggle. SPDT 70p. DPDT 80p.
Standard toggle. SPST 34p. DPDT 48p.



Slide switches (DPDT) miniature or standard 15p.
Push to make switch. 15p. Push to break switch. 20p.
Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow & black. 14p.



MISCELLANEOUS


Connection cable available in single or stranded packs of eight colours.

Single	Stranded
8 metre pack 18p	18p
40 metre pack 85p	80p

BATTERY CLIPS

Battery clips for PP3 with lead. 6p each.
Battery clips for PP9 with lead. 10p each.
Miniature crocodile clips in red or black. 8p each.
Red or black probe clips. 20p each.

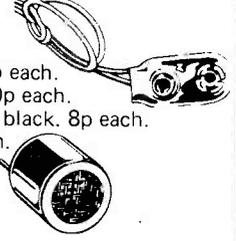Murata Ultrasonic Transducers. 180p each. 350p pair.




PANEL METERS

High quality 2" wide view meters. Zero adjustment. Back illumination wiring. Available in 50 uA, 100 uA, 500 uA, 1 mA, 100 mA, 500 mA, 1 A. £4.75 ea. VU meter similar style. £1.40 ea.



SLIDE POTENTIOMETERS

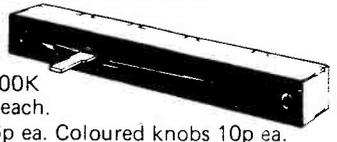Good quality 60mm travel slider with 80mm fixing centres. Available from 5k - 500k in log and linear. 55p each. Suitable black knobs 6p ea. Coloured knobs 10p ea.



We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



BARCLAYCARD & ACCESS WELCOME.



PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.


76 College Road, Bromley, Kent BR1 1DE.

ALL PRICES INCLUDE 15% V.A.T.

nascom

imp

PLAIN PAPER PRINTER

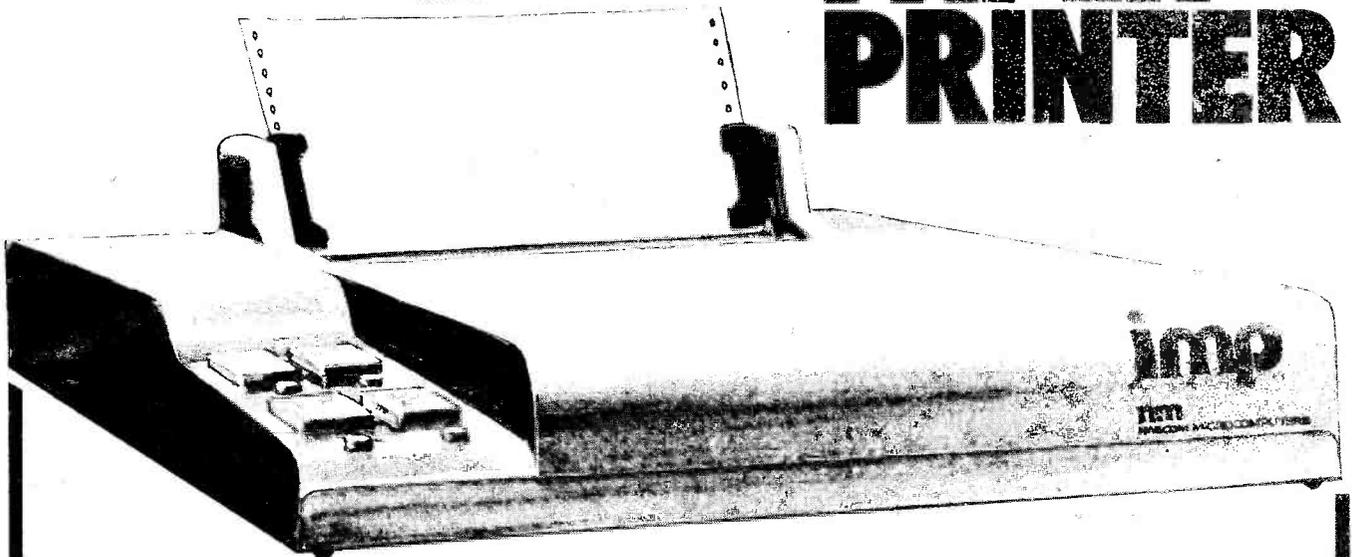

BOXED AND BUILT FOR ONLY £325 PLUS VAT

FEATURES

- Serial RS232 interface.
- 80 characters wide.
- Bi-directional printing.
- 60 lines per minute.
- 10 line print buffer.
- 96 character ASCII set. (includes upper/lower case, \$, #, £)
- Automatic CR/LF.
- 8½" paper (pressure feed).
- 9½" paper (tractor feed).
- Tractor/pressure feed.
- Baud rate from 110 to 9600.
- External signal for optional synchronisation of baud rate.

The Nascom IMP plugs straight into a Nascom 1/2 but is **usable with all other micro systems**. Parallel option will be available shortly.

TO NASCOM MICROCOMPUTERS LTD
92 BROAD STREET
CHESHAM
BUCKS



Nascom Microcomputers

Tel: 02405 75155


NM/ET/2
Please send me.....Nascom IMPs at £325
each plus VAT plus £2.50 p&p

NAME _____

ADDRESS _____

ACCESS/
BARCLAYCARD NO _____

ETI MARKET PLACE

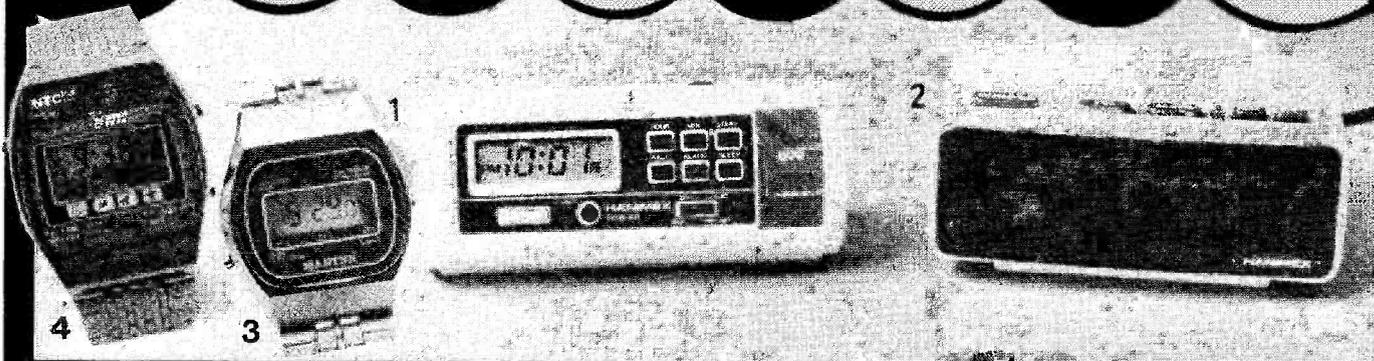

1 CLOCK RADIO

How about a round clock radio which can double as a very smart desk clock — as we can testify!

To time, rotate one end of the cylinder to display the frequency selected. Most of the functions are controlled by a push-button panel and the display is a large, clear LCD affair.

Made by Hanimex, the battery clock radio comes in white, white or white. It will lull you to sleep and then turn itself off an hour later and waken you to the sound of Radio 1, or music if you prefer.

£17.95

To CLOCK RADIO offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

2 DIGITAL ALARM

This mains-only Hanimex alarm has a large 12-hour display incorporating AM/PM and alarm set indicators. You can have a dim or bright display at the touch of a switch. Fast and slow setting buttons make time setting simplicity itself. You can forget about knocking these accidentally in the morning scramble to turn off the alarm, as a locking switch is fitted under the clock. A 9-minute snooze switch completes the list of all mod. clock cons.

£10.60

To: DIGITAL ALARM offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

3 LCD CHRONO

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

The LCD display shows seconds as well as hours and minutes. Press a button and you get the date and day of the week.

Press another button and you have an accurate stopwatch with hundredths of seconds displayed, giving the time up to an hour. There's a lap time facility, too — and of course a back light.

£11.95

To: LCD WATCH offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

4 LCD ALARM CHRONO

This is no ordinary watch. It's a slim, multi-function, dual time LCD alarm chronograph.

This model will show hours, minutes, seconds, date, day of the week, stopwatch, split time, alarm and alternate dual time zone — not all at once of course. There's a night light, too.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The alarm is beefy enough to wake you up in the morning and get you to work on time (or wake you up when it's time to go home).

£16.95

To: ALARM/CHRONO LCD WATCH offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

All prices include 15% VAT and postage

Examples of Marketplace offers can be seen at our Charing Cross Road offices. Please mark your envelope with the offer that you want.

HOME COMPUTING BARGAINS

All of this month's offers have full keyboards, use your tv as a vdu and will read and write onto most cassette recorders — Ohio Scientific Superboard II fully assembled, 8K basic, 4K ram **£188** + vat. Tandy TR80 level II basic, converted to UK tv standard, includes modulator and psu, 16K ram **£450** + VAT.

SINCLAIR PRODUCTS

PFM200 **£52.89**, case **£3.40**, adaptor **£3.40**, connector kit **£11.27**. Microvision tv **£91.44**, mains adaptor **£6.88**, PDM35 **£29.76**, mains adaptor **£3.40**, case **£3.40**, DM350 **£71.82**, DM450 **£102.71**, DM235 **£52.66**. Accessories for all 3 models: — rechargeable batteries **£7.99**, mains adaptor/charger **£3.94**, case **£6**. Enterprise prog calculator **£23.27**. New 10MHz scope **£149**.

COMPUTER GAMES

Chess challenger 7 **£84**. Voice challenger **£239**. Checker challenger 2 **£46**. Checker challenger 4 **£84**. Atari video computer **£147**. Cartridges **£14.32**. Star Chess **£62**. Chess champion 5 **£61**.

CONTINENTAL SPECIALITIES PRODUCTS
EXP300 **£6.61**, EXP350 **£6.61**, EXP225 **£1.84**, EXP650 **£4.14**, EXP4B **£2.64**, LP2 **£20.70**.

TV GAMES

Tank battles kit **£6.34**, AY-3-8500 chip **£5.27**, kit **£4.26**. Stunt cycle AY-3-8760 chip **£12.46**, kit **£4.26**. 10 game paddle 2 AY-3-8500 chip **£10.25**, kit **£7.03**. Racing car chip AY-3-8603 **£13.63**. Modified shoot kit **£5.28**. Rifle kit **£5.27**. Colour generator kit **£9.05**. Joystick 220K **£1.80**.

MAINS TRANSFORMERS

6-0-6V 100ma 76p, 11a **£2.60**, 9-0-9V 75ma 76p, 1a **£2.22**, 2a **£2.89**, 12-0-12V 100ma 92p, 1a **£2.75**, 15-0-15V 1a **£3.09**.

JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 Watts **£2.08**. JC20 10 Watts **£3.14**.

FERRANTI ZN414

IC radio chip **85p**, extra parts and pcb for radio **£4.10**. Case **£1.06**.

PRINTED CIRCUIT MATERIALS

PC etching kits: — economy **£2.32**, standard **£4.36**. 50 sq. ins pcb **86p**, 1lb FeCl **£1.30**, etch resist pens: — economy **50p**, date 84p, drill bits * 32in or 1mm **27p**, etching dish **89p**, laminate cutter **82p**.

S-DECS AND T-DECS

S-Dec **£3.79**, T-Dec **£4.59**, u-DecA **£4.69**, u-DecB **£7.16**, 16 dil adaptor **£2.31**.

SWANLEY ELECTRONICS

DEPT ETI, 32 Goldsea Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 30p to the total cost of your order for postage. Prices include VAT unless stated. Lists 24p post free. Overseas customers deduct 13%. Official credit orders welcome.

BATTERY ELIMINATORS

3-way types with switched output and 4 way multi-jack: — 3/4V/6V 100ma **£2.39**, 6/7 1/2V 9V 300ma **£3.14**. 100ma radio types with press stud connectors 9V **£3.57**, 6V **£3.57**, 4 1/2V **£3.57**, 3+9V **£4.79**, 8+6V **£4.79**, 4+7 1/2V **£4.79**. Cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug **£3.57**. Fully stabilized type 3/6/7 1/2V 9V 400ma **£5.76**. Car converters 12V DC input, output 9V 300ma **£1.19**, output 7 1/2V 300ma **£1.19**, output 3/4V/6/7 1/2V/9/12V 800ma **£2.66**.

BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4 1/2V **£1.49**, 6V **£1.49**, 9V **£1.49**, 4 1/2+4 1/2V **£1.92**, 6+6V **£1.92**, 9+9V **£1.92**. Cassette type 7 1/2V 100ma with din plug **£1.49**. Heavy duty 13 way types 4 1/2V/6/7 1/2V/11/13/14/17/21/25/28/34/42V 1A **£4.95**, 2A **£7.72**. Car converter input 12V DC, output 6/7 1/2V/9V 1A stabilized **£1.35**.

STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. 8-way types 3/4V/6/7 1/2V/9/12/15/18V 100ma **£1.74** (**£2.50**), 1A **£2.98** (**£5.10**), 2A **£4.10** (**£6.87**). Variable voltage models 2-18V, 100ma **£2.12** (**£2.98**), 1-30V 1A **£2.98** (**£5.95**), 1-30V 2A **£4.98** (**£11.24**).

BI-PAK AUDIO MODULES

AL30 **£4.04**, PA12 **£7.17**, PS12 **£1.42**, T538 **£2.70**, S450 **£2.93**, AL81 **£4.97**, PA100 **£17.33**, SPM80 **£4.57**, BM780 **£6.08**. Stereo 30 **£20.57**, MA60 **£36.23**.

COMPONENTS

1N4148 0.9p, 1N4002 3.1p, 741 8 dil **16p**, 723 14 dil **31p**, NE555 8 dil **25p**, bc183, bc213, bc547, bc549 4.2p, bc182, bc184, bc212, bc214, bc548 5p, tp31c, tp32c 30p, tp41c 39p, bd131, bd132 27p, plastic equiv bc107 5p, fuses 20mm x 5mm cartridge .15, .25, .5, 1, 2, 3, 5 Amp quickblow 1p, anti-surge 3.6p, resistors 5% 1/4W £12 10R to 10M 1p, 0.5p for 5p+ of one value, polyester capacitors 250V 015, 068, .1mf 1.5p, .01n .033, .33 2.8p, .022, .047mf 3.3p, .22 47mf 4.9p, polystyrene capacitors E12 63V 10 to 1000 pf 3p, 1n2 to 10n 4p, ceramic capacitors 50V E5 22pf to 47n 2p, electrolytic capacitors 50V .5, 1, 2mf 5p, 25V 5, 10mf 5p, 16V 22, 33mf 5p, 47, 68mf 3.5p, 100mf 6p, 330, 470mf 9p, 100mf 10p, zeners 400mW E24 2V7 to 33V 7p, preset pots subminiature 0.1W horiz or vert 100 to 4M7 6p, potentiometers 1/4W 4K7 to 2M2 log or lin, single 27p, dual 67p, 1/4in red LEDs 8.7p, ic sockets 8 dil 8.7p, 14 dil 10.1p, 16 dil 12.2p.



Wilmslow Audio

THE firm for speakers!

Send 30p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossovers, etc., and discount price list.

- AUDAX ● BAKER ● BOWERS & WILKINS ●
- CASTLE ● CELESTION ● CHARTWELL ● COLES ●
- DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ●
- FANE ● GAUSS ● GOODMAN'S ● I.M.F. ●
- ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ●
- LOWTHER ● MCKENZIE ● MONITOR AUDIO ●
- PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ●
- SEAS ● TANNOY ● VIDEOTONE ●
- WHARFEDALE ● SHACKMAN ● AUDIOMASTER ●
- TANGENT ● STAG ● YAMAHA

WILMSLOW AUDIO Dept. ETI

SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

Discount HiFi, etc., at:
5 Swan Street

TEL. WILMSLOW 529599 FOR SPEAKERS
WILMSLOW 526213 FOR HI-FI

7400	12p	7476	35p	74160	90p	4013	50p
7401	12p	7480	50p	74161	100p	4015	80p
7402	12p	7481	85p	74162	100p	4016	45p
7403	12p	7482	75p	74163	100p	4017	80p
7404	12p	7483	80p	74164	115p	4018	80p
7405	18p	7484	100p	74165	120p	4019	50p
7406	30p	7485	75p	74166	140p	4020	100p
7407	35p	7486	35p	74167	200p	4022	95p
7408	18p	7489	200p	74170	200p	4023	25p
7409	18p	7490	35p	74173	120p	4024	55p
7410	12p	7491	80p	74174	90p	4025	20p
7411	20p	7492	40p	74175	90p	4026	150p
7412	18p	7493	35p	74176	85p	4027	50p
7413	30p	7494	85p	74177	80p	4028	85p
7414	50p	7495	70p	74178	160p	4029	100p
7416	30p	7496	60p	74179	140p	4030	60p
7417	30p	7497	180p	74180	95p	4032	100p
7420	16p	74100	130p	74181	180p	4033	150p
7421	30p	74104	65p	74182	90p	4040	100p
7422	18p	74105	65p	74184	140p	4043	95p
7423	30p	74107	35p	74185	140p	4046	120p
7425	30p	74109	55p	74188	320p	4047	100p
7426	40p	74120	115p	74190	100p	4048	60p
7427	30p	74121	25p	74191	100p	4049	45p
7428	35p	74122	50p	74192	100p	4050	50p
7430	18p	74123	50p	74193	100p	4054	130p
7432	25p	74125	45p	74194	100p	4055	130p
7433	40p	74126	60p	74195	100p	4056	135p
7437	30p	74128	75p	74196	100p	4060	115p
7438	35p	74130	130p	74197	80p	4066	60p
7440	15p	74131	100p	74198	150p	4068	22p
7441	70p	74132	75p	74199	150p	4069	20p
7442	70p	74135	100p	74293	125p	4070	30p
7443	115p	74136	80p	74LS00	15p	4071	20p
7444	115p	74137	100p	74LS11	285p	4072	20p
7445	100p	74141	70p			4075	25p
7446	95p	74142	200p			4077	40p
7447	60p	74143	300p			4081	20p
7448	60p	74144	300p			4082	20p
7450	18p	74145	75p			4093	80p
7451	18p	74147	180p			4501	20p
7453	18p	74148	130p			4507	55p
7454	18p	74150	100p			4510	100p
7460	18p	74151	70p			4511	150p
7470	30p	74153	70p			4516	120p
7472	30p	74154	100p			4518	100p
7473	35p	74155	65p			4520	100p
7474	30p	74156	85p			4528	100p
7475	35p	74157	70p			4583	80p

LINEAR		LM348N		SAS660		TBA810	
CA3039	70p	LM380	80p	SAS670	270p	TBA820	100p
CA3046	70p	LM381N	150p	SL917B	650p	TBA920Q	80p
CA3060	225p	LM382	120p	SN76668N	100p	TCA270S	250p
CA3065	200p	LM391	170p	SN76003N	170p	TCA270Q	250p
CA3076	250p	LM555	25p	SN76013N	150p	TCA760	300p
CA3080	75p	LM565	125p	SN76013ND	130p	TCA4500A	300p
CA3084	250p	LM709C	40p	SN76023N	150p	TDA1004	300p
CA3085	80p	LM710T05	65p	SN76023ND	130p	TDA1008	320p
CA3086	50p	LM710DIL	65p	SN76033N	180p	TDA1022	600p
CA3088	185p	LM723T05	40p	SN76131N	115p	TDA1024	125p
CA3089	225p	LM723DIL	40p	SN76227N	150p	TDA1034	250p
CA3090AQ	400p	LM733	120p	SN76228N	160p	TDA2002	320p
CA3123E	200p	LM739	150p	SN76668N	85p	TDA2020	320p
CA3130	100p	LM741	20p	TAA300	250p	TL081	50p
CA3140	70p	LM747	70p	TAA350	250p	TL082	100p
CA3161E	150p	LM748	40p	TAA550	35p	TL083	110p
CA3162E	450p	LM1303N	95p	TAA570	250p	TL084	130p
CA3189E	250p	LM1458	60p	TAA661B	150p	UAA170	200p
FX209	760p	LM3900	60p	TAA700	340p	XR320	250p
LD130	460p	LM3909N	70p	TAA790	340p	XR2003	150p
LF356	90p	MC1310P	150p	TAD100	150p	XR2206	400p
LF357	90p	MC1312P	160p	TAD110	130p	XR2207	400p
LM211H	240p	MC1314P	190p	TBA120A	60p	XR2208	590p
LM300T05	170p	MC1315P	230p	TBA120S	70p	XR2216	675p
LM301AN	30p	MK50398	650p	TBA120T	90p	XR2264	440p
LM301T05	.45p	MM5314	380p	TBA480Q	190p	XR2265	440p
LM304	190p	MM5316	470p	TBA520Q	190p	XR2567	250p
LM307N	60p	NE529K	150p	TBA530Q	190p	XR4136	150p
LM308T05	100p	NE555	25p	TBA540	220p	XR4151	350p
LM308DIL	100p	NE556	70p	TBA550Q	250p	XR4202	150p
LM309K	140p	NE562B	420p	TBA560C	240p	XR4212	150p
LM310T05	150p	NE566	160p	TBA641A12	250p	XR4739	150p
LM311T05	150p	NE567	170p	TBA700	200p	ZN414	95p
LM317K	350p	SAD1024	1400p	TBA720Q	240p	ZN1034E	200p
LM324	70p	SAS560	155p	TBA750Q	200p	95H90	800p
LM339	70p	SAS570	150p	TBA800	90p	11C90	1400p

IN 4148 DIODES BY ITT/Texas, 100 for **£1.50**
Static RAM 2102 1024 x 1 bit 450 nano sec **£1.00** each
2112 256 x 4 bit 450 nano sec **£2.50**
Murata Ultrasonic Transducers 40kHz **£1.80** each
£3.20 pair

In response to numerous requests we can now supply the ETI Equalizer Kit.

Post and Packing 25p
Add 15% VAT to total order
Minimum order: £1.00

T. POWELL

306 ST. PAULS ROAD, HIGHBURY CORNER, LONDON, N.1. TEL: 01-226 1489
Barclay / Access credit cards accepted

HUM FILTER

Got a hum problem that's making your hi-fi distinctly lo-fi?

Our natty notch filter cuts the moronic mains monotone down to size.

The magnetic field around the transformer in the power amplifier can couple to the preamp or tape deck. Also, the location of nearby 240V mains wiring can cause problems that can be very difficult to overcome. In theory, if the equipment and leads have been properly shielded and earthed this problem shouldn't exist. In practice it's a very different story.




This project aims at overcoming some of the problems of mains induced hum by using a notch filter at the hum frequency of 50 Hz. At this frequency any signal present will be attenuated. At frequencies either side of the notch the response should return to the unattenuated input level.

The 'Q', or Quality Factor, of a tuned circuit — which the RC network in this circuit forms, determines the bandwidth, or narrowness, of the amplitude response of the circuit (see the diagram). As this circuit forms a notch filter, the Q of the circuit determines the narrowness of the notch.

With a high-Q notch the frequency response of the circuit will dip suddenly around the notch frequency. Frequencies a little either side of the notch centre frequency will be little affected. If the Q is low, frequencies some way either side of the notch frequency will be attenuated. The actual attenuation at the notch frequency is greater with a high-Q circuit than with a low-Q circuit.

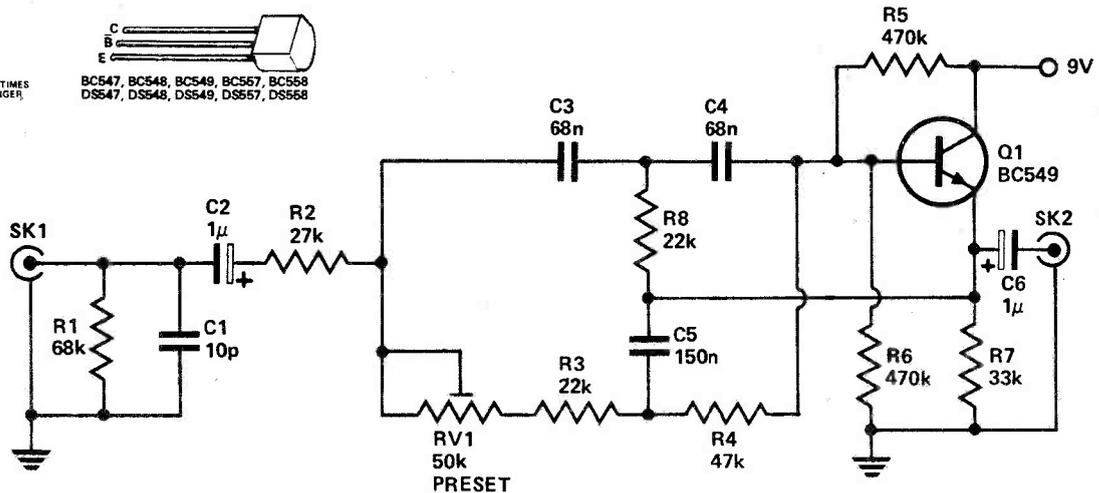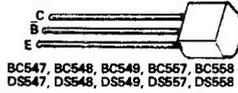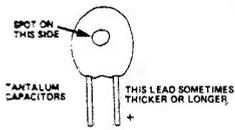High-Q circuits have the disadvantage that slight changes in component values, due to temperature changes etc, will affect the centre frequency. Tuning of the circuit to frequency is also quite critical. Lower-Q circuits do not suffer





NOTE
ONLY ONE CHANNEL HAS BEEN SHOWN FOR CLARITY. THE COMPONENT NUMBERING OF THE OTHER CHANNEL BEGINS at 101 i.e. R101 R102 etc.

Fig. 1. Circuit diagram of one channel of the hum filter.

so much from this disadvantage.

The design Q chosen for this project was a compromise between the constraints of critical tuning and drift effect and good attenuation at the notch with little effect on nearby frequencies. Peak attenuation at the notch centre frequency of 50 Hz is around 80 dB while attenuation of only 3 dB is obtained at 40 Hz and 58 Hz. There is some audible effect on the bass response of a system, but this is minimal.

Construction



Mount the resistors and capacitors on the board first. Be sure the orientation of the tantalum capacitors is correct. These are polarized and can only be installed one way round. Next, install the preset pot. Finally, solder the transistor in place.

The circuit is run from a single nine volt battery. The current consumption of the prototype was 200 uA so the battery life should be good for several months. If it is found that battery life is not long enough a power switch could be fitted.

The filter can be used almost anywhere in the amplification chain since its overload margin is very high (typically 8 V p-p). It should obviously be placed after the point where the hum is being picked up. If the hum is in the turntable and the magnetic phono input of the amplifier since the input impedance is 47 k shunted by 10 pF, which should suit most magnetic cartridges.

Once the filter is in place, the presets are adjusted so that the hum is brought to a minimum by adjusting each channel independently.

HOW IT WORKS

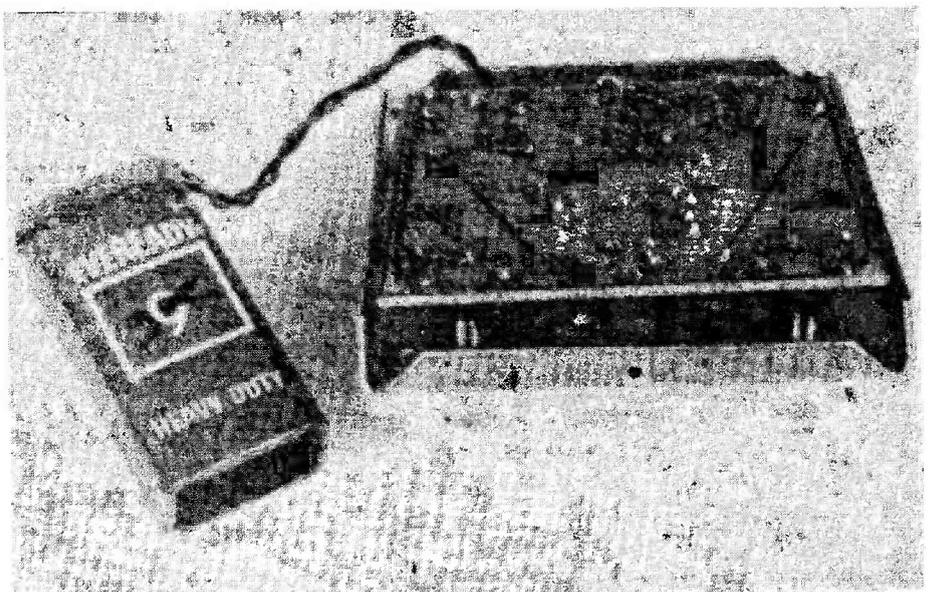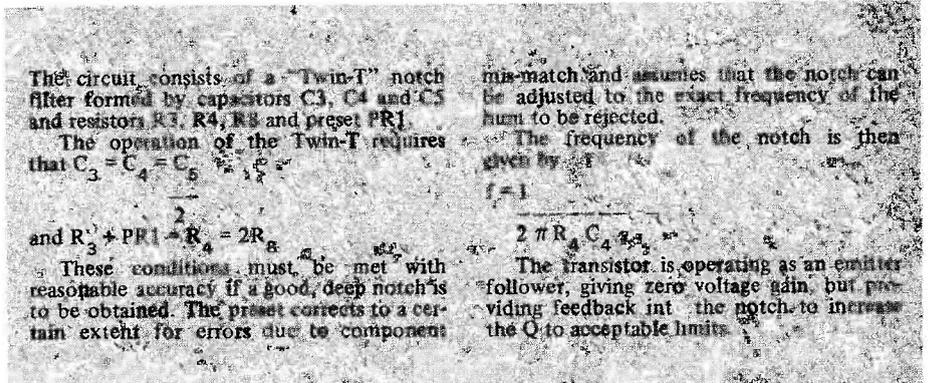

► The finished PCB fitted to the front panel, with the battery on flying leads.

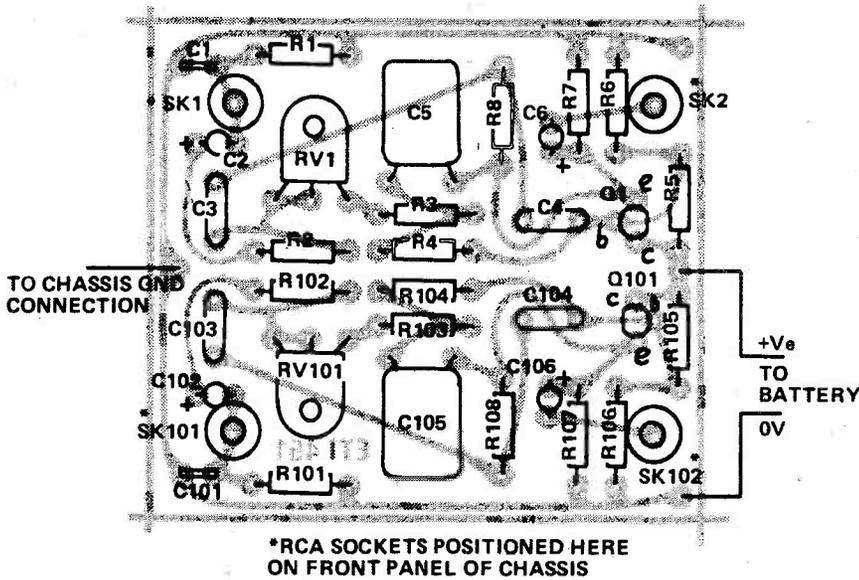


Fig.2. Component overlay.

PARTS LIST

Resistors all 1/4W, 5%

R1, R101 68k
 R2, R102 27k
 R3, R103, 8, 108 22k
 R4, R104 47k
 R5, R6, R105, R106 470k
 R7, R107 33k

Capacitors

C1, C101 10pf ceramic
 C2, C102, 6, 106 1u tantalum
 C3, C4, C103, C104 68n polyester
 C5, C105 150n polyester

Potentiometers

RV1, RV101 50k min preset

Semiconductors

Q1, Q101 BC549, BC109



Miscellaneous

ET1 451 PCB, box to suit, 4 panel mounting.

Components for 100 Hz operation

R4, R104 22k
 R8, R108 10k

Replace R3 with wire link.

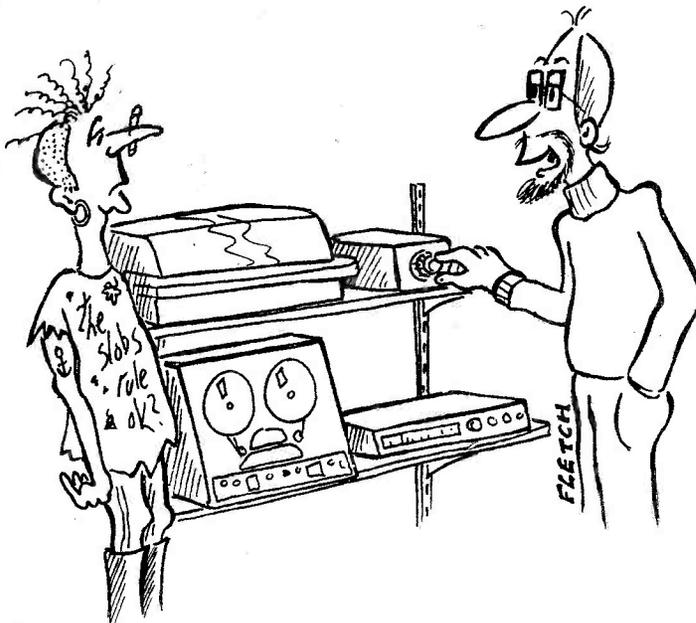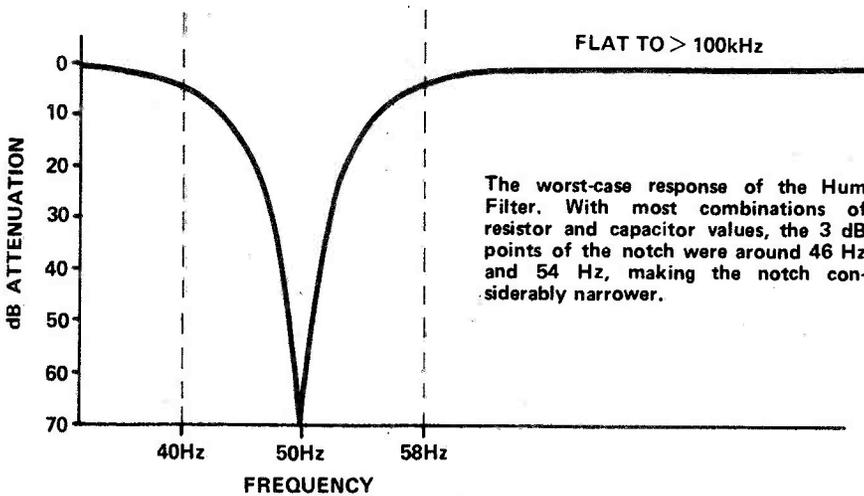

"IT'S A GREAT HUM FILTER - WON'T LET ANY PUNK ROCK THROUGH AT ALL!"

BUYLINES

You shouldn't have any difficulty in getting hold of any of the components for this project. We haven't bothered to box our prototype. You can use anything from a plain aluminium box to a classy wooden case - whatever takes your fancy.

Britain's Best Breadboard Buy at Breadboard '79

**FREE
ENTRY TICKET
WORTH £1.00
WITH EVERY PURCHASE**

All over Britain, hobbyists are discovering Britain's Best Breadboard Buys. At the London Breadboard exhibition '79 on Stand Nos. F1, F2 and G1, G2, CSC will be exhibiting their full range of breadboards.

Here is your chance to obtain a special ticket for Breadboard '79 worth £1.00 absolutely FREE.

Cut out the coupon below and take it along to one of our listed dealers, and make a purchase of any of our breadboards and receive your special FREE ticket — see you at Breadboard '79.

Take the coupon to any of these main dealers:

LONDON

Rastra Electronics Ltd., 279-281 King Street, Hammersmith, London W6

Cubegate Ltd., Audio Electronics, 301 Edgware Road, London W2 1BN

Technomatic Ltd., 17 Burnley Road, London NW10 1ED

Precision Instrument Labs., Instrument House, 727 Old Kent Road, London SE15

MANCHESTER

Shudehill Supply Co., 53 Shudehill, Manchester M4 4AW

BUCKINGHAMSHIRE

West Hyde Development, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET

Best Electronics (Slough) Ltd., Unit 4 Farnburn Ave., Slough, Bucks SL1 4XU

KENT

Lawtronics, 13a High Street, Edenbridge, Kent TN8 5AX

NEWCASTLE

Airken Bros., 35 High Bridge, Newcastle upon Tyne

SCOTLAND

Marshalls, 85 West Regent Street, Glasgow G2

F. Brown & Co., 45 George IV Bridge, Edinburgh EH1 1E3

LEEDS

Leeds Amateur Radio Club, Cookridge Street, Leeds 1


HERTFORDSHIRE

BI-PAK, 3 Baldock Street, Ware, Herts.

CONTINENTAL SPECIALTIES CORPORATION



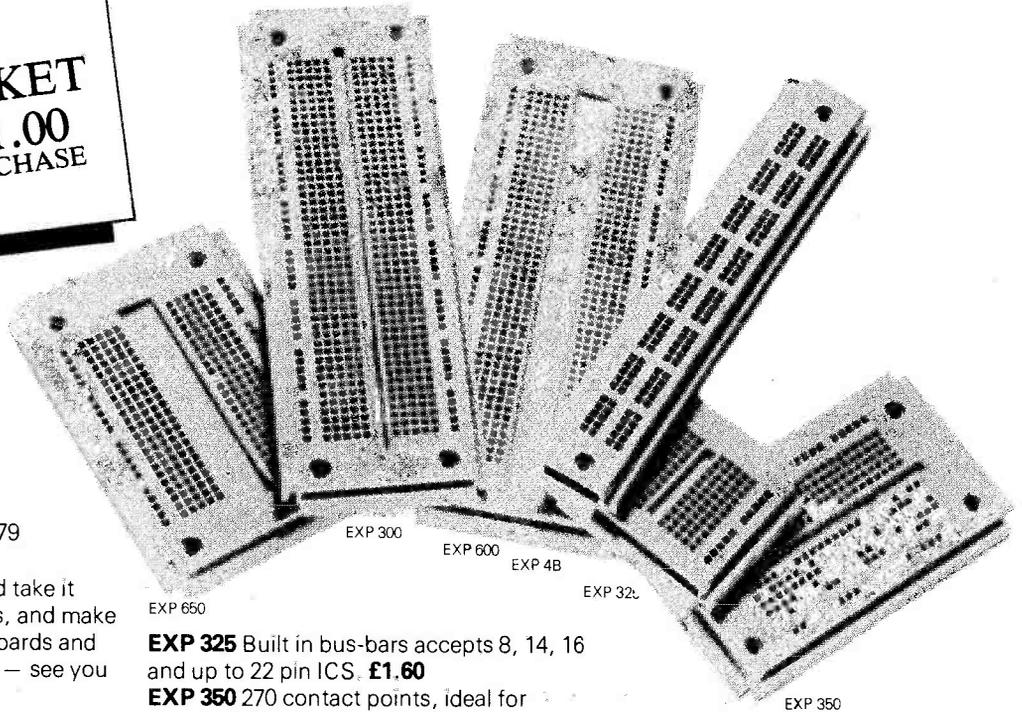CSC UK LTD. EUROPE, AFRICA, MIDEAST
Dept 9CC2 Shire Hill Industrial Estate Units 1 and 2, Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682. Telex: 817477



EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. **£1.60**

EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**

EXP 650 For microprocessor chips. **£3.60**
EXP 4B An extra 4 bus-bars in one unit. **£2.30**

EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**

EXP 600 6" centre channel makes this the Microprocessor Breadboard. **£6.30**

PB6 Professional breadboard in easily assembled kit form. **£9.20**

PB100 Kit form breadboard recommended for students and educational uses. **£11.80**

The above prices do not include P&P and 15% VAT

The Experimenter System

4 ways to order Experimenter Systems

- EXP 300PC which includes one item.
A matchboard pre-drilled PCB — £1.32
- EXP 302 which includes three items.
Three 50-sheet scratchboard workpads — £1.68
- EXP 303 which includes three items.
Two matchboards and an EXP 300 solderless breadboard — £8.60
- EXP 304 which includes four items.
Two matchboards and EXP 300 breadboard and a scratchboard workpad — £9.30

This coupon entitles the holder to a free ticket worth £1.00 to Breadboard '79, with the purchase of any listed breadboards

1. EXP 325 £2.70	Qty. Reqd.	2. EXP 350 £4.48	Qty. Reqd.
3. EXP 650 £5.00	Qty. Reqd.	4. EXP 4B £3.50	Qty. Reqd.
5. EXP 300 £7.75	Qty. Reqd.	6. EXP 600 £8.39	Qty. Reqd.
7. PB6 £11.73	Qty. Reqd.	8. PB 100 £14.72	Qty. Reqd.

Experimenter System

1. EXP 300PC £2.38	Qty. Reqd.	2. EXP 302 £2.79	Qty. Reqd.
3. EXP 303 £11.04	Qty. Reqd.	4. EXP 304 £11.85	Qty. Reqd.

Boxed prices include P&P and 15% VAT

If no dealer in your area contact CSC direct.

Continental Specialties Corporation, (U.K.) Limited, Dept 9CC2

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex Tel. (0799) 21682

NAME

ADDRESS

FREE catalogue tick box

I enclose cheque/PO for £
or debit my Barclaycard, Access, American Express card

No. Exp. date
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.



C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection): electronic variable dwell circuit (maximises spark energy at all speeds): pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases). Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TCI).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service.



Suretron Systems (UK) Ltd.
Piccadilly Place, London Rd., Bath BA1 6PW. Tel: Bath (0225) 23194

Name
Address

Phone order with Access: Barclaycard
VAT and P & P inc.

Quantity
required

ES200: Neg	£13.95	£11.95	
C300: Pos	£17.95	£15.95	
C300: Neg	£17.95	£15.95	
Tacho Adapt. TCI		£3.90	

I enclose
chq/PO's
£
Chq No.

STRATHAND SECURITY

WE HAVE EXPANDED TO NEW PREMISES AT 32 ST. ANDREW'S SQUARE, GLASGOW, WHERE WE CAN NOW OFFER AN EVEN BETTER SERVICE, WITH A LARGER RANGE OF PRODUCTS AT BETTER PRICES

Our Telephone Number and Telex No. remain unchanged

Solfan Microwave — 15M Range — neat and unobtrusive — ideal for home and office. Requires 12V DC at 130 MA. Normally closed contacts open under attack conditions: Walk test lamp built in.

This month's price inclusive of V.A.T. and P. and P. **£74.75**

- Flush Reed Switch and Magnet **£1.00**
- Surface Reed Switch and Magnet **£1.00**
- Pressure Pad, large **£2.50**
- Pressure Pad, stair size **£1.75**
- Bell 12V DC 6-inch Heavy Duty, very loud **£11.50**
- Horn Sounder 110 DBA 12V DC 0.6A **£22.00**

All prices include V.A.T. at 15%, postage and packing.

Many other items too numerous to detail. Price List free with s.a.e. Catalogue, giving wiring details, etc., only £1.00 refunded on orders over £10.00.

THIS MONTH'S BARGAIN OFFER

Bell Cover — plastic coated steel — normally **£8.50** — this month **ONLY £6.50**

Special discounts for orders over £250.00

All goods are held in stock and are despatched normally within 24 hours. For prompt service Phone Nancy on 041-552 6731.

Callers Welcome



STRATHAND



32 St. Andrew's Square, Glasgow, G1 5PL

Tel: 041-552 6731 or 2

Telex: 777268 (24 hours' service)

You've heard about it

Read about it — HERE IT IS

AVAILABLE EX-STOCK
COMPLETE KIT AS PER
MANUFACTURER'S SPECIFICATION

With provision for 8K on board expansion. Excludes 4118 x 8*

INCLUDES FREE 16K EXPANSION
VALUE £140 includes ALL parts with every kit

NASCOM-2
ON DEMONSTRATION NOW

£295 +15% WITH
VAT FREE
16K EXPANSION WORTH £140

AVAILABLE ONLY FROM US ON THE COUPON BELOW

OPTIONAL EXTRAS
3 AMP POWER
SUPPLY VAT 15%
£29.50 Post £1.50
For NASCOM-2

8 OFF 4118*
For NASCOM-2
PURCHASERS
£80 Early
Delivery

RS232 COMPATIBLE

80 COLUMN PRINTER brand new
List price £550. If sent by carrier £5 extra

OUR PRICE
£325 + VAT
15%

FULL MANUFACTURER'S WARRANTY — DON'T DELAY, ORDER TODAY

Please send me my **NASCOM-2 KIT** with the **FREE 16K EXPANSION** for **£295 + VAT**.

I enclose remittance to cover

Name & Address

Also in stock NASCOM-1 • ELF • TRS80 as previously advertised




HENRY'S



Computer Kit Division
404 Edgware Road, London, W2, England
01-402 6822

SPECIALS

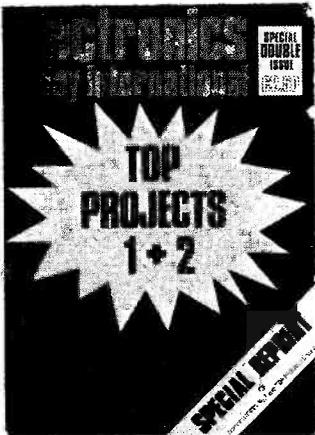

TOP PROJECTS

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp., low power laser, printmeter, transistor tester, mixer preamp., logic probe, Ni-Cad charger, loudhailer, 'scope callibrator, electronic ignition, car theft alarm, turn indicator canceller, brake light warning, LM3890 circuits, temperature alarm, aerial matcher, UHF-TV preamp., metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

Book 3: SOLD OUT!

Book 4: £1.00 + 25p P&P.

Sweet sixteen stereo amp., waa-waa, audio level meter, expander/compressor, car theft alarm, headlamp reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit ...

Book 5: £1.00 + 25p P&P.

5W stereo amp., stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, general purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter ...

Book 6: £1.00 + 25p P&P.


Graphic equaliser, 50/100W amp. modules, active crossover, flash trigger, "Star and Dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show ...



ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.

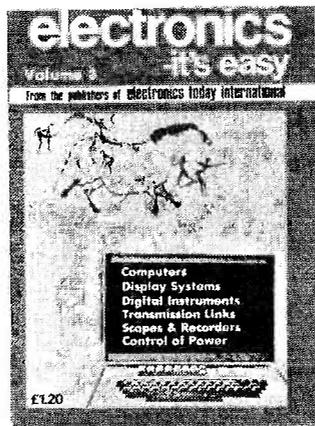

ELECTRONICS — IT'S EASY

Books 1, 2 & 3.

Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics.

£1.20 + 25p P&P each.

FROM THE PUBLISHERS OF
ELECTRONICS TODAY INTERNATIONAL

ETI CIRCUITS No 2

£1.50

ETI CIRCUITS

Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.

ORDER FROM
Specials Modmags Ltd, 145 Charing Cross Road, London WC2

Postage and packing also refers to overseas. Send remittance in Sterling only.
Please mark the back of your cheque or PO with your name and address.

NOW OUT!

TOP PROJECTS

Book 7: £1.25 + 25p P&P.

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, IB metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.

from ETI



RAVEN ON...

This month Dave Raven, of Metac Electronics, has a bash at crystal gazing into the future of computers and delves into chip reliability.

Predicting the future in electronics is a regular feature of TV and the press with "Tomorrows World" and newspaper features on technology. People not involved in science probably have difficulty believing the forecasts since they are quite often so far outside what we already understand.


Home computers and Robotics are two areas which receive quite a lot of attention since they are predicted to be areas which will have major effects on the ways in which we work and live. At a recent symposium held in France by a computer manufacturer, experts assembled to discuss the future. It was predicted that there will be at least four major computer revolutions during the 1980s. The component processors revolution forecast for 1979/80 begins with the basic building blocks for computers and communication systems, large scale integration and very large scale integration of devices, hardware, intelligent machine products, people appliances, digital automation products, communications ICs and intelligent data communication satellite systems. All this resulting in components becoming the end product.

Phase two will begin 1981/83 with the Component Computer revolution. This will provide intelligent data management systems and communications subsystem components with the machine/computers becoming just components. Carrying on in 1983/85 we should have the component memory age. This kicks off with the basic building block for information systems, distributed memory, a system component revolutionising com-

munications, information appliances, a data base computer and knowledge based systems. This results in memory becoming components and offices becoming portable machines. Phase four brings the component systems revolution forecast for 1985/88. The component systems will further revolutionise our institutions leading to the end of the main frame computer and allow factories to become machines. The era will be the "system on a wafer technology", communications will substitute for travel and buildings and an information society will emerge. Computers become components and factories become machines. Computer evolution is increasing tenfold every decade and chip technology at 100x/decade while innovation is going at 1000x/decade.

Robots for Robots

People amplifier appliances, the knowledge based system and robots. In the 1990s we can expect intelligent robots, androids and world linked robots. Also, would you believe worker/slave robots for robots. If you find a credibility gap emerging between yourself and the prophets of the future it may be of interest to read this extract from The Times of January 28th 1926 — "Members of the Royal Institution and other visitors to a laboratory in an upper room in Frith Street, Soho, on Tuesday, saw a demonstration of apparatus invented by Mr J. L. Baird. For the purpose of the demonstration the head of a ventriloquist's doll was

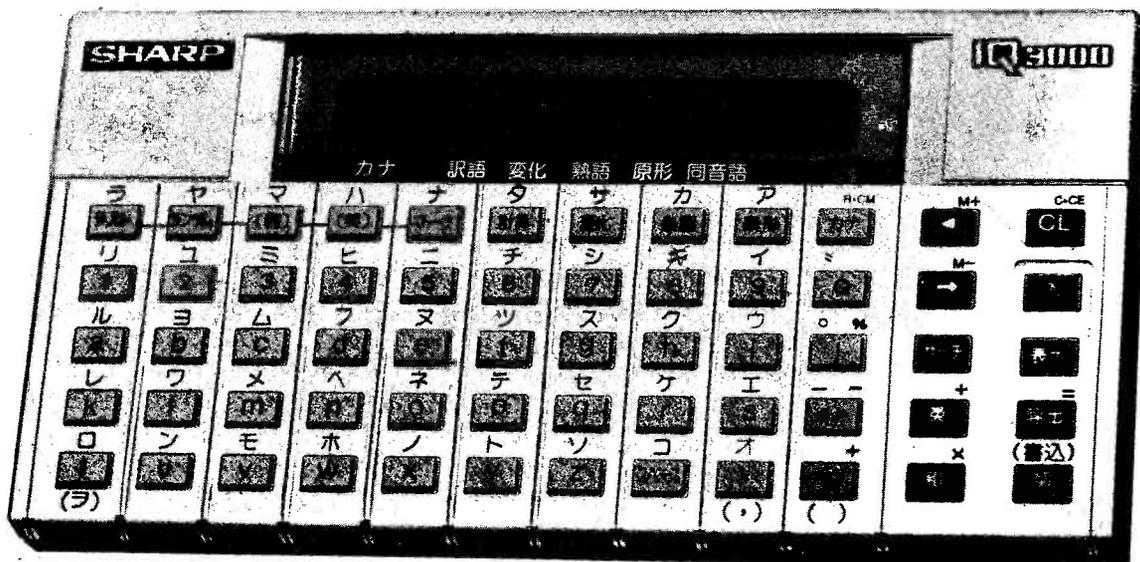

manipulated as the image to be transmitted through the human face was also reproduced, first on a receiver in the same room as the transmitter and then on a portable receiver in another room. The visitors were shown recognisable reception of the movement of the dummy head and a person speaking. The image transmitted was faint and often blurred, but substantiated a claim that through the 'televisor' as Mr Baird has named his apparatus, it is possible to transmit and reproduce instantly the details of movement and such things as the play of expression on the face."

The Cathode Ray tube was of course still only a suggestion made back in 1907 by Cambell Swinton in England and Boris Rosing in Russia. So far, though, this suggestion had produced no satisfactory system of television.

Global Games

Electronic home entertainment equipment is largely imported into the UK from Japan and Hong Kong. Some items are made in Taiwan and South Korea. However, these two countries have stronger links with America. Several European firms have set up manufacturing in special export zones in India which have very attractive tax benefits. Both Philips and Rank Radio are in India, also many other companies have goods manufactured in the Far East with their own brand name on. Hong Kong is particularly strong in exporting to England due mainly to our colonial ties. Goods from Hong Kong have been much maligned over the years for low quality probably due to the cheap plastic toy image they are best known for. Early electronic products were of varying quality but since this new technology was not completely debugged it was not only Hong Kong that had problems (reference UK made TV games, calculators and electronic watches).

The high failure rate of electronic goods at the onset of production is nearly always caused by the chip. The low yields of TV game, calculator and watch chips is well documented but as usual the problems are eventually solved and the yield dramatically improves. Now with calculators, TV games and many watch chips the producer just cranks the handle and out they come by the bucketful.

Nipon Word Box

Having referred to the possibility of an electronic dictionary last month it is not surprising that one has now appeared, such is the speed of development in electronics. Made in Japan this time by Sharp it will be going on sale next month.

It features 48 kilobytes of read-only memory together with logic and display control circuits. The liquid crystal display is in dot-matrix and this enables it to run for about 1,000 hours on three silver-oxide batteries.

The dictionary is for Japanese-English, English-Japanese and is intended primarily for Japanese people learning English. It has a central processing unit, two display-control chips and four 12-kilobyte ROMs encoded with a total of 2,500 English words, 300 English compounds and 5,000 Japanese words. Conjugations of English verbs are provided and the dictionary form can be called up from another tense at the push of a button. One further novel feature is a test key for checking the spelling of an English word with a reply of "good" or "wrong". It can also process incorrect or incomplete information. If a user tries to translate "speak" the display will respond with "speak?"

ETI

V MOS POWERFETS & CHEAP LINEARS	FASTER BREEDS OF LS TTL, CMOS, DAC/ADC
★VN67AF (60v, 2A, 15W, TO202) 85p	★AM25LS161 (40MHz min 74LS161) 75p
★VN10KM (60v, 1/2A, 1W, TO92+ tab) 60p	★AM25LS174 (50MHz min 74LS174) 70p
TO202 Heat Clip 12p	★AM25LS191 (35MHz min 74LS191) 90p
TO92 Heat Clip 8p	★AM25LS251 (9nS max 74LS251) 65p
VMOS Design Catalog (96 page) 20p	★AM25LS253 (9nS max 74LS253) 65p
CA3080 (Programmable OTA) 70p	4001B (t _r 25nS typ. @ 10v) 14p
CA3140 (BIMOS, drives TTL) 38p	4007UB (t _r 20nS typ. @ 10v) 14p
LM308 (Precision opamp) 25p	4011B (t _r 25nS typ. @ 10v) 14p
LM733 (120MHz diff. amp) 50p	4013B (f _{reg} 25MHz typ. @ 10v) 28p
LM741 (Famous, minidip) 18p	4016B (BW 90MHz typ. @ 10v) 33p
LM3900 (Quad opamp substitute) 43p	4017B (f _{reg} 16MHz typ. @ 10v) 55p
MC3401 (Cheaper ditto) 30p	4020B (f _{reg} 25MHz typ. @ 10v) 70p
NE529 (10nS Comparator) 145p	4069UB (t _r 20nS typ. @ 10v) 14p
★TL081 (BIFET, fastslew) 29p	DAC08 (10MHz, 0.19%, 8 bit DAC) 225p
★TL074 (Quad TL081 + low noise) 130p	2502 (25MHz SAR for above) 555p
78L05 (5%, TO92, 5v reg.) 29p	★DAC08 + 2502 + NE529 (=2uS ADC) 900p
709C (T05, 12v/uS decomp) 15p	

Free brief data on ★ items. Full data 25p/item. Prices inc. P&P 25p
Mail Order Only

J. W. RIMMER 367 GREEN LANES
LONDON N4 1DY

PROTON ELECTRONICS

MC1458 35p	LEDs, red 0.125" 9p
741 metal car. Same pin config. as plastic 8-pin 14p each	Green 0.2" 12p Yellow 12p
NE555 25p	0.2" Clips 2p
741 plastic 8-pin DIL 18p	Resistors 0.5w 5% E12 Carbon Film 10Ω - 10MΩ 1p
BC107 7p BC108 7p	
BC109 7p BC147 7p	
BC148 7p BC158 7p	
BC182 7p BCY70 9p	
BCY71 9p BCY72 9p	
BC117 18p BC143 20p	
BF180 25p OC71 15p	
2N3055 35p	
IN4148 2p IN4004 3 1/2p	
IN4005 3 1/2p IN4007 4 1/2p	
IA400V Wo4 Bridge Rect. 30p	
Zeners 400mw 5% 8p	

Post and packing 25p C.W.O.

DISCOUNT: 10+ off one value, 10% off, except on LEDs, ICs, Zeners.

1A, 2& 4 STOPES ROAD, RADCLIFFE MANCHESTER M26 0TN

ELECTRONIC CAR ELECTRICS

FITS ALL 12 VOLT SYSTEMS **2 YEAR G'TEE**

Here is an instrument the size of a matchbox that mounts on or under your dash in just a few minutes and will display the condition of your battery, and monitor your charge rate. The display shows red and yellow stripes when all is well. Faults are shown as red only or yellow only, and our unique fault finding guide helps you track them down.

TRY THE C-MORE ON YOUR CAR

We'll despatch it by return and if you don't like: ★ **THE HIGH BRIGHTNESS LED DISPLAY** ★ **THE EASE OF INSTALLATION** ★ **OUR UNIQUE FAULT FINDING GUIDE** ★ or anything else. Send it back within 10 days for a refund of the purchase price.

Please send **C-MORE'S** at **£6.35 ea.** (inc. VAT) (+27p U.K. p&p, 50p Airmail, Export, please).

To: _____

Cheque / P.O. / I.M.O. Value.

To: **HARVELEC (Dept. ET)**
1 Formby Avenue, St. Helens
Merseyside WA10 3NW
Regd. in U.K. No.: 2395248

All this for lower cost than conventional instruments that offer less

McLAREN AUDIO BY POST AT DISCOUNT PRICES.

20w per channel Amplifier only **£52.95** Post Free

McLaren, Scotland's leading audio manufacturer, offer a fully guaranteed 20w per channel stereo amplifier direct from the factory for just **£52.95 post free**. Features base, treble, volume balance controls and push button selectors for P/U, Radio, Auxiliary, Tape, Mono, Hi-filter and On/Off. Harmonic distortion better than 0.05% at -3dB of full rated output. Superb black finish with wood surround. Send cheque or P.O. to **GR International Electronics, Almondbank, Perthshire PH1 3NQ**. Goods sent by security delivery within 21 days of receipt. Full money back guarantee if not satisfied. For further information or details of cassette players, B tracks, matched record deck or speakers, write or phone Mr W Latta, Almondbank (073 883) 441.

INTERVAL TIMER

The ultimate in analogue - scale precision timers. This inexpensive wide-ranged relay-output unit spans 1 minute to 20 hours in three switch-selected ranges and has a long term calibration accuracy better than 1%.


Electronic timer units have numerous home, hobby and engineering applications. They can be designed to have either analogue or digital "Time set" indicators or scales, on which the required timing period is initially set. Their relay-contact outputs can be used to control lamps, heaters, battery chargers, photographic enlargers etc.

Analogue-scale timer circuits have the advantage of low cost. Most previously published circuits of this type, however, have had very restricted maximum timing ranges (fifteen minutes or less) and have suffered from very poor long-term accuracy (20%, or worse), due to the use of electrolytic timing capacitors and high-value timing resistors. Digital-scale timer circuits, on the other hand, have the advantage of high accuracy, but the disadvantage of relatively high cost.

Our new wide-range timer gives you the best of both worlds. It is an analogue-scale device that uses digital frequency division techniques to give a very wide timing range (1 minute to 20 hours), but uses a basic clock generator with non-electrolytic timing capacitors and consequently has a high degree of intrinsic long-term accuracy (better than 1%). The timer is inexpensive, having a typical component cost (excluding the relay) of three or four pounds. The unit consumes zero current when it is in the 'standby' mode and thus does not need a separate on/off switch.

CONSTRUCTION

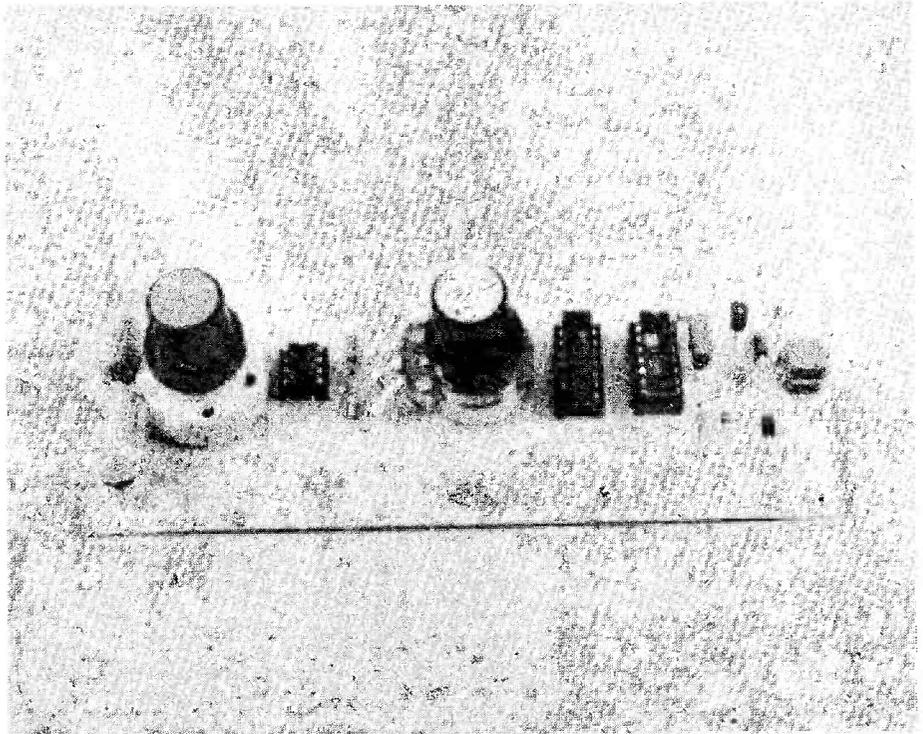All of the components of this unit (including the switches and the pot but excluding the relay) are assembled on a single PCB and construction should present few problems. The three ICs should be mounted in suitable holders. The two switches are



PCB-mounting types (see components list). Note that we have made up the 12 value of C2 by wiring two capacitors in parallel.

Take special care to relate the circuit diagram to the PCB overlay when connecting the relay and the power supply to the unit. The PCB is provided with five external connection points (one is rather sneakily hidden to the left of push-button PB1 on the overlay). Two of these connections go to the relay coil, one goes to supply zero, one goes to one of the relay contacts, and the remaining connection goes to the other relay contact and also to the supply positive. If the relay fails to latch on when you first give the unit a functional check, suspect an incorrect connection to the relay.

When construction is complete,

check that the unit is fully functional by momentarily closing PB1 and checking that the relay locks on for the timing period. You can then, if you wish, mount the unit in a suitable box and calibrate the RV1 scale against a clock on the two lowest timing ranges. The calibration of the top (100min-20 hours) timing range will be a factor of precisely ten above the middle (10 min - 2 hours; timing range).

BUYLINES

There should be no problems in obtaining any of the components used in the timer.

All ICs are common types available from most components shops.

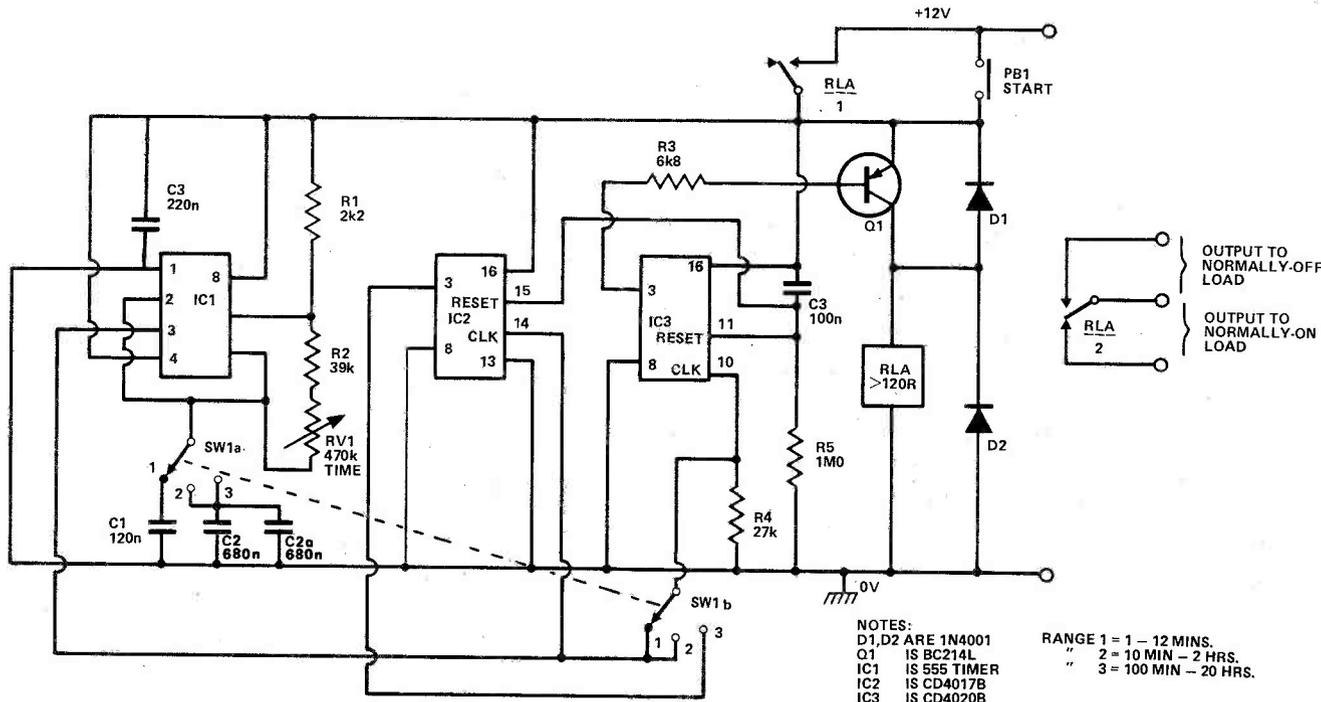


Fig. 1. Circuit diagram.

PARTS LIST

RESISTORS All 1/4W, 5%

R1	2k2
R2	39k
R3	6k8
R4	27k
R5	1M0

POTENTIOMETER

RV1	470k
-----	------

CAPACITORS

C1	120n polycarbonate
C2,a	680n polyester

SEMICONDUCTORS

IC1	NE555
IC2	CD4017B
IC3	CD4020B
Q1	BC214L
D1,2	1N4001

MISCELLANEOUS

PB1	momentary push button
SW1	2-pole 3 way rotary switch

Relay to suit.
 Foil pattern.

NOTE: The value of C3, shown on the circuit diagram and component overlay, is 220n.

HOW IT WORKS

In this circuit IC1 is a 555 timer, connected in the astable mode, and is used as a clock generator for the IC2 and IC3 frequency divider circuitry. IC2 is a 4017 decade divider. IC3 is a 4020 14-stage binary counter and in this particular application effectively divides the clock frequency by a factor of 8192.

Power is applied to the circuit by momentarily closing PB1, at which moment the two counters are set to zero via C3 and the relay is driven on via Q1. As the relay turns on its contacts change over and maintain the power supply connections to the unit when PB1 is subsequently released. The IC1 astable starts to generate clock pulses as soon as power is applied.

On range 1 (1-12 mins) the astable period is determined by C1 and R2-RV1. The clock signal is divided down by IC3, which changes state on the arrival of the 8192nd pulse and turns the relay off and breaks the supply connections to the circuit. A similar action takes place on range 2 (10 mins - 2 hours), except that the clock frequency is determined by C2 and R2-RV1.

On range 3 (100 mins to 20 hours) the clock frequency is again determined by C2 and R2-RV1, but in this case the frequency is divided by both IC2 and IC3, so that the relay turns off and breaks the supply connections on the arrival of the 81920th clock pulse.

The spare (RLA/2) set of RLA change-over contacts can be used to control external circuitry.

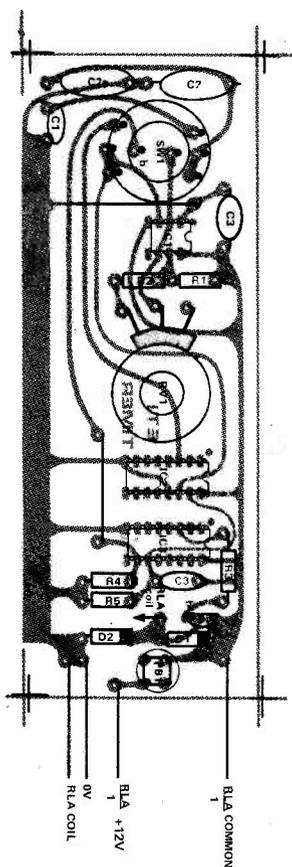


Fig. 2. Component overlay.



IT'S A DOGS LIFE!

Mighty mongrel strikes again!

Stop your powerful pooch carving up your carefully collected ETIs with his canine choppers and live in hardback harmony with a profusion of precious project books by armour-plating your archives.

Invest in an ETI binder. You know it makes sense.



You can have any colour you like as long as it's black.

Send a mere £3.20 to:
ETI Binder
 145 Charing Cross Road
 London WC2H 0EE

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS

STEREO PRE-AMPLIFIER POWER AMPLIFIER

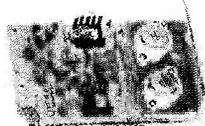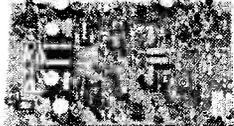

CPR 1 — THE ADVANCED PRE-AMPLIFIER. The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV, distortion < 0.05% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp signal levels. Signal to noise ratio 86dB, slew-rate 3V/uS. T.H.D. 20Hz—20kHz < 0.08% at any level.

F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138x80x20mm. Supply to be ±15 volts.

MC 1 — PRE-PRE-AMPLIFIER. Suitable for nearly all moving-coil cartridges. Sensitivity 70/170uV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

XO2:XO3 — ACTIVE CROSSOVERS. XO2 — two way, XO3 — three-way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1 — POWER SUPPLY. The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS. It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification. T.H.D. typically .01% any power 1kHz 8 ohms. T.I.D. insignificant, slew rate limit 25V/uS, signal to noise ratio 110dB, frequency response 10Hz-35kHz — 3dB stability unconditional, protection drives any load safely, sensitivity 775mV (250mV or 100mV on request), size 120x80x25mm.

POWER SUPPLIES. We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).


POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier)

POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.

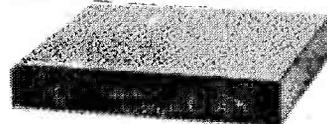PRE-AMPLIFIER KIT
 THIS INCLUDES ALL METALWORK, POTS, KNOBS, ETC. — TO MAKE A COMPLETE PRE-AMP WITH CPR 1(S) MODULE AND THE MC1(2) IF REQUIRED.



POWER AMPLIFIER MODULES

CE 60B 60W/8 ohms 35-0.35v	£19.52
CE 100A 100W/8 ohms 35-0.35v	£23.02
CE 100B 100W/8 ohms 45-0.45v	£25.96
CE 170A 170W/4 ohms 45-0.45v	£31.00
CE 170B 170W/8 ohms 60-0.60v	£33.97

TOROIDAL POWER SUPPLIES

CPS1 for 2xCE 60B or 1xCE 100A	£16.56
CPS2 for 2xCE 100A or 2/4xCE 60B	£18.80
CPS3 for 2xCE 100B or 1xCE 170A	£19.75
CPS4 for 1xCE 100B	£17.12
CPS5 for 1xCE 170B	£24.15
CPS6mk 2xCE 170A or 2xCE 170B	£25.53

HEATSINKS

Light duty, 50mm, 2 C/W	£1.44
Medium power, 100mm, 1.4 C/W	£2.35
Disco/group, 150mm, 1-1 C/W	£3.04
Fan, 80mm, state 12U or 240v	£19.70

POWER AMP KIT

2x4 C/W, 65 max. with two 170W modules	£31.05
--	--------

THERMAL CUT-OFF, 70°C

	£1.54
--	-------

Distributors:
 Minic Teleproduktur
 Box 12035
 S-750 12
 Uppsala 12
 Sweden

Badger Sound Services Ltd., 46 Wood Street, Lytham St. Annes, Lancashire FY8 1QG.

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

POWER AMP KIT £35.03

PRE-AMPS

These are available in two versions — one uses standard components, and the other (the S), uses MO resistors where necessary and tantalum capacitors.

CPR1	£31.65
CPRIS	£40.87
MC1	£21.28
MC1S	£33.17
Pre-amp Kit	£38.07

ACTIVE CROSSOVERS

XO2	£15.16
XO3	£23.58

POWER SUPPLY

REG1	£6.90	TR6	£1.97
------	-------	-----	-------

BRIDGE DRIVER, BD1

Obtain up to 340W using 2x170W amps and this module.
 BD1 £5.75

CRIMSON ELEKTRIK


1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 553506.
 U.K. — please allow up to 21 days for delivery

AUDIO AND TEST EQUIPMENT CENTRE

RETAIL MAIL ORDER EXPORT

ALL PRICES INCLUDE VAT

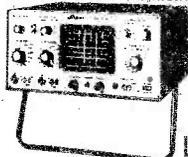Telephone your order with Access and Barclaycards or send cheque with order.



LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm

SCOPES — (UK P/P £1.50 ea.)

3" 5MHz single beam	102.00
4" 5MHz single beam	125.00
5" 10MHz single beam	170.00
Super 6 6MHz single beam	166.00
Super 10 10MHz dual trace	239.00
14D15 Scope x 15MHz dual trace	325.00
4D25 Scope x 25MHz dual trace	414.00
PROBES x 1 x 10 14.50, x 10 9.95 x 1 7.95. For Super-6/10/4D25	
SINCLAIR 10MHz Miniscope	159.85

FREQUENCY COUNTERS

MAX 50 50MHz 6 digit pocket counter	61.00
MAX 100 100MHz 8 digit portable counter	88.75
MAX 550 550MHz 6 digit pocket counter	106.00
500 MHz Prescaler for max. 50 or max. 100	40.00
PFM200 Sinclair 200MHz Pocket Counter 8 digit	53.00
OPT07000 8 digit, 800MHz Portable 1Hz RES with N/CADS	139.95

DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit LED	52.95
PDM25 Sinclair Pocket 4 1/2 digit LED	71.90
DM350 New Sinclair 3 1/2 digit with 10 amp range	74.45
DM450 New Sinclair 4 1/2 digit with 10 amp range	106.45
(30kV Probes 19.99, Mains adaptors 4.00, DM carrycase 8.95)	
M1200 Bench Portable 2 1/2 digit LED Resolution 1µA/0.1mv/0.01mm	67.50
935 Data Precision 3 1/2 digit hand-held LCD 2 amp AC/DC	118.85
198. Low cost 3 1/2 digit general purpose LCD	52.95

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1/T1.2/T1.2/TM3A (TM3 AC volts only), some with AC current, etc.

TM11 Incredible 120 Range Electronic Multi-meter	158.00
TM38 AC Micro voltmeter 3MHz >4 Megohm	161.75
TM3A	139.50
360TR 100k/volt 23 Range (plus transistor checker), Large scale	29.95
PROE 20k/volt 26 Range Large scale	29.95
70E1 50k/volt 36 Range Multi-meter	22.95
TMK50K 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)	22.95
530R 20k/volt 52 Range Pocket Multi-meter	36.75
7200 20k/volt 22 Range Double Multi-meter	17.95
5100K 20k/volt 25 Range Pocket Multi-meter	19.10
RE132m/171-2 20k/volt 16 Range Popular Multi-meter	11.95
LT22 20k/volt 19 Range Pocket Multi-meter	14.50
LT101 1k/volt 12 Range Pocket Multi-meter	6.95
RE142m 20k/volt 17 Range Multi-meter	13.50
RE152m 20k/volt 19 Range Multi-meter plus transistor check	18.95
AT205 50k/volt 21 Range Multi-meter	26.95
TR202 20k/volt 23 Ranges / Transistor Checker / Checker/Continuity Checker	19.95

AVO 3a and a large range of replacement tests leads in stock

GENERAL EQUIPMENT

SE250 Signal Injector	6.15
TE7 Signal Tracer AF/RF	9.95
SWR50 SWR/Power Meter	19.50
LP30 50MHz Low Pass Filter	4.95
CX3A 150 watt 3 way AE Switch	7.50
DC25KV 100 Meg HV Probe	11.95
PNS10 38 Value Resis. Box	3.95
RP124 0/25V 0/1 Amp P-S Stabilised Single Meter	62.00
RP230M 0/30V 0/1 Amp P-S Twin Meters	85.00
TR1000 Transistor checker in/out circuit	11.95
GGD63 Signal injector	3.95
LR1 Transistor/Diode Checker	21.50
3101 Clamps Meter 0/1k Ohm 0/150/300/600 AC Volts 0/300 amp	35.95
SWR6 SWR & FS Meter	10.50
SWR10 SWR Meter	12.50
MS319 2x100 Watt Audio Watt Meter	13.95
*500V Megohmmeter 500 Megohms	51.00
*2 1/2 Amp Variable Transformer	21.95

GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges	
TG152D	86.25
TG152Dm (with meter)	107.50
TG200 Series RC Oscillators Sine/Square output. 1Hz-1MHz 12 Ranges	
TG200D	113.95
TG200Dm (with meter)	139.50
TG200Dmp (meter & line control)	145.90
4001 Digital Pulse Generator 0.5Hz-5MHz	105.00
2001 Function Generator-Sine/Square/Triangle/TTL	86.00
SG2500 (RF) 6 bands 250kHz-300MHz	49.95
AG761 (Audio) sine 19Hz-220Hz square 134Hz-100kHz	61.00
ARF300 (RF-Audio) 18Hz-200MHz	78.50

PROTO BOARD IN STOCK
KITS PR 6 9.20, PR 100 11.80.
SEPARATES EXP300 5.75, EXP600 5.30, Q778 1.30, EXP48 2.30.

LOGIC PROBES AND MONITORS

LT2000 Economy Probe. 10MHz	11.95
LM1 Monitor	33.00
LP1 Probe 10MHz	35.50
LP2 1.5MHz	20.50
16 pin IC test clip	1.95


PIEZO HORN TWEETERS

Up to 100 watts each. No x-over reqd. Only	4.95 ea.
Rared Horns	6.50
Midrange Flared Horns	9.95
(P-F Z0p per 1 or 2, 30p per 3 to 5)	

DRILLS AND DRILL KITS

9 and 12 volt Operated. 1/4" max.	
SMALL DRILL with collets	6.85
MEDIUM DRILL with 3 collets	9.90
SMALL DRILL with 20 drills, etc.	16.85
SMALL DRILL with 6 P/C drills	12.55
MEDIUM DRILL with 20 drills, etc.	16.95
MAINS Eliminators	9.95
VARIABLE Speed	13.95
12 volt 1/4" Heavy Duty Drill	12.50

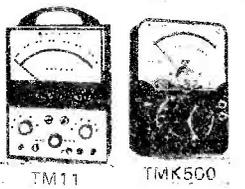TV SOUND
High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. 8.50 (UK P&P 50p). As reviewed by 'Popular Hi-Fi', July '79




SPECIAL OFFER
GEO 10+10 watt Tuner/Amplifier. MW/LW/SW/Stereo FM. Supplied as two easy to connect units. £24.95 P&P £1

WE SELL
Kef, Seas, Audax, Fane, Goodmans, Motorola, Passives
Speakers/Kits, etc.
Also Irons, Tools, etc.

FREE CATALOGUE
SEND STAMPED (12" x 10" U.K.)
ADDRESSED ENVELOPE (MIN 9" x 5")
FOR YOUR COPY NOW

CALL IN AND SEE FOR YOURSELF
PRICES CORRECT AT 8/10/79
AUDIO ELECTRONICS
301 EDGWARE RD., LONDON W2 1BN
01-724-3564. OPEN 9-6, MON-SAT.
ALSO AT 248 TOTTENHAM COURT ROAD, W 1

— CLEF KITS —

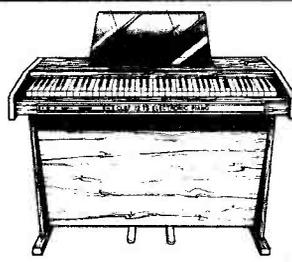

SUB-KITS
Reduce the cash outlay during the building process — details in the lists.

KEYBOARDS
We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

- 49 NOTE C-C £23.80
 - 73 NOTE F-F £37.00
 - 88 NOTE A-C £45.00
- All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

NEW KITS
This space reserved for December release of Electronic Rotor! (See us at BREADBOARD '79).

BUILDING SERVICE
We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists.

DEMONSTRATION CASSETTES
Please specify Ensemble or Piano at £1.50 each for ten minute content. Cost may be deducted from subsequent orders.

INFORMATION
Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & Insurance.

VISITS
Are welcome by appointment, otherwise Mail Order Only.

EXPERT
Enquiries welcome — in Australia please contact JAYCAR (Sydney).

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS
Six and 7 1/2 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use, from our top quality Component kits.

SIX OCTAVES — £184
7 1/2 OCTAVES — £209

P.E. STRING ENSEMBLE
The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT — £164
Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.

P.A.'s — SPEAKERS — CABINETS

Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

GLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)
16 Mayfield Road, Bramhall, Cheshire SK7 1JU. 061 439 3297

The latest from the U.S.A. Pinball Wizard

Featured in last issue as a project

Contains everything except case and controls	HOME TV GAME BROUGHT TO YOU AS B/W KIT	Play at home on your own TV Sound from TV Play 7 games with 4 options on each game
	Basic Kit	4-Pinball games 2-Basket games 1-Breakout game Limited edition Order now, save disappointment
Mains adaptor	£3.90	
	£28.90 Inc.	

NEW! Versatile car alarm kit. Can be used for car, caravan, boat etc. See review in November Hobby Electronics. Build it yourself for only **£18.90** very complete kit.

27MHz MONITOR £18.70
CB CAR AERIALS (GUTTER MOUNTING) £13.90

LOOK!
SPECIAL OFFER. Limited quantity **MARKSMAN** electronic game. Consists of a Pistol and an Owl target. Shoot the owl dead centre and it responds with flashing eyes and a chirping noise.
Sells in shops for £10-£14
Now Only **£5.90**

SPACE ALERT ONLY £15.90 EACH
AUTO RACE

FOOTBALL VERSION £21.50

CHESSE CHAMPION **NEW PRICE!**
6-Level Chess Computer.
New Low Price £54.95, with adaptor.
STAR CHESSE colour TV Game. A space age Chess game.
£60.10 Our Price **£63.35**, with adaptor.
ELECTRONIC MASTERMIND Play nine games against the computer. 3, 4 or 5 digits. ~~£15.00~~ Now **£12.90**.
CHROMA-CHIME 24-tune door chimes. **KIT £10.50. BUILT £15.95.**

LOOK!!!
5-pin DIN to 4 x 3.5mm JACK PLUGS. Leads can be used for Audio by replacing Jack Plugs with Phono plugs or use it with your computer by changing DIN plug to Phono plugs. **ONLY £1.25.**

N.I.C
27 Sidney Road, London N22 4LT
01-889 9736
S.A.E. with all enquiries please
Please allow up to 21 days for delivery

BUY nascom-2 NOW AND GET A FREE 16K RAM BOARD

The lack of availability of the MK4118 RAMs has seriously delayed the launch of the Nascom 2, so we have decided to relaunch the product with an offer few will be able to refuse.

The Nascom 2 will be supplied without the optional user 4118s. Instead, we will supply a 16K dynamic RAM board and the interconnect for the NASBUS – absolutely FREE. This board allows further expansion to 32K. Also, when the 4118s become available, customers taking advantage of this offer can have the 8K for just £80 (plus VAT).

Meanwhile, the empty sockets on the Nascom 2 can be filled with 2708 EPROMs allowing dedicated usage, now with 1.6, or 32K of extra RAM. All the other features of the Nascom 2 are available and these include:

MICROPROCESSOR

Z80A 8 bit CPU which will run at 4MHz but is selectable between 2/4 MHz.

HARDWARE

12" x 8" PCB through hole plated, masked and screen printed. All bus lines are fully buffered on-board. PSU: +12v, +5v, -12v, -5v.

MEMORY

- 2K Monitor-NAS SYS 1 (2K ROM)
- 1K Workspace/User RAM
- 1K Video RAM
- 8K Microsoft BASIC (MK 36000 ROM)

INTERFACES

New 57-key Licon solid state keyboard
Monitor/domestic TV

On-board UART provides serial handling for Kansas City cassette interface (300/1200 baud) or the RS232/20mA teletype interface.

Totally uncommitted PIO giving 16 programmable I/O lines.

The Nascom 2 makes extensive use of ROMs for on-board decoding. This reduces the chip count and allows easy changes for specialised industrial use of the board. On-board link options allow reset control to be reassigned to an address other than zero.

The 1K video RAM drives a 2K ROM character generator providing the standard ASCII characters with additions – 128 characters in all. There is also a socket for an optional graphics ROM on-board.

NASCOM DISTRIBUTORS

Henrys Radio (London W2)	Camera Centre (Barrow-in-Furness)
Microdig (Liverpool)	Strathand (Glasgow)
Interface Components (Amersham)	Byte Shop/Computerland Group
Comp Components (New Barnet)	Adda Computers (Ealing)
Electrovalue (Egham & Manchester)	Electronic Services (Sheffield)
Lock Distribution (Manchester)	Business & Leisure Microcomputers (Kenilworth)
Eley Electronics (Leicester)	A & G Knight (Aberdeen)
Target Electronics (Bristol)	P & O Computers (Belfast)
CC Electronics (Torquay)	



£295 PLUS VAT

TO NASCOM MICROCOMPUTERS LTD
92 BROAD STREET
CHESHAM
BUCKS

Tel: 02405 75155 Nascom Microcomputers
NM/ET/1

Please send me..... Nascom 2 kits
(complete with construction article and
extensive software manual for the monitor and
BASIC) at £295 plus VAT plus £1.50 p&p.
And 3A PSUs at £29.50 plus VAT
plus £1.00 p&p. And optional
graphics ROMs at £15.00 plus VAT.

NAME _____

ADDRESS _____

ACCESS/
BARCLAYCARD NO _____



NewBear Books



INTRODUCTION TO MICROCOMPUTING

Volume 0 The Beginners Book	A. Osbourne	£ 5.95
Volume I Basic Concepts	A. Osbourne	£ 5.95
Volume II Some Real Products	A. Osbourne	£18.95
Volume III Some Real Support Devices	A. Osbourne	£11.95
Understanding Microcomputer & Small Computer Systems	Scelbi	£ 7.56
An Introduction to Personal & Business Computing	R. Zaks	£ 5.75
Getting Acquainted with Micros		£ 7.95
Getting Involved with your Own Computer, A guide for Beginners		£ 4.75
The First Book of Microcomputers	Moody	£ 3.60
A Consumers Guide to Personal Computing and Microcomputers		£ 5.65
Peanut Butter & Jelly Guide to Micro's		£ 6.20

BASIC BOOKS

Introduction to Basic	J. B. Morton	£ 6.50
Beginning Basic	P. E. Gosling	£ 2.95
Introduction to Basic	P. J. Hartley	£ 1.95
Some Common Basic Programmes Illustrated Basic	A. Osbourne	£ 6.45
Learning Basic Fast	Alcock	£ 2.25
Microcomputer Basic	De Rossi	£ 6.30
The Basic Workshop	K. Schoman Jnr.	£ 4.50
Discovering Basic (a problem solving approach)	R. E. Smith	£ 4.90
The User's Guide to North Star Basic	R. Rogers	£10.00
Basic with Business Applications	Hayden	£ 5.56
Basic and the Personal Computer	Dwyer & Critchfield	£10.36
A Guided Tour of Computer Programming in Basic	Dwyer/Kaurman	£ 4.16
Basic Basic. (An Introduction to Computer Programming in Basic Language)	J. S. Coan	£ 5.00
Advanced Basic. Applications & Problems	J. S. Coan	£ 5.50

PASCAL

Pascal: User Manual & Report	Springer-Verlag	£ 5.52
Problem. Solving Using Pascal	Springer-Verlag	£ 7.84
Programming in Pascal	P. Grogono	£ 7.50
A Practical Introduction to Pascal	A. Addyman	£ 3.50
An Introduction to Programming & Problem Solving with Pascal	Schneider	£ 9.50

SC/MP

Guide to SC/MP Programming		£ 3.75
SC/PM Assembly Language Programming Manual		£ 6.45
A Guide to Kitbug. KEMITRON		£ 0.95

COBOL

Cobol Programming	Nickerson	£ 6.95
Learning Cobol Fast	De Rossi	£ 6.20
Cobol with Style	Hayden	£ 4.20

6800 BOOKS

6800 Programming for Logic Design	A. Osbourne	£ 5.95
6800 Assembly Language Programming	A. Osbourne	£ 6.95
Using the 6800 Microprocessor		£ 5.65
77-68 6800 Microprocessor Design Manual		£ 7.50
6800 Software Gourmet Guide Cook Book	Scelbi	£ 7.95
Practical Microcomputer Programming (6800)	Weller	£17.56
The 6800 Microprocessor		£ 3.60
6800 Applications Manual	Motorola	£10.50
Programming the 6800 Micro	Southern	£ 8.00

Z80 BOOKS

Z80 Programming for Logic Design	A. Osbourne	£ 5.95
Z80 Technical Manual	Zilog	£ 4.00
Z80 PIO Technical Manual	Zilog	£ 2.75
Z80 Programming Manual	Zilog	£ 4.50

Z80 Microcomputer Handbook	W. Barden	£ 6.95
Practical Microcomputer Programming (Z80)	Weller	£23.96

8080 BOOKS

An 8080 Interpretive Debugger		£ 3.96
Practical Microcomputer Programming (8080)	Weller	£17.56
8080A Bugbook	Larson	£ 6.95
8080A/8085 Assembly Language Programming		£ 6.95
8080 Programming for Logic Design	A. Osbourne	£ 5.95
8080 Software Gourmet Guide Cook Book	Scelbi	£ 7.95
8080/8085 Software Design	(Titus)	£ 7.50
8080 Machine Language Programming for Beginners		£ 5.10
An Editor/Assembler for 8080/8085		£11.50

6502

The Best of Micro 6502 Journal		£ 5.99
6502 Applications Handbook	Zaks	£ 8.95
First Book of Kim		£ 7.00
6500 Hardware Manual		£ 7.50
6500 Programming Manual		£ 7.50
Programming the 6502 SYBEX	Zaks	£ 7.95
Programming a Micro. 6502	Caxton Foster	£ 7.95

FORTRAN

Elementary Computer Programming Fortran IV	Boguslausky	£ 6.30
--	-------------	--------

GAMES

32 Basic Programs for the PET COMPUTER		£ 9.95
101 Basic Computer Games		£ 5.50
Games, Trick & Puzzles for a Hand Calculator	W. Judd	£ 2.49
Games with a Pocket Calculator		£ 1.75
Star Ship Simulation		£ 5.10
Game Playing with Basic		£ 4.10
Game Playing with Computers	D. Spencer	£10.20
Game Playing with Basic		£ 4.20
SARGON-A Chess Computer Program in Z80 Assembly Language		£ 9.50
Chess & Computers	D. Levy	£ 7.16
Chess Skill in Man & Machine	P. Frey	£11.84

COOKBOOKS

Active Filter Cookbook	Lancaster	£10.45
CMOS Cookbook	Lancaster	£ 6.95
OP-AMP IC Cookbook	Jung	£ 9.50
IC Timer Cookbook	Jung	£ 7.50
TTL Cookbook	Lancaster	£ 6.95
T.V. Typewriter Cookbook	Lancaster	£ 7.50
Cheap Video Cookbook	Lancaster	£ 5.10

PRACTICAL APPLICATION AND DATA BOOK

Memory Databook by National Semiconductor		£ 3.10
CMOS Databook by National Semiconductor		£ 3.10
TTL Databook by National Semiconductor		£ 3.10
Data Acquisition Handbook		£ 2.50
WB-1 A TTL Microcomputer Design Manual		£ 6.50
Fundamentals of Digital Computers	D. Spencer	£ 7.50
National Semiconductors Interface Circuits Data Book		£ 3.10
G.I. Data Catalogue		£ 3.50
Semiconductor Circuit Design Vol. 1		£ 6.30
Semiconductor Circuit Design Vol. 2		£ 6.50
Semiconductor Circuit Design Vol. 3		£ 6.50
Semiconductor Circuit Design Vol. 4		£ 6.50
Semiconductor Circuit Design Vol. 5		£ 6.50
Digital Troubleshooting	R. Gasperini	£ 7.00

INSTANT DESPATCH SERVICE**
SEND FOR FULL BOOKLIST.

Official orders (min. £10). Barclaycard and Access welcome.
 All book prices include First Class post and packing.

NEWBEAR MAIL-ORDER: 40 Bartholomew Street, Newbury, Berks. Tel: 0635 30505
NORTHERN SHOWROOM: 220-222 Stockport Road, Cheadle Heath, Stockport Tel: 061 491 2290

CHESS MACHINES SURVEY

With the Christmas of the chess computer rapidly approaching, Ian Graham has been mating his way through the electronic playmates.

Well, not much mating actually. I did manage to mate with a couple of the computerised companions on their lowest level.

As my chess isn't up to comparing the programs these machines use, I decided to play them off against one another. On their lowest level, the games were evenly matched. There were lots of stalemates. The Voice Chess Challenger managed to win all but one of its games. So, once, and once only, I heard the Voice Chess Challenger announce 'I lose'.

Perhaps more differences would have shown up at higher levels of play. However (and it's a big however), if all the games were playing at a ten minute

response time and if one assumes 25 moves each for black and white in each game, the E.T.I chess computer league would have taken over three weeks of button-pushing, 24 hours a day, to play. No thank you.

Whether you're looking for a portable or desk top game, one complete with board or complete without one, or even a game that talks to you, there's one in our survey.

At the end of the survey you'll find a table bringing together the chess games, their suppliers, prices and their most important features. Prices are changing so often that, if you're thinking of buying a system, give a few of the suppliers a ring to confirm the latest prices.

BORIS

Boris is probably the most infuriating of the computer opponents. **It comments on your game.** After considering your next move at length and finally plucking up enough courage to actually move the piece, you sit back with a smug grin on your face. Then the machine responds with 'RUBBISH', flashing on its display. It's enough to shake anyone's confidence in his game.

One welcome feature on both Boris and the Boris Diplomat is an easy way of checking where the pieces are on the board. There's nothing worse than manoeuvring into position to take the computer's Queen to find that it wasn't where you thought it was anyway. All the playmates will allow you to check the state of the board. Usually they assign a numerical value to each piece. The display shows the position of each square and the value of the piece on it. The two Boris's go one better. They display the square location and a stylised outline of the piece on it. The outlines are difficult to decipher at first, but soon become familiar.

A card board (a cardboard what? — No, a chess board made from card) is supplied with Boris, but I think it's totally unnecessary. If you can afford the £165 or so for Boris you're likely to have enough pennies left over for a decent board, if you haven't got one already.


Unlike the other games, which have a series of levels of play to choose from, Boris has a built-in 100 hour timer. The longer a response time you set on the timer, the longer Boris has to think about his/it's next move and the higher the level at which it plays.

Boris can be set to play either white or black. If you don't

like the situation you've played yourself into, you can change sides and make Boris take over your pieces.

You don't have to start every game from the beginning. Any problem or advanced stage of play can be set up on the board and entered rank by rank into Boris's memory. If Boris's response to one of your moves is rather disturbing, you can go back to where you were and try a different move.

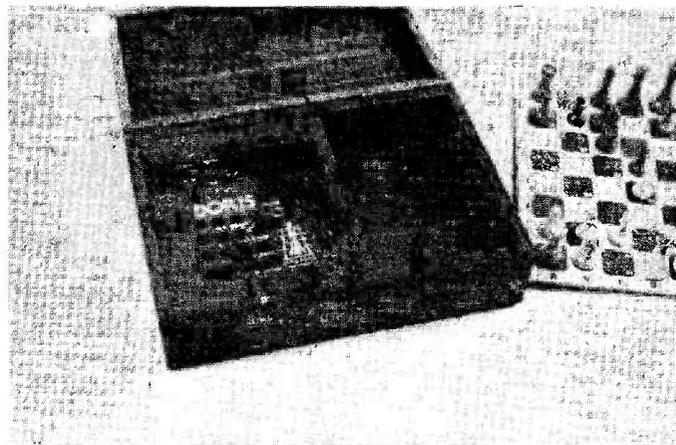As you can see, Boris comes in an attractive walnut case, with a compartment for the pieces and mains adaptor. ►




BORIS DIPLOMAT

My first impressions of the Boris Diplomat were less than favourable. I found that the flickering LED display was set at an awkward viewing angle. The keyboard, although large and clearly laid out, was unsatisfactory in use. It was absolutely rigid and, in the absence of sound effects, I had to glance at the display after each key pressing to ensure that the move had, in fact, been successfully entered. The chess board itself is even smaller than the keyboard and the pieces almost microscopic.


Having got all that off my chest, let me now say that I think Boris Diplomat is the perfect travelling chess computer. It's completely self-contained. You could quite happily sit on the BA shuttle to Glasgow or the 8.20 from Staines to Waterloo (the sardine special) with Boris Diplomat on your knee flashing it's gems at you.

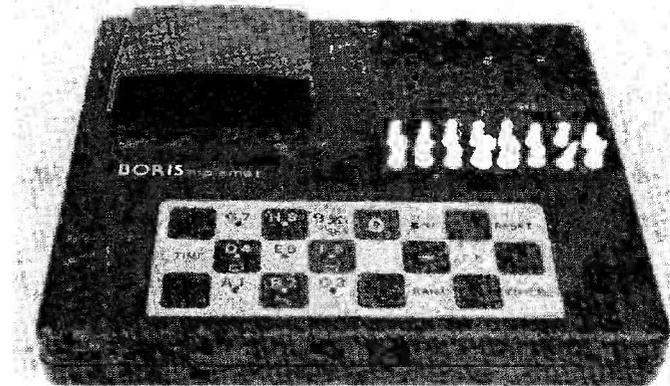The Diplomat shares the features of its big brother Boris. It doesn't have a series of levels. Instead it has an internal timer which can be set to give a response time of up to 100



hours. The longer you give the Diplomat to think, the higher the level of its play.

COMMODORE CHESSMATE

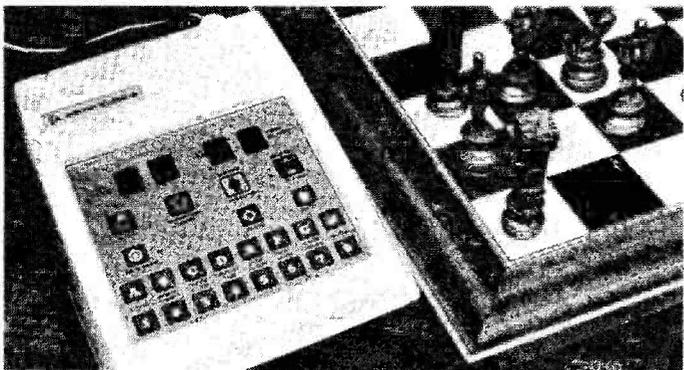

Commodore's Chessmate is another newcomer to the market. This computerised mate didn't stir any great feelings either for or against it, on the whole. Although it employs the same control method as Chess Champion (separate keys/touch pads for the letter and number of each square location) I didn't find it at all awkward to use. On pressing each touch pad, a trill of tones signals

successful pressing. Another trill accompanies the appearance of Chessmate's response on the display.

My only criticism is that there is no on/off switch for the sound effects. They *do* become a little irritating after a couple of games. The control panel is well laid out and more colourful than most.

There are eight levels of play *and* internal black and white 60 minute timers. Unlike all the other systems, which automatically reset to level one at the beginning of each new game, Chessmate resets to level 4 — its average level.


Chessmate copes quite happily with castling and en passant but it trusts you to observe the correct rules of castling. It will also check where the pieces are on the board, assigning a numerical value to each piece for identification. An illegal move is answered by a pair of flashing question marks on the display.

The computer companion's memory stores 32 familiar chess openings — from the Bishop's game to the Nimzo-Indian defence. It chooses one of these at random and tries to follow it for 16 moves, after which it has to think for itself.

CHESS MATE


Not to be confused with Commodore's Chessmate, this Chess Mate isn't on the market yet. It's a battery (rechargeable)/mains game complete with fold out board. It will play at ten levels with average response times of from eight seconds to a day and a half. As with all the other games in our survey you can set up any problem on the board, so you don't have to start every game at the beginning.

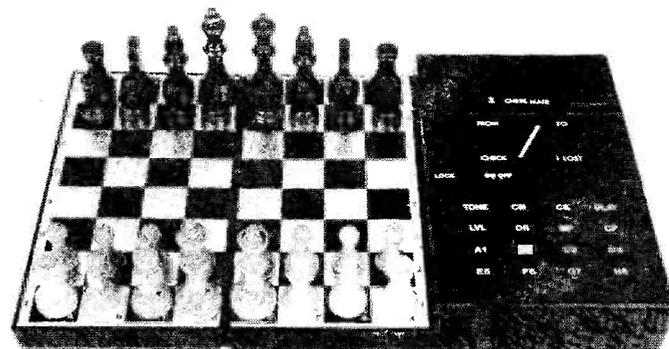The prototype I saw had one minor disadvantage. The board folds away very neatly to make a compact portable game. No, that's not the disadvantage. Unlike the Boris Diplomat which is self-contained with its set of on-board pieces, this game has no provision for carrying pieces. So, you have to carry around a little bag of pieces separately. However, there may be enough space in the folding board



to accommodate them when the game finally appears on the market.

CHESS CHAMPION

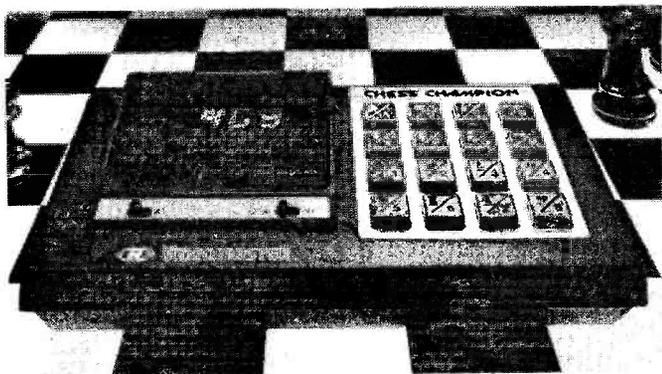

You have to supply your own board when you play against the Champion. The good news is that the Champ's price has come down recently. (Wonder if it's anything to do with the competition from the new Commodore Chessmate?) It has six levels of play — from an instant

response beginners level to the marathon 2-day computing time level (for correspondence chess).

As chess computers go, the Champion is a simple animal. It will only play black. Special moves need special treatment. The execution of the en passant move is a little puzzling. To take the Champion's black pawn en passant, you enter your white pawn's diagonal move. Now, you have to remove the black pawn from the board as seen by C.C., so you have to enter what appears to be an illegal sideways move to erase the C.C.'s pawn from its memory. Castling? The Champ castles at the first opportunity.

You may have noticed that Chess Champion has more keys than most of its brethren. Whereas one key usually serves for both the letter and number of a square's location eg C3, Chess Champion has a separate key for each. In my humble opinion, as a fully paid up member of the button-pusher's union, the Champ would be a much more attractive proposition if it incorporated dual-function buttons or touch pads, perhaps with a button-press sound effect.

CHESS CHALLENGERS


This latest addition to the Chess Challenger range is a bit special. It talks to you. It not only repeats every move, it tells you which piece it's moving and, if it's taking something, which piece it's taking. If you're stuck for a move, the Voice C.C. will even whisper a few suggestions in your shell-like. If you're a bit slow off the mark, the machine will remind you that you really ought to get a move on. It's no slow-coach itself, with response times of about half those of its predecessors.

There are nine levels of play plus an H level. If you select H, the chatty Challenger goes on thinking about its next move until you tell it to stop. Checking the position of pieces on the board is simplicity itself. Each time you press the PV key, the computer-generated voice tells you which piece is on each square and whose piece it is. Positions are also shown on the display. Like Chess Challenger 10, the Voice C.C. comes with magnetic pieces. However, the usual Challenger touch keypad for a pushbutton pad with a click action.

For all the Micro-men (and women) in Readerland, the Voice Challenger uses 96K of ROM for program and operational stages, 32K bits of ROM for voice generation and 8K bits of RAM for scratch pad and intermediate storage. The heart of the clever bits is a Z80-A, 8-bit CPU. The unit is preprogrammed with 48 standard opening moves which it will select either randomly or under your command.

This is by far the most expensive chess computer on sale now, but it *does* have the most powerful program yet to appear on the market. If you're a serious club player, and a wealthy one at that, the Voice Chess Challenger is the most competent opponent (non-human, that is) you can face today.

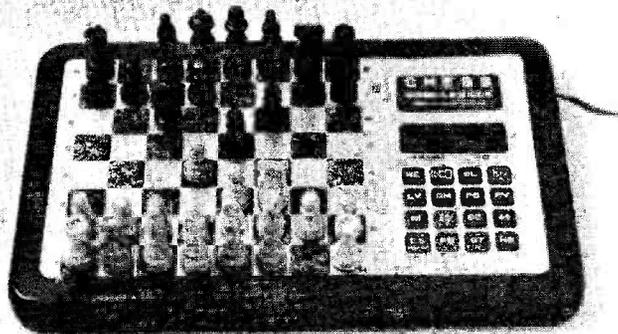I hoped this Challenger would make full use of its voice and show a little character by blowing a raspberry when it won, but it just said "check and mate", like a well programmed American dalek.



Chess Challenger 10 is a ten level opponent in an attractive package with an integral board and magnetic pieces. The calculator-style touch pad has a positive click action *and* sound effects. The manufacturers — Fidelity Electronics of Miami — have included a sound off switch. Whilst sound effects are useful to indicate successful key pressing, they can get rather monotonous and irritating after a while. The challenger 10 has one big advantage over its star successor, the voice box — it's around £80 cheaper — but its chess program is not as powerful or as fast.

Chess Challenger 7 was the first of the Challenger series to retail at under £100 and the last to appear before the Challenger acquired the power of speech.

It incorporates all the features of its predecessors plus a few extras. It will play against you (naturally), but it will also play against itself (if you're into spectator chess). You can change sides in mid-game and see how the Challenger gets out of the mess you got into. Not surprisingly, it looks very like its predecessor, the Challenger 10. ▶

ATARI CHESS CARTRIDGE

If you're buying a programmable TV games centre, or if Santa Claus is bringing you one, you've probably got your eyes on the Atari Video Computer Systems. It's an expensive way of playing chess — over £200, including £45 just for the chess cartridge.


I thought it would be unfair to test the chess cartridge only. To give the system a fair and complete trial I decided to try out all the games cartridges I could get my hands on. There were air-sea battles, space wars, golf, basketball, breakout and many more cartridges. About a month later I thought I was sufficiently familiar with the system to try the chess cartridge. My eyes resumed their by now customary square shape as the board appeared on the screen.

My first criticism is that the board could be much larger. It sits in the middle of the screen with a large unused border round it. The pieces are controlled by a joystick with a push button. When the cursor is moved onto a piece, the piece is 'picked up' by pushing the button, then moved with the joystick and finally 'released' by pushing the button again. This sort of control method always seems at first to be a bit of a long-winded business, but soon becomes second nature. You have to decide for yourself whether it will interfere with your game.

There are eight levels of play. I assumed that level one was the simplest and level eight the most difficult. Silly me.

Level eight is the simplest followed by levels one to seven.

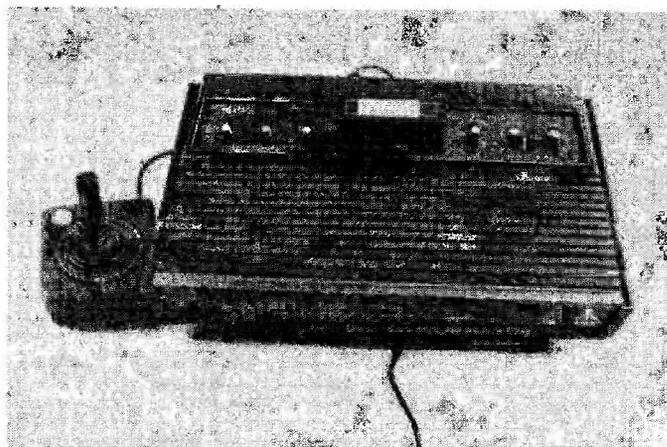The Atari Videocomputer system and chess cartridge are available from Videotime Products, who can supply the full range of games cartridges. The cartridges are mostly £14.95 each. The exceptions are chess at £45 and backgammon at £34.50.



	SUPPLIERS AND PRICES					GAME FEATURES				
	K	AJD	NIC	CGL	V	POWER	LEVELS	INTEGRAL BOARD	CONTROLS	SOUND
BORIS	169.95	187.50	•	•	•	M	T	NO	PB	NO
BORIS DIPLOMAT	94.50	94.77	•	•	•	M/B	T	YES	TP	NO
CHESS CHALLENGER 7	98.50	99.65	99.95	99.95	•	M	7	YES	TP	NO
CHESS CHALLENGER 10	155.25	159.50	169.95	169.95	•	M	10	YES	TP	NO
VOICE CHESS CHALLENGER	229.95	245.00	249.95	249.95	•	M	10	YES	PB	YES/S
CHESS CHAMPION	•	54.50	54.95	•	•	M	6	NO	PB	NO
COMMODORE CHESSMATE	59.95	•	59.95	•	•	M	8	NO	TP	YES
CHESS MATE	95.00	•	•	•	•	M/B	10	YES	PB	YES/S
ATARI CHESS CARTRIDGE	45.00	•	•	•	45.00	M	8	YES	JB	YES

Power: M — mains
B — battery

Levels: T — internal timer

Sound: YES/S — sound effect may be switched off.

Controls: PB — push buttons
TP — touch pads
JP — joystick and push-button

NIC — N.I.C. Models
27 Sidney Road
London N22 4LT
Tel: 01-889 9736

AJD — AJD Direct Supplies Ltd
102 Bellegrave Road
Welling
Kent DA16 3QD
Tel: 01-303 9145

CGL — Computer Games Ltd
Spectrum House
48 Cambridge Road
Barking
Essex
Tel: 01-591 5654

V — Videotime Products
56 Queens Road
Basingstoke
Hants RG12 1REA
Tel: (0256) 56417
(0256) 26620

K — Kramer & Co
9 October Place
Holders Hill Road
London NW4 1EJ
Tel: 01-203 2473
(mail order only)

The list of suppliers is by no means exhaustive. Many of the High Street hi-fi stores will have a chess machine or two in the window. Prices vary a lot, so it's worth shopping around, especially with Christmas coming up and some prices coming down. STOP PRESS — Latest prices from Mountaineers: Commodore Chessmate — £58.00, Boris — £155.25, Boris Diplomat — £90.00, Challenger 10 — £155.25, Challenger 7 — £88.00, Voice Challenger — £230.00.

ETI

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safefloc

Minimum & Sub Miniature Milli-amps	Ref. Price	P&P
3-0-3	200 238	2.25 .60
3-0-3.6	1A 1A	212 2.65 .65
3-0-9	100	13 1.95 .60
3-0-9	330 330	235 1.80 .60
3-8-9 0-8-9	500 500	207 2.40 .65
3-8-9 0-8-9	1A 1A	208 3.50 .65
3-15 0-15	200 200	236 1.80 .60
3-20 0-20	300 300	214 2.40 .80
20-12-0-12-20	700(DC)	221 3.15 .80
0-15-20 0-15-20 1A 1A		206 4.25 .95
0-15-27 0-15-27 500 500		203 3.70 .80
0-15-27 0-15-27 1A 1A		204 5.75 .95

50 VOLT (Pri: 220-240V) Sec: 0-19-25-33-40-50V			
Amps	Ref. No.	Price	P&P
0.5	102	3.25	.80
1.0	103	4.25	.95
2.0	104	6.95	1.10
3.0	105	8.25	1.10
4.0	106	10.50	1.20
6.0	107	14.75	1.40
8.0	118	19.85	1.60
10.0	119	23.75	2.10

60 VOLT (Pri: 220-240V) Sec: 0-24-30-40-48-60			
Amps	Ref. No.	Price	P&P
0.5	124	3.50	.80
1.0	126	5.25	.95
2.0	127	7.20	1.10
3.0	125	10.75	1.20
4.0	123	12.00	1.40
5.0	40	13.80	1.50
6.0	120	17.25	1.50

AUTO TRANSFORMERS Input/Output Tapped 0-115-210-240V			
VA (Watts)	Ref. No.	Price	P&P
20	113	2.30	.80
75	64	3.75	.80
150	4	5.25	.95

Input/Output Tapped 0-115-210-220-240V			
Amps	Ref. No.	Price	P&P
300	53	8.85	1.10
500	67	10.50	1.40
1000	84	18.25	1.50

Also: 1500/2000/3000VA

MAINS ISOLATING (Centre Tapped & Screened)

Pri: 120/240V Sec: 120/240V			
VA (Watts)	Ref. No.	Price	P&P
60	149	6.25	.95
100	150	7.25	1.20
200	151	10.75	1.20
250	152	12.95	1.40
350	153	15.95	1.50
1000	156	36.75	3.10

12 AND/OR 24 VOLT Pri: 220-240 Volts			
Amps	Ref. No.	Price	P&P
12V	24V		
0.5	0.25	1.11	1.95 .65
1.0	0.5	213	2.40 .80
2	1	71	2.90 .80
4	2	18	3.70 .80
6	3	70	5.25 .85
8	4	108	7.10 1.10
10	5	72	7.90 1.10
12	6	116	8.50 1.10
16	8	17	10.50 1.20
20	10	115	13.50 1.40
30	15	187	16.50 1.40
60	30	226	33.00 1.70

30 VOLT (Pri: 220-240V) Sec: 0-12-15-20-24-30V			
Amps	Ref. No.	Price	P&P
0.5	112	2.50	.80
1.0	79	3.25	.80
2.0	3	5.25	.95
3.0	20	5.95	1.10
4.0	21	6.25	1.10
5.0	51	9.25	1.10
6.0	117	10.75	1.10
8.0	88	14.00	1.40
10.0	89	16.25	1.40

Please add VAT at 15%
Barclaycard and Access facilities
available
Trade and Education Welcome

BAYDIS

7a William Street,
Herne Bay, Kent
Herne Bay 64586

Master Electronics

The practical way

No maths needed~
No dull theory~

Step by step we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- 1) BUILD AN OSCILLOSCOPE
- 2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS
- 3) CARRY OUT OVER £) EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK

Also

- We provide practical tuition for:-
- 3) Digital Electronics
 - 1) Radio amateurs licence.
 - 4) Computer Technology
 - 2) City and Guilds certificates.
 - 5) Test instrument kits

Mark your interest(s) with an x in box provided.

British National Radio & Electronics School,
P.O. Box 156, Jersey, Channel Islands


NAME _____ ETOI. 12

ADDRESS _____ (block caps please).

GREENWELD

443A Millbrook Road Southampton SO1 0HX

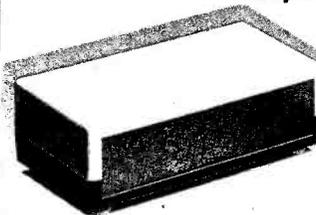ALL PRICES INCLUDE VAT @ 15% - JUST ADD 30p POST



THE AMAZING GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

1A 400V RECTIFIERS

Plastic, like 1N4004, type 388F these diodes have preformed leads for horizontal mntg (15mm FC). Supersave price - 100 for £2.30; 500/£10; 1000/£18.

1000 RESISTORS £2.50!!

New stock just arrived - Carbon Film 2% & 5%, 1/4 & 1/2w, all brand new, but have pre-formed leads, ideal for PC mntg. Enormous range of popular mixed values for just £2.50/1000; £11/5000; £50/25,000.

POWER DARLINGTON PAIR

Plastic power (TOP66 case) transistors type 80695A/BD696A. Just look at the spec!! 70W 8A 45V - Hfe 750 @ 4A!! Special low price - £1.20 per pair.

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock i/p; fully TTL compatible; low power dissipation. Supplied with data £2.75.

BUZZERS & MOTORS

Z401 Powerful 6V DC, all metal construction. 50mm dia x 20mm 70p.
Z402 Miniature type, 3-9V, only 22-15x16mm. Very neat 65p.
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only £1.
Z451 12V high torque motor 30mm dia x 40mm high, with 10mm spindle, 65p.
Z452 6V DC motor with gearbox giving final shaft speed 700 rpm. Spindle is threaded OBA. Ex-equip £1.
Z453 As above but 300 rpm and unthreaded spindle £1.
A372 Audible Warning device - solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied £1.50.

VU METERS

Voo2 Twin type, 2 metres 40x40mm and driver board, supplied with circuit and connection data, £3.50.
Voo3 New type, just in. Twin type moulded in one piece, 80x40mm (no driver board but suitable circuit supplied) £2.50.

LINEAR IC BARGAIN

We have just received a large consignment of popular linear IC's that have failed the manufacturer's stringent tests. However, on checking through a few hundred we have found that quite a large proportion tested in a simple oscillator circuit are functional, so are offering them in packs as follows:

Type	Package	% Good	Qty	Price
702	14DIL	65	25	£1.20
709	8DIL	75	20	£1.20
709	14DIL	50	30	£1.20
710	T099	30	40	£1.20
710	14DIL	30	40	£1.20
720	14DIL	80	20	£1.20
741	T099	40	25	£1.20
748	T099	70	15	£1.20

Connection data is supplied. One of each pack, £8.50.

VEROCASE SALE!!

Four popular sizes of Verocase at drastically reduced prices - these were part of their standard range (75-1411 etc) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No	Size	Price
21050	205x140x75mm	£2.70
21051	180x120x65mm	£2.20
21052	154x85x60mm	£1.70
21053	125x65x40mm	£1.40

DIL SOCKETS

Low profile by TI at lowest ever prices!

Pin	Price	Pin	Price
1-99	100-499	500+	
8 pin	.095	.075	.065
14 pin	.105	.085	.075
16 pin	.12	.095	.085
18 pin	.155	.125	.10
20 pin	.19	.15	.12
22 pin	.21	.17	.14
24 pin	.24	.19	.15
28 pin	.26	.21	.16
40 pin	.32	.26	.21

BULK BARGAINS

All new full spec devices. Prices per 100 inc VAT (orders not accepted for less than 100 of one type at these low prices!!)

AD161/2PR	£48	BF255	£8
BC107	£7	BF394	£4
BC108	£6	BF450	£7
BC109	£7	BF451	£5
BC114	£6	BFY17	£12
BC117	£5	BFY50	£14
BC125	£5	BFY51	£14
BC147	£5	BFY52	£14
BC148	£5	BSY95A	£10
BC149	£5	BU205	£65
BC159	£5	BU206	£65
BC172C	£5	2N1132	£12
BC182B	£4.50	2N2369	£12
1k	£35	2N2894	£12
10k	£310	2N2926Y	£5
BC183B	£5	2N3268	£5
BC184L	£5	2N3053	£13
BC212	£5	2N3054	£13
BC213L	£5	2N3055	£34
BC237	£5	2N3442	£100
BC238B	£5	2N3583	£34
BC252	£7	2N3618	£78
BC308B	£6	2N3702	to £5
BC230	£7	2N3708	
BC238	£8	2N4401	£5
BC337	£8	2N4403	£6
BC348	£5	2N5401	£19
BC351	£14		
BC557A	£5		
BCX33	£5	DIODES	
BD131	£19	1N4001	£3.50
BD132	£20	1k	£28
BD181	£50	1N4004	£4.50
BD184	£60	1k	£39
BD246	£25	1N4006	£5.50
BD525	£25	1k	£46
BD526	£25	1N4148	£2.30
BD173	£13	1k	£17
BF181	£17		
BF195	£5	ICs	
BF197	£5	741 8dil	£13.50
BF198	£5	555	£21.75
BF241	£5	723 14dil	£32
		723 T099	£30

Resistors - 1/4W 5% carbon film, these values only: 220R, 470R, 1k, 3k9, 4k7, 33k, 47k, 220k, 18R. All at £4 per 1,000 (min qty of one value) or £35 per 10,000 any mix.

SCR PANEL & REED PANELS

Z525 Contains 11 800mA 60V 2N5061 SCRs, 11 6V8 zeners, 11 1N4004 diodes plus Rs, Cs, etc. Only £1.
Z526 10 24V reed relays, 22 1N4004, 10 Weird lcs, Rs, Cs, etc. 60p
Z527 2x6V reed relays, 6x2S030 or 2S230, 6x400V reeds, plus Rs.


Only 50p

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current: 0-150 mA. Resistance: 0-100.000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE


£6.95

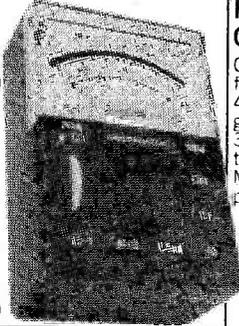

6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 ms gate time. Accuracy is 3 ppm at 25°C or less then ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Reg. 9V battery. 22-351. REG. PRICE


£79.95

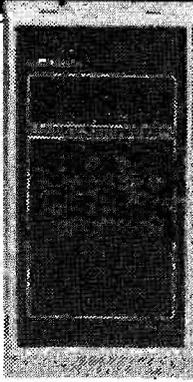

MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301k-1 megaohm. 0-100-1k-101C-100K-3 megaohms. Reg. 9V battery. 22-209.


REG. PRICE
£29.95

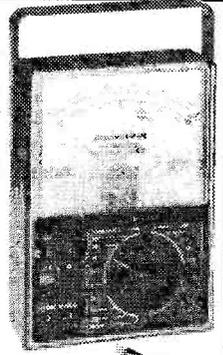

TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE **£9.95**

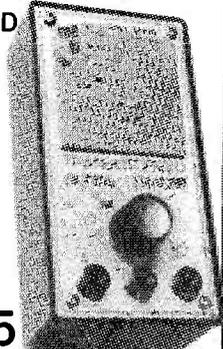

DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE **£19.95**



SIGNAL INJECTOR


For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**

AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.


REG. PRICE **£1.99**

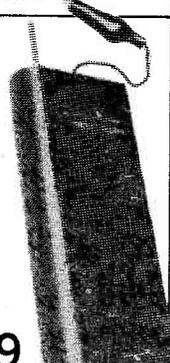

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.


REG. PRICE **£229.95**

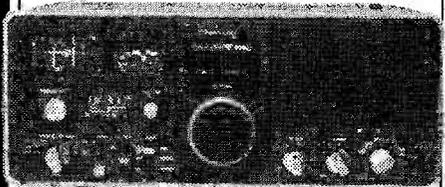

DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.


REG. PRICE
£9.95

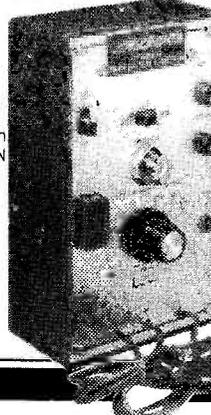

VARIABLE POWER SUPPLY

Power project boards, IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**

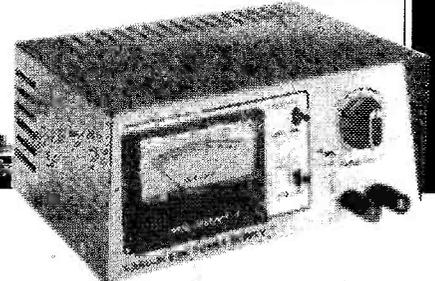

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.


KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80.

TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

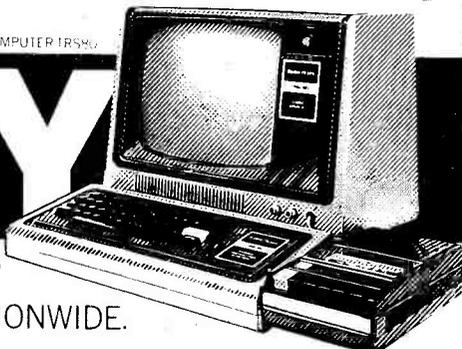OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.

Amesbury, Banbury, Basingstoke, Bournemouth, Bristol, Cardiff, Chester, Exeter, Glasgow, Harrogate, Ipswich, London, Luton, Manchester, Milton Keynes, Newcastle, Nottingham, Oxford, Peterborough, Reading, Southampton, Stevenage, Telford, Torquay, Wakefield, Walsley, Warrington, Wolverhampton.


Prices may vary at individual stores.

NOISE GENERATOR

An inexpensive unit that produces white noise digitally and can be used as the basis of a special sound effects system.

White noise can be simply described as a signal containing a full spectrum of quite randomly generated frequencies or tones, all with randomly determined amplitudes, but which have equal mean power when averaged over a reasonable unit of time. The basic sound of white noise resembles that of hissing steam, but this sound can be greatly modified, to give a variety of special sound effects (such as wind, waves, surf, jet roar, etc), by passing it through low-pass or narrow-band filters.

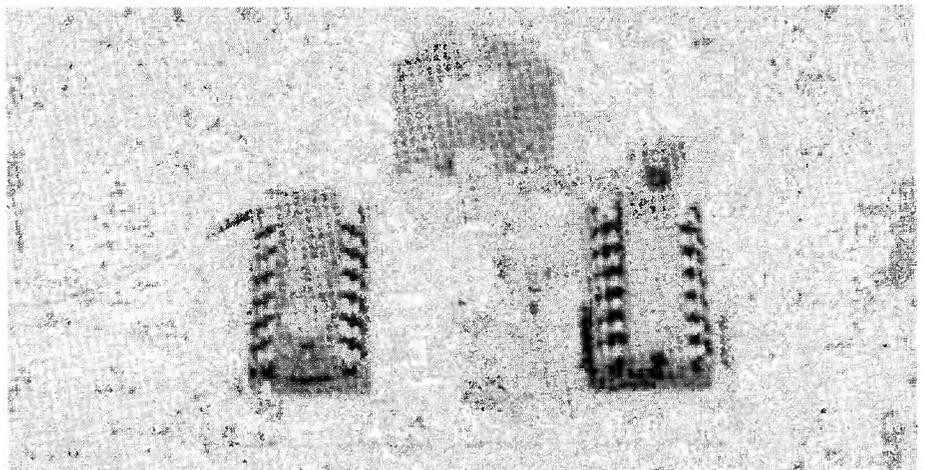Most of the white noise generator circuits that have been published in the electronics press in recent years have been analogue designs. They have taken the relatively low-level white noise outputs of selected 'leaky' Zener diodes or of special (and expensive) 'noise' diodes and then amplified these signals to a level suitable for general use. A major problem with these circuits has been that they



have given highly unpredictable end results, with circuits of identical designs giving outputs that range from non-existent to excellent.

Our new ETI design is a digital unit, and does not suffer from the deficiencies of the earlier analogue circuits. Its output is produced via a clock generator and a pseudo- or apparently-random shift register. The

output has all of the basic characteristics of a conventional white noise signal, but in reality has a pre-programmed pattern that is faithfully reproduced in all units that are built from the design. The amplitude of the output signal is inherently large, and required no further amplification before being fed to external filter networks.


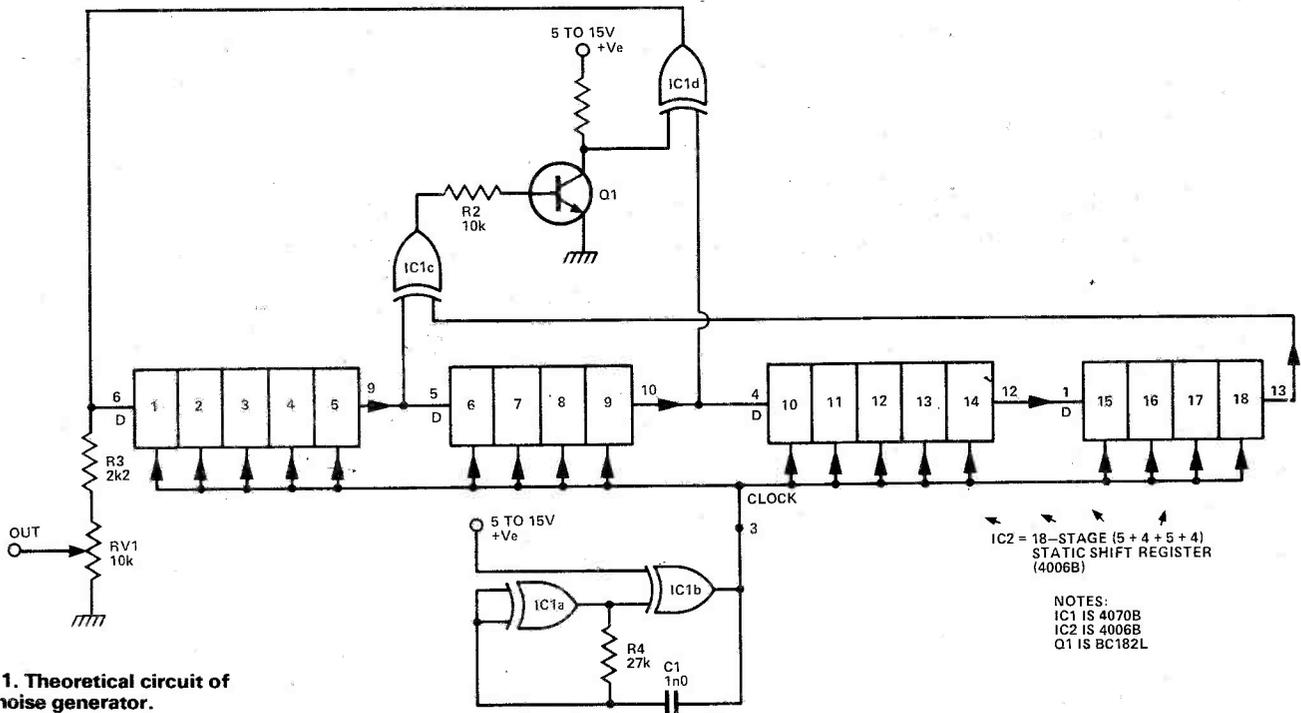


Fig. 1. Theoretical circuit of the noise generator.

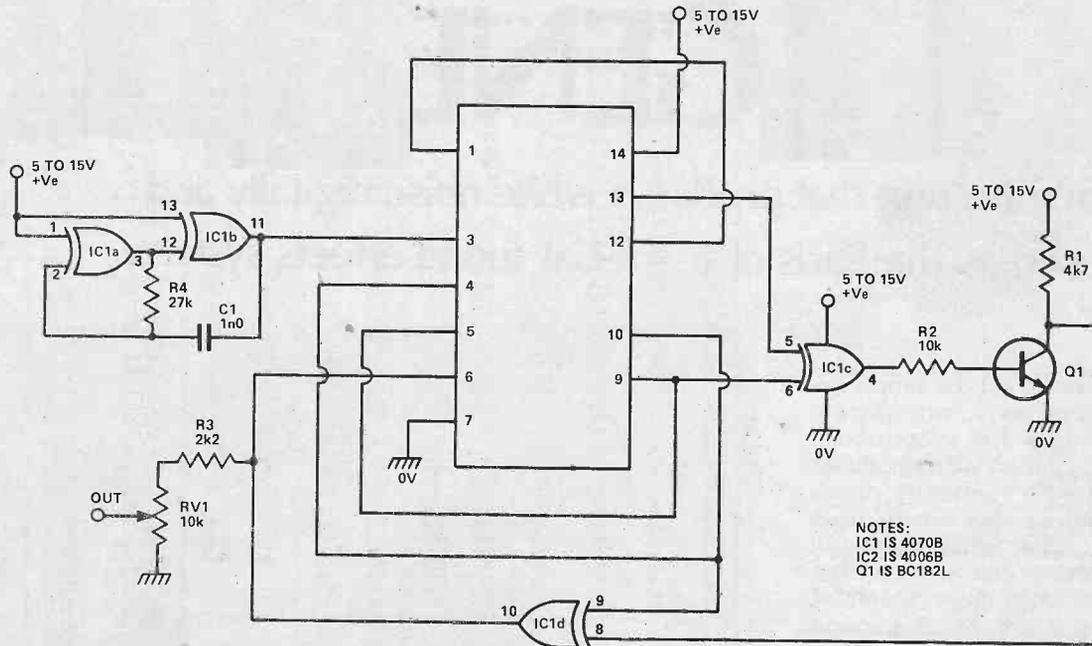

NOTES:
IC1 IS 4070B
IC2 IS 4006B
Q1 IS BC182L

Fig. 2. Practical circuit of the noise generator.

Construction

The circuit uses only two IC's, one transistor, and half a dozen passive components, so construction is simplicity itself. As the ICs are CMOS devices, they should be handled with due care, and preferably should be mounted on the PCB via suitable

sockets or via Soldercon pins. When construction is complete, check the performance by connecting a crystal earpiece or microphone across the output terminals, and switch on. If all is well, the unit will produce a hissing noise like escaping steam.

ETI

BUYLINES

No problems here. All components are standard parts, available from most mail-order suppliers advertising in this issue.

HOW IT WORKS

The theoretical circuit of the generator is shown in Figure 1, and a more practical representation is shown in Fig 2. IC2 is an 18-stage (3 + 4 + 5 + 4) static shift register, in which the logic (0 or 1) information on the Data terminal is fed forward one step on the arrival of each new pulse from the IC1a-IC1b 30 kHz clock generator. IC1c and IC1d are Exclusive-OR gates, and are used in conjunction with inverter-connected Q1 to feed various outputs of IC2 back to the Data terminal in such a way that the data feeds through the register in an APPARENTLY random or jumbled fashion.

In reality a complex sequence of 0's and 1's flows through the register, repeating once every few seconds and producing an apparently random jumble of fundamental frequencies. Since these fundamental frequencies are produced digitally, however, they each produce a vast number of harmonics which, when subsequently (externally) filtered, produce a signal that appears to vary randomly in both frequency and amplitude and thus to have all the basic characteristics of white noise.

PARTS LIST

RESISTORS All 1/4W, 5%		CAPACITOR	
R1	4k7	C1	1n0 polystyrene
R2	10k		
R3	2k2		
R4	27k		
POTENTIOMETER		SEMICONDUCTORS	
RV1	10k	IC1	4070B
		IC2	4006B
		Q1	BC182L

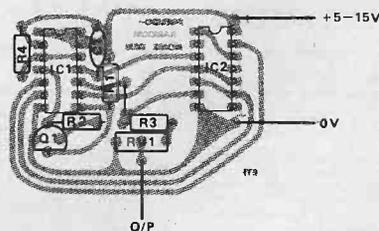



Fig. 3. Component overlay.

Greenbank

Greenbank Electronics
(Dept T12E) 92 New Chester Road, New Ferry
Wirral, Merseyside L32 5AG
(Tel. 051-645 3391)

TERMS, VAT, CWO. Cheques ext payable to Greenbank Electronics. Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 30p (+5p VAT = 35p) per order. Export: NO VAT but add 30p (Eire), 75p (Europe) and £2.50 elsewhere.
(Phys. universities, govt. depts. etc. can telephone their orders for immediate despatch on account.)

PROMBOX 12

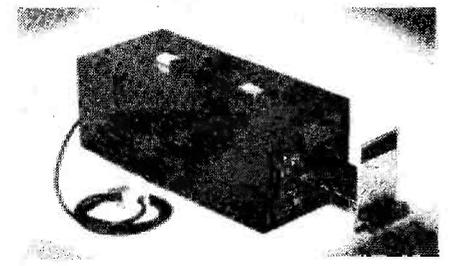

An easy to use unit designed for both the professional and amateur UV-prom eraser

- Features**
- Can erase up to 12 proms
 - Special short wave ultraviolet tube
 - Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life)
 - Sliding tray carries proms on conductive foam
 - Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open
 - "Mains On" and "Tube On" indicators
 - Smart textured case with carrying handle and feet
 - Complete instructions supplied

Supplied complete with mains plug and two metres of flex

£63.63

COMPUTER BOARDS

The following is an extract from our leaflet ref. 'MP4', which is available free on request (a 9" x 6" SAE helps, but is not essential). See Microprocessor section to the right for board prices.

For many people the wide choice of micro-processors now available presents a difficult choice. To understand any particular microprocessor in depth a development system is almost essential. However in the past to understand more than one several separate development systems have had to be purchased.

The reason that separate systems, one for each processor, have been necessary is due to the fact that individual microprocessors have their own individual features: in one case to access memory a separate read strobe and write strobe is required. In another a 'read/write' line is used in combination with a combined strobe called 'valid memory address and phi-2'. With some processors, the same address bus can be used for both memory and 'input/output ports', under the control of a 'memory request' or an 'input/output request' control line.

Naturally, if a development system takes advantage of any of the particular unique features of any particular microprocessor, this makes it more difficult to graft some other unrelated microprocessor onto the same bus at a later date. A Universal Micro System provides a basic bus structure on which any one micro-processor can be connected. The system uses a CPU (Central Processor Unit) card which is separate from the rest of the system, and this allows the same memory and interfaces to be retained when a different MPU is used.

The basic system bus consists of data and address buses together with read and write strobes. By locating the data input (Keyboard) and output (VDU) in the memory space then such chips as the 8080/8085 family, which normally use input/output ports, can now be used without any fundamental change to the bus (and as a bonus, users of these MPU's have all the ports entirely free for their own purposes).

The range of p.c.b.'s includes boards to implement a memory-mapped VDU, cassette interface, keyboard interface, PROM programmer, and a number of RAM and ROM cards. All the cards are of International Size 114 x 203 mm (4 1/2" x 8") except for the larger power PSU a power supply card. This latter card is sized so that it can be bolted to the side of a standard 4" chassis module which is then compatible with the other cards. The cards have a standard 43-way edge connector, with one position used for polarisation.

We do not propose to defend the (relatively) small number of bus connections (42) against such standards as the 'S100' 100-pin bus. The S-100 bus, as originated in America, is bigger and better. It is also more expensive. In the same way, a Ford 'Granada' is bigger and better than a Ford 'Corina', but it doesn't mean a Corina isn't good value for money, who knows - it may even be better value!

The International Size card is the recommended size for most '3U' 19" rack systems. These racks, as made by Vero, Crichtley, etc., and a variety of modules and blank cards are obtainable to aid individuals in customising their own system. (A convenient trade source of suitable hardware is the firm 'R.S. Components', but we would be happy to supply in case of difficulty.)

It is appropriate to mention that this range of cards is not meant to compete with any of the excellent computer kits which can be obtained. The purchase of these types of kits simply acts as an unpaid (or at least underpaid) assembly worker. If the standard components are put together correctly the computer works, if they're not it doesn't. In the end each and every one is virtually identical.

The range of boards in the Universal Micro System are entirely different. You choose your microprocessor, memory, interfaces, etc., what addresses will be used, you choose whether or not to use our software, somebody else's, or indeed your own. Don't be too alarmed if your level of experience does not permit you to take this sort of decision with confidence - we are always here to offer guidance if asked, we'll even tell you if the system is unsuitable for your needs, in the unlikely event that it is.

As mentioned on the last page, a brave attempt has been made to begin the design of a Universal Micro System, to provide a sufficiently flexible arrangement to permit the system to grow over the years, and not to become obsolete overnight. To permit this flexibility, wherever possible 'patch areas' have been provided on the boards. A 'patch area' is an undedicated dual-in-line pattern which can accommodate an extra integrated circuit for your own use. Often these can be used to add some extra memory, or some extra address decoding. An extra supply voltage can be developed using an integrated circuit regulator, or gates can be added to allow separate 'Memory Request' and 'Input/Output Request' control lines on a memory card which does not already have this facility.

Of course we know that there are many people who would faint clean away at the thought of cutting printed circuit tracks, adding extra integrated circuits and bits of wire in the way described above, but it is not for these people that this sort of system has been designed. We would like to think of this system as a basis on which you can build your own personal design, perhaps as an alternative to the use of 'Veroboard' or etching your own p.c.b.'s. (Further sections give an outline of each card in turn. Although we have in mind all sorts of exotic future developments (e.g. high resolution graphics, floppy disc controllers, dynamic high-density RAM cards, programmable VDU front panels, colour displays, light pens, sound generators etc.) we prefer to keep quiet about them until they actually exist. All of the cards described actually exist, and at the time of writing (September 1979) none are in stock. (We plan it so they are all in stock, but people will insist on buying them, without caring what havoc they wreak in our stock control!)

CMOS

These cut prices for Amateur Users and Export. Note: Industrial users - quantity prices available. Mostly Motorola, RCA

4000	15p	4042	75p	4089	£1.50	4119	£2.68	4631	£1.45
4001	17p	4043	94p	4093	£3.50	4122	£5.00	4632	£1.27
4002	17p	4044	90p	4094	£1.90	4131	TBA	4634	£5.13
4006	£1.05	4045	£1.45	4095	£1.05	4132	£4.36	4636	£3.69
4007	18p	4046	£1.28	4096	£1.05	4135	£3.73	4637	£1.23
4008	87p	4047	87p	4097	£3.72	4140L	£1.38	4638	£1.25
4009	50p	4048	58p	4098	£1.10	4150	£2.67	4639	91p
4010	50p	4049	48p	4099	£1.45	4151	£2.67	4641	£1.14
4011	18p	4050	48p	4096I	N/S	4152	TBA	4643	£1.59
4012	18p	4051	72p	40100	£2.50	4161	£2.18	4648	£3.69
4013	42p	4052	72p	40101	£1.60	4162	£2.42	4652	£1.59
4014	86p	4053	72p	40102	£2.12	4164	£4.00P	4654	£3.87
4015	99p	4054	72p	40103	£2.12	4165	£4.00P	4654	£1.19
4016	99p	4055	£1.28	40104	£1.09	4500	£6.95	4556	78p
4017	85p	4056	£1.34	40105	£1.06	4501	17p	4557	£3.86
4018	85p	4057	£25.70	40106	61p	4502	91p	4558	£1.14
4019	48p	4058	£4.80	40107	68p	4503	69p	4559	£3.89
4020	99p	4059	£1.15	40108	£5.36	4504	£5.71	4559	£1.64
4021	91p	4060	£1.15	40109	£5.57	4506	51p	4560	£1.89
4022	99p	4061	£10.00	40110	£3.39	4507	55p	4561	65p
4023	20p	4063	£1.09	40182	£1.40	4508	£2.48	4562	£5.33
4024	65p	4064	N/S	40192	£1.40	4510	99p	4566	£1.59
4025	19p	4065	N/S	40193	£1.40	4511	£1.38	4568	£2.38
4026	£1.80	4066	57p	40194	£1.18	4512	81p	4569	£2.57
4027	45p	4067	£3.80	40257	£1.48	4515	£2.68	4580	£5.74
4028	81p	4068	22p	4160	£1.08	4516	£1.08	4581	£2.62
4029	99p	4069	20p	4161	£1.08	4517	£1.08	4582	98p
4030	58p	4070	23p	4162	£1.06	4518	£1.02	4583	75p
4031	£2.05	4071	21p	4163	£1.08	4518	£1.02	4583	43p
4032	£1.00	4072	21p	4174	£1.08	4519	51p	4585	£1.20
4033	£1.45	4073	21p	4175	99p	4520	£2.08	4585	£1.20
4034	£1.96	4075	23p	4194	£1.08	4521	£1.88	4595	£1.20
4035	£1.11	4076	85p	4408	£6.59	4522	£1.06	4597	£2.32
4036	£2.45	4077	23p	4409	£5.59	4524	N/S	4598	£2.65
4037	£1.00	4078	21p	4410	£6.73	4526	£1.08	4599	£6.95
4038	£1.08	4081	20p	4411	£9.58	4527	£1.52	4600	99p
4039	£2.45	4082	21p	4412P	£9.43	4528	£1.14	4700	£1.75
4040	£1.05	4085	74p	4415V	£7.50	4530	85p		
4041	80p	4086	75p	4415V	N/S	4530	85p		

74C

74C00	24p	74C03	£1.29	74C164	£1.04	74C305	£7.26	74C926	£4.84
74C02	24p	74C05	£1.29	74C165	£1.04	74C309	94p	74C927	£4.84
74C03	24p	74C06	£4.38	74C170	90p	74C312	54p	74C928	£4.84
74C04	24p	74C08	85p	74C175	90p	74C319	£1.63	74C948	TBA
74C08	24p	74C09	85p	74C192	110	74C310	£6.78	74C954	54p
74C10	24p	74C09	£1.04	74C193	110	74C311	£7.13	74C956	61p
74C14	£1.41	74C107	£1.22	74C195	£1.04	74C312	£7.13	74C957	54p
74C20	24p	74C150	£4.12	74C200	£6.78	74C314	£1.41	74C958	61p
74C24	24p	74C151	£2.46	74C201	£1.06	74C315	£1.10	74C959	£4.13
74C32	24p	74C154	£3.67	74C203	£1.06	74C317	£1.83	74C959	£1.83
74C42	82p	74C157	£2.20	74C204	£1.73	74C321	£1.83	74C960	£1.83
74C48	£1.38	74C160	£1.10	74C201	54p	74C322	£3.66		
74C73	54p	74C161	£1.10	74C202	54p	74C323	£3.73		
74C74	54p	74C162	£1.10	74C203	54p	74C324	TBA		
74C76	54p	74C163	£1.10	74C204	54p	74C325	£4.84		

MODULATORS

UM111:	£36 UHF Ch.36 Vision Modulator	£2.50
UM123:	1UH Ch.36 Vision Modulator with baseband (for computers etc)	£4.70
UM123:	FM Sound Sub-carrier Modulator	£2.50

NEW SWITCH MODE PSUs

AC 5221S	5V/10A, remote sense	£63.25
AC 8221S	5V/5A +12V/1A	£78.90
AC 9221S	as 8221 but also -5V/10A	£84.30

Typically 70% efficient. Oims. 4" x 8 1/2" x 2"

MICROPROCESSORS

COMPUTER BOARDS	8080 MPU	6502 MPU	CMOS
114 x 203 mm flip-chip, with gold plated edge connector.	6800 MPU	6802 MPU	6801 (128 x 8 RAM)
Bordered SC/MP CPU £7.95	6801 (128 x 8 RAM)	6802 (6821 PA)	6803 (128 x 8 RAM)
SC/MP Processor £5.95	6803 (6821 PA)	6804	6805A
Z80 CPU card £7.50	6804	6805	6806
Z80 VU 'set' £7.50	6805	6806	6807
VU 'B' £7.50	6806	6807	6808
VU 'G' (three) £7.50	6807	6808	6809
EPROM Programmer £7.95	6808	6809	6810
AK PROM board (£204s) £5.95	6809	6810	6811
AK PROM board (£270s) £5.95	6810	6811	6812
2K RAM board (2102s) £7.95	6811	6812	6813
2K RAM board (2102s) £7.95	6812	6813	6814
8K RAM board (2114s) 1K £7.95	6813	6814	6815
Keyboard Interface £7.50	6814	6815	6816
PSU 5v +12v, ±12v board £7.50	6815	6816	6817
PSU 5v, -12v board £4.95	6816	6817	6818

COMPUTER BOARDS	8080 MPU	6502 MPU	CMOS
114 x 203 mm flip-chip, with gold plated edge connector.	6800 MPU	6802 MPU	6801 (128 x 8 RAM)
Bordered SC/MP CPU £7.95	6801 (128 x 8 RAM)	6802 (6821 PA)	6803 (128 x 8 RAM)
SC/MP Processor £5.95	6803 (6821 PA)	6804	6805A
Z80 CPU card £7.50	6804	6805	6806
Z80 VU 'set' £7.50	6805	6806	6807
VU 'B' £7.50	6806	6807	6808
VU 'G' (three) £7.50	6807	6808	6809
EPROM Programmer £7.95	6808	6809	6810
AK PROM board (£204s) £5.95	6809	6810	6811
AK PROM board (£270s) £5.95	6810	6811	6812
2K RAM board (2102s) £7.95	6811	6812	6813
2K RAM board (2102s) £7.95	6812	6813	6814
8K RAM board (2114s) 1K £7.95	6813	6814	6815
Keyboard Interface £7.50	6814	6815	6816
PSU 5v +12v, ±12v board £7.50	6815	6816	6817
PSU 5v, -12v board £4.95	6816	6817	6818

74LS

74LS00	14p	74LS27	28p	74LS76	40p	74LS125	60p	74LS163	£1.18
74LS01	14p	74LS28	40p	74LS77	40p	74LS126	60p	74LS164	£1.14
74LS02	14p	74LS29	27p	74LS78	£1.15	74LS127	95p	74LS165	75p
74LS03	16p	74LS30	37p	74LS79	£1.18	74LS128	55p	74LS166	£2.26
74LS04	16p	74LS31	39p	74LS80	43p	74LS129	85p	74LS167	£2.88
74LS05	16p	74LS32	39p	74LS81	39p	74LS130	85p	74LS168	£1.09
74LS06	16p	74LS33	28p	74LS82	89p	74LS131	£1.06	74LS169	£1.06
74LS07	16p	74LS34	28p	74LS83	89p	74LS132	£1.06	74LS170	£1.06
74LS08	22p	74LS35	28p	74LS84	89p	74LS133	£1.06	74LS171	£1.06
74LS09	22p	74LS36	28p	74LS85	89p	74LS134	£1.06	74LS172	£1.06
74LS10	20p	74LS37	28p	74LS86	89p	74LS135	£1.06	74LS173	£1.06
74LS11	22p	74LS38	28p	74LS87	89p	74LS136	£1.06	74LS174	£1.06
74LS12	22p	74LS39	28p	74LS88	89p	74LS137	£1.06	74LS175	£1.06
74LS13	22p	74LS40	28p	74LS89	89p	74LS138	£1.06	74LS176	£1.06
74LS14	22p	74LS41	28p	74LS90	89p	74LS139	£1.06	74LS177	£1.06
74LS15	22p	74LS42	28p	74LS91	89p	74LS140	£1.06	74LS178	£1.06
74LS16	22p	74LS43	28p	74LS92	89p	74LS141	£1.06	74LS179	£1.06
74LS17	22p	74LS44	28p						

SERVICE TRADING CO

FT3 NEON FLASH TUBE

High intensity, multi-turn, high voltage, neon glow, discharge flash tube. Design for ignition timing etc. £1.50 P&P 25p (£2.01 inc. VAT). 3 for £3. P&P 50p (£4.03 inc. VAT & P).

WHY PAY MORE?!

MULTI RANGE METERS Type MF15A. AC/DC volts 10, 50, 250, 500, 1000, Ma 0-5, 0-10, 0-100. Sensitivity 2000V, 24 ranges, dimensions 133 x 93 x 46mm. Price £7.00 plus 50p P&P (£8.63 inc. VAT & P).



TRIAC.

Raytheon tag symmetrical Triac. Type Tag 250/500V, 10 amp 500 p.w. Glass passivated plastic triac. Swiss precision product for long term reliability. £1.25 P&P 10p (£1.55 inc. VAT & P) (inclusive of date and application sheet). Suitable Diac 22p.

0 to 60 MINUTES CLOCKWORK TIMER. Double pole 15 amp 230V AC. Contacts (no dial). £1.50. P&P 30p (£2.07 inc. VAT & P). N.M.S.

MERCURY SWITCH

Size 27m x 5mm, 10 for £5.00 P&P 30p, total including VAT £6.10. Min. quantity 10. N.M.S.


230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete with 5 blade 6 1/2" or 4 blade 3" aluminium fan. New reduced price £3.00 P&P 65p (£4.20 inc. VAT & P). N.M.S.



21-WAY SELECTOR SWITCH with reset coil

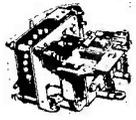The ingenious electro-mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil. 230/240V AC operation. Unit is mounted on strong chassis. Complete with cover. Price £5.50 P&P 75p (£7.19 inc. VAT & P). N.M.S.




A.E.G. CONTACTOR

Type LS6/L11. Coil 240V 50Hz. Contacts — 3 make: 600V : 20 amp, 1 break: 600V : 20 amp. Price: £5.50 + 50p P&P (£6.90 inc. VAT & P). N.M.S.

TORIN BLOWER

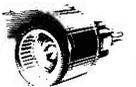220/240V AC Aperture 10x4 1/4cm overall size 16 x 14cm. Price £3.75 P&P 75p (incl. VAT £5.18). Other types available. SAE for details. N.M.S.



24V DC BLOWER UNIT

USA made 24V DC 0.8 amp blower that operates well on 12V 0.4 amp DC producing 30 cu ft min at normal air pressure. Maximum housing dia 110mm, depth inc motor 75mm, nozzle length 19mm, dia 22mm. Ideal for cooling mobile equipment, car, caravan, etc. £4.50 P&P 75p (£6.04 inc. VAT & P). N.M.S.

SMITH BLOWER.


Type FFB 1706. Small quiet smooth running, 240V, AC operation. Output aperture 45 x 40cm. Overall size 135 x 165cm. Flange mounting. Price £4.25 P&P 75p. (Total, £5.75 incl. P & VAT). N.M.S.

MINIATURE UNISELECTOR

12V 11 way 4 bank (3 non-bridging, 1 homing). £3.00 P&P 35p (£3.85 inc. VAT & P).

MICRO SWITCHES

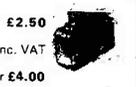
Sub min lever m/switch type MML46, 10 for £2.50 + VAT = £2.88 (£3.22 inc. VAT & P). Type 3 115M 906T 10 for £2.50 post paid (£2.88 inc. VAT & P).



BF lever operated 20A c/o, m. Unimax USA, 10 for £4.00 P&P 50p (min. order 10) (£5.18 inc. VAT & P). D.P. C/O lever m/switch, mfg. by Cherry Co. USA. Precious metal, low resistance contacts. 10 for £2.50, P&P 30p. Total inc. VAT £3.22 (min 10). N.M.S.

HEAVY DUTY SOLENOID

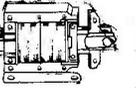Mfg. by Magnetic Devices. 240V AC. Intermittent operation. Approx. 20lb. pull at 1.25in. Ex. equip. Tested. Price £4.75 + 75p P&P (£6.33 inc. VAT & P). R & T.



PYE EYETHER 240V AC Solenoid. Approx 1lb pull. 1/4" travel, intermittent rating. Price £1.00 P&P 20p (£1.38 inc. VAT & P). N.M.S.

WESTOOL TYPE MMB MODEL 2 240V AC. Approx. 1 1/4 lb pull at 1/2 inch. Rating 1. Price £1.50 P&P 20p (£1.96 inc. VAT & P). N.M.S.

18-24V DC 0.7hm Coil Solenoid. Push or Pull. Adjustable travel to 3/16in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25mm. Price: 3 for £2.40 + 30p P&P (min. 3 off) (£3.10 inc. VAT & P).

240V AC SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet outlet. Precision made. British mfg. Price £3.50 Post 50p (£4.60 inc. VAT & P). N.M.S.



INSULATION TESTERS (NEW)

Test to IEE spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L 8in. W 4in. H 6in. weight 6lb. 500 VOLTS 500 megohms. £49.00 Post 80p (£57.27 inc. VAT & P) 1000 VOLTS 1000 megohms. £55.00 Post 80p (£64.17 inc. VAT & P)



SAE for leaflet.

YET ANOTHER OUTSTANDING OFFER New ILMFD 600V Duffiler wire ended capacitors, 10 for £1.50 P&P 50p (£2.30 inc. VAT & P). (Min 10). N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230V AC 50/60

OUTPUT VARIABLE 0/260V AC

BRAND NEW. All types.

200W (1 Amp) fitted A/C volt meter

0.5 KVA (Max. 2 1/2 Amp)	£17.50
1 KVA (Max. 5 Amp)	£22.50
2 KVA (Max. 10 Amp)	£37.00
3 KVA (Max. 15 Amp)	£45.50
5 KVA (Max. 25 Amp)	£74.00
10 KVA (Max. 50 Amp)	£168.00
17 KVA (Max. 75 Amp)	£260.00

Carriage and V.T extra

LT TRANSFORMERS

0-10V-15V at 3 amp (ex new equip) £2.50 P&P 50p (£3.45 inc. VAT)

13-0-13V at 1 amp £2.50 P&P 50p (£3.45 inc. VAT)

25-0-25V at 2 1/2 amp £4.50 P&P 75p (£6.04 inc. VAT & P)

0-4V/6V/24V/32V at 12 amp £18.50 P&P £1.90 (£23.46 inc. VAT & P)

0.6V/1.2V at 20 amp £14.70 P&P £1.50 (inc. VAT £18.63)

0-12V at 20 amp or 0-24V at 10 amp £12.00 P&P £1.50 (£15.53 inc. VAT & P)

0.6V/1.2V at 10 amp £8.25 P&P £1.25 (inc. VAT £10.93)

0.6V/1.2V/1.7V/1.8V/2.0V at 20 amp £19.00 P&P £1.50 (£23.58 inc. VAT & P)

0-10V/17V/18V at 10 amp £5.00 P&P £1.50 (inc. VAT £13.80)

JOB LOT: Primary 240V, Secondary 8V at 1.66 amp. Size 3 x 2 x 2in. Price £1.50 P&P 50p. (Total £2.30 incl. P & VAT). N.M.S.

Other types in stock, phone for enquiries or send SAE for leaflet.

POWER RHEOSTATS

New ceramic construction, vitreous enamel enameled winding, heavy duty brush assembly, continuously rated.

25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm £2.40 Post 20p (£2.99 inc. VAT & P). 50 WATT 250 ohm £2.90 Post 25p (£3.62 inc. VAT & P). 100 WATT 1/5/10/25/50/100/250/300/1500/1k/1.5k/2.5k/5k ohm. £5.90 Post 35p (£7.19 inc. VAT & P).

Black Silver Skirted Knob calibrated in Nos. 1-9, 1 1/2 in. dia brass bush. Ideal for above Rheostats. 28p ea.

SPECIAL OFFER

BERCO type L RHEOSTAT

85 ohm 300 watt 1.86 amp £7.50 P&P 50p (Total £9.20 inc. VAT). N.M.S.

BLOWER/VACUUM PUMP

3 phase AC motor, 220/250V or 380/440V, 1.425 rpm 1/4 hp cont. Direct coupled to William Allday Alcosa carbon vane blower/vacuum pump. 0.9 cfm 8 hp. Price £22.00 P&P £2.00 (£27.60 inc. VAT & P). N.M.S.

STROBE! STROBE! STROBE!

- ★ **HY-LIGHT STROBE KIT Mk. IV**
- ★ Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240V AC operation. Speed adjustable 1-20 fps.
- ★ Designed for large rooms, halls, etc. Light output greater than many (so called 4 Joule) strobes. Price £19.00 post £1.00 (£23 inc. VAT & P). Specially designed case and reflector for Hy-Light £8.80 Post £1.00 (£11.27 inc. VAT & P).
- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★
- ★ **ULTRA VIOLET BLACK LIGHT**
- ★ **FLUORESCENT TUBES**
- ★ 4ft 40 watt £8.70 (callers only £10 inc. VAT). 2ft 20 watt £6.20. Post 75p (£7.99 inc. VAT & P). (For use in stan bi-pin fittings). Mini 12in 8 watt £2.80. Post 35p (£3.62 inc. VAT & P). 9in 6 watt £2.25 Post 35p (£2.99 inc. VAT & P). 6in 4 watt £2.25 Post 35p (£2.99 inc. VAT & P).
- ★ Complete ballast unit for either 6", 9" or 12" tube 230V AC op. £3.50 plus P&P 45p (£4.54 inc. VAT & P). Also available for 12V DC op. £3.50 plus P&P 46p (£4.54 inc. VAT & P).
- ★ 400 watt uv lamp and ballast complete £31.50. Post £3 (£39.68 inc. VAT & P). 400 watt UV lamp only £11.25. Post £1.20 (£14.32 inc. VAT & P).
- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Price only £60.70 (£69.81 inc. VAT & P).

S.A.E. (Footscap) for further details. Post 75p



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (Footscap) for details

XENON FLASH GUN TUBES

Range of Xenon tubes available from stock. S.A.E. for full details.



RELAYS

230/240V AC Relays: Arrow. 2 c/o. 15 amp £1.50 (£1.96 inc. VAT & P). T.C.E. open type 3 c/o. 10 amp £1.10 (£1.50 inc. VAT & P).

DC Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.38 inc. VAT & P). Sealed 12V 2 c/o 7 amp octal base. £1.00 (£1.67 inc. VAT & P). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.78 inc. VAT & P). 24V. Sealed 12V 3 c/o 7 amp 11-pin £1.35 (£1.78 inc. VAT & P) (lamps = contact rating). P&P on any Relay 20p.

Other types available — phone for details. N.M.S.

Very special offer. 0-12V D.C., 2 make contacts, new ITT3 for £1.75 + 25p P&P inc. VAT £2.30.

Diamond H heavy duty AC relay 230/240V AC, two c/o contacts 25 amps at 250V AC £2.50 P&P 50p. (£3.45 inc. VAT & P&P) Special base 50p.

METERS (New) — 90mm DIAMETER

AC Amp., Type 62T2: 0-1A, 0-5A, 0-20A. AC Volt. 0-15V, 0-300V. DC Amp. Type 65C5: 0-2A, 0-10A, 0-20A, 0-50A DC Volt. 0-15V, 0-30V. All types £3.50 ea. + P&P 50p (£4.40 inc. VAT). 0-50A DC, 0-100A DC. Price £5.00 + 50p P&P (£6.33 inc. VAT).



GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

115 lb. ins., 110 volt, 50Hz, 2.8 amp, single phase, split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled. In-line gearbox. Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm. Length 115mm, ex-equipment tested £12.00 Post £1.50 (£15.53 inc. VAT & P). Suitable transformer 230/240 volt £8.00 Post 75p (£10.06 inc. VAT & P). R & T.



GEARED MOTORS

28 c.p.m. 20lb. inch 115V AC Reversible motor.


71 r.p.m. 10 lb. inch. 115V AC Reversible motor.

Both types similar to above drawing. Price either type £4.75 + 75p P&P (£6.33 inc. VAT & P&P)

Supplied with transformer for 240V AC operation £7.25 + P&P £1. (£9.49 inc. VAT & P&P). N.M.S.

FRACMO MOTOR

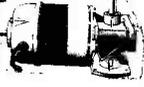58rpm 50lbs inch 240V AC reversible, 0.7 amp, shorplingth 35mm, dia. 16mm, weight 6 kilos 600 grams. Price £15.00 P&P £1.50 (£18.98). N.M.S.



FRACMO MOTOR

1400 rpm HP 1-30 continuously rated 115V AC fitted with anti-vibration cradle mounting. Supplied complete with transformer for 230-240V AC op. £10.00 P&P £1.00 (Total £12.65 inc. VAT). N.M.S.

PARVALUX MOTOR TYPE S.D.2

12V DC shunt 1/30th ph motor. Continuously rated 4,000 rpm. Price £10.00 P&P 75p (£12.36 inc. VAT & P). N.M.S.

PARVALUX 230/250V AC MOTOR

Type SD18 240V AC reversible 30 rpm 50lbs inch. Price £15.00 P&P £1.50 (£18.98 inc. VAT). N.M.S.



CITENCO

FHP motor type C 7333/15 220/240V AC 19 rpm reversible motor, torque 14.5 kg. Gear ratio 144:1. Brand new incl. capacitor, our price £14.25 + £1.25 P&P (£17.83 inc. VAT & P). N.M.S.



CROUZET — 230/240V AC 2 rpm synchronous geared motor £2.90 P&P 30p (Total £3.68 inc. VAT). N.M.S.

HAYDON — 230/240V AC 1 rpm synchronous geared motor £2.90 P&P 30p (Total £3.68 inc. VAT). N.M.S.

REVERSIBLE MOTOR 230V AC

General Electric 230V AC, 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 90mm. Spindle 5/16 dia. 20mm long. Ex-equipment tested £3.00. Post 50p (£4.03 inc. VAT & P).

BIG INCH

Tiny precision-built 3 rpm USA motor size only 1 x 1 1/2" 100V AC operation supplied with resistor for 230V AC. Price: £2.00 P&P 20p (£2.53 inc. P & VAT). 4 for £5.00 postpaid (£5.75 inc. VAT). N.M.S.

12V DC GEARED MOTOR

Precision built miniature motor, 6/12V DC operation. Incredibly powerful for size. Approx speed at 6V 60 rpm 40 ma Approx speed at 9V 80 rpm 50 ma Approx speed at 12V 120 rpm 60 ma Size 2.7mm dia. 38mm length, weight 55 gram. Drive spindle 5 mm x 2 mm dia. Price: £2.50 post paid (£2.88 inc. VAT).

REDUCTION DRIVE GEARBOX

Ratio 72:1. Input spindle 1/4 x 1/4 in. Output spindle 1/4 x 3in. long. Overall size approx: 120 x 98 x 68mm. All metal construction. Ex-equip. tested. Price: £2.00 + 50p P&P (£2.88 inc. VAT).

'VENNER TYPE' ERD TIME SWITCH

200/250V AC 30 amp. 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour spring reserve and day omitting device. Built to highest Electricity Board specification. Price £9.00 P&P 75p (£11.21). R & T.



SANGAMO WESTON TIME SWITCH

Type S251 200/250V AC 2 on 2 off every 24 hours. 20 amps contacts with override switch, diameter 4" x 3". price £8.00 P&P 50p (£8.78 inc. VAT & P). Also available with solar disk. R & T.

AEG TIMESWITCH

200/250V AC 1 on/1 off every 24 hours, 80 amp contact (ideal storage heaters). Spring reserve £10.00 P&P 50p (Total £12.08 inc. VAT). N.M.S.

AC MAINS TIMER UNIT

Based on an electric clock, with 25 amp single-pole switch, which can be preset for any period up to 12 hrs, ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p. (Total inc. VAT & Post £3.05). N.M.S.




2-CAM PROGRAMMER

Crouzet 1 rpm, 115V AC Motor operating 2 P&P 50p (£1.96 inc. VAT & P). Can be used on 240V AC with either C 25 250V 250W capacitor or 5 KΩ wirewound Resistor 7 watt (not supp) Price £2.50 + 50p P&P (£3.45 inc. VAT & P)

MINIATURE 24-HOUR TIMESWITCH (German mfr.)

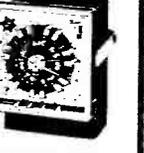240V A.C. operation. Spring reserve 36 hours. 20 amp contacts, one on-off every 24 hours. Calibrated in two hour steps 15 min. on-off period 6 hours. Day Omission. Unusual feature with these switches is that trips may be removed at any time. Individual days to be programmed as required. Size only 3 1/4" x 4" x 2 1/4" Price £6.50 + 50p P&P (£8.05 inc. VAT & P)



N.M.S. — New Manufacturers Suppl. R & T — Recommended and Tested

All Mail Orders — Callers

— Ample Parking

Showroom open Mon-Fri.

SERVICE TRADING CO

57 BRIDGMAN ROAD CHISWICK LONDON W4 5BB 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10.00

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ

Tel: 01-437 0576



MICROFILE

Henry Budgett's comments last month spurred some of you to take up pen and phone. This month micro-man brings news from the North and gives the Beeb a plug.

My little plea for help over the problems involved in modem style connection of home computers has borne some fruit. A very helpful gentleman, who just happens to work for the PO, wrote in with a few comments. Apparently the Post Office regard acoustic modems as attachments in much the same way as answering machines and there are a considerable number of specifications to be met. Such items are the maximum sound level of -13 dBm and the maximum sound pressure at the transmitter of 0.5 Newtons per square metre. Type approval for these kinds of devices should be obtained and I gather that ad-lib experimentation may be frowned on, so take care!

It should also be noted that hard wiring of a computer to the PO lines is definitely *not* on. I didn't suggest it last month, but just in case it has crossed your mind . . . forget it.

One other comment that was thrown in from another PO person was that there is a rather critical frequency around 2200 Hz. A tone of this frequency will cause the exchange to close down your call, slightly embarrassing. You have a bandwidth of 300 to 3500 Hz to play with so steer clear of this area. Full technical details of the specifications are contained in Technical Guide No 11, which should be obtainable from the telephone section of the Post Office.

And finally on this subject, I understand that Greenbanks cassette interface for their SCMP system has provision for an op-amp to be connected for direct tape head drive. It should prove possible to use this to drive a loudspeaker for our purposes. The board is currently being re-designed so contact them soon for details. Many thanks to Mike for his helpful comments on the Post Office's position.

Standard Letters

A vast epistle squeezed its way into my mailbag this week after my diatribe on standards last month. One problem . . . there was a lot in it about misspelling and general misuse of Her Britannic Majesty's English but not a sausage (courtesy of *That's Life*) on computer jargon. Have you no shame, or perhaps you were all stunned into silence? Please will someone say something, hopefully polite, as the article was supposed to inspire general comment.

Plea For Clubs

Not a single word from anyone this month. Are you all too busy to write to Microfile with your news? Many thanks to

those who have filled in the little form and sent it back. If any club hasn't had one please let us know as we are trying to produce a second Club Directory for CT and we go to press in four weeks. After all, if the Beeb think it's good enough to use what have you got to lose, poetic stuff.

BBC Speaks Out

A superb pair of programmes were broadcast this month on Radio 4. Called "Machines with Mouths" and "Machines with Ears" they dealt with speech synthesis and recognition systems and techniques which are currently being used. Having worked in this area for a number of years I found them to be excellently produced and most enjoyable. A definite pat on the back for the Science Department. What was even more impressive was that it was done on radio. One would expect this kind of subject to be tackled on a programme such as *Horizon*. It was also amusing to hear many voices from the past (such as my old boss) expounding their views on the subject. A repeat soon one hopes, how about it?

News From The North

Microdigital have released the first of a series of Nasbus based general purpose interface boards. This one has sixteen relays and is addressable to any two consecutive ports on the Nascom. Power requirements are a modest 250 mA on both the $+12$ and $+5$ volt rails and the unit is supplied as a kit complete with sockets for all IC's along with a manual and sample software. Price is around the $\pounds 50$ mark.

The ACFA single board computer that we had a slight mix-up over a month or so back is currently being re-engineered for the new 6809 CPU and some more I/O. The problems caused by the NTSC (Nasty Television System for Computers) have now been overcome and a demo model will shortly be going round the shows. Look out for it, it may suit your needs.

The Liverpool software gazette has just been launched priced at $50p$ per issue or $\pounds 6$ per year for twelve copies. It is packed with software and reviews, including a look at Pascal on the Apple. One of the most interesting items is the complete listing of the M5 language, which has now gone public, for the Nascom. For more details on the language see our review in CT May. The magazine is not intended for the beginner as it assumes a reasonable knowledge of computers. Details on all these products can be obtained from Microdigital at 25 Brunswick Street, Liverpool 2.

ETI


**Next
Month**

Hobby Electronics


Have we got an issue for you next month? Yes of course we have, just cast your tired eyes over this little lot. (Tired eyes can be avoided by refraining from reading lesser electronic magazines)

SCALEXTRIC SPECIAL

Yes folks, HE's done it again. Just in time for Christmas. The HE workshop staff have been really getting their noses to the grindstones and have tirelessly, without any regard for personal health, been playing with their Scalextric set. Whilst they were doing so one of them had a bright idea, 'how about doing some projects on this lads?' He was quickly silenced and play recommenced. A little while later, after this momentous statement sunk in, they thought about it and actually all agreed, it was a good idea. So now we proudly present the last word in electronic Lap Counters, Precision Hand Controllers and other amazing things to grace your layout. Miss it at your peril.

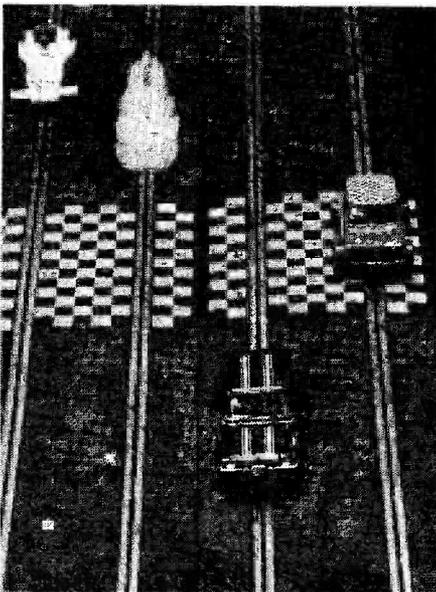

RING MODULATOR

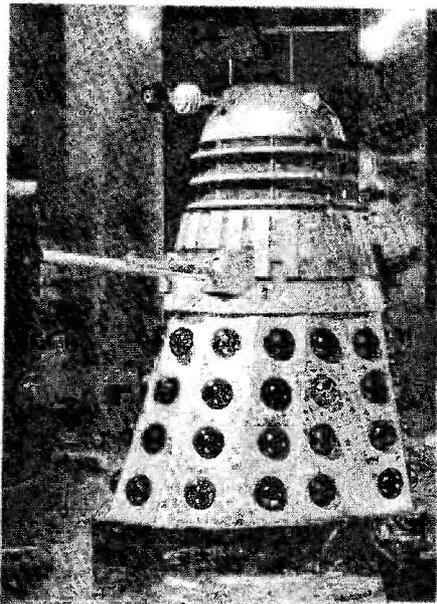

Where do we get them from? Now you can really sound like a Dalek. This neat little unit, designed for use on stage, at home, or just for good old fashioned fun will faithfully reproduce the dulcet tones of those amiable creatures from the planet Skaro. If you don't want to be a Dalek then it will create an interesting range of other effects too. Maybe we'll hang one on HEBOT. You never Know

UNIUNCTION TRANSISTOR

Our brainy chief designer Ray Marston takes time off from his train controller to look at those oft maligned, collectorless transistors that are known to all and sundry as Unijunctions. So pay attention because we might be coming round your house to ask you questions about them.


TV-THE CONTINUING STORY

This month Rick Maybury looks at the other end of the TV system, the box that sits in the corner of your living room. Find out just what happens when the on off switch is twiddled, the educated electron strikes again.

PROJECT FAULT FINDING

Gasp . . . your project didn't work, if it wasn't our fault (is it ever?) then it must be your fault. Keith Brindley, who has had to deal with one or two faulty projects in his time discusses the heart wrenching subject of dead projects.


HEBOT GROWS UP

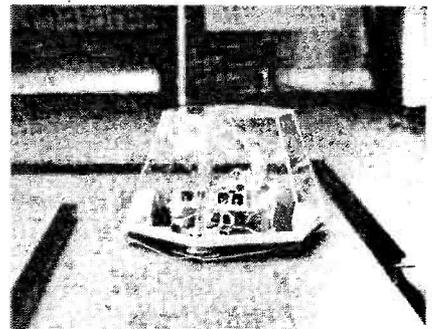

We are expecting HEBOT to start a craze (seriously) the combination of a really well designed, sturdy chassis at a very reasonable price, coupled with our unique electronic circuitry, brings the world of advanced robotics to within everyone's grasp. This month after completing the basic drive circuitry we go on to explore tactile senses, optical stimuli and self survival instincts. HEBOT is the first serious attempt in this country to bring the world of Robotics into the seventies, others have tried and failed, we know we are going to succeed. Frighten the cat, amaze the neighbours but above all DO NOT MISS IT.

The December issue will be on sale November 9th

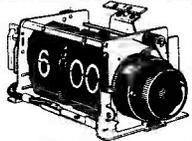The items mentioned here are those planned but circumstances may affect the actual contents



MECHANISM WITH ALARM

£5.00



Assemble it in an evening!
MECHANISM & CASE
(inc. assembly instructions)

£6.99

DIGITAL 24 HOUR CLOCK

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS

AS USED IN **BRAUN** DIGITAL CLOCKS

THREE FOR £13.50 MECHANISMS 10 FOR £39. 100 FOR £300

- AC MAINS
- SIZE 6 3/4 x 2 3/8 x 2 3/4

Your receipt is a 2-year guarantee

HALF PRICE OFFER

HENRY'S Radio

DELIVERY FROM STOCK

HENRY'S RADIO
404 EDGWARE ROAD,
LONDON W2 1ED 01-723 1008

EXPORT ENQUIRIES INVITED

BARCLAYCARD DELIVERY FROM STOCK



QUALITY REEL TO REEL & CASSETTE TAPE HEADS


<p>B12-01 MONO PLAYBACK £1.89</p> <p>B12-02 MONO RECORD/PLAYBACK £4.02</p> <p>B24-01 STEREO PLAYBACK £3.30</p> <p>B24-02 STEREO RECORD/PLAYBACK £6.66</p> <p>B24-03 STEREO GLASS FERRITE REC/PLBK £11.60</p>	<p>SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS</p> <p>E12-09 MONO/STEREO ERASE £1.85</p> <p>B22-02 TWIN HALF TRACK RECORD/PLBK £5.97</p> <p>C44RPS02 QUAD QUARTER TRACK REC/PLBK £9.37</p> <p>C22ES02 TWIN HALF TRACK ERASE £4.72</p> <p>MAGNETIC TAPE HEADS CATALOGUE 25 PENCE</p>
---	--

PLEASE ENCLOSE 30p P&P WITH ORDER ALL PRICES INCLUDE VAT

MONOLITH
THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

Great new Crofton double!

Self contained
MONITOR PCB

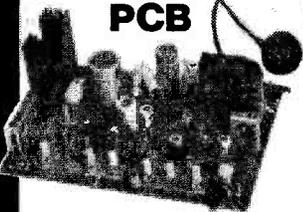

self contained **10" MONITOR**



- Compact size, 5" x 7"
- Complete with power and video plugs, plus leads
- Scan coil assembly as standard supplied
- Transformers, tubes, and surrounds available
- 15v Mains or 12v DC power
- Ideal for O.E.M. use

- Totally enclosed
- All transistorised
- Suitable for analogue signals or alphanumerics
- Operable on 220v Mains or 12v DC power
- Comparable to wire frame monitors

ONLY **£35.50** ONLY **£85.00**

EX VAT AND P&P

Crofton Electronics

Crofton Electronics Limited, 35 Grosvenor Road,
Twickenham, Middlesex. Tel.: 01 891 1923

All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip-on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the normal.

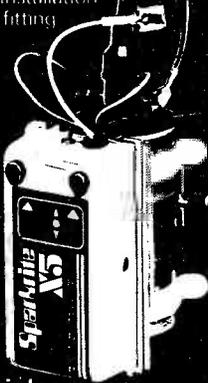There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE EVERYTHING NEEDED
Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy"

Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. ET1 12
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard I enclose cheque/PO's for

Inc. V.A.T. and P.P. QUANTITY REQ'D

X5 KIT £16.95	£
ACCESS OR BARCLAY CARD No. _____	Cheque No. _____

Send SAE if brochure only required.

WE'VE MOVED

Special just in full spec. 1702A (intel) £2.50 each p/p 20p. 74125 (tri-state buffers) 4 for £1.00. P&P 20p.

IS423 STUD MOUNTING RECTIFIERS 10A 400V. Silly price, 10 for £2 P&P 20p.

MC1303L Dual Stereo Preamp, plus data £1 P&P 20p.

7in NYLON CABLE TIES 100 for £1.50 P&P 20p. 1 watt Audio amp pcb (LM380) 9 to 18V DC. £1.50. P&P 30p.

ML723 (TO100). Monolithic adjustable voltage regulator. Plus or minus 2v-6v, 6v-8v, 8v-37v to 150mA plus data 55p P&P 20p.

PCB KEYBOARD 65mm x 82mm 18 key clickers less key tops. ideal hexadecimal. 35p each, P&P 20p. Hewitt Packard 4 digit displays 12 pin DIL 0.11" common cathode (LED red) £1.50 P&P 20p (few only).

CANNON D-TYPES. Only ones left: 15 way socket 50p, 37 way plug 80p, 50 way socket £1.20, 50 way wire wrap socket £1.30, 25 way ribbon plugs 90p. Cinch 25-way plastic cover 60p, Metal cover and retainer 80p. P&P 20p.

FULL SPEC. SGS2N3055 30p each. 10 for £2.75. P&P 20p.

SUPERSAVER 1 Haydon 240V AC 50 cycles 6 digit minute time. Panel mounting 2 1/2" dia. approx. £2. P&P 30p.

SUPERSAVER 2 Hybrid Systems DAC 371-8 (8-bit) DIL packaged + data, ideal MPU users. brand new £2 price smash! now £1.75 each (fraction of original cost) P&P 20p.

SUPERSAVER 3. LM 323K Voltage regulator, 5v at 3-amp, £3.50 each. P&P 20p.

MEMORIES 2708 £6.85. Character Generator MM5240 2560 bit, 64 x 8 x 5 plus data £2.95 (full spec.) P&P 20p. 2112 (200Ns) £3.00. P&P 20p. 21L02 (250ns) £1.15. P&P 20p.

SUPERSAVER 4. RS338-383 miniature decade thumbwheel switch £1.35 P&P 20p.

SUPERSAVER 5. SN74116 (dual 4 bit latch) 75p P&P 20p. SN74181 Arithmetic logic unit/function generator 80p P&P 20p. SN74194 (4 bit shift register) 50p P&P 20p. SN74198 (8 bit shift register) 75p P&P 20p.

SUPERSAVER 6. BC108B 8p 100 for £7.00 P&P 20p.

SUPERSAVER 7. 4 digit 7 segment bubble display (NSA1540A) ex-equipment 5 for £1.00 P&P 20p.

9-WAY MALE/FEMALE connector (Elco 8129) 0.1 inch pitch. PCB mounting ideal for bussing two PCBs together 35p/pair P&P 20p.

LEDS (red) TIL209 10p, 100 @ £8.50. 0.2" 12p. ORP12 95p. Voltage regs LM340T + 5V £1. LM340T + 12V £1. SGS 15V 3amp £1. LM342 + 15V (250 milliamps) 45p. (v cassette recorder motors, voltage speed regulated, terrific value 95p.) LM711 CH (voltage comparator) 25p.

Happy Christmas to all our customers and ETI staff.

All enquiries, SAE please. P&P same for quantities except where greater than £1.

Due to move we have no catalogue. A new one is being produced, available shortly.

Rush orders as some stocks are limited.

Phone orders on Barclaycard now taken for Mail Order.

New Retail Premises open now. Mon., Thur., Fr. & Sat. 9.30-6.00 (lunch 1.00-2.00). Many one-off computer bargains & components at surplus prices. We are situated at 11 Hercies Road, Hillingdon, Middlesex (just off A40) phone Uxbridge 55399. Supplies equipment/components purchased for cash.

L. B. ELECTRONICS
11 HERCIES ROAD
HILLINGDON
MIDDLESEX UB10 9LS, ENGLAND



Hand held Computer games
We have selected the best available
It's you against the computer!

UFO MASTER BLASTER STATION

More sophisticated than DESTROYER. Guide missiles to destroy UFOs which may change course or disappear!


£22.50



GRANDSTAND 4-in-1

Calculator/Auto Race/Code Breaker (as Digits)/Blackjack. Convenience — skill — Brainpower — Luck?


£22.50

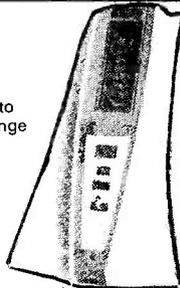

AMAZE-A-TRON

Over 1 million mazes to defeat! 1 or 2 players Electronic sound effects

£17.25

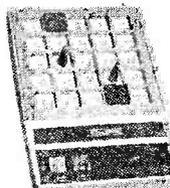

GRANDSTAND DESTROYER

Protect your convoy from destroyers

£14.95

GRANDSTAND SOLITAIRE

Challenging and absorbing

£14.95


DIGITS (As Mastermind)

Deduce four random numbers

£13.95

MICROPROCESSORS

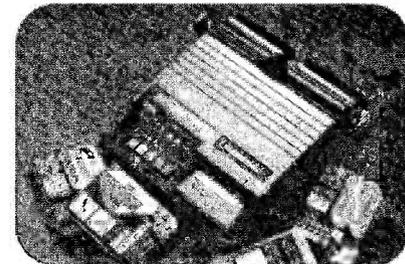FAIRCHILD GRANDSTAND
Video Entertainment Computer **£74.95**




19 plug-in pre-programmed memory cartridges now available. **Each £12.50**

LCD PROGRAMMABLES

With **non-volatile** stores and memories and almost infinite programmability (using FA-1).

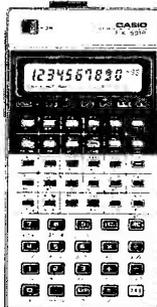1500 hours continuous use battery life. 51 scientific functions. 3/4 x 2 1/4 x 5 1/2 ins. Wallet.



FX-501P 11 memories, 128 functional steps, 5 levels (.), 9 subroutines, 4 levels. (RRP £64.95.) **£54.95**

FX-502P 22 memories, 256 functional steps, 10 levels (.), 9 subroutines, 9 levels. (RRP £84.95.) **£74.95**

FA-1 Adaptor **£19.95**

Optional FA-1 permits programme/data storage on standard cassette tape recorder for re-entry later.

CASIO CLOCK/ CALCULATORS

THE INCREDIBLE AQ-2000

Watch, full calendar, two alarms, stopwatch, time memory, count-down alarm, 8 digit calculator. Displays any monthly calendar from 1901 to 2099. Memories and displays 3 optional important dates. Full memory, %, K, square roots. One year battery life, 1/4 x 2 1/2 x 4 7/16th ins. Wallet. (RRP £27.95.) **£24.95**



MICRO MQ-11

Specifications as AQ-2000 but with "kiss" keys and smaller case 3/16th x 2 1/2 x 3 1/2 ins. Wallet with window for display. (RRP £29.95) **£26.95**



MELODY 80 Electronic Melody Maker

Clock, auto-calendar. Two alarms, alarm/timer (3 different tunes). Stopwatch measuring net, lap and 1st and 2nd place times from 1/10th second to 24 hours. Calculator with full memory, %, square roots. One year battery life. 5/16th x 4 1/2 x 2 1/4 ins. Wallet. Desk stand. (RRP £25.95) **£23.95**



CQ-82 Multi Alarm Clock

4 independent alarms, one with snooze feature. Nightlight. Calculator with %, square roots. One year battery life. 1 1/4 x 5 1/2 x 2 1/4 ins. (RRP £22.95) **£19.95**

NEW SCIENTIFICS

COLLEGE FX-80

6 + 2 digit LC Display. Approx. 4,000 hrs. continuous use from 2 AA size batteries. 37 scientific functions, P to R, R to P, ENG key, Pi, cube root, 6 levels (.), Memory. 3/4 x 3 x 5 1/2 ins. (RRP £17.95) **£15.95**


FX-68 Card

As FX-80 but without ENG key, 500 hrs. battery. 3/16th x 2 1/2 x 3 3/8 ins. Wallet. (RRP £22.95) **£19.95**



CASIO FX-2600

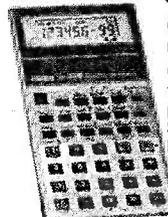Ultra slim—5/32in
6 + 2 digit LC Display, 43 scientific functions. Non volatile memory. Auto power off 6 levels parenthesis. Standard deviations. R to P, O to R, ENG, FIX, SCI, RND and Random number keys. 5/32in x 2 1/4 x 4 7/8 in. **£19.95**



CASIO FX-3200

As above but 10 digits **£21.95**

CASIO FX-310

As FX-2600 but 50 scientific functions. 1/4 x 2 1/2 x 5 1/4 in. **£17.95**

CASIO FX-510

10 digit version of above **£19.95**



TEMPUS

SEE OPPOSITE PAGE
FOR ORDERING DETAILS

From Casio's New Collection we present some of the most sophisticated executive watches available today.

FROM CASIO — THE NEXT STEP FORWARD IN TIME

New Lithium batteries, lasting up to 5 years or more, totally eclipse most SOLAR watches

ALARM CHRONOGRAPHS

STAR BUY

LATEST MODEL

Displaying hours, minutes, seconds, date, am/pm; or hours, minutes, alpha day, date, am/pm. With automatic 28, 30, 31 day calendar.

83QS-27B

4 year battery, 1/10th second chrono to 12 hrs., measuring net, lap and 1st and 2nd place times. 24 hour alarm. Hourly chimes. Backlight. Mineral glass. Stainless steel encased. Water resistant to 66 feet (RRP £31.95)

£27.95



You cannot fight against the future. Time is on our side

(V. E. Gladstone)

Displaying hours, minutes, seconds, day; and with day, date, month and year automatic calendar, pre-programmed to the year 2030.

(Available soon)



81QS-33B

5 year battery. Chrome plated case, water resistant to 66 feet. (RRP £31.95)

£27.95

1/100th second chrono to seven hours. Net, lap and 1st and 2nd place times. Selectable 12 or 24 hour display.

24 hour alarm. Selectable hourly chime facility. Backlight. Mineral glass face.

81CS-36B

As above but: Stainless steel case, water resistant to 100ft. (RRP £39.95.)

£35.95



There is no present like the time

F-8C TIME/DATE WATCH

3 year battery. Hours, minutes, seconds, date, day, am/pm. Auto 28, 30, 31 day calendar. Backlight. Resin case/strap. Mineral glass. water resistant to 55 feet. (RRP £12.95.)

£10.95

N.B. This watch does **NOT** have a stopwatch. If you have been misled by others, you are legally entitled to your money back and costs.



We are never knowingly undersold and will try and match or beat any other advertised price, providing the advertiser has stocks.

Please note We are NOT selling the Hong Kong watches which are currently proliferating on the market.

In common with Citizen and Seiko, Casio watches are outstandingly reliable, with typical failure rates of under 1%. Casio's service time is normally an impressive 2-3 weeks and they have comprehensive stocks of spares

Why spend money on less reliable watches?

CASIO LADIES' WATCHES

Superbly styled stainless steel cases, with mineral glass face, water resistant to 100 feet. LC Display of hours, minutes, 10 seconds, seconds by flash, am/pm; And with day, date and month.



86CL-22B
£37.25



86QL-12B
£31.95



86QL-10B
£26.50

Most CASIO products available from stock. Send 25p for illustrated brochures and membership of our CHRISTMAS CLUB. EXTRA DISCOUNTS on many items.

CASIO CHRONOGRAPHS

Constant LC Display of hours, minutes, seconds, am/pm and day (12 or 24 hour). Dual time (12 or 24 hour). Automatic day, date, month and year calendar, pre-programmed to year 2030. Chronograph measures net, lap and 1st and 2nd place times from 1/100th second to 7 hours. Backlight. Mineral glass face. Guaranteed water resistant.

NEW MODEL 95QS-32B

4 year battery. Superbly styled brass case, heavily chrome plated. Water resistant to 66 feet. (RRP £27.95.)

£23.95



95QS-31B

4 year battery. Stainless steel encased. Water resistant to 66 feet. (RRP £27.95.)

£23.95



95CS-31B

Solid stainless steel case.

Water resistant to 100 feet.

(RRP £34.95.)

£29.95



Time never stands still with Casio

F.200 SPORTS CHRONOGRAPH

Hours, minutes, seconds, am/pm; and with day, date and month auto calendar. 1/100 sec chrono to 1 hour. Net, lap and 1st and 2nd place times. Resin case and matching strap. Mineral glass. Water resistant to 66 ft (2 at.). Silver oxide battery. RRP £17.95

£15.95




Price includes VAT, P&P. Send your cheque, P.O. or phone your ACCESS or B'CARD number to: —

TEMPUS

Dept. ETI, Beaumont Centre, 164-167 East Rd., Cambridge CB1 1DB. Tel. 0223 312866

AIRCRAFT BAND CONVERTER

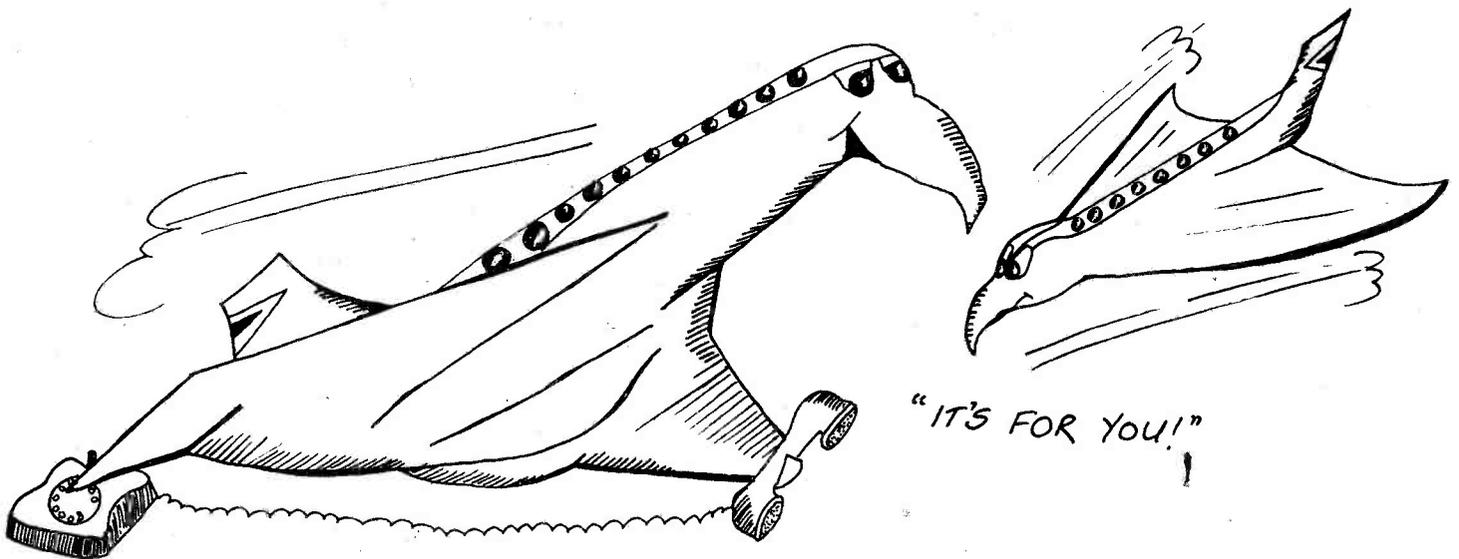Listen in to the world's airlines with the ETI Biggles detector and your own short wave radio.



Domestic aircraft communications, both private and commercial, generally involve a pilot talking from his plane to a traffic controller at an airfield as well as talking to other pilots. Signals from aircraft can be heard over quite long distances as they are flying quite high and thus the horizon, from the aircraft, can be up to several hundred miles away.

There are 360 channels allocated in the aircraft band, each assigned a specific use or for use in a particular area. Amplitude modulated (AM) transmission is used which simplifies the requirements for a receiver to listen on this band.

The Converter

Why a converter — why not a complete receiver? Firstly, a shortwave listener will already have a receiver. A converter to 'change down' the aircraft band frequencies to a suitable band between

3 MHz and 30 MHz is a simple, and inexpensive, solution. For those wishing to monitor some portion of the aircraft band the output of the converter could be connected to an ordinary multi-band transistor portable to provide quite adequate results. Alternatively, a fixed frequency IF (intermediate frequency) strip with detector and audio stages could be constructed.


The converter is crystal locked — that is, a quartz crystal oscillator is mixed with the signals from the antenna, the signals then appearing at a lower frequency at the converter output. The frequency of the crystal used will determine the frequency band of the converter output.

For a number of reasons, we chose the output (or IF) frequency to be around 10 MHz. Inexpensive crystals are available for the aircraft band to give an IF output from the converter of 10.7 MHz — a standard IF frequency. The

same crystals can be employed if you wish to use a tunable shortwave receiver following the converter. There is a minor inconvenience though — the tunable receiver's dial has no simple relationship to the input frequency. The advantage is that inexpensive crystals cost around half that of a crystal made to order to provide a direct frequency relationship.

As the converter has quite a deal of gain, resulting in very good sensitivity, an RF Gain control has been provided. Very strong signals on a channel near to the one being monitored may cause interference. Judicious use of the RF gain control will reduce or remove the interference while enabling you to still hear the desired signal. Then again, a very strong signal on the channel you are monitoring may overload your receiver, resulting in very distorted reception. Reducing the RF gain will remove the problem.

Fig.1 Circuit diagram.

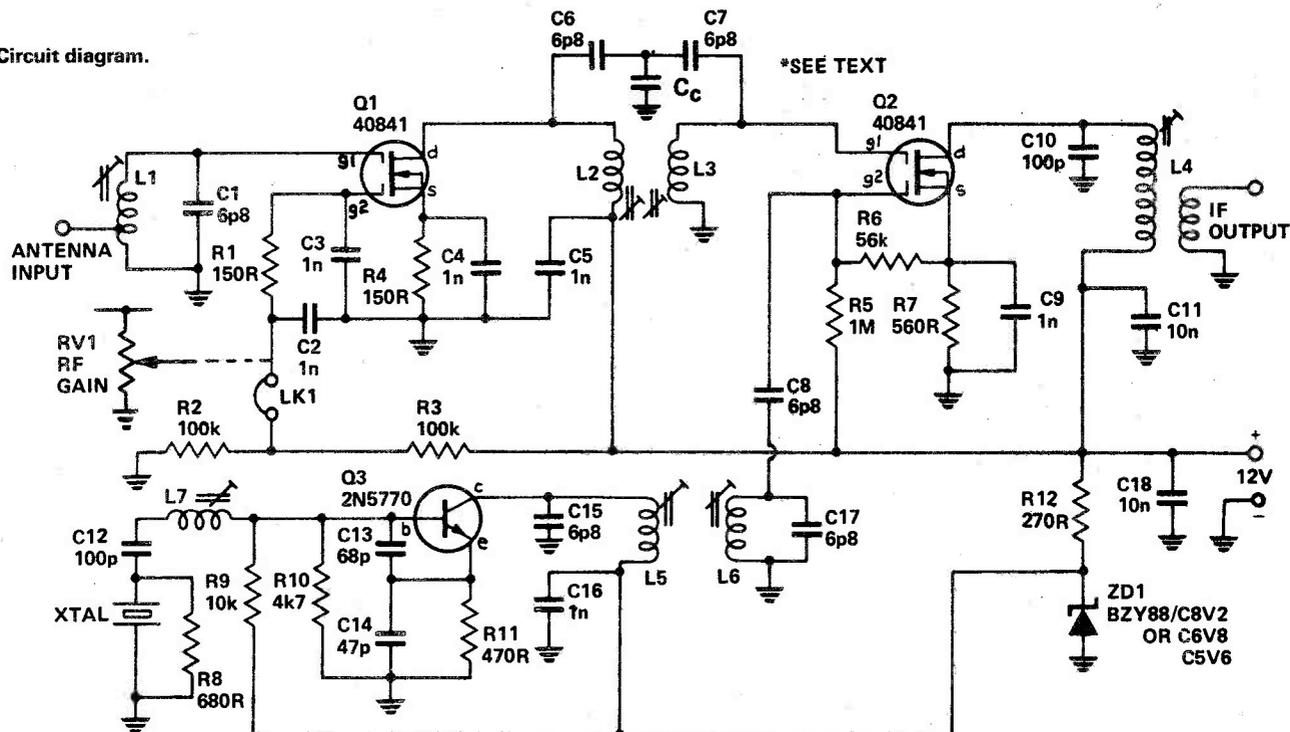

Construction

The printed circuit board has been specially designed for this application and no other construction technique should be employed unless you are very experienced in circuit construction at these frequencies.

It is best to commence construction by mounting the coil formers. They may be glued on the board over the pilot holes or the board drilled to the appropriate diameter for the base of the formers and then gluing the formers in place. Use the shield cans to locate and/or hold the formers on the board. It is wise to insert the slugs in the formers *after* gluing to avoid accidentally gluing them to the formers. The best type of glue to use is one of the 'instant' bond glues such as "Superglue". Many glues available will not bond to substrate materials — particularly fibreglass material.

The next step is to wind the coils. They may be wound *in situ* if you wish, alternatively they may be wound on a suitable diameter former (such as a 5 mm or 3/16" drill shank) and then slipped over the formers on the board.

Take careful note of winding direction and the start and finish connections. Refer to the component overlay when soldering the coil leads in place. Do not mount the shield cans until all the minor components have been soldered in place.

When mounting the minor components take particular care with orientation of the transistors, FETs and the

HOW IT WORKS

The circuit is quite straightforward, comprising an RF stage (Q1), a mixer (Q2) and an overtone crystal oscillator/multiplier (Q3). Dual-gate MOSFETs are used in the RF and mixer stages as they have good gain, low noise figure and good freedom from crossmodulation and overload problems.

Signals from the antenna are first amplified by Q1 and passed to gate-1 of the mixer Q2. The oscillator Q3 is set to a precise frequency by the crystal. The injection frequency to gate-2 of the mixer is derived from the collector of Q3, being two or three times the crystal frequency. The signal frequency and the crystal frequency are mixed in Q2, their difference is selected by the tuned circuit in the drain — this is the desired output frequency.

A low-Q tuned circuit (L1-C1) is used between the antenna input and gate-1 of Q1. The antenna input impedance is matched to the impedance of the gate to optimise noise figure. The drain of Q1 is coupled to gate-1 of the mixer Q2 via a double-tuned, bandpass coupling circuit consisting of L2, C6, C7 and L3. A combination of inductive coupling and

common-emitter coupling is used to achieve a wide bandwidth.

Gate-2 of Q2 requires a bias of +6V for full stage gain. A link between gate-2 decoupling (R1, C2, C3) and the junction of R2-R3 allows for the connection of a gain control potentiometer.

The mixer has about 1V5 of bias applied to gate-3. The conversion frequency is injected at this gate and a small amount of forward bias improves the mixer conversion gain. The output, of IF, is coupled via L4 which is resonant at 10 MHz with C10. This is a low-Q tuned circuit for the broad bandwidth necessary if the tunable IF receiver is used.

The crystal oscillator stage, Q3, is designed to cope with either third or fifth overtone crystals and may double or triple the crystal frequency in the collector. Tuning circuit L5-C15 selects the appropriate harmonic. Energy is coupled from L5 to L6 which is resonated to the required frequency with C17. These two tuned circuits filter the injection frequency. This prevents any spurious mixing occurring in Q2.

Coil L7 is used to 'trim' the crystal.

zener diode. All components should be mounted right down on the board to minimise lead length. Stakes or pins should be used for the connections to the antenna input, IF output and dc connections.

There is provision on the pc board to mount a crystal socket for a 'style-D' crystal. These have a 12 mm pin spacing and stand about 20 mm high. Alternatively, if the smaller size crystals are used, having a pin spacing of 5 mm or pigtail connections, then they may be soldered in place under the board. Take

care when doing this. Do it quickly and use the minimum amount of heat to avoid damaging the crystal.

If desired, the crystal may be mounted separate from the board. Keep lead length between the crystal and the board connections as short as practicable in this case.

The shield cans for the coil assemblies should be mounted last. It may be a wise idea to check that the converter is working before soldering the shield pins to the pc board.

The completed converter may be ►


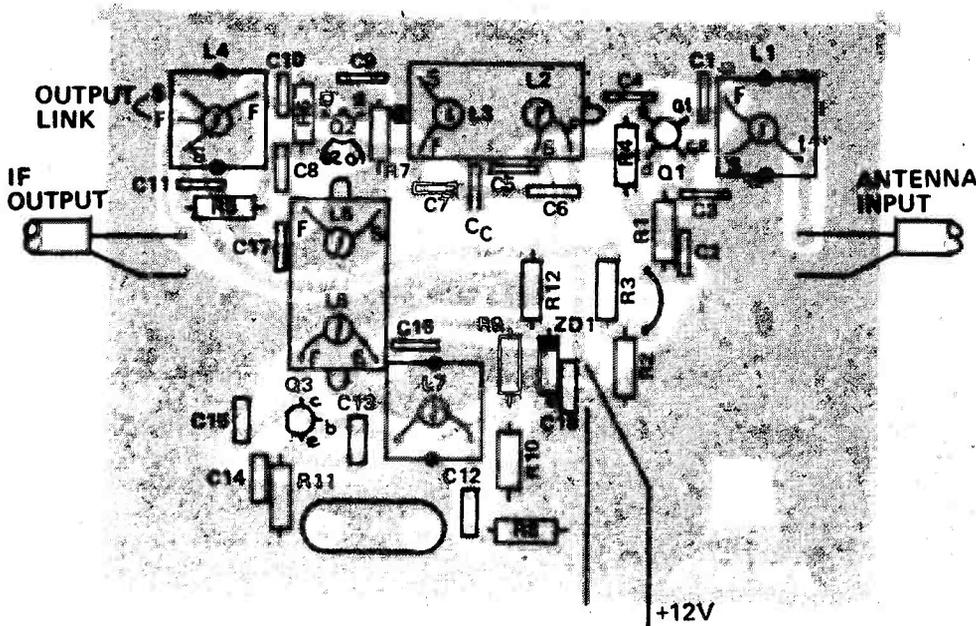


Fig. 2 Component overlay.

PARTS LIST

- Resistors all 1/4W 5%
- R1,4 150R
 - R2,3 100k
 - R5 1M
 - R6 56k
 - R7 560R
 - R8 680R
 - R9 10k
 - R10 4k7
 - R11 470k
 - R12 270R
- Potentiometer
- RV1 100k
- Capacitors
- C6 22p ceramic
 - C1,5,17 6p8 ceramic
 - C2,C5 1n ceramic
 - C6,C8 6p8 ceramic
 - C10,12 100p ceramic
 - C11,18 10n ceramic
 - C13 68p ceramic
 - C14 47p ceramic
 - C16 1n ceramic
 - C18 10n ceramic
- Semiconductors
- Q1,2 MFE131, 40673, 40841
 - Q3 2N3563, 2N3564, 2N5770
 - ZD1 BZY88/CRV or /C6V8 or /C5V6 or /C5V1
- Miscellaneous
- 1 x 12/I Neosid coil formers
 - 3 x 7100 Neosid screening cans
 - 2 x 7100 Neosid screening cans
 - 7 x Neosid ferrite slugs, 4 x 5 x 10/F29 coil wire
 - crystal - see text
 - box (see text), 2 coax sockets
 - 2 x 20 mm, 6 BA spacers, nuts, bolts, etc
- *Resistor values may be plus or minus one standard value either side of those quoted without ill effect. Capacitor values should not be altered.

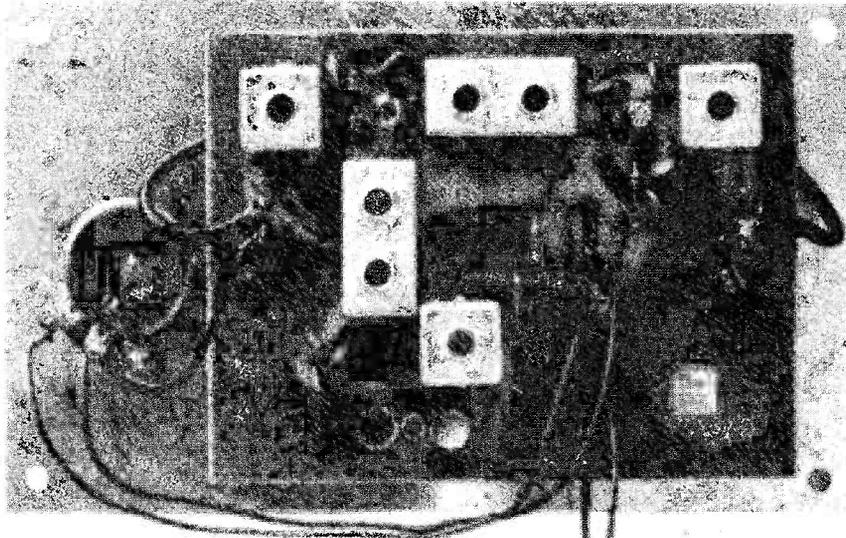

The PCB fitted to its front panel, showing connections to the gain control, RV1.

mounted, we used a small box measuring 159 x 96 x 50 mm overall. They are available from a number of component suppliers. The board was mounted on the aluminium panel using two spacers. Antenna and IF output sockets, along with the RF gain pot, were also mounted on the panel and power leads taken through a hole in the side of the box. Small lengths of coax cable were used to connect the input and output sockets to the board connection.

Control

The particular method of alignment will depend on how you will be using the converter. To commence the alignment you will need to have on hand the appropriate aligning tool. You will need a plastic screwdriver-tip alignment tool

to suit the Neosid ferrite cores. They are readily available from many suppliers.

You will need a power supply delivering between 12 and 15 volts; the converter will draw between 30 and 50 milliamps. A receiver with a S-meter is a decided advantage when aligning the converter. You will need a signal generator, with AM modulation, covering the range of 118-126 MHz.

If you are using a tunable receiver for the IF, then the following procedure should be followed:

Connect the converter to the receiver. Use a short length of coax cable. If the converter is working you will notice an increase in the noise level on a sensitive receiver when power is applied. You can check that the crystal oscillator is working by removing the crystal tem-

porarily - a decrease in the noise from the receiver will be noticed.

1. Set the receiver frequency to the middle of the tuning range of the converter's output. The converter RF gain should be at maximum all through the alignment procedure.
2. Tune the slug in L4 to obtain a peak in the receiver noise level.
3. Set all the other coil slugs flush with the tops of the coil formers.
4. Using the signal generator, with a fairly high output level, peak L4 again for best signal strength.
5. Set the generator to a frequency near 119 MHz and tune the receiver until you pick up the signal. Now adjust the slugs in L2 and L6 for best signal strength. Decrease the output of the signal generator so that these

adjustments are made on a fairly weak signal.

6. Set the generator to a frequency near 125 MHz, or the highest frequency in which you are interested, and tune the receiver until you pick up the signal. Adjust the slugs in L1 and L5 for best signal strength. Keep the generator output at a low level for best results.

7. Now set the generator to a frequency half way between these two frequencies. Tune the receiver to pick up the signal and adjust the slug in L3 for best signal. Check the adjustment of L4.

8. Return to 119 MHz and peak the slug in L2 again.

9. Repeat the procedure, 'touching up' each slug.

If the converter is to be used on one channel, or a couple of channels less than 1 MHz apart, then all the coils need only be adjusted for best signal strength on one channel.

Overall sensitivity of the converter-receiver system is very good, signals as low as 0.2 uV being clearly audible. The gain control range is about 20 dB.

CHOOSING A CRYSTAL

The frequency injected at gate 2 of the mixer FET, Q2, may be above or below the signal frequency by an amount equal to the IF frequency. For a turnable receiver used as an IF, the injection frequency should be lower than the *lowest* signal frequency by 10 MHz. Thus, as you tune the receiver upwards in frequency from 10 MHz, you will tune signals above the lowest aircraft band frequency (118 MHz). In this way there will be a simple relationship between the signal frequency and the receiver's dial. If 10 MHz equals 118 MHz, 10.5 MHz will equal 118.5 MHz, and so on. For this situation the injection frequency will be $118 - 10 = 108$ MHz. As the crystal oscillator output (collector of Q3) is twice the crystal frequency, the crystal frequency should be half of 108 MHz = 54 MHz.

If you use a tunable receiver than a fifth overtone crystal at 54.000 MHz should be ordered. Tolerance and adjustment range also have to be specified. A value of 20 parts per million (ppm) for tolerance and adjustment range is satisfactory. Firms such as Bright Star Crystals or Hy-Q should be able to supply a crystal to order.

Alternatively, a crystal at one-third the injection frequency may be used. Taking the 108 MHz injection frequency, as just illustrated a 36 MHz crystal may be used.

To determine the crystal frequency required for any case, use the following formula:

$$\text{Crystal} = \frac{\text{lowest signal frequency} - \text{IF}}{2 \text{ or } 3}$$

Inexpensive crystals intended for use in 'scanning' receivers are available from Dick Smith's. These provide an injection frequency *above* a particular aircraft channel frequency for the standard IF frequency of 10.7 MHz. For example, for the 125.8 MHz channel, the injection frequency is 136.5 MHz. These crystals have the channel frequency marked on them, not the crystal frequency.

SETTING THE CRYSTAL FREQUENCY

If you require accurate frequency readout then the crystal frequency will need 'trimming'. Coil L7 is provided for this purpose. For best results a digital frequency meter capable of measuring to 150 MHz is necessary.

Lightly couple the DFM to L5 or L6 via a small value capacitor and see if you get a sensible reading. You may need to connect it directly across gate-2 of the mixer, Q2.

Adjust L7 until you obtain the correct injection frequency according to the crystal chosen.


BUYLINES

Components for this project are available from Catronics Ltd, Communications House, 20, Wallington Square, Wallington, Surrey SM6 8RG.


Coil Data

Wind L2, L3, L4, L5, L6 and L7 *clockwise* up the former. L1 is wound *anti-clockwise* up the former. The start of each coil is the 'cold' or 'earthy' end. All slugs are F29 type ferrite.

- L1 5 turns, 22 B & S tinned copper wire spaced over 10 mm, tap at 2 turns from cold end.
- L2, L3 6½ turns, 22 B & S enamelled wire, spaced over 8 mm.
- L4 25 turns closewound with enamelled wire, any gauge between 25 and 30 B & S, 5 turn link at top of former.
- L5, L6 5½ turns, 22 B & S enamelled wire, closewound.
- L7 *10 turns, 22 B & S enamelled wire, closewound, for crystals in the range 30 MHz to 50 MHz.
*6 turns for crystals in the range 50 to 70 MHz.

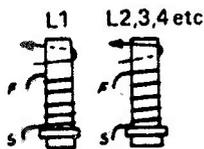

WINDING DIRECTION

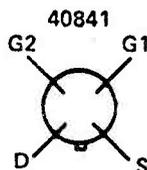

UNDERSIDE VIEW

ELECTROVALUE

LEADING DIRECT SUPPLIERS FOR



NASCOM MICROCOMPUTERS

AND FULL SUPPORTING RANGE OF ITEMS TO ENABLE YOU TO WORK AT PROPER PROFESSIONAL LEVELS

- ★ Appointed Nascom stockists
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

We are also Appointed Distributors for the fine products of:

SIEMENS, ISKRA, RADIOHM, VERO AND MANY OTHER FAMOUS MANUFACTURERS

It's a good deal better from

ELECTROVALUE LTD

Dept ETI 11 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB
(London prefix: 87; STD 0784. Phone: Egham 33603. Telex 264475.
Phone: Egham 3603. Telex 264475.
Northern Branch (Personal shoppers only). 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

Be among the first to get your

FREE CATALOGUE 10 by sending in your name and address NOW. (124 pages packed with items and illustrations).

● We pay postage in U.K. on orders list value £5 or over. If under, add 27p handling charge.

● We give discounts on C.W.O. orders, except items marked Net or N in our catalogue price list.

5% on orders, list value £10 or more.

10% on orders list value £25 or more.


Not applicable to Access or Barclaycard orders

● We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

● We guarantee

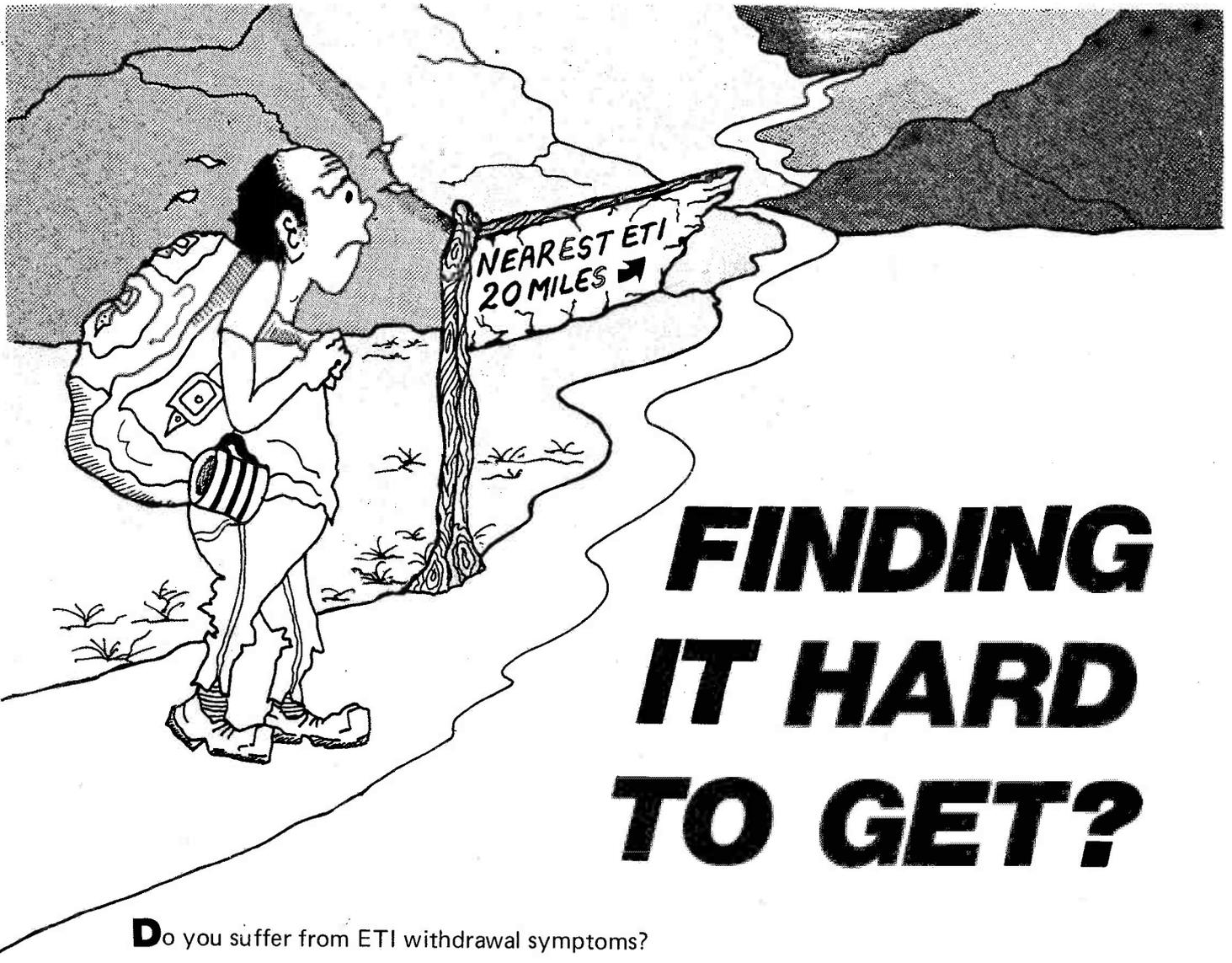all products brand new, clean and to maker's spec. No seconds, no surplus.



FINDING IT HARD TO GET?

Do you suffer from ETI withdrawal symptoms?

Do you break out in a cold sweat every month, wondering where your next ETI's coming from?

Do you have holes in your socks?

The answers to these and many other vital questions of today can be found in ETI subscriptions. For only £7.00 (£8.00 overseas) you can have twelve issues of ETI (all different) and cunningly spread over the entire year. You'll never again have to pack sandwiches, don haversack and set out on a monthly trek around the newsagents.

Relax in your armchair and wait for the satisfying sound of the best electronics mag in the country (unbiased opinion) dropping onto your welcome mat, delivered by hand to your door.

Send your subscription fee direct to

ETI Subscriptions
Map Publications
PO Box 35
Bridge Street
Hemel Hempstead
Herts.



DESIGNER'S NOTEBOOK

Project Editor Ray Marston passes around a few design problems with LEDs and chews a CMOS 555!

The path of the electronics design engineer is fraught with nasty booby traps in the form of seemingly simple little circuits which fail, in practice, to work in the anticipated manner. Take, for instance, one of the problems that faced the ETI projects team when the 'AMBUSH' game was being designed last year (see the April '79 issue).

Ambushed by LEDs

This particular booby trap centred on the LED 'attack' display that was used in the 'ambush' game. In essence, the display comprised four unequal-length lines of LEDs. All LEDs were driven from the outputs of a single 4017, but the lines were selected one at a time by a multiplexer, so that only one LED was on at any given moment. A greatly simplified diagram of the original (defective) version of this display is shown in Fig. 1. Although this diagram shows only three columns of LEDs, with a maximum of three LEDs in any one column, it does illustrate the basic 'trap' perfectly well.

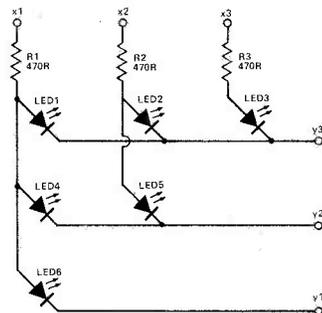


Fig. 1. A simplified view of the original Ambush LED lines.

In this diagram, the 'x' lines are driven by the outputs of the 4017, so that one line is high (at +12V) at any given moment and the other two lines are at zero volts. The 'y' lines are driven by a multiplexer or multi-way single-pole switch, which pulls one line to zero but leaves the other two lines open-circuit at any given moment of time.

Figure 2 shows the results that were (rather naively) expected from the circuit under two specific operating conditions and compares them with the results that were actually obtained. In Fig. 2a, +12V was fed to the x1 line

x1	x2	x3
+12V	0V	0V
y1	y2	y3
0V	0/c	0/c

x1	x2	x3
0V	0V	+12V
y1	y2	y3
0V	0/c	0/c

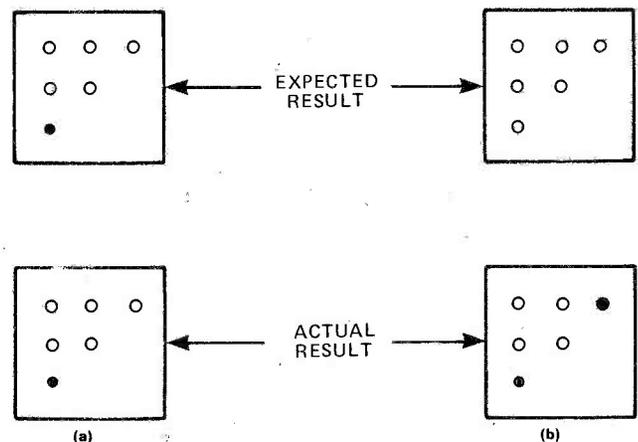


Fig. 2. Given the operating conditions, shown (top), these are the results which were expected (middle) and actually obtained (bottom).

and the y1 line was coupled to zero volts. As expected, LED 6 illuminated.

In Fig. 2b, +12V was fed to the x3 line and the y1 line was coupled to zero volts. It was expected that no LEDs would illuminate. In practice, LEDs 3 and 6 illuminated. Equally confusing results were found to occur in certain other combinations of switching position.

If you read last month's 'Notebook,' which dealt with LED pitfalls, you'll have already figured out the cause of the 'ambush' problem(!) If not, Fig. 3. illustrates the cause of the trouble quite well. The problem arises because of the low reverse breakdown voltages (5V in this case) of the LEDs. In this particular instance, forward current was flowing through LEDs 3 and 6 via reverse-biased LED 1, which had gone into the Zener mode.

The solution to this particular design problem is shown in Fig. 4. Here, ordinary diodes are used in place of all absent LEDs in the matrix, so that a ready conducting path exists in all switching positions, and no LEDs therefore become reverse biased. When this circuit is applied to the

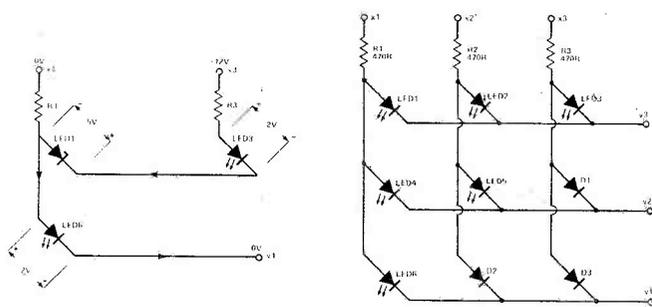


Fig. 3 (left) Low reverse breakdown voltages cause the problem here. Fig. 4 (right). Replacing absent LEDs with ordinary diodes is the solution here.

Fig. 2b situation, D3 conducts and all LEDs remain off.

As we pointed out last month, LEDs can be tricky little brutes.

We ran into a rather intriguing little problem when building the hand-held remote-control unit for 'The Beast' that is featured in this month's issue of ETI. The problem was that the unit's up/down counter was giving erratic operation. We knew that the fault was one of construction, rather than design, so laboriously went through all the normal troubleshooting procedures and finally isolated the fault (by intuition, rather than anything else) to the area of the 4093B dual-oscillator circuit shown in Fig. 5.

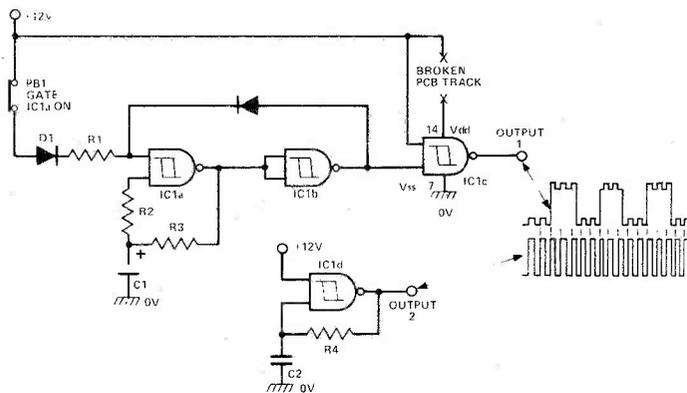


Fig. 5. A broken track caused problems in this 4093B dual oscillator, but proved difficult to find.

As you can see from the circuit, the fault was actually caused by a broken track connection to the IC's positive supply terminal. In practice, however, this simple fault was the devil's own job to find, for the following reasons:

First, the PCB was double-sided, which made it difficult to trace some of the tracks on visual inspection. Next, normal test-meter checks showed that a near-enough 12V supply did in fact appear on positive supply terminal 14 of the IC. Finally, oscilloscope inspection of the output terminals of the IC showed that the two oscillator waveforms of the circuit (see Fig. 5.) were indeed present, further strengthening the belief that the positive supply connection was OK. Suspicion was caused, however, by the fact that the waveform from output 1, which should have been a clean square wave, showed signs of being amplitude modulated by waveform 2. The fault was eventually located visually.

Figure 7 illustrates how the circuit managed to work and produce a 'supply voltage' on its pin-14 V_{DD} terminal, in spite of the broken supply rail track connection. The diagram shows the internal gate protection network that is fitted to each one of the input terminals of the 4093B. On gates IC1c and IC1d one of these inputs is taken directly to the positive supply rail, enabling supply current to flow to the V_{DD} terminal via RA and D1, and thus power the oscillator circuits!

So how's that for an unusual 'beasty' story?

CMOS 555 -- 7555

If you've ever played with the ubiquitous 555 timer chip (and who hasn't?), you'll know that it has a few inherently unpleasant characteristics, as well as a whole stack of good ones. It does not, for example, like supply voltages that are significantly below 5V, and it typically draws a hefty 10mA of quiescent current when operating from a 15V supply. Worst of all, it draws a massive 400mA 'spike' of current from the supplies as it transitions from one state to another, and this spike tends to play havoc with any digital circuitry that is powered from the same supply lines.

Fig. 6. (Below). A rationalised comparative summary of the bipolar and CMOS 555s.

PARAMETER	TEST CONDITION	BIPOLAR 555	CMOS 555	UNITS
SUPPLY VOLTAGE RANGE		4.5 to 16	2.0 to 18	V
OPERATING TEMP. RANGE		0 to +70	-20 to +70	$^{\circ}$ C
SUPPLY CURRENT, TYP.	$V_{CC} = 15V, R_L = \infty$	10	0.1	mA
OUTPUT CURRENT, MAX		200	100	mA
POWER DISSIPATION, MAX		600	200	mW
TRANSITION 'SPIKE' CURRENT, TYPICAL	$V_{CC} = 15V$	400	10	mA
TIMING ERROR, MONOSTABLE	$R = 2k\Omega$ to 100k	1	2	$^{\circ}$
INITIAL ACCURACY, TYP	$C = 100n$			$^{\circ}$
THERMAL DRIFT, TYP	$V_{CC} = 15V$	50	50	ppm. $^{\circ}$ C
DRIFT WITH V_{CC} , TYP		0.1	1.0	$^{\circ}$ V
THRESHOLD CURRENT		100	.01	nA
TRIGGER CURRENT		0.5	10^{-5}	μ A
RESET CURRENT		0.1	2×10^{-8}	mA
OUTPUT RISE TIME, TYP	$R_L = 10M, C_L = 7pF$	100	40	nS
OUTPUT FALL TIME, TYP	$R_L = 10M, C_L = 7pF$	100	40	nS
PROPAGATION DELAY OF TRIGGER PULSE, TYP	V_{trig} MINIMUM LEVEL = 0V, TEMP = 25 $^{\circ}$ C	100	310	nS
MINIMUM PULSE WIDTH REQUIRED FOR TRIGGERING	V_{trig} MIN LEVEL = 0V, $V_{CC} = 15V, TEMP = 25^{\circ}$ C	20	90	nS

You'll be pleased, therefore, to hear that Intersil have recently introduced a CMOS version of the 555 timer, known as the ICM 7555, which does not suffer from the basic defects of the bipolar version. Specifically, it can operate over the supply voltage range 2V0 to 18V, typically draws only 100uA quiescent from a 15V supply, and draws a trivial 10mA 'spike' of current when transitioning. Additionally, the required threshold, reset, and trigger currents of the CMOS device are several orders of magnitude down on the bipolar version, enabling timing resistors (for example) to be given values of hundreds of megohms.

Twice As Nice?

On the debit side, this new CMOS chip costs twice as much as the bipolar version, has worse initial-timing-accuracy and drift-with-voltage characteristics, has poorer output current drive and power dissipation capability, and

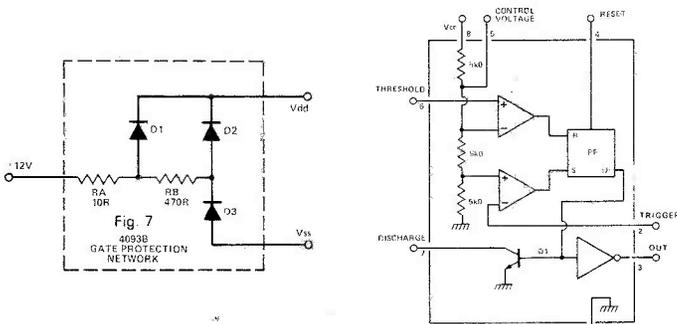


Fig. 7 (left) the internal gate protection network of the 4093B. Fig. 8 (right) The internal circuitry of the familiar bipolar 5555.

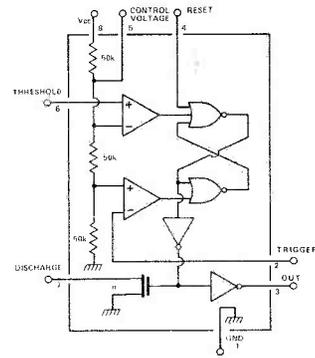


Fig. 9. The internal circuitry of the CMOS 555.

has worse propagation delay and pulse-triggering characteristics. A 'rationalised' comparative summary of the characteristics of the two devices is shown in Figure 6.

Figures 8 and 9 show the simplified internal circuits of the two devices. Note particularly the great differences in the relative values of the voltage divider chains that are used in the different versions of the IC.

The CMOS and bipolar versions of the IC are housed in identical packages. The CMOS chip can be used as a plug-in replacement in existing 555 bipolar circuits. The reverse is not necessarily the case, since the CMOS version can use timing and other resistance values that are several orders of magnitude greater than is possible with the bipolar version.

If you want to play with the ICM 7555, you can buy it from Watford Electronics, whose advert appears elsewhere in this issue.

ETI

WE'RE OUT TO FINISH

YOU OFF!

Rapitape #
eti PANEL TRANSFERS

MOD MAGS 1977 no 1

GOOD AND PROPER!

... or at least your projects. If there is one thing which is impossible to do at home is lettering front panels to professional standards. At least until now. If you cast your eyes right a while you'll see our new panel transfers sheet, which has been carefully designed to allow you to do exactly that.

The transfers are easily rubbed down, and the two sheet set contains a mass of lettering and -uniquely- control scales for both rotary and slider puts.

Each sheet measures 180mm X 240mm and comes packed flat in a stiff cardboard envelope for protection. There should be enough for dozens of projects here - and the longer you wait the worse they'll look!

Send £1.75 (includes VAT and postage) for the two-sheet set to:
Panel Markings
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF.

CALCULATORS

SCIENTIFIC

***SPECIAL OFFER**
TEXAS T159 together with PC100C
(Complete as manufacturer's specifications)
£285.00

- TEXAS/HP Accessories available
- *TEXAS T159 (Card prog 980 prog steps of 100 mem) **£156.50**
 - *TEXAS T158 (New Key prog 480 steps or 60 mem) **£80.00**
 - *TEXAS PC100C (Printing Unit for T158/T159) **£140.00**
 - *TEXAS T157 (Key Prog 8 mem, 150 Keystrokes/50 Prog Steps) **£25.00**
 - *TEXAS T145 (New updated version of the Texas T140) **£19.00**
 - *TEXAS TI PROGRAMMER (Hexadecimal Oct) **£46.50**
 - *TEXAS T151 (10 mem 32 Prog Steps, Stat/Sci) **£26.30**
 - *TEXAS T150 LCD (Sci/Stat, 2 Con Mem) **£23.00**
 - *TEXAS T125 LCD (Sci/Stat) **£18.50**
 - *TEXAS T53 (Sci, 32 Prog Steps, Coa Mem +80 Prog List, Applications book) **£25.00**

Make more of your Texas T158/59 Calculator MATH/UTILITIES MODULE

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs.

Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

- Module includes:
- Prompter, Alpha Messages.
 - Printer Formatting, Superplotter.
 - Sorting, Data Arrays.
 - Data Packing, Prime Factors.
 - Hyperbolic Functions.
 - Gamma/Factorial.
 - Random Numbers.
 - Normal Distribution.
 - Interpolation, Roots of a Function.
 - Minimax, Romberg Integration.
 - Differential Equations.
 - Discrete Fourier Series.
 - Calculator Status.
 - Variable Arithmetic Module Check.

- *TEXAS T158 with Maths/Utilities **£90.00**
- *TEXAS T159 with Maths/Utilities **£186.50**
- *TEXAS T158 with Applied Statistics **£80.00**
- *TEXAS T159 with PC100C & Applied Statistics **£305.00**

WINTER SALE

*TEXAS T159 Calculator (complete as manufacturer's spec, master module, charger, etc.), PLUS statistics module and extra set of 40 Blank Prog Cards with wallet, etc.
ONLY £180

NEW TEXAS T158C*

Continuous program facility on all 480 program steps/60 mem, even when calculator switched off **£79.50**

- *TEXAS T58C (complete plus Applied Stats. Module) **£99.00**
- *TEXAS T58C + PC100C **£208.00**

- *CBM Pro 100 (72 Step Prog) **£29.50**
- *HP33E (8 mem Pro Sci/Stat) **£49.00**
- *HP33E (Advanced Sci with Statistics) **£37.50**
- *HP31E (New Sci replaces HP21) **£25.50**
- *HP37A (C, Prog 224 Steps 26 Mem) **£188.70**
- *HP37A (Fully prog with Printer) **£384.35**
- CASIO AQ2000 (updated AQ1000 Cal, 3-Way Stopwatch/Alarm plus Date Calendar) **£22.00**
- CASIO FX3100 (LCD Sci Std/DP/Rec.) **£22.50**
- CASIO FX8000 (as above + Stop Watch/Alarm) **£27.73**
- CASIO FX501P (Sci, LDC Prog, 128 Steps, 11 Mem) **£46.00**
- CASIO FX502P (Sci, LDC Prog, 256 Steps, 22 Mem) **£84.00**
- CASIO Prog Adapter — permits Progs to be recorded on to standard cassette recorders for replay on Casio FX501P/FX502P at later stage **£23.00**

COMMODORE PET COMPUTER

with 8K bytes RAM 2001.8 **£550**
Pet 2001/16N **£675.00**
Fully guaranteed Warranty by CBM

OHIO SCIENTIFIC'S SUPERBOARD II **£188.00**

NOW IT'S YOU AGAINST 'COMPUTERS'

BORRIS the most advanced chess computer yet. Borris is ideal for the learning and improving your chess game from beginner to master. Borris can play against himself, has Alpha-Numeric prompting to help improve play and by simple switching you have facility to follow Borris's thinking while the analysis position before making a move. Walnut case, wooden chessmen, board mains adaptor, etc **£135.00**

CHESS CHALLENGER '10' (10 Levels of beginner to master) **£118.00**

CHESS CHALLENGER '7' (7 levels of game) **£76.50**

'VOICE' CHESS CHALLENGER **£200.00**

COMMODORE 'CHESSMATE' (8 levels — 32 International openings — ideal game for learning) **£50.00**

FREE — mains/Charger included

GOODS FULLY GUARANTEED. PRICES EXCLUDE VAT (ADD 15%) BUT INC. P&P CHEQUE WITH ORDER

Company/Hospital and Government orders accepted by phone

Barclaycard/Visa/Access accepted by phone

Tel. 01-455 9823

EXPORT ORDERS WELCOMED

Air Freight/Air Post Delivery

Quotations on request.

MOUNTAINDENE
22 Cowper St., London, EC2

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4½in **£2.50** with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8-10-12 T.O.S. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1**.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals ½in kit or ¼in kit. **£1** complete. State size.

All orders dispatched promptly.
All post paid

Shop and Trade enquiries welcome
Special Transfers made to order

E. R. NICHOLLS
P.C.B. TRANSFERS

DEPT. ETI 11
46 LOWFIELD ROAD
STOCKPORT, CHES. 061-480 2179

CALCULATORS

INCLUSIVE PRICES!!!
TEXAS INSTRUMENTS

- T133 sci **£11.95**
 - T125 L.C.D. sci/stats **£19.95**
 - T144 L.C.D. financial/stats **£31.95**
 - T145* electronic slide rule **£21.95**
 - T150 L.C.D. sci/stats **£22.95**
 - T11760 L.C.D. datacard **£19.95**
 - TI PROGRAMMER **£41.95**
 - T142* prog/finance/stats **£41.95**
 - T157* 50 step prog **£25.95**
 - T158* 480 step prog **£64.95**
 - T158C* with prog retention **£76.95**
 - T158* NAVIGATORIC **£99.95**
 - T159* 960 step prog the ultimate **£169.95**
 - PC100C printer for 58/59 **£142.95**
 - MATH/UTILITIES Library **£22.95**
 - APPLIED STATS Library **£22.95**
 - ELECTRICAL ENG. Library **£22.95**
 - MARINE NAVIG. Library **£22.95**
- *Including adaptor/charger

ELECTRONIC LEARNING AIDS

- Little Professor, 5 years up **£12.95**
- DATAMAN, 7 years up **£17.95**
- SPELLING B, 6 years up **£16.95**
- CASIO MATH PET, 5 years up L.C.D. **£19.95**

CASIO

- AQ2000 L.C.D. time/date/alarm/calc **£33.95**
- MELODY 80 L.C.D. musical alarm **£23.95**
- FX COLLEGE 80 L.C.D. sci **£15.95**
- FX3100 L.C.D. sci **£23.95**
- FX8000 as above plus alarm/stop **£28.95**
- FX202P **£35.95**
- FX501P L.C.D. 128 step prog **£46.95**
- FX502P L.C.D. 256 step prog **£64.95**
- FX5000EP mains sci plus printer **£129.95**
- FA1 Adaptor to cassette for 501/502 **£19.95**

CANON

- P10D portable print/display **£59.95**
- P1014D 10 digit print/display **£105.95**
- PHILIPS 0185 POCKET MEMO **£59.95**
- CALLSAVER Mk. 3 telephone answering m/c **£149.95**

Full range of TEXAS, CASIO, CANON, DECIMO, SHARP and IBICO calculators, plus PHILIPS dictation equipment supplied at lowest prices.

CALCULATOR SALES & SERVICE

ARROW WORKS, ARROW ROAD
REDDITCH B98 8NN
TEL: REDDITCH (0527) 43169

Car Audio

Manual MW/LW

Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

£10.25 + £1.00 Post

Push-Button MW/LW

One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

£15.95 + £1.00 Post

Stereo FM/Cassette + MW

Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at **£50 up**.

£40.95 + £1.00 Post

Stereo Speaker Set

Suitable for above stereo unit. Good quality in surface mounted casing, 5W nominal, 8W peak.

£4.00 (pair)

+ 70p Post

Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

£1.60 + 30p Post

Metal Detectors

Treasure Tracer Mk III

The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit. **£18.60 + £1.00 Post**
Built **£23.95 + £1.00 Post**

★ Induction Balance Model

Built with sensitivity up to 10 in on single coin; fitted with speaker and meter; PP3 battery; 7in dia search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is **£39.95!**

£24.50 + £1.00 Post

All goods guaranteed one year
10-day money-back offer. Goods
ex-stock at time of going to press
Callers by appointment only please
Send a s/e for illustrated leaflet

Minikits Electronics Ltd.
6d Cleveland Road
S. Woodford
London E18 2AN

ETI BOOK SERVICE

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

BEGINNERS

Beginners Guide to **Electronics** Squires £3.35
Beginners Guide to **Transistors** Reddihough £3.35
Electronic Measurement Simplified C. Hallmark £2.20
Electronics Self Taught Ashe £4.40
Beginners Guide to **Integrated Circuits** Sinclair £3.35
Principles of **Transistor Circuits** S. Amos £5.50
Understanding Electronic Circuits Sinclair £4.10
Understanding Electronic Components Sinclair £4.10
Beginners Guide to **Radio** King £3.35
Beginners Guide to **Audio** Sinclair £3.35

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00
Video Cookbook £7.00
TTL Cookbook £7.55
The Basic Cook £4.00 inc. p/p
IC Converter Cookbook £9.50

APPLICATIONS

Advanced Applications for **Pocket Calculators** I. Gilbert £4.20
Fire and Theft Security Systems B. Weis £2.00
How To Build Electronic Kits Capel £2.10
Linear Integrated Circuit Applications G. Clayton £5.40
Function Circuits Design & Applications Burr Brown £15.95
110 Electronic Alarm Projects R. M. Marston £3.95
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.95
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.95
110 Thyristor Projects Using SCRs R. M. Marston £3.95
Handbook of IC Circuit Projects Ashe £2.30
Practical Electronic Project Building Ainslie and Colwell £2.60
110 Wave Form Generator Projects R. M. Marston £3.95

TV AND HI-FI

Audio Handbook G. King £7.50
Cassette Tape Recorders J. Earl £5.25
Solid State Colour TV Circuits G. R. Wilding £7.30
Hi-Fi Loudspeakers and Enclosures Cohen £9.45
How To Build Speaker Enclosures Badmateff £3.90
Master Hi-Fi Installation King £3.45
Colour TV Servicing King £8.40

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £5.10
Practical Digital Design Using ICs J. Greenfield £12.70
Designing With TTL Integrated Circuits Texas Instruments £9.05
How To Use IC Circuit Logic Elements J. Streater £3.65
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.95
Understanding CMOS Integrated Circuits R. Melen £4.00
Digital Electronic Circuits and Systems R. M. Morris £3.50
MOS Digital ICs G. Flynn £5.10

COMPUTING

Microprocessors and Microcomputers B. Soucek £19.00
Microprocessors D. C. McGlynn £9.00
Introduction to Microprocessors Aspinall £6.40
Beginners Guide to Microprocessors £4.70
Beginners Basic Gosling £3.35

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £3.30
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £3.95
Experiments With Operational Amplifiers Clayton £3.40
Designing With Operational Amplifiers Burr Brown £16.65
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.40
Op-Amp Circuit Design & Applications J. Carr £4.00

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10
Test Instruments for Electronics M. Clifford £2.40
Working with the Oscilloscope A. Saunders £4.10
Servicing With the Oscilloscope G. King £6.50
Radio Television and Audio Test Instruments King £6.80

SERVICING

Electronic Fault Diagnosis Sinclair £3.20
Rapid Servicing of Transistor Equipment G. King £3.45
Tape Recorder Servicing Manual Gardner Vol. 1: 1968-70 £9.10
Vol. 2: 1971-74 £9.10
FM Radio Servicing Handbook King £5.45

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.50
Digital Signal Processing Theory & Applications L. R. Rabiner £23.80
Electronic Communication Systems G. Kennedy £8.50
Frequency Synthesis. Theory & Design Mannassewitsch £23.40
Principles of Communication Systems H. Taub £8.10

THEORY

Introduction to Digital Filtering Bogner £10.50
Transistor Circuit Design Texas Instruments £9.35
Essential Formulae for Electrical and Electronic Engineers N. M. Morris £1.65
Modern Electronic Maths Clifford £6.70
Semiconductor Circuit Elements T. D. Towers £7.40
Foundations of Wireless Electronics M. G. Scroggie £5.50
Colour Television Theory Hudson £6.20


REFERENCE

Transistor Tabelle (Includes physical dimensions) £4.10
Electronic Engineers Reference Book (Ed. 4) L. W. Turner £34.00
Solid State Circuit Guide Book B. Ward £2.25
Electronic Components M. A. Colwell £2.60
Electronic Diagrams M. A. Colwell £2.60
Indexed Guide to Modern Electronic Circuits Goodman £2.30
International Transistor Selector T. D. Towers New update £8.70
International FET Selector T. D. Towers £4.35
International Op-Amp Linear IC Selector Towers £7.50
Popular Valve/Transistor Substitution Guide £2.25
Radio Valve and Semiconductor Data A. M. Bell £3.45
Master Transistor/Integrated Circuit Substitution Handbook £6.20
World Radio TV Handbook 1978 (Station Directory) £8.00
Radio, TV and Audio Technical Reference Amos £30.00
TV Technicians Bench Manual (New Ed.) Wilding £5.10


MISCELLANEOUS

Integrated Electronics J. Milman £7.90
Microelectronics Hallmark £3.90
Practical Solid State DC Supplies T. D. Towers £6.20
Practical Triac/SCR Projects for the Experimenter R. Fox £2.25
Printed Circuit Assembly Hughes & Colwell £2.60

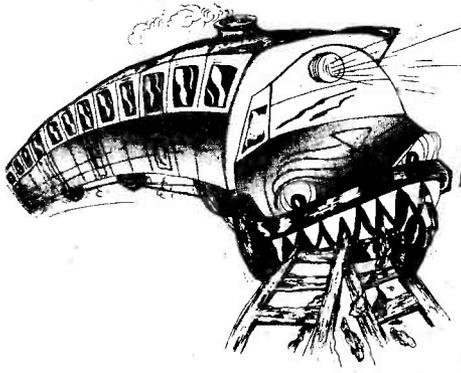Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy
way of getting your hands
on the right title.



MODEL TRAIN CONTROL SYSTEM

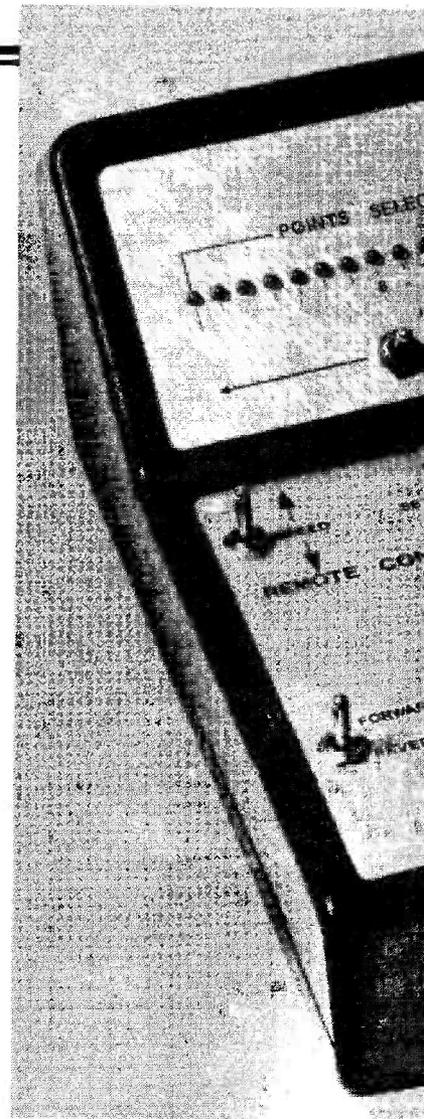

This month you can sink into your armchair and watch the locos locomote under the fingertip command of your remote controller.

Encoder/Transmitter

The major part of the encoder (Fig 2) circuit is wired up on a double-sided PCB, with the LED Readout circuitry implemented on an additional single-sided board. The display board is identical (apart from component numbering) to that used in the Train and Points-Controller units, and construction should present no problems.

The most important point to notice on the double-sided PCB is that wire-wrap IC sockets are used in the construction, to enable solder connections to be made to tracks on either or both sides of the PCB where necessary. All pin-throughs and other components that pass through tracks on both sides of the PCB should, naturally, be soldered to both tracks. Bearing these points in mind, construction should present few problems if the overlay is followed with due care.

When construction of the two boards is complete, you can temporarily interconnect the two circuits and

give them a functional check, in conjunction with the 'How It Works' section. The 16-LED display should be fully variable via Points Selector switch SW4. If you have a 'scope, you can check that the output waveform conforms to Fig 1 by triggering the 'scope via pin 9 of IC5.

When the boards have been given a functional check, fit the into a suitable box and couple them up to their controls and indicator LEDs. If you are

using a 2-wire control system, you will have to fit a couple of 6 volt cells into the controller to provide a 12V supply. In the 3-wire system, the 12V supply is derived from the decoder/data distributor unit via the third wire. You can, if you wish, fit the controller with an ON/OFF switch wired in series with the positive supply line.

On our prototype unit we used a 2-pole 4-way DIL switch in the SW1 'System Select' position, the switch is


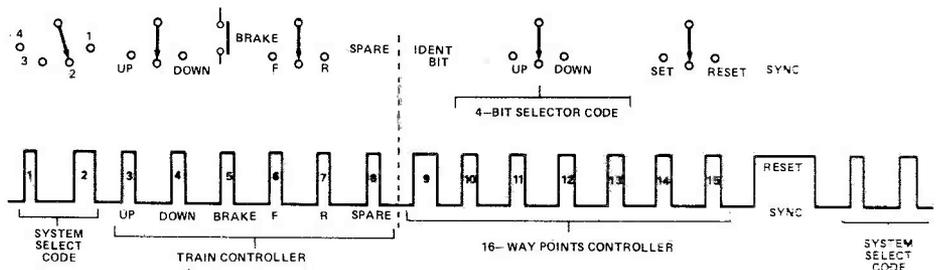


Fig. 1. The 15-bit 'simultaneous' code used by the remote control system.

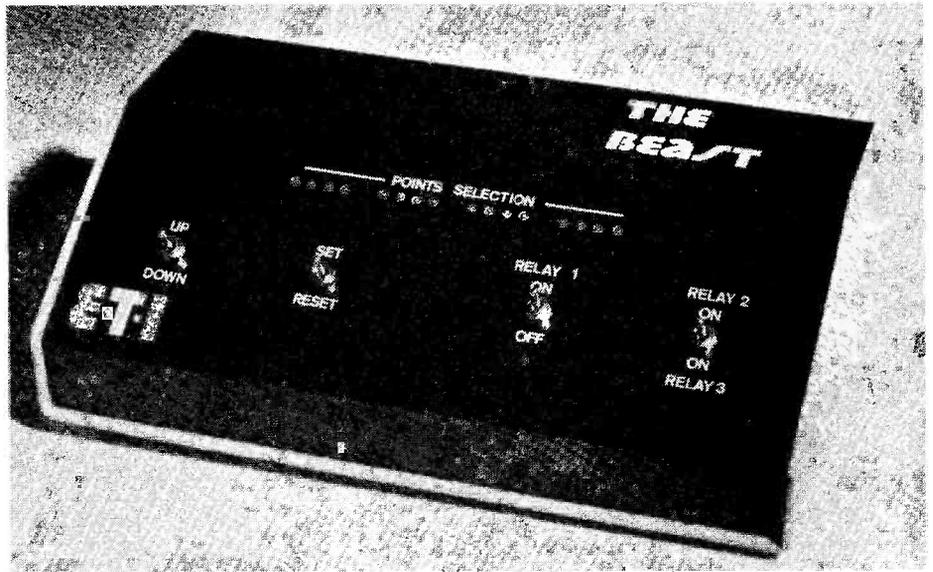

The points controller (above) can control up to sixteen sets of points or relays. It can activate several times per second. The set of points chosen is shown on the row of LEDs on the front panel. Think about your own particular points control needs before you start to build this unit. The data distribution unit is shown on page 91.

epoxied to the front panel. Our controller unit connects to the decoder/data-distributor unit via approximately 3.5 metres of 3-core coiled cable and a 3-pin DIN plug and socket.




The train controller (above) gives exceptionally fine speed control, from crawl to supersonic (well nearly). There's also a built-in track cleaner to keep things running smoothly.

The main power supply unit (below) has electronic overload on its output and can power up to four sets of track systems simultaneously.



REMOTE CONTROL ENCODER

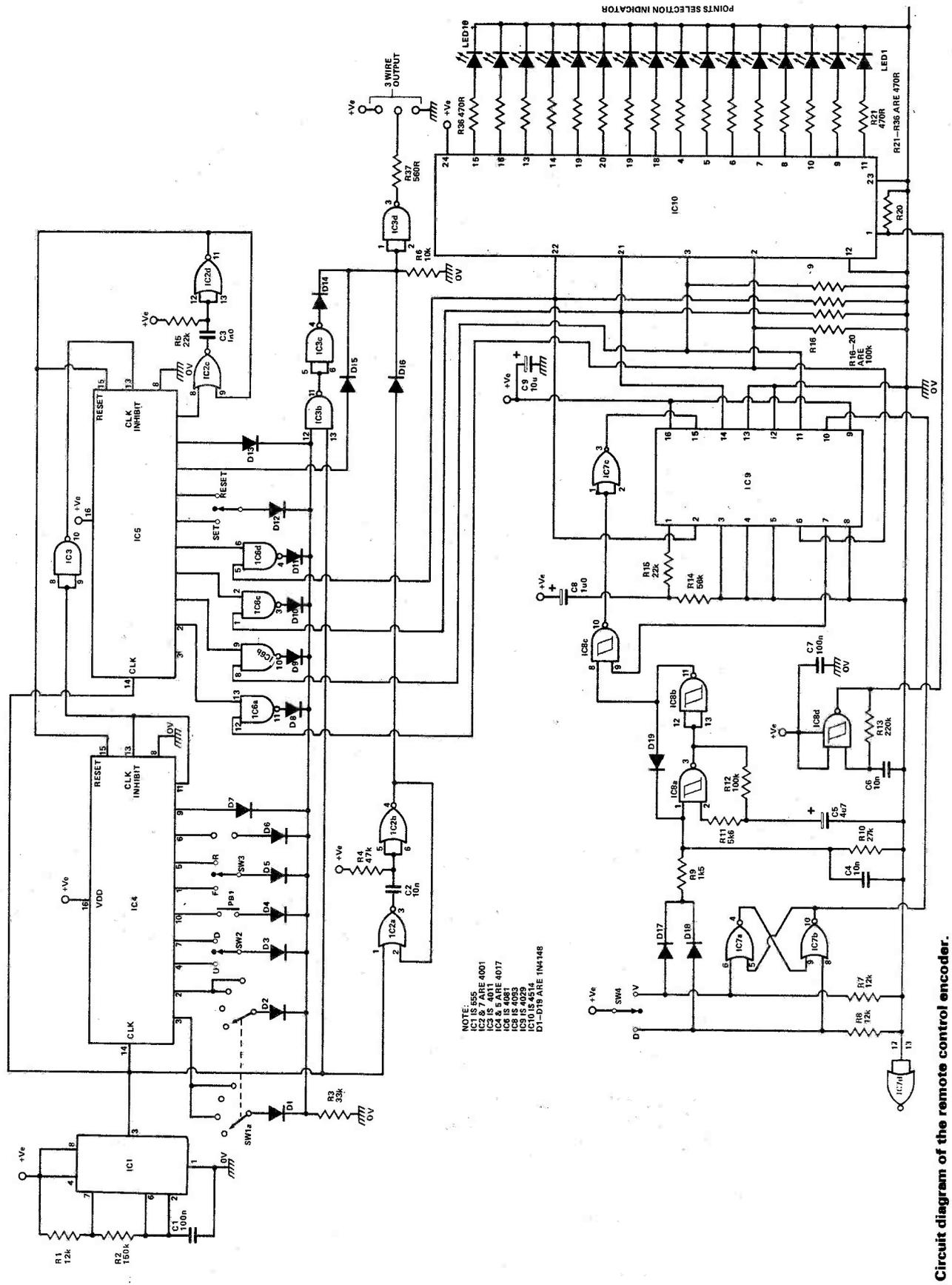

NOTE:
 IC1 IS 7414
 IC2 & 3 ARE 7410
 IC4 & 5 ARE 7400
 IC6 IS 7401
 IC7 IS 7404
 IC8 IS 7402
 IC9 IS 7403
 IC10 IS 7407
 D1-D13 ARE 1N4148

Fig. 2. Circuit diagram of the remote control encoder.

HOW IT WORKS

The circuit of the remote control encoder is shown in Figure 8. Here, IC1 and IC2, together with IC3 and IC4, are wired together as a 17-stage decade counter with 17 decoded outputs and are clocked at a 500 Hz rate via IC5. IC2a and IC2b form a monostable multivibrator that produces a narrow pulse on the arrival of each clock pulse and its outputs are fired with the outputs of the counter via D14-D15, D16 and R6, to form a serial chain of negative-going output pulses from R32.

Bits 10 to 13 of the code (derived via IC5) originate as the 4-bit outputs of up/down counter IC9, which functions in the same way as the Points Select counter of the F-6 Power Switch Selector circuit. The 4-bit output of IC9 is decoded and fed to a 4-bit LED display on the hand-held transmitter/encoder unit, to give the operator a visual indication of the number of the point that has been selected.

The optional remote-control system uses a serial 15-bit shift register IC8, as shown in Figure 7. The code comprises the fifteen bits, each influenced by 2.025

bits, a 3 nS reset or synchronizing pulse, all transmitted within a 30 kHz carrier. A narrow code bit, representing a '0' or '1', is represented by a wide code bit, representing a '1' or 'ON' logic state.

The five two bits of the code are used to select the desired (one of four) track system. Bits 1 to 5 are used to ensure the track is on that track. The remaining three bits are used to select and activate the (up to 16) points on that track system.

When the remote control system was being developed, we considered the possibility of using an ultrasonic, infra-red, or radio link between the transmitter/encoder and the receiver/decoder, but rejected all three systems on sound technical and/or ergonomic grounds. We finally settled on the use of a 3- or 3-wire flexible link, that can be simply plugged into any one of a number of jack sockets scattered around the house. We finally settled on the use of a two-wire control system, identical except that the 2-wire transmitter/encoder uses its own 1.2 volt battery supply, while the 3-wire unit derives its 1.2 volt supply from the receiver's battery unit.

PARTS LIST

R1, R2	10k	C1	100 polyester
R3	150k	C2	4.7 15V electrolytic
R4	33k	C3	100 15V electrolytic
R5, R5	47k	C4	100 15V electrolytic
R6	10k	C5	55
R7	10k	C6	4001
R8	10k	C7	4011
R9	10k	C8	4017
R10	10k	C9	4061
R11, R16-20	100k	C10	4093
R12	220k	C11	4029
R13	50k	C12	4514
R14	470k	C13	1N4148
R21, R2	500k	C14	1N4148
R22	500k	C15	1N4148
R23	500k	C16	1N4148
R24	500k	C17	1N4148
R259	500k	C252	1N4148
R260</			

PARTS LIST

R1	10K
R2	10K
R3	20K
R4	5K
R5	27K
R6	2K
R7	10K
R8	20K
R9	20K
R10	20K
R100	20K
C1	100n polyester
C2	100n polyester
C3	100n polyester
C100	100n polyester
D1	100n polyester
D2	100n polyester
D3	100n polyester
D100	100n polyester
ZD1	17V 400mA

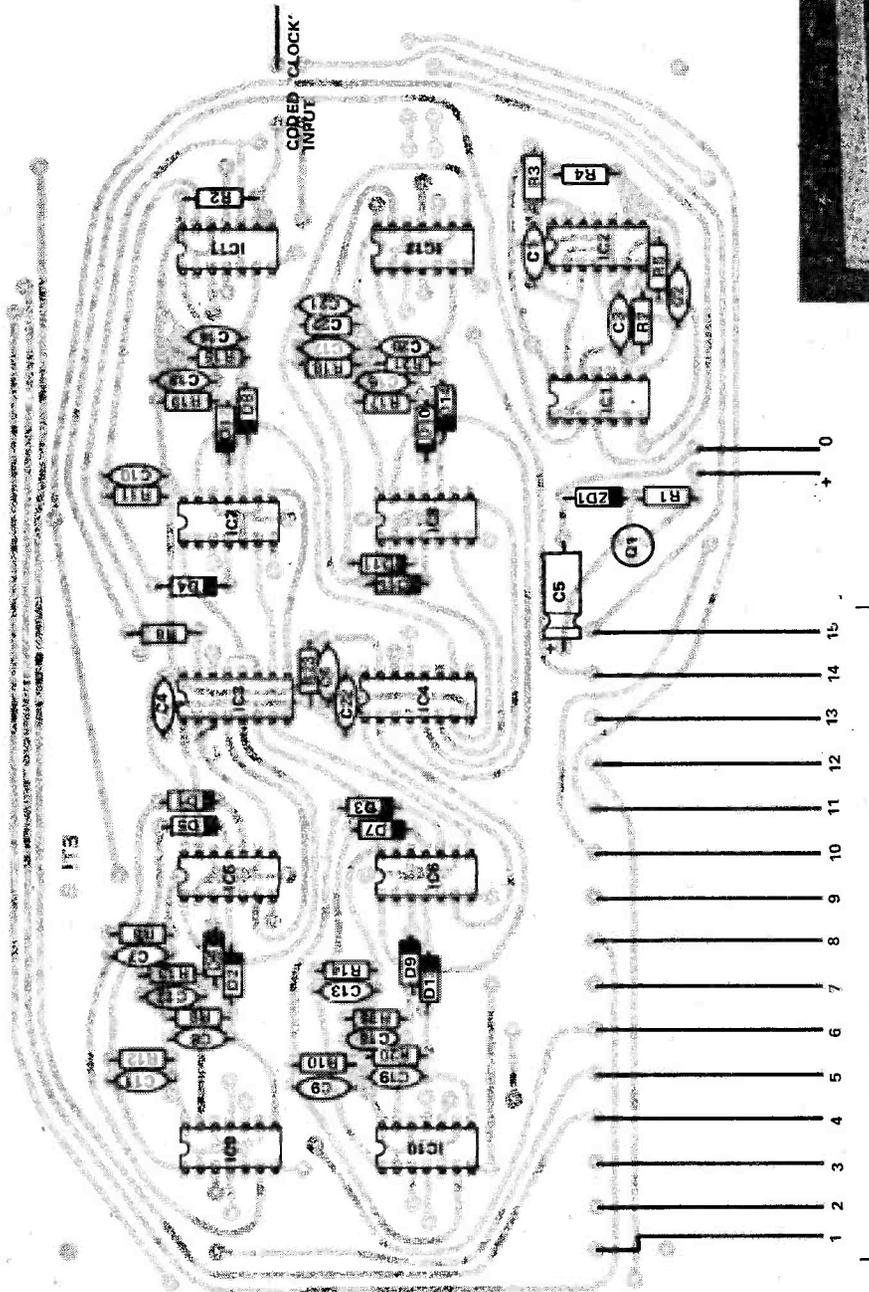


Fig. 5. Component overlay of the remote control decoder.


Remote Control Decoder

The complete decoder (Fig. 4) circuit is built on one double-sided PCB. This board uses conventional IC holders, and construction should present few problems if the overlay is followed with care.

When construction is complete, connect the board to an 18 volt power supply, connect the input signal from the encoder/transmitter, and give the circuit a full functional check in conjunction with the 'How It Works' sec-

tion. Should the circuit fail to work correctly, suspect (1) a wiring error, (2) a component failure, or (3) and out-of-tolerance component in one of the two monostables built around IC2.

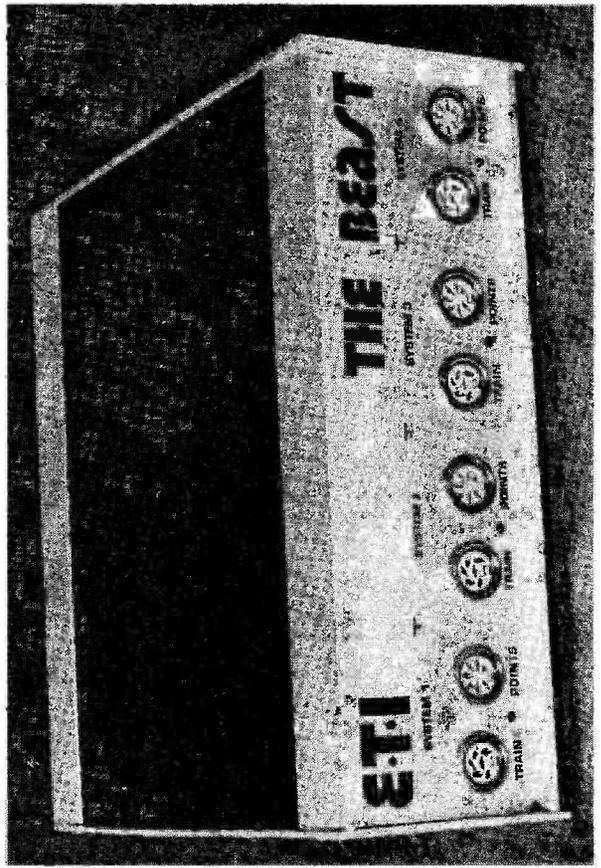The Beast is then complete and ready to use. If you want to get maximum value from the remote control facility, you can fit a three-wire 'ring' circuit around your complete model railway layout, with 3-pin DIN sockets wired into the ring at roughly 4 metre intervals, so that you can operate the remote controller from any position around the layout!





20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/2" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility. **£31.90** p&p £3.00

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4 to 15 ohms speakers. **£31.50** p&p £3.00

SPECIAL OFFER


30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge. **£57.00** + p&p £6.00

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audez tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance. **£18.25** Per stereo pair £3.65 p&p

BSR P200

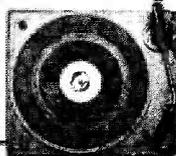Belt drive chassis turntable unit semi-automatic, cueing device. **£25.50** p&p £2.60
A D.C. QLM 30 Mk III Magnetic Cartridge to suit. **£7.95**




BSR Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **OUR PRICE £11.25** p&p £2.75

GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth. **£8.15** p&p £2.05 Size 12" x 8 1/2"

UNIT AUDIO STAND

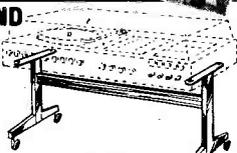Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors. **£3.95** £2.25 p&p 24" x 12 1/2" x 11 1/2" approx.



BARGAIN FOR PERSONAL SHOPPERS ONLY Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones. **£35.75** complete with speakers.

Micro Cassette Recorder Pocket size—home or office use or when travelling. **£14.25**

Battery operated fluorescent camping lamp. Runs off 8 U2 batteries. **£4.80**


Mullard

AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE

PRICE & AT OVER **25** PER PACK

SEE OUR PRICES

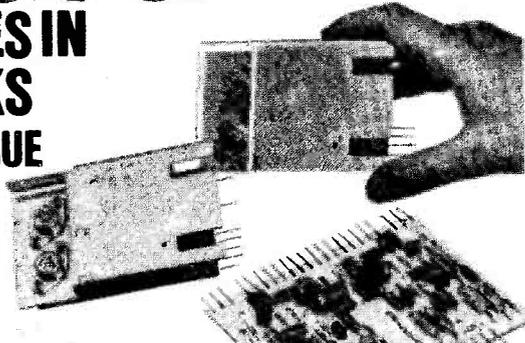- 1** PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £5.00** p+p £1.00
- 2** PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2. Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE £7.65** p+p £1.00



ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus £1.50 p&p


Two Way Speaker Kit

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" x 5" approx. 5 ohm mid-range tweeter with two 5 ohm mid-range crossover capacitors. **£4.05** per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT.

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit. Size approximately 9 1/4" x 8 3/4" x 4". **£12.25** p&p £2.25

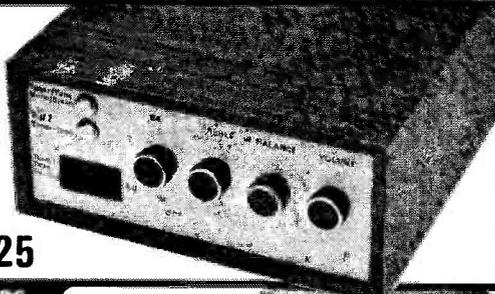

BARGAINS FOR PERSONAL SHOPPERS

- LCD Solar 5 function** with backlite stainless steel finish case and strap. **£7.40**
- LCD Solar Chrono 9 function** with backlite stainless steel finish case and strap. **£9.55**
- Chrono stop watch 9 function** with back lite stainless steel finish case and strap. **£8.95**
- Solar Alarm LCD** stainless steel case and strap. **£21.95**
- AM/FM DIGITAL CLOCK RADIO** Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer. **£12.20**



100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/4" Brushed aluminium fascia and rotary controls. Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **£66.45** p&p £4.05



50 WATT MONO DISCO AMP

Size approx. 13 3/8" x 5 1/4" x 6 3/4" 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. **£30.60** p&p £2.70




- 100 Watt Power Amp Module **£14.25**
- Mains power supply for above unit **£3.60**
- DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers **£20.45**
- 'VIDEOMASTER' Super Score TV Game with pistol mains operation **£15.95**
- PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock, LW, MW, SW, VHF mains/battery operation **£42.90**
- ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. **£24.50**

FOR PERSONAL SHOPPERS ONLY

DUO II SPEAKERS

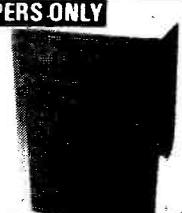Attractive teak finish, modern design, incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz Impedance 8 ohms Power 15 watts RMS 18 1/2" x 13 1/2" x 7 1/2" Per stereo pair approx. **£16.50**



FOR PERSONAL SHOPPERS ONLY

STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95** Size approximately 47" x 15 1/2" x 15"



323 EDGWARE ROAD, LONDON W2
21E HIGH STREET, ACTON W3 6NG
ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%

All items subject to availability. Price correct at 15.10.79 and subject to change without notice

NOTE: Persons under 16 years not served without parent's authorisation.

TOUCH SWITCH

A unique relay-output bistable touch switch that works on the capacitive loading principle. It uses a single touch contact, and is unaffected by moisture and dirt.


Most touch switch circuits published in recent years use a pair of metal contacts as sensors. When human skin resistance bridges these contacts, a readily-detectable indication of the touch action is given. A major problem with this type of circuit is that, since it is simply a resistance-sensing system, it can easily be disabled by any conductive medium, such as dirt or moisture, that bridges the contacts.

The ETI touch switch does not suffer from this problem. It is activated via the capacitive loading that occurs when a person touches or is 'coupled' to a single sensor contact. This contact can take any one of a large variety of forms. It can be a piece of metal the size of a pin head, or a piece of wire with a length variable from a fraction of a centimetre to several metres, or a large plain or highly decorated metal plate or printed circuit board. In the latter two cases, the plate or board can even be covered in an insulating material, such as plastic or varnish, since it is not necessary to actually touch the metal of the sensor to cause circuit operation, but merely to be capacitively coupled to it.

Our touch switch has a relay output and gives bistable operation. If you 'touch' the sensor contact once, the relay turns on and latches into that state until the next time you touch the sensor, at which point the relay turns off. You can use the relay contacts to control house lights, etc, in which case you get alternate touch-ON, touch-OFF, touch-ON, etc, operation.

Construction And Use

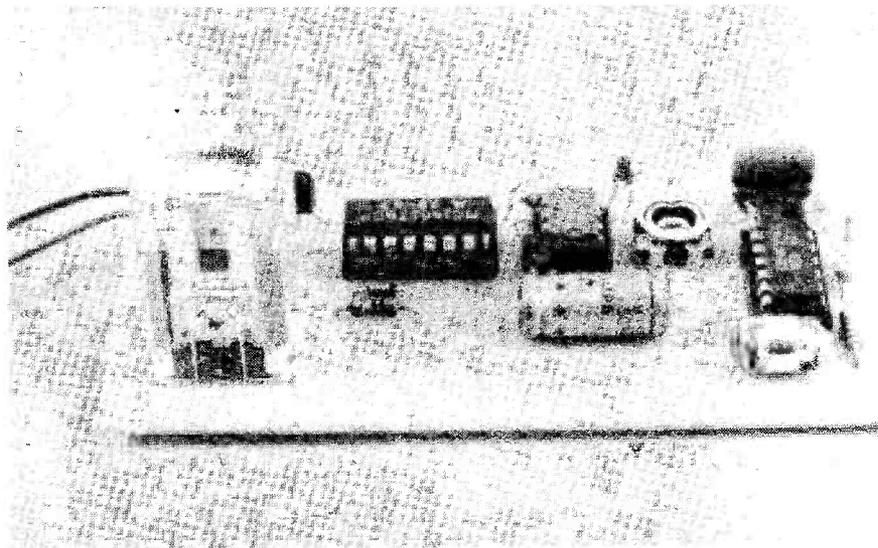All electronic components are mounted on a single PCB, leaving only the battery and relay output con-



nections and a single lead to the touch pad to be soldered, so you should have no trouble in construction. Use IC sockets and double check that all semiconductors are inserted correctly before initial switch on. When construction is complete, connect a suitable touch pad (a length of wire, or a metal plate, etc) in place, connect up the relay and apply power to the circuit.

Initial setting up of the circuit is quite simple, but is necessary whenever a different touch pad is connected to the unit. Turn the present pot fully anti-clockwise and then, with the touch pad untouched, adjust the pot clockwise until LED 1 just comes on and the relay is heard to operate. Note the setting of the pot. Now touch the sensor pad firmly, and turn the pot slowly anti-clockwise until the LED just goes out. Note the new setting of the pot. Release the touch pad and adjust the pot to half way between the two settings. You should now find that the LED and relay activate whenever you touch the sensor and that the LED turns off again (but the relay does

not) when the sensor is released. This setting up procedure gives an optimum sensitivity/stability performance.

Scope For Proximity

There is plenty of scope for experimenting with this circuit. If a touch pad with a large surface area (a metal plate or an area of foil) is used and the circuit is set for maximum sensitivity, it will act as a proximity switch. The proximity range can be maximised by taking the negative supply line of the circuit to earth via the mains ground line.

You'll notice from the circuit diagram that only one half of dual J-K flip-flop IC3 is used. Consequently, if you want to make two touch switches and are capable of doing a little of your own design work, you can make the second switch by simply duplicating the C2, rectifier, and IC2 circuitry, using the spare half of IC3, and feeding the new C2 from the output of the existing IC1 oscillator circuit.

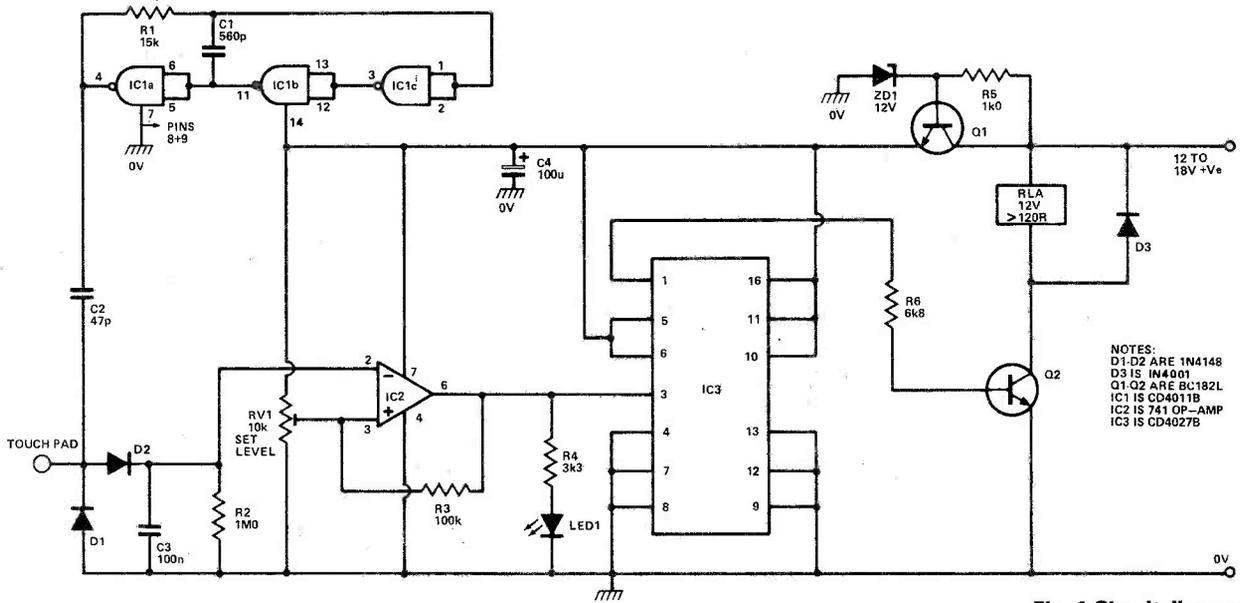


Fig. 1 Circuit diagram.

HOW IT WORKS

IC1 forms an astable multivibrator clocking at a frequency in the region of 100 kHz. Capacitor C1 forms a capacitive voltage divider effect with stray capacitance of the touch pad, which, after rectification via D1 and 2, charges capacitor C2. This voltage varies according to the capacitance of the touch pad, which in turn varies as it is touched. The voltage across C2 is, therefore, dependent on whether the touch pad is touched or not.

IC2 forms a comparator, using only a small amount of positive feedback, which compares the voltage across C2 with that from the wiper of level preset RV1. As the voltages cross, upon touching the pad, the output of IC2 goes high and LED 1 lights. Preset RV1 can be adjusted to suit any form of touch pad.

The output of IC2 is fed to the clock input of IC3, a dual JK type flip-flop. This device output changes state ie on/off or off/on, with every pulse input and consequently turns the relay on and off via transistor switch Q2.

Transistor Q1 forms a series pass regulator with R5 and ZD1 to maintain a stable voltage for the main part of the circuit, so that the delicate balance is not upset with variations in applied voltage.

BUYLINES

There should be no problems in obtaining any components for this project.

PARTS LIST

RESISTORS All 1/4W, 5%

R1	15k
R2	1M0
R3	100k
R4	3k3
R5	1k0
R6	1k0

POTENTIOMETER

RV1	10k min horiz preset
-----	----------------------

CAPACITORS

C1	560p polystyrene
C2	47p polystyrene
C3	100n polyester
C4	100u 16V electrolytic

SEMICONDUCTORS

IC1	4011
IC2	741
IC3	4027
Q1,2	BC182L
D1,2	1N4148
D3	1N4001
ZD1	12 volt 400mW
LED 1	TIL 220 or similar

MISCELLANEOUS

12V relay 120R coil or greater

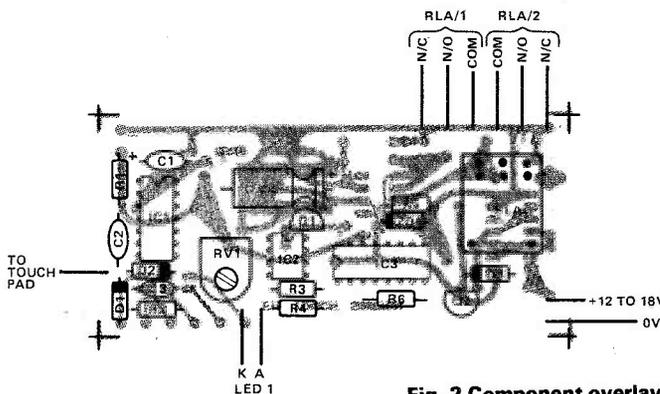


Fig. 2 Component overlay.

Codespeed Electronics

PO BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, PO3 5BJ

ELECTRONIC MAIL ORDER SPECIALISTS

New, Full Spec. Devices

LED WRISTWATCH I.C. Super value I.C. in 24 pin 'legless flatpack' style package for maximum space saving. With data A snip at only 99p. Cat. No. 208
0.1" LED WRISTWATCH DISPLAY. Also in a 'legless flatpack' style package. This display matches the wristwatch I.C. shown above. With data. Only 99p. Cat. No. 209
CASH SAVER Purchase one each of catalogue numbers 208 AND 209 for only £1.50.
POLARIZING FILTER MATERIAL 0.006" thick plastic film. Any size cut - even 1 sq. inch. Max. width 19". Any length. Only 2p per sq. inch. Cat. No. 701
BRIGHT ORANGE DISPLAY 9 digit, 7 segment gas discharge display. 0.25" high digits. With data 75p. Cat. No. 310
OMM CHIP MM5530 dvm chip. Builds into high accuracy dvm or panel meter. Requires additional circuitry. Supplied with data and circuit. Only £3.95. Cat. No. 404
MINI 6 DIGIT LED DISPLAY 6 digit, 7 segment display from Texas. Common cathode, multiplexed, with 0.1" digits. £1.00. Cat. No. 306
MM5314 CLOCK CHIP A super value digital clock chip for only £1.99. With data. Cat. No. 207
4 DIGIT LCD A high contrast, easy to solder display with four 0.5" high non-multiplexed digits. £6.99 each with data. Cat. No. 206
DIGITAL ALARM CLOCK MODULE Complete with giant 0.84" LED display. Add transformer and switches for complete clock. With data only £6.50. Cat. No. 205
GIANT LED DISPLAY Common cathode, non-multiplexed super 4 digit LED clock display. Lots of other uses too. Only £3.95 each. Cat. No. 204
WRISTWATCH LCD A high contrast 3 1/2 digit wristwatch LCD with centre colon. Supplied with polarizers and data. Only £1.00. Cat. No. 202
MEMORIES MM2102 static 1024 bit memories. A snip at 99p each. With data sheet. Cat. No. 102
20 KEY KEYBOARDS Calculator keyboards, excellent key action. 20 keys per board. 2 keyboards for £1.00. Cat. No. 101
PROGRAMMABLE UNIJUNCTIONS Four MEU21 PUT S (similar to 2N6027). Makes long delay timers, oscillators, etc. With data and applications sheet. 4 for 50p. Cat. No. 402
HYBRID CIRCUITS 8 resistors and 8 capacitors built into each hybrid circuit. Ideal values for semiconductor circuits. Excellent for minimizing PCB component space. 10 Hybrids for 50p. Cat. No. 801
 25 germanium diodes 50p. 10 switching diodes 35p. Mini slider switches (2 pole change-over) 16p each. Momentary switches (spring loaded) with 1 n.o. contact 15p each. Mono jack sockets 23p each. Stereo jack sockets 25p each. Slide control knobs (state colour) 12p each. Rotary control knobs (push-on). Black with coloured cap (state colour) 20p each.

Untested Items

REJECT CALCULATORS Production line rejects. Yields lots of goodies when stripped down (not much wrong with some we tested). Only £2.50 each. Cat. No. 104
LED DISPLAYS (Untested - no guarantee) 10 seven segment LED displays. 0.127" digits common cathode. 10 for £1.00. Cat. No. 311.

Postage and Packing please add 35p

(Overseas orders add 90p)

Satisfaction guaranteed or return for replacement or refund

Send medium sized S.A.E. for your free copy of our new Autumn Catalogue (Issue No. 6)

CODESPEED'S DESIGN, DEVELOPMENT AND PRODUCTION TEAMS ARE ALSO AT YOUR SERVICE FOR QUANTITY/BATCH PRODUCTION.

Now, complete your system!



Citronic MM313 Mixer
 Ideal for the DIY enthusiast building up a complete disco system 4/8 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £89.70

The ultimate range of speakers

We carry a great selection of high quality chassis for the DIY speaker constructor. 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.80, or our fabulous Piezo Horns which handle a 6K - 20K frequency range in any PA system up to 100W (No X over required) and cost only £6.32 each.




Projectors

Come and see our specially selected projectors from £50.60 (Issue Multi-fact 150) to £83.37 (Tutor IIE DDU) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



Turntables

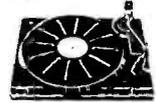

Our unsurpassed Disco accessories has enabled us to select the best turntables for your requirements. For example the new BSR 1200 belt drive. ONLY £79.75

Roptlights

Great effect at discos. 7 metres long. Multiway connectors. 4 channel. £46.00 (inc. pack of spare bulbs)

Buigin Octal plugs and sockets

There's always hundreds of Buigin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. #552 SOCKET 10.69. #551 PLUG £1.72

Multiway Cables
 4 core (6A) 63p/metre
 5 core (6A) 78p/metre
 6 core (6A) 92p/metre

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

PERSONAL CALLERS ONLY

Roger Squire's
 DISCO CENTRES
 ALL SHOPS OPEN TUE-SAT
 LATE NIGHT WED
 (UP TO 8 PM)
 LONDON 176 Junction Road, N19, 150yds. Tottenham Park, Tube Station. Tel: 01 272 7474
 BRISTOL 129 Church Road, Redfield House, St. George's, 1 mile from end of M32. Tel: 0272 560550
 MANCHESTER 251 Deansgate, 15 mins from City Centre. Tel: 061 831 7676
 GLASGOW 1 Queen Margaret Road, off Ocean Margaret Drive, Kilmarnock 20, just behind the BBC. Tel: 041 946 3303

Now Converted to 50Hz for UK TV's!

SUPERBOARD II

£188 + VAT


Full 8K basic and 4K user RAM
 Built and tested

Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers
- 4K static RAM on board expendable to 8K
- Full 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory (besides 4K user memory), features uppercase, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters

Extras

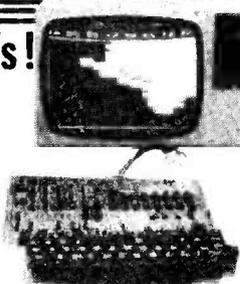- Power Supply & modulator £29.50 + VAT
- 610 Expansion board with 8K ram and dual drive miniflopp chip £188 + VAT
- 1P CD3P minifloppy disk, cased and with power supply £312 + VAT
- Injection moulded case within 6 weeks
- 4K Ram upgrade kits £35 + VAT



We are dealers for the rest of Ohio scientific range of computers. The widest range produced by any micro-computer manufacturer, this includes:-

- C2-4P A professional 4K basic in-ROM computer cased and with power supply
- C2-8P DF A 32K basic in ROM computer with dual 8" floppydisk drives for serious personal and small business use
- C3-DEM A 32K computer with 3 micro-processors (6502, 6800, Z80) and dual 8" floppy disk drives

Full business, word processing and cate base management is available for all disk based systems.

Write for catalogue for further details

Software

Tapes at £5.50 + VAT

Homonyms*, Counter*, Trig Tutor, Bar Graph, Definite Integral, Basic Math, Presidents*, Powers, Electronics Equations, Spelling Quiz, Solar System, Continents, Add Game, Math Intro, Base Ten Converter, Math Blitz*, Inventory Demo, Ratio Analysis, Advertisement, Statistics I, Salary Demo*, Annuity I, Annuity II, Interest on Loans, Loan Finance, Uneven Cash Flows, Personal Destroyer, Hide & Seek, Star Wars, Black Jack, New York Taxi, 23 Matches, Lander*, Etch-a-Sketch, Space War*, Battleship*, Cryptography.

Tapes at £7.30 + VAT:-

Hangman, Mathink, Trend Line, Straight & Constant Depreciation, Address Book*, Checking Account, Savings Account, Bio-rhythm, Hectic.

Tapes at £11.00 + VAT:-

Word Processor**, Programmable Calculator, Tiger Tank

Basic Tutor Tape:- £26.40+VAT

Assembler editor with Manual £25 + VAT

Extended monitor with Manual £10 + VAT

OTUS SOUND

4 MORGAN STREET
 LONDON E3 5AB


TELEPHONE: 01-981 3993
 TELEX: 261426 ATN. LOTUS SOUND

FLASH TRIGGER

Fascinating freeze frame photos from frenetic action with our phenomenal flash trigger.

If raindrops keep falling on your head, now is the time to build ETI's fabulous flash trigger and catch them bouncing back. See astounding shapes as everyday objects perform a dynamic ballet (Usually too fast for the unaided eye to see).

Of course, you will need a camera and a flash gun. However, even the cheapest electronic flash guns usually have a flash duration of one thousandth of a second or less — fast enough to catch drops of liquid performing their complex aerobatics or freeze a shattering light bulb. If you want to stop a humming bird in flight or investigate instant insects then you will probably have to look elsewhere for your equipment. The attraction of this unit is that it needs no fancy ancillary equipment; you don't need an SLR, just a simple camera whose shutter can be locked open and something to photograph. With a powerful flash gun, even a pinhole camera will do!

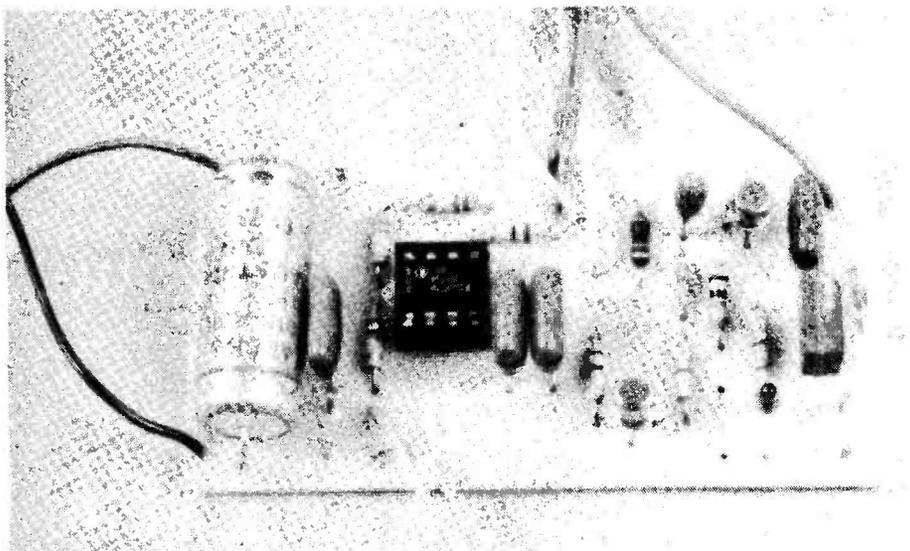

SCR1. Check polarity with a voltmeter but carefully as there may be several hundred volts present.

In use, the unit is switched on and adjusted until it triggers reliably from the chosen sensor. Set up your


camera according to the guide table supplied with the flash. Remember that the apertures given relate to the flash-to-subject distance. Place your camera for the best picture (open the shutter) and enjoy instant exposure!

Construction

The unit is assembled on one PCB with flying leads connecting the controls. Power is supplied by a PP3 battery or any nine volt DC source.

There are no links to make on the board and none of the components are sensitive to static electricity or otherwise delicate making this an attractive project for assembly by a beginner or student.

A socket is recommended for IC1. These chips do not often fail but it can be infuriating to have to desolder one of you suspect it. In any case, a socket removes any chance of damage from excessive heat. The only point to watch is the orientation of the semiconductors. Use the ones specified; they're cheap and readily available. Make sure you connect the flash gun the right way round across

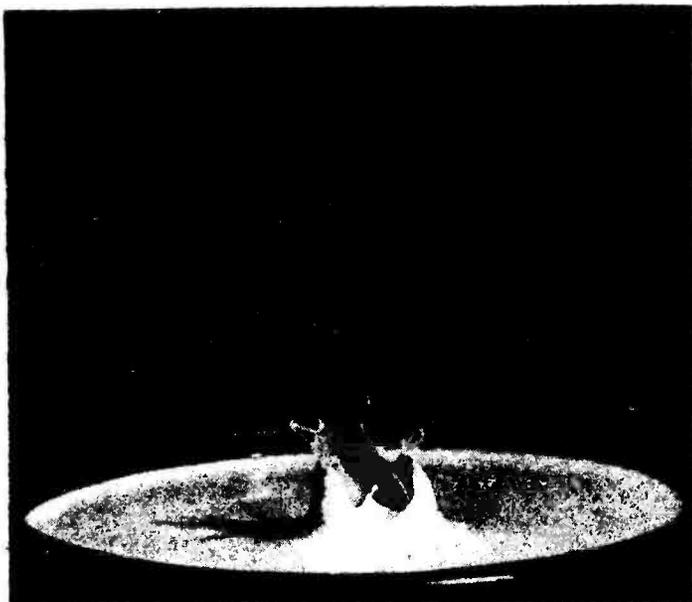

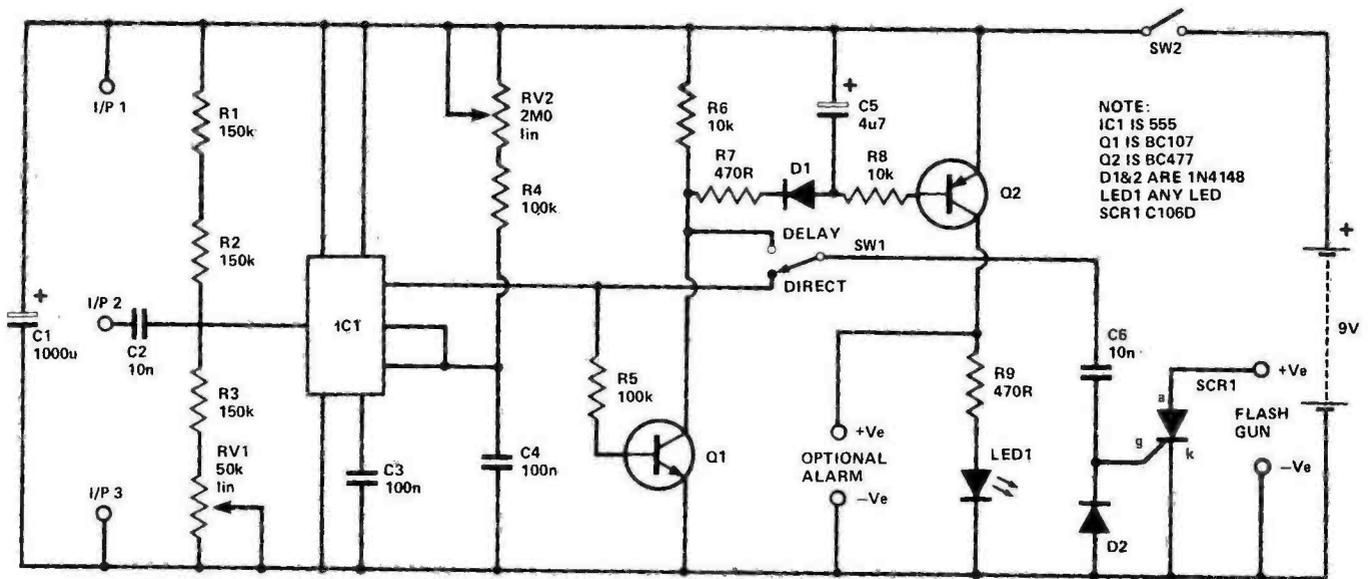


Fig. 1. Circuit diagram for the Flash Trigger project,


HOW IT WORKS

IC1 is a 555 timer connected in the monostable mode. The timing period is determined by RV2, R4, C4 and is adjustable between 11mS and 231mS with the values shown. The trigger input of the chip is held just above its firing potential of one third supply voltage by adjustment of RV1 which acts as a sensitivity control. A negative-going signal is coupled to the input by capacitor C2. Note that the values of R1,2,3,RV1 provide a medium input impedance and screened cable may be required when the sensor must be separated from the unit.

When IC1 is 'fired', its output (pin 3) goes high for the monostable period. With SW1 switched to 'direct', this positive going pulse will fire the SCR and discharge the flash enabling the unit to be used as a slave flash. There will be a finite delay owing to rise time of phototransistor response, propagation delay within IC1 and rise time of its output. However, this will be measurable in microseconds and should be negligible.

When used in the 'delay' mode, the output pulse is inverted by Q1 causing the flash to fire on the trailing edge of the monostable pulse. To avoid repeated use of the flash when setting up the unit, indicator LED 1 is provided. Each negative excursion of Q1 collector causes C5 to charge via R7, D1 effectively stretching the monostable pulse and providing a clearly visible flash. An optional alarm; for example a solid-state-buzzer, can be connected into the circuit providing audible indication of triggering. C1 provides overall decoupling. Supply current is about 10mA.

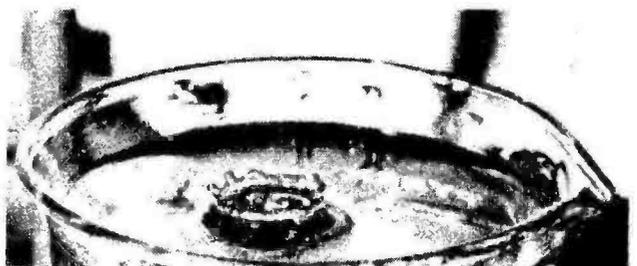Below: what to do with it once you've built it. Taken with an ET1 Flash Trigger.



PARTS LIST

RESISTORS All 1/4W, 5%

R1,2,3	150k
R4,5	100k
R6,8	10k
R7,9	470R

POTENTIOMETERS

RV1	50K lin
RV2	2M lin

CAPACITORS

C1	1000u electrolytic
C2,6	10n polyester
C3,4	100n polyester
C5	4u7 tantalum

SEMICONDUCTORS

IC1	555
Q1	BC107
Q2	BC477
SCR1	C106D
D1,2	1N4148
LED 1	any LED

MISCELLANEOUS

SW1 SPDT SW2 SPST PCB
flash-gun-connector, photo-
transistor, crystal mic. 9V battery

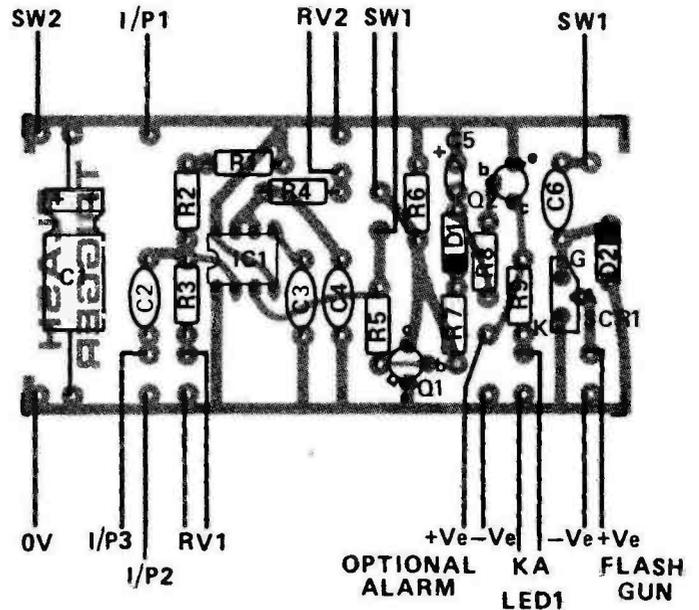


Fig. 3. Component overlay.

C106D



TIL78



BUYLINES

The electronic components will be available from major component suppliers. A suitable flash gun connector should be obtainable from photographic equipment dealers.

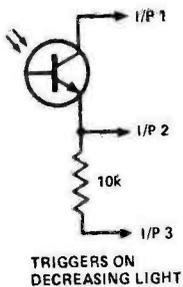
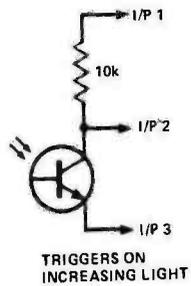


Photo transistor is TIL78

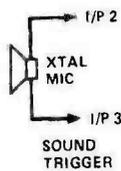


Fig. 2. Wiring details for different triggers.

