

# electronics today


INTERNATIONAL

JULY 1980 60p



**STEREO IMAGE CO-ORDINATOR**  
Move Your Sound Around

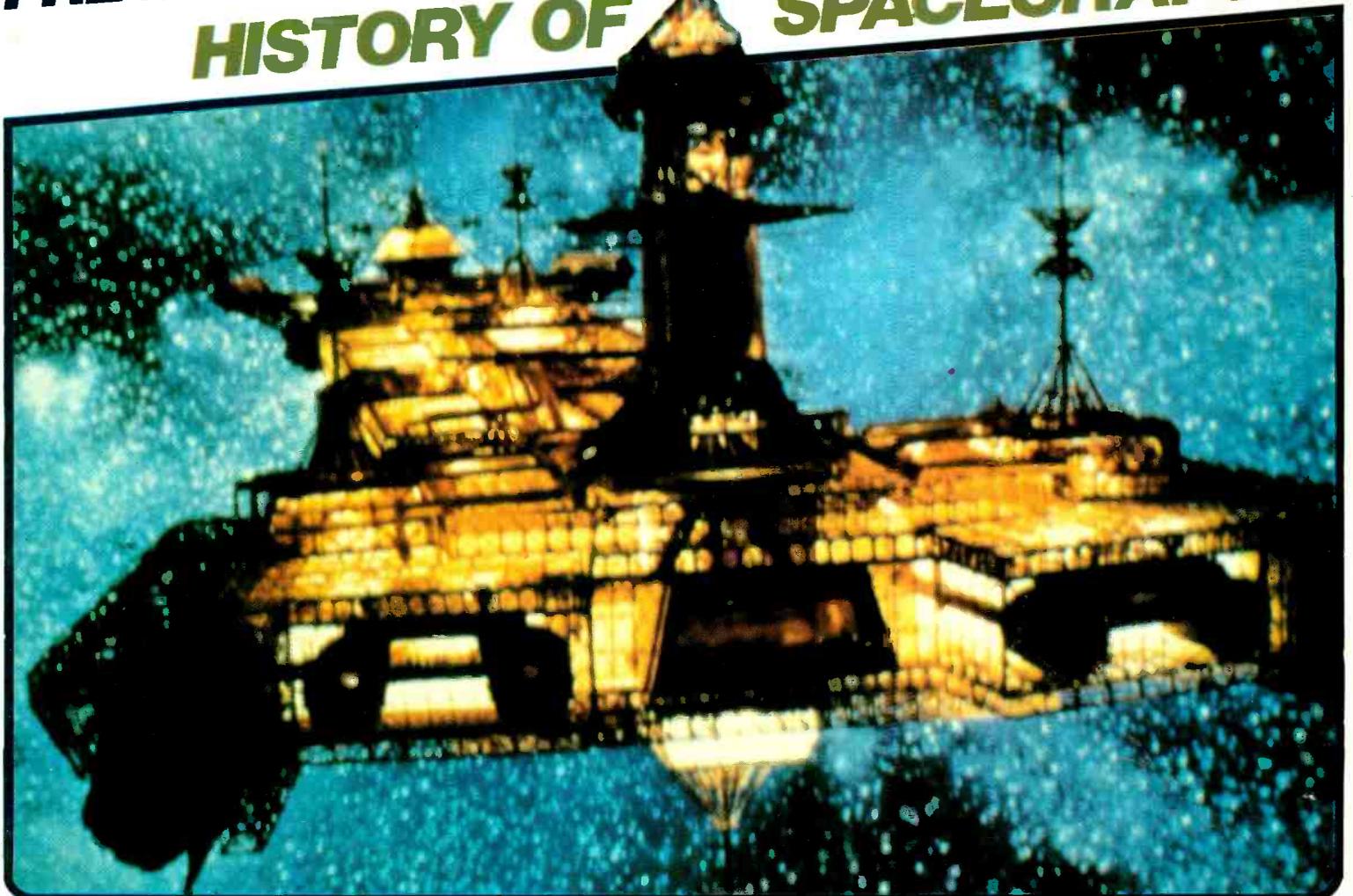**DESIGNING ACTIVE FILTERS**  
**LOUDSPEAKER PROTECTION UNIT**  
**FREQUENCY METER**  
**HISTORY OF**  
**TIME CONSTANTS?**  
**SPACECRAFT**



... NEWS ... PROJECTS ... MICROPROCESSORS ... AUDIO ...

# TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

All kits also available as separate packs (e.g. P.C.B., component sets, hardware sets, etc.). Prices in FREE CATALOGUE

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an affective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal trim!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price!

**COMPLETE KIT  
ONLY  
£168.50 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)


**INCREASED CAPACITY AT OUR BIG NEW FACTORY  
MEANS MANY PRICES DOWN! ALL OTHERS FROZEN!**

**WE'VE MOVED!  
NEW FACTORY UP!  
PRICES DOWN!**
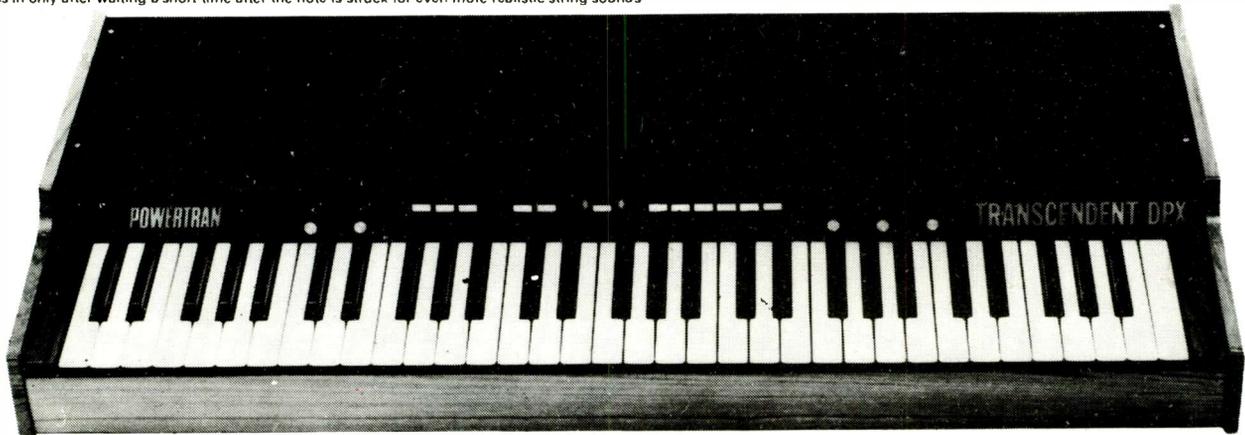
# TRANSCENDENT DPX

**DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER  
ANOTHER SUPERB DESIGN BY SYNTHESIZER EXPERT TIM ORR — PUBLISHED IN ETI**

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

**COMPLETE KIT ONLY £299.00 + VAT!**

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing etc., etc.)

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc. even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1,200!

**POWERTRAN**

**ORDERING INFORMATION AND MORE KITS  
INCLUDING THE BLACK HOLE ON PAGE 9**



# electronics today

JULY 1980 VOL 9 NO 7 **INTERNATIONAL**

## FEATURES

- DIGEST 8 If it matters it's here.
- DESIGNING FILTERS 17 Do it yourself it's easier!
- HISTORY OF SPACEFLIGHT 24 What goes up...
- ANTI-MATTER EXPLAINED 32 NOTHING to do with Star Trek
- DESIGNERS NOTEBOOK 37 A flash of LED knowledge.
- AUDIOPHILE 43 Atomic theory amplifier?
- TIME CONSTANTS 49 Have you the capacity for this?
- MICROFILE 53 Sinclair ZX 80 examined.
- TECH-TIPS 57 This is all your fault!
- RAVEN ON 63 News from around the world

## PROJECTS


- IMAGE CO-ORDINATOR 68 Moving sound reproduction?
- PORCH LIGHT 77 Don't be left out in the dark.
- STATE VARIABLE FILTER 84 Two for Project 80 synthesisers.
- ENVELOPE SHAPER 88
- LOUDSPEAKER PROTECTOR 95 Cone preservation device.
- FREQUENCY METER 99 Linear cycle counter.

## INFORMATION

- A RECORD NEW OFFER 13 Some cheap discs to slip.
- ETI NEXT ISSUE 15 Next months machinations.
- ETI SPECIAL OFFER 41 Seek Seikos here.
- SUBSCRIPTIONS OFFER 61 Buy 1980, get 1999 FREE!!
- BINDERS 61 Keeping it all together.
- ETI BOOK SERVICE 81 Fine print indeed.
- ETIPRINTS 92 No other way is worth it.
- PCB FOIL PATTERNS 103 Board level decisions.



Image co-ordinating p.68

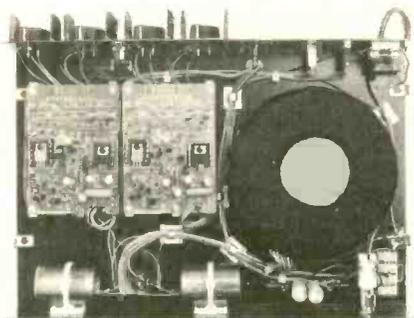

Quantum sounding off p.43

### OVERSEAS EDITIONS

- AUSTRALIA : Roger Harrison  
Editor
- CANADA : Halvor Moorshead  
Editor
- GERMANY : Udo Wittig  
Editor
- HOLLAND : Anton Kriegsman  
Editor



Member of the  
Audit Bureau  
of Circulation

EDITORIAL AND ADVERTISEMENT OFFICE  
145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5

Ron Harris B.Sc.  
Ian Graham B.Sc.  
Tina Boylan  
Diego M. Rincon  
Dee Camilleri, Enzo Grando,  
Lorraine Radmore, Lorraine Stout  
Paul Edwards, Tony Strakas,  
Ray Marston  
John Fitzgerald  
Steve Ramsahdeo  
Christopher Surgenor  
Steven Rowe  
Sandie Neville  
T.J. Connell

Editor  
Assistant Editor  
Editorial Assistant  
Art Director  
Production

Technical Illustrators  
Project Editor  
Project Engineers  
Project Development  
Group Advertisement Manager  
Advertisement Manager  
Advertisement Production  
Managing Director

PUBLISHED BY  
DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road, WC2  
Argus Distribution Ltd. (British Isles)  
12-18 Paul Street, London  
Gordon & Gotch Ltd. (Overseas)  
QB Limited, Colchester

PRINTED BY

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

©MODMAGSLTD. 1980 All material is subject to worldwide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

# WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
 MAIL ORDER, CALLERS WELCOME  
 Tel. Watford (0923) 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 40p TO ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type.  
 400V: 1nF 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 48p; 1µF 64p; 2µ 282p.  
 160V: 10nF, 12n, 39n, 100n, 150n, 220n 11p; 330n, 470n 19p; 680n, 1µF 22p; 2.2µ F32p; 4.7µ F36p.  
 1000V: 10n, 15n, 20p, 22n 22p; 47n 26p; 100n 38p; 470n 53p; 1µF 175p.

**POLYESTER RADIAL LEAD CAPACITORS: 250V:**  
 10n, 15n, 22n, 27n 5p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p, 470n 17p; 680n 19p; 1µ 22p; 1.5µ 30p; 2µ 34p.

**FEEDTHROUGH CAPACITORS:**  
 1000pF/350V 8p

**ELECTRONIC CAPACITORS:** (Values are in µF) 500V: 10 50p; 47 78p; 250V: 100 85p; 83V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8p; 10, 15, 22, 11p; 32, 47, 50, 12p; 63, 100, 27p; 50V: 50, 100, 220, 25p; 470, 32p; 1000, 60p; 40V: 2.33, 8p; 10, 12p; 2200, 3300, 85p; 4700, 98p; 35V: 10, 33, 7p; 330, 470, 32p; 1000, 50p; 25V: 10, 22, 47, 80, 100, 8p; 160, 220, 250, 15p; 470, 25p; 640, 1000, 35p; 1500, 50p; 2200, 45p; 3300, 77p; 4700, 85p; 15V: 10, 47, 7p; 100, 125, 8p; 220, 330, 14p; 470, 20p; 1000, 1500, 30p; 2200, 36p; 10V: 100, 7p; 640, 12p; 1000, 16p.

**TANTALUM BEAD CAPACITORS**  
 35V: 0.1µF 0.22, 0.33, 0.47, 0.68, 1.0µF, 2.2µF, 3.3, 4.7, 25V: 10, 20V: 1.0µF, 2.2µF, 3.3, 4.7, 10, 15p; 16V: 22p, 28p, 47, 100, 50p; 220, 80p; 10V: 15, 22p, 33, 24p; 100, 35p; 6V: 47p, 68, 100, 28p; 3V: 10p.

**MYLAR FILM CAPACITORS**  
 100V: 0.001, 0.002, 0.005, 0.01µF 7p  
 0.015, 0.02, 0.04, 0.05, 0.056µF 8p  
 0.1µF, 0.2, 0.22, 0.5, 0.47µF 12p

**CERAMIC CAPACITORS 50V**  
 Range: 0.5pF to 0.003pF 4p  
 0.015µF 0.022µF, 0.100µF 5p  
 0.047µF, 0.1µF, 0.2µF, 7p

**SILVER MIC (Values in pF) 3.3, 4.7, 6.8, 10, 12, 18, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220, 11p each**  
 250, 270, 300, 330, 360, 390, 470, 600, 800, 820, 16p each  
 1000, 1200, 1800, 2000, 26p each

**POLYSTYRENE CAPACITORS:**  
 10pF to 1nF 8p; 1.5nF to 47nF 10p

**MINIATURE TYPE TRIMMERS**  
 2.5-6pF, 3-10pF, 10-40pF 22p  
 5-25pF, 5-45pF, 60pF, 88pF 30p

**COMPASS TRIMMERS**  
 4.0pF, 10-80pF, 25-190pF 30p  
 100-500pF 45p, 400-1250pF 58p

**GAS & SMOKE DETECTORS**  
 TGS 812 & 813 41Sp; Socket 25p

**JACKSONS VARIABLE CAPACITORS**  
 DILICON 100/300pF 205p  
 500pF 250p  
 6.1 Ball Drive  
 4511/OAF 145p  
 Dial Drive 4103  
 1.6/36.1 775p  
 Drum 54mm 55p  
 D-1.365pF 325p  
 0.02 365pF 395p

**RF CHOKES**  
 1.5µH 4.7, 10, 22, 33, 47, 100, 200, 470, 1500, 1mH, 2.5, 5, 10, 60p each  
 43mH 100

**VEROBOARD** 0.1 0.15 0.1 (copper clad) (plain)  
 58p 51p 42p  
 2 1/2 x 5 1/2 58p 62p  
 3 1/2 x 5 1/2 68p 82p  
 3 1/2 x 3 1/2 58p 68p 85p  
 2 1/2 x 1 1/2 204p  
 3 1/2 x 1 1/2 264p 229p  
 4 1/2 x 1 1/2 345p

**FERRIC CHLORIDE** 1lb bag Anhydrous 125p + 35p P&P  
 Spare spool (wire) 80p Combs 7p each

**DALO ETCH RESIST PEN** + spare tip 75p

**COPPER CLAD BOARDS**  
 Fibre Single Double SRBP  
 Glass sided sided 9.5" x 8.5"  
 6" x 6" 90p 110p 95p  
 6" x 12" 150p 195p

**DIL PLUGS (Headers)**  
 14 pin 35p; 16 pin 40p; 24 pin 85p; 40 pin 375p

**DIL SOCKETS (TEXAS) Low Wire**  
 8pin 10p 25p  
 14pin 12p 25p  
 16pin 13p 40p  
 18pin 16p 52p  
 20pin 22p 65p  
 22pin 25p 70p  
 24pin 36p 78p  
 28pin 39p 85p  
 36pin 105p  
 40pin 109p

**EDGE CONNECTORS:**  
 (Double type)  
 8BA1008 108  
 8BA1009 108  
 8BA1010 108  
 8BA1099 108  
 8BA1100 108

**POTENTIOMETERS:** Rotary, Carbon, Track 0.25W Log & 0.5W Lin. 470Ω, 680Ω, 1KΩ & 2KΩ (Linear only) Single Gang 29p  
 5KΩ 2MΩ Single Gang Log & Lin. 29p  
 5KΩ 2MΩ Single Gang 0.5 Switch 69p  
 5KΩ 2MΩ Double Gang Log & Lin. 29p  
 Wire Wound Single Turn 1 Watt 200 105p

**SLIDER POTENTIOMETERS**  
 0.25W Log & Linear values 60mm  
 5KΩ-500KΩ dual gang 60p  
 10KΩ 500KΩ single gang 80p  
 Self Stick Graduated Bezels 30p

**PRESET POTENTIOMETERS**  
 0.1W 50Ω-5MΩ Miniature Vertical & Horizontal  
 0.25W 100Ω-3-3MΩ vert. larger 10p  
 0.25W 200Ω-4-7MΩ Vert. 10p  
 Cermet, Precision, multitrn, 0.75W 30p  
 1000-1000µ 40p

**RESISTORS** - Erie make 5% Carbon Miniature High Stability, Low noise  
 RANGE VAL 1.99 100+  
 1/4W 2.20-4.7M E24 2p 1p  
 1/2W 2.20-4.7M E24 2p 1p  
 1W 2.20-10M E12 5p 4p  
 2W Metal Film 100-1MΩ 6p 4p  
 1.3-0.5W 50Ω-1M E24 8p 6p  
 100+ price applies to Resistors of each type not mixed values

**COMPUTER ICs**  
 2102 125  
 2102-2 250  
 2112-2 299  
 2112 299  
 2708 595  
 2708 595  
 2708 595  
 4047 850  
 4047 850  
 6503 850  
 6504 850  
 6505 850  
 6520 525  
 6532 1050  
 6551 1150  
 6800 800  
 6810 360  
 6821 500  
 6850 485  
 6852 485  
 6853 485  
 6854 485  
 8085A 1220  
 81S95 130  
 81S96 130  
 81S97 140  
 8251 70  
 8054 125  
 8726A 235  
 8728A 280  
 8795N 160  
 8797N 150  
 AY-3-1015 550p  
 AY-5-1013 395  
 AY-5-2376 920  
 CP1610 920  
 DM8123 200  
 MC1488 85  
 MC1489 90  
 MC1441 1020  
 MC1442 1520  
 MK4027-2 470  
 CA3048 214  
 MC3049 132  
 CA3075 213  
 MC3080E 65  
 MC3081 95  
 MC3085 95  
 CA3089E 215  
 CA3090 135  
 CA3123E 150  
 CA3130 90  
 NE515 80  
 CA3140 48  
 NE543K 180  
 IC17106 795  
 IC17107 975  
 CL8038CC 340  
 NE566 55  
 ICM7205 1150  
 ICM7215 1050  
 ICM7216A 1950  
 ICM7216B 1950  
 ICM7216C 1950  
 ICM7217A 790  
 ICM7224 785  
 ICM7227A 885  
 LD130 452  
 LF353 97  
 LM10 395  
 LM301AP 23  
 LM308T 36  
 LM311 150  
 LM315 195  
 LM324A 45  
 LM339 40  
 LM349 90  
 LM379 125  
 LM380 135  
 LM381N 145  
 LM382 125  
 LM387 150  
 LM1458 40  
 M252AA 625  
 AY-5810 735  
 CA1011 110  
 CA3012 150  
 CA3014 157  
 CA3018 68  
 CA3019 70  
 CA3020 186  
 CA3023 181  
 CA3028A 80

**BRIDGE RECTIFIERS**  
 MC1441 1020  
 MC1442 1520  
 MK4027-2 470  
 CA3048 214  
 MC3049 132  
 CA3075 213  
 MC3080E 65  
 MC3081 95  
 MC3085 95  
 CA3089E 215  
 CA3090 135  
 CA3123E 150  
 CA3130 90  
 NE515 80  
 CA3140 48  
 NE543K 180  
 IC17106 795  
 IC17107 975  
 CL8038CC 340  
 NE566 55  
 ICM7205 1150  
 ICM7215 1050  
 ICM7216A 1950  
 ICM7216B 1950  
 ICM7216C 1950  
 ICM7217A 790  
 ICM7224 785  
 ICM7227A 885  
 LD130 452  
 LF353 97  
 LM10 395  
 LM301AP 23  
 LM308T 36  
 LM311 150  
 LM315 195  
 LM324A 45  
 LM339 40  
 LM349 90  
 LM379 125  
 LM380 135  
 LM381N 145  
 LM382 125  
 LM387 150  
 LM1458 40  
 M252AA 625  
 AY-5810 735  
 CA1011 110  
 CA3012 150  
 CA3014 157  
 CA3018 68  
 CA3019 70  
 CA3020 186  
 CA3023 181  
 CA3028A 80

**ZENERS**  
 Range 2V7 to 39V 400mW  
 8p each  
 Range 3V3 to 33V 1.3W  
 15p each

**LINER ICs**  
 702 75  
 709 14 pin 38  
 710 16 pin 67  
 733 97  
 747 8 pin 17  
 748 8 pin 36  
 753 8 pin 150  
 810 159  
 LM315 195  
 LM324A 45  
 LM339 40  
 LM349 90  
 LM379 125  
 LM380 135  
 LM381N 145  
 LM382 125  
 LM387 150  
 LM1458 40  
 M252AA 625  
 AY-5810 735  
 CA1011 110  
 CA3012 150  
 CA3014 157  
 CA3018 68  
 CA3019 70  
 CA3020 186  
 CA3023 181  
 CA3028A 80

**NOISE**  
 Z5J 180

**SCRs Thyristors**  
 IA/50V 37  
 IA/100V 42  
 IA/200V 47  
 IA/400V 55  
 5A/600V 39  
 5A/800V 43  
 5A/1000V 48  
 5A/1200V 52  
 12A/100V 42  
 12A/200V 47  
 12A/300V 52  
 12A/400V 55  
 12A/500V 59  
 12A/600V 63  
 12A/800V 68  
 12A/1000V 72  
 12A/1200V 76  
 12A/1500V 80  
 12A/2000V 84  
 12A/2500V 88  
 12A/3000V 92  
 12A/3500V 96  
 12A/4000V 100  
 12A/4500V 104  
 12A/5000V 108  
 12A/5500V 112  
 12A/6000V 116  
 12A/6500V 120  
 12A/7000V 124  
 12A/7500V 128  
 12A/8000V 132  
 12A/8500V 136  
 12A/9000V 140  
 12A/9500V 144  
 12A/10000V 148  
 12A/10500V 152  
 12A/11000V 156  
 12A/11500V 160  
 12A/12000V 164  
 12A/12500V 168  
 12A/13000V 172  
 12A/13500V 176  
 12A/14000V 180  
 12A/14500V 184  
 12A/15000V 188  
 12A/15500V 192  
 12A/16000V 196  
 12A/16500V 200  
 12A/17000V 204  
 12A/17500V 208  
 12A/18000V 212  
 12A/18500V 216  
 12A/19000V 220  
 12A/19500V 224  
 12A/20000V 228  
 12A/20500V 232  
 12A/21000V 236  
 12A/21500V 240  
 12A/22000V 244  
 12A/22500V 248  
 12A/23000V 252  
 12A/23500V 256  
 12A/24000V 260  
 12A/24500V 264  
 12A/25000V 268  
 12A/25500V 272  
 12A/26000V 276  
 12A/26500V 280  
 12A/27000V 284  
 12A/27500V 288  
 12A/28000V 292  
 12A/28500V 296  
 12A/29000V 300  
 12A/29500V 304  
 12A/30000V 308  
 12A/30500V 312  
 12A/31000V 316  
 12A/31500V 320  
 12A/32000V 324  
 12A/32500V 328  
 12A/33000V 332  
 12A/33500V 336  
 12A/34000V 340  
 12A/34500V 344  
 12A/35000V 348  
 12A/35500V 352  
 12A/36000V 356  
 12A/36500V 360  
 12A/37000V 364  
 12A/37500V 368  
 12A/38000V 372  
 12A/38500V 376  
 12A/39000V 380  
 12A/39500V 384  
 12A/40000V 388  
 12A/40500V 392  
 12A/41000V 396  
 12A/41500V 400  
 12A/42000V 404  
 12A/42500V 408  
 12A/43000V 412  
 12A/43500V 416  
 12A/44000V 420  
 12A/44500V 424  
 12A/45000V 428  
 12A/45500V 432  
 12A/46000V 436  
 12A/46500V 440  
 12A/47000V 444  
 12A/47500V 448  
 12A/48000V 452  
 12A/48500V 456  
 12A/49000V 460  
 12A/49500V 464  
 12A/50000V 468  
 12A/50500V 472  
 12A/51000V 476  
 12A/51500V 480  
 12A/52000V 484  
 12A/52500V 488  
 12A/53000V 492  
 12A/53500V 496  
 12A/54000V 500  
 12A/54500V 504  
 12A/55000V 508  
 12A/55500V 512  
 12A/56000V 516  
 12A/56500V 520  
 12A/57000V 524  
 12A/57500V 528  
 12A/58000V 532  
 12A/58500V 536  
 12A/59000V 540  
 12A/59500V 544  
 12A/60000V 548  
 12A/60500V 552  
 12A/61000V 556  
 12A/61500V 560  
 12A/62000V 564  
 12A/62500V 568  
 12A/63000V 572  
 12A/63500V 576  
 12A/64000V 580  
 12A/64500V 584  
 12A/65000V 588  
 12A/65500V 592  
 12A/66000V 596  
 12A/66500V 600  
 12A/67000V 604  
 12A/67500V 608  
 12A/68000V 612  
 12A/68500V 616  
 12A/69000V 620  
 12A/69500V 624  
 12A/70000V 628  
 12A/70500V 632  
 12A/71000V 636  
 12A/71500V 640  
 12A/72000V 644  
 12A/72500V 648  
 12A/73000V 652  
 12A/73500V 656  
 12A/74000V 660  
 12A/74500V 664  
 12A/75000V 668  
 12A/75500V 672  
 12A/76000V 676  
 12A/76500V 680  
 12A/77000V 684  
 12A/77500V 688  
 12A/78000V 692  
 12A/78500V 696  
 12A/79000V 700  
 12A/79500V 704  
 12A/80000V 708  
 12A/80500V 712  
 12A/81000V 716  
 12A/81500V 720  
 12A/82000V 724  
 12A/82500V 728  
 12A/83000V 732  
 12A/83500V 736  
 12A/84000V 740  
 12A/84500V 744  
 12A/85000V 748  
 12A/85500V 752  
 12A/86000V 756  
 12A/86500V 760  
 12A/87000V 764  
 12A/87500V 768  
 12A/88000V 772  
 12A/88500V 776  
 12A/89000V 780  
 12A/89500V 784  
 12A/90000V 788  
 12A/90500V 792  
 12A/91000V 796  
 12A/

# WATFORD ELECTRONICS

## THE DIGITAL FREQUENCY METER with a Difference



- 0-150MHz in 5 ranges
- Large 8 digit display for high accuracy
- Period and time interval facility
- Unit counter up to 99,999,999
- 10MHz crystal timebase
- Hold and reset buttons plus built-in PSU

All these features and more for less than half the price of an ordinary frequency meter. The DF2000 has all its components including the displays, switches and transformer mounted on one double sided PC board. Assembly is simplicity itself especially since interwiring has been eliminated. This is a high quality design and will make a truly professional digital frequency meter that any constructor will be proud to own.

Price: Only **£64.50** Kit (P&P 65p). Probes: Optional extra **£8.75**

Ready built and tested: **£75.50** (65p p&p)

<b>WATFORD'S BOOKSHOP CORNER (No VAT on Books)</b> Silicon Chip & You 250p Future With Microelectronics 400p Illustrating BASIC 250p Programming in BASIC for Business 690p Full ASCII Coded 56 Key 400p KEYBOARD Type 756 Only <b>£39.95</b> (incl. data) KEYPAD 4x4 matrix Reed Switches <b>£3.50</b>	<b>BASIC Computer Games 550p</b> Some Common BASIC Programs <b>750p</b> 32 BASIC Programs for FET <b>950p</b> Z80 Assembl. Lang. Programming <b>750p</b> Z80 Microcomputer Handbook <b>690p</b> 6502 Assembl. Lang. Programming <b>750p</b> C202 Programming the 6502 <b>750p</b> Practical Intro. to PASCAL <b>400p</b> TTL Cook-Book <b>700p</b> CMOS Cook-Book <b>750p</b> (p&p please add 40p)	<b>SWITCHES</b> TOGGLE 2A, 250V SPST <b>28p</b> DPST <b>34p</b> DPDT <b>38p</b> 4 pole on/off <b>54p</b> <b>SUB-MIN TOGGLE</b> SP changeover <b>59p</b> SPST on/off <b>54p</b> SPST biased <b>85p</b> DPDT 6 tags <b>70p</b> DPDT centre off <b>79p</b> DPDT biased <b>115p</b>	<b>SLIDE 250V:</b> 1A DPDT <b>14p</b> 1A DPDT c/over <b>15p</b> 1/2A DPDT <b>13p</b> 4 pole 2-way <b>24p</b> <b>PUSH BUTTON</b> DPDT Black Body Red, Blue, Grn., Yell. <b>125p</b> SRM Momentary <b>125p</b> <b>MINI. Non Locking</b> Push to Make <b>15p</b> Push Break <b>25p</b> Push to c/over <b>85p</b>
ASTEC RF Modulators <b>250</b> Special Widebandwidth for Computers <b>470</b> Sound Modulator <b>250</b>	<b>DIL SWITCHES</b> 4-way SPST <b>110</b> 6-way SPST <b>120</b> 8-way SPST <b>145</b> <b>RELAYS</b> RLE SPCO <b>175</b> RL6B DPCO <b>215</b>	<b>ALUM. BOXES WITH LID</b> 3x2x1" <b>55</b> 2 1/2x5 1/2x1 1/2" <b>75</b> 4x4x1 1/2" <b>75</b> 4x2 1/2x1 1/2" <b>70</b> 4x5 1/2x1 1/2" <b>90</b> 4x2 1/2x2" <b>80</b> 5x4x2" <b>107</b> 6x4x2" <b>110</b> 7x5x2 1/2" <b>145</b> 8x6x3" <b>185</b> 10x7x3" <b>240</b> 10x4 1/2x3" <b>228</b> 12x5x3" <b>230</b> 12x8x3" <b>275</b>	<b>PANEL METERS</b> FSD 60x46x35mm <b>15p</b> 0-500µA <b>0.100µA</b> 0-500µA <b>0.500µA</b> 0-1mA <b>0.1mA</b> 0-50mA <b>0.50mA</b> 0-100mA <b>0.100mA</b> 0-500mA <b>0.1A</b> 0-1A <b>0.25V</b> 0-50V AC <b>0.300V AC</b> 0-300V AC <b>S</b> 'VU' <b>445p each</b> 4 1/2x3 1/2x1 1/2" <b>0.50µA</b> 0-100µA <b>0.500µA</b> 0-500µA <b>595p each</b>

<b>CRYSTALS</b> 100KHz <b>323</b> 455KHz <b>383</b> 1MHz <b>323</b> 1.008M <b>395</b> 1.28MHz <b>392</b> 1.6MHz <b>323</b> 1.8MHz <b>323</b> 1.8432MHz <b>362</b> 2.4576MHz <b>362</b> 3.2768M <b>323</b> 3.57954M <b>195</b> 4.000MHz <b>290</b> 4.032MHz <b>323</b> 4.433619M <b>135</b> 5.0MHz <b>355</b> 5.185M <b>323</b> 5.24288M <b>323</b> 6.0MHz <b>323</b> 6.5536M <b>200</b> 7.80M <b>323</b> 8.0MHz <b>392</b> 8.08333M <b>362</b> 8.967237M <b>362</b> 9.375M <b>323</b> 10.0MHz <b>323</b> 10.7MHz <b>323</b> 12MHz <b>392</b> 14.31818M <b>362</b> 18MHz <b>323</b> 18.432M <b>323</b> 20.0MHz <b>323</b> 27.648M <b>323</b> 38.6667M <b>350</b> 48.0MHz <b>323</b> 100.00MHz <b>323</b>	<b>TRANSFORMERS (Mains Prim. 220-240V)</b> 6-0.6V 9-0.9V, 12-0.12V 100mA <b>95p</b> 3VA: 0-6V 0-6V (PCB mounting) <b>150p</b> 8VA: 6V-5A 6V-5A 9V-4A 12V-3A <b>215p</b> 12V-3A 15V-25A 15V-25A <b>215p</b> 12V: 4.5V-1.3A 4.5V-1.3A 6V-1.2A 6V-1.2A 12V-5A 12V-5A 15V-4A 15V-4A 20V-3A <b>235p</b> (30p p&p) 24VA: 6V-1.5A 6C-1.5A 9V-1.3A 9V-1.3A 12V-1A 12V-1A 15V-8A 15V-8A 20V-6A 20V-6A <b>320p</b> (55p p&p) 50VA: 6V-4A 6V-4A 9V-2.5A 9V-2.5A 12V-2A 12V-2A 15V-1.5A 15V-1.5A 20V-1.2A 20V-1.2A 25V-1A 25V-1A 30V-8A 30V-8A <b>385p</b> (60p p&p) 100VA: 12V-4A 12V-4A 15V-3A 15V-3A 20V-2.5A 20V-2.5A 30V-1.5A 30V-1.5A 40V-1.25A 40V-1.25A 50V-1A 50V-1A <b>695p</b> (74p p&p). (NB p&p charge to be added above our normal postal charge.)	<b>ALUM. BOXES WITH LID</b> 3x2x1" <b>55</b> 2 1/2x5 1/2x1 1/2" <b>75</b> 4x4x1 1/2" <b>75</b> 4x2 1/2x1 1/2" <b>70</b> 4x5 1/2x1 1/2" <b>90</b> 4x2 1/2x2" <b>80</b> 5x4x2" <b>107</b> 6x4x2" <b>110</b> 7x5x2 1/2" <b>145</b> 8x6x3" <b>185</b> 10x7x3" <b>240</b> 10x4 1/2x3" <b>228</b> 12x5x3" <b>230</b> 12x8x3" <b>275</b>	<b>PANEL METERS</b> FSD 60x46x35mm <b>15p</b> 0-500µA <b>0.100µA</b> 0-500µA <b>0.500µA</b> 0-1mA <b>0.1mA</b> 0-50mA <b>0.50mA</b> 0-100mA <b>0.100mA</b> 0-500mA <b>0.1A</b> 0-1A <b>0.25V</b> 0-50V AC <b>0.300V AC</b> 0-300V AC <b>S</b> 'VU' <b>445p each</b> 4 1/2x3 1/2x1 1/2" <b>0.50µA</b> 0-100µA <b>0.500µA</b> 0-500µA <b>595p each</b>
------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

<b>VOLTAGE REGULATORS</b> 1A TO3 +ve -ve <b>220p</b> 5V 7805 <b>175p</b> 7912 <b>220p</b> 12V 7812 <b>175p</b> 7912 <b>220p</b> 15V 7815 <b>175p</b> 18V 7818 <b>175p</b> 1A TO220 Plastic Casing 5V 7805 <b>60p</b> 7905 <b>65p</b> 12V 7812 <b>60p</b> 7912 <b>65p</b> 15V 7815 <b>60p</b> 7915 <b>65p</b> 18V 7818 <b>60p</b> 7918 <b>65p</b> 24V 7824 <b>60p</b> 100mA TO92 Plastic Casing 5V 78L05 <b>30p</b> 79L05 <b>65p</b> 6V 78L62 <b>30p</b> 8V 78L82 <b>30p</b> 12V 78L12 <b>30p</b> 79L12 <b>65p</b> 15V 78L15 <b>30p</b> 79L15 <b>65p</b>	<b>OPTO</b> LEOs with Clips TIL209 Red <b>13</b> TIL211 Grn. <b>17</b> TIL212 Yel. <b>18</b> TIL220 2" Red <b>14</b> 2" Green, Yellow or Amber <b>18</b> Square LEDs, Red Green, Yellow <b>36</b> LD271 Infra Red <b>40</b> SFH205 Detector <b>60</b> TIL32 Infra Red <b>58</b> TIL78 Detector <b>70</b> BARGRAPH Red 10 segments <b>225</b> LS400 <b>255</b> OCP71 <b>120</b> ORP12 <b>63</b> ORP61 <b>45</b> 2N5777 <b>45</b>	<b>ISOLATORS</b> IL74 <b>48</b> TIL111/2 <b>85</b> TIL114 <b>95</b> TIL117 <b>110</b> LCD 3 1/2 Digit <b>875</b> LCD 4 Digit <b>975</b>
------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------

**ETI Projects: Parts available for: Digital Test Meter, DM900, 60W Amplifier System. Send SAE plus 5p for list.**

LS202 <b>345</b> LS352 <b>185</b> 4011 <b>24</b> 4050 <b>48</b> 4162 <b>125</b> 4520 <b>115</b>	LS221 <b>120</b> LS353 <b>185</b> 4012 <b>24</b> 4051 <b>80</b> 4163 <b>125</b> 4521 <b>250</b>	LS240 <b>225</b> LS355 <b>65</b> 4013 <b>45</b> 4052 <b>80</b> 4174 <b>130</b> 4522 <b>150</b>	LS241 <b>225</b> LS366 <b>65</b> 4014 <b>85</b> 4053 <b>80</b> 4175 <b>120</b> 4526 <b>150</b>	LS242 <b>232</b> LS367 <b>65</b> 4015 <b>85</b> 4054 <b>130</b> 4194 <b>125</b> 4527 <b>160</b>	LS243 <b>232</b> LS368 <b>65</b> 4016 <b>42</b> 4055 <b>135</b> 4408 <b>790</b> 4528 <b>120</b>	LS244 <b>225</b> LS373 <b>180</b> 4017 <b>82</b> 4056 <b>135</b> 4409 <b>790</b> 4529 <b>175</b>	LS245 <b>270</b> LS374 <b>180</b> 4018 <b>28</b> 4057 <b>2650</b> 4410 <b>790</b> 4530 <b>89</b>	LS247 <b>135</b> LS375 <b>150</b> 4019 <b>48</b> 4059 <b>575</b> 4411 <b>1020</b> 4531 <b>165</b>	LS248 <b>135</b> LS377 <b>199</b> 4020 <b>99</b> 4080 <b>130</b> 4412F <b>1520</b> 4532 <b>140</b>	LS249 <b>135</b> LS378 <b>185</b> 4021 <b>105</b> 4061 <b>1225</b> 4412V <b>1520</b> 4534 <b>575</b>	LS251 <b>130</b> LS379 <b>215</b> 4022 <b>95</b> 4062 <b>995</b> 4415F <b>850</b> 4536 <b>395</b>	LS253 <b>130</b> LS384 <b>50</b> 4023 <b>25</b> 4063 <b>120</b> 4415V <b>850</b> 4538 <b>160</b>	LS257 <b>115</b> LS385 <b>420</b> 4024 <b>75</b> 4066 <b>58</b> 4419 <b>320</b> 4539 <b>135</b>	LS258 <b>120</b> LS386 <b>85</b> 4025 <b>25</b> 4067 <b>430</b> 4422 <b>570</b> 4541 <b>150</b>	LS259 <b>160</b> LS390 <b>140</b> 4026 <b>180</b> 4088 <b>26</b> 4432 <b>1050</b> 4543 <b>175</b>	LS261 <b>450</b> LS393 <b>140</b> 4027 <b>48</b> 4069 <b>26</b> 4435 <b>1050</b> 4549 <b>295</b>	LS266 <b>75</b> LS395 <b>210</b> 4028 <b>82</b> 4070 <b>30</b> 4440 <b>999</b> 4553 <b>440</b>	LS273 <b>180</b> LS396 <b>199</b> 4029 <b>105</b> 4071 <b>25</b> 4450 <b>350</b> 4554 <b>175</b>	LS275 <b>320</b> LS398 <b>275</b> 4030 <b>60</b> 4072 <b>25</b> 4451 <b>350</b> 4555 <b>85</b>	LS279 <b>88</b> LS399 <b>230</b> 4031 <b>225</b> 4073 <b>25</b> 4452 <b>450</b> 4556 <b>75</b>	LS280 <b>250</b> LS445 <b>140</b> 4032 <b>125</b> 4075 <b>25</b> 4490F <b>750</b> 4557 <b>425</b>	LS283 <b>190</b> LS447 <b>195</b> 4033 <b>175</b> 4076 <b>99</b> 4490V <b>750</b> 4558 <b>130</b>	LS290 <b>130</b> LS490 <b>150</b> 4034 <b>210</b> 4077 <b>48</b> 4501 <b>28</b> 4559 <b>290</b>	LS293 <b>130</b> LS668 <b>105</b> 4035 <b>125</b> 4078 <b>30</b> 4502 <b>125</b> 4560 <b>235</b>	LS295 <b>215</b> LS669 <b>105</b> 4036 <b>365</b> 4081 <b>88</b> 4503 <b>75</b> 4561 <b>95</b>	LS298 <b>215</b> LS670 <b>270</b> 4037 <b>115</b> 4082 <b>28</b> 4506 <b>75</b> 4562 <b>595</b>	LS299 <b>420</b> LS673 <b>750</b> 4038 <b>118</b> 4085 <b>90</b> 4507 <b>60</b> 4566 <b>190</b>	LS300 <b>175</b> LS674 <b>850</b> 4039 <b>360</b> 4086 <b>90</b> 4508 <b>325</b> 4568 <b>299</b>	LS302 <b>175</b> 4040 <b>105</b> 4089 <b>150</b> 4510 <b>99</b> 4569 <b>250</b>	LS320 <b>270</b> 4041 <b>80</b> 4093 <b>89</b> 4511 <b>150</b> 4572 <b>48</b>	LS323 <b>450</b> 4000 <b>18</b> 4042 <b>80</b> 4094 <b>240</b> 4512 <b>98</b> 4580 <b>595</b>	LS324 <b>200</b> 4001 <b>18</b> 4043 <b>95</b> 4095 <b>105</b> 4513 <b>225</b> 4581 <b>350</b>	LS325 <b>320</b> 4002 <b>24</b> 4044 <b>95</b> 4096 <b>105</b> 4514 <b>265</b> 4582 <b>150</b>	LS326 <b>300</b> 4003 <b>24</b> 4045 <b>175</b> 4097 <b>350</b> 4515 <b>298</b> 4583 <b>125</b>	LS327 <b>315</b> 4007 <b>22</b> 4046 <b>130</b> 4098 <b>115</b> 4516 <b>120</b> 4584 <b>64</b>	LS346 <b>185</b> 4008 <b>82</b> 4047 <b>98</b> 4099 <b>190</b> 4517 <b>450</b> 4585 <b>140</b>	LS347 <b>150</b> 4009 <b>40</b> 4048 <b>65</b> 4160 <b>125</b> 4518 <b>105</b> 40106 <b>95</b>	LS348 <b>190</b> 4010 <b>48</b> 4049 <b>45</b> 4161 <b>125</b> 4519 <b>70</b>
-------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------	-------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------

ETI JULY 1980

# QUESTION?

1. Is your hobby home computing or electronics?
2. Do you understand the application of IC's, Transistors, Diodes, etc?
3. Have you used or applied analogue or digital techniques?
4. Are you applying TTL Logic to your home computer?
5. Are you programming your home computer using simple software techniques?

If the answer is YES to any of these questions then why not consider turning your hobby into a career — applying your knowledge to servicing electronic equipment ranging from basic terminals and data processing machines through to advanced micro-processor systems.

We will train you through to advanced technology at the company training school, fitting the individual in at their own level.

We have vacancies over the whole of the U.K. especially in the London area, with the successful applicants working from home, usually in a radius of no more than 60-70 miles.

We supply all tools and test equipment, plus a company car which is available for private use.


If you are interested, then why not contact **Mr. C. Marklew on 0249 813771** to discuss your own career opportunities in confidence, or write to:

## KODE SERVICES LIMITED

Station Road, Calne, Wiltshire
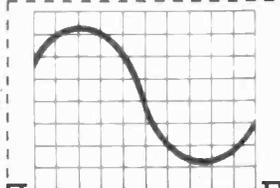
# Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years. Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages. Learn the technology of the future today in your own home.



## TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE.


Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

Block Caps. Please  
 Post now, without obligation to  
 ETI 7  
**British National Radio & Electronics School.**  
 P.O. Box 156, Jersey, Channel Isles

**FREE BROCHURES**

No previous knowledge is necessary. — Just clip the coupon for a brochure

## Complete Audio/Tuner Kits

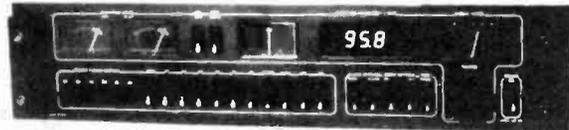

### Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules .....£171.35 inc.  
Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder .....£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

### Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching HMDSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMDS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works.  
Only one version of this item: Complete kit .....£178.25 inc. Carr. £5.

### Preamplifier

More features and facilities, thanks to DC switching and control design

Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/outs, 2 low pass, 2 high pass active filters, genuine volume related loudness, 1dB channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N+, THD -75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

## Semiconductors

### Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST

CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TD4420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.95	IDA1220	1.61	KB4413	2.24
TBA120S	1.15	TDA1083	2.21	KB4417	2.53
KB4406	0.80	TDA1062	2.24	MC3357P	3.16




SL1610	1.84	SL1626	2.80
SL1611	1.84	SL1630	1.86
SL1612	1.84	SL1640	2.17
SL1613	2.17	SL1641	2.17
SL1620	2.50	SL6600	4.31
SL1623	2.80	SL6640	3.16
SL1624	3.77	SL6690	3.68
SL1625	2.50	MC1496	1.44

### VARICAP DIODES.....

A section from our PL:

BA102	0.35	16:1 ratio AM tuning	
BB204	0.41	KV1215 9v triple	2.93
BB105	0.41	KV1211 9v dual	2.01
BB109	0.31	KV1225 25v triple	3.16
MVAM2	1.93	BB212 9v dual	2.25

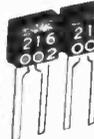

### POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).  
2SK133 120v N-ch 100W MOSFET £6.33 2SJ48 Pch complement £6.33  
2SK135 160v N-ch 100W MOSFET £7.29 2SJ50 Pch complement £7.39  
PA101B Kit for 100W MOSFET PA less Heatsink £16.10. (£23 inc heatsink/bkt)

### ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

### Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OKI

KB4445 - 4 channel dig.prop. FM TX IC, 30mW out (amplifiable) -£2.30 inc  
KB4446 - 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. £2.65.  
KB4445/6 pair: £4.75. New 8 page data sheet 35p + SAE. More RC ICs in list

### CMOS, LPSNTTL, TTL, MPU:

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

### Coming Soon.....

Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here:


### SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX OP 0.2uV basic sensitivity in HF. Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

## Radio/Audio/Communications Modules
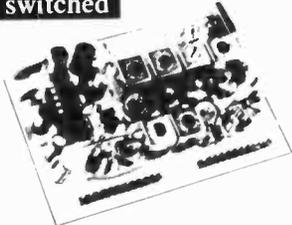
### LW-MW-SW-SW DC tuned and switched

91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands MW/LW: £15.58 +1SW £16.73



### VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

### Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output

944378-2 £26.45



### Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

### Various digital frequency displays

The World's largest range of receiver DFM's is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility. 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



## Components

### Crystal Filters

Most popular types are available ex-stock, and in quantity.

10.7MHz	25kHz Channel spacing 8pole	£16.67
	12½kHz	£17.82
	2.4kHz SSB	£19.78
	M. nolithic dual roofing filter	£2.30
34.5MHz	1.µB loss, 80dB stopband HF first filter in synth. RX	£36.80
RC XTALS	FM pairs (no spilt)	£3.74
	AM pairs	£3.57
USB/LSB	Xtals for 10.7SSB filter	£2.88 ea



### Piezo Sounders

The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency, 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz) The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)



### Keyboard switches and caps

From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCM81101 is shown here, with the KT5 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCM81101 : 17p, KT5 : 16p - or 29p/pair



### LCD CLOCKS

Clocks use 1.5v at 15uA only.

### LCD DVM

DVM 9v/1mA

CM161:	7mm LCD 12/24hr, alarms etc	£11.44 each
CM172:	13mm, 12hr, alarms, timer etc	£14.32 each
CM174:	13mm, 12hr, min/sec stopwatch	£14.32 ea
DVM 176:	ICM7106 based LCD 3½digit	£22.36 each



## WHAT'S NEW at AMBIT

NEW PRICELIST/SHORTFORM: 28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :

£1.50 each - or free with pairs of HMOS and the PA101B

Everything you should know about HMOSFET devices theory and applications.

Please send an SAE with all enquiries. Phone orders by ACCESS but minimum £5. Callers welcome

CATALOGUES 60p ea. all three for £1.60. PRICES SHOWN HERE INCLUDE VAT. POST/PACKAGE CHARGE NOW 35p

**ambit**  
INTERNATIONAL

PLEASE. Commercial MA terms on application. Goods are offered subject to availability, prices subject to change so please phone and check if in doubt.

Parts 1-3 AMBIT catalogues 60p ea, or £1.60 the lot.

200 North Service Road, Brentwood, Essex


TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

The NEW

# VIDEOTONE

YOU CANNOT BUY CHEAPER - YOU CAN ONLY GET LESS FOR YOUR MONEY!
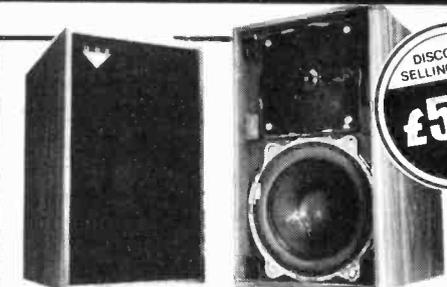
## Introduces DIRECT SELLING - the Ultimate Discount!!!




DISCOUNT SELLING PRICE  
**£50.00**

### LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. Now at lowest ever prices.

D 100	£38
Minimax 11	£44
GB3	£50
GB2	£60
GBS	£207
D 93	£40

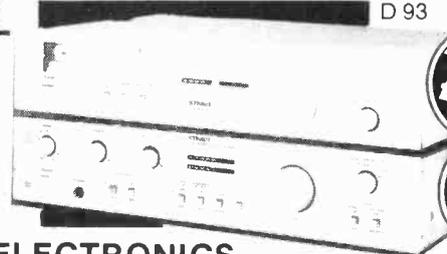

DISCOUNT SELLING PRICE  
**£68.00**

DISCOUNT SELLING PRICE  
**£75.00**

### ELECTRONICS

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

30 watt amp MC input SA4130	£75.00
Stereo Tuner ST4120	£68.00
Cassette full features SC3200	£98.00
50 Watt amplifier WA7700	£77.00
20 Watt amplifier LA2020	£58.00

### CORAL CARTRIDGES

Fast becoming one of the top names

**MOVING COIL**  
UK's No. 1 Cartridge

MC 81	£48.87
777EX	£35
777E	£25

**MOVING MAGNET**

555SX	£7.28
555E	£14.22
666E	£32.48



**HEAD AMP**

H300	£51.75
T100	£24.75

**HEADSHELLS**

S100	£6
S101	£7
S200	£4



### MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

### TURNTABLES


Sansui SR222 Mk2	£69.00
JVC LA 11	£64.00
JVC SLQ 3	£140.00

**The SMART WAY TO BUY HI-FI**



### IN CAR ELECTRONICS

FM AM Receiver with fully integral auto reverse cassette	£48
10 Watt Cassette player	£20
7 Watt Cassette player	£15

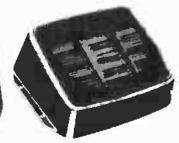

### LOUDSPEAKERS

Small Wedge	£2.95
Door Mount	£9.95
Large Door mount	£18.00



DISCOUNT SELLING PRICE  
**£9.69**

### HEADPHONES

HP 90 Headphone	£12.65
HP 80 Headphone	£9.69

Superbly made with top flight performance.

SEND FOR OUR LATEST FREE BROCHURE AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.



VIDEOTONE  
98 CROFTON PARK ROAD,  
CROFTON PARK, LONDON SE4  
Tel: 01-690 8511/2

Please send me your Direct Selling Brochure and list of sales outlets.

Name \_\_\_\_\_  
Address \_\_\_\_\_

ETI/7/80

**ALL PRODUCTS ON DISPLAY & CONTINUOUS DEMONSTRATIONS**

ALL PRICES INCLUDE VAT

# DIGEST

## Continental Time

An attractive new instrument from CSC offers time and frequency measuring capabilities plus signal conditioning facilities.

The model 5001 has two DC-coupled BNC inputs, both of 1M plus 20 pF input impedance with a sensitivity of 20 mV RMS. Each has three position attenuator (x1, x10 and x100), a positive/negative going slope selector and a variable trigger-level control. Maximum frequency at the A input is specified as 10 MHz and at the B input as 2 MHz. Readings can be held on the display for a variable period.

The frequency counter, with a maximum input frequency of 10

MHz, has a selectable resolution of 100 Hz, 10 Hz, 1 Hz or 0.1 Hz.

The period measurement mode, with a range of 400 nS to 10 S and a maximum input frequency of 5 MHz, can resolve to 100 nS, 10 nS, 1 nS or 100 pS depending on the range chosen.

Time intervals from 200 nS between a rising edge at the A input and the next rising edge at B can be measured, with resolution down to 100 pS.

The ratio of cycles appearing at the A input per cycle at B can also be displayed. The unit will count the number of rising edges arriving at A before the reset button is pushed, in the count mode.


Power consumption is 10 W. The model 5001 Universal Counter-Timer is available at £185 plus VAT from Continental Specialties Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.


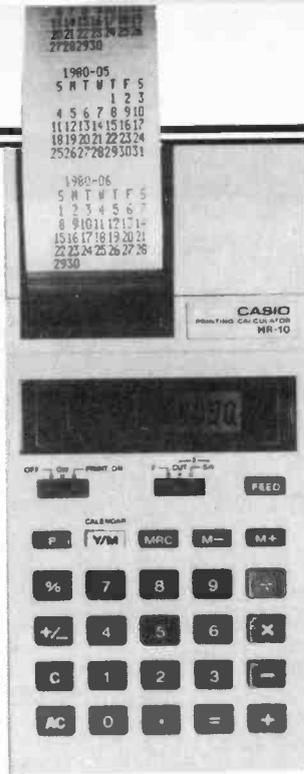
## Look Out Busby

Phillips' M100 Direct Speech System is part of a new range of intercom equipment being launched for the 1980's. Fully compatible with the existing M100 system, its built-in microprocessor enable instant 'hands free' voice links between two and many thousand stations and extra stations are simply plugged into the eight pair parallel cable and reprogrammed within seconds. The keyboard layout includes an improved volume control and privacy button as well as standard optional functions such as automatic call-

back, triplex conversations, group call and links with the DP600 digital paging system through a coupler. There is also facility for twelve programmable direct call buttons for frequently called stations. The M100 system therefore dispenses with the need for a large central exchange and the expense of wiring every station to it. It is available from Pye Business Communications, Cromwell Road, Cambridge CB1 3HE. The BBC has already shown interest in this system by placing a £75,000 order with Pye to instal internal communications in the Beeb's News Department at Television Centre, this covers seven floors and initially 140 stations will be installed. It will replace part of the existing custom-built system.



## Calculate-A-Calendar

The casio HR10 is a slightly out of the ordinary printing calculator, in that apart from all the usual functions and a 10 digit display, it has the capacity to print calendars to order. Simply key in any year and month between January 1901 and December 1099 and it will print out a full conventional calendar. Press add or subtract and it will print the month following or preceding it. The unit can be used either with four AA batteries, rechargeable battery pack or mains adapter. The HR-10 is 3 1/2" wide by 6 3/4" deep and 1 3/4" high. Recommended price is £35.95 including VAT. So, if you want to find out which day of the week your Granny was born on...

## Battery Farming

1980 may well herald a new era for the motor vehicle, this is due to the Chancellor of the Exchequer abolishing Excise Duty from electric vehicles. The interest recently shown in this form of transport is being further strengthened by the forthcoming Drive Electric '80 exhibition to be

held at the Wembley Conference Centre in London during October this year. It will be an international show case of electrically powered vehicles. In Great Britain over a thousand new electric road vehicles are made each year and only here do electrically powered vehicles run as many as 300 million miles each year. The intention of the conference and exhibition is to prove the reliability and performance of the electric vehicle and to extend its acceptability as a means of transport.



## Pinball Prices Slashed

Remember the ETI Pinball Wizard project, featured in the November 1979 issue? It has proved to be so popular (hundreds have been built) that the supplier has made a further bulk purchase of the chips.

ETI readers can now buy the PCB and chip for a mere £9.95 all inclusive only if you send off the attached form.

To: Pinball Offer, NIC,  
61 Broad Lane, London N15 4DJ  
Please send me  
Pinball Wizard PCB/Chip sets at  
£9.95 per set. I enclose cheque/  
PO payable to NIC for  
NAME .....  
ADDRESS .....

# CHROMATHEQUE 5000



Panel size 19.0" x 3.5". Depth 7.3"


This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

# POWERTRAN

## 5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT  
ONLY  
**£49.50 + VAT!**

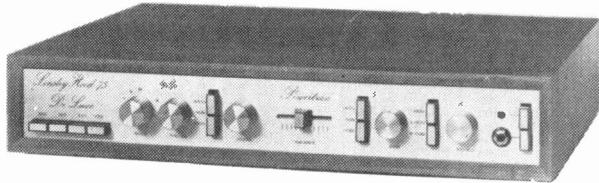


### DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in *Hi-Fi News and Record Review* and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc and full instructions—in fact everything!

All kits also available as separate packs (eg PCB, component sets, hardware sets etc) Prices in our FREE CATALOGUE

Matching Tuners. See our FREE CATALOGUE

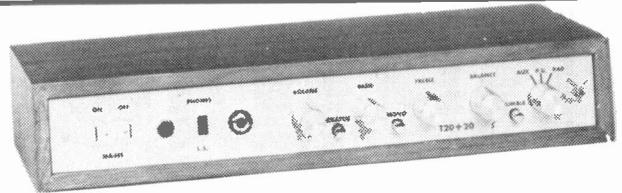

### T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in *Practical Wireless*, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30-watt version of this kit (T30+30) is also available for **£38.40 + VAT**.

# BLACK HOLE

## MUSIC EFFECTS DEVICE AS FEATURED IN *ELECTRONICS TODAY INTERNATIONAL*.

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a 'spacey' feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity input, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY **£49.80 + VAT (SINGLE DELAY LINE SYSTEM)**


De Luxe version (dual delay line system) also available for **£59.80 + VAT**


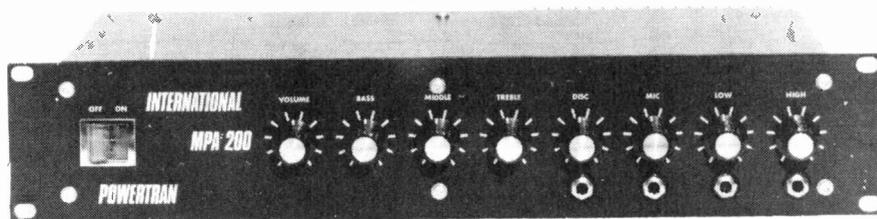
# MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

Featured as a constructional article in *ETI*, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wide range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.



Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT  
ONLY  
**£49.90 + VAT!**  
MATCHES THE  
CHROMATHEQUE 5000  
PERFECTLY!

NEW FACTORY ON SAME INDUSTRIAL ESTATE  
ADDRESS AND PHONE NUMBER UNCHANGED

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

# POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3NM

ANDOVER  
(STD 0264) 64455

**PRICE STABILITY:** Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until August 31st 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.


**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1 handling and documentation.

**U.K. ORDERS:** Subject to 15% surcharge for VAT. No charge is made for carriage or at current rate if changed.

**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

**SALES COUNTER:** If you prefer to collect kit from the factory call at Sales Counter. Open 9 a.m. - 12 noon, 1-4.30 p.m. Monday-Thursday.

<b>TTLs by TEXAS</b> 74285 360p 4019 45p 93 SERIES 74290 150p 4020 100p 9301 160p 74500 60p 745114 120p 74300 60p 74293 150p 4021 110p 9302 175p 74504 60p 745124 300p 7401 12p 74298 200p 4022 100p 9308 316p 74505 75p 745132 160p 7402 12p 74365 100p 4023 27p 9310 275p 74508 75p 745133 75p 7403 14p 74366 100p 4024 50p 9311 275p 74510 60p 745138 225p 7404 14p 74368 100p 4025 130p 9312 160p 74520 60p 745139 225p 7405 15p 74390 200p 4026 130p 9314 165p 74530 60p 745157 250p 7406 40p 74393 200p 4027 84p 9321 225p 74537 90p 745175 250p 7407 40p 74490 225p 4029 100p 9322 150p 74564 60p 745194 350p 7408 17p 74LS SERIES 4030 55p 9334 360p 74574 90p 745241 450p 7409 19p 74LS00 14p 4031 25p 9368 400p 74585 30p 745260 225p 7410 15p 74LS02 15p 4033 180p 9370 200p 74586 180p 745373 500p 7411 24p 74LS03 18p 4034 200p 9374 200p 74587 120p 745374 500p 7412 20p 74LS04 16p 4035 110p 7413 30p 74LS05 25p 4036 295p 7414 40p 74LS08 22p 4037 110p 7415 40p 74LS10 20p 4038 110p 7416 27p 74LS13 40p 4039 25p 7417 27p 74LS13 40p 4040 100p 7420 17p 74LS14 72p 4041 80p 7421 40p 74LS15 45p 4042 80p 7422 22p 74LS20 20p 4043 90p 7423 34p 74LS21 40p 4044 90p 7424 30p 74LS27 38p 4045 100p 7425 40p 74LS30 20p 4046 100p 7426 40p 74LS32 27p 4048 55p 7427 34p 74LS32 27p 4048 55p 7428 36p 74LS37 36p 4049 50p 7429 30p 74LS38 36p 4050 49p 7430 30p 74LS42 70p 4051 80p 7431 30p 74LS42 70p 4051 80p 7432 30p 74LS42 70p 4051 80p 7433 40p 74LS47 90p 4052 80p 7434 35p 74LS51 24p 4053 80p 7435 35p 74LS55 50p 4054 150p 7440 17p 74LS73 50p 4055 125p 7441 70p 74LS74 36p 4056 135p 7442A 60p 74LS75 45p 4059 600p 7443 112p 74LS76 45p 4060 140p 7444 112p 74LS83 40p 4063 120p 7445 100p 74LS85 100p 4066 55p 7446 93p 74LS86 40p 4067 450p 7447A 75p 74LS90 50p 4068 27p 7448 80p 74LS92 70p 4069 20p 7449 80p 74LS93 60p 4070 30p 7450 17p 74LS93 60p 4071 25p 7451 17p 74LS96 110p 4072 25p 7452 34p 74LS107 80p 4073 25p 7453 17p 74LS109 80p 4073 25p 7454 17p 74LS112 100p 4075 25p 7455 100p 74LS113 90p 4076 107p 7456 30p 74LS114 45p 4077 27p 7457 34p 74LS122 90p 4078 72p 7458 34p 74LS124 180p 4089 138p 7459 35p 74LS125 60p 4093 80p 7460 50p 74LS126 60p 4094 250p 7461 100p 74LS132 95p 4096 95p 7462 84p 74LS133 30p 4097 340p 7463 84p 74LS133 30p 4097 340p 7464 84p 74LS133 30p 4097 340p 7465 84p 74LS133 30p 4097 340p 7466 84p 74LS133 30p 4097 340p 7467 84p 74LS133 30p 4097 340p 7468 84p 74LS133 30p 4097 340p 7469 84p 74LS133 30p 4097 340p 7470 84p 74LS133 30p 4097 340p 7471 84p 74LS133 30p 4097 340p 7472 84p 74LS133 30p 4097 340p 7473 84p 74LS133 30p 4097 340p 7474 84p 74LS133 30p 4097 340p 7475 84p 74LS133 30p 4097 340p 7476 84p 74LS133 30p 4097 340p 7477 84p 74LS133 30p 4097 340p 7478 84p 74LS133 30p 4097 340p 7479 84p 74LS133 30p 4097 340p 7480 84p 74LS133 30p 4097 340p 7481 84p 74LS133 30p 4097 340p 7482 84p 74LS133 30p 4097 340p 7483 84p 74LS133 30p 4097 340p 7484 84p 74LS133 30p 4097 340p 7485 84p 74LS133 30p 4097 340p 7486 84p 74LS133 30p 4097 340p 7487 84p 74LS133 30p 4097 340p 7488 84p 74LS133 30p 4097 340p 7489 84p 74LS133 30p 4097 340p 7490 84p 74LS133 30p 4097 340p 7491 84p 74LS133 30p 4097 340p 7492 84p 74LS133 30p 4097 340p 7493 84p 74LS133 30p 4097 340p 7494 84p 74LS133 30p 4097 340p 7495 84p 74LS133 30p 4097 340p 7496 84p 74LS133 30p 4097 340p 7497 84p 74LS133 30p 4097 340p 7498 84p 74LS133 30p 4097 340p 7499 84p 74LS133 30p 4097 340p 7500 84p 74LS133 30p 4097 340p 										<b>TRANSISTORS</b> BF259 36p TIP30A 48p 2N3442 140p 40364 120p 10A 400V 200p AC126 25p BF39 25p TIP30C 60p 40408 75p 25A 400V 400p AC127/8 25p BF40 25p TIP31A 58p 40409 85p AC176 25p BF41 25p TIP31B 62p 40410 85p AC187/8 25p BF42 25p TIP32A 68p 40411 300p AF116 50p BF43 25p TIP32C 82p 40412 300p AF117 50p BF44 25p TIP33A 90p 40413 300p AD161/2 45p BF45 25p TIP33C 114p 40414 300p AU107 200p BF46 25p TIP34A 115p 40415 300p BC107/8 11p BF47 25p TIP35A 125p 40416 300p BC109 11p BF48 30p TIP35C 290p BC117 20p BF49 30p TIP36A 270p BC147/8 9p BF50 30p TIP36B 270p BC149 10p BF51/2 30p TIP36C 340p BC151/8 10p BF52 30p TIP37A 115p BC159 11p BF53 30p TIP37B 115p BC169C 12p BU104 225p TIP41 130p BC177/8 12p BU105 190p TIP42 130p BC217 15p BU108 250p TIP43 130p BC182/3 10p BU109 225p TIP44 130p BC184 11p BU205 200p TIP45 130p BC187 30p BU206 200p TIP46 130p BC212/3 11p BU406 145p TIP47 130p BC214 12p E300 50p TIS43 34p BC217 15p E308 50p TIS93 30p BC327 16p E310 50p 2TX108 12p BC337 16p MJ2501 225p 2TX300 13p BC461 36p MJ2955 90p 2TX500 15p BC477/8 30p MJ3001 225p 2TX502 18p BC516/7 50p MJE3055 100p 2TX504 30p BC517 18p MJE3055 100p 2N696 35p BC518 18p MJE3055 100p 2N697 25p BC519 18p MJE3055 100p 2N698 45p BC520 18p MJE3055 100p 2N706A 25p BC521 18p MJE3055 100p 2N918 45p BC522 18p MJE3055 100p 2N930 18p BC523 18p MJE3055 100p 2N1131/2 20p BC524 18p MJE3055 100p 2N1131 25p BC525 18p MJE3055 100p 2N1132 25p BC526 18p MJE3055 100p 2N1133 25p BC527 18p MJE3055 100p 2N1134 25p BC600 18p MJE3055 100p 2N1207 25p 										<b>MEMORIES</b> 21-12L 120p 21-12H 120p 21-12J 120p 21-12K 120p 21-12L 120p 21-12M 120p 21-12N 120p 21-12P 120p 21-12Q 120p 21-12R 120p 21-12S 120p 21-12T 120p 21-12U 120p 21-12V 120p 21-12W 120p 21-12X 120p 21-12Y 120p 21-12Z 120p 21-13L 120p 21-13M 120p 21-13N 120p 21-13P 120p 21-13Q 120p 21-13R 120p 21-13S 120p 21-13T 120p 21-13U 120p 21-13V 120p 21-13W 120p 21-13X 120p 21-13Y 120p 21-13Z 120p 21-14L 120p 21-14M 120p 21-14N 120p 21-14P 120p 21-14Q 120p 21-14R 120p 21-14S 120p 21-14T 120p 21-14U 120p 21-14V 120p 21-14W 120p 21-14X 120p 21-14Y 120p 21-14Z 120p 21-15L 120p 21-15M 120p 21-15N 120p 21-15P 120p 21-15Q 120p 21-15R 120p 21-15S 120p 21-15T 120p 21-15U 120p 21-15V 120p 21-15W 120p 21-15X 120p 21-15Y 120p 21-15Z 120p 21-16L 120p 21-16M 120p 21-16N 120p 21-16P 120p 21-16Q 120p 21-16R 120p 21-16S 120p 21-16T 120p 21-16U 120p 21-16V 120p 21-16W 120p 21-16X 120p 21-16Y 120p 21-16Z 120p 21-17L 120p 21-17M 120p 21-17N 120p 21-17P 120p 21-17Q 120p 21-17R 120p 21-17S 120p 21-17T 120p 21-17U 120p 21-17V 120p 21-17W 120p 21-17X 120p 21-17Y 120p 21-17Z 120p 21-18L 120p 21-18M 120p 21-18N 120p 21-18P 120p 21-18Q 120p 21-18R 120p 21-18S 120p 21-18T 120p 21-18U 120p 21-18V 120p 21-18W 120p 21-18X 120p 21-18Y 120p 21-18Z 120p 21-19L 120p 21-19M 120p 21-19N 120p 21-19P 120p 21-19Q 120p 21-19R 120p 21-19S 120p 21-19T 120p 21-19U 120p 21-19V 120p 21-19W 120p 21-19X 120p 21-19Y 120p 21-19Z 120p 21-20L 120p 21-20M 120p 21-20N 120p 21-20P 120p 21-20Q 120p 21-20R 120p 21-20S 120p 21-20T 120p 21-20U 120p 21-20V 120p 21-20W 120p 21-20X 120p 21-20Y 120p 21-20Z 120p 										<b>DIODES</b> BY127 12p 3A 400V 60p BY128 12p 3A 400V 60p BY129 12p 3A 400V 60p BY199 12p 3A 400V 60p BY200 12p 3A 400V 60p 										<b>TRIACS</b> 3A 400V 60p 3A 500V 70p 3A 600V 80p 3A 700V 90p 3A 800V 100p 3A 900V 110p 3A 1000V 120p 3A 1100V 130p 3A 1200V 140p 3A 1300V 150p 3A 1400V 160p 3A 1500V 170p 3A 1600V 180p 3A 1700V 190p 3A 1800V 200p 3A 1900V 210p 3A 2000V 220p 3A 2100V 230p 3A 2200V 240p 3A 2300V 250p 3A 2400V 260p 3A 2500V 270p 3A 2600V 280p 3A 2700V 290p 3A 2800V 300p 3A 2900V 310p 3A 3000V 320p 3A 3100V 330p 3A 3200V 340p 3A 3300V 350p 3A 3400V 360p 3A 3500V 370p 3A 3600V 380p 3A 3700V 390p 3A 3800V 400p 3A 3900V 410p 3A 4000V 420p 3A 4100V 430p 3A 4200V 440p 3A 4300V 450p 3A 4400V 460p 3A 4500V 470p 3A 4600V 480p 3A 4700V 490p 3A 4800V 500p 3A 4900V 510p 3A 5000V 520p 3A 5100V 530p 3A 5200V 540p 3A 5300V 550p 3A 5400V 560p 3A 5500V 570p 3A 5600V 580p 3A 5700V 590p 3A 5800V 600p 3A 5900V 610p 3A 6000V 620p 3A 6100V 630p 3A 6200V 640p 3A 6300V 650p 3A 6400V 660p 3A 6500V 670p 3A 6600V 680p 3A 6700V 690p 3A 6800V 700p 3A 6900V 710p 3A 7000V 720p 3A 7100V 730p 3A 7200V 740p 3A 7300V 750p 3A 7400V 760p 3A 7500V 770p 3A 7600V 780p 3A 7700V 790p 3A 7800V 800p 3A 7900V 810p 3A 8000V 820p 3A 8100V 830p 3A 8200V 840p 3A 8300V 850p 3A 8400V 860p 3A 8500V 870p 3A 8600V 880p 3A 8700V 890p 3A 8800V 900p 3A 8900V 910p 3A 9000V 920p 3A 9100V 930p 3A 9200V 940p 3A 9300V 950p 3A 9400V 960p 3A 9500V 970p 3A 9600V 980p 3A 9700V 990p 3A 9800V 1000p 3A									
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--	--	--	--	--	--	--	--	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--	--	--	--	--	--	--	--	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--	--	--	--	--	--	--	--	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--	--	--	--	--	--	--	--	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--	--	--	--	--	--	--	--

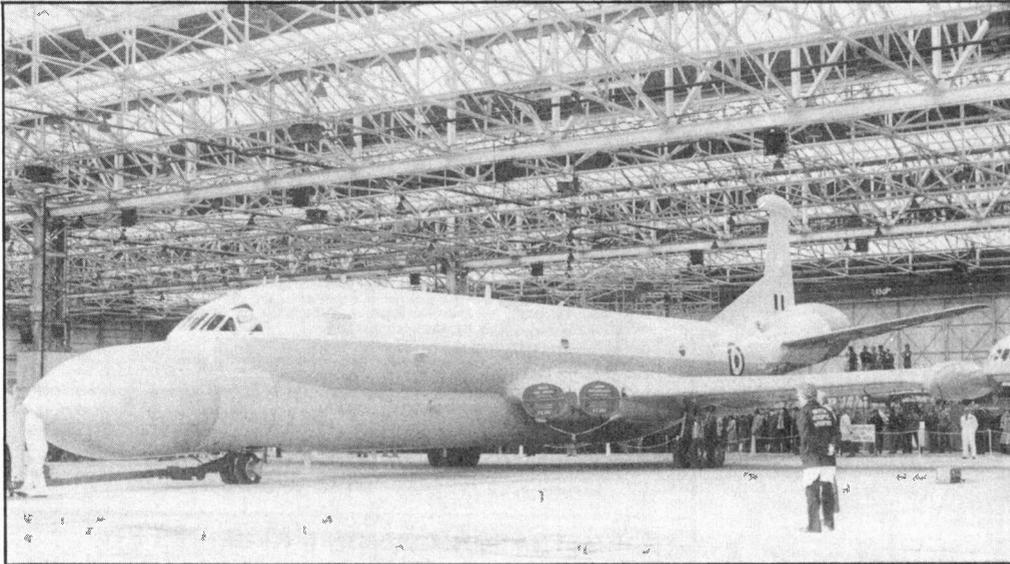

## Nimrod the Mighty Hunter

The latest addition to Britain's Airborne Early Warning (AEW) system was recently unveiled at a British Aerospace airfield 'somewhere' in Cheshire. The modified Nimrod aircraft is the first of a fleet of eleven ordered by the RAF.

The AEW radar system has been undergoing development

since 1977. Ground-based radar cannot see beyond the horizon. The airborne system carried by Nimrod can see further and, therefore, give earlier warning of approaching enemy aircraft.

Nose and tail radomes give the aircraft its odd bulbous appearance. The sophisticated avionics, designed by Marconi with electronic warfare in the crowded airways of Europe in mind, can detect ships and aircraft even against strong ground or sea 'noise' or deliberate jamming and can eliminate friendly craft. In ad-

dition to the active radar, there is a passive system, carried as sensors on each wing tip, to analyse and classify radiation received from targets.

Nimrod AEW has been designed to be fully compatible with other AEW systems, such as the American AWACS. Information can be transmitted from Nimrod AEW to the ground, ships, other aircraft or to virtually anywhere in the world via satellite link.

The first aircraft is due to make its first flight in August and enters service with the RAF in 1982.


## Martian Gremlins

Hot news from our science correspondent on Mars — the Viking 2 Lander isn't a well space-craft at all. Its on-board battery is presenting a low profile: It's flat. There isn't sufficient charge to keep the transmitter going.

Viking Lander 2 now sits on the rusty planet at its landing site in Utopia Planitia, where the daytime temperature rarely gets above  $-115^{\circ}\text{C}$ . It has been working in that temperature since it landed there on September 3rd 1976.
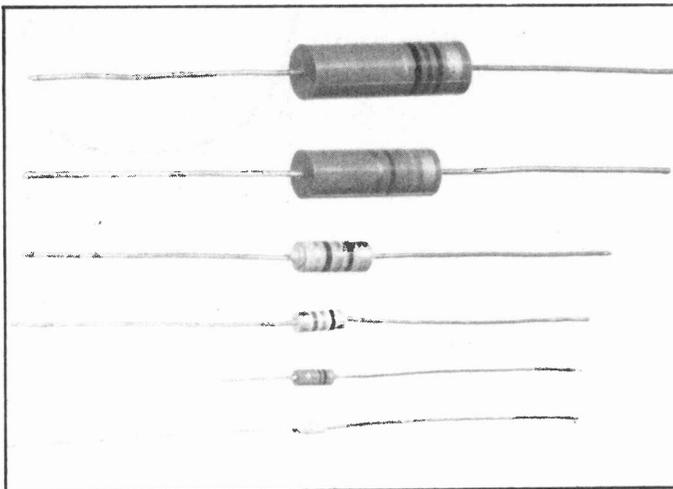
## Circuit Handbook (June)

We missed a denominator out of the equation for  $E_0$  accompanying Fig.11 p.60. The first term of the equation should read  $(RA + RB)/RB$ . Also, on p.61, in the equation for  $E_{in}$  below Fig.12c, 'bandwidth' should not be squared. Therefore, two lines down, '20,000' should not be squared. In the design example the resistor noise effective resistor is  $RA/(RB + RC) \approx 1k\Omega$ . The thermal noise term is then derived from Fig.12b.



## Choked Up

Gone are the days when chokes looked like lumpy coils of wire. The new range of ultra miniature moulded RF chokes from RBS Capacitors look more akin to the common or garden carbon resistor.

The series 8 chokes have a body length of only 5 mm and a diameter of only 2 mm (free

magnifying glass with every order?). They come in values of 0.1  $\mu\text{H}$  to 10,000  $\mu\text{H}$  with minimum Q from 35 to 95.

These military spec components can tolerate up to 1000 V RMS and if you fancy fixing your private jet's radio with one, you can use it up of 70,000 feet. Ten percent tolerance is standard, but five percent is available.

For further information on the Series 8 chokes contact RBS Capacitors Ltd, Orchard Works, Vencourt Place, London W6.


## Flat Caps

Looking a bit like microscopic liquorice all sorts, the new range of capacitors from Welwyn Electric are designed specifically for micro-microelectronic applications. The largest of the range is only 3 mm x 2.5 mm x 1.8 mm.


Initial production will cover values from 1 pF to 100 nF in two dielectrics. BX is suitable for most applications and NPO can be used where high temperature stability

is required. Three working voltages are available — 50 V, 100 V and 200 V. The components have no leads. They have palladium silver terminations for flat soldering onto a substrate or PCB.

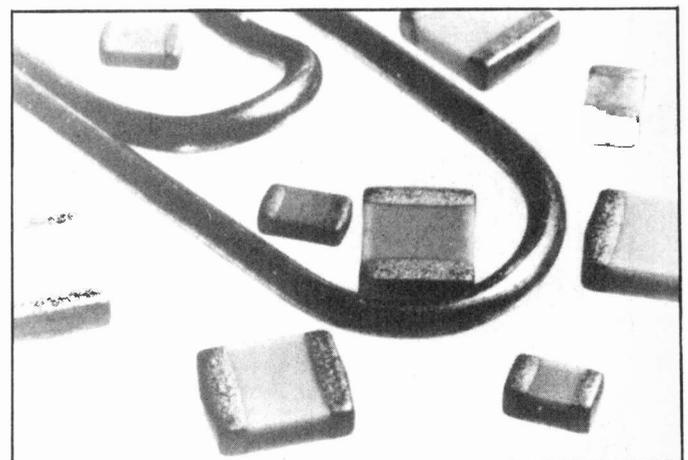For further information on the new range of small multilayer chip capacitors contact Welwyn Electric Ltd, Bedlington, Northumberland NE22 7AA.





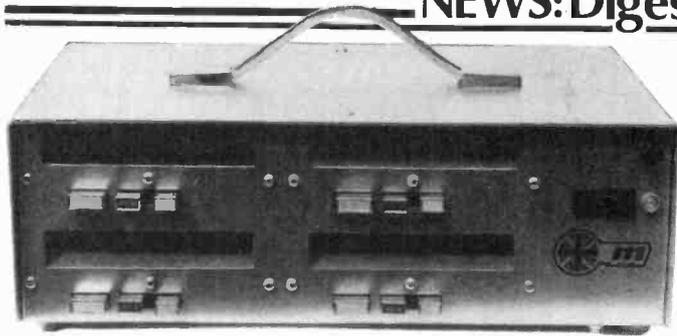

## Cassette Copying

Foxebay have announced the introduction of the first portable machine capable of making three copies at a time. Despite its name, the 3-Kassette-Copier is British made. It costs less than all other two copies cassette copiers.

Foxebay's copier is compatible with both half track IEC and quarter track Japanese formats. It uses the compatible C-format

(erase tracks 3 & 4, record onto track 4). A Hi-Lo switch can compensate for over-recorded/distorted masters and the auto recording takes care of the rest.

There is also a portable seven cassette copying version, consisting of the three-cassette machine linked to a slave four-cassette unit.

The 3-Kassette-Copier (£398 plus VAT) and the 7-Kassette-Copier (£796 plus VAT) are available from Foxebay Ltd. 41/43 Charlbert Street, London NW8 6JN.

## Project 80

The Project 80 Modular Synthesiser is alive and well! A number of readers, who have already invested a great deal of time and money in Project 80 modules, are a little concerned that we do not feature a module in every issue.

The modular synthesiser was conceived as a series of projects, each of which was complete in itself. However, if you build all of them and put them in one box with a keyboard, you end up with a formidable synthesiser.

Occasionally we will miss amonth, but Project 80 will continue to the end of its natural life span.

## Inscrutable Japanese

JVC are holding their Third Tokyo Video Festival in December this year. In celebration of this they are holding a competition to judge video compositions from all over the world. The prize is an all expenses paid trip to Japan, a trophy and 300,000 yen (£699). So if you have a yen (ouch) to try for it, all you need is a video camera, recording on 1/2" or 3/4" tape in any format. The film should be no more than 20 minutes in length and black and white or colour programmes are equally acceptable.

## JVC Super Range


JVC have just revealed their new range of equipment, including three new turntables, four new amplifiers, four tuners, four receivers and five new metal tape cassette decks.

All four of the new AX series of amplifiers and two receivers incorporate what JVC describe as 'a remarkable innovation in amplifier design - the development of Super A amplification'. JVC claims that this combines low distortion and high efficiency. Well, we'll let you know what we think when we get one to play with.

Two of the new turntables

feature another JVC technical innovation, the Electro-Dynamic Servo Tonearm. The arm senses record eccentricity, warp, etc and compensates for their effects. Tracking force and anti-skating force can be adjusted electronically with no contact between the arm and other parts of the turntable.

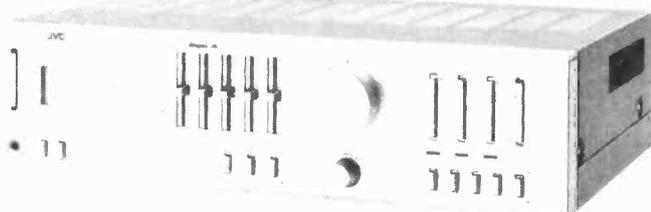The range of metal tape cassette decks includes a budget model selling for under £100. You can build up one of nine recommended, rack-mounting systems from the separates to suit your needs and your pocket.



# SPECIAL OFFER

## TEN YEARS OF



# ELTON JOHN'S GREAT HITS

Yes, 10 years of Elton John's Great Hits in 5 superb albums beautifully boxed and supplied together with a full-sized, full-colour pop art poster. For the Elton fans this is a must!

### EARLY YEARS:

Includes: Lady Samantha: Take me to the Pilot: Country Comfort: Friends.

### ELTON ROCKS:

Includes: The Bitch is Back: Crocodile Rock: Pinball Wizard: Saturday Nights Alright for fighting.

### SINGLES:

Includes: Daniel: Lucy in the Sky with Diamonds: Philadelphia Freedom: Rocket Man.

### MOODS:

Includes: Sweet Painted Lady: Love Song: High Flying: Bird: Blues for my Baby and me.

### CLASSICS:

Includes: We all fall in love sometimes: Curtains: Love lies Bleeding: Captain Fantastic and the Brown Dirt Cowboy.

To obtain your boxed Album complete the coupon below and send it together with your cheque/P.O. made payable to Modmags Ltd. Allow 21 days for despatch.

**£12.50**  
including post,  
packing & V.A.T.

Please send me . . . . . Elton John Albums  
@ £12.50 each incl. post & packaging.  
I enclose my cheque/PO No. . . . .

NAME . . . . .

ADDRESS . . . . .

Send coupon and cheque/PO to :  
MODMAGS LIMITED  
Sales Office (Ref : REC)  
145, Charing Cross Road,  
London WC2H 0EE.

### BOOKS BY BABANI

BOOK NO	DESCRIPTION	£ P
BP6	Engineers & Machinists Ref. Tables	0.50
BP14	2nd Book Transistor Equivs & Subs	1.10
BP24	52 Projects Using IC741 (or equiv)	0.95
BP26	Radio Antenna Book Long Distance Reception & Transmission	0.85
BP27	Giant Chart of Radio Electronic Semi-conductor & Logic Symbols	0.60
BP32	Build Metal & Treasure Locators	1.00
BP34	Practical Repair & Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier	1.25
BP36	50 Ccts. use Germ./Sil./Zener Diodes	0.75
BP37	50 Projects using Relays /SCRs/Triacs	1.25
BP39	50 Field Effect Trans Projects	1.25
BP40	Digital IC Equivs & Pin Connection	2.50
BP41	Linear IC Equivs & Pin Connection	2.75
BP43	How to make Walkie Talkies	1.25
BP44	ICC555 Projects (Revised & Enlarged Edition)	1.75
BP45	Projects on Opto-electronics	1.25
BP46	Radio Circuits using ICs	1.35
BP47	Mobile Discharge Handbook	1.35
BP48	Electronics Projects for Beginners	1.35
BP49	Popular Electronic Projects	1.45
BP50	IC LM3900 Projects	1.35
BP51	Electronic Music & Creative Tape Recording	1.25
BP52	Long Distance Television Reception (TV DX) For the Enthusiast	1.45
BP53	Practical Electronic Calculations & Formulae	2.25
BP55	Radio Stations Guide	1.45
BP56	Electronic Security Devices	1.45
BP57	How to Build Your Own Solid State Oscilloscope	1.50
BP58	50 Circuits using 7400 Series ICs	1.35
BP59	Second Book of CMOS IC Projects	1.50
BP60	Practical Construction of Pre-amps/Tone Controls/ Filters & Attn	1.45
BP61	Beginners Guide to Digital Techniques	0.95
BP62	Elements of Electronics — Book I	2.25
BP63	Elements of Electronics — Book II	2.25
BP64	Elements of Electronics — Book III	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors & Computing	1.75
BP67	Counter driver & numeral Display projects	1.75
BP68	Choosing & Using your Hi-Fi	1.85
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.50
BP160	Coil Design & Construction Manual	0.75
BP202	Handbook of Integrated Circuits Equivs & Substitutes	1.00
BP211	First Book of Diode Characteristics & Equivalents & Substitutes	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	0.85
BP217	Solid State Power Supply Handbook	0.85
BP221	28 Tested Transistor Projects	1.25
BP224	50 CMOS IC Projects	0.95
BP226	Build Advanced Short wave receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
RCC	Resistor Colour Code Disc	0.20

### BRACKETS

Right-angle mounting brackets. Ideal for mounting, PCB, panels etcetera into boxes and cases

1BSWG — Mild steel — short face has slotted hole 6.5cm x 3.7cm long face has 3.7cm diam hole

0/NO: 1726 Height 15cm, length 15cm, width 10cm £0.06

0/NO: 1727 Height 25cm, length 15cm, width 10cm £0.07

### SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.16
DPDT standard slide	1974	£0.17
Toggle switch SPST 1 1/2 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on-off mains switch	1977	£0.58
Push switch — Push to make	1978	£0.16
Push switch — Push to break	1979	£0.21

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.81
Miniature SPST toggle 2 amp 250V ac	1959	£0.86
Miniature DPDT toggle 2 amp 250V ac	1960	£0.92
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.09
Push-button SPST 2 amp 250V ac	1962	£1.04
Push-button SPST 2 amp 250V ac	1963	£1.09
Push-button DPDT 2 amp 250V ac	1964	£1.38

**MIDGET WAFER SWITCHES**

Single bank wafer type — suitable for switching at 250V ac 100mA or 150V dc in non-reactive loads make-before-break contacts. These switches have a spindle 0.25 in dia and 30 indexing

Description	No.	Price
1 pole 12 way	1965	£0.55
2 pole 6 way	1966	£0.55
3 pole 4 way	1967	£0.55
4 pole 3 way	1968	£0.55

Description	No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac	1970	£0.29

### ANTEX IRONS

1943	15 watt iron element ceramic fitted with 3/32" bit	£5.12
1947	Replacement element for 1943 iron	£2.33
1944	Iron coated bit 3/32" for 1943 iron	£0.58
1945	Iron coated bit 1/16" for 1943 iron	£0.58
1948	General purpose 18 watt iron fitted with iron coated bit	£5.12
1952	Replacement element for 1948 iron	£2.22
1949	Iron coated bit 3/32" for 1948 iron	£0.58
1951	Iron coated bit 1/16" for 1948 iron	£0.58
1951	Iron coated bit 3/16" for 1948 iron	£0.58
1931	Highly popular x 25 25 watt quality iron ceramic shafts to provide near perfect insulation breakdown voltage of 1500 volts AC and a leakage current of only 3.5uA and another shaft of stainless steel to ensure strength	£2.00
1935	Replacement element for 1931 iron	£0.58
1932	Iron coated bit 1/16" for 1931 iron	£0.58
1933	Iron coated bit 3/32" for 1931 iron	£0.58
1934	Iron coated bit 1/16" for 1931 iron	£0.58
1953	SK1 kit contains 15 watt iron with a 3/16" bit plus two spare solder, heat-sink and a booklet "How to solder", in presentation display box	£7.28

### VEROBOARD

2201	2.5"x5" .1 Copper	£0.71	2211	2.5"x2.5" .15 Copper	£0.63
2202	2.5"x3.75" .1 Copper	£0.81	2212	3.75"x1.75" .15 Copper	£2.38
2203	2.5"x1.1" .1 Copper	£2.14	2213	3.75"x5" .15 Copper	£0.90
2205	3.75"x3.75" .1 Copper	£0.71	2217	3.75"x1.75" .1 Plain	£1.79
2206	3.75"x1.75" .1 Copper	£2.76	2218	1.75"x2.5" .1 Plain	£0.44
2207	4.75"x1.75" .1 Copper	£3.61	2219	5"x3.75" .1 Plain	£0.68
2208	2.5"x1" .5 in jack	£0.85	2223	2.5"x3.75" .15 Plain	£0.37
2204	3.75"x5" .1 Copper	£0.79	2225	5"x3.75" .15 Plain	£0.56
2210	2.5"x5" .15 Copper	£0.64			

### BIB HI-FI ACCESSORIES

806	J Compact tape head cleaning kit	£1.22
810	23 Tape Editing kit	£2.65
811	24 Cassette Tape editing and joining kit	£2.76
813	29A Salvage cassette	£0.51
814	31 Cassette Head cleaning tape	£0.71
817	36A Record & Stylus cleaning kit	£0.46
818	41 Groove Kartidge tape head cleaner	£1.24
819	42 Groove Kleen auto metal record cleaner	£2.65
826	52A Cassette storage tray (holds 10)	£0.92
827	53 Hi-Fi stereo test cassette	£3.17
829	60 Chrome finish Groove Kleen (plastic)	£2.12
834	69 Anti-static Hi-Fi cleaning liquid	£0.35
838	78 Cassette hand tape winder	£1.50

### WIRE CONNECTORS

Entirely new range of connectors for Discrete wire. Uniquely designed Wirepost is soldered to the P.C. Board. A pre-stripped wire is inserted into the connector and easily locked by pressing the housing down. The wire is alternatively removed by lifting the housing. Tin alloy plated contacts ensure good as gold performance.

Housing consists of Thermo plastic polyester.		
1728	Single connector in red/black or white	£0.12 inc. VAT
1729	Threeway connector black ONLY	£0.23 inc. VAT
1730	Fourway connector black ONLY	£0.28 inc. VAT

### FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0.18
1 1/2" x 1/2" x 1/2" chassis mounting	507	£0.14
1 1/4" car in-line type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1 1/4"	510	£0.37

QUICK BLOW 20mm					
Type	No.	Type	No.	Type	No.
150mA	611	7p	1A	615	6p
250mA	612	6p	1.5A	616	7p
500mA	613	6p	2A	617	6p
800mA	614	8p	2.5A	618	7p

ANTI-SURGE 20mm					
Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK-BLOW 1 1/4"					
Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634

NUTS AND BOLTS					
BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head Supplied in multiples of 50					
Type	No.	Price	Type	No.	Price
1/4" OBA	839	£1.38	1/2" OBA	846	£0.37
1/2" OBA	840	£0.86	3/4" OBA	847	£0.29
1" OBA	842	£0.75	1 1/4" OBA	848	£0.46
1/2" 2BA	843	£0.52	1/2" 6BA	849	£0.24
1/4" 2BA	844	£0.60	1/4" 6BA	850	£0.29
1" 4BA	845	£0.51			

BA NUTS — packs of cadmium plated full nuts in multiples of 50					
Type	No.	Price	Type	No.	Price
08A	855	£0.83	48A	857	£0.35
28A	856	£0.55	68A	858	£0.28

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50					
Type	No.	Price	Type	No.	Price
08A	859	£0.16	48A	861	£0.14
28A	860	£0.14	68A	862	£0.14

SOLDER TAGS — Hot linned supplied in multiples of 50					
Type	No.	Price	Type	No.	Price
08A	851	£0.46	48A	853	£0.25
28A	852	£0.32	68A	854	£0.25

### AUDIO LEADS

No.	Type	Price
107	FM Indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	£0.86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m	£0.98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead. Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios. 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.21
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£1.04
120	Car stereo connector. Variable geometry plug to fit most car cassettes. 8 track cartridge and combination units. Supplied with inlined fuse power lead and instructions	£0.89
123	6.6m Coded Guitar Lead Mono Jack plug to Mono Jack plug. Black	£1.73
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.86
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.86
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.86
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.50
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5. Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m	£0.86
134	5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm	£0.78
136	Coded stereo headphone extension lead. Black. Length 6m	£2.01
178	AC mains lead for calculators. etc.	£0.52

### TRANSFORMERS

MINIATURE MAINS Primary 240V			
No.	Type	Price	
2021	6V-0-6V 100mA	£1.04	
2022	9V-0-9V 75mA	£1.04	
2023	12V-0-12V 100mA	£1.29	

MINIATURE MAINS Primary 240V with two independent secondary windings			
No.	Type	Price	
2024	MT780-0-6V 0-6V RMS	£1.84	
2025	MT150-0-12V 0-12V RMS	£1.84	

1 AMP MAINS Primary 240V			
No.	Type	Price	
2026	6V-0-6V 1 amp	£2.88	P & P 45p
2027	9V-0-9V 1 amp	£2.30	P & P 45p
2028	12V-0-12V 1 amp	£2.99	P & P 55p
2029	15V-0-15V 1 amp	£3.16	P & P 66p
2030	30V-0-30V 1 amp	£3.97	P & P 86p

**STANDARD MAINS Primary 240V**

Multi-tapped secondary mains transformers available in 1/2 amp, 1 amp and 2 amp current rating. Secondary taps are 0.1-9.25-33.40-50V. Voltages available by use of taps. 7.8, 10, 14, 15, 19, 25, 31, 33, 40, 25-0-25V.

No.	Rating	Price	
2031	1/2 amp	£3.91	P & P 86p
2032	1 amp	£5.06	P & P 86p
2033	2 amp	£6.27	P & P £1

2035 240V Primary 0-55V @ 2A Secondary

**SPECIAL OFFER**

2042 240V Primary 0-20V @ 2A Secondary. By removing 5 turns for each volt from the secondary winding any voltage up to 20V @ 2A is easily obtainable. Ideal for the experimenter.

£1.50 P & P 86p

### CASES AND BOXES

INSTRUMENT CASES. In two sections, vinyl covered top and aluminium bottom, front and back					
No.	Length	Width	Height	Price	
155	8in	5 1/2in	2in	£1.73	
156					

---

---

# ETI NEXT MONTH

ON SALE JULY 4th

---

## 100W MOSFET Amplifier

---

Yet another in the long line of top line audio projects from ETI. Next month we give you a 100 + 100W power amp with bargraph output display, separate PSUs for each channel and a brilliant sound that puts this unit at the very top end of audio today. You will find it costs a lot less than you think to build, too.

---

## Electromagnetic Pulse Effect.

---

Never heard of it eh? Most people haven't — yet EMP could be the deciding factor in a nations fight for survival during nuclear attack. With the international situation steadily worsening around us, the facts ETI has turned up about Britain's susceptibility to EMP are very, very disturbing and make mandatory reading for anyone concerned with keeping civilisation alive in the age of the Bomb!

As an indication of the situation, did you know that in 1958 a small warhead test in the Johnstone Islands produced power systems failure in Hawaii, **SOME 1000 KM FROM THE EXPLOSION**, due to EMP? (The British Isles are approx. 800 km in length).

---

## Video Today — And Tomorrow

---

Next month ETI takes a detailed look at the expanding world of home video and offers a buyers guide to inform the intending purchaser. In addition we have a look at the next 12 months from Richard Dean (editor — TV and Home Video) — probably the leading writer in the field today.

---

## Circuits Appetiser

---

How many times have you glanced at book titles all neatly aligned on a shelf and wondered just how interesting they *really* are? Well, as of next month maybe we can help. "110 Timer Circuits for the Home Constructor" has just been released by Newnes and ETI is publishing a chapter from it next month. Circuits galore and full details of this very nifty little volume. It is hoped that more books will receive this treatment in the future.

---

## Projects, Projects, Projects, Projects.


---

In addition to that truly amazing MOSFET AMPLIFIER we have a further four constructional projects for you next month. There is an excellent VCA module which fits in with Project 80 if you're following it. Also we give full details of an ULTRASONIC BURGLAR ALARM which could ensure that any visitors you get are at least invited. Two test gear "quickness" are featured in the shape of a LINEAR CAPACITANCE METER with good accuracy and easy construction and a very versatile LOGIC PROBE to allow you to hunt out those missing bits.

With all this how can you possibly *not* buy ETI next month?

---

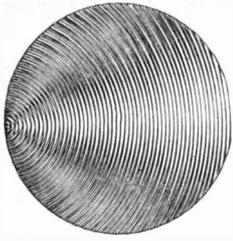
Articles mentioned herein are in an advanced state of preparation, however, circumstances may dictate changes to the final contents.




# B.K. ELECTRONICS
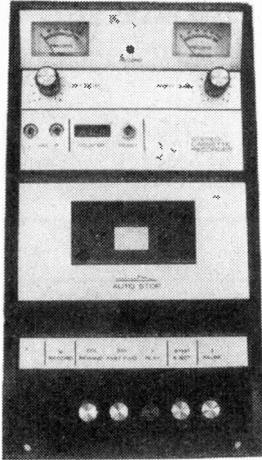
## A SOUND CHOICE

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



**STEREO CASSETTE TAPE DECK ASSEMBLY.** Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. For horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. **Features:** Pause control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual level controls, twin mic, input sockets, AC erase system, LED record indicator. (Separate power amplifier required.) **Input Sensitivity:** 6 MV (with level control set at max). **Input Impedance:** 47 kOhms. **Output Level:** To both left and right hand channels 150 MV. **Output Impedance:** < 10k. **Signal to noise ratio:** 45 dB nominal. **Power Supply Requirements:** 12V AC at 300M/A. **Connections:** All connections to the unit are via a wander lead terminated with a nine pin plug (socket provided). **Dimensions:** Top panel — 11 1/2in x 6 1/2in. Mechanism fits through a cut out 5 1/4in x 10 1/2in. Clearance required under top panel 2 1/4in. Supplied complete with circuit diagram etc. **Price £30.50** plus £2.50 postage and packing.

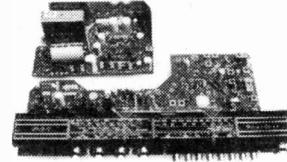

**GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS.** Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ±3dB.


**Tape Sensitivity:** Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz — 108MHz. Long wave 145kHz — 108kHz. Medium wave. 520kHz — 1620kHz. Short wave. 5.8MHz — 16MHz. **Size:** Tuner — 2 3/4in x 15in x 7 1/2 in approx. Power amplifier — 2in x 7 1/2in x 4 1/2in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £21.50** plus £2.50 postage and packing.




**SCOTT AM/FM STEREO TUNER MODEL 516.** This Scott tuner is one of the top American makes and is offered at a very realistic price. **Features:** ★ FM tuning range 87.5 to 108 MZ ★ AM tuning range 535 to 1605 kHz ★ Usable FM sensitivity 6.2dBf 2.2µV ★ 300 ohm & 75 ohm Aerial inputs for FM ★ Signal strength tuning meter ★ Stereo beacon indicator ★ Ferrite aerial for AM ★ Mute switch. **Size:** Height 5in, Width 14 1/2in, Depth 12in. Silver front panel. Black body. Modern stacking format. **Price £40.50** plus £2.50 postage and packing.
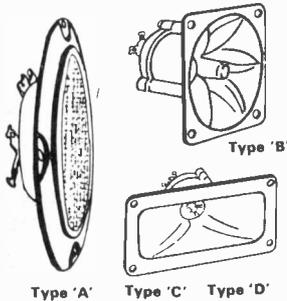
### PIEZO ELECTRIC TWEETERS — MOTOROLA


Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series).



**Type 'A'** 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price £3.80 each.**  
**Type 'B'** 3 1/2in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.80 each.**  
**Type 'C'** 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £6.20 each.**  
**Type 'D'** 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £9 each.**  
Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

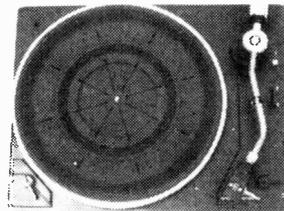


### DE-SOLDERING PUMP

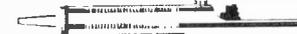

**JVC TURNTABLE.** JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.  
★ 'S' shaped tone arm.  
★ Belt driven.  
★ Full size 12in platter.  
★ Precision calibrated counterbalance weight (0.3 grms.)  
★ Anti-skate (bias) device. Nylon thread weight.  
★ Damped cueing lever.  
★ 240V AC operation, (50Hz).  
★ Cut-out template supplied.  
**Size** — 12 3/4in x 15 3/4in (approx).  
**Price £29** plus £2.50 postage and packing.


This de-soldering pump made to a very exacting specification is ideal for the removal of small components from printed circuit boards, etc. Comes complete with spare PTFE tip. **£5.30** post free.

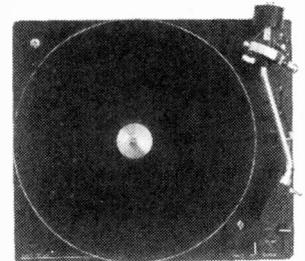**BSR P163 BELT DRIVE TURNTABLE.** This famous B.S.R. turntable is ideal for disco/hi-fi use and is offered at a special price of **£22** plus £2.50 postage and packing. Suitable stereo magnetic cartridge type TTC/J2203. **Price £4** post free. (Also available separately.)


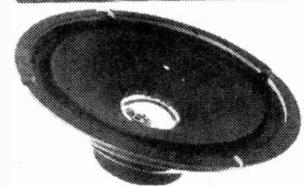
### LOUDSPEAKER

High quality full range 8" loudspeaker. 10 watts RMS. 8OHM. Rolled surround with aluminium centre dome. **Price £3.50 each** + 75p Postage and Packing.



# B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.

# FILTER DESIGN

Following up his supplementary efforts last month, Tim Orr tackles the subject of Active Filters in the same explanatory manner.

The frequency response plot of a first order low pass filter (Fig.1) reveals several important features. The break frequency  $F_c$ , is defined as the point at which the output signal is attenuated by 3 dB. The curve then approximates to a -6 dB/octave roll off slope. By using a straight line approximation it is easy to calculate attenuations caused by the filter. For example, an 8 kHz sinewave filtered by a 1 kHz first order lowpass filter will be attenuated 18 dB, a reduction in level of almost one tenth. The calculation is simple; 8 kHz is 3 octaves above 1 kHz. The filter attenuates at 6 dB per octave, therefore the final attenuation is  $3 \times 6 = 18$  dB.

To increase the roll off slope, the filter order must be increased, figure 2. When constructing high order filters, it is necessary to assemble them out of smaller filter sections each having different Q factors. A high order filter constructed from sections all having the same Q factor will have a very 'unabrupt' frequency response curve, which is generally not what is required.

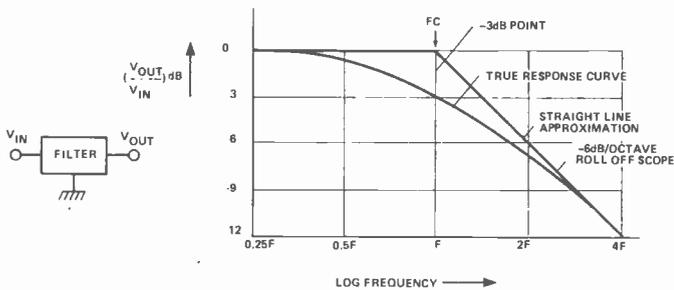


Fig.1. Frequency response of a first order low pass filter.

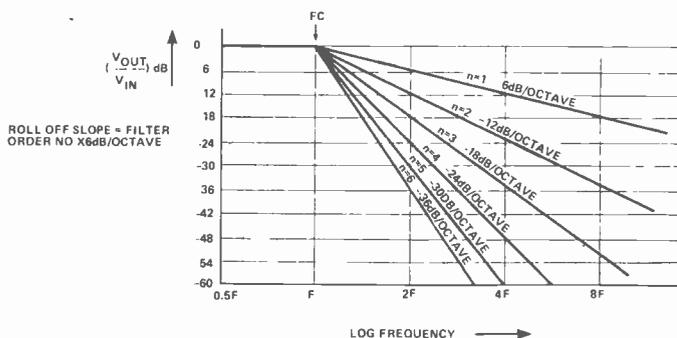


Fig.2. Filter roll-off slopes. As n increases so does the roll-off.

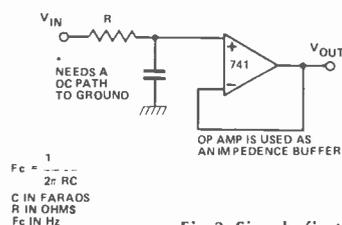


Fig.3. Simple first order low pass filter.

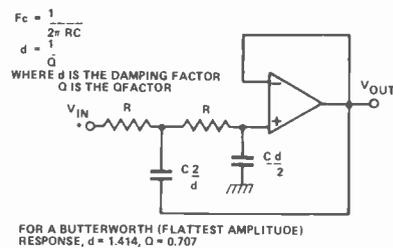


Fig.4. Second order unity gain Sallen and Key low pass filter.

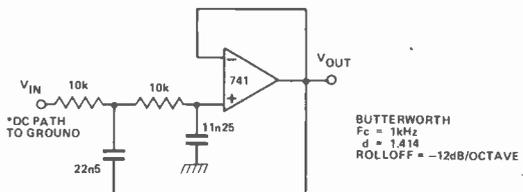


Fig.5a. Second order low pass filter, 1 kHz.

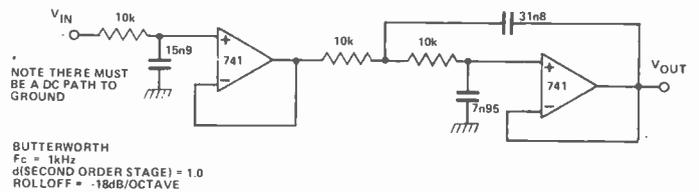


Fig.5b. Third order low pass filter, 1 kHz.

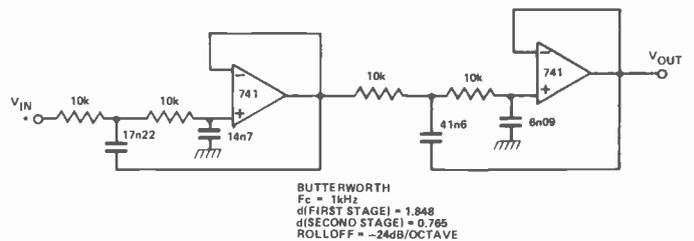


Fig.5c. Fourth order low pass filter, 1 kHz.

A simple first order filter (Fig.3) merely requires a resistor, a capacitor and a voltage follower. A second order filter (Fig.4) requires two RC networks. This circuit has a 'flattest amplitude' response (when it has a Q of 0.7) and is often referred to as a Butterworth response. The response may be modified by altering the Q factor, but in all the following examples a Butterworth response has been chosen. This design is known as a 'unity gain Sallen and Key' filter. The Q factor is determined by the ratio of the two timing capacitors. This often leads to a circuit design which employs non-preferred capacitor values as can be seen in the three filters by a process known as scaling. For instance, if the required break frequency is 5 kHz, then the resistors, or the capacitors in the filter should be reduced by a factor of five. If say the filter in figure 5a had to be redesigned to operate at 250 Hz,

then the required component changes would be to change the 10k resistors to 40k. Active filters generally employ op amps and so care should be taken so as not to operate them near to their bandwidth limit, which would cause the filter response to be degraded. A 741, for instance, should not be used for frequencies above 50 kHz.

Figure 6 shows the effect of varying Q in a low pass filter. Generally, the response that is wanted is the 'flattest amplitude' curve. A fourth order filter (Fig.5c) is constructed from a low Q and high Q filter. The overall response of this filter is seen in figure 7. Note that the flattest amplitude curve (A) is made up out of the product of curves B and C. The peak in the high Q curve (C) is flattened out by the droop of the low Q curve (B).

The problem of having different and unpreferred capacitor values is greatly reduced by using an 'equal component' design, figure 8a,b,c. The Q factors are controlled by the gain of the op amp and so the capacitor values are all the same. Note that these filters provide a voltage gain which is in fact

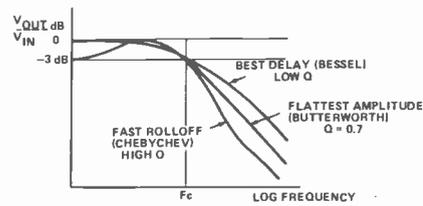


Fig.6. Frequency response versus Q factor.

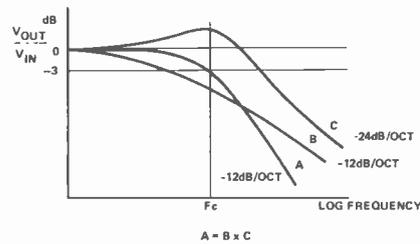


Fig.7. Combining high and low Q factors.

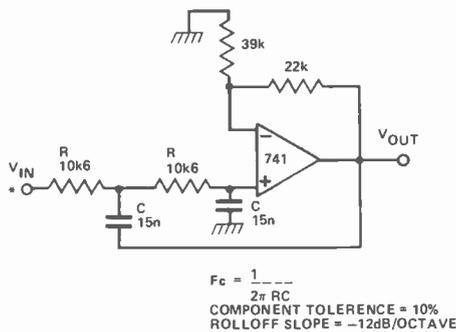


Fig.8a. Second order low pass filter, 1 kHz.

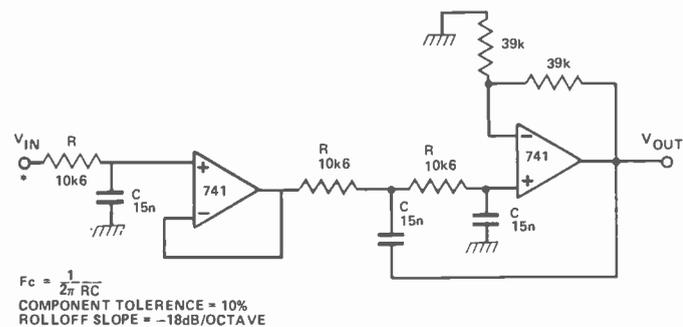


Fig.8b. Third order low pass filter, 1 kHz.

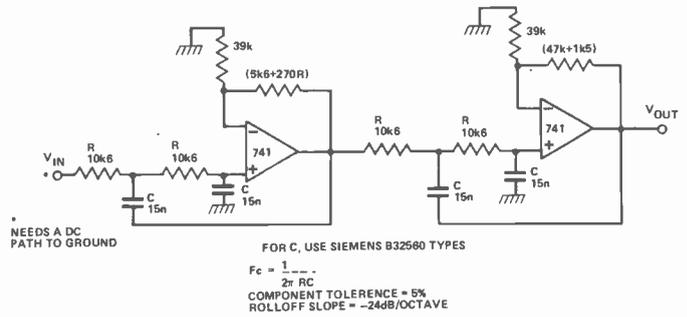


Fig.8c. Fourth order low pass filter, 1 kHz.

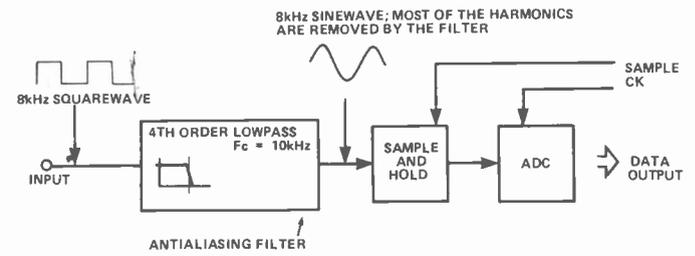


Fig.9. Use of a low pass filter in an ADC system.

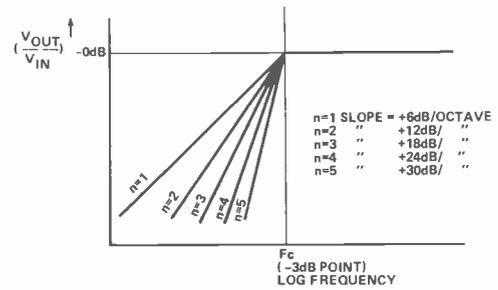


Fig.10. Frequency response of different orders of high pass filter.

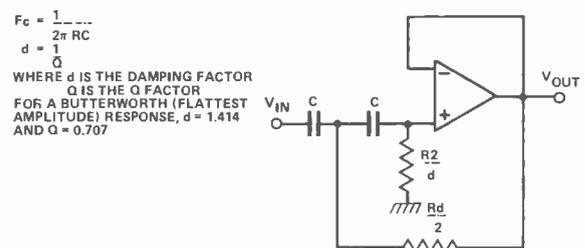


Fig.11. Unity gain Sallen and Key high pass filter.

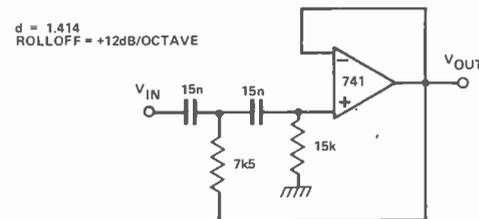


Fig.12a. Second order Butterworth 1 kHz high pass filter.

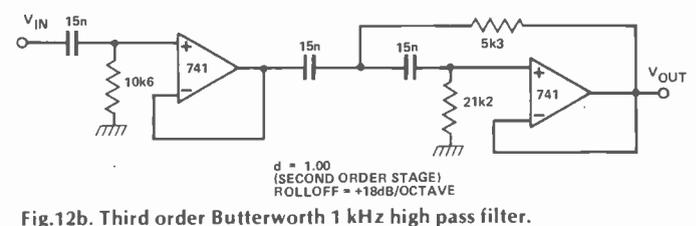


Fig.12b. Third order Butterworth 1 kHz high pass filter.

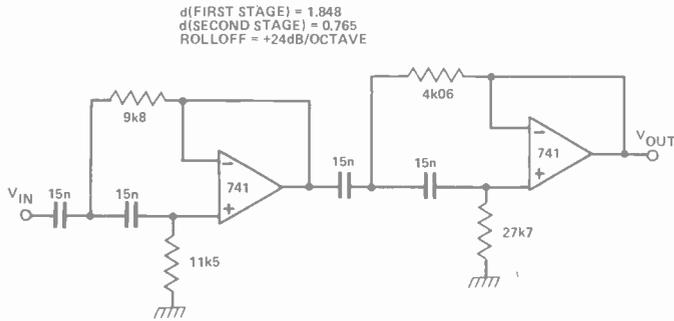


Fig.12c. Fourth order Butterworth 1 kHz high pass filter.

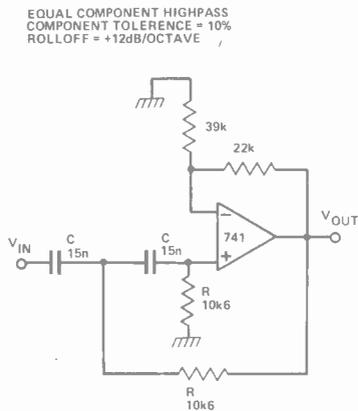


Fig.13a. Second order Butterworth 1 kHz high pass filter.

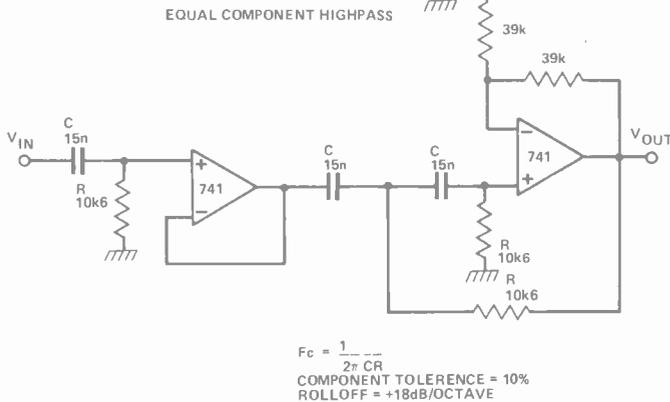


Fig.13b. Third order Butterworth 1 kHz high pass filter.


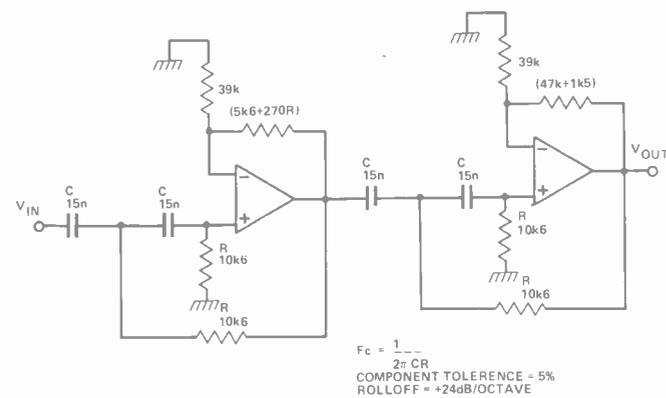


Fig.13c. Fourth order Butterworth 1 kHz high pass filter.

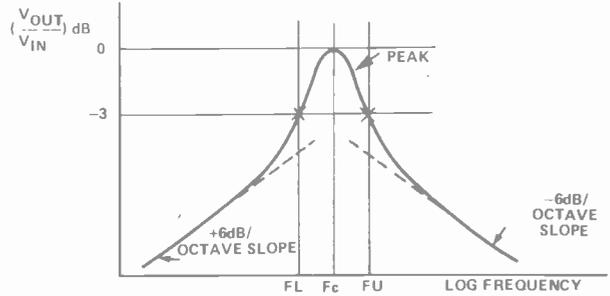

FC = CENTRE FREQUENCY  
FU = UPPER -3dB POINT  
FL = LOWER -3dB POINT

$FU - FL = \text{BANDWIDTH (FBW)}$   
 $Q = \frac{FC}{\text{FBW}}$

Fig.14. Band pass response (single pole).


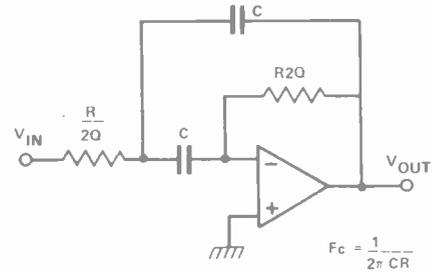


Fig.15. Single pole multiple feedback band pass filter.

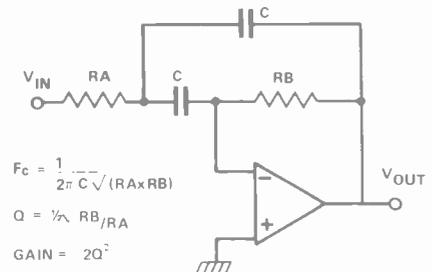

C	RA	RB	Fc	Q	GAIN
15n	10k6	10k6	1kHz	0.5	x 0.5
15n	5k305	21k22	1kHz	1.0	x 2.0
15n	2k652	42k44	1kHz	2.0	x 8.0
15n	1k326	84k88	1kHz	4.0	x32.0

Fig.16. Multiple feedback filter selection chart.

the product of the DC gains of each amplifier. Frequency scaling can be performed by modifying the R and/or the C components. Capacitors generally are available in E6 or E12 values, whereas resistors can be obtained in the E24 series, and so it is usually much easier to scale the R components, keeping them within the range 1k to 100k. Low pass filters find many uses in audio processing and are often used in data acquisition systems (Fig.9). The high pass filter (Fig.10) is exactly complementary in operation to the low pass device. The unity gain Sallen and Key structure is seen in figure 11 with calculated values for second, third and fourth order filters in figure 12a,b,c. Also there are calculated values for 'equal component' realizations in figure 13a,b,c.

The band pass response is defined in figure 14. This can be realized with a single op amp circuit, the multiple feedback band pass filter, figure 15. Calculated values are seen in the chart of figure 16. The maximum Q should be kept below a

value of 20 at 1 kHz, otherwise the filter may become unstable and oscillate. Frequency scaling may be performed by multiplying the R or the C components with a constant. High Q, high frequency operation is not possible with this design because the op amp runs out of bandwidth.

The state variable filter (Fig.17) overcomes this problem by using the bandwidth of three op amps. Q factors of several hundred at 1 kHz are obtainable with this circuit. It also produces four outputs; high, low, band pass and notch, making it a very versatile design. The frequency may be scaled by altering the R or the C components and also the Q factor is separately programmable and is invariant with frequency. The all pass filter (Fig.18) has a flat frequency response, which in

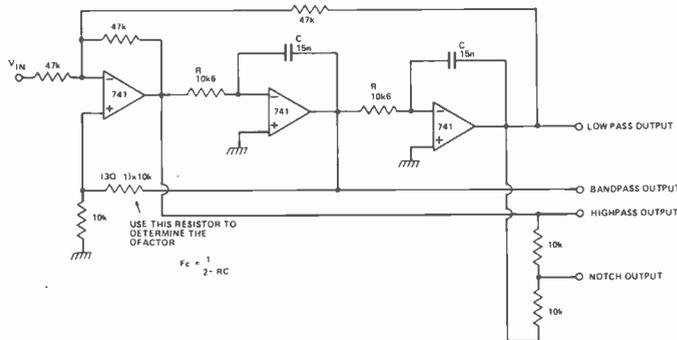
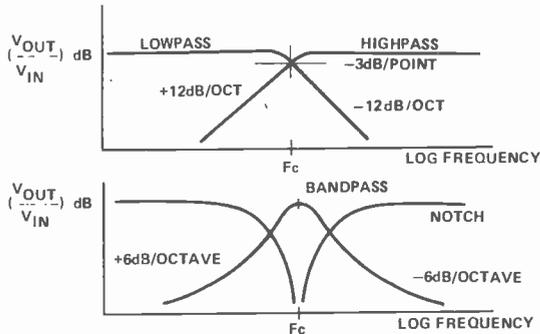


Fig.17. State variable filter.

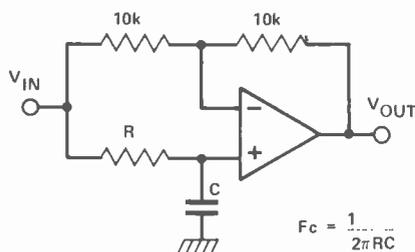
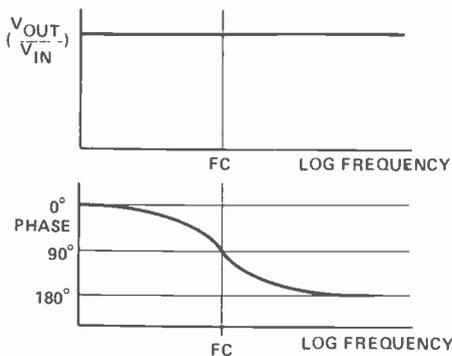


Fig.18. All pass filter.

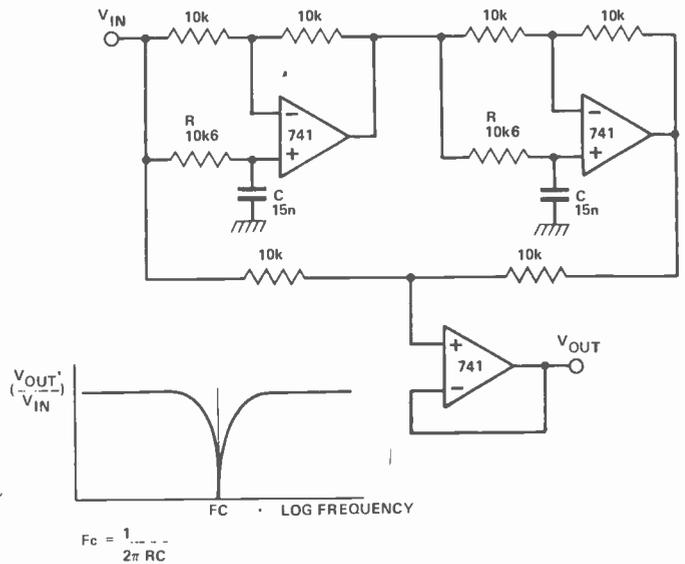


Fig.19. Notch filter using all pass sections.


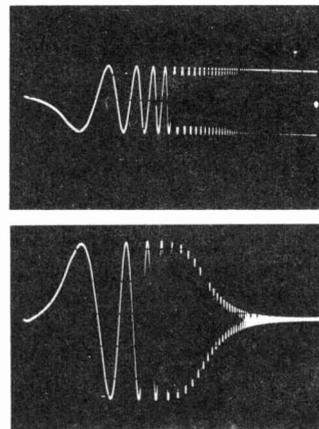


Fig.20. Testing filter design with an oscilloscope. 'Scope traces from points A and B are shown left (A above, B below).

itself is of no use at all. However, it does suffer a 180° phase shift as a function of frequency. By cascading two stages (Fig.19) it is possible to obtain a 180° phase shift at the frequency Fc. This phase shifted signal when mixed with the original will give a notch response due to the cancellation of the two signals.

Testing active filters is very easy if you have a swept sine wave generator and an XY oscilloscope (Fig.20). The frequency response appears as a linear amplitude versus log frequency display. It is generally possible to sweep five times a second, which gives an almost continuous display and allows you to see immediately the effect of any changes that you make to the filter.

ETI

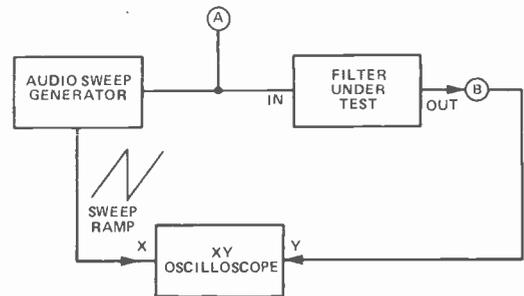

# 1999 A FUTURE HISTORY

Cross our palms with silver and see the future unfold. Beware of imitations. This is no guesstimate of what *might* happen – this *is* the future.

Using our very own time machine, a closely guarded secret of the ETI project team, we dispatched a team of reporters to 1999. They brought back stories of a world where World War III is history and robots are causing real problems.

Illustrated in full colour, ETI 1999 is a must for every future historian. Find out what tomorrow holds for you . . . . . now!

**£ 1.50**

Plus 30p postage and packing.  
Send your cheque/P.O. to  
Sales Office (Specials), Modmags Ltd,  
145 Charing Cross Road,  
London, WC2H 0EE

# MITRAD

MITRAD

QUARTZ L.C.D.s AT THEIR BEST!

MITRAD

## GENT'S CHRONO ALARM FRONT BUTTON


Brand new 1980 style. Basic working modes of chronograph. 24-hour alarm and dual time zone. Constant display of hours, mins, secs and weekday indication with am/pm, T2 and A1 flags. Date indication. The chrono runs to 1/10th sec, with the 1/10th's running along the bottom of the watch. It has a twelve hour capacity. The 24-hour alarm system is actuated for a full 60 seconds. Dual timing facilities give the watch the added touch of compactness. Back-light, closely woven adjustable stainless steel strap.



ONLY £15.50
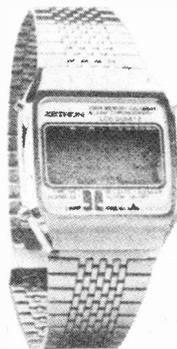
## GENT'S MEMORY CALENDAR ALARM CHRONO

LATEST TECHNOLOGY! Constant display of hours, mins, secs, weekday and snooze alarm indication. A further two optional display modes are available, one being the calendar and month, which can be increased or decreased to give the appropriate month of the year. A 1/100th sec chrono with split and lap mode facilities is built into the watch. A 24-hour alarm with a 10 minute snooze function is also standard to the watch. A further feature is the back-light and fully adjustable stainless steel strap.



VALUE AT £19.95


## GENT'S QUARTZ ANALOGUE

A truly superb timepiece with extreme accuracy. A choice of two colours on this outstanding watch are available, blue or white.

The calendar in the watch can be set to give a readout in either French or English with date indication being automatic.

An infinitely adjustable stainless-steel strap is built in as part of the watch.

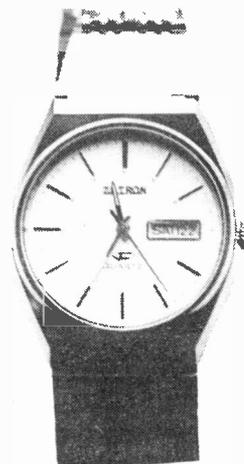The watch is fitted with a long-life battery and comes with luminous markings to aid night-time vision.



YES ONLY £19.95

## GENT'S ALARM CHRONO 12/24 CYCLE

A really superb watch and module. It can be set as a 12- or 24-hour watch with hours, mins, secs, am/pm and weekday indication always on display. A unique calendar is built into the watch. You can have month followed by date or date followed by month, it's entirely up to you. A 24-hour alarm can be set to any time within a 24-hour period.

The chronograph has a 12-hour capacity and runs at 1/10's. Split and lap mode facilities are available.

Battery hatch, mineral glass, long-life battery and a closely woven adjustable stain-



less steel strap finish the watch off with impeccable looks.

ONLY £16.50

## THINKING OF BUYING A NEW DIGITAL WATCH— THEN CONSULT OUR

FREE FULL-COLOUR CATALOGUE FIRST

TEL. OR WRITE FOR YOUR COPY (0536) 522024

## GENT'S FOUR-BUTTON ALARM LM40

A very compact and sleek-looking GENT'S Alarm Watch.

Constant display of Hours, Mins, and Secs., with an optional display of Month, Date and Weekday.

A very effective alarm is built in which can be set within a 24-hour period, and is activated for 60 seconds.

Back Light and a closely woven adjustable stainless-steel strap finish the watch off.

ONLY £10.25



## GENT'S CHRONOGRAPH

Probably the best looking chrono on the market. Constant display of hours, mins, secs with am/pm indication. Also month, date and weekday indication. 1/100th and 1/10th sec with split and lap mode facilities. Back-light, closely woven adjustable stainless steel strap.



SPECIAL £8.95

## LADIES' DRESS WATCH

An extremely popular ladies 5-function watch. Finished in gold.

Constant display of Hours and Mins, with Month and Date being available.

Auto-Calendar

Back Light and a closely woven adjustable strap.


£10.50



## LADIES' SUGARCOATED

Another superb ladies watch with that extremely popular sugar frosted finish. Links can easily be removed from the strap and the clasp has a spring mechanism built in to give a comfortable fitting. Constant display of hours and mins, with month, date, secs, auto calendar and back-light.

£10.50

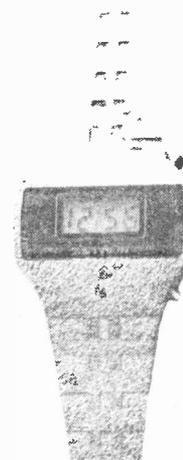

MITRAD WHERE RELIABILITY, STYLE AND ELEGANCE REALLY COUNT MITRAD

# MITRAD

MITRAD

QUARTZ L.C.D.s AT THEIR BEST

MITRAD

## GENT'S MELODY ALARM CHRONO DUAL TIME

This watch is super slim. Only 7mm thick, but has 5 independent working modes. (1) Normal watch. Hours, Mins., Secs., A.M./P.M. and mode square indication. The weekday can be set in any of three different languages, French, English and German.


(2) Countdown Alarm: Presetable to 24 hours, with the musical tune playing for 1 minute. (3) Ordinary alarm which can be set within a 24-hour period and lasting for 60 seconds.

(4) Dual timing facilities.

(5) Chronograph: This runs to a 1/100s. Freeze and split and lap mode facilities are standard.

This watch is finished in 3 micron gold and comes with a closed strap.

Back Light.

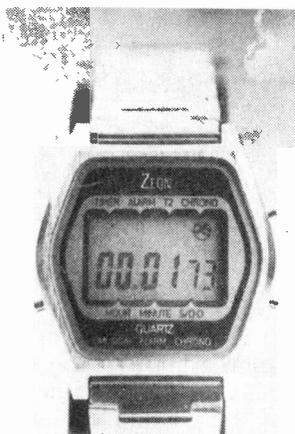

**SPECIALLY PRICED AT £14.95**

## ZEON DIGITAL ANALOGUE ALARM

★ EXCLUSIVE ★


We are proud to be able to offer you this scoop purchase. One of the finest pieces of modern technology.

The analogue section can be set as a conventional hand watch and is totally independent of the L.C.D. section.

The digital part of the watch has the following functions:

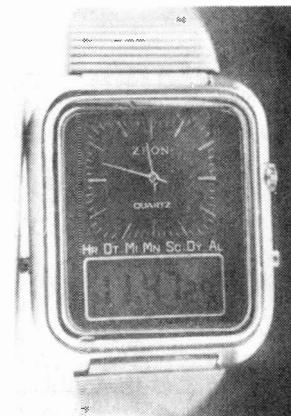1. Constant display of Hours, Mins. and Seconds.
2. Optional Display of Date, Month and Weekday.
3. A unique alarm system, which can be set to any time within 24 hours, and is actuated for a full 40 seconds. A five-minute snooze is also available.

The watch is finished off with a Backlight and an infinitely adjustable stainless-steel strap.



**BUY NOW  
AT £34.95**

## GENT'S CHRONOGRAPH SOLAR ALARM

The slimmest Chrono Solar Alarm in the World. Only 7mm thick.

This watch has a genuine solar panel. You can take the battery out and the watch will still function as normal. Battery hatch. Mineral glass.

Constant display of Hours, Mins. and Secs. with Date Flag. Optional display of Hours, Mins. and Date.

The alarm can be set to any time within a 24-hour period and is actuated for a full 60 seconds.

The chrono runs to a 1/10th Sec. with a maximum capacity of 24 hours. Lap Time and Freeze Facilities are available.

Dual timing facilities are readily available.

Back Light. Fully adjustable stainless-steel strap.

This watch is available in gold or silver.

**OFFERED AT £19.95**



## GENT'S MELODY MULTI-CHIME ALARM CHRONO

Latest technology! Constant display of hours, mins and secs, week-day, date and month with mode and chime indication display. The musical alarm once actuated plays the tune "Oh Suzanna". Two further alarm systems are incorporated in this outstanding watch: (i) 24-hour alarm, (ii) count-down alarm. The watch can be set to chime on every full hour. A 1/100th sec chrono is standard to the watch. Can be switched off. Mineral glass face. The watch also has a battery hatch backlight and infinitely adjustable stainless steel strap.



**VALUE AT £19.95**

MITRAD

THE UNRIVALLED RANGE

MITRAD

We are able yet again to offer you the above watches plus a complete quartz watch range. All at unrivalled prices. Just look at the following points:

- (i) 48-hour despatch guaranteed on both retail and trade orders.
- (ii) Full instructions and 12 month manufacturer's guarantee.
- (iii) Our own free back-up service.
- (iv) 10-day full money refund if not completely satisfied.
- (v) Free felt presentation case with each watch.

MITRAD

★ FULL COLOUR CATALOGUE NOW AVAILABLE ★

Write or phone for your free copy. Trade lists on application.

Earn £££s selling watches to all your friends. P/P per item 85p which includes insurance. Cheques or P.O.s made payable to Mitrad and sent to (Dept. ET1), 58 Windmill Avenue, Kettering, Northants, NN16 8PA.

**Telephone (0536) 522024**

---

---

# A HISTORY OF SPACECRAFT

Ian Graham takes a well illustrated look at Spacecraft past and present and discovers just how far we've come in the twenty three since Sputnik.

**O**n April 12th 1961, a charred ball weighing over 10,000 lbs lay in a field near the village of Smelovka. Inside lay Yuri Gagarin, the first man to orbit the Earth and begin Man's adventure in space. Gagarin's flight marked the culmination of a research programme going right back to the first artificial satellite, Sputnik 1. Less than a month after Sputnik 1 proved the orbital equations correct, Sputnik 2 carried the first live passenger into orbit (apart from stowaway bacteria on-board Sputnik 1). The first 'cosmonaut' was a dog called Laika.

America boldly went where only one man had gone before, when, barely a month after Gagarin, Alan Shepard made a fifteen minutes sub-orbital hop to a height of 116 miles. In February 1962 a silver-suited John Glenn wedged himself into the cramped confines of his Mercury 6 capsule and made the first three orbits of the American experience in space. By then, however, Russia had established a commanding lead. Herman Titov had already spent more than a day orbiting the Earth in Vostok 2. The list of Russian firsts continued — first double flight, first woman in space, first three-man craft, first space-walk, etc. The six Vostok flights (from April 1961 to June 1963) made 259 orbits, in comparison with a grand total of 34 orbits for the six Mercury flights from May 1961 to May 1963.


## Human Satellite


Gemini gave astronauts invaluable experience in long duration flight and the rendezvous and docking manoeuvres necessary for an Apollo-type moon mission and for future space station operations. In less than two years there were a staggering ten Gemini flights. In the same time Russia flew only one mission — Voshkod 2. (Voshkod 1 was the first three man spacecraft. It flew four years before the first Apollo. Voshkod 2 carried a crew of only two). It achieved yet another first for Russia — Alexei Leonov's space-walk. It was the first time a man had left his craft and orbited the Earth as a human satellite, albeit still tethered to his craft. Three months later Ed White spent 21 minutes outside his Gemini 4 spacecraft for America's first space-walk.

Gemini 3 carried the first computer into space. Although it was glossed over at the time, largely overshadowed by the impact of Leonov's space-walk, it was an important development in manned spaceflight. The astronaut was no longer a passenger carrying out predetermined routines or commands from the ground.

He could make independent decisions on, for example, course corrections based on information on position, thrust, etc from his on-board computer. In addition, whereas most of the Mercury systems were carried inside the pressurised compartment with the astronaut, many of the Gemini systems were removed to a separate instrument module. The astronaut benefited by gaining a more spacious cabin and the system became more flexible, allowing the astronaut to work outside the craft on any defective instrument. Gemini 5, an eight day flight, proved that men could work in space without any adverse effects for the duration of a moon-landing mission.

Rendezvous and docking manoeuvres were practiced between two manned Gemini craft and between Gemini and the unmanned Lockheed Agena target vehicle. Gemini 6 should have rendezvoused with an Agena but when the Agena failed it used Gemini 7 instead. The craft manoeuvred to within 2m of each other. Gemini 8 achieved the first docking, but the operation nearly ended in disaster. Shortly after docking, a jammed open thruster rocket started the couplet tumbling faster and faster. The crew, Neil Armstrong and David Scott, broke free from the target vehicle and ended the mission two days earlier than planned — survivors of the first major emergency in space. Gemini 11 carried out the first computer-controlled re-entry.

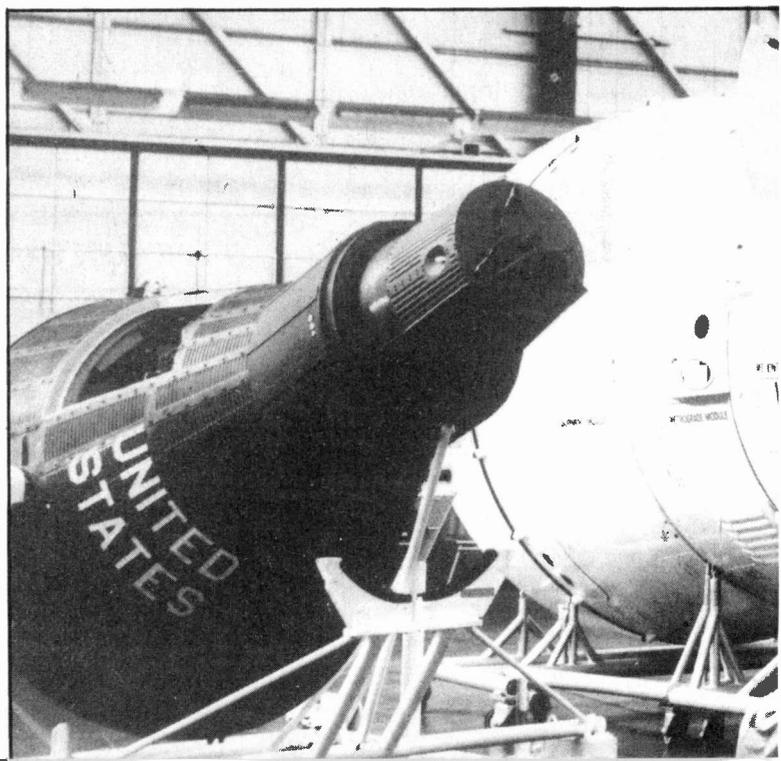

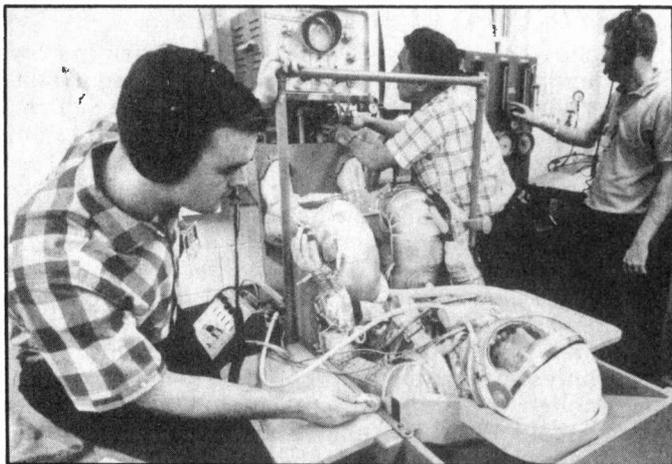


Before flight a Mercury astronaut's pressure suit was thoroughly tested.
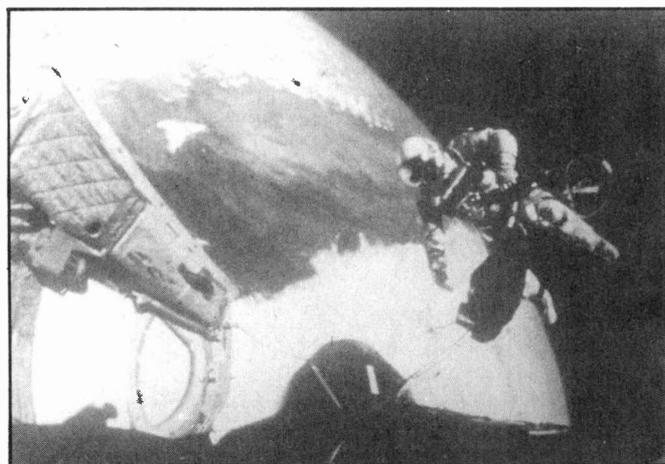
## Apollo

The next stage in America's successful space programme, now well ahead of Russia's, was the flight testing of the Apollo moon-landing systems and procedures. A Saturn 1 lifted the first Apollo Command Module into Earth orbit in May 1964. The first Apollo crew (Virgil Grissom, Roger Chaffee and Ed White) climbed aboard Apollo 204 for a countdown rehearsal on January 27th, 1967 and the Command Module hatch was bolted down. A fire started unseen, somewhere below Grissom's feet and spread to nylon netting, fastenings and insulation material. In the 100% oxygen atmosphere it took only 15 seconds from Chaffee's first warning for the fire to burn through to the outer shell of the spacecraft. All three astronauts were dead before the hatch could be opened.

The Apollo programme was immediately suspended. A quick release mechanism was developed for the access hatch. Although pure oxygen continued to be used in space, ground operations were carried out with the safer 60/40 oxygen/nitrogen atmosphere (gradually changed to 100% oxygen after launch by the environmental control system). Less flammable materials were used in the cabin. Where non-metallic materials had to be used, they were positioned so as to behave as a fire break. The design of electrical equipment, location



The first American astronaut to make a space-walk — Ed White in orbit around Mother Earth.

of wiring and equipment checking procedures were also reviewed.

Nearly two years after the fire, the Apollo programme was resumed. Apollo 7 successfully tested the hardware in Earth orbit for eleven days in October 1968. Only two months later NASA reached for the moon. Apollo 8 was the first manned craft to be launched by the giant Saturn 5, necessary for the circumlunar mission. You may remember Commander Borman's reading of a passage from Genesis against the backdrop of another world on Christmas morning, 1968. Borman, Lovell and Anders could not have landed on the moon if they'd wanted to — they did not carry a Lunar Module.


Apollo 9, the first manned mission with a Lunar Module, remained in Earth orbit rehearsing rendezvous and docking manoeuvres with the LEM (Lunar Excursion Module). While Schweickart was standing on the LEM porch he took the memorable photographs of Scott's head and shoulders out of the CM access hatch. Apollo 10 combined the experience gained from Apollo 8 and 9, taking the LEM to within 15 kms of the moon's surface.

## Tranquillity Base

Approximately one million people were at Cape Canaveral on July 16th 1969 to see Apollo 11 blast off for the moon. The television audience was around 500 million. After a trouble-free flight, Armstrong and Aldrin separated their Lunar Module from Collins' Command Module and began their descent. Armstrong interrupted the automatic landing sequence and flew the LEM manually when he saw boulders ahead, making it impossible to land. He finally touched down with only 2% of his fuel left.

I've met many, many people (not all space nuts like me) who sat up all night to watch the fuzzy image of Armstrong descending the LEM ladder and stepping off the landing pad on to the dusty surface of another world at 3.56 am on July 21st, 1969. Aldrin joined him and together they loped around the surface placing scientific instruments and collecting samples. On their return to Earth the astronauts put on Biological Insulation Garments and were transferred to the Mobile Quarantine Facility to isolate any bacteria which they may have brought back from the moon.

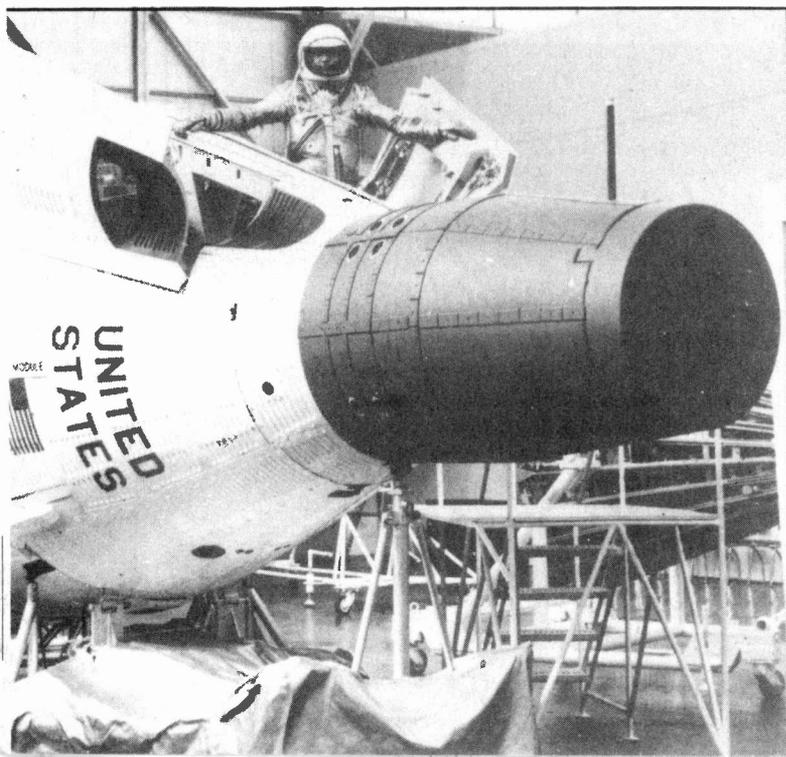The Mercury capsule was just large enough to carry one astronaut. By comparison Gemini was a deluxe model.





Apollo 10's Saturn 5 stands on the launch pad atop its mammoth transporter.



Edwin Aldrin deploys the Apollo 11 solar wind experiment.

## Strike A Light

Apollo 12 and 13 were more eventful than the first moon landing. Apollo 12 was struck by lightning at take-off. Fortunately, neither the spacecraft nor the Saturn 5 launch vehicle were damaged. When the Apollo 13 Command, Service and Lunar Modules were more than 200,000 miles from Earth on their way to the moon, the astronauts felt a jolt and saw power and oxygen readings rapidly fall on their control panel. The moon-landing was abandoned. To conserve fuel it was decided to let the spacecraft swing round the moon and return to Earth. The crew moved into the Lunar Module, now aptly nicknamed the 'lifeboat'. Systems were powered down — the only way that the craft could be kept operational long enough for the return to Earth. Reduced power meant a cold, dimly lit cabin. The LEM air conditioner could not cope with the extra volume of both CM and docking tunnel. To keep carbon dioxide down to a safe level, the crew improvised an air conditioner from materials on board.


When the Service Module was discarded just before re-entry, the crew saw for the first time the extent of the damage. One panel (4m x 1.8m) had been blown away completely, exposing a tangle of pipes and tanks. It was later found that heater switches had welded closed causing an oxygen tank to overheat and explode. It wasn't known if the explosion had damaged the CM's heat shield. However, re-entry went as planned and the crew of Apollo 13, launched at 13.13 (Houston time) on April 13th, returned safely to Earth. In 1972, four flights later, the programme was brought to a close with Apollo 17, the last of three missions intended to devote more energy to Apollo's scientific potential. Despite six moon landings and the return of over 380 Kg of rock samples, the origin of the moon is still not conclusively proven.

Meanwhile in the USSR
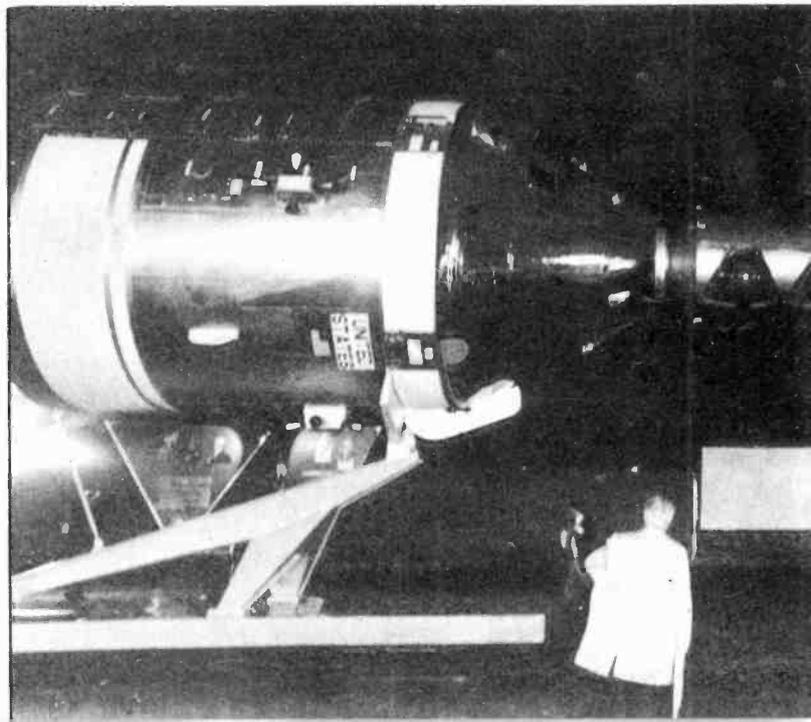
## Meanwhile In The USSR

Like Apollo, the Soviet Soyuz programme had its setbacks. The test flight of Soyuz 1 seems to have been cut short. After re-entry, the parachutes failed to open properly and the spacecraft crashed to Earth, killing the one-man crew (Vladimir Komarov).

Further flights achieved the first docking of two manned craft and the first welding in space. Soyuz 11 (June



1971) spent 23 days docked with Salyut 1. The flight went well until re-entry, when contact with the crew was lost. On opening the access hatch after a normal re-entry, the three man crew was found to be dead. The craft had suffered rapid depressurisation in the upper atmosphere. From then on the crew wore spacesuits (during re-entry at least) instead of light overalls and flying helmets. The additional life support gear carried meant that the crew had to be reduced from three to two.

The Soyuz programme continued, successfully carrying out astronomical, Earth resources, EVA (space-walking) and hardware experiments.

The first post-launch abort occurred several minutes after what would have been Soyuz 18 lifted off. When the third stage began to go astray, the spacecraft was automatically detached from the launcher and brought down. The next flight (Soyuz 18) prepared the way for the joint US/USSR Apollo/Soyuz link-up.

The Apollo/Soyuz Test Project (ASTP) was agreed on as early as 1972, with a planned launch date of July 15th 1975. Both craft did, in fact, take off on July 15th 1975 and docked for a total of 48 hours. Minor problems included failure of the Soyuz TV system. The huge television audience had to be content with pictures of Soyuz taken from Apollo. Stafford became the first US astronaut to fly in a Russian Spacecraft.


### Secret And Wet

Soyuz 22 achieved the dubious honour of being, it is believed, the first manned spy satellite. Its unusual orbit took it over a major NATO exercise. Soyuz 23 achieved yet another first — the first Soviet splashdown. During its descent high winds pushed the craft off course and into a lake. The crew were unhurt.
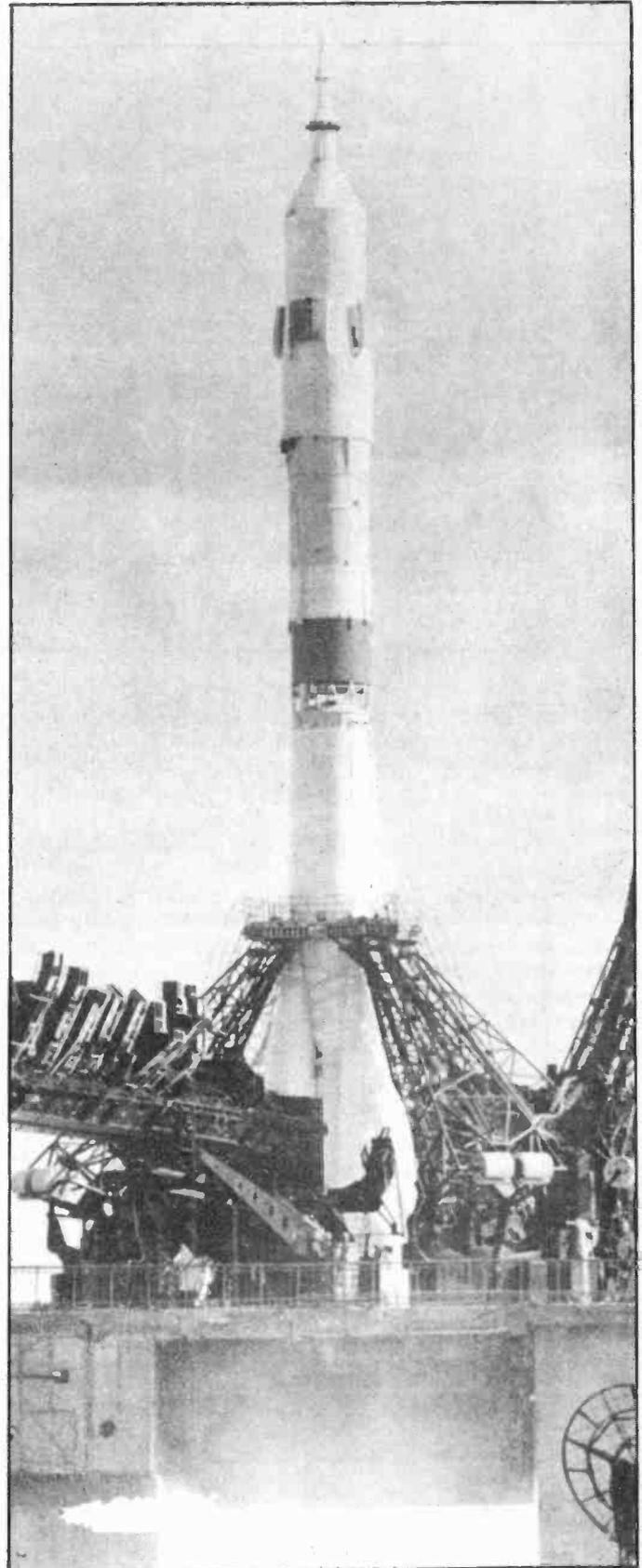
### Stations In Space


In the early to mid seventies, both the Soviet and American space programmes moved into their second generation. The hugely expensive one-shot all or nothing flight gave way to the space station. Once again Russia led the way with Salyut 1 (April 1971). The first few years of the programme were beset with technical problems with both the Salyut space stations and the Soyuz crew transporters, but Soviet persistence had paid off by 1975. The Soyuz 18 crew set up a new Soviet duration record of almost 64 days on-board Salyut 4.

Unlike Skylab, there appear to be two distinct types



The Russian end of the Apollo/Soyuz Test Project — Soyuz, still clamped down to the launch pad.

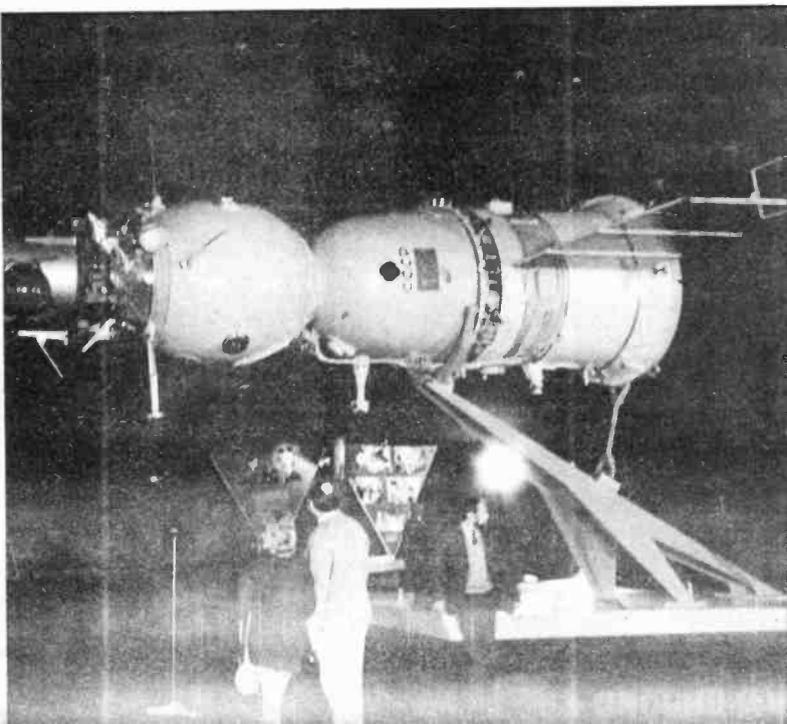The Soyuz/Apollo spacecraft cluster with the newly designed docking module.





The first captive flight of America's Space Shuttle on the back of a NASA 747.

of Salyut craft. One performs a civilian role, similar to Skylab, but the other is part of a separate military programme.

## Skylab

In May 1973 Skylab 1 lifted off, launch vibration being so great as to seriously damage the craft. The meteoroid/thermal shield had been torn away completely, turning the workshop interior into an orbiting oven. The debris from the shield had also ripped off one of the solar panels, giving the spacecraft its familiar lop-sided appearance.

The laboratory was only made habitable by the installation, by the Skylab 2 crew, of a makeshift sun-shade over the workshop.

## Life Out There

Astronauts complained of stuffiness and congestion of the inner ear for as long as twelve weeks. Red blood cell production was disturbed for about nine weeks. Hygiene and waste management seemed to constitute the most annoying problems. Urine was spilled. Astronauts found if they missed a meal they would experience flu-like symptoms. Heavy exercise helped

crews make more rapid recovery after their return to Earth. Health problems amounted to minor skin infections and eye trouble.


Results from the first few years of space station operation will themselves take years to analyse. The Skylab crews brought back over 40,000 pictures of the Earth's surface and over 180,000 frames of film of the Sun. They also carried out melting, welding and brazing experiments. One of the Earth Resources experiments identified a possible deposit of copper in Nevada. It may be worth several billions of dollars — more than the cost of the entire space programme to date.


## Planes In Space

The most exciting development so far in space hardware is that of the Space Shuttle — a plane capable of being launched with the aid of strap-on boosters, flying on to orbit and returning to Earth, landing like a conventional aircraft.

Although the Commander and Pilot could take

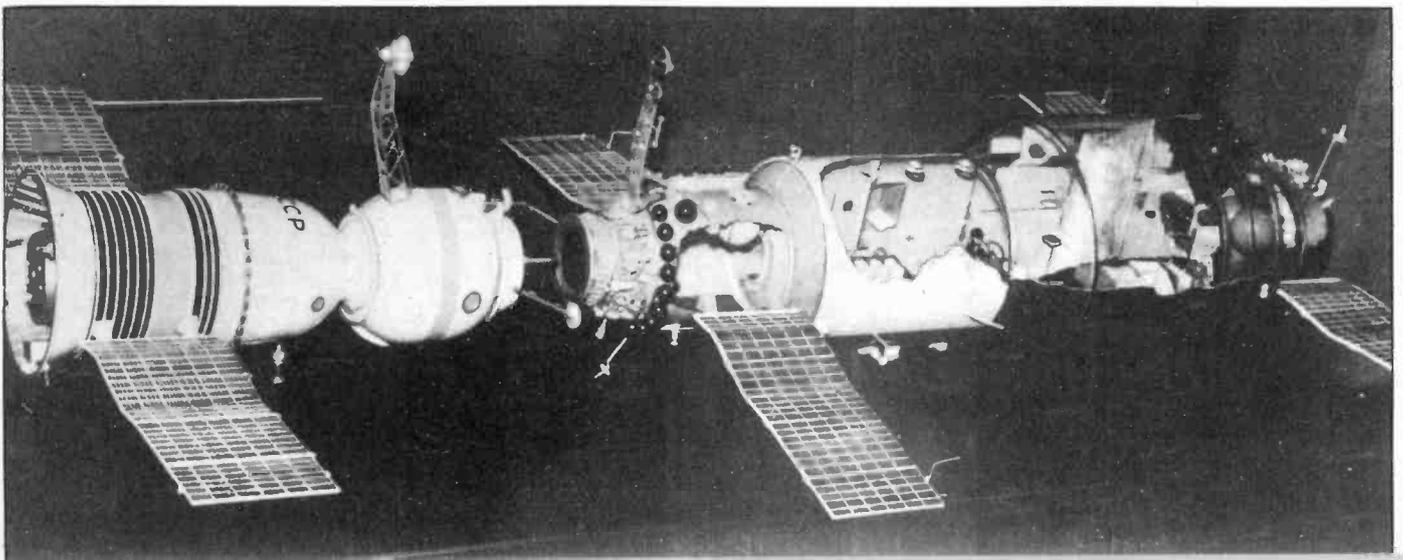A cut-away model of the Salyut space station with Soyuz 11.



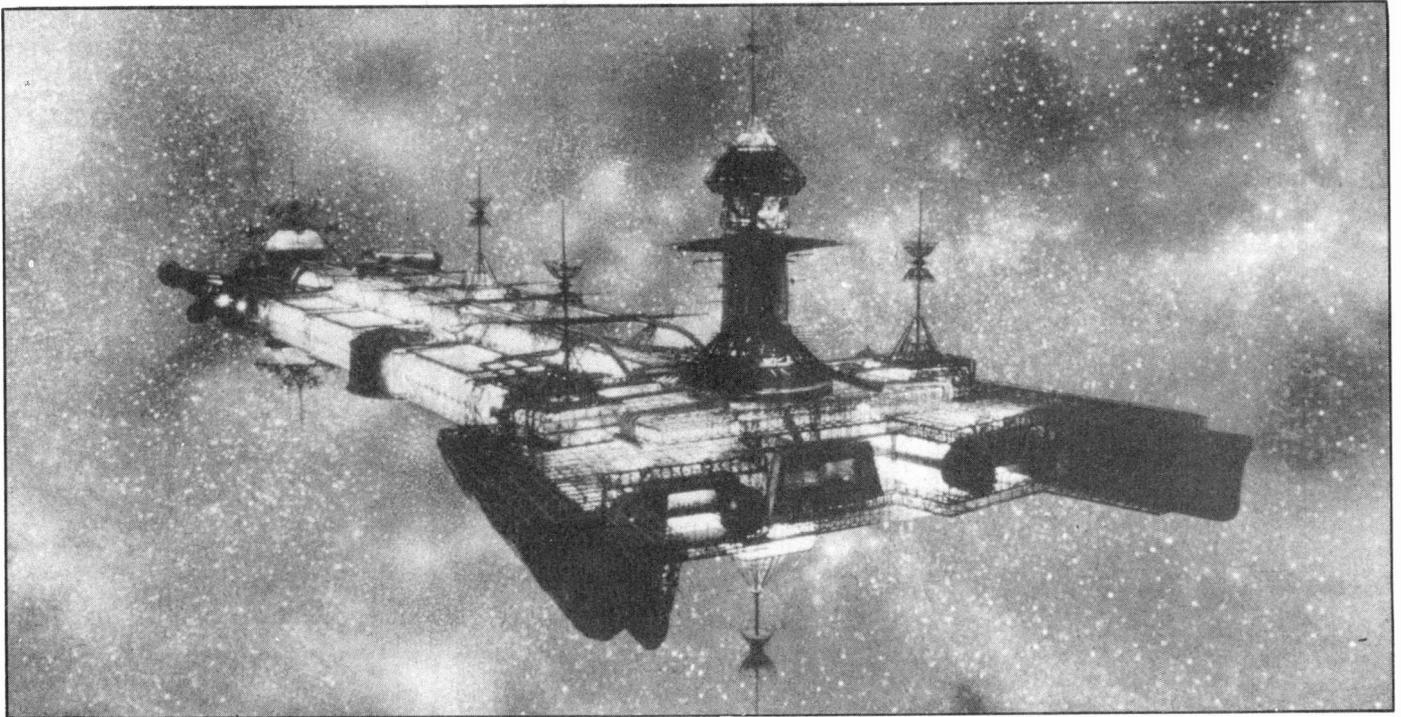

The shape of things to come — the mile-long 'Palomino' spacecraft featured in Walt Disney's 'The Black Hole'.

manual control, the Space Shuttle is such a complex flying machine that it is usually flown with the aid of computers or completely under computer control.

After take-off the two boosters fall away and are recovered from the ocean to be used again. The huge external tank, whose fuel powers the Orbiter's three main engines almost to orbit, is discarded and breaks up in the atmosphere. Once in orbit, 44 tiny rocket motors position the Shuttle accurately.

With the cargo doors open, satellites can be launched or collected for repair by using the Remote Manipulator System — a remotely controlled arm made by Spar Aerospace in Canada.

A variety of materials protect the craft from the enormous temperatures of re-entry. The nose of the Orbiter reaches over 1400°C. Normally the crew will not interrupt the completely automatic landing sequence. After landing, the Orbiter is serviced and repositioned on the launch pad for its next flight.

Technical problems have caused a serious of post-

ponements to the first launch, which is now not expected until at least November 1980.

### The Competition

America may appear to be way ahead of the Soviet Union, but there is already news of a Soviet Space Shuttle. So far very little information has been released. Known as the Raketoplan (Rocket Plane), it measures 60m long (probably including the launcher) and 8m across with three main engines. A prototype has already been test flown, dropped from a Tu-95 bomber.

### Coming Soon


What does the future hold? The Space Shuttle is the first spacecraft to offer the possibility of carrying into orbit raw materials of prefabricated elements from which larger structures can be constructed. Film buffs may recall the Space Shuttle approaching the spinning wheel station in Stanley Kubrick's film of Arthur C Clarke's '2001: A Space Odyssey'. Which of the current rash of space westerns will prove as prophetic as 2001 is sure to be — 'The Black Hole' perhaps, with its spaceship modelled on Brighton pier, or Star Wars, with its World War I dog fights in space?

Table 1. A comparison of manned spacecraft to date.

	MERCURY	GEMINI	APOLLO	SKYLAB	SHUTTLE	VOSTOK	VOSHKOD	SOYUZ	SALYUT
LAUNCH WEIGHT (kg)	1935	3792	5558	90265	68000	2400	5320	6000	18700
BASE DIAMETER (m)	1.89	3.05	3.90	6.58	.	2.3	.	2.63	4.1
LENGTH (m)	2.90	5.60	3.48	36.12	37	2.3	.	10.63	22
WORK VOLUME (m <sup>3</sup> )	.	1.558	5.97	361.4	71.5	.	.	9	100
WINGSPAN (m)	.	.	.	.	23.7	.	.	10.06	.

ETI
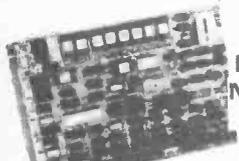
## NASCOM-2 MICRO-COMPUTER FREE 16k RAM Board New improved RAM B



only **£335**  
+ VAT  
IMMEDIATE  
DELIVERY



780A 8 bit. This will run at 4 Mhz but is selected between 2/4/Mhz.  
On-board, addressable memory, 2K  
2K Monitor — Nas-sys 1. 1K Video  
RAM  
(MK 4118), 1K work space/User  
RAM  
(MK 4118) (8K Microsoft Basic)  
(MK 3600 ROM) (8K Static RAM/  
2708E).

**Microprocessors** Z80A, 8 bit CPU. This will run at 4Mhz but is selectable between 2/4 Mhz. This CPU has now been generally accepted as the most powerful 8 bit processor on the market.

### INTERFACE

**Keyboard** New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding.

**T.V.** The lv peak to peak signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T V.

**I.O.** On-board UART (Int. 6402) which provides serial handling for the on-board cassette interface or the RS232/20mA teletype interface.

The cassette interface is Kansas City standard at either 300 or 1200 baud. There is a link option on the NASCOM-2 for 2400 Baud.

The RS232 and 20mA loop connector will interface directly into any standard teletype.


The input and output sides of the UART are independently switchable between any of the options — i.e. it is possible to have input on the cassette and output on the printer.

**PIO** There is also a totally uncommitted Parallel I/O (MK 3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.

**Documentation** Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.

**Basic** The Nascom 2 contains a full 8K Microsoft Basic in one Rom chip with additional features like DEEK, DOKE, SET-RESET for simple programming.

## SYSTEM KITS from £225

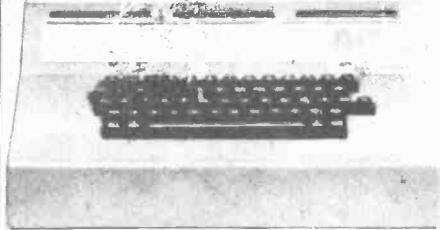

### Microprocessor board\* (Nascom 2)

4MHz Z80 CPU, TV or Video + 1200 baud  
Kansas City + Serial RS 232 printer  
Interfaces; Keyboard; 128 character ASCII plus  
128 Graphics in 2 x 2K ROM; free 16-way  
parallel port; 8k BASIC; NAS SYS operating  
monitor. £280 built and tested.

### Firmware & MOS ICs

Zeap Assembler (4, 1K x 8 EPROMS) £50  
Nas Pen text editor (2, 1K x 8 EPROMS) £30

### Floppy disc system

Double sided, double density 5 1/4 in disc giving  
280K bytes formatted, including controller  
board /PSU /Housing and interconnects. £480.  
Controller board £127.50 Second Disc £240.  
CP/M £80.

### System 80 housing

High strength GRP moulding  
Accepts 12 x 8 Nascom 2 CPU board, four 8 x 8  
expansion boards £85 incl frame racking,  
interconnects and motherboard.

### Expansion Boards\* (in kit form)

16K RAM £127.50 • 32K RAM £175  
48K RAM £220  
High Resolution Programmable Graphics £90  
Colour Board Kit £140  
High Resolution Colour add on £37.50

All prices subject to VAT (add 15%)

No more slaving over a hot soldering iron! The Nascom 1 is now supplied BUILT!  
Britain's biggest small system is available fully constructed for you to slot into your own housing for the ridiculously low price of £140 plus VAT (kit price still only £125 plus VAT).

## nascom-1

12" x 8" PCB carrying 6LSI MOS packages, 16 1K MOS memory packages and 33 TTL packages. There is on-board interface for UHF or unmodulated video and cassette or teletype. The 4K memory block is assigned to the operating system, video display and Eprom option socket, leaving a 1K user RAM.


The MPU is the standard Z80 which is capable of executing 158 instructions including all 8080 code.

NASCOM-1  
**£125** + VAT  
P&P £1.50

## NASCOM PRODUCT LIST + VAT

I/O board kit less I/O chips	45.00
UART + BAUD rate generator + crystal for I/O board	16.00
CTC — MK3882 multiple interrupt driven clock generator for I/O board	8.25
P/I/O — MK3881 + interconnect for I/O board	8.50
P/I/O interconnect only (for I/O board)	3.80
Econographics kit for additional 128 characters (N1 only)	30.00
2708/2716 Programmer suitable for N1 and N2 under NAS-SYS	20.95 + VAT
Nascom 19" rack mounting card frame for N1 and N2	32.50
Nas-DA disassembler 3 EPROM for Nas-sys	37.50
MK36271 8K BASIC in 8K x 8 ROM	40.00
Naspen VS in 2 EPROM	30.00
Nas-sys monitor in 2 EPROM	25.00
NASBUG T2 1 x EPROM	12.50
Nasbug T4 2 x EPROM	25.00
Tiny Basic 2 x EPROM	25.00
Super Tiny Basic 3 x EPROM	37.50
Super Tiny Basic upgrade 1 x EPROM	12.50
<b>Tape Software</b>	
ZEAP 1, 2 tape and documentation for N1	30.00
ZEAP 2 tape and documentation for Nas-sys	30.00
8K BASIC tape and documentation for N1	15.00
<b>MEMORIES Discounts 10% for 4, 15% for 8, 20% for 16</b>	
MK3880 (Z80) for N1	7.50
MK3880-N4 (Z80A) for N2	7.95
MK4116 16K x 1 dynamic RAM	7.50
MK4027 4K x 1 dynamic RAM	2.25
2102 1K x 1 static RAM	1.00
4118 1K x 8 static RAM	12.75
Unprogrammed 2708	7.50
Unprogrammed 2716	19.95
IM6402 UART	4.50
2114 1K x 4 Static RAM	3.95
8080A	5.25

## NASCOM IMP

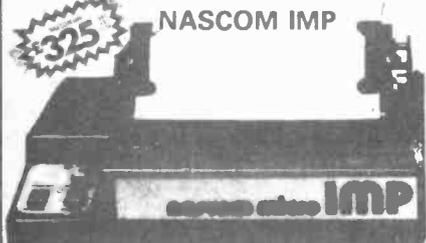

### PLAIN PAPER PRINTER

Fully built and housed in a stylish enclosure for just **£325** plus VAT. Interfaces with all micro computers

The Nascom IMP (Impact Matrix Printer) features are

- 60 lines per minute
- 80 characters per line
- Bi-directional printing
- 10 line print buffer
- Automatic CR LF
- 96 character ASCII set (including upper lower case \$ £)
- Accepts 8 1/2" paper (pressure feed)
- Accepts 9 1/2" paper (tractor feed)
- Tractor pressure feed
- Baud rate from 110 to 9600
- External signal for optional synchronisation of baud rate

**IDEAL FOR WORD PROCESSING**

## COMPUTER KEYBOARDS



**TASA** 56 key touch sensitive keyboard. All ASCII characters including control keys. Parallel output with strobe. Shift lock. Keys coded in 3 colours to indicate function. 18 V DC at 35 mA. 15" x 6.25" x 0.385" thick. Black resin encapsulated.  
**£49.50 + VAT**

**Star Devices** Mk III 71 key touch sensitive keyboard. With numeric pad. All ASCII characters including control keys. Auto key repeat. Parallel output with strobe. Shift lock with indicator LED. Built in beeper with Javel control. 5 V DC at 300 mA. 15" x 7" x 1.25". Grey case with white keys on blue.  
**£48.50 + VAT**


**Carter** 57 key ASCII keyboard. Conventional keyboard. 128 ASCII characters including control keys. Parallel output with strobe. Shift lock + 5V and -12 V DC. 12" x 5.5" x 1.5". Black keys with white legends.  
**£39.34 + VAT.**

**FERRANTI** — "SIZE 14 x 6 x 3" SLOPING FRONT

55 Key ASCII Coded in steel case. Complete with Plug and Cable with circuit to convert to T T L levels. In good condition at only **£25 + VAT**. P/P £2.50

## CENTRONICS QUICK PRINTER

LIST PRICE  
£459.00  
INCL. VAT

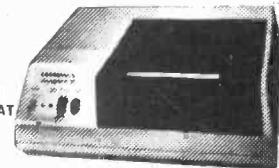

OUR PRICE  
£195.00  
+ VAT

### EXCLUSIVE TO HENRY'S 50% OFF MAKER'S PRICE

for: • Software selectable 20, 40 and 80 column using 120mm aluminium-ised paper, 1 roll supplied.

**PET**, • 150 lines per minute.

**NASCOM** Centronics parallel data interface for Nascom, Tandy, etc.

• 240 volt mains input, ASCII character set

• Paper feed, and on/off select switches

• 'BELL' signal. Weight 10lbs

Size: 13" x 10 1/2" x 4 1/2"

• New, boxed and fully guaranteed

**POST PAID Price £195.00 + VAT**

See **COMPUTING TODAY** Recommendations

March / May issues

# TANGERINE

COMPUTER SYSTEMS LONDON STOCKISTS

Microtan 65 Kit, Inc VAT	£79.35
Microtan 65 Assembled, incl. VAT	£90.85
Tanex (min. con) Kit, incl. VAT	£49.45
Tanex Assembled, incl. VAT	£60.95

Lower case pack, incl. VAT	£10.90
Chunky Graphics Pack, incl. VAT	£7.50
20 Way Keypad, incl. VAT	£11.50
Mini-mother board, incl. VAT	£9.95

Complete Tangerine range available

SEND FOR COMPLETE COMPUTER BROCHURE FREEPOST TO ADDRESS BELOW

Your London & National Nascom Distributor.  
Export Orders deduct VAT, but add 5% carriage  
Official Export & Educational Orders welcome  
Our Telex 262284 Mono Ref. 1400 Transonics

ADD VAT  
15%  
TO YOUR  
ORDER  
EXCEPT  
WHERE  
STATED




**Henry's**

Computer Kit Division  
404 Edgware Road, London W2 1ED, England I.E.D.  
01-402 6822



# 'TUSCAN' FROM TRANSAM

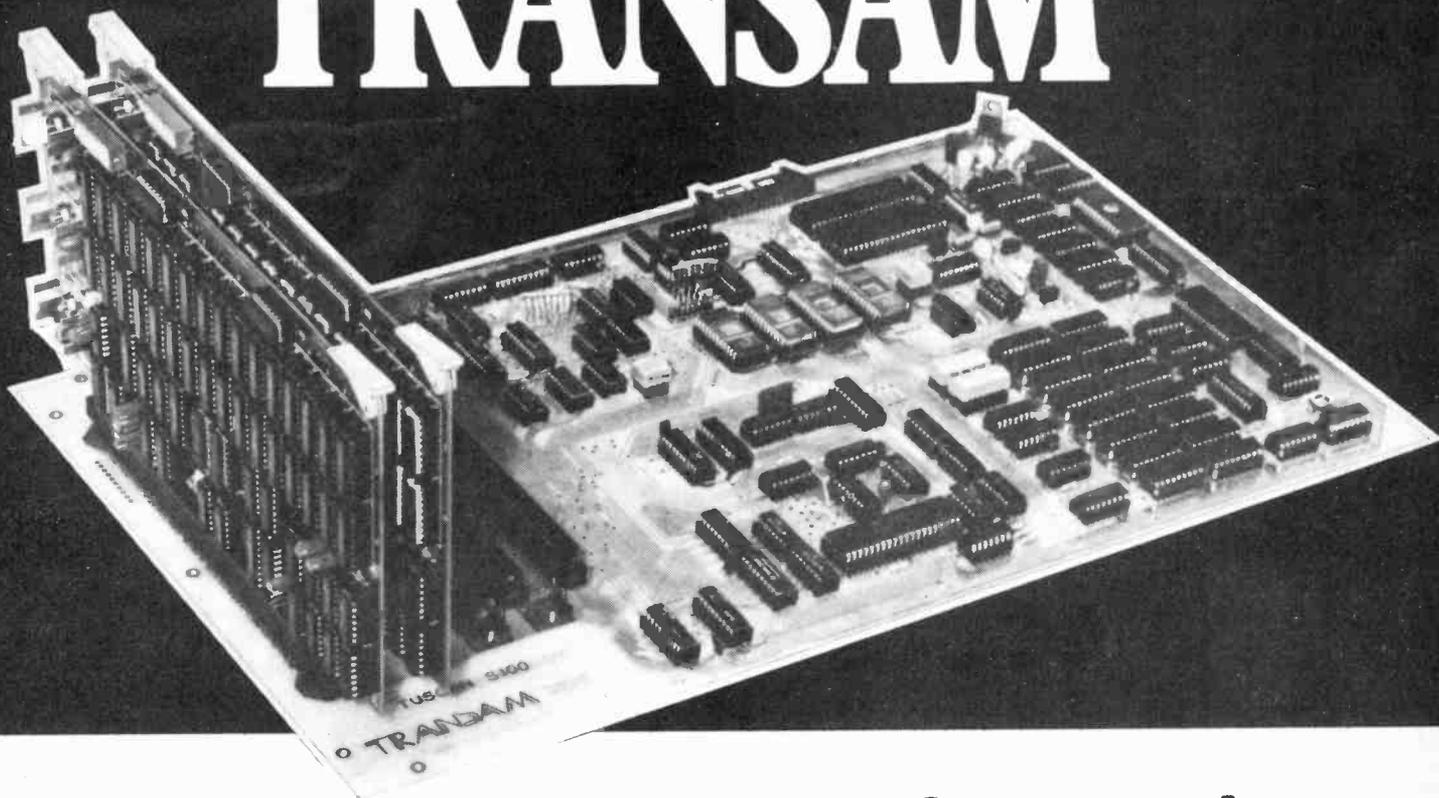

## Take a step up to your next Computer!

### THE CONCEPT

How many ways are there to build an S100 system? Not many, and all expensive. TUSCAN changes all that.

Five S100 boards on one single board—just for starters. Plus five extra slots for future expansion.

What a combination! Z80 and S100 with the TRANSAM total package of system and applications software.

How do we do it? Our prices start at £195 and you can build up in easy stages to a fully CP/M compatible disc based system. Something to think about!

### THE HARDWARE

The first Z80 single board computer with integral S100 expansion. British designed to the new IEEE (8 BIT) S100 specification, the TUSCAN offers total system flexibility. A flexibility available now.

The board holds the equivalent of a Z80 cpu card, 8k ram, 8k rom video and I/O cards with 5 spare S100 expansion slots and offers a price/performance ratio which is hard to beat.

Just compare our price with a commercial S100 ten slot motherboard with this specification.

### THE SOFTWARE

TUSCAN offers the user the choice of system monitor, editor, resident 8k basic, resident Pascal compiler or full CP/M disk operating system. All options are upwards

compatible and fully supported with applications software. Both 5¼" and 8" drives are supported in double density.

### THE PACKAGE

TUSCAN is available in kit form or assembled. With several hardware and software options to suit your requirements and budget. Attractive desk top case also available holds 2 x 5¼" Drives.

# TRANSAM

## NOBODY DOES IT BETTER!

Send to Transam Components Ltd., 12 Chapel Street, London NW1

I am interested in the TUSCAN Z80 based single board computer with S100 expansion and enclose a S.A.E. for further details.

Name \_\_\_\_\_

Address \_\_\_\_\_


Telephone \_\_\_\_\_

# ANTI~ MATTER

Does antimatter really exist or is it a figment of your imagination? Have you an antimatter double in another universe? A.S. Lipson explains.

**A**ntimatter is, figuratively speaking, the very stuff of which science fiction is made. Most of us have heard of it somewhere or other, but the most we actually know about it can be summarised in the immortal sentence from a TV series that will remain un-named, 'Ye cannae mix matter with antimatter, Captain. . .'. So what is this stuff? If it's 'antimatter' does it have 'antiweight'? Has it actually been made? Read on . . .

In 1928, a British physicist, Paul Dirac, had developed an equation which seemed to solve an awful lot of the problems current in physics at the time. (Among these was the prediction and explanation of a quantity known as the 'giromagnetic ratio' of the electron — but that is really another story.) There was only one slight snag. In addition to ordinary matter, the equation seemed to be saying something about something rather different — a sort of 'negative energy' particle, previously unknown. Well, to cut a long story short, this eventually led to a theoretical understanding of what became known as 'antimatter'. The only thing left to do was to look for it and in due course antimatter was actually found! (Physicists are

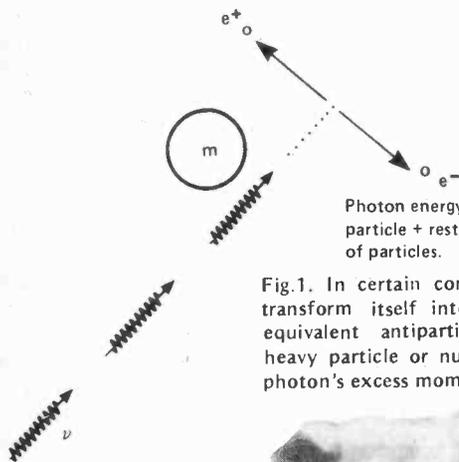

Photon energy = recoil energy of heavy particle + rest mass energy of particles + kinetic energy of particles.

Fig.1. In certain conditions, a photon can spontaneously transform itself into an electron and a positron (its equivalent antiparticle). The photon must pass by a heavy particle or nucleus which absorbs most of the photon's excess momentum.

ingenious fellows; they have to be to get their grants.) In fact, it turned out that antimatter had already been noticed in sub-atomic reactions, but had been interpreted as anomalous results!

## Doing The Impossible

We have said that antimatter was found. It would be more correct to say that antimatter equivalents of sub-atomic particles were found. It all started off with the antimatter equivalent of the electron, in fact, and the people involved with its discovery were so excited about it that, instead of just calling it an 'anti-electron', they gave it a special name — the positron.

It wasn't long before other 'anti-particles' began to be discovered. Corresponding to the already known proton and neutron, which exist in the nuclei of atoms, there were an 'anti-proton' and 'anti-neutron'. In fact, right through to the present day, as more and more sub-atomic particles were discovered, it has been found that each has, corresponding to it, an anti-particle of equal mass (with the exception of a few particles which appear to be their own anti-particles). This was exciting! If every particle known had a corresponding anti-particle, then just as ordinary matter is made up of atoms, themselves made up of sub-atomic particles, it might be possible for there to be matter which was in the same way made up of 'anti-atoms', which would themselves be made up of anti-particles. . . Antimatter! Fine. There was just one small problem — anti-matter in any form, even just anti-particles, isn't very easy to contain. In fact, it would probably be fair to say that containing anti-matter is one of the closest things to 'impossible' that the physicists have cooked up yet. To understand this, we'll have to go right back to the discovery of the positron. . .

## Disappearing Act

So far, we have completely omitted to say exactly what it is that is so special about antimatter. We can find this out most easily by looking at the way the positron — the 'anti-electron' — behaves. Now, the positron had a few rather interesting properties. In every way possible, it seemed to be the exact opposite of the electron; whereas the latter was negatively charged, the positron was positively charged (hence its name) and so on. The positron did not have negative mass, though. Negative mass, so far, is still in the realms of science fiction. Antimatter has positive mass, and hence, weight. This was interesting enough as it was, but things only really started to get going when a positron met an electron. If this happened the two particles would disappear into nowhere and a high energy particle of light, or 'photon' would be created. This was, in fact, an actual demonstration of the truth of Einstein's equation  $E = mc^2$ , which says that mass and energy are equivalent. Under the right circumstances (such as meeting antimatter) mass can be turned into energy. When an electron collides with a positron, then the mass in each of them gets turned into pure energy and this is given off in the form of light photons. Pretty impressive eh? The same thing happens when other particles meet their own anti-particles; they disappear and all their mass is turned into energy, which is given off in the form of photons. The more massive the sub-atomic particle, the more energy is contained in the photons. When a proton and anti-proton meet and 'mutually annihilate', for instance, the energy produced is 1836 times as much as that produced when an electron and positron meet, because the proton and anti-proton have masses 1836 times as great as the electron and positron.

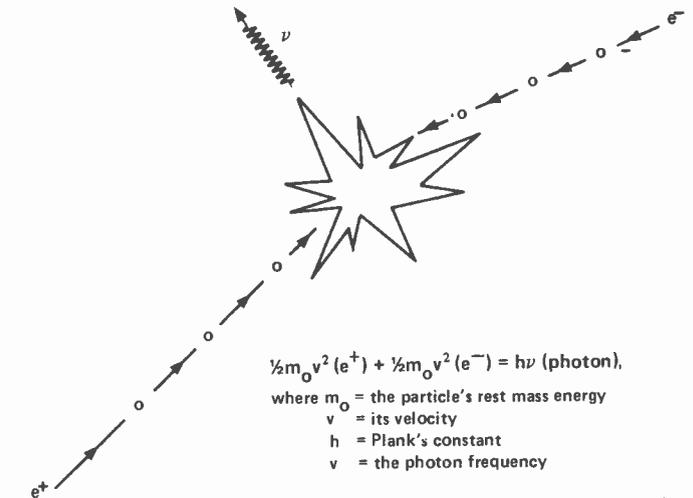


Fig.2. When an electron and positron meet, they annihilate one another and produce a photon whose energy ( $E=h\nu$ ) equals the combined rest mass energies of the particles.

## Let There Be Light

It now becomes apparent why it is so difficult to contain antimatter in normal containers; if we tried to do so, the positrons would quickly meet electrons, the anti-protons would meet protons and so on. All in all, the antimatter, together with an equal mass of the container, or whatever else was handy, would disappear and a lot of energy would be produced. A lot of energy. According to Einstein's equation (which has been very thoroughly tested), even a very small amount of mass, is equivalent to an incredibly large amount of energy. If a matchstick could be completely turned to energy, there would be enough produced to keep a 100 watt light bulb burning brightly for several centuries!

So far it looks as though the only likely way of containing antimatter would be to hold it in very strong magnetic fields, but the technique is far from perfected. Even if we could contain it easily, which so far we can't, there would remain the problem of obtaining antimatter in reasonable quantities. It is extremely rare and when it is found, (or made, in high energy particle accelerators) it always consists of sub-atomic particles; nothing anything as complicated as 'anti-atoms'. Certainly, antimatter has not been made in sufficiently large quantities even to weigh, with the most sensitive instruments available — supposing that we could weigh it without it reacting with matter and producing enough energy to blow up the balance we were using . . .

The rarity of antimatter has presented a problem to physicists, who like everything to be symmetrical in the universe; there is no apparent reason why there should be more matter than antimatter in the universe and yet antimatter seems to be very rare. This has led some people to suggest that, in fact, there is just as much antimatter as matter, but not in this galaxy. Perhaps about half of all galaxies are made out of antimatter, and half of matter; so, there is just as much of each kind of matter and the universe is nicely symmetrical. If this is so, then it is possible that, sometimes, out in space, a large quantity of matter might meet a large quantity of antimatter and the whole lot would disappear, giving off vast quantities of energy in the form of radiation. If this happens, our astronomers might see this radiation, and deduce what was going on. . . It is a fascinating idea. And just think; if there are 'anti-galaxies', then maybe some of them carry life. Perhaps, somewhere, an 'anti-person' is reading a positronics magazine and wondering about the possibility of galaxies made of matter. . .

**OLIVETTI PRINTER & KEYBOARD type Te 300**  
with PUNCH & READER. Upper case ASCII with V24 Interface. 240 volt operation.  
**£125 each**

**INFRA RED IMAGE CONVERTER type 9606 (CV 144)**  
1 3/4" diameter. Requires single low current 3KV to 6KV supply. Individually boxed. With data  
**£12.50 each P&P 75p** Infra Red Lamps also advertised

**STEPPING MOTORS**  
200 steps — 20 oz./in. torque.  
12/24 volt input, 4 wire.  
**£12 each P&P £1.50**

**STEPPING MOTORS**  
200 steps. 20 oz./in. torque.  
120 volt operation, 3 wire.  
**£4 each P&P £1.50**

**709 DIL 14 PIN OPERATIONAL AMPLIFIERS**  
at **8p each**  
100 off 25% discount

**MINIATURE KEYBOARD**  
Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 ea.** P&P 65p

**BLUE THERMAL PAPER**  
430ft. roll, 8 1/2" wide  
**£2 per roll.** P&P £1.75

**CONVERT THIS UNIT TO A SUPER BATTERY CHARGER**  
Attractive green ministry quality case with removable top & bottom plates — heavy duty power switches — high powered resistors to control current — good quality centre mounted Amp Meter — strip of wing nut terminals on front panel which can be used for connecting leads.  
**ALL THIS FOR £3.50.** P&P £2  
**FOUR UNITS FOR £12.** Carriage £5.

**RXs** 770R used **£120**  
730/10 used **£85**  
Limited quantity only

BC172	5p	MC4001	15p	TIS92	10p	BC337	8p
BZ984V7	10p	MC4012	15p	TIS93	10p	BC327	8p
BZ9843V	10p	MC4020	75p	2N3704	8p	BC251	5p
2N3006	5p	74C20	25p	2N5447	5p	BC171A	5p
1N4305	5p	74C08	25p	2N5449	5p	BT60	5p
BZX79C12	10p	74C10	20p	2N3053	15p	4013	30p
BC2128	5p	MC4049	35p				
SN76550	5p						
IC 7451	10p						

**MUST CLEAR POLARAD SPECTRUM ANALYSER**  
5" Display. These are supplied with STU 2 plug-in. 1 to 45 GHZ.  
**£85 each**

**STEPPING MOTORS**  
6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts 12/24 recommended.  
**£1.50 each P&P 75p or 5 for £5 p&p £1.50.**

**LARGE QUANTITY OF PHOTOMULTIPLIERS**  
all with information. British approx. 2" window **£2 ea.** British approx. 5" window **£3.50 ea.** American approx. 2" window **£4 ea.** Special American version by RCA **£6 ea.**  
P&P all photomultipliers **£1.50 ea.**

**TRANSISTOR INVERTER**  
115V AC, 1.7Amp input. Switching is at 20KHZ. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuit supplied.  
**£1.25 each P&P £2**

**KEYBOARD PAD**  
Size 3 x 2 1/2 x 2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.  
**£4 each P&P £1**  
or **5 for £15 P&P £2**

REGULATORS — att at **45p each.** MC7805: 7812; 7815; 7912; 7915.  
MC1496L **70p**  
16 pin DIL Socket **10p.** 14 pin DIL Socket **8p**  
LED type TIL 209 Red with holder **10p each**  
SLOTTED OPTO SWITCH supplied with data — normally over **£2.** OUR PRICE **75p each.**  
ROCKER SWITCHES 2 pole c/o — **15p each**  
Spring Action TERMINALS — normally over **30p ea.** OUR PRICE **15p each**  
TOROIDAL TRANSFORMER 0-115V-230V Input 13.5V — 0 — 13.5V rated 8VA output **£1.70 each.** P&P 75p.  
Sub-min TRANSFORMER 0-120-240V Input: 12V-0-12V rated 4VA Output **75p each P&P 50p**  
**L.E.D.s**  
Standard White 12p; Standard Yellow 15p; Small White 8p.

**RXs** 770R Mk. II 940  
24V INVERTOR VERSION SPECIAL GOVT. QUALITY

**VERY FEW OF THESE PRICE ON APPLICATION**

We still have a large quantity of **TEST GEAR, OSCILLOSCOPES, SIGNAL GENERATORS ETC,** and they are priced to move.  
Callers welcome or write or Better Still PHONE for details

**MAGNETOS NEW BOXED**  
Originally for 14 cyl-gipsy  
Very adaptable  
**£4.75 each**

**TANTALUM BEAD CAPACITORS.** 4.7uf 25V 10 off **£1;** 100 off **£7.50.**  
TEXAS Low Profile 40 pin IC Sockets **45p each.**  
**SMALL TRANSFORMER.** 240V input. Output 2 windings 12V & 24V 1 amp. **£2 each.**

**SO SIMPLE — SO SAFE**  
Fit a push button CIRCUIT BREAKER. Small, compact: 3 ratings 0.8, 1.8 & 10AMP. State which one when ordering **75p each.**

**AMP METER 2 1/2" dia.**  
Scaled 0-60. Basic 75MV FSD. Complete with external 60Amp Shunt. **£2.50 each.** P&P **£1.50.**

**DIODES**  
All new full spec. devices. IN3063; BAX 13; IN4148; IS44. 100 off **£1.50** — 1,000 off **£10.**

Miniature **MOTORS** 12V with geared wheel (8 teeth 3/16" dia) Size 1 1/4 x 1/4" dia New **30p ea.**  
**MOTOR** 12V DC with pulley and integral semiconductor. Speed Control. New **£1 ea.**  
**LEDEX ROTARY SOLENOIDS.** 115V DC. No switch assembly. **15p ea.**  
**DIAMOND H CONTROLS ROTARY SWITCH.** Single pole 10-way Printed Circuit Mount. New **10p ea.**  
**DELAY LINE.** 50 nanosecs 3 connections, ground-in-out. Size 2 x 7.16 x 16" New **25p ea.**  
**PULSE TRANSFORMER.** Sub min. Size 1/2 x 5/16 x 1/4" Secondary centre tapped. New **20p ea.**  
**MOTOR** by Inland Motor Corp. DC High Torque. Reversible. Usable torque at 5V. Max voltage 24V **£2.50 ea.** P&P **£2.**  
**REMO TV TYPE MULTIPLIER.** Two high voltage outputs and focus **£1 each.**  
**DON'T TAKE CHANCES.** Use the proper EHT CABLE. **10p per metre** or **£7.50 per 100 metre/drum.** P&P **1/4**  
**MOTOR** by Eastern Air Devices Inc. 125V reversible with toothed shaft (10 teeth 1/4" dia). Size 2 1/4 x 2 1/4" dia **75p ea.** P&P **£1**  
**PHOTOGRAPHIC LAMPS.** Pearl 230V 500 watt. Screw cap **75p ea.** Box of 12 **£5.50.** P&P **£1.50**  
**MYSTERY IC PACK.** Some 40 pin — good mixture — all new devices. **25 ICs for £1.** P&P **50p.** You find out what they are and we will buy the information from you.  
**VACUUM PUMPS — TRAPS, ETC.** Send for list.  
**DECOUPLING CAPACITORS.** 0.05mfd 10V, 0.01mfd, 0.1mfd 50V, 0.047mfd 250V. All values 100 for **£1.**  
**E.H.T. CAPACITORS** 500pf 8KV **20p each.**  
**10-WAY MULTI COLOUR RIBBON CABLE.** New. **40p per metre.** **10 metres for £3.**  
**GE C UHF 4-button tuner** **£1.50 each.**  
**CENTAUR 115V FANS** 4 1/2" x 4" x 1 1/2" **£4.50 ea.**  
**EX-USED equipment tested.** **60p each.**  
**POTTER & BRUMFIELD TIMER RELAY.** 115V AC. Heavy duty. 7 pole c/s with 2 second delay. Charge R & C for different timing **50p each.**  
**SPEAKERS** 2 1/2" — 50 ohm 0.7W. New **40p each.**  
**RAPID DISCHARGE** capacitors 8mfd 4kV **£5 each.** P&P **£2.**  
**BIG INCH MOTOR.** 110V AC 3 rpm 50 cycle. Very small. **50p each.**  
**CONTACTORS.** Heavy Duty 24V DC 5 make **£1 each.**  
**GE C UHF VHF 6-button tuner** **£2 each.**  
**DIGITAL 24-HOUR CLOCK** with built-in alarm as used in Braun Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 6 1/2 x 2 1/4 x 2 1/4" **ONLY £3.75 each.**  
**931A PHOTO MULTIPLIER** in stainless steel container with window and built in resistor network. **£2 each.** P&P **£1**  
**SLIVER CONTROL 500W.** Log Single track. Complete with knob. Length 3 1/2" **25p each.**  
**RANCO 250V 18A THERMOSTATS** with Control knobs calibrated 50-200 degree C **£2.50 each.**  
**SOLID STATE UHF TUNERS.** **30c each.** P&P **£1**  
**BRAND REX** blue wire wraps. 30 metres for **£1.**  
**SIN SLOD RUBBER RINGS** (1" dia rubber). Keep the kids jor

dog) happy 4 for **£1.** P&P **£1.50**  
**TRANSFORMERS**  
**AUTO 240V input** 115V 1 Amp output **£1.25 each.** P&P **£1.25.**  
**240V input.** Soc. 6V. 1.86A Bkw. Size 2 1/2 x 2 x 2" Good quality **£1.50 ea.** P&P **£1**  
**240V input Soc.** 12V 0.92A. Size 2 1/2 x 2 x 2" Good quality. **£1.50 ea.** P&P **£1**  
**240V input 12V 100MA.** Size 60 x 40 x 42mm **50p each.**  
**240V input.** Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm **£1 ea.**  
**115V input.** Soc. 5V 250MA. Size 1 11/6 x 1.5 x 1 1/4" **2 for 50p.**

**VARIACS EX-Equipment** Good condition 8 Amps **£25 ea.**  
**20 AMPS** **£35 ea.**  
Some 3 phase available. Please enquire

**CRYSTALS**  
19.2KHZ FLAT METAL CASE — **50p each.**  
10 MHZ B7G **50p each.**

**LOUD HALLERS**  
Transistorised — hand-held — no leads — standard internal batteries supplied. Howl switch.  
**£20 each.** P&P **£2**

**TRANSFORMERS** — Standard Mains input  
Secondary outputs  
6KV 0.125A **£15 ea.**  
3440V 0.66A with matching 40H Choke **£30** the pair  
3KV 50MA **£8 ea.** 4 Volts 250 Amps **£10 ea.**  
18KV 30MA **£60.**  
22.5KV 110MA **£50 ea.** 5KV 300MA **£15.**  
60KV 0.0273 **£150.** 12KV 30MA **£20.**  
MULTI PURPOSE MAINS TRANSFORMER 4 windings each winding 0-10-110-125 at 48A **£15 ea.**  
425V 50HZ 2 Wire input. Output 8 5KV 2.55KVA. Could be run on 240V at 1/2 rating **£15 ea.**  
STEP DOWN ISOLATING TRANSFORMER Input 220. 250V 50HZ Output 115V 1.8KVA. BRAND NEW. These are very conservatively rated **£20 ea.**

**CAPACITORS**  
2mfd 5KV **£4 ea.** 0.5 mfd 10KV **£4 ea.**  
0.5 mfd 5KV **£4 ea.** 8 mfd 2.5KV **£4 ea.**  
CARRIAGE on these units will be charged at cost.

**INFRA RED QUARTZ LAMPS.** 230V 620 Watts. Size 1 3/2" x 1/2" dia **£1.50.**  
**BRIDGE RECTIFIER.** 2 Amp **50p ea.**  
**PHOTODIODE DETECTOR** 4" fly leads. **25p ea.**  
**AMPHENOL.** 17-way chassis mount edge connectors 0.1 spacing. **15p ea.**  
I.F.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) **60p ea.**  
**FANS.** 115V 13 Watts. Size 3 1/4 x 3 1/4 x 1 1/2" BRAND NEW. **£4.50 ea.** Secondhand **£2.50 ea.**

7453	5p	74H74	12p	75325	£1
7451	5p	74H51	7p	SN15862	4p
7402	12p	74538	10p	MC4028	69p
7476	20p	74502	12p	7417	14p
7495	35p	74154	70p	7441	40p
74122	12p	74C02	18p	74C86	50p
74C00	17p	74C04	18p	74C161	24p
		74C74	18p		

**SEMICONDUCTORS** 1N4005 — 5p; 1N4003 — 3p.  
At 5p each:  
3BC147; BC148B; BC157; BC158; BC237; BF197; OA90; OAB1; BA154; BA243  
At 25p each: TIP31; TIP41A; 2N5966; AF139; 2TX341; BY127 10p; BF181 20p; BD239 49p; BD241 40p; MA343AT 40p; BD228 50p; BD233 & BD234 Comp Pair 25W — 80p per pr. at 50p each.  
**REGULATOR** T8A625 8 to 20V in — 5V out 100MA T05 Con. 50p each BF256C 20p. TV AMPLIFIER T8A 120 20p each.  
**Integrated Circuits**

**MOTOROLA DUAL** in Line 6 pin Opto Coupler **30p each.** Gold plate tester version **50p each.**  
**EPROMS** 2708 **£5.50 each.**  
**TELEPHONES** 706 style black or grey **£5.50 each.** 746 style black or grey **£7.50 each.** Older style black **£2.50 each.** P&P **£1.50** per telephone.  
Honeywell humidity controllers **50p each.**  
**THYRISTOR TIMER.** Solid State. 15 secs adjustable (reset) in plastic r/c case. Standard 7-pin base. Series delay **50p each.**  
**MINIATURE PC MOUNT SLIDE SWITCH.** Single pole 3-way **10p each.**  
**VARIACS.** 2 amp Standard 240 Volts **£10 each.** P&P **£2**  
**ELECTROSTATIC VOLTMETERS.** 7.5KV **£8 each.** P&P **£2**  
Other ranges available. Please enquire.  
**TRIMMERS.** Sub min 0.25 to 1.25p to 4.5p 7 to 45p **All at 6p each.**  
**CROWN** replacement MOTOR for IBM GOLFEBALL TYPEWRITER 115volt 50HZ 1350 rpm **£4.50 ea.** P&P **£2**  
**SMITHS** encapsulated transistorised AUDIBLE WARNING DEVICES 4V-12V. Can be driven from TTL **65p each.**

MINIMUM ORDER **£3** VALUE OF GOODS. MINIMUM P&P **£1** — where P&P not stated please use own discretion — excess refunded. CARRIAGE ALL UNITS **£5.** P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS  
**CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.**  
**BARCLAYCARD (VISA) and ACCESS** taken. Official orders welcome.

**CHILTMHEAD LTD**  
NORWOOD ROAD, READING TELEPHONE NO. READING 669656  
(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")

## SPECIAL REPORT

### FREE

to all readers

# Don't buy a digital watch until you read this report

There are so many digital watches on the market, with varying functions, that the average person is bound to feel somewhat confused.

A new survey of the electronic watch industry has been produced to clarify this confusion and to give an unbiased and objective answer to the many questions that are constantly being raised.

- \* How accurate are electronic watches?
- \* Who makes Seiko's?
- \* What is the importance between brand names?
- \* Is solar power worth the extra money?
- \* What are the most important features in a watch?
- \* When will prices stop falling?

The survey answers all of these questions and tells you what to look for in a quartz watch; how they work; why the prices vary so much; what the future holds.

### FREE OFFER

Send today for this free technical report, plus news of a unique Metac offer to beat all special offers.

Complete the coupon below and send it FREEPOST (no stamp required) and we will post, **Same Day Despatch**, the technical report giving you all you need to know about electronic watches and details of our special offer.

by Trevor Raven.  
C.Eng. AMBIM, MIERE

## Which is the best watch?



These four watches are very different in price, durability and functions. How would you choose between them?

This unbiased and objective report helps you to make this decision and gives you a deeper insight into the rapidly changing and exciting world of the micro-chip.

For your free copy of the report, complete and return the coupon to: Metac Electronic & Time Centres, 24-hour Despatch Centre, FREEPOST, 47A High St., Daventry, Northants.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

ET17



**MECHANISM WITH ALARM**

£5.00



Assemble it in an evening!  
**MECHANISM & CASE**  
Inc. assembly instructions

£6.99

## DIGITAL 24 HOUR CLOCK

● SILENT RUNNING  
● LARGE ILLUMINATED NUMERALS

AS USED IN BRAUN DIGITAL CLOCKS

THREE FOR £13.50      MECHANISMS 10 FOR £39. 100 FOR £300

**HALF PRICE OFFER**

# Henry's Radio

EXPORT ENQUIRIES INVITED

**HENRY'S RADIO**  
404 EDGWARE ROAD,  
LONDON W2 1ED      01-723 1008

DELIVERY FROM STOCK



## MONOLITH

**QUALITY REEL TO REEL & CASSETTE TAPE HEADS**

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01 MONO PLAYBACK	£1.89	E12-09 MONO/STEREO ERASE	£1.85
B12-02 MONO RECORD/PLAYBACK	£4.02	B22-02 TWIN HALF TRACK RECORD/PLBK	£5.97
B24-01 STEREO PLAYBACK	£3.30	C44RPS02 QUAD QUARTER TRACK REC/PLBK	£9.37
B24-02 STEREO RECORD/PLAYBACK	£6.66	C22ES02 TWIN HALF TRACK ERASE	£4.72
B24-RP STERED GLASS FERRITE REC/PLBK	£11.60	MAGNETIC TAPE HEADS CATALOGUE 25 PENCE	

AUDIO AND HI-FI CATALOGUE 180 PAGE FULL COLOUR! 50 PENCE

## MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.  
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER  
ALL PRICES INCLUDE VAT

## TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units  
Multimeters - Semi Conductors - Timers - Safefloc

**Minimum & Sub Miniature**

Volts	Milli-amps	Ref. No.	Price £	P&P
3-0.3	200	238	2.55	65
0.6-0.6	1A 1A	212	2.95	70
9-0.9	100	13	2.25	65
0.9-0.9	330 330	235	2.10	65
0.8-9, 0.8-9	500 500	207	2.70	70
0.8-9, 0.8-9	1A 1A	208	3.80	70
0-15, 0-15	200 200	236	2.10	65
0-20, 0-20	300 300	214	2.70	85
20-12.0-12-20	700(DC)	221	3.45	85
0-15-20, 0-15-20	1A 1A	206	4.55	100
0-15-27, 0-15-27	500 500	203	4.00	85
0-15-27, 0-15-27	1A 1A	204	6.05	100

**12 AND/OR 24 VOLT**  
Pri: 220-240 Volts

Amps	24V	Ref. No.	Price £	P&P
0.5	0.25	111	2.25	70
1.0	0.5	213	2.70	85
2	1	71	3.20	85
4	2	18	4.00	85
6	3	70	5.55	90
8	4	108	7.40	1.15
10	5	72	8.20	1.15
12	6	116	8.80	1.15
16	8	17	10.80	1.25
20	10	115	13.80	1.45
30	15	187	16.80	1.45
60	30	226	33.30	1.75

**30 VOLT (Pri: 220-240V)**  
Sec: 0-12-15-20-24-30V

Amps	Ref. No.	Price £	P&P
0.5	112	2.80	85
1.0	79	3.55	85
2.0	3	5.55	1.00
3.0	20	6.25	1.15
4.0	21	6.55	1.15
5.0	51	9.55	1.15
6.0	117	11.05	1.15
8.0	88	14.30	1.45
10.0	89	16.55	1.45

**50 VOLT (Pri: 220-240V)**  
Sec: 0-19-25-33-40-50V

Amps	Ref. No.	Price £	P&P
0.5	102	3.55	.85
1.0	103	4.55	1.00
2.0	104	7.25	1.15
3.0	105	8.55	1.15
4.0	106	10.80	1.25
6.0	107	15.05	1.45
8.0	118	20.15	1.65
10.0	119	24.05	2.15

**60 VOLT (Pri: 220-240V)**  
Sec: 0-24-30-40-48-60

Amps	Ref. No.	Price £	P&P
0.5	124	3.80	.85
1.0	126	5.55	1.00
2.0	127	7.50	1.15
3.0	125	11.05	1.25
4.0	123	12.30	1.45
5.0	40	14.10	1.55
6.0	120	17.55	1.55

**AUTO TRANSFORMERS**  
Input/Output Tapped 0-115-210-240V

VA (Watts)	Ref. No.	Price £	P&P
20	113	2.60	.85
75	64	4.05	.85
150	4	5.55	1.00

**Input/Output Tapped**  
0-115-210-220-240V

Amps	Ref. No.	Price £	P&P
300	53	10.05	1.15
500	67	10.80	1.45
1000	84	18.55	1.55

Also 1500/2000/3000VA

**MAINS ISOLATING (Centre Tapped & Screened)**  
Pri: 120/240V      Sec: 120/240V

VA (Watts)	Ref. No.	Price £	P&P
60	149	6.55	1.00
100	150	7.55	1.25
200	151	11.05	1.25
250	152	13.25	1.45
350	153	16.25	1.55
1000	156	37.05	3.15

Please add VAT at 15%  
Barclaycard and Access facilities available  
Trade and Education Welcome

## BAYDIS

7a William Street  
Herne Bay, Kent  
Herne Bay GA586

# STEVENSON

## Electronic Components

**AT LAST! OUR NEW 1980/81 CATALOGUE IS NOW AVAILABLE.**

Our new catalogue is just packed with components. It contains 100 illustrated pages detailing over 3000 line items. These include:

Amplifier modules	Connectors	Meters
Books	Desoldering tools	Ni-cad cells
Breadboards	Drills	Op-amps
Cabinets	Etching equipment	Rams
Cables	Heatsinks	Resistors
Capacitors	IC sockets	Switches
CMOS	Knobs	Tools
Crossovers	Mains Transformers	Triacs

Included with our catalogue you will receive:

- a reply paid envelope for your first order.
- a mail order form to facilitate rapid despatch
- a 50p discount voucher to be used against mail order purchases over £10.00.

Available now by post from the address below at a cost of

Due to stock and administrative problems over the last few months, the quality of our service had suffered considerably. These problems have now been resolved and we are confident that we can now offer the quality of service we had been accustomed to. We wish to convey our apologies to any customers who have been inconvenienced.

### TRANSISTORS

AC127 25p	BC547 8p	TIP30C 70p
AC128 25p	BCY71 18p	TIP2955 65p
AD161 40p	BD131 35p	TIP3055 60p
AD162 40p	BD132 35p	ZTX107 12p
BC107 10p	BD139 35p	ZTX108 12p
BC108 10p	BD140 35p	ZTX109 12p
BC109 10p	BFX29 25p	ZTX300 14p
BC147 9p	BFX84 26p	ZTX500 15p
BC178 16p	BFY50 23p	2N3053 25p
BC182 10p	BFY51 23p	2N3055 55p
BC182L 10p	MJ2955 98p	2N3702 9p
BC184 10p	TIP29C 60p	2N3703 9p
BC184L 10p		2N3704 9p
BC212 10p		2N3819 22p
BC212L 10p		2N3905 10p
BC214 10p		2N5777 50p
BC214L 10p		


### CMOS

4001 25p	4025 25p	4072 25p
4002 25p	4026 150p	4081 30p
4006 95p	4027 50p	4082 30p
4007 25p	4028 90p	4085 85p
4011 30p	4029 110p	4093 80p
4013 45p	4040 110p	4095 110p
4015 85p	4042 85p	4510 90p
4016 48p	4046 110p	4511 100p
4017 80p	4048 60p	4518 90p
4018 90p	4049 50p	4520 110p
4020 110p	4050 50p	4527 165p
4022 100p	4052 80p	4528 100p
4023 25p	4060 120p	4532 125p
4024 60p	4066 63p	4543 170p
	4068 25p	4583 80p
	4069 25p	4585 115p
	4070 25p	
	4071 25p	

### SKTS

Low Profile Texas

8 pin	9p	22pin	20p
14pin	11p	24pin	22p
16pin	12p	28pin	26p
18pin	16p	40pin	38p
20pin	18p		

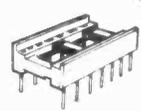

### SWITCHES

TOGGLE

Standard	SPST 40p	DPDT 55p
Miniature	SPDT 80p	DPDT 90p
Subminiature	SPST 65p	DPDT 85p

SLIDE Standard DPDT 17p. Miniature 16p each.  
PUSH Push to make 16p. Push to break 22p

### TTL

7400 15p	7447 65p	74123 50p
7401 15p	7448 65p	74125 60p
7402 15p	7472 35p	74126 60p
7404 16p	7473 38p	74132 70p
7406 38p	7474 36p	74141 95p
7408 22p	7475 40p	74145 90p
7410 18p	7476 40p	74150 120p
7413 35p	7483 80p	74154 110p
7414 56p	7485 80p	74157 80p
7420 16p	7486 35p	74164 120p
7427 30p	7488 35p	74165 120p
7430 30p	7490 45p	74174 100p
7432 35p	7492 55p	74175 95p
	7493 45p	74190 100p
	7494 70p	74191 100p
	7495 70p	74192 100p
	7496 70p	74192 100p
	7497 70p	74196 100p

### PACKS

Specially designed packs intended for development work at a considerable saving.

¼w resistors. 10 of each value 4.7ohm to 1Mohm. a total of 650 resistors. 530p each.

½w resistors. 10 of each value 4.7ohm to 1Mohm. a total of 650 resistors. 875p each.

Presets. Pack of 5 of each value from 100ohms to 1Megohm. a total of 65 presets. 390p each.

LED's. Pack containing 10 of each colour LED 0.2 size. Total of 30 Led's + clips. 450p each.

Zeners. Pack of 5 of each value from 2U7 to 33V. A total of 130 zeners. 880p each.

### OPTO

Red	0.125in.	0.2in.
Green	TIL209	TIL220 10p
Yellow	TIL211	TIL221 16p
Clips	TIL213	TIL223 16p
		3p

### DISPLAYS

DL704	0.3in	CC	130p
DL707	0.3in	CA	130p
FND500	0.5in	CA	100p

All prices include VAT. Please add 50p carriage on orders below £15. Contact our sales office with your requirements on 01-464 5770




# 76 College Road, Bromley, Kent BR1 1DE.

36

ETI JULY 1980

# DESIGNER'S NOTEBOOK

In this month's 'Notebook' Ray Marston looks at practical applications of a neat little eight pin National chip, the LM3909 LED flasher/oscillator

A common and seemingly trivial task often facing the design engineer is that of providing an illuminated (glowing or flashing) indication of the ON state of a piece of electronic equipment or the location of a passive device (fire extinguisher, emergency switch, etc) in a darkened room.

These tasks are obviously easily solved if mains power is readily available, but can present serious problems when battery powered equipment is concerned. LED indicators typically draw 12 mA or more when illuminated and can thus place a fairly heavy strain on small supply batteries. LEDs, in any case, drop two or more volts under the ON condition and can thus not readily be powered from battery voltages below 3V or so.

National Semiconductors provided an ingenious solution to this problem some years ago when they introduced the eight pin LM3909 LED flasher/oscillator chip. This device acts basically as a low duty cycle (brief ON period, long OFF period) oscillator that provides a voltage-doubled high-current pulse to an external LED. Because of the voltage-doubling facility, the IC can flash a LED even when powered from cell voltages down to 1V1. Because of the low duty cycle facility, the device can provide high pulse currents (up to 100 mA) while still drawing very low mean currents (typically 0.3 to 1.5 mA) and can thus provide months, or even years, of continuous operation from a single 1V5 cell.

CELL SIZE	ESTIMATED BATTERY LIFE UNDER CONTINUOUS OPERATION	
	STANDARD CELL	ALKALINE CELL
AA	3 MONTHS	6 MONTHS
C	7 MONTHS	15 MONTHS
D	1.3 YEARS	2.6 YEARS

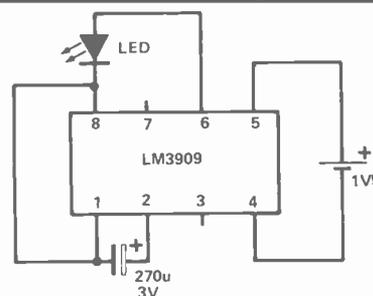


Fig.2. Practical 1V5 LED flasher with details of estimated battery life. Nominal flash rate is 1 Hz and typical average drain current is 0.63 mA.

## The LM3909

The internal circuit of the LM3909, together with typical external connections for 1V5 flasher operation, is shown in Fig.1. In this application, the LED receives current (via the 270 uF capacitor and the internal 12R resistor and Q3) for only about 1% of the time. For the remaining part of each operating cycle all transistors except Q4 are off. The 20k resistor from Q4's emitter to supply common draws only about 50 uA. The 270 uF capacitor is charged through the two 400R resistors connected to pin 5 and through the 3kΩ resistor connected to pin 4 of the circuit.

Transistors Q1-3 remain off until the 270 uF capacitor becomes charged to about 1 V. This voltage is determined by the junction drop of Q4, its base-emitter voltage divider and the junction drop of Q1. When the voltage at pin 1 becomes a volt more negative than that at pin 5 (the supply positive terminal) Q1 begins to conduct and then turns Q2 and Q3 on.

The LM3909 then supplies a pulse of high current to the LED. The current amplification of Q2 and Q3 is between 200 and 1000: Q3 can handle over 100 mA and rapidly pulls pin 2 close to supply common (pin 4). Since the 270 uF capacitor is charged at this time, its other ter-

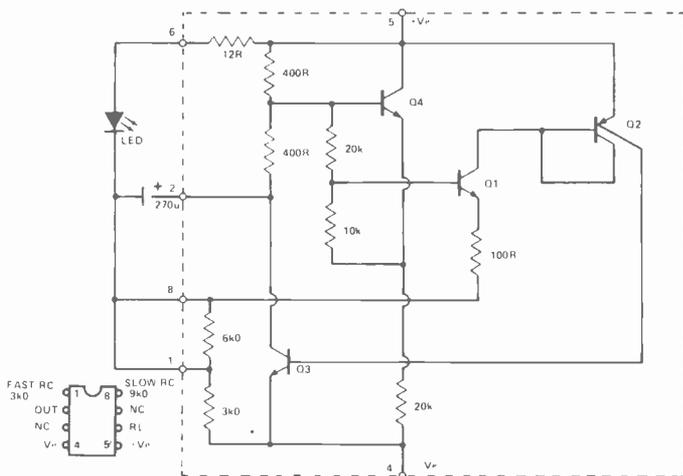


Fig.1. The internal circuit and practical connections of the LM3909 low voltage LED flasher/oscillator IC. The IC outline is also shown.

minal at pin 1 goes below the supply common; the voltage at the LED is then higher than the battery voltage; the internal 12R resistor (between pin 5 and 6) limits the LED current to a safe value.

Thus, the 270 uF capacitor alternately charges via the 3k0 timing resistor and discharges via the LED and 12R resistor. In some other applications, the short between pins 1 and 8 can be removed, enabling the capacitor to charge through a total of 9k0, with a consequent reduction in duty cycle and mean current consumption.

If voltage boosting is not needed (with or without current limit), loads can be hooked directly between pins 2 and 6 or pins 2 and 5 of the IC.

Let's look now at some practical applications.

## LED Flasher/Indicator Circuits

Figure 2 shows the Fig.1 1V5 flasher circuit redrawn in a practical configuration. The circuit gives a brief flash once every second or so and typically draws an average current of only 0.63 mA. As you can see from the table, this circuit will give from three months to 2.6 years of continuous operation from a battery, depending on the size and type of cell that is used.

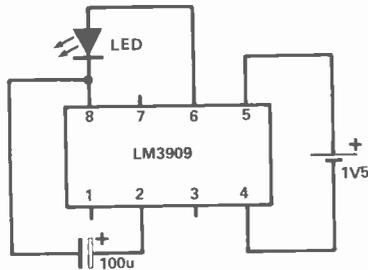


Fig.3. Minimum power 1V5 flasher. Nominal flash rate is 1.1 Hz and average drain current is 0.32 mA.

An even longer life can be obtained from the 'minimum power' flasher circuit of Fig.3. This is similar to the one described above, except that the short is removed from between pins 1 and 8, causing the capacitor to charge via 9k0 of internal IC resistance and so operate with a reduced duty cycle and reduced mean current consumption. The circuit has a typical current drain of 0.32 mA.

The Fig.2 and Fig.3 circuits are of particular value as 'indicator' or 'locator' beacons for use on fire extinguishers, emergency lanterns, torches, emergency switches, etc. The operating frequencies of these circuits are heavily dependent on supply voltage, as indicated in Fig.4. This circuit is similar to that of Fig.3, except that it is designed for 3 V operation, in which case the timing capacitor value has to be increased by a factor of 2.7 for approximately the same flash rate.

Figure 5 shows another variation of the 1V5 flasher circuit. In this case the internal timing resistors are

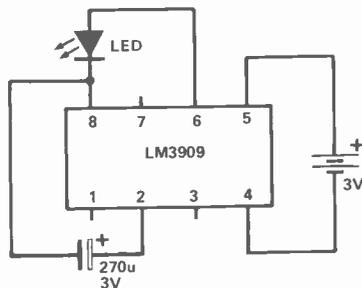


Fig.4. 3V 1 Hz flasher consumes an average current of 0.77 mA.

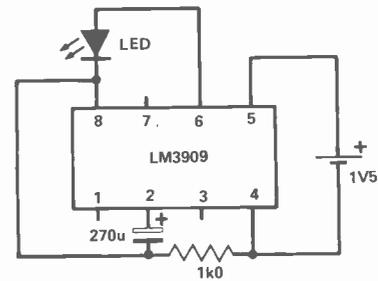


Fig.5. Fast 1V5 blinker. Flash rate is 2.6 Hz and drain current is 1.2 mA.

shunted by an external 1k0 resistor, thereby reducing the charge time constant of the circuit and causing the flash rate to increase (to 2.6 Hz) and the duty cycle and mean current consumption to rise. The circuit gives a more noticeable flasher indication than the three earlier circuits, but at the expense of 1.2 mA of mean current drain.

If you enjoy experimenting with circuits, you can build the variable rate flasher of Fig.6. The rate is variable from zero to 20 Hz via the 2k7 potentiometer. The two external 68R resistors are used to stabilise the duty cycle of the circuit and maintain a fairly steady apparent brilliance level in the LED as the rate is varied.

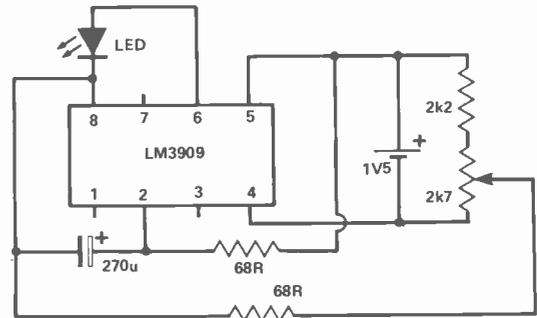


Fig.6. Variable rate flasher. The rate is variable from zero to 20 Hz.

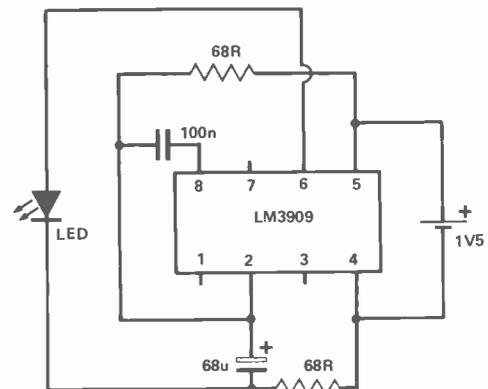


Fig.7. High efficiency 'continuous' 1V5 LED indicator. The circuit provides a steady but dim illumination by pulsing the LED at 2 kHz. Drain current is 4 mA.

The Fig.7 circuit is designed to give apparently continuous illumination of the LED when powered from a 1V5 cell. The circuit in fact acts as a 2 kHz square wave generator, the two external 68R resistors being used to approximately equalise the on and off times of the generator. The circuit gives a dim LED illumination and has a battery drain of about 4 mA. LED brilliance can be increased, if required by using the alternative connections of Fig.8, but at the expense of 12 mA of battery drain.

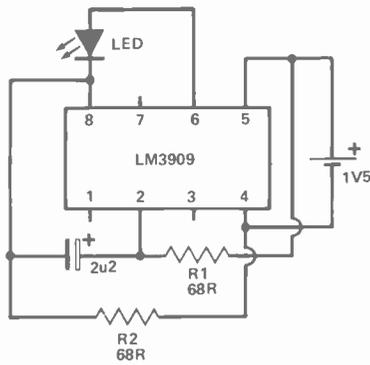


Fig.8. This 1V5 circuit gives an apparently steady and continuous LED indication. Battery drain is 12 mA.

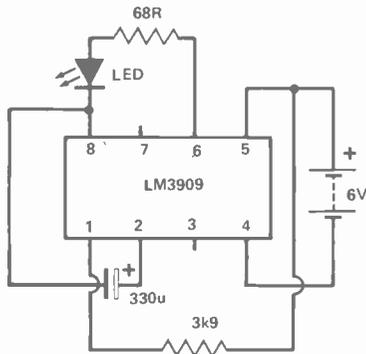


Fig.9. This 6 V flasher operates at about 1 Hz.

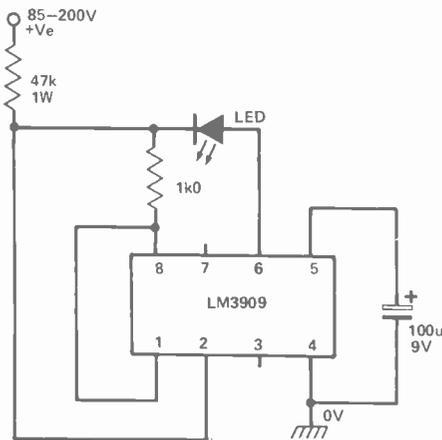


Fig.10. This LED flasher circuit can be operated from any supply in the 85-200 V range.

All of the LED flasher circuits that we've looked at so far are intended for operation from 1V5 or 3 V supplies. Most of these designs can in fact be used, in slightly modified form, at voltages up to 6 V, as shown by the circuit of Fig.9. Note in this case that a 68R resistor is wired in series with the LED, to limit its drive currents.

The LM3909 IC has a 6V5 zener built in between pins 2 and 4 (not shown in Fig.1). This fact is put to practical use in the flasher circuit of Fig.10, which can be powered from any DC supply in the 85-200 V range. The 100 uF timing capacitor is connected between pins 4 and 5 in this application.

ETI

# CALCULATORS.

## SCIENTIFIC

**\*SPECIAL OFFER**  
TEXAS T159 together with PC100C  
(Complete as manufacturer's specifications)  
**£285.00**

TEXAS/HP Accessories available	
*TEXAS T159 (Card prog 960 prog steps of 100 mem)	<b>£156.50</b>
*TEXAS T158 (Key prog 480 steps of 60 mem)	<b>£60.00</b>
*TEXAS PC100C (Printing Unit for T158/159)	<b>£140.00</b>
*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes/50 Prog Steps)	<b>£25.00</b>

For your Texas T158/59 Calculator  
**ELECTRICAL ENG. MODULE**  
**LEISURE (GAMES) MODULE**  
**STRUCTURAL ENG. MODULE**  
**NOW AVAILABLE**

*TEXAS TI PROGRAMMER (Hexadecimal Oct)	<b>£46.50</b>
*TEXAS T151 /iii (10 mem 32 Prog Steps Stat/Sci)	<b>£26.30</b>
TEXAS T150 LCD (Sci/Stat. 2 Con Mem)	<b>£23.00</b>
TEXAS T125 LCD (Sci/Stats)	<b>£17.00</b>
TEXAS T53 (Sci. 32 Prog Steps-Coa Mem + 80 Prog List Applications book)	<b>£25.00</b>

Make more of your  
Texas T158/59 Calculator  
**MATH/UTILITIES MODULE**

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

Module includes:

**Prompter. Alpha Messages. Printer Formatting. Superplotter. Sorting. Data Arrays. Data Packing. Prime Factors. Hyperbolic Functions. Gamma/ Factorial. Random Numbers. Normal Distribution. Interpolation. Roots of a Function. Minimax. Romberg Integration. Differential Equations. Discrete Fourier Series. Calculator Status. Variable Arithmetic. Module Check.**

*TEXAS T158 with Maths/Utilities	<b>£90.00</b>
*TEXAS T159 with Maths/Utilities	<b>£186.50</b>
*TEXAS T158 with Applied Statistics	<b>£80.00</b>
*TEXAS T159 with PC100C & Applied Statistics	<b>£305.00</b>

### SUMMER SALE

\*TEXAS T159 Calculator (complete as manufacturer's spec. master module, charger, etc.) PLUS statistics module and extra set of 40 Blank Prog. Cards with wallet. etc.  
**ONLY £180**

### NEW TEXAS T158C\*

*Continuous program facility on all 480 Program steps/60 mem even when calculator switched off	<b>£79.50</b>
*TEXAS T158C (complete plus Applied Stats. Module)	<b>£99.00</b>
*TEXAS T158C + PC100C	<b>£208.00</b>

*HP33E (8 mem. Pro Sci/Sta)	<b>£50.75</b>
*HP32E (Advanced Sci with Statistics)	<b>£40.50</b>
*HP67A (K Prog 224 Steps 26 Mem)	<b>£188.70</b>
*HP97A (Fully prog with Printer)	<b>£384.35</b>
HP41C (the newest calculator from HP)	<b>£173.48</b>
HP41C Card Reader/Printer etc. Now in stock	<b>£242.00</b>
CASIO FX8000 (10 dig Sci/Sta. Stop Watch/Alarm)	<b>£27.73</b>
CASIO FX501P (Sci. LCD Prog. 128 Steps 11 Mem)	<b>£47.50</b>
CASIO FX502P (Sci. LCD Prog 256 Steps 22 Mem)	<b>£65.00</b>
CASIO Prog Adaptor — permits Progs to be recorded on to standard cassette recorders for replay on Casio FX501P/FX502P at later stage	<b>POA</b>

### LEXICON LANGUAGE TRANSLATOR

(With 6 Lang. Module — French / Italian / German / Spanish etc)  
**£128.70**

### NOW IT'S YOU AGAINST 'COMPUTERS'

<b>CHESS CHALLENGER "7"</b> (7 Levels of game)	<b>£76.50</b>
<b>CHESS CHALLENGER "VOICE"</b> (10 Levels — beginner to Master Plus) The strongest Prog yet in this series — twice as fast as the other challengers. A microprocessor with 128,000 to 160,000 bits of read only Mem. Over 8000 bits of Random Access Mem. Teaches opening & end game solutions. Plays against itself. Solves book problems etc. — and in addition IT SPEAKS. Complete with Deluxe playboard, hand carved men with magnetised base plus Deluxe carry case	<b>£170.00</b>
<b>SARGON.</b> The most advanced chess game yet with ad on module availability for other games POA (Our price inc. FREE rechargeable battery pack)	

\*FREE — mains/Charger included\*

### LEARNING AIDS

TEXAS DATAMAN (Number Games-Table learning etc. 5/10 yrs)	<b>£18.00</b>
TEXAS SPELLING B (Spelling Games ideal 5/10 years)	<b>£22.50</b>
TEXAS SPEAK AND SPELL (for older children 8/13 years)	<b>£39.95</b>

### IDEAL FOR STUDENTS

ALL WITH LCD DISPLAY	
TEXAS T120 (Jun Sci + Con Mem)	<b>£13.00</b>
TEXAS T135 (Sci/Stat C Mem)	<b>£17.00</b>
TEXAS T138 (Sci/Con Mem-Pola Rec Cony Dec Deg conv/ Deg Min Sec)	<b>£19.95</b>

GOODS FULLY GUARANTEED PRICES EXCLUDE VAT (ADD 15%)

Company/ Hospital and Government orders accepted by phone

Barclaycard/ Visa/ Access accepted by phone

**TEL. 01-455 9823**

EXPORT ORDERS WELCOMED

Air Freight/ Air Post Delivery  
Quotations on request

# MOUNTAINDENE

22 Cowper St., London, EC2

TTL  
CMOS  
74LS  
LEDS

# LB ELECTRONICS

LINEAR  
RAMS  
EPROMS  
SURPLUS

TELEPHONE:  
UXBRIDGE 55399

**PCB OFFERS**  
(1A) 100 bit shift register PCB, 115mmx94mm containing 9x7491, 6x7496 and 1x7441. Terrific bargain 85p, p&p 30p.  
(1B) Audio amp PCB (LM380) 9-18v d.c. output 2 1/2 watts into 8 ohm with heatsink. 1.25 watt 40hm without heatsink. £1.50 p&p 25p.  
(1C) PCB 215mm x 290mm 12xTMS 3122J (or sim.) Hex 32-bit Shift Reg. + 39 ICs. £2. + 50p p&p (limited stocks)

**MPU CORNER**  
2112 (200ns). £3. 2714 (450ns) £4.50.  
1702 £2.50. £3. 2708 (400ns) £6.25.  
2716 (Single Rail) £19.00.  
74125 4 for £1 + p&p 25p.  
MK 1002P (Dual 128 bit Shift Reg) 35p.  
LM711CH (Voltage Comparator) 30p.  
MMS240 Character Generator + Data 2560 Bit (64 x 8 x 5) £3.50, p&p 25p.  
(All Full Spec)

2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 25p.

**D TYPE CONNECTORS**  
15 Way: wirewrap plugs only 75p.  
25 Way: ribbon plugs £1.20.  
25 Way: plug (solder) £1.00.  
25 Way: sockets (solder) £1.00.  
37 Way: plug £1.40.  
50 Way: skt (wirewrap) £1.65.  
50 Way: skt £1.45, p&p 15p.

**COVERS**  
37 Way: 80p. (plastic) p/p 25p.  
25 Way: 65p. (plastic) p/p 25p.

**DISPLAYS**  
MAN 72 7 seg CC £1.25 p&p 25p.  
Burroughs Planplex 9 Dig. + skt and bezel £1.00, p&p 25p.  
LED 3 Digit DIL 55p, p&p 25p.  
Bommar 9 digit 1in LED with red bezel. (As used in calculators). £1.00 + 25p p&p.

**SUPERSAVER**  
Ribbon Cable Headers 16 DIL Jermyn, gold plated, with cover 45p, p&p 25p.

**SUPERSAVER 2**  
Tantalum Capacitors 25 volt 4.7 uF. 14 for £1.00, p&p 25p.

**SUPERSAVER 3**  
Stepping motors, 40mm dia. 70mm long 5mm shaft (approx), 12-24V torque 340 GMC. Brand new, give away price £2.50, p&p 40p.

**SUPERSAVER 4**  
HYBRID SYSTEMS DAC 371-8 8 Bit. DIL packaged, ideal MPU users with data. £2.95, p&p 25p.

**SUPERSAVER 5**  
LM 323K Voltage Regulator. 5 volt 3A. £4.50, p&p 25p.

**SUPERSAVER 6**  
RS 338-383 Miniature Decade Thumbwheel Switch. £1.65, p&p 25p.

**SUPERSAVER 7**  
SN 74116 Dual 4 Bit latch 75p, p&p 25p.  
SN 7418 Arithmetic Logic Unit, 80p, p&p 25p.  
SN 74194 4 Bit Register, 50p p&p 25p.

**SUPERSAVER 8**  
SN 74198 8 Bit Shift Register, 75p p&p 25p.

**SUPERSAVER 9**  
BC 108b 8p each or 100 for £7. P&P 25p.

**SUPERSAVER 10**  
4 Digit 7 segment LED Bubble Display. NSA 1540A Ex equipment. 5 for £1, p&p 25p.

**SUPERSAVER 11**  
STAR OFFER. Dynamic hand microphone 200 ohm with lead and 5 pin plug. £1.25 (unrepeatable) p&p 30p.

**SUPERSAVER 12**  
TMS 3128NC Static shift register, £1.50, p&p 25p.

**SUPERSAVER 13**  
PL259 (UHF) Elbow Connectors, 50p each, p&p 25p.

**SUPERSAVER 14**  
1S423 Stud mounting rectifiers, 440v, 10A, giveaway price, 10 for £2, p&p 25p.

**SUPERSAVER 15**  
20K Painton multiturn trim pots, PCB mounting, per box of 14 £2.50, p&p 25p.

**SUPERSAVER 16**  
Astec UM1163E 36 modulator plus PAL colour PCB (faulty). Few only £2.25, p&p 30p.

**LEDs (Full spec).**  
TIL209, red 10p. 0.2in, red 12p. 0.2in, green 28p. 0.2in, yellow 28p.  
RL54 red Axial lead. 15p.  
P&p on all above 25p.

**VERNITRON** Ceramic filters type FM4 10 7MHz 45p, p&p 25p.

**TRANSISTORS**, 8D236 40p, BC183L 10p, BF195 10p, SGS 2N3055 30p, p&p on all 25p.

TBA 810S, with data. 85p, 4-way DIL switches, 75p. MC1303 Dual Stereo preamp with data, £1.25.

7in. Nylon cable ties 100 for £1.50. All p&p 25p.

**NEW SN76477** (Yes, back in stock). Sound Generator IC (Train, plane, explosion, laser gun etc.). with data £3.25, p&p 25p.

**PCB KEYBOARD**, 65mm x 82mm. 18 key Clickers less Key tops, ideal Hexadecimal use 35p, p&p 25p.

**CAPACITOR SCOOP**, 1.600uF at 10v, 1600uF at 25v. Axial lead. 2 dozen for £1 + 25p p&p.

**PAPST** min-fans 80mm x 80mm (approx) 220V 50Hz Brand new £8, p&p £1 (limited stocks).

Pewec Boxer. As above but 115v at £4.50 + £1 p&p.

IEC mains chassis plug with filter 250V 6 amps. Ideal for MPU users. Equivalent to RS238-429 £2.50, each p&p 30p. (Limited stocks.)  
Suitable cable socket 65p each, p&p 25p.

**GIVEAWAY**  
22 pin low profile DIL socket, gold plated  
20p EACH  
p&p 25p

**WE STOCK PETS**  
8K version £599. SAE for the PET SORCERER software lists at discount prices.

We can also offer a 48-hour repair service for out of warranty PETS. Telephone for details. PET edge connector 40x04 £1.40 each p&p 25p.

**IC HOLDERS (Low-profile)**  
8 DIL 12p 14 DIL 15p  
16 DIL 17p 18 DIL 20p  
22 DIL 28p 24 DIL 35p  
28 DIL 45p All p&p 35p

**WE STOCK** a vast range of TTL, CMOS some 74LS. MINIATURE TOGGLES, etc.  
**PSUs**. We have a large stock of power supplies at very realistic prices (callers).

**RELAYS**  
ITT 700 ohm Single pole changeover. 45p. BANOR resettable double pole changeover 12V £1. Both p&p 25p.

**CIRCUIT BREAKERS**  
4450v AC 65v DC 0.5A 50p; ditto 7A 80p, p&p 25p.

**ALLEN KEYS**, 7/16in 5p; 12 for 50p; p&p 25p.

**ASR33** (with tape punch reader), generally overhauled, £225 inc. VAT.

**CALCOMP MODEL 140** 8in Disc Drive fully tested, £195 inc VAT, carriage & cost.

**MEMOREX 651** dual disc drives complete with power supplies and format electronics (sorry, no data as yet). £350 each inc. VAT. Recordaid telephone answering machines (GPO line matching transformer removed) sold as is from £2 to £10 depending on condition. Fitted with very nice standard cassette deck. With circuit diagrams. SORRY BUT FOR CALLERS ONLY.

Terms cash with order (official orders welcomed from colleges, etc.) All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

**FOR THE PROFESSIONAL USER**. CP Clare Keyboard switches with buttons (blank) 65p each p&p 25p.  
Gould PMA 47/10 0.15V 3A Brand new £45 p&p £3.50. Many more in stock but in small numbers. Please phone for requirements.

**PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING**

Surplus stocks purchased for cash

**LB ELECTRONICS**  
11 HERCIES ROAD  
HILLINGDON, MIDDLESEX  
UB10 9LS, ENGLAND

All enquiries s.a.e. please  
New retail premises, now open Mon, Thurs Fri, and Sat, 9.30-6.00. Lunch 1.2-1.15 weekdays. Closed all day Wednesday. We are situated just off the A40 Opposite Master Brewer.



**UXBRIDGE 55399**

All components full spec.

## KRAMER & CO PRESENT THE LATEST IN CONSUMER ELECTRONICS

**BARGON 2.5 MODULAR CHESS SYSTEM.** Contact us for price. Unparalleled strength through entire game. Opening Book Library. Mate-in-two problems solved in two minutes. Seven computer strength levels. Instructional mode features. Plays by USCF & BCF Rules. Audio Alert System. Exclusive rank display and position verification. Position programming. Backspace control. Tournament timer. Move monitor. Battery extra. Position storage memory. Halt/hint control. Changing sides. Alphabetic display.

As recommended by ETI


Rechargeable batteries available at special price, S.A.E.



**'7 LEVEL' Chess Computer** at a realistic price. Plays black, white or itself. Seven levels of play from beginner to expert. Does not permit illegal moves. Castles, Kingside, Queenside, En Passant. Plays opening defences such as Sicilian, French, Ruy Lopez, Queens Gambit declined. Analyses as many as 3,024,000 board positions. Establish your own position and watch the computer react. Pawn promotion sides changeable in Mid-Game. Size 12 1/2 x 8 x 1 inch. Mains powered. **VOICE CHESS CHALLENGER** available. P.D.A.



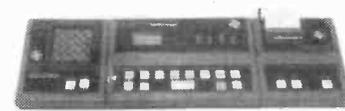**SUPER SYSTEM III** LCD display of International symbols for all moves. Plays black/white or itself. Timed playing strength 0 secs to 100 hours. All International Chess Rules inc. Draw by 3 & 50 move rule. Move Counter. Set up your own position. Position verification. Illegal moves rejected. Automatic Casting & En-Passant. Computer does much more. £154.95. This is the start of a system. To fit your needs optional extras include: Rechargeable Power Pack. LCD Chess Board £106.95. Memory Unit to store games for up to 1 year. Plus the world's first Electronic Printer to record moves. SAE for details and prices of accessories. **AS RECOMMENDED BY ETI.**



**SPACE INVADERS Game Program**  
The ultimate Game Programme with 112 game variations including Moving Shields, Zig-zagging Laser Bombs, Fast Laser Bombs, Invisible Invaders and 1 & 2 Player Games! This superb cartridge uses the joystick controllers and costs only £27.50 incl VAT plus 50p Post and Packing. Order Now!  
Atari with space invaders. £148



**SENSORY CHESS CHALLENGER 8**

**Major Features**

- 1) No keys to press.
- 2) New sensory playing surface automatically tells the computer your every move.
- 3) The playing squares light up to graphically show you the computer's next move.
- 4) Eight levels of play.
- 5) Dry cell battery operated, or through the mains using the adaptor supplied.
- 6) Quick, easy, position verification feature.
- 7) Analyses as many as 3,024,000 board positions.

£129

**ATARI BASIC PROGRAMMING**



Orders being booked for July delivery. £34.50.

**ADVENTURE** — Adventure plays like the addictive Dungeons and Dragons fantasy role playing board game and includes the added dimension of video. A wicked magician has stolen an Enchanted Goblet and hidden it somewhere in the Kingdom. The object of the game is to rescue the Goblet and replace it inside the Golden Castle where it belongs — no easy task. Three deadly dragons and a black bat hinder your quest, but scattered throughout the Kingdom are objects to help you slay the dragons and outwit the evil magician. £22.50 plus 50p P&P.



**ELMAC 4810 CRT 5MHz scope** £120 + VAT. As recommended by ETI. The best selling 5MHz 4" CRT scope in the UK. Time-base include sweep range — 100 msec/div to 1µ sec/div in 5 steps. 3" also available. £66 + VAT.



Free 10:1 Probe  
**Elax 5810 5" CRT (12.5MHz)** £181.71 + VAT. Vertical axis. 1 deflection sensitivity 10mV/div. Bandwidth — DC DC 12.5MHz (between 3dB points). AC 2Hz 12.5MHz (between 3dB points). Rise time 20n sec. Input Attenuator — 12 step — 10mV/div to 50V/div in 1-2.5 sequence calibrated. Time Base — Sweep range 0.5µ sec/div to 0.1 sec/div in 12 steps, calibrated with <5 expansion. Fine control. Variable between steps includes TB calibration position.



**SINCLAIR SC110 (mini scope)** £146.20.  
PEM 200 £58.20. DM 450 £102.46.  
DM 350 £76.99. PDM 35 £34.50.  
DM 235 £55.80.

We will match any lower price if competitor has stock. SAE for comprehensive chess reports on all the above.

**Kramer & Co., Dept. ETI 9, October Place, London NW4. Tel: 01-203 2473. Telex 888941. Attn: K7.**  
Visa, Access, Barclaycard & Company orders accepted. Orders by telephone/telex. Open Mon-Fri (Sunday by appointment only).

# DOUBLE SEIKO OFFER



**FIRST  
TIME  
UNDER  
£50**



**£39.95  
ALL INC**

Two Super Seikos – offered for the first time in living memory for under £50. How do we do it? You can say that again. How do we do it?

**£49.95  
ALL INC**

Let's look at the simple Seiko first – a dependable chronograph with no nonsense operation. At the touch of a button you can select either the things that normal watches do i.e. telling the time or a stopwatch display with the usual split/lap time facility.

The next Seiko is a bit clever. It's an alarm chronograph with a locking facility. What does that mean, I hear you say. Buttons are prone to being pushed, especially buttons that reset the watch time. However, with this remarkable wrist piece you can just press the LOCK button and pushing all the other controls suddenly has no effect. Full chronograph and alarm facilities we also featured.

## SEIKO DOUBLE WATCH OFFER

Name .....

Address .....

.....

.....

Please send me ..... Seiko Chronograph(s) at £39.95 each.

..... Seiko Alarm Chronograph(s) at £49.95 each

I enclose a cheque/PO made payable to Modmags Ltd for £ .....

Modmags Ltd.,  
Sales Office (Ref. Seiko Offer),  
145, Charing Cross Road,  
London WC2H 0EE.

# MORE BIG VALUE FROM YOUR TANDY STORE

## 1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current: 0-150 mA. Resistance: 0-100,000 ohms. Accuracy:  $\pm 3\%$  full scale on DC ranges,  $\pm 4\%$  on AC ranges. Complete battery. 22-027. REG. PRICE

**£6.95**



## 6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then  $\pm 30$  Mhz on 10 MHz! Overload-protected 1 meg input. Sensitivity, 30 mV up to 30 MHz. Req. 9V battery. 22-351. REG. PRICE

**£79.95**



## MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts: 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-30 1C-1 megaohm. 0-100-1k-10 1C-100K-3 megaohms. Req. 9V battery. 22-209.


REG. PRICE **£29.95**



## TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE **£9.95**

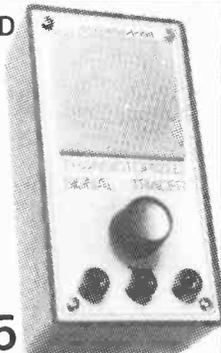

## DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.


REG. PRICE **£19.95**



## SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**

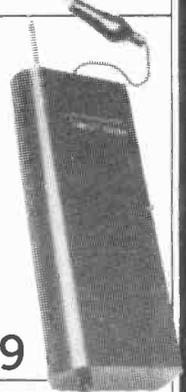

## AC/DC CIRCUIT TESTER


Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

## REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSb and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.


REG. PRICE **£229.95**

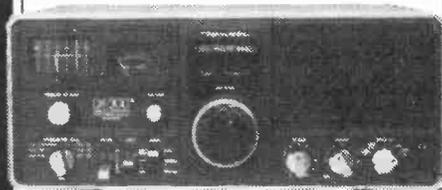

## DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.

REG. PRICE **£9.95**

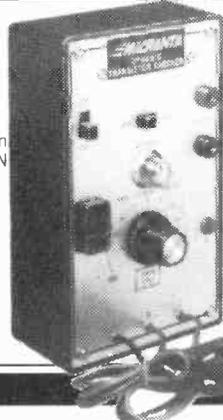

## VARIABLE POWER SUPPLY

Power project boards, IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**




You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRASH

# TANDY

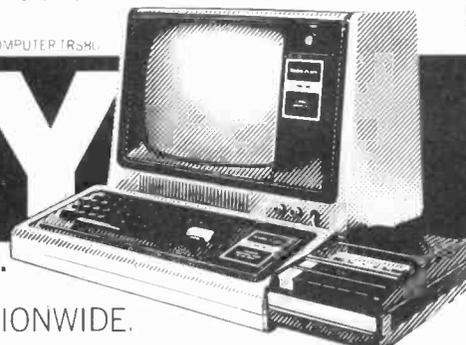

## TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access: Barclaycard and Trustcard welcome. Prices may vary at individual stores.

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.

# AUDIOPHILE

**A small step for an electron, a quantum jump for amplifiers? Being unable to resist the obvious puns, Ron Harris takes a searching look at one of Britain's newest amplifier stars.**

**S**how-time again this month. Spent an editorial hour or eight wandering around the hallowed halls of the Cunard Hotel. My annual pilgrimage to the Far East (or London) this — all face the Mecca Bingo Hall and pay homage to the gods of high technology.

Frankly, though, I thought this year's offering a little below the standard that this event has set itself in the past. Somehow there did not seem to be that charisma, that indefinable something, that electric charge to propel the visitor from room to room, eyes goggling at the plethora of mind mangling miracles wrought since last he trod these boards. . . . .

Or to put it another way a lot of it was boring. Naturally there were exceptions, but somehow the best demos were given by companies showing established products. One which particularly caught my ear was the minute A4-14 active loudspeakers, from Audio Pro. These have a sub-woofer built in to the enclosures and are capable of bone bleaching sound levels with a bass that sounds a lot larger than its 20' x 12 x 10 inches. The sound is simply stunning and would appeal to a very large number of people, I think.

Also making an impressive debut was the new JBE loudspeaker, with its unusual 'four-box' approach. The bass drivers are separately housed and would win no prizes for appearance despite the well finished enclosures. Still, the sound was very nice indeed, being well balanced and possessing excellent transient ability. Nice legs, shame about the facia?

B & W's new offspring is also worth a listen if you get a chance.

Aside from that people like Trio, Shure, Goldring, STD, Quad and Crimson made the most pleasing noises to be detected, others being either too full of people or too empty of ideas to attract the attention. KEF 105s appeared to have been breeding quietly between the staircases — there were hundreds of them everywhere.

The prize for making WORST use of your equipment (if you'll pardon the expression) goes to Audiostatic of Holland. They were showing off a quite incredible electrostatic 'panel' speaker with built-in valve amplifier — and making a right mess of it when we went in. I only

hope things improved later on. The sounds I heard have done much to persuade the average audio man that perhaps his idols have clay feet after all.

One little twenty second burst of a very well recorded opera is the only reason I bother to mention them at all. Inspid musical wallpaper and delicate solo flute is no way demonstrate such a systems capability in a crowded, noisy environment.

If you've got it — flaunt it, don't flute it.


## Quantum Amplification

Having started somewhat slowly, Quantum Electronics are well on the way to becoming one of Britain's most successful amplifier manufacturers. At that miserable Hi-fi 80 exhibition their room was one of the few that was continually carpeted with wall to wall people, which did detract considerably from the demonstration, admittedly. This sort of thing need not concern the Audiophile reader, however, as I'd already arranged for a review model.

Listening is infinitely more pleasant sat sitting at home, in front of the speakers you know and love, than packed into a tiny hotel room like a demented sonic sardine trying to pick up some of the sound waves being absorbed by the solid wall of bodies around you.

The particular combination from Quantum under scrutiny here is the 102 pre-amp and 204 power amp. It is available in many many forms, from ready built and tested, down to modules and hardware. In former form it will cost you £80.41 (102) and £153.42 (204). Modules (minus metalwork) cost £51.75 and £109.42 (204 kit).

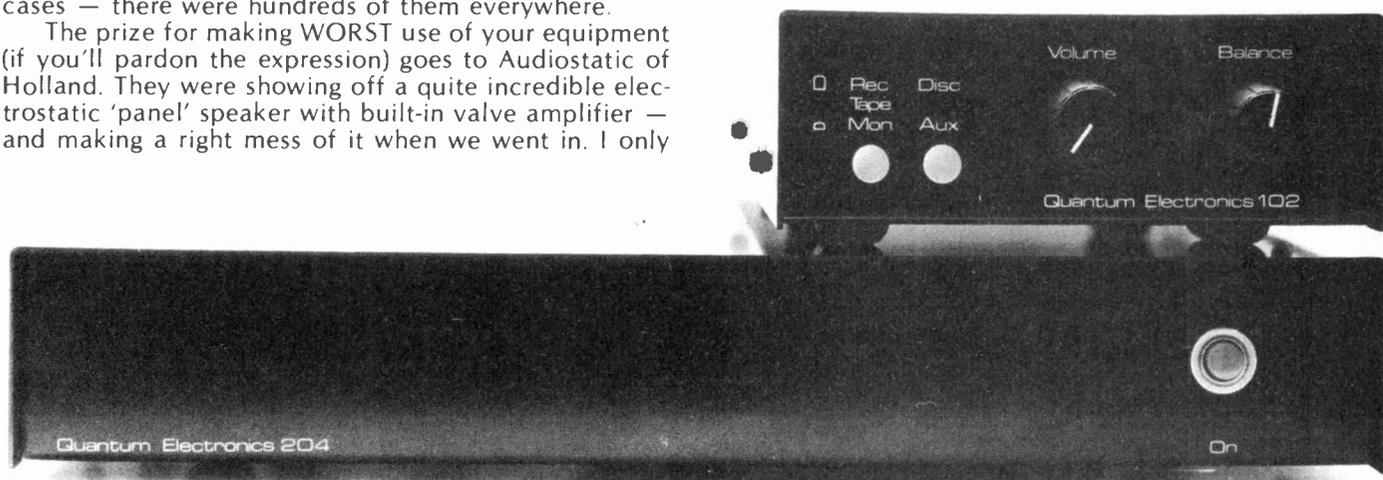It is worth a few words to point out that Quantum are in no way, shape, size or form connected with, or any



part of; Crimson Elektrik, the company that is now their biggest rival. Tim Nind, Quantum's designer and brain trust, left Crimson to form Quantum and is rightly giggled by being repeatedly referred to as part of the company he is now in battle against. The products are both black(!) and that is as far as any similarity goes.


## One Oh Two Preamp

The 102 replaces Quantum's earlier 'dual-version' machine, employing instead a very well thought out 'matching card' system to cater for all sorts of pickup cartridge from moving coil on down through any sort of magnetic variation.



Above: the 102 Quantum pre-amp full frontal. It is black, of course.

A small edge connecting PCB is plugged into the main PCB and carries the input matching components. Thus by changing card any pickup loading can be optimised. Handy for people upgrading, the pre-amp never dates. Even handier for deranged souls like me who are always swopping cartridges around. A link has to be made/removed on the board for MC/MM, however, and I fail to see why this could not have gone on the matching card, too.

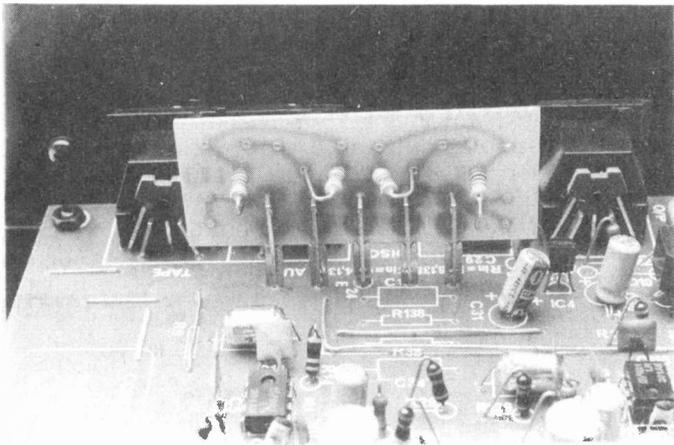

Above: the matching board for the pickup input in close-up. Note the nicely worked up edge connections. This particular board is for a Shure V15 IV pickup, I think. Trouble was I tried so many it is now impossible to remember which one was in when the camera went off!

Inputs and outputs are via DIN, with phono for disc. As I cannot abide DIN plugs of any sort, this drove me around the nearest loop, but no criticism intended, of the Quantum. As you can see from the photographs, controls have been "minimised" to a volume and balance with input selector arrangement. Adequate in most situations, but Baxandall help you if you live in an

awkward room as there is no tonal correction facility at all. Still, if you need it build an equaliser as treble and bass probably won't help anyway.

Tape sensitivity is variable by on-board switching and as all hardware is of board mounting variety there is little chance for noise/hum et al to creep in past the shielded cables that festoon most other equipment.

Table One displays the numbers, both claimed and measured, to which I'll return some paragraphs further on.

## Two Oh Four Power?

Long black boxes would appear to be the only way British companies can produce amplifiers. Where has all the chromium gone? I think the correct word to describe this shade of approach is functional.



Above: the 204 power amplifier. Finished in an unusual black (!?)

The 204 unit consists of two 110W audio modules, PSU with toroidal transformer (which buzzes audibly!) and separate supply for the pre-amp ( $\pm 15V$ ) One DIN (yeuk!) carries out the pre-amp volts and carries in the signal for amplification. Neat. Speaker output is via 4mm plugs. Thank God *this* isn't DIN.

The hardware package is more or less standard across the range, so that you can house any power you like, up to around 200W, in the same box.


Table One

PARAMETER	SPECIFIED	MEASURED
THD	< 0.15% to clipping Moving Coil < 0.1% to clipping	below noise floor unmeasurable
Input Sensitivity & Overload	Disc 3.5mV or 100uV standard Variable Tape 150mV Disc 34dB Tape infinite	Disc overload 35dB at 3.5mV and 100uV
Signal to Noise	Disc 70dB ref 3.5mV or 52dB ref 100uV Tape 96dB	65dB/50dB 85dB
Frequency Response	Disc $\pm 1dB$ RIAA 50Hz-20kHz Tape —	agreed $\pm 1dB$ , 20Hz-20kHz
Separation	46dB at 1kHz, 36dB at 20kHz	45dB, 38dB (R on L)
Outputs & Impedances	775mV and 150mV tape 600R max, 1k $\Omega$ on disc, 10k on aux	agreed agreed


Table Two

PARAMETER	SPECIFIED	MEASURED
Output Power (RMS, 8R at 1kHz)	110W	121W
Peak Delivery	300 VA	205W
Signal to Noise Ratio (unweighted)	> 100dB	102dB
THD (any level to clipping)	< 0.015%	below noise
Gain	30dB	agreed
Power Bandwidth ( $-3dB$ )	6Hz-50kHz	5Hz-45kHz
Damping Factor (50Hz)	80	agreed
Input Impedance	50k	agreed
Protection Operation Load	[4R]	[4R3]

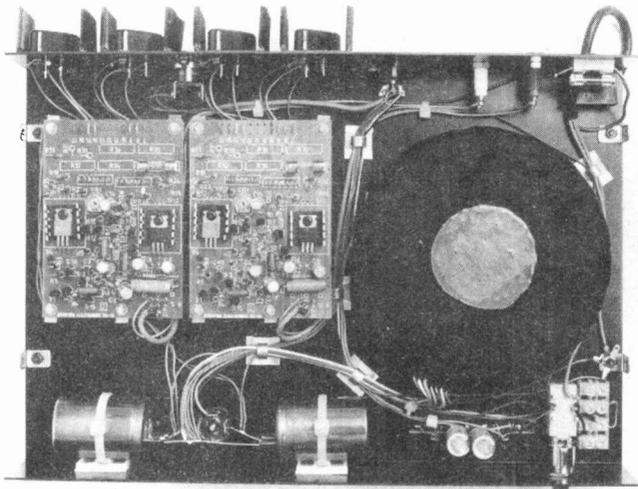Tables One and Two. These are for the pre-amp and power amp respectively, comparing the claims against the measurements.



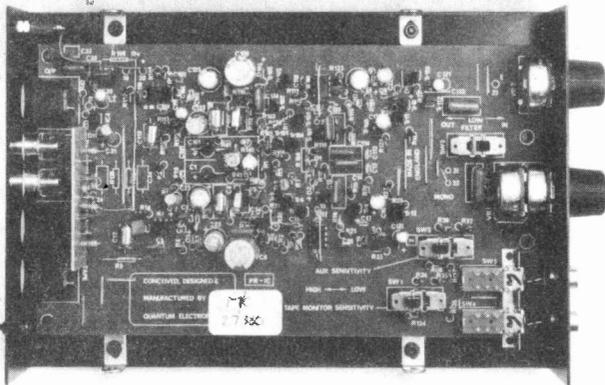Above: the 204 power amp revealed. Note the huge toroidal mains transformer and pre-amp PSU board away to the left. Separate heatsinks are used for each power output device. Below: a de-cased 102 pre-amp. Most components are PCB mounted to cut down interwiring. Instructions on pickup matching are written on the inside of the lid! (not shown).



## Figuring Out The Figures

In summary of Tables One and Two we can say that the Quantum 102/204 is an amplifier of better than average noise performance with excellent distortion figures — or lack of them — which has a high enough overload on the disc input to ensure that no problems will ever be encountered in normal use.

The S/N on moving coil input is very good indeed, practically up to moving magnet input standards and has little hum component to give trouble. No mean feat this. My review model was set-up, to match the inevitable Coral MC81 as a 'norm', but I spent many a happy hour playing with the matching cards for Ortofon, Goldring and Shure moving magnet designs. The moving coil input bettered Coral's own H300 head amp for noise and distortion — which suggests that the self-standing Quantum moving coil pre-amps would be worth a look or two.

The 204s figures are unimpeachable — with the exception of that minimum impedance into protection. I would like to have seen around 2R there — the lower the better I suppose. Still it is honestly specified and lower impedance driving modules are available if you're troubled. In use the 204 drove my 105 IIs with no sign of distress at all. Check your speaker impedance curves before matching though. Better safe than burning.

## What A Turn On

Funny how all reviewers leave discussing the sound of equipment until the end of an article, as though we test it all out first, THEN sit and listen. No chance. Just like everyone else it's a case of home with the packages, out of the boxes and CLICK . . . . . In fact unwiring it all to start injecting boring test signals is the worst part of this job.

Quite frankly I didn't know what to expect from the Quantum, I knew the sound of its competitor Crimson well and respected it as the best module sound around and comparisons are inevitable I suppose. A direct AB test will have to wait though as our German edition has our Crimson set-up at present and is more than a little reluctant to part company with it. Damn cheek if you ask me, who won the war anyway?

So it is to the Lecson AC1/AP3 II combination that the Quantum was to be referenced, using KEF 105 II speakers and Coral MC81 and Ortofon/SME 30H cartridges. (The sound of the latter grows on me the more I hear it.)

With the 102 set to moving coil, the first thing I noticed was the much better noise performance. At first I thought something wasn't connected! The sound is open and beautifully rich in all the little things that make music on a good system worth listening to. The pre-amp is very good indeed, but I felt that against the Lecson the 204 lacked bass punch. The lowest registers were not as well defined, or as 'coherent'. Mid-range and treble were little different.

## Summary

In a word — yes. A good solid product which does its job superbly and gives excellent value for money, both in terms of its sound quality and its engineering. Home built hi-fi has a new championship contender!

## Marantz Esotec

Below: the new Marantz Esotec TT 1000 turntable. This employs a glass and aluminium 'sandwich' as a base and a 5mm thick glass turntable mat. The idea is to cancel any resonances due to the base material and produce a truly non-resonant support. Air suspension is employed to hold this massive machine clear of the ground and the motor is claimed to have sufficient power to reach full speed in ¼ turn. Released in September — price not yet fixed, but will be VERY high.



**How do you  
put over 2,000  
different tools  
and toolkits into  
one envelope?**



The New Toolrange Catalogue is still the only comprehensive single source of electronic tools and production aids. Products from over 100 top manufacturers are available from stock. For your free copy of the new catalogue contact Toolrange today.

**toolrange**

Upton Road, Reading, Berks. RG3 4JA  
Telephone: Reading (0734) 22245 Telex: 847917

## DIGISOUND LIMITED

*—providing a service to all who  
are interested in electronic  
music*

### ETI 80. MODULAR SYNTHESISER


Complete kits or P.C.B.'s and individual components supplied. Front panels now available in 1.15mm white PVC clad steel with holes and lettering to the style shown in ETI. Also blank panels allowing you to put other modules in the same format. Exclusive suppliers to the U.K. hobby market for customised I.C.s from Solid State Music and Curtis Electromusic Specialties for use in music and other audio applications. I.C.'s include voltage controlled oscillators, filters, amplifiers and envelope generators. Also stocks of the elusive Q81 temperature compensating resistor (1k, 1%).

Send S.A.E., or 12p in stamps, for current price list of components and range of synthesiser modules available.



**DIGISOUND LIMITED,**  
13 THE BROOKLANDS, WREA GREEN,  
PRESTON, LANCs. PR4 2NQ  
Tel.: 0772 683138 (MAIL ORDER ONLY)

## HARD LABOUR?

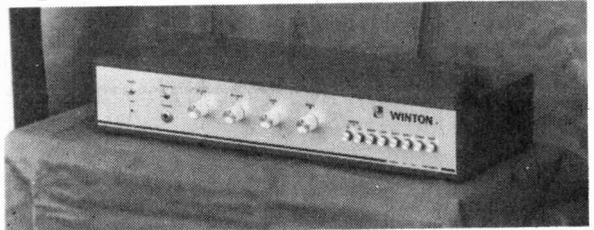

Not exactly, about 20 hours spent building the amplifier that was the success story of 1979, and has no peers in 1980.

The WINTON, 50+50 watts of real Hi-Fi using power Mosfet's and a specification and performance that is totally unprecedented in this price range.

You will find it an interesting and absorbing project, serve time and get your just deserts.

Act Now, send us a 10p stamp and we will send you a spec' sheet that will make you sit quietly for a while reflecting just how ordinary some amps really are, or get involved at once, send us your cheque for the best value in Hi-Fi kits around

**Power MOSFET's rule, ok?**

**COMPLETE KIT**, of all parts necessary to build the P.W. WINTON **£133.50**

**SPECIAL LIMITED OFFER £115**

Order with complete confidence (C.W.O. only please) from:

**T.&T. ELECTRONICS**  
Green Hayes, Surlingham Lane, Rockland St. Mary, Norwich,  
NR14 7HH. Telephone 05088 632

**PRICE INCLUSIVE OF V.A.T. & CARRIAGE.**  
Callers by appointment only

ETI JULY 1980

# GREENWED

443A Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 40p post

## OUT NOW THE NEW 1980 GREENWED CATALOGUE

### FEATURES INCLUDE:

- 60p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 40p + 35p POST

### BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES

**K001** 50V ceramic plate capacitors. 5%, 10 of each value 22pF to 1,000pF, total 210. **£3.68.**  
**K002** Extended range 22pF to 0.1µF. 330 values **£5.53.**

**K003** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ. 110 altogether for **£5.07.**

**K004** Mylar capacitors, min 100V type 10 each all values from 1,000pF to 10,000pF Total 130 for **£4.05.**

**K007** Electrolytic capacitors 25V working small physical size 10 each of these popular values 1 2.2, 4.7, 10, 22, 47, 100µF Total 70 for **£3.59.**

**K008** Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for **£6.05.**

**K021** Miniature carbon film 5% resistors CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.15.**

**K022** Extended range. Total 850 resistors from 1R to 10M **£8.50.**

**K041** Zener diodes 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for **£16.37.**

### REGULATED PSU PANEL

Exclusive Greenwed design — better spec, than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready to test — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply

**SPEC** Output voltage 0-28V  
Output current 20mA-2A  
Source Impedance 0R1  
Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options **£6.75**

### TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number — almost all are full spec. devices. Some have bent leads. Over 30 different types have been found by us including BC184/212/238/307/328 BF196/77, ZTX107/8/9/342/450/550, etc. Only available as a mixed pack at **£3** per 100, **£7** per 250 **£25** per 1000

### BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer — all metal construction. 50mm dia x 20mm **70p.**  
Z402 Miniature type buzzer. 6, 9 or 12V only 22x15x16mm. Very neat **53p.**

Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only **£1.**

A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied **£1.50.**

W892 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket **85p.**  
W890 DIL Reed relay SPCO 2.4-10V 20DR coil. Only **£2.20.**

See last month's ad for other items

### COMPONENT PANELS

Z525 Contains 11 800mA 60V 2N5061 SCR's, 11 6V8 zeners, 11 1N4004 diodes plus Rs, Cs, etc. Only **£1.**  
74 Series ICs — Gates and complex logic, 20 asstd ICs on panels **£1;** 100 ICs **£4.**  
Z527 2x6V reed relays 6x2S030 or 2S230 6x400V reeds, plus Rs. Only **50p.**

### TM4030 RAM

4096 bit dynamic RAM with 300ns access time, 470ns cycle time; single low capacitance high level clock i/p. fully TTL compatible; low power dissipation. Supplied with data **£2.75.**

### VEROCASE SALE!!!

Only one size left now — these have sold very fast — if you want a 1/2 price case like 75-3008, only in GREEN, order one now!! 21051 180x120x85mm **£2.30.**

### BULK SUPPLIES

All new full spec. devices. Prices are for a minimum of 100 of any one device and exclude VAT, which must be added at 15%. Minimum order value from this section is **£10+VAT+post. VAT receipt on request.**

AC187K	.20	BF757	.27
AD161/2	.45	BF840	.17
BC107	.07	BFW43	.32
BC108	.08	BFY17	.19
BC109	.07	BFY50	.13
BC114	.06	BFY51	.13
BC117	.07	BFY52	.13
BC118	.05	BFY56A	.16
BC119	.14	BFY56A	.16
BC125	.06	BFY64	.15
BC139	.14	BR101	.28
BC147	.05	BRX48	.085
BC148	.05	BRV46	.17
BC148B	.05	BSX20	.075
BC149	.05	BSY38	.12
BC159	.05	BSY56	.10
BC168C	.055	BSY82	.19
BC169C	.055	BSY85	.23
BC172C	.05	BSY95A	.085
BC177	.07	BT121	.80
BC182B	.045	BU205	.60
BC1838	.045	BU206	.60
BC184L(T05)	.045	BU407	.60
BC212	.045	CV7001	.23
BC212B	.045	CV7493	.19
BC213L	.045	CV7588	.18
BC214L(T05)	.045	HE0475	.085
BC237	.05	MJE340	.22
BC237B	.05	MPS2369	.08
BC237C	.055	MPS3638A	.06
BC238B	.06	MPS8515	.06
BC239B	.055	MPSA66	.24
BC252	.07	OC44	.19
BC256A	.05	OC45	.17
BC308	.05	OC139	.26
BC308B	.055	OCP71	.63
BC320	.07	PBC108	.065
BC328	.07	TIP27	.22
BC337	.07	TIP41A	.28
BC348	.07	TIP42A	.29
BC351	.14	TIP2955	.46
BC413	.05	TIP3055	.45
BC485B	.06	TIS91	.12
BC486A	.06	ZTX107	.06
BC546B	.06	ZTX212	.06
BC547C	.055	ZTX214	.06
BC548B	.05	ZTX303	.07
BC556A	.06	ZTX311	.07
BC556B	.06	ZTX313	.06
BC557A	.06	ZTX341	.07
BC737	.07	ZTX450	.06
BCX32	.05	ZTX501	.96
BCX33	.05	ZTX503	.07
BCY32	.12	ZTX550	.06
BCY71	.11	2N1021	.94
BCY72	.10	2N1132	.16
BD112	.64	2N1377	.62
BD131	.18	2N1711	.18
BD132	.18	2N1893	.16
BD133	.18	2N2369	.12
BD137	.20	2N2646	.34
BD138	.20	2N2894	.12
BD181	.40	2N2926Y	.045
BD184	.45	2N2926R	.045
BD246	.30	2N3053	.13
BD278A	.32	2N3064	.36
BD433	.32	2N3065	.30
BD525	.24	2N3442	.08
BD526	.24	2N3583	.42
BD543A	.30	2N3618	.80
BD695A	.45	2N3702-10	.045
BD696A	.45	2N4124	.24
BF173	.13	2N4400	.08
BF181	.15	2N4401	.06
BF195	.055	2N4403	.06
BF196	.055	2N4410	.06
BF197	.055	2N5193	.20
BF198	.055	2N5195	.22
BF241	.055	2N5401	.17
BF255	.075	2N5447	.06
BF257	.19	2N5831	.08
BF258	.20	2N6121	.16
BF324	.13	2SC536	.05
BF337	.19	2SC1617	.62
BF355	.18	2SC2068	.43
BF394	.055	2SC2073	.45
BF414	.065		
BF450	.095	Send SAE for latest bulk buyers list.	
BF451	.08		

# TUNE IN!

## Build the World Famous CHROMA-CHIME



Give your friends a warm welcome


This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries
- Fully Guaranteed

\* Save pounds on normal retail price by building yourself.

ONLY  
**£11.95**  
+ 75p p&p  
UK ONLY

## TMS 1000N

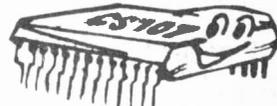

— MP0027A Micro-computer chip  
available separately if required. Full  
24 tune spec device fully guaranteed.

This unique chip can be used not only for  
electronic door chimes but for other projects  
requiring musical output: New low price only

**£4.95** inc p & p  
Free applications manual  
and data supplied with device!  
(Or 30p separately)

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE  
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:  
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

I enclose cheque/PO value £ \_\_\_\_\_  
or debit my ACCESS/BARCLAYCARD account no.


Signature \_\_\_\_\_

# CHROMATRONICS
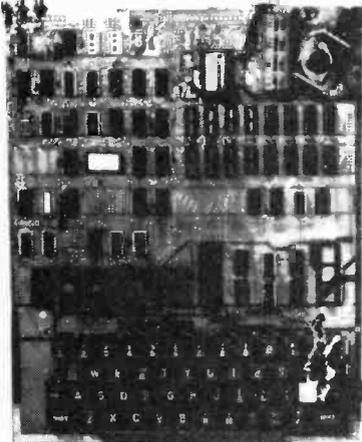
# CHROMASONIC electronics

56 FORTIS GREEN ROAD MUSWELL HILL LONDON N10 3HN  
TELEPHONE 01-883 3705 01-883 2289

*your soundest connection in the world of components*



**Demonstration At Our Shop**  
(enter through stationers)

**NOW AVAILABLE**  
Low cost computer in kit form

## UK101

**NO EXTRAS NEEDED**  
**SIMPLY HIT**  
**'RETURN' AND GO**

As seen in  
P.E.  
August to November '79

Kit price  
only **£199 + VAT**

**NEW**  
**MONITOR**  
**FOR UK101**  
**£22.00**  
**+ VAT**

**EXTRA**  
**4K MEMORY**  
**8x2114**  
**ONLY**  
**£32 + VAT**

**INCLUDED FREE**

Sample tape with extended  
machine code moditor and  
disassembler

Price includes RF modulator and  
power supply  
**ABSOLUTELY NO EXTRAS**  
**NEEDED**

Also available ready assembled,  
tested and ready to go  
only **£249 + VAT**

Build, understand, and  
program your own  
computer for only a  
small outlay

**6502 Assembler / Editor for UK101 £14.90 + VAT**

## STOP PRESS

The latest edition of our 'STOP PRESS' is now available, and contains an up-to-date price list showing all the items that we stock. Just send an S.A.E. or phone for your FREE copy.

Dynamic RAMS		Interface		CASE AVAILABLE		LS series					
	£			£24.50							
4027	3.01	8205	3.00	LM3065N	1.50	SN76660N	0.75	74LS125	0.36	74LS279	0.57
4050 (200ns)	2.50	8212	2.00	LM3900N	0.50	SN76666N	0.75	74LS126	0.36	74LS283	1.09
4050 (350ns)	2.35	8216	2.08	LM3905N	1.00	TAA263	2.20	74LS132	0.60	74LS289	4.50
4060 (300ns)	2.39	8224	2.77	LM3080E	0.67	CA3080E	0.67	74LS133	0.39	74LS290	0.91
4116	5.75	8228	4.13	CA3081	1.30	CA3081	1.30	74LS136	0.36	74LS293	0.91
		8251	5.00	CA3082	1.30	CA3082	1.30	74LS138	0.65	74LS295	1.30
		8253	6.93	CA3086	0.45	LM3911N	1.10	74LS139	0.65	74LS298	1.16
		8255	4.95	CA3088	1.75	M252 81 AA	7.50	74LS145	0.97	74LS348	1.39
				CA3090Q	3.95	M253 81 AA	7.95	74LS151	0.81	74LS352	1.04
				CA3097E	1.85	MC1310P	1.00	74LS153	0.52	74LS353	0.92
				CA3123E	1.70	MC1312P	1.85	74LS154	1.30	74LS362	4.21
				CA3130E	0.85	MC1314P	3.35	74LS155	0.72	74LS365	0.47
				CA3140E	0.36	MC1315P	5.50	74LS156	0.72	74LS366	0.47
				CA3160E	1.00	MC1327P	0.95	74LS157	0.57	74LS367	0.47
				CA3600E	3.69	MC1330P	1.00	74LS158	0.57	74LS368	0.47
				ICL8038BC	3.57	ICL8038BC	3.57	74LS160	1.09	74LS373	0.78
				ICL8038CC	8.82	MC1351P	1.20	74LS161	0.69	74LS386	0.36
				ITT7120	3.40	MC1352P	1.35	74LS162	1.16	74LS393	0.84
				LF351N	1.90	MC1375P	1.73	74LS163	0.69	74LS668	1.17
				LF356N	0.40	MC1445L	2.95	74LS164	1.06	74LS670	1.71
				LM301AH	0.80	MC1456CG	1.75	74LS165	0.72		
				LM301AN	0.36	MC1458CP1	0.45	74LS166	1.65		
				LM307H	0.25	MC1495L	5.98	74LS168	1.71		
				LM307N	0.66	MC1496P	0.75	74LS169	1.71		
				LM308N	0.43	MC3302P	0.65	74LS170	1.72		
				LM308N	0.95	MC3340P	1.59	74LS173	0.81		
				LM308N	0.55	MEM780	2.48	74LS174	0.97		
				LM308T	0.95	NE531N	1.00	74LS175	0.97		
				LM319H	2.25	NE540L	2.97	74LS181	2.77		
				LM322N	3.87	NE555N	0.22	74LS188	0.44		
				LM324N	0.50	NE556N	0.60	74LS189	2.08		
				LM339N	0.50	NE560N	3.25	74LS190	0.86		
				LM348N	0.90	NE561N	3.95	74LS191	0.86		
				LM370N	2.90	NE562N	3.95	74LS192	1.04		
				LM371H	2.05	NE565N	1.10	74LS193	1.04		
				LM373N	2.90	NE566N	1.20	74LS194	0.86		
				LM374N	2.90	NE567N	1.35	74LS195	0.97		
				LM377N	1.75	SAA1024	3.40	74LS196	0.97		
				LM378N	2.05	SAA1025	4.85	74LS197	0.97		
				LM379S	2.05	SL414A	1.90	74LS221	0.92		
				LM380N8	0.85	SL440	2.90	74LS220	2.08		
				LM380N	0.75	SD6000V	2.98	74LS221	2.08		
				LM381N	1.45	SN75491N	0.75	74LS222	2.08		
				LM381AN	2.50	SN75492N	0.85	74LS224	2.08		
				LM382N	1.20	SN76001N	0.95	74LS225	2.08		
				LM386N	0.78	SN76003N	1.98	74LS228	2.50		
				LM387N	0.95	SN76008K	1.60	74LS247	1.09		
				LM389N	0.95	SN76013N	1.40	74LS248	1.09		
				LM725CN	2.25	SN76013ND	1.40	74LS249	1.09		
				LM1303N	1.00	SN76018K	1.50	74LS251	0.96		
				LM1808N	1.95	SN76023ND	1.30	74LS252	0.92		
				LM1812N	5.40	SN76033N	2.00	74LS253	0.92		
				LM1820N	1.00	SN76532N	1.55	74LS257	0.92		
				LM1820N	1.98	SN76544N	1.25	74LS258	0.92		
								74LS259	1.39		
								74LS261	4.50		
								74LS266	0.37		
								74LS273	1.70		

**8 x 4116**  
only  
**£40.00**  
**+ VAT**

**21L02**  
**8 for**  
**£7.00**

**16 for**  
**£13.00**

**32 for**  
**£25.00**

**64 for**  
**£45.00**  
All excluding VAT

All prices are EXCLUSIVE of VAT. Postage and packing 30p (computers charged at cost). CALLERS WELCOME. Hours 9.00 am-6.00 pm (enter through stationers). TRADE and EXPORT inquiries welcome. Phone your orders through our ORDER-RING line quoting your ACCESS or BARCLAYCARD number (Min. tel order £5).

# CAPACITORS AND TIME CONSTANTS

A.S.Lipson takes the bull by the time constants and explains how to use capacitors in timing circuits.

Those little brown discs or large blue cylinders that do funny things to your multimeter if you try to measure their resistances are frequently used as AC coupling devices, but they are also of great use in timing circuits. A resistor and capacitor together can produce a changing voltage whose magnitude at any moment can easily be calculated.

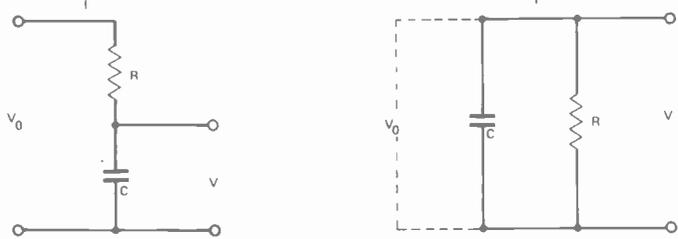


Fig.1 Series and parallel RC networks.

## First The Circuits

The first circuit in Fig. 1 consists of a resistor,  $R$  in series with a capacitor,  $C$ . A voltage,  $V_0$ , is applied across the combination and the output voltage (that across the capacitor) is monitored. The output voltage ( $V$ ) slowly rises from zero, coming closer and closer to the value of  $V_0$ , although it never actually quite reaches it. A graph showing output voltage plotted against time is shown in Fig. 2a. It is found by experiment that the rate of increase of voltage becomes smaller if either  $R$  or  $C$  are increased, and greater if either is decreased. That is, the voltage rises more slowly for large values of  $R$  and  $C$  than it does for small values of  $C$ . In fact, if we take the product  $R \times C$ , ( $R$  in ohms,  $C$  in Farads) we find that this gives the time (in seconds) required for the output voltage  $V$  to reach about two thirds the value of  $V_0$ .

The second of the two circuits consists of a capacitor and resistor connected in parallel. The capacitor is charged by an external source to a voltage  $V_0$ , and then disconnected. The output voltage,  $V$  is monitored once again. Here, we find that  $V$  slowly decreases from  $V_0$  to zero, getting smaller and smaller, but, again never quite making it (Fig. 2b). Again, it is found that the voltage changes more slowly if either the resistance or the capacitance (or both) are increased and changes faster if they are decreased.

## Time Constant

The product  $R \times C$  is called the 'time constant'  $\tau$  (the greek letter Tau) of the circuit and it can be used to find rough values for  $V$  at different times. It turns out that, no

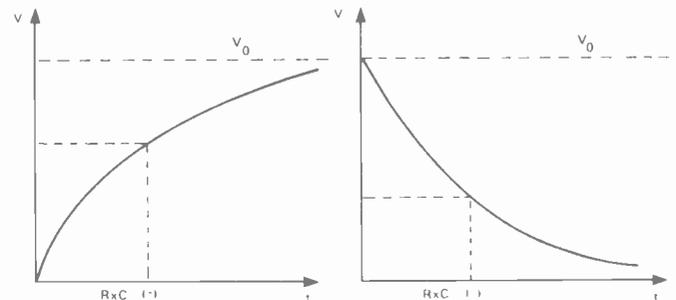


Fig.2 The output voltages associated with the RC networks of Fig.1.

matter how long the voltage has been changing in the circuit, it always takes  $\tau S$  for the voltage across the capacitor (in the first circuit) to increase by two thirds of the remaining voltage. eg If  $V_0$  is 9V, and the output voltage  $V$  at a time  $t$  is 4V, then after  $\tau S$ , at time  $t + \tau$ ,  $V$  will have risen by two thirds of  $(9 - 4)$  volts, or 3 1/3 volts. This can be used to plot a graph of  $V$  against time. At  $\tau$  seconds,  $V$  will be two thirds of  $V_0$ . At  $2\tau S$ ,  $V$  will have risen by two thirds of the remaining voltage, ie by two thirds of  $1/3 V_0$ , and will thus have risen to eight ninths (approximately) of  $V_0$ . Similarly, voltages at  $3\tau S$ ,  $4\tau S$  and so on may be calculated and plotted on a graph (Table 1 and Fig. 3). A line may then be drawn in freehand, joining the points, and approximate values for  $V$  at different times calculated.

This is all very well for rough values, but it is of considerably less use if we want to find exact figures — especially at times much less than the time constant. Fig. 4 shows a freehand curve drawn onto the first three calculated points on a graph. We know nothing from our method about the voltage before it reaches 2/3 of its final value, except that it starts at zero. The correct graph could be A or B or anything in between — we have no way of knowing,

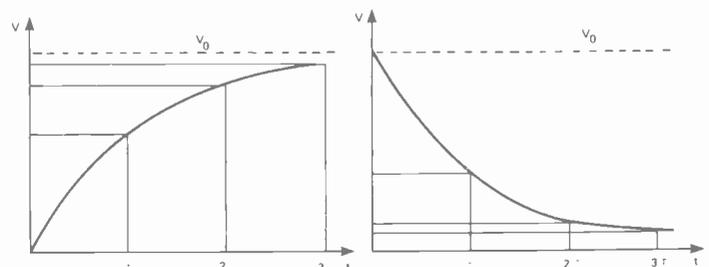


Fig.3 Plotting graphs of output voltage against multiples of time constant.

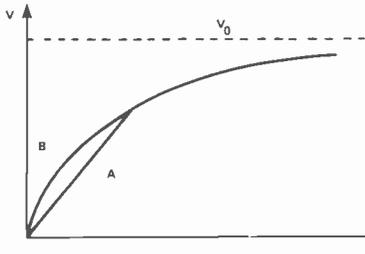


Fig.4 A freehand curve drawn onto the first three points calculated.

## Curve Drawing (No, Not . . .)

It is an interesting and useful property of the way in which the voltage changes in these circuits that, at any instant, if the voltage continued to increase (or decrease) at the same rate, it would reach its final value in exactly  $\tau S$ . The reason why it doesn't actually do this is simply that the rate of increase is not constant. As the voltage becomes larger (Fig.1a) or smaller (Fig.1b) its rate of change decreases. However, as has been stated, if the rate of increase of the voltage,  $dV/dt$  was constant from any time  $t$ , then  $V$  would reach  $V_0$  (or zero, as the case may be) at time  $t + \tau$  (Fig.5).

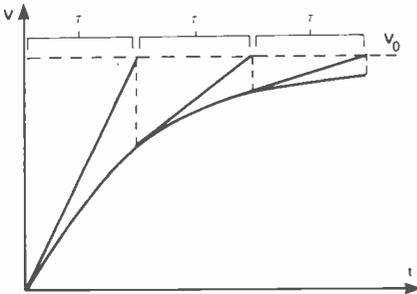


Fig.5 V tends towards  $V_0$ .

We can make use of this property of the curve. Mark on the graph (Fig.6) a line representing the final voltage,  $V_0$ , of the system. Now mark along this line a distance  $\tau$  from the beginning (point A) and draw in a straight line from this point to the origin, 0. This, then, will give a fair approximation to the voltage as it changes in the first few moments. Now choose a point on this line, near the bottom (P1). Mark a distance  $\tau$  along from P1 and find the point on the line representing  $V_0$  directly above. Call this point B. Draw a line from P1 to B. Now choose a point P2, near P1 on this line, and repeat the same process. Eventually, the lines shape themselves round a curve, which turns out to be a fair approximation to the graph of voltage plotted against time.

This method is fine, but it has three great disadvantages; it takes a long time to draw the curve this way, it isn't very accurate beyond about  $2\tau$  and (as you will have realised if you had to read the last few paragraphs more than four times) it's complicated. If we want to find values of  $V$  beyond  $\tau$  seconds, we can use the first method of drawing the graph and if we want values of  $V$  for times less than  $\tau$  seconds, this second method can be used, but it is simpler, if we only want to know one value,

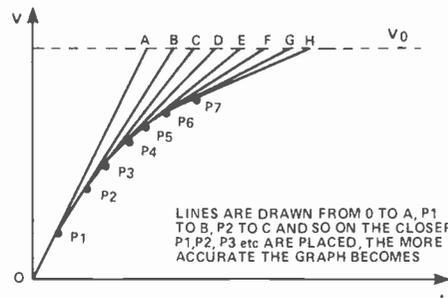


Fig.6 This method of drawing graphs is reasonably accurate up to twice the time constant.

LINES ARE DRAWN FROM 0 TO A, P1 TO B, P2 TO C AND SO ON THE CLOSER P1, P2, P3 etc ARE PLACED, THE MORE ACCURATE THE GRAPH BECOMES

## Capacitors.

We are so used to thinking in terms of currents and voltages that it is very easy to forget the existence of a more basic quantity — charge. Charge is what passes when a current exists. Current, then, is actually rate of passage of charge. Now capacitance is defined as the ratio of the charge stored in a component to the voltage developed across it. That is, if  $C$  is the capacitance in Farads,  $Q$  is the charge in coulombs and  $V$  is the voltage,

$$C = \frac{Q}{V} \quad \text{or} \quad Q = VC$$

We can differentiate each side of the equation:-

$$\frac{dQ}{dt} = \frac{d}{dt}(VC) = V \frac{dC}{dt} + C \frac{dV}{dt}$$

Now  $C$  is a constant, so  $dC/dt$  is zero:-

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

Finally, we can see that, since current is rate of flow of charge,  $dQ/dt$  is the current flowing into the capacitor, so

$$I = C \frac{dV}{dt}$$

Now let's take another look at the circuit in Fig.1a. If we assume that no current is being drawn from the output, then the current into the capacitor must equal the current through the resistor. The voltage across the resistor, though,  $V_R$ , is obviously equal to  $V_0 - V$ , and by Ohm's law;

$$(V_0 - V)/R = I$$

Therefore,

$$(V_0 - V)/R = C \frac{dV}{dt} \quad \text{or} \quad V_0 - V = RC \frac{dV}{dt}$$

This is the differential equation that must be solved to find  $V$ . The mathematicians out there might like to show that the equation is solved by

$$V = V_0 (1 - e^{-t/RC})$$

where  $e$ , as any scientific pocket calculator will tell you, is 2.7182818 and  $t$  is the elapsed time. This is the equation we can use for precise values. We'll do an example; a 9V power source is connected across a series combination of a 47k resistor and a 10uF capacitor. What is the voltage across the capacitor after 0.6 S? Fitting the values into the equation:-

$$\begin{aligned} V &= V_0 (1 - e^{-t/RC}) \\ &= 9 \times (1 - \exp(0.6 / (4.7 \times 10^4 \times 10^{-5}))) \\ &= 6V49 \end{aligned}$$

(If you don't believe me, try it . . .)

A similar sort of argument works for the circuit in Fig.1b. The output voltage  $V$  is given, by Ohm's law, by

$$V = IR$$

However,  $I$  in this case is the current flowing out of the capacitor, and so it is given by the relation

$$I = -C \frac{dV}{dt}$$

Hence we have

$$V = -RC \frac{dV}{dt}$$

And we find that this differential equation has the solution

$$V = V_0 e^{-t/RC}$$


where  $V_0$  is the voltage to which the capacitor was charged.

Let us suppose we have a 200 uF capacitor in parallel with a 330k resistor. The capacitor is charged up to 12 V and the supply removed. What is the voltage across it after 2 S? Well, plugging these values into our equation,  $V_0$  is 12 V,  $t$  is 2 S,  $R$  is  $3.3 \times 10^5$  ohms, and  $C$  is  $2 \times 10^{-4}$


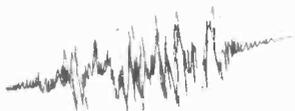
## HOME

- Steam train and whistle (80019). Simulates the sound on steam and whistle **£6.50**  
 Clap switch (79026). You clap your hands and the light comes on **£6.60**  
 Elekdoorbell (79095). Program your own signature **£22.00**  
 Touch dimmer (78065). Room lighting controlled by single touch **£6.80**  
 TV sound modulator (9925) **£3.75**  
 Simple sound effects (79077) **£5.70**  
 Electronic nuisance (80016) **£3.85**  
 Ultrasonic transmitter (audio) (79510) **£7.65**  
 Ultrasonic receiver (audio) (79511) **£9.95**  
 DJ killer (79505) **£8.80**  
 Quiz master (79033) **£6.50**  
 Variable fuzz-box (9984) **£6.55**  
 Ioniser (9823). Produces a high concentration of negative ions **£9.55**  
 Oscillographics (9979). Random displays patterns on your oscilloscope **£11.25**  
 Cackling egg timer (9985). Times your egg, then clucks like a hen! **£7.20**  
 Pools forecaster (79053). Weighs up the odds and could win you a fortune **£8.15**  
 Loudspeaking telephone amplifier (9987). Amplifies signal without direct connection **£11.50**  
 Sensitive lightmeter (9886). Light measurement using silicon photodiode **£12.55**  
 Nicad charger (79024). Automatically prevents over charge of cells **£15.20**  
 Proximity detector (9974). Detects movement in a room (electric field change) **£9.80**  
 Central alarm (9950). Master station slave station **£10.85**  
 Alarm unit **£3.10**  
 Touch tuning FM preselect unit (79519). With digital display **£17.50**  
 Talk funny (80052). Deliberate electronic distortion of speech and music signals using a single IC, the 2206 **£9.60**  
 Colour generator (80027). Using coloured light for an effective display **£19.70**  
 Pools predictor (79053) **£8.15**



## HIGH FREQUENCIES

- Aerial amplifier (80022). Improves the sensitivity of an existing receiver specify VHF/UHF **£5.45**  
 UHF/VHF modulator (9976). Generates a carrier for TV signals **£6.25**  
 Mini shortwave receiver (9920). Interesting introduction to SW radio **£6.95**  
 FM IF strip (78087). Using the CA 3189 limiter demodulator IC **£13.05**  
 Stereo decoder (79082). Compatible with the FM IF strip **£15.10**  
 Digital tuning scale (80021). A sophisticated digital frequency indication **£46.30**  
 Ohm aerial (80076.1 + 2). A practical shortwave aerial for 1.8-30MHz **£10.30**

Buying one of our PROJECT PACKS will save you the frustration of tracking down those evasive components that hold up the completion of your project. Our packs include Printed Circuit Board, all the components listed in the article together with sockets and solder. Cases, knobs, etc. can be supplied as extra items if required. Ask for more information!


## MUSIC

- Chorosynth (80060). A cheap mini-synthesizer **£57.90**  
 Elektor vocoder (80060). The first vocoder designed to be built from a kit with excellent features. It has 10 channels **£162.50**  
 Front panels for vocoder per channel **£1.25**  
 Analog reverberation unit (9973). Kit with 1 SAD 1024 **£27.70**  
 Piano. Excellent kit of an electronic piano with three voices.  
 Master tone oscillator/generator **£37.00**  
 Octave PCB (9914) **£18.75**  
 Filter PCB (9981) **£16.50**  
 Power supply (9979) **£19.05**  
 Digital reverberation unit main board **£67.20**  
 Extension boards **£46.30**
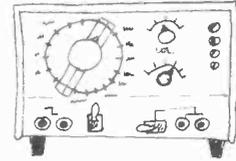
## NEW - NEW



- \* **Battery protection (80109)**. Forgetting to turn off the headlights need no longer be a motorist's nightmare. This project is designed to monitor the battery voltage and switch off the lights automatically in all kinds of motor vehicles **£5.15**
- \* **Transistorignition (80084)**. A system which combines the most significant advantages of other systems including the conventional system! **£20.45**
- \* **A dip-stick probe (80102)**. There are all kinds of indicators and warning lights in modern cars, but an oil temperature indicator is rarely included. The easiest way to add this type of indicator to an existing car is to mount a temperature sensor in the dip-stick.  
 Project without dip-stick **£3.65**  
 Dip-stick with indicator (short) **£11.00**  
 Dip-stick with indicator (long) **£11.45**
- \* **Intelligent wiper delay (80086)**. This wiper delay only needs to be told once what is required of it. It will then carry out your orders until you change them, which you can at any time. **£15.85**
- \* **Active car aerial (80018-1 + 2)**. If there is one place to use a good aerial it is in a car **£13.85**
- \* **Stop thief! (80097)**. There are all sorts of systems for protecting cars, but this one is unusual: it is deception, rather than protection. **£4.20**
- \* **Battery voltage indicator (80101)**. Only a few components are needed to obtain an optional indication of the battery condition: a single lamp that changes colour as the battery goes into the danger area **£6.85**



## MEASURING

- Digital thermometer (80045)  
 LCD display (supplied without relay) **£28.95**  
 LED display (supplied without relay) **£23.20**  
 Relay (two pole changeover) **£2.45**  
 AC millivoltmeter (79035). FET input meter circuit and audio generator **£6.30**  
 Universal digital meter (79005). Digital replacement for pointer instruments **£14.65**  
 Precision timebase (9448). Generates a precision 1 Hertz pulse **£13.10**  
 Power supply for timebase **£5.40**  
 Universal timebase (78100). Crystal controlled timebase **£18.70**  
 1/4 GHz counter (9887 1 + 2 + 3 + 4). Excellent kit count up to 250 MHz **£98.15**  
 Minicounter (9927). 1KNz 4 digit display **£27.70**  
 Audio analyser (9932). An analyser which can point the deficiencies in a particular audio chain or environment **£14.80**  
 Spot sinewave generator (9948). Programmable sinewaves with less than 0.0025% THD **£12.95**  
 Simple function generator (9453). Sine, square and sawtooth outputs **£27.70**  
 Sinewave generator (79019). Always sinewaves when you need them **£8.90**  
 TV scope basic version (9968 1/5). Produces display up to 1 KHz on TV **£34.50**  
 TV scope advanced version (9969 1/3). Converts basic scope to 100KHz bandwidth **£48.25**  
 Digscope (9926) **£32.35**  
 Digitalrad (79088). A digital capacitance meter with a wide range **£25.10**  
 Gate dipper (79514). Checks the resonant frequency of a circuit **£16.00**

## AUDIO

- Equaliser (9832). Single channel audio equaliser with slidepots **£17.70**  
 with turnpots **£15.60**  
 with preset pots **£13.95**  
 UAA180 LED meter (9817). A two-channel display meter with LEDs **£13.00**  
 Peak programme meter (9850). For use with UAA180 LED meter to give stereo audio display **£13.00**  
 Luminant (9949 1 + 2 + 3). A novel LED audio level indicator **£20.70**  
 Parametric equaliser (9897)  
 filter section (9897-1) **£6.45**  
 Tone control section (9897-2) **£5.20**  
 Audio analyser (9932). An analyser which can pinpoint the deficiencies in a particular audio chain or environment **£14.80**  
 Preconsonant (9954). A high-performance amplifier **£5.75**  
 Consonant (9945). A complete audio control preamplifier **£34.65**  
 Toppreamp (80031). Mini preamplifier for Topamp or any other Hi-Fi poweramp **£34.30**  
 Topamp (80023). Hybrid audio power amplifier with OM 931 (output 30 watt) **£18.50**  
 with OM 961 (output 60 watt) **£33.40**  
 Stentor (79070). A portable amplifier ideally suited for PA **£30.00**  
 Assistentor (79071). A preamp for use with Stentor **£7.00**  
 Elektornado (9874). A 2 x 50 watt or single 100-watt power amplifier **£19.50**  
 Electret microphone preamp (9866). Compact design that fits into the mike **£4.85**

## HOW TO ORDER:



Send a cheque or postal order to **DORAM ELECTRONICS LTD., Fitzroy House, Market Place, Swaffham, Norfolk, PE37 7QH**. All our prices include V.A.T. Please add 40p for postage and packing.


Office hours Monday-Friday, 9 a.m. to 5 p.m.  
 Telephone Swaffham (0760) 21627. Telex 817912.

# a de boer company



# WERSI at AURA SOUNDS
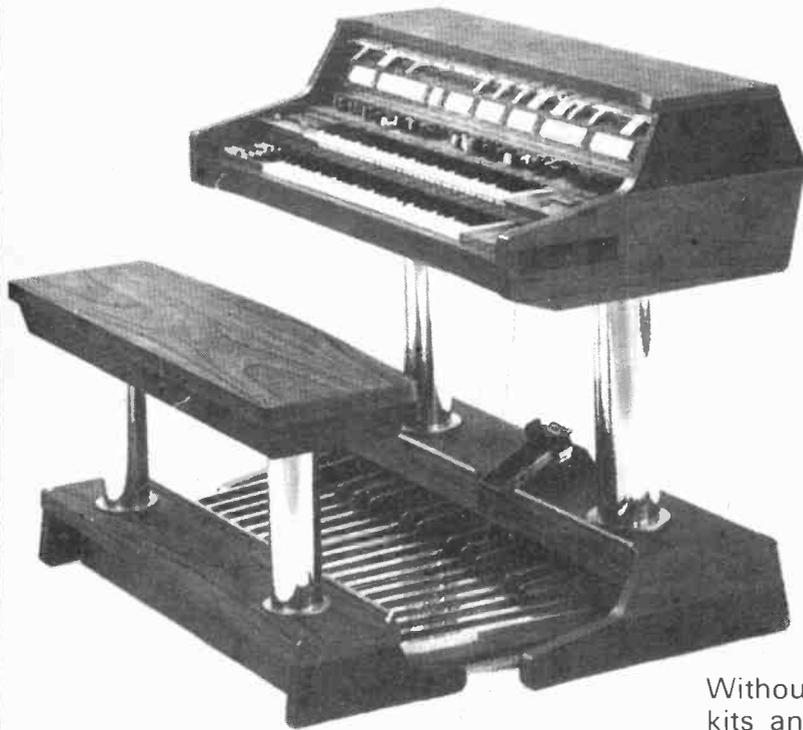
## Tomorrow's Electronic Organ Kit is Here



**POSSIBLY A NEW NAME TO YOU, BUT KNOWN IN OVER 25 COUNTRIES FOR THE SUPERIOR INSTRUMENTS WHICH THIS GERMAN COMPANY PRODUCE.**

USED BY WEST GERMAN BROADCASTING SERVICE. PLAYED BY KLAUS WUNDERLICH AND OTHER FAMOUS ORGANISTS.

WERSI is the first kit producing company applying the latest achievements of the space age technology. This has decisive effects on the technical and musical quality of WERSI'S electronic organs for the do-it-yourselfer.

The application of modern integrated circuits, so called ICs, simplifies the organ construction considerably. A single IC may replace up to 10,000 conventional electronic components.

In addition, ICs save a lot of space and they are extremely reliable devices.


WERSI, however, went a step farther yet. IC's which were not available on the open market, were developed for specific purposes by WERSI engineering. They are being produced by the most highly reputed IC manufacturers in the world. The result: economical electronic organs with the most up-to-date techniques and unsurpassed musical capabilities.

Without doubt the most comprehensive kits and the most up-to-date designs available today. Just consider a few of the features:

- Precision Master Generator, using MOS-LS1.
- Integrated electronic keying in 1<sup>2</sup>L technology.
- Unique — All switch functions are programmable.
- Even the smallest organ has drawbars in addition to fixed stops.
- Craftsman-made cabinets available in five veneers.
- Ready-made wiring harnesses eliminate errors.

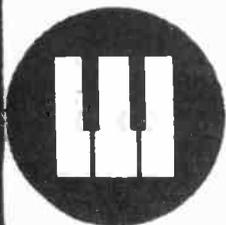**WERSI MAKES DO-IT-YOURSELF CONSTRUCTION EASIER THAN EVER BEFORE AT A FRACTION OF THE PRICE OF THE FULLY ASSEMBLED WERSI RANGE. GET THE FACTS NOW.**

**AURA SOUNDS** 14-15 Royal Oak Centre, Brighton Rd., Purley, Surrey. Tel: 01-668-9733  
and at 17 Upper Charter Arcade, Barnsley, W. Yorks Tel: Barnsley (0226) 5248.



**Send now for the 104 page full-colour catalogue.**

Please send me the full colour WERSI catalogue, price lists and supporting literature (weighing 1 lb!) I enclose a cheque/p.o. for £1.00.

Name.....

Address.....

Send to Aura Sounds (ET12), 14 / 15 Royal Oak Centre, Brighton Rd., Purley, Surrey.

# MICROFILE

By popular request Henry Budgett reviews the Sinclair ZX 80 microcomputer kit.

Ever since the first announcements and press comments on the new Sinclair ZX 80, Microfile's phone has been ringing with readers asking for a review. Well, after a few months of controversy and careful study here is the report you've all been waiting for.

## Kitted Out

If a system such as the ZX 80 is offered in kit form, it is often worth buying it in this form to save the odd few pounds and so we took a kit and built it. There are few components that raise any eyebrows and the whole thing was slotted neatly together in less than two hours. Whilst we were putting it together we also built in the suggested modification to change the video from black on white ("standard") to white on black ("normal") and this has proved very useful.

The instructions supplied with the kit are adequate and clear enough to allow any reasonably competent constructor to achieve success. There is a circuit diagram of sorts. We found great difficulty in deciphering the various bits and pieces so it would not be of any great help in debugging a "dead" system.

## The Great Turn On

The first thing to be said about the ZX 80 is that it worked, albeit a little hesitantly. I am rather accustomed to full size keys and have yet to come to terms with a touch keyboard. It does work very well, though, and shows no signs of wearing away even after weeks of hard use. The TV picture produced by the system is less than satisfactory. The much publicised juddering when keys are pressed is not in the least beneficial and, when you actually get round to running a program, the blank and flickering screen is positively unnerving.

The BASIC has been another point of considerable controversy. Inside the 4K ROM is a compressed Integer BASIC, the character set and the (minimal) operating system or monitor. This BASIC may give the beginner a feel for high level language programming but anyone who has used systems such as PETs or Apples will find it very restrictive. The single keystroke programming facility is certainly not my cup-of-tea. I'm too used to typing the whole thing out, but it would be of benefit to the beginner.

## Manual Intercourse

The "Course in BASIC Programming" that is supplied with the system is a very poor substitute for books such as "Basic BASIC" and "Illuminating BASIC" but is adequate for finding your way round the ZX 80. The format needs to be considerably improved, odd and even chapter numbers are aimed at different people. There are a number of errors; some are corrected in an addendum, but several trap the unwary.



The explanation of many of the functions of the system is very poor indeed and in some cases can lead one rather up the garden path. The best function concealed within the system is the Editor, truly a marvellous system. We did wonder why they had made it so good. It must use up a fair proportion of the available space which, it could be argued, would be better used by providing more BASIC functions.

## The Ins And Outs

Tape interfaces come in many different disguises. The ZX 80 is no exception and offers an "around 300 Baud" audio cassette interface which works tolerably well. You can experience trouble if you leave both input and output jacks connected to the tape recorder but I gather a note to this effect is being included in the manual. The VDU is less praiseworthy, the aforementioned flicker being just one of its little quirks. The problems really start to occur when you find that the program crashes every time you fill the screen. The cause is that the VDU is acting as a serial output device and needs a buffer. When the buffer is full it stops everything and tells you — nasty!

We also encountered another interesting VDU quirk for which there appears to be little explanation. On some TVs you encounter you will find that white on black is unreadable but black on white is, or vice versa. We also discovered, again no explanation is offered, that the system would produce a double (ghost) image on some colour sets. The designer assured us that the modulator was not, as we had suspected, a cheaper version that could not handle the bandwidth so there must be something funny going on.

## Hardware Design

A certain number of design features of the ZX 80 are worthy of note. It is generally understood that an eight bit micro, with its sixteen bit address bus, can have up to



NewBear's New Brain — a professional, hand-held micro ..... coming soon.

64K of memory hung on it. The ZX 80 offers a maximum of 16K of RAM and a (possible) 16K of ROM, done by moving PC tracks around. What you may well ask has happened to the other 32K? Sorry chaps, but it is used for other things like decoding the keyboard, so the thoughts of giant, disc based systems fade rather rapidly. Whilst on the topic of memory it should be noted that the 3K Sinclair RAM boards are *not* capable of being "piggy backed", you'll have to wait for the 15K RAM plane. You cannot use the cheaper dynamic RAM either because the RFSH signal produced by the Z80 CPU is utilised by the video synchronisation circuitry and this means that instead of getting a mean refresh every 2 mS that the dynamic memory needs, it may have to wait 20 mS, which is cutting things very fine. Under normal operating conditions this might not cause problems, but if the temperature of the RAM chips rises then they may well start to lose data.

The final oddity in the design of the hardware is the lack of a crystal controlled clock. It uses a ceramic filter instead. This is not to be recommended as it simply isn't accurate enough. The ZX 80 runs at 3.25 MHz, which is a multiple of the TV linebase frequency. The filter appears to be used to save a couple of divider chips and possibly pass this saving on in a reduced price, but it should be remembered that the earlier Sinclair computer, the now defunct Mk 14, was equipped with a crystal and cost about half the price.

## Expansion Capabilities

Apart from the memory expansion problems mentioned earlier, there is another, more subtle, problem that will occur when the user wishes to attach that most popular of peripherals, the printer. This problem arises because the ZX 80 does not use the normal ASCII character code set but its own. This means that to interface to a printer, a task of more than average complexity, the user will have to write a look-up table routine to convert between the two code sets.

However, the first thing that any expansion minded user must do is to put buffers onto all the bus lines. Space and pricing have omitted these and, although it is hoped that Sinclair will produce a buffer board, it does not appear to rank highly on their list.

Mention has been made of certain possible add-ons like Prestel and it is worth making the point that, because the ZX 80 uses a serial output screen format rather than a memory mapped type, it will be almost im-

possible to connect exotic systems such as Viewdata and Teletext. In the same way it is impossible to use the ZX 80 for playing interactive video games of the Space Invaders type.

## Software

At the moment there is not much commercial software available. The Users Group is probably the best source after magazines like Computing Today, but there are very strong indications that a professional software house will be supplying the user with a range of programs. For users who are looking for software now the following points should be borne in mind;

- a) the BASIC is Integer only,
- b) the cassette format is not "standard",
- c) you can't use interactive graphics, PEEK and POKE,
- d) The BASIC is not compatible with Microsoft types, in *either* direction.

## Conclusion

Sinclair and his Science of Cambridge team have produced what is probably the forerunner of the 1980 generation of personal computers and in common with most "firsts" it has a number of faults that its competitors will rapidly seek to iron out of their, yet to be released, products. The currently poised opposition include Acorn with their Atom, NewBear with the New Brain and (allegedly) Sharp with a similar type of system. The competition is going to be fierce and as yet Sinclair is the only runner in the race.

As regards the system we feel that it would probably make a starting point for the complete beginner, but for anyone experienced in microcomputing it may not have sufficient facilities compared with other low cost systems like Acorn and Tangerine. The lack of proper machine code access may put the system down in some people's opinions but as a first time system for the complete beginner, be they in the classroom or at home, it is currently the cheapest and that may well be the overriding factor.

## New from NewBear

Newbury, the terminal company who opened the NewBear computing shops to gain access to the world of microcomputing, have launched a professional hand-held micro for anyone from businessmen to the hobbyist. Called New Brain it contains a 16K Compiling BASIC, 2K RAM which is expandable to 4K in static or 16K in dynamic, a full size QWERTY keyboard, single line display with direct video output and enough I/O to make most systems look a bit undernourished. The whole thing is battery powered, with charger capability and uses a COPS chip from National Semi to look after the keyboard and display (which powers down after 60 seconds of inaction). The main computing is provided by a Z80 which only powers up when you actually RUN a program. The machines we were shown at the Press launch were unfortunately only half built and they are not expected to be available until at least September, so we can't get our hands on one yet. When we do we'll tell you what it does but expect the prices to be from £150 (video only) to £250 (full system). One feature that I will tempt you with is the fact that they have committed themselves to Prestel — it has a button on the front marked Viewdata.

**ETI**

**NEW** **CT4000 CLOCK/APPLIANCE TIMER KIT**

The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay Kit (MK2). The kit includes a PCB, keyswitches, IC, 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.

Size: 10x12x4.5cms  
Colour: Black

**ONLY £25.25**



**D.V.M. THERMOMETER KIT**

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3Ma 9V supply (PP3 battery).

**£20.75**

**TOUCH CONTROL LIGHTING KITS**

These KITS replace light switches and fit up to 300 Watts of lighting. No rewiring, fit plaster depth boxes, insulated touchplates. Easy to follow instructions.

**TD300K TOUCHDIMMER**. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamps. Neon lamp helps find the switch in the dark. **£6.50**

**TDE/K Extension Kit** for TD300K for 2-way switching, etc. **£1.50**

**TSD300K TOUCHSWITCH & DIMMER**. Single touchplate, small knob controls brightness. **£5.50**

**TS300K TIME DELAY TOUCHSWITCH**. Turns off after preset delay (2 secs. to 3½ mins.). **£4.30**

**LD300K Conventional Lightdimmer** **£2.90**

**MINI KITS**

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

**MK1 TEMPERATURE CONTROLLER / THERMOSTAT**. Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. **1KW £3.50**

**INTEGRATED CIRCUITS**

555 Timer **21p**  
741 Op. Amp. **19p**  
AY-5-1224 Clock **£2.60**  
AY-3-1270 Clock/Timer **£4.50**  
AY-3-1270 Thermometer **£8.20**  
ICL7106 DVM (LCD drive) **£7.00**  
LM377 Dual 2 W Amp **£1.45**  
LM379S Dual 6W Amp **£3.50**  
LM380 2W Audio Amp **80p**  
LM382 Dual/low noise Preamp **£1.00**  
LM386 250mW low voltage Amp **75p**  
LM1830 Fluid Level Detector **£1.50**  
LM2907 f-v Converter (8 pin) **£1.40**  
LM2917 f-v Converter (14 pin) **£1.60**  
LM3909 LED Flasher / Oscillator **55p**  
LM3911 Thermometer **£2.10**  
LM3914 Dot/Bar Driver **£2.10**  
MM74C911 4 digit display controller **£6.50**  
MM74C915 7 segment-BCD converter **96p**  
MM74C926 4 digit counter with 7 seg o/p **£4.50**  
S5688 Touchdimmer **£2.50**  
S9263 Touchswitch 16-way **£4.85**

**MK2 SOLID STATE RELAY**. Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

**MK3 BAR/DOT DISPLAY**. Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

**MK4 PROPORTIONAL TEMPERATURE CONTROLLER**. Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. **1.5KW £5.25** **3KW £5.55**

**MK5 MAINS TIMER**. Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. **£4.50**

**INTEGRATED CIRCUITS**

SN76477 Complex Sound Generator **£2.52**  
TB800 5W Audio Amp **58p**  
TB810AS 7W Audio Amp **85p**  
TDA1024 Zero Voltage Switch **£1.20**  
TDA2020 20W Audio Amp **£2.85**  
ZN1034E Timer **£1.80**

All ICs supplied with data sheets  
Data Sheets only 5p each device

**DO MAGAZINE REMOTE CONTROL PROJECTS MAKE YOU SEE INFRA RED?**

How many times have you considered building a remote control project but were put off by the dozens of ICs, special coils, lenses and other hard to get components, not to mention the need for a well equipped lab, to set the unit up? T.K. ELECTRONICS have changed all that. Three ICs can build a sophisticated system that requires only a capacitor and resistor to set the clock frequency (which can drift up to 20% without affecting performance). Control radios, Hi-Fi (including bass, treble and volume), lighting, toys, garage doors, etc. Still not convinced? Then look at the prices!

**ML922 10-channel Receiver and 3 Analogue Outputs** **£4.20**  
**ML926 16-channel Receiver (4 Momentary binary outputs)** **£1.40**  
**ML928 16-channel Receiver (4 Latched binary outputs)** **£1.40**

Data sheets (per device) **5p**

These ICs can also be used with ultrasonic and radio links, depending on range, cost and speed of operation. For more details, why not give us a ring — we will be pleased to advise you.

**LD271 IR Emitting Diode** **36p**  
**SFH205 Photodiode Detector** **95p**  
**SL480 IC Pulse Amplifier** **£1.40**  
**SL490 Keyboard Controlled Encoder/Transmitter** **£2.40**

**NEW** If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel ON/OFF infra red transmitter and receiver. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a preamplifier, bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. The minimum range is 20 feet.

**ONLY £12.00 (Order as RC500K)**

**INTEGRATED CIRCUITS**

SN76477 Complex Sound Generator **£2.52**  
TB800 5W Audio Amp **58p**  
TB810AS 7W Audio Amp **85p**  
TDA1024 Zero Voltage Switch **£1.20**  
TDA2020 20W Audio Amp **£2.85**  
ZN1034E Timer **£1.80**

All ICs supplied with data sheets  
Data Sheets only 5p each device

**TRIACS**

400V Plastic Case (Texas)

3A	49p	16A	90p
8A	58p	20A	165p
12A	85p	25A	190p
6A with trigger			80p
8A isolated tab			65p
Diac			18p

**SPECIAL OFFERS**

orders must be received by 30.6.80

10x8pin sockets	65p	10x555	£1.80
10x14pin sockets	£1.00	10x741	£1.60
10x16pin sockets	£1.15	25x20" Red Leds	£1.50
10x18pin sockets	£1.40	ORP12	50p
100xSoldercon pins	40p	2N3055	40p


**ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER — CALLERS WELCOME BY APPOINTMENT**

**TK Electronics**  
(ETI), 106 STUDLEY GRANGE ROAD  
LONDON W7 2LX. TEL. 01-579 9794



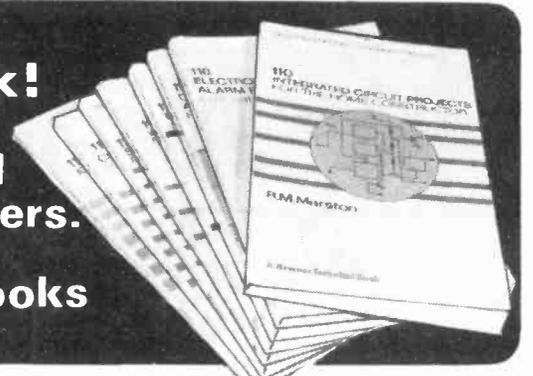**110 projects in every book!**

The '110' books have been acclaimed by enthusiasts, students and engineers. Each contains 110 different circuit applications. Use them as project books or as source books for circuit ideas.



- |                                                                                                                       |                                                                                                                  |
|-----------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------|
| 110 CMOS Digital IC Projects for the Home Constructor<br>R. M. MARSTON 0 408 00216 6 <b>£3.95</b>                     | 110 Operational Amplifier Projects for the Home Constructor<br>R. M. MARSTON 0 408 00153 4 <b>£3.95</b>          |
| 110 Electronic Alarm Projects for the Home Constructor<br>R. M. MARSTON 0 408 00269 7 <b>£3.95</b>                    | 110 Semiconductor Projects for the Home Constructor — Second Edition<br>R. M. MARSTON 0 408 00322 7 <b>£3.95</b> |
| 110 IC Timer Projects for the Home Constructor<br>JULES H. GILDER 0 408 00480 0 <b>£3.95</b>                          | 110 Thyristor Projects using SCRs and Triacs<br>R. M. MARSTON 0 408 00074 5 <b>£3.95</b>                         |
| 110 Integrated Circuit Projects for the Home Constructor — Second Edition<br>R. M. MARSTON 0 408 00309 X <b>£3.95</b> | 110 Waveform Generator Projects for the Home Constructor<br>R. M. MARSTON 0 408 00353 7 <b>£3.95</b>             |

Available from your bookshop or in case of difficulty direct from the publishers.

**Newnes Technical Books**  
Borough Green, Sevenoaks, Kent TN15 8PH

# Happy Memories

4116 200ns	£3.95	4116 150ns	£5.50
2114 200ns	£3.95	2114 450ns	£3.45
2708 450ns	£4.95	2716 5 volt	£13.50

**MEMOREX** mini discs soft sectored  
**£19.95** per ten

## SALE

We're moving shortly to new premises and don't want to carry much


Bargains for all

All prices include VAT, 30p postage on orders below £10

Access and Barclaycard

All orders to:

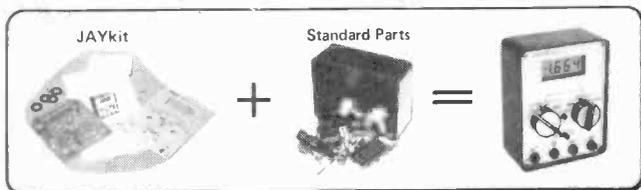**Dept. ETI**  
**19 Bevois Valley Road**  
**Southampton, Hants. SO2 0JP**  
**Telephone (0703) 39267**



DM-2



**DIGITAL MULTIMETER**

- ★ DC Volts . . . . . 1mV to 1000V
- AC Volts . . . . . 1V to 500V
- DC Current . . . . . 0.1mA to 0.2A
- Resistance . . . . . 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



**FUNCTION GENERATOR**

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments  
21 Gladeside, Bar Hill,  
Cambridge CB3 8DY

Tel: (0954) 80285

Please send:

- DM-2 @ £5.45  
 FG-1a @ £4.95  
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.


**JAYkits**

Name \_\_\_\_\_

Address \_\_\_\_\_

# ELECTROVALUE

SUPPLIERS OF COMPONENTS THAT COUNT

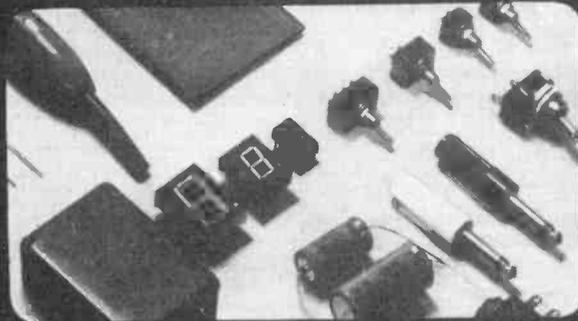

<b>SIEMENS</b> SEMI-CONDUCTOR CAPACITORS FERRITES	<b>NASCOM</b> MICRO COMPUTERS AND ANCILLARIES	<b>VERO</b> BOARDS CASES & KITS
<b>ISKRA</b> RESISTORS	<b>RADIOHM</b> POTENTIOMETERS	<b>BREADBOARDS</b> SOLDER TOOLS
	<b>OPTO-ELECTRONICS</b>	<b>SWITCHES</b> <b>CATALOGUE 10</b>

## OUR MINI-SELECTION POINTS THE WAY!

### EXAMPLE ONE - SOLDERING IRONS

Aryx 50	£12.08 net	Antex x 25	£4.83 net
Isotip	£25.90 net	Desolder tool SR3A	£7.48 net
Antex C	£4.83 net	500 gm reel solder	£6.61 net

### EXAMPLE TWO - PRINTED CIRCUIT MATERIALS

PCB's 300 x 150 mm		Etch Resist Pen	£1.14
SRBP S/S £1.38	D/S £1.73	Breadboards	
F/Glass S/S £1.96	D/S £2.13	Bimboard 12£9.23	
Positive resist 75cc	£1.67	Eurobreadboard	£6.56 net
Ferric Chloride 500 g	£3.45	T-DeC	£5.18

### EXAMPLE THREE - SWITCHES

Chrome toggle		13A time switch adaptors	
Std. SPDT 65p	DPDT 89p	Smiths TS100	£14.43 net
Min. SPDT 66p	DPDT 92p	Wavechange, Lorlin, 1P12W, 2P6W, 3P4W, 4P3W	46p each

### EXAMPLE FOUR - CAPACITORS BY SIEMENS

**Polyester 7.5mm PCM**  
1, 1.5, 2.2, 3.3, 4.7µF, 10, 15, 22, 33, 42µF 8p each, .1µ 12p, .15µ 15p, .22µ 18p, 33µ 21p, 47µ 27p, 68µ 34p, 10mm PCM 1µ 37p.  
**Electrolytic, axial, (µ F/V)**  
1/40 24p, 1/100 15p, 2.2/25 24p, 2.2/63 15p, 4.7/16 24p, 4.7/40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 19p, 47/10 18p, 47/25 18p, 47/40 16p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 55p.  
Also full supporting ranges of other ceramic, plastic and electrolytic caps.

### EXAMPLE FIVE - POTENTIOMETERS BY RADIOHM

Single gang lin or log	34p	(Twin types stereo matched)	
Twin gang lin or log	93p	Slider knobs	10p each
Mono slider lin or log	83p	Presets lin, horiz, or vert	10p
Twin slider lin or log	136p		

### EXAMPLE SIX - RESISTORS

1/4W 2.3p 1W 6p  
Wirewound from 21p

### AND AS FOR SEMI CONDUCTORS . . .

1N914	6p	40673	99p	MU481	£1.70	T1P41A	69p
1N4007	9p	AC128	36p	MJ481	£1.88	T1P41C	74p
1N4148	5p	AC176	67p	MJ2955	97p	T1P42A	89p
1N5402	19p	AD136	£4.25	MJE2955	£1.13	T1P42C	74p
2N1599	£1.01	AD149	£1.01	MJE3055	£1.00	T1P2955	69p
2N2369A	24p	AD161	40p	MPSA12	42p	T1P3055	69p
2N3055	81p	AD162	52p	MPSA63	44p	T1S43	40p
2N3702-11	11p	AF127	43p	OA47	14p	W02	35p
2N4443	£1.78	AL102	£1.84	OA90	8p	2T107.9	14p
2N4444	£2.28	BA379	29p	OA91	8p	2T300	14p
2N4991	98p	BB103	43p	OA202	16p	62T500	16p
2N5457-9	45p	BB104	70p	OC29	£1.23		
40HF40	£2.25	BB105	37p	OC36	£1.18		
40361	49p	C106D1	52p	T2800D	£1.20		
40362	49p	E1110	82p	T1P31A	52p		
40636	£1.69	E1210	97p	T1P32A	52p		

**INFORMATION** - To show everything we supply would take about seven pages of closely packed type in this journal - the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 - OUR 120 PAGE CATALOGUE FREE FOR THE ASKING.

**PRICES AND V.A.T.** - All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

**POSTAGE** - For orders up to £5.75 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

**DISCOUNTS** - 5% allowed on non-net items if order value exceeds £11.50. 10% if order value exceeds £29. Quantity discount prices on most components.

**ELECTROVALUE LTD.** Dept. 55 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 264475.

Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945

# TECH TIPS

## Multi-Flash Trigger

R O'Rourke, Eastleigh

This circuit provides a cheap and safe system for parallel connection for electronic flashguns and prevents damage to shutter sync. contacts.

Electronic flashguns used for photography usually have a voltage of between +200 V and +400 V present at the trigger input connector.


The flash unit operates when the trigger is grounded (by the shutter sync. contacts) and a current pulse of between 1 and 3 amps, lasting about 10 to 30 microseconds is carried by the sync. contacts.

Direct connection of electronic flashguns in parallel can cause two major problems:

- (a) Different makes or powers of flashguns may have different operating voltages and may therefore be damaged by parallel connection.
- (b) Shutter contacts could be damaged or burned by the excess current of multiple gun operation.

This circuit overcomes these two problems as follows:

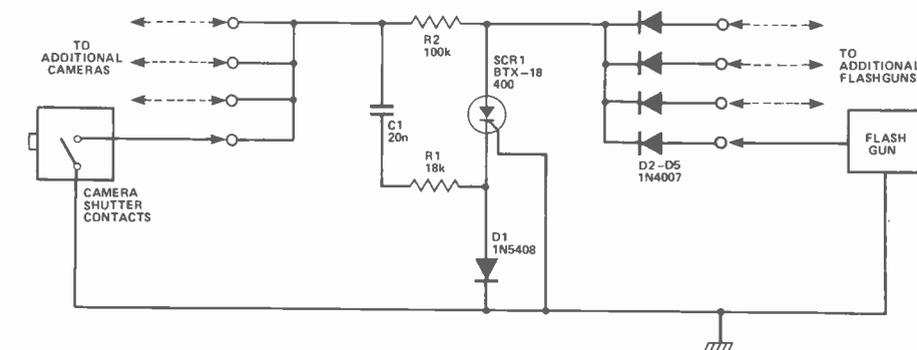- (a) Diodes D2 to D5 effectively isolate the hot side of each flashgun from the next and also prevent the high voltage appearing on the unused flashgun contacts.
- (b) The SCR trigger circuit operates as follows:



When one or more flashguns are connected to the unit, the cathodes of D2-D5 rise to a high positive value, say +200 V.

C1 is charged via R2, R1 and D1 in a time constant  $C1 \times (R1 + R2) = 0.02 \times 118 \text{ k} = 2.36 \text{ ms}$ .

SCR1 is non-conductive at this time as its cathode is slightly positive and its gate is grounded.

When the shutter contacts of a camera connected to the device are closed the R2 end of C1 is grounded and therefore the R1 end is driven negatively to -200 V. This enables a negative current pulse to be delivered to the cathode of SCR1 (D1 allows SCR cathode to go negative) of about 11 mA, for about 360  $\mu\text{s}$  duration, this


pulse turns on the SCR which then carries the trigger current of the flashguns.

When the flashguns fire the trigger voltage drops to zero and the SCR turns off. C1 will recharge as the voltage of the flashguns recover ready for the next flash.

As can be seen, the maximum current through the camera contacts is thus reduced even with a flashgun voltage of 400 V, to only 22 mA.

When using more than one flashgun in a direct lighting system, allowance should be made for the increased guide number:-
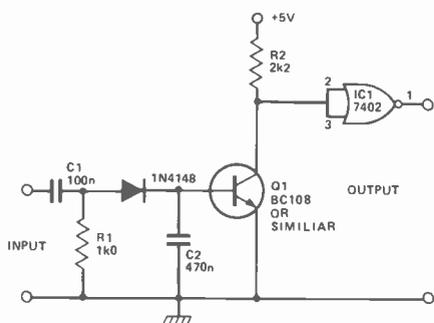
$$\text{Effective Guide Number} = \sqrt{a^2 + b^2 + c^2 \dots}$$



## Simple Cassette Interface

R Thomas, Port Talbot

The cassette interface on my NASCOM1 has never worked correctly and despite many frustrating fault finding sessions the only solution was to replace it. No originality is claimed for this circuit. Indeed anyone with a basic knowledge of electronics or radio will recognise part of it as an envelope detector or demodulator. No alteration of the cassette output of the NASCOM is required assuming it dumps properly.

Take the output of the 7402 to the serial input link LK3.

Component values are not that critical and by inserting another resistor and capacitor of the same value in front of C1 and R1 the response will be improved, although I did not find these necessary. The interface does require a fairly large input signal and the volume setting is rather precise but once set the interface should work perfectly. Although built for the NASCOM, the interface will work with any low speed cassette interface system that switches an audio frequency on or off.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

## VDU Shift Control


R J Cheason, Fareham

Most low cost VDU boards using the SFF96364 do not have the facility to adjust the monitor/TV picture left or right. This circuit was developed for a VDU board using the 'Triton' design but is suitable for any board using the same controller.

The SFF96364 outputs a pulse on Pin 10 enabling the picture - point oscillator. The counter/divider then outputs a pulse to the controller every character, stepping the character address. After 64 characters Pin 10 goes low.

The modified circuit uses the positive going edge from Pin 10 to trigger a monostable whose pulse length is set by RV1 and C1. When the monostable's output goes high it triggers a flip flop into the high state. After the current line has been output, the input from Pin 10 goes low clearing the flip flop and stopping the picture - point oscillator.

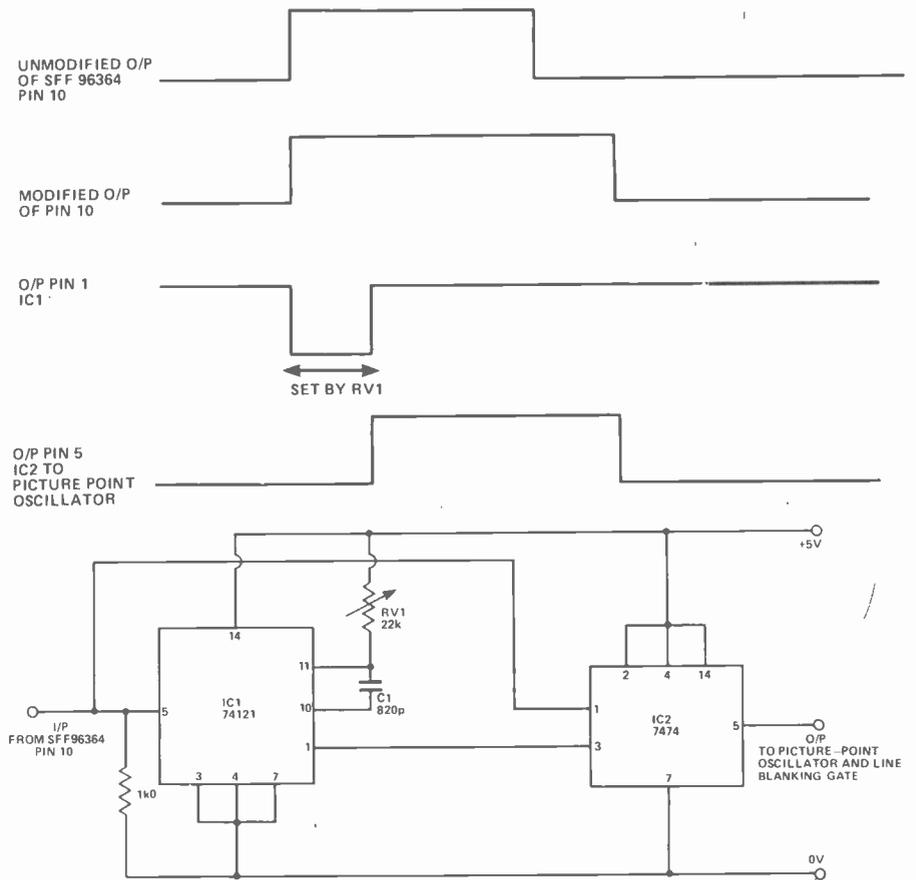In practice slight jittering was caused by interference on the supply lines, but it was found that a capacitor of about 100 uF across the supply close to IC1 cured this problem.




## Soft Limiter

J.P. Macaulay, Crawley

One of the fundamental differences between valve and transistor amplifiers is their behaviour when driven into clipping. The valve amps go into so-called soft clipping whilst their transistorised counterparts generate large quantities of harmonic distortion. The circuit shown simulates the soft clipping of valve amplifiers and is intended to be used between the power amplifier's input and the preamplifier's output.

R4 and R5, decoupled by C2 set a half supply reference for the non-inverting input of the op amp. Input signals are fed into the inverting input via the DC blocking capacitor and R1, the latter defining small signal gain and input impedance.

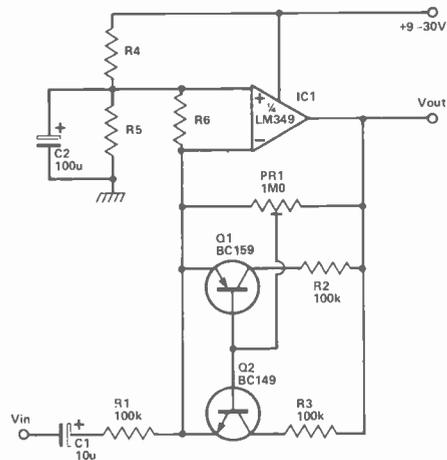
For small signals the amplifier's output is an exact unity gain copy of the input. As the signal level increases, however, the time will come when the voltage across the output and slider of PR1 will be sufficient to bias Q1 or Q2 on. When this occurs the feedback



increases due to the shunting effect of R2 and R3.

The net effect is that musical peaks above a certain threshold are reduced in amplitude to prevent the power amplifier going into hard clipping. As a result distortion is noticeably decreased, whilst the subjective loudness appears unaffected.

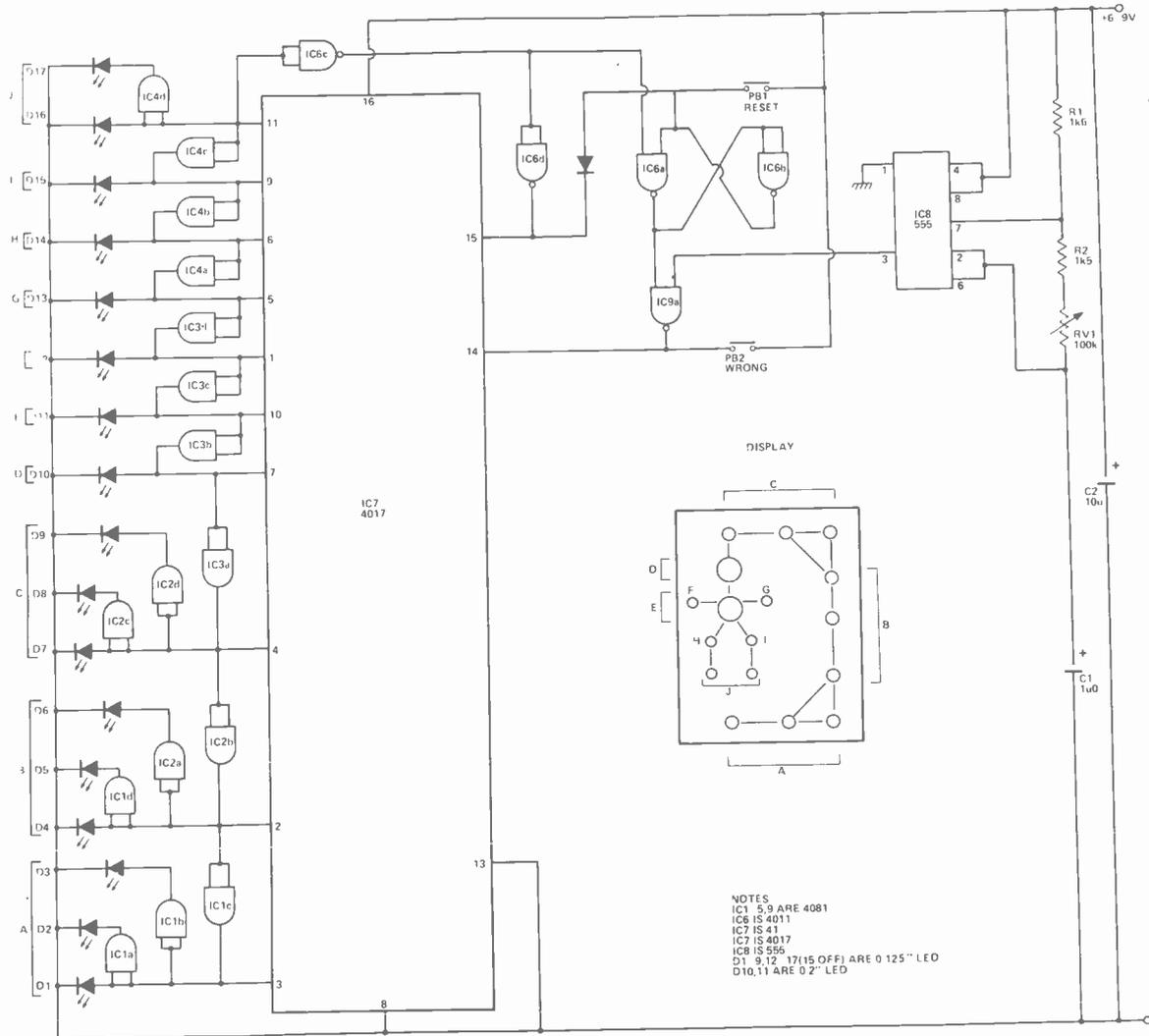The circuit is adjustable in operation between 130 mV and 10 V rms input sensitivity by means of PR1. To set the circuit up simply set the slider so that it is shorted to the output of the amp. Play some music at high volume through the system and adjust until the harshness just disappears. It's easier to do than describe.



## Electronic Hangman

G.N. Durant, Selby

The circuit diagram shows a design for an Electronic Hangman Game. The scoring display is made up of 0.125" and 0.2" LEDs, as shown. The controls consist of two one pole make push-buttons. The first button is pressed every time a letter is wrongly guessed. At the start of the game, the other button is pressed, to reset the display, blanking it. When a letter is wrongly guessed the 'wrong' button is pressed once, and the first part of the display, (A), is illuminated. Every time another wrong letter is guessed, the 'wrong' button is pushed, and the next part of the display is lit up. When the display is all lit up, and the victim is 'hung', the display automatically blanks.

Now this is where the clever bit comes in. To show that the victim has lost, the display is blanked, then the first part of the display lights itself, then the next part and then the one

after that. In fact, all the parts light up in sequence, until the last part lights, when the display blanks again, and the whole 'chasing' process starts again. This process repeats itself until the 'Reset' button is pressed, when the display blanks, ready for a new game to begin.

The circuit consists of eight ICs, one of them being a 4017B CMOS device. This device is a ten stage decade counter. Each output is fed directly to its own LED and, because some outputs require more than one LED and there is not enough current from the 4017 to drive more than one, the affected outputs are connected to a CMOS 'AND' gate which is in turn connected to a LED, so the required power is obtained from the power supply and not the outputs of the 4017. The input of the 4017 is triggered by a push button connected to the positive supply rail, so when it is pushed (Wrong button) the IC is triggered and the next part of the LED display is illuminated. The 'lower' LEDs are kept lit by another

AND gate, connected as a chain linking each output of the 4017, so their outputs will go high, when a 'higher' LED is lit.

When the top LED is lit, another AND gate (gate 3, IC 6) goes low, locking a latching flip-flop formed by gates 1 and 2 of IC6, a CMOS NAND gate. This latch allows the output of an astable multivibrator to go to the trigger input of the 4017 and to start the automatic sequencing. The reset button makes the input of one of the gates go high, unlatching the flip flop and resetting the display. The small preset varies the clock rate over a wide range, speeding or slowing the sequencing.


If desired, a 'Display PCB' can be designed to ease the LED wiring. When the circuit is known to be functioning correctly, lines can be painted onto the display to join up the LEDs, and to make them appear as a 'picture'.

When all the LEDs are illuminated, the circuit will take a great deal of current, so a mains power supply is advised.

## 24 TUNE DOOR CHIMES
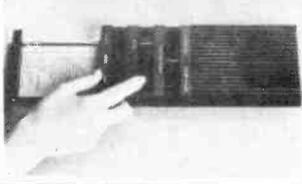
### DOOR TUNES £17.13 + VAT


Waddington's Videomaster announce a doorbell that doesn't go Brrringing, Ding-Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES
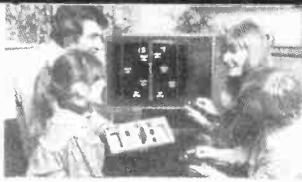
### PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



### EXTRA CARTRIDGES:

**ROAD RACE** - £8.87 + VAT.  
Grand Prix motor racing with gear changes, crash noises  
**SUPER WIPEOUT** - £9.17 + VAT.  
10 different games of blasting obstacles off the screen.  
**STUNT RIDER** - £12.16 + VAT.  
Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.  
**NON-PROGRAMMABLE TV GAMES**

6 Game - COLOURSCORE II - £13.50 + VAT.  
10 Game COLOUR SPORTSWORLD £22.50 + VAT.

## CHESS COMPUTERS

### STAR CHESS - £65.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18v mains adaptor, full instructions and twelve months guarantee.



### CHESS CHALLENGER - £85.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.



### ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

### OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:


**CHESS CHAMPION** - 6 LEVELS £47.39 + VAT.  
**CHESS CHALLENGER** - 10 LEVELS - £138.70 + VAT.  
**BORIS** - MULTI-LEVEL TALKING DISPLAY £163.04 + VAT.

## DRAUGHTS COMPUTERS

### CHECKER CHALLENGER 2 LEVELS £43.00 + VAT 4 LEVELS £78.00 + VAT

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.
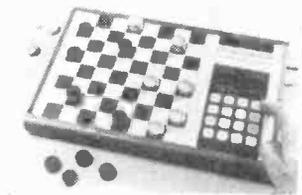
### PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



## FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.  
Callers welcome at our shop in Welling - demonstrations daily - open from Sat 5-3.0pm, Mon-Sat 10am-1pm Wed.  
To order by telephone please quote your name, address and Access/Barclaycard number.  
Postage and Packing FREE.

**AJD DIRECT SUPPLIES LIMITED, Dept. E77 102 Bellegrove Road,  
Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)**

## AUDIO AND TEST EQUIPMENT CENTRE

Telephone your order with Access and Barclaycards or send cheque with order.



RETAIL  
MAIL ORDER  
EXPORT  
ALL PRICES  
INCLUDE VAT



LONDON'S TEST GEAR CENTRE

OPEN 6 DAYS A WEEK 9 am-6 pm

HAMEG • TRIO • LEADER • SINCLAIR • LASCAR • LEVELL • CSC

Test Equipment now in stock - send large s.a.e.

SCOPES - (UK P/P £2.50 ea.)

HM 307-3 10MHz single beam with Component Tester 170.00  
HM 312-8 20MHz dual trace 287.50  
HM 412-4 20MHz sweep delay dual trace 402.50  
SINCLAIR 10MHz Miniscope. P/S 4.00, Nicads 7.95, Case 8.80 152.50  
PROBES x1/x10 12.95, x10 10.50, x1 8.50, x100 16.95

### FREQUENCY COUNTERS

OPTO 7010 9 digit, 600MHz Portable. 0.1Hz Resolution with NICADS 139.95  
MAX 60 50MHz 6 digit pocket counter 81.00  
MAX 100 100MHz 8 digit portable counter 88.75  
MAX 550 550MHz 6 digit pocket counter 106.00  
500 MHz Prescaler for max 50 or max 100 40.00  
PFM200 Sinclair 200MHz Pocket Counter 8 digit 54.50  
OPTIONAL P/S 4.00, Connector Pack. PFM200 69.95  
c721BR, 10MHz 8 Digit Panel Mounting 55.80  
c721BRP, 150MHz version 68.25

### DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit LED 56.50  
PDM35 Sinclair Pocket 3 1/2 digit LED 36.50  
DM350 Sinclair 3 1/2 digit with 10 amp range 78.50  
DM450 Sinclair 4 1/2 digit 107.95  
M1200 Bench Portable 3 1/2 digit LED, Resolution 1µA, 0.1mv/0.01ohm SPECIAL PRICE NOW £59.50  
LMM200 Lascar 3 1/2 digit 2A LCD Bench 0.1% 86.85  
LM2001 Lascar 3 1/2 digit 2A LCD Hand 0.1% 51.70  
LM200 Lascar 3 1/2 digit 2A LCD Economy 0.5% 43.40  
ME502 3 1/2 digit 10a LED plus transistor tester £43.95

### MULTI-METERS - GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges (TM3 AC volts only), some with AC current, etc.\*

TM11 incredible 120 Range Electronic Multi-meter\* 172.50  
TM3B AC Micro voltmeter 3MHz > 4 Megohm (large scale) 166.75  
TM3A AC Micro voltmeter 3MHz > 4 Megohm 149.80  
360TR 100k/volt\*\* 26 Range (plus transistor checker). Large scale 34.95  
7080 20k/volt 26 Range Large scale 26.95  
7081 50k/volt 36 Range Multi-meter, range doubler 19.95  
NH85 2kv 10 Range Multi-meter 6.95  
NH86 20k/volt 22 Range Popular Multi-meter 10.95  
LT101 1k/volt 12 Range Pocket Multi-meter 5.95  
YN380TR 20k/volt 19 Range Multi-meter plus transistor check 24.95  
AT205 50k/volt 21 Range Multi-meter 7.95  
ATI 2k/volt 12 Range Multi-meter Deluxe 22.95  
TMK500 30/volt 23 Range Multi-meter, with case 16.95  
AT1020 20/volt 19 Range Multi-meter with transistor tester Deluxe 28.50  
AT2050 50k/volt 21 Range Multi-meter Deluxe 29.95  
AT210 100k/volt\*\*

\*AVO 8s and a large range of replacement tests leads in stock

### GENERAL EQUIPMENT

SE250 Signal Injector 4.95  
TE7 Signal Tracer AF/RF 9.95  
SWR60 SWR/Power Meter 13.95  
DRS10 36 Value Res. Box 3.95  
RP124 0/24v 0/1 amp P/S Stabilised 42.00  
RP324 3 amp version 54.00  
RP230M 0/30v 0/1 amp P/S Twin Meters 85.00  
TR1000 Transistor checker in/out circuit 11.95  
MOD63 Signal injector 8.65  
C3022 Transistor/ Diode Checker 19.95  
3101 Clamp Meter 0/1 Kohm, 0/150/300/600 AC volts 0/300 amp 32.95  
SWR40/9 SWR & FS Meter 10.50  
SWR10 SWR Meter 10.95  
MS319 2x100 Watt Audio Watt Meter 13.95  
500V Megohmmeter 500 Megohms 51.00  
2 1/2 amp Variable transformer 21.95

### GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges 82.00  
TG152Dm (with meter) 113.85  
TG200 Series RC Oscillators Sine/Square output. 1Hz-1MHz 12 Ranges  
TG200D 124.20  
TG200Dm (with meter) 149.50  
TG200Dmp (meter & fine control) 155.25  
4001 Digital Pulse Generator 0.5Hz-5MHz 105.00  
2001 Function Generator-Sine/Square/Triangle/TTL 86.00  
SG2030 (RF) 6 bands 250KHz-300MHz 49.95  
6052 PAL VHF/UHF Colour Bar Generator 250.00  
AG781 (Audio) sine 19Hz-220Hz square 19Hz-10kHz 61.00  
ARF300 (RF-Audio) 18Hz-200MHz 78.50

### PROTO BOARD IN STOCK

KITS PR 6.20, PR 100 1.80.  
SEPARATES EXP300 5.95, EXP600 6.50, EXP350 3.45, EXP650 3.95

### LOGIC PROBES AND MONITORS

LT2000 Economy Probe 10MHz 8.95  
LM1 Monitor circuit powered 33.00  
LP1 Probe 10MHz 35.50  
LP2 1.5MHz 20.50  
16 Pin IC test clip 1.95

### PIEZO HORN TWEETERS

Up to 100 watts each. No x-over req'd. Only 4.95 each.  
Flared Horns 6.50  
Midrange Flared Horns 9.50  
(UK Post Free)

### DRILLS AND DRILL KITS


9 to 12 volt Operated. 1/8" max.  
SMALL DRILL with collets 6.85  
MEDIUM DRILL with 3 collets 9.90  
SMALL DRILL with 20 drills/tools 13.88  
MEDIUM DRILL with 20 drills/tools 18.95  
MAINS Eliminator 9.95  
VARIABLE Speed 13.95  
12 volt 1/4" Heavy Duty Drill 12.50  
MAINS DRILL with tool set 19.95

### TV SOUND

High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. £8.50 (UK P&P 50p)  
PRICE INCREASE AS FROM 1/6/80

SPECIAL BULK PURCHASE  
SEC 10x10 watt  
Tuner/Amplifier  
MW/LW/SW/Stereo FM. Supplied as two easy to connect units.  
£21.95 P&P £1.50

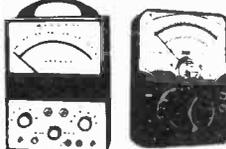IN STOCK NOW  
Large range of speakers and kits, public address equipment, microphones, mixers, security systems, intercomms, ham equipment. See catalogue



TM11 TMK500

CALL IN AND SEE FOR YOURSELF

PRICES CORRECT AT 1/6/80

## AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN  
01-724 3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W 1

FREE CATALOGUE

SEND STAMPED (17½p UK) ADDRESSED ENVELOPE (MIN. 9½ x 6½) FOR YOUR COPY NOW

# Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately twelve issues and is attractively bound and blocked with the ELECTRONICS TODAY INTERNATIONAL logo.

Price U.K. £3.95 including postage, packing and V.A.T., overseas orders add 30p. Why not place your order now and send the completed coupon with remittance to:-

EASIBIND LTD., 4 UXBRIDGE STREET, LONDON W8 7SZ. Tel: 01-727 0686

Please allow 3/4 weeks for fulfillment of order.

**it's easy with EASIBIND**

Easibind Ltd, 4 Uxbridge St, London, W8 7SZ.

Nat. Giro No. 5157552.

## Order Form

ELECTRONICS TODAY INTERNATIONAL

I enclose p.o./cheque value .....

for ..... binders

Years required .....

BLOCK LETTERS PLEASE

Name .....

Address .....

Date .....

Registration No. 307469



## QUANTITY PRICES — SAVE — SAVE — IMMEDIATE DELIVERY (incl. VAT)

### NEW STOCKS BELOW MANUFACTURERS' PRICES. Postage & packing add 50p per order

**SN74141N IC** 50p ea. **MULLARD BCD Decimal Decoder-Driver** 10 for 44p ea. 100 for 40p ea. 1,000 for 35p ea.  
**DISPLAYS** by Hewlett-Packard. Seven segment DL707 (5082-7750) 95p. Common anode half inch red display brand new in maker's cartons 6 for £5. 50 for 70p ea.  
**TV SOUND.** High quality sound through your hi-fi. Simply plug into your aerial socket. £8.50, as reviewed Popular Hi-Fi.  
**BURROUGHS 8 DIGIT** Panaplex calculator display 7 segment .025" digits. Neon type with red bezel socket and date. £1.95 ea. 10 for £17.  
**HONEYWELL PROXIMITY DETECTOR** integral amplifier 8V DC £3.50 ea. 10 for £30.  
**MULLARD T8A800** IC audio amplifier 95p ea. 10 for £8. 100 for £70.  
**RCA CA3088** FM IF £1.50, 10 for £12.  
**RCA CA3090A** FM decoder £2.50, 10 for £20, 100 for £175.  
**BU205 TEXAS**, £1.50 ea. 10 for £12, 100 for £100 per 1,000 85p ea.  
**TEXAS 10 WATT I.C. AMPLIFIER** SN76018 5-pin package. £1.25  
**BU208 T03 Texas TV power transistors** £1.75 ea. 10 for £15, 100 for £120, 1,000 for £1 ea.  
**MC1310P-SN76115N** FM stereo decoder £1.20 ea. 10 for £1 ea. 100 for 85p ea.  
**MULLARD AD161-AD162** Matched pairs. Pair 80p. 10 pairs £8. 100 pairs £50.  
**Cartons of 600 pairs £250 EX STOCK**  
**RADIATION DETECTORS** Quartz Fibre Dosimeters. Pen type with clip with lens and scale. Current list price £25 Q-5R in new condition tested set ready for use only £5.95.  
**TV TUNERS** by Mullard UHF 38 mcs size 3 1/4 x 2 1/4 x 1 1/4 £2.50 ea. 10 for £20. 100 for £175. 500 for £750. 1,000 for £1,250.  
**MULLARD TUNER MODULES** with data LP1171 combined AM/FM IF strip £3.50. LP 1179 FM front end with AM tuning gang. used with LP1171 £3.50. LP1171 and 79 pair £5.75. 10 pairs for £50.  
**CA3085 RCA POSITIVE VARIABLE REG.** 5 volt 100m amp variable. 18-24V 55p ea. 10 for £5. 100 for £35.  
**MULLARD LP1157 AM tuner modules** with circuit £2.50 ea. 10 for £20, 100 for £175.  
**LUSTRAPHONE RIBBON MIKE** £1.50, + pre amp on chassis 3 x 2 x 1 in. 10 for £12.50.  
**TAA661B** (14 pin DIL) IC TV sound and FM amplifier-detector by ATES on p. circuit board with other parts. Complete with data & connections 60p. 10 for £5. 100 for 40p ea.  
**DRYFIT RECHARGEABLE BATTERY.** 6 volt 4.5 amp/h. Size 6" x 3 1/2" x 1 1/2" at half price. Brand new £7.50, post 50p.

### MARRIOTT TAPE HEADS Quarter track

Type	Each	Per 10
XRPS 18R/Replay	£3.00	£25.00
XRPS36R/Replay	£4.00	£35.00
RSP63/track	£2.25	£20.00
XES11 Erase	£1.25	£11.00

### MAINS TRANSFORMERS all 200/250V IN

Type	Current	Size	Price
12V	100m/a	1 1/2 x 1 1/2 x 1 1/2	£0.95
12V	100m/a	1 1/4 x 1 1/4 x 1 1/4	£1.35
6-0-6V	300m/a	a 2 x 2 x 2	£1.50
12V	2 amps	3 x 2 1/2 x 2 1/2	£2.95

**STEREO CASSETTE TAPE HEAD.** High quality replacement for most machines record/replay with mounting bracket £2.95.

**DYNAMIC MICROPHONE.** Low imp Foster insert £1.45, 10 for £11, 100 for £100.

**TWO GANG MINIATURE VARICAP TUNER** 500pf with tuning knob, size 3 x 1 1/2 x 1 1/2 in. £1.25 ea. 10 for £10. 100 for £85.

**ATES U14552 AUDIO IC AMPLIFIER 14 PIN** DIL 300m watts 55p ea. 10 for £4.50, 100 for £35, 1,000 for 30p ea.

**GENERAL ELECTRIC 2 + 2 watt IC stereo audio** chips with circuit & data £1.95 ea.

**RCA CD4029AE** 16 pin DIL presatgate up down counter 85p each. 25 for £15, 100 for £50.

**ATES U14552 AUDIO IC AMPLIFIER 14 PIN** DIL 300m watts 55p ea. 10 for £4.50, 100 for £35, 1,000 for 30p ea.

**GENERAL ELECTRIC 2 + 2 watt IC stereo audio** chips with circuit & data £1.95 ea.

**RCA CD4029AE** 16 pin DIL presatgate up down counter 85p each. 25 for £15, 100 for £50.

**ATES U14552 AUDIO IC AMPLIFIER 14 PIN** DIL 300m watts 55p ea. 10 for £4.50, 100 for £35, 1,000 for 30p ea.

**GENERAL ELECTRIC 2 + 2 watt IC stereo audio** chips with circuit & data £1.95 ea.

**RCA CD4029AE** 16 pin DIL presatgate up down counter 85p each. 25 for £15, 100 for £50.

**ATES U14552 AUDIO IC AMPLIFIER 14 PIN** DIL 300m watts 55p ea. 10 for £4.50, 100 for £35, 1,000 for 30p ea.

**GENERAL ELECTRIC 2 + 2 watt IC stereo audio** chips with circuit & data £1.95 ea.

**RCA CD4029AE** 16 pin DIL presatgate up down counter 85p each. 25 for £15, 100 for £50.

# SUBSCRIPTIONS

This year we present a new twelve-part, non-fiction series — ETI 1980. . . . . available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £10.00 we'll send you twelve issues of ETI PLUS A free copy of ETI 1999, a chronicle of future times including the first report of World War III. You've never seen anything like it before.

To claim your FREE ETI 1999 (and a years' supply of ETI, of course) send your PO or cheque direct to

ETI Subscriptions  
 MAP Publications  
 PO Box 35  
 Bridge Street  
 Hemel Hempstead  
 Herts.





**Freepost  
Birmingham  
B19 1BR  
021-233-2400**

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Miniature Low Value				Polyester Radial Leads				RESISTORS					
Electrolytic Axial Leads -10% to +50% Tol.				Polystyrene, Axial, ±1% Tol., >=63V DC Wkg. Ceramic Plate, Radial, Low K, 100V DC Wkg. Ceramic Plate, Radial, Med K, 100V DC Wkg. Ceramic Plate, Radial, High K, 83V DC Wkg.				Dipped Type, C280/352 Style Moulded Type, 10.2mm Pitch				Carbon Film, Fixed 0.25W, E24 Values, 10R-10M, 5% Tol. 2 each 0.5W, E12 Values, 10R-4M7, 10% Tol. 3 each					
µF	V d.c.	18	26	40	63	pF	424	832	150	180	270	470	820	360	360	Cap 352 Cap 380 + Value	Order Code
1.0						10			10	10	10	10	10	10	10	10	10
2.2						12			12	12	12	12	12	12	12	12	12
3.3						15			15	15	15	15	15	15	15	15	15
4.7						18			18	18	18	18	18	18	18	18	18
6.8						22			22	22	22	22	22	22	22	22	22
10						27			27	27	27	27	27	27	27	27	27
15						33			33	33	33	33	33	33	33	33	33
22						47			47	47	47	47	47	47	47	47	47
33						56			56	56	56	56	56	56	56	56	56
47						68			68	68	68	68	68	68	68	68	68
68						82			82	82	82	82	82	82	82	82	82
100						100			100	100	100	100	100	100	100	100	100
150						120			120	120	120	120	120	120	120	120	120
220						150			150	150	150	150	150	150	150	150	150
330						180			180	180	180	180	180	180	180	180	180
470						220			220	220	220	220	220	220	220	220	220
680						270			270	270	270	270	270	270	270	270	270
1000						330			330	330	330	330	330	330	330	330	330
1500						470			470	470	470	470	470	470	470	470	470
2200						680			680	680	680	680	680	680	680	680	680

P.C.B. Components: Date Pen: Blue Ink, Slow Drying 98 Pen 33PC

C-MOS (BUFFERED)				74LS				LINEAR				SEMICONDUCTORS											
HEF4002	22	HEF4044	105	HEF4512	316	74LS00	19	74LS03A	106	74LS174	141	74LS273	172	CA3046	84	IN914	5	2N3705	10	BC182L	12	BFX85	29
HEF4001	22	HEF4046	133	HEF4514	318	74LS01	19	74LS05	104	74LS175	119	74LS274	173	CA330E	77	IN4001	5	2N3773	297	BC184	12	BFY51	17
HEF4002	22	HEF4047	109	HEF4515	376	74LS02	19	74LS06	39	74LS181	305	74LS279	177	CA3130E	99	IN4002	5	2N3820	39	BC184L	12	BFY52	20
HEF4003	22	HEF4048	119	HEF4516	476	74LS03	19	74LS09	59	74LS190	317	74LS280	181	CA3140E	48	IN4003	5	2N3904	9	BC121L	12	BLK65	262
HEF4008	100	HEF4051	87	HEF4518	118	74LS04	27	74LS193	76	74LS192	319	74LS290	196	CA3199E	293	IN4007	9	2N3909	9	BC214	11	BRV39	50
HEF4011	22	HEF4052	90	HEF4519	87	74LS05	27	74LS199	82	74LS193	319	74LS291	196	LM339N	78	IN4008	5	2N3950	35	BC214L	12	BSX20	21
HEF4012	22	HEF4053	90	HEF4520	118	74LS06	27	74LS199	126	74LS194	321	74LS292	207	LM339N	78	IN4009	5	2N3959	35	BC247	13	CL850	2850
HEF4013	22	HEF4056	67	HEF4521	235	74LS10	19	74LS107	41	74LS195A	119	74LS293	207	LM339N	78	IN4010	5	2N4013	31	BC247L	13	CL850A	2850
HEF4014	105	HEF4057	475	HEF4522	235	74LS11	26	74LS109	45	74LS196	162	74LS294	207	LM339N	78	IN4011	5	2N4017	21	BC247L	13	CL850B	2850
HEF4015	100	HEF4058	475	HEF4523	150	74LS12	26	74LS112	45	74LS197	132	74LS295	207	LM339N	78	IN4012	5	2N4019	46	BC247L	13	CL850C	2850
HEF4016	57	HEF4059	22	HEF4524	138	74LS13	48	74LS113	45	74LS198	132	74LS296	207	LM339N	78	IN4013	5	2N4020	46	BC247L	13	CL850D	2850
HEF4017	100	HEF4060	22	HEF4525	138	74LS14	74	74LS114	45	74LS199	132	74LS297	207	LM339N	78	IN4014	5	2N4021	46	BC247L	13	CL850E	2850
HEF4018	100	HEF4061	22	HEF4526	138	74LS15	26	74LS125	53	74LS200	206	74LS298	207	LM339N	78	IN4015	5	2N4022	46	BC247L	13	CL850F	2850
HEF4019	58	HEF4072	23	HEF4527	98	74LS16	19	74LS126	53	74LS201	206	74LS299	207	LM339N	78	IN4016	5	2N4023	46	BC247L	13	CL850G	2850
HEF4020	112	HEF4073	23	HEF4528	98	74LS17	26	74LS132	78	74LS202	206	74LS300	206	LM339N	78	IN4017	5	2N4024	46	BC247L	13	CL850H	2850
HEF4021	107	HEF4074	22	HEF4529	456	74LS18	26	74LS136	49	74LS203	117	74LS301	206	LM339N	78	IN4018	5	2N4025	46	BC247L	13	CL850I	2850
HEF4022	103	HEF4075	22	HEF4530	214	74LS19	35	74LS138	99	74LS204	117	74LS302	206	LM339N	78	IN4019	5	2N4026	46	BC247L	13	CL850J	2850
HEF4023	22	HEF4076	22	HEF4531	214	74LS20	19	74LS139	99	74LS205	117	74LS303	206	LM339N	78	IN4020	5	2N4027	46	BC247L	13	CL850K	2850
HEF4024	76	HEF4077	23	HEF4532	214	74LS21	27	74LS143	88	74LS206	117	74LS304	206	LM339N	78	IN4021	5	2N4028	46	BC247L	13	CL850L	2850
HEF4025	22	HEF4078	23	HEF4533	113	74LS22	35	74LS144	138	74LS207	29	74LS305	206	LM339N	78	IN4022	5	2N4029	46	BC247L	13	CL850M	2850
HEF4026	244	HEF4079	23	HEF4534	122	74LS23	19	74LS145	93	74LS208	321	74LS306	206	LM339N	78	IN4023	5	2N4030	46	BC247L	13	CL850N	2850
HEF4027	57	HEF4080	80	HEF4535	98	74LS24	35	74LS146	93	74LS209	117	74LS307	206	LM339N	78	IN4024	5	2N4031	46	BC247L	13	CL850O	2850
HEF4028	89	HEF4081	80	HEF4536	149	74LS25	27	74LS147	93	74LS210	117	74LS308	206	LM339N	78	IN4025	5	2N4032	46	BC247L	13	CL850P	2850
HEF4029	113	HEF4082	80	HEF4537	149	74LS26	35	74LS148	93	74LS211	117	74LS309	206	LM339N	78	IN4026	5	2N4033	46	BC247L	13	CL850Q	2850
HEF4030	58	HEF4083	80	HEF4538	149	74LS27	26	74LS149	93	74LS212	117	74LS310	206	LM339N	78	IN4027	5	2N4034	46	BC247L	13	CL850R	2850
HEF4031	250	HEF4084	219	HEF4539	149	74LS28	60	74LS150	93	74LS213	117	74LS311	206	LM339N	78	IN4028	5	2N4035	46	BC247L	13	CL850S	2850
HEF4032	138	HEF4085	114	HEF4540	149	74LS29	27	74LS151	138	74LS214	117	74LS312	206	LM339N	78	IN4029	5	2N4036	46	BC247L	13	CL850T	2850
HEF4033	107	HEF4086	714	HEF4541	149	74LS30	48	74LS152	117	74LS215	117	74LS313	206	LM339N	78	IN4030	5	2N4037	46	BC247L	13	CL850U	2850
HEF4034	94	HEF4087	23	HEF4542	149	74LS31	27	74LS153	144	74LS216	117	74LS314	206	LM339N	78	IN4031	5	2N4038	46	BC247L	13	CL850V	2850
HEF4035	107	HEF4088	107	HEF4543	149	74LS32	35	74LS154	117	74LS217	117	74LS315	206	LM339N	78	IN4032	5	2N4039	46	BC247L	13	CL850W	2850
HEF4036	107	HEF4089	107	HEF4544	149	74LS33	35	74LS155	117	74LS218	117	74LS316	206	LM339N	78	IN4033	5	2N4040	46	BC247L	13	CL850X	2850
HEF4037	94	HEF4090	230	HEF4545	149	74LS34	46	74LS156	117	74LS219	117	74LS317	206	LM339N	78	IN4034	5	2N4041	46	BC247L	13	CL850Y	2850
HEF4038	93	HEF4091	135	HEF4546	149	74LS35	46	74LS157	220	74LS220	220	74LS318	206	LM339N	78	IN4035	5	2N4042	46	BC247L	13	CL850Z	2850
HEF4039	80	HEF4092	157	HEF4547	149	74LS36	39	74LS158	220	74LS221	121	74LS319	206	LM339N	78	IN4036	5	2N4043	46	BC247L	13	CL850AA	2850

Plastic Boxes - Boss Industrial Mouldings				SWITCHES				SEMI-CONDUCTORS				VERO ELECTRONICS PRODUCTS			
Moulded Box and Close Fitting Lined Lid ABS Box, C/W Brass Bushes, and Lid in Orange				Miniature Toggle - Honeywell				Secondary may be connected in series or parallel to give wide voltage range Primary 0.220, 240V				2.5" x 5" 1" pitch Veroboard			
Order Code	Case	Order Code	Case	SPDT	C/OH	SPDT	Double Bias To Centre	SPDT	Single Bias To Centre	SPDT					

# RAVEN ON

Dave Raven of Metac Electronics reports on a revitalised Swiss watch industry and the programmer catastrophe.

To make a fortune in electronics is not an unrealistic ambition in the 1980's. It compares favourably with the earlier successes of entrepreneurs at the turn of this century, making fortunes from the boom in bicycles and then motor cars. Similarly, young dynamic companies have emerged all over the world feverishly setting up new businesses that are associated with the enormous boom in the microchip industry.


At this time of year students face a major challenge in the examination room which they perceive as directly affecting their future careers. With the right results at hand the next task is to start selecting a suitable job with prospects for the future. If electronics and cash are the big motivators, then much thought must be given, since some areas of this industry will in the next decade be prepared to part with larger sums than others. Supply and demand is still the order of the day, even in science, and if cleaning ladies are in short supply then they will command a higher salary than say a PhD Physicist.

The increasing popularity of microcomputers has placed industry on a direct collision course with a major obstacle. With some careful planning now our intrepid students may find this rich in rewards by the mid 1980's. A software crisis large enough to slow down the whole business of microcomputer expansion is looming high over the horizon. The simple arithmetic which can confirm this shows that although the numbers of microcomputer designs is increasing by 30% a year the cost of implementing the designs will double. In the USA it has been estimated that by 1990 they will require at least one million software engineers and since the electrical engineers graduating at present can be numbered in only thousands it is described as a "programmer catastrophe".

In addition to the limited educational system which is seen as a further major contribution to the potential software crisis, the cost of developing software is also seen as having serious consequences. The cost of purchasing the hardware is expected to change little since this reflects the increased memory capacity of the microchips. However, software costs have risen dramatically. The alternative open to the semiconductor giants is to develop more complex microchips which contain software packages within. Thus a programmer can reduce the time taken to assemble his software. This is similar to the developments of earlier circuit designs which have progressed from single discrete transistor design to designing with complex blocks of circuits. The cost of these new developments are enormous and only a few very large manufacturers can undertake projects on this scale.
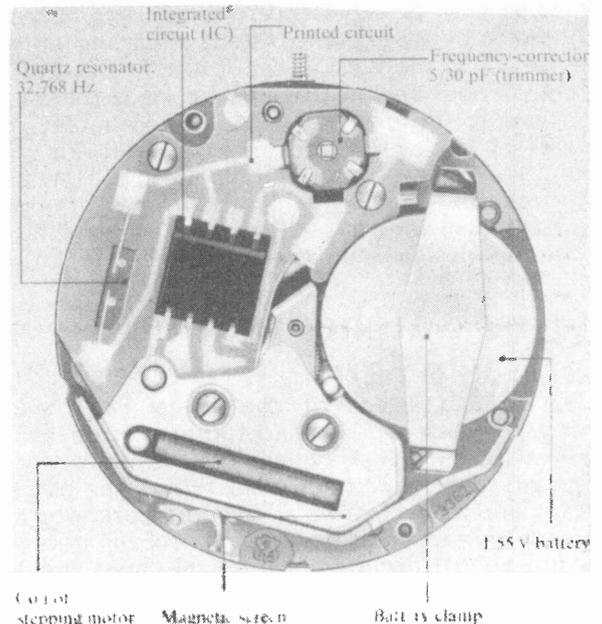
## Microchip R & D

In the USA the Department of Defence have decided to implement a 200 million dollar programme for the development of very high speed integrated circuits (VHSIC). This money will be granted to companies in private industry to make it easier for them to build the



The new quartz analogue watch modules now look very similar to their digital counterparts. Typical thickness for these models is about 3.9 mm. Swiss companies have a great deal of experience in producing these and it will present a major challenge to Japanese and Hong Kong assembled watches.

advanced chips the military need and to stimulate the development of "integrated systems". Other American companies such as Intel will spend up to 150 million dollars on capital equipment in 1980 as part of their "integrated systems" programme. For the next decade or so I sincerely hope we don't have cause to fall out with the Americans since, as the decline of our own ability to fabricate microcircuits continues, we will be less able to compete in the manufacture of industrial equipment without supplies of devices from the USA.

Whilst other major industrialised countries are sinking cash into research programmes the UK Government have just announced that they intend to resist pressure for further state aid. The micro-electronics Industry Support Programme has been cut (not increased) from £70 million to £55 million over a five year period. Also the microprocessor Awareness Programme has retained its budget of £55 million over a three year period. This total cash is less than one medium sized USA company will spend on R & D during the same period. As for spending £55m on making people aware of micro-electronics I would have thought that regular reading of the electronics Press in the UK and USA would wake people up sufficiently to what is happening. This would of course be a lot cheaper and the real spending should be done on making devices. I suspect that most of this money will be spent on making up for the lack of technical education and ignorance that results from the narrow curriculum of the schools and universities where many of the nation's leaders spend their youth.





New generation of quartz LCD Watches. Sabre Alarm Chronograph uses standard watch cells and measures only 3.9 mm thickness.

It is easy to grow cynical on matters which are not every day problems to government. However, I am personally convinced that urgent attention must be given to our country's future role in electronics. The solution to our avoiding a software crisis and indeed an industrial crisis in Britain lies here within our shores. We can very soon find plenty of aware people if the cash is available to support them. Personalities like Derek Roberts who currently heads the GEC Hirst Research Centre and John Bass from Plessey, to name but two individuals, must have quite a lot of experience in organising microchip development between them. Instead of carting parties of TUC officials to the West Coast of America in search of awareness about how microchips are made they should take a bus to Towcester, Swindon or Wembley. Here they will see just as much technology and its all British. Forget Inmos factories in Colorado Springs. How about setting up something twenty minutes from Heathrow Airport or at least within easy distance of some of the best microcircuit designers in the world, here in England.

## Swiss watches return at Basle Fair.

The annual event of the Basle Fair, held in Switzerland each Spring, incorporates probably the largest exhibition held anywhere in the world for watches and clocks. This very traditional fete is the assembly point for watch buyers from all over the world who place orders for their full year's requirements. Exhibitors at the show are almost exclusively from the Swiss Industries with just a smattering of other European companies. Walking through the lavish exhibits of such famous names as Omega, Tissot and Rolex it was very hard to believe that the Swiss watch industry had just emerged from five years of nightmare competition. This of course was a result of the enormous increase in quartz electronic watches during this period.

The sudden arrival of LED and then LCD watches and the continued rapid developments of microchip technology produced shock waves which must have threatened the existence of many of the smaller watch producers. Hong Kong, who were at the very heart of this watch revolution, increased their market share in watches from being a net importer of watch modules from Switzerland to becoming the world's largest watch exporter and in terms of value of watch exports they now rank third.

The way in which the Swiss watch manufacturers operate must have considerably altered in the past five years, with a number of mergers and trading agreements taking place. The saving grace, however, seems to be the Swiss watch manufacturers' strong financial resources and also their ability to withstand change and rapidly learn new techniques.

The presentation by manufacturers at Basle for both digital and analogue display watches was of a very high standard. My biggest surprise, however, came from the strong contingent of quartz analogue watches. These models, which I previously thought were extinct, have risen once again in quite a different form. The first impression was that this was confirmation of the demise of the Swiss watch industry. Then after closer inspection I realised how much slimmer and neater these little beasts looked. I was left in little doubt that these will be well received in the watch market place despite my own prejudices towards mechanical displays. I feel their

popularity stems from the neater, cleaner looking design and also this new slimline case, which dispels the cause for much complaint in the past. Also quite a number of people, particularly those over a certain age, experience difficulty in seeing the digital display without spectacles. My additional suspicion for the strong emergency of quartz analogue was that the Swiss were probably struggling to keep up with the current level of high technology in the digital quartz. This was also quickly dispelled, I am pleased to report, since the electronic varieties were every bit as advanced as anything yet seen coming out of the Far East.

Quartz analogue watches deserve some further mention in particular because of the technical achievements which have occurred during their redevelopment. The Swiss have of course a long tradition in the manufacture of traditionally designed watches and they also have a large number of credits for new development work in the manufacture of watches. It was here that the thinnest watch ever made was produced in 1975 (1.2 mm). Its conception was quite revolutionary and was described at the time as defying the logical laws of watch mechanics. This same company incidentally has been taken over this past year by one Japanese company called K. Hattori, who, you may or may not know, own the brand name of Seiko.

On the new technology front, Bulova announced their rather unusual watch which drives its energy from the body's own heat. A voltage produced from the thermoelectric elements is transformed through a sophisticated electric circuit to the required voltage necessary to operate the watch. On attaining the required level of voltage, this energy is directed towards an accumulator, which is in effect a rechargeable battery. The average body temperature of 37°C delivers at the case back more than 1000 uW of "heat" power. The power consumed to operate a typical quartz wristwatch containing a tiny battery is approximately 2 uW. The device that Bulova has perfected receives from the thermo-generator approximately 8-12 uW. Therefore, the electric energy produced is four to six times greater than that which is consumed in operating the watch.

One other Swiss company in strong evidence was Buler, whose range of ultra slim analogue and digital models will certainly be serious competition for the Japanese quality watches. The new twelve digit quartz electronic model from Buler must be the most advanced module coming on the market this year and will further increase the market share for Swiss-made electronic watches.

ETI

See us on Stand 161  
at SCOTELEX and  
Stand A51 and A52  
at LEETRONIX

# The Logic Probes

## Spend Less

## Test More



### LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

**£31.00\***



### LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,


replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £11.92)

**£18.00\***

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

\*price excluding P.&P and 15% VAT.

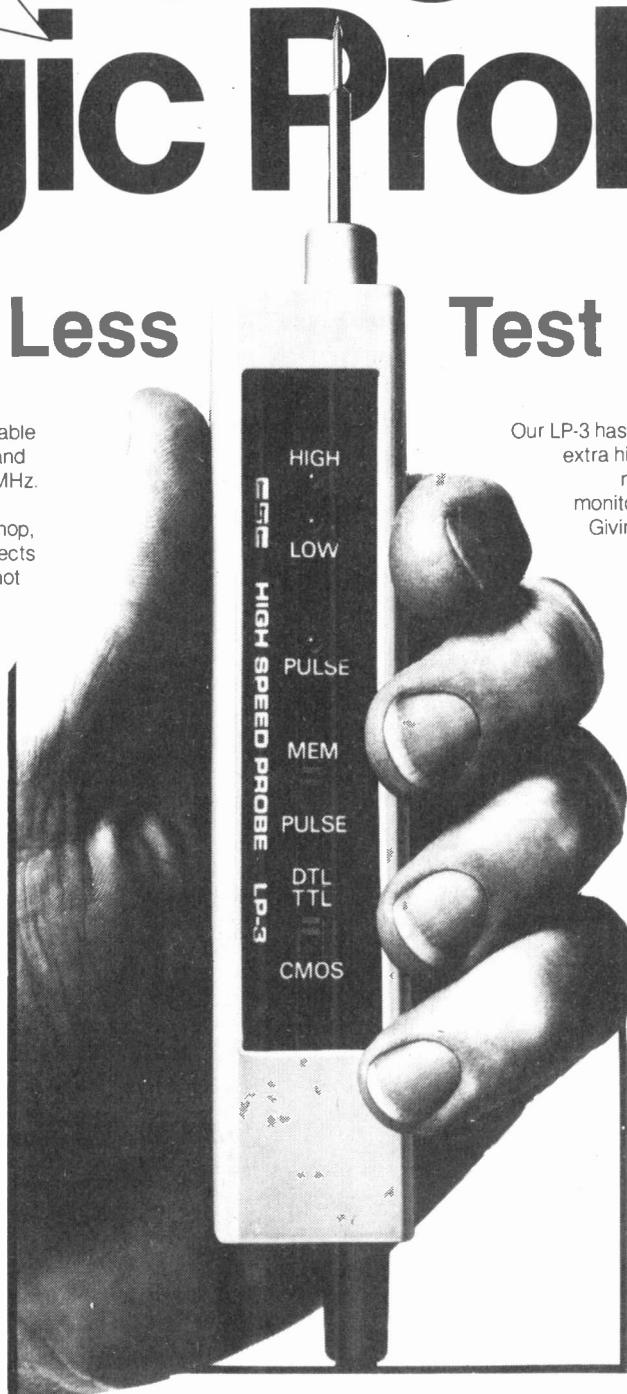

### LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz.

Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

**£49.00\***



### The New Pulser DP-1


The Digital Pulser: another new idea from C.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

**£51.00\***



CONTINENTAL SPECIALTIES CORPORATION

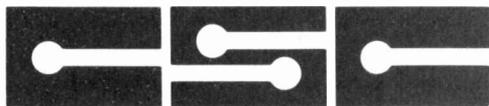

C.S.C. (UK) Ltd., Dept. 911, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.  
Prices include P&P and 15% VAT

LP-1	£37.38	Qty	LP-2	£22.14	Qty	LP-3	£58.08	Qty	DP-1	£60.38	Qty	LPK-1	£14.86	Qty
------	--------	-----	------	--------	-----	------	--------	-----	------	--------	-----	-------	--------	-----

Name \_\_\_\_\_ Address \_\_\_\_\_

I enclose Cheque/P.O for £ \_\_\_\_\_ or debit my Barclaycard/Access/  
American Express card no. \_\_\_\_\_ exp date \_\_\_\_\_

FOR IMMEDIATE ACTION — The C.S.C. 24 hour, 5 day a week service  
Telephone (0799) 21682 and give us your Barclaycard, Access, American Express  
number and your order will be in the post immediately.

For FREE  
catalogue  
tick box

C.S.C. (UK) Limited, Dept.911  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.

Telephone: Saffron Walden (0799) 21682  
Telex: 817477

# Marshall's

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA  
Industrial Sales: 01-328 1009  
Mail Order: 01-624 8582  
Also retail shops: 325 Edgware Road, London W2.  
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.  
108A Stokes Croft Bristol.

## CAPACITORS:

Mullard Ceramic 63v range  
1pF to 10,000pF E 24 range  
all at £0.06 each  
Siemens Ceramic 63v B37448/9  
.01: .022: .033: .047mF @ £0.06  
.068: .1mF @ £0.08: .22mF @  
£0.11

CSF High Voltage Ceramic Discs  
Prices £0.07 to £0.18 Range  
100pF to 10,000pF

Voltage range up to 6Kv.  
See catalogue for details.  
Comprehensive range Siemens  
Layer Polyester Caps: .001 to  
3.3mF

Prices £0.07 to £0.63.  
See catalogue for details.  
Large range of Mullard/Siemens  
Electrolytic Axial/Radial  
Capacitance values 1.0mF to  
10,000mF

Voltage ranges 25v: 40v: 63v:  
100v:

Prices and types as catalogue  
Also Mullard C280; Siemens  
B32231/4 and B32110. All prices  
net + VAT and postage/packaging.

## TOOLS BAHCO

Side Cutter with Bezel.  
Side Cutter without Bezel.  
End Cutter without Bezel.

Vero Metal Shears.  
Other items as catalogue.



## BOXES & CASES

See catalogue for full range.  
Aluminium boxes 13 sizes.  
Rexine Covered boxes 7 sizes.  
NEW RANGE TMEC CASES  
Send S.A.E. for details & types  
Price range, £14.04 to £17.00  
ABS PLASTIC BOXES

3" x 2 1/4" x 1 3/8" Prices as  
3 3/4" x 2 3/4" x 1 3/8" catalogue  
4 1/2" x 3 3/4" x 1 1/2"

8" x 4 1/4" x 3"  
BAZELLI INSTRUMENT CASES  
5 sizes.

Miscellaneous hardware  
including  
Vero Board: Superstrips:  
Vero Breadboard.  
Vero boxes (see catalogue for  
full range).



Card Frames: Fliptop boxes:  
etc etc.

## 1980 CATALOGUE

U.K.: 65p post paid  
Europe 85p post paid  
Rest of World £1.25  
post paid

Mail order: 01-624 8582



## TTL see catalogue for full range

SN7400N	£0.14	SN7491AN	£0.54
SN7401N	£0.14	SN7492N	£0.31
SN7402N	£0.14	SN7493N	£0.32
SN7403N	£0.14	SN7494N	£0.80
SN7404N	£0.14	SN7495N	£0.55
SN7405N	£0.15	SN7496N	£0.34
SN7406N	£0.34	SN7497N	£1.80
SN7407N	£0.26	SN74100N	£1.10
SN7408N	£0.15	SN74107N	£0.21
SN7409N	£0.16	SN74118N	£0.76
SN7410	£0.15	SN74119N	£1.20
SN7411N	£0.15	SN74121N	£0.25
SN7412N	£0.20	SN74122N	£0.48
SN7413N	£0.28	SN74123N	£0.42
SN7414N	£0.47	SN74124N	£0.53
SN7416N	£0.22	SN74125N	£0.40
SN7417N	£0.22	SN74141N	£0.50
SN7420N	£0.15	SN74145N	£0.64
SN7423N	£0.18	SN74148N	£1.05
SN7425N	£0.19	SN74150N	£0.79
SN7426N	£0.19	SN74151N	£0.55
SN7427N	£0.19	SN74153N	£0.55
SN7430N	£0.15	SN74154N	£0.90
SN7432N	£0.17	SN74155N	£0.60
SN7437N	£0.21	SN74157N	£0.59
SN7438N	£0.21	SN74160AN	£0.70
SN7440N	£0.15	SN74161AN	£0.70
SN7441AN	£0.52	SN74162AN	£0.70
SN7442N	£0.40	SN74163AN	£0.70
SN7445N	£0.66	SN74164N	£0.80
SN7446AN	£0.48	SN74165N	£0.80
SN7447AN	£0.48	SN74167N	£0.79
SN7448N	£0.45	SN74174N	£0.80
SN7450N	£0.15	SN74175N	£0.63
SN7451N	£0.15	SN74176N	£0.74
SN7453N	£0.15	SN74177N	£0.73
SN7454N	£0.15	SN74180N	£0.70
SN7456N	£0.15	SN74181N	£1.65
SN7470N	£0.26	SN74182N	£0.83
SN7472N	£0.24	SN74184N	£1.29
SN7473N	£0.25	SN74185AN	£1.10
SN7474N	£0.25	SN74186N	£1.35
SN7475N	£0.31	SN74187N	£1.84
SN7476N	£0.26	SN74189N	£2.26
SN7480N	£0.39	SN74190N	£0.74
SN7481N	£0.71	SN74191N	£0.79
SN7482N	£0.71	SN74192N	£0.79
SN7483N	£0.60	SN74193N	£0.79
SN7484N	£0.95	SN74196N	£0.74
SN7485N	£0.70	SN74197N	£0.74
SN7486N	£0.74	SN74198N	£1.29
SN7489N	£1.66	SN74199N	£1.09
SN7490AN	£0.33		

## SOLDERING EQUIPMENT

IRONS-ANTEX  
15 watt C15 £3.95  
15 watt CCN £4.20  
17 watt CX17 £4.20  
25 watt X25 £4.20  
Stand £1.50



## DESOLDERING TOOL

Solder £6.50



## SINCLAIR INSTRUMENTS

Digital Multimeter  
" " PDM35 £ 34.50  
" " DM235 £ 52.50  
" " DM350 £ 72.50  
" " DM450 £ 99.00  
Digital Frequency Meter  
PFM200 £ 49.80  
Low Power Oscilloscope  
SC110 £139.00

## CRIMSON ELEKTRIK HI FI MODULES

CE608 Power Amp £18.26  
CE1004 " " £21.30  
CE1008 " " £23.91  
CE1704 " " £30.43  
CE1708 " " £30.43  
CPS1 Power Unit £16.96  
CPS3 " " £20.43  
CPS6 " " £26.09  
CPR1 Pre Amp £29.57  
CPR1S Pre Amp £38.70

All prices + VAT + postage/  
packaging

## KNOBBS & SWITCHES

Big selection as catalogue  
Also Resistors; Presets; Pots;  
Opto; Semiconductors etc.

# interface components

## TRANSISTORS

AC128	15p	BF200	29p
AC187K	30p	BF336	33p
AC188K	30p	BFX30	32p
ACV17	90p	BFX86	26p
AD149	55p	BFX88	22p
AF127	35p	BFY50	13p
AS217	120p	BFY51	13p
AU113	150p	BFY64	28p
BC107	7p	BFY90	56p
BC108	7p	BSX19	80p
BC108A	7p	BSY95A	16p
BC108C	7p	BU204	149p
BC136	15p	BU208	150p
BC140	28p	OC29	89p
BC141	30p	OC43	50p
BC142	25p	2N696	15p
BC143	28p	2N930	20p
BC147	6p	2N1132	19p
BC147B	6p	2N1304	40p
BC149C	7p	2N1613	12p
BC159	9p	2N1711	15p
BC160	35p	2N2217	20p
BC167A	10p	2N2219A	20p
BC178	12p	2N2221	18p
BC182	8p	2N2368	15p
BC182L	9p	2N2369	14p
BC183	9p	2N2894A	20p
BC183L	9p	2N2904	15p
BC184L	9p	2N2904A	15p
BC186	20p	2N2905	15p
BC212	9p	2N2906	15p
BC212L	9p	2N2926B	10p
BC213B	9p	2N2926C	10p
BC227	13p	2N3442	102p
BC232B	13p	2N3702	8p
BC337	16p	2N3704	8p
BC338	11p	2N3705	8p
BC440	32p	2N3708	8p
BC547	9p	2N3709K	8p
BC548	9p	2N3866	35p
BC550	14p	2N3906	10p
BC558	12p	2N4058	12p
BCY34	99p	2N4427	60p
BCY39	229p		
BCY58	16p	AA119	10p
BCY70	12p	BA154	9p
BCY71	12p	BA156	9p
BCY72	12p	IN4001	4p
BF179	25p	IN4002	4p
BF183	25p	IN4003	5p
		IN4005	5p
		IN4148	5p
		IS44	3p

## OPTO

Leds		
125 Red	10p	
125 Orange	10p	
125 Yellow	10p	
2 Red	10p	
2 Green	10p	
2 Clear	10p	

## DISPLAYS

704	110p
727	160p
741	160p
747	160p
750	160p

## REGULATORS

7805	57p
7812	57p
7815	57p
7818	57p
7824	57p
7905	140p
7912	140p
7915	140p
7918	140p
7924	140p
LM320T5	149p
LM320T8	149p
LM320T15	149p
LM330T18	149p
LM340T5	74p
LM340T15	74p
LM340T18	74p

## TRIACS

4A 400V	54p
4A 600V	66p
6A 400V	60p
6A 600V	66p
8A 400V	66p
8A 600V	72p
10A 400V	72p
10A 600V	84p
15A 400V	108p
15A 600V	126p

## TTL

7400	9p
7401	9p
7402	9p
7403	9p
7404	10p
7405	14p
7406	30p
7407	30p
7408	17p
7409	17p
7410	12p
7412	12p
7413	25p
7414	45p
7416	25p
7417	25p
7418	25p
7419	24p
7420	28p
7427	28p
7430	14p
7432	22p
7438	26p
7442	48p
7447	50p
7450	15p
7451	15p

## with internal trigger diac

74LS124	115p
74LS132	89p
74LS139	79p
74LS151	89p
74LS155	91p
74LS156	89p
74LS157	69p
74LS165	69p
74LS168	139p
74LS174	99p
7485	25p
7491	63p
7492	35p
7493	28p
7494	63p
7495	63p
74100	110p
74107	30p
74121	25p
74122	36p
74123	44p
74145	72p
74154	80p
74157	60p
74161	85p
74175	63p
74180	84p
74181	151p
74191	80p
74192	80p
74193	80p
74194	80p
74LS175	89p
74LS190	110p
74LS192	115p
74LS194	115p
74LS195	115p
74LS196	95p
74LS197	125p
74LS267	89p
74LS280	99p
74LS273	199p
74LS323	59p
74LS378	159p

## BRIDGES

	2A	50V	100V	200V	400V	600V
	4A	45p	52p	60p	75p	100p
		52p	60p	68p	82p	105p
		60p	68p	75p	90p	112p

## DIL SOCKETS

8 pin	10p
14 pin	12p
16 pin	13p
20 pin	15p
24 pin	30p
40 pin	40p

## CMOS

4000	14p	4072	17p
4001	14p	4073	17p
4002	14p	4075	19p
4006	69p	4076	75p
4007	16p	4077	35p
4008	79p	4081	19p
4009	36p	4082	17p
4010	36p	4160	105p
4011	19p	4161	105p
4012	16p	4162	105p
4014	59p	4163	105p
4015	73p	4402	36p
4016	42p	4404	110p
4017	79p	4412	86p
4018	79p	4445	174p
4019	45p	4446	148p
4020	89p	4507	99p
4021	83p	4511	89p
4022	79p	4512	89p
4023	16p	4514	229p
4024	45p	4515	229p
4025	17p	4516	99p
4026	129p	4520	70p
4027	39p	4522	125p
4028	59p	4526	125p
4029	89p	4531	125p
4030	40p	4535	92p
4034	1250p	4556	69p
4035	750p	4581	269p
4042	750p	4582	115p
4043	69p	4584	59p
4044	109p	4585	99p
4049	45p		
4050	63p		

# Greenbank


Greenbank Electronics  
(Dept TTE) 92 New Chester Road, New Ferry  
Wirral, Merseyside L62 5AG  
(Tel. 051-645 3391)



**TERMS, VAT, CWO.** Cheques etc payable to Greenbank Electronics and crossed. Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 35p (+5p elsewhere = 40p) per order. Export: MO VAT but add 35p (Eire), 75p (Europe) and £2.50 elsewhere. Access: Barclaycard, Visa, telephoned orders accepted. (Polys, universities, gov depts, etc can telephone their orders for immediate delivery on account.)



## UV EPROM ERASERS

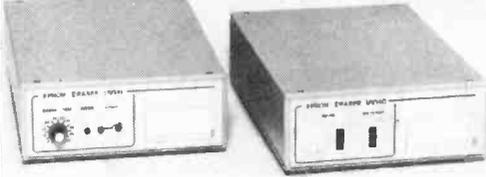

Two easy to use units designed for both the professional and amateur UV-prom user.

### Features:

- Can erase up to 14 proms.
- Special short wave ultraviolet tube.
- Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life).
- Sliding tray carries proms on conductive foam.
- Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
- "Mains on" and "Tube On" indicators.
- Smart textured case.
- Complete instructions supplied.
- Supplied complete with mains plug and flex.

Model UV141. Price £77.70

Also available without timer as

Model UV140. Price £61.20

PROM WASHING SERVICE: 50p each prom

## COMPUTER BOARDS

The following is an extract from our leaflet ref. 'MP4', which is available free on request (a 9" x 6" SAE helps, but is not essential). See Microprocessor section to the right for board prices.

For many people the wide choice of microprocessors now available presents a difficult choice. To understand any particular microprocessor in depth a development system is almost essential, however in the past to understand more than one several separate development systems have had to be purchased.

The reason that separate systems, one for each processor, have been necessary is due to the fact that individual microprocessors have their own individual features in one case to access memory a separate read strobe and write strobe is required, in another a 'read/write' line is used in combination with a combined strobe called 'valid memory address and phi-2'. With some processors, the same address bus can be used for both memory and input/output ports, under the control of a 'memory request' or an 'input/output request' control line.

Naturally, if a development system takes advantage of any of the particular unique features of any particular microprocessor, this makes it more difficult to graft some other unrelated microprocessor onto the same bus at a later date. A Universal Micro System provides a basic bus structure on which any one micro-processor can be connected. The system uses a CPU (Central Processor Unit) card which is separate from the rest of the system, and this allows the same memory and interfaces to be retained when a different MPU is used.

The basic system bus consists of data and address buses together with read and write strobes. By locating the data input (Keyboard) and output (VDU) in the memory space then such chips as the 8080/8085 family, which normally use input/output ports, can now be used without any fundamental change to the bus (and as a bonus, users of these MPU's have all the ports entirely free for their own purposes).

The range of p.c.b.'s includes boards to implement a memory-mapped VDU, cassette interface, keyboard interface, PROM programmer, and a number of RAM and ROM cards. All the cards are of International Size 114 x 203 mm (4 1/2" x 8") except for the larger power PSU A power supply card. This latter card is sized so that it can be bolted to the side of a standard 4" chassis module which is then compatible with the other cards. The cards have a standard 43-way edge connector, with one position used for polarisation.

We do not propose to defend the (relatively small) number of bus connections (42), against such standards as the 'S100' bus. The S-100 bus, as it originated in America, is bigger and more expensive. In the same way, a Ford 'Granada' is bigger and more expensive than a 'Cortina', but it doesn't mean a 'Cortina' is a better value than a 'Granada'.

**NEW! 'ISBUS-1.1'**  
Low-cost commercial quality computer back board. 1.3" x 4 3/8" approx, for the International Standard (114x203mm) cards. Although intended for the 86-way double sided connector, it can be used with the 43-way connector specified for the computer boards we advertise. (Pin 37 is used for polarisation.)  
Takes up to 13 cards on 1" centres, and provides for 4 power rails, 58 parallel address/data etc. bus lines and 3 'daisy chains'.  
More details in our free leaflet 'ISB-1.1'.  
Existing enquirers Note Leaflets have been delayed, but will follow soon.

## CMOS

These cut prices for Amateur Users and Export. Note: industrial users - quantity prices available. Mostly Motorola, RCA

4000 18p	4042 80p	4096 95p	4451 £3.81	4549 £4.38
4001 25p	4043 90p	4097 £3.40	4461 £3.93	4552 £14.85
4002 25p	4044 90p	4098 £1.20	4462 £4.41	4553 £4.50
4006 95p	4045 £1.45	4099 £2.00	4490F £4.20	4554 £3.80
4007 18p	4046 £1.10	4100 £2.20	4490VP £3.14	4555 78p
4008 80p	4047 £1.00	4101 £1.32	4500 £6.95	4556 72p
4009 40p	4048 55p	4102 £1.80	4501 29p	4557 £3.86
4010 50p	4049 45p	4103 - £1.80	4502 £1.20	4558 £1.25
4011 25p	4050 49p	4104 99p	4503 70p	4559 £4.38
4012 18p	4051 80p	4105 99p	4505 £5.71	4560 £2.50
4013 50p	4052 80p	4106 90p	4506 50p	4561 81p
4014 84p	4053 80p	4107 60p	4507 55p	4562 £5.60
4015 84p	4054 £1.50	4108 £4.70	4508 £2.90	4566 £1.59
4016 45p	4055 £1.25	4109 £1.00	4510 99p	4568 £2.38
4017 80p	4056 £1.35	4110 £3.00	4511 £1.50	4569 £2.50
4018 89p	4059 £6.00	4114 £2.50	4512 90p	4572 40p
4019 45p	4057 £1.10	4182 £1.40	4514 £2.65	4580 £4.77
4020 99p	4052 £1.00	4192 £1.40	4515 £3.00	4581 £2.62
4021 £1.10	4063 £1.20	4193 £1.40	4516 £1.40	4582 £1.14
4022 £1.00	4066 55p	4194 £1.18	4518 £1.00	4584 90p
4023 27p	4067 £4.50	4195 £1.18	4519 80p	4585 £1.27
4024 50p	4068 27p	4257 £1.48	4520 £1.00	4587 £2.44
4025 £1.30	4069 27p	4161 99p	4521 £2.50	4588 £2.98
4026 27p	4071 25p	4162 99p	4522 £1.11	4599 £6.95
4027 50p	4072 25p	4163 99p	4526 £1.08	4700 £1.75
4028 84p	4073 25p	4174 90p	4527 £1.50	
4029 99p	4075 25p	4175 £1.15	4528 £1.11	
4030 55p	4076 £1.07	4176 £1.16	4529 £1.30	
4031 £2.00	4077 29p	4177 29p	4530 70p	
4032 £1.31	4078 29p	4469 £9.37	4531 £1.45	
4033 £1.80	4079 29p	4470 £9.37	4532 £1.30	
4034 £2.00	4081 27p	4471 £10.72	4534 £5.60	
4035 £1.10	4082 27p	4472 £10.72	4536 £3.69	
4036 £2.95	4085 74p	4473 £10.72	4537 £2.10	
4037 £1.15	4086 72p	4474 £10.72	4538 £1.20	
4038 £1.20	4089 £1.38	4475 £10.72	4539 97p	
4039 £2.95	4093 90p	4433 £12.30	4540 £1.19	
4040 £1.00	4094 £2.50	4434 £10.72	4541 £1.80	
4041 80p	4095 95p	4435 £3.81	4542 £1.80	

## 74C

74C00 33p	74C76 81p	74C163 £1.72	74C904 85p	74C926 £7.26
74C02 33p	74C77 81p	74C164 £1.62	74C905 £10.89	74C927 £7.26
74C04 33p	74C78 96p	74C165 £1.62	74C906 85p	74C928 £7.26
74C08 33p	74C79 £1.57	74C173 £1.35	74C907 85p	74C929 £17.90
74C10 33p	74C80 £2.28	74C174 £2.27	74C908 £1.44	80C95 85p
74C14 £2.12	74C81 £1.28	74C175 £1.27	74C909 £2.45	80C96 92p
74C16 £2.12	74C82 £1.28	74C182 £2.59	74C910 £1.10	80C97 92p
74C20 42p	74C83 £1.28	74C183 £1.72	74C911 £1.10	80C98 92p
74C22 42p	74C84 £1.28	74C184 £1.72	74C912 £1.69	80C99 92p
74C24 £1.38	74C85 £1.28	74C185 £1.72	74C913 £1.72	80C99 £2.90
74C28 £2.07	74C86 £1.72	74C186 £2.69	74C918 £1.59	80C99 £2.90
74C32 42p	74C87 £1.72	74C187 £2.69	74C921 £1.77	27.00 MHz £3.92
74C42 £1.38	74C88 £1.72	74C188 £2.69	74C922 £5.49	30.565 MHz £3.92
74C48 £2.07	74C89 £1.72	74C189 £2.69	74C923 £5.49	48.000 MHz £3.23
74C52 42p	74C90 81p	74C190 £1.72	74C924 85p	100.000 MHz £3.23
74C56 42p	74C91 72p	74C191 £1.72	74C925 85p	116.000 MHz £3.23

## MODULATORS

UM111, E36 UHF CA.36 Vision Modulator £2.50
UM1231 UHF CA.36 Vision Modulator wide bandwidth for computers etc. £4.70
UM1263 FM Sound Sub-carrier Modulator £2.50

## SWITCH MODE PSUs


AC 220V 5V/10A £69.90
AC 220V 5V/5A, 12V/1A, -12V/1A, -5V/0.1A £86.80
AC 240V 5V/5A, 12V/1A, -12V/1A, -5V/0.1A £126.50




## MICROPROCESSORS

COMPUTER BOARDS	6800 MPU	6800	INTERFACE
114 x 203 mm fiberglass, with gold plated edge connector.	£6.95	£5.95	81LS95/6/7/8 £1.40
Buffed SC/MP CPU £9.40	£9.95	£7.75	75491 LED driver 50p
SC/MP Frontboard £9.40	£12.00	£3.96	75492 92p
280 CPU card £9.40	£12.00	£3.96	27425 85p
VDU 'A' set £8.90	£12.00	£3.96	8726 £2.64
VDU 'B' set £8.90	£12.00	£3.96	8727 £2.64
VDU 'G' three £9.40	£12.00	£3.96	8728 £2.64
EPROM Programmer £9.40	£12.00	£3.96	8729 £2.64
4K PROM board (£204s) £9.40	£12.00	£3.96	8730 £2.64
8K PROM board (£270s) £9.40	£12.00	£3.96	8731 £2.64
16K PROM board (£270s) £9.40	£12.00	£3.96	8732 £2.64
24K PROM board (£270s) £9.40	£12.00	£3.96	8733 £2.64
32K PROM board (£270s) £9.40	£12.00	£3.96	8734 £2.64
40K PROM board (£270s) £9.40	£12.00	£3.96	8735 £2.64
48K PROM board (£270s) £9.40	£12.00	£3.96	8736 £2.64
56K PROM board (£270s) £9.40	£12.00	£3.96	8737 £2.64
64K PROM board (£270s) £9.40	£12.00	£3.96	8738 £2.64
72K PROM board (£270s) £9.40	£12.00	£3.96	8739 £2.64
80K PROM board (£270s) £9.40	£12.00	£3.96	8740 £2.64
88K PROM board (£270s) £9.40	£12.00	£3.96	8741 £2.64
96K PROM board (£270s) £9.40	£12.00	£3.96	8742 £2.64
104K PROM board (£270s) £9.40	£12.00	£3.96	8743 £2.64
112K PROM board (£270s) £9.40	£12.00	£3.96	8744 £2.64
120K PROM board (£270s) £9.40	£12.00	£3.96	8745 £2.64
128K PROM board (£270s) £9.40	£12.00	£3.96	8746 £2.64
136K PROM board (£270s) £9.40	£12.00	£3.96	8747 £2.64
144K PROM board (£270s) £9.40	£12.00	£3.96	8748 £2.64
152K PROM board (£270s) £9.40	£12.00	£3.96	8749 £2.64
160K PROM board (£270s) £9.40	£12.00	£3.96	8750 £2.64
168K PROM board (£270s) £9.40	£12.00	£3.96	8751 £2.64
176K PROM board (£270s) £9.40	£12.00	£3.96	8752 £2.64
184K PROM board (£270s) £9.40	£12.00	£3.96	8753 £2.64
192K PROM board (£270s) £9.40	£12.00	£3.96	8754 £2.64
200K PROM board (£270s) £9.40	£12.00	£3.96	8755 £2.64
208K PROM board (£270s) £9.40	£12.00	£3.96	8756 £2.64
216K PROM board (£270s) £9.40	£12.00	£3.96	8757 £2.64
224K PROM board (£270s) £9.40	£12.00	£3.96	8758 £2.64
232K PROM board (£270s) £9.40	£12.00	£3.96	8759 £2.64
240K PROM board (£270s) £9.40	£12.00	£3.96	8760 £2.64
248K PROM board (£270s) £9.40	£12.00	£3.96	8761 £2.64
256K PROM board (£270s) £9.40	£12.00	£3.96	8762 £2.64
264K PROM board (£270s) £9.40	£12.00	£3.96	8763 £2.64
272K PROM board (£270s) £9.40	£12.00	£3.96	8764 £2.64
280K PROM board (£270s) £9.40	£12.00	£3.96	8765 £2.64
288K PROM board (£270s) £9.40	£12.00	£3.96	8766 £2.64
296K PROM board (£270s) £9.40	£12.00	£3.96	8767 £2.64
304K PROM board (£270s) £9.40	£12.00	£3.96	8768 £2.64
312K PROM board (£270s) £9.40	£12.00	£3.96	8769 £2.64
320K PROM board (£270s) £9.40	£12.00	£3.96	8770 £2.64
328K PROM board (£270s) £9.40	£12.00	£3.96	8771 £2.64
336K PROM board (£270s) £9.40	£12.00	£3.96	8772 £2.64
344K PROM board (£270s) £9.40	£12.00	£3.96	8773 £2.64
352K PROM board (£270s) £9.40	£12.00	£3.96	8774 £2.64
360K PROM board (£270s) £9.40	£12.00	£3.96	8775 £2.64
368K PROM board (£270s) £9.40	£12.00	£3.96	8776 £2.64
376K PROM board (£270s) £9.40	£12.00	£3.96	8777 £2.64
384K PROM board (£270s) £9.40	£12.00	£3.96	8778 £2.64
392K PROM board (£270s) £9.40	£12.00	£3.96	8779 £2.64
400K PROM board (£270s) £9.40	£12.00	£3.96	8780 £2.64
408K PROM board (£270s) £9.40	£12.00	£3.96	8781 £2.64
416K PROM board (£270s) £9.40	£12.00	£3.96	8782 £2.64
424K PROM board (£270s) £9.40	£12.00	£3.96	8783 £2.64
432K PROM board (£270s) £9.40	£12.00	£3.96	8784 £2.64
440K PROM board (£270s) £9.40	£12.00	£3.96	8785 £2.64
448K PROM board (£270s) £9.40	£12.00	£3.96	8786 £2.64
456K PROM board (£270s) £9.40	£12.00	£3.96	8787 £2.64
464K PROM board (£270s) £9.40	£12.00	£3.96	8788 £2.64
472K PROM board (£270s) £9.40	£12.00	£3.96	8789 £2.64
480K PROM board (£270s) £9.40	£12.00	£3.96	8790 £2.64
488K PROM board (£270s) £9.40	£12.00	£3.96	8791 £2.64
496K PROM board (£270s) £9.40	£12.00	£3.96	8792 £2.64
504K PROM board (£270s) £9.40	£12.00	£3.96	8793 £2.64
512K PROM board (£270s) £9.40	£12.00	£3.96	8794 £2.64
520K PROM board (£270s) £9.40	£12.00	£3.96	8795 £2.64
528K PROM board (£270s) £9.40	£12.00	£3.96	8796 £2.64
536K PROM board (£270s) £9.40	£12.00	£3.96	8797

# STEREO IMAGE CO-ORDINATOR

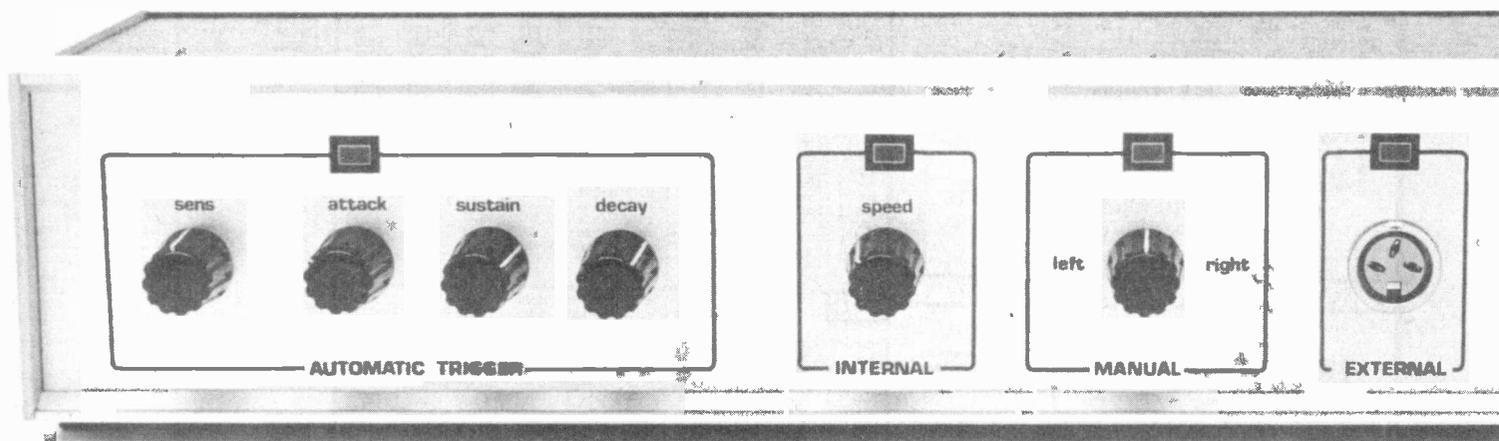

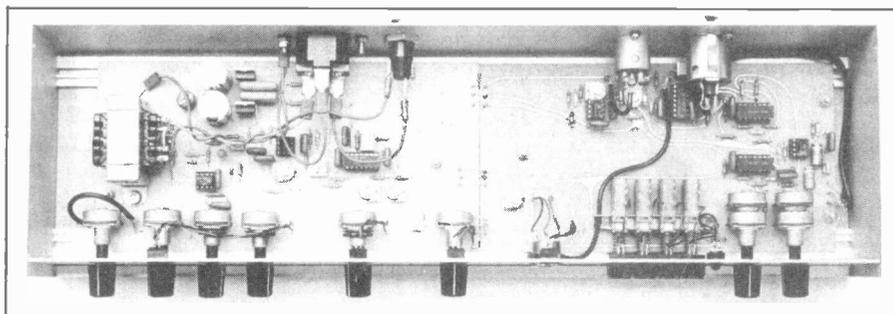Following his article on the 1537A VAC, Keith Brindley comes up with a complete application using this most resourceful chip.



Perhaps an explanation is required! What, you may ask, is a Stereo Image Co-ordinator? Briefly it's a panning control — simple? — well, not so simple. Panning is an effect whereby you apply a single mono sound source and derive two independent adaptations of that original sound, which together form the inputs to a stereo (or 2 x mono) amplifier. By varying the amplitude of these two adaptations, the stereo image they produce can be altered providing an apparently moving sound source. It is an effect used quite often in recording studios usually with modern rock and pop music. Commercial units are now available (though not as effective or as good as the ETI Stereo Image Co-ordinator), which produce the effect live, for stage work, but in the past panning has been predominantly a studio technique.

## Not Only But Also

The ETI Stereo Image Co-ordinator produces the usual effect of panning using a manually turned pot, but added to this are the exclusive facilities of automatic control over the image produced. The use of these facilities obviously allows

the musician to concentrate on the music rather than the equipment.

Control over the stereo image is provided by four methods:

Manual — a single pot positions the image wherever required.

Sweep — the image is swept from one channel to the other at a variable rate, automatically.

Automatic Trigger — the instant a note is played or sung the image is swept from one side to the other at a completely variable rate.

External — control is accorded by an externally applied voltage eg from a foot pedal.

The unit utilises the 1537A Voltage Controlled Attenuator which as ETI readers will know is the high quality (good enough for studio applications), recently introduced, integrated circuit for VCA use. All other active components used in the audio section of the circuit are high quality, low noise types which coupled with the considerations of careful PCB design should allow the builder to construct a device which is at home in the studio as well as in live stage work.



This box of tricks gives you the opportunity to try out what has up to now been an effect used predominantly in the studio. The stereo sound image can be controlled automatically or manually. You can position the image in one place and keep it there or continually sweep the image between channels ..... and more.

Any input signal within the range 10 mV to 10 V AC should successfully operate the device, although obviously the best signal to noise ratios will be obtained with the larger values of input signal.

The overall signal gain of the Image Co-ordinator is approximately 6 dB, which allows for a unity gain output signal when the level pot is at approximately three-quarters of its rotation.

## Construction

The project consists of two printed circuit boards which together hold all components, switches, pots, etc apart from the nine LEDs. This makes construction a proverbial "doddle" and ensures high standards and a good chance of first time success.


Roughly speaking, the right hand board includes all components to the right hand side of the circuit diagram and similarly the left hand board includes all left side components. The left hand board also contains the PSU.

PCB mounting pots and switches are used throughout eliminating the use of flying leads, therefore cutting down the

possibility of pickup in the audio section. Any jumpers or wires only carry DC control voltages or power and are, therefore, of no problem. There is one exception, however, and that is the connection between the Auto Trig output on the right hand board and the Auto Trig input on the left hand board. This should be screened lead taken neatly, either under or over the boards, keeping it away from the PSU section.

The right hand board is double sided whilst that of the left hand is single sided with jump leads. Neither are too difficult to construct, although it is worthwhile when building up the project to construct each stage separately, testing as you go along eg start with the PSU then the automatic trigger, then the sweep, etc, etc. In this way any faults which develop can be traced to one particular area very quickly. Actually this constructional method is highly recommendable with any project! Test procedures are described in the section on Setting Up.

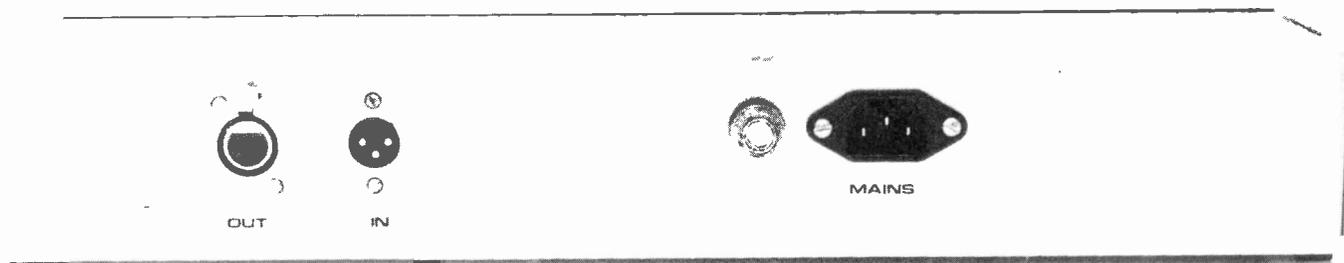IC sockets are advisable though not necessary, likewise cermet presets, although more expensive, present easier setting up and a high quality than their cheaper carbon colleagues.



The simple layout of the rear panel -- mains in, signal in, signal out.

## HOW IT WORKS

The main function of the unit is to create an impression of a stereo image from a single signal from a musical instrument. This is done by feeding the signal via IC4 (a quad op-amp) to 2 parallelled VCAs whose output amplitudes are controlled by an external control voltage. These VCAs form the output channels and are buffered by IC8a and b, providing drive for a stereo power amplifier. The stereo image is created simply by allowing the signal output from one channel to be greater than that from the other channel. The origin of the sound thus appears closer to the first side of the sound field than it does to the latter.

Interested readers who wish to know more about the VCA chips in question should refer to the March 1980 edition of ETI for a detailed discussion of the 1537A VCA.

IC5 provides phase split control voltages of 0 to -10 volts DC and -10 to 0 volts DC from a single input voltage of 0 to +10 volts DC. RV15 provides a depth control which simply limits the effect of the control voltages applied to the VCAs. IC5a inverts the DC control whilst IC5b inverts and also offsets it so that both outputs are in the range 0 and -10 volts, although 180° out of phase. IC5a also is a fairly high impedance buffer so as not to load the source.

SW1a gives selection of whichever source is required, there being three internal, sweep, manual and automatic trigger and one external method of controlling the stereo image. The corresponding LEDs are also switched in via SW1 allowing an indication of which function is in use at the switch and also at the function controls — see photographs. LED 1 is a special type of LED with an integral IC to provide an intermittent, flashing display. As this is in series with two other LEDs (2 and 6, 3 and 7, 4 and 8, or 5 and 9, dependent on SW1) then all three LEDs will flash on and off simultaneously.

External control of image is provided so that, for example a foot pedal can be used to control positioning of the applied signal within the stereo field. RV10 adjusts for various values of pots inside the pedal, although 100k lin is the nominal value.

RV12 acts as the manual pot in an identical fashion to an external control pedal pot but positioned on the front panel.

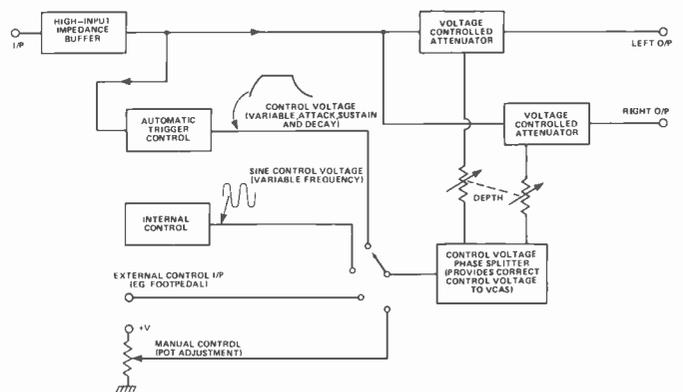
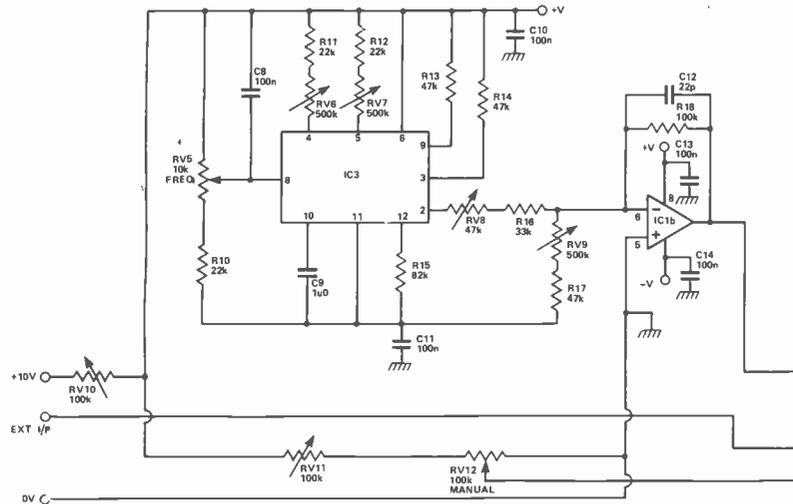
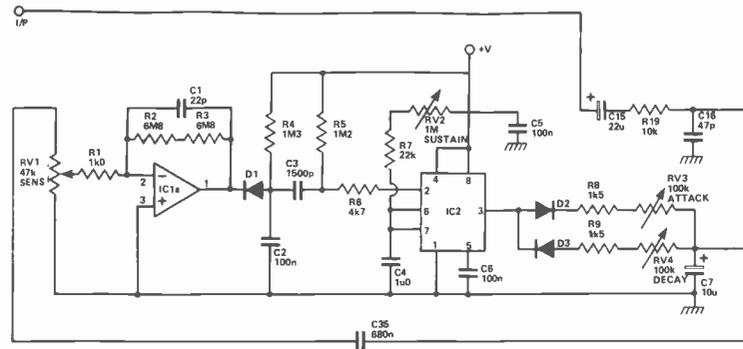


Fig.1. Block diagram of the Stereo Image Co-ordinator.

The signal switches which comprise SW1 a and b might be slightly difficult to get hold of so it is worthwhile taking your PCB along with you to make sure you get the right ones. Also see Buylines. Various other types are around but in our (dare we say it?) vast experience, these switches are by far the most superior for signal switches, which demand low resistance contacts and low noise levels. If you use the same push-fit knobs for the switches ie coloured transparent fronts you may like to do the same as us with the consecutive function marker LEDs and glue them into position inside the switch knobs so that the flashing indication is visible through the front of the switch. The square type of LEDs now available are ideally suited for this application. Alternatively the LEDs can be panel mounted vertically above the switch front. If LED 1, a flashing LED with integral IC, cannot be obtained an ordinary LED can be used in its place — but replace ZD1 with a suitable limiting resistor eg 560R.

The control marking LEDs should be positioned close to the corresponding controls in order that the user can clearly see which function is in use.

Finally use PCB pins for external connections so that when the two boards are fixed in their case side by side the nine links can be soldered into position along with input and output connections, without removing the boards.


## Setting Up

After the PSU section is complete, it can be tested to make sure that the correct supply rails, +15 V, 0 V and -15 V are obtained.

The components around the automatic trigger should be

inserted next (R1-9, C1-7, IC1 and 2, RV1-4 and D1-3). This can be tested by applying an AC signal of about 500 mV at its input on the left hand board whilst watching the voltage across C7. (All four pots should be mid-position). This voltage should increase from 0 V to about +12 volts then after a short time decrease back down to 0 V DC.

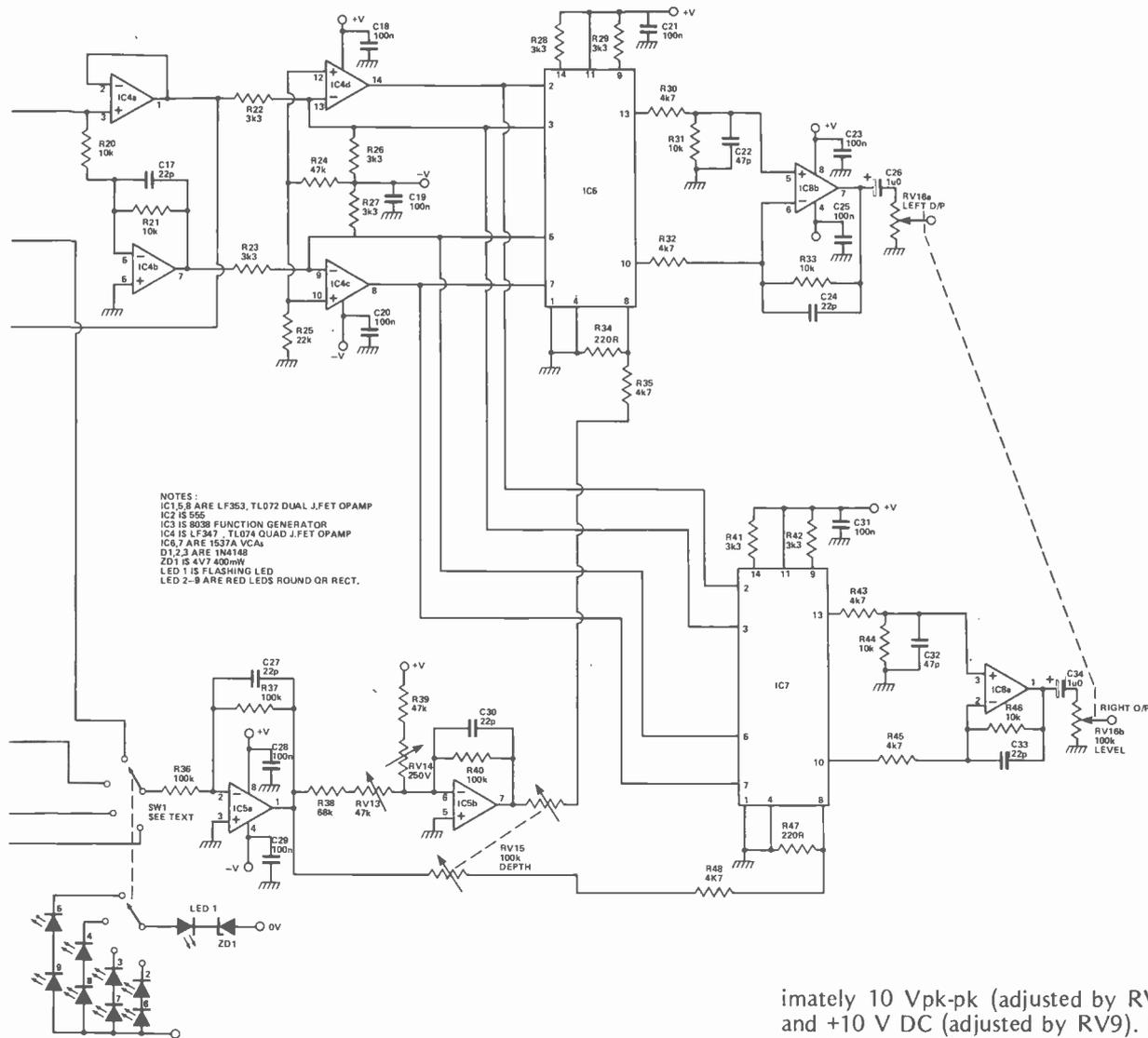
The sweep generator circuit can be built up next (R10-18, C8-14, IC3 and RV5-9) and tested. Set all pots and presets to mid-position. The DC output voltage at pin 7 of IC1 should be a low frequency near sine-wave oscillation approx-



NOTES:  
 IC1,5,8 ARE LF353, TL072 DUAL J-FET OPAMP  
 IC2 IS 855  
 IC3 IS 8038 FUNCTION GENERATOR  
 IC4 IS LF347, TL074 QUAD J-FET OPAMP  
 IC6,7 ARE 1537A VCA  
 D1,2,3 ARE 1N4148  
 ZD1 IS 4V7 400mW  
 LED 1 IS FLASHING LED  
 LED 2-9 ARE RED LEDs ROUND OR RECT.

Fig.2. (left) Circuit diagram. Note the orientation of LEDs connected to signal switch SW1.

Fig.3. (below) Power supply producing +15,0,-15 volts output.

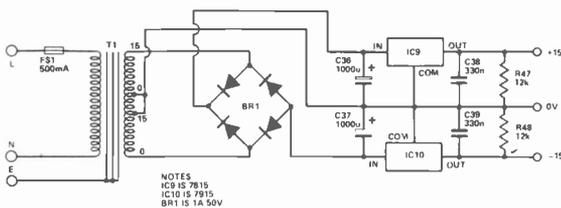

NOTES:  
 IC9 IS 7815  
 IC10 IS 7815  
 BR1 IS 1A 50V

## BUYLINES

The dual and quad op amps are available from the better mail order companies, if you cannot obtain them from your local stockist. Electrovalue supply the printed circuit mounting pots.

The signal switches were RS Components stock and these may have to be ordered through a retail stockist. They are worth the bother of obtaining.

The case is a West Hyde Developments type CL2CDJ. Finally the 1537A VCA chips can be obtained from Aphex Audio Systems UK Ltd., 35 Britannia Row, London N1 8QH.


imately 10 Vpk-pk (adjusted by RV8 and varying between 0 and +10 V DC (adjusted by RV9). By altering RV6 and RV7 which control the charge and discharge rates of capacitor C9 (which in turn controls the overall frequency and shape) the best setting can be found whereby RV5 controls the frequency of the sine wave between approximately 0.1 Hz and 10 Hz. Fairly careful adjustment of these two presets is necessary and it is a distinct advantage if a scope is available with a slow time base so that the waveform can be studied for purest sine wave.

The manual control function circuitry is simple consisting of only two components RV11 and RV12. The DC voltage at the wiper of RV12 should vary between 0 and 10 V dependent on wiper position and is adjusted by RV11.

The external control circuit is equally as simple but an external pot is necessary in the shape of a foot pedal. RV10 adjusts for a wiper voltage of 0 to 10 V DC for different values of pot. Alternatively a control voltage of 0 to 10 V DC relative to chassis can be fed in from some external control circuit.

The control voltage phase splitter is next to be assembled and set up (R36-40, C27-30, IC5 and RV13,14). With a known input voltage of 0 to +10 V DC (derived best from the manual pot by pressing the manual switch and varying the pot) the voltage at pin 1 of IC5 should be 0 to -10 V DC the op amp being a simple unity gain inverter. The output at pin 7 should be the same size pk to pk (adjusted by RV13) but 180° out of phase ie -10 to 0 V DC (adjusted by RV14).

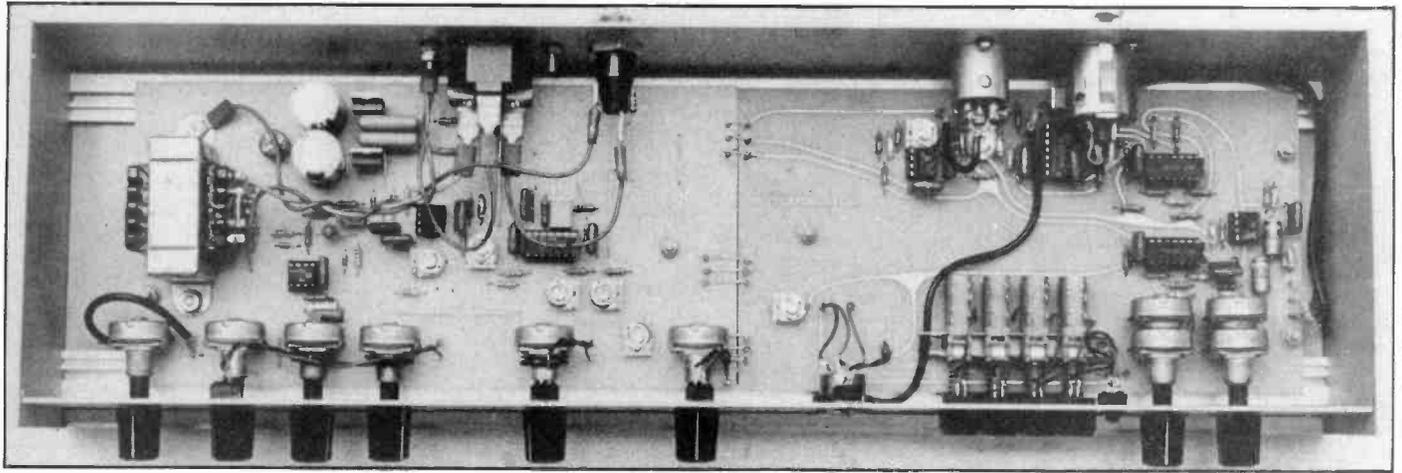There is no further setting up to be undertaken so the rest of the circuit can be installed and testing of the whole job undertaken.



Construction should pose no problems. The two PCBs hold almost all of the components and controls.

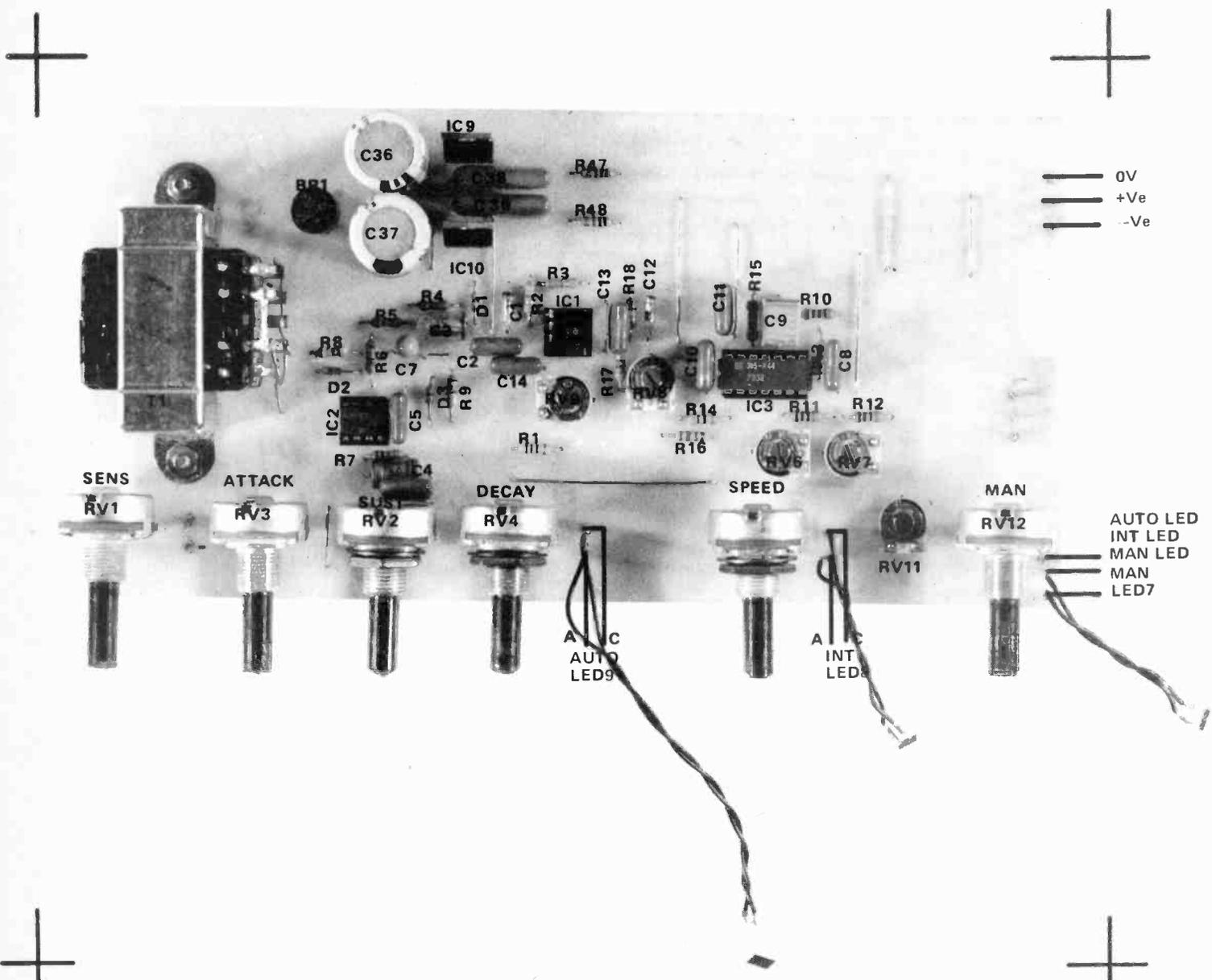


Fig.4. Component Overlay for the single sided board, which carries the power supply.

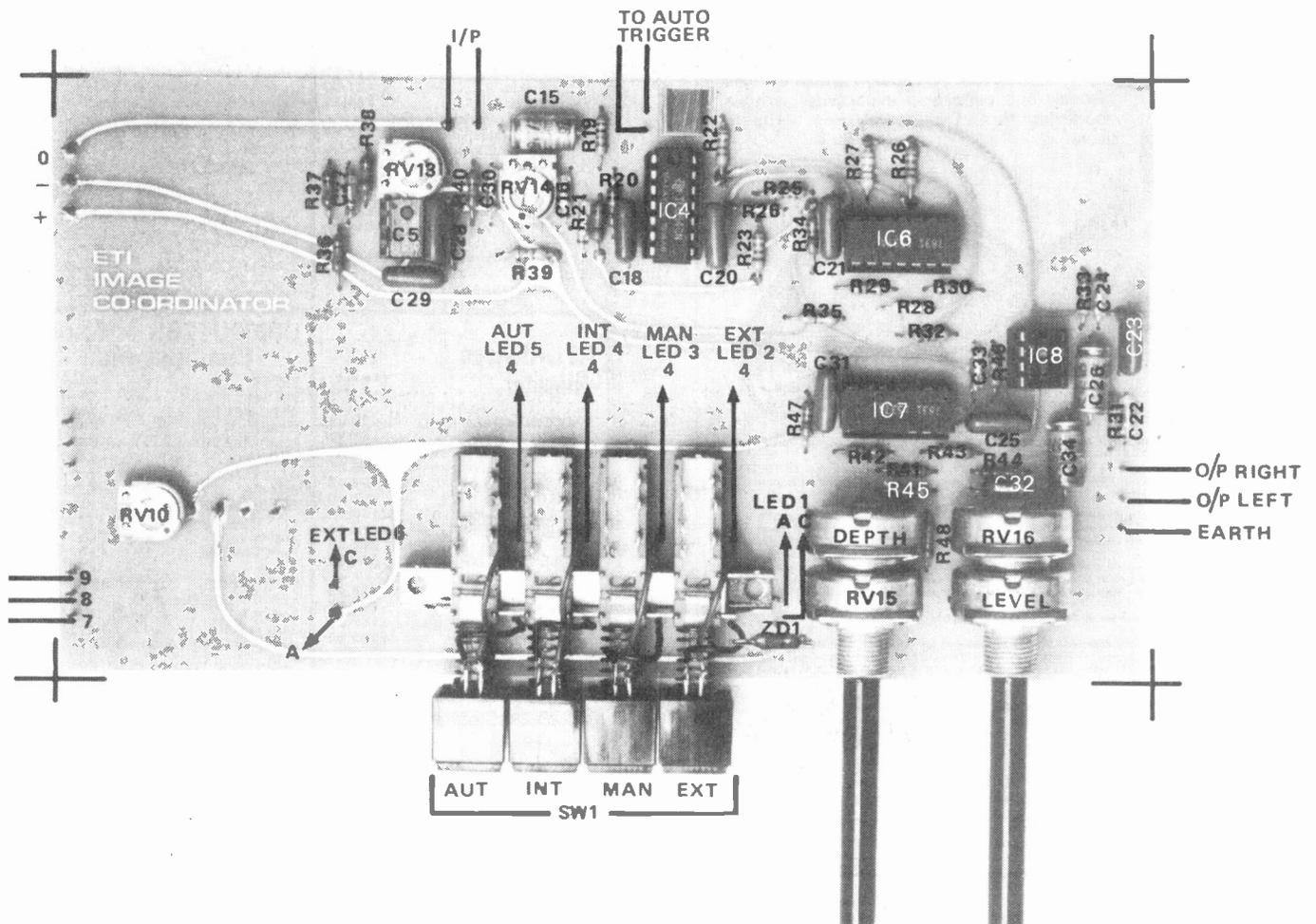


Fig.5. Component Overlay of the double sided board.

## PARTS LIST

### RESISTORS All 1/4W, 5%

R1	1k0
R2,3	6M8
R4,5	1M2
R6,20,32,35,43,45	4k7
R7,10,11,12,25	22k
R8,9	1k5
R13,14,17,24,39	47k
R15	82k
R16	33k
R18,36,37,40	100k
R19,20,21,31,33,44,46	10k
R22,23,26,27,28,29,41,42	3k3
R34	220R
R38	68k
R47,48	12k

### POTENTIOMETERS

RV1	47k log PCB mounting pot
RV2	1M0 lin PCB mounting pot
RV3,4,12	100k lin PCB mounting pot
RV5	10k lin PCB mounting pot
RV6,7,9	500k min horiz cermet preset
RV8,13	47k min horiz cermet preset
RV10,11	100k min horiz cermet preset
RV14	220k min horiz cermet preset
RV15	100k lin dual PCB mounting pot
RV16	47k log dual PCB mounting pot

### CAPACITORS

C1,12,17,24,27,30,33	22p polystyrene
C2,5,6,8,10,11,13,14,18,19,20,21,23,25,28,29,31	100n polyester
C3	1500p polystyrene
C4,9,26,34	1u0 25V electrolytic
C7	10u 16V electrolytic
C15	22u 25V electrolytic
C16,22,32	47p polystyrene
C35	680n polycarbonate
C36,37	1000u 25V PCB electrolytic
C38,39	330n polyester

### SEMICONDUCTORS

IC1,5,8	LF353, TL072 etc dual op amp
IC2	555
IC3	8038
IC4	LF347, TL074 etc quad op amp
IC6,7	1537A
ZD1	5V1 zener 400mW
LED 1	Flashing red LED
LED 2-9	Red LED
D1-3	1N4148

### MISCELLANEOUS

SW1a and b	4 off push button signal switches 2 pole
	C/O + appropriate hardware (see text)
T1	15-0-15 6VA mains transformer
FS1	500mA fuse + panel mounting holder
	Mains connector, input and output sockets case (see Buylines).

## BUILD YOUR OWN METAL DETECTOR VLF/TR VCO/TR IB/TR BFO ...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.



**Shadow VLF/TR.** Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target, now you can reject nails bottle caps even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.  
The head is thermally and capacitively shielded.  
4 modes: deepseeking VLF plus 3 TR discriminating ranges.  
Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI.  
Complete kit now only £87.87 inc. VAT & post!

**Individual parts:** Search head £21.33 PCB £8.80 Case £5.33 Adjustable shaft assy £5.10 LM393 £1.12. Manual (gives more info. than ETI article — and extra function) £1.12. All inc. VAT & post! (Other parts also available separately)

**Shadow TR/1B** (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. Complete kit £25 + VAT (post & Pkg. £1.80).

**Shadow TV/VCO.** An advanced version of the TR/1B. Use as a sensitive 1B machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. Kit price £29 + VAT (post £1.80).

Matching stereo headphones for all Shadow models £4.90 + VAT (post paid).

**Beginners BFO model.** A very detailed assembly manual and pre-wound coils make this an ideal first project. Simple high efficiency circuit. Full size (not a toy) but weighs only 300gms (10.5oz) with battery! FREE STETHOSCOPE HEADSET with every order. ALTS kit: £12 + VAT (post £1.80). Padded high Z headphones £4.50 + VAT (post paid).

**Shell Kit:** Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions £8.25 + VAT (post £1.50).

**ALTEK** (ETI), 1 Green Lane  
Walton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please. Phone (093 22) 44110 anytime!

## HAND HELD GAMES

Supersonic Mastermind	£21.00
Galaxy Invaders	£22.95
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
*Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
*DIGITS (like Mastermind)	£14.95

ALL GAMES HAVE SOUND EFFECTS EXCEPT \*

## ATARI video computer . . . . . £138

SPACE INVADERS CART	£29.95
STAR CHESS T.V. Game	£63.35
DATABASE Prog. T.V. Game	
NEW £89.95	
CHESSMATE 8 Level	NEW £59.95
CHESS CHALLENGER 7	£99.00
CHESS CHALLENGER 10	£160.00
VOICE CHALLENGER	£219.00
CHECKER CHALLENGER 2	£54.00
CHECKER CHALLENGER 4	£90.00
ZODIAC Astrology Computer	
NEW £29.95	
Snooze Alarm	£14.90
EL-MAC 5MHz Scope	£139.90
RADAT 10MHz Scope	£169.00

## The latest from the U.S.A. PINBALL WIZARD

★ Still available ★  
Featured in Nov. issue of E T I  
Home TV Game — B/W Kit  
Basic Kit **£28.90**  
Contains everything except box and controls  
Box & Controls — **£6.50**. Mains Adaptor — **£3.90**  
Play 7 games with 4 options on each game  
4-Pinball games 2-Basket, 1-Breakout  
Versatile car alarm kit **£18.90**  
See review in Hobby Electronics November  
CHROMA CHIME 24 tune door chimes kit **£10.75** Built **£15.95**  
C.B. Aerials and Accessories

## COMPUTERS — Home, Business etc.

PET 8K	£550.00
PET 16K	£670.00
SORCERER 8K	£747.50
SORCERER 16K	£874.00
SORCERER 32K	£887.75
SUPERBOARD II 4K	£172.45
UK 1.01 Kit 4K	£226.85
Built 4K	£286.35
TR80 Level 2 16K	£409.40
5 1/4" Floppy Drive	£288.65
Dual Drive	£506.00
NASCOM 2 Kit	£339.25
2 Built	£396.75
HEATH WH89	£1,805.00
HEATH WH14 Printer	£586.50
Softy Kit	£115.00
Softy Built	£138.00
Intelligent EPROM Programmer	

PRINTERS: FLOPPY DISC: BOOKS

S.A.S. Enquiries. Please allow up to 21 days for delivery. All prices inc. of VAT.

**N.I.C.**  
61 BROAD LANE, LONDON N.15 4DJ  
Day 01-808 0377; Eve 01-889 9736

<p><b>MOTORS.</b> 1.5V Motor motors 22P. Sub. min. 78g. 115V DC 3 rpm motor 52p. Replacements 8 track 12V DC motor 55p. Geared motor motors, 2 1/2 rpm, 75p. 115V AC 4 rpm motor 95p. Cassette motor, 5-6V DC ex. equip. 70p. 9V DC Cassette motor 95p. 6V Cassette motor, new standard jap. type £1.25.</p>	<p><b>RECORDING TAPE.</b> Low noise mylar, supplied unboxed: 7" 1200' £1.00, 7" 1800' £1.45, 10" 3600' £5.00. BLANK CASSETTES. C50 10 for £2.75, C90 10 for £3.85. LOW COST 1/2" TAPE SPLICER £1.95.</p>	<p><b>SPECIAL OFFER DEC TYPE BREAD-BOARDS.</b> Micro Dec 7" with 2 1/2 pin DIN carriers £3.95. Micro Dec "B" with 2 integral 16 pin DIN carriers £3.95. Both breadboards approximately half original selling price.</p>	<p><b>MOTOROLA PIEZO ELECTRIC TWEETERS</b>  3" direct radiating type £3.65 3.5" flush mounting super horn £4.50</p>	<p><b>TRANSFORMERS.</b> All 240V DC primary (postage per transformer is shown in brackets after price). MINATURE RANGE 6-0-6V 100ma, 9-0-9V 75ma, 12-0-12V 50ma all 70p each (15p), 12V 200ma 75p (15p), 0-6-0-6 280ma £1.20 (20p), 6V 500ma £1.10 (22p), 12V 2A £2.35 (45p), 12V 4A £2.85 (45p), 15-0-15V 1A £2.25 (45p), 20-0-20V 2A £3.55 (54p), 0-12-12-0-30V 2A £4.75 (54p), 20V 2.5A £2.35 (54p).</p>	<p><b>KRT101 M/METER.</b> 1,000 opv. 1KV AC/DC Volts, 150ma DC current, Resistance 0-25K, 0-100K, £4.35.</p>
<p><b>BUZZERS.</b> Miniature solid state type, 33 x 17 x 15mm, 70db at 3 volt, 15ma drain, operates at 1.5V DC 75p each. LDUB 12 volt buzzer 50 x 30mm 53p. Carriers 12V Miniature alarm siren £7.85, 6-volt version 55p. 12V DC SIREN, air metal relay type, high pitched wail, £8.50. Rotary alarm siren, 12V DC, red plastic unit with mounting bracket, 68 x 75mm £4.50.</p>	<p><b>TOOLS.</b> SOLDER Sucker, good suction, teflon nozzle, £4.99. Side cutters 5" £1.45, Pliers 5" £1.45. NEON DRIVER 8" LONG 55p. HIYAMA 16 pin IC test clip £1.85. 5 PIECE precision screwdriver sets, in individual handles, £1.05. JUMPER TEST LEAD SETS 10 pairs all leads with insulated cross each end 90p. CRIMPING TOOL, a combination type for crimping red, blue and yellow terminations also incorporates a wire stripper (p. 80) and wire cutter, insulated handles, only £2.30.</p>	<p><b>COPPER LAMINATED PRINTED CIRCUIT BOARD.</b> Fibreglass Single Sided type (approx. 2mm thick) 150x95mm 40p, 200x90mm 55p, 250x145mm 65p. Double-sided Fibreglass 1mm thick, 180x135mm 45p. PAXOLIN BASE TYPE: (2mm thick), 180x135mm 40p, 280x200mm 50p.</p>	<p><b>PIEZO TWEETERS.</b> require no crossover and can be used with systems up to 100 watts. Frequency response 3.8 to 20KHz.</p>	<p><b>TRIAK XENON PULSE TRANSFORMERS.</b> 11 (6P style) 32p, 11 plus 1 sub. min. pcb mounting 65p.</p>	<p><b>MMS5 M/METER.</b> 2,000 opv. 1KV AC/DC Volts, 100ma DC, Resistance 0-10K, 0-1MEG, £5.50.</p>
<p><b>RELAYS.</b> 2 types both operate on 12V DC, sealed plastic case types, 1-350 ohm with 2 make 5 amp contacts 75p, 2-1,000 ohm with 2 changeover 1 amp contacts 75p.</p>	<p><b>MICROPHONES.</b> Min. Tie pin. Del. ess. deaf aid and battery (supplied) £4.95. Low cost condenser ECM105 00ml, 600ohms, on/off switch standard jack plug £2.95. EM507 Condenser, uni, 600ohms, 30-10kHz, highly polished metal body, £7.95. DYNAMIC stick microphone dual imp., 600ohms or 20k, 70-15kHz, attractive black metal body, £7.75. EM506 Condenser, cardioid, uni, 600ohms or 50k, heavy chromed copper case, £12.95. DYNAMIC P.A. Mike, mobile radio etc., thumb switch 50k imp, £3.75. CASSETTE replacement microphones with 2.5/3.5 plugs £1.35. INSERT crystal replacement 35 x 10mm 40p. GRUINDIG Electrical units, with built in FET preamp 3-5V DC, £1.00.</p>	<p><b>TAPE HEADS.</b> Mono cassette, £1.75. Stereo cassette £3.90. Standard 8 track 50p. £1.95. 8SH MM 1330 1/2 track 50p. 6SR 5090 1/2 track £2.10. 7010 dual head assembly 2 heads both 1/2 track A/P with built in erase £1.25.</p>	<p><b>RANK ARENA</b> stereo cartridge preamplifier modules, suitable for magnetic cartridges, new, supplied with connection details, £1.95.</p>	<p><b>PROJECT BOXES.</b> Sturdy ABS black plastic boxes with brass inserts and lid, 75 x 56 x 35mm 65p, 95 x 7 x 35mm 75p, 115 x 9 x 37mm 87p.</p>	<p><b>VERO HAND HELD BOX.</b> White ABS, 24in x 3.7in tapered, with screws 68p each.</p>
<p><b>SPECIAL OFFER SEMICONDUCTORS.</b> 2K502 2CRs 18p, 8X504 opto isolator 25p, CA3130 95p, 1B800 50p, 7DA1151 25p, 741 22p, 723 35p, NE555 24p, AD161/2 70p pair, 2K3055 30p, 1H4005 10 for 35p, 80238 28p, 60430 28p, 7415 35p, 7814 75p, 71L 305 alpha numeric display £2.50, MAR6A 3mm LED displays 45p, Min. LEDs 30p, LEDs 0-2" CLEAR 15p, GREEN 12p, RED 10p, Infra-red clear LED 30p, MPU131 PUTs 40V, 200ma, 375mw 15p, 2N3773 £1.70, Texas R1038 (T03) Power trans. 50p, TAG4443 SCR 45p.</p>	<p><b>LED VU METERS.</b> Utilise sophisticated LED control circuit with adjustable rise and decay times via external capacitor. Spec: Response — 20Hz to 100KHz, Tolerance within ± 0.1, operates on 12-15V DC, 82mm long, 50mm high. MONO VERSION ..... £6.95 STEREO VERSION ..... £10.95</p>	<p><b>SWITCHES.</b> Sub. min. Toggle, SPST 8 x 5 x 7mm, 42p, DPDT (8 x 7 x 7) 55p. DPDT Centre off (12 x 11 x 9mm) 77p.</p>	<p><b>FINNED HEATSINKS.</b> Supplied undrilled 4mm thick, 27mm high, 75 x 124mm 60p, 150 x 124mm 95p. Smaller version 2.7mm thick, 75 x 108mm 48p. TRANSISTOR SOCKETS T05 or T08 5p each, T03 type 15p each.</p>	<p><b>VERO POTTING PLASTIC</b> boxes with lid and screws 70 x 50 x 20mm, black, 43p each.</p>	<p><b>CLIFF CLICKTEST.</b> 13 amp mains connector, ideal for workshop, etc., provides rapid and safe mains connection, tough moulded case and lid with neon indicator and fuse 15.15.</p>
<p><b>NEW STOCK ITEM</b> — We are now stocking Expo mini hand-held drills, these are a precision British-made tool, ideal for P.C. board drilling, model makers etc. They operate on 12V DC. Drill kit supplied in plastic hinged case, with drill and 21 accessories, drills, sanders, reamers, buffers, etc. complete kit only £14.25. Drill only £7.25. Drill stand to suit vertical drill press £12.95 (postage 86p).</p>	<p><b>16 pin D.I.I. SWITCHES</b> only 42p each.</p>	<p><b>RIBBON CABLE</b> 8-way single core miniature 22p per metre.</p>	<p><b>MURATA TRANSDUCERS, REC/SENDER.</b> MA041 40KHz £3.50 pair.</p>	<p><b>ANTEX SOLDERING IRONS.</b> All 240V AC. Model C 15 watts £3.95. Model ICX 17 watts £2.95. Model X25 25 watts £3.95. ST3 SOLDERING IRON STAND suits all AnTex Irons £1.66.</p>	<p><b>POWER SUPPLIES.</b> Switched type plugs into a 13 amp socket has 3-4, 5-6, 7.5 and 9 volts 0 c out of either 100 or 400ma. Resistance £3.45. HZ244R stabilised power supply 3-6-7.5-9V DC at 400ma, has polarity reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current £5.50.</p>

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for illustrated lists.

**PROGRESSIVE RADIO**  
31 CHEAPSIDE, LIVERPOOL L2 2JD  
ALL ORDERS DESPATCHED BY RETURN POST

*It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.*

**Understand Digital Electronics**

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

**DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00**

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

- Book 1** Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.
- Book 2** AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.
- Book 3** Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.
- Book 4** Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters, shift registers; half-adders.



**DESIGN OF DIGITAL SYSTEMS £12.50**

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



**Flow Charts and Algorithms**

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

**THE ALGORITHM WRITER'S GUIDE £4.00**

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

**Microcomputers are coming - ride the wave! Learn to program.**

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.



**COMPUTER PROGRAMMING IN BASIC £9.00**

- Book 1** Computers and what they do well, READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.
- Book 2** High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF... THEN, GO TO; limitations of computers; problem definition.
- Book 3** Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
- Book 4** Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

**THE BASIC HANDBOOK £11.50**

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

**FORTRAN COLORING BOOK £5.40**

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

**A.N.S. COBOL £4.40**

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

**GUARANTEE - No risk to you**

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

- .... Digital Computer Logic & Electronics @ £7.00
- .... Design of Digital Systems @ £12.50
- .... Algorithm Writer's Guide @ £4.00
- .... Computer Programming in BASIC @ £9.00
- .... BASIC Handbook @ £11.50
- .... Fortran Coloring Book @ £5.40
- .... A.N.S. Cobol @ £4.40

**FOUR WAYS TO PAY**

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M.Ch  Barclay/TrustC/Visa  Am Exp.  Diners
- 4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service

Card No. \_\_\_\_\_ Signed \_\_\_\_\_  
**THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE AIRMAIL**  
 Eur. N.A.F. Mid.E. add 1/2 to price of books: Jpn. Aus. N.Z. Pcf. add 1/2 elsewhere add 1/2

Name \_\_\_\_\_

Address \_\_\_\_\_

U.K. Delivery: up to 21 days (or send 50p for 1st cl.p.)  
 Cambridge Learning Enterprises, Unit 12 Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England


Proprietors: Drayridge Ltd, address as above. Reg. in Eng. No. 1328762

# STOCKTAKING CLEARANCE SALE!

Thousands of Modules must go at Trade Prices  
**DIRECT TO THE PUBLIC**  
**RING 01-689 4138**

and Order Now whilst stocks last

**LB3100SLC**  
**£20.80**  
+ £3.12 VAT

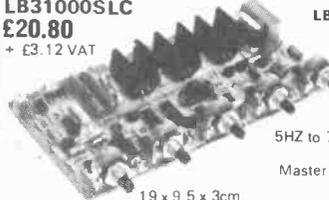

**LB3100SLC SOUND TO LIGHT/CHASER.**  
THE MOST ADVANCED SOUND TO  
LIGHT MODULE AVAILABLE, WITH  
AUTOMATIC SWITCHING TO CHASE  
UPON ABSENCE OF A MUSIC INPUT.


3 Channels, 1000w each. Fully fused.  
Very high input impedance. Electronic filters.  
5HZ to 70KHZ bandwidth. Operates from 1/4 to 300w  
sound input. Triac zero voltage triggering.  
Master Vol/Bass/Mid/Treble/Chase speed controls

19 x 9.5 x 3cm.

**LB3100SL SOUND TO LIGHT.**  
A SUPERB PERFORMING SYSTEM  
AT AN INCREDIBLY LOW PRICE.

3 channels, 1000w each. Fully fused.  
Very high input impedance. Operates  
from 1/4 to 300w sound input.  
Third order filters. Zero voltage fired.  
Master/Vol/Base/Mid/Treble controls.

**LB3100SL £14.89**  
+ £2.23 VAT

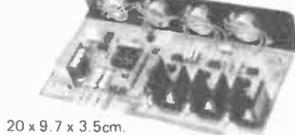


20 x 9.7 x 3.5cm.

**LB8100LC CHASER**

An 8 channel chaser with speed and  
chase return delay. Can be wired as a 4  
channel. (Rope light controller.)

**£18.43**  
+ £2.76 VAT

**LB8100LC**  
19 x 9.5 x 3cm

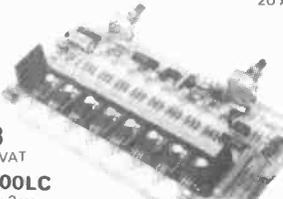


1000w per channel. CMOS circuitry.  
Zero voltage fired. Can be footswitch  
triggered. Additional modules can be  
cascaded to form 16, 24, 32 chan. ect

**LB4100LS SEQUENCER**  
LOGIC RANDOM SEQUENCER, WITH TWO  
SPEED CONTROLS OFFERING A WIDE  
RANGE OF EFFECTS.

4 channels, 1000w each. CMOS circuitry  
Zero voltage fired.

**LB4100LS**  
**£12.18**  
+ £1.83 VAT

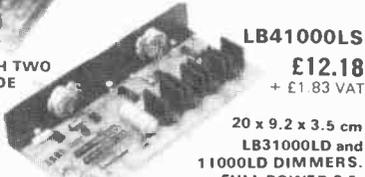

20 x 9.2 x 3.5 cm

**LB3100OLD and**  
**1100OLD DIMMERS.**

**FULL POWER 3 &**  
**SINGLE CHANNEL**  
**LIGHTING DIMMERS**

**FOR USE IN CLUBS/PUBS/**  
**THEATRES/SCHOOLS, ETC.**

1000w per channel. Fully fused phase controlled  
Full input and individual Triac filters.


**LB3100OLD £10.22** **LB100OLD £4.66**  
+ £1.53 VAT + 70p VAT

**NEW! LBACOI**

3-channel active crossover module with 18dB boost  
control of lift Bass mid or treble bands. Available with  
crossover frequencies of 200 or 300 and 2k or 3kHz  
(please specify) — **£12.46** + £1.87 VAT.

**LBPSUI ±15v supply for LBACOI £4.31** + 65p VAT

**LB3100OLD**

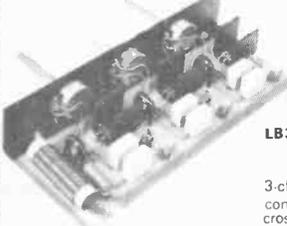

20 x 7.8 x 3.5

**POWER AMPS. 250, 150, 100 & 25w. etc.**  
**RUGGED TOUGH DEALING AUDIO**  
**POWER AMP MODULES.**

LB250	LB150	LB100	LB25
10HZ to 25KHZ S/N 110 dB THD 0.1% 0.5v SENS <b>£27.48</b> + £4.12 VAT	10HZ to 25KHZ S/N 110 dB THD 0.1% 0.5v SENS <b>£18.43</b> + £2.76 VAT	10HZ to 25KHZ S/N 110dB THD 0.1% 0.5v SENS <b>£12.66</b> + £1.90 VAT	20HZ to 60KHZ S/N 90 dB THD 0.07% 0.5v SENS <b>£7.79</b> + £1.17 VAT

**PREAMPS**

**LBPA3.** Complete stereo disco preamp  
system. Comprising of L&R deck mixers,  
mic mixer, deck and mic tone stages, mic  
auto fade over decks, PFL, output  
drivers and its own regulators.

**LBPA2.** General purpose 4  
chan. mixer/ tone stage.

**LBPA1.** Stereo  
Hi-Fi System



**LBPA 1 £13.57**  
+ £2.04 VAT

**LBPA2 £11.97**  
+ £1.80 VAT

**LBPA3-M (magnetic  
deck inputs) £21.36**  
+ £3.20 VAT

**LBPA3-M**  
20.4 x 9.5cm

**LBPA3-C (ceramic  
deck inputs) £21.36**  
+ £3.20 VAT

**LBRLD1.** Relay de-  
layed speaker connec-  
ting device placed  
between Amp &  
Speaker  
**£4.96** + 74p VAT




**LB250PS £17.04**  
+ £2.56 VAT

**LB150PS £12.52**  
+ £1.88 VAT

**LB100PS £10.22**  
+ £1.53 VAT

**LB25PS £7.79**  
+ £1.17 VAT

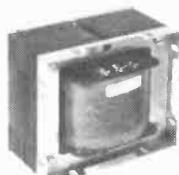

**LB250PS**

**YOU REQUIRE A BOARD THAT'S MIGHTY COMPETITIVE, RELIABLE,  
MANUFACTURED FROM THE HIGHEST QUALITY COMPONENTS, OF HIGH  
PERFORMANCE, TESTED AND INSPECTED, SUPPLIED WITH CONNECTION  
AND CCT, DGM AND GUARANTEED. IN TWO LETTERS YOU REQUIRE L & B.**

For your FREE catalogue, with full spec, send a 12p stamp  
Trade and Overseas inquiries welcome  
P/Packing FREE in the UK except power supplies  
(£1.00)

**L. & B.  
ELECTRONICS (ETI)**

**45 WORTLEY ROAD  
WEST CROYDON  
SURREY CRO 3EB  
TEL. 01-689 4138**



# Wilmslow Audio

**THE firm for speakers!**

**SEND 50P FOR THE WORLD'S BEST CATA-  
LOGUE OF SPEAKERS, DRIVE UNITS, KITS,  
CROSSOVERS ETC, AND DISCOUNT PRICE  
LIST.**

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS -  
CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD -  
DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMAN'S -  
HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS -  
KEF - LOWTHER - McKENZIE - MISSION - MONITOR AUDIO -  
MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS -  
RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNOY -  
VIDEOTONE - WHARFEDALE.

## WILMSLOW AUDIO

**SWAN WORKS, BANK SQUARE  
WILMSLOW, CHESHIRE SK9 1HF**

**Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF  
DRIVE UNITS, KITS, ETC.**

**Tel. 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI  
AND COMPLETE SPEAKERS.**

## CALCULATORS

**CASIO FX 501/502P PROGRAMMABLE Lcd**

(Featured Feb. ETI)

FX 501P 10+2 digit, 128 step, 11 memories	<b>£43.43</b>
FX 502P 10+2 digit, 256 step, 22 memories	<b>£50.83</b>
FA1 Adaptor cassette interface	<b>£17.35</b>
MASTERPACK 150+ programmes on tape with manual	<b>£13.87</b>
FX501P+FA1+Masterpack	<b>£68.65</b>
FX 502P+FA1+Masterpack	<b>£86.04</b>
*TEXAS TI51-111 32 step 10 memory	<b>£25.17</b>
TEXAS TI53 Lcd 32 step constant memory	<b>£22.57</b>
*TEXAS TI57 50 step 8 memory	<b>£23.44</b>
*TEXAS TI58 480 step 60 memory	<b>£58.22</b>
*TEXAS TI58C as above with prog retention	<b>£73.87</b>
*TEXAS TI59 960 step 100 memory mag card	<b>£150.39</b>
TEXAS PC100C Printer for 58/58C/59	<b>£136.48</b>
TEXAS PC100C IF ORDERED WITH 58/58C/59	<b>£130.39</b>



**PROGRAMME LIBRARIES FOR TI58/58C/59**

AVIATION	<b>£22.57</b>	<b>SCIENTIFICS 10 DIGIT Lcd</b>	
APPLIED STATISTICS	<b>£22.57</b>	CASIO FX100	<b>£13.00</b>
BUSINESS DECISIONS	<b>£22.57</b>	CASIO FX510	<b>£16.48</b>
ELECTRICAL ENGINEERING	<b>£22.57</b>	CASIO FX3200	<b>£18.22</b>
MARINE NAVIGATION	<b>£22.57</b>	CASIO FX5000 10 MEM	<b>£24.30</b>
MATHS/UTILITIES	<b>£22.57</b>	CASIO FX8100	<b>£20.83</b>
LEISURE	<b>£22.57</b>	SHARP EL5806 (8+2)	<b>£15.61</b>
STRUCTURAL ENGINEERING	<b>£54.74</b>	SHARP EL5808 (8+2)	<b>£13.87</b>
SURVEYING 11	<b>£54.74</b>	SHARP EL5812	<b>£16.48</b>
PC100C PAPER ROLLS TEXAS TP30250 10 OFF	<b>£19.09</b>	NATIONAL NS108	<b>£15.61</b>
BATTERY PACK'S state model or BP number	<b>£6.04</b>		
<b>SCIENTIFICS 8 DIGIT Lcd</b>			
CASIO FX68	<b>£16.48</b>		
CASIO FX80	<b>£12.13</b>		
CASIO FX81	<b>£11.26</b>		
CASIO FX330	<b>£13.87</b>		
CASIO FX2600	<b>£16.48</b>		
CASIO FX7100	<b>£20.83</b>		
SHARP EL503	<b>£11.26</b>		
TEXAS TI25 or TI35	<b>£16.48</b>		
TEXAS TI25	<b>£19.96</b>		
TEXAS TI42 M.B.A. 32 step 12 memory finance/stats	<b>£35.61</b>		
TEXAS TI PROGRAMMER	<b>£43.43</b>		
TEXAS TI44 Lcd constant memory statistical	<b>£25.17</b>		
TEXAS LITTLE PROFESSOR	<b>£11.26</b>		
TEXAS DATAMAN	<b>£17.35</b>		
TEXAS SPEAK AND SPELL	<b>£38.22</b>		
CASIO FX5000EP mains printer. List £196.48	<b>£136.48</b>		

**CLOCK CALCULATORS**

CASIO MQ6 micro card watch in leather case	<b>£17.35</b>
CASIO PW81 hourly chime/ alarm	<b>£13.00</b>
CASIO ML81 hourly chime/ 2 alarm/ timer/ date/ musical	<b>£19.09</b>
CASIO ML71 card version of ML81 with 1 alarm	<b>£19.09</b>
CASIO AQ1500 day/ date/ stopwatch	<b>£13.87</b>
CASIO AQ2000 special low price	<b>£17.35</b>
CASIO AQ2200 hourly chime/ alarm/ calendar/ stopwatch	<b>£17.35</b>
CASIO MQ12 card version of above	<b>£17.35</b>

TELEPHONE ANSWERING MACHINES twin cassette  
PRICES EXCLUDE V.A.T. PLEASE ADD 15% PACKING & DELIVERY FREE

**CALCULATOR SALES & SERVICE**

**Arrow Works, Arrow Road, Redditch B98 8NN**  
**Tel. Redditch (0527) 43169**



# AUTOMATIC PORCH LIGHT

Take yourself home in style and don't be left in the dark with this ingenious Reader's Design from Mr P. Dakin

An automatic porch or outside light is a valuable asset to people who want their homes to have that 'some one about' look, and the convenience of the front door or drive lit when returning home during the hours of darkness. The circuit to be described will turn on a lamp when it is dusk and turn it off at dawn. There is, of course, a master On-Auto Off switch. The unit will handle lamps up to 500 W, with a 240 V supply, 250 W with a 115 V supply, and in the off state draws approximately 20 mA. The heart of the unit is the common 555 switching IC, but used in an *uncommon* configuration.

## Construction

Fit all the components except C3, which is fitted after testing. The board is designed to fit into a MK type 2140 surface mounting wall box. The LDR may be mounted into the blanking plate MK type 3827, as shown in Fig.2, or remote from the unit.

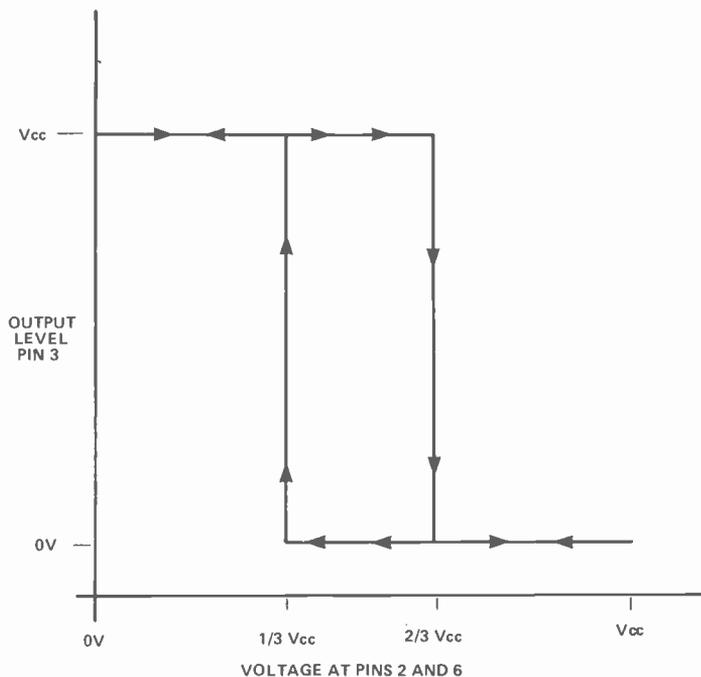


Fig.1. IC1 is used as a level detector with hysteresis.

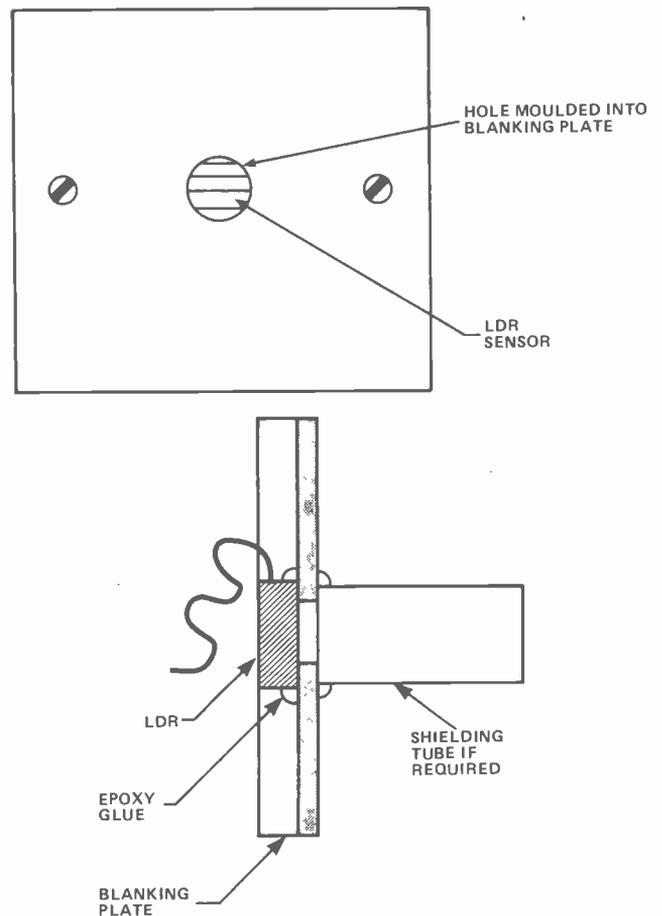


Fig.2. The LDR is mounted in the blanking plate (top). A shielding tube may be fitted if necessary (above).

## Setting Up and Testing

Having built the board, check for solder splashes and dry joints. Set RV1 to mid-position, connect a lamp, the LDR and the mains. A WORD OF CAUTION, there is mains and rectified mains on the board, also the tab of the thyristor is connected to its anode. Be careful where you put fingers and voltmeter.

Now switch on. If the LDR is in a light area, nothing will happen. Darken the LDR and the lamp will light. Increase the light around the LDR and the lamp will extinguish. The exact setting of RV1 will depend on the

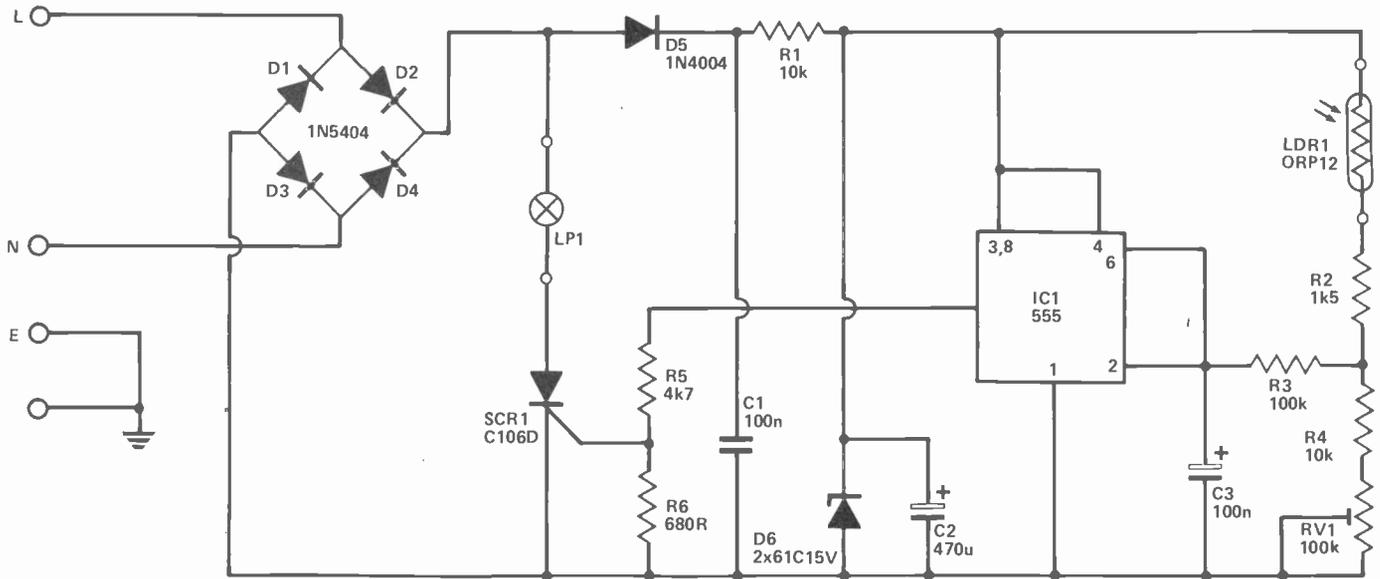


Fig.3. Circuit diagram. A common or garden 555 is at the heart of the unit.

## HOW IT WORKS

Figure 3 shows the full circuit diagram of the unit. Light Dependent Resistor LDR1 is the sensor for the system. Its resistance depends upon the amount of light falling on it, the more light the lower its resistance. IC1 is used as a level detector with hysteresis. The 555 has inbuilt resistance levels of  $\frac{1}{3}V_{cc}$  and  $\frac{2}{3}V_{cc}$ . When the voltage on pins 2 and 6 rises above  $\frac{1}{3}V_{cc}$  the output, pin 3, swings low, and as the voltage falls below  $\frac{1}{3}V_{cc}$  the output goes high as shown in Fig.1.

RV1 is adjusted so that the unit switches on at the required light level. R3 and C3 form a 10 S time constant. This is the time it takes for the voltage on pins 2 and 6 to rise to  $\frac{1}{3}V_{cc}$ , assuming C3 charges from 0 V, and is included to reduce the possibility of false triggering, eg passing car headlamps, or children with torches! The supply for the circuit is via D1-D5, R1, and regulated by D6. C2 is supply smoothing.

The external lamp is switched by the thyristor SCR1. A thyristor was chosen because it is easier to trigger than a triac, and does not have a radio frequency interference problem in this configuration. The disadvantage of this method is that a diode bridge, D1-D4, is required, and the bridge must be capable of handling the lamp current.

It was found with early prototypes that mains transients could cause the lamp to flicker when nearing the lower (switch on) threshold level. A comprehensive filter circuit has been included, comprising D5, R1, C1 and C2.

Any high frequency spikes on the mains supply will pass via D1-D5 and be decoupled to the negative side of the supply by C1. The impedance of C1 being smaller than the value of R1. Should the mains voltage fail or fall for a few cycles, C2 would try to discharge through R1 and the lamp circuit. D5 and C2 hold the supply high for this short period, D5 being reversed biased.

The thyristor used is the C106D sensitive gate type. This requires 0V8 cathode to gate, and 200 V gate current. It is triggered from the output of the 555. R5 and R6 form a potential divider to give approximately 2 V cathode to gate, sufficient to ensure reliable triggering. R5 also ensures the gate returns to the same potential as the cathode when the output of the 555 goes low, thus ensuring the thyristor remains untriggered.

The circuit may be modified for 115 V operation by reducing the value of R1 to 4k7 (2 W). The other components remain the same. However, because of the reduction in the supply voltage, the maximum wattage that can be switched is reduced to 250 W the current through the diode bridge D1-D4 and thyristor SCR1 being 2 A maximum.

## BUYLINES

All components used are standard and should be readily available from most mail order stockists.

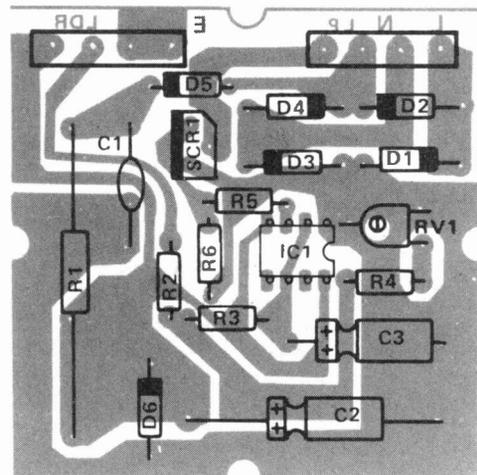


Fig.4. Component overlay. THERE IS MAINS AND RECTIFIED MAINS ON THIS BOARD.

## PARTS LIST

Resistors All $\frac{1}{4}W$ except where stated	
R1,4	4k7 4W (2W for 115V)
R2	1k5
R3	100k
R5	4k7
R6	680R
Potentiometers	
RV1	100k
Capacitors	
C1	100n 400V polyester
C2	470u 25V electrolytic
C3	100u 25V electrolytic
Semiconductors	
D1-D4	1N5404 or similar
D5	1N4004 or similar
D6	BZX61 C15V
SCR1	C106D or similar
IC1	NE555
LDR1	ORP 12

Miscellaneous  
PCB, PCB mounting terminal block RS No. 423-762, Surface mounting box MK list No. 2140, Blanking plate for box MK list No. 3827, 2 screws M3.5 Pan Head, Small heat sink (aluminium 1mm x 25mm x 10mm).

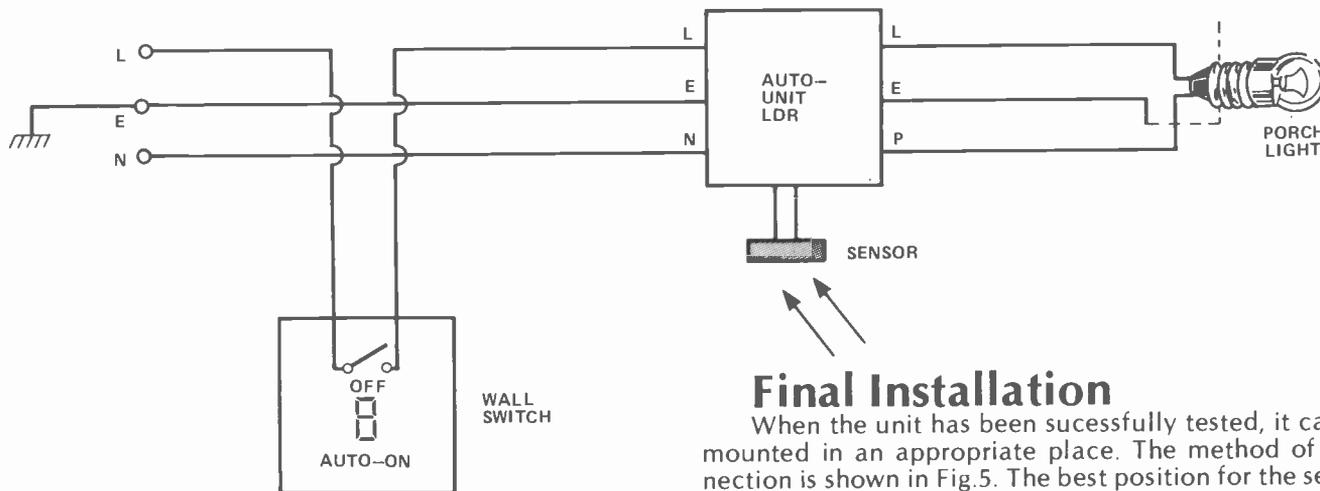


Fig.5. Method of connection of the unit to the house mains wiring.

location of the sensor, and is best set when the unit is finally installed. RV1 and R4 values give ample adjustment for most situations. If however, the adjustment of RV1 is insufficient in the clockwise direction, the value of R4 can be increased to 47k. When all is satisfactory, fit C3. Recheck that the unit does not respond to short dark or light periods.

## Final Installation

When the unit has been successfully tested, it can be mounted in an appropriate place. The method of connection is shown in Fig.5. The best position for the sensor is an outside location away from the influence of traffic, street lamps and neighbours' lights. If a suitable location cannot be found, a small tube to shade the sensor can be fitted which will increase its directivity, as shown in Fig.2. This completes the construction of the unit.

If the completed unit is mounted externally, some form of weather proof seal must be made between the box and the blanking plate. The best type of sealer to use is silicone bath sealer. Spread a small amount on the mating surfaces of the box and tighten down the plate. The sealer will harden and prevent water entering. **ETI**


## AT BLINKIN' LAST! COLOURBOARD II

THE NEW 50HZ COLOUR VERSION OF OHIO SCIENTIFIC'S SUPERBOARD II IS HERE AND LIKE A TON OF BRICKS DOWN CRASHES THE PRICE OF STANDARD SUPERBOARD II.

50HZ UK BLACK AND WHITE SUPERBOARD II  
 £159.95 + VAT POST FREE  
 COLOURBOARD-II £205 + 15% VAT
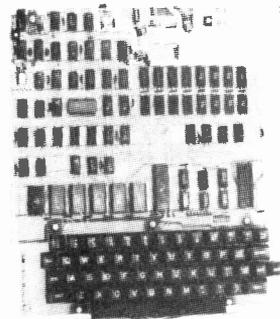
### THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST

- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★
- ★ If bought with superboard or colour board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT.
- ★ Modulator and power supply kit £5.95 (£9.95). 4K extra ram £19 (£24).
- ★ Case £19 (£24). Cassette recorder £13 (£15).
- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★




### SINCLAIR PRODUCTS



PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, mains adaptor £6.88. PDM35 £34.23, mains adaptor £4.20, case £2.07. DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models — rechargeable batteries £7.99, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95. New SC110 10MHz oscilloscope £144.95.

### COMPUTER GAMES

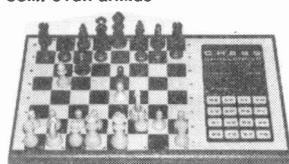

Chess challenger 7 (illustrated) £84. Chess champion 6 £49.95. Checker challenger 2 £46. Star Chess £62. Grandstand video entertainment computer £79.95. Videocarts £12.60. Philips G7000 Videopak home computer £139. Video paks £12.95. Atari Videocomputer £129. Cartridges £14.85 (except chess £43.95 and backgammon £33.95).


## SWANLEY ELECTRONICS

Dept. ETI, 32 Goldslee Road, Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13%. Official credit orders welcome.
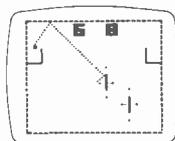
### TV GAMES

AY-3-8500 chip £5.95. Kit £4.26. Stunt cycle AY-3-8760 chip £13.71, kit £4.95. 10 game paddle 2 AY-3-8600 chip £19.25, kit £7.03. Racing car chip AY-3-8603 £13.63. Modified shoot kit £5.28. Colour generator kit £9.05.



### MAINS TRANSFORMERS

6-0-6V 100ma 80p, 1 1/2 £2.60, 9-0-9V 75ma 80p, 1a £2.40, 2a £3.94, 12-0-12v 100ma 80p, 1a £2.90, 15-0-15V 1a £3.15.

### JC12 and JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 watts £2.08. JC20 10 watts £3.54.

### CONTINENTAL SPECIALITIES PRODUCTS

EXP300 £6.82, EXP350 £3.65, EXP325 £1.84, EXP650 £4.14, EXP48 £2.64.

### STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. TTL computer supplies 5V 2A £3.13 (£7.44), 5V 4A £5.12 (£12.60), 8-way types 3/4 1/2 6/7 1/2 9/12/15/18V 100ma £1.84 (£2.60), 1A £3.30 (£6.50), 2A £5.60 (£9.84). Variable voltage models 2-18V 100ma £1.84 (£2.60), 1-30V 1A £3.30 (£6.75), 1-30V 2A £5.60 (£12.10).

### PRINTED CIRCUIT MATERIALS

PC etching kits — economy £2.42, standard £4.76, 40 sq ins pcb 49p, 1 lb FeCl £1.50. Etch resist pens — economy 50p, dalo 84p. Drill bits 1/32" or 1mm 34p. Etching dish 92p. Laminate cutter £1.20.

### BI-PAK AUDIO MODULES

AL30A £4.53, PA12 £9.31, PS12 £1.75, TS38 £2.70, S450 £27.90, AL60 £5.62, PA100 £19.24, SPM80 £5.26, BMT80 £6.06, Stereo 30 £23.94, AL80 £8.56.




### COMPONENTS

IN4148 0.09p, 1N4002 2.9p, 723 14 di 33p, NE555 8 di 24p, 741 8 di 18p, bc547, bc549, bc182, bc184, bc212, bc214, bc548 5.9p, 1118, np32c 36p, tip11c 40p, bc132 27p, plastic equiv bcy72 4.5p, fuses 20mm x 5mm cartridge .15, .25, 5, 1, 2, 3, 5Amp quickblow 1p, resistors 5% 1/4W £12 10R to 10M 1p, 0.8p for 50+ of one value, polyester capacitors 160V .015, .068mf 2.6p, 1mf 4.0p, 01mf 3.0p, .022, .033mf 3.3p, .047mf 4.0p, 15, .33mf 4.9p, .47mf 6.0p, polystyrene capacitors E12 63V 10 to 1000pf 3p, 1n2 to 10n 4p, ceramic capacitors 50V E6 22pf to 47n 2p, electrolytic capacitors 50V 5, 1, 2mf 5p, 25V 5, 10mf 5p, 16V 22, 33mf 5p, 47, 68mf 3.5p, 100mf 5p, 330, 470mf 9p, 1000mf 11p, zeners 400mw E24 2V7 to 33V 7p, preset pots sub-miniature 0 1W horiz or vert 100 to 4M7 7p, potentiometers 1/4W 4K7 to 2M2 log or 1in single 27p, dual 71p, 1/4" red LEDs 9.7p, ic sockets 8 di 8.7p, 14 di 10.1p, 16 ki 12p.
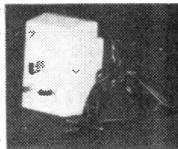
### BATTERY ELIMINATORS

3-way types with switched output and 4 way multi jack — 3/4 1/2 6V 100ma £2.87, 6/7 1/2 9V 300ma £2.84, 100ma radio types with press-stud connectors 9V £3.77, 6V £3.77, 4 1/2V £3.77, 9+9V £4.99, 6+6V £4.99, cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £3.57, fully stabilized type 3/6/7 1/2 9V 400ma £5.97, car converters 12V dc input, output 7 1/2V 300ma £1.19, output 3/4 1/2 6/7 1/2 9/1 1 1/2 V 800ma £2.76.



### BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4 1/2V £1.49, 6V £1.49, 9V £1.49, 4 1/2+4 1/2V £1.92, 6+6V £1.92, 9+9V £1.92, cassette type 7 1/2V 100ma with din plug £1.49, heavy duty 13-way types 4 1/2 6/7 1/2 8 1/2 11 13 14 17 21 25 28 34 42V 1A £5.52, 2A £8.80, car converter input 12V dc, output 6/7 1/2 9V 1A stabilized £1.35.

### S-DECS AND T-DECS

S-Dec £3.79, T-Dec £4.59, u-Dec £4.69, U-Dec £7.16, 16 di adaptor £2.31.

# POWERFETS

Some day all power transistors will be made this way!

	CHAN	VDS max V	ID max A	PDISS max W	RDS(ON) Type (Ω)	Case	Price
BD512	P	60	1.5	10	†(3.5)	T0202	85p
BD522	N	60	1.5	10	2.5	T0202	80p
VMP4	N	60	2.0	25	2.0	380-50E	1250p
VN10KM	N	60	0.5	1.0	4.0	T092†	55p
VN64GA	N	60	12.5	80	0.3	T03	750p
VN67AF	N	60	2.0	15	2.0	T0202	75p
2SJ49	P	140	7.0	100	1.0	T03	395p
2SK134	N	140	7.0	100	1.0	T03	395p

†1/p protected (four selection: VN/VM, 96-page Design Cat. 20p. Heat clips T0202 12p, T092 8p.

**MANUFACTURERS/DESIGNERS.** We will be stocking Powerfets by IR, TI and Interil as well as by Hitachi, IIT and Siliconix. We can advise you on applications and type selection, supply samples and quantities.

**REMEMBER** Powerfets need virtually no drive current, switch in nanoseconds, and are 2nd breakdown free, etc. etc.

Part No.	Price	Description
CA3026	70p	HI-FI ON TWO CHIPS
CA3080E	70p	HA12017 (Preamplifier 0.001% distortion 83dB S/N in phone application) 99p
CA3140E	38p	HA1397 (Poweramp 20 watts in 8Ω 0.02% distortion (typ) 195p)
DAC08	250p	Both with data and circuits
DM2502	555p	<b>POWERFET AMPLIFIER</b> semiconductor sets. High power designs offering very low distortions.
LM308	50p	'80 watt (†THD 0.008%) £8.75
LM3900	43p	'120 watt (†THD 0.004%) £16.65 (with circuits)
MC3401	30p	into 8Ω (at all powers and all audio frequencies)
NE529	145p	<b>ADVANCED DISCRETE BIPOLARS</b>
NE555	25p	2SA1083(P) (80v, 100mA)
SAD1024	1050p	2SC2545(N) (NFO, 2dB 19p)
SD532	30p	2SA872(P) 90v 16p
TDA1022	600p	2SC1775A(N) 120v, 50mA, 17p
TL081	29p	2SB716A(P) 140v 19p
TL082	55p	(low Cob, 1p8 typ = low distortion)
2102	80p	
4011B	17p	
709	15p	
710	25p	
733	50p	
741	18p	
78L05/12	29p	

**SCOPE TRACE DOUBLER P.C.B.**  
Built C/W shift, chan select, choprate controls and instructions. Useful display from DC to 10MHz. Runs from 9v battery £9.95

**VCA** High quality design offers attenuation from 0dB to -90dB S/N 90dB THD 0.01%, B/W DC to 100KHz. Complete component set and circuit £2.25


TL081CP 23p!  
Sp. price 'til 30/6/80.  
2µ S ADC chip set (DAL08, DM2502, NE529) with data £9  
FX309 ('Single bit' A/D, D/A. Store speech in RAMs) with data £7.50

Brief data on everything in new lists S.A.E.  
P&P 30p. Mail order only. Prices inc.

## J. W. RIMMER

Tel. 01-800 6667  
367 GREEN LANES  
LONDON N4 1DY

# MONITORS MONITORS MONITORS

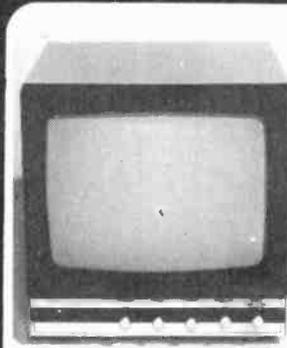

Uncased from 3" to 12"  
Cased from 5" to 20"

Semi professional or professional available from stock.

Monitor PCB's including Transformers and Tubes also in stock.

Phone or write for details.

## CROFTON ELECTRONICS

Crofton Electronics Limited  
35 Grosvenor Road, Twickenham, Middx.  
Tel: 01 891 1513

MAIL ORDER ONLY

## DELTA TECH & CO.

62 NAYLOR ROAD, LONDON, N20 0HN

Please add 35p for P&P

<b>RESISTORS (5% E12)</b> 10 Ohms to 10Mohms <b>PRESETS (15W HORIZONTAL)</b> 100 Ohms to 2 Mohms <b>POTENTIOMETERS (1/4W)</b> Linear & Log Scales 4.7k Ohms to 2.2Mohms <b>VEROBOARDS (1" COPPER)</b> 2.5" x 5" 3.75" x 5" <b>ZENER DIODES (400mW)</b> 5V6 5p* 2V7 to 33V <b>POLYSTYRENE CAP (50V)</b> 10 pF to 1000 pF <b>CERAMIC CAP (50V)</b> 33 pF to 4700 pF <b>POLYESTER CAP (100V)</b> 1 nF to 68 nF 100 nF 150 nF 220 nF 330 nF 470 nF 1µF 680µF 13p 1µF 2.2µF 22p 3.3µF 15p* 4.7µF 15p* <b>ELECTROLYTIC CAP (µF/V)</b> 1/25 to 47/25 6p 68/25, 100/35 8p 150/25, 160/25 220/25 10p 640/16 5p* 1000/10 5p* 1000/25 22p 1500/25 20p* 2200/6 3V 10p*	7812/15 65p 7818/24 65p 7905 75p 7912/15 75p 7918/24 75p <b>DIL SOCKETS</b> 8 pin *7p 14 pin *9p 16 pin *10p 18 pin 16p 22 pin 20p 24 pin 21p 28 pin 25p 40 pin 35p <b>DIODES</b> BY127 12p OA47 8p OA91 6p OA200 6p OA202 9p 1N916 5p 1N4148 4p 1N4001/2 4p 1N4003 5p 1N4004/5 6p 1N4006/7 8p 1N5400 13p 1N5401 14p 1N5402 15p 1N5404 16p	LF351N 44p LF356N 85p LM301AN 30p LM308N 55p LM318N 120p LM318H 120p LM324N 57p LM339N 52p LM348N 90p LM377N 175p LM380N 90p LM381N 120p LM382N 130p LM1310N 115p LM3900N 55p LM3909N 75p MC1496P 80p NE531 110p NE555 22p NE556 55p NE566 140p TBA641B 200p TBA800 75p TBA 810S 110p ZN414 100p ZN1034E 220p CMOS AE 4000 16p 4001 22p 4002 15p 4006B 70p 4007 *13p 4008 80p 4009 40p 4010 44p 4011 22p 4012 20p 4013B 35p 4014 80p 4015B 75p 4016 44p 4017 50p 4018 80p 4019 45p 4020B 95p 4021 85p 4022 *70p 4023 22p 4024B 50p 4025 20p 4027 45p 4028 60p 4029 82p 4030 *35p 4035 107p 4041 75p	4042 70p 4043/4 88p 4047 92p 4048 55p 4049 35p 4050B 44p 4066 50p 4069 *16p 4070B 20p 4071/2 20p 4072 20p 4073 20p 4081/2 20p 4086 80p 4089 80p 4095 100p 4511B *70p 4516/8 100p 4520/8 70p 7400/1 13p 7402/3 13p 7404/5 13p 7406 18p 7407 25p 7408 16p 7409 13p 7410 13p 7411 18p 7412 15p 7413 23p 7414 39p 7416 20p 7417 28p 7420 15p 7421 15p 7422 17p 7427 20p 7428 25p 7430 14p 7432 17p 7433 24p 7437/8 13p 7440 10p 7441 55p 7442 *32p 7443 50p 7444 90p 7445 64p 7446 65p 7447A 45p 7448 62p 7450 10p 7451/3 13p 7454 10p 7460 13p 7470 20p	7472 19p 7473 *16p 7474 *17p 7475 26p 7476 25p 7480 32p 7485 80p 7486 18p 7490 *22p 7491 57p 7492 30p 7493 *20p 7494 30p 7495 40p 7496 45p 7497 200p 74100 60p 74105 43p 74107 22p 74109 40p 74110 40p 74118 90p 74121 22p 74122 30p 74123 45p 74125/6 37p 74132 48p 74141/5 46p 74150 55p 74151 47p 74153 43p 74154 66p 74155 46p 74156 42p 74157 38p 74160 70p 74161 55p 74162 60p 74163 45p 74164/5 56p 74166 85p 74173 70p 74174/5 55p 74177 60p 74180 35p 74181 80p 74182 45p 74190 50p 74191/2 50p 74193/4 50p 74195/6 70p 74197 54p 74198 100p 74199 90p	AC128 20p AC153 25p AC176 22p AC187/8 22p AC187K 30p AD149 65p AD161/2 40p AF114 30p AF124 35p AF125/6 35p AF127 35p AF139 40p AF239 44p BC107/8 10p BC109 10p BC117 23p BC142/3 30p BC147/8 10p BC149 10p BC157/8 12p BC159 12p BC167 14p BC169C 13p BC171 10p BC173 8p BC177/8 16p BC179 16p BC182B 10p BC182L *7p BC183B 10p BC184 10p BC186 25p BC207/9 13p BC212 10p BC212L *7p BC213L 10p BC214 10p BC214L *8p BC238 18p BC261B 14p BC301/3 32p BC328 17p BC338 17p BC461 40p BC477 23p BC478 23p BC261B= SUPER BC478 BC479 23p BC547/8 12p BC549 12p BC557/8 14p BC559 14p BCY70 18p BCY71/2 18p BD115 58p	BD121/3 75p BD124 81p BD131/2 35p BD135 to BD140 35p BF178 30p BF180 34p BF181 8p BF183 34p BF184/5 25p BF194 12p BF195/6 12p BF197 12p BF224B 14p BF244B 35p BF258 28p BF259 40p BFR39 28p BFR79 32p BFX29 25p BFX84 25p BFX87/8 25p BFY50/1 20p BFY52 22p BFY39 50p BSX19 12p BSX20 22p BU205 150p BU208 210p MJ2955 110p MJE340 52p MJE2955 110p MJE3055 80p MPF102 45p MPF103/4 40p MPF105 40p MPF106 45p MPSA06 26p MPSA56 26p MPSU06 60p OC28 92p OC35 92p TIP29 40p TIP29B 42p TIP30 40p TIP30B 42p TIP31/2 40p TIP33 65p TIP33C 70p TIP34A 75p TIP35E 200p TIP36A 200p TIP36B 210p TIP41A 60p TIP42A 60p TIP2955 70p	TIP3055 55p ZTX107/8 12p ZTX109 12p ZTX300/1 14p ZTX302/3 18p ZTX304 23p ZTX311 18p ZTX341 22p ZTX500/1 15p ZTX502 20p ZTX503 17p ZTX504 24p 2N696/7 20p 2N698 20p 2N706 14p 2N914 20p 2N918 35p 2N1131 20p 2N1302/3 35p 2N1304 35p 2N1306 30p 2N1613 25p 2N1711 13p 2N1893 25p 2N2217 18p 2N2219 23p 2N2222A 23p 2N2369 17p 2N2484 25p 2N2646 46p 2N2904/5 21p 2N2966/7 21p 2N2926G 10p 2N3053 20p 2N3054 40p 2N3055 45p 2N3055B 50p 2N3442 140p 2N3702 to 2N3711 11p 2N3772 120p 2N3773 250p 2N3819 21p 2N3820 40p 2N3823 70p 2N3866 *55p 2N3903/4 15p 2N3906 15p 2N4037 45p 2N4058/9 10p 2N4060/1 10p 2N5457/8 40p 2N5459 40p 2N6027 *25p
---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

FOR TRADE ONLY

SEND FOR TRADE PRICE LIST

SPECIAL OFFERS THIS MONTH

# ETI BOOK SERVICE

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

## BEGINNERS

Beginners Guide to Electronics Squires £3.45  
Beginners Guide to Transistors Reddihough £3.45  
Electronics Self Taught Ashe £4.60  
Beginners Guide to Integrated Circuits Sinclair £3.45  
Understanding Electronic Circuits Sinclair £4.20  
Understanding Electronic Components Sinclair £4.20  
Beginners Guide to Radio King £3.45  
Beginners Guide to Audio Sinclair £3.45

## COOKBOOKS

TV Typewriters Cookbook £7.75  
CMOS Cookbook £8.20  
Active Filters £11.30  
IC Timer Cookbook £7.50  
IC Op-Amp Cookbook £10.00  
Video Cookbook £7.00  
TTL Cookbook £7.55  
The Basic Cook £4.00 inc. p/p  
IC Converter Cookbook £9.50

## APPLICATIONS

Fire and Theft Security Systems B. Weis £2.15  
How To Build Electronic Kits Capel £2.35  
110 Electronic Alarm Projects R. M. Marston £3.95  
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.95  
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.95  
110 Thyristor Projects Using SCRs R. M. Marston £3.95  
110 Wave Form Generator Projects R. M. Marston £3.95

## COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book £12.00  
Beginners Guide to Computers and Microprocessors with Projects C. Adams £6.05  
Basic Computer Games Ahl £5.40  
Basic for Home Computers A self-teaching guide B. Albrecht £5.40  
Illustrating Basic D. Alcock £3.00  
Intro to Microprocessors Aspinall £6.55  
Z-80 Microcomputer Handbook W. Barden £7.75  
How to Program Microcomputers W. Barden £7.25  
Introduction to Microcomputers and Microprocessors A. Barna £8.60  
Microprocessors in Instruments and Control R. J. Bibbero £12.60  
Basic Basic J. S. Coan £7.80  
Advanced Basic J. S. Coan £7.30  
Getting Acquainted with Microprocessors L. Frenzel £7.25  
Beginners Guide to Microprocessors C. M. Gilmore £4.90  
Beginners Guide to Home Computers Grossworth £4.50  
Beginning Basic R. E. Gosling £4.75  
Microprocessor Programming for Computer Hobbyists N. Graham £7.15  
Miniprocessors from Calculators to Computers Heiserman £5.00  
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.40  
Basic Programming J. G. Kemeny £6.70  
Microprocessor Systems Design E. Klingman £17.00  
Intro to Microprocessors Leventhal £17.00  
Microprocessors — Technology, Architecture & Applications D. R. McGlynn £9.20  
Interactive Computing with Basic Monro £3.65  
Basic with Style P. Nagin £4.25  
Software Design for Microcomputers Ogden £7.20  
Microcomputer Design Ogden £7.25  
Microcomputer Base Design Peatman £5.70  
Hands on Basic with a PET Peckham £9.00  
Basic — A hands on method Peckham £6.95  
6800 Software Gourmet Guide and Cookbook Scelbi £8.90  
8080 Software Gourmet Guide and Cookbook £8.90  
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.35  
8080/8085 Software Design Titus £7.60  
57 Practical Programs & Games in Basic Tracton £6.65  
Microcomputer Primer M. Waite £6.50  
Your Own Computer Waite £1.60  
Microprocessor/Microprogramming Handbook Ward £6.20

## LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £5.35  
Practical Digital Design Using ICs J. Greenfield £12.70  
Designing With TTL Integrated Circuits Texas Instruments £9.35  
How To Use IC Circuit Logic Elements J. Streater £3.80  
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.95  
Understanding CMOS Integrated Circuits R. Melen £4.15  
Digital Electronic Circuits and Systems R. M. Morris £3.65  
MOS Digital ICs G. Flynn £5.25

## TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10  
Working with the Oscilloscope A. Saunders £4.25  
Servicing with the Oscilloscope A. King £6.65  
Radio Television and Audio Test Instruments King £7.00

## OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.45  
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £3.95  
Designing With Operational Amplifiers Burr Brown £18.35  
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.55  
Op-Amp Circuit Design & Applications J. Carr £4.15

## COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.65  
Digital Signal Processing Theory & Applications L. R. Rabiner £24.40  
Electronic Communication Systems G. Kennedy £8.75  
Frequency Synthesis. Theory & Design Mannasewitsch £23.80  
Principles of Communication Systems H. Taub £8.40

## THEORY

Introduction to Digital Filtering Bogner £10.60  
Transistor Circuit Design Texas Instruments £9.75  
Modern Electronic Maths Clifford £6.95  
Foundations of Wireless Electronics M. G. Scroggie £5.25

## REFERENCE


Electronic Engineers Reference Book (Ed. 4) L. W. Turner £34.50  
Electronic Components M. A. Colwell £2.70  
Electronic Diagrams M. A. Colwell £2.70  
International Transistor Selector T. D. Towers New update £10.20  
International FET Selector T. D. Towers £4.35  
International Op-Amp Linear IC Selector Towers £7.65  
Radio Valve and Semiconductor Data A. M. Bell £3.60  
Radio, TV and Audio Technical Reference Amos £30.40

## MISCELLANEOUS

Electronic Fault Diagnosis Sinclair £3.55  
Integrated Electronics J. Milman £8.20  
Practical Solid State DC Supplies T. D. Towers £6.40  
Practical Triac/SCR Projects for the Experimenter R. Fox £2.35  
Printed Circuit Assembly Hughes & Colwell £2.70

Fallen behind recent advances?  
Just starting out?  
Need a decent reference book?  
ETI Book Service provides an easy  
way of getting your hands  
on the right title.

# SOUTHEAST ENGLAND'S ELECTRONICS CENTRE

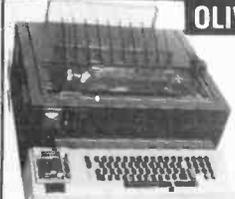

## OLIVETTI TE318

ONLY  
**£130**  
+ CARR  
+ VAT

The cheapest way to I/O to your computer, 80 column high quality printer, friction feed, serial ASCII in and out, RS232, feather light keyboard, and inbuilt 8 bit paper tape punch and reader. Supplied in good condition with interface data and accessories but untested, unguaranteed. What more could you ask for.  
1" Paper tape 75p per roll + pp 40p.  
**HURRY WHILE STOCKS LAST.**

## DYNAMIC RAM SCOOP!

INTEL 1103A 18 pin DIL 150 ns IK Rams guaranteed full spec. complete with data.  
8 for £2.99 16 for £4.99  
32 for £8.50 64 for £13.99  
18 pin DIL sockets 8 for £1.60

## VENTEK WORD PROCESSOR VDU TERMINALS

Still a few available. The VDU with the GREEN screen. Made by the VENTEK Co. with the following spec: 12" monitor, 24 lines x 80 characters, upper and lower case with descenders, 85+ keyboard, auto repeat, ASCII, RS232 interface, adjustable baud rates, full cursor control, edit function, character(s) flash etc., etc. Latest technology used, mostly 74LS with dynamic rams.  
Supplied in 2 grades  
Grade 1 Complete tested and working £275.00 + VAT  
Grade 2 Condition as seen or described £225.00 + VAT  
Carriage Extra  
Although Grade 1 sold tested and working no guarantee offered. Anyone with circuits/manuals please contact us.

## HY GRADE SMOOTHING CAPS

MULLARD - PLESSEY - MALLORY - SPRAGUE  
1500mf 100v 60p 3300mf 40v 50p  
3300mf 63v 70p 1mf 600v MYLAR 28p  
10,000mf 15v £1+ 22,000mf 16v £1.10+  
100mf 250v 45p 2100mf 200v £2.50+  
\*Ex equipment tested +P.P. 40p

## SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductor components, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed.  
50 + BAG £2.95 100 + BAGS £5.15

## MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages 110 V.A.C. £5.05 + pp 65p OR 240v A.C. £5.15 + pp 65p DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2"

## ELECTRONIC COMPONENTS & EQUIPMENT 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads for unbeatable value! Sold by weight

2.5kls £ 4.75+pp £1.25 5kls £ 6.75+pp £1.80  
10kls £11.75+pp £2.25 20 kls £19.99+pp £4.75

## ISOLATED 240v 4 AMP & 10 AMP SOLID STATE RELAYS

Interface your MPU etc. with the outside world made by the famous "Astralux" Co. They consist of a miniature plastic module with mounting holes containing a reed relay for isolation, choke and triac. 12-20 volts D.C. at a few milliamperes enable on/off control of A.C. loads up to 10 amp! The 10 amp version should be mounted on a heatsink. 100's of uses including power control, lighting, etc. etc.  
Dimensions: 4 amp, 1 1/2" x 1" x 1 1/2" 10 amp, 1 1/2" x 1 1/2" x 1 1/2"  
4 amp £1.45 10 amp £2.10 complete with circuit

## IBM SELECTRIC I/O GOLF BALL TYPEWRITERS

Ideal for word processor applications, will accept a host of different typefaces for all correspondence uses. Supplied in good working order. After seeing the printer only version advertised at over £900.00 we must be mad asking only £295.00 + carr. & VAT. Why pay a fortune? Even if your computer fails you still have a first class typewriter at your disposal!  
ACULAB interface unit for PET, TRS80, SORCERER £165.00 + VAT.

## OPTO SMASH!

TIL 302/MAN 7 7 segment LED readout common anode direct drive (via resistors) from 7447 £1.10 each  
TIL 119/OC72 Darlington opto isolator 3 for £1.00  
TIL305 0.3 7 x 5 matrix LED alphanumeric readouts £3.75 each.  
PHOTO TRANSISTOR Fairchild FPT-100 NPN silicon 30v 25ma 4 for £1.00

## DISPLAY I.C. AND TRANSISTOR BARGAINS NEVER CHEAPER

All I.C.'s and Transistors by well known manufacturers and fully guaranteed. No fall outs. Comprehensive data on I.C.'s 15p per type.  
2N4351 N channel MOS FET.  
2N4352 P channel MOS FET.  
60p each £1.00 per pair  
HIGH VOLTAGE NPN POWER SWITCHING transistors BVcbo 600v BVceo 500v BVebo 15v I c 5 amps Pc 125 watts HFE 60 typ ft. 2.5 mhz ideal invertors, etc. TO3 £1.60 each 4 for £5.40.  
BF258 NPN 250v @ 200ma 45p each 3 for £1.08.  
I.R. BS801 2.5 amp 100v bridge rec. P.C. mount long leads 35p each 4 for £1.08.  
IN4998 4 amp 100v P.C. mount diodes long leads 14p each 10 for £1.10.  
LM309K + 5v 1.2 amp regulator £1.10 each 6 for £5.35.  
AGFAC10 computer grade cassettes complete with library cases 68p each, 10 for £5.50  
IN4004 SD4 1 amp 400v diodes 7p each 18 for £1.00.  
I.R. 12 amp BRIDGE RECS. 400 volt £1.25 each.  
POWER DARLINGTON SCOOP!  
MJ1000 NPN 50v 90v 5 amps TO3 35p each  
2N6385 NPN 80v 100v 10 amps TO3 £1.25 each  
MJ4030 NPN 60v 150v 15 amps TO3 £2.25 each

## DECADE 0-9 THUMBWHEEL SWITCHES

Stackable, gold plated contacts, dim. 33 x 43 x 8 mm. 90p each, 10 for £5.50.  
Miniature Continental Series 12VDC 4c/o plug in relays £1.30 each.  
Greenpar 50Ω BNC Chass. socket single hole fixing 65p  
C90 Audio Cassettes screw type construction 45p each 3 for £1.00.  
Bulbs 24v 14 watt white frosted S.B.C. 8 for £1.00.  
Bulbs 12v 100 watt clear, base similar S.B.C. 45p each.  
S.B.C. Bulb Holders All steel cad. plated panel mount easily fixed via nut and round hole, ideal disco displays, scoreboards, etc. 4 for £1.10.  
VMOS VMPI Silicon TO3 power FET 0-60v, DC-200 mhz will drive direct from CMOS etc. £1.50 each, full date 30p.  
Heavy Duty Flat Insulated Earth Braid 100-200 amp braided tinned copper in heavy clear PVC sheath 50p per metre. £6 for 15 metres + P.P. £1 per 15 metres.  
BULGIN miniature 6 way male chassis mount socket and matching free plug 60p each, 2 for £1.10.  
Red L.E.D.'s full spec. 0.2 14p each, 10 for £1.25.  
Red L.E.D.'s 0.125 10p each 10 for 80p  
Dynamic Stick Mics 600Ω with built in on/off switch complete with lead and min. jack plug £1.15 each, 10 for £10.00.  
TOS HEATSINKS "Thermalloy" black anodised press on aluminium finned type 18p each, 8 for £1.00.

## BURROUGHS SELF SCAN DISPLAYS

A masterpiece of electronic engineering. This unit could be described as a miniature VDU. Module consists of an 18 digit display area, mounting bezel, on board character generator and decoder driver circuitry, all measuring only 8.5" x 2.25" x 1.34". By inputting a 6 bit ASCII T.T.L. code 18 GIANT 0.4" full alpha numeric characters may be displayed simultaneously, addition of external logic enables the unit to scroll along just like a newscaster. Internal 64 character repertoire, or external inputs for special characters are provided. Power requirements +5v, -12, and 250v.  
Supplied brand new, complete with data £55.00 + £1.25pp.

## BARGAINS GALORE!

In our walk round Warehouse NOW open Monday to Saturday 9.30-5.30

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below. 100's of bargains for callers



## SUPER 77 KEY KEYBOARD KIT

We've done it again! We've purchased a large quantity of C.P. CLARE top quality keyboard read switches plus full QWERTY keytop sets and thrown in a PCB to enable you to customise the keys just as YOU want them, just add and wire an encoder chip and you can arrange ASCII, BAUDOT, anything! Adding up to a quality keyboard which would normally cost around £100.00. Supplied with layout and assembly info at only £26.99 + £1.50pp.

## HOW TO GET HERE

Victoria, London Bridge or Holborn Viaduct to Thornton Heath. 1 minute from Thornton Heath Station.

## POWER SUPPLY UNITS

5 VOLT 2.5/8 AMP TTL Made for TTL this compact ex computer systems unit features a 10 amp transformer. DC outputs of 5 volts @ 2.5 amps and 7.5 volts @ 5 amps are available. The 5v output is fully regulated and smoothed with electronic current limiting. May be easily modded for 5 volts @ 7-8 amps. Sold complete with circuit, believed working but untested. £8.25 + £1.60pp.  
5 VOLT 5 AMP An extremely compact unit measuring only 125 x 175 x 83 mm, almost fully enclosed with terminal type connections. Features such as adjustable volts and current limit make it ideal for an MPU system. Sold as new. £14.99 + £1.60pp.  
" + " & " - " 12-15v @ 250 ma. ITT Powercard. Measuring only 140 x 80 x 40 mm, this precision totally enclosed PSU should meet all your memory and negative rail requirements. Individual pots allow independent adjustment of both the plus and minus supply rails. Supplied BRAND NEW with circuit and edge connector at only £12.75 + £1.00pp.

## KEYBOARDS

### ★ 76 KEY ASCII CASED ★

At last a coded 75 key cased ASCII keyboard at the right price. Housed in an attractive light grey case, this unit was originally made for ICL for use in airport reservation systems so only the BEST parts were used. It has everything, we think, to meet your most exacting requirements, numeric keypad, upper and lower case, cursor controls, single 5 volt rail, serial and parallel data outputs, plus eight LEDs mounted on the case. Supplied with circuits, believed brand new, but may have minor scratches on cases.  
Only £43.50 + £1.60pp

### ★ LOW PRICE CHASSIS ★



A special bulk purchase enables us to offer the above keyboard at a lowest ever price. 49 coded keys encoded into a direct TTL compatible 7 bit output. Features such as delayed strobe, 5 volt D.C. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector, at a secondhand "no time to test" price of only **£20.00 + P.P. £1.60**  
SUPER CASED VERSION Same as above spec. but housed in attractive two tone moulded, free standing case. Unit also includes an all TTL parallel to serial converter (no details) etc.  
**£27.50 + P.P. £1.85**

## TOROIDAL TRANSFORMERS

HP 240v pri. sec. 2 x 30v @ 4 amps 2 x 18v @ 1 amp £11.00 - p.p. £1.95  
dimensions 4 1/2" x 2 1/2"  
PR 240v pri. sec. 15 0-15 @ 2 amps dimensions 3" x 2 1/2" £4.95 - p.p. 99p  
TM 240v/110v pri. sec. 15 0-15 BvA dimensions 2 1/2" x 1" £1.95 - p.p. 30p  
All voltages measured off load.

## HIGH EFFICIENCY SMITHS RADIAL BLOWERS

Are your hot parts sweating? Then keep them cool with our high efficiency radial snail type blowers. Made by Smiths, designed for continuous use in expensive electronic equipment very powerful and quiet, gives massive air flow to prolong component life and reliability. Easily mounted, air aperture 2 1/2" x 3". Ideal linear etc.  
Please state 240v or 110v operation. 50hz only.  
**BRAND NEW £4.55 P.P. £1.60**

# ELECTRONICS

Dept. WW, 64-66 Melfort Rd., Thornton Heath, Surrey. MAIL ORDER Telephone 01-689 7702 or 01-689 6800 INFORMATION

Unless otherwise stated all prices inclusive of VAT. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 40p per order. Bona Fide account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.

**NEW**

# CONSTRUCTORS PACK 7

## ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

**\* EASY TO BUILD \* PUSH BUTTON TUNING \* MODERN STYLING DESIGN \* ALL NEW UNUSED COMPONENTS \* 6 WATT OUTPUT \* READY ETCHED & PUNCHED P.C.B. \* INCORPORATES SUPPRESSION CIRCUITS**



The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard-IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

**£10.50** p&p £1.75

**CONSTRUCTORS PACK 7A**  
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.  
**£1.95** Per Pack, p & p £1.00  
Pack 7A may only be purchased at the same time as Pack 7.  
**NOTE:** Constructor's pack 7A sold complete with radio kit **£15.20** including p&p

**A FEATURED PROJECT IN PRACTICAL ELECTRONICS**



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only. Mon-Sat 9.30am-5.30pm Closed Thursday  
21 E HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

**NEW 12+12 AMPLIFIER KIT**



An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free. Size 9 1/4" x 8 1/4" x 4" approx with kit. **£13.95** p&p £2.55

**TWO WAY SPEAKER KIT** To suit above amp. Comprising 2, 8" approx Phillips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65

Available only to first time purchasers of the 12 + 12 kit.

**50 WATT MONO DISCO AMP**



**£30.60** p&p £3.20

Size approx 13 3/4" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infegral push-pull switches. Independent bass and treble controls and master volume.

**NOW AVAILABLE**



**30 + 30 WATT STEREO AMPLIFIER**

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and push buttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 3" x 10" approx. **£32.90** p&p £3.30

**BUILT AND READY TO PLAY**

**Mullard AUDIO MODULES IN BARGAIN PACKS**

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS

**CURRENT CATALOGUE PRICE AT OVER £25 PER PACK SEE OUR PRICES**

**1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £5.00** p&p £1.10

**2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **ill. OUR PRICE £7.65** p&p £1.15

**ACCESSORIES** Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

**Two Way Speaker Kit** Comprising of two 8" x 5" approx 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p **£4.05**

**£76.00** p&p £4.00

**100 WATT MONO DISCO AMP** Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10 1/4"

Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak

**EMI SPEAKER BARGAIN**

Stereo pair 350 kit. System consists of 13" x 8" approx woofer with rolled surround, 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max 8 ohm impedance. **£18.25** Per stereo pair p&p £4.20

**BSR P200** **£25.50**

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00

Shure M75 6 Magnetic Cartridge to suit **£7.95**

**BSR** Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 i.p.m spindle adaptor ideally suited for home or disco use. **OUR PRICE £12.25** p&p £2.75

**PHILLIPS RECORD PLAYER DECK GC037**

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY.

**BARGAIN OFFER**  
Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00. **OUR £11.95** PRICE p&p £2.50



323 EDGWARE ROAD, LONDON W2  
21 E HIGH STREET, ACTON W3 6NG  
ACTON - Mail Order only, No callers  
ALL PRICES INCLUDE VAT AT 15%  
All items subject to availability. Price correct at 1.5.80 and subject to change without notice.  
All enquires Stamped Addressed Envelope.  
NOTE: Persons under 16 years not served without parent's authorisation.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON. Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

# STATE VARIABLE FILTER

Choose one of seven filter responses with this voltage controlled state variable filter design by R.C. Blakey for your Project 80 modular synthesiser.



The Voltage Controlled State Variable Filter has low pass, high pass, band pass and notch filtering capabilities. The first three responses are available as both two pole (12 dB/octave) and four pole (24 dB/octave) filters. Manual and external control of resonance is included.

## Design Features

The state variable filter using three operational amplifiers, as shown in Fig.1, is probably familiar to most readers.

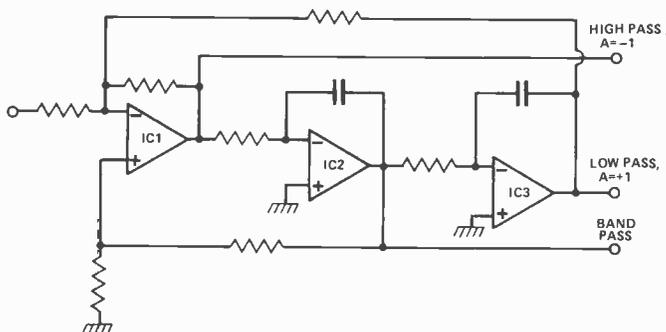


Fig.1. Circuit diagram of a state variable filter using three op amps.

A simple way to convert this into a voltage controlled filter is to interpose operational transconductance amplifiers (eg CA3080) prior to the two integrators around IC2 and IC3. Voltage control of Q (or resonance) can also be obtained by using an OTA in the feedback to the non-inverting input of IC1. This is the basis of the present design. Such a filter gives 12 dB/octave low and high pass responses and second order band pass response. By placing two such filters in series it is possible to increase the roll-off characteristics by a factor of two. In practice, however, this is often difficult due to component mismatching which results in uneven roll-off characteristics. The problem has been minimised in this design by using a customised integrated circuit from

Solid State Micro Technology for Music, namely, the SSM2040. This device contains four closely matched transconductance amplifiers and an exponential generator which is common to the four cells. For resonance control the relatively new LM13600, dual transconductance amplifier, is used in the feedback of the two stages of state variable filters. Both manual and external voltage control of resonance is provided and while these controls are additive the maximum useful range is our standard 0 to 10 volts into 100k.

Seven filter responses are available, one at a time, via a selector switch — low pass (12 and 24 dB/octave); high pass (12 and 24 dB/octave); band pass (2nd and 4th orders); and notch. The low pass and high pass outputs are 180° out of phase and so combining these outputs results in a notch. A notch filter is of limited use in synthesis since the ear only responds to frequencies present and not to frequencies which are absent. The latter may sound rather obvious but since the notch filter allows most frequencies to pass the ear cannot detect the difference between the original and filtered signals, except in some exceptional circumstances or unless the notch is fairly wide.

The filter has three signal inputs and the combined signal should not exceed 10 volts peak to peak. An attenuating potentiometer has been provided on one of the inputs and if mixing of signals is required then external attenuating controls can be used. The filter has approximately unity gain at maximum resonance feedback.

Frequency response control is obtained using the exponential converter within the SSM2040 and an attenuating network, with adjustment, allows the 1 V/octave characteristic to be obtained. Initial frequency (zero control voltage) is set to approximately 20 Hz and the filter has a 1,000:1 control range. Control Input 1 is used for keyboard input; Control Input 2 has an attenuating potentiometer for use in conjunction with an envelope shaper, etc; a Coarse control provides manual sweep over 10 octaves and a Fine control is included for more accurate initial setting and has an adjustment range of one octave. Temperature stability should not be

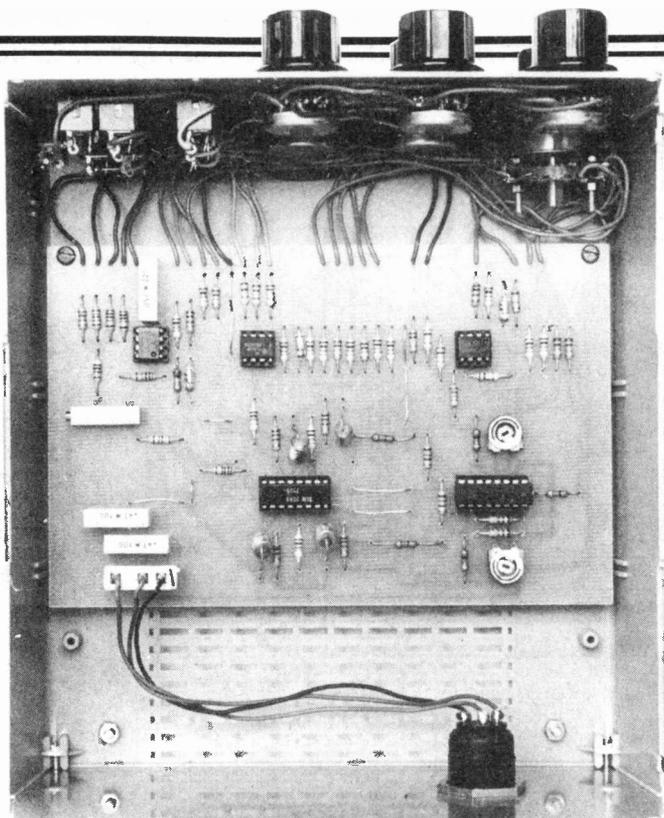


Fig.2. The voltage controlled state variable filter can be built into this Teko Alba case (see Buylines) as a 'stand alone' project.

a problem under normal circumstances. If required, however, R47 may be replaced by a Q81, 1k $\Omega$ , 1% temperature compensating resistor.

## Construction

The first point to note is that the SSM2040 outputs (OUT, CAPACITOR and IN) are not short circuit protected and shorting any of these to either supply will generally blow the circuit, although connections to ground can be tolerated for several seconds. Some additional resistors have been used to provide additional safeguard in the latter circumstances. Take particular care on both the orientation of this IC and when any probes are connected to components on the PCB, for whatever reason.

Identify and solder the seven wire links before installing components. The capacitors around the SSM2040 will accept both preformed (as illustrated) and normal polystyrene capacitors. When all components have been installed, the two holes remaining around IC1 are for installing a Q81 temperature compensating resistor, when required. The manual resonance control (RV2) may be wired via the jack socket used for the external resonance control such that the former is disabled when external control is in use. The manual and external controls may also be wired up independently but no increase in gain will be achieved when their combined voltages exceeds the equivalent of about 10 volts into 100k, eg manual control half way and five volts external input. In fact the resonance will begin to decrease somewhere above 10 volts.

The most complicated task is wiring up the switch

but this should not pose any problems if reference is made to both the circuit diagram and the PCB layout.

## Setting Up And Calibration

First adjust the module to achieve the seven filter responses. These can be readily observed on an oscilloscope by using the VCLFO and VCO as a sweep frequency generator, as described for the 80-6 filters. There are, however, only two adjustments to make in order to ensure that the seven responses are present (assuming no wiring errors) and these can be made by ear with the aid of an amplifier, as shown below.

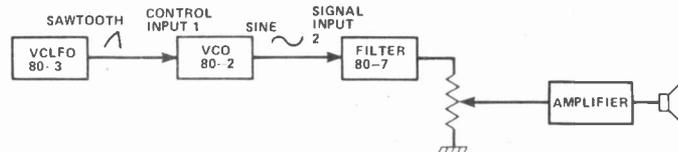


Fig.2. The seven filter responses can be inspected with the circuit shown above.

Set Coarse frequency controls on VCLFO and filter 80-7 to mid position and to zero on the VCO. With the edge connections of the filter facing you and the components uppermost set the wipers of both PR1 and PR2 to about the 9 o'clock position. Put selector switch on BP2 output and slowly turn PR1 anti-clockwise. Initially there may be no output but then a low pass output will be heard. Further rotation of PR1 will result in a fairly abrupt change from low pass to band pass and this is audibly obvious. PR1 should be left at this setting. Now switch to LP4 output and turn PR2 slowly clockwise. Initially nothing will be heard and then a low pass response. PR2



If you wish to build all of the Project 80 modules and install them in a single case with keyboard, mount the PCB on this front panel. At the end of the series you'll have a matching set.

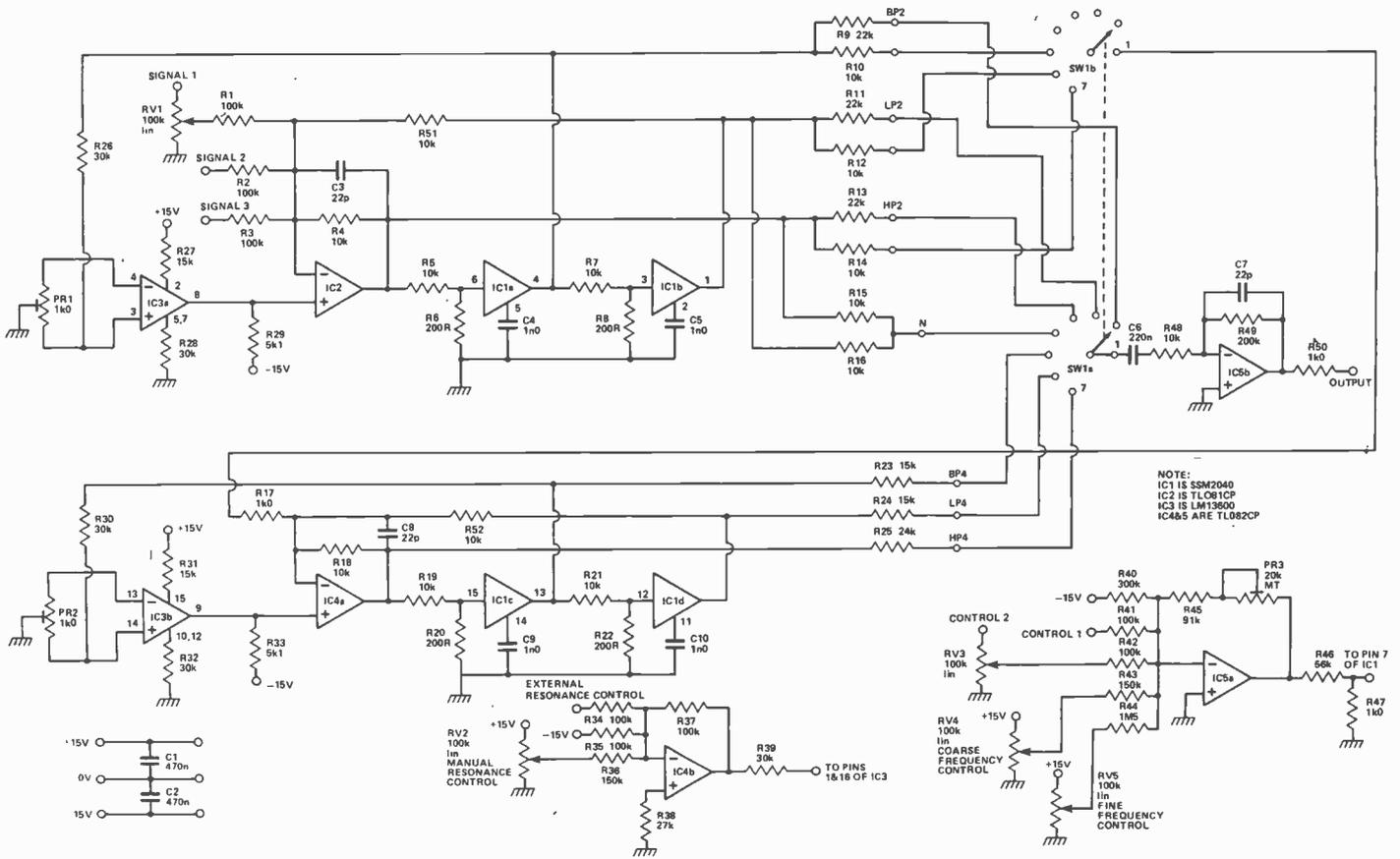


Fig.2. Circuit diagram of the state variable filter.

## HOW IT WORKS

The SSM2040, VCF produced by Solid State Micro Technology for Music, contains four independent filter sections which may be interconnected to provide a wide variety of filter responses. Each section contains a transconductance amplifier followed by a buffer and by using two of these sections with an external op amp a state variable filter may be realised as shown below.

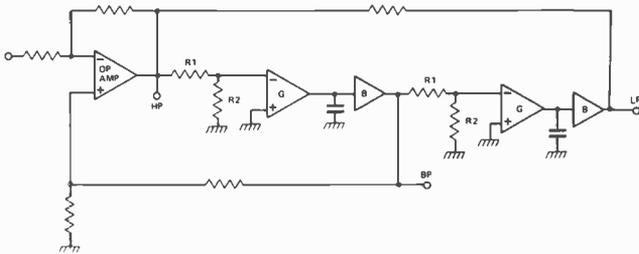


Fig.3. Using the sections of the SSM 2040 and an op amp to form a state variable filter.


The signal levels into the gain cells should be limited to 2mV RMS and since R2 should be 200 R for optimum control rejection then R1 is 10k with a 1 V signal at the op amp output. The equivalent input noise for the SSM2040 is 0.5 uV RMS at 20 Hz to 20 kHz so a signal to noise ratio of about 90 dB is achieved. In the first state variable filter section around IC3a, IC2, IC1a and IC1b a 10 V signal into R1, 2 or 3 is reduced by IC2 and R4 to produce the 1 V into attenuating resistor network R5, 6. The two pole low pass, high pass and band pass filter responses are derived and a notch produced by combining the low and high

pass outputs which are 180° out of phase. These four outputs are connected to the rotary switch, SW1a and the signal restored to its original level by R49, R50 and IC5b. The signals are AC coupled into IC5b to remove any DC offsets.

The low pass, high pass and band pass outputs from the first stage are also separately connected to rotary switch, SW1b and fed into the second stage formed around IC3b, IC4a, IC1c and IC1d. The four pole outputs derived in this section return to switch SW1a and are available via IC5b, as before.

Resonance control is provided by an LM13600 (IC3), dual transconductance amplifier, interposed between the band pass output and the non-inverting input of the filters external op amps (IC2 and IC4a). The amount of feedback is controlled by the current developed across R39 and this has been commoned for both halves of the LM13600. Manual control is obtained via RV2 and R36 into IC4b and external voltage control via R34 into the same input summing node. The control voltage should be limited to an equivalent of 10 V into 100k.

Frequency control is common to all four amplifiers in the SSM2040 and best results for a 1,000 to 1 sweep in the range 20 Hz to 20 kHz is obtained with +90 V at pin 7. Resistor R40 connected to -15 V provides approximately +90 mV and a lower frequency limit of about 20 Hz. A 0 to +10 V control voltage into Control Inputs 1 or 2 will then allow frequency adjustment over a range of ten octaves. Manual adjustment over a ten octave range is provided by the Coarse Frequency Control (RV4 into R43) and Fine Frequency Control over a range of one octave by RV5 into R44. Precise adjustment of the 1 V per octave response is achieved by adjusting the gain of IC5a using PR3.

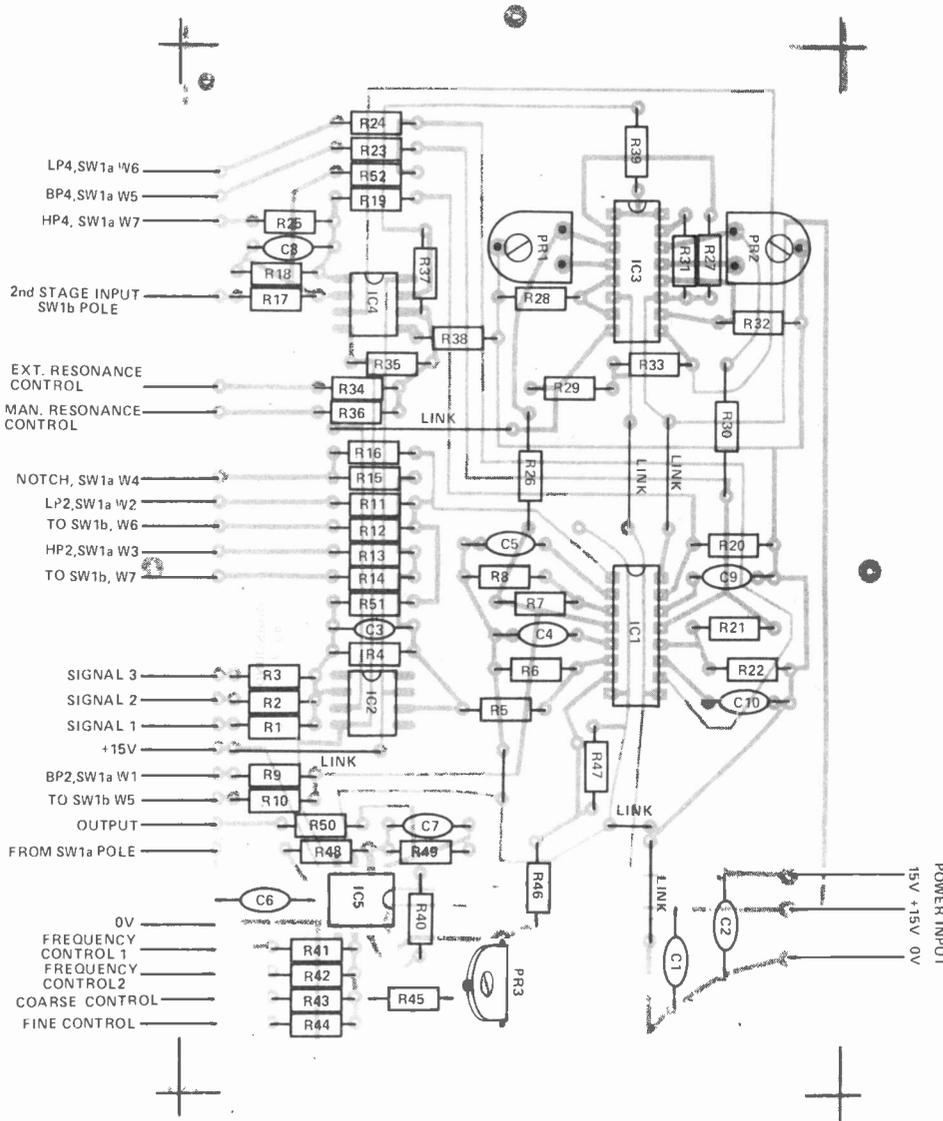

## PARTS LIST

Resistors 1/4W, 5% carbon film except where stated

R1,2,3,34,35,37	100k
R4,5,7,10,12,14,15,16,18,19,21,48,51,52	10k
R6,8,20,22	200R
R9,11,13	22k
R17,50	1k
R23,24,27,31	15k
R25	24k
R26,28,30,32,39	30k
R29,33	5k1
R36	150k
R38	27k
R40	300k, 1% metal film
R41,42	100k, 1% metal film
R43	150k, 1% metal film
R44	1M5
R45	91k, 1% metal film
R46	56k, 1% metal film
R47	1k0, 1% metal film
R49	200k

### Potentiometers

RV1,2,3,4,5	100k linear
PR1 2	1k0 carbon
PR3	20k cermet multiturn

### Capacitors

C1,2	470n polyester
C3,7,8	22p polystyrene
C4,5,9,10	1n0 polystyrene
C6	220n polyester

### Semiconductors

IC1	SSM2040
IC2	TL081CP, or equivalent
IC3	LM13600
IC4,5	TL082CP, or equivalent

### Miscellaneous

SW1	2 Pole 7 (or more) Way Rotary Switch
-----	--------------------------------------

should be left at the setting where the low pass output commences. The selector switch can then be turned through its seven outputs to check that the appropriate response is present and these can be clearly identified by ear. If an oscilloscope is available then switching to BP2, LP4 and HP4 outputs and making minor adjustments to both PR1 and PR2 may result in some improvement to the filter responses.

The final step is to calibrate the filter for 1 V/octave frequency control. The 80-7 filter will not oscillate at maximum resonance feedback and so the best approach is to observe the maximum signal amplitude using an oscilloscope. Connect the sinewave output from a VCO to Signal Input 2. Connect the LP4 output to an oscilloscope, set VCO frequency to about 250 Hz and adjust RV4 (Coarse Control) and RV5 (Fine Control) to obtain maximum signal amplitude. Increase voltage on Control Inputs 1 of both VCO and VCF by exactly 1 V and adjust PR3 until maximum amplitude is restored. Repeat the above steps until calibration is achieved. If an oscilloscope is not available then an alternative ap-

proach is to set all VCF controls to zero and apply about 4 V to Control Input 1 and measure the voltage at the junction of R46 and R47, using a high input impedance voltmeter. Increase the control voltage by exactly 1 V and then adjust PR3 to obtain an 18.0 mV change at the junction of R46 and R47. Again repeat the procedure until an 18.0 mV change is obtained for a 1.000 V change in control voltage.

## BUYLINES

An 80-7 State Variable Filter module kit (PCB plus components) is available for the inclusive price of £20.10 from Digisound Ltd, 13 The Brooklands, Wrea Green, Preston, Lancs PR4 2NQ.

The modules are cased in Teko Alba A23G cases (order code TEK A23G), available from West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET at £4.43 each all inclusive.

# ENVELOPE SHAPER

**Tamper with your time constants. This Project 80 design by R.C. Blakey gives full control of Attack, Decay, Sustain and Release.**

The envelope generator is based on the SSM2050, a voltage controlled transient generator produced by Solid State Micro Technology. Using this IC all that is necessary to vary the time constants for the Attack (A), Initial Decay (D) and Final Decay or Release (R) is a voltage applied to the appropriate pin via a scaling resistor. A minimum range of 2 mS to 20 S is available for each of the three timing functions. The voltage response is exponential which means that the most useful time range utilises the highest proportion of the associated control potentiometer. The attack output is nominally 0 to 10 V and the Sustain level (S) is simply a voltage applied to Pin 12.

It has separate gate and trigger inputs whereby a combined gate and trigger pulse will initiate a full ADSR response; a trigger applied after the first one and while the gate pulse is still present will restart the attack response and a gate pulse on its own will generate an AD contour. When the gate pulse is released the final decay commences, as is usual with ADSR and AD envelope shapers.



Fig.1. Wave forms associated with envelope processing.


The time constants may be trimmed so that any number of ADSR's can be adjusted to exactly the same scale. Also an adjustment to ensure that the sustain voltage accurately matches the peak attack voltage is provided. The output buffer in the SSM2040 is adequate for most practical purposes but to retain our 'plug in anything to anywhere' philosophy an external buffer has been added. Other features included are external initiation of the ADSR or AD contours, for example, from a manual push button, as well as provision to use gate and trigger pulses derived from TTL logic.

## Construction

The PCB is designed to take two envelope generators and as usual will fit either a panel or the TEKA ALBA A23G case. If the latter is used then there is only sufficient panel space to sensibly install a single envelope generator.

Construction is very straightforward and the only points to note are the single wire link and the opposed orientation of the SSM2050 and the 741 buffer.

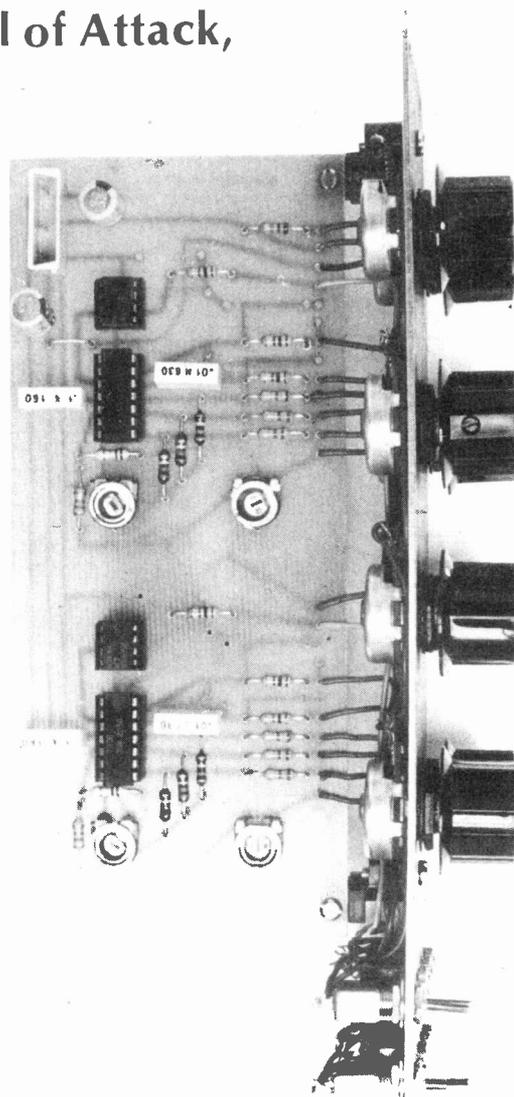An on-off switch, SW1, is connected across the inputs marked 'TRIGGER (CMOS)' and 'GATE (CMOS)' so



that when only single pulses are available, eg, manual gating, then both the ADSR (SW1 closed) and AD (SW1 open) responses can be obtained. The manual gating can be added by connecting a push to make switch between the PCB connections marked 'OUTPUT FOR MANUAL GATE' and 'MANUAL GATE'. The push button may be panel mounted but the preferred approach is to take the former connection to a jack socket and to use an external hand, or foot, switch connected to two jack plugs. These jack plugs go to the Gate (G) input and the Manual input (from R11). The option and type of switch is left to the constructor.

Resistors R12, R13 and R14 are not part of the basic kit but are to be installed by constructors who are using TTL logic to derive gate and trigger pulses. Also in this case the switch, SW1, is connected across the PCB con-

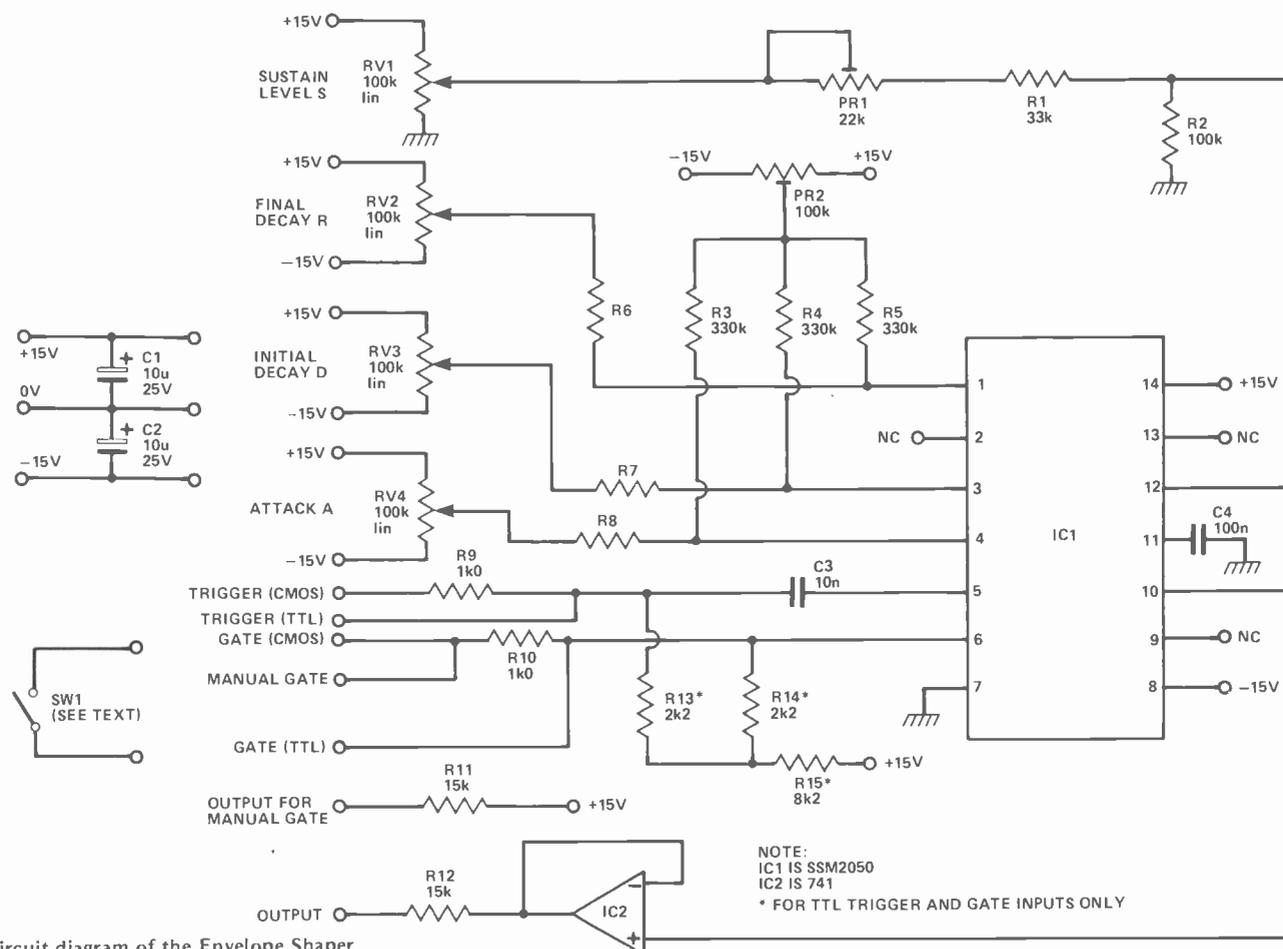


Fig.2. Circuit diagram of the Envelope Shaper.

## HOW IT WORKS

The SSM2050 Voltage Controlled Transient Generator contains a voltage controlled resistor to generate the nominally exponential slopes and various logic devices to define the states. An attack flip-flop (AF/F) is set by the trigger pulse and reset by either NOT GATE or the attack comparator determining that the output has reached +10 V. Thus ATTACK = GATE and AF/F; INITIAL DECAY = GATE and NOT AF/F; FINAL DECAY = NOT GATE. Each state is characterised by a nominally exponential approach to a characteristic voltage; these being +13 V, sustain voltage and 0 V for attack, initial decay and final decay respectively.

The input stages of the SSM2050 logic inputs have a lateral PNP structure which protects them from excess voltages. Their sensitivity is 750  $\mu$ A or 1V5 max., these being the minimum current and voltage required to trigger the SSM2050. For 5 V, 10 V and 15 V CMOS gate and trigger inputs these requirements are met using 1k, 10k and 15k resistors respectively to these inputs.


The attack, initial decay and final decay inputs have a nominal impedance of 3k1 and a time constant sensitivity of 18 mV/octave with a 100n timing capacitor (C4). An increasing positive voltage increases the time constant. Thus R6, 7 and 8, connected to +15 V via the rotary controls RV2, 3 and 4, will have nominal values of about 300k to achieve a five decade timing range from 2 mS to 20 S. The input impedance, however, varies by up to +25% between devices. Fortunately the impedance may be measured with a high input impedance ohmmeter as the resistance between pins 1 and 7 and so the appropriate scaling resistor may be selected by multiplying this resistance by 100 and adding 10k. The nearest E24 resistor is chosen and more precise adjustment of timing is achieved by injecting a small offset voltage via PR2 and R3, 4 and 5. The attack voltage may vary between 10 and 11 volts and PR1, R1 and R2 provide a means of matching the maximum sustain voltage to the peak attack voltage. The sustain level can then be varied from 0 to 100% of attack voltage using RV1.

As an additional safeguard the output of the SSM2050 has been buffered by IC2 configured as a voltage follower.

nections marked 'TRIGGER(TTL)' and 'GATE(TTL)' to provide the same function as before. For manual gating with TTL a push to break switch should be connected between 'GATE(TTL)' and 0V, since the gate and trigger pulses are held high by the additional resistors.
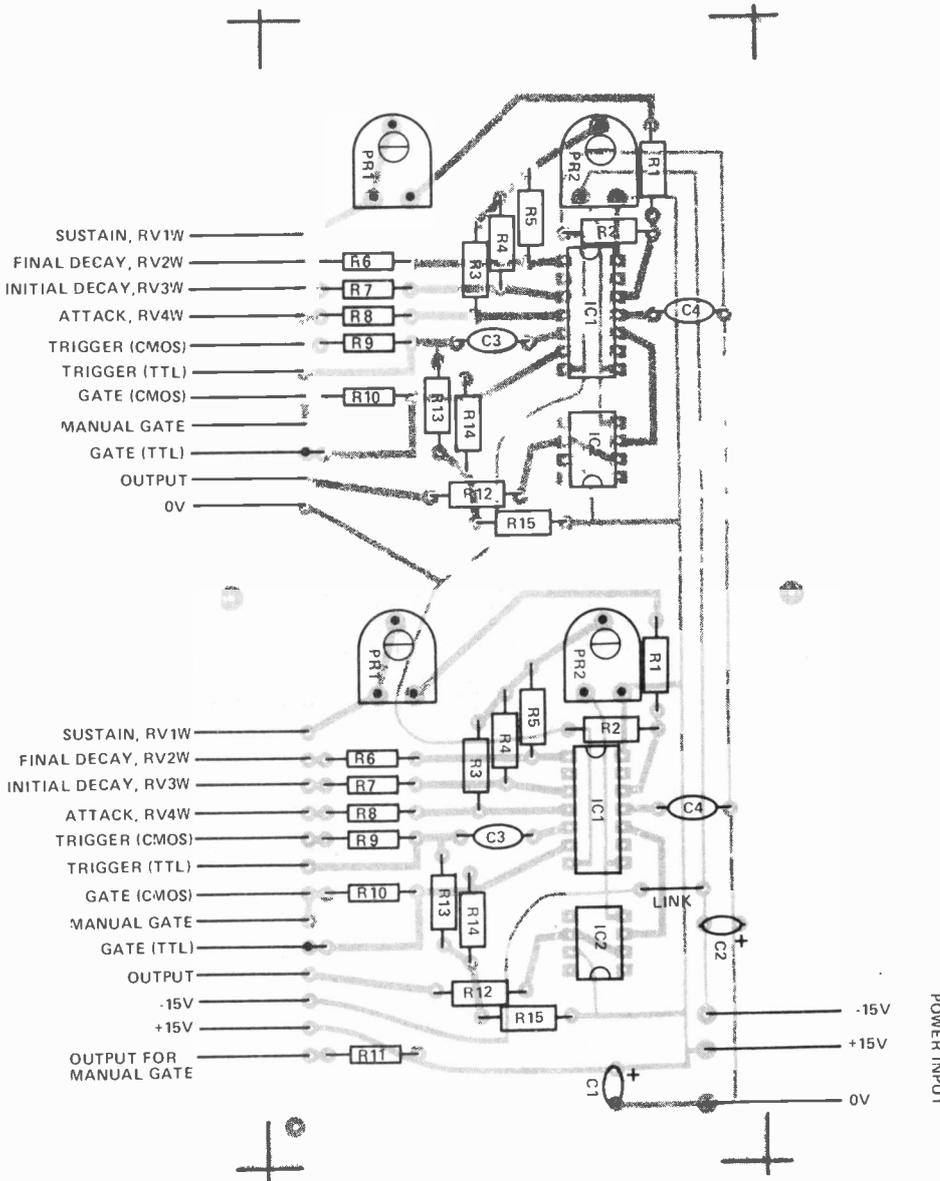
## Setting Up And Calibration

Provide a means of manually gating the envelope generator as described in the previous section and the switch may be constructed from two strips of metal, if necessary. Connect the output to a voltmeter set to a DC range of 15V and turn Attack control (RV4) to about 3 o'clock position and all other external controls to zero. Put SW1 in the ADSR position (gate and trigger commoned), turn PR1 fully anti-clockwise and PR2 about mid position. Apply power to the module, depress the manual button and keep held down while observing the voltmeter. The voltage should steadily rise and will probably take between 5 and 20 seconds to reach about 10V. Since the module is not calibrated the time taken may be outside of the range stated. The important point is that the voltage increases to a maximum of about 10V and then drops sharply to zero. If this response is observed then set Sustain control (RV1) to mid position and RV2, 3 and 4 to about the 3 o'clock position (a little less if the time to reach 10V was greater than 10 seconds in the previous step or a little more if the time was less than 5 seconds). Press button and hold down as before. The voltage should now rise to about 10V and then decay at the same rate to a voltage of approximately 5V and remain steady. On releasing the button there will be a final decay to about 0V. Finally, open switch SW1 to check



## PARTS LIST

### Resistors 1/4W, 5% Carbon film

R1	33k
R2	100k
R3,4,5	330k
R6,7,8	see text
R9,10,11	1k0
R11	15k

### Potentiometers

RV1,2,3,4	100k linear
PR1	22k carbon
PR2	100k carbon

### Capacitors

C1,2	10u 25V electrolytic
C3	10n polyester
C4	100n polyester

### Semiconductors

IC1	SSM2050
IC2	LM741CN, or equivalent

### Miscellaneous

SW1	Sub Min SPST (or SPDT) switch
-----	----------------------------------

Fig.3. Component overlay.

the AD response and repeat the last step. This time the voltage should rise to about 5V and maintain this value until the button is released which will initiate the decay to about zero. Note that in the AD mode the Initial Decay control (RV3) determines the attack time and the Sustain level controls the amplitude of the AD contour. The above demonstrates that all functions are operational.

The next step is to adjust the sustain voltage to match the peak attack voltage. Close SW1; set RV4 to about 3 o'clock; RV1 fully clockwise; RV2 and RV3 to the zero. Depress the manual button, observe the voltmeter and note whether there is a discernible drop in voltage after the attack has reached its peak. If so, turn PR1 clockwise and repeat the last step. Repeat until peak attack voltage and sustain level are matched. The adjustment to PR1 must be made in small increments so as to avoid having a higher sustain voltage than the attack voltage, otherwise malfunction of the SSM2050 can occur. It is therefore better to err on the safe side and wait until the envelope shaper is connected to the VCA at which time any mismatch between the two voltages can be checked by ear and a minor adjustment made to PR1 to correct it, if necessary.

The final step is to adjust the time constants and this calibration is only required for the Attack time control (RV4). The module should be in the ADSR mode (SW1 closed) and all other control pots set to zero. If an oscilloscope with a triggered sweep is available then the gate and the oscilloscope can be simultaneously triggered and PR2 adjusted to give an attack time of 2 mS when RV4 is at zero. An alternative method is to time the attack period, for example, by observing a voltmeter connected to the output and measuring the time between pressing the manual push button and the voltage dropping sharply. With the latter method adjust RV4 so that there is 10V0 at its wiper, trigger the module and adjust PR2 until the time taken is 9 S (slightly more than less). When this time is obtained turn RV4 to zero and check that a fast response time is obtained.


## BUYLINES

A single 80-8 module with PCB and all components shown on the circuit diagram for CMOS inputs is available from Digisound Limited for £9.83 and a dual unit for £17.02, both inclusive of postage and VAT.

# Quantum Electronics

## UNBEATABLE PERFORMANCE, UNBEATABLE PRICES

FROM £162.21

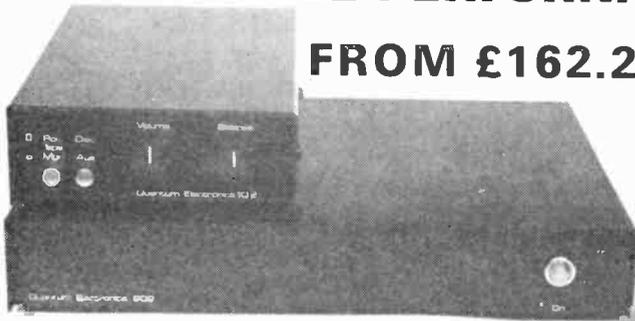

Have you noticed how the top end audio equipment has risen in price out of reach of many people? Even some kits are now very expensive. Well, while others make inflated claims about cost-effective designs Quantum is the only one to deliver the goods. At **£215.66** our 102/202 pre-power combination is the lowest cost British amplifier to cater for moving-coils and it gives a very generous 45W per channel. It is also available in kit form for a mere **£162.21!** Our 102/204 at **£237.81** is the lowest cost 110W British amplifier or in kit form it is **£184.35**. So how has this come about? We have not scrimped on the electronics. For instance, the pre-amplifier, though sparse in controls, uses no less than six I.C.s and 22 transistors in a unique and elegant circuit configuration. We have not lost out on performance. The overall t.h.d. of the pre-/power amplifier is below .01% at 1kHz, typically below .005% at 10W with a slew rate of 35V/uS. The main reason our prices are so low is that we have taken steps in the design to produce a low cost method of assembly, and we have then priced them accordingly. This is exemplified in our 102 pre-amplifier, which, because of its single board construction, we can offer for **£80.41** ready built or in a "no soldering" 20 minute easy build kit for **£70.95**. If this was in a more conventional package of module, loose pots, sockets, etc. we would have to charge more for no improvement in performance, just the dubious privilege of hours of fiddly wiring!

The 102, shown above with a 202, is all that virtually anyone requires, catering for auxiliary, 2 or 3 head tape and moving coil or magnetic cartridge. The sensitivity and load for the disc input is specified by a small, cheap (**£3.30**) plug-in card, which makes it ideal if you might upgrade to moving coil from magnetic — just buy a new card or change the existing components. Cards are available off the shelf to suit the majority of popular cartridges but full matching information is supplied with each pre-amplifier. When used with our 202 or 204, all that is required is a special connecting lead, called AC1 at **£3.98**. For use with other power amplifiers there are mains power supplies both ready built and in kit form. These are described fully in our detailed information, as are our moving coil head amplifier modules and kits.

Our 205s are the ultimate in low cost super-fi. Designed to drive any loudspeaker this is a mono power amp to be used in pairs for stereo, giving 145W r.m.s. into 8 ohms, 260W r.m.s. into 3 ohms, with a transient power of 600VA into 2 ohms. A complete system, including pre-amplifier, ready built is **£385** plus leads or in kit form for **£277** plus leads, the price you might pay for a low power system. The full range is described in our information.

Our power amplifier kits are supplied with ready built and tested printed circuit boards and are complete down to the last washer. They require only simple assembly and point to point wiring following the detailed instructions and wiring diagrams.

Pre-Amplifier, built 102, **£80.41**; kit **£70.95**. Lead, AC1, **£3.98**. 45W, 202 built, **£131.27**; P2 kit **£87.28**. 110W, 204 built, **£153.42**; P4 kit **£109.42**.

### MODULES, SUPPLIES

The module used in the 102 pre-amplifier is available separately as the C2, at **£51.75**, and is complete including all pots, switches and sockets requiring only a  $\pm 25V$  supply a kit for which the CS1 is **£12.13**.

We have the widest range of power amplifier modules, from 45 to 260W r.m.s. in the popular L bracket mounting up to 170W "module rating" and in medium and high dissipation formats using large separate heatsinks. These achieve the highest standard of reproduction but can be used in stage or P.A. applications. We also have power supplies for use with these modules, all using toroidal transformers. Our largest is for two 260W modules, using a massive 500VA transformer. Full details in our information. We have too many items to describe in such a small space but here are a few examples:


QE1708 — L bracket mounting giving 150W r.m.s. / 8 ohms on our MS3 supply **£31.96**  
 M1508 — As QE1708 but with the power transistors mounted on a 76mm heatsink **£35.79**  
 MS3 — Toroidal power supply for 1 or 2 QE1708s or M1508s **£26.28**  
 M2603 — Giving 150W/8 ohms, 260W r.m.s. / 3 ohms this uses four 150W power transistors mounted on two 76mm heatsinks **£50.28**  
 MS5 — Toroidal power supply for 1 or 2 MS2603 **£39.58**

## 10% OFF!

**YES! IF YOU SEND AN ORDER TO REACH US BY 14 JULY ENCLOSING THIS AD. YOU CAN DEDUCT 10% FROM ALL OUR NORMAL PRICES! BEAT THAT!**

### \* NEW SPEAKER KITS \*

Have you wondered why the existing sources of speaker kits offer a bewildering choice of systems, particularly combinations of 200mm bass unit and tweeter? Don't they know which ones are best? If so, why bother with the rest! Well we have sorted out these super kits so you can order in confidence, knowing you get our full endorsement of their performance and value. The kits incorporate professionally finished front baffles with the drive units already mounted so all the fiddly work is done for you. All that is left to do is to make a simple box. Crossover networks, foam and terminals are also included.

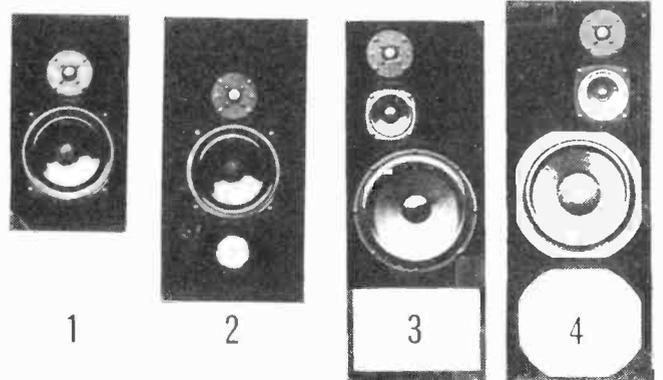

**System 1.** Small bookshelf design using Son Audax 200mm bass unit and 25mm dome tweeter, giving very good results from a small enclosure.


**System 2.** Using similar drive units to system 1 this is a larger reflex design intended to be used on a stand. We can enthusiastically recommend this as the best 2-unit kit we have heard to date with a smooth and extended bass response and excellent stereo image.

**System 3.** A 3-way I.B. system using a Seas 250mm bass unit, Seas 120mm midrange and Son Audax 25mm dome tweeter. A floor standing design cleverly incorporating a stand at the bottom of the enclosure. Order now for August delivery.

**System 4.** The most sophisticated, most expensive and undeniably the best speaker kit on the market using a 250mm Volt bass unit with a 250mm Volt ABR for the bass, a very specially treated Peerless mid range unit and a Son Audax 25mm dome tweeter. The Rolls Royce of speaker kits comes with the active drive units mounted on the front baffle and the ABR on the rear baffle. A floor mounting design incorporating a stand as above. Excellent bass response and smooth untiring mid band and treble are the result of countless hours of dedicated development by one of the country's leading designers. Capable of very high sound levels when used with a good amplifier, such as our 205s. Orders accepted now for August delivery.

We will also be retailing selected drive units at competitive prices. Please ask for details.

System 1 **£69.00**. System 2 **£89.00**. System 3 **£159.00**. System 4 **£359.00**. Son Audax 200mm bass, 20B25J4 **£13.50**. 25mm tweeter, HD100D25 **£9.00**.

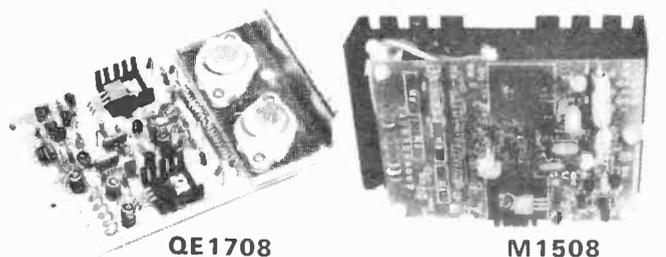

QE1708

M1508

### 8 ALBION ST., LEICESTER

Write or phone for our full information. All prices include VAT and carriage. Export is no problem — all equipment can be wired for 110V — send for quote by return.

Enquiries are invited from retailers and trade. Excellent discounts available.

If you don't see what you want, ask. Tel: (0533) 546198.

# ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).


## PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

<b>038A</b>	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79	<b>049A</b>	ETI 80 - VCO and VCLFO	Feb 80	<b>032B</b> <b>033</b>	Fuel Level Monitor, Alarm, screen controller Dynamic Noise Reducer	Sep 79
<b>038B</b>	Hum Filter Dice Logic Probe	Dec 79	<b>040B</b>	ETI 80 - PSU Tuning Fork Filter Coin Toss	Feb 80	<b>040A</b> <b>042B</b>	Touch Dimmer, Battery Charger RC Guardian (Top,Bottom)1&2	Apr 80
<b>038C</b>	Function Generator	Dec 79	<b>041A</b>	ETI Audiophile ETI VCA Signal Trace ETI HC Electromyogram	Mar 80	<b>043</b>	IR60 preamp, Receiver, PSU, Servo Tester, VU-PPM	May 80
<b>039</b>	Buffer Moving Coil Preamp Process Controller	Jan 80	<b>041B</b>	VCM Heater Controller	Mar 80	<b>044A</b>	IR60 Function Board (Top & underside) Control Circuit, Line Transmitter, Tape Response Meter Ohmmeter	June 80
<b>039A</b>	Hum Filter Logic Probe	Dec 79	<b>042A</b>	300W Amp Module	Apr 80	<b>044B</b>	FM receiver PSU & Monitor Amp Drum Synth (function board)	June 80
<b>039B</b>	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79	<b>033</b>	Fuel Level Monitor, Alarm, Screen Controller Dynamic Noise Reducer	Sep 79			
<b>039C</b>	Function Generator	Dec 79	<b>042B</b>	Touch Dimmer, Battery Charger, RC Guardian (Top, Bottom) 1 & 2	Apr 80			
			<b>043</b>	IR60 Preamps, Receiver, PSU, Servo Tester VU-PPM	May 80			

## HOW IT WORKS

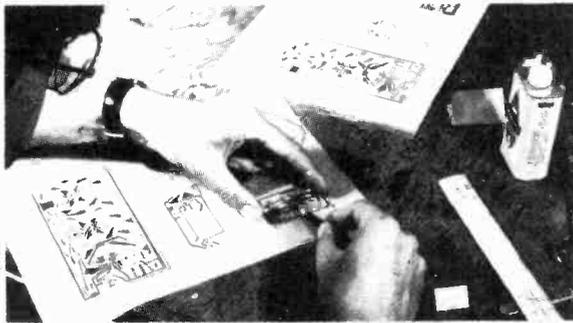

*Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!*

## BUY LINES

### ORDER TODAY


Send a cheque or P O (payable to ETI Magazine) to  
ETI PRINT, ETI MAGAZINE  
145 Charing Cross Road, London WC2H 0EE

**95p** INC P & P

# SUPERIOR QUALITY AND RELIABILITY
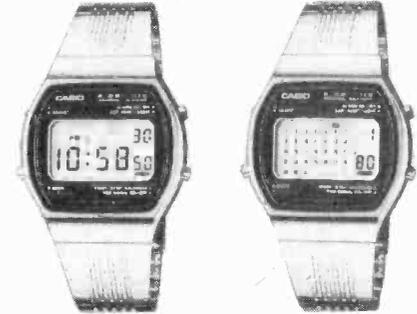
## CASIO'S NEW EXECUTIVE WATCH

**79CS-51B ALARM CHRONOGRAPH**  
Full month calendar, tone control, hourly chimes



Hours, minutes, seconds, am/pm and date. Calendar display. Day, date, month and year. Monthly calendar from the year 1901 to 2099. 1/10 sec. stopwatch to 12hrs. Net, lap, 1st & 2nd. 24-hour alarm with 10 step tone control. Hourly chimes, backlight, lithium battery. **Stainless steel case 8.6mm thick. Mineral glass, water resistant.** (RRP £44.95)

**£39.95**

## OUR BEST-SELLING WATCH

### CASIO C-80 CALCULATOR WATCH

(Finger-touch keyboard). Hours, minutes, seconds, am/pm, day, date, month, auto calendar pre-programmed to 2009. Professional 24-hour stopwatch: net, lap, 1st & 2nd place to 1/100 sec. **Dual time. (24-hour).** Nightlight. 8 digit calculator. **Water resistant.** Glass. Black resin case/strap. 44.9mmx35.8x10.2mm

**ONLY £24.95**

Hundreds sold!



**F-80.** As above but with black resin case/strap with S/S back and front trim.

**£19.95**

**NOW AVAILABLE GOLD PLATED**

**83 QGS-41B (RRP £44.95)**

**£39.95**

F-8C **£9.95**; 111QS-34B **£14.95**; F-200 **£12.95**; 95QS-42B **£17.95**; 95QS-36B **£19.95**; 56QS-38B **£24.95**; 56QS-50B **£34.95**; B1QS-40B **£24.95**; 29CS-49B **£29.95**.

**LADIES' CASIO** 10 models from **£12.95**



### 83QS-41B ALARM CHRONOGRAPH

S/S encased. Mineral glass. Water resistant. 3 YEAR BATTERY. Hours, minutes, seconds, date, am/pm, or hours, minutes, alpha day, date am/pm, 24-hour alarm, hourly chimes. Stopwatch from 1-10 second to 12 hours; net, lap and 1st and 2nd place. Nightlight.


**ONLY £24.95**

## NEW 11-NOTE MELODY MAKER

**CASIO ML-82**


Clock, calendar, musical alarm, hourly chimes, 1/10 second stopwatch to 24 hours, net, lap and 1st & 2nd place. Calculator with musical keys, full memory, %, square roots. 9/32 x 2 1/2 x 4 3/4 inches. ONE YEAR BATTERIES (RRP £22.95)

**£19.95**

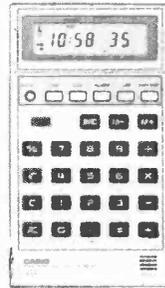

## NEW METRIC CONVERTER / CALCULATOR

**CASIO MC-34 CARD**

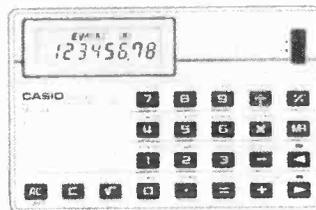


34 conversion functions, 17 metric, 17 reversible. Distances, weights, areas, volumes and temperatures. Calculator with GT memory, %, square roots, 1,100 hours batteries. 5/32 x 3 3/4 x 2 1/2 ins.

(£13.95) **£11.95**

**Casio's guarantee is only valid if goods are purchased from an authorised dealer, who WON'T advertise lower prices than ours. Nevertheless we promise to BEAT (sensible) lower prices IF the advertisers have stocks.**

**Send for our FREE LEAFLET "The whole truth about digital watches."**

## OUR BEST SELLING CALCULATOR

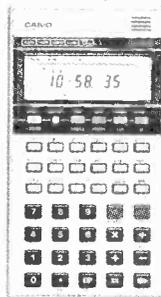

**FX-8100**

1 YEAR BATTERIES. Hours, minutes, seconds, am/pm, day. Calendar pre-programmed to year 1999. 24-hour alarm. Alarm timer interval timer, or 1/100 second stopwatch: net, lap, 1st and 2nd, place Fractions, % cube roots, 5 levels parentheses, hyperbolics, standard deviations, co-ordinates, conversions. X to Y, X to M. 1/4x2 3/4x5 1/8" (RRP £27.95)

**ONLY £24.95**

**HUNDREDS SOLD!**

## OTHER CALCULATORS

**WITH CLOCK, ETC.**

PW-81 **£14.95**; AQ-1500 **£14.95**; MQ-6 **£19.95**; MQ-12 **£19.95**; AQ-2200 **£19.95**; ML-71 **£22.95**; ML-81 **£22.95**; HR-10 **£29.95**.

**SCIENTIFICS. With clock.** FX-7100 **£24.95**. Others: FX-81 **£12.95**; FX-100 **£15.95**; FX-330 **£15.95**; FX-510 **£19.95**; FX-3200 **£21.95**.

# SEIKO

**PRICES SLASHED!**

## TS1 Alarm Chronograph



With countdown alarm. Hours, minutes, seconds, alpha day and date on upper display; and day, date, month, alarm and hourly chimes. Countdown alarm (upper display). Stopwatch from 1/100 sec to 12 hours; net, lap, and 1st and 2nd place times. Stainless steel. Glass.

**Only £44.95**

## TS7 Alarm Chronograph

100M Water Resistant. Suitable for swimming, water skiing etc. Hours, minutes, seconds, day, date and month. Programmable weekly alarm. Interval alarm timer up to 16 hours. Hourly chimes. Stopwatch, 1/100 second to 20 minutes, then seconds to 12 hours. Upper display — lap times. Lower display — Total time.



**ONLY £64.95**

## TS5 World Time / Alarm



Two Alarms, local and world time (dual tones). Hourly chimes. Normally displays hours, minutes, seconds, day, or optionally hours, minutes, day, date, month. World time mode displays an atlas with each of the 19 time zones highlighted when selected. Date and summer time functions.

**Stainless £59.95**  
**Gold Plated £84.95**

## TS4 Calculator Alarm

Hours, minutes, seconds, day and date, month, am/pm. Alarm (2 tones) hourly chimes. 8 digit calculator with constants, delta, %. Water resistant. 2 year battery with hatch. Approx. 9mm thick + 0.5mm for keys.



**Stainless £59.95**  
**Gold Plated**  
**£84.95**

## TS2 Alarm Chronograph



Comprehensive display of hours, minutes, seconds, day, date and month. 24 hour alarm and hourly chimes. Stopwatch from 1/100 second to 20 minutes, then seconds to 20 hours. Upper display—lap times. Lower display—total time. S/Steel encased—8mm thick plus front buttons.

**Only £39.95**

## ILLUSTRATED CATALOGUE

Casio and Seiko products. Send 25p to: TEMPUS (Information and Service Centre), 19-21 Fitzroy Street, Cambridge CB1 1EH. (Refundable on purchase).

## RETURN OF POST SERVICE

Postal and telephone orders received before 4.00 p.m. will normally be despatched the same day by FIRST CLASS POST

Send your order by **FREEPOST** (2nd class post — no stamp required). Please phone urgent orders or use first class mail.


**PRICE includes VAT, P&P. Send your Company Order, Cheque or P.O. or phone your ACCESS or B'CARD number to:**

# TEMPUS

**Tempus (Dept. ETI)**  
**FREEPOST, 164-167 East Road**  
**Cambridge CB1 1BR. Tel. 0223 312866**

**MONEY SAVING BARGAIN**  
EX-STOCK FROM US

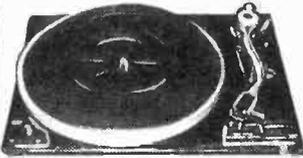**J.V.C. BELT DRIVEN**  
**TURNTABLE**  
WITH STEREO MAGNETIC  
AUDIO TECHNICA  
CARTRIDGE



**LIST PRICE OVER £50**

J.V.C. Turntable supplied complete with Audio Technica AT10 stereo magnetic cartridge. Belt driven

- \* 'S' shaped tone arm.
- \* Modern design
- \* Full size 12" platter.
- \* Calibrated counter balance weight (0.3 grms).
- \* Anti-skate (bias) device.
- \* Size — 12 3/4" x 15 3/4" (approx)

AT ONLY  
**LIMITED STOCKS £25.99**  
PLUS VAT £3.89 Post £2 50

**GEC HIGH QUALITY STEREO**

**10 + 10 watt AMPLIFIER**  
**WITH AM/FM STEREO TUNER**  
**IDEAL FOR THE HOME**

A cancelled export order brings you this offer from the world-famous firm of G.E.C.

AM/FM stereo Tuner Amplifier Ready built. Comprising of a tuner/pre-amp. board and separate power supply/power amp. board with wiring diagram.  
Rotary Controls: Tuning, on/off volume, balance, treble, bass, Stereo Beacon indicator.  
Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), LW, MW, SW.

Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.

Frequency Response: 60Hz-20KHz within  $\pm 3$ dB.  
Tape Sensitivity: Output — typically 150 mv. Input — 300 mv for rated output.

Disc Sensitivity: 100 mv (ceramic cartridge)  
Radio: FM (VHF) 87.5MHz-108MHz.


Long Wave 145KHz-265KHz

Medium Wave 520KHz-1620KHz.

Short Wave 5.8KHz-16MHz.

Size: Tuner — 2 1/2 in. x 1 1/2 in. x 7 1/2 in. Power Amp — 2 in. x 7 1/2 in. x 4 1/2 in.

**LOW PRICE OFFER**

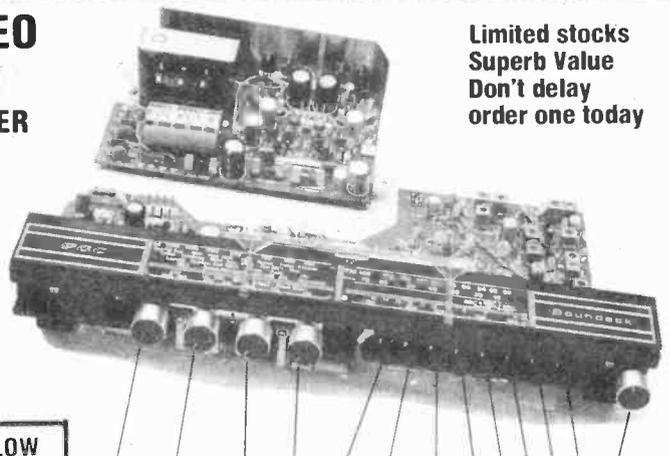

ON/OFF BALANCE, TREBLE, BASS, MONO TAPE Phono AFC FM LW MW SW Tuning, Volume

**Fully Guaranteed Ex-Stock**

**SUITABLE SPEAKERS IN CABINETS**


**PAIR 10 WATTS**

**£19.95 INC. VAT**

POST £2.50 Pair

**ONLY £19.95**  
+ VAT £2.99  
CARRIAGE £2 50

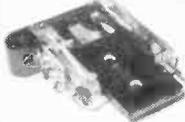**CAR STEREO CASSETTE MECHANISM made for MOTOROLA**



- \* Front loading 12 volt transistorised
- \* Speed & Voltage control
- \* Ex-equipment — Tested O.K.

- \* Limited stocks
- \* Size
- \* Takes standard C60 cassette

**ONLY £7.50**

INC. VAT  
POST 80p



**Henry's**  
Phone (01) 723 1008/9  
404 Edgware Road, London W2, England I.E.D.



PRO M25 Professional capacitor boom-arm microphone by Eagle. A graceful 60 cm boom-arm capacitor studio microphone using a cardioid capsule. A high standard of finish for in-vision use and yet robust enough to withstand long periods between maintenance. Supplied complete with 1 red and 1 black windshield and 6 metres of twin screened cable terminating at the microphone end in an XLR connector.  
Impedance: 600 ohms (floating). Response: 20-18,000 Hz. Sensitivity: -70 dBV.  
Cable: 6 metres two conductor shielded. Connector: XLR 3-11C. Battery type: HP7.

**LIST PRICE £37.40**  
**OUR PRICE £19.95**  
inc VAT  
POST £1 50


**PORTABLE PRECISION**

A RANGE OF 3 1/2 DIGIT LCD MULTIMETERS OFFERING HIGH PRECISION AND EXTENDED BATTERY LIFE. ALL TYPES FEATURE FIVE FUNCTION OPERATION (AC AND DC VOLTS, AC AND DC CURRENT, RESISTANCE) WITH ABILITY TO CHECK DIODES. 0.5" LCD DISPLAY WITH 'BATTERY LOW' WARNING. AUTO-POLARITY, AUTO-ZERO. FULL PROTECTION AGAINST TRANSIENTS AND OVERLOADS WITH ABILITY TO WITHSTAND MAINS ON ANY RANGE. RUGGED ABS CASES AND A COMPREHENSIVE 1-YEAR WARRANTY.

The LMM-200 is a compact handheld multimeter with 0.5% basic accuracy and 15 different ranges. It measures AC/DC voltage from 0.1mV to 500V, AC/DC current from 0.1  $\mu$ A to 2 Amps and resistance from 0.1  $\Omega$  to 2M $\Omega$ . 200 hour battery life.

The LMM-2001 is an identical instrument but with a 0.1% basic accuracy.

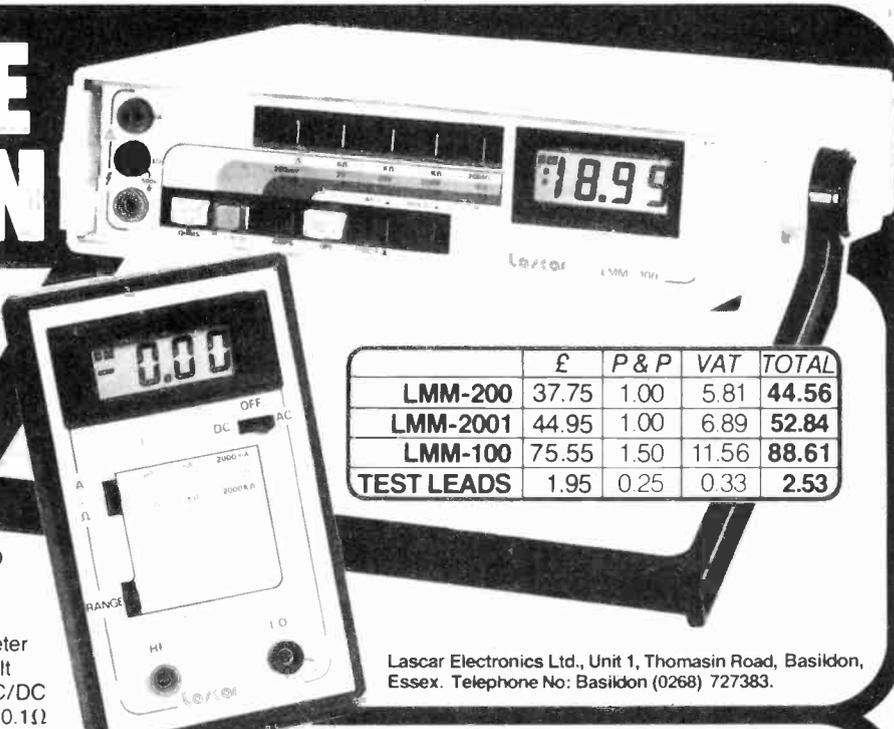The LMM-100 is suitable for field or bench use. It has a basic accuracy of 0.1% and 25 different ranges. It measures AC/DC voltage from 0.1mV to 1KV, AC/DC current from 0.1  $\mu$ A to 2 Amps and resistance from 0.1  $\Omega$  to 20M $\Omega$ . Battery life is over 2,000 hours. It also features a unique 'digital hold' facility and adjustable carrying handle.



	£	P & P	VAT	TOTAL
LMM-200	37.75	1.00	5.81	44.56
LMM-2001	44.95	1.00	6.89	52.84
LMM-100	75.55	1.50	11.56	88.61
TEST LEADS	1.95	0.25	0.33	2.53

Lascas Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.

To: Lascas Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data

LMM-100 £88.61  LMM-200 £44.56  LMM-2001 £52.84  TEST LEADS £2.53

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel No \_\_\_\_\_

I enclose cheque/P O value \_\_\_\_\_

# LOUDSPEAKER PROTECTION MODULE

**M**odern transistor power amplifiers use the technique of DC coupling between the low level amplifier stages and between the output stages and the loudspeaker. This has the advantage of removing coupling capacitors from the signal path, decreasing parts count and improving performance at low frequencies.

Older transistor amplifiers used a single supply rail so the transistors operated between the supply voltage and ground. Since an AC signal has both negative and positive excursions the power amp was designed so that a DC voltage was present on the output stage. Positive excursions would cause an increase of this DC voltage while negative excursions decrease the voltage. Since DC cannot be applied directly to a loudspeaker it was necessary to insert a capacitor, called a blocking or output capacitor, between the output stage and the loudspeaker. The load impedance of the loudspeaker is around  $8R$  so the capacitor has to be 5000  $\mu F$  to 10,000  $\mu F$  before an acceptable low end performance can be obtained.


The solution to these problems was DC coupling. The power amp is run from a 'split supply' so that the output transistors are supplied from a positive and negative supply voltage. The average of these supply rails is zero volts, so the output can be connected directly to the loudspeaker. Both positive and negative excursions are possible due to the split power supply.

## Coupling Fault

Unfortunately, DC coupling also has its disadvantages. The biggest of these is the possibility of damage to the loudspeakers in the case of power amp failure. Since all the stages are DC coupled, a fault anywhere in the power amp can cause the output stage to swing hard against one of the supply rails. The most common power amp fault is a condition in which one or several of the output or driver transistors is destroyed, and this almost always causes the full DC voltage from one of the supply rails to be applied directly to the loudspeaker. The loudspeaker cone is slammed against the suspension and the power dissipation in the voice coil causes a rapid increase of voice coil temperature. In this condition most woofers will survive for only a few seconds.

This type of fault is all too common and is the most expensive fault likely to occur in a modern hi-fi system. Some top line amplifiers have built in protection circuits with relays that disconnect the loudspeakers should this condition occur, but these are the minority.

**Make your loudspeakers immune to everything except music and the End of The World with our comprehensive protection circuit.**

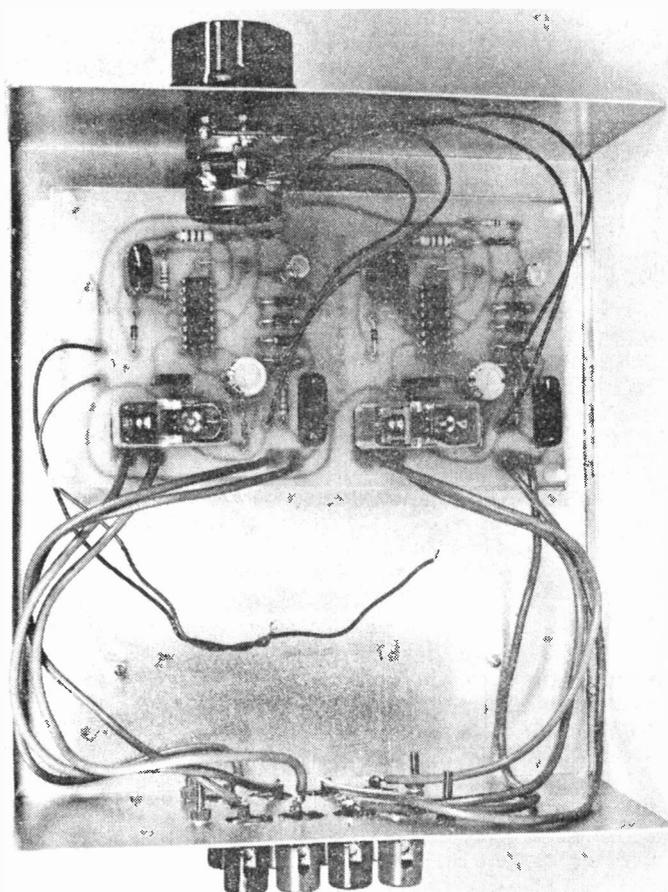

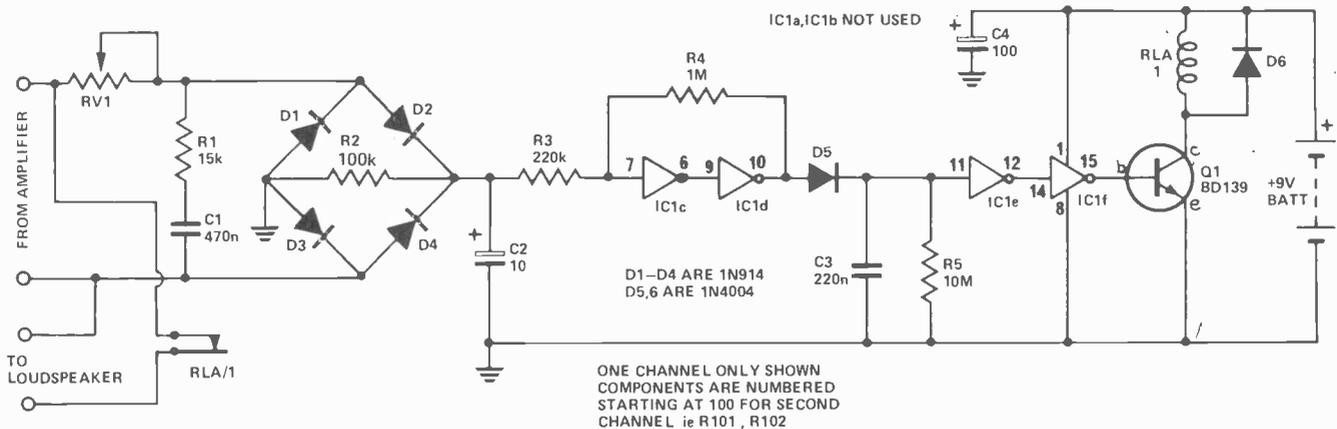


Fig.1 (above) The circuit diagram for the loudspeaker protection unit. Note that one channel only is shown and that on the PCB components for the second channel are numbered from 100 to avoid confusion. Relay RLA1 should be a 12 V type with the facility for one, at least, pair of changeover contacts. This project has been designed such that it does

not place a significant load upon the amplifier itself during usage, such that the damping to the speaker is unaffected. Secondly the high input impedance of the protector ensures that a load-sensitive amplifier is unlikely to be pushed into colouration by your decision to save your loudspeakers from destruction if it cracks up.

## Remedy

This circuit 'looks' at the loudspeaker wires and protects the loudspeakers in two ways. The presence of any DC automatically trips the relay and disconnects the loudspeaker. The protector also looks at the amount of power applied to the loudspeaker. It allows high power transients but will disconnect the loudspeaker if the applied power exceeds the loudspeaker rating for more than about 50 milliseconds. In this way the advantage of the improved high power amplifiers is not lost but the loudspeaker is still protected. The circuit includes a two-second monostable delay circuit so that the loudspeaker is automatically reconnected approximately two seconds after the 'fault condition' has been removed.

The project is designed around two standard CMOS ICs. This ensures a very low current consumption and obviates the need for a power switch. This is important since a fault with an amplifier could well occur at the moment of turn-on and it is essential that the loudspeaker protector is already on. When the relay trips, the circuit pulls around 50 mA for each relay so it is important that battery is capable of supplying 100 mA during relay operation. There should be no problem with the battery lasting for its shelf life, providing the relays are not tripped more than very occasionally.

## Construction

Solder the resistors, capacitors, diodes and relay first. The diodes and electrolytic capacitors must be inserted the right way round as shown on the pc board overlay. Lastly, solder the transistors and ICs on the board. Again, these devices must be oriented correctly.

The prototype was constructed in a general purpose steel box but this is not critical. The front panel is fitted with a stereo 100k potentiometer. This sets the trip point of the protector so that it can be adjusted for your particular loudspeakers. The rear panel holds the terminals for the wires from the amplifier and loudspeakers. The wiring to the rear panel and to the front potentiometer is shown in the wiring diagram.

Finally, make the connection to the battery.


## HOW IT WORKS

The signal voltage from the amplifier is rectified by a full-wave bridge consisting of diodes D1, D2, D3 and D4. The potentiometer RV1 and the resistor R1 and capacitor C1 form a potential divider that determines the sensitivity of the circuit. At normal signal frequencies C1 has a relatively low impedance and the resistance across the diode bridge becomes that of resistor R1, i.e.: 15 k. As the frequency approaches DC however, the impedance of this capacitor increases, increasing the sensitivity of the circuit. If a DC voltage is presented to the input C1 acts as an open circuit and the protector is therefore at its most sensitive.

Signal voltages from the full wave rectifier are averaged by the capacitor C2 and R2, and then applied to a Schmitt trigger. The Schmitt trigger is formed from the resistors R3, R4, IC1c and IC1d. This circuit will only respond to a voltage level greater than a preset amount. When this voltage is exceeded (around 6V5 in this case) the output goes positive charging C3 through diode D5. This diode prevents C3 from being discharged by the Schmitt trigger when its output goes low again so the capacitor can only be discharged by the 10 M resistor R5. This takes about two seconds to this circuit is in reality a simple and effective monostable. Another two stages of the IC drive the transistor which is in series with the relay coil. Diode D6 protects the transistor from large back-EMF voltage spikes produced when the relay is turned off.
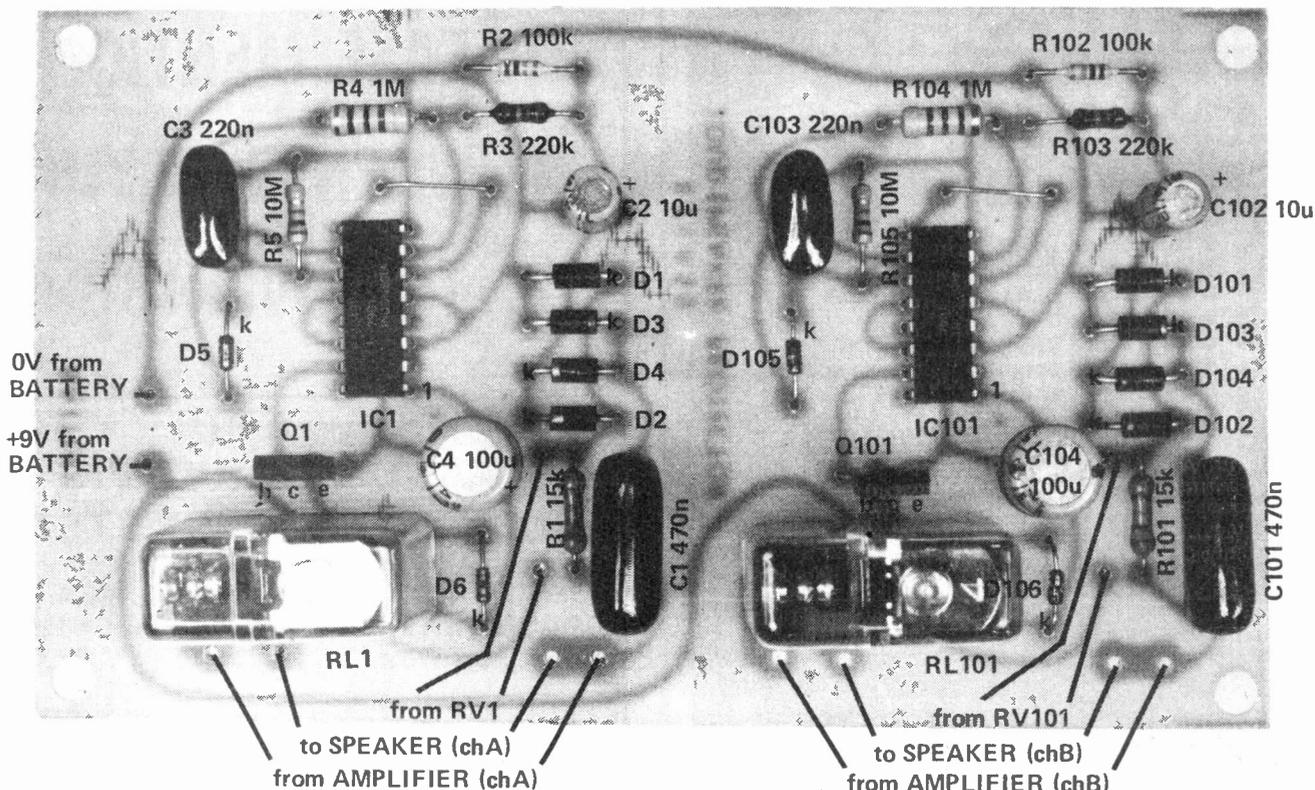
## Testing

Check the orientation of all polarised components including the transistors and ICs. If all is well cut two short lengths of speaker cable and connect the output of the amplifier to the input of the loudspeaker protector. Connect the speaker cables to the output of the protector. Now switch on the hi-fi system. Choose music with reasonably even amplitude for this test. Turn the front panel level control on the loudspeaker protector for the lowest power and slowly increase the amplifier volume.



## PARTS LIST

Two of each of the following is required for stereo.

Resistors all  $\frac{1}{2}W$ , 5%

R1 15k  
R2 100k  
R3 220k  
R4 1M  
R5 10M

Potentiometers

RV1 100k lin. (dual)

Capacitors

C1 470n polyester  
C2 10u 25V electrolytic  
C3 220n polyester  
C4 100u 25V electrolytic

Semiconductors

Q1 BD139  
D1-D4 1N4002, or similar  
D5, D6 1N914 or similar  
IC1 4049B

Fig.2. (above) The component overlay for a stereo version of the loudspeaker protection module. Note the '100 upwards' component numbering of the second channel. Apart from the battery connections, the PCB is, in fact, symmetrical. Mains power was not employed because it is important that the module is operating at amplifier power up and the best way to ensure this is to use battery power! In normal use the battery (PP6) will last well-nigh its normal shelf-life as it draws virtually zero power until tripped. If you run the circuit so that it continually operates something is amiss — so stop it!

## BUYLINES

Nothing unusual used in this circuit, so your local neighbourhood component emporium should be able to supply with no problems.

One thing we have heard in the past is that high value 5% resistors are not easy to obtain. In this design lower values of R4 and R5 must not be substituted.

When the power to the loudspeakers exceeds that set by the potentiometer the protector should trip in and disconnect the loudspeakers.

Turn the amplifier down, and the loudspeakers should be reconnected after about two seconds. Since loudspeaker power figures are a rather dubious quantity, it is probably best to establish the correct setting for the loudspeaker protector experimentally rather than just setting it to the rated power handling of your loudspeakers. Your ears are the best indication that the

system is being strained. Set the loudspeaker protector so that it trips just below that volume where distortion starts to occur.

We have done extended tests on the protector, even to the point of connecting expensive loudspeakers and inducing power amp faults that would otherwise destroy a loudspeaker in seconds. In all of these tests the loudspeaker protector has performed well and it is a comforting thought that should a power amp fault occur, it will not take your loudspeakers with it.

**ETI**

# All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

## ..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.


The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.

**Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.**
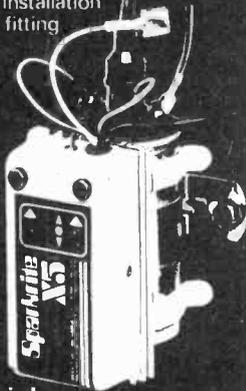
### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."



# Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. ET1/7  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name \_\_\_\_\_

Address \_\_\_\_\_

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D

I enclose cheque/PO's for

X5KIT £16.95

ACCESS OR BARCLAY CARD No.

£

Cheque No.

Send SAE if brochure only required

PLEASE MENTION  
ETI WHEN REPLYING  
TO ADVERTS

## BUILD YOUR OWN FM RADIO CONTROL SYSTEM

TRANSMITTER BASIC KIT £36.00  
RECEIVER KIT ..... £18.40  
SERVOS from ..... £12.00

Send remittance of £2 for circuits and constructional data to:

TELERADIO R/C, 325 FORE STREET, EDMONTON  
LONDON N9 0PE, 01-807 3719

CLOSED THURSDAYS

## — CLEF KITS —



### NEW — ELECTRONIC ROTOR

Two-speed organ rotor simulator plus a three-phase chorus generator on a single PCB (8"x5"). Kit includes all components — IC sockets throughout — mains operation and stereo headphone driver PCB. Easily integrated with existing organ. Component kit £89.00.

### KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

49 NOTE CC £23.80

73 NOTE F-F £37.00

88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

### BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists

### INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted. All prices include V.A.T. carriage & Insurance

### VISITS

Are welcome by appointment, otherwise Mail Order Only.

### EXPORT

Enquiries welcome — in Australia please contact JAYCAR (Sydney)

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

### JOANNA 72 & 88 PIANOS

Six and 7¼ Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use from our top quality Component kits.

SIX OCTAVES — £207

7¼ OCTAVES — £232

### P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT — £169

Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.

### P.A.'s — SPEAKERS — CABINETS


Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

**CLEF PRODUCTS (ELECTRONICS) LIMITED** (Dept. E.T.I.)


16 Mayfield Road, Bramhall, Cheshire SK7 1JU. 061 439 3297
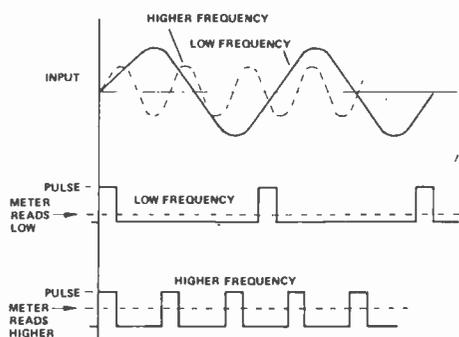
# LINEAR FREQUENCY METER

A project dedicated to all those hundreds of times you've needed to know one cycle from another and been frequently left wanting.



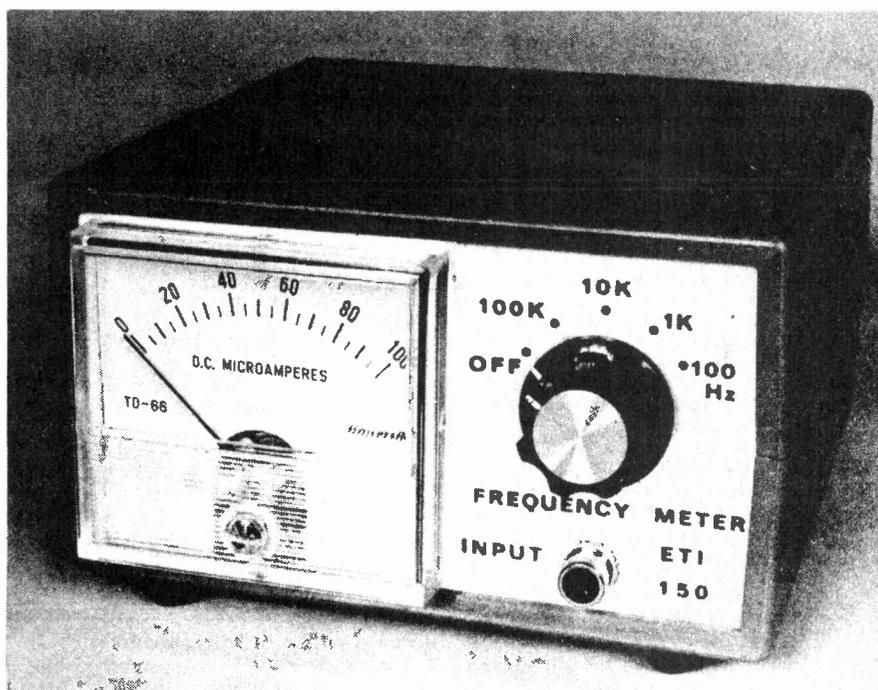Above: waveform diagrams which indicate two possible sources of incorrect reading using a DFM. The drawings are self-explanatory on the whole.



There are many applications in the home workshop where simple audio frequency measurements are required. When experimenting with oscillators, building or repairing function generators etc, it is often handy to have some means of measuring frequency — accuracy to the last Hertz is not always required and thus a full-blown digital counter is not warranted.

This project will enable you to measure frequency from around 100 Hz right up to 100 kHz with an accuracy of a few percent. It is inexpensive to build but performance is quite adequate to meet a large number of needs in any hobbyist's workshop. Accuracy is unaffected by the waveshape of the signal being measured and the unit will accept signal levels as low as 200 mV. The input is fully protected against high signal levels and against DC voltages up to the rating of the input capacitor, C1. The input is also fully floating above earth — a useful feature.

The frequency meter may be powered from an internal 9 V battery or from a battery eliminator. A suitable socket may be installed on the rear of the cabinet.

## Circuit Features

The circuit generates a series of short pulses at the same frequency as the input. These pulses drive a moving-coil meter the current through which will be the average amplitude of the pulse waveform; that is, it will integrate the pulses. This average will be proportional to the ratio of time the pulse is on to the time it is off. The time the pulse is on, that is — the pulse width, is fixed. At low frequencies, the time the pulse is off will be much, much longer than the time the pulse is on. Thus, the average current through the meter will be quite low. At higher frequencies, the time between pulses will be quite short and the average current through the meter will be quite a bit higher (as shown in the diagram). Thus, as the frequency of the pulses is proportional to the input frequency, the pulse on/off ratio, and therefore the meter current, will be proportional to the input frequency. The meter can be calibrated directly in frequency as the relationship is a linear one. We have used a 100  $\mu$ A movement for convenience as it does not have to be rescaled.

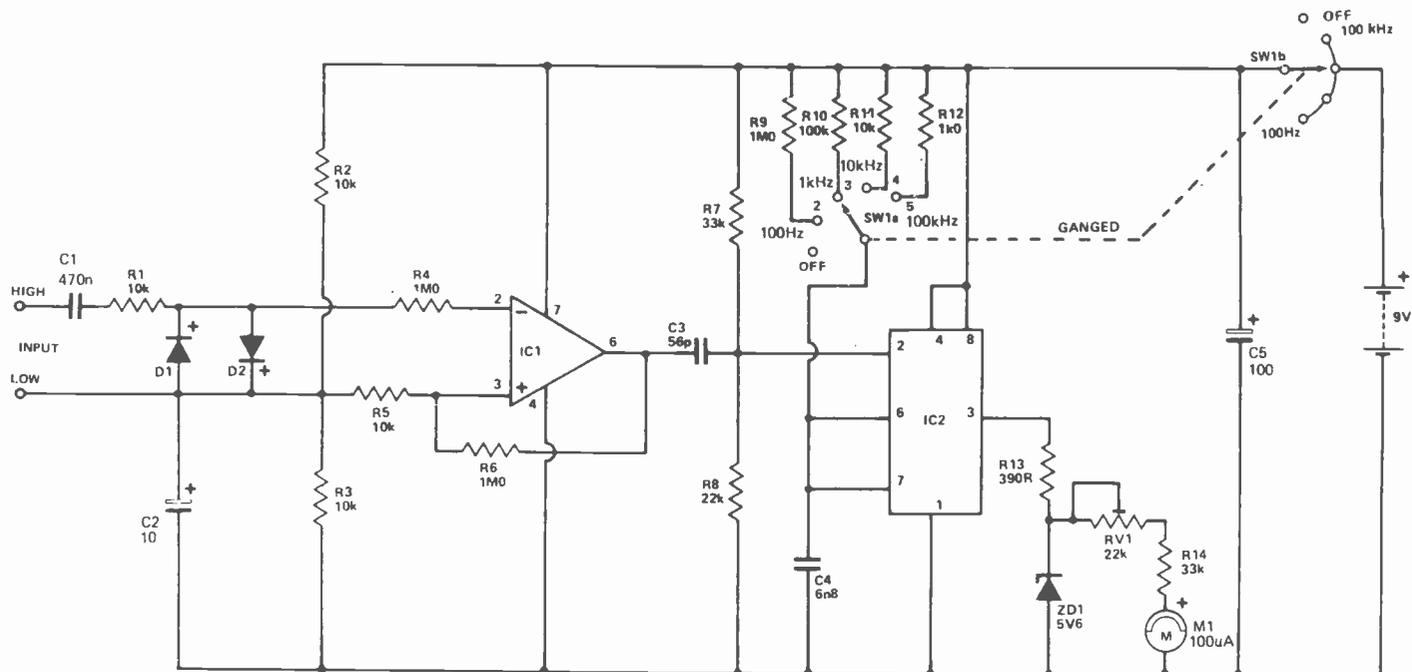


Fig.1. A full circuit diagram for the linear frequency meter.

## HOW IT WORKS

The circuit consists of an op-amp operated as a Schmitt trigger to amplify and square the input signal, followed by a 555 timer wired as a monostable, giving a short output pulse of fixed width for each cycle of input signal. This pulse drives a moving-coil meter, the reading being an average of the pulse amplitude, which is proportional to the pulse frequency. As the pulse frequency is directly related to the input frequency, the meter reading is directly proportional to the input frequency.

The input signal is coupled into IC1 via C1, which provides DC blocking. Protection from overload caused by high amplitude input signals is provided by a diode clipper consisting of D1, D2 and R1. The diodes are connected in an inverse-parallel arrangement so that both positive and negative peaks, above the diode forward conduction voltage, are clipped.

IC1 is a fast op-amp connected as a Schmitt trigger with amplification, as mentioned above. Resistors R5 and R6 provide hysteresis, a 'dead band' in the action of the Schmitt, centred on zero input level. This dead band ensures that the Schmitt ignores noise pulses.

As the unit is required to operate from a single supply, for convenience, R2 and R3 bias the input of IC1 at half the supply voltage.

The output of IC1 is a train of square waves at the same frequency as the input. The output of IC1 is differentiated to provide short trigger pulses for the 555 timer, IC2. The differentiating network consists of C3, R7 and R8. This network is arranged to provide a trigger pulse that is always shorter than the output pulse of the 555. Capacitor C3 is selected to give the shortest possible pulse to the 555 consistent with reliable triggering.

The output of the 555 monostable will be a pulse of fixed width, determined by the range resistors, R9 to R12, and capacitor C4. The ranges are arranged to give a 75% output duty cycle at frequencies of 100 Hz, 1 kHz, 10 kHz and 100 kHz on the input.

The output pulse from the 555 is clipped at 5V6 by a zener diode, ZD1, to avoid inaccuracies caused by falling battery voltage (as the battery ages). The meter responds to the average value of the clipped pulses. As the frequency increases, the duty cycle (on/off ratio) of the pulse train increases, increasing the average voltage and thus the meter current in direct proportion. Thus the reading on the meter will be linearly related to frequency.

The lowest range is 100 Hz full-scale deflection, the highest, 100 kHz.

Only two cheap IC's are used in the whole design, a 3140 op-amp and a 555 timer. The 3140 amplifies and squares the input signal and was selected for its high slew rate, wide frequency response and high input impedance. The output of this stage will be a square wave of the same level for all input signal levels and waveforms.

The pulses are generated by a 555 timer connected as a one-shot monostable giving a single pulse output for each input cycle. The monostable has four ranges giving decade scales on the meter. A fifth position on the switch is used as a power switch.

Regulation of the output pulses by a zener diode preserves the accuracy of the unit with falling battery voltage.

## Construction

As mentioned previously, we constructed our prototype in a plastic box. This has the advantage that the unit can be operated fully floating from earth — handy in some situations. Check placement of components on the front panel and the positioning of the PCB inside before commencing major assembly. It's probably best to assemble the components on the board first. Take care with the orientation of the ICs, diodes and tantalum capacitor.

The input capacitor, C1, can be obtained in several voltage ratings. Polyesters are available in ratings of 100 V, 250 V and 630 V. If all your work is with solid-state circuitry, a 100 V type will be more than adequate. If you anticipate using your unit with say, valve equipment, the highest rating type for C1 is recommended. The rating applies to the combined voltage that may be present on the input, plus the possible peak value of the input signal.

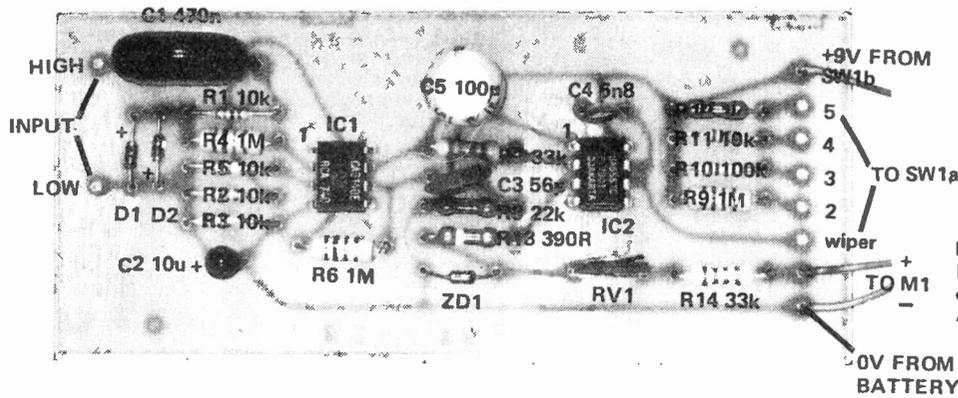


Fig.2. Component overlay for the ETI Linear Frequency Meter. Note the input and output connections from the PCB carefully. A couple of crossed wires here and ...

## PARTS LIST

Resistors All 1/2W, 5%	
R13,5,11	10k
R4,6,9	1M
R7,14	33k
R8	22k
R10	100k
R12	1k
R13	390R
Potentiometer	
PR1	22k Trimmer
Capacitors	
C1	470n polyester
C2	10u tantalum
C3	56p ceramic
C4	6n8 polyester
C5	100u 25V electrolytic
Semiconductors	
D1,2	1N914 or similar
ZD1	5V6, 400mW zener diode
IC1	3140 op amp
IC2	555 timer
Miscellaneous	
M1	100uA meter, SW1 two pole five position wafer switch.

## BUYLINES

As one of the criteria in designing the project was that it would be assembled from easy to obtain bits and pieces, it is (or should be) unlikely that any problems will be encountered in that area! Boxing is not critical at all and the ever-present Vero range would serve as well as the one we employed here.

## SPECIFICATION

Frequency	10Hz to 100kHz in four decade ranges
Minimum input	200 mV RMS
Maximum input	250 V peak AC or DC (dependent on voltage rating of C1)
Supply voltage	9 V

A 630 V rated capacitor will be physically larger than a 100 V type and the leads may have to be shaped to fit the capacitor on the board.

Once the board is assembled, the major components can be assembled onto the front panel of the case. We made up an overlay for the front panel.

The board may be mounted anywhere convenient in the case and wires run to the front panel for the input and switch connections. Make sure the board does not get in the way of the meter when the front panel is in place.

The unit may be powered from an internal battery, which makes it a handy portable unit. If you wish to operate the unit from a plugpack battery eliminator, then we recommend you purchase a unit giving a nominal 6 V DC output. The current requirement for the project is quite modest and the output of these small battery eliminators is dependent on the load. A 6 V unit will typically deliver 9 V or so under a light load.

If you do decide to use one of these units, a socket matching the unit's plug will have to be mounted on the rear panel and leads run to the supply rail pads on the board. If you wish to have the option of both battery and mains operation, then a small SPDT toggle switch should be mounted on the rear panel also and wired into the circuit.

## Calibrating It

Calibration of the frequency meter is very easy, aided by the fact that it has a very high input impedance.

With the unit switched to the 100 Hz range, touch your finger to the input. There will usually be enough 50 Hz field from the electrical wiring in a building to drive the input. This will cause a deflection on the meter and RV1 should then be adjusted to give a meter reading of 50 (half scale). Move the unit near house wiring to increase the amount of signal to the input if a reading cannot be obtained.

If a signal generator of known accuracy is available the instrument can be calibrated on any range. Only one range need be calibrated as the others will automatically fall into line.

If it is impossible to obtain any reading on the meter, the coupling capacitor (C3) may have to be increased in value to say 100pF or 150pF. This component has been selected to give a very short trigger pulse into the 555 and has been found to work correctly, using the value shown in the circuit, with several different ICs.

Selecting the 100 kHz range will connect power to the unit and the unknown signal can then be applied to the input. Set the reading and switch to a lower range if required.

1

**GENTS QUARTZ LCD, 5-function.** Hours, minutes, secs, month, date, backlight.  
**ONLY £4.95**

2

**GENTS QUARTZ LCD, SAME AS 1 - Alternative style.**  
**ONLY £4.95**

3

**QUARTZ LCD Slim Chronograph, 11-function.** Hours, mins, secs, 6 digit-month, date, day of week, 1/100 sec stopwatch, split and lap modes, backlight.  
**ONLY £7.95**


4

**QUARTZ LCD ALARM, 6 digit, hours, mins, secs, day, date. 24-hour alarm with on/off indicator.**  
**ONLY £8.95**

5

**QUARTZ LCD Alarm/Chronograph, 22 functions.** Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split and lap modes, 12 and 24 hour modes, 24 hour alarm.  
**ONLY £14.95**

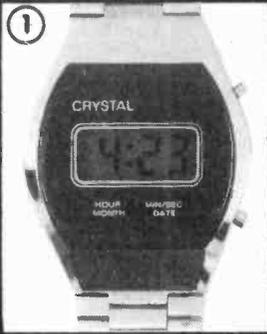We don't believe you can find better value combined with quality, than these - our special introductory prices. Compare the savings we offer and order now.




6

**QUARTZ LCD Musical Multi-Alarm/Chronograph, 6-digit.** Hours, mins, secs, day, date, 1/100 second stopwatch, split and lap modes, 24 hour alarm, countdown timer/alarm, dual time zone.  
**ONLY £14.95**

14

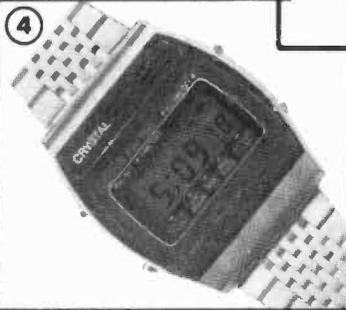**CREDIT CARD CALCULATOR.** Very slim with standard 4 functions plus memory, percentage and square root. Complete with a mock leather wallet with credit card pocket.  
**ONLY £6.95**



7

**QUARTZ LCD Memory Bank/Alarm.** Normal time, alarm and snooze alarm functions with a complete month's calendar displayed at the press of a button.  
**ONLY £16.95**

13

**BELTIME 29F. Alarm/Chrono.** Advanced and accurate, this watch has 8 time functions, 4 alarm functions and 17 chronograph functions. Complete with backlight and stainless steel bracelet.  
**ONLY £19.95**



12

**GENTS ANALOGUE QUARTZ.** Conventional display, accuracy normally associated with digital watches. Automatic calendar, elegant and robust.  
**ONLY £19.95**



8

**LADIES QUARTZ LCD, 5-function as Gents No. 1.** Available with black or white face.  
**ONLY £5.95**


11

**LADIES QUARTZ LCD SAME AS 10.** Alternative "Round" shape. Available in gold or silver colour.  
**ONLY £8.95**



9

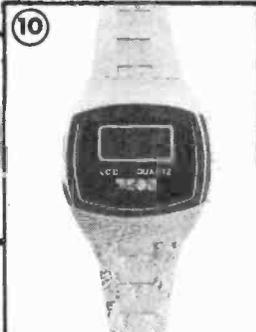**LADIES QUARTZ LCD, SAME FUNCTIONS AS 8.** - Alternative style. Available with black or white face.  
**ONLY £5.95**



10

**LADIES QUARTZ LCD, 5 functions.** Dress Style. Functions same as 1. Available in gold or silver colour.  
**ONLY £8.95**

*All watches have fully adjustable, matching stainless steel straps, and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required.*

*All products carry a Full 7-Day Money-Back Reassurance, plus 12-Month Guarantee. Prices include VAT.*



Send stamped addressed envelope for Colour Brochure of 120 other bargains.

**KEELMOOR LTD**

**78 CASTLE STREET,  
MELBOURNE, DERBY,  
DE7 1DY**

Please send me items ..... (list numbers)

I enclose cheques / POs for £ .....



NAME .....

ADDRESS .....

Please add 35p P/P per item

ET12

# PCB FOIL PATTERNS



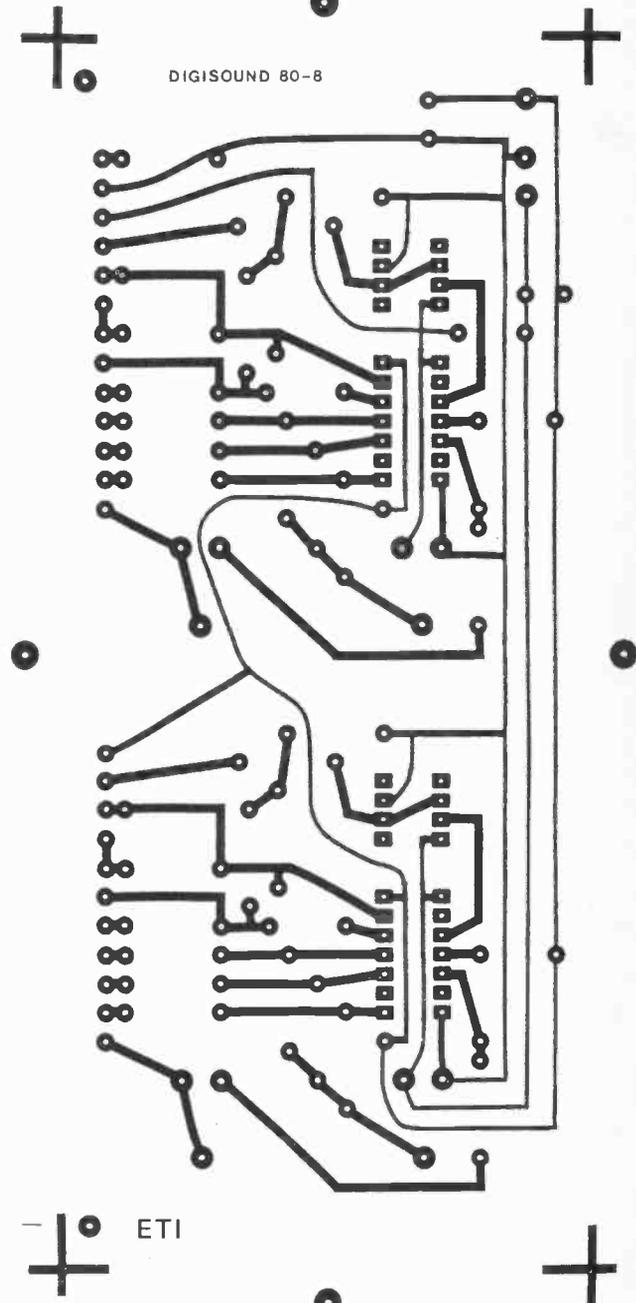
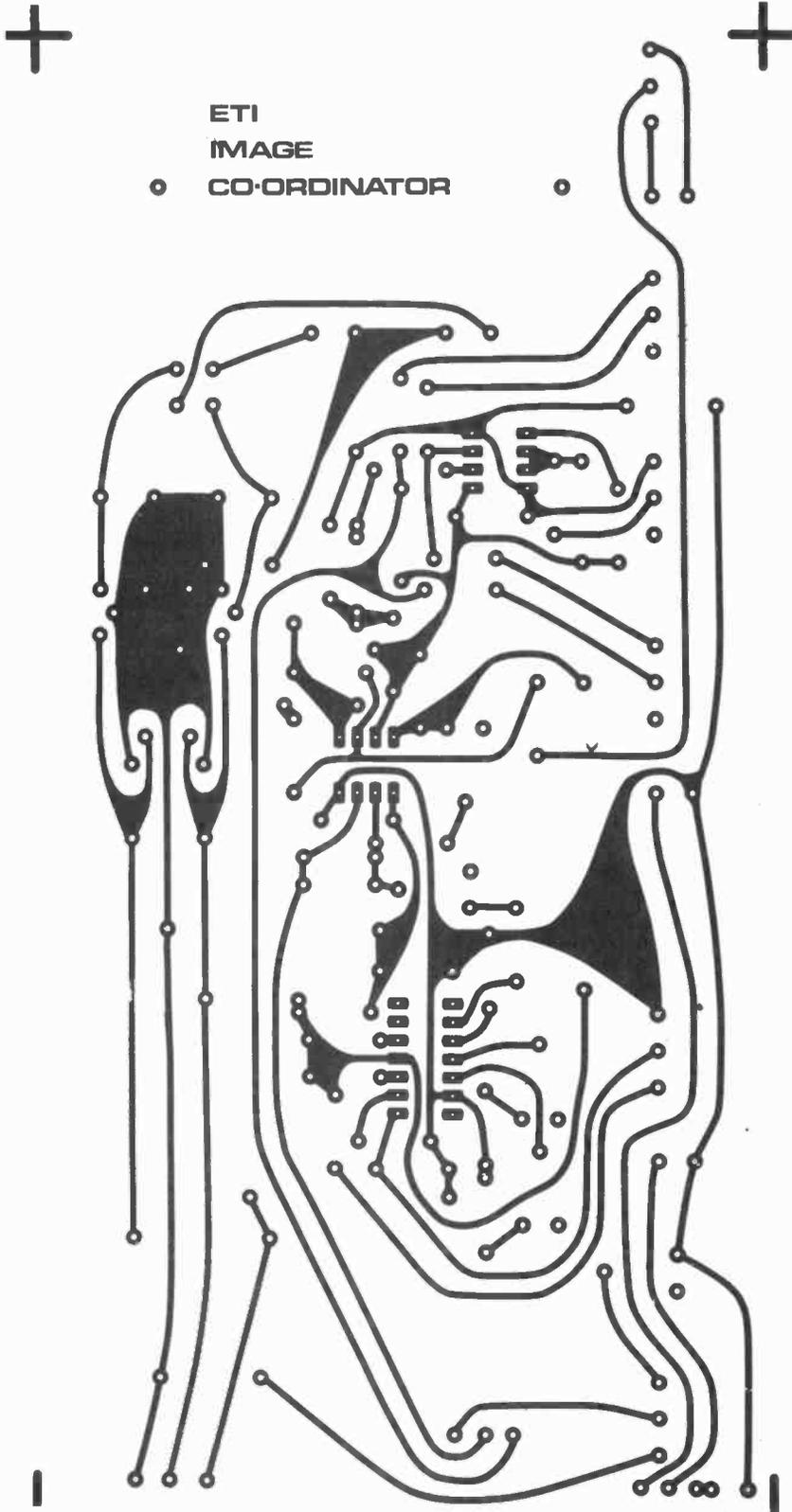


ETI  
IMAGE  
CO-ORDINATOR

Topside

ETI  
IMAGE  
CO-ORDINATOR

Bottom

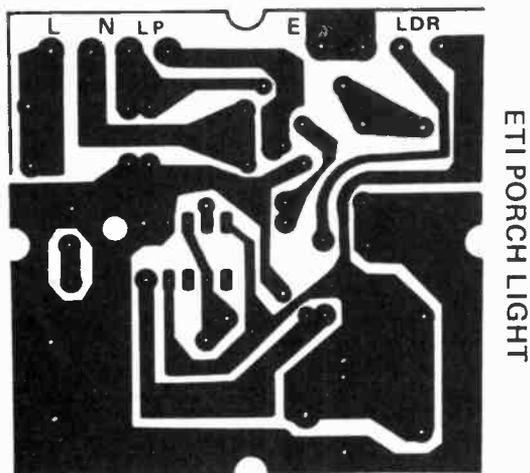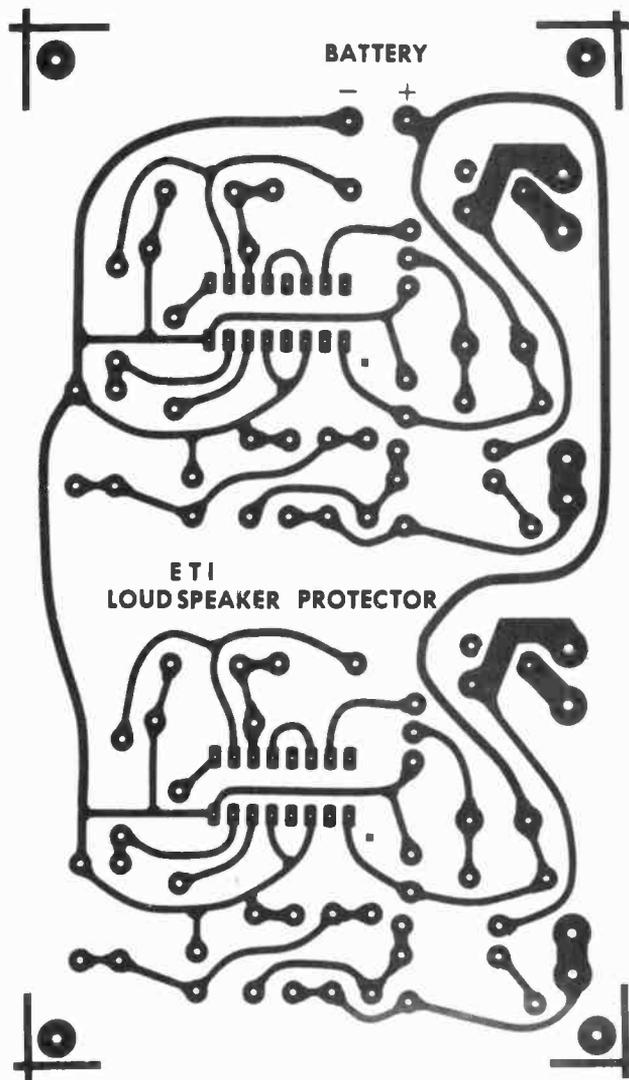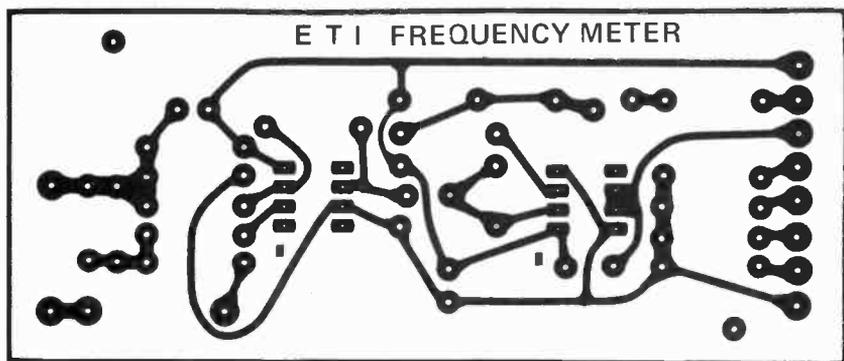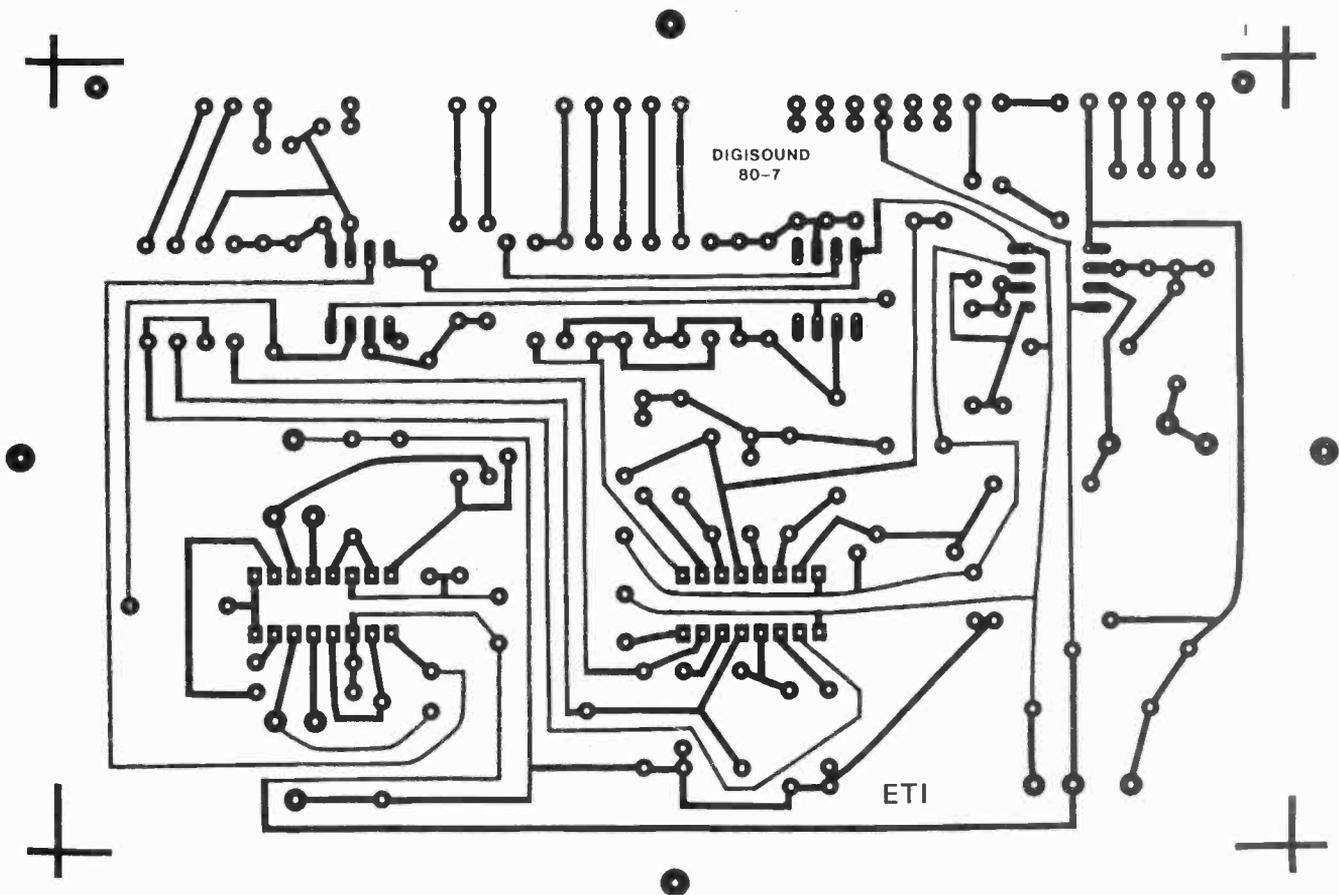

### ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in **£3.00** with all symbols for direct application to P.C. board. Individual sheets 30p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8-10-12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

### FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1.20**.

### GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/8in kit or 1/4in kit. **£1.20** complete. State size.

All orders dispatched promptly.

All post paid

Shop and Trade enquiries welcome  
Special Transfers made to order

**E. R. NICHOLLS  
P.C.B. TRANSFERS**  
DEPT. ET17

**46 LOWFIELD ROAD  
STOCKPORT, CHES. 061-480 2179**

## ARE YOU INTO THE C.B. SCENE?

If so, a 9" x 4" SAE will bring you free details of our carefully selected range of C.B. Accessories.

MAIL ORDER ONLY

Post today to:

## POLAR ENTERPRISES

**2 SWORDS HOUSE  
HIGH STREET  
CROWTHORNE, BERKSHIRE  
TEL. 03446 71714**  
(24-hr. Answering Service)

REMEMBER! UNTIL C.B. BE-  
COMES LEGAL WE DO NOT  
SELL RIGS.

## Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR,  
PORTSMOUTH, HANTS, PO3 5BJ


**REJECT FLUORESCENT CALCULATORS**, modern, fluorescent, 10 function calculators with memory. Most repairable but no guarantees. **£2.99** each. **ALARM CLOCK I.C.** MM5316, brand new, with date **£2.29** each. **POLARIZING FILTER** 0.006" thick plastic film. Any size cut, max. size 15" by 250 feet. **2p** per square inch. **DIGITAL MULTIMETER CHIP** MM53301.C. to build a 4 1/2 digit multimeter. With data **£3.49** each. **WRISTWATCH LCD** supplied with polarizers and data. **99p** each. **0.8" LED DISPLAY** 4 digit, common cathode, with data. **£3.75** each. **LED ALARM CLOCK MODULE** with 0.7" high digits, with data **£5.99** each. **10 UNTESTED LED DISPLAYS** you to test. 0.1" digits, common cathode **99p**. **LED WRISTWATCH I.C.** Mostek MK5030, with data **95p** each. **LED WRISTWATCH DISPLAY** type DIS501. 0.1" digits. (Matches MK5030 I.C.) With data **95p** each. **NOTE** the MK5030 and DIS501 are in "legless flatpack" style package and require some fairly fine soldering. **20 KEY CALCULATOR KEYBOARDS**, 2 for 99p (not for use with NORTEK 4204 calc. chip). **REJECT LED CALCULATORS**, some repairable, but all good value for spares. **£2.50** each. **MINI SLIDE SWITCHES** 2 pole change-over contacts. **15p**. **PUSH-BUTTON SWITCHES** spring loaded (momentary) with one or 0 contact **14p**. **LM555 TIMER I.C.** supplied with applications booklet **23p** each. **LED CALCULATOR DISPLAY** 8 digit, common cathode, multiplexed, 0.1" digits. With data **99p**. **2102 MEMORIES**, Static memories for the micro man. With data **95p**. **CALCULATOR CHIP**, Nortek 4204, 4 function and constant. With data **80p**. **MINI REED RELAYS** 500 ohm coil, 12V d.c. One no.o. contact **79p** each. **QUALITY SUBMINIATURE REED SWITCHES**, brand new, extremely sensitive **39p** each. **4" CABLE TIES**, 25 tywraps for only **35p**.

POST AND PACKING ADD 35p (OVERSEAS ORDERS ADD £1)

**MORE GOODIES IN OUR CATALOGUE. SEND MEDIUM-SIZED S.A.E. FOR YOUR FREE COPY.**

**VAT: ADD 15% TO TOTAL COST (INCLUDING POST AND PACKING)**

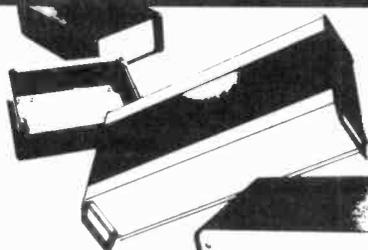**FULL SATISFACTION GUARANTEE ON ALL ITEMS**



### WEST HYDE CASES FOR E.T.I. PROJECTS

**Soil Probe** (July 1979) Order Code BOC 410

**Bench Amplifier** (August 1979) Order Code WEC 801

**Audiophile Pre-Amp** (October 1979) Order Code CL2 CDL

**Audiophile Power Amp** (October 1979) Order Code CL2 CGL

**Audiophile PSU** (October 1979) Order Code CL2 AEL

**Pinball Wizard** (November 1979) Order Code TEK 364

**Points Controller** (December 1979) Order Code BOC 680

**Moving Coil Pre-Amp** (January 1980) Order Code CL2 ADJ

**Synthesiser Project** Order Code TEK A23G

# WH

PLEASE ASK FOR OUR FREE  
80-PAGE CATALOGUE AND PRICE LIST

THE BIGGEST SELECTION OF CASES IN EUROPE



# WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED, UNIT 9, PARK STREET INDUSTRIAL ESTATE, AYLESBURY, BUCKS. TEL: 0296 20441

### 8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory

### 2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code

### GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

### MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters

### KANSAS CITY

low error rate tape interface

**NEW FACTORY UP!  
PRICES DOWN!**

Increased capacity at our big new factory means many prices down! All others frozen!



Cabinet size 19 0" x 15 7" x 3 3" Television not included in price

### 2 MICROPROCESSORS

Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10<sup>-99</sup> to 9 x 19<sup>99</sup> to 8 figures plus 2 exponent digits

### EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

### RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

### 1K MONITOR

resident in EPROM

### SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB

**COMPLETE KIT NOW ONLY**


**£225 + VAT**

# POWERTRAN
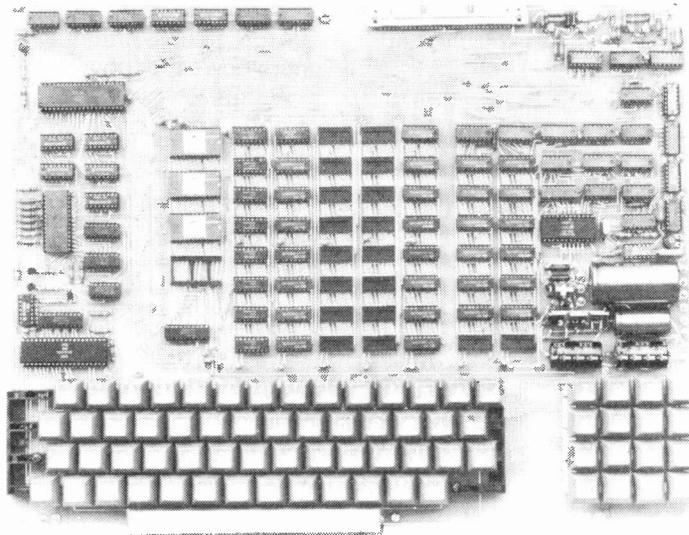
## PSI Comp 80. Z80 Based powerful scientific computer Design as published in Wireless World

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete!

Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer, 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.



Value Added Tax not included in prices

**PRICE STABILITY:** Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until August 31st 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1.00 handling and documentation.

**U.K. ORDERS:** Subsequent to 15% surcharge for VAT. No charge is made for carriage. \*Or current rate if changed.

**SECURICOR DELIVERY:** for this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

**SALES COUNTER:** If you prefer to collect your computer from the factory call at Sales Counter. Open 9 a.m. - 12 noon, 1-4.30 p.m. Monday - Thursday.

### KIT ALSO AVAILABLE AS SEPARATE PACKS

For those customers who wish to spread their purchase or build a personalised system the kit is available as separate packs eg. PCB (10" x 12.5") £43.20. Pair of keyboards £34.80. Firmware in EPROMS £30.00. Toroidal transformer and power supply components £17.60. Cabinet (very rugged, made from steel, really beautifully finished) £26.50. P.S. Will greatly enhance any other single board computer including OHG SUPERBOARD for which it can be readily modified. Other packs listed in our FREE CATALOGUE.

### PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion socket is made via a ribbon cable.

#### Mother board:

Fibre glass double sided plated through hole PCB 8 7" x 3 0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug. **£39.90**

#### 8K Static RAM board

Fibre glass double sided plated through hole PCB 5 6" x 4 8" **£12.50**  
Set of components including IC sockets, plug and socket but excluding RAMS **£11.20**  
2114L RAM (16 required) **£5.00**  
Complete set of board components 16 RAMS **£89.50**

#### 8K ROM board

Fibre glass double sided plated through hole PCB 5 6" x 4 8" **£12.40**  
Set of components including IC sockets, plug and socket but excluding ROMS **£10.70**  
2708 ROM (8 required) **£8.00**  
Complete set of board components 8 ROMS **£78.50**

New Factory on same Industrial Estate  
Address and Telephone Number unchanged

UK Carriage FREE

# POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER HANTS SP10 3NM

ANDOVER  
(0264) 64455

# Britain's first computer kit.

## The Sinclair ZX80.

# £79.95

Price breakdown  
 ZX80 and manual: £69.52  
 VAT: £10.43  
 Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

### 'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); *everything!*

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done: connect it to your TV... link it to an appropriate power source\*... and you're ready to go.

### Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVED and LOADED on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

### Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

\*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon)

### The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:

- **Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.**
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input-to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols
- All characters printable in reverse under program control.
- Lines of unlimited length




### Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines.



And Benchmark tests show that the ZX80 is faster than all other personal computers.

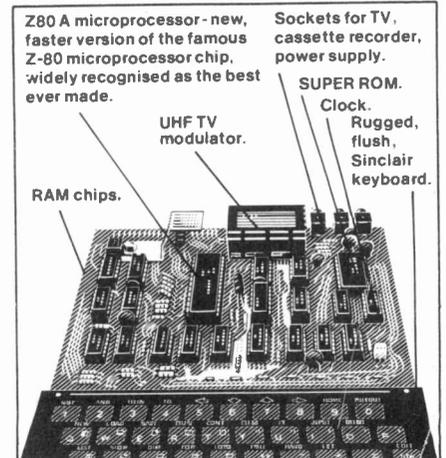No other personal computer offers this unique combination of high capability and low price.






# Simply ahead...

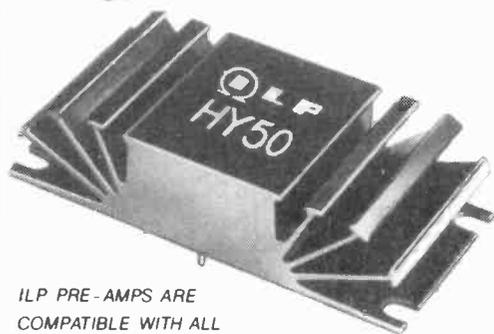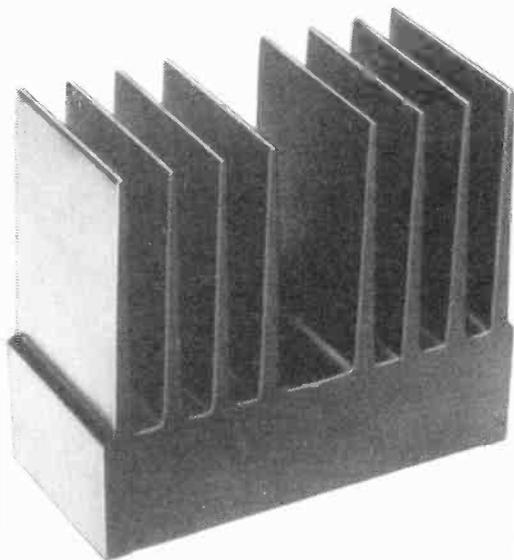

ILP PRE-AMPS ARE  
COMPATIBLE WITH ALL  
ILP POWER AMPS AND PSUs
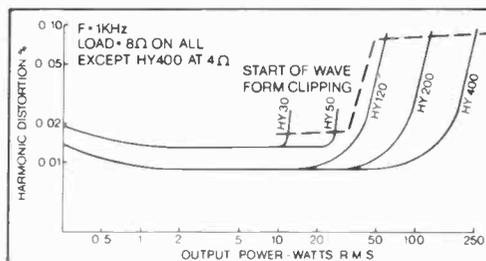
## POWER AMPLIFIERS

ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pick-ups, tuners, etc. using digital or analogue sound sources.



Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	100 dB	-20 0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	100 dB	-25 0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100 dB	-35 0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100 dB	-45 0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100 dB	-45 0 +45	114x100x85	1 15Kg	£27.68 + £4.15

Load impedance - all models 4 Ω - ∞  
Input sensitivity - all models 500 mV  
Input impedance - all models 100K Ω  
Frequency response - all models 10Hz - 45 KHz - 3dB

## POWER SUPPLY UNITS



ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled laminated transformer, for smaller PSU's - in the other, for larger PSU's, ILP toroidal transformers are used which are half the size and weight of laminated equivalents, are more efficient and have greatly reduced radiation.

PSU 30 ± 15V at 100mA to drive up to 12 x HY6 or 6 x HY6-6 £4.50 + £0.68 VAT

THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS

PSU 36 for 1 or 2 HY30's £8.10 + £1.22 VAT

PSU 50 for 1 or 2 HY50's £8.10 + £1.22 VAT

PSU 60 with toroidal transformer for 1 HY 120 £9.75 + £1.46 VAT

PSU 70 with toroidal transformer for 1 or 2 HY 120's £13.61 + £2.04 VAT





PSU 90 with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT

PSU 180 with toroidal transformer for 1 HY400 or 2 x HY200 £23.02 + £3.45 VAT



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.

# this time with two new pre-amps

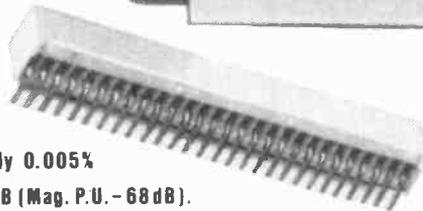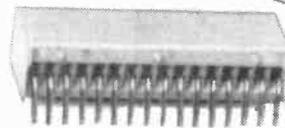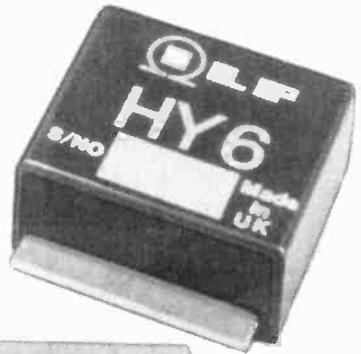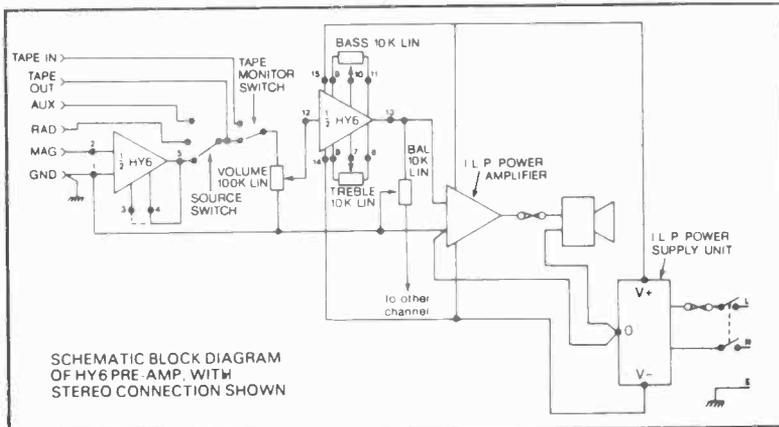

## HY6 mono HY6-6 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers – HY6 for mono operation, HY6-6 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

Sizes – HY6 45 x 20 x 40mm HY6-6 90 x 20 x 40mm Active Tone Control circuits provide +12dB cut and boost. Inputs Sensitivity – Mag PU – 3mV Mic – selectable 1.2mV All others 100mV Tape O/P 100mV Main O/P – 500mV; Frequency response – DC to 100KHz – 3dB

**HY6** mono  
£5.60  
+VAT 84p

**HY6-6** stereo  
£10.60  
+VAT £1.59

Connectors included

B6 Mounting Board  
78p + 12p VAT

B6-6 Mounting Board  
99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90 dB (Mag. P.U. – 68 dB).
- HIGH OVERLOAD FACTOR – 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY ±15V to ±50V.

NO QUIBBLE  
5 YEAR GUARANTEE  
7 DAY DESPATCH ON ALL ORDERS  
BRITISH DESIGN AND MANUFACTURE  
FREEPOST SERVICE  
– see below

★ ALL U.K. ORDERS DESPATCHED POST PAID  
**HOW TO ORDER, USING FREEPOST SYSTEM**

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope – we pay postage on all letters sent to us by readers of this journal.



**ILP**  
**ELECTRONICS LTD.**

FREEPOST 4, Graham Bell House, Roper Close,  
Canterbury, Kent CT2 7EP.  
Telephone (0227) 54778 Telex 965780

Please supply .....

..... Total purchase price £.....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No. ....

NAME .....

ADDRESS .....

Signature .....

# CLASSIFIED INFORMATION

Send to :  
ELECTRONICS TODAY INTERNATIONAL  
145, Charing Cross Road,  
London WC2H 0EE. Tel. 01 - 439 7449.

**Semi-Display:-**  
1-3 insertions — £6.00 per single column centimetre  
4-11 insertions — £5.50 per s.c.c.  
12 insertions — £5.00 per s.c.c.  
**Classified:-**  
23 pence per word (minimum 25 words)  
Box number on application (Personal ads only)

**ALL ADVERTISEMENTS IN THIS SECTION MUST BE PRE-PAID**  
Closing date: 1st Friday in month preceding publication.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components  
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices  
P.C. Boards to individual designs  
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Full range of etch resist transfers and other drawing materials for p.c. boards

Send 15p for catalogue.

**RAMAR CONSTRUCTOR SERVICES**  
MANSONS ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel. 4879

### MEMORY MART

'UK 101' 'Superboard' 4K RAM ..... £30 each  
Memory Expansion ..... £3.75 each  
2114 1Kx 450 small ns ..... £5.00 each  
2708 UV prom 650 small ns

P&P 20p  
C.O.D. 60p extra  
**MEMORY MART**  
19 Weatherby Gardens  
Hartley Wintney, Hants

**PET COMPUTER 8K.** Calculator type keys. 2 years old. No manual. £445 o.n.o. Cash Pigott, Cambridge. Phone 76865 evenings please



**C  
A  
M  
E  
R  
A**

£114.99 + P/P £3.45  
Optional extra manual  
£6 Total £124.44

**BEST OFFER EVER**  
Camera Kit, Lens,  
Vidicon & Modulator

**CROFTON**

Tel: 01-891 1923 For full details



ONLY  
**£1.85**  
(Incl. P&P)

### SPECIAL PURCHASE TEMP. GAUGES

Remote sensor on 38" capillary, snap fitting in 55 mm hole. Adjustment screw on back.

10-amp Connector Block — in units of two segments. Pack of 100 segments.  
**£3.00 (incl. P&P)**



**L.E.M. SERVICES**  
239 RUGBY ROAD  
LEAMINGTON SPA CV32 6DY  
WARWICKSHIRE

### DIGITAL CAPACITANCE METER



1 pF—2 μF in 5 ranges, on board selector. Precision resistor network and giant displays give direct readout in pF, nF and μF. Acc. 0.5% ASSEMBLED, ONLY **£24.94** including p&p. Overseas add £1.50 airport.  
Precision Measurements, P.O. Box 70 Giles Lane, Canterbury, Kent CT1 2UU

### MK14 PRINTER

This fully built, tested and ready to go printer connects directly to your unexpanded MK14 computer. It prints a full character set of up to 21 characters per line at 50 characters per second on standard paper. You need only a simple 12-volt power supply to drive it. All electronics are included. Only thirty bytes of software are required to print characters. Send SAE for sample print and full details. **Price £112.00.**

### MK14 VDU

This VDU connects to your MK14 I/O chip to give a 64 character x 16 Line VDU. On board modulator, 64 ASCII and 64 graphic characters. Minimal software requirements. Has its own memory (1K). Full flashing cursor control. Crystal controlled for rock steady display. **Price £59.90.** Send SAE for details.

### MK14 TO Z80 CONVERSION

Plug this conversion board into your SC/MP socket and have the power of the Z80, and amazing power of the AdEC-1 interpreter, with its 4-function arithmetic, versatile graphic control, edit facilities, conditional jumps, etc. So easy to use, you will learn to use it in a few hours. Kit price **£29.95** incl postage. Your MK14 repaired and conversion fitted if required. Machine code monitor available instead of interpreter at same price 2K basic version and extra 1K ram kit **£49.95.** Send SAE for details.

### COMPUTER REPAIRS

Any computer repaired at a fixed price. Eg. MK14 **£2.50.** Nascom 1 **£5.** Nascom 2 **£12.** Ring for others. Plus parts and postage

PHONE REDDITCH (0527) 61240 evenings  
**REDDITCH ELECTRONICS**  
21 FERNEY HILL AVENUE  
REDDITCH, WORCESTERSHIRE B97 4RU

## VIDEO MUSIC



Videograph II links to the aerial socket of your tv and provides a full colour GIANT oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

**New** — signal invert control, integral square wave generator. **Plus** — full details for testing your audio system for transient distortion, crosstalk etc

Complete **£29.95** Luxury cabinet and Kit only **controls. £14.95**

READY-BUILT UNIT **£59.95** + £1.50 P&P

**WILLIAM STUART SYSTEMS LTD**  
Dover House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD  
Telephone: Brentwood (0277) 810244

### COLOUR MODULATOR

Kit **£9.95** FOR ALL TV GRAPHICS!

+ VAT Red, Green, Blue inputs (can be mixed)  
Ready-built, Inc. UHF Available now! Nascom Colour Kit  
£14.95 + VAT Modulator **£45.00** plus VAT + Graphics Software

**WILLIAM STUART SYSTEMS**  
Dover House, Billericay Road, Herongate, Brentwood, Essex  
CM13 3SD Tel (0277) 810244  
Barclaycard / Access welcome

### SOLARTRON CT436 OSCILLOSCOPE.

Good condition £60. Akai 4000 Reel to Reel Tape Deck, excellent condition £55. Phone Beguildy 273.

### SPEED — VERSATILITY — ECONOMY



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers, to carry out work on—  
\*P.C.B. REPAIRS \*ANALOGUE BREADBOARDING \*SIMPLE LOGIC WIRING \*COMPLEX INTERCONNECTING OF MICROS AND MEMORIES.

EURO INTROKIT **£14.84.** PROJECT INTROKIT **£8.27.** PENCIL WITH LOADED BOBBIN **£2.44.** WIRE DISTRIBUTION STRIPS:—  
GLUE FIX 20/pkt 6" LONG **£2.80.** ADHESIVE 0-36/TUBE PRESS FIX 20/pkt 2" LONG **£2.92.** SINGLE EUROCARD HIGH DENSITY 3 PLANE (36x16 PIN DILS) **£4.50.** DOUBLE EUROCARD, WITH CAPACITY OF 84x16 PIN DILS **£7.25.** PROJECT CARD, HIGH DENSITY S-SIDED 20x14 PIN DILS **£2.65.** BOBBINS - BLUE 4/pkt **£2.12.** GREEN 4/pkt **£2.12.** PINK 4/pkt **£2.12.** GOLD 4/pkt **£2.12.** 1 OF EACH COL. **£2.20.** TINNED COPPER WIRE 4/pkt **£2.12.** RECOMMENDED SOLDERING IRON FOR ROADRUNNER HOBBYIST **£4.80.**

Please add 40p for p&p + 15% VAT to all orders.

FOR FURTHER INFORMATION  
ON ROADRUNNER PRODUCTS  
SEND LARGE S.A.E. TO:—

**T.J. BRINE ASSOCIATES,**  
56B, HIGH STREET, HASLEMERE,  
SURREY.

**FOR SALE**

**ETI**  
**PCIB's**

Buy it with Access  
BARCLAYCARD

**TRS 80 SOFTWARE NOW AVAILABLE**

**CROFTON ELECTRONICS LIMITED**

35 GROSVENOR ROAD, TWICKENHAM MIDDLESEX TW1 4AD · Tel: 01-891 1923

**200 COMPONENTS £4.** 100 diodes 85p. 150 caps £1.50. 100 resistors 85p. All mixed. Lists 15p. Sole Electronics (ETI), 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

**AERIAL BOOSTERS.** Improve weak VHF radio and television reception, price £6. S.a.e. for leaflets, Electronic Mailorder Ltd., 62 Bridge Street, Ramsbottom, Bury, Lancashire BLO 9AGP.

**LINSLEY-HOOD 75 WATT AMPLIFIERS** constructed and repaired. Power amp modules from £13.75, fully built and tested. Details free. I. G. Bowman (Dept. ETI), 59 Fowey Avenue, Torquay, S. Devon.

**TRANSFORMERS MANUFACTURED** to specification, many popular types ex-stock. Fast turn around on volume production. Send enquiries to Louth Transformers, Queen Street, Louth, Lincs. Tel: (0507) 606436.

**RECHARGEABLE BATTERIES**

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. S.A.E. FOR LISTS. £1.45 for Booklet. "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDWERE, SUTTON COLDFIELD, WEST MIDLANDS. 021-354 9764, or see them at TLC, 32 Cravens Street, Charing Cross, London, W.C.2.

**DIGITAL WATCH BATTERY REPLACEMENT KIT**



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send **£7.50** for complete kit and get into a fast-growing business. Prompt despatch.

**WATCH BATTERY REPLACEMENT CO. (ET14)**  
11 Percy Avenue, Ashford, Middx., TW15 2PB

**FREE 1980 AMTRON CATALOGUE** with new range of kits and equipment cabinets. Send S.A.E. Amtron UK Ltd., 7 Hughenden Road, Hastings, Sussex TN34 3TG. Tel: Hastings 436004.

**KITSWITCH Hex Keyboards**, wired to any format, 25 coloured keys, £12.75, also Reed-operated keyboards, up to 40 keys. — Details: 185 Musley Hill, Ware, Herts. Ware (0920) 61944.

**CIRCUIT DESIGN**, Prototype construction; Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

**CHEAPER THAN A VISIT TO THE PICTURES.** Latest top quality films pre-recorded on videocassettes from only £6. Full details from G.T. Technical Video Library (10a ETI), 119 Oxford Street, London W1R 1PA.

**VHF CONVERTER.** (Varicap). 28 to 30MHz tuneable IF. Highly sensitive unit £7.50 inc. post. Other models available. SAE data, lists. H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.


**SEIKO ANALOGUE AND DIGITAL QUARTZ.** The very latest products at highly competitive prices. Personal service. Unbiased advice. Analogue day/date £35. Ultra thin dress from £42. Sports 100 from £60. Digital alarm chrono/timer £39. Calendar alarm £45. Dress alarm/timer £52. Calculator alarm £55. Programmable alarm chrono £58. Plus many more interesting Japanese products. Send S.A.E. for illustrated list to: Powditch-Digital, 5 De-Verre Gardens, Ilford, Essex. No callers please.

**BOOKS . . . BOOKS . . . BOOKS** — Large range of Electronic Books in stock. Send s.a.e. for list. — Servio Radio, Dept. ET17, 156-8 Merton Road, Wimbledon, London SW19 1EG.

**771B METAL DETECTOR.** Build the best. Special integrated circuits. Printed circuit board and full instructions. Only £12.50 inclusive special offer. 117 Horton Road, Brighton BN1 7EG.

**£5 OSCILLOSCOPE.** Standard junk box components plus approx. another £5. (Total components approx. £12). This unit plugs into TV aerial socket and converts TV to oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge CB4 4BL.

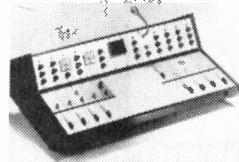FLEXIBLE — EXPANDABLE — BUDGETABLE  
**THE COMMUNITY MIXER KIT**



Not just another Mixer — but designed specifically for Hospital Radio, Talking Newspapers and similar users.

Is there such a word as 'Budgetable'? Consult  
**PARTRIDGE ELECTRONICS**  
56 Fleet Road, Benfleet, Essex SS7 5JN  
or call (03745) 3256 for the answer.  
Barclay and Access welcome

**FOR SALE.** UK101 uncased, full board 8k ram, includes manual plus extras £315 ono. Also Sinclair PDM35 plus transformer £25. Phone 01-422 9246 (evenings).

**STOP PRESS Superboard Compatible!**  
**UK101 TRS 80**  
**COLOUR YOUR NASCOM!**



**DAZZLING COLOUR GRAPHICS FOR NASCOM 1 & 2**  
Genuine bit addressable "pixel" system for straightforward programming of pictorial or mathematical functions.

8 Colour display plus 8 colour independent background facility. Full documentation with **FREE SOFTWARE**, powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems — send us diagrams etc of your b & w video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.

**NOW AVAILABLE FOR LIMITED PERIOD AT £45 Plus VAT**

**WILLIAM STUART SYSTEMS LTD**  
Dower House, Billerica Road, Brentwood, Essex CM13 3SD  
Telephone Brentwood, 0277 810244

**BARGAINS FOR THE ELECTRONIC HANDYMAN**  
**BRANDED LED DIGITAL ALARM CLOCKS**



(1) (2) (3)

Returned to Service Department within guarantee period

(1) With alarm repeat — S R S P of £17.00 offered at **£3.95 inc VAT**  
(2) With luxury lamp and repeat alarm as featured in most major U K Mail Order catalogues. S R S P £31.00—offered at **£7.95 inc V A T**  
(3) With integral luxury light and repeat alarm also as featured in most major U K Mail Order catalogues. S R S P of £32.00—offered at **£7.45 inc V A T**

These will be sold as received from our customers with the existing fault(s) and without guarantee

**UK ONLY**  
Discounts available on large bulk purchases  
**PRESCOTT CLOCK AND WATCH COMPANY LIMITED**  
Prescott House, Humber Road, London NW2 6ER

## 50Hz SUPERBOARDS BRITISH MODEL

FROM £159.95 + VAT

Fully built set up and tested

**AUTHORISED dealer back-up**

Free cursor control backspace, etc. tape

C.T.S., 1 Higher Calderbrook  
Littleborough, Lancs.

Tel. Littleborough 79332 any time

## TIME WRONG?

**MSF CLOCK** is ALWAYS CORRECT — never gains or loses, self setting at switch-on. 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, Auto GMT/BST and leap year, also second-in-a-month **STOP CLOCK** and parallel BCD output — for your computer, alarm, etc. receives Rugby time signals, 1000Km range, now get **ABSOLUTE TIME, £49.80. 60KHZ RUGBY RECEIVER**, as in MSF Clock, serial data output, built-in antenna, £13.70.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage, etc., money-back assurance so **SEND off NOW**

**CAMBRIDGE KITS**

45 (TG) Old School Lane, Milton, Cambridge

# AD INDEX

AJD DIRECT SUPPLIES	60	KRAMER & CO.	40
ALTEK INSTRUMENTS	74	LASCAR ELECTRONICS	94
AMBIT INTERNATIONAL	6	LB ELECTRONICS	40
AUDIO ELECTRONICS	60	L&B ELECTRONICS	76
AURA SOUNDS	52	MAPLIN	116
BAYDIS	36	MARSHALLS	66
BI-PAK SEMICONDUCTORS	14	METAC	35
BK ELECTRONICS	16	MICRO-CIRCUITS	12
B.N.R.S.	5	MIDLAND TRADING	22 & 23
BUTTERWORTHS	55	MONOLITH	36
CALCULATOR SALES & SERVICE	76	MOUNTAIN DENNE	39
CAMBRIDGE LEARNING	75	E. R. NICHOLLS	106
CHILTMead	34	NIC MODELS	74
CHROMASONICS	48	POLAR ENTERPRISES	106
CHROMATRONICS	47	POWERTRAN ELECTRONICS	2, 9 & 107
CLEF PRODUCTS	98	PRODUCT LAUNCH LTD.	21
CODESPEED	106	PROGRESSIVE RADIO	74
COM.P. COMP. COMP	115	QUANTUM	91
CROFTON ELECTRONICS	80	J. W. RIMMER	80
C.S.C.	65	R.T.V.C.	83
DELTA TECH & CO.	80	SCIENCE OF CAMBRIDGE	108 & 109
DIGISOUND LTD.	46	C. N. STEVENSON	36
DISPLAY ELECTRONICS	82	SWANLEY ELECTRONICS	79
DORAM ELECTRONICS	51	TANDY	42
E.D.A.	98	TECHNOMATIC	10
ELECTROVALUE	56	TELERADIO	98
GREENBANK	67	TEMPUS	93
GREENWELD	47	TK ELECTRONICS	55
GMT ELECTRONICS	62	TOOLRANGE LTD.	46
HAPPY MEMORIES	56	TRANSAM COMPONENTS	31
HENRY'S RADIO	30, 36, 61 & 94	T&T ELECTRONICS	46
ILP ELECTRONICS	110 & 111	VIDEOTONE LTD.	7
INTERFACE COMPONENTS	66	WATFORD ELECTRONICS	4 & 5
JAYEN DEVELOPMENTS	56	WEST HYDE DEVELOPMENTS	106
KEELMORE LTD.	102	WILMSLOW AUDIO	76
KODE SERVICES	5		

### A Surplus & Ex Equipment Clearance Offer!

**NEW QUALITY STEREOAMP CHASSIS**  
60w. (RMS) protected 90w. plastic outputs. Controls + selector, all din. sockets, smoothing, Heatsinking, 12/50v. wkg. Tested + data £9.95 inc. (leaflet sae).  
K. Lawrence, 1 Regent Road, Ilkley, W. Yorks.

**TI-57, 58, 59 GAME SOFTWARE!** Inc. "Meltdown Syndrome", "Lunalander", "Fruit Machine + Nudge," etc. Write P. J. Lynch, 48 Coleridge Cres., Worthing, Sussex. For free catalogue inc. SAE.

## XZ80 users!!!!!!!

Low-cost plug-in memory cards available.

NOW: 1K **£29.95**  
2K **£39.95**  
3K **£49.95**

Our cards come ready built/tested. Prices fully inclusive.

Dept. ZX  
**FLAIR MARKETING CO.**  
9 Park Hill Road  
The Arbours, Northampton

## COURSES

# CCAT

# COURSES IN ELECTRONICS

### BSc IN ELECTRONIC ENGINEERING

A four-year part-time degree course for mature students. Of particular interest to those engaged in Digital, Telecommunications or Central Systems. Entry qualification required is an HNC or equivalent in Electrical and Electronic Engineering or Applied Physics. This CNA degree is considered by the Council of Engineering Institutions as meeting their C. Eng. academic requirements.

### CEI PART II

One year full-time or two years' part-time course in preparation for the CEI Part II examination which is the present academic qualification for Chartered Engineers. Subjects offered include Electronics, Communication, Central and Computer Engineering. Entrants should have passed CEI Part I or have been exempted; holders of HNC and endorsements of HND are so qualified.

Further details and application forms are available from the Information Office, Room G219, Cambridgeshire College of Arts and Technology, Cambridge CB1 2AJ. Telephone (0223) 63271.

**ELECTRONIC SYSTEMS.** Advanced level G.C.E.? Join the sixth form at South East London School, Mornington Road, London SE8 4BL. Full range advanced level courses available. Details 01-692 1803.

EXTENSIVE COURSES IN

## BASIC AND PASCAL

including hands on mini-computer operation

These intensive courses are intended to instruct from minimal knowledge to an operational capability of computer programming.

Courses are fully residential, allowing maximum time for instruction and programming.


**BASIC** — Weekends from Friday Evening to Sunday Afternoon.

**PASCAL** — Weekdays Monday Morning to Friday Afternoon inclusive

For further details, dates available, fees  
Phone (0401) 43139, or write  
**CLEVELAND BUSINESS SERVICES**  
(Dept. ETI-2), Cleveland House  
Routh, North Humberside HU17 9SR

# COMPUKIT UK101 EUROPE'S FASTEST SELLING ONE BOARD COMPUTER.

**SPACE INVADERS PROG.**  
£5 + VAT

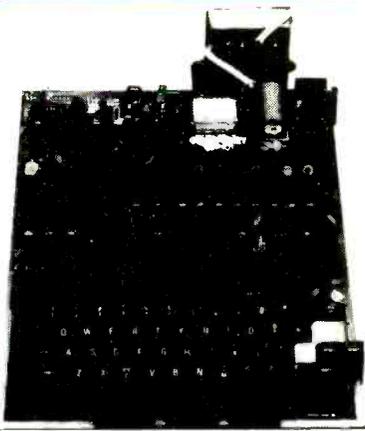

- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape Interface on board.
- ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

Build, Understand and Program your own Computer for only a small outlay	<b>KIT ONLY £199 + VAT NO EXTRAS NEEDED</b>	<b>AVAILABLE READY ASSEMBLED &amp; TESTED READY TO GO FOR £249 + VAT</b>
Specialty designed case for CompuKit in orange/black With room for accessories <b>£29.50 + VAT</b>	<b>6502 Assembler/Editor for CompuKit £14.90 + VAT</b>	

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programs. By pressing the C key the world of Basic is open to you.

This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use.  
Because of the enormous volume of users of this kit we are able to offer a **new reduced price** of **£199 + VAT**

**NEW MONITOR FOR COMPUKIT UK101** • In 2K Eprom 2716  
• Allows screen editing • Saves data on tape  
• Flashing cursor • Text scrolls down **£22.00 + VAT**

- 8MHz Super Quality Modulators **£4.90**
- 6MHz Standard Modulators **£2.90**
- C12 Computer Grade Cassettes 10 for **£4.00**
- Super Multi-rail P S U +5 -5 +12v **£29.50**
- Anadex Printer Paper—2000 sheets **£25.00**

## NASCOM-2 MICRO-COMPUTER



With **FREE 16K RAM Board Type B**

only **£305 + VAT**

Your choice of freebies with every Nascom 2 purchased from us  
**either FREE POWER SUPPLY OR FREE GRAPHICS ROM OR FREE VERO CASE TO TAKE NASCOM 2**

**Microprocessors** Z80A 8 bit CPU This will run at 4MHz but is selectable between 1/2/4 MHz This CPU has now been generally accepted as the most powerful, 8 bit processor on the market

**INTERFACE**  
**Keyboard** New expanded 57 key Licon solid state keyboard especially built for Nascom Uses standard Nascom, monitor controlled, decoding

**T.V.** The tv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T.V.

**I.O.** On-board UART (Int 6402) which provides serial handling for the on-board cassette interface or the RS232 20mA teletype interface  
The cassette interface is Kansas City standard at either 300 or 1200 baud This is a link option on the NASCOM-2  
The RS232 and 20mA loop connector will interface directly into any standard teletype

The input and output sides of the UART are independently switchable between any of the options — i.e. it is possible to house input on the cassette and output on the printer

**PIO** There is also a totally uncommitted Parallel I/O (MK3881) giving 16, programmable, I/O lines These are addressable as 2 x 8 bit ports with complete handshake controls

**Documentation** Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic

**Basic** The Nascom 2 contains a full 8K Microsoft Basic in one ROM chip with additional features like DEEK, DOKE, SET, RESET for simple programming




only **£356 + VAT**

### TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard Comes complete with easy to follow manuals, UK Power Supply — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available

## THE ATARI VIDEO COMPUTER SYSTEM

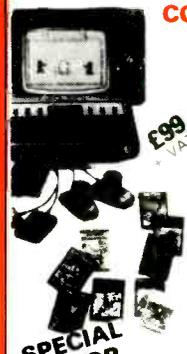

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous. You'll have thrill after thrill, whether you're in the thick of a dogfight, screeching around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on colour TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

**Cartridges now available** All at **£13.90** each + VAT  
Basic maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score, Space War, Sky Diver, Air Sea Battle Codebreaker, Miniature Golf.

**SPECIAL SCOOP**  
**SPACE INVADERS CARTRIDGE**  
**£27.00 + VAT**  
Ex-Stock

Extra Paddle Controllers — **£14.90 + VAT**      \*Keyboard Controllers — **£16.90 + VAT**

## NEW REDUCED PRICES

- 8K **£449**
- 16K **£549**
- 32K **£649**



RRP £795 for 32K **The PEDIGREE PETS**


Very popular for home & business use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard. All with green screen. Extra cassette deck **£55** Full range of software available
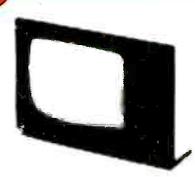
## NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.



**MINI KIT** PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct **£14.90 + VAT**  
**OR** PCB **£2.90** MAIN LSI **£8.50** Both plus VAT



## video 100

12" BLACK & WHITE LOW COST VIDEO MONITOR

RRP £79

only **£69 + VAT**

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3dB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

**COMP SHOP**  
"Europe's Largest Discount Personal Computer Store"

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS** number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

**14 Station Road, New Barnet, Hertfordshire, EN5 1QW** Telex: 298755 **TELCOM G**  
**Telephone: 01-441 2922 (Sales) 01-449 6596**  
**OPEN - 10 am - 7 pm — Monday to Saturday**  
**Close to New Barnet BR Station — Moorgate Line.**

★ **NOW in IRELAND** at: 80 Marlborough St., Dublin 1. Tel: Dublin 749933

**COMP COMPUTER COMPONENTS**  
(Part of the Compshop Ltd. Group)



# STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy  
and **STEP UP TO  
MAPLIN SERVICE  
NOW**




Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

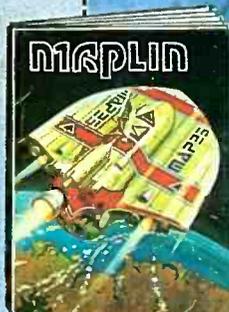

# MAPLIN

**ELECTRONIC SUPPLIES LTD**

All mail to:-

**P.O. Box 3, Rayleigh, Essex SS6 8LR.**

**Telephone: Southend (0702) 554155.**

**Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).**

**Telephone: Southend (0702) 554000.**