

AUDIO....COMPUTING....MUSIC....RADIO....ROBOTICS...

OWER PACKED — bv

Powertran's black boxes are packed with punch. Not only are they superb kits to buy and build they really do the job! Imaginative and ingenious design goes hand in hand with top quality materials and outstanding performance capability. With their smart black styling the kits harmonise visually as well as musically.

Your can built each unit independently for its set task and then gradually increase your array until you have a complete bank of formidable controllable power.



Complete Kit - E49.90 + VAT



Complete Kit - £49.50 + VAT









MPA 200 is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes rt ideal for the first-time builder.

CHROMATHEQUE 5000 5-channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects - each channel can handle up to 500W yet minimal wiring is needed with our unique single-board design.

ETI VOCODER - 14 channels, each with independent level control, for maximum versatility and Intelligibility, Two Input amplifiers - for speech/excitation - each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts.

SP2 200 twice the power with two of the reliable, durable and economic amps from the MPA200; fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout - up to leven over!) the standard of high priced factory-built units.

DJ90 Storeo Mixer - this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike in-put. Other 'plus' features are auto-panning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulatica, in short everything ... the whole works - AND - under £100 complete! (We have illustrated the DJ90 teamed in our Jwn console with the Chromatheque and an SP2 200 and speakers.

Complete Kit - E97.50 + VAT





Digital Delay Line - our latest kit! With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo & vibrato are obtained. The basic lut is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,0001 Complete lat (400 mS delay) £135. Parts for extra 400 mS delay £9.500.



WORLD LEADERS IN ELECTRONIC KITS

luite simply the best way to make music

Maney Back Guarantee — If you are not completely setained with your Powersen Kitchen, an angend condition within 10 days for full refund. The Setaining Practice Elit — To assist the beginner are will scapily, on request with your Bell bit order, a free soldering practice bit with each ics and supply.

STREET, Instrument. © Component Packs — Most kits are available as separate packs Hs.g. PCB component sats, hardware sets (BC). Picces in our FREE catalogues.

Ordering = Full ordering details, delivery service, and seles counter opening = dutside back of this issue.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.



DIGEST

ELECTROMUSIC TECHNIQUES

CRIMSON COMPETITION

and build some speakers for it

DESIGNER'S NOTEBOOK

Circuits to experiment with

Win yourself a hi-fi. **KIT REVIEW**

Sample our delights

News at nine

EDITORIAL AND ADVERTISEMENT OFFICE 145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.

FEATURES

9	READ/WRITE	. 54
177	Get it off your chest	14
17	Bright sparks might win it	. 61
33	10th BIRTHDAY SUPPLEMENT	63
	Happy birthday to us	
35	BIRTHDAY COMPETITION	64
1	Win a decade's subscription	99
	Putting on the stylus	00
-	VEROCOMPETITION	11
	Some prize boxes	
	TECH TIPS.	13
1	CASIO COMPETITION 1	17
4	For cool, calculating types	
15	ENTRYFORMS1	33
	Only one cut required	

PROJECTS

ACCURATE VOLTAGE MONITOR 23	ROB
Check out your battery	For p
COMPUTER EXPANSION	
This'll blow your EPROM	Contraction
AUTOMATIC CONTRAST METER 39	- 60T
Something unusual	1001
for photographers	
12 ····································	
	SOLI
10 ·	



SOUND EFFECTS 1 50 Bomb drop and explosion HIGH IMPEDANCE 100 MHz PROBE . 57 Top flight test gear

NEXT MONTH'SETI

BOOK SERVICE

Ever onward, ever better

Read all about it

OT CONTROLLER PART 2 94 roducing PWM



We conclude with the construction	
SOUND EFFECTS 2	118
Steam train and whistle	
GUITAR PRACTICE AMP	121
Cheap, and keeps your neighbours	
cheerful	
FOIL PATTERNS	136
This is where our boards find lodging	

INFORMATION

15	PCB SERVICE 44
	Why mess with ferric chloride?
	SUBSCRIPTIONS 125
	Advance booking

Ron Harris B.Sc: Editor Peter Green: Assistant Editor Tina Boylan: Editorial Assistant Rory Holmes: Project Editors Phil Walker: Alan Griffiths: Advertisement Manager Paul Wilson-Patterson: Group Art Editor T.J. Connell: Managing Director

PUBLISHED BY Argus Specialist Publications Ltd. 145 Charing Cross Road, London WC2H OEE. DISTRIBUTED BY: Argus Press Sales & Distribution Ltd., 12-18 Paul Street, London EC2A 41S (British Isles) PRINTED BY QB Limited, Colchester, COVERS PRINTED BY: Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS

AUSTRALIA — Roger Harrison CANADA — Halvor Moorshead GERMANY — Udo Wittig HOLLAND — Anton Kriegsman



Member of the Audit Bureau of Circulation

Electronics Today is normally published on the first Fri-day in the month preceding cover date. || SArgus Specialist Publications Etd 1982. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards All pitters and data contained in advertisements are ac expeted by us in good faith as carect at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations aftecting price or availability which may occur after the publica-tion has closed for press.

Subscription Rates, UK £11.95 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

WATCODD FLEOTDONIOC	TRANSISTORS
WAILOKD FFFFIKOWIP2	ACTER B 002112 10 017000 20 007002 10 278100 10 202211 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202201 00 202200 00 202200 00 20200 00 20200 00
THE CARDIFF ROAD, WATFORD, HERTS, ENGLAND	ACTUR D COLTA 10 07100 H MPL-12 H CTUB1 10 101075 278 26107 10 ACTUR D COLTA 10 07100 H MPL-12 H CTUB1 10 101075 278 26107 10 ACTUR D COLTA 10 071078 H MPL-14 40 271080 H 271080 H 271080 H 271080 H
Tel. Wattord (0923) 40588. Telex. 8956095	ACTUS 20 MILLION MI 077M AL 007VIII AL 27X2MA 17 PAREDO 8 200294 HA ACTUS 20 MILLION MI 077M AL 007VIII AL 27X2MA 17 PAREDO 8 200294 HA ACTUS 20 MILLION MILLION AL 007MILLION AL 27X2MA 20 PAREDO 8 2004
ALL DEVELES BRAND NEW PULL SPEC. AND PULLY QUARANTELD, ORDERS DES- PATCHED BY RETURN OF POST TERMS OF BUSINESS CASH-CHEOLE	ACT 10-10 75 00 2011 10 00 00 20 00 10 10 10 10 10 10 10 10 10 10 10 10
TUTIONEL OFFICIAL ORDERS ACCEPTED, TRADE AND EXPORT INCLURY WELCOME	
CONT. AN SURFACE ACCESS ONDERS WELCOME	ADTEL & COMPA B (12) (12) (12) (12) (12) (12) (12) (12)
VAT Expert orders to VAT, Applicates to U.E. Contraction only of the state of the s	AFTER DE BERES DE BERES DE CETERS DE CETERS DE DEBES DE DEBES DE DESES DE DE DESES DE DE DE DE DESES DE
Regen Undergrund Di Daten, Biglin Angen Brech, Open Mander in Beterley 1 Stor in 6 Star Angen Free Car Factory space evaluate.	ATTA R ATTA B BTTN 10 PTAL B ATTA 1 AND 1
CLACTION VINC CAPACINONIC DOPUNG AND OF 100 NO. 67 No. 67 No. 64 No. 10, 11, 13, 13 Day 6 Year 6 6 Yo Nam: 16, 22, 22m 33 Ving of tag vinc true tool No. 52m 57 No. 67 No. 37 Jun, 67	Ad 220 TO 02/VE2 (4) AD 22/VE2 XI TO/22 40 20/12/V/3 AD 20/2200 40 44471 100 AL227 VED 02/VE3 10 02/VE3 XI TO/20 42 20/12/01 40 20/42/M 40 44471 100 02/12/ VED 02/VE3 10 02/VE3 11 TO/20 42 20/12/01 40 20/42/M 40 4047A
"The time 200 when 200 Mills, 400 Mills, 400 Mills, 1000 Mills, 2000 Mills, 400 Mills, 400 Mills, 400 Mills, 400 Mills, 400 Mills, 1000 Mills, 10000 Mills, 1000 Mills, 10000 Mills, 1000 Mills, 1000 Mills, 1000	22-1010 12 02-10-11 10 07-10 10 10 10 10 10 10 10 10 10 10 10 10 1
1445-845 1791 4897 1884 885 197 1263 2455 447 3388 1885 2768 1385 1995 2388 1445 2768	12 102 1 10 11 12 11 11 11 11 11 11 11 11 11 11 11
POLYESTER CAPACITORS And Line Line Tree	10 THE 12 00112 00 00120 00 00120 00 1922C 00 1922C 00 1922C 00 00120 00 00120 00 00120 00 1922C 00 19
the two day like the like the day one way the to take Ad the take to the like the	UC111/1 A 00732-27 C 02/25 TR 1712 A 12276A A 20 2017 A 0 C 1713
tone with the fort the fort and forther the the forther the tone to be the body and	05 100 20 001100 00 0000 00 000 000 000 00
the second secon	05-1479 10 05222 66 05207 20 17736 19 27230 6 2607 6 8 05-14 0 05245 6 12,409 60 176414 10 27230 3 2600 8
TANY IN LAS DE AD CAPACITORS POTENTIONS TERM Caller Caller Bran 100 100 100 100 100 100 100 100 100 10	Control of Control of University of Petrol of
to bie der 19 13 tie 49 48 40 40 Bie beit benet Geren ben bin bien. Ber 100 120. 100	CCVLIVE V CCNNA B. 44,0 300 44 19971/2 40 243884 7 8 24474 80 44
Tige Tory 15 (2) Aller 13 (2) May 100 Sing party Sange Carly Core Cores Top May 100 Aller State Tory 100 Aller State Sange State State State State State State	CC107A 10 07-10 10 00.037 10 107004 00 702041 00 00000 00 000000 00 702040 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 7020000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 702000 00 7020000 00 70200000000
The dis still by the 120 June to 120 June	12 110 1 11 11 11 11 11 11 11 11 11 11 11
CARLING CAPACITORS SEV	
25- 47-4 to the the control to hear the second to hear one of the terms of terms	
	REMA N DESSA N WEAT N WAAT N REPAIR N REAL N
the title total for the ti	
Roversen Concernant An ICa Are and a Can are and a factor	TO Sectored. MD Towners, and towner
Maintain training from the participant of the part of t	Image: Control and Contro and Contro and Control and Control and Control and Control and Co
COMPANIES THE PARAMENT IN THE CAP	TO TO <thto< th=""> TO TO TO<!--</td--></thto<>
2 100 10 100 100 100 100 100 100 100 100	a statistica de l'ante de la companya de la company
RESISTORS Carbon Film High The High And The And The Carbon Stability Low Noise Ministure, They in the And The And	
RANGE VAL 1-69 100	
Verill 2 211 4547 624 2p 1p erstand of federative in the con- travel 2 211 4547 612 2p 1p erstand of the con- travel 2 211 4547 612 2p 1p	
110/ 2 211 1M11. E 12 Bp 4p ctas a chaos 2000 2000 100 200 100 ctas 200 200 200 200 200 200 200 200 200 20	
100 price applies to Resistors of each matchy is Reserve in Colling	1754 Ten excerne de tagene de 127 27 hinto de 12.129 de 138 de 127 07 hinto de 128 de 128 de 127 de 128 de
volue not miced	
AATO B RECTIFIERS BERNE IN LA	Image: state state Addition The state The state The state The state The state The state <ththe state<="" th=""> The state <</ththe>
PTID 24 CATERY # 75 SERIES CENTER CONTENTS	M Milling Mail Milling
CALL PAR LANGER A REAL PROPERTY OF LINEAR ICS	n winn Fu titt an han a hitty fa ban ta titty
	Mail Mail <th< td=""></th<>
Pilot All 4 Ramento 71 to 100 all Statemento 100 (all all all all all all all all all all	THE LABORTY CON COLUMN TO LABOR LABOR LABOR LABORTY CON LABORTY CO
Vitigation 17 Auryor 2013 rs Aurgory 40 Pris UB 47 5 0019 68 6 UB Prisatil 19 2717 5 300 60 20009 60 Pris 00 20009 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000 60 2000	The second secon
10 100 10 100 100 100 100 100 100 100 1	
	Tech 20 001077 10 2010 21 100 100 100 100 100 100 100
NOISE AND THE CARD TH	
VARICAPS CARDO SI TCAT IN CARDO IN CARDO IN CARDO	
Finite of the test of the province of the province of the test of test of the test of test	
Brander State I successive and a state of the state	The second part and the second part of the second part of the second part of the

SWITCHES			VERCEDARD 810	PLUGS & SOCRETS	PANEL	RELAYS
	Seen Star 18 mete		117 - 3 W The Car Do Barret 310	ACI Pus baner in	METERS	Et Barnaty Open, 200-A. Str.
SAS-AND TOURS			Pla - 1" By The Photo DEC.	Alternative and an internative	0 Stand	R. 12 FARLE OF IN OF LINE
	1	april to 8 may	244 - 17 130p 211p	Lan Marco 140 140 140	A-001 C	RE NO WE RED TOVIES TOVI LINES RE NO SHED TOVIES SOV 1000
	ROTARY Mains D	POV & Amp	April fare culture 1100 Dimitations 1 70	間はなな	1 dana	a 1 water to the ante
Cold under af Ba	and all			The law lite	B titlend	Devalue Patte Roomany Open
CIPET 3 peochang	Make a multimore t	and there as	Spars Samp Re I Same to By		0.500mA	Mangharts and and TCD maget
Janes 2 may 1984		· Drawnesi	Finding Cont Garden In The Advance	1	6 20V	SPC0
DI-DI ANIV	Machanian any		tille = 100 MM	1000 100 100 100	a por Ac	INFERANC TIDOVA.SON' IND
DEDT IA CHER THE	The shore senters of	adara brasti ta ta	COPPER CLAD BOARDS	2 4 4	a	EDU and, OVE TH DC, 250% AC, SA. These of them
PUBLICUTTON AL		Aufg and the	pitte with the bit of	See transfert 119 119	CRYSTALS	10,0 111 1701 est, 04 1041 2004 AC
	Spacers 40 Serees	•	6' x 12 1940 1950	CO AMAL (Th)	SE TERLING SER SERLING 270	Ut at The rest of the set state
DET manant Make	BOCHER MARTIN		TERAD Law the Colling Tonto	227 2 2 2 2		CONTENENTAL Crases Type Relays
Name of Street of Street	NOCHER MANSION	Cont and the	2 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	Und Connectury (681) CB		DAY MONA
THE DESIGNATION				Senter SO230 Round Channe die	1.852 #	2 pers orever 12r to 2002 Febr
	16 pm	Catto Americani		BAGN OCTAL HOV GALMA	2.0.00	A gate some to to the tank
	Bright product Coll 1486 1	No 200 100		Pug Phil 1989. Samer BB	3.77851 228 3.57544 100	Hat Press Then Day KS
		2 2 2 4		Des annen merennen der		AL THAT I BE VAL DIE THEY THEY
Callen D Minute			An Page Sectors Covers Piles	Santa and Jackson und Har	international and	20hp
	NOL .	ett di angi tita		Jaho externion rokca	1.4230 1944 130 1	Tige P0 3730 Yes
TRANSFERRE	Continues pr	and the same state of	17-may 2010 2010 2010 2010	Diese Billip Hann Star		
TRANSFORME	Si Pain MPY	VOLTAGE REG	GULATORS CAME IN		Annany B	DV DV & 12V Ho
Pra her a has her	4 104 2-15V 4 134	14 103	10000	All Parts		A Da Jon Jon Jo
PA SHARA SHE	AND WING MA	177 7913 1465	THE INCOME OF	the stant many many frage. Sectors		2 Year Chin, Soll or State Man
Danised Spin Dables by				Burn W Commissions		Fur Die detaufter of antituction and Team Game May Property Brites
2+ 194 4.254 12480 2=4 844 264		· · · · · · · · · · · · · · · · · · ·		Samuer Land Coller Assembly	13 mm-1 200	Mattern America Colten Manually, Subdur and Organis schemes reserve
2+124 0 BAE 2+104 G. 64	Sublevie SA			Witten frein bes, fermen 6100		and in Seath Considers die Trans Tolers 2 a 213
2-184 664 2-204 664	2000 12A 2+124 1A	2017 1024 105	The Tange He	27 Weg. Denden Brann Mr. 1976		Banner für abnere Big
The part of part	CA NEVOA	WEITER TONE PAR	He County TELAS BE TOATATE PERS	ANTER BOLDIARIS ROM	77 4 Mar. 20	ABTEC UN MODULATONS
	W 24 2-200-2 84	2 2 2 2 2 2 E	There's a the state of a state	CITER AND CITER AND	27 Millio 248	Disadard Galage
ANALASSING STREET, & BAT	THERE IN STREET FREE		the state of the s	COUNTRY MEDICICIUM AND		The second
May charge to be added the mail plant of the spin	ever and chare or		TALIS DE DIG LARVE	Server Spil, exercised data Alle		Th Assessments Burley Considered
cmos		OPTO SLEC.	TALS D AND AND AND	Seen Sta. essenter des Sta Seen Sta. essenter des Sta Start Starten all garge Sta		Th Assessment Burner Countries
CMOS		OPTO ELEC-	PR.12 BD Marco 2.207 to Marco 2.077	Control of the second second	WATFORD'S	Th Accessinging Bytes Consultance Book Shop CORNER
CMOS		OPTO ELEC- TRONICS	PIL 12 TO PIL 15 TO PIC 15 TO PIC 12 TO	Construction Construction	WATFORD'S	Th Automotive Bytes Connectores BOOK SHOP CORNER In Revealed Editors BOOK SHOP CORNER
		OPTO ELEC- TRONICS	Pill, 12 Pill, 13 Pill, 15	Greating and and the start of the second start	WATFORD'S WATFORD'S	Th Arrangenging Signer Counsilores Eliter Al ports anditation BOOKSHOP CORNER In (Revised Edition) Elitop Stop Book (Comproherging) Filip
dbr More and a second designed CMOS 4071 dots 4021 dots 4021 dots 4021	as dill top top as top top top as top top top as top top top as top top top top top top top top top top top top top top top	OPTO ELEC- TRONICE	PBL12 BD PUTER CORNER OVIC 20 Million Computer, Connect ovig VIC Construction Computer, Connect ovig VIC Construction Contended on a final OVIC 20 Million VIC Tractor Page 9 BD CPS, Bodirectment, Conversion (RS222) B IPSON MARKETY Has Pression for	Construction Construction Server Standards Construction Server Standards Construction Construction of the Construction Construction of the Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construct	WATFORD'S WATFORD'S The Cost Book Burgson Child's Dur Child Share	Comparison of the second
Alton Alton CMOS 607 GOD 16 GOD 17 GOD 16 GOD 17 GOD 16 GOD 17 GOD 16 GOD 16 GOD 16 GOD 16 GOD 16 GOD 16 GOD 16 <td>All Control and othere is an intervention of the second and othere is an intervention of the second and other is an interventin other is an intervention of t</td> <td>OPTO ELEC- TRONICS</td> <td>PBL12 BD PBL13 BD PBL13 BD PBL13 BD PBL13 DD PBL13 DD</td> <td>Construction Construction Const</td> <td>WATFORD'S WATFORD'S WATFORD'S Contractions The Contractions The Contractions Chorage of Chorage Share Chorage Share Ch</td> <td>Comparison of the second second</td>	All Control and othere is an intervention of the second and othere is an intervention of the second and other is an interventin other is an intervention of t	OPTO ELEC- TRONICS	PBL12 BD PBL13 BD PBL13 BD PBL13 BD PBL13 DD	Construction Const	WATFORD'S WATFORD'S WATFORD'S Contractions The Contractions The Contractions Chorage of Chorage Share Chorage Share Ch	Comparison of the second
Alter Property and Comparison CMOS 6000 GODO		OPTO ELEC- TRONICS	PBL12 BD PBL12 BD PBL13 BD PBL14 BD	Construction Construction Construction Series Blannach Series Blannach Series Blannach Series Blannach Series Blannach Construction Construction Construction Construction Construction Processories Construction Construction Processories Construction Construction Processories Construction Construction Processories Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construction Construct	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	The Announce of the analysis of the analy
Chick's Chick's Chick's 600 Chic	20 41.32 19 20 41.32 19 20 41.34 000 20 41.34 000 20 41.34 000 20 41.34 000 20 41.34 000 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34 100 20 41.34	OPTO ELEC- TRONICS	PBL13 BD	Construction of the second state of the second	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	Th Annexempling Bighter Counsellance BOOKSHOP CORNER a (Review) Editorial a (Review) Editorial BOOKSHOP CORNER a (Review) Editorial BOOKSHOP CORNER a (Review) Editorial BOOKSHOP CORNER a (Review) Editorial BOOKSHOP CORNER BOOKSHOP CO
Alter birter Alter CMACS Constant Constant CODE 14 COTS CODE 15 CODE CODE 15 CODE CODE 15 CODE CODE CODE	Josephilic Josephilic <thjosephilic< th=""> Josephilic Josephil</thjosephilic<>	OPTO ELEC- TRONICS	PB.13 BD PB.2 JIP 10	Construction of the second sec	WATFORD'S WATFORD'S WATFORD'S CHOSE THE Costs Boo TTE Costs Boos Booguage CMOS Du CMOSI Costs Boos Boostanty BASIC A Boost BASIC Abor of BASIC	Thi Annual Carlos Ballon Connailance BOOKSHOP CORNER In Annual Californi BODD BOOKSHOP CORNER In Annual Californi BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BODD BO
Alter burget Alter burget CMAOS Constant COMOS Constant CODE Mail CODE CoDE CODE CoDE CODE CoDE	20 45.32 100 20 65.34 500 20 65.34 500 20 65.34 500 20 65.34 500 20 65.34 500 20 65.34 500 20 65.34 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.4 500 20 65.6 510 20 65.6 510 20 65.6 510 20 65.6 510 20 65.6 510 20 65.7 500 20 65.7 500 20 65.7 500 </td <td>OPTO ELEC- TRONICS</td> <td>PSL-12 The Part of Part of Second Secon</td> <td>Constructions Constructions of the second se</td> <td>WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S Cost Soci Tri Cost Soci Tri Cost Soci Child Correct Soci Child Correct Soci Advanced BASIC BASIC Correct Soci Marchael Casic Serve Common BASIC BASIC Correct Soci Serve Common BASIC Practical BaSIC Campo Serve Common BASIC Practical Servers Basic Practical Servers Servers Servers Programment Servers Servers</td> <td>Thi Auronaughing Bigster Capacitance BOOKSHOP CORNER a (Ravitani Edition) ESSO addecki (Companyerspiret) 7880 addecki (Com</td>	OPTO ELEC- TRONICS	PSL-12 The Part of Part of Second Secon	Constructions Constructions of the second se	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S Cost Soci Tri Cost Soci Tri Cost Soci Child Correct Soci Child Correct Soci Advanced BASIC BASIC Correct Soci Marchael Casic Serve Common BASIC BASIC Correct Soci Serve Common BASIC Practical BaSIC Campo Serve Common BASIC Practical Servers Basic Practical Servers Servers Servers Programment Servers Servers	Thi Auronaughing Bigster Capacitance BOOKSHOP CORNER a (Ravitani Edition) ESSO addecki (Companyerspiret) 7880 addecki (Com
Alter Property and design CMOS 4000 GOD 14 6070 GOD 14 6070 GOD 14 6070 GOD 16 6070 GOD	JB 4522 100 JB 4522 100 JB 4535 200 JD 4541 100 JD 4545 100 JB 4542 200 JD 4545 200 JD 4562 450	OPTO ELEC- TRONICS	PB-12 BD PB-22 PPUTER CORNER PTL-15 BD PDUTER CORNER VIC 20 Micro Computer. Connects ordy VIC 20 Micro Computer. Computer. VIC 20 Micro	Construction Construction of the second seco	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S Control down TTL Control	Th Automatigning Bigster Carponitionne BOOKSHOP CORNER a (Revited Edition) EDD addeck (Companylengting) 7880 Stop addeck (Companylengting) 7880 Stop add
Alter Proping and Analysis CAROS Gazz M Gazz M <t< td=""><td></td><td>CPTO ELEC- TRONICS UNIT RETERENT DECEMPTOR INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOM</td><td>PBL 12 BD PBL 13 BD PBL 13 BD PBL 14 DPUT BBL 2.20V to PBL 2.2</td><td>Construction of the second sec</td><td>WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFOR</td><td>The Annual Construction of the Constructi</td></t<>		CPTO ELEC- TRONICS UNIT RETERENT DECEMPTOR INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOMENT INCOM	PBL 12 BD PBL 13 BD PBL 13 BD PBL 14 DPUT BBL 2.20V to PBL 2.2	Construction of the second sec	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFOR	The Annual Construction of the Constructi
Children Verget, allocito 1 de allocita Children Verget, allocita		COPTO ELEC- TRONICS	PB.13 BD PB.22 PV B PB.23 PV B PB.22 PV B PV	Constrained of the second of t	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S COULT AND AND CAUSE CANAGE AND ADD AND AND AND SAME CANNED SAME CANNED AND SAME CANNED AND MALE SAME AND MALE SAME AND AND AND AND MALE SAME AND AND AND AND AND MALE SAME AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND AND	Th Antenenging Byster Corrections BOOK SHOP CORNER a (Ravitad Edition) EDD Book SHOP CORNER a (Ravitad Edition) EDD Bob Bob Bob Bob Bob Bob Bob Bob
Alter of the action Alter o	20 41.32 1.9 20 41.32 1.9 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.34 1.00 20 41.35 1.00 20 41.35 1.00 20 41.35 1.00 20 41.35 1.00 20 41.35 1.00 20 41.35 1.00 20 41.35 1.00 20 41.35 1.00 20	OPTO ELEC- TRONICS	PR.13 BD PR.15 BD PR.15 BD PROVIDER CORNER VIC 30 Mileo Computer. Connects srig VIC 30 Mileo Computer. Connects MILEOT 19 Traces Feed. 9 VIC 30 Mileo Computer. Computer MILEOT 2 Vice for manage VIC 30 Mileo Computer angle VIC 30 MILEOT 12 Coheren Friese MILEOT 2 Vice for manage VIC 30 MILEOT 12 Coheren Friese VIC 30 MILEOT 12 Friese VIC 30 MILEOT 1	Constant of an entry of a second and a second a second and a second and a second and a second and a second	WATFORD'S WATFORD'S WATFORD'S Contractions The Contractions The Contractions The Contractions The Contractions The Contractions The Contractions The Contractions The Contractions CMOBI	The Antenenspire Byster Counsilianse BOOKSHOP CORNER a (Raviewal Editoria) EBDO BOOKSHOP CORNER a (Raviewal Editoria) EBDO addesite (Comproherspire) Pilip addesite (Comproherspire) Pilip adde
Alter Alter Alter CAMCOS 4072 GDD 14 4072 GDD 14 4073 GDD 14 4075 GDD 10 4077 GDD 10 4070 GDD 10 4070 GDD 10 4071 GDD 10 4071 <	Jo Chi Ji Composition JB Chi Ji Composition JD Chi Ji Composition <td< td=""><td>OPTO ELEC- TRONICS</td><td>PR.13 BD PR.2 BP PR.25 BD PROVIDER CORNER VIC 20 Million Computer. Connects sty VIC 20 Million Content Pacet. VIC 20 Million ContentPacet. VIC 20 Million Content Pacet. VIC 20</td><td>Control of a control of a contr</td><td>WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S Containing the Containing Status Containing Status Containing Status Child Centre Boost Marca BASIC Computer Samuel Status Containing Status</td><td>Th Antenenciping Bighter Counciliance Enderse Ar parts eventstor BOOKSHOP CORNER a (Reviewal Editoria) EDD addecta (Companyingsing) Pillip addecta (Companying) Pillip adde</td></td<>	OPTO ELEC- TRONICS	PR.13 BD PR.2 BP PR.25 BD PROVIDER CORNER VIC 20 Million Computer. Connects sty VIC 20 Million Content Pacet. VIC 20 Million ContentPacet. VIC 20 Million Content Pacet. VIC 20	Control of a contr	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S Containing the Containing Status Containing Status Containing Status Child Centre Boost Marca BASIC Computer Samuel Status Containing Status	Th Antenenciping Bighter Counciliance Enderse Ar parts eventstor BOOKSHOP CORNER a (Reviewal Editoria) EDD addecta (Companyingsing) Pillip addecta (Companying) Pillip adde
Alter of the action CAMOS CODE 14		CPTO ELEC- TRONICS USD are Class Barriston II Barriston III Barriston III Barriston III Barriston II Barriston II Barristo	PR.13 BD PR.2 BP PR.25 BD PR05.2 IPP to PR05.	Control of the second of the s	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	CODD
Alter of the action CAMOS CODE 14	Josef III Josef III Josef III Jan Gill 100 100 100 Jan Gill 100 61.31 100 Jan Gill 100 61.31 100 Jan Gill 100 100 100 </td <td></td> <td>PR.13 BD PR.15 BD PR.15 BD PR05.2.IIIV III PR05.2.IIIV PR05.2.IIV PR05.2</td> <td>Constant of supervised and the second second</td> <td>WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S COMPACTOR COMPACTOR CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL</td> <td>Carrowskie Gripper Constitutes Constand Constitutes Constitutes Constitutes Constitut</td>		PR.13 BD PR.15 BD PR.15 BD PR05.2.IIIV III PR05.2.IIIV PR05.2.IIV PR05.2	Constant of supervised and the second	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S COMPACTOR COMPACTOR CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL CANNEL	Carrowskie Gripper Constitutes Constand Constitutes Constitutes Constitutes Constitut
Before Description Description CAMOS Construction Construction GDD0 14 GD73 GDD0 10 GD71 GD71 10 GD70	20 41.32 110 20 41.32 110 20 41.34 900 20 41.34 900 20 41.35 115 20 41.35 115 20 41.35 116 20 41.35 116 20 41.35 116 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.45 910 20 41.210	COPTO ELEC- TRONICS USA	 PR.13 BD Parts 2.2010 Bits 2.2010 Bits 2.2010 Bits 2010 B	Constrained of the second of t	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFOR	The Accession of the section of the
Children Property and decaya Children	20 41.32 100 20 41.32 100 20 41.34 400 20 41.34 400 20 41.34 400 20 41.34 110 20 41.34 110 20 41.34 110 20 41.34 110 20 41.34 110 20 41.34 110 20 41.34 110 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 120 20 41.34 40.34 20 41.34 40.34 20 41.34 20.34 21 41.35		 PR.13 BD PR.15 BD Provid 2001 Bits of 2001	Control of the second s	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S CASHC Constant Annual SASC Advanced BASIC Advanced BASIC Advanced BASIC Advanced BASIC Advanced BASIC Man BASIC Computer Same Computer SASC Advanced BASIC Advanced BASIC Advanced BASIC Advanced BASIC Advanced BASIC Man BASIC Computer Same Computer Sasc Man BASIC Computer Same Computer Sasc Man BASIC Computer Computer Sasc Mark BASIC Computer Computer Sasc Computer Sasc Co	The Accessingling Bigster Caynesitance BOOKSHOP CORNER a (Revited Edition) EDD advest (Camputersport) Pille Books (Camputersport) Pille Books (Camputersport) Pille Books Computer State advest advest Books (Camputersport) Pille Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Books Bo
Alter of the action Alter o	20 41.32 1.9 20 61.34 6000 61.34 20 61.34 6000 1111 20 61.34 6000 1111 20 61.34 6000 1111 20 61.34 1000 1111 20 61.34 1000 1111 20 61.34 1000 1111 20 61.34 1000 1111 20 61.34 1000 1111 20 61.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34 1000 1000 40 64.34		 PR.13 Bio Prot. 2. 2011 Biol. 2. 2011 Biol. 2. 2011 Biol. 2. 2011 Biol. 2011 Biol	Control of the second of the s	WATFORD'S WATFORD'S WATFORD'S WATFORD'S Common Tit, Date Rec Tit, Cost-Book Barner Chors Date Choraver Chors Basic Annot a Chora Basic Annot a Chora Basic Annot Annother Theoreman Annot Annot Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annother Annoth	The Accessing by Byter Counsilianse BOOKSHOP CORNER a (Rave Ar part evelation) BOOKSHOP CORNER a (Rave and Edition) a (Comparison of the accessing a (Co
Alter of the action Alter o	Jac Chi Jia Composition Jac Chi Jia Com		 PR.13 BD PR.15 BD Prod. 2.2010 B Prod. 2.2	Anno tips estimation of the second and the second a	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	The Accessing in the second se
Alter of the action Alter of the action Alter of the action Child State Concerned action Child State Concerned action Child State	Josephilic Josephilic <thjosephilic< th=""> Josephilic Josephil</thjosephilic<>		 PR.13 BD PR.15 BD PR.15 BD Prob.2 Jahr to 2014A Prob.2 Jahr to 2014A Prob.2 Jahr to 2014A Prob.2 Jahr to 2014A Prob.2 Million Companyative Comments and an CP3. De directionals, Comments and CP3. De directionals, Comments and	An or the control of the second of the secon	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	Th Assessment of States BOOKSHOP CORNER a (Rave Ar part evaluation BOOKSHOP CORNER a (Ravea Ar part evaluation a (Ravea Ar part
Alter of the action Alter of the action Alter of the action Charles Alter of the action Charles Mail (1975) Conce Conce Conce Conce Conce Conce Conce Conce Conce Conce Conce Conce Conce Conce		Control Canada C	 PR.13 BD PR.13 BD PR.15 BD PR.	A directly to a callow TV. Sull bare stand official garage a directly to a callow TV. Sull programme Callow a Sull of the Source Source of the source of the source of the source of the source of the source of the source of the Source Source of the source of the source of the source of the of the source of	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	Cable C
Before Accessed Accessed CAMOS Composition Composition Composition CODE 14 COP3 Composition Composition CODE 14 COP3 Composition Composition <td< td=""><td></td><td>CONTRACTORY OF THE CASE OF THE</td><td> PR.13 BD PR.13 BD PR.15 BD PR.16 BD PR.</td><td>A directly to a callow TV. Sull ber and all garage a directly to a callow TV. Sull Crossession and garage a directly to a callow TV. Sull Crossession and the second and th</td><td>WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S ADD OF SALES ADD OF SALES ADD OF SALES ADD OF SALES Proceedings of Sales ADD OF SALES Proceedings of Sales ADD OF SALES Proceedings of Sales ADD OF SALES Proceedings of Sales ADD OF SALES ADD</td><td>The Account of the Composition of the Composition</td></td<>		CONTRACTORY OF THE CASE OF THE	 PR.13 BD PR.13 BD PR.15 BD PR.16 BD PR.	A directly to a callow TV. Sull ber and all garage a directly to a callow TV. Sull Crossession and garage a directly to a callow TV. Sull Crossession and the second and th	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S ADD OF SALES ADD OF SALES ADD OF SALES ADD OF SALES Proceedings of Sales ADD OF SALES Proceedings of Sales ADD OF SALES Proceedings of Sales ADD OF SALES Proceedings of Sales ADD	The Account of the Composition
Before Accessed above CAMOS Construction CODE 14 COTO CODE COTO COTO CODE COTO COTO CODE COTO COTO CATO COTO			 PR.13 BO Micro Contents of the second state of the second	Consistent of the second of th	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFOR	The Accession of the section of the
Before Access of a second decayant CAMOS Construction CODE 14 COTO COTO 14			 PR.13 BD PR.15 BD PR.15 BD Prob.2.2010 Bits of Computer Units of the Computer Commence of the Computer Commence of the Computer Commence of the Computer Commence of the Computer Compu	Consistent of the second of th	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S ADD 10 ADD 10 AD	The Account of the action of t
Alter V-reg Alter V-reg CADD Alter V-reg GOD 14 GP7 GOD 15 GP7 GOD 16 GOD 16 <			 PR. 13 BO Micro Composition Web Sciences (Composition Composition Com	Consistent of the servers of the ser	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S Manager SASC Additional Additional Same SASC Camputer Same SASC Camputer SASC Camputer SASC Camputer SASC Camputer	The Account of the Ac
Alter of the action Alter o			 PR. 13 Biology Provided States of the second states of the seco	Consistent of the second of th	WATFORD 18 Jan 1998 WATFORD 18 WATFORD 1	The Accessive and a second sec
Alter of the action Alter o			 PR.13 Bio Provide the second second	Consistent of any of the second of the second of any of the second of th	WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S WATFORD'S	The Accession of the second states of the second st

1

Sinclair ZX81 Personal Comp the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold,

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surpnsed by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



Every 2x8t comes with a comprohensive specially anthen manual + a compare course in BASIC programming, from higt pencyptes to compres programs

Kit: £49.⁹⁵

Higher specification, lower price how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80'

New, improved specification

 Z80A micro-processor - new faster version of the famous Z80 chip, widely recognised as the best ever made.

 Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.

 Unique syntax-check and report codes identify programming errors immediately.

 Full range of mathematical and scientific functions accurate to eight decimal places.

 Graph-drawing and animateddisplay facilities.

- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops
- Randomise function useful for

games as well as serious applications. • Cassette LOAD and SAVE with

- named programs
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack

 Able to drive the new Sinclair ponter.

 Advanced 4-chip design: microprocessol, ROM, RAM, plus master chip - unique, custom-built chip replacing 18 ZX80 chips

Built: £69.⁹⁵

Kit or built – It's up to you! You'll be surprised how easy the ZX81 kit is to build; just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.





ICIDII

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16⁴

Use it for long and complex programs or as a personal database Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX. Software - the Business & Household management systems for example.



Available nowthe ZX Printer for only £49.⁵⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further intructions.

At last you can have a hard copy of your program listings - particularly

How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST - use the no-stampneeded coupon below. You can pay useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions

by cheque, postal order, Access, Barclaycard or Trustcard. EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt and we have no doubt that you will be.

7

CRY	Bam	Code	Nom price	Total 8
	Sincleir 2001 Personal Computer kil(s). Price includes 2001 BASIC manual, encludes mains edisplor.	12	49.95	
	Ready-assembled Sinclair 2381 Personal Computer(s) Price includes 2381 BASIC menual and mains adaptor.	11	60_95	
	Meine Adaptorte) (600 mA at 9 V DC nominel enregulated).	10	8.95	
	18K BYTE RAM pace	18	40 95	
	Sincleir 2X Printer	27	40.95	
	BIC BASIC ROM to fit ZXBD.	17	18.95	
	Post and Packing.			2.95
UP	ease bok if you require a VAT receipt		TOTAL E	
") en "Piel	close a cheque/postal order payable to Sincialr Reserves the charge to my Access/Barcleycard/Trustcard acco	unt no.	L for E	
") en "Plei	close a cheque/postal order payable to Sinclair Reserves use charge to my Access/Barclaycard/Trustcard acco e dester/complete es approable	unt no.	L for E	
") en "Plet "Plet	close a cheque/postal order payable to Sinclair Reserves se charge to my Access/Barclaycard/Trustcard acco e dests/complete as apaicable	unt no.		
") en "Piec "Piec Nam Addr	close a cheque/postal order payable to Sinclair Reserves charge to my Access/Barclaycard/Trustcard acco	unt no.		
9 en Plei Nom Nam	close a cheque/postal order payable to Sinclair Reservise charge to my Access/Barclaycard/Trustcard acco e deete/complete as applicable a: Mr/Mra/Miss	unt no.		



NEWS:NEWS:NEWS:NEWS:NEWS:NEWS





ETI PRICE DECREASE

Readers will have no doubt noticed (painfully!) the cover price increase on this issue of ETI. We apologise for this, but are happy to say it is ONLY FOR THIS ISSUE and the price returns to 75p with the May issue.

The one-month jump was made necessary by the sheer size of this special issue. We hope you will agree it is worth it. If you could see the price of paper these days...(moan, moan).

Thank you for sticking with us through thick and thin... (and 10p1)

Tempus Fugit

It's felt a little uncomfortable working in the ETI office this month; must be something to do with the sackcloth and ashes we're wearing. During the last few insues several of our reviews have featured Casio products, but we have consistently failed to credit the company which lent us the review models. The kindly folk in question are Tempus of 38 Burleigh Street, Cambridge CB1 1DC and we'd like to thank them for all the help they've been giving us. Tempus are leading Casio specialists and if there's something from Casio you're having problems obtaining, they will doubtless be as nice to customers as they are to us.

Sun-Day Driving

A volkswagon Dasher car is presently being tested carrying a rool-rack of AEG-Telefunken solar modules which convert solar energy directly into electric current. The small 160 W 'solar power plant' of the test car complements the dynamo and charges the battery. This means that fuel consumption can be reduced by approximately five percent. As yet the cost of manufacturing these solar panels makes them uneconomical to use, but with the rising prices of fuel, it is foreseeable that low-priced solar generators will enter the market. Not only that, future car generations will make increased use of electricity, for example with automatic startstep devices and pollution-free electrical energy for air conditioning in cars in warm countries. Great idea — but where will you put the luggage?



Tweeters That Go Cheap Well, not just the tweeters, in Wfact, Mullard have a 40 W

V fact. Mullard have a 40 W speaker system consisting of an B" woofer as well as a high-power testile dome tweeter. They form part of a new low-price, two-way, selfbuild audio' kit (whew!) being marketed by DK Electromics. The BIE Electronics crossover unit have been combined with spring-loaded terminals and recessed mounting panel. The complete system, when built into the 23 litre enclosure, by capable of handling 40 W comfortably. All this for the small outlay of £13.90 plus VAT and £1.50 carriage per kH2 Get yours now from BIE Electronics Ltd, 37 Whitehouse Meadows, Eastwood, Leigh-On-Sea, Esses S59 STY.



Heading For The Top

Headphones seem to be getting so Sennheiser, that well-known manufacturer of headphones, has decided to launch a pair of their own lightweight 'phones. The new model HD40 is soon to be released in the UK and weighs only 60 grammes with estremely light contact pressure. They can be supplied with either a three or seven metre lead, the seven metre variety incortrating a volume control in the lead so that you don't have to march all that way back to the amp if it's too loud. Another feature is that each ear-piece can be revolved on the headband by 90 degrees if you have a funny shaped head or you want to store them compactly (!). The Sennheiser HD40 will be launched in the UK with a suggested selling price, including VAT, of £16.55. For those of you interested in technical spece frequency response is 22 to 18,000 Hz, impedance is 600 ohms, characteristic SPL is 90 dB and distortion factor < 1.2%.

Electroware, OK?

K Machine and Tool (UIE) Ltd Uhave launched a new division aimed at providing the electronics user with a really wide range of electronic hardware. All the products in the range will be available to everyone involved in building electronic equipment - that in cludes engineers, students, teaching stall, laboratory techni-cians and, not least, the hobbyist. The 40-page catalogue contains various products selected from OK's bench tool range - plus some new items - and includes soldering irons, wire-wrapping hits, IC tools, PCBs, cases, enclosures, connectors, sockets and test instruments to name just a lew. Electroware in distributed throughout the UK by leading electronic and computer stores. Catalogues are free, but send 30p for postage and packing. If you want any further information or one of their catalogues contact OK Machine & Tool (UK) Ltd. Dutton Lane, Eastleigh, Hants SOS 4AA.

Lack of ZX81 memory iving you headaches.?



The Memotech 64K Memopak

The growth of interest in computer use caused by the introduction of the Sinclair ZX81 has made new and exciting demands on the ingenuity of electronic engineers. At Memotech we have focused our attention on the design of an inexpensive, reliable memory extension.

The Memopak is a 64K RAM pack which extends the memory of the ZX81 by a further 56K. Following the success of our 48K memory board the new memory extension is designed to be within the price range expected by Sinclair users. It plugs directly into the back of the ZX81 and does not inhibit the use of the printer or other add-on boards. There is no need for an additional power supply or for leads.

The Memopak together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts such basic commands as 10 DIM A(9000)

K-E79

0-8K ... Sinclair ROM

8-16K...Memopak memory which can switch in or out in 4K blocks to leave space for memory mapping.

12-16K...Memopak memory which holds its contents during cassette loads and allows communication between programmes. 16-32K...This area can be used for basic programmes and assembly

language routines.

32-64K...32K of RAM memory for basic variables and large arrays.

With the Memopak extension the ZX81 is transformed into a powerful computer,

suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

M	Please debit my BARCLAYCARDIACCESS* account number:	Please rush me: 64K RAM, Assembled	Ouantity Price Total
MEMOTECH	*Please delete anichever does not apply Signature		
Memotech Ltd 3 Collins Street	Date NAME ADDRESS	Payroll Programme	VAT 0 15%
Oxford · OX4 1XL Tel · 722102/3/4/5	To: Memotech Ltd., 3 Col	llins Street, Oxford, OX4 1XL	ETI TOTAL Telephone (0865) 722102

NEWS:NEWS:NEWS:NEWS:NEWS:NEWS

High-res Printing

N4542, a high-speed, highresolution printer which combines a new type of Fleshammer' printhead with advanced microprocessor control to make it equally suited to text printing, label or bar code production, and graphics output. Using 260-character-persecond bidirectional two-colour printing and a 14 s 9 dot-matrix format, the 4542 can produce a virtually unlimited range of characters as well as different grey scales in graphics applications. In normal text-printing applications, the 4542 features proportional spac-ing justified right-hand margin and an extensive set of up to \$12 characters in 11 national repertoirs with red/blach, elongated and underlining facilities. For label printing a variable-use option is

available which allows characters or bar codes to be generated in 95 different sizes from 2.52 mm up to 240 mm. Selection of size and position is easily controlled by software commands. In the graphics mode scanning semi-graphics and 10 levels of grey/red scale are available to illustrate reports with histograms, curves and diagrams, as well as generating half-tone illustrations in applications such as tomography, process monitoring and computer-aided design. The hey to the versatility of the 4542 is the point-head, which consists of a set at nine stored-force flesible metal hammers mounted directly on a magnet armature. No adjustment or lubrication is necessary, wear is minimal, and a 'floating mount means that the correct paper/print-head distance is always maintained irrespective of the paper thickness or number of copies. Further information is available from Hi-Tek Distribution Limited, Trafalgar Way, Bar Hill, Cambridge, CB3 BSQ.



BT Bill Beater

Following the success of the Telcost TNA25 from the Ansatone Corporation, it was decided that a single line unit should be manufactured. The new machine offers a range of functions which are all designed to save money by monitoring telephone use. Amatone's single line Telcost 1 has teatures including a 24-hour clock display, which instantly shows the cost of a call as soon as a user is connected with a number dialled. The unit also has a built-in printer which records details of the call including cost and number dialled. It also prints out the date, time, machine identification number and the duration of the call. Telcost 1 has a built-in memory which retains information even if the machine is disconnected from a power source. It also gives a special security midnight printout each night which frustrates any attempts to conceal the day's telephone costs by the destruction of the daily printout sheet. The machine is virtually tampe-proof as the printout will indicate if it has been disconnected from the line at any time or if any information parameters have been changed. The machine has provision for it to be reprogrammed at any time to enable the user to keep in line with British Telecom unit rate charges and the date, time and identification number can be changed for any reason if the machine is moved to a new location. This desh-top unit is no higger than a telephone and for an investment of around £249 could help to cut out the abase of telephones in both large and small companies.

Small And Beautiful

Hafled as the World's Smallest, Lightest and Lowest Power Consumption' television, the TH3-W3V from Matsushila certainly caught our editorial eye. Closer inspection revealed a colour TV set with a 3° colour picture tube, only 115 mm s 86 mm s 123.5 mm in size and 1.5 kg in weight. Power consumption is a mere 9.5 W and it operates on AC power, car batteries and on optionally available rechargeable batteries. Vet, despite its small size, it is equipped with video inputioutput terminals and operates as a colour monitor and a video tuner when connected to a video camera and a portable VTR, respectively. This 3° colour TV was launched on to the japanese market in mid-December 1961 at the approximate price of C200. It is due for launch in the US in June this year and, hopefully, will be seen in this country shortly after. Further details will be supplied by National Panasonic (UK) Ltd. 300(113 Bath Road, Slough SL1 6JB.



Sticky Clips

Brandauer adhesive cable clips prom Stotron provide an imespensive method of fising round or ribbin cables to clean, dry surfaces. The range can handle round cables from just a few millimeters up to 19 mm and flat ribbon cables from 13 mm to 75 mm can be accommodated by a selection of clips with widths in stages of 6 mm. The adhesive is instant acting and polyethylene pads provide high levels of insulation, where necessary, further information is available from Stotron Ltd, Unit 1, Maywood Way, twyhouse Lane, Mastings, East Susset.

Video Victory

Thern EASI have just announced that agreements have been signed with Telefunken and JVC to form a holding company for the manufacture of video consumer electronics products in Europe. Thomson Brandt was originally intended as a fourth partner, but this was not possible. However, the three other parties hope an opportunity will arise for Thomson-Brandt to join the venture.

Products manufactured by the joint venture will include VHS video cassette recorders. VHD video disc players and video cameras.





NEWS:NEWS:NEWS:NEWS:NEWS:NEWS

Grabbed By The Dooleys

Those tireless chapples down at Casio have taken time off from disguising BASIC computers and arcade games as pochet calculators and watches, and have turned their attention to the music scene. Although there is undoubtedly a market for top-flight organs and synthesisers amongst home musicians, many people will prefer something more modest for financial reasons, because the living room is too small or because they can't figure out what all the knobs do. At the other end of the scale (sorry), the type of hand-held organ made notorious by Roll Harris is a little too limiting. With the Casiolone 701, Casio have not just produced a solution to this problem but a radically new type of instrument.

The CT-701 is not just a 61-key polyphonic (eight voice) minisynthesiser, but also contains an on-board computer that acts as a built-in sequencer; among other things. You can play along with the built-in rhythm unit, store your own music in memory and play it back automatically, or just load the machine with a Casio music score and let it get on with things by itself. The latter function is quite estraordinary — Casio supply the music scores as bar codes and you read them into the machine using a light pen (like those at supermarket check-out desks). In melody guide mode you can even teach yourself to play the instrument, as LEDs above each key light up to tell you which note to play next.

Twenty preset sounds are available, such as pipe organ, flute, piano, oboe, bassoon etc. plus the synthesised drum sounds of the rhythm unit and the pneooum sound so beloved by producers of disco records. Opinions of the preset sound quality vary from "beautiful" (Casio) through "very good" (an indepen-dent reviewer) to "too sharply filtered" (another independent reviewer). Since they can't agree and we haven't heard it (though, we're trying hard to get our muchy paws on one), you II have to listen to one yourself before parting with any cash, but professional musiclass seem to like it -- the Dooleys use Castotone mini-keyboards in their stage shows (fellow headbangers may not see this as a compliment). With so much packed into such a compact case (only slightly larger than the actual keyboard) and such a low price (about ESOO). Casio would certainly seem to have done it again



ZX Revamp

For those of you who are serious F23-01 owners (is there such an animalf) or would simply like to disguise the machine, there is a professional standard keyboard and enclosure now available from Protos Computer Systems. The keyboard is the first of a range of peripherals to make the computer suitable for more heavy-duty use. The 40-key Sinclair coded hoard uses top quality mechanical contact type key switches with relegendable tops. A steel mounting board holds the keys firmly in position and a high quality printed circuit board completes the board's electrical circuit. Connection to the Sinclair board is made by a llexible connector which is a

push fit to the sockets provided on the ZXB1. Access to the edge board connector is via a side port on the Protos enclosure and tape injout. power and UHF connections are made through the rear. To fit the Protos entails removing the Sinclair board from the black ABS case it comes in and fixing it inside the Protos enclosure with four Phillips type screws. No soldering is required and all electrical connections are plug/sochet connec tions provided either on the Sinclair or the Protos. Further details on this and other forthcom ing peripherals can be obtained from Protos Computer Systems Frome Computing, 20 Ashtree Road, Frome, Somerset BA11 2AS. Please onclose a large SAE with any enquiries.

Power For Peanuts

Grenson Electronics, designers supplies for the Nuclear Research Industry have come up with a series of bench power units. The first unit in the series is priced at 659 and gives a variable stabilised output up to 30 V at 2 A in two ranges, has foldback re-entrant short circuit protection and current and voltage metering. This unit is also available in hit form at only E3S and further details are from Grenson Electronics Ltd, Nigh March Road, Long March, Industrial Estate, Daventry, Northants NN11 4HQ.



Miniature Magnification

New from Stotron Ltd is the Scope Mark 111 pocket microscope with stand. Priced at under E20 It is a useful tool for laboratories, schools, workshops, service engineers and the electronics, electrical, automotive, print and graphic trades. Uncle Tom Cobbley and all? It is 125 mm long, with 20s magnification and a graticule showing linear and angular measurements. Illumination is powered by standard 1VS 'pen-light' batteries and a microstand (with spring clips for sample slides) is available as an option so that the device can be used like a conventional microscope. Further details on this device are available from Stotron Ltd, Unit 1, Haywood Way, Ivy House Lane, Hastings. East Sussex.



Thin Meters

Sitam 1td of Torquay in Devon Sare to market a range of very thin edgewise meters manufactured by General Electric of the USA. There are three sizes in the range with case widths of 30 mm, 63 mm and 89 mm and the units are scaled for vertical or horizontal presentation. The special feature of this design is the extreme thinness; the smallest has an overall depth of face of only 13 mm and the two larger sizes of about 17 mm. The smallest model has a rear-access zero set and a simple spring-clip method of mounting. The two larger models have front access zero set at end of scale and a slide brachet form of mounting. They incorporate jewelled pirot movements with special high-torque magnets for reliable and accurate operation. The standard meters are available enstoch from Silam and have a maximum sensitivity of So microamperes. Scale markings can be produced to suit individual requirements. Further details of these and Silam's own range of meters are available from Silam Limited. Woodland Road, Torquay, Devon TQ27AV.



HIFI STEREO AMPLIFIER KITS

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty.

These new kits offer the choice of moving magnet or moving coil inputs, 40 or 100 watts per channel, in fact, everything that made the previous models so popular is imcluded but with added style, easier construction and a full two year warranty.

The New Range Consists of The CK 1010 Stereo Pre Amplifier The CK 1404 WPC Power Amplifier The CK 1100 WPC Power Amplifier

CK 1010

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled' and tested therefore construction is simply a matter of point to point wring and mechanical assembly of the connections and controls to the pre punched chassis.

The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

CK 1040

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsInks, wire and connectors are included and protection is provided from short circuit outputs.

CK 1100

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard.

When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kitbuild field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few — such as the KA-1000 (500 +) — are of comparable standard . . . I can say no more than that for £250 it (CK1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

ETI FEB 1982

SPECIAL INTRODUCTORY OFFER 10-15% OFF!

As a special incentive to buy our new range of D.I.Y. Hifi Kits, we are offering the range for a limited period at silly discount prices

The offer closes on March 31st, with prices this low, demand is sure to be heavy, so order now and avoid delays at the same time save £££'s

CK 1040 - BRP (119 00	0
SUBTINI LIIJ.UU	
CK 1100 - RRP (149.00	9
SPECIAL PRICE E130.8	0
MICZK - HKP L25.00	D
PSK - RRP (20.00.	n

Barclaycard or Access accepted, otherwise send C.W.O. C.O.D. £1.00 extra All prices include P&P to anywhere in the U.K. Export: Write for pro-forma



FREEPOST, 9 CLAYMILL ROAD LEICESTER LE4 52D, ENGLAND TEL 0533 761920, TLX 34694





How would you like a 10 MHz oscilloscope about the size of a targe lunchbox? Can't afford one? Then build this one — it's the main project in ETI next month.

SLOT CAR CONTROLLER

Let's not beat about the bush. Slot cars are fun. If you're as keen on slot cars and electronics as we are, you'll be equally appalled at the crude control systems provided in the basic sets. Naturally we decided something should be done about the situation and came up with this project. You can have controlled acceleration with overshoot, dynamic braking. 'electronic' fuel tanks — and all from quite a simple circuit. There'll also be some advice on how to tune your cars to get the ultimate in performance from them. A must to read for kids of all ages.

COLUMN LOUDSPEAKER DESIGN

Now this is good stuff. One of the bugbears of public address systems is acoustic feedback, which can be largely overcome by the use of a highly directional sound source. This directs the sound into the audience, where it's needed, and away from the microphone, where it isn't. This article describes the design of a novel column loudspeaker design that is cheap and highly effective.

ROBOT CONTROLLER PART 3

In next month's ETI we continue this series with the construction information for this month's analogue pulse width modulation controller, plus full details and a PCB for a dual digital PWM controller. This will not only be of interest to roboticists but to anyone who needs to control the speed of DC motors

> Articles described have are in an advanced state of preparation. Housever, circumitances may dictate changes to the final contents.

ETI APRIL 1982

DVMEG

Any scholars out there will know that D is Roman for 500. Since V stands for volts, it will come as no surprise that this project generates 500 V to enable the leakage current through insulation to be tested using the built-in meter. In effect it is a high-voltage resistance meter for measuring values above about 1M0 — hence the last part of the name. We don't just throw these things together, you know!

BREADBOARDING SYSTEMS

There appears to have been a veritable explosion in the number of breadboarding and prototyping systems available to industry and the hobbyist, next month we'll be taking a look at some of them. Both solderwrap and insulation displacement techniques will be examined and we'll have an exclusive first review of a major new development from a leading manufacturer. Not to be missed!





NEW RANGE QUALITY POWER LOUD-BPLAKERS [19", 12" and 8"]. These toudspeakers pro deal for both full and dece applications. Both the 12" and 13" units have heavy duty do cast chasses and aumentum contro domes. All three units have white speaker cores and are fitted with attractive code stummuce transference index and pro-fitted with attractive code stummuces transference and Pricet-

19" 100 wett R.M.S. Impedance Bohm So or magnet, 2" aluminium vace cel Resonant Frequency 2012, Frequency Resonant to 2 Stitle, Sensitivity 91:08 Price \$32 eedb. (2:50 Pocking and Car-

12" 100 west R.M.B. Impedance 8 ohm, 50 oz. magnet, 2. eluminum voco cel Resonant Frequency 25Hz, Frequency Response to 40Hz, Senshvety 95d8. Price (23,70 eesh, (2.50 Pacting and Carnege each.

8" 50 west R.M.B. Impedance 8 ofrms, 20 oz. 11/5" pluminium votce ppl, Rosenaria Frequency 40%, Proparezy Resenance to 60%, Senatively 10x8. Also available with block zone fined with block motil presentive pr8. Price White zone (2,50 cps8, Block consequel (3,67 cps4, P. P. (1,22 cps4).

PIEZO ELECTRIC TWEETERS - MOTOROLA

TYPE B

TYPE

TYPE F

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to exit to 100 watts imore if 2 put in series). FREE SUPPLIED WITH EACH TWEETER. added to establing speaker systems of up series). FREE EXPLANATORY LEAFLETS



TYPE TO BLEAVERED 315" super hars, For general purpose specifies, data and P.A. systems at: Price (6.35 each.

TYPE C MEMORYAN 2" + 5" white depart version and quality daces mit. Price ES.46 each.

TYPE TO BERNIESSAU ?" + 6" webs dage ham. Upper frequency regionse retained extending down to mill range GE/kgt, Guitable for high quarky 16-8 systems and quality deces. Price (5.19 quark.

TYPE TO IKEN HEEAD TS." have tweeter with attractive alver finish plan. Suitable for H-B monitor systems (EE. Price (4.3) each

TYPE ♥ ISSN1057AJ Cased version of type ♥. Pres exercting setallite tweeter, Perfect add on teaceter for conventional loudepaster TV-F P Interview/AL Canadi General - Orfact and on twenter for conventioned localpeaker systems. Price (19,78 each. U.E. pact free Let SAE for Piece teaffeet).



Va Materia

Matching 3 way loudspeakers and crossover

Build a quality 60wort PMAS ayatam Bahma Build a quality 60 watt R.M.S. system.

- + 18 Woeler
- # 3" Tweeter
- + S" Mid Range
- + 3 way crossover

Auto fairing da-Filled with attractive cast stumming has culpheans and mesh protective grills at cumulation and ing protocover grads to the APA emission on doing a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker latitics. All three units have automatic converse dama and rolled foam pursound. Crossover com-bines sping-leaded touchspaces forminate and mounted metal.

Price (22.60 per lat + 22.50 postage and gaph-OF BUTY, PTC

A superb general purpose bain cena taud-spoolor: 50 os magngt. 2 dumunium voco col. Rollad surround. Resonant fra-quency: 2546, Fraguentur respenses to 1304t. Senathvity 95d8, Impedance Bohm. Attractive blue cone with aluminium centre dama. centre deme Price (17.50 each + C2.10 PSP

SPEAKER

APPROVED

tone full range touckpeaker. Mag! for ridel systems etc. Choled faiting extrement over cares Atlation impedance #15 work RMS #1" vaca cal #13ee magnut #Frequency range EP/15000rg Price: (5.50 each + 75p P&P



Your Anglin Modules with i Versions prove supply and hast sing. Supplied as complete built and based will Can be fitted in markes. Auditory statistical supply and drive circuit moreported to power on L.I.O. V.o. mater controlles as on

SPECIFICATION: Man subput power 100 works R.M.S. (ChiP100 Looks, Open and shart circuit presh 4-16 share Frequency Responses(2010-3800/r 3200/r 3200 Sanatavay far 100 worts 100mV of 100 7.1.0.0 00.1% Size: 300 + 115 + 00mm Paten Carp Marin OMP 150W -78.60





MA

QE.

B.K. ELECTRONIC

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All Berns packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



12" 00 wort R.M.B. toudsposter

TYPE 'A' EXPERIMAN'S' round with pro wire maph, class for bookshalf and m signed HA-8 speakers. Price (2-6) each.

TYPE C

TYPE

ELECTROMUSIC **TECHNIQUES**

Tim Orr, our tame electronic designer, emerged from his workshop this month just long enough to hand over this bundle of circuits for the ardent build-it-yourself musician.

irtually all of the electronic music synthesisers that have been produced to date employ analogue circuits to generate the synthesised sounds. The process is known as subtractive synthesis, and operates by dynamically filtering out parts of the spectrum of a signal that is often rich in harmonics. The results are instant, easy to modify and relatively inexpensive to implement. It is not possible to produce an arbitrary output spectrum, and so it is very difficult to synthesise realistic copies of naturally generated sounds. This can be done using a digital technique known as harmonic synthesis, whereby the sound is constructed by precisely defining the amplitude and phase of each of the harmonics. These are then added together to produce the output. However, natural sounds are constantly varying and so the data defining all the harmonics must also vary. Harmonic synthesis can produce very realistic sounds and is in itself a powerful technique for generating completely new sounds, but the hardware is a combination of sophisticated microprocessor and digital technology and so is outside the scope of this article.

When we hear a sound we unconsciously analyse it for useful information; "Who wants another drink?" for example. Nobody knows how the human brain analyses incoming sounds, but it does it with incredible speed and sophistication. It can extract precise information from sounds (speech perception), it can experience pleasure from a rich harmony, or it can even learn to ignore certain sounds, such as a ticking clock. The brain is very good at perceiving pitch (or at least it thinks it is; it is also a fairly good liar); see Fig. 1. When you hear a pure tone you

5		URE TONE	Fig. 1 Pitch pe	rception.	
-FUND		TINGING TONE	Fig. 2 (below) with table show temperament t	Keyboard wing equa uning.	l layout I
PITCH + FR	EQUENCY - T				
		MOTE	FREQUENCY INNI	1.0000	
		0	201.0	1.0600	
		~	305.3	1 1 2 28	KEYBO
		Dist	211.1	1,1002	
-	A DECOMPANY INC.	54	326.7	1.2599	
AD	22.9	54	349.2	1 3348	
	55.0	54.0	370.0	1.4142	
A2	110.0	GA	392.0	1.0983	
A	220.0	Gel	419.3	1.5874	
M	440.0	Al	440.0	1.6618	
45	0.000	A4.0	466 1	1,7818	
1 46	1700.0	M	493.9	1.6877	

1.8877

\$21.2

ETI APRIL 1982

A6

1780.0

will get a strong impression of its pitch. You will not be able to define its frequency in Hertz, but you will be able to remember its pitch. A sawtooth has a strong harmonic structure but even so-you will get the same pitch perception. The ringing tone has virtually no energy at the fundamental frequency and yet it is still possible to correctly perceive the pitch of the signal, although it is more difficult than for the pure tone.

Most musical instruments produce a range of notes. Some instruments, like violins, can produce a continuous range of frequencies; because, unlike the guitar, there are no frets along the neck of the instrument. Keyboard instruments have fixed tuning: the piano, for example. The keyboard is an excellent choice for controlling a synthesiser, as it is easily converted so that it generates suitable electrical signals and it is widely accepted by musicians. Equal temperament tuning is used, that is there are twelve notes per octave and they are spaced at intervals of the twelfth root of two (that is 1.0594631) along an exponential curve, as in Fig. 2.

When You Hear The Tone...

The keyboard is used to define the fundamental pitch of a sound, but the actual shape of the waveform will determine its harmonic structure (Fig. 3). A sinewave is a pure tone and has no harmonics. A-halfwave-rectified sine wave contains a fundamental plus a series of even harmonics. A fullwave-rectified sine wave is composed entirely of even harmonics. The squarewave and the triangle are both composed of a series of odd harmonics; in fact if you lowpass filter a square wave you can produce a triangle. The triangle is a fairly pure tone, with little of the energy in the waveform contained in its harmonics. The sawtooth is a rich waveform, having both odd and even harmonics

The harmonic structure of all these waveforms extends to infinity, but the drawings only show the first 15 harmonics. If we call the harmonic number n, then the harmonic amplitude is easy to define. The rate at which the harmonic amplitude













Fig. 5 The effects of frequency modulation.



Fig. 6 The effect of filtering an excitation signal.

of the sound. The format is usually a mobile filter and this makes it possible to dynamically alter the sound colour. If the formant has a sharp resonant peak, then the output signal will ring as it passes the harmonics of the excitation.

Another parameter that characterises a sound is its

Fig. 3 Harmonic structure of various standard musical waveforms.

decreases is 1/n for the sawtooth and square wave and 1/n² for the half and fullwave rectified sine wave and the triangle. Figure 4 shows a sawtooth being constructed from harmonics. The sum of the harmonics is beginning to look like a sawtooth. As more harmonics are added (with the correct phase and amplitude) the sum will converge upon the correct sawtooth shape. An interesting effect can be produced by changing the mark/space ratio of the square wave. This modifies the odd harmonic spectrum and introduces even harmonics. The mark/space ratio is often dynamically modified as a synthesis process.

Frequency modulation is often employed in synthesisers to produce vibrato and other dramatic pitch change effects. Figure 5 shows some of the effects of frequency modulation. As the modulation depth is increased, frequency sidebands are generated. Their spacing and amplitude are determined by the modulation depth and the modulation and carrier frequencies. To precisely calculate them involves some complex maths and Bessel functions (which I have forgotten all about). To make matters worse, synthesisers usually use voltage controlled oscillators with an exponential transfer function, which tends to exponentially distort the sideband positions. But so what! Music synthesisers are all about making music and not the calculation of sidebands. If a particular electronic device produces a useful musical effect, then use it, don't analyse it.

The output from an oscillator is known as an excitation signal. This defines the pitch of the signal, and to a certain extent the harmonic content of the final signal. It is common practice to filter the excitation signal (Fig. 6). The frequency response of the filter is referred to as a formant. The formant modifies the harmonic spectrum of the excitation, producing a colouration amplitude contour or envelope (Fig. 7). A sound that has a sharp attack and a slow release is similar to a plucked instrument. Other envelopes will make the sound seem like something else.

Building Blocks

Most synthesisers are constructed from standard building blocks, and most of these blocks are voltage controlled. This is a very powerful concept, because it enables you to control a unit with a combination of control voltages and/or audio signals. Building blocks can be patched together in any arbitary order to produce any system that is wanted. Some standard building blocks are detailed below.

Voltage Controlled Oscillator Used to generate the pitched excitation signals. Often a VCO will generate a wide range of waveforms. The control sensitivity is usually +1 V/octave. Therefore a one twelfth of a volt change will alter the oscillator pitch by one semitone. The exponential control law is a very powerful concept. If a VCO is being driven so that it produces a melody, then adding +1 V to the control input will transpose the melody up by one octave. Thus musical transpositions are very simple to produce. Often more than one VCO will be used, so that a rich chord is obtained.

Voltage Controlled Filter This is used as a formant for the excitation signal. The VCF is generally a lowpass filter, but it can often be a multi-mode device with lowpass, highpass, bandpass and notch responses. The VCF also has a Q (resonance) control. The control sensitivity is +1 V/octave for the frequency parameter, and undefined for the Q.

Voltage Controlled Amplifier The VCA controls the level of audio signals. The control law can be linear or logarithmic. The VCA is usually controlled by an ADSR unit and is employed to generate signal envelope contours. The device is a two guadrant multiplier.

Attack, Decay, Sustain, Release unit The ADSR is used to generate the signal envelope contour and also the VCF sweep waveform.

Ring Modulator This is a four quadrant multiplier or balanced multiplier. The output voltage is the product of the two input signals. It is often used to generate discordant or clangerous sounds.

0.66

0.54

0.54

0.45

NORE CUI

10

Noise source Generates random noise, which can be used in the synthesis of non-pitched sounds such as explosions. Filtered or sampled noise can be used as a random control voltage.

Low Frequency Oscillator These oscillators are used to generate vibrato in the VCO or a filter sweep in the VCF.

Keyboard Musical control interface, generating pitch voltages of +1 V/octave and also a gate signal to indicate that a note is pressed. A monophonic keyboard only allows one note at a time to be pressed, but if more than one can be pressed simultaneously then the system is polyphonic.

There are several other building blocks such as flangers, sequencers, frequency shifters, and pitch detectors, but there isn't enough space to deal with them.

Polyphonic synthesisers tend to be voice-based; ie all the building blocks are pre-routed to form a voice (Fig. 8). Modular systems are not pre-routed and have to be patched, either with lots of jack-to-jack patch leads or via a matrix patch board using patch pins. Patch leads are relatively inexpensive, but the leads get in the way and it is often difficult to see just what you have patched. Matrix patch boards are easy to understand, but they suffer from crosstalk and a large board (60 by 60) might cost £500!



19





SLOW ATTACK, SLOW DELAY - "PIPE ORGAN

Fig. 7 (Above) Two typical amplitude contours, or envelopes.

Fig. 8 (Top right) The standard synthesiser voice.

Fig. 9 (Right) Silicon diode transfer characteristics.

Diode Data

20

The silicon diode has an exponential transfer function, that is the diode current increases exponentially for linear increments in the diode voltage (Fig. 9). This can be used to turn linear changes from, say, a keyboard into exponential or musical intervals in a VCO. The required musical range is probably no more than 200 to 1 and so a suitable operating current would be 0.5 uA to 100 uA, thus avoiding the non-exponential parts of the curve. The silicon diode is temperature dependent (it is often used as a thermometer) and so great care must be used to avoid thermal problems. The junction voltage changes by - 1.9 mV/°C, but a semitone change is equivalent to 1.5 mV, therefore a 1°C change could result in a 1.27 semitone change in pitch! Figure 9 shows two temperature effects in operation; there is a large shift and the slope of the line changes.

Figure 10 illustrates the equations that determine the diode operation. Two facts emerge from these equations. First, an 18 mV change in V_{BR} will double the current I_{O} and second, this parameter has a temperature coefficient of $-0.33\%/^{\circ}C$. Both the temperature problems can be resolved by using a circuit similar to that shown in Fig. 11. Transistor Q1 is run at constant current (12 uA) by the op-amp. Q2 is used as the exponentiator transistor. The emitter of Q2 is held at a voltage of about -0V6. Any voltage change at the base of Q2 will result in an exponen-



ETI APRIL 1982

A couple of LFO units are shown in Fig. 14. All four output

waveforms can be usefully employed to sweep VCOs and

VCFs. Often the waveforms are mixed together to produce

strange frequency modulations. When the sawtooth is fed into

one side of a ring modulator and noise into the other, a beat

track can be generated; it sounds a bit like a cymbal being hit.

In 'the old days' noise sources were made by amplifying the noise current of a diode junction that was zenering. These were

LFO Circuits

Noise Generators

tial change in the collector current of Q2. Q1 and Q2 are in thermal contact and so any temperature change will effect both equally. Thus the -1.9 mV/°C factor is cancelled out by Q1 acting as a compensating thermometer for Q2. The slope change is removed by using a temperature sensitive resistance (Q81 - Tel Labs) which has an equal but opposite temperature coefficient to the diode junction. This resistor is often in thermal contact with the matched transistors. If this circuit is connected to a linear current controlled oscillator, a musical VCO is produced.

VCO Circuits

Figure 12 is the circuit for an exponential VCO using an exponential current source. The oscillator is a standard trianglesquare wave device. IC2 is a current-controlled integrator; the slow rate at its output is equal to IABC/C. This voltage is buffered by IC3 which drives a Schmitt trigger IC4. The output of IC2 ramps up and down between the two hysteresis levels which are determined by the two clamping diodes connected to the output of IC4. Any stray capacitance on the output of IC4 will slow down the Schmitt trigger and this will make the VCO go flat at high frequencies. Also the propagation time delay around the oscillator will cause a flattening out ot the response at high frequencies. These effects can be nulled out but they may not even affect things if the VCO frequency is kept relatively low.

A very good VCO is shown in Fig. 13. It is a monolithic device, the CEM3340 from Curtis Electromusic Specialities Inc who make a range of electronic music devices. As can be seen, very few external parts are needed to implement the VCO. All the temperature compensation is performed inside the chip. Triangle, sawtooth and variable mark/space square wave outputs are simultaneously available. The mark/space ratio is a voltage controlled parameter. A sync input is also provided so that the VCO can be slaved to another oscillator.



300 1 PEED RANGE

2208

m

a bit unreliable, and always involved selecting the device. However, noise can be generated digitally with a maximum length pseudorandom sequence generator (Fig. 15). The noise spectrum is relatively flat and always the same. If you slow down the clock rate you can get some interesting sounds; I think that this is used on some TV games. If a longer shift register is used, say 30 or 40 stages (the 4006 is 18 stages long), and the noise source is turned on, a tone is initially heard which gradually changes into noise as the sequence becomes more scrambled up. You can purchase a monolithic noise generator (pseudorandom); it is the MM5837 made by National Semiconductor, also sold by AMI with the part number \$2688.



Fig. 15 A digital noise source (top) and a noise generator chip (bottom).

Five pages gone already, and we've still only scratched the surface of this fascinating subject. In part two next month, Tim Orr will continue his discussion of electromusic techniques with yet more circuit building blocks.

Fig. 14 A triangle/square wave LFO (top) and a sawtooth/pulse LFO (bottom).

ETI

introducing



Aura Sounds have pleasure announcing the Comet, the "Band in One" organ, is now available through our branches. Once again the Comet achieves the optimum performance in its class.

It offers:-

The WERSI Comet

THE COM

- Numerous realistic and interesting tonal colours with guitar voices, synthesiser and other modern sounds together with the more traditional drawbar and orchestral sounds
 - Playing aids include chord memory, WRS, Keyboard Selector, Wersi matic rhythm and automatic accompaniment section plus much, much more

CLANE UP OF CAMET KEYBOARD

• Comet can accept up to four satellite keyboards (in addition to the 2 keyboards on the organ — a five man band can play on one instrument.

• Wersi have simplified self assembly even more, with plug in circuits etc.

· Ergonomic playing table cases operation.

The Comet is available in the elegant lines of the spinet (W10-S) and with chromed steel legs (W10 T) for transportability.

The Comet, the Organ to see us through the eighties - available now.

For more details of this superb organ, ring us now on 01-668 9733 or write to Aura Sounds Ltd. at the Purley Branch.

are the first company to successfully market WERSI

AURA SOUNDS LTD.

organs and hits in the U.K. We have modern showrooms where we pride ourselves you will receive a friendly welcome Why not pop in and see the WERSI range for yourself — we can always arrange a free demonstration. We also offer a free technical telephone support service which is second to none.

Alternatively, fill in the coupon below for free details. For immediate action telephone 01-668 9733 24 hour answering service.

AURA SOUNDS LTD.
14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.
Tel: 01-668 9733
17 Upper Charter Arcade, Barnsley, Yorkshire.
Tel: (0226) 5248
1729 Coventry Road, Sheldon, Birmingham.
Tel: 021-707 8244
Micro Centre, Albany Road, Newquay, Cornwall.
Tel: Newquay 5953

WERSI and AURA - The Winning Combination

THE COMET TRANSPORTABLE WIGT

	2	
T SPIN	ET WIOS	
Ple	ase send me FREE, all	the details of The Comet and
NA AD	DRESS	

Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.

PROJECT

ACCURATE VOLTAGE MONITOR



This simple, low-cost instrument can be built into power supplies or used as a portable or fixed 'battery condition' monitoring meter. Design by Simon Campbell and Roger Harrison.

ommon storage batteries to power nominal 12 V DC electrical systems have a terminal voltage that ranges from a little over 10 V when discharged to around 15 V when fully charged, the operating voltage being somewhere in the range 11V5 to 13V8. Lead-acid batteries, for example, may have a terminal voltage under rated discharge that commences at around 14V2 and drops to about 11V8. A 12 V (nominal) nickel-cadmium battery may typically have a terminal-voltage under rated discharge that starts at 13 V, dropping to 11 V when discharged.

Equipment designed to operate from a nominal 12 V DC supply may only deliver its specified performance at a supply voltage of 13V8 — mobile CB and amateur transceivers being a case in point. Other DC operated equipment may perform properly at 12V5 but 'complain' when the supply reaches 14V5.

To monitor the state of charge/discharge of a battery, a battery-operated system or the output of power supplies, chargers, etc, a voltmeter which can be easily read to 100 mV over the range of interest (10 to 15 V) is an invaluable asset. This project does just that.

The Circuit

An LM723 variable voltage regulator is employed to set an accurate 'offset' voltage of 5 V, and the meter (M1) plus the trimpot RV2 and R3 make up a 5 V meter, with the trimpot allowing calibration. The negative terminal of the meter is connected to the output of the 723 so that it is always held at 5 V 'above' the circuit negative line. The positive end ETI APRIL 1982 of the meter goes to a zener which will not conduct until more than 5 V appears between the circuit + ve and - ve lines. Thus the meter will not have forward current flowing through it until the voltage between the + ve and - ve rails is greater than 10 V, and will read full scale when it reaches 15 V (after RV2 is set correctly).

The meter scale limits may be adjusted by setting the output of the 723 higher or lower (adjusted by RV1) and setting RV2 so that the meter has an increased or decreased full-scale deflection range.

A variety of meter makes and sizes may be used.

Construction

Mechanical construction of this project has been arranged so that the PCB can be accommodated on the rear of any of the commonly available moving coil meter movements. We chose a meter with a 55 mm wide scale (overall panel width, 82 mm). A meter movement with a large scale is an advantage as it is considerably easier (and more accurate) to read than

HOW IT WORKS.

The meter, M1, is a 1 mA meter with series resistance — made up of R3 and RV2 — so that it becomes a 0-SV voltmeter. The negative end of the meter is maintained at S V above the circuit negative line by the output of IC1, a 723 adjustable regulator. The positive end of the meter is connected to the circuit positive line via ZD1, a 4V7 zener diode. Thus, no 'forward' current will flow in the meter until the voltage between the circuit negative line and the circuit positive line is greater than S + 4.7 = 9V7.

Bias current for the zener is provided by a FET, Q1, connected as a constant current source so that the zener current is accurately maintained over the range of circuit input voltage. This ensures the zener voltage remains essentially constant so that meter reading accuracy is maintained.

The trimpot RV1 sets the output voltage of the 723. This determines the lower scale voltage. Trimpot RV2 sets the meter scale range, less resistance decreases

Diode D1 protects the circuit against damage from reverse connection.

23



Fig. 1 Circuit diagram for the Voltage Monitor.

PROJECT : Voltage Meter

Having chosen your meter, drill out the PCB to suit the meter terminal spacing first. The components may then be assembled to the board in any particular order that suits you. Watch the orientation of the 723, ZD1, the FET and particularly D1. The latter is an 'idiot diode'. That is, if you have a lapse of concentration or forethought and connect your project backwards across a battery, the fuse will blow and not the project. Fuses are generally found to be cheaper than this project!

Seat all the components right down on the PCB as the board may be positioned on the rear of the meter with the components facing the meter. The size of C2 may give you a little trouble. Polyesters are generally too large and therefore unsuitable. We used a ceramic type capacitor — as commonly used on computer PCBs as bypasses. Alternatively, a 100n tantalum capacitor (+ ve to pin 2 of IC1) may be used. The actual value or type of capacitor is not all that critical.

We have used multiturn trimpots for RV1 and RV2 as they make the setting up a whole lot easier

Calibration

For this you will need a variable power supply covering 10 to 15 V and a digital multimeter (borrow one for the occasion).

First set the 10 V point. Connect the digital multimeter across the power supply output and adjust the power supply to obtain 10.00 V. Set the mechanical zero on the meter movement to zero the meter's pointer. Connect the unit to the power supply output and adjust RV1 to zero the meter needle.

Next, set the power supply to obtain 15.00 V. Now adjust RV2 so that the meter needle sits on 15 V (full scale). Check the meter reading with the power supply output set at various voltages across the range. We were able to obtain readings across the full scale within \pm half a scale reading (\pm 50 mV). With a 2% FSD accuracy meter the worst error may be about \pm one scale division.

BUYLINES.

Only one thing to comment on here; when you purchase your LM723 (or uA723 same thing) make sure you get the version that comes in a T099 case, not the DIL version. The PCB is designed for the 10 pin version as shown in the overlay and the DIL type won't fit. Speaking of PCBs, as usual you can get it from us using the order form on page 44.

-	PAI	RTS LIST_	
Resistors	(all ¼W, 5% metal film)	Semicon	ductors
R1	470R	IC1	LM723 (see Buylines)
R2	390R	Q1	2N3819
R3	1k0	D1	1N4002 or similar
		ZD1	4V7 400 mW or 1 W zener
Potention	meters		
RV1.2 10k cermet multiturn Miscella		neous	
	horizontal trimpot	M1	1 mA meter (see text)
		FS1	500 mA fuse and In-line fuse
Capacito	rs		holder
C1	4u7 10 V tantalum	PCB (see Buylines); meter scale to suit	
C2	100n ceramic	meter; red and black cable, etc.	
C3	10u 10 V tantalum		



Fig. 2 Component overlay for the Voltage monitor. Note that IC1 is in a 10-pln T099 case.

BATTERY CONDITION AND TERMINAL VOLTAGE

The 12 V battery, in its many forms, is a pretty well universal source of mobile or portable electric power. There are lead-acid wet cell types, lead-acid gel electrolyte (sealed) types, sealed and vented nickel cadmium types, and so on. They are to be found in cars, trucks, tractors, portable lighting plants, receivers, transcelvers, aircraft, electric fences and microwave relay stations — to name but a few areas.

No matter what the application, the occasion arises when you need to reliably determine the battery's condition state of charge, or discharge. With wet cell lead-acid types, the specific gravity of the electrolyte is one reliable indicator. However, it gets a bit confusing as the recommended electrolyte can have a different S.G. depending on the intended use. For example, a low duty lead-acid battery Intended for lighting applications may have a recommended electrolyte S.G. of 1.210, while a heavy-duty truck or tractor battery may have a recommended electrolyte S.G. of 1.275. Car batteries generally have a recommended S.G. of 1.260. That's all very well for common wet cell batteries, but

measuring the electrolyte S.G. of sealed lead-acid or nickel-cadmium batteries is out of the question.

With NICads, the electrolyte doesn't change during charge or discharge.

Fortunately, the terminal voltage is a good indicator of the state of charge or discharge. In general, the terminal voltage of a battery will be at a defined minimum when discharged (generally between 10 and 11 V), and rise to a defined maximum when fully charged (generally around 15 V). Under load, the terminal voltage will vary between these limits, depending on the battery's condition.

Hence a voltmeter having a scale 'spread' to read between these two extremes is a very good and useful indicator of battery condition. It's a lot less messy and more convenient than wielding a hydrometer to measure specific gravity of the electrolytef

The charge and discharge characteristics of typical lead-acid and sealed NICad batteries are given in the accompanying figures.

ETI

Micro-processor universal Timer

This incredibly versatile programmable timer can control up to 20 functions at accurately timed intervals over a period of a week. Originally developed for industrial and laboratory use it offers many interesting and enciting oceable ties for the amateur constructor Based on a pre-programmed TMS 1000 Microprocessor. the unit provides a 24 hour clock with four independent relay

** controlled outputs with a programmeble period of one week. Up to 20 daily or weekly programmable

functions can be bet via a keyboard. Any of the timer functions can be assigned to control any one of the four relay outputs thus providing almost unlimited programming possibilities.

No previous experience of microprocessor programming is necessary since the manual explains all the possible operations, clearly and simply, enabling the inexperienced user to be fully conversent within one hour. Completed programme steps are indicated by LED's The kit comes complete with printed panel and may be installed either as a 'built-in' or a 'free standing' unit. A stabilised power supply mounted on a separate printed circuit board is supplied with the unit. It requires the addition of a 12V, 1A transformer. There is space on the board for

up to four output control relays. One is supplied with the ldt. Further relays meybe ordered separately as required. Price: fexcluding wooden housing as Justrated) \$48.37 inclusive of VAT and DELIVERED FREE on U.K. mainland.

APPLICATIONS

The programmable timer can provide central control of domestic electrical cooking, heating and entertainment equipment. The possibilities are limited only by the imagination of the user Control of house lighting to discourage intruders; control of TV or audio equipment; sound or video recording control; autometic plant watering, automatic pet doors or feeding - are a few simple examples. For the professional or industrial user many uses in this area of process control will be found

TECHNICAL DATA

invested on separate acts with space for a ace for up to four output CONTROL BRITCHING

Please send me your free catalogue of Velleman electronic fits:

dard relays forte suggind with bitt will switch 2A, undergrad relation may be presented separately

NICROPROCESSOR TMPS 1000 DISPLATE 12000 7 segment LED in programme fungtion and interest depters LED DIFFICULTY GRADE: 2

P.O. Box 30, St. Leonards on Ses, East Sussex TN37 7NL Tel: Hastings (0424) 753246

Name Address



THE VELLEMAN KIT RANGE 2 Water

Mono VU using LED's 7 W sitt amplifue Demma 1000 W sit Dummer 1000 Wert o High precision stephetich Marchener and the second target 20 Wett monor M oscillator Steres VU using LED's and mone pre a BD Wett open antalian Power supply 1 Amp Power supply for stores 60 Watt amplifier mang light of second nate dia 1 counte Transietor grieton d pereran D Ha crystal base channel infra red remote control litenemitter at receiver) Infra red detection system (transmitter or PROPERTY N antral darm und FM starse decoder High quality FM tuner Digital frequency counter for re CE power supply 3.5 Amp 12V 0100-070 Digital thermometer FM stereo receiver (19 m, rack.me 2 channel who red remote central light dimmer (transmitter or receiver) telles sed receiver for tuner 62968 telles red transmitter for tuner 62968 Yape, slide synchronizer 3 channel coloured light organ 20 cm display (common anode) 20 cm display (common cathode) In tone ball HAY DE 1 Amp Unwertal cover supply Light computer neveral stores pre amplifier teres RIAA corrector amplifier Universal & digit up/idown counter with reprocessor doo had with 25 horses. 40 Watt audio ampifiar Electric drill speed control Microprocessor controlled [PROM programmer that formal

programmer (built and tested) 64 and start/stan

Repair Service available for a nominal charge) If your soldering technique is not quite what it should be!

Any technical enquiries welcomed in writing -and will be answered promptly by letter.

TRADE ENQUIRIES WELCOME

Limited

ETI

COMPUTER EXPANSION SYSTEM

How's your memory? If you're lacking EPROM and the ability to program it, the fourth of our expansion cards is just what you need. Design by Watford Electronics.

his month we present an EPROM programmer and associated EPROM cards suitable for the machine code freak to store away those beloved extra routines or the space invaders freak to capture his aliens in 0's and 1's for life.

The first major consideration when designing an EPROM programmer is just what EPROMs should it be capable of blowing. There is more than just a little confusion here. There are two basic types of EPROM currently available — those that run off a three rail supply and those that run from a

and the state of the second

A6-2 C	D 23-A8
A5-3 0	P 22-A9
A4-4 C	P 21-Vpp
A3-6 C	o 20-CS
A2-6 C TEXAS 2516	D 19-A10
A1-7 C	p 18-PGM
A0-8 0	p 17-07
00-9 C	0 16 - 06
Q1-10 Q	p 15-05
02-11 c	p 14-04
V _{SS} -12 C	p 13-03
P	-
A7-1 d•	0 24-V _{CC}
A7-1 d •	0 24-V _{CC} 0 23-A8
A7-1 d • A6-2 d A5-3 d	0 24-V _{CC} 0 23-A8 0 22-A9
A7-1 C+ A6-2 C A5-3 C A4-4 C	0 24-V _{CC} 0 23-A8 0 22-A9 0 21-V _{PP}
A7-1 d A6-2 d A5-3 d A4-4 d A3-5 d	D 24-V _{CC} D 23-A8 D 22-A9 D 21-V _{PP} D 20-OE
A7-1 d • A6-2 d A5-3 d A5-3 d A3-4 d A3-6 d A2-6 d INTEL 2716	0 24-V _{CC} 0 23-A8 0 22-A9 0 21-V _{PP} 0 20-OE 0 19-A10
A7-1 d • A6-2 d A5-3 d A4-4 d A3-5 d A2-6 d INTEL 2716 A1-7 d	24-V _{CC} 23-A8 22-A9 21-V _{PP} 20-OE 0 19-A10 0 18-CE
A7-1 d • A6-2 d A5-3 d A4-4 d A3-5 d A2-6 d INTEL 2716 A1-7 d A0-8 d	5 24-V _{CC} 5 23-A8 5 22-A9 5 21-V _{PP} 5 20-OE 5 19-A10 5 18-CE 5 17-O7
A7-1 d A5-2 d A5-2 d A5-3 d A4-4 d A3-5 d A2-6 d INTEL 2716 A1-7 d A0-8 d O0-9 d	9 24-V _{CC} 9 23-A8 9 22-A9 9 21-V _{PP} 9 20-OE 9 19-A10 9 18-CE 9 17-07 9 16-06
A7-1 d A5-2 d A5-2 d A5-3 d A4-4 d A3-5 d A2-6 d INTEL 2716 A1-7 d A0-8 d C0-9 d D1-10 d	24-V _{CC} 23-A8 22-A9 21-V _{PP} 20-OE 0 19-A10 0 18-CE 0 17-O7 0 16-O6 0 15-O5
A7-1 d A5-2 d A5-2 d A5-3 d A4-4 d A3-5 d A2-6 d INTEL 2716 A1-7 d A0-8 d C0-9 d D1-10 d O2-11 d	D 24-V _{CC} D 23-AB D 22-A9 D 21-V _{PP} D 20-OE D 19-A10 D 18-CE D 17-07 D 16-O6 D 15-O5 D 14-O4

Fig. 1 You can program these EPROMs

26

single + 5 V rail. The two sizes of PROM most popular at the moment are 2K x 8 and 4K x 8. Ahal here manufacturers have had some fun. Intersil and others like calling their triple rail PROMs 2716 and 2732 whereas Intel make their 2716 and 2732 single rail; not to be missed out Texas try to settle the balance by nominating their EPROMs 2516 and 2532; both are single rail!

To clear up the matter our programmer will program single rail EPROMs only, these being the most popular. It will program the Texas 2516 2K x 8 EPROM and Intel 2716 2K x 8 EPROM as these are pin-for-pin compatible (see Fig. 1). However, 2532

HOW IT WORKS

PROM PROGRAMMER

The hearl of this board is two 6520 peripheral input-output chips — they serve to generate the address bus, the data and control signals for the chip being programmed.

R1 and C1 generate the power up reset; C4, 5 and 6 are included in for decoupling. The rather peculiar need of the V_{pp} pin for 0, + 5 V and + 25 V is met by the PSU and switching circuit. Transformer T1 supplies 30 V AC to the bridge which rectifies it and feeds it to smoothing capacitor C3. IC3 and ZD1 regulate this to + 25 V DC. C2 is included in the interests of stability. Transistors Q1 and Q2 handle the switching of V_{pp} between 0, 5 and 25 V. This output is then fed to the DIL switch and then to the V_{pp} pin of the EPROM to be programmed. Ports A and B of IC2 are used to generate the address bus — note A12 is connected to pin 1 of the EPROM (on a 28 pin basis) for use later with 2764 EPROMS. The data bus is generated by port A of IC1, while port B of IC1 generates the control for V_{pp} and the C3 and PGM lines which are switched with A11 to the correct pins of the EPROM by the DIL switch.

Inputs to the 6520s are straight from the expansion sockets — ϕ 2 being used to enable the chips to reduce power consumption. and 2732 4K x 8 EPROMs are not compatible and we have stuck to the 2532, as this then allows for use of the new 2764 8K x 8 EPROMs with the minimum alteration (see Fig. 2). If you wish to program 2764's then you must make the alterations to correct the \overline{OE}/V_{PP} and \overline{CS} lines. A12 has been brought to pin 1 and power (V_{cc}) to pin 28.

Selection of the type of EPROM you want to program is made by means of a quad DIL switch. This switch is unusual in that each section operates two oppositely biased single pole switches — this means it can be

A7-1 0		24-Vcc		
A6-2 C		0 23-A8		
A5-3 C		0 22-A9	2516	263
A4-4 C		p 21-Vpp		
A3-5 q	TEXAS THAS 2516 2K±8 THAS 2532 4K±8	p 20	- 25	PG
A2-6 Q		0 19-A10		
A1-7 q		p 18	- PGM	A
A0-8 C		p 17-07		1
00 9 0		p 16-06		
01-10 d		p 15-05		
02-11 d		0 14-04		
ss-12 c		p 13-03		
NC-1 a	• •	P 28-VCC		
A12-2 0		0 27-NC		
A7-3 a		0 26 NC		
A6-4 0		0 25-A8		
A5-5 C		0 24-A9		
A4-6 0		p 23-A11		
A3-7 Q	MOSTEK 2764 BK±8	p 22-OENPP		
A2-8 0		p 21-A10		
A1-9 0		p 20-CS		
A0-10 d		0 19 07		
00-11 0		0 18-06		
01-12 0		0 17-06		
02-13 0		p 16-04		
Vss-14 g		p 16-Q3		

Fig. 2 ... or these ones.

ETI APRIL 1982

PROJECT



Fig. 3 Circuit diagram of the EPROM programmer, with details of SW1. ICX is the EPROM to be programmed.



Fig. 4 Overlay for the EPROM programmer. The zero insertion force socket position has extra holes to allow for 2764s.

ETI APRIL 1982

PARTS LIST					
PROM PROGRAMMER					
Resistors (a	11 ¼ W, 596)				
R1.2	1k0				
R3	22k				
Capacitors					
CI	4u7 25 V axial electrolytic				
C2.4.5.6	100n ceramic				
C3	470u axial electrolytic				
Semicondu	ctors				
IC1.2	6520/6820				
1C3	78L05				
Q1	2N3904				
Q2	2N3906				
ZD1	20 V, 1W3 zener diode				
BR1	1 A, 50 V bridge rectifier				
Miscellane	bus				
SW1	Quad DPST DIL switch				
PCB (see Buylines): DIL sockets:					
transforme	r (6 VA, 0-15-0-15)				

used as a 4 pole changeover switch and makes it ideal for the job. Two of the four sections are used for chip power (+5 V) and the programming can be destroyed if V_{pp} is applied with V_{qc} disconnected. The other two sections are used to switch CS, PGM and A11 to the correct pins of the ZIF socket according to whether a 2516 or 2532 is to be used.







A similar method has been used on the EPROM card. As there are four sets of switches needed for four EPROMs a 16 pin header four and socket have been used. You can make up a header for four 2516s and two 2532s and easily change the role of the board by simply exchanging header plugs. This retains better flexibility than jumper links and is cheaper than the method previously considered. The DIL header plug can be wired as in Fig. 3. Refer to Fig. 7 for an explanation of how the header plug is

Construction

wired.

Construction of the two boards is very straightforward — follow the overlays given here. Note that if you want to move the card around in memory then simply break the connections CS5, CS6 to CS2 of the 6520 and re-make to the CS line you desire.

Use two Veropins or similar to bring the 30 V AC from the transformer to the board — unfortunate as it is using a transformer mounted off the PCB to generate the V_{ex} voltage, it is about the only practical way from a computer that has supply rails of 0 and 5 V.

Fit the 28 pin DIL socket at the IC1 position on the EPROM board. This is to allow experimenters to fit a 2764 8K chip at a later date.

When you have finished you will have a very powerful means of customising your system to your own specifications. To mention one use: you could burn a renumber routine into ROM and then while writing a BASIC program simply renumber by calling the routine through the USR(X) function.

E

29

MICROCOMPUTER COMPONENTS AND SYSTEMS LOWEST PRICES FASTEST DELIVERY



ETI APRIL 1982

electronics tod BOOKS How to order: indicate the books required by ticking the books and Argus Specialize Publications Ltd., Hill Charing Cross Road, London Atring any please. All prices include P & P. P.	ay international ERVICE send this page, together with your payment, to ETI Book Service, WC2 OLE. Moke choques payable to ETI Book Service. Payment in Wide may be subject to change without notice
Beginners Guide to Electronics Squires 64.50 Beginners Guide to Integrated Circuits Sincler 64.50 Beginners Guide to Audio Sincler 64.50 Beginners Guide to Audio Sincler 64.50 Beginners Guide to Audio Sincler 64.50 Introducing Mieroprocessers BE.20 Understanding Electronic Circuits Sincler 64.50 Introducing Mieroprocessers BE.20 Understanding Electronic Components Sincler 65.30 CV Typewriters Cookbook 69.55 Color Cookbook 61.55 C 000 Cookbook 61.55 C 000 Cookbook 61.05 C 000 Cookbook 61.05 Beginner 7 Guide Electronic Components Sincler 65.30 Philes Cookbook 61.55 C 000 Cookbook 61.05 Beginners Guide Cookbook 61.05 Beginners Guide Cookbook 61.05 Beginners Guide Cookbook 61.05 C 000 Cookbook 61.00 D 000 Cookbook 61.00 C 000 Cookbook 61.00 C 000 Cookbook 61.00 C 000 Cookbook 61.00 D 010 Thiers 000 Cookbook 61.00	Microprocessors and Microcomputers for Engineering Students and Technicians Woolland (E.S.8) Digital Counter Handbook Frenzel (E.S.8) Digital Counter Handbook Frenzel (E.S.8) Digital Counter Handbook Frenzel (E.S.8) Digital Counter Games for TRSDO Apple-Pet Chance (E.S.8) Mow to Build Your Own Working Robot Pet Datesta (E.S.8) Mow to Build Your Own Working Robot Pet Datesta (E.S.8) Mow to Build Your Own Working Robot Pet Datesta (E.S.9) How to Statistic Computers Barden (E.S.9) How to Statistic Computers Barden (E.S.9) Mow to Troubleshoot and Repeir Microcomputers Law (E.S.9) More Computer Pergrammes and Interfacing with Experiments Statigard (11.46) Propermants In Artificial Intelligence for Small Computers (7.28) Mow to Grouble of Microcomputers Johnson (2).76 Digital Signal Processing, Theory and Applications Reper (2).40 Momer (2).40 More Court Design Heartbook Dation of active (1).55 Electronic Components Bartence Book Turner (82.00) Microprocessors Reference Book Turner (82.00) Betronic Engineers Reference Mow (10.70) Interduction to Digital Filtering Boor (13.00)



ETI APRIL 1982

BIRTHDAY COMPETITION.

WIN A CRIMSON ELEKTRIK **CK1010/CK1100 100 W AMPLIFIER WORTH £230!**

Below are 16 amplifier parameters. Choose the ten you think contribute most to a good quality sound and place them in order of importance. For example if you think that Flat Frequency Response is the most important factor determining good amplifier sound, place 'E' in the first box.

Fill in your name and address on the coupon and list your ten letters (in order) on the outside back of the envelope. Closing date is April 30th 1982, and you must use the coupon provided on page 133. Multiple entries are acceptable, but each must be on a separate coupon.

RULES

- I. Choing dote is April 20th 1902, and all entries performance of the response of the entries of the entri

- 1
- only. The judger decision is to be considered final and a correspondence will be entered into concorning d .

- Wide Bandwidth
- B Precise RIAA Equalisation
- Separate PSU for Each Channel C
- D **High Power Output**
- **Flat Frequency Response** E
- Low Harmonic Distortion F
- G Low Crosstalk
- H.
- Stability of output under any loading
- Ability to drive low impedance Adequate heatsinking
- K.
- Conservatively-rated output stage L
- M. Provision of tone controls
- DC Coupling N
- Short Circuit Protection P
- R. Low Feedback
- €. Flat open-loop response.





OEM USERS

New amplifier boards to meet new

needs

New Signals

With digital audio now a reality and third generation noise reduction techniques with us already, the dynamic range of programme material is about to shoot up by a phenomenal 30dB. If the amp you work with at the moment can just cope, it's going to be in serious trosuble when faced with the new signals. The clipping that will result will sound nasty and probably kill tweeters with its high frequency energy content.

J.W.R. have already solved the problem for you with their new high power PFAs. Designed to meet the exacting requirements of heavy duty P.A. and the even more exacting requirements of audiophile use, the ultra wide dynamic range modules can handle the most demanding of source signals.

The PFA/HV

The four powerfet module is designed to run from supply rails up to ± 100V. Rated at 300W continuous RMS into 4 and 8 ohms and 250W into 16 ohms, the module can sustain, for musically significant periods of time, RMS powers of 500W into 8 ohms and 900W into 4 ohms, It also has the ability to drive 70V line distribution systems directly, obviating the need for expensive and quality compromising transformers.

This amp is designed particularly with music in mind. We anticipate usage often at only 50W to 100W average levels leaving 10dB of headroom.

PFA 500

This module uses 8 H-PAK powerfets and is designed to produce a continuous RMS output current of 25 amps and will run from a supply of up to ± 70 volts. The Unit will drive 250W continuous RMS into 8 ohms, 450W into 4 ohms, 600W into 2 ohms and 700W into 1 ohm.

Numerous features are included in the board to optimise efficiency. The H-Paks (thermally more efficient than TO3) are presented at ninety degrees to the P.C.B. so they can bolt directly onto the heatsink, instead of via the usual angle bracket. The resultant chip to heatsink thermal resistance is very low keeping junction temperatures down and efficiencies up. The Powerfet supply rails are kept separate from the rest of the amp. This enables the driver stage to be run from slightly higher rails resulting in larger undistorted output swings at little extra cost.

In addition a bridge mode input pin is available on board permitting instant bridge mode between any two boards without the need for separate inverting amps. Powers comfortably in excess of 1KW can be delivered into 4 ohms in this configuration.

N.B. The new boards exhibit the same exemplary noise and distortion performance of the PFA80/120,

OPTIONS

We are particularly sensitive to a manufacturers individual requirements, and all our boards come with many options (including higher slew rates, response tailoring etc.). The chances are we've got what you're looking for, and if not, we can probably do it for you by next week!

INTERESTED? Phone Phil Rimmer on 01 800 6667 with your application requirement.



THE POWERFET AMPLIFIER



(100



....

ALLANT, IN.

0 12. 6000 / 1 40 / 10 / 10

Man-Million + 148 8.000% tes Color and Saray Call To units of a Matter 45. Fb 2 ----10 A 7 AM

anner an a Grant Care a

THE POWERFET SPECIALISTS J. W. RIMMER Mail order only to Dept ETU11, 148 Quarry Street, Liverpool L25 6HQ. Telophone: 051-428 2651 Tachascel en 367 Green Lanes, London N4. 107. Tel; 01-800 6667

ETI APRIL 1982

PAN

1297

FEATURE

Fancy a pair of Wharfedale E70s? Can't afford them? Then why not build 'em yourself? Peter Freebrey underwent the mystic rites of woodworking and saved himself over £100.



F or many years now there have been speaker manufacturers who have marketed kits for the 'do-it yourself' audio enthusiast. At the present time there are several well known and respected firms supplying high quality kits. One such firm is Rank Hi Fi who manufacture the Wharfedale range. Their approach to this market is the Wharfedale Speakercraft series of drive units and crossovers, together with the constructional information necessary to duplicate their ready-built units using these same components. If the demand is there someone will supply that demand. such is the case with Wilmslow Audio who sell kits of the cabinets to suit the Wharfedale units. This review follows the construction of the E70 system using the WE70 flat-pack cabinet kit.

Why build loudspeaker kits? Well, one obvious answer is to save money; often the cost of a kit is very much less than buying the completed unit. If you are reasonably competent at woodwork, it is perfectly feasible to start from scratch with just a large sheet of flooring grade ½ ° chipboard. An electric power saw makes the job much easier and can also give a better edge to the cut. It is often the edges which concern people as they are going to be visible somewhere around the loudspeaker cabinet and it is easy to think that to get rid of the ugly sight of these will be difficult. This is not necessarily true, there are several ways in which unsightly edges may be hidden from view. The simplest answer is not only to buy a kit of speakers, crossovers, and so on, but perhaps to buy a ready-cut cabinet kit as well — this does not rid you of dealing with edges, but at least they are all cleanly cutf

ETI APRIL 1982

I had heard that Wilmslow kits were of a very high standard several people having commented upon the ease with which they went together. That sort of build-up sometimes takes a bit of living up to and I waited for the delivery of the WE70 kit with some uncertainty. When they arrived my initial reaction was favourable; all cuts were clean and the method of construction looked simple and sensible. The sides, top and base are rebated by about 1/6" This not only gives you a better mechanical joint, but also makes it almost impossible to get any voids or gaps which is good, acoustically speaking. It also means that with the minimum of care the cabinet will slot together into its correct shape with no unsquare corners or leaning sides. Included with the kit were two cardboard transmission tubes for the mid-range units, acoustic damping material, grille material (both black plastic foam for the reflex port and cloth for the front), nylon grille plugs and sockets, 3 mm wander plugs and sockets for loudspeaker lead connections, and the screws to fix the speaker units themselves. Last but not least there are written instructions on how to assemble the kit.

16 Steps To Heaven

Step one in the instructions is to examine the panels for transit damage. Presumably if any damage is noticed, Wilmslow Audio should be contacted as soon as possible. Step two is to remove all dust, etc from the panels. Any excess of wood dust from the sawing operation can only do harm so vacuum all surfaces. If there were any build-up of sawdust at the surfaces to be glued that sawdust could conceivably impair any glue joints and also cause the fit of the joints to be out of true.

Step three is to assemble the cabinet without gluing to check the fit. It is also suggested that panels be swapped around to find the optimum results. This step proved to be most encouraging. I assembled one unit (panels only) and held it together with just one turn of linen tape (no string please - it can bite into the corners of the chipboard and cause you extra work later). The cabinet felt as firm as a rock. No glue, just wellfitting joints. Thus encouraged I rapidly got on to step four, which was to paint the face of the baffle board matt black. I gave it a couple of coats of sanding sealer - not so much to get a 'de luxe' finish but to seal the wood surface. Chipboard is pretty thirsty stuff and you can use up a lot of paint if you do not seal the surface first. Just be careful not to get any of the sealer or paint on the edges, as this may affect the glue joint you have to make later

Step five is to glue the midrange enclosures (transmission tubes) to the baffle boards, using plenty of glue to ensure an airtight seal. The baffle boards are recessed to take the cardboard tubes so it is easy to line up for position. I used Evostik Resin W, which is a PVA wood-working adhesive for all glue joints. It is easy to apply and may be cleaned off the hands/clothes as it is water soluble. Just don't put your speakers out in the rain! Light pressure to a PVA glued joint gives a better joint so I placed one of the side panels across the top of the four tubes to ensure a light even pressure. Rather than apply liberal amounts of glue in one dose I used sufficient so that a *small* bead of glue was squeezed out all around the tube. This was smoothed around with a handy finger and when dry a further fillet of glue was applied all round the tube/baffle joint. Four pleces of approximately 1° thick polyurethane foam are supplied which must be



glued to the rear (outside) end of the baffle tubes. Wharfedale recommend a hard rubber pad at this position but as this 1° foam is to be compressed to about 3/16° it probably is just as good.

Step six is probably the most critical point in the whole construction procedure, for at this point the cabinet panels are glued together. This entails gluing five of the six panels, the south (the side furthest from the mid-range enclosures) is placed in its position while the glue is setting but is not glued. This enables you to work inside the cabinet, fitting the crossover, acoustic wadding etc.

Wharfedale suggest that the acoustic wadding be attached to the inside of the panels before you reach this step. Wilmslow Audio suggest that the wadding be fixed after the panels have been glued. Although I only learnt of Wharfedales' suggestion after I had completed step six, I favour the Wilmslow approach for several reasons.

If the wadding is stuck/tacked or stapled to the panels before they are fitted together two things may happen: 1) some of the wadding may inadvertantly get caught between the panels and cause either an air gap or 2) force the cabinet to go together 'out of true'. Also, with the wadding in place you cannot inspect the inside comers to check that there is a continuous fillet of glue all along the joint.

If you choose the Wilmslow way you will have to cut the wadding to fit around the mid-range enclosures but in practice this proved to be a very simple task.

Getting A Grip

Holding the whole thing together while the glue sets is quite a teaser. I was fortunate to have a set of excellent clamps known as Jet System Clamps made by TMT Design Ltd of Learnington Spa. They cost about £10 per clamp but are worth their weight in gold for this type of job. The problem comes from the 1" thick foam stuck to the rear of the mid-range enclosures; this tends to force the back panel out of position. Wilmslow suggest either that clamps be used or that the joints be held firmly together with masking tape. It is possible with masking tape but only just; remember that unlike your trial fitting in step three, the foam pads are being compressed to about 3/16" and all but one panel has glue all along the edges and is quite capable of sliding all over the place! I bought a wide webbing strap from a camping shop to assist the initial stages of holding the four vertical panels approximately in place while I set up the clamps. The cost of the strap was wasted as I could not get enough tension in it to overcome the spring in the foam. ... a linen tape would have done just as well! If you are going to use masking tape then get someone to help apply the pressure to hold the front and back panels in position while you apply the tape. Lastly, cut up a thin polythene bag and place four pieces inside each comer of the panel that is not to be glued; it would be a shame if this stuck tirmly to the rest of the panels by accident!

It is useful to have a rubber-faced hammer at this stage as, having clamped or taped the cabinet firmly together, you may wish to tap the panels firmly but lightly into position. A hammer and a block of wood do the trick just as well, but try not to mark or dent any edges. The places to look for out of true joints are the corners. remember once the glue has set there is nothing you can do, so a few light taps now can save the day. Wipe off excess glue with a damp cloth. Wipe from the centre of each panel out towards the edge, try not to get any glue smeared over the panels.

Having completed step six the rest of the construction is plain sailing. Step seven is simply to remove the loose side when the glue has set (leave for at least 24 hours). I then put a small fillet of glue all around the inside of all joints BUT not up to the edges where the last panel is to fit... we want it to go back from whence it came!

Step eight is to place the drive units and reflex port trims in the baffle board and mark accurately where pilot holes for the fixing screws are to be drilled. Although the chipboard is high density it has a fairly soft texture so it is well worth buying a new ½ " drill bit. This ensures the pilot holes are clean and in the right place ... wom bits tend to wander! Although I'm sure it is unnecessary I drilled all my pilot holes just deep enough for the screws by slipping a small rubber sleeve over the drill bit at the right depth. No-one could accuse me of having any extra holes or air gaps here!

Step nine is to position the grille frame on the front of the cabinet with the cabinet lying on its back. Use masking tape to hold it in position and carefully drill a pilot hole through the grille and into the baffle board. I used a 1/16" drill bit and drilled four holes, one in each corner section of the grille frame. These holes can now be drilled out to the correct size to accept the nylon plugs and sockets that hold the grille in place. Wilmslow supply eight plugs/sockets for each grille but as Wharfedale suggested that four would be sufficient I chose the latter. It is far easier to line up four holes than eight! For the socket in the baffle board I used a 7/16" bit and for the grille and only to a depth of %-5/16". The 1/16" pilot hole may be filled with wood filler
but when the grille material is fitted I doubt that these holes can be seen. If you are happy with the finish on the baffle board then glue the sockets in now, if not, then wait until you have quite finished before fixing them In position. Do not stick the plugs in the grille until you have fixed the material in place. I used a quickset epoxy glue for these fittings.

Step 10 is to glue the black, acoustically transparent foam over the inside of the reflex port aperture. You can use either PVA glue or quickset epoxy, just be careful not to get any of the adhesive on the foam where it is over the port.

Step 11 is to position the crossover network inside the cabinet on the rear panel opposite the bass unit aperture. Before you screw it into position check that the leads from the drive units can reach their appropriate tags! Wharfedale recommend that the crossover has a piece of felt or foam between it and the panel to prevent any vibration rattles. Also in step 11 is the fitting of the input terminals through the rear panel, I smeared the threads on these sockets with some latex glue, again to ensure that there would be no air gaps. Solder the leads from the crossover to these terminals. make sure they are connected correctly, red to red and black to black!

Step 12 is to cut three 5° discs of wadding and place these in the mid-range tubes. The Wharfedale instructions that come with every Speakercraft unit specify that the packing density of this wadding should increase towards the back of the tube and that the tube should be completely filled with wadding. In view of this 1 cut two extra discs and fluffed out those towards the front of the tube.

It's In The Bag

Step 13 is to line the inside of the cabinet with the acoustic wadding and glue the remaining side into place. Now comes the tricky bit — how do you slide the wadding up behind the midrange tubes? The wadding catches on the side panel and snags up behind the tubes! Easy — get a large polythene bag 12" or more wide and about 15" to 18" long, slide the wadding into the bag, slide the bag plus the wadding up behind the tubes and, lightly holding the wadding in place, pull out the bag. Cutting the wadding to fit round the tubes sounds fiddly but turned out to be quite easy. Cut the holes for the tubes smaller rather than larger as the wadding will easily stretch to fit comfortably in place. No wadding on the loose side panel before you glue it into place! The wadding may be tacked or stapled into place.



The wadding is tacked or stapled in place.

Step 14 is to attach the wires to the drive units — observing the correct polarity (if in doubt refer to the Speakercraft instructions and double-check every connection), and screw all units and ports to the cabinet. Wire up and fit the bass unit last as the bass aperture gives you ample room to work inside the cabinet connecting wires to the crossover. The wires from the mid-range units come through small holes in the tubes and these holes should be sealed after you have connected the wires to the crossover. The fitting of the drive units should only be started after the glue joints of the final side have thoroughly set and any glue fumes have completely cleared. The comment regarding fumes is highly pertinent if you are not using a water-based adhesive. There is a possibility that the fumes could affect certain plastics used in the construction of the drive units.

Step 15: You have two working loudspeaker systems, so connect them to your amplifier and sit back and enjoy your favourite record.

Step 16. The cabinets are now ready for their final cosmetic treatment. There are a number of options open to you, they may be:

veneered either by you or a local cabinet-maker.

covered in iron-on veneer or plastic laminate.

 sealed and then painted (preferably sprayed) in colour of your choice.

 Wilmslow Audio also suggest the use of a 'Contact' type covering as these can be obtained in very realistic wood-grain finishes.

Whichever method you opt for you will probably have to attend to the cabinet edges/joints before you can proceed. Due to the small but noticeable tolerances in the cutting of the panels, the amount of glue and the pressure used during the construction, there are likely to be a few panels that are slightly proud of the edges that butt up to them. There are several ways to solve these problems but the simplest is to use one of the proprietary wood fillers. Which choice depends upon your choice of finish.

If the cabinets are to be covered in plastic laminate you can afford to use one of the more easily worked fillers such as Fine Surface Polyfilla, Alabastine or Plaster of Paris. If, on the other hand, you are going to cover them with "Contact" or simply spray-paint them then I would suggest a tougher type of filler that is less likely to crack or crumble. My choice here would be one of the car body fillers — they are easier to sand than some of the loaded general-purpose fillers from the DIY shop. So you are less likely to sand away the wood from the cabinet instead of the filler!

The grille material must be stretched over the grille frames and either tacked/stapled or glued (or both) to the inside of the frame. The material supplied by Wilmslow Audio stretched easily and evenly; I smeared PVA glue over the rear faces of the frames (having first painted them black) and stapled the material in place while the glue set. When set I trimmed off the excess material (having removed the S0-odd staples) and ran another bead of the adhesive over the edge of the material.

Looking back on the construction of this E70 loudspeaker system using the WE70 flat-packs, I can only say that I am very satisfied with the way they went together. There were one or two instructions that could have been a little clearer but they have been covered in this article. Common sense would probably have solved any uncertainties but I chose to phone Rank. Hi Fi to confirm my conclusions. The people I spoke to did not know that I was writing this review and so it is a pleasure to say the they could not have been more helpful. This entire project has been enjoyable from first to flast.

-BUYLINES -

Wilmslow Audio sell the complete WE70 package (flat pack, drivers and all components for two speakers) for E220 plus E8 carriage. Wilmslow Audio, 35/39 Church Street, Wilmslow, Cheshire SK9 1AS.

37

ETI



PROJECT

METER

ONTRAST

AUTOMATIC CONTRAST METER

What's black and white and read all over? Answer — a photographic negative, providing you've built this simple and useful device. Design and development by Rory Holmes.

ontrast ratio is a very important quality of photographic negatives that must be assessed during the printing process, in order to select the correct grade of photographic paper. The contrast of negatives depends on the type of film used, the lighting conditions and the developing process; consequently five grades of printing paper are available to enable the full range of tones from black to white to be reproduced from any negative. Grade 1 is termed the softest and it is used with the highest contrast negatives. At the other end of the scale, grade 5 is the hardest paper, which will enhance the tonal variations of poor contrast negatives.

During the design stage of this project we experimented initially with two separate photodetectors which measured the instantaneous light difference between two points. There are a number of problems with this approach, as the photodiodes and their associated amplifiers must be carefully matched in light sensitivity.

Secondly, the lightest and darkest points of the image must be known exactly, and the two photodetectors need to be simultaneously positioned on these points while the reading is taken. This is an awkward business at the best of times, but especially so in a darkroom!

We considered that a different

approach was required and developed the circuit of Fig. 1 to overcome some of these difficulties. Only one photodetector is used and the peak positive and negative voltages obtained from different light levels are followed and stored independently by sample and hold circuits.

Now, as long as the photodiode is scanned at some time through the lightest and darkest points of the image, the peak detectors will memorize the maximum and minimum voltages, and thus provide a contrast measurement.

The photodetector input stage of our meter is rather unusual in its configuration. Photodiodes are usually



Fig. 1 Circuit diagram of the Contrast Meter.

used in the 'photovoltaic mode' where the photocurrent developed and measured is linearly proportional to the light intensity. Our input amplifier has an extremely high input impedance and thus measures the open circuit voltage generated by the photodiode. This voltage is logarithmically proportional to irradiance as the graph of Fig. 2 illustrates. This is a very convenient property since the sampling circuitry can now work on the log of the light level to provide maximum and minimum values. By simply subtracting these two values with a differential amplifier we obtain a voltage that is logarithmically proportional to the ratio of the maximum and minimum light levels, ie the contrast.



Meter Made

The ETI contrast meter was intended primarily to determine the paper grade for a well balanced print; consequently a 10 LED bargraph type meter is sufficiently accurate for calibrating the five grades of paper. At today's prices this also works out somewhat cheaper than a moving coil meter and is less prone to damage. After calibration, the meter will be found very easy to use. It is switched on with the 'sample/hold' switch in the 'hold' position and placed down flat on the enlarger base with the photodetector probe anywhere in the image area. (The photodiode has been mounted in a separate probe with its amplifier in order to keep it as close to the focused image plane as possible. If it were much higher than this the detecting element would pass through an unfocused image, giving a false contrast reading).

Any red safety lights should be switched off before the reading is taken to avoid error since the photodiode is responsive at this wavelength. The sample/hold switch should now be moved to the sample position; this will clear any previous reading and start measuring light variations. Now the photodiode may be moved across the image and through the areas that look the brightest and darkest, This can be done quite slowly thanks to the peak detectors' long memory time; however, several areas should be scanned to ensure the recording of the true maximum and minimum. The eye can be deceived quite easily by those cunning optical illusions lurking among the shades of grey!

During the scanning process the reading on the LED scale will increase and finally level-off at the true contrast ratio when the black and white peaks have been covered. Before removing the meter from the image area the sample/hold switch should be set to 'hold'. The meter will now be immune to further light variations and will continue to display the contrast reading for a considerable time, thanks to the even longer memory of the sample/hold circuitry!

A true ratio is provided by the meter and thus the contrast reading for a given negative will be independent of the light source intensity and enlargement size (photographic aberrations known as "circles of confusion" may produce sources of error under certain conditions). Negatives may thus be compared or matched for contrast.

Construction

The meter is built into a slim style plastic enclosure produced by OK Machine and Tool company. This houses the battery and main PCB on which all the parts are mounted. Since the light sensing element must be as close to the enlarger base plane as possible, we have mounted it externally on a separate small PCB with its associated amplifier. A probe to house the external sensor is made from a short length of aluminium channel extrusion. Figure 3 shows the



dimensions for the probe; if the aluminium channel proves difficult to obtain, a piece of the slotted aluminium extrusion used for commercial shelf-racking systems is ideal. This is available from most DIY stores in short lengths with the required internal width. After filing or cutting to the right size, a piece of insulating tape should be stuck down on the inside to prevent shorting out the PCB. As shown in the diagram, a hole is drilled on the end for bolting it to the bottom of the case. This bolt should eventually be connected to circuit ground, thus providing screening for the photoamplifier. The two PCBs for probe and main meter circuits are laid out as one board, and should be sawn apart along the lines shown on the foil patterns.

For other construction arrangements, the circuit can be left as a single board, since the interconnections are already made.

Three wires are used to connect the two boards together as indicated on the overlay; these should pass through a small hole drilled in the case side where the metal probe case is bolted on. When the probe board is mounted and stuck down in its channel, a piece of thin aluminium sheet is cut to form a lid with appropriate holes for the photodiode and preset. (The photodiode case is internally connected to the cathode, so it must not short against the lid).

Calibration

Start with preset PR1 fully clockwise to set a gain of 1; also set PR2 fully anticlockwise, setting the voltage required to illuminate the lower end of the bargraph at zero. First, measure a high contrast negative that is known to require grade 1 paper for a good average contrast after developing. Initially a low contrast reading will be obtained, say about grade 4 or 5. Now, adjust PR1 anticlockwise to increase the gain of the photoamplifier. Take another measurement, when the contrast reading should be greater. Repeat this process until a grade 1 is consistently recorded.

Now select a negative with very poor contrast ratio, one known to require paper grade 5 for bringing out the contrast. Take measurements several times while adjusting only PR2 clockwise, until the bottom end of the scale illuminates at grade 5. The other contrast grades should now fall linearly between these points and can be checked for accuracy.

Although the bargraph display has a low resolution and accuracy, the rest of the metering circuit is obviously much better than this; consequently a moving coil meter could easily be added to measure the contrast voltage for those who may desire greater resolution. The general circuit arrangement consists of a photo-amplifier which feeds a voltage, derived from varying light levels in an enlarger, to a pair of peak detectors. One follows the peak positive voltage and the other the peak negative voltage. The capacitors used for storing the voltage peaks in the followers also form part of sample and hold circuits which are then switched to hold after measurement. Their outputs represent the maximum and minimum values of light intensity. A differential amplifier then computes the ratio of these values and the result is displayed on an LED bargraph meter.

on an LED bargraph meter. IC1, a CA3140 CMOS op-amp, is used as the photodetector amplifier. It is configured as a non-inverting DC amplifier with a gain variable from unity to about 10, set by PR1. Although IC1 can have input and output voltages all the way to ground, this facility is not used owing to the driving requirement of the TL084 quad op-amp. This requires inputs at least 1 V above ground, and thus IC1's output is offset by a eference voltage of 3V9 provided by R1, ZD1 and C1. The anode of the photodiode is connected via R2 to the non-inverting terminal of IC1 which has an effectively infinite input impedance. Thus the open circuit voltage generated by the photodiode is amplified according to the gain set around IC1 and appears at the output on pin 6 added to the reference voltage.

The voltage at point A (ignoring the reference offset) will be logarithmically

NOTE: k = CATHODE

HOW IT WORKS

proportional to the intensity of incident light, owing to the properties of the photodiode (see Fig. 2) R4 and C2 form a simple filter to remove 100 Hz ripple caused by AC mains bulbs. This voltage is fed directly to the peak detectors. These circults are essentially the same, the difference being the polarity of the rectilier diodes. They operate in exactly the same way, and we shall deal only with the peak positive voltage follower.

Assume initially that the CMOS analogue switch IC3c is open and IC3d is closed. C5 will be connected to the output of op-amp IC2c via the rectifiers D4 and 5 (we can ignore the action of R7 for the moment). C5 will charge up via the rectifiers to the most positive voltage peak when the voltage at point A on the non-inverting terminal is greater than the capacitor voltage applied to the inverting terminal. The voltage held on C5 will droop over a period of time due to leakage current through the rectifiers D4 and 5 and the input bias current of IC2c. IC2c was chosen as a FET opamp with a low input blas current and R7 is included to reduce the diode leakage current

IC2d is connected to C5 as a straightforward high Impedance voltage follower to buffer the stored voltage. When the input voltage to IC2c at point A drops below the peak value, IC2c's output will go negative, reverse biasing D4. However, IC2d applies the capacitor voltage via R7 to the anode of D5, effectively removing

0V +9V

A A

leakage current through D.5.

The peak positive value of the signal at A thus appears at point C, and likewise the peak negative value at point B. When the analogue switch IC3d is now opened, C5 is disconnected from the peak detector and acts in conjunction with IC2d as a sample and hold circuit thus isolating the measured values from further light variations.

When SW1 is open, R8 and R5 hold the control pins 13 and 5 of IC3 low, opening both analogue switches. This is the 'hold' mode. When SW1 is now closed, the control pin 13 is taken high, switching to the 'sample' mode. C3 and R5 produce a positive pulse (about 50 mS) on control pin 5 to briefly short out D4 and D5, so resetting the peak detector to the current voltage at point A. When C3 has charged the IC3c switch will open again, allowing the peak detector to function.

IC4 is wired as a differential amplifier with a gain of 2, to subtract the voltage at point C from point B. Since these voltages are the log of the light levels, the output on pin 6 will represent the contrast ratio of these light values.

IC5 is a standard LED bargraph driver, the LM3914. The input voltage on pln 5 is converted linearly to Illuminate one LED on a scale of 10. Full scale deflection (LED 10) is set internally at 1V2; the zero scale deflection is set by PR2 anywhere between 0V and 1V2 during the calibration process. C6, a 10 uF tantalum, is required for IC5 to ensure stability from oscillation.

Fig. 4 (Left) Component overlay for the meter (showing the board uncut).

	Resistors R1, 3, 8 R2, 11, 12 R4 R5 R6, 7, 9,
	Presets PR1 PR2
	Capacito C1 C2
	C4, 6 C5 Semicon IC 1,4
	IC2 IC3 IC5 D1 D2, 3, 4,
	LED1-10 Miscellar SW1, 2 Case (see PP3 9 V
RII PRZ ELI KOLED9	The phot
	the one general j we used 28 mm. 1 the order

PARTS LIST		
Resistors (all 1/4 W. 5%)		
R1. 3. 8	10k	
R2, 11, 12	100k	
R4	2k2	
R5	1M0	
R6, 7, 9, 10	47R	
Presets	7.0	
PRI	100k subminiature horizon-	
	tal preset	
PR2	1k0 miniature horizontal	
	preset	
Capacitors		
CI	10u 35 V tantalum	
i ci	22u 25 V tantalum	
lä	220u 16 V electrolytic	
C4.6	82n nolvcarbonate	
C5	68 n ceramic	
Semiconduc	tors	
IC 1 A	CA3130	
102	TLASS	
103	4066B	
lics	143914	
01	RPY65	
02 3 4 5	1N4148	
LED1-10	3 mm red LED	
Ation Bernard		
Miscellaneous		
Swit, 2 miniature side switches		
PP3 9 V battery (preferably alkaline type).		

BUYLINES.

The photodiode specified in the Parts List is the one used in our prototype, but any general purpose type should do. The case we used is a Pactec type HP, size 146 x 91 x 28 mm. The PCB is available from us using the order form on page 44 — price is £2.12.

ETI





ETIPCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore!

Now you can buy your boards straight from the designers — us! As of this issue all (noncopyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be stree it's accurate, and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that NO OTHER BOARDS ARE AVAILABLE. If it's not listed, we don't have it!

APRIL 79	C1 00	MARCH 81	61.00	NOVEMBER 81	67. P.1
Click Eliminator	£4.98	Engineer's Stethoscope	£1.34 (Voice-Over Unit	E2.98
		APRIL 81	C	J Car Alarm	E2.11
JUNE 79		U Musical Box	L1.90	Phone Bell Shifter	2.22
Accentuated Be	at metronome LL/U	Urum Machine(two boards)	63.40		
FEBRUARY 80		Li Guitar Note Expander	LLAU	DECEMBER 81	C2 00
C Tuning Fork	£1.96	III IN C. M.		Acconometer (two boards)	61.49
		D Man dell Sand Controller	62 30	Common Tester	61.10
MARCH 80		Astenna Estender	62.40	J component rester	61.14
U Signal Tracer	E1.70	Alien Attack	61 94	IANUARY 82	
		LED levellery Cross	£1.10 [Parking Meter Timer	£1.78
AUGUST 80	C1 00	Soural(two hoards)	E1.98 (Infant Guard	£1.35
U UNUS LOBIC Tes	Lor 62.10	Star (two boards)	£1.99 T	Cuitar Tuner (two boards)	E4.48
Capacitance Me	ar Alarm 52.15	U Waa-phase	£1.15		
U Ultrasonic Burgi	ai / i al i i i i i i i i i i i i i i i i i		-	FEBRUARY 82	121
OCTOBER 80		JULY 80	6	Ripple Monitor	£1.56
Cassette Interfac	te £2.20	System A A-MM A-MC	£1.99 (Pest Monitor	E1.39
C Fuzz/Sustain Bon	E2.45	System A A-PR	£3.88 (I Ching Computer (two boards)	E3.98
NOVEMBER M		Smart Battery Charger	£1.48	Moving-magnet stage	12.85
Touch Buzzer	£1.45	N STREET	1	Moving-coil stage	12.85
Light Switch	£1.45	AUGUST 81			
Metronome	\$1.45	U System A Power Amp(A-PA)	E3.50	MARCH 82	63.63
2W Power Amo	E1.45	L Flash Sequencer	22.58	Infinite Improbability Detector	64.33
RIAA Preamolifi	er E1.45	Hand-clap Synthesiser	12.98	Capacitance Meter (two boards)	29.63
Audio Test Osci	lator 62.35	Heartbeat Monitor	1.37	RODOT MOTOR COntroller	61.40
DI COLUMN DE DE		U watchdog Home Security	62.00	Cigni wand	@ 1540
DECEMBER 80		(two boards)	E.J. 76	ADDIE 87	
D Resolution	E4.10			Watemiler	63.39
	E1 90	SEPTEMBER 61		Contrast Mater	62.12
- rour input water	61.70	U Mains Audio Link (three boards)	13.31	Sound Effects hoard	£1.80
JANUARY 81		L'aboratory PSU	6.3.40	High Impedance Probe	£1.48
LED Tacho	£3.10			Guitar Practice Amp	E5.68
Multi-Option Si	ten £2.40	OCTOBER 81		Accurate Voltage Monitor	E1.54
Universal Timer	E2.48	Enlarger Timer	\$2.55		
FEBRUARY 81		Sound Bender	E1.99		
Infra red Alarmi	(four boards) E4.98	C Thermal Alarm	E1.97		
D Pulse Generator	E2.68	Micropower Pendulum	£1.66		
			-		17 a (197)

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H OEE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices may be subject to change without notice.

Total for boards	Estates
Add 40p p&p	0.40
Total enclosed	ε



ETI APRIL 1982

14

DESIGNERS NOTEBOOK

Five into one does go. This month Don Keighley explains all about sampling and time-division multiplex systems, and looks closely at the advantages of pulse-width modulated telecommunications networks.

S ampling is a process we can undertake if we want to combine many different signals on to a single transmission line. The transmission line can be of any type such as wire, radio, or optical. Combining several signals into one is called 'multiplexing' and can save the expense of having many separate lines. Sampling is used in a specific type of multiplexing called time-division multiplexing (TDM) which I'll explain later. The other form of multiplexing — frequency-division multiplexing (FDM) — is the basis of all standard radio transmissions. Each signal to be transmitted is mixed with a carrier wave (or radio frequency) on to a set frequency within the radio spectrum. Thus many signals can be transmitted and received by radio link — one on each defined frequency of the radio spectrum.

Figure 1 shows an illustration of sampling. In the figure, a sinusoidal signal (known as the message signal) has a series of values taken at regular intervals. These sample values can be used to represent the message signal. For instance, we can pass the actual DC values of the samples, ie their voltages, along the line. At the other end of the line the sample values, or pulses as they are usually called, are converted back into the message signal, simply by passing them through a lowpass filter. The filter removes the high frequency pulses and thus re-creates the envelope of the original message signal — as shown by the sinewave of Fig. 2.

One of the most important questions arising is — How often do we need to sample the message signal? It is obvious that if the signal is sampled too few times we won't be able to

reconvert the pulses into the message signal at the receiving end of the transmission line.

The minimum number of samples is given by the sampling theorem, which states that a message signal of bandwidth B Hz can be represented by a set of sample values taken at a frequency of 2B Hz. For example, an audio system has a frequency response of 20 Hz to 20 kHz. Its bandwidth is thus 20,000 - 20 = 19,980 Hz. The audio signal of the system can thus be represented if samples are taken at $2 \times 19,980$ Hz = 39,960 Hz.

But the minimum number of representative samples (2B Hz) isn't the easiest number of samples to convert back into the message signal. It's usual to take a greater number of samples because doing so makes the reconversion easier. To see why this is so we've got to take a look at the spectra of the transmitted samples and see how they differ when different sample frequencies are used. Figure 3 shows the possible spectrum of a message signal such as an audio signal. It's the sort of result you would see on the screen of a spectrum analyser. Frequency f_m is the maximum frequency contained in the signal. The lowest frequency contained is 0 Hz (the signal extends down to DC); so the bandwidth of the message signal is $f_m - 0 = f_m$ Hz.

When the message signal is sampled at a frequency f_1 , the overall spectrum looks something like that shown in Fig. 4 and consists of components at harmonics of the sampling frequency, with upper and lower sidebands around them, as well as the original spectrum of the message signal. In Fig. 4 you can see the sampling frequency, f_p is more than twice f_m — hence there is a gap between the highest frequency of the higher sideband of a



Fig. 1 A message signal can be represented by a series of sample values of the signal.



Fig. 2 If the series of sample values is passed through a lowpass filter the original message signal is recreated.

FREQUENCY

Fig. 3 Power density spectrum of typical audio signal. The higher frequency component in the signal is f_m . The signal extends down to 0 Hz, so the bandwidth of the signal is f_m Hz.





45







Fig. 6 Sampling frequency less than 21 ... A lowpass filter cannot be used to recreate the original message signal.



Fig. 7 A simple time-division multiplex (TDM) system.

component and the lowest frequency in the lower sideband of the next component. This gap between bands means that a simple lowpass filter can be used at the receiver to pass only the message signal and not the higher components: so the message signal is recreated.

With a sampling frequency of only $2f_m$ (Fig. 5) the highest frequency of one band and the lowest frequency of the next occur at the same point. A simple lowpass filter would filter out some of the message signal, as shown in the figure. A more complex lowpass filter (with a steeper roll-off slope) could be used to correctly recreate the message signal.

In Fig. 6, f_3 is less than $2f_m$ and, as you would expect, the spectrum shows how message signal and sidebands overlap. A lowpass filter cannot be used to recover the whole of the message signal without letting through part of the next sideband.

TDM Tricks

A simple TDM system is shown in Fig. 7, in block diagram form. Each signal to be transmitted is connected to an input of switch SW1. This switch, although shown in the diagram as a mechanical-type switch, will be of electronic construction in a real TDM system, so that a high switching speed can be obtained. The output signal from the switch is transmitted along the transmission line to switch SW2, which connects each receiver, in turn, to the line. Providing the switches are operating fast enough so that the sampling theorem is fulfilled ($f_{x} \ge 2f_{m}$) for all the message signals, everything is fine and we have five signals passing down one line.

The whole process of sampling and TDM is a form of modulation because only a representation of the message signal is transmitted, not the actual signal. And because pulsed samples of the message signal are transmitted, we call the process pulse modulation.



Fig. 8 Pulse-width modulation. The width of each pulse varies in accordance with the amplitude of the message signal.



Fig. 9 Pulse-position modulation. Each pulse's position, with respect to a reference point, varies in accordance with the message signal amplitude.



There are various forms of pulse modulation which can be used in a TDM system, all relying on the fact that the original sample values control some property of corresponding pulses. The one just described uses the DC value (ie amplitude) of the pulses and is therefore known as pulse-amplitude modulation. Other forms of pulse modulation are: pulse-width modulation (where the width of the pulses is varied according to the sampled value) and pulse-position modulation (the position of the pulse, relative to a reference position, is proportional to the sample value). Figures 8 and 9 show examples of these pulse modulation systems and the sampling frequencies of both must follow the sampling theorem — the sampling frequency must be at least twice that of the message signal bandwidth. There is a final pulsed system, in which each sampled value is converted into a train of binary digits. This is, strictly speaking, a digital system and doesn't concern us here; however the system must still follow the sampling theorem.

Practical Matters

With careful design all the pulse modulation systems can give good results in TDM but perhaps the best — because it's easy to use, has a high immunity to interference and yet needs a minimum of component hardware — is pulse-width modulation (PWM). Figure 10 shows a block diagram of a PWM microphone/loudspeaker set-up — such as you might have in a multi-station intercom system or similar.

We can investigate the modulation and demodulation blocks in more detail, as in Fig. 11 and 12. Figure 11 shows a simplified pulse-width modulator. It consists of an oscillator to provide sampling pulses at a rate of over $2f_{m}$, so that the sampling theorem is fulfilled. In a good quality audio modulator, the sampling rate is therefore over 40 kHz and the time between pulses must be $1/f_{e} = 25 \text{ uS}$.

The pulse duration is less than this, say 1 uS, and each pulse charges the capacitor C1 to full voltage. After charging, the capacitor is linearly discharged via the constant current source. The cycle repeats itself at every pulse. The capacitor's discharge rate is a product of the capacitor/constant current time constant, which should be about 2 uS. Comparator IC1 compares the ramp discharge with the incoming audio signal — when the non-inverting input voltage is above that of the inverting input

FEATURE : Designer's Notebook



Fig. 11 A pulse-width modulator in detail.

the comparator output is high; when the non-inverting input is below the inverting input the output is low. Thus the output is high the instant of every sampling pulse, but falls low again after a time which is linearly related to the amplitude of the audio signal. In other words, the width of the pulse is modulated by the audio signal.

A pulse-width demodulator is shown in Fig. 12. A capacitor with a parallel constant current source is again used and the incoming width-modulated pulses cause a charge/discharge cycle similar to that in the modulator. The average DC level of charge across the capacitor is dependent on the width of the pulses — the wider the pulse, the higher the DC level. Buffer IC1 prevents loading of the voltage across the capacitor and the output is lowpass filtered by capacitor C2 to remove the sharp spikes of the sampling pulses, thus re-creating the original audio message signal.



Fig. 12 A pulse-width demodulator can be built using the same basic components used in a pulse-width modulator.

The advantages of such a system aren't always immediately obvious, but you must remember that the audio signal is being represented by a pulse of nominal width 2 uS in a cycling time of 25 uS. This means that 12 different, high-quality audio signals can be time-division multiplexed down that transmission line simultaneously and without interference — and this is just a simple system. With a shorter nominal pulse width and more accurate modulators and demodulators, many more signals can be multiplexed on to a single transmission line.

It's all down to economics really. When you look at a large telecommunications system like the telephone network, there are literally thousands upon thousands of miles of expensive copper cable. By putting 100 telephone conversations down one line the overall cable cost is only 1/100th of that of a nonmultiplexed system. Makes sense, doesn't it!









PROJECT

SOUND EFFECTS 1: BOMB DROP

One of the attractions of the more sophisticated video games seen in 'fun' arcades these days is the realistic array of sound effects that go with the action — gunshots, bomb whistles and explosions, etc. Make some yourself with just one IC. Design by Phil Wait.

These 'cannon shots' and explosions that go with the popular 'Space Invaders' video games and its variants add a measure of interest, feedback and stimulation to the action in which you participate on screen. Those sounds are electronically synthesised — that is, they consist of a complex mixture of waveforms that make up the required sound.

A 'bomb drop and explosion' is a remarkably complex sound when analysed carefuly. Looking at it simply, there is a descending tone followed by a burst of noise that dies away in intensity. The descending tone starts at quite a high pitch and is not a 'pure' tone (ie a sine wave). The explosion is a burst of noise that commences suddenly and dies away slowly in a recognisable way (usually exponentially). While it is possible to electronically produce very nearly an exact replica of a bomb drop and explosion, some compromises are acceptable to reduce the complexity and cost of the task and yet produce a recognisable replica of the sound.

To produce such sound using conventional components transistors, diodes, op-amps, resistors and capacitors — would require a whole legion of components. Fortunately, the IC maufacturers can come to our rescue here and much of the circuitry can be incorporated into a complex integrated circuit requiring the addition of a minimum of external components and the appropriate interconnections to synthesise the required sound. Generating a wide variety of sounds fortunately requires only a limited number of functional blocks, such as: a noise generator, voltage controlled oscillators, multivibrators, envelope generators (a sort of modulator), mixers and amplifiers. Tim Orr discusses such circuitry elsewhere in this issue

Texas Instruments, the giant USbased component and equipment manufacturer, have designed a series of complex function ICs for various applications and among them is the SN76488 Complex Sound Generator. This chip contains both linear and digital circuitry and is intended for use in applications requiring audio feedback to the user — video games, pinball, alarms, toys, etc, or industrial indicators, feedback controls and the like. Power consumption is quite low, allowing battery operation, and only a single supply rail is required.

The SN76488 is contained in a 28-pin package and can be purchased for less than £5. It is quite a versatile chip, but we have chosen to describe how to obtain only two sound effects, these being a bomb drop and explosion, and a steam train and whistle. The former is described here; the latter appears on page 118.

Construction

Both the projects described use the one PCB design. Only the required components are assembled into the board according to each overlay diagram to obtain the required sound generator. Naturally enough, the polarity of the IC should be noted as well as the polarity of electrolytic and tantalum capacitors used. Commence construction by assembling the passive components, followed by the IC. This is not a CMOS device and no special care is required, apart from being careful not to bend any pins under the device when inserting it. If you wish, a socket may be used for the IC. This way, you can assemble both projects and purchase only one IC, swapping between the boards as you need to use them

4.84 Tes

LA.

Bat 90



Fig. 1 Circuit diagram of the Bomb Drop and Explosion sound effects board.

PROJECT : Sound Effects

Wiring to the switches, the speaker and the supply should be attached last.

The unit may be mounted in any convenient-sized box and the speaker mounted on the front. Alternatively, it may be wired into an existing piece of equipment. We'll have to leave these arrangements up to you.

Projectile Project

This produces a 'bomb drop and explosion' sound at the press of a button. Alternatively, the push-button PB1 could be replaced by a pair of relay contacts operated by a piece of equipment or a transistor (emitter to pin 9, collector to other side of PB1) that is turned on by a logic high applied to its base via a resistor.

This project is one of the most complex, using almost every functional block within the SN76488. Varying R3 and C3 a little will vary the pitch range of the 'bomb drop' (desending whistle), while varying R4 or C4 a little will alter the characteristics of the explosion. Note that it is generally easier to 'fine tune' things by varying the resistor values. The duration of the event can be varied by changing the value of either C1 or R1 and the decay of the explosion can be changed by varying R5 (varying C5 produces quite gross changes in the decay period).

Watch that you insert the link on the PCB in this one, located at the 'notch' end of the IC.

PARTS LIST.

	11 A. M. B. B. B.	
Resistors	(all ¼ W, 5%)	
R1,2,5	1M0	
R3	470k	
R4	20k	
Capacitor	5	
C1.5	4u7 16 V PCB electrolytic	
C2	22u 16 V tantalum	
C3	4n7 ceramic	
CA	470p ceramic	
Ch	10n ceramic	
C7	100u 16 V PCB electrolytic	
Semicond	uctors	
IC1	SN76488 (see Buylines)	
Miscellan	eous	
PB1	SPST push-button switch	
PCB (see	Buylines); 50 mm diameter 8 ohm	
speaker; F	P3 battery and clip.	

BUYLINES.

Very few components and very few supply problems with this one. The SN76488 is an improved version of the Texas SN76477 and can be obtained from Technomatic. The PCB will cost you £1.80 from our PCB Service; see page 44 for details.



Fig. 2 Component overlay for the Bomb Drop board.



HOW IT WORKS.

This unit employs most of the function blocks in the SN76488. The SLF provides a linearly Increasing voltage waveform, or ramp, to the VCO, taking several seconds for the ramp voltage to rise from zero to maximum value. The causes the VCO to produce a tone which 'glides' down in pitch, making the 'bomb drop' effect. The explosion is generated by the Noise Generator/Filter and the Envelope Generator. It starts with a burst of noise, which dies away in intensity exponentially in a few seconds.

The whole sequence is triggered by operating the pushbutton, PB1. This applies a high (\pm 5 V) to the input of the System Inhibit block, pin 9. This in turn triggers the One Shot and the Envelope Generator. At the commencement of the One Shot timing period, the One Shot triggers the 5LF HI/LO Sync, starting the SLF, and the VCO does its things. At the end of the One Shot timing period the Envelope Select Logic becomes operative, the SLF is disabled and the Envelope Generator commences to do its thing. The Mixer selects the VCO output at the start of the One Shot timing period and the Noise Generator/Filter output at the end of the One Shot timing period. Thus the two sounds are switched through to the audio output stage in sequence, the Envelope Generator modifying the noise so that It dies away, the time it takes to do so being controlled by the time constant of R5, C5.

The starting pltch of the VCO is determined by R3 and C3, the rate of rise of the voltage ramp produced by the SLF is determined by C2 and R2, while the One Shot timing period is determined by the time constant of C1 and R1. The frequency characteristics of the broad-band noise produced by the Noise Generator are modified by R4 and C4 connected to the noise filter control plns (5 and 6).

Audio output is coupled to the loudspeaker via C7; a 100µF electrolytic capacitor.

ET

THE 1982



Our prices are the lowest authorised dealers are allowed to advertise; lower prices = no Casio guarantee (E&OE). Nevertheless we can beat any lower price by 5%°. We have scanned last month's magazine for you and marked the lowest price we could find against a

CASIO



SYMPHONIC ALARM CLOCK

WORLD BEATERS_





28 instruments over 4 octaves, Fee voice methody function with puch hurther satection. Version on disability cases Auto Churd for and Reger or auto fill in variation Cases Auto Churd for and Reger or auto paying of major mitter and 7th chards with bass. Tan functional controls including pitch, AC only, 4 3/8 + 38 3/8 + 11 3/4, Weight 17.52b.



"Sen of excess . . . The two happelithorth damoverses the Casesana's talam. for spathing cristel clear tones. Even more impressive is the clar Matsate Makert de techungets over 4 peteres. A velop memory function

B beginversets over 4 potence. A value methany function with push button patentian. 3 values a strange and surtain. Pach control, O/P jocks. AC only, $316 \times 3616 \times 1115^{-1}$. If Bibs.



2) Instructional parts for decision. Built in otheres and metalsh. Plath control. AC same 30.3/8 = 11.3/4 = 4.6/6. Waght 16,85s.

VL-TONE (VL-1) Monophonic



VL.1 records and plays back to to 100 rotes as a restory, with nameroy break-in. Old LEV PLAV or AUTO PLAV of S and the second set of the second second set of the second set

Price includes VAT and PAP. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:



LEADING CASIO SPECIALISTS Dapi, ETI 38 Burleight Street, Cambridge CBI 1DG Telephone: 0223 312866

ETI APRIL 1982

CATALOGUE

ON REQUEST

1515p stamp

appreciated

THE SENSATION OF THE JAPANESE MUSIC FAIR

Designed by a genius. Controlled by a computer. Programmed by a laser. Played by amateurs professionally and by professionals superbly.

THE NEW CASIOTONE 701

what is going to become THE instrument of 1982, ..., probably the best instructive oard I have come across. But it is also a top line musical instrument capable of satisfying the most proficient musician ..., I suggest you place your orders now," board & Music Reyeri. opens up home music making for all the family ..., one of the most advanced music ling aids so far developed ..., this instrument is going to be one of the biggest sellers of "(Electronics & Music Mekeri. keyboard I h even the mos

1982 *



Complete Programmable Polyphonic Keyboard **ONLY £495** (RRP £555)

- Input an entire piece of music, specially scored in bar code and read by a light pen attached to the instrument. Atternatively, program your own melodies (max. 345 steps), chords (max. 201 steps) and tempo, via the texposed, into the extensive memory, (up to 5 minutes playing or more) with full editing facilities.
- 3 WAY PLAYBACK
- 3-WAY PLATBACK. Automatic playback of the entire piece: melody, chord, bass and rhythm with arpeggio. Follow the melody as it plays via lamps above each individual key. Manual melody playing, guided by the keyboard lamps, with automatic bass and rhythm 2.
- accompaniment. ONE KEY PLAY facility, allows the melody line to be played, simply by stroking one key. Non-players can become Instant Musicians! The 5 octave, B-note polyphonic keyboard can be split into 2 & 3 octaves and a different *
- 46
- The 5 octave, 8-note polyphonic keyboard can be split and 2 of 3 octaves and a different voice can be selected for the accompaniment, 20 "breathtailingly clear and bright" pre-set instruments and voices. 3-way chord section: Fingered, Memory and Casiochord auto accompaniment, 16 rhythm accompaniments with "fill in" variation and two percussion effect burttons, Start/Stop, Synchro, Tempo and Balance controls. Variable Vibrato and Sustain, 1/p & o/p jecks. Integral amplifing/apeaker, Music book, AC only, Dims: 5 x 37 3/4 x 13 4/16", Optional extrat; Foot pedals, Hard case.

CREDIT. 0% Interest, % deposit, 12 monthly repayments. (Not MT-31, MT-40 or VL-1), or reduced rates for longer period. INTEREST (0%) on ACCESS, B'CARD or VISA for first 9 months, for any keyboard purchase over £90. FREE





£100 COMPUTER

"Can do the job of a micro costing four times as much"!

Personal Computer World CASIO FX-702P POCKET COMPUTER

ONLY £99.95 Manufacturer's price reduction 1/2/82 Plus FREE MICROL Professional Programming Pack (RRP (9.95) Or we will beat any lower advertised price by 5%

Eat your hearts out, H-P, Sharp and Texas!

The Casio FX-702P features: The biggest program storage capacity (up to 1680 steps), the biggest data storage capacity (up to 226 memories), and the widest range of math, science and statistica functions (55 in all, including Regression and Correlation), the most powerful English-like BASIC program-writing language and the fastest operation, for results without waiting! Subroutines; 10 levels, FOR: NEXT looping: B levels, Comprehensive edit, debug and trace modes, 240 hours bettery life. 17 x 165 x Ecmm.

FA-2. Cassette adaptor for bulk storage of programs and data, with powerful file name and remote control options. DNLY £19.95.

FP-10. Permanent hard copy printer; full 20 character line width, fast 40 character per second print speed, 2,600 lines par noll. (Low cost replacement rolls, (2,60 for five), 5,000 to 9,600 lines battery life. Rechargeable battery pack, NP-4M, printes 13,000 lines (66,90). Mains adaptor, AD-4150, (5).

FP-10 Printer ONLY 644.95 Plus FREE Pack worth £5, or we will beat any lower price by 5%

SYSTEM PRICES - Save up to (50 on RRP	
PACK A: FX-702P + MICROL Professional Programming Pack	(99.95
PACK B: FX-702P + FA 2cassette interface + PPP + PROCOS	£139.96
PACK C: FX-702P + FP-702P + FP-10 Printer + FA-2 + PPP + PRO	DCOS E179.95

MICROL PROCOS for the 702P. Exclusive to TEMPUS

Now you can create powerful, reliable programs in just minutes with this advanced integrated operating system, even if you have never programmed a computer before! "Visicalc-type" system answers "what if" questions and analyses trends. On ready-to-run cassette, with user

CASIO FX-602P The World's Fastest Programmable?

- 500 -----00000 000000
- LCD alpha/numeric (dot matrix) scrolling display. Variable input from 32 program steps with 88 memories, to 512 steps with *
- 22 memories. Memory and program retention when switched off. Up to 10 pairs unconditional jumps (GOT0). Conditional jumps and count jumps. Indirect addressing. Manual jump Up to 8 subroutines, up to 9 lavela. 50 scientific functions, all usable in moments. 22 memories. *
- #
- *
- 46
- PAM (Algebraic) with 33 brackets at *
- 11 levels. Program and data storage on cassette program and data storage on cassette *
- tape using optional FA-2 remote control adaptor, £19.95. Compatible with the FX-501P and *
- FX-502P 9.6 x 71 x 141.2mm. 100g. *

ONLY £74.95

"... basically a revision of the MT-30 (one of my all time favourita electronic keyboards)," Electronics & Music Maker. Similar to the MT-40 but without the rhythm box, bass and auto functions. Dimensions: As MT-40. Weight: 2,0kg (4,4b) induding batteries.

(RRP £79)

ONLY £69

TEMPUS

Plus FREE MiCROL Professional Programming Pack (RRP (9.95) Or we will beat any lower advertised price by 5%



READ/WRITE

Dear Mr. Ron Harris Sir.

We seem to have been hearing quite a bit about System A recently; technically it looks a rather nice amplifier. However, it's difficult to tell how good commercially-produced units are with only limited information available about them. So what about the other end of the problem - what does System A sound like, compared with other amplifiers? Unfortunately, I can't see any of the hi-fi mags doing a review of it, so - how about you doing one (totally unbiased, of course) please, pretty please? Come on, put your reputation on the line!

Yours grovellingly, M.R. Barrett Hove.

Certainly not. Someone might chop it off!

System A has a comparable sound to any of the more highly regarded

commercial units. Listening tests we have conducted over the months since the creature's completion, have shown it (the power amps) to have a more detailed and open midrange/top than ANY we have compared it to. The top commercial boxes — Threshold, Monogram, Carver, etc can exhibit a better bass control than the System A however, but as to whether or not that is important for your particular application (ie loudspeaker), I could not say (because you haven't told me what speakers you've got, have you?).

Anyone contemplating building a System A is welcome to write to us for advice on speaker matching.

Dear Sir,

I read with interest the articles in the July and August editions of ETI describing the construction of the System A Audio Amplifier, as I have been on the lookout for a high-quality

class A amplifier design for some time. My particular interest in class A stems from the fact that I own a pair of Lowther loudspeakers - these units are almost ridiculously sensitive, requiring only some 10 W or so of input to produce the equivalent sound output of a conventional 100 W system. Given this sensitivity, most high quality class AB amps are only ticking over when driving a pair of Lowthers, and hence are working at the highest distortion end of their operating range. Hence the interest in class A, where no penalty is paid for operating the amplifier at low levels of power output, However, before going ahead and building the System A, I would like the answers to a couple of questions. Firstly, the July article heralds System A as "quite simply the best, designed to out-perform even commercial equipment." There is, however, no objective assessment or comparison to back up this claim, and before laying out the not insignificant construction cost. I would like to see the amplifier reviewed, preferably alongside its "competition" in the commercial amplifier field. Is this a possibility?

Secondly, the high power output of the System A seems more than a slight degree of overkill in the context of my



FEATURE

Lowthers. Is it reasonable, therefore, to construct a lower power version of the power amp section? If so, what modifications should be made to the present design? Yours sincerely, T. lettree. **Milton Keynes**

Taking the two points you raise, in order; first we feel it is inappropriate for us to review our own product against anyone else's. (Would you believe us anywayi) 'Objective' would not be an appropriate word to apply to such a test.

System A has aroused a great deal of interest and we know that a large number of sets have been completed. There is probably, however, a larger number of people still who would tackle the project, if only they could get to hear one first! Accordingly any owners of a System A who would be prepared to let a fellow ETI reader have a listen, can write to us and we'll run the letters herein. Secondly the high power output of the amp will not be wasted, even on your Lowthers, it will simply provide you with more headroom - and hence a cleaner sound with better bass output on transients.

Dear Mr Harris.

I am writing for advice on the purchase of an amplifier and speakers combination. I list my present system below

> Home-brew 10 W amp Ferguson (?) 3-way speakers (actually 2-way, 3-cone) Realistic 31-987 Craphic Equaliser Hitachi D-225 Cassette Deck Pioneer PL-300 turntable (the latest addition!)

The amplifier now ceases to be of any great use in terms of power. although quality is more than adequate (based on Bi-Pak ALJOA). I have considered NAD 3020, Pioneer SA-110, and also the "Audiophile" amp, the MOSFET amps from JW Rimmer, and the Linsley-Hood kit from Powertran The last three give me extra headroom. and I would like to feed them into AR18 speakers from Acoustic Research.

Basically, I would like your opinion on the Linsley Hood 75 De Lune/AR18 combination, plus any comments on the other "possibles"

Also, the Pioneer PL300 I have just bought is certainly the best turntable I

have heard at the price (£79.95), and I can't help wondering why it gets so little attention. Perhaps you can fill me in?

Thank you for your valuable time. D. Crary. Ilford, Essex

PS When is Felicity Kendall to return to our screens?

The AR18 is a fine unit and if you like the sound of them, go ahead and buy yourself a pair. You haven't named your cartridge so I've no idea if It matches.

Ditch the equaliser, with decent speakers and amp, you won't need it!

As to amplifiers, from the units you mention the Linsley Hood power amps are the best bet, but the preamp of that unit is getting a bit long in the tooth now, although the sound quality is still very good by any standards. Have a listen to the Crimson CK1010/1100 setup before you decide, however, as it is in your price range and offers a highquality alternative.

The Ploneer PL300 I have not been able to listen to at any length and must thus refrain from commenting upon!



TECHNOMATIC

"TECHNOMATIC" compliments "ETI" on its 10th anniversary and takes this opportunity to announce some facts about "TECHNOMATIC". ETI readers and our customers, have seen, over a number of years, our advertisements containing product listings etc., but no details on our policies or capabilities. We now rectify this situation for sake of completeness.

Our aim is to supply prime grade components which are fully guaranteed and backed by manufacturer/distributor. We stress the fact that we are totally quality and value conscious and handle components from major manufacturers.

Our volume buying enables us to obtain preferential prices and the savings are passed onto the customers in the form of low prices — sometimes lower than trade!

As a matter of routine, we provide "by return of post" service, and all orders received by 3.30 pm are despached on the same day. Our in depth stock holdings enable us to do this. Why not test us on your next order?

And some more facts:

LONDON'S No 1

We stock the widest range of micro processors in LONDON

We are fully authorised distributors to the hobbyist market for TEXAS INSTRUMENTS, World's No 1 semi conductor manufacturer.

We are a major distributor of ACORN COMPUTERS who manufacture ATOM, ECONET and BBC microcomputers. Other dealerships include VERO, OK Machine Tool, GSC, ILP, and AP PRODUCTS.

We carry large stocks of MICROS, MEMORIES, TTLs, CMOS, LINEARS, OPTO-Devices, TRANSISTORS and other semi-conductors. We can normally offer ex-stock deliveries to volume buyers at special prices.

Our connector range includes: TI Sockets, IDC connectors, Euro connectors, Min-D connectors, Juniper Leads and a variety of Edge connectors.

We also carry in stock EPROM programming equipment including Softys, ganged programmers, erasers etc.

GET THE BEST VALUE FOR YOUR MONEY

TECHNOMATIC LIMITED

15/17 BURNLEY ROAD LONDON NW10 1ED Tel 01-452 1500/450 6597 Telex 922800 305 EDGEWARE ROAD LONDON W2 Tel 01-723 0233

LONDON'S No 1 RETAIL COMPONENT OUTLET

PROIECT

INSTRUMENT PROBE

This probe will allow you to make CRO or frequency meter/timer measurements on high impedance circuits with waveforms having rise times as fast as three or four nanoseconds. Cost is well below commercial equivalents. Design by Jonathan Scott.

ost readers would be aware that, when taking a measurement on electronic circuitry, the input impedance of the measuring instrument must be much greater than the impedance of the circuit to which it is attached, otherwise the accurary of the measurement suffers. The input impedance of the majority of oscilloscopes is generally 1M0 with a parallel capacitance of between 20pF and 40pF. For a wide variety of applications this is perfectly adequate and will suffice for measurements of frequencies up to 5 MHz or so. The input impedance of the CRO falls with increasing frequency owing to the falling reactance of the input capacitance. For example, a capacitance of 30pF — which may be made up of direct input capacitance plus cable capacitance - has a reactance of only 500 ohms at 10 MHz The input capacitance also affects the rise time of the input - that is, the speed at which a 'step' input will rise from the 10% amplitude value to the 90% amplitude value.

The input impedance of an oscilloscope can be effectively raised, and the capacitance decreased, by using a 'stepdown' probe. For example, a 'x10' probe will generally have an input impedance of 10M and a parallel capacitance of between 5pF and 15pF. While this improves the input impedance there are two trade-offs Firstly, unless elaborate (and expensive) compensation is employed, the rise time is degraded, and secondly, maximum sensitivity is decreased by a factor of 10. As Murphy's law would have it, your CRO will run out of grunt just when you need it most.

Taking the situation with digital counter/timers, we find similar problems. Those that operate beyond 30 MHz or 50 MHz generally employ a prescaler with an input impedance of 50 ohms - which is perfectly all right if you're working on low impedance circuits and/or with high signal levels. But there are those occasions when you need a high impedance input and a fast (high frequency) rise time. As with the CRO, this is where your



It's times like these you need this project; a x 1 active instrument probe using a special buffer IC with an input impedance of typically 100,000 megohms! - that's 10¹¹ ohms - a very low input capacitance of around four to five picofarads, a fast rise time (around three nanoseconds) and a bandwidth of 100 MHz. Output impedance is around 50 ohms and the device is capable of driving capacitive loads up to several thousand picofarads. Thus it is eminently suited for use with high speed, wide bandwidth oscilloscopes and digital frequency meter/timers at frequencies up to 100 MHz. Output impedance is close to 50 ohms and it is thus suited to drive both high impedance instrument inputs and low impedance inputs (which are generally 50 ohms).

Design

It's all done inside a special IC an LH0033CG from National Semiconductors. This is described as a 'fast buffer amplifier'. (It has a companion designated LH0063, described as a 'damn fast buffer amplifier!). The LH0033 is a directcoupled FET-input voltage follower/buffer (gain \approx 1) designed to provide high current drive at frequencies from DC to over 100 MHz. It will provide ±10 mA into 1k0 loads (±100 mA peak) at slew rates up to 1500 V/uS, and the chip exhibits excellent phase linearity up to 20 MHz No offset voltage adjustment is required as the unit is constructed using specially selected FETs and is laser-trimmed during construction. Input is directly to the gate of a



junction FET, operated as a source follower, driving a complementary output pair of bipolar transistors.

Regulated plus and minus supplies of 15 V each provide power to the IC. Low-power three-terminal regulators are used to keep the unit compact. An external unregulated supply of between 18 and 22 V at around 50 mA is required to power the probe.

The supply pins on the IC need to be well bypassed over a wide frequency range so that the IC can maintain its characteristics, and the construction has been specially arranged to achieve this. Axial lead solid tantalum capacitors are used to bypass the IC's supply pins at the lower frequencies, while low inductance ceramic capacitors are employed as bypasses for the higher frequencies. A double-sided fibreglass PCB is used to preserve the high frequency response and the high input impedance, and the layout is arranged to permit direct connection to the probe tip and provide low input capacitance.

However, the presence of the PCB substrate will degrade the input impedance, surprisingly enough, and you can drill out the area of board immediately beneath pin 5 of the IC and solder the pin directly to the probe tip. For those who wish to go 'all the way' (as Frank Sinatra sings), the plastic insulation of the probe tip can be replaced with a similar piece of Teflon — if you can afford it and have access to a lathe.

The maximum input voltage permissible, when driving a high impedance load, is plus or minus 15 V. When driving a 50 ohm load, maximum input voltage permissible is only plus or minus 10 V (limited by maximum output current). No input protection has been included. However, if you are only working with circuits where voltages are no greater than about 1 V peak-to-peak, protection can be added by putting two diodes back-to-back in parallel with the input, along with a 10M resistor. The maximum input voltage figures include any DC voltages present, plus the superimposed signal voltage

At this stage it is only fair to tell you that the LH0033CG is an expensive device (by comparison). But compare the total cost of this probe to a similar commercially-made type and you won't catch your breath a second time!

Construction

The project is constructed on a small double-sided fibreglass PCB with

BYPASSING

Supply lead bypassing is important in order that the LH0033 can operate correctly over the full bandwidth from DC to 100 MHz. To ensure this, the bypassing has been specially arranged and the techniques employed are probably unfamiliar to many readers.

The output circuit signal return path for the IC is via the ground and the two supply rails. Any significant impedance in series with this path (or paths) will subtract signal from the output load. Thus, the supply rail bypassing has to present an impedance which is a fraction (like one-tenth or better) that of the minimum output load impedance. Here, the minimum output load is about 100 ohms (R1 + 50 ohms instrument input impedance) and the supply bypassing impedance should ideally be less than 10 ohms across the frequency range.

The bypassing on each supply rail to the tC leads here takes advantage of the characteristics of three separate components to cover three sections of the frequency range.

From DC to around 100 kHz, each three-terminal regulator (IC2, IC3) has an output impedance well below one ohm, rising to four or five ohms at 1 MHz, as shown in Fig. 1. The two tantalum capacitors, C1 and C3, then take over.

Solid tantalum capacitors have a characteristic impedance that falls with frequency according to its value, which then 'flattens out' in the region around 500 kHz — 1 MHz, rising to a few ohms around 10 MHz, as can be seen in Fig. 2. Thus, C1 and C3 serve as effective bypasses across the range from around 100 kHz to around 10 MHz. Axial lead tantalum capacitors were chosen as their construction exhibits the slowest impedance rise following the minimum impedance value.

To provide bypassing over the decade from 10 MHz to 100 MHz, capacitors C2 and C4 have been specially chosen and positioned on the PCB. For the prototype, 'chip' ceramic capacitors were used. These tiny, 'naked' chips of ceramic with a capacitor embedded in them are probably the most effective bypass capacitors made. The leads and physical construction of all capacitors form an inductance which is



effectively in series with the capacitance of the component. The combined effect forms a series resonant circuit, the frequency of which (that is, the self-resonant frequency of the component) is mainly dependent on the length of the connecting leads, the particular construction of the capacitor and the way in which it is mounted. Ceramic chip capacitors, being a tiny block with connecting pads or surfaces on each end, have extremely low values of series inductance and thus very high self-resonant frequencies - see Fig. 4. Now, any value of chip capacitor between 1n0 and 10n can be used for C2 and C4. The self-resonant frequency of a 1n0 chip capacitor is somewhat above 100 MHz (as per Fig. 4), but that of a 10n chip is between 40 MHz and 50 MHz. Now, this isn't a problem, for the chip's impedance falls with frequency as usual until near the self-resonant frequency where it falls rapidly, reaching a minimum at the self-resonant frequency. Above that frequency its impedance rises again, but is still low enough for effective bypassing.

Ordinary ceramic disc and plate capacitors behave in much the same way. The self-resonant frequency of a typical 5 mm diameter disc or 5 mm square plate capacitor depends on the lead length, as shown in Fig. 5. Thus, you could use 470pF or 1000pF (1n0) capacitors of this type for C2 and C4, provided you installed them on the underside of the board with absolute minimum lead length.



Fig. 3 Ceramic chip capacitors shown about actual size.



components mounted on both sides of the board. Commence by soldering in place the components that go on the top side of the board, leaving IC1 until last. Note that the positive leads of both C3 and C8 are soldered to the groundplane areas on both the top and the bottom sides of the board. Take care with the orientation of the tantalum capacitor, as well as IC2 and IC3. Having done that, solder C2, C4, C5 and C6 to the bottom side of the board. Now you can install IC1. You will have to juggle the legs a little. Push the can as far down on the board as you're able; its base should sit no more than 3 mm from the board.

Now that you have everything in place, check it all. It seems pretty simple, but Murphy's law will ensure that the simplest things have the highest stuff-up rates!

All's well? — now you attach the output coax cable to the underside of the board, plus the DC input and ground (0 V) wires. But — before you do, slip the output end piece of the probe case over the cable and supply wires, push it down about 150 mm or so and then slip the case of the probe case down the wires. This saves slipping them over the other end of the whole business and sliding them all the way to the probe.

The probe tip can be attached and soldered in place last of all. Now you can screw it all together and attach the appropriate plugs to the other end of the cable and supply wires.

With the construction completed, you can power up and try it out. Note that the transformer suggested in our power supply is but one of many suitable types. Any transformer that will deliver at least 26 V AC at a load of about 50 mA will suffice. Alternatively, any dual polarity DC supply having an output between 18 and 22 V at 250 mA will power the probe.

Note

Always take care that you don't exceed the input voltage limitation; LH0033s are expensive.

BUYLINES

Ceramic chip capacitors and solid tantalum axial capacitors are a trifle unusual; however, they are stocked by C.T. Electronics (Action) Ltd, 267 & 270 Acton Lane, London W4 5DG. (They also stock the BNC plug should you have any problems there). We will be selling the double-sided board through out PCB Service — the order form is on page 44.

Resistors (all	1/4 W, 596)	Semiconductors		
R1	47R	IC1	LH0033CG	
R2, R3	68R	IC2	78L15A	
		IC3	79L15A	
		D1-D4	"IN4001,2,etc. (if required)	
Capacitors				
C1, C3	3u3 16 V solid tantalum axial-leads	Miscellaneous PCB (double-sided fibreglass); RG58U coax		
C2, 4, 5, 6	10n ceramic block	cable and BNC plug; T1 - (if required)		
C7, C8	10u 25 V tantalum	240 V to 30 V transformer or similar; op-		
C9, C10	470u 35 V electrolytic	tional 10M/1/2 W 5% resistor and 2 x 1N914		
	(if required)	dlodes; wire; probe housing.		

ADTO HIS



Fig. 2 Component overlays for the top of the board (top) and the bottom of the board (bottom!). SOLDER BRAID

HOW IT WORKS.

This instrument probe employs a wideband hybrid voltage follower/buffer IC, the LH0033, with very close to unity gain, that features a very high input impedance and a low output impedance. It requires regulated, well-bypassed supply rails. Two three-terminal low power regulators provide plus-and-minus 15 V supplies from an unregulated input.

The internal circuit of the LH0033 is shown below. Basically, it consists of a FET Input stage (Q1), operated as a source follower. The other FET, Q4, provides a constant current source for the source blas of Q1, while Q2 and Q3 are connected as diodes and provide blas for the bases of Q5 and Q6. Resistors R1 and R2 are laser trimmed in manufacture so that the IC meets the offset voltage specification. As Q1 has a constant current source load, the input impedance at the gate of Q1 is very low. The output of the source follower drives a complementary pair output stage, Q5-Q6. Thus the IC, will have a very high input Impedance, a very low output im-pedance and a gain very close to unity. With appropriate construction employed for the internal devices, the bandwidth over which the device will operate can be made very wide indeed. The - 3dB point for the LH0033 is 100 MHz.

As the device is direct-coupled, DC levels will be maintained between input and output.

Bypassing requirements for the IC's supply leads are explained elsewhere in the article.

To provide regulated plus-and-minus 15 V rails for the IC, two three-terminal regulators are employed, a 78L15A for the positive rail and a 79L15A for the negative rail. These can supply up to 100 mA and have a very low output impedance up to several hundred kilohertz, which is exploited for low frequency bypassing. Each supply rail requires an unregulated input of between 18 V and 22 V. Decoupling of the supply leads provided by R2/C7 on the positive rail and R3/C8 on the negative rail. The input terminal of each regulator is bypassed to prevent instability.

As the input voltage is limited to a maximum equal to the supply rails (high impedance load), input protection may be added in applications where only low level signals are being examined. As shown in the main circuit, this protection consists of two 1N914 diodes connected back-to-back in parallel with a 10 M resistor across the input. Signals above 1 V peak-to-peak will be clipped, preventing any damage to the IC. If very fast rise time signals are to be examined then better protection for the IC can be obtained by using hot-carrier diodes such as the HP 5082-2800 instead of the 1N914s.

ETI

59



ETI APRIL 1982

60

BIRTHDAY COMPETITION

WIN A ECT

Hands up all those who had trouble starting their cars during the recent appalling weather. Don't you wish your car was fitted with an electronic ignition to make the most of your battery, as well as increasing the life of your contact breaker and giving you more miles to the gallon into the bargain?

The prize in this competition is a Total Energy Discharge ignition unit designed by Electronize Design, a company with a great deal of experience in the field. The unit is supplied as a kit of parts and is easy to assemble.

To win this kit you have to answer these two questions:-

(1) The standard ignition circuit, using a coil and contact breaker, has been fitted to virtually all mass produced cars for 60 years. Who designed it? (We'll accept surname only).

(2) In a four-cylinder engine, firing the cylinders in the order 1-2-3-4 would lead to excessive engine vibration. Give one

firing sequence commonly used to overcome this problem.

Write your name, address and answers on the form on page 133 (there's no need to cut up this page) and send it to us by April 30th, 1982. (All right, you can put your hands down now!)

RULES

- Closing date is April 30th 1982, and all entries path marked later than fills date will be decounted.
 The company provided in the magazine must be used. Photocopies are NOT acceptable.
 Employees of ASP and their relatives are nut eligible for music.

- entry. The judger' declaims is to be considered final and an correspondence will be entered late concerning the competition. 4



ELECTRONICS NOW! The PRACTICAL way!

This new style course will enable anyons to have a real understanding of electronics by a modern, practical and viaual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a selfemployed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is evailable to whom you can write personally at any time, for advice or help during your work. A Cartificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-FI and microprocessor/computer equipment.

and DOING

SIDIDIING

New Job? New Career? New Hobby? Get into Electronics Now!

Total I	Please send your brochure without any obligation to	I am interested in. ETIM IDE
N. H. R. R.		COURSE IN ELECTRONICS
COLOUA BROCHURE	NAME	RADIO AMATEUR LICENCE
	ADDRESS	MICROPROCESSORS
		LOGIC COURSE
		OTHER SUBJECTS
Restance Brand	BI OCK CAPS PI FASE	
POST NOW TO:	nal Dadia & Floatnenias Cahaal	Pooding Popla DC1100
DUITER I MAUTO	nal Randor Electronics School	Reading, Derks. Non Tor.



IF YOU'VE READ THE LAST TEN YEARS OF ETI WIN THE NEXT **10 FREE!**

In 1979 who reviewed Star Chess for ETI?

- Who first wrote the series "Electronics Tomorrow"?
- 10. The 100 W Guitar Amplifier (the first one!) appeared when?
- 11. Microfile is the title of ETI's regular computing hardware section. In which issue did it first appear?
- 12 In what year did we publish a synthesiser, an LED multimeter and an FM tuner in successive months?
- 13 What was "The Beast"?...
- 14. How many parts of the popular "Electronics It's Easy" series were published in ETI?.
- 15. How many editors has ETI had in the past years?
- 16. In October 1976, who was ETI's Assistant Editor?
- 17. Who designed the Transcendent DPX?
- 18. Which issue began "Project 80"? ____
- 19. The 4600 synthesiser is one of our all-time most popular projects. In which issue did the series begin? _
- 20. DIY Polyphonic keyboards came to ETI when?
 - RULES

 - Clining date is April 30th 1902, and all retries path marked later than this date will be discounted. The compan previded in the magazine must be used. Photocoepies are NOT acceptable. Employees of ASP and their relatives are not eligible for
 - The judges' doctation is to be coundered final and re will be entered take concurring the

This is a special competition for our regular readers. We're offering a ten year subscription to ETI as a 'thank you' prize for supporting us this far. All the questions refer to back copies of our magazine and will be easy if you've kept the issues! (Surveys tell us that over 90% of readers keep ETI for longer than a yearf) Index issues will be particularly useful, but will not give you all the answers. Fill in the coupon on page 133 - you don't need to ruin this issue - and don't forget your name and address! In the event that no one gets all the answers correct, the highest number of right answers will win. In the event of a tie, it will be the earliest postmark that takes the ten year subscription.

Read the questions carefully before answering.

- 1. Which issue was designated a "4 Channel Sound Special Issue"?
- 2. Who edited the May 1973 issue of ETI?
- 3. What month did the first issue of ETI appear in Britain?
- 4. What makes March 1979 good theatre?
- 5. ETI published the first-ever TV games project. In which issue? .
- 6. Which IC is featured in the July 1976 "Data Sheet"?
- 7. The amplifier on the cover of the February 1982 issue has also appeared on a previous cover of ETI. Which one?

10 YEARS ON

-----O +5V

1 89

IC19a

19 22 23

410 A9 A8 A7 A6.

07 06

11

.

11

11

11

11

6

AO

R/V

CS

13

12

12

7 16 15

24

18

ISSN 0142-7229

1972 - 1982

RA

140

+5V 0-111

LKRAM

6

10

11

10

11

3

21

m

13

14

3

2

13

14

3

2

17

13

14

6

5

min

G2

30-5

m

+5V O

ME MANAL

The last ten years have been the most dramatic in the history of electronics. Tracing back, you can chart the explosive growth of the "consumer electronics product" from the first — highly expensive — calculators, through digital watches and the like — to the fully-equipped home computer.

When compiling this issue – ETI's 10th Birthday, as I'm sure you've noticed by now – it occurred to us that we had the entire course of electronics charted out for us – within the news pages of ETII News Digest has always figured very highly in our readers surveys and companies mentioned therein have often commented upon the interest the feature generates.

Accordingly we went back and read every single news page from April 1972 through to April 1982. (Yes, it did take a long time). Lo and behold! History unfolded!

It was all there — the first calculators, the first watches, the beginnings of LCD, the first MPU chips, cheap memory, the Space Shuttle tests, bubble storage announced — and failed, CB radio underway, FETs on the hobbyist market, CMOS finally becoming cheaper than TTL — and the lunacies! We found quite a few of those, in fact. Witness the Queen's speech that wasn't and the TV game with ball-bearing scoreboard.

You will find them all in the following pages, the successes, the failures, the achievements...and the gaffs. We have gone through the mountain of material available and put together what we think is a truly historic collection. (Sounds good that doesn't it — should be in the British Museum.)

Reading through you will be presented with the fascinating and surprising history of electronics, 1972-1982. Check the dates each item appeared. Some of them will astound you. When was the first TV game on sale? The first LED watch? When could you buy a home computer in the UK? As to the ladies who crop up all the way through, we've no idea how they got there — they've nothing to do with us and they are most certainly not included just because we thought you would enjoy seeing them again. Enjoyment has got nothing to do with it.

It is an interesting conjecture as to what we will be able to include in our 21st Birthday Issue. Any guesses?

13

12

5 CLR

R14

110

IC10c

15

IC18

OF ADL TO LC CK

10

0+5V

(04)

0 11



TV GAMES COME OF AGE

It is just over two years since the first TV games started to appear in pubs since then a lot has happened in this field with a large number of small companies marketing various units by a variety of methods. Although the TV games have received a considerable

amount of publicity they have not yet caught on in a big way.

"No one who has ever played TV games has ever said anything derogatory about the concept", Richard Fairhurst of Videomaster Ltd., told ETI, ' they may not like the price or the packaging but they always like the idea".

ETI NEWS NOV 1975



Doctor Who

One of our readers, Mr. S. Knowles of Hampshire, sent us scope picture he took whilst

designing with a Textronix 7403 on \$00 nS/div with x10 expand. It seems he was looking for a pulse, but he may well have dis-covered the secret of time travel?



Pet Chip

This should appeal to those of you who spent your hard. earned pennies on a 'pet rock.'

We recently received a letter from an anonymous dad who made an apparently trivial Christmas presi for his daughter. However, since then he has been inundated with Conversion 1

ETT NEWS MARCH 1980

Mr A. Nonymous painted a face on one end of an IC (pet IC. you see) and made a matchstick cage for it complete with watch battery feeding bowl.

The chip should quickly LATCH on to its new OHM. As for feeding, a few BITS of CURRENTS a day should be AMPle Just let it NOR away to Its heart's content. You can teach it tricks.

Ta. Mr Nonymous, We haven't had a good groan in

bbc get it taped

The BBC and 3M have collaborated to develop a new tape recording system claimed to provide 90 dB noise figure. The system will accommodate 32 tracks on one-inch tape at an undisclosed tape speed.

ETI NEWS JULY 1973

PIEZOELECTRIC HEADPHONES

The Pioneer SE-700 are the first high fidelity headphones to use the piezoelectric effect. As the audio signals reach the headphones, the driver elements of ultra-thin aluminiumcoated high-polymer film expand and contract accordingly, creating "breathing" motion. Tonal characteristics are comparable to those of the electrostatic type headphones, but the SE-700 require no matching transformer.

ETI NEWS MAY 1975

its a wide word

Intel. Zilog and Motorols are taking their places in the front rank on the grid for this years expected race to 16 bit MPU siles. All three have comprohably show the nature of

their teeth at next months US Solid State Circuits Conference. The pause between this and letting loose of the hounds as it were will almost certainly mean late autumn production.

SHORTS

Every Ready — now called Berec have released four rechargable msumer batteries, in the HP2 HP11, HP7 and PP3 varieties. Chargers are also available. An unphenuminal loss of dry I power these days.

Officert drive turntables ves But direct drive hIPUS? Also yes - now. The \$2000 is a new release from AMI which can drive flouorescent displays directly, with HT drive and 7-segment decoding on Also on board 61 x 4 RAM and IK ROM Intended for low last apple-

🌒 Ingersail — the tick tock people - are into electronics. They have released three TV games. three clock radius two Door Chimes, and a port-able micro cassette player, Photo shows one of their w IV games It must be Christmas

ETI NEWS JAN 1979

· Fairchild are making a big fuss about having their FISK Dynamic 16K RAMs available at last Access times vary from 150 ns to 300 ms.



On yer nurks ETI NEWS MARCH 1978

TALKING IN TRAINS



British Rail's plans for 150 mph trains include improved communication systems between drivers and guards. Also planned are passenger address systems.

A range of equipment – known as EMTEL – has been designed specifically for this task by Britain's Nelson Tansley Ltd.

The main problem to be overcome was the impossibility of providing a special cable, running the length of the train, on which to carry the signals. The equipment was therefore designed to accommodate any continuous circuit, for example, the control wires for the lighting relays which (in British Rail), are the only conductors always connected throughout any passenger train. In this case, departure from the ideal of a 600 ohm noise-free line is caused by the connexion across the wires of many relay solenoids, the impedance of which is not only complex, but variable.

ETI NEWS JULY 1972

LASER MISSILE INTERCEPTOR

The US armed forces may soon have a laser missile interceptor. Air Force reports state that prototype deuterium fluoride lasers have been successfully tested at "very very high" power outputs.

Power output is apparently so high that the laser beam burns straight through heavy gauge stainless nickel steel plate.

ETI NEWS JULY 1975

BIAS - AUTOSELECTION

Cassette tape recorders that have been designed specifically for use with chromium dioxide tapes require special bias switching facilities.

At present this is done manually. However the latest BASF "SM" chromium dioxide cassettes have a notch on the rear of the cassette (in addition to the tab now used to prevent erasure of recorded material) and, hope BASF – and Philips who are backing the system – future cassette players will have a switch mechanism actuated by this tab to bring in the necessary bias circuitry.

ETINEWS APRIL 1972



It had to happen. The integrated circuit is so old that it has earned its place in a museum, Doesn't it make you feel old? The world's first IC, invented by Jack Kilby of Teams instruments in 1958, is one of three exhibits on loan from TI in Dallas for the 'Challenge of the Chip exhibition at the Science Museum, The other two are the first silicon transistor and the first single chip microcomputer.

7/16 in

ETI NEWS MAY 1980

GETTING READY FOR COMMERCIAL RADIO

Commercial radio is on its way; anyone doubting this should tune around the medium wave band where tests transmissions are already being conducted. Contracts for the supply of the transmitters and the aerials have been placed with EMI, the value of the order is put at £160,000. ET! NEWS MAY 1973

LIGHTING THE WAY

Many local authorities are now using a street lighting control system in which a photoelectric cell measures the light level and varies the input to a thick film heating element controlling a temperature sensitive switch. The street lights are therefore automatically switched on at dusk and off at dawn, which means that light is provided only when it is needed and ensures that electricity is not wasted.

shorts

Tandy is doing well with its home computer in the USA, and is expanding, both physically and financially, that side of the

• New from GI - the Cricket chip. The AY-3-8910 is a programmable sound generator and is controlled. software needing only a power sup ply and clock to begin chirping or hooting or

3-15mA.

Hong Kong King

Some numbers to tick off on your fingers. In the first six months of the year Hong Kong exported 16 million watches (worth [77m]. These break down as 61% mechanical, 29% LCD and only 10% LED and quartz analogue com-

ETI NEWS OCT 1978

bined Surprising LED figures eh?

Germany developed a sudden lust for these nontockers and their imports leapt up by 287%, putting them as the second largest consumers - behind the US and ahead of us! ETINEWS NOV 1978

forget who not?

You know we've quite forgotten why we used this photo at all. Now let's see something to do with TV games? Anyway the editorial desks have been bereft of nice lady photos lately - so this one app eared as an oasis amid the

dusty filing trays. P.S. Binatone the people who make the box in front - don't ask what box or in front of what or we won't

speak to you again -

claim to now taken over half the TV game market - the magic 51% in fact,

ETI NEWS NOV 1978

Pocket Companion

Not just an electronic dictionary or a translator of an appointments dury of an en clopedia, but something of all these rolled into one, the Brainbank' is hailed as the world's first packet information and language centre laboratory.

Brainbank is programmed via a series of interchangeable. plug in memory cells, so you have virtually unhmited information storage possibilities (armed with a bucket full of memory cells).

Each language cell, which contains 32K of ROM holds about 1200 of the most common

words, stored individually and in groups of up to fifty in categomes such as travelling and hud The program also includes short phrases, automatically currects spelling errors and explains words with double neurings (with its double en-

The information centre's heart is a Mostek 3670 microprocessor Memory cells are currently available on diet and nutrition, first aid, taxation and a thesaurus. New cells will be come available every month A custom cell service is also

Brainbank will cost around (150 plus £20 or less for each additional cell. We will tell you more about this little marvel. when we can get hold of one to play with,



ETINEWS JULY 1976

Its applications are wide, being ideally suited as a fault indicator mounted onto portable equipment and Instrument panels, or for localised warning of such things as intruders and/or fire

BE WARNED (IN A SMALL WAY!) The Mini-Bleeptone 525 is a unit

ous signals of up to 80dBa with current consumption ranging from

which provides a choice of two contin-

NEW LC DISPLAYS FOR WATCHES

A new series of Liquid Crystal displays have been announced by Beckman for digital watches. These display hours and minutes continually with either date or seconds, selected by a push-button. Contrast ratio is



20:1. power requirement is 1 microwatt so that even with constant readout battery life is over a year. LC modules are available for both 3V and 6V models and a CMOS compatible. Beckman Instruments Ltd., Queensway, Glenrothes, Fife, Scotland. ETINEWS OCT 1978

ETINEWS JAN 1980

Computerised control and data recording equipment that can handle information from up to 413 different sources will be used in the development of Britain's tracked hovertrain during its period of full-scale development.

From this console, commands will be transmitted by radio to the hovertrain and radioed signals from the measuring instruments inside the vehicle will be received, recorded and analysed.

The 25-ton vehicle straddles the track and is supported approximately an inchabove it by a system of fans employing the hovercraft principle. The linear motor consists of an aluminium strip set into the top of the track as the motor's "stator", and a complex set of electrical windings mounted inside the body shell, Power is picked up from a trackside rail,

The train made its first run over a mile of the track recently, watched by visiting experts and the press from several countries. It performed perfectly during the slow speed run and is now expected to reach speeds of up to 90 moh during the next two months.

The hovertrain has been designed and constructed by Tracked Hovercraft

300 MPH HOVERTRAIN - PUBLIC SHOWING



ETI NEWS APRIL 1972 (OUR FIRST EVER NEWS ITEM!)

Ltd., a company set up by Britain's National Research Development Council, and would be capable of providing a link between central

RED TAPE GAGS THE QUEEN!

ing.

wee small hours of January In the 19th 1903, Marconi established the first two-way communication across the Atlantic. Messages were en-changed between the American president Theodore Roosevelt and the British King Edward VIL To mark the 75th anniversary of this event, the Cornish Radio Amateur Club have organised a team of sixty local amateurs to run GB3 MSA (Marconi's Seventy-fifth Anniversary). The station was run 24 hours a day, from the

Something **Bugging You?**



14th to the 22nd January, from the lounge of the Poldhu Hotel in sunny Cornwall - only metres away from the spot Marcom used.

Transmitting on 80m, 20m and 2m the team had already made 1 100 contacts in \$1 countries when ETI contacted them on the 16th! All the equipment was owned by the club and its members and set up for the week specially. On the American side was another station, KMI CC, based in Cape Cod. KMI CC was run by

With the increase in telephone

developed a simple to use, yet sophisticated successor to their

Scanlock radio surveillance receiver.

It is called the Scanlock Mark VB and

is a last, easy means of detecting and

locating an eavesdropping transmit ter as well as being capable of

routine 'sweep' searches of high level meetings rooms. Carried in a vehicle

it can also locate any bleeper bug us ed for 'trailing'. The Scanlock is not limited to the conventional radio receiver's

range of 88-108 MHz. It covers the

wider frequency spectrum of 10-1800 MHz and its automatic

weep' mode scars this range four times a minute. Finally all that is

necessary is to press the "Locate' but-

ion and use the hand-held wand to

puide you to where the bug is

ocated. The kit is the size of a small

briefcase, weighing 6.3 kg, complete

with spare battery pack. There is also

provision for mains usage. For fur-ther information contact Audiotel

International Ltd at Saddlers Court,

Vately, Surrey, GU177EX.

tapping and boardroom bugg

Audiotel International have

London and the airport planned for Foulness, its passengers completing the journey in gulet pollution-free comfort in about 20 minutes

the local tiarnstaple, Mass radio club with the help of the Radio Club of America

Now for the red tape ... President Carter sent a message via KM1 CC and the Queen wanted to send a and the Queen wanted to send a reply via GB3 MSA, just like Edward VII did back in 1903. The Home Office said that if she did, it would break a condition in all British amateurs licences - namely the one about not passing on messages from 3rd parties' So after 2 years preparatton the Cornish Amateurs and the Queen were denied permission to reply to President Carter.

ETI NEWS MARCH 1978

CONCORDE BAN?

Whilst we are currently bombarded with PR material extelling the 'virtues' of the Concorde supersonic airliner it is interesting to note that in the USA Senator Alan Cranston has introduced a bill, co-sponsored by Senators Edward Muskie and Caliborne Pell, to prohibit overseas supersonic transports from landing at any US airports or flying over US territory at supersonic speeds.

The SSTs which carry less than half the passenger load of a 747 make ten times as much noise on take-off and landing. ETI NEWS JULY 1972

RICE LOGIC?

Later this summer - about June -National Semiconductor and Kellog's are to hook up on a promotional deal. All Kellog cereal packets will carry coupons for reductions on National calculators. Barley credible is it not? ETINEWS JULY 1976






hammer fet-ish

A new range of low cos **VMOS** power FETs in plastic have been introduced by Siliconix These devices are aimed at replacing conventional bipolar transistors in a great many applications. This development in VMOS technology has cut the price of such devices by a third enabling them to compete directly with hunder devices ETINEWS APRIL 1978



CALCULATOR CHIPS NOW LESS THAN FI

Calculator chips prices continue their inexorable fall in price. Latest prices in the USA for four function eight digit MOS chips are now as low as 40p

to 80p. Even the complex scientific calculator chips are down to £6 or less compared to £20 this time last **ve**ar

MOS Technology Corporation for instance are selling a single chip scientific unit for £7.

ETT NEWS JULY 1975

ETINEWS DEC 1977

sailing into space

A 12 bladed solar sail spacecraft is a new candidate for mankind's first interplanetary shuttle. Designed to be employed in the 1980s its first use might well be a rendezvous with Halley's Comet in 1986.

The "heliogyru' sail uses a helicopter type design with 12 'blades' composed of reflective aluminium plastic film, and deployed in two tiers of six each. After launch from the space shuttle, centrifugal force

would open the blades to their 4% MILE length. (They're 28ft. wide). The craft sits in the centre of the array

The craft would be slowly spun by the sun's photon radiation, and complete a rotation every three minutes. A square sail, and hence windjamming to the stars, was rejected in favour of the blades, which now fight it out with an ion stream prop ulsion system for NASA consideral

ANTI-SKID CONTROL

A Decade of Electronics

The first standard i.c.'s designed specifically for the automotive market have been announced by Fairchild. Both are complex linear circuits developed over the past two years as 'custom' circuits before being added to the standard product line.

ETLNEWS OCT 1973

ELECTRONIC CHEQUEBOOK CALCULATOR

A pocket calculator that will hold and display bank cheque account balances for a year or more is shortly to be announced by the US Mostek Corporation.

During the times that the calculator is 'off' data is stored in a static shift register (drawing a mere 100 microemps). This data is then clocked solely when access is required.

The unit is expected to retail for less than £16 and will be built into a plastic chequebook holder.

ETENEWS JULY 1975

BUBBLING OVER

Next year Rockwell are hoping to launch their now developed one--megabit bubble memory price? One millicent per bit!

Their device can operate up to 300kHz and measures 10 x 9.5mm and is designed for a 1.8 micron. bubble diameter, ETI NEWS SEPT 1977

ACC AFTER ONE YEAR

Now moving into its second year of existence the Amateur Computer Club has now formulised its activities into a constitution and has a membership of over 200. ETTNEWS AUG 1974

Power Cuts On The Way

I a 1968 your 20 inch colour telly uning 90° deflection would have consumed over 200 W. Now, the ligure is around 65 W. A new development from Finland will further reduce that to about 40 W.

The system, which results in a reduction of about 40% in power consumption, has been incor-porated in the Salora G Series of portable colour sets. The design is basically a 90% efficient couple between the power supply and picture tube using an induction transfer system. The resultant cool running improves reliability and extends operational life.

The G Series, with its 16, 20 and 22 inch models, will operate from a standard 60A/hour 12 V battery for 15 hours, or from mains for as long as you pay your bills.

All the models feature automatic electronic tuning, fine

tuning and memory plus add-on options for remoted control, 12 V battery and video frequency intertace unit.

Salora products are available in the UK from Salora (UK) Ltd. 25A Techno Trading Estate, Swin don SN2 6EZ.

Bowmar has Texas's range and in homing in Texas are being sued for \$3 million by Bowmar who allege the supply of a large number of defective cal-

number of detective car-culator keyboards. • XR4741 to you. No-thing to do with sci.ft but a new quad op.amp. Very low noise and better than 2416 all compares A wait a 741 in all respects. Avail-

able from RASTRA at 275 King St. Hammersmith. London WS. Ideal for audio projects where the hissing of summer curcuns

The Government's hi-fl firm. Strathem are to launch their new SM2000 turntable in the autumn. which will replace the SMA2 model. Once again the unit looks technically sound --- maybe success at last for nationalised-fi? ETI NEWS OCT 1978

ETTNEWS SEPT 1980



Extremely pure silica glass has been manufactured for at least 40 years longer than jet aircraft have been around. Now it is to aid and abet the



ultimate aircraft - the U.S. Space Shuttle. Made into tiles (composed of 96% silica glass) of which 34,000 are used, the material covers well over 70% of the surface of the Shuttle.

These tiles are incredible heat 'shedding' devices (see photo) and will be expected to withstand temperatures of up to 1260°C for 100 re-entries into the atmosphere. Previous heat shields were destroyed on re-entry.

Each tile is precisely milled to fit exactly against the curvature of the Shuttle body, thus making the composite craft as light as possible, and as aerodynamic as is feasible. This does however mean that no two of those 34,000 tiles are alike! Imagine the little man in a white coat with the job of fitting them to the aircraft - a huge 3-D jigsaw puzzle with only one solution out of 34,000 (i.e. 34,000 x 33,999 x 33,998...x 1) possibilities! Rather him than me.

ETI NEWS MARCH 1977

ORACLE ON AIR

ORACLE, JTV's Teletext system (see ETI, July 1975) began an on-eir experiment on the ITV network on 30th June. Operating the experiment are two editorial teams and three computer systems. At ITN there is an editorial team (plus computer) for news and associated information. At London Weekend Television there will be an aditorial team preparing public service and similar information pages, and the second computer. At Thames Television the third computer will be used to insert data into the network during the Monday to Friday broadcasting period with LWT taking over for the weekend transmissions. It is hoped that there will soon be sets with decoders in the main entrace lobbies of ITN House, London Weekend Television's South Bank Studios and Thames Television's Euston Studios. so that visitors can interrogate the system and see how ORACLE works.

ETI NEWS SEPT 1975

WATCHES FACE COLLAPSE!

Five companies have dropped production of digital watches, due entirely to the price war raging around the product. Gruen, Benrus, Armin Litronix and Gillette have decided the wrist borne digit is not for them. Those still there are sufferin too. Bulova are expected to make a loss this year. Gillette in fact pulled out before they pulled in, scraping well laid plans to burst into the 'marketplace' at the eleventh hour.

ETI NEWS SEPT 1977

EIS DOLBY RADIOS SOON?

Even the cheapest of domestic radio receivers may soon have Dolby circuitry inbuilt according to Alan Gregory of the Signetics Corporation, manufacturers of the NE545 Dolby IC

chip. Gregory believes that the inclusion of the chip (which will be sold to manufacturers for less than a dollar will increase the price of domestic receivers by a pound at the most. ETI NEWS APRIL 1975

SCREEN TEST

ETI NEWS JAN 1979

The UK is now Hung Kong-Sargest market for TV games. We absorbed 20% of their export in the field, some 523 300 items if you please, in the first eight monities of this year Germany, finished second on 27's and the USA came third with 13's Somewhat of a surprise

and a shame, that we take more than the States of these items. I always thought she had more taste



If the latest gouder from Texas Instruments is as successful as we think it will be, the next generation will speak with an American accent? Called "Speak & Spill" it is a box that talks to the kids (with a "standard" American accent). and theoretically helps them pronounce new words correctly – it also compares how the kids spell the word with the correct (American) spelling, and indicates whether they gave the right answer

ETI NEWS AUG 1978

A Decade of Electronics

A POCKET CALCULATOR IN EVERY HOUSEHOLD

"By the mid-70's the pocket electronic calculator will be as much an essential part of the household as the transistor radio is now". This is the prediction made by Sinclair Radionics.

Recent market research confirms that increasing numbers of the population are becoming aware of the possible applications of pocket electronic calculators. This is most marked in the educational field, at school and college levels although considerable interest is also being shown on the domestic front by husbands and wives who are able to use a calculator to help control the family budget.

ETINEWS DEC 1973

THE END OF THE AMP?

A British invention (three cheers!) could well mark the end of the amplifier as a circuit block. A new device called a 'voltage-to-current transactor' can do everything an op-amp can - but better. Invented by Professor Gosling and Carl Brinker, the device contains no passive components at all, and consists of a network of transistors.

The advantages are that it integrates smoothly rather than as a series of steps, follows an input quicker and with a wider dynamic range, is smaller in chip form and uses less external components. A VCT can also double as a transformer!

ETINEWS OCT 1976

FIELD EFFECT LC DISPLAYS

Siemens incorporate the field effect

displays with low operating voltages.

10:58

All the liquid crystal displays in

held effect technology have dark symbols on a light background and are suitable for reflection operation, all with high contrast ratios, low

principle in their new liquid crystal

Blonde

Bombshell

Now be honest with yourself aren't there times during those long cold winter days when you could do with one of these in your office. No, unfortun-atery I don't mean Blondie in the white pants. The blonde bombshells here are the brushed aluminium boxes of ITT Terryphone's new solid state intercom units

The intercom, which doubles as a security and alarm system. condists of a master unit and from one to nine sub-units. The system is easily installed in many configuration

Simple press-button-to-talk operation is featured on the master and sub-units. Each sub-unit can be called independently from the master unit, or all sub-units can be called simultaneously. Pressing the self-latching security button allows noises from children, equipment, burglars, etc to be picked up and transmitted to other parts of the premises. So. the intercom can be used as a security system in small businesses of a baby alarm at home

Each sub-unit comes com plete with cable and cable fixing pads for £20 each. The master unit costs £85 and comes with a mains plug and a screwdriver. Talking of Blondie - she can install an intercom in my office any time

Further details of this system is available from ITT Terryphone, Station Approach, London Road, Bicester, Oxon C006 7BZ

ETI NEWS JAN 1980



BANDING TOGETHER

The Editor. Electronics Today International. 6 Ebury Street.

We were most pleased to read the article "C.B. for Britain" in your July usue. The Citizens' Band Association is campaigning for the establishment of a VHF Citizens' Band in the UK and agrees with nearly all the points you make.

We have prepared a technical proposal for a VHF FM Chizens' Band which is being sent to the Home Office for discussion and contains a number of proposals to ensure that a British Citterna' Band suffers from few of the disadvantages of the American one. These Proposals include: Modulation shall be FM which avoids many problems of TVI. BCI and audio equipment break-in. 3 Each transcriver should contain an automatic identifying signal which is transmitted revery time the transmit key is depressed. This means that anyone misuding Citizens' Band easily be identified. 3. Transmission time should be limited to 75 seconds to prevent channels being monopulsed. Apart from the above, and a few purely technical proposals concerning standards which should be high enough to prevent interference to other services but not to unnecessarily high as to price Clitzens' Band equipment out of the market, we believe that a British Critzens' Band should have a minimum of regulations.

Membership of the CBA is (1.50 p.a. for individuals and (5 for elubs.

Yours faithfully.

be driven by CMOS and other ICs. ETINEWS MARCH 1975

operating voltage and low power draw. Such features allow the displays to

James M. Bryani, President, Citizens Band Amoristion.

ETI NEWS OCT 1976

STEERING WHEEL? WOT STEERING WHEEL?



We had a very careful second look at this photograph, vowed to give up wine, women, and especially song, (for at least five minutes) then decided yes he was in the back seat, and yes the car was moving. Visions of a huge hoax flashed to the editorial mind frenzied navvies rushing about with the backdrop to simulate movement tiny men crammed into the wing mirrors steering via cunning Chinese arrangements of levers and gears. The mind boggled.

Alas the answer is nought so scandalous. Ouite simply an Australian electronics enthusiast has packed his car full of voice recognition and MPU circuitry to the end that it will now obey verbal commands - even by walkie-talkie up to a range of 12 miles (Naturally it obeys only its owners voice).

The car has a CCTV system Installed which enables the driver to see behind him – very useful in injon country. Infra red sensors pick up red traffic lights and brake the car automatically – no we're not joking. Radar ranging maintains a constant distance with respect to the car in front, and sensors apply the brakes should the car come too close to any object – even people.

All this makes it a better driver than most of us.

ETI NEWS NOV 1976

right hook

In a historic ruling, the US Supreme Court has confirmed that private individuals have the right to buy or make their own telephone equipment and connect it to the US telephone network. Under the ruling it will be legal to houk up as many devices at the user wishes computer controlled systems. 'phone diverters, memory dualiers, picturephones etc. etc. The only restriction is that the various bits must meet the relevant FCC requirements.

ETI NEWS APRIL 1978

DIGITAL RECORDING

Japan's Nippon Columbia company have developed a digital recording technique. The new equipment, said to cost over £125,000 unas pulse code modulation. Advantage of this technique is its virtual imperviousness to noise and distortion. Further details will be published as they come to hand.

ETI NEWS JAN 1973

LASER STICK FOR THE BLIND

A stick specially designed for blind persons gives the bearer a loud sonic signal in the event of impediment in his path at wrist height or above. The new device was commissioned by the Swedish Institute for the Handicapped and work on the project was initially financed by the Swedish Board for Technical Development (STU), The prototype stick comprises a 1.3-metrelong tube made of glassfibrereinforced plastic. To it is attached a gallium-arsenide laser, a midget transmitter and receiver, and an amplifier. The power source is a tiny nickel-cadium accumulator. The laser beam's trajectory is almost at right-angles to the stick's length, and as such sticks are normally held forward at an angle of about 45 degrees to the ground, the beam is directed both upward and forward. The laser sends about 1000 pulses per second and when one of these meets an object - such as a lorry, car or a road sign - it is reflected back to the stick, where it is electronically transformed into a sonic warning signal to alert the bearer. ETI NEWS NOV 1972

Dynachem Industry Protection

New Dimensions in Chemistry

GIRL BY INSTALMENTS!

Electronics manufacturers throughout Europe are receiving a series of unusual sales leaflets from a manufacturer of specialist chemicals used in the making of printed circuit boards. Dynachem are sending out four leaflets spaced at regular intervals. On the front of each will be printed a tantalising part of the company's DYNAGIRL, an exquisite young lady well worth a second look. By keeping the leaflets, the recipient will be able to build up a complete picture. On the reverse sides will be information about the company's range of photo-resists, plating solutions, brighteners, cleaners and ancillary chemicals.

X





ETI NEWS SEPT 1961

Mini Discs

Philips, Sony and PolyGram have declared the Compact Disc Digital Audio System ripe for production. These companies are manimous in the belief that this new system will eventually replace the LP as we know it. PolyGeam Records Operations and CBS/Sony have now put their productions on Compact Disc. It is not expected that the CD will be on the market before the autumn of next sear.

STEREO CONTROL UNIT

Connect this unit to your existing power amplifier, and at your fingertips you will have a degree of control over the audio spectrum previously unattainable with conventional tone control systems. JVC's unique Model SEA-10 takes the full audio range of 20 to 20,000Hz and divides it up into five discrete frequency bands centred at 40, 250, 1000, 5000, and 15,000Hz. Each band can then be varied independently by 2 12dB using the professional type slider controls with 2dB click stops.





CARTRIDGE PERCUSSION UNIT

Bandmaster Limited of Gloucester Street, Glasgow, have designed a rhythm unit called the Powerhouse

which uses multi-track continuous tape loop to produce multi bar synchronised "live" percussion rhythms.



The way things are going, the adjective 'digital' will uson be dropped when talking about test gear. The advantages of digital readout are overwhelming compared to the standard meter (which has of course an analogue readout) and most new quality

d

test equipment utilises direct digital readout. One of the recently introduced DMM's is the Alpha from Advance Electronice; amongst the many attractive features is the price of £55. ⁶

ETTNEWS JUNE 1973

MPG meter.....

A Decade of Electroni

A device called a Mileage Computer (what else?) from the Young Corporation in America is designed to produce a digital readout of miles per gallon being obtained from a vehicle at any given instant.

The device is composed of speed and distance sensors, fuel level indicator and calculator circuit. A sensor attached to the speedo picks up pulses every revolution to provide some of the info needed.

The MPG meter will sell at around \$20 in the USA. ETTNEWS DEC 1977

COLOUR PREJUDICE?

Official figures for the number of homes with colour TV's, i.e. those with a license, have just exceeded 50% of the total. Some lesser mortals might well be tempted to conjecture how high the total would be if the un-licensed felons in our midst could be stood up and counted. Naturally we refrain from any such thoughts. ETt NEWS DEC 1976

TELEPHONE COMPONENTS

High-standard telephony today relies on components and function elements whose design and properties render them equally suitable for use in completely different fields. Read-only memories, MT components, keylock connectors and automatic cutouts are some examples of such components.

The MT (magnetic-core transistor) component developed detection of switching criteria in dc signalling systems, has a magnetic core with a rectangular hysteresis loop to detect signals which are amplified by the transistor. The core and transistor circuits are operated at the same potential and the defined Y es/No statements can be evaluated electronically or via relay circuits.

ETI NEWS APRIL 1973

PLASTIC BOXES

Vero Electronics Limited have recently become distributors for the Odenwalder Kunststoffwerk range of plastic products which include a range of plastic boxes. These are manufactured from high impact polystyrene, which is suitable for machining, engraving and silk screen printing. The upper portion of the box is coloured light grey and the lower portion, dark grey. The latter is provided with integral fixing points for dircuit boards. The boxes can be free standing or wall mounting and should provide an attractive enclosure for reader's projects.

Vero Electronics Limited, Industrial Estete, Chandler's Ford, Eastleigh, Hants. ETI NEWS JAN 1974



Polaroid are about to release an automatic focusing camera that uses an ultra-sonic transducer to measure distance.

* Computers stores in the US are opening up literally every day — we have just heard that 700 have been identified by someone preparing an exhibition! In addition to those dedicated to Home computers, office equipment suppliers and camera shops are at the forefront when it comes to jumping on the bandwagon; even Macey's stores have now got a computer department in some of their stores. Sanyo have demonstrated a 6 mm thin solid state green and black television. The display is made out of 6,144 green LEDs in an area only 50 mm by 75 mm. They hope to have a commercial set by 1981.

* A radar based overspeed detector is in use in the U.S. of A, the unit measures your speed and lights up a neon sign saying YOUR SPEED IS..., REDUCE SPEED. The unit is very effective, only problem was the local hot-rodders using it to check their top speed! Problem solved by limiting display to 75 instead of 90.

ETI NEWS SEPT 1978



SOVIET RADAR BLAMEO FOR HIGH HEART DISEASE

A Russian radar tracking station near the Finnish town of Ilomaritsi may be responsible for a sharp increase in heart disease and cancer according to Dr. Milton Zaret, an American microwave expert.

The Finnish border towns have the highest rate of heart disease in the world and cancer has increased inexplicably.

ETI NEWS JULY 1975

BLUE RESEARCH

Your choice of LED colours might include blue in the not so distant future. The new devices, being developed by Stemena, use silicon carbide and are predicted to have a forward voltage drop of 4 V at 50 mA.

ETI NEWS OCT 1979

CMOS IN PLASTIC PACKAGES

Motorola Semiconductors have just announced that 39 devices from their standard CMOS logic family are now available in plastic packages. In the past, ceramic packages have been used for all CMOS devices

ETI NEWS SEPT 1973

FAIRCHILD TO MAKE CONSUMER PRODUCTS

The USA's Fairchild group are actively planning to enter the consumer products market, according to a usually reliable source.

Fairchild's first products are believed to be a low-end of the market onechip hand-held calculator with 8-12 digits. However several industry commentors query Fairchild's ability to produce the necessary MOS chips, quoting Lester Hogan's (president of Fairchild) own description of his company's performance in the MOS field as 'disappointing'.

ETI NEWS JUNE 1974

the little cb that santa forgot

Citizen Band - radio manufacturers around the world are crying into their transceivers after Xmas. They expected a boost to sales to revive their drooping business, and it didn't materialize. Seems no-one wanted to contact anyone eite - not even the reindeer.

ETI NEWS MARCH 1978

Watch This!

If you're sich of digital watches, how about taking a look at this watch from Casio. Its all analogue, but with a difference. It's fully electronic and has no moving parts. It uses LCD and has conventional hours, minutes and sweep seconds hands The Model ANBCL is designed to be attractive and fashionable, face colour matches the synthetic strap. Hour positions are marked by standard Roman numerals and all the time settings and adjustments are handled by two buttons, keeping the compact gold-plated watch case simple and uncluttered. The display shows hour and minute hands, and seconds indication is by a third sweep hand or as a series of marks on the face edge to show ac-cumulated seconds Accuracy is to within 15 seconds a month RRP is 627 95, but products of this type are often sold cheaper. Further information can be obtained from Casio Electronics Co Ltd. 28 Scrutton Street, London EC2A 4TY

ETINEWS NOV 1981



GREENWEL

443A Milbrook Road Southempton SO1 CHX

All prices include VAT at 15% - just add 50p post

CONGRATULATIONS TO ETI ON THEIR 10TH ANNIVERSARY

Here are some special Bargains to celebrate!!!

ET1 Electrolytic Pack - 10 each of these PC many types: up //1 .07/88, 1/80 [2,2/80, 4.7 40, 10 23, 20078] top: 10.027/88, 17/18, 47/40, 100 18, 100 28, 220-58, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1000/18, 1

4.7 40, 10-40, 22 40 23/28, 47/18, 47/48, 100 18, 100 18, 220-40, 100/28, 100/18, 1000 180 caps for CB 86 173 1A revue - 28 each Halder, 3, 8 5 7, 7 and 100 for (2,85 173 1A revue - 28 each Halder, 3, 8 5 7, 7 and 100 for (2,85 173 1A revue - 28 each Halder, 3, 8 5 7, 7 and 100 for (2,85 173 1A revue - 28 each 14,000, 1, 100, 100, 100, 000 for (2,85 174 176, each - 6 each of M000, 02 45, 10, 10, 20 20, 07, 70, 74, 00, 00, 00, 00, 10, 1, 100, 20 100, 20 100, 07 100, 1/ 100, 10, 10, 10, 10, 10, 20 20, 07, 70, 74, 00, 00, 00, 00, 10, 1, 121 Total D0 chapt for (14,85 175 100 / 124 each energy diverse - 10 for (2 176 20 / 124 each energy diverse - 10 for (2 177 200 / 4A Trace - 6 for (1 177 200 / 4A Trace - 6 for (1 177 200 / 4A Trace - 6 for (1 177 200 / 4A Trace - 6 for (1 177 10, 10 / 10 / each caps - 2 for (1 177 10, 10 / 10 / each caps - 12 for (1 177 10, 10 / 10 / each caps - 12 for (1 177 10, 10 / 10 / each caps - 12 for (1 177 10, 10 / 10 / each caps - 12 for (1 177 10, 10 / 10 / each caps - 12 for (1 177 10, 10 / 10 / each caps - 12 for (1 177 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 10, 10 / 10 / each caps - 12 for (1 170 / 10 / 10 / each caps - 12 / 10 / 10 / each caps - 12 / 10 / 10 / each caps - 12 / 10 / 10 / each caps - 10 / 10 ET11 Maris transformer 12-8-12V MmA, 2 for part (1 ET12 100 Islan MB doctor (2

STABILIZED PSU PANEL



A198 A versatio statistical power supply with both versage (B-200) and current GBmA-2A1 fully version. Many uses in: tench PEU, Need charger gph overcon-tening. Pand ready bulk, tested and calibrated (2.3% Suitable transformer and ants ES 00. Full data mended

SPECIAL ETI **BIRTHDAY OFFER** (Aren't we nice!!!!)

The above PSU transformer galls, heat eon and smart calificat to mours it of its, plus serving chapters in talks.

JUST £24.95

MIXED LED PACK

now full epoc by Micro, Fonchold, I. Yollem, Green, Amber, Coar, 3 mm. Poch of 50 assist (2.05, 250 (15 Red. Vola

1W AMP PANELS

4011 11 Currence audio amp intended for card alayer on panel 05 + 65mm including will control and position, complete with tendes. Again from amp discusivy built around UNISON or TEASION, there is a entral circuit using & venesitors atom, canonican data bapping. 041 Y 11.00

OP-AMP PSU KIT

A 190 Al parts + statisticities to make a SDmA + 10, 0, - 19V supply trait make liquit. Only (1,0)

P.C. ETCHING KIT MkV

The basit value In exching him on the marker - contains 100 pg ins capper (bid baped). Partic Chanda, Etch resist pan, abranin classes, two mineauxe dell bla, etching den and expructants. Ad tor (4.65).

PANELS

2021 Panel with 19220 (24042) on small host chil, 2402223 daud remeator, 2 GC148, dada, capa, reparent, cap. Obs. 2027 Rend rather panel 2027 Revel relay panel -- contains 2 = 0V code, 6 = 25030 or 25230, 8 = 400v recto = 8x 90p.

ZAR Pack of an computer param contenent N serve ICs Lots of different gates and compten logit. At ICs are marked with type

r codo far shant is suspined. 30 ICs (1 00, 100 ICs (4 00 ASC4 Glack, come 50 + 50 + 78mm and actual losis. PCB mands has 24V rood roboy, 200V 7A SCR. 4 = 5A 200V roots otc. 05p.

CHEAP CHIPS 78477 See 0 IC (1 25

2102A RAM 8 for C3 MIL4027 shift reg 8 for E5 00.13 gan Here + DANKA uA70MG - unit ray (1.20 No.5112 Duel Phys Pres & for (1 FiL311 meadocrimer dealey a anth decode 0-9 and 4-1 with sets (2.16

DEVELOPMENT PACKS

These packs of brand new t components are designed to uctor a complete range so the kipt while is to have adverses required. They sha give a substantial arving over buying individual parts. 8.001 50V corposit, pipes cap

sech while 22pf to 1,000pf, total 210 (4.80

K882 Extended range 22pF to 8.1. Volume even 1000pd eve of a granter talavance, 10 of each value 22, 27, 30, 30, 47, 68, 68, 62, 108, 138, 150, 180, 228, 270, 330, 380, 478, 540 488, 830, 1000 1900 220 2300 4788, 4800 01, 016 022, 033 047 NICE (7.86

1003 (280 or similar Polyanter capacitars, 10 each of the Interesting 01, 015, 022, 033, 607, 688, 1, 19, 22, 33 and 61-4 PMCE (5.40

A Air Prince (18.40 K054 Arvier capacitors: Small dies verflast maximing 100V, 10 each of the following, 501, 5012, 0018, A018, 0022 0027, 0030, 0030, 0047, 0056, 0050, 0030, 0030, 0047, 0056, 0050, 01, 7688 130 capacitors PRINCE (4.76

1007 Decretyte: capacitars 20V acting and physical size and or redat tests 10 each of the following 1, 2,2, 4,7, 10, 22, 47, 100uf Total 70 capacitors, PERCE C3.00 8.000 Enter

La.W Koos Lotendad range, as abave, also including 220, 670 and 1000x8 at at 25% Teatr of 100 capacitions. PRICE (5.28) K623 CR35 resistors of amilian, manaphane to restrict probability of another patient to 5%, as used in reserve at another to 16, 213 another to take the resistors. Testal 610 resistors. Patient 610 resistors. PRICE (5.55

K041 Zener diades 400mW 5%. 10 each af all the volume from 2V7 to 38V. Total -----

200 Januars, PRICE (15.85 15051 LEDs, Pace of 60 compraining 10 sach roll, grown and yollow 2mm and Smin together with ctas. PRICE (25.95

UHF TUNERS

GJE Synamia MI720 Channels 21-1

VHF TUNERS

Type F3720 (CCalls by Sylve in Surgar of ante CLOD

RELAY/TRIAC PANEL MKII

INTER P 3837A PCB 165 + Reve constituting a regular of companyation 2 + 12V DPCD non-relaxes, SC1400 10A 400V etcs, BB every 19 + 144001 dectm, 246001 SCR, 2 + 2mm LED + 3 + 2143704, PS 6 C1 - Amazing value - I tanget expensive, pero metuid care among BP Cur prop for the panel, pet E1 60

LIE DETECTOR



Ball a law, this property of an Oper

1000 RESISTORS (2.50

Vertice part porchased analysis is relating participants, and can reace a distance after up that media two years ago, at the same priorities (\$22 - 300 missed is and \$14 5% cateor Bin realizes, portunities for PCB array Environce comp of professional for PCB array Environce (\$10 28), 628

200 ELECTROLYTICS £4.00

ESSI Large control of account offerent, account crossed tasks for PCB money 1-+ 100567, 10-407 24 news Auf agest control services, not church cultiff 200 (4, NOC (17.00

CAPACITOR BARGAINS

2200-7 1007 cores (2) + 60mm das 76pr 10/15-66, 220-7 107 sound bis 100 2.23 1000 (16 das -100-7 2007 102 - 60mm das 78, 10 6.20 200-7 2007, 102 - 100 - 50-7 2007 core 75 -60mm das, 60p 10 (2) 1007 (20 1007 20 4.50)

Common date, dates
Color
Color</td

TOROIDAL TRANSFORMER

Horve de a dinne dans 110 July pt., 104 db, 6 Jr 56, 300 0 Jd. stast for pr manutary. VOU's de, Spaciel ten ption (5 6

TRANSFORMERS Marra primary, BPV 35A stite (20.60 Marra pt. 1107 15A stit (20. 35A (46.60

DISC CERAMICS

Salah dana

Man des

C 20-1 UV there do Mart for decending Mill C 20 To 1000 CBAB Ford of dec constant Parts of the comprise and it

1N4006 DIODES

Spectar p.ochase of 1A rects, Resame made, Packed in boom of 200, 03.00 per box, 4 boom (20,00 Minanta (20

AUDIBLE WARNING DEVICE

to proving any and the second of the second second

NICAD CHARGER

Versible unit für Gerging AA, C, O and PPD benturks: Charger/stat cellink, LED reducers of each of the 5 charging parels. Mains passified, 210 - 300 - Sthen, CT, B

ULTRASONIC ALARM - E14.85

mail in a 120 A dianty began and be to Despite has shift the inter the

SOLENOIDS AND RELAYS

WET Selected unter AND RELAYS unit and an 344 (Repr pd Norm band) po the part 27 + W + Norm Bag WEE Many 3604 (resp. . Ind

WHER Manne Jall's as estimated. 19% and ryates, both or golf, 10mm mount, 10 - 20 - 10mm. Only 71 100

The second state for the second state sta

AMAZINGI COMPUTER GAMES PCB's for PEANUTEII

A 1948 194 computer games with the best sector and Lages 5 and States and the st to affer a manufact the prices

STARBIRD

Examples explore sender and Stanling two black mails explore sender and Stanling two black from sender to an Stahl and her heat to generate op, destinating water when period dears. From senders to an Stahl and her lites of two streeting. PCB water and set setting complete activity and her dear and period ban dear and trade PPB. PCB water 10 + Elimit Christop PPB.

SIMON'

BirmCvit The edgest of this period to to regard connectivy a langue and langue exploratio of eignate in 3 different gamma. Supervision inducted: PCB compton charg, workford, translated and langua, and is super-containing, compatible with espection floweds PP9 and 2 v. HP11, PCB size 120 m 120mm, Onty CLID

COMPUTER BATTLEBHIPS

"COMPUTER and the east paper decrement probably one of the east paper decrement probably and the east paper of the second makes is the major of the FCB at a certain maket, alternish in may call function perfective readed, alternish the two down of the second the based for its certained the second city, and of the based for its certained the second city, SADBUT sound IC, TMS SIBB - processing the data, Fig. C1, one is see 100 - 1 Main City, SADBUT readed, base 100 - 1 Main City, SADBUT

MICROVISION Cartiligan

Const and the connecting a hotory and space. Taxad an order to contain the an appl and an and appl and and appl and appl and appl and appl and apply a Canada and apply a Canada apply

ONLY Zip eachil

LOGIC 5 PANEL

Yestert Legit & new sall out - but on fure spill PCB's still 10 LED's and chip an, but re tayloaget. Rot tasted Sbp



Destruit conductor test - for maximum texacity - patt proof. I retilize contentioned four a twender, then rate again to a terr methor, Only other the test contentioned o for contest supervise will the destruction contest the contest supervise will the destruction contest them. These each to acted to react asparence and the destinat contain These can be and to approve a very al. Orange day, filmer a dama daug. O 01.00 and the suffrage supplier at the Child

1982 CATALOGUE

print, Bull the log new 1982 3 address shauld be made by two March 10 - Sand The for your

WHOLESALE LIST

We have to statch namy willing of companying -we supply thege. M/O companying, Bahash, toducted them set: Can no supply state, has for substitut them set: Can no supply state, has for substitut them set: Can no supply state, has for substitute the set of the set of the set of the substitute to set of the set of the set of the bulk duyon for

NEW CONTROL SYSTEM FOR SLR CAMERAS

Electronic shutter speed and exposure controls can now be built into single lens reflex cameras without mechanically modifying the camera bodies or lenses.

A new control system, developed by Matsushita Electrical Industrial Corporation, measures the light at a preset aperture (in less than two

milliseconds) and then sets exposure time accordingly, Control range varies from 0.0005 seconds to four seconds - dependent upon lens aperture and film speed.

Prior to the Matsushita development, it was necessary to have a light measuring device accommodated behind the main lens - calculating light intensity with the lens held wide open. ETI NEWS JULY 1975

RIDING HIGH

The next step in America's space programme is the tesing of NASA's space shuttle. Landing tests are to be carried out in mid 1977. Amazingly the machine will be launched 'piggyback' from a Jumbo 7471 Several



flights will be made to ensure stability before the shuttle is actually released. Trust Americans to build the worlds largest airliner and then carry people outside it! ETI NEWS AUG 1976

A new edition of ETI starts this month - Elrad in

Elrad: ETI Germany.....

Germany The name Elrad itself means nothing and is simply an amalgamation of electronics and radio. It is being published by Heinz Heise in Hanover and is edited by Udo Wittig ETI NEWS JAN 1978

COSMOS NOW CHEAPER THAN TTL FOR MAJORITY OF DIGITAL SYSTEMS

RCA has announced further price reductions in its CD4000 range of COS/MOS integrated circuits. The reductions range from 35% to 60%. The biggest price reductions have affected the more established MSI devices of the CD4000 range, with many types being reduced by over 50%

As a result of the price cuts, many of the popular TTL devices are currently more expensive than the equivalent COS/MOS functions.

ETI NEWS SEPT 1975

CB2B

361

JULY

NEWS

A t long last a specification has been published by the Home Office for the legalisation of Citizen's Band radio. Two frequencies will be allocated 934.025 to 934.975 MHz and 27 60125 to 27.99125 MHz. For the 934 MHz (AM) frequencies the maximum power is 8 W (25 W ERP). 20 channels at 50 kHz channel spacing Hand-held units are restricted to 3 W PEP On the 27 MHz (FM) ire quencies the maximum privaters & W (2 W ERP), 40 channels at 10 kHz spacing, frequence tolerances a 1.5 kHz Mashmum frequency deviation: \$2.5 LHz. Adjacent channel pimer: - 10 dB to 2 uW, purious emission less than 50 nH

PLAY-ALONG-WITH-RCA

Single chip I/O for video games is the laudible aim of messers. RCA. To be introduced in January the device is primarily a vertical and horizontal synching circuit designed for use with RCA's 1802 MPU. Price could well be around £12 when and if introduced into this country.

ETI NEWS DEC 1976

CBM AGAIN!



Right - now you've stopped staring at the picture can we proceed with this month's news. Thank you. Once again our old friends CBM have managed to get in on the act. The above watches - yes watches - represent their

long-awaited entry into the digital watch market - with the 5,000 series. All three use a common module, with the casings making for a price range of £17.50£21.00

ETI NEWS JAN 1977



CZECH ON CALCULATOR PRICES ETINEWS MAY 1976

A typical dour Czech day. The rain sleets across Prague. Somewhere in the back streets well away from the patrols and the populace, Ivan scuttles into a dingy corner shop.

There, amid the Western papers and naughty mags, he spots the object of his desires.

Eyes alight he lifts the proscribed machine from the rack, and carries it reverently to the counter, behind which stands the owner.

"How much?" he stammers, hands shaking.

"Novus 650 comrade? To you, £172. Crossed the border this morning right under the army's noses." he looks around furtively, and leans across the counter, whispering.

"Interested in the REAL thing eh comrade? "Ivan nods. The man reaches below the counter and produces a battered show box. Ivan's eyes are wide by now, riveted to the lid as it lifts. Inside lies a full frontal scientific, a HP 45.

Ivan faints.

Now before you dismiss this as merely the alcoholic follies of the ETI staff, following a party, let us inform you dear reader, that whilst we may be guilty of slight embroidery, our flight of fancy is based on fact.

It seems our Eastern friends consider pocket calculators to be highly prized items, and will pay vast sums to acquire them. What would cost you or I £7, our Ivan would need £172 to own. For that HP 45 you could possibly get a weekend with Siberian Sue, belle of the Balkans.

The reason behind this black marketing and smuggling is that calculator ships are not produced behind the ferric curtain and the machines are banned from importers fists by the governments, to preserve foreign exchange as their value is so high.

I wonder how they count it?

FOUR CHANNEL DISCS

In the UK the EMI group have announced plans to release guadraphonic discs – using the CBS developed 'SQ Matrix' system – in April, The company claims that the new discs will be fully compatible with existing stereo equipment, ETI NEWS APRIL 1972

COMPUTER 'ON A CHIP' WITH CASSETTE TAPE

A new byte-orientated micro-computer with its own in-built cassette tape backing storage has been produced by Computer Electronics Ltd, of Saffron Walden, Essex, as part of its range of cassette tape data systems.



Believed to be one of the first 'processors on a chip' computers to be developed in this country, the complete computer fits on one of the company's standard printed circuit cards. ETI NEWS AUG 1973

TV GAMES LSI CHIP AVAILABLE SOON

Rumours have been abounding for about a year now that an LSI chip for television games was being developed.

We now have definite news that Logic Leisure, a British Company have produced a chip which will produce four TV games, with two variations on each, giving eight permutations. There is score and sound facility. Type number is not yet known but the chip is suitable for both 625-line, 50Hz and 525-line, 60Hz.

It is hoped that the chip will be on sale in October and the price tag is going to be in the £10-£12 range (plus VAT). U.K. distributorship is in the hands of Television Sprots Co. Ltd., 6 Half Moon Street, Mayfair, London, WIY 7RA. ETI NEWS AUG 1975

CALLING ALL K95, R2D2s, ROBBIES, C3P0s, MICROMICE etc. etc.....

ETI is very keen in getting a robot dialogue going. Anyone out there on the other side of the printers jnk interested in robotics, especially anyone actually building robots of WHATEVER complexity - should contact us here at ETI If possible how about some photographs of your machines? They may well be in line for an appearence in ETI. So come on, lets be hearing from you -ALL of you - take pen in hand (or get the robot to do it) and write to 1979 The Editor. ETI Magazine, NON

145 Charing Cross Road, London WC2. Mark your envelope "ROBOTS" So we can deal with it with our usual machine - like_ efficiency.

brief news

NEWS

NASA have received weak signals from Skylab for the first time in four years. The possibility of sending it deeper into space is being considered....

A study by the American National Institute for Occupational Safety and Health (Niosh) has concluded that VDUs in use in the offices of the New York Times are not responsible for cataracts developed by two copy editors working there.

ETI NEWS SEPT 1978

Hitachi MAGic

Hitschi have bettery pack watch the sperimental colour video camera combined with a video tape recorder — provisionally christered the MAG Camera". Using high density recording techniques, the combination is little bigger than an 8 mm circe camera. The camera using W⁶ tape, is almost as small as an audio camerte and allows two hours of recording/playback. The complete unit weight only 2.6 kg. including a rechargeable battery pack. Watch this space for news on development of the MAG Camera.





From a firm called James Niell comes the Micro 2000 to rise into our News Digest with carefully measured precision. This instrument gets our vote for the best innovation of the year already! A digital micrometer no less.

As you can see from the picture, it actually reads out a measurement in seven-segment format. Goodbye verniers. It has so many features and advances, it is perhaps best simply to list them.

Accuracy to ± 0.002 mm., with a 'constant force' spindle and selfcalibration facility. As soon as it is switched on, the 2000 self zeros.

The zero reset means that it can be used as a comparator against a known standard, and variations from that can

BRITISH? PRECISELY!



be read directly. Also in awkward situations, the instrument can be

zeroed, utilised, and then removed to he read. ETI NEWS JUNE 1977

Sat 54

Well, it was Satcorn 3 actually, but the plot in reminiscent of that old, old American telly series. The Car 54 in this case, however, was an RCA communications satellite, last heard of in December, 22,000 miles above mother Earth

If anyone finds a communications satellite answering to the name of Satcom 3, send it to RCA, nto us. Mind you, if it has gone up in a puff of smoke, it has probably burned up on its way back to Earth NASA quick to assure us that it won't cause another Skylah incident. So. you needn't dust off your anti-Skylab umbrella, yet. ETI NEWS MARCH 1980

HP AT A (CALCULATED) LOSS:

Hewlett-Packard - renowned for their up market calculators, are apparently running this section of the business at a loss. Equipment and other activities are keeping then in the black, and H.P. cite the delays occurring on the introduction of new models as the cause for this. Also named as a culprit is "severe price erosion in the pocket calculator marketplace". Pick the bones out of that ye rivals of the beast.

ETI NEWS NOV 1976

CEEFAX AND ORACLE SYSTEMS COMBINED

The BBC and IBA, together with BREMA and the Broadcasting Department of the Home Office have agreed on a unified system of data broadcasting.

Until now the BBC have been working on CEEFAX, the IBA on ORACLE. Both systems allow a TV viewer to select at will from a number of different 'pages' of information and put these onto his screen.

ETI NEWS JULY 1974

Text To Talk

KurzwellComputer Products of Carrieridge, Massachussetts has developed a machine to turn written text into speech

The machine contains an optical scanner, a small computer, a small synthesiser and a loudsomaker unit.

The page to be read is placed over the scanning unit which then converts the written text to digital signals for the computer. The computer then converts them into sound

ETI NEWS APRIL 1980

A computer system cal A computer system cap able of controllins the lighting and heating in up to one hundred buildings to one hundred buildings has been set up in London by Honeywell. The system. by Honeywell is the first of by Money well. The system, called BOSS, is the first of its kind in the UK ETINEWS MAY 1978

ELECTRONICS ENGINEERS SALARIES FALL BEHIND

The 'Survey of Seleries', published by the Management Survey Centre this August, shows that the salaries of electronic engineers working for large companies have stagnated whilst other engineers' salaries have increased. Senior chemists have done best - their salaries have increased 3-4 times more quickly than the average.

For a senior professional in development (with major responsibilities) the median salary is £4,174; for electronic engineers in particular the median at this level is £3,720.

ETI NEWS OCT 1973

tunk calls

From the land that brought us Muzak and MPUs comes the Junk call - the same as Junk mail but verbal! A machine is being used to dial up to 1,000 numbers a day and make a prerecorded sales pitch, unlike junk mail there is no way of knowing when the call will be junk or not. By dialing up numbers from 0001 to 9999 the machine annoys everybody who answers on a particular exchange, even if you hang up it holds the line open until the pitch is finished - this has caused emergency calls to be delayed in some cases.

Ten states are considering legislation to curtail the activ ities of the machines. However they intend to exempt charities. polisters and politicians. Some people want an electronic 'no thanks' sign to be developed. although nobody is quite sure how I would work. What next?

ETINEWS SEPT 1978

ANRS INTEGRATED INTO A SINGLE IC CHIP

In 1972, JVC first introduced their Automatic Noise Reduction System (ANRS) into their top-range cassette decks. Since then, ARNS has been incorporated into a wide range of tape decks. Recent improvements however, in cassette deck quality and the possibility of "noise-reduced" FM broadcasts have meant improvements in the quality of noise reduction systems and the application of these systems to components other than cassette tape decks.

To meet these new requirements, JVC has recently completed the development of the ANRS IC.



ETINEWS OCT 1975





AUDIOPHILE

Soon burglars won't be bothering to nick your whole hi-fi; they'll just take the cartridge. This month Ron Harris reviews two new pickups, one with a gemstone cantilever and the other a work of modern art.

News just in of a new piece of British circuitry genius. This is a new protection circuit, soon to be added to a famous manufacturer's product, which is claimed to make an amplifier totally invulnerable electrically.

Totally in this case means "even from 240 V mains at input or output". Ultra-fast relays are set at the output and on the supply lines to the PCB. These are driven from the new circuit, which has as its final stage a voltage amp with an incredibly high slew rate. This ensures a high speed of operation for the relays.

Out Of Phase

The protection circuit operates like this: if an amplifier is suddenly faced with a massive input signal, the ratio of the feedback signal to input will drop dramatically. A comparator senses the change and a 'low-feedback' signal is generated. This by itself is sufficient to trip the supply relays, so that the overload cannot be passed on to the output stages, thus destroying them — and probably the speakers.

A second block within the circuitry watches the supply rails and any surges which are outside the requirements of normal drive will trip the protection circuit, since this is a "low-feedback likelihood situation" as the designer puts it. Great play is made of the fact that the music signal and the feedback voltage are in anti-phase at the point of comparison, so no interaction within the buffer is likely 'Anti-phase reset', as it is called, thus introduces no colouration. Hence the protection reset of the relays can occur either in the case of low feedback-to-signal ratio, or in event of an "overload likelihood". I suppose this is where the somewhat pompous title of the circuit is derived — Anti-Phase Reset In Low Feedback (Or Overload) Likelihood.



Shure MV30HE

A dedicated offshoot of the renowned V15 IV design, the MV30HE is for use in the SME Series III or IIIS only. The cartridge is built into a SME carryarm such that no headshell is used, or needed.

The moving components are those of the V15, save that no damper is provided. The cartridge body is all new, however, and quite a few problems it must have given them getting the coils and poles into a body as slim as this. The design is so arranged that the point of bearing intersection and the stylus line up parallel to the record. This will tend to aid stability in the replay of warped records.

As in the V15 a hyperelliptical stylus is used, which will give lower distortion results than either a spherical or elliptical tip. Tip mass is commendably low and output level is on a par with the V15 IV.

Once fitted into the SME the MV30HE looks very smart indeed is and visually extremely classy!

Testing an Armful

In the lab the MV30HE had an easy time passing just about every test. It tracks as well as the V15 IV and measures slightly better. There is no higher technical accolade than that. The LF resonance came out — surprisingly — at around 16 Hz, a little higher than optimum in my opinion. Best values are somewhere around 10-12 Hz so as not to affect extreme LF reproduction. Best tracking was obtained at around 1.0 g, and no improvement was forthcoming for increased force.

Frequency response was boringly perfect at 20 Hz — 20 kHz ± 1.3 dB with a separation figure of 27 dB at 1 kHz. Compliance measured very high at 34 cu, so only the smallest damping paddle is required. It is required however — see later.

Instructive Stuff

The instruction booklet is worth a special mention. It is a straight 'copy' of the SME style, right down to the little diagrams with ticks and crosses for right and wrong answers. Some sort of deal has been struck here, methinks!

One point that I just have to mention here; I could not,

At long last Quad have released their new tuner, the FM 4. It was shown for the first time at the Audio 82 exhibition in Swins Cottage recently. Designed to match the Quad 44 control unit (preamp to the rest of us) the FM - only unit has digital tuning and seven pre-set stations. Programme locations are stored in memory.

A tuning knob has been retained in preference to a set of pushbuttons, since Quad say it is easier to use.

Brief Specification:

Full limiting	1.V	IF Rejection	100 dB
Distortion (1 KHz)	0.15%	Image Rejection	80 48
Capture Ratio	2.5 dB	Crosstalk (1 KHz)	40 dB

NEWS

The MV30HE set up In a Series III. About the best looking piece of of hi-fi you'll ever see. As the compliance is very high only the smallest damper paddle Js required, despite the lack of dynamic stabiliser (as fitted to V15 IV).

> in any circumstances, get the arm to balance out using the recommended mixture of weights and spacers in the SME. Despite Shure patiently showing me the same arm set up perfectly in *their* Series III, would it balance once I left the factory? It would not! I would be most interested to hear from any MV30HE purchaser as to balance requirements. I agree the total mass is 11.8 g but I'll be damned to an eternity of music centres playing Barry Manilow before I'll agree that an MV30HE balances in an SME Series III with four weights and six spacers.

Down To Sound

I suppose the obvious comparison with the MV30HE must be the V15 IV. So, as I'm getting old and predictable (I still hunger after Felicity Kendal...) that was the first pickup against which I auditioned the unit. Frankly, I had expected to discern no difference, and initial tests confirmed this to some degree. However, having settled in at home with my own system around me and the reassuring brandy in hand, subtle differences began to manifest themselves. The MV30HE has a more coherent sound - the mid-range is more open under close examination and the bass is 'cleaned-up' and tighter, if a little more prominent. These are exactly the changes to be expected from a unit which simply matches the arm better, but has a higher resonance. Which, of course, if I'd thought about, is exactly the MV30HE/V15 IV relationship. Serves me right for being so sure of myself! In comparison to the market as a whole, the MV30HE/SME pickup stands well-up with the best. The damper is not significantly missed, provided the SME paddle is employed. Leave it off and boom is liable to result, as is a certain lack of stability on warped records. A limited application, then, but a very creditable performance and one which will compete with Shure's own V15 IV. After all, if you've got an SME and were contemplating a V15 IV, the MV30HE is a better bet all around. It is no more expensive than the V15 IV with a CA1 arm to hold it and it provides a cleaner, more refined performance. All in all, a nice touch Shure. Whither goest thou now?

NEWS : Audio

DAVANACS ...

Dynavector Karat Ruby

Both this month's cartridges are unusual in their own way; Dynavector's Karat is notable for its gemstone cantilever. This 2.5 mm long piece of single-crystal ruby is cut with a laser to accept the stylus (diamond) and then allowed to cool, thus fixing the stylus in place. The length is remarkably short, since Dynavector say that the less material the stylus information has to pass through, the higher will be the fidelity of the output.

Wave propagation through a medium is something not many of us take up as a hobby, but someone down at Dynavector must have it all well sussed! Apparently this equation:-

$$\frac{\mathsf{EI}}{\mathsf{m}}\frac{\partial^4 \mathsf{y}}{\partial \mathsf{x}^4} + \frac{\partial^2 \mathsf{y}}{\partial \mathsf{t}^2} - \rho \frac{\mathsf{EI}}{\mathsf{m}} \left(\frac{\mathsf{l}}{\mathsf{E}} + \frac{\mathsf{y}}{\mathsf{G}}\right) \frac{\partial^4 \mathsf{y}}{\partial \mathsf{x}^2 \partial \mathsf{t}^2} + \frac{\rho^2 \mathsf{y}}{\mathsf{m}\mathsf{G}}\frac{\partial^4 \mathsf{y}}{\partial \mathsf{t}^4} = \mathsf{G}$$

$$C_{B} = \alpha \sqrt{2\pi^{f}} \left[1 - \frac{1}{4} \beta \frac{2\pi^{f}}{\alpha^{2}} + \frac{1}{4} \delta^{I} 2\pi^{f} \right]^{2} + \cdots$$

where E = Young's modulus; I = secondary moment of section area; G = shear modulus; m = mass per unit length of a cantilever; p = density of the cantilever material; x = distance from the end of the cantilever; y = flexural displacement of the cantilever; r = constant; t = time.

sums up the vibrational behaviour of a cantilever under dynamic conditions. It can also be used to prove that rigid materials, such as ruby and diamond, make for better cantilevers than boron, berylium and the rest.

(There is a 'big brother' to the Ruby, which has a diamond cantilever and costs around £450 as opposed to the Ruby's £100. If I can persuade the ever-helpful Dynavector into lending one I hope to report on the differences soon. Maybe if I say "please"....?)

Temperate Zones of Test

Another piece of original thinking has gone into solving the problem of temperature dependence and damping material. The only rubber used in the Karat is to prevent the cantilever taking its jewelled self up into the body whilst playing records. Normally the pivot damping in a cartridge is accomplished by a rubber block and this is prone to suffer from changes in temperature and slow deterioration as it ages — the Karat suffers neither of these weaknesses.

In fact, due to the short rigid construction of the cantilever, the Ruby requires no damping at all.



Under test the Karat showed a ruler flat response from 100 Hz to 30 kHz of under \pm 0.5 dB! It was only 1 dB down at 30 Hz and separation measured an excellent 24 dB at 1 kHz and a more than adequate 18 dB at 20 kHz. Stylus resonance fell at 49 kHz and in the SME Series III (what else?). LF resonance was well placed at 12 Hz, below audibility and above warps. Tracking was exemplary for a moving-coil unit — at 1.75 g it tracked all my test bands perfectly; the first moving coil to do so. Bias was set for 2.0 g, a high value, but one that worked well. In actual use the Karat was never caught out by any recorded information.

If at this point you're looking around the pages in search of the usual response graphs, don't bother — I haven't included any. If you really want to see a straight line, go buy a ruler. Dishearteningly disappointing for us cynics.

Listening Out

As the Karat Ruby matches the SME Series III so well, it was left in that arm all through the listening test. One brief excursion into a Linn Itokk showed the two to be completely incompatable in my opinion, as the sound stage broke up and the bass became so loose as to be positively flapping! Strange that, as both are capable of much better and there is little on paper to point to such obvious mutual abhoration.

The loudspeakers used were my trusty KEF 105 II's fed by a variety of amplification from Crimson, Monogram and Trio. Source equipment remained at Thorens 160S/SME III throughout.

On the very first LP side I played with the Ruby it was obvious that here was something special. The sound is so detailed and open, with such tight control of the bass that it makes you sit up and take notice of the music. This is a Cartridge that will be much appreciated by reviewers, as it is so easy to listen through for long periods.

In fact there is little I can say against the Karat. It is a trifle recessed — I cannot account for this impression from the lab results, however, but it remains a definite impression — but is so relaxed and balanced a sound that none but the most obnoxious could find aught to quibble with. The sound quality reminded me greatly of the Ortofon MC30, but with greater resolution of complex passages and a more extended bass end.

At around £100 the Karat Ruby is an excellent bargain. Even accounting for the required step-up device, this pickup is required listening for anyone in the market. I have no hesitation in saying that it out-performs many units costing much, much more and will give more musical pleasure than just about any other cartridge I know.

Mind you, I haven't heard the Karat Diamond yet ... but can it really be worth £350 more? On this evidence I would doubt it! (Pause while Dynavector work out whether this is a compliment or an insult....)

ELECTRONIC IGNITION Makes a good car better



TOTAL ENERGY DISCHARGE disctronic on groot all the known advantages of the best capacitive discharge systems

PEAK PERFORMANCE -------- higher output voltage under all

IMPROVED ECONOMY ----- no loss of ignition performance

- FIRES FOULED SPARK PLUGS no other system can better the capacitize discharge system's ability to fire fouled plugs.
- ACCURATE TIMING -- prevents contact ever and arcing by reducing load to a few volts and a fraction of an amp

SMOOTH PERFORMANCE ---- immune to contact bounce and effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK -- 3% times the energy of ordinary pacitive systems - 3% times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems - essential for use on modern cars with week fuel max barns.

- BETTER STARTING -- full spark power even with low hartery.
- CORRECT SPARK POLARITY unlike most ordinary C.D. systems e correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered techometers.
- L.E.D. STATIC TIMING LIGHT for accurate setting of the angine's ost important adjustr
- LOW RADIO INTERFERENCE Sully suppressed supply and absence of inverter "spiket" on the output reduces interference to a minimal level.
- DESIGNED IN RELIABILITY an unharantly more reliable circuit combined with too quality components - plus the 'ultimate insurance of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

It provides a top performance ctronic ignition system at less then half the grice of competing ready built systems. The full includes everything needed, even a length of solder and a timy tube of heatsink compound. Detailed easy to follow instructions, complete with circuit diagram, are provided -- all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue and EVERYDAY ELECTRONICS December "81 Issue

FITS ALL NEGATIVE EARTH VEHICLES. 6 or 12 volt , with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS current impulse types (Smiths pre '74) require an adaptor PRICE 22.05

STANDARD CAR KIT Assembled and Tested	£ 14.85 £ 24.95	PLUS E1.00 U.K.
	£ 22.95	P. & P. Prices
Assembled and Tested	£ 34.70	VAT.

ELECTRONIZE DESIGN

Dept. D. Magnus Road, Wilnecote Tamworth, 877 58Y Phone: (0827) 281000

VISA

DIMENSIONE.

12.5 cm 8.9 cm 4.3 cm Lead length 100.0 cm

Longth

Watth

Handys

0

As a KIT OF READY

BUILT

TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer burn times and other marketing fantasies. It is only necessary to consider that, even in a small angine, the burning fuel releases over 5000 times the energy of the spark to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The assential function of the speris is to start that combustion as quickly as possible and that requires a high power sperk

The traditional capacities discharge system has this high power spark but, due to it's very short spark duration and consequential low spark energy, is incompatible with the week dir/fuel mixtures used in modern cars. Because of this most stanufacturers have abandoned capacitive discharge in favour of the chasper inductive system with it's low power but very long duration spark which guarantees that sconer or later the fuel will ignits. However, a spark lasting 2000µS at 2000 rev/min. spans 24 degrees and 'leter' could meen the actual fuel lightion point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DESCHARGE system. This gives ignition of the meakest mixtures with the minimum of timing delay and veriation for a smooth efficient angine.

- SUPER POWER DISCHARGE CIRCUIT A brand new technique prevents energy being reflected back to the storage capacitor, giving 3% times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weekest fuel mixtures without the ignition delay associated with lower power "long burn" inductive syste
- HIGH EFFICIENCY INVERTER A high power, regulated inverte arful enough to sture twice the provides a 370 volt energy source - pow energy of other designs and regulated to provide sufficient output even with a bettery down to 4 volts.
- PRECISION SPARK TIMING CIRCUIT This circuit removes all meanted signals caused by contact volt drop, contact shuffle, contact bounce, and automal transients which, in many designs, can cause timing errors or demaping un timed spartis. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level - just sufficient to keep the contacts clean.

YPICAL SPECIFICATION	TOTAL ENERGY DISCHARGE	CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY (STORED ENERGY)	36 mJ 136 mJ	10 mJ 65 mJ
SPARK DURATION	500 pS	160 -5
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD SOPF + 500 KC EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µ\$	34 00

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

		Telex 291429	
ALUMINIUM BOXES:	BLACK PLASTIC BOXES	SEMICON	DUCTORS
17 5 75a7 50a1 50a 11 2010 5a2 10000 CD 10	Ball-Brun, S22	We of course carry a full range o	I transistors, diodes, CMOS, TTI
9-4+2 25+1 50+ (101 8+57 2+28 1mm)	11/a Zis Zinnen	Linears, Triacs, Thyristors and ot	her devices but lack space to prin
10 445 25a1 50m (101 6a123 4a30 5mmt11.13	Tibelbelben	long boring lists. Suffice to say w	we will beat most of our compet
17 bebefen (BR beld belli demit	17th SObelGaust	tors on price, availability and qual	ity of product.
13 Santa Jin (152 da 101 Sarte Bente C1.30		I ne tollowing are available in el	normous quantity, generous trad
14 2min.2m. (177 8x127 8x18 @mmi	BLUE REXINE COVERED	BC184L - BUY89C - BER87 -	21X342(000) - 21X542(000)
The State State of the State of	RET Set Ma 2 Min. (752 4:114 2:53 Mineri (1.55	BY208, Our price 2.00p -	2N3373, Our price 1.80p
117 Hard, Stadam (254 durt 14 Janie James	RB2 Befelber (200 2x127 Gullb 2mm) (2 52	74LS Se	ries TTL
14 tänlisten 1206 het27 dis 26 Januari. (2.53	104 11adarlin (278.4a192 4a101 5mm)	The following numbers are held in	n quantity. Maximum savings.
	RBS 1147 Stad Store (278 de 185 Se 114 Janua) (2.88	102 103 221 269 272	. /3/5/6,1381/0.
		Standard TTL	4 30 235
DEL	VC	7401 02 06 05 15	. 20 25 75 86 123
RED	415	452.	
CALENCE AL		Heetsinks	
Omron Verley Siemens etc. 21	0.00	Hedpoint TV4 (for TU-220 peckage	15p en discount on any
4PCO	100p Bases 20p		and a second of the anacount on dry
		CONNE	CTORS
UBMIN POWER, 5A contacts, sm	all physical size, 4PCO	RFCONNECTORS	MAINS CONNECTORS
	100p, bases 25p	BNC Plug (50A or 75A) 50p	US pattern 2 pin flat plugs
	d 11-Bin 2 and 2 BCO homes with	BNC Line socket	sockets, line sockets all 20p ea
Amp contact rations Ry Schra	ch Bar Omron etc.	Electer Afric	LEC EUropiugs
the second second second	Only 2.000 m	SMF 450	Bulain 3 pin 6 Amo plug and
	- 4.63	PL259 Plug 400	free socket
ETTER LOW PHOPILE (Type AZS	and 6)	Reducer	Cannon LNE latching mains free
ist in, a large quantity or that par	these at a fraction of list area in	SO239 Flange Chassis socket	socket
to ratching types, we can other	accompany full data supplied on	40p	Chassis mounting plugs 1.50
quest. Send SAF or ring for list	engemends. Fon oare supplied on	PL258 Double socket	EDGE CONNECTORS (AL
dente office on the or the office		PL259 to BNC (male) adaptor	GOLD PLATEDI
IL Holays	0.1.1.00	PET100 churce	18 way no
	Uniy 1.00p ea	PET100 Chessis socket 500	22 way 1.0
		N-Type Plugs (Amphenol)	2x22 way 1.5
	OUEO	N-Type Chassis sockets (SHF	0.1 pitch
SWIT	CHES	Amphenol)	24 way
Energy offe	and the second second	MULTIWAY CONNECTORS	37 way
Speciel one	rs include.	We carry good stocks of new	40 way
LUMINATED	2. Since and the second sec	and bargain priced used D-	2 50 2x 78 way 22 00 78 We
con 01-800 push fit 2PCO switch	hes. Separate bulb contacts (TVe	from 9 to 50 way	2.00 EX/0 HOT 4.00
inger on rated contacts, lenses t	Only 1 50n	Example:	
ATCHING INDICATORS	500 ea	New D15 socket	
tention: Licon stocks rapidly	diminishing - BUY NOW and	New D9 plug	
AVE		AUDIO CONNECTORS	
		We stock all types of jack, phone	e and DIN plugs too numerous t
JCKEN		list, phone for details in professio	onal types we have:
ST. Bed push fit 28-20mm sta	Hard type	duty nickel plated sized with cable	clamp in 2, 3, 4, 5 and 6 way
ST. Amber, push fit 14:30mm	tenderd type		Only £1.00 per p
the second s		Switchcraft XLR Series, the profe-	ssionals choice
DTARY		A34M 3 pin free plug	
12W, 2P6W, 3P4W Lortin type	50p es.	A3F 3 pin free skt	1.82
TTW Elma gold plated adjustabl	e. High quality	D3F 3 pin chassis plug	1.10
1000		FUSES 20mm OR To AS 100 11	Winch OR 70 A/S 120 Minute
rollet, arm or standard	400 41	eech.	the set of the set of the set of
roller, arm or standard	50p ea	HOLDERS: 20mm P/M 35p, Char	ssis mounting 10p. 1% Inch Pan
		mounting 40p. C/M 10p. 1 inch P	/M 250,
	and a second second second	MAINS FILTERS: Computer grad	de but ideal for HiFi, etc. 8 or 1
DPDT; 5=DPDT, gold contacts, b	ERG & CTS, only 80p	Amp.	(
		SLOW MOTORS: Mains of 1154	operation, great for timing pu
dustrial type 2 Pole 12A/600V	£1.50	NEON BULRS: We have very larg	e quantities in stock
8 Pole 10A/380V/	3.00	QI BULBS: 50W 12V projector typ	e, to clear
10 Pole 12A/600V	3.00	LOCTITE: Penetrating adhesive. It	really sticks. SOML for only.
		DIGITAL MULTIMETERS: Supe	rb value, copy of profession
CAF	SLE	model. Full ranges end specs.	OUR PRICE EA
ar cable stock must be seen to h	e believed, so it is impossible to	INKOU METERS: Tough depend	Cable Multimeter ZUK/V sens. Fu
I I AU ELECTRICIANS DUY	our 2.5mm2 for only CE/100 and	CAR SPEAKERS 3 way 20 war	shell mounting 4" Rass drive
5mm2 only 25/100. VIDEO CABL	E. UR75 750 Coax Mil spec only	2%" Midrange 1" Tweeter In	nternel passive crossover Gra
WIO BELDEN CABLE. Hook	ip wite in 24, 20 and 18 AWG	sound £12/pr. PLUS 4" driver B	ALL SPEAKERS, real 20W output
per prices MAINS CABLE in 0.	5mm", 0.75mm" 1mm", 1.5mm".	crisp, clean sound, a genuine bar	gain at
BIBRON CARLE Motor	Tor TOOM. MULTICOMES of all	SOLDER: 60/40 185WG, 500gm E	8.50 250gm £3.50
OWNER THOOLIN LABLE. WY YO GOL	L WITH THOIL SHE TOP YOU'S HT.	IRONS: Antex X25 £4.50 Antex C	15 £4.50, 12V 25W long £6.

ETI APRIL 1982

C.T.ELECTRONICS (ACTON) LTD

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone. 01-994 6275

Telex 291429

STABILISED POWER SUPPLIES

FARNELL A15: 210/240V 1P. Dual Op. 12-17v per rail at 100mA. Remote sensing, current limit protection. (164x130x38mm), with manual. £12.

FARNELL 7/38C: 120/240V 1P. Adjustable current limit. Remote sensing. (188x96x93mm.) Two versions available: 15V at 2A or 30V

at 1A, £15 es. COUTANT OA2: Op. amp, psu, 120/240V IP. Dual Op. 12-15v at 100mA. (138x80x45mm.) £12 es. or 2 for £22.

BRANDENBURG Photomultiplier PSU, 19in, rack mounting. Metered, current limit protection, 374 300V-1KV at 5mA 376 660V-1K6V at 10mA

375 500V-1K5V at 6mA.

Ali models £40. PIONEER MAGNETICS POWER SUPPLIES

5V 150 amp, output Input 115 vac. (Switchmode) Price (120 each.

Various other makes of power supplies in stock. Please send for lists. S.A.E. please.

D TO A CONVERTERS 15MHz, 8 BIT

By Micro Consultants Ltd. 500 cable drive op. Linearity 0.25%, max. 0.125% typ. Settling time. 2V step 70nS typ. 2MV step 50nS colour television transmission standard. Diff. gain 0.5% diff. phase shift 0.5° types red 802 and MC2208/8. Unused. Ex-maker's pack SPECIAL OFFER PRICE: 620

NEW IN STOCK

A range of high quality transformers SPECIALLY WOUND for us, By buying direct we can offer these superb SPLIT PRIMARY & SECONDARY transformers at highly competitive prices.

OVA	0-12, 0-12 0-15, 0-15 2, 20		0-12V. 0-12V
12VA	0-4V5. 0-4V5 0-6V, 0-6V 0-9V, 0-9V	50VA	0-20V, 0-20V 0-6V, 0-6V 0-9V, 0-9V
	0-12V, 0-12V		0-12V, 0-12V
20VA	0-4V5 0-4V5	120VA	0-30V, 0-30V 0-40V, 0-40V

CASED AUTO TRANSFORMERS

240V Cable Input, American outliet socket.

Rating Pri	Ce 750VA	623 50
300VA (13	00 1000VA	(27.00
500VA	00 1500VA £36.00	
Other Transformers	1 12VA	
1.2VA. 6-0-6. 9-0-9. 12-0-12	0-12. 0-12	2 960
	14 18VA	
1.5VA	9-0-9	2 640
12V	Do 24VA	
15V	00 12-0-12	3.360
2.4VA	12V	4 840
12-0-12	AVOE 08	
24V(pcb)	00 15-0-15	1.62p
AVA	36VA	
5-0-5	25 909	4 700
6VA	SOVA	
24	50 0-2-4-6-8 10	6 00p

VERO PRODUCTS

Veroboard 0.1 Copper	ADI	ple proto board	\$ 4.00p
2 1/2x346	70p Ver	o boxes - 2 to	ne arev/white
21/2=5	800 pia	stic boxes	
14ax 34a	800 412	211	1 990
Wax5	900 417	x156	2 220
Vax 17 2	400 414	#2\6#1\6	2 610
Van 17	150 714	#4 46 x 2 46	1 750
7x17	200 714	Var214 Jaliofro	ot)
	Ver	o ARS Black PL	astic Boxes
A protect	800 A14	w144-14	780
	780 784	14x214	1.420
The Public of the State of the	Var	00:00 450/10	a Stand of
V-Q Board 1	300	1100 Teach cul	Bara 61 18a
DIP Board (113x156mm)	260 400	N TOOL TYBER CUI	AMAR CITED
S DIP Board (100x 160mm)			
	00-		

4 MILLION I.T.T. ELECTROLYTICS NEW AND BOXED NOW IN STOCK

EN 1212 AXIAL EN 1235 RADIAL

The whole range available at unbeatable prices. Send for list.

5 million Disc Ceramics In stock. Ceramic plate. Multi-layer ceramic, Low voltage discs. Monolithics. Ceramics. High voltage discs. Subminiature plate, epoxy cased. Send for lists or please phone for details.

MULLARD: Series 106 Computer grade electrolytics 10.000uF at 16V. Brand new and boxed. 390 SPRAGUE: Series 360 Computer grade electrolytics 3,300 at 40V. Brand new and bosed. 350 ... SIEMENS: Procond Radial Polyester Film Capacitors, 104F at 63V. Brand new

Only 40p Quantity available

RESISTORS - PRESETS - POTS

CARBON FILM YeW from IRQ to 12M Only £1/100 or £5/1000 METAL OXIDE: TR4, TR5, TR6, TR8 in £24 range, by Electrosil or 2% 1% Save EEEs on manufacturer's prices A 10 69

WIREWOUND: We specialise in Welwyn Vitreous Enamelled W-series types in 21/W to 12 Watt. Also a good selection of HSA type clad power resistors and TV dropper replacement sections

HIGH STABILITY: 0.1% Tolerance Resistors for instrumentation purposes. By Filmet or Welwyn JK, 10K, 30K, 1M. "Only 30p ea. PRESETS: Skeleton and enclosed, horizontal or vertical Piher qual-ity presets, Range from 100P to 5M. Popular PT10 size 10p each AND GREAT DISCOUNTS ON QUANTITY.

CERMET PRESETS. Top quality presets, good range stocked

Only 15p ea MULTITURN PRESETS: %" and 1%" Bourns type Only 50p each. SPECIALI 100K 15 turn %". Only 20p each.

SWITCHED POTS. Push switch pots from AB. In 22K lin and 100K lin. Switch independent of pot action 300 ...

RESISTOR NETWORKS Large range in DIL & SIL packages by Beckman & AB. Send SAE or phone for list. WELWYN STRAIN GAUGE. (Precision Micro-Measurements).

Micro-Measurements). Romulus Michegan type MA 09-50084-350. Our price £1.25 ea. List price £3.85 Large quantities available.

WE PURCHASE

Surplus component stocks, redundant materials, obsolete computers, for cash.

We also collect - distance no object. Just call:

C. T. Electronics (Acton) Ltd.

267 & 270 Acton Lane, London W4 5DG Telephone 01-747 1555: 01-994 6275.

Telex 291429

This advertisement is marrie of our excess stucid-adding. We also have excellent stress of sector order to a marrie caldre-etc. etc. For further details send for nor lists and retail providationer phone or visit our shop. All processes esclasse of VAT fand P&P. Minimum Mail Order (5 - P&P + VAT. Government departments, schools, colleges, traite and export well once

1.10 am 6 am ----CONTINUES.

ROBOT MOTOR CONTROL

This month we feature a control board for last month's motor driving board. This is part 2 in a series of DIY robot modules — collect them all! Design and development by Rory Holmes.



In this second part of the series on the ETI intelligent programmable mobile we shall describe the design of an analogue pulse width modulator for controlling the motor driver stage featured last month. We shall also take a brief look at some of the modules being offered later in the series which can be added in stages to enhance the motorised vehicle. The intention is to build up to a complete computerised mobile.

A lot of flexibility has been allowed for in the actual use and configuration of the modules, as we are well aware that constructors interested in this type of project have firm ideas of their own on the final form and capabilities of their mobile. Construction and interconnection details for all the modules we are presenting will be given along with guidelines to a range of applications.

The facilities we have planned for the mobile will continue with the digital motor control and an on-board programmable computer for overall control of other modules. A lightweight manipulator arm complete with teaching arm has also been designed, for mounting on the front of the mobile, it is powered by four radio control servo motors and the electronics interface between the servos and computer will be described along with details of the arm mechanics. Optical proximity detectors for object sensing, and infra-red tachogenerators for speed sensing will also be featured on the ETI mobile.

It is hoped that the designs will also prove useful as stand-alone modules for individual use in other applications. Optical proximity detectors, for example, have numerous applications in batch counting, limit sensing, detection, alarms and so on

The digital pulse width modulator in next month's issue will find many uses in the control of analogue functions, how about a computer interfaced to a pulse width modulated optical data link, for analogue information transmission? Our version will control two pulse width modulated channels, with a resolution of one part in 256, via an eight bit data port modulation being achieved solely by logic to satisfy the all-digital purists.

Optical Proximity Detectors

These have been designed as small independent units with as much in-built versatility as possible. The circuitry is housed in a short length of aluminium tube axially aligned in the detector direction, with three external connecting points, ground, positive supply, and an open collector digital output. A number of detectors can thus be easily mounted in strategic locations. All circuit operating parameters are independent of the supply voltage, which can be anywhere between 5 and 35 V at a current of 20 mA.

The proximity switch works on the principle of transmitting and detecting a modulated infra-red beam. The infrared transmitter receives 1 A peak current pulses, of 10 uS duration, with a modulation frequency of 1 kHz. The 100:1 duty-factor thus achieved allows high currents to be used to increase the detection range, while reducing the average supply current to only 10 mA.

The sensor can be set by a preset pot, accessible through a small hole, to detect an object at any distance in the range 1 cm to 35 cm.

A small amount of hysteresis is Introduced into this switching distance to ensure clean switching thresholds and stability of the output signal. The use of tuned detector amplifiers provides excellent infra red Interference rejection.

Analogue Speed Control

The analogue speed control has

PROJECT

FORWARD/REVERSE

PULSE WIDTH

COLLECTOR OF 03

COLLECTOR OF 04



·12



Fig. 3. How PWM waveforms may be generated using a comparator.

SON DUTY GYCLI

Fig. 1 Various voltages associated with the circuitry around Q3. The control voltage is measured at point A in Fig. 5.



Fig. 2 PWM motor driving waveforms for last month's circuit.

been devised for manual control of the main traction motors; it provides two pulse width modulated signals suitable for the motor driver amplifier.

The circuit is designed to provide a linear control-voltage-to-pulse-width relationship for greater flexibility in application, and to simplify the addition of speed feedback velocity control.

The modulator can be built either single or dual, and the manual control section, if not required, is easily omitted. Speed control is achieved via two remote potentiometers, allowing speed to be set in either forward or reverse directions Independently for each traction drive.

Since both motors are controlled via switching amplifiers from the same battery supply, it is important to reduce the peak currents that are drawn. This can be achieved by offsetting the phase of the switching waveforms relative to each other, such that at 50% duty cycle modulation, power

BUYLINES.

No problems here with any of the components specified — most mall order companles who advertise in the magazine will be able to supply everything. We can supply the PCB — see page 44 for details. Fig. 4 The waveforms needed by our motor driver board, published last month. (Q3 and Q4 refer to last month's circuit.)

1000 41

An internal view of the driver unit showing the interwiring to the bridge rectifier of one channel. Constructional details for the pulse width modulator will appear next month.

HOW IT WORKS_

The circuit for the dual analogue pulse width modulator is shown in Fig.5; it will be seen that each channel is identical with the exception of the circuitry around the CMOS gates IC1 and IC4. As described earlier the two switching waveforms must be the same frequency and synchronized 180° out of phase, to distribute the motor current peaks more evenly through the cycle. This is achieved by synchronizing both pulse generators to a master clock based around IC1a and b. A 20 kHz square wave is generated by this conventional astable arrangement and its frequency, set by R1 and C1, is fairly independent of supply variations.

The output of IC1d at pin 6 provides a buffered square wave in the same phase as the output on pin 10 of IC1b. C2 and R3 differentiate the positive-going edge of the square wave to produce a very short logic low pulse at the output of Schmitt inverter gate IC1c. In similar fashion C9 and R16 produce a logic high pulse coinciding with the negative-going square wave edge. IC4b further inverts this signal to a logic low pulse. Two separate trains of 500 nS negative-going pulses are thus provided in the correct phase relationship for resetting the charging cycle of two sawtooth oscillators as described below.

The pulse width modulators are iden-

tical from here on and we shall refer to the topmost circuit for description. Voltage controlled pulse width modulation is, in principle, very simple; a ramp waveform (sawtooth) is applied to one input of a comparator and the modulation voltage to be encoded is applied to the other, producing the required PWM squarewave at the comparator output. Figure 3 illustrates this operation.

Due to the design requirement of a linear relationship between control voltage and pulse width, a constant current source formed from Q2 is used to generate the linear ramp waveform. LED1 and the baseemitter junction of Q2 are forward blased by R6 and together define a temperaturecompensated voltage across R7 which in turn defines a constant emitter and collector current of about 1 mA. C3 is charged up negatively from this current, until the negative-going reset pulse arrives from inverter IC1c. This pulse turns Q1 hard on for very short period (500 nS), during which C3 is completely discharged, taking the ramp voltage back to +8 V. This process repeats at the clock frequency of 20 kHz, providing a negative-going sawtooth of about 3 V peak-to-peak referenced to the +8 V rail.

IC3b, the comparator used to perform the modulation, is an LF353 dual op-amp, chosen for its large bandwidth and high slew-rate. The inverting terminal on pin 2 is fed from the ramp waveform, while the noninverting terminal is fed from op-amp IC3a, an inverting amplifier configured to sum control voltage inputs relative to a 4 V reference.

The potential divider R11 and R12 provides the 4 V reference to the non-Inverting terminal of IC3a, and the control voltage applied to R13 at point A is summed relative to the 4 V. An offset voltage set by PR1 is also summed at the Inverting terminal of IC3a, and is used to bring the control voltage into the correct operating range and for setting a deadband region on the manual control pot RV1.

The output of op-amp IC3b (and indeed most others) will not swing to the full supply rail voltages, so the inverter gate IC1e is used to buffer the square wave to full CMOS logic levels.

The manual control system included in this circuit enables a single potentiometer to control the speed in both forward and reverse directions. When the pot is at centre travel, and for a certain deadband around this point, the motor must be stopped and no switching pulses should occur (ie the PWM signal is continuously low). As the pot is turned in either direction from its midpoint, the pulse width should in-



31

PROJECT : Robot Motor Control Part 2

crease and this requires a positive-going input voltage to the summing amplifier IC3a. The forward/reverse logic level should also change state as the pot moves through its midpoint. Q3 provides the necessary voltage transfer function from the pot RV1 to the control voltage summing amplifier, as explained graphically in Fig. 1.

The emitter and collector resistors of Q3 are both equal and the base voltage is taken directly from the slider of the manual control pot RV1. The output voltage is taken from the collector of Q3 to feed the summing amplifier, and will be held at +8 V via R9 when Q3 is switched off. As the slider of RV1 moves toward the centre of travel, the base voltage rises, slowly turning on Q3 and lowering the collector voltage.

on Q3 and lowering the collector voltage. When Q3 is turned hard on as RV1 reaches its mid-point, R9 and 10 will form a potential divider giving 4 V as the minimum control voltage. Further increase of base voltage can now only increase the emitter and collector voltages back up to the positive rail, reaching a maximum at one V_{be} drop from the +8 V rall.

During the above process the voltage on the emitter of Q3 rises from zero to the same maximum voltage, and is fed to the inverting terminal of IC2, a CA3140 used as a comparator. The other comparator input receives 4 V derived from the potential

will be switched alternately to each motor. This spreads the current peaks more evenly over the switching cycle. divider R11 and R12. This provides the required forward/reverse signal that corresponds to each half of the control pot. Inverter gate IC1f buffers the output of IC2.

C7 and C8 provide supply decoupling for both channels, while C5 and C6 provide further smoothing for the 8 V zener regulator formed by R16 and ZD1. This 8 V reference rail is used for two reasons; firstly to allow for fluctuation in the 12 V battery power supply that would otherwise affect the output pulse width, and secondly to ensure that the op-amp supply voltage is well above the maximum input voltage.

The resistor marked as Rx in the circuit shows where a speed feedback voltage will be added to the controller to close the velocity control loop. An infra-red tachometer module to directly sense the traction speed will be described later in the series.

If the manual control input is not required, the components associated with this can be simply omitted (ie RV1, R8, R9, R10, C4, Q3, IC2 and their equivalents in the other channel). Control voltages may now be fed to the unconnected end of R13, where a variation of 3 V, set by PR1 to be anywhere in the range 0 V to 8 V, will provide 100% control of the output pulse width. Forward/reverse switching must also be applied to the input of IC1f on pin 3.

Construction and setting up with interconnection details for the motor driver will be described next month.

PARTS LIST								
Resistors (all %W, 5%)								
R1	100k							
R2	15k							
R3,6,17,20	2k7							
R4,18	470R							
R5,7,8,19,								
21,22	1k0							
R9,10,23,24	22k							
R11,12,25,26	10k							
R13,15,27,29 1M0								
R14,28	330k							
R16,29	150R							
Potentiomete	ers							
RV1,2	10k linear							
PR1,2	10k linear miniature							
horizontal preset								
Capacitors								
1020	100 ceramic							
62,7	150 polyasheaste							
CA 11	2u2 25 V tantalum							
1 C5 7 12	100n certanic							
66 13	220u 16 V avial electrolytic							
CB	100u 25 V axial electrolytic							
	tood as it and circuity ite							
Semiconductors								
IC1	40106B							
IC2,5	CA3140							
IC 3,6	LF353							
IC4	4093B							
Q1,4	8C214L							
Q2,3,5,6	BC184L							
LED1,2	red LED							
ZD1,2	8V2 400 mW zener diode							
Miscellanous PCB (see Buylines)								



ETI

RONICS LTD Tel: 01 452 0161

CRICKLEWOOD is a new name in electronics, but CRICKLEWOOD has been the home of electronic components since the 1960s, originally under a different name which many of you will be familier with, but as they are still trading it would be unethical to mention their name. TRY OUR SERVICE & WE HOPE YOU WILL BE DELIGHTED!

Our phones are always manned and your written queries always receive a reply.

	T-COP		Variation.	1 45		10	VANA	-	L.M. STAR		increase .		-	1	htt	9.40			10.017 8.0	27			Plant Angel
	12		No Called				Ven Halls	2	Children .	-	Collars.	1.00	104 Mar	8.10	2010	1	A DECEMBER	111	None and		2 2	1 00	EP SHEET AL.
	123	1	THE LOCAL	1	10 and 100				LACCOMP.		No Sector	1.00	TDAJER	-		0.00	74.5373		7-12-19-10 - 2 - 10 	121 1		1 H	THE PARTY OF
2	Visition of	2	The party of	1.0	Manuf shad a felte		111.1 100 111.1 100		1. Margan	13		100	"DAJER	1.10				1		4.5		12	
	210.00	-	11.3483	15			WAY MENT	-	L. Martinetters	-		6.00	"DAJEN		Territy		No. 5300	13	10,000	au 1	10 E J	1	-0-0 00.400
		2	Con Miles	1	122		WALFT OF CAR			1.00		5 12	The set	3.64	Namps Tel:00	7.0	10.0300	1.0	10.000 LA		No. 8271 No. 8734	1 10	-
	Same -	1	10.310		Property	-	Sanata -	1.8				1 1	TLOOP	22	Turing .	836	14,5300	12	Salaria a d		10 0.23 76 0.23	12	Marte other and
1		10	Stranger I		Designation of	1.00	ALC: N		LARPITE	1	1007	1.10	7,000	1	14100			12	0.0001		60 670 10 10 10	1.70	(i) plays installed
	and the state	-		12	Bry Max		a start		1000171	1.00	PLL BA	2.00	TLAN	5.00	1427	110	10.00	18			10 A 10 A	12	Page plane
	(*************************************		Thursday,	Ē	6717b	100			-	1.0	PLL BOA	1	LA NIME	1.00	76.5	m	Pas Berl	1E		COMPLETE OF	Ca CAU Bita	38	Surgerin .
	Frans -		-	1.2	Stands City		DEPENDAN NEWTON		L'AND THE .	1.4	SAD STREAM	10	UPCORCE .	1.00	Tes. Anno			18		Mart P	20 AV	3.70	Annual International
	77 = 1,00 77 = 300		The little	- 10	8,34 Sant 2 4 479	-	1700-1700			i Ven	1.00	12	Statistics.		Sec. Mar	12		L.			8. CT	6 CR	and the states of
	T to just	-	The set	1	1.3 1000	-	1 JULZ JUL		Colleges -		in the second	12	2.4					1.00			Bi Alba	1.00	The second second
	Tates .	100	1000 7		1 In Lorent	-	E TREDOPT IS	Ē]	CARDON DATE	10	SLATES.	1.0	1-2		10.40	1	200 17	-				32	anter freiten
		Up Mp	Contraction of		2.5 0000		1.00000-7-0	2	MITTAN	10			275.30	-	16.11	1		-	第二 元 二 元 二 二		100 0000	12	THE IS
	T all a		(nation) (nation)	- 19	「たち」	1.10	1 Junio (* 134)	2	CARDING IN B	-	SAAPS.	10	-	110	213		President President	1			의 말	12	
1	and the second			- 2	the site and	-	1 Jandow Sta	2	Contraction of			TE		00	14,621	1		1		The other		12	TTTEL P
	Bearing .	2					1.70000-210	2	.010		S. Server			1	4.6.0	-	140.0	1.00		Memohies	T Start	12	TUPE A
1	Parent and	-	10(2:02)	-		2	1 Juncovite	-		13		10			10,300	14		-		1100	and Streams		
1	Banatina G	5	Saula IS			N.	A Junit Gal. Jun	3		in		10			200. 3.00 201. 5.00		NULL N	1.00		1000.0	B VILLET	1.0	Quality 2
1		1	ACCESSION OF		304 6492,63 805	1.36	E JUNE DA JUN	2		18	P. State	- 19m	1.1	2	PR. 68	1	THE PARTY OF	2.00			and pressions	12	CONTRACTOR
			10 10 10	-	ton Pas, D	-	I THE DAJOR	2	L BASPINS	10		10		22	No. 10		10010			in an	IN TAS		
	in the second	-	10134	aller .	Contraction of the		A SHECOME	2	L'ALER AN	1	Sector of	1		3	No. 55	1		1.00	4722 1 10	12 1			Title of La
-	22_	2	-	1.00	2 7 1 1		E JERLOP INJ	21	LASSING .	1.0	201.70.220 \$41.70.720		122	-	Peter La	15			4C34 5.67		- Pasties		-
		15	Times -		100	1.0	C JURGOW Sea	21	Line search	1.0	Statistics of the second se	12			Tel D	E		10		1996 1 S	a man	-	a many to
	Turnet .	1	AA30	10	April Pas. de	-	C SHEEPOPPER	21	L COTTERNO		Section of		NOT THE	R	The Sta	1	100-07	1.		50% 5 01 10 0	10 10 10 10 10 10 10 10 10 10 10 10 10 1	R	1.
ł			AATE		(2) when	-					Spatt .	10			1.00		NUMPERS	1.00		0046 L			
	Young E	5	ANT	-	THE THY	1.60	COLLER OF		Contraction of the	1.01	VANID	12	1430	-	Per. 105	-	1010	1.00	-	Tentes 2		B	A ALIMAN A
I	9 - 884	· .			ELECTRO	INCE					TATES .	18			Tel. and		100,000			41.50			1.1
1	1.2		BA * 10		Trans and		AP1 188		La Carl Hanna	-	9479-19	10			Paul State	1.00	146.39	:				-	a martine a d
1	TICHEN	-	6.4 *30 6.4 *42				Art 1278			E	-	12		5	14.50	1.00	THE PLANE			2840			a contrary
I	44 14 MIC	17	8.4.144 8.4.195	2		1.00	A+3-0012		LAST METER	1	TAATE				144,3 140 744,3 113		THE OWNER STREET	12		01. 10CH 071	Tana In		1. mar. 1.
1			8-4-1985 8-4-1982		07438	4,24	CARD I		LAPY	-	S ALANA	10			Res aver	10	THE R. LEWIS	12	10	10 pm 8.		21	2 bellan. I t
1	TICTIMA	-	84.383	Star Mari	100	12		E.	All the second	.3		1E			Teland	-	CF admin	1.78		A Designation			in ones is
L			BAJ-7		brank .	8.83			LM CB	문	-	15			10,110		Aller TO I			COMPANY	-	Tel.	Corante Inter III
T			BAD'S		BARNER .	4.10	CARTE		L ST STORE			12	121		2.110	27.0	748476 1			ADURAN B			
1	75 104	24	BATTS .	1	COM 13	-		Ĕ	LasterCars	-	TAANTA .	10		3	74.513 74.513		Participa	0.00		ADCIDIO IN		-	AFCER 18
1	14 15 UR		6.4% (0) 6.4.6%	-		-				10	Tant's	1.0			74,9145		2000	1.5		6+5 33% 12	Contraction of the		199
т	1 C 1000		BATE .	The Real	0010	10	A BOR	-	LAPS MORE		140-0		31273			1.0		121	5	201-107 B			Pe
ł		-	BA THE		LUBA	-	CARD I	E.	Lante States	1	TRADI	1		5	214			1			and the second second		
1	- Transform				Lange -	-	CARR I			1.00	TRA SER	10				1	10.00	13		1212		21	
ł					Lon L	-	CVANERS 3	SI		12	To-Angel				5 .57	2		10		UCODI 3.	A light in	51	PCCM 10
I				3	L.D.B.A.	-	CARDA I			1.00	TRADE	1.00		E			Name I	1.5				21	
1	Bar 201-46 (7)			1	LOUTO	2	(Aller)			18		1.00			20	12	-			Salarian a		ΞI	PC P 201 5 4
ł	1.7 erry pros		0 31		Lines	2	(Aller I			1.2	The little	12			Par. 5 - 60	- 22	1	18		100.0037 23 100.00700 14	1.9 Amp 71	. 1	
L			8191962	1.20		1.0	100			13	TEAL D	1Ê.			10.010	10	1 841 978			1 222 2			
т			CT THE		60.00	13	CARE		Line second	븮	Thates .	12		Ξ.	100		-	12		Construction of the	Tipes -	1.00	Print a st
F	and the state of the		8 - 325	1.0	1001	12	SALE I				TRADER .	1.81 1.82			6.1 T) 6. N		196	2.00	1	2332	in a state	: 1	P-100 2 0
1	TV Thurborn				1.64					2.77	TRADIC.	8.87	1		5 41	1.00	3.0	10	-uniterers in the	ALC: N			
ł	17 Sec. 6000 1		BARRAL PR		10400		i and			13	TRADITIO	10	No will be	E	20 0 C	1.00	10.00	121	THE SALE	BAANDER B			P. 600 4 1
	Contraction				2000	12		-	L SECTOR FREE	1	1 A44 - 68 -	-	20110	-	-	1	HE Canton	170	dia . Rea	BAASSID 10		1.00	
F	177 10 1	-		1.0				-	-	1.	TRACT'S	1 10	Deres.	2		-	Per al	R	AL COLOS	Annual B	Contraction of	1 23	-
Ŀ	17131		-		10.00		CA111		- NETWOOR		TRA TIBAG	1.07	Parts .	Ř.	212		ne ·			THOMAS B			and Real and
Ł	Tanaca -			1	1.0	ie I	SHEEL I	21			TRA TRO	14	10131	E	1		Pet J	E		1 ACRES 1	A LANDAR		Law logal
	California a	-	7730	-	520	15	(Alian		No.	1	TRA TELS	8.90 Billy	10-31	2	S.D.E	-	14.10	-		C	In the second		
	California.		144.1	3	20.01		Ser.		L BUTTERS S	1	TRADE	F	Torgan I	2	No. 6340		22	10		m.m. 1	the same	-	
	- CERE - 3A	-	1772	E	P.L.F.M.	1.00	SAME I		Sec.	16	PRAB	1	Participant -	-	Pa. 5345		Dec m	1.36	-		N and a	3	the star and
			04 4	1	1410	ie l	SAME 1	-	-	10	TO-ARE	12	Panal	1	14.124	1	HCID	1.10		11.000 t.) 11.000 t.)	2.5	-	BANK BELL
1	T-COURSE	-	O-mille	5		1	SAME I			15	PEARING	1.0	Do da	1	San Line	-	No. 10	LIS			A to A party		
	Canada (Bri	-	-Constant	-	10.01	-	SAME I	=	Sales Parts	12	TC A MIC	1 40	hunan	-	100	3	THE M	1.00		HOW	OORDER		And Property lies
1	-		200	The	1233	14	CAN'IN .		-	-	NCATTO .		113	-	Pray Lines	-	Ber the	1.00	1. Mail orde	r by return			
	INSTANCES	-00	Statement .	2	12.00		SALE I		L BEALERSON		T. And	3 464	Deres .	-	Carling .		Man -]	12	Access,	Barcleyce	d (Vise),	Ап	noncan Es
F	THE REAL	-	and the second s	-	21,400	1	PARTING I	F	Line Steel		TE Adda	-	Terma Terma	Photo:	20.00	1	C S	14	press: Pick	up phone	& quote n	um	ber or sen
1	and description	in	ALC: YOU	-		0	270	F	Ares Balles		PEA'S	1.00	Excess Partie	2	THE CARD	10		1.16	card numbe	r in post (not card) v	with.	expiry det
	and a characteristic for		Sector Sector		To be bring	-	-				122	1	No.	1.5	TA. LONG	15	Har ville	1.00	the Call in the	r passant	andre Or		S. Manda
1			E L	-			LC7135	- 22	, un trem		TCANE	12	Tendo Tendo	Salaria Galaria	1.10	2	No. 1 March 1	11	to Sabarde	personal		Part 1	- o minoride
	ninaz (10		E	VAL				3	1.00	TC ARE	10	Territo	-	Hand States	10	10,10	1 10	Please add	VAT at	15% 6 7	00	oto to a
Г	-		2 4000		the title	2	Sin I	100	33	10	T BAA VOID	1.00	Aurilian I	-	No. 6 (2)	12		1.00		0	rders		
	THE PARTY			-	The state	-	L'ENT	83-p		4.75	TO-A VERS	1.05	101 10 101 72	1.000	14. 5 APR	2.34	NC.	1.20		(More for I		da)	
	The state		-	-		-	UPIERS I	F	121	3.76	The was	10	Part På	1	No. A APP	3.81	Mail and	1 ph	Cr	ich lewood	Electroni	cs L	td
		-		-	Y-1	-	Landon		12140	10	7 Dan - 482	1	Terring		" the	1.00	Nacional Indiana	1	4	Cricklew	ood Broad	wa	V.
		1			-	-	LAPYNCH A		Sectory -	1 40	The star		Tax 27	1	2.12	10	HACENER !!			Londo	NW2 JET		
1	THE REAL	10		and a	BA P	-	Abenging wi	201	Brithell -		TRAJES	0.32	HINDS -	Sec.	THE OWNER	5 mg	Television in the	1 17		Tet O	492 0161		

ETI APRIL 1982

HOW TO SUCCEED IN THE ELECTRONICS BUSINESS:



ETI APRIL 1982

PROJECT

SOLID STATE REVERBUNIT

Where have all the spring lines gone? Gone to lesser projects in other magazines, that's where. Meanwhile we present this cheap, simple, but high-quality unit using solid state technology. Design by Charles Blakey.



A t last — a reverberation unit which is not a pseudo echo effect and does not suffer from the defects of spring line devices. The unit described below will interface with virtually any preamplified signal and is ideal for direct use with most musical instruments or for incorporating in the 'echo-send' line of mixers. The design has been made possible by a new 3328-stage bucket brigade device having six tapped delays and capable of producing a useful reverberation time of about three seconds.

Sound emitted in an enclosed space will be subjected to both simple and multiple reflections from internal surfaces. Since these surfaces are at varying distances, the time for these reflections to occur and then decay by absorption will vary. The effect is a build-up of sound known as reverberation. When playing a musical instrument in the home, small studio or some other venue, the decay time can be very small coupled with a high absorption loss; the result is a weak sound when compared to recorded music or to live music played in a large hall

Until now the only low-cost method of simulating acoustic reverberation has been the use of spring lines. These units, however, are prone to vibration, require a high

power consumption for effective driving and are prone to producing distorted resonant peaks. Furthermore it is not possible to adjust the reverberation time and in many instances a short reverberation can be very effective. Another option has been available for some years, namely, the use of bucket brigade devices to electronically delay signals. While claims have been made for reverberation effects based on these products, a realistic unit would require at least three dual 512-stage BBDs. such as the Reticon SAD1024A. The cost and complexity of the latter approach puts it beyond the reach of the average constructor.

Beyond The Pail

The reverberation unit utilises the MN3011, which is the latest in a series of bucket brigade devices for audio applications to come from National Panasonic. They are all fabricated in PMOS and for a start you can forget most of what you may have read about the disadvantages of PMOS BBDs. It is a fact that they are somewhat limited in clocking speed (10 kHz to 100 kHz) and also have a limited bandwidth, typically 10 to 12 kHz. The latter, however, is not usually a limitation since the bandwidth is often restricted by the desire for long delay times. What makes the series ideal for audio applications is their low insertion loss, low distortion and excellent signal-tonoise ratio and for the MN3011 the specified values are 0 dB, 0.4% and 76 dB respectively.

The IC is unusual in that it has 12 pins but is the length of a normal 18-pin package, the functional block diagram and pinout for the MN3011 is shown in Fig. 1. As is normal with such devices it requires two power supplies, Vop and Vcc, the former may be up to 18 V with respect to ground while Voc should be +1 V higher than Voo Bucket brigade, or charge coupled, devices are analogue shift registers which operate by sampling the input signal at a rate determined by an external clock. The signal level at the time of sampling is stored on an internal capacitor, this charge is then clocked down a series of capacitors by means of internal switches. The transfer process is accomplished by a dual clock whose outputs are in antiphase and so are alternately opening and closing adjacent switches. It will be apparent that the slower the clock speed the longer the delay. Since the devices operate at high clocking speeds the input signals are faithfully reproduced at the output.

The most interesting feature of the



Fig. 1 Pinout and internal layout of the MN3011. The centre three pins on each side of this 18 pin package are absent.

MN3011 is that it has six tapped delays and Fig. 1 shows the number of stages for each tapping. The tappings are not evenly spaced since otherwise the reverberant sound would have a distinct flutter. If the device was being clocked at 10 kHz then the delays from outputs one to six would be 19.8, 33.1. 59.7, 86.3, 139.5 and 166.4 milliseconds respectively. If these delay times are mutiplied by 0.33 then one obtains the equivalent room path length for one trip, ie the longest delay is equal to a room length of 55 metres (181 feet). Reverberation time is usually measured as the time taken for the power to decay to one millionth of its initial level (60 dB down). For the present design the time was measured for the output level to fall to one hundredth of its initial level (-40 dB) and at the longest delay this was found to be about three seconds.

Blocks 'n Clocks

The block diagram of the circuit for the reverberation unit is shown in Fig. 2. First there is the dual clock driver, which is another National Panasonic device, the MN3101. It has an oscillator, divider and wave form shaping and produces the dual clock pulses required by the MN3011. It reduces component count and is lower in cost than other alternatives, such as a 4007. A further advantage is that it also generates the required V_{CC} voltage.

The unit will operate satisfactorily



with any input signal greater than 280 mV RMS and higher input signals are attenuated by the input potentiometer. The signal is also reduced by half in amplifier A1 and inputs higher than 140 mV to the first filter are indicated by a LED peak detector circuit. Although the MN3011 will accept signal levels up to 780 mV before the distortion value stated earlier is exceeded, it will become apparent that the effect of reverberation can lead to reinforcement of signals and consequently this has to be allowed for. The only preset in the circuit is used to apply a bias voltage to the signal. The precise value of this voltage is not very critical in the current design and the object is to keep the signal at a level where it will not be distorted or clipped within the BBD.

The main problem with BBDs is the inability to completely cancel out the clock pulses and these can form audible cross products with the input signal. In order to prevent this foldover distortion, the bandwidth of the input signal should be limited to between a half and a third of the clock frequency. Filter F1 in Fig. 2 is a lowpass filter with a cut-off frequency of 3.6 kHz. This may seem rather low but in fact it is equivalent to the upper reverberation limit of most spring lines and the BBD scores in respect of low frequency responses since springs usually give rise to 'booming' below 100 Hz. The limited bandwidth is compensated by mixing the original signal with the reverberated signal at the output stage. The filtered signal goes to the MN3011 and the six output stages are summed to give a composite signal with different delay times. This signal is again filtered with a lowpass filter with a cut-off frequency of 3.6 kHz, to remove residual clock glitches, prior to mixing with the original signal at the output amplifier, A2.

The most important feature, however, is that the signal from the longest delay is returned, slightly attenuated, to the input and subjected to further delays. This is the reverberation effect and with the times given earlier the sound will simulate the effect of the first reaching a surface 55 metres away (assuming slowest clocking rate) and then being reflected back as well as being reflected from other surfaces closer than the 55 metre surface. The whole process is repeated until the original delayed signal and its reflections die away. In the meantime new signals are being recycled and the overall effect is a build-up of sound reverberation

Construction

The construction is very straightforward but the following precautions should be observed. First,



Fig. 2 Block diagram of the ETI Solid State Reverberation unit.

ETI APRIL 1982

PROJECT : Solid State Reverb

BUYLINES.

The PCB and a kit of components for the reverberation unit is available for £32.00, inclusive of postage and VAT, from Digisound Limited, 13 The Brooklands, Wrea Green, Preston, Lancs PR4 2NQ. The power supply may also be obtained for an inclusive price of £7.00. As the PCBs are copyright they will not be available from our PCB Service; however, the foil patterns are reproduced at the back of the magazine. National Panasonic do not distribute active components in the UK and the ICs may only be obtained from Digisound.



Fig. 4 Circuit dlagram of a suitable PSU for this project.



Fig. 3 Component overlay for the reverberation unit.

make sure you get the correct orientation of the ICs which are clearly shown on the component overlay. Second, the MN3011 is a CMOS device and with the advent of 'B' series devices we have all become rather careless as regards handling such ICs. For the MN3011, however, take the precaution of working on a grounded

PSU PARTS LIST_

Capacitors								
C1.2 470u 35 V PCB electrolytic								
C3,4 100n polyester								
C5,6 10u 35 V PCB electrolytic								
Semiconductors								
IC1 78L15								
IC2 79L15								
BR1 0A9 DIL type								
Miscellaneous PCB (see Buylines); PCB-mounting								
transformer (15-0-15, 6 VA); 500 mA mains fuse and chassis-mounting holder.								

PARTS LIST.

Resistors (All	% W 5% except where stated)	PR1	47k miniature horizontal			
82579						
12 22 22 29	100k	Canacitors				
D2 34	c1h	C1 2	100 35 V PCB electrolytic			
04	2200	CIA	100n polvester			
D4	11.3	65	22u 35 V PCB electrolytic			
R0 13 37 34	18.3	66	200 polyester			
NO, 12, 2/, 31	33R (7)	67 10 13	alon poryent			
R 10,27,37	4/K	30.22	220n nolveturene			
K11, 30	201	Ca 14 15	arop purystyretic			
R 14, 16, 16, 20,	P() 40/	21.24	2.2 62 V PCP electrolytic			
22,24	56k 1%	61,64	303 03 V PCD electrolytic			
R15	100k 1%	C9,11,12,				
R17	110k 1%	18,19	2n7 polystyrene			
R19	120k 1%	C16	2n2 polystyrene			
R21	130k 1%	C17	270p polystyrene			
R23	150k 196	C23	33p polystyrene			
R25	160k 196					
R 26	200k	Semiconduc	tors			
R28	82k	IC1	T1074			
R35	18k	IC2, 4	LM358			
R36	1k0	IC3	MN3011			
R38	36k	ICS	MN3101			
R40	68k	D1	1N4148			
		LED1	5 mm red LED			
Potentiomete	N/6	Miscellaneo	us			
RV1	100k logarithmic	SK1.2	mono jack sockets			
RV2	10k logarithmic	PCB (see Bu	vlines): IC sockets: case (Vero			
RV3	470k linear	order.no. 91-2673G).				

metal surface, such as a piece of aluminium foil, do not insert the IC with the power on and do not use a soldering iron on the PCB with the IC installed.

The PCB supplied with the kit has a ground plane to reduce interference from and to other electronic equipment as well as to reduce noise. This feature allows greater freedom in locating the unit, eg it does not have to be housed in a separate metal case. A ground plane comprises a metallized surface on the component side except for small areas around the holes for the components. Ensure that the component leads do not touch the ground plane - which is not difficult and preferably solder the resistors and axial capacitors in place with a thin piece of card between the component and the board so that the former are not in physical contact with the ground plane. After soldering the card is removed. The latter step is not essential. The one wire link must be made with insulated wire. The ground plane has to be connected to the 0 V line and some 15 mm from where the latter is connected to the PCB there is a hole marked 'join'. A piece of wire should be placed through this hole and soldered on both sides of the PCB.

The PCB has been laid out such that the BBD and clock are as far away as practical from the signal input and output. This separation should be maintained if the unit is housed in a box and all wiring should be kept as short and as neat as practical, with the audio connections being made with miniature screened cable.

The unit requires a ± 15 V power supply and the current consumption is a miserly 13 mA at ± 15 V and 9 mA on the -15 V line. If a separate power supply is required then a suitable PSU is shown in Fig. 4. A PCB-mounted transformer is preferred, and it should be mounted as far away from the BBD as practical. The photographs show the unit inside a Vero 'G' range case with internal dimensions of approximately 218 x 138 x 50 mm.

HOW IT WORKS

The input signal is attenuated by RV1 and also by the inverting amplifier built around IC1a which has a gain of about 0.5. From IC1a the signal goes three ways. A comparator built around IC1b forms a peak detector to indicate optimum signal level, while RV2 and R35 allow mixing of the original signal with the reverberated signal in the inverting amplifier configured around IC1c. The component values in this section are such that equal proportions of the two signals may be mixed. Finally the signal also passes to two active filters constructed around IC2 which have a 12 dB/octave roll-off for each stage and a cut-off frequency of 3.6 kHz.

From the above filter stages the signal passes into the MN3011 and the six delay outputs are summed by the resistor network formed by R14 to R25. Note that the shorter the delay, the less the attenuation. From the longest delay (pin 4) the signal goes via R25 back to the input of the filter and thus provides recycling of the delayed signal in order to generate a true reverberation effect. The reverberated signal is filtered by two active filters constructed around IC4 and these have the same characteristics as the Input filters. Between the active filter stages some passive filters have also been added to increase the roll-off; the loss in these filters is compensated by increasing the gain of the active filters.

The dual clock for the MN3011 is provided by IC5 and with the components shown, the clock frequency may be manually varied with RV3 over the range 10 kHz to 100 kHz, allowing maximum first pass delays from 16.64 to 166.4 milliseconds. Pin 8 of IC5 provides the V_{GG} voltage for the MN 3011. Since both IC3 and IC5 are P-channel CMOS it would be normal to operate them from a -15 V supply. Voltages are, however, relative and by connecting + 15 V to the ground pin and ground (0 V) to the Vpp pin they will operate happily with positive signal inputs. R1 and C5 prevent clocking signals getting back into the power lines. The filters are also operated from a single + 15 V supply and this avoids any problems which may arise from excessive bipolar signals, ie they will be clipped at + 15 V or ground and not damage the BBD. The bias voltage required by the BBD and the filters is primarily to allow them to accept bipolar signals; this voltage is provided by the resistive divider using components R39, PR1 and R40 and is applied to the non-inverting input of the filter op-amps.



Fig. 5 Circuit diagram for the ETI Reverb.

PROJECT : Solid State Reverb

Setting Up And Use

The only setting up required is adjustment of PR1. If a sinewave source is available then the latter may be used as the signal source and PR1 adjusted by ear, or with an oscilloscope, for minimum distortion. Alternatively measure the voltage at the junction of PR1 and R40 and adjust PR1 to give a reading of 6V2

The unit has a signal-to-noise ratio of better than 60 dB but this requires that it is operated with the peak indicator LED just glowing or occasionally illuminating. The output level will vary from about 0V5 to 1 V RMS, depending on the amount of mbung of the original signal, and these levels should ensure adequate response from most amplifiers, mixers, and so on. In other words, by keeping input signals at maximum level the amplifier setting will be such that during periods of no signal the residual noise will not be obtrusive. This is common practice with recorders, many of which have much lower signal to noise ratios.





For the man who has everything else...

there is the ETI binder. Spend your nights enjoying the finer things in life, secure in the knowledge that the liner magazines of life are safe and sound. Order one now, and let the Joneses keep up with you.

ETI Binders cost E3.95 each for UK residents, including postage, packing and VAT, For overseas orders add 30p. Send the completed coupon together with your remittance

ETI Binders, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Piease allow three-four weeks for fulfillment of order.

Please send me	ORDER E71 Binders	FORM I enclose	cheque	postal ord	ler fo
I wish to pay by Ac	cess Barclayca	rd. Please	debri m	, account	
5224		II			
1929		TT			٦
Connect of the second					
Varne					
Address					

ETI APRIL 1982

Theno ILS LOS

SUPERSALE IN

I ful mar brand App descent

2114 (attorne) (1.05. 4116 (200m) (1.15. 2700 (1.26. 2340 transfer until (20 00. NeC 2732 (26.00. 2132 (26.00) stored devices. Device devices. Devices. Device devices. Devices. Device devices. Device devices. Device devices. Device devices. Device devices. Device microsomp mestar movement filmer * Filmen Supplier complete and mete and path, tas batteries Q + 4 Set (7.88 + 52 p/p.

SALF CONTAINED in the second invested digital recorders investes with data array key and with 10 data LEO databas is madare exteriors and charge Lama data (26 per evenera, Sarry,

STATULES the profile PCB rates 12 8 other a.C. contacts His 0/9

D TYPE COMMECTORS

9 Way Sachal tatter 76 9 Way warning plag (1.0 19 Way Pag taster 11.6 19 Way Sachar taster (1.6 2 Way Pag taster (1.6 3 Way Sachar taster (1.6 3 Way Sachar taster (1.6 3 Way Pag taster (1.6 5 Way Pag taster (1.6) 5 Way Pag taster (1.6 New Sector

Di Way Purg Institut (2 00 PrP an album Ma

COVERS

2 Way Grants (L.B. B Way Faster (L.B. 25 Way Faster B), 3 Visy (News) (L.B. 3 Way Gants (Y' ages (L.B. 19 Way Faster (B), 19 Way Mean By

a like

5082/7414 4 out DR. deploy

ant decimal point, high bright The second

SUPERSAVER 1 Dit, house Plags the coverol 14 way 16p, 16 way 20p, 24 way 16p ted gold placed pic 20p. Anatog teacher places. 14 Vitry 75p, 16 Way 60p, 24 Way (128) Conception planning typed pp 30p Analog 60 Hander plags PCB Meaning 1in 20 Way southed Big 40 Way no 11 pp 30p. gupterstaven 2

BUPERSAVER S

34 34 may (17 = 13) . I" maximum parcing edge connectors for dec drives etc. (2.50 each, p/p 36.

SUPERSAVER 6 VIDEO LEAD Pres with PL30 prop CL60 1 th ment p/p Her

SUPERLAVER 2

Physikers Type 16 May 100 Yers 1000 Yers of 22 errors \$1.66 each Limited enough of 25 may 51.66 each Stud resulted roctilizes, hype 40 Hr 100 (250 yers), 40 error, 4 to (2.68 pr) 35p

SUPERSAVER 8 ONE ONLY - TEXAS SILENT 700 TERMINAL R5322 110 boud As now - CES Combys of cost

SUPERSAVER VELLEMAN EPROM Programme In COS But COD - VA' S.A.E. for full description testint

SUPERSAVER 10

Tangerine Microson 65 Blank PCB Dond new pile circuit degram (A.M. prp 05p 1862 based, 1K orr

SUPERGAVER 8 PAPET Links PAN 3%" = 3%" = 1.8" deep. 220v 50%, Grand reps and bosed, (0.50 prp (1.00

LB ELECTRONICS

SUPERSAVER 12 2 Smm power plug and 2 maters of calls, Suissis for Acon Asan, 2181 etc. Only (1.00 per 10 p/p 38p. Trade angustas automa.

SUPERSAVER 14 BOX FANS 115V 50-50-11 120mm + 120mm Nova, E4.50 PVP (1 00)

PYP (1 00, SUPPREAVER 15 EK IV" measure reason, PCB mounting, per bas of 14 (2) 56. As above 16 and 501, peo 30 SUPERSAVER 16 OPTRON OPTO SLOTTED SWITCH (Type OPB 8143 (1), peo 208

SWITCH ITYPE Chp Dis BUPERSAVER 17 VU METER down a Sorver ap-prox. overall case. Face mas Sorver a 20mm approx. Drand now (1,15 ptp. 20p. filent at nurchesp?s.netl. purchasp?s.netl.

SUPERSAVER 19 SALS PCD AMP (LNSID) Linuard Gener - Berri agenor, 0-12v DC 55p p5p 25p SUPERSAVER 19

EUTERBAYUN 19 10 DIGT Ribadi LEO display, L 123m depit staal. Wath burd on driver chilp and burd-in tyne Date dream segated brand news, (1 50 pdty 30),

SUPERGAVER 20 41gin JUMPER LEAD, 16 DL header to 16 DL header, 95p php 30p

21mm JUNE A LEAD 14 DR. er to 14 Dit hoader ----

SUPERAVER.22 1% rept of solder 18 SIVE 64/30 day (5.60 ptp ftp

A TERRIPIC GIVEAWAY, MC HEB RESE RECEIVER. Bond Res 40p cost. 10 for (2.85 Large costrifus p.c.s. pity 30p.

SURPLUS SUPERSAVER 22 16K EPROM PCB 278mm = 18mm taxes 8 1; 45 optimes = optimes decoder togic renged as 18t to 18; Serry no data, C3.59

HAMS PROM

Pro 100 JUST AMBYED targe quantity of assoring Microwave Wave Guides, values bands + notes sources from (B, Calurs only.

LINEAN

CMO6 SCOOP CD4012 10 to (1.85, CD4013 10 to (2.35, CD4010 Nbp and), CD4019 10 to (2.35, CD4021 10 to (6.65, CD4023 10 to (2.35, CD4027 10 to (2.35, CD4023 10 to (6.65, CD4023 10 to (2.35, CD4020 10 to (2.35, P/P Nbp pr

GIVEAWAY 18 pm love profit di sechet 13p EACH or 8 for £1

AUGATIC SOCRETS. (The best ave

24 Dis 1000 16 Di 30p

WE STOCK a vest hange of TTL CMOS, some 74LS, Milloua TLIRE TOGGLES, ctt. PEUS, We have a large stock of power supplies at very realistic prices tomana

Mich Linds WICL Sope connector , ** 75 Way gold global halve arapi (1.65 each p/p 35p/p Bip. REG PCB lises components), SV 1 prop. 12V 1 pmp and heathink (Constraint) Brand com. (1.00, Heatpink anty, SSp. P/P

TELEPHONE UXBRIDGE 55399

PL255 SOCKET CHASSIS MOUNT, Noy ply 300 TRANSFORMERS 012, 034 1 mmp (2.56, PSP 500 TTL SALE 7410 Bp. 7413 18p. 7416 18p. 7400 28b. 74155 68b. 10734 68b. 74161 34285 (2.38)

-WARY PAY POLISIDE? - Just an

ved Amphanel 20-mov play nd eacher (used) to fit all your fear. Only (2.75 per pair P.P. me.

Torma cash with order lofficial orders welcomed from gel-tages, atcl All organist sale pieces. All prices inclusion of VAT, unlage otherwise stated. Postage as shown per flam.



ALL PRICES INCLUENT OF VAT UXBRIDGE 55399

16.47

21.13

11.25

46.94

14.92

12.56

48.12

19.78

25.13

18.47

59.00

12.54

11,19 38.85

54.00

12.53

12.00

8.44 25,25

11.10

12.33

15.25

11.00

1.30

18.72

17.82

8.21

-

6.47

NE STOP SHOPPING

No need for unlimithed projects because you are unable to obtain that last

We stock complete sets of parts for ETI projects - leaving you to concentrate on the electronics and construction

3 WAYS TO BUY:

FULL KITS - include printed circuit board, all componente, hardware, IC sochets, case allc. (Not betterise).

	LESS CASE - as above but lass the case			
į	PCB - PCB MOUNTED COMPONENTS - PCB	phus all	the parts	s which
1	are mounted on the board - plus lads, potentiom	eters +	off beer	free b
1	conductors.	FULL	LESS	PCB
		KIT	CARE	PLUS
	INCOMPTENDED DET MAN 83	10.00	0.00	
	HOBOT MOTOR CONTROL (DI ALLMAN P	10.00	23.75	
	1 Children Contraction and E	33.07	134 30	
	I CHING COMPUTER FID &, IN DOCE			
	MOVING CON STAGE	12.00		
	MOVING MAGNET STAGE	44-4		
	PEST CONTROL En EP		_	
	INFANT GUARD IN 87		_	-
	PARKING METER TIMER IN 87			
	GUITAR TUBER Jon 87	21.98	28.27	10.00
	ALCOHOMETER Der 81	128.49	733.00	
	COMPONENT TESTER Pre El	E7.88	66.17	
	COMPONENT TEATER DE OF BI	C10.000	64.50	
	AUSIC PROCESSOR Nov. 81	40.00		22.04
	PMONE BELL SMIFTER May 81	10.00	12.01	
	VOICE OVER LIMIT No. 41	77 87	21 22	14.17
	CAR ALARM New 81	12.00	14.44	12 80
	ENLARGER THAT BOR ST	74.64	10.00	
	SOUND RENDER ON P	20.78	10.70	13.77
	MICROPOWER THERMAL ALARM OT ET			
	MICROPOWER PENDULUM On ET		5.50	_
	LAR PSU Sept 81		37.00	22.40
	WATCHDOG SECURITY ALARM Aug BI	41.13	1111	18.98
	RECHARGEABLE BATTERY	10.00		-
	HEARTBEAT MONITOR Aug 81	26.28	21.65	13.80
	HANOCLAP SYNTHESISER Aug 81	29.98	23.58	18.44
	FLASH SEQUENCER Aug 81, Loss flash sochets.	38.65	29.28	21.25
	SMART BATTERY CHARGER JUN BI	31.00	25.98	1.04
	WAH PHASE June 81, Loss pedal	-	12.44	9.14
	LED JEWELLERY June 81	-	2.47	-
	Star - 9.41 - Sovel	-	7 20	-

INFRA RED ALAAM Fob 81 MULTI OPTION SIREN Jan 81 4 INPUT MIXER Doc 80 21.83 26.91 18.77 16.71 MUSICAL DOORBEL DEC 80 10.61 MUSICAL DOORBEL DEC 80 11.61 94.10 RIAA PRE AMP Istered Nev 80. METRONOME Nov 80. SUSTAINEPUZZ BOX Oct 80. 6.83 -6.00 24.59 21.49 CASSETTE INTERFACE Oct ID. ULTRASONIC BURGLAR ALARM Aug ID. CAPACITANCE METER Aug ID. CMOS LOGIC TESTER Aug ID. 11.57 28.82 22.98 18.46 20.26 10 97 -SIGNAL TRACER Mer ED 11.98 TUNING FORK Feb 10. 12.40 CLICK ELIMINATOR April 78. 61.68 46.57 GUITAR EFFECTS LINIT And 78 14.78 10.07 COMPLEX SOUND GENERATOR Oct 78 21.97 THIS MONTHS PROJECTS **GUITAR TUNER** WRITE (BAE) OR PHONE Full lut as described in Jan FOR PRICES Hype do not have the gamp of (CTL), which includes the project you will need to order the transaction report all on order the transaction reports all on order the transaction reports Reprint evaluate approximation (Rep. approximation of the second of the second of the second approximation of the second of the second of the second approximation of the second of the 82. Includes case, pobs and meter etc £28.98 An perts evalable annersteh-MAGENTA ELECTRONICS LTD. FULL 135 HUNTER STREET, burton OIB TRENT, STAFFS, DE14 2ST 0283 65435. 9-5 MON FRI. MAIL ORDER OHLY

-

Access and Barclaycard (Mas) orders accepted by phone or post.

Mari Respublic & B.F.P.Q. Surger de-duct Wills from prices shown, Payment must be in senting.

ALL PRICES INCLUDE VAT

ADD 450 PBP TO ALL ORDERS

S.A.E. WITH ALL ENQUIRIES PLEASE

ALIEN ATTACK IN BI MINI DRILL SPEED CONTROLLER June 81 DRUM MACHINE April 61 MUSICAL BOX Apri 81. MUSICAL BOX April 81. ENGINEERS STETHOSCOPE Mar 81. SOUND PRESSURE LEVEL METER Fob 81.



ETI APRIL 1982

AUTORANGING CAPACITANCE METER

Look — no hands! The only control on this piece of test-gear is the on/off switch; the only connection is to the test terminals. This month — construction. Design and development by Phil Walker.


PRO

his is a fairly complex project and should only be attempted by those with a good deal of constructional experience. It is well worthwhile checking the PCB for shorts between tracks before doing anything else. Ensure that there is a hole through the board under the PR1 position to facilitate adjustment later.

Put links through the board at all positions marked with a dot on the overlay and solder on BOTH sides of the board. The other components may now be inserted into the board preferably using sockets for all the ICs except IC4 and IC15. IC4 is a T092-type package 100 mA regulator and does not need a socket, while IC15 may foul PR1 if a socket is used.

The LEDs should not be fitted until the board is test-fitted in position as





Fig. 2 Component overlay for the display board. Insert the link under the display first.

PARTS LIST Resistors (all 1/4 W, 5% except where stated) Capacitors IC15 LF353 470R R1.2 10o ceramic ICM7224 C1 IC16 R3,4,5, Q1,7,8,9, Q2-6 **C2** 1n0 ceramic BC182L 28-37 15k C3-7 100n ceramic BC212L R6,25 41.7 **C**8 100u 10 V tantalum Q3-7 BC 2121 R9 10k D1-6 1N4148 R10,14,17, LED1-7 miniature green LEDs 100 21 R11,15,18, Semiconductors 22,23 74L504 1k0 IC1 74L590 R12 100R 1% IC2,3 Miscellaneous 78L05 R13 1M0 5% or better IC4 miniature 10 MHz crystal XTAL1 4518B R16 1k0 1% IC 5.8 SW1 **DPDT** toggle switch 4053B R19 10k 1% IC6 IC7 SK1,2 press terminals (one red, one R 20 100k 196 4029B black) R24,27 27k 2% 109 4013B 1k8 IC10 4051B PCBs (see Buylines); 31/2 digit LCD display; IC R26 R24,27 271 296 IC11 4049B sockets; display socket (if required); PP9 battery and connectors; PP3 battery and connec-IC12 40128 tors; mounting hardware; case (Vero 220 x Potentiometer 4011B IC13 PR1 47k miniature horizontal preset 156 mm sloping front box, order no. 65-2523E) IC14 4001B

they are intended to protrude through the panel as indicators. Attach power supply wires and fit up to the panel, position the LEDs and solder in position.

Assemble the display board components and attach the logic and power supply wires from the main board. Wire the remaining power leads via the on/off switch to the battery connectors and attach the two boards to the front panel using pillars or long bolts and lock nuts. Our prototype just fitted into a slope fronted instrument case made by Vero Industries (see Parts List).

BUYLINES

Very few unusual components in this project: all the logic is standard CMOS. The ICM7224 and the LCD display is stocked by Watford Electronics, while the LF353 is available from Rapid Electronics. The two PCBs can be ob-tained from our PCB Service, advertised on page 44.

ETI APRIL 1982

FT

		Cieff Canana	n pit anatie	In Granden	in Einetren	NES and pressed		OUADTT	VEROBORIY
Greenban		rices at 15%	Expert: 10	te betate dri	sorwise 40p (Euro)	Past etc:: UK 80g [[] [Europe] and	ALD - INCASE	32 Milling Iwatch (2.50	B.1" Plack with copper strips Prima 1" day b of S(1.0)
Greenbank Electronics (Dept 74E), 92 Chester Road, Nev	Entry 1350 discutors	h, Access Ba	ectoycard, Vi pla, elc con	sa, telaphana telephana B	nd orders how order	sccepiet rs for immediate		60 KH2 (3.95 100 8 KH2 (2.90	21"x11" 130 21"x3" 130
	desparch on acc	aust j		hese cut pr	ices for A	Amateur Users and quantity prices	Esport available,	204 8 634 C3 52 252 144 634 C3 52	31/1 12 31/1 630 21/1 12/1 950
Offered as an alternative to the well established in ELEPTIC ADD 280 COMPLETER 6	International Sur Computer Cards	CMOS	S		Mostly	Motorola RCA	4531 (1.30	307.2 ID42 E3.52 312.5 KHz C3.52 455.0 KHz C3.10	47"#17" 13.26 47"#179" (4.38 0.1" Panboard
The Custom 80 System has been designed as a	fully expandable modular computer system. The	4001 1 1	14p 4043 14p 4043	70p 40 56p 40	184 C1 185 9	48 4410 67.20 100 4411 68.96	4532 £1.10 4534 [5.00	1.000 MHz 62.95 1.008 MHz 63.59	(nn strips) 31,**=21.**********************************
The colour VDU card gives a teletast formal, 2 pixel graphics, contiguons, non contiguons, sm	A lines of 40 characters, upper case, lower case, se height, double height, memory mapped etc.	4006 4007	660 4045 180 4046	11 70 40 750 40	396 1 397 (3. 398 1	10p 4412VP EL.00 20 4415V (4.80 10p 4422 (5.66	4537L 626.10 4538 (1.16	11 Mile 0.2	31/2.07 31/2.032 Termine page 11.50.50
The lift is supplied with all the components for monochrome T V set.	r colour and is used with your own collear or	4009	400 4047 400 4048	7%p 40 56p 40	999 1 0100 C1	No 4433 67 70 12 4435V (5.40	4539 E1.16 4541 E1.19	1 6432 MHz 2250 2 000 MHz 2250	1.0.00 mart 21.50 00 manbeart 23.00
driven giving fast response to heystrokes. On a driven giving fast response to heystrokes. On a addition to the 18. of VDU test RAM1 and speci	his card is included 16 of user RAM (this is in a for 6 2K EPROM such as the CSVS operating	4011 4012 4011	15p 4050 18p 4051	30p 40 78p 40	0101 C1 0102 C1	30 4450 £3.80 80 4461 £3.93 75 4467 £4.41	4549 C3.56 4552 C14.55	2 4576 MHz C3.97	Palinachen ten C1.62
system. The ROM and RAM can be switched b made of the dynamic RAM expansion cards	y software, which is desirable if full use if to be	4014	750 4053 660 4054	70p 40	0104 1 0105 [1	150 4490PP £3.50 15 4490VP £3.14	4563 £2.99 4564 £1.36	2 56250 Millio (2.62 3 000 Millio (2.62 3 1106 Millio (2.75	NO CO 25 NOT CA 00.
(66Hz, Fue use can be made of the 200A's p (vectored) interrupts. The CPU can meet wait at	owerful interrupt structures, including mode 2- ates when requested and utilises pulsed reset for	4015 4017 4018	32p 4055 48p 4055 68p 4056	C1 25 C1 20 C1 20	0107 0 0108 £4	NOp 4502 (1.20 1.50 4503 70p	4556 560 4557 £3.20	3 579545 MHz 61.76 3 93216 MHz 63.87	DIL SOCKETS
For a full 648 system two RAM expension card	is are required. (These may be purchased singly if	4019 4020	42p 4080 61p 40521	90p	0109 C1 0110 C3	100 4505 CB.71 100 4505 50p 177 4507 40p	4558 C1.20 4559 C3.95 4560 C1.89	4 000 MPg 11.90 4 002 MPg 21.90 4 095 MPg 01.99	8p/10p/10p 16/20/22 pm
The microcomputer cards plug into the Custon tithe high quality Custom 80 rack, which is in turn f	n 80 Micro Bus circuit board which is mounted in Ented with a case conversion bit or a good looking	4022	660 4065 20p 4067	360 4 (3.90 4	0180 C1 0161 C1	184 4508 22.85 184 4510 68p	4561 81p 4562 E4.95	1 4 194304 MHz 81.89 1 4 433619 MHz 81.25 4 400 MHz 81.25	24/28/40 pm 25pi28pi20p
For high spaced machine code work the CSV measurmum use to be made by the user's own of	S operating system has been designed to allow, regrams, of the various subroutnes and utilities	4024 4025 4026	450 4059 190 4059 1.30 4070	22p 20p	0163 £1	164 4512 7hp 164 4613 £1.99	4568 (2.30 4569 (1.75	4 800 MHz E1.84 4.9152 MHz E3.20	24pin Tastasi linar teps are reartise force £6.00
Contained in the fermiore. Programs can be stored using nemed files on	n casaette. The dual casaetta interface includes	4027 4028	38p 4071 58p 4072 77p 4073	20p 4	0181 CB 0182 C1 0192 C2	1.03 4514 C1.95 1.00 4515 £1,00 1.41 4516 750	4580 \$4.60 4581 £2.50	Linn Wer C.N.	EDGE CONNECTORS
selectable between 300 and 2400 band. The card For users who would prefer to write programs	also has a 280A counter timer circuit, in BASIC there is a 4K integer BASIC supplied on	4030	500 4075 1.70 4076	20p 40	0193 C2	L41 4517 E4.15 05 4518 42p	4587 99p 4583 90p	5 185 MHz C120 5 24288 MHz C125 8 295 MHz C125	43 milly 42.1" patter with ummp, potentiting start pile 37 Same unter (1 xt 42) 62.11
cessatte sape. It includes commends for setting point!, draw to tine!, erase to tine! etc. A 12K Cur	colour, black and white, graphics etc. PLOT (a stom 80 BASIC is in development and this will be ions.	4033 C	1.66 4077 1.66 4078 1.95 4081	28p 40 28p 40 25p 41	0257 £2 160 1	131 4529 78p 15p 4521 (2.00	4597 12.44 4598 12.90	6.144 MMz 62.70 6.400 MMz 63.20	Boulite sidtet (2 # 42)64.10
Also in development is an interface to hoppy d If you are working on a tight budget, the varie	ses tand disc operating systems). Sus tills of parts can be purchased one at a time.	4035 4037 C	1,15 4082 1,15 4085	28p 4	161 1 162 1 163 1	99p 4522 61.11 99p 4526 95p 99n 4527 61.15	4700 £1.78 1CM7038A	8 55360 MMz E139 7 000 MMz E138 2,168 MHz E2.54	
prices range from (34 09 Hor the Micro Bus Lift w (24 56 Hor the colour VDU Bitu) Sect for more databal to some SAE is not made	th 5 connectors) or (43.22 for the CPU kits up to ;	4039 C	2.79 4086 590 4089	700 4 61.40 4	174 1 175 £1	99p 4528 80p 06 4529 £1.30	£4.25	7 680 MHz 21.50 7 86432 MHz 23.20	(All Plan steps)
BO price His. NEW RI	ELEASE	4041	780	- 4	194 (1	74C904 97p		6 08333 MHz 23.00 6 36660 MHz 23.20	CA TURE 400 CA THE 140
We are now able to see the bare PCB a documentation Custom 60 CPU (18.83, Custor Custom 80 32K RAM (21.25, Custor 60 VOU	n 80 KBP E19 39, Custom 80 Micro Bus E13 87, - 1 (23.70) Ask us for details of Bate Boards for	740	7408	C1.36 7-	4C164 E1	100 74C905 67183 100 74C905 57p 106 74C907 57p	74C927 (5.91 74C928 (5.91	10.000 MHz C1.00	LES SHOPLAYS
Custom ED System	TEROTANET IN ERACER	74002	280 74C8 280 74C8 280 74C8	67p 74 64.62 74 89p 74	4C173 1 4C174 1 4C175 1	130 74C908 (1.00 13p 74C908 (1.00	74CS29 (17.0) 74CS30 (17.0)	10 245 MHz C3.2 10 700 MHz C3.2	6. 777. 778 C2.60 8. 787. 798. C1.60
TEA MICHOSYSTEMS	EL HOMP I OF EMPLEY	74C08 74C10 74C14	280 74C90 280 74C90 300 74C10	90p 74 C108 74	4C192 E1 4C193 E1	116 74C910 (7.46	80C95 850 80C96 925	11 000 MHz C3.50 12 000 MHz C3.50	PHE 586-586 [1.29
ESS - E032		74C20 74C30	280 74CH 280 74CH	50 CLIN 7	4C200 07 4C221 0	45 74C912 C7.30 74C914 C1.46 74C915 C1.15	80C98 \$2; 82C19 £6.20	14.31016 Miles 23.63 16.000 Miles 23.63	Axtar Bate G yo B.
A low-cost alternative to the above staters	IUV 140 1413 claimed by the manufacturer to	74C42 74C48 £	950 74C1	57 C2.28 7	4C374 E1	74C918 £1.10 24C921 £17.07 57p 74C922 £17.07	anc30 (2.50	18.000 MHz (2.5) 18.432 MHz (2.1) 19.358 MHz (2.1)	61.76
erase up to 37 chips in 15-30 mins. This is the no timer, power switch or salary interfoct	switch The user places up to 32 chips into	74074	50p 74C1	57 CL16 74	4C902 4C903	790 740923 88.49 870 740925 68.99		20 1131 MHz C2 11 20 1131 MHz C2 11	01.000 CHINA 17.6-12244 C2.00 18.3053 C3.30
toose conducting toam in the eresure tray to gre held in place by the UV tube which sits	in the tray, (Unkie the UV 140,141, no : a seenage of UV light but the menufa-	74LS	74LS	55 30p 7 53 £1 50 7	4LS161	390 74LS243 850 390 74LS244 800	74L5387 37p 74L5388 66p	26 690 MHz 12.9 27 0 MHz 13.5	IN. 19785 EL.10
state that incident light from this device is o	uite sale at distances above 12 inches 1 (Ormensions - 325 # 64 = 38mm)	74LS00 74LS01 74LS02	12p 74LS 13p 74LS 14p 74LS	73 25p 7 74 25p 7 75 25p 7	4LS164 (1 4LS156 4LS156	1.70 74LS245 EL18 39p 74LS247 40p 39p 74LS248 65p	74LS373 75c 74LS374 75c 74LS374 75c	27.546 MHz C12 36.5656 MHz C12	
SYSTEM CARDS	EPROMPT ERASER Price E33	74L S03 74L S06 74L S05	14p 75LS 16p 74LS 15p 74LS	76 20p 7 78 24p 7 83 50p 7	4LS157	350 74L5249 680 360 74L5251 400 410 74L5153 400	74LS377 800	48 000 MHz 62.5 100 000 MHz 62.5 116 000 MHz 63.6	10399 E7.90
International cards (mostly Kemitron) A range of International \$114 - 203mm set (and)	Two sasy-to-use units designed for both	74LS08	150 74LS	85 70p 7 85 38p 7	41.5161	#1p 74L5257 48p 41p 74L5258 40p	74LS384 84c	TRANSISTORS	DIL RESISTORS
er to build up a complete system. Burther details evaluable on request An hearts are epore glass	The professionel and emeteur UV promuser user	74LS11 74LS12	150 74LS	91 80p 7 82 36p 7	415164	48p 74L5280 21p 75p 74L5281 £1.98	74L \$393 600 74L \$395 £1 9	BC 177 20 BC 213L 10	P RESISTORS Carbon Rm, high
with gord plated edge plut New bare-board prices	Can erase up to 14 proms Special shortwave uffra violet tube	74LS13 74LS14 74LS15	300 74LS 480 74LS 150 74LS	93 30p 7 95 45p 7 96 (1.16 7	4415100 4415170 (* 1415170	150 74LS286 250 1.70 74LS273 100 720 74LS275 250	74, 5396 (1.1) 74, 5398 (2.7) 74, 5398 (2.7)	BC 548 14 BC 548 14 2N 3700/4/5/5 10	p range 2p mach 100 of one value £1.00
428 3 200 CPU (11 80 SCMP 2 SC/MP CPU (11 60 SCMP 2 SC/MP CPU (10 70	 Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exercisite which may shorten) 	74L S20 74L S21	15p 74LS 15p 74LS	107 43p 7 109 30p 7	4L 5174	72p 74LS279 88p 58p 74LS283 45p	74.5445 €1 40 74.5447 €1.4	2% 3820 45 TIP 2955 60	
MXD-2 10K of 4116 C11 50 MXA-1 7K of 2102 C11 50	promitiel Sliding tray carries promis on conduct	74L526 74L527 74L520	160 74LS 200 74LS	112 JOD 7 113 40p 7 114 35p 7	4LS183 C	1.30 744.5290 57p 2.75 74L5293 44p 54p 74L5295 (2.16	74.5400 E1 80 74.5608 E1.77 74.5609 E1 56	DIODES	100 100 100 DBS
MXA 3 8K of 2114 E11.60 PRSL&B K of 2708 E19.76 IP-2 input Port E13.60	 Safety interlock switch prevents the juming circuit from operating and 	74L 530 74L 532	18p 74LS 15p 74LS 16p 74LS	122 44p 7 123 56p 7 124 01.05 7	4LS191 4LS192 74LS193	58p 74L5298 £1.38 58p 74L5324 £2.00 65p 74L5324 £2.00	741.5670 21.7	IN 4148	o tall, dell, the state to make o the 22 of , 0 of at 10 and 100 of 11
OP-3 Output Port E11.80 S10.4 #S232 Iten6i E11.80 RP.3 Press Programmer E11.80	switching on the tube with the tray open	74L 537 74L 530	16p 74LS	125 30p 7	74LS194	40p 74LS32612.90 40p 74LS32612.94	74S	IN 5401 15 LA BRIDGE 150V 22	¢
TPA-2 SC/MP Tacu Interface E10.78 DCR-6 SC/MP Keyboard Interface	Smart testured case Complete instructions supplied	74L540 74L542 74L547	16p 74LS 36p 74LS 40p 74LS	136 28p 7 138 36p 7	74L S195	60p 74LS327 E2.80 58p 74LS347 [1.48 85p 74LS348 [1.88	74504 736	SIL RESISTORS	
VDU-A (10.76 VDU-B (10.76	Supplied complete with mains plug and their	741,548	80p 74LS 60p 74LS 150 74LS	130 360 7 145 75p 1 147 £1.70 1	74L 5221 74L 5240 74L 5240	80p 74LS352 [1.85 96p 74LS353 [1.85 96p 74LS353 [1.85		8 = 10K (9 pm) 46 8 = 46(7 (9 pm) 46	p -
New boarss expected soon YOU IL (anyge board YOU 32x24 £16.16	Model UV 141 - Price E77.70 Also available without timer as	741.554	150 7415	148 99p 7	ALS242	150 74L5366 17p		1000 A.D.	UNIT MODILE ATOPS
MP-87 (8070 CPU) C18.95 M28-4 (280A CPU) C28.96 MXD-6 (286K Dynamic Ram) C33.60	Model UV 140 - Price £61 20	_	M	ICKOI ISER	UN N	DAMICS	SA	1000 03.10	UMITITESE Vision modulator TV game or cheep campu
DC-21S D. Disk Controller! (18.8) DC-4 (D D. Disk Controller! (23.80 HDA-1 (Herd Disk Adaptor! (23.80	Comprehensive information on the 280, DPU, I also in the bound data books described before	PHL CTC	0525/21 0522		£4.85	0710 100.200+5 0+4710 0101	CALL CR	T CONTROLLER Uarts	UM1233 E36 Wide Sanderste
SOFTWARE ZYMON 1 Monitor (2K) E14 IB HCS BASIC (2K) E14 IB	Mostali 200 Programming Manual lapo pagest fully detailed explanation of all	ros 300 No 200	20032	200	14.10	UV ERASABLES SIDE 512+0	05 AV-3	-1015 CLOP	computer VOU type
SWITCH MODE PSUS	op codimissionibly terginge. Mentet 200 Microcomputer Deta Beek	appros	ZBOA PIO ZBOA CTC		£1.78 £4.00	27182316 21-6 10	£1.85	(1.0)	Sandwidth vision modula- ter with intercarrier sound.
AC 54215 5V/20A F08 20 AC 54215 5V/10A 12V/3A 12V/3A 5V/8.1A (128.50	475 pagette concerns 200 instruction set and information and specifications of the 28	tanà)	200A 5101	5000	(1.36)	272 4-15-	CLIN C	HAB. GEN KEVBOARD ENCODIR	VOLTAGE INC
OPEN CARD SWITCH MODE PSU PULLY ASSEMBLED P.C.B. CARD HU + 18 Same Organs + Nr BA SWIBA DWITA DV/TA	Mostal Micromputer Systems Data Book 220 pages contains of the Mostal	Lappros range al	6802 MPU 5809		(4.25 (8.76	PROM WASHING SI S0g each prom	MVICE NO-1	-2513 fbs. Uppercasel	7805 45c 7906 56p
ACEDA SW/26, 219/26, 129/6 134, 107 - 107 -	microcomputer circuit boards and software elit. The weight all the data pack is approxim	atuly 1.0	58A10 (128 5 6820 8821	n ERAM	C1.30	SPARE ERASER T	CIG.00	FILMWARE	7912 40c
Fully Assertion: Call, ND + MDress + 76 30W Overvit primer Type 710 + 5W or 6A activestite to + 19V itt	Price: £14.85 (There is no VAT on this i	in but	MICHADA		C1.60 C1.20	UV PROM ERAS	C01.20 01 (77.30)	cludes commented listing	VOLTAGE CONVERTER
24." Tree 7151 + 57 et 34. + 127 et 1.34	plasse and an extre ELUD towards the composinger	R W 90	SCHP II II	NP B RAN 10	-	EPROMPT	CILID: 16 2	(MON 200 (1 x 2516 or 1 1 2708) E14.95 (Teny Basic for 200 (1 x 1	only systems, to octan - 12V - 12V, or dual 12V power for
T.V. MONITOR P.C.B. for DEM	EUROCARD 19" CARD F	RAME	PUE 0154 AA	ON IN	0.0	111.5 10107 171.5 10107 171.5 10	900 2 900 4K 9	516J E14.95 518L for SC MP 48 ± 27081	ASCII keyboards, RS 232 In- terfeces, dynamic RAMs atc. All types need - SV input.
Der 12" 10" Black ale unte Cit I fill argene 20mit 4 altan a I d manaer a nadest tast flagrettalty un Cit	a mett) fit gener tetreten strift. Antennanerurs	128.84	COSMAC	COP 1882CE	CL.30 (16.85	1400 1400	62p (4)	NUBL-MMM for SCIMP H # 1000 (49.95	Size of each module leached og pensi 34 22 26 34 10mm
De C.B.T. « procetti j Preset conveto contrast brightness, etc. are excluded, a media éreter etc. 15 foi:	ing the party Connector membres strate (part) date per ye (connector membres strate (part) date per ye (connector base (str	C3.27 C19.00	COP 1884	S tilbentiv 460	f8.45 InSi	75482	11 50 11 1	lettor Jumor (1 x 2708) (15.05	+12V output 125 BlmAU E4 95 Type ADIN-12A10
Companie under inger Suppliet und cartal bieft im	C33.50 Dr fit tills separate 20 10 - 0 spe casel Dies 41612 Eurocard Connects	E 32.50	2114 3863 2114 3865	IL ANN SIDES	2	47 34010 FD 1271	(5.95 11/2 (18.00 ETH	K ELBUG (3 = 5204) (35.90 BUG (1 # 5204) (35.90	-12V output 125 64mA) EA M Type ADIO 12A10 2 12V, dual output 2 m 112-
KEYBOARD CASES	E10.14 64 mer facter rent s +s (64-10)	63.34 62.71	10116 0 eff		0.0	0131 0135	(2.60 ETL (2.60 ETL)	BUG 2 (1 x 5204) E14.95 BUG 2 (1 x 5204) C14.95 APACE IT x 5204) C14.95	42mA1 (5.25
DTU R JIEUMAR Panel sure 430 + 115mm	samaal a mer becan rees a +b (\$6.194)	(4.24		-					

BIRTHDAY COMPETITION.

WIN £50's WOR1 **OF VFROBOXE**



There's no doubt that no matter how clever the project you've built is, your friends and family are not going to be impressed with it if you display it in a cardboard box or the proverbial tobacco tins. What's more, the feeling of satisfaction you get from project-building can be that much greater if you end up with something that looks as good as commercial equipment.

One of the companies with the largest range of cases is Vero Industries. They've given us a collection of their cases worth £50, and we're going to give them to one of you - but the lucky recipient has to have

answered these three questions correctly.

(1) How many boxes in the pile on the left? (There are no concealed box tops).

(2) How many of this month's projects are housed in Veroboxes?

(3) Is the Vero 'G' range of cases made from plastic or metal?

Answers on the form on page 133 please, together with your name and address, to reach us before April 30th, 1982.

RULES

- 35
- 3.
- Chaining data is April 30th 1982, and all entries part marked later than this date will be decreanted. The ecupses provided in the magazine must be used. Photocophies are NOT acceptable. Employees of ASP and these relatives are not objetile for entries. ь.
- entry. The judget decision is to be considered final and to correspondence will be entered into concerning the competition.

EI B RONICS 201

DITPE COMMECTORS	
9 way r/angle skt	[1.25
9 way looklar) sht	(0.75
9 wey loring) pig	(0.75
15 way tw/wrap) pig	[1.00
15 wey (aolder) pig	CO 85
15 wey lookder! ekt	CO 95
25 wey lealder! pig	(1.85
25 wey looider! sht	C1.85
25 wey line/pelree) pig	2.05
25 way line/pairce) sht	(2.65
25 way (w//whap) sit .	(2.00
37 way lookder/itail) pig	(1.80
37 wey loolder/tail1	£1.80
50 way lookler/tail) plg	(2.00
50 way looider/tell) sht	(2 00
TYPE COVERS	
Bredia Brance	-
	P DA DEC

Plastic 9 way	(0 0)
Plastic 15 may	(0 60
Please 25 way	(0.95
Plastic 37 way	C1.00
Plastic 50 yeary	C1 20
Motel 15 way	(0.96
Motel (FTT) 25 wey	(1.00
Motel 25 viley	(1 25
Metel IITT) 50 wey	C1.28
Metal 50 way	C1.05
P/P on all above day	

SUPERSAVER 30

PAPET Miniton 3%" og 1%" to 220V. 90 HZ. Brand new breed breed CO 50 PHP 500

SUPERSAVER 31

UECL Gold plated Edge can nector .1" 75 way (1.65 PP 45p feere wrep!

SUPERSAVER 32

12 Volt Relay, P.C.B. Mintg S/pole d/CHANGE over (0.65 PIP 26p

SUPERSAVER 33

JECKSON NICAD CB.75 Bett charger for 4 x AA, D, D. Same as above plue P.P.1 (10 00 PP (1 00 each

SUPERSAVER 34 ANTEX 15 wett solder nor

14.95 PIP 780

SUPERSAVER 35

A Treat 12. 16 meters of 16 core 01.10 cable with non-standard 10 TYDE DID/MAY C1 SO PHP C1 00

SUPERSAVER 15

Mains laad 2 meters - with moulded LE.C. mains plug 6A 2004 E1.00 much PIP 500

SUPERSAVER 37

MERTRON M 423783 16 WWY bues rail, 4 for £1.00 PIP 35p

SUPERSAVER 18 TISB Andrey L.D.C. Connectors 26 way straight plug 66p

660 40 way straight plug 40 way R/A plug E1 w 40 way R/A plug E1 w 55p PIP 25 each 100

SUPERSAVER 39

mourning, 4 for 12p., 12W plg 12p each 16W plg & sht 45p for pair. 2W pig to skit 25p for pair 3V old by thit improved 45p for per-P P 260

SUPERSAVER 40

1" 30 x 30 Gold ploted P.C.B plug. E1 00 each 20 way PCB sht 20p each. JOW plg 1" R/A 50p each P/P 250 each

SUPERSAVER 41 AUGAT IC sats (The best sual abia) round turned pins I.C., pin cuts a groove in the sht for 100% connection reliability. 16 way 20p. 18 way 25p: 24 way 50p each P/P 25p.

SUPERBAVER 42

eder pigs (gold pi 14 way (no CVR) 18p eech 16 way ino CVRI 25p each 24 wey ino CVRI Sin each 14 wey HDR pigs with CVR 45o each 16 wey HOR pigs with CVR 60o each Analoy 14 way HOR plgs RBN 1/2 Php Analoy 15 way HDR pigs RBN 1/10 95m Analoy 24 way HDR plgs RBN ET SO PYP 15p each

SUPERSAVER 43

INTAR

2516 used fully erazed guaran teed replacement single end. EPROM 350ns E1,65 each: Ten for £17.00 P.P FREE

SUPERSAVER 44

Tangerine Microten 65 blenk P.C.B. Brand new - circ dia-gram (64.50 66502 based, IK on board: P/P 50p each

MICRO REVOLUTION

The new ZB Processor complete P.C.B and parts to produce this new R. S. 232 CPU. But in tim BASIC and AK RAM only 4.8 by 4.5". Price on application. Further details to follow,

SUPERSAVER 45

M.C. 1489 RS 232 Receiver LC. 46p each PIP 20p

2016HPWASH 48		
2708	CL.85	POSTA
1702	(E.00 ee.	ONE IT
2732	(\$ 50 es.	SEVER
2532	(8 50 m.	YOUR
2114 (480ne)	£1.00 es	
2114L (460ns)	£1.35 en	SUPPO
2114 (200ne)	C1.45 co.	6251
4116 (200mai)	E1.00 ma.	8253
Quenety on above	P.O.4	8224
P/P FREE		P/P 360

HAMSPHOMS PLUS TELEPHONE UXBRIDGE 55399 SUPERSAVER 47

Appros, 2 meters + com in with pigs either and (1.00 eaci

SUPERSAVER 49

64 way Delid1612 edge con nectors to fit Microsan etc. ph or shi (3.45 each PJP 35p each

Amphanol 35 way pig to stu luced to fit all your (2.76 per par PIP 36

SUPERSAVER 50

2.5mm Power ptg + 2 metres of cable to fit Acom Atom 2001 etc. etc. Only £1.00 for 10, P/P 250. TRADE ENGLIRIES WELCOM

OSTAGE STATED IS FOR

NE ITEM IF YOU OADER OUR OWN DISCRETION.

UPPORT DEVICES (1 00 eec! 151 50 EL.00 mech 24 (2 00 eect

24.5 L.B. ELECTRONICS 11 HERCIES ROAD, HILLINGDON, MIDDLESEX UB10 9LS **TEL: UXBRIDGE 55399**

P/P 360 SUPERSAVER 46 FND 500 9" LED displays sag. Red 65p each Larg quarkity P.O.A. P/P 35p





L & B

ELECTRONIC MODULES PROFESSIONAL ENGINEERING

BY PROFESSIONALS

45 Wortley Road, West Croydon Serrey CNI 208, Tol. 01-653 4130

ETI APRIL 1962

COD sprease

PLANE NOTE THE COMPANY HAS NO COMMETTION WITH LE ELECTRONICE OF

£19.20

FEATURE

TECH TIPS Frequency-To-Phase Controlled Power

Supply

Dilbay Singh (B.Tech), Crawley

The circuit shown in the diagram was initially designed to obtain a phasecontrolled power supply to use with a ¼ horsepower stepping motor. The phase angle can be varied over the complete cycle period and is dependent on the frequency of the input. Clearly the circuit can be used to control resistive loads such as lamps or motors.

The first stage of the circuit consists of a frequency-to-voltage converter. C1, R1, and Q1 effectively differentiate and amplify the input signal waveform to provide triggering pulses for the 555 timer, which is used in the monostable mode. The output of the monostable is used to charge C3 by a constant amount of charge every time a pulse is received at the base of Q2. The voltage across C3 acts as an input to the common collector stage formed by Q3. The voltage across C3 is DC-shifted by means of the zener diode ZD2 to a suitable value, providing the input to the trigger IC (the Mullard TCA280A). The TCA280A provides the phase control signal for the gate of the thvristor.

A triac may be used in place of the thyristor, if phase-controlled AC is required.

The component values shown are suitable for providing phase control using frequencies in the range 200 Hz-8 kHz on the control input. The firing angle can be varied from 0° at 8 kHz to 170° at 200 Hz.



Fully Debounced Keyboard

Graham Kyte, Bexleyheath

This circuit produces a debounced output whenever a key is pressed. Each matrix point is scanned in turn and the output of the 4052 data distributor goes high when a pressed key is detected. This stops the scanning oscillator (555) for about 10 mS and a 'key pressed' output is produced, thus enabling the BCD output to be stored in a latch or otherwise made use of. The use of CMOS ICs enables current consumption to be minimised, making the circuit suitable for operation in a car. The circuit is easily modified for a larger number of keys by using an eightway data distributor (with relevent counter made from three I-K flip-flops rather than the two as used here).



The Tips is an ideas income and is not atsuff at the beginner. We regret we cannot a series and the set of the series and the set of the series of the serie

ETI APRIL 1982

1

Remote Camera Release

Geoffrey Ammon, Welling

When taking photographs from a distance, a pneumatic remote release is normally used. These will only work over a limited distance and it is not always possible to tell if the camera has operated. This simple circuit uses a low current trigger circuit to operate the camera and provides a visible indication that the camera or flashgun has worked correctly.

The circuit operation is as follows. When the remote release push-button PB1 is operated, a current flows via the extension lead, which may be a 100 metres or more in length, to switch transistors Q3 and Q4. This combination provides the load current of up to 2 A for the camera release solenoid. When the flashgun fires, light falling on the CdS cell



base of Q1. When Q1 switches on it will discharge C2, extending the pulse duration to about one second. While C2 is charging Q2 will be turned on, causing a large enough current to flow in the extension lead to operate LED1. If a flashgun is

not used, the camera flash contacts (SW1) may be connected to bypass the CdS cell and remotely operate the indicator LED1.



Cheap PET Cassette

D.J. Cocker, Portsmouth

In view of the price of the Commodore cassette unit, the following adaptation may be of interest. I have been using this arrangement for some time and have experienced very few problems. In order to signal the PET when the PLAY key has been pressed, a switch mus be incorporated into the cassette key assembly – a small microswitch is ideal. This is an improvement on the Commodore unit, in which any key activates the switch, leading to confusion and ambiguity. The 'signal present' LED is very useful in locating the start and end of the data tape. The cassette recorder is supplied with power from the PET, batteries only being required for fast forward and rewind functions -- a switch should be fitted to facilitate this. When the PLAY key is depressed, the PET has control of the tape motor. It may be found necessary to disable any tone control circuitry or AGC which may be fitted in the cassette recorder. Any suitable TTL Schmitt gate may be used as IC1.



Room Thermometer J. P. Macaulay, Crawley

With the advent of the LM3911 temperature controller IC the task of measuring temperature has become simple in the extreme. The internal circuitry of this device comprises a temperature sensing element, an op-amp and a stable reference voltage. The device gives, in its simplest form, a stable 10 mV change in output for every '1° change in temperature over the range -25 to 85°C. For the application of room thermometer it is only necessary to utilise part of this range from, say, 0° - 50°C. The circuit to be described measures this range.

The figure shows the complete circuit of the thermometer. The meter, a 500 uA FSD type, is connected between the output and inverting input of the internal op-amp. Resistor R1 connects the inverting input to the output of the 741 op-amp. This is used with 100% AC and DC feedback to form a unity gain voltage follower with a current output capacity of several milliamps. The input of the 741 is connected to the slider of PR1 which in turn is connected across the stable supply voltage produced by the IC. D1 and D2 protect the meter from overrange temperatures and thus protect its delicate movement from harm.

Once-completed, a calibration can be made with a room thermometer of known accuracy. Simply leave the equipment in the room for 10 minutes or so for its own temperature to stabilise and then adjust PR1 until both thermometers read the same; the calibration is now complete.

FEATURE : Tech Tips

Enlarger Timer

C. E. Basson, South Africa

The circuit of the enlarger timer can time periods from 0 to 99.9 seconds in 0.1 second steps. PR1, C1, R1, IC1a,b form an oscillator that feeds a 10 Hz signal to the first 4017 counter stage. Either the 'carry out' or '0' outputs of IC2 and IC3 can be used to feed the next stage, as the frequencies are the same and the positivegoing edges of the pulses appear at the same time. Outputs '0' to '9' go high in sequence as the pulses are received at the 'clock in'. The desired time is selected by SW2, SW3 and SW4.

Q1 is used as an inverter and with the NAND gate it performs the same function as an AND gate. As soon as the desired time is reached, all the inputs on the gate will be high and this will trigger SCR1. The relay will be turned on and switch off the enlarger lamp. The lamp will remain off until the circuit is reset.

The circuit can be resetted by closing SW1a and opening SW1b and SW1c. SW1a will reset the 4017s and keep them in the reset condition. SW1b will remove the current from SCR1 to reset it. SW1c prevents the light from going on when in the reset condition. When SW1 is switched back to normal, the light will go on and remain on for the desired time.





Comprehensive CMOS Logic Gate Test Rig

David Ian, Surrey

This simple test rlg will check out all possible functions of any type of dual input CMOS logic gate allowing, for example, a faulty gate to be pinpointed so that the rest of the IC may still be used.

Each gate is provided with a green LED to Indicate a high output and a red LED to show a low output.

Use a 14-pin holder for the IC and orientate the LEDs to relate to their appropriate gate.

SW1 connects power and a logic 1 to all inputs: press A to put a 0 onto one input of each gate; B puts 0 onto the other inputs; A and B togther force all inputs low.

A milliammeter in series with a 9 V supply should only indicate the current drawn by the LEDs, ie about 7 mA per LED. An appreciably higher reading indicates a completely faulty IC.

No. 1 CLAY Te	IAL AS GATE ROAD 1. 0223 24825	SOCIATE , CAMBRIDG 7 TLX 81744	S IE CB1 4JZ 15	COMPUTERS We stock computers and accept Sinclair ZX 81 in part exchange. Minimum of £20.00 is offered for your ZX81 in part exchange for a VIC 20 or Arcom colour Computers.
Computer LC.s 2144-20010 2144-200.P10 27144-200.P10 2532 4.10 4116-15075 4115 200 66 6116 475 9516 7.50 6000 275 6002 1.60 6009 875 6610 1.15 6010 1.15 6021 1.15 6021 1.15 6023 1.60 6009 875 6010 1.15 6021 1.15 6021 1.15 6021 1.15 6023 1.60 6009 875 6021 1.15 6021 1.15 6023 1.60 200 2	77 12 78 15 100 12 110 15 110 15 110 15 111 16 111 17 111 18 111 19 111 10 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 111 11	132 44 138 30 148 55 151 30 154 80 155 38 156 38 157 30 161 37 162 40 163 38 164 46 165 90 173 69 173 69 174 46 165 97 197 50 240 87 241 87 242 78 244 80 247 80 247 80 247 80 247 80 247 80 257 70 200 55 370 70 370 56 371 70	Vortage Regu 7005 5V - 255 7012 12V - 35 7012 15V - 35 7012 15V - 35 7012 15V - 35 7012 12V - 35 7012 12	NEW Domestic cassette INTERFACE for VIC 20 ONLY £17.00 Simply connects your VIC 20 to any Cassette player. A bargain at half the usual price. NEW VIC 20 Memory expansion Packs 3K RAM

The Finest Amplifiers deserve the Finest Kits

The Electronics Today System A, designed by Stan Curtis comprises two monophonic Class A Power Amplifiers and a modular pre-amplifier of such superlative performance that they stand comparison with commercial products in any price range.



DRAMATIC PRICE REDUCTION!

Increased production has enabled us to slash the price of the complete system (two power amps; pre-amp & powerunit) by 30% to £386 incl VAT & carriage.

YES a 30% Price Reduction! But no reduction in performance.

Details and price list from:

Braithwaite KITS

215, High Street, Offord Cluny, Huntingdon, Cambs. (0480) 811659

BIRTHDAY COMPETITION,

PROGRAMMABLE CALCULATOR

CASIC FX-762



That's right — in this competition we're offering you a chance to win the fabulous Casio FX-702P pocket BASIC computer, kindly donated for the occasion by Tempus. The features of this computer include:—

AT ROCAES DATA

A scrolling LCD alphanumeric dot matrix display A memory which can be varied between 1680 program steps and 26 memories to 86 program steps and 226 memories

Auto power off

All data and programs are retained in the memory when the computer is switched off

Up to 10 different programs may be stored at once

Subroutines may be nested to 10 levels

FOR/NEXT loops may be nested to eight levels Full debugging and editing facilities

55 built-in functions (including regression and correlation), all of which may be used in programs

Program or data storage on tape (using an FA-2 adaptor)

All this would normally cost you £134.95 (recommended retail price) but it can be yours – FREE – if you can answer one simple (!) question. Eyes right First, let A = STR\$(the product of 7K (in decimal) and the standard audio bandwidth). We'll use this later. Now, add the UK AC mains frequency to yellow/violet/red and divide by the number of our modular synth project. Divide the result into VAL(RIGHT\$(A\$,4))-VAL(MID\$(A\$,5,3))/LEN(A\$). Add to this result the difference between our office street number and the TTL prefix. Multiply by the log (to base 10) of the sum of the digits of a CMOS quad EXNOR IC divided by the number of pins on a 555. Finally, add the decimal number represented in binary by 10111.

If you've managed all that (hint – people who know BASIC well have an advantage), write the answer on the entry form (page 133) with your name and address and send it to us by April 30th 1982. Answers to six decimal places, please.

RULES

- 5. Closing date is April 10th 1983, and all entries pastmatical later than this date will be discounted.
- 2. The coupon provided in the managine must be used
- Photocoptes are NOT acceptable
- The judger decision is to be considered final and an
- convertigendence will be entered into concerning the

PROJECT

SOUND EFFECTS 2: STEAM TRAIN

Railway modellers looking for something special to improve their layout need look no further. Our second sound effect project simulates a steam train and whistle. Design by Phil Wait.

A shh, the nostalgial If you're young at heart, old in years, or both, then this is for you — a steam train (chuff-chuff) and whistle. The electronic construction details are given on page 50 in the bomb drop project; but for that authentic touch, deft constructors can also fashion a cow-catcher out of tinned copper wire to attach to the unit!

The chuff-chuff runs continuously once power is applied and the whistle sounds when the push-button is pressed. The VCO is used to provide the whistle while the SLF modulates the noise generator/filter output to produce the steam train's chuff-chuff sound. The chuff-chuff rate may be varied by changing the values of R1 and C1, while the chuff-chuff sound may be varied by changing the values of R2 and C2. For a special effect, you can control the chuff-chuff rate manually by replacing R1 with a 1M0 potentiometer.





Fig. 1 Circuit diagram of the Steam Train and Whistle unit.

HOW IT WORKS.

In this unit the Noise Generator/Filter is employed to produce the basic 'steam engine' sound, this being modulated by the SLF to produce the 'chuff-chuff' so characteristic of steam locomotives. The whistle is produced by the VCO, which is set to a particular non-varying pitch, and the output is switched into the audio input pin to produce the whistle.

The broadband noise from the Noise Generator is modified by the Noise Filter, the frequency characteristics being determined by RS and C3 connected to the Noise Filter Control pins (5 and 6). The Noise Filter Output is fed via the Mixer and the Envelope Generator (which doesn't function here) to the audio output stages. The SLF square wave output effectively modulates the noise to produce a noise burst followed by a silent period, then another noise burst. Thus the chulf-chulf sound is produced. This sound is continuous whilst power is applied to the unit.

A resistive divider, R3/R4, provides about 1V8 at the VCO frequency to a convenient pitch within its range, providing a suitable pitch for the whistle. The VCO output is coupled to the audio input (pin 10) via C4 and the push-button, P81. When P81 is pressed, the whistle is heard over the chuff-chuff sound.

The SLF frequency is determined by C1 and R1, while the combination of R2/C2 and the voltage on pin 15 determines the VCO frequency. Output to the loudspeaker is coupled via C5, a 100uF electrolytic capacitor.

PARTS LIST.

Resistors (a	II 1/4 W. 5%)
R1	330k
R2	470k
R3	56k
R4	100k
RS	1k0
Capacitors	
C1	1u0 16 V tantalum
C2, 3	470p ceramic
C4	10n ceramic
C5	100u 16 V PCB electrolytic
Semicondu	ictors
IC1	SN76488 (see Buylines)
Miscellano	us l
PB1	SPST push-button switch
PCB (see B	uylines); 50 mm diameter 8 ohm
speaker; Pl	P3 battery and clip.

ETI APRIL 1982

ETI

118









PROJECT

GUITAR PRACTICE AMPLIFIER

Simple construction, low cost, good performance and super neighbour relations are the features of this project! Design and development by David Tilbrook.

ETI 452

This project has been designed to enable guitarists to put in long hours of practice and still keep that high power amp in the cupboard, where it belongs! It is a compact amp capable of about 7 W into a 4 ohm load. This is enough power for practice purposes and just think of the greatly improved relations you will have with your neighbours.

We were in a considerable quandary as to how to present the project, whether it should be done as a complete practice unit with inbuilt speaker or simply as an amplifier to be connected to an external speaker. Finally we chose a compromise. The PCB has been designed in such a way that it can be used as a totally selfcontained unit. The heatsinks for the output stage have been mounted on the PCB so that the only components separate to the board are the power transformer, 240 volt power switch controls, input and output jacks. We have shown the project mounted in its own box with power transformer but it should be a simple matter to construct the whole unit inside a small loudspeaker cabinet.

The unit has two inputs so that two guitars can be mixed together using the relative settings of the two input level controls. A preamp output enables your main high power amp to be driven from the guitar practice amp using the practice amp as foldback.

We provided the PCB with the necessary circuitry for a battery input but you might elect not to use this feature. If so diode D8 and the battery switch can be omitted with points 'A' and 'C' connected together by a wire link.

Construction

Construction of the project is reasonably simple since it is almost entirely devoted to construction of the PCB. Start as always by mounting the resistors and non-polarised capacitors. Mount the tantalum and electrolytic capacitors next, being careful to orient them correctly. These components could be irreparably damaged if inserted the wrong way around. Mount the LM301 IC, transistors and diodes, again being careful to insert these the correct way round.

Finally the output devices can be mounted. Although the transistors are in TO220 packages, our PCB is laid out to accept heatsinks drilled for TO3 transistors. The overlay and photograph should make the construction method clear. Cut the centre (collector) lead off. This lead is connected to the case of the transistor internally, so in this case, electrical connection is made through the mounting screw that also serves to hold the heatsink in place. Place the heatsinks on the PCB and secure with the lower nut and bolt (not used to mount the transistors). There is only one right way round. Bend the leads of the output transistors and, using a small amount of thermal compound, mount the transistors with the leads protruding through the PCB.

Secure each transistor with a nut and bolt through both the transistor 'flag' and heatsink. Use a star washer between the head of the bolt and the copper pad on the PCB to ensure good electrical contact. Now the base and emitter leads can be soldered to their pads.

The prototype unit was constructed in a steel box measuring



HOW IT WORKS

The two input stages formed around Q1 and Q2 are identical. Resistors R1, R2 and R4 form a very stable biasing configuration around Q1. The gain of this type of circuit is determined by the values of R3 and R4 (specifically, the gain is R3/R4). The load impedance on the output of the Input stages is in parallel with R3, effectively decreasing the total value of impedance from collector to ground. Remember that, as far as signal is concerned, the positive supply rall is a short circuit to ground, since it is connected to ground through C17, a 22004F capacitor. When all these factors are taken into account the gain of the first stage is about 10 since the impedance from collector to ground is about 4k7.

The signal, which should now be around 200 mV, is then applied to the input of the second stage through potentiometers RV1 and RV2. The 22k resistors R9 and R10 prevent the output of one of the stages being shorted to ground when the other is turned right down.

The second stage works in exactly the same manner as the input stages, resistors R11, R12 and R14 forming the bias network for Q3. The voltage present on the collector of Q3 is around 9 V which is approximately half the supply voltage. This is used to bias Q4 which is an emitter follower. This type of amplifier has no voltage gain but provides a low output impedance to drive the preamp output socket. Q3 has a gain of approximately 10. If the volume controls RV1 and RV2 are used in their middle positions, the voltage out will be around one tenth of the voltage at their inputs since these are logarithmic pots. So, the signal voltages into Q3 should be in the order of 20 mV. This will be amplified to a level of 200 mV and applied to the input of the power amp. The power amp has been designed to deliver full power with an input voltage of 300 mV, so the amp should be easily driven to full output with usable settings.

Since this is a guitar amplifier, it will spend most of its life hard into clipping. The output stage had to be robust! The basis of the output stage is the LM301 op-amp. This device gives all of the voltage gain in the power amp. The output IC1 is fed through a voltage follower Q5. This has no voltage gain and, like Q4, serves to decrease the impedance feeding the output stage. The three diodes, D1, D2 and D3, maintain 1V8 between the bases of Q6 and Q7. Each of these transistors will drop approximately 0V6 across their base-emitter junctions. This leaves a total of 0V6 to be dropped by the two 33R resistors, R24 and R25. Since these are of equal value they will each drop OV3 and hold this voltage across the base-emitter junctions of the two output transistors Q8 and Q9. As these transistors require 0V6 to turn on they will remain off until the applied signal voltage causes the voltages on their bases to rise above 0V6. The extra 0V3 needed to turn on the output devices will be supplied by a mere 10 mA of current through the 33R resistors. Resistor R22 forms a feed back loop around the entire output stage to decrease distortion, stabilise the DC output voltage and set the overall gain of the power stage (a process too difficult to go into here).

The op-amp will at all times attempt to make the DC voltage at the output equal to that voltage set up on its positive input. This voltage is determined by the potential divider formed by R18, R19 and R20. Since this is also the main input to the power amp any noise which might be on the positive supply rail(and supplies can get very noisy sometimes!) will be comnunicated directly to the input of the power amp, only to be amplified and applied to the loudspeaker. Capacitor C12 prevents this from happening by bypassing to ground any noise above a frequency of around 0.1 Hz. approximately 250 x 210 x 80 mm. Mount the pots and switches on the front panel, using the pot and switch nuts to secure the front escutcheon if you have one. Mount the output and battery input sockets on the rear panel. If you are using a battery input socket use something different to the output socket (which is usually a two-pin DIN socket or a 6.5 mm jack socket) to avoid confusion.

Mount the power transformer and make the 240 V connections. The mains lead should be terminated immediately inside the case into a terminal block and the earth lead secured firmly to the chassis by a solder lug bolted to the case using a star washer. This lead must be the longest. A length of 240 V cable should be used between the terminal block and the power switch. Wire the transformer to the power switch as shown in the circuit diagram, then wrap the whole switch with insulation tape or enclose in large diameter heat-shrink tubing so that no 240 V connection is exposed.

Finally, the fully-loaded PCB can be secured into the case using short metal spacers. If Veropins are used, all the connections to the board can be made after the board has been mounted. Connect the front panel controls, rear panel sockets and input sockets, using short lengths of shielded cable to make the connections to the two inputs and preamp output.

PROJECT : Guitar Practice Amp



Resistors (all 1/2W, 5%)

390k

47k

6k8

22L

546

242

39k

120k

417

33**R**

22k logarithmic

100 35 V tantalum 100p disc ceramic 150 16 V tantalum

10p disc ceramic

470u 25 V PCB electrolytic 2u2 35 V tantalum

47u 25 V PCB electrolytic

470R

R1,5,11

R3,7

R13

R18

R22

R23

R24.25

RV1,2

C3,4,8, C9 C10 C11,13 C12

C14

Capacitors C1,2,5,6,7 C3,4,8,15

Potentiometers

R 2,6,12,20

R4,8,14,17

R9.10.19

R15,16,21

Fig. 2 Component overlay for the amplifier. The original design used a BC639/BC640 complementary pair for Q6 and Q7, and these are shown on the overlay, but they may prove hard to obtain. Consequently the PCB we will be supplying is laid out for a BC140/BC160 pair, which have different pad layouts — the b,c and e pads are etched onto the board for your guidance.

Powering Up

Make a final check of the wiring and PCB. If all is well, apply power. A slight turn on thump should be heard at the moment of turn on. If the 'Input 1' volume control is now wound up, some hiss should be heard from the loudspeaker. Do the same check on the other input. There is no set-up procedure since the power amp stage is operating in class B and requires no bias adjustment.

BUYLINES

Lots of nice, standard, easy-to-obtain components in this project, so you shouldn't encounter any problems with supply. The PCB will be available fro our PCB Service at the price listed on page 44.

PARTS LIST_

C16	1000u 25 V PCB electrolytic
C17	2200u 25 V PCB electrolytic
Semicon	ductor
JC 1	114201
O14	DCCAD DC100
Q14	BC549 or BC109
QS	BC 557 or BC179
Q6	BC140
Q7	BC160
Q8	TIP31
Q9	TIP32
D1-3	1N914
D4-8	1N4004
Miscella	neous
SK1-4	mono jack sockets
SK5	DIN socket for other type -
	see text)
SW1	DPDT toggle switch (mains
	rated
SW2	DPST toggle switch
Transform	ner (12.0.12.0. 20 VA) TO 3 type PC B.
mountin	hastinks PCR (see Ruylines) care
to cuit a	incations, rep (see Duynnes); case
to suit; n	OUNTINE DATOWARC.

ETI



New CLEAN N CHECK is a unit machine maintenance pack

The patented "Drive Analyser will check in seconds the drive mechanism of your cassette machine to locate faults which can lead to damage and breakdown

If the Drive Analyser shows no fault, then you can confidently use the tape head and capstan cleaning solutions provided to ensure optimum performance

Proper maintenance of any machine should consist not only of cleaning, but also of checking the mechanism

The Clean-n-Check pack contains

- Head cleaning solution.
- . Capstan cleaning solution.

o Cleann C

- . Cotton buds and holder.
- . Drive analyser cassette with indicator registering as faulty/normal/service required soon, on play/rewind/ FFwd functions of your cassette player.

The check drive analyser is presently being used by growing numbers of hi-fi service organisations.



This model is not suitable for use with car cassette players.

CAMBRIDGE LEARNING SELF-INSTRUCTION COURSES

A PRACTICAL DIGITAL ELECTRONIC KIT FOR LESS THAN £20 以



SUITABLE FOR BEGINNERS

Learn the wonders of digital electronics and see how quickly you are designing your own of digital

Splatingtone be used to beginners. BIL switches, resisters, reparting your out creates. The hit contains: swee LS TTL integrated circuits, breathoard, LEDs, and all the build interesting digital circuits; and other rempensate to build integrating digital circuits; and there rempensate to build integrating digital circuits; bills a work clear and there used instruction admost failed available separa-cately). All this comes in a pathet size plastic wallst for only El9-mp inc. VAT and pbp. This course is for true to generate a set of the separate set of the set of the separate set of the set o only Clark

STAN

662 FAN

- needs up coldering tron. soks plenty of questions, but never braves you stuck and helpiess. traches press. about fault-finding, improvisation, and
- subsystem checking.

subsystem checking. • the only entra you need is a GIV battery (Ever Ready 1209, or similar), or a stabilized SV power supply. Using the same breadboard you may construct literally millions of different circuits. This course teaches bockesn legic, going, 8-5 and J-X Ripflops, shift registers. ripple counters, and half-adders. Lock out for our supplementary bits which will demonstrate advanced aeithmetic circuits, opto-electronics, 7-argment displayers. displays etc.

Other self-instruction courses from Combridge Learning Ltd

COMPUTER PROCRAMMING IN BASIC DIGITAL COMPUTER LOGIC AND ELECTRONICS DESIGN OF DIGITAL SYSTEMS C10.50 C 0.50 614.00

Please send for full details (see coupon below).

CHARANTEE So risk to you. If you are not completely solisfied, your memory will be refinded upon return of the item in good condition within 28 days of receipt.

CAMPBRIDGE LEADWING LIMITED, Lum 14 DIVERMILL " PREEPOST, ST 1YES, CAMPS, PAI7 489, ENGLASD, TELEPHONI NY IVES 04001 67446. VAT Nº 313028022 DIVERSILE SITE.

prices include worldwide protage atractl is entra age ask for prepayment invoice . Line A.C. No 7700198.

Please allow	26 deys	fer de livet	TY IN UE	
Please send	e e e e e e e			
	RETES P	619.90		
	details of	your other	self-snotrert	ten reurors.

I 1

Î

for C..... Loorning Ltd ("delete obere applicable)

Please charge Byt Access / American Enpress / Barclaycard / Dimers Club Eurocard / Visa / Mastercharge / Trunkcard · Access

Supery Dote Crodit Card So

Segnature..... Totophone orders from card holders accepted on 0680 67666

Overseas customers (including Eire) should send a bank deaft in sterling drawn on a London bank, or quote credit card

100							

Lant		. Los	raind l	tested.	Lints 34	tivermill fote,	FREEPOST.
Se l	¥#6.	jiho M.C	ingdon,	Camba.	PLI7	ibt, England.	Degistered
in E	malo	nd Be	133876	27.			



If you're about to start on a new project, you're no doubt looking for the right enclosure. With around 1,000 different cases and 250,000 case parts currently in stock, we must be your number one choice. Why not send for our catalogue, price £1 including P&P.

Month	Project	Case	
April 1981	Drum Synthesiner	BOC 668	
June 1981	Antenne Extender	BOA 115	
July 1981	Super Dice	BOC 450G	
September 1981	LAB PSU	SWF 222X	
November 1981	Music Processor	CL2 ADJ	
	Voice over Unit	ACE 150K	
December 1981	TV Sound Tuner	CL2 AFL	
	Component Teater	MIN 030	West Hyde Developments Limiter
		A MIN OTRA	Unit 9, Park Street Industrial Estate, Aylesbury, Bucks
February 1982	I Chino Computer	BOC 708	Telephone: (0296) 20441. Teles:: 03570 W HYDE G
April 1982	Water Heater Controller	BOC 450	

The MICRO-PROFESSOR ...

MICRO-PROFESSOR is a low-cost Z80 based microcomputer which provides you with an interesting and inexpensive way to get into the microprocessor world. MICRO-PROFESSOR is a microprocessor learning tool for students, hobbyists and personnel. It is also an ideal microprocessor educational tool for teaching in schools and universities. Besides. MICRO-PROFESSOR is more than a learning tool. It provides a wide range of applications such that you will be surprised at its amazing power.

The main object of MICRO-PROFESSOR is for the user to understand the software and hardware of a microcomputer easily and conveniently. Besides the complete hardware/software system, you have the User's experiment manual available to you. It includes self-learning text with 20 experiments which range from simple software programming to design a complex electronic game.

2K bytes of monitor source program with documentation is also provided in the manual. It shows how to write system programs including system initialization, keyboard scan, display scan, tape write and tape read.

APPLICATIONS:

MICRO-PROFESSOR

Learning and teaching tool Low cost prototyping tool Low cost development tool Tester

> MICRO-PROFESSOR is a trade mark of Multitech industrial Corporation.

Process controller Electronic game Electronic music box Master mind Timer Noise generator Home appliance control Burglar alarm System control simulation ... and many more.



280 is a trade mark of Zilog Inc.

solves the `mystery' of micro-processors.

TECHNICAL SPECIFICATION

CPU	Z80 CPU high performance microprocessor with 158 instructions
SOFTWARE COMPATIBILITY	Capable of executing Z80/8080/8085 machine language program
RAM	2K bytes expandable to 4K bytes.
ROM	2K bytes of sophisticated monitor expandable to 8K bytes
INPUT/OUTPUT	24 system I/O lines.
MONITOR	2K bytes of sophisticated monitor. It scans the keyboard and executes the command entered immediately after the power is turned on. The monitor includes: system initialization, keyboard scan, display scan tape write and tape read.
DISPLAY	6 digit 0.5" red LED display.
AUDIO CASSETTE INTERFACE	165 bit per second average rate for data transfer between memory and cassette tape.
EXTENSION CONNECTORS	Provides all buses of CPU, channel signals of CTC and 1/O port bus of PIO for user's expansion.
COUNTER TIMER CIRCUITS	Socket is provided. Z80 CTC IC extra
PARALLEL I/O CIRCUITS	Socket is provided. 280-P10 IC extra
SPEAKER AND SPEAKER DRIVER CIRCUITS	A 2.25" - diameter speaker is provided for user's applications.
USER AREA POWER REQUIREMENT	Provides a 3.5" x 1.36" wire wrapping area for user's expansion. Single + 5V DC.
USER'S AND EXPERIMENT MANUAL	Complete self-learning text with experiments and applications
OPTIONS (Prices on application)	Z80 – CTC EPROM programmer board Prototyping board Z80 – PIO Speech synthesiser board Audio Cassette, 2K Ram
KEYBOARD	36 keys including 19 function keys, 16 hex-digit keys and 1 user defined key.
Use the unique MICRO-PROFES	SOR to truely understand the inside workings of microprocessors

Open up a whole new spectrum of projects in home electronics, or simply use the MICRO-PROFESSOR as a practical learning/teaching aid.



Flight Electronics Ltd.

Please allow 21 days for delivery Flight Electronics Ltd. Flight House, Quayside Road, Bitterne Manor, Southampton, Hants SO2 4AD. 0 Tel: (0703) 34003/31323

Surface report manufact convertien from every strate from every SW to SW waters over a state constraint under a state state over a state constraint under a state state	1000 (17160 15" de families Indendade baned 1000 des. Menes for (3.6 - 5" de f1.0	PORODAL & 115-2297 mark Cooper 13,5-0 13,57 mmd 6VA, 61.75 m 19 mR F10, TODODAL & UD-2017 mark Cooper 6 CP. 1975 per uniting Seasonated	WAYNE KERR BROOM 8221 (79 cs. WAYNE KERR (BRVERSAL BROOK 8531 KARCON SIONAL GENERATOR TYRDIO/15 IS ARON SIONAL GENERATOR TYRDIO/15 IS ARON MAL
Fand 100r () New Des 35 + 35 + 1 CONTach Fans 100r Des 45 + Secondarie (2.00 m.	5" Secondred (2.00 cs 6% + 15" time (4.00 cs	TRANSFORMES - Por (1,8) as \$ 10 units 16. Our to anargaments, 18) shot filter, Groy, Buc, Grow 15.80 as 10 of 16). Disastance (1 as	AVO VALVE TESTER CT ND
New He as 10 at 13 PLASE TRANSPORTERS, Sub S	a b - Brit - b" facestary	No and (27.8). No anno lines ar Gray (7.80 an Order Basis data (2.80 an	TILITY PA PRINTING
NE of CE USE AND pales & common	whereas games any so, is an exam.	SOME BAT TRANSFORMERS & CAPACITORS means events or press	Kalitä das purete and rasideri
DAMOND + CONTROLS BOTANY BA	ATCH Single pain 18 way, Printed	VARACE - 2 Any, to approximate Grant conditions (12 as POP (3	POPULA DE RACE CABRET (188)
STOPPOLG MOTORS - 300 Same 20 (andre samples. 13/304 implet. 8 andre. Jehn samples 1304 implet 3 andre. 14 and	Transport for environment (NEV AC 1.2 Anny enjoy. Sweptung or 2004), Output existings from Peak Cean, Can to document to tenter the composition Const Exception (1.2) as PEP (2, 10 off (10) Corresponds	Av 6 or 2 Mar 2 Mar 2
STOPPOLE SOTORS - 5 Vol 13 A	ng agarpton 3 tiles. PPS 8 220, an its cast as a tanks. 12.207 with	Convert the unit to a SUPER SATTERY CRAMES. Advances gram- restance grammer in the second sec	TWE D Book Top This Car DC Difference (D)
wan an Dr Ft SD an 8 fer 15. Sender Pr. 7 Th SPanifen Parten, Sa		called by - high paper resource to control current - partie manifold any near - any national terminals of front panel for conserving tools. Children Part III robust with TA THI Control III.	Trift & Sarah Trans Line Land AC Differenter
ALL AND AN CASE AND	Rip analitier & Nor (1). a 2 2 2 4 4 4 5 1 april 2011 (1).75 cm.	Minutery Walkal &d ang to Date Cats are 10% + 5% + 5%" and 20	TYPE O Common Armente
When Fill AFVECARD PAD See 3 - 2% - 2"	and and it also been beener	extends for new CL2 PyP (6.	TVPD 0 Tomatican Rus Tano (19)
POP (2 00 DON'T TAKE CHANCES Up the prior	- 047 Cable 10p mans. (7.50 100	have provide a school of the second of the second s	TVM a Diffusional Company
AAPO DISCHARGE CAPACITORS -	Ma See 15" de - 5" FLB m	*CODELE SUPERIC Control of the same to for (2.7) a COME Code, v within an annual to 2 metrics. The same to all finds table of (14) https://www.same.com/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/annual/a	TVT 151 Earling.
E M.T. CAPACITOS SE P ETV SE CO OCCUPLING CAPE & Bands 101, 0			Resident type 4334 AC BC colle: ALDED GENERATOR AC DC context, stress coll. Type 7137
CAPACITORS of a to cath. 2004 22	ar Bitt, 5 Banda Mille, 5.5 of Miles.	the stand of the stand and the stand of the	
to to the factor the further the top	Correge Louis saturated the 300°C	Card & Burney Land Trunche (1.48 ep. 18 eff (1.2	Single and Pulling the Source of the Source
BRANCING CAMPACE MERTS &	the fract the scapped Hp on	SOLO STATI Les Tudit Men (1 es 10 el les 1 en 1	
Thanking challers - Al Brand Name Auto 2004 topol 1104 1 Array subput Ch.	B an	Anterior D' anterior D' an Anterior D' D' an, NAA hep 200 04 an Aponeo Anterior by RCA 18 an UALLAND MANY Landed D'D- 18 an HOMPY MALL STAR COURT FAMILY USE and an INCOMPANY	Solid States Video In. be & Ear Sync. (29 cost.
Seller segue San Ciry William San 40 - Seller San Die USe (Dr William Sin 63	- Green Rips and - G - Green (1 and	TVEN 12/40 Million and 10 mile for Part (2 40 Build Traditional Parties ages and 8% million (2 gas and Part (2 4 mile 110	SCOPE STALE CASE was abarded bud envent and man handle. Bank change with prop ip sort 8 cables had concerning but 9
Saller Ingene Sam 2 marridrage City and Saller Saller Ingene Sam 2 marridrage City and Saller Saller Saller & City Saller Ingene Sall (3-4)	1 Anna Ban 2's - 2 - 3" Cl es. Ry using dya The an, 10 all fit.		treates, of the section, 1% mayores 3 means ranks catter, and the section, and the section and PCB (the s Tachella 10000010-catter by the
	005 19 10100 04 040	KAGING & POSTAGE FLID, VAT 41 15% MUST IN A	ded to TOTAL of GOODS & PACKAGING, BUT
PLEASE ensure sufficient in	onice is sent to cover PAC	KAGING and Postage to see data in us dispatching in	Bur order. CALLERS VERY WELCOME STRICTLY SS taken. Official orders wolcome
	C	HILTMEADIT	
NORWO	OD ROAD READ	ING	NE NO. READING 669656
Nonite	Grid survey tell past Reading	Yoshulagi Calago in King's Road than first right look on right fo	and with "Spatial When" I
POTOSA SUPPLY: For mores and	1200 B M	ARCH SALE	0CP12 00 07 500 140 Jet120 200 NoLA 0CP12 00 07 500 120 Jet120 200 300 Jet120 0CP13 00 07 500 200 Jet2 100 200 300 Jet2 100 300
POWER SUPPLY: For manys and TTL Restricted LAVIN: Built tested ALADOVE ress reportering: MER-		ARCH SALE	BC712 BP BF HIS MP PETHOD PBP BC712 BP BF HIS MP PETHOD PBP BC713 BP BF HIS PETHOD PBP PETHOD PBP BC713 BP BF FHIS PBP PETHOD PBP PETHOD BC714 BP PETHOD PBP PETHOD PBP PETHOD BC714 BP PETHOD PBP PETHOD PBP PETHOD BC714 BP PETHOD PETHOD PETHOD PETHOD PETHOD BC714 BP PETHOD PETHOD PETHOD PETHOD
POWER SUPPLET for manage and The Reprinter Laboratory Bulls restore water A ADOVE the transformer Billy PCE for allower of UV of thy CERAINC CAPACITORS (EDV)		ARCH SALE Part	BCCP12 BP BP MB MD JNY1305 ZIP MAUA BCCP13 BP BP MB MD JNY1305 ZIP MAUA BCCP13 BP BP ZIP ZI
POWER SUPPLET. For manys and The Same and the Second Second Second Second Second Second Poli for same or Nor HV CERAMIC CARACTIONS (SEV) Stor to 10 SOCION Control Second Second Second Control Second Second Second Control Second Second Second Control Second Second Second Second Second Second Second Second Second Second Second Second Second Second Second Second Second Second Second Seco		ARCH SALE Part Part Part Kd SAE for built offers Part Part Part Part Kd SAE for built offers Part Part Part Part Maximum file Linit file Part Part Part Part Maximum file Linit file Part Part </td <td>BC(H2) BP BF HIS HP 2HY100 2DP MAIA BC(H2) BP BF HIS HP 2HY100 2DP 2D 2D</td>	BC(H2) BP BF HIS HP 2HY100 2DP MAIA BC(H2) BP BF HIS HP 2HY100 2DP 2D
POINTER SUPPLIES, For manage and The Experiment Lide IV. Built tends without a supervision of the other All ADOVE was transformer with CERA and CARACTORS (STM) Start to the Start On VETYTERIE CARACTORS (STM) Topic to TEXP On VETYTERIE CARACTORS (STM) Topic to TEXP On VETYTERIE CARACTORS (STM) Start to Start Start to Start to Start Start to Start to Start Start Start Start Start Start to Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start Start		ARCH SALE Part A Part	BC2112 BD BF LIB MD APTING FBP MAIA BC2112 BD BF LIB MD APTING FBP
POWER SUPPLY, T. for many and The Experiment LADAR Constrained All ADOVE was investment with PCS for gamma investment with CERAINCE CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN) Supply 5.0.500 - 100 - 100 - 100 CONSTRAINED CAPACITORS (SEN)		ARCH SALE Partial	BCCR12 BP BF HID Mp ZMTIDS ZDP MAIA BCCR12 BP BF HID MP ZMTIDS ZDP MAIA BCCR12 BP BF HID ZDP ZMTIDS ZDP ZMTIDS ZDP MAIA BCCR12 BP BF HID ZDP ZMTIDS ZDP
POWER SUPPLET, For many part The Experiment Lake By Each stand All ADDVR was requirement PCI for spin-set UP of UP PCI for Standard Canadian Constant PCI VESTIGUES CANADIC CANADITIONS (SWIT) PCI VESTIGUES CANADIC CANADITIONS (SWIT) PCI VESTIGUES PCI VESTIGUES		ARCH SALE Part	CCP12 CD DF LID HD ZPT TIGS ZPD MAAA DCCP12 CD DF LID HD ZPT TIGS ZPD ZPD <t< td=""></t<>
POWER SUPPLET, P. For many and The Experiment LADAR AND BURGHT AND AS ADOVE was unaniserant AND PCS for down or UN or VIV CERAANCE CAPACITORS EMPL Date to 3000000 AND PCS VERTHERE CAPACITORS (MICH ON VERTHER CAPACITORS (MICH O			BC2712 BD BF LIB MD APTING FED MAAA BC2712 BD BF LIB MD APTING FED
POWER SUPPLY, T. For many and TTL Expenses LAVIV, Evel hands ALLADVIS are insurance with PCS for gamma LAVIV, Evel CERAINC CAPACITORS (ENV) Def to gamma CAPACITORS (ENV) ALLADVIS AND ALLADVIS CERAINC CAPACITORS (ENV) ALLADVIS AND ALLADVIS ALLADVIS AND ALLADVIS SUPPLY ALLADVIS ALLADVIS ALLADVIS VIEND CAPACITORS (ENV) ALLADVIS ALLADVIS VIEND CAPACITORS (ENV) ALLADVIS ALLADVIS VIEND CAPACITORS (ENV) ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS ALLADVIS			BC(71) BD BF 100 HD 2017120 200 MOAA BC(71) BD BF 100 HD 2017120 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200 200
POINTER SUPPLIE: For manys and The Experiment Labor for Early and All ADOVE was requirement with PCS by class or UN or VN CERAINER CARACTIONS (ETV) Early to NOTION CONTROLLED CARACTIONS (ETV) Day to NOTION CARACTIONS (CARACTIONS (ETV) Day to NOTION CARACTIONS (CARACTIONS (ETV) Day to NOTION CARACTIONS (CARACTIONS (CAV) TO/ to NOTION CARACTIONS (CARACTIONS CARACTIONS (CARACTIONS CARACTIONS (CARACTIONS CARACTIONS (CARACTIONS CARACTIONS) CARACTIONS (CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARACTIONS CARA			BC2712 BD BF LIB HD ZMT120 ZMD ZMD1 BC2713 BD BF LIB HD ZMD1 ZMD ZMD1 ZM
POWER SUPPLY, T. For many and TT. Bagement LAUTY, C. Par many and AS ADOVE was unaview and PCS for down or UN or UV CRAANCE CAPACITORS INTO TOUTY TYTERE CAPACITORS INTO TOUTY TYTERE TOUTY TYTERE CAPACITORS INTO TOUTY TYTERE CAPACITORS INTO TOUTY TYTERE TOUTY TYTERE CAPACITORS INTO TOUTY TYTERE TOUTY TYTERE			BC2712 BP BF MD MD MTIME Pape MAAA BC2712 BP BF MD ATE MTIME Pape MAAA BC2713 BP BF MD ATE MTIME Pape MAAA BC2714 BP BF MD Pape Pap
POINTER SUPPLY, 17, 7 or many and TTL Experiment LADAR W. Built stand ALL ADDVE was executive and ALL ADDVE was executive and PCS for gamma to U.V. V. V. Star CERAANCE CAPACITORS (SEV) Supply 10, 2000°			CC712 C0 DF LID Mp ZPT120 ZD MAA CC712 C0 DF LID Mp ZPT120 ZD ZPT to ZDD
POINTER SUPPLY, T. For many and The Bagement LAVIN. Built stated without a second state of the second Al ADOVE was requirement with PCS by class or UN or VW 1990 CERAANC CAPACITORS (SIM) by 0.00000 and 0.0000 (SIM) COVERTINGUE CAPACITORS (SIM) Covers of UN of the Sol of the LACTRON UNIC CAPACITORS (SIM) Covers of UN of the Sol of the SIM of the Sol of the Sol of the Sol of the Sim of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the SIM of the Sol of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the Sol of the SiM of the Sol of the Sol of the Sol of the SiM of the Sol o			CC171 DD DF LIB MD PFT120 PFD MAAA DC171.3 DD DF LIB MD PFT120 PFD MAAA DC171.3 DD DF LIB PFD PFT120 PFD MAAA DC171.3 DD DF LIB PFD PFT120 PFD MAAA DC171.3 DD DF VID PFD PFT270 PFD MAAA DC171.4 DD DF VID PFD PAAAA PFD MAAA DC171.4 DD DF VID PFD PAAAA PFD MAAA DC171.4 DD DF VID PFD PAAAA PFD MAAA DC172.5 PFD DFVD PFD PAAAA PFD PAAAA DC172.6 PFD DFVD PFD PAAAA PFD PAAAA DC172.7 PFD PFD PAAAA PFD PAAAA PFD PAAAA PFD PAAAA PFD PAAAA PFD
POWER SUPPLY, T. For many and The Experiment LADIEN. Built stands ALL ADDIVE was understand MEADOVE was understand with CERAANCE CAPACITORS INTO CERAANCE CAPACITORS INTO The Stands of UNIT AND ADDIVE CERAANCE CAPACITORS INTO The Stands of UNIT ADDIVE CERAANCE CAPACITORS INTO The Stands of UNIT ADDIVE STANDARD OF THE STANDARD OF THE ELECTRON VICE CAPACITORS INTO THE STANDARD OF THE STANDARD OF STANDARD OF THE STANDARD OF STANDARD OF THE STANDARD OF STANDARD OF THE STANDARD OF THE STANDARD OF THE STANDARD O			BC2712 BP BF LIB Mp MPTIDS Pape MAAA BC2712 BP BF LIB Mp MPTIDS Pape MAAA BC2713 BP BF LIB Mp MPTIDS Pape MAAA BC2714 BP BF LIB Mp MPTIDS Pape MPTIDS Pape BC2714 BP SPTID Pape MPTIDS Pape MPTIDS Pape Pape BC2714 BP SPTID Pape MPTIDS Pape
POWER SUPPLY, Y, Pay many and The Experiment LAVIEW End testand ALL ADDVE was experimental MED PCS for down or UN or VW 1989 CERAINCE CAPACITORS (EEV) Supply to 30 CODE COLORING CAPACITORS (EEV) Supply to 30 CODE COLORING CAPACITORS (EEV) To 30 CODE CODE COLORING OF THE CAPACITORS (EEV) TO A VERTER (EEV) TO A VERTER CAPACITORS (EEV) TO A VERTER CAPACITORS (EEV)	U 2010 CONTRACTOR CONT		CC712 CD DF LID HD HD HT HD HT HD HT HD
POINTER SUPPLY, T. For many and The Baseman LADVIN, Bull status ALADOVE was unaversary bits PCE for down or UNP of W. BEAAMC CAPACITORS SIMP CERAAMC CAPACITORS SIMP CREAMER CAPACITORS SIMP CREAMER CAPACITORS SIMP CREAMER CAPACITORS SIMP CREATING CAPACITORS (SIMP) CREATING (SIMP) CREATING CAPACITORS (SIMP) CREATING CAPACITORS (SIMP) (SIMP) CREATING CAPAC			CC712 DD DF LIM MD MTIME FROM DC712 DD DF LIM MD MTIME FROM MD
PONULIE SUPPLY, T. Fur manage and The Experiment LADVIN. Built stands MALADOVE was understand with the supervised LADVIN. Built stands CERAANCE CAPACITORS (STAT) Deck for supervised and the supervised CERAANCE CAPACITORS (STAT) Day to SUBJ SUBJ AND AND AND AND AND CERAANCE CAPACITORS (STAT) Day to SUBJ Day of the supervised of the SUBJ Day of the SUBJ Day of ELACETER, TTE CAPACITORS (SUBJ Day 12) Mg. and the SubJ Day ELACETER, TTE CAPACITORS (SUBJ Day 12) Mg. and the SubJ Day ELACETER, TTE CAPACITORS (SUBJ Day 12) Mg. and the SubJ Day PERCE SUBJ Day of the SUBJ Day SUBJ Day SUBJ DAY SUBJ DAY SUBJ Day SUBJ Day of the SUBJ Day SUBJ Day SUBJ DAY SUBJ DAY SUBJ DAY SUBJ D			SC272 SP (M) Mp (M) MP (M) MP (M) MP (M) SC272 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC271 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC271 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC271 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC271 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC271 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC271 SP (M) SP (M) Mp (M) Mp (M) Mp (M) SC270 SP (M) Mp (M) Mp (M) Mp (M) Mp (M) SC280 SP (M) Mp (M) Mp (M) Mp (M) Mp (M) SC280 SP (M) Mp (M) Mp (M) Mp (M) Mp (M) SC280 SP (M) Mp (M) Mp (M) Mp (M) Mp (M) SC280 Mp (M) Mp (M) Mp (M) </td
POWER SUPPLY, Y. P. J. Improve and TY. Expansion LADVIN. Built sense ALL ADVING two providences and ALL ADVING two providences and PCS for generative and two pro- rest of the sense of LYA or YW. SERVING CERALING CAPACITORS (EEV) Supply to SCOPE CONTROL VIEW CAPACITORS (EEV) ALL ADVING DE LADAL OF ALL CONTROL VIEW CAPACITORS (EEV) SUPPLY SUPPLY CAPACITORS (EEV) ALL ADVING DE LADAL OF ALL CONTROL VIEW CAPACITORS (EEV) SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY CONTROL VIEW CAPACITORS (EEV) ADVING DE LADAL OF ALL OF A SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY SUPPLY			BC272 BP FAIR Mp ANTING Part 100 Part 10
POWER SUPPLY, T. For many and The Baseman LADVE Build states AS ADOVE was unaverage with PCS for down or UNP of W. Bay CERAANC CAPACITORS SUPPL CONTENT REAL AND THE SUPPLY CERAANCE CAPACITORS SUPPLY CONTENTS IN A CONTENT OF SUPPLY CONTENTS IN A CONTENT OF SUPPLY CONTENTS OF SUPPLY AND SUPPLY CONTENTS OF SUPPLY CONTENTS OF SUPPLY AND SUPPLY CONTENTS OF SUPPLY CONTENTS OF SUPPLY AND SUPPLY CONTENTS OF SUPPLY C			CC712 DD DF LID HD HT LD FFT LD HD HD CC712 DD DF LID HD HT LD HT LD HD <
PONULIE SUPPLY, Tr. For manage and Th. Expansed LADVIV. Built states ALADVIE was unaview bits PCS for down or UN- VIV. BAR CERAANCE CAPACITORS INTO Day to SUDO CONTENTION CAPACITORS INTO The Content of the VIV. State and to SUDA Day of the Content of the SUBAR Day of the Content of SUBAR DAY SUBAR DAY INTO ELACTRON VTIC CAPACITORS INTO The Content of the Content of SUBAR DAY OF THE CAPACITORS INTO THE CONTENT OF THE SUB- CONTENTS OF THE CONTENT OF THE ELACTRON VTIC CAPACITORS INTO The Content of the Content of SUBAR DAY OF THE CONTENT OF THE ELACTRON VTIC CAPACITORS INTO THE CONTENT OF THE SUB- CONTENT OF THE CONTENT OF THE SUBAR DAY OF THE SUBAR DAY INTO THE SUBAR DAY OF THE SUB- CONTENT OF THE SUBAR DAY INTO THE SUBAR DAY OF THE SUBAR DAY INTO THE OF CONTENT OF THE SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF THE SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF THE SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF THE SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF THE SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF THE SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF SUBAR DAY INTO THE SUBAR DAY INTO THE SUBAR DAY OF SUBAR DAY INTO THE SUBAR DAY INTON			CC712 DD DF LIM MD MTIME FPL MAIA DC713 DD DF LIM MD MTIME FPL MD MTIME FPL MD MTIME FPL
POWER SUPPLY, Y. P. P. march and The Expansion LADIEV. Built heads All ADOVE was experiments. May PCS by device or UN- VIV. Exp CERAINCE CAPACITORS (ENV) Supply 10, 00000° PCS by device or UN- VIV. Exp CERAINCE CAPACITORS (ENV) Supply 10, 0000° PCS by device or UN- VIV. Exp CERAINCE CAPACITORS (ENV) Supply 10, 0000° PCS VERTHER CAPACITORS (ENV) FOR TO SUPPLY IN FOR COMMING COMPANY IN THE CAPACITORS (ENV) FOR TO SUPPLY IN FOR COMMING COMPANY IN TO 20 OF COMMING COMPANY IN TO 20 OF COMMING COMPANY IN THE CAPACITORS (ENV) FOR TAXING DATE OF COMMING COMPANY IN THE CAPACITORS (ENV) FOR TAXING DATE OF COMMING COMPANY IN THE CAPACITORS (ENV) FOR TAXING DATE OF COMMING COMMING THE COMMING OF COMMING COMMING TAXING DATE OF COMMING TAXING COMMING TAXING DATE OF COMMING TAXING DATE COMMING TAXING DATE OF COMMING TAXING TAXING DATE COMMING TAXING DATE OF COMMING TAXING TAXI			
POWER SUPPLY, Y. P. J. Improve and TY, Expansion LAVIV, Bull Sector ALA ADDVE was insurface and MEADVE was insurface and the sector of UN or VIV 1990 CERAINED CAPACITORS (SEN) In Construction of UN or VIV 1990 CERAINED CAPACITORS (SEN) In Construction of UN of VIV 1990 CERAINED CAPACITORS (SEN) In Construction of UN of UN of VIV 1990 IN 1990 CERAINED (SECTORS) INFO UNITY INSUE CAPACITORS (SEN) INFO UNITY INSUE OF INSUE CAPACITORS INFO UNITY INSUE CAPACITORS (SEN) INFO UNITY INSUE OF INSUE CAPACITORS (CAPACITORS (SEN) INSUE CAPACITORS (SEN) INFO UNITY INSUE OF INSUE CAPACITORS (SEN) INSUE OF INSUE OF INSUE OF INSUE (SEN) INSUE OF INSUE OF INSUE CAPACITORS (SEN) INSUE OF INS			
PONULIE SUPPLY, T. Fur manage and The Experiment LADAR IV. Built status ALADARYS was unavailances: Million 2010 and 100 and 100 and 100 and CERAANCE CANACTTORS INTO CERAANCE CANACTTORS INTO Data to SUPA 2010 and 100 and 100 and the SUPPLY and 100 and 100 and 100 and Data to SUPA 2010 and 100 and 100 and 100 and Data to SUPA 2010 and 100 and 100 and 100 and Data to SUPA 2010 and 100 and 100 and 100 and Data to SUPA 2010 and 100 and 100 and 100 and Data to SUPA 2010 and 100 and 100 and 100 and Data to SUPA 2010 and 100 and 100 and 100			
PONISE SUPPLY, V. P. W. Increases and The Experiment LADER. Build States All ADOVE was experimentary Map PCS by device or UNA VIEW CERALANCE CAPACITORS (ENV) Supply 10, 000000 CERALANCE CAPACITORS (ENV) Supply 10, 000000 CERALANCE CAPACITORS (ENV) Supply 10, 000000 CERALANCE CAPACITORS (ENV) Supply 10, 000000 CERALANCE CAPACITORS (ENV) Supply 10, 000000 CERALET DO, 100000 CERALET DO, 1000000 CERALET DO, 100000 CERALET DO, 100000 CERALET DO, 100000 CERALET DO, 1000000 CERALET DO, 100000 CERALET DO, 1000000 CERALET DO, 10000000000 CERALET			
POWER SUPPLY, T. For many and The Experiment LAVIEW End handle ALL ADDVE was experiments with PCS for down or UNA of W. 1999 CERAANCE CAPACITORS (EDV) Supply 5.00000 CERAANCE CAPACITORS (EDV) Supply 5.00000 TO VETTING CAPACITORS (EDV) SUPPLY 5.00000 SUPPLY 5.000000 SUPPLY 5.00000 SUPPLY 5.000000 SUPPLY 5.00000 SUPPLY 5.000000 SUPPLY 5.0000000 SUPPLY 5.0000000 SUPPLY 5.0000000 SUPPLY 5.0000000 SUPPLY 5.0000000 SUPPLY 5.0000000 SUPPLY 5.00000000 SUPPLY 5.00000000 SUPPLY 5.00000000 SUPPLY 5.0000000 SUPPLY 5.0000000000 SUPPLY 5.0000000			

ETI APRIL 1982

5

movinc

the new MC88E from

The new MC88E represents a breakthrough in high output moving coil cartridges. No step-up device or amp is required and it is available at a sensational price of only £29.95. yet generating high magnet-

The high output voltage of 2.5mV does away with the of 17 cu's. The result is a add to the expense of using range of 20Hz - 40KHz, most previous moving coil cartridges.

just how advanced the tech- conventional cartridges. nology that has produced this breakthrough is - a miniaturised and specially shaped armature; unique coil winding technique; a magnet that is so compact.

ic flux density; compliance need for a head amplifier or cartridge with flat frequency step-up transformer, which response over the super wide removing the distortion caused by certain frequencies. We can t emphasise enough, which can be found in many Coral's considerable experience in moving coil cartridges has enabled them to offer the ultimate in quality and performance at this incredibly low price.

We welcome callers to our South London Showroom for demonstrations.

• Engiries and information phone: 01-690 8511, Ex. 32. All products are only available direct or from selected. authorised dealers throughout the U.K.



BATTERIES NIC rechargasble, GE buttons or tabs	AD unvented BRID Hitsch state MDA1 PM7A	GES 100 32p 12 64p	W005 25p W02/4 26p 55840 44p	1	
C'UILLBAH12 C'UILLBAH12 D'U24AH12V PP3.05AH12V CHARGER for all t	(2.00) (2.00) (2.02) (2.12) (2.13) (2.13) (2.13) (2.13) (2.13) (2.13) (2.14) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2.15) (2	RS 8 3v to 18v 1/85 1W 3v	3 to 33v 7p	I SAARCAS	
ELECTROLYTIC	PLUG IN LEAD	5 05	BUZZER 12V		PS1 AA
Bo mm	22/60v 11x5	5mm Jo	FUSES	No Court	AB 67
1 13x6 2.2 13x6 3.3 13x6	4.7/63v 11=6 10/63v 12=8 22/35v 13=8	5p 7p 8p	100mA 500m4 1A/2A	ACH ID ACH ID AC	TIME COOR
8.8 13a7 10p	47/38v 12x10 100/26v 13x10 220/36v 17x10	50 50 90	6p	S Twee S	A NE
22 19±9 47 19±10 100 21±13	1000/100 TAGS 1500 6v3 25 x 15	11p 39p 17p	PCB FUSE CUPS 20	AC RM 110/100 1170 1170 1170 1170	C FMF
220 31:13	CERAMIC BE 10PF - 3K3PF	- EG ONLY.	bp	DIES MTO IND	A Rayer 1 Buger 1
TOL 10% BY EVO	Aller Sp PCM	125 T Green	11.208	GOO S A 5 M S	MILOO MILOO
.0022/400v 11 .0033/400v 11 .0047/400v 11	33/100v 15 33/100v 15 37/280v 22 0 00/100v 15	Yellow 2' TH	220 120	CETOR CETOR CETOR CETOR CETOR CETOR CETOR CETOR	50K Du 772CA F 172CA F HOLD S PP3. CM 778 CM 778 INAL P
.01/630v 10 .022/280v 10 .033/250v 10	All at 12p 1.0/100v 15 1.5/100 22	Red Yellow BIG DI	10p 13p SCOUNTS	CAPA CAPA	POTS SOULC HELAU VALVI SPEAU SUAP SUAP SUAP SUAP
047/100v 10 .000/100v 10 .1/200v 10	2.2/100 22 All at 18p 3.3/100v 22	2 CLIP	BULK		
POLVESTER AXL	0% TANT BEAD Sm	n 20%		z	
01-400- 33-10 022-250- 47-25 047-250- 68-40	0v .1. 36 0v .22 36 0v .47 35	7p 43 8p 10	25 12p 25 24p	IEMS	.T.C
1 160v 1 0 25 22 400v 1 5 10	0. 10 36 1 0. 2.2 20 1	2p 100 2p 150	10 340 96 400	Y OR	S 1
0100ES by ITT, MI AA215 . 9p BAX12/16 3p	ALL SESCOSEM, TEXA OA47 5p OA40/01 6p	IN 1000ED 11/916 11/4001	12 30	EVER OT	TEL.
84127 7p 87127 7p 87205 19p	0A200/2 11p RPG108 3p S28A/71 90p	1N4004 1N4007 1941249	3 Yip 6p 2p	S MITH VITH	L L
8YX10 30p CV8790 5p	14270 6p 14914 2p	IN5401	/2 11p	NES NES	O H'Z
ICe DIL PlishihiG (301 (8) 22p 308 (8) 42p	565 (8) 19p 565 (14) 42p	747 (14 1310 (1 1458 (8	44 49p 27p		STAP
311 (8) 41p 324 (14) 36p 339 (14) 44p	565 (144 95p 567 (8) 95p 708 (14) 21p	3046 (1 3080 (8 3140 (8	4) 59p 1 83p 1 82p		SHE SHE
380 (14) 06p 380 (14) 05p 381 (14) 64p	710(14) 32p 725-181 £1.38 741 (8) 15p	3900 (1 3914 (1 13800 (4) 43p 8) 62.36 16) 99p	STOC ENOI DETA	NE3 O
ICs OIL PINNING	-) MISC				111
TLOE2P (81 98p LF351 (80 64p LF353 (80 98p	2114N 200 C1 20 4116 200 10p 8116 450 C1 20	5821P4 6850P () 6852 (24	401 C1.68 241 C1.68 61 C2.45		
214414 (3) [2,34 21425 (16) [3,40	6800P (40) 22.87 6802P (40) 25.81	8085A 8	01 (2.75 40 (5.76	TION	-
ICo LPB 74LS N	CMOS BUF 40 N	ф (74 N	SCRII	
00 10p 74 16p 02 12p 10 30p 04 12p 109 24p 05 12p 122 44=	01 12p 16 34p 02 12p 17 48p 06 48p 18 48p	29 48p 40 48p 41 52p	00 to 40 19p 42 24p	DE	
08 14p 138 38p 10 12p 240 75p 14 38p 244 76p	00 52p 21 54p 11 16p 22 54p 12 20p 21 16p	46 80p 49 28p	51 15p 70 17p		
27 14p 367 38p 30 12p 374 72p 33 16p	13 34p 24 42p 14 48p 25 12p 15 48p 27 38p	66 34p 69 16p 81 20p	132 69p 193 96p i 194 36p i		1 1
SOCKETS GOL	2 490 D T.J. & PIN 70, 14 PIN 8	93 38p . 16 PHH 9p	107 GCP	>	
POTS CERMET H	V. STANFORD 24 Pin 1 ORIZ round plug in 50R,	100R, 10K,	100K 11p	0	
RESISTORS	E12 % W C FILM 5% 1g BT 105 77p BT 151 Bbp C 20463 77p 245061 %	M FILM 21 1060 35p	3p		500
SWITCH PUSI 250v 17p ROCKER	BUTTON PCB MTG 6P	IN MAKE 8	REAK 250- 190		
TRANSISTORS AC127/8 25p AC176 25p	80232/6/8 29p 90537/8 33p 80675A 49p	1193056 11543 11590/01	430 27p 8p		L L L
AD161/2 28p AD161/2 28p AU113 (1.61	8F258 9 24p 8F258 9 24p 8F337/8 21p	273(212A 2N695/8 2N918/30	6p 19p 0 150		d b DTA
BC108/8 12p 8C109 10p 8C109 10p	8FY50 51 190 8RY38 24p	2%1613 2%1711 2%2218/1	280 19p 150		
6C141/2/3 19p 8C177/8/9 12p 8C182/8/L 6p	85129 19p 80126 £1.02 80205.6 950	2N2369A 2N2646 2N2865.3	160 NIT		
BC183/B/L 6p BC184/B/LB 9p BC212/8 6p	8U208 83p 8U326A 61.02 8U787 69p	2N3053 2N3054 2N3055	22p 21p		ER E
BC214/B/LB 9p BC237 8 9p BC238 6p	MU2501 E1.09 MU2001 E1.09 MUE340 30p	2N3442 2N3702/4 2N3708/1	590 G 70 G		ORD
8C327/8 9p 8C337/8 9p 8C477/8 9p	MPSA05 14 14p MPSA05 14 14p MPSA42:3 12p	2N3771/2 2N3773 2N3804 6	130 C		HLI HLI
8C5478 30 8C5488 3p 8C5498 3n	0C38/71 890 T(P29/30 17p T(P31A/82A 200	2N5320 2 2N5447/9	29p C 9p S		H W at 1
8C567/8/8 9p 8CV76/71 14p 8D112/116 69p	TIP41A/42A 37p TIP47 21p TIP110/115 37p	2N5550 2N6028 2N6107/8	12p 12p 37p	E	CAS
80131/2 250 80135/6 220	TIP121/126 36p TIP2566 43p .	2N6385 784820	69p 47p	NAN	Pay
LM 309K £1.12 LM 317K £2.36	LM 723H 28p LM7805/15 42p	LM78	12 330 O	<00 c	w w w

EX STOCKI Image: Construction of the state o	. £4.95 . £5.95 . £5.95 . £6.95 . £11.44	Kit keyboard £20.75 Built keyboard £25.75 Case for keyboard £10.30 Built keyboard in case £36.15 16 bit LED board (kit) £9.50 24 line in/out port £16.95 built £18.96 3 channel music bd £18.95 Motherboard with 2 connectors £15.75 built £18.95 Motherboard with 2 connectors £15.75 built £18.50 23 way edge connector £2.95 23 way male connector £1.30
ACTION OF THE PARTY OF THE PART		
DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY, MAN DILY,	Al Freedows for 2 of the system Al Freedows for 2 of the system PIEZO TWO PIEZO TWO ORDER BY POST AUDI SOIL Edward Tet 01 Also at Hear	A server All Food of. Someters Bill Freedoms Server All Food of. Someters Serv

MICRO 19 Mill St., Bodefe EX39 2JR, Englas Telephone Bidefo	TIMES wid, North Devon ad (ETLA) rd (023 72) 79750		ACCESS BUILDAYLARD
		nc philad suf ma 5 non-shares alan. Na tara dijan Optana 622.55	Served, Univ., Office Onterfreedments Ad reaso served rem. Mr eggs
	ATTO POD DDC Trives of horo- Unions Po May Ugo Antonioni APPER SOLD Sold Trive Ga Sol Trive G	Amountains Amountains Sampion C.1.00 Sampion C.1.00 (5.00 C.1.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (5.00 (CADD AND TO SHOULD HERE AND AND TO SHOULD HERE AND AND TWING PRECED ON REQUEST WITH COMPLEX ON THE COMPLEX ON T
	COMPACT Care Comp (1) Obj 1. Chan (1)	(1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (1000 (CONTURTING OF GHE & HOS STANDARD Compares 5.2 The West Standard Compares 5.2 The West Standard Compares 5.2 The West Standard Compares 5.2 The West Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard Standard
616 16 16 18 18 18 18 18 18 18 18 18 18 18 18 18		100 100 10 10 10 10 10 10 10 10 10 10 10	OF EPHONES Restaurer Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest Rest R
	201500 (140) 2015101 (140) 2015101 (140) 2015101 (140) 201501 (110) 201501 (110) 201501 (110) 201501 (110) 20150 (111111 111111 111111 111111 111111 11111	VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOLTAGE VOL

Нарру М	em	Or	ies
Part type	1 off	25-99	100 up
4116 200ns 4116 250ns 2114 200ns Low power 2114 460ns Low power 4118 250ns 6116 150ns CMOS 2708 460ns 2716 460ns 6 volt 2716 460ns three rail 2732 450ns Intel type	.96 .90 1.20 1.10 3.25 4.95 1.96 2.25 6.40 4.25	.86 .80 1.10 1.00 2.95 4.45 1.85 2.15 6.00 3.96	.65 .60 .95 .85 2.66 3.65 1.75 1.96 4.96
2532 450ns Texas type 280A-CPU (4.75 280A P10 Low profile IC sockets: Pins 8 20 15p 22 18p 24 19	4.25 64.25 pp. 14 10	3.95 280A-CT p. 16 11p 0 13p	3.36 3.36 C £4.25 18 14p,
Soft secotred floppy discs per 1 6 Inch SSD (17.00 5 Inch SSDD 8 Inch SSD (19.25 8 Inch SSDD	10 in plasti E19 25 5 k E23 65 8 k	c library cu nch DSDD nch DSDD	660: 621.00 625.50
Access & Barclevcard welcome	Write or pl orders und	hane for lis ler (15 and	VAT to
Government & Educational ord Trede accounts operated, p Prices are still tending to drop, s buy	ers welcom hone or wr shone for a	ne, £15 min ite for deta quote bei	inum its fore you

Happy Memories (ETI), Gladestry, Kington. Herefordshire HR5 3NY Tel: (054 422) 618 or 628

1



New production capacity at Canterbury has increased our range. decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types Order using

		-		the FREEPOST	ALC: NO
		7 X 44 7	1.10	Trade enquiries are Support of upd number and and regimes name	weicome.
afs)a treatherne	KB2473554	55 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0			1 100 100 100 100 100 100 100 100 100 1
	12112120000	81.500 5 60 5 60 5 60 5 60 5 60 5 60 5 60	0 0 00 0 0,00 00 0 0		
1.555				1000 0.4.4 1000 0.4.2 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 1000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000 0.0 10000	
sick and			10-m - 1* 61 - 0 0		

INFORTANT' Regulation — All velopes general are PULL LONG, Passe and regulation figure to secondary velope to obtain all fault velope.

The bonefits of ILP toroidal transformers

ILP baseds transformers are unity helt the weight and height of their laminuted equivalentitis, and are available with 1104, 2204 or 2404 primiumes coded as follows

For 1904 primary meet "O in place of "E in type number

For 2204 primary (Europe) ment. 1" in place of "IL" in type number

For 2409 primary (UII) insert 2" in place of 11 in type number

How to order Prospect

Here to arbitr Presport. Uto File Coupon or a separatile sineet of paper, to order these products or any products from other IL-P Electronics advertisements. No stamp is needed 4 you address to Freepost. Chaptes and postal orders must be created and paulos to the PEterborius L to cash meast be regedened. C.O. D. — add SE to table order value. Access and Barcancard electronic Al UE orders such product of descept of incompt of order for single and unal quantity orders. Also eventstin of Hastmaine. Major: Washalls. Retrievalue of statutes Electronics.

-----Plasse send me the following B.P. mobules -Konclese Chapue Plane Gabli my Access /Burchycard No Nove Acoress Spanne Part to: 4.9 Electronics LLB: Proposit 2: Scillion Balt mouse: Passe Date Contentiony C12 3(2): Rorit, Englishe Response (M277): Scillion (M277): Galt Scillion (M277) ET 1/4 9 0 mm d TRANSFORMERS AY AHEAD.STA







by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2. retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

POPULAR HI-FI

Switching to the Minimaus from any of the others produced an open and natural sound as though something had been taken away. It had, the colour-ation had gone." Comparative test OCTOBER 1978.

HI-FI ANSWERS Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound 10 big!" JANUARY 1875

PRACTICAL HI-FI & Audio The depth, clarity and openness of sound produced is quite astonishing", JUNE "75 WHAT HI-FI

. the ability of the Mini-

max to take a lot of power and still sound good could be decisive" - Comparative t Comparative test. APRIL 1977.

PRACTICAL HI-FI The little Videotone scored highly for such a small inexpen-JANUARY 1981.

Specification: ecommended amplifier power: 10 to 40 wetts rms into 8 ohms. 80Hz - 20KHz 1 5dB. Frequency Respon Inish: natural teak, veneer with black frets. Size: 10 7/8" high, 6 3/6" unde 7 1/2" deep. Weight: 4.1 Kgs (9 lbs) each.

ONLY (69 95 A PAIR

• We welcome callers to our South London Showroom for demonstrations.

• Engiries and information phone: 01-690 8511, Ex. 32 All products are only available direct or from selected authorised dealers throughout the U.K.



ENTRY FORM

CRIMSON COMPETITION

IGNITION COMPETITION

1

2 **BIRTHDAY COMPETITION** 1.-2.

3				
4	100 C			
5				
6.	The second second		1	
7				
8				
0				
10				
11				_
12				_
12		0		_
13		_		_
14				
15,				
10	_	_	_	
17		_	_	
18				_
19				
20				_

VERO COMPETITION

1.... 2.

3.

CASIO COMPETITION

The answer is .

to six decimal places.

RULES_

Choing date is April 19th 1912, and all entries path moleculater than this date will be discussed. The coupen provided in the magazing must be used Photocopies are NOP acceptable. Implements of ASP and their relatives are not obgible to 3. 4 diper decision is to be considered final and produces will be entered into compressing Name Address_

IMPUTER WAREH MONDAY SATURDAY WIRE WRAP SETS.

26a 268

BULK BUY SPECIALS

RAM SCOOP 4110 200 45 0 10 (12.05 4154 200 85 (3.54 each 2102 656 65 8 for C5.50 ----

TELETYPE ASR33 1/O TERMINALS



From £195 - CAR - VAT my standard ASR33 data to mo, including ASCII toyboard Many features and protect for data I/O, oute data datact circulary, 15232 cand interface, 114 basis, 8 to paper teor punch and reader for off time data proparation and redevelopity charge and relation data storage. Supand. d in good condition and in working order transf. From Ward (12,54 - VAT

1983) was 20m any markers (136 00 - 1817 Sound proof enclosure C25 00 + VAT

DIABLO S30 DISK DRIVES

Another phone at allows us to offer your even grapter savings on this superb 2.5 MB formatted hard disk gries. Two types are eventable both fully refurbished and electronically identical, the only difference to the convenience of changing the disk

mete.

mcca. B30 france leader, such change via france destriction of the set state of the set state of the set of t

Correspo & insurence on eners (15.00 + up hely DEC REOS MOVA TEXAS comparates forther mis-

MAINS FILTERS

. . 505 A10 5 arro (8 86

DC SYSTEM SUPPLY

and 240 Vice operations for the second secon 00

NATIONAL MA 1012 LED **CLOCK MODULE**

12 HOUR + ALARM + 50/80 HZ

me module as used in most ALARMACLOCK dos today the only difference is our price! All effortions are mounted on a PCB measuring only a 12" and by addition of a fee selectes and 5.16 - sp and by addition of a few switches and 6/16 pile AC you have a multi-function damn cock at a action of cost. Other features insteads encour mark on pile, alarm set, power fail indicates, feature accords current, machulated damn output dit. pland brand new with he data only E5.25

0/

10



the part th analysis of the bring you the mail C 's Te Carb. P.C.B. L. Seben a Constraint nes. Be ----The the BARGAIN PARCEL OF A LIFETH to all companients of groupshay preasi of to be worth at least 3 since what you the wo ment on Sold by weight 566 C 6.75- pp C1.80 2066 C15.30- pp C6.75 2.566 (4.75-00 (1.25 1000 (11.75-10 (2.25

----"OLIVETTI TE300" PRINTER/TERMINALS

CONNECTORS

1.10

1.20

1.30

A complete L/D terminet with integral 8 hole paper tape punch and reader, full ASCII heyboard, 120 column printer, and control

unit. The primer is capable of 150 baud with a serier TTL, or balanced input-output add in good overall condition but unsetted Complete

with circuit ungluaranteed. Connect direct to your micro at ONLY (199.00 + £11.50 car +

0.05

1.00



24 Pes Yers 28p

14 Pm Gatt 22a

18 Pm Batt 24p

100 PCL Min Bat

Ones upon an on any plantit in other tax separt Passe happy link, and happ to unless much of my province of all he first any highlight out of the sum the second for the shade of the second bar Security Section (e) and (e) a

12. 0 100 mp (X. ant / Saf's and annually a ball familing beraufer & Saf and C. and a family be antimated to plan a famil of other vallages. All angent an bragte of to be best part on residen put minute out on the balance of to use as that fore tents Bith energy species 200v meter spot. They are as GPD and may have mixer memoires on the form partic. C16 50 cm + C2 50 p+p cm to an and a cm to a c

Get intermetion on 1000 a of stock 18.30 to 0900 IT'S FREE!

NOW OPEN

9.30 5 30

C10

GATA CASSITTES

10 for (5 75

Int WAT

140 BOC PL6 10.

75 () BHC PLS 100

HIGH SPEED

A sugar part of expressing reals by \$1 Late Lat. Do

n and speed" ages to the DPL the Marter 13 is and the factor of the factor o

same little hand hit home SUB/1288 must

en ener (en e) en eren ter en te

Augusta anagina anto Pill as (185.00 + (3.50 antags + 181 "Parameter day to apartal to antantar to Pills

DISTEL ©

Dial our Database!

10.00

dar das bits Mars fathers out

PLIM PLE Ma

saras ser al

SOFTY 1 & 2 seare development output notifies and for despect busis, da, Erabas apon hast aurgery or 2716, 2700 an os apos, rands EPROMS or omotions (PROM/ROM/ROM

and while deploying contents on definition TV is tabletta (118 - ear - 1817 Optional 2718, 2718 notae Card (no - 1917 PBU (220 - (1.80 can - 1917) Sate 21 to 2716/2722 (189 - 1917)

> 9" VIDEO MONITORS

En-antinenest #" Materia Value Mondars 75 Q came lipst, wend but expensioni. 639.95 +67.56 carriage + WIT, Complete with creati

SEMICONDUCTOR **GRAB BAGS**

a di an "anna dia bapti" ranga at 16 175, anna 66 5 1804 mani "Angley 175," près taga at a près albuit s

H

FULLY CASED

ASCII CODED

A state the trans are PRECE and the event addressing early. The 7100 angle state 0 00 - 440 results are grant a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 MB (7200 a season 0.8 M 100, 0 16 M 1

(235.00 + 3.50 upr + up (266.00 + 3.50 upr + up (20 00 and (8 00 at the first of d)

n coor FBL eners 2 040 eners (38.50 + ser + set in coor fills eners) determine (18.50 + set 10 es, the set

COOLING FAN SPECIAL

THE OWNER AND A DAY

08 11 DA TROBUCE P

12 5 4 5 with large large BAAND HERE \$10 Massedard of all ar marting



Dopt E T.L. 64-66 Muller M. Thomas H INFORMATION Croydes, Serrey, Tet 81 080 7782 or 81 689 0800 an second of prices inclusion of VAT. Cash with order Uniper all's enter rakup (2.00 Prices and Pastage quetted for UIL only. Where past and pattern nut indicated places and 80p per anter. Suns Petro consumt orders maximum (20.00. Queen and teate enquiries watcome. Orders despetche some day where privates, 3% surphargs on Access and Barcantant orders

KEYBOARDS	
Entering and Entering	
Singly fair for U.S.A. made by the cord Minard WHE Server of cased francessing serveral for manual of the mage section usery right form	
Important to basis set det. Til o Calif. and ar-based tors process to longerest fundant, of RCA basis parameter	
UPDR 7 bis Suly coded ausput with demyod deales on. UPDR Surveys UPDR with research and	122
VPRES Saver, ACCO. 2004 and TTL colpet, with 6 estactable Band Fores VERS Saver or UPPE, with moment and	(14.20 (14.34
Prog and cases for WHIL WHIT (2.25 Prog for WHIL WHIL EXTEN	(1 B)
CHEER NOW OF SENS FOR BITALS	
SVD.C. POWER SUPP Sillioning the reason Sill OV - demon	

rang but ut nt inne



A complete L/O term

in ball another eventues at the effort star Fig. A nearest tail purchase evolution of to other yes the engand production of protein of a to better of the fits material case of our (2005), Unitary dis very takent is many purchases to charactery, if there is a heat of factors with of electronics do not play to PCB and takent to prochasion and you will be made and the manual of the regurdential of the mast exerting

LX180L MATRIX PRINTER

STANDARD FUELCHICK CONTRACTORS - Fuel ASCIT character set - Standard at - Adam - Fiszer, VOIt spage exerciser - 2 case contracted band reads up to 1800 - 18 contractors per load - Product reactage - 2 case contracted band reads up ports - 4 happe forms, solar porget, double verdit, solar logis, contracted by the contract of perdate ports - 4 happe forms, solar porget, double verdit, solar logis, contracted - United verdit, contracted by to 1900 - 190 contractors per load - Product reacting of the 19 moles - Said contracted before to 1900 - 190 contractors of 770 specific periods contracted by the 19 moles - Said contracted construction - Ada collevance of 770 specific periods contracted by the 19 moles - Said contracted by the 1900 contracted of 770 specific periods contracted by the 1900 contracted by the specific periods of 770 specific periods contracted by the 1900 contracted by the specific periods of the 1900 contracted by the 1900 contracted by the 1900 contracted by the specific periods of 1900 contracted by the 1900 contr

Al the sel man, set shabeted be BAADO tight & Day £525 went

0/TIQNAL_EXTRAG* boson case-options(25:00 * 16s builter (30:00 * Second region for emulations dual forms (35:00 * Face stand 646:00 * speciator camage 615:00 Ar tams plus VAT data sheet on request. OPTIONAL EXTRAG "IN

8" FLOPPY DISK DRIVES



999 LIN

L

1800

Copportial 0.1

176 13 70" 5 23 70" 3 70 117" 4 7" 117"

73p 83p 83p 98p

2240 4.76





E sarpte - va 5 pms Every dam has a 5 year no quictore guarantee or includes had connection date. So wind your order FREEPOST today

Last impedance, of models, 4 dim ---intensity impediation, of models 100% of mit impediates at models, 500 mK. Frequency response, all models 1512-504-1325. BPDLAR Standard, with heatsinty

		0.57	or on			-	-	-
Voor te	315	1=0	140 100 hit		50.00	-	Pres or this	-
HA 20	There is the	0.005%	<0 005%		36 e 60 e 40	240	68.78	17.78
-	30ar4-82	0.015%	200 OD	· 76x 30	Artist	200	EN 56	10.13
47 120	10m/4-01	0.01%	<8 008 N	13-40	120 = 70 = 40	610	C70 @	(17
AV 300		0015	A MIN		10 + 10 - 10	55	(71 3)	1 13
HV 480	240-07-62	105	(/m ()	143-30	121.0 78 2. 10		C35 (6)	00
	andred and					-	-	_

-----· B+@ 128 - 34 - 67 / 69 / 69 / 69 / 69 10 100 130-400 0.05 coms -0.00 10-0.00 75 17-73 10-4 11 400 Minutes 3 01 40 100 - 452 30 100 + 70 - 70 375 519 50 (00 33

Protection Loan line momentary short prove regionally 10 strict j Servir alle 1567 just Rise sime Suri. Su'il cano 100xb. Frequency incomes (-3xB) 1592; 50xHz, Input senatively 100xb rins. Input impedance 100xb2. Damping factor (382/100Hz (>400

HEATY DUTY with heats who

Contraction of the local division of the loc		-						
these to	110				Server	34	23	
05. 04		0 0rm	< 8 000 %	13-40	120 m 70 m 50	95	125 85	177 -
-0.765	130m / 4-61	0.01%	<0.000	145-19	170 = 70 = 60	-	17.4	(77 10
	2400 442	0.01%	<0.00%		1.79 - 28 - 100		(0) 42	(19.6)
HEAVY BUTY without heatsmas								
	die 1 m	0.01%	<0.005	-3-0	14 = 30 = 31	7m	(22 82	110.04
-0 707	130m 4482	0.05	< 10 km	- 45+ 50	50 x 75 x 50	20.	177.57	(1) 43
100 0000	Salar and	1.000	10.000					



Protection Load law, PERMANENT SHORT CRCQAT ideal for deck group use should evidence of shert circuit not be immediately appendit. The Heavy Duty range can deale additional output power divides and complementary protection circuitry with performance space as for standard lyces.

Now to order Prospect. Use this couper, or a separate sheet of paper to order these products, or any products from other LPE tectionics, advertisements, to starro is reached lybu address to Prespect. Chooses and poster orders must be created and payable to it. P Electronics Ltd cash elimit to registered C.O.D. — add E1 to total order willing. Access and Berceycard nationne. All UK orders sent pour lese estats 7 days d'recest d'order



ide purchase price Nonclose Cheque

Postal Orders Presse debit my Access/Burcsaycard to

ALC: N

400 055



INE Money Grow





Above: the PCB for the Voltage Monitor.



Above: the two foils for the double-sided 100 MHz High Impedance Probe PCB.



Above: the board for the two sound effects projects.

Left: the board for the Guitar Practice Amplifier. Please note the alteration to the pad layout for Q6 and Q7.

The Computer Expansion PCBs are the copyright of Watford Electronics and are not reproduced here. Readers wishing to etch their own boards should contact Watford for the foil patterns.

PCB Foil Patterns





Microcomputers are here teach yourself to program! Learn BASIC. the easiest and most widespread language for the small computer. 60 illustrated lessons teach the essentials of good programming: problem definition, coding, flowcharting, debugging and clear documentation. And don't you even need a computer!

£10.50 inc p&p

ZX81 Supplement

When used in conjunction with the above course, it enables you to your knowledge to the apply Sinclair ZX81 microcomputer. It includes some amusing programs to help get you started on the new machine.

50 pence if purchased with CPB. 75 pence (inc p&p) if purchased alone.

Credit card orders may be phoned through on 0480-67446 (24 hrs).

Cambridge Learning

Unit 14A Rivermill Site, FREEPOST. St lves, Cambs PE17 4BR England VAT No 313026022 Giro No 2789159

All credit cards accepted. Prices include worldwide All credit cards accepted. Prices include worldwide post and packing (airmail extra - ask for prepayment involce). Overseas customers (inc Eire) should send a bank draft in steeling drawn on a london bank, or quote credit card number. Allow 28 days for delivery in the UK. Guarantee No risk to you. If you are not completely satisfied, full refund given on return of the Item, in good condition, within 28 days. Please send me:

.... Computer Programming in BASIC (CP8) £10.50 ZX81 Supplement 50p with CPB 75p alone

.... FREE BOOKLIST I enclose a cheque/PO for £ Or charge my Expiry date..... credit card Signature..... Name..... Address.....

Cambridge Learning Lid. Unit 144 Rivermill Stie. FREEPOST. St. Ives, Cambs. PE17 4BR, England. Registered in England No 13287621 -----

Above: the board for the ETI Contrast Meter. You may use the board

as it is or cut it in two where marked, as we did.



600 RESISTORS

High quality Carbon Fem 1519 9% 612 union O union 10 car of IS INCLUDING VAT PEP

COVE COMPONENTS

to Benchmand Rd Cove

CHEAP hard copy. Teletype 32 ASR 75 Baud, as new, (55. Basidon 22254, around for best.

TRANSCENDANT 2000 Bound Working almost new. Extres, £189. Offers. Minisonic MK2, £129, Phone Bridge 01-735 1862.

NEW 1982 ACE COMPONENT CATALOGUE Let your problems be our business Be certain; have your components delivered quickly and efficiently and get that project working Send 30p now for the easy to use 1982 Catalogue to: Ace Mailtronix, Dept E.T.I. 3A. to: Ace Mailtronux, Dept E.T.I. 3A, Commercial Street, Batley, W. Yorks WF17 5HJ.

MAN ORDER PROTECTION SCHEME

where compares Precision and ender advertisers in the gaptime and pay by part is advance of dathway, this plagates (Receivers Foolsy International rail consider to compare the advances of the advances are should become shored or batterupt, provided. You have not reapped the goulds or had your manage missional and

- Arrest and
- relational, and You write to die publisher of this publication Bire-banks foodly internacional singlibung the position nat center than 20 days from the day you sort your order and nat isser than 2 months from that day Please do not work und the task moment to be farm up. When you write, we will tell you how to make your chain and what evidence of payment a moment.

Importation of the second seco

consumina The guarantee covers only advance payment eent in direct response to an obvertigement in the mag-cover least, for example, payments made in response to consequent, etc. received as a result of anoval ing such advantisemental. Classified advantisements and shall be

PARAPHYSICS JOURNAL (Russian) translations); Psychotronic Generators, Kirfianography, gravity lasers, telo kinesis Details SAE 4 x 9". Paralab. Downton, Wilts

AMAZING ELECTRONICS PLANS. Lawers, Super-powered Cutting Rifls, Pistol, Light Show, Ultrasonic Force Fields, Pocket De-fence Weeponry, Giant Tesla, Satellite TV echnics, 150 more projects. Catalogue - From Plancentre, 16 Mill Grove, Pyrotech 950 Bilbrook, Codsall, Wolverhampton,

SECURITY ALARMS Kits from [37. Full range of accessories. MFP Ltd, Herrison Road, Endington, Berningham 824 9A8. 021-373 0450.

PROXIMITY SENSORS infra-red range 3 inch single 5-7V supply ideal for mobile robots £21.95 leaflet. Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent, Staffs.

COPPER CLAD BOARD double sided fibre glass. 10 sheets 12" x 8" £6.00. 6 sheets 12" x 8" £4.00, including P&P. Complete PCB service, Davron, 1 Bankside, off New Street, Cheimsford.

CENTURION BURGLAR ALARM EQUIPMENT Send SAE for free list or a cheque/PO for E5.95 for our special offer of a full sized decoy bell cover. To Centurion Dept ET1265, Wakefield Rd., Huddersheld W Yorkshire. Access & Barclaycard Telephone orders on 0484 35527

CIRCUIT DESIGN, Prototype construction. ensingue or Digital, Siangle Circuits or Complete Instruments/Systems, Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Part, Taunton, Somerset, TA4 1ET, or Phone Bradford on Tone (082-348)

DO YOU TRANSMIT AUDIO SIGNALS OVER CABLE **CIRCUITS**?

We manufacture a full range of interface equipment for transmission of audio signals over private wire of telephone circuits, from Narrow Band STD systems (300Hz-3 4kHz) up to Wide Band Music Circuits

PARTRIDGE ELECTRONICS (A. C. Partridge Ltd.) 56 Fleet Road, Benfleet, Essex Tel: (STD 03745) 3256 We also manufacture audio mixers and sub-ass emblies



FTI APRIL 1982

DIGISOUND 80 MODULAR SYNTHESISER

A synthesiser for the professional and amateur keyboard player, for education and for the beginner. The DIGISOUND 80 suits all levels of keyboard skill. If you want to know how, then read on.



BEGINNERS: A small synthesiser may be assembled at a price comparable with pre-set types. The DIGISOUND 80 has unique facilities and you can learn about electronic music synthesis with the aid of our User's Manual. When you are ready to go beyond the "minisynth' stage then simply add more modules to suit your requirements and your purse.

EDUCATION The modular concept is Ideal for teaching both music and the physics of sounds. The microprocessor add-on converts it to a project of even wider application.

KEYBOARD PLAYERS: The use of the ALPHADAC 16 microprocessor controller allows up to 16 voices in the polyphonic mode as well as providing many other real time keyboard control routines. NEW recording/ composing/sequencing programs provide you with the opportunity to create exciting music — imagine playing back a composition with each voice set to a different instrument!

KEYBOARD SKILL: The ALPHADAC programs have facilities for composing and recording in both real time and not real time. The latter allows entry of notes at any speed and subsequent playback at the required tempo. The not real time mode is essential to synthesists of limited skill and a boon to the experienced player.

THE DIGISOUND 80 - IN ANY CONFIGURATION - OFFERS YOU THE BEST PRICE/PERFORMANCE CHARACTERISTICS

Kits supplied ex stock and ready built modules, or complete synthesisers, are available to order.

NEW IC's from Curtis electromusic Specialties; NEW modules; NEW users manual plus easy to follow construction notes.

Write or telephone for more information from the ELECTRONIC MUSIC SPECIALISTS:







DIGISOUND (80) Modular Synth Cased & Calibrated, Contents: 6 UCO's, 1 LFO, 4 LP Filters, 2 State Variable Filters, 3 Dual UCA's, 2 Dual ADSR's, 2 UC Envelope Generators, 2 Processors, 1 Dual Ring Modulator, 1 Noise/S-hold, 1 UC Mixer, 1 External input, 1 Stareo amp. 1 A per rail PSU, £500.00 DAC Boards, Keyboard & Keyboard Controller (200 ano. Solartron 10 meg Scope (50 ono. All items must go. Owner emigrating Contact P. Lewis, 50 Acres Lane, Stalybridge, Cheshire,



Designed to specifically detect body heat and motion





Martin Buildings, Stonehouse St., Middlesbrough Cleveland Telaphone No. 0642 829238

. . . estruded heatsn's, tested, outranteed 24 120 watts/8 ohms, 120v/2A supply; £13,95 240 watts/4 ohms, 120v/4A supply; £19.95 400 watts/2 ohms, 120v/7A supply; £29.95 clies pre amps available Post/ Wite pecking 60p. Stamp for details, Quantity Audio-Tech., 8 Parsons Close, Church Crookhem, Aldershot, Hents GU13 0HL. Tel: 02514 22303. T. & J. ELECTRONICS COMPONENTS Quality components, competitive prices Illustrated catalogue 45p 98 Burrow Road, Chigwell, Essen. CLOSE ENCOUNTERS GROUP. Personal introductions/dances, parties, talks, social events. Meet interesting, attractive opie. All areas. - Tel. (Liverpool) 051-931 2844 (24 hours). SPARE PARTS For all digital watches Betteries, crystale, displays etc. Send SAE for full list. Profords, Copnersdrive, Holmer-

ETI International 4800 Synthesiser: fully working, maplin case and front panel. Immeculate, £450 ano. Calin Jenkins, 6 John Street, Pontrypridd, Treforest, Mid-Glem

green, Bucks HP156SG.

MOS-FET AUDIO MODULES

diacount

KEYBOARD, 74 key, ASCII output, cased, connection diagram, £55; HP keyboard, 107 key, uncoded, only C36, Tektronia 581A Scope, type 82D/B plug in module, probe, menuals £150 + Carr. SAE for details, 14 Lechlede Gardens, Fareham, Hants

1000 ASSTD 5% resistors, pre-formed for PC8 mounting, C2.50 50 asstd full-spec LED's, 3 & 5mm, all colours, C3.20, 50 asstd full-spec transistors, BC182/212/237/308 etc C3.00 100 sestid PC mntg electrolytics, C3.00 One of each pack [11, All past free, SAE Wholesale list. PC Electronics 1, Thornhill, ETI, Romany Road, Whiteparish, Salebury,

ONE PCB by Cemeche gives you ALL the following facilities for your ZX81: fully buffered 8K memory; 8 output - 13 input lines; 8-bit D/A + A/D conversion; wire-wrap area for your own circuits.

Quality fully documented pre-drilled silk-screened fibregless board. PCB, circuit diagram and example software £12.95 from Cemeche Ltd., 135 Cromwell Rd., London SW7. Access/Barclaycard accepted.

BURGLAR alarm equipment, Ring Bradford (0274) 308920 for our catalogue, or call at our large showrooms opposite Odsal Stadium, CW.A.S. Ltd.





Courses in Electronics

BSc IN ELECTRONIC ENGINEERING

A four year part-time degree course for mature students. Of particular interest to those engaged in Digital, Telecommunications or Control Systems. Entry qualification required is an HNC or equivalent in Electrical and Electronic Engineering or Applied Physics. This CNAA degree is considered by the Council of Engineering Institutions as meeting their C.Eng. academic requirements.

CEI PART II

One year full-time or two years part-time course in preparation for the CEI Part II examination which is the present academic gualification for Chartered Engineers. Subjects offered include Electronics, Communication, Control and Computer Engineering, Entrants should have passed CEI Part I or have been exempted; holders of HNC and endorsements or HND are so qualified.

Further details and application forms are available from the Information Office, Room I308, Cambridgeshire College of Arts and Technology, Cambridge, CB1 2AJ, Telephone (0223) 63271.



Motal cased 9" PM101 CROFTON MONITOR

10 MHZ Bandwidth P4 Standard Also available with P31, Price on application.

NEW-PRINCE MONITOR



High resolution 24 MHz Bandwidth P31 (green) and P4 high resolution standard. Price on application,

Dealer and OEM enquiries welcome

CROFTON ELECTRONICS LTD 35 Grosvenor Roed, Twickenham, Midda TW1 4AD 01-891 1923/1513

WRONG TIME?

MSF CLOCK IS ALWAYS CORRECT - never gains or losse. SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, euto GMT/EST and leap year, can expand to Years, Months, Weekdays and Milliseconds, also parallel BCD output for computer or alarm etc. STOPCLOCK and audio to record and show time on playback, receives Rugby 60KHz atomic time signale, built-in antenne, 1000Km range, GET the RIGHT TIME, only (152,80, 60KHZ RUGBY RECEIVER, as in MSF Clock, serial data

output for computer etc, decoding details, £17,50. Each fun-to build kit includes all parts, printed circuit, case,

postage etc. instructions, money back assurance so GET yours NOW

> CAMBRIDGE KITS 45 (TD) Old School Lane, Milton, Cambridge



pre-amps (HY12 and HY69), to a dual starte pre-amp (HY71), first a new guilar pre-amp (HY72), Each gives the very best reproductor tops your equipment that pre-money (an Juy, and all are protected against shert circuit and errorg patery All LP methods are compasses with each other — comprise them to circuit amp audo hystem. Every tem carries a 5 year no curbotic guarantee and includes full connection data. pre- amps (HY12 and HY66), to a chail startes pro

C.,

So send your proor today - the Prespost coupon reacts no starre

iddenly instant of two 8,P encaps

PRE-AMPS

Natur Nati	Value	10Pct 8 Dars	Current	-	Pres m 1917
	Mint pre any	ליינינט פאר איז	10 mi	04	(6.44
109.9	Stanue pro ango	Test training rates carbody, me - source covers	10-11	un	(L 12)
111.15	New pro amp	Mines the signer site see with teasuring sequerisetie contrast	-	() h	(6 72
147 66	Starms pre-amp	The organism, with rough to rise rais) consider-task from Face tary, with round of Mass Traditional and round of Mass Traditional	20.54	FM CP	17 19
	Mano pro arres	Two rows churtels, may calindap me and	70 mi	(1 W	(19.65
10.21	Dust stares pro amp		20 ~4	ty B	(107)
	Cultor pre-ang	Arguettes for two guders thread a facto are reg with separate adverse fight, traces and many	Phase	(1) (0)	117 25
177 PS	Storeg pro ang	Then charters and dising two regists who are with base-way range trails contrast	20-14	67 M	50 15

-

Cloren recipio conversiones. All reported Tepes + Hall recording Te + 200 metanolasis, escalang direpport relations for recordina recipione. Balancia recipio en VETO metanolasi de la 200 al direc-Metala te HVT27 metanolasi de la 200 al direc-Metala te HVT27 metanolasi de la 200 al direc-

How to order Prospect

Use this coupon or a separate sheet of paper to order nose products, or any products from other K.P. Electronics advertisements, the stamp is needed if you adcress to Freepost Cheques and postal orders must be created and physicles to 0.P Electronics Ltd. cash allott for registered. C 0 D ---- add C1 to total order value, Access and Barclaycard electrice. All LIK orders task past free electric 7 days of recent of and

team sent me the laterang I.P modues

מום משר השום מרכי Peula Orders Annipur Cheque Int Money Order Peane debt my Access / Barcleycard No harte 400 955 **September** ET 4/4 Parto 6.9 (Uppersonal) (Upperson) 2 Contart Set House Date Contentury (12 710 nove (instance Templane (8227 55778) Templane (8777) 64723 Tem Sebutes to (0777, 6477) Ten (0)./m ELECTRONICS LTD AHEAD.STA

	* BIG EARS *	AERIAL AMPLIFIERS Improve weak television reception. Price (6.70, S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lanceshire BLO 9AGH.	VHRIFM TRANSMITTER KIT. New IC design means low price and better perform- ance. Smaller than all imitations — ideal bug etc. Receive on domestic radio (VHF 88- 106MHz). Instructions etc all included. Only £1.95+30p P&P. (Unlicensable). M. Henry. Dept ETI, 30 Westholme Gerdene, Ruislip.
The data was in the law was in law was in law was in law was in the law was in law was in the l	THE PARTY CONTINUE AND THE ADDRESS OF THE ADDRESS O	A9 CORDLESS TELEPHONES Build your own simple and inexpensive units. Send £3.00 for plans to: j. F. Ashlay, Birley Grange Cottage Ferm, Baslow Road, Cutthorpe, Derbyshire.	"MAGIC" proximity (no metal touchplate), light dimmer kit, replaces domestic lightswitch, Illuminated frontplate, (19.48, Printers; Epson MX80T I (197, MX80F/T I
IONISEER KIT (Mains Operated) Superior in building of refreshing ions, Without liers of moving parts if but sout a building of refreshing ions, Without liers of moving parts if but sout a building of refreshing ions, Without liers of moving parts if but sout a building of refreshing ions, Without liers of moving parts if but sout a building of refreshing ions, Without liers of moving parts if but sout a building of refreshing ions, Without liers of moving parts in the south of refreshing ions, Without liers of moving parts in the south of refreshing ions, with the water from a fourname, Billing your room. The result? Your at least fresh parts, PCB and full instructions International international water from a fourname, Billing your room. The result? Your at least fresh, pure, crips and wonderthy refreshing. A soutable case including from parts in con switch, sith in the source of the south full instructions International water from a fourname, filling your room. The result? Your at least fresh, pure, crips and wonderthy refreshing. A soutable case including from parts (N Barcelaycerd) / Access welcome International water from a fourname, filling your room. The result? Your at least fresh, pure, crips and wonderthy refreshing. Mathematication for any soutable case including from parts (N Barcelaycerd) / Access welcome. International water from a fourname, filling your room. The result? Your at least fresh mathematication. Reserved water from a fourname for the fourname for the fourname for the fournation. International		PRINTED CIRCUITS, Make your own sim- ply, cheaply and quickly! Goiden Fotolac light sensitive lacquer – now greatly im- proved and very much faster. Aerosol cans with full instructions. E2.25. De- veloper 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass boerd, approt. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics. Castle Drive, Pras Sands, Penzance, Cornwall.	(441. Prices inclusive. Tremorian Data Systems, Torrs Park, litracombo, Devon. WANTED Circuite or service information on Negard Oscilloscope type DT103 and power supply. Will buy or hire. Tel. evenings or weekends 44063 Cheltenham or write Watton, 245 Prestbury Road, Cheltenham.
USE ELECTRONICS TODAY INTERNATIONAL'S CLASSIFIED (30p per word, minimum 15 words. Box Nos. £2.00 extra or £9.00 per single column centimetre – all prepaid). Just write your ad on the form below and send it with your cheque, made payable to A.S.P. Ltd, to Jenny Naraine, 145 Charing Cross Road, London WC2 0EE. 2 3 4 5 7 8 9 10 12 13 14 15	The second proce sean talephone are applied for test than (10 by advanced and well proven design case validate remponents and consists to any context and the or no modulation for any land prov (2,35 to devalue innoit despine or ford tan details. Price set Payr Clear return o part of case (MIDIAANDS) patter Conditions (Not any inspection) (The same imponent)	Pure flow of ions pours out like water from air feels fresh, pure, crips and wonderfully re All parts, PC8 and full instructions A suitable case including front panel, neon e Price includes post & VAT. From EPOST IN 29A Advance Werks, 44 Walkers F Hours, Mon. Fri 9	a fountain, filling your room. The result? Your Areshing. (12.50 wrtch, all: (10.50 Barcleycard/Access welcome DWELL Need, London N1 Tel 01 226 1489 5 pm Sat 9-4 30 pm
2 3 4 5 7 8 9 10 12 13 14 15 12 13 14 15 12 13 14 15	USE EL (30p per word, mi	ECTRONICS TODAY INTERNATIONA nimum 15 words. Box Nos. £2.00 extra centimetre — all prepaid). on the form below and send it with yo	L'S CLASSIFIED or £9.00 per single column ur cheque, made payable to
2 3 10 7 8 9 10 12 13 14 15	Just write your ad A.S.P. Ltd, to) Jenny Naraine, 145 Charing Cross Ro	ad, London WC2 0EE.
12 13 14 15 10 10 10 10	Just write your ad A.S.P. Ltd, to	Jenny Naraine, 145 Charing Cross Ro	ad, London WC2 0EE.
	Just write your ad A.S.P. Ltd, to	Jenny Naraine, 145 Charing Cross Ro	5 10
	Just write your ad A.S.P. Ltd, to 2 6 7 11 12	Jenny Naraine, 145 Charing Cross Ro	5 10 15
	Just write your ad A.S.P. Ltd, to 1 2 6 7 11 12	Jenny Naraine, 145 Charing Cross Ro	5 10 15
	Just write your ad A.S.P. Ltd, to 1 2 5 7 11 12	Jenny Naraine, 145 Charing Cross Ro	5 10 15

I enclose my cheque/P.O. for the value of £



FINAL RADIO AND **ELECTRONICS EXHIBITION** AT BELLEVUE

by the NORTHERN AMATEUR RADIO SOCIETIES ASSOCIATION in the

LANCASTER HALL **BELLEVUE, MANCHESTER** on SUNDAY 4th APRIL 1982

Doors open at 11 a.m.

The North's Premier Amateur Radio and Electronics Event

Internet Rar Gula Guide Grond Raffle Construction Content Antenew Conten R.S.G.B. Involved Raffle Society's Stands and Trapity Henre Office and Raynet Stands The following Boders have Societ speciel er Bien

forms Ltd. J. Bear A Broom Radiatronics Lone Bactronics P.M. Bactronics P.A.G. Electronics Q.S. Electronics Personal Charges Recovering Ltd Television Person Ran Decornics Electr-Sutton Placteuring S. M.C. Llack Tweedyl Ltd Value

Amethur Radio Escharge The Ameteur Radio Since Microscov Madulas Jake's Radio Nem Cross Radio W. H. Washington Totacom Totacom Load Ameteur Radio Annual Annual Passo Packer Communications More Pitta List Onto Mosteling Contro Communications R & G.B. Boots Scores Areasan Antoin

Stephens Jones Lat Informed Dectories Bredbury Dectories Capital Dectories S. S. Dectories The Computer Jurit Shap Arrow Dectories Lat Bred Othersein Royd Electronics Ace Madeores Ltd. Contractor Components Components J.M.G. Electronics Sets Comm. Syst. Ltd M.J.C. Dectronics



The lists contain all cabinet components - accurately machined for easy assembly - all drive units, crossover networks, ecouetic wedding, refer port trim, nuts, bolts, terminals, grille fabric, etc. The cabinets can be painled or stained or finished with iron on veneer. Easy, toolproof assembly instructions are supplied - no electronic or woodworking Enowledge necessary.

Prices: E50 bit £182 per pair including VAT, carriage and insurance E 8 E70 hit E220 per pair including VAT, carriage and insurance £ 8 E90 bit £330 per pair including VAT, cernage and insurance £10 Pro E90 bit E369 per pair including VAT, cerriage and insurance E10 Credit terms available: Deccent 20%, balance over 12 months inherges currently 31 2 APR



MIXERS FADERS DRIVERS MORE-**NEW FROM** ILP

Just some of the 28 new artesty Just some of the 28 new amaningly compact incluies from fLP Electronics. Bream B Bader is decrements modules — you'll find more new products in the amos and pre-amos. advertments

All UP modules are compatible with each other - you can compline them to create All UP modules are compatible with each other - you can compline them to create anost any audo system. Together they form the most exciting and versatile moduler assembly system for constructors of all ages and segmence. Every date from UP comes a 5 year no quickle guarantee and includes fue connection data. So send your order on the Prospect coupon below today?

	Michael	Wed & Stats		Pres Pre VIV	
HTH 7	Non room	Monte angre suprate and pro-	10 44	08	0.15
HA B	State and	The charact and many he sport aloate	10 mil	17.10	66.20
3497 31	Mana minar	Most the signals merore — with some family, contrast	No.	G .9	\$7.50
	Store real	has channels, and making the speek realized	20 mA	E9 M	\$7 95
HV 24	Starts rear	That channels and many the squars into one - with these and tiess capitude	and	£13.17	(71 45

AND OTHER EXCITING NEW MODULES

	Madute	Mill E data	Garrant	-	Ince a Vill
107 13	Non Works	Programments gast/LED surface once.	10 44		0.0
HTT GT*		the stress transporter in the states. In state range,		EN4 70	(1 5)
HY 72		Provides expensions effects	20 má	(3.67	60
an n		Handlin has puters there are tand are not	20.04	C14 00	6 91
117 76	Stores surfict materia	Analos las d'ample, auth switching are d'	24	To be arrested	
HU 77	States Vill	Propriessing per 120 average group.	20 ml	(10.64	66

For each mounting an eccentrol B & mounting last to makets white wint3 (1).50 ms white (2 Fe ms VH2) B & mounting lasts to makets white wint3 (1).50 ms white (2 Fe ms VH2) "All matches are encounted and incluse cap on each semantics. All serves tags with Point and the matches encounted and incluse cap on each semantics. All serves tags with Point 20 plasme weathy with Madeles with to WH3) massure d5 x 20 x dimens with to WH77 massure B # 20 plasme weathy with Madeles with to WH3) massure d5 x 20 x dimens with to WH77 massure B # 20 plasme.

FP 480 BRIDGING UNIT FOR DOUBLING FOWER

Designed spacetly by EP how with any two power angeliars of the same type to double the power output obtained and will function with any EP power supply in totally seated CBBD, tare 45 x 50 x 20wm with edge convector. If thus tecomes possible to obtain 400 wates mile (angle channel) intel®D. Contributery distortion less than 0 005 %. Price 15 51 %r, Val. (Ex, Val. (E4, 7%)

How to order Freepost

Use this coupon, or a separate sheat of paper, is order, these products, or any products from other CP Electronics advertisements, the stamp is needed if you address to Freepost. Chaques and postal orders must be crossed and payable to LPElectronics Lid cash must be registered. C 0 D — add E1 to total order value, Access and Barcteycard welcome As ust orders sort past loss within 7 days of receipt of order

Provide samp may the totowing ©P modulus
ומש פאר האופי פרכי
Henclase Cheque
Passe didit my Access Barchycard No
Lune
Ad07955
Square
ET 5/4 Poll to 10 Exchange Line Freedood 2 Guiden Bar Marie Case. Company C12 XEP werk England
Improve (0777) 54770 Justinga (0777) 54723 Toos tasS70
FLECTRONICSITO
IAY AHEAD STAY WITH US



Don't miss the May issue of E.T.I. Phone Jennie on 01-437 1002 for all your classified advertising requirements Deadline Friday March 5th

It's easy to complain about advertisements.

The Advertising Standards Authority. If an advertisement is wrong, we're here to put it right. ASA Ltd. Book House Tompton Pace London WCE 2001



Please mention E.T.I. when replying to all adverts


10.00 efficient LP power succines are designed to give you ten design of the party of planning audio Assemblies fore of the diamon models have toroidal handlermers, menufactured on new cost efficient high technology machines a our own tactory. So we keep the Interviews is our can tactory. So see leap be outility to and the price down. If power supplies are compatible mith all other ILP acouves — contoine trains to produce almost any sudic system. All carry the ILP 5 produce almost any sudic system. All carry the ILP 5 prior no cylichith guarantee and include full contection calls So send your order on the Freepost (outpon tenses today) POWER SUPPLY UNITS Verill In For starsuits \pm 120 continuous of 1002-th series to a non-mar of 120 mL σ are 1002 PEas 30 C3 10 64 10 The following and also more the WHE-file sames except HVFL? solution requires the PEU 3D Plan 36 1 - 2 - 11 - 12 (1.17) (1.10) P34 50 1 - 2 ----10 10 10 10 10 PSU 60 THE MY LOD BY LODING LODING 1210 (m m) (m M PSA 05 1 ... WOS 120/1 - WOS 120/ 1 (7) Q 07 ייני מייפני מוייפני אייפני אוי נופי ו מי נופי See Ker PLU 75 1 - 2 405 10-405 100 6.00 60.00 1 = 107 700/107 100/100 700/100 700 PSL 90 5 27 0 27 1 5 405 780 405 207 P50 95 1 W 77 TW 22 Plu 10 72117 200-10 200-10 200-10 200 0 (24 SI (27 3) 1 or 2 MOS 205-MISS 2207/1 H MOS 409 1 H MOS 4007 PSU ND CN 60 C7 6 All modules incorporate 4UP toroidal transformatis except PSU 30 and PSU 35 which include our gen aminated Yanslemens How to order Presset!" Here is and receptat: Use this compart, or a separate sheet of paper, to order these modules or any products from other CP Electronics advertisements. No stange is needed 4 you address to Freepost. Chapters and passed others must be crusted and payable to UPElectronics Lid cash must be registered. C. D. — add CT to total order value. Access and Bancheycard extreme. All UR orders sent post free wather 7 days of recept of order. Plase send the telewing IV modules Idal purchase price indian Chapa Posta Orders ME Morey Order Phase debit my Access/Barc aycard tep Marrie . Address South And to 4.P (Inclosus Ltd. Fragmer 2: Generation races: Assor Case Contentury C12 70P. new (Inguise Television 40727) 14778: Technica 407271 04723. Seen 105780. ET 6/4

ETI APRIL 1982

ELECTRONICS LTD

EAD.STAY

Redio. Television & Electronica in Redio. Television & Electronica in Redio. Television & Electronica in Redio. Television de Electronica in reserve pour es a neuconer io me Redi in de situado y working in the industry. ICS can provide you with the spectalised television go accessed

Personal Turtion and Guaranteed Success

The expert and personal guidance by fully qualified tutors, bocked by the ICS guarantee of twition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that twist you best and in your own home. In the words of one of our many successful students. "Since starting my course, my safery has trabled and I am supecting a further increase when my course is completed."

City and Guilds Cartificates

Excellent job prospects event these who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians Radio, T.V. Electronics Technicians Radio Ameteurs Electrical Installation Work

Diploma Courses

Colour T.V. Servicing CCTV Engineering & Staintenance Electronic Engineering and Programming Radio, T.V. and Audio, Engineering & Servicing Electrical Engineering, Installations & Contracting

Other Career Courses

Non

1

A wide range of other technical and professional courses are evoluble including GCE.

To ICS, Dept. 7205, Intertext House, London SW8 4UU

Age To ICS, Dept. **T285**, Intertext House, London SW8 4UU or telephone 01 622 9911 (all hours)

AD INDEX

A d Electronics	
Ambit International	86 & 100
Amtron (UK) Ltd	
Audio Electronica	66 & 130
Audio Video Services	136
Aura Sounde	
Ri Dek Semiconductors	42 6 43
DK Electropics	16 6 61
Dir Check Star I td	
	62
Boss Industrial Mouldings	119
Braithwaite Kite	
Calculator Sales & Service	
Cambridge Kits	141
Cambridge Learning	91 6 124
Castle Electropica	8
Childmond I td	128
Clel Products	
Cricklewood Electropics	98 6 99
Crimene Components	
Colmoon Clokally	. 14
Castron Electronica	
CT Electronics 1 ed	92 6 93
C.I. Electronics Etd	128
Distance I ad	139
	134
Display Electronics	
E.U.A.	105
Electronize Design	120
Electro Supplies	79
Electrovalue	126 6 177
Flight Electronics	110
Greenbank	
Greenweid	121
Happy Memories.	110
Health Electronics	126
Henry a Radio.	
Hy-Telt	
ILP	143 8 145
LB Electronics.	143 & 145 106 & 111 112
LB Electronics.	143 8 145 106 6 111
LB Electronics. L& B Electronics. Lectro Lines	143 8 145 106 6 111
LB Electronics. L& B Electronics. Lectro Lines LEM Services.	143 & 145 106 & 111
LB Electronics. L& B Electronics. Lectro Lines LEM Services. Linton Electronics.	143 & 145 106 & 111
LP 131, 130, 133, 141, LB Electronics. Lectro Lines LEM Services. Linton Electronics. Magenta Electronics.	143 & 145 106 & 111
LP 131, 130, 133, 141, LB Electronics. Lectro Lines LEM Services Unton Electronics. Megenta Electronics Mawson Associates.	143 8 145 106 6 111 .112 .145 .54 .130 .106
LP	143 8 145 106 6 111 .112 .145 .54 .130 .106
LP LB Electronics. Lectro Lines Lectro Lines LEM Services Linton Electronics Magenta Electronics Mawson Associates. Memotech Ltd Micro Times	143 8 145 106 6 111 145
LP LB Electronics. Lectro Lines Lectro Lines LEM Services Linton Electronics Magenta Electronics Memotech Ltd Micro Times Midwich Computer Co.	143 8 145 106 6 111 145 .54 .130 .106 .125 .10 .131 .30
LP LB Electronics. Lectro Lines Lectro Lines LEM Services Linton Electronics Magenta Electronics Mewson Associates. Memotech Ltd Micro Times Midwich Computer Co. Namal Associates	143 8 145 106 6 111
LP	143 8 145 106 6 111
LP LB Electronics. Letto Unes Letto Unes LEM Services Unton Electronics Magenta Electronics Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics	143 8 145 106 6 111
LP	143 8 145 106 6 111
LP	143 8 145 106 6 111 145 54 130 106 125 106 131 30 116 143 136 107 6 148
LP	143 & 145 106 & 111 145
LP	143 & 145 106 & 111 145 .64 .130 .06 .125 .00 .131 .00 .131 .00 .131 .00 .135 .107 & 148 .125 .77 & 130 .97
LP	143 & 145 106 & 111 145 .54 .130 .06 .125 .10 .131 .30 .16 .143 .136 107 & 148 .25 .10 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .130 .131 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .137 .136 .136 .137 .136 .136 .137 .136 .136 .137 .136 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .136 .137 .137 .137 .136 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 .137 377 374 377 377 377 377 377 377 377 377 377 377 377 377 377 3777 377 3777 37777 37777 37777777777
LP	143 8 145 106 6 111 145 .64 .130 .06 .125 .00 .131 .30 .106 .125 .10 .131 .30 .136 .143 .136 .107 5 148 .12 .77 5 130 .97 .34 .55
ILP LB Electronics. Le B Electronics. Letto Unes Limton Electronics. Magenta Electronics. Mawson Associates. Memotech Ltd. Micro Times. Midwich Computer Co. Namal Associates. N.A.R.S.A. Parndon Electronics. Powertran Electronics. Powertran Electronics. Redditch Electronics. Relay-A Quip J. W. Rimmer Riscomp Ltd. Roadrunner Electronics.	143 8 145 106 6 111
LP LB Electronics. Lectro Lines Letto Lines LEM Services Linton Electronics Magenta Electronics Mawson Associates. Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics. R.T.V.C.	143 8 145 106 6 111 145 54 130 106 125 10 131
LP LB Electronics. Lectro Lines Lectro Lines LEM Services Linton Electronics Magenta Electronics Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A. Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Relay-A Quip J, W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silica Shop	143 8 145 106 6 111 145 54 130 106 125 106 125 107 131 30 116 143 136 107 6 148 137 137 136 107 6 148 122 77 6 130 97 34 55 120 60 72
LP LB Electronics. Lectro Lines Lettro Lines LEM Services Linton Electronics Magenta Electronics Mawson Associates. Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A. Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silica Shop Silicon Speech Systems	143 8 145 106 6 111 145 .64 .130 .06 .125 .00 .126 .106 .125 .00 .131 .30 .116 .143 .30 .116 .143 .30 .116 .143 .30 .126 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .00 .125 .00 .00 .00 .00 .00 .00 .00 .0
ILP LB Electronics. Lectro Lines Lettro Lines Lettro Electronics. Magenta Electronics. Mawson Associates. Memotech Ltd. Micro Times Midwich Computer Co. Namal Associates. N.A.R.S.A. Parndon Electronics. Powertran Electronics. Redditch Electronics. Relay-A Quip J. W. Rimmer Riscomp Ltd. Roadrunner Electronics. R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research.	143 & 145 106 & 111 145 .64 .130 .06 .125 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .126 .00 .00 .00 .00 .00 .00 .00 .0
ILP LB Electronics. Lectro Lines Lettro Lines Lettro Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research Solid State Security	143 & 145 106 & 111 112 145 .64 .130 106 .125 .10 .131 .30 .143 .136 107 & 148 .12 .77 & 130 .97 .34 .55 .120 .60 .72 .54 .54 .125 .54 .54 .54 .54 .54 .54 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .125 .10 .131 .135 .107 & 148 .55 .120 .57 .120 .57 .57 .57 .57 .57 .57 .57 .57
LP LB Electronics. Lectro Lines Letto Lines LEM Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research. Solid State Security Swanley Electronics	143 & 145 106 & 111 112 145 .64 .130 106 .125 .10 .131 .30 .16 .131 .133 .136 107 & 148 .12 .77 & 130 .97 .34 .55 .120 .60 .72 .54 .64 .130 .131 .135 .135 .130 .135 .135 .130 .136 .135 .136 .136 .136 .136 .136 .136 .136 .136 .137 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .136 .126 .137 .136 .136 .136 .126 .136 .126 .136 .126 .136 .126 .126 .126 .137 .136 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .120 .126 .120 .120 .126 .120 .126 .120 .126 .120 .126 .120 .126 .120 .126 .120 .126 .120 .126 .126 .120 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .126 .127 .126 .126 .127 .126 .126 .127 .126 .127 .126 .127 .126 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127 .127
ILP LB Electronics. Lectro Lines Lectro Lines Let M Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Switt of Wilmslow	143 & 145 106 & 111 112 145
ILP LB Electronics. Lectro Lines Lectro Lines Let M Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics R.T.V.C, Silica Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Switt of Wilmslow Technology Resources	143 & 145 106 & 111 112 145 54 130 106 125 10 131 30 116 143 136 107 & 148 107 & 148 107 & 148 107 & 148 127 & 130 97 34 55 120 60 72 54 6, 7 & 147 125
ILP LB Electronics. Lectro Lines Lectro Lines Let Services Linton Electronics Magenta Electronics Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A. Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics RT.V.C. Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Switt of Wilmslow Technology Resources Technomatic Ltd	143 & 145 106 & 111 112 145 54 130 106 125 106 125 106 125 107 131 30 116 143 136 107 & 148 107 & 148 107 & 148 107 & 148 122 .77 & 130
ILP LB Electronics. Lectro Lines Lectro Lines Let Services Linton Electronics Magenta Electronics Mawson Associates. Memotech Ltd Micro Times Midwich Computer Co. Namal Associates. N.A.R.S.A. Parndon Electronics Redditch Electronics Redditch Electronics. Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics. R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research. Solid State Security Swanley Electronics. Switt of Wilmslow Technology Resources Technomatic Ltd	143 & 145 106 & 111 112 145
ILP LB Electronics. Lectro Lines Lettro Lines Lettro Electronics. Magenta Electronics Mawson Associates. Memotech Ltd Micro Times Midwich Computer Co. Namal Associates. N.A.R.S.A. Parndon Electronics. Powertran Electronics. Redditch Electronics. Redditch Electronics. Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics. R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research. Solid State Security. Swanley Electronics. Swift of Wilmslow Technology Resources Tachnomatic Ltd Timedata Ltd	143 & 145 106 & 111 112 145
ILP LB Electronics. Lectro Lines Letto Lines Letto Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C Silica Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Swift of Wilmslow Technology Resources Technomatic Ltd Timedata Ltd Timedata Ltd TK Electronics	143 & 145 106 & 111 112 145 .64 .130 .06 .125 .00 .125 .00 .126 .10 .131 .30 .131 .30 .136 .135 107 & 148 .125 .120 .60 .72 .54 .64 .54 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .125 .00 .00 .125 .00 .00 .00 .00 .00 .00 .00 .0
ILP LB Electronics. Le B Electronics. Letto Unes Letto Services Linton Electronics. Magenta Electronics Mawson Associates. Memotech Ltd. Micro Times Midwich Computer Co. Namal Associates. N.A.R.S.A Parndon Electronics. Powertran Electronics. Powertran Electronics. Redditch Electronics. Relay-A Quip J. W. Rimmer Riscomp Ltd. Roadrunner Electronics. R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research. Solid State Security Swanley Electronics. Switt of Wilmslow Technology Resources Technomatic Ltd Timedata Ltd. TK Electronics. Velleman (UK) Ltd.	143 & 145 106 & 111 112 145 .64 .130 106 .125 .10 .131 .30 .116 .131 .30 .116 .135 107 & 148 .125 .107 & 148 .125 .120 .60 .72 .54 .64 .55 .120 .60 .72 .54 .67 & 147 .125 .61 .77 & 130 .72 .54 .55 .120 .60 .72 .54 .54 .54 .55 .120 .60 .72 .54 .54 .55 .120 .60 .72 .54 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .61 .54 .55 .120 .60 .72 .54 .61 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .72 .54 .55 .120 .60 .54 .55 .120 .60 .54 .55 .120 .60 .54 .55 .120 .60 .54 .55 .120 .61 .54 .55 .120 .60 .54 .55 .120 .61 .54 .55 .120 .60 .54 .55 .120 .61 .54 .55 .120 .61 .54 .55 .54 .55 .120 .54 .55 .54 .55 .120 .54 .55 .54 .55 .55 .120 .54 .55 .55 .120 .54 .55 .55 .120 .54 .55 .55 .120 .54 .55 .55 .120 .54 .55 .55 .120 .54 .55 .55 .120 .54 .55 .55 .55 .120 .54 .55 .55 .55 .55 .55 .55 .55
ILP LB Electronics. Lectro Lines Lectro Lines Let M Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silics Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Swift of Wilmslow Technology Resources Technomatic Ltd Timedata Ltd Timedata Ltd Timedata Ltd. Videotona Ltd.	143 & 145 106 & 111 112 145 54 130 106 125 10 131 30 116 143 135 107 & 148 12 77 & 130 97 34 55 120 60 72 54 6, 7 & 147 125 61 47 126 54 55 120 60 72 54 55 120 60 72 54 125 120 60 72 54 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 131 135 125 125 125 125 125 125 125 12
ILP LB Electronics. Lectro Lines Lectro Lines Let Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics Roadrunner Electronics R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Switt of Wilmslow Technology Resources Technomatic Ltd Timedata Ltd TK Electronics Veileman (UK) Ltd. Videotone Ltd. Watford Electronics.	143 & 145 106 & 111 112 145 54 130 106 125 10 131 30 116 143 136 107 & 148 107 & 148 107 & 148 107 & 148 120 60 72 54 6, 7 & 147 125 61 47 124 56 & 83 52 & 53 120 48 & 49 .25 129 & 133 4 & 5 & 133 .25 .25 .25 .25 .25 .25 .25 .25
ILP LB Electronics. Lectro Lines Lectro Lines Let M Services Linton Electronics Magenta Electronics Mawson Associates Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics R.T.V.C. Silica Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Switt of Wilmslow Technology Resources Technomatic Ltd Timedata Ltd TK Electronics West Hyde Developments	143 & 145 106 & 111 112 145 54 130 106 125 10 131 30 116 143 136 107 & 148 107 & 148 107 & 148 107 & 148 107 & 148 55 120 60 72 54 6, 7 & 147 124 56 & 83 52 & 53 120 48 & 49 25 129 & 133 4 & 5 125
ILP LB Electronics. Lectro Lines Lectro Lines Let Services Linton Electronics Magenta Electronics Memotech Ltd Micro Times Midwich Computer Co. Namal Associates N.A.R.S.A. Parndon Electronics Powertran Electronics Redditch Electronics Redditch Electronics Redditch Electronics Relay-A Quip J. W. Rimmer Riscomp Ltd Roadrunner Electronics RT.V.C. Silica Shop Silicon Speech Systems Sinclair Research Solid State Security Swanley Electronics Switt of Wilmslow Technology Resources Technomatic Ltd Timedata Ltd Timedata Ltd Watford Electronics West Hyde Developments Wilmslow Audio	143 & 145 106 & 111 112 145 54 130 106 125 106 125 107 131 300 116 143 136 107 & 148 107 & 148 107 & 148 107 & 148 107 & 148 107 & 148 120 60 72 54 60 72 54 60 72 54 61 47 124 56 & 83 52 & 53 129 & 133 4 & 5 125 129 & 133 4 & 5 125 125 145 145 125 126 127 128 129 129 129 129 131 120 125 129 129 129 120 120 125 120 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 125 120 120 120 125 120 120 120 120 120 120 120 120

Make the most of your Sinclair ZX Computer... Sinclair ZX software on cassette. per cassette.

The unprecedented popularity of the ZX Series of Sinclair Personal Computers has generated a large volume of programs written by users.

Sinclair has undertaken to publish the most elegant of these on pre-recorded cassettes. Each program is carefully vetted for interest and quality, and then grouped with other programs to form a single-subject cassette.

Each cassette costs (3.95 (including VAT and perp) and comes complete with full instructions.

Although primarily designed for the Sinclair ZX81, many of the cassettes are suitable for running on a Sinclair ZX80-if fitted with a replacement 8K BASIC ROM

Some of the more claborate programs can be run only on a Sinclair ZX Personal Computer augmented by a 16K-byte add-on RAM pack

This RAM pack and the replacement ROM are described below. And the description of each cassette makes it clear what hardware is required.

8K BASIC ROM

The 8K BASIC ROM used in the ZX81 is available to ZX80 owners as a drop-in replacement chip. With the exception of animated graphics, all the advanced features of the ZX81 are now available on a ZX80-including the ability to run much of the Sinclair ZX Software.

The ROM chip comes with a new keyboard template, which can be overlaid on the existing keyboard in minutes, and a new operating manual.

16K-BYTE RAM pack

The 16K-byte RAM pack provides 16-times more memory in one complete module. Compatible with the ZX81 and the ZX80, it can be used for program storage or as a database.

The RAM pack simply plugs into the existing expansion port on the rear of a Sinclair ZX Personal Computer,



Cassette 1-Games

For ZX81 (and ZX80 with 8K BASIC ROM) ORBIT-your space craft's

mission is to pick up a very valuable cargo that's in orbit around a star. SNIPER - you're surrounded

by 40 of the enemy. How quickly can you spot and shoot them when they appear? METEORS - your starship is

cruising through space when you meet a meteor storm. How long can you dodge the deadly danger?

LIFE-J.H. Conway's 'Game of Life' has achieved tremendous popularity in the computing world. Study the life, death and evolution patterns of cells.

WOLFPACK - your naval destroyer is on a submarine hunt. The depth charges are armed, but must be fired with precision.

GOLF-what's your handicap? It's a tricky course but you control the strength of your shots.

Cassette 2-Junior Education: 7-11-year-olds

For ZX81 with 16K RAM pack CRASH-simple addition-with the added attraction of a car crash

if you get it wrong. MULTIPLY - long multiplication with five levels of difficulty. If the answer's wrong -

the solution is explained. **TRAIN-multiplication tests** against the computer. The winner's

train reaches the station first. FRACTIONS - fractions

explained at three levels of difficulty. A ten-question test completes the program.

ADDSUB-addition and subtraction with three levels of difficulty. Again, wrong answers are followed by an explanation.

DIVISION - with five levels of difficulty. Mistakes are explained graphically, and a running score is displayed

SPELLING - up to 500 words over five levels of difficulty. You can even change the words yourself.

Cassette 3-Business and Household For ZX81 (and ZX80 with 8K

BASIC ROM) with 16K RAM pack

TELEPHONE - set up your own computerised telephone directory and address book. Changes, additions and deletions of up to 50 entries are easy.

NOTE PAD-a powerful, easyto-run system for storing and

120/303

retrieving everyday information. Use it as a diary, a catalogue, a reminder system, or a directory. BANK ACCOUNT -a

sophisticated financial recording system with comprehensive documentation. Use it at home to keep track of 'where the money goes,' and at work for expenses, departmental budgets, etc.

Cassette 4-Games

For ZX81 (and ZX80 with 8K BASIC ROM) and 16K RAM pack

LUNAR LANDING-bring the lunar module down from orbit to a soft landing. You control attitude and orbital direction - but watch the fuel gauge! The screen displays your flight status-digitally and graphically.

TWENTYONE - a dice version of Blackjack.

COMBAT-you're on a suicide space mission. You have only 12 missiles but the aliens have unlimited strength. Can you take 12 of them with you?

SUBSTRIKE - on patrol, your frigate detects a pack of 10 enemy subs. Can you depth-charge them before they torpedo you?

CODEBREAKER-the computer thinks of a 4-digit number which you have to guess in up to 10

tries. The logical approach is best! MAYDAY - in answer to a distress call, you've narrowed down the search area to 343 cubic kilometers of deep space. Can you find the astronaut before his life-support system fails in 10 hours time?

Cassette 5-Junior Education: 9-11-year-olds

For ZX81 (and ZX80 with 8K BASIC ROM)

MATHS-tests arithmetic with three levels of difficulty, and gives your score out of 10.

BALANCE-tests understanding of levers/fulcrum theory with a

series of graphic examples. VOLUMES -- yes' or 'no' answers from the computer to a

series of cube volume calculations. AVERAGES - what's the average

height of your class? The average shoe size of your family? The average pocket money of your friends? The computer plots a bar chart, and distinguishes MEAN from MEDIAN.

BASES-convert from decimal base 10) to other bases of your choice in the range 2 to 9.

TEMP-Volumes, temperatures - and their combinations.

How to order

Simply use the order form below, and either enclose a cheque or give us the number of your Access, Barclaycard or Trustcard account. Please allow 28 days for delivery. 14-day money-back option.



Sinclair Research Ltd. 6 Kings Parade, Cambridg Cambs., CB21SN. Tel: 0276 66104.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GUIS 2818. Please print Please send me the stems I have indicated below. Qty Code Item thempeter Tend

	21	Canvette 1-Games	(1.95	
	22	Consette 2 - Junior Education	£1.95	
	23	Cossette 3- Business and Household	(3.95	
	31	Cassette 4-Games	£1.95	
·	25	Cassette 5 - Junior Education	(21.95	
	17	*SK BASIC ROM for ZXB9	Z19.95	
	18	*Bilk RAM pack for ZXBI and ZXB0	248.95	
		*Post and packing (Mappingable)	(2.95	
			Total (

"Piease add (2.95 to total order value only if ordering RUM and/or RAM. I enclose a cheque/PO to Sinclair Research Lid for f hanne P/Basela

a nemoti from	orge may resses	i i	LINEYCE	10101 0	1	1	1		1		4		1.11.1
These del	ete as applica	Mit.	(errolle)	art of the o				in Chan		1	a che a		
Name: Me	Mrs.Miss	1	1	1	1	1	1	1	1	1	L	1	111
Address:	C.L.L	1		1	1	1	I.	1	8	1	1	1	Intel
11	111	1	1	1	1	1	1	1	1	1	1	+	1. ET 104.1

For more than eleven years Powertran have been designing and manufacturing the finest quality electronic kits. All of our now considerable range have featured in the electronics press and literally thousands have been bought and built by contractors in the UK and World-wide.

Our philosophy is always the same — we offer ingenuity and originality in the construction phase by using only top class designers. We offer machines with power, versatility and performance — capability fully equal to their factory built rivals. We offer only the highest quality materials and components throughout to ensure years of useful and reliable service, we offer clear comprehensive and easy to follow construction manuals to place our kits within the scope of the careful first time builder as well as the dedicated enthusiast.

Our hallmark of success lies in the number of our clients who have built our whole range — many assembling several units for others to use often on the professional music scene.

We believe in taking every care throughout — months spent checking and testing the design and development. Vigorous checking of every component, constant pre-despatch quality control, careful packaging...even door to door delivery by Securicor!

We are naturally very proud of our Transcendent range of synthesizers designed by Tim Orr and regularly featured in ETI. They represent the best in constructional interest and in musical performance.

TRANSCENDENT POLYSYNTH A lour octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match. Complete tit (275,00 plus VAT temple valce) Extra voice (up to three more) 42,00 plus VAT

PRECISION - by

EXPANDER — A new matching 4 voice expander to team up with your polysynth for even a greater range and capability Complete Lt C249.00 plus VAT

TRANSCENDENT DPX — Offers a five octave keyboard with power to match. Two exploit outputs foan be used simultaneously) to give herpsichord and pano/honkytonit or reed with strings/brass and both are fully polybhonic. Other iserures include switchable bouch sensitivity and a chorus ensemble unit with strong/mild effect switching. An advanced design made simple with our clearly and out instruction manual.

CONTRACTOR DATE OF THE PARTY OF

POWERIRAN

Complete lut [295.00 plus VAT

TRANS/CENDENT 2000 - Attrough only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The lut is well within the scope of the first time builder buy it, build it play it! You will know you have made the right choice, Complete like (165.00 plus VAT

POWERTBAN

THE FIRST WORDS AND THE LAST WORD IN

ELECTRONIC KITS

1024 COMPOSER - Come sight up to the minute with this new design. It will control your synthesizer with a sequence of up to 1024 notes - or an equal selection of shorter sequences. The Composer is mans powered with automatically charged battery to preserve your programme after switch-off. Complete tut (25, 00 plus VAT)

DEMONSTRATION TAPE --- Demonstration tape now available of all three kits (30 minutes) (2 00



AUSENIHI POSINI

TRANSCENDENT 2000 ----

120 • 20 — Originally designed by Texas Engineers. This is a 20 yeart amplified withtrue Hi-Fi performance at a minimal cost. New features include true Tromdal transformer, new wringusingle dircuit board and improved presentation. An ideal diginners project Complete Alt (29,50 plus VAT. Also T30 + 30 – 30 watt version complete

. . .

10



LINSLEY HOOD 75 DE LUXE — A 75 watt amplifiet organality published in Hi-EI Nows, Superb performance characteristics with less than (01% distortion. Modular construction with 14 interconnecting loadle — withally no wring so assembly is easy as is subsequent checking and maintenance. Complete kit £75.00 plus VAT

Quite simply the best way to make music



WORLD LEADERS IN ELECTRONIC KITS.

PRICE STABILITY: Order with confidence integrative of any brice changes and will harvaur all prices in this adverterment und the end of the month following the month of publication of this make. Geness and VAT site changes encluded EXPORT ORDERS, he VAT Postage charged at actual cost plus (1 handing and

December 14100. M.K. OADERE: Subject to 1915 succharge for VAT. No charge 6 media for carriage, or at oursers rate of chargest. Drepues, Access, Binchards accessed. SECURICOR DELIVERTS / or the ophonal servers RLK. manand ompt and E2.50 IVAT enclosued per tel. FREE ON ORDERS OvER (190). SALES COUNTER: If you prefer to collect hid from the factory, call at Sates Counter. Open (to m. 12 noon, 1-4.30) is. Monder-Thursday

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3WW (0264) 64455.