

electronics today

ISSN 0142-7329

MARCH 1980

60p

DISCRIMINATING METAL LOCATOR

Be choosy with this
VLF design




BLACK HOLES
The Whole Truth!

**VOLTAGE
CONTROLLED MIXER**
1537 VCA CIRCUITS
EXTRACTING TV HI-FI

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an affective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features. The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal trim!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for between £500 and £700!

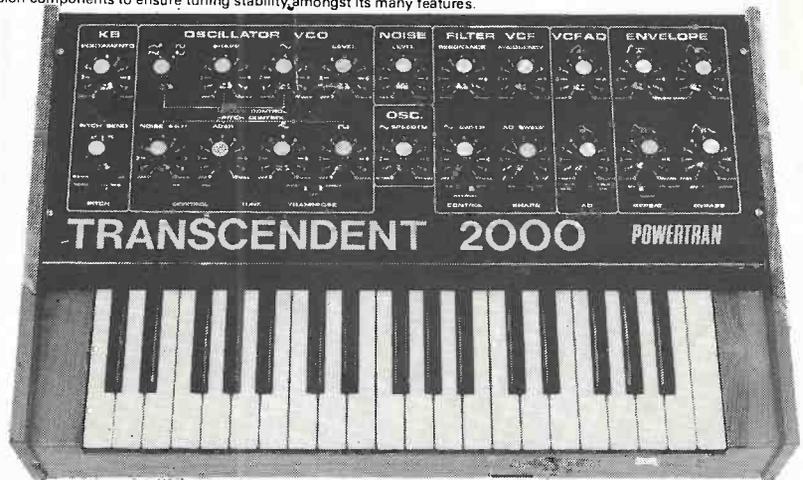

Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

**COMPLETE KIT
ONLY
£168.50 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!


**WE'VE MOVED!
NEW FACTORY UP!
PRICES DOWN!**

**INCREASED CAPACITY AT OUR BIG NEW FACTORY
MEANS MANY PRICES DOWN! ALL OTHERS FROZEN!**

TRANSCENDENT DPX

DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

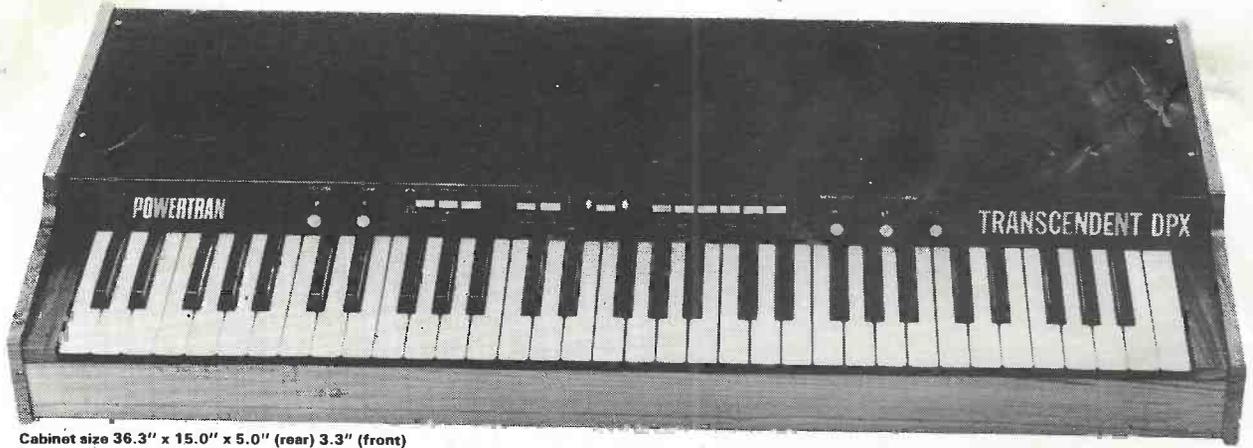

Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

COMPLETE KIT ONLY £299.00 + VAT!

To add interest to the sounds and make them more natural there is a chorus / ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing etc., etc.) and an interface socket (25 way D type) is provided for this purpose.


Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1,200!

POWERTRAN

**ORDERING INFORMATION
AND MORE KITS ON PAGE 8**

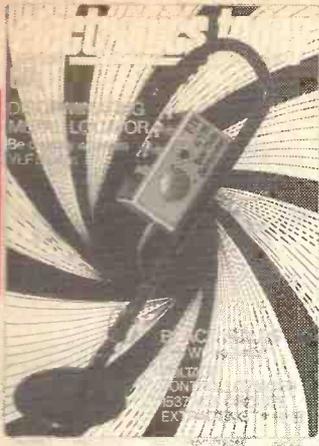
All kits also available as separate packs (e.g. P.C.B., component sets, hardware sets, etc.). Prices in FREE CATALOGUE.



hole truth p20



start digging here p.78

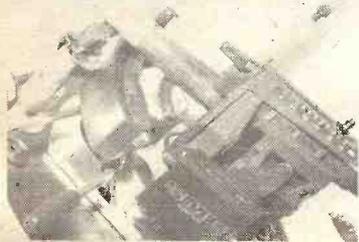

guess what p.51

electronics today

MARCH 1980 Vol 9, No 3 INTERNATIONAL

FEATURES

DIGEST	9	... and now the good news
BLACK HOLES	20	Bottomless pits
	1537	A new chip explained
DESIGNERS NOTEBOOK	41	Walking rings and other miracles
RAVEN ON	46	Inside information
AUDIOPHILE	51	The latest in sound news
TV SOUND	72	A few hints for the courageous
TRANSLATOR	84	A new words box
TECH TIPS	93	Readers ideas

PROJECTS

SIGNAL TRACER	26	Better late than never
MUSCLE METER	56	Read any good biceps?
HEATER CONTROL	67	A posh thermostat
METAL LOCATOR	78	A discriminating locator
VOLTAGE CONTROLLED MIXER	87	Project 80 VCM

INFORMATION

SPECIALS	17	The best of ETI
ETI APRIL	29	Crystal ball time
MARKETPLACE	39	Shopping with ease
HE APRIL	49	The hobby's future
BE AN ETI MAN!	53	Time to come and join us
ETIPRINT	75	Lay it all down
BOOKS	77	Words of wisdom

INTERNATIONAL EDITIONS

AUSTRALIA	Colyn Rivers Publisher Roger Harrison Acting Editor
HOLLAND	Anton Kriegsman Editor-in-Chief
CANADA	Graham Wideman Editor
GERMANY	Udo Wittig Editor



EDITORIAL AND ADVERTISEMENT OFFICE
145 Charing Cross Road, London WC2H 8DEE. Telephone 01-437 1002/3/4/5

Ron Harris, B.Sc	Editor
Ian Graham B.Sc	Assistant Editor
Diego M. Rincon	Art Director
Dee Camilleri	Production
Paul Edwards, Tony Strakas	Technical Illustrators
Joanne Barseghian	
Ray Marston	Project Editor
Keith Brindley, John Fitzgerald	Project Engineer
Steve Ramsahadeo	Project Development
Margaret Hewitt	Administration
Lorraine Stout	Editorial Secretary
Christopher Surgenor (Manager)	Advertising
Sandie Neville	Ad. Production
Steve Rowe	Ad. Representative
Halvor Moorshead	Editorial Director

PUBLISHED BY
DISTRIBUTED BY

PRINTED BY

Modmags Ltd., 145 Charing Cross Road
Argus Distribution Ltd. (British Isles)
Gordon & Gotch Ltd. (Overseas)
QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

Britain's first comp

A complete personal computer for a third of the price of a bare board.

Also available ready assembled for £99⁹⁵

The Sinclair ZX80.

Until now, building your own computer could easily cost around £300—and still leave you with only a bare board for your trouble.

The Sinclair ZX80 changes all that. For just £79.95 you get *everything* you need to build a personal computer at home...PCB, with IC sockets for all ICs; case; leads for direct connection to your own cassette recorder and television; everything!

And yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers on the market at several times the price. The ZX80 is programmed in BASIC, and you could use it to do quite literally anything from playing chess to running a power station.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. Once assembled, it immediately proves what a good job you've done. Connect it to your TV set...link it to an appropriate power source*...and you're ready to go.

Your ZX80 kit contains...

- Printed-circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to any portable cassette recorder (to store programs) and domestic TV (to act as VDU).
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion board plugs in to take up to 3K bytes extra RAM chips. (Chips also available—see coupon.)

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

Two unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.


The unique Sinclair BASIC interpreter... offers remarkable programming advantages:

- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.



- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

...and the Sinclair teach-yourself BASIC manual.

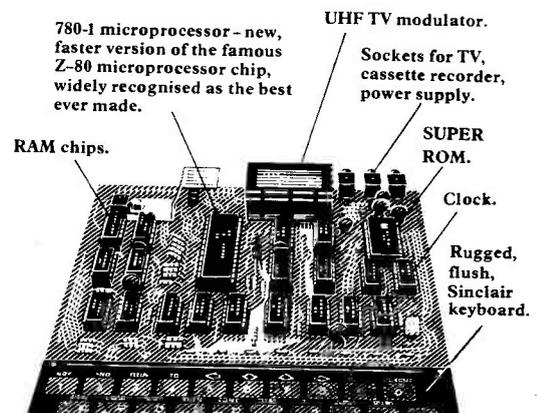If the features of the Sinclair interpreter listed alongside mean little to you—don't worry. They're all explained in the specially-written 96-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming—from first principles to complex programs. (Available separately—purchase price refunded if you buy a ZX80 later.)



lete computer kit.

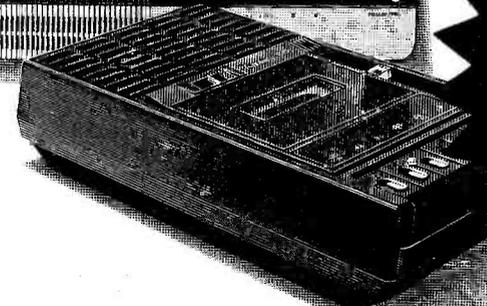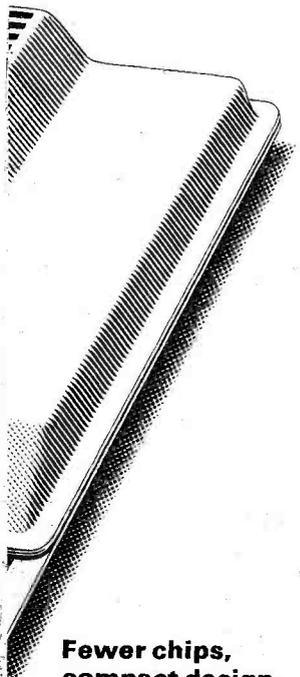

£79⁹⁵
 Including VAT.
 Including post and packing.
 Including all leads and components



Fewer chips, compact design, volume production – more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed onto fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer, because the ZX80's brilliant design packs the RAM so much more tightly. (Key words, for instance, occupy just a single byte.)

To all that, add volume production – and you've that rare thing: a price breakthrough that really is a breakthrough.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Whether you choose the kit or the ready-made, you can be sure of world-famous Sinclair technology – and years of satisfying use. (Science of Cambridge Ltd is one of the Sinclair companies owned and run by Clive Sinclair.)

To order, complete the coupon, and post to Science of Cambridge for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied.

**sinclair
ZX80**

Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

Order Form

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.

Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	
	TOTAL		£

NB. Your Sinclair ZX80 may qualify as a business expense.

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £

Please print

Name: Mr/Mrs/Miss _____

Address _____

ET1/3/80

ELECTROVALUE CATALOGUE 10

HAD YOURS YET?

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

FREE

(You don't even have to pay postage in the U.K.)

IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

- **We give discounts** on C.W.O. orders, except for a few items market Net or N in our price lists.
5% on orders, list value £10 or more
10% on orders list value £25 or more.
Not applicable on Access or Barclaycard purchase orders.
- **We pay postage** in U.K. on C.W.O. orders list value £5 or over. If under, add 30p handling charge.
- **We stabilise prices.** by keeping to our printed price lists which appear but three or four times a year.
- **We guarantee** all products brand new, clean and maker's spec. No seconds, no surplus.
- **Appointed distributors** for SIEMENS, VERO, ISKRA, NASCOM and many others.

OUR NEW CATALOGUE No 10

Full 128 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

ELECTROVALUE LTD

HEAD OFFICE (Mail Orders)
28(D) St. Judes Road, Englefield Green, Egham, Surrey
TW20 OHB. Phone: 33603 (London prefix 87. STD 0784)
Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)
680 Burnage Lane, Burnage, Manchester M19 1NA
Phone: (061) 432 4945.

AUDIO AND TEST EQUIPMENT CENTRE

RETAIL
MAIL ORDER
EXPORT
ALL PRICES
INCLUDE VAT

Telephone your order with Access and Barclaycards or send cheque with order.



LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm

SCOPES — (UK P/P £1.50 ea.)

HAMEG	
HM 307-3 10MHz single beam with Component Tester	170.00
HM 312-8 20MHz dual trace	287.50
HM 412-4 20MHz sweep delay	402.50
Super 10 10MHz dual trace	239.00
4025. Scope x 25MHz dual trace	414.00
SINCLAIR 10MHz Miniscope. P/S 4.00. Nicads 7.95. Case 8.50	162.50
PROBES 15.40. x 10 10.50 x 1 8.50	

DIGITAL MULTIMETERS

DM235 Sinclair portable 3½ digit LED	56.50
PDM35 Sinclair Pocket 3½ digit LED	36.50
DM350 New Sinclair 3½ digit { with 10 amp range	78.50
DM450 New Sinclair 4½ digit { (30kV Probes 19.00. P/S 4.00. DM Nicads 7.95. Cases 8.50.)	107.95
M1200 Bench Portable 3½ digit LED. Resolution 1µA/0.1mv/0.01ohm	87.50
935 Data Precision 3½ digit hand-held LCD (2 amp AC/DC)	99.95
195. Low cost 3½ digit general purpose LCD	49.95
197. Pocket Low cost 3½ digit LCD	39.95

FREQUENCY COUNTERS

OPTO 7010 9 digit, 600MHz Portable. 0.1Hz Resolution with NICADS	113.95
MAX 50 50MHz 6 digit pocket counter	61.00
MAX 100 100MHz 8 digit portable counter	88.75
MAX 550 550MHz 6 digit pocket counter	106.00
500 MHz Prescaler for max 50 or max 100	40.00
PFM200 Sinclair 200MHz Pocket Counter 6 digit	54.50
OPTIDAL P/S 4.00. Connector Pack	9.95

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1/IT-2/T12/TM3A/TM3 AC volts only, some with AC current, etc.

TM11 incredible 120 Range Electronic Multi-meter	158.00
TM3B AC Micro voltmeter 3MHz > 4 Megohm (large scale)	151.75
TM3A AC Micro voltmeter 3MHz > 4 Megohm	139.50
3607R 100k/volt 23 Range (plus transistor checker). Large scale	34.95
7080 20k/volt 26 Range. Large scale	26.95
7081 50k/volt 36 Range Multi-meter	19.95
7200 20k/volt 22 Range Double Multi-meter	17.95
NH55 20k/volt 22 Range Popular Multi-meter	16.95
LT101 1k/volt 12 Range Pocket Multi-meter	5.55
YN3607R 20k/volt 19 Range Multi-meter plus transistor check	13.95
AT205 50k/volt 21 Range Multi-meter	24.95
NH55/110 2k/volt 10 Range Multi-meter	6.95
TMK500 30/volt 23 Range Multi-meter, with case	22.95
AT1020/TR202 20/volt 19 Range Multi-meter with transistor tester	16.95
AT210 100k/volt 21 Range Multi-meter	25.95

AVD 8s and a large range of replacement tests leads in stock

GENERAL EQUIPMENT

SE250 Signal Injector	4.95
TE7 Signal Tracer AF/RF	9.95
SWR50 SWR/Power Meter	13.95
DR510 36 Value Resis. Box	3.95
RP124 0/24v 0/1 amp P/S Stabilised	42.00
RP124 2 amp version	54.00
RP230N 0/30v 0/1 amp. P/S Twin Meters	65.00
TR1000 Transistor checker in/out circuit	11.95
MOD83 Signal injector	8.65
C3022 Transistor/Diode Checker	19.95
3101 Clamp Meter 0/1 K ohm. 0/150/300/600 AC volts 0/300 amp	32.95
SWR40/9 SWR & FS Meter	10.50
SWR10 SWR Meter	10.95
MS319 2x100 Watt Audio Watt Meter	13.95
500V Megohm meter 500 Megohms	81.00
2½ Amp Variable transformer	21.95

DRILLS AND DRILL KITS

9 to 12 volt Operated. ¼" max.	
SMALL DRILL with collets	9.85
MEDIUM DRILL with 3 collets	9.90
SMALL DRILL with 20 drills/tools	13.95
SMALL DRILL with mains eliminator and 20 drills/tools	23.50
MEDIUM DRILL with 20 drills/tools	16.95
MAINS Eliminators	9.95
VARIABLE Speed	13.95
12 volt ¼" Heavy Duty Drill	12.50

TV SOUND

High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. 6.50 (UK P&P 50p)
As reviewed by 'Popular Hi-Fi', July '79

GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges	
TG152D	86.25
TG152Dm (with meter)	107.50
TG200 Series RC Oscillators Sine/Square output. 1Hz-1MHz 12 Ranges	
TG200D	113.95
TG200Dm (with meter)	139.50
TG200Dmp (meter & fine control)	145.90
4001 Digital Pulse Generator 0.5Hz-5MHz	105.00
2001 Function Generator-Sine/Square/Triangle/TTL	85.00
SG2030 (RF) 6 bands 250kHz-300MHz	49.95
AG781 (Audio) sine 19Hz-220Hz square 19Hz-100kHz	81.00
ARF50 (RF-Audio) 18Hz-200MHz	78.50

PROTO BOARD IN STOCK


KITS PR 6.20, PR 100 11.80.
SEPARATES EXP300 £.95, EXP600 6.50, EXP350 3.45, EXP650 3.95

LOGIC PROBES AND MONITORS

LT2000 Economy Probe. 10MHz	8.95
LM1 Monitor circuit powered	33.00
LP1 Probe 10MHz	35.50
LP2 1.5MHz	20.50
16 Pin IC test clip	1.95

PIEZO HORN TWEETERS

Up to 100 watts each. No x-over reqd. Only 4.95 each. Flared Horns 6.50
Midrange Flared Horns 8.50 (P/P 20p per 1 or 2, 30p per 3 to 5)

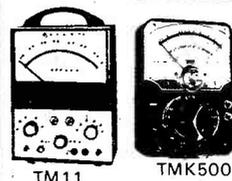


TM11



TMK500

NEW BULK PURCHASE
GED 10+10 watt
Tuner/Amplifier
MW/LW/SW/Star/FM. Supplied as two easy to connect units.
£21.95 P&P £1.50

WE SELL
Kef, Seas, Audax, Fane, Goodmans, Motorola, Peerless
Speakers/Kits etc
Also PA Equipment, etc

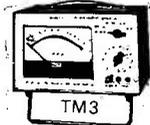

TM3

CALL IN AND SEE FOR YOURSELF

PRICES CORRECT AT 3/3/80

AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724 3564. OPEN 9-6. MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W.1

FREE CATALOGUE


SEND STAMPED
15p UK
ADDRESSED ENVELOPE
(MIN. 3x5)
FOR YOUR COPY NOW.

You can't beat The System.


The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.

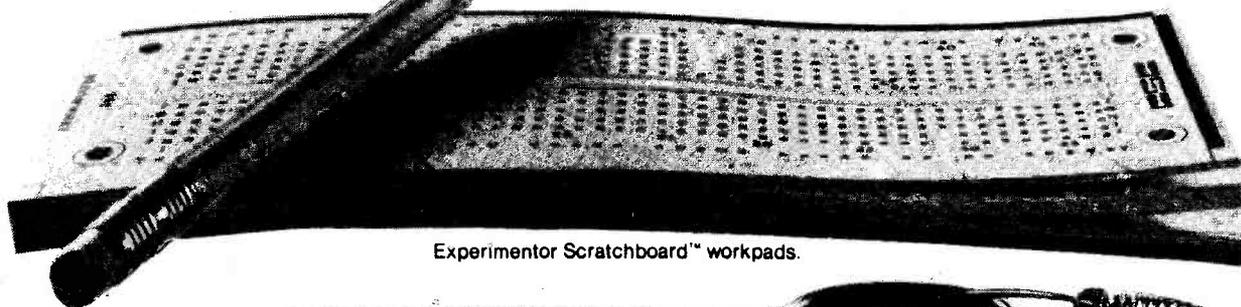

Experimentor Scratchboard™ workpads.

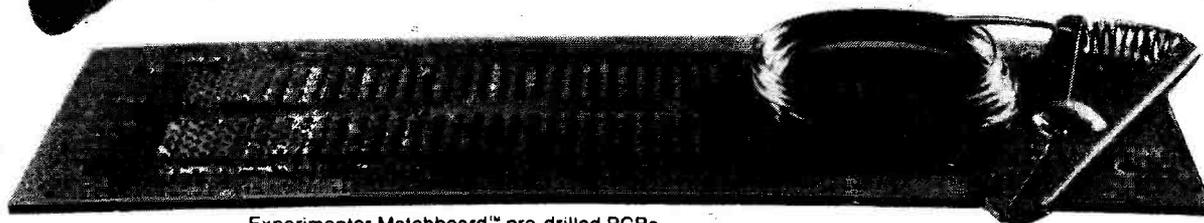

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item A Matchboard pre-drilled PCB £1.32	2. EXP-302, which includes three items Three 50-sheet Scratchboard workpads £1.68	3. EXP-303, which includes three items Two Matchboards and an EXP-300 solderless breadboard £8.60	4. EXP-304, which includes four items Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad £9.30
---	--	--	--

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited,
Dept. 9W Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477.

CONTINENTAL SPECIALTIES CORPORATION, DEPT. 9W

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____

Address _____

Inc P&P and 15% VAT

1. EXP 300PC £2.38	Qty. Reqd.	2. EXP 302 £2.79	Qty. Reqd.
3. EXP 303 £11.04	Qty. Reqd.	4. EXP 304 £11.85	Qty. Reqd.

FREE Catalogue tick box
I enclose cheque/ PO for

£ _____

Phone your order with Access, Barclaycard or American Express

Card No. _____ Expiry date _____

CHROMATHEQUE 5000



Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

POWERTRAN

5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT

ONLY

£49.50 + VAT!


MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

COMPLETE KIT

ONLY

£49.90 + VAT!

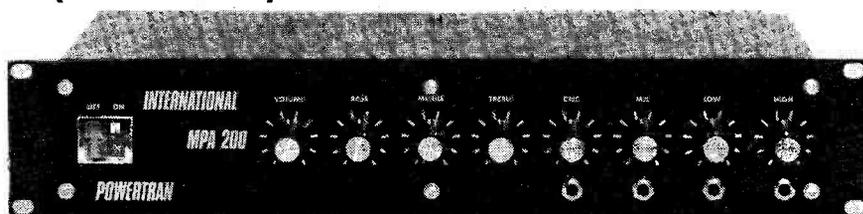
**MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!**



Panel size 19.0" x 3.5". Depth 7.3"


Featured as a constructional article in *ETI*, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 2000 is simplicity itself with minimal wiring needed making construction very straightforward.

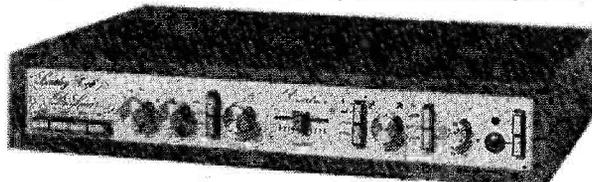The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.




DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in *H-Fi News and Record Review* and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

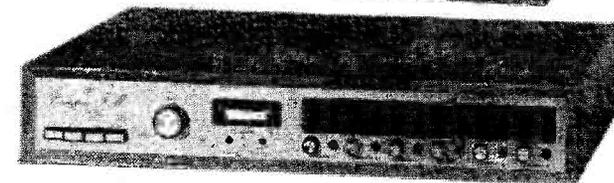

WIRELESS WORLD FM TUNER £70.20 + VAT

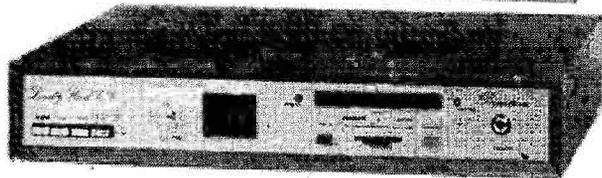A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder, incorporating active filters for "birdy" suppression.



LINSLEY-HOOD CASSETTE DECK £79.60 + VAT

This design, published in *Wireless World*, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control.

T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in *Practical Wireless*, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for **£38.40 + VAT**.

MATCHING TUNERS — SEE OUR FREE CATALOGUE!

COMPLETE KITS: Our complete kits really are complete. All of the projects shown on this page are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet (last 4 kits on this page), or professional quality rack mounting cabinet (first 2 kits on this page), cables, nuts, bolts, etc., and full instructions — in fact everything!

All of the kits shown on this page are available as separate packs for those customers who wish to spread their purchase or perhaps make their own cabinets or metalwork. Prices are given in our **FREE CATALOGUE**.

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until April 30th, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m.-4.30 p.m. Monday-Thursday.

**NEW FACTORY ON SAME INDUSTRIAL ESTATE
ADDRESS AND PHONE NUMBER UNCHANGED**

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455



DIGEST



For Starters

The Dema System is a compact electronic ignition unit introduced by Maywood Technical Developments. Priced at £49.50 including VAT and postage, the unit is aimed at both the private motorist and the fleet operator.

The system incorporates a variable pulse width circuit to determine when the voltage stored on capacitors should be switched by thyristor to the HT coil and spark plugs. It monitors the revs and varies the duration of the spark to achieve as near as possible complete initiation of combustion.

The system can be installed by unskilled staff in about half an hour without having to make any alterations to the vehicle.

The Dema System is available from Maywood Technical Developments Ltd, Peake House 232 High Street, Harlington, Hayes, Middlesex UB3 5DS.

Tantless

It seems that there isn't a lot of tantalum ore about these days. Although it hasn't exactly been the first item on News at Ten, it means there's a shortage of tantalum powder, from which the capacitors are made. Supply and demand just isn't working in our favour. As demand keeps on rising, the known reserves are being exhausted. That inevitably means that tantalum capacitors are bound to increase in price rapidly over the next year or two.

Red Hot Radar

Under Chairman Brezhnev Soviet defence spending has increased from half to almost double that of America.

A Senate Subcommittee heard recently that the latest Soviet airborne tactical look-down/shoot-down radars are believed to be superior to any system now used by American forces.

Russian missile guidance systems can now match their American counterparts. Russia is also annually devoting several times America's spending on research into high energy laser research.

Radiation Hazard

Have you any old ex-government equipment with luminous dials or pointers? (They may not now be luminous because of phosphor degeneration).

Mr. Manning of Birmingham University has informed us of a radiation hazard that may exist from some ex-government equipment.

He was moved to write to us after examining a revolution counter, containing two large moving coil meters with edge-wise scales about 100 mm long,

scaled 6-14-18-22-26-30 and marked 'Engine Speed Hundreds of RPM'.



The graduations and numbers are filled with radium activated luminous paint, applied very thickly. At 10 cms from the scales a Geiger counter registered 1000 counts per second. With alpha and beta radiation blocked, the count rate was still 100 cps. As Geiger counters are only one or two per cent efficient for gamma rays, the true rate may be






several thousand per second. In that event the radioactive paint used is such a strong source (several millicuries) that one would require a licence to use it for teaching purposes.

If you have any ex-government equipment with luminous dials or pointers — better safe than sorry, have it properly disposed of if you think it may be a radiation hazard. Warning — don't burn the equipment; that will simply spread the radium through the air.


TTLs by TEXAS 7400 11p 74251 140p 4018 89p 7400 11p 74259 250p 4019 45p 7400 11p 74278 200p 4020 100p 7401 12p 74279 110p 4021 110p 7402 12p 74280 150p 4022 22p 7403 14p 74283 150p 4023 22p 7404 14p 74293 150p 4024 50p 7405 20p 74298 200p 4025 20p 7406 32p 74365 100p 4026 130p 7407 32p 74366 100p 4027 90p 7408 32p 74367 100p 4028 90p 7409 15p 74390 200p 4030 55p 7410 15p 74393 200p 4031 55p 7411 24p 74490 225p 4032 200p 7412 24p 74491 225p 4033 200p 7413 30p 74502 18p 4036 295p 7414 30p 74503 18p 4037 115p 7415 30p 74504 18p 4038 120p 7416 27p 74505 25p 4040 100p 7417 27p 74506 25p 4040 100p 7420 27p 74510 25p 4041 80p 7421 40p 74511 40p 4042 80p 7422 22p 74512 40p 4043 90p 7423 34p 74513 40p 4043 90p 7425 30p 74514 72p 4046 110p 7426 40p 74515 45p 4047 100p 7427 34p 74520 40p 4048 55p 7428 17p 74521 40p 4048 55p 7430 17p 74522 38p 4049 40p 7432 30p 74530 20p 4050 48p 7433 40p 74532 27p 4052 80p 7434 35p 74533 27p 4053 80p 7435 35p 74534 27p 4053 80p 7440 35p 74551 24p 4054 125p 7441 70p 74555 30p 4055 150p 7442A 60p 74573 30p 4056 135p 7443 112p 74574 36p 4060 115p 7444 112p 74575 45p 4063 120p 7445 100p 74576 45p 4063 120p 7446A 80p 74583 110p 4066 55p 7447A 80p 74585 100p 4067 45p 7448 50p 74586 40p 4069 20p 7450 17p 74592 40p 4070 30p 7451 17p 74593 40p 4071 22p 7452 17p 74594 40p 4071 22p 7454 17p 74596 110p 4072 22p 7460 17p 745107 45p 4073 22p 7470 36p 745109 80p 4076 107p 7472 36p 745113 90p 4081 22p 7474 30p 745114 45p 4082 72p 7475 30p 745122 80p 4086 22p 7476 35p 745123 70p 4093 80p 7480 50p 745125 60p 4094 250p 7481 100p 745126 60p 4095 95p 7482 100p 745132 95p 4096 95p 7483A 80p 745133 30p 4097 340p 7484 110p 745136 55p 4099 200p 7486 34p 745139 75p 40100 220p 7489 170p 745145 120p 40101 220p 7490A 30p 745147 220p 40102 180p 7491 40p 745148 175p 40104 95p 7492A 40p 745151 100p 40105 90p 7493A 94p 745152 100p 40106 90p 7494 94p 745154 200p 40106 90p 7496 65p 745155 90p 40107 80p 7497 180p 745156 90p 40108 470p 74100 130p 745157 90p 40110 300p 74104 65p 745160 130p 40114 250p 74107 36p 745161 100p 4411 110p 74109 55p 745162 140p 4502 120p 74110 55p 745163 100p 4507 50p 74111 70p 745164 120p 4508 290p 74112 130p 745166 180p 4510 95p 74119 200p 745173 110p 4511 150p 74120 200p 745174 110p 4512 80p 74121 22p 745175 110p 4513 250p 74122 48p 745180 110p 4515 300p 74123 48p 745190 250p 4516 110p 74125 55p 745191 100p 4518 100p 74126 60p 745192 100p 4520 100p 74128 75p 745193 100p 4521 100p 74132 75p 745195 140p 4527 150p 74135 50p 745196 120p 4528 100p 74136 50p 745197 120p 4538 120p 74137 50p 745220 175p 4539 180p 74141 50p 745240 175p 4543 180p 74142 200p 745241 175p 4556 72p 74145 200p 745242 170p 4560 250p 74147 190p 745243 170p 4569 250p 74148 150p 745244 195p 4569 250p 74150 100p 745245 250p 4572 40p 74151A 70p 745247 140p 4584 90p 74153 70p 745248 140p 4584 90p 74154 100p 745249 140p 4584 90p 74155 90p 745251 140p 4001A 90p 74156 90p 745253 140p 40085 200p 74157 70p 745257 120p 14411 1100p 74159 180p 745258 180p 14412 1100p 74160 100p 745259 180p 14433 1100p 74161 100p 745266 180p 14599 290p 74162 100p 745273 175p 14599 290p 74163 100p 745279 90p CD2210 350p 74164 120p 745298 240p CD2211 700p 74165 130p 745324 200p CD2212 700p 74166 120p 745348 200p CD2210 350p 74167 200p 745365 100p ICs 74170 200p 745367 100p ICs 74172 450p 745368 100p MC1488 100p 74173 120p 745373 180p MC1489 100p 74174 120p 745374 180p 25S10 350p 74175 80p 745378 200p 707 Gr 140p 74176 80p 745390 160p 75107 170p 74177 90p 745393 160p 75150 180p 74178 90p 745445 140p 75123 230p 74180 90p 745688 100p 75322 300p 74181 180p 745689 100p 75324 375p 74182 180p 745670 400p 75325 375p 74184A 150p 4000 150p 75363 350p 74185 150p 4001 17p 75365 350p 74186 320p 4002 17p 75451 72p 74190 90p 4006 90p 75491/2 90p 74192 90p 4008 80p 8128 250p 74193 90p 4009 40p 8129 80p 74194 90p 4010 50p 8196 200p 74195 90p 4011 17p 81S95 140p 74196 90p 4012 50p 81S96 140p 74197 90p 4013 84p 81S97 140p 74198 150p 4014 84p 81S98 140p 74199 150p 4015 84p 9601 110p 74200 150p 4016 84p 9602 220p 74221 180p 4017 80p 9603 180p	93 SERIES 9301 180p 9302 175p 9308 310p 9310 275p 9311 275p 9312 160p 9314 225p 9316 120p 9321 225p 9322 225p 9334 180p 9368 200p 9370 200p 9374 200p	VEROBOARDS 0.1 0.15 (cover each) 2.5 x 3.75" 45p 43p 2.5 x 5" 57p 51p 3.75 x 3.75" 57p 51p 3.75 x 1.75" 64p 64p 4.75 x 1.75" 220p 194p Pkt of 100 pins 50p Spot face cutter 118p Pin insertion tool 86p Vero WinPro Pen + 2 wire spools + combs 370p Combs 7p	TRANSISTORS AC126 25p BF299 35p BF329 25p BF440 25p BF441 25p BF442 25p BF1000 25p	LINEAR ICs AY-0212 600p AY-1313 800p AY-1320 320p AY-15050 140p AY-12270 840p AY-12240 240p AY-1315 800p AY-1317A 775p CA3019 80p CA3046 70p CA3048 225p CA3090E 72p CA3096 225p CA3098E 225p CA3090A 375p CA3106 90p CA3106C 90p CA3181E 140p CA3162E 450p CA3189E 400p DAC1408-B 200p FX201 750p ICL7106 850p ICL8038 340p ICM7555 80p LF358P 95p LM104C 450p LM301A 120p LM311 120p LM318 200p LM319 225p LM324 90p LM339 120p LM348 85p LM377 175p LM380 75p LM381AN 140p LM390 36p LM710 50p LM725 300p LM733 100p LM747 18p LM748 18p LM748B 35p LM2917 250p LM3900 70p LM3909 70p LM3911 130p LM3912 130p LM4136 120p MC1310P 150p MC1458 48p MC1495L 350p MC1496 100p MC3346P 120p MC3360P 100p MK50398 750p 11C90 1400p	MEMORIES 2102/2L 120p 2107B 120p 2111/2 400p 2112/2 300p -2114 525p 4022/2L 375p 4044 900p CHARACTER GENERATORS 990p J2574C 100p MCM6576 100p RO-32513 UC 600p RO-32513 LC 650p SN74S282AN 1350p	ROM/PROMS 71301 700p 745198 700p 745287 350p 745387 350p 745470 350p 745471 650p 745571 650p 825477 750p 93427 400p 93436 400p 93446 650p 93448 1000p	CPUs 1800 120p 1800A 120p 8502 120p 8800 900p 8802 1250p 8080A 1250p 8085A 1400p 1NS0060 1100p 280 1100p 280A 1250p	EPROMS 1702A 500p 2516 120p 2708 80p 2716 80p	SUPPORT DEVICES 3245 400p 6532 1100p 6821 500p 6850 500p 8205 220p 8212 325p
---	--	---	---	---	--	--	--	--	---

PCB FOIL PATTERNS

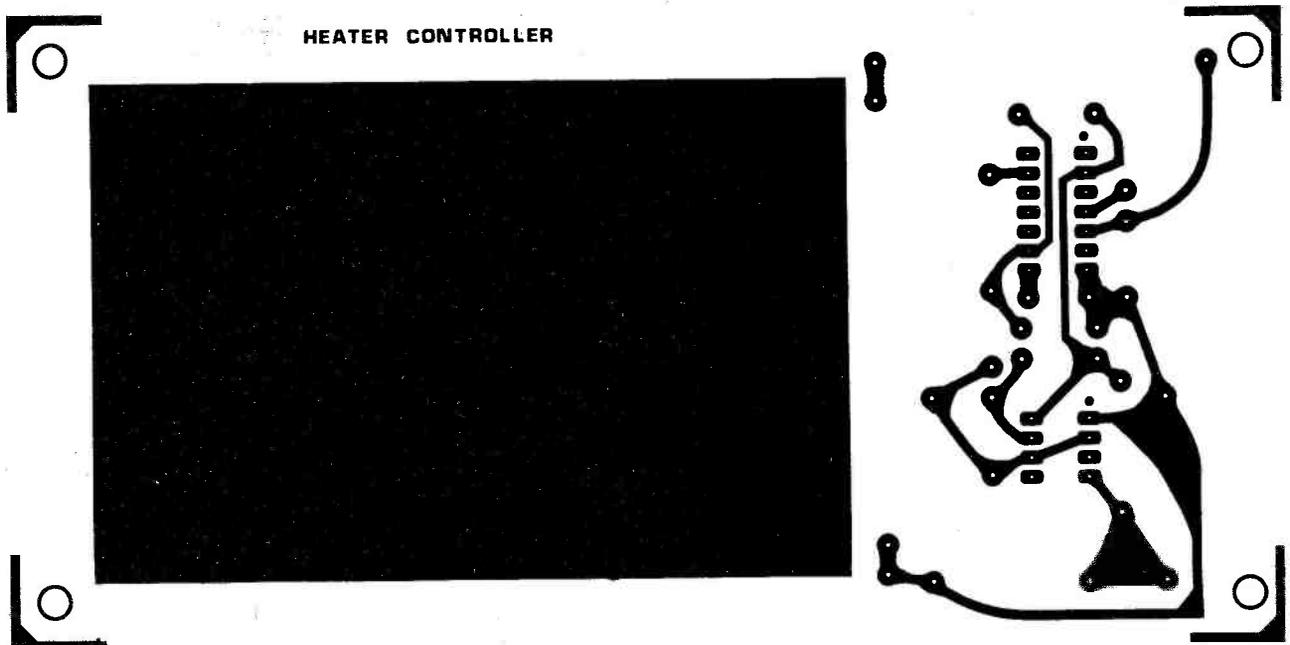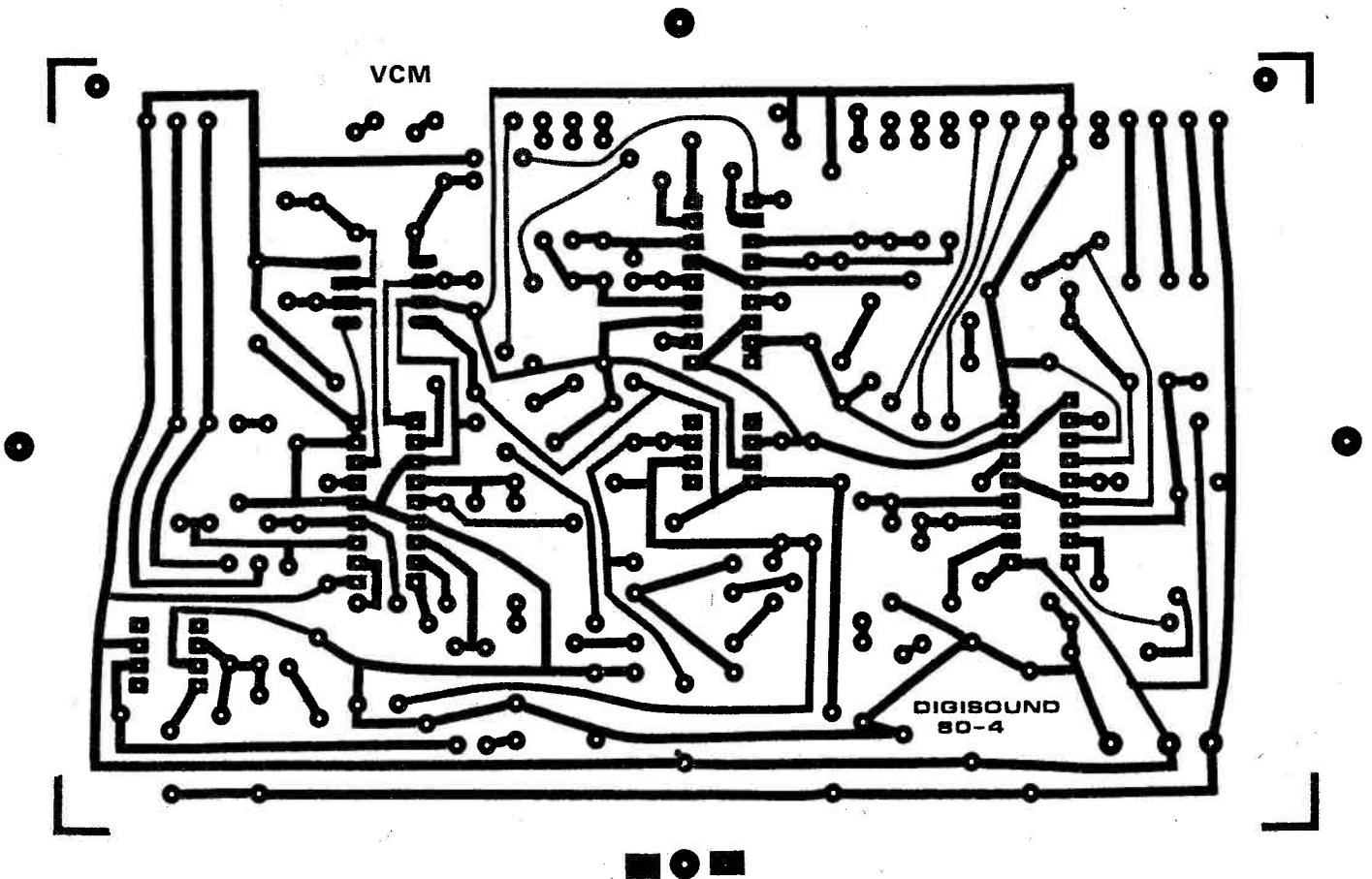

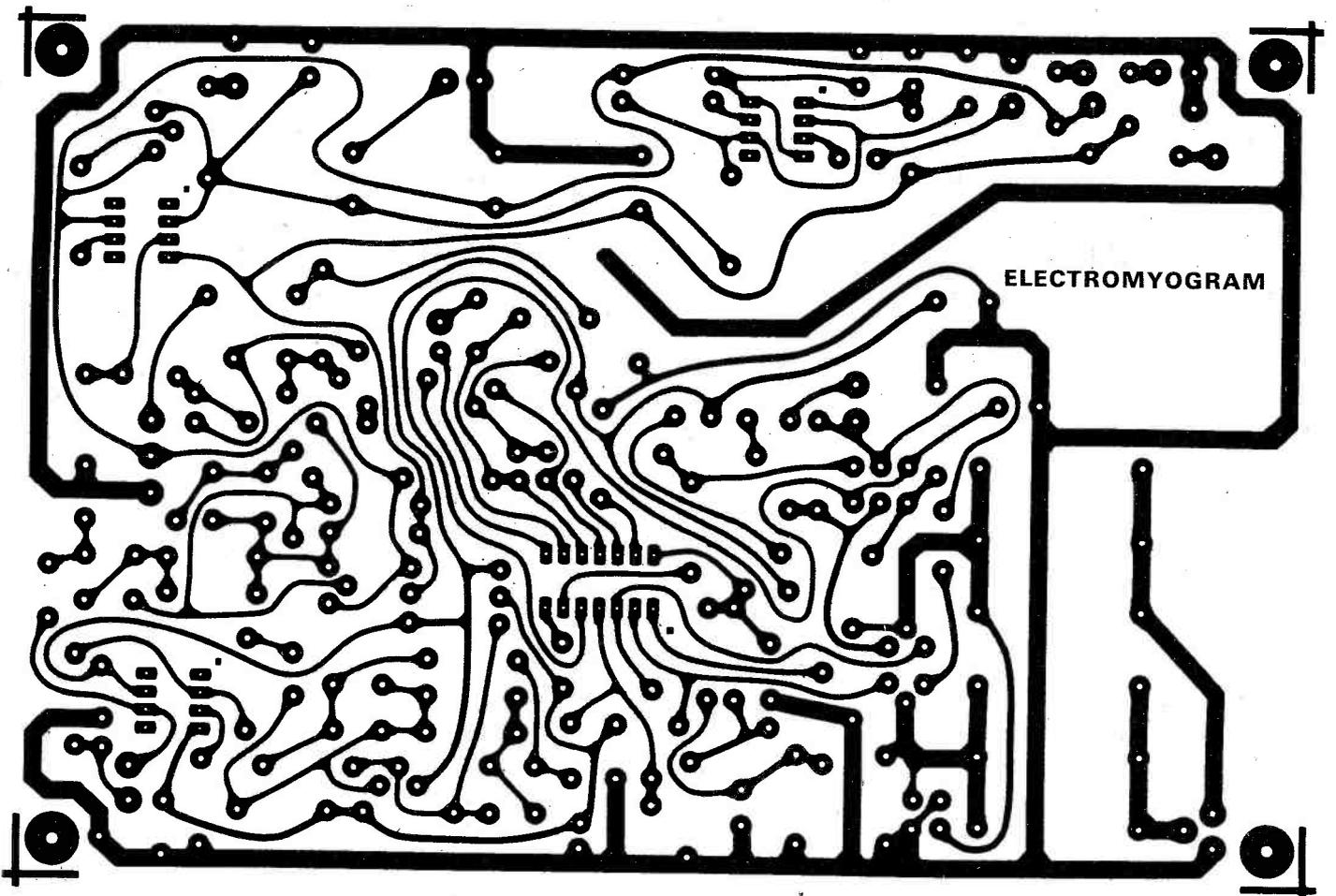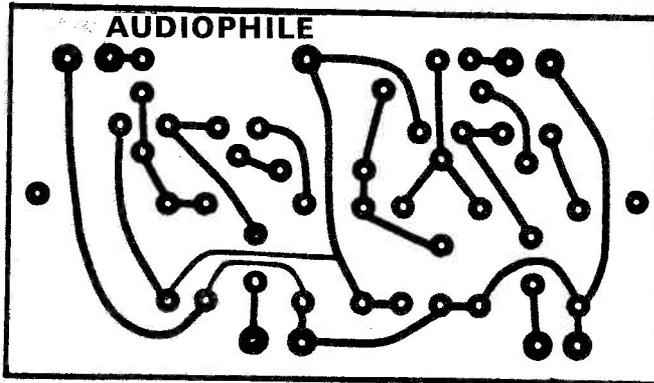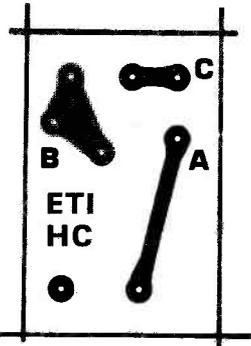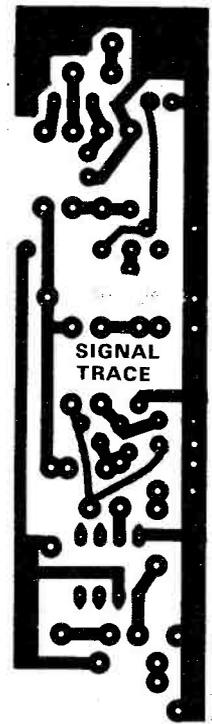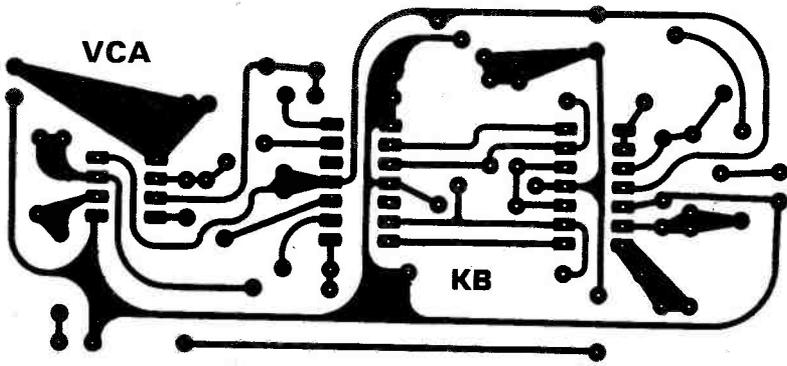


RANDOM ELECTRONIC EASY DICE

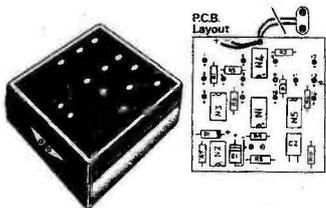

Self Assemble £3.95
Ready Built £4.75
Roll Out Model £5.25
INCLUSIVE VAT.

ADD 25p. POSTAGE PER DICE
SUPER VALUE!

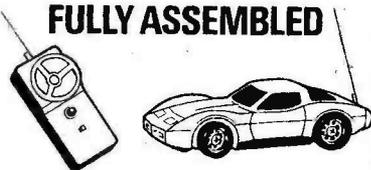5 FUNCTION RADIO CONTROLLED CORVETTE FULLY ASSEMBLED



£22.50 + 60p. p+p

CLOCK ALARM KIT FULL INSTRUCTIONS



£12.95 + 25p. p+p

T.V. GAMES B/WHITE
£8.95 + 25p. p+p

24 TUNE ELECTRONIC
DOOR CHIMES
£14.50 + 25p. p+p

CALCHEC EDUCATIONAL
CALCULATOR
£2.25 + 25p. p+p

ORDER FROM

Menorcrest Electronics Ltd.
1 Hatton Court
Ipswich Suffolk
Tel: 0473-210151/2

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in
£2.50 with all symbols for direct
application to P.C. board. Individual
sheets 25p each. (1) Mixed Symbols (2)
Lines 0.05 (3) Pads (4) Fish Plates and
Connectors (5) 4-Lead and 3-Lead and
Pads (6) DILS (7) BENDS 90° and 130°
(8) 8-10-12 T.O.S. Cars (9) Edge
Connectors 0.15 (10) Edge Connectors
0.1 (11) Lines 0.02 (12) Bends 0.02 (13)
Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over
250 symbols, signs and words. Also
available in reverse for perspex, etc.
Choice of colours, red, blue, black, or
white. Size of sheet 12in x 9in. Price £1.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours
red, blue, black or white. Each sheet
12in. x 9in contains capitals, lower case
and numerals 1/2in kit or 1/4in kit. £1
complete. State size.

All orders dispatched promptly.

All post paid

Shop and Trade enquiries welcome
Special Transfers made to order

E. R. NICHOLLS
P.C.B. TRANSFERS

DEPT. ET13

46 LOWFIELD ROAD
STOCKPORT, CHES. 061-480 2179

CALCULATORS

SPECIAL LOW PRICE ON PROGRAM- MABLES

CASIO	
FX 501P128 step prog	£47.95
FX 502P 256 step prog	£65.95
FA1 Adaptor to cassette	£19.95
TEXAS INSTRUMENTS	
TI42MBA 32 step	£40.95
TI53 32 step	£24.95
TI57 50 step	£25.95
TI58 480 step	£65.95
TI58C with power off memory	£84.95
TI59 960 step	£169.95
PC100C Printer cradle	£148.95
Maths/Utilities	£23.95
Electrical engineering	£23.95
Applied statistics	£23.95
Business decisions	£23.95
Marine navigation	£23.95

TEXAS Full range available	
TI25 Students scientific	£19.95
TI35 Sci L.c.d.	£20.95
TI44 L.c.d. Sci/Stats	£31.95
TI50 L.C.D. Sci/Stats	£21.95
TI1760 Datacard	£18.95
TI Programmer	£41.95

CASIO	
MATH PET L.c.d. Learning aid	£19.95
CO82 Multi Alarm Clock	£18.95
ML831 Musical Keys "NEW"	£13.95
AQ2000 Alarm/Stop/Date	£23.95
FX68	£18.95
FX80	£14.95
FX310	£16.95
FX510	£18.95
FX2600	£18.95
FX3200	£20.95
FX5000	£27.95
FX5000EP Scientific Mains Printer	£139.95
Conversion Master! Solve the metric problem with the IBICD 067 only	£16.95
Telephone Answering Machines	£169.95

ALL ADVERTISED GOODS FROM STOCK
PRICES INCLUDE POST, PACKING, AND V.A.T.

CALCULATOR SALES & SERVICE

ARROW WORKS, ARROW ROAD
REDDITCH B88 8NN

TEL: REDDITCH (0527) 43169

Callers by appointment only please.

Codespeed Electronics


P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR,
PORTSMOUTH, HANTS. PO3 5BJ

8 DIGIT 0.1" LED DISPLAY multiplexed, common cathode 99p each. DIGITAL ALARM CLOCK MODULE with 0.7" display. With data £5.99 each. 4 DIGIT CLOCK LCD 0.5" digits, supplied with data, £4.99 each. MM5316 digital alarm clock chip, with data, £2.29 each. REJECT CALCULATORS Untested, but good value for spares, £2.50 each. LED WRISTWATCH IC Mostek MK5030, with data, 95p each. LED WRISTWATCH DISPLAY type DIS501, 0.1" digits, with data 95p each. SUPER SAVER Purchase an MK5030 and a DIS501 for only £1.50 the pair. NOTE the MK5030 and DIS501 are housed in a "legless flatpack" style package and require some fairly fine soldering. 20-KEY KEYBOARDS calculator keyboards, 2 for 99p (not for use with NORTEC4204 calc. chip). 4 DIGIT 0.8" LED DISPLAY common cathode, with data £3.75 each. DIGITAL MULTIMETER CHIP MM5330 IC to build a 4 1/2 digit multimeter, with data, £3.49 each. SUPER QUALITY JACK SOCKETS 1/4" (6.35mm) jack sockets, mono 23p each, stereo 25p each. SLIDE POT KNOBS please state colour required, 11p each. ROTARY VOLUME CONTROL KNOBS nice style, 18mm diam. Black with coloured cap, please state colour required, 15p each. 10 LED DISPLAYS Untested material, 0.1" digits, common cathode, 95p. 8 DIGIT 0.1" LED DISPLAY multiplexed, common cathode, 99p. 555 TIMER IC with data and applications booklet, 23p. POLARIZING FILM max. 19" wide, any length, only 2p per sq. inch. Any size cut. SLIDER SWITCHES 2 pole, change over, 15p each. PUSH BUTTON SWITCHES spring loaded (momentary) with one n.o. contact, 14p each. CALCULATOR CHIP Nortec 4204, 4 function and constant, with data, 80p. 2102 MEMORIES Dynamic memories for your micros, with data 95p each. MM5314 digital clock chip, with data, £1.99 each. WRISTWATCH LCD, supplied with polarizers and data sheets, 99p each.

NEW CATALOGUE AVAILABLE FROM JANUARY. SEND S.A.E. FOR YOUR FREE COPY POST AND PACKING PLEASE ADD 35p (OVERSEAS ORDERS ADD 90p)

V.A.T. ADD 15% TO THE TOTAL OF GOODS AND P&P

FULL SATISFACTION GUARANTEE ON ALL ITEMS

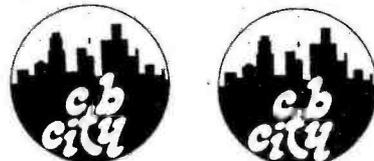

C.B. CITY LTD.

119d PROSPECT ROAD
FARNBOROUGH, HANTS.
0252-318141
(EVES. & WEEKENDS)

C.B. CITY is dedicated to all present and future Citizen Band Enthusiasts.

We stock a full range of everything you are likely to require and more. If not, we can most probably obtain it.

Duff Rig?? Then why not take advantage of our repair service — absolute confidence guaranteed.

Access, Credit Cards accepted.

Just send 3 x 10p stamps for our 16-page fully illustrated comprehensive catalogue.

REMEMBER!! Until C.B. becomes legal we DO NOT sell rigs.

CLASSIFIED INFORMATION


Semi-Display:—

1-3 insertions — £6.00 per single column centimetre
 4-11 insertions — £5.50 per s.c.c.
 12 insertions — £5.00 per s.c.c.

Classified:—

23 pence per word (minimum 25 words)
 Box number £1.00 extra

ORGANISE YOUR COMPONENTS!

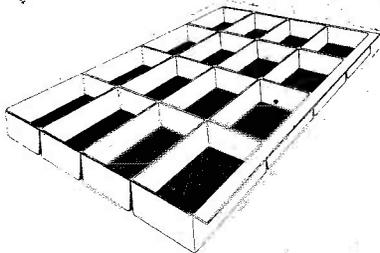

COMTRAYS

Store resistors, capacitors, IC's, screws, etc. Ideal for organising your project components — saves all that searching around while constructing. Plastic trays with 16 compartments, each compartment 3/4 x 2 1/4 x 1 1/2 ins. deep.

£2.10 each, including p.p. and VAT
 Four for £7.60 (64 compartments)
 Eight for £13.80 (128 compartments)

Cheque or P.O. to:

HELISTAR SYSTEMS LTD.
 150 WESTON ROAD
 ASTON CLINTON
 AYLESBURY, BUCKS HP22 5EP
 Tel. Aylesbury 630364

Nascom 1 plus P.S.U., documentation, spares, software, cased, £220. Also Motorola MEK D2, PSU, documentation and 77/68 V.D.U. PCB. £110. All fully working.—101 Village Road, Bromham, Bedford, MK43 8HU. Tel. Oakley 2867.

For Sale: Olivetti TE300 ASR 10CPS (Paper Tape Punch/Reader included) Terminal for Sale. Full working condition. £300.— Telephone 995 8038 (day) or 749 2750 (evgs.).

TRANSCENDENT 2000 SYNTHESIZER, built from Powertran kit, fully working to ETI Specification, with foot pedal and output lead. Must sell, hence £250. Tel: 01-660 3835 (Croydon).

INTENSIVE WEEKEND COURSES IN BASIC

including hands-on mini computer operation.

This short intensive course is intended to instruct from minimal knowledge to an operational capability of computer programming in BASIC high level language. The course is fully residential from Friday evening to Sunday afternoon.

Option of non-residential weekend, weekday evening and weekday courses available if required.

For further details of dates available, fees, etc.:

Phone (0401) 43139, or write to:
 Dept. ETI
CLEVELAND BUSINESS SERVICES
 Cleveland House, ROUTH
 Beverley, North Humberside

SOUND EFFECTS. Factory clear out. Top quality. Flangers, Phasers, Fuzz, Voice boxes, etc. Working units, Non-working units, Boxes only, PCBs. Cheap. Ideal for musician/experimenter. Phone Radrage (024026) 2707 for details.

10 LEDs mixed colours — sizes £1.15, 100 mixed diodes **85p**. 50 mixed transistors **95p**. Lists **15p**. Sole Electronics (ETI), 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

TOP QUALITY 1N4148 specification diodes on bandolier. 500, 1000, 5000 for £3, £5, £20. D. Johnston, 12 Balgillo Road, Dundee DD5 3LU.

LEDs Red Gre Yel	Orange L 74	55p	ORP 12 Ltr	62p
12cm 10p 16p 18p	LED DISPLAYS		00711 Photo Ir	40p
2in 11p 16p 18p	707 3in CA	90p	SFX25 Photo Ir	150p
4in Red GMYW	747 3in CA	170p	Photo Bar/Range	50p
AC125/6/7/8	2N2219	22p	V RES 1A Plastic	
AD161/162	2N2004/5/6/7	20p	SV 12V 15V 18V 24V	
AF17	2N2004/5/6A	22p	per 50p eq 85p	
AF124/5/6/7	2N2222(N)	9p	100mA T0092 + va	
AF139/239	2N2222(N)	11p	Types only	
BC107/8/9	2N3053	16p	Best adjustable ± 8 to	
BC107/8/9C	2N3054/3055	45p	20V 100mA	£2
BC147/8/9	2N3052/3/4	3p	723 DIL14	44p
BC157/8/9	2N3772	3p	709 all	28p
BC167/8/9	2N3003/4/5/6	12p	741 8 pin	18p
BC169C	2N2846	48p	748 DIL	35p
BC177/8/9	718430JT	25p	747 DIL 14	50p
BC182/3/4L	8F244	32p	LM301 TO5	25p
BC189/7	MPF 102	32p	LM308 DIL8	90p
BC212/3/4L	2K819	20p	LM3909 DIL 14	65p
BCY70/71/72	2K323	20p	CA 3130	80p
BD131/132	2N5245	85p	CA 3140	80p
BD139/140	2N5457/8/9	32p	555 Timer	22p
BF184/5/6/7	2N6827	34p	556 2x555	80p
BF189/40	1N814/4148	3p	LM380 DIL 14	80p
BF193/80	1N816	3p	LM391 DIL 14	140p
BFY59/51	1N4001/2	4p	TBA800 OIL	70p
BFX29/84/85	1N4003/4	6p	CA3046 Array	75p
BS119/20	1N4005/6	7p	NE565	130p
MJE2955	1N4007	8p	NE566 vcc	135p
MJE3055	3A Triac 50V 12p		ZN414	85p
MP4045/06	100V 14p 200V 16p		BRIDGES	
MP455/56	400V 10p 600V 24p		1A 2 10A 50V 22p	
OC71	10A/100V stud 22p		3p 150p	
TP229A/30A	8A100/156	11p	100 25p 40p	
TP314/32A	8AX16	8p	200 28p 45p 170p	
TP414/42A	8Y127	12p	400 34p 50p	
TP35/36/8	0A47/70/0A95		PCB Pen	60p
2N697	0A90/91	7p	Insulation kits	
2N706	0A79/0A81	10p	TO3/66/220	5p
2N1711	0A200/0A202	8p	LED Clips	3p

SCRs	50V 100V 400V	Diode SOCKETS	8pin 10p	ZENERS
T051A	28p 32p 40p	14pin 11p	15pin 12p	2.7-33V
T066 3A	32p 34p 48p	18pin 18p	20pin 20p	400mW 8p
STUD 7A	54p 58p 70p	22pin 22p	24pin 25p	1.3W 16p
Triac 400V 2A 70p	10A 1E	28pin 30p	40pin 35p	Diac 20p

ISLAND DEVICES 9 MAPLEFIELD PARK STREET, ST. ALBANS, HERTS AL2 2BD
 Prices inclusive Post & Pack 20p


ALL ADVERTISEMENTS IN THIS SECTION MUST BE PRE-PAID

Closing date: 1st Friday in month preceding publication.
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

Cheques and postal orders should be crossed and made payable to 'Electronics Today International.'

CLASSIFIED ADS, E.T.I., 145 CHARING CROSS ROAD, LONDON WC2H 0EE. (TEL: 01-437 1002).

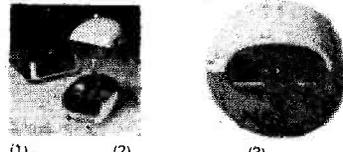BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.
 (1) With alarm repeat — S.R.S.P. of £17.00 offered at **£3.95** inc. VAT.
 (2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at **£7.95** inc. V.A.T.
 (3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues, S.R.S.P. of £32.00—offered at **£7.45** inc. V.A.T.
 These will be sold as received from our customers with the existing fault(s) and without guarantee.
Discounts available on large bulk purchases
PRESCOTT CLOCK AND WATCH COMPANY LIMITED
 Prescott House, Humber Road, London NWZ 6ER

CIRCUIT DESIGN, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherthorn Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

MK. 14. Replace calculator type display with full size FND 500 displays, PCB, filter and instructions, £2. 25-way keyboard, complete kit, £10. Useful notes on Mk. 14, 50p. Rayner, "Kismet," High Street, Colnbrook, Bucks.

E.T.I. 4600 SYNTHESIZER. Maplin cabinet, 4-octave keyboard joystick, patch-board, fully calibrated, ready to play. Only three modules to complete. £410 o.n.o. Phone Harpenden 60958.

STOP PRESS: Superboard Compatible!
UK101 TRS 80
COLOUR YOUR NASCOM!

DAZZLING COLOUR GRAPHICS FOR NASCOM 1
 Genuine bit-addressable "pixel" system for straightforward programming of pictorial or mathematical functions.
 8 Colour display plus 8 colour independent background facility. Full documentation with FREE SOFTWARE: powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems — send us diagrams etc of your b & w video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.
NOW AVAILABLE FOR LIMITED PERIOD AT £45 Inclusive of VAT and postage.
WILLIAM STUART SYSTEMS Ltd Dower House, Billerica Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

ETI PCB'S
 Buy it with Access
 BARCLAYCARD

Available for most ETI projects from day one of ETI, phone your order.

SPECIAL OFFER—Single sided Pax PCB mat, four off, 4 3/4" x 6 1/2", 99p all up.

CROFTON ELECTRONICS LIMITED
 35 GROSVENOR ROAD, TWICKENHAM MIDDLESEX TW1 4AD • Tel: 01-891 1923

DIY with the PROFESSIONALS

Construct your own mixer, large or small, from our range of commercial electronic sub units. The same high-quality units used to construct our own audio mixers supplied to radio stations, public buildings, government depts. etc. Now available in kit form or assembled and tested. Plus full range of panels, metal frames etc. Postal enquiries to **Dept. D.E.T.**

PARTRIDGE ELECTRONICS

(A. C. Partridge Ltd)
56 Fleet Road, Benfleet, Essex
Telephone (STD 03745) 3256

WANTED: ELECTRONIC COMPONENTS, Redundant Stock, Test Equipment, Tools, Machines, Hardware; Factories cleared. Immediate cash decision. Contact: Mr. Quirk, "Q" Services Electronic (Camberley) Ltd., 29 Lawford Crescent, Yateley 871048, Camberley, Surrey.


Stereo Slide Controls. 100 K Ohm Linear Pots. 60mm. stroke. 80mm Fixing. 10 for £4 post paid. — CASS, 110 Blackmoor Drive, Liverpool, L12 8RA.

TGS GAS SENSORS 812 & 813. Send addressed envelope 6½" x 9" for Tech. Data and Prices. Design service also available. Asti Supplies Ltd., Shannon, Co. Clare, Ireland.

Programmable Calculators with 56-page instruction book plus Program Library, new and booked. £12.50 including P/P, insurance. — F. S. Butler, 511 Fulbridge Road, Peterborough, PF4 6SB. Tel: 0733 71958.

Linsley-Hood Amplifiers constructed and repaired. Power Amp Modules from £13.75. I. G. Bowman (Dept. ETI), 59 Fowey Avenue, Torquay, S. Devon.

VIDEO MUSIC

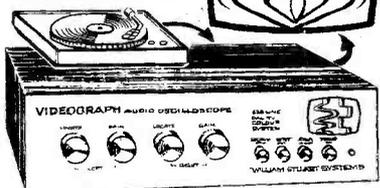

Videograph II links to the aerial socket of your tv and provides a full colour GIANT oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. **Plus** — full details for testing your audio system for transient distortion, crosstalk etc.

Complete Kit only £26.95 **Luxury cabinet and controls. £12.95**

READY BUILT UNIT £49.95 + £1.00 P&P

WILLIAM STUART SYSTEMS Ltd. Telephone: Brentwood (0277) 810244
Power House, Miller Way Road, Herongate, Brentwood Essex CM13 3SD

50Hz SUPERBOARDS BRITISH MODEL

from **£190** + VAT

Fully built, set up and tested

AUTHORISED dealer back-up

Free cursor control backspace, etc. tape

C.T.S., 1 Higher Calderbrook Littleborough, Lancs.

Tel. Littleborough 79332 any time

MEDICAL PHYSICS TECHNICIANS

YOUR EXPERIENCE COULD LEAD TO A HAPPY EXPERIENCE IN HAMPSTEAD . . . working at the Royal Free Hospital, Britain's newest and largest teaching hospital.

We offer an experienced Technician (Grade IV — Electronics) the chance of working on the design and construction of specialised electronic equipment, which will be used in both research and clinical applications. This is an excellent opportunity for a man or woman who holds a City and Guilds Final Technological Certificate in appropriate subjects and ideally has experience in the use of both analogue and digital circuit techniques.

You will be working with four other Technicians and, apart from your design work, you will be expected to carry out maintenance on a wide range of commercial apparatus within our purpose-built and well-equipped workshop.

In addition to the salary of £4280-£5504 (including all allowances — starting point depending on qualifications and experience), we offer a first-class working environment and a superb choice of facilities which include a good staff restaurant, a social club and a brand new recreation and leisure centre with a large sports hall, swimming pool and bar.

If you would like to find out more, write to the Personnel Department, The Royal Free Hospital, Pond Street, NW3, or telephone 01-794 0500, ext. 4286. Please quote reference 0761.

Camden & Islington Area Health Authority (T).

A SUPERB QUALITY STEREO POWER

AMPLIFIER OFFER! Protected output of 60w (RMS-8Ω) Stereo via din socks. Case inc., controls vol., select, etc., Power Smoothing, 12/35v wkg. 0.03% Thd. 22 trans., 1 amp drivers — 90.w plastic outputs. Tested — Boxed — data £11.95. Queries s.a.e. please. Klifco Electronics, 1 Regent Road, Ilkley, W. Yorks LS29 9EA.

SITS-VAC

H.N.C. IN ELECTRONICS?

Put your well earned qualifications to good use by joining our expanding Medical Engineering Section!

We are responsible for the maintenance of Important Life-Saving Medical Equipment and have several opportunities for Technicians with sound knowledge and experience of maintaining any of the following equipment:

Anaesthetic Apparatus, Therapeutic and Diagnostic Physiological Measurement Machinery, Laboratory and Special Electro-Medical equipment.

Salary range £4605-£6918 depending on qualifications.

If you would like to know more about these posts please contact: **Mr. D. L. Hall, District Engineer (021) 554 3801 Ext. 4838**, or obtain an application from from:

**District Works Officer
Dudley Road Hospital
Birmingham B18 7QH**

Closing date ten days after publication of this advertisement. Please quote Ref. 619/ET.

HOLIDAY RELIEF STAFF

WEST LONDON

ASSISTANT FILM RECORDISTS

To undertake the operation of tape, disc and 16mm recording and replay equipment in Sound Transfer areas and Dubbing Theatre Record Rooms. (Ref. 2025/ET).

ASSISTANT DUBBING MIXERS

To undertake the operation of disc and tape machines, to select and introduce sound effects and music required during the dubbing process and to act as an Assistant to the Dubbing Mixer, as and when required. (Ref. 2024/ET).

A knowledge and experience of film sound transfer and dubbing methods, coupled with an understanding of the use of sound in television film production is essential, also normal hearing.

Salary: £4,185-£4,535 p.a. (Salaries review due in April). Staff will be required on a temporary basis for approximately 3 months, and will be expected to work on a shift basis (not nights) when a shift allowance rate will be paid.

Contact us immediately for application form (quote ref. and enclose s.a.e.): **BBC Appointments, London W1A 1AA. Tel. 01-580 4468, Ext. 4619.**

BBC tv



CCTV CAMERA

£114.99 + P/P £3.45
Optional extra manual: £6. Total £124.44.

BEST OFFER EVER
Camera Kit, Lens,
Vidicon & Modulator

CROFTON

Tel: 01-891 1923 For full details

COLOUR MODULATOR

Kit **£9.95** FOR ALL TV GRAPHICS!
Red, Green, Blue inputs (can be mixed).
Available now: Nascom Colour Kit.
£45.00 inc. Graphics Software.

WILLIAM STUART SYSTEMS
Dower House, Billericay Road, Herongate, Brentwood, Essex
CM13 3SD Tel: (0277) 810244
Barclaycard/Access welcome

MSF CLOCK

NOW GET ABSOLUTE TIME. Always correct, never gains or loses, auto GMT/BST and Leap Year. 8 digits show DATE, HOURS, MINUTES and SECONDS, also parallel BCD output and second-in-a-month STOP CLOCK, receives Rugby time signals, built-in antenna. EXACT TIME for **£48.80**.

60KHz Rugby Receiver, as in MSF Clock, 1000KHz range, audio and serial data outputs, **£13.75**.

V.L.F.7 EXPLORE 10-150KHz Receiver, **£10.70**.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage, etc., money back assurance, so SEND off NOW.

CAMBRIDGE KITS

45 (TC), Old School Lane, Milton, Cambridge

DIGITAL CAPACITANCE METER

1 pF-2 µF in 5 ranges; on-board selector. Precision resistor network and giant displays give direct readout in pF, nF and µF. ASSEMBLED, ONLY **£22.92** ALL INC. Overseas add £1. Precision Measurements, P.O. Box 70, Giles Lane, Canterbury, Kent, CT1 2UU.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories.

Selected range of popular components
Full range of HE printed circuit boards, normally ex-stock, same day despatch at competitive prices.
P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Full range of etch resist transfers, and other drawing materials for p.c. boards.

Send 15p for catalogue.


RAMAR CONSTRUCTOR SERVICES
MASON'S ROAD
STRATFORD-ON-AVON
WARWICKS, Tel. 4879

PROCESS PHOTOGRAPHY. 2:1 reductions of P.C.B. artwork, etc. Prices for positives: 5½ x 7 £3.50, 7 x 11 £4.50, 11 x 14 £6.00. Return of post + 50p or while you wait for afternoon callers. D.J.S. Electronics, Totterdown Centre, 140 Wells Road, Totterdown, Bristol BS4 2AQ, 0272 776289.

TRANSCENDENT 2000: Synthesizer. Why wait to build your own. Fully built. Play it for yourself, £200 o.n.o. Kidderminster O562-741631 (after 6 p.m.).

E.T.I. back numbers most issues from 1973. Also TTL, semiconductors, caps, resistors, R.S. components (switches, etc.) cheap. S.A.E. please. Chamberlain, 9 Goffs Close, Crawley, Sussex.

DIGITAL WATCH BATTERY REPLACEMENT KIT

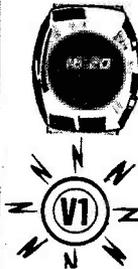

These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send **£7.50** for complete kit and get into a fast-growing business. Prompt despatch.

WATCH BATTERY REPLACEMENT CO. (ET10)
11 Percy Avenue, Ashford, Middx., TW15 2PB

FOR SALE:

Electronics Today International (April 1972 to November 1979)
Electronics Tomorrow (single issue)
Hobby Electronics (November 1978 to October 1979)
Computing Today (March 1978 to September 1979)
Personal Computing World (May 1978 to May 1979)
Offers to: N. V. Pedersen, 19 Belgrave Street, Brighton, or phone Brighton 692789.

ADVERT INDEX

AJD DIRECT SUPPLIES	70
ALYK INSTRUMENTS	48
AMBIT INTERNATIONAL	23
AUDIO ELECTRONICS	59
BARINGSLOCK LTD	6
BAYDIS	38
BI PAK SEMICONDUCTORS	14
BK ELECTRONICS	62
CALCULATOR SALES & SERVICE	102
CAMBRIDGE LEARNING ENTERPRISES	70 & 71
C. B. CITY LTD	102
CHILMEAD	37
CHROMASONICS	57
CLEF PRODUCTS	76
CODESPEED	102
COMP. COMP. COMP.	106 & 107
CRIMSON ELEKTRIK	84
CROFTON ELECTRONICS	62
C.S.C.	7
DELTA TECH & CO	26
ENGSOUND LTD	28
E.B.A.	53
ELECTROVALVE	6
GREENBANK	56
GREENWELD	85
GWT ELECTRONICS	24 & 25
HAMEG LTD	86
HENRY'S RADIO	85
I.L.P. ELECTRONICS	38, 85 & 94
JPS	44 & 45
L.B. ELECTRONICS	85
L & B ELECTRONICS	18
LEYTRONICS	76
MARLIN	19 & 108
MARSHALL	48
MEMORCREST	102
METAC	54 & 55
MINIKITS	103
MOUNTAINDENE	15
E.R. NICHOLS	102
NIC MODELS	48
POWERTRAM COMPUTERS	48
POWERTRAM ELECTRONICS	2 & 8
PROGRESSIVE RADIO	38
PROTON ELECTRONICS	38
J. W. RIMMER	38
ROMANE ELECTRONICS	38
R.T.V.C.	76
SCIENCE OF CAMBRIDGE	62
C. N. STEVENSON	4 & 5
STEVE'S ELECTRONICS	40
SURETRON	84
SWANLEY ELECTRONICS	18
TANDY	28
TECHNOMATIC	10
TEMPUS	53
TK ELECTRONICS	84
TRANSLAN	98
VIDEOTIME PRODUCTS	12 & 13
WATFORD ELECTRONICS	88
WEST HYDE DEVELOPMENTS	88
WILMSLOW AUDIO	28

Car Audio

Manual MW/LW

Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

£10.25 + £1.00 Post

Push-Button MW/LW

One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

£15.95 + £1.00 Post

Stereo FM/Cassette + MW

Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

£40.95 + £1.00 Post

Stereo Speaker Set

Suitable for above stereo unit. Good quality in surface mounted casing, 5W nominal, 8W peak.

£4.00 (pair)

+ 70p Post

Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

£1.60 + 30p Post

Metal Detector

★ Induction Balance Model

Built with sensitivity up to 10in on single coin; fitted with speaker and meter; PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

£24.50 + £1.00 Post

All goods guaranteed one year, 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for illustrated leaflet.

Minikits Electronics Ltd.
88D Hainault Road
Leytonstone
London E.11

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes 10 for	£4.00
Super Multi-rail P.S.U. +5 -5 +12v	£29.50
Nascom I with Nas-sys	Special Price
Kit	£125.00
Assembled } Limited quantities	£140.00
ETI Breakout Game — Chip and PCB	£9.90
S100 Expansion Motherboard for Nascom I	£39.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Disks 5¼" Hard & Soft Sectored	£3.50
Floppy Disk Library Case 5¼"	£3.50
Lexicon Language Translator	£125.00
Modules for Lexicon	£29.00
Eprom Boards	£63.00
8K Static Ram Boards — S100	£110.00
Grandstand Video Game	£59.00
Cartridges for Grandstand	£11.99
George Risk Ascii Keyboard	£39.00
Cartridges for Atari — Full Range in Stock	£13.90
Interface PET IEEE — Centronics Parallel Not decoded	£49.00
Decoded	£77.00
Interface to Centronics parallel for TRS80	£75.00
Verocases for Nascom 1 & 2 etc.	£22.50
Keyboard Cases	£9.90
Electric Pencil for TRS80	£29.00

only **£399**
- VAT



TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time-buyers. Just plug in and go. Full Range of Software Available

NEW REDUCED PRICES

8K **£449**
16K **£549**
32K **£649**



RRP £795 for 32K **The PEDIGREE PETS**

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen. Extra cassette deck **£55** Full range of software available

32K **£690**
+ VAT



EXIDY SORCERER

For Personal or Business Use. 32K or 48K memory, 8K Microsoft Basic in ROM. Dual Cassette I/O, RS232 I/O, Parallel I/O (Centronics). Expansion available through optional extra S100 Motherboard. 69 Key keyboard including 16 key numeric pad.

S100 EXPANSION — £199

RRP £975 for 48K

48K — **£690**
+ VAT



ITT 2020

Full colour into your own colour T.V. PALSOF 9 digit floating point Basic in ROM as standard. Low and High resolution graphics. Built in loudspeaker. Compatible with most Apple Hardware add-ons and software.

only **£295** + VAT

Expand your TRS80 by 32K. 32K Memory on board. Centronics parallel port. Disk controller card. Real time clock. Requires Level II Basic. Interface for 2 cassette decks complete with power supply.

TRS80 EXPANSION INTERFACE

RRP £540



only **£499**
+ VAT

ANADEX DP8000

Super Quality — Low cost printer. Tractor Feed with full 96 ASCII character set. Accepts RS232C at band rates between 100 and 9600 and Parallel 8 bit data. Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, CompuKit etc.

RRP £690

only **£590** + VAT



IBM SELECTRIC GOLFBALL

Refurbished IBM Golfball Printers to new specs. Accepts Centronics parallel data. Friction feed. Prints at 15 cps. Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, CompuKit etc.

video 100




12" BLACK & WHITE LOW COST VIDEO MONITOR

RRP £79

only **£69** + VAT

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video output
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum in Central 80% of CRT; 550 Lines Minimum beyond central 80%.

HITACHI PROFESSIONAL MONITORS


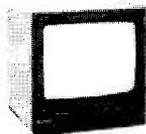


9" — **£129**
12" — **£199**

- **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability.
- **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved in picture center.
- **Stable picture** Even played back pictures of VTR can be displayed without jittering.
- **Looping video input** Video input can be looped through with built-in termination switch.
- **External sync operation** (available as option for U and C types)
- **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

A PROFESSIONAL WORD PROCESSING SYSTEM AND IT'S A COMPUTER AS WELL.

FOR ONLY **£3250** + VAT

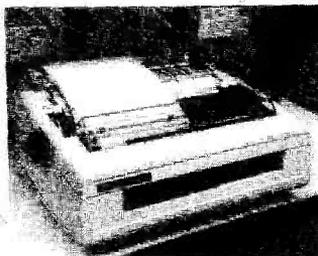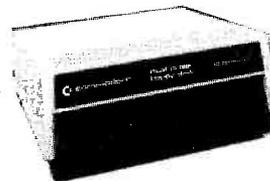

PET 32K — This is the standard 32K Pet from Commodore. Reverse video and graphics allow the WordPro Package to give simple clear and easy to read displays.

2040 Disk Drives Twin disk drives allow large high speed storage for your letters, or paragraphs. Plugs in the back of the PET.

NEC Spinwriter NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel,

giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds.

55 characters per second bidirectional printing — with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.

WordPro II The heart of the system — consists of a ROM and diskette. The ROM is inserted into a space socket inside the Pet. One of the most versatile Word Processing Packages around.

NASCOM-2 MICRO-COMPUTER



only **£295**
+ VAT

Microprocessors Z80A. 8 bit CPU. This will run at 4MHz but is selectable between 1/2/4 MHz. This CPU has now been generally accepted as the most powerful, 8 bit processor on the market.

INTERFACE

Keyboard New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding.

T.V. The tv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T.V.

I.O. On-board UART (Int 6402) which provides serial handling for the on-board cassette interface or the RS232/20mA teletype interface.

The cassette interface is Kar'sas City standard at either 300 or 1200 baud. This is a link option on the NASCOM-2.

The RS232 and 20mA loop connector will interface directly into any standard teletype.

The input and output sides of the UART are independently switchable between any of the options — i.e. It is possible to house input on the cassette and output on the printer.

PIO There is also a totally uncommitted Parallel I/O (MK3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.


Documentation Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.

Basic The Nascom 2 contains a full 8K Microsoft Basic in one ROM chip with additional features like DEEK, DOKE, SET, RESET for simple programming.

With free 16K RAM board.

COMPUKIT UK101

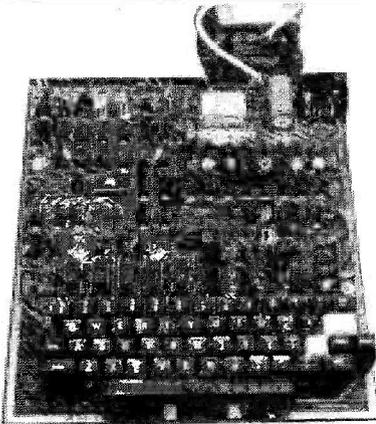EUROPE'S FASTEST SELLING ONE BOARD COMPUTER



Simple Soldering due to clear and concise instructions compiled by **Dr. A.A. Berk, BSc. Ph.D.**

- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape Interface on board.
- ★ Free Sampler Tape including powerful Dissampler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

Build, Understand and Program your own Computer for only a small outlay.

KIT ONLY **£199** + VAT
NO EXTRAS NEEDED

AVAILABLE READY ASSEMBLED & TESTED
READY TO GO FOR **£249** + VAT

Specially designed case for CompuKit in orange/black. With room for accessories. **£29.50** + VAT

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programs. By pressing the C key the world of Basic is open to you.


This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use.

Because of the enormous volume of users of this kit we are able to offer a **new reduced price of £199** + VAT

THE NEW TRS80 SURPRISE — MODEL II

Fast and expandable!

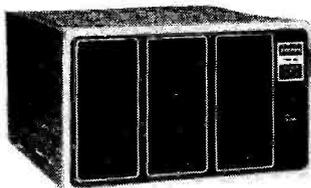Model II operates at twice TRS-80's high speed.



In addition to either 32 or 64 thousand characters (bytes) of internal Random Access Memory, one built-in 8" floppy disk stores an additional one-half million bytes, including the Disk Operating System. And you can easily expand up to a four-disk system for up to two-million bytes of storage.

Model II features upper and lower case letters. Its built-in 12" high-resolution video monitor displays 24 lines of 80 normal characters. The professional 76-key keyboard (with "calculator" keypad) includes advanced functions such as Control, Escape, Caps, Hold, Repeat. The keyboard is detachable and moveable for convenient data entry.

You get the enhanced Level III version of TRS-80's already-famous Level II BASIC language and "TRS-DOS" operating system, automatically loaded in memory when you "power up." (About 24K of RAM is used by this software.)

Each time you power up, Model II thoroughly tests itself to insure proper operation. Your chosen program can appear immediately, without any intermediate steps or questions to answer.

Versatility ... plug-in expandability

Built-in input/output capabilities include two RS-232C channels, and one Centronics parallel port. Future expansion is provided for through four plug-in slots for optional PC boards.

32K 1-Disk Model II

£1999.00 + VAT

64K 1-Disk Model II

£2200.00 + VAT

3 DISK EXPANSION

500K per Drive gives total of 1.5M Byte for only **£1399** + VAT

Just Plug In

WE ARE NOW EX-STOCK



Why do people buy more from COMPSHOP than anywhere else?

- ★ **LARGER STOCKS** — we hardly ever run out
- ★ **GOOD SERVICE** — we give extended warranties on all our products.
- ★ **EXCELLENT REPAIR SERVICE** — Through Compcare we repair and maintain most makes of personal computers.

LAST YEAR WE SUPPLIED TO THE PUBLIC — LARGE & SMALL
16,000 Television Games & 7,000 Computer Systems



Compcare is a company that has been set up to provide servicing and maintenance for the popular makes of micro-computers i.e. Sorcerer, Pet, Apple, TRS80, Nascom, CompuKit. Our charges are £7 per hour plus parts.

Because of the extensive range of spare parts stocked you can usually expect your micro to be repaired within 10 days for an average charge of £14 labour.

Emergency 24 hour repairs can be handled for a £10 surcharge where possible.
CompuKits and Nascoms unsuccessfully constructed will be charged a standard £25.

THE ATARI VIDEO COMPUTER SYSTEM

£138
+ VAT



Atari's Video Computer System now offers more than 1300 different game variations and options in twenty great Game Program™ cartridges!

Have fun while you sharpen your mental and physical coordination. You can play rousing, challenging, sophisticated video games, the games that made Atari famous.

You'll have thrill after thrill, whether you're in the thick of a dogfight, screaming around a racetrack, or dodging asteroids in an alien galaxy. With crisp bright colour (on colour TV) and incredible, true-to-life sound effects. With special circuits to protect your TV.

Cartridges now available All at £13.90 each + VAT

Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle Codebreaker*, Miniature Golf.

Extra Paddle Controllers
— **£14.90** + VAT

*Keyboard Controllers
— **£16.90** + VAT



Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number.
CREDIT FACILITIES ARRANGED — send S.A.E. for application form.
14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G
Telephone: 01-441 2922 (Sales) 01-449 6596
OPEN - 10 am - 7 pm — Monday to Saturday

Close to New Barnet BR Station — Moorgate Line.

COMP COMPUTER COMPONENTS

(Part of the Compsshop Ltd. Group)



MAPLIN



This superb organ – build the first working section for just over £100. Full specification in our catalogue.




Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



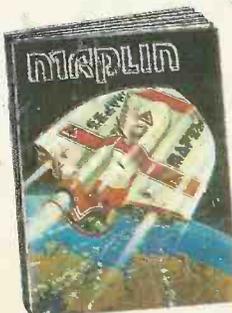61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.

A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____

ADDRESS _____

ETI 3 / 80



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.

MAPLIN
ELECTRONIC SUPPLIES LTD


All mail to:-
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex.
(Closed on Monday).
Telephone: Southend (0702) 554000.

New Babanis

Amaze your friends with the number of uses to which you can put a single IC. You won't be short of ideas with 'Single IC Projects' by R. A. Penfold. This 127 page volume from Bernard Babani is divided into five sections, covering low level audio circuits, audio power amplifiers, timers, operational amplifiers and miscellaneous circuits.


Each circuit suggestion begins with a brief description of the chip used, together with a table of its chief characteristics. In each case a circuit diagram, practical layout, constructional details and parts list is given. These twenty simple projects could be yours for £1.50.

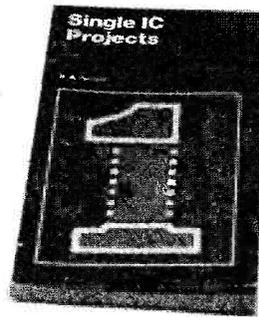Also from Babani is Book 3 in their Elements of Electronics series. Book 3 continues this introduction to electronics with sections on semiconductor physics and characteristics. Basic semiconductor applications are described, including



rectifiers, amplifiers, oscillators and switches. Book 3 of Elements of Electronics by F. A. Wilson (204 pages) is priced at £2.25.

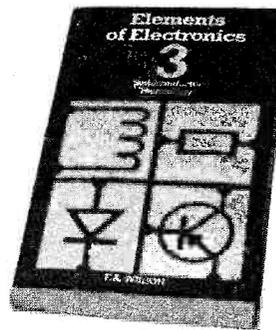If you have trouble getting these books they are available direct from the publisher, Bernard Babani (Publishing) Ltd,



The Grampians, Shepherds Bush Road, London W6 7NF. A complete catalogue of Radio and Electronics Books is also available from this address. Please send a stamped, addressed envelope. When ordering books, please send enough to cover postage.

Anti-Gravity Meter

You won't have a smashing time with this meter. The 3012 from Dorman Smith Instrumentation is a drop proof pocket tester giving DC volts (0V3 to 1000V), DC current (50 uA to 300 mA), AC volts (10V to 1000V) and resistance (10k to 1M ranges).

The meter will withstand being dropped from one metre — the height of the average workbench or jacket pocket. It incorporates a taut band movement and fuse protection. Power is from a size AA 1V5 battery.

The 3012 pocket test is available for £27 plus VAT including batteries, test leads, soft case and strap from Dorman Smith Instrumentation, Blackpool Road, Preston PR2 2DQ.

Tick Talk

If you have about a hundred dollars to spare you can invest it in the latest in alarm watches. The communicator, from Windert, uses a 64 kilobyte memory chip to carry its computer voice. It 'tells' you the time, talks you awake in the morning and nags you if you don't get up (makes the wife redundant).

The time, alarm and snooze messages are to be available in English, French, German and Spanish. In the not-so-distant future Windert have prophesied the development of programmable voice command watches and even the sci-fi cliché — watches with built-in TV screens and transmitters.

See-Thru Tops

Boss Industrial Mouldings have extended their BIM 2000 range of Bimboxes to include a new two part, deep profile version. Base and lid are available in black, grey, orange or blue, with the additional option of a clear lid. As with the rest of the Bimbox range, the new versions have 5.08 mm (0.2in) spaced slots on all sides of the base to support 1.5 mm PCBs.

The clear lid version is ideal for applications where viewing of, but not necessarily access to, internal components is required. The new Bimboxes, each 80.2x150.4x76 mm, are available from Boss Industrial Mouldings Ltd, 2 Herne Hill Road, London SE24 0AU.


Sat 54 Where Are You?

Well, it was Satcom 3 actually, but the plot is reminiscent of that old, old American telly series. The Car 54 in this case, however, was an RCA communications satellite, last heard of in December, 22,000 miles above mother Earth.

If anyone finds a communications satellite answering to the name of Satcom 3, send it to RCA, nto us. Mind you, if it has gone up in a puff of smoke, it has probably burned up on its way back to Earth. NASA quick to assure us that it won't cause another Skylab incident. So, you needn't dust off your anti-Skylab umbrella, yet.

CMOS Class

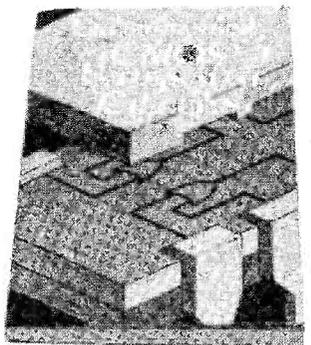Having trouble getting to grips with your CMOS? Understanding CMOS Integrated Circuits by Roger Melen and Harry Garland is an introduction to CMOS, covering everything from how the chips are made to a few simple practical CMOS circuits.



Almost half of the book is devoted to a summary of types of logic gates, semiconductor physics and CMOS fabrication techniques. The remainder gets down to the nitty gritty — CMOS circuit design, including waveform generators and information-processing circuits.

This 144 page American paperback is available in the UK from Prentice/Hall International, 66 Wood Lane End, Hemel Hempstead, Herts, HP2 4RG for £3.60.


Key Box

If you have a QWERTY keyboard, we can now tell you where to put it. Vero have introduced an attractive two-tone brown 17in. wide modular keyboard enclosure designed to house most universal layout QWERTY keyboards.

The front panel can be slid out for service or programming by removing the base screws and the end moulding, so there are no visible fixing screws on the front panel.

The enclosure can be supplied in non-standard lengths to allow the addition of extra key-pads, etc.

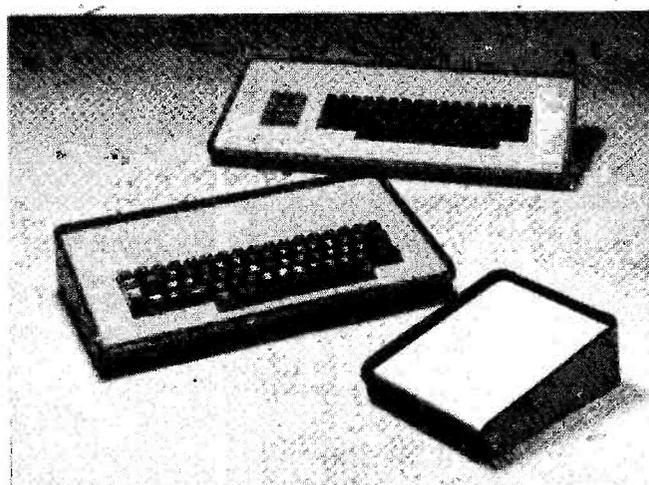The modular keyboard enclosure is available from Vero Electronics Ltd, Industrial Estate, Chandler's Ford, Eastleigh, Hampshire SO5 3ZR.



WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME
Tel. Watford (0923) 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY POSTAGE. P&P add 30p to ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type.
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 48p; 1µF 64p; 2µ 82p.
160V: 10n, 12n, 33n, 100n, 150n, 220n 11p; 330n, 470n 19p; 680n, 1µF 22p; 2.2µF 32p; 4.7µF 36p.
1000V: 10n, 15n 20p; 22n 22p; 47n 26p; 100n 38p; 470n 53p; 1µF 175p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10n, 15n, 22n, 27n 5p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p; 680n 19p; 1µ 22p; 2µ 30p; 4µ 34p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF).
500V: 10 40p; 47 85p; 250V: 100 25p; 470 32p; 1000 50p; 40V: 22, 33, 8p; 100 12p; 2200, 3300, 85p; 4700, 98p; 35V: 10, 33, 7p; 330, 470, 32p; 1000, 50p; 25V: 10, 22, 47p; 80, 100, 180, 8p; 220, 250, 13p; 470, 640, 25p; 1000, 27p; 1500, 30p; 2200, 40p; 3300, 45p; 4700 85p; 18V: 10, 47, 68, 7p; 100, 125, 9p; 220, 33p; 14p; 470, 16p; 1000, 1500, 20p; 2200, 34p; 10V: 10, 10p; 840, 12p; 1000, 14p.
TAG-END TYPE: 450V: 10µF 180p; 70V: 4700, 186p; 64V: 3300 130p; 2500 88p; 80V: 4700 150p; 3300 105p; 2200 89p; 10µF: 15,000 399p; 4700 120p; 4000 82p; 3300 83p; 2500 85p; 30V: 4700 90p; 25V: 15000 185p; 6400 106p; 4700 85p; 3300 80p; 2200 80p.

TANTALUM BEAD CAPACITORS: 35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2µF, 3.3, 4.7, 6.8, 8.2, 25V: 1.5, 1.0, 20V: 1.5, 15V: 1.0µF, 10µF, 13p each.
16V: 15, 22, 25p, 47, 100, 220 40p.
10V: 15, 22, 33, 47, 100, 220 30p.
6V: 47, 68, 100, 20p; 3V: 100 20p.

MYLAR FILM CAPACITORS: 100V: 0.001, 0.002, 0.005, 0.01µF 7p; 0.015, 0.02, 0.04, 0.05, 0.056µF 7p; 0.1µF, 0.2, 1.1µF, 50V: 0.47µF 12p; 0.407µF 5p; 0.1µF, 0.2µF 7p.

CERAMIC CAPACITORS 50V: Range: 0.5pF to 10,000pF 4p; 0.015µF, 0.022µF, 0.033µF 5p; 0.0407µF 5p; 0.1µF, 0.2µF 7p.

SILVER MICA (Values in pF): 3.3, 4.7, 6.8, 10, 12, 18, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220 9p each; 250, 270, 300, 330, 360, 390, 470, 600, 800, 820 16p each; 1000, 1200, 1800, 2000 20p each.

POLYSTYRENE CAPACITORS: 10µF to 1nF 9p; 1.5nF to 47nF 10p.

MINIATURE TYPE TRIMMERS: 2.5-6pF, 3-10pF, 10-40pF 22p; 5-25pF, 5-45pF, 60pF, 88pF 30p.

COMPRESSION TRIMMERS: 3-40pF, 10-80pF, 25-190pF 30p; 100-500pF, 450p 400-1250pF 58p.

GAS & FLAME DETECTORS: TGS 812 & 813 415p; Socket 25p.

JACKSONS VARIABLE CAPACITORS: Dielectric 100/300pF 175p; 500pF 205p; 6-1 Ball Drive 115p; 45/11/DAF 650p; Dial Drive 4103 61/36-1; Drum 54mm 40p; 0-1-365pF 245p; 0-2 365pF 275p.

RF CHOKES: 1µH, 4.7, 10, 22, 33, 47, 100, 200, 470, 750, 1mH, 2.5, 5, 10 30p each; 43mH 100 80p each.

VERO BOARD: 0.1, 0.15, 0.15 (copper clad) (plain) 46p 39p 24p; 2 1/2 x 3 1/2 55p 50p 31p; 2 1/2 x 3 3/4 55p 50p 31p; 3 1/2 x 5 75p 67p 43p; 2 1/2 x 1 7/8 189p 135p 82p; 3 1/4 x 1 7/8 218p 180p 120p; 4 1/4 x 1 7/8 280p 183p; Pkt of 36pins 20p DIP Board 268p; Spot face cutter 85p; VQ Board 90p; Pin insertion tool 120p; EURO BREADBOARD 530p; VERO BREADBOARD 340p.

FERRIC CHLORIDE: 1lb bag Anhydrous 95p + 35p P&P

DALGETT RESIST P&P: + spare trip 78p

COPPER CLAD BOARDS: Fibre Single-sided 9RP; Glass sided 5RP; 8" x 6" 75p; 8" x 12" 130p; Double-sided 8RP; 9.5" x 8.5" 80p.

SOLDERING PENS: 100 50p; 500 200p; 14pin 35p; 16pin 39p.

DIL SOCKETS (TAXES) Low Wire Prof. Wasp: 8pin 10p; 12pin 15p; 14pin 15p; 16pin 15p; 18pin 15p; 20pin 22p; 22pin 25p; 24pin 30p; 26pin 35p; 28pin 35p; 30pin 105p; 40pin 50p 109p.

EDGE CONNECTORS: 2-Dial type: 10pin .1 156p; 12pin .15 156p; 14pin .15 156p; 16pin .15 156p; 18pin .15 156p; 20pin .15 156p; 22pin .15 156p; 24pin .15 156p; 26pin .15 156p; 28pin .15 156p; 30pin .15 156p; 32pin .15 156p; 34pin .15 156p; 36pin .15 156p; 38pin .15 156p; 40pin .15 156p.

FERRIC CHLORIDE: 1lb bag Anhydrous 95p + 35p P&P

DALGETT RESIST P&P: + spare trip 78p

COPPER CLAD BOARDS: Fibre Single-sided 9RP; Glass sided 5RP; 8" x 6" 75p; 8" x 12" 130p; Double-sided 8RP; 9.5" x 8.5" 80p.

SOLDERING PENS: 100 50p; 500 200p; 14pin 35p; 16pin 39p.

DIL SOCKETS (TAXES) Low Wire Prof. Wasp: 8pin 10p; 12pin 15p; 14pin 15p; 16pin 15p; 18pin 15p; 20pin 22p; 22pin 25p; 24pin 30p; 26pin 35p; 28pin 35p; 30pin 105p; 40pin 50p 109p.

EDGE CONNECTORS: 2-Dial type: 10pin .1 156p; 12pin .15 156p; 14pin .15 156p; 16pin .15 156p; 18pin .15 156p; 20pin .15 156p; 22pin .15 156p; 24pin .15 156p; 26pin .15 156p; 28pin .15 156p; 30pin .15 156p; 32pin .15 156p; 34pin .15 156p; 36pin .15 156p; 38pin .15 156p; 40pin .15 156p.

FERRIC CHLORIDE: 1lb bag Anhydrous 95p + 35p P&P

DALGETT RESIST P&P: + spare trip 78p

COPPER CLAD BOARDS: Fibre Single-sided 9RP; Glass sided 5RP; 8" x 6" 75p; 8" x 12" 130p; Double-sided 8RP; 9.5" x 8.5" 80p.

SOLDERING PENS: 100 50p; 500 200p; 14pin 35p; 16pin 39p.

TRANSISTORS

AC125	35	BC214L	10	BFR81	24	TIP31A	38	2N1671B	120
AC126	25	BC307B	12	BFR88	105	TIP31C	43	2N2160	350
AC127	22	BC308	12	BFX81	46	TIP32A	58	2N2171	43
AC128	20	BC327	12	BFX84	28	TIP32C	58	2N218A	34
AC129	27	BC328	12	BFX85	28	TIP33C	70	2N219A	22
AC142	28	BC338	12	BFX87	28	TIP34	85	2N220A	23
AC176	25	BC441	27	BFY50	21	TIP34C	82	2N221A	23
AC177	60	BC461	27	BFY51	21	TIP35A	135	2N222A	20
AC178	60	BC467	27	BFY52	21	TIP35C	165	2N223A	23
AC198	60	BC477	35	BFY53	25	TIP36A	145	2N224A	20
AC200	60	BC516	38	BFY54	20	TIP36C	185	2N225A	23
AC211	60	BC517	10	BFY64	40	TIP41A	105	2N226A	20
AC221	40	BC547	40	BFY71	40	TIP41B	55	2N227A	23
AC222	60	BC548	10	BRY39	39	TIP42A	64	2N228A	25
AC228	60	BC549C	15	BSK20	20	TIP42B	82	2N270A	55
AC239	90	BC556	15	BSK26	15	TIP120	72	2N2905A	22
AC241	39	BC557	10	BSV95A	18	TIP121	70	2N2906	22
AD149	75	BC558	10	BU105	115	TIP142	125	2N2907	22
AD161	42	BC559	57	BU205	125	TIP147	145	2N2907	22
AD162	42	BCY30	80	BU208	215	TIP2955	60	2N2926G	10
AF114	60	BCY39	78	E421	75	TIP3055	48	2N3011	24
AF115	60	BCY40	48	MD9001	179	TIS43	43	2N3053	18
AF116	60	BCY41	14	MJ481	65	TIS44	45	2N3054	65
AF117	60	BCY70	14	MJ2955	105	TIS45	45	2N3055	45
AF118	75	BCY71	16	MJ2956	104	TIS46	45	2N3056	45
AF139	40	BCY72	25	MJE370	58	TIS88	35	2N3442	10
AF178	75	BC124	115	MJE371	54	TIS90	20	2N3663	14
AF186	50	BD031	42	MJE520	75	TIS91	24	2N3702	10
AF187	50	BD032	42	MJE521	74	ZTX107	11	2N3704	10
AG221	60	BD133	50	MJE2955	90	ZTX108	11	2N3705	10
BC107	10	BD135	30	MJE3065	70	ZTX109	11	2N3706	10
BC107B	10	BD136	30	MPP102	66	ZTX300	13	2N3707	10
BC108	10	BD137	30	MPP103	36	ZTX301	16	2N3708	11
BC108B	10	BD138	35	MPP104	36	ZTX302	20	2N3709	11
BC109	10	BD140	30	MPP105	36	ZTX303	17	2N3710	10
BC109B	12	BD144	188	MPSA05	15	ZTX304	24	2N3711	10
BC109C	12	BD145	175	MPSA06	16	ZTX314	24	2N3712	10
BC114	20	BD205	110	MPSA12	22	ZTX326	45	2N3772	185
BC115	60	BD245	70	MPSA12	22	ZTX341	20	2N3773	255
BC117	60	BD246	82	MPSA56	22	ZTX500	15	2N3819	40
BC119	28	BD434	70	MPSU02	58	ZTX502	17	2N3820	20
BC140	28	BD517	85	MPSU05	50	ZTX503	15	2N3823	70
BC142	26	BD695A	85	MPSU06	50	ZTX504	25	2N3836	90
BC143	26	BD696A	85	MPSU07	50	ZTX505	25	2N3837	90
BC147	9	BF115	25	MPSU08	50	ZTX506	25	2N3838	90
BC148	8	BF116	25	MPSU09	50	ZTX507	25	2N3839	90
BC148B	10	BF158	25	MPSU10	50	ZTX508	25	2N3840	90
BC149	9	BF173	25	MPSU11	50	ZTX509	25	2N3841	90
BC149C	9	BF177	25	MPSU12	50	ZTX510	25	2N3842	90
BC153	24	BF178	30	MPSU13	50	ZTX511	25	2N3843	90
BC154	13	BF179	38	MPSU14	50	ZTX512	25	2N3844	90
BC157	10	BF180	20	MPSU15	50	ZTX513	25	2N3845	90
BC158	10	BF194	11	MPSU16	50	ZTX514	25	2N3846	90
BC159	11	BF195	12	MPSU17	50	ZTX515	25	2N3847	90
BC160	28	BF196	12	MPSU18	50	ZTX516	25	2N3848	90
BC161	28	BF197	12	MPSU19	50	ZTX517	25	2N3849	90
BC161A	28	BF198	12	MPSU20	50	ZTX518	25	2N3850	90
BC161B	28	BF199	12	MPSU21	50	ZTX519	25	2N3851	90
BC161C	28	BF200	12	MPSU22	50	ZTX520	25	2N3852	90
BC161D	28	BF201	12	MPSU23	50	ZTX521	25	2N3853	90
BC161E	28	BF202	12	MPSU24	50	ZTX522	25	2N3854	90
BC161F	28	BF203	12	MPSU25	50	ZTX523	25	2N3855	90
BC161G	28	BF204	12	MPSU26	50	ZTX524	25	2N3856	90
BC161H	28	BF205	12	MPSU27	50	ZTX525	25	2N3857	90
BC161I	28	BF206	12	MPSU28	50	ZTX526	25	2N3858	90
BC161J	28	BF207	12	MPSU29	50	ZTX527	25	2N3859	90
BC161K	28	BF208	12	MPSU30	50	ZTX528	25	2N3860	90
BC161L	28	BF209	12	MPSU31	50	ZTX529	25	2N3861	90
BC161M	28	BF210	12	MPSU32	50	ZTX530	25	2N3862	90
BC161N	28	BF211	12	MPSU33	50	ZTX531	25	2N3863	90
BC161O	28	BF212	12	MPSU34	50	ZTX532	25	2N3864	90
BC161P	28	BF213	12	MPSU35	50	ZTX533	25	2N3865	90
BC161Q	28	BF214	12	MPSU36	50	ZTX534	25	2N3866	90
BC161R	28	BF215	12	MPSU37	50	ZTX535	25	2N3867	90
BC161S	28	BF216	12	MPSU38	50	ZTX536	25	2N3868	90
BC161T	28	BF217	12	MPSU39	50	ZTX537	25	2N3869	90
BC161U	28	BF218	12	MPSU40	50	ZTX538	25	2N3870	90
BC161V	28	BF219	12	MPSU41	50	ZTX539	25	2N3871	

WATFORD ELECTRONICS

THE DIGITAL FREQUENCY METER with a Difference



- 0-150MHz in 5 ranges.
- Large 8-digit display for high accuracy
- Period and time interval facility.
- Unit counter up to 99,999,999
- 10MHz crystal timebase
- Hold and reset buttons plus built-in PSU.

All these features and more for less than half the price of an ordinary frequency meter. The DFM2000 has all its components including the displays, switches and transformer mounted on one double sided PC board. Assembly is simplicity itself especially since interwiring has been eliminated. This is a high quality design and will make a truly professional digital frequency meter that any constructor will be proud to own.

Price: Only **£64.50** Kit (P&P 65p).
Probes: Optional extra **£8.75**

OHIO SUPERBOARD II
Only **£188.00**

Superboard II is supplied fully assembled and tested to British TV specification. Also included at no extra cost 4 manuals and a Cassette with programmes. Requires +5V or +3A and a Video Monitor or TV with RF converter to be up and running. (Data sheet supplied). We can also supply the RF Converter and Power Supply in Kit form or ready-built.

8K Microsoft BASIC in ROM. 4K Static RAM — on BOAPD expandable to 8K. Full 53 Key Keyboard with Upper Lower Case & User programmability and a lot more. See it for yourself. Continuous demonstration on at our retail shop.

Power Supply Kit (5V/3A) incl. RF Converter **£21.50**
Ready-built & Tested **£28.50**
Extra 4K of RAM **£35.00**
Specialty Designed Case **£25.00**
810 Expansion Board with 8K RAM **£188**
Assembler Editor plus Manual **£25**
Extended Monitor plus Manual **£10**
Basic Tutor Tapes **£27**

SWITCHES	SLIDE 250V:
TOGGLE: 2A, 250V 14p	1A DPDT 14p
SPST 25p	1A DPDT c/over 15p
DPST 34p	1/2A DPDT 13p
DPDT 38p	4 pole 2-way 24p
4 pole on/off 54p	
SUB-MIN TOGGLE	PUSH BUTTON
SP chopper 60p	Spring loaded 60p
SPST on/off 54p	SPST on/off 60p
SPST biased 85p	SPDT c/over 85p
DPDT 6 tags 70p	DPDT 6 Tag 85p
DPDT centre off 79p	
DPDT Biased 115p	

ROTARY: Make your own multiway Switch. Adjustable Stop Shafting Assembly Accommodate up to 6 Wafers **75p**
Mains Switch DPST to fit **34p**
Break Before Make Wafers. 1 pole/12 way. 2p/6 way. 3p/4 way. 4p/3 way. 6p/2 way. **47p**
Spacer and Screen **5p**
ROTARY: (Adjustable Stop)
1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way **41p**
ROTARY: Mains 250V AC. 4 Amp **45p**

CRYSTALS

100kHz	323
455kHz	383
1MHz	323
1.036M	385
1.28MHz	382
1.6MHz	323
1.8MHz	323
1.6432MHz	382
2.4576MHz	382
3.2768M	323
3.57954M	195
4.000MHz	290
4.032MHz	323
4.433619M	135
5.0MHz	323
5.185M	323
6.9536M	200
7.680M	323
8.86723M	323
9.375M	323
10.0MHz	323
10.7MHz	323
12MHz	382
14.3181MHz	300
18MHz	323
17.432M	323
20.0MHz	323
27.648M	323
48.0MHz	323
100.000MHz	323

TRANSFORMERS (Mains Prim. 220-240V)

6-0-6V. 9-0-9V. 12-0-12V 100mA	95p
3VA: 0-6V-0.6V (PCB mounting)	150p
8VA: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A	195p
12V: 4.5V-1.3A 4.5V-1.3A; 6V-1.2A 6V-1.2A; 12V-5A 12V-5A; 15V-4A 15V-4A; 20V-3A 20V-3A	220p (20p p&p)
24VA: 6V-1.5A 6V-1.5A; 9V-1.3A 9V-1.3A; 12V-1A 12V-1A; 15V-8A 15V-8A; 20V-6A 20V-6A	290p (45p p&p)
50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-8A 30V-8A	350p (50p p&p)
100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A	850p (60p p&p). (N.B. p&p charge to be added above our normal postal charge.)

ALUM. BOXES WITH LID

3x2x1" 54
2x4x5x1 1/2" 72
4x4x1 1/2" 70
4x2x4x1 1/2" 70
4x5x4x1 1/2" 88
4x2 1/2x2" 72
5x4x2" 98
6x4x2" 108
7x5x2 1/2" 145
8x6x3" 185
10x7x3" 210
10x4 1/2x3" 175
12x5x3" 215
12x8x3" 255

PANEL METERS

FSD	60x46x
	35mm
	0-50µA
	0-100µA
	0-500µA
	0-1mA
	0-5mA
	0-10mA
	0-50mA
	0-100mA
	0-500mA
	0-1A
	0-2A
	0-25V
	0-50V AC
	0-300V AC
"VU"	445p each

ETI Projects:

Parts available for: Click	
Eliminator	
DFM2000	
Frequency Meter	
DM900, Audiophile Amp, 60W Amplifier	
System. Send SAE plus 5p for list.	

VOLTAGE REGULATORS

1A TO3 +ve -ve	
5V 7805 145p	7905 220p
12V 7812 145p	7912 220p
15V 7815 145p	
18V 7818 145p	
1A TO220 Plastic Casing	
5V 7805 65p	7905 75p
12V 7812 65p	7912 75p
15V 7815 65p	7915 75p
18V 7818 65p	7918 75p
24V 7824 65p	
100mA TO92 Plastic Casing	
5V 78L05 30p	79L05 65p
6V 78L62 30p	
8V 78L82 30p	
12V 78L12 30p	79L12 65p
15V 78L15 30p	79L15 65p
LM300H 170p	LM327 270p
LM305H 140p	LM723 38p
LM309K 135p	TA8550 50p
LM317K 360p	TBA425B 95p
LM231K 550p	TDA1412 150p
LM325N 240p	78H05 +5/-5A 55p
LM326N 240p	78H6 +5 to +24 65p

OPTO ELECTRONICS

LEDs with Clips	13
TIL108 Red	17
TIL211 Grn.	17
TIL212 Yel.	18
TIL220 2" Red	14
2" Green, Yellow or Amber	18
Square LEDs, Red, Grn., Yel.	36
TIL32 Infra Red	58
TIL78	7
LS400	255
OCF71	120
ORP12	63
ORP61	85
2N5777	45
ISOLATORS	
IL74	48
TIL111/2	85
TIL114	95
TIL117	110
7 Segment Displays	
TIL307	675
TIL312 3" CA	105
TIL313 3" CC	105
TIL321 5" CA	115
TIL322 5" CC	115
DL704 3" CC	99
DL707 3" CA	99
DL747 3" CA	180
FD357 Red	180
3" Green CA	180
6" Green CA	225
LCD 3 1/2 Digit	875
LCD 4 Digit	975

326	284	4010	38	4048	58	4099	145	4516	120	4549	375
327	288	4011	28	4049	48	4180	109	4517	382	4553	398
347	148	4012	18	4050	48	4181	109	4518	102	4554	150
348	186	4013	42	4051	72	4182	109	4519	55	4555	65
352	228	4014	80	4052	73	4183	109	4520	108	4556	72
353	228	4015	82	4053	72	4174	110	4521	228	4557	451
365	65	4016	45	4054	110	4175	99	4522	149	4558	105
366	65	4017	82	4055	128	4194	108	4526	149	4559	375
367	65	4018	87	4056	135	4408	720	4527	162	4560	210
368	66	4019	38	4057	1650	4409	720	4528	99	4561	65
373	180	4020	99	4059	480	4410	720	4529	145	4562	533
374	180	4021	95	4060	115	4411	958	4530	85	4566	165
375	160	4022	85	4061	1200	4412F	1250	4531	135	4569	280
377	212	4023	22	4062	92	4412V	1050	4532	115	4572	26
378	184	4024	66	4063	110	4435	65	4534	675	4580	585
379	215	4025	19	4066	58	4415V	500	4536	365	4581	297
384	86	4026	180	4067	380	4419	280	4538	142	4582	130
390	230	4027	45	4068	22	4422	545	4539	105	4583	75
393	380	4028	81	4069	20	4433	895	4541	135	4584	63
395	218	4029	66	4070	32	4435	825	4543	155	4585	105
396	215	4030	58	4071	21	4440	1275				
398	276	4031	205	4072	21	4450	295				
399	230	4032	100	4073	21	4451	295				
445	150	4033	145	4075	23	4452					
447	144	4034	199	4076	85	4490F	695				
490	180	4035	111	4077	40	4490V	525				
668	182	4036	335	4078	21	4501	19				
669	182	4037	100	4081	20	4502	20				
670	248	4038	108	4082	21	4503	69				
		4039	320	4085	74	4506	51				
		4040	105	4086	52	4507	55				
		4041	85	4087	40	4508	25				
		4042	15	4093	150	4508	297				
		4043	94	4094	78	4510	99				
		4044	95	4095	105	4512	98				
		4045	145	4096	105	4513	208				
		4046	128	4097	372	4515	285				
		4047	87	4098	110	4515	298				

Direct Meter

Zycomm's combined VSWR and power meter offers direct reading of both functions without interpolation.

Autorangeing for power output covers 20 W to 2 kW in three ranges. VSWR can be measured from 1:1 to infinity.


Separate sensing heads, supplied to cover each frequency range, can be connected at any position in the feed line. Forward and reverse power can be displayed as either peak or rms

readings.

The electronic comparator included in the meter allows constant readout of VSWR regardless of power variation. It gives a true indication during speech on SSB.

You'll need a 240 V 50 Hz supply to operate the meter.

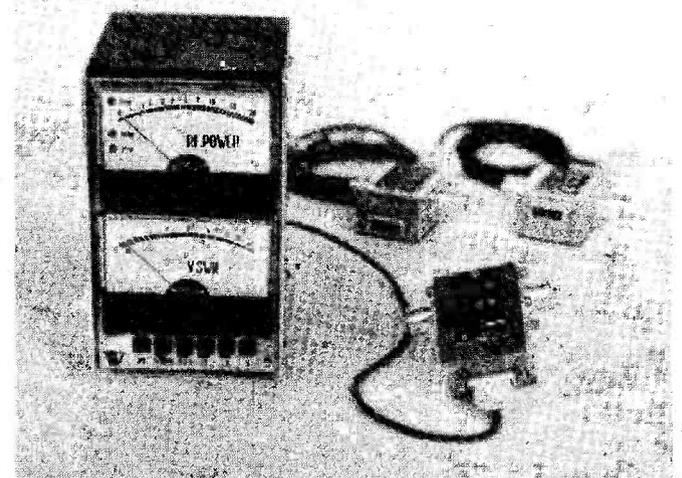The combined VSWR and power meter is available from ZycommElectronics Ltd, 47-51 Pentrich Road, Ripley, Derbyshire DE5 3DS.



End of Chess

If you saw our survey of Chess Machines in December, you will have gathered that the idea is to play a game from start to finish against the computer. The latest chess machine is a little different in that it only plays end games.

C/E, S (score), P (peek?) and R (response). On top of all that there is a four digit LCD display.

With the mini mind you get seven booklets, each containing fifty different problems. More booklets will be printed to catch up with the Chess Master's memory of several thousand problems. Each booklet represents a different level of play.

It's a mini machine, measuring only 105 x 63 x 8 mm — not much bigger than a credit card calculator. It looks a bit like a calculator, too. On the front panel there are eight buttons numbered one to eight (for listing moves) and five instruction buttons — E (to enter move),

Li and Fung Trading are making a thousand Chess Masters everyday in Hong Kong. More on the mini mind when we can get one to play with.

Vee Needen Sie

With a bit of luck we will once again be amazed, astounded and generally boggled by the versatility of ETI readers. This time, we'd like to hear from anyone who can translate technical German (ideally Dutch, too) into English for us.

the odd page of unpronounceable tutonic text and turning it into the equally odd page of English, why not drop us a line or two or three.

We could employ the services of professional agencies in the field, but we'd prefer to get an ETI reader in on the act. So, if you think you're up to taking

Although we moved offices a few months ago, a lot of our mail is still being sent to our old address, so make sure you send the account of your terrific translational talents to us at 145 Charing Cross Road, WC2 (full address on the contents page.)

Great 1980 Sale

SUPER SOUND SAVING! DINDY LOW NOISE CASSETTES

SJ30	10 C30	15 min per side	£2.00
SJ35	10 C46	23 min per side (LP)	£2.50
SJ31	10 C90	45 min per side	£3.50
SJ32	10 C120	40 min per side	£4.50

ALL REDUCED! CAPACITOR PAKS

16201	18 electrolytics	4.7u-10u	£4.36
16202	18 electrolytics	10u-100u	£4.36
16203	18 electrolytics	100u-880u	£4.36
ALL 3 at SPECIAL PRICE of £1.30			
16160	24 ceramic caps	22p-82p	£1.74
16161	24 ceramic caps	100p-390p	£1.74
16162	24 ceramic caps	470p-3300p	£1.74
16163	24 ceramic caps	4700p-0.047p	£1.74
ALL 4 at SPECIAL PRICE of £1.80			

RESISTOR PAKS

16213	60 1/2w resistors	100ohm-B20ohm	£1.50
16214	60 1/2w resistors	1K-8.2K	£1.50
16215	60 1/2w resistors	100K-820K	£1.50
16216	60 1/2w resistors	100K-820K	£1.50
ALL 4 at SPECIAL PRICE of £1.50			
16217	40 1/2w resistors	100ohm-B20ohm	£1.80
16218	40 1/2w resistors	1K-8.2K	£1.80
16219	40 1/2w resistors	10K-82K	£1.80
16220	40 1/2w resistors	100K-820K	£1.80
ALL 4 at SPECIAL PRICE of £1.80			

IC SOCKET PAKS

SJ36	14	8 pin	2N3819	£0.17
SJ37	12	14 pin	2N5458	£0.18
SJ38	11	16 pin	2N4220	£0.28
SJ39	8	18 pin	2N4860	£0.25
SJ40	7	20 pin		
SJ41	6	24 pin		
SJ42	5	24 pin		
SJ43	4	28 pin		
SJ44	3	40 pin		
All at ONLY £1.00 EACH				

F.E.T.s

2N3819	£0.17
2N5458	£0.18
2N4220	£0.28
2N4860	£0.25
(PROGRAMMABLE UNIJUNCTION)	
2N6027	£0.25
BRV56	£0.25

VOLTAGE REGULATIONS

Positive	Case TO220	Negative	
UA7805	£0.65	UA7905	£0.70
UA7812	£0.65	UA7912	£0.70
UA7815	£0.65	UA7915	£0.70
UA7818	£0.65	UA7918	£0.70
UA7824	£0.65	UA7924	£0.70
UA723 14 pin DIL	£0.35		
LM309K T03	£1.10		

OPTOELECTRONICS

1510	707 LED display	Price each	£0.70
1511	747 LED Display	Price each	£1.50
1512	727 LED Display	Price each (dual)	£1.55

L.E.D.s

		Price each
SJ78	125 LED Diffused	RED £0.08
SJ79	2 LED Diffused	RED £0.08
SJ120	125 LED Bright	RED £0.09
SJ121	2 LED Bright	RED £0.09
1502	125 LED Diffused	GREEN £0.11
1505	2 LED Diffused	GREEN £0.11
1503	125 LED Diffused	YELLOW £0.11
1506	2 LED Diffused	YELLOW £0.11
SJ80	2 LED Bright	YELLOW £0.14
SJ82	2 LED Clear illuminating	RED £0.10
SJ83	125 LED Clear illuminating	RED £0.10

2nd QUALITY L.E.D. PAKS

1507	10 assorted colours & size	£0.65
S122	10 .125 RED	£0.50
S123	10 .2 RED	£0.50

L.E.D. CLIPS

1508/125	.125	5 for £0.10
1508/2	.2	5 for £0.12

SJ81	1 Infra RED emitter - Fairchild FP100	£0.25
SJ98	5 Photo Detector MEL11 + Data	£1.00
ORP12	NORP12 Cad Cell	£0.45
SJ99	4 ITT 5870 ST Nikia Tubes	£1.00
SJ29	Mexas NPN silicon transistors 2S503=BC108 TO-18 metal can - perfect & coded	50 off £2.50 - 100 off £4.00 - 1,000 off £35.00

SPECIAL OFFER

SJ100 12v Electric Drill 7,500 RPM for all your PCB drilling complete with 2 drills .1 & .15 **£5.50**

SUPER DUPER COMPONENT BOX

Min. 3 lbs in weight consisting of a fantastic assortment of Electronic Components - Pots, Resistors, Condensers, Switches, Relays, Board-Semiconductors, wire, hardware, etc. etc. etc.
"This is a large box and is sent separate to your order"
\$140 £2.50 including p&p

CALCULATOR CHIP

GOM2-C500	24 pin MOS	£0.50
-----------	------------	-------

IC INSERTION/EXTRACTION TOOL

2015		£0.35 each
------	--	------------

BI-KITS AUDIOMODULES AT PRE-INCREASE PRICES!

AMPLIFIERS

AL10	3 watt Audio Amplifier Module 22-32v supply	£2.87
AL20	5 watt Audio Amplifier Module 22-32v supply	£3.74
AL30A	7-10 watt Audio Amplifier Module 22-32v supply	£4.36
AL60	15-25 watt Audio Amplifier Module 30-50v supply	£5.39
AL80	35 watt Audio Amplifier Module 40-60v supply	£8.44
AL120	50 watt Audio Amplifier Module 50-70v supply	£13.74
AL250	125 watt Audio Amplifier Module 50-80v supply	£20.49

STEREO PRE-AMPLIFIER

PA12	Supply voltage 22-32 volts input sensitivity 300mv suit: AL10/AL20/AL30	£7.78
PA100	Supply voltage 24-35 volts inputs. Tape, Tuner, Mag P.U., suit: AL60/AL80	£16.05
PS200	Supply voltage 35-70 volts inputs. Tape, Tuner, Mag P.U., suit: AL30/AL120/AL250	£16.59

MONO PRE-AMPLIFIERS

MM100	Supply voltage 40-65 volts inputs: Mag, P.U., Microphone, Max. output 500mv	£11.30
MM100G	Supply voltage 40-65 volts inputs: 2 Guitars, Microphones, Max. output 500mv	£11.30

POWER SUPPLIES

PS12	24v Supply suit 2 x AL10, 2 x AL20, 2 x AL30 & FA12/450	£1.80
SPM80	-33v Stabilised supply - suit 2 x AL60, PA100 to 15 watts	£4.40
SPM120/45	45v Stabilised supply - suit 2 x AL60, PA100 to 25 watts	£5.80
SPM120/55	55v Stabilised supply - suit 2 x AL80, PA200	£5.80
SPM120/65	65v Stabilised supply - suit 2 x AL120, PA200, 1 x AL250, PA200	£5.80
SG30	15-0-15 Stabilised power supply for 2 x GE100MK11	£3.80

MISCELLANEOUS

MPA30	Stereo Magnetic Cartridge Pre-Amplifier - input 3.5mv Output 100mv	£2.98
S.450	Stereo FM Tuner supply voltage 20-30v - Variable tuned	£23.24
STEREO 30	Complete 7 watt per Channel Stereo Amplifier Board - includes amps, pre-amp, power supply, front panel, knobs etc - requires 2050 Transformer	£19.18
RP124	5 watt 12 volt max. - Siren Alarm Module	£3.50
GE100MK11	10 channel mono-graphic equaliser complete with sliders and knobs	£23.00
VPS30	Variable regulated stabilised power supply 2-30 volts 0.2 amps	£7.60
PS250	Consists - 1 capacitor & 4 diodes for constructing unregulated power supply for AL250 to 125 watts	£3.78

TRANSFORMERS

2034	1.7 amp 35v suit SPM80	£5.40
2035	2 amp 55v	£5.35
2036	750mA 17v suit PS12	£3.20
2040	1.5 amp 0-45v-55v suit SPM120/45, SPM120/55v	£5.20
2041	2 amp 0-55v-65v suit SPM120/55, SPM120/65v	£5.80
2050	1 amp 0-20v suit Stereo 30	£3.25
1725	150mA 15-0-15v suit SG30	£1.77

ACCESSORIES

139	Teak Cabinet suit Stereo 30, 320 x 235 x 81mm	£5.45
140	Teak Cabinet suit STA15 425 x 290 x 95mm	£7.50
FP100	Front Panel for PA100 & PA200	£1.80
BP100	Back Panel for PA100 & PA200	£1.60
GE100FP	Front Panel for one GE100MK11	£1.75
2240	Kit of parts including Teak Cabinet, chassis, sockets, knobs to build 15 watt stereo amplifier	£19.95

DIODES

Type	Price	Type	Price	Type	Price
AA119	£0.06	QA70	£0.06	IN4004	£0.09
BA100	£0.08	QA79	£0.08	IN4005	£0.07
BA148	£0.13	QA81	£0.08	IN4006	£0.08
BA173	£0.13	QA90	£0.08	IN4007	£0.09
BAX13	£0.05	QA91	£0.08	IN5400	£0.12
BAX16	£0.06	QA95	£0.08	IN5401	£0.13
QA200	£0.06	IN34	£0.06	IN5402	£0.14
QA202	£0.07	IN80	£0.07	IN5404	£0.15
9Y100	£0.18	IN4148	£0.05	IN5406	£0.19
BY126	£0.12	IN4001	£0.04	IN5407	£0.23
BY127	£0.14	IN4002	£0.04	IN5408	£0.28
QA47	£0.06	IN4003	£0.05	IS44	£0.03

LINEAR

Type	Price	Type	Price	Type	Price
CA270	£0.95	SL413A	£1.75	T8A810	£0.85
CA3089	£1.70	SN76013N	£1.65	T8A820	£0.65
CA3090	£3.00	SN76023N	£1.60	uA703	£0.20
LM380	£0.80	SN76115	£1.60	uA709C	£0.25
LM381	£1.35	TAA550	£0.30	uA710	£0.25
LM3900	£0.50	TAA521A	£1.80	uA711	£0.26
MC1310P	£0.85	TBA120B	£0.60	741P	£0.16
NE555	£0.18	TBA641A	£1.10	TAA661	£1.25
NE556	£0.55	TBA800	£0.75	TAA661B	£1.25

SPECIAL OFFER

COMPONENT PAKS

O/N/O	Quantity		E p
SJ1	200	Resistors mixed values	£0.50
SJ2	200	Carbon resistors 1/2 watt preformed	£0.50
SJ3	100	1/2 watt resistors mixed values	£0.50
SJ4	60	1/2 watt resistors mixed values	£0.50
SJ5	50	1-2 watt resistors mixed pot values	£0.50
SJ6	50	Precision resistors 1-2% tol. mixed	£0.50
SJ7	30	5-10 watt wirewound resistors mixed	£0.50
SJ11	150	Capacitors mixed types & values	£0.50
SJ12	60	Electrolytics all sorts mixed	£0.50
SJ13	50	Polyester / polystyrene capacitors mixed	£0.50
SJ14	50	C280 type capacitors mixed	£1.00
SJ15	40	High quality electrolytics 100-470mf	£1.00
SJ16	40	Low volts electrolytics mixed up to 10v	£0.50
SJ17	20	Electrolytics transistor types mixed	£0.50
SJ18	20	Tantalum bead capacitors mixed	£0.50
SJ20	2	Large croc clips 25A rated	£0.30
SJ21	Large 7 1/2" Mains Neon Tester	screwdriver	£0.85
SJ22	Small pocket size 'Mains Neon Tester'		£0.85
SJ23	Siemens 220V AC Relay DPDT contacts 10amp rating - housed in plastic case		£1.00
SJ24	Black PVC tape (1/4) 15mm x 25m - 1 strong tape for electrical & household use	0.35 roll 1.50 5 rolls	
SJ25	100 Silicon NPN transistors all perfect & coded - mixed types with data & equivalent sheet		2.50
SJ26	100 Silicon PNP transistors all perfect & coded - mixed types with data & equivalent sheet		2.50
SJ27	50 Assorted pieces of SCR's diodes & rectifiers incl. stud types all perfect - no rejects fully coded - data incl.		2.50
SJ28	20 TTL 74 series gates - assorted 7401 - 7460		1.00
SJ33	PC Board - mixed bundle PCB fibreglass paper single & double sided - super value		2.50
SJ34	200 sq. ins. (approx) copper clad paper board		£0.80
SJ37	100 sq. ins. (approx) copper clad fibre glass		£0.80
SJ47	8 Dual ganged carbon pots log & lin mixed values		1.00
SJ50	20 Assorted slider knobs - chrome/black		1.00
SJ51	1 Switchbank 5 way incl. push knobs		1.00
SJ52	1 Pak of vero board approx 50 sq. ins mixed		1.00
SJ53	1 Mammoth IC Pack: approx 200 200pcs assorted fall-out integrated circuits including logic 74 series, linear-audio and DTL many coded devices but some unmarked - you to identify		1.00
SJ54	20 Slider pots mixed values & sizes		1.00
SJ56	1 100K lin 40mm slider pots		£0.50
SJ57	1 100K log 40mm slider pots		£0.50
SJ58	6 1K lin 40mm slider pots		£0.50
SJ59	6 5K lin 40mm slider pots		£0.50
SJ60	4 5K log 50mm single		£0.50
SJ61	4 100K log 50mm single		£0.50
SJ62	5 15mm chroma knobs standard push fit		£0.50
SJ63	1 Instrument knob - black winged (29x20mm) with pointer 1/4" standard screw fit		£0.15
SJ64	1 Instrument knob - black/silver aluminium top (17x15mm) 1/4" standard screw fit		£0.12
A56	DUAL SLIDER POTS: 45mm travel		
SJ65	10K log	0.25 each	
SJ66	100K lin	0.25 each	
SJ67	Chrome slider knobs to fit	0.10 each	
SJ68	30 ZTX300 type transistor NPN pre-formed for P/c Board - colour coded blue - all perfect		1.00
SJ69	30 ZTX500 type transistor PNP pre-formed for P/c Board colour coded white - all perfect		1.00
SJ70	25 BC107 NPN to 106 case perfect transistors code C1359		1.00
SJ71	25 BC177 NPN TO106 case perfect transistors code C1395		1.00
SJ72	4 ZN3055 silicon power NPN transistors T03		1.00
SJ73	6 T064 SCR's 5 amp assorted 50v-400v all coded		1.00
SJ74	8 Way ribbon cable - colour coded individually PVC insulated solid lined copper conduction	0.2 meter	
SJ75	FM coax cable - plain copper conduction cellular polythene insulated and plain copper braided PVC sheath - impedance 75 ohms	0.10 meter	
SJ7			

CALCULATORS

SCIENTIFIC

***SPECIAL OFFER**
TEXAS T159 together with PC100C
(Complete as manufacturer's specifications)
£285.00

TEXAS/HP Accessories available

*TEXAS T159 (Card prog 960 prog steps of 100 mem)	£156.50
*TEXAS T158 (Key prog 480 steps of 60 mem)	£60.00
*TEXAS PC100C (Printing Unit for T158/159)	£140.00
*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes / 50 Prog Steps)	£25.00

For your Texas T158/59 Calculator

ELECTRICAL ENG MODULE

Ideal for design / systems and engineering technical assistants.
Module now available. POA.

*TEXAS T145 (New updated version of the Texas T140)	£19.00
*TEXAS TI PROGRAMMER (Hexadecimal Oct)	£46.50
*TEXAS T151/iii (10 mem 32 Prog Steps Stat / Sci)	£26.30
TEXAS T150 LCD (Sci / Stat. 2 Con Mem)	£23.00
TEXAS T125 LCD (Sci / Stats)	£18.50
TEXAS T53 (Sci. 32 Prog Steps-Coa Mem + 80 Prog List Applications book)	£25.00

Make more of your Texas T158/59 Calculator MATH/UTILITIES MODULE

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

Module includes:

Prompter. Alpha Messages. Printer Formatting. Superplotter. Sorting. Data Arrays. Data Packing. Prime Factors. Hyperbolic Functions. Gamma / Factorial. Random Numbers. Normal Distribution. Interpolation. Roots of a Function. Minimax. Romberg Integration. Differential Equations. Discrete Fourier Series. Calculator Status. Variable Arithmetic. Module Check.

*TEXAS T158 with Maths/Utilities	£90.00
*TEXAS T159 with Maths/Utilities	£186.50
*TEXAS T158 with Applied Statistics	£80.00
*TEXAS T159 with PC100C & Applied Statistics	£305.00

WINTER SALE

*TEXAS T159 Calculator (complete as manufacturer's spec. master module, charger, etc.). PLUS statistics module and extra set of 40 Blank Prog. Cards with wallet, etc.
ONLY £180

NEW TEXAS T158C*

*Continuous program facility on all 480 Program steps/60 mem even when calculator switched off	£79.50
*TEXAS T158C (complete plus Applied Stats. Module)	£98.00
*TEXAS T158C + PC100C	£208.00

*CBM9190R (9 mem Sci. / Stat)	£27.50
*CBM Pro 100 (72 Step Prog)	£29.50
*HP33E (8 mem. Pro Sci / Sta)	£49.00
*HP22E (Advanced Sci with Statistics)	£37.50
*HP31E (New Sci replaces HP21)	£25.50
*HP67A (C Prog 224 Steps 26 Mem)	£188.70
*HP97A (Fully prog with Printer)	£384.35
HP41C (the newest calculator from HP)	POA
CASIO AQ2000 Cal. (3-Way Stopwatch / Alarm plus Date Calendar)	£23.00
CASIO FX510 (10dig Sci / Stat)	£20.00
CASIO FX8000 (as above + Stop Watch / Alarm)	£27.73
CASIO FX501P (Sci. LCD Prog. 128 Steps. 11 Mem)	£47.50
CASIO FX502P (Sci LCD Prog 256 Steps. 22 Mem)	£65.00
CASIO Prog Adaptor — permits Progs to be recorded on to standard cassette recorders for replay on Casio FX501P / Ex502P at later stage	POA

LEXICON LANGUAGE TRANSLATOR

(With 6 Lang. Module — French / Italian / German / Spanish etc) **£128.70**

OHIO SCIENTIFIC'S SUPERBOARD II **£188.00**

BORRIS the most advanced chess computer yet. Borris is ideal for the learning and improving your chess game from beginner to master. Borris can play against himself, has Alpha-Numeric prompting to help improve play and by simple switching you have facility to follow Borris's thinking while he analyses position before making a move. Walnut case, wooden chessmen, board mains, adaptor, etc

CHESS CHALLENGER "10" (10 Levels of beginner to master)	£147.75
CHESS CHALLENGER "7" (7 Levels of game)	£78.50
CHESS CHALLENGER "VOICE" (10 Levels — beginner to Master Plus) The strongest Prog yet in this series — twice as fast as the other challengers. A microprocessor with 128,000 to 160,000 bits of read only Mem. Over 8000 bits of Random Access Mem. Teaches opening & end game solutions. Plays against itself. Solves book problems etc — and in addition IT SPEAKS. Complete with Deluxe playboard, hand carved men with magnetised base plus Deluxe carry case.	POA
COMMODORE "CHESSMATE" (8 levels — 32 International openings — ideal game for learning)	£50.00

CHALLENGER "BRIDGE" (Advanced double computer — teacher / beginner to Master)
Can play 1/2, 3 or even 4 hands — rejects illegal bids etc.
Deluxe hardwood housing / Deluxe carry-case **£239.00**

FREE — mains / Charger included

GOODS FULLY GUARANTEED PRICES EXCLUDE VAT
(ADD 15%) BUT INC. P&P CHEQUE WITH ORDER

Company / Hospital and Government orders accepted by phone

Barclaycard / Visa / Access accepted by phone

TEL. 01-455 9823

EXPORT ORDERS WELCOMED

Air Freight / Air Post Delivery
Quotations on request

MOUNTAINDENE

22 Cowper St., London, EC2

Greenweld 1980

We've just received our copy of Greenweld's 1980 component and equipment catalogue.

Every catalogue is sent out complete with a first class reply paid envelope (worth a small fortune these days) and five 12p discount vouchers to offset the cost of the catalogue.

Why should you buy the latest edition, if you have last year's? Well, if you don't send off for the 1980 edition, you'll miss out on all the new lines appearing in the catalogue AND somehow Greenweld have managed to reduce some of their prices. You'll also miss out on a copy of the latest bargain list (sent with every catalogue). As soon as the new Vero catalogue is available, that will be included too.

You can get all this for 40p plus 20p postage from Greenweld Electronics, 443 Millbrook Road, Southampton SO10HX.

Sci-Fi Easter

If you're into sci-fi, don't make any plans for Easter. Write 100 times in your gold embossed, leather-bound, page-a-day desk diary (or the nearest cigarette packet) — Albacon 80, the 31st UK Science Fiction Convention will be held in Glasgow over the Easter weekend.

From 4-7 April 1980 at the Albany Hotel, Glasgow, you can drift off into another world of sci-fi movies, lectures, discussions, a banquet and even a fancy dress do. You can join Albacon by sending off your £7 to the membership secretary Gerry Gillin, 9 Dunnotar Street Ruchazie, Glasgow G33.

Synthesiser (Feb)

There were a couple of minor errors in the Synthesiser project last month. The circuit diagram of the Power Supply on page 65 of the February issue shows C3 and C8 as 2n2. The correct value is, as shown in the Parts List, 2u2 25V tantalum. Now have a look at Fig 4 on page 69. C1-4 should go to ground. Also, PR3 should go to ground.

Now the bad news for anyone who uses the foil patterns published in ETI. The synthesiser foil patterns somehow got turned round the wrong way.

Audiophile AMP (Oct)

Some readers have experienced problems with RF oscillation in the power amp modules. If you're having trouble with this, place a 1000 p capacitor across each output transistors base/collector leads.

Super Index

In January we published an index to our 1979 projects and features. Thank goodness indexing only comes round once a year. We recently received a copy of a monster catalogue, listing projects published during 1978 in sixteen popular electronics and hi-fi magazines, including ETI, Hobby Electronics and Computing Today.

The projects are listed under 36 subject headings, from aeriels to time-keeping. Also included are dates of publication of alterations and amendments to projects published up to August 1979, together with additions to the 1972-77 index. Unlike our own index this one includes ETI Tech Tips features.

The 1978 volume of the Electronics Projects Index is available for £1.30, including post and packing, from its compiler (obviously a very patient man) Mr M L Scaife, Central Library, Northumberland Square, North Shields, Tyne & Wear, NE30 1QU.

Vero Cat

Last month, we gave you details of the new Vero packaging catalogue, Vero Electronics have asked us to point out that this catalogue is only available to the electronics trade. Their press release was sent to us in error. However, the good news is that Vero's new catalogue for the hobbyist will be available at the beginning of March.

Pet Chip

This should appeal to those of you who spent your hard-earned pennies on a 'pet rock,' when they were all the rage.

We recently received a letter from an anonymous dad who made an apparently trivial Christmas presi for his daughter. However, since then he has been inundated with orders.

Mr A. Nonymous painted a face on one end of an IC (pet IC, you see) and made a matchstick cage for it complete with watch battery feeding bowl.

The chip should quickly LATCH on to its new OHM. As for feeding, a few BITS of CURRENTS a day should be AMPle. Just let it NOR away to its heart's content. You can teach it tricks. In time it will learn to CHARGE and FLIP-FLOP, or even VOLT small objects.

Ta, Mr Nonymous. We haven't had a good groan in ages.

Electronic Circuit Design No. 1

Selected Reprints from **electronics today**

Introduction

Since ETI was originally launched in Britain in April 1972 we have published nearly 5000 pages of editorial matter; much of this has been devoted to electronic projects of course. In our history we have republished the best of these projects in Top Projects No 1-No 7, we have also reprinted the Tech-Tips and other circuits in Circuits Book No 1 and No 2 and our beginners series Electronics-It's Easy is now on its third reprint.

We have not however, until now, brought together the best features dealing with electronic design. Nearly

1500 pages have been devoted to this in recent years and this special is the first of a series of three which will bring together the best 250-300 of these.

Although some features are from quite early issues they have only been included because we feel that 'age' has not withered them.

We hope that the contents help the reader understand at least some of the aspects of electronic circuit design.

Halvor Moorshead
Editorial Director — ETI

Contents


- CMOS
How to use these versatile ICs
- Audio Amplifiers
Jobs over the design principles
- Tim C...
- ies
ained
- de to SCR
setu cr
- Motors 54
- 59
- 70

Electronic Circuit Design No. 1

Selected Reprints from
electronics today

£1.25

NEW FROM ETI!

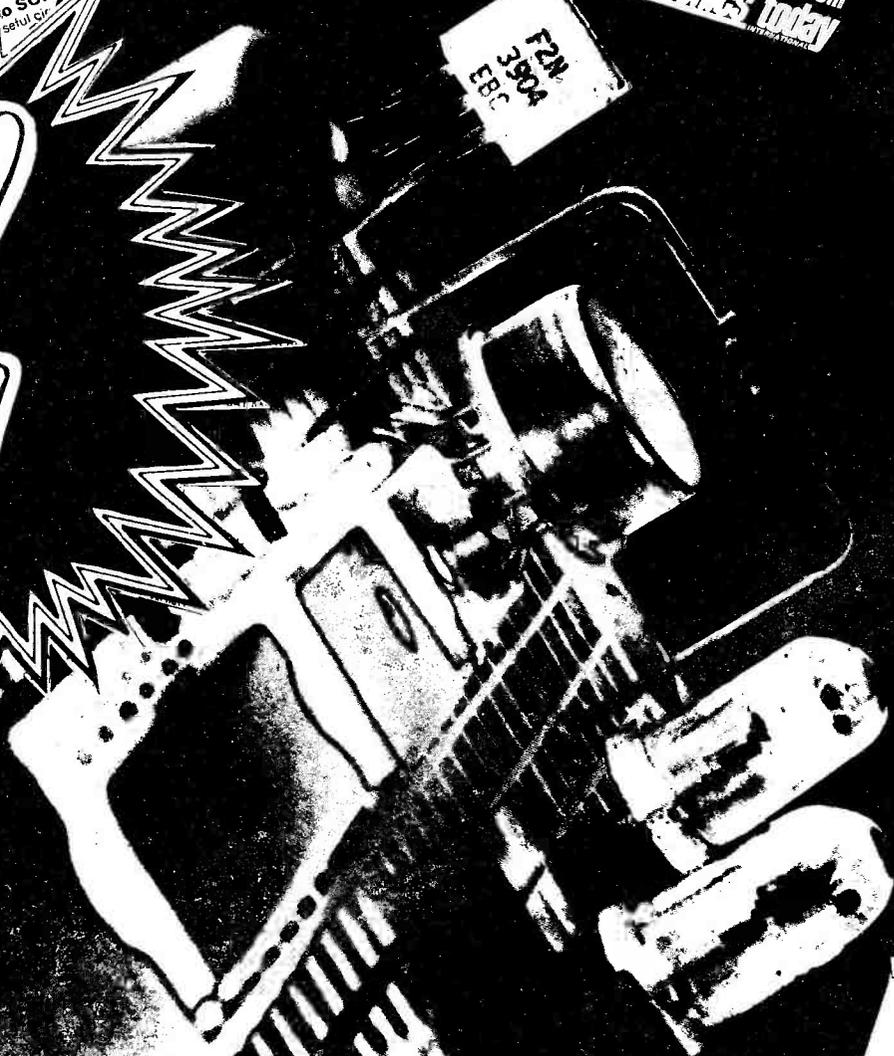


**VOL.1
OUT NOW**

**VOL.2
OUT
FEB 1st**

AT YOUR NEWSAGENT
Or order from: Specials,
Modmags Ltd, 145 Charing
Cross Road, London, WC2H
0EE. Send cheque/PO for
£1.25 + 25p (P&P) (per
volume) and please
write your name and
address on the back
of your payment.

SPECIALS

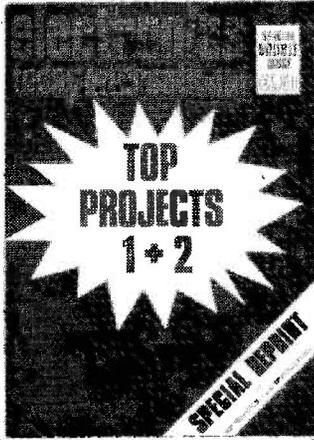

TOP PROJECTS

Book 1+2: £2.50 + 25p P&P

Master mixer, 100W guitar amp., low power laser, printmeter, transistor tester, mixer preamp., logic probe, Ni-Cad charger, loudhailer, scope calibrator, electronic ignition, car theft alarm, turn indicator canceller, brake light warning, LM3800 circuits, temperature alarm, aerial matcher, UHF-TV preamp., metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp, and many more.

Book 5: £1.00 + 25p P&P

5W stereo amp., stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice.

Book 6: £1.00 + 25p P&P.

Graphic equaliser, 50/100W amp, modules, active crossover, flash trigger, "Star and Dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show.

ETI CIRCUITS Books 1 & 2

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data.


Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P.

FROM THE PUBLISHERS OF
ELECTRONICS TODAY INTERNATIONAL

ETI CIRCUITS No 2

£1.50

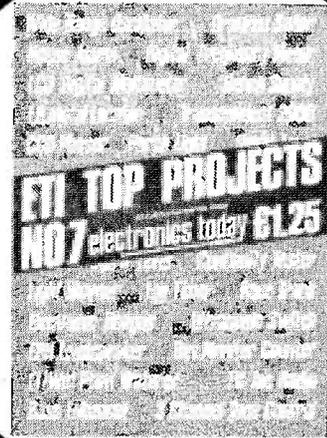

TOP PROJECTS

Book 7: £1.25 + 25p P&P

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, IB metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.



ELECTRONICS — ITS EASY

Combined volume.

This, our latest work, is a complete collection of our ever popular beginners series. Previously published in three volumes.

£3.60 + 50p P&P.



ORDER FROM

Specials Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE

Postage and packing also refers to overseas. Send remittance in Sterling only. Please mark the back of your cheque or PO with your name and address.


FROM ETI

LIGHTING & AMPLIFIER MODULES FROM L & B

01-689 4138

YOU'VE ALL HEARD OF OUR SUPERB MODULES, AND IF YOU HAVEN'T, IT'S TIME YOU DID, SO READ ON! SHOWN HERE ARE A RANGE OF THE MOST RELIABLE SYSTEMS ON THE MARKET.

LB31000SLC
£29.90

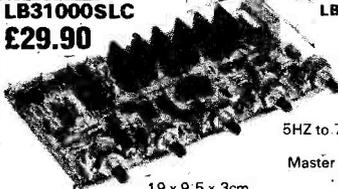

19 x 9.5 x 3cm.


LB31000SL SOUND TO LIGHT. A SUPERB PERFORMING SYSTEM AT AN INCREDIBLY LOW PRICE.

3 channels. 1000w each. Fully fused. Very high input impedance. Operates from 1/4 to 300w sound input. Third order filters. Zero voltage fired. Master/Vol/Bass/Mid/Treble controls.

LB31000SLC SOUND TO LIGHT/CHASER. THE MOST ADVANCED SOUND TO LIGHT MODULE AVAILABLE, WITH AUTOMATIC SWITCHING TO CHASE UPON ABSENCE OF A MUSIC INPUT.

3 Channels. 1000w each. Fully fused. Very high input impedance. Electronic filters. 5HZ to 70KHZ bandwidth. Operates from 1/4 to 300w sound input. Triac zero voltage triggering. Master Vol/Bass/Mid/Treble/Chase speed controls.

LB31000SL £21.40

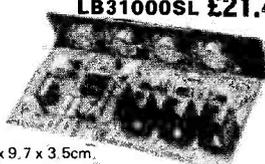

20 x 9.7 x 3.5cm.

LB81000LC CHASER A FULLY DIGITAL 8 CHANNEL CHASER, ALLOWING VARIATION OF CHASE SPEED AND CHASE RETURN DELAY.

1000w per channel. CMOS circuitry. Zero voltage fired. Can be footswitch triggered. Additional modules can be cascaded to form 16, 24, 32 chan. ect.

£26.50


LB81000LC
19 x 9.5 x 3cm.

LB41000LS SEQUENCER LOGIC RANDOM SEQUENCER, WITH TWO SPEED CONTROLS OFFERING A WIDE RANGE OF EFFECTS.

4 channels, 1000w each. CMOS circuitry.

Zero voltage fired.

LB31000LD

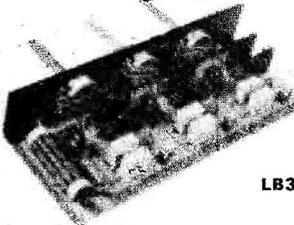

20 x 7.8 x 3.5

POWER AMPS, 250, 100 & 25W RMS. RUGGED TOUGH DEALING POWER AMP MODULES.

LB250
10HZ TO 25KHZ
S/N 110DB
THD 0.3%

LB100
10HZ TO 30KHZ
S/N 80DB
THD 0.4%

LB25
25HZ TO 50K
S/N 90DB
THD 0.07%

£39.50

£18.20

£11.20

PREAMPS

LBPA3. Complete stereo disco preamp system. Comprising of L&R deck mixers, mic mixer, deck and mic tone stages, mic auto fade over decks, PFL, output drivers and its own regulators.

LBPA2. General purpose 4 chan. mixer/tone stage.

LBPA1. Stereo Hi-Fi System



LBPA1 £19.50


LBPA2 £17.20

LBPA3-M (magnetic deck inputs) £30.70

LBPA3-C (ceramic deck inputs) £30.70

LBPA3-M
20.4 x 9.5cm

LB250PS

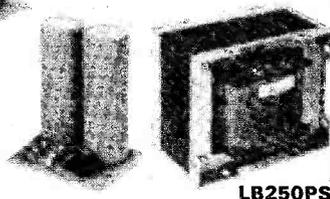

POWER SUPPLIES

Three types of powerful supply units for our power amps. Consisting of a varnish-impregnated mains transformer and rectifier board (fuse protected).

LB250PS £24.50

LB100PS £14.70

LB25PS £11.20

LB250
31 x 15 x 3.5cm

YOU REQUIRE A BOARD THAT'S MIGHTY COMPETITIVE, RELIABLE, MANUFACTURED FROM THE HIGHEST QUALITY COMPONENTS, OF HIGH PERFORMANCE, TESTED AND INSPECTED, SUPPLIED WITH CONNECTION AND CCT, DGM AND GUARANTEED. IN TWO LETTERS YOU REQUIRE L & B.


All prices shown are inclusive of VAT.
For further information, s.a.e. to Trade and Overseas inquiries welcome. P/Packing FREE in the UK except power supplies (£1.00).

L & B

45 WORTLEY ROAD
WEST CROYDON
SURREY CR0 3EB
TEL. 01-689 4138

2 SUPERB NEW KITS!

!!LOOK!!

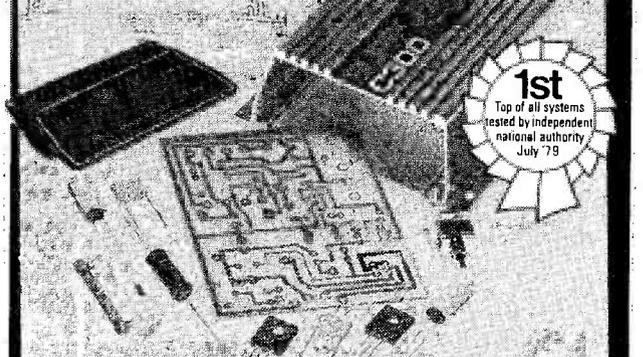

1st
Top of all systems tested by independent national authority July '79

C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection): electronic variable dwell circuit (maximises spark energy at all speeds): pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases). Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TC1).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer.

Fully illustrated comprehensive instructions and full technical back up service.

SUREFIRE ELECTRONIC IGNITION

Suretron Systems (UK) Ltd. Dept. ET14
Piccadilly Place, London Rd., Bath BA1 6PW. Tel: Bath (0225) 23194

Name

Address

*Phone order with Access Barclaycard VAT and P & P inc.

Quantity required

ES200: Neg	£13.95
C300: Pos	£17.95
C300: Neg	£17.95
Tacho Adapt. TC1	£3.90

Enclose cheq/PO's

£ Chq No.

MARPLIN


ELECTRONIC SUPPLIES



PRINTED CIRCUIT DRILLS
 Miniature 12V DC drills designed for drilling pcb's.
 Small drill: Order as BW03D Price £3.75
 Large drill: Order as BW02C Price £10.63



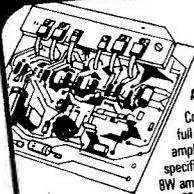ANTI-STATIC MAT & GUN
 Turntable mat removes static from discs while they are playing.
 Order as LX10L Price £3.19
 Gun removes static charge from discs. After use dust no longer clings and may be easily brushed off.
 Order as LX04E Price £8.90



AMP KITS
 Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications.
 8W amp kit: Order as LW36P Price £3.83
 50W amp kit: Order as LW35Q Price £13.73
 150W amp kit: Order as LW32K Price £14.89




HEADPHONES
 High quality stereo headphone with large padded headband and slider volume controls
 Order as WF14Q Price £8.17



CONDUCTIVE PAINT
 Repair pcb's, car demisters, etc., with this silver paint. Phial contains 3gm.
 Order as FY72P Price £2.12.



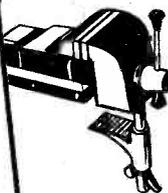McKENZIE POWER SPEAKERS
 High quality, high power speakers.
 12in. 50W 8Ω Order as XQ79L Price £18.20
 12in. 50W 16Ω Order as XQ80B Price £18.20
 12in. 80W 8Ω Order as XQ81C Price £26.92
 12in. 80W 16Ω Order as XQ82D Price £26.92
 15in. 150W 8Ω Order as XQ83E Price £56.00
 15in. 150W 16Ω Order as XQ84F Price £56.00



MINIATURE VICE
 Small modellers vice in tough plastic with metal faced jaws. Clamps to bench. Jaws width 41mm, maximum opening 30mm.
 Order as FY53H Price £2.45



20,000 OHM/VOLT MULTIMETER
 A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +22dB. Complete with test leads, battery and instruction leaflet.
 Order as YB83E Price £14.88




ELECTRET MICROPHONES
 Super quality genuine electret microphones operating on 1.5V battery (HP7-type) supplied.
 Cassette type with miniature jack plug.
 Order as YB33L Price £3.84
 Omnidirectional low-cost with standard jack plug.
 Order as YB34M Price £3.54
 Unidirectional 90°Ω with standard jack plug.
 Order as YB35Q Price £3.45
 Unidirectional 600Ω/50kΩ dual with standard jack plug (pictured).
 Order as WF34M Price £16.77



WIRING TOOLS
 Miniature box-jointed wiring pliers with insulated handles and return spring.
 Order as BR69A Price £4.52
 Miniature box-jointed side-cutters with insulated handles, return spring and precision cutting edges.
 Order as BR70M Price £4.45
 End-action wire strippers, fully adjustable, insulated handles.
 Order as BR76H Price £5.85



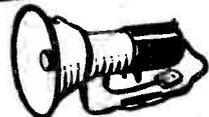
CLOCK MODULE
 Module requires only transformer and two push switches to operate 4-digit, 0.7in red LED display. Alarm and radio outputs. Battery back up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue.
 Order as XL14Q Price £8.41




MEGAPHONE
 High quality megaphone with differential microphone. Requires eight HP11 batteries (not supplied). Shoulder strap for portable operation.
 Order as XQ72P Price £49.50



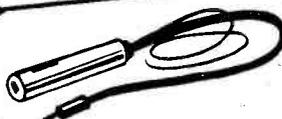
DEMAGNETISER
 Tape head demagnetiser with curved probe ideal for cassette tape heads. Cures hiss due to permanently magnetised heads. Amazing low price.
 Order as FO62S Price £4.15



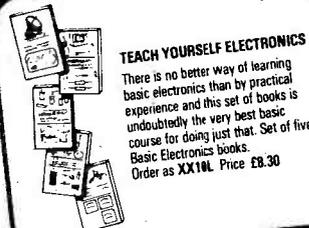CAR AERIAL BOOSTER
 High gain car aerial booster for long, medium, short and VHF bands. Negative earth cars only. Very easy to fit - just plugs in plus one wire to +12V. We have measured gains of 20dB at 90MHz!
 Order as XX37S Price £5.49



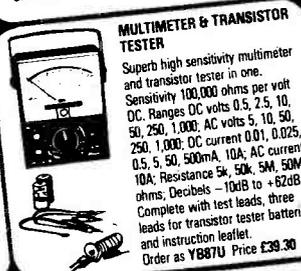
TEACH YOURSELF ELECTRONICS
 There is no better way of learning basic electronics than by practical experience and this set of books is undoubtedly the very best basic course for doing just that. Set of five Basic Electronics books.
 Order as XX19L Price £8.30



MULTIMETER & TRANSISTOR TESTER
 Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A; Resistance 5k, 50k, 5M, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet.
 Order as YB87U Price £39.30



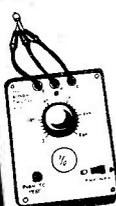TURNABLES
 Autochanger complete with stereo ceramic cartridge and circuit to make a complete low-cost record player ideal for the young pop fan.
 Order as XQ00A Price £18.48
 Single-play rim-drive turntable with stereo ceramic cartridge.
 Order as XB23A Price £23.49
 Single-play belt-drive turntable 'S' shaped tone arm.
 Order as XB25C Price £30.63



TRANSISTOR TESTER
 Accurate transistor tester measures dynamic gain, identifies unknown transistors, also ideal for matching transistors into pairs.
 Order as LH05F Price £11.86



QUICKTEST
 A safe and quick way to connect to the mains. Just snap the wires under the sprung keys and close the lid. Completely safe both open and closed.
 Order as YB21X Price £6.54

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until May 8th 1980. Export customers deduct 13% and export postage will be charged extra at cost.
 Please use order code.
 All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER.



ELECTRONIC SUPPLIES LIMITED

All mail to (ET1380), PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155. Shop: 284 London Road, Westcliff-on-Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000

BLACK HOLE THEORY

**You've read the book and seen the film, now hear the gospel
on Black Holes according to Ian Graham**

To understand what a black hole is and how it is formed, let's first have a look at the life of a star, for, under the right conditions, the death of a star may herald the birth of a black hole. The birthplace of stars is within the clouds of material between the stars. These clouds collapse under their own gravitational fields. Local regions of increased density form condensation nuclei whose gravitational fields grow gradually stronger as more and more material is attracted towards them. As these embryonic stars (protostars) continue to contract their temperature begins to rise, producing internal heating and emitting radiation into the surrounding space. When the temperature is high enough for hydrogen fusion to begin, contraction ceases.

The greater part of the star's life-time is then occupied with burning its hydrogen fuel, forming helium, which sinks deep into the core. Eventually, when the hydrogen is almost exhausted, the star's temperature begins to fall and the core begins to contract. We must now look at the star, not as a homogeneous ball of burning gas, but as a relatively heavy core surrounded by a lighter envelope. There is a constant battle between thermal forces, trying to blow the star apart and gravitational forces trying to crush it. Contraction of the core causes a rise in temperature, temporarily halting contraction and causing an expansion of the envelope ie the star appears to be growing larger. The remaining hydrogen is burnt off in the outer layers, sending more helium to the core. Eventually the core collapses under the immense pressure of the upper layers and this is accompanied by an enormous expansion of the envelope, forming a red giant.

Great Balls Of Fire

The final episode in the star's life depends on its mass. Let's take the route that will take us to a black hole. The core continues contracting, helium fusing to form carbon and successively heavier elements. Eventually it collapses rapidly, blowing off the envelope in a supernova explosion during which the single star may outshine an entire galaxy.

The explosion may destroy the core completely or it may leave a small core. However, if the star was more than two or three times as massive as our own Sun, the core surviving a supernova will rapidly collapse. Theorists predict that the collapse will continue until the core radius reaches zero. This hugely massive, but dimensionless point in space is called a singularity.

No Escape

The singularity has such a strong gravitational field that light itself cannot escape ie the escape velocity of the body is greater than the speed of light. The further we are from the black hole, the lower is the escape velocity (the gravitational force decreases with the square of our distance from the body). At a particular distance from the singularity, the Schwarzschild radius, the escape velocity equals the speed of light. Within this event horizon, nothing escapes.

For a body of mass (M), the Schwarzschild radius (R_s) is given by:

$$R_s = \frac{2GM}{c^2}$$

(G is Newton's gravitational constant and c is the speed of light).

If we let M be the mass of our own Sun, R_s turns out to be 3 kms. So, why isn't the Sun a black hole? Its radius is much larger than 3 kms, so beyond this event horizon the Sun's hydrogen fusion reactor can radiate its energy out into space, but if the Sun's mass was to be compressed to a diameter of less than 3 kms, it would become a black hole.

If we look at our own Earth and the bodies around us in the solar system and even the Milky Way galaxy as a whole, we find that they all rotate ie they all have angular momentum.

The angular momentum (L) of a rotating body of mass (m), radius (r) at an angular velocity of ω is given by:

$$L = m\omega r^2$$

If a rotating body such as the remnant of an exploded star, begins to contract ie r gets smaller, the angular velocity (ω) must increase in order that angular momentum may be conserved. Depending on its mass a black hole may rotate at about 1000 times a second. A black hole is such a dense body that one the size of a proton would weigh in at about ten thousand million tonnes!

Just as the Earth bulges slightly at the equator and is flattened at the poles due to centrifugal force, the much greater rotation of a black hole results in a much more severe deformation. The equations predict that a black hole is not a sphere at all. It may be similar in profile to a spiral galaxy (like the Milky Way) ie a disc with a bulge at its centre.

All this speculation on the formation and structure of a black hole may seem to be purely academic. After all, how do you go about finding a black hole to prove that it exists and verify its structure and behaviour? Even if you knew where to look, how would you observe something from which no light can escape?

Stellar Striptease

You may not be able to see the black hole itself, but it should be possible to observe what it does to any matter near it. The best candidate for detection would be a black hole and a star orbiting each other — a binary system. Material should be stripped from the star and wind its way round the black hole, forming a disc, finally disappearing beyond the Schwarzschild radius like water funnelling down your bath plug-hole. As the matter crowds together for its last dive to oblivion, its temperature rises until it is hot enough to radiate at X-ray wavelengths.

The search for X-ray sources could not begin until the space age because radiation in the X-ray region of the spectrum cannot penetrate the Earth's atmosphere. One of the earliest X-ray sources discovered by orbiting telescopes was Cygnus X-1, in the constellation of Cygnus. The X-ray source accompanies a visible blue giant star. The visible star's speed was found to be varying along a sine wave, so it must have an invisible companion around which it is orbiting.

Most of the light emitted by the system appears to arise, not from the visible blue star, but from helium gas sucked from it and circulating around its invisible companion. The companion's mass has been calculated as more than the critical three solar masses, so it is likely to be a black hole.

Another system likely to become a household name among black hole hunters is V861 Scorpii (the V indicates that its brightness appears to vary). This variation over a period of about eight days is due to a dark body orbiting

(and eclipsing) a blue supergiant. Like Cygnus X-1, V861 Scorpil is a binary system.

Dark Star

In both these cases, the dark star could be either a black hole or a neutron star. A neutron star is a body where the matter from a collapsed star core is compressed so tightly that electrons and protons are pushed together to form neutrons. Again, mass is the determining factor. If the mass is less than about three Suns, the body will be a neutron star. If it is above the critical mass, it should be a black hole.

Shaking The Edifice

Life was much simpler for scientists in Victorian times. Through classical Newtonian physics, everything under the Sun (and beyond it) seemed describable and predictable. It was just a matter of time before the scientists achieved a comprehensive understanding of the universe and determined the physical laws to describe all the processes therein, from the subatomic level upwards. Then along came trouble-makers like Planck and Einstein, who showed that an electromagnetic wave could behave like a stream of particles. In classical physics a wave is not the same as a particle and never the twain shall meet. Not content with shaking the foundations of prevailing physics, Einstein (leader of the popular front for the liberation of physics) went on to predict the effects of very dense bodies on time itself.

Space and time are inextricably intertwined. Close to a black hole space is curved so severely that time itself loses its meaning. Stephen Hawking and Roger Penrose working at Cambridge saw the possibility that any object (including a spacecraft) falling towards a rotating black hole may not fall into the murderous singularity, but may miss it, to reappear elsewhere in our universe (or another universe) an instant later. Einstein's theories predicted the possibility of bridges between the warped planes of space. However, black holes were then believed to be non-rotating bodies, so that any matter falling over the event horizon could not help but hit the singularity.

Instant Travel

If only a small fraction of the matter falling into a rotating black hole misses the singularity, what becomes of it? It must reappear at the other end of the tunnel an instant later, maybe light years away from where it disappears. So, there must be points in space where matter appears to be spewing forth from nowhere — white holes. Now, if black holes are almost undetectable because of their blackness,

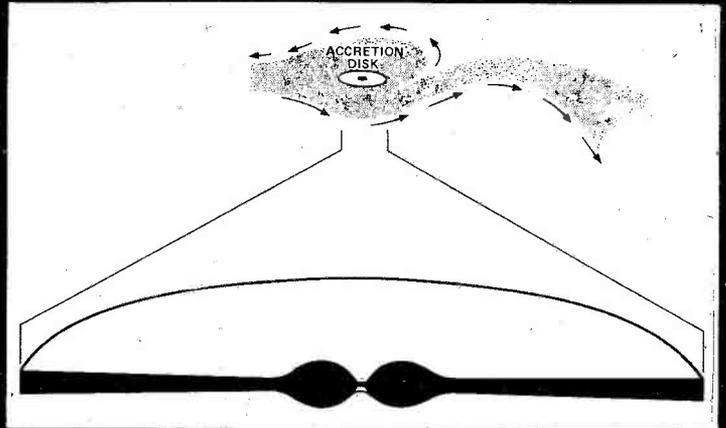


Fig. 2. As matter is sucked from the giant star towards the black hole, it builds up an accretion disc around the event horizon.

the detection of white holes should be simplicity itself. Indeed there are galaxies, known as Seyferts (after the man who identified them in 1943) which resemble galaxies like the Milky Way, but for one characteristic. The centre of a Seyfert is very bright and smaller than usual, and it emits radiation at frequencies which the Milky Way absorbs. The galactic nucleus seems to be an exploding ball of matter and energy — possibly a white hole.

Sci-Fi

The black hole may seem to be a futuristic concept. In fact, Laplace realised that if a body was massive enough, its escape velocity would exceed that of light, as far back as 1798. That black holes might make possible travel across light years of space in an instant (or even time travel) sounds more like science fiction.

Before we can verify the theories and check out the equations we will have to get the hang of interstellar travel, or find a black hole in the solar system. Cygnus X-1 is about 600 light years away. As for black holes in the solar system — it's not as crazy as you might at first imagine. The Big Bang, from which the universe is believed to have begun, would have produced the magnitude of pressures necessary to produce black holes in their millions. Our galaxy could be sprinkled with these tiny Big Bang black holes. When a study of the Sun, looking for neutrinos produced in nuclear reactions at its centre, found none, one researcher suggested that a small black hole in the Sun itself may satisfy the findings.

It may sound like science fiction . . . but for how much longer?

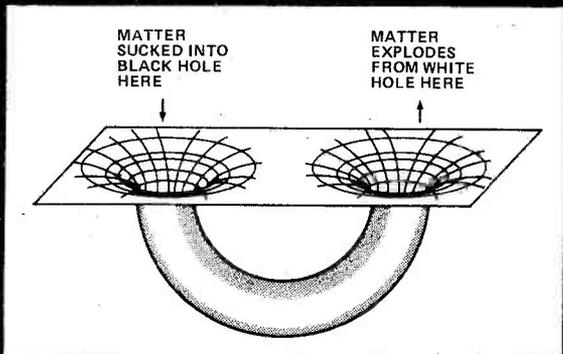


Fig. 1. If all the matter disappears into a black hole, it must appear somewhere else at a White Hole.

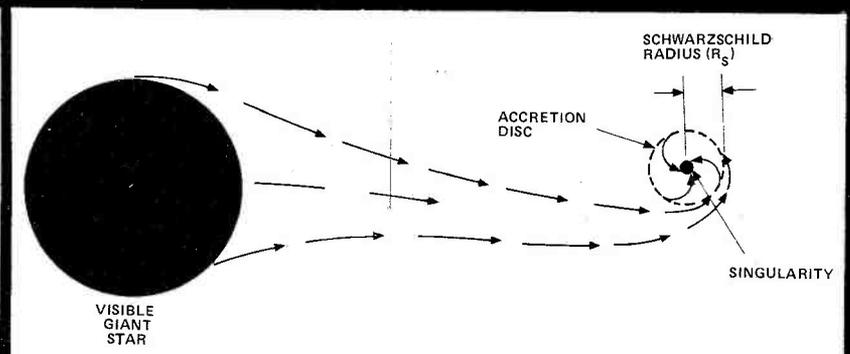



Fig. 3. The black hole and its giant companion star orbit one another, as the hole strips material from the star.

IT'S HAPPENED AGAIN!

THE PART THREE CATALOGUE IS PUBLISHED & WE HAVE MOVED TO BIGGER PREMISES.

Yes, it's here at last - the all new Part Three Catalogue. Fun for all the family, and the usual update on all that is new, worthwhile and exciting in the world of Radio and Communications. A big section on frequency synthesis techniques covering broadcast tuners, to communication quality transmitter systems. More new products than ever - RADIO CONTROL parts, crystal filters, ceramic filters for 455kHz and the new range of TOKO CFSH low temperature coefficient types for 10.7MHz. Details on new radio ICs, including the new HA11225, the CA3189E lookalike with 84dB signal to noise, and adjustable muting threshold. Radio control ICs - and an updated version of the RCM&E 8 channel FM receiver - now with an Ambit designed screened front end, with 27MHz ceramic bandpass filter, LCD panel clock/timer modules - the neatest and best LCD panel DVM yet (only £19.45 each + VAT), the new 5 decade resolution DFM3 for LW/HF/VHF with LCD readout. The DFM6 with fluorescent display to 10kHz resolution on VHF, 1kHz on SW. A 1kHz HF synthesiser with five ICs - the list is endless. Get your copy of the catalogue now. Post publication price is 60p (inc PP etc). The previous two sections are also required for a complete picture: Parts 1 & 2 £1 the pair, All 3 £1.50. And don't miss our spot the gibbon contest, together with a quiz to see if you can spot the differences between a neolithic cave drawing and a circuit diagram of one of our competitor's tuners.


Updated RCME FM radio control RX kit

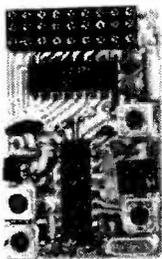

- 8 Channel RC receiver (FM)
- Single IC RF/IF/Detector
- Single IC decoder
- 27MHz ceramic filter input
- FET RF stage with double tuned bandpass filter
- Dual ceramic filter IF
- Based on RCM&E FM system
- Best quality SLM servo connector block
- ONLY £16.10 inc VAT (kit) (includes new SLM case)


DOES YOUR ONE GLOW GREEN IN THE DARK ??

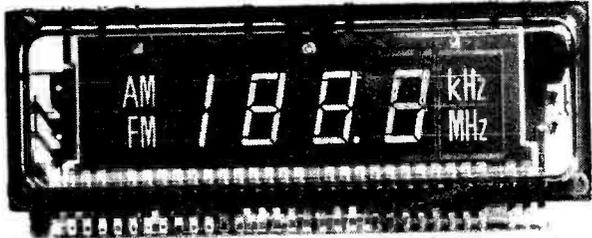Our DFM4 does, since it uses a vacuum fluorescent display for direct readout of MW/LW/FM. Basically the same as the DFM2, (LCD Version). £24.45 kit (inc VAT) Transformer with all necessary windings for DFM4 - £2.50 inc VAT.



Not illustrated here - but also now available is the DFM6. This is a vacuum fluorescent display version of our immensely popular DFM3 (LCD). Resolution is 100Hz to 3.9999MHz, 1kHz to 39.999MHz, and 10kHz to 200.00MHz±; all standard IF offsets (inc. 10.7MHz on shortwave) are available via diode programming.

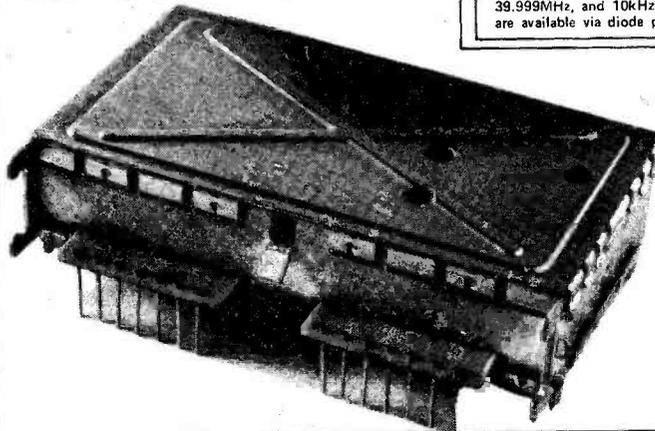New series of radio modules in fully screened cans:



UM1181 VHF band 2 VARICAP TUNERHEAD

5 tuned circuit, with image/spurri better than -80dB, buffered LO output, MOSFET RF stage, FET IF preamp, tunes with only 1% to 8v, -9dBm 3rd order intercept. 10% price £12.00 inc VAT. (100off/ OA)

911225 FM IF strip with all mod-cons for the HiFi tuner: All types use 80dB S/N Hitachi IC, with muting, AFC, AGC, meter outputs for signal level and centre zero. IF preamp stage

'A' Dual linear phase ceramic filters, with MOSFET (AGC'd) IF preamp and a 3rd narrow filter with DC filter selection. Dual tuned FM detector stage. £23.95 inc VAT (built)

'B' Dual ceramic filters, single tuned detector stage £14.95 inc VAT (All 'A' series units are set up with a spectrum analyzer for best THD)

91072 AM RADIO TUNER MODULES - DC TUNED and DC SWITCHED Available February '80

All include buffered LO output, mechanical IF filter (TOKO CFMQ) 1-10v tuning bias, switching by a single pole to earth

A MW/LW (150 to 350kHz LW range) with ferrite rod antenna

B As 'A' but also including SW1 or SW2 (specify.)

SW1 = 1.8 to 4MHz SW2 = 5 to 10MHz

C With both SW ranges

Prices - one off INC VAT

'A' £14.43 'B' £15.90 'C' £17.50 (Custom types OA)

There is a danger - when advertising in some magazines - that because we do not find space to list everything we sell in every ad., that some readers forget about half the ranges we stock. So to summarize the general ranges:

- TOKO Chokes, coils for AM/FM/SW/MPX, Audio filters etc Filters: Ceramic for AM/FM, LC for FM, MPX etc. Polyvaricons ICs for radio, clock LSI, radio control MPX decoders etc
- Micrometals Dust iron cores for toroids for resonant and EMI filters Toroid mounts
- Hitachi Radio/audio/mpx linear ICs 100W MOSFETs, small signal FETs, MOSFETs and bipolar

And the following groups of products from a broad range of sources:

Semiconductors - specializing in radio devices, Plessey SL1600, EUROPE's best selection of AM/FM and communications devices. Power MOSFETs, WORLD'S LOWEST NOISE AUDIO small signal transistors, BAR graph LED drivers for linear and log. CD4000 series CMOS, TTL/LPSNTTL, standard linears (741, 301, 3080 etc). MPUs, memories. Small signal transistors from AEG BC237/8/9 families etc. (1000 off BC239C : 5.2p ea) LEDs: AEG 3mm/5mm round, 2.5x5mm flat, red, green, orange, yellow. The best prices you will find for quality products. MOSFETs for RF signal processing, including the BF960 UHF device, and 3SK51 for VHF. Varicap diodes for 17:1 capacity ratio tuning

FREQUENCY READOUT LSI from OKI, with a one-chip answer to most digital frequency display needs (and various modules).

Crystal and ceramic ladder filters from leading manufacturers, ferrite rods, various ferrite beads and a range of crystals for 'standard' frequencies and both AM and FM radio control at 27MHz. Trimmer capacitors.

METERS - a new range of linear movement types, plus many 'indicator' types for VU, all types of tuning indicators etc.

SOCKETS - a new range that are better quality than Texas low profile, yet better priced.

Modules for AM/FM/STEREO, complete kits for tuners, audio amplifiers from Larshot.

SWITCHES - complete low cost DIY systems for push button arrays, keyboard switches.

DOUBLE BALANCED MIXERS - MCL SBL1, replacement for MD108 etc. And cheaper.

OUR LATEST MOVING EXPERIENCE :: At last, we have moved to the address below. There is car parking for customers approaching via North Service Road (an extension of North Road Avenue, entrance opposite the Brentwood Fire Station.) Pedestrian access from the High Street (alongside 117 High Street). The new building is six times bigger than our Gresham Road offices, and we will be installing a much expanded sales counter in the fullness of time. NEW TELEPHONE NUMBER (0277) 230909, TELEX NUMBER (as before) 995194 AMBIT G. See you there!

200 North Service Road, Brentwood, Essex.



Freeport
Birmingham
B19 1BR
021-233-2400

- FREEPOST ON ORDERS
- ACCESS
- VAT INCLUSIVE PRICES
- VISA
- ADD 30p P&P
- CASH
- 24 HR PHONE ANSWERING SERVICE
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED


CAPACITORS						Electrolytic Axial Leads						Electrolytic Radial Leads						Miniature Low Value						Polyester Radial Leads																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																							
Electrolytic Axial Leads						Cap 015 + µF + V.d.c.						-10% to +50% Tol.						Cap 034 + µF + Volts						Cap 424						Cap 630						Cap 629																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
µF	V.d.c.	16	25	40	63	µF	V.d.c.	6.3	10	15	25	35	40	50	63	pF	424	632	100	150	220	330	470	630	100	150	220	330	470	630	µF	352	380	424	470	510	560	630	710	800	910	1000	1100	1200	1300	1500	1800	2200	2700	3300	3900	4700	5600	6300	7100	8000	9100	10000	11000	12000	13000	15000	18000	22000	27000	33000	39000	47000	56000	63000	71000	80000	91000	100000	110000	120000	130000	150000	180000	220000	270000	330000	390000	470000	560000	630000	710000	800000	910000	1000000	1100000	1200000	1300000	1500000	1800000	2200000	2700000	3300000	3900000	4700000	5600000	6300000	7100000	8000000	9100000	10000000	11000000	12000000	13000000	15000000	18000000	22000000	27000000	33000000	39000000	47000000	56000000	63000000	71000000	80000000	91000000	100000000	110000000	120000000	130000000	150000000	180000000	220000000	270000000	330000000	390000000	470000000	560000000	630000000	710000000	800000000	910000000	1000000000	1100000000	1200000000	1300000000	1500000000	1800000000	2200000000	2700000000	3300000000	3900000000	4700000000	5600000000	6300000000	7100000000	8000000000	9100000000	10000000000	11000000000	12000000000	13000000000	15000000000	18000000000	22000000000	27000000000	33000000000	39000000000	47000000000	56000000000	63000000000	71000000000	80000000000	91000000000	100000000000	110000000000	120000000000	130000000000	150000000000	180000000000	220000000000	270000000000	330000000000	390000000000	470000000000	560000000000	630000000000	710000000000	800000000000	910000000000	1000000000000	1100000000000	1200000000000	1300000000000	1500000000000	1800000000000	2200000000000	2700000000000	3300000000000	3900000000000	4700000000000	5600000000000	6300000000000	7100000000000	8000000000000	9100000000000	10000000000000	11000000000000	12000000000000	13000000000000	15000000000000	18000000000000	22000000000000	27000000000000	33000000000000	39000000000000	47000000000000	56000000000000	63000000000000	71000000000000	80000000000000	91000000000000	100000000000000	110000000000000	120000000000000	130000000000000	150000000000000	180000000000000	220000000000000	270000000000000	330000000000000	390000000000000	470000000000000	560000000000000	630000000000000	710000000000000	800000000000000	910000000000000	1000000000000000	1100000000000000	1200000000000000	1300000000000000	1500000000000000	1800000000000000	2200000000000000	2700000000000000	3300000000000000	3900000000000000	4700000000000000	5600000000000000	6300000000000000	7100000000000000	8000000000000000	9100000000000000	10000000000000000	11000000000000000	12000000000000000	13000000000000000	15000000000000000	18000000000000000	22000000000000000	27000000000000000	33000000000000000	39000000000000000	47000000000000000	56000000000000000	63000000000000000	71000000000000000	80000000000000000	91000000000000000	100000000000000000	110000000000000000	120000000000000000	130000000000000000	150000000000000000	180000000000000000	220000000000000000	270000000000000000	330000000000000000	390000000000000000	470000000000000000	560000000000000000	630000000000000000	710000000000000000	800000000000000000	910000000000000000	1000000000000000000	1100000000000000000	1200000000000000000	1300000000000000000	1500000000000000000	1800000000000000000	2200000000000000000	2700000000000000000	3300000000000000000	3900000000000000000	4700000000000000000	5600000000000000000	6300000000000000000	7100000000000000000	8000000000000000000	9100000000000000000	10000000000000000000	11000000000000000000	12000000000000000000	13000000000000000000	15000000000000000000	18000000000000000000	22000000000000000000	27000000000000000000	33000000000000000000	39000000000000000000	47000000000000000000	56000000000000000000	63000000000000000000	71000000000000000000	80000000000000000000	91000000000000000000	100000000000000000000	110000000000000000000	120000000000000000000	130000000000000000000	150000000000000000000	180000000000000000000	220000000000000000000	270000000000000000000	330000000000000000000	390000000000000000000	470000000000000000000	560000000000000000000	630000000000000000000	710000000000000000000	800000000000000000000	910000000000000000000	1000000000000000000000	1100000000000000000000	1200000000000000000000	1300000000000000000000	1500000000000000000000	1800000000000000000000	2200000000000000000000	2700000000000000000000	3300000000000000000000	3900000000000000000000	4700000000000000000000	5600000000000000000000	6300000000000000000000	7100000000000000000000	8000000000000000000000	9100000000000000000000	10000000000000000000000	11000000000000000000000	12000000000000000000000	13000000000000000000000	15000000000000000000000	18000000000000000000000	22000000000000000000000	27000000000000000000000	33000000000000000000000	39000000000000000000000	47000000000000000000000	56000000000000000000000	63000000000000000000000	71000000000000000000000	80000000000000000000000	91000000000000000000000	100000000000000000000000	110000000000000000000000	120000000000000000000000	130000000000000000000000	150000000000000000000000	180000000000000000000000	220000000000000000000000	270000000000000000000000	330000000000000000000000	390000000000000000000000	470000000000000000000000	560000000000000000000000	630000000000000000000000	710000000000000000000000	800000000000000000000000	910000000000000000000000	1000000000000000000000000	1100000000000000000000000	1200000000000000000000000	1300000000000000000000000	1500000000000000000000000	1800000000000000000000000	2200000000000000000000000	2700000000000000000000000	3300000000000000000000000	3900000000000000000000000	4700000000000000000000000	5600000000000000000000000	6300000000000000000000000	7100000000000000000000000	8000000000000000000000000	9100000000000000000000000	10000000000000000000000000	11000000000000000000000000	12000000000000000000000000	13000000000000000000000000	15000000000000000000000000	18000000000000000000000000	22000000000000000000000000	27000000000000000000000000	33000000000000000000000000	39000000000000000000000000	47000000000000000000000000	56000000000000000000000000	63000000000000000000000000	71000000000000000000000000	80000000000000000000000000	91000000000000000000000000	100000000000000000000000000	110000000000000000000000000	120000000000000000000000000	130000000000000000000000000	150000000000000000000000000	180000000000000000000000000	220000000000000000000000000	270000000000000000000000000	330000000000000000000000000	390000000000000000000000000	470000000000000000000000000	560000000000000000000000000	630000000000000000000000000	710000000000000000000000000	800000000000000000000000000	910000000000000000000000000	1000000000000000000000000000	1100000000000000000000000000	1200000000000000000000000000	1300000000000000000000000000	1500000000000000000000000000	1800000000000000000000000000	2200000000000000000000000000	2700000000000000000000000000	3300000000000000000000000000	3900000000000000000000000000	4700000000000000000000000000	5600000000000000000000000000	6300000000000000000000000000	7100000000000000000000000000	8000000000000000000000000000	9100000000000000000000000000	10000000000000000000000000000	11000000000000000000000000000	12000000000000000000000000000	13000000000000000000000000000	15000000000000000000000000000	18000000000000000000000000000	22000000000000000000000000000	27000000000000000000000000000	33000000000000000000000000000	39000000000000000000000000000	47000000000000000000000000000	56000000000000000000000000000	63000000000000000000000000000	71000000000000000000000000000	80000000000000000000000000000	91000000000000000000000000000	100000000000000000000000000000	110000000000000000000000000000	120000000000000000000000000000	130000000000000000000000000000	150000000000000000000000000000	180000000000000000000000000000	220000000000000000000000000000	270000000000000000000000000000	330000000000000000000000000000	390000000000000000000000000000	470000000000000000000000000000	560000000000000000000000000000	630000000000000000000000000000	710000000000000000000000000000	800000000000000000000000000000	910000000000000000000000000000	1000000000000000000000000000000	1100000000000000000000000000000	1200000000000000000000000000000	1300000000000000000000000000000	1500000000000000000000000000000	1800000000000000000000000000000	2200000000000000000000000000000	2700000000000000000000000000000	3300000000000000000000000000000	3900000000000000000000000000000	4700000000000000000000000000000	5600000000000000000000000000000	6300000000000000000000000000000	7100000000000000000000000000000	8000000000000000000000000000000	9100000000000000000000000000000	10000000000000000000000000000000	11000000000000000000000000000000	12000000000000000000000000000000	13000000000000000000000000000000	15000000000000000000000000000000	18000000000000000000000000000000	22000000000000000000000000000000	27000000000000000000000000000000	33000000000000000000000000000000	39000000000000000000000000000000	47000000000000000000000000000000	56000000000000000000000000000000	63000000000000000000000000000000	71000000000000000000000000000000	80000000000000000000000000000000	91000000000000000000000000000000	100000000000000000000000000000000	110000000000000000000000000000000	120000000000000000000000000000000	130000000000000000000000000000000	150000000000000000000000000000000	180000000000000000000000000000000	220000000000000000000000000000000	270000000000000000000000000000000	330000000000000000000000000000000	390000000000000000000000000000000	470000000000000000000000000000000	560000000000000000000000000000000	630000000000000000000000000000000	710000000000000000000000000000000	800000000000000000000000000000000	910000000000000000000000000000000	1000000000000000000000000000000000	1100000000000000000000000000000000	1200000000000000000000000000000000	1300000000000000000000000000000000	1500000000000000000000000000000000	1800000000000000000000000000000000

GMT
ELECTRONICS

**Freepost
Birmingham
B19 1BR
021-233-2400**

- ACCESS
- VISA
- CASH
- CHEQUE

FULL SPEC KIT TELETEXT DECODER

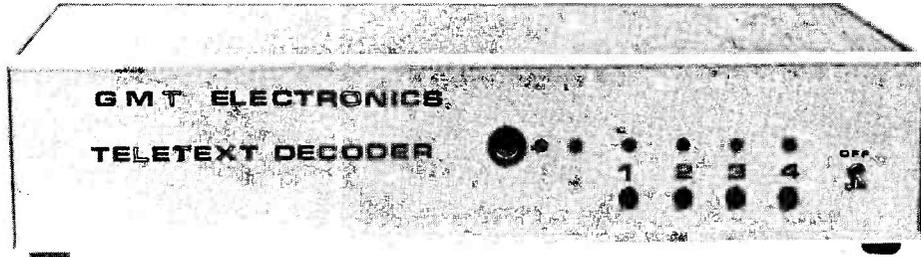

- STATE OF THE ART L.S.I. CIRCUITS
- DOUBLE HEIGHT CHARACTER SELECTABLE FOR LEGIBILITY
- CHARACTER ROUNDING - EFFECTIVELY DOUBLES DEFINITION
- ULTRASONIC REMOTE CONTROL
- HIGH QUALITY THROUGH PLATED P.C.B.
- ALL I.C. MOUNTED ON SOCKETS
- PREALIGNED UHF/IF MODULES
- NEEDS NO INTERNAL CONNECTION TO THE TELEVISION SET
- SIZE 430mm x 90mm x 220mm
- SUPPLY 240v 50Hz 35w
- *NEW *TOUCH CONTROL KEYPAD* NEW*

INCLUDES TUNER, P.S.U., DECODER, REMOTE KEYBOARD, P.A.L. ENCODER, U.H.F. MODULATOR CASE WITH SCREENED AND PUNCHED FRONT PANEL.


— **£189.90 inc VAT. P & P £3.00.**

FULL TELETEXT MANUAL IF BOUGHT SEPARATELY — **£2.50 P & P £0.50.**

P.C.B.'S AND L.S.I. I.C.'S NOT SOLD SEPARATE FROM KITS.

P & P INCLUDES CARRIAGE, PACKING AND INSURANCE

DOPPLER RADAR ALARM

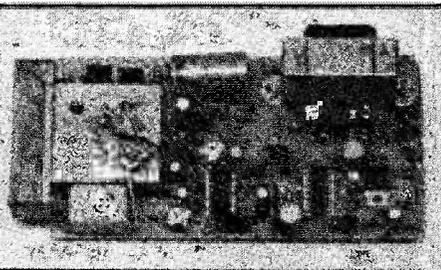


Do your goodies need protecting? No need to run miles of wire, and hack window and door frames to pieces. Just build a Doppler Radar Alarm kit. It can be mains or battery operated (external battery required), and is triggered by any movement in its detection area. It incorporates an arming delay - to enable you to leave its detection field safely, and a trigger delay (0 to 45 seconds), so you can catch the thief red handed without a prior warning having been given.

The unit provides a 12 volt output, normally high (low on alarm), to supply an external remote relay, which is not supplied. The unit has an integral buzzer to give an indication when the unit is being armed, and when triggering is complete. The unit comes complete with a suitable case.

DOPPLER RADAR ALARM **£39.50**

F.E.T. POWER AMPLIFIER

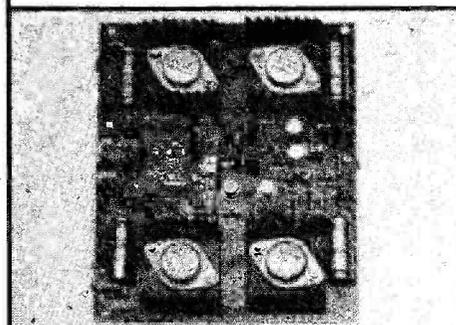

Bring your Hi-Fi up to date. Available now is a 100 watt audio amplifier using POWER MOSFETS. The POWER MOSFET has several advantages over bipolar transistors. It has good frequency response, no carrier storage delay, thermal stability, no secondary breakdown, and high input impedance. The MOSFET Amplifier has been designed to deliver a continuous power output of 100 watts with full heatsinking into 8 ohms from 5 Hz to 100 kHz with no more than 0.01% total harmonic distortion, which is about a tenfold improvement on ordinary bipolar techniques. The high output impedance and thermal stability of the MOSFET reduces the size of the total circuit by about 30%. The kit does not include a case.

reduction
POWER MOSFET AMPLIFIER MODULE **£27.50**

SIGNAL TRACER

eti signal tracer

10M 10pF signal probe detects audio, mains fields and amplitude modulated RF.

HOW IT WORKS

It has been said that a signal tracer is just an amplifier with a diode at the front. In fact, for many applications, just such an arrangement is all that is required. This design fulfills the above description and then some!

Boasting a high input impedance and good sensitivity, the unit drives a small loudspeaker or personal earphone with good volume. Power may be derived from the equipment under test or a separate nine volt supply may be used. Use of the specified case ensures a neat and attractive project. The case is identical to that used in the CSC logic probe kit and comes complete with detachable probe, power supply leads and a small piece of perforated board (not needed here). Its place is taken by the PCB. The case comes complete with cut-outs for three indicator LEDs. Only one is used in this design to accommodate the power indicator LED and the other two may be blanked off or simply left vacant.

Construction

Use of the PCB is really essential. Quite apart from the problem of fitting all the bits in the case, layout is critical to avoid stray feedback and spurious oscillation. Owing to the limited space available in the case, the physical size of the components is important and the smallest available components should be used. Note that C3 lies over R3, 4 and capacitors C5, 9 need to lie on their sides. A flying lead link should be taken from R2 (Q1 drain) to C2. This may be done on the underside of the board and should be as short and direct as possible. LED 1 is mounted on the board and is self-supporting.

In use, the unit should be connected to a nine volt supply and a loudspeaker plugged into SK1; use screened cable to avoid stray feedback. As a simple test, hold the probe within a couple of centi-

PARTS LIST

Resistors

R1	10M
R2,12	1k0
R3,10	1k5
R4	2k7
R5	150k
R6	18k
R7	10k
R8	470R
R9	2
R11	10R

Capacitors

C1	10p ceramic
C2,4,6	10n ceramic
C3	6u8 tantalum
C5,9	47n tantalum
C7	220u electrolytic
C8	2u2 tantalum
C10	47n ceramic
C11	100u tantalum

Semiconductors

IC1	LM386
Q1	2N3819
Q2	BC109
LED 1	any 0.125" LED
D1	1N4004

Miscellaneous

case, socket, 8 ohm earphone or loudspeaker

To provide high input impedance with good sensitivity a FET input stage is used. Q1 is connected as a common source amplifier, decoupled to AC by C3, with the output taken across R2. This stage is coupled to Q2 by C4. Q2 operates as an AM detector and audio amplifier. The output is taken across R7 and is decoupled to RF by C5. The power supply to this section of the circuit is provided via R10 smoothed by C7. A small integrated audio amplifier forms the output stage. IC1 provides its own input bias and the output automatically centres at half the supply voltage. C10 and R11 prevent instability. The output is coupled via C11 to an eight ohm personal earphone or loudspeaker. Shielded cable should be used to prevent stray feedback to the input stage. Overall power is supplied via D1 which protects against accidental reversal of the supply leads. Power is indicated by LED 1. As this component is sited near the input stage its power supply is decoupled by C9 to prevent instability due to stray feedback. When used with 9 volt battery equipment, power may be derived from the circuit under test. When a separate supply is used to power the probe, a connection should be made from 0 V to the earth of the equipment under test. Bear in mind the voltage rating of C1; for a small ceramic capacitor, this may be only fifty volts or so.

BUYLINES

The LM386 is available from Watford Electronics. The remaining components are unexceptional and should be readily available. The case is manufactured by Continental Specialties Corporation, type CTP-1. Continental Specialties Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.


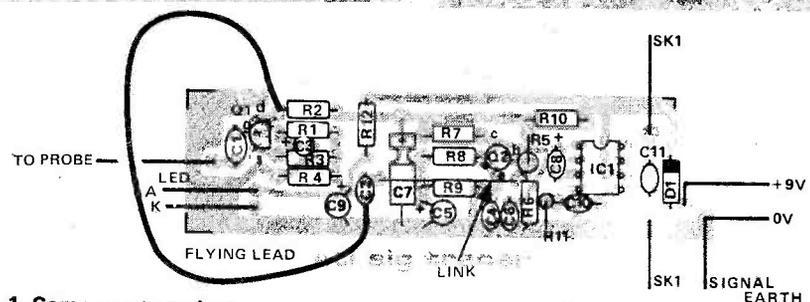


Fig. 1. Component overlay.

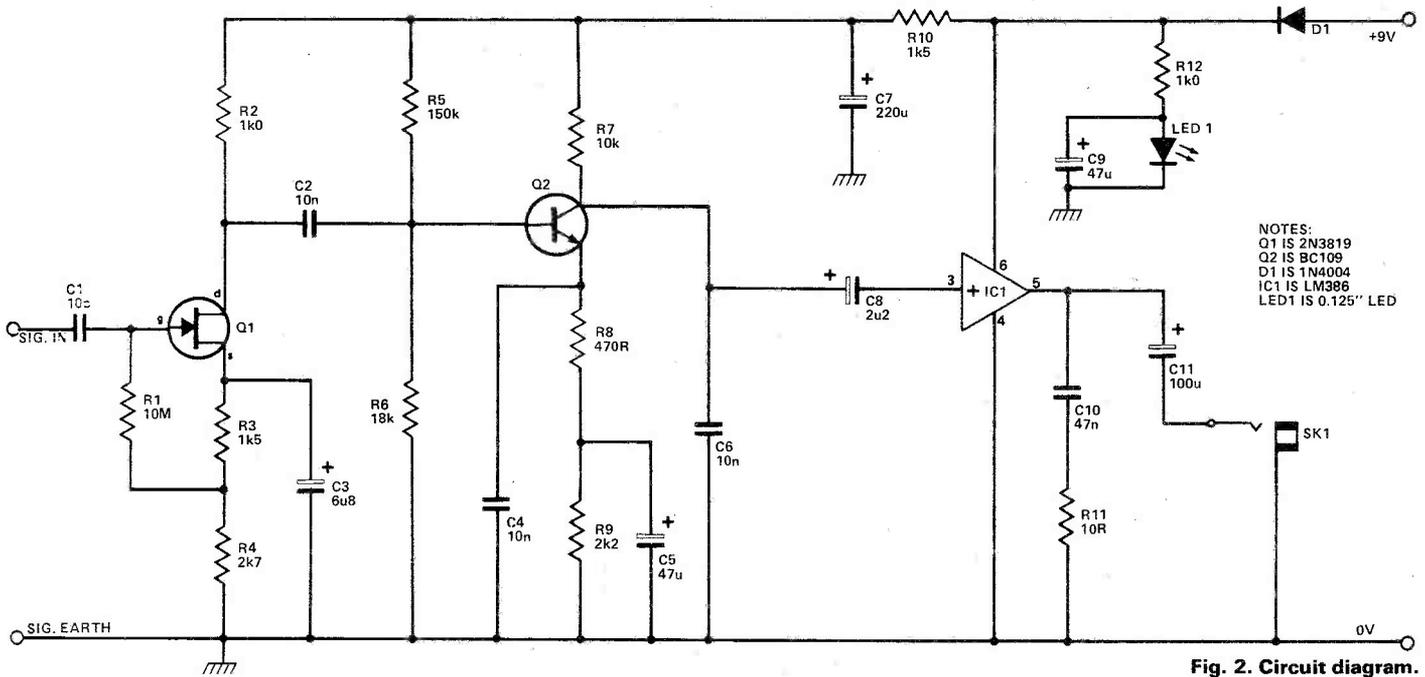

NOTES:
 Q1 IS 2N3819
 Q2 IS BC109
 D1 IS 1N4004
 IC1 IS LM386
 LED1 IS 0.125" LED

Fig. 2. Circuit diagram.

metres of a live mains lead. A loud hum or buzz should be heard. When using the tracer with a separate power supply from the equipment under test a wire should be taken from 0 V to the equipment's earth to provide a signal return

path. Remember that the input capacitor C1 may only be rated at about fifty volts if you are thinking of working with high voltage equipment. As well as detecting low level audio, the probe may also be used to detect radio-

frequency signals at frequencies up to and above 10 MHz. Sensitivity is quite adequate to make the unit useful with TRF receivers and signals are easily detected in conventional medium-long wave superhets. **ETI**

IT'S A DOGS LIFE!

Mighty mongrel strikes again!

Stop your powerful pooch carving up your carefully collected ETIs with his canine choppers and live in hardback harmony with a profusion of precious project books by armour-plating your archives.

Invest in an ETI binder. You know it makes sense.

You can have any colour you like as long as it's black.

**Send a mere £3.20 to:
 ETI Binder
 145 Charing Cross Road
 London WC2H 0EE**

electronics today

international


What to look for in the April issue: on sale March 7th

CIRCUIT SUPPLEMENT

Next month's ETI carries something really special — a SIXTEEN PAGE circuit supplement for the experimenter. All the circuits have been tried and tested by us, making this the most reliable reference yet. If there is anything you need a circuit for or any circuits you need something for this is the place to find it. No less than 50 in all. Half a hundred of the best you'll find anywhere.

Well worth keeping for that inevitable future time when you'll NEED ONE or more of the priceless little gems lying amid these pages.

50 TESTED
CIRCUITS
TO BUILD

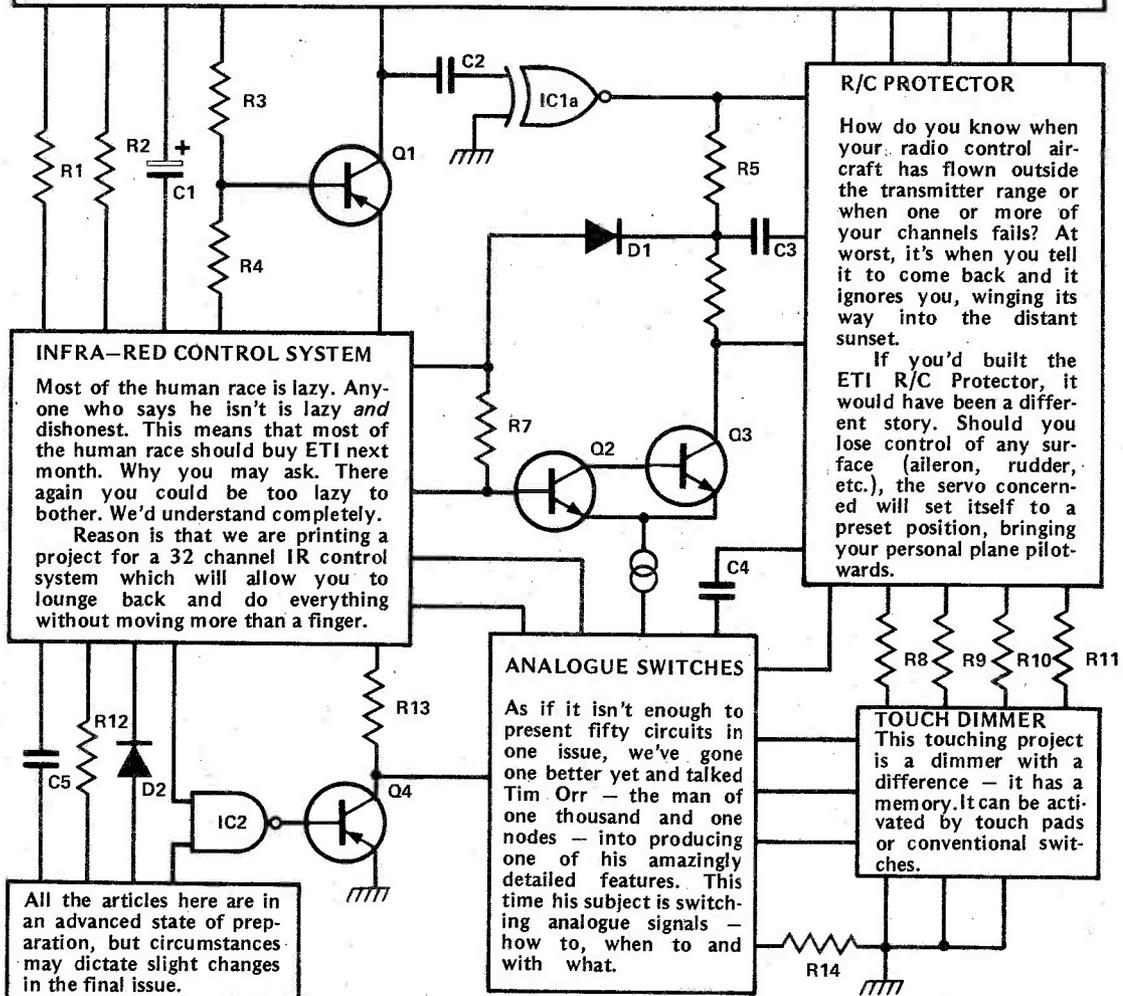

THE 1537 VCA

Keith Brindley brings you up to date with the latest offspring of the silicon chip family - complete with practical applications.

There is always a great deal of excitement generated in electronics on the arrival or introduction of a new circuit, concept or chip, particularly if the system is potentially a field leader. The 1537A chip is just that! The specifications which the device can offer in situ are well above those of any similar preceding systems. Table 1 gives a listing of specifications, which can be obtained in the correct applications.

Parameter	Specification
Bandwidth	DC-200kHz
T.H.D., 20Hz-20kHz	0.004%
I.M.D. (SMPTE TEST)	0.03%
Noise	-90dBv, ± 1 dB (worst case, unity gain)
Overshoot and Ringing	None
Slew Rate	> 10v/usec, symmetrical & constant
Input Impedance	20K Ω
Maximum Input Level	+20dBv
Gain	0dB (Unity)
Maximum Attenuation	>94dB
Control Voltage	0 to +10V
DC shift vs. Attenuation	≤ 5 mV
Power Requirements	Regulated ± 15 V at +25, -33mA

Table 1. The maximum possible specifications available from a 1537A system.

With harmonic distortion of 0.004% and a signal/noise ratio of over 90 dB the system is of course well suited to studio applications, although use in this environment is by no means its only area of involvement. The IC itself seems at first glance, somewhat highly priced at around £6, but nevertheless, it requires few extra components to produce a VCA system of the superb quality (suggested in the specifications of Table 1) and overall represents good value for money to the amateur and professional engineer alike.

Amplifier Or Attenuator

The term VCA is normally used as an abbreviation of the phrase Voltage Controlled Amplifier, but in its simpler modes the 1537A is, strictly speaking, a voltage controlled attenuator ie with a maximum gain of unity. The inventors, do, however, stress that connection of the 1537A into the feedback loop of an amplifier (such as an op amp) produces a voltage controlled amplifier. The applications section of this article show how this can be achieved.

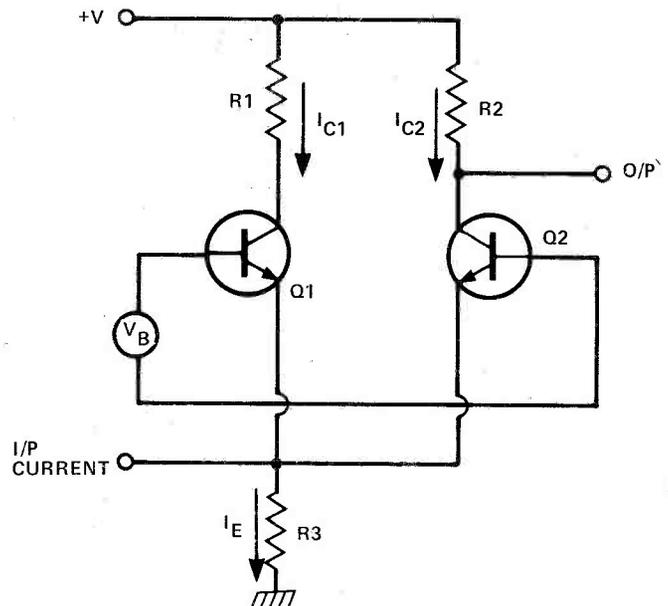


Fig. 1. A differential pair of transistors — the basis of a VCA.

The operation of the 1537A VCA depends upon the gain control function of a differential pair of transistors as in Fig. 1. The transistors in Fig. 1 are connected at their emitters. The current through R3 (I_E) is, therefore, approximately equal to the sum of their two collector currents I_{C1} and I_{C2} through R1 and R2 respectively. The relative bias voltage, V_B , between the two bases determines the relative collector currents. If we now apply an input signal current to the joined emitters we obtain output signal currents through R1 and R2, the sizes of which are determined by the bias voltages. In other words, by altering this bias voltage we alter the size of the output signals.

Figure 2 shows a simplified internal circuit of the 1537A chip giving pin numbers and external load and emitter resistors necessary for operation. There are two basic gain control circuits within the chip, similar to that in Fig. 1 (built around Q1, 2 and Q5, 6) except for three main differences: — the diode connection of the transistor pair not used for signal output ie Q1 and Q6, which reduces the distortion due to transistor gain differences. — the addition of buffers around Q4 and Q8 to reduce loading of the output collectors of the gain transistors, in turn allowing idealised characteristics over the full gain range. — the use of transistors Q3 and Q7 as voltage to current converters enabling the input to be applied as a voltage rather than as a current.

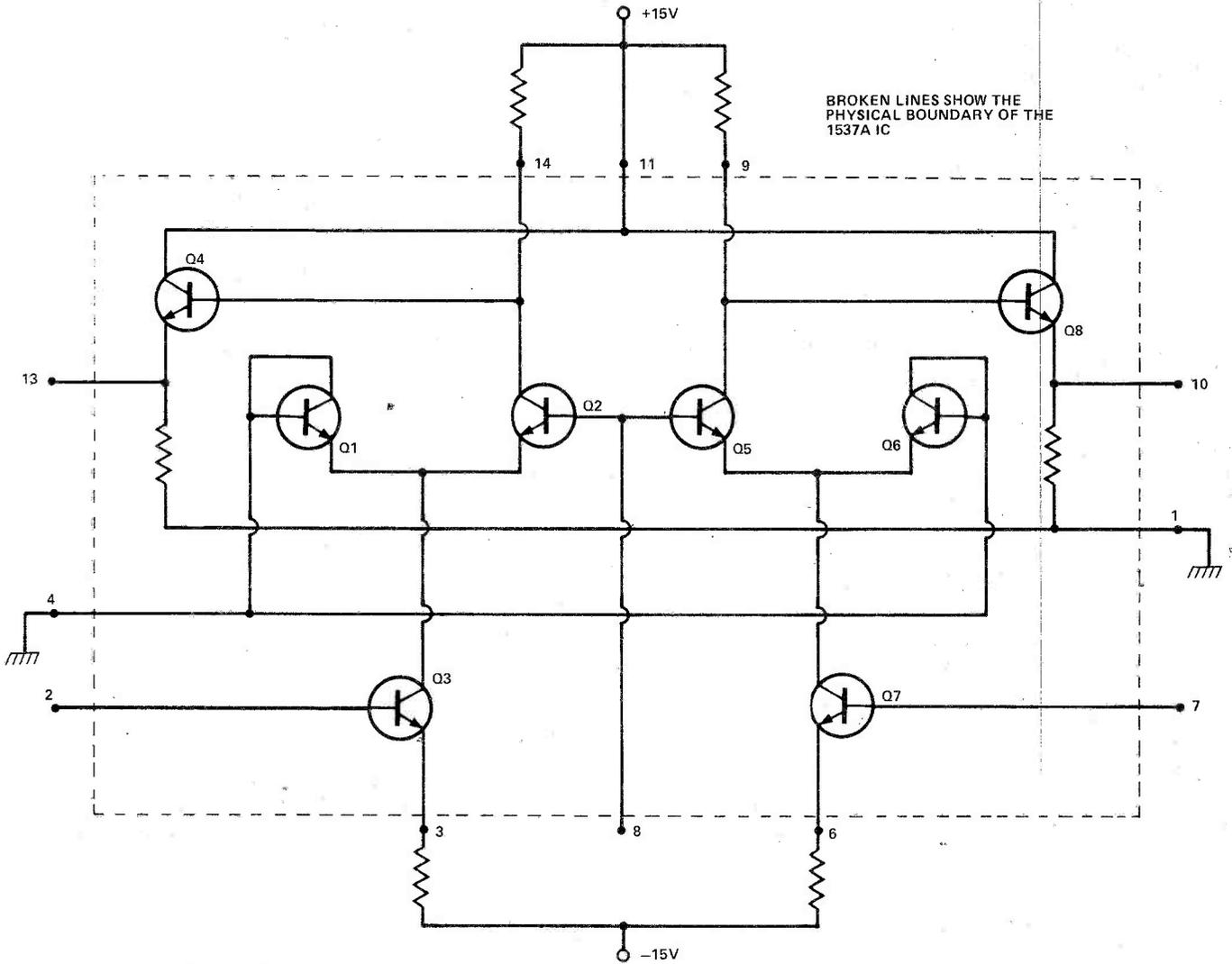


Fig. 2. A much simplified internal circuit of the 1537A IC, showing external load and emitter resistors.

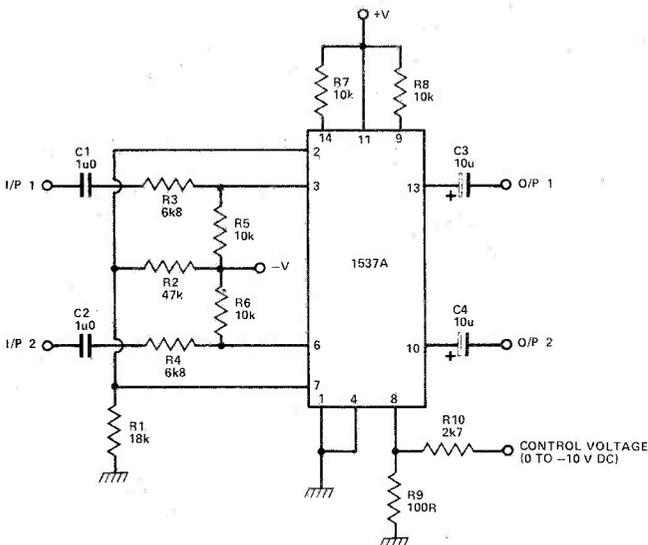


Fig. 3. The simplest mode of operation of the 1537A — a low input impedance stereo VCA with a negative going control voltage.

There is, however, a much more subtle difference, on top of this and that is the use of large geometry transistors. The effect of larger geometry transistors can improve second order intermodulation by as much as ten times for a tenfold increase in transistor size. Noise can also be reduced by about 10 dB for a similar increase in geometry.


This leads us now to the simplest mode of operation of the 1537A using each gain control circuit individually, although the control voltage affects the gain of each circuit simultaneously (Fig. 3).

The ratio of R9 and R10 is calculated to allow a control voltage range of 10 volts (ie 0 to minus 10 V), altering the gain of the system from 0 dB to about -90 dB. The input impedance of the circuit to applied signal is low and ideally buffers should be placed before this circuit. Although this circuit does not give studio quality specifications it will, however, still produce results in the "high fidelity" range, providing impedance matches are considered.

Figure 4 shows a circuit application which gives a higher impedance input. Also included is an inverting stage in the control voltage link which allows a voltage of 0 to + 10 volts to be used for controlling attenuation.

Although any operational amplifier could be used for ICs 1, 2 and 3 in the previous circuit, it should be fairly ►

Fig. 4. A higher input impedance stereo VCA with positive going control voltage.

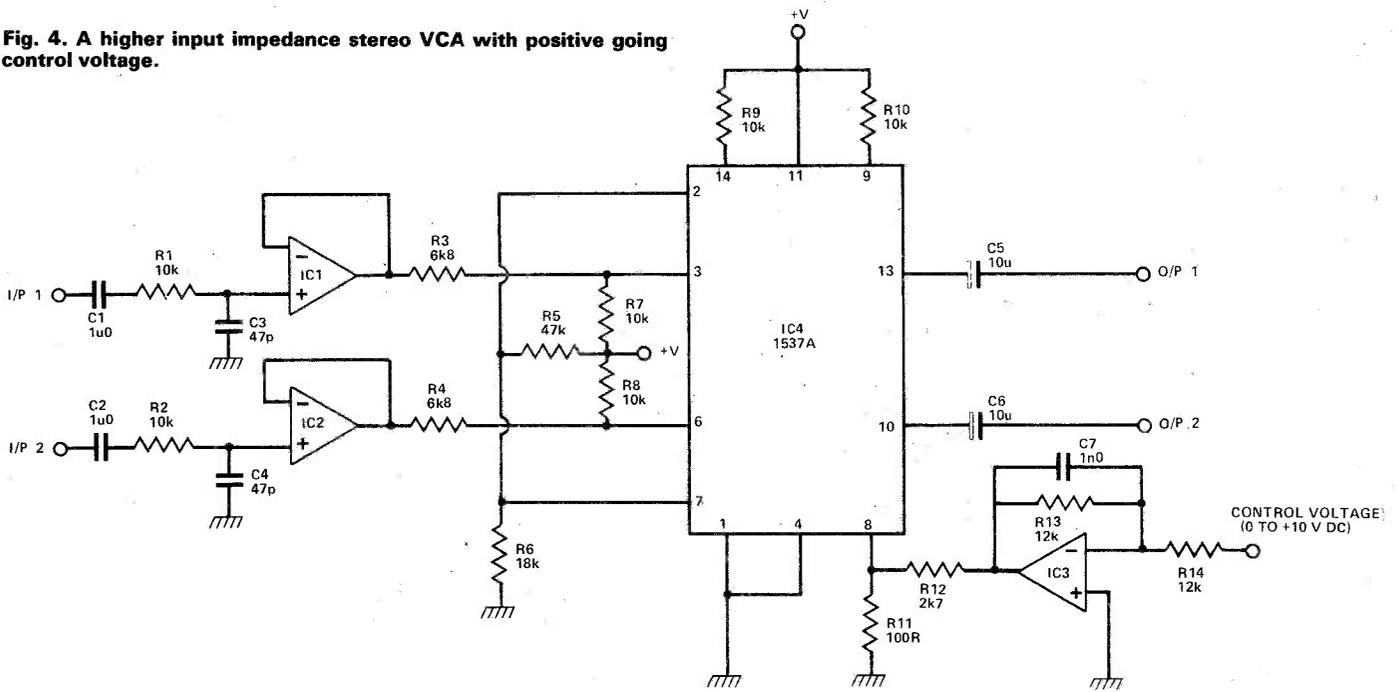

apparent that the noise, distortion and bandwidth specs of the circuit are limited to those of the op amps used.

Either of the two circuits of Figs. 1 and 2 can be adopted as the voltage controlled gain heart of a stereo system. Their outputs are about 10 dB down on the inputs so necessary amplification should be given before or after the attenuator.

Coming Up To Scratch

Now, three more developments to the circuitry can be undertaken to improve the specifications to those of Table 1. Figure 5 shows the circuit of the ideal system capable of these high specs.


Firstly, actively linearised voltage to current sources (op amp 3 and 4 in Fig 5) improve distortion figures when

using a wide range of input signal voltages.

Secondly, paralleling of the two individual gain control circuits (ie the same input signal is fed to both devices at their inputs and mixed at their outputs) gives a 3 dB improvement in S/N ratio.

Finally, a technique is utilised which is complementary to the previous development of parallel devices, whereby the same input is applied to both gain control devices but 180 degrees out of phase. The two outputs are combined in a differential amplifier to give a single ended output. The differential amp is formed around op amp 6. This technique has the effect of reducing DC shift caused by bias and control voltages and with careful adjustment of RV1, the minimal DC shift now left at the output can be reduced even.

Fig. 5. Full specification mono VCA (showing component numbers and values of a practical circuit).

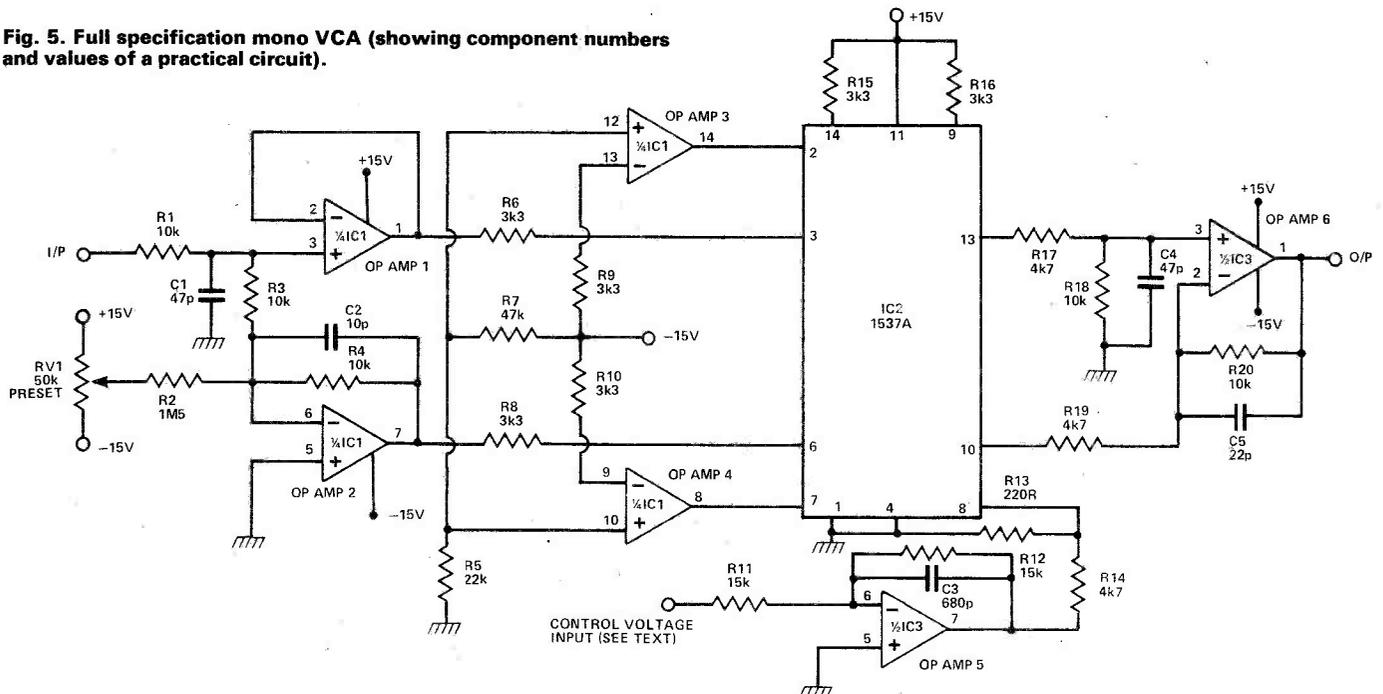

further to near (if not actually) zero. The prototype circuit shown, upon testing, actually gave no DC shift at all (or at least none measureable on our test equipment).

The complete circuit can be used as an exceptionally high quality VCA whose signal input can be anything from a few millivolts through to about 20 volts pk to pk without distortion. The lack of DC blocking capacitors at the input and output means that the system can be used to control a DC voltage applied to the input. AC signals up to well over 200 kHz are easily catered for, due to the system's wide bandwidth.

The overlay in figure 6 shows the component layout on printed circuit board of the circuit. The PC design is given in the Foil Pattern section of this issue and will enable interested readers to build the system and get first hand experience of it. As far as we know this article is the first of its kind to present a circuit in a form where "experimenters" can benefit easily and directly from the written text whilst simultaneously using the device in a tried and tested form.

Construction

If the circuit board layout is followed then there should


be no problems. IC holders are advisable though by no means necessary. RV1 should be a good quality type (cermet), to assist in setting up the output offset shift to zero, cheaper quality presets can sometimes be tricky to adjust in low voltage DC applications of this nature. Op amps 1 to 4 in the circuit are combined in IC1 and can be of a wide range of types from a quad 741 type (3403) upwards. Obviously, if you wish to obtain the best specs the quality of the op amps are critical. LF 347 or TL 074 will give the best results.

Similarly op amps 5 and 6 are included in IC3 and LF 353 or TL 072 are of optimal quality.

Setting Up

The system should work without any adjustment for an AC signal and varying the control voltage from 0 to 10 volts should give total control over the output amplitude. Some setting up will be required if the input is to be DC, though. This is best achieved by earthing the input. Measure the output voltage using a high impedance voltmeter (it should only be the order of a few millivolts). Adjust RV1 until a complete sweep of control voltage ie from 0 to 10 volts produces only minimal change in DC output voltage. The

Fig. 6. Overlay of PCB of the 1537A VCA module.

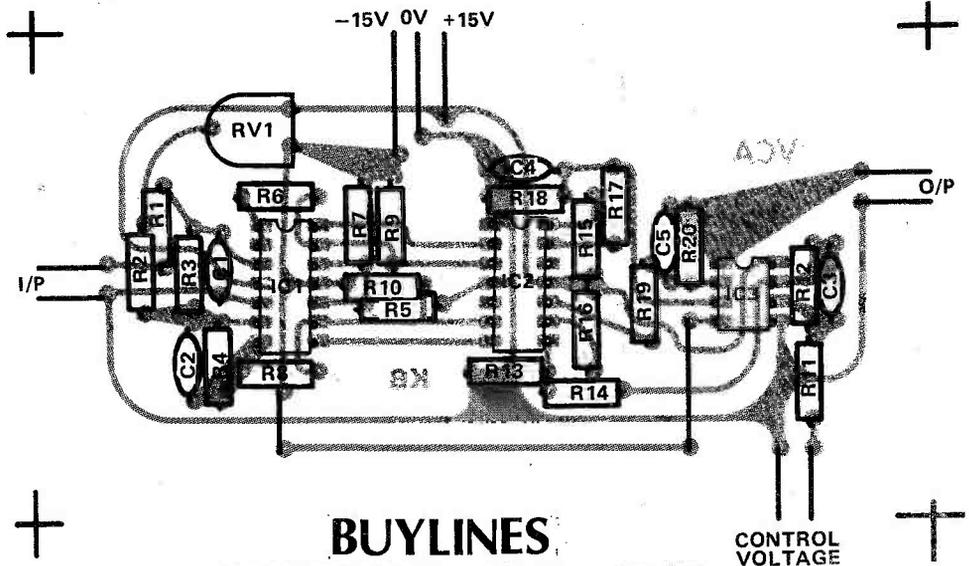

PARTS LIST

RESISTORS All kW, 5%	
R1,3,4,18,	10k
20	
R2	1M5
R5	22k
R6,8,9,10,	3k3
15,16	
R7	47k
R11,12	15k
R13	220R
R14,17,19	4k7
PRESET	
RV1	50k min horiz cermet
CAPACITORS	
C1,4	47p polystyrene
C2	10p polystyrene
C3	680p polystyrene
C5	22p polystyrene
SEMICONDUCTORS	
IC1	TL074, LF347 etc.
IC2	1537A
IC3	TL072, LF353 etc.
MISCELLANEOUS	
IC Holders	
PCB	

BUYLINES

Most of the larger mail order companies will be able to help with the quad and dual op amps if you experience any difficulty in obtaining them.

The 1537, however, is presently obtainable only from Apex Audio Systems Ltd. Their address is 35 Britannia Row, London N1 8QH. They have kindly agreed to offer the IC to ETI readers at the reduced rate of £5.00 each including VAT, which is 15% off the normal price. However, this is dependent on small quantity CWO orders and the special code 'ETI APHEX 101' must be quoted with your order.

All other components should be easily obtainable.

circuit is now completely set up to accept an input signal in the frequency range DC to 200 kHz. At minimum attenuation the system operates as a unity-gain wide range, high quality buffer, with a reasonably high input impedance and low output impedance. Variation of the DC control voltage over the range 0 to 10 volts will produce over 90 dB of attenuation of the output signal.

If an overall gain is required in the circuit, resistors R18 and R20 can be changed as in Table 2.

GAIN	R18 & R20
0dB	10k
6dB	22k
10dB	33k
15dB	56k

Table 2. The values of R18 and R20 to give the required overall gain in the VCA system of Fig. 5.

The control voltage range of 10 volts can be altered as required simply by changing the ratio of resistors R13 and R14 to suit.

To our knowledge, there is no officially recognised standard symbol for a VCA and rather than redraw the whole circuit of figure 5 upon every reference to the circuit we thought it better to invent a symbol for the purposes of this article. A horizontal trapezoid shape appeared to be the ideal symbol, as shown in Fig. 7. It symbolizes the system as a modular buffer amplifier, whose output (symbolized by the top line), decreases as the control voltage (the bottom line), increases. We shall use the modular symbol of a VCA whenever reference is made to the circuit of Fig. 5, although any VCA module of another design should function in the applications which we give.

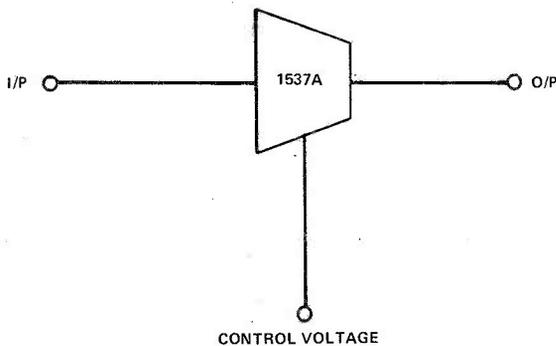


Fig. 7. The ETI symbol of a VCA module.

Use of the 1537A system module as a DC controlled analogue gate can produce many effects. Amplitude modulation of the signal occurs and the usual associated effects are observed. For instance, in Fig. 8 we can see a simple but high quality tremelo unit. Transistors Q1 and Q2 are connected as a phase shift oscillator and buffer, with speed and depth controls whose varying DC output is connected directly to the control port of the 1537A module. The frequency range of the oscillator is approximately 2 to 5 Hz. Altering the values of all three capacitors will change the main frequency, though that stated will give the best results.

The control voltage in the last application was varied as a sine wave of course, but there is no reason why other waveforms eg square, could not be used for control purposes. Figure 9 shows a 555 operating in the astable

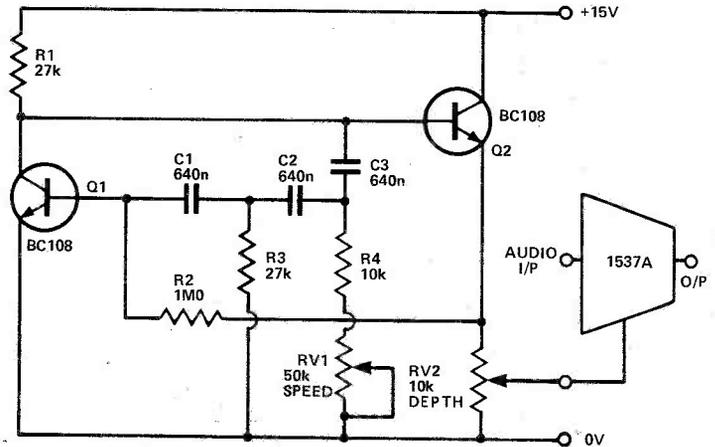


Fig. 8. A simple tremolo circuit.

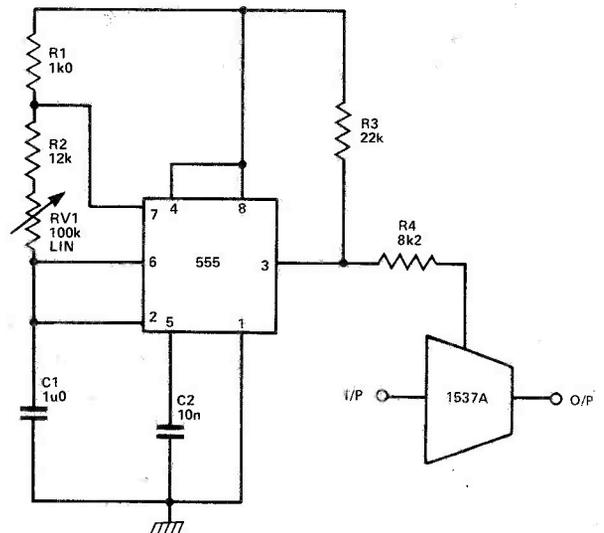


Fig. 9. A Dalek type sound generator.

mode with a frequency range of approximately 5-50 Hz. The output signal will be modulated with the square wave and the overall product is a Dalek type sound if a vocal signal is applied to the 1537A module.

This square wave control can be taken one stage further if the control voltage is the output from a monostable as in Fig. 10. A tone burst generator can be very easily constructed with this mode of operation. In a tone burst

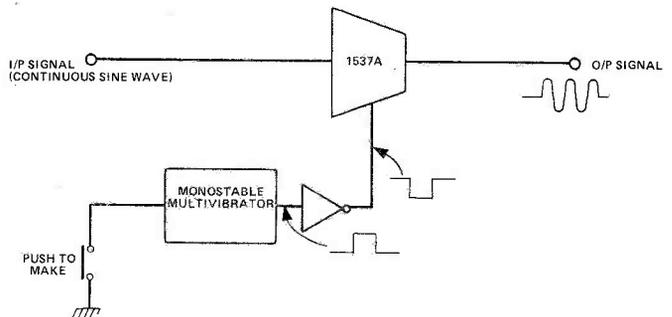


Fig. 10. A simple system enabling the construction of a tone burst generator.

generator, a rectangular envelope 50-500 μ s long is formed around a single sine wave frequency of normally 1 kHz. Tone burst generators are useful for testing the transient response of speakers. A push to make switch is used to provide the trigger to fire the multivibrator, producing the correct length pulse which in turn is inverted to form the control voltage pulse, applied to the control port of the 1537A.

The previous applications have all used automatic waveform control of the applied signal to produce the required attenuation characteristics, but this is not a necessary trait. The control voltage can be simply tapped off a variable resistor having the maximum control voltage range (ie 10 volts) across it. In this way, altering the position of the wiper alters the attenuation of the applied signal. The pot acts quite simply as a volume or level control. Ordinary non-DC volume controls can suffer from pick-up problems because the signal itself is being rotated through the pot. As only DC is applied to the pot in this application no pick-up can occur and the control can be remotely mounted from the module with no screened cable being necessary. Figure 11 shows such a volume control.

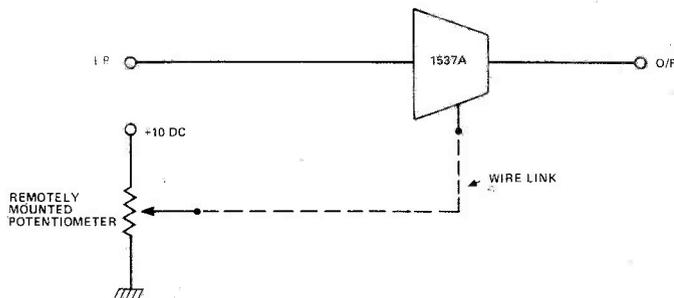


Fig. 11. Remotely (wire-linked) controlled volume control.

This remote control facility can be utilised in an audio mixer which includes remote faders for each channel. Figure 12 shows the general idea of such a circuit. An op amp is used as a summing amplifier into which the output of each channel's VCA is fed and mixed. The mix is relative to the control voltage applied from the remote faders to each VCA. The circuit allows for up to N inputs, where N to practical limits will probably be a maximum of about 12, but with careful layout techniques, there is no reason why this cannot be increased further.

Figure 13, shows an interesting outline to enable digital control of the VCA, say from a computer link. In order that the computer can operate in real-time, ie control of the VCA is not just its only job, it is necessary for the interface to provide a latch for the digital word. The output of this latch is changed to a linear DC voltage by the D/A (digital to analogue) convertor whose output is taken to the control port of the VCA.

The digital latch, once set by a strobe pulse, provides the facility that after the volume required has been found, the computer is free to perform other tasks. When the volume is to be altered, the latch is reset to the new digital input.

The last six applications of the 1537A VCA system have simply shown methods of providing a control voltage (automatically, manually or digitally) to control the module in its function as an analogue gate. The following section begins with the assumption that the control voltage is already present, perhaps by one of the previous methods.

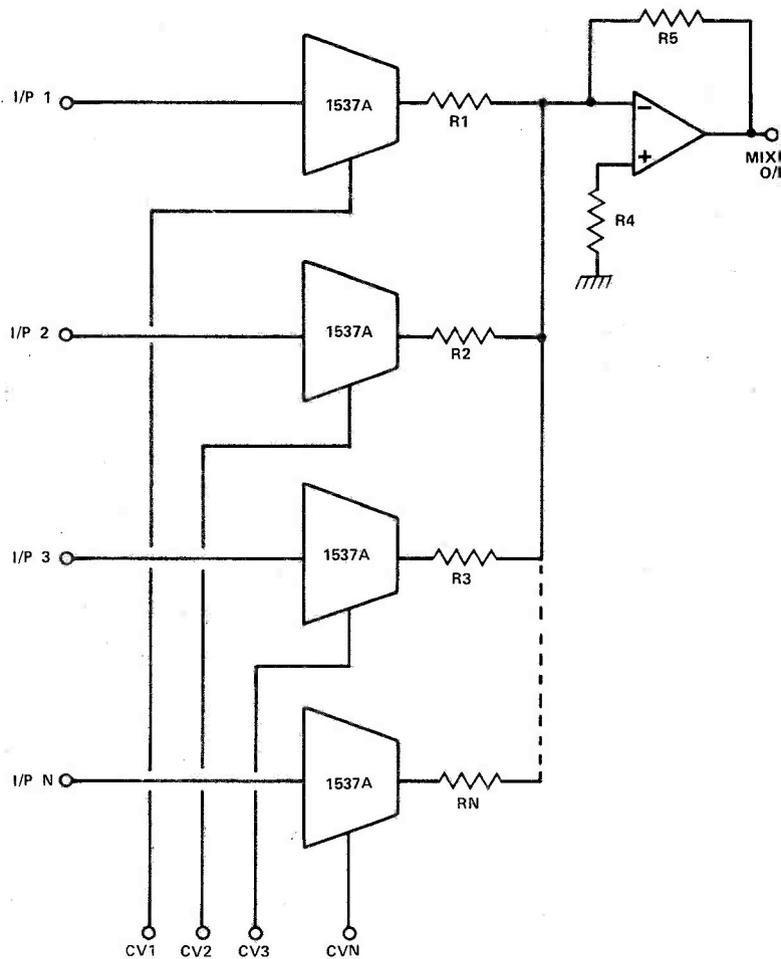


Fig. 12. High quality, remote fader controlled mixer.

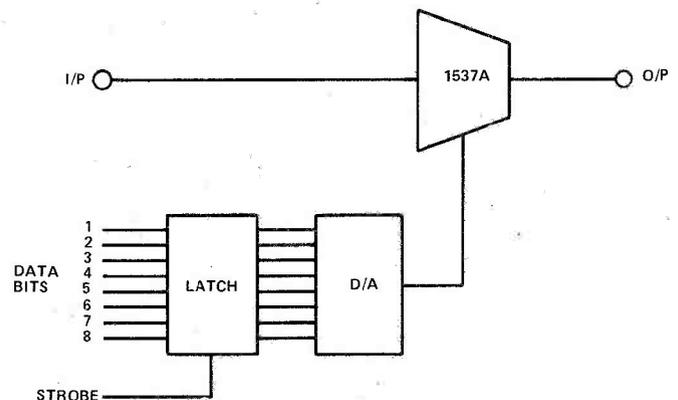


Fig. 13. Main components of a digitally controlled attenuator.

Applications

Consequently the next few circuits show the system in a much more versatile role — not just as an analogue gate, but one in where the system itself becomes part of a larger system. Figures 14 and 15 give details of circuit in which the 1537A module is used in the feedback loop of conventional operational amplifiers to allow voltage controlled ►

amplifiers to be constructed. The resistance values used give gains of approximately 1 to 100 over the VCA control voltage range and an inverting VCamp and a non-inverting VCamp can be easily built as shown.

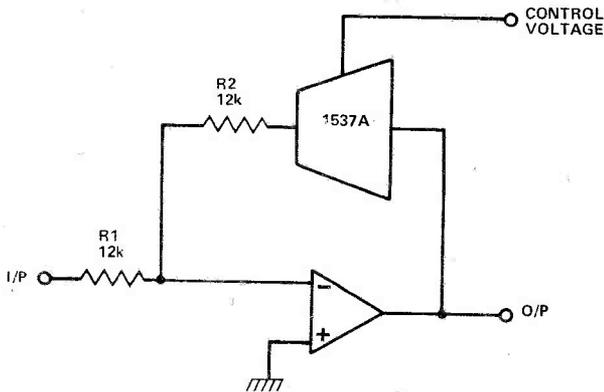


Fig. 14. A non-inverting controlled attenuator.

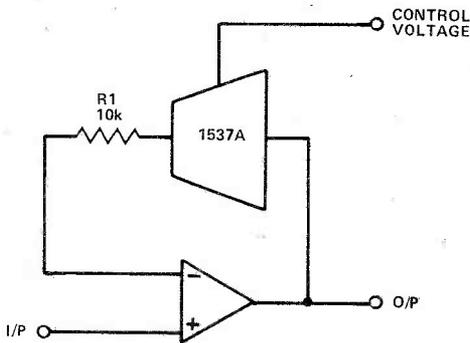


Fig. 15. An inverting voltage controlled amplifier.

A voltage controlled resistor is shown in the application of figure 16. The apparent resistance, R_1 , is given approximately by the formula

$$\frac{R_1}{1 - A}$$

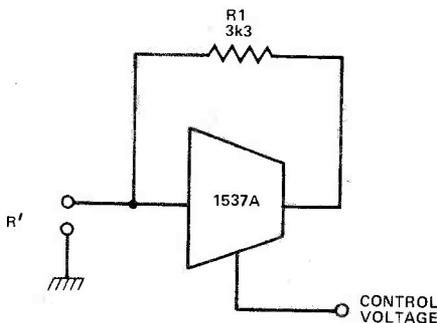


Fig. 16. A voltage controlled variable resistor.

where A is the gain of the VCA module (remembering that it has a maximum gain of unity). The value of R_1 shown gives an apparent voltage controlled resistance of 7 k to 100 k over the ten volt control voltage range.

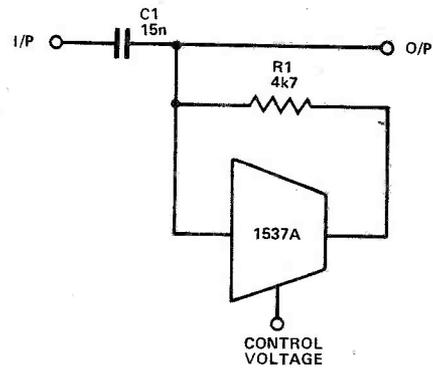


Fig. 17. A voltage controlled High Pass Filter.

The effect of a VCR (voltage controlled resistor) is used in the final two applications as the control element in filter circuits. Figure 17 shows a simple voltage controlled high pass filter. The component values shown filter out all frequencies below the variable limit of 1-2 kHz. Adjustment of the control voltage alters the lower cutoff point.

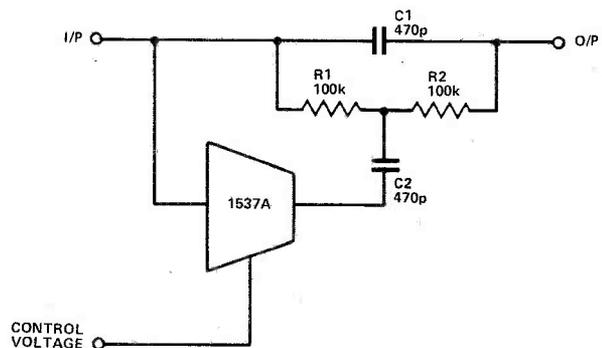


Fig. 18. A voltage controlled Band Reject (Notch) Filter.

Figure 18 consists of the circuit of a voltage controlled band reject or notch filter whose depth of notch is adjusted by the control voltage. The component values shown set the frequency at about 300 Hz and depth of notch is variable from 0 dB to about -15 dB.

Conclusions

The applications given in this article show the 1537A chip to be a very versatile device. It is remarkably easy to work with, a fact which is borne out by the quality (in technical terms) of the circuitry in the breadboarded fashion of our experimental design work, let alone in the modular fashion allowed by the use of our PCB layout. We can foresee many more applications of this device to come in the future. Thanks go to Aphex Audio Systems UK Ltd for their help in obtaining data on the 1537A. They are at present the only suppliers of the chip in this country and have kindly offered a 15% reduction in price to ETI readers quoting the code given in Buylines.

ETI

OLIVETTI PRINTER & KEYBOARD type Te 300

with PUNCH & READER. Upper case ASCII with V24 Interface. 240 volt operation.

£125 each

TELETYPE MODEL 390
with PUNCH & READER
£325 each

HONEYWELL VDU
1920 Character Upper Case ASC11. With edit and block transmission. Limited quantity with data
NEW LOW PRICE £200 each

BRUEL & KJOER EQUIPMENT

AUDIO FREQUENCY SPECTROMETER type 2112 **£175 ea.**
BEAT FREQUENCY OSCILLATOR type 1013 **£140**
BEAT FREQUENCY OSCILLATOR type 1014 **£140**
BEAT FREQUENCY OSCILLATOR type 1022 **£140**
AUTOMATIC VIBRATION EXCITER CONTROL type 1018 **£90**
AUTOMATIC VIBRATION EXCITER CONTROL type 1019 **£90**
AUTOMATIC VIBRATION EXCITER CONTROL type 1016 **£90**

RECORDERS with Paper **£85 each**

INFRA RED IMAGE CONVERTER type 9606 (CV 144)

1 3/4x2" diameter. Requires single Low current 3KV to 6KV supply. Individually boxed. With data
£12.50 each P&P 75p
Infra Red Lamps also advertised

STRATHEARN AUCTION — YES WE WERE LARGE PURCHASER OF COMPONENTS & TEST GEAR

The following is a selection from the purchases

BC327	8p	2N3704	8p	BT660	5p	MC1458	15p
BC327	8p	2N5447	5p	LM82CP	15p	LM3900	30p
BC251	5p	2N5448	5p	TIS92	10p	4013	30p
BC171A	5p	2N3053	15p	TIS93	10p	741	12p

Timer 555 **15p**
16 pin DIL Socket **10p**. 14 pin DIL Socket **8p**
LED type TIL 209 Red with holder **10p each**
SCLOTTED OPTO SWITCH supplied with data — normally over **£2**. OUR PRICE **75p each**
MICROSWITCHES SPCO — **12p each**. SP — **8p each**
ROCKER SWITCHES 2 pole c/o — **15p each**
Spring Action TERMINALS — normally over **30p ea.** OUR PRICE **15p each**
TOROIDAL TRANSFORMER 0-115V-230V Input. 13.5V — 0 — 13.5V rated 8VA output **£1.70 each**. P&P 75p
Sub-min TRANSFORMER 0-120-240V Input. 12V-0-12V rated 4VA Output **75p each** P&P 50p

ALL GOODS ARE GUARANTEED TO BE NEW AND FULL SPEC. DEVICES. **100 off discount 25%** — other discounts by arrangements.

POLARAD SPECTRUM ANALYSER

5" Display. These are supplied with STU 2 plug-in. 1 to 4.5GHZ.
£125 each

TELEQUIPMENT SERVICE SCOPE MINOR

Modern style — Small size 5x7x11" approx. Circuit diagram supplied.
£55 each

4K RAM

Signetics
22 pin with data type 2680

65p each

Four for £2

STEPPING MOTORS

6/12 position with additional where the rotor coils. Device can be used as a tach. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p or 5 for £5 P&P £1.50.

IF YOU CONSIDER THE PRICE ON ANY OF OUR ADVERTISED ITEMS TOO HIGH — PLEASE MAKE US AN OFFER WE CAN CONSIDER

TEKTRONIX Spectrum Analyser Plug-in 1L30 **£425 ea.**
TEKTRONIX 1A4 Plug-in **£325 ea.**
ADVANCE Oscilloscope type OS250 DB. DC-10MHZ **£225 ea.**
WOLKE WOV & FLUTTER METER ME105 **£175 ea.**
ADVANCE AC Voltmeter VM77E **£100 ea.**
HEWLETT PACKARD RMS Voltmeter type 3400A **£150 ea.**
MARCONI Spectrum Analyser type. TF1094, 100HZ to 30MHZ with 8HZ resolution 5" display. Complete with trolley **£75 ea.**
R&S GEN BN 41026 SCR 1000-19000MHZ **£120**
R&S GEN BN 41027/2 SBR 1700-2700MHZ **£140**
R&S GEN BN 41022 SDR 300-1000MHZ **£90**
R&S GEN BN 41023/2 SDAF AM/FM Video **£200**
R&S GEN BN 1524 USUV 0.9-2.7 GHz **£180**
R&S GEN BN 4105 SMLM Power Sig Source **£180**
R&S GEN BN 2412/50 NRD 0-3200MHZ **£120**
R&S GEN BN 4242 SWH 50KHZ-12MHZ **£120**
R&S POLYSKOP BN 4244 SWOB **£300**
R&S GEN BN 4105 SMLM 30-305 MHz **£75**
R&S GEN BN1523 USUV 280-340 MHz **£120 ea.**
R&S GEN BN4222 WID 30-300MHZ **£120**
FERROGRAPH Recorder Test Set RTS 2 **£350**
HEWLETT PACKARD Oscilloscope type 120B **£190**
HEWLETT PACKARD AC Converter type 3461A **£240**
HEWLETT PACKARD Synchronizer type 8708A **£250**
RACAL Auto Freq Converter 803R 500MHZ **£80**
COMU DC Voltage Standard 303B **£350 ea.**
AVO Precision meter **£75 ea.**
PVE Ph Meter Model 79 **£120**
POLARAD Sig source Model 1208A 7-11GHZ **£120**
FLUKE RMS Voltmeter type 910A **£50**
TELEVIC SWEEPER SM2000 0-1800MHZ in 3 plug-in units **£150**
WAYNE KERR Bridge CT 530 with adaptor **£150 ea.**
TELEVIC SWEEPER SO 3 450-900MHZ with markers **£65 ea.**
TWENTY MILLION Megohm meter Bby E.1. **£40 ea.**
AVO 8 Mk 3 or similar **from £50**
HEWLETT PACKARD Oscilloscope type 140A with Reflector-meter plug-in **£250**
MARCONI type TF801D/1 **£150**
COSOR CDU130 small, compact main/battery Oscilloscope. Batteries supplied **£240**
LABGEAR UHF/VHF PAL Colour Bar Gen. CM6052/CB **£90 ea.**

MARCONI GEN TF1066B **£350**
RANK FLETTER Meter type 1740 **£50 ea.**
AVO Sig Gen HF135/Taylor 68A/M **£120 ea.**
TEK scope 545A with H plug-in **£125 ea.**
TEK scope 545A with CA plug-in **£175 ea.**
H.P. scope 175A 50MHZ Dual trace **£175 ea.**
Single Trace **£125 ea.**
WAYNE KERR Universal Bridge CT375 **£75 ea.**
MARCONI Wave Analyser TF2330 **£500 ea.**
NOISE GENERATOR CT410 — covers audio to VHF **£8 ea.**
RAGARD Pulse Generator 5002C **£50 ea.**
MARCONI Wave Analyser type TF455E **£40 ea.**
SOLAARON DVM LM1420 with AC unit LM1477 **£1,500**
CALCOMP Drum Plotter type 564 **£120**
MARCONI Bridge TF868B **£25 ea.**
VARIACS EX-Equipment Good condition 8 Amps **£35 ea.**
20 AMPs
Some 3 phase available. Please enquire.
CARRIAGE ALL UNITS **£4 ea.**

CRYSTALS
19.2KHZ FLAT METAL CASE — **50p each.**
10 MHZ B7G **50p each.**

EX-NAVAL 4th dia STEEL DISHES. NEW CRATED. 1 ft deep at centre. These are plain steel dishes with holes for various aerial options. **£22.50 ea.** Carriage **£4.**

LISTS AVAILABLE — WRITE OR PHONE.

TRANSFORMERS — Standard Mains input.

Secondary outputs.
6KV 125A **£15 ea.**
3440V 0.66A with matching 40H Choke **£30 the pair.**
8V 600 Amps **£25.**
5KV 300MA **£15.**
12KV 30MA **£20.**
3KV 50MA **£8 ea.** 4 Volts 250 Amps **£10 ea.**
18KV 30MA **£80.**
22.5KV 110MA **£50 ea.**
60KV 0.0273 **£150.**
Input 200V 50HZ Sec 100KV 0.05 **£150.**
MULTI PURPOSE MAINS TRANSFORMER 4 windings each winding 0-10-110-125 at 4 BA **£18 ea.**
42.5V 50HZ 2 Wire Input. Output 8.5KV 2.55KVA. Could be run on 240V at 1/2 rating **£15 ea.**
STEP DOWN ISOLATING TRANSFORMER. Input 220, 250V 50HZ Output 115V 1.8KVA BRAND NEW. These are very conservatively rated **£20 ea.**
CAPACITORS
10mfd 10KV DC Working **£4 ea.**
2mfd 5KV **£4 ea.**
0.5 mfd 5KV **£4 ea.**
200mfd 4KV Rapid discharge **£10 ea.**
0.5 mfd 10KV **£4 ea.**
5 mfd 2 KV **£4 ea.**
CARRIAGE on these units will be charged at cost.

INFRA RED QUARTZ LAMPS. 230V 620Watts. Size 1 3/4" x 3/4" dia. **£1.50**. P&P 50p.
BRIDGE RECTIFIER. 2 Amp **50p ea.**
PHOTODIODE DETECTOR 4" fly leads, **25p ea.**
A SUPERIOR KEYBOARD. Size 3 x 2 1/2" x 2" high with 12 Alpha Reed Switches. Blue keys marked in green 0-9 and a star with one black. NOW **£4 ea.** P&P 75p.
AMPHENOL. 17-way chassis mount edge connectors 0.1 spacing. **15p ea.**
I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) **50p ea.** P&P 50p.
FANS. 115V 13 Watts. Size 3 1/4 x 3 1/4 x 1 1/2" BRAND NEW. **£4.50 ea.** Secondhand **£2.50 ea.** P&P 75p.
MOTOROLA REGULATORS. type 7812 12V 1 amp **85p ea.**
Miniature MOTORS 12V with geared wheel (8 teeth 3/16" dia). Size 1 1/4 x 3/4" dia. New **30p ea.**
MOTOR 12V DC with pulley and integral semiconductor Speed Control. New **£1 ea.** P&P 50p.
LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. **15p ea.**
DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New **10p ea.**
DELAY LINE. 50 nanosecs. 3 connections, ground-in-out. Size 2 x 7/16 x 1 1/8". New **25p ea.**
PULSE TRANSFORMER. Sub min. Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New **20p ea.**
MOTOR by Inland Motor Corp. DC High Torque. Reversible. Usable torque at 5V. Max voltage 24V **£2.50 ea.** P&P £1.
REMOT TYPE MULTIPLIER. Two high voltage outputs and focus **£2 ea.** P&P £1.
DON'T TAKE CHANCES. Use the proper EHT CABLE. **10p per metre or £7.50 per 100 metre/drum.** P&P £1.50.
MOTOR by Eastern Air Devices Inc. 125V reversible with toothed shaft (10 teeth 1/4" dia). Size 2 1/4 x 2 1/4" dia **75p ea.** P&P £1.
PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap **75p ea.** Box of 12 **£5.50** P&P £1.50.
Decoupling CAPACITORS 0.05mfd 10V. Size 0.25" between leads 1/4" height. **100 for £1** P&P 50p.
CAPACITORS 0.01mfd. Size 5/16" between leads. 1/2" height. **100 for £1** P&P 50p.
MYSTERY IC PACK. Some 40 pin — good mixture — all new devices. **25 ICs for £1**. P&P 50p. You find out what they are and we will buy the information from you.
SUPERB 19" RACK CABINET. Approx 4" 6" high x 33" deep. Instrument front panel position can be adjusted. Chocolate colour. These are new but have slight scratches and imperfections — hardly noticeable. **£35 each**. Car. **£4**
VACUUM PUMPS — TRAPS, ETC. Send for list.
10-Way Multi-Colour Ribbon Cable. New. **40p per metre**. P&P 50p.
SPEAKERS 2 1/2". 50 ohm 0.2W. New **40p each**. P&P 50p.
RAPID DISCHARGE capacitors 5mfd 4KV. **£5 each**. P&P £1.50.

GECH UHF 4 button tuner. **£2.50 each**. P&P 85p.
BIG INCH MOTOR 110V AC 3 rpm 50 cycle. Very small **50p each**. P&P 50p.
CENTAUR 115V AMS. 4.5 x 4 x 1 1/2" **£4.50 each**. P&P 75p.
EX-USED Equipment, tested **60p each**. P&P 75p.
POTTER & BRUMFIELD TIMER RELAY, 115V AC. Heavy duty, 7 pole c/s with 2 second delay Charge R & C for different timing **50p each**. P&P 85p.
CONTRACTORS. Heavy Duty 24V DC 5 brake **£1 each**. P&P 85p.
GECH UHF/VHF 6 button tuner **£4.50 each**. P&P £1.
DIGITAL 24-HOUR CLOCK with built-in alarm as used in Braun Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 9 1/2 x 2 1/4 x 2 1/4". **ONLY £3.75 each**. P&P 50p.
931A PHOTO MULTIPLIER in stainless steel container with window and built-in resistor network. **£2 each**. P&P £1.
SLIDER CONTROL 500W. Log Single track. Complete with knob. Length 3 1/2". **25p each**. P&P 25p.
RANCO 250V 1A THERMOSTATS with Control knobs calibrated 50-200 degrees F. **£2.50 each**. P&P £1.
SOLID STATE UHF TUNERS. 30 acc **£1 each**. P&P 75p.
BRAND REX blue wire wraps. 30 metres for **£1**. P&P 25p.
5in SOLID RUBBER RINGS (1" dia. rubber). Keep the kids (or dog) happy. **4 for £1**. P&P £1.25.

TRANSFORMERS
AUTO 240V Input 115V. 1 Amp output **£1.25 each**. P&P £1.25.
240V Input Soc. 8V. 1.86A 8kw. Size 2 1/2 x 2 x 2". Good quality. **£1.50 ea.** P&P £1.
240V Input Soc. 12V 0.92A. Size 2 1/2 x 2 x 2". Good quality. **£1.50 ea.** P&P £1.
240V Input 12V 100MA. Size 60 x 40 x 42mm **50p each**. P&P 75p.
240V Input Soc. 12V-12V 50MA. Size 53 x 45 x 40mm. **£1 each**. P&P 75p.
115V Input Soc. 5V 250MA. Size 1 1/8 x 1.5 x 1 1/4" **2 for 50p**. P&P 75p.

SEMICONDUCTORS
At 7p each.
1M3063 1544.
At 5p each.
BC147, BC148B, BC157, BC158, BC237, BF1197, OA90, OA81, BA154, BA243.
At 25p each.
TIP31 TIP41A 2N5296, AF139, 2TX341
BY 123 10p. BF181 20p. BD239 40p. BD241 40p. MA343AT 40p. BD228 50p. BD233 & BD234 Comp Pair 25W — **80p per pair** at 50p each.
Regulator TBA35 8 to 20V in — 5V out 180MA TDS Con. **50p each**. BF266C 20p.
TV AMPLIFIER TBA 120 **20p each**.

Integrated Circuits
7453 **5p** 709 **15p** 75325 **£1**
7451 **5p** 74474 **12p** SN15862 **4p**
7401 **5p** 74H51 **7p** MC4028 **50p**
7402 **12p** 74538 **10p** 74717 **14p**
7476 **20p** 74502 **12p** 7441 **40p**
7495 **35p** 74154 **70p**

MOTOROLA DUAL in Line 6 pin Opto Coupler **30p each**. Gold plate tester version **80p each**.
AN640 4K RAMS STATIC 5 Volt ceramic **£4 each**.
7206 **£5.50 each**. P&P 25p.
TELEPHONES. 706 style Black or Grey. **£5.50 each**. 746 style Black or Grey **£7.50 each**. Older style Black **£2.50 each**. Postage **£1 each**.
Honeywell humidity Controllers **50p each**. P&P 40p.
THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in plastic relay case. Standard 7 pin base. Series delay **80p each**. P&P 85p.
MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3-way **10p each**.
DIGITAL to ANALOGUE CONVERTER. 8 bit will fit standard ITI socket. With data. **£2.50 each**. P&P 25p.
VARIACS. 2 amp Standard 240 Volts **£10 each**. P&P £1.50.
ELECTROSTATIC VOLTMETERS. 7.5KV **£5 each**. P&P £1.
Other ranges available. Please enquire.
TRIMMERS. Sub min 0.25 to 1.25pf. 1 to 45pf. 7 to 45pf. **All at 8p each**.
CROWN replacement MOTOR for IBM GOLFBALL TYPEWRITER 115Volt 50HZ 1350 rpm. **£4.50 ea** P&P £1.50.

Minimum order **£3** value of goods. P&P or Carriage and VAT at 15% on total must be added to all orders.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome

CHILTMHEAD LTD

NORWOOD ROAD, READING. TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")

ETI MARKET PLACE



1 CLOCK RADIO

How about a round clock radio which can double as a very smart desk clock — as we can testify!

To time, rotate one end of the cylinder to display the frequency selected. Most of the functions are controlled by a push-button panel and the display is a large, clear LCD affair.

Made by Hanimex, the battery clock radio comes in white, white or white. It will lull you to sleep and then turn itself off an hour later and waken you to the sound of Radio 1, or music if you prefer.

£17.95

To CLOCK RADIO offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

2 DIGITAL ALARM

This mains-only Hanimex alarm has a large 12-hour display incorporating AM/PM and alarm set indicators. You can have a dim or bright display at the touch of a switch. Fast and slow setting buttons make time setting simplicity itself. You can forget about knocking these accidentally in the morning scramble to turn off the alarm, as a locking switch is fitted under the clock. A 9-minute snooze switch completes the list of all mod. clock cons.

£10.60

To: DIGITAL ALARM offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

3 LCD CHRONO

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

The LCD display shows seconds as well as hours and minutes. Press a button and you get the date and day of the week.

Press another button and you have an accurate stopwatch with hundredths of seconds displayed, giving the time up to an hour. There's a lap time facility, too — and of course a back light.

£11.95

To: LCD WATCH offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

4 LCD ALARM CHRONO

This is no ordinary watch. It's a slim, multi-function, dual time LCD alarm chronograph.

This model will show hours, minutes, seconds, date, day of the week, stopwatch, split time, alarm and alternate dual time zone — not all at once of course. There's a night light, too.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The alarm is beefy enough to wake you up in the morning and get you to work on time (or wake you up when it's time to go home).

£16.95

To: ALARM/CHRONO LCD WATCH offer
ETI Magazine, 145 Charing Cross Road
London, WC2

Name

Address

All prices include 15% VAT and postage

Examples of Marketplace offers can be seen at our Charing Cross Road offices.

Please mark your envelope with the offer that you want and order separately from offers shown elsewhere in ETI.

STEVENSON

Electronic Components

CMOS			
4001	13p	4020	50p
4002	13p	4022	50p
4007	13p	4023	13p
4009	30p	4024	40p
4011	13p	4025	13p
4012	13p	4026	90p
4013	28p	4027	28p
4015	50p	4028	45p
4016	28p	4029	55p
4017	47p	4040	55p
4018	55p	4041	55p
		4042	55p
		4043	50p
		4044	50p
		4049	25p
		4050	25p
		4060	80p
		4066	30p
		4068	13p
		4069	13p
		4070	13p
		4071	13p
		4072	13p
		4081	13p
		4093	36p
		4510	60p
		4511	60p
		4512	65p
		4518	60p
		4528	60p

FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	7475	20p
7401	10p	7476	20p
7402	10p	7485	55p
7404	12p	7486	20p
7406	22p	7489	135p
7408	12p	7490	25p
7410	10p	7492	30p
7413	22p	7493	25p
7414	30p	7494	45p
7420	12p	7495	35p
7427	20p	7496	45p
7430	12p	74121	25p
7432	18p	74122	35p
7442	38p	74123	38p
7447	45p	74125	35p
7448	50p	74126	35p
7454	12p	74132	45p
		74141	55p
		74145	55p
		74148	90p
		74150	55p
		74151	40p
		74154	65p
		74157	40p
		74164	55p
		74170	100p
		74174	55p
		74177	50p
		74190	50p
		74191	50p
		74192	50p
		74193	50p
		74196	50p
		74197	50p
		74199	90p

OPTO			
LED's	0.125in.	0.2in	each 100+
Red	TIL209	TIL220	9p 7.5p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	
DISPLAYS			
DL704	0.3 in CC		130p 120p
DL707	0.3 in CA		130p 120p
FND500	0.5 in CC		100p 80p

SKTS			
8pin	8p	18pin	14p
14pin	10p	20pin	16p
16pin	11p	22pin	17p
24pin	18p	28pin	22p
32pin	22p	40pin	32p
3 lead T018 or T05 socket. 10p each			
Soldercon pins: 100:50p 1000:370p			

PCBS			
Size in.	VEROBOARD		
2.5 x 1	0.1in. 0.15in.	Vero	
2.5 x 3.75	14p	Cutter	80p
2.5 x 5	45p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	
Single sided pins per 100 40p 40p			
Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.			
'Dalo' pens. 75p each.			
Five mixed sheets of Alfac. 145p per pack.			

RESISTORS			
Carbon film resistors. High stability, low noise 5%.			
E12 series. 4.7 ohms to 10M. Any mix:			
0.25W	each	100+	1000+
	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.			
METAL FILM RESISTORS			
Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix:			
0.25W	each	100+	1000+
	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS. OVER 2500 ITEMS LISTED.



LINEAR			
LF356	80p	NE531	98p
LM301AN	26p	NE555	23p
LM308	60p	NE566	60p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	TBA800	70p
LM379S	410p	TBA810S	100p
LM380	75p	TD1022	620p
LM3900	50p	TL081	45p
LM3909	65p	TL084	125p
LM3911	100p	ZN414	80p
MC1458	32p	ZN425E	390p
MM57160	590p	ZN1034E	200p


TRANSISTORS			
AC127	17p	BCY72	14p
AC128	16p	BD131	35p
AC176	18p	BD132	35p
AD161	38p	BD139	35p
AD162	38p	BD140	35p
BC107	8p	BFY50	15p
BC108	8p	BFY51	15p
BC108C	10p	BFY52	15p
BC109	8p	MJ2955	98p
BC109C	10p	MPSA06	20p
BC147	7p	MPSA56	20p
BC148	7p	TIP29C	60p
BC177	14p	TIP30C	70p
BC178	14p	TIP31C	65p
BC179	14p	TIP32C	80p
BC182	10p	TIP32C	80p
BC182L	10p	TIP2955	65p
BC184	10p	TIP3055	55p
BC184L	10p	ZTX107	14p
BC212	10p	ZTX108	14p
BC212L	10p	ZTX300	16p
BC214	10p		
BC214L	10p		
BC477	19p	1N914	3p
BC478	19p	1N4001	4p
BC548	10p	1N4002	4p
BCY70	14p	1N4006	6p
BCY71	14p	1N4010	4p
		1N5401	13p
		BZY88 ser.	8p
		ITT Full spec. product.	
		1N4148	£1.40/100.

CAPACITORS			
TANTALUM BEAD			
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V			each 8p
4.7, 6.8, 10uF @ 25V			13p
22 @ 16V, 47 @ 6V, 100 @ 3V			16p
MYLAR FILM			
0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1			3p
			4p
POLYESTER			
Mullard C280 series			
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1			5p
0.15, 0.22			7p
0.33, 0.47			10p
0.68			14p
1.0uF			17p
CERAMIC			
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF			2p
RADIAL LEAD ELECTROLYTIC			
63V 0.47 1.0 2.2 4.7 10			5p
	22 33 47		7p
			13p
			20p
25V 10 22 33 47			5p
			8p
			10p
			15p
			23p

CONNECTORS			
JACK PLUGS AND SOCKETS			
2.5mm	unscreened	screened	socket
3.5mm	9p	13p	7p
Standard	9p	14p	8p
Stereo	16p	30p	15p
	23p	36p	18p
DIN PLUGS AND SOCKETS			
	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p
1mm PLUGS AND SOCKETS			
Suitable for low voltage circuits. Red & black. Plugs: 6p each Sockets: 7p each.			
4mm PLUGS AND SOCKETS			
Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each			
PHONO PLUGS AND SOCKETS			
Insulated plug in red or black			9p
Screened plug			13p
Single socket	7p	Double socket	10p

SPECIAL OFFERS

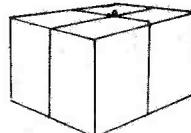A range of special offer items valid during February. All orders placed for these items must be received during February.



Pack of 3 x LM380	225p	200p
Pack of 30 x 1N4001	120p	100p
Pack of 4 x FND500	400p	350p
Pack of 15 x 2N3702	120p	100p
Pack of 15 x BC107	120p	100p
Special pack of nuts + bolts containing over 600 4BA + 6BA nuts, bolts and washers	330p	250p
Pack of 4 red + 4 black crocodile clips	64p	50p
Mixer control knobs, per 100 (mixed) colours to suit	1400p	1300p

MULTIMETERS


A really smart looking multimeter with an impressive specification for such a small size. The very clean scale in white and green on a black background makes this meter very easy to read. The D.C. Impedance of this meter is 4K ohms per volt which is exceptionally good compared with the vast majority of multimeters of a similar size. £5.95 each.



SPECIFICATION

DC Volts	5V 25V 250V 500V (4K ohms/V)
AC Volts	10V 50V 500V 1000V (2K ohms/V)
DC Current	250uA 250mA
Resistance	0 - 600K (7K ohms centre)

PANEL METERS

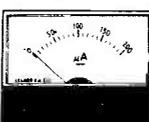

High quality 2" wide view meters. Zero adjustment. Back illumination wiring. Available in 50 uA, 100 uA, 500 uA, 1mA, 100mA, 500mA, 1A. £4.95 ea. VU meter similar style. £1.50 ea.

SLIDE POTENTIOMETERS

Good quality 60mm travel slider with 80mm fixing centres. Available from 5k - 500K in log and linear. 55p each. Suitable black knobs 6p ea. Coloured knobs 10p ea.



We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 50p for P & P, no charge for orders over £15. Official orders welcome. All prices valid to April 1980.



BARCLAYCARD & ACCESS WELCOME.



Mail orders to: STEVENSON (Dept ET)

76 College Road, Bromley, Kent BR1 1DE.



DESIGNER'S NOTEBOOK

ETI's chief design engineer, Ray Marston, discusses the use of CMOS counter/divider ICs.

A common task facing the electronics design engineer is that of producing simple digital counter/divider networks, which produce an output frequency or count rate that is some fixed fraction of the original input frequency or count rate. This month's "Notebook" discusses the use of CMOS ICs in such applications.

4013 and 4027 Flip Flops.

The two most basic counter/divider ICs in the CMOS range are the 4013 dual D-type flip-flop and the 4027 dual J-K flip-flop. Figure 1 shows the outlines and pin notations of these two devices, which each contain two independent flip-flop stages sharing common supply connections. Each of these packages can be used to give division ratios of 2, 3 or 4.

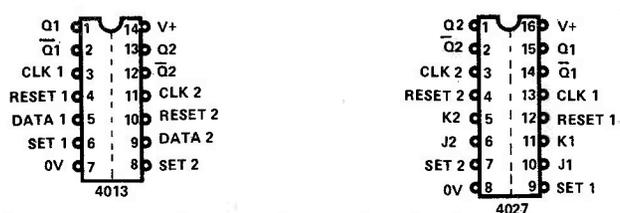


Fig. 1. Outlines and pin notations of the 4013 dual D and the 4027 dual J-K CMOS flip-flops.

A single 4013 'D' stage can be made to act as a divide-by-two counter by grounding its SET and RESET pins and coupling its DATA pin to its Q output, as shown in Fig. 2a. A single 4027 J-K stage can be made to act as a divide-by-two counter by grounding its SET and RESET pins and connecting its J and K pins to the positive supply rail, as shown in Fig. 2b. Both of these circuits change state on the positive-going transition of the input clock signal, which must have rise and fall times of less than 5 uS. The 4013 is very fussy about the shape of its input clock signals and tends to be rather temperamental in operation. The 4027 is not too fussy about its clock signals and is very easy to work with.

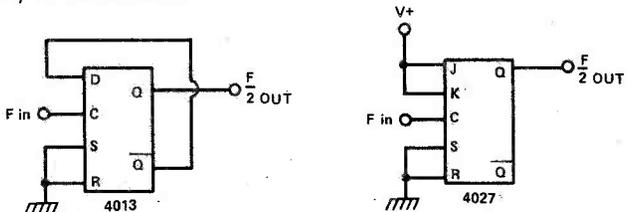


Fig. 2. Divide-by-two counters made from D-type (left) and J-K (right) flip-flop stages.

Ripple Counters

Figure 3 shows how two divide-by-two 'D' or J-K flip-flop stages can be wired in series to give an overall division ratio of four (2²). Fig. 4 shows how three such stages can be

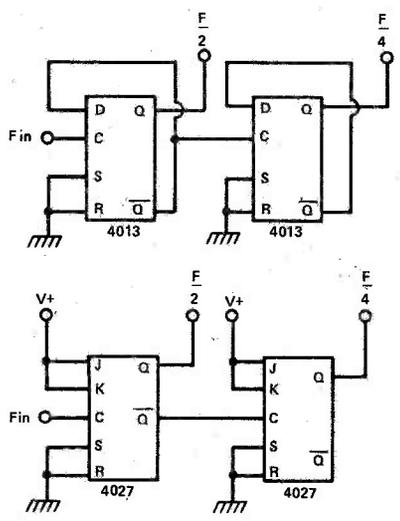


Fig. 3. D and J-K versions of divide-by-four ripple counters.

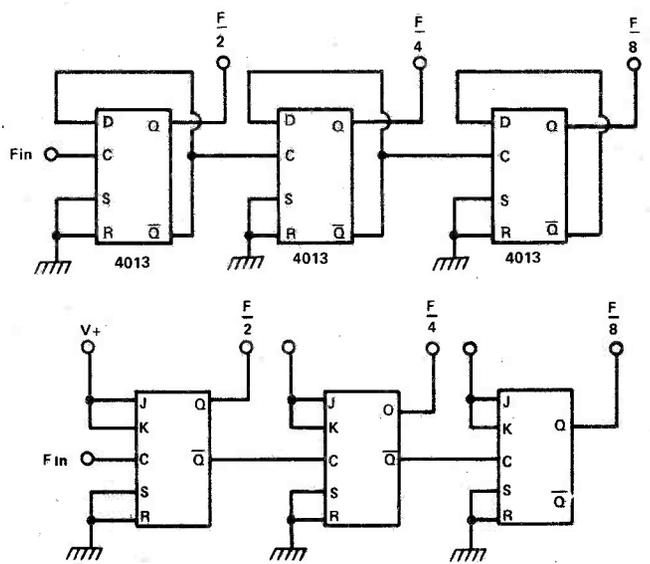


Fig. 4. D and J-K versions of divide by eight ripple counters. ▶

wired in series to give a division ratio of eight (2^3). Note that each counter stage is clocked at precisely half the rate of (an octave below) the preceding stage, so that the clock signal seems to 'ripple' through the counter chain. Also note that, as is made clear in Fig. 5, the final division ratio is equal to 2^n , where 'N' is the number of counter stages. Thus, four stages give a ratio of $2^4=16$, five stages give $2^5=32$, six give $2^6=64$, seven = 128 and so on.

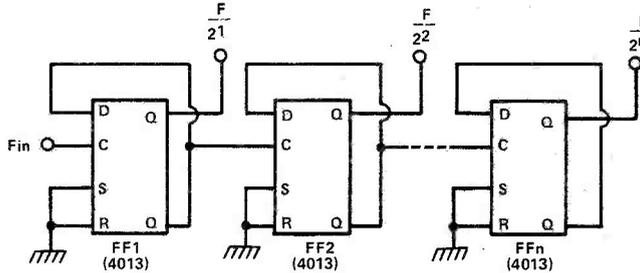


Fig. 5. D version of divide-by- 2^n ripple counter.

A detail not made clear in the above diagram is that, since the counters of a 'ripple' circuit are effectively wired in series, the propagation delays of the individual stages in the counting chain add together to give a fairly long total delay at the end of the chain. If each stage has a delay of 100 nS and there are ten stages, the total propagation delay is 1 μ S. Consequently, the final output signal will not change state until 1 μ S after the arrival of the original input clock signal that initiates that change of state. The counter states of the 'ripple' type of counter are thus not in perfect synchrony with the original clock signal and this type of circuit is consequently known as an asynchronous counter.

4013 and 4027 counters can be cascaded to give any desired number of ripple stages. When more than two stages are required it is usually economic, however, to use a special-purpose MSI ripple-carry binary counter/divider IC. Figure 6 shows the outlines and functional diagrams of three popular ICs of this type.

The 4024 is a seven-stage ripple unit with all seven outputs externally accessible: it gives a maximum division ratio of 128. The 4040 is a twelve-stage unit with all twelve outputs accessible: it gives a maximum division ratio of

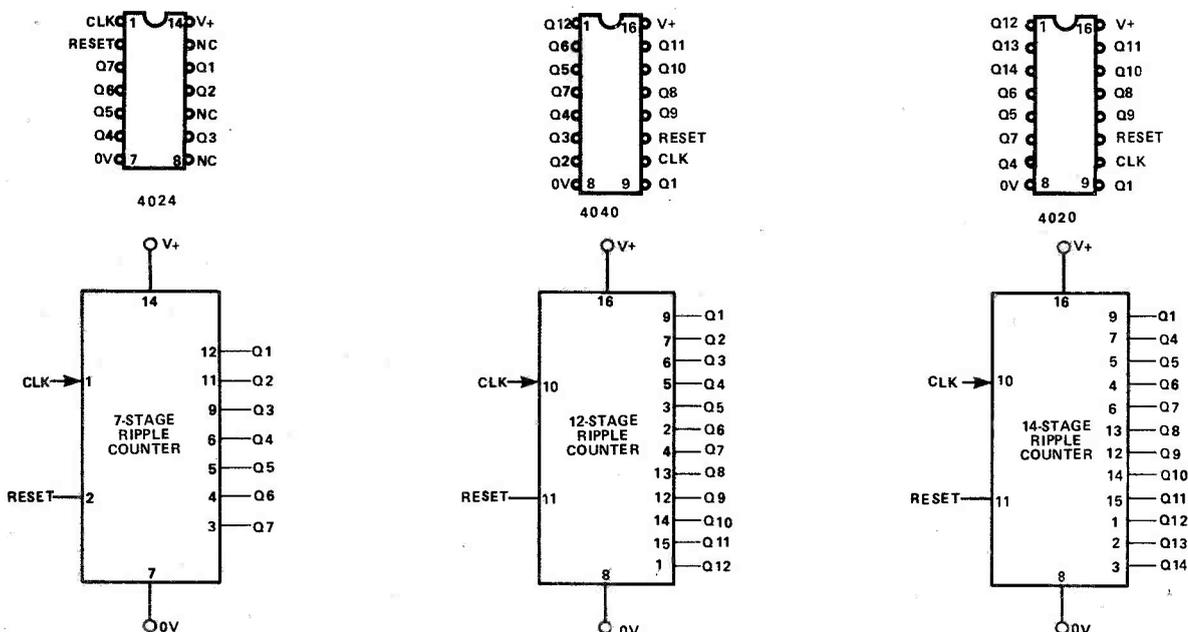


Fig. 6. Outlines (above) and functional diagrams (below) of three popular CMOS multi-stage ripple counters.

4096. The 4020 is a fourteen-stage unit with all outputs except 2 and 3 externally accessible: it gives a maximum division ratio of 16 384.

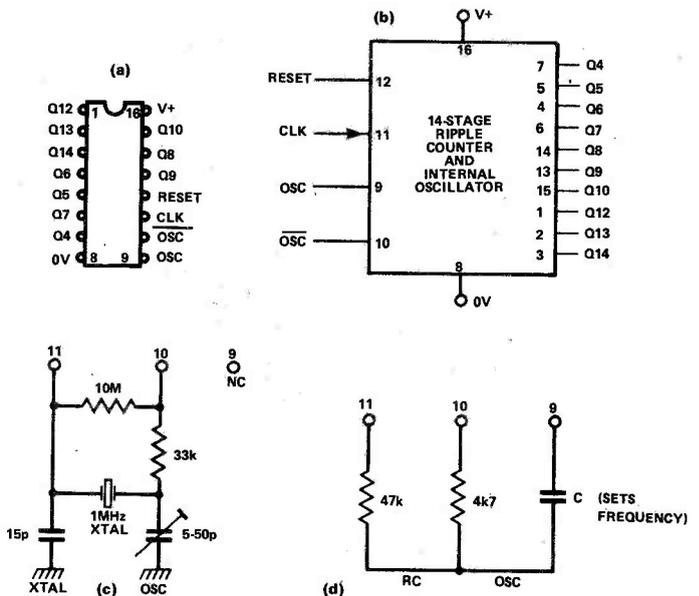


Fig. 7. Outline (a), functional diagram (b), and alternative oscillator connections (c and d) of the 4060 fourteen-stage ripple counter.

Fig. 7 shows the outline and functional diagram of a special-purpose ripple-carry unit, the 4060. This is another fourteen-stage unit, but does not have outputs 1, 2, 3 or 11 externally accessible. The special feature of the 4060 is that it incorporates a built-in clock oscillator circuit. The diagram shows the connections for using the internal circuit as either a crystal or an RC oscillator.

The 4020, 4024, 4040 and 4060 ICs are all provided with Schmitt trigger action on their input terminals and trigger on the negative transition of each input pulse. All counters can be set to zero by applying a high level on the RESET line.

'Walking Ring' or 'Johnson' Counters

An alternative to the ripple type of counter is the so-called 'walking ring' or 'Johnson' counter. In these counters, all counter stages are clocked in parallel and the stages are cross-coupled so that the response of one stage to a clock pulse depends on the states of the other stages. Fig. 8 shows the connections for making a divide-by-three counter from two J-K stages and Fig. 9 shows the connections for making a divide-by-five counter.

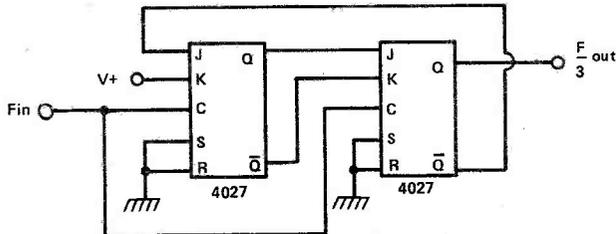


Fig. 8. J-K version of a divide-by-three 'walking ring' or 'Johnson' counter.

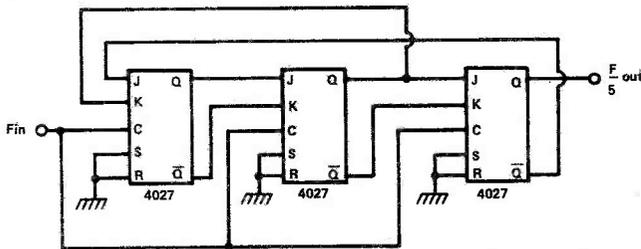


Fig. 9. J-K version of a divide-by-five 'walking ring' or 'Johnson' counter.

A major advantage of the 'walking ring' or 'Johnson' counter is that, since all stages are clocked in parallel, the outputs of the completed counter are subjected to only a single stage of propagation delay. Consequently, the system gives synchronous operation and outputs give glitch-free decoding.

4018 Divide-by-N Counter

When count numbers greater than four are required, it is economic to use MSI ICs such as the 4018, rather than the 4013 or 4027. The 4018 is a five-stage 'Johnson' counter that can be made to divide by 2, 3, 4, 5, 6, 7, 8, 9 or 10 by merely cross-coupling its terminals in suitable ways. The IC features a Schmitt trigger on its clock input line and clocks on the positive transition of the input signal.


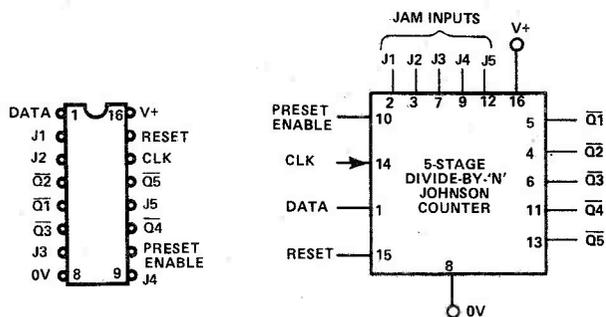
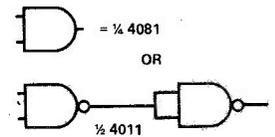


Fig. 10. Outline and functional diagram of the 4018 presetable divide-by-N counter.

Figure 10 shows the outline and functional diagram of the 4018. Fig. 11 gives methods of cross-coupling the IC to give division ratios from two to ten. On even division,

ratios, no additional components are needed. On odd ratios, a two-input AND gate is required in the feedback network. This gate can be a single 4081 AND stage, or can be made from two 4011 NAND stages.

- DIVIDE-BY-2 = $\overline{Q1}$ TO DATA
- DIVIDE-BY-3 = $\overline{Q1} \overline{Q2}$ TO DATA
- DIVIDE-BY-4 = $\overline{Q2}$ TO DATA
- DIVIDE-BY-5 = $\overline{Q2} \overline{Q3}$ TO DATA
- DIVIDE-BY-6 = $\overline{Q3}$ TO DATA
- DIVIDE-BY-7 = $\overline{Q3} \overline{Q4}$ TO DATA
- DIVIDE-BY-8 = $\overline{Q4}$ TO DATA
- DIVIDE-BY-9 = $\overline{Q4} \overline{Q3}$ TO DATA
- DIVIDE-BY-10 = $\overline{Q5}$ TO DATA

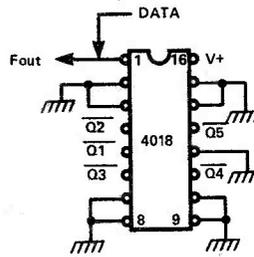

CONNECTIONS FOR DIVIDE-BY-N OPERATION

Fig. 11. Methods of connecting the 4018 for divide-by-two to divide-by-ten operation.

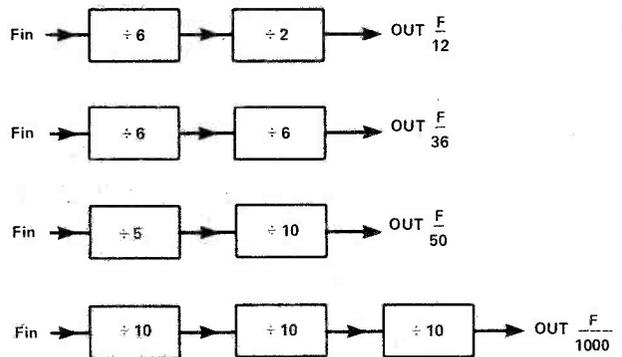


Fig. 12. Typical examples of division by numbers greater than ten.


Greater-Than-Ten Division

Even division ratios greater than ten can usually be obtained by simply cascading suitably scaled counter stages, as show in Fig. 12. Thus, a divide-by-two and a divide-by-six stage give a ratio of twelve, a divide-by-six and a divide-by-six give a ratio of 36 and so on. Non-standard and uneven division ratios can be obtained by using standard counters such as the 4018 and decoding their outputs to generate suitable counter-reset pulses on completion of the desired count.

ETI

Simply ahead . . .

ILP'S NEW GENERATION OF HIGH

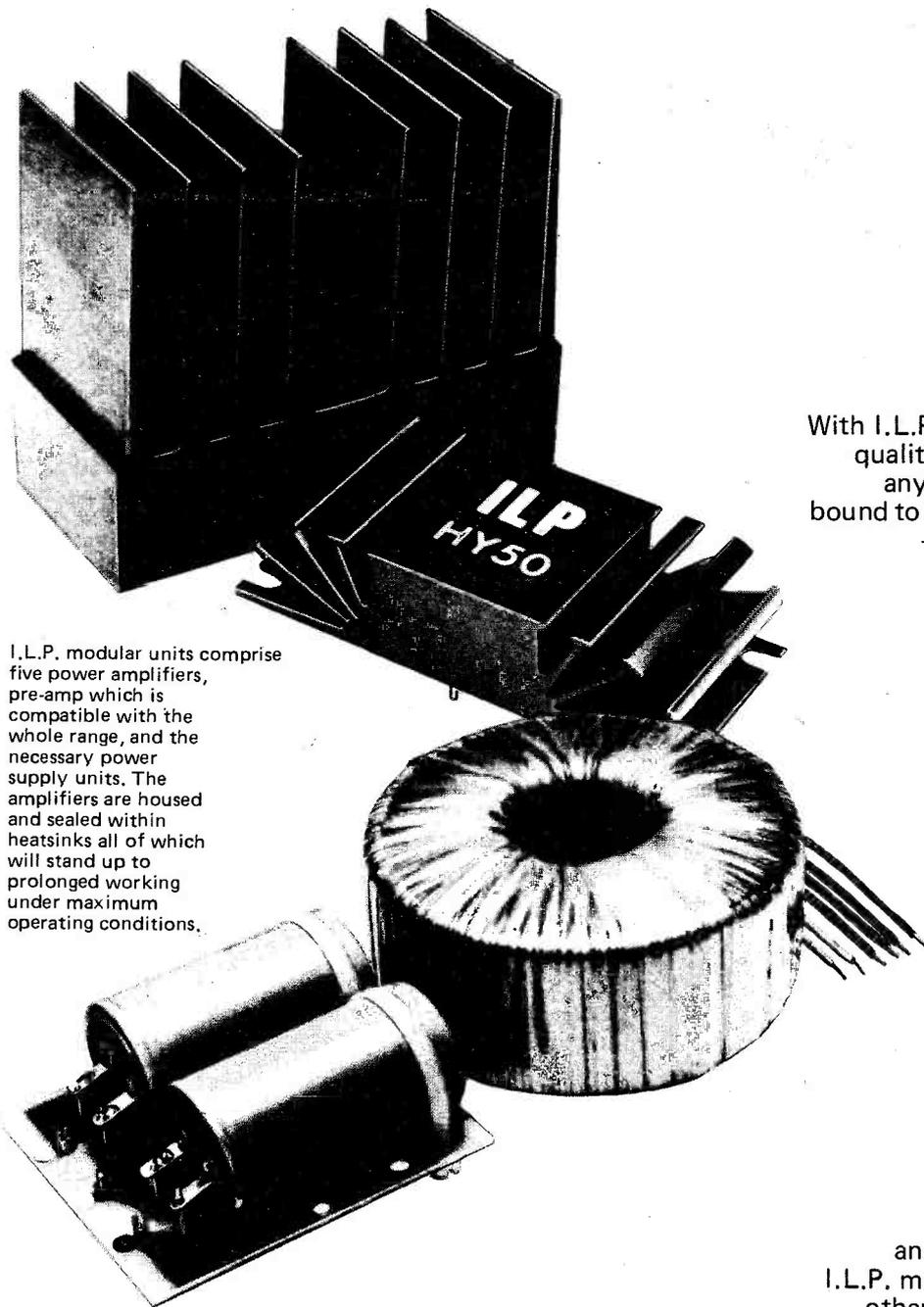

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.

With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance — and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain — the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.



**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

ALSO AVAILABLE FROM A NUMBER OF SELECTED APPOINTED STOCKISTS

and staying there

PERFORMANCE MODULAR UNITS


HY5 PRE-AMPLIFIER

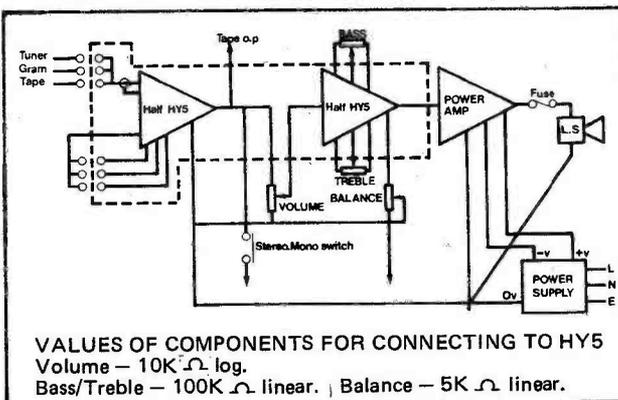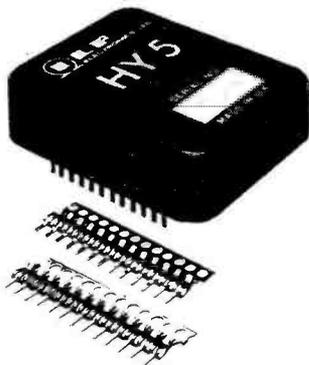

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm, and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

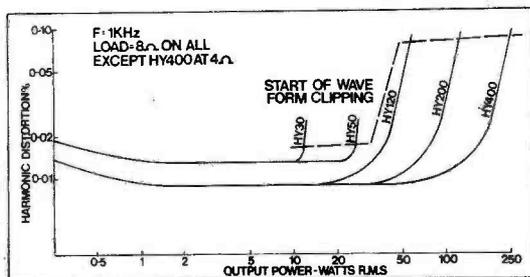

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0 +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance — all models 4 - 16 Ω
 Input sensitivity — all models 500 mV
 Input impedance — all models 100K Ω
 Frequency response — all models 10Hz - 45Hz - 3dB

THE POWER SUPPLY UNITS

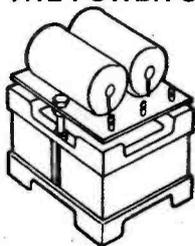

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	$\pm 15V$ at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

**NO QUIBBLE
 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 INTEGRAL HEATSINKS
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE
 —see below**

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



I.L.P.

ELECTRONICS LTD.

FREEPOST 4, Graham Bell House, Roper Close,
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 Telex 965780

Please supply Total purchase price £

I enclose Cheque Postal Orders International Money Order

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature



RAVEN ON...

Dave Raven looks at the High Street discount war and suggests how you can spend £2500

High street discounting is not a topic we normally discuss in the annals of a high technology magazine.

However, it does have a special relevance to ETI, since we are not against a bit of discount, but more important, the discounting of electronic goods is directly related to the subject of high technology. With 17% inflation, in what other field can you predict with confidence that prices of certain manufactured goods will fall. This ironic contradiction of market forces is brought about by the rapid development of micro-chip technology. Products which contained two components are quickly reduced to one, assembly operations are halved producing double the output, which effectively reduces the price.

This is clearly very confusing to consumers of these goods, but conserve your energy worrying about it, since the customer is on a winner. The man to spare a thought for is your local High Street retailer of electrical goods and, of course, the local jeweller. Cast your mind back to 1964 before the end of retail price maintenance. For years it was simple to place an order with a firm of reputable wholesalers who promptly deliver a mixed variety of stock items which are marked up with the usual standard profit margin and proudly displayed in the window, end of selling job. Customers came streaming in, picked up the goods and paid him his profit, thank you kindly. No point in the customer shopping around, since everything costs the same in all the shops.

Then, at a stroke, Mr Heath removed retail price maintenance, making it illegal for a manufacturer to dictate at what price his goods must be sold. In addition, our membership of the common market introduced further legislation forbidding any form of price rigging by a manufacturer. This resulted in one recent case where a company was fined nearly £200,000 by the EEC for its part in a breach of these regulations.

The effect of discounting on small traders was severe. However, they were afforded some protection by manufacturers who have blatantly broken the laws, but now, in addition to the normal type of discounting which usually works by operating on a smaller profit margin, cutting out the wholesale operation and going for a high turnover, we have the introduction of a fast moving technology which causes discounting of a new kind. This threat protects no one including the large multiple suppliers, as it takes them so long to select a product and

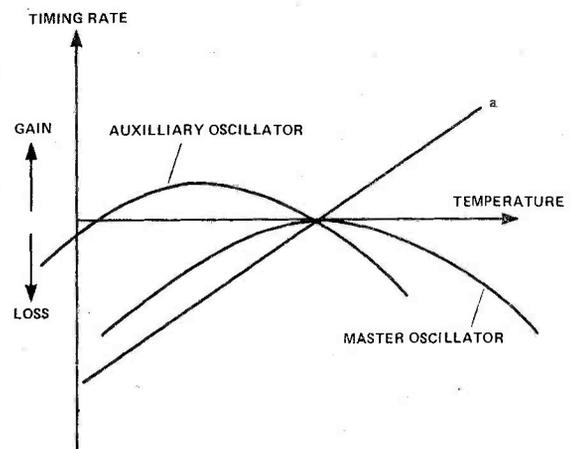


Fig. 1. The difference in oscillating frequency between the master oscillator and auxiliary oscillator is computed line (a).

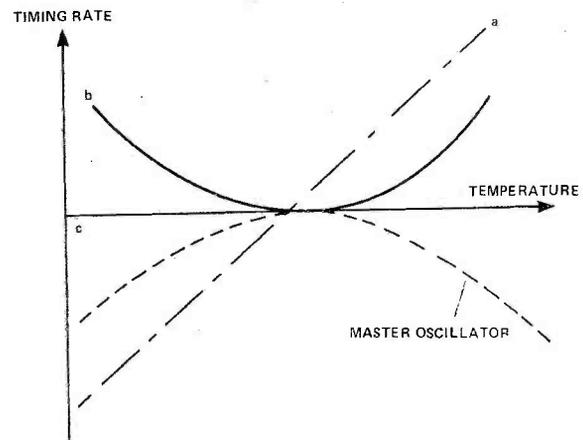


Fig. 2. The straight line (a) obtained by computation is squared and compensated for through a microprocessor in the circuit curve (b). The sum of curve (b) and the characteristic curve for the master oscillator is computed to form a straight line, which is not affected by temperature change.

promote it. Also, their buyers are not up to date with the technological changes. We now have a situation whereby the large chain stores who have grown to fame on the bulk purchase of items which are then distributed throughout their retail outlets, suddenly find that the electronic clock, watch, TV game, etc. selected for promotion in May or June is out of date and over priced by Christmas.

The effect of this during Christmas 1979 was clear to see. Apart from brand leaders such as Casio in the watch field there was little choice in the multiple stores. The shops that I did see selling unknown brands of electronic watches were grossly over priced and the product was out of date. It is obvious that buyers have been very cautious in their purchases of electronic products, probably hoping that soon there will be some sort of price stability.

The future for the small retailer in all of this looks very bleak. First he suffers a loss of trade due to discounting and now he suffers further losses because his wholesaler supplies him with out of date products at too high a price. The only way around this one, I am afraid, is for him to get his jacket off and run round to the wholesaler/importer and see what is going on. Probably he should travel wider for his purchases (even to Hong Kong if necessary).

For the big retail chain more misery is on the horizon, since the price rigging and cartel type operations which have been in existence are soon to crumble. The relevant government department has already invited companies which practice discounting such as Argos, Comet and Tesco to submit evidence of manufacturers that are refusing to supply them, because they discount. With an impending retail trade depression it seems certain that big battles lie ahead in the High Street and of course Mr. Consumer is smiling all the way to the Bank.

The loss of small local dealers for consumer electronic goods is obviously not to be welcomed, since their small size and flexibility usually provides an efficient after-sales service. In the case of jewellers selling quartz watches I think they have already shown that these are not suitable places from which to buy. Their profit margins are much too high for a product which thrives on low profit margin and a fast turnover. The servicing is minimum and a central service centre can service a large group of stores very efficiently and batteries, etc. can always be fitted at local level.

To try and forecast the future for the retail trade in consumer electronics is not easy, but it looks certain that the large multiple stores will have to look closely at their buying methods and probably work closer with the very companies that are setting the price structure for micro-chip goods in the UK.

One company I know, whose name I would not divulge even if you inserted hot watch batteries up my nails, has increased its turnover by 20 times in three years and is all set to start discounting on the discount, so watch out Woolies.


Slimming Time

If you are not worried by the news that the Japanese are predicted to be big in making aero engines then you should be, since that is about the last major piece of technology we are still any good at. In addition to this, the sight of the latest Seiko version of an electronic watch is enough to make you give up and go home if you happen to be a watch designer. Styled in their usual superb way, these latest slimline models are as thin as some watch bracelets, which makes them look almost tasty enough to eat, let alone wear

on your wrist. The 18 carat gold digital man's watch measures a total of 1.79mm in thickness overall. The watch module is a mere 1.38mm thick including battery.

The analogue version is 18 carat gold and also only 1.79mm thick overall. The price for both models is slightly thicker than average, a real snip at £2500 each. Accuracy of Seiko watches has been improved using a traditional electronic technique of twin quartz oscillators for a temperature compensating circuit. The pair of crystal oscillators have different temperature characteristics and each of the crystal oscillators are oscillating independently. The temperature change is detected and this is then compensated for using a microprocessor which in turn corrects the watch accuracy, thus achieving an approximate accuracy of plus or minus 10 seconds a year.

ETI

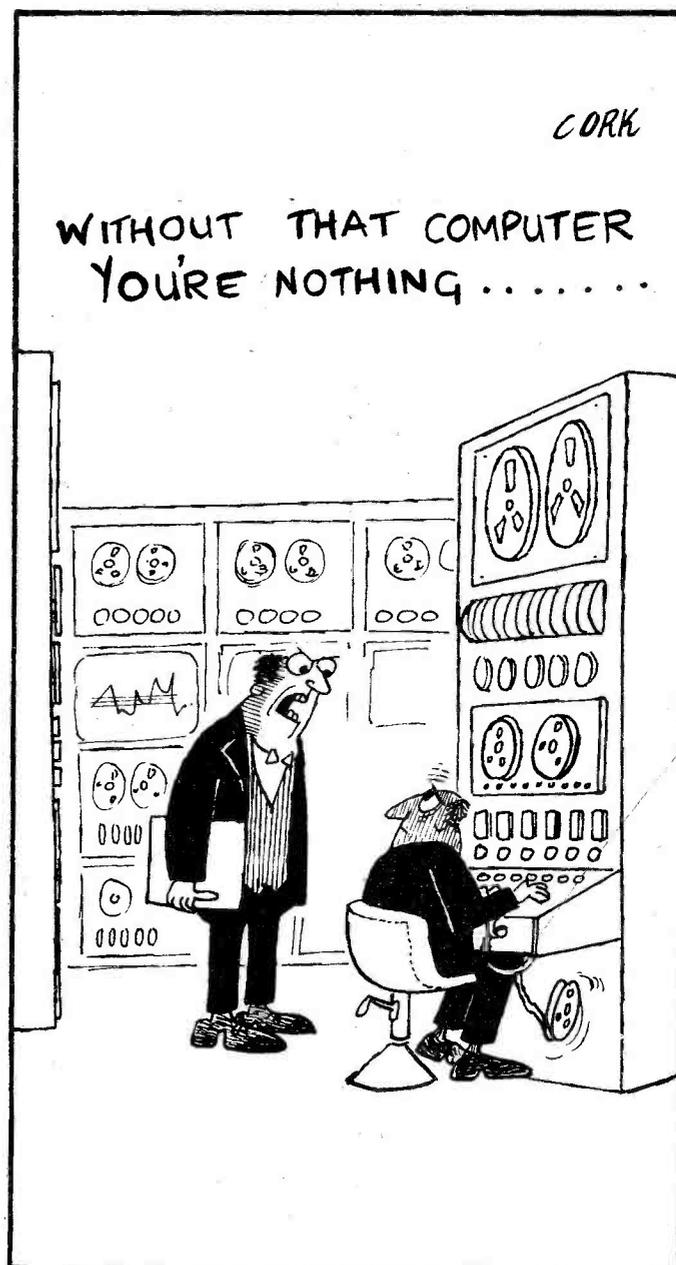

HAND HELD GAMES

Mattel Space Alert	£15.90
Mattel Auto Race	£15.90
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
DIGITS (like Mastermind)	£14.95
DESTROYER	£16.95

ALL GAMES HAVE SOUND EFFECTS EXCEPT MATERMIND AND DIGITS

The latest from the U.S.A. PINBALL WIZARD

★ Still available ★
Featured in Nov. issue of E.T.I.
Home TV Game — B/W Kit

Basic Kit £28.90

Contains everything except box and controls

Box & Controls — **£6.50**. Mains Adaptor **£3.90**

Play 7 games with 4 options on each game

4-Pinball games 2-Basket, 1-Breakout

Versatile car alarm kit **£18.90**

See review in Hobby Electronics November

CHROMA CHIME 24 tune door chimes kit **£10.50** Built **£15.95**

C.B. Aerials and Accessories

CHESS COMPUTERS ETC.

STAR CHESS T/V Game	£63.35
DATABASE Prog. T/V Game	
NEW £89.95	
CHESS CHAMPION 6 Level	£54.95
CHESSMATE 8 Level	NEW £59.95
CHESS CHALLENGER 7	£99.00
CHESS CHALLENGER 10	£160.00
VOICE CHALLENGER	NEW £230.00
BRIDGE CHALLENGER	NEW £290.00
CHECKER CHALLENGER 2	£54.00
CHECKER CHALLENGER 4	£90.00
ATARI Video Computer	£159.00
ZODIAC Astrology Computer	
NEW £34.95	

Selection of Commodore Watches & Calculators

COMPUTERS — Home, Business etc.

PET 8K	£632.00
PET 16K New Keyboard	£776.00
SORCERER 8K	£747.50
SORCERER 16K	£874.00
SORCERER 32K	£987.75
SUPERBOARD II 4K	£216.20
UK101 Kit 4K	£228.85
Built 4K	£286.35
NASCOM 1 Kit	£189.75
1 Built	£247.25
NASCOM 2 Kit	£339.25
2 Built	£396.75
HEATH WH89	£P.O.A.

Keyboard, VDU, Floppy Disc, 16K all in one

PRINTERS: FLOPPY DISC: BOOKS

S.a.e. Enquiries. Please allow up to 21 days for delivery

N.I.C.

61 BROAD LANE, LONDON N.15 4DJ
Day 01-808 0377; Eve 01-889 9736

BUILD YOUR OWN METAL DETECTOR

VLF/TR VCO/TR IB/TR BFO . . .

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.

Shadow TR/1B

Shadow VLF/TR. The worlds most advanced metal detector in kit form. Full discrimination; rejects nails, bottle caps, Aluminium foil and ring pull tabs! Full ground effect exclusion over normal of high permeability soils. 4 modes — deepseeking VLF plus 3 TR discriminating ranges! Instant tuning recall via push button memory circuit. Variable sensitivity and volume controls. Built-in speaker, headset jack, and meter for discrimination and battery check functions. Long life from inexpensive batteries. Fully adjustable shaft; length and head angle. Waterproof head, capacitive and thermally shielded. Complete kit as described in ETI. **Only £85 + VAT** (post & pkg. £1.50).

Hardware only. Shell, S/Head, PCB, Case. **£44 + VAT** (post & pkg. £1.50)
FREE FOR PURCHASERS OF COMPLETE KIT: Details and parts for extra switched function which sounds the tone for good & bad or just good finds when in discriminating mode!

Shadow TR/1B (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. **Complete kit £25 + VAT** (post & Pkg. £1.50).

Shadow TR/VCO. An advanced version of the TR/1B. Use as a sensitive IB machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. **Kit price £29 + VAT** (post £1.50).

Matching stereo headphones for all Shadow models £4.90 + VAT (post paid).

Beginners BFO model. A very detailed assembly manual and pre-wound coils make this an ideal first project. Simple high efficiency circuit. Full size (Not a toy) but weighs only 300gms (10.5ozs) with battery! **FREE STETHOSCOPE HEADSET** with every order. **ALT3 kit: £12 + VAT** (post £1.50) Padded high Z headphones **£4.50 + VAT** (post paid).

Shell Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions **£8.25 + VAT** (post £1.50).

ALTEK

(ETI), 1 Green Lane
Watton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please.
Phone (093 22) 44110 anytime!

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

Our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, ICs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Transistors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's budget Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including ICs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post, or post paid from Marshall's, Kinggate House, Kinggate Place, London NW6 4TA. Also available from any branch to callers 50p.

Get a great deal from Marshall's for quality electronic components 1979/80 50p

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/4. Also 325 Englewood Road, W2. Tel: 01-721 4242. Glasgow: 85 West Regent Street, G2 2GD. Tel: 041-314 4133. And Bristol: 106A Stokes Cross, Bristol. Tel: 0272 445017.

**Next
Month**

Hobby Electronics

MOBILE MICROELECTRONICS



We have managed to "persuade" one of the country's leading motoring journalists into writing a feature for us. He will be taking a look at the impact electronics has been making on the world of automotive engineering and some of the advances we can expect in the next few years.

Already we have cars (if you can afford them) like the Aston Martin Lagonda that are almost completely computer controlled, is this the shape of cars to come? We think so, find out all about it next month.

SHORT WAVE RADIO

Have you ever wondered why there are so few designs around for really simple SW radios? We think it's because most designers are a bit afraid of RF circuitry. After all digital equipment is so easy to design, most of the hard work has already been done by the IC designer.

So, we at HE have girded the loins, put our noses to the grindstone and come up with a really first-class design for a SW radio. We won't promise it'll cover 27 MHz (after all, there's not much to listen to, is there?) on the other hand it just might. Miss next month's copy and you will never know.

PETTING IT TOGETHER



Rick Maybury's latest report from the west coast of America comes from the Commodore factory in Silicon Valley California where the famous PET computer is assembled. The PET is probably the best known of all the minicomputer systems and Commodore have lost no time in carving out for themselves a very large slice of the market, find out why next month.


25 WATT MODULE

Here we have Keith Brindley putting the finishing touches to the prototype of the 25 Watt modular Amplifier for next month's HE. The final design will be built on a PCB and should set a new standard in medium power amplifiers. This project should be ideal for use in a home-built stereo system. Although we haven't published a purpose-built pre-amp it will happily work alongside the Tantrum pre-amp and virtually any other design, depending of course how far you want to go.

By using readily available components it should cost appreciably less than the commercial modules on the market.

To save you the trouble of finding a suitable PSU design we are publishing one designed for the job.

TOUCH SWITCH

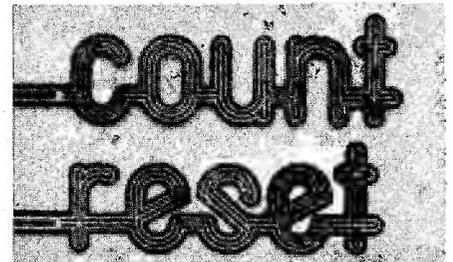


How would the world of amateur electronics exist without the ubiquitous touch switch? How have we got the nerve to publish another? Simple, they are easy to build and are a really great introduction to electronics.

Add a touch of class to your projects with next month's super design. Featuring novel circuitry and using only two inexpensive ICs with genuine capacitive operation we feel sure this one is going to be a winner. Ten channels are available and any one may be selected under fingertip control. Full constructional details next month. We know that you won't want to miss it.

PSU MODULE

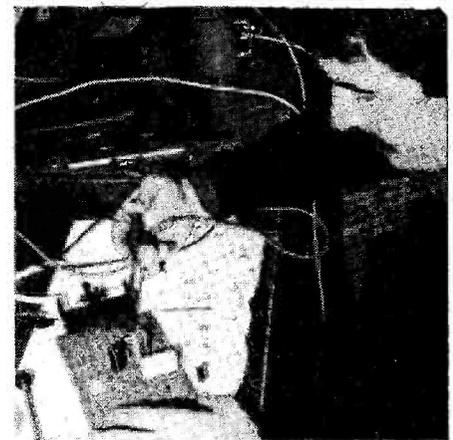To complement the 25 watt power amplifier module we have designed a purpose-built PSU. The power supply to be described next month will happily drive two 25 watt modules (with some to spare) and will still be relatively cheap and easy to build.



The March issue will be on sale February 8th

The items mentioned here are those planned but circumstances may affect the actual contents



AUDIOPHILE

Ron Harris brandishes his safety raiser at a dust bug and has news for Audiophile Amp fiddlers

Tis a strange thing but the higher quality record deck you have, the more attention needs to be lavished upon it to keep it happy and operating. Not for the *real* hi-fi enthusiast the arm that raises itself from the groove after a hard side's tracking, thus liberating the ear from the repetitive click with which all composers, modern or baroque, somehow seemed to end every recorded piece. Oh no, it's not that easy.

It is only, apparently, upon the semi or totally automatic machines which populate the foothills surrounding peak-fi that such cantilever bending mechanisms are to be found. To be sure in the past couple of years' operation has moved ever more toward a gentleness suitable for the most compliant of stylus carriers.

Alas, though, noses still head rapidly skyward at a sniff of automation.

Not that there have not been devices marketed to add a refined touch of convenience to the first division decks before. There have. Never successfully enough, though. Anyway, wanting both my cake and digestion of it, I purchased myself the latest of this line, the Audio Technica "Safety Raiser".

Before we go ANY further, I absolutely refuse to make so much as a single pun around that name. Whatever blade at AT thought it up can keep his giggles to himself! I will simply applaud the sharp edge of his wit.

With anything resembling justice this beautifully engineered little device would sell a million. It looks superb and the action is so smooth and gentle that even the most hidebound purist must begin to question the value of listening to the run-out groove.



Lift-off

The trip lever is positioned so that it lies in the path of the pickup arm as it swings across at the end of the side. Once touched it leaps back out of the way, magnetically releasing the damped action platform to rise up and take the stylus away from all this, so to speak.

The required force on the trip lever to achieve this is so minute that it could not possibly be said to interfere with the arm anymore than would a passing butterfly breathing on it. Before fitting it I spent a good half-hour with the thing in the middle of my desk trying to touch the trip lever, without triggering the arm lift.

One thing's for sure — I ain't no butterfly, passing or otherwise. A big kid maybe, but butterfly no. Ah well, mine is not to do and fly . . .

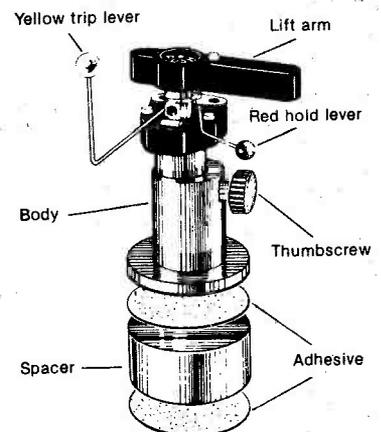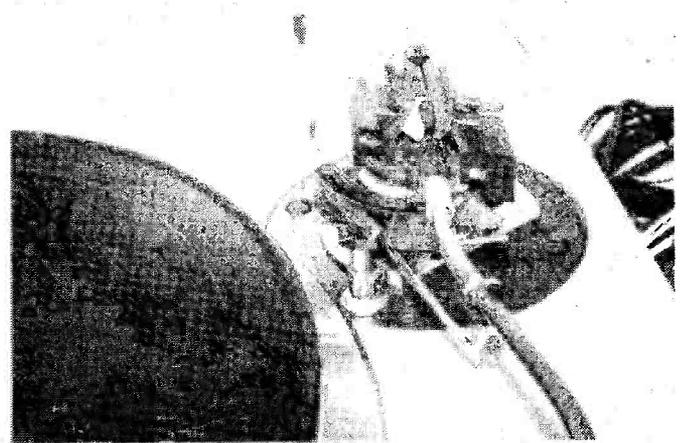In use the Raiser is a delight, although positioning it could prove a problem in some cases. I had a devil of a time persuading it to sit under an SME III such that it avoided the edge of the turntable, but reached the arm when it went for it.




The little safety raiser in situ, i.e. stuck under the SME III, and what all the bits are for! The yellow lever is the one which the arm contacts on its way across the LP, thus triggering the action.

The height adjustment must be tightened up solidly, since you have to push the platform down after every operation and if you haven't tightened the screw enough . . .

Anyway, it's not often you can spend as little (circa £11) on the hi-fi and get such a welcome return. After all — admit it, oh ye followers of the holy musicality, there are times when you simply *cannot* get to the deck at once — aren't there?

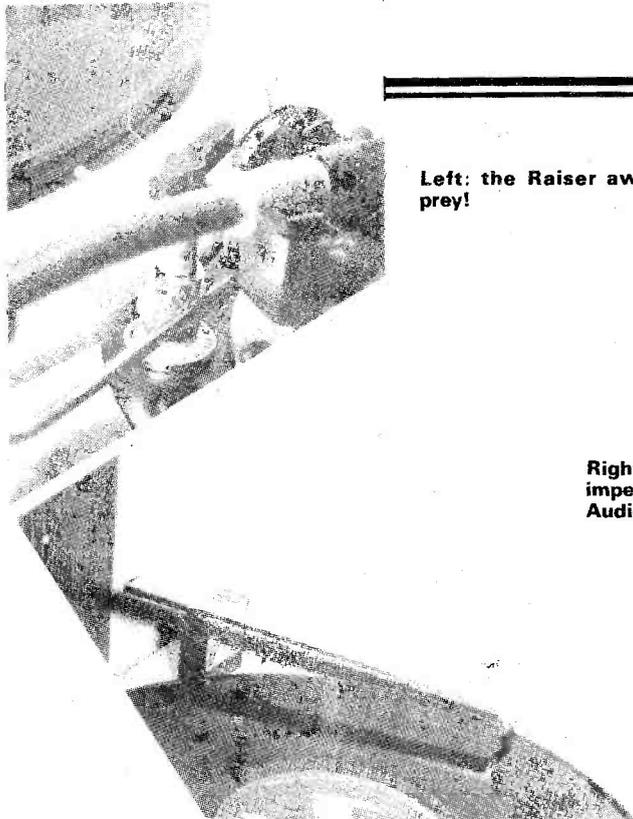No? Hmm . . . you're more dedicated to this hobby than I thought. Didn't Daddy ever take you aside for a little talk . . . ? ▶



Left: the Raiser awaiting its prey!

Right: circuit diagram of the low impedance driver circuit for the Audiophile Amp.

Above: the Decca record brush in action. Note the earthing wire snaking away in the background.

Brush Up On Carbon

While I was meandering around the local audio emporium in search of the Raiser, I promised myself I'd finally replace my ageing Dust Bug — which is now so old it has a good claim to have kept the Magna Carta records clean.

After a deal of bewilderment in the face of the veritable horde of appliances vended to trail a brush across an LP, I settled on the Decca version as potentially the most useful.

Despite the varying claims for all these contraptions, their aim is usually identical. The purpose *should* be to sweep the grooves just ahead of the stylus, picking out any debris lurking therein to prevent it gathering around the diamond and suffocating its tracking ability.

Decca claim a static removal ability too, as do droves of the others. The bristles of the brush are conductive carbon fibre and an earth return lead is provided to attach to the deck earth. The scheme is that any local static charge will be grounded by the passage of the brush before the pickup reaches it.

Besides all this I simply thought the Decca was a nice looking little device and a bit more individual than most.


Since I've been using it I can report a definite drop in perceived surface noise, quite dramatic at times in fact. It seems that earth path *does* lead somewhere after all.

The device has been around a while I know, but has probably been buried under a mound of similar offerings from beyond the edge of the Empire in a lot of shops.

It deserves better! It works very well indeed — at least give it a look over next time you're browsing around, the brush-off would be un-just!

Audiophile Amp

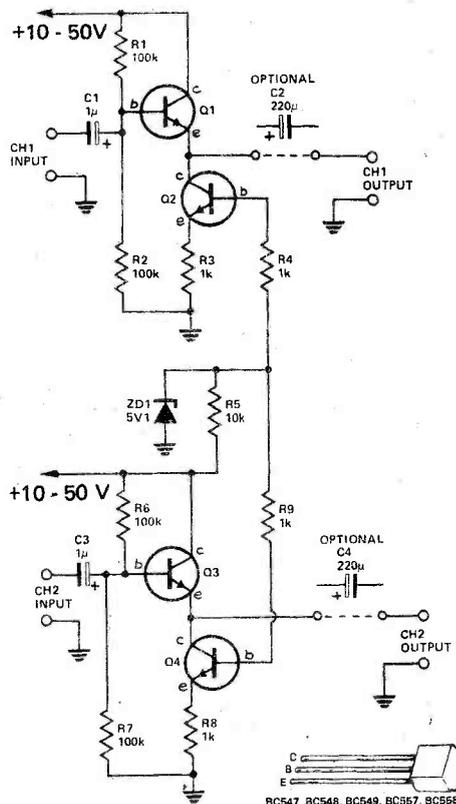Amongst the many bits of paper with stamps on that that funny little man with the flat cap (and head?) keeps dropping all over our floor every morning has been some correspondence on the Audiophile amp.



PARTS LIST

Resistors — All ½W, 5%

R1,2,6,7 100k
R3,4,8,9 1k0
R5 10k

Capacitors

C1,3 1u0 35V tantalum
C2,4 200u 35V electrolytic


Semiconductors

ZD1 5V1 400mW zener
Q1-Q4 BC547, BC107 etc.

It seems that some fickle fiddlers out there are using the power amps of this superb design, but not the pre-amp. Tsk, Tsk terrible people. Anyhow this may just cause problems. Our pre-amp was designed as a low impedance driving source for the power amps, the input impedance of which varies with frequency from a few kilo-ohms at extreme LF to hundreds of ohms at the top end.

If you go driving this with a high impedance output, the amplifier will load down the driving current at HF, causing distortion. With a low output impedance pre-amp (50R) no symptoms need be expected. However it is for the rest I speak these words of doom.

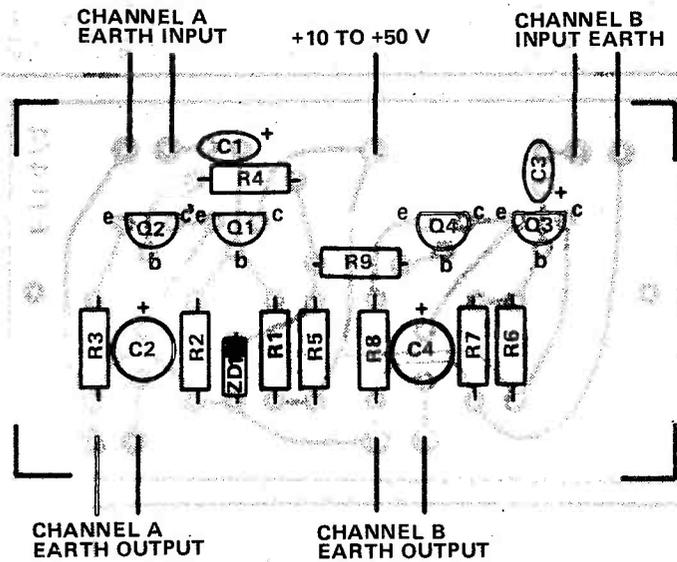As there is no chance of anyone out there abandoning the idea of separating the Audiophile system, it falls to us to do the decent thing and provide a low impedance driver which will allow greater compatibility with the universe in general. The circuit given here will do just that.



Above: component overlay for the low impedance driver circuit. The PCB is to be found hiding with the rest of its kind.

It consists of two emitter followers, Q1 and Q3 with constant current generators in their emitters. Both the latter share a common reference, ZD1, which feeds the bases of Q2 and Q4, setting their emitter voltages at 4V4.

These transistors will always pass the exact amount of current required to maintain that emitter voltage, regardless of supply voltage. The constant current generators are to limit supply current and dissipation of the emitter followers when used with a high supply rail. It also lowers output resistance.

Output is derived via the optional blocking capacitors C2 and C4, which can be omitted if our modules are ALL you're driving with this buffer, but as we don't trust you Fit them if any other equipment at all is to be linked to the circuit. Replace the C1 capacitor in the power amp with a 220u (35V), with positive lead towards the input, if you leave out the blockers.

We've provided a PCB layout which we would advise using, and be careful with earthing arrangements — use the signal earths wherever possible.

Trailing Trailers

Next month I'm taking a look at some of the best of budget hi-fi. A heated conversation arose here some little while ago about just what level of fidelity could be obtained for £300 or less.


Everyone had their own ideas and tastes. Trouble is some of the combatants showed a deplorable *lack* of taste — would you believe not all of them had the sense to see that Felicity Kendal is the most beautiful woman in creation. Given that obvious blind spot in their make-up how can one possibly listen further?

I went ahead and assembled *my* £300 system despite the heathen howling hereabouts, and am presenting the results next issue.

I must confess there is one component I am not entirely happy about, but the amp and cartridge are real gems and together barely cost £100.

ETI

ETI NEEDS YOU!

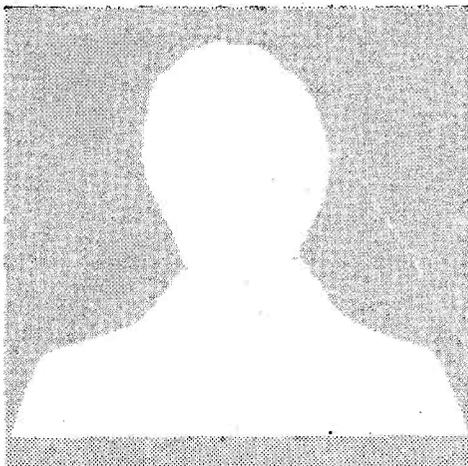

ETI is seeking to expand its staff once more and we are looking for a Project Engineer to join our ranks. In order to complement existing staff skills within our organisation we expect that the successful candidate will have had some experience with MPU based designs. He need not have been a specialist.

Our Engineer will be designing and testing projects for the magazine — and writing them up! This is the easiest part of the job and has caused no-one any problems yet, even though none of our existing staff were journalists prior to joining us.

We are flexible as to age and salary, but imagine that the successful applicant will be paid around £5000 p.a. — more for someone exceptionally qualified for the job.

Applications, including a C.V., should be addressed to :

The Editor,
ETI Magazine,
145 Charing Cross Road,
London WC2H 0EE.

Please mark your envelop "Project Engineer"

Metac

ELECTRONICS & TIME CENTRES

QUARTZ LCD 11 Function

Slim chronograph


12:30^{pm}
Hours mins secs

8 14TH
Month date day

0:00⁰⁰
Min secs 1/10 1/100

6 digit, 11 functions.
Hours, mins., secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs, mins., Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Same day despatch

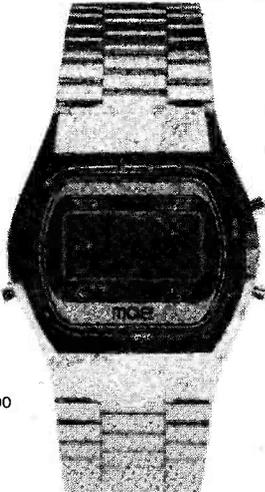

Price only
£9.95

Also available
**SOLAR
CHRONOGRAPH
M9 - Price £11.95**

M3 Price includes POST & PACKING

QUARTZ LCD Lady's Day Watch

Hours, mins, secs, day, date, back light, auto calendar.

12:30
Hours mins

8 14
Month date

:45
Secs

Fully adjustable bracelet only 25x20mm and 6mm thick. Silver or gold.

M15 Same day despatch



Price only

£7.95 P&P included

QUARTZ LCD ALARM

With snooze alarm

12:30^{pm}
Hours mins secs

8 14TH
Month date day

7:30^A
Alarm

6 Functions plus Alarm:
Conference signal, 5 minute snooze alarm, Conference signal sounds 4 secs., before main alarm to give advance warning and an option to cancel. Snooze sounds 5-mins., after main alarm and is always preceded by the conference signal.

Same day despatch



Price only
£9.95

M4 Price includes POST & PACKING

QUARTZ LCD Lady's Cocktail Watch

Beautifully designed with a very thin bracelet

12:30
Hours mins

8 14
Month date


:45
Secs

Hours, mins, secs, day, date, backlight and auto calendar. Bracelet fully adjustable to suit all wrists. State gold or silver finish. Only 25x20x6mm

M18 Same day despatch

Price only

£14.95 P&P included

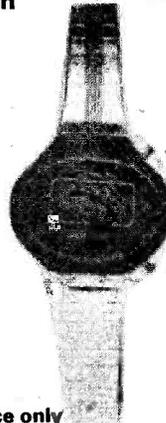

QUARTZ LCD ALARM CHRONOGRAPH

With 12/24 display

12:30^{pm}
Hours mins secs


8 14TH
Month date day

0:00⁰
Min sec 1/10th

Alarm
Hours, mins, secs, day of week, Month, date, day of week, alarm, hour, mins, a.m./p.m. 24 or 12 hour display mode. Alarm test. Chronograph, lap time, stop watch 1/10th secs.

Price only
£13.95

Same day despatch

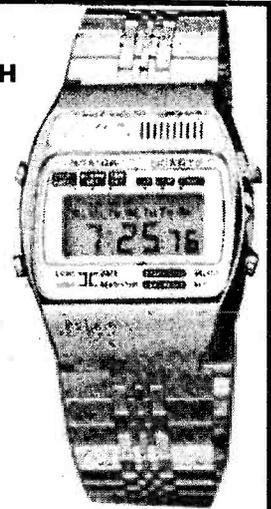

Also available
**SOLAR ALARM CHRONO
M7 - Price £17.95**

M16 Price includes POST & PACKING

Metac Guarantee All Metac products carry 12 months guarantee and we also refund your money if not satisfied with our goods or service in the first 10 days. Metac's well-equipped service centre minimises service delays. Please note we do not delay your order to clear cheques.

Telephone your order using

Barclaycard/Access

Number on



03272-76545

24-hour answering service

OR COMPLETE THE
COUPON

HANIMEX Electronic LED Alarm Clock



Features and Specification:
Hour minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43lbs (0.65 kg).

M13 **£10.20** Thousands sold!
Mains operated. POST & PACKING incl.
Same day despatch.

QUARTZ LCD 5 Function

Hours, mins, secs., month, date, auto calendar, back light, quality metal bracelet. 6mm thick

12:30
Hours mins

8 14
Month date


:45
Secs

Price only

£6.95

POST & PACK incl.

M1 Same day despatch

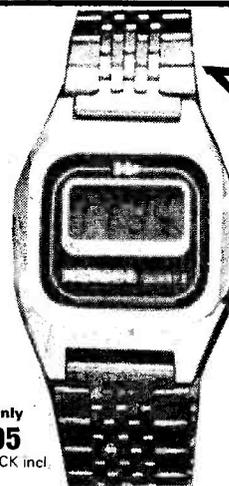

NEW 24 HOUR DESPATCH SERVICE: METAC have opened a new even faster mail order and service centre at DAVENTRY. Orders received before 3.30pm will be despatched same day.

**VISIT OUR ELECTRONIC TIME CENTRES
AND SEE ONE OF THE MOST IMPRESSIVE QUARTZ WATCH RANGES IN BRITAIN**

LONDON
327 Edgware Rd,
London W.2
Telephone: 01-723 4753

DAVENTRY
67 High Street
Daventry, N'ants
Telephone: 03272 76545 / 77659

NORTHAMPTON
St Giles Square,
Northampton
(Open 1st Feb. 1980)

QUARTZ MELODY


Alarm Chronograph
(incredible watch)



Count-down Timer



Alarm

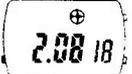

Time Zone



Chronograph

5 independent working modes, day of week in English, French or German (just select the one you like). Hours, mins, secs, day, date, count-down alarm, dual time zone, 1/100th sec. stopwatch. Lap/split time, 1st and 2nd place times. Melody test function.
34 Functions



**Price only
£19.95**

Same day despatch
Price includes
POST & PACKING

M30

**CASIO CHRONO
95QS-32B**

Stainless steel case, water resistant to 66 feet. Hours, mins, secs, am/pm, year, month, date, day. Auto-calendar pre-programmed until the year 2029. 12/24 hour. Stopwatch function. Range 7 hours. 1/100 sec. (Mode) Net time/lap-time/1st-2nd place times. Dual time function. Accuracy 15 secs per month. Battery life approx 4 years.



Same day despatch
**Price only
£23.95**
including POST & PACKING

M22

**CASIO ALARM
CHRONO
81CS-36B**

Hours, mins, secs, day, and also day, month and year perpetual automatic calendar. 100th sec chronograph to 7 hours. Net time/lap/time/1st and 2nd place times. User optional 12/24 hr display. 24 hourly chime. Backlight, mineral glass, stainless steel. Water resistant to 100ft. Battery life approx 4-years.



Same day despatch
**Price only
£35.95**
including POST & PACKING

M25

**CASIO F-200
Sports Chrono**

Attractive Man's watch in black resin with mineral glass. Hours, mins, secs, am/pm. Month, date, alpha-numeric day. Auto-calendar set 28th Feb. Stopwatch working range 1 hour, units 1/100 sec. Mode. Net Time/lap/time/1st-2nd place times. Accuracy approx 15 secs per month. Battery 12 months.



**Price only
£15.95**


Same day despatch

including POST & PACKING

M24

**CASIO F-8C
3 Year Battery Life**

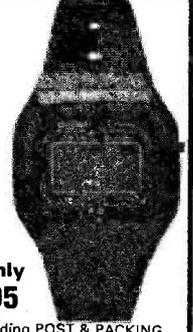Hours, mins, secs, am/pm, date, day. Auto calendar set 28th Feb. Accuracy 15 secs per month. Battery life approx 3 years.



Same day despatch


**Price only
£10.95**

including POST & PACKING

M36

**SEIKO
CHRONOGRAPH
NEW STYLE**

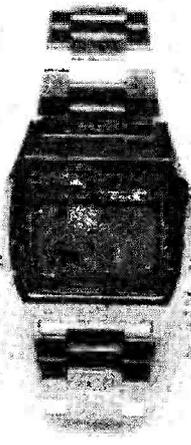Hours, mins, secs and day of the week. Month date and day of the week. Stopwatch display — Hours, mins, secs up to 12 hours (mins, secs, 1/100 secs up to 20 minutes). Lap timing. Continuous time measurement of two competitors. Stainless steel, mineral glass.



**Price only
£39.95**

Same day despatch
including POST & PACKING

M33

**SEIKO Alarm
Chronograph**

With WEEKLY Alarm. Hours, mins, secs, month, date, day, am/pm. Weekly alarm — can be set for every day at designated time e.g. 6.30 am on Mon, Wed and Friday. Alarm set time displayed above time of day. Full stopwatch functions, laptime, split etc.



**Price only
£79.95**

including POST & PACKING

Same day despatch

M10

**SEIKO DIGI-ANA
CHRONOGRAPH**

Time and Calendar function
Analog part display; hr, min, sec. Digital part display; hr, min, sec, date, day and colon. Calendar-month, date, day. Stopwatch — hr, min, sec, 1/100 sec. Lap/stop and stop marks. Counter function. Time and calendar setting function.



**Price only
£79.95**

Same day despatch
including POST & PACKING

M62

POST COUPON TO: METAC (24-hour despatch centre) FREEPOST (No stamp required), 47a High Street, Daventry, Northants

Please complete both coupons

Please send me
I enclose PO/Cheque value
Barclaycard/Access No.
Name
Address

**From: METAC Electronics & Time Centre, (ETI)
47a High Street, Daventry, Northants.**

Name
Address

POST, PACKING AND VAT included in price

ELECTROMYOGRAM

ETI's latest biofeedback box converts the electrical impulses associated with moving a muscle - any muscle - into observable outputs. Either audio output or a meter reading can be obtained and if you can't relax with this, try reading ETI again!

The design and construction of an electromyogram presents some unique problems. The object is to detect the minute electrical signals produced by the 'firing' of muscle fibres in a particular muscle. For our purpose metal electrodes of some sort are attached to the skin over the muscle(s) of interest. For a relaxed muscle, these signals are fractions of a microvolt in amplitude. That's a small enough signal to detect on its own without having to find it amongst *volts* of 50 Hz hum that will be present in the body - induced from power and light wiring.

When the body is grounded, this hum will drop to typically one volt peak-to-peak, but trying to see one microvolt in one volt of unwanted noise (50 Hz hum here) isn't easy.

The overall block diagram of the unit is shown in the drawing.

Battery operation is essential as, with any device connected directly to the body, the possibility of accidental contact with mains potential from a mains-operated unit is very real - with lethal results.

The instrument is called upon to detect quite small signals in the presence of large amounts of noise. It should have variable gain control - adjustable by the user, a threshold control so that small variations of a large signal may be readily detected, a visual indication (a meter) and an audible output that follows the convention of rising pitch or pulse rate for increasing muscle activity, and vice versa. Also some form of band-pass filtering to sort out the predominant muscle signal which is in the 100 Hz to 500 Hz range, and selectable integration of the feedback response was considered desirable.

Biasing the differential input stage is important and this is discussed in the "How it Works" section. One trimpot is used to set up the input stage for correct operation. Once set up, any of the component values may be varied by +/- 10% without affecting the CMRR.

The choice of this type of first stage has resulted in a very low noise figure. The prototypes (we built two) had measured noise figures close to 150 nV at the input. This equals the performance of the best commercial units we have seen.

To provide some integration of the muscle activity level, so that the meter and audible responses are not too rapid (as researchers have found undesirable in some instances), switched capacitors are provided to provide integration times of about 0.5 second and 4 seconds - selected by a front panel switch. ▶



PARTS LIST

Resistors All 1/4W, 5%

R1,2,18,	220k
31	
R3,7,9	4k7
R4,25,26	100R
R5,6	2M2
R8,10,11,	1M0
22,23,40,41	
R12,45	1k0
R13	8k2
R14-17,	47k
27-30	
R19,32	270k
R20,24,33,	10k
38,39,42,47	
R34	330k
R35	560k
R36	5M6
R37	3M3
R43	390k
R44	470k
R46	680R
R48	2k7
R49	18k
R50	27R

Potentiometers

RV1	1M0 linear
RV2	5k0 linear
RV3	1k0 linear
RV4	1k0 trimmer

Capacitors

C1-C6	1u0 polyester
C7,8,29,30	1n0 polyester
C9,10,12,	33u 16V tantalum
19,20,23,35,	
41	
C13,31,34,	100n polyester
21	
C14-17,	68n polyester
24-17	
C11,36	100n 25V
C18	22n polyester
C22,39,40	1000u 25V
C28	47n polyester
C32	220n polyester
C33	150n polyester
C37	470u 25V
C38	47u 25V

Semiconductors

D1,2	1N914
D3,4	1N4004
Q1,2	BC559
Q3,4	BD140
Q5-7	BC549
IC1	LM3900
IC2,3	741
IC4	555

Switches

SW1,2	SPST
SW3,4	DPDT

H - TO MONITOR OUTPUT
RCA SOCKET ON BACK PANEL

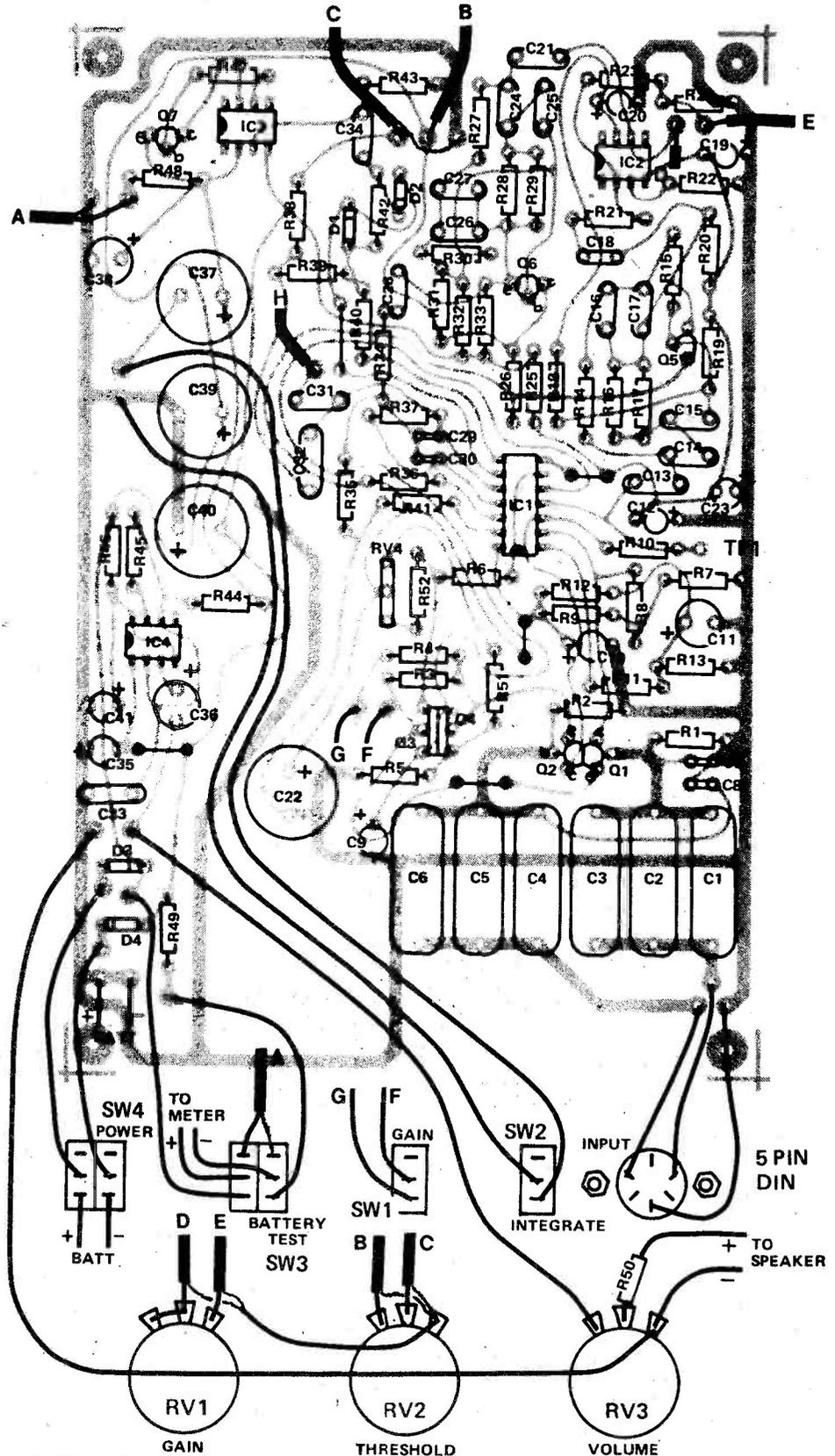


Fig.1. (Above) Component overlay for the electromyogram board.

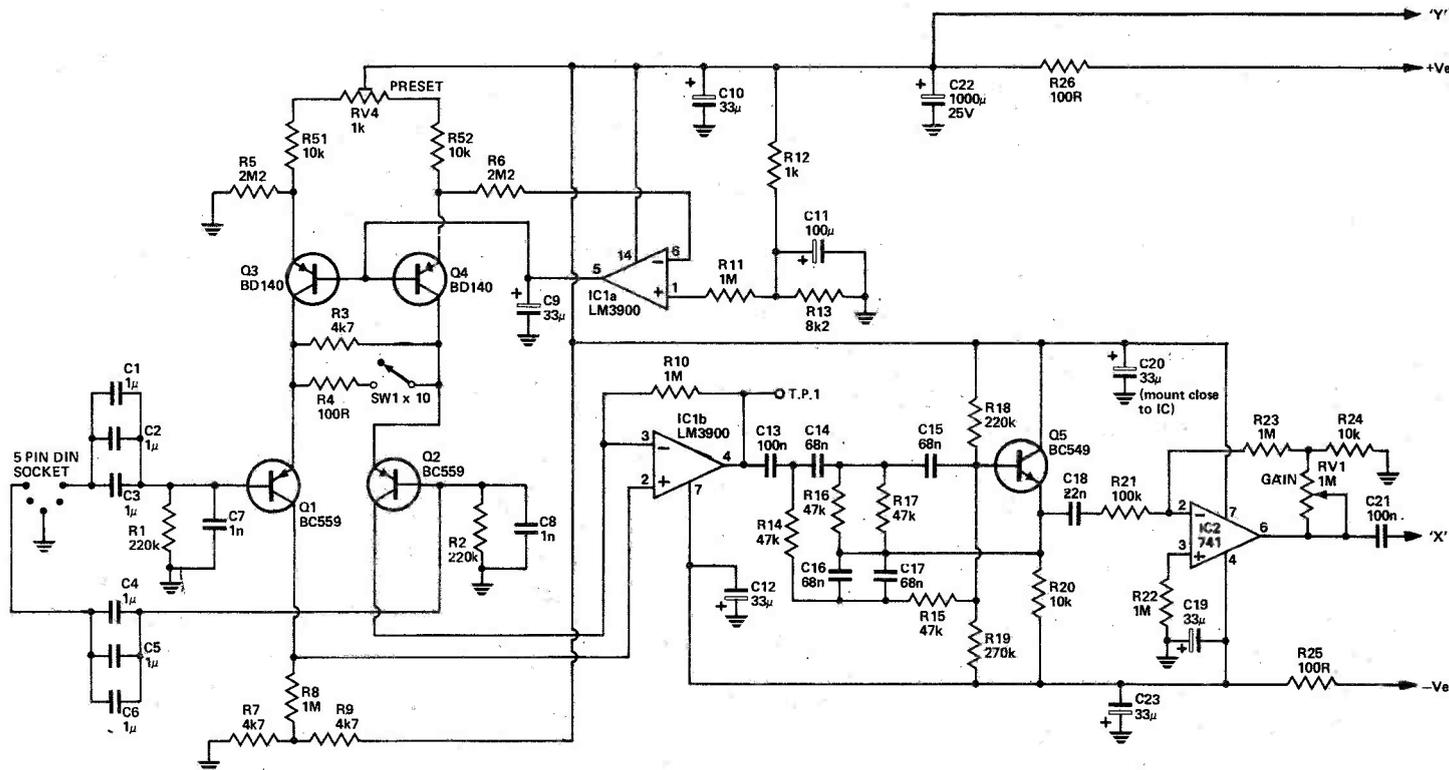


Fig.2. (Above) Circuit diagram of the unit. Note the battery connections carefully.

Since the circuit is fairly complex, a detailed analysis of its operation is best tackled by looking at the individual stages in turn, from input to output.

Input signals from sensors on the body drive Q2 and Q1 which are arranged as a differential pair. Emitter current, and thus collector current, for Q1 and Q2 is derived from a precision constant current source comprised of Q3, Q4 and IC1a. Transistors Q1 and Q2 share the current supplied by the constant current source. If Q1 (for example) is driven harder, by an input signal, than Q2 then, while the collector current of Q1 increases, there will be a corresponding decrease in the collector current of Q2.

Now, the collectors of Q1 and Q2 are each connected to the input of IC1b, one amplifier in an LM3900's quad op-amp package. The amplifiers in the LM3900 package have the special feature that they amplify current differences applied to the inputs.

To ensure a high common-mode rejection ratio, the quiescent (no signal) collector currents of Q1 and Q2 must be held very close to a fixed amount. Hence, the precision constant-current source.

To derive this constant current source for Q1 and Q2 the two bases of Q3 and Q4 are driven by the output of IC1a. The non-inverting input (marked +) of IC1a is driven by a fixed voltage derived from a voltage divider (R12, R13) from the positive supply rail. C11 is a bypass capacitor to prevent supply rail variations modulating this reference voltage.

The inverting input (-) of IC1a is coupled to the emitter of Q4 placing this transistor in the feedback loop of IC1. The

op-amp (IC1a) will attempt to maintain the current flowing through its inputs at a constant level, thus maintaining the base-emitter current through Q4, and therefore the collector current, constant at nominally, 100 mA. Assuming Q3 has similar gain to Q4, its collector current will be the same. The 1k preset, RV4, allows adjustment of the two collector currents to offset any slight differences in gain.

The input stage gain is determined by the value of the resistance between the emitters of Q1 and Q2. The lower this resistance, the higher the gain. The 'x10' switch simply connects a 100 ohm resistor in parallel with R3, increasing the gain.

Capacitors C7 and C8 ensure high frequency stability through bypassing the bases of Q1 and Q2 at frequencies above the range of interest.

To ensure good common-mode rejection ratio, it is essential that the bases of Q1 and Q2 each receive the same level of input signal. As the input is AC-coupled the characteristics of the input coupling capacitors must closely match each other. If stranded 10% capacitors are used the slightly different impedances of each will limit the common mode rejection. The solution we adopted was to use several capacitors in parallel so that the slight capacitance variations, and corresponding impedance variations, average out. It is important therefore that these six capacitors, C1-C6, are all the same type.

Supply rail decoupling for the input stages is provided by R25, R26 and C22, C23.

Two 50 Hz hum filters are employed, as can be seen in the block diagram, one

immediately following the differential input stage, the other between the variable gain stage and the band-pass filter.

Both 50 Hz filters employ a 'twin-T' circuit - as used in our Hum Filter project, ETI-451.


In the first hum filter, Q5 is connected as an emitter follower, the twin-T components connected to provide feedback at 50 Hz. In order to obtain a high circuit Q and thus good rejection at 50 Hz, the value of the resistance formed by R16 and R17 (paralleled) must be as close as possible to half the value of R14 and R15. As the latter are 47k resistors, the best way to obtain a value of half that is to connect two 47k resistors in parallel.

Similarly, for the second hum filter, Q6 is the active component and the filter consists of C24, 25, 26, 27 and R27, 28, 29 and 30. Resistors R28 and 29 form a resistance half that of R27 and 30 to provide good rejection at the notch frequency.

These stages provide a total of 20 dB rejection at 50 Hz.

Following the first hum filter is a variable gain stage employing a 741 op-amp. This is quite a conventional amplifier, gain variation being provided by RV1, a 1M potentiometer connected in the feedback path of the 741. RV1 is a front panel control. Gain is variable between 10 and 1000.

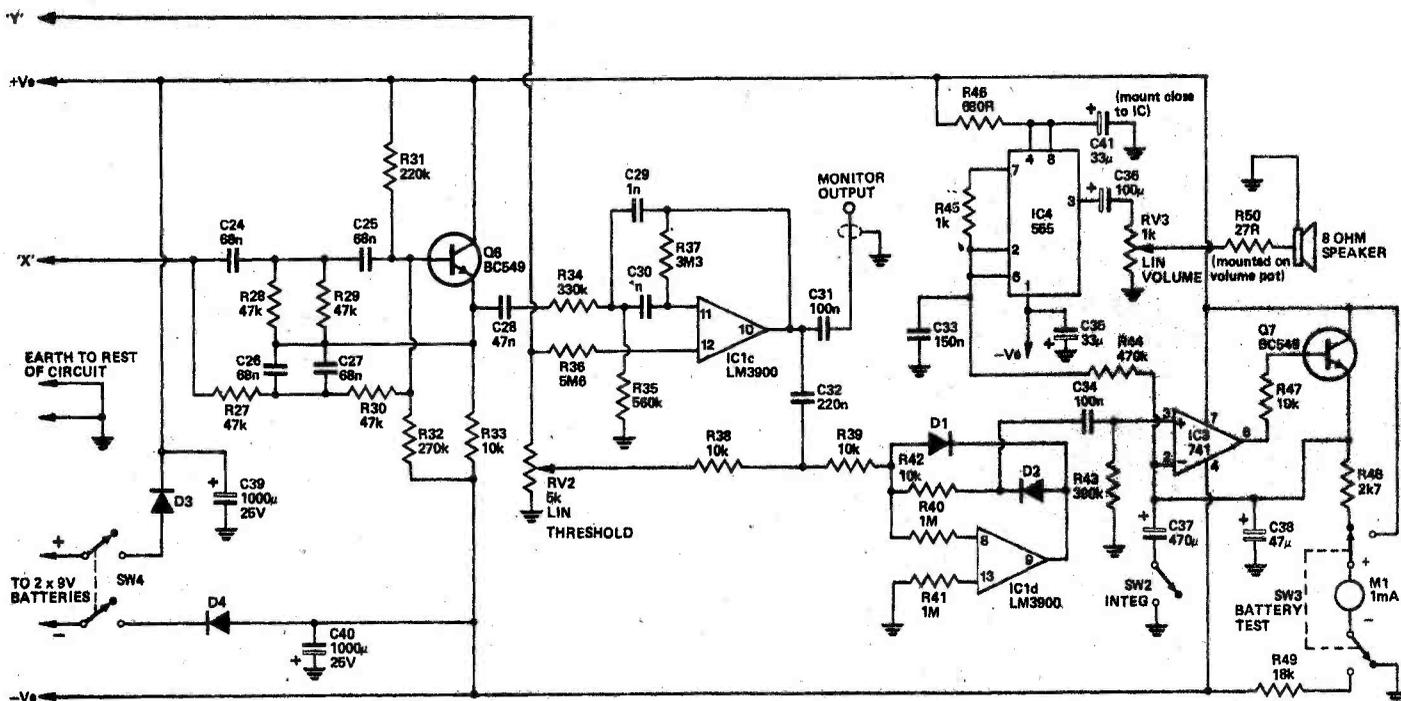To avoid problems arising from large output offset voltages and unstable gain settings, the feedback for the 741 has been arranged via a voltage divider consisting of R23 and R24, the gain potentiometer being connected between the op-amp output and the junction of these two resistors.



HOW IT WORKS

The gain of the circuits is given by the equation:

$$\text{GAIN} = R_{23} + \frac{R_{23} RV1}{R_{24}} + RV1$$

Signal levels at the output of the variable gain stage are around 1V. Any hum exceeding this level could easily cause clipping in succeeding stages and the purpose of the second hum filter is to prevent this.

The bandpass filter employs one op-amp from the LM3900 package, IC1c. A filter network, consisting of R34, R35 and R37 and C29 and C30, is connected around a feedback path between the op-amp output and its inverting input. This provides a bandpass extending from 100 Hz to 500 Hz which encompasses the range of interest for the muscle fibre signals. At midband (250 Hz), the gain of this stage is roughly four.

A monitor output is taken from the output of IC1c so that the muscle activity waveforms (filtered) may be viewed on an oscilloscope if desired.

This consists of a precision rectifier that passes only the positive peaks of the signal that are greater than a preset DC voltage — determined by potentiometer, the threshold control on the front panel.

The output of the bandpass filter is mixed with a DC voltage derived via the positive supply rail by the potentiometer RV2. The resultant signal — the AC muscle activity signal superimposed on a DC voltage

— is then applied to the input of the precision rectifier. This involves IC1d, D1 and D2 and resistors R39, 40, 41 and R42. The latter two resistors convert the current-differencing input of the LM3900 into a conventional voltage-input op-amp.

Positive-going signals of less than 0.5 V, above the voltage present on the junction of R39 and R40 will be amplified by the full open-loop gain of IC1d. The output of this stage increases rapidly until D2 conducts, the stage then has only unity gain (x 1), determined by the ratio of R42 and R39.

Output from the precision rectifier is taken from the cathode of D2 and will consist of the amplified, positive-going part of the muscle fibre signals that are above the positive voltage set by the threshold potentiometer, RV2.

Diode D1 ensures that the gain of the stage remains at unity gain for the negative-going portions of the muscle fibre signals from the output of IC1c.

This consists of an op-amp (IC3) with an emitter-follower stage (Q7) connected in the negative feedback path. The emitter of Q7 drives the meter.


The threshold stage output is coupled to the input of IC3, a 741, via a 100nF capacitor, C34. Resistor R47 limits the base current of Q7 to a safe value as the 741 will provide much more current than the transistor will stand! A signal from the output of the threshold circuit will be amplified by IC3, causing Q7 to turn on, charging C38.

The meter is connected to read the charge on C38, via M1. The more signal that appears above the threshold, the longer Q7 will be turned on increasing the charge in C38, thus increasing the meter reading. The circuit will respond quickly to increasing input signal, showing a corresponding increase in the meter reading. As the signal decreases, the meter reading slowly returns to zero, the meter reading being a function of the capacitance between the emitter of Q7 and ground. This provides for some integration of the signal level variations.

The integrate switch, SW2, connects a 470 µF capacitor (C37) in parallel with C38 (47 µF). With this in circuit (integrate switch 'on'), the meter takes some four seconds to drop from full scale to zero.

This provides an audio output, consisting of a series of pulses, the repetition rate being an indication of muscle activity.

The emitter of Q7 is coupled to IC4, a 555 timer, via R44. Current through this resistor charges C33 until the voltage on pin 6 of IC4 reaches 2/3 of the voltage on pins 4 and 5. At this point, pin 7 of the 555, previously appearing as an open circuit, will conduct discharging C33 via R45. Once the voltage on pin 2 drops below 1/3 of that on pins 4 and 5, pin 7 returns to an open circuit condition, allowing C33 to charge again. In this manner, the 555 oscillates providing pulses on pin 3 to the speaker, via RV1, which serve as a volume control. As the voltage at the emitter of Q7 varies according to the variation in muscle activity signals, the rate at which C33 charges will vary. This varies the pulse repetition rate of the 555 oscillator in sympathy with the variations in muscle activity.

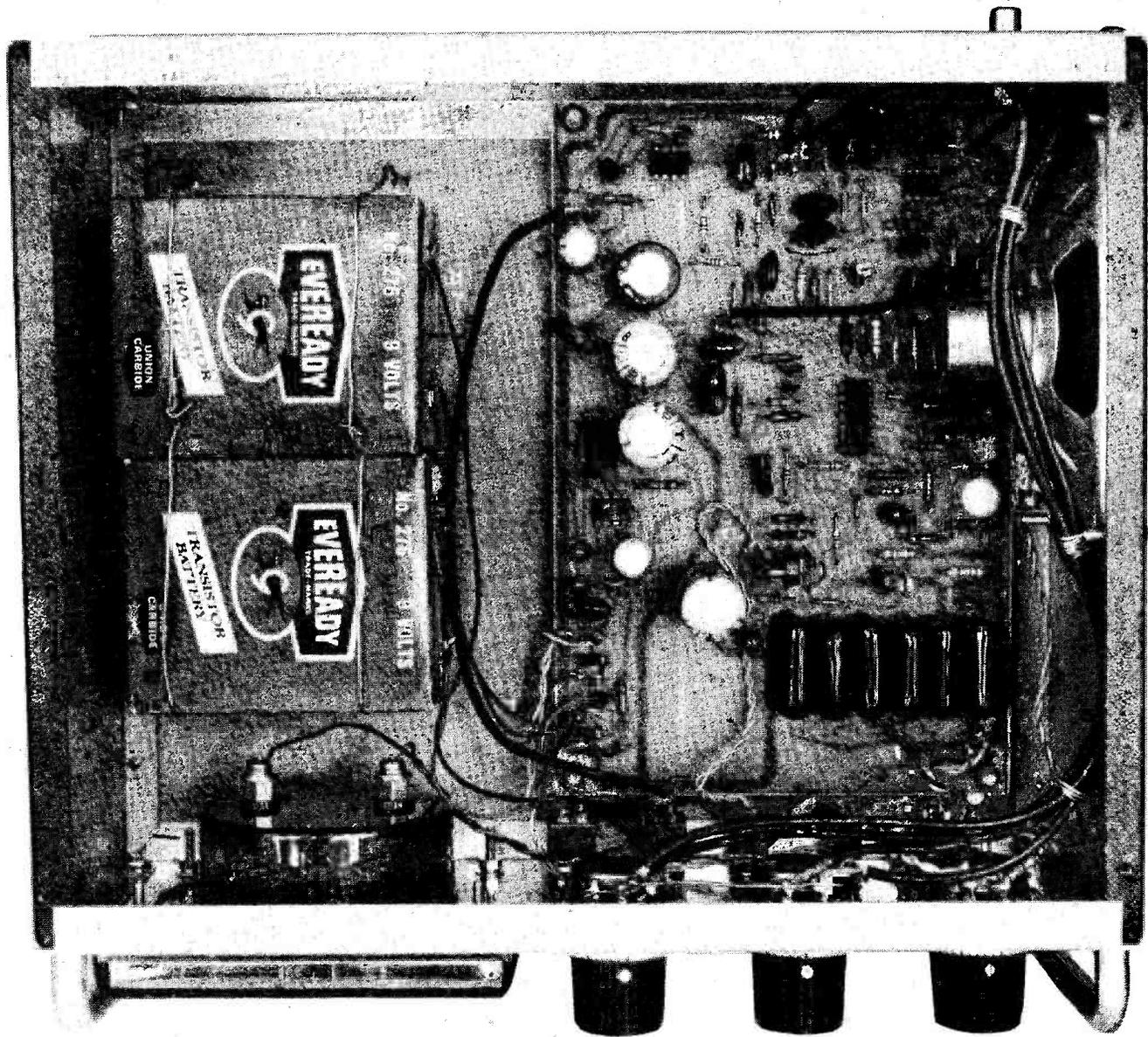

The case will hold the PCB, batteries and the loudspeaker. Note the positions of the front panel controls.

The audible output is derived from the meter drive so that it corresponds with the visual feedback response provided by the meter. This consists of a voltage-controlled oscillator (VCO) that provides a series of pulses to drive a speaker. The VCO employs a 555 timer IC.

Originally, it was intended to use a tone for the audio output. However, battery consumption on the prototype was almost 150 mA — at best! Battery life would be very limited at this consumption. A class A audio output stage is necessary to provide a tone output, and these are quite inefficient. Using a pulse output enables us to reduce the total current consumption to 20 mA.

Muscle Building

Construction is best commenced with the board. This method of construction is recommended as layout of the various stages is critical to avoid feedback or interaction between stages as one LM3900 package does sterling service in several parts of the circuit!

Assembly of the board should start with the resistors and capacitors. We found it easier to leave the six 1 μ input capacitors until the input transistors (Q1-Q4) were mounted. Be sure to check the polarity of the electrolytic and tantalum capacitors.

Finish loading the board by inserting the diodes, transistors and ICs. The input transistor pair, Q1 and Q2, must be mounted so that their flat faces are touching to provide thermal coupling. The best way to do this, to avoid straining anything, is to solder only the collectors and emitters of Q1 and Q2 at first. Smear some thermal paste on the two flats and then tie the two transistors together using a link of enamelled (coil) wire — this prevents the possibility of shorts to the transistor leads should the loop slip off at some time. Tighten the loop by taking the ends in a pair of pliers and twisting until the transistors are held tightly together. Once this is done, solder the base leads.

The two BD140s, Q3 and Q4, also need to be mounted together. As they are in TO-126 packages they may be bolted together. It is necessary to use an insulating washer between them to prevent the collector contacts touching. Use thermal paste to improve the thermal coupling.

Once these devices are mounted, six 1u input capacitors may be soldered into place.

If you use board pins, the external connections to the board may be made after it is mounted in the case, otherwise, now is the time to attach all the leads going to the externally-mounted components.

Pinned Down

As high gain stages are used in several places, the circuit is sensitive to noise or signals radiated from other parts of the board. The 555 VCO output can be especially troublesome, so use shielded cable to connect the output of the 555 to the volume control. The only resistor not mounted on the board (R50) is mounted between the wiper terminal of the volume control and one of the loudspeaker terminals.

There are a number of other connections that should be made with shielded cable and these are shown in the wiring diagram.


There is sufficient room inside the cabinet to accommodate a variety of 9 V batteries. The type of connection to the battery will depend on the particular style of battery used.

The speaker is mounted on one side of the cabinet and the monitor output (and RCA coax socket) is mounted on the back.

On the front panel, the switches should be mounted first, followed by the pots and the meter.

Although the common mode rejection of the input is better than 100 dB this will be degraded drastically if the contact to the skin is not good enough. To enable the input stage CMRR to effectively reduce 50 Hz hum it is necessary to ensure that the hum is exactly the same level on both inputs. For this reason the construction of the electrodes is very important.

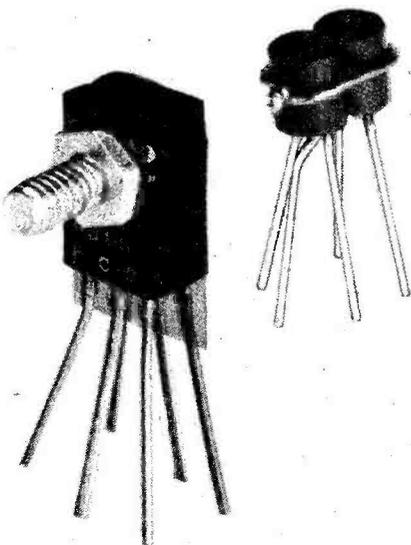The two input leads are made by soldering the centre conductor of the shielded cable to small metal discs about the size of 5p pieces. Cut the earth braid back enough so that it cannot touch the electrode. The braids of the two input cables are connected to pin 2 of the five-pin DIN plug (the grounded pin). This pin is also connected to the shield



Thermal stabilisation is achieved by mounting the input transistors together as shown and described in the text. Note the insulating piece between the BD140s.

BUYLINES

The design uses no unusual components, despite its complexity. The electrodes can be made at home easily enough, although commercial units, we believe, are available. Any of the bio-feedback firms, Aleph One etc will be able to supply.

of the third cable which becomes the ground electrode. The centre conductor of this cable is not used and the other end of the braid is soldered to another metal disc. Use a slightly larger disc (about the size of a 10p piece) as this helps to ensure a good ground connection to the body.

Before powering up, check the board. Check the orientation of all the polarised components — electrolytic and tantalum capacitors, transistors, ICs and diodes. If everything is all right, switch the unit on with the battery switch in the test position. With 9 V batteries the meter should read about 9. If the battery switch is now switched off the meter should immediately fall to zero provided the gain control is turned fully down. If the volume control is turned to full on a slow clicking should be heard.

Now, measure the voltage (with respect to earth) at the test point (TP1) at the output IC1a (pin 4). With the x10 switch in the x1 position adjust the preset pot to obtain zero volts.

If the gain control is now increased, the meter reading will move along with the frequency of the clicks.

Threshold Advances

Now, advance the threshold control and the meter reading and click frequency should decrease. This threshold control works by varying the minimum signal required to cause a meter response. The higher the threshold control is set, the higher the input signal must be to cause a meter response. The threshold can be set just above the noise level so that even a very small input signal can be detected.

The electrodes can now be connected to the body and plugged in. The ideal way to secure the electrodes to your skin is to use a band of Velco tape, although we found Band-aids okay. If all three electrodes are placed reasonably close to each other along the inside of the arm (earth between the others) they can be secured in place all at once with a single wide band of Velco wrapped right around the arm. Some electrode paste may be used between the electrodes and the skin to improve the contact. This is available from some distributing chemists and medical suppliers, although it is relatively expensive. We found moistening the electrode to be a good alternative.


Once the electrodes are attached to the arm and plugged into the EMG monitor a reading should be easily obtained. Start with the gain and threshold controls set fully anti-clockwise, the gain switch in the X1 position and the integrate switch off.

If the arm is tensed the meter should indicate muscle activity readily. With these settings the EMG is really acting as a strength meter. Relaxing the arm, the gain switch can be switched to the x10 position and the gain control slowly increased. With each gain increase, the threshold can be increased slightly to cancel any increase in noise that may have occurred, although don't overdo the use of the threshold control until you are familiar with the unit as it is easy to cover up muscle activity as well as noise.

Eventually you should reach a stage such that the gain control can be set at maximum but with muscle activity held so low that the meter reads about 2 to 3. This isn't easy!

Some experimentation with electrode placement will indicate how to get good results on particular muscles.

B.K. ELECTRONICS

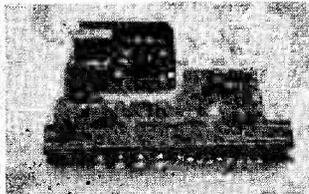

AM/FM Stereo Tuner Amplifier chassis (originally designed for installation into a music centre) Ready built, comprising of a tuner/pre-amp. board and separate power supply/power amp. board. Note: Interconnection wiring diagram supplied.

Rotary Controls: Tuning, on/off volume, balance, treble, bass.
Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), L.W. M.W. S.W.
Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.
Frequency Response: 60Hz-20KHz within ± 3 dB.
Tape Sensitivity: Output — typically 150 mv. Input — 300 mv for rated output.
Disc Sensitivity: 100 mv (ceramic cartridge)
Radio: FM (VHF) 87.5MHz-108MHz. Stereo beacon lamp.
Long Wave: 145KHz-265KHz.
Medium Wave: 520KHz-1620KHz.
Short Wave: 5.8MHz-16MHz.
Size: Tuner — 2 3/4in. x 1 1/2in. x 7 1/2in. Approx. Power Amp — 2in. x 7 1/2in. x 4 1/2in. Approx.
240 volt AC operation. Complete with circuit diagram. Price — £22.00 + £2.50 P&P.

LOUDSPEAKER. High quality 8" loudspeaker, 10 watts RMS 8 ohm. Rolled surround with aluminium centre cone. £5.00 + £1.00 P&P.

STEREO MAGNETIC CARTRIDGE BARGAIN. Acos M6EX stereo magnetic cartridge with tapered bi-radial diamond styli. Recommended tracking weight between 1 and 2 grms. Output 2.8 MV into 47 Kohms. 12.5mm (1/2 inch) fixings with a recommended retail price of £27.00. This is offered at a very special price of £9.00 (Post Free).

LOUDSPEAKERS. Genuine walnut veneered cabinets with fabric fronts — size 11 1/2" x 9 3/4" x 5". Fitted with 8" x 5" units rated at 6w RMS, 8 ohms. £9.75 per pair + P&P £2.50.

ELECTROLYTIC CAPACITORS (CAN TYPE). 3300 μ f 25v working. 40p + 30p P&P. 2500-2500 μ f (dual type) 63vv. 70p + 30p P&P.

TRANSFORMERS (0-240v primaries). 16v-0-16v @ 2 amps £2.50 + £1.00 P&P. Dual voltage 0-12v, 0-35v @ 4 amps or 1.5 amps respectively £2.50 + £1.00 P&P.


MAIL ORDER ONLY (DISCOUNT FOR QUANTITY)
 Cheque/Postal Orders with Order Please

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex.

Great new Crofton double!

Self contained MONITOR PCB

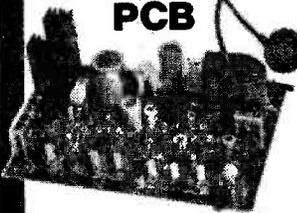

- Compact size, 5" x 7"
- Complete with power and video plugs, plus leads
- Scan coil assembly as standard supplied
- Transformers, tubes, and surrounds available
- 15v Mains or 12v DC power
- Ideal for O.E.M. use

- Totally enclosed
- All transistorised
- Suitable for analogue signals or alphanumeric
- Operable on 220v Mains or 12v DC power
- Comparable to wire frame monitors

ONLY **£35.50** ONLY **£85.00**
 EX VAT AND P&P

OHIO SUPERBOARD II
£188 + V.A.T.


Crofton Electronics

Crofton Electronics Limited, 35 Grosvenor Road, Twickenham, Middlesex. Tel.: 01 891 1923



10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo pre-amplifier module, two LP1173 power amplifiers with integral heat-sinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance) switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit. Size approximately 9 1/4" x 8 1/4" x 4" p&p £2.25 **£12.25**

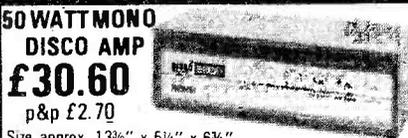

50 WATT MONO DISCO AMP

Size approx. 13 3/4" x 5 1/4" x 6 1/4"
 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. **£30.60** p&p £2.70



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and push-buttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/4" x 3" x 10" approx. **NEW feature**—units now includes a built in four channel stereo sound facility. **£31.90** £3.00 p&p

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK



SEE OUR PRICES

- PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£5.00** p+p £1.00
- PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **illus. OUR PRICE £7.65** p+p £1.00

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus £1.50 p&p

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT Per stereo pair plus £1.55 p&p **£4.05**



323 EDGWARE ROAD, LONDON, W2
 2H HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
 All items subject to availability. Price correct at and subject to change without notice.
 All enquiries Stamped Addressed Envelope.

NOTE: Persons under 16 years not served without parent's authorisation.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4 to 15 ohm speakers **£31.50** p&p £3.00

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts-RMS 20 watts max. 8 ohm impedance. **£18.25** Per stereo pair £3.65 p&p

BSR P200 £25.50

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £2.60
 Shure M75 6 Magnetic Cartridge to suit. **£7.95**



BSR Manual single play record deck with auto return and cueing lever fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use. OUR PRICE £12.25 p&p £2.75

BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00. **OUR PRICE £11.95** p+p £2.50

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

NEW FROM CASIO FOR 1980

A new range of high quality water-resistant watches at unbeatable prices

111QS-34B 8 digit display of hours, minutes, seconds and date. Lithium battery. Similar to F-8C but with chromed metal case, s/s bracelet (£17.95) **£14.95**

F-80 A major price breakthrough for a quality alarm chronograph. Lithium battery. Black resin case with stainless steel trim. Real value for only **£19.95**

95QS-36B Chronograph. 1/100 second timing to 7 hours. Net, lap and 1st & 2nd place. Dual time. 12 or 24 hour display. Day, date, month and year calendar pre-programmed to 2029. Lithium battery. Stainless steel case (£24.95) **£19.95**

81QS-35B Alarm chronograph. Similar to above with with alarm and hourly chime facility instead of dual time. Lithium battery. Stainless steel (£34.95) **£29.95**

Full details and illustrations on request. S.A.E. or stamp, please

CASIO HR-10

Probably the world's smallest print and display calculator

10 digit LCD display. Electric discharge printing system. Decimal mode selector. Prints full-month calendar for any month from 1901 to 2099. 3 key full access memory. Sign change and percentage keys. 3 way power source. Dry batteries/rechargeable batteries/AC mains adaptor. 1 1/2 x 3 1/2 x 6 1/2 inches. 40.5 x 88 x 168 mm.) £34.95E

ONLY £29.95

CALCULATOR ALARM CLOCKS

MELODY 81 A more melodic version of the ML-80 at a lower price! With alarms, alarm timer and 1/10 second stopwatch (£27.95) **£22.95**

ML-71 Similar to above but credit card size (£27.95) **£22.95**

MQ-12 Credit card size with alarm, 1/10 second stopwatch and full-month calendar display (£24.95) **£19.95**

Full details and illustrations on request. S.A.E. or stamps, please

MASTER PACKAGE DEAL CASIO FX-501P and FX-502P Programmable calculators

SEE LAST MONTH'S ETI FOR A GLOWING REVIEW OF THE FX-502P "The best thing since sliced bread"

FX-501P (£64.95 Usual price) **£54.95**

FX-502P (£84.95 Usual price) **£74.95**

FA-1 (£24.95 Usual price) **£19.95**

Master Pack (Premier publications) **£17.95**

We will supply the Master Pack for **ONLY £5**

When you buy the 501P/502P and

FA-1

FX-501P + FA-1 + MP **ONLY**

£79.90

FX-502P + FA-1 + MP **ONLY**

£99.90

Master Pack comprises CASSETTE with over 150 ready-to-run programmes and USER MANUAL.

Full details on request. Large S.A.E. or stamp please

DON'T FORGET. We are never knowingly undersold and will try to match or beat any advertised price providing the advertiser has stocks

Price includes VAT and P&P. Send cheques, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS Dept. ETI, Beaumont Centre, 164-167, East Road, Cambridge CB1 1DB. Telephone 0223 312866

All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented "clip on" easy fitting

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the normal

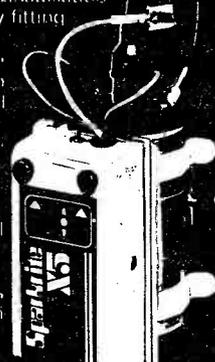There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE EVERYTHING NEEDED

Die pressed case - Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver, says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. ETI/3
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

inc. V.A.T. and P.P.

QUANTITY REQ'D.

I enclose cheque/PO's for

X5 KIT £16.95

£

ACCESS OR BARCLAY CARD No.

Cheque No.

Send SAE if brochure only required.

ELECTRONIC TRANSLATOR

Ian Graham reports on his adventures with the Brainbank electronic information centre.

Whilst phrase books are valuable little tomes for those of us with the 'why can't foreigners speak English?' syndrome, it can be infuriating to have to thumb through the food, health and shopping sections to find out how to ask an impatient Parisian police person where their copy of Blackpool Tower is.

As I see it you have two alternatives. You could follow Jonathan Miller's observation of the British abroad. If you speak to a foreigner loud enough and sufficiently slowly, clearly enunciating every word, he's bound to understand you . . . eventually. The assumption is that all foreigners can speak English perfectly well, but are too bloody-minded to use it.

However, if you don't suffer from galloping xenophobia, you will accept that some of the onus of being understood abroad lies with you. Wouldn't it be simpler if you could select the word you want from hundreds of others without going through the others first? The Ami Memory System allows you to do that *and* a lot more.

Multi-Access


Although it can be used as a calculator and a desk diary, its chief use (and the reason why it's likely to be bought) is as an electronic translator. It can cope with single words and short phrases. You can also get at the words in a number of ways.

Four stores are accessible through the keyboard. Buttons L1, L2 and L3 permit access to plug-in memory cells. L4 is a general-purpose on-board memory. It contains common imperial/metric conversions, gallons to litres, etc and over twenty common words and phrases, available in French, Spanish and German.

Button-Pushing

On receiving the 'Brainbank', the first thing you must do is turn it upside down. Some of its capabilities are inscribed on its bobby.

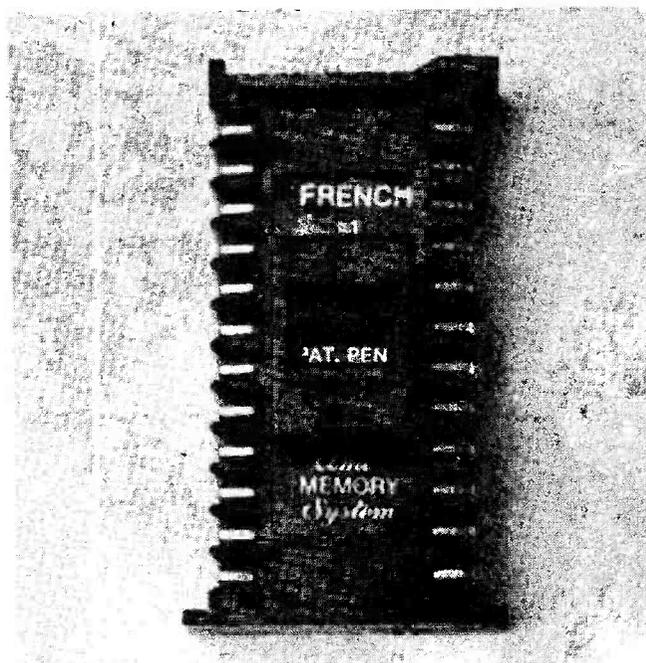If you know the word you want to translate, you can punch in the English word. On the model I had, L1 was in English, L2 French and L3 German. So, to translate your word into French, just press L2, the screen blanks for a moment, then up comes your translation. It couldn't be simpler.




Schooldays might be a bit more fun, if you could plug in one of these to learn French. It's one of Brainbank's memory cells.

Re-Search

But what happens if the Box of tricks doesn't know your word? Let's take an example. Translate ABILITY into German. When you punch in ABILITY and press L3 for German, each letter is miraculously transformed into a dotless question mark. The Brainbank doesn't understand you. You can now press the SCH (search) key. The machine will then start taking letters off the end of your word until it recognises what is left and can compare it with words it knows. ABILITY is cut down to AB. Brainbank (or BB to its friends) will then go through its store of English words beginning AB. The first one is ABLE. So, you can now have a bash at forming your sentence a slightly different way.

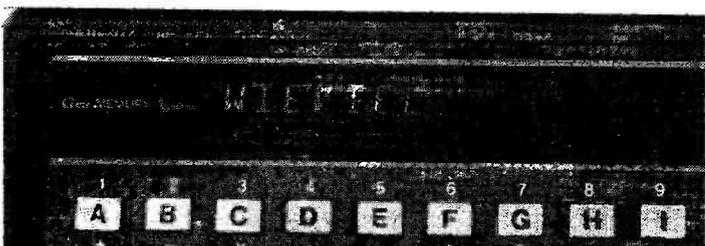If you're not a superb speller of the Queen's lingo, the search facility eliminates any difficulties arising from your own bad spelling. You can see the memory cycling through all the possible words on the display.



At the touch of a button you can translate straight from English to French or German and vice versa.

Although L1 is programmed in English, you don't have to swap the chips round in order to translate, say, from French into English. As you're strolling down the rue and you see an arrow directing you to the gare, switch BB on, press L2 (for French), punch in GARE and press L1 (for English) — Up flashes TRAIN STATION.

Phrases

If you want a well known phrase, the chances are that you won't have to enter the whole thing, letter by letter. Have a look at BB's botty again. You can press PHR (phrase) plus any one of 26 letters, each of which represents a word or a complete phrase. For instance, pressing PHR plus V will enter 'Do you change traveller's cheques?' Pressing PHR twice plus a letter will enter partial phrases eg PHR PHR D

will flash 'I am looking for . . .' on the display.

You can also access words by category eg pressing HOTEL plus LRN will make BB cycle through words relating to hotels. Pressing LRN again stops the cycling process and you can translate the word you want.

Summing Up

BB can also be used as a calculator, albeit a rather slow one. The calculation of two times four takes around three seconds, so BB is unlikely to be bought as a pocket calculator alone. However, it is convenient to have the simple four function calculation facility built in. It saves carrying an extra box around.

Extras

BB has one or two luxury extras. If you would prefer to see the words moving from right to left across the display instead of flashing up at the same end everytime, you can do just that with the ROT (rotate) key.

If you can soak up the words faster than BB's standard rate you can speed things up with the F/S key.

Hardware

Six plug-in language cells were available when we first heard about BB (English, French, German, Spanish, Italian and Portuguese) with Japanese and Arabic due in the following weeks. Each cell holds 1200 of the most common words, together with 25 complete and 25 partial phrases. Up-rated cells containing 9,600 words should soon be available. That's good news, as even 1200 words is rather restricted.


Cells covering pronunciation, diet and nutrition, first aid, taxation and a thesaurus are already complete. A cocktail mixer guide, a spelling guide and word games and puzzles are on the way. Blank cells which the user can program through the keyboard are also imminent.

The Brainbank is powered by four HP7-size cells (giving ten hours of continuous operation) or by rechargeable nickel cadmium batteries.

Your cheque for £150 or thereabouts will buy you one Brainbank, complete with mains adaptor, battery charger and one free cell. Extra cells will cost less than £20. Brainbank is marketed in the UK by Ring Electric.

If you want to see Brainbank 'in the flesh', it is on display at the 'Challenge of the Chip' exhibition at the Science Museum in London until June.

ETI

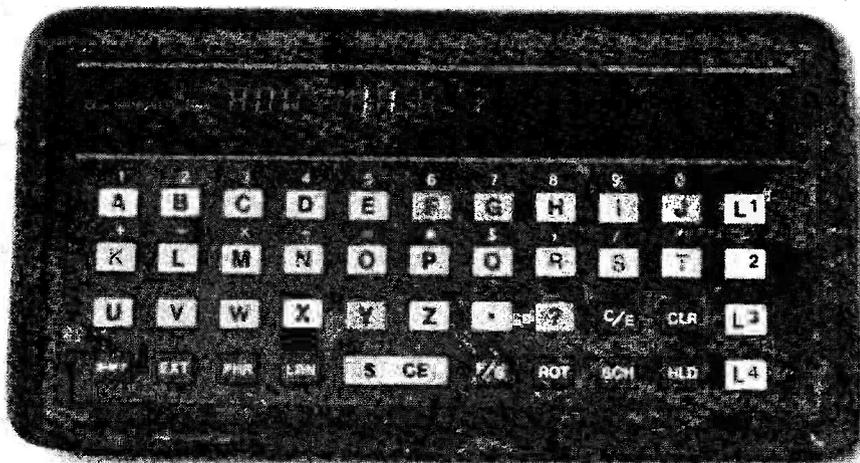

One criticism of Brainbank is the keyboard layout. A QWERTY board would be much quicker to operate. You can use the superior symbols and numerals by using the shift button just as on a normal typewriter OR by pressing the EXT button, you can use Brainbank as a calculator until the next time you press the CLR button.

HEATER CONTROL

A hyper-efficient circuit that can be used to give automatic precision control of any electric heater unit with a power rating not exceeding 3 kW. The unit can maintain room temperatures to within 0.5 C of a pre-set value


This unusual project is designed to impart automatic precision electronic control or regulation to virtually any electric convector or radiant bar heater with a power rating not exceeding 3kW. The heater is simply plugged into the electronic controller, which uses a remotely-mounted sensor/control unit to sense room temperature. The circuit can maintain the room temperature within 0.5° C of a pre-set value. Desired temperatures can be pre-set via the sensor/control unit.

The action of the ETI controller is such that, when first activated, it turns the heater on at full power until the room temperature rises to within a degree or two of the desired temperature and then progressively reduces the heater power output until the precise desired temperature is attained. From that point on, the controller maintains the room temperature within 0.5°C or so of the desired value and automatically adjusts the heater power output so that it exactly balances the thermal losses of the room: if an additional person enters the room, the controller reduces the heater output by an amount equal to that person's radiant body heat, thereby maintaining a thermal balance.

Zero RFI

Conventional thermostat-controlled electric heaters suffer from two major defects. First, their crude on/off electro-mechanical switching action gives poor thermal regulation and causes room temperatures to vary in a repeating series of thermal overshoots and under-shoots. Secondly, because the thermostat switching action is not synchronised to the mains frequency, the thermostat causes high switch-surge currents to be generated and generates a high level of RFI (radio-frequency interference).

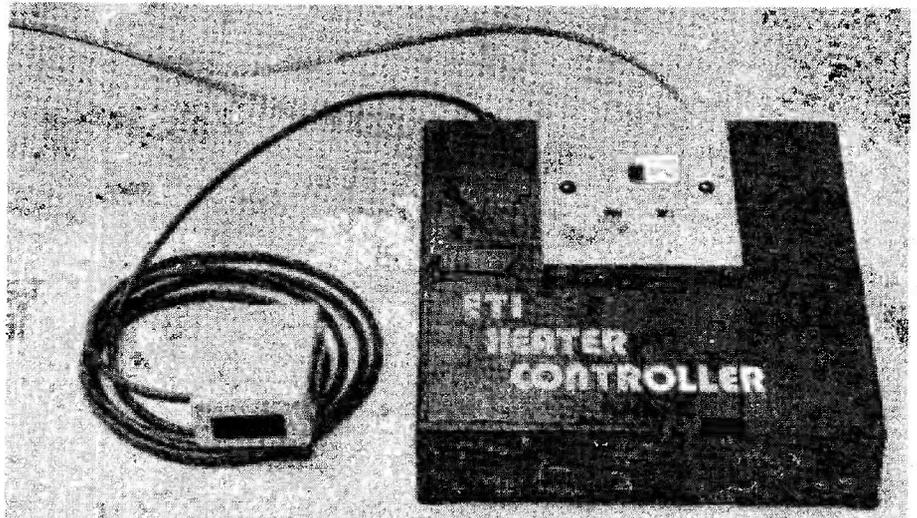The ETI controller, by contrast, uses a solid-state mains-synchronised triac to switch up to 2kW of mains



power to the heater. The switching action is synchronised to the 'zero crossover' points of the mains cycles and consequently causes virtually zero RFI generation. The triac is controlled via a thermistor proportional or 'burst fire' control circuit which enables the mean power output of the heater to be infinitely varied between zero and maximum and thereby enables the temperature to be regulated with negligible over-shoot or under-shoot.

The complete control unit uses only a handful of components, including two ICs and the triac. It can be built in an evening, at a total cost of about £15, including the case and 13A output socket.

Construction

Construction should present few problems. The unit uses two PCBs. The small board holds the remotely-located RV1-TH1 sensor/control components. All remaining components are mounted on the larger board, which is housed in the main units case. The 2N5574 triac is fixed to a large (64mm x 100mm) heat sink which is bolted directly to the PCB. The two ICs are mounted in suitable holders. The completed PCB is bolted

to the case base-plate via stand-off insulators.

The remotely-located sensor/control board is mounted in a small (25mm x 50mm x 72mm) plastic Vero 'potting' box, which can be fixed in a suitable location via sticky-pads. The lower end of the box must be cut away to allow air to reach the temperature-sensing thermistor. A small hole should be drilled in the front of the case to allow screwdriver access to the RV1 'set temperature' pot.

On our prototype, we used a 3-pin DIN socket to connect the sensor unit to the main unit. You can use direct wiring if you prefer. When you complete the interwiring of the unit, remember to use adequately rated cables and plugs and sockets: the unit is intended to carry up to 13 amps of mains current!

Note that there is no need to fit the unit with fuses or on/off switches, as these should already be provided via your mains plug and socket. If the triac does short-circuit, the heater will simply lock on and no significant damage will be done.

Using the Unit

When construction is complete, plug ▶

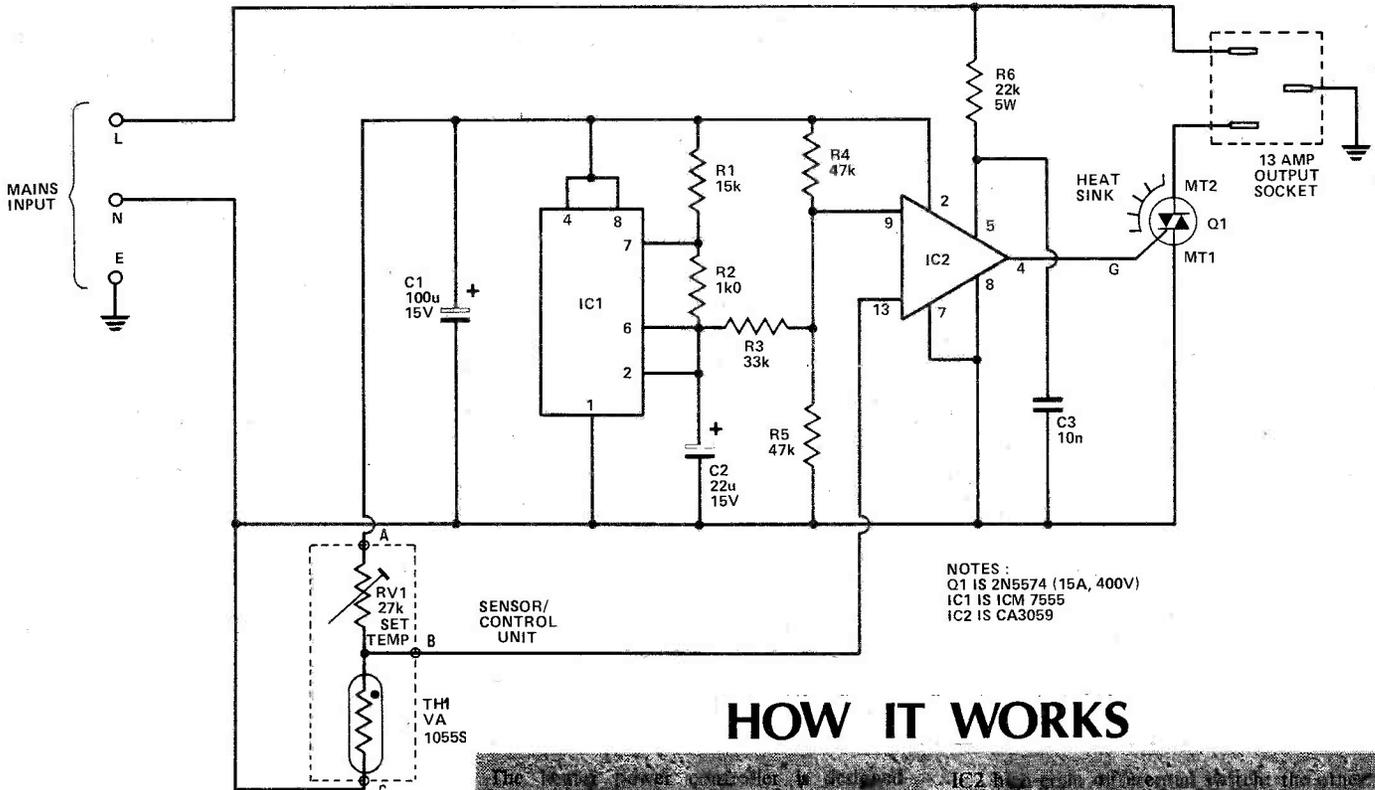


Fig. 1. Circuit diagram of the heater controller and remote sensor unit.

a heater into the unit, plug the unit into the mains and give the unit a functional check: if possible, temporarily wire a lamp in parallel with the heater, as this will give you a visual indication of the functional operation. Adjust RV1 and check that the heater/lamp load can be turned on and off via the preset pot. When RV1 is set to a value corresponding with the prevailing ambient temperature, power should pulse to the load at the timebase rate and the heater output should set to some value below maximum. If this action is obtained, the circuit is functioning correctly and you can complete the installation of the system.

When you install the system, be sure to fit the sensor/control unit in a position away from draughts and local sources of heat. Set RV1 by trial and error so that the heater produces a reduced output at the desired room temperature. If your heater is provided with its own thermostat, set the thermostat to maximum.

If your heater is fitted with a built-in lamp, you'll find that an annoying 'pulsing' action occurs as the heater power is regulated. You can overcome this problem by either disconnecting

The heater controller unit is designed around a 555 timer, plus a second purpose of an on-off controller which has a 1000V version of the well known 555 timer.

The sensor unit is made up of a 555 timer, which acts as a pulse generator, and a 1000V power MOSFET, which is used as a switch. The sensor unit is powered via a 15V supply, which is fed from the mains via a transformer. The pulse rate and amplitude of the output are set by the values of the resistors and capacitors in the circuit. The output of the sensor unit is connected to the heater unit, which is a 1000V power MOSFET. The heater unit is powered via a 1000V supply, which is fed from the mains via a transformer. The heater unit is controlled by the sensor unit, which provides a pulse to the gate of the MOSFET, which in turn switches the heater on and off.

The sensor unit section is detailed in Fig. 1, which shows a mains transformer, a 1000V power MOSFET, and a 1000V power MOSFET. The sensor unit is powered via a 15V supply, which is fed from the mains via a transformer. The pulse rate and amplitude of the output are set by the values of the resistors and capacitors in the circuit. The output of the sensor unit is connected to the heater unit, which is a 1000V power MOSFET. The heater unit is powered via a 1000V supply, which is fed from the mains via a transformer. The heater unit is controlled by the sensor unit, which provides a pulse to the gate of the MOSFET, which in turn switches the heater on and off.

the lamp or providing it with an independent connection to the mains input terminal of the controller unit. ETI

HOW IT WORKS

IC2 has a gain of 10,000, which is the other side of the output, it is fed from the top of the output of RV1. The output of IC2 is connected to the heater unit, which is a 1000V power MOSFET. The heater unit is powered via a 1000V supply, which is fed from the mains via a transformer. The heater unit is controlled by the sensor unit, which provides a pulse to the gate of the MOSFET, which in turn switches the heater on and off.

When the room temperature is higher than a preset level, the sensor unit sends a pulse to the heater unit, which in turn switches the heater on. The heater unit is powered via a 1000V supply, which is fed from the mains via a transformer. The heater unit is controlled by the sensor unit, which provides a pulse to the gate of the MOSFET, which in turn switches the heater on and off.

As the room temperature falls below the preset level, the sensor unit sends a pulse to the heater unit, which in turn switches the heater off. The heater unit is powered via a 1000V supply, which is fed from the mains via a transformer. The heater unit is controlled by the sensor unit, which provides a pulse to the gate of the MOSFET, which in turn switches the heater on and off.

If the room temperature drops below the preset level, the sensor unit sends a pulse to the heater unit, which in turn switches the heater off. The heater unit is powered via a 1000V supply, which is fed from the mains via a transformer. The heater unit is controlled by the sensor unit, which provides a pulse to the gate of the MOSFET, which in turn switches the heater on and off.

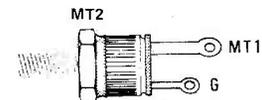


Fig. 2. Q1 outline

PARTS LIST

Resistors

R1	15k
R2	1k0
R3	33k
R4,5	47k
R6	22k 5W

Potentiometers

RV1	22k 0.25W horizontal preset
TH1	VA1055s

Capacitors


C1	100u 25V electrolytic
C2	22u 25V electrolytic
C3	10n polyester C280

Semiconductors

IC1	ICM7555
IC2	CA3059
Q1	2N5574 (15A 400V)

Miscellaneous

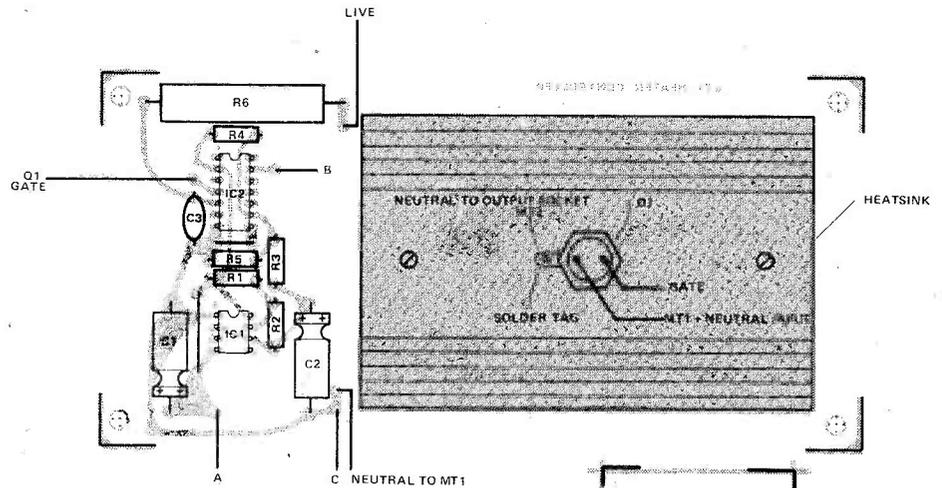13A MK socket; 3pin plug + socket;
 1/2" grommet; 1/4" grommet; Vejo
 potting box order code 202-21025K
 heatsink 100mm x 65mm.



BUYLINES

The case chosen for the Heater Power Controller was obtained from CSC Ltd (see below for address), order as DMC-1.

The CA3059 IC can be purchased from Marshall's, all other components used are readily available from major stockists that advertise in this issue.
CSC (UK) Limited,
 Shire Hill Industrial Estate,
 Saffron Walden, Essex CB11 3AQ
 Phone: (0799) 21682.

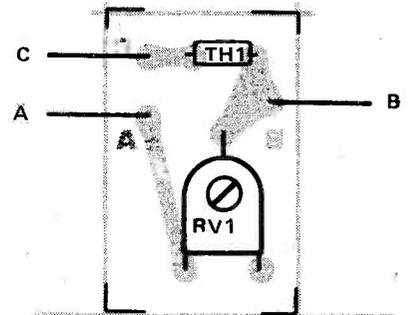


Fig. 3a (top) Component overlay of main control unit.
 Fig. 3b (above) Component overlay of remote sensor.

WEST HYDE CASES FOR E.T.I. PROJECTS

Soil Probe (July 1979) Order Code BOC 410

Bench Amplifier (August 1979) Order Code WEC 801

Audiophile Pre-Amp (October 1979) Order Code CL2 CDL

Audiophile Power Amp (October 1979) Order Code CL2 CGL


Audiophile PSU (October 1979) Order Code CL2 AEL

Pinball Wizard (November 1979) Order Code TEK 364

Points Controller (December 1979) Order Code BOC 680

Moving Coil Pre-Amp (January 1980) Order CL2 ADJ

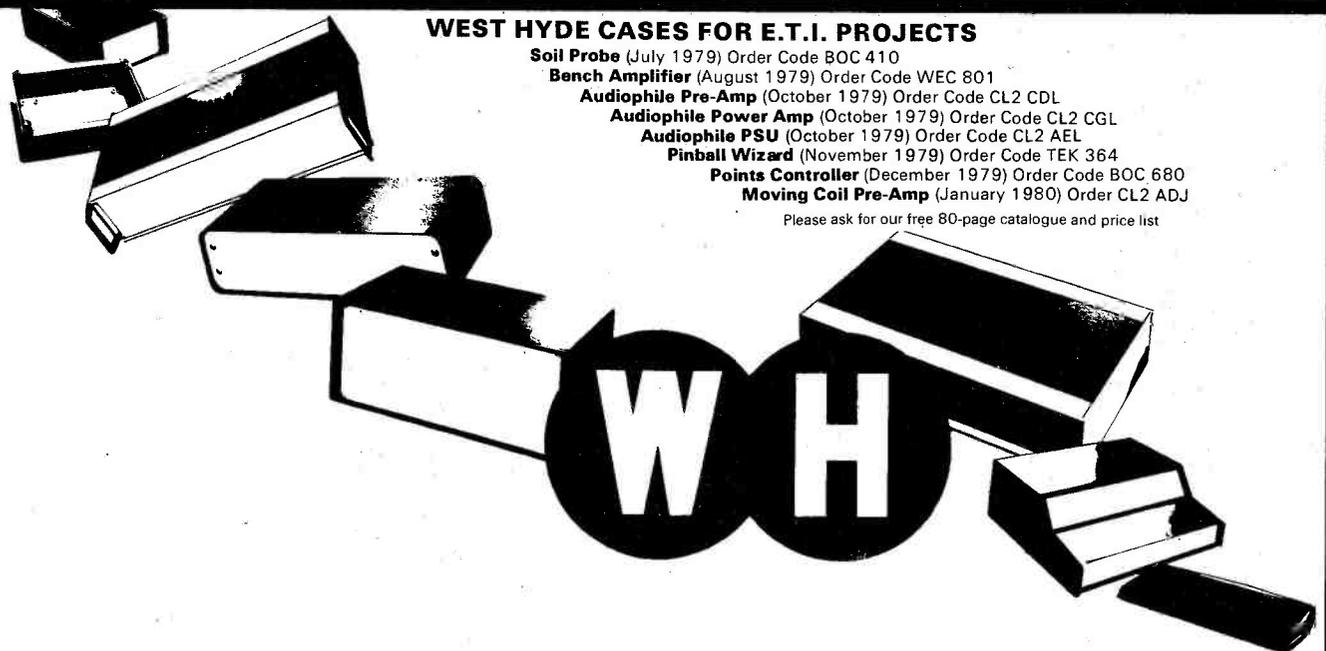Please ask for our free 80-page catalogue and price list



THE BIGGEST SELECTION OF CASES IN EUROPE

WEST HYDE



WEST HYDE DEVELOPMENTS LIMITED, UNIT 9, PARK STREET INDUSTRIAL ESTATE, AYLESBURY, BUCKS. TEL: 0296 20441

24 TUNE DOOR CHIMES

DOOR TUNES £17.19 + VAT

Waddington's Videomaster announce a doorbell that doesn't go Brrringgg, Ding-Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



T.V. GAMES

PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are bell serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES:

ROAD RACE - £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

SUPER WIPEOUT - £8.17 + VAT.

10 different games of blasting obstacles off the screen.

STUNT RIDER - £12.11 + VAT.

Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.

NONPROGRAMMABLE TV GAMES

9 Game - COLOURSCORE II - £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS


STAR CHESS - £95.00 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces, Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour (or black and white) on your TV screen. Based on the moves of chess, it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free TV mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 - £95.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Castling, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.

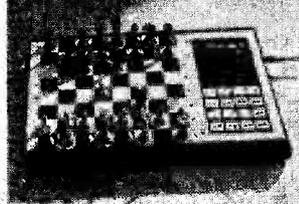

ELECTRONIC CHESS BOARD TUTOR £17.37 + VAT

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than our recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.


OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:
CHESS CHAMPION - 6 LEVELS £47.30 + VAT.
CHESS CHALLENGER - 10 LEVELS - £130.70 + VAT.
BORIS - MULTI-LEVEL TALKING DISPLAY £163.04 + VAT.

DRAUGHTS COMPUTERS

CHECKER CHALLENGER 2 LEVELS £43.00 + VAT 4 LEVELS £78.00 + VAT

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

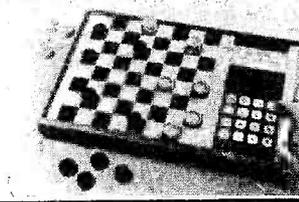PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.
 Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon-Sat (9am-1pm Wed).
 To order by telephone please quote your name, address and Access/Barclaycard number.
 Postage and Packing FREE.

**AJD DIRECT SUPPLIES LIMITED, Dept. ET3 102 Bellegrave Road,
 Welling, Kent DA16 3DD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)**

Microcomputers are coming - ride the wave! Learn to program

Millions of jobs are threatened, but millions more will be created through the microcomputer revolution. Will YOU sink or swim? Be one of the people who welcomes computers and the end of boring jobs.

Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency - all you need to start with is a knowledge of simple arithmetic and the use of decimals. And you don't need a computer.

This unique course comes as four A4 books, written by three authors well-known in the fields of microcomputing, self-instruction and writing clear English. In 60 straightforward lessons you learn the five essentials: problem definition, flowcharting, coding the program, debugging, and preparing clear documentation.

Every lesson has thought-provoking questions and we never ask for mindless drudgery. You will know that you are mastering the material and feel a rare satisfaction. Harder problems are provided with a series of graded hints, a unique and really helpful approach. So you never sit glassy-eyed with your mind a blank. First time through, you may need to read most of the hints, but you will soon learn to tackle tough programming tasks - such as writing programs for computer games, preparing graphs on an output printer, calculating compound interest tables and estimating costs.

COMPUTER PROGRAMMING IN BASIC £7.50

Book 1 Computers and what they do well; READ, DATA, PRINT; powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT; RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

FORTRAN COLORING BOOK £5.40

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others-this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

A.N.S. COBOL £4.40

Covers the most widely used computer language in business today. It teaches how to write a COBOL program and compile it effectively, paying proper attention to spelling, punctuation, and format.

THE ALGORITHM WRITER'S GUIDE £3.75

FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

The Algorithm Writer's Guide explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.



Cambridge Learning Enterprises

Understand Digital Electronics

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

- Book 1 Binary, octal and decimal number systems; conversion between number systems.
- Book 2 AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables.
- Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates.
- Book 4 R-S and J-K flip flops; binary counters, shift registers and half adders.

DESIGN OF DIGITAL SYSTEMS £11.50

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

- Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2 OR and AND functions; logic gates; NOT, exclusive-OR NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

O-LEVEL ENGLISH LANGUAGE £7.00

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on COMPREHENSION, Book 2 covers SUMMARY, PUNCTUATION & SPELLING, and Book 3 coaches you in the principles of COMPOSITION. Size: 3 A4 volumes totalling 250 pages.

SELF-INSTRUCTION COURSES



CAMBRIDGE LEARNING ENTERPRISES, UNIT 18 RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS PE17 4BR, ENGLAND.
TELEPHONE: ST. IVES (0480) 67446

All prices include worldwide postage (airmail extra)
If order comes to £15 or more, deduct £2
Please allow 21 days for delivery

GUARANTEE No risk to you.

If you are not completely satisfied your money will be refunded when books are returned in good order.

Please send me the following books:

- **Computer Programming in BASIC (4 books) at £7.50**
- **The BASIC Handbook at £11.50**
- **FORTRAN Coloring Book at £5.40**
- **A.N.S. COBOL at £4.40**
- **Algorithm Writer's Guide at £3.75**
- **Digital Computer Logic & Electronics (4 books) at £7.00**
- **Design of Digital Systems (6 books) at £11.50**
- **O-Level English Language (3 books) at £7.00**

I enclose a *cheque/PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Diner's Club/Access/Barclaycard/Visa/Eurocard/Mastercharge/Trustcard Account No.

(*delete where applicable)

Signature.....

Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers (inc. Eire) should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

Name

Address

Cambridge Learning Enterprises, Unit 18, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England.

TELEVISION SOUND

Rick Maybury takes the back off his telly (and his life in his hands) for ETI to give a few hints on improving TV sound

There was a rumour some years ago that one of America's top Hi-Fi manufacturers was using old television loudspeakers instead of fancy new ones in their systems. That actually makes some sense when you consider the amount of use the average telly speaker gets. The cone tends to lose its stiffness and enables it to cover a greater range of frequencies. Whether you believe this or not, one fact is beyond dispute. The TV speaker is probably the most 'used' speaker in any piece of household audio.

It is, therefore, surprising to consider that the circuitry devoted to handling audio frequencies within a TV set and the speaker that produces the sound was up to only a few years ago (and still is with some manufacturers) actually considered a nuisance. In the ideal world of the TV set designer there would be no sound. This is perhaps best illustrated by the speakers used. They are deliberately shaped to take up the minimum space. Elliptical speakers on their own may not seem too bad but just consider where they are sited. One manufacturer (who shall remain nameless) actually put it at the back, unable to find anywhere it could be usefully placed. Side facing speakers are not uncommon (even one on the bottom of the cabinet). Within the last five years something of a revolution has been taking place. Tone controls have been spotted on some sets. The growing awareness of the set-maker to the interest in audio have stirred the advertising men, looking for new features to sell their boxes. This has led to some rather dubious claims for quality, so it is perhaps a good time to look at the transmitted signal which, unless someone has managed to do without it, remains the be-all and end-all of the sound that emanates from your telly.

The quality of the transmitted sound is relatively high. The main factor from the broadcaster's point of view is source. The video tape recorder is probably the worst in that respect. The tape used for VTRs is designed for just that. The oxide particles that make up the catering are aligned to optimise the helical scanning of the VTRs recording/playback head. The audio track is usually arranged on the bottom edge of the tape and nearly always recorded in a linear fashion. Because of this the best bandwidth that can be expected will be around 10 kHz.

Live broadcasts and telecine material will do a little better, provided that the audio material is carefully handled something like 12 kHz can be expected.


The best quality undoubtedly comes from the 'simulcast' and separate synchronised audio recording. The audio material is recorded quite apart from the video on high quality studio tape recorders. At no time is this material ever allowed to come in contact with lesser machines and in theory at least, will have a bandwidth of something like 18 kHz. What it will be like by the time it comes out of your loudspeaker is another story.

At present there are two methods of transmitting a composite sound and vision signal used in the UK TV system.

The first and most obvious is to send the audio on a slightly different frequency or carrier to that of the video signal. This is the method used for domestic TV broadcasting at the moment. It has the rather glamorous sounding title of Intercarrier Sound. It involves transmitting the FM encoded audio on a carrier 6 MHz above the vision carrier. For instance, channel 21 on band IV — the video is

used in place of circuitry around trap L1, C1 — no twiddling possible! Please DO NOT attempt to twiddle anything before the intercarrier trap you will only regret it and that's a promise.

Fig. 1. Twiddling points within the sound signal path. (a) 6 MHz intercarrier sound trap coil, L1. (b) Balance circuitry for setting up coincidence detector demodulator now widely found on sets using TBA120 sound and IF detector ICs. (c) Ceramic filter sometimes

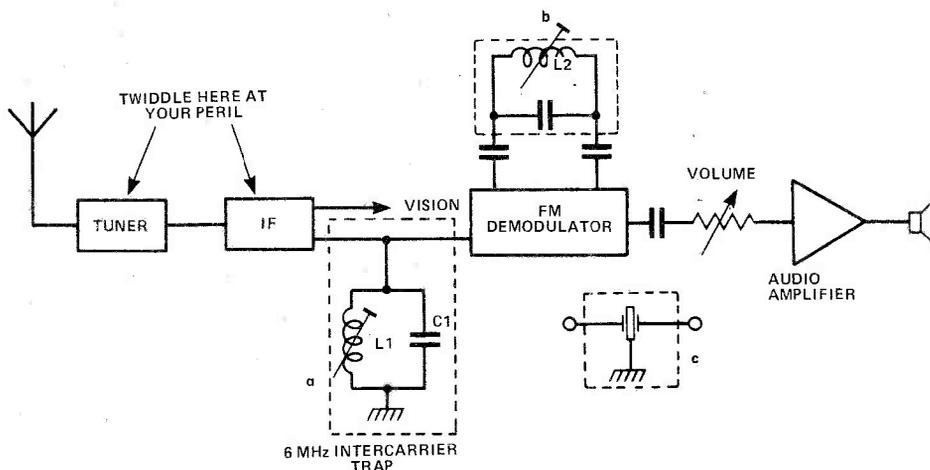

transmitted on a frequency of 471.25 MHz whilst the accompanying audio is to be found on 477.25 MHz. We will deal with Intercarrier Sound demodulation in more detail later on.

The second, less obvious method rejoices under the name of Sound in Sync or SIS. This is not used for normal broadcast transmissions but for transmission of audio between studio and transmitter or relay stations. This is a rather cunning technique utilising the space 'inside' the line synchronisation pulse that occurs at the beginning of every TV line. This pulse is sited at a point on the TV waveform 'below black level'. This means it occurs below a pre-determined voltage at which the TV receiver will recognise it as picture information. The sync pulse lasts for approximately 4.7 microseconds and occurs at a repetition rate of 15.625 kHz (line timebase frequency).

Because SIS occurs in a synchronisation pulse it has to be removed if the signal is to be displayed. Within the studio environment a filter is used to remove SIS for insertion in studio monitors. It is removed at the transmitter prior to encoding into intercarrier sound for normal broadcast.

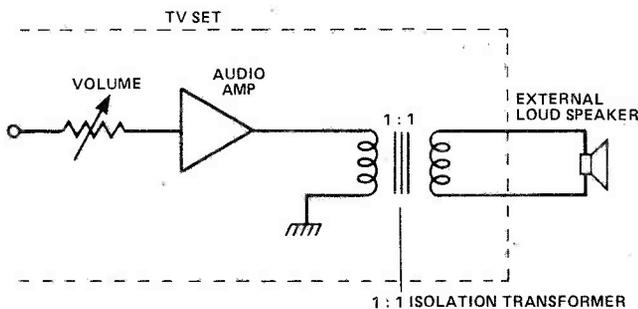


Fig. 2. Connecting an external speaker to a set with a live chassis (see fig. 4). Of course, if the set has an isolated chassis, the transformer is unnecessary and a direct connection may be made. Ensure the replacement speaker matches the impedance and power handling of the original.

Inter Sound

The broadcast sound is FM modulated onto a carrier with an impressive 8 MHz bandwidth. The peak FM deviation, ie the amount by which the signal deviates around the centre frequencies, is 50 kHz. This compares with a 75 kHz deviation on FM sound radio. The sound and vision signals make uneasy bedfellows, even being 6 MHz apart. A variety of problems can arise with these two signals, sharing as they do a great deal of common circuitry within the TV receiver — not the least being intermodulation resulting in a loud irritating buzz, aptly called Intercarrier Buzz.

Those are the bare bones of TV sound. From a critical standpoint the signal that leaves the TV transmitter is rarely the same one as the one coming from the set's loud-speaker.

If it is your wish to improve upon what greets your ears every night you have a problem. Basically you are limited by the original design. You have two courses of action open to you. Firstly you can take it upon yourself to build a

complete tuner/IF/demodulator. This is not recommended for the faint of heart. To get round this a couple of enterprising manufacturers have got TV sound tuners on the market. You would be hard pressed to improve upon them, let alone do it as cheaply.

The second, more practical route is to make the best of a bad job and improve upon what you already have.

The first and most obvious problem is perhaps the hardest to cure. That is the initial design. Modern receivers of the last few years have at least made some attempt to demodulate the sound responsibly. If your set is more than five years old — forget it. Proceed to step 2.

Step one. The aerial, the first link between the speaker and the incoming signal must be OK. As a general rule of thumb if the picture looks OK the sound will be. The colour TV is a very good indicator of signal quality being far less forgiving than a monochrome set. Look for noise or snow on the picture. If there is any, get a better aerial/move to an area with better reception/give up and proceed to step two.

The second principle of step one (confusing isn't it?) comes under the heading of alignment. Two symptoms to look for. Number one is intercarrier buzz. No big prizes for guessing how to recognise it. The second symptom of the second principle of step one (Prize for understanding that bit now available from the ETI offices) is called sound on vision. This is not necessarily detrimental to the sound quality but you might as well sort it out whilst you're at it.

Both these maladies point to one thing; poor alignment. The obvious remedy consists of whipping the back off your telly and twiddling the appropriate components. But hold on, which one. Most tellies have forty or fifty presets, coils, trimmers, etc just waiting for the eager, would-be twiddler. The answer here is arm yourself with a manufacturers' service sheet. You will be able to locate the audio section on the diagram quite easily. Just look for the loud speaker, amplifier section and decoder. On a modern colour TV just before the demodulator there will be a trap circuit. This usually consists of an LC network or a ceramic filter. For the sake of sanity DO NOT twiddle anything before this section. You will be entering the realms of IF alignment where only bold men tread, especially if you haven't got a wobulator. If you have, then you have our deepest sympathy (and why are you reading this anyway because your set should be perfectly aligned?)

Now having located the demodulator/audio section take a deep breath. **First thing to do is check up on your life insurance. Many thousands of volts run around the innards of tellies. Let them run up an errant finger and down your other arm, (the one clutching the gas pipe) and it won't really matter how bad your sound is on your TV set. The only noises you'll be hearing will be the strumming of heavenly harps (If you're lucky).**

Start again, are you sound of wind, limb and brain. Yes? Then look for the vision signal trap. Does it consist of a LC network. If it does, mark the position of the slug relative to the coil, with one eye on a reflected image of the screen (use a mirror in front of the set) and the other on your shaking hand. Twiddle, no more than half a turn either way. Look for any striation on the screen (that's wavy lines). If they disappear back off and try the other way. If on the other hand the picture contorts with the sound coming from the set then go back to the starting point.

To make matters clear, if there is sound on vision this may cure it, it may also cure intercarrier buzz. If nothing changes or gets worse then return the slug to its original position.

Our next twiddle, or first, if you didn't have the first, ▶

should be found around the demodulator circuit. As the sound is FM modulated you may be lucky and have a ratio-detector type decoder. If you have, chances are that there is another twiddle in store.

This time we will be setting up the decoder by ear. There is no practical way round it. Just twiddle and listen, keep looking at the screen, though nothing really terrible should happen. As always, make sure you know the starting point and NEVER twiddle more than half a turn either way. That way at least you should be able to get back to where you started without too much bother.

If neither of these exercises did anything for you, now is the chance for you to proceed to step two. It must be said however that if the sound is still really dreadful your IF stage is probably in need of attention. The only really capable people are the manufacturers themselves. Have a word with your local (friendly) TV serviceman about doing a swap. Most sets in the last few years use modular construction so the IF strip and/or tuner might just unplug and easily substitute for another.

tions I am about to make blow my set/house/self/cat up. If you can hold your hand on your heart and still pick up that soldering iron with an easy conscience, then proceed.

As we said earlier, the loudspeakers used in TVs can be particularly nasty items. Why not replace your one with a nice big 12in woofer? It won't fit in the case. Solution, disconnect the existing speaker making notes of impedance, power rating, etc and replace. Problem number one is likely to be the high voltages running around the speaker. Most modern colour sets have a metal chassis at around half mains potential. This is because of the types of power supply used do not employ mains transformers, or, if they do, they are of the auto type with no separate primary and secondary. You have been warned. Let not your fingers touch these wires or you will know all about it. Problem number two with this procedure is called visual/audio image separation. Be sure not to site the speaker too far away from the screen. You will have the disturbing effect of seeing the picture in front of you and the sound coming from one side or another. This is especially irritating when watching Crossroads, as it can appear that Meg Richardson is at the same time on telly and somewhere in your living room. To be avoided at all costs.

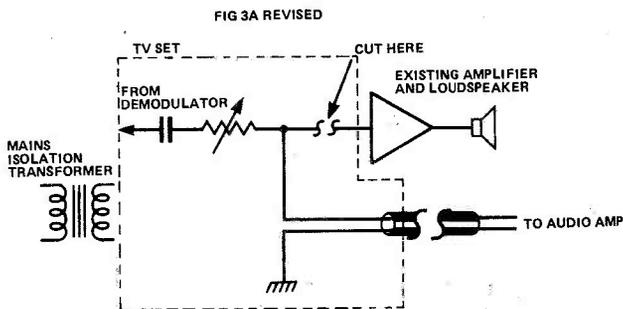


Fig. 3a. By isolating the set with a 1:1 mains isolation transformer, connections to the outside world should be safe. If your set has an isolated chassis, you should be OK.

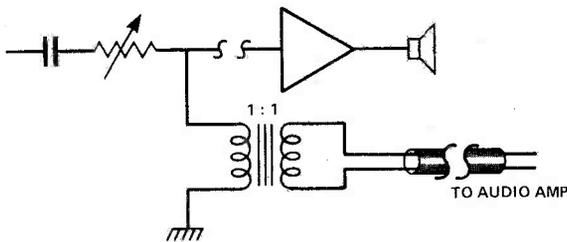


Fig. 3b. Using a 1:1 isolation transformer to prevent nasty shocks. The isolation transformer shown in fig. 4 is, however, the best solution for safe connection.

The Famous Step Two

Step two exists for those of you who are either scared of rooting about in the back of 'live' TV sets or have tried step one without success.

This involves modifications to your set. Two things must be ascertained before you pick up that soldering iron. Firstly, the set must be your own. It's no good trying to tell the man from Radio Rentals that you were trying to improve his set. Be assured something nasty will happen if you do. The second thing to consider is, will I mind if the modifica-

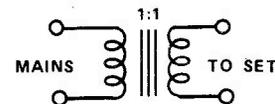


Fig. 4. Recommended method of isolating a TV set with a live chassis. Please note that the transformer should be rated at a minimum of 500 watts for a colour set.

The Step Three Bit

Step three is for the intrepid only. Going back to your trusty manufacturers' diagram, try to locate the point of entry of the audio signal into the audio output stage. Most manufacturers do this around the volume control area. The trick we are about to play here is to take this point, sever the connection between the volume control and the audio stage and introduce it to your expensive hi-fi equipment. The proviso in step two still holds good, but this time add expensive Hi-Fi to the list of things that could be blown up.

Because we still have the live chassis situation, you must first rid the wires coming from your set of any high voltages. A 1:1 mains isolation transformer is the only practical answer. Now you have to determine the impedance and level of the signal coming out of the demodulator. There is only one reliable way to do this. Measure the level on a 'scope. Use your judgement for the impedance. Safest bet (though don't blame us if it's not) is to assume it will be a fairly hefty signal and treat accordingly. All being well and nothing nasty happening, place your speakers either side of the telly and switch to Mono. You may be rewarded with a really rich sound, complete with a full set of tone controls. On the other hand you may be left with a smouldering mass of high technology that was the telly and the Hi-Fi. Seriously though, any of these methods outlined here should only be attempted if you have a very good grounding in electronics. **Do not on any account muck around with your set unless you know what you are doing.** If you don't then save up and buy yourself a TV sound tuner and you'll live to read all the complaints about this article next month from irate TV manufacturers.

ETI

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

026 Motor Speed Controller (2 Boards For Controller) Battery Indicator	July 79	033 LED Audio Display (2 boards) (topside pattern) Bench Amp NICD Charger	Aug 79	036D Power Switch Selector (double sided)	Nov 79
027 CCD Phaser Rev. Monitor	Project Book Seven	034 Cable Tester Reaction Tester Speech Compressor Preamp Power Supply Rectifier & De-Thump Board Power Amp (2) (price £1.60)	Nov 79	037A Encoder (double sided)	Dec 79
028 Race Track, Spirit Level Egg Timer, Bongos Bench Supply, Oscillator	Project Book Seven	035 Oven Leakage Detector Pinball Wizard	Nov 79	037B Decoder (top side)	Dec 79
029 Bass Enhancer Digital Freq. Meter (4 boards)	Project Book Seven	036A 3 x Display Board Relay Activator Points Controller	Nov 79	037C Decoder (bottom side)	Dec 79
030 ETIWET, Continuity Tester Metal Locator, Light Dimmer Ultrasonic Switch (2 boards)	Project Book Seven	036B Data Distributor (double sided)	Nov 79	038A Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79
031 Tone Control House Alarm (2 boards) Torch Finder	Project Book Seven	036C Train Speed Controller Track Cleaner & Electronic Pot (double sided)	Nov 79	038B Hum Filter Dice Logic Probe	Dec 79
032 LED Audio Display (2 boards) (underside pattern)	Aug 79			038C Function Generator	Dec 79
				039 Buffer Moving Coil Preamp Process Controller	Jan 80

HOW IT WORKS



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

BUY LINES

ORDER TODAY

Send a cheque or P. O. (payable to ETI Magazine) to:

ETI PRINT, ETI MAGAZINE
145 Charing Cross Road, London WC2H 0EE

80p INC P & P

LOW POWER SCHOTTKY TTL — EX STOCK

Device	Price	Device	Price	Device	Price
74LS00	13p	74LS85	80p	74LS174	65p
01	13p	86	36p	175	65p
02	13p	90	40p	190	100p
03	15p	93	70p	191	100p
04	14p	95	85p	192	100p
05	25p	107	40p	193	100p
08	30p	109	50p	196	100p
09	20p	112	50p	221	100p
10	19p	113	50p	244	220p
11	23p	114	50p	245	290p
12	25p	123	80p	247	100p
13	30p	125	30p	248	100p
14	40p	126	30p	249	90p
20	17p	132	50p	251	90p
21	21p	138	45p	279	165p
26	30p	139	75p	279	50p
27	15p	151	80p	283	100p
28	30p	153	45p	290	90p
30	15p	155	65p	293	100p
32	17p	156	90p	298	93p
37	20p	157	90p	352	110p
38	30p	158	70p	353	110p
40	17p	160	100p	366	50p
47	52p	161	100p	367	60p
49	52p	162	100p	368	55p
74	33p	163	130p	374	180p
75	32p	164	100p	386	35p
76	38p			670	150p

LOW PROFILE DIL SOCKETS BY TEXAS

8 Pin	8p	18 Pin	12p	24 Pin	16p
14 Pin	9p	20 Pin	13p	28 Pin	19p
16 Pin	10p	22 Pin	15p	40 Pin	30p

VERO PRODUCTS

Vero Wiring Pen (inc. 1 spool wire)	248p
2 X Spare Spools	85p
Spot Face Cutter	95p
Veroblock Breadboards	283p

VEROBOARD PCBs

2.5" x 5"	65p
2.5" x 3.75"	54p
2.5" x 17"	198p
3.75" x 5"	65p
3.75" x 17"	250p


CALCULATORS

Texet 1500	375p	Brain Wave	770p
Texet 1800	640p	Trader	900p
Scientific 2001	725p	LCD 300	940p

TERMS
Please add 35p for P&P plus 15% VAT to all orders. Export orders no VAT but postage at cost. Prompt delivery on all orders, Cheques, POs, Money Orders to be made payable to:—

ROMANE ELECTRONICS
64 Newlyn Drive, Sale, Cheshire. M33 3LE
Tel. 061-962 2606

— CLEF KITS —

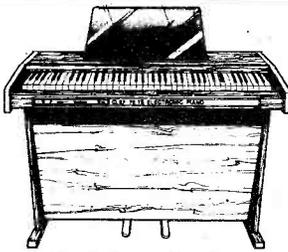

NEW — ELECTRONIC ROTOR
Two-speed organ rotor simulator plus a three-phase chorus generator on a single PCB (8" x 5"). Kit includes all components — IC sockets throughout — mains operation and stereo headphone driver PCB. Easily integrated with existing organ. Component kit **£89.00**.

KEYBOARDS
We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.
49 NOTE C-C **£23.80**
73 NOTE F-F **£37.00**
88 NOTE A-C **£45.00**
All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE
We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists.

INFORMATION
Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & Insurance.

VISITS
Are welcome by appointment, otherwise Mail Order Only.

EXPORT
Enquiries welcome — in Australia please contact JAYCAR (Sydney).

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.
JOANNA 72 & 88 PIANOS
Six and 7/4 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use, from our top quality Component kits.
SIX OCTAVES — **£184**
7 1/4 OCTAVES — **£209**
P.E. STRING ENSEMBLE
The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.
COMPONENT KIT — **£164**
Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.
P.A.'s — SPEAKERS — CABINETS
Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)
16 Mayfield Road, Bramhall, Cheshire SK7 1JU. 061 439 3297

MEN'S QUARTZ LCD
15 functions telling hours, mins., secs., month, date, plus back lighting, auto calendar.
Accuracy guaranteed by tuning fork quartz at 32768KHZ.
Only **£6.95** (inc. VAT P&P) Same day despatch

MUSICAL ALARM/CHRONO WITH 2 TIME ZONE
* 6 digits complex watch with chrono, musical alarm, alternate time zone with backlight
* Alphanumeric display of day-of-week in three languages: English, French and German (selected by user)
* The Chronograph, alarm and time zones can be used simultaneously, the flashing flags remind of all the running modes.
* When chronograph counts more than one hour and it is stopped, then the display will show hour, minute, second, hundredth alternatively.
Only **£24.95** (inc. VAT P&P) Same day despatch

LADY'S 5-FUNCTIONS WATCH
Gold/silver colour finish
* Hours, mins., secs., month, date, plus back light.
* Cocktail style
* 12 months' guarantee
Only **£12.95** (inc. VAT P&P) Same day despatch

LADY'S 5-FUNCTIONS WATCH
* Hours, mins., secs., month, date, back light
* Stainless steel 8mm thick.
Only **£9.95** (inc. VAT P&P) Same day despatch

LCD CLOCK
— 5 functions LCD car clock with back lighting.
— 4 digits display for month, date, hour, minute and second.
— Automatic month update for 4 years' operation.
— Simple 2 switch display and setting.
— Less than 1 cm. thick, mounts in, on or under dash in minutes.
— Can be used as table-clock by lifting the back support.
— Bright black digits, easy to read.
Only **£9.95** (including VAT P&P)

MEN'S LCD ALARM with Snooze
24hr. "Alarm"
* Hrs., mins., sec., date, month, day of week plus back light.
* 6 digits, 3 flags, plus continuous display of day and date or seconds
* 12-month guarantee
Only **£11.95** (inc. VAT P&P) Same day despatch

MEN'S "ALARM" CHRONO
— Hr., min., sec., day, date, month, B/light.
* 1/10 chronograph. Lap time.
* 6 digit plus day.
* 12/24 hour option.
* Month, date/date month
* 10mm thick
Only **£18.95** (inc. VAT P&P) Same day despatch

MEN'S CHRONOGRAPH
* 6 functions telling hr., min., sec., month, date., day of week, plus back light.
* Auto calendar
* 1/100 of seconds counting up to 1 hour.
* Time lapping to freeze the time with continuous timing.
12-month guarantee
Only **£10.95** (inc. VAT P&P) Same day despatch

LEYTRONICS LTD
12 Little Newport Street London WC2 7JJ Phone 01-437 4910

Payment can be made by sending cheque or postal order. Write your name and address and order details clearly. All products carry one year guarantee and full money back 10-day reassurance. Battery fitting service is available at our shops. All goods are sent by first-class post.

Shop open 7 days per week, 12 noon to 8 p.m.

ETI BOOK SERVICE

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

BEGINNERS

Beginners Guide to **Electronics** Squires £3.35
Beginners Guide to **Transistors** Reddihough £3.35
Electronics Self Taught Ashe £4.40
Beginners Guide to **Integrated Circuits** Sinclair £3.35
Understanding Electronic Circuits Sinclair £4.10
Understanding Electronic Components Sinclair £4.10
Beginners Guide to **Radio** King £3.35
Beginners Guide to **Audio** Sinclair £3.35

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00
Video Cookbook £7.00
TTL Cookbook £7.55
The Basic Cook £4.00 inc. p/p
IC Converter Cookbook £9.50

APPLICATIONS

Fire and Theft Security Systems B. Weis £2.00
How To Build Electronic Kits Capel £2.10
110 Electronic Alarm Projects R. M. Marston £3.95
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.95
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.95
110 Thyristor Projects Using SCRs R. M. Marston £3.95
110 Wave Form Generator Projects R. M. Marston £3.95

COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book £12.00
Beginners Guide to Computers and Microprocessors with Projects C. Adams £5.70
Basic Computer Games Ahl £5.25
Basic for Home Computers A self teaching guide B. Albrecht £4.95
Illustrating Basic D. Alcock £2.60
Intro to Microprocessors Aspinall £6.50
Z-80 Microcomputer Handbook W. Barden £7.75
How to Program Microcomputers W. Barden £7.25
Introduction to Microcomputers and Microprocessors A. Barna £8.60
Microprocessors in Instruments and Control R. J. Bibbero £12.60
Basic Basic J. S. Coan £7.80
Advanced Basic J. S. Coan £7.30
Getting Acquainted with Microprocessors L. Frenzel £7.10
Beginners Guide to Microprocessors C. M. Gilmore £4.85
Beginners Guide to Home Computers Grossworth £4.50
Beginning Basic R. E. Gosling £4.75
Microprocessor Programming for Computer Hobbyists N. Graham £7.10
Miniprocessors from Calculators to Computers Heiserman £5.00
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.00
Basic Programming J. G. Kemeny £6.55
Microprocessor Systems Design E. Klingman £17.00
Intro to Microprocessors Leventhal £16.70
Microprocessors — Technology, Architecture & Applications D. R. McGlynn £9.00
Programming Microprocessors McMurrain £5.50
Interactive Computing with Basic Monro £3.65
Basic with Style P. Nagin £4.25
Software Design for Microcomputers Ogdin £7.00
Microcomputer Design Ogdin £7.00
Microcomputer Base Design Peatman £7.00
Hands on Basic with a PET Peckham £8.70
Basic — A hands on method Peckham £6.95
6800 Software Gourmet Guide and Cookbook Scelbi £8.00
8080 Software Gourmet Guide and Cookbook £8.00
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.20
8080/8085 Software Design Titus £7.60
57 Practical Programs & Games in Basic Tracton £6.60
Microcomputer Primer M. Waite £6.50
Your Own Computer Waite £1.50
Microprocessor/Microprogramming Handbook Ward £6.20

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £5.10
Practical Digital Design Using ICs J. Greenfield £12.70
Designing With TTL Integrated Circuits Texas Instruments £9.05
How To Use IC Circuit Logic Elements J. Streater £3.65
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.95
Understanding CMOS Integrated Circuits R. Melen £4.00
Digital Electronic Circuits and Systems R. M. Morris £3.50
MOS Digital ICs G. Flynn £5.10

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10
Working with the Oscilloscope A. Saunders £4.10
Servicing with the Oscilloscope A. King £6.50
Radio Television and Audio Test Instruments King £6.80

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.30
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £3.95
Designing With Operational Amplifiers Burr Brown £16.65
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.40
Op-Amp Circuit Design & Applications J. Carr £4.00

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.50
Digital Signal Processing Theory & Applications L. R. Rabiner £23.80
Electronic Communication Systems G. Kennedy £8.50
Frequency Synthesis, Theory & Design Mannasewitsch £23.40
Principles of Communication Systems H. Taub £8.10

THEORY

Introduction to Digital Filtering Bogner £10.20
Transistor Circuit Design Texas Instruments £9.35
Modern Electronic Maths Clifford £6.70
Foundations of Wireless Electronics M. G. Scroggie £5.00

REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner £34.00
Electronic Components M. A. Colwell £2.60
Electronic Diagrams M. A. Colwell £2.60
International Transistor Selector T. D. Towers New update £8.70
International FET Selector T. D. Towers £4.35
International Op-Amp Linear IC Selector Towers £7.50
Radio Valve and Semiconductor Data A. M. Bell £3.45
Radio, TV and Audio Technical Reference Amos £24.85

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair £3.20
Integrated Electronics J. Milman £7.90
Practical Solid State DC Supplies T. D. Towers £6.20
Practical Triac/SCR Projects for the Experimenter R. Fox £2.25
Printed Circuit Assembly Hughes & Colwell £2.60

Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy way of getting your hands on the right title.

METAL LOCATOR

For discriminating treasure hunters, we present the Shadow metal locator from Altek, featuring deep-seeking VLF and discriminating operation.

The design of professional quality metal detectors is a specialist field which up until now the commercial manufacturers have kept very much to themselves. This design incorporates many of the latest techniques in push button VLF discriminators which have hitherto been the subject of well guarded trade secrets. The detector performs as well as commercial models costing over £200.

It uses a ready made search head, as a home-made one would have no hope of giving the results needed for a design of this nature (would you use a home-made speaker with your hi-fi?). The search head from Altek enables depths of over 12" for a single coin to be achieved.

Construction

The use of sockets for IC1 and IC5 is not recommended due to the increased risk of leakage currents in the push button circuitry. C12 is a very critical component. Its value is not too important but it must be of the highest quality, have low dielectric absorption and high resistance. Polycarbonate types were used, but polystyrene would be equally suitable.

To keep the design as tidy as possible 20 way ribbon cable is used to connect the board to the controls. As each colour appears twice they are differentiated by indicating from which side of the ribbon they come — either white or black (the colour of the wire at the edge of the ribbon). Circuit pins are used at all other connection points so that wires can be attached after the board is installed in the case.

Setting Up

When construction is complete and the detector appears to function it is necessary to make sure that the Rx



coil has been properly connected. Due to the way the head is aligned it is not possible to check it until this stage.

Hold the head away from all metal and set the controls as follows: MODE and GROUND fully anticlockwise. ALL OTHERS at mid-rotation. Depress the tuning button and hold it in, rotate the TUNE control until the meter needle is approx mid scale. Release the button and bring the head close to a metal object — the meter should be deflected to the right. If it goes left, reverse the wires from the Rx coil (see diagram).

Use

Using the detector and interpreting the results is very much a matter of experience but the following notes will help.

Tuning

To adjust, the push button must be depressed. When tuned to your satisfaction release the button. If the tuning point drifts then it can be brought back simply by pushing the button for a second or two. When first switched on the memory retune button will be needed every few seconds but as thermal equilibrium is established it will be needed less often.

Sensitivity


It is not necessary to set the sensitivity to maximum to achieve the greatest depth. Amplification is so great that a maximum setting may bring on instability. Experiment intelligently with it — mid-rotation is about right.

Ground

This only works in the VLF mode. Its setting is quite critical. First set the tuning with the head away from the ground. Move the head down to the ground and observe the meter. If it swings left — rotate GROUND clockwise, if it swings right — turn anticlockwise. Hold the head away from the ground and depress the button to reset the tuning. Repeat this procedure until the meter does not deviate when the head is lowered. A slight misadjustment is tolerable but if it is turned too far clockwise the detector will work in "reverse". When VLF is selected the detector is in its most sensitive mode.

Discrimination

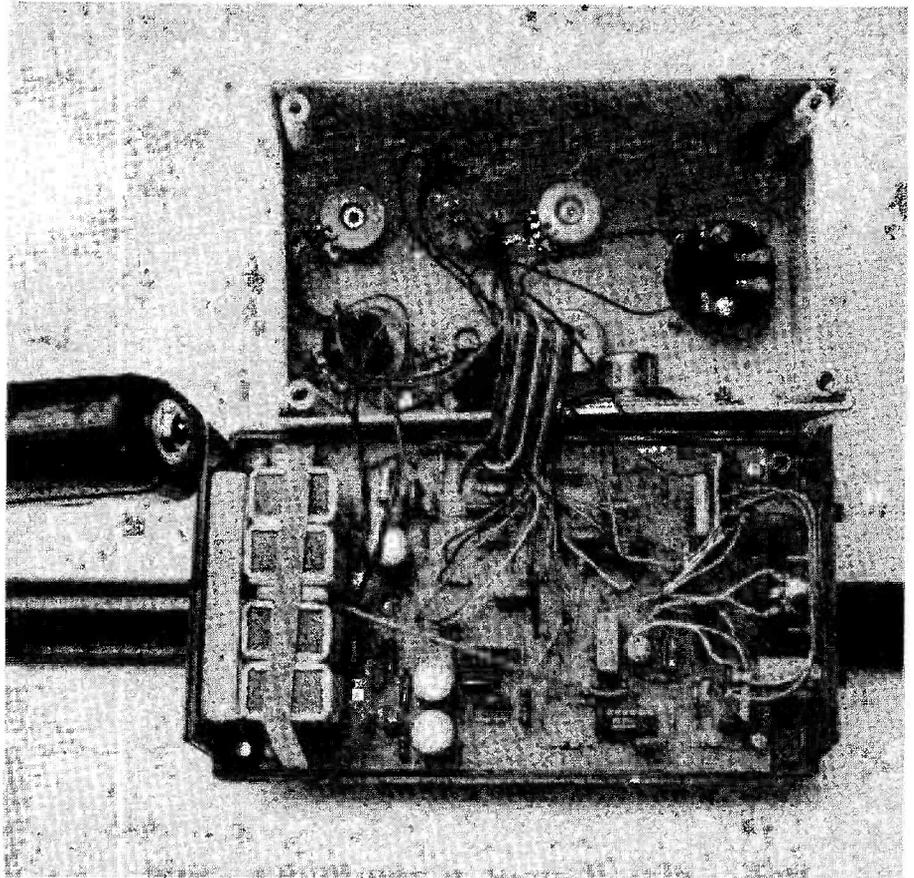It only functions when a TR mode is selected. The degree of discrimination




Connections from the PCB are taken to the top panel controls by 20 way ribbon cable.

is controlled jointly by the MODE (coarse setting) and the DISCRIMINATION (fine setting) controls. Together they set the point at which the resistance of the target causes a left or right deflection on the meter. The circuit in this design is very good indeed. It is possible to differentiate between a can ring pull and a gold ring, for example. However, the discrimination control reduces sensitivity slightly. It is best to use a detector of

this type in VLF mode until a target has been found and then use discrimination to determine its likely value!

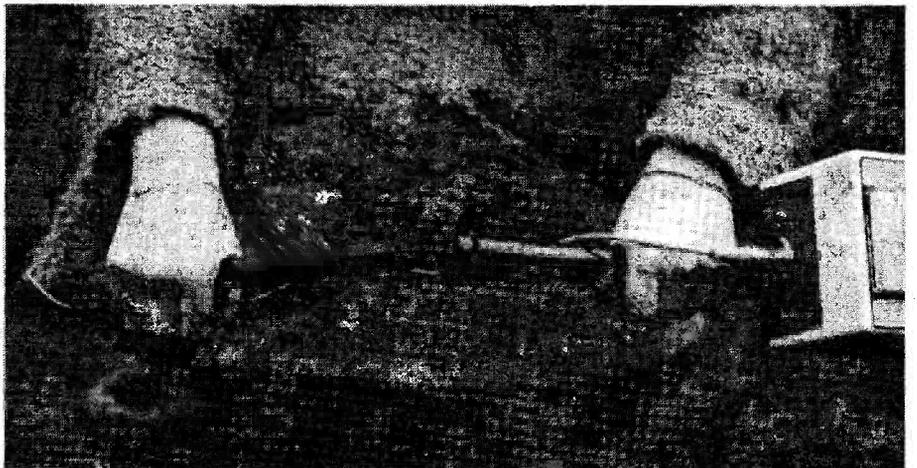Finally we ought to point out that in the UK it is necessary to obtain a licence before using a metal detector. This is not necessary elsewhere. Application forms can be obtained from: Home Office, Radio Regulatory Dept., Waterloo Bridge House, London S.E.1.



No, we haven't broken it. The two-piece shaft is telescopic, accommodating varying altitudes of treasure hunter.

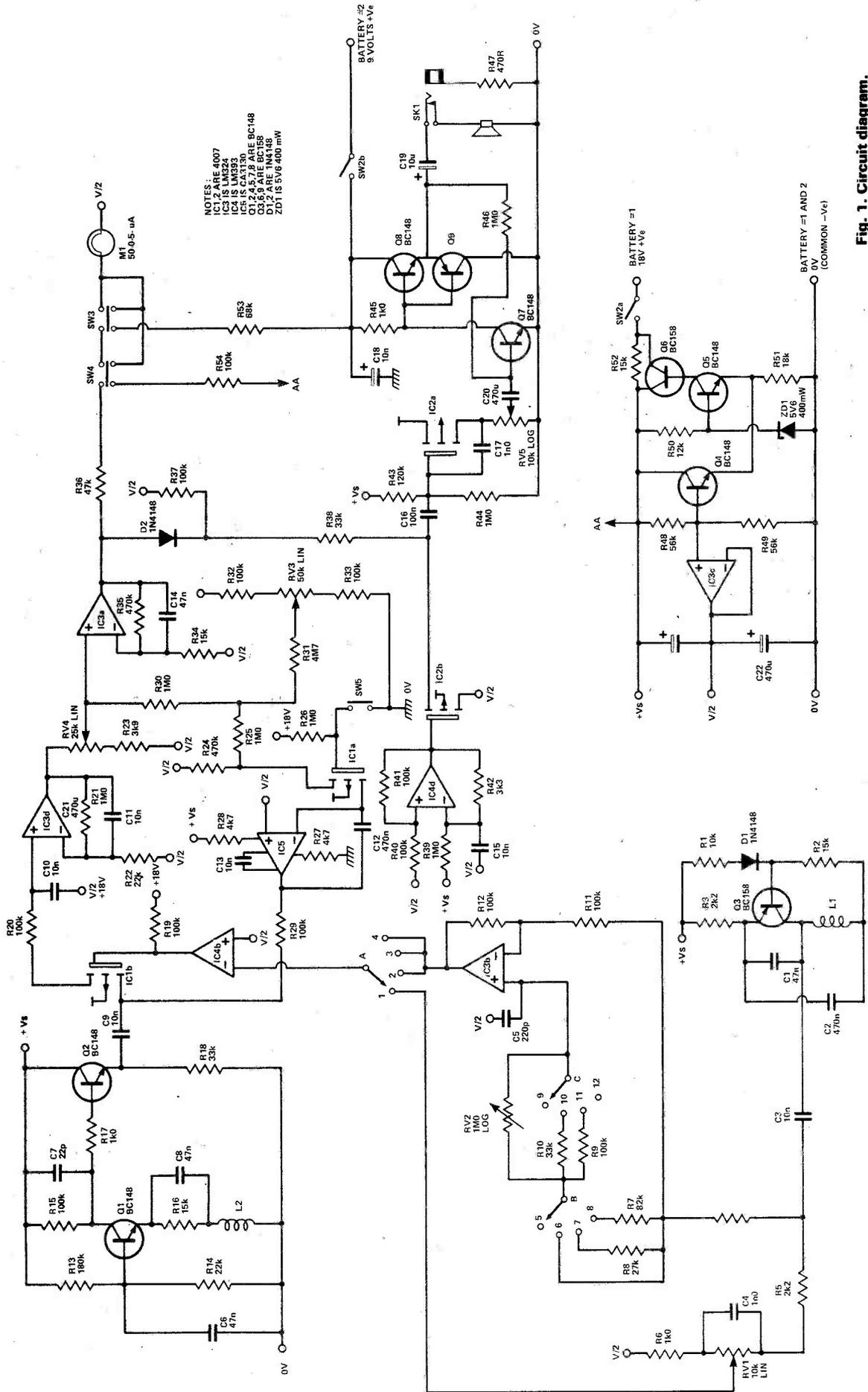


Fig. 1. Circuit diagram.

HOW IT WORKS

L1 and L2 are the TX and its coils in the search head. The signal is drive L1 is produced by Q1 and associated components which generate a sine wave of approx 16 kHz. Part of this signal passes via C3 to the phase shift section which produces a reference signal for the "phase comparator". When the VLF mode is selected, RV1 (ground control) and C4 provide a variable phase advance of 0 - 180°. The suitably modified signal is squared up by the precision voltage comparator IC1 and applied to the gate of the phase comparator IC1b. Meanwhile the signal picked up by L2 passes through Q1 and Q2 which amplify but do not distort or shift the phase, and meet the reference signal at IC1b.

The signal emerging from IC1b is a DC signal upon which superimposed are AC components corresponding to the phase coincidence of the reference and received signals. This is integrated by IC3d and a portion of the resulting signal is tapped off by the sensitivity control RV4. This is further amplified by IC3e and applied to the meter and via D7 to the audio gate IC2b.

Audio is generated by an auzible formed from the remaining half of the voltage comparator IC3a and after being gated by IC2b is amplified by IC2a, Q7, Q8 and Q9. RV5 is the volume control push button, IC1a form the heart of the voltage tuning system. Part of the voltage from RV4 is added to a voltage

determined by the position of the slider search head. The signal is applied to the base of IC1a when the tuning button is depressed. The normally high source to drive the instance falls and allows current to flow through the FET and build up as a voltage across C12. IC3 inverts and buffers the voltage to provide a DC bias for the phase comparator. The change of bias at L1b in turn affects the DC conditions at L1a (via Q3 and RV4). In other words a negative feedback loop is established which near the tuning button is present. Within a second or two the new DC level settles down and the button is released. The system is then maintained by the charge held on C12.

The power supply to the audio section is supplied, but due to the precision nature of the DC levels in the control section, stabilization is required. A Zener diode is voltage reference for the differential amplifier formed by Q4 and Q5, which carries the audio pair elements Q6, R32 about a small current to Q4 and Q5 at switch on to ensure that Q4 starts conducting. The base of Q4 must always be at 50% of the unregulated supply (R44 -R49). This point is buffered by IC3c as a V2 supply. C11, C13 and C20 are decoupling components. Special attention has been given to cutting down the current consumption. The control section only takes 1.5 mA and the audio section less than 2 mA when absent of other loading headphones.



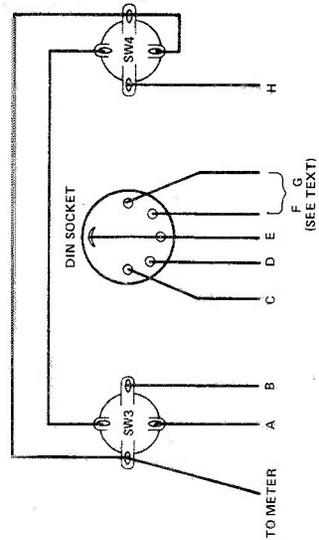


Fig. 2. Connection details for DIN plug and socket and SW3, 4. Note the tag lengths on SW3, 4.

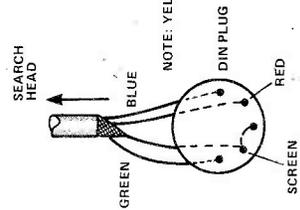

You'll need a driving lesson before you commence twiddling with this control panel.

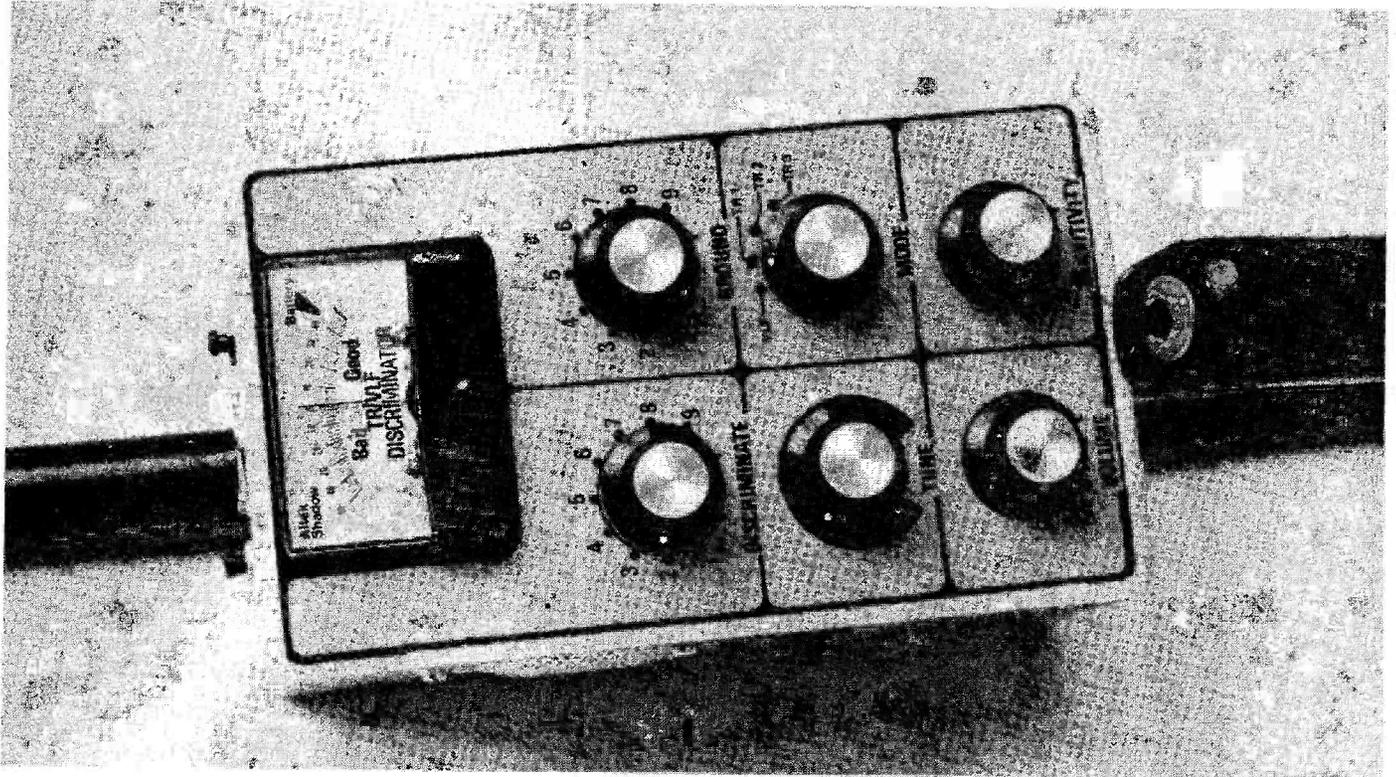


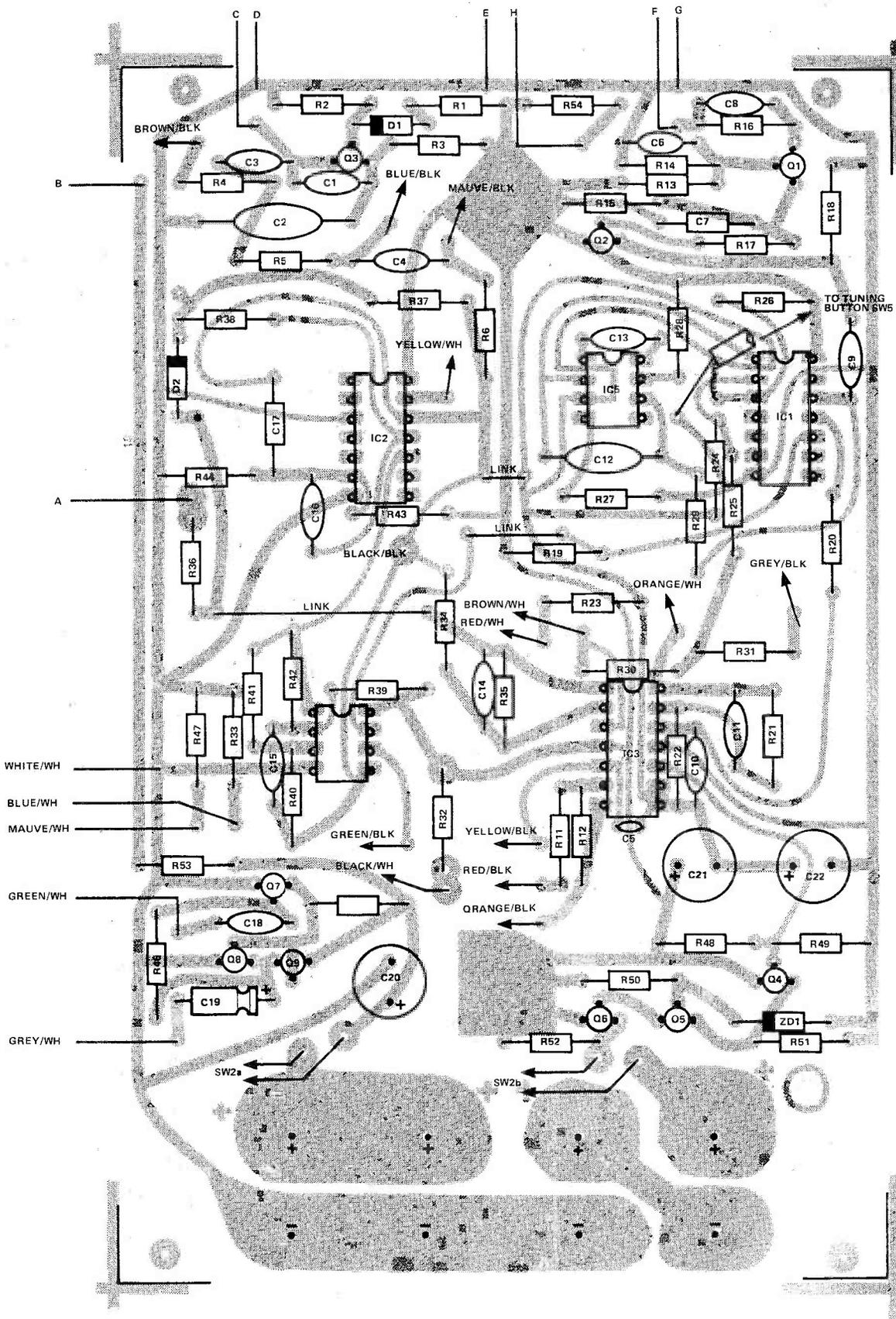


Fig. 3. Component overlay.

Fig. 4. Connections to controls on the front panel.

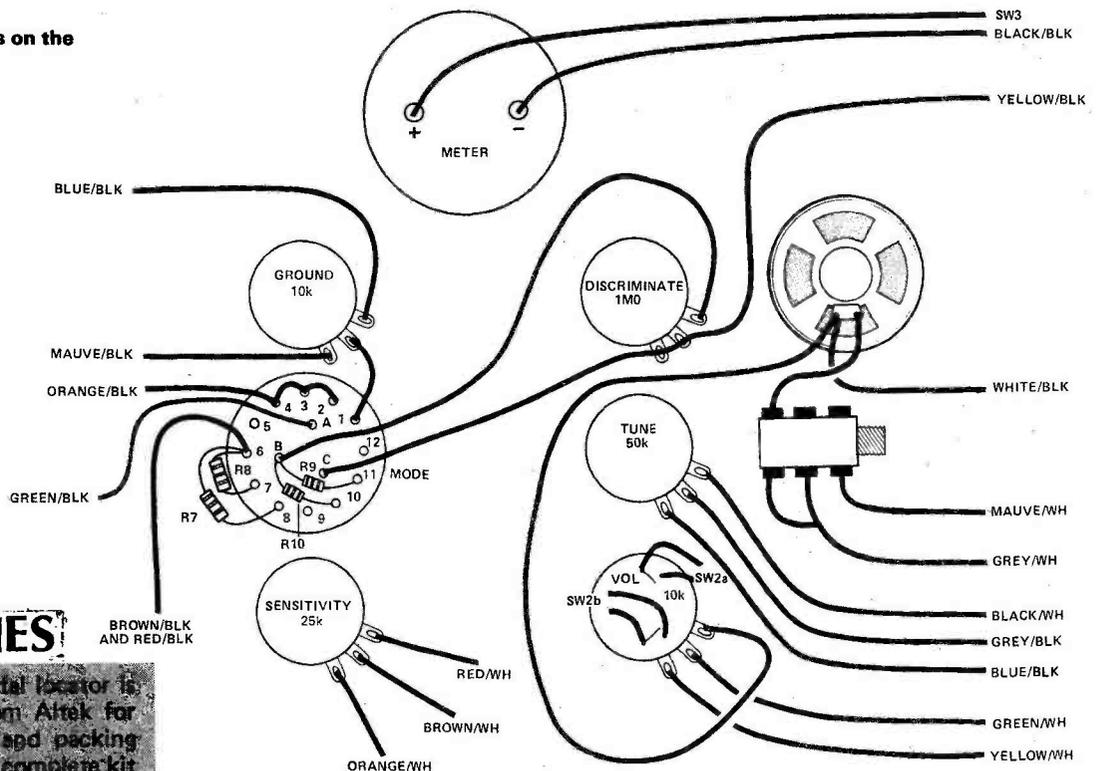

CONNECTION DETAILS FOR CONTROLS, METER, SPEAKER AND JACK SOCKET

BUYLINES

The Radsw VLF/TR metal locator is available in kit form from Aitek for £65 plus VAT (Postage and packing £1.50). Purchasers of the complete kit will also receive free parts and details of an extra switched function to sound a tone for 'good' and 'bad' or just 'good' finds when in discriminate mode.

A hardware kit is also available. It includes shell, search head, PCB and case and costs £47 plus VAT (P and P £1.70) from Aitek.

Aitek (ETI)
Green Lane
Wotton-on-Thames,
Surrey

PARTS LIST

RESISTORS All ¼W, 5%

R1	10k
R2,16,34	15k
S2	
R3,5	2k2
R4,51	18k
R6,17,45	1k0
R7	82k
R8	27k
R9,11,12	100k
15,19,20,29	
72,33,37,40	
41,54	
R10,18,38	33k
R13	180k
R14,22	22k
R21,2,26	1M0
10,19,44,46	
R23	3k9
R24,35	470k
R27,28	4k7
R31	4M7
R36	47k
R42	3k3

R43	120k
R47	470R
R48,49	56k
R50	12k
R51	18k
R53	68k

POTENTIOMETERS

RV1	10k lin
RV2	1M0 log
RV3	50k lin
RV4	25k lin
RV5	10k log

CAPACITORS

C1,6,8,14	47n polyester
C2	470n polyester
C3,9,10,11	10n polyester
13,15,18	
C4,17	1n0 polystyrene
C5	220p ceramic
C7	22p polystyrene
C12	470n polycarbonate
C16	100n polyester

C19	10u 25V electrolytic
C20,21,22	470u 16V electrolytic

SEMICONDUCTORS

IC1,2	4007
IC3	LM324
IC4	LM393
IC5	CA3130
Q1,2,4,5	BC148
7,8	
Q3,6,9	BC158
DI,2	1N4148
ZD1	5V6 400mW

MISCELLANEOUS

50.0 50 nA meter, 8R 2½" speaker, ¼" stereo jack socket, 6 knobs, 2 double pole c/o push buttons, single pole make push button, 3p 4W rotary switch, 5 way 180° latching DIN plug and socket, PCB, search head, shaft and handle, case to suit, 4 pairs PP3 battery connecting studs, 20 way ribbon cable.

24 HOUR CLOCK/ APPLIANCE TIMER KIT

Switches any appliance up to 1KW on and off at preset times once per day. Kit contains AY-5 1230 IC, 0.5" LED display.

Mains supply, display drivers, switches, LEDs, triac, PCBs and full instructions.
CT1000K Basic Kit £14.90
CT1000KB with white box (56x131x71mm) £17.40 Ready-built £22.50

DVM/THERMOMETER KIT

Based on the ICL 7106. This kit contains a PCB resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display.

Components are also included to enable the basic DV kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery).

£20.75

LEDS

0.1" Red 8p
0.1" Green 12p
0.1" Yellow 12p
0.2" Red 8p
0.2" Green 12p
0.2" Yellow 12p
0.2" LED Clips 3p
Rectangular Red LED 10p
Rectangular Green LED 20p
Rectangular Yellow LED 21p

DISPLAYS

DL32 Red 0.3" cc (pin compatible with EL704) 70p
DL307 Red 0.3" cc (pin compatible with DL707) 70p
DL847 Red 0.8" cc (pin compatible with DL747) £1.80
DL350 Red 0.8" cc (pin compatible with DL750) £1.80
DL727 dual 0.5" cc Red £1.50

IC SOCKETS

8 pin 8p
14 pin 12p
18 pin 17p
24 pin 24p

RESISTORS

1/4 W 22 ohm, 10M E12 Series Pack of 10 (one value) 10p
10 Packs (10 values) 80p

TRIACS

400V Plastic Case (Texas) 80p
3A 49p 16A 180p
8A 55p 20A 185p
12A 70p 25A 190p
6A with trigger 80p
8A isolated tab 65p
Disc 18p

INTEGRATED CIRCUITS

555 Timer 21p
741 Op Amp 19p
AY-5-1230/2 Clock/Timer £2.60
AY-5-1224 Clock £4.20
AY-3-1270 Thermometer £8.20
ICL7106 DVM (LCD drive) £7.00
LM377 Dual 2W Amp £1.45
LM379S Dual 6W Amp £3.50
LM380 2W Audio Amp 80p
LM382 Dual low noise preamp £1.00
LM386 250mW low voltage amp 75p
LM1830 Fluid Level Detector £1.50
LM2807 1-v Converter £1.40
LM3909 LED Flasher/Oscillator 55p
LM3911 Thermometer £1.20
LM3914 Dot/Bar Driver £2.10
MM57160 (stag) Timer £5.90
MM74C911 4-digit display controller £6.50
MM74C915 7-segment-BCD converter 96p
MM74C926 4-digit counter with 7-seg outputs £4.50
S566B Touchdimmer £2.50
S9263 Touchswitch 16-way £4.85
T8A800 5W Audio Amp 58p
T8A810AS 7W Audio Amp 85p
TDA1024 Zero Voltage Switch £1.00
TDA2020 20W Audio Amp £2.85
ZM1034E Timer £1.80
All ICs supplied with data and circuits. Data sheets only 5p

MINI KITS

These KITS form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB short instructions and all components.

TEMPERATURE CONTROLLER/THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. PCB (4cm sq.) potentiometer, plus all other components included, with instructions. 500W £3.20 1KW £3.50

SOLID STATE RELAY

Ideal for switching motors, lights, heaters, etc from logic. Opto isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. £2.60

BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

BURST FIRE/PROPORTIONAL TEMPERATURE CONTROLLER

Based on the TDA1024 Zero Voltage Switch this kit contains all the components required to make a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. 1.5kW £5.25 3kW £5.55

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 30p P&P. MAIL ORDER — CALLERS WELCOME BY APPOINTMENT.

TK Electronics

(ET1) 106 STUDLEY GRANGE ROAD LONDON, W7 2LX. TEL: 01-579 9794

SOUTH WALES

FOR TTL, CMOS, LINEARS, DISCRETES, PASSIVES, HARDWARE, TOOLS, CASES, TRANSFORMERS, ETC. CLOCKS, LEKTROKIT, BREADBOARDING AND VERO DEALERS

BOOKS BY NATIONAL, IOR, BABANI
SPECIAL OFFER LIST. ALL BRAND NEW. FULL SPEC.

DIL SOCKETS—GOLD PLATE	
8 pin	27p
14 pin	11p
16 pin	12p
18 pin	15.5p
22 pin	21p
24 pin	24p
28 pin	27p
40 pin	32p
4013 CMOS	24p
7401 TTL	7.5p
4017 CMOS	70p
7447 TTL	75p

THYRISTOR 1A, 200V MADE BY ITT, TYPE CRS 1/20AF 30p.
BRIDGE RECTIFIER BY MOTOROLA 1.5a, 50v 28p.
20k LIN-POT BY AB (+1) 20p, (+10) 19p.
100k LIN MOULDED TRACK (+1) 55p, (+10) 50p.
RELAY 4 POLE C/O, 12v COIL, £1.00.
20mm Q/B FUSES 150mA, 500mA, 4a, 5a, 50p for 10.
GLASS ENCAPULATED REED SWITCHES £1 for 10.
DIGITAL METERS TYPE DM235 SINCLAIR MULTIMETER £58.
PDM 35 SINCLAIR MULTIMETER £34.99.
TFM 200 SINCLAIR FREQUENCY METER £53.
TMK 500 £33 LT22 £15.10
TMK 500 TUB £41 KRT 101 £7
CASE FOR ABOVE £8
ALL PRICES VAT INCLUSIVE : PLEASE ADD 25p PACKAGE AND POST

SEND YOUR ORDERS TO:
STEVE'S ELECTRONICS
15/17 THE BALCONY, CASTLE ARCADE
CARDIFF, CF1 2BU TEL: (0222) 41905
OR VISIT US AT THE SHOP—
OPEN TUESDAY TO SATURDAY 9-5.30 FRIDAY 12.30-7
Mail and Official Orders Accepted

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS

STEREO PRE-AMPLIFIER POWER AMPLIFIER



CPR 1 — THE ADVANCED PRE-AMPLIFIER. The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV, distortion < .005% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp signal levels. Signal to noise ratio 86dB, slew-rate 3V/uS. T.H.D. 20Hz—20kHz < .008% at any level.

F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138x80x20mm. Supply to be ± 15 volts.

MC 1 — PRE-PRE-AMPLIFIER. Suitable for nearly all moving-coil cartridges. Sensitivity 70/170uV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

XO2:XO3 — ACTIVE CROSSOVERS. XO2 — two way, XO3 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1 — POWER SUPPLY. The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS. It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification. T.H.D. typically .01% any power 1kHz 8 ohms. T.J.D. insignificant, slew rate limit 25V/uS, signal to noise ratio 110dB, frequency response 10Hz-35kHz — 3dB stability unconditional, protection drives any load safely; sensitivity 775mV (250mV or 100mV on request), size 120x80x25mm.

POWER SUPPLIES. We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.

PRE-AMPLIFIER KIT
THIS INCLUDES ALL METALWORK, POTS, KNOBS, ETC — TO MAKE A COMPLETE PRE-AMP WITH CPR 1(S) MODULE AND THE MC1(2) IF REQUIRED.

POWER AMPLIFIER MODULES	
CE 608 60W/8 ohms 35-0-35v	£19.52
CE 1004 100W/4 ohms 35-0-35v	£25.96
CE 1008 100W/8 ohms 45-0-45v	£31.90
CE 1704 170W/4 ohms 45-0-45v	£33.97
CE 1708 170W/8 ohms 60-0-60v	£33.97

TOROIDAL POWER SUPPLIES	
CPS1 for 2xCE 608 or 1xCE 1004	£18.56
CPS2 for 2xCE 1004 or 2/4xCE 608	£19.75
CPS3 for 2xCE 1008 or 1xCE 1704	£17.12
CPS4 for 1xCE 1008	£24.15
CPS5 for 1xCE 1708	£25.53
CPS6mk 2xCE 1704 or 2xCE 1708	£25.53

HEATSINKS	
Light duty, 50mm, 2 C/W	£1.44
Medium power, 100mm, 1-4 C/W	£2.35
Disco/group, 150mm, 1-1 C/W	£3.04
Fan, 80mm, state 120 or 240v	£19.70
Fan mounted on two drilled 100mm heatsinks 2x4 C/W, 65 max with two 170W modules	£31.05

THERMAL CUT-OFF, 70°C	£1.54
------------------------------	-------

POWER AMP KIT	£35.03
----------------------	--------

PRE-AMPS	
These are available in two versions — one uses standard components, and the other (the SL) uses MO resistors where necessary and tantalum capacitors.	
CPR1	£31.65
CPRIS	£40.87
MC1	£21.28
MC1S	£33.17
Pre-amp Kit	£38.07

ACTIVE CROSSOVERS	
XO2	£15.16
XO3	£23.58

POWER SUPPLY		
REG1	£6.90 TR6	£1.91

BRIDGE DRIVER, BD1	
Obtain up to 340W using 2x170W amps and this module.	
BD1	£5.78

CRIMSON ELEKTRIK

1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 553508
U.K. — please allow up to 21 days for delivery

Badger Sound Services Ltd., 46 Wood Street, Lytham St. Annes, Lancashire FY8 1QG.

All prices shown are UK only and include VAT and post. COD 90p extra. £100 limit. Export is no problem please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

JPS FOR ELECTRONICS T.T.L. standard and L.S., C.M.O.S., linear, micro-processor I.C.s, consumer circuits, semi-conductors, resistors, capacitors, Vero products, Eagle products, etc.

thandar INSTRUMENTS

By Sinclair Electronics
SC110 Scope 10MHZ
10MV/DIV £159.85



PFM200 FQ METER
20HZ-200MHZ
£57.27

DIGITAL METERS

DM235 3 1/2 Digit 21 range £57.27
DM350 3 1/2 Digit 34 range £79.35
DM450 4 1/2 Digit 34 range £113.85
PDM35 3 1/2 Digit 16 range £34.44
Full range of accessories available
Large S.A.E. for more details

na/com-2

Micro-Computer
Kit 20K on board
memory 8K Micro soft
basic Z80A CPU 4MHZ
£339.25 inclusive



na/com-1 4K Kit £143.75

Assembled £161.00
3 amp power supply £33.93
Full range of expansion accessories
available Large S.A.E. for more details

A selection from our range of surplus new or ex-equipment electronics.
Untested except where stated.

TEN TURN POTS 50K £2.00

Counter Dial for above £1.50

15W AUDIO AMP P.C.B.s with circuit
2 for £1.50

MINI WAFER SWITCHES

2 pole 6 way 40p. 6 pole 2 way shorting
30p. 1 pole 3 way 30p

3 POLE C/O TOGGLE SWITCHES

250V 10A 50p

SELECTIVE CALL UNITS ENCODER

AND CONTROL HEAD. 12V Operation
5 thumb wheel switches 37TTL
74 series. I.C.s 32 8KHZ XTAL Reed Relay
13 transistors 2 min relay 8 edge
connectors + components and 2 nice
cases. £9.80

MULTI-POLE CONNECTORS

Sub min plug and socket 15 way £1.00
20 way £1.00

STANDARD CONNECTORS plug and

socket 18 way £1.00, 12 way £1.00
4 way 70p, 2 way 60p

EDGE CONNECTORS 18 way -15 40p

PANEL METERS Scale 0-25 MA

Basic FSD 10 MA 2 3/4" x 2 1/4" £2.50

L.E.D. WATCH MODULES 4 for £2.00

CALCULATOR PCBs complete

untested most work 3 for £3.20

METER CASES AVO Style

9 3/4"H x 6 3/4"W x 3 1/2"D black £3.00

RELAYS 12V 4 pole c/o about 5 amp

including base 80p

MIN FANS 3" x 3" x 1 1/2" 115 VAC £2.00

KNOBBS 1/4 black 4 for 25p

HEAT SINK with 3 new power

transistors 8" x 2 1/2" x 3/4"

40251 SIM to 2N3055 x 2

40318 NPN 300V 35W £1.50

NEONS Red Lens 12p

PROJECT BOARD 4 I.C. 60p, 2 I.C. 30p

Transistor 22 strips x 5" 50p

13 ASSORTED PANELS mainly for
components but some can be repaired £5

Lists 20p + large S.A.E. VAT inclusive prices. Add 50p p.p. on orders under £10
Cat. Available shortly 75p

JPS Dept., E.T.I., 9 East Street, Colne, Huntingdon, Cambs. 0487 840710

QUANTITY PRICES — SAVE — SAVE — IMMEDIATE DELIVERY

NEW STOCKS BELOW MANUFACTURERS' PRICES.

Postage & packing add 50p per order.

SN74161N IC 80p ea.

BCD Decimal Decoder-Driver 10 for 44p ea. 100 for 40p ea. 1,000 for 35p ea.

DISPLAYS by Hewlett-Packard. Seven segment DL707 (5082-7750) 95p. Common anode half inch red display brand new in maker's cartons 6 for £5.50 for 70p ea. 1,000 for 55p ea.

TV SOUND. High quality sound through your hi-fi. Simply plug into your aerial socket. £6.50, as reviewed Popular Hi-Fi.

BURROUGHS 8 DIGIT Panaplex calculator display 7 segment 0.25" digits. Neon type with red bevel socket and date. £1.95 ea. 10 for £17.100 for £140.

HONEYWELL PROXIMITY DETECTOR integral amplifier 8V DC £3.50 ea. 10 for £30.

MULLARD TBAB00. IC audio amplifier 95p ea. 10 for £8. 100 for £70. 500 for £300.

RCA CA3089. FM IF £1.50, 10 for £12.

RCA CA3090A. FM decoder £2.50, 10 for £20, 100 for £175.

BU 205 TEXAS. £1.50 ea. 10 for £12, 100 for £100.

2N3055 90V version TO3 power 10 for £3.50, 100 for £28, 500 for £125, 1,000 for £200.

BUZ08. TO3 Texas TV power transistors £1.75 ea. 10 for £15, 100 for £120, 1,000 for £1 ea.

MC1310P-SN76115N FM stereo decoder £1.20 ea. 10 for £1 ea. 100 for 85p ea.

MULLARD AD161-AD162. Matched pairs. 1 pair 80p, 10 pairs £5.

Cartons of 600 pairs £250 EX-STOCK

RADIATION DETECTORS Quartz Fibre Dosimeters.

Pen type with clip with lens and scale 0-50R. Originally over £5 OUR PRICE 95p EACH. 10 for £8. 100 for £80, 1,000 for £500.

ORP12 light dependent resistance Mini Type. 2 for £1, 10 for £4, 100 for £35.

TV TUNERS by Mullard UHF 38 mcs size

3 3/4x2 3/4x1 1/4 £2.50 ea. 10 for £20, 100 for £175, 500 for £750, 1,000 for £1,250.

MULLARD TUNER MODULES with data

LP1171 combined AM/FM IF strip £3.50. LP 1179 FM front end with AM tuning gang, used with LP1171 £3.50. LP1171 and 79 pair £5.75, 10 pairs for £50, 100 pairs for £400.

CA3085 RCA POSITIVE VARIABLE REG.

Switch 100m amp variable 1.8-24V 55p ea. 10 for £5, 100 for £35, 1,000 for £300.

MULLARD LP1157 AM tuner modules with circuit

£2.50 ea. 10 for £20, 100 for £175.

LUSTRAPHONE RIBBON MIKE £1.50, + pre amp on chassis 3x2x1in. 10 for £12.50.

TAA618 (14 pin x 1 1/2") IC TV sound and FM amplifier-detector by ATES on p.c. board with other parts. Complete with data & connections. 60p. 10 for £5, 100 for 40p ea. 500 for 35p ea.

PREVIOUS LINES IN STOCK

MARRIOTT TAPE HEADS Quarter track

Types Each Per 10 Per 100

XRPS18 Record/Replay £3.00 £25.00 £200.00

XRPS36 Record/Replay £4.00 £35.00 £250.00

XES11 Erase £1.25 £11.00 £100.00

MAINS TRANSFORMERS all 200/250V IN

Type Current Size Price

12V 100m/a 1 1/2 x 1 1/2 x 1 1/2 £0.85

12V 500m/a 1 3/4 x 1 3/4 x 1 3/4 £1.35

12V 2 amps 2 3/4 x 2 3/4 x 2 1/2 £2.50

Per 10 less 10% per 100 less 20%

PHOTO CONDUCTIVE CELL £1.25. High power

Cds cell 600mw for control circuits. Resistance 800ohm to 4K. Max volts 240. Size 1 1/2 x 7/16in. 10 for £11, 100 for £100.

DYNAMIC MICROPHONE. Low imp. Foster insert. £1.45, 10 for £11, 100 for £100.

UHF TUNER BY GEC. 38mc/s with slow motion tuning. Size 5x3x2in. £3 ea. 10 for £25, 100 for £220, 500 for £1,000.

TWO GANG MINIATURE VARICAP TUNER

500pF with tuning knob, size 3x1 1/2x1 1/2in. £1.25 ea. 10 for £10, 100 for £85.

ATES UI4552 AUDIO IC AMPLIFIER 14 PIN

DIL. 300m watts 55p ea. 10 for £4.50, 100 for £35, 1,000 for 30p ea.

GENERAL ELECTRIC 2+2 watt IC stereo audio

chips with circuit & data £1.85 ea.

RCA CD4025AE 16 pin DIL. presettable up down

counter 80p each. 25 for £15, 100 for £50, 1,000 for £355 (in anti static tubes of 25).

UHF TV TUNER (preamp) with BF180 55p each.

Built on PC board 2x2in (sold without data) 10 for £4.50, 100 for £35, 1,000 for £250.

MARCONI IC Oscillator Data (TO99 can) 30p

ea. 10 for £2, 100 for £15, 1,000 for £125.

PLESSEY SL432A IC IF amplifier (TO99 can) 85p

ea. 10 for £6, 100 for £38, 500 for £150.

VHF MODULATORS for TV games 55p ea. 2

transistors—on built PC board 2 1/2 x 1 1/2in. 10 for £4, 100 for £35, 500 for £150.

RF Filters for above modulators 20p ea. with

components and coils on built p.c. circuit, size 2x2x1 1/4in. 10 for £3.50, 100 for £30, 500 for £125.

HIGH VOLTAGE TV TRIPLER DIODES by IIT

stick type per 10 £1.50, per 100 £18, per 1,000 £85.

TBA625 ATEs voltage regulators 55p ea. 5 volts

100m/amps (TO99) per 10 £4.50, per 100 £39, per 1,000 £280. 12V TBA625B also.

16 PIN low profile DIL sockets 12p. 10 for £1,

100 for £8, 1,000 for 6p.

THYRISTORS Motorola 2N5061 0.8 amp 60

volt 19p, 10 for 15p ea, 100 for 13p ea, 1,000 for 11p ea, 10,000 for 10p ea


ULTRASONIC TRANSDUCERS 40 KC's.

Pair at £2.95, 10 pairs at £2.90 pair, 100 pairs at £2.20 pair

GREENWELD

443A Millbrook Road Southampton SO1 0HX

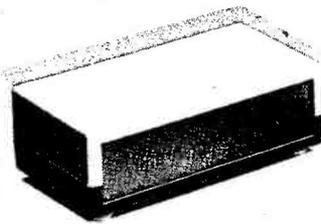All prices include VAT at 15% — Just add 30p post



VEROCASE SALE!!

Four popular sizes of Verocase at drastically reduced prices — these were part of their standard range (75-1411, etc) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No	Size	Price
21050	205 x 140 x 75mm	£2.70
21051	180 x 120 x 65mm	£2.30
21052	154 x 85 x 60mm	£1.75
21053	125 x 65 x 40mm	£1.45

DIL SOCKETS

Low profile by TI at lowest ever prices!

	1-99	100-499	500+
8 pin	.095	.075	.065
14 pin	.105	.085	.075
16 pin	.12	.095	.085
18 pin	.155	.125	.10
20 pin	.19	.15	.12
22 pin	.21	.17	.14
24 pin	.24	.19	.15
28 pin	.26	.21	.16
40 pin	.32	.26	.21

BULK BARGAINS

All new full spec devices. Prices per 100 inc VAT (orders not accepted for less than 100 of one type at these low prices!!)

AD161/2PR	£48	BF255	£8
BC107	£7	BF394	£4
BC108	£6	BF450	£7
BC109	£7	BF451	£5
BC114	£6	BFY17	£12
BC117	£5	BFY50	£14
BC125	£5	BFY51	£14
BC147	£5	BFY52	£14
BC148	£5	BSY95A	£10
BC149	£5	BU205	£65
BC159	£5	BU206	£65
BC172C	£5	2N1132	£12
BC182B	£4.50	2N2369	£12
1k	£35	2N2894	£12
10k	£310	2N2926Y	£5
BC183B	£5	2N2926R	£5
BC184L	£5	2N3053	£13
BC212	£5	2N3054	£34
BC213L	£5	2N3055	£34
BC237	£5	2N3442	£100
BC238B	£5	2N3583	£145
BC252	£7	2N3618	£78
BC308B	£6	2N3702	£10 to £5
BC230	£7	2N3708	
BC128	£8	2N4401	£5
BC337	£8	2N4403	£6
BC348	£5	2N5401	£19
BC351	£14		
BC557A	£5		
BCX33	£5	1N4001	£3.50
BD131	£19	1k	£28
BD132	£20	1N4004	£4.50
BD181	£50	1k	£39
BD184	£60	1N4006	£5.50
BD246	£25	1k	£46
BD525	£25	1N4148	£2.30
BD526	£25	1k	£17
BD173	£13		
BF181	£17	ICs	
BF195	£5	741 8dill	£13.50
BF197	£5	555	£21.75
BF198	£5	723 14dill	£32
BF241	£5	723 TO99	£30

Resistors — 1/4W 5% carbon film, these

values only: 220R, 1k, 4k7, 33k, 39k, 47k, 220k, 330k, 18R. All at £4 per 1,000 (min qty of one value) or £35 per 10,000 any mix.

All other values from 1R to 10M @ £1/100, £7.10/1,000 per value.

INVERTER

Prepare for the Power Cuts! Ready built inverter, 24V DC 290x55x37mm, will power 6x8W fluorescent tubes. Circuit supplied. Only £2.90.

COMPONENT PANELS

2525 Contains 11 800mA 60V 2N5061

SCRs, 11 6V8 zeners, 11 1N4004 diodes plus Rs, Cs, etc. Only £1

74 Series ICs — Gates and complex logic, 20 asstd ICs on panels £1; 100 ICs £4.

2527 2x6V reed relays, 6x2S030 or 2S230, 6x400V rects, plus Rs. Only

50p

OUT NOW THE NEW 1980 GREENWELD CATALOGUE

FEATURES INCLUDE:


- 60p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE 40p + 20p POST

1A 400V RECTIFIERS

Plastic, like 1N4004, type 388F these diodes have preformed leads for horizontal mntg (15mm FC) Supersave price — 100 for £2.30; 500/£10; 1000/£18.

1000 RESISTORS £2.50!!


A Range of Performance from... ...HAMEG

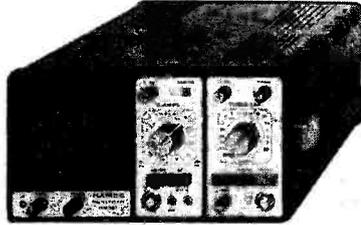

PERFORMANCE AND RELIABILITY
ARE THE SEALS FIRMLY STAMPED
ON THE COMPLETE HAMEG RANGE
AND IT IS A COMPLETE RANGE

Model	Description	Price (£)
HM307	Single Trace DC-10MHz Plus Built-in Component Tester	149
HM312	Dual Trace DC-20MHz, 5mV/cm, Full X-Y, 30MHz Trigger, Plus TV Trigger	250
HM412	Dual Trace DC-20MHz, 2mV/cm, X-Y, 40MHz Trigger, Plus Sweep Delay	350
HM512	Dual Trace DC-50MHz, 5mV/cm, X-Y, 70MHz Trigger Sweep Delay, Plus Single Shot, Sweep Delay and After Delay Trigger	580
HM812	Dual Trace as per HM512. Plus Storage, Automatic Storage and Variable Persistence	1325

Prices UK List ex VAT

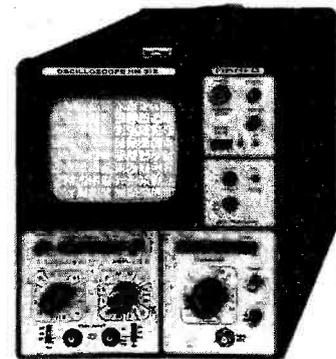

For FULL DETAILS and
DISTRIBUTOR LIST
Contact

Hameg Ltd.,
74-78 Collingdon St.,
Luton,
Beds.
LU1 1RX.

Tel: (0582) 413 174



Wilmslow Audio

THE firm for speakers!

Send 30p stamp for the world's best catalogue of
Speakers, Drive Units, Kits, Crossovers, etc., and
discount price list.

● AUDAX ● BAKER ● BOWERS & WILKINS ●
CASTLE ● CELESTION ● CHARTWELL ● COLES ●
DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ●
FANE ● GAUSS ● GOODMANS ● I.M.F. ●
ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ●
LOWTHER ● MCKENZIE ● MONITOR AUDIO ●
PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ●
SEAS ● TANNOY ● VIDEOTONE ●
WHARFEDALE ● SHACKMAN ● AUDIOMASTER ●
TANGENT ● STAG ● YAMAHA

WILMSLOW AUDIO Dept. ETI

SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

Discount HiFi, etc., at:
5 Swan Street

TEL. WILMSLOW 529599 FOR SPEAKERS
WILMSLOW 526213 FOR HI-FI


TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safeloc

Minimum & Sub Miniature					50 VOLT (Pri: 220-240V) Sec: 0-19-25-33-40-50V				
Volts	Milli-amps	Ref. No.	Price £	P&P	Amps	Ref. No.	Price £	P&P	
3-0-3	200	238	2.45	.65	0.5	102	3.45	.85	
0.6, 0.6	1A 1A	212	2.85	.70	1.0	103	4.45	1.00	
9-0-9	100	13	2.15	.65	2.0	104	7.15	1.15	
0.9, 0.9	330 330	235	2.00	.65	3.0	105	8.45	1.15	
0-8-9, 0-8-9	500 500	207	2.60	.70	4.0	106	10.70	1.25	
0-8-9, 0-8-9	1A 1A	208	3.70	.70	6.0	107	14.95	1.45	
0-15, 0-15	200 200	236	2.00	.65	8.0	118	20.05	1.65	
0-20, 0-20	300 300	214	2.60	.85	10.0	119	23.95	2.15	
20-12-0-12-20	700(DC)	221	3.35	.85	60 VOLT (Pri: 220-240V) Sec: 0-24-30-40-48-60				
0-15-20, 0-15-20	1A 1A	206	4.45	1.00	Amps	Ref. No.	Price £	P&P	
0-15-27, 0-15-27	500 500	203	3.90	.85	0.5	124	3.70	.85	
0-15-27, 0-15-27	1A 1A	204	5.95	1.00	1.0	126	5.45	1.00	
12 AND/OR 24 VOLT Pri: 220-240 Volts					2.0	127	7.40	1.15	
	Amps	Ref. No.	Price £	P&P	3.0	125	10.95	1.25	
12v	24V				4.0	123	12.20	1.45	
0.5	0.25	111	2.15	.70	5.0	40	14.00	1.55	
1.0	0.5	213	2.60	.85	6.0	120	17.45	1.55	
2	1	71	3.10	.85	AUTO TRANSFORMERS				
4	2	18	3.90	.85	Input / Output Tapped 0-115-210-240V				
6	3	70	5.45	.90	VA	Ref. No.	Price £	P&P	
8	4	108	7.30	1.15	(Watts)				
10	5	72	8.10	1.15	20	113	2.50	.85	
12	6	116	8.70	1.15	75	64	3.95	.85	
16	8	17	10.70	1.25	150	4	5.45	1.00	
20	10	115	13.70	1.45	Input / Output Tapped 0-115-210-220-240V				
30	15	187	16.70	1.45	300	53	9.05	1.15	
60	30	226	33.20	1.75	500	67	10.70	1.45	
30 VOLT (Pri: 220-240V) Sec: 0-12-15-20-24-30V					1000	84	18.45	1.55	
	Amps	Ref. No.	Price £	P&P	Also 1500/2000/3000VA				
0.5	112		2.70	.85	MAINS ISOLATING (Centre Tapped & Screened)				
1.0	79		3.45	.85	Pri: 120/240V Sec: 120 240V				
2.0	3		5.45	1.00	VA	Ref. No.	Price £	P&P	
3.0	20		6.15	1.15	(Watts)				
4.0	21		6.45	1.15	60	149	6.45	1.00	
5.0	51		9.45	1.15	100	150	7.45	1.25	
8.0	117		10.95	1.15	200	151	10.95	1.25	
8.0	88		14.20	1.45	250	152	13.15	1.45	
10.0	89		16.45	1.45	350	153	16.15	1.55	
					1000	156	36.95	3.15	

Please add VAT at 15%
Barclaycard and Access facilities
available
Trade and Education Welcome

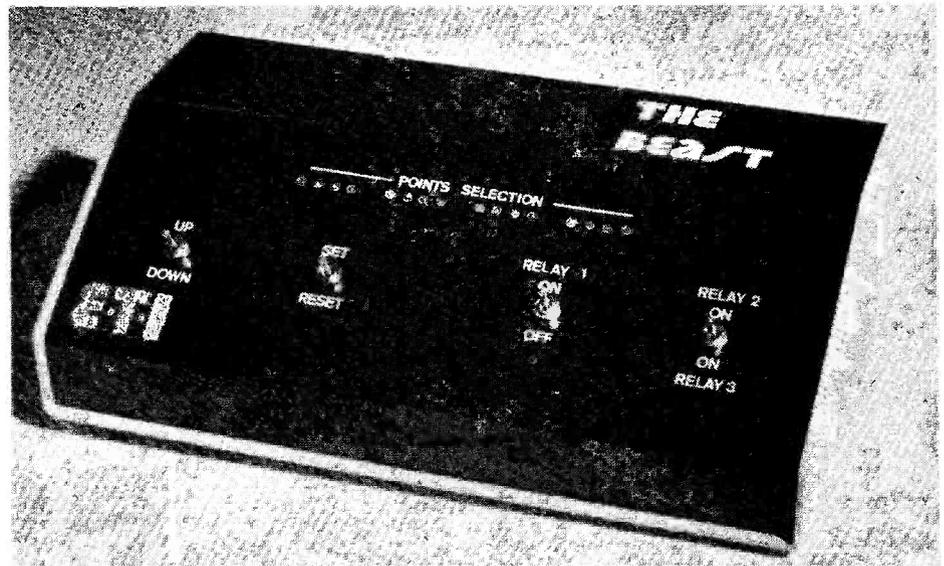
BAYDIS 7a William Street
Herne Bay, Kent
Herne Bay GA5 8BE



The points controller (above) can control up to sixteen sets of points or relays. It can activate several times per second. The set of points chosen is shown on the row of LEDs on the front panel. Think about your own particular points control needs before you start to build this unit. The data distribution unit is shown on page 91.

epoxied to the front panel. Our controller unit connects to the decoder/data-distributor unit via approximately 3.5 metres of 3-core coiled cable and a 3-pin DIN plug and socket.

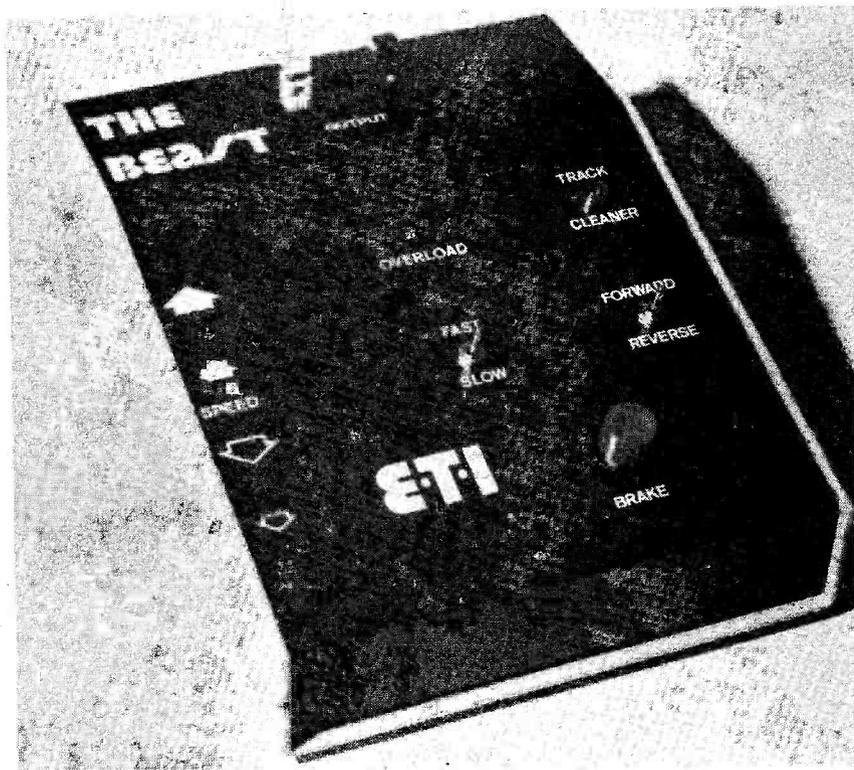The main power supply unit (below) has electronic overload on its output and can power up to four sets of track systems simultaneously.



The train controller (above) gives exceptionally fine speed control, from crawl to supersonic (well nearly). There's also a built-in track cleaner to keep things running smoothly.



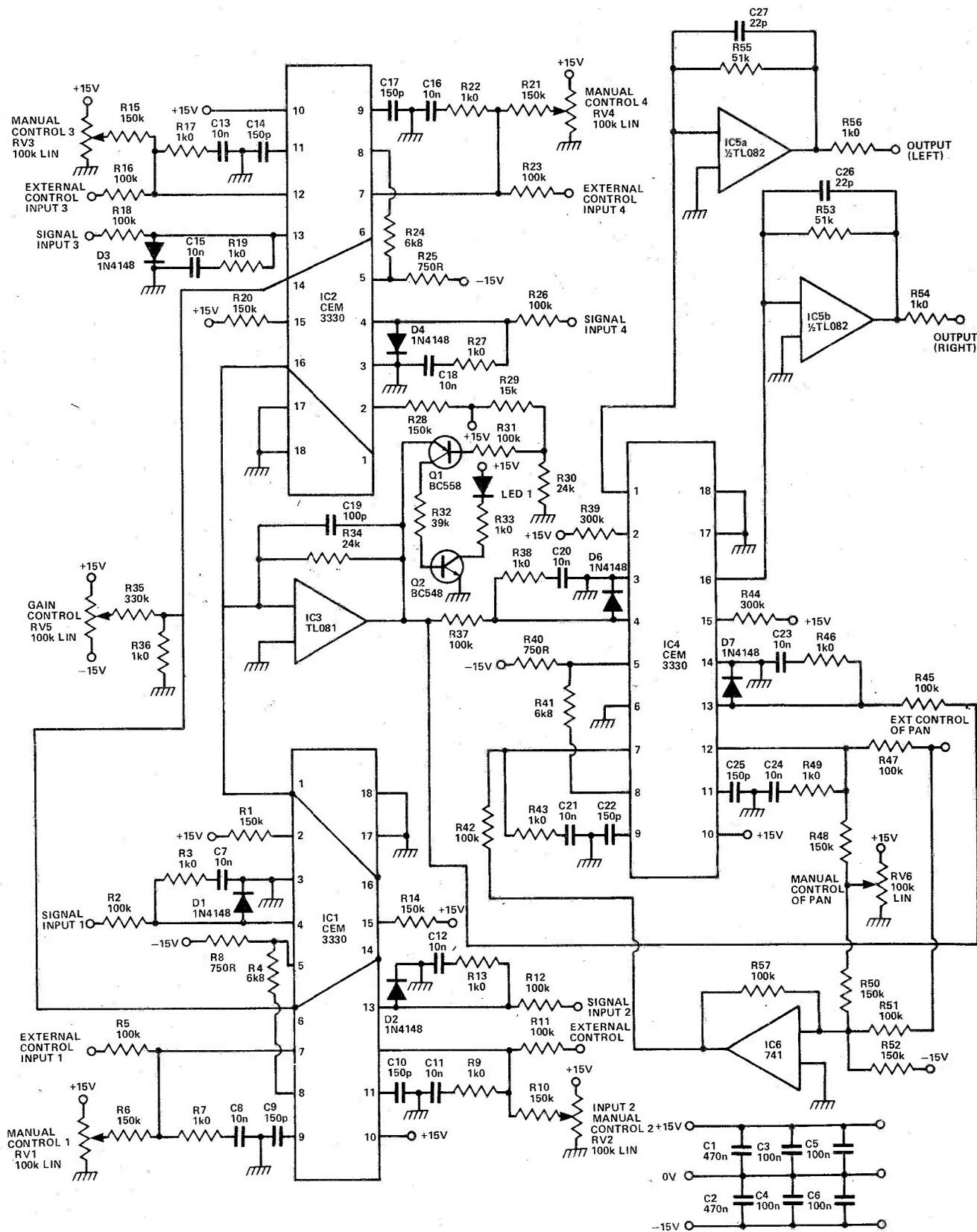


Fig.1. Circuit diagram of the voltage controlled mixer.

HOW IT WORKS

The CEM 3330, from Curtis Electronics Specialties, contains two voltage controlled amplifiers each of which consists of a variable gain cell and a log converter. The gain cell is the current-in, current-out type and has simultaneous linear and exponential controls. The log converter generates the multiplier of the linear control input current while transmitting the exponential control input unchanged to its output.

Reference to the circuit diagram and Pin 1 to 9 of IC1 illustrate the basic principle of the design and some of the features of the CEM 3330. The signal input (Pin 4) is a summing node and can, therefore, accept multiple inputs. In this application where we require independent control over each input only one input has been provided and with R2 = 100k the signal level should be kept to $\pm 10V$. R3 and C7 are compensation components and the diode, D1, is to prevent latch-up problems. R1 connected to +15V provides a reference current to the gain cell and this current should be limited to 100 μA for best linearity. The design is based on proportional mixing of up to four signals and thus the linear control input is used to independently control the gain of each signal input. Again, this is a summing node input at Pin 7 which allows manual control of gain via RV1 and R6 or external control via R5 without additional op amps. By using a 150k resistor for R6 the control pot can make use of the standard +15V supply and provide the same gain as a 10V external control signal applied to the 100k resistor. R5, R7 and C8 compensation network stabilise the log converter. C9 is for compensation of the gain cell. A master gain control is obtained by injecting a small voltage into the exponential control input (Pin 6). This voltage is derived from RV5, R13 and R34 and is common to the four input stages.

The overall gain of the VCA is given by:

$$A_v = \frac{R_2}{R_1} \times \frac{I_{CE}}{I_{REF}} \times \frac{V_{CE}}{V_T}$$

where R_2 is the value of the output resistor (R14), R_1 the signal input resistor (R2), I_{CE} the linear control current developed across R5 (or R6), I_{REF} the current input to Pin 3 via R1, and V_{CE} the exponential control voltage. This equation indicates how the mixer may be altered to suit other signal and control levels.

One of the unique features of the CEM 3330 is that the operating point of the amplifiers may be set anywhere from Class B to Class A according to which parameters are most important in a particular application. The quiescent standby current of the signal-carrying transistors is varied by placing a resistor between the IEX pin (Pin 5) and the idle current adjust pin (Pin 8). In this application the amplifiers are run Class AB with the 6k Ω resistor (R4) providing a standby current of about 7 μA .

The four signal input and control stages are identical and their output currents are summed at IC3 and converted to a voltage across R34. This voltage is applied to Q1 which is turned on when the peak output voltage is about 0V (normal signal level for the synthesiser), which is set by the voltage divider R29, R30. Q2 is also turned on when this peak voltage is reached and the LED (D5) will then light up. At constant amplitude high frequency the LED will tend to glow dimly but intermittent peak voltages are clearly indicated.

The output voltage from IC3 also goes to both VCAs in IC4 which is configured in a similar manner to ICs 1 and 2 except that the exponential output is provided. The amplifiers and associated op amps (IC5a) and (IC5b) are set to unity gain when a 10V control voltage is applied to R42 or R47. The panning effect is obtained through IC6 and associated components which provides a 10V output with zero volts at R47 or RV6, and 0V when there is 10V at R47 or when RV6 is fully clockwise. The left and right outputs are obtained by converting the current to a voltage across resistors R55 and R53 respectively. The use of op amp, IC5, provides low impedance outputs.

The CEM 3330 may be trimmed for precision control of gain and for use in high quality audio applications. The arrangement used in this design is entirely satisfactory for its intended use with high signal levels.


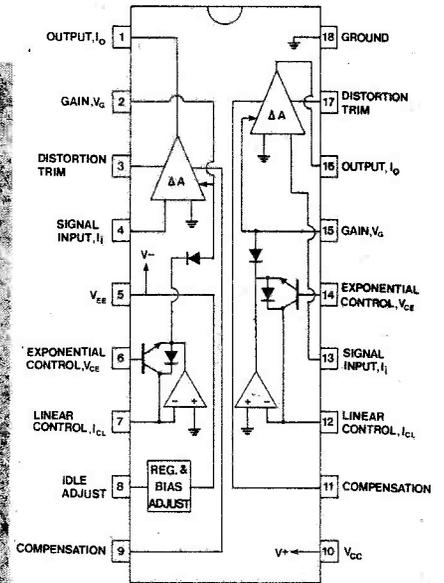


Fig. 2. The internal structure of the CEM 3330 dual VCA.

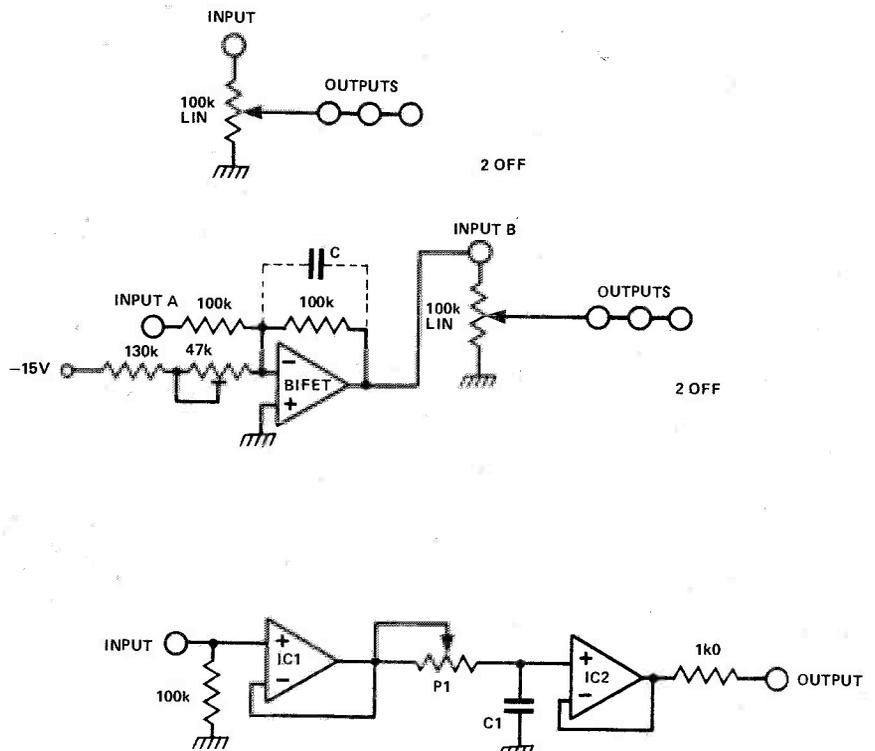

○ = JACK SOCKET

Fig. 3. Circuit diagram of the simple processor.

PARTS LIST

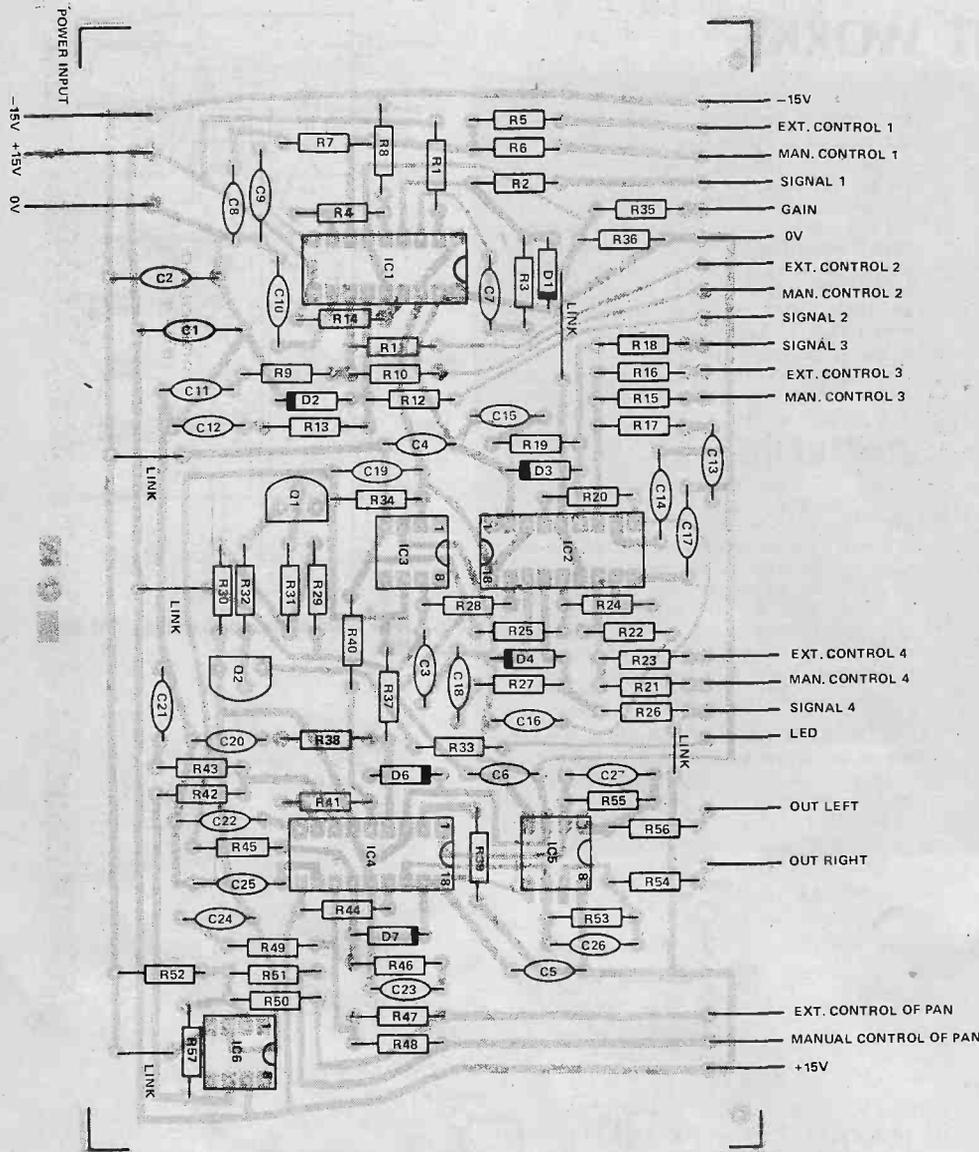


Fig.4. Component overlay of the VCM.

RESISTORS

R1,14,20,	150k 1% metal film
28,50,52	
R2,5,11,	100k
12,16,18,23,	
26,31,37,42,	
45,47	
R3,7,9,13,	1k0
17,19,22,27,	
33,36,38,43,	
46,49,54,56	
R4,24,41	6k8
R6,10,15,	150k
21,48	
R8,25,40	750R
R29	15k
R30,34	24k
R32	39k
R35	330k
R39,44	300k 1% metal film
R51,57	100k 1% metal film
R53,55	51k

POTENTIOMETERS

RV1-6	100k lin
-------	----------

CAPACITORS

C1,2	470n polyester
C3,4,5,6	100n polyester
C7,8,11,12,	10n polyester
13,15,16,18,	
20,21,23,24	
C9,10,14,	150p polystyrene
17,22,25	
C19	100p polystyrene
C26,27	22p polystyrene

SEMICONDUCTORS

IC1,2,4	CEM3330
IC3	TL081CP or equivalent
IC5	TL082CP or equivalent
Q1	BC558
Q2	BC548
D1,2,3,4,6,	1N4148 (1N914)
7	
D5	Red LED

Using The Mixer

A few guidelines on use are given to demonstrate the versatility achieved by incorporating voltage control.

1. A simplistic view would be to consider the mixer as four voltage controlled amplifiers with a common output. One technique often applied to a VCA is amplitude modulation (tremolo). Usually, however, the VCA is one of the last stages and, if a number of signals have been combined in a conventional mixer prior to the VCA, then the total signal has to be amplitude modulated. Using the voltage controlled mixer only parts of the signal need be modulated and the resultant effect can be more pleasing.

2. One of the early works with a synthesiser was Morton Subotnick's "The Wild Bull," recorded in 1968. In this work extensive use is made of a sawtooth waveform (high harmonic content) which is separated into four octave bands to provide the signals for a four-channel voltage controlled mixer. Each channel was controlled by an ASDR envelope shaper gated from a sequencer. This arrangement allows the separate timbral characteristics of any sound to

be independently treated. Furthermore, by varying the speed of the sequencer the characteristics of the sound can be made to vary widely, for example, as the rate is increased the four bands begin to sound simultaneously. Only a simple digital sequencer is required for the above and the voltage controlled mixer becomes the heart of a useful music making instrument within the body of the synthesiser. This type of approach is particularly useful for those without access to multi-track recording equipment.

3. Adding and subtracting waveforms from two or more oscillators set to different pitches has not been widely used with synthesisers due to the tendency for the voltage controlled oscillators to track at different rates. The latter makes it impossible to maintain the same tone quality over several octaves. With the incorporation of synchronising facilities in modern VCOs this problem is overcome and additive and subtractive synthesis is a worthwhile field of exploration. Of course, subtractive synthesis is already widely employed by filtering techniques but more subtle tones can be obtained by mixing techniques.

BUYLINES

The voltage controlled mixer PCB and all the components shown on the circuit diagram are available for £24.62 including postage and VAT from Digi-sound Limited, 13 The Brooklands, Wrea Green, Preston, Lancashire PR4 2NQ.

4. A major application of the voltage controlled mixer is the ability to alter loudness and harmonic content with pitch. One of the criticisms of 'live' electronic music is the precise nature of its sounds and the initial excitement of a new sound turns to boredom as the brain adversely reacts to its repetitive nature. By applying the keyboard control voltage (or its inverse, or a proportion of either) to one or more of the mixer control inputs then the amplitude or harmonic content (often both) will vary with pitch and so provide a useful means of dynamically altering the timbral characteristics of the sound.

5. Applying a low frequency waveform to the pan control input can produce some interesting spatial and rotational effects, but for greatest impact this technique should be used sparingly.

6. Mention has been made of waveforms, envelope shapers and keyboard voltage for control of the mixer and in common with other voltage controlled modules any variable voltage source may be used. A foot pedal control adapted to provide a 10V output is particularly useful in conjunction with a mixer.

Processor Module


As discussed in Part 1, the low output impedance and high input impedance of the modules allows one output to drive several inputs without overloading or introducing appreciable errors. Thus attenuators should be on inputs rather than outputs so that their level can be independently adjusted. Likewise the modules should ideally have a number of commoned output sockets to facilitate distribution of the signal to other modules.

Additional attenuating potentiometers and jack sockets add to cost and also take up valuable panel space and so for situations where the controls are used infrequently a distribution panel was discussed last month.

A suggested configuration for the module (a 'processor') is two distribution blocks which allow one input to be distributed to three outputs with or without attenuation.

Secondly, there are a further two

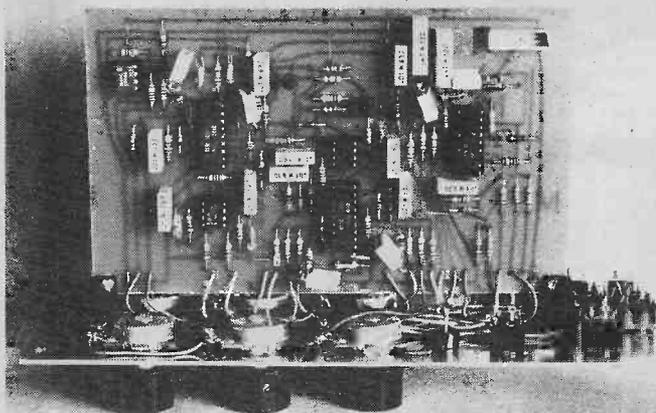The mixer PCB attached to its front panel.



blocks which may be used as above, or the signal may be inverted via an op amp. In this instance inverting means subtracting the input voltage from 10 volts and not turning a positive input voltage into a negative one. This is achieved by adding components R3 and TP1 to a conventional unity gain inverter.

Another addition is the so-called 'lag processor' which is simply a low pass filter and akin to the usual portamento circuit. This is useful for slowing down fast control signals and also for delaying control signals.

Construction



Because of the simple construction of the circuits no printed circuit board is shown but a few construction hints may be of value. For the inverter a BIFET type op amp (LF 351, TL 081, etc) should be used to prevent distortion of high frequency or fast signals. The main precaution is to keep the signal input resistor close to the inverting pin. A small capacitor (10 or 22p) across the op amp also reduces the likelihood of instability. Furthermore, if you decide to install more than two inverters on a board then 100nF decoupling capacitors mounted close to the power supply pins of the IC will prevent the tendency of these devices to talk to one another. The circuit should be wired up so that the inverter stage is disabled when input jack socket 'B' is in use.

A LM1458 type op amp should be adequate for most applications of the lag processor. $RV1 = 2M2$ and $C1 = 220nF$ will provide sufficient delay and since short delays are the most useful a polyester capacitor may be employed.

ETI

Panel layout of the mixer.

The mixer PCB installed in its case.

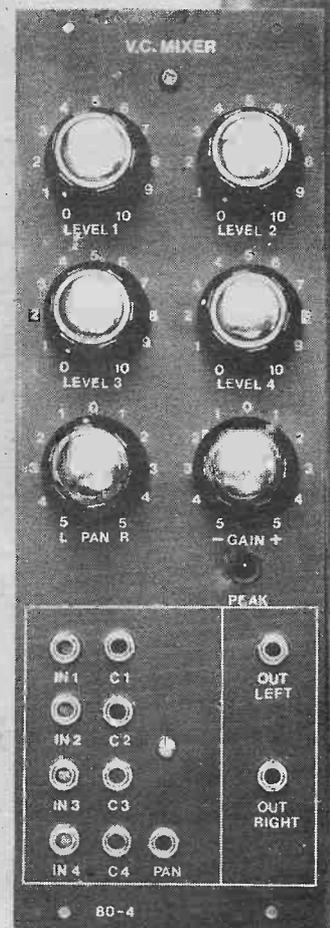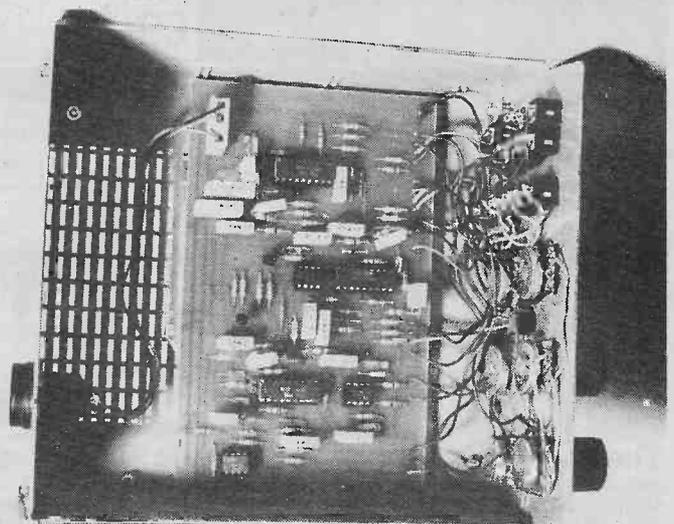


MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE

£6.95

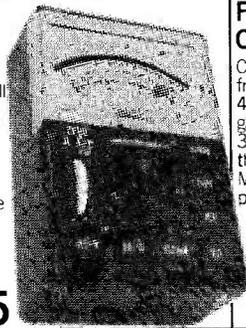

6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Reg. 9V battery. 22-351. REG. PRICE

£79.95




MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megaohm. 0-100-1k-101C-100k-3 megaohms. Reg. 9V battery. 22-209.

REG. PRICE


£29.95

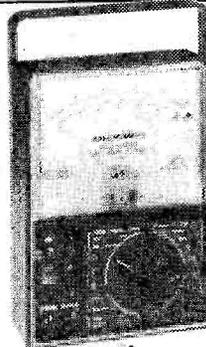

TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE **£9.95**

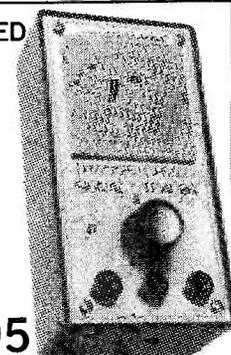

DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.


REG. PRICE **£19.95**



SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE **£2.79**

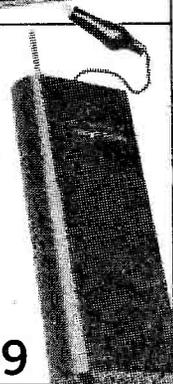

AC/DC CIRCUIT TESTER


Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSb and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.


REG. PRICE **£229.95**

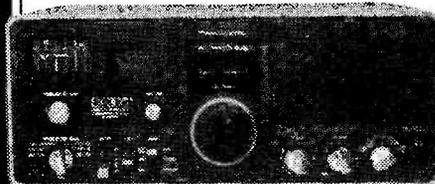

DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.


REG. PRICE **£9.95**

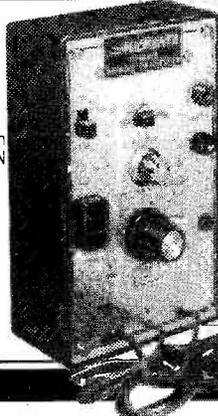

VARIABLE POWER SUPPLY

Power project boards. IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**

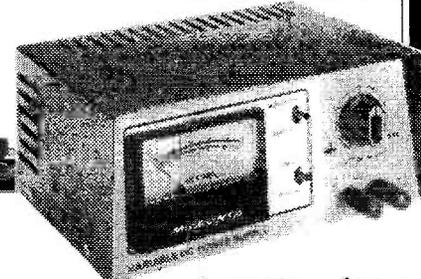


You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

TANDY

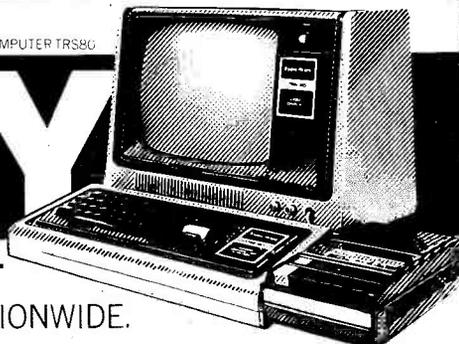

TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access. Bank America. Trustcard. We'll be there.

Prices may vary at individual stores.

The largest electronics retailer in the world.

* Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



TECH TIPS

Example game of "Grand-Prix".

Winner is the first player to travel 1000 km. Pre-load store 3 with 0.25.

Grand Prix

M. R. Harrison

Grand Prix can be played on the following calculators — Casio fx-201p and Casio Profx-1.

The game is played by the calculator explaining the conditions of the road by means of a skill factor. The conditions are as below:

- 1.5+ Excellent conditions and on a straight.
- 1.4+ Very good.
- 1.3+ Good.
- 1.2+ Reasonable road surface but bends in road. Take care.
- 1.1+ Greasy road surface due to water.
- 1.0+ Oil !!!! DANGER.

The player whose turn it is, decides how fast he dare travel without crashing. The faster the speed the further the distance the player's car will travel. The winner is the first person to travel a chosen distance.

The game is played as follows:

1. Press start.
2. Skill factor is shown for player 1.
3. Player 1 enters his required speed.
4. Total distance player 1 has travelled will only be displayed if player 1 did not crash.
5. Skill factor is shown for player 2.
6. Player 2 enters his required speed.
7. Total distance player 2 has travelled will only be displayed if player 2 did not crash.
8. Go to stage 2.

The first part of the program is to obtain a random number between 0 and 1. This is done by multiplying another number between 0 and 1 again by -3.94. To the result, 1 is continually added until the result becomes positive. This result is used in obtaining the next random number in the same way and also in the next stage of the program, which is to obtain a skill factor. The skill factor is found by dividing the random number previously calculated by 2 and then adding on 1.021.

Player 1			Player 2		
Skill Factor	Speed (kmph)	Dist Travelled (km)	Skill Factor	Speed (kmph)	Dist Travelled (km)
1.03	10.00	0.15	1.49	100.00	80.81
1.17	20.00	5.92	1.44	90.00	crash!!
1.35	30.00	24.46	1.21	20.00	88.14
1.28	23.00	35.91	1.49	110.00	177.44
1.15	20.00	41.21	1.49	120.00	274.60
1.16	20.00	46.78	1.46	120.00	crash!!
1.27	30.00	61.15	1.03	15.00	275.08
1.45	110.00	crash!!	1.30	35.00	293.68
1.41	100.00	crash!!	1.46	100.00	crash!!
1.30	35.00	crash!!	1.45	80.00	354.48
1.32	35.00	80.86	1.34	37.50	376.95
1.25	25.00	92.16	1.09	20.00	crash!!
1.22	23.00	101.14	1.23	25.00	387.13
1.14	20.00	107.94	1.34	44.00	crash!!
1.27	25.00	119.92	1.04	10.00	387.43
1.46	90.00	189.52	1.28	33.00	403.72
1.50	150.00	crash!!	1.12	15.00	406.67
1.13	17.50	193.55	1.08	20.00	crash!!
1.26	25.00	204.90	1.07	12.00	407.96
1.30	35.00	223.93	1.38	50.00	441.47
1.07	10.00	225.01	1.31	45.00	crash!!
1.38	52.00	259.54	1.09	15.00	443.53
1.25	30.00	crash!!	1.13	17.50	447.14
1.11	15.00	262.25	1.16	20.00	452.72
1.46	90.00	crash!!	1.27	30.00	

ETC

By keeping a record of one's attempts, the player can soon realise how fast he may go with certain skill factors.

For a new game, stores 7 & 8 have to be cleared.

GRAND-PRIX

Steps:—

ST*0: GOTO9: I=9: GOTO8:	13
GOTO9: I=K2: GOTO8: GOTO0:	27
SUB*9: 3=3x6:	36
ST*4: 3=3+9:	45
IF3=K0:4:5:5:	57
SUB*8: IM=3÷K2+0:	69
ANS IM:	72
2=9 10 ^x x IM TAN:	80
I=I3K3:	87
ENT IM:	90
1=IM: IF IM=2:1:1:3:	105
ST*1: I=I+K3:	115
IM=3SINx1+IM:	124
ANS IM:	127

Pre-load memory stores as below:—

Store 9	1
Store 6	-3.94
Store 0	1.021
Store 3	any number between 0 and 1.

Rad-Deg-Grad switch *must* be set on "Radians".
For a new game, stores 7 & 8 have to be cleared.

All these only from HENRY'S



IN STOCK
WITH FREE POWER SUPPLY.

NASCOM-2 + FREE 16K RAM

Here's an offer you can't refuse:

Because of the lack of availability of MK 4118 RAMs, Nascom Microcomputers is supplying its Nascom 2 without the 8 spare 4118s but with a FREE 16K dynamic RAM board.

When the 4118s become available, Nascom 2 purchasers can have them at the special price of £80 + VAT for the 8K. So, for £295 plus VAT this is what you get:

NASCOM-2 with 32K RAM
£345 VAT
P&P 1.50

Buy British It's Best!!

MEMORY

- 16K RAM board (expandable to 32K).
- 8K Microsoft BASIC.
- 2K NAS-SYS 1 monitor.
- 1K Video RAM.
- 1K Workspace/Scratchpad RAM.
- Main board sockets for the 8x4118s or 2708 EPROMS.

No more slaving over a hot soldering iron - the Nascom 1 is now supplied BUILT!
Britain's biggest small system is available fully constructed for you to slot into your own housing for the ridiculously low price of £175 plus VAT (kit price still only £165 plus VAT). **EX-STOCK**

nascom-1
12" x 8" PCB carrying 5LSI MOS MOS memory packages. There is on-board unmodulated operating user RAM. Board Z80 which executing 158 instructions including all 8080 code.

With NAS-SYS **SCOOP KIT NOW ONLY FULLY GUARANTEED** Less P10 **£125**

MEMORIES

- MK4116 16K **£7.00**
- DYNAMIC RAM**
- 8 for **£55.00**
- MK 4027 4K **£3.80**
- 8 for **£27**
- 2708 **£8.50**
- 2102 **£1.20**
- 2716 **£32.00**
- Full List P.O.R.

MICROPROCESSOR

- Z80A which will run at 4MHz but is selectable between 1/2/4 MHz.

HARDWARE

- Industrial standard 12" x 8" PCB, through hole plated, masked and screen printed. All bus lines are fully buffered on-board.

INTERFACES

- Licon 57 key solid state keyboard.
- Monitor/domestic TV interface.
- Kansas City cassette interface (300/1200 baud) or RS232/20mA teletype interface.

The Nascom 2 kit is supplied complete with construction article and extensive software manual for the monitor and BASIC.

EXPANSION NASCOM-1

- *Expansion buffer board **£32.50**
- MEMORY KITS (include all hardware)
- 8K **£85**
- 16K **£140**
- 32K **£200**
- *I/O board with decoders and all hardware except ICS will accept up to 3 PIOs, 1 CTV and 1 UART **£35**
- NEW T 4 operating system in (2) 2708 EPROMS UPWARDS **£25.00**
- COMPATIBLE FROM T2 and B-BUG **£25.00**
- NAS SYS 1. MONITOR **£25.00**

Programming Manual £4.50

- *Power supply for up to 32K expansion Mk II **£24.50**
- *8A power supply for larger than 32K expansion **£60.00**
- *Expansion card frame **£29.50**
- *EPROM programmer **£13.95**
- SMART-1 **£74.95**
- Tiny Basic **£25.00**
- Super Tiny Basic (with editor and machine utility routines) **£35.00**
- Zeap assembler editor **£32.00**
- 8K BASIC ROM **£40.00**
- Naspen Text Handler **£30.00**
- Disassembler **£9.95**

NASCOM IMP
£325 VAT P&P £2.50

NASCOM-1 BUILT
£140 VAT P&P 1.50

NEW

The Nascom IMP (Impact Matrix Printer) features are:


- 60 lines per minute.
- 80 characters per line.
- Bi-directional printing.
- 10 line print buffer.
- 96 character ASCII set (includes upper/lower case).
- Automatic CR/LF.
- Accepts 8 1/2" paper.

- Optional tractor feed.
- Baud rate from 110 to 9600
- External signal for optional synchronisation of baud

NASCOM IMP PLAIN PAPER PRINTER

Fully built and housed in a stylish enclosure for just **£325 plus 15% VAT**. Interfaces with all micro computers. Deliveries Ex-Stock.

HALF PRICE OFFER

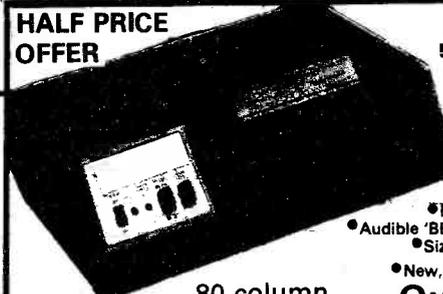

80 column

CENTRONICS P1 PRINTER

EXCLUSIVE TO HENRY'S 50% OFF MAKER'S PRICE


- Software selectable 20, 40 and 80 column using 120mm aluminium-lined paper. 1 roll supplied.
- 150 lines per minute.
- Centronics parallel data interface for Nascom, Tandy, etc.
- 240volt mains input.
- ASCII character set
- Paper feed, and on/off select switches
- Audible 'BELL' signal. Weight 10lbs
- Size: 13" x 10 1/2" x 4 1/2" LIST PRICE £400

Our Price £195.00

plus VAT post FREE

Spare paper £9 for 3 Rolls + VAT

FERRANTI COMPUTER KEYBOARDS

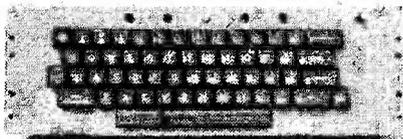

60 Key ASCII Coded in steel case
Latched output complete with Plug & Cable with circuit to convert to T.T.L. levels.

In good condition at only **£25** + VAT P/P £2.50

Your London & National Nascom Distributor.
Export Orders deduct VAT, but add 5% carriage
Official Export & Educational Orders welcome
Our Telex 262284 Mono Ref. 1400 Transonics

COMPUTER SEND BROCHURE 15p FREE



Henry's

Computer Kit Division
404 Edgware Road, London, W2, England
01-407 6822




Gyrator Smoother

J. P. Macaulay

Although this circuit was developed to supply a well smoothed supply to a stereo class A amplifier it is well suited to many other applications. The circuit is based on the dual op amp LM358. A1 is used as an gyrator, C1 being amplified by the ratio of R3 to R4, ie 1000X. The simulated capacitor thus formed between the output of A1 and ground is 100n.

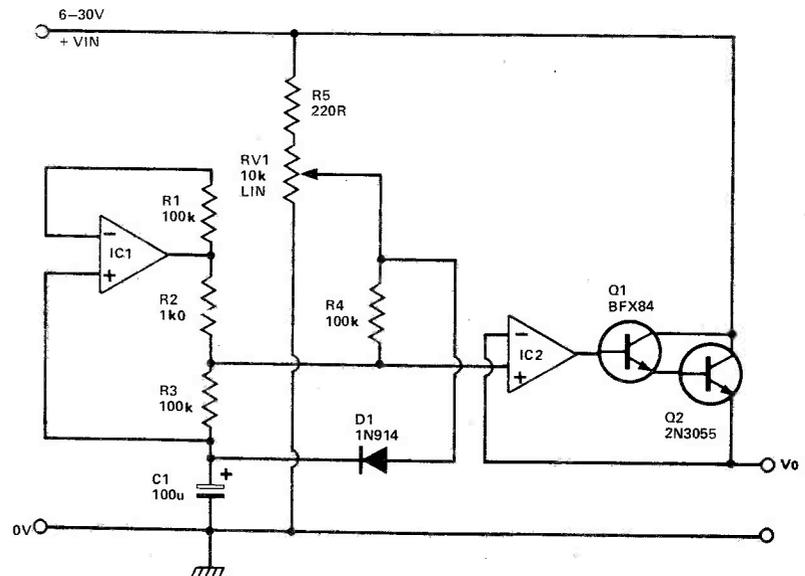R5 and RV1 set the output voltage whilst R4 in series with the 'capacitor' forms a smoothing network with a time constant of 10,000 seconds! In order to avoid protracted turn on times the diode, D1, rapidly charges C1 to within 0V6 of the nominal output voltage within two seconds. Ripple is not measurable with the prototype when supplying 3A into a load. A2 and the Darlington



output pair Q1 and Q2 form a voltage follower with an output current

capacity in excess of 10A, if Q2 is mounted on a hefty heatsink.


Motorcycle Anti-Theft Alarm

C. R. Goble

IC1a,b form a monostable triggered by mercury switch S1. IC1c then provides a low output, allowing the charge on C5 to decay over a couple of seconds through R7. After this short delay IC1d allows RL1 to sound the alarm bleeper and the astable around IC2a,b flashes the bike headlight via RL2. After a period the monostable resets and arms the

circuit once more. If the battery leads are cut then another astable around IC2c,d will switch the bleeper on and off continuously, via RL1, until disarmed by lockswitch S2. C4 discharging prevents the alarm from sounding for about 20 seconds after initial arming. RL2 contacts should be suitably rated and, ideally, RL1 should take only a low current to help con-

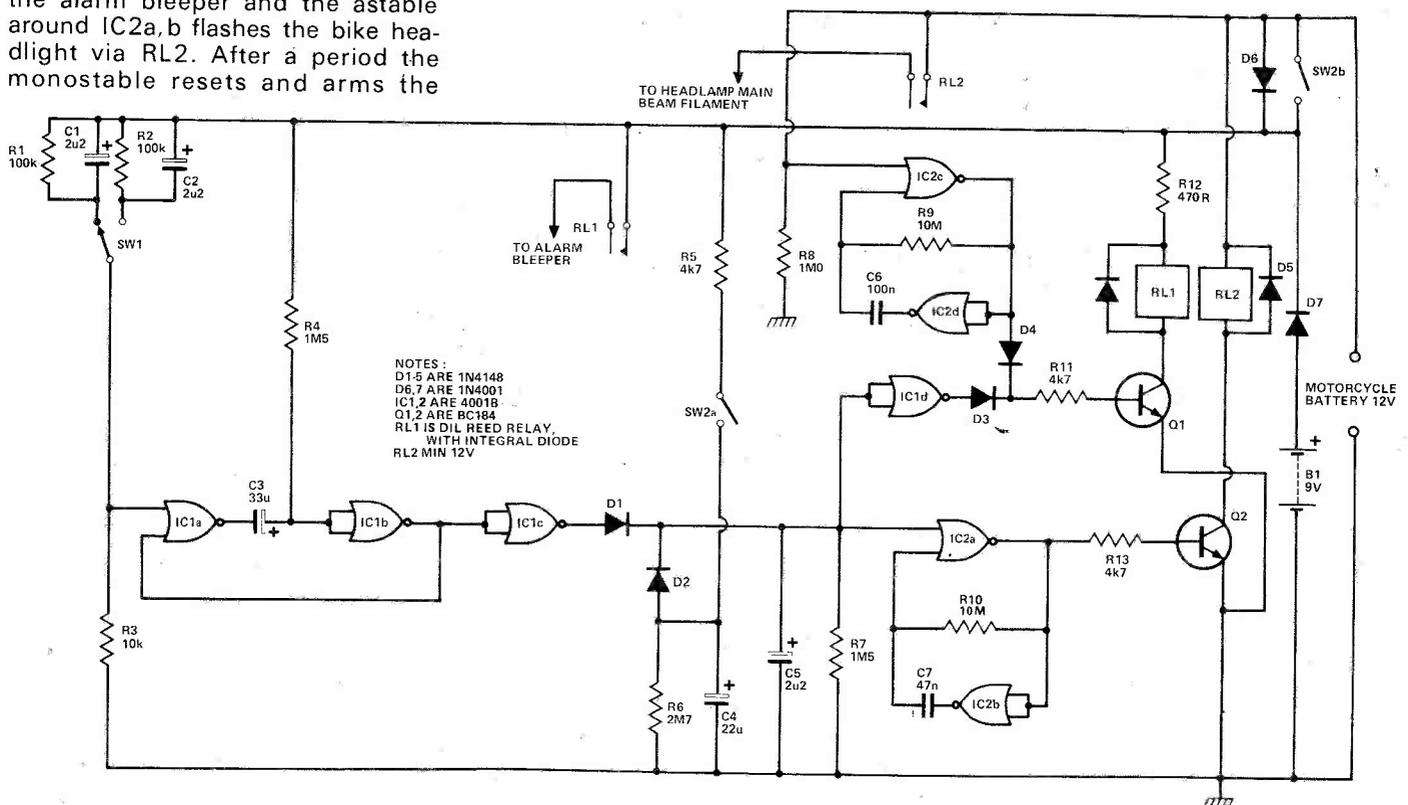serve standby power. Current drain when untriggered amounts to that through S1.6V operation is possible with 6V relays although values may need altering to preserve timing. Mercury switch S1 can be formed either from one double switch or from two single switches, mounted across the 'bike and wired to give a changeover action.



8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

KANSAS CITY

low error rate tape interface.

2 MICROPROCESSORS

Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10^{-99} to 9×19^{99} to 8 figures plus 2 exponent digits.

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

resident in EPROM.

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.

**COMPLETE KIT
NOW ONLY
£249 + VAT**



Cabinet size 19.0" X 15.7" X 3.3". Television by courtesy of Rumblelows Ltd., price £5B 62

Kit also available as separate packs: e.g. PCB, Keyboards, Cabinet, etc.

**NEW LOW
PRICE!**

POWERTRAN

PSI Comp 80. Z80 Based powerful scientific computer Design as published in Wireless World, April-September, 1979.

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete!

Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board. 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer. 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.

PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion plug socket is made via a ribbon cable.

Mother board:

Fibre glass double sided plated through hole P.C.B. 8.7" x 3.0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug **£39.90**

8K Static RAM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" **£12.50**
Set of components including IC sockets, plug and socket but excluding RAMs **£11.20**
2114L RAM (16 required) **£5.00**
Complete set of board, components, 16 RAMS **£89.50**

8K ROM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" **£12.40**
Set of components including IC sockets, plug and socket but excluding ROMs **£10.70**
2708 ROM (8 required) **£8.00**
Complete set of board, components, 8 ROMs **£78.50**

Floppy Disk, PROM programmer and printer interface coming shortly!


Value Added Tax not included in prices

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until April 30th, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subsequent to 15% surcharge for VAT. No charge is made for carriage. *Or current rate if changed.

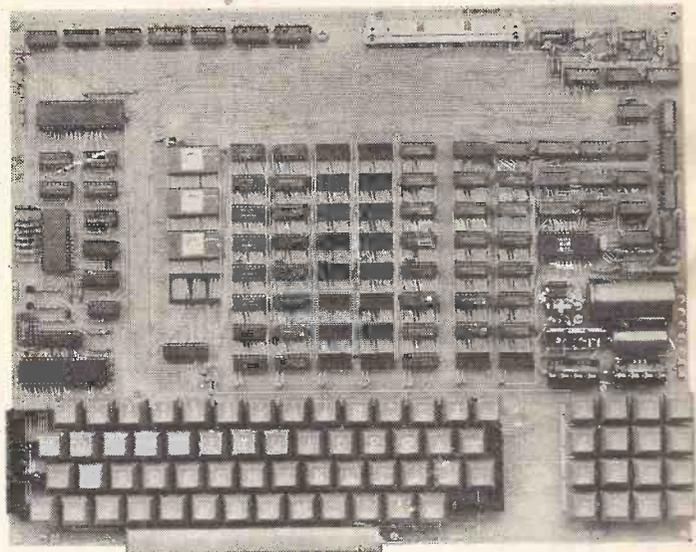SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.



UK Carriage FREE

POWERTRAN COMPUTERS

(a division of POWERTRAN ELECTRONICS)

PORTWAY INDUSTRIAL ESTATE

ANDOVER

ANDOVER HANTS SP10 3NM

(0264) 64455


TRANSAM

COMPONENTS AND SYSTEMS FROM TRANSAM COMPUTERS

- CP/M
- BASIC
- PASCAL

TRITON IS IMPRESSIVE!

PRACTICAL COMPUTING REVIEW DEC. 79.

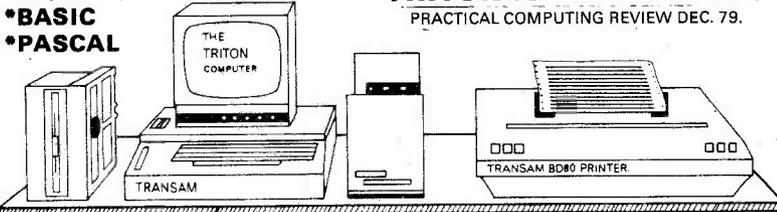

TRITON COMPUTER SYSTEM.

Designed for ease of construction and flexibility. Kits come complete and all components and software are available separately. UK designed and supported. Fully documented hardware and software and a totally flexible approach to system building. Powerful and easy to use system monitors - a range of languages available. Firmware is Eprom based and upgrading from one level to the next is easy.

- L4.1 with 1k monitor 2k basic £286
- L5.1 with 1.5k monitor 2.5k basic £294
- L6.1 with 2k monitor 7k basic £399
- L7.1 with 2k mon 8k extended basic £409
- L8.1 4k ed/mon 20k res pascal £611
- L9.1 CP/M disc based system P.O.A.
- 8k ram card kit (2114L) £97
- 8k Eprom cards (EXCL 8x2708) £31
- Motherboard expansion 8 slot £50
- Trap-res assm/edit etc (8x2708) £80
- Transam BD80 Bi-dir printer £595
- TVM10 video monitor 9" £79
- Eprom prog (2708) kit £29.50

SEND FOR OUR CATALOGUE FOR FULL DETAILS OF TRITON FEATURES!

CP/M AVAILABLE NOW FOR TRITON

Disc operating system complete with text editor, assembler, debugger, system utilities and complete file management. Makes Triton fully CP/M compatible and able to run CP/M based software. Triton will support up to four 5 1/4 or 8" drives single or double density full CP/M software user group facilities available. SAE for details.

DISK DRIVES & POWER SUPPLIES

SHUGART



- SA400 5 1/4" drive £205.00
- SA800 8" drive £380.00
- Power one quality power supplies
- CP249 1x5 1/4 PSU £33.00
- CP323 2x5 1/4 PSU £60.00
- CP205 1x8" PSU £56.00
- CP206 2x8" PSU £76.00

TCL PASCAL CP/M compatible

A standard Pascal compiler available on a resident (20k) Eprom based configuration* or available to run under CP/M on 8" disc plus documentation. CP/M version £90 - P.O.A.

DIL PLUG SOCKETS & SWITCHES

W/WRAPSKTS	OILSKTS	DILPLUGS	DILSWITCHES
8DIL 0.20	8DIL 0.14	14DIL 0.80	14DIL 1.20
14DIL 0.25	14DIL 0.15	16DIL 0.85	7DIL 1.15
16DIL 0.42	16DIL 0.17	SCOTCHFLEX 6DIL	1.80
18DIL 0.60	18DIL 0.24	14DIL 1.30	16WZIF* 4.95
24DIL 0.52	20DIL 0.27	16DIL 1.50	24WZIF* 6.20
28DIL 0.74	24DIL 0.30	24DIL 2.80	
40DIL 0.95	28DIL 0.36		
	48DIL 0.50		


ZERO INSERTION FORCE

FULL RANGE OF MICRO SUPPORT CHIPS - IN STOCK

SN74LS00N	22	SN74LS04N	21	SN74LS138N	95	SN74LS195AN	95	SN74LS325N	2.55	SUPPORT	2.20	RAMS	2.32
SN74LS01N	22	SN74LS05N	21	SN74LS139N	95	SN74LS199N	1.20	SN74LS326N	2.55	8212	2.20	2101	2.32
SN74LS02N	26	SN74LS06N	1.50	SN74LS145N	1.20	SN74LS197N	1.20	SN74LS327N	2.55	8216	2.80	2102L4	1.20
SN74LS03N	26	SN74LS07N	35	SN74LS148N	1.25	SN74LS221N	1.25	SN74LS352N	1.35	8224	2.80	2111	2.32
SN74LS04N	26	SN74LS074N	40	SN74LS151N	65	SN74LS240N	2.20	SN74LS353N	1.50	3853 (FR)	10.00	2112	2.46
SN74LS05N	26	SN74LS075N	46	SN74LS153N	60	SN74LS241N	1.90	SN74LS356N	65	8228	4.20	6810	4.00
SN74LS08N	20	SN74LS076N	35	SN74LS154N	1.60	SN74LS242N	1.90	SN74LS366N	65	8228A	1.75	8154	11.50
SN74LS09N	22	SN74LS078N	35	SN74LS155N	1.25	SN74LS243N	1.95	SN74LS367N	65	8128	1.90	2114L-450	5.50
SN74LS10N	18	SN74LS079N	1.15	SN74LS156N	1.25	SN74LS244N	2.10	SN74LS368N	65	8522	8.75	2114L-250	7.60
SN74LS11N	26	SN74LS080N	1.10	SN74LS157N	60	SN74LS245N	3.60	SN74LS373N	1.75	8251	6.00	74C820	11.00
SN74LS12N	25	SN74LS086N	40	SN74LS158N	99	SN74LS247N	1.25	SN74LS374N	1.70	8253	11.00	74C921	11.00
SN74LS13N	55	SN74LS080N	65	SN74LS160N	1.15	SN74LS248N	1.95	SN74LS375N	1.72	8255	6.00	74C929	11.00
SN74LS14N	89	SN74LS081N	99	SN74LS161N	1.15	SN74LS249N	1.30	SN74LS377N	1.75	8257	£11.00	4027	5.00
SN74LS15N	25	SN74LS082N	90	SN74LS162N	1.15	SN74LS251N	1.45	SN74LS378N	1.32	8259	12.50	4044	7.00
SN74LS20N	22	SN74LS083N	65	SN74LS163N	90	SN74LS252N	1.25	SN74LS379N	1.40	8155	12.50	4045	7.00
SN74LS21N	26	SN74LS086AN	1.20	SN74LS164N	1.50	SN74LS257N	1.40	SN74LS381N	3.85	6402	5.00	4060	7.00
SN74LS22N	26	SN74LS086N	1.75	SN74LS165N	1.70	SN74LS258N	95	SN74LS386N	57	8821P	4.50	2107	7.80
SN74LS26N	29	SN74LS107N	39	SN74LS166N	1.45	SN74LS259N	1.45	SN74LS390N	1.98	8850P	4.80	4116158 for 8100	
SN74LS27N	35	SN74LS109N	39	SN74LS168N	1.85	SN74LS260N	39	SN74LS393N	1.50	8852P	5.50	4118	20.00
SN74LS28N	35	SN74LS112N	39	SN74LS169N	1.95	SN74LS261N	3.50	SN74LS395N	1.80	AY52378	11.50	Z80P10	8.00
SN74LS30N	25	SN74LS113N	44	SN74LS170N	2.50	SN74LS263N	39	SN74LS396N	1.70	MC14411	12.00	Z80CIC	8.00
SN74LS32N	27	SN74LS114N	44	SN74LS173N	2.20	SN74LS273N	1.85	SN74LS398N	2.75	M57109	12.43	Z80AIP10	9.50
SN74LS33N	39	SN74LS122N	79	SN74LS174N	1.15	SN74LS279N	79	SN74LS399N	1.80	M57160	10.00	Z80ACTC	9.50
SN74LS37N	29	SN74LS123N	90	SN74LS175N	1.05	SN74LS280N	1.75	SN74LS424A	4.50	M57161	10.00	EPROMS	
SN74LS38N	29	SN74LS124N	1.60	SN74LS181N	2.75	SN74LS283N	1.80	SN74LS445N	1.25	TMS8011	5.00	1702	5.00
SN74LS40N	25	SN74LS125N	65	SN74LS182N	1.75	SN74LS289N	1.00	SN74LS447N	1.25	81LS91	1.80	5204	2.20
SN74LS42N	79	SN74LS126N	65	SN74LS183N	1.75	SN74LS293N	1.80	SN74LS490N	1.95	81LS92	1.80	2708	8.00
SN74LS47N	95	SN74LS132N	75	SN74LS182N	1.45	SN74LS295AN	2.20	SN74LS498N	95	81LS97	1.80	2516	25.00
SN74LS48N	95	SN74LS133N	39	SN74LS183N	1.75	SN74LS298N	2.20	SN74LS499N	95	81LS98	1.80	2532	50.00
SN74LS49N	1.08	SN74LS136N	40	SN74LS194AN	1.89	SN74LS324N	1.80	SN74LS670N	2.70				

DPS.1 MAINFRAME - PASCAL SYSTEM

\$100 to IEEE spec

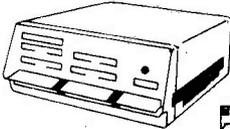

WE STOCK THE FULL RANGE OF \$100 CARDS AND ACCESSORIES

ITHACA


PASCAL/Z build your own Pascal Micro Development system. IEE - \$100 bus system using DPS1 mainframe. Supports K2, ASSEMBLEZ and PASCAL/Z on 8" disc.

\$100 BOARDS

- 8K Static RAM board (450ns) £123.75
- 8K Static RAM board (250ns) £146.25
- Z80 cpu board (2MHz) £131.25
- Z80 cpu board (4MHz) £153.75
- 2708/2716 EPROM board £63.75
- Prototype board (bare board)
- Video display board (64x16, 128U/Ascii) £108.75
- Disc controller board £131.25
- K2 disc operating system £56.25
- ASSEMBLEZ Macro Assm £37.50
- PASCAL/Z compiler £131.25

MULTIWAY CONNECTORS

INSULATION PIERCING	35/70	4.60
20 way plug	2.30 39/72	4.74
26 way plug	2.70 40/80	5.00
34 way plug	3.30 43/86	5.50
50 way plug	4.80 50/100	5.80
20 way skt	3.40	GOLD. 156 PITCH
26 way skt	4.00 6/12	1.25
34 way skt	4.80 10/20	1.50
30 way skt	6.00	2.00
EDGE CONN PCB	15/30	2.20
GOLD 1" PITCH	18/36	2.30
22/44	3.20 22/44	2.65
25/50	3.60 28/56	3.30
28/56	3.90 36/72	3.90
30/60	4.15 43/86	4.60

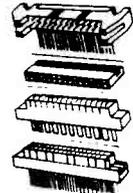

64 way DIN male 2.50
64 way DIN female 4.50

VISIT OUR SHOWROOM

WE ALSO STOCK - A comprehensive range of books-magazines, VERO products including \$100 and Eurocard and Wire Wrap equipment, Weller soldering equipment, Ribbon Cables, tools, tapes, diskettes and connectors.

CRYSTALS	4MHz	2.10	F813850	9.50
100k	4.43M	1.00	8080A	6.33
200k	5MHz	1.70	8809	24.00
1MHz	6MHz	2.70	280	8.00
1000k	7MHz	2.70	280A	15.00
1843k	7.168M	2.50	8085A	12.95
2MHz	8MHz	2.70	6502	8.00
2457k	10MHz	2.70	SCMP11	10.00
3276k	10.7M	2.70	8802	13.95

ALL PRICES

Exclude VAT & P/P
VAT 15% P & P 40p on small orders.
For larger items please Tel.
Telephone credit card orders accepted subject to £5 min.
RAPID MAIL ORDER SERVICE




CATALOGUE

NEW A4 SIZED ONLY 40p & S.A.E.



1980

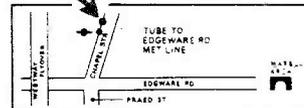VISIT OUR SHOWROOM SOON
9.30-5.30 Mon-Fri
1.30-2.30 closed lunch
9.30-5.00 Sat
Thursday half day 1.30



TRANSAM COMPONENTS LTD, 12 CHAPEL STREET, LONDON NW1

Tel: 01-402 8137 Telex: 444898

TTL CMOS 74LS LEDs

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

PCB OFFERS
 (1A) Video Store PCB 115mm x 94mm containing 10xTMS 3409 (4x80 Dyn Shift Reg.) + Discretes, etc. £2 each, p&p 30p (limited stocks).
 (1B) Audio amp PCB (LM380) 9-18v d.c., output 2½ wats into 8 ohm with heatsink. 1.25 watt 4ohm without heatsink. £1.50 p&p 25p.
 (1C) PCB 215mm x 290mm 12xTMS 3122J (or sim.) Hex 32-bit Shift Reg. + 39 ICs. £2 + 50p p&p (limited stocks).

MPU CORNER
 2112 (200ns) £3. 2114 (450ns) £4.50.
 1702 £2.50; 2708 (400ns) £7.25
 2716 (Single Rail) £28.50.
 74125 4 for £1 + p & p 25p.
 MK 1002P (dual 128 bit Shift Reg) 35p.
 LM711CH (Voltage Comparator) 30p.
 MM5240 Character Generator + Data 2560 Bit (64 x 8 x 5) £3.50, p & p 25p.

(All Full Spec)
D TYPE CONNECTORS
 9 Way: plg 40p, skt 40p.
 15 Way: plg 40p, skt 50p.
 15 Way: wirewrap, plugs only 75p.
 25 Way: plg £1.00, skt £1.00. (RS232).
 25 Way: ribbon plugs £1.20.
 25 Way: ribbon sockets £1.20.
 37 Way: plg £1.40, skt £1.40.
 50 Way: skt (wirewrap) £1.65.
 50 Way: skt £1.45. p&p 25p

COVERS
 37 Way: 80p.

DISPLAYS
 MAN 72 7 seg CC £1.25, p/p 25p.
 Burroughs Panaplex 9 Dig. + skt and bezel £1.00, p/p 25p.
 LED 3 Digit DIL 55p, p/p 25p.
 LED 4 Digit DIL HP 5082 CC 0.11" (RED), £1.50, p/p 25p.

SUPERSAVER
 Ribbon Cable Headers 16 DIL Jernym, gold plated, with cover. 45p, p&p 25p.
SUPERSAVER 2
 Tantalum Capacitors 25 volt, 4.7 uF, 14 for £1.00, p & p 25p.
SUPERSAVER 3
 Mercury Batteries 1.35v 1AH. Dia. 15mm, height 18mm, 35p, p & p 25p.
SUPERSAVER 4
 HYBRID SYSTEMS DAC 371-8 8 Bit. DIL packaged, ideal MPU users with data. £2.95, p & p 25p.
SUPERSAVER 5
 LM 323K Voltage Regulator, 5 volt 3A, £4.50, p & p 25p.
SUPERSAVER 6
 RS 338-383 Miniature Decade Thumbwheel Switch, £1.65, p & p 25p.
SUPERSAVER 7
 SN74116 Dual 4 Bit latch 75p. p&p 25p.
 SN74181 Arithmetic Logic Unit. 80p, p&p 25p.
 SN74194 4 Bit Shift Register, 50p, p&p 25p.
 SN74198 8 Bit Shift Register. 75p p&p 25p.

SUPERSAVER 8
 BC108b 8p each or 100 for £7.00, p & p 25p.
SUPERSAVER 9
 4 Digit 7 segment LED Bubble Display, NSA 1540A Ex equipment, 5 for £1, p & p 25p.
SUPERSAVER 10
 9 way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, 35p, p & p 25p.
SUPERSAVER 11
 500 ohm multitrans trimpos PCB mounting, 30p, p & p 25p.
SUPERSAVER 12
 TMS 3128NC Static shift register, £1.50, p & p 25p.

SUPERSAVER 13
 PL529 (UHF) Elbow Connectors, 50p each, p & p 25p.
SUPERSAVER 14
 15423 Stud mounting rectifiers, 400v 10A, giveaway price, 10 for £2, p & p 25p.
SUPERSAVER 15
 20K Painton multitrans trimpos, PCB mounting, per box of 14 £2.50, p & p 25p.
SUPERSAVER 16
 Astec UM1163E 36 modulator plus PAL colour PCB (faulty). Few only £2.25, p&p 30p.

LEDs (Full spec)
 TL209, red, 10p. 0.2in. red 12p. 0.2in. green 28p. 0.2in. yellow 28p.
 RL54 red Axial lead, 15p. P&P on all above 25p.
VERNITRON Ceramic filters type FM4 10 7MHz 45p, p&p 25p.

TRANSISTORS, BD236 40p, BC183L 10p, BF195 10p, SGS 2N3055 30p, p&p on all 25p.
 TBA 810S, with data, 85p, 4-way DIL switches, 75p, MC1303 Dual Stereo preamp with data, £1.25. 7in. Nylon cable ties 100 for £1.50. All p&p 25p.
NEW SN76477 (Yes, back in stock). Sound Generator IC (Train, plane, explosion, laser gun etc.), with data £3.25, p&p 25p.

PCB KEYBOARD, 65mm x 82mm, 18 Key Clickers less Key tops, ideal Hexadecimal use 35p, p&p 25p.

PACKAGED 10-WAY REED relay 12V coil terrific value 50p, p&p 25p.

IR12T20T BRIDGE RECTIFIER 12A 200V, single or 3 phase, 95p, p&p 25p.

NEW PERANCEA CASES: These superb cases now stocked in the DIN range incorporating the following features. Matt black finished bezels snap fitting onto case

front, firmly retaining either of the front panes provided, one aluminium, one RED anti-reflective. Each case has two sets of guides with rear panel slots for PCB mounting
 Types available:
 DIN 145B H48xW96xD75(mm) £3.75
 DIN 236B H36xW72xD120(mm) £3.00
 DIN 146B H48xW96xD120(mm) £3.80
 P&P 25p. SAE for leaflet.

WE STOCK PETS
 8K version £599. SAE for PET SORCERER software lists at discount prices.
 We can also offer a 48-hour repair service for out of warranty PETS. Telephone for details. PET edge connector 40x40 £1.40 each p&p 25p.

IC HOLDERS (Low profile)
 8 DIL 12p 14 DIL 15p
 16 DIL 17p 18 DIL 20p
 22 DIL 28p 24 DIL 35p
 28 DIL 45p All p&p 35p

WE STOCK a vast range of TTL, CMOS, some 74LS, MINIATURE TOGGLES, etc.
PSUs. We have a large stock of power supplies at very realistic prices (callers).

RELAYS
 ITT 700 ohm Single pole changeover. 45p BANOR resettable double pole changeover 12V £1, both p&p 25p.

CIRCUIT BREAKERS
 450v AC 65v DC 0.5A 50p; ditto 7A 80p; p & p 25p.
ALLEN KEYS, 7/16" 5p; 12 for 50p, p&p 20p.

FOR CALLERS ONLY (or carriage at cost)
1 ONLY VIATRON 21 Data management system comprising processor, video monitor, cassette tape drive, keyboard, modem in-

terface, 4 lines of 80 characters per tape file record. Autosearch/list facilities. £125 + VAT (with manual).

1 ONLY MOORE REED miniport DT106 portable data terminal. 110 baud keyboard/printer with internal modem and ACOUSTIC COUPLER for connection to telephone. Standard ASCII code, Full/Half duplex, 80 char. per line. £300 + VAT.

1 ONLY GEC 9000 Visual Display Unit. Green phosphor, cursive character gen. 600/1200 baud asynchronous serial £95.
Shugart 801/8" drive (fully tested on exercisor) £300 inc. of VAT.

Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

FOR THE PROFESSIONAL USER. Gould mg5-20B PSU 5V 20A. Brand new and boxed (switching) £65 p&p £3.
 Gould PMA 47/10 0-15V 3A. Brand new £45 p&p £3.50. Many more in stock but in small numbers. Please phone for requirements.

LB ELECTRONICS
 11 HERCIES ROAD
 HILLINGDON, MIDDLESEX
 UB10 9LS, ENGLAND

New retail premises, now open Mon., Thur., Fri. and Sat. 9.30-6.00. Lunch 1-2.15 weekdays. We are situated just off the A40. Opposite Master Brewor.

UXBRIDGE 55399
 All components full spec.

LCD SNOOZE ALARM
 24-hr. alarm Hours, Mins., Secs., date, month, back-light, auto. calendar. Adjustable stainless steel bracelet, 12-month guarantee.

VT10
 Same day despatch
ONLY £10.95 (inc. VAT, P&P)



NEW LOW PRICE! LCD ALARM CHRONOGRAPH
 All usual features. Perpetual calendar, day, date. 24-hr. alarm with on/off indication. 1/10 second chronograph measuring set, lap and first and second place times. Dual time zone facility. Night light. 12-month guarantee.

ONLY £14.95 (inc. VAT, P&P)

Same day despatch Same as ETI spec.

VT06



50 HZ SUPERBOARD II
£216.20 inc. VAT

CASE — £29.95 inc.
 4k RAM — £40.25 inc.
 (8 x 2114)
 COLOUR — £59 inc.
 BUILT ADD ON



SOLAR LCD ALARM CHRONO
 * WATER RESISTANT (no vents)
 * MINERAL GLASS
 * ALL STAINLESS STEEL
 * ONLY 7mm THICK

24-hr. alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light.

ONLY £29.95 (inc. VAT, P&P)

Same day despatch

VT16



BELTIME CHRONOGRAPH
 9 Functions Hours, mins, secs, day, date, month, interchange feature, automatic calendar, backlight, net time/lap time. Stainless steel bracelet, 8mm thick

VT07
 Same day despatch
 (inc. VAT P&P)



ATARI VCS System
 — Most popular top range micro-video game
 Current cartridges — Air Sea Battle (27), Space War (17), Outlaw (16), Video Olympics (50), Breakout (12), Basketball (2), Surround (14), Blackjack (7), Basic Maths (8), Codebreaker (20), Hunt & Score (8), Miniature Golf (2), Skydiver (5), Street Racer (27), Chess (8), Levels Backgammon (8), Brain Games, Bowling.

Cartridges mostly — £14.95 inc.
 CHESS (8 levels) — £45.00 inc.
 BACKGAMMON — £34.50 inc.
 SUPERMAN — £23.25 inc.
 INDY 500 — £34.50 inc.
 ATARI VCS — £149.95 plus additional cartridge of your choice

SOLAR LCD ALARM CHRONOGRAPH
 24-hr. alarm with on/off indication 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility. Night light. details on request. Same day despatch.

ONLY £19.95 (inc. VAT, P&P)

Same day despatch

VT12



12-month guarantee. 15% VAT included. Cheques or P.O.s or telephone Card No. to Allow 7 days delivery unless specified



VIDEOTIME PRODUCTS, 56 QUEENS ROAD
 BASINGSTOKE, HANTS RG21 1REA. Tel: (0256) 56417 or 26620 TLX: 858747
 FACTORY AGENTS WANTED MONEY BACK GUARANTEE OFFERS SUBJECT TO AVAILABILITY. TRADE ENQUIRIES WELCOME

