

electronics today

ISSN 0142-7229

MAY 1980

60p

THE
ULTIMATE
KIT SURVEY



CHORUS MACHINE

**Infra-Red
Remote Control
LED VU**

Servo Tester

**Calculated
Watch Offer**



TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

All kits also available as separate packs (e.g. P.C.B., component sets, hardware sets, etc.). Prices in FREE CATALOGUE.

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an affective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features. The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal trim!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price!

**COMPLETE KIT
ONLY
£168.50 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)


**WE'VE MOVED!
NEW FACTORY UP!
PRICES DOWN!**

**INCREASED CAPACITY AT OUR BIG NEW FACTORY
MEANS MANY PRICES DOWN! ALL OTHERS FROZEN!**

TRANSCENDENT DPX

**DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER
ANOTHER SUPERB DESIGN BY SYNTHESIZER EXPERT TIM ORR — PUBLISHED IN ETI**

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

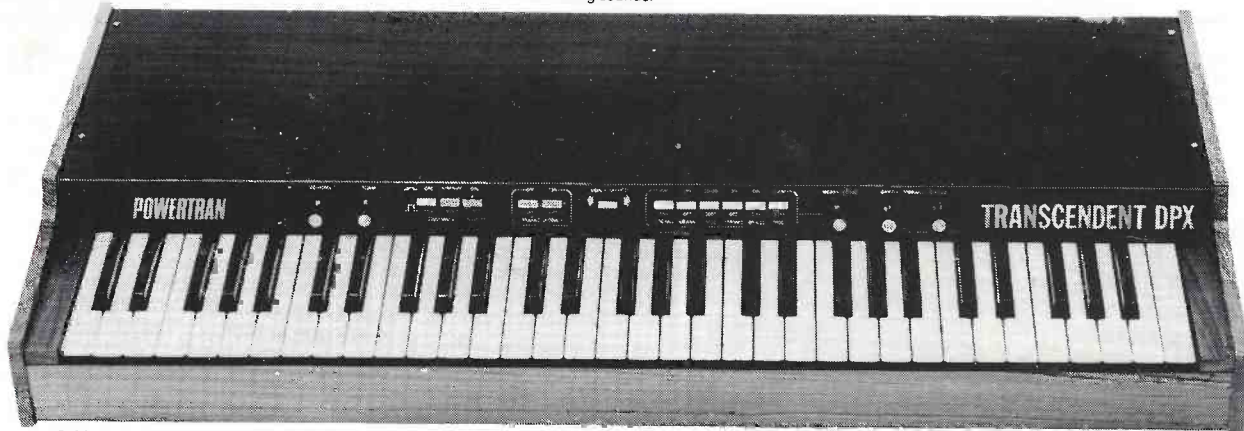

Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

COMPLETE KIT ONLY £299.00 + VAT!

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing etc., etc.)

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1,200!

POWERTRAN


**ORDERING INFORMATION AND MORE KITS
INCLUDING THE BLACK HOLE ON PAGE 8**



get kitted p.59



feeling peaky? p.78

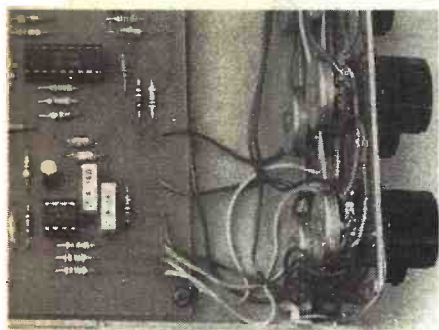

cut off point p.20

electronics today

MAY 1980 Vol 9, No 5

FEATURES

- | | | |
|------------------------|-----|-------------------------|
| DIGEST | 8 | Read it here first |
| MICROFILE | 28 | Micro-men take note |
| UNCERTAINTY PRINCIPLE | 40 | Are you sure? |
| AUDIOPHILE | 44 | Mining for iron on tape |
| ELECTRONICS KIT SURVEY | 59 | The ultimate overview |
| DESIGNERS NOTEBOOK | 84 | On the circuits circuit |
| RAVEN ON | 99 | Sizing up some gates |
| TECH TIPS | 105 | It's all yours! |
| PCB PATTERNS | 115 | Don't be foiled! |

PROJECTS

- | | | |
|----------------|----|--------------------------|
| MUSIC FILTERS | 20 | Four for Project 80 |
| REMOTE CONTROL | 33 | Do it from afar |
| SERVO TESTER | 52 | Mechanism checker |
| LED VU METER | 78 | Useful and pretty! |
| CHORALISER | 90 | Play along with yourself |

INFORMATION

- | | | |
|------------------|-----|----------------------------|
| CALCULATOR WATCH | 17 | Count the savings! |
| COMPUTING TODAY | 31 | Next issues offerings |
| ETI NEXT MONTH | 42 | What'll we do next? |
| BOOK SERVICE | 76 | No finer print |
| ETI 1999 | 96 | Don't miss this! |
| MARKETPLACE | 103 | Our regular amazing offers |
| ETIPRINTS | 111 | Make it easy on yourself |
| HE PREVIEW | 119 | The future Hobby! |

OVERSEAS EDITIONS

- | | |
|-------------|------------------|
| AUSTRALIA : | Roger Harrison |
| | Editor |
| CANADA : | Halvor Moorshead |
| | Editor |
| GERMANY : | Udo Wittig |
| | Editor |
| HOLLAND : | Anton Kriegsman |
| | Editor |



Member of the
Audit Bureau
of Circulation

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5

- | | |
|----------------------------------|-----------------------------|
| Ron Harris B.Sc. | Editor |
| Ian Graham B.Sc. | Assistant Editor |
| Tina Boylan | Editorial Assistant |
| Diego M. Rincon | Art Director |
| Dee Camilleri, Enzo Grando, | Production |
| Lorraine Radmore, Lorraine Stout | |
| Paul Edwards, Tony Strakas, | Technical Illustrators |
| Joanne Barseghian | |
| Ray Marston | Project Editor |
| Keith Brindley, John Fitzgerald | Project Engineers |
| Steve Ramsahdeo | Project Development |
| Christopher Surgenor | Group Advertisement Manager |
| Steven Rowe | Advertisement Manager |
| Sandie Neville | Advertisement Production |
| T.J. Connell | Managing Director |

PUBLISHED BY DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road, WC2H 0EE
Argus Distribution Ltd. (British Isles)
12-18 Paul Street, London
Gordon & Gotch Ltd. (Overseas)
QB Limited, Colchester

PRINTED BY

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

©MODMAGS 1980. All material is subject to worldwide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

If you want to get started in microcomputers - START HERE!

Microtan 65 is the most advanced, most powerful, most expandable, microcomputer available ~ It also happens to be the most cost effective!


An IDEAL educational aid.

FEATURES

- Based on the powerful 6502 microprocessor.
- Superb 1K monitor - TANBUG
- 1K RAM for user program, stack and display memory.
- Expands into a system.
- 136 page, software/hardware users manual.

● CONNECTS TO AN UN-MODIFIED DOMESTIC T.V. RECEIVER.

Expansion is via TANEX. In its minimum configuration TANEX offers 1K RAM, cassette interface, 16 parallel I/O lines, a TTL serial I/O port, two 16 bit counter timers, data bus buffering and memory mapping. Fully expanded TANEX is powerful, offering 7K RAM, 6K ROM, 8K Microsoft BASIC; 32 parallel I/O lines; two TTL serial I/O ports; a third serial I/O port with RS232 20mA loop. Full modem control and 16 programmable baud rates; four 16 bit counter timers, cassette interface; data bus buffering and memory mapping. Even in minimum configuration TANEX is supplied fully socketed.

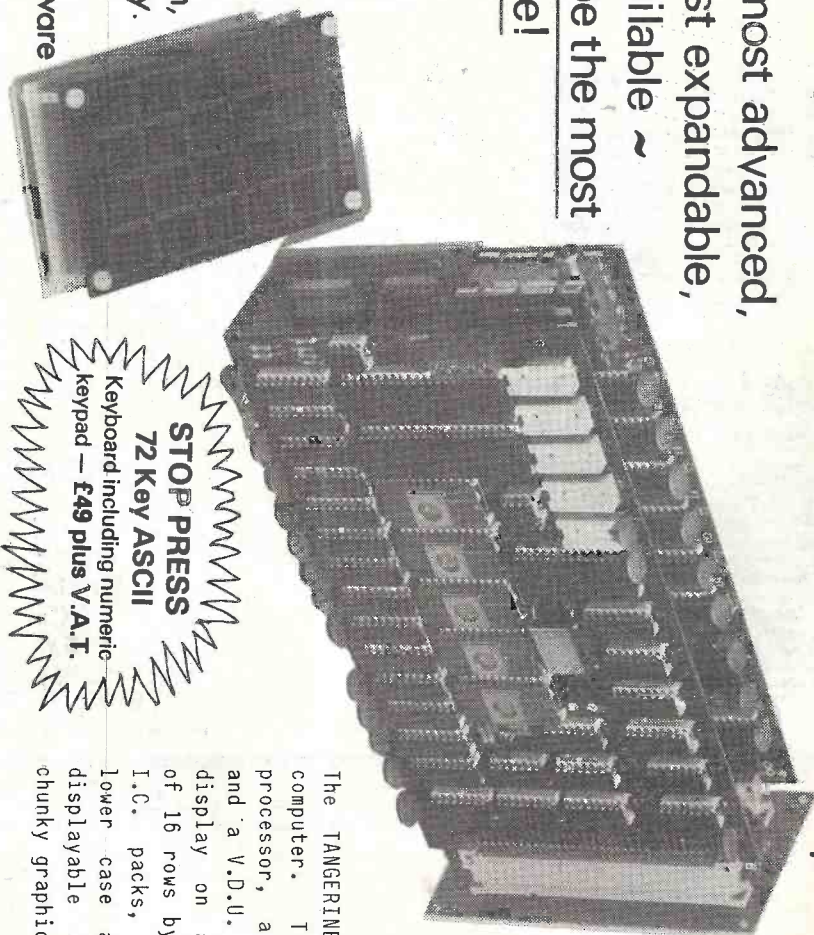

STOP PRESS
72 Key ASCII
Keyboard including numeric keypad — £49 plus V.A.T.

The TANGERINE MICROTAN 65 is a 6502 based micro-computer. The MICROTAN 65 includes a 6502 micro-processor, a superb 1K monitor TANBUG, 1K RAM, and a V.D.U. section which produces an alphanumeric display on an unmodified domestic T.V. receiver of 16 rows by 32 characters. There are two optional I.C. packs, one provides the MICROTAN 65 with lower case alphanumerics (making a total of 128 displayable characters) and the other providing chunky graphics (64x64 pixels).

from

£69
plus VAT

Available as a kit,
or assembled and tested.

For comprehensive information, price list and details of all MICROTAN products, send coupon & 12p stamp without delay.

Name
Address

FOREHILL, ELY, CAMBS.
TEL. (0353)3633


TANGERINE
COMPUTER SYSTEMS LIMITED

BEWARE! RADIO ACTIVITY



The new MK III FM tuner sitting under the Dorchester multiband AM/FM tuner

Revisions to the Mark III include a centre zero tuning indicator meter and silent preset switching

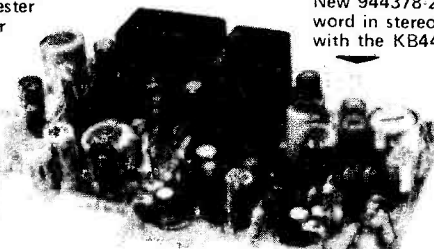

New 944378-2, the last word in stereo decoders with the KB4437/4438.

Choosing the products to advertise each month can be quite a task at AMBIT, since we tend to introduce at least one new line per week. So it is nearly impossible to say all we would like in this space - other than to bring you as far up to date as possible with current events. The major medium for finding out about what we have to offer is our unique catalogue system, and we ask that you invest in a copy of parts 1, 2 & 3 since many questions we are asked can be readily answered by reference to these.

Each part costs 60p, or £1.60 for all three current editions. We are also launching a new and greatly elongated version of our PRICE LIST, which now includes a large number of quantity listings, and many items not previously listed. The new style price list is a quick reference short form to our general catalogues - available FOC with a large (A4) SAE please.

As a result of the soaring price of oil - and the subsequent huge increases in the cost of wax for Mr Tom Jackson's famous moustache, the Post Office have increased their charges (Feb. 4th). Accordingly, our standard cover charge has been increased to 35p per order (CWO).

COMPONENTS

DIGITAL FREQUENCY READOUTS / SYNTHESISER SYSTEMS

Ambit has the biggest range of digital frequency readout systems for various applications in Broadcast and Communications. Prices range from £18.50 for a complete AM/FM broadcast frequency display (kit of DFM2). Most are detailed in the latest catalogue.

TUNING SYNTHESIZERS are also heavily featured, and we offer our first complete system covering MW/ LW/ SW2 and FM based on Hitachi parts. The unit is retrofittable to voltage tuned radio systems - and will shortly be incorporated in a complete tuner project. Cost for the synthesiser will be circa £40. A versatile communications system based on the new Mullard 2 IC system is nearing completion, together with 16 station CMOS memory and optical shaft encoder system with fast tune facility. Synthesiser circa £70, memory £50.

Latest semiconductor news:

CMOS, TTL and LPSN TTL are in stock (ask for our OSTs price leaflet). Some of the very popular types are still "difficult" but we have things like 4011s, 4017s at the time of writing.

RADIO ICs - interesting developments here, we now have the Hitachi HA11225 and the HA12412 ultra high specification members of the CA3089E family. The PLESSEY SL1600 range now includes the SL6600 high performance PLL NBFM IF and detector.

CA3089E	2.11	HA1197	1.61	SD6000	4.31	SL1610	1.84	SL1626	2.80
CA3189E	2.53	CA3123E	1.61	TDA4420	2.59	SL1611	1.84	SL1630	1.86
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38	SL1612	1.84	SL1640	2.17
HA11225	2.47	TBA651	2.53	MC1350P	1.38	SL1613	2.17	SL1641	2.17
HA12412	2.81	TDA1090	3.51	KB4412	2.24	SL1620	2.50	SL6600	4.31
KB4420	1.95	TDA1220	1.61	KB4413	2.24	SL1623	2.80	SL6640	3.16
TBA1206	1.15	TDA1083	2.24	KB4417	2.53	SL1624	3.77	SL6690	3.68
KB4406	0.80	TDA1062	2.24	MC3357P	3.16	SL1625	2.50	MC1496	1.44

TRANSISTORS: New lower prices, wider range, large stocks. Also the world's lowest noise audio devices (2SC2546E and 2SA1084E) first from AMBIT of course. Power MOSFETs & all sorts of other devices. Our 3SK51 MOSFET replaces the 408XX and 40673 families.

BC237-8-9	0.092	2SC1775	0.207	2SA1084E	0.368	BF256	0.437	BFY90	1.03
BC307-8-9	0.092	2SA872A	0.207	2SC2547E	0.391	2SK55	0.368	BF224	0.263
BC413-5	0.115	2SD666A	0.345	2SA1085E	0.391	2SK168	0.402	BF274	0.207
BD414-6	0.126	2SB646A	0.345	2SK133	6.32	3SK51	0.62	BFT95	1.138
BC546-556	0.138	2SD760	0.52	2SJ48	6.32	3SK60	0.667	VN66AF	1.092
BC550-560	0.138	2SB720	0.52	2SK135	7.29	BF960	1.426	2N4427	0.977
BC639-640	0.265	2SC2546E	0.368	2SJ50	7.29	3SK48	1.426	J176	0.747

RADIO CONTROL: A special section for all RC fans. New and exciting stuff:

KB4445/KB4446: complete 4 channel RX/TX dig.prop IC pair RF&control in one 4.75p
MSL9362/MSL9363: logic section of a four channel dig.prop link, with switch opt. 3.75p
NE5044: Signetics versatile 7 channel encoder, suitable for mixing etc. £2.14 ea
NE544 Signetics famous servo driver IC £2.07 MC3357P as used in RCME design £3.16 ea
AMBIT RCX4: RCME FM system compatible, complete RX kit with box, connector and AMBIT design screened front end with 27MHz ceramic filter £16.10 (kit)
XTALS: FM pairs £3.74 (no splits) TX is fund. 1/2 op frequency, RX 3rd OT 455kHz
AM pairs £3.57 (no splits). Both 3rd OT types, again RX IF at 455kHz

MODULE NEWS

We are at last able to quote for quantities of our modules, following a program of standardization and revision to speed manufacture and test. The following types are the results of the standardization program:

UM1181	5 varicap MOSFET input VHF band 2 tunerhead	£12.00 inc
911225 A	High Performance FM IF system, with switched BW	£23.95 inc
911225 B	Single BW filters, single tuned detector	£14.95 inc
91072 A	DC tuned and single pole switched MW LW tuner	£14.43 inc
91072 B	As type 'A' but with either SW1 or SW2 band	£15.90 inc
92242 A	Combined LW/MW tuner, with FM IF detector section	£29.00 inc
92242 B	As 92242A but with 5-10MHz SW section	£34.00 inc

All are supplied housed in screened metal cases 97x56x24mm, with all connections along a single edge, suitable for verticle or horizontal mounting.

Previously advertized units are still available - although there may have been some price changes in the latest edition of the Price List (Date Feb.80). A separate leaflet covering the new range of modules is available from April 80, with an A4 SAE please.

NEW LINE: ALPS switches and rotary potentiometers. With a general catalogue that's over 3 inches thick, we cannot begin to offer a comprehensive list of what we can offer - but we are already stocking the keyboard switches, keyswitches, pushbutton switches etc. In particular, the pushbutton switches really put all others in the shade (shadow?) when it comes to quality and price. A special new shortform is being prepared (and may be ready when you read this). All the potentiometers and switches you could ever need from a single source. Keypad switches cost as little as 15p ea (1 off), with a range of two part caps for easy legending. You must see the shortform catalogue (30p) and our new pricelist for full details of this huge range of components



AMBIT SHOP NOW OPEN

We are gradually getting our caller sales area sorted out, with displays of the products on offer and a browsers corner to sit and study data/catalogues. Call in next time you are in the area - parking outside the door.

Keyboard switch SCK41505 typ 6m ops 23p each (1-24)

COMPUTER CAPABILITIES

Ambit has been keeping a low profile on the subject of the MPU and its applications. Interestingly enough, the first project we offer with MPU content does rather more in the way of processing than simply playing a daft game, or looking like an enormous calculator. Our MPU facility and expertise is now for hire on a fully commercial basis. Z80, 6800, 6809, 2650 etc.



NEW LINE: DC/DC+AC converters for fluorescent displays TOKO CPS series 12v 1N, -20 and 3v AC out at 65mA. Thick film design £2.34 ea Qty. prices OA

GENERAL INFORMATION

Ambit stocks the following ranges of components for ex-stock volume delivery: SIGNAL COILS, CERAMIC, MECHANICAL and CRYSTAL FILTERS, RADIO ICs for AM/FM/SSB, TOROID CORES FOR RADIO and EMI FILTER CIRCUITS, INDICATING and PANEL METERS, AUDIO ICs, RF TRANSISTORS, PETS, MOSFETS, DIODES (PIN, VARICAP, SCHOTTKY), PASSIVE DBMs (like M0108 etc), IC SOCKETS, LEDs, TRIMMER CAPS, SWITCHES, KEYBOARD SWITCHES, TUNERHEADS, IF AMPS, AM RADIO MODULES, etc etc

NEW LINE: DVM176 - the definitive ICM7106 LCD DVM module. 3 1/2 digit £22.37 ea.

CM161: LCD 12/24hr alarm clock/day/date/backlight (eq. RS308-499) 7mm digits £11.44 each
CM174: LCD 12hr alarm clock/stopwatch/backlight with 30mm height digits £14.32 each

CATALOGUES 60p ea., all three for £1.60
PRICES SHOWN HERE INCLUDE VAT
POST/PACKAGE CHARGE NOW 35p

ambit
INTERNATIONAL

CWO PLEASE: Commercial MA terms on application
Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

— 111 —

WATFORD ELECTRONICS

THE DIGITAL FREQUENCY METER with a Difference



All these features and more for less than half the price of an ordinary frequency meter. The DFM2000 has all its components including the displays, switches and transformer mounted on one double sided PC board. Assembly is simplicity itself especially since interwiring has been eliminated. This is a high quality design and will make a truly professional digital frequency meter that any constructor will be proud to own.

Price: Only £64.50 Kit (P&P 65p). Probes: Optional extra £8.75

Full ASCII Coded 56 Key Keyboard Type 756 Only £39.95+ (incl. data)	SWITCHES Push-button SRL DPDT Latching SRM DPDT Momentary	125 125	SWITCHES TOGGLE: 2A, 250V SPST 28p DPST 34p DPDT 38p 4 pole on/off 54p	SLIDE 250V: 1A DPDT 14p 1A DPDT c/over 15p 1/2A DPDT 13p 4 pole 2 way 24p
4x4" Keypad 18 Keys. Read switches. Extremely reliable. Only 450p.	DIL SWITCHES 4-way SPST 6-way SPST 8-way SPST	110 120 145	SUB-MIN TOGGLE SP changeover 59p SPST on/off 54p SPST biased 85p DPDT 6 tags 70p DPDT centre off 79p DPDT Biased 115p	PUSH BUTTON Spring loaded SPST on/off 60p SPDT c/over 65p DPDT 6 Tag 85p
ASTEC RF Modulators	RELAYS RL6 SPCO RL6B DPCO	250 175 215	ROTARY: Make your own multiway Switch. Adjustable Stop Shifting Assembly. Accommodate up to 6 Waters 40p Mains Switch DPST to fit 40p Break Before Make Waters. 1 pole/12 way 2p/6 way. 3p/4 way. 4p/3 way. 6p/2 way 56p Spacer and Screen 6p	MINI. Non Locking Push to Make 15p Push Break 25p Push to c/over 85p

CRYSTALS 500KHz 323 455KHz 383 1MHz 323 1.008M 395 1.28MHz 323 1.6MHz 323 1.8MHz 323 1.8432MHz 362 2.4576MHz 362 3.2768MHz 323 3.57954MHz 195 4.000MHz 290 4.032MHz 323 4.433619M 136 5.0MHz 355 5.185M 323 6.5536M 200 7.680M 323 8.86723M 323 9.375M 323 10.0MHz 323 10.7MHz 323 12MHz 392 14.3181MHz 300 18MHz 323 18.432M 323 20.0MHz 323 27.648M 323 48.0MHz 323 100.00MHz 323	TRANSFORMERS (Mains Prim. 220-240V) 6-0.8V, 9-0.9V, 12-0.12V 100mA 95p 3VA: 0-6V 0.6V (PCB mounting) 150p 8VA: 6V, 5A, 6V, 5A, 9V, 4A, 9V, 4A, 12V, 3A 215p 12V, 3A: 15V, 25A 15V, 25A 215p 12V, 4.5V, 1.3A 4.5V, 1.3A, 6V, 1.2A 6V, 1.2A 235p (20p p&p) 24VA: 6V, 1.5A 6V, 1.5A, 9V, 1.3A 9V, 1.3A 320p (45p p&p) 12V, 1A 12V, 1A, 15V, 8A 15V, 8A, 20V, 6A 320p (45p p&p) 20V, 6A 320p (45p p&p) 50VA: 6V, 4A 6V, 4A, 9V, 2.5A 9V, 2.5A, 12V, 2A 12V, 2A, 15V, 1.5A 15V, 1.5A, 20V, 1.2A 20V, 1.2A, 25V, 1A 25V, 1A, 30V, 8A 30V, 8A 365p (50p p&p) 100VA: 12V, 4A 12V, 4A, 15V, 3A 15V, 3A, 20V, 2.5A 20V, 2.5A, 30V, 1.5A 30V, 1.5A, 40V, 1.25A 40V, 1.25A, 50V, 1A 50V, 1A 695p (60p p&p). (N.B. p&p charge to be added above our normal postal charge.)	ALUM. BOXES WITH LID 3x2x1" 54p 2x4x5x1 1/2" 72p 4x4x1 1/2" 72p 4x2x4x1 1/2" 70p 4x5x4x1 1/2" 88p 4x2x2x2" 98p 5x4x2" 108p 6x4x2" 145p 7x5x2 1/2" 185p 8x6x3" 210p 10x4x4x3" 175p 12x5x3" 215p 12x8x3" 265p	PANEL METERS FSD 50x46x35mm 0-50uA 0-100uA 0-500uA 0-1mA 0-5mA 0-10mA 0-50mA 0-100mA 0-500mA 0-1A 0-2A 0-25V 0-50V AC 0-300V AC "S" "VU" 445p each 4 1/2x3 1/2x1 1/2" 0-100uA 0-500uA 595p each
--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

ETI Projects: Parts available for: Click Eliminator DFM2000 Frequency Meter, DM900, Audiophile Amp, 60W Amplifier System. Send SAE plus 5p for list.	VOLTAGE REGULATORS 1A TO3 +ve -ve 5V 7805 145p 7905 220p 12V 7812 145p 7912 220p 15V 7815 145p 18V 7818 145p 1A TO220 Plastic Casing 5V 7805 65p 7905 75p 12V 7812 65p 7912 75p 15V 7815 65p 7915 75p 18V 7818 65p 7918 75p 24V 7824 65p 100mA TO92 Plastic Casing 5V 78L05 30p 79L05 65p 6V 78L62 30p 8V 78L82 30p 12V 78L12 30p 79L12 65p 15V 78L15 30p 79L15 65p LM300H 170p LM327 270p LM305H 140p LM723 38p LM309K 135p TAA550 50p LM317K 35p TBA625B 95p LM323K 550p TDA1412 150p LM325N 240p 78H05 +5/5A 550p LM326N 240p	OPTO LEDs with Clips TIL209 Red 13 TIL211 Grn. 17 TIL212 Yel. 18 TIL220 2" Red 14 2" Green, Yellow or Amber 18 Square LEDs, Red, Green, Yellow 36 LD271 Infra Red 40 SFH205 Detector 90 TIL32 Infra Red 58 TIL78 Detector 70 BARGRAPH, Red 10 segments 225 LS400 255 OC71 121 ORP12 63 ORP61 85 2N5777 45 ISOLATORS IL74 48 TIL111/2 85 TIL114 95 TIL117 110 Bargraph 225	7 Segment Displays TIL307 675 TIL312 3" CC 105 TIL313 3" CC 105 TIL321 5" CC 115 TIL322 5" CC 115 DL704 3" CC 99 DL707 3" CC 99 DL747 5" CA 180 FND357 Red 120 3" Green CA 150 6" Green CA 215 LCD 3 1/2 Digit 875 LCD 4 Digit 975
-------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

LS299 420 LS300 175 LS302 175 LS320 270 LS323 450 LS324 200 LS325 320 LS326 300 LS327 315 LS346 185 LS347 150 LS348 180 LS352 185 LS353 185 LS355 65 LS356 65 LS367 65 LS368 65 LS373 180 LS374 180 LS375 150 LS377 199 LS378 185 LS379 215 LS384 50 LS386 420 LS386 85 LS390 140 LS393 140 LS395 210 LS396 199 LS398 275 LS399 230 LS445 140 LS447 195 LS490 150 LS668 105 LS669 105	LS670 270 LS673 75 LS674 850 CMOS* 4000 18 4001 18 4002 24 4005 92 4007 22 4008 82 4009 40 4010 48 4011 24 4012 24 4013 45 4014 85 4015 85 4016 82 4017 82 4018 88 4019 48 4020 99 4021 105 4022 96 4023 25 4024 75 4025 25 4026 180 4027 48 4028 82 4029 105 4030 60 4031 225 4032 125 4033 175 4034 210 4035 125	4036 365 4037 115 4038 118 4039 360 4040 105 4041 80 4042 80 4043 95 4044 95 4045 175 4046 130 4047 98 4048 95 4049 45 4050 48 4051 80 4052 80 4053 80 4054 130 4055 135 4056 135 4057 1900 4059 575 4060 130 4061 1225 4062 95 4063 120 4064 58 4067 430 4068 26 4069 25 4070 30 4071 25 4072 25 4073 25 4076 25 4077 48	4078 30 4079 88 4082 28 4085 90 4086 90 4089 150 4093 89 4094 240 4095 105 4096 105 4097 350 4098 115 4099 190 4100 125 4101 125 4102 125 4103 130 4104 125 4105 125 4106 125 4107 125 4305 125	4501 28 4502 125 4503 75 4504 75 4505 75 4506 75 4507 60 4508 325 4509 99 4510 99 4511 150 4512 95 4513 225 4514 265 4515 299 4516 120 4517 150 4518 105 4519 70 4520 115 4521 250 4522 150 4523 150 4524 150 4525 150 4526 120 4527 175 4528 120 4529 175 4530 89 4531 165 4532 140 4533 140 4534 575 4535 385 4536 130 4537 135 4538 135 4539 135 4540 135 4750 135	Full ASCII coded 56 Key Keyboard £42.50 4" x 4" Keypads £4.50 RF Modulators £2.50 Wideband Modulators £4.70 Sound Modulators £2.50
------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------

Make sure of your new Heathkit catalogue.. write now.



Keep up to date with the world's finest electronic kits—with the new Heathkit catalogue. 48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers. Heathkit make it easy to build, easy on your pocket, and, as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the new Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (E.T.5.), Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the new Heathkit catalogue. I enclose 25p in stamps.

Name _____

Address _____

E.T.5.

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.

HEATHKIT

DIGEST

Sony Screen Machine


One of the more significant product releases this month was the new Sony C7 video recorder. It has several features which mark it out as the best design yet for home usage. Although Sony themselves placed great emphasis upon the solenoid controls and IR Control System these will bring little more than a yawn to the lips of anyone with the faintest claim to technical knowledge.

Of far greater interest will be the superbly conceived set-up procedure (under MPU control) and the versatile times.

Tuning in most VCRs is both time consuming and patience destroying. The C7, once locked to the set with a panel control, will automatically search the band looking for stations and load any it finds into pre-set locations for easy user access.

(It's about time someone did something like this anyway).

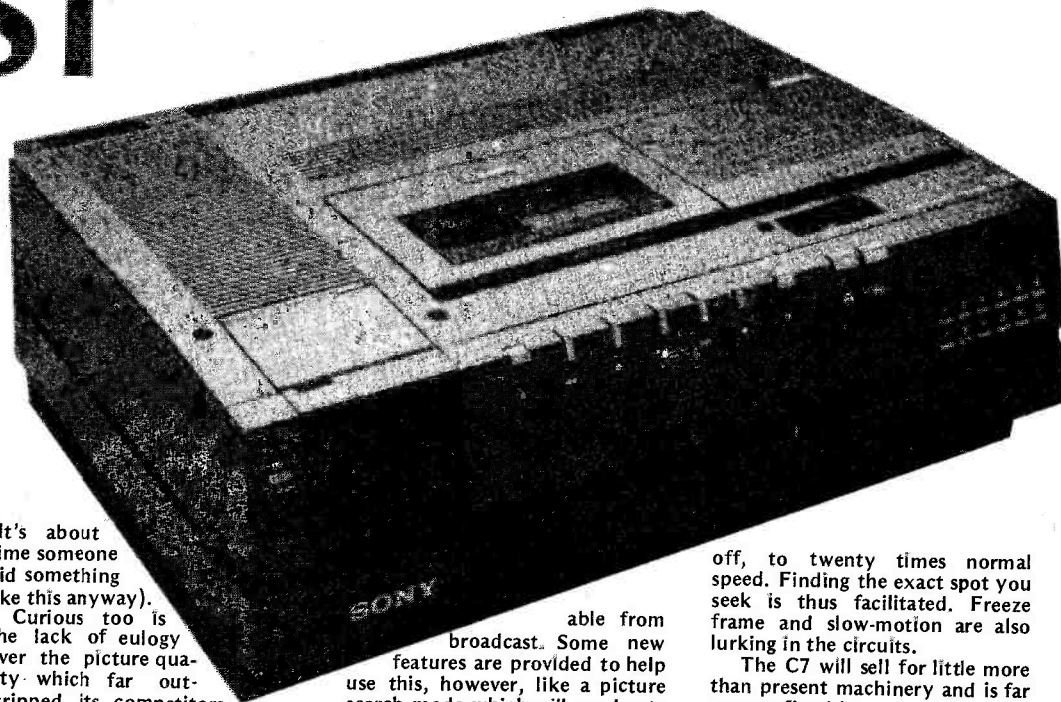
Curious too is the lack of eulogy over the picture quality which far outstripped its competitors, being all but indistinguish-



able from broadcast. Some new features are provided to help use this, however, like a picture search mode which will accelerate the tape, in vision with the sound

off, to twenty times normal speed. Finding the exact spot you seek is thus facilitated. Freeze frame and slow-motion are also lurking in the circuits.

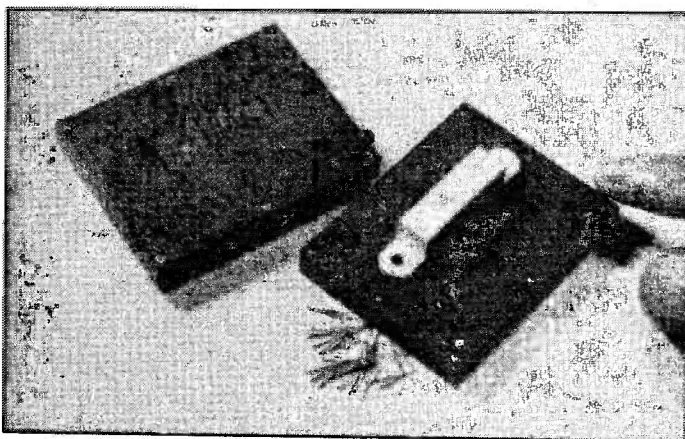The C7 will sell for little more than present machinery and is far more refined in several important areas. Should do well.



Universal Test Socket


FI have developed a new test socket called the Textool GRID ZIP. It can be either PCB mounted or fixed to front panels using mounting screws. The makers claim an operating life of greater than 25,000 insertions, and one economy feature is the ability to mount more than one device per socket plate, and spare plates can be supplied to increase the utility of the socket.

You can use this test socket with any standard or non-standard device if the leads fit within a 14 x 21 grid (on 0.1" lead centres). The socket consists of a top plate with guide indentations on a 0.1" grid, a camplate to provide the Zero Insertions

Pressure clamping operation and a base plate holding the plated beryllium copper contacts. So, once the top plate has been drilled to take the device leads, contacts are placed in the desired locations in the base plate and the cam assembly is dropped onto them. The resulting 'sandwich' is held together by eight screws running through the edges. In use this means that a device is simply dropped onto the pre-drilled holes and the clamping lever is flicked down to clamp the contacts onto the device leads, so no strain is put onto the device and good electrical contact is ensured, this in turn means extended contact life. Average contact resistance is less than 0.005 ohms. In a production situation, incorrect insertions are virtually eliminated as there is only one set of socket holes.

Micro-Data Systems' 3 digit panel meter combines economy with high performance. Accuracy is 0.05% with resolution to 100 μ V and the scale allows four digit resolution of quantities up to 4,000, rather than the 2,000 to which other units are limited. A 5 volt supply is required. The naked PCB construction incorporates a red filter, enabling direct panel mounting without the need for a separate bezel. Prices are from £19.95 (one off) down to £14.95 each, if you can find a use for fifty of them.

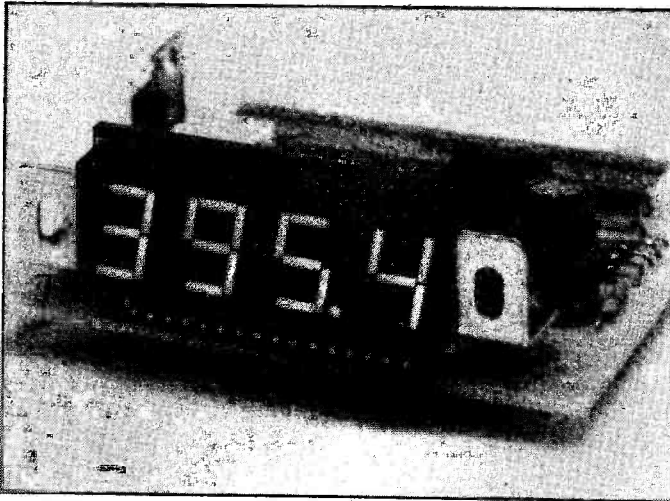Further details from Micro-Data Systems, Office Suite 1, Coach Mews, The Broadway, St. Ives, Huntingdon, Cambs PE17 4BN.



Technical Queries

We've had an impassioned plea from our automatic telephone answering machine (our receptionist) about an item which we published some time ago in Digest. Although we have suspended our telephone answering service for ETI technical queries, we are still receiving a number

of calls every day from readers asking for technical help. Our receptionist is unable to accept these calls.

Unfortunately we are unable to answer technical questions by telephone. If you are having problems with an ETI project, please write with full details and enclosing a stamped, addressed envelope.

CHROMATHEQUE 5000



Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

POWERTRAN 5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT

ONLY

£49.50 + VAT!



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in *Hi-Fi News* and *Record Review* and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc and full instructions — in fact everything! Matching TUNERS and CASSETTE DECK — see our free catalogue!

All kits also available as separate packs (eg PCB, component sets, hardware sets etc). Prices in our FREE CATALOGUE.



T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in *Practical Wireless*, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30W version of this kit (T30+30) is also available for **£38.40 + VAT**.

BLACK HOLE

THIS MONTH'S FRONT COVER FEATURE!

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a 'spacey' feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity input, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY **£49.80 + VAT** (single delay line system)

De Luxe version (dual delay line system) also available for **£59.80 + VAT**

MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

Featured as a constructional article in *ETI*, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.



Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT
ONLY

£49.90 + VAT!

MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until July 31st, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.

U.K. ORDERS: Subject to 15%* surcharge for VAT. No charge is made for carriage, *or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter, Open 9 a.m.-12 noon, 1-4.30 p.m. Monday-Thursday.

NEW FACTORY ON SAME INDUSTRIAL ESTATE
ADDRESS AND PHONE NUMBER UNCHANGED

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

Your Commodore PET System

The Commodore PET is Britain's best selling microcomputer and the most popular choice in every field:-

* In Education for teaching Computer Science and as a teaching aid for other subjects.

* In Science and Engineering for solving problems and for monitoring laboratory equipment.

* In Business the PET system can be put to a wide range of functions including Payroll, Accounting, Statistical Analysis, Stock Control and Word Processing.

A SELF-CONTAINED MICRO-COMPUTER FROM £550.



Not least of its attractions is the price of a PET - from £550 for a self contained unit, to under £2,500 for the complete system including Floppy Disk Unit and high-speed Printer. Ask your nearest Commodore dealer below for details about Commodore hardware, software and training courses.

Our Dealer* Network

LONDON

Capital Computer Systems,
W1. 637 5551
ACE (by Top TV Ltd), SW1. 730 1795
Micro Computer Centre,
SW14. 876 6609
Logic Box Ltd, SW1. 222 1122
Sumlock Bandain Ltd, EC1. 250 0505
Da Vinci Computers Ltd,
NW4. 202 9630
L & J Computers, NW9. 204 7525
Adda Computers, W1. 408 1611
CSS Business Equipment Ltd,
E8. 254 9293
Advanced Management, EC2. 638 9319
Metyclean Ltd, SW1. 828 2511
Microcomputation,
Southgate. 882 5104
T.L.C. World Trading Ltd, WC2. 839 3894

HOME COUNTIES

Orchard Electronics Ltd,
OXON. 0491 35529
D. L. Chittenden Ltd, CHESHAM. 4441
J. R. Ward Computers Ltd,
MILTON KEYNES. 562850
Dataview Ltd, COLCHESTER. 78811
South East Computers Ltd,
HASTINGS. 426844
Symtec Systems Ltd,
SOUTHAMPTON. 38868
Alphascan Ltd, BANBURY. 75606
Super-vision, SOUTHAMPTON. 774023
Millhouse Designs Ltd,
ALTON. (042) 050374
Micro Facilities Ltd, MIDDX. 979 4546
DDM, BRENTWOOD. 230480
Stuart R. Dean Ltd, SOUTHEND. 62707
Alpha Business Systems,
HERTFORD. 57423
HSV Microcomputers,
BASINGSTOKE. 62444
HSV Microcomputers,
SOUTHAMPTON. 22131
RUF Computers (UK),
BURGESS HILL. 45211
Wego Computers Ltd,
CATERHAM. 49235

T. & V. Johnson, CAMBERLEY. 62506
T. & V. Johnson, OXFORD. 721461
Petalect Electronic Services Ltd,
WOKING. 23637/21776

Business Electronics,
SOUTHAMPTON. 738248
Amplicon Micro Systems Ltd,
BRIGHTON. 562163
Bromwall Data Services Ltd,
HATFIELD. 60980/64840
MMS Computer Systems,
BEDFORD. 40601
Isher-Woods, LUTON. 416202
Sumlock Bandain, NORWICH. 26259
CSE (Computers), READING. 61492
Oxford Computer Systems,
WOODSTOCK. 811976

MIDLANDS & STH. HUMBERSIDE

Taylor Wilson Systems Ltd,
KNOWLE. 6192
Betos (Systems) Ltd,
NOTTINGHAM. 48108
Holbrook Business Systems,
DERBY. 368088
Lowe Electronics Limited,
MATLOCK. 2817
Davidson-Richards Ltd,
DERBY. 366803/4
Ardent Data Processing,
LEICESTER. 22255
Tekdata Ltd, STOKE-ON-TRENT. 813631
C.S.M. Computer Systems,
BIRMINGHAM. 360 6264

Business & Leisure Microcomputers,
KENILWORTH. 512127
Caddis Computer Systems Ltd,
HINCKLEY. 613544
Allen Computers, GRIMSBY. 40568
CPS (Data Systems) Ltd,
BIRMINGHAM. 707 3866
Camden Electronics,
BIRMINGHAM. 773 8240
Cliffstock (Computer Systems) Ltd,
WOLVERHAMPTON. 24221

YORKSHIRE & NTH. HUMBERSIDE

Microprocessor Services,
HULL. 0482 23146
Microware Computers, HULL. 562107
Computer Workshop, LEEDS. 788466
Hallam Computer Systems Ltd,
SHEFFIELD. 663125
Ackroyd Typewriters Ltd,
BRADFORD. 31835
Oatron Micro Centre,
SHEFFIELD. 585490
Yorkshire Electronics Service Ltd,
MORLEY. 522181
Sheffield Computer Centre,
SHEFFIELD. 53519

NORTH EAST

Dyson Instruments, DURHAM. 66937
Currie & Maughan,
GATESHEAD. 774540
Wards Office Supplies,
GATESHEAD. 605915

Tripoint Associated Systems,
SUNDERLAND. 73310
Newcastle Computer Services,
NEWCASTLE UPON TYNE,
[0632] 615325

SOUTH WALES & WEST COUNTRY

Computer and Design,
BROADSTONE. 0202 697341
A. C. Systems, EXETER. 71718
Computer Supplies (Swansea),
SWANSEA. 290047
Sigma Systems Ltd, CARDIFF. 21515
Devon Computers, PAIGNTON. 526303
Bristol Computer Centre,
BRISTOL. 23430
J. A. D. Integrated Services,
PLYMOUTH. 62616
Sumlock Tabdown Ltd, BRISTOL. 26685
Radan Computational Ltd,
BATH. 318483
T. & V. Johnson Ltd, BRISTOL. 422061

NORTH WEST & NORTH WALES

B. & B. Computers Ltd, BOLTON. 26644
Megapalm Ltd, CARNFORTH. 3801
Tharstern Ltd, BURNLEY. 38481
Fylde Business Machines Ltd,
PRESTON. 731901
Preston Computer Centre,
PRESTON. 57684
RPL Microsystems, DOUGLAS. 4247/8

LIVERPOOL

Microdigital, LIVERPOOL. 227 2535
Rockliff Brothers Ltd,
LIVERPOOL. 521 5830

MANCHESTER

Cytek (UK) Ltd,
MANCHESTER. 832 7604
Executive Reprographic Ltd,
MANCHESTER. 2281637
Sumlock Manchester Ltd,
DEANS GATE. (0618) 834 4233
Computer Workshop,
MANCHESTER. 832 2269
Professional Computer Services Ltd,
OLDHAM. 061-624 4065
D. Kipping Ltd, SALFORD. 834 6367
Catlands Computers Ltd,
WILMSLOW. 527166

SCOTLAND

Microcentre, EDINBURGH. 225 2022
Thistle Computers, KIRK WALL. 3140
McAllister Business Equipment,
EDINBURGH. 336 2402

IRELAND

Softech Ltd, DUBLIN. 784739
Medical and Scientific,
LISBURN. 77533

*This is a list of dealers participating in associated advertising and not a full list.

commodore
We made small computers big business.

Commodore Information Centre, 360 Euston Road, NW1 3BL. 01-388 5702

ETI MAY 1980

ion of Ford motor cars and integrated circuit production. The graphs clearly show that production costs are related to the accumulated experience. I would imagine this can be repeated using a host of other products, washing machines for example, which offer a similar picture.

Making Bubbles

The accumulated expertise of chip manufacturers has been most significant in solid state memories with the rapid development of random-access and read only memories, charged-coupled devices and magnetic-bubble memories. Storage capacities of memory devices will continue to increase through 1980. However, an end is in sight to the straight-line growth curve of semiconductor memory densities. Instead of memory capacity doubling every two years this will stretch out to three and four years now that the limits of optical lithography are under pressure.

One of the most exciting developments which has been progressing quietly during the past few years is bubble memories. Already announcements are being made of quarter-million-bit bubble memories which could be followed by a megabit device this year and then a 4 megabit memory in the mid 1980's. Bubbles will soon begin to encroach on markets now dominated by the other technologies. With the larger storage densities and the non-volatile memory, this means data can be retrieved even after power loss. Bubble memories occupy less space than either semiconductor memories or floppy discs for the same storage capacity. Access times are in milliseconds which is comparable to other magnetic storage devices but very much slower than semiconductor memories.

At present bubble devices cannot provide portable storage which means a chip cannot be removed and filed away then later plugged into another system. With present costs and performance characteristics, magnetic bubbles seem to pose the biggest threat to storage systems between 300,000 and 3 million bits of data storage. They will threaten the lower end of the tape cassette, floppy disc and fixed-head disc markets. The fabrication and operation of bubble devices was for a long time quite a mystery to me which has prompted me to write about them. It is almost as difficult to accept as the holes theory was when learning about transistors.

Most magnetic bubble memories use a magnetic garnet crystal grown on a non-magnetic substrate. When no magnetic field is applied to the magnetic garnet film, domains in the thin film form serpentine patterns of upward (positive) and downward (negative) magnetization. It is possible to actually see the magnetic patterns using red light and polarising microscope, which greatly simplifies development work. When a magnetic field is applied by sandwiching the chip between two permanent magnets, the magnetic bias expands domains in the bias direction and shrinks those polarised in the opposite direction. At a certain field strength, the serpentine patterns shrink to small cylindrical magnetic domains or 'bubbles'. Typical bubble diameters range from 2 to 30 micrometers determined by the material and the bias.

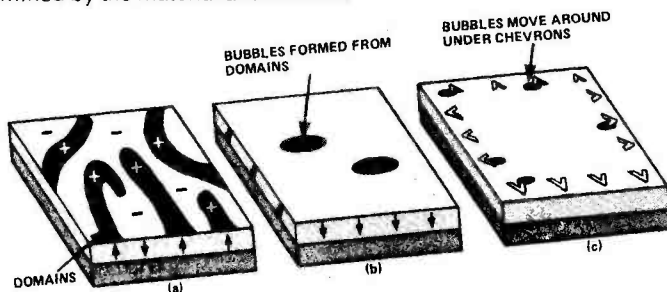


Fig.2(a). serpentine patterns occur naturally in the crystal.
(b) the bubbles form from domains when a bias is applied, from a permanent magnet.
(c) the bubbles move around under the chevrons when a rotating field is applied.

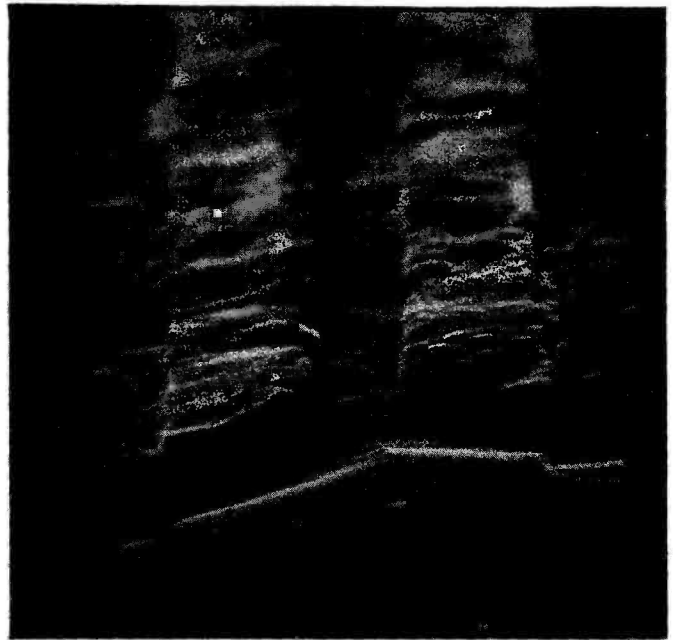


PHOTO 2 (top): the channel following metal deposition.

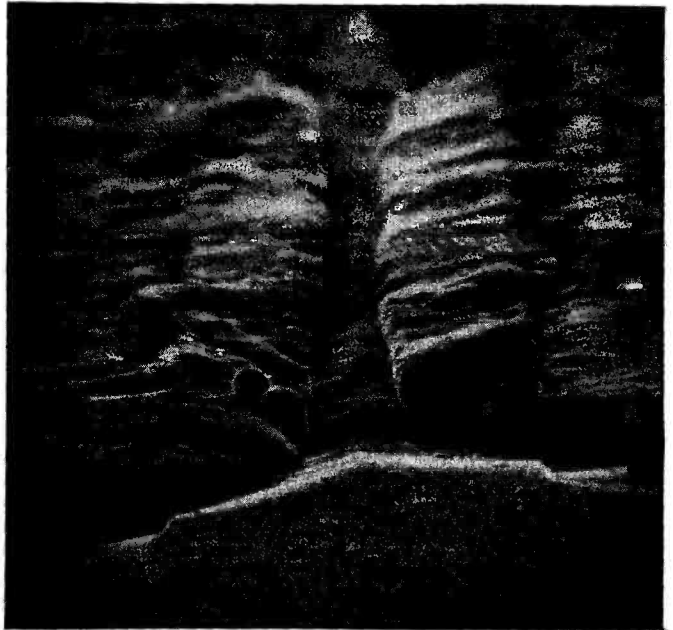


PHOTO 3 (above): breakdown! The overhang has collapsed.


In memory or logic devices the bubbles can be used to represent data, since the presence of a bubble can signify a binary 1 and the absence of a bubble can signify a binary 0. Bubbles can be generated by altering the bias field with a current pulse through a small conductive loop deposited on the chip. The current pulse produces a magnetic field opposite to that of a bias field thus producing a new bubble. Conversely, bubbles can be annihilated by applying a local field in a direction aiding the bias field. New techniques in magnetic bubble technology will eliminate the bulky field coils and permalloy layer by using a pair of conducting layers instead of magnets to move the bubbles. These and other improvements will further reduce the size, weight and manufacturing cost of bubble memories and will also speed data flow and increase bit densities.

ETI

TRANAM

COMPONENTS AND SYSTEMS FROM TRANAM COMPUTERS

•CP/M
•BASIC
•PASCAL

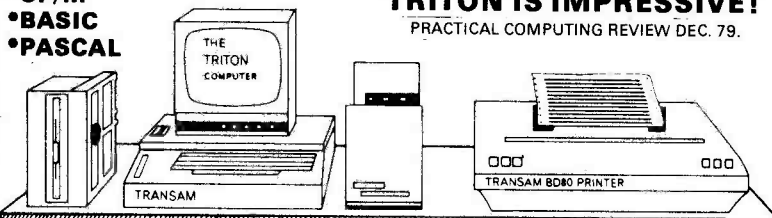

TRITON IS IMPRESSIVE!
PRACTICAL COMPUTING REVIEW DEC. 79.

TRITON COMPUTER SYSTEM.

Designed for ease of construction and flexibility. Kits come complete and all components and software are available separately. UK designed and supported. Fully documented hardware and software and a totally flexible approach to system building. Powerful and easy to use system monitors - a range of languages available. Firmware is Eeprom based and upgrading from one level to the next is easy.

- L5.2 with 1.5k monitor 2k basic £294
- L7.2 with 2k monitor 8k extended basic £409
- L8.2 4k ed/monitor 20k res Pascal £611
- L9.2 CP/M disc based system p.o.a.
- 8k Ram Card Kit (2114 1) £97
- 8k Eprom Cards (Excl 8x2708) £31
- Motherboard Expansion 8 slot £50
- Trap-Res Assm/ Edit etc (8x2708) £80
- Transam BD80 81-Dir Printer £595
- TVMIO Video Monitor 9" £79
- Eprom Prog (2708) kit £29.50

SEND FOR OUR CATALOGUE FOR FULL DETAILS OF TRITON FEATURES!

CP/M AVAILABLE NOW FOR TRITON

Disc operating system complete with text editor, assembler, debugger, system utilities and complete file management. Makes Triton fully CP/M compatible and able to run CP/M based software. Triton will support up to four 5 1/4 or 8" drives single or double density full CP/M software user group facilities available. SAE for details. CP/M Disk + manuals (8) £75.00

DISK DRIVES & POWER SUPPLIES

SHUGART



SA400 5 1/4" drive	£205.00
SA800 8" drive	£380.00
Power one quality power supplies	
CP249 1x5 1/4 PSU	£33.00
CP323 2x5 1/4 PSU	£60.00
CP205 1x8" PSU	£58.00
CP206 2x8" PSU	£76.00

TCL PASCAL CP/M COMPATIBLE


A standard Pascal compiler available on a resident (20k) Eprom based configuration" or available to run under CP/M on 8" disc plus documentation. CP/M version £120. *P.O.A. TCL Pascal Manual and specification £6.50.

DIL PLUG SOCKETS & SWITCHES

W/WRAP SKTS	DIL SKTS	DIL PLUGS	DIL SWITCHES
8DIL 0.20	8DIL 0.15	14DIL 0.80	40DIL 1.20
14DIL 0.35	14DIL 0.15	18DIL 0.85	70DIL 1.75
16DIL 0.42	16DIL 0.17	SCOTCHFLEX 8DIL	1.80
18DIL 0.50	18DIL 0.24	14DIL 1.30	18wZIF* 4.85
24DIL 0.52	20DIL 0.27	16DIL 1.50	24wZIF* 6.20
28DIL 0.74	24DIL 0.30	24DIL 2.80	
40DIL 0.95	28DIL 0.36	48DIL 0.50	

ZERO INSERTION FORCE

DOUBLE DENSITY \$100 DISK CONTROLLER

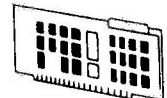

Suitable for Triton, DPS-1, etc. Built and tested Will drive Shugart compatible 8" or 5 1/4". Drives single or double sided. Uses the 1791 chip and CPU independent crystal.


Manual 50p + SAE. BOARD £195.00 + V.A.T.

FULL RANGE OF MICRO SUPPORT CHIPS - IN STOCK

CHIP	PRICE	CHIP	PRICE	CHIP	PRICE	CHIP	PRICE
SN74LS00N	22	SN74LS54N	21	SN74LS138N	96	SN74LS195AN	85
SN74LS01N	22	SN74LS55N	21	SN74LS139N	96	SN74LS196N	120
SN74LS02N	26	SN74LS563N	150	SN74LS145N	120	SN74LS227N	255
SN74LS03N	26	SN74LS573N	35	SN74LS148N	175	SN74LS221N	125
SN74LS04N	26	SN74LS574N	40	SN74LS151N	85	SN74LS240N	220
SN74LS05N	26	SN74LS576N	46	SN74LS153N	90	SN74LS241N	190
SN74LS08N	20	SN74LS578N	35	SN74LS154N	180	SN74LS242N	190
SN74LS09N	22	SN74LS579N	35	SN74LS155N	125	SN74LS243N	195
SN74LS10N	18	SN74LS583AN	115	SN74LS156N	125	SN74LS244N	210
SN74LS11N	28	SN74LS585N	110	SN74LS157N	60	SN74LS245N	360
SN74LS12N	28	SN74LS586N	40	SN74LS158N	80	SN74LS247N	125
SN74LS13N	65	SN74LS590N	65	SN74LS160N	115	SN74LS248N	195
SN74LS14N	60	SN74LS591N	90	SN74LS161N	115	SN74LS249N	130
SN74LS15N	25	SN74LS592N	90	SN74LS162N	115	SN74LS251N	145
SN74LS20N	20	SN74LS593BN	65	SN74LS163N	90	SN74LS253N	125
SN74LS21N	28	SN74LS594N	120	SN74LS164N	190	SN74LS257N	140
SN74LS22N	28	SN74LS596N	175	SN74LS165N	175	SN74LS258N	95
SN74LS25N	30	SN74LS107N	38	SN74LS166N	175	SN74LS259N	145
SN74LS27N	35	SN74LS109N	39	SN74LS168N	185	SN74LS260N	38
SN74LS28N	36	SN74LS112N	39	SN74LS169N	185	SN74LS261N	350
SN74LS30N	25	SN74LS114N	44	SN74LS170N	250	SN74LS266N	38
SN74LS32N	27	SN74LS114N	44	SN74LS173N	220	SN74LS273N	185
SN74LS33N	30	SN74LS123N	79	SN74LS174N	115	SN74LS275N	79
SN74LS37N	29	SN74LS123N	79	SN74LS175N	105	SN74LS280N	175
SN74LS38N	29	SN74LS124N	150	SN74LS181N	275	SN74LS283N	180
SN74LS40N	25	SN74LS125N	65	SN74LS180N	175	SN74LS280N	180
SN74LS42N	75	SN74LS126N	65	SN74LS181N	175	SN74LS283N	180
SN74LS47N	65	SN74LS127N	75	SN74LS182N	145	SN74LS285AN	220
SN74LS48N	85	SN74LS133N	39	SN74LS183N	175	SN74LS286N	220
SN74LS49N	100	SN74LS136N	40	SN74LS184AN	185	SN74LS287N	220

DPS.1 MAINFRAME - PASCAL SYSTEM

\$100 to IEEE spec

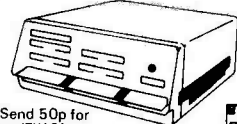

Send 50p for our ITHACA catalogue.



ITHACA

PASCAL /Z build your own Pascal Micro Development system. IEEE- S100 bus system using DPS1 mainframe. Supports K2 ASSEMBLE /Z and PASCAL /Z on 8" disk

Complete system £2910

\$100 BOARDS



8k Static RAM board (450ns)	£89.00
8k Static RAM board (250ns)	£117.00
280 cpu board (2MHz)	£105.00
280 cpu board (4MHz)	£123.00
2708 / 2716 EPROM board	£57.00
Prototype board (bare board)	£15.00
Video display board (64 x 16, 128U/L Ascii)	£108.75
Disc controller board	£131.25
K2 disc operating system	£45.00
ASSEMBLE /Z Macro Assm	£37.50
PASCAL /Z compiler	£205.00
PASCAL /Z CP/M	£235.00
16k Static RAM	£275.00


DOUBLE DENSITY CP/M NOW AVAILABLE - CONTACT US FOR DETAILS

VISIT OUR SHOWROOM

WE ALSO STOCK: - A comprehensive range of books and magazines. Vero products including S100 and Eurocard and Wire Wrap equipment, Weller soldering equipment, Ribbon cables, tools, tapes, diskettes, connectors and OK Tool range. Systems continuously on display in our showrooms.

CRYSTALS		4MHz	2.10	F8 (3850)	9.50
100k	3.00	4.43M	1.00	8080A	8.33
200k	3.70	5MHz	2.70	8809	24.00
1MHz	3.80	6MHz	2.70	Z80	8.00
1000k	3.60	7MHz	2.70	Z80A	15.00
1843k	3.00	7.168M	2.50	8085A	12.95
2MHz	1.50	8MHz	2.70	6502	8.00
2457k	3.05	10MHz	2.70	SCMP11	10.00
3276k	2.70	10.7M	2.70	6802	13.95



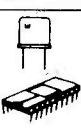


ALL PRICES

Exclude VAT & P/P
VAT 15% P. & P. 40p on small orders.
For larger items please Tel.
Telephone credit card orders
accepted subject to £5 min.
RAPID MAIL ORDER SERVICE



CATALOGUE

NEW A4 SIZED
ONLY 50p + S.A.E.

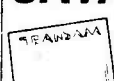

VISIT OUR SHOWROOM SOON
9.30-5.30 Mon-Fri
1.30-2.30 closed lunch
9.30-5.00 Sat
Thursday half day 1.30



TRANAM COMPONENTS LTD, 12 CHAPEL STREET, LONDON NW1

Tel: 01-402 8137 Telex: 444898

FROM CASIO—THE NEXT STEP FORWARD IN TIME

New Lithium batteries, lasting up to
5 years or more

CASIO F8C. Time in 6 digits, hrs, mins, secs, with date and day am/pm display. Three year battery.

CASIO 950336B. Time display in hrs, mins, secs with am/pm, day of week, calendar display year, month, date, day. Chronograph 1/100th sec lap and 1st, 2nd place times, to 7hrs. Dual time and 12-24hr display, auto calendar to 2029, 5 year battery.

LATEST MODELS. The 1980 models will now be available. Prices and details on application. Be sure you are buying latest model.



LCD PROGRAMMABLES



FX501P. Scientific 11 memories, 128 steps (RRP £64.95) **£52.95.**

FX502P. Scientific 22 memories, 256 steps (RRP £84.95) **£72.95.**

FA1. Adaptor for above (RRP £24.95) **£19.95** or just **£9.95** when you buy FX501P or FX502P at the same time. **SAVE £10 at least.**

CASIO POCKET/CLOCK CALCULATORS

PLB POCKET CALC. $+/-/ \times / \div$ memory $\sqrt{}$ % with constant and case **£9.45**

C082 desk calculator with clock and four alarms, slim style **£18.95**

A02000 calc with clock, 2 alarms, countdown alarm, calendar with memory, stopwatch, $+/-/ \times / \div \sqrt{}$ % keys M+ M-MRC **£23.95**

A02200 calc with clock alarm stopwatch, calendar display and full month display date calculations, $+/-/ \times / \div \sqrt{}$ % keys M+ M-MRC **£19.45**

A01500 8 digit calculator with clock, calendar, lap & 1st, 2nd place 1/10th sec stopwatch **£14.45**

ML71 musical calc, 11 tones clock calendar, stopwatch and alarms **£22.45**

ML720 calculator with 11 musical tones, $+/-/ \times / \div$ K with memory, card style **£14.45**

ML880. As above in leatherette case, 1500 hr battery life, 8 digits, slim **£14.45**

MQ6 mini-card size calc, watch calendar, stopwatch with case & chain for waistcoat **£19.45**

MQ12 slim card calc with watch, stopwatch, calendar, full month display and alarm **£19.45**

QL10 calc watch calendar date calculations, 2 alarms & countdown alarm & lighter **£39.95**

PW81 slim card calc with watch and calendar, smart case with window **£14.45**

NO21 hand held calculator with watch, latest model, $+/-/ \times / \div \sqrt{}$ % memory **£10.45**

ML81 slim calc/watch/calendar alarm 1 & 2 alarm countdown/stopwatch/time signal on the hour/3 programmed melodies/11 tones on keys, 8 digit calc **£22.45**

HR10 hand held or desk print and or display calculator with calendar key. Will print out any full month till 2099, $+/-/ \times / \div \sqrt{}$ % K and memory & sign change key **£29.45**

FX81 scientific, 37 functions, latest model, 8 digit up to 4000hr battery continuous **£12.45**

FX1000 new model, college, 39 scientific functions, 10 digit up to 7500 hrs battery continuous **£15.45**

FX2600 latest slim scientific 43 functions, 8 digit LCD display, auto power off **£18.95**

FX3200. As above with 43 functions, 10 digit RND / RAN / FIX / SCI / keys deg, rad, gra **£20.95**

FX7100 39 function 8 digit with clock alarm/timer alarm / stopwatch 1/100 sec to 10 hrs **£23.95**

FX68 slim 38 functions scientific parenthesis calculation to 6 levels, 8 digit **£18.95**

FX310 scientific 50 function 8 digit RND, RAN, Fix & SCI keys, 3 modes deg, rad, gra **£16.95**

FX510 scientific 50 function 10 digit as above 1000 hrs continuous use, auto cut off **£18.95**

FX330 scientific 43 function 8 digit latest model, 1100 hrs continuous use, slim style **£15.95**

All other Casio Calculators **P.O.A.**

SPECIAL OFFERS

LAMBDA latest model chronograph. Displays hour, minutes, seconds, month, date, day, Chronograph 1/100th sec. 1st, 2nd place times. Fully adjustable stainless steel strap, and case back with battery hatch. Slim style with night light, 1 year guarantee **£10.45**

SAXON ALARM CHRONOGRAPH Seiko style. Displays hours, minutes, seconds, am/pm and day indicator. Auto month, day, date 24-hour alarm setting. Chronograph in 1/10th sec. 1st, 2nd place times. 12 or 24 hour display. Nightlight. 1 year guarantee. **£15.45**


CASIO WATCHES & CALCULATORS. For full details please send 20p for watch or calculator details or both. Please state interest.

TERMS OF BUSINESS: Please note all above products include VAT, P&P and insurance. Please send cheque or PO made payable to B. Bamber Electronics or phone and use your Access or Barclaycard. Callers most welcome Tues-Sat 9.30am-5.30pm.

B. BAMBER ELECTRONICS

Dept ETI, 5 Station Road, Littleport, Cambs, CB6 1QE.

Tel. ELY (0353) 860185

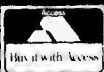

BUMPER 1980 CATALOGUE

1980 CATALOGUE. A selection of items below from our catalogue, the products we stock are by: Eagle, Weller, Draper, Spirallux, Knipex, Servisol, Jaybeam, Vero and Amrod plus many others. Books by Barnards & Babani and Newnes. Send £1.35 and you will receive main catalogue plus four bi-monthly shortform catalogues to keep you up to date with prices and special offers. Main catalogue contains 140 pages. 2 free 50p vouchers with shortform this month.

EAGLE MA780T Electric fully automatic 6 section retractable car aerial with built-in voltage sensor. Remote drive system makes fitting easier. Aerial length, 1.000mm, below wing 220mm, lead length 9.000mm. flexible drive link 700mm. Price **£18.95** plus VAT.

EAGLE DD7 Paging microphone, impedance 600 ohm or 50K ohms, sensitivity 2.25mV at 50K ohms, frequency response 300-9000 Hz. Desk or wall mounted. **£14.85** plus VAT.

EAGLE MULTIMETER EM50 50,000 opv. DC volts: 0-1200 volts. AC volts: 0-1200 volts, DC current 0-6A. Resistance 0-10 megohms. Price **£18.95** plus VAT.

DRAPER super-chrome 1/4" square drive socket sets, 38 piece, 9 AF hexagon sockets, 3 AF bi-square sockets, 11 MM hexagon sockets, 9 BA hexagon sockets, and 6 accessories. Price **£12.75** plus VAT.

SPIRALLUX metric nut spinner sets, contains 8 nut spinners, 4, 4.5, 5, 5.5, 6, 7, 8, 9, 10mm. Packaged in a plastic wallet with cellulose acetate handle. Price **£7.93** plus VAT.

WELLER TCP3 IRONS 24 volt series, 3 wire power units, for application requiring earthed tip. TCP3 irons **£13.84**. PU3D power units **£24.12** plus VAT.

WELLER instant heat guns Model No 81000 **£12.21** each plus VAT. **WELLER** cordless soldering irons Model No VC100 **£28.47** plus VAT.

JAYBEAM "STEREOBEAM" VHF/FM antennas Model SM62, folded dipole and reflector with universal clamp, **£8** each. Full range of Jaybeam aerials and accessories available. (See 1980 Catalogue).

ECA TVT80/80 semiconductor equivalent and data books. Data covering 12,000 transistors and more than 60,000 equivalents. 2 volumes. **£8**, 20p VAT.

ONYX DE-SOLDER TOOLS model SR3A, desoldering pump with built-in safety guard. Price **£6.50** plus VAT.

ICTEST CLIPS, clip over IC while still soldered to pcb or in socket. Gold plated pins, ideal for experimenters or service engineers, 28 pin DIL **£1.76**, 40 pin DIL **£2**. Or save by buying one of each for **£3.90**.

IC AUDIO AMP. PCB output 2 watts into 3 ohm speaker. 12 volt DC supply. Size approx 5 1/2" x 1 1/2" x 1" high, with integral heatsink, complete with circuits. **£2** each.

NICAD CHARGER CONVERTER. PCB (Low power inverter). Size 4" x 1 1/4" x 1" high. 12v dc supply. 60v dc output through pot on pcb for charging portable batteries from mobile supply. Size approx 5 1/2" x 1 1/2" x 1" high, with integral heatsink (not supplied). **£2** each.

10-7 MHz SSB XTAL FILTERS (2-4kHz bandwidth). Low imp. type. Carrier and unwanted sideband rejection min -40dB (needs 10-69835 and 10-70165 atials for USB/LSB, not supplied). Size approx 2" x 1" x 1" **£10** each.

LOW PASS FILTERS (Low imp. type). 2.9MHz small metal encapsulation. Size 1 1/2" x 1/4" x 3/4". **75p** each.

BSR AUTOCHARGE RECORD PLAYER DECKS with cure device. 33-45-78 rpm for 7", 10", 12" records. Fitted with SC12M stereo ceramic cartridge and stylus. Brand new **£12** each.

XTALS FOR TV SYNC GEN. 20-25kHz for 405 line, BTG glass type. **£2** each.

RED LEDs (Min. type) 5 for 70p.

VIDICON SCAN COILS (Transistor type, but no data), complete with vidicon base **£6.50** each. Brand new.

UR41 ATTENUATOR CABLE. Nominal 77 ohm, overall dia. approx 1/4". Att. per 100ft: 100MHz 215dB, 200MHz 316dB, 600MHz 449dB, 300MHz 625dB. Ideal for Rx or Low power TX fixed attenuators. Supplied with attenuation graph, 4 metres for **£1**.

HIGH QUALITY RELAYS. 4 pole C/O, 3A contacts, 12v dc coil, 150 ohms. Size approx. 1" x 3/4" x 1 1/4", with plastic covers. **80p** each or 2 for **£1.50**.

OSMOR REED RELAY COILS (for reed relays up to 1/4" dia., not supplied) 10v 50 ohm coil, 2 for **50p**.

RADIOTELEPHONE EQUIPMENT

PYE WESTMINSTER W15AM high band and low band available. Set complete and in good condition but are less speakers, mikes, cradles and LT leads (sets only) **£70** each.

PYE BASE STATION F27 low and high band, few only at **£75** each.

PYE BASE STATION F30AM low and high band, with and without T/T. Prices from **£22** each.

PYE CAMBRIDGE AM1PS (Boot Mount) low band, 12.5kHz, sets only, no control gear, good condition. **£20** each.

PYE UHF LINK U450L base Station Tx **£15**, Rx **£15** or **£25** for the two. Sold as seen.

PYE BC14 battery charger for PF1 (Pocketfone) batteries, will charge up to 12 Tx batteries and 12 Rx batteries at the same time. **£15** each.

PYE RTC CONTROLLER units, for remotely controlling a VHF or UHF fixed station radiotelephones over landlines. **£20** each.

PYE PF1 Pocketfones suitable for conversion to 70cm, sets complete but few batteries, supplied with service manual, **£28** per pair.

PYE TELECOM Yagi aerials, 4 element, very rugged construction, 71.1 MHz (ideal for four metres). Brand new **£10** each.

DISGUISED MOBILE AERIALS (dustbin lids). Available in mid band and high band. Brand new **£5** each.

PYE WESTMINSTER W15AMB (Boot Mount) low band complete with control gear and accessories, good condition, **£80** each.

PYE WESTMINSTER W30AM low band, sets only no control gear, complete and in good condition, **£45** each.

AM 10.7MHz IF PCB WITH XTAL FILTER

AT26805/10 25kHz spacing. Order code WS9 **£15**

AT26805/11 50kHz spacing. Order code WS10 **£10**

AM TX MULTIPLIER/DRIVER PCB

AT26838/13 B band (will tune high band). Order code WS11 **£10**

AT26838/14 low band. Order code WS12 **£10**

TX FILTER W15AM

AT10787/21. Order code WS13 **£4**

AT10787/23. Order code WS14 **£4**

AT10787/30. Order code WS15 **£4**

TERMS OF BUSINESS:

Cheque or P.O. Phone or quote Access or Barclaycard No. Please add **15% VAT** on above goods. **CARRIAGE:** Packing and carriage charges for all orders under £5 nett invoice value add 75p. Orders over £5 but less than £20, 50p. Orders over £20, carriage paid.

THE AMATEUR RADIO & ELECTRONICS SHOW OF THE YEAR!

Northern
Radio Societies Association

RADIO & ELECTRONICS EXHIBITION

BELLE VUE MANCHESTER

**SUNDAY, 27th
APRIL, 1980**

Doors open at 11 a.m.


- ★ INTER-CLUB QUIZ
- ★ CONSTRUCTION CONTEST
- ★ RSGB BOOKSTALL
- ★ GRAND RAFFLE
- ★ AMATEUR COMPUTER CLUB STAND
- ★ RADIO SOCIETIES STANDS
- ★ CLUB STAND TROPHY
- ★ HOME OFFICE & TELETXT EXHIBITS
- ★ OVER 50 TRADE STANDS FEATURING RADIO EQUIPMENT, MICRO-PROCESSORS, HOME COMPUTERS AND COMPONENTS
- ★ AMPLE CAR PARKS AND LEISURE FACILITIES FOR THE FAMILY!

Talk-in for FM mobiles via GB4NRS and GB8NRS on 145.55 MHz and 433.20 MHz.


Admission 30p including Raffle Ticket and Exhibition Plan.

ENTER AT REAR OF BELLE VUE, OPPOSITE MAIN CAR PARK — OFF HYDE ROAD, A57.

DOUBLE SEIKO OFFER

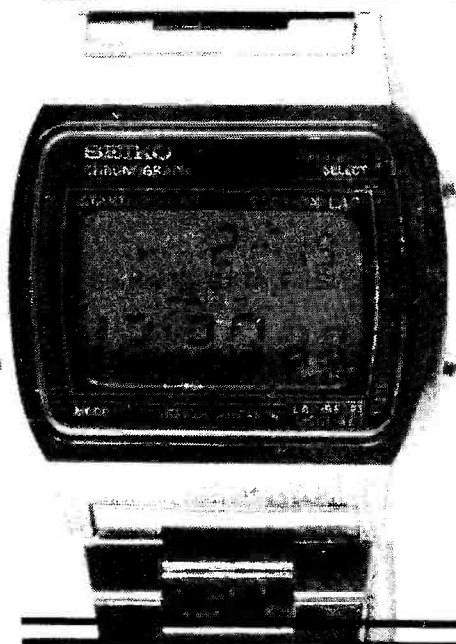

**FIRST
TIME
UNDER
£50**

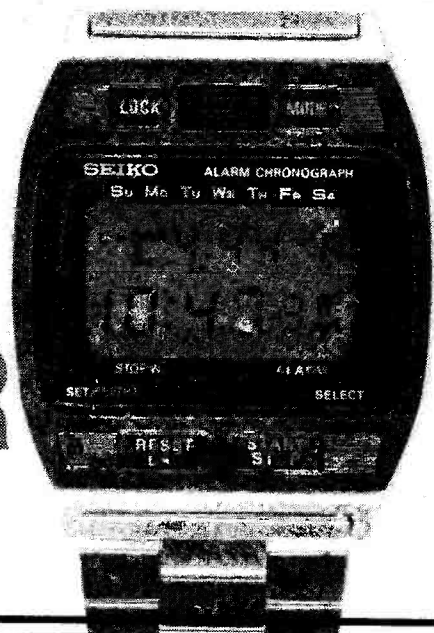

**£39.95
ALL INC**

Two Super Seikos — offered for the first time in living memory for under £50. How do we do it? You can say that again. How do we do it?

**£49.95
ALL INC**

Let's look at the simple Seiko first — a dependable chronograph with no nonsense operation. At the touch of a button you can select either the things that normal watches do i.e. telling the time or a stopwatch display with the usual split/lap time facility.

The next Seiko is a bit clever. It's an alarm chronograph with a locking facility. What does that mean, I hear you say. Buttons are prone to being pushed, especially buttons that reset the watch time. However, with this remarkable wrist piece you can just press the LOCK button and pushing all the other controls suddenly has no effect. Full chronograph and alarm facilities we also featured.

SEIKO DOUBLE WATCH OFFER

Name

Address

.....

.....

Please send me Seiko Chronograph(s) at £39.95 each.

..... Seiko Alarm Chronograph(s) at £49.95 each

I enclose a cheque/PO made payable to Modmags Ltd for £

Modmags Ltd.,
Sales Office (Ref. Seiko Offer),
145, Charing Cross Road,
London WC2H 0EE.

MICROCHIPS AT MICRO PRICES

Compare our prices before you buy elsewhere. All brand new, prime.

MEMORIES

2102 LHPC Low par, high performance 250ns	99p
2114 Low power high speed 300NS	2.95
4116 Dynamic RAM	3.50
NEW P4315 4K CMOS static RAM, low power 450ns	12.95

EPROMS

1702A	3.75
2708	4.50
2716 Single 5V supply	13.95

UART

AY-5-1013A	2.98
AY-3-1015	3.98

CHARACTER GENERATOR

RO-3-2513 UC	4.50
--------------	------

FLOPPY DISK CONTROLLER

FD 1771 Single Density	
IBM Compatible	19.95
FD 1791 Dual Density	
IBM Compatible	39.95

SUPPORT DEVICES

MC14412VL	7.97
-----------	------

KEYBOARD ENCODER

AY-5-2376	7.95
-----------	------

INTERSIL CHIPS ARE DOWN

Due to bulk purchase we are able to offer unbeatable prices on INTERSIL CHIPS. Compare our prices below distributors!

ICL7106CPL	5.95
ICL7107CPL	6.95
ICL8038CCPD	2.95
ICM7216AIJ1	18.75
ICM7216BIP1	16.75
ICM7555IPA	80p

LINEAR ICs

709	30p	NE555	18p
723	33p	NE556	50p
741	17p	RC4136	90p
747	40p	SN76477N	1.95
748	25p	TL071	40p
LM301AN	25p	TL074	1.30
LM311	42p	TL081	35p
LM318	70p	TL082	80p
LM324	35p	TL084	1.10
LM339	35p	TL490, New	1.75
LM380	60p	XR2206	3.00
LM1496	60p	XR2207	3.75
LM3900	45p		

VOLTAGE REGULATORS

7805/7812 55p	78H05SC 5.75
7905/7912 65p	78HGKC 6.25

UNIVERSAL SCR

C106D 400V 5a	35p
---------------	-----

NEW!

AY-3-8910

Bang

ZAP

Clang

Tweet

AY3-8910 PROGRAMMABLE SOUND GENERATOR

The AY3-8910 is a 40 pin LSI chip with three oscillators, three amplitude controls, programmable noise generator, three mixers, an envelope generator, and three D/A converters that are controlled by 8 BIT WORDS. No external pots or caps required. This chip hooked to an 8 bit microprocessor chip or Buss (8080, Z80, 6800 etc.) can be software controlled to produce almost any sound, it will play three note chords, make bangs, whistles, sirens, gunshots, explosions, bleats, whines, or grunts. In addition, it has provisions to control its own memory chips with two IQ ports. The chip requires +5V @ 75ma and a standard TTL clock oscillator. A truly incredible circuit. Only £8.25 + VAT.

60 page manual with S-100 interface instructions and several programming examples £2.25 extra (No VAT).

Texas Instruments Low Profile Sockets

Contacts	Price
8 PIN	.06
14 PIN	.07
16 PIN	.08
18 PIN	.11
20 PIN	.13
22 PIN	.14
24 PIN	.15
28 PIN	.18
40 PIN	.25

SALE

DISPLAY LEDs AT LOWEST PRICES

DL 704/DL 707
FND 500/FND 510

99p
99p

THE MOST VERSATILE LIQUID CRYSTAL DISPLAY

1.8:8.8

1.24 25+ 100+
£4.45 £5.50 £4.95

LCD 106 6.45 5.50 4.95
5" Field effect LCD display featuring 3½ digits, colon, plus/minus sign, 3 decimal points and "LO BAT" indicator. Ideal for DMMs, DPMs, digital thermometers, AM/FM radio readouts. Just look at the features. Ultra low power consumption, high contrast ratio, wide viewing angle, rapid response, proven sealing techniques, superior MTBF, reflective aluminium foil. Over 300,000 already sold! Perfect interface for Intersil 7106 and 7116. 40 PIN DIL

SE 01 Sound Effects Kit NEW

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator, designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3¼" x 3" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosion, Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100MW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included.)

COMPLETE KIT ONLY £12.50
P&P 50p + VAT

From T.1. TL490 BAR/DOT DRIVER IC. Drives 10 LEDs with adjustable analog steps. Units are cascaded up to 10 (100 steps). Drives LEDs directly. Great for voltage, current or audio displays. Similar in features to LM3914 with specs and circuit notes. ONLY £1.75 NEW!

Ordering information: For orders under £50 add 50p p & p. Add 15% VAT to total. All items are subject to prior sale and therefore subject to availability. Prices are subject to change without notice.

Micro Circuits


4 Meeting Street
Appledore, Nr. Bideford
North Devon EX39 1RY
Tel. Bideford (02372) 79507
Telex 8953084

LIGHTING & AMPLIFIER MODULES FROM L & B

01-689 4138


YOU'VE ALL HEARD OF OUR SUPERB MODULES, AND IF YOU HAVEN'T, IT'S TIME YOU DID. SO READ ON! SHOWN HERE ARE A RANGE OF THE MOST RELIABLE SYSTEMS ON THE MARKET.

LB31000SLC
£29.90

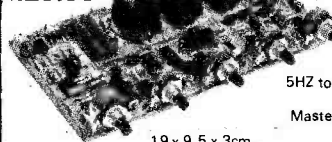

LB31000SL SOUND TO LIGHT.
A SUPERB PERFORMING SYSTEM
AT AN INCREDIBLY LOW PRICE.

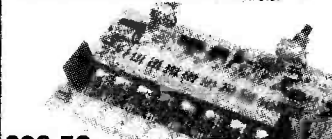3 channels. 1000w each. Fully fused. Very high input impedance. Operates from ¼ to 300w sound input. Third order filters. Zero voltage fired. Master / Vol / Base / Mid / Treble controls.



£26.50

LB81000LC
19 x 9.5 x 3cm.

LB41000LS SEQUENCER
LOGIC RANDOM SEQUENCER, WITH TWO
SPEED CONTROLS OFFERING A WIDE
RANGE OF EFFECTS.
4 channels. 1000w each. CMOS circuitry.
Zero voltage fired.



20 x 7.3 x 3.5
POWER AMPS, 250, 150, 100 & 25w, etc.
RUGGED TOUGH DEALING AUDIO
POWER AMP MODULES.

LB250	LB150	LB100	LB25
10KHZ to 25KHZ S/N 110 dB THD 0.1% 0.5v SENS	10KHZ to 25KHZ S/N 110 dB THD 0.1% 0.5v SENS	10KHZ to 25KHZ S/N 110dB THD 0.1% 0.5v SENS	20KHZ to 60KHZ S/N 90 dB THD 0.07% 0.5v SENS
£39.50	£26.50	£18.20	£11.20

PREAMPS

LBPA3. Complete stereo disco preamp system. Comprising of L&R deck mixers, mic mixer, deck and mic tone stages, mic auto fade over decks, PFL, output drivers and its own regulators.

LBPA2. General purpose 4 chan. mixer / tone stage.

LBPA1. Stereo Hi-Fi System



LBPA1 £19.50
LBPA2 £17.20
LBPA3-M (magnetic deck inputs) £30.70
LBPA3-C (ceramic deck inputs) £30.70


YOU REQUIRE A BOARD THAT'S MIGHTY COMPETITIVE, RELIABLE, MANUFACTURED FROM THE HIGHEST QUALITY COMPONENTS, OF HIGH PERFORMANCE, TESTED AND INSPECTED, SUPPLIED WITH CONNECTION AND CCT, DGM AND GUARANTEED. IN TWO LETTERS YOU REQUIRE L & B.

All prices shown are inclusive of VAT.
For your FREE catalogue, with full spec, send a 12p stamp
Trade and Overseas inquiries welcome
P/Packing FREE in the UK except power supplies (£1.00).

LB31000SLC SOUND TO LIGHT/CHASER.
THE MOST ADVANCED SOUND TO
LIGHT MODULE AVAILABLE, WITH
AUTOMATIC SWITCHING TO CHASE
UPON ABSENCE OF A MUSIC INPUT.

3 Channels. 1000w each. Fully fused. Very high input impedance. Electronic filters. 5HZ to 70KHZ bandwidth. Operates from ¼ to 300w sound input. Triac zero voltage triggering. Master Vol / Bass / Mid / Treble / Chase speed controls

LB31000SL £21.40

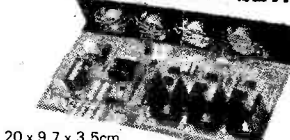

LB81000LC CHASER
A FULLY DIGITAL 8 CHANNEL
CHASER, ALLOWING VARIATION
OF CHASE SPEED AND CHASE
RETURN DELAY.

1000w per channel. CMOS circuitry. Zero voltage fired. Can be footswitch triggered. Additional modules can be cascaded to form 16, 24, 32 chan. ect.



LB41000LS
£17.50

20 x 9.2 x 3.5 cm

LB31000LD and 11000LD DIMMERS.
FULL POWER 3 & SINGLE CHANNEL
LIGHTING DIMMERS FOR USE IN
CLUBS/PUBS/THEATRES/SCHOOLS, ETC.

1000w per channel. Fully fused phase controlled. Full input and individual Triac filters.

LB31000LD £14.70 LB11000LD £6.70



LB250
27 x 15 x 3.5cm

POWER SUPPLIES

Four types of powerful supply units for our power amps. Consisting of a varnish-impregnated mains transformer and rectifier board (fuse protected).


LB250PS £24.50
LB150PS £18.00
LB100PS £14.70
LB25PS £11.20



LB250PS

45 WORTLEY ROAD
WEST CROYDON
SURREY CR0 3EB
TEL. 01-689 4138

TECH TIPS

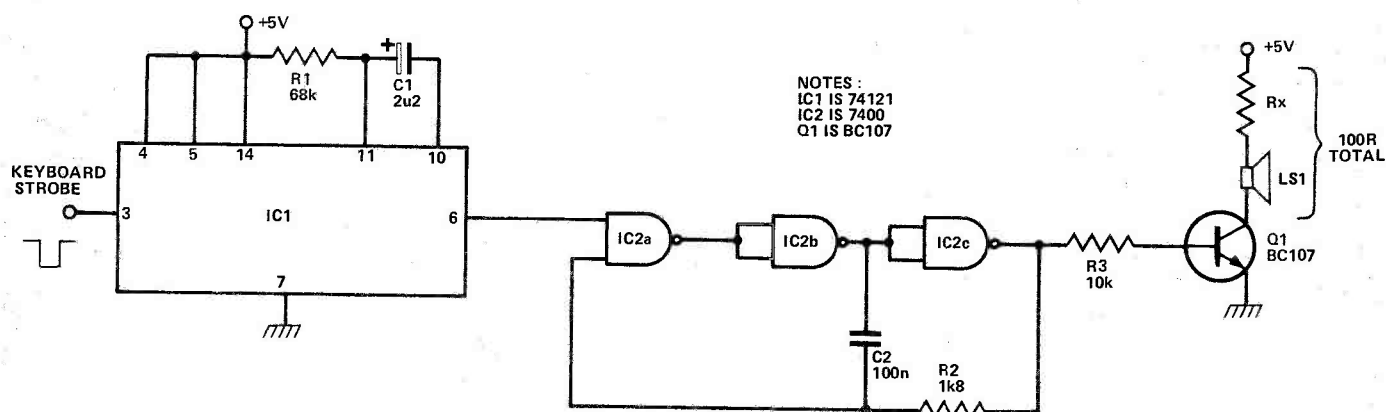

Keyboard Audio Feedback

JA Tarlton, Nottingham.

When typing data into a computer it can become a nuisance if the operator has to keep looking up at the VDU screen merely

to check if the character typed has been accepted. This often occurs when the keyboard lacks a positive feel.


This circuit provides a positive indication of keyboard operation. It consists of a monostable multivibrator with a duration

of approximately 100 ms and a TTL oscillator running at 2 kHz feeding a loudspeaker. In operation the strobe signal from the keyboard triggers the monostable which in turn switches the oscillator on, producing a tone from the loudspeaker.

Simple Ten Watt Amplifier

A Hiley, Woking.

This is an extremely simple and inexpensive general purpose amplifier. The design is conventional, the only point of interest being that the output transistors are under-biased: This means that there is no possibility of thermal runaway - it should, however, introduce large amounts of distortion, but, in fact, due to the high level of negative feedback employed, the distortion is reasonably low. Frequency response is extremely good.

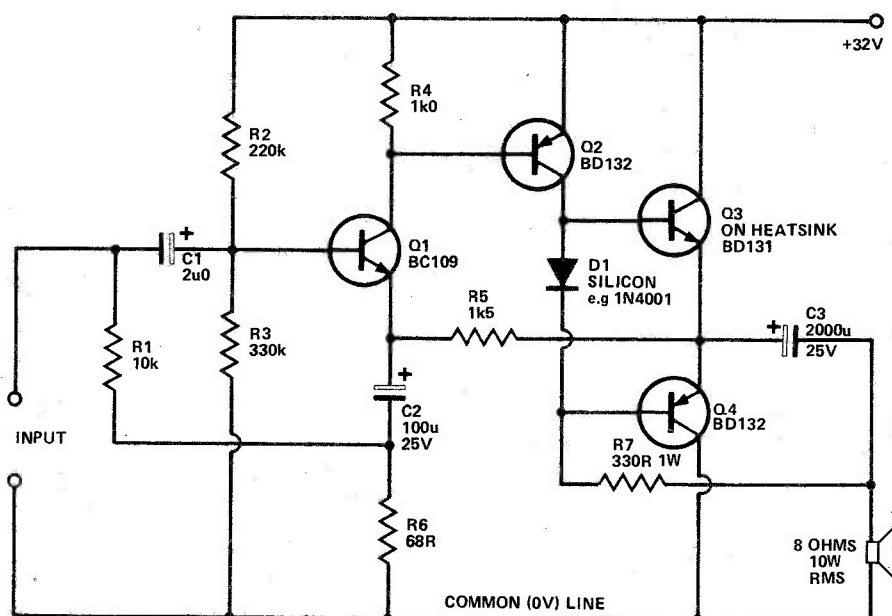

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

The finest amplification kits from Crimson Elektrik

CPR 1 — THE ADVANCED PRE-AMPLIFIER. The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slew rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion <0.005% at 30dB overload 20kHz. Following the stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. Signal to noise ratio 86dB; slew-rate 3V/uS; T.H.D. 20Hz — 20kHz <0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ± 15 volts.

MC 1 — PRE-AMPLIFIER. Suitable for nearly all moving-coil cartridges. Send for details.

X02: X03 — ACTIVE CROSSOVERS. X02 — two way, X03 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1 — POWER SUPPLY. The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

** NEW ISSUE 5 **

POWER AMPLIFIERS. Our new issue 5 power amplifier modules have automatic shut-down that will not allow serious overloads for more than 0.1 sec — thus vastly increasing reliability at elevated temperatures. Other improvements to the circuitry have improved the subjective qualities which keeps CRIMSON even further ahead of the field.



POWER SUPPLIES. We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

PRE-AMPL KIT

This includes all metalwork, pots, knobs, etc., to make a complete pre-amp with the CPR 1 (S) module if required.

All prices shown are U.K. only and include V.A.T. and post. C.O.D. 90p extra £100 limit. Export is no problem, please write for specific quote. Send large S.A.E. or 3 International Reply Coupons for detailed information.

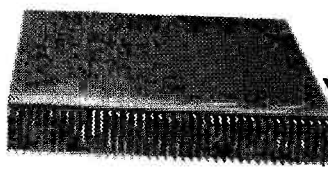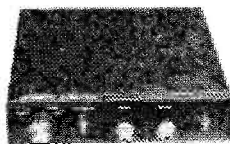POWER AMPLIFIER KIT. The kit includes all metalwork, heatsinks and hardware to house any two of our amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up services enable a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES	
CE 608	£21.00
CE 1004	£24.50
CE 1008	£27.50
CE 1704	£35.00
CE 1708	£35.00

HEATSINKS	
Light duty, 80mm, 2 C/W	£1.70
Medium power, 100mm, 1.4 C/W	£2.70
Disco/group, 150mm, 1.1 C/W	£3.50

Fan mounted on two drilled 100mm heatsinks	
2x4 C/W 65 max. when used with two 170W modules	£36.00

THERMAL CUT-OFF, 70C

TOROIDAL POWER SUPPLIES

CPS1 for 2x CE 608 or CE 1004	£19.50
CPS3 for 2x CE 1004 or 1/2 x CE 1008	£23.50
CPS6 for 1/2 CE 1704 or 1/2 CE 1708	£30.00

POWER AMP KIT £35.50

PRE-AMP KIT £39.80

PRE-AMPS

These are available in two versions — one uses standard components, and the other (the S), uses MO resistors where necessary and tantalum capacitors

CPR 1	£34.00
MC1	£26.00
CPR 1S	£44.50
MC 1S	£37.50

ACTIVE CROSSOVER

X02	£19.00
X03	£28.35

POWER SUPPLY


REG1	£9.30	TR6	£2.50
------	-------	-----	-------

BRIDGE DRIVER, BD1

Obtain up to 340W using, 2x170W amps and this module

BD1	£7.25
-----	-------

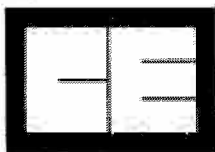
U.K. — Please allow up to 21 days for delivery
*Write for free literature or send 50p for application/users' manual.



Crimson Elektrik

1a STAMFORD STREET, LEICESTER LE1 6NL.
Tel. (0533) 553508

OHIO SCIENTIFIC SUPERBOARD II

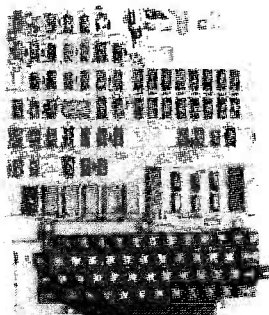

IMMEDIATE DELIVERY FROM STOCK
£149.95 + 15% VAT POST FREE



THE UNIQUE SPECIAL
OFFER YOU CAN'T RESIST


- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★
- ★ If any of the below items are bought, with Superboard we will supply them at the reduced prices shown first. They are also available separately at the bracketed prices. Add 15% VAT. ★
- ★ Modulator and power supply kit £4.95 (£7.95). 4K extra ram £18.40 (£24). ★
- ★ Case £19 (£21). Cassette recorder £12.13 (£14.74). ★
- ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

SINCLAIR PRODUCTS



PFM200 £51.95, case £2.07, adaptor £4.03, connector kit £11.27. Microvision TV £69, mains adaptor £6.88. POM35 £34.23, mains adaptor £4.03, case £3.40. DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models: — rechargeable batteries £7.99, mains adaptor/charger £4.03, case £8.90. Enterprise prog calculator £19.95. New SC110 10MHz oscilloscope £144.95.


COMPUTER GAMES

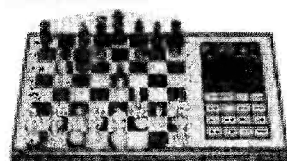

Chess challenger 7 (illustrated) £84. Chess champion 6 £49.95. Checker challenger 2 £46. Star Chess £62. Grandstand video entertainment computer £79.95. Videocarts £12.60. Philips G7000 Videopack home computer £149. Video paks £12.95. Atari Videocomputer £147. Cartridges £14.85 (except chess £43.95 and backgammon £33.95).

TV GAMES

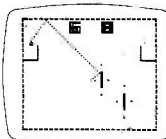Tank battles kit £8.34. AY-3-8500 chip £3. Kit £7.26. Stunt cycle AY-3-8760 chip £13.71, kit £4.95. 10 game paddle 2 AY-3-8600 chip £10.25, kit £7.03. Racing car chip AY-3-8503 £13.63. Modified shoot kit £5.28. Rifle kit £5.27. Colour generator kit £9.05.



MAINS TRANSFORMERS

6.0-6V 100ma 80p, 1 1/2 £2.60. 9.0-9V 75ma 80p, 1a £2.90, 2a £3.94. 12.0-12V 100ma 92p, 1a £2.90. 15.0-15V 1a £3.15.

JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 watts £2.08. JC20 10 watts £3.14.

CONTINENTAL SPECIALTIES PRODUCTS

EXP300 £6.61. EXP350 £3.62. EXP325 £1.84. EXP650 £4.14. EXP48 £6.64. LP2 £20.70.

STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. TTL computer supplies 5V 2A £2.95 (£6.45), 5V 4A £3.95 (£10.32). 8-way types 3/4V 16/7V 19/12/15/18V 100ma £1.84 (£2.60), 1A £3.30 (£6.50), 2A £5.60 (£9.84). Variable voltage models 2-18V 100ma £2.12 (£2.98), 1-30V 1A £3.30 (£6.75), 1-30V 2A £5.60 (£12.10).

PRINTED CIRCUIT MATERIALS

PC etching kits: — economy £2.42, standard £4.76. 40 sq. ins. pcb 45p. 1 lb. FeCl £1.50. etch resist pens: — economy 50p, delo 84p. drill bits 1/32" or 1mm 34p. etching dish 92p. laminate cutter £1.20.

BI-PAK AUDIO MODULES

AL30A £4.08. PA12 £8.38. PS12 £1.58. TS38 £2.70. S450 £25.06. ALB5 £5.06. PA100 £17.33. SPMB0 £4.74. BMT80 £6.06. Stereo 30 £21.57. ALB0 £7.71.



COMPONENTS

1N4148 0.9p. 1N4002 2.9p. 1N4004 3.4p. 723 14 dii 33p. NE555 8 dii 24p. 741 8 dii 18p. bc183, bc213, bc547, bc549 4.9p. bc182, bc184, bc212, bc214, bc548 5.5p. tip31c, tip32c 3.6p. tip41c 40p. bd132 27p. plastic equiv bcy72 4.5p. fuses 20mm x 5mm cartridge .15. 25, .5, 1, 2, 3, 5amp quickblow 1p. anti-surge 3.6p. resistors 5% 1/4W E12 10R to 10M 1p. 0.8p for 50+ of one value. Polyester capacitors 250V .015, .068, .1mf 1.5p, .01mf 3p, .022 .033mf 3.3p, .047mf 3.5p, .15, .22, .33, .47mf 4.9p. Polystyrene capacitors E12 63V 10 to 1000pf 3p. 1n2 to 10n 4p. Ceramic capacitors 50V E5 22pf to 47n 2p. Electrolytic capacitors 50V .5, 1, 2mf 5p, 25V .5, 10mf 5p, 16V 22, 33mf 5p, 47, 68mf 3.5p, 100mf 6p, 330 470mf 9p, 1000mf 11p. Zeners 400mw E24 2V7 to 33V 7p. Preset pots subminiature 0.1W, horiz or vert 100 to 4M 7p. Potentiometers 10k 4K7 to 2M 2 log or 1in single 27p, dual 71p. red LEDs 9.7p. IC sockets 8 dii 8.7p, 14 dii 10.1p, 16 dii 12p.

BATTERY ELIMINATORS

3-way types with switched output and 4-way multi jack: 3/4V/6V 100ma £2.67, 6/7V/9V 300ma £2.84. 100ma radio types with press-stud connectors 9V £3.57, 6V £3.57, 4V £3.57, 9+9V £4.79, 6+6V £4.79, 4 1/2+4 1/2V £4.79. cassette recorder mains unit 100ma with 5 pin din plug £3.57. Full size 240 type 3/5 7/7V/9V 400ma £5.97. Car connectors 12V dc input, output 9V 300ma £1.19, 6V 300ma £1.19, output 2 1/2V 6V 300ma £2.66.



BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4V £1.49, 6V £1.49, 9V £1.49, 4+4+4+4V £1.92, 6+6V £1.92, 9+9V £1.92. cassette recorder 7V 100ma with 5 pin din plug £1.49. Heavy duty 13-way types 4V £1.49, 6V £1.49, 9V £1.49, 21 25 28 34 42V 1A £5.52, 2A £8.80. car-converter input 12V dc output 6V 12V 9V 1A stabilized £1.35.

S-DECS AND T-DECS

S-Dec £3.79. T-Dec £4.59. J-DecA £4.69, u-DecB £7.16. 16 dii adaptor £2.31.

SWANLEY ELECTRONICS

Dept. ET1, 32 Goldsel Road, Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13% Official credit orders welcome

Memory Test-T159

JK Porter, Gravesend.

The game is basically a test of mental agility and determines how many digits the player can successfully retain in his memory, whilst having to do deductive thinking at the same time. Because you can pre-set the level of difficulty, the game is suitable for all ages, and at its upper skill level it is very difficult indeed.

A series of numbers will be shown, each being displayed for about one second. This is an example:

0.7849

The numbers to watch are the first three digits of the mantissa, that is, the 7, 8 & 4. Deduce the number's highest digit, and remember it. In this case, it is the 8, since you ignore the last digit. If, as in 0.5884, the highest digit occurs twice, only remember it once. Do this for all the numbers flashed at you, (determined by the number you place in Memory 0 at the beginning of the game). So, if you choose to have 6 numbers displayed, you will eventually remember 6 digits. When the program stops, multiply all these digits together. By subtracting the number now in Memory 4, you can see how far you are, and if too high, or too low. (Positive number, too high; negative number, too low).

PROCEDURE


1. LRN. Key in program. LRN. RST.
2. 2nd FIX 4.
3. I STO 4.
4. Quantity of numbers you wish to be shown, e.g. 6 STO 0, You will be shown 6 numbers.
5. Key in all-decimal number, e.g. 0.675432. R/S.
6. Game runs.
7. When program halts, multiply together the requisite digits. Subtract from this the quantity held in Memory 4 to find the result.
8. Continue from 3.

LOC	CODE	KEY			
00	34 6	SUM 6	14	32 2	STO 2
01	33 6	RCL 6	15	61 1	SBR 1
02	35	Yx	16	32 3	STO 3
03	30	2nd π	17	33 1	RCL 1
04	85	=	18	22	x t
05	-35	INV Yx	19	33 2	RCL 22
06	05	5	20	76	2nd $x \geq t$
07	85	=	21	22	x t
08	-49	INV 2nd INT	22	33 3	RCL 3
09	36	2nd PAUSE	23	76	2nd $x \geq t$
10	34 6	SUM 6	24	51 5	GTO 5
11	61 0	SBR 0	25	33 7	RCL 7
12	32 1	STO 1	26	39 4	2nd PRD 4
13	61 1	SBR 1	27	51 6	GTO 6
			28	86 5	2nd LBL 5
			29	39 4	2nd PRD 4
			30	86 6	2nd LBL 6
			31	56	2nd DSZ
			32	71	RST
			33	00	0
			34	81	R/S
			35	71	RST
			36	86 0	2nd LBL 0
			37	55	X
			38	01	1
			39	00	0
			40	85	=
			41	32 5	STO 5
			42	49	2nd INT
			43	-61	INV SBR
			44	86 1	2nd LBL 1
			45	33 5	RCL 5
			46	-49	INV 2nd INT
			47	61 0	SBR 0
			48	-61	INV SBR

Cascade Timer

P R G Reynolds, Benfleet.

This device will give timing periods in excess of one hour, using the minimum of external components, together with an inexpensive CMOS integrated circuit. The high input impedance of CMOS circuits is used to provide two cascaded timing networks. Network RV1-C1-R1 gives a variable time delay before sending output 1 low. This output is buffered and inverted, before initiating the timing sequence associated with the second network, R2-C2. Output 2 is again fed to the second buffer before connection to an output display via Q1. A flashing display was chosen in this case for two reasons. First, to conserve current in an already economical circuit. Second, a flashing display is more immediately noticeable. However, there is no reason why an alternative display should not be used.

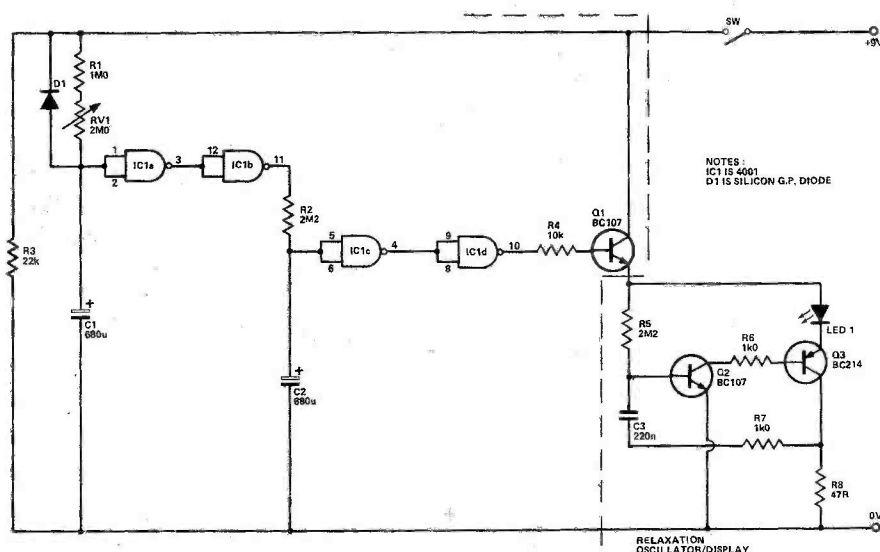

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all...

Our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, ICs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc. etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including ICs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2OD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

TTL CMOS 74LS LEDs

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

PCB OFFERS

(1A) 100 bit shift register PCB, 115mmx94mm containing 9x7491, 6x7496 and 1x7441. Terrific bargain 85p, p&p 30p.
(1B) Audio amp PCB (LM380) 9-18v d.c. output 2 1/2 watts into 8 ohm with heatsink. 1.25 watt 40hm without heatsink. £1.50 p&p 25p.
(1C) PCB 215mm x 290mm 12xTMS 3122J (or sim.) Hex 32-bit Shift Reg. + 39 ICs £2. + 50p p&p (limited stocks)

MPU CORNER

2112 (200ns), £3. 2114 (450ns) £4.50.
1702 £2.50. 2708 (400ns) £6.25.
2716 (Single Rail) £19.00.
74125 4 for £1 + p&p 25p.
MK 1002P (dual 128 bit Shift Reg) 35p.
LM711CH (Voltage Comparator) 30p.
MM5240 Character Generator + Data 2560 Bit (64 x 8 x 5) £3.50, p&p 25p.
(All Full Spec)

D TYPE CONNECTORS

15 Way: wirewrap plugs only 75p.
25 Way: ribbon plugs £1.20.
25 Way: ribbon sockets £1.20.
37 Way: plug £1.40, skt £1.40.
50 Way: skt (wirewrap) £1.65.
50 Way: skt £1.45, p&p 25p.

COVERS

37 Way: 80p. (Plastic) p/p 25p.

DISPLAYS

MAN 72 7 seg CC £1.25 p&p 25p.
Burroughs Panaplex 9 Dig. + skt and bezel £1.00, p&p 25p.
LED 3 Digit DIL 55p, p&p 25p.
Bowmar 9 digit 1in LED with red bezel. (As used in calculators). £1.00 + 25p p&p.

SUPERSAVER

Ribbon Cable Headers 16 DIL Jermyn, gold plated, with cover 45p, p&p 25p.

SUPERSAVER 2

Tantalum Capacitors 25 volt. 4.7 uF. 14 for £1.00, p&p 25p.

SUPERSAVER 3

Stepping motors, 40mm dia. 70mm long 5mm shaft (approx). 12-24V torque 340 GMC. Brand new, give away price £2.50, p&p 40p.
Pewec Boxer. As above but 115v at £4.50 + £1.00 p&p.

SUPERSAVER 4

HYBRID SYSTEMS DAC 371-8 Bit. DIL packaged, ideal MPU users with data. £2.95, p&p 25p.

SUPERSAVER 5

LM 323K Voltage Regulator, 5 volt 3A, £1.50, p&p 25p.

SUPERSAVER 6

RS 338-383 Miniature Decade Thumbwheel Switch, £1.65, p&p 25p.

SUPERSAVER 7

SN74116 Dual 4 Bit latch 75p, p&p 25p.
SN7418 Arithmetic Logic Unit, 80p, p&p 25p.
SN74194 4 Bit Register. 50p p&p 25p.

SUPERSAVER 8

BC 108b 8p each or 100 for £7.00, p&p 25p.

SUPERSAVER 9

4 Digit 7 segment LED Bubble Display, NSA 1540A Ex equipment, 5 for £1, p&p 25p.

SUPERSAVER 10

9 way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCB's together. Superb value, 35p, p&p 25p.

SUPERSAVER 11

STAR OFFER. Dynamic hand microphone 200 ohm with lead and 5 pin plug. £1.25 (unrepeatable) p&p 30p.

SUPERSAVER 12

TMS 3128NC Static shift register, £1.50, p&p 25p.

SUPERSAVER 13

PL259 (UHF) Elbow Connectors, 50p each, p&p 25p.

SUPERSAVER 14

1S423 Stud mounting rectifiers, 440v, 10A, giveaway price, 10 for £2, p&p 25p.

SUPERSAVER 15

20K Painton multivibrator trim pots, PCB mounting, per box of 14 £2.50, p&p 25p.

SUPERSAVER 16

Astec UM1163E 36 modulator plus PAL colour PCB (faulty). Few only £2.25, p&p 30p.

LEDs (Full spec).

TIL209, red 10p, 0.2in, red 12p, 0.2in, green 28p, 0.2in, yellow 28p.

RL54 red Axial lead. 15p.

P&p on all above 25p.
VERNITRON Ceramic filters type FM4 10 7MHz 45p, p&p 25p.

TRANSISTORS, 80236 40p.

BC183L 10p, BF195 10p, SGS 2N3055 30p, p&p on all 25p.
TBA 8105, with data. 85p, 4-way DIL switches. 75p. MC1303 Dual Stereo preamp with data. £1.25.

NEW SN76477 (Yes, back in stock).

Sound Generator IC (Train, plane, explosion, laser gun etc.), with data £3.25, p&p 25p.

PCB KEYBOARD, 65mm x 82mm.

18 key Clickers less key tops, ideal Hexadecimal use 35p, p&p 25p.

PACKAGED 10-WAY REED relay 12V coil terrific value 50p.

p&p 25p.
PAPST min-fans 80mm x 80mm (approx) 220V 50Hz Brand new £8, p&p £1 (limited stocks).

NEW PERANCEA CASES.

These superb cases now stocked the DIN range incorporating the following features. Matt black finished bezels snap fitting into case

front, firmly retaining either case front panes provided, one aluminium, one RED anti-reflective. Each case has two sets of guides with rear panel slots for PCB mounting.

Types available:
DIN 1458 £3.75
H48xW96x0.75mm
DIN 2368 £3.00
H36xW72x0.120mm
P&p 25p. SAE for leaflet.

WE STOCK PETS

BK version £599. SAE for the PET SORCERER software lists at discount prices.

We can also offer a 48-hour repair service for out of warranty PETs. Telephone for details. PET edge connector 40x04 £1.40 each p&p 25p.

IC HOLDERS (Low-profile)

8 DIL 12p 14 DIL 15p
16 DIL 17p 18 DIL 20p
22 DIL 28p 24 DIL 35p
28 DIL 45p All p&p 35p

WE STOCK a vast range of TTL, CMOS, some 74LS, MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

RELAYS

ITT 700 ohm Single pole changeover. 45p. BANOR resettable double pole changeover 12V £1, both p&p 25p.

CIRCUIT BREAKERS

4450v AC 65v DC 0.5A 50p; ditto 7A 80p, p&p 25p.

ALLEN KEYS, 7/16in 5p; 12 for 50p; p&p 25p.

Olivetti line printer with tape punch and reader, upper and lower case. With stand £295. Phone for more details.

CALCOMP MODEL 140 Bin Disc Drive fully tested. £195 inc VAT, carriage & cost. CALCOMP 140 Bin Fault on PCB £120 in VAT, carriage & cost.

PERTEC FD 400 U2. Dropped by an idiot. Damaged front panels. £60 each inc VAT, carriage & cost. Recordall telephone answering machines (GPO line matching transformer removed) sold as is from £2 to £10 depending on condition. Fitted with very nice standard cassette deck. With circuit diagrams SORRY BUT FOR CALLERS ONLY.

Terms cash with order (official orders welcomed from colleges etc). All enquiries s.a.e. please. All prices inclusive of VAT unless otherwise stated. Postage as shown per item.

FOR THE PROFESSIONAL USER. Gould mg5-208 PSU 5. 20A. Brand new and boxed (switching) £65 p&p £3.

Gould PMA 47/10 015V. 3A Brand new £45 p&p £3.50. Many more in stock but in small numbers. Please phone for requirements.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING


Surplus stocks purchased for cash

LB ELECTRONICS

11 HERCIES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND


All enquiries s.a.e. please

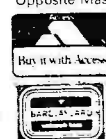New retail premises now open Mon., Thurs. Fri. and Sat. 9.30-6.00. Lunch 1-2.15 weekdays. We are situated just off the A40 Opposite Master Brewer.



UXBRIDGE
55399

All components full spec

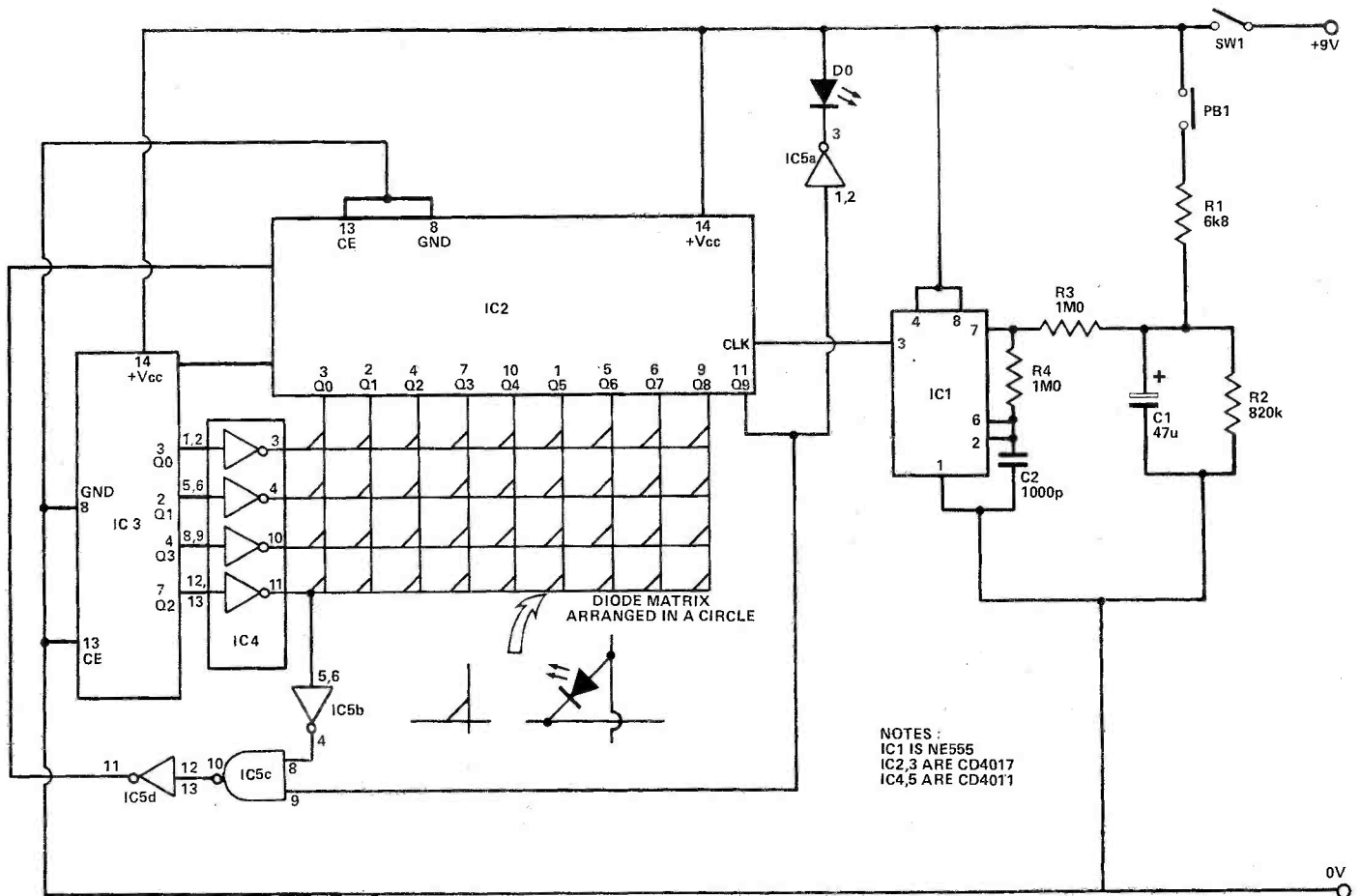

Electronic Roulette

AC Dickens, Leicester.

The advantage of this design over ten number versions, is that all 37 numbers are catered for, as in a conventional game, and the electronic circuit remains cheap and simple.

Initially, when PB1 is depressed, C1 charges via R1. The voltage on IC1 pin 7 rises, causing IC1 to start generating pulses which rapidly increase in frequency. IC2 & IC3 are decade counters, arranged so that each one of the 36 red LEDs in the matrix is illuminated in turn. The gates of IC5 are arranged so that D₀ (which is green in my circuit) is illuminated after D₃₁, and followed by D₁. Hence an apparent cir-

cular motion is generated. After the 'wheel' has been spun, PB1 is released. C1 now discharges via R2 and R3, so that the 'wheel' apparently slows down and then stops at one of the 37 numbers, each of which has an equal probability of occurring. The running time, and speed of 'revolution' can easily be altered by changing the value(s) of appropriate capacitor(s) or resistor(s).

Cassette Tape Preamp

R Willis, Felsted.


Preamp circuits utilising the LM382 low-noise preamp chip have been used in ETI before. However, when using them in conjunction with a cassette player the results can be disappointing as the cassette equalisation was to NAB standards.


This circuit is equalised for the Philips cassette system and will provide a high quality output of about 100 to 200 mV when driven from a stereo tape head.

The circuit will work on supply voltages from +10 V to +40 V, taking about 10 mA and is suitable for industrial, PA, do-

mestic, portable and automatic application. In operation R1-C1 and R3-C11 provide RF immunity. R2-C4 and C15-C16 provide the 120 uS time constant. C3-C5-

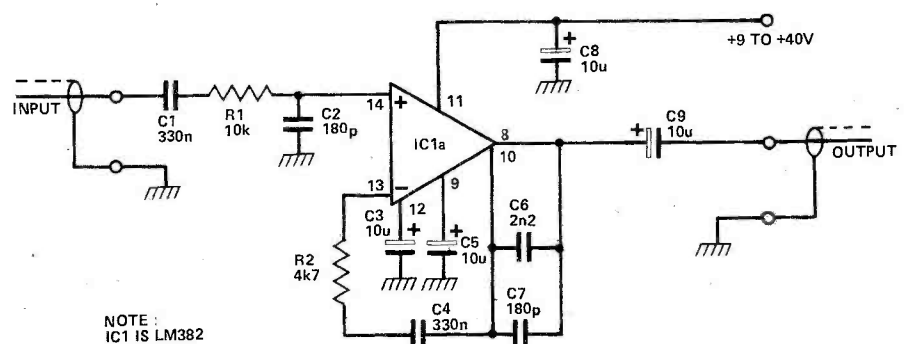C12-C14 decouple the internal feedback loop of the IC and C8 decouples the supply line. C1-C8-C10-C17 AC couple the input and output screened wires.



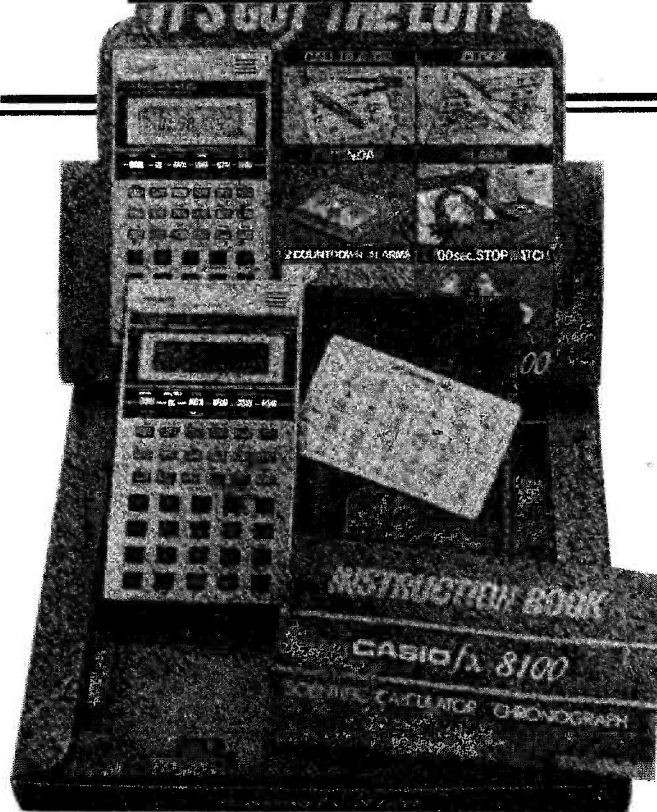

Calculating Casio

This is a slightly better than usual scientific calculator/chronograph from Casio measuring 6.6 mmH x 70 mmW x 129 mmD. Its electronic buzzer will give hours of amusement to its proud owner as it can be used with its alarm, two countdown alarms, or hourly time signal, and boy, is it loud! Not only that, but this fine piece of technology has a calendar indicating year, month, date and day with a programmed range from March 1st 1976 to December 31st 1999, if they don't make you obsolete by then! "That's all very well", you cry, "but what does it actually do?" Well, 46 scientific functions include: 4 basic calculations, constants for $+/-x/-/x^y/x^{1/y}$, parenthesis calculations up to five levels, accumulation to the memory, fraction calculations, percentage calculations, statistical calculations, obtaining standard deviation sexagesimal to

decimal conversion, trigonometric/inverse trigonometric functions, hyperbolic/inverse hyperbolic functions, common and natural logs, exponentiations (antilogarithms, exponentials, powers and roots), squares, square roots, cube roots, reciprocals, factorials, conversion of coordinate system, sign change, register exchange, Pi entry and scientific notation. (Phew).


But that's not all — capacity for entry or basic calculations is 8-digit mantissa, or 8-digit mantissa plus 2-digit exponent up to $10^{19.9}$. Fraction calculation capacity is maximum 3-digit mantissa for each integer, numerator or denominator and at the same time maximum 6-digit mantissa for the sum of each part. All this from its one little chip: C-MOS-LSI crystal oscillator. Amazing isn't it? But not quite as amazing as the 144-page instruction book that tells you how to make it do all these things. The normal price is £27.95, or £24.95 from Tempus.

Third Hand

Have you ever wished, whilst fiddling with your circuitry, that your hands didn't act like a bunch of sausages? Well, Telpro have produced an aid for the harassed electronics handyman in the form of the Multi-Purpose Work Holder. One side has a series of holes for gripping objects from 1 mm in diameter (component leads, etc) to 20 mm in diameter. The reverse side is serrated to hold flat objects such as circuit boards. A spring loaded knob allows the clamp pressure to be varied.

The clamp is mounted on a universal joint allowing 360° rotation and 180° tilt from vertical to horizontal and can be locked in any position. The clamp is detachable from its metal stand which has sucker feet, so that an alternative stand for fitting to a bench vice can be used. This is available as an optional extra. Metal and nylon jaws are supplied with the holder as standard.

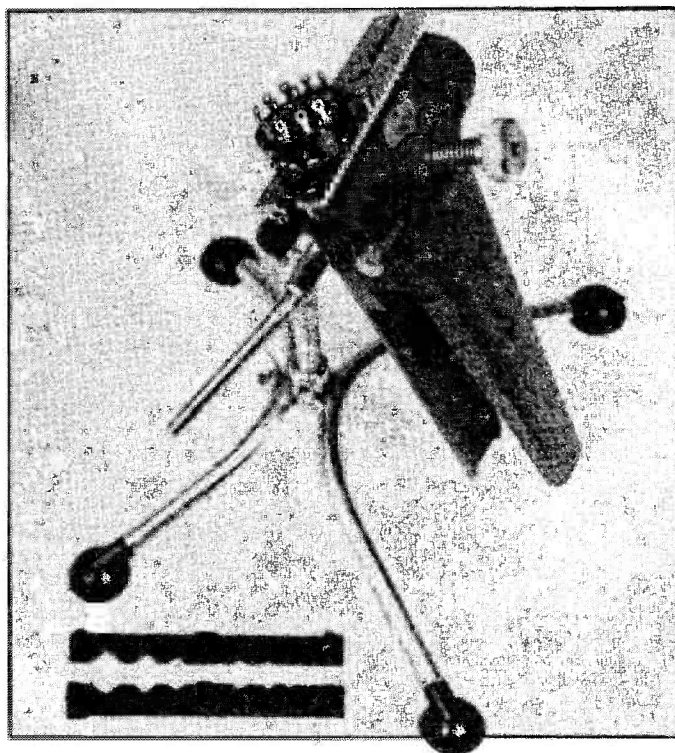So gone are the days of squashing things and dropping them just as you're getting the wire onto the pin... blast! it slipped out of my fingers.



Stripping News

AB Engineering has produced a new wire stripper and cutter based on their popular AB MK 100 and called the MK 001. It has an improved locking device and features a knurled knob

adjustment to control stripping depth, a retaining clip to keep it closed and a curved cutting edge for clean wire cutting. The price is £1.85 and further details of this and the company's large range of tools are available from: AB Engineering Company, Timber Lane, Woburn, Beds. MK17 9PL.

MEMorable Big Brother

MEM are to launch two new programmable logic controllers for controlling automatic machinery. Memaster 500 can handle no less than 512 channels and can store up to 4096 logic instructions. If your system requires more than that, doubling the memory capacity is possible at relatively low cost. If your control requirements are a little more modest the smaller Memaster 80 system may be what you need.

Memaster 500 is rather unusual in that it incorporates a digital input filtering system and a timer and counter unit with direct manual adjustment. The controller fits into a standard rack mounting system. Modular design makes for easy servicing. The controlling program can be tested in slow motion and, if necessary, printed out or burned permanently into UVEPROM (ultraviolet erasable PROM).

You can get further details of this sophisticated new PLC system from MEM Electronics Division, Regency House, 101 Hagley Road, Birmingham B16 8LA.

NEW

CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

*** EASY TO BUILD * 5 PUSH BUTTON TUNING * MODERN STYLING DESIGN * ALL NEW UNUSED COMPONENTS * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B. * INCORPORATES SUPPRESSION CIRCUITS**



The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

£10.50 p&p £1.75

CONSTRUCTORS PACK 7A
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

£1.95 Per Pack, p & p £1.00.
Pack 7A may only be purchased at the same time as Pack 7.
NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

A FEATURED PROJECT IN PRACTICAL ELECTRONICS

R T V C

323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.
21 E HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat
9.30am-5.30pm
Closed Thursday

NEW 12+12

AMPLIFIER KIT

An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—taps, speakers and headphones. By the press of a button it transforms into a 24 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free.

Size 9 1/2" x 8 1/2" x 4" approx. with kit. **£13.95**
NOTE: for use with 4 to 8 ohms speakers. p&p £2.55

TWO WAY SPEAKER KIT To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65.

Available only to first time purchasers of the 12 + 12 kit.

50WATT MONO

DISCO AMP

£30.60

p&p £3.20

Size approx 13 1/2" x 5 1/2" x 6 1/2"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infegral push-pull switches. Independent bass and treble controls and master volume.

NOW AVAILABLE

30 + 30 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers.
Size 14 1/2" x 3 1/2" x 10" approx.
BUILT AND READY TO PLAY p&p £3.30 **£32.90**

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK **SEE OUR PRICES**

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£5.00** p&p £1.10

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. illus. OUR PRICE **£7.65** p&p £1.15

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p £1.70 **£4.05**

R T V C

323 EDGWARE ROAD, LONDON W2
21 E HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at 5.30 and subject to change without notice.
All enquiries Stamped Addressed Envelope.
NOTE: Persons under 16 years not served without parent's authorisation.

£76.00 p&p £4.00
100 WATT MONO DISCO AMP

Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10 1/2"
Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

EMI SPEAKER BARGAIN

Stereo pair 350 hrs. System consists of 13" x 8" approx. woofer with rolled surround. 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance.

£18.25

Per stereo pair p&p £4.20

BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00
Shure M75 B Magnetic Cartridge to suit. **£7.95**



BSR

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use. p&p **£12.25** £2.75

PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete
UNBEATABLE OFFER AT BUYER COLLECT ONLY

BARGAIN OFFER
Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00. **OUR PRICE £11.95** p&p £2.50

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N IRELAND ONLY

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

033	LED Audio Display (2 boards) (topside pattern) Bench Amp NICD Charger	Aug 79	036D	Power Switch Selector (double sided)	Nov 79	039A	Hum Filter Logic Probe	Dec 79
034	Cable Tester Reaction Tester Speech Compressor Preamp Power Supply Rectifier & De-Thump Board Power Amp (2) (price £1.60)	Nov 79	037A	Encoder (double sided)	Dec 79	039B	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79
035	Oven Leakage Detector Pinball Wizard	Nov 79	037B	Decoder (top side)	Dec 79	039C	Function Generator	Dec 79
036A	3 x Display Board Relay Activator Points Controller	Nov 79	037C	Decoder (bottom side)	Dec 79	049A	ETI 80 — VCO and VCLFO	Feb 80
036B	Data Distributor (double sided)	Nov 79	038A	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79	040B	ETI 80 — PSU Tuning Fork Filter Coin Toss	Feb 80
036C	Train Speed Controller Track Cleaner & Electronic Pot (double sided)	Nov 79	038B	Hum Filter Dice Logic Probe	Dec 79	041A	ETI Audiophile ETI VCA Signal Trace ETI HC Electromyogram	Mar 80
			038C	Function Generator	Dec 79	041B	VCM Heater Controller	Mar 80
			039	Buffer Moving Coil Preamp Process Controller	Jan 80	042A	300W Amp Module	Apr 80

HOW IT WORKS



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

BUY LINES

ORDER TODAY

Send a cheque or P.O. (payable to ETI Magazine) to:

ETI PRINT, ETI MAGAZINE
145 Charing Cross Road, London WC2H 0EE

95p INC P & P

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Electrolytic Radial Leads				Miniature Low Value				Polyester Radial Leads			
Electrolytic Axial Leads				Order Code				Order Code				Order Code			
-10% to +50% Tol.				-10% to +50% Tol.				Polyethylene, Axial, ±1% Tol., ±63V DC Wkg.				Dipped Type, C280/352 Style			
µF	V.d.c.	16	25	40	63	100	150	µF	424	632	100	µF	352	360	360
1.0								1.2	100	18	9	0.001	7	7	9
1.5								1.5	120	18	9	0.0015	7	7	9
2.2								1.8	150	18	9	0.002	6	7	22
3.3								2.2	180	18	9	0.003	6	7	33
4.7								2.7	220	18	9	0.004	6	7	47
6.8								3.3	270	18	9	0.005	6	7	68
10								4.7	330	18	9	0.01	6	8	1.0
15								6.8	390	20	6	0.015	6	8	1.5
22								10	470	20	6	0.022	6	8	2.2
33								15	560	20	6	0.033	6	8	3
47								22	680	20	6	0.047	6	8	4
68								33	820	20	6	0.068	7	8	
100								47	1000	20	6				
150								68	1200	20	6				
220								100	1500	20	7				
330								150	1800	20	7				
470								220	2200	20	7				
680								330	2700	20	7				
1000								470	3300	20	7				
1500								680	3900	20	7				
2200								1000	4700	25	8				


INTEGRATED CIRCUITS																LINEAR																Voltage Regulators	
4000 Buffered C-MOS – High Speed																7400 T.T.L.																	
HEF4000	22	HEF4004	1-05	HEF4512	138	N7400N	13	N7444N	92	N74122N	40	N74193N	91	N74LS28N	35	N74LS138N	99	N74LS253N	117	CA3046	84	CA3086	77	LM3090AN	41	UA723CN	42						
HEF4001	22	HEF4048	1-33	HEF4514	313	N7401N	14	N7446N	85	N74123N	77	N74194N	73	N74LS30N	19	N74LS139N	99	N74LS275N	117	CA3140E	99	CA3108E	48	UA7805CU	78	UA7805CU	78						
HEF4002	1-12	HEF4049	57	HEF4515	374	N7402N	13	N7447N	85	N74124N	37	N74195N	73	N74LS31N	27	N74LS140N	99	N74LS276N	117	CA3189E	293	LM318N	34	UA7812CU	78	UA7812CU	78						
HEF4006	1-12	HEF4049	57	HEF4516	127	N7403N	14	N7447AN	13	N74125N	37	N74196N	135	N74LS33N	35	N74LS145N	138	N74LS277N	117	LM319N	34	LM319N	34	UA7815CU	97	UA7815CU	97						
HEF4007	22	HEF4050	57	HEF4517	478	N7404AN	16	N7448AN	92	N74126N	38	N74196N	122	N74LS37N	35	N74LS155N	93	N74LS261N	321	LM330N	78	LM330N	78	UA7812CU	97	UA7812CU	97						
HEF4008	1-00	HEF4051	87	HEF4518	118	N7405N	16	N7450N	14	N74127N	38	N74221N	31	N74LS38N	35	N74LS156N	93	N74LS266N	64	LM338N	104	LM338N	104	UA7815CU	97	UA7815CU	97						
HEF4011	22	HEF4052	90	HEF4519	69	N7406N	32	N7451N	14	N74145N	57	N74279N	61	N74LS40N	77	N74LS167N	93	N74LS273N	140	LM381AN	198	LM381AN	198	UA78L05CS	38	UA78L05CS	38						
HEF4012	22	HEF4053	90	HEF4520	118	N7407N	16	N7452N	14	N74147N	58	N74282N	60	N74LS42N	60	N74LS168N	97	N74LS274N	117	LM393N	156	LM393N	156	UA78L12CS	38	UA78L12CS	38						
HEF4013	57	HEF4066	62	HEF4521	235	N7408N	68	N7453N	16	N74148N	58	N74385N	59	N74LS51N	27	N74LS169N	129	N74LS290N	117	MC3403P	156	MC3403P	156	UA78L15CS	38	UA78L15CS	38						
HEF4014	1-05	HEF4067	475	HEF4526	124	N7409N	16	N7456N	14	N74150N	51	N74386N	59	N74LS54N	27	N74LS161N	117	N74LS293N	119	NE531T	131	NE531T	131										
HEF4015	1-00	HEF4088	22	HEF4532	150	N7410N	14	N7470N	28	N74151N	46	N74387N	59	N74LS55N	27	N74LS162N	144	N74LS298N	149	NE538T	259	NE538T	259										
HEF4016	1-12	HEF4089	57	HEF4533	638	N7411N	14	N7471N	28	N74152N	46	N74388N	59	N74LS57N	39	N74LS163N	144	N74LS299N	149	NE568N	28	NE568N	28										
HEF4017	1-00	HEF4070	22	HEF4539	129	N74121N	14	N7473N	28	N74154N	91	N74389N	59	N74LS57N	44	N74LS164N	119	N74LS366N	121	NE568N	66	NE568N	66										
HEF4018	1-00	HEF4071	23	HEF4543	194	N74131N	23	N7474N	24	N74155N	24	N74389N	46	N74LS76N	46	N74LS170N	220	N74LS367N	121	NE566N	171	NE566N	171										
HEF4019	58	HEF4072	23	HEF4555	96	N74141N	34	N7475N	34	N74156N	46	74LS		N74LS78N	39	N74LS173N	132	N74LS368N	121	NE570N	485	NE570N	485										
HEF4020	1-12	HEF4073	23	HEF4556	98	N74146N	21	N7476N	30	N74157N	43	N74LS00N	19	N74LS83AN	106	N74LS174N	144	N74LS373N	173	NE571N	505	NE571N	505										
HEF4021	1-00	HEF4074	23	HEF4557	104	N74147N	21	N7477N	30	N74158N	43	N74LS01N	19	N74LS84N	104	N74LS175N	144	N74LS374N	173	NE572N	515	NE572N	515										
HEF4022	-03	HEF4076	130	HEF4585	122	N7420N	14	N7483N	63	N74160N	63	N74LS02N	19	N74LS86N	39	N74LS181N	306	N74LS375N	171	NE573N	515	NE573N	515										
HEF4023	22	HEF4077	22	HEF4724	214	N7421N	16	N7485N	80	N74161N	63	N74LS03N	19	N74LS90N	59	N74LS189N	307	N74LS378N	155	NE574N	515	NE574N	515										
HEF4024	78	HEF4078	23	HEF40039	11	N7425N	19	N7486N	25	N74162N	63	N74LS04N	27	N74LS92N	76	N74LS191N	317	N74LS386N	56	NE575N	515	NE575N	515										
HEF4025	22	HEF4079	23	HEF40098	9	N7426N	20	N7487N	40	N74163N	63	N74LS05N	27	N74LS93N	76	N74LS192N	317	N74LS387N	155	NE576N	515	NE576N	515										
HEF4026	2-44	HEF4082	23	HEF40106	76	N7427N	20	N7489N	57	N74164N	86	N74LS06N	27	N74LS95N	82	N74LS193N	317	N74LS388N	155	NE577N	515	NE577N	515										
HEF4027	57	HEF4085	80	HEF40180	149	N7428N	23	N7492N	40	N74165N	86	N74LS07N	27	N74LS96N	126	N74LS194N	161	N74LS389N	155	NE578N	515	NE578N	515										
HEF4028	89	HEF4086	80	HEF40161	149	N7430N	14	N7493N	40	N74166N	86	N74LS10N	19	N74LS97N	41	N74LS195AN	119	N74LS390N	156	NE579N	515	NE579N	515										
HEF4029	113	HEF4093	65	HEF40162	149	N7432N	20	N7494N	57	N74170N	122	N74LS11N	26	N74LS98N	45	N74LS196N	132	N74LS391N	156	NE580N	515	NE580N	515										
HEF4030	518	HEF4094	219	HEF40163	149	N7433N	21	N7495AN	57	N74171N	122	N74LS12N	26	N74LS99N	45	N74LS197N	132	N74LS392N	156	NE581N	515	NE581N	515										
HEF4031	2-50	HEF4104	208	HEF40174	149	N7437N	21	N7496N	57	N74173N	122	N74LS13N	45	N74LS100N	45	N74LS198N	132	N74LS393N	156	NE582N	515	NE582N	515										
HEF4035	138	HEF4502	114	HEF40175	149	N7438N	21	N74100N	92	N74180N	55	N74LS14N	45	N74LS101N	45	N74LS199N	132	N74LS394N	156	NE583N	515	NE583N	515										
HEF4040	107	HEF4505	714	HEF40192	149	N7439N	30	N74107N	26	N74180N	57	N74LS15N	45	N74LS102N	45	N74LS200N	132	N74LS395N	156	NE584N	515	NE584N	515										
HEF4041	89	HEF4506	210	HEF40193	175	N7440N	30	N74108N	45	N74181N	205	N74LS16N	45	N74LS103N	45	N74LS201N	132	N74LS396N	156	NE585N	515	NE585N	515										
HEF4042	83	HEF4510	131	HEF40194	149	N7442N	51	N74116N	45	N74182N	51	N74LS17N	45	N74LS104N	45	N74LS202N	132	N74LS397N	156	NE586N	515	NE586N	515										
HEF4043	100	HEF4511	157	HEF40195	149	N7443N	92	N74121N	28	N74182N	91	N74LS18N	45	N74LS105N	45	N74LS203N	132	N74LS398N	156	NE587N	515	NE587N	515										

Zener Diodes		Voltage Regulators	
400mV CMVT-C33	LM340	LM3090AN	41
BZ78/BZX79	LM340	LM3090AN	41
1-Voltage	9	LM3090AN	41

Plessey I/C's	
SL440	331
SL445	128
SL610	245
SL611	245
SL620	369
SL621	369
SL622	369
SL816	369
SL817	

CASES - Boss Industrial Mouldings				OPTO ELECTRONICS				SWITCHES				SEMICONDUCTORS																															
Small Desk Console - Boss Industrial Mouldings				Light Emitting Diodes, Individual				Miniature Toggle - Honeywell				Diodes																															
Slope Front Console, Recessed Top				.125" (3mm) Red				SPDT				IN914				8C182L				12																							
ABS Base, C/W Brass Bushes, In Orange				Green				SPDT C/O/H				61 SW 8A1011				IN4001				5				8C184				12															
1mm Aluminium Top Panel Finished Grey				Yellow				SPDT Double Bias To Centre				87 SW 8A1021				IN4004				7				8C212L				12															
Order Code				LED3 Clip				SPDT Single Bias To Centre				90 SW 8A1051				IN4007				9				8C214				12															
W161, D96, H39 (57)				214				Case B1M1005 OR				SPDT Bias				84 SW 8A1061				IN5402				15				8C214L				12											
W215, D130, H47 (73)				308				Case B1M1006 OR				DPDT				99 SW 8A2011				IN2218A				31				8C547				12											
Plastic Boxes - Boss Industrial Mouldings				2" (5mm) Red				16 OCY94A				DPDT C/O/H				111 SW 8A2021				2N2369				21				8C548				12											
Moulded Box and Close Fitting Flanged Lid				Green				20 OCY96				DPDT Double Bias To Centre				123 SW 8A2041				2N2646				46				8C549				12											
ABS Box, C-W Brass Bushes, and Lid In Orange				Yellow				5 LED5 Clip				DPDT Single Bias To Centre				123 SW 8A2051				2N2926G				13				8C557				12											
Order Code				Photoreistors				SP				Push To Make, Momentary				62 SW 8531				2N3053				19				8C558				12											
L112 W62 D31				99				Case B1M2003 OR				SP Push To Break, Momentary				62 SW 8533				2N3054				19				8C559				12											
L150 W60 D50				131				Case B1M2005 OR												2N3055				55				8C560				12											
L190 W110 D60				223																2N3055				55				8C561				12											
Plastic Boxes with Metal Lids				Phototransistors				SP												2N3055				55				8C562				12											
Recessed Top Box				QCP71				220 QCP71												2N3055				55				8C563				12											
ABS Base, C/W Brass Bushes, In Orange				BPX25				195 BPX25												2N3055				55				8C564				12											
1mm Aluminium Top Panel Finished Grey				BPX29				195 BPX29												2N3055				55				8C565				12											
Order Code				Photocoupler				FCD820				165 FCD820												2N3055				55				8C566				12							
L85 W56 D29				112				Case B1M4003 OR												2N3055				55				8C567				12											
L111 W71 D42				150				Case B1M4004 OR												2N3055				55				8C568				12											
L161 W96 D53				208				Case B1M4005 OR												2N3055				55				8C569				12											
Diecast Boxes				D.I.L. Sockets				8 Pin Low Profile Socket Tin				12 DIL SKT 8												2N3055				55				8C570				12							
Diecast Box and Flanged Lid				14 Pin Low Profile Socket Tin				12 DIL SKT 14																2N3055				55				8C571				12							
Aluminium Box and Lid in Natural Finish				16 Pin Low Profile Socket Tin				10 DIL SKT 16																2N3055				55				8C572				12							
Order Code				Heatsinks				Individual Type for 1 x T05 50° C/W				12 Sink 5F												2N3055				55				8C573				12							
L113 W63 D31				124				Case B1M5003 NA				Individual Type for 1 x T066 105° C/W				20 Sink TV2												2N3055				55				8C574				12			
L152 W82 D50				215				Case B1M5005 NA				Individual Type for 1 x T03 7.2° C/W				20 Sink TV3												2N3055				55				8C575				12			
L192 W113 D61				334				Case B1M5006 NA				Individual Type for 1 x T0126 17° C/W				20 Sink TV5												2N3055				55				8C576				12			
Small Desk Consoles				Individual Type for 1 x T0220 17° C/W				20 Sink TV5																2N3055				55				8C577				12							
Slope Front Console, Recessed Top																								2N3055				55				8C578				12							
ABS Base, C/W Brass Bushes, In Orange																								2N3055				55				8C579				12							
1mm Aluminium Top Panel Finished Grey																								2N3055				55				8C580				12							
Ventilation Slots In Base																								2N3055				55				8C581				12							
Order Code																								2N3055				55				8C582				12							
W105 D143 H32 (56)				236				Case B1M6005 OR																2N3055				55				8C583				12							
W170 D143 H32 (56)				312				Case B1M6006 OR																2N3055				55				8C584				12							
W170 D214 H32 (87)				431				Case B1M6007 OR																2N3055				55				8C585				12							
P.C.B. Components				Dato Pen, Blue Ink, Slow Drying				98 Pen 33PC																2N3055				55				8C586				12							

FULL SPEC KIT TELETEXT DECODER

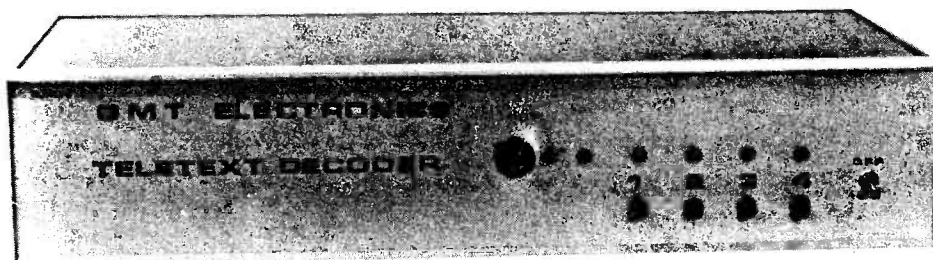

- STATE OF THE ART L.S.I. CIRCUITS
- DOUBLE HEIGHT CHARACTER SELECTABLE FOR LEGIBILITY
- CHARACTER ROUNDING - EFFECTIVELY DOUBLES DEFINITION
- ULTRASONIC REMOTE CONTROL
- HIGH QUALITY THROUGH PLATED P.C.B.
- ALL I.C. MOUNTED ON SOCKETS
- PREALIGNED UHF/IF MODULES
- NEEDS NO INTERNAL CONNECTION TO THE TELEVISION SET
- SIZE 430mm x 90mm x 220mm
- SUPPLY 240v 50Hz 35w
- NEW *TOUCH CONTROL KEYPAD* NEW

INCLUDES TUNER, P.S.U., DECODER, REMOTE KEYBOARD, P.A.L. ENCODER, U.H.F. MODULATOR CASE WITH SCREENED AND PUNCHED FRONT PANEL.

— £189.90 inc VAT. P & P £3.00.


FULL TELETEXT MANUAL IF BOUGHT SEPARATELY — £2.50 P & P £0.50.

P.C.B.'S AND L.S.I. I.C.'S NOT SOLD SEPARATE FROM KITS.

P & P INCLUDES CARRIAGE, PACKING AND INSURANCE

SEE LAST MONTHS ADVERTISEMENT FOR COMPONENT RANGE AND PRICES


F.E.T. POWER AMPLIFIER

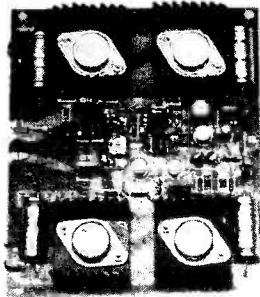

Bring your HI-FI up to date. Available now is a 100 watt audio amplifier using POWER MOSFETS. The POWER MOSFET has several advantages over bipolar transistors. It has good frequency response, no carrier storage delay, thermal stability, no secondary breakdown, and high input impedance. The MOSFET Amplifier has been designed to deliver a continuous power output of 100 watts with full heatsinking into 8 ohms from 5 Hz to 100 kHz with no more than 0.01% total harmonic distortion, which is about a tenfold improvement on ordinary bipolar techniques. The high output impedance and thermal stability of the MOSFET reduces the size of the total circuit by about 30%. The kit does not include a case.

POWER MOSFET AMPLIFIER MODULE £27.50

DOPPLER RADAR ALARM

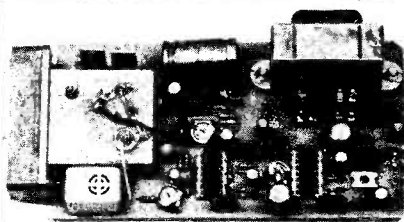


Do your goodies need protecting? No need to run miles of wire, and hack window and door frames to pieces. Just build a Doppler Radar Alarm kit. It can be mains or battery operated (external battery required), and is triggered by any movement in its detection area. It incorporates an arming delay - to enable you to leave its detection field safely, and a trigger delay (0 to 45 seconds), so you can catch the thief red handed without a prior warning having been given.

The unit provides a 12 volt output, normally high (low on alarm), to supply an external remote relay, which is not supplied. The unit has an integral buzzer to give an indication when the unit is being armed, and when triggering is complete.

The unit comes complete with a suitable case.

DOPPLER RADAR ALARM £39.50

1 AMP P.S.U.

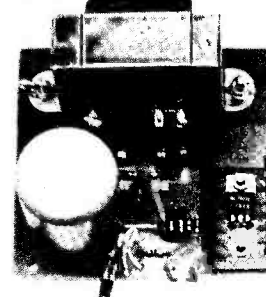

Need a one amp power supply at five volts or twelve volts? Fed up with lash ups? Here is a basic 'no frills' 1 amp P.S.U. kit, based on the well known ua7800 series three terminal regulators. When assembled, all components, including the transformers, are mounted on the printed circuit board. Use the module as a bench power supply, or as part of a piece of equipment.




1 AMP PSU - 5 VOLTS £6.00




1 AMP PSU - 12 VOLTS £7.50


PCB FOIL PATTERNS

Shown below are the foil patterns for the months projects. The Black Hole PCB is shown overleaf. The Infra-Red remote control project will be concluded next issue — at which time details of the transmitter circuit and PCB will be given.

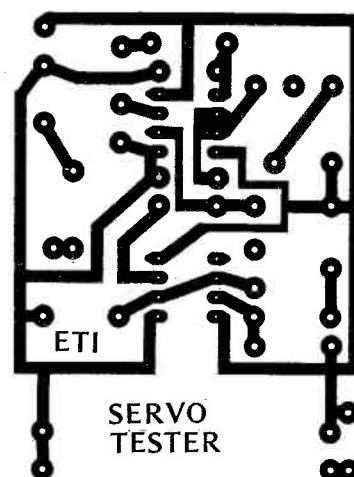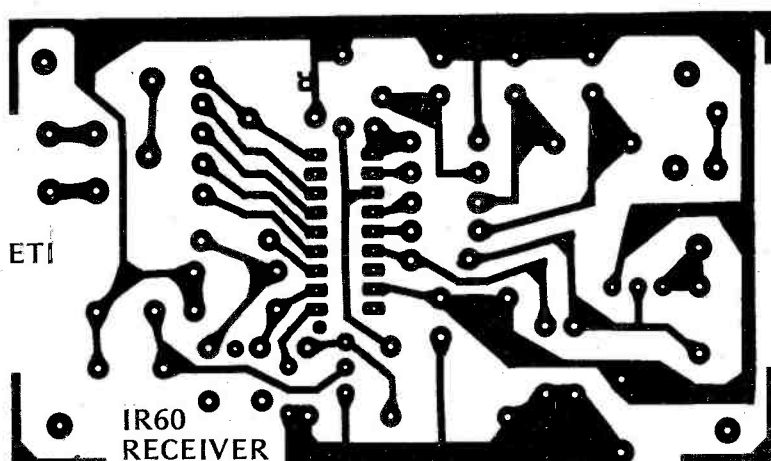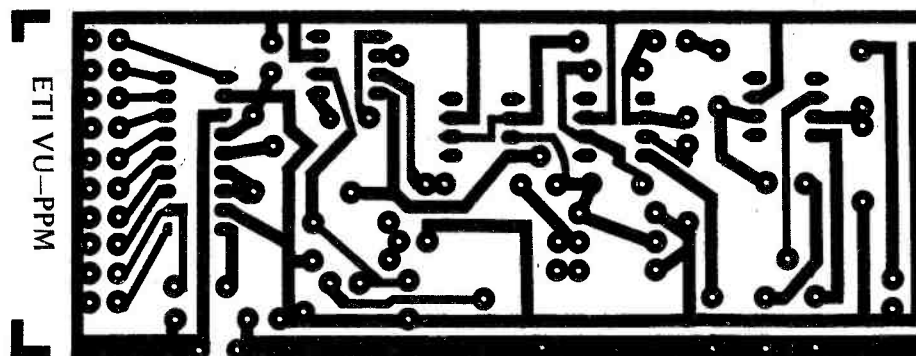Companies producing boards of ETI projects should note that both the Chorus Machine and Voltage Controlled Filter PCBs are copyrighted to Powertran and Digisound respectively — and may not thus be reproduced other than by individuals for their own usage in a one-off basis.



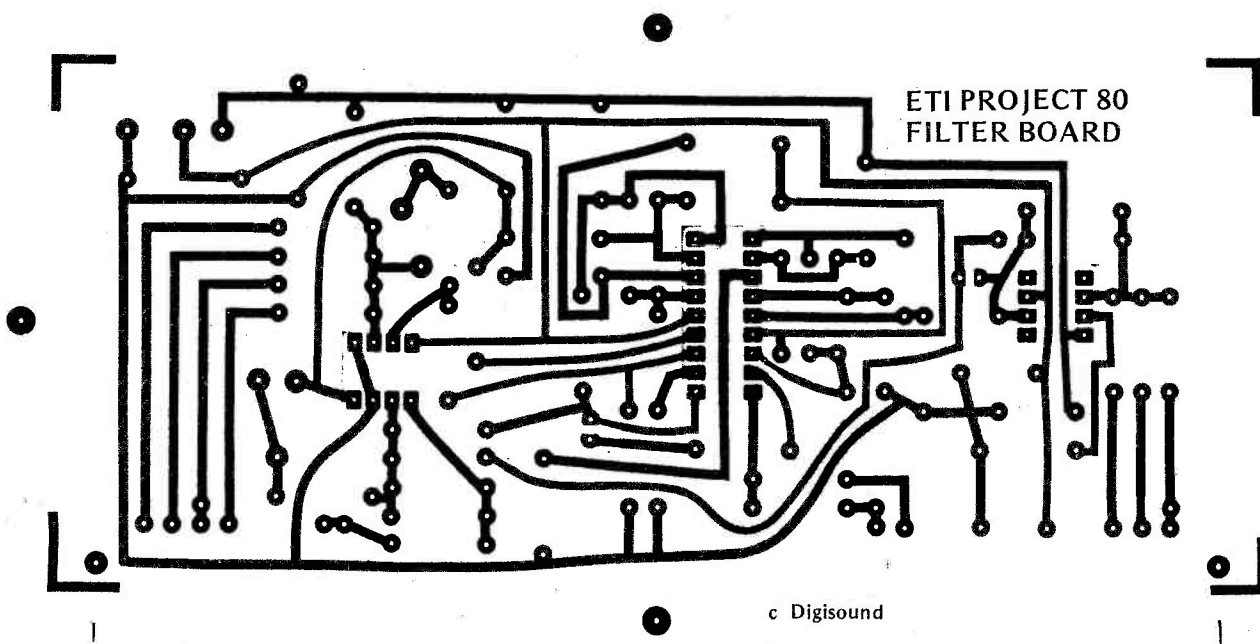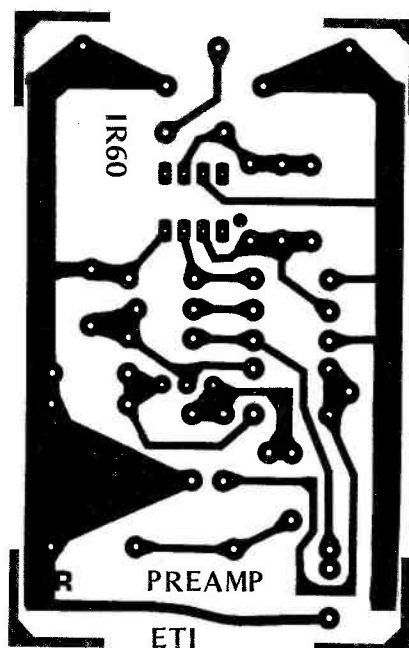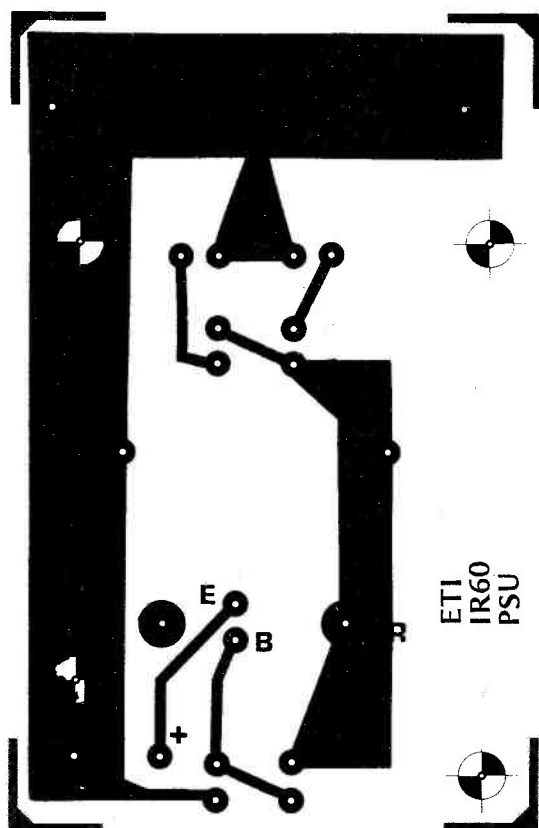

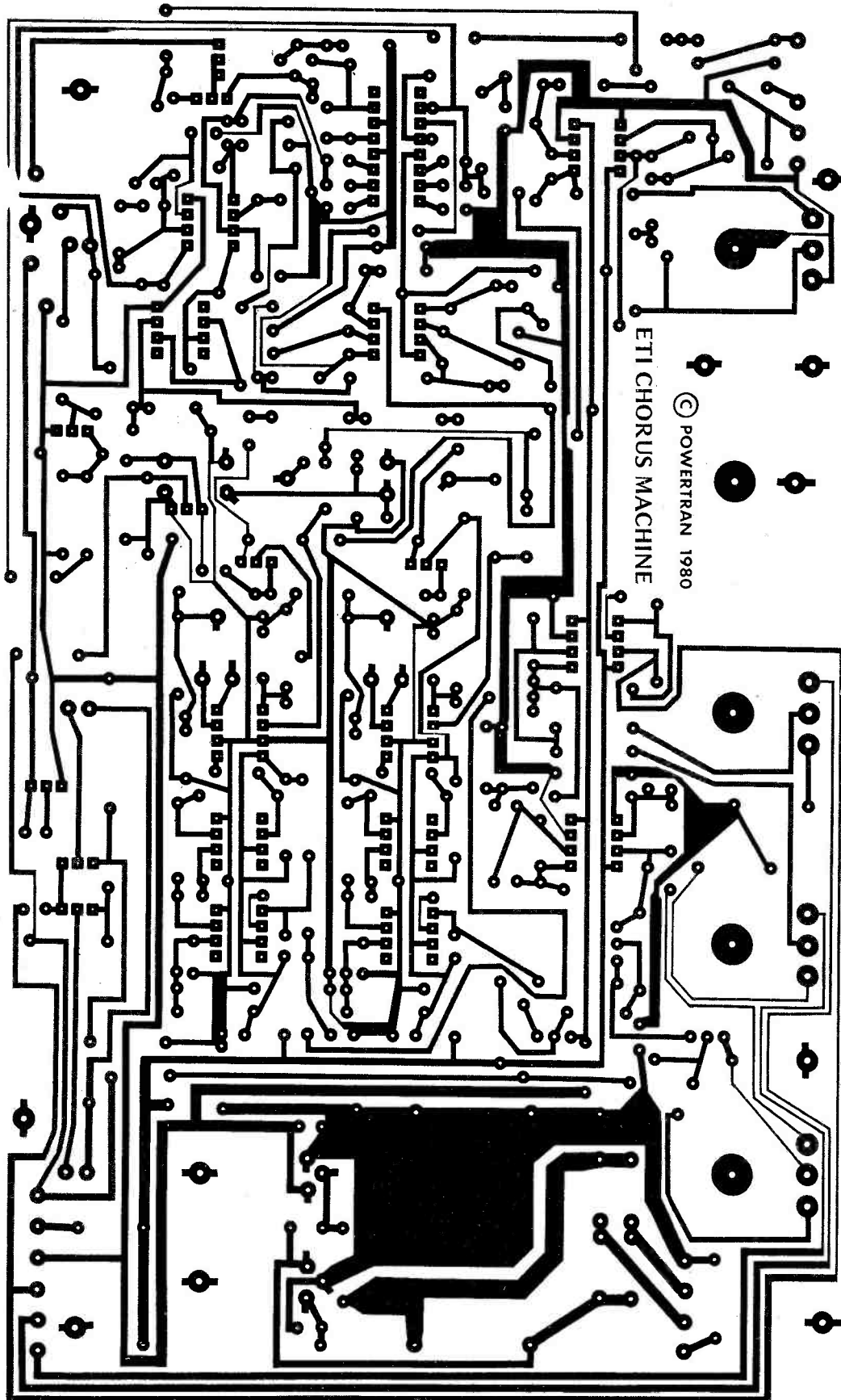

AUDIO AND TEST EQUIPMENT CENTRE

Telephone your order with Access and Barclaycards or send cheque with order.



RETAIL
MAIL ORDER
EXPORT
ALL PRICES
INCLUDE VAT



LONDON'S TEST GEAR CENTRE

OPEN 6 DAYS A WEEK 9 am-6 pm

SCOPES—(UK P/P £2.50 ea.) ★TRIO SCOPES NOW AVAILABLE

HAMEG	
HM 307-3 10MHz single beam with Component Tester	170.00
HM 312-8 20MHz dual trace	287.50
HM 412-4 20MHz sweep delay dual trace	402.50
Super 10 10MHz dual trace	239.00
SINCLAIR 10MHz Miniscope P/S 4.00, Nicads 7.95, Case 8.80	152.50
PROBES x1/x10 12.95, x10 10.50, x1 8.50, x100 16.95	

FREQUENCY COUNTERS

OPTO 7010 9 digit, 600MHz Portable, 0.1Hz Resolution with NI-CAOS	139.95
MAX 50 50MHz 6 digit pocket counter	61.00
MAX 100 100MHz 8 digit portable counter	88.75
MAX 550 550MHz 6 digit pocket counter	106.00
500 MHz Prescaler for max 50 or max 100	40.00
PFM200 Sinclair 200MHz Pocket Counter 8 digit	54.50
OPTIONAL P/S 4.00, Connector Pack PFM200	£9.95
C7216R 10MHz, 8 Digit Panel Mounting	55.80
C7216RP 150MHz version	88.25

DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit LED	58.50
PDM35 Sinclair Pocket 3 1/2 digit LED	36.50
DM350 Sinclair 3 1/2 digit with 10 amp range	78.50
DM450 Sinclair 4 1/2 digit	107.95
(30kV Probes 15.95, P/S 4.00, DM Nicads 7.95, Cases 8.80)	
M1200 Bench Portable 3 1/2 digit LED, Resolution 1µA/0.1mv/0.01ohm	87.50
LMM100 Lascar 3 1/2 digit 2A LCD Bench 0.1%	66.85
LM2001 Lascar 3 1/2 digit 2A LCD Hand 0.1%	51.70
LM200 Lascar 3 1/2 digit 2A LCD Economy 0.5%	43.40

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges (TM3 AC volts only), some with AC current, etc.★

TM11 incredible 120 Range Electronic Multi-meter★	161.00
TM3B AC Micro voltmeter 3MHz > 4 Megohm (large scale)	152.95
TM3A AC Micro voltmeter 3MHz > 4 Megohm	138.00
360TR 100k/volt★	34.95
7080 20k/volt	26.95
7081 50k/volt	19.95
NH55 2kV	66.85
NH56 20k/volt	10.95
LT101 1k/volt	5.95
YN360TR 20k/volt	13.95
AT205 50k/volt	24.95
AT1 2k/volt	7.95
TMK500 30/volt	22.95
AT1020 20/volt	16.95
AT2050 50k/volt	28.50
AT210 100k/volt★	29.95

AVO 8s and a large range of replacement tests leads in stock

GENERAL EQUIPMENT


SE250 Signal Injector	4.95
TE7 Signal Tracer AF/RF	9.95
SWR50 SWR/Power Meter	13.95
DR510 36 Value Resis. Box	3.95
RP124 0/24v 0/1 amp P/S Stabilised	42.00
RP324 3 amp version	54.00
RP230N 0/30v 0/1 amp. P/S Twin Meters	85.00
TR1000 Transistor checker in/out circuit	11.95
MOD63 Signal injector	8.65
C3022 Transistor/Diode Checker	19.95
3101 Clamp Meter 0/1 K ohm, 0/150/300/600 AC volts, 0/300 amp	32.95
SWR40/5 SWR & FS Meter	10.50
SWR10 SWR Meter	10.95
MS319 2x100 Watt Audio Watt Meter	13.95
500V Megohmmeter 500 Megohms	51.00
2 1/2" Amp Variable transformer	21.95

DRILLS AND DRILL KITS

9 to 12 volt Operated, 1/4" max.	
SMALL DRILL with collits	6.85
MEDIUM DRILL with 3 collits	9.90
SMALL DRILL with 20 drills/tools	13.95
MEDIUM DRILL with 20 drills/tools	16.95
MAINS Elm. meters	9.95
VARIABLE Speed	13.95
12 volt 1/4" Heavy Duty Drill	12.50
MAINS DRILL with tool set	19.95

TV SOUND

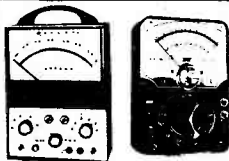
High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. 6.50 (UK P&P 50p) As reviewed by 'Popular Hi-Fi', July '79



TM11 TMK500

NEW BULK PURCHASE
GEC 10+10 watt
Tuner/Amplifier.
MW/LW/SW/Stereo FM. Supplied
as two easy to connect units. £21.95 P&P £1.50

WE SELL
Kef, Seas, Audax, Fane,
Goodmans, Motorola
Pearless
Speakers/Kits etc
Also PA Equipment, etc

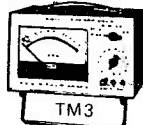

TM3

CALL IN AND SEE FOR YOURSELF

PRICES CORRECT AT 1/4/80


AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724 3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W.1.

FREE
CATALOGUE

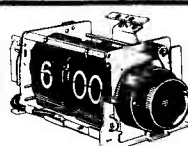SEND STAMPED
ADDRESS ENVELOPE
(MIN. 9 1/2 x 6 1/2")
FOR YOUR COPY NOW



MECHANISM
WITH ALARM



Assemble
it in an evening!
MECHANISM & CASE
Inc. assembly instructions

DIGITAL 24 HOUR CLOCK

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS

AS USED IN BRAUN
DIGITAL CLOCKS

£5.00

£6.99

THREE FOR £13.50

MECHANISMS 10 FOR £39. 100 FOR £300

- AC MAINS
 - SIZE 6 1/2 x 2 3/4 x 2 3/4
- Your receipt is a 2-year guarantee

HALF PRICE OFFER

**HENRY'S
Radio**

HENRY'S RADIO
404 EDGWARE ROAD,
LONDON W2 1ED

EXPORT
ENQUIRIES
INVITED
01-723 1008



DELIVERY
FROM STOCK

VMOS POWERFETS

VMP4 (25W, 10dB at 200MHz. min.)	£12.50
VN67AF (15W, 2A, 2A, TO202)	75p.
VN10KM (1W, 1/4A, TO92)	55p
BD512 (P-chan. 10W, 1 1/4A, TO202/3)	85p. 10 + 80p
Heat clips TO202 12p, TO92 8p. VN/VM Design Cat.	20p.
2FK134/2FK49 (100W, 140V, 7A)	£6 each

TLO81CP 29p, 10 + 27p, 25 + 25p. TLO82CP 55p, 10 + 50p, 25 + 45p

CA3026	70p	LM3900	43/2
CA3080E	70p	709	15p
CA3140E	38p	710	25p
MC3401	30p	733	50p
DAC08	250p	741	18p
DM2502	555p	78L05/12	29p
NE529	145p	2102	80p
08 + 2502 +		FX309 (superior	
529 = 2µADC £9		delta mod)	£7.50
+ LSTTL/CMOS			
SD5 32 (µ power op amp)			30p

Scope trace doubler P.C.B. D.C. - 10MHz, c/w with controls and manual. Built £9.95
VCA (0 → 90dB, THD <0.1%, S.R. 10V/µS) all components plus circuit £2.25

Brief data on everything in new lists. S.A.E.

P&P30p. Mail order only. Prices inc. Tel. 01-800 6667

J. W. RIMMER 367 GREEN LANES
LONDON N4 1DY

E PROMS

Surplus to requirements

2708 £6.00 each

4716 £25.00 each

Parts sent by return.

Programming Service if required.

Please add VAT (15%) and 30p P&P

BARINGLOCK LTD.

31 Ashdown Avenue

Saltdean, Brighton

Telephone: 01-686 1922

PROTON ELECTRONICS

SAME-DAY SERVICE - NOTE NEW ADDRESS

SHARP ELB140 CREDIT CARD CALCULATOR 3mm THICK E15

BC107	7p	BC158	8p	BC328	14p	BD131	33p	BFY51	17p
BC108	7p	BC159	8p	BC337	15p	BD132	33p	TIP30	38p
BC109	7p	BC182	7p	BC338	14p	BD135	38p	2N2904	19p
BC147	7p	BC212	8p	BC557	8p	BD136	38p	2N2905	19p
BC148	7p	BC213	8p	BCY70	12p	BD139	34p	2N2907	19p
BC149	7p	ZTX214	8p	BCY71	12p	BD140	34p	2N3054	49p
BC157	8p	BC327	16p	BCY72	12p	BFY50	17p	2N3055	40p

555	19p	LM3900	48p	7805 5V Regulator	TO3100p	IN4001	4p
741	15p	TBA810	95p	W04 1A 400V Bridge	30p	IN4004/	65p
TLO82	60p	MC1310P	110p	Led Green or Yellow 0.2"	11p	IN4007	7p
CA3046	55p	MC1458	40p	Led Red 0.2"	10p	IN914	3p
		709	29p	741 Metal Can 8 Dill	14p	IN4148	2p

SPECIAL OFFER: 741 Metal Can 10 for 120p

Resistors 0.5W 51. Carbon Film E12 Values 100-10MΩ 1p. Polyester Caps 0.01-0.1µ-0.1µ 3p; 15, 22, 33 5p; 47 8p; 68 8p; 1µ 10p. Electrolytics All 25V 4.7µ-22µ 4p; 47-68 6p; 100 8p; 220, 330 12p; 470 16p. 1000 PC Mount 20p; 6800 65p; 10,000 95p; Panel Mounting Neons 20V 20p.

All Full Spec. Guaranteed. C.W.O. P. & P. 30p. Mail Order Only.

70 BRIGGS FOLD ROAD, EGERTON
BOLTON, BL7 9SQ

Greenbank

Greenbank Electronics
(Dept. T5E) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel: 051-645 3391)

UV EPROM ERASERS



Two easy to use units designed for both the professional and amateur UV-EPROM user.

Features:

- Can erase up to 14 proms.
- Special short wave ultraviolet tube.
- Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life).
- Sliding tray carries proms on conductive foam.
- Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
- "Mains on" and "Tube On" indicators.
- Smart textured case.
- Complete instructions supplied.

Supplied complete with mains plug and flex.

Model UV141. Price £77.70

Also available without timer as

Model UV140. Price £61.20

PROM WASHING SERVICE. 50p each prom

COMPUTER BOARDS

The following is an extract from our leaflet ref. 'MP4', which is available free on request (a 9" x 6" SAE helps, but is not essential). See Microprocessor section to the right for board prices.

For many people the wide choice of micro-processors now available presents a difficult choice. To understand any particular microprocessor in depth a development system is almost essential, however in the past to understand more than one several separate development systems have had to be purchased.

The reason that separate systems, one for each processor, have been necessary is due to the fact that individual microprocessors have their own individual features: in one case to access memory a separate read and write strobe is required, in another a 'read/write' line is used in combination with a combined strobe called 'valid memory address and phi-2'. With some processors, the same address bus can be used for both memory and input/output ports, under the control of a 'memory request' or an 'input/output request' control line.

Naturally, if a development system takes advantage of any of the particular unique features of any particular microprocessor, this makes it more difficult to graft some other unrelated microprocessor onto the same bus at a later date. A Universal Micro System provides a basic bus structure on which any one micro-processor can be connected. The system uses a CPU (Central Processor Unit) card which is separate from the rest of the system, and this allows the same memory and interfaces to be retained when a different MPU is used.

The basic system bus consists of data and address buses together with read and write strobes. By locating the data input (Keyboard) and output (VDU) in the memory space then such chips as the 8080/8085 family, which normally use input/output ports, can now be used without any fundamental change to the bus (and as a bonus, users of these MPU's have all the ports entirely free for their own purposes).

The range of p.c.b.s. includes boards to implement a memory-mapped VDU, cassette interface, keyboard interface, PROM programmer, and a number of RAM and ROM cards. All the cards are of International Size 114 x 203 mm (4 1/2" x 8") except for the larger power PSU A power supply card. This latter card is sized so that it can be bolted to the side of a standard 4" chassis module which is then compatible with the other cards. The cards have a standard 43-way edge connector, with one position used for polarisation.

We do not propose to defend the (relatively) small number of bus connections (42), against such standards as the 'S100' 100-pin bus. The S-100 bus, as it originated in America, is bigger and better. It's more expensive. In the same way, a Ford 'Granada' is bigger and better than a Ford 'Cortina', but it doesn't mean a Cortina isn't good value for money.

The International Size modules are a variety of systems. These modules are the firm 'R.S. Systems'.

Low-cost commercial quality computer back board, 13 1/2" x 4 1/2" approx, for the International Standard (114x203mm) cards. Although intended for the 86-way double sided connector, it can be used with the 43-way connector specified for the computer boards we advertise. (Pin 37 is used for polarisation.)

Takes up to 13 cards on 1" centres, and provides for 4 power rails, 58 parallel address/data etc. bus lines and 3 'daisy chains'.

Expo glass, tinned, price £11.50 'ISB-1.1'.

More details in our free leaflet 'ISB-1.1'.

Further details on request

Further details on request

Further details on request

Further details on request

TERMS, VAT, CWO. Cheques etc payable to Greenbank Electronics. Add VAT at all prices at 15% except where stated otherwise. Post etc: UK 35p (+5p VAT = 40p) per order. Export: NO VAT but add 35p (Eire), 75p (Europe) and £2.50 elsewhere. Access, Barclaycard, Visa, telephoned orders accepted. (Polys, universities, govt depts, etc can telephone their orders for immediate despatch on account.)

CMOS

These cut prices for Amateur Users and Export. Note: industrial users - quantity prices available. Mostly Motorola, RCA

4000 15p	4042 75p	4089 1.50	4419 1.27
4001 17p	4043 94p	4093 63p	4422 1.50
4002 17p	4044 90p	4094 1.90	4431 TBA
4006 1.05	4045 1.45	4095 1.05	4433 1.11.32
4007 1.8p	4046 1.28	4096 1.05	4437 1.25
4008 87p	4047 87p	4097 1.22	4438 91p
4009 50p	4048 59p	4098 1.10	4451 1.26.67
4010 50p	4049 48p	4099 1.45	4452 TBA
4011 18p	4050 48p	4099 N/S	4453 1.19
4012 18p	4051 72p	4100 1.25	4454 1.09
4013 42p	4052 72p	4101 1.61	4455 1.38.7
4014 86p	4053 72p	4102 1.22	4456 1.19
4015 89p	4054 1.10	4103 1.22	4457 1.38.7
4016 45p	4055 1.28	4104 1.09	4458 1.19
4017 89p	4056 1.34	4105 1.06	4459 1.38.7
4018 89p	4057 1.25.70	4106 61p	4460 1.19
4019 48p	4058 1.48.00	4107 61p	4461 1.19
4020 91p	4059 1.15	4108 1.58	4462 1.19
4021 91p	4060 1.15	4109 1.02	4463 1.19
4022 86p	4061 1.10	4110 1.02	4464 1.19
4023 20p	4062 1.09	4111 1.02	4465 1.19
4024 56p	4063 1.09	4112 1.02	4466 1.19
4025 19p	4064 N/S	4113 1.02	4467 1.19
4026 1.80	4065 57p	4114 1.02	4468 1.19
4027 45p	4066 57p	4115 1.02	4469 1.19
4028 81p	4067 57p	4116 1.02	4470 1.19
4029 99p	4068 22p	4117 1.02	4471 1.19
4030 58p	4069 20p	4118 1.02	4472 1.19
4031 22.05	4070 23p	4119 1.02	4473 1.19
4032 1.00	4071 21p	4120 1.02	4474 1.19
4033 1.45	4072 21p	4121 1.02	4475 1.19
4034 1.96	4073 21p	4122 1.02	4476 1.19
4035 1.96	4074 21p	4123 1.02	4477 1.19
4036 22.45	4075 21p	4124 1.02	4478 1.19
4037 1.08	4076 21p	4125 1.02	4479 1.19
4038 1.08	4077 21p	4126 1.02	4480 1.19
4039 22.45	4078 21p	4127 1.02	4481 1.19
4040 1.05	4079 21p	4128 1.02	4482 1.19
4041 80p	4080 75p	4129 1.02	4483 1.19

74C

74C00 24p	74C01 24p	74C02 24p	74C03 24p
74C04 24p	74C05 24p	74C06 24p	74C07 24p
74C08 24p	74C09 24p	74C10 24p	74C11 24p
74C12 24p	74C13 24p	74C14 24p	74C15 24p
74C16 24p	74C17 24p	74C18 24p	74C19 24p
74C20 24p	74C21 24p	74C22 24p	74C23 24p
74C24 24p	74C25 24p	74C26 24p	74C27 24p
74C28 24p	74C29 24p	74C30 24p	74C31 24p
74C32 24p	74C33 24p	74C34 24p	74C35 24p
74C36 24p	74C37 24p	74C38 24p	74C39 24p
74C40 24p	74C41 24p	74C42 24p	74C43 24p
74C44 24p	74C45 24p	74C46 24p	74C47 24p
74C48 24p	74C49 24p	74C50 24p	74C51 24p
74C52 24p	74C53 24p	74C54 24p	74C55 24p
74C56 24p	74C57 24p	74C58 24p	74C59 24p
74C60 24p	74C61 24p	74C62 24p	74C63 24p
74C64 24p	74C65 24p	74C66 24p	74C67 24p
74C68 24p	74C69 24p	74C70 24p	74C71 24p
74C72 24p	74C73 24p	74C74 24p	74C75 24p
74C76 24p	74C77 24p	74C78 24p	74C79 24p
74C80 24p	74C81 24p	74C82 24p	74C83 24p
74C84 24p	74C85 24p	74C86 24p	74C87 24p
74C88 24p	74C89 24p	74C90 24p	74C91 24p
74C92 24p	74C93 24p	74C94 24p	74C95 24p
74C96 24p	74C97 24p	74C98 24p	74C99 24p

MODULATORS

UM111: 636 UHF Ch.36	UM112: 636 UHF Ch.36	UM113: 636 UHF Ch.36	UM114: 636 UHF Ch.36
UM115: 636 UHF Ch.36	UM116: 636 UHF Ch.36	UM117: 636 UHF Ch.36	UM118: 636 UHF Ch.36
UM119: 636 UHF Ch.36	UM120: 636 UHF Ch.36	UM121: 636 UHF Ch.36	UM122: 636 UHF Ch.36
UM123: 636 UHF Ch.36	UM124: 636 UHF Ch.36	UM125: 636 UHF Ch.36	UM126: 636 UHF Ch.36
UM127: 636 UHF Ch.36	UM128: 636 UHF Ch.36	UM129: 636 UHF Ch.36	UM130: 636 UHF Ch.36
UM131: 636 UHF Ch.36	UM132: 636 UHF Ch.36	UM133: 636 UHF Ch.36	UM134: 636 UHF Ch.36
UM135: 636 UHF Ch.36	UM136: 636 UHF Ch.36	UM137: 636 UHF Ch.36	UM138: 636 UHF Ch.36
UM139: 636 UHF Ch.36	UM140: 636 UHF Ch.36	UM141: 636 UHF Ch.36	UM142: 636 UHF Ch.36
UM143: 636 UHF Ch.36	UM144: 636 UHF Ch.36	UM145: 636 UHF Ch.36	UM146: 636 UHF Ch.36
UM147: 636 UHF Ch.36	UM148: 636 UHF Ch.36	UM149: 636 UHF Ch.36	UM150: 636 UHF Ch.36
UM151: 636 UHF Ch.36	UM152: 636 UHF Ch.36	UM153: 636 UHF Ch.36	UM154: 636 UHF Ch.36
UM155: 636 UHF Ch.36	UM156: 636 UHF Ch.36	UM157: 636 UHF Ch.36	UM158: 636 UHF Ch.36
UM159: 636 UHF Ch.36	UM160: 636 UHF Ch.36	UM161: 636 UHF Ch.36	UM162: 636 UHF Ch.36
UM163: 636 UHF Ch.36	UM164: 636 UHF Ch.36	UM165: 636 UHF Ch.36	UM166: 636 UHF Ch.36
UM167: 636 UHF Ch.36	UM168: 636 UHF Ch.36	UM169: 636 UHF Ch.36	UM170: 636 UHF Ch.36
UM171: 636 UHF Ch.36	UM172: 636 UHF Ch.36	UM173: 636 UHF Ch.36	UM174: 636 UHF Ch.36
UM175: 636 UHF Ch.36	UM176: 636 UHF Ch.36	UM177: 636 UHF Ch.36	UM178: 636 UHF Ch.36
UM179: 636 UHF Ch.36	UM180: 636 UHF Ch.36	UM181: 636 UHF Ch.36	UM182: 636 UHF Ch.36
UM183: 636 UHF Ch.36	UM184: 636 UHF Ch.36	UM185: 636 UHF Ch.36	UM186: 636 UHF Ch.36
UM187: 636 UHF Ch.36	UM188: 636 UHF Ch.36	UM189: 636 UHF Ch.36	UM190: 636 UHF Ch.36
UM191: 636 UHF Ch.36	UM192: 636 UHF Ch.36	UM193: 636 UHF Ch.36	UM194: 636 UHF Ch.36
UM195: 636 UHF Ch.36	UM196: 636 UHF Ch.36	UM197: 636 UHF Ch.36	UM198: 636 UHF Ch.36
UM199: 636 UHF Ch.36	UM200: 636 UHF Ch.36	UM201: 636 UHF Ch.36	UM202: 636 UHF Ch.36
UM203: 636 UHF Ch.36	UM204: 636 UHF Ch.36	UM205: 636 UHF Ch.36	UM206: 636 UHF Ch.36
UM207: 636 UHF Ch.36	UM208: 636 UHF Ch.36	UM209: 636 UHF Ch.36	UM210: 636 UHF Ch.36
UM211: 636 UHF Ch.36	UM212: 636 UHF Ch.36	UM213: 636 UHF Ch.36	UM214: 636 UHF Ch.36
UM215: 636 UHF Ch.36	UM216: 636 UHF Ch.36	UM217: 636 UHF Ch.36	UM218: 636 UHF Ch.36
UM219: 636 UHF Ch.36	UM220: 636 UHF Ch.36	UM221: 636 UHF Ch.36	UM222: 636 UHF Ch.36
UM223: 636 UHF Ch.36	UM224: 636 UHF Ch.36	UM225: 636 UHF Ch.36	UM226: 636 UHF Ch.36
UM227: 636 UHF Ch.36	UM228: 636 UHF Ch.36	UM229: 636 UHF Ch.36	UM230: 636 UHF Ch.36
UM231: 636 UHF Ch.36	UM232: 636 UHF Ch.36	UM233: 636 UHF Ch.36	UM234: 636 UHF Ch.36
UM235: 636 UHF Ch.36	UM236: 636 UHF Ch.36	UM237: 636 UHF Ch.36	UM238: 636 UHF Ch.36
UM239: 636 UHF Ch.36	UM240: 636 UHF Ch.36	UM241: 636 UHF Ch.36	UM242: 636 UHF Ch.36
UM243: 636 UHF Ch.36	UM244: 636 UHF Ch.36	UM245: 636 UHF Ch.36	UM246: 636 UHF Ch.36
UM247: 636 UHF Ch.36	UM248: 636 UHF Ch.36	UM249: 636 UHF Ch.36	UM250: 636 UHF Ch.36
UM251: 636 UHF Ch.36	UM252: 636 UHF Ch.36	UM253: 636 UHF Ch.36	UM254: 636 UHF Ch.36
UM255: 636 UHF Ch.36	UM256: 636 UHF Ch.36	UM257: 636 UHF Ch.36	UM258: 636 UHF Ch.36
UM259: 636 UHF Ch.36	UM260: 636 UHF Ch.36	UM261: 636 UHF Ch.36	UM262: 636 UHF Ch.36
UM263: 636 UHF Ch.36	UM264: 636 UHF Ch.36	UM265: 636 UHF Ch.36	UM266: 636 UHF Ch.36
UM267: 636 UHF Ch.36	UM268: 636 UHF Ch.36	UM269: 636 UHF Ch.36	UM270: 636 UHF Ch.36
UM271: 636 UHF Ch.36	UM272: 636 UHF Ch.36	UM273: 636 UHF Ch.36	UM274: 636 UHF Ch.36
UM275: 636 UHF Ch.36	UM276: 636 UHF Ch.36	UM277: 636 UHF Ch.36	UM278: 636 UHF Ch.36
UM279: 636 UHF Ch.36	UM280: 636 UHF Ch.36	UM281: 636 UHF Ch.36	UM282: 636 UHF Ch.36
UM283: 636 UHF Ch.36	UM284: 636 UHF Ch.36	UM285: 636 UHF Ch.36	UM286: 636 UHF Ch.36
UM287: 636 UHF Ch.36	UM288: 636 UHF Ch.36	UM289: 636 UHF Ch.36	UM290: 636 UHF Ch.36
UM291: 636 UHF Ch.36	UM292: 636 UHF Ch.36	UM293: 636 UHF Ch.36	UM294: 636 UHF Ch.36
UM295: 636 UHF Ch.36	UM296: 636 UHF Ch.36	UM297: 636 UHF Ch.36	UM298: 636 UHF Ch.36
UM299: 636 UHF Ch.36	UM300: 636 UHF Ch.36	UM301: 636 UHF Ch.36	UM302: 636 UHF Ch.36
UM303: 636 UHF Ch.36	UM304: 636 UHF Ch.36	UM305: 636 UHF Ch.36	UM306: 636 UHF Ch.36
UM307: 636 UHF Ch.36	UM308: 636 UHF Ch.36	UM309: 636 UHF Ch.36	UM310: 636 UHF Ch.36
UM311: 636 UHF Ch.36	UM312: 636 UHF Ch.36	UM313: 636 UHF Ch.36	UM314: 636 UHF Ch.36
UM315: 636 UHF Ch.36	UM316: 636 UHF Ch.36	UM317: 636 UHF Ch.36	UM318: 636 UHF Ch.36
UM319: 636 UHF Ch.36	UM320: 636 UHF Ch.36	UM321: 636 UHF Ch.36	UM322: 636 UHF Ch.36
UM323: 636 UHF Ch.36	UM324: 636 UHF Ch.36	UM325: 636 UHF Ch.36	UM326: 636 UHF Ch.36
UM327: 636 UHF Ch.36	UM328: 636 UHF Ch.36	UM329: 636 UHF Ch.36	UM330: 636 UHF Ch.36
UM331: 636 UHF Ch.36	UM332: 636 UHF Ch.36	UM333: 636 UHF Ch.36	UM334: 636 UHF Ch.36
UM335: 636 UHF Ch.36	UM336: 636 UHF Ch.36	UM337: 636 UHF Ch.36	UM338: 636 UHF Ch.36
UM339: 636 UHF Ch.36	UM340: 636 UHF Ch.36	UM341: 636 UHF Ch.36	UM342: 636 UHF Ch.36
UM343: 636 UHF Ch.36	UM344: 636 UHF Ch.36	UM345: 636 UHF Ch.36	UM346: 636 UHF Ch.36
UM347: 636 UHF Ch.36	UM348: 636 UHF Ch.36	UM349: 636 UHF Ch.36	UM350: 636 UHF Ch.36
UM351: 636 UHF Ch.36	UM352: 636 UHF Ch.36	UM353: 636 UHF Ch.36	UM354: 636 UHF Ch.36
UM355: 636 UHF Ch.36	UM356: 636 UHF Ch.36	UM357: 636 UHF Ch.36	UM358: 636 UHF Ch.36
UM359: 636 UHF Ch.36	UM360: 636 UHF Ch.36	UM361: 636 UHF Ch.36	UM362: 636 UHF Ch.36
UM363: 636 UHF Ch.36	UM364: 636 UHF Ch.36	UM365: 636 UHF Ch.36	UM366: 636 UHF Ch.36
UM367: 636 UHF Ch.36	UM368: 636 UHF Ch.36	UM369: 636 UHF Ch.36	UM370: 636 UHF Ch.36
UM371: 636 UHF Ch.36	UM372: 636 UHF Ch.36	UM373: 636 UHF Ch.36	UM374: 636 UHF Ch.36
UM375: 636 UHF Ch.36	UM376: 636 UHF Ch.36	UM377: 636 UHF Ch.36	UM378: 636 UHF Ch.36
UM379: 636 UHF Ch.36	UM380: 636 UHF Ch.36	UM381: 636 UHF Ch.36	UM382: 636 UHF Ch

Send your orders to:—

DEPT ETI 5, PO BOX 6, WARE, HERTS. Tel 0920-3182

Visit our NEW shop: 3 BALDOCK ST., WARE HERTS. Telex: 817861

BOOKS BY BABANI

BOOK NO	DESCRIPTION	£ p
BP6	Engineers & Machinists Ref. Tables	0.80
BP4	2nd Book Transistor Equivs & Subs	1.10
BP24	52 Projects Using IC741 (or equiv)	0.95
BP26	Radio Antenna Book Long Distance Reception & Transmission	0.85
BP27	Giant Chart of Radio Electronic Semi-conductor & Logic Symbols	0.80
BP32	Build Metal & Treasure Locators	1.00
BP34	Practical Repair & Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier	1.25
BP36	50 Ccts use Germ/Sil/Zener Diodes	0.75
BP37	50 Projects using Relays / SCRs / Triacs	1.25
BP39	50 Field Effect Trans Projects	1.25
BP40	Digital IC Equivs & Pin Connection	2.75
BP43	How to make Walkie Talkies	1.75
BP44	KC555 Projects (Revised & Enlarged Edition)	1.25
BP45	Projects on Opto-electronics	1.35
BP46	Radio Circuits using ICs	1.35
BP47	Mobile Discotheque Handbook	1.35
BP48	Electronics Projects for Beginners	1.45
BP49	Popular Electronic Projects	1.35
BP50	C.L.M 3900 Projects	1.25
BP51	Electronic Music & Creative Tape Recording	1.45
BP52	Long Distance Television Reception (TV-DX) For the Enthusiast	2.25
BP53	Practical Electronic Calculations & Formulae	1.45
BP55	Radio Stations Guide	1.45
BP56	Electronic Security Devices	1.50
BP57	How to Build Your Own Solid State Oscilloscope	1.35
BP58	50 Circuits using 7400 Series ICs	1.60
BP59	Second Book of CMOS IC Projects	1.60
BP60	Practical Construction of Pre-amps/Tone Controls/Filters & Attr	1.45
BP61	Beginners Guide to Digital Techniques	0.95
BP62	Elements of Electronics — Book I	2.25
BP63	Elements of Electronics — Book II	2.25
BP64	Elements of Electronics — Book III	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors & Computing	1.75
BP67	Counter driver & numeral Display projects	1.75
BP68	Choosing & Using your Hi-Fi	1.45
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.80
BP160	Coil Design & Construction Manual	0.75
BP202	Handbook of Integrated Circuits Equivs & Substitutes	1.00
BP211	First Book of Diode Characteristics & Equivalents & Substitutes	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	0.85
BP217	Solid State Power Supply Handbook	0.85
BP221	28 Tested Transistor Projects	1.25
BP224	50 CMOS IC Projects	1.35
BP226	Build Advanced Short wave receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
RCC	Resistor Colour Code Disc	0.20

BRACKETS

Right-angle mounting brackets. Ideal for mounting, PCB, panels et cetera into boxes and cases.
18SWC — Mild steel — short face has slotted hole 6.5cm x 3.7cm long face has 3.7cm diam. hole
O/N0.1726 Height 15cm, length 15cm, width 10cm £0.06
O/N0.1727 Height 25cm, length 15cm, width 10cm £0.07

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.16
DPDT standard slide	1974	£0.17
Toggle switch SPST 1 1/2 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on-off mains switch	1977	£0.58
Push switch — Push to make	1978	£0.16
Push switch — Push to break	1979	£0.21

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST — moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.35
	BLACK	1981	£0.35
	WHITE	1982	£0.35
	BLUE	1983	£0.35
	YELLOW	1984	£0.35
	LUMINOUS	1985	£0.35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1986	£0.81
Miniature SPST toggle 2 amp 250V ac	1989	£0.86
Miniature DPDT toggle 2 amp 250V ac	1980	£0.91
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.07
Push-button SPST 2 amp 250V ac	1962	£1.04
Push-button SPST 2 amp 250V ac	1963	£1.09
Push-button DPDT 2 amp 250V ac	1964	£1.34

MIDGET WAFER SWITCHES
Single bank wafer type — suitable for switching at 250V ac 100mA or 150V dc in non-reactive loads make-before-break contacts. These switches have a spindle 0.25 in dia and 30 indexing.

Description	No.	Price
1 pole 12 way	1985	£0.55
2 pole 6 way	1986	£0.55
3 pole 4 way	1987	£0.55
4 pole 3 way	1988	£0.55

MICRO SWITCHES	No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac	1970	£0.29

OPTOELECTRONICS

NEW INCREASED RANGE — ALL 1ST QUALITY LEDS (diffused)				
O/no.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (125)	RED	£0.10
1502	MIL3232 (TIL211)	3mm (125)	GREEN	£0.16
1503	MIL3331 (OP212A)	3mm (125)	YELLOW	£0.16
1504	ARL4850 (FLV117)	5mm (2)	RED	£0.10
1505	MIL5251 (TIL222)	5mm (2)	GREEN	£0.16
1506	MIL5351 (MV5353)	5mm (2)	YELLOW	£0.16
1509	FLV111	5mm (2)	(ill. Red)	£0.12

SUPER 'HI-BRITE' TYPE				
O/no.	Type	Size	Colour	Price
1521	MIL32	3mm (125)	RED	£0.11
1522	MIL52	5mm (2)	RED	£0.11
1514	ORP12 Light dependent resistor			£0.70
1520	OCPT1 Photo transistor			£0.40

LED CLIPS				
O/no.	Type	Size	Colour	Price
1508/125	pack of 5	125 clips		£0.17
1508/2	pack of 5	2 clips		£0.21

DISPLAYS:				
O/no.	Type	Size	Colour	Price
DL703	7 segment D.P. left (.3" height)		Common Anode	o/no. 1523 £0.85
DL707	7 segment D.P. left (.3" height)		Common Anode	o/no. 1510 £0.92
RED Single Digit			Common Anode	o/no. 1524 £2.08
DL527	7 segment D.P. left (.5" height)		Common Anode	o/no. 1512 £2.07
RED Two-Digit Reflector			Common Anode	o/no. 1511 £1.73
DL727	7 segment D.P. right (.5" height)		Common Anode	o/no. 1512 £2.07
RED Two-Digit Light Pipe			Common Anode	o/no. 1511 £1.73
DL747	7 segment D.P. left (.6" height)		Common Anode	o/no. 1511 £1.73
RED Single Digit Light Pipe			Common Anode	o/no. 1511 £1.73

OPTO-ISOLATORS				
O/no.	Type	Size	Colour	Price
CL74	Single Channel 6 pin DIP standard type — optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor			o/no. 1497 £0.61
CLD74	Multi-Channel 8 pin DIP Two Isolated Channels			o/no. 1498 £1.22
QL74	Multi-Channel 16 pin DIP Four Isolated Channels			o/no. 1499 £2.69

MEL 11 (TIL1) NPN LIGHT DETECTOR				
O/no.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (125)	RED	£0.10

WIRE CONNECTORS

Entirely new range of connectors for discrete wire. Uniquely designed Wirepost is soldered to the P.C. Board. A pre-stripped wire is inserted into the connector and easily locked by pressing the housing down. The wire is alternatively removed by lifting the housing. Tin alloy plated contacts ensure good as gold performance.
Housing consists of Thermo plastic polyester.
172B Single connector in red/black or white £0.12 inc. VAT
1729 Three-way connector black ONLY £0.23 inc. VAT
1730 Four-way connector black ONLY £0.28 inc. VAT

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm X 5mm chassis mounting	506	£0.18
1 1/4in X 1/4in chassis mounting	507	£0.14
1 1/4in car inline type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1 1/4in	510	£0.37

QUICK BLOW 20mm					
Type	No.	Type	No.	Type	No.
150mA	611	7p	1A	615	6p
250mA	612	1.5A	616	7p	4A
550mA	613	2A	617	508	5A
800mA	614	2.5A	618	7p	621

ANTI-SURGE 20mm					
Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK-BLOW 1 1/4in					
Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634

All 5p each					
Type	No.	Type	No.	Type	No.
0BA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

All 6p each					
Type	No.	Type	No.	Type	No.
0BA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

NUTS AND BOLTS

BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50.					
Type	No.	Price	Type	No.	Price
1in 0BA	839	£1.38	1/4in 4BA	846	£0.37
1in 0BA	840	£0.86	1/4in 4BA	847	£0.29
1in 2BA	842	£0.75	1in 6BA	848	£0.46
1/4in 2BA	843	£0.52	1/4in 6BA	849	£0.24
1/4in 2BA	844	£0.80	1/4in 6BA	850	£0.29
1in 4BA	845	£0.51			

BA NUTS — packs of cadmium plated full nuts in multiples of 50.					
Type	No.	Price	Type	No.	Price
0BA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50.					
Type	No.	Price	Type	No.	Price
0BA	859	£0.16	4BA	861	£0.14
2BA	860	£0.14	6BA	862	£0.14

SOLDER TAGS — Hot tinned supplied in multiples of 50.					
Type	No.	Price	Type	No.	Price
0BA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

AUDIO LEADS

No.	Type	Price
107	FM indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	£0.86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m	£0.98
115	1 & 4. Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead.	£1.44
117	Fitted plug and socket	£0.78
118	AC mains connecting lead for cassette recorders and radios. 2 metres	£1.21
119	5 pin DIN plug to stereo headphone jack socket	£1.04
120	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£0.89
121	Car stereo connector. Variable geometry plug to fit most car cassettes. 8 track cartridge and combination units. Supplied with inlined fuse power lead and instructions	£1.72
122	6.6m Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£0.85
123	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.85
124	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.85
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.85
126	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.85
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.49
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5. Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m	£0.86
134	5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm	£0.78
136	Coiled stereo headphone extension lead. Black. Length 6m	£2.01
178	AC mains lead for calculators, etc	£0.52

TRANSFORMERS

MINIATURE MAINS Primary 240V					
No.	Type	Price			
2021	6V-0-6V 100mA	£1.04			
2022	9V-0-9V 75mA	£1.04			
2023	12V-0-12V 100mA	£1.29			

MINIATURE MAINS Primary 240V with two independent secondary windings					
No.	Type	Price			
2024	MT280-0-6V 0-6V RMS	£1.84			
2025	MT150-0-12V 0-12V RMS	£1.84			

1 AMP MAINS Primary 240V					
No.	Type	Price			
2026	6V-0-6V 1 amp	£2.88	P & P	45p	
2027	9V-0-9V 1 amp	£2.30	P & P	45p	
2028	12V-0-12V 1 amp	£2.60	P & P	55p	
2029	15V-0-15V 1 amp	£3.16	P & P	65p	
2030	30V-0-30V 1 amp	£3.97	P & P	86p	

STANDARD MAINS Primary 240V					
No.	Rating	Price			
2031	1/2 amp	£3.81	P & P	86p	
2032	1 amp	£5.08	P & P	86p	
2033	2 amp	£6.27	P & P	81	

2035 240V Primary 0-55V @ 2A Secondary					
No.	Type	Price			
2035	240V Primary 0-55V @ 2A Secondary	£7.30	P & P	£1	

SPECIAL OFFER					
No.	Type	Price			
2042	240V Primary 0-20V @ 2A Secondary. By removing 5 turns for each volt from the secondary winding any voltage up to 20V @ 2A is easily obtainable. Ideal for the experimenter.	£1.50	P & P	86p	

CASES AND BOXES

INSTRUMENT CASES. In two sections, vinyl covered top and sides, aluminium bottom, front and back.					
No.	Length	Width	Height	Price	
155	8in	5 1/2in	2in	£1.73	
156	11in	6in	3in	£2.92	
157	6in	4 1/4in	1 1/4in	£1.78	
158	9in	5 1/4in	2 1/4in	£2.43	

ALUMINIUM BOXES. Made from bright alu., folded construction each box complete with half-inch-deep lid and screws.					
No.	Length	Width	Height	Price	
159	5 1/4in	2 1/4in	1 1/2in	£0.85	
160	4in	4in	1 1/2in	£0.85	
161	4in	2 1/4in	1 1/2in	£0.85	
162	5 1/4in	4in	1 1/2in	£0.87	
163	4in	2 1/2in	2in	£0.87	
164	3in	2in	1in	£0.60	
165	7in	5in	2 1/2in	£1.43	
166	8in	6in	3in	£1.82	
167	6in	4in	2in	£1.18	

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front — strong construction easily accessible.					
No.	Length	Width	Height	Price	
169	2 1/2in	5 1/4in	2 1/4in	£5.45	
168	1 1/4in	7 1/4in	4in	£8.31	

Terms cash with order. Cheques/Postal Orders made payable to Bi-Pak at above address



TTL by TEXAS.				93 SERIES				VEROBOARDS 0.1 0.15				TRANSISTORS				DIODES				THYRISTORS			
7400	11p	74278	280p	4018	85p	9301	160p	2.5x3.75"	(copper clad)	AC126	25p	BF259	35p	1P30A	48p	2N3442	140p	40361/2	45p	10A 400V	200p		
7400	80p	74279	110p	4021	110p	9302	175p	2.5x3"		AC127	78p	BF393	25p	1P30C	60p	2N3553	240p	40364	120p	25A 400V	400p		
7401	12p	74280	110p	4022	100p	9303	316p	3.75x3.75"		AC176	25p	BF440	25p	1P31A	58p	2N3584	240p	40408	70p				
7402	12p	74281	110p	4022	100p	9310	275p	3.75x3.75"		AC187/8	25p	BF440	25p	1P31C	62p	2N3643/4	240p	40409	85p				
7403	14p	74290	150p	4023	27p	9311	275p	3.75x1.7"		AF116	50p	BF440	25p	1P32A	88p	2N3643/4	240p	40410	85p				
7404	14p	74293	150p	4023	27p	9312	275p	4.75x1.7"		AD161/2	45p	BF440	25p	1P33A	88p	2N3704/5	12p	40411	300p				
7405	14p	74298	200p	4025	20p	9314	165p	4.75x1.7"		AD161/2	45p	BF440	25p	1P33C	88p	2N3706/7	12p	40412	300p				
7406	14p	74305	100p	4026	130p	9316	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P34A	115p	2N3708/9	12p	40413	300p				
7407	14p	74306	100p	4027	80p	9321	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P35A	115p	2N3710/1	12p	40414	300p				
7408	14p	74307	100p	4028	84p	9322	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P36A	115p	2N3712/3	12p	40415	300p				
7409	14p	74308	100p	4029	100p	9323	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P37A	115p	2N3714/5	12p	40416	300p				
7410	14p	74309	100p	4030	100p	9324	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P38A	115p	2N3716/7	12p	40417	300p				
7411	14p	74310	100p	4031	200p	9325	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P39A	115p	2N3718/9	12p	40418	300p				
7412	14p	74311	100p	4032	200p	9326	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P40A	115p	2N3720/1	12p	40419	300p				
7413	14p	74312	100p	4033	200p	9327	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P41A	115p	2N3722/3	12p	40420	300p				
7414	14p	74313	100p	4034	200p	9328	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P42A	115p	2N3724/5	12p	40421	300p				
7415	14p	74314	100p	4035	200p	9329	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P43A	115p	2N3726/7	12p	40422	300p				
7416	14p	74315	100p	4036	200p	9330	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P44A	115p	2N3728/9	12p	40423	300p				
7417	14p	74316	100p	4037	200p	9331	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P45A	115p	2N3730/1	12p	40424	300p				
7418	14p	74317	100p	4038	200p	9332	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P46A	115p	2N3732/3	12p	40425	300p				
7419	14p	74318	100p	4039	200p	9333	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P47A	115p	2N3734/5	12p	40426	300p				
7420	14p	74319	100p	4040	200p	9334	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P48A	115p	2N3736/7	12p	40427	300p				
7421	14p	74320	100p	4041	200p	9335	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P49A	115p	2N3738/9	12p	40428	300p				
7422	14p	74321	100p	4042	200p	9336	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P50A	115p	2N3740/1	12p	40429	300p				
7423	14p	74322	100p	4043	200p	9337	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P51A	115p	2N3742/3	12p	40430	300p				
7424	14p	74323	100p	4044	200p	9338	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P52A	115p	2N3744/5	12p	40431	300p				
7425	14p	74324	100p	4045	200p	9339	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P53A	115p	2N3746/7	12p	40432	300p				
7426	14p	74325	100p	4046	200p	9340	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P54A	115p	2N3748/9	12p	40433	300p				
7427	14p	74326	100p	4047	200p	9341	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P55A	115p	2N3750/1	12p	40434	300p				
7428	14p	74327	100p	4048	200p	9342	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P56A	115p	2N3752/3	12p	40435	300p				
7429	14p	74328	100p	4049	200p	9343	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P57A	115p	2N3754/5	12p	40436	300p				
7430	14p	74329	100p	4050	200p	9344	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P58A	115p	2N3756/7	12p	40437	300p				
7431	14p	74330	100p	4051	200p	9345	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P59A	115p	2N3758/9	12p	40438	300p				
7432	14p	74331	100p	4052	200p	9346	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P60A	115p	2N3760/1	12p	40439	300p				
7433	14p	74332	100p	4053	200p	9347	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P61A	115p	2N3762/3	12p	40440	300p				
7434	14p	74333	100p	4054	200p	9348	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P62A	115p	2N3764/5	12p	40441	300p				
7435	14p	74334	100p	4055	200p	9349	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P63A	115p	2N3766/7	12p	40442	300p				
7436	14p	74335	100p	4056	200p	9350	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P64A	115p	2N3768/9	12p	40443	300p				
7437	14p	74336	100p	4057	200p	9351	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P65A	115p	2N3770/1	12p	40444	300p				
7438	14p	74337	100p	4058	200p	9352	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P66A	115p	2N3772/3	12p	40445	300p				
7439	14p	74338	100p	4059	200p	9353	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P67A	115p	2N3774/5	12p	40446	300p				
7440	14p	74339	100p	4060	200p	9354	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P68A	115p	2N3776/7	12p	40447	300p				
7441	14p	74340	100p	4061	200p	9355	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P69A	115p	2N3778/9	12p	40448	300p				
7442	14p	74341	100p	4062	200p	9356	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P70A	115p	2N3780/1	12p	40449	300p				
7443	14p	74342	100p	4063	200p	9357	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P71A	115p	2N3782/3	12p	40450	300p				
7444	14p	74343	100p	4064	200p	9358	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P72A	115p	2N3784/5	12p	40451	300p				
7445	14p	74344	100p	4065	200p	9359	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P73A	115p	2N3786/7	12p	40452	300p				
7446	14p	74345	100p	4066	200p	9360	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P74A	115p	2N3788/9	12p	40453	300p				
7447	14p	74346	100p	4067	200p	9361	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P75A	115p	2N3790/1	12p	40454	300p				
7448	14p	74347	100p	4068	200p	9362	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P76A	115p	2N3792/3	12p	40455	300p				
7449	14p	74348	100p	4069	200p	9363	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P77A	115p	2N3794/5	12p	40456	300p				
7450	14p	74349	100p	4070	200p	9364	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P78A	115p	2N3796/7	12p	40457	300p				
7451	14p	74350	100p	4071	200p	9365	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P79A	115p	2N3798/9	12p	40458	300p				
7452	14p	74351	100p	4072	200p	9366	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P80A	115p	2N3800/1	12p	40459	300p				
7453	14p	74352	100p	4073	200p	9367	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P81A	115p	2N3802/3	12p	40460	300p				
7454	14p	74353	100p	4074	200p	9368	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P82A	115p	2N3804/5	12p	40461	300p				
7455	14p	74354	100p	4075	200p	9369	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P83A	115p	2N3806/7	12p	40462	300p				
7456	14p	74355	100p	4076	200p	9370	225p	4.75x1.7"		AD161/2	45p	BF440	25p	1P84A	115p	2N3808/9	12p	40463	300p				
7457	14p	74356	100p	4077	200p	9371	225p	4.75x1.7"		AD161/2	45p	BF440	25p										

SEIKO

NEW CASIO CALCULATORS AND WATCHES

TSi Alarm Chronograph



With countdown alarm. Hours, minutes, seconds, alpha day and date on upper display; and day, date, month, alarm and hourly chimes. Countdown alarm (upper display). Stopwatch from 1/100 sec to 12 hours; net, lap, and 1st & 2nd place times. Stainless steel. Glass.

Only £57.50

TS7 Alarm Chronograph

100M Water Resistant. Suitable for swimming, water skiing etc. Hours, minutes, seconds, day, date and month. Programmable weekly alarm. Interval alarm timer up to 16 hours. Hourly chimes. Stopwatch, 1/100 second to 20 minutes, then seconds to 12 hours. Upper display — lap times. Lower display — Total time.



Only £74.95

TS5 World Time / Alarm



Two Alarms, local and world time (dual tones). Hourly chimes. Normally displays hours, minutes, seconds, day; or optionally hours, minutes, day, date, month. World time mode displays an atlas with each of the 19 time zones highlighted when selected. Date and summer time functions.

Stainless £79.95
Gold Pl £99.95

H127 Analogue / Digital

Independent analogue display. Digital hours, minutes, seconds, day; and day, date, month, 1/100 second stopwatch to 20 minutes, then seconds to 12 hours; net lap and 1st & 2nd place. Single counter to 9,999 or dual counter to 99.



(£95) **£69.95**

SEIKO. The world's largest manufacturer of high quality watches. Solid stainless steel cases and bracelets, unless otherwise stated. Scratch resistant glass. Splash resistant. Typically 2 year + battery life. Accuracy: ± 15 seconds per month or better.

BARGAIN BASEMENT

Clearance offers while stocks last.

95QS, 32B. Chrome plated version of 95QS-36B above. **£16.95**


CQ-82 Clock, 4 alarms (one with snooze), calculator **£13.95**

HQ-21 Clock, calculator **£8.95**

UFO Master Blaster Station (RRP £24.95) Was **£22.50**

Granstand Adam. 4 games, one as "Simon says", was **£22.50**

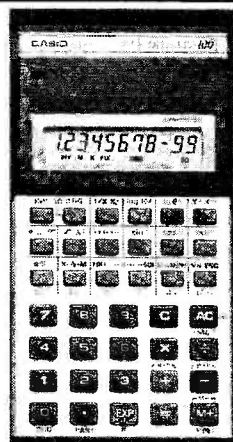Grandstand 4-in-1. Was **£22.50** **£16.95**



FX-100

SCIENTIFIC

LCD, 10 digits, 44 scientific functions, 6 levels (), standard deviations, coordinates conversions, sexagesimal conversions, fractions, cube roots, FIX, SCI, NORM, ENG, RND and RAN (random number). 7,500 hours battery 3/4 x 3 x 5 1/2 inches.

£15.95 (£17.95)

MELODY


81

(ML-81)

(RRP £24.95)

£22.95

More musical than the Melody 80

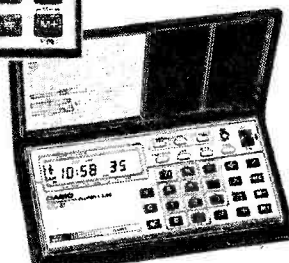

ML-81. 11 Note Melody Maker

Clock, 200 year auto calendar. Two musical alarms, countdown timer and hourly chimes. 1/10 second stopwatch measuring net, lap, and 1st & 2nd place times to 24 hours. Calculator with full memory, %, square roots, 1 year battery life from two RW42 batteries. 5/16" x 4 1/2" x 2 1/4".


ML-71

(24.95)

£22.95

As ML-81 but 1 alarm.

No $\sqrt{}$ 3/16" x 3 3/8" x 2 1/4".

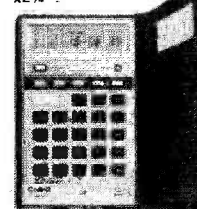

AQ-2200

£19.95 (£21.95)

Permanent display of full month calendar. Clock, alarm, hourly chimes. Stopwatch from 1/10 second to 12 hours; net, lap, 1st & 2nd place times. Calculator with full memory, %, $\sqrt{}$, 1 year batteries. 9/32 x 2 1/2 x 4 1/2".



MQ-12

(RRP £21.95)


£19.95

Card version of AQ2200. No $\sqrt{}$ 3/16" x 3 3/8" x 2 1/4".

MQ-6 £19.95. HR-10 Mini Printer £29.95. FX-81 £12.95. FX-80 £13.95. FX-330 £15.95. FX-310 £17.95. FX-510 £19.95. FX-2600 £19.95. FX-3200 £21.95. FX-501P £54.95. FX-502P £74.95. FA-1 £19.95. Master Pack deal + £5.

ILLUSTRATED CATALOGUE

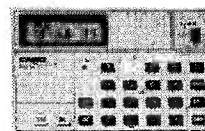Casio and Seiko products. Send 25p to: TEMPUS (Information and Service Centre), 19-21 Fitzroy Street, Cambridge CB1 1EH.



CASIO PW-81

6 digit clock, 24-hour alarm, hourly chimes. 8 digit calculator, with full memory, % 3/16 x 3 3/8 x 2 1/4".

£14.95 (£17.95)

83QS-41B ALARM CHRONOGRAPH

Stainless steel encased, mineral glass, water resistant, 3-YEAR BATTERY. Hours, minutes, seconds, date, am/pm; or hours, minutes, alpha day, date, am/pm. 24-hour alarm, hourly chimes. Stopwatch measures net, lap and 1st and 2nd place from 1/10 second to 12 hours. (£29.95)

£24.95

(Similar to illustration)



F-80 Alarm Chronograph



Black resin case, mineral glass. Water resistant. 3 YEAR BATTERY. Hours, minutes, seconds, date, am/pm; or hours, minutes, alpha day, date am/pm. 24 hour alarm, hourly chimes. Stopwatch from 1/10 second to 12 hours; net, lap and 1st and 2nd place. Nightlight.

£19.95 (£24.95)

95QS-36B Chronograph

Stainless steel, mineral glass. Water resistant. 5 YEAR BATTERY. Hours, minutes, seconds am/pm and day (12 or 24 hours). Dual time (12 or 24 hour). Day, date, month and year calendar. Stopwatch from 1/100 sec to 7 hours; net, lap and 1st & 2nd place times.

(£24.95) **£19.95**



111QS-34B

Superbly finished chrome plated case, mineral glass. Water resistant. Comprehensive display, hours, minutes, seconds, am/pm, day and date. Button for nightlight.

£14.95 (£17.95)

F-8C Black resin cased version, **£19.95**

F-200 Sports. Now only **£12.95**

Ladies' Casio watches



L-10 Disco

£12.95



L-20 Chrome

£14.95



87QL-18B

£27.95

All display hours, minutes, seconds, am, pm. And day, date and month. Stopwatch/dual time facility.

RETURN OF POST SERVICE

Postal and telephone orders received before 4.00 p.m. will normally be despatched the same day by FIRST CLASS POST.

Send your order by **FREEPOST** (2nd class post — no stamp required). Please phone urgent orders or use first class mail.

PRICE includes VAT, P&P. Send your Company Order, Cheque or P.O. or phone your ACCESS or B'CARD number to:


TEMPUS

Tempus (Dept. ETI)
FREEPOST, 164-167 East Road
Cambridge CB1 1BR. Tel. 0223 312866

Our retail shop will be moving soon. Personal callers, please telephone first for details.

Casio's new SUPERCALC!

It's got the lot!

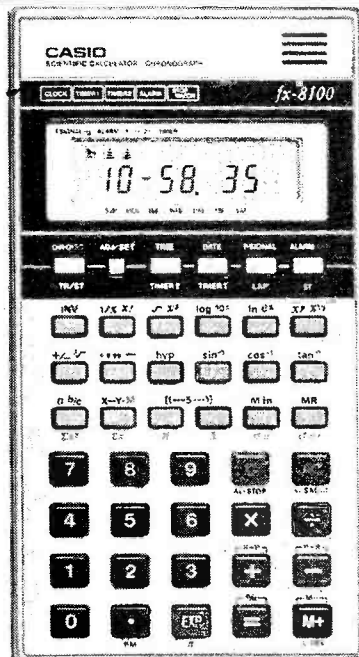


You always wanted a calculator that does everything except make tea —

HERE IT IS!

CASIO FX-8100 (left) 46 scientific functions, clock, calendar, alarm, countdown alarm, interval alarm timer, hourly chimes, 1/100sec stopwatch. ONE YEAR BATTERY LIFE approx. (continuous use). LC Display; 8 digit mantissa plus 2 digit exponent. 5 level parentheses, full access memory. Trigs, logs, hyperbolics, standard deviations, co-ordinate conversions, sexagesimal to decimal conversions, fractions, percentages, cube roots, sign change, register exchange, Pi entry etc. **CLOCK** displays hours, minutes, seconds, am/pm and day. **CALENDAR** pre-programmed to 1999; day, date, month and year. **24-hour ALARM**, hourly chimes. **Countdown ALARM TIMER**, interval (repeater) alarm timer or 1/100 second **STOPWATCH** measuring net, lap and first and second place times to 10 hours. 6.6 × 70 × 129mm (1/4 × 2.3/4 × 5.1/8 inches). Leatherette wallet. RRP £27.95.

All this for ONLY £24.95!

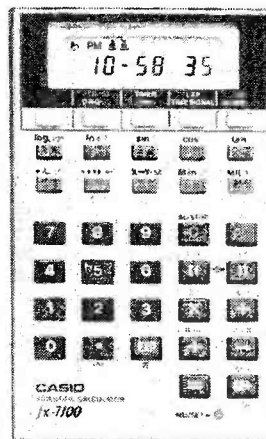

Casio FX-7100

RRP
£27.95
**ONLY
£24.95**

FX-7100 (above). Card version of the FX-8100. ONE YEAR BATTERY LIFE, 8 digit display and 39 scientific functions (does not have hyperbolics, fractions or calendar function). With clock, alarm, and hourly chimes. Interval alarm timer or 1/100 sec stopwatch. Wallet. 3.1/16 × 2 1/8 × 3 1/8 inches.

CASIO ★★★★★ Star Buys ★★★★★ SEIKO

CASIO 81QS-35B ALARM CHRONOGRAPH




**ONLY
£29.95**

RRP
£34.95

Stainless steel, mineral glass, water resistant. 5-YEAR BATTERY. Hours, minutes, seconds and day. Day, date, month and year calendar pre-programmed to 2029. 12- or 24-hour display. **24-hour alarm, hourly chimes, stopwatch** from 1/100 second to 7 hours, measuring net, lap and first and second place times. Backlight for night time viewing.

CASIO C-80 CALCULATOR WATCH

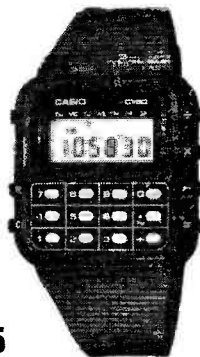

**ONLY
£24.95**

RRP
£29.95

Black resin, mineral glass, water resistant. FINGER-TOUCH KEYBOARD. Hours, minutes, seconds, am/pm and day. Day, date and month auto calendar pre-programmed to 2009. Professional 24-hour **stopwatch** measuring net, lap and first and second place times to 1/100 second. **Dual time, 24-hour. 8 digit calculator.** Backlight for night-time viewing. 44.9 × 35.8 × 10.2mm.

SEIKO TS2 ALARM CHRONOGRAPH



**ONLY
£47.50**

Stainless steel encased, Glass, splash resistant. 2-YEAR BATTERY. Comprehensive display of hours, minutes, seconds, day, date and month. **24-hour alarm and hourly chimes. Stopwatch** from 1/100 second to 20 minutes, then seconds to 20 hours. Upper display — lap times, lower display — total time. 8mm thick — 8.8mm including front buttons.

Please send cheques, postal orders. Company orders or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

(mail order only)
Tempus
(Dept. ETI)
FREEPOST
164-167 East Road
Cambridge CB1 1BR

(Catalogues, information
and service centre)
Tempus
19-21 Fitzroy Street
Cambridge CB1 1EH

Telephone: 0223 312866

Prices include VAT and Post and Packing

To: Tempus (Dept. ETI), FREEPOST, 164-167 East Road, Cambridge CB1 1BR ETI 5

Please send me

Remittance enclosed £

Access or Barclaycard number

Name

Address

Post code

FM/AM STEREO TUNER AMPLIFIER CHASSIS

Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together.

Note Circuit diagram and interconnecting wiring diagrams supplied.


Rotary Controls Tuning, volume, balance, treble and bass.

Push Button Controls Mono, Tape, Disc, A.F.C., FM (VHF), LW, MW, SW.

Power Output 7 watts RMS per channel into 8ohms (10 watts music).

Tape Sensitivity output typically 150mv. Input 300mv for rated output.

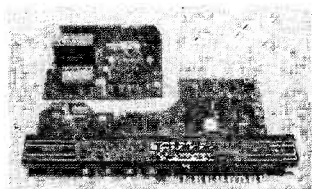Disc Sensitivity 100mv (ceramic cartridge).



Stereo Beacon Indicator LED or bulb.
Size Tuner — 2 3/4" x 15" x 7 1/2"
approx. Power amp. 2" x 7 1/2" x 4 1/2"
approx.
Price £22.00 + £2.50 Postage and Packing.

J.V.C. TURNTABLE

J.V.C. Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

★ 'S' shaped tone arm.

★ Belt driven.

★ Full size 12" platter.


★ Precision calibrated counter balance weight (0-3 grms).

★ Anti-skate (bias) device. Nylon thread weight.

★ Cut-out template supplied.


Size — 12 3/4" x 15 3/4" (approx.).

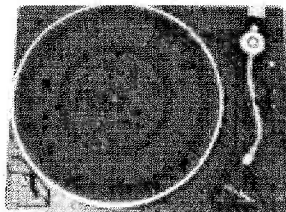Price £29.90 + £2.50 Postage and Packing.



PIEZO ELECTRIC TWEETERS — MOTOROLA

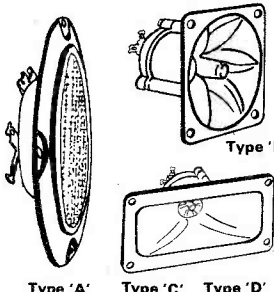Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series).



Type 'A' 3" round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price £3.80 each.**

Type 'B' 3 1/2" super horn. For general purpose speakers, disco, and P.A. systems, etc. **Price £4.80 each.**

Type 'C' 2" x 5" wide dispersion horn. For hi-fi systems and quality disco etc. **Price £6.20 each.**

Type 'D' 2" x 6" wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £9.00 each.**

Post and Packing, all types, 15p each (or S.A.E. for Piezo leaflets).

LOUDSPEAKER

High quality full range 8" loudspeaker. 10 watts RMS. 80HM. Rolled surround with aluminium centre dome.

Price £3.50 each + 75p Postage and Packing.



STEREO MAGNETIC CARTRIDGE BARGAIN

Acos M6EX stereo magnetic cartridge with tapered bi-radial diamond styli. Tracks between 1 and 2 grms. Retail price **£27.00.**

Special Price £7.90 — Post free.

LIGHT DIMMER CONTROL 800 watt (ready built)


240v/800watt light dimmer switch. This smart white unit readily replaces existing square switch plates.

Price £3.90 + 30p Postage and Packing.

Similar to above with additional facility of photo-cell to switch light(s) on automatically at the onset of darkness, and off during daylight.

Price £4.30 + 30p Postage and Packing.

DE-SOLDERING PUMP

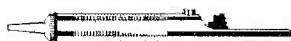

This de-soldering pump made to a very exacting specification is ideal for the removal of small components from printed circuit boards, etc. Comes complete with spare PTFE tip. **£5.30** post free.

RESISTANCE SUBSTITUTION DISC

A neat swivelling disc (65mm diam.) provides close tolerance substitution of 36 preferred values. From 50hm to 1meg.ohm. Complete with leads and croc-clips. **Price £4.50** — Post free.

B.K. ELECTRONICS

37 Whitehouse Meadows
Eastwood, Leigh-on-Sea
Essex, SS9 5TY

★ S.A.E. for components list etc. ★ Official orders welcome. ★ All prices include V.A.T. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam.

DIGISOUND

KITS AND SPECIAL PRODUCTS FOR ELECTRONIC MUSIC

I.Cs FROM SOLID STATE MICROTECHNOLOGY

SSM 2020 Dual Voltage Controlled Amplifier	365p
SSM 2030 Voltage Controlled Oscillator	485p
SSM 2040 Voltage Controlled Four Stage Filter	485p
SSM 2050 Voltage Controlled Transient Generator	365p

Complete set of Application Notes and Specifications for the above at 50p post paid, or 30p if added to an order for components. No VAT on data and stamps will be accepted in payment.

I.Cs FROM CURTIS ELECTROMUSIC SPECIALTIES

CEM 3310 Voltage Controlled Transient Generator	400p
CEM 3320 Voltage Controlled Four Stage Filter	390p
CEM 3330 Dual Voltage Controlled Amplifier	400p
CEM 3340 Voltage Controlled Oscillator	600p


Complete sets of Application Notes and Specification for the above at 50p post paid, or 30p if added to an order for components.

TEL LABS Q81, 1k, 1% 3500ppm temperature compensating resistor **185p**

OTHER COMPONENTS (Prices in pence)

741-8	23	LF 351	38
723-14	40	TL 081	38
1458-8	44	MC 34002/TL 082	65
LF 347	130	CA 3080E	63
LM 348	90	LM 13600	125

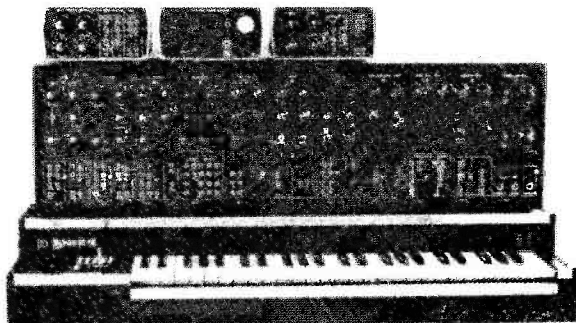All other components used in our kits are available separately and these are listed in the March 1980 price list — sent with orders or on receipt of 15p in stamps.



KITS FOR ETI 80 MODULAR SYNTHESISER. Components as specified in the issue of ETI listed, which also contains the constructional details for the kits. Glass fibre and roller tinned PCB. I.C. sockets.

KIT 80-1 ± 15V Power Supply (Feb. 80) **£16.70**

KIT 80-2 Voltage Controlled Oscillator (Feb. 1980) **£16.10**

KIT 80-3 Voltage Controlled Low Frequency Oscillator (Feb. 1980) **£16.10**

KIT 80-4 Voltage Controlled Mixer (March 1980) **£21.10**

KIT 80-6 Voltage Controlled Filters (May 1980) **£11.50**

PCBs SEPARATELY:

KIT 80-1	£1.60	KIT 80-4	£2.60
KIT 80-2/80-3	£2.10	KIT 80-6 (All types)	£1.60

PCB and Kit for 80-5 (Processor) available shortly.

9 x 3 inch panels for modules 80-2, 80-3, 80-4, and 80-6L to the design shown in ETI and made from white plastic coated steel with black lettering are available at £2.50 each.

PLEASE ADD 30p P&P TO TOTAL ORDER AND THEN ADD VAT AT CURRENT RATE



DIGISOUND LIMITED,
13 THE BROOKLANDS, WREA GREEN,
PRESTON, LANCs. PR4 2NQ
Tel.: 0772 683138 (MAIL ORDER ONLY)

QUANTITY PRICES — SAVE — SAVE — IMMEDIATE DELIVERY

NEW STOCKS BELOW MANUFACTURERS' PRICES. Postage & packing add 50p per order. Prices incl. VAT.

SN74141N IC 50p ea.
BCD Decimal Decoder-Driver 10 for 44p ea. 100 for 40p ea. 1,000 for 39p ea.
DISPLAYS by Hewlett-Packard. Seven segment OL707 (5082-7750) 95p. Common anode half inch red display brand new in maker's cartons 6 for £5.50 for 70p ea. 500 for 60p ea.
TV SOUND. High quality sound through your hi-fi. Simply plug into your aerial socket. £6.50, as reviewed Popular Hi-Fi.

BURROUGHS 8 DIGIT Panaplex calculator display 7 segment 0.25" digits. Neon type with red bevel socket and date. £1.95 ea. 10 for £17.

HONEYWELL PROXIMITY DETECTOR integral amplifier 8V DC £3.50 ea. 10 for £30.

MULLARD TBA800. IC audio amplifier 95p ea. 10 for £8. 100 for £70. 500 for £300.

RCA CA3089. FM IF £1.50, 10 for £12.

RCA CA3090AOL. FM decoder £2.50, 10 for £20, 100 for £175.

BU 205 TEXAS. £1.50 ea. 10 for £12. 100 for £100 per 1,000 85p ea.

2N3055 80V version TO3 power 10 for £3.50. 100 for £28. 500 for £125.

BUC08 TO3 Texas TV power transistors £1.75 ea. 10 for £15. 100 for £120. 1,000 for £1 ea.

MC1310P-SN76115N FM stereo decoder £1.20 ea. 10 for £10. 100 for 85p ea.

MULLARD AD161-AD162 Matched pairs 1 pair 80p, 10 pairs £8, 100 pairs £50.

Cartons of 800 pairs £250 EX-STOCK

RADIATION DETECTORS Quartz Fibre Dosimeters. Pen type with clip with lens and scale 0-5R. Originally over £5 OUR PRICE 95p EACH.

10 for £8. 100 for £70. ORP12 light dependent resistance Mini Type. 2 for £1. 10 for £4.50. 100 for £40.

TV TUNERS by Mullard LHF 38 mcs size 3 1/2x2 1/4x1 1/4 £2.50 ea. 10 for £20. 100 for £175. 500 for £750. 1,000 for £1,250.

MULLARD TUNER MODULES with data LP1171 combined AM-FM IF strip £3.50. LP 1179 FM front end with AM tuning gang, used with LP1171 £3.50. LP1171 and 79 pair £5.75, 10 pairs for £50. 100 pairs for £400.


CA3085 RCA POSITIVE VARIABLE REG. 5volt 100mAmp variable. B-24V 55p ea. 10 for £5. 100 for £35. 1,000 for £300.

MULLARD LP1157 AM tuner modules with circuit £2.50 ea. 10 for £20. 100 for £175.

LUSTRAPHONE RIBBON MIKE £1.50, + pre amp on chassis 3x2x1in 10 for £12.50.

TAA861B (1 1/4 pin DIL) IC TV sound and FM amplifier-detector by ATES on p.circuit board with other parts. Complete with data & connections. 60p. 10 for £5. 100 for 40p ea. 500 for 35p ea.

MOST PREVIOUS LINES IN STOCK

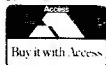

HENRY'S

EXPORT ORDERS add 10% for carriage

All mail to:
 404 Edgware Road
 London W2 England
 Phone 01-723 1008
 TELEX 262284 TRANSONICS. REF. 1400



MARRIOTT TAPE HEADS Quarter track

Type Each Per 10 Per 100

XRPS18 R/Replay £3.00 £25.00 £200.00

XRPS36 R/Replay £4.00 £35.00 £250.00

RSP63 1/2 track £2.25 £20.00 £175.00

XES11 Erase £1.25 £11.00 £100.00

MAINS TRANSFORMERS all 200/250V IN

Type Current Size Price

12V 100mA 1 1/2 x 1 1/2 x 1 1/2 £0.95

12V 500mA 1 1/4 x 1 1/4 x 1 1/4 £1.35

12V 2amps 2 1/4 x 2 1/4 x 2 1/4 £2.50

Per 10 less 10%; per 100 less 20%.

STEREO CASSETTE TAPE HEAD. High quality replacement for most machines record/replay with mounting bracket £2.95.

DYNAMIC MICROPHONE. Low imp. Foster Insen. £1.45, 10 for £11, 100 for £100.

UHF TUNER BY GEC. 38mc/s with slow motion tuning. Size 5x3x2in. £3 ea. 10 for £25.

TWO GANG MINIATURE VARICAP TUNER 500pf with tuning knob, size 3x1 1/2x1 1/2in. £1.25 ea. 10 for £10. 100 for £85.

ATES U14552 AUDIO IC AMPLIFIER 14 PIN DIL. 300m watts 55p ea. 10 for £4.50, 100 for £35. 1,000 for 30p.

GENERAL ELECTRIC 2+2 watt IC stereo audio chips with circuit & data £1.95 ea.

RCA CD4029AE 16 pin DIL. presettage up down counter 85p each, 25 for £15, 100 for £50, 1,000 for £350 (in anti static tubes of 25).

UHF TV TUNER (preamp) with BF180 55p each. Built on PC board 2x2in (sold without data) 10 for £4.50, 100 for £35, 1,000 for £250.

HELICAL TO TURN POTS BY M.P.C. 2.5 watts 5% tolerance, type MM105. British made. 47 ohms/100/220/470 1k/2.2k/4.7k/47k. All at our price £1.95 ea. Manufacturers list price £3.80. Quantities:

Per 10 £1.50 ea.
 Per 100 £1.25 ea.
 Per 1,000 £1.00 ea.

WIRE WOUND MINIATURE M.P.C. controls **BRITISH MADE M/2/13 ALL AT 60p each**

47 ohms 2.2k Per 10 50p ea.
 220 4.7k Per 100 45p ea.
 470 10k Per 1000 40p ea.
 1k 47k

RELAYS min open type. 6/8V change over 85p. P 10 75p ea. P 100 65p. P 1,000 50p ea. Min. 9/12V 2p cover 200 ohm £1.20.

TBA625 ATES voltage regulators 55p ea. 5 volts 100mAmps (TO99) per 10 £4.50, per 100 £39, 100 for £8. 1,000 for 8p ea.

THYRISTORS Motorola 2N5061 0.8 amp 60 volt 11p. 10 for 15p ea. 100 for 13p ea. 1,000 for 11p. 10,000 for 10p.

ULTRASONIC TRANSDUCERS 40 KC's. Pair at £2.95, 10 pairs at £2.50 pair.

ELECTROVALUE

SUPPLIERS OF



SIEMENS SEMI-CONDUCTOR CAPACITORS FERRITES	NASCOM MICRO COMPUTERS AND ANCILLARIES	VERO BOARDS CASES & KITS
ISKRA RESISTORS	RADIOHM POTENTIOMETERS	BREADBOARDS SOLDER TOOLS
	OPTO-ELECTRONICS	SWITCHES CATALOGUE 10

OUR MINI-SELECTION POINTS THE WAY!

EXAMPLE ONE — SOLDERING IRONS

Aryx 50 Isotip Antex C	£12.08 net £25.90 net £4.83 net	Antex x 25 Desolder tool SR3A 500 gm real solder	£4.83 net £7.48 net £6.61 net
------------------------------	---------------------------------------	--------------------------------------------------------	-------------------------------------

EXAMPLE TWO — PRINTED CIRCUIT MATERIALS

PCB's 300 x 150 mm SRBP S/S £1.38 F/Glass S/S £1.96 Positive resist 75cc Ferric Chloride 500 g	D/S £1.73 D/S £2.13 £1.67 £3.45	Etch Resist Pen Breadboards Bimboard 12x9.23 Euroboardboard T-DeC.	£1.14 £6.56 net £5.18
------------------------------------------------------------------------------------------------------------	------------------------------------------	--------------------------------------------------------------------------------	-------------------------------------

EXAMPLE THREE — SWITCHES

Chrome toggle Std. SPDT 65p Min. SPDT 66p	DPDT 89p DPDT 92p	13A time switch adaptors Smiths TS100 Wavechange, Lorlin, 1P12W, 2PWV, 3P4W, 4P3W	£14.43 net 46p each
-------------------------------------------------	----------------------	--------------------------------------------------------------------------------------------	----------------------------

EXAMPLE FOUR — CAPACITORS BY SIEMENS

Polyester 7.5mm PCM
 1, 1.5, 2.2, 3.3, 4.7µF, 10, 15, 22, 33, 42µF 8p each. 1µ 12p, 15µ 15p, 22µ 18p, 33µ 21p, 47µ 27p, 68µ 34p, 100mm PCM 1µ 37p.
Electrolytic, axial, (µ F/V)
 1/40 24p, 1/100 15p, 2/25 24p, 2/25 15p, 4/7 16 24p, 4/7 40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 18p, 47/10 18p, 47/25 18p, 47/40 15p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 65p.
 Also full supporting ranges of other ceramic, plastic and electrolytic caps.

EXAMPLE FIVE — POTENTIOMETERS BY RADIOHM

Single gang lin or log Twin gang lin or log Mono slider lin or log Twin slider lin or log	34p 93p 83p 136p	(Twin types stereo matched) Slider knobs Presets lin, horiz, or vert @	10p each. 10p
----------------------------------------------------------------------------------------------------	---------------------------	------------------------------------------------------------------------------	------------------

EXAMPLE SIX — RESISTORS

1 1/2W 2.3p 1W 6p
 Wirewound from 21p

AND AS FOR SEMI CONDUCTORS ...

1N914 6p 1N4007 9p 1N4148 5p 1N5402 19p 2N1599 £1.01 2N2369A 24p 2N3055 81p 2N3702-11 11p 2N4443 £1.78 2N4444 £2.28 2N4991 98p 2N5457-9 45p 40HF40 £2.35 40361 40p 40362 49p 40636 £1.69	40673 99p AC128 36p AC176 67p AD136 £4.25 AD149 £1.01 AD181 40p AD162 52p AF127 43p AL102 £1.84 BA379 29p BB103 43p BB104 70p CB105 37p C106D1 52p E1110 92p E1210 97p	MU481 £1.70 MU491 £1.98 MJ2955 97p MJE2955 £1.13 MJE3055 £1.00 MPSA12 42p MPSA63 44p OA47 14p OA90 8p OA202 16p OC29 £1.23 OC36 £1.18 T2800D £1.20 TIP31A 52p TIP32A 52p	T1P41A 69p T1P41C 74p T1P42A 69p T1P42C 74p T1P2955 69p T1P3055 69p T1S43 40p W02 35p 27x107.9 14p 27x300 14p 62Tx500 16p
---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------

This list is but a fraction of what we carry.

INFORMATION — To show everything we supply would take about seven pages of closely packed type in this journal — the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 — OUR 120 PAGE CATALOGUE FREE FOR THE ASKING.

PRICES AND V.A.T. — All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

POSTAGE — For orders up to £5.75 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

DISCOUNTS — 5% allowed on non-net items if order value exceeds £11.50. 10% if order value exceeds £29. Quantity discount prices on most components.

ELECTROVALUE LTD. Dept. 55 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 264475.

Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

QUESTION?

1. Is your hobby home computing or electronics?
2. Do you understand the application of IC's, Transistors, Diodes, etc?
3. Have you used or applied analogue or digital techniques?
4. Are you applying TTL Logic to your home computer?
5. Are you programming your home computer using simple software techniques?

If the answer is YES to any of these questions then why not consider turning your hobby into a career — applying your knowledge to servicing electronic equipment ranging from basic terminals and data processing machines through to advanced micro-processor systems.

We will train you through to advanced technology at the company training school, fitting the individual in at their own level.

We have vacancies over the whole of the U.K. especially in the London area, with the successful applicants working from home, usually in a radius of no more than 60-70 miles.

We supply all tools and test equipment, plus a company car which is available for private use.

If you are interested, then why not contact **Mr. C. Marklew** on **0249 813771** to discuss your own career opportunities in confidence, or write to:

KODE SERVICES LIMITED

Station Road, Calne, Wiltshire

8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link-selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

KANSAS CITY

low error rate tape interface.

**NEW FACTORY
UP!
PRICES DOWN!**

Increased capacity at our
big new factory means
many prices down! All
others frozen!



Cabinet size 19.0" x 15.7" x 3.3". Television not included in price

2 MICROPROCESSORS

Z80 the powerful CPU with 158 instructions, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10^{-9} to 9×10^{99} to 8 figures plus 2 exponent digits.

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

resident in EPROM.

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.

**COMPLETE KIT
NOW ONLY**


£225 +VAT!

POWERTRAN

PSI Comp 80. Z80 Based powerful scientific computer
Design as published in Wireless World

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete!

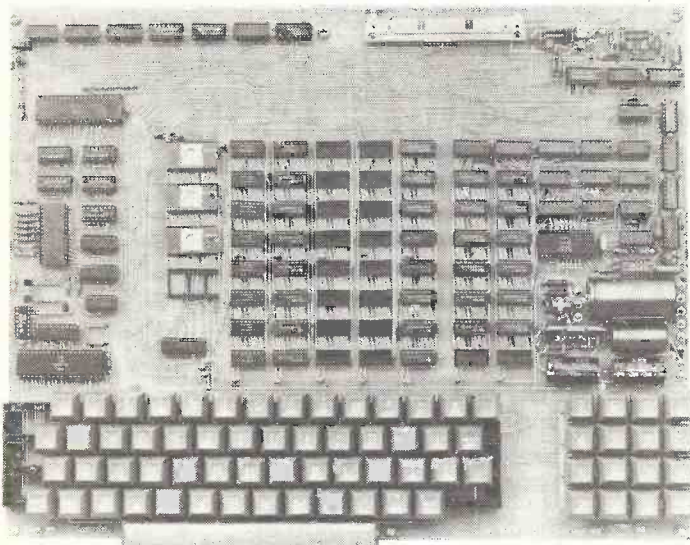Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer. 2K Basic and 1K monitor in EPROMs and, of course, wire, nuts, bolts, etc.



Value Added Tax not included in prices

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until July 31st, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1.00 handling and documentation.

U.K. ORDERS: Subsequent to 15% surcharge for VAT*. No charge is made for carriage. *Or current rate if changed.

SECURICOR DELIVERY: for this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect your computer from the factory, call at Sales Counter. Open 9 a.m.-12 noon, 1-4.30 p.m. Monday-Thursday.

KIT ALSO AVAILABLE AS SEPARATE PACKS

For those customers who wish to spread their purchases or build a personalised system the kit is available as separate packs eg. PCB (16" x 12.5") £43.20. Pair of keyboards £34.80. Firmware in EPROMS £30.00. Toroidal transformer and power supply components £17.50. Cabinet (very rugged, made from steel, really beautifully finished) £26.50. P.S. Will greatly enhance any other single board computer including OHIO SUPERBOARD for which it can be readily modified. Other packs listed in our FREE CATALOGUE.

PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion socket is made via a ribbon cable.

Mother board:

Fibre glass double sided plated through hole P.C.B. 8.7" x 3.0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug

£39.90

8K Static RAM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" £12.50
Set of components including IC sockets, plug and socket but excluding RAMs £11.20
2114L RAM (16 required) £5.00
Complete set of board, components, 16 RAMS £89.50

8K ROM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" £12.40
Set of components including IC sockets, plug and socket but excluding ROMs £10.70
2708 ROM (8 required) £8.00
Complete set of board, components, 8 ROMs £78.50

New Factory on same Industrial Estate
Address and Telephone Number unchanged

UK Carriage FREE

POWERTRAN COMPUTERS

(a division of POWERTRAN ELECTRONICS)

PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NM

ANDOVER
(0264) 64455

OLIVETTI PRINTER & KEYBOARD type Te 300
with PUNCH & READER. Upper case ASCII with V24 Interface. 240 volt operation.
£125 each

INFRA RED IMAGE CONVERTER type 9606 (CV 144)
1 1/2 x 2" diameter. Requires single low current 3KV to 6KV supply. Individually boxed. With data
£12.50 each P&P 75p Infra Red Lamps also advertised

STEPPING MOTORS
200 steps — 20-oz/in. torque.
12/24 volt input, 4 wire.
£12 each P&P £1.50

STEPPING MOTORS
200 steps. 20-oz/in. torque.
120 volt operation, 3 wire.
£4 each P&P £1.50

EX-MINISTRY SMALL COMPACT WIDE RANGE VOLTMETER SOLIO STATE
AC Rang 1mV to 500V Full Scale 10HZ-100KHZ. DC Range 4V to 400V Full Scale.
ONLY £20 ea. P&P £2.50

4K STATIC RAM
type 9140
£4 each. 8 for £24

709 DIL 14 PIN OPERATIONAL AMPLIFIERS
at **8p each**
100 off 25% discount

MINIATURE KEYBOARD
Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 each**

BLUE THERMAL PAPER
430ft. roll, 8 1/2" wide
£2 per roll. P&P £1.75

In spite of our shift towards Components we couldn't resist buying a large quantity of **SIEMENS TEST GEAR** — at Low Low Prices. Hence an extensive list.
All items at **£35 each.**

STEPPING MOTORS
North American Philips. 5 volt 3.3 amp operation. 2 wire. PPS 0-200 revs per min. 0-250 used. Tested.
£16 each P&P £1.50

STEPPING MOTORS
6/12 position with additional where the rotor is coils. Device can be used as a tachometer. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p or 5 for £5 p&P £1.50.

POLARAD SPECTRUM ANALYSER
5" Display. These are supplied with STU 2 plug-in. 1 to 4.5GHZ.
£125 each

TELEQUIPMENT SERVICE SCOPE MINOR
Modern style — Small size 5x7x11" approx. Circuit diagram supplied.
£55 each

BC172	5p	MC4001	15p	BC337	8p	2N3704	5p
BZ884V7	10p	MC4012	15p	BC327	8p	2N5447	5p
BZ8813V	10p	MC4020	75p	BC251	5p	2N5449	5p
2N3006	5p	74C20	25p	BC171A	5p	2N3053	15p
1N4305	5p	74C08	25p	TIS92	10p	8FT60	5p
BZX79C12	10p	74C10	20p	TIS93	10p	4013	30p
BC121B	5p	MC4049	35p				
SN76550	10p						
IC 7451	5p						

TRANSISTOR INVERTER
115V AC, 1.7Amp Input. Switching is at 20KHZ. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuit supplied.
£1.25 each P&P £2

KEYBOARD PAD
Size 3 x 2 1/2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.
£4 each P&P £1
or **5 for £15 P&P £2**

REGULATORS — att at **45p each.** MC7805; 7812; 7815; 7912; 7915.
16 pin DIL Socket **10p.** 14 pin DIL Socket **8p**
LED type TIL 209 Red with holder **10p each**
SLOTTED OPTO SWITCH supplied with data — normally over £2. OUR PRICE **75p each.**
ROCKER SWITCHES 2 pole c/o — **15p each**
Spring Action TERMINALS — normally over **30p ea.** OUR PRICE **15p each**
TOROIDAL TRANSFORMER 0-115V-230V Input 13.5V — 0 — 13.5V rated 8VA output **£1.70 each.** P&P 75p.
Sub-min TRANSFORMER 0-120-240V Input: 12V-0-12V rated 4VA Output **75p each P&P 50p.**
L.E.D.s
Standard White 12p; Standard Yellow 15p; Small White 8p.

EX-MINISTRY OSCILLOSCOPES
type CT316
Single Beam. DC-6MHZ. Size 8 1/2 x 11 x 20.
only **£37.50 each.**

NOT US
ROSS 7 x 50 MONOCULARS
Hence **£27.50 each**

We still have a Comprehensive list of **MANUALS** — phone or send for your requirements.

STC ATTENUATORS
Push button. Diecast case
£3 each

TANTALUM BEAD CAPACITORS. 4.7uf 25V. 10 off **£1;** 100 off **£7.50.**
TEXAS Low Profile 40 pin IC Sockets **45p each.**
SMALL TRANSFORMER. 240V Input. Output 2 windings 12V & 24V 1 amp. **£2 each.**

SO SIMPLE — SO SAFE
Fit a push button CIRCUIT BREAKER. Small, compact-3 ratings 0.8; 1.8 & 10AMP. State which one when ordering. **75 each.**

AMP METER 2 1/2" dia.
Scaled 0-60. Basic 75MV FSD. Complete with external 60Amp Shunt. **£2.50 each.** P&P £1.50.

DIODES

All new full spec. devices.
IN3063; IN4148; IS44
100 off **£1.50 — 1,000 off £10**

VARIACS EX-Equipment Good condition 8 Amps **£25 ea.**
20 AMPS **£35 ea.**
Some 3 phase available. Please enquire.

CRYSTALS
19.2KHZ FLAT METAL CASE — **50p each.**
10 MHZ B7G **50p each.**

EX-NAVAL 4ft dia STEEL DISHES. NEW CRATED. 1ft. deep at centre. These are plain steel dishes with holes for various aerial options. **£22.50 ea.** Carriage £5.
TWO FOR **£40.** Carriage £5.

TRANSFORMERS — Standard Mains input.
Secondary outputs.
6KV 0.125A **£15 ea.**
3440V 0.66A with matching 40H Choke **£30 the pair.**
3KV 50MA **£8 ea.** 4 Volts 250 Amps **£10 ea.**
18KV 30MA **£80.**
22.5KV 110MA **£50 ea.** 5KV 300MA **£15.**
60KV 0.0273 **£150.** 12KV 30MA **£20.**
MULTI PURPOSE MAINS TRANSFORMER 4 windings each winding 0-10-110-125 at 0.8A **£15 ea.**
425V 50HZ 2 Wire input. Output 8.5KV 2.65KVA. Could be run on 240V at 1/2 rating **£15 ea.**
STEP DOWN ISOLATING TRANSFORMER. Input 220. 250V 50HZ Output 115V 1.8KVA. BRAND NEW. These are very conservatively rated **£20 ea.**
CAPACITORS
0.5 mfd 10KV **£4 ea.** 2mfd 5KV **£4 ea.**
8 mfd 2.5KV **£4 ea.** 0.5 mfd 5KV **£4 ea.**
CARRIAGE on these units will be charged at cost.

INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 1 1/2" x 1/4" dia. **£1.50.**
BRIDGE RECTIFIER. 2 Amp **50p ea.**
PHOTODIODE DETECTOR 4" fly leads. **25p ea.**
AMPHENOL. 17-way chassis mount edge connectors 0.1 spacing. **15p ea.**
I.F.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) **60p ea.**
FANS. 115V 13 Watts. Size 3 1/4 x 3 1/4 x 1 1/2" BRAND NEW. **£4.50 ea.** Secondhand **£2.50 ea.**

Miniature **MOTORS** 12V with geared wheel (8 teeth 3/16" dia). Size 1 1/4 x 1/4" dia. New **30p ea.**
MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New **£1 ea.**
LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. **15p ea.**
DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New **10p ea.**
DELAY LINE. 50 nanoseconds. 3 connections. ground-in-out. Size 2 x 7/16 x 1/16". New **25p ea.**
PULSE TRANSFORMER. Sub min. Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New **20p ea.**
MOTOR by Inland Motor Corp. DC High Torque. Reversible. Usable torque at 5V. Max voltage 24V **£2.50 ea.** P&P £2.
REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus. **£1 each.**
DON'T TAKE CHANCES. Use the proper EHT CABLE. **10p per metre or £7.50 per 100 metres/drum.** P&P 1/4.
MOTOR by Eastern Air Devices Inc. 125V reversible with toothed shaft (10 teeth 1/4" dia). Size 2 1/4 x 2 1/4" dia **75p ea.** P&P £1.
PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap **75p ea.** Box of 12 **£5.50.** P&P £1.50.

DECOUPLING CAPACITORS. 0.05mfd 10V; 0.01mfd; 0.1mfd 50V; 0.047mfd 250V. All values 100 for **£1.** E.H.T. Capacitor 500pF 9KV **20p each.** 10-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10 metres for **£3.**
GEC UHF 4-button tuner. **£1.50 each.**
CENTAUR 115V FANS 4 1/2 x 4 x 1 1/2" **£4.50 ea.**
EX-USED equipment, tested. **60p each.**
POTTER & BRUMFIELD TIMER RELAY. 115V AC. Heavy duty. 7 pole c/o's with 2 second delay. Charge R & C for different timing **50p each.**
SPEAKERS 2 1/2". 50 ohm 0.2W. New **40p each.**
RAPID DISCHARGE capacitors 8mfd 4kV **£5 each.** P&P £2.
CONTACTORS. Heavy Duty 24V DC 5 make **£1 each.**
GEC UHF/VHF 6-button tuner **£2 each.**
DIGITAL 24-HOUR CLOCK with built-in alarm as used in Braun Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 6 1/2 x 2 1/4 x 2 1/4". **ONLY £3.75 each.**
931A PHOTO MULTIPLIER in stainless steel container with window and built-in resistor network. **£2 each.** P&P £1.
SILVER CONTROL 500W. Log Single track. Complete with knob. Length 3 1/2". **25p each.**
RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degree C **£2.50 each.**
SOLID STATE UHF TUNERS. 30 acs **£1 each.**
BRAND RED blue wire wraps. 30 metres for **£1.**
5in SOLID RUBBER RINGS (1" dia. rubber). Keep the kids (or dog) happy. 4 for **£1.** P&P £1.50.
TRANSFORMERS
AUTO 240V input 115 V. 1 Amp output **£1.25 each.** P&P £1.25.
240V input. Soc. 6V. 1.86A 8kw. Size 2 1/2 x 2 x 2". Good quality. **£1.50 ea.** P&P £1

240V input Soc. 12V 0.92A. Size 2 1/2 x 2 x 2". Good quality. **£1.50 ea.** P&P £1.
240V input 12V 100MA. Size 60 x 40 x 42mm. **50p each.**
240V input. Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm. **£1 ea.**
115V input. Soc. 5V 250MA. Size 1 11/16 x 1 1/2 x 1 1/4". **2 for 50p.**
SEMICONDUCTORS
1N4005 — **5p;** 1N4003 — **3p.**
At **5p each:**
13BC147, BC148B, BC157, BC158, BC237, BF197, OA90, OA81, BA154, BA243.
At **25p each:**
TIP31, TIP41A, 2N5956, AF139, 2TX341.
BY127 10p, BF181 20p, BD239 45p, BD241 40p, MA343AT 45p, BD228 50p, BD233 & BD234 Comp Pair 25W — **80p per pr.** at **50p each.**
REGULATOR TBA625 B to 20V in — 5V out 180MA TD5 Con. **35p each** BF265C 20p.
TV AMPLIFIER TBA 120 20p each.

Integrated Circuits

7453	5p	74H74	12p	75315	£1
7451	5p	74H51	7p	SN15862	4p
7401	5p	74538	10p	MC4028	65p
7402	12p	74502	12p	7417	14p
7476	20p	74154	70p	7441	40p
7495	35p	74C02	16p	74C86	50p
74121	10p	74C04	18p	74C161	24p
74122	12p	74C74	18p		
74C00	17p				

MOTOROLA DUAL in Line 6 pin Opto Coupler **30p each.** Gold plate tester version **50p each.**
EPROMS 2708 **£5.50 each.**
TELEPHONES 706 style black or grey **£5.50 each.** 746 style black or grey **£7.50 each.** Older style black **£2.50 each.** P&P £1.50 per telephone.
Honeywell humidity controllers **50p each.**
THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay **50p each.**
MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3-way **10p each.**
DIGITAL to ANALOGUE CONVERTER. 8 bit will fit standard TTL socket. With data. **£2.50 each.**
VARIACS. 2 amp Standard 240 Volts **£10 each.** P&P £2.
ELECTROSTATIC VOLTMETERS. 7.5KV **£8 each.** P&P £1.50. Other ranges available. Please enquire.
TRIMMERS. Sub min. 0.25 to 1.25pF. to 4.5pF. to 4.5pF. All at **6p each.**
CROWN replacement MOTOR for IBM GOLF-BALL TYPEWRITER 115V 50HZ 1350 rpm. **£4.50 ea.** P&P £2.
SMITHS encapsulated transistorised AUDIBLE WARNING DEVICES 4V-12V. Can be driven from TTL **65p each.**

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1 — where P&P not stated please use own discretion — excess refunded. CARRIAGE ALL UNITS £5. P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.


CHILTMead LTD

NORWOOD ROAD, READING

TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")

KRT101 M/Meter, 1.00
opv. 1KV AC/DC Volt
150ma DC current. Resis-
tance 0-2.5k, 0-100K, £4.3



NH55 M/METER, 2.00
opv. 1KV AC/DC Volt



YMS68 M/METER
20,000 spv., 1KV AC/
Volts, 250ma DC., 4 resi

POWER SUPPLIES. Switched type plug into a 13 amp socket has 3-4, 5-6, 7.5 and volts 0 cut out at either 100 or 400mA switchable £3.45. HC244R stabilised power supply 3-6-7.5-9V DC at 400mA, has polarising reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current £5.50.

ALL ORDERS DESPATCHED BY RETURN POST

**35p P&P
VAT
additional**

DELTA TECH & CO.

62 NAYLOR ROAD, LONDON, N20 0HN

Please add 35p for P&P

RESISTORS (1/4 W)

10 ohms to 10 Mohms 1.5p

PRESETS (.15W Horizontal)

100 ohms to 2 Mohms 8p

POTENTIOMETERS (1/4 W)

Linear & Log Scale

4.7 Kohms to 2.2 Mohms 30p

VEROBORDS (0.1" Copper)

2.5" x 5" 55p

3.75" x 5" 65p

ZENER DIODES (400mW)

2.7V to 33V 8p

CERAMIC CAP (50V)

33pF to 47nF 3p

POLYSTYRENE CAP (50V)

10pF to 1,000pF 5p

POLYESTER CAP (100V)

1nF to 88nF 6p

100nF, 150nF 7p

220nF, 330nF 8p

470nF, 9p 880nF, 10p

1uF: 14p 2.2uF: 20p

3.3uF: 22p 4.7uF: 24p

ELECTROLYTIC CAP (uF/V)

1/25 to 47/25 6p

68/50, 100/35 8p

150/25, 200/12 9p

220/25, 250/12 10p

470/25, 500/30 13p

1000/10: 14p 1000/25: 22p

1500/25: 26p 2200/6: 20p

OPTO/DISPLAY

2N5777 55p

OC71 65p

OC71 65p

DL704 110p

DL707 110p

0.125" x 0.2" 40p

LEDs:

Red 10p

Green 14p

Yellow 14p

.125" Clip 3p

.2" Clip 4p

DIL SOCKETS

8 pin 11p

14 pin 13p

2A/400V

W02M 20p

W06M 30p

VOLTAGE REGULATORS

7805 70p

7812/15 70p

7818/24 70p

7905 90p

7912/15 90p

7918/24 90p

DIODES

BY127 10p

OA47 8p

OA91 8p

OA200 6p

OA202 9p

1N418 5p

1N4148 4p

1N4001/2 4p

1N4003 5p

1N4004/5 6p

1N4006/7 8p

1N5400 13p

1N5401 14p

1N5402 15p

1N5404 16p

LINEAR CIRCUITS

709-8 40p

709-105 40p

710-14 33p

710-14 33p

747-14 22p

747-14 22p

748-8 44p

CA3018 70p

CA3028A 85p

CA3046 70p

CA3054 40p

CA3080 75p

CA3130 100p

CA3140 55p

CF31N 65p

LF356N 85p

LM301AN 32p

LM308N 60p

LM318N 200p

LM324N 75p

LM339N 60p

LM348N 90p

LM377N 175p

LM380N 90p

LM381N 140p

LM382N 130p

LM3131ON 150p

LM3900N 55p

LM3909N 70p

MC1496P 85p

NE531 150p

NE555 25p

NE556 60p

NE566 140p

TBA641B 200p

TBA800 75p

TBA810S 110p

ZN414 100p

ZN1034 220p

CMOS

4000 18p

4001/2 18p

4006 70p

4007 18p

4008 84p

4009 40p

4010 42p

4011/2 18p

4013 40p

4014 85p

4015 75p

4016 44p

4017 55p

4018 80p

4019 45p

4020 95p

4021/2 85p

4023 18p

4024 58p

4025 18p

4027 45p

4028 70p

4029 82p

4030 60p

4035 107p

4041 75p

4042 70p

4043/4 88p

4047 92p

4048 55p

4049 35p

4050 44p

4066 50p

4069 18p

4070/1 18p

4072/3 18p

4081/2 18p

4086 80p

4510 100p

4511 100p

4516 100p

4518 100p

4520 100p

4528 100p

TTL

7400/1 13p

7402/3 13p

7404/5 13p

7406/7 20p

7408/9 13p

7410 13p

7411 18p

7412 15p

7413 27p

7414 31p

7416/7 25p

7420 14p

7421/2 17p

7427 20p

7428 25p

7430 14p

7432 18p

7433 24p

7437/8 15p

7440 10p

7441 56p

7442 51p

7443 70p

7444 80p

7445 75p

7446 65p

7447 55p

7448 62p

7450 10p

7451/3 13p

7454 10p

7459 13p

7460 10p

7470 20p

7472 21p

7473 28p

7474 24p

7475 34p

7476 20p

7480 25p

7485 80p

7486 11p

7490 35p

7491 45p

7492 30p

7493 35p

7494 50p

7495 40p

7496 50p

7497 200p

74100 70p

74105 43p

74107 20p

74109 40p

74110 40p

74118 90p

74121 26p

74122 30p

74123 45p

74125/6 37p

74132 48p

74141 50p

74145 55p

74150 78p

74151 48p

74153 43p

74154 90p

74155 46p

74156 40p

74157 43p

74160 64p

74161 55p

74162/3 64p

74164 78p

74165 70p

74166 85p

74173/4 70p

74175 60p

74176 64p

74177 60p

74180 50p

74181 80p

74182 45p

74190 75p

74191 70p

74192 50p

74193 64p

74194 70p

74195 57p

74196 100p

74197 80p

74198 135p

74199 90p

TRANSISTORS

AC128/7 23p

AC128 23p

AC128/176 23p

Mt. pr. 42p

AC153 30p

AC176 23p

AC187/8 23p

AD149 70p

AD161/2 40p

AF114 40p

AF124 45p

AF125 35p

INTENSIVE WEEKEND COURSES IN BASIC

including hands-on mini com-
puter operation.

This short intensive course is intended to instruct from minimal knowledge to an operational capability of computer programming in BASIC high level language. The course is fully residential from Friday evening to Sunday afternoon. Option of non-residential weekend, week-day evening and weekday courses available if required.

For further details of dates available, fees, etc.:

Phone (0401) 43139, or write to
Dept. ETI
CLEVELAND BUSINESS SERVICES
Cleveland House, ROUTH
Beverley, North Humberside

ULTRASONIC ALARM KITS

Single Unit construction —screw connections. 240V operation with battery back-up option. 15-foot detection range internally preset. Delay on leaving and entry, invalid movement delay, self-cancelling alarm, approx. 2 mins. KITS INC. F/G PCB, ABS BOX, HARDWARE ALL COMPS. 240V UA/S (open collector output) £16.95. 240V UA/R (relay output contacts) £19.65. Piezo Sounder 12V 18mA 105db 1 mtr. £8.20. Built and tested units KIT price + £7.00. All prices inclusive — CWO — UK mail order.

G.J.D. ELECTRONICS, 105 Harper Fold Road
Radcliffe, Manchester, M26 0RQ


MK. 14 CONVERSION. Plug this conversion board into the SC/MP socket and have the power of a Z80, AND the amazing power of the AdEC-1 interpreter. With its 4-function arithmetic, versatile graphic control, edit facilities, conditional jumps, etc. So easy to use; you will learn to use it in a few hours. Kit price £29.95 inc. postage. Built price £34.85. Your MK14 repaired and conversions fitted if required. No need to remove a working soldered in MPU. Machine code monitor available instead of interpreter at same price. VDU version with 2K BASIC and extra 1K RAM. Kit £49.95, built £54.85. SEND SAE for details or PHONE REDDITCH (0527) 61240 evenings. REDDITCH ELECTRONICS, 21 FERNEY HILL AVE., REDDITCH, WORCESTERSHIRE B97 4RU.

E.T.I. 4600 SYNTHESISER. Maplin Cabinet, 4 octave keyboard, joystick, patch-board, fully calibrated, ready to play. Only three modules to complete. £325 o.n.o. Phone: Harpenden 60958.

ACORN COMPUTER. Built and working. Hexadecimal, cassette interface, 6502 Micro, Manuals, etc., included. Only £70. PSU if required, £5. Tel. (0235) 23601. After 4 p.m. please (Abingdon).

SMALL REED SWITCHES 10p. Magnets 7p. Powerful lenses 30p, 30 Untested ICS 35p, 4700 MFD 25v 35p. Postage 20p. Grimsby. Electronic Components, Lambert Road, Grimsby, Humberside. List 14p.

ETI PCB's

Buy it with Access


Available for most ETI projects from day one of ETI, 'phone your order.

SPECIAL OFFER—Single sided Pax PCB mat. four off, 4 1/4" x 6 1/2", 99p all up

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD • Tel: 01-891 1923

SLOAN ELECTRONIC EQUIPMENT 117 Orby Drive, Belfast BT5 6AG		
NE555 8 pin DIL 18p	10-way rotary switch. Make before break . . . 22p	741 8-pin DIL 18p
	2-pole changeover. BA/ 250v a.c. rocker . . . 22p	
PP3 Battery Clip 12p	BC337 9p. BC327 . . . 4p	100 Resis- tors 85p
	35p Post and Pack	

CLASSIFIED INFORMATION

Semi-Display:—

- 1-3 insertions — £6.00 per single column centimetre
- 4-11 insertions — £5.50 per s.c.c.
- 12 insertions — £5.00 per s.c.c.

Classified:—

- 23 pence per word (minimum 25 words)
- Box number on application (Personal ads only)
- £1.00 extra to cover 5 replies.

ALL ADVERTISEMENTS IN THIS SECTION MUST BE PRE-PAID

Closing date: 1st Friday in month preceding publication.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

Please insert the advertisement below in the next available issue of Electronics Today International for insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed and made payable to Electronics Today International)

NAME

ADDRESS

Send to : Margaret Hewitt
ELECTRONICS TODAY INTERNATIONAL
145, Charing Cross Road,
London WC2H 0EE.
Tel. 01 - 439 7449.

DIY with the PROFESSIONALS

Construct your own mixer, large or small, from our range of commercial electronic sub units. The same high quality units used to construct our own audio mixers supplied to radio stations, public buildings, government depts. etc. Now available in kit form or assembled and tested. Plus full range of panels, metal frames etc. Postal enquiries to **Dept. D.E.T.**

PARTRIDGE ELECTRONICS

(A. C. Partridge Ltd)
56 Fleet Road, Benfleet, Essex
Telephone (STD 03745) 3256

STOP PRESS: Superboard Compatible!
UK101 TRS 80

**COLOUR
YOUR
NASCOM!**



DAZZLING COLOUR GRAPHICS FOR NASCOM 1 & 2

Genuine bit-addressable "pixel" system for straightforward programming of pictorial or mathematical functions.

8 Colour display plus 8 colour independent background facility. Full documentation with FREE SOFTWARE: powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems — send us diagrams etc of your B & W video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.

NOW AVAILABLE FOR LIMITED PERIOD AT **£45** Plus VAT

**WILLIAM
STUART
SYSTEMS Ltd**

Dower House, Billericay Road, Billericay, Essex CM13 3SD.
Telephone: Brentwood (0277) 810244

DIGITAL CAPACITANCE METER



1 pF—2 μF in 5 ranges; on board selector. Precision resistor network and giant displays give direct readout in pF, nF and μF. Acc. 0.5%. ASSEMBLED, ONLY **£24.94**. ALL INC. Overseas add £1.50.

Precision Measurements, P.O. Box 70 Giles Lane, Canterbury, Kent CT1 2UU.

CIRCUIT DESIGN, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathcote, Heatherton Park, Taunton, Somerset TA4 1ET, or Phone Bradford-on-Tone (082-346) 536.

TRANSCENDENT 2000. Fully working, foot pedal, internal spring reverb, £230, o.n.o. AKAI 4000DS Mk. 2, excellent condition, £150. Pair electret condenser, microphones, high quality, £25. Tel. 0206 211309 (Colchester) evenings.

£5 OSCILLOSCOPE. Standard junk box components plus approx. another £5. (Total components approx. £12). This unit plugs into TV aerial socket and converts TV to oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge CB4 4BL.

CAPACITOR BARGAIN PACKS

best quality £1 + 25p PP ea

50 x 4.7 μF/10V Tef Tantalum	30 x 47 μF/10V Bead Tantalum
50 x 0.1 μF/100V Radial Polyester	40 x 0.1 μF/250V Radial Polyester
80 x 0.01 μF/400V Axial Polyester	20 x 1 μF/160V Axial Polyester
10 x 15 μF/450V Tag and Lytics	7 x 32 μF/450V Tag and Lytics
20 x 1000 μF Feed thro' small screw in type	

SCOTT, 37 Regent Street, Rowhedge, Essex

MEMORY MART

'UK 101' 'Superboard' 4K RAM

Memory Expansion £32.00
2114 1k. 4 each £4.00
2708 UV prom each £5.50

P. & P. 20p
C.O.D. 60p extra

MEMORY MART

19 Weatherby Gdns.
Hartley Wintney, Hants.

50Hz SUPERBOARDS BRITISH MODEL

FROM **£179** + VAT

Fully built, set up and tested

AUTHORISED dealer back-up

Free cursor control backspace, etc. tape

C.T.S., 1 Higher Calderbrook

Littleborough, Lancs.
Tel. Littleborough 79332 any time

DIGITAL WATCH BATTERY REPLACEMENT KIT




These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send **£7.50** for complete kit and get into a fast-growing business. Prompt despatch.

WATCH BATTERY REPLACEMENT CO. (ET12)
11 Percy Avenue, Ashford, Middx., TW15 2PB

NEW

MICROTYPE
SERIES 80
MICROCOMPUTER CASE

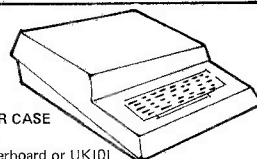

Ready Cut for Superboard or UK101 Complete with screws and instructions. Also available with uncut keyboard for homebrew enthusiasts. Produced in strong, black ABS plastic. Please state type when ordering. ONLY **£17.50** + VAT Post and packing inclusive. Send Cheque or Postal Orders to: Microtype, PO Box 104, Hemel Hempstead, Herts. HP2 7QZ SAE for Details.



C12 BRANDED DIGITAL QUALITY CASSETTES With library box and index card. 10 for 36p ea + VAT. Send **£5.40** (includes p&p and VAT).

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT — never gains or loses. 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also second-in-a-month STOP CLOCK and parallel BCD output, receives Rugby time signals, 1000Km range, ABSOLUTE TIME **£48.80**.

60KHZ RUGBY RECEIVER, as in MSF Clock, serial data output, built-in antenna. **£13.70**.

NO RADIO 4? 200KHz Converter, suits any Med. Wave receiver, get ALL the NEWS. **£11.40**.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (TE) Old School Lane, Milton, Cambridge



**C
A
M
E
R
A

C
C
T
V**

£114.99 + P/P £3.45
Optional extra manual
£6. Total **£124.44**

BEST OFFER EVER

**Camera Kit, Lens,
Vidicon & Modulator**

CROFTON

Tel: 01-891 1923 For full details



**WE CAN'T PRODUCE
RABBITS BUT WE CAN
PRODUCE RESULTS**

& whether you are buying, selling or exchanging let ETI's classified advertisement section work wonders for you.

Ring Margaret Hewitt

on
01-439-7449

CALCULATORS.

SCIENTIFIC

*SPECIAL OFFER

TEXAS T159 together with PC100C
(Complete as manufacturer's specifications)
£285.00

TEXAS/HP Accessories available	
*TEXAS T159 (Card prog 960 prog steps of 100 mem)	£156.50
*TEXAS T158 (Key prog 480 steps of 60 mem)	£60.00
*TEXAS PC100C (Printing Unit for T158/159)	£140.00
*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes / 50 Prog Steps)	£25.00

For your Texas T158/59 Calculator
ELECTRICAL ENG. MODULE
LEISURE (GAMES) MODULE
STRUCTURAL ENG. MODULE
NOW AVAILABLE

*TEXAS T1 PROGRAMMER (Hexadecimal Oct)	£46.50
*TEXAS T151 (10 mem 32 Prog Steps Stat/Sci)	£26.30
TEXAS T150 LCD (Sci/Stat. 2 Con Mem)	£23.00
TEXAS T125 LCD (Sci/Stats)	£17.00
TEXAS T53 (Sci. 32 Prog Steps-Coa Mem + 80 Prog List Applications book)	£25.00

Make more of your Texas T158/59 Calculator MATH/UTILITIES MODULE

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

Module includes:

Prompter. Alpha Messages. Printer Formatting. Superplotter. Sorting. Data Arrays. Data Packing. Prime Factors. Hyperbolic Functions. Gamma / Factorial. Random Numbers. Normal Distribution. Interpolation. Roots of a Function. Minimax. Romberg Integration. Differential Equations. Discrete Fourier Series. Calculator Status. Variable Arithmetic. Module Check.

*TEXAS T158 with Maths/Utilities	£90.00
*TEXAS T159 with Maths/Utilities	£186.50
*TEXAS T158 with Applied Statistics	£80.00
*TEXAS T159 with PC100C & Applied Statistics	£305.00

SPRING SALE

*TEXAS T159 Calculator (complete as manufacturer's spec. master module, charger, etc.). PLUS statistics module and extra set of 40 Blank Prog. Cards with wallet, etc.

ONLY £180

NEW TEXAS T158C*

*Continuous program facility on all 480 Program steps/60 mem even when calculator switched off	£79.50
*TEXAS T158C (complete plus Applied Stats. Module)	£99.00
*TEXAS T158C + PC100C	£208.00

*HP33E (8 mem. Pro Sci/Sta)	£50.75
*HP32E (Advanced Sci with Statistics)	£40.50
*HP67A (K Prog 224 Steps 26 Mem)	£188.70
*HP97A (Fully prog with Printer)	£384.35
HP41C (the newest calculator from HP)	£173.48
CASIO FX8100 (10 dig Sci/Sta. Stop Watch/Alarm)	£27.73
CASIO FX501P (Sci. LCD Prog. 128 Steps 11 Mem)	£47.50
CASIO FX502P (Sci. LCD Prog 256 Steps. 22 Mem)	£65.00
CASIO Prog Adaptor — permits Progs to be recorded on to standard cassette recorders for replay on Casio FX501P/Ex502P at later stage	POA

LEXICON LANGUAGE TRANSLATOR

(With 6 Lang. Module — French / Italian / German / Spanish etc)

£128.70

NOW IT'S YOU AGAINST 'COMPUTERS'

CHESS CHALLENGER "7" (7 Levels of game)	£76.50
CHESS CHALLENGER "VOICE" (10 Levels — beginner to Master Plus) The strongest Prog yet in this series — twice as fast as the other challengers. A microprocessor with 128,000 to 160,000 bits of read only Mem. Over 8000 bits of Random Access Mem. Teaches opening & end game solutions. Plays against itself. Solves book problems etc — and in addition IT SPEAKS. Complete with Deluxe playboard, hand carved men with magnetised base plus Deluxe carry case	POA
SARGON. The most advanced chess game yet with ad on module availability for other games	POA

FREE — mains/Charger included

LEARNING AIDS

TEXAS DATAMAN (Number Games-Table learning etc. 5/10 yrs)	£18.00
TEXAS SPELLING B (Spelling Games ideal 5/10 years)	£22.50
TEXAS SPEAK AND SPELL (for older children 8/13 years)	£39.95

IDEAL FOR STUDENTS ALL WITH LCD DISPLAY

TEXAS T120 (Jun Sci + Con Mem)	£13.00
TEXAS T135 (Sci/Stat C Mem)	£17.00
TEXAS T138 (Sci/Con Mem-Pola Rec Cony Dec Deg conv/ Deg Min Sec)	£19.95
CASIO FX3200 (Sci/Stat 10 Dig)	£19.00

GOODS FULLY GUARANTEED PRICES EXCLUDE VAT (ADD 15%)

Company / Hospital and Government orders accepted by phone

Barclaycard / Visa / Access accepted by phone

TEL. 01-455 9823

EXPORT ORDERS WELCOMED

Air Freight / Air Post Delivery
Quotations on request

MOUNTAINDENE

22 Cowper St., London, EC2

NEWS:Digest

April Fool


Did you spot our deliberate mistakes (well, that's our story) last month? You may have found the contents page listing a shade inaccurate after the circuit supplement. As the supplement is extra to the magazine, its pages are numbered separately. So, to find

the Touch Dimmer, for instance, take 16 (the size of the supplement) from 87 and there it is on page 71.

We've already had numerous letters and phone calls about the disembodied program listing which appears on the last Tech Tip page. So, you want to know what it is? Have a look at Tech Tips this month.



It had to happen. The integrated circuit is so old that it has earned its place in a museum. Doesn't it make you feel old? The world's first IC, invented by Jack Kilby of Texas Instruments in 1958, is one of three exhibits on loan from TI in Dallas for the 'Challenge of the Chip' exhibition at the Science Museum. The other two are the first silicon transistor and the first single chip microcomputer.

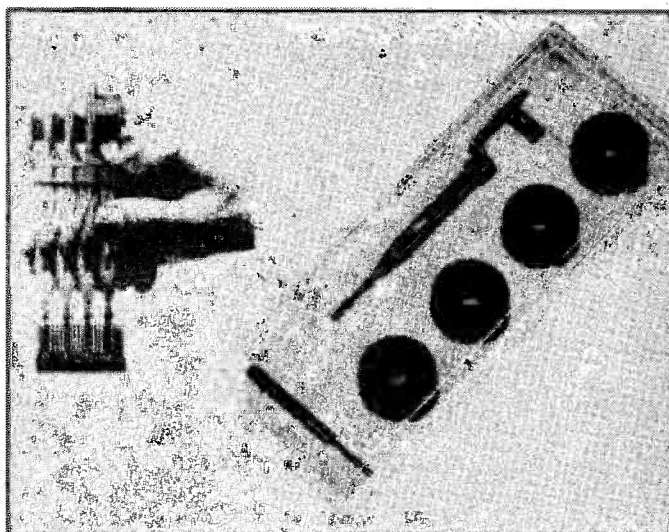

Wrap Up

This low cost wire wrapping kit caught our eye. We reckoned it was inexpensive enough for any hobbyist or small scale producer to consider buying.

It wraps 30 AWG wire onto standard 0.0025in square posts without stripping or slitting the insulation. It can 'daisy chain' continuously through several points or can be used in the point-to-point mode; it also has a

built-in wire cut-off device for terminating the final connection of each chain.

The JWK-6 kit contains the 'Just Wrap' wrapping tool, the JUW-1 unwrapping tool and four 50ft wire refill cartridges, one each of red, white, blue and yellow insulation for colour coding. All packaged in a sturdy clear plastic box. The 'Just Wrap' kit is available at £18.65 excluding VAT and delivery from: OK Machine & Tool (UK) Ltd, Dutton Lane, Eastleigh, Hants SO5 4AA.

LAMP STRINGS

New 40 Lamp Strings approx. 25ft. long. Each Lamp has individual socket and can be easily replaced. Suitable for 230V Operation.

Ideal for DISCOS, SHOP DISPLAYS, FAIRGROUNDS, etc.

LS3—4 Strings one ea. Red, Green, Blue, Yellow £15.00

SL1—100 Spare Lamps, 25 each Colour £5.75

SS1—Single String (State Colour) £4.50

Prices INCLUDE VAT and P&P, plus Instructions, etc. (No soldering is needed to use these items).

TRADE ENQUIRIES INVITED

JH ASSOCIATES LTD.

52 Silver Street, Stansted, Essex
Tel. 0279 814929.

Telex: 81675 J-LAMPS G

OLIVETTI TE300 ASR 10CPS (Paper Tape Punch/Reader included). Terminal for sale. Full working condition. £195. Telephone 995 8038 Day or 749 2750 Eves.

E.T.I. 4600 SYNTHESIZER. Recently completed, fully calibrated and ready to play. Must sell to finance next project, hence first reasonable offer accepted. Phone Hull (0482) 497944 office hours.

FREE 1980 AMTRON CATALOGUE with new range of kits and equipment cabinets. Send S.A.E. Amtron UK Ltd., 7 Hughenden Road, Hastings, Sussex TN34 3TG. Tel: Hastings 436004.

5 MHZ PORTABLE OSCILLOSCOPE FOR SALE. Heathkit model 10-4540. Built and working as new. Manual supplied. £100 o.n.o. — Tel. Waltham Cross 27351 (evgs.).

CALCULATOR KEY BOARDS. High quality, seventeen, tactile, diaphragm keys, two switches. Aluminium module, 10 x 8 cm. £1 per unit, 6 for £5. P&P inclusive. Linklater, 13 Kiver Road, London, N.19.

TTL 74 PACK. 10 Assorted, top quality devices, good selection, £1 per pack. Also 555 timers, 20p each. Postage and packing 25p. L. Starling, 8 Ashwell Road, Bygrave, Herts.

GOOD HOME WANTED for pair of Celestion Ditton 66 loudspeakers, excellent condition (ex-ETI Audiophile System) £200. Buyer collects. Ring Erith 47706 after 7 p.m.

TGS GAS SENSORS 812 & 813. Send addressed envelope 6½" x 9" for Tech. Data and Prices. Design service also available. Asti Supplies Ltd., Shannon, Co. Clare, Ireland.

If you find an ad unacceptable, don't turn the page: turn to us.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

AD. INDEX

AJD DIRECT SUPPLIES	49	INTRACEPT ELECTRONICS	69
AKHTER INSTRUMENTS	39	JAYEN DEVELOPMENTS	29
ALCON INSTRUMENTS	26	JEREMY LORD SYNTHESISERS	69
ALTEK INSTRUMENTS	68	KODE SERVICES	123
AMBIT INTERNATIONAL	5	LASCAR ELECTRONICS	58
AUDIO ELECTRONICS	117	LB ELECTRONICS	108
AURA SOUNDS	77	L & B ELECTRONICS	104
AUTEX INTERNATIONAL	47	L.S.M. PRODUCTS	87
B. BAMBER	102	MAGNUM AUDIO	68
BARINGLOCK LTD.	117	MAPLIN	98 & 132
BAYDIS	47	MARSHALLS	108
BI-PAK SEMICONDUCTORS 18 & 19	122	METAC	27
BK ELECTRONICS	89	MICRO CIRCUITS	104
T. J. BRINE ASSOCIATES	81	MIDLAND TRADING CO.	14 & 15
CALCULATOR SALES & SERVICE	38	MIGHTY MICRO	85
CAMBRIDGE LEARNING ENTERPRISES	125	MOUNTAINDENE	13
CHILTMead	80	E. R. NICHOLLS	39
CHROMASONICS	63	NIC MODELS	87
CLEF PRODUCTS	39	N.R.S.A.	102
CODESPEED	10	N.T.C.	81
COMMODORE SYSTEMS	131	POLAR ENTERPRISES	127
COMP, COMP, COMP	106	POWERTRAN COMPUTERS	124
CRIMSON ELEKTRIK	63	POWERTRAN ELECTRONICS	2 & 9
CROFTON ELECTRONICS	43	PRENTICE-HALL	49
C.S.C.	127	PROGRESSIVE RADIO	126
DELTA TECH & Co.	122	PROTON ELECTRONICS	117
DIGISOUND	48	J. W. RIMMER	117
DISPLAY ELECTRONICS	32	ROMANE ELECTRONICS	29
DORAM ELECTRONICS	81	R.T.V.C.	110
E.D.A.	86	SCIENCE OF CAMBRIDGE	54 & 55
ELECTRO-TECH	123	SINCLAIR ELECTRONICS	39
ELECTROVALUE	87	SONASONICS	89
FRINGEWOOD ELECTRONICS	112 & 113	C. N. STEVENSON	30
GMT ELECTRONICS	68	SURETRON SYSTEMS	69
GP INDUSTRIAL	118	SWANLEY ELECTRONICS	106
GREENBANK	88	TANGERINE	4
GREENWELD	97	TECHNOMATIC	12
HAMEG LTD.	58	TELERADIO	89
HAPPY MEMORIES	7	TEMPUS	120 & 121
HEATHKIT	62, 117 & 123	TK ELECTRONICS	97
HENRY'S RADIO	56 & 57	TRANSAM COMPONENTS	107
ILP	63	VIDEOTONE	16
INTEGREX LTD.	126	WATFORD ELECTRONICS	6 & 7
INTERFACE COMPONENTS		WILLIAM STUART SYSTEMS	89
		WILMSLOW AUDIO	58

COMPUKIT UK101

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER



Simple Soldering due to clear and concise instructions compiled by
Dr. A.A. Berk, BSc. PhD.

★ 6502 based system — best value for money on the market.
★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

Build, Understand and Program
your own Computer for
only a small outlay

KIT ONLY **£199** + VAT
NO EXTRAS NEEDED

AVAILABLE READY
ASSEMBLED & TESTED
READY TO GO FOR **£249** + VAT

Specially designed case for CompuKit in orange/black.
With room for accessories. **£29.50** + VAT

6502 Assembler/Editor for CompuKit **£14.90** + VAT

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programs. By pressing the C key the world of Basic is open to you.

This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use.

Because of the enormous volume of users of this kit we are able to offer a **new reduced price of £199** + VAT

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes 10 for	£4.00
Super Multi-rail P.S.U. +5 -5 +12v	£29.50
ETI Breakout Game — Chip and PCB	£9.90
S100 Expansion Motherboard for Nascom I	£39.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Disks 5 1/4" Hard & Soft Sector	£3.50
Floppy Disk Library Case 5 1/4"	£3.50
Eprom Boards	£63.00
8K Static Ram Boards — S100	£110.00
Cartridges for Grandstand	£11.99
George Risk Ascii Keyboard	£39.00
Cartridges for Atari — Full Range in Stock	£13.90
Interface PET IEEE — Centronics Parallel Not decoded £49.00 Decoded £77.00	
Interface to Centronics parallel for TRS80	£75.00
Verocases for Nascom 1 & 2 etc.	£22.50
Keyboard Cases	£9.90
Electric Pencil for TRS80	£29.00

NASCOM-2 MICRO-COMPUTER



only **£295**
+ VAT

Your choice of freebies with
every Nascom 2 purchased from us
either **FREE POWER SUPPLY**
OR **FREE GRAPHICS ROM**
OR **FREE VERO CASE TO**
TAKE NASCOM 2

Microprocessors Z80A, 8 bit CPU. This will run at 4MHz but is selectable between 1/2/4 MHz. This CPU has now been generally accepted as the most powerful, 8 bit processor on the market.

INTERFACE

Keyboard New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding.

T.V. The lv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T V.

I.O. On-board UART (Int.6402) which provides serial handling for the on-board cassette interface or the RS232/20mA teletype interface.

The cassette interface is Kansas City standard at either 300 or 1200 baud. This is a link option on the NASCOM-2. The RS232 and 20mA loop connector will interface directly into any standard teletype.

The input and output sides of the UART are independently switchable between any of the options —

i.e. it is possible to house input on the cassette and output on the printer.

P.I.O There is also a totally uncommitted Parallel I/O (MK3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.

Documentation Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.

Basic The Nascom 2 contains a full 8K Microsoft Basic in one ROM chip with additional features like DEEK, DOKE, SET, RESET for simple programming.

With free 16K RAM board.

only **£356** + VAT




**TRS80
LEVEL 2 16K**

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals, UK Power Supply — Cassette Leads — Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available.
Model with numeric key pad **£389** + VAT
4K Level I — machine only **£251** + VAT

NEW REDUCED PRICES

8K **£449**
16K **£549**
32K **£649**

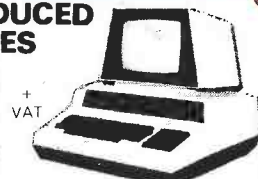


RRP **£795**
for 32K

The PEDIGREE PETS

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen.

Extra cassette deck **£55** Full range of software available

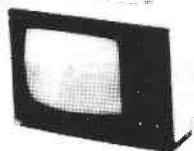

video 100

12" BLACK & WHITE
LOW COST VIDEO
MONITOR

RRP **£79**

only **£69** + VAT

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3dB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum in Central 80% of CRT; 550 Lines Minimum beyond central 80%.

COMP SHOP
"Europe's Largest Discount
Personal Computer Store"

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMP SHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number.

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G

Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday

Close to New Barnet BR Station — Moorgate Line.

★ NOW in IRELAND at: 80 Marlborough St., Dublin 1. Tel: Dublin 749933

COMP COMPUTER
COMPONENTS

(Part of the Compshop Ltd. Group)



STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**



Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____



MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.


Warp Factor 1

You may have seen this gadget demonstrated on telly a while ago. The Zerostat Z-track tone arm/cartridge damper has an effective mass of only ½ gm. It manages to improve tracking ability, reduce mechanical and acoustic feedback, attenuate unwanted subsonic signals (protecting the amplifier from overloading and the speakers from excessive cone movement) and minimise the effects of record warps.

The Z-track damper fits on to

most head shells. It contains a tiny, silicone fluid-damped piston and rides on a low-friction PTFE skid wide enough to ride on the record surface without tracking. Life expectancy is of the order of 1,000 12" sides. Badly warped records magically become playable and mildly warped records sound as if they were perfectly flat.

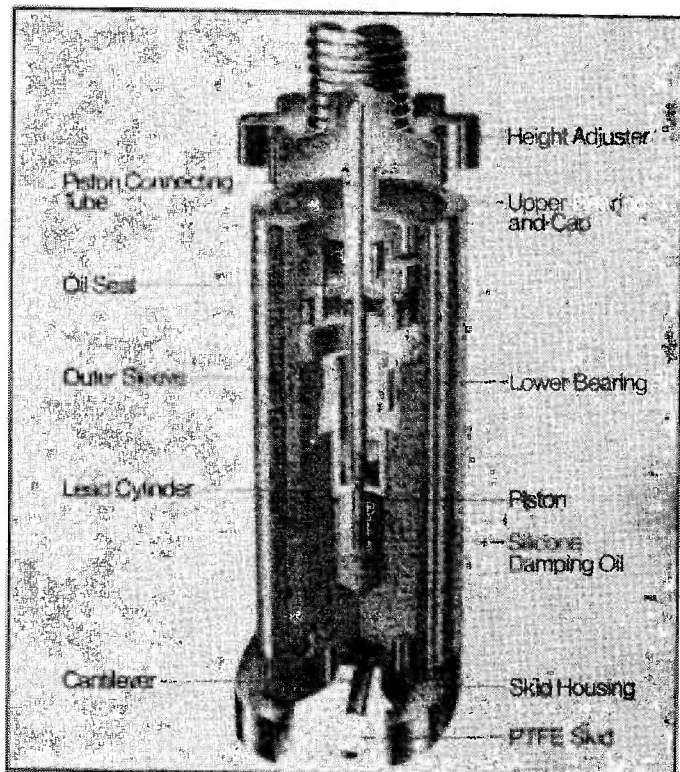The Z-track is adjustable for most tone arm/cartridge combinations. Cost? — £9.95, about the price of two LPs. For further information contact Zerostat Components Ltd, St Ives, Cambs PE17 4LF.



Creditel

You'll soon be able to make phone calls by credit card. The Post Office has just ordered a quarter of a million plastic telephone credit cards for the likes of you and I.

Charges for using the card will be included on your phone bill. As anyone can use a card to make

a call (just give the operator the card number), it's vital to keep it in one of those important little places where no-one else can get at it.

The Post Office has arranged with some foreign countries that credit card calls may be made back to the UK from abroad. You still have to pay in the end, though.

Comparatively New

The uA193/293/393 series of dual comparators from Fairchild consists of two independent precision voltage comparators, specifically designed to operate from a single power supply of +2 to +36 volts.

The devices feature a Darling-ton connected PNP input stage which allows the input common-mode voltage to include ground. Current drain (independent of the

supply voltage rail) is low (400 uA) and offset voltage is only ±2 mV for the military version. Use of a split power supply is also possible.

Applications include simple analogue to digital converters, MOS clock timers and high voltage digital logic gates. The uA193 series comparators are direct replacements for the LM193 family. Further information, application notes, etc are available from Fairchild Camera & Instrument (UK) Ltd, 230 High Street, Potters Bar, Herts EN6 5BU.

MITRAD (MIDLAND TRADING COMPANY) ZETRON!

Take you into the Eighties with two really superb pieces of modern technology

GENT'S ALARM CHRONO (12/24 CYCLE)

A really superb watch and module with numerous facilities available. It can be set as a 12 or 24-hour watch with hours, minutes, seconds, a.m./p.m. and weekday indication always on display. A unique calendar is built into the watch. You can have month followed by date or date followed by month. It's entirely up to you. A 24-hour alarm can be set to anytime within a 24-hour period whether in the 12 or 24 cycle.

The chronograph has a twelve-hour capacity and runs at 1/105. Split and lap mode facilities are available.

Battery hatch, mineral glass, long life battery and a closely woven adjustable stainless steel strap finish the watch off with impeccable looks.

ONLY £16.50!

GENT'S QUARTZ ANALOGUE

A truly superb timepiece with extreme accuracy. A choice of two colours on this outstanding watch are available. Blue or white.

The calendar in the watch can be set to give a readout in either French or English, with date indication being automatic.

An infinite adjustable stainless steel strap is built in as part of the watch.

The watch is fitted with a long-life battery and comes with luminous marking to aid night-time vision.

ONLY £19.95

**ZETRON! WHERE RELIABILITY
STYLE AND ELEGANCE
REALLY COUNT ZETRON!**



MITRAD

(MIDLAND TRADING COMPANY)

ZETRON! THE UNRIVALLED RANGE IN ELECTRONIC DIGITAL WATCHES. ZETRON!

GENTS (4 BUTTON) CHRONO

A new style chronograph with two buttons either side of the watch. Constant display of hours, mins, secs with the added feature of weekday and am/pm indication. Month, date and weekday is an optional display with date indicator. The chrono has split and lap mode facilities running to 1/100sec, 10 function, 4 flags and 6 digits. Back-light and adjustable stainless steel strap.


ONLY £8.95



GENTS CHRONO ALARM (FRONT BUTTON)

Brand new 1980 style. Basic working modes of chronograph, 24 hour alarm and dual time zone. Constant display of hours, mins, secs and weekday indication with am/pm, T2 and A1 flags. Date indication. The chrono runs to 1/10th sec, with the 1/10th's running along the bottom of the watch. It has a twelve hour capacity. The 24 hour alarm system is actuated for a full 60 seconds. Dual timing facilities give the watch the added touch of compactness. Back-light, closely woven adjustable stainless steel strap.

ONLY £15.50

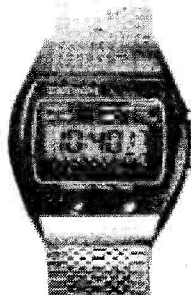

GENTS MELODY ALARM CHRONO

Brand new 1980 style. Another unique watch from the Zetron range. Constant display of hours, mins, secs, weekday, am/pm and mode square flag indication. The chrono runs to a 1/10th sec with split and lap mode facilities. Dual timing facilities are available. A musical tune "Yellow rose of Texas" is used as the alarm system, which plays for 20 secs. The tune can also be activated at an instant with the press of a button. Back-light. Another unique feature is the fact that the infinite adjustable stainless steel strap is built in as part of the watch.


ONLY £17.75



GENTS MEMORY CALENDAR ALARM CHRONO

LATEST TECHNOLOGY! Constant display of hours, mins, secs, weekday and snooze alarm indication. A further two optional display modes are available, one being the calendar and month, which can be increased or decreased to give the appropriate month of the year. A 1/100th sec chrono with split and lap mode facilities is built into the watch. A 24 hour alarm with a 10 minute snooze function is also standard to the watch. A further feature is the back-light and fully adjustable stainless steel strap.

VALUE AT £19.95

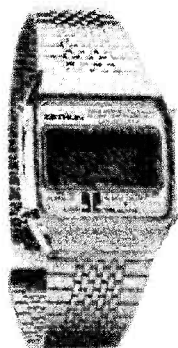

GENTS MELODY MULTI CHIME ALARM CHRONO

Latest technology! Constant display of hours, mins and secs, weekday, date and month with mode and chime indication display. The musical alarm once actuated plays the tune "Oh Suzanna". Two further alarm systems are incorporated in this outstanding watch: (i) 24 hour alarm; (ii) count down alarm. The watch can be set to chime on every full hour. A 1/100th sec chrono is standard to the watch. Can be switched off. Mineral glass face. The watch also has a battery hatch backlight and infinitely adjustable stainless steel strap.

VALUE AT £19.95



LADIES COCKTAIL

Elegance and style for the lady with the discerning taste. In gold or silver finish with matching bracelet. Constant display of hours and mins with month, date, secs, auto calendar and back-light.

VERY SPECIAL £10.50



LADIES SUGAR

Another superb ladies watch with that extremely popular sugar frosted finish. Links can easily be removed from the strap and the clasp has a spring mechanism built in to give a comfortable fitting. Constant display of hours and mins, with month, date, secs, auto calendar and back-light.

£10.50



GENTS CHRONOGRAPH

Probably the best looking chrono on the market. Constant display of hours, mins, secs with am/pm indication. Also month, date and weekday indication. 1/100th and 1/10th sec with split and lap mode facilities. Back-light, closely woven adjustable stainless steel strap.


SPECIAL £8.95



GENTS FRONT BUTTON ALARM

Latest style! Constant display of hours, mins, secs, am/pm, weekday and alarm indication. A further two optional display modes are available. The watch comprises of 7 digits, 12 function and is programmed to the year 2009. The alarm can be set to any time within 24 hours and operates for 30 sec. Back-light and a closely woven adjustable stainless steel strap finish the watch off with a really superb sleek look, only 8mm thick.

£13.25

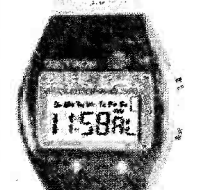

ZETRON! WHERE RELIABILITY, STYLE AND ELEGANCE REALLY COUNT ZETRON!

Before buying a digital watch, consider the following points we offer:

- (i) 48 hour despatch guaranteed.
- (ii) Full instructions and 12 month guarantee.
- (iii) 10 day money back guarantee if not completely satisfied.
- (iv) Free felt presentation case with each watch.
- (v) Our own personal satisfaction guarantee.

Phone or write for full comprehensive catalogue on the complete range of digital watches we carry. Large discounts available for bulk buyers. Trade lists on application. P&P per item 85p which includes insurance. Cheques or PO's should be made payable to **MITRAD** and sent to **Dept (ETI), 58 Windmill Ave, Kettering, Northants, NN16 8PA. Kettering 522024 (STD 0536).**

SAVE-SAVE-SAVE!

HI-FI AT DIRECT TO YOU PRICES!

LOUDSPEAKERS
ON 21 DAY
HOME TRIAL!

**The
SMART WAY
TO BUY
HI-FI**

**ALL
PRODUCTS ON
DISPLAY & CONTINUOUS
DEMONSTRATIONS**

In our showrooms, all products are available on continuous demonstration including comparisons with competitive products. Bring your own records. Discuss your problems with fully qualified staff. Ours is a proper demonstration, not a cramped, overstocked shop.

**LOADS OF
BARGAINS**

MOST LEADING MAKES AVAILABLE

SPEAKERS
Minimax II

£44.00

GB 3

£50.00

GB 2

£60.00

SA4130 30 watt
amplifier

£75.00

FST4120 stereo
tuner

£68.00

SC3200 cassette
deck

£98.00

WA7700 50 watt
amplifier

£77.00

Coral cartridges

MC81

£48.87

777EX

£35.00

HEADPHONES

HP80

£9.69

HP90

£12.65

*The
NEW*

VIDEOTONE

FULL DEMONSTRATION STUDIOS
CALL IN TODAY —NO PARKING
PROBLEMS

98 CROFTON PARK ROAD CROFTON PARK SE4

Tel: 01-690 8511/2 Open 9 am to 5.30 pm. Mon to Sat

SEIKO CALCULATOR ALARM

OVER 30% OFF
NORMAL SELLING
PRICE

Features:

TIME DISPLAY
DAY/DATE/MONTH DISPLAY
8-DIGIT CALCULATOR WITH %
FULL ALARM FACILITY
STAINLESS STEEL BRACELET
EASY BATTERY CHANGE
(AVERAGE LIFE : 2YRS)



£69.95 All Inc.

Don't count on this

ever appearing cheaper anywhere else. We don't think it will somehow. Yet again ETI brings you the best of modern technology at ridiculous prices. Following up our extremely successful offer on Seiko's first calculator watch last year we thought that since they'd improved the timepiece, we'd improve the offer!

The watch is no larger than a normal un-calculator un-alarm job but boasts enough facilities to make Big Ben jealous! And with the price as small as the watch we don't see how you can live without one!

To ETI Calculator Watch Offer, Modmags Sales Office,
145 Charing Cross Road, London WC2H 0EE.

I enclose cheque/PO nos. to value for
Seiko Alarm-Calculators.

Name

Address

.....

SEMICONDUCTORS

TRANSISTORS

Part	Price	Type	Part	Price	Type	Price	Type	Price	Type	Price
AC107	£0.23	BC134	£0.21	BD178	BF179	£0.32	ZTX109	£0.12	2N3416	£0.33
AC113	£0.23	BC135	£0.17	BD179	BF80	£0.32	ZTX130	£0.14	2N3417	£0.33
AC115	£0.23	BC136	£0.21	BD180	BFK29	£0.25	ZTX132	£0.10	2N3514	£1.15
AC117	£0.35	BC137	£0.21	BD181	BFK30	£0.35	ZTX1302	£0.18	2N3615	£1.21
AC117K	£0.35	BC139	£0.37	BD182	BFK84	£0.25	ZTX1303	£0.18	2N3616	£1.21
AC121	£0.23	BC140	£0.35	BD183	BFK85	£0.28	ZTX1304	£0.23	2N3646	£0.10
AC122	£0.16	BC141	£0.32	BD184	BFK86	£0.29	ZTX1330	£0.17	2N3702	£0.09
AC125	£0.25	BC142	£0.22	BD185	BFK87	£0.30	ZTX150	£0.15	2N3703	£0.09
AC126	£0.21	BC143	£0.25	BD186	BFK88	£0.25	ZTX150	£0.14	2N3704	£0.09
AC127	£0.21	BC145	£0.53	BD187	BFK90	£0.43	ZTX1502	£0.18	2N3705	£0.08
AC128	£0.18	BC147	£0.08	BD188	BFY50	£0.20	ZTX1503	£0.14	2N3706	£0.09
AC128K	£0.30	BC148	£0.08	BD189	BFY51	£0.20	ZTX1504	£0.29	2N3707	£0.09
AC132	£0.23	BC149	£0.08	BD190	BFY62	£0.20	ZTX1531	£0.29	2N3708	£0.08
AC133	£0.23	BC150	£0.08	BD195	BFY63	£0.20	ZTX1550	£0.29	2N3708A	£0.08
AC137	£0.23	BC151	£0.25	BD196	BP19	£0.44	2N388	£0.41	2N3709	£0.08
AC141	£0.25	BC152	£0.25	BD197	BP120	£0.44	2N388A	£0.44	2N3710	£0.08
AC141K	£0.35	BC153	£0.29	BD198	BP19/20	£0.92	2N404	£0.23	2N3711	£0.08
AC142	£0.42	BC154	£0.22	BD199	BSX25	£1.87	2N524	£0.48	2N3772	£1.84
AC142K	£0.42	BC155	£0.12	BD200	BSK19	£1.01	2N527	£0.58	2N3773	£2.53
AC151	£0.23	BC158	£0.08	BD201	BSV25	£0.18	2N589	£0.53	2N3829	£0.21
AC153	£0.25	BC159	£0.12	BD202	BSV26	£0.18	2N589	£0.53	2N3829	£0.21
AC153K	£0.35	BC160	£0.30	BD207	BSV26	£0.18	2N696	£0.15	2N3821	£0.69
AC154	£0.23	BC161	£0.44	202mp	BSV27	£0.18	2N697	£0.14	2N3823	£0.69
AC155	£0.23	BC167	£0.14	BD203	BSV28	£0.18	2N698	£0.14	2N3803	£0.12
AC156	£0.23	BC168	£0.14	BD204	BSV28	£0.18	2N699	£0.37	2N3804	£0.12
AC157	£0.29	BC169	£0.10	BD203	BSV28	£0.18	2N708	£0.08	2N3806	£0.12
AC165	£0.23	BC169C	£0.12	204mp	BSV39	£0.22	2N708A	£0.14	2N3806	£0.12
AC166	£0.23	BC170	£0.10	BD205	BSY40	£0.33	2N707	£0.55	2N4058	£0.14
AC167	£0.23	BC171	£0.10	BD206	BSY41	£0.33	2N708	£0.16	2N4059	£0.16
AC168	£0.29	BC172	£0.10	BD207	BSY51	£0.15	2N711	£0.35	2N4060	£0.16
AC169	£0.29	BC173	£0.10	BD208	BSY51	£0.15	2N717	£0.35	2N4061	£0.14
AC171	£0.29	BC174	£0.17	BD222	BSY95A	£0.82	2N718	£0.35	2N4061	£0.14
AC176	£0.21	BC175	£0.40	BD225	BRV39	£0.52	2N718A	£0.58	2N4061	£0.14
AC176K	£0.30	BC177	£0.18	BD232	BU105	£1.84	2N726	£0.33	2N4923	£0.73
AC178	£0.29	BC178	£0.18	BD233	BU105/02	£2.24	2N727	£0.33	2N5135	£0.12
AC179	£0.29	BC179	£0.18	BD233	BU204	£1.81	2N743	£0.23	2N5136	£0.12
AC180	£0.29	BC180	£0.18	BD235	BU204	£1.81	2N744	£0.23	2N5138	£0.12
AC180K	£0.32	BC181	£0.10	BD236	BU208	£0.92	2N914	£0.25	2N5172	£0.12
AC181	£0.32	BC182	£1.25	BD237	BU208/02	£2.59	2N918	£0.35	2N5192	£0.84
AC181K	£0.32	BC182	£0.10	BD238	BU208/02	£2.59	2N929	£0.23	2N5245	£0.36
AC187	£0.21	BC183	£0.10	BD239A	MJE2955	£1.09	2N930	£0.21	2N5294	£0.49
AC187K	£0.32	BC183L	£0.10	BD240A	MJE3440	£0.60	2N946	£0.46	2N5296	£0.41
AC188	£0.32	BC184	£0.10	BDY11	MJE119	£0.92	2N1131	£0.21	2N5457	£0.37
AC188K	£0.32	BC184L	£0.10	BDY11	MPF102	£0.32	2N1132	£0.21	2N5457	£0.37
ACV17	£0.40	BC186	£0.25	BDY17	MPF104	£0.40	2N1302	£0.17	2N5459	£0.40
ACV18	£0.40	BC187	£0.25	BDY20	MPP105	£0.40	2N1303	£0.21	2N5551	£0.41
ACV19	£0.40	BC207	£0.13	BDX77	MPSA005	£0.23	2N1304	£0.21	2N6027	£0.39
ACV20	£0.40	BC208	£0.13	BF115	MPSA006	£0.23	2N1305	£0.21	2N6121	£0.81
ACV21	£0.40	BC209	£0.13	BF116	MPSA007	£0.23	2N1306	£0.28	2N6122	£0.81
ACV22	£0.40	BC212	£0.10	BF118	MPSA56	£0.23	2N1307	£0.35	2N6123	£0.81
ACV27	£0.40	BC212L	£0.10	BF119	ND120	£0.21	2N1308	£0.35	2N6124	£0.81
ACV28	£0.37	BC213	£0.10	BF121	OC20	£2.13	2N1309	£0.35	2S302A	£0.49
ACV29	£0.56	BC213L	£0.10	BF123	OC22	£1.73	2N1699	£0.40	2S303	£0.64
ACV30	£0.40	BC214	£0.10	BF125	OC23	£1.73	2N1699	£0.40	2S303	£0.64
AD130	£0.40	BC214K	£0.40	BF125	OC23	£1.73	2N1699	£0.40	2S303	£0.64
AD130K	£0.81	BC225	£0.30	BF152	OC26	£1.15	2N1711	£0.23	2S305	£0.92
AD140	£0.69	BC226	£0.41	BF153	OC26	£1.15	2N1880	£0.52	2S306	£0.92
AD142	£0.98	BC227	£0.18	BF154	OC28	£0.92	2N1893	£0.35	2S321	£0.68
AD143	£0.86	BC238	£0.18	BF155	OC29	£1.09	2N2147	£0.86	2S322	£0.49
AD149	£0.69	BC239	£0.17	BF156	OC31	£1.04	2N2148	£0.81	2S322A	£0.49
AD150	£0.69	BC239A	£0.17	BF156	OC36	£0.92	2N2149	£0.81	2S323	£0.66
AD162	£0.40	BC301	£0.32	BF158	OC41	£0.23	2N2150	£0.40	2S323	£0.66
AD161/2	£0.81	BC302	£0.33	BF159	OC42	£0.25	2N2193	£0.44	2S325	£0.00
AF124	£0.35	BC303	£0.32	BF160	OC45	£0.28	2N2194	£0.44	2S326	£0.82
AF125	£0.35	BC304	£0.44	BF162	OC44	£0.23	2N2217	£0.25	2S327	£0.82
AF126	£0.35	BC305	£0.18	BF163	OC45	£0.28	2N2218	£0.25	40311	£0.42
AF127	£0.35	BC308	£0.18	BF166	OC71	£0.28	2N2218A	£0.23	40313	£1.09
AF139	£0.40	BC337	£0.17	BF165	OC72	£0.28	2N2194	£0.44	40314	£0.99
AF178	£0.69	BC338	£0.17	BF167	OC74	£0.30	2N2219A	£0.28	40317	£0.46
AF179	£0.69	BC440	£0.35	BF173	OC75	£0.35	2N2220	£0.23	40326	£0.46
AF180	£0.69	BC440	£0.35	BF176	OC76	£0.40	2N2221	£0.23	40327	£0.52
AF186	£0.69	BC441	£0.44	BF178	OC77	£0.35	2N2221A	£0.25	40346	£0.52
AF186K	£0.69	BC461	£0.44	BF178	OC81	£0.68	2N2222	£0.23	40347	£0.75
AF239	£0.44	BC477	£0.23	BF179	OC81D	£0.28	2N2222A	£0.23	40348	£0.75
AL102	£1.38	BC478	£0.23	BF180	OC82	£0.28	2N2368	£0.21	40360	£0.41
AL103	£1.36	BC479	£0.23	BF181	OC82D	£0.35	2N2369	£0.16	40362	£0.44
ASV26	£0.44	BC547	£0.12	BF182	OC83	£0.30	2N2369A	£0.16	40406	£0.52
ASV27	£0.44	BC548	£0.12	BF183	OC83	£0.30	2N2421	£0.29	40407	£0.40
ASV28	£0.44	BC549	£0.12	BF184	OC139	£0.92	2N2421	£0.29	40408	£0.60
ASV29	£0.44	BC550	£0.16	BF185	OC140	£0.92	2N2646	£0.54	40409	£0.60
ASV50	£0.35	BC556	£0.16	BF186	OC169	£0.40	2N2711	£0.25	40410	£0.86
ASV51	£0.35	BC567	£0.15	BF187	OC170	£0.40	2N2712	£0.25	40411	£0.00
ASV52	£0.35	BC558	£0.16	BF188	OC171	£0.40	2N2714	£0.25	40430	£1.09
ASV53	£0.35	BC559	£0.16	BF189	OC20	£0.40	2N2804	£0.21	40476	£1.84
ASV54	£0.35	BC560	£0.16	BF190	OC20	£0.09	2N2805	£0.21	40477	£1.84
ASV55	£0.35	BCY31	£0.63	BF195	OC20	£0.09	2N2905	£0.21	40492	£0.81
ASV56	£0.35	BCY32	£0.69	BF196	OC202	£1.38	2N2905A	£0.23	40512	£0.55
ASV57	£0.35	BCY33	£0.63	BF197	OC203	£0.98	2N2905A	£0.23	40512	£0.55
ASV58	£0.35	BCY34	£0.69	BF198	OC204	£1.04	2N2906	£0.18	40594	£1.04
ASV73	£0.35	BCY70	£0.17	BF199	OC205	£1.32	2N2906A	£0.22	40636	£1.27
AU102	£1.61	BC171	£0.17	BF200	OC205	£1.32	2N2907	£0.23		
AU110	£1.61	BC172	£0.17	BF202	OC205	£1.32	2N2907	£0.23		
AU113	£1.61	BC210	£0.69	BF222	OC145	£0.46	2N2923	£0.25		
BC107	£0.09	BC211	£0.69	BF224	OC129A	£0.46	2N2924	£0.17		
BC107A	£0.09	BC212	£0.69	BF240	OC20	£0.20	2N2925	£0.17		
BC107B	£0.10	BD115	£0.58	BF241	OC20	£0.20	2N2926G	£0.10		
BC107C	£0.10	BD116	£0.58	BF242	OC20	£0.20	2N2926Y	£0.09		
BC108	£0.09	BD121	£0.92	BF257	OC20	£0.20	2N2926Y	£0.09		
BC108A	£0.09	BD123	£0.75	BF258	OC20	£0.20	2N2926R	£0.09		
BC108B	£0.09	BD124	£0.81	BF259	OC20	£0.20	2N2926B	£0.09		
BC108C	£0.12	BD131	£0.40	BF262	OC20	£0.20	2N3010	£0.75		
BC108D	£0.09	BD132	£0.40	BF263	OC20	£0.20	2N3011	£0.17		
BC109	£0.09	BD133	£0.40	BF264	OC20	£0.20	2N3053	£0.20		
BC109B	£0.10	132mp	£0.92	BF271	OC20	£0.20	2N3054	£0.20		
BC109C	£0.12	BD133	£0.46	BF272	OC20	£0.20	2N3055	£0.48		
BC113	£0.18	BD135	£0.44	BF273	OC20	£0.20	2N3391	£0.23		
BC114	£0.18	BD136	£0.40	BF274	OC20	£0.20	2N3391A	£0.25		
BC115	£0.22	BD137	£0.40	BF324	OC20	£0.20	2N3392	£0.23		
BC116	£0.22	BD138	£0.40	BF325	OC20	£0.20	2N3393	£0.23		
BC116A	£0.22	BD139	£0.41	BF337	OC20	£0.20	2N3394	£0.23		
BC117	£0.23	BD140	£0.41	BF338	OC20	£0.20	2N3395	£0.23		
BC118	£0.16	BD139P	£0.38	BF457	OC20	£0.20	2N3402	£0.24		
BC119	£0.29	140mp	£0.92	BF458	OC20	£0.20	2N3403	£0.24		
BC120	£0.46									

74 SERIES TTL ICs

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	€0.19	7427	€0.28	7473	€0.29	7410	€0.41	74166	€0.90
7401	€0.19	7428	€0.28	7474	€0.29	7411	€0.41	74167	€0.90
7402	€0.13	7430	€0.15	7475	€0.33	7418	€0.92	74175	€0.75
7403	€0.13	7432	€0.25	7476	€0.29	74119	€1.36	74176	€0.67
7404	€0.13	7433	€0.35	7480	€0.51	74121	€0.28	74177	€0.67
7405	€0.35	7437	€0.24	7481	€0.98	74122	€0.28	74180	€1.73
7406	€0.21	7438	€0.92	7482	€0.24	74123	€0.60	74181	€0.67
7407	€0.25	7440	€0.14	7483	€0.67	74136	€0.60	74182	€0.60
7408	€0.15	7441	€0.58	7484	€1.01	74141	€0.63	74184	€0.81
7409	€0.15	7442	€0.46	7485	€0.78	74145	€0.63	74190	€0.78
7410	€0.15	7443	€0.81	7486	€0.25	74150	€0.78	74191	€0.71
7411	€0.20	7444	€0.89	7487	€0.69	74151	€0.55	74192	€0.69
7412	€0.17	7445	€0.75	7490	€0.37	74153	€0.55	74193	€0.55
7413	€0.28	7446	€0.69	7491	€0.74	74154	€0.94	74194	€0.71
7414	€0.58	7447	€0.55	7492	€0.40	74155	€0.58	74195	€0.69
7415	€0.26	7448	€0.64	7493	€0.35	74156	€0.58	74196	€1.21
7416	€0.13	7449	€0.64	7494	€0.44	74157	€0.58	74197	€1.21
7420	€0.13	7451	€0.13	7495	€0.58	74160	€0.57	74198	€2.13
7421	€0.23	7453	€0.13	7496	€0.58	74161	€0.71	74199	€2.13
7422	€0.18	7454	€0.13	74100	€0.98	74162	€0.71		
7423	€0.24	7460	€0.13	74104	€0.45	74163	€0.71		
7424	€0.25	7470	€0.29	74105	€0.28	74164	€0.78		
7426	€0.28	7472	€0.23	74107	€0.28	74165	€0.78		

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	€ 0.18	CD4015	€ 0.94	CD4026	€ 1.38	CD4043	€ 1.01
CD4001	€ 0.23	CD4016	€ 0.49	CD4027	€ 0.58	CD4044	€ 0.94
CD4002	€ 0.18	CD4017	€ 0.94	CD4028	€ 0.78	CD4045	€ 1.61
CD4005	€ 1.06	CD4018	€ 0.98	CD4029	€ 0.98	CD4046	€ 1.60
CD4006	€ 1.06	CD4019	€ 0.98	CD4030	€ 0.55	CD4047	€ 1.00
CD4008	€ 1.06	CD4020	€ 0.49	CD4031	€ 0.82	CD4048	€ 1.15
CD4009	€ 0.52	CD4021	€ 0.94	CD4035	€ 1.38	CD4050	€ 0.55
CD4010	€ 0.55	CD4022	€ 0.94	CD4037	€ 1.09	CD4054	€ 1.27
CD4011	€ 0.23	CD4023	€ 0.22	CD4040	€ 1.01	CD4055	€ 1.15
CD4012	€ 0.23	CD4024	€ 0.22	CD4041	€ 0.51	CD4056	€ 0.85
CD4013	€ 0.48	CD4025	€ 0.72	CD4042	€ 0.83	CD4058	€ 0.20

LINEAR ICs

Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£1.75	LM301	£0.33	NE566	£0.69	UA747C	£0.69
CA3014	£1.75	LM304	£0.33	NE567	£1.33	UA747C	£0.69
CA3018	£0.75	LM308	£1.15	NE566	£1.73	UA748	£0.69
CA3020	£1.86	LM309	£1.73	NE567	£1.96	72748	£0.40
CA3028	£0.92	LM380	£0.98	UA702C	£5.73	748P	£0.40
CA3035	£1.01	LM381	£1.67	72702	£0.53	SN76013N	£0.40
CA3036	£1.15	LM3900	£0.67	UA703	£0.29		£2.01
CA3042	£1.73	MC1303	£0.98	UA709	£0.29	SN76023	£0.73
CA3043	£1.73	MC1303L	£0.98	UA709	£0.53	SN76110	£1.73
CA3046	£0.81	MC1311	£0.98		£0.29	76111	£1.73
CA3052	£1.84	TBA120	£0.60	UA710C	£0.46	SN7666C	£0.24
CA3054	£1.27	MC1312	£2.19	72710	£0.35	SL414A	£2.24
CA3075	£1.73	MC1350	£1.38	UA711C	£0.37	TAA5508	£0.49
CA3081	£1.73	MC1352	£1.61	72711	£0.37	TAA621A	£2.30
CA3089	£2.30	MC1469	£3.39	UA723C	£0.52	TAA6218	£1.78
CA3090	£4.14	MC1496	£1.04	72723	£0.52	TAA681	£2.83
CA3102	£2.19	NE536	£3.06	UA741C	£0.26	TAD100	£1.86
CA3130	£0.07	NE536	£1.09	72741	£0.23	UA8540	£2.42
CA3140	£1.81	NE555	£2.33	741P	£0.26	TBA810S	£0.60

DIODES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AA110	\$0.09	BAX13	\$0.08	BY164	\$0.50	OA10	\$0.40	SD10	\$0.07
AA120	\$0.09	BAX16	\$0.09	BY176	\$0.86	OA12	\$0.40	SD19	\$0.07
AA129	\$0.09	BY100	\$0.25	BY206	\$0.35	OA70	\$0.09	IN34	\$0.08
AA30	\$0.10	BY101	\$0.25	BY210	\$0.52	OA79	\$0.12	IN34A	\$0.08
AA213	\$0.17	BY106	\$0.25	BY211	\$0.52	OA81	\$0.12	IN914	\$0.07
BA100	\$0.12	BY114	\$0.25	BY212	\$0.46	OA85	\$0.12	IN916	\$0.07
BA102	\$0.37	BY124	\$0.25	BY213	\$0.46	OA90	\$0.12	IN1418	\$0.07
BA103	\$0.14	BY126	\$0.17	BY216	\$0.47	OA91	\$0.12	IS44	\$0.06
BA154	\$0.14	BY128	\$0.17	BY217	\$0.47	OA99	\$0.12	IS920	\$0.07
BA155	\$0.18	BY128	\$0.18	BY218	\$0.12	OA12	\$0.82		
BA173	\$0.17	BY130	\$0.20	BY219	\$0.41	OA200	\$0.09		
BB104	\$0.48	BY133	\$0.24	OA5	\$0.69	OA202	\$0.09		

TRIACS

2 amp Volts	T05 Case No.	Price	10 amp Volts	Price
100	TR12a/100	£0.36	100	TR110a/100 £0.89
200	TR12a/200	£0.59	200	TR110a/200 £1.06
400	TR12a/400	£0.82	400	TR110a/400 £1.29

BRIDGE RECTIFIERS

SILICON 1 amp			SILICON 2 amp		
Type	No.	Price	Type	No.	Price
50v RMS	BR1 50	£0.23	50v RMS	BR2 50	£0.52
100v RMS	BR1 100	£0.25	100v RMS	BR2 100	£0.55
200v RMS	BR1 400	£0.29	200v RMS	BR2 200	£0.60
400v RMS	BR1 400	£0.41	400v RMS	BR2 400	£0.67
			1000v RMS	BR2 1000	£0.78

SILICON 10 amp			SILICON 25 amp		
Type	No.	Price	Type	No.	Price
50v RMS	BR10 50	£1.73	50v RMS	BR25 50	£2.18
200v RMS	BR10 200	£1.96	200v RMS	BR25 200	£2.13

Access & Barclaycard accepted. Giro a/c no. 3887006. All prices include VAT.

Add 50p postage per order

Visit our NEW shop: 3 BALDOCK ST., WARE HERTS. Telex: 817861

AUDIO LEADS


No.	Type	Price
107	FM indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	£0.86
114	5 pin DIN plug to 5 pin DIN plug connected to pins 3 & 5. Length 1.5m	£0.98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead. Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios. 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.21
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£1.04
120	Car stereo connector. Variable geometry plug to fit most car cassettes. 8-track cartridge and combination units. Supplied with lined fuse power lead and instructions	£0.99
123	6.6m Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£1.72
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.85
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.85
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.85
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.49
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5. Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs Connected pins 3 & 5. Length 1.5m	£0.86
134	5 pin DIN plug to 2 Phono sockets Connected pins 3 & 5. Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs Connected pins 3 & 5. Length 23cm	£0.78
136	Coiled stereo headphone extension lead. Black. length 6m	£2.01
178	AC mains lead for calculators. etc	£0.52

19

PROJECT 80 FILTERS

Not one project but four. The Project 80 VCF can be constructed as any of the most useful configurations. Circuit design by Charles Blakey.

In the first article of this series (February 1980) it was stated the project is suitable for both the enthusiast and the beginner in electronic music. It is reasonable to assume that the enthusiast already has some equipment and so the ETI 80 modules offer the opportunity to extend, or upgrade, their current system. Assuming that the existing equipment is compatible with modules having an exponential frequency control response then one of the problems that is encountered is the level of signals employed. Most of the ETI 80 modules can readily be adapted to accept other signal levels. For example, we could have zero referenced the input to the following filters and omitted the buffer stage, although the high input impedance for some filters may have led to problems with noise pick-up. By including an op amp input stage we have avoided the latter potential hazard and at the same time provided a standard input summer.-

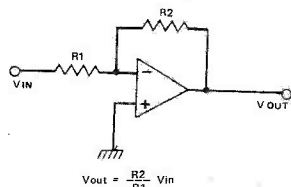


$$V_{out} = \frac{R_2}{R_1} V_{in}$$


$$\text{with } V_{out} = \frac{R_2}{R_1} V_{in}$$

If one is therefore currently using 5V P-P signals, instead of the 10V P-P employed in this project, then the only change required is to double R2 so that the other components around the special ICs employed remain unchanged. In the case of some synthesisers which combine the worst of both worlds and have very low signal levels and low input impedance then both R1 and R2 can be altered to normalise the input to that of the existing synthesiser.

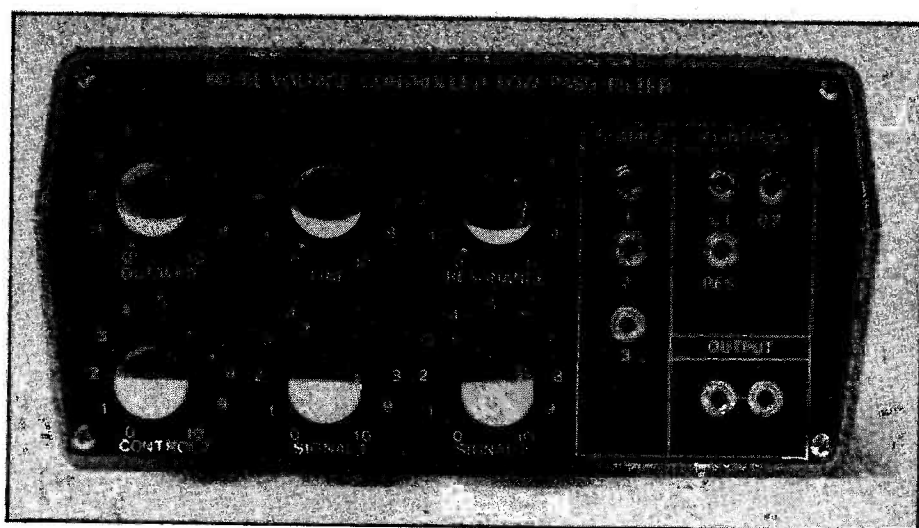Likewise, most modules will have a similar buffer at the output which allows the signals to be attenuated to their original level, for example in the case of the 5V signal then R2 has to be halved.



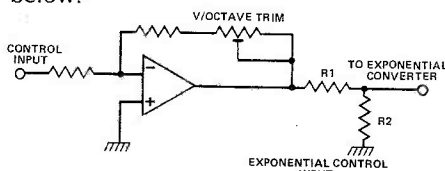Another minor problem may be the frequency response characteristics, for example, a synthesiser with a 0.5V per octave scale. All ETI 80 modules will have one or more scaling resistors which in the case of the current filter design is of the type shown below.-



where R1 and R2 are scaling resistors to give approximately 18 mV to the exponential converter for each volt applied at the keyboard control input. For the above mentioned example the only change required is doubling R2.

The final problem of compatibility is likely to be power supplies. This is most easily overcome by having separate supplies for the modules employed from this project. In most instances, however, the ETI 80 series can be run from power supplies as low as ± 9 V but this will require a number of component changes. Digisound Limited

will be pleased to advise readers of these changes.

Filters

This month we are featuring the four filters most widely used in music synthesisers. They are four pole filters with one volt per octave control of their cut-off, or centre, frequency. Voltage control of signal regeneration is also included.

Filters are normally used in three modes. Firstly, subtractive synthesis, in which partials are subtracted from complex waveforms to effect changes in tone quality. Next, in timbre modulation which allows more complex waveforms to be developed by continuously altering the amplitude of the partials present during the duration of the sound. The latter may be accomplished by using a low frequency oscillator to vary the cut-off frequency of the filter. A widely employed variation of the latter technique is the use of an envelope generator, triggered by the keyboard, to control the cut-off frequency. In this way a tone can be produced, using a low pass filter, which begins with the fundamental

followed by an increasing number of partials. The third technique is resonant synthesis in which the regeneration of the signal is increased to a level which will cause the filter to oscillate on receiving a sharp impulse, eg from an envelope generator set to minimum time constants or from a square wave and so on. This technique is widely used to produce percussive sounds.


The four filter types provided are:-

Low Pass Filter. This will pass all frequencies up to the cut-off point and beyond this the frequencies are sharply attenuated at a rate of 24 dB/octave. By increasing the resonance control a band of frequencies around the cut-off point are emphasised and the more regeneration used the more 'electronic' the sound becomes. Low pass filtering is useful in simulating the tonal characteristics of several conventional instruments.

High Pass Filter. This passes all frequencies above the cut-off point and the roll-off below this point is again 24 dB/octave. The effect of high pass filtering is therefore to remove the fundamental and lowest partials and leave only the weak upper partials. It does not therefore find widespread use in subtractive synthesis of waveforms although a sawtooth and a high pass filter will produce some bright string sounds. This filter is also of use in filtering white noise. It is not normal to include resonance control with a high pass filter because of its limited application but since its inclusion has a very small effect on the cost in the current design it has been included. Its effect is the same as with the low pass filter, namely, to emphasise a band of frequencies about the cut-off point.

Band Pass Filter. This will pass a band of frequencies at the pole frequency of the filter. It is derived from two poles of high pass followed by two stages of low pass filtering thus giving a roll-off of 12 dB/octave in either side of the centre frequency. The effect of the resonance control in this instance, however, is to emphasise the centre frequency and so effectively increase the roll-off. This filter is used in imitative synthesis but more commonly a number of band pass filters need to be employed to obtain realistic results. Similarly, a more versatile band pass filter may be created by using independent low and high pass filters so that the width of the pass band can be altered over a wide range.

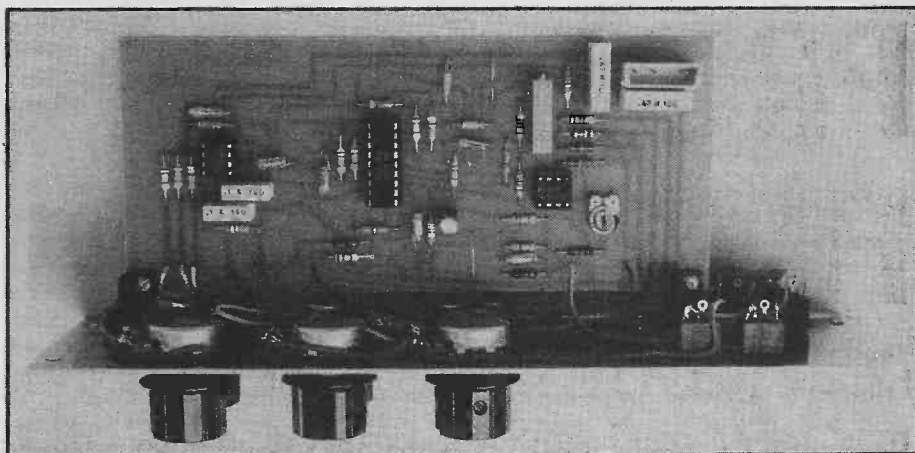Phase Shift Filter. This is an allpass filter with mixing of the original signal to create two deep notches. The effect of regeneration is to sharpen the corners of the notches and effectively increase their depth. The 'phasing' effect is well known and most of the low cost commercial 'phasers' only have two notches. A particular advantage of the design described below is its low



noise but even so we believe that six notches are a minimum for good phasing effects.

Which Filter?

As one's experience in music synthesis increases it will be found that good quality filters (low noise and tracking capability) are essential for both innovative and imitative synthesis and that this will usually be achieved by combining various types of filter in series or parallel. Our recommendation for beginners is to start with the low pass filter, which finds the most widespread use in music synthesis, and the state variable filter to be described in the next article since this will have low pass, high pass, band pass and notch responses.

Filter Design

The design is based on another customised IC from Curtis Electromusic Specialties, namely the CEM 3320, to realise the most important filter types employed in music synthesis. This voltage controlled filter IC has four independent filter stages which may be interconnected to provide a wide variety of filter responses. The pole frequency of the four stages is controlled by a single exponential generator which has a minimum range of ten octaves. The IC also includes a separate transconductance amplifier whose output is connected to the first filter stage and in the present design is used to provide manual or external voltage control of regeneration.

Some music synthesists argue that the ideal filter should have complete cut-off at its pole frequency. Certainly filters with a 24 dB/octave roll-off are considerably more useful than designs with lower roll-off. (12 and 24 dB/octave slopes will be included in the state variable filter design which is featured in the next article of this series). This combination of 24 + 12, or 24 + 24 dB/octave filters will provide the versatility we are aiming for in this project.

Each of the filters has been designed to accept our standard 10V P-P signal level and to output a similar signal level. The term 'similar signal level' is used since allowance has to be made for the enhancement of the centre frequency as the amount of feedback is increased through the resonance control. For example, the band pass filter has an output of about 3V P-P at lowest Q (no feedback) whereas at maximum Q this peak level will approach 11V. The filters are controlled over a 1000:1 frequency range and their lowest frequency is typically in the range 20 to 25 Hz. The standard one volt per octave frequency response is employed and when calibrated the filters will track the oscillators accurately over the important range of the keyboard. Beyond this range the one volt per octave control falls off but this is acceptable for filters. Manual and external voltage control of frequency are provided and the manual adjustment includes both coarse and fine adjustment. One of the external frequency control inputs has an attenuating potentiometer which is required when the filter is used in conjunction with an envelope generator or external waveforms for timbre modulation. Three signal inputs are included to simplify mixing of waveforms prior to filtering. Two of these have attenuating potentiometers and the third is fixed at one third of the maximum gain of the other two inputs. The fixed input may be altered to suit individual requirements and it may be coupled to a potentiometer external to the module.

Temp. Temper

Although the four filter stages of the CEM 3320 are fully temperature compensated the frequency control input is not. If the methods of construction outlined in the first article are followed then frequency changes due to temperature should not be a problem.



A major advantage gained by using the CEM 3320 is the low signal to noise ratio and also low distortion when compared to popular designs using discrete components.

Construction

Since the PCB is designed to accept four filter configurations care should be exercised with component placement and both the component overlays and circuit diagrams should be examined if there is any doubt. The spacing between PCB holes for resistors and polystyrene capacitors is 12.5 mm and for the electrolytic capacitors is 2.5 mm. If your component leads are of different lengths to the above then you are putting it in the wrong place!

Note the two wire links on the PCB and take particular care, as always, on orientation of the ICs. The control input to the resonance cell (pin 9 of IC 3) is a low impedance input at near ground potential. The two inputs to this cell, via R6 and R7 shown in Figure 2, can be used for either manual or external voltage control. To have both facilities requires the use of the recommended jack socket method of construction, or some other switching technique which is evident from the following. Dual operation is achieved by connecting a 24k resistor, R7A, to the +15V supply line to RV3 and then taking the output from RV3 via a jack socket to R7, so that the manual control is disabled when the external control is in use. In the latter case R6 need not be installed.

A number of the input and output connections to the PCB have two holes and

this will apply to many of the ETI 80 modules. The second hole may be used for hard wiring but they are intended for future expansion of the system.

Calibration

A simple check can be made of the frequency control input and whether RV5 and RV6 have been wired up correctly. With IC3 removed and the coarse and fine controls fully anti-clockwise measure the voltage at the junction of R14 and R15 and adjust PR1 to obtain +155 mV. Now turn RV5 (coarse control) fully clockwise and the voltage should be about -25 mV.

Turn off power and insert IC3, power up, turn RV3 (resonance control) fully anti-clockwise and RV5 (coarse control) to about mid position. Measure the voltage at the output of the filter module and adjust PR2 until a zero reading is obtained. This offsets the DC voltage at the output of Pin 10 of IC3.

The last step is to calibrate the filter so that it will track the oscillators. The resonance control feedback resistor has been chosen so that the filter will oscillate when some frequency control is present, thus turning the filter into a low distortion sine wave oscillator. A calibrated VCO should be available at this time which will greatly simplify calibration of the filter. Any of the following techniques may be used in addition to treating it as an oscillator and using the methods described for the VCO.

1. Beat frequency technique. Apply about 3V5 to control input 1, which will become the keyboard input, to give a frequency of

about 250 to 300 Hz when RV3 is rotated to the point where oscillation is sustained - as heard through one side of the amplifier. Connect a calibrated VCO to the other side of the stereo amplifier and apply an external control voltage to the VCO until there is zero beating. Increase voltage to both VCO and VCF frequency control inputs by exactly one volt and then adjust PR1 until no beat frequency is heard.

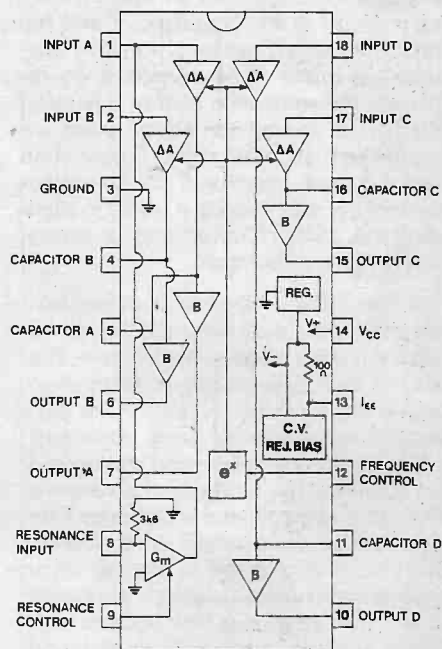


Figure 1. the CEM 3320 pinout.

HOW IT


Each of the filter stages of the CEM 3320 contains a variable gain cell followed by a high impedance buffer. The variable gain cell is a current-in, current-out device (as opposed to the traditional voltage-in, current-out type) whose output current, I_{out} , is given by

$$I_{out} = (I_{REF} - I_{in}) e^{-V_C/V_T}$$


$$\text{where } V_T = kT/q \text{ and } I_{ref} = \frac{0V48_{cc} - 1V3}{100k^*}$$

*±25%

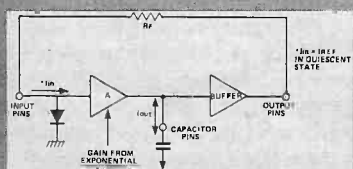The input to the variable cell is a forward biased diode to ground. The input thus presents a low impedance summing node at a nominal 650 mV above ground. The required input currents may therefore be obtained with resistors terminating at this input node.




Thus each stage is set up with a feedback resistor, R_f , from the buffer output to the variable gain cell input and with the capacitor connected to the output of the variable gain cell. In the DC state, the buffer output will always adjust itself so that I_{REF} flows into the input. For lowest control voltage feedthrough and maximum peak to peak output signal, the quiescent output voltage of each buffer, V_{ODC} , should be $0.48 V_{CC} - 0V65$. In the present design where V_{CC} is +15 V, the feedback resistors (R21, R24, R26 and R29) are 100k, then the DC output of each buffer will be a nominal +6V5 and I_{REF} a nominal 60 μA . The output impedance of the variable gain cell, although high, has a finite value. This impedance is reflected back to the input as an AC resistance of nominally 1M in parallel with the feedback resistor, R_f , regardless of control voltage value.

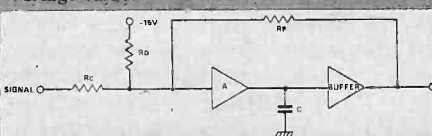

If the first stage of the low-pass filter is coupled to a ground-referenced direct coupled signal output, then the quiescent DC output will shift down 0V6 and a capacitor

(C7) is used to avoid this situation. For the first stage, the I_{REF} requirement is met using only R_f (R21). The subsequent stages should, however, be set for unity gain and since these will have the current from the feedback resistor (nominally 60 μA) as well as the current developed across R_C by the DC output of the preceding stage (nominally 66 μA) it is necessary to sink the excess current and this is done with a bias resistor, R_b , of 240 k connected to the negative supply.

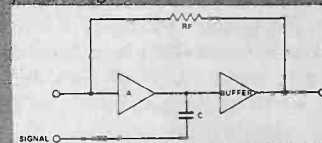For the simplest case, the high pass filter, each stage is shown below



I_{REF} is supplied only through the feedback resistor, R_f , and the voltage gain is unity, irrespective of the value of this resistor. For best results, however, the impedance of the signal source to stage one should be low compared to $R_f/4$.

The band pass filter is derived by connecting two stages of high pass with two stages of low pass filtering. The allpass configuration is used to generate a phase shift filter by taking part of the original

2. Lissajours figures. Same procedure as (1) but outputs from VCO and VCF are coupled to the X and Y inputs of an oscilloscope to generate Lissajours figures, ie a stable circle using sine waves when both amplitude and frequency are matched.

3. Maximum signal amplitude. Another approach with an oscilloscope is to apply a signal of about 250 Hz from a calibrated VCO to signal input 1 of the filter and observe the output of the filter on the oscilloscope. Apply a voltage to control input 1 of the filter until the point where the output reaches its maximum amplitude is observed. A small amount of resonance will help. Increase control voltage to both VCO and VCF by exactly one volt and adjust PR1 until maximum amplitude is restored.

If an oscilloscope is available then the VCO and VCLFO may be used as a sweep

frequency generator to examine the response characteristics of the filters. These should be connected as shown below:-

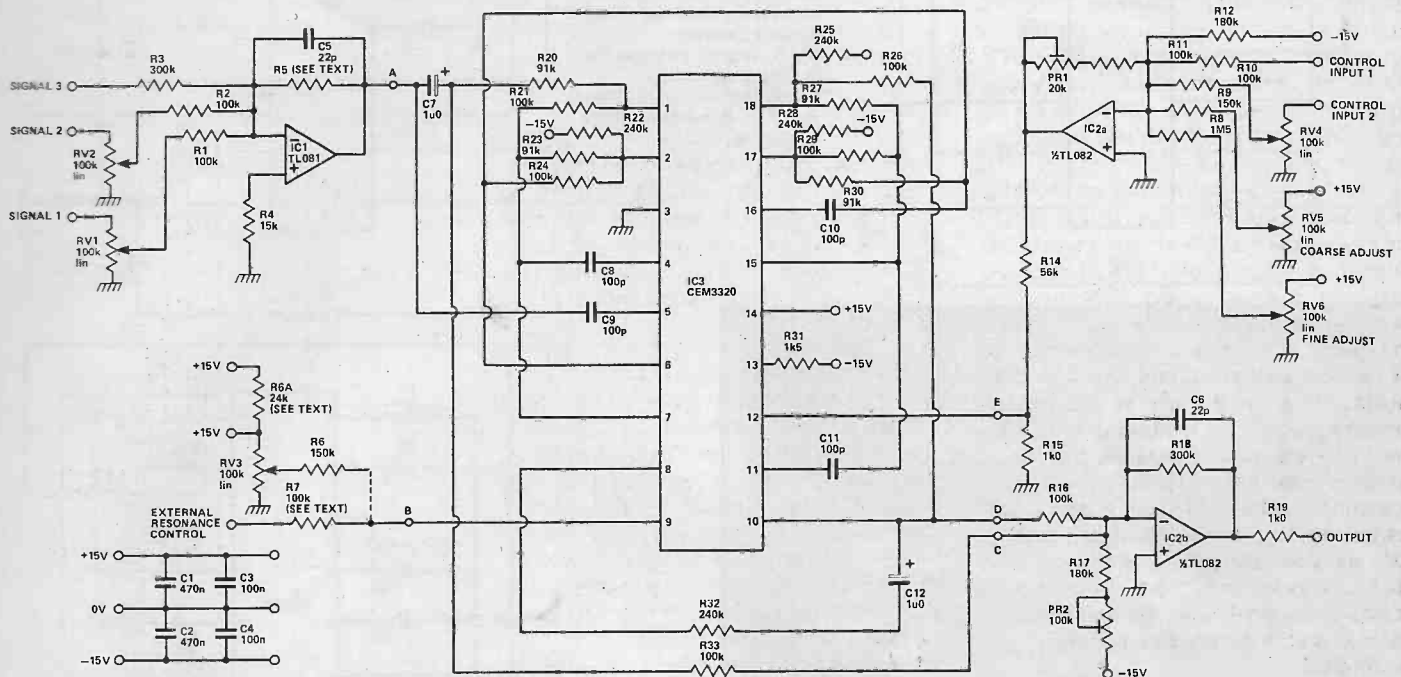
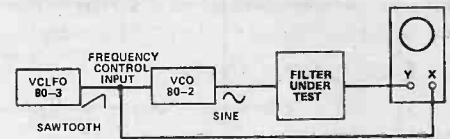


Figure 2. full circuit diagram of the phase-shift filter.

WORKS

signal, via R33, to the output stage. In both cases the purpose of resistors R20 to R30, when used, is evident from the above discussion.

The CEM 3320 contains a traditional transconductance type of amplifier. It has a separate signal voltage input (pin 8) and since this has an impedance of nominally 3k6 the input is referenced to ground and so when the signal is taken from the signal output of the IC a coupling capacitor (C12) is required. The output of the gain cell is connected to stage one of the filter (pin 1) and in this project the amplifier is used to provide voltage control of resonance. In controlling resonance a current is applied to pin 9 using R6 or R7. This input is of low impedance with a potential near ground and its characteristics are such that the transconductance of the cell increases more slowly with increasing current. The latter results in finer resolution as the critical point of oscillation is reached. The amount of signal feedback is governed by R32 and its value has been chosen such that with 100 uA of control current (our standard 10 volts via R7), oscillation will just occur, although operating conditions will influence the actual starting point. In other words, we have chosen the value so as to avoid sine waves of large amplitude which would become clipped in the first filter stage and

cause a shift in frequency.

In order to minimise power dissipation the negative supply of the CEM 3320 is regulated at -13V9 with an internal shunt regulator. This reduces warm up drift of the pole frequencies on powering up as well as allowing virtually any negative supply greater than -4 V to be used. The current limiting resistor, R31, must always be included and is calculated as follows

$$R_{EE} = \frac{V_{EE} - 2V_7}{.008}$$

which for our standard -13 V supply requires a resistor of 1k5. A positive supply of +15 V is connected directly to pin 4 but supplies in the range +9 to +18 V may be used although this will influence both power dissipation and peak to peak output swing.

IC1 forms a conventional input summer for up to three signal inputs, two of which may be attenuated with rotary controls (RV1 and RV2) included on the panel. R5 determines the signal level into the filter and based on an input of 10 V p-p its value has been chosen such that the signal will not be clipped in the filter even when the maximum useful regeneration is applied. IC2b forms the output stage and the signal is amplified by R18 to ensure that the VCF will have approximately unity gain at maxi-

mum resonance. R17 and PR2 allow cancellation of the DC voltage at pin 10 of the CEM 3320; IC2b also serves as a buffer stage for IC3 since the buffers within the filter are not short circuit protected.

The frequency range of the filters is governed initially by the capacitors C8 to C11, which have been selected to provide a lower cut-off frequency in the range of 20 to 25 Hz. The CEM 3320 has an exponential converter within the device which simultaneously controls the current gain of each section. An input of 18 mV/octave is required to pin 12 and an increasing positive control voltage lowers the pole frequency of the filter. Furthermore, for best results the input to pin 12 should be maintained between -25 mV and +155 mV. IC2a therefore provides an input summer for two external control voltages (via R10 and R11), a coarse control (RV5) for a ten octave range and a fine control (RV6) over a one octave range. It also serves to invert the input voltage to the same sense as other modules, namely, an increasing positive voltage increases pole frequency; to sum an offset voltage through R12 to give an initial voltage at pin 12 of approximately +155 mV; and by adjusting the gain with PR1 to allow the one volt per octave response of the filter to be developed at the junction of R14 and R15.


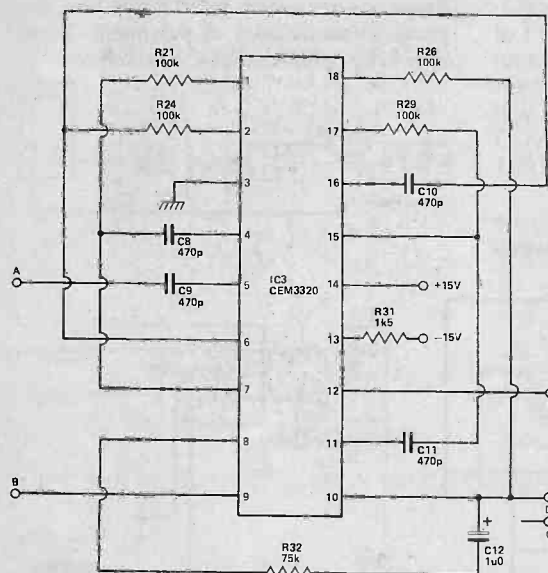
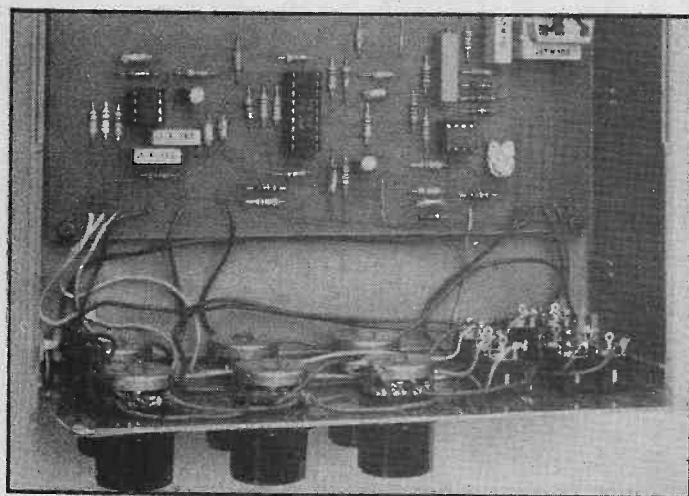
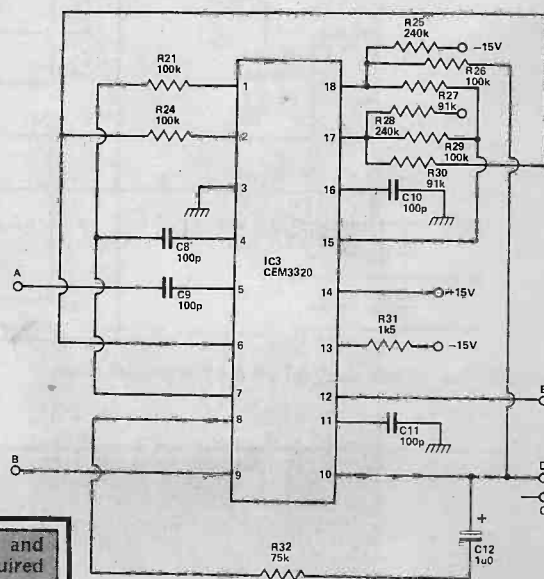


Fig.3. (left) the filter configured for high-pass operation showing component changes.
Fig.4. (right) changes for low pass operation.
Fig.5. (below right) changes for band-pass filter operation.

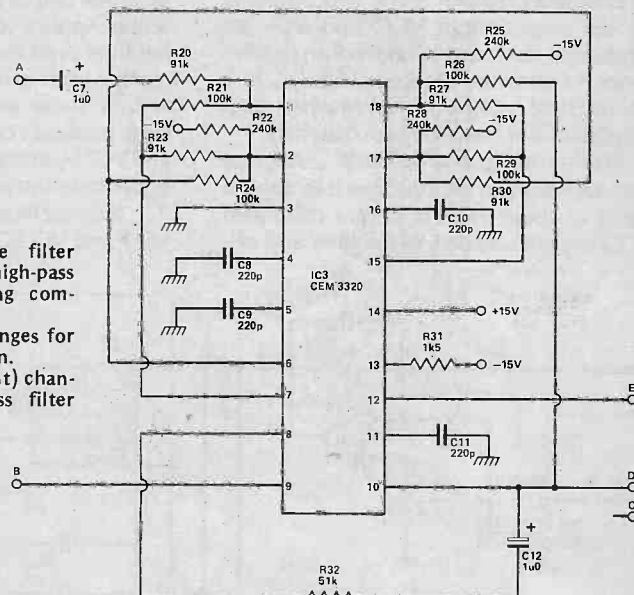

BUYLINES

The PCB and all components shown in the appropriate circuit diagram are available from Digisound Limited for £13.20 per

filter, inclusive of postage, packing and VAT. Please specify filter type required when ordering.

PARTS LIST

Components common to all filters

RESISTORS, 5%, 1/4W carbon film

R1,2,7,16

21,24,26,29 100k

R3,18 300k

R4 15k

R6,9 150k

R8 1M5

R17 180k

R19 1k0

R31 1k5

R6A 24k

RESISTORS, 1%, 1/4W metal film, 100ppm T.C.

R10,11 100k

R12 180k

R13 91k

R14 56k

R15 1k0

POTENTIOMETERS

RV1,2,3,4

5,6 100k

PR1 20k multiturn cermet

PR2 100k carbon

CAPACITORS

C1,2 470n polyester

C3,4 100n polyester

C5,6 22p polystyrene

C12 1u0 PCB electrolytic

SEMICONDUCTORS

IC1 TL 081, or equivalent

IC2 TL 082, or equivalent

IC3 CEM 3320

ADDITIONAL COMPONENTS FOR LOW

PASS FILTER, 80-6L

RESISTORS 1/4W, 5% carbon film

R5 36k

R20,23,27,

30 91k

R22,25,28 240k

R32 51k

CAPACITORS

C8,9,10,11 220p polystyrene

C7 1u0 PCB electrolytic

ADDITIONAL COMPONENTS FOR HIGH

PASS FILTER, 80-6H

RESISTORS 1/4W, 5% carbon film

R5 24k

R32 75k

CAPACITORS

C8,9,10,11 470p polystyrene

ADDITIONAL COMPONENTS FOR BAND

PASS FILTER, 80-6B

RESISTORS 1/4W, 5% carbon film

R5 33k

R25,28 240k

R27,30 91k

R32 75k

CAPACITORS

C8,9,10,11 100p polystyrene

ADDITIONAL COMPONENTS FOR

PHASE SHIFT FILTER, 80-6P

RESISTORS 1/4W, 5% carbon film

R5 12k

R20,23,27,

30 91k

R22,25,28,





32 240k

R33 100k

CAPACITORS

C8,9,10,11 100p polystyrene

C7 1u0 PCB electrolytic

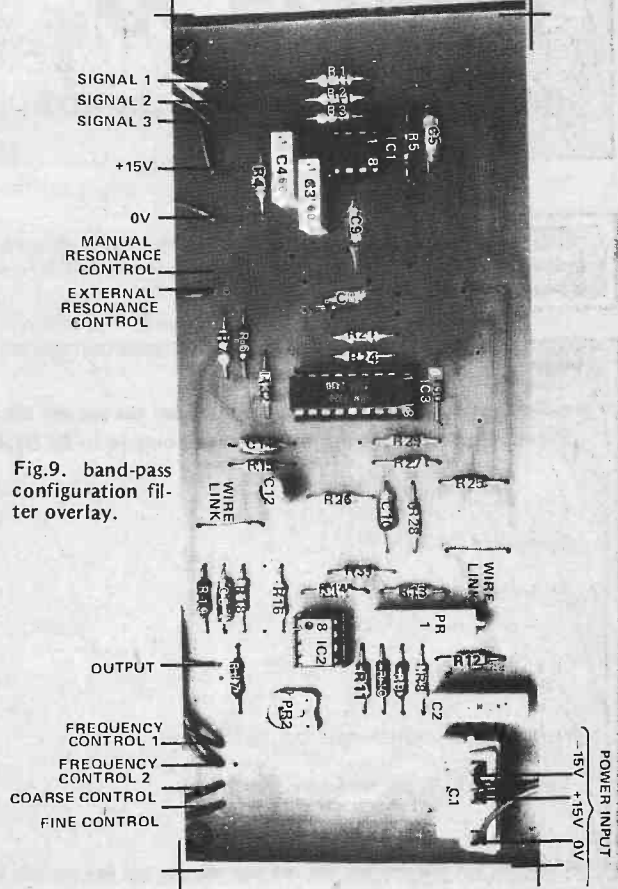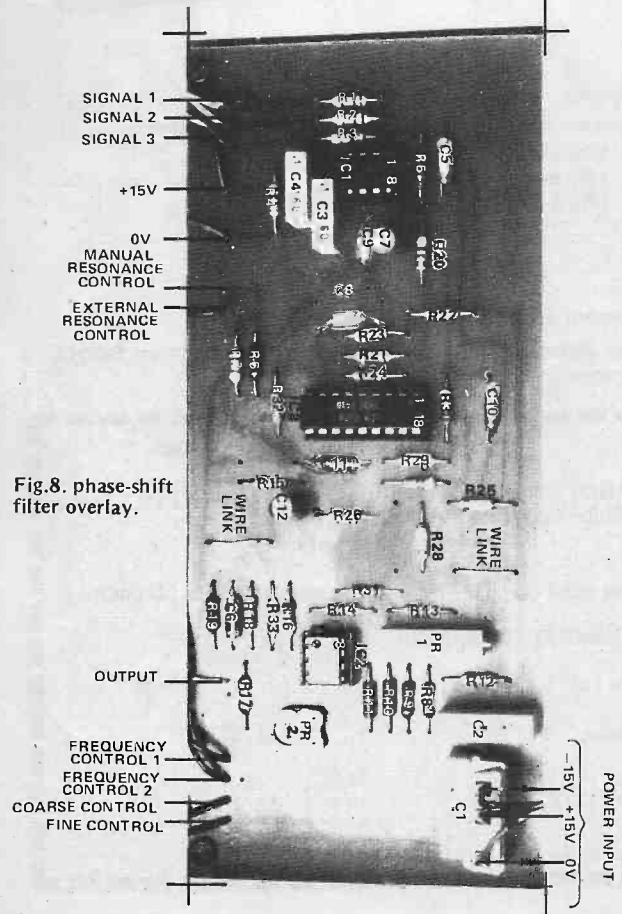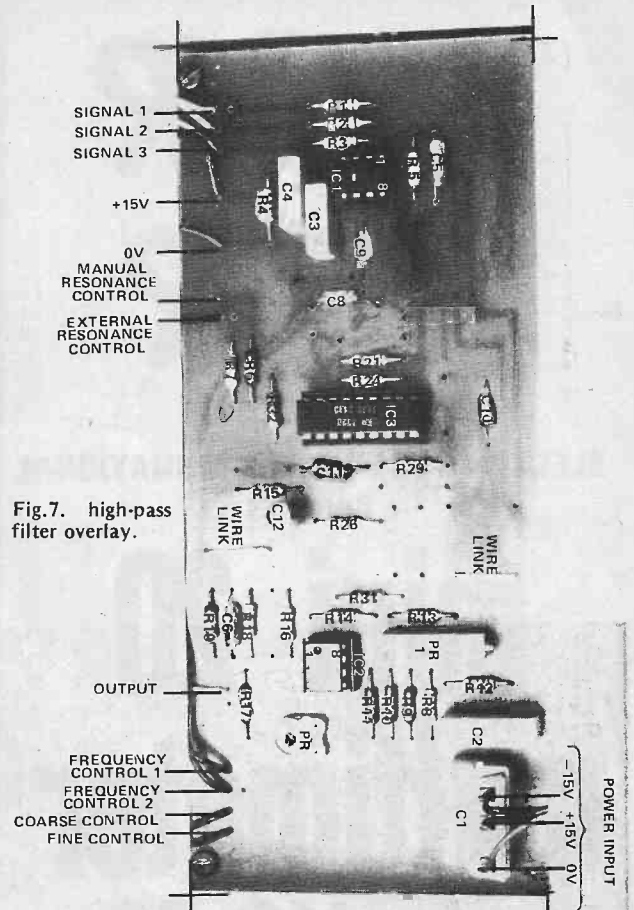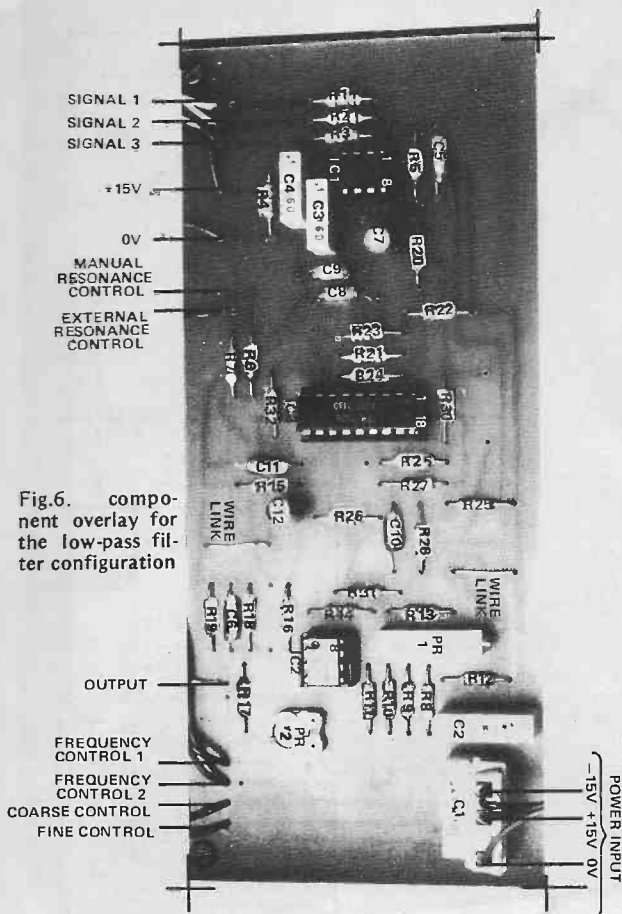

SUPER OFFER

to
ELECTRONICS TODAY INTERNATIONAL
Readers


mini 20 multimeter only £19.50

**INCLUSIVE OF POST & PACKAGE
AND V.A.T.**

The Mini 20 Multimeter is an ideal instrument for the constructor.

This Special Offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10 on the normal retail price.

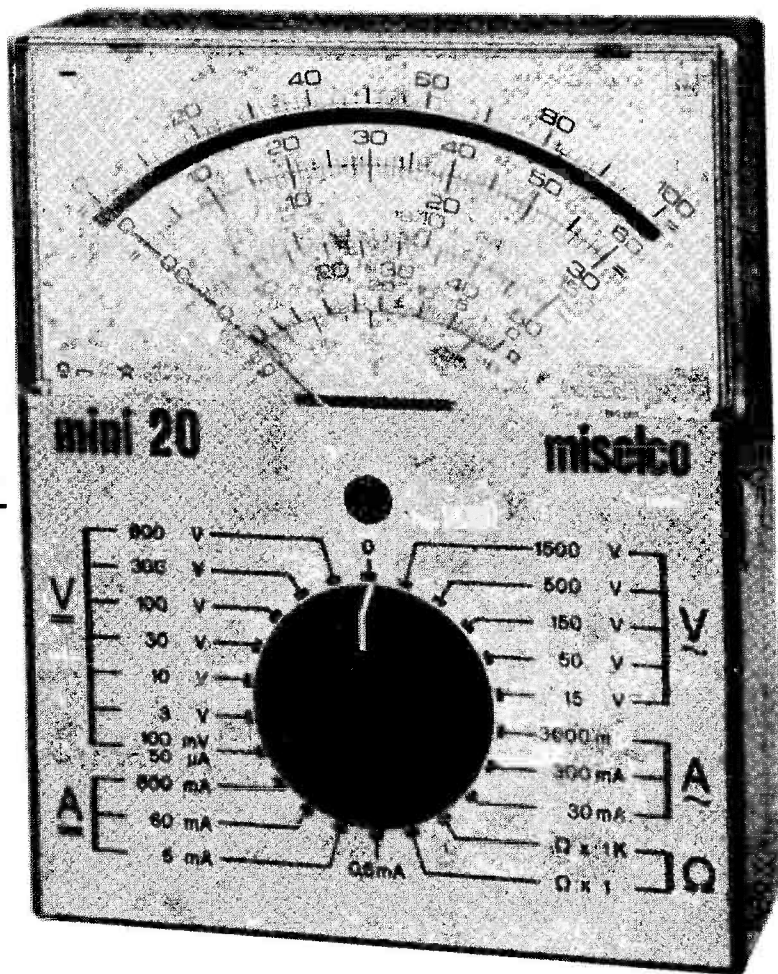The 21 ranges cover all likely requirements. Operation is straight-forward, just turn the 22-position selection switch to the required range.



Sensitivity 20kΩ/V d.c. 4kΩ/V a.c.

Ranges extend from

100mV to 600V d.c.	30mA to 3A a.c.
15V to 1,500V a.c.	0 to 2kΩ
50μA to 600mA d.c.	0 to 2MΩ

Movement protected by internal diode and fuse.

The instrument is supplied complete with case, leads and instructions.

Please complete both parts of the coupon in BLOCK CAPITALS

OFFER CLOSES MAY 31, 1980

Name

Address

From: Alcon Instruments Ltd. (ETI Offer)

19 Mulberry Walk, London, SW3 6DZ

To: Alcon Instruments Ltd. (ETI Offer)
19 Mulberry Walk, London SW3 6DZ

Mail order only

Please send me meter/s at £19.50 each

I enclose P.O./Cheque No. Value

Name

Address


Please allow 28 days for delivery

Don't buy a digital watch until you read this report

There are so many digital watches on the market, with varying functions, that the average person is bound to feel somewhat confused.

A new survey of the electronic watch industry has been produced to clarify this confusion and to give an unbiased and objective answer to the many questions that are constantly being raised.

by Trevor Raven.
C.Eng. AMBIM. MIERE

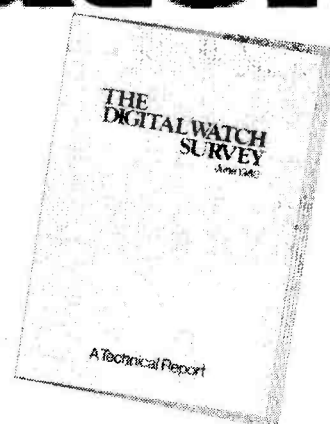

- * How accurate are electronic watches?
- * Who makes Seiko's?
- * What is the importance between brand names?
- * Is solar power worth the extra money?
- * What are the most important features in a watch?
- * When will prices stop falling?

The survey answers all of these questions and tells you what to look for in a quartz watch; how they work; why the prices vary so much; what the future holds.

FREE OFFER

Send today for this free technical report, plus news of a unique Metac offer to beat all special offers.

Complete the coupon below and send it FREEPOST (no stamp required) and we will post, **Same Day Despatch**, the technical report giving you all you need to know about electronic watches and details of our special offer.

Which is the best watch?



These four watches are very different in price, durability and functions. How would you choose between them?

This unbiased and objective report helps you to make this decision and gives you a deeper insight into the rapidly changing and exciting world of the micro-chip.

For your free copy of the report, complete and return the coupon to: Metac Electronic & Time Centres, 24-hour Despatch Centre, FREE-POST, 47A High St., Daventry, Northants.

Name _____

Address _____

ET15

MICROFILE

Henry Budgett reveals Nascom's new goodies and the latest club news.

A somewhat slimmer than usual Microfile this month owing to a distinct lack of anything much to talk about, and a surfeit of Tangerine! The springtime is generally supposed to be a time of blossoming forth and judging by my letters file on Computer Clubs they are no exception.

Clubbed To Death

Taking the pile in no particular order we have Mr J Fieldhouse of 18 Seaford Road, Broadfield, Crawley in West Sussex who informs me of the recent formation of a club. This is open to anyone with an interest in personal computers and it is hoped to hold weekly meetings with a newsletter to be published at regular intervals. If you live in the area contact him at the above address or ring on Crawley 542509. Tony Rycroft of the South Yorkshire Personal Computing Group has moved on and the group secretary, Paul Sanderson of 8 Vernon Road, Totley, Sheffield S17 3QE Tel 0742- 351895, is now the person to contact for details. They hold meetings on the second Wednesday of each month in Room F135 of St George's Building, Sheffield University. Another newly set up organisation is the Anglia Computer User Group which is open to anyone in East Anglia who has an interest in computers for either professional or hobby reasons. Contact can be made to Jan Rejzl at 128 Templemere, Sprowston Road, Norwich NR3 4EQ or by phone on Norwich 402311.

Surrey is the target for the next micro invasion with the Surrey Micro Processor Society run by Mike Patrick of 28 West Drive, Cheam, Surrey. They are holding about two meetings a month with an annual sub of £5, £3 for juniors or OAPs, and currently have around 40 members. The West Midlands Amateur Computer Club have been updated and their vital information is that they meet on the second and fourth Tuesdays of each month. The venue is Elmfield School in Love Lane, Stourbridge and they usually start around 7.30. The sub for the year is £3 or £2 if still in full-time education. For more information contact John Tracey at 100 Booth Close, Kingswinford, West Midlands or ring Brierly Hill 70097. They are well equipped with 8 PETs, 12 N1s, 5 N2s 3 TRS 80s plus about 20 others. Anyone in mid Sussex? Well if there is - and you are interested in micros - contact Bernard Langton who is forming a micro club. Get in touch with him at 228 St Leonards Road, Horsham, Sussex RH13 6AU.

The Grampian Amateur Computer Society, well known for their spelling mistakes, have sent me an update. They meet every second Monday at the Holiday Inn, Bucksburn, Aberdeen and have over 30 members. All their news is published in a regular newsletter and they have their own Acorn. For further information contact the secretary at Orton Cottage, Burnside, Lumphanan, Kincardineshire, Grampian, Scotland. Whilst north of the border I shall mention the



Scottish Amateur Computer Society who have sent me a copy of their Newsletter and Bulletin. They meet on the first Wednesday of each month at the Grosvenor Hotel, Haymarket, Edinburgh at about 7.30pm. They publish the newsletter quarterly and for further information you should contact the secretary, Alastair Macpherson, at 6 Curriehill Castle Drive, Balerno, Edinburgh 14.

And whilst on the subject of newsletters, did you know that there was an Ohio Scientific UK User Group? Well neither did I. Tom Graves is the man to contact if you own one. C1 or 2 and Superboard are the current interests but they would like to expand to the disc systems. The address to write to is 19a West End, Street, Somerset BA16 0LQ.

System 80 Makes Two Into One

Nascom have at last turned the single board into a complete system with the launch of System 80. Basically all they have done is to produce a range of boards for the Nasbus and a case to put them all in. However, before you all start to think about long delivery times they do promise that all the boards are in the production state and although the launch is over the next few months they will all arrive.

The starting point is the case which accepts a "2" and its keyboard plus four more boards. Included is space for a power

supply and sockets for printer and cassette. The bad news is that if you own a "1" you won't be able to spend your £85 unless you are prepared to do quite a lot of hacking to fit a bufferboard in, Vero are rumoured to have a rack system on the stocks that may well be the answer.

Next is the good news that Nascom have finally ditched the 16K RAM plane, the one labelled 'Instant Disaster', and produced one that offers a choice of 16, 32 or 48K of dynamic with locatable boundaries and page mode so you could have four on a "2"! Price is £225.

At last they are also announcing some I/O in the shape of a board with three PIOs, a CTC and a UART. Price is £45 for the board and TTL, £8.50 per PIO, £8.25 for a CTC and £16 for the UART. The graphics capability of the "2", not bad anyway, has been expanded out of all proportion with two new boards, a programmable graphics generator at £90 and a dual standard colour board whose price is not yet decided.

For those of you who are not satisfied with lowly cassette storage discs will be here soon. The board has been designed but due to component shortages it will be the last released, probably in July. The controller card is designed to handle up to four 5¼" units and will cost £127.50. It should also be possible to use 8" units but no support is planned. A complete dual double-sided, double-density system will set you back £690.

The second major item of news to emerge from the launch is that the "2" will now be sold at £225 but there will be no on-board RAM (4118) other than the video and scratchpad and no free 16K board. Some firms like Henry's are still doing the offer on their own so look out for bargains.

Tangy Fruit

After last month's little piece on the Microtan 65, which even got the unimpressable Mr Graham converted to micromania (see Kit Survey), I have been so swamped with calls and letters that I'm going to print the address so you can all go and pester them rather than me. Tangerine Computer Systems Ltd., Forehill, Ely, Cambridgeshire. Their telephone number is 0353-3633. The expansion board, Tanex, is now available and the slight delay was caused by one of the nastiest little problems I've heard in a while. The prototype worked, they laid out the board using a distributors data sheet and sent it off to be made up. Result of the exercise was that the PCB didn't work. The reason? Whoever drew up the data sheet muddled up a couple of IC pins and every board had to be scrapped. So a gentle word of warning, only use manufacturers genuine data, not some free give away!

Post Script

Two late items that arrived. The inaugural meeting of the Croydon Mini/Micro Computer Group is to be held on Tuesday 22nd of April at 7.00pm in the Central Reference Library, Katharine Street, Croydon. Anyone interested should contact Vernon Gifford, 111 Selhurst Road, London SE25 6LH. If you won't be able to attend but are still interested he would like to know your areas of special interest before the meeting if possible.

The second item is to explain why there is no ZX-80 follow-up as promised. Simple really, we haven't got one yet, but perhaps for next issue so don't despair.

ETI

LOW POWER SCHOTTKY TTL - EX STOCK

Device	Price	Device	Price	Device	Price
74LS00	13p	74LS76	38p	74LS164	100p
01	13p	85	80p	174	65p
02	12p	86	36p	175	65p
03	13p	90	40p	190	100p
04	14p	93	70p	191	100p
05	25p	95	85p	192	100p
08	30p	107	40p	193	100p
09	20p	109	50p	196	100p
10	16p	112	50p	197	100p
11	23p	113	50p	221	100p
12	25p	114	50p	244	220p
13	30p	123	80p	247	100p
14	40p	125	30p	248	100p
20	17p	126	30p	249	90p
21	21p	132	50p	251	90p
26	30p	136	45p	273	165p
27	15p	138	45p	279	50p
28	30p	151	80p	283	100p
30	15p	153	85p	290	90p
32	17p	155	65p	293	100p
37	20p	156	90p	298	93p
38	30p	157	70p	352	110p
40	17p	158	70p	353	110p
47	52p	160	100p	366	50p
49	52p	161	100p	367	60p
73	40p	162	100p	368	55p
74	33p	163	130p	374	180p
75	32p			386	36p

LOW PROFILE DIL SOCKETS

8 Pin	8p	18 Pin	12p	24 Pin	16p
14 Pin	9p	20 Pin	13p	28 Pin	19p
16 Pin	10p	22 Pin	15p	40 Pin	30p

VERO PRODUCTS

Vero Wiring Pen (inc. 1 spool wire)	248p	2.5" x 5"	65p
2 x Spare Spools	85p	2.5" x 3.75"	54p
Spot Face Cutter	95p	2.5" x 17"	198p
VeroBlock Breadboards	283p	3.75" x 5"	65p
		3.75" x 17"	250p

VEROBOARD PCBs

2.5" x 5"	65p
2.5" x 3.75"	54p
2.5" x 17"	198p
3.75" x 5"	65p
3.75" x 17"	250p

CALCULATORS


Textet 1500	375p	Brain Wave	770p
Textet 1800	840p	Trader	800p
Scientific 2001	725p	LCD 300	940p

TERMS

Please add 35p for P&P plus 15% VAT to all orders. Export orders no VAT but postage at cost. Prompt delivery on all orders. Cheques, POs, Money Orders to be made payable to:-

ROMANE ELECTRONICS

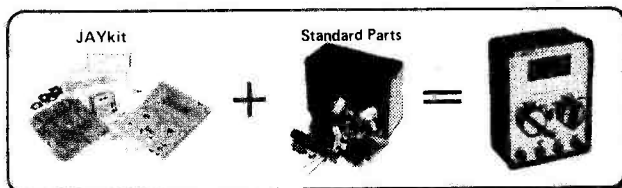64 Newlyn Drive, Sale, Cheshire. M33 3LE
Tel. 061-962 2606



DM-2



DIGITAL MULTIMETER

- ★ DC Volts 1mV to 1000V
- ★ AC Volts 1V to 500V
- ★ DC Current 0.1mA to 0.2A
- ★ Resistance 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayen Developments, 21 Gladside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments
21 Gladside, Bar Hill,
Cambridge CB3 8DY
Tel: (0954) 80285

Name _____

Address _____

Please send:

- ☐ DM-2 @ £5.45
☐ FG-1a @ £4.95
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.


JAYkits

OPTO

LED's	0.125in.	0.2in	each
Red	TIL209	TIL220	10p
Green	TIL211	TIL221	15p
Yellow	TIL213	TIL223	15p
Clips	3p	3p	
DISPLAYS			
DL704	0.3 in CC		130p
DL707	0.3 in CA		130p
FND500	0.5 in CC		100p

SKTS

Low profile by Texas

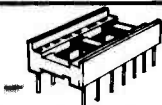

8 pin	10p	18 pin	16p	24 pin	22p
14 pin	12p	20 pin	18p	28 pin	26p
16 pin	13p	22 pin	20p	40 pin	38p
3 lead TO18 or TO5 skt.					12p each.
Soldercon pins:					100 for 60p.

PCBS

VEROBOARD

Size in.	0.1in.	0.15in.	Vero
2.5 x 1	16p	—	Cutter 110p.
2.5 x 3.75	52p	45p	
2.5 x 5	60p	55p	Pin insertion tool 150p.
3.75 x 5	70p	70p	
3.75 x 17	250p	210p	
SS pins/100	45p	45p	
Fibreglass board:			80p each.
Altec — 33p per sheet.			

RESISTORS

E12 series. 4.7 ohms to 10M. Any mix:			
each	100+	1000+	
0.25W	1p	0.9p	0.85p
0.5W	2p	1.5p	1.3p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Megohm (650 res) 0.5W £8.50. 0.25W £5.30.			
METAL FILM RESISTORS			
very high stability, low noise rated at 1/2W E24 series. Any mix:			
each	100+	1000+	
0.25W	4p	3.7p	3.5p

POTENTIOMETERS

Preset vertical or horizontal 100 ohms — 1M			
Rotary 5K-2M2 Log or Lin single			30p
Rotary 5K-2M2 Log or Lin double			90p
Slide 60mm travel 5K-500k Log or Lin, single			60p
Suitable knobs for above with coloured caps in red, blue, green, grey, yellow and black. Rotary controls 16p each. Slide type 12p each.			

MISC.

Murata Ultrasonic Transducers	350p pair
64mm 8ohm speakers	100p each
64mm 64 ohm speakers	100p each
SRB 17W soldering iron	430p each
Reel of 22swg solder (39.6m)	320p each
Desoldering tool	510p each
Precision screwdriver set	170p each
Titan Electric drill	1095p each
Miniature 606 and 909 at 100mA transformers	110p each

SWITCHES

TOGGLE			
Standard	SPST 36p	DPDT 50p	
Miniature	SPDT 75p	DPDT 85p	
Subminiature	SPST 58p	DPDT 78p	
SLIDE			
Standard		DPDT 17p	
Miniature		DPDT 16p	
ROCKER (10A rating)			
SPST 34p each.	SPST 46p each.		
ROTARY			
1P12W, 2P6W, 4P3W or 3P4W			51p each
Key operated DPDT (Yale key)			395p each
PUSH			
Non locking - push to make			16p each
- push to break			22p each
Locking - SPST			75p each
- DPDT			100p each

REGULATORS

REGULATORS	LM317T	220p
	LM323K	480p
	LM723	40p
100mA + ve	1A + ve	1A - ve
78L05 30p	7805 70p	7905 85p
78L12 30p	7812 70p	7912 85p
78L15 30p	7815 70p	7915 85p

TRANSISTORS

AC127	22p	BC548	11p	TIP32C	60p
AC128	22p	BCY71	16p	TIP2955	66p
AC176	22p	BCY72	15p	TIP3055	53p
AD161	40p	BD131	40p	ZTX107	12p
AD162	40p	BD132	40p	ZTX108	12p
BC107	12p	BD133	40p	ZTX300	14p
BC108	10p	BD139	33p	ZTX500	15p
BC108C	10p	BD140	33p	2N3054	56p
BC109	12p	BFY50	23p	2N3055	50p
BC109C	12p	BFY51	23p	2N3702	9p
BC147	9p	BFY52	23p	2N3704	9p
BC148	9p	MJ2955	100p	2N3706	9p
BC177	16p	MPSA06	16p	2N3819	20p
BC178	16p	MPSA56	16p	2N3904	10p
BC182	10p	TIP29C	60p	2N3905	10p
BC182L	10p	TIP30C	48p	2N3906	10p
BC184	10p	TIP31C	50p	2N5459	33p
BC184L	10p			2N5777	50p
BC212	10p	DIODES			
BC212L	10p	1N914	4p	1N4006	7p
BC214L	10p	1N4148	3p	1N5401	14p
		1N4002	5p	BZV85ser.	8p
		1N4148	£1.50 per 100.		

CAPACITORS

POLYSTYRENE			
High quality foil type. 63V working, 5% tol.			
22pf to 100pf			7p each
1500pf to 0.01uF			9p each
TANTALUM BEAD			
0.1, 0.15, 0.22, 0.33, 0.47, 0.68			10p each
1 & 2.2uF @ 35V			18p each
4.7, 6.8, 10uF @ 25V			22p each
22 @ 16V, 47 @ 6V, 100 @ 3V			
MYLAR			
0.001, 0.01, 0.022, 0.033, 0.047			4p each
0.068, 0.1			5p each
POLYESTER			
Mullard C280 series			
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1			6p ea.
0.15, 0.22			8p each
0.33, 0.47			12p each
0.68			17p each
1.0uF			22p each
CERAMIC			
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF			2p each
MINIATURE TRIMMERS			
Miniature film type, in 1.4pF — 5pF, 2pF — 22pF, 2pF — 22pF, 2pF — 10pF, 5.5pF — 65pF. 22p each			
RADIAL LEAD ELECTROLYTICS			
63V 0.47 1.0 2.2 4.7 10			6p each
	22 33 47		8p each
100			16p each
	220		20p each
25V 10 22 33 47			6p each
100			8p each
	220		12p each
	470		18p each
1000			28p each

PACKS

Specially developed packs intended for development work.			
1/2W CF resistor, 10 each value E12 series 4.7 ohm to 1 Megohm (650 total)			530p each
1/2W CF resistor, 10 each value E12 series 4.7 ohm to 1 Megohm (650 total)			850p each
1/2W MF 1% resistor, 10 each value E24 series 51 ohms to 330k (930)			2950p each
Preset potentiometers 5 each value from 100 ohms to 1 Megohm (65)			390p each
Polyester capacitors 5 each value 0.01 to 2.2uF (70)			690p each
Ceramic plate capacitors 10 each value 22pF to 0.01uF (310)			575p each

CONNECTORS



DIN PLUGS AND SOCKETS	plug	chassis socket	line socket
2 pin	8p	8p	12p
3 pin	12p	10p	12p
5 pin 180°	12p	11p	17p
5 pin 240°	14p	11p	22p

JACK PLUGS AND SOCKETS	unscreened	screened	socket
2.5mm	10p	15p	8p
3.5mm	10p	16p	9p
Standard	16p	30p	19p
Stereo	23p	39p	22p
1mm PLUGS AND SOCKETS			
Suitable for low voltage circuits, Red & Black. Plugs: 7p each. Sockets: 8p each.			
4mm PLUGS AND SOCKETS			
Available in blue, black, green, brown, red, white and yellow. Plugs: 12p each. Sockets: 13p each.			

STEVENSON

Electronic Components

CMOS

4000	20p	4023	20p	4054	120p	4502	120p
4001	20p	4024	50p	4060	120p	4507	60p
4002	20p	4025	20p	4063	120p	4508	330p
4006	90p	4026	160p	4066	60p	4510	80p
4007	20p	4027	45p	4068	20p	4511	90p
4008	95p	4028	85p	4069	20p	4512	80p
4011	30p	4029	85p	4070	20p	4516	80p
4012	20p	4031	220p	4071	20p	4518	80p
4013	35p	4033	150p	4072	20p	4520	80p
4014	80p	4036	350p	4073	20p	4527	90p
4015	80p	4039	300p	4075	20p	4528	90p
4016	30p	4040	110p	4076	90p	4529	150p
4017	65p	4041	85p	4077	20p	4531	150p
4018	90p	4042	80p	4078	20p	4532	130p
4020	100p	4043	95p	4081	20p	4538	160p
4022	100p	4046	110p	4082	20p	4543	110p
		4048	60p	4086	75p	4566	170p
		4049	45p	4093	60p	4588	120p
		4050	45p	4095	110p	4589	420p
		4051	70p	4098	120p	4581	330p
		4053	80p	4501	20p	4585	110p

LSTTL

74LS00	16p	74LS47	80p	74LS126	45p	74LS175	90p
74LS01	22p	74LS48	90p	74LS132	80p	74LS190	90p
74LS02	16p	74LS54	22p	74LS136	50p	74LS191	90p
74LS03	22p	74LS73	35p	74LS138	75p	74LS192	90p
74LS04	16p	74LS74	35p	74LS139	75p	74LS193	90p
74LS08	22p	74LS75	40p	74LS151	60p	74LS195	90p
74LS10	22p	74LS76	40p	74LS155	65p	74LS196	90p
74LS13	38p	74LS78	45p	74LS156	80p	74LS197	85p
74LS14	65p	74LS83	68p	74LS157	70p	74LS221	100p
74LS20	22p	74LS85	85p	74LS158	65p	74LS251	70p
74LS21	22p	74LS86	40p	74LS160	75p	74LS266	35p
74LS27	28p	74LS90	40p	74LS161	68p	74LS290	80p
74LS30	22p	74LS93	55p	74LS162	80p	74LS365	55p
74LS32	30p	74LS95	65p	74LS163	80p	74LS366	55p
74LS37	40p	74LS107	45p	74LS164	80p	74LS367	55p
74LS42	60p	74LS114	40p	74LS165	80p	74LS368	55p
		74LS123	80p	74LS173	135p	74LS386	50p
		74LS125	45p	74LS174	95p	74LS670	200p

TTL

7400	12p	7442	40p	7493	30p	74157	40p
7402	12p	7445	50p	7496	38p	74164	55p
7404	14p	7447	50p	74121	29p	74165	55p
7408	16p	7448	45p	74123	40p	74174	55p
7410	14p	7473	23p	74125	38p	74177	50p
7413	24p	7474	23p	74126	36p	74190	50p
7414	39p	7475	26p	74132	46p	74191	50p
7420	14p	7476	25p	74141	48p	74192	50p
7427	22p	7485	55p	74145	48p	74193	50p
7432	18p	7486	18p	74148	90p	74194	50p
		7490	30p	74150	55p	74196	50p
		7492	30p	74154	68p	74197	50p

LINEAR

LM301A	30p	LM3915	280p	TDA1008	350p
LM308	70p	LM3911	120p	TDA1022	630p
LM318	85p	LM13600	160p	TDA1024	120p
LM324	52p	MC1496	80p	TDA2020	360p
LM339	55p	LM1458	40p	TL071	75p
LM348	100p	LM1830	180p	TL072	135p
LM377	170p	MC3340P	135p	TL074	200p
LM378	230p	MC3360P	135p	TL081	45p
LM3795	410p	MM57160	650p	TL082	85p
LM380	80p	NE531	110p	TL084	125p
LM381	140p	NE555	23p	TL170	60p
LM382	120p	NE556	60p	XR2209	360p
LM383	200p	NE566	120p	XR2207	450p
LM386	90p	NE567	120p	ZN414	80p
LM387	120p	NE570	420p	ZN419	POA
LM389	100p	NE571	460p	ZN424	150p
LM391	170p	NE5537	POA	ZN425E	420p
LM1310	140p	QAC136	100p	ZN460	360p
LM2917	280p	SAD1024	1310p	ZN1034	230p
LM2924	160p	SN76477	230p		
LM3900	60p				

computing today

**OUT
APRIL 11TH**

**PICK UP YOUR
COPY SOON!**

STOCKMARKET SIMULATION:

If you lie awake at night dreaming of what you would do with that £1000 gift that will always arrive in the post tomorrow, dream no longer. In a remarkable game program written for the TI59 we have a complete stockmarket where you can buy and sell, wheel and deal, bear and bull to your hearts content.

Whilst the stock exchanges of reality are curious and wonderful establishments this game is based on proper theories and a full and detailed explanation of the processes needed is given. So, if you don't own a TI59 do not despair you will be able to use the information to implement the game on virtually any programmable system.

So if you want to be among the market leaders next month invest your sixty pence in our May issue, it could be the best investment you'll ever make.

Does your car or motorcycle seem to want more money than you bargained for? The author of our Home Finance program presents a second offering which will cater for your automotive expenses.

The program runs on the family PET but is easily adaptable to any BASIC using system with the PETs facilities. Access is available to a number of accounts for details of repair and servicing costs and reminders are given about the life expectancy of wearable items such as tyres.

If you depend on your car and can't account for the money you spend, load up and discover where its all going to. Rumour has it that Panther De Ville owners with that optional PET may be buying all copies so get to the newsagents early.

DRIVEN TO DESPAIR?

TRITON REVISITED

ETIs own computer system is over a year old now, and changes have been made since its conception that make it rather more than a single board computer.

In our continuing series of owners reports on popular machines John Hiscott takes his system through the stages of development and lays his observations open to the public eye.

No, that's not the art of making connections, but a glossary of the "hundred most used terms" in home and hobby computing. Many of our enquiries start out with, 'I can't tell the difference between RAM and ROM' so we decided to reveal all.

As an aid to simulating conversation this pull out extra should not be missed, you might even learn the elusive art of confusion!

TERMINOLOGY

DORAM

a de boer company



Buying one of our project packs will save you the frustration of tracking down those elusive components that hold up the completion of your project. Our packs include PCB, all the electronic components, sockets, solder and a description!

HOME

- Steam train and whistle (80019). Simulates the sound on steam and whistle **£6.50**
- Clap Switch (79026). You clap your hands and the light comes on **£6.60**
- Elektrobell (79095). Program your own signature tune **£22.00**
- Touch dimmer (78065). Room lighting controlled by single touch **£6.80**
- TV sound modulator (9925) **£3.75**
- Simple sound effects (79077) **£5.70**
- Electronic nuisance (80016) **£3.85**
- Ultrasonic transmitter (audio) (79510) **£7.65**
- Ultrasonic receiver (audio) (79511) **£9.95**
- DJ killer (79505) **£8.80**
- Quiz master (79033) **£6.50**
- Variable fuzz-box (9984) **£6.55**
- Ioniser (9823). Produces a high concentration of negative ions **£9.55**
- Oscillographics (9979). Random displays patterns on your oscilloscope **£11.25**
- Cackling egg timer (9985). Times your egg, then clucks like a hen! **£7.20**
- Pools forecaster (79053). Weighs up the odds and could win you a fortune **£8.15**
- Loudspeaking telephone amplifier (9987). Amplifies signal without direct connection **£11.50**
- Sensitive lightmeter (9886). Light measurement using silicon photodiode **£12.55**
- Nicad charger (79024). Automatically prevents over charge of cells **£5.20**
- Proximity detector (9974). Detects movement in a room (electric field change) **£9.80**
- Central alarm (9950). Master station **£11.20**
- Slave station **£10.85**
- Alarm unit **£3.10**
- Touch tuning FM preselect unit (79519). With digital display **£17.50**
- Talk funny (80052). Deliberate electronic distortion of speech and music signals using a single IC, the 2206 **£9.60**
- Colour generator (80027). Using coloured light for an effective display **£19.70**
- Temperature controlled soldering iron station including transformer (9952) **£11.65**
- Soldering iron for 9952 (Antex XTC-CTC) **£18.35**
- Pools predictor (79053) **£8.15**



- Interface for up-systems (79101) **£6.75**
- BASIC microprocessor (79075). 4K Basic interpreter in Rom. Based on SC/MP **£57.75**
- TV Games computer (79073 1+2+3). Designed around the Signetics 2650. It enables you to design and play games of your own invention rather than rely on pre-programmed modules. All the electronic components, PCBs and a software record **£219.00**
- Junior computer (80089 1+2). Now in stock. Ask for details **£92.80**

MEASURING

- 3/4 Digital thermometer (80045). LCD display (supplied without relay) **£26.95**
- LED display (supplied without relay) **£23.20**
- Relay (two pole changeover) **£2.45**
- AC millivoltmeter (79035). FET input meter circuit and audio generator **£6.30**
- Universal digital meter (79005). Digital replacement for pointer instruments **£14.65**
- Precision timebase (9448). Generates a precision 1 hertz pulse **£13.10**
- Power supply for timebase **£5.40**
- Universal timebase (78100). Crystal controlled time base **£18.70**
- 1/4 GHz counter (9887 1+2+3+4). Excellent kit count up to 250 MHz **£98.15**
- Minicounter (9927). 1 MHz 4 digit display **£27.70**
- Audio analyser (9932). An analyser which can point the deficiencies in a particular audio chain or environment **£14.80**
- Sport sinewave generator (9948). Programmable sinewaves with less than 0.0025% THD **£12.95**
- Simple function generator (9453). Sine, square and sawtooth outputs **£27.70**
- Sinewave generator (79019). Always sinewaves when you need them **£8.90**
- TV scope basic version (9968 1/5). Produces display up to 1 KHz on TV **£34.50**
- TV scope advanced version (9969 1/3). Converts basic scope to 100KHz bandwidth **£48.25**
- Digiscope (9926) **£32.35**
- Digifard (79088). A digital capacitance meter with a wide range **£25.10**
- Gatedipper (79514). Checks the resonant frequency of a circuit **£16.00**

MICROPROCESSOR

MP

- Elekto SC/MP μ P-system
- SC/MP Board and RAM Input/Output Board (9846 1+2). These two units demonstrate the working of the SC/MP chip (National Semiconductor). Data is fed in by digital switches and read out by LED's (databus) **£27.60**
- CPU (Central Processing Unit) Card 9851. The heart of the system. The board contains all the ICs needed to control the system by RAM I/O and included room to hold the control program (monitor) which is added later **£57.45**
- Memory extension (9883). You will be able to work with interrupt requests now and the card contains 3/4K of RAM and a 1/2k of Eprom **£49.95**
- Bus Board. A simple way of interconnecting the various boards of the system
- Extension for 3 boards (9857) **£3.35**
- Extension for 6 boards (80024) **£5.40**
- Hex input/output board (9893). You can work in hexadecimal format now via 16 alphanumeric and 10 control keys. Output is displayed on 8 seven segment displays **£52.65**
- ELBUG. This is the monitor programme stored in 3 Eproms **£37.00**
- Power supply (9066). Gives an output of +5 volt - 3 amp and 12 volt - 0.5 amp which is more than enough to run the complete system (including transformers) **£20.95**
- 4K RAM card (9885) 4096 x 8 bits of memory to expand the system **£92.55**
- Cassette interface (9905). This board enables you to record and replay programs on a simple cassette recorder **£14.95**
- ASCII Keyboard (9965). This simple unit based around the AY-5-2376 encoder provides all the alphanumeric and control functions used in the ASCII 8-bit format **£46.30**
- Elekterminal (9966). One of the cheapest and most reliable systems for displaying data on a domestic television **£69.55**
- Elekterminal Extension (79038). With the aid of the extension board the memory capacity of the elekterminal can be expanded to four pages (each of 16 lines and 64 characters) **£35.50**

AUDIO

- Equaliser (9832). Single channel audio equaliser with slidepots **£17.70**
- with turnpots **£16.60**
- with preset pots **£13.95**
- UAA180 LED meter (9817). A two channel display meter with LEDs **£13.00**
- Peak programme meter (9860). For use with UAA180 LED meter to give stereo audio display **£13.00**
- Luminant (9949 1+2+3). A novel LED audio level indicator **£20.70**
- Parametric Equaliser (9897). Filter section (9897-1) **£6.45**
- Tone control section (9897-2) **£5.20**
- Audio analyser (9932). An analyser which can pinpoint the deficiencies in a particular audio chain or environment **£14.80**
- Preconsonant (9954). A high performance disc amplifier **£5.75**
- Consonant (9945). A complete audio control preamplifier **£34.65**
- Toppreamp (80031). This preamplifier for Topamp or any other HiFi poweramp **£34.30**
- Topamp (80023). Hybrid audio power amplifier with OM 931 (Output 30 Watt) **£18.50**
- with OM 961 (Output 60 Watt) **£33.40**
- Stentor (79070). A portable amplifier ideally suited for PA **£30.00**
- Assistentor (79071). A preamp for use with Stentor **£7.00**
- Elektornado (9874). A 2 x 50 Watt or single 100 Watt power amplifier **£19.50**
- Electret microphone pre-amp (9866). Compact design that fits into the mike **£4.85**

MUSIC

★ Organ (7911 db). A new concept in organ-building. This live-active organ has 12 voices, sustain and tremelo with touch controlled switching. The PCB construction keeps the amount of wiring to a minimum. The organ is built in modular form with the possibility of adding extensions at a later date. One rhythm unit is already available.

- Organ less keyboard **£149.00**
- Organ with 5 octave keyboard **£219.00**
- Rhythm section **£33.00**

(Kit includes power supply with transformer, all PCBs, connectors, components). The Elekto Format is an instrument of advanced specifications that bears comparison with many commercially available synthesizers, but at a fraction of the cost.

- Interface (9721-1) **£18.15**
- Interface receiver (9721-2) **£3.60**
- (These two kits links keyboard and instrument)
- Power supply (9721-3). Including transformer and heatsink **£32.35**

- Keyboard divider (9721-4). You need one PCB per octave **£2.25**
- Voltage controlled oscillator VCO (9723) **£46.30**
- Voltage controlled filter VCF (9724) **£21.40**
- Voltage controlled filter VCF (9725) **£12.95**
- Attack, delay and sustain ADSR (9726) **£18.50**
- Voltage controlled amplifier VCA (9726) **£16.95**
- Low frequency oscillators (LFOs) **£11.15**
- Noise model (9728) **£11.85**
- COM output module (9729) **£32.20**
- 24 dB VCF module (9953) **£22.35**
- Resonance filter model RFM (9951) **£7.95**
- Ring modulator (79040) **£1.50**
- Front panels for format per module
- ★ Chorosynth (80060). A cheap mini-synthesizer **£57.90**

- ★ Elekto vocoder (80060). The first vocoder designed to build from a kit with excellent features. It has 10 channels **£162.50**
- Front panels for vocoder per channel **£1.25**
- Analog reverberation unit (9973). Kit with 1 SAD 1024 **£27.70**
- Piano. Excellent kit of an electronic piano with three voices
- Master tone oscillator / generator **£37.00**
- Octave PCB (9914) **£18.75**
- Filter PCB (9981) **£19.05**
- Power supply (9979) **£67.20**
- Digital reverberation unit Main board **£46.30**
- Extension boards

HOW TO ORDER:

Send a cheque or postal order to DORAM ELECTRONICS Ltd., Fitzroy House, Market Place, Swaffham, Norfolk PE37 7QH. All our prices include VAT, please add 40p for postage and packing.

Office hours Mon.-Fri. 9 a.m. to 5 p.m. Telex: 817912
Telephone: Swaffham (0760) 21627

* = NEW KITS

a de boer
company

INFRA RED REMOTE CONTROL SYSTEM

Make things happen at a distance without lifting a finger. There is no limit to the application of our ultra-versatile IR60 control system. Part 1: receiver


Multi function hand-held remote-control facilities are the 'in-thing' in modern Hi-Fi systems and music centres, but also have lots of other potential applications in domestic fields such as lighting and heating control, home security control, etc. We have never published a **really** sophisticated remote control system in ETI - until now.

Like all good modern remote control systems, our system uses an infra-red data link which is highly efficient, gives a good range, is not unduly directional and which, unlike ultrasonic systems, is remarkably interference-free. (Ultrasonic systems are, incidentally, now regarded as rather quaint, even though they do still occasionally appear in amateur-designed form in some of the other electronic magazines).

So what is so special about our system and what does it do? The system comprises two basic units, a hand-held 16-key transmitter and a mains-powered receiver-decoder unit. The two units together give control of three independent 64-step analogue channels, 16 'selector' channels, two bistable channels, and one on/off relay channel or switch. The hand-held unit is powered by a PP3 battery, which gives an operating life of about six months in normal use and gives a typical control range of about 15 metres.

The control system uses state-of-the-art LSI chips in the transmitter and receiver and is highly sophisticated in both technology and performance. The outputs of the receiver consist of three analogue voltages, one relay output, one 4-bit binary output and two single-bit binary outputs. How you interface these outputs to external devices is largely up to you: a few notes on the subject are given in this month's 'Designer's Notebook': we'll also be presenting some suitable interface projects and systems in future issues of ETI.

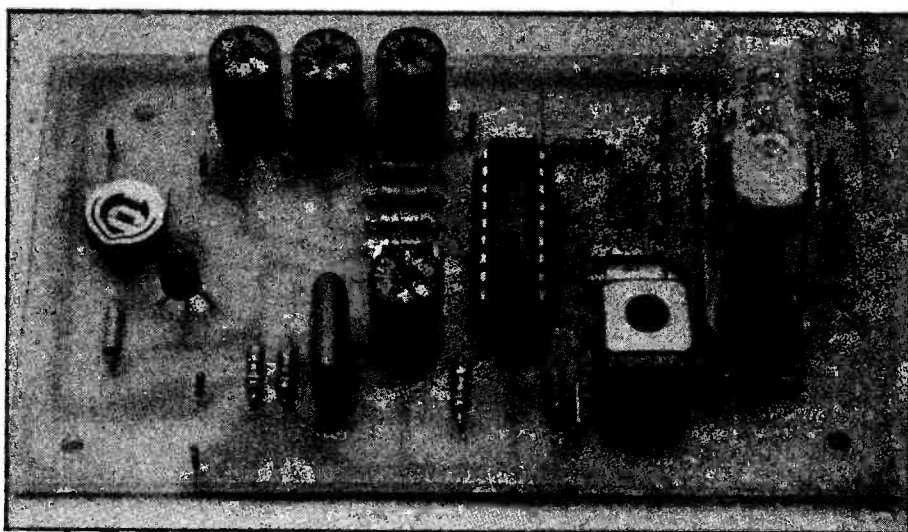The control action of the system is very sophisticated and is best understood by referring to Tables 1 and 2, which give detailed descriptions of the transmitter switch functions and the receiver output functions



Receiver board of the IR60. Details of the transmitter will follow next month.

SWITCH NUMBER	PIN CODE	FUNCTION	RECEIVER OUTPUT ACTION
1	1c	STANDBY (OFF)	Turns relay RLA off.
2	2c	ON	Turns relay RLA on.
3	1b	MUTE	Reduces volume output level rapidly to zero.
4	83a	VOLUME +	Increases volume output level.
5	83b	VOLUME -	Decreases volume output level.
6	83c	ANALOGUE 1 +	Increases Analogue 1 output level.
7	83d	ANALOGUE 1 -	Decreases Analogue 1 output level.
8	84a	ANALOGUE 2 +	Increases Analogue 2 output level.
9	84b	ANALOGUE 2 -	Decreases Analogue 2 output levels.
10	1d	RESERVE 1	Switches Reserve 1 (RSV1) output between high and low states on alternate operations.
11	2d	RESERVE 2 / ON	Switches Reserve 2 (RSV2) output between high and low states on alternate operations: Turns RLA on.
12	2a	PROGRAM STEP + / ON	Increments binary channel-select output by one step per operation: Turns RLA on.
13	2b	PROGRAM STEP - / ON	Decrements binary channel-select output by one step per operation: Turns RLA on.
14	5a	CHANNEL 1 / ON	Sets binary output to 0000 (Channel 1) state: Turns RLA on.
15	6d	CHANNEL 8 / ON	Sets binary output to 1110 (Channel 8) state: Turns RLA on.
16	8d	CHANNEL 16 / ON	Sets binary output to 1111 (Channel 16) state: Turns RLA on.

Table One: receiver output functions of the IR60.

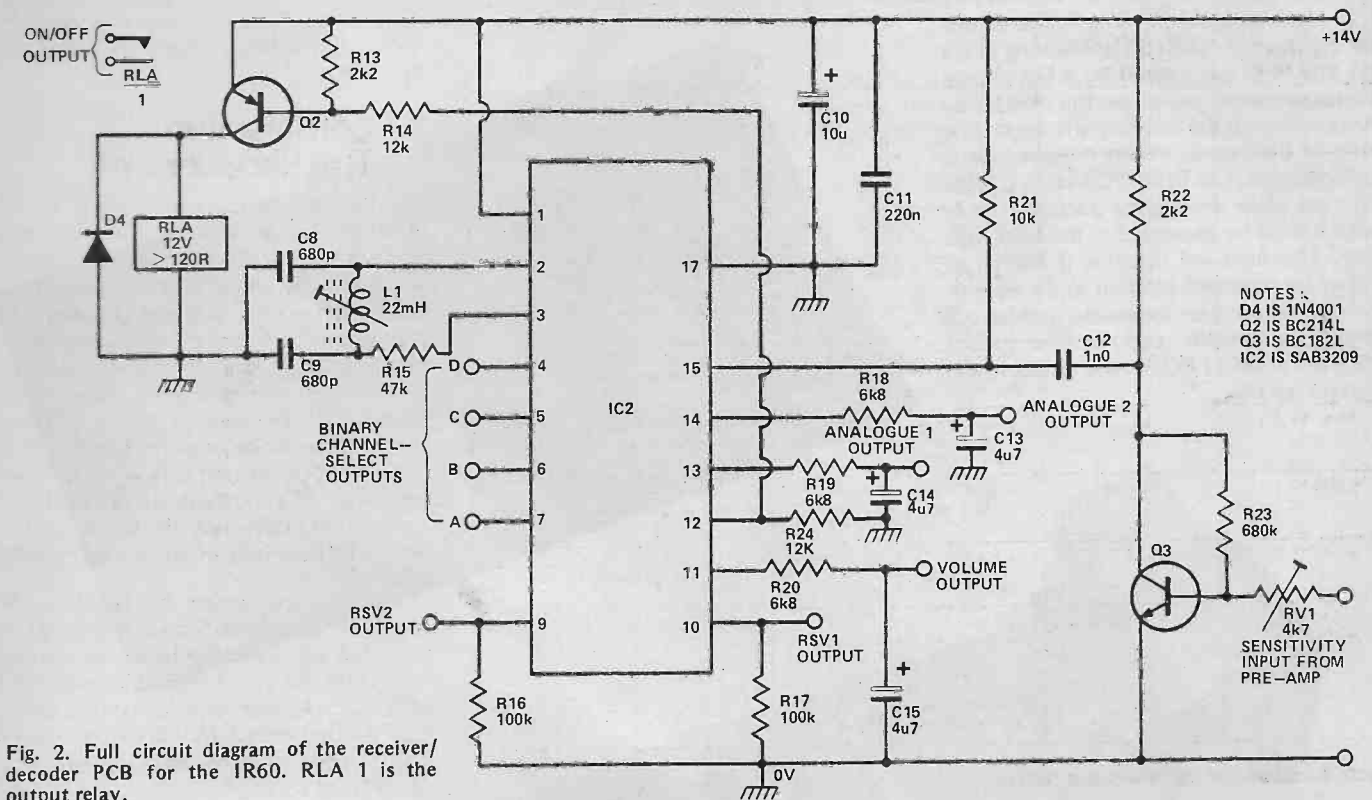


Fig. 2. Full circuit diagram of the receiver/decoder PCB for the IR60. RLA 1 is the output relay.

HOW IT WORKS

The coded infra-red signal from the transmitter is detected and amplified by the receiver unit and ultimately causes some receiver output function to occur. The receiver unit comprises three main sections, the infra-red receiver preamplifier, the main receiver/decoder unit and the power supply.

The transmitted IR code signal has a basic frequency of about 30 kHz (half of the transmitter clock frequency) and is detected by IRD1 in the receiver preamp and amplified first by Q1 and then by IC1. A problem in designing IR preamplifiers is that the circuit not only has to provide high gain for long range operation but also must not saturate when the transmitter is placed only a few inches from the receiver.

With the latter point in mind, R1-D2-D1 and C2 are used to prevent the bias point of Q1 shifting under heavy drive conditions. D2 and D3 clip the level of the final IC1 output signal, to prevent overdriving of following stages. The values of C2-C3-C4-C5 and C7 are chosen to make the preamplifier

reasonably frequency selective, thereby ensuring a good low-noise figure. The pre-amp unit must be mounted in a screened case.

The output of the preamp is further amplified by Q1 on the main receiver/decoder board and then fed to the pin 15 signal input terminal of IC2, the P-MOS LSI receiver chip. This chip is provided with a clock oscillator (L1-C8-C9-R15) which is tuned to the transmitter clock frequency (double the serial code frequency). The chip checks the serial code input signal for correct number of bits, bit duration, etc, processes it and then 'dumps' the resulting code signal into a register, from which it is then converted into a useful output action.

The IC2 outputs from pins 4 to 7 form a 4-bit binary signal that can be used to externally select any one of 16 channels. The outputs of pins 9, 10 and 12 are single-bit signals that can be set high or low via the transmitter commands: the output of

pin 12 is used to activate a relay (which can be used for switching power to an external circuit, etc) via Q2.

The IC provides three analogue output signals (at pins 11, 13 and 14). Each of these outputs takes the form of a 1 kHz (approx) square wave that can have its mark/space ratio (and thus its mean level) varied over a full span in 64 discrete steps via the transmitter command signals. These variable mark/space signals are converted to DC analogue voltages via low-pass filters (C13-R18, C14-R19, C15-R20) and can be used to control external voltage-controlled attenuators and amplifiers (for remote gain control) and filters (for remote tone control), etc.

The preamp and main receiver/decoder boards are each powered from a regulated 14 volt supply derived from the mains via T1-D5-D6-C16 and series-regulator network Q4-ZD1-R25. The circuit is required to supply current up to only a couple of hundred milliamps.


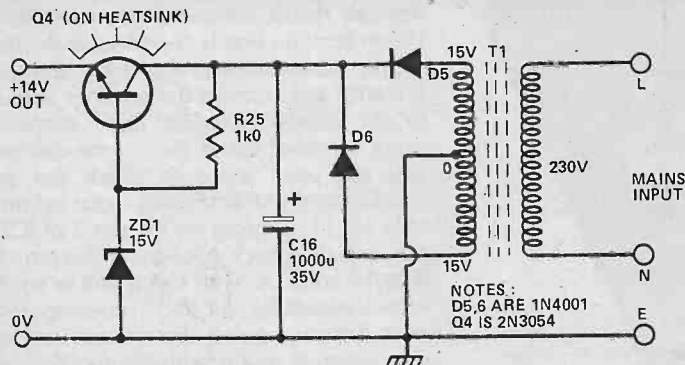
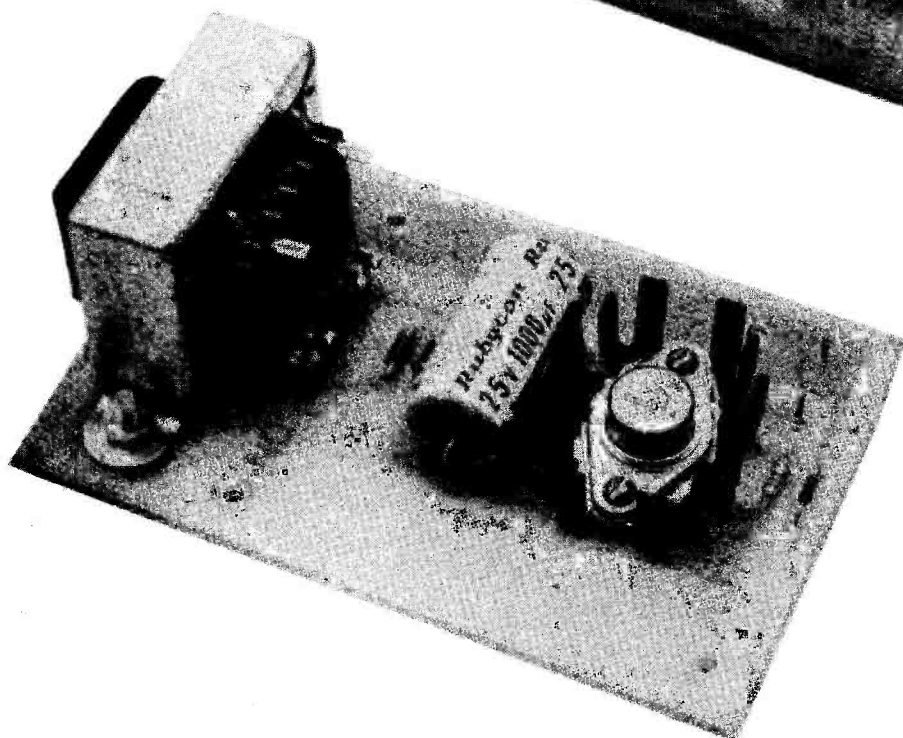


Fig. 3. (left) circuit diagram of the PSU for the IR60 system.

BUYLINES

The SAB3209 IC could present a problem for your local component emporium. However, Electrovalue and Watford Electronics are stockists for this IC. The relay and infra-red detector can also be purchased from Watford Electronics. L1 was obtained from Ambit International. All other components are common types and should not pose any problem.

Next, build the pre-amp PCB as shown on the overlay. The odd positioning of C1 on this PCB was caused by a last-minute correction to our prototype: this mod is also responsible for the two empty holes on one side of the board. When construction is complete you can fit the PCB into a screened case (dare we suggest a tobacco tin?), which must be grounded to the zero volts line. The infra-red detector (I RD1) can either be mounted external to the case or can be mounted on the inside, looking out through a suitable aperture. Take special care to connect I RD1 to the circuit in the correct polarity.

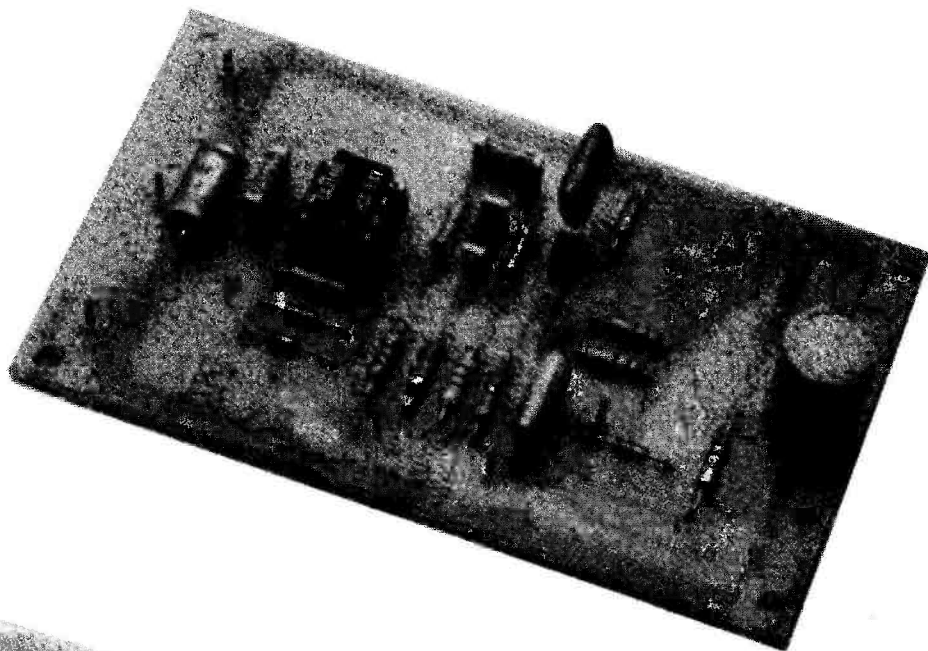


Shown here are the three PCBs which comprise the IR60 receiver system.

Top: the preamp board.



Left: a PSU suitable for driving the system.

Below: the decoder board.

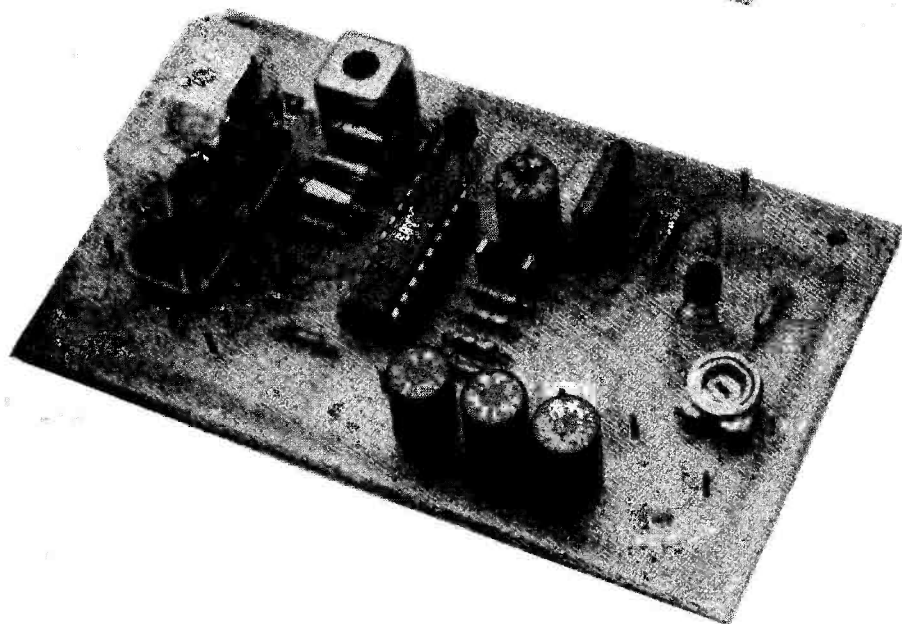

Finishing Off

Finally, build up the main receiver/decoder board, complete with relay RLA. When construction is complete, make the supply connections to the board and the pre-amp and connect the pre-amp output to the receiver/decoder input terminal using screened cable. Switch the unit on and use your 'scope to check that an approximately 60 kHz clock signal (adjustable via L1) appears on the pin 3 of IC2. You can also check that signal-input pin 15 is at 14 volts DC with half a volt or so of noise (adjustable via RV1) superimposed on it. If the two points above check out OK your receiver unit is probably functioning correctly.

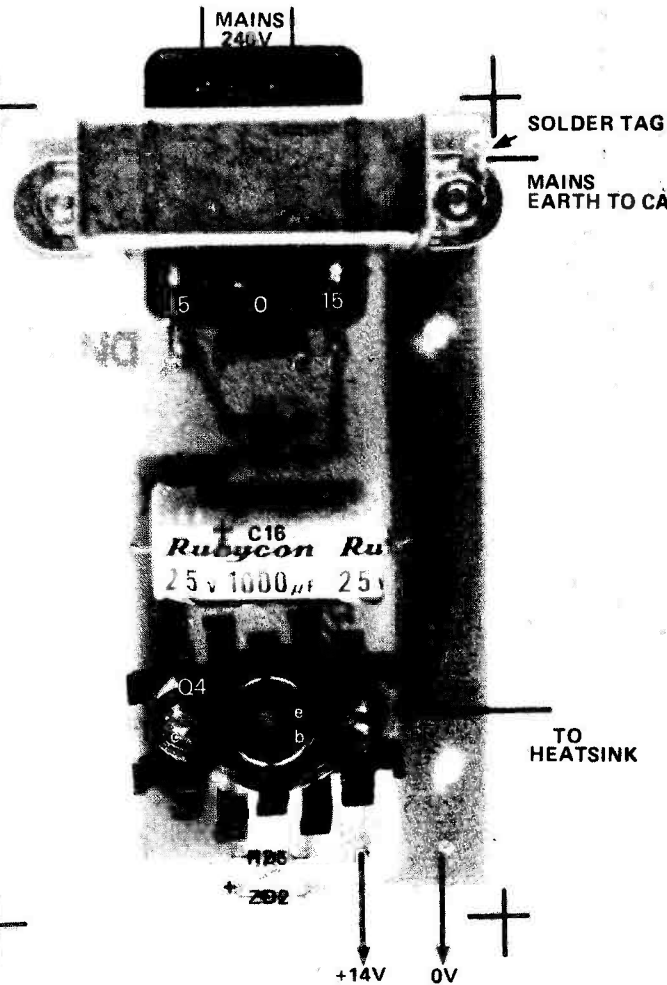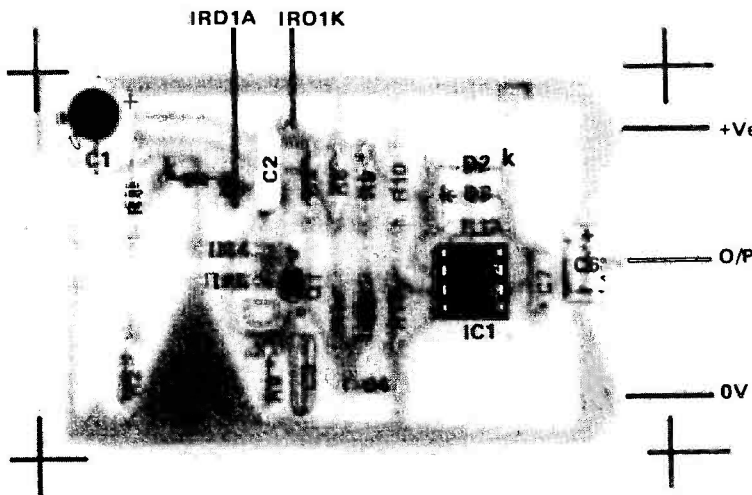

PARTS LIST

RESISTORS All 1/4W 5%

R1	22k
R2	8k2
R3,31	10k
R4	1M2
R5	1M0
R6,15	1k0
R7,9	3k3
R8,18,19,20	6k8
R10,11,15	47k
R12	470k
R13,22	2k2
R14,24	12k
R16,17	100k
R23	640k

POTENTIOMETERS

PV1	4k7 min horiz preset
-----	----------------------

CAPACITORS

C1	22µ 63V PCB electrolytic
C2	47n polyester
C3	10n polyester
C4	1n5 polycarbonate
C5	1n0 polycarbonate
C6	2u2 63V electrolytic
C7	4n7 polycarbonate
C8,9	680p polystyrene
C10	10u 63V PCB electrolytic (Siemens type)
C11	220n polyester
C12	1n0 polycarbonate
C13,14,15	4u7 63V PCB electrolytic (Siemens type)
C16	1000u 35V electrolytic

SEMICONDUCTORS


IC1	CA3140
IC2	5AB320F
Q1,3	BC182L
Q2	BC214L
Q4	2N3054
D1-3	1N4148
D4-6	1N4001
IRD1	SFH205
ZD1	15V 400mW Zener

MISCELLANEOUS

RLA	12V > 120R SP C/O PCB relay
L1	22 mH variable coil type
	87BN132-HM2
T1	15-0-15 8VA
	Screened case 115 x 65 x 35 mm

These overlays are for the PCBs in the receiver system. Reference to these and the photos on the facing page should facilitate construction.

Next month: Transmitter details.

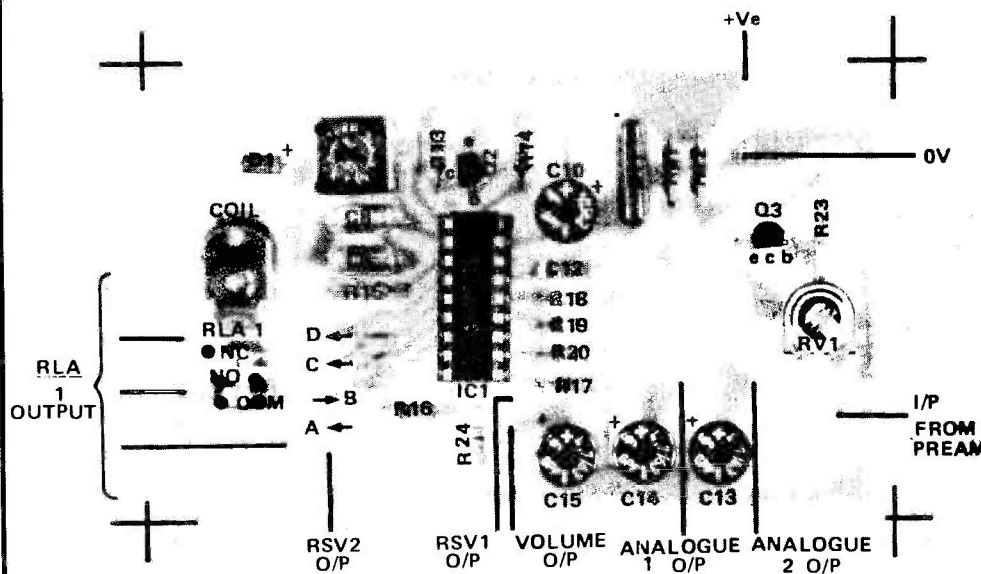

ETI

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.50

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

Book 1 Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.

Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.

Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.

Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.

DESIGN OF DIGITAL SYSTEMS £11.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates: NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.


THE ALGORITHM WRITER'S GUIDE £3.75

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.



Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.

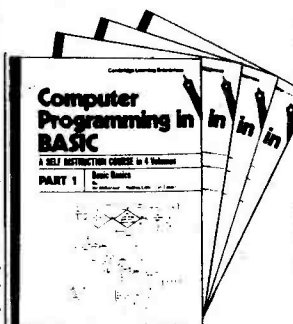

COMPUTER PROGRAMMING IN BASIC £7.50

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

FORTRAN COLORING BOOK £5.40

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

A.N.S. COBOL £4.40

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

GUARANTEE - No risk to you

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

....Digital Computer Logic & Electronics @ £7.00

....Design of Digital Systems @ £11.50

....Algorithm Writer's Guide @ £3.75

....Computer Programming in BASIC @ £7.50

....BASIC Handbook @ £11.50

....Fortran Coloring Book @ £5.40

....A.N.S. Cobol @ £4.40

All prices include worldwide surface mailing costs (airmail extra)

IF YOUR ORDER COMES TO OVER £18, DEDUCT £2

Cheques/PO's payable to Cambridge Learning Enterprises or charge to Access/Barclaycard/Diners Club/etc
account no

Telephone orders from credit card holders accepted on 0480-67446. Overseas customers (inc Eire) use credit card, or bank draft in sterling drawn on a London bank, or International Money Order (add £1 handling charge.)

Name

Address

.....

Cambridge Learning Enterprises, Unit 10, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.

MELODY MULTI-ALARM CHRONO

- ★ Four Independent Modes
- ★ Normal watch
- ★ 24-hour musical alarm
- ★ Second time zone
- ★ Chronograph 1/10 sec

Melody test function, back light and lots of other features.



A101
£17.95

A62
£16.95



DUAL TIME ALARM-CHRONO

Incorporates high quality SANYO module, hours, mins., secs., day, date, alarm, chrono, dual-time, special battery hatch, mineral glass front.

- ★ Ladies' Cocktail Watch £9.95
 - ★ Ladies' Solar Alarm £11.95
 - ★ Gent's 6 Digit Alarm £9.95
 - ★ Gent's Memory Calendar Alarm Chrono £21.95
 - ★ 24 Tune Electronic Door Chime £13.95
 - ★ Videomaster Compute-a-Tune: 3 octave keyboard; replay with added musical effects £19.95
 - ★ Videomaster Star Chess £59.95
 - ★ Database Video Game £79.95
- S.a.e. for leaflet and price list on video games.

GUARANTEE:

We will refund your money if not satisfied with our goods (return goods within 7 days in good condition). All our prices are inclusive of P&P—no hidden extras.

**AKHTER
INSTRUMENTS LTD.**
11-15 BUSH HOUSE
HARLOW, ESSEX CM18 6NS
Ring on Cheap Rate 6 p.m.-8 p.m.
0279 414464

Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR,
PORTSMOUTH, HANTS. PO3 5BJ

8 DIGIT 0.1" LED DISPLAY multiplexed, common cathode **99p** each. **DIGITAL ALARM CLOCK MODULE** with 0.7" display. With data **£5.99** each. **4 DIGIT CLOCK LCD** 0.5" digits, supplied with data, **£4.99** each. **MM5316** digital alarm clock chip, with data, **£2.29** each. **REJECT CALCULATORS** Untested, but good value for spares, **£2.50** each. **LED WRISTWATCH IC** Mostek MK5030, with data, **95p** each. **LED WRISTWATCH DISPLAY** type DI5501, 0.1" digits, with data **95p** each. **SUPER SAVER** Purchase an MK5030 and a DI5501 for only **£1.50** the pair. **NOTE** the MK5030 and DI5501 are housed in a 'legless flatpack' style package and require some fairly fine soldering. **20-KEY KEYBOARDS** calculator keyboards, 2 for **99p** (not for use with NORTEC4204 calc. chip) **4 DIGIT 0.8" LED DISPLAY** common cathode, with data **£3.75** each. **DIGITAL MULTIMETER CHIP** MM5330 IC to build a 4 1/2 digit multimeter, with data, **£3.48** each. **SUPER QUALITY JACK SOCKETS** 1/4" (6.35mm) jack sockets, mono **23p** each, stereo **25p** each. **SLIDE POT KNOBS** please state colour required, **11p** each. **ROTARY VOLUME CONTROL KNOBS** nice style, 18mm diam. Black with coloured cap, please state colour required, **18p** each. **10 LED DISPLAYS** Untested material, 0.1" digits, common cathode, **95p**. **6 DIGIT 0.1" LED DISPLAY** multiplexed, common cathode, **99p**. **555 TIMER IC** with data and applications booklet, **23p**. **POLARIZING FILM** max. 19" wide, any length, only **2p** per sq. inch. Any size cut. **SLIDER SWITCHES** 2 pole, change over, **15p** each. **PUSH BUTTON SWITCHES** spring loaded (momentary) with one n.o. contact, **14p** each. **CALCULATOR CHIP** Nortec 4204, 4 function and constant, with data, **80p**. **2102 MEMORIES** Dynamic memories for your micros, with data **95p** each. **WRISTWATCH LCD**, supplied with polarizers and data sheets, **99p** each.

NEW CATALOGUE (No. 7) NOW AVAILABLE.
SEND MEDIUM S.A.E. for YOUR FREE COPY.
POST AND PACKING PLEASE ADD 35p (OVER-SEAS ORDERS ADD 90p)

V.A.T. ADD 15% TO THE TOTAL OF GOODS AND P&P
FULL SATISFACTION GUARANTEE ON ALL ITEMS

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in **£3.00** with all symbols for direct application to P.C. board. Individual sheets 30p each.
(1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8—10—12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1.20**.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/4in kit or 1/4in kit. **£1.20** complete. State size.

All orders dispatched promptly.

All post paid


Shop and Trade enquiries welcome
Special Transfers made to order

**E. R. NICHOLLS
P.C.B. TRANSFERS**

DEPT. ET15

**46 LOWFIELD ROAD
STOCKPORT, CHES. 061-480 2179**

The Thandar 10MHz Portable Oscilloscope

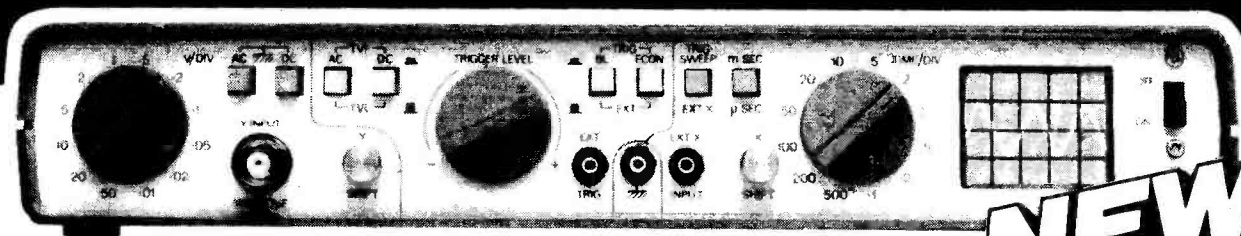

NEW

**A low weight, low power Oscilloscope
that provides workshop facilities but
with true portability £139.00 + VAT**

The Thandar Portable Oscilloscope is a breakthrough in development. Now, for the first time, every engineer, service-man and technician can carry with him this piece of electronic test gear weighing less than 2 pounds, yet having the performance of most standard bench oscilloscopes. The Thandar Portable Oscilloscope is less than 2" thick. It is based around a 2" diagonal CRT and has a 10 MHz bandwidth with sensitivity down to 10mV per division. Full trigger facilities are provided, including Bright Line Auto with TV Line and Frame positions. The superb ergonomic design of the Thandar Portable Oscilloscope enables it to be carried in a briefcase or toolkit. It can be held in one hand or operated whilst hung around the neck.

Send now for further details or call at your local Thandar Stockist.



**Sinclair Electronics Ltd.,
London Road, St. Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: 0480 64646. Telex: 32250**

Sinclair Electronics Ltd. reserve the right to alter prices and specifications on Thandar equipment without prior notice.

To
**Sinclair Electronics Ltd,
London Road, St. Ives,
Huntingdon, Cambs, PE17 4HJ.**

Please send me further technical information, price list and stockist list of the Thandar Portable Oscilloscope. I am also interested in

Digital Multimeters
Pocket Multimeters
Pocket Frequency Meters

Name:

Address:

thandar
SINCLAIR ELECTRONICS LTD

HEISENBERG'S UNCERTAINTY PRINCIPLE

It affects all aspects of electronics. It is a fundamental concept as basic as ABC to a physicist and this is the easiest way to find out more about it. A.Lipson explains.

Most people who read a lot of science fiction (as I must confess I do) have probably heard of Heisenberg's Uncertainty Principle at some time or other, but the vast majority are, if you'll pardon the pun, very uncertain as to its nature. Well, never fear; a paragraph or two hence you, too, will be able to confuse friends, relatives and the cat....

Exactly Where?

The uncertainty principle as such was first stated by a German physicist, Werner Karl Heisenberg, in the late 1920s. He said, essentially, that it is impossible to measure both the position and momentum of particle simultaneously. Now this wasn't quite such a stupid statement as it sounds - what he actually meant by this was that, in measuring either the position or momentum of a particle, you must necessarily be affecting the other in a way which is unpredictable and, in the case of small particles such as electrons, significant. At this point the reader may feel inclined to cry out 'Ah, but I can tell exactly where something is just by looking at it and that doesn't affect its momentum, does it?'. Well, sorry to disappoint you, but you're wrong on two counts. You cannot tell *exactly* where something is just by looking at it - there is a slight uncertainty of the order of the wavelength of the light you are using - and even looking at a thing *does* affect its momentum. Light, you see, is made up of particles. In order to look at an object, it is necessary to bounce some light particles - called photons - off that object. Now these particles carry momentum, and so when they bounce off the object, they must necessarily change its momentum, as well. For normal objects, as large as the ones we're used to, this doesn't make a lot of difference, but if you start working on the atomic scale, with electrons, etc, then a photon or two can make a lot of difference. Before we say any more, let's have a look at the basic equation that Heisenberg actually used (No need to get worried - it's the only equation we'll see, and isn't all that difficult to understand).



$$\Delta p \times \Delta x \geq \frac{h}{2\pi}$$

In this equation, the symbol Δp stands for the uncertainty in the momentum of an object, Δx stands for the uncertainty in the object's position, the symbol h stands for a constant (known as 'Planck's Constant') and the symbol \geqslant means 'is at least as big as'. Heisenberg said, then, that if we find the product of the uncertainties in position and momentum, then they will be at least as big as $\frac{h}{2\pi}$, which has a value of about 1.05×10^{-34} joule seconds. (Exactly why it is measured in units called joule-seconds is rather irrelevant to the present discussion, so we shall leave it for some other time). Now, as you can see, this is a pretty small value approximately given by a zero followed by a decimal point and thirty three more zeros before we put a 1 down. This explains why we do not see the effects of the uncertainty principle in real life - given the uncertainty in position or momentum of an object that we have found experimentally, the uncertainty in the other can still be incredibly small. Let us take the case of the magazine you are presently holding. We will suppose, for the sake of simplicity, that, using a very good microscope you can measure its position accurate to within one wavelength of light, or about 0.00005 centimetres (which is about as accurate as you could get, using light). Then we find from the uncertainty principle that the magazine must have a momentum whose uncertainty must be at least $\frac{h}{2\pi \times px}$ or about $0.000000000000000000000000000002 \text{ kg m s}^{-1}$.

Speedy Accuracy

[illegible]

Effective Measurement

In fact, once you start thinking about it, all the uncertainty principle says is that it is impossible to measure something without affecting it in some way and this is almost common sense. As we have seen, looking at something to check its position must necessarily affect its momentum. It is impossible to measure the voltage across, say, a capacitor, without removing a little of the charge, and so lowering the voltage. You cannot check the pressure in a car tyre without the gauge you use removing a little of the air, and so on.


Impossible Position

Heisenberg's Uncertainty Principle is that it is impossible to measure position or momentum of an object without affecting the other in a random and unpredictable way. In the same vein, Albert Einstein once proved from the uncertainty principle that it is impossible to measure both the energy and time involved in an interaction. This is rather less obvious than the other cases we have examined, but it is indeed so.


How Smart Is Alec?

The uncertainty principle, then, means that we can no longer, in physics, talk of the exact position, momentum, etc of a particle; we can only talk in terms of probabilities - where a particle is likely to be, what the average velocity of a bunch of particles is likely to be under given circumstances, and so on. That is, until some smart alec comes along and proves it all wrong.....

ETI

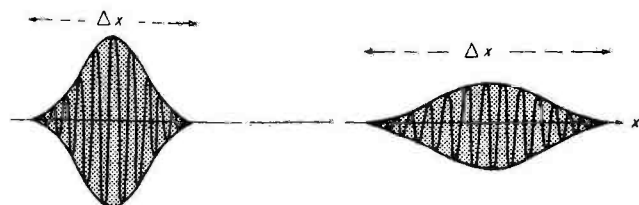

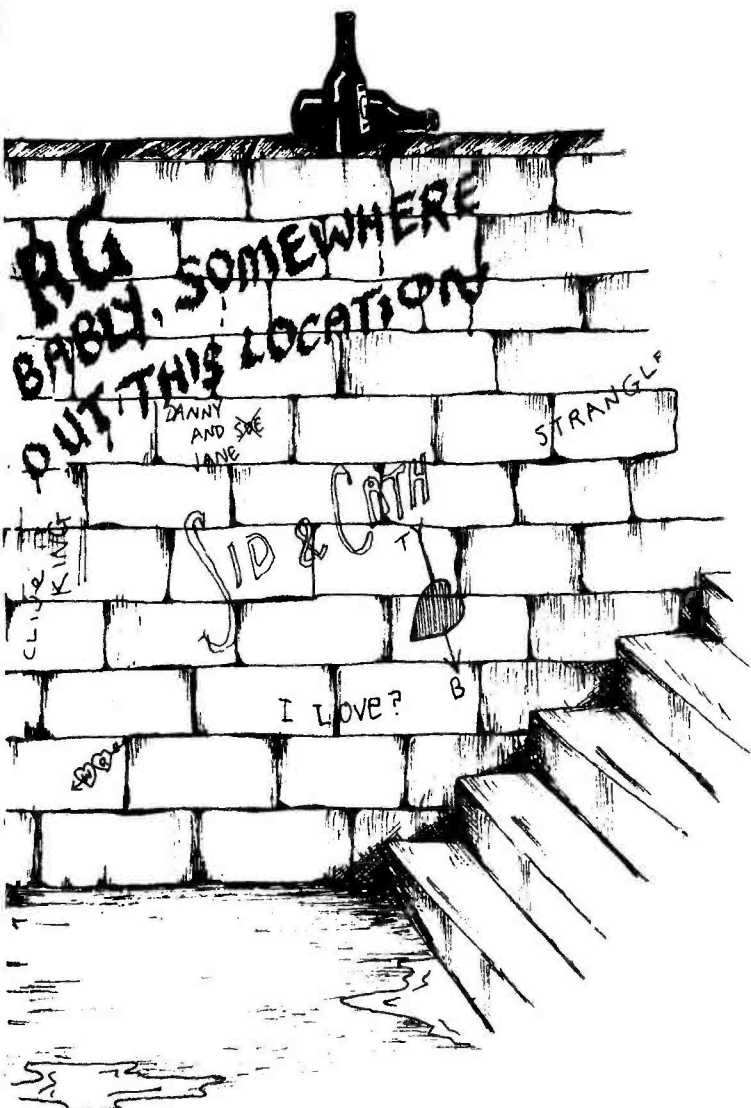Energy and mass are equivalent. The position of a particle, therefore, cannot be measured with absolute certainty. There must always be an uncertainty of Δx in the measurement of x .



ETI JUNE 1980

WHAT TO LOOK FORWARD TO
IN OUR NEXT ISSUE!
ON SALE MAY 2ND.

DESIGNERS HANDBOOK

Now this is the one that even we've been waiting for. Many is the rainy Sunday that has passed with the enthusiast huddled intent over his workbench. Many too are the times he has howled loud into the storm when a project fails to operate for the want of one small piece of circuitry to link this with that or that with this, that or the other.

Information to allow him to design his own circuits quickly and simply is sadly lacking. Books take everything too seriously and at too much length. Looking anything up takes hours — by which time the rain has stopped and

Next month we present our Analogue Designers Handbook from the man of many nodes, Tim Orr. He presents the quick and easy way to amplifiers, filters, oscillators etc. etc. — and they'll be all your own work! Can you afford to miss it?

DRUM SYNTHESISER PROJECT

No, I don't believe you've never heard one of these. Just about every single produced in the last millenium has those noises all over it. You know, those noises — the ones that sound like a cat being stepped on backwards at great speed.

If you really don't know what we're going on about you'd better read ETI next month hadn't you?

HOUSE WIRING

So you think you know how it's done eh? Just wait until you pull the bathroom cord one day and the toast pops up: switch on the hall light only to have the TV burst into life Before long the house is a mass of ripped out wiring and is echoing to the sound of slamming front doors as enraged spouses storm into the sunset. Don't do it until you've read our superb article from Ray Marston next month!

FM LINE DISTRIBUTION

Have hi-fi in any room in the house without extra wires. Superb sound that follows you around. Uses the mains to (safely) distribute an audio signal anywhere the wires are connected to. The answer to a million prayers!

TAPE RECORDER RESPONSE OPTIMISATION SYSTEM

It's one hell of a title for an extremely straightforward little device that will allow you to optimise bias conditions on any tape recorder. Works with a minimum of fuss and doesn't cost more than the Empire State Building to construct.

ANTI-MATTER

Better forget the Star Trek reaction pods. Throw away the tickets to another Universe. Instead read our explanation of the real truth (?) behind around and for anti-matter.

Articles mentioned herein are in an advanced state of preparation, however, circumstances may dictate charges to the final contents.

The Proto-Board®

Now circuit designing is as easy as pushing a lead into a hole ...

No soldering
No de-soldering
No heat-spoilt components
No manual labour
No wasted time



For quick signal tracing and circuit modification
For quick circuit analysis and diagramming
With or without built-in regulated power supplies
Use with virtually all parts — most plug in directly, in seconds.
Ideal for design, prototype and hobby

NO	MODEL NO	NO OF SOLDERLESS TIE POINTS	IC CAPACITY (14 pin DIP's)	UNIT PRICE	PRICE INC. P&P 15% VAT	OTHER FEATURES
1	PB 6	630	6	9.20	11.73	Kit
2	PB 100	760	10	11.80	14.72	Kit
3	PB 101	940	10	17.20	21.21	
4	PB 102	1240	12	22.95	27.83	
5	PB 103	2250	24	34.45	41.34	
6	PB 104	3060	32	45.95	54.56	
7	PB 203	2250	24	55.15	65.14	5V @ 1A
8	PB 203A	2250	24	74.70	87.63	5V ± 15V
9	PB 203AK	2250	24	59.00	69.57	5V ± 15V & Kit

Tomorrows tools for todays problems

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited,
Dept. 9U Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ.
Telephone: Saffron Walden (0799) 21682
Telex: 817477.

C.S.C. (UK) Ltd., Dept 9U Shire Hill Industrial Estate, Unit 1, Saffron Walden Essex. CB11 3AQ

1	Qty Req	2	Qty Req	3	Qty Req	4	Qty Req	5	Qty Req	6	Qty Req	7	Qty Req	8	Qty Req	9	Qty Req
---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard, Access.

American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The C.S.C. 24 hour 5 day a week service
Telephone (0799) 21682 and give us your Barclaycard, Access,
American Express number and your order will be in the post immediately

For FREE catalogue tick box ☐

AUDIOPHILE

What have lovely Latin ladies got to do with metal? What has D-day got to do with hi-fi? Confused? You won't be after this month's episode of... Audiophile. Ron Harris tries to put some iron in his system with Sony's new TCK 55 II

It all started with a phone call one dark and rainswept Tuesday.

'Metal' said the voice on the phone.

'Well no-one's perfect' said I defensively.

'No no metal tapes' said the voice hurriedly.

'Plastic poodles' said I not wishing to appear dim.

'Why did you say that?' enquired the voice, a little hurt.

'I dunno, seemed to fit somehow' said I, reddening rapidly.

'Look here, if you persist upon being silly.....'

'You started it mush. What metal anyway?.....' that was the magic question and the golden key to communication. It transpires that the voice belonged to Mr. Sony (UK) wishing to discourse upon the subject of iron tapes and machines to play them on. Our telephone operator introduced him as a, quote, geezer wot wants to iron someit art wiv yer, unquote. Articulate our switchboard.

Despite this highly inauspicious genesis the word about heads to pass ferric substances across at 1/78 IPS managed to find an editorial ear and this month's Audiophile came, screaming, into the world.

Some Sony Day

As the sidehead says the machine I'm looking at is a new model from Sony, the TCK55 II. One of a range of metal-ready decks. Sony get themselves a fair few mentions herein, simply because they have a superb PR department and make some excellent hi-fi (or is that the influence of the PR men again?). Whenever we've needed something quickly (which is always) or have cried out into the night for assistance, they have been one of first people to put out a helping hand - so once I had decided it was time to take a look at reasonably priced (i.e. less than a Rolls) example of this new fangled metallic machinery it came as no surprise to find them ready and able to help at shorter than short notice.

It was also they who gave birth, in this country, to the Elcaset - a tape format much beloved of this particular editorial personage. I find it hard to forgive you lot out there for killing it off the way you did. Why did not hordes of you besiege hi-fi shops and hand over vast sums of money to procure an EL7? It was a magnificent medium and one that I will long defend as having been all that cassettes were supposed to have been.

Still, people see things differently I suppose. I dare say that there is one Englishman, somewhere, who remebers D-day for walks in the park, kisses in the sunshine and falling gently in love with a beautiful Latin lady over a candlelit dinner, treasuring the day for the warmth in her eyes...

Switch In Appearance?

Metal tapes look set to provide that vital step-up in cassette performance that has been missing so far. At a price. Their transient handling and H.F. extension is far enough superior to the more normal oxide blends to be acknowledged as a new standard of performance.

It is the fact that much higher levels of signal can be recorded at high frequencies (over 6 dB at 15 kHz) for the same distortion figure that gives the new formulation a much cleaner top end performance and transient behaviour. Distortion overall should also be lower.

Equalisation for the new type has been standardised at 70 μ s (the same curve as for CrO₂ tapes) but bias has to be around 10 dB higher, due to the iron's much higher coercivity. Erase heads too must therefore be capable of more 'muscle' to achieve a satisfactory 'wipe-out'.


This extra electronics manifests itself, as usual, as an extra switch on the front panel! In the case of TCK55 II considered here an extra slide position on both the bias and equalisation selectors.


Facilitating Uses

This machine offers a goodly number of features, for its price, and one of the nicest is called 'AUTO-PLAY'. Pressing both the Rewind and Play buttons causes the machine to rewind to the start of the tape then begin playing automatically. No more standing by the deck counting down the seconds while your tea goes cold.


Of course if we could all remember to reset the memory to 000 every time, then that function could serve this requirement too, but do we? No chance! A simple and useful addition then, and like all the best ideas obvious once you see it!

Metering too is well thought out here. Normal VU meters monitor each channel for average readings and a centre bar of LEDs reads peak level. Between the two it is easy to obtain a good setting - and to see how woefully slow VU meters are! With metal tapes you set higher than normally and peaks up to +4 dB produced no audible distortion or compression, thereby proving both the tape and head circuitry.

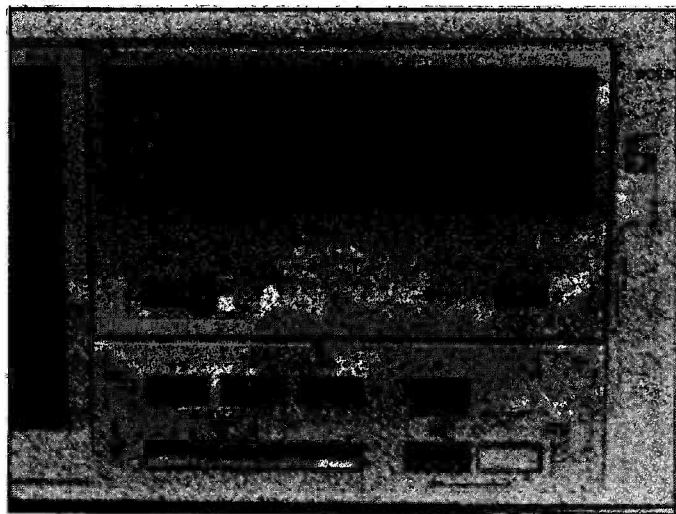

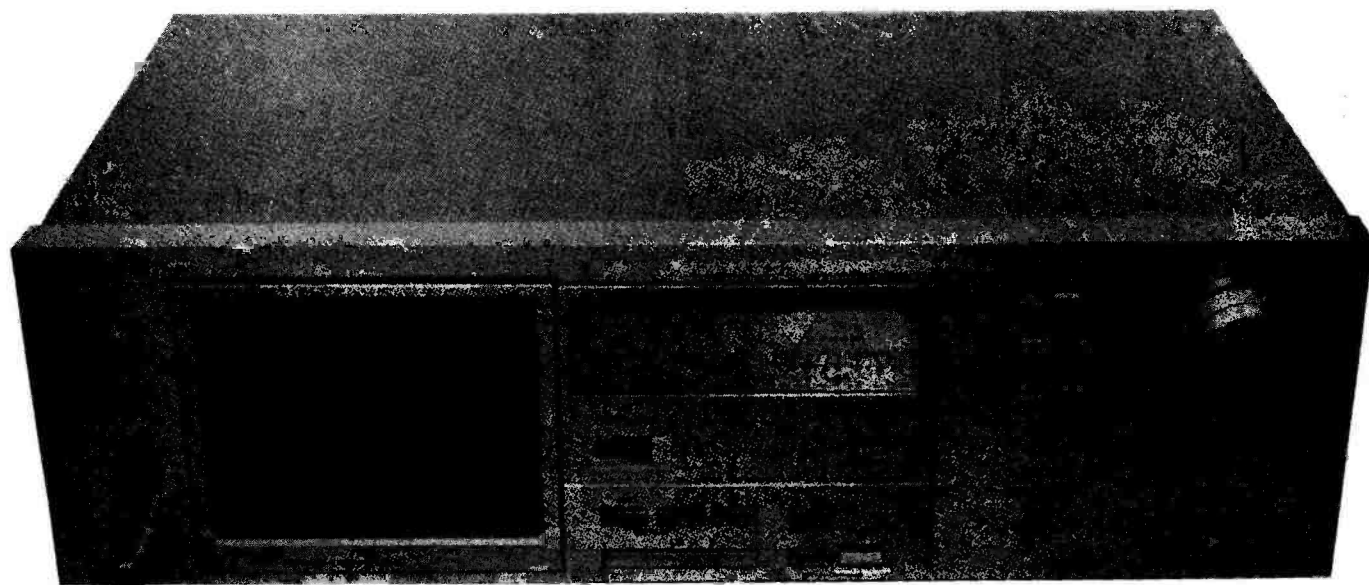

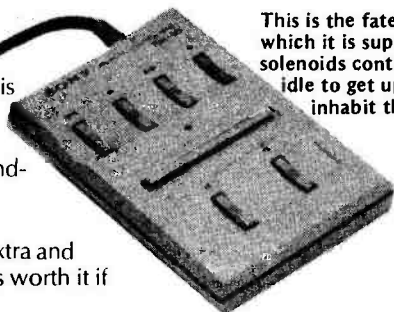The control panel is solenoid operated and full remote control is thus possible via a hand-held function selector (RM-50) which front panel. This is an extra and costs around £20, but is worth it if you're as lazy as I am.



This is the fateful machine itself. The remote control unit (RM50) is shown plugged into that which it is supposed to be plugged into. Control is by DC voltages passed via the cable to the solenoids controlling the functions. Very useful too if your legs have dropped off, or are just too idle to get up to push the buttons. The cable is more than long enough— unless you happen to inhabit the Albert Hall.

The controls work smoothly and positively and I could not possibly fault them. Somehow though I didn't like them at all. No criticism implied they were just not to my taste.

As usual with this company's offerings the whole n operates with a smoothness and efficiency that is totally pronal. It makes me almost wish a button would drop off or someth anything to show some fallibility in those inscrutable Or ental designers.

Mute Point

Another unusual feature is the 'REC. MUTE' which provides for four-second blank periods to be inserted into the recordings auto-


matically. Sony say it is useful for removing radio commercials and the like. I contend the point not at all, being totally confused by the thing.

Making recordings on the TCK55 II proved to be very easy indeed, with the LED metering quickly proving its worth in use. I tried the machine with a wide selection of tapes, from Sony's own new AHF and Metal to TDKs SA and MAR formulations. Generally speaking the best results came from their own brand and Maxell. EXCEPT when I reached the iron settings. More of that in a moment.


Wow-What Flutter?

On test the TCK55 II came out very well indeed. Taking an extract from the results:- (overleaf)

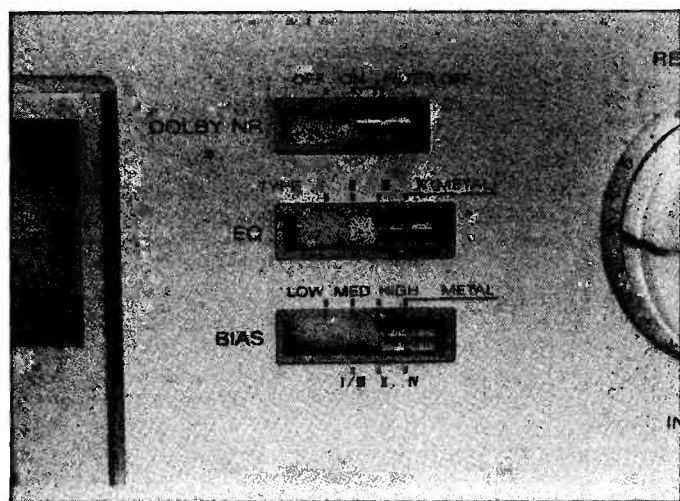Far left: a close-up of the metering provided on the TCK55 II and the control panel beneath it. Note the LED column which reads peak level better than meters ever could. Not a new idea, but well executed here.



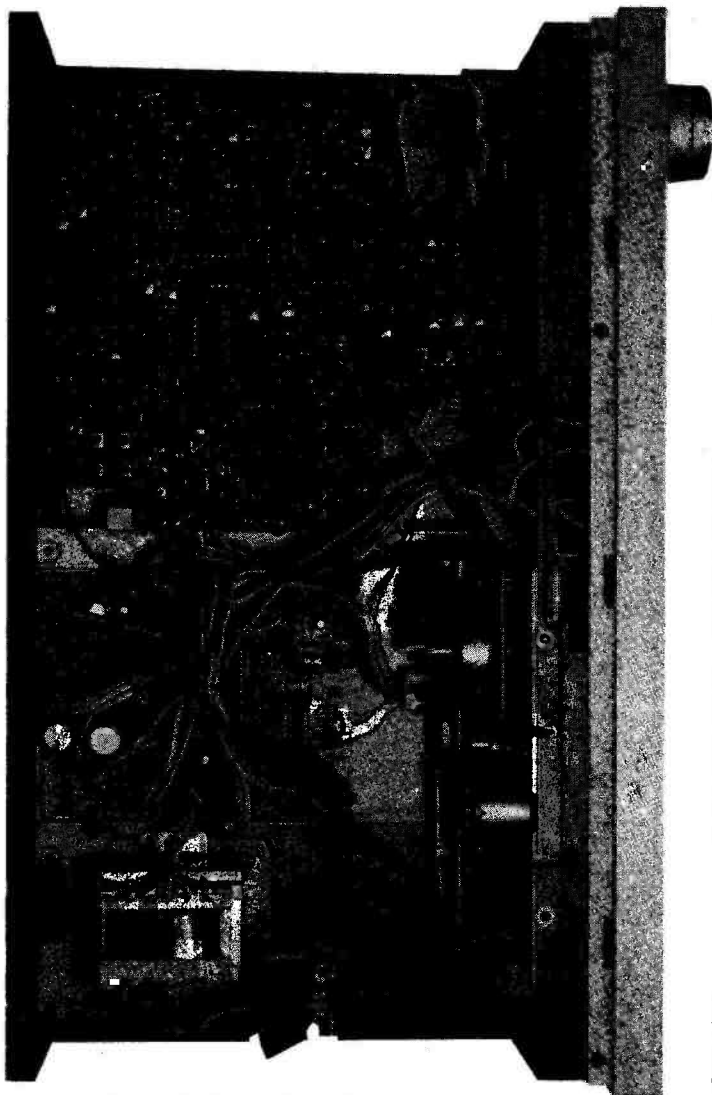Left: the bias and equalisation controls. Sony provide a useful table which gives recommended settings for a wide variety of tape types in their instruction book. The numerals on the panel refer to this table. Strangely my sample of the machine seemed over-biased for Sony's own metal tape, preferring instead TDK's formulation. There's loyalty for you!



Above: oh how unfair! The TCK 55 II stripped naked before the world. PCB construction is to a commendably high standard.

TABLE ONE :- TEST RESULTS

Input sensitivity (line)	90 mV	
Wow and Flutter (DIN)	±0.08%	
Frequency response:-		
TDK SA tape	30 - 16 kHz ±2 dB	
SONY AHF tape	33 - 15 kHz ±3 dB	
SONY METAL tape	40 - 15 kHz ±4 dB	see text
TDK METAL tape	26 - 18 kHz ±2 dB	see text
MAXELL UDXL 1 tape	30 - 16 kHz ±3 dB	
MAXELL XDXL 2 tape	30 - 16 kHz ±2 dB	
Spooling time (C60)	1 min. 4 sec.	
Distortion (333 Hz):-		
METAL tape at Dolby level	0.9%	
SONY AHF at Dolby level	1.6%	
Dynamic Range (TDK METAL)	+67 dB	
S/N ratio, Dolby on, TDK METAL, (10 kHz)	-64 dB	

I don't propose to spend weeks mulling over those figures, just the interesting ones need to be mentioned. Firstly that W/F rating I didn't believe and so I did it again. OK so now I believe it. Just. It's pretty good!!!

I am surprised by the Sony metal tape results and would listen to claims that I had some bad tapes. TDK metal performed superbly at all times.

Using TDK metal really showed what a difference this tape is capable of making to a sound system. With care taken in the recording stages this £200 cassette deck produced results that were all but indistinguishable from the original disc. There remains none of the tell-tale compression, dullness or lack of life that would betray an average recording.

This is not the first metal deck I've listened to, but if one includes the price in the consideration, then it is certainly the most impressive. Even a year ago this standard of sound from a cassette at £200 would have been nonsense, an ad. man's dream.

Sound Out

I compared the TCK55 II to an EL7 Elcaset machine and a Revox B77 reel-to-reel and on sound alone it was difficult to tell them apart. The Revox was running at 7½ ips and undoubtedly turned in the most accurate reproduction of the three. It would, however, take a good pair of ears and very high quality source material to allow it to be reliably distinguished from the far cheaper TCK55 II. Even then only on a good day with the wind in the right direction....

I would very much like to lay hands and ears on the TCK75, a machine which a little bird tells me is better yet and more versatile, albeit at higher cost. However, there can be no doubt that the TCK55 II itself is an imposing statement of the quality reproducible from the (high price) medium of metal tapes. It performs exceedingly well on the more mundane formulations too and can be highly recommended to anyone in search of a tape machine to add to his domestic sound system.

Moaner's Return

Following my moan in the February issue about the non-availability of racks for Pioneer systems (unless you want to shell out a few hundred pounds for a complete system) I had a few interesting phone calls. It seems that Britain, for the time being, is the odd man out as far as Pioneer racks are concerned. I'm told that most European countries will supply Pioneer racks as separate items. However, if you have problems with the foreign lingo, why not go west, young man? If you should find yourself in the Republic of Ireland in the near future, make a bee-line for 41 Fitzwilliam Street in Dublin. There you'll find the emporium of Radio Import Ltd, who will be more than happy to flog you a brand new Pioneer rack on its own. Get in touch with them for latest prices, but as a guide the Rolls-Royce of the range - the CB 900 - will set you back a shade over £100. Sounds expensive, but a CB 900 from Pioneer on this side of the Irish sea will be around £90 when it finally becomes available - in about three months.

Ian Graham

Let Us Say

Below an epistle from a man of taste who is undeservedly threatened by his own brother due to an unsatiable craving to play bass guitar. There are problems, however. Read on....

25th February 1980
Dear Audiophile,

I have an electric guitar which I intend to 'play' through my brother's Hi-Fi system. However we have been told that to do so will damage the Hi-Fi.

Is this correct? If so what can I do about it? At present my brother brandishes a length of lead plumbing whenever I pick up my guitar - other people only do this when I touch the strings.

While on the subject, how about a project for a guitar practice amp - with a headphone output for the sake of neighbours' sanity?

Finally, we entirely agree with your opinions about Felicity Kendal. We strongly suggest that you attempt to have published the enclosed picture. This will help convert those unbelievers who may have been unconvinced by the previous photo - A commendable effort but not as fine a likeness as she deserves.

Yours faithfully,
I Rickwood.
Norwich

26th February 1980

Dear Sir,

Bass guitars and hi-fi don't mix. Sad, but true. Attempts to replay said stringed thing in this manner will probably result in one wall of your room being re-papered with a pair of speaker cones.

Good for the decor but lousy on the music. This is due to the amount of energy that the guitar will produce and the shape of the note. With no processing, i.e. recording, disc cutting etc. etc. (and no automatic level control!!!) you are more than liable to blow the bass speakers straight out of the cabinets.

As this is the point at which I suspect your kin will begin to rearrange your anatomy this is a Bad Thing. By all means use a pair of good dynamic headphones with the amplifier - this you will not damage. The headphones should survive better than your ears and are therefore safe!

I enclose a circuit for a practice amplifier we haven't got around to publishing, but which Hobby Electronics shortly will, - it might interest you more than that length of lead plumbing. Buy yourself a good 12" PA speaker to go with it.

As to a better picture of Felicity.....

ETI




"YOU HAVE BEEN WARNED"

and you will be if you install a

LONG RANGE SUPER SNOOPER

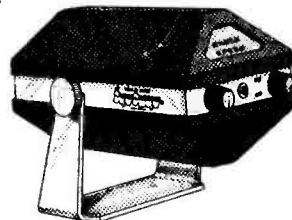Easily fitted—no difficult wiring—plugs into your cigarette lighter socket. Know what lies ahead with your LONG RANGE SUPER SNOOPER Radar Detector — simply the best there is. Recommended by 'Motor' Magazine 5 May, '79. £132.00 inc. VAT.



Send your cheque or use Access Card to have your Long Range sent by return.

Sole Importers

AUTEX INTERNATIONAL LTD.

1-3 Lancelot Road
Wembley, Middlesex HA0 2DG
01-903 1190



Name

Address

ET5

The Advertising Standards Authority have told us to advise purchasers that a licence is required for the use of this device. However, technically this unit is a radio receiver within the meaning of the Wireless Telegraphy Act 1970, Sec. 3. Should you inadvertently receive signals other than amateur transmission, the unit must be disconnected.

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safebloc

Minimum & Sub Miniature

Volts	Milli-amps	Ref. No.	Price £	P&P
3-0.3	200	238	2.55	.65
0.6, 0.6	1A 1A	212	2.95	.70
9-0.9	100	13	2.25	.65
0.9, 0.9	330 330	235	2.10	.65
0.8-9, 0.8-9	500 500	207	2.70	.70
0.8-9, 0.8-9	1A 1A	208	3.80	.70
0-15, 0-15	200 200	236	2.10	.65
0-20, 0-20	300 300	214	2.70	.85
20-12-0-12-20	700(DC)	221	3.45	.85
0-15-20, 0-15-20	1A 1A	206	4.55	1.00
0-15-27, 0-15-27	500 500	203	4.00	.85
0-15-27, 0-15-27	1A 1A	204	6.05	1.00

12 AND/OR 24 VOLT

12v	24v	Ref. No.	Price £	P&P
0.5	0.25	111	2.25	.70
1.0	0.5	213	2.70	.85
2	1	71	3.20	.85
4	2	18	4.00	.85
6	3	70	5.55	.90
8	4	108	7.40	1.15
10	5	72	8.20	1.15
12	6	116	8.80	1.15
16	8	17	10.80	1.25
20	10	115	13.80	1.45
30	15	187	16.80	1.45
60	30	226	33.30	1.75

30 VOLT (Pri: 220-240V)

Amps	Ref. No.	Price £	P&P
0.5	112	2.80	.85
1.0	79	3.55	.85
2.0	3	5.55	1.00
3.0	20	6.25	1.15
4.0	21	6.55	1.15
5.0	51	9.55	1.15
6.0	117	11.05	1.15
8.0	88	14.30	1.45
10.0	89	16.55	1.45

50 VOLT (Pri: 220-240V)

Amps	Ref. No.	Price £	P&P
0.5	102	3.55	.85
1.0	103	4.55	1.00
2.0	104	7.25	1.15
3.0	105	8.55	1.15
4.0	106	10.80	1.25
6.0	107	15.05	1.45
8.0	118	20.15	1.85
10.0	119	24.05	2.15

60 VOLT (Pri: 220-240V)

Amps	Ref. No.	Price £	P&P
0.5	124	3.80	.85
1.0	126	5.55	1.00
2.0	127	7.50	1.15
3.0	125	11.05	1.25
4.0	123	12.30	1.45
5.0	40	14.10	1.55
6.0	120	17.55	1.55

AUTO TRANSFORMERS

Input/Output Tapped 0-115-210-240V

VA (Watts)	Ref. No.	Price £	P&P
20	113	2.60	.85
75	64	4.05	.85
150	4	5.55	1.00

Input/Output Tapped

0-115-210-220-240V	Ref. No.	Price £	P&P
300	53	10.05	1.15
500	67	10.80	1.45
1000	84	18.55	1.55

Also 1500/2000/3000VA

MAINS ISOLATING (Centre Tapped & Screened)

Pri: 120/240V Sec: 120/240V

VA (Watts)	Ref. No.	Price £	P&P
60	149	8.55	1.00
100	150	7.55	1.25
200	151	11.08	1.25
250	152	13.25	1.45
350	153	16.25	1.55
1000	156	37.05	3.15

Please add VAT at 15%
Barclaycard and Access facilities
available
Trade and Education Welcome

BAYDIS

7a William Street
Herne Bay, Kent
Herne Bay G4586



SOUTHEAST ENGLAND'S ELECTRONICS CENTRE

OLIVETTI TE318

ONLY
£130
+ CARR
+ VAT

The cheapest way to I/O to your computer, 80 column high quality printer, friction feed, serial ASCII in and out, RS232, leather light keyboard, and inbuilt 8 bit paper tape punch and reader. Supplied in good condition with interface data and accessories but untested, unguaranteed. What more could you ask for.

1" Paper tape 75p per roll + pp 40p.
HURRY WHILE STOCKS LAST.

STOP PRESS! WORD PROCESSOR VDU TERMINALS

Just arrived a VDU with a green screen! As yet no time to obtain full details but we'll make a start. Made by the famous Ventek Co. They have the following spec: 12" monitor, 24 lines x 80 characters, upper and lower case with descenders, 85 plus keyboard, numeric keypad ASCII, RS232C serial interface, adjustable baud rate, full cursor control, edit function, character(s) flash function, etc, etc, latest technology used, mostly 74LS with plug in dynamic rams, supplied in 3 grades

Grade I complete tested and working £275.00 + VAT
Grade 2 complete less some keypads £250.00 + VAT
Grade 3 condition as seen or described £175.00 + VAT
Although grade 1 sold working no guarantee is offered. Carriage extra. New rams available 95p each. P.S. Anyone with circuits or manuals please contact us.

HY GRADE SMOOTHING CAPS
MULLARD - PLESSEY - MALLORY - SPRAGUE
1500mf 100v 60p* 3300mf 40v 50p
3300mf 63v 70p* 1mf 600v MYLAR 28p
10,000mf 15v £1+ 22,000mf 16v £1.10+
100mf 250v 45p 2100mf 200v £2.50+
*Ex equipment tested +P.P. 40p

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed. 50 + BAG £2.95 100 + BAGS £5.15

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex-equipment 'Muffin Fans' almost silent running and easily mounted. Available in two voltages 110 V.A.C. £5.95 + pp 65p OR 240v A.C. £6.15 + pp 65p. DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2".

ELECTRONIC COMPONENTS & EQUIPMENT
66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

7lb £ 5.25 + pp £1.25 14lb £ 7.95 + pp £1.80
28lb £13.75 + pp £2.25 56lb £22.00 + pp £4.75

ISOLATED 240V 4 AMP & 10 AMP SOLID STATE RELAYS

Interface your MPU etc. with the outside world made by the famous "Astralux" Co. They consist of a miniature plastic module with mounting holes containing a reed relay for isolation, choke and triac. 12-20 volts D.C. at a few millamps enable on/off control of A.C. loads up to 10 Amp! The 10 amp version should be mounted on a heatsink. 100's of uses including power control, lighting, etc, etc. Dimensions: 4 amp, 1 1/2" x 1" x 1/2", 10 amp, 1 1/2" x 1 1/2" x 1". 4 amp £1.45 10 amp £2.10 complete with circuit

DATA STORAGE MEDIUMS

RACAL C10 "Supergrade" cassettes complete with library cases 66p each 10 for £5.45
VERBATIM 5 1/4" soft sector mini disks £3.45 each 10 for £31.63

OPTO SMASH!

TIL 302/MAN 7 7 segment LED readout common anode direct drive (via resistors) from 7447 £1.10 each
TIL 119/OC72 Darlington opto isolator 3 for £1.00
TIL305 0.3" x 7 x 5 matrix LED alphanumeric readouts £3.75 each
PHOTO TRANSISTOR Fairchild FPT-100 NPN silicon 30v 25ma. 4 for £1.00

DISPLAY I.C. AND TRANSISTOR BARGAINS NEVER CHEAPER

All I.C.'s and Transistors by well known manufacturers and fully guaranteed. No fall outs. Comprehensive data on I.C.'s 15p per type.
2N4351 N channel MOS FET.
2N4352 P channel MOS FET.
60p each £1.00 per pair.
HIGH VOLTAGE NPN POWER SWITCHING transistors BVcbo 600v BVceo 500v BVbeo 15v 1c 5amps Pc 125 watts HFE 60 typ ft 2.5 mhz ideal invertors, etc. TO3 £1.60 each 4 for £5.40

BF258 NPN 250v @ 200ma 45p each 3 for £1.08
I.R. BSB012 5 amp 100v bridge rec P.C. mount long leads 35p each 4 for £1.08
IN4998 4 amp 100v P.C. mount diodes long leads 14p each 10 for £1.10
LM309K + 5v 1.2 amp regulator £1.10 each 6 for £5.35
2N1671B unijunction 450mw 30v 48p each 3 for £1.00
IN4004 SD4 1 amp 400v diodes 7p each 18 for £1.00
I.R. 12 amp BRIDGE RECS. 400 volt £1.25 each

POWER DARLINGTON SCOOP!
MJ1000 NPN 60v 90w 8 amps TO3 95p each
2N6385 NPN 80v 100w 10 amps TO3 £1.25 each
MJ4330 NPN 60v 150w 16amps TO3 £2.25 each

PLESSEY EDGE STACKABLE DECADE THUMBWHEEL SWITCHES. Gold plated contacts dimensions 2" x 2" x 1/8" 85p each 8 for £5.35.

Miniature Continental Series 12VDC 4c/o plug in relays £1.30 each.

Greenpar 50Ω BNC Chass. socket single hole fixing 65p

C90 Audio Cassettes screw type construction 45p each 3 for £1.00.

Bulbs 24v 14 watt white frosted S.B.C. 8 for £1.00.

Bulbs 12v 100 watt clear, base similar S.B.C. 45p each.

S.B.C. Bulb Holders All steel cad. plated panel mount easily fixed via nut and round hole, ideal disco displays, scoreboards, etc. 4 for £1.10.

VMOS VMP1 Siliconix TO3 power FET 0-60v, DC-200 mhz will drive direct from CMOS etc. £1.50 each, full date 30p.

Heavy Duty Flat Insulated Earth Braid 100-200 amp braided tinned copper in heavy clear PVC sheath 50p per metre. £6 for 15 metres + PPE 1p per 15 metres.

BULGIN miniature 6 way male chassis mount socket and matching free plug 60p each, 2 for £1.10.

Red L.E.D.'s full spec. 0.2" 14p each, 10 for £1.25.

Red L.E.D.'s 0.125" 10p each 10 for 80p.

Dynamic Stick Mics 600Ω with built in on/off switch complete with lead and min. jack plug £1.15 each, 10 for £10.00.

T05 HEATSINKS "Thermalox" black anodised press on aluminium finned type 18p each, 8 for £1.00.

HARDWARE PACK Don't be stuck for the right nut and bolt for the job. Pack contains B.A. Metric, Unified, Self Tap, etc. Nuts, Bolts, Screws, Washers, etc. in Brass Bronze and Steel. All steel items plated. Average contents 400-600 pieces.

MANY HUNDREDS OF TRANSFORMERS IN STOCK - SEND SAE FOR LIST

ONE OFF SPECIALS

"Hewlett Packard" HP67 pro. calc. £150.00 + VAT
3KW 240v 50Hz to 3KW 120V 60Hz converter £375.00 + VAT
"Wordplex" 8 user word processor system, CPU, dual 8 floppy's etc £950.00 + VAT

BARGAINS GALORE!

In our walk round Warehouse
NOW open Monday to Saturday 9.30-5.30

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

SUPER 77 KEY KEYBOARD KIT

We've done it again! We've purchased a large quantity of C.P. Clare top quality keyboard! Read switches + full QWERTY Keytop sets and thrown in a PCB to enable you to customise the keys just as YOU want, just add and wire an encoder chip and you can arrange ASCII, BAUDOT, anything to a quality keyboard which would normally cost around £100.00! Supplied with layout and assembly info. at only £26.99 + pp £1.50.

HOW TO GET HERE

Victoria, London
Bridge or Holborn
Viaduct to
Thornton Heath.
1 minute from
Thornton Heath
Station.

SCOOP OF THE YEAR HAZELTINE H1200 V.D.U. TERMINAL

Due to a fantastic bulk purchase, we are now able to offer this superb terminal at a price almost below the cost of manufacture! Features include: 12" screen, 55 key TTY keyboard, full ASCII, RS232 interface, adjustable baud rate 75 to 9600, 12 lines x 80 characters (upgradable to 24 x 80), cursor control, lower case option, plus many other features.

Brand new at only
£250 CARR.
+ VAT.

FULL Technical Manual available

POWER SUPPLY UNITS

5 VOLT 2.5 AMP T.T.L. P.S.U.
Made for T.T.L. this compact ex computer systems unit features a 10 amp transformer with D.C. outputs of 5 volts @ 2.5 amps and 7.5 volts @ 5 amps. The 5 volt output is fully regulated and smoothed and has electronic current limiting. May be easily modified for 5 volts @ 7.8 amps, believed working but untested. 240v A.C. input. Complete with circuit.

£8.25 P.P. £1.60

KEYBOARD

A special bulk purchase enables us to offer the above keyboard at a lowest ever price. 49 coded keys encoded into a direct TTL compatible 7 bit output. Features such as delayed strobe, 5 volt D.C. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector, at a secondhand

"no time to test" price of only
£20.00 + P.P. £1.60
SUPER CASED VERSION Same as above spec. but housed in attractive two tone moulded, free standing case. Unit also includes an all TTL parallel to serial converter (no details) etc.

£27.50 + P.P. £1.85

TOROIDAL TRANSFORMERS

HP 240v pri. sec. 2 x 30v @ 4 amps 2 x 18v @ 1 amp £11.00 + p.p. £1.95 dimensions 4 1/2" x 2 1/2"
PR 240v pri. sec. 15 0 15 @ 2 amps dimensions 3" x 2 1/2" £4.95 + p.p. 99p
TM 240v/110v pri. sec. 15 0 15 8vA dimensions 2 1/2" x 1" £1.95 + p.p. 30p
All voltages measured off load.

HIGH EFFICIENCY SMITHS RADIAL BLOWERS

Are your hot parts sweltering? Then keep them cool with our high efficiency radial snail type blowers. Made by Smiths, designed for continuous use in expensive electronic equipment very powerful and quiet, gives massive air flow to prolong component life and reliability. Easily mounted, air aperture 2 1/2" x 3". Ideal linear etc. Please state 240v or 110v operation. 50Hz only.

BRAND NEW
£4.55 P.P. £1.60

ELECTRONICS

Dept. E.T.I. 64-66 Melfort Rd., Thornton Heath, Surrey. Telephone: 01-689 7702

MAIL ORDER INFORMATION

Unless otherwise stated all prices inclusive of VAT. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 40p per order. Bona Fide account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.

SPEC FR

Based on ideas from
ETI's Tech Tip
pages, with the
addition of data
tables and a
comprehensive
index ETI Circuits
No.1 is essentially
an ideas directory.
A surfeit of circuits
for £1.50.

ETI
CIRCUITS
No.1

Electronics
— It's Easy

Electronics really
can be easy with the
aid of this exercise
in electronics
education.
Previously three
separate
publications, we've
brought it all
together, in one
volume for £3.60.

Electronic Circuit
Design

£1.25

This is the first of a series of three
volumes of the best features from ETI
dealing with electronic circuit design.
Volumes 1 and 2 are now available at
£1.25 each. Watch this space for news of
Vol.3.

The popular 'Into Electronics' series
from Hobby Electronics plus other
introductory articles to the field of
electronics, from making your own PCBs
to making sense of computing jargon.
£1.00.

MODM

The Top Projects series continues. Prices of
those not shown are TP3, 4, 5 and 6 — £1
each; TP7 — £1.25. ETI Circuits now has a
No.2, also £1.50.

Please add 30p postage and packing per
magazine, except for Electronics Its Easy for
which we need an extra 80p.

Please make cheques & POs payable to
Modmags Ltd.

SPECIALS FROM



MODMAGS LTD

All Modmags Specials may be ordered from

Modmags Ltd, Sales Office (Ref: Specials)
145 Charing Cross Road,
London WC2H 0EE.

electronics
today international

**TOP
PROJECTS
1+2**

The first two volumes of the Top Projects series sold out many moons ago, but due to continuing demand, we have brought them together and reprinted them as one volume. Top Projects 1+2. £2.50.



Electronics Tomorrow takes a look at the trends and developments of one year and examines their implications for the future, including project for beginner and seasoned project builder alike. Only 75p.



Transducers in Measurement and Control is a broad summary of common transducers vital to our technological age, from general principles to practical applications. £3.00.

ETI TOP PROJECTS
No 4
electronics today international

Full Amp Bk. P.W. Car Alarm
Push Button Dialing
Audio Multimeter
Digital Tracking P.S.U.
Photo Timer
Emergency Beacon
Logic Probe
Light Extender
Car Arm Bandit
Car Flasher
Headlight Reminder
Temperature
Switch Supply
Thermocouple
Power Meter
Ceramic Cartridge
Controlling

ETI Top Projects No 4 gives you details of nearly thirty of the most popular projects from the pages of ETI. Whether you're into audio, motoring or photography there's something in TP4 for you. £1.00.


SERVO TESTER

So your radio control has lost control and you have no way of knowing whether the offending component is receiver or servo. Fear not. All is not lost yet, ETI's Project Team provide the answer.

So your model is not functioning correctly and you're not sure of the cause of the trouble. Is it the transmitter, the receiver, or the servo? If your servo is a modern 3-wire positive-pulse type (aren't they all?) you can rapidly eliminate it from your list by simply coupling it up to our servo tester. The tester is powered from the servo's supply battery and feeds standard fully-variable 1 mS to 2 mS 'decoder' output pulses to the servo input for test purposes. The test set also features a pulse 'trim' control and incorporates variable frame length (1 mS to 28 mS) and pulse-amplitude controls, for the benefit of those enthusiasts who like to really put a servo through its paces.

The entire test set is built up on a single PCB and can be powered from all servo supplies in the 3 to 12 volts range. As you can see from the photos, we've not bothered to box the unit, since its probable utilisation rate does not justify the additional expense involved.

Not much to say here. Everything is built up on a single PCB, so construction couldn't be easier. The two ICs are CMOS versions of the 555 timer (essential for low voltage operation) and should be mounted in suitable sockets. On our prototype we've made the five output connections available via Veropins, but in practice we advise you to make the servo connections (and possibly also the servo battery connections) via a socket that is compatible with your existing R/C system.

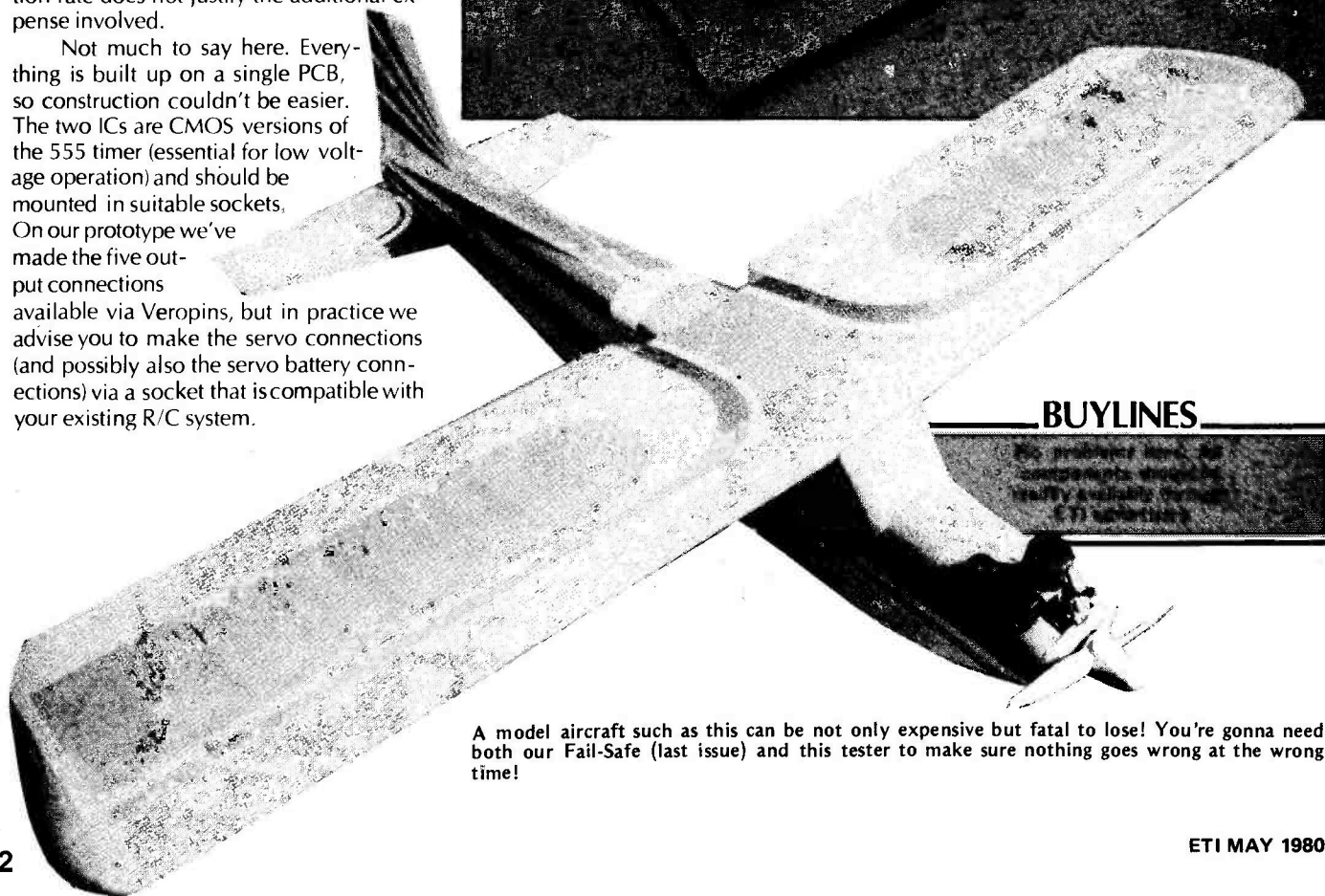

BUYLINES

No problem here, all components should be readily available through ETI's suppliers.


A model aircraft such as this can be not only expensive but fatal to lose! You're gonna need both our Fail-Safe (last issue) and this tester to make sure nothing goes wrong at the wrong time!

HOW IT WORKS

is a conventional multi-channel 'proportional' radio control system a variable-width (1 mS to 2 mS) pulse is passed to each servo via the transmitter - receiver - decoder link roughly once every 20 mS (the frame time). The pulse width of each channel is variable at the transmitter (via a joystick, etc.) and determines the position of the servo. At 1 mS the servo may, for example, be full left, at 1.5 mS 'neutral' and at 2 mS full right.

Our servo test set works by internally generating a conventional positive control pulse at a normal frame rate and feeding the pulse directly to the servo input. The unit is powered from the servo's own battery supply via the D1-C1 decoupler network. Circuit operation is quite simple. IC1 is wired as a free running astable multivibrator and acts as the 'frame' generator. The frame length is variable from 13 mS to 28 mS via RV1 and is used to trigger pulse-generating monostable IC2 via C3. The output pulses of IC2 are fed to the servo input via amplitude control RV2. The output pulse widths are variable over the nominal range 1 mS to 2 mS via RV3 but can be 'trimmed' over a limited range via RV4.

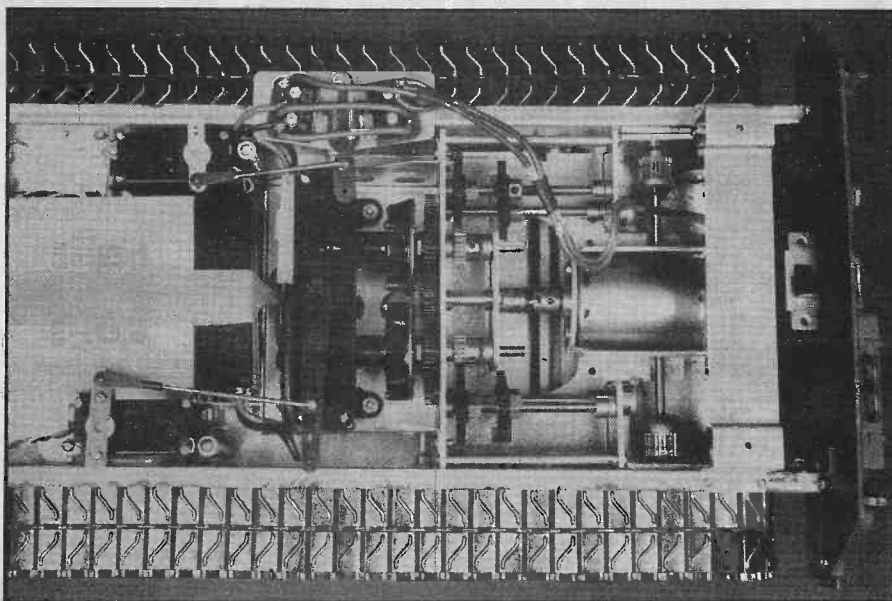IC1 and IC2 are CMOS versions of the 555 timer and give stable operation at supply potentials down to about 3 volts.



Above: the Servo layout on the ETI Leopard Tank used for our R/C project last year. Servo failure here could result in total destruction of a very expensive model - and whoever happened to be in the way when those metal tracks cease to obey commands!

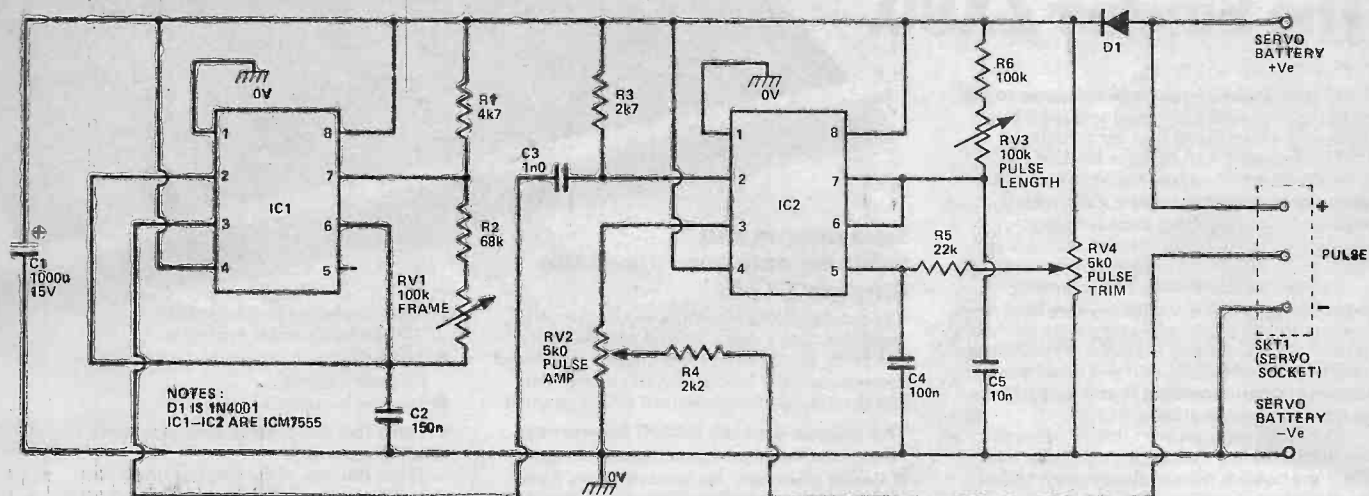


Fig.1. Full circuit diagram for the Servo Tester.

PARTS LIST

RESISTORS All 1/4W, 5%

R1	4k7
R2	68k
R3	2k7
R4	2k2
R5	22k
R6	100k

POTENTIOMETERS

RV1,3	100k min horiz preset
RV2,4	4k7 or 5k0 min horiz preset

CAPACITORS

C1	1000u 25V electrolytic
C2	150n polycarbonate
C3	1n0 polycarbonate
C4	100n polycarbonate
C5	10n polycarbonate

SEMICONDUCTORS

IC1,2	ICM7555
D1	1N4001

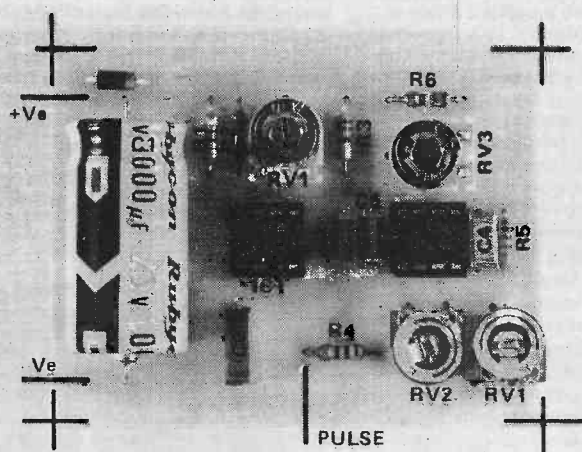


Fig.2. (left) the component overlay for the unit.

Britain's first comp

A complete personal computer for a third of the price of a bare board.

Also available ready assembled for £99⁹⁵

The Sinclair ZX80.

Until now, building your own computer could easily cost around £300 – and still leave you with only a bare board for your trouble.

The Sinclair ZX80 changes all that. For just £79.95 you get *everything* you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to your own cassette recorder and black and white or colour television; everything!

And yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers on the market at several times the price. The ZX80 is programmed in BASIC, and you could use it to do quite literally anything from playing chess to running a power station.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. Once assembled, it immediately proves what a good job you've done. Connect it to your TV set... link it to an appropriate power source*... and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs – all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be **SAVED** and **LOAD**ed on to any portable cassette recorder.
- **FREE** course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately – see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. Extra RAM chips also available – see coupon.

* Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

Two unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter... offers remarkable programming advantages:


- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability – takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.

- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

... and the Sinclair teach-yourself BASIC manual.

If the features of the Sinclair interpreter listed alongside mean little to you – don't worry. They're all explained in the specially-written 128-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.)

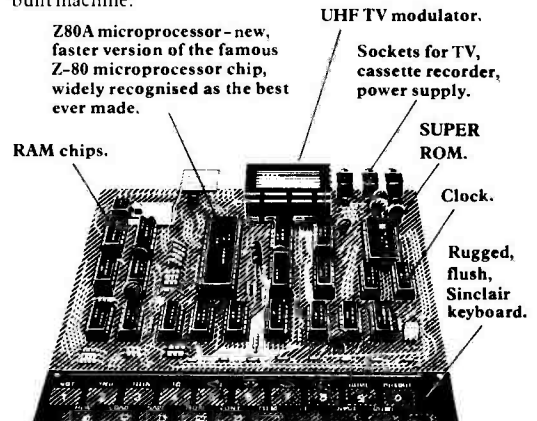A hardware manual is also included with every kit or built machine.



ETI MAY 1980

Complete computer kit.

£79⁹⁵

**Including VAT.
Including post and
packing.
Including all leads
and components**

**Fewer chips,
compact design,
volume production –
more power per pound!**

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer – typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines.

And Benchmark tests show that the ZX80 is faster than all other personal computers.

No other personal computer offers this unique combination of high capability and low price.

**The Sinclair ZX80. Kit: £79.95.
Assembled: £99.95. Complete!**

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Whether you choose the kit or the ready-made, you can be sure of world-famous Sinclair technology – and years of satisfying use. (Science of Cambridge Ltd is one of the Sinclair companies owned and run by Clive Sinclair.)

To order, complete the coupon, and post to Science of Cambridge for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied.

**Sinclair
ZX80**

Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ETI MAY 1980

Order Form

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.

Please send me:

Quantity	Item	Item price	Total
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	
	TOTAL		£

NB. Your Sinclair ZX80 may qualify as a business expense.

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £

Please print

Name: Mr/Mrs/Miss

Address

(ETI/4/80)

Simply ahead..

I.L.P.'s PROVEN RANGE OF HIGH

Chosen in more countries throughout the world than any other U.K. make

I.L.P. constructional modules are different. Whereas most others come with components neatly arranged on open P.C.B.s with little else, I.L.P. modules are encapsulated within totally adequate heatsinks and need no extra components to complete them. As a result, I.L.P. power amplifiers, pre-amp and matching power supply units are infinitely more rugged, impervious to working in extremes of temperature and can be easily positioned to requirement. No additional metal work is needed to take away heat, connections are minimal and utterly simple. Circuitry, workmanship and performance are of the highest standards, equal to the demands of loudspeakers, pick-ups, tuners, digital signals, etc., even more exacting than those of today, making amplifier systems less than the best completely inadequate. Now study the tested and guaranteed specs. for I.L.P. That is why more people in more countries prefer these British designed and made modules.

- FIVE POWER AMPLIFIERS EACH ENCAPSULATED WITHIN LARGE HEATSINK.
- PRE-AMP/ACTIVE TONE CONTROL MODULE COMPATIBLE WITH ALL I.L.P. AMPS AND POWER SUPPLIES.
- SEVEN MATCHING POWER SUPPLY UNITS (FOUR WITH TOROIDAL TRANSFORMERS).
- EASY ASSEMBLY DESIGNS WITH WELL PRESENTED INSTRUCTIONS.

Why toroidal?

Toroidally wound transformers are more compact than their conventionally laminated equivalents, being only half as high and heavy. Their circular profile ensures greater operating efficiency and as such are particularly valuable in heavy duty applications. We have our own production section for winding and making toroidal transformers enabling us to offer this much sought-after type at competitive prices. Four of the larger models in our range of power supply units are now supplied with this type.



**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS

and staying there

PERFORMANCE MODULAR UNITS

HY5 PRE-AMPLIFIER

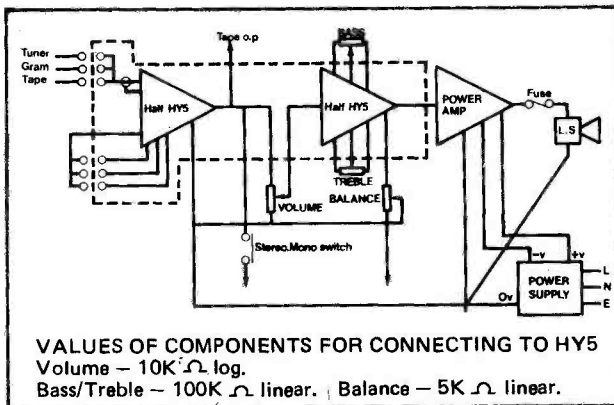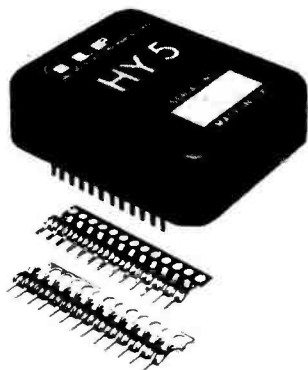


VALUES OF COMPONENTS FOR CONNECTING TO HY5
Volume — 10K Ω log.
Bass/Treble — 100K Ω linear. Balance — 5K Ω linear.

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz—0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

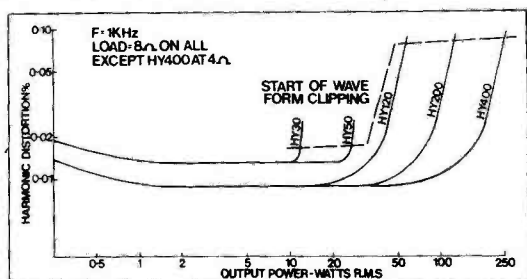

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/ Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance — all models 4 - 16 Ω
Input sensitivity — all models 500 mV
Input impedance — all models 100K Ω
Frequency response — all models 10Hz - 45KHz - 3dB

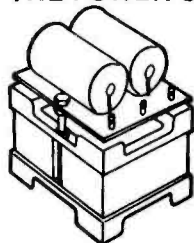THE POWER SUPPLY UNITS (Laminated and Toroidal)



I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	±15V at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

NO QUIBBLE
5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
INTEGRAL HEATSINKS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE
—see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope — we pay postage on all letters sent to us by readers of this journal.



ELECTRONICS LTD.

FREEPOST 6, Graham Bell House, Roper Close
Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 Telex 965780

Please supply Total purchase price £.

I enclose Cheque ☐ Postal Orders ☐ International Money Order ☐

Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature



Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS - CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD - DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMAN - HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS - KEF - LOWTHER - MCKENZIE - MISSION - MONITOR AUDIO - MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS - RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNOY - VIDEOTONE - WHARFEDALE.

WILMSLOW AUDIO

**SWAN WORKS, BANK SQUARE
WILMSLOW, CHESHIRE SK9 1HF**

**Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF
DRIVE UNITS, KITS, ETC.**

**Tel. 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI
AND COMPLETE SPEAKERS.**

Happy Memories

4116 200ns	£4.50	4116 150ns	£5.50
2114 200ns	£3.95	2114 450ns	£3.45
2708 450ns	£4.95	2716 5 volt	£16.95
21L02 450ns	85p	21L02 250ns	£1.25

VERBATIM mini discs soft sectored—with FREE library case **£19.95** per ten.

SALE

We're moving shortly to new premises and don't want to carry much.

Bargains from Saturday, 26th April

All prices include VAT. 30p postage on orders below £10.

Access & Barclaycard

All orders to:

**Dept. ETI
19 Bevois Valley Road
Southampton, Hants, SO2 0JP
Telephone (0703) 39267**

PORTABLE PRECISION


A RANGE OF 3½ DIGIT LCD MULTIMETERS OFFERING HIGH PRECISION AND EXTENDED BATTERY LIFE. ALL TYPES FEATURE FIVE FUNCTION OPERATION (AC AND DC VOLTS, AC AND DC CURRENT, RESISTANCE) WITH ABILITY TO CHECK DIODES. 0.5" LCD DISPLAY WITH 'BATTERY LOW' WARNING. AUTO-POLARITY, AUTO-ZERO. FULL PROTECTION AGAINST TRANSIENTS AND OVERLOADS WITH ABILITY TO WITHSTAND MAINS ON ANY RANGE. RUGGED ABS CASES AND A COMPREHENSIVE 1-YEAR WARRANTY.

The LMM-200 is a compact handheld multimeter with 0.5% basic accuracy and 15 different ranges. It measures AC/DC voltage from 0.1mV to 500V, AC/DC current from 0.1µA to 2 Amps and resistance from 0.1Ω to 2MΩ. 200 hour battery life.

The LMM-2001 is an identical instrument but with a 0.1% basic accuracy.

The LMM-100 is suitable for field or bench use. It has a basic accuracy of 0.1% and 25 different ranges. It measures AC/DC voltage from 0.1mV to 1KV, AC/DC current from 0.1µA to 2 Amps and resistance from 0.1Ω to 20MΩ. Battery life is over 2,000 hours. It also features a unique 'digital hold' facility and adjustable carrying handle.

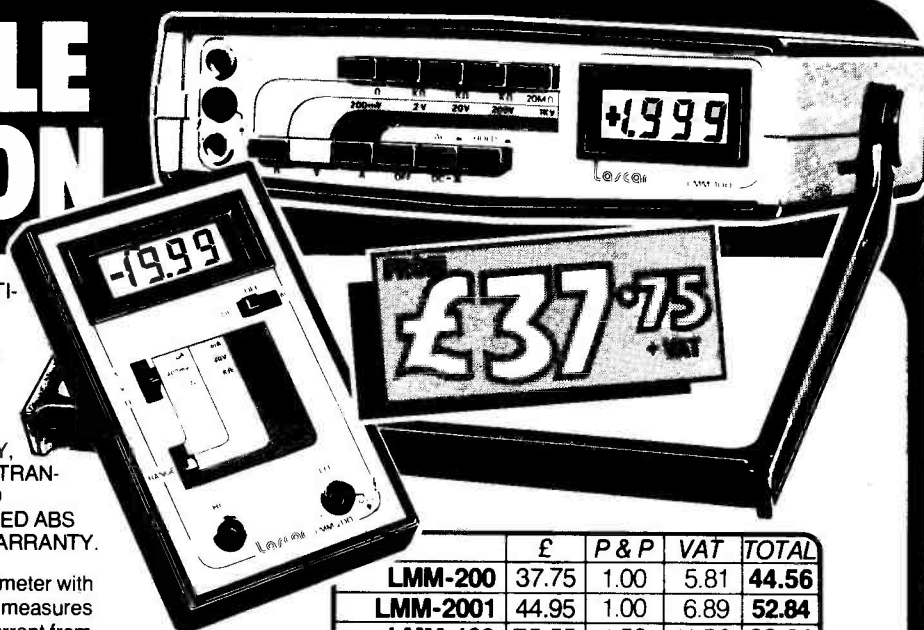Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex.
Telephone No: Basildon (0268) 727383.



	£	P & P	VAT	TOTAL
LMM-200	37.75	1.00	5.81	44.56
LMM-2001	44.95	1.00	6.89	52.84
LMM-100	75.55	1.50	11.56	88.61
TEST LEADS	1.95	0.25	0.33	2.53

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data ☐

LMM-100 £88.61 ☐ LMM-200 £44.56 ☐ LMM-2001 £52.84 ☐ TEST LEADS £2.53 ☐

Name _____

Address _____

Tel. No. _____

I enclose cheque/P.O. value _____

KIT SURVEY

You have, no doubt, heard

of the much-quoted phrase, first uttered by French philosopher Rene Descartes — I pay income tax, therefore I am. If you want to stop your wallet slimming faster than you feed it, one way of curtailing the financial anorexia is to buy the kit version of your favourite amplifier, electronic ignition, computer, etc. The range of kits available seems to be endless. We decided to get as many of them as possible together in one place to find out what you get for your money.

I invited about 40 companies to send me kits for our survey. All accepted my invitation, but only 20 or so came up with the goods in time. Some were awaiting delivery of components (main transformers, displays, etc.) and were unwilling to send part kits. Others seemed reluctant to take advantage of some free publicity.

You'll notice that there are few kits in the audio or hi-fi market. In the earliest stage of preparation of the survey it was decided to exclude any kit built from modules. This automatically excluded some of the household names in high quality amplifier design. It would also have been impractical to include loudspeaker kits, each requiring a cabinet. This pruning of the available merchandise was necessary to cut down the size of the survey to something manageable.

I built as many of the kits as time permitted and made a

brief evaluation of each. A key to the points system used is shown. The ETI INDEX at the end of each kit review is intended only as a very rough guide. The rating was based entirely on the kit used for the survey.

The standard of kits supplied was generally very high. Six rules of construction reared their heads up out of the piles of components on and around my desk.

1. Before you unpack the components, read the instruction manual through at least once and look out for warnings about component handling. Some kits contain fragile displays and/or static sensitive CMOS ICs. If you find a note of errata, write the corrections in at the appropriate places.
2. Check that the kit is complete. Work your way down the component list and tick off each component as you check it.
3. Have a look at the PCB. Make sure there are no solder bridges between tracks.
4. Make sure you have the right tools for the job. If you try to build a microcomputer board with a hot poker or an oxyacetylene torch, you're likely to come to grief. For the fine work I invested in a low voltage (6 volts at 1 amp) iron with a fine tip and used 22 swg solder. (A temperature-controlled soldering station is even better). You'll also need long-nosed pliers, sidecutters, a couple of small screwdrivers (one slot and one Philips) and a pair of wire strippers.
5. When you begin construction, follow the instructions in the correct order. It's sometimes tempting to leave a particularly difficult or tedious part of the kit and work on something a little more interesting.
6. Don't be too eager to plug in the finished kit and try it before you've checked it properly for mistakes. Look for blobs of solder bridging across PCB tracks. Check that diodes, electrolytic capacitors, transistors and ICs have all been put in the right way round. Where possible use IC sockets. It's not only extremely difficult to unsolder an IC from a board but; if you're using a double-sided board, you can irreparably damage the board.

ACORN COMPUTERS

Company	Acorn Computers Ltd, 4A Market Hill, Cambridge.		
Kit	Acorn Microcomputer		
Price	£70.20		
Complexity	C	Instruction Manual	2
Circuit Diagram	1	Finish	3
Contents	0	Fault-Finding Guide	0

This was the first microcomputer kit that I tackled and I learnt a lot from it — mainly from my mistakes. First of all, *do* check that all the components are there.

Companies do make mistakes. Acorn sent an incomplete keyboard assembly. One phone call later and the missing bits were on my desk next day — good service and worth a couple of bonus points on the ETI Index.

As with the majority of these kits, component positions, but not values, are marked on the PCB, so a good, clear components list is essential. I turned from the construction part of the manual to the end to find the components list. This list should, I feel, be included within the construction section. The layout of Acorn's manual encourages the constructor to use the sections out of order — potentially disastrous. So, the second of the cardinal rules 'read

the instruction manual *before* you even unpack the kit'. Unlike Microtan 65, Acorn does not display its wares on a television set. It uses a small seven segment display. While building the kit I had nightmares about the eyestrain I was bound to suffer trying to read this tiny display. Wrong again. In fact, angled properly, the display is perfectly adequate. Acorn's manual gives full details of power supply requirements. An attractive 'User's Manual' introduces the machine and how it works, with details of the 6502 microprocessor, including application programs.

ETI INDEX 8C

ALTEK

Company	Altek, 1 Green Lane, Walton-On-Thames, Surrey.		
Kit	Shadow VLF/TR discriminating metal locator		
Price	£79.70		
Complexity	B		
Circuit Diagram	1		
Contents	3		
Instruction Manual	3		
Finish	3		
Fault-Finding Guide	0		

ETI featured this most discriminating of metal locators in the March 1980 issue. The project was an instant success, the demand far surpassing even Altek's own expectations.


The kit includes all the necessary hardware — a case for the electronics, handle, adjustable shaft and search head. I've had a number of phone calls and letters from DIYers who want to make their own search head to save some money. Altek are reluctant to release full details of the coil assembly, understandably. They have also told me that even if full details were published, the coil assembly would be beyond the capabilities of most home constructors, requiring sophisticated test gear to set it up properly.

The kit assembly instructions assume some electronics experience, but if you do run into problems, Altek are just a phone call away. Construction doesn't pose any particular problems. The plastic case supplied is not drilled, so a bit of elbow grease is called for. Altek make things as easy as possible by marking the hole centres on the case and providing a paper drilling template. Before you start ventilating your case, notice

that the PCB mounting bosses are closer together at one end of the case than the other, so the case has a front and a back.

Before you rush out and dig up your back garden, remember that use of a metal locator requires a licence. Altek's kit includes an application form. You can buy the shadow VLF/TR Quad Mode Discriminator (to give it its full title) manual from Altek for £1. If you're starting out in metal locating and find the VLF/TR kit a little on the pricey side or you'd like to cut your teeth on something a little less complex, there are metal locators in Altek's range to suit just about everyone's needs and pocket.

ETI INDEX 10B

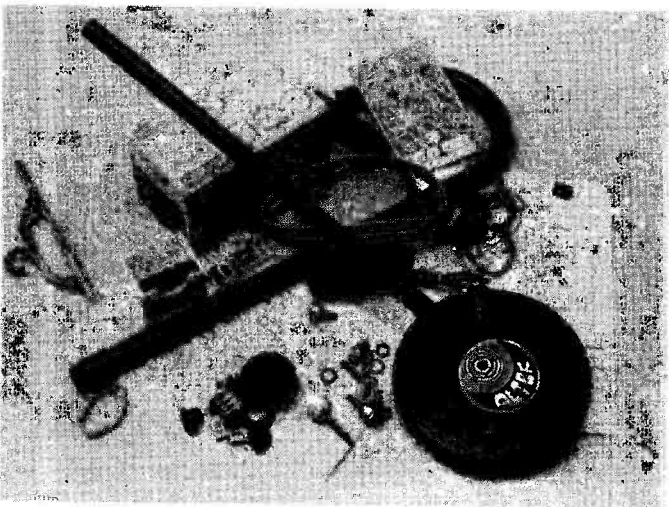

CATRONICS

Company	Catronics Ltd, Communications House, 20 Wallington Square, Wallington, Surrey SM6 8RG.		
Kit	40 W 2 m Power Amplifier		
Price	£22		
Complexity	B		
Circuit Diagram	1	Finish	1
Contents	3	Fault-Finding Guide	0
Instruction Manual	2		

When you unpack your 2 m Power Amplifier kit, hold the PCB up to the light and find that there are no component mounting holes, don't write a nasty letter to Catronics demanding a drilled PCB. The components are mounted on the foil side of the board. Before you pick up your soldering iron, read the instruction leaflet. Two points are worthy of note. If the power transistor is cracked, chipped or broken, run for the hills. The transistor contains beryllia, a toxic compound, so read the warning carefully. Secondly, before you begin, note that the heatsink and case should be taped together, so

that you can drill the mounting holes. Input and output holes also have to be drilled in the blank case. Thereafter construction is no problem. The component overlay is a little difficult to follow, but the inclusion of a photo of the PCB is very helpful.

Catronics, the VHF communications specialists, also supply a complete kit for the ETI VHF Airband Converter (Dec1979). ETI INDEX 7B


CHROMASONIC ELECTRONICS

Company	Chromasonic Electronics, 56 Fortis Green Road, Muswell Hill, London N10 3HN.		
Kit	75-X 10 Watt Audio Amplifier		
Price	£3.95 + VAT		
Complexity	A	Instruction Manual	2
Circuit Diagram	1	Finish	0
Contents	3	Fault-Finding Guide	0


Chromasonic sent me a sample of their 75-X 10 watt audio amplifier. They also have a 7 watt version — the 75-B — based on the TBA10AS IC. The heart of the 75-X is a TCA940. The first step of construction is to snip off three unwanted pins of the IC. Take a few seconds to identify the right pins. You'll feel very silly if you cut the wrong ones. Thereafter construction is very straightforward.

Neither a power supply nor a loudspeaker are included in the kit. However, circuit diagrams are provided for the amplifier itself, a suitable power supply and tone control network.

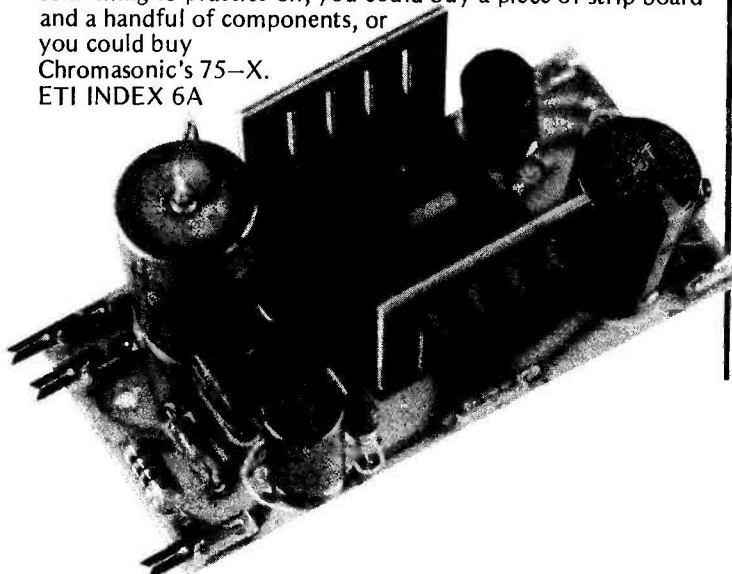If you've never soldered a joint in your life and you want something to practice on, you could buy a piece of strip board and a handful of components, or you could buy Chromasonic's 75-X. ETI INDEX 6A



CLEF PRODUCTS

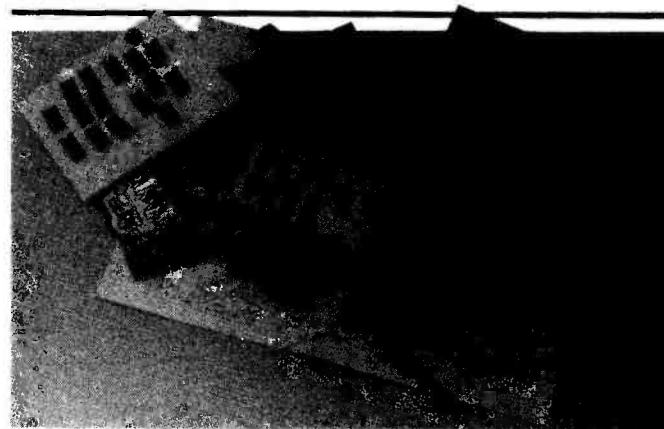

Company	Clef Products (Electronics) Ltd, 16 Mayfield Road, Bramhall, Cheshire SK7 1JU.		
Kit	Electronic Rotor CPK 1200.		
Price	£89.00		
Complexity	C	Instruction Manual	2
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	0

When I considered including electronic organs, pianos, etc in the kit survey I had nightmares about crates of woodwork and keyboard assemblies walling me in behind my desk. So, I asked Clef Products if they could simply send me a sample PCB and component packs.

They sent an electronic rotor — a device designed to electronically simulate a two speed mechanical rotor — speaker system and also provide a three-phase chorus generator to enhance organ tones and produce a string chorus effect. For your £89 you get a large bag bulging with boards and components. An 8" x 5" PCB contains the full rotor — chorus

All these only
from HENRY'S



IN STOCK
WITH FREE
POWER SUPPLY

NASCOM-2 + FREE 16K RAM

Here's an offer you can't refuse:

Because of the lack of availability of MK 4118 RAMs, Nascom Microcomputers is supplying its Nascom 2 without the 8 spare 4118s but with a FREE 16K dynamic RAM board.

NASCOM-2
with
32K RAM
£345 VAT
P&P 1.50

When the 4118s become available, Nascom 2 purchasers can have them at the special price of £80 + VAT for the 8K. So, for £295 plus VAT this is what you get:

MEMORY

- 16K RAM board (expandable to 32K).
- 8K Microsoft BASIC.
- 2K NAS-SYS 1 monitor.
- 1K Video RAM.
- 1K Workspace/Scratchpad RAM.
- Main board sockets for the 8x4118s or 2708 EPROMs.

**Buy
British
It's
Best!!**

No more slaving over a hot soldering iron - the Nascom 1 is now supplied BUILT!
Britain's biggest small system is available fully constructed for you to slot into your own housing for the ridiculously low price of £175 plus VAT (kit price still only £165 plus VAT). **EX-STOCK**

nascom-1
12" x 8" PCB carrying 5LSI MOS MOS memory packages. There is on-board unmodulated RAM. The...
Less P10 £125

With NAS-SYS
SCOOP KIT NOW ONLY
FULLY GUARANTEED
Standard Z80 which executing 158 instructions including all 8080 code.

NASCOM IMP
£325 VAT
P&P £2.50

MEMORIES		
+ VAT	£ p	
3880 (Z80)	7.50	
3880 N4 (Z80A)	7.95	
2102-L	1.00	
2114	3.95	
4027	2.50	
4116	7.50	
4118	12.75	
2708	7.50	
2716	19.95	
6402	4.50	
8080(A)	5.25	
QUANTITY	4 Less	10%
ANY ONE	8 Less	15%
TYPE	16 Less	20%

MICROPROCESSOR

- Z80A which will run at 4MHz but is selectable between 1/2/4 MHz.

HARDWARE

- Industrial standard 12" x 8" PCB, through hole plated, masked and screen printed. All bus lines are fully buffered on-board.

INTERFACES

- Licon 57 key solid state keyboard.
- Monitor/domestic TV interface.
- Kansas City cassette interface (300/1200 baud) or RS232/20mA teletype interface.

The Nascom 2 kit is supplied complete with construction article and extensive software manual for the monitor and BASIC.

EXPANSION NASCOM-1

- *Expansion buffer board **£32.50**
- MEMORY KITS (inclusive all hardware)
 - 8K **£85**
 - 16K **£140**
 - 32K **£200**
- *I/O board with decoders and all hardware except ICS will accept up to 3 PIOs, 1 CTV and 1 UART **£35**
- NEW, T.4 operating system in (2) 2708 EPROMS UPWARDS **£25.00**
- COMPATIBLE FROM T2 and B-BUG **£25.00**

NAS SYS 1. MONITOR **£25.00**

Programming Manual	£4.50
*Power supply for up to 32K expansion Mk II	£24.50
*8A power supply for larger than 32K expansion	£60.00
*Expansion card frame	£29.50
EPROM programmer	£13.95
SMART-1	£74.95
Tiny Basic	£25.00
Super Tiny Basic (with editor and machine utility routines)	£35.00
Zeap assembler editor	£32.00
8K BASIC ROM	£48.00
Naspen Text Handler	£36.00
Disassembler	£9.95

NASCOM IMP PLAIN PAPER PRINTER


Fully built and housed in a stylish enclosure for just £325 plus 15% VAT. Interfaces with all micro computers. Deliveries Ex-Stock.

- Optional tractor feed.
- Baud rate from 110 to 9600
- External signal for optional synchronisation of baud

The Nascom IMP (Impact Matrix Printer) features are:

- 60 lines per minute.
- 80 characters per line.
- Bi-directional printing.
- 10 line print buffer.
- 96 character ASCII set (includes upper/lower case).
- Automatic CR/LF.
- Accepts 8 1/2" paper.

HALF PRICE OFFER

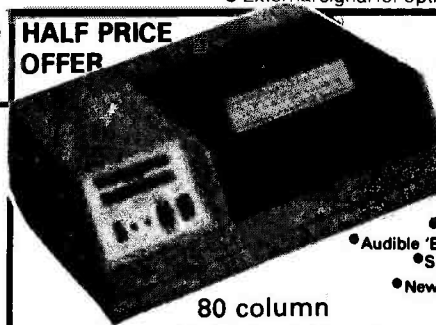

80 column

AS RECOMMENDED BY COMPUTING TODAY
CENTRONICS P1 PRINTER

EXCLUSIVE TO HENRY'S
50% OFF MAKER'S PRICE

- Software selectable 20, 40 and 80 column using 120mm aluminium-ised paper. 1 roll supplied.
- 150 lines per minute.
- Centronics parallel data interface for Nascom, Tandy, etc.
- 240volt mains input.
- ASCII character set
- Paper feed, and on/off select switches
- Audible 'BELL' signal Weight 10lbs
- Size: 13" x 10 1/2" x 4 1/2" LIST PRICE £400
- New, boxed and fully guaranteed

Price £195.00

plus VAT post FREE

Spare paper £4 per roll + VAT

FERRANTI COMPUTER KEYBOARDS

SOLID
STURDY
CASE



SIZE
14"x6"x3"
SLOPING
FRONT

60 Key ASCII Coded in steel case
Latched output complete with Plug & Cable with circuit to convert to T.T.L. levels.

In good condition
at only

£25 + VAT
P/P £2.50

Your London & National Nascom Distributor.
Export Orders deduct VAT, but add 5% carriage
Official Export & Educational Orders welcome
Our Telex 262284 Mono Ref. 1400 Transonics

**COMPUTER SEND
BROCHURE 15p
FREE STAMP**




HENRY'S

Computer Kit Division
404 Edgware Road, London, W2, England
01-407 6822



MONITORS MONITORS MONITORS

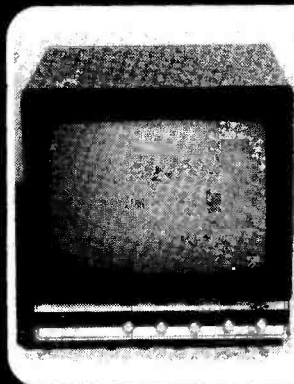

Uncased from 3" to 12"
Cased from 5" to 20"

Semi professional or
professional available
from stock.


Monitor PCB's including
Transformers and Tubes
also in stock.

Phone or write for
details.

CROFTON ELECTRONICS

Crofton Electronics Limited
35 Grosvenor Road, Twickenham, Middx.
Tel: 01 891 1513

CLEF KITS

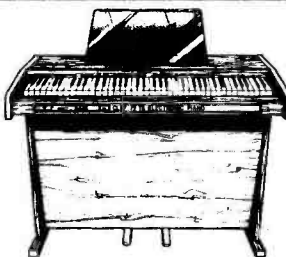

NEW — ELECTRONIC ROTOR

Two-speed organ rotor simulator plus a three-phase chorus generator on a single PCB (8"x5"). Kit includes all components — IC sockets throughout — mains operation and stereo headphone driver PCB. Easily integrated with existing organ. Component kit **£89.00**.

KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

49 NOTE C-C **£23.80**

73 NOTE F-F **£37.00**

88 NOTE A-C **£45.00**

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists.

INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & insurance.

VISITS

Are welcome by appointment, otherwise Mail Order Only

EXPORT

Enquiries welcome — in Australia please contact JAYCAR (Sydney).

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS

Six and 7 1/4 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use, from our top quality Component kits.

SIX OCTAVES — **£195**

7 1/4 OCTAVES — **£220**

P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT — **£164**


Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.

P.A.'s — SPEAKERS — CABINETS

Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)

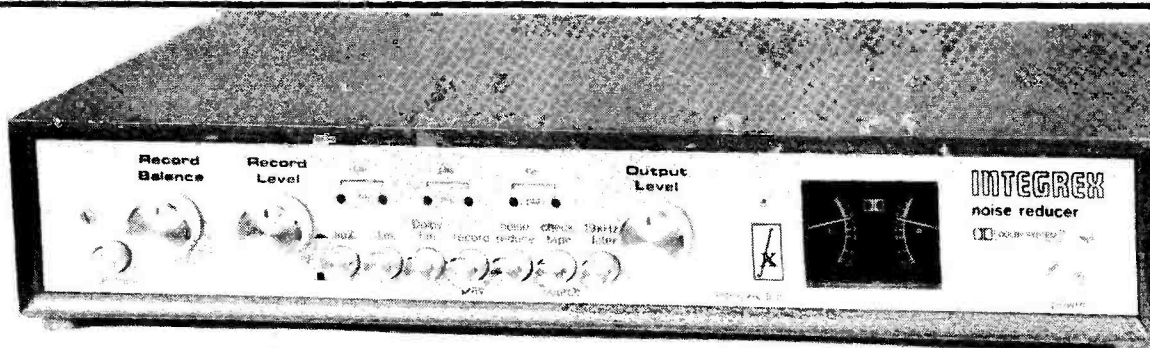16 Mayfield Road, Bramhall, Cheshire SK7 1JU. 061 439 3297



DOLBY[®] 'B' NOISE REDUCTION UNIT

Trademark of Dolby Laboratories Inc.

Add DOLBY to your tape system!

Featuring

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions
- all inputs and outputs are adjustable
- suitable for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines
- solid mahogany cabinet
- 240v ac mains operated

Dolby level cal tapes are available for open-reel use and for cassette (specify which). **Price £2.40** (inclusive)

- We guarantee full after-sales technical and servicing facilities
- High performance Tuner Amp. Tuners and surround sound available

Prepare for B.B.C. Quadraphonic Broadcasts — Send for details of our Ambisonic H.J. decoder kit

Typical performance

Noise reduction better than 9dB weighted.
Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content).
Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%.
Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output.
Dynamic Range > 90dB
30mV sensitivity.

KIT PRICE £43.90 + VAT

INTEGREX LTD.

Please send SAE for complete lists and specifications
Portwood Industrial Estate, Church Gresley
Burton-on-Trent, Staffs, DE11 9PT
Burton-on-Trent (0283) 215432. Telex 377106



system, using some twenty ICs. Sockets are provided for all of them — that's what I like to see. (Have you ever tried desoldering a duff chip?). The second (2¼" x 2") board carries components for the low impedance stereo headphone driver circuit. Mains power supply components are also supplied.

The PCBs are labelled with component values, rather than numbers. Some legends are a little indistinct, so a full components listing is given as a double check. All nine controls are included as preset pots on the PCB, but you can replace

them with external pots, if necessary. Holes in the PCB allow operation of the presets if you want to keep the controls on-board.

If you already have an electronic organ, you can add on this unit for some interesting effects, or you could use it as an experimenters' kit for use with your own signal source. A system interconnection diagram is provided, showing the unit placed between the signal source and existing power amplifiers.

ETI INDEX 9C

COMPU-TECH SYSTEMS


Company	Compu-Tech Systems.		
Kit	Car Security System		
Price	£11.95 + Siren (£7.75)		
Complexity	B	Instruction Manual	3
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	0

This design from Compu-Tech was published in ETI last month. It's an add-on unit for the ETI car alarm (also designed by Compu-Tech) published in December 1978. The original unit protected both the car itself (by monitoring all doors and disabling the ignition when set) and the car's accessories. There is an entry and exit delay before the horn is sounded, so you don't have to fit any external switch.

Construction is quite straightforward and the use of the familiar Incar connectors allows the unit to be fitted easily to almost any car.

The later add-on unit allows simultaneous sounding of the horn and flashing of lights and brake lights when the alarm is activated, whilst maintaining complete isolation between these circuits when in normal use.

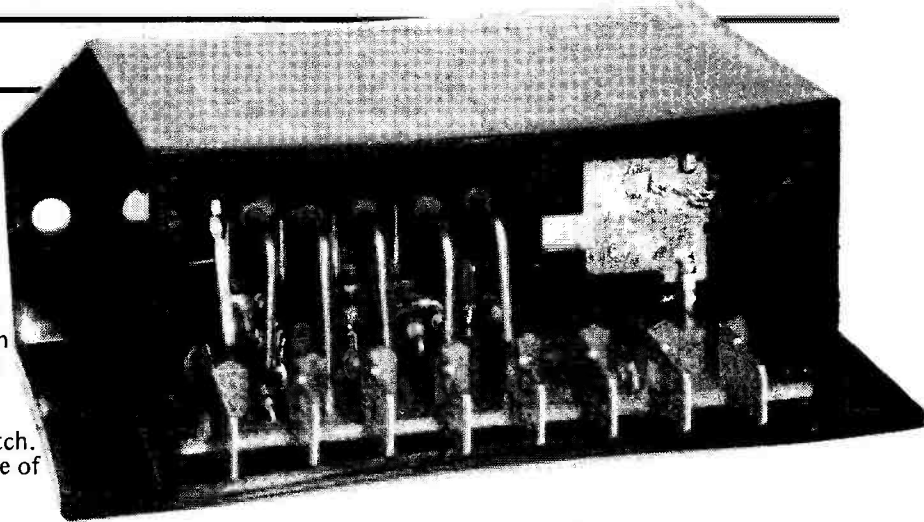Both kits are constructed on compact PCBs, housed in attractive, weather resistant plastic cases. A complete kit of



parts for the original alarm unit is still available from Compu-Tech for £14.75 (PCBs only — £1.00 each). You can buy a complete kit of parts for the add-on system for £11.95 (siren £7.75 extra and PCBs only £1.00 each). Both kits and siren are available for £29.95 all inclusive (a saving of £4.50).

ETI INDEX 10B

CONTINENTAL SPECIALTIES CORPORATION


Company	Continental Specialties Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.		
Kit	Logic Probe Kit LPK-1		
Price	£11.92 + VAT		
Complexity	A		
Circuit Diagram	1		
Contents	3	Finish	3
Instruction Manual	3	Fault-Finding Guide	1

CSC, better known for their Proto-Board and Experimentor Systems, say you can build this full-performance logic probe kit 'in just a few hours of easy assembly'. I think even a newcomer to project building should be able to have a working probe in a lot less than a few hours with the aid of CSC's excellent, step-by-step instruction manual. The most difficult operation is persuading the PCB to fit inside the compact case — so no constructional problems here.

The 203A 'powered' Proto-Board is now also available as a kit (the 230AK) — a sturdy box with a large area of Proto-Board on top and a 5 V at 1 A and separate internally adjustable 7-18 V at 0A5 supplies inside.

The 230AK kit came in handy when I finished my Microtan computer kit. The 5 volt, 1A outlet was the perfect power supply. Then I used my completed logic probe kit to inspect the logic state of the computer chip pins.

ETI INDEX 11A

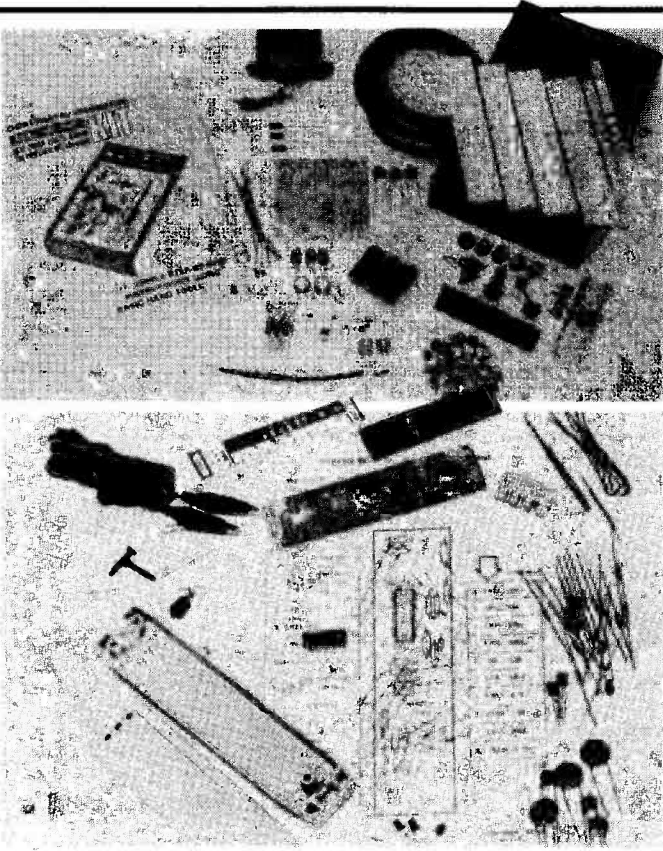

DIGISOUND

Company	Digisound Ltd, 13 The Brooklands, Wrea Green, Preston, Lancashire PR4 2NQ.		
Kit	24 dB per octave low pass VCF		
Price	£18.08		
Complexity	B	Instruction Manual	3
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	0

Digisound sent me a kit from outside the ETI 80 range (the modular synthesiser series which we began in February this year). They sent a 24 dB/octave low pass voltage controlled filter with voltage control of resonance. Coarse and fine pot controls give a range of ± 5 octaves and ± 1 octave respectively.

With the PCB and component pack you will receive two important pieces of paper. The first gives some general notes on construction with details of Digisound's technical service, should you be unable to get your kit working. The second includes a circuit diagram, component overlay, component lists and more detailed construction, testing and calibration notes. For calibration you'll need a previously calibrated VCO.

Digisound's kits seem to have a lot less paperwork with



them than other kits of comparable cost and complexity. However Digisound manage to pack a great deal of useful information into a small space and yet keep it perfectly readable and understandable.

ETI INDEX 10B

ELECTRONIC DESIGN ASSOCIATES

Company	Electronic Design Associates, 82 Bath Street, Walsall WS1 3DE.		
Kit	Sparkrite X5 inductive discharge Electronic Ignition		
Price	£16.95		
Complexity	A	Instruction Manual	3
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	1

This spark of genius arrived well packaged with separate component packs. The instructions include a 'how to solder' section and the parts list gives resistor colour codes, so you're not likely to go wrong unless you're colour blind. EDA also operate an after-sales technical advice service, just in case you *do* have any problems. If you're not often under the bonnet of your Rolls, don't worry, fitting instructions are included.

All in all a useful, attractive and easy to build kit. When it's finished you don't have to bolt it on somewhere. It comes complete with clips, so that you can simply push it on to your coil. Connection is then a matter of attaching a few wires to the existing circuitry and you're off. No more cold morning push starts.


ETI INDEX 11A



GP INDUSTRIAL ELECTRONICS

Company	GP Industrial Electronics, Skardon Works, Skardon Place, North Hill, Plymouth PL4 8HA.		
Kit	Softy EPROM Programmer		
Price	£115 + PSU (£23)		
Complexity	C		
Circuit Diagram	1		
Contents	3		
Instruction Manual	1		
Finish	3		
Fault-Finding Guide	1		

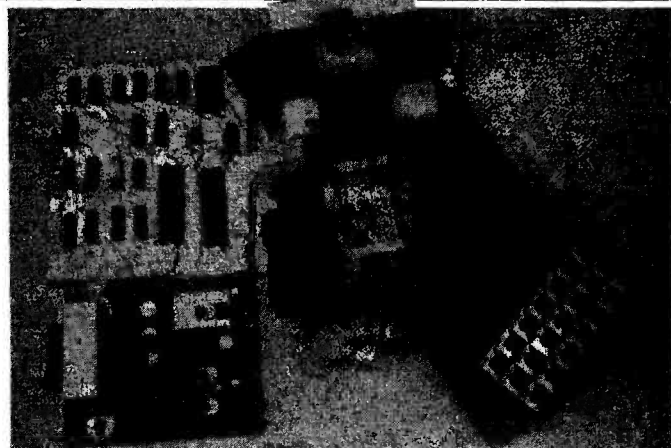Henry Budgett of Computing Today, anxious to put his expert computing knowledge to good use, got cracking on this one (and soon wished he hadn't). He reports that the PCB is double-sided but not plated through, so you have to make some two hundred connections before you can put the first



KIT FINDER

	Acorn Computers	Altek Instruments	Ambit International	Aura Sounds	Cambridge Kits	Catronics	Chromasonic	Chromatronics	Clef Products	Comp Comp Comp	Compu-Tech Systems	CSC	Crofton Electronics	Digisound	Electronic Design Associates	Electro-Tech Components	GJD Electronics
ALARMS																	
AMPLIFIERS																	
CASSETTE DECKS																	
COMPUTING																	
DICE																	
DOLBY																	
DOOR CHIMES																	
ELECTRONIC IGNITION																	
GAMES																	
LIGHT SHOW																	
METAL LOCATORS																	
RADIO CONTROL																	
SYNTHESISERS																	
TELETEXT																	
TEST GEAR																	
TIMERS																	
TUNERS																	
TV CAMERA																	

The addresses of companies who did not supply kits for the survey, but who are included in the quick index, are shown below. The addresses of companies who did supply kits are shown with the appropriate kit report.

Ambit International,
200 North Service Road,
Brentwood, Essex.

Aura Sounds,
14-15 Royal Oak Centre,
Brighton Road,
Purley, Surrey.

Cambridge Kits,
45 Old School Lane,
Milton,
Cambridge CB4 4BS

Chromatronics,
River Way,
Harlow, Essex.

Comp Comp Comp.,
14 Station Road,
New Barnet,
Herts EN5 1QW

Crofton Electronics Ltd.,
35 Grosvenor Road,
Twickenham,
Middlesex.

Electro-Tech Components Ltd.,
364 Edware Road,
London W2

GMT Electronics,
Freepost,
Birmingham B19 1BR

Computers of all sorts and their accessories all go by the name of computing in this index, so thumb through the magazine for the company's advertisement to find out exactly what they can supply. Clocks have been included under the heading of timers.

[illegible]

**Maplin Electronic Supplies Ltd.,
PO Box 3,
Rayleigh,
Essex SS6 8LR**

**Science of Cambridge Ltd.,
6 Kings Parade,
Cambridge,
Cambs CB2 1SN**

**Transam Components Ltd.,
12 Chapel Street,
London NW1**

SOFTY INTELLIGENT EPROM PROGRAMMER



THE COMPLETE MICROSYSTEM DEVELOPMENT TOOL

SOFTY is a small computer which is designed to be a complete and useful tool in its own right. SOFTY may be used in three main ways: As a 2k block of intelligent memory forming part of the memory map of a system under development. As an intelligent EPROM programmer for 2708S/2716S. As a control computer in its own right. Write or telephone for full details:

SOFTY is available NOW — ex-stock

Only £120 + VAT built and tested

£100 + VAT kit £20 + VAT built power supply

£145 + VAT built and tested, converted for 2508/2516 Programming (conversion details are supplied with every SOFTY purchased)

Prices include postage and packing

The SOFTY system is covered by a money back guarantee and our fast repair / advise service.

GP INDUSTRIAL ELECTRONICS LIMITED

Skardon Works, Skardon Place, North Hill, Plymouth PL4 8HA.

Telephone: Plymouth (0752) 28627

BUILD YOUR OWN METAL DETECTOR VLF/TR VCO/TR IB/TR BFO...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.



Shadow VLF/TR. Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nails bottle caps even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.

The head is thermally and capacitively shielded. 4 modes: deepseeking VLF plus 3 TR discriminating ranges. Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI.

Complete kit now only £79.70 inc. VAT & post!
Individual parts: Search head £21.33 PCB £6.80 Case £5.33 Adjustable shaft assy. £5.10 LM393 £1.12. Manual (gives more info. than ETI article — and extra function) £1.12. All inc. VAT & post! (Other parts also available separately)

Shadow TR/IB

Shadow TR/IB (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. **Complete kit £25 + VAT (post & Pkg. £1.80).**

Shadow TV/VCO. An advanced version of the TR/IB. Use as a sensitive IB machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. **Kit price £29 + VAT (post £1.80).**

Matching stereo headphones for all Shadow models £4.90 + VAT (post paid).

Beginners BFO model. A very detailed assembly manual and pre-wound coils make this an ideal first project. Simple high efficiency circuit. Full size (not a toy) but weighs only 300gms (10.5ozs) with battery! **FREE STETHOSCOPE HEADSET** with every order. **ALT3 kit: £12 + VAT (post £1.80).** Padded high Z headphones £4.50 + VAT (post paid).

Shell Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions £8.25 + VAT (post £1.50).

ALTEK


(ETI), 1 Green Lane
Walton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please. Phone (093 22) 44110 anytime

FANTASTIC INTRODUCTION OFFER

Newly introduced to our Catalogue — low price, high quality

MULTI RANGE TEST METERS

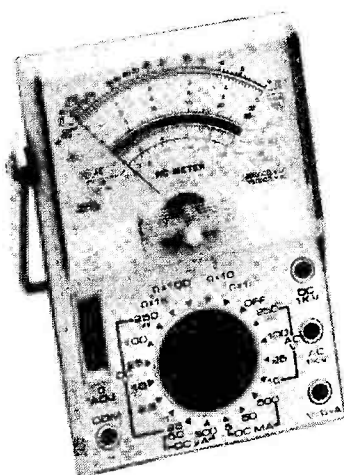

Specification:

Voltage

Model MM-102
DC: 0.25, 1, 2.5, 10
25, 100, 250, 1000
AC: 10, 25, 100,
250, 1000

Sensitivity

DC: 20,000 Ohms/Volt
AC: 10,000 Ohms/Volt

Decibels

DC Current

—20 to +20 db
50, 500µA
5, 50, 500mA

Ohmmeter

30 Ohms centre scale

Power Supply

Size

Weight (incl. battery)

Four Ranges:
0.6 k. Ohms
0.60 k. Ohms
0.600 k. Ohms
0.6 M. Ohms
Single 1.5V cell
135 x 91 x 39mm
280 gms.

Model MM-101
DC & AC 10, 50
250, 1000

2,000 Ohms/Volt
—10 to +22 db
100mA


60 Ohms centre scale

Two ranges:
0-10 k. Ohms
0-1 M. Ohms

Single 1.5V cell
90 x 60 x 29mm
92 gms.

Mirrored scale
Overload protection
Carrying handle doubles as bench stand

Mirrored scale

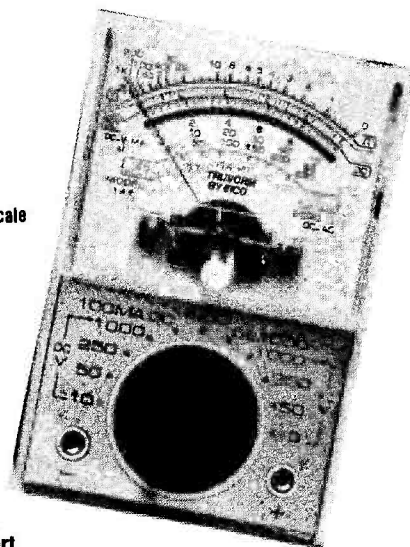

Delivered price. £13.99 U.K. £15.99 Export £5.95 U.K. £7.95 Export
Inclusive of battery, test leads and instruction booklet

Also available: Delpak voltage regulators and power supplies, Delpak keypads and keyboards, Futaba keyboard switches, Futaba vacuum fluorescent displays, I.Cs. from OKI; Power amplifiers, filters, stereo image width control, compressor/expander, active crossovers, power supplies, plus all pots, switches, etc.

MAGNUM AUDIO LTD.

Dept. ETI 5, Hazelbury Crescent
Luton LU1 1DF. Tel: (0582) 28887
Send large S.A.E. for details

BIO ACTIVITY TRANSLATOR™



Natural Bio Electric signals are monitored by an electrode attached to the leaf. When amplified and filtered, a VCO, VCA and other exclusive synthesiser circuits are controlled by the potential to produce tracking sequences of notes. These follow in pitch, rhythm and volume the ever changing signal.

Components include: 6IC's, 3 Transistors, 11 Diodes, 19 Capacitors, 50 Resistors, PCB, L.S., all Hardware and professional teak finish case.

Output available for either audio amplification or a directly coupled signal from the biological amplifier for use with oscilloscope or chart recorder.

A Biological Amplifier and Sound Synthesiser in one Instrument.


Ready Assembled £35.25; Kit £27.35

All prices include P & P and VAT
Please allow 21 days for delivery

JEREMY LORD SYNTHESISERS LTD.
(Dept EM)

3 Charterhouse, Eltringham Street, London, SW18 1TD

TRULY PORTABLE COLOUR BAR GENERATOR

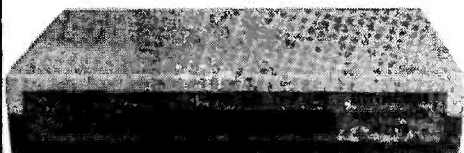

**ONLY
£59.50**
Inclusive
(In kit
form)

- ★ Fully self-contained, includes built-in rechargeable battery and power unit/charger
- ★ Five standard test patterns viz. Colour Bars, Red Raster, Crosshatch, Linearised Grey Scale and Peak White.
- ★ Kit comes complete with **PROFESSIONALLY FINISHED** Case and Tinned, Printed and Drilled P.C.B.
- ★ Size only 8" x 5½" x 1½"
- ★ Ready-built and tested version —

£88.25 inclusive

NASCOM 1 & 2 COLOUR GRAPHICS BOARD

- ★ Runs on a Minimum Nascom 1 or 2
- ★ 8 Background and 8 Foreground Colours
- ★ Continuous shapes may be constructed using the 3072 Colour addressable cells.
- ★ Text and Colour Graphics may be mixed anywhere on Screen.
- ★ The complete kit, including Test programs only

Available from: **£22.50** inclusive
INTRACEPT ELECTRONICS LTD.
DEPT. ET1, 203 PICTON ROAD
WAVERTREE, LIVERPOOL 15
TEL: 051-733 3042



1st

Top of all systems
tested by independent
national authority
July '79

C300/ES200

high performance electronic ignition to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection); electronic variable dwell circuit (maximises spark energy at all speeds); pulse processor (overcomes contact breaker problems); Coil governor (protects coil); Long burn output. Negative earth only. Compatible with all rev counters.

C300. In its ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths Jaeger rev. counters code RVI on dial will require adaptor type ICI).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer.

Fully illustrated comprehensive instructions and full technical back up service.

SUREFIRE

ELECTRONIC IGNITION

Suretron Systems (UK) Ltd.

Piccadilly Place, London Rd., Bath BA1 6PW. Tel: Bath (0225) 23194

Dept. ET15

Name

Address

*Phone order with Access Barclaycard
VAT and P & P inc

Quantity
required


ES200: Neg	£13.95
C300: Pos	£17.95
C300: Neg	£17.95
Tacho Adapt. TC1	£3.90

Enclose
chg. P.O.'s
£
Chq No

component in. The parts list is incomplete (not listing the modulator or the hardware — nuts, bolts, keys, etc). Constructional notes are almost non-existent. However, a warning is included for the constructor — 'A professional level of understanding is expected and assumed.'

This is definitely *not* a kit for beginners as a thorough knowledge of computer systems is required to build it into your system. At £115 it's a bit pricey, especially if you don't understand what you're doing. If you *do* end up with an expensive book-end, send it back to GP Industrial Electronics with a cheque for £20. They'll sort it out and charge you for any parts they think you've shuffled off to the great reject bin in the sky.

ETI INDEX 9C

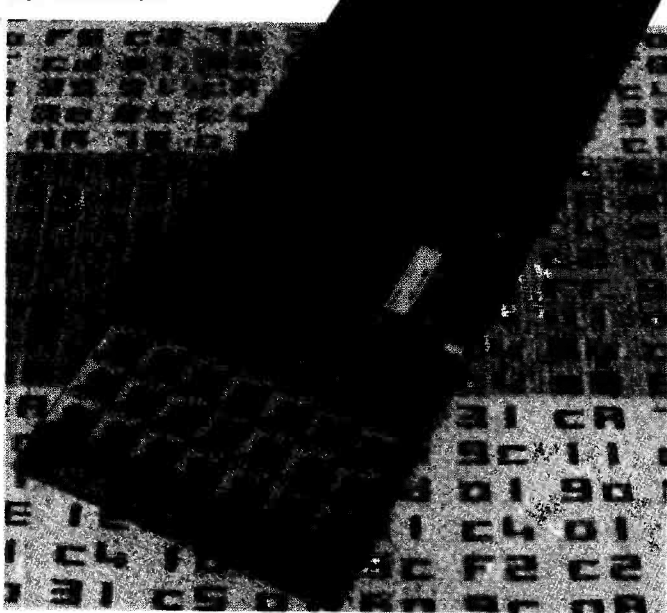

HEATHKIT

Company	Heathkit, Bristol Road, Gloucester GL2 6EE		
Kit	Quartz Clock Timer GC-1415		
Price	£43.63		
Complexity	B	Instruction Manual	3
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	1

Heathkit's excellent instruction manual greatly simplifies construction of this sophisticated quartz clock/timer, bringing it within the range of ability of more constructors. That makes sound economic sense. The more people who are capable of building the kit, the bigger the potential market.

Although it's not the simplest of kits, Heathkit's manual assumes nothing. It starts from the basics with notes on soldering. The kit is intended for installation in your car (a mounting bracket and adhesive pads are supplied), but, with the addition of a 12 volt DC supply, you have a 12 hour, 4 digit clock with trip-timer and stopwatch functions attractive enough to grace your mantelpiece (at home, not in the car!). If you *are* going to fit it in your car, full fitting instructions are given for negative earth vehicles.

I haven't a great deal to say about this kit — the sign of satisfaction and trouble-free construction, well-known, to be typical of the well-prepared and presented Heathkit products.


ETI INDEX 11B

HENRY'S RADIO

Company	Henry's Radio, Computer Kit Division, 404 Edgware Road, London W2.
Kit	Nascom 2
Price	£295 + VAT
Complexity	C
Circuit Diagram	1
Contents	2
Instruction Manual	3
Finish	3
Fault-Finding Guide	1

If you're not already acquainted with Nascom 2 or anything of comparable constructional complexity, opening the boxes of boards and seemingly endless bags of components can be a traumatic experience. There are an awful lot of holes in the PCB that have to have something soldered into them. Where to begin the endurance test?

The manual offers good advice. 'Do *not* begin construction now. Read through all the documentation at least twice.' Construction times can range from under 10 hours to over 40, 30 hours being the average. The manual advises you not to work for more than 2 or 3 hours at a stretch — good advice. It then goes through each stage of construction with diagrams, where necessary. This isn't the sort of kit that you can start on the dining room table and clear the bits away every time dinner, tea, supper, etc come around. That's the easiest way to lose bits and destroy chips. Find a place where everything can lie undisturbed for days at a time. It also helps if you

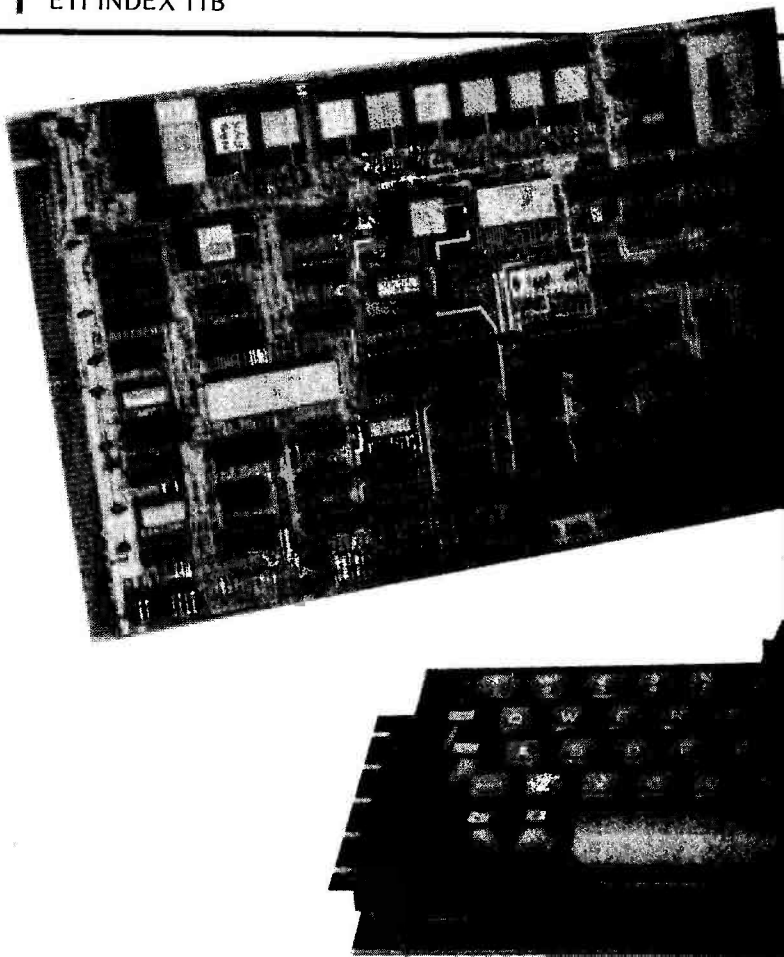

INTEGREX

Company	Integrex Ltd, Portwood Industrial Estate, Church Gresley, Burton On Trent, Staffordshire DE11 9PT.		
Kit	Dolby Noise Reducer		
Price	£50.48		
Complexity	C	Instruction Manual	2
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	0

If you bought a cassette deck without Dolby noise reduction and don't feel like trading it for a machine with Dolby, you could build the Integrex Dolby Noise Reducer as a separate unit. Integrex claim that their design is the only 'add-on' Dolby processor kit in the world.

Integrex's preface to the construction notes advises you to check that all the components have been packed and sent in good condition. It may seem obvious, but it's always worth reminding the newcomer to kit-building. The remainder of the instruction leaflet takes the form of a reprint of the magazine article describing the system. One useful feature is the inclusion of a note of the most common constructional errors — collect one bonus point as you pass go in lieu of a point for the absent troubleshooting guide.

INTRACEPT ELECTRONICS


Company	Intracapt Electronics Ltd, 203 Picton Road, Liverpool L15 4LG.		
Kit	Nascom colour graphics board		
Price	£22.50		
Complexity	B	Instruction Manual	2
Circuit Diagram	1	Finish	2
Contents	3	Fault-Finding Guide	0

If you already have a Nascom 1 or 2, this kit enables you to produce colour graphics under software control. The background can be set to one of eight colours (including black and white) by altering the contents of address 0C00 or by


have a high SQ (stamina quotient) or BT (boredom threshold) because there is a lot of intricate soldering to get through before you come to the interesting bit — switching on. The only serious error a careless constructor might make is in the connection of the keyboard to the processor PCB. It is possible to plug the keyboard into the wrong position. Then, at switch-on you find you no longer have a working keyboard. This was drawn to my attention by a recent phone call to Computing Today from an electronics engineer who, of course, ignored the instruction manual. Being a professional, he didn't need to read the manual. He blew up his keyboard. 'Read through all the documentation at least twice.'

Because of the non-availability of 4118 chips, Nascom 2s are currently being supplied without the 4118s, but with a free 16K dynamic RAM board. When 4118s are again available, Nascom 2 buyers will be able to get hold of them at the special price of £80 + VAT for the 8K.

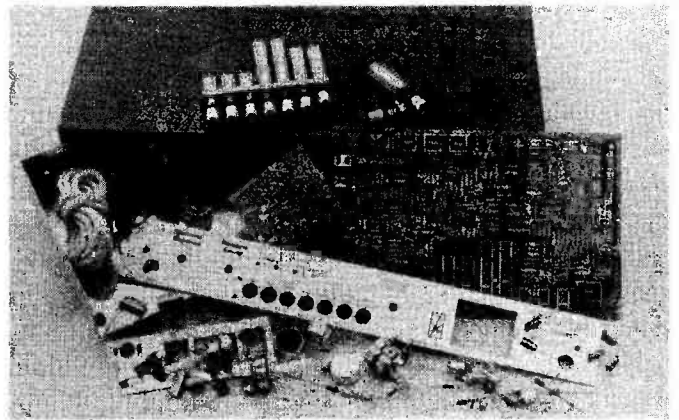Henry's Radio are also offering a free power supply. If you get your Nascom 2 from Nascom, without 4118s and without the 16K RAM board you can expect to pay £225. ETI INDEX 10C



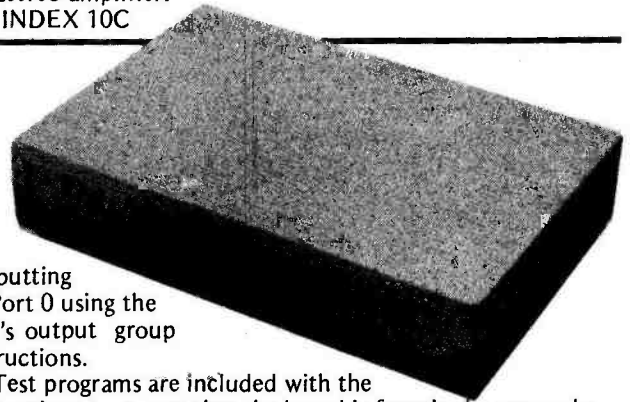The PCB and components come with all the necessary hardware — an aluminium chassis and an attractive mahogany sleeve. The unit matches other Integrex products in both appearance and electronically, in terms of input/output signal parameters and standardised DIN sockets. So, having built your Dolby system you can then build a matching FM tuner and stereo amplifier. ETI INDEX 10C




outputting to Port 0 using the Z80's output group instructions.

Test programs are included with the instructions to ensure that the board is functioning properly (Nasbug and Nas-Sys versions are supplied). The colour graphics modulator may be used with Nascom 1 or 2 and the appropriate alterations to Nascom's main board in order to use the colour graphics option are given, together with a testing procedure.

Intracapt also supply a colour bar generator kit primarily for the field service engineer. It's a useful diagnostic tool for troubleshooting colour telly faults. It can display the standard waveforms and colour bar pattern. From them, if you know what you're doing, you should be able to spot decoder faults (incorrect matrixing, ident, colour balance, demodulator phasing, delay line adjustment, etc.). The five patterns available (blank raster, grey scale, cross-hatch, colour bar and red raster) should enable a service engineer to accurately adjust and service colour television in the home.

ETI INDEX 8B

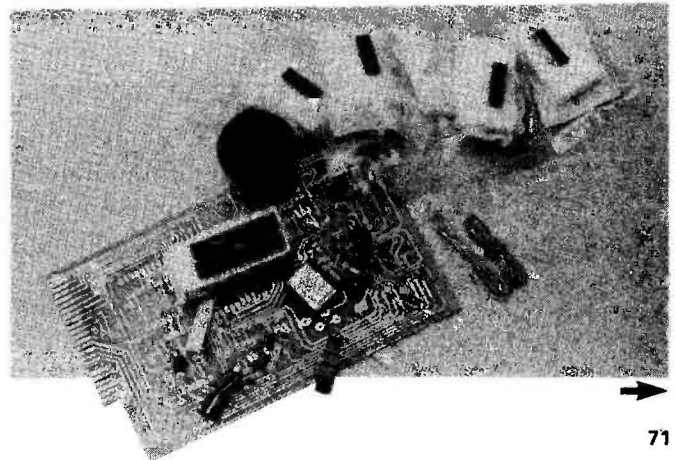


JAYEN DEVELOPMENTS

Company	Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY. Jaykit DM-2 Digital Multimeter £5.45		
Kit	B	Instruction Manual	2
Price	1	Finish	3
Complexity	3	Fault-Finding Guide	1
Circuit Diagram			
Contents			

I must confess that the idea of a kit without components struck me as about as useful as a handful of rice pudding for resurfacing the M1. However, I take it all back. In fact, it's not a bad idea at all. What do you need to turn a tobacco tin project into something a shade more sophisticated? You could start with a well-made PCB and a professional-looking front panel. Well, if you send off your pennies to Jayen, that's exactly what they send you — PCB plus front panel. You also get a shopping list for components, which you can buy for £23.75 from an address given by Jayen. Jaykit's FG-1a Function Generator is also sold in this form. Nice idea.

ETI INDEX 10B

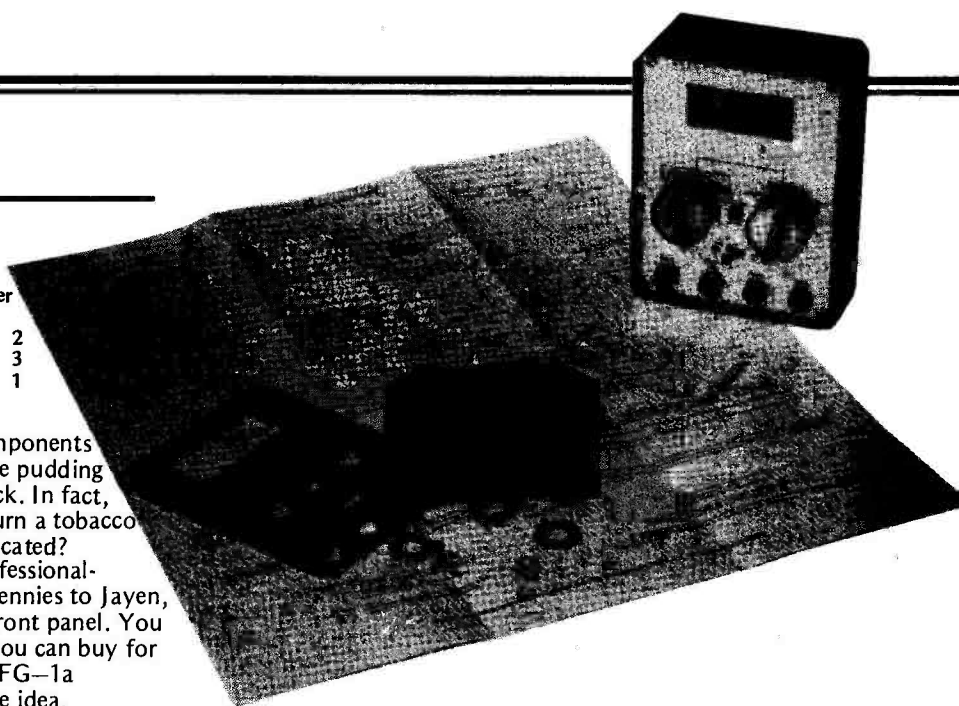

JEREMY LORD SYNTHESISERS


Company	Jeremy Lord Synthesisers Ltd, 3 Charterhouse, Eltringham Street, London SW18 1TD. Bioactivity Translator £27.35		
Kit	B	Instruction Manual	2
Price	1	Finish	3
Complexity	3	Fault-Finding Guide	0
Circuit Diagram			
Contents			
Instruction Manual			
Finish			
Fault-Finding Guide			

This instrument has been getting a lot of publicity recently in the national Press and on radio. It works on the principle that plants generate minute electrical potentials which the translator can amplify and use to control a synthesiser. The sound output follows the signals from the plant in pitch, rhythm and volume.

In practice, however, the device responds more to movement of the plant. I suspect this has something to do with the design of electrodes used — based loosely around a common or garden hairclip and conductive foam pads. However, the principle is sound and the system works.

What's it like to build? Construction posed no problems. The PCB fits neatly into the smart teak finish case and a self-adhesive plastic sheet gives the front panel a professional appearance. It's a self-contained unit — you don't have to plug it into your amplifier. Synthesiser, amplifier, controls, batteries and loudspeaker are all housed in a single box.

ETI INDEX 9B

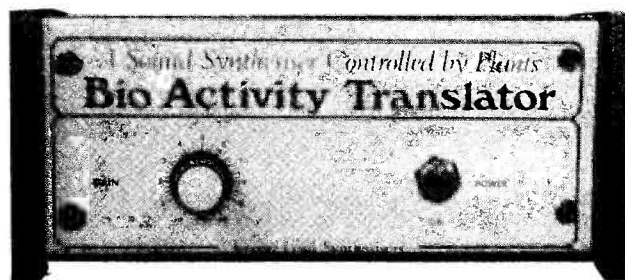


NIC

Company	NIC, 61 Broad Lane, London N15.		
Kit	Pinball Wizard		
Price	£39.30		
Complexity	B	Instruction Manual	2
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	0
Instruction Manual			
Finish			
Fault-Finding Guide			

The Pinball Wizard black and white TV game was featured exclusively in the November 1979 issue of ETI. NIC purchased 500 of the games chip used in this kit. As Pinball Wizard has been selling well, I should get in touch with NIC as soon as possible, to avoid disappointment.

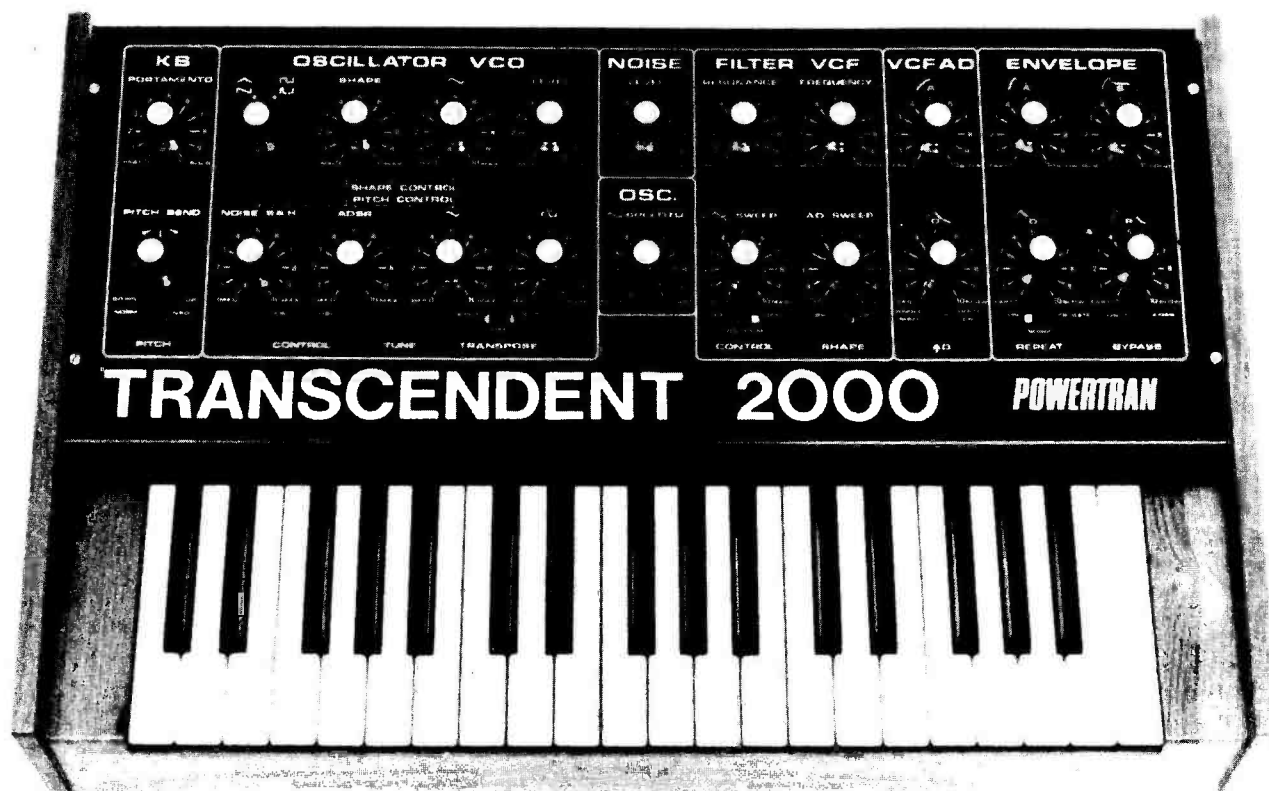The chip does most of the work, so there are few extra components on the board, simplifying construction. You can buy everything you need from NIC for £39.30, or you could invest in just the basic kit of PCB and components for £28.90. The box and controls are £6.50 extra and the mains adaptor another £3.90.



POWERTRAN ELECTRONICS

Company	Powertran Electronics, Portway Industrial Estate, Andover, Hants SP10 3NM.		
Kit	Transcendent 2000		
Price	£168.50 + VAT		
Complexity	C	Instruction Manual	3
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	0

Powertran Electronics sent us a Transcendent 2000 single board synthesiser to have a look at. It's a 3 octave instrument transposable 2 octaves up or down giving an effective 7 octave range. Features include portamento, pitch blending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, amongst many, many others.

It's definitely not a beginners' kit, although we can't give you a full account of any constructional difficulties, because Powertran wouldn't let us build it. However, I can tell you that the kit comes absolutely complete, right down to the mains plug. The components are separated into 16 packs, each with a separate component listing, greatly facilitating component checking.

ETI INDEX 10C

The game includes pinball, basketball and breakout options, selected by push button. The star was undoubtedly breakout. Everyone here at ETI who borrowed the game became hopelessly addicted to breakout. You find that you have to have just one more game to try to get the maximum score of 864 by demolishing two walls of bricks with seven balls . . . and then just one more game . . . and then . . .

NICs shop is packed with goodies, from a car alarm kit to computer kits (Nascom 2 and the UK101) including the Heathkit H14 Line Printer. Why not pop round for a browse.

ETI INDEX 9B




SURETRON SYSTEMS

Company	Suretron Systems (UK) Ltd, Piccadilly Place, London Road, Bath BA1 6PW.
Kit	Surefire C3000 Electronic Ignition
Price	£17.95
Complexity	A
Circuit Diagram	1
Contents	3
Instruction Manual	2
Finish	3
Fault-Finding Guide	1

Construction is straightforward — just work your way down the list of assembly instructions. Copious diagrams show how components should be mounted. One group of components must be mounted very close to the PCB as a choke is mounted above them. Be careful how you hold the board when you're trying to persuade the choke pins to locate properly in the holes. When they snap into position, I can assure you that the pointed pins go through fingertips like a hot soldering iron through butter. Although the kit is designed for negative earth vehicles, alterations are given for positive earth vehicles. When construction is complete Suretron's panel stickers give the kit a professional finish.


Fitting your new space-age electronic ignition system involves drilling a few holes in your precious auto-not-so-mobile. If you follow all the instructions, but the little box still suffers rejection problems from your motor, a flick of a switch returns the engine to conventional ignition operation until you can sort out the trouble.

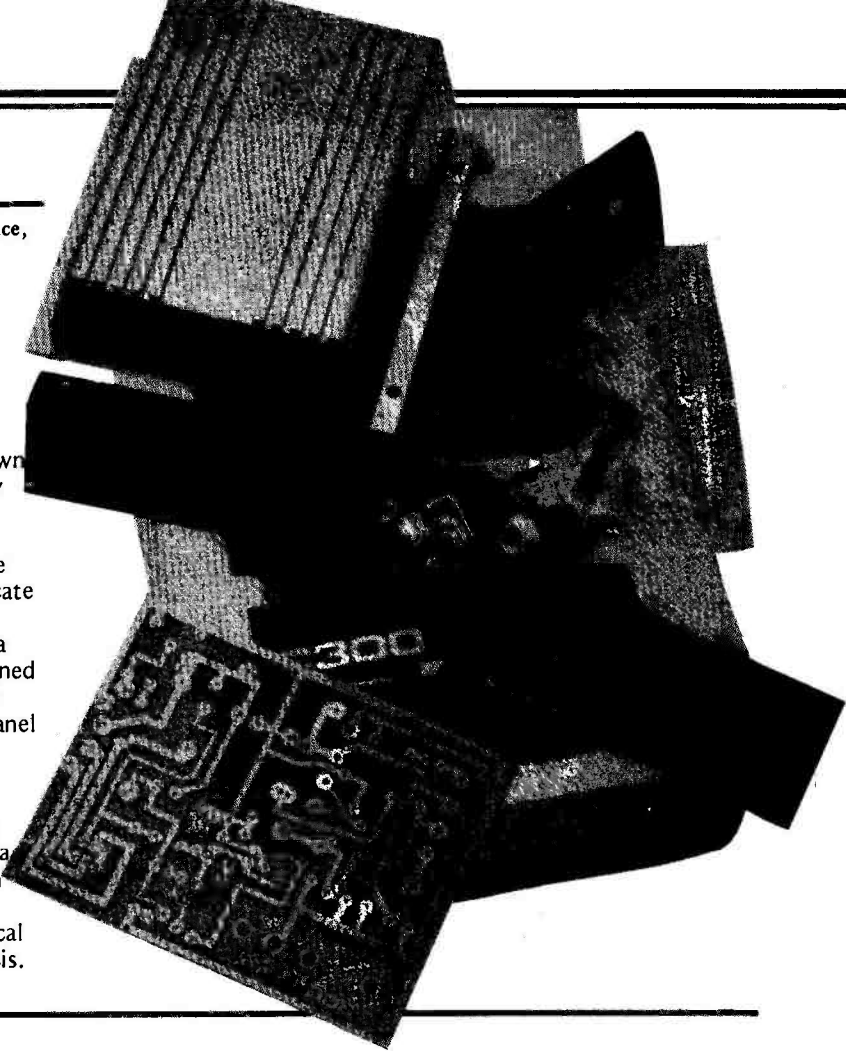If problems persist Suretron operate a telephone technical service or you can return the unit to them for fault diagnosis. ETI INDEX 10A



TANGERINE COMPUTERS

Company	Tangerine Computers, Forehill, Ely, Cambs.
Kit	Microtan 65
Price	£69 + VAT
Complexity	C
Circuit Diagram	0
Contents	3
Instruction Manual	3
Finish	3
Fault-Finding Guide	0

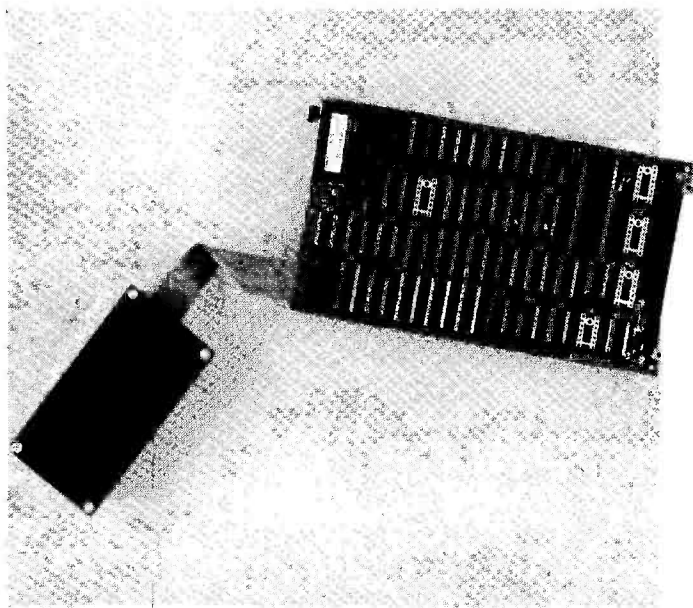

The arrival of this kit on my cluttered desk made a little bit of history at ETI. It kindled in my well-thumbed grey cells something approaching enthusiasm for computing — something which I had previously thought impossible. I grasped Microtan in both hands and made for the wilds of Staines. The kit is presented in the form of a ring binder. Open the first page and there is your basic kit. Free the PCB from its cling-film and underneath it you find the components, neatly laid out on double sided tape, making component checking as easy as falling off a soldering iron. Construction shouldn't pose any problems, as it's just a matter of identifying the component and plugging it into the position marked on the PCB. I reckon if I, with no past experience of computing, or computer kits, can build this kit and have it working in an evening of not very arduous soldering, then anyone can. Mind you, before I started, I equipped myself with a fine tipped iron and very fine solder.


Once it's working you can plug in extra ICs to give lower case and graphics options. If you find hexadecimal machine code as baffling as I do, you can add an expansion unit (TANEX) and a BASIC interpreter, so that you can talk to the machine through an ASCII keyboard in something resembling English. The excellent manual, also included in the ring binder, gives a few sample programs. Within hours of getting my hands on this kit, I was blissfully blasting marauding aircraft out of the sky with my telly-bound missile.

I've quite arbitrarily given this kit a bonus of five on the ETI INDEX for getting just about everything right and providing excellent value for money. I'd recommend Microtan 65 to anyone with a modicum of soldering experience and an interest in computing. ETI INDEX 14C

TK ELECTRONICS

Company	TK Electronics, 106 Studley Grange Road, London W7 2LX.		
Kit	DVM/Thermometer		
Price	£20.75 + VAT		
Complexity	B	Instruction Manual	2
Circuit Diagram	1	Finish	2
Contents	3	Fault-Finding Guide	0

This kit was featured as a Kit Review subject in Hobby Electronics (October 1979). HE built the digital thermometer version. When you've decided which version of the kit you want to construct you have to build a decimal point driver. Three circuits are suggested — two give a fixed DP and the third a floating point. The thermometer uses a fixed DP. No provision is made for the DP driver on the board and its components are not included with the kit, but this shouldn't cause any problems, especially if you have the typical constructors' junk box of components.

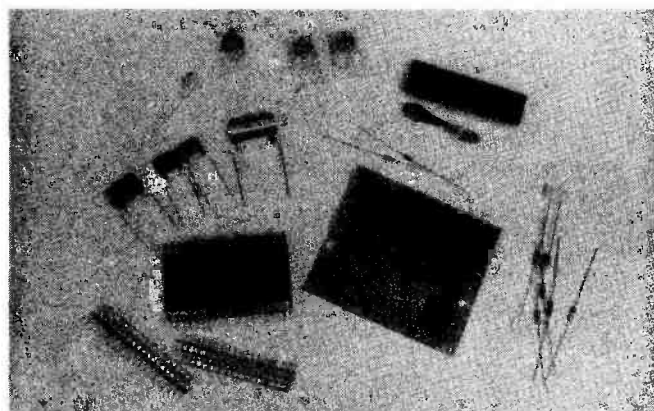

The diode sensor proved to be reliable and the thermometer appeared to be sensitive to temperature changes
ETI INDEX 8B


WATFORD ELECTRONICS

Company	Watford Electronics, 33-35 Cardiff Road, Watford, Herts.		
Kit	DM 900 Digital Multimeter		
Price	£60 + VAT		
Complexity	C	Instruction Manual	2
Circuit Diagram	1	Finish	3
Contents	2	Fault-Finding Guide	1

I hope you know your colour code for resistor tolerances. Watford's DM 900 kit uses 1, 2 and 5 per cent resistors and there's no explanation of the coding in the instructions. The only minor irritation to mar this otherwise well presented kit was that the complement of 64 single-ended Vero pins was about thirty short. The PCB, although double-sided, does not have plated through holes. So, links between the top and under side of the board are made by Vero pins.

Construction is fairly straightforward, being a matter of finding a component on the parts list and soldering it into the correct position marked on the PCB. You'll have to drill the plastic case to take the three test sockets, although the front control panel comes ready drilled and with the meter scales marked.

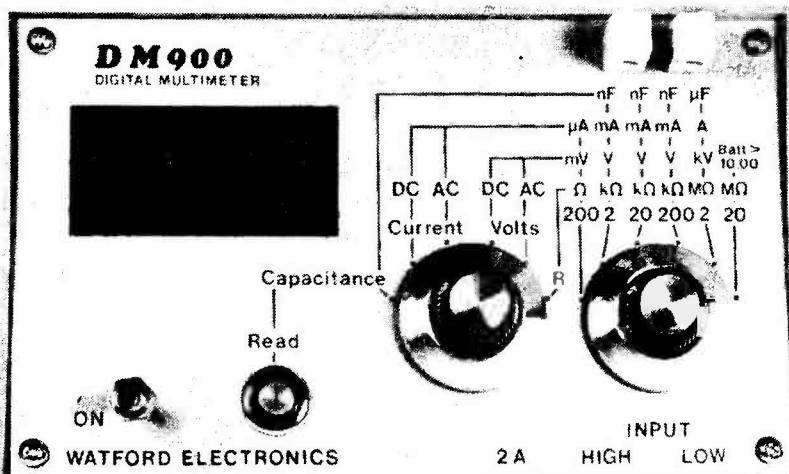You can buy the kit assembly instructions separately for £1.00 (free with kit) if you have an alternative supply of



components. However, if you are not building the DM900 from Watford's kit, don't skimp on components to save a few pence. Get the best. You can't expect to make an accurate meter if you use, for instance 10% or even 5% resistors throughout.

ETI INDEX 9C

WILLIAM STUART SYSTEMS

Company	William Stuart Systems, 137 Billericay Road, Herongate, Brentwood, Essex.		
Kit	Videograph		
Price	£26.95 + cabinet and controls £12.95		
Complexity	B	Instruction Manual	3
Circuit Diagram	1	Finish	3
Contents	3	Fault-Finding Guide	1


If you want to buy a Christmas present for your hi-fi system, this luxury box of tricks is a bit out of the ordinary. It actually displays sound waves in colour on any normal television set. Left and right hand channels are shown in contrasting colours. Press a button to invert one channel. Peak signals make the background cycle through eight colours.

The Videograph also has a test signal generator. You can record the clean square wave on your cassette recorder, playback the signal through Videograph and actually see the distortion introduced by your system. You can actually see the flutter, wow, low frequency and transient response of your recorder, amplifier, etc.

Construction is a matter of plugging components into two

well-marked PCBs according to the clear instruction sheets. The chassis is pre-drilled with an attractive front panel. William Stuart Systems offer a repair service if things go drastically wrong.

ETI INDEX 11B

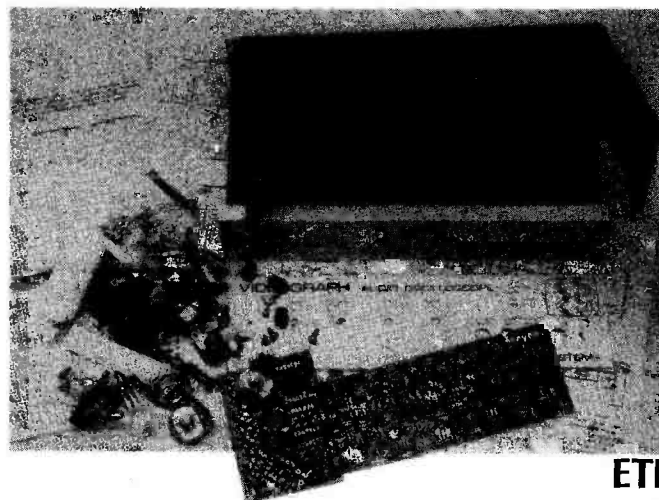

ETI BOOK SERVICE

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires £3.45
Beginners Guide to Transistors Reddihough £3.45
Electronics Self Taught Ashe £4.60
Beginners Guide to Integrated Circuits Sinclair £3.45
Understanding Electronic Circuits Sinclair £4.20
Understanding Electronic Components Sinclair £4.20
Beginners Guide to Radio King £3.45
Beginners Guide to Audio Sinclair £3.45

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00
Video Cookbook £7.00
TTL Cookbook £7.55
The Basic Cook £4.00 inc. p/p
IC Converter Cookbook £9.50

APPLICATIONS

Fire and Theft Security Systems B. Weis £2.15
How To Build Electronic Kits Capel £2.35
110 Electronic Alarm Projects R. M. Marston £3.95
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.95
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.95
110 Thyristor Projects Using SCRs R. M. Marston £3.95
110 Wave Form Generator Projects R. M. Marston £3.95

COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book £12.00
Beginners Guide to Computers and Microprocessors with Projects C. Adams £6.05
Basic Computer Games Ahl £5.40
Basic for Home Computers A self-teaching guide B. Albrecht £5.40
Illustrating Basic D. Alcock £3.00
Intro to Microprocessors Aspinall £6.55
Z-80 Microcomputer Handbook W. Barden £7.75
How to Program Microcomputers W. Barden £7.25
Introduction to Microcomputers and Microprocessors A. Barna £8.60
Microprocessors in Instruments and Control R. J. Bibbero £12.60
Basic Basic J. S. Coan £7.80
Advanced Basic J. S. Coan £7.30
Getting Acquainted with Microprocessors L. Frenzel £7.25
Beginners Guide to Microprocessors C. M. Gilmore £4.90
Beginners Guide to Home Computers Grossworth £4.50
Beginning Basic R. E. Gosling £4.75
Microprocessor Programming for Computer Hobbyists N. Graham £7.15
Miniprocessors from Calculators to Computers Heiserman £5.00
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.40
Basic Programming J. G. Kemeny £6.70
Microprocessor Systems Design E. Klingman £17.00
Intro to Microprocessors Leventhal £17.00
Microprocessors — Technology, Architecture & Applications D. R. McGlynn £9.20
Interactive Computing with Basic Monro £3.65
Basic with Style P. Nagin £4.25
Software Design for Microcomputers Ogden £7.20
Microcomputer Design Ogden £7.25
Microcomputer Base Design Peatman £5.70
Hands on Basic with a PET Peckham £9.00
Basic — A hands on method Peckham £6.95
6800 Software Gourmet Guide and Cookbook Scelbi £8.90
8080 Software Gourmet Guide and Cookbook £8.90
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.35
8080/8085 Software Design Titus £7.60
57 Practical Programs & Games in Basic Tracton £6.65
Microcomputer Primer M. Waite £6.50
Your Own Compuqer Waite £1.60
Microprocessor/Microprogramming Handbook Ward £6.20

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £5.35
Practical Digital Design Using ICs J. Greenfield £12.70
Designing With TTL Integrated Circuits Texas Instruments £9.35
How To Use IC Circuit Logic Elements J. Streeter £3.80
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.95
Understanding CMOS Integrated Circuits R. Melen £4.15
Digital Electronic Circuits and Systems R. M. Morris £3.65
MOS Digital ICs G. Flynn £5.25

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10
Working with the Oscilloscope A. Saunders £4.25
Servicing with the Oscilloscope A. King £6.65
Radio Television and Audio Test Instruments King £7.00

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.45
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £3.95
Designing With Operational Amplifiers Burr Brown £18.35
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.55
Op-Amp Circuit Design & Applications J. Carr £4.15

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.65
Digital Signal Processing Theory & Applications L. R. Rabiner £24.40
Electronic Communication Systems G. Kennedy £8.75
Frequency Synthesis. Theory & Design Mannassewitsch £23.80
Principles of Communication Systems H. Taub £8.40

THEORY

Introduction to Digital Filtering Bogner £10.60
Transistor Circuit Design Texas Instruments £9.75
Modern Electronic Maths Clifford £6.95
Foundations of Wireless Electronics M. G. Scroggie £5.25

REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner £34.50
Electronic Components M. A. Colwell £2.70
Electronic Diagrams M. A. Colwell £2.70
International Transistor Selector T. D. Towers New update £10.20
International FET Selector T. D. Towers £4.35
International Op-Amp Linear IC Selector Towers £7.65
Radio Valve and Semiconductor Data A. M. Bell £3.60
Radio, TV and Audio Technical Reference Amos £30.40

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair £3.55
Integrated Electronics J. Milman £8.20
Practical Solid State DC Supplies T. D. Towers £6.40
Practical Triac/SCR Projects for the Experimenter R. Fox £2.35
Printed Circuit Assembly Hughes & Colwell £2.70

Fallen behind recent advances?

Just starting out?


Need a decent reference book?

ETI Book Service provides an easy way of getting your hands on the right title.



WERSI

at AURA SOUNDS

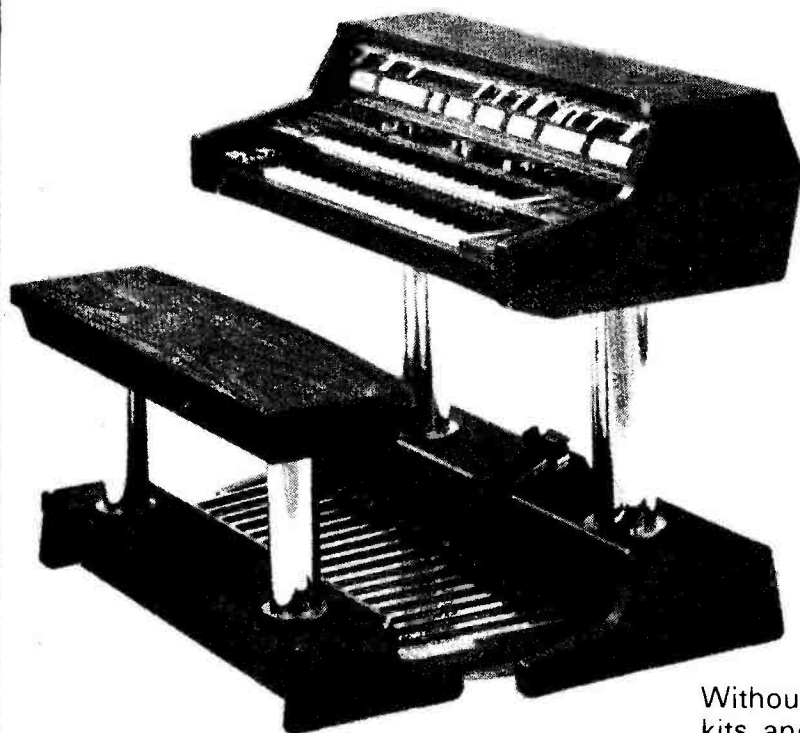

Tomorrow's Electronic Organ Kit is Here

POSSIBLY A NEW NAME TO YOU, BUT KNOWN IN OVER 25 COUNTRIES FOR THE SUPERIOR INSTRUMENTS WHICH THIS GERMAN COMPANY PRODUCE.

USED BY WEST GERMAN BROADCASTING SERVICE. PLAYED BY KLAUS WUNDERLICH AND OTHER FAMOUS ORGANISTS.

WERSI is the first kit producing company applying the latest achievements of the space age technology. This has decisive effects on the technical and musical quality of WERSI'S electronic organs for the do-it-yourselfer.

The application of modern integrated circuits, so called ICs, simplifies the organ construction considerably. A single IC may replace up to 10,000 conventional electronic components.

In addition, ICs save a lot of space and they are extremely reliable devices.

WERSI, however, went a step farther yet. IC's which were not available on the open market, were developed for specific purposes by WERSI engineering. They are being produced by the most highly reputed IC manufacturers in the world. The result: economical electronic organs with the most up-to-date techniques and unsurpassed musical capabilities.

Without doubt the most comprehensive kits and the most up-to-date designs available today. Just consider a few of the features:

- Precision Master Generator, using MOS-LS1.
- Integrated electronic keying in 1²L technology.
- Unique — All switch functions are programmable.
- Even the smallest organ has draw-bars in addition to fixed stops.
- Craftsman-made cabinets available in five veneers.
- Ready-made wiring harnesses eliminate errors.

WERSI MAKES DO-IT-YOURSELF CONSTRUCTION EASIER THAN EVER BEFORE AT A FRACTION OF THE PRICE OF THE FULLY ASSEMBLED WERSI RANGE. GET THE FACTS NOW.

AURA SOUNDS 14-15 Royal Oak Centre, Brighton Rd., Purley, Surrey. Tel: 01-668-9733
and at 17 Upper Charter Arcade, Barnsley, W. Yorks Tel: Barnsley (0226) 5248.



**Send now
for the
104 page
full-colour
catalogue.**

Please send me the full colour WERSI catalogue, price lists and supporting literature (weighing 1 lb!) I enclose a cheque/p.o. for £1.00.

Name

Address

Send to Aura Sounds (PE1) 14/15 Royal Oak Centre, Brighton Rd., Purley, Surrey.

LED VU METER

An excellent way to watch what goes on in those secretive screened leads. Can be adapted to various levels of operation.

This unit will not replace the conventional VU or PPM meter; no LED display could fulfill the spec. However, with an output in 3 dB steps and a choice of a dot or bar display, it will make a useful and attractive addition to any audio system.


5 Into 1 = 10

With the log function achieved directly inside IC5, the use of four separate op-amps to condition the signal may seem extravagant. However, the circuit design precludes the use of a conventional quad op amp package like the 324 and the final circuit exploits the good, all-round, economical performance of the 741s and the extremely high input impedance of the 3140s. The display consists of ten LEDs and these can be illuminated in a dot or bar format. Selection is by a SPDT switch, or a wire link may be permanently connected. Sensitivity of the unit is high. The gain of the first amplifier stage is adjustable and a full scale reading can be obtained with an output of just a few millivolts.

To keep down cost and avoid complex circuitry, a half-wave rectifier has been used. The meter has switchable resistors giving a peak programme response with fast attack and slow decay and a volume unit response with slower approximately equal response times. The response characteristics for each mode may easily be changed by selection of a few resistors and have little interaction with each other.

Construction And Setting Up

Use of our PCB makes construction simplicity itself and results in quite a compact and attractive unit. The PCB has been designed to accommodate stackable rectangular LEDs as shown in our photos. However, any type and colour of LEDs may be used. There are only four wire links to be inserted and the remaining components may be inserted as they come to hand. It is good practice to leave the semiconductors until last and use of sockets for the ICs makes substitution for fault-finding easy. Although ICs 3 and 4 feature FET input

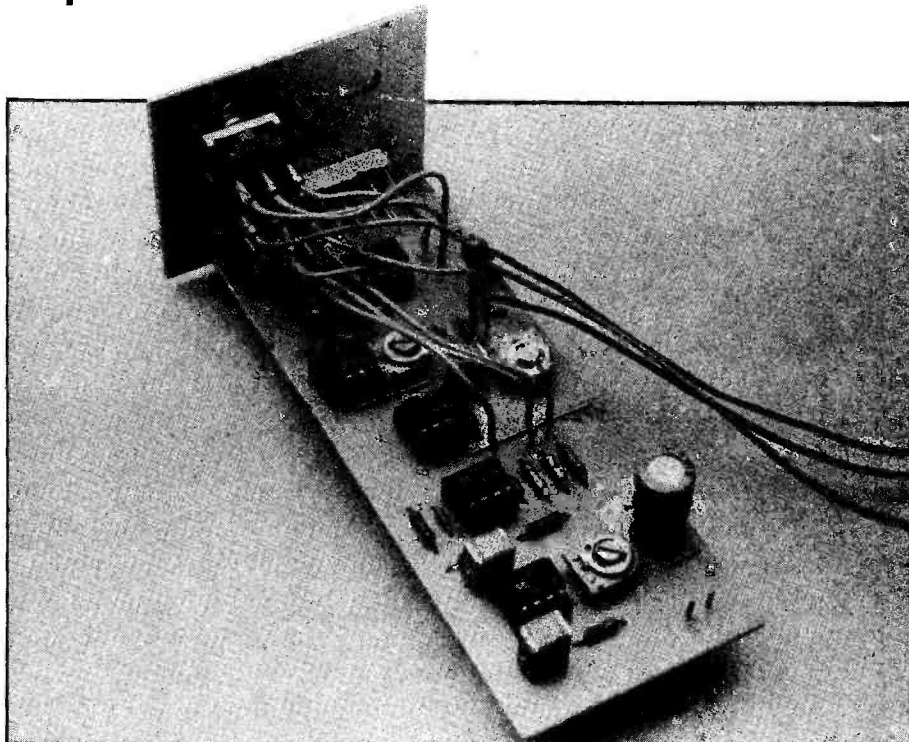

stages, these are well protected and no special handling precautions are required.

When completed, the unit may be set up by short-circuiting the input and, with a DC-coupled scope or sensitive voltmeter connected to the output (pin 6) of IC4, adjusting RV2 until the output reaches 0 V. Then apply the maximum signal you wish to indicate and with the unit set to VU adjust RV1 for a full scale reading. Now switch to PPM and adjust RV3 until a full scale reading is just obtained. The unit will cover a wide range of input levels, though for very high input signal levels you may have to attenuate the driving signal. A simple resistive divider will easily accomplish this. Do yourself a favour and have a peak at better VU today.

BUYLINES

The 3915 is available from Technomatic. Stackable rectangular LEDs are available from Watford Electronics. The other components should be readily obtainable.

PARTS LIST

RESISTORS All 1/4W 5%	
R1,10	100k
R2,3,4	10k
R5	2M
R6	10M
R7,9	22k
R8	47k
R11	1k
POTENTIOMETERS	
RV1	10k min turn, preset
RV2,3	100k min turn, preset
CAPACITORS	
C1,2	470n polycarbonate
C3	100u electrolytic
C4	100n polycarbonate
C5,6	10k tantalum
SEMICONDUCTORS	
IC1,2	741
IC3,4	3140
IC5	LM3915
D1,2	1N4148
LEDs	any LED
MISCELLANEOUS	
PCB, DPDT switch, SPDT switch, connectors, etc.	

A power supply of plus and minus six volts is recommended. A lower voltage may restrict the output swing of IC4 making a full scale reading unobtainable in the 'PPM' mode. Too high a positive supply may result in destruction of IC5 through excessive dissipation. Absolute maximum dissipation for this chip is 660 mW. If you use a positive supply greater than 6 V then the LEDs should be returned to the positive supply via a dropper resistor or a zener diode. IC5 produces either a 'dot' or 'bar' display depending on the connection of pin 9 to pin 11 or to the positive supply. Although SW2 is shown on the circuit diagram, the connection may be made permanently with a wire link.

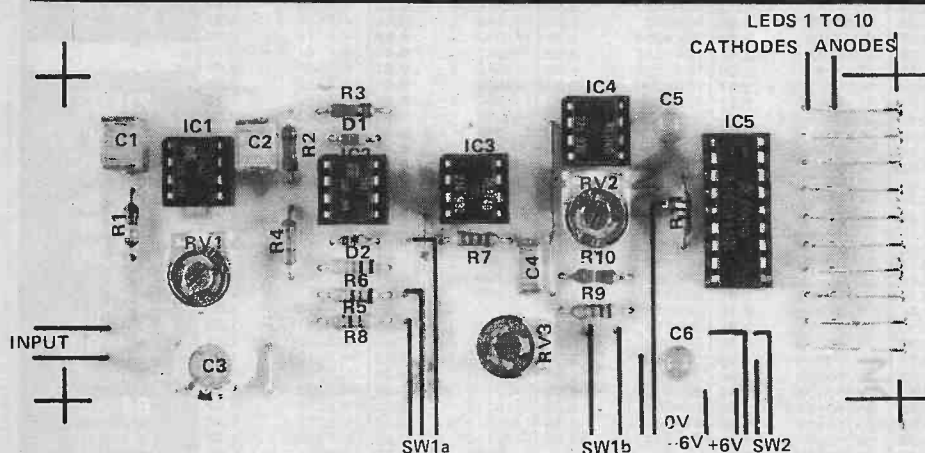


Fig.2. Component overlay. The rectangular LEDs are all mounted along the right edge of the board.




Use of stackable LEDs makes for an attractive panel layout.

CHROMASONIC electronics

56 FORTIS GREEN ROAD MUSWELL HILL LONDON N10 3HN
TELEPHONE 01-883 3705 01-883 2289

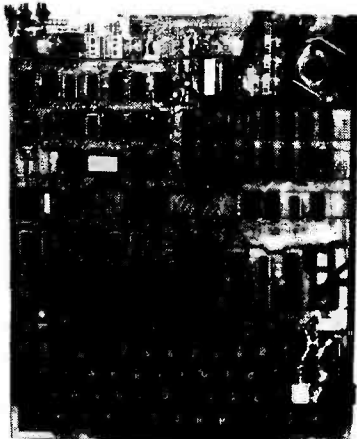your soundest connection in the world of components



Demonstration At Our Shop
(enter through stationers)

NOW AVAILABLE
Low cost computer in kit form

UK101

**NO EXTRAS NEEDED
SIMPLY HIT
'RETURN' AND GO**

As seen in
P.E.
August to November '79

Kit price
only **£199 + VAT**

AVAILABLE SOON

COLOUR ADD-ON CARD

Enables you to choose your foreground, the background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form. Phone for details.

STOP PRESS

The latest edition of our 'STOP PRESS' is now available, and contains an up-to-date price list showing all the items that we stock. Just send an S.A.E. or phone for your FREE copy.

**EXTRA
4K MEMORY
8x2114
ONLY
£32 + VAT**

INCLUDED FREE
Sample tape with extended
machine code monitor and
disassembler

Price includes RF modulator and
power supply
**ABSOLUTELY NO EXTRAS
NEEDED**

Also available ready assembled,
tested and ready to go
only **£249 + VAT**

Build, understand, and
program your own
computer for only a
small outlay

**NOW
AVAILABLE
CASE
£17.50**


Dynamic RAMS		Interface		PLUS Superboard II only £188 + VAT		LS series		74LS125		74LS279					
4027	3.01	8205	3.00	CA3046	0.65	LM3065N	1.50	SN76660N	0.75	74LS00	0.18	74LS126	0.36	74LS283	0.57
4050 (200ns)	2.50	8212	2.00	CA3053	0.72	LM3900N	0.50	SN76666N	0.75	74LS01	0.18	74LS132	0.38	74LS289	1.09
4050 (350ns)	2.35	8216	2.08	CA3075	2.00	LM3905N	1.00	TAA263	2.20	74LS02	0.18	74LS133	0.60	74LS293	4.50
4060 (300ns)	2.39	8224	2.77	CA3080	0.67	LM3909N	0.68	TAA320A	0.50	74LS03	0.18	74LS136	0.39	74LS290	0.91
4116	5.76	8228	4.13	CA3080E	0.67	LM3911N	1.10	TBA120S	0.70	74LS04	0.19	74LS138	0.38	74LS293	0.91
Static RAMS		8251	5.00	CA3081	1.30	M252 B1 AA	7.50	TBA231	1.00	74LS05	0.20	74LS139	0.85	74LS295	1.30
2102A	1.16	8253	6.93	CA3082	1.30	M253 B1 AA	7.50	TBA520Q	1.00	74LS08	0.22	74LS145	0.85	74LS298	1.16
2102A-2	1.16	8255	4.95	CA3086	0.45	M255 B1 AA	7.95	TBA540Q	1.00	74LS09	0.20	74LS151	0.87	74LS348	1.39
2111A-1	1.70	Baud Rate		CA3089	1.76	MC1310P	1.00	TBA530Q	1.50	74LS10	0.20	74LS153	0.81	74LS352	1.04
2112A-2	2.35	Generators		CA3090Q	3.95	MC1312P	1.85	TBA550Q	1.50	74LS11	0.20	74LS154	0.52	74LS353	0.92
21102	0.98	MC14411	5.87	CA3097E	1.85	MC1314P	3.35	TBA560Q	1.50	74LS12	0.18	74LS155	1.30	74LS362	4.21
2114	4.50	MM5307	9.38	CA3123E	1.70	MC1315P	5.50	TBA651	1.80	74LS13	0.37	74LS156	0.72	74LS365	0.47
4035 (1000ns)	1.07	UARTS		CA3130E	0.85	MC1327P	0.95	TBA750Q	1.80	74LS14	0.65	74LS157	0.72	74LS366	0.47
4045 (250ns)	6.15	AY-5-1013	3.90	CA3140E	0.36	MC1330P	1.00	TBA800	2.64	74LS15	0.18	74LS158	0.57	74LS367	0.47
5257 (TMS4044)	6.93	MM5303	5.04	CA3160E	1.00	MC1350P	1.20	TBA810S	0.83	74LS20	0.18	74LS160	1.09	74LS373	0.78
6810	3.48	TMS6011NC	3.55	ICL8038BC	8.82	MC1351P	1.20	TBA810AS	1.24	74LS22	0.18	74LS161	0.69	74LS386	0.36
ROMS		2708 only £5.75 + VAT		ICL8038CC	3.40	MC1352P	1.35	TBA820Q	1.00	74LS26	0.18	74LS162	1.16	74LS393	0.84
2513 (U.C.)	6.25	Integrated Circuits		ITT7120	1.90	MC1375P	1.73	TBA920Q	0.76	74LS27	0.18	74LS163	0.89	74LS668	1.17
2513 (L.C.)	6.25	703 (8 pin)	0.95	LM307H	0.66	MC1445L	2.95	TBA990Q	1.50	74LS28	0.18	74LS164	1.06	74LS670	1.71
CPU		709 (8 pin)	0.35	LM307N	0.43	MC1456CG	1.75	TCA270Q	1.00	74LS29	0.18	74LS165	0.72	8 x 4116 only £40.00 + VAT	
6800	5.90	709 (14 pin)	0.38	LM308N	0.95	MC1458CP1	0.45	TCA730	3.97	74LS30	0.18	74LS166	1.65		
8080	4.95	709 (T099)	0.45	LM318N	1.95	MC1495L	5.98	TCA740	3.97	74LS32	0.26	74LS168	1.71		
9900	26.05	710 (8 pin)	0.36	LM319H	2.25	MC1496P	0.65	TDA1054	1.20	74LS33	0.26	74LS169	1.71		
Z80	9.00	710 (14 pin)	0.38	LM322N	3.87	MC3302P	0.65	TDA1327	2.48	74LS37	0.39	74LS170	1.72	21L02 8 for £7.00	
6502	9.50	710 (T099)	0.45	LM324N	0.50	NE531N	1.00	TDA1352	1.35	74LS38	0.23	74LS173	0.81		
E-PROMS		711 (8 pin)	0.36	LM339N	0.50	NE540L	2.97	TDA2020	3.20	74LS40	0.18	74LS174	0.97		
1702AQ	5.16	711 (14 pin)	0.40	LM348N	0.90	NE555N	0.22	TL072CP	0.95	74LS42	0.65	74LS175	0.97		
2708	5.75	711 (T099)	0.87	LM370N	2.90	NE556N	0.60	TL074CN	1.50	74LS47	0.81	74LS181	2.77	16 for £13.00	
2716	17.50	711 (14 pin)	0.87	LM371H	2.05	NE556N	0.60	TL081CP	0.95	74LS48	0.81	74LS188	0.44		
T.V. Controller		739 (14 pin)	1.80	LM373N	2.90	NE556N	0.60	TL082CP	0.95	74LS49	0.81	74LS189	2.08		
SFF96364	10.50	741 (8 pin)	0.18	LM377N	2.90	NE565N	1.10	TL084CN	1.05	74LS51	0.18	74LS190	0.86		
Buffers		741 (14 pin)	0.35	LM378N	1.75	NE566N	1.35	UAA170	1.98	74LS54	0.18	74LS191	0.86	32 for £25.00	
74365	0.52	741 (T099)	0.42	LM379S	2.05	NE567N	1.35	UAA180	1.98	74LS55	0.18	74LS192	1.04		
74366	0.52	747 (14 pin)	0.70	LM380N	0.85	SAA1024	3.40	ZN404	0.80	74LS57	0.33	74LS193	1.04		
74367	0.52	748 (8 pin)	0.33	LM380N8	0.75	SAA1025	4.85	ZN414	0.80	74LS74	0.30	74LS194	0.86		
74368	0.52	748 (14 pin)	0.45	LM381N	1.45	SL414A	1.90	ZN417E	1.90	74LS75	0.40	74LS195	0.97	64 for £45.00 All excluding VAT	
81LS95	1.25	748 (T099)	0.48	LM381AN	2.50	SD6000V	2.90	ZN423T	1.05	74LS76	0.27	74LS196	0.97		
81LS96	1.25	753 (8 pin)	1.50	LM382N	1.20	SN75491N	0.85	ZN424E	1.15	74LS78	0.78	74LS197	0.97		
81LS97	1.25	AY-10212	5.80	LM386N	0.78	SN75492N	0.75	ZN425E	0.80	74LS83	0.78	74LS221	0.92		
81LS98	1.25	AY-1-5050	1.90	LM387N	0.95	SN76001N	0.95	ZN426P	0.80	74LS85	0.81	74LS240	2.08	All prices are EXCLUSIVE of VAT. Postage and packing 30p (computers charged at cost). CALLERS WELCOME. Hours 9.00 am-6.00 pm (enter through stationers). TRADE and EXPORT inquiries welcome. Phone your orders through our ORDER-RING line quoting your Access or Barclaycard number (Min. tel order £5).	
8T26	1.90	AY-1-5051	1.45	LM388N	0.95	SN76003N	1.98	ZN458A	1.35	74LS86	0.27	74LS241	2.08		
8T28	1.90	AY-16721 / 6	1.95	LM389N	0.95	SN76008K	1.60	ZN459CP	2.73	74LS88	0.57	74LS242	2.08		
8T29	1.57	AY-3-8500	5.00	LM390N	0.95	SN76013N	1.40	ZN1034E	1.90	74LS90	0.97	74LS243	2.08		
8T96	1.57	AY-5-1224	2.40	LM397N	0.95	SN76018K	1.40	ZN1040E	1.90	74LS91	0.69	74LS245	2.50		
8T97	1.57	AY-5-3507	4.15	LM398N	0.95	SN76023N	1.40	ZN1066E	5.85	74LS92	0.60	74LS247	1.09		
8T98	1.57	AY-5-4007	6.30	LM399N	0.95	SN76028K	1.50	ZN116E	4.95	74LS93	0.60	74LS248	1.09		
8T99	1.57	CA3036	1.10	LM399N8	0.95	SN76033N	1.30	ZN134J	26.95	74LS95	1.16	74LS249	1.09		
8T98	1.57	CA3045F	1.40	LM1820N	1.00	SN76532N	2.00			74LS96	0.32	74LS251	0.96		
				LM1830N	1.98	SN76544N	1.25			74LS107	0.32	74LS253	0.92		
										74LS109	0.32	74LS257	0.92		
										74LS112	0.32	74LS258	0.92		
										74LS113	0.32	74LS259	1.39		
										74LS114	0.32	74LS261	4.50		
										74LS122	0.69	74LS266	0.37		
										74LS123	0.72	74LS273	1.70		
										74LS124	1.39				

All prices are EXCLUSIVE of VAT. Postage and packing 30p (computers charged at cost). CALLERS WELCOME. Hours 9.00 am-6.00 pm (enter through stationers). TRADE and EXPORT inquiries welcome. Phone your orders through our ORDER-RING line quoting your Access or Barclaycard number (Min. tel order £5).

L.C.D.

DIGITAL

STOPWATCH

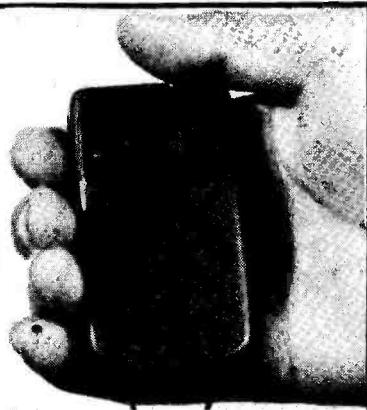

At last a hand-held digital LCD stopwatch at a realistic price. Times to maximum of one hour in 1/100ths seconds with one shot, sequential, lap and 'Taylor' functions. Also displays real time in hours, minutes and seconds with day and date. Thousands of these watches have been purchased by laboratory workers throughout the UK. Now available for Athletes, Sportsmen, Joggers, Sailors, Astronomers, Doctors, Nurses, Hobbyists, etc., etc.

Only 40 x 80 x 50mm and weighing little more than one ounce the watch comes complete with batteries, internal light, lanyard, instructions and one year's no quibble guarantee.

Price £18.20


including VAT & Postage. Cash with order, from:

NORTHERN TECHNICAL AND CHEMICAL SERVICES (Dept. ETI)

331 East Prescott Road, Liverpool L14 2DD

Tel: 051-228 4690

Trade and Export enquiries welcomed

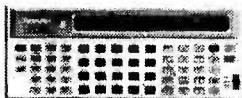

NEW, SHARP Lcd, 61 function, 15 level parenthesis.

EL5101 16 Digit, 48 step, 1+5 mem.

£46.95

EL5100 24 Digit, 80 step, 1+5+10 mem.

£56.95



CASIO FX 501/502P PROGRAMMABLE Lcd
(Featured Feb. ETI)

FX 501P 10+2 digit, 128 step, 11 memories £49.95

FX 502P 10+2 digit, 256 step, 22 memories £69.95

FA1 Adaptor cassette interface £19.95

MASTERPACK 150+ programmes on tape with manual £15.95

FX501P+FA1+Masterpack £78.95

FX 502P+FA1+Masterpack £98.95



CASIO 48 Function Lcd

FX310 8-digit £16.95

FX510 10-digit £18.95



CASIO 41 Function Lcd

Super Slim

FX2600 8 digit £18.95

FX3200 10 digit £20.95



CASIO FX 5000 Lcd

48 Function 10+2 digit, 10

memories £27.95



CASIO FX 8000 Lcd

41 function 8 digit stopwatch

with lap, multi-timer and alarms,

10+2 digit £29.95

CASIO FX81 Lcd updated FX80, 37 function, 8-digit, £15.95

CASIO FX68 Lcd, small 38 function, 8 digit £18.95

CASIO HR 10 Lcd, mini printer with calendar £28.95

CASIO MELODY B1 musical watch, calendar, 2 alarm, timer £21.95

CASIO AQ 2000 watch, calendar, 2 alarm, timer £23.95

TEXAS PROGRAMMABLES

*TI 58 172 function 480 step, 60 memories £66.95

*TI 58C above plus constant programme and memory retention £83.95

*TI 59 177 function card programmable 960 step, 100 mem. £172.95

PC 100C Printer cradle for TI 58/58C/59 £156.95

T159 + PC100C £321.95

Programme Libraries Maths/Stats/Electrical/Business each £23.95

TEXAS Scientific TI125 or TI 35 Lcd £19.95

*Includes Adaptor/Charger.

*** PRICES INCLUDE POST, PACKING AND 15% VAT ***
Full range of CASIO, TEXAS and SHARP AVAILABLE

**CALCULATOR SALES & SERVICE, ARROW WORKS, ARROW ROAD
REDDITCH B98 8NN. Tel: REDDITCH (0527) 43169**
Callers by appointment only please



All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation is even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE SE VERYTHING NEEDED

Die pressed case. Ready drilled, aluminium extruded base and heat sink. coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

**Electronics Design Associates, Dept. ETI/5
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791**

Name _____

Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD

I enclose cheque/PD's for

X5KIT £16.95

ACCESS OR BARCLAY CARD No. _____

£
Cheque No. _____

Send SAE if brochure only required.

DESIGNER'S NOTEBOOK

Ray Marston devotes this month's 'Notebook' to an in-depth look at the Siemens IR60 system that forms the basis of the infra-red remote control system described in this issue.

The infra-red remote control project is based on the Siemens IR60 system that is copiously described in Siemens data books and applications notes. Now, the uninitiated amongst you might think that the ETI design team deserves absolutely no credit for merely converting an application note into a real-life project. Those professional design engineers amongst you who are familiar with so-called 'Applications Notes' may, however, well feel otherwise. Let me explain.

Application Notes

One of the most important lessons that the aspiring design engineer must learn is that manufacturer's data and application notes must **never** be regarded as sources of pure facts. In reality, they are simply propaganda sheets that are designed, within legal constraints, to help boost the sales of the manufacturer's products. They are designed to emphasise the good features of the product by play down or ignore its deficiencies.

Data/application sheets vary considerably in quality from one manufacturer to another. One of the major American companies, for example, produces notes with excellent descriptive texts, but 30% of their application circuits don't (and could never) work. Japanese notes come in pidgin English interspersed with Croatian technical terms.

The upshot of all this is that when we tried to use the Siemens IR60 system we first had to spend three days decyphering the text and then spent another six days (literally) debugging the system. Still, enough of this waffle: The IR60 system is very good, so let's look at it.

The IR60 System

IR60 is a sophisticated infra-red remote control system that is capable of handling sixty code instructions (in practice 30 of these instructions are not decoded by the system's receiver but are read out on a serial interface, from which they can be fed to auxiliary decoder circuitry). The system is designed around two 18-pin P-MOS LSI packages and has exceptionally high immunity to false operation through noise, etc. The manufacturer claims system operating ranges of 30 - 40 metres. The receiver has three analogue outputs, one 4-bit (16 channel) binary output, three single-bit outputs and a serial interface for additional versatility.

The system is specifically designed to give remote control of

INST NO.	KEY CODE	SERIAL CODE FED CBA	FUNCTION	RECEIVER OUTPUT ACTION
0	1a	000 000	NORMAL POSITION/ON.	Volume sets to 1/3, Analogue 1 and 2 set to 1/2. RLA on. Volume reduces rapidly to zero.
1	1b	001 001	QUICKTONE	Turns RLA off.
2	1c	010 010	STANDBY	Switches RSV1 output between high and low states on alternate operations.
3	1d	011 011	RESERVE 1	Increments binary channel-select output by one step per operation: Turns RLA on.
4	2a	100	PROGRAM STEP +/ON	Decrements binary channel-select output by one step per operation: turns RLA on.
5	2b	101	PROGRAM STEP -/ON	Turns RLA on.
6	2c	110	ON	Switches RSV2 output between high and low states on alternate operations.
7	2d	111	RESERVE 2 /ON	Turns RLA on.
8	3a	001 000		Not evaluated by SAB3209 receiver, but read out at serial interface.
9	3b	001 001		
10	3c	010 010		
11	3d	011 011		
12	4a	100		
13	4b	101		
14	4c	110		
15	4d	111		
16	5a	010 000	CHANNEL 1 / ON	Sets binary output to 0000: Turns RLA on.
17	5b	001 001	CHANNEL 2 / ON	Sets binary output to 0001: Turns RLA on.
18	5c	010 010	CHANNEL 3 / ON	Sets binary output to 0010: Turns RLA on.
19	5d	011 011	CHANNEL 4 / ON	Sets binary output to 0011: Turns RLA on.
20	6a	100	CHANNEL 5 / ON	Sets binary output to 0100: Turns RLA on.
21	6b	101	CHANNEL 6 / ON	Sets binary output to 0101: Turns RLA on.
22	6c	110	CHANNEL 7 / ON	Sets binary output to 0110: Turns RLA on.
23	6d	111	CHANNEL 8 / ON	Sets binary output to 0111: Turns RLA on.
24	7a	011 000	CHANNEL 9 / ON	Sets binary output to 1000: Turns RLA on.
25	7b	001 001	CHANNEL 10 / ON	Sets binary output to 1001: Turns RLA on.
26	7c	010 010	CHANNEL 11 / ON	Sets binary output to 1010: Turns RLA on.
27	7d	011 011	CHANNEL 12 / ON	Sets binary output to 1011: Turns RLA on.
28	8a	100	CHANNEL 13 / ON	Sets binary output to 1100: Turns RLA on.
29	8b	101	CHANNEL 14 / ON	Sets binary output to 1101: Turns RLA on.
30	8c	110	CHANNEL 15 / ON	Sets binary output to 1110: Turns RLA on.
31	8d	111	CHANNEL 16 / ON	Sets binary output to 1111: Turns RLA on.

Table 1. Relationships between transmitter key codes and receiver actions on basic instructions.

modern TV sets but can in practice be used to control a whole range of domestic and industrial devices. The infra-red remote control system featured in this month's issue of ETI is based on the IR60 system, but uses only 16 of the 60 available instructions and has an effective range of only (!) 15 metres.

The essence of the action is that the SAB 3210 transmitter chip receives input 'instructions' via an 8-row (1 to 8) by 4-column (a to d) matrix that can be activated by key switches. Each key can thus be allocated an instruction number, which in turn is related to a key code number (2d, 8a, etc). Whenever a key is operated the IC detects the action and generates a start-bit plus 6-bit serial code word which is transmitted to the receiver via the infra-red link, where the word may or may not be decoded may or may not cause some useful action to be performed.

The transmitter can produce 32 basic code words using 1-row/1-column key combinations, plus another 32 extension words

INST NO.	KEY CODE	SERIAL CODE FED CBA	FUNCTION	RECEIVER OUTPUT ACTION
32	81a	100 000		
33	81b	001		
34	81c	010		
35	81d	011		
36	82a	100		
37	82b	101		
38	82c	110		
39	82d	111		
40	83a	101 000	VOLUME +	Increases volume output level.
41	83b	001	VOLUME -	Decreases volume output level.
42	83c	010	ANALOGUE 1 +	Increases analogue 1 output level.
43	83d	011	ANALOGUE 1 -	Decreases analogue 1 output level.
44	84a	100	ANALOGUE 2 +	Increases analogue 2 output level.
45	84b	101	ANALOGUE 2 -	Decreases analogue 2 output level.
46	84c	110	ANALOGUE 3 +	
47	84d	111	ANALOGUE 3 -	
48	85a	110 000		
49	85b	001		
50	85c	010		
51	85d	011		
52	86a	100		
53	86b	101		
54	86c	110		
55	86d	111		
56	87a	111 000		
57	87b	001		
58	87c	010		
59	87d	011		
60		100		Not used.
61		101		Not used.
62		110		END instruction.
63		111		Not permitted, due to ambiguity in biphasic code.

Table 2. Relationships between transmitter key codes and receiver actions on Extension instructions.

when using a 2-row/1-column key combinations in which '8' always forms one of the two rows. For the benefit of those readers who may wish to modify the ETI system, the relationships between instruction numbers, key codes, transmitter codes and receiver output functions are shown in Table 1 for the basic codes and in Table 2 for the Extension codes.

Transmitter Connections

The method of connecting keys to the SAB 3210 for the 32 basic codes is quite straightforward, as shown in the manufacturer's basic application circuit of Fig. 1. Use of the extension instructions calls for a slightly more complex approach, with pairs of diodes connecting row-8 and one other row to one of the four columns so that actuation of a key connects two rows to one column. Fig. 2 shows the manufacturer's diagram for making a 60 key matrix, using both basic and extension connections.

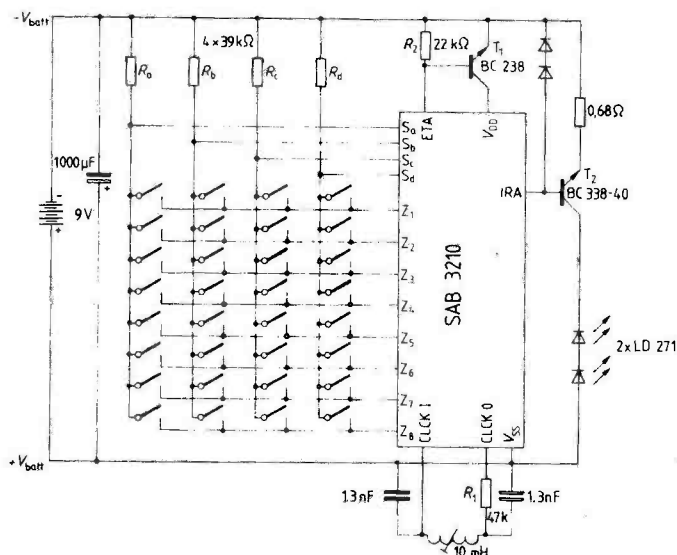


Fig. 1. Manufacturer's application circuit, showing method of connecting keys for the 32 basic codes.

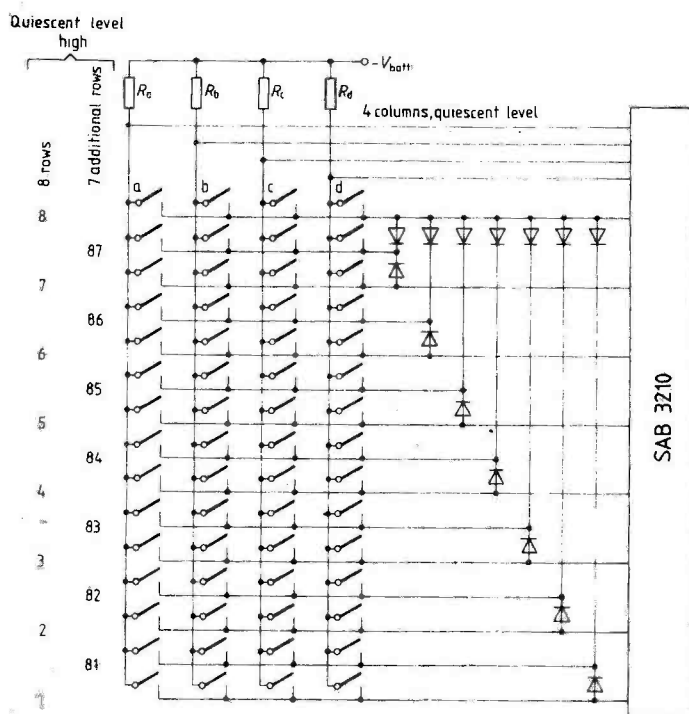


Fig. 2. Manufacturer's diagram showing connections for a 60-key matrix using both basic and extension instructions.

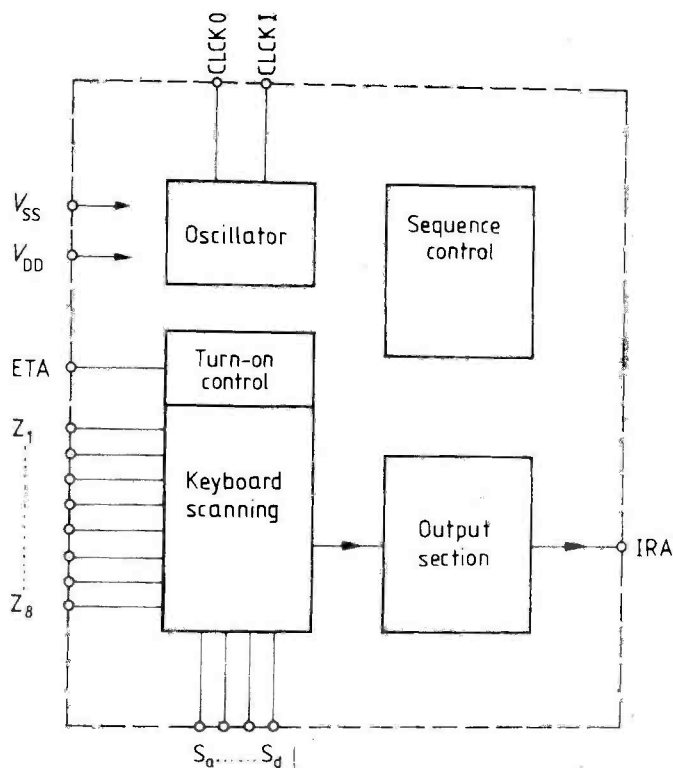


Fig. 3. Block diagram (left) and pin notations (right) of the SAB3210 transmitter IC.

Fig. 3 shows the pin connections and the simplified block diagram of the SAB 3210 IC, which incorporates (amongst other things) a keyboard scanner circuit. When we were developing our

prototype unit on Microdeck we found that the deck's intercapacitance between pin 16 (the '8' row) and ground caused the scanner to 'see' the '8' row as a closed switch whenever the transmitter was activated, thus causing the incorrect code to be transmitted when basic operation was required (it took us two days to discover the cause of the incorrect operation). We overcame this bug by trying pin 16 of the IC high with a 220k resistor: for good measure, we tied pins 11 and 12 (rows 3 and 4) high as well.

One reason it took us so long to trace this fault was because of the unusual nature of the Biphase serial code sent out by the transmitter. Fig. 4 is a reproduction of the manufacturer's timing/waveform diagram. What happens here is that the transmitted signal carries 'imaginary' markers: a pulse immediately following the marker is regarded as a '1'. Thus, the biphase signal shown in Fig. 4 is, reading from F to A, equal to 100 110.

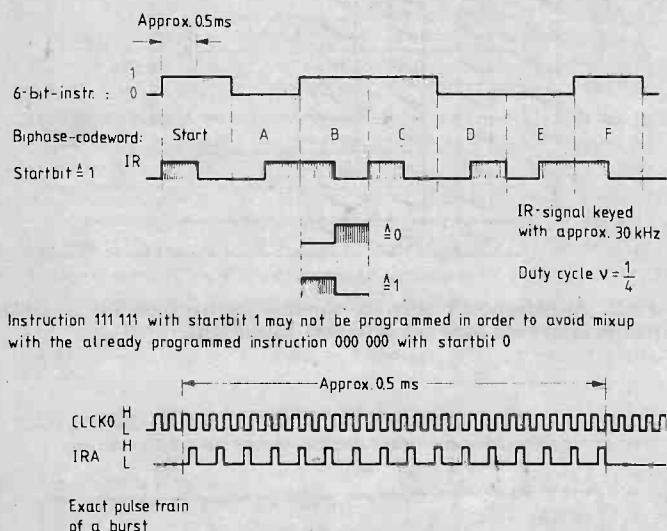


Fig.4. Reproduction of the manufacturer's transmitter timing/waveform diagram.

The Receiver Pre-Amplifier

The manufacturer produces a special pre-amplifier chip, the TDA 4050, for use with the IR60 system. Using this chip, they claim control ranges of up to 30 - 40 metres. We played with his chip for a couple of days but never managed to stop the damn thing oscillating. We then noticed the small print in the application data that said that the pre-amplifier 'should advantageously be mounted in a double-screened case', at which point we gave up and designed our own pre-amp.

One of the problems involved in IR pre-amp design is that the circuit must not only provide very high gain for long-range operation, but also must not saturate when the transmitter is placed only a few inches from the receiver. Our unit works well in both respects.

As a matter of general interest, we've reproduced the manufacturer's TDA 4050 pre-amp applications circuits in Fig. 5. The TDA 4050 IC should be available from Electrovalue.

Receiver/Decoder Circuits

The basic IR60 system is designed for use with the highly sophisticated SAB 3209 receiver IC. This chip checks the incoming code signal for 'sense' (number of bits, bit duration, etc), processes it and then both 'dumps' the resulting code signal at the serial interface and simultaneously passes it on to a register, from which it is

then used to control the binary and analogue outputs. The processing action gives a very high immunity against noise and against signals of the wrong carrier frequency.

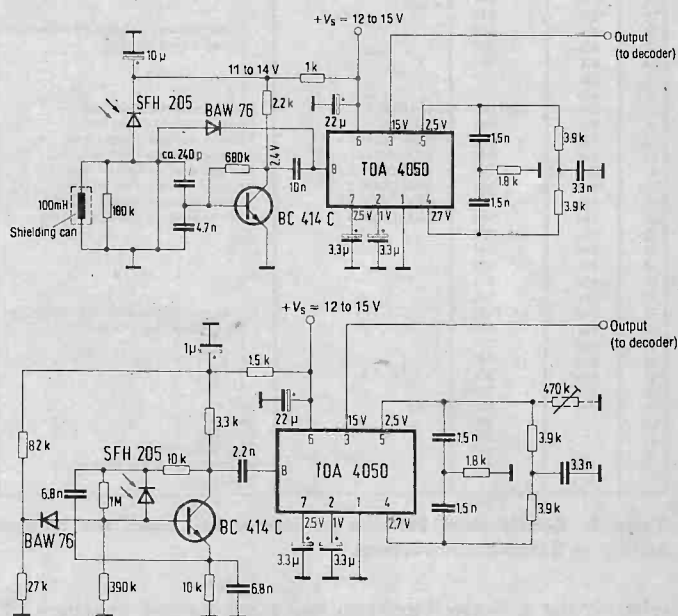


Fig.5. Two Siemens applications circuits showing methods of using the TDA4050 IR preamplifier IC.

Fig. 6 shows the pin designations of the SAB 3209 receiver IC, which provides three analogue, one 4-bit binary and three single-bit outputs. Siemens make a similar receiver chip, the SAB 4209, which has four analogue outputs: this chip is unlikely to be available through amateur electronics dealers, but could be of interest to those of our readers who are professional design engineers.

Pin connection

Pin No.	Pin designations
1	V _{SS} , supply voltage +12 V
2	CLKO, clock output
3	CLKI, clock input
4	PRGD, program control output
5	PRGC, program control output
6	PRGB, program control output
7	PRGA, program control output
8	PC, program change strobe input/output
9	RSV2, spare output
10	RSV1, spare output
11	VOLU, volume control output
12	ONOFF, standby output
13	BRIG, brightness output
14	COLO, color contrast output
15	RSIG, signal input, remote control
16	DLEN, I-bus input/output
17	V _{DD} , supply voltage 0 V
18	DATA, I-bus input/output

Fig.6. Pin designations of the SAB3209 receiver IC.

Siemens produce a number of 'special' (professional) support chips for use with the IR60 system. Fig 7, for example, shows the standard receiver application circuit, which also illustrates the use of the SAB 3211 display decoder/driver chip, which gives a visual readout of the selected binary-coded 'channel' number on a multi-segment LED display.

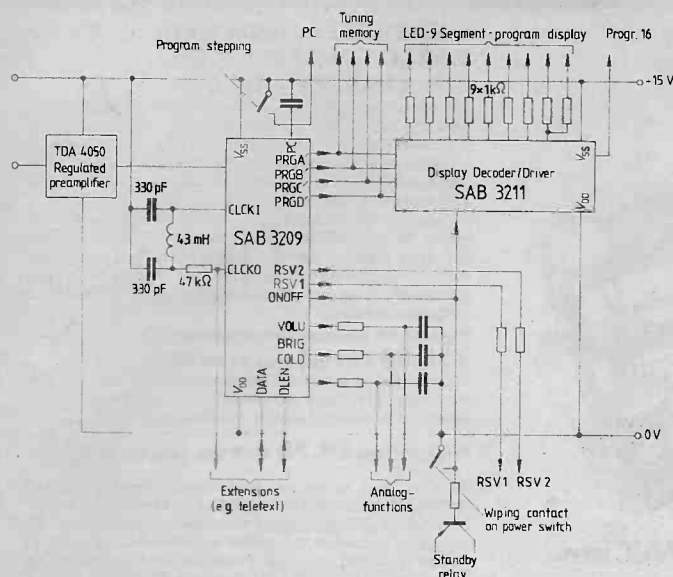


Fig.7. Siemens SAB3209 receiver application circuit, which also shows the use of the 'special' SAB3211 chip.

Another 'special' IC is the SAB 3271 receiver chip, which specifically decodes the transmitted 6-bit serial instruction code signal into the form of six parallel outputs, which can be decoded by additional circuitry to make all 60 'instructions' available for external use.

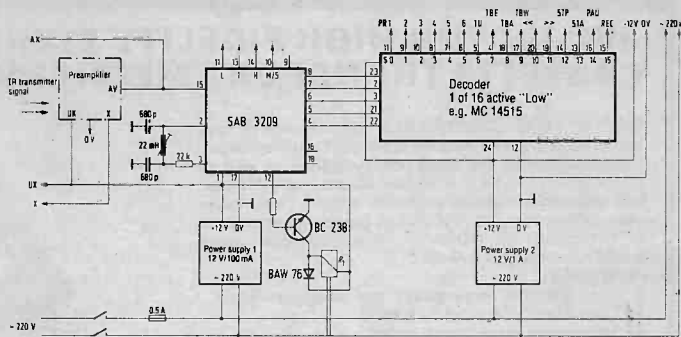


Fig.8. Siemens circuit showing the method of decoding the 4-bit binary output to give 16 output channels.

Interface Circuits

Interfacing the outputs of the SAB 3209 receiver to external circuitry calls for a certain amount of individual ingenuity. The signal-bit outputs can each be used to drive a relay via a transistor buffer, as already shown in the ETI remote control system elsewhere in this issue. The 4-bit binary output can be decoded into sixteen 'selector' channels by using the Siemens circuit as shown in Fig. 8. ICs such as the CD4066 can be used as on/off signal switches, driven from the outputs of the above channel selector.

The three analogue output channels can be used to control voltage-controlled attenuators or amplifiers (for volume control) and filters (for tone control, etc) by using some of the many circuits shown in previous issues of ETI. The VCA article shown in the March '80 issue gives some useful circuits.

ETI

Superboard II

At these prices why waste time and money on unauthorised kit copies? Just a little more in price than Sinclair for a whole lot more and fully expandable!

610 Expansion Board 8k RAM
ONLY £159.95 + VAT
IP CD3P Minifloppy Disc, Cased,
PSU, 2 copies Dos ONLY £289+VAT
Set of 4k RAM (Superboard users
only) ONLY £30 + VAT
Plastic Case, Beige ONLY £26+VAT
Challenger IP-Metal Cased, Super-
board, PSU modulator ONLY £220 +VAT

NOW
£159.95

NOW ON SHOW
IN THE
SCIENCE MUSEUM

Super Print 800

80 COLUMN HIGH
PERFORMANCE IMPACT PRINTER

The ideal companion for PET, APPLE, TSR80,
Exidy, Superboard, Compukit, Ohio
Challengers and most micro's

Rugged metal enclosure makes it ideal
for home computing, small business
systems, data logging etc.

*RS-232, 20mA, IEEE 488 and Centronics I/O
*16 Baud Rates to 19,200
*60 Lines per minute - Bidirectional
*5 print densities 72,80,96,120 or 132 Chr/Line
*Self Test Switch
*Tractor and Fast Paper Feed/Graphics

NEW

SOFTY


INTELLIGENT EPROM PROGRAMMER

Connects Directly to TV.

Develop, Copy, Burn, Verify 2708, & with mod 2516

Softy is a versatile product and each application will be different by definition. When Softy is connected via a serial (RS 232) or parallel link with any small computer capable of supporting an assembler a simple and Capable Product Development System is performed. For product developments less than 2k of firmware Softy may be the only development tool you need.

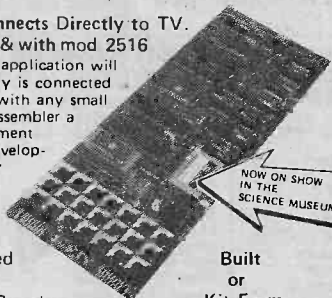ONLY £120+VAT Built & Tested
£100+VAT Kit
£20+VAT Built - Power Supply



Built
or
Kit Form

ZT Driving Computer

ADD A NEW DIMENSION
TO YOUR CAR WITH
COST EFFECTIVE FUEL
MANAGEMENT

*Miles per gallon - Instant *Miles per gallon - Average *Miles per
hour - Instant *Miles per hour - Average *Gallons used since fillup
*Miles to empty *Elapsed Time *Time to empty *Time on trip
*Miles on trip

Accuracy: Time: + 30 secs/month
Speed: + 0.5 mph - Instant
+ 0.005 mph - Average
Fuel Used: + 3%

Takes only about
2 hours to fit

ONLY £77.50 + VAT



Mighty Micro

In association with Watford Electronics

BUY IN CONFIDENCE - In the event that we are unable to deliver your goods within 7 days, we do not bank your remittance until such time we have the goods to despatch. If on receipt of your order, the goods do not meet with your satisfaction, return within 7 days for full refund. All goods covered by manufacturers guarantee.

Please add VAT at 15%. Carriage extra, will advise at time of order. Official orders welcome. Product details on request. Trade and export enquiries welcome.
33 CARDIFF ROAD, WATFORD, HERTS. WD1 8ED
Tel: (0923) 38923 (Sales) or 40588/9 Open 9 am to 5.30 pm Mon-Sat.
Close to Watford Football Ground. Nearest Station: B.R. Watford.




ELECTRO-TECH COMPONENTS LTD.

JVC-VICTOR HIGH FIDELITY STEREO CASSETTE TRANSPORT MECHANISM

ELECTRO-TECH COMPONENTS have secured a very large quantity of cassette transport mechanisms, equipped with all the latest improvements, as well as "SEN ALLOY" type 1.5 micron record/replay heads, and solenoid-controlled autostop action. These were manufactured by JVC/VICTOR of Japan to specification of TANDBERG OF NORWAY. This mechanism alone would normally cost over £50.

FEATURES:

- ★ Close-tolerance, high-quality, top loading transport.
- ★ "Sen-Alloy" (SA type) R/P head.
- ★ Solenoid-driven autostop circuit.
- ★ Automatic head cleaning device.
- ★ Air damped "soft" cassette eject.
- ★ Miniature microswitches for switching.
- ★ Pre-aligned heads and calibrated motor speed regulator built in.
- ★ Three-digit tape position counter.
- ★ Six-function keyboard controls "Record," "Rewind," "Forward," "Play," "Stop/Eject," "Pause."
- ★ PCB connectors and cables attached.
- ★ High-mass balanced flywheel with permanent lubrication spindle.
- ★ Full specifications for motor, heads and switches available on request.

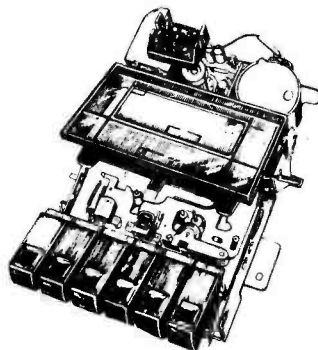

£14.95 VAT inc.
plus £1.00 P&P

★ CASSETTE DECK KIT BASED ON DESIGN OF MR. LINSLEY-HOOD ★

We have developed an outstanding stereo cassette kit with the aid of Mr. Linsley-Hood, to complement the improved specification and latest important advances in cassette electronics since the original design was published. The kit is ideal for use in conjunction with the JVC transport mechanism (left).

Included in the kit are two fibreglass PCB's, drilled and plated for immediate assembly, two VU meters, Dual LED Peak Meters, Variable Bias system, Power Supply, over 10 micro-circuit IC's for the most up-to-date performance, as well as monitoring amplifier, test and calibration cassette, etc.

Price of Kit (without transport mech.)

£35.95 VAT inc. plus £1.00 P&P.

Also available. A custom-designed case for the Kit, this is a fully screened enclosure, sloping panel, satin anodised, wood end panels, professional finish.

Price of Case £9.75 VAT Inc. plus £1.00 P&P

Readers will know of the original LINSLEY HOOD CASSETTE DECK design, published in May 1976. Subsequent articles by Mr. Linsley-Hood have confirmed that the design far exceeded his original expectations, so much so that he published a number of improvements, modifications, and additional features to the original design, which are now incorporated in this Kit.

OFF THE SHELF
DELIVERY ON THESE




BRAND NEW FROM FLUKE... NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:
A peak hold switch which can be used in AC or DC for volts and current functions.
Audible continuity testing and level detection for sensing logic levels.
A temperature (°C) range for use with a thermocouple.

£135

Carriage and Insurance £3

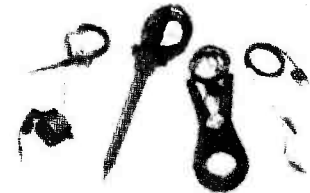The following accessories are in stock now
Y8008 Touch and Hold Probe **£18.00**
80K-40 High Voltage Probe **£45.00**
81RF RF Probe to 100 MHZ **£32.00**
80T-150C Temperature Probe (°C) **£55.00**
801-600 Clamp-on AC Current Probe **£50.00**



HERE IT IS... THE EVER POPULAR 8022A HAND-HELD DMM

Consider the following features:
6 resistance ranges from 200 ohm-20 ohms.

8 current ranges from 2mA-2A AC/DC.

10 voltage ranges from 200 mv-1000v DC-200 MC-750V AC.
Pocket size — weighing only 370 gms.

Full overload protection — will withstand 6kv spikes.
Rugged construction — virtually indestructible.

Meets tough military specs. — drop proof.

In line, pushbutton operation for single-handed useage.

Incorporates low power CMOS chip for low power consumption.

All this plus a 2-year full guarantee.



For only £89

Carriage and Insurance £3

Soft carrying case £7 extra

Even more sophisticated the Fluke 8020A


Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £112

Carriage and Insurance £3.00

A handsome soft carrying case is included (this model only)

OFF THE SHELF
DELIVERY ON THESE

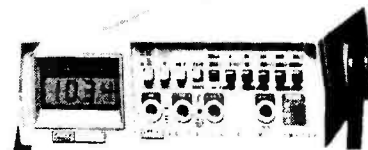

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than even offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature:

10 voltage ranges from 200mv-1000v dc, 200mv-75v ac. 3 conductance ranges from 2mS-200nS.

6 resistance ranges from 200Ω-20mΩ—the 8012A has two additional resistance ranges 2Ω and 20Ω. 10 current ranges from 200μA-2A AC/DC—the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £159 8012A £179

Carriage and Insurance £3

The 8010A is also available with two rechargeable Nicad size C batteries installed in option -01a + **£179.00**



TMK500 MULTIMETER 30,000 OPV

A study and reliable instrument.
Has internal buzzer. AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000.

DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000 DC current: 0 to 50 uA, 5 mA, 50 mA, 12 amp.

Resistance: 0 to 6K, 6 meg, 60 meg.

Decibels: -20 to +56 db.

Short test: Internal buzzer.

Size: 160 x 110 x 55 mm.

£20.50 P&P 75p

CHROME DIOXIDE CASSETTES

Limited quantity only. Excellent quality little known brand (Italian). Satisfaction guaranteed. C90s only. Price per six (minimum quantity) **£6 inc. VAT, P&P 75p** any quantity.

FERRIC OXIDE CASSETTES

Excellent quality (Italian) C120s only. price per 6 (min. quantity) **£5 incl. VAT, P&P 75p** any quantity.

This offer only applies while stocks last

PLEASE ADD 15% VAT TO ALL ORDERS

EXCEPT WHERE ITEMS
MARKED
"VAT INCLUDED"


CALLERS WELCOME

We are open 9 a.m.-6 p.m.
Monday-Saturday.
We carry a very large selection of electronic components and electro-mechanical items.
Special quotations on quantities.

BENDIX MAGNETIC CLUTCH

Superb example of electro-mechanics. Main body in two sections, coil section fixed with 3/8" sleeve, drive section rotating on outer perimeter. Uniting plate has 3/8" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission 24V D.C. 240 m/a.

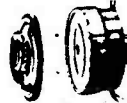Dozens of uses in Home, Farm Workshops & Lab.



**£4.75
P&P 75p**

ROTARY STUD SWITCH

PLESSEY 30-way, 2 bank, Single pole. Contacts 1 amp 240v. AC/DC. 005Ω res. Make before break. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 1/8" dia. overall 2 1/8" deep plus 1 1/8" x 1/4" dia. psindle.




**£3.25
P&P 50p**

ELECTRO-TECH COMPONENTS LTD.

364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

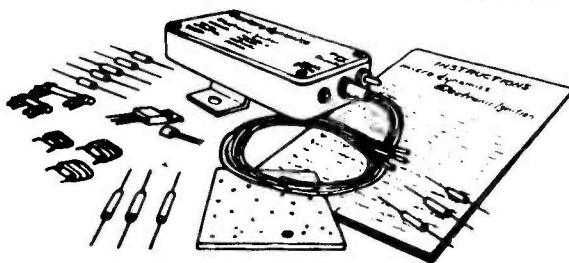At last A Professional Electronic Ignition — in kit form



Years of ignition experience gained, both in competition and with turbo charged engines, has enabled Micro-Dynamics to bring the kit builder a new concept in electronic ignition.

Only high grade passive components and carefully selected semi-conductors are used in this comprehensive kit which includes a fully prepared printed circuit board and painted case. Ample wire, solder and heat sink compound are provided as well as a comprehensive vehicle installation kit. Assembly time should be about 1 to 2 hours with the aid of the complete illustrated building and fitting instructions.

As it was developed through competition, this kit system incorporates all the best features claimed for ignition improvement as well as a unique waterproof switch for high reliability. The system requires a 12volt negative earth supply and is suitable for all engines with coil and contact breaker ignition up to 8 cylinders.

micro-dynamics
MD1 Kit

£17.67
PRICE All inclusive

Also available are fully encapsulated and "Burn-in" tested units built on the same production line as the competition systems.

PRICE £31.50

Send SAE if brochure only required.

Starfire
Electronic Ignition

The only system with UNIQUE circuitry that produces a Maximum Energy Spark (M.E.S.) at every engine speed. No other known system has this patent applied for, feature. Starfire is the most efficient inductive system easily fitted using only basic tools. Designed by a team with many years experience in automotive electronics, it is manufactured in England to the highest standards.



£19.49
All inclusive

Recommended Price **£27.49**

Delay-Lite

INTERIOR LIGHT DELAY UNIT FOR CARS
Maintains and fades interior light for 10 to 20 seconds after drivers door is closed.
— NO MORE FUMBLING IN THE DARK!



£3.45
PRICE

L.S.M. Products, PO Box 51,
FREEPOST, 411 Croydon Road,
Caterham, Surrey CR3 6UD
Tel: Caterham (0883) 49281

24 hour answering service

PRICE INCLUDES POST, PACKING & VAT



HAND HELD GAMES

Supersonic Mastermind	£21.00
Galaxy Invaders	£22.95
Mattel Space Alert	£15.90
Mattel Auto Race	£15.90
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
DIGITS (like Mastermind)	£14.95
DESTROYER	£16.95

**ALL GAMES HAVE SOUND EFFECTS
EXCEPT MASTERMIND AND DIGITS**

The latest from the U.S.A. PINBALL WIZARD

★ Still available ★
Featured in Nov. issue of E.T.I.
Home TV Game — B/W Kit
Basic Kit **£28.90**
Contains everything except box and controls
Box & Controls — **£6.50**. Mains Adaptor — **£3.90**
Play 7 games with 4 options on each game
4-Pinball games 2-Basket. 1-Breakout
Versatile car alarm kit **£18.90**
See review in Hobby Electronics November
CHROMA CHIME 24 tune door chimes kit **£10.50** Built **£15.95**
C.B. Aerials and Accessories

ATARI video

computer **£145**

STAR CHESS T.V. Game	£63.35
DATABASE Prog. T.V. Game	
NEW	£89.95
CHESS CHAMPION 6 Level	£54.95
CHESSMATE 8 Level	NEW £59.95
CHESS CHALLENGER 7	£99.00
CHESS CHALLENGER 10	£160.00
VOICE CHALLENGER	NEW £230.00
BRIDGE CHALLENGER	NEW £290.00
CHECKER CHALLENGER 2	£54.00
CHECKER CHALLENGER 4	£90.00
ZODIAC Astrology Computer	
NEW	£29.95
Snooze Alarm	£14.90

Selection of Commodore Watches & Calculators

COMPUTERS — Home, Business etc.

PET BK	£550.00
PET 16K	£670.00
SORCERER 8K	£747.50
SORCERER 16K	£874.00
SORCERER 32K	£887.75
SUPERBOARD II 4K	£172.45
UK101 Kit 4K	£226.85
Built 4K	£286.35
TR80 Level 2 16K	£440.00
5 1/4" Floppy Drive	£288.65
Dual Drive	£508.00
NASCOM 2 Kit	£339.25
2 Built	£396.75
HEATH WH89	£1,805.00
HEATH WH14 Printer	£586.50
Softy Kit	£115.00
Softy Built	£138.00
Intelligent EPROM Programmer	

PRINTERS: FLOPPY DISC: BOOKS

S.a.s. Enquiries. Please allow up to 21 days for delivery. All prices inc. of VAT.



N.I.C.
61 BROAD LANE, LONDON N.15 4DJ
Day 01-808 0377; Eve 01-889 9736




Random Electronic


EASY DICE

Build your own 'EASY DICE' from the 5 integrated circuits and full components supplied, including box and descriptive instructions.

Complete
or
Kit

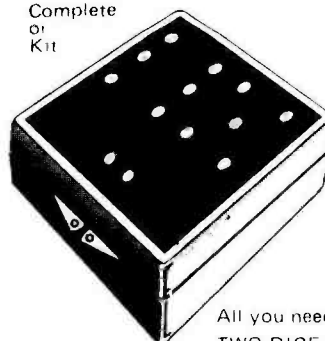

P.C.B.
Layout

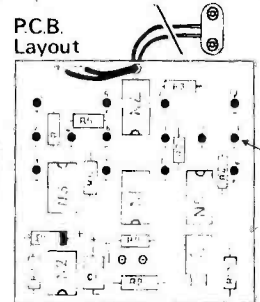

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL

- a *Self Assemble Dice **£4.50** plus 25p p&p
- b *Ready built Dice **£5.45** plus 25 p&p
- c *Roll out model **£5.95** plus 25p p&p

Order now from: **Fringewood Electronics Ltd.**
1 Hatton Court, Ipswich, Suffolk. 0473 210151

Amount enclosed £


Name

Address

please state amount required in appropriate box a b c

GREENWELD

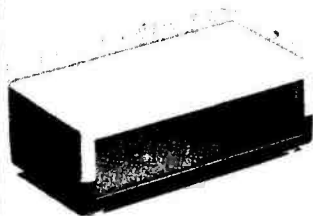443A Millbrook Road Southampton SO1 0HX
All prices include VAT @ 15% — just add 40p post



VEROCASE SALE II

Three popular sizes of Verocase at drastically reduced prices — these were part of their standard range (75-1411, etc) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No	Size	Price
21051	180x120x65mm	£2.30
21052	154x85x60mm	£1.75
21053	125x65x40mm	£1.45

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia x 20mm 70p.
Z402 Miniature type buzzer, 6, 9 or 12V, only 22x15x16mm. Very neat 53p.
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only £1.

A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied £1.50.
W892 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket 85p.
W890 DIL Reed relay SPCO 2.4-10V, 200R coil. Only £2.20

POWER DARLINGTON PAIR

Plastic power (TOP66 case) transistors type BD695A/BD696A. Just look at the spec!! 70W 8A 45V — Hfe 750 @ 4A!! Special low price — £1.20 per pair.

VU METERS

Voo2 Twin type. 2 metres 40x40mm and driver board, supplied with circuit and connection data. £3.50.

Voo3 New type, just in. Twin type moulded in one piece, 80x40mm (no driver board but suitable circuit supplied) £2.50.

OUT NOW THE NEW 1980

GREENWELD CATALOGUE

FEATURES INCLUDE:

- 60p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 40p + 20p POST

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1,000pF. Total 210 £3.89.
K002 Extended range 22pF to 0.1µF. 330 values £8.53.

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £8.07.

K004 Mylar capacitors, min 100V type 10 each all values from 1,000pF to 10,000pF. Total 130 for £4.05.

K007 Electrolytic capacitors 25V working max physical size. 10 each of these popular values: 1, 2, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.69

K008 Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for £8.05.

K021 Miniature carbon film 5% resistors CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors £6.15.

K022 Extended range. Total 850 resistors from 1R to 10M £8.50.

K041 Zener diodes 400mW 6V BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for £16.37.

INVERTER

Prepare for the Power Cuts! Ready built inverter, 24V DC 290x55x37mm, with power 6x8W fluorescent tubes. Circuit supplied. Only £2.90.

COMPONENT PANELS
Z525 Contains 11 800mA 60V 2N5061 SCRs, 11 6V8 zeners, 11 1N4004 diodes plus Rs, Cs, etc. Only £1

74 Series ICs — Gates and complex logic, 20 assid ICs on panels £1; 100 ICs £4.
Z527 2 x 6V relays, 6x 25030 or 25230, 6x 400V reals, plus Rs. Only 50p

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time, 470ns cycle time; single low capacitance high level clock I/P; fully TTL compatible; low power dissipation. Supplied with data £2.75.

SOFTY

INTELLIGENT EPROM PROGRAMMER

* Replaces monitor ROM and circuit needed to test programs on most microprocessors.

* Hexadecimal data may be written to any location.

* Contents of all memory addresses visible on-screen.

* Connects to system under development as ROM/RAM.

* Useful as control computer in its own right. User-programmable to perform complex control functions. Keys may be assigned to user-programmed functions.

* Ideal training aid. Execution by internal microprocessor will halt at set breakpoint (which may be substituted for any program instruction) and contents of internal registers will be displayed.

* Crystal controlled one-microsecond micro-circuit for timing and delay functions. INS 8060 has on-chip programmable timer.

* Two eight-bit I/O ports. Port A may be used in strobed or tri-state modes and will generate interrupt.

* Universal assembler functions: block shifts, hexadecimal addition and subtraction, insertion or deletion of instructions, matching of specific bytes etc.

* International standard card-edge. Similar prototyping cards widely available.

* Fast cassette interface — over 2000 baud-equivalent — for program storage (TRANS-WIFT).

* On-board EPROM programmer. Fastest possible device permits reading from same socket and verifies program.

* Copies Software — any memory device wired to address/data lines can be copied on screen, tape or EPROM.

* Can reprogram itself to perform special operations by substituting firmware ROM.

VAT inclusive prices: Softy in kit form £115.00.

Softy ready built and tested £138.00.
Ready built PSU (+ & -5V, +12V, +27V) £23.00

Or send £1 for Instruction Manual (Refundable on purchase of Softy).

REGULATED PSU PANEL

Exclusive Greenweld design — better spec than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: Output voltage 0-28V
Output current 20mA-2A
Source Impedance 0R1
Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only £6.75

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number — almost all are full spec. devices, some have bent leads. Over 30 different types have been found by us including 8C184/212/238/307/328; BF196/7; 2TX107/8/9/342/450/550 etc. Only available as a mixed pack at £3 per 100; £7 per 250; £25 per 1000.

£1 BARGAIN PACKS

All packs £1 EACH. ANY 25 PACKS £22

Pack No.	Contents
K101	16 BC239B transistors
K102	15 BC349A transistors
K103	10 BC548B transistors
K104	18 BC182B transistors
K105	18 BC184L transistors
K107	18 BC213L transistors
K108	8 2N5060 thyristors, 30V 0.8A TO92 case
K109	15 BC114 transistors
K110	4 BD131 transistors
K111	4 BD132 transistors
K112	12 3A 100V rects, wire ended
K113	30 DA002 rects 150V 0.5A
K114	15 XK6116 (BF241) transistors
K115	18 SP1218 (2N3702) transistors
K116	10 MPS101 NPN 140V TO92
K117	10 BF450 PNP TV IF amp transistor
K118	18 ME4101 NPN 60V AF low noise
K119	10 2N5401 NPN 160V TO92
K120	6 pre 25D96/25B496 AF O/P aim to AC12B/17B
K121	20 7V5 400mW zeners
K122	10 VR625 5.2V 2.2W zener
K123	10 56V 1W zener
K124	50 0.02µF disc ceramic
K125	200 1k 5A 1/4W carbon film resistors
K126	100 3000pF 63V polystyrene preformed caps
K127	25 27µF 25V axial lead caps
K128	25 15µF 40V do
K129	8 AA113 diodes
K131	10 VA1086 thermistor
K133	20 3 way 5A term blocks
K134	50 unmarked untested OC71 type transistors
K135	30 4.7µF 10V radial elec
K136	34 AC187K transistors
K137	5 18µF 100V disc-polarised caps
K138	30 1/4" coil former with slug
K139	40 0.02µF 50V mylar caps
K140	30 0.05 do
K141	40 0.01µF 400V axial caps (C296)
K142	25 wire ended nonstd size, 90V
K143	200 square mica insulation 25mm sq.
K144	30 1R5 3W wirewound resistors
K146	25 330µF 4V axial caps
K148	30 transformer former type X228
K149	12 Ferrite rod type X036
K150	10 switches type W430
K151	12 0.125" red LED's
K152	10 0.2" red LED's
K154	15 5 pin 180° Din socket, clip fix

BULK BUYERS CORNER

All new full spec. devices. Prices are for a minimum of 100 of any one device and exclude VAT, which must be added at 15%. Minimum order value from this section is £10 + VAT + post. VAT receipt on request.

AC187K .20	BC485B .06	BF355 .18	PN109 .055	2N5401 .17	Diodes .02	MINIATURE CERAMIC CAPS	Electrolytic Caps
AD181/2 .45	BC486A .06	BF394 .055	TIP32 .22	2N5447 .06	1N4148 .02	Thompson/CSF miniature type in the following values:	2.2/25 R .028
BC107 .07	BC546B .06	BF414 .06	TIP 41A .28	2N5831 .06	per 1000 .016	3.9pF, 4.7pF, 22pF, 33pF, 47pF, 68pF, 82pF, 100pF, 560pF.	2.2/63 A .028
BC108 .06	BC547C .055	BF450 .095	TIP 42A .28	2N6121 .16	per 1000 .025	2700pF ±10%, ±5% except 10%, ±20%.	4.7/10 R .022
BC109 .07	BC548B .05	BF451 .09	TIP 2955 .46	2SC536 .05	per 10,000 .021	Prices: up to 82pF	4.7/25 R .028
BC114 .06	BC556A .06	BF757 .27	TIP 3055 .46	2SC1617 .62	1N4004 .038	100pF	4.7/35 R .030
BC117 .07	BC556B .06	BF840 .17	TIS91 .12	2SC2068 .43	per 1000 .032	560pF	4.7/50 R .034
BC118 .05	BC557A .06	BFW43 .32	2TX107 .06	2SC2073 .45	1N4006 .048	2700pF	4.7/63 R .038
BC119 .14	BC737 .07	BFY17 .19	2TX122 .06	TTL IC's	per 1000 .034	101µF	10/16 R .030
BC125 .06	BCX32 .05	BVFSO .13	2TX214 .06	7401 .08	Zener diodes	1000pF	10/25 R .032
BC139 .14	BCY33 .05	BFY51 .13	2TX303 .07	7404 .10	400mW BZY88 or similar 5: All voltages from 2V7 to 36V.	560pF	10/25 R PC .022
BC147 .05	BCY32 .12	BFY52 .13	2TX311 .07	7405 .09	1N4741 11V 1W .042	2700pF	10/50 A .040
BC148 .05	BCY71 .11	BFY56A .16	2TX313 .06	7417 .18	1N4742A 12V 1W .06	101µF	10/100 R .042
BC148B .05	BCY72 .10	BFY56A .16	2TX341 .06	7420 .10	ZPY12 12V 1.6W .075	154020A 20V 1.5W .045	15/40 A .030
BC149 .05	BCY72 .10	BFY64 .15	2TX450 .06	7430 .09	1T0107 1.5W .075	1T0107 1.5W .075	22/10 R .021
BC159 .05	BCY72 .10	BR101 .28	2TX501 .96	7442 .47	1T0107 1.5W .075	1T0107 1.5W .075	22/25 A .028
BC168C .055	BCY72 .10	BR101 .28	2TX501 .96	7445 .47	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC169C .055	BCY72 .10	BR101 .28	2TX501 .96	7446 .47	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC172C .05	BCY72 .10	BR101 .28	2TX501 .96	7447 .14	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC177 .07	BCY72 .10	BR101 .28	2TX501 .96	7474 .17	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC182B .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC183B .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC184L (TOS) .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC187 .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC212 .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC212B .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC213 .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC213L .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC214L (TOS) .045	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237 .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237B .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237C .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237D .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237E .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237F .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237G .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237H .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237I .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237J .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237K .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237L .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237M .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237N .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237O .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237P .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237Q .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237R .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237S .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237T .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R .028
BC237U .05	BCY72 .10	BR101 .28	2TX501 .96	7493 .24	1T0107 1.5W .075	1T0107 1.5W .075	22/25 R

BUILD YOUR OWN FM RADIO CONTROL SYSTEM

TRANSMITTER BASIC KIT £36.00
RECEIVER KIT £18.40
SERVOS from £12.00

Send remittance of £2 for circuits and constructional data to:

**TELERADIO R/C, 325 FORE STREET, EDMONTON
 LONDON N9 0PE, 01-807 3719**

CLOSED THURSDAYS

GIVE YOUR HOME-BUILT METAL DETECTOR THE PROFESSIONAL LOOK

Now available, a complete kit of parts to house your detector, comprising high quality black A.B.S. vacuum formed 10 1/2" square head halves, vacuum formed top case assy all the anodised metal tubing fully adjustable, and injection mouldings screws etc, order as kit. S.E.1. Price **only £17.25 inc. VAT**.
 Also available, with pre-wound and set up head assy with head module, for T.R. metal detector, complete with circuits and application notes to produce your own I.B./T.R. unit. Order as kit. S.E.2. **£23.50 inc. VAT**.
 Kit S.E.3. Comprises of kit 2 but with P.C.B. and components to produce a three I.C. three transistor metal detector with meter and audio output, inc. everything you need, high quality meter and headphones, etc. **Only £39.95p inc. VAT**.
 All the above kits are carriage paid.

SPECIAL OFFER TO "ETI" READERS £1 OFF THE ABOVE KITS ORDERED BEFORE APRIL 30th.
 Components available for building your own designs, S.A.E. for lists of parts.

SONASONICS ELECTRONICS

11a PARK ROAD, ASHFORD, KENT, TN24 8LU
 TEL. 0233 35871 (24 answering service)

VIDEO MUSIC



Videograph II links to the aerial socket of your tv and provides a full colour GIANT oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. **Plus** — full details for testing your audio system for transient distortion, crosstalk etc.

Complete Kit only £29.95 **Luxury cabinet and controls. £14.95**

READY-BUILT UNIT **£59.95** + £1.50 P&P

**WILLIAM
STUART
SYSTEMS Ltd**

Bower House, Bittericay Road,
 Herongate, Brentwood
 Essex CM13 3SD
 Telephone: Brentwood (0277) 810244

SAVE OVER **£2.60** WITH OUR SPECIAL OFFER



£7.45

recommended 420° C
 soldering iron

£5

Prices include p&p & VAT

E.T.I. SPECIAL PROJECT KIT

Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers to carry out.


- ★ PCB REPAIRS
- ★ ANALOGUE BREADBOARDING
- ★ SIMPLE LOGIC WIRING—PROJECTS
- ★ COMPLEX INTERCONNECTING OF MICRO-PROCESSORS, MEMORIES, ETC.

ETI OFFER KIT CONSISTS:


1 pencil, 1 project PCB, Wire Distribution Strips and adhesive 4 bobbins of wire for colour coding — Logic wiring, and one bobbin of tinned copper wire — PCB repair and analogue breadboarding.

Send large SAE for further details on ROADRUNNER products — but remember, this offer closes June 1st!!

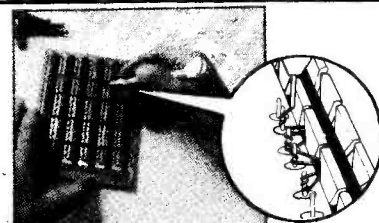
**IF
YOU
PLACE
AN
ORDER
FOR 5
KITS
ONE WILL
BE
FREE!!
(5 for
£29.80)**



WIRING OF LOGIC, MICROS AND MEMORIES

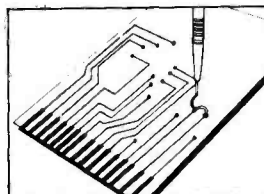

PCB REPAIR
 MAIL ORDER
 ONLY

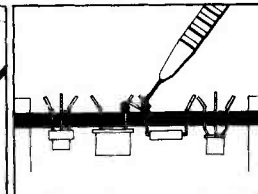

ANALOGUE BREADBOARDING
 OFFER CLOSING JUNE 1st

Please use BLOCK CAPITALS

PLEASE SEND ME Kits @ **£7.45** each or X5 Kits
 Irons @ **£5** each (@ **£29.30**)

I enclose P.O. / Cheque No.

Value

Access / Barclaycard No.

NAME

ADDRESS

To: T. J. BRINE ASSOCIATES (ETI OFFER)
56b HIGH STREET, HASLEMERE
SURREY GU27 2LA

THE BLACK HOLE

Tim Orr, the prolific producer of music machines, presents the Black Hole Chorus Machine. Choose chorus effect or vibrato and control it all by footswitch.

The black hole is a musical effects device for processing natural and synthetic sounds. It has two modes of operation, chorus and vibrato. In the chorus mode the input signal is delayed (12 mS) by an analogue delay line. It is then mixed back with the original signal. This delay time is not long enough for a distinct second image to be heard, but it is noticeable, particularly as the time delay is slowly modulated. The sound produced by this process has a sort of 'spacey' feel to it as though the input signal was being accompanied by a faint chorus. What is, in fact, happening is that a comb filter has been produced (Fig. 1) with notches spaced at about every 90 Hz. As the delay time is modulated these notches move up and down in frequency producing a colouration of the sound similar to phasing. This, coupled with the short time delay, produces the 'spacey' colouration known as a chorus effect. A manual speed control allows the user to vary the modulation speed. A slow modulation is best suited for guitar and keyboard instruments, whereas a faster speed, which introduces a noticeable pitch modulation, works well on vocals. Another chorus mode is available to switch in a second delay line modulated in antiphase.

The vibrato mode is essentially the same as the chorus; the only things that change are the modulation waveform (triangular sweeps for the chorus sinusoidal sweeps for the vibrato) and the frequency range. As this is 2 to 13 Hz, a definite pitch modulation is produced. The controls that effect the vibrato are speed and modulation depth. The vibrato is not just pure frequency modulation, there is also amplitude modulation which produces a slightly more interesting effect.

The vibrato/chorus selection is made with a footswitch. Two LEDs indicate which effect has been selected and also the modulation speed. The input amplifier has a manual level control plus a high impedance-high level/low impedance-low level selector switch, thus enabling a wide range of input levels to be accommodated. The largest input level is 4V5 rms, and the smallest level for overload is 5 mV rms; a range of nearly 60 dB. An overload LED indicates the onset of distortion.

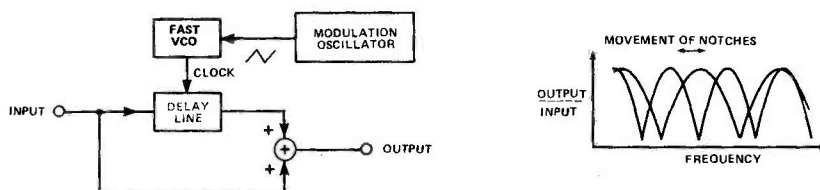


Fig. 1. Block diagram of a comb filter.

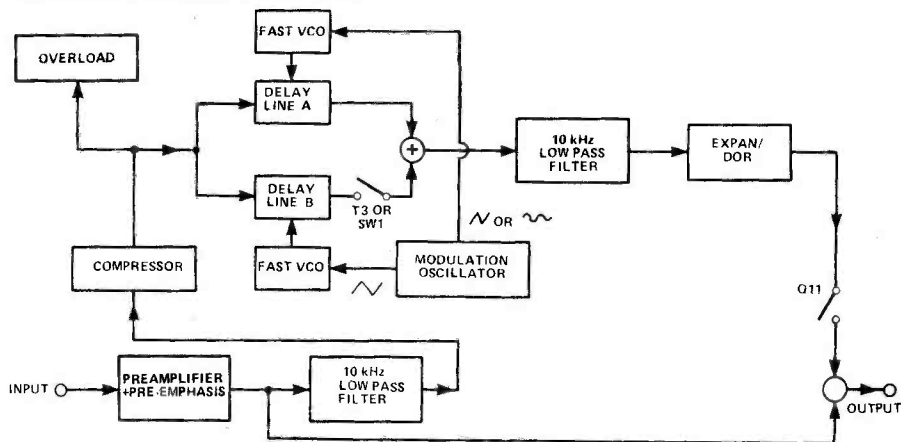


Fig. 2. Block diagram of the Black Hole choraliser system.

	LOW	HIGH
MAXIMUM INPUT LEVEL	1.25Vpp	13Vpp
MAXIMUM INPUT LEVEL SENSITIVITY	15mVpp	150mVpp
INPUT IMPEDANCE	10k	110k
SIGNAL TO NOISE RATIO	68dB	74dB

MAXIMUM OUTPUT LEVEL	1Vpp
OUTPUT IMPEDANCE	600ohms
VIBRATO SPEED	2 - 13 Hz
CHORUS SPEED	0.3 - 3.3 Hz


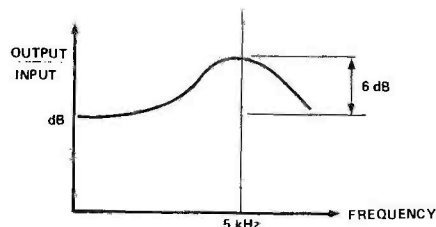


Fig.3. (top) Performance specification.

Fig.4. (above) Frequency response of pre-emphasis, IC11 pins 5, 6, 7.

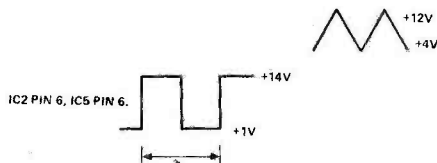- * REMOVE ALL ICs. TEST FOR $\pm 15V$ AT IC9,10. THE UNREGULATED RAILS WILL BE APPROXIMATELY $\pm 22V$. REPLACE ALL ICs AND RECHECK PSU.
- * IC11 PIN 1,7 AND IC12 PIN 1,7, WILL HAVE THE AUDIO INPUT SIGNAL WITHOUT ANY DC BIAS.
- * COMPRESSOR OUTPUT. IC13 PIN 10, HAS A DC BIAS OF APPROX. $+7V$ PLUS THE AUDIO INPUT SIGNAL.
- * FAST VCO. IC1 PIN 6 AND IC4 PIN 6



Z VARIES FROM ABOUT 22 μ S TO 28 μ S, IT BEING SWEEP BY THE MODULATION OSCILLATOR IC7.

* DELAY LINE OUTPUT

VIEW PR1 WIPER

INJECT A 1 kHz SINEWAVE. VARY ITS AMPLITUDE SO THAT IT IS 2Vpp AT THE VIEWING POINT. ADJUST PR2 SO THAT THE WAVEFORM IS SYMMETRICALLY BIASED BETWEEN THE TWO CLIPPING LEVELS. NEXT ADJUST PR1 SO THAT THE CLOCK SIGNAL IS NULLED. REPEAT FOR DELAY LINE B, USING PR3,4, VIEWING PR3 WIPER.

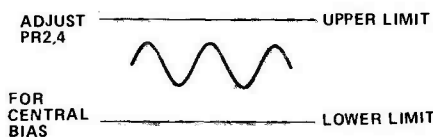


Fig.5. (above and above left) Alignment notes.



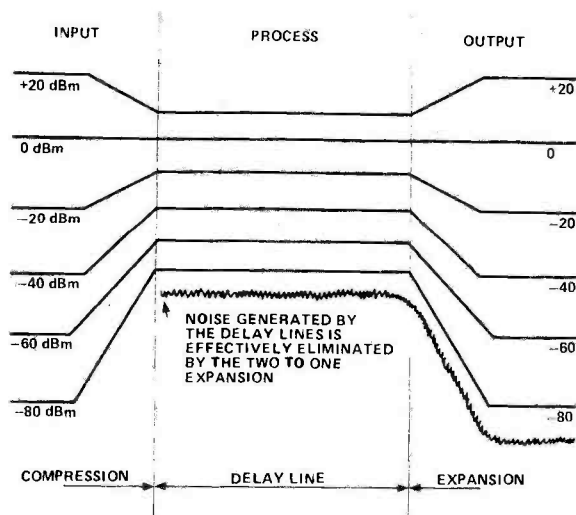
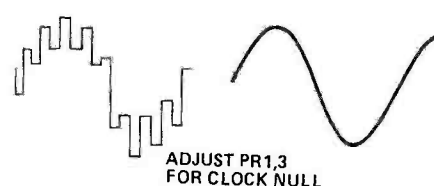



Fig.6. (left) Using a compander system to remove delay line noise.

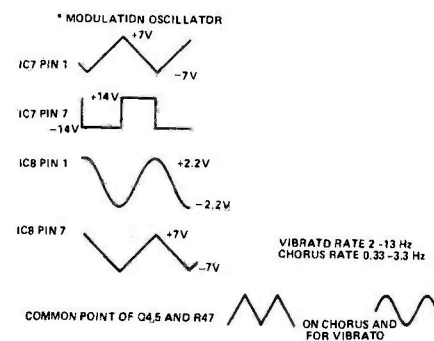

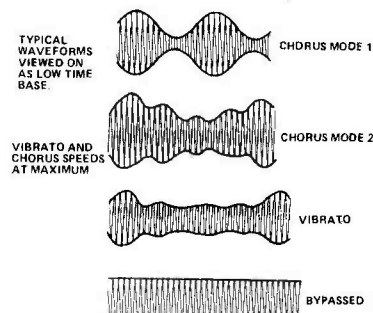- * POST FILTER. IC15 PIN 7. RECOVERED AUDIO SIGNAL WITH NO DC BIAS.
- * EXPANDER. IC13 PIN 7. RECOVERED AUDIO SIGNAL WITH $+5V$ DC BIAS.
- * OUTPUT SIGNAL. IC15 PIN 1. INJECT A 500 Hz SINEWAVE INTO THE UNIT. A MODULATED OUTPUT SIGNAL WILL BE SEEN.



You don't want to have to fumble for a lot of controls on the rear panel, so it's plain and simple — power on/off. No chance of accidentally hitting the power switch when you're operating Black Hole by footswitch.

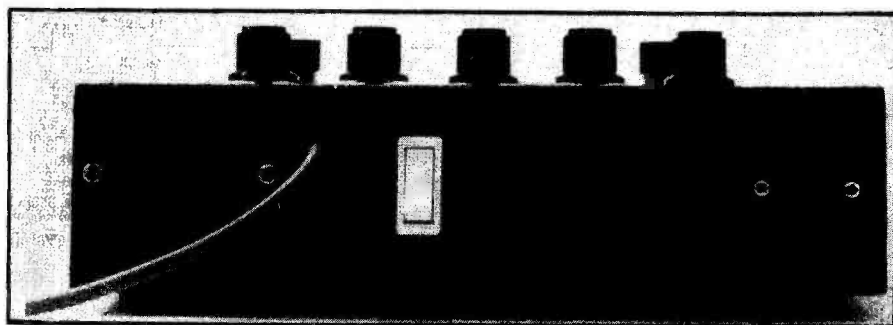

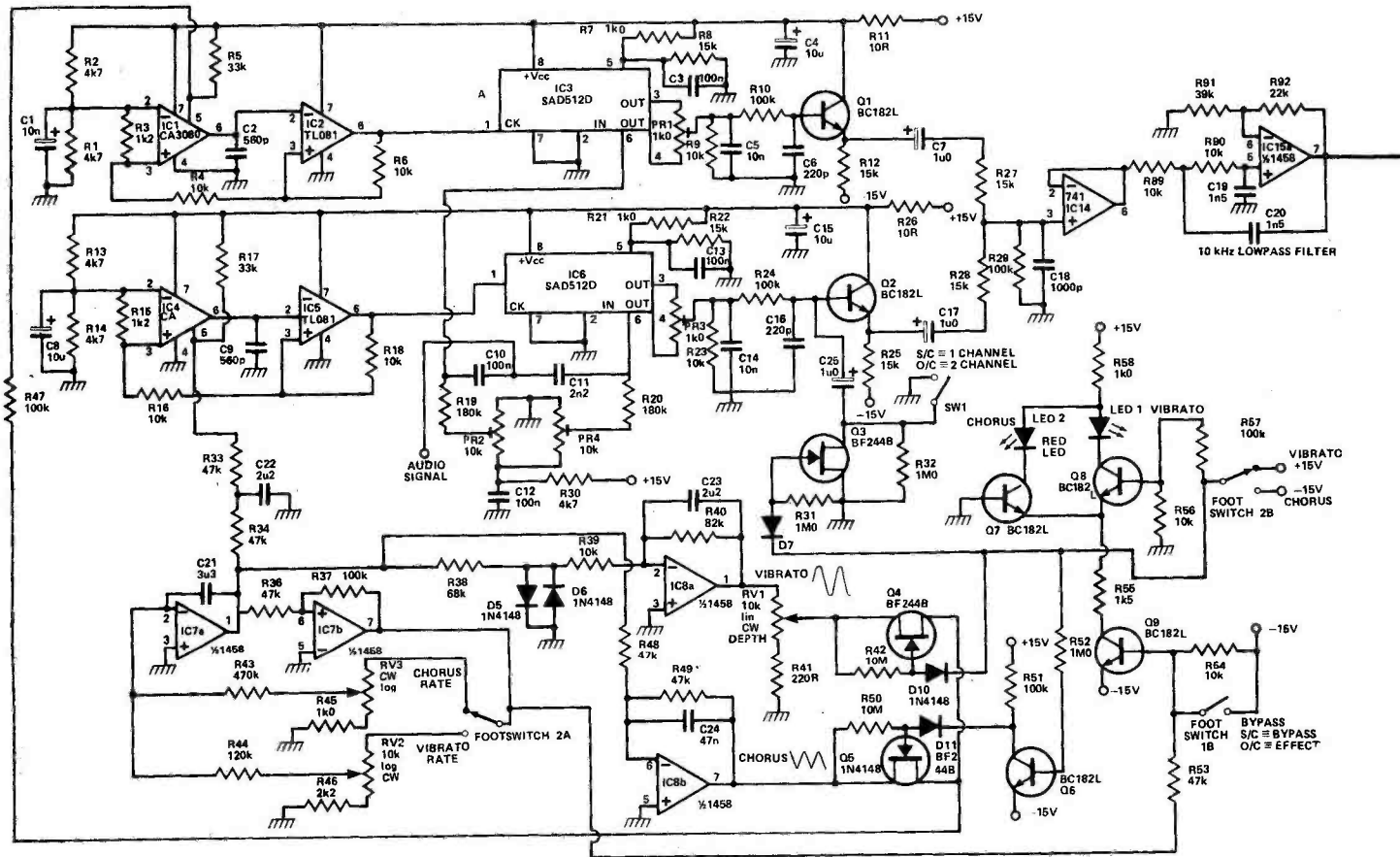


Fig.7. Circuit diagram. This circuit includes the footswitch controls for bypass, chorus, vibrato and chorus and vibrato rate.



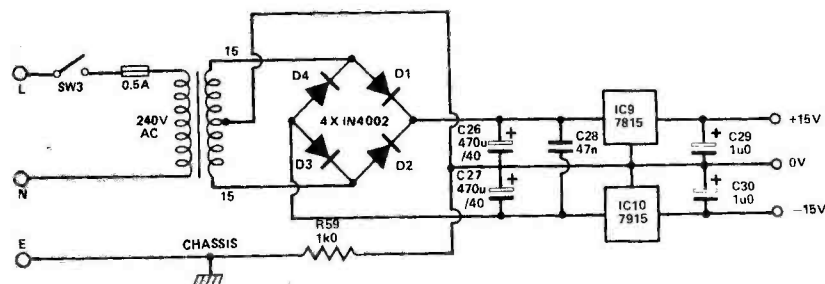
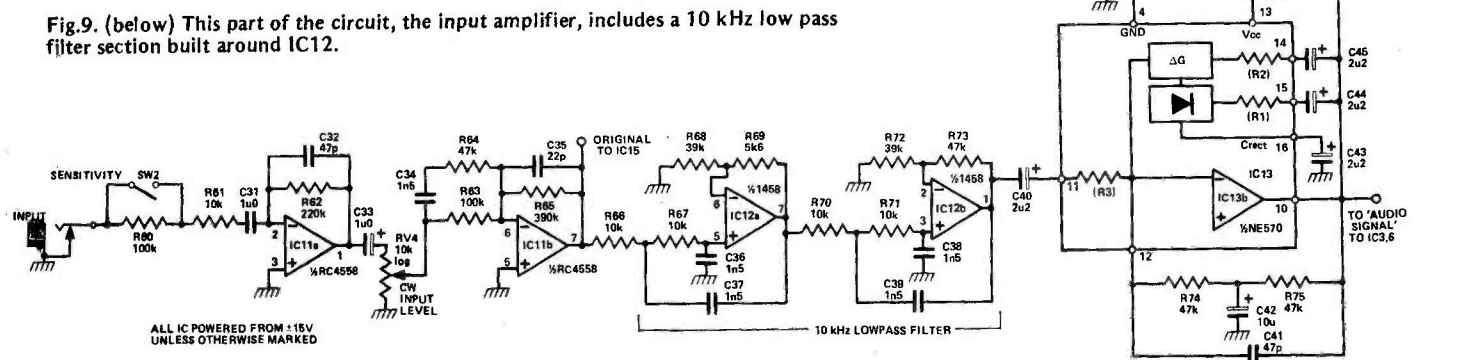


Fig.8. (left) Circuit diagram of the Black Hole's power supply.

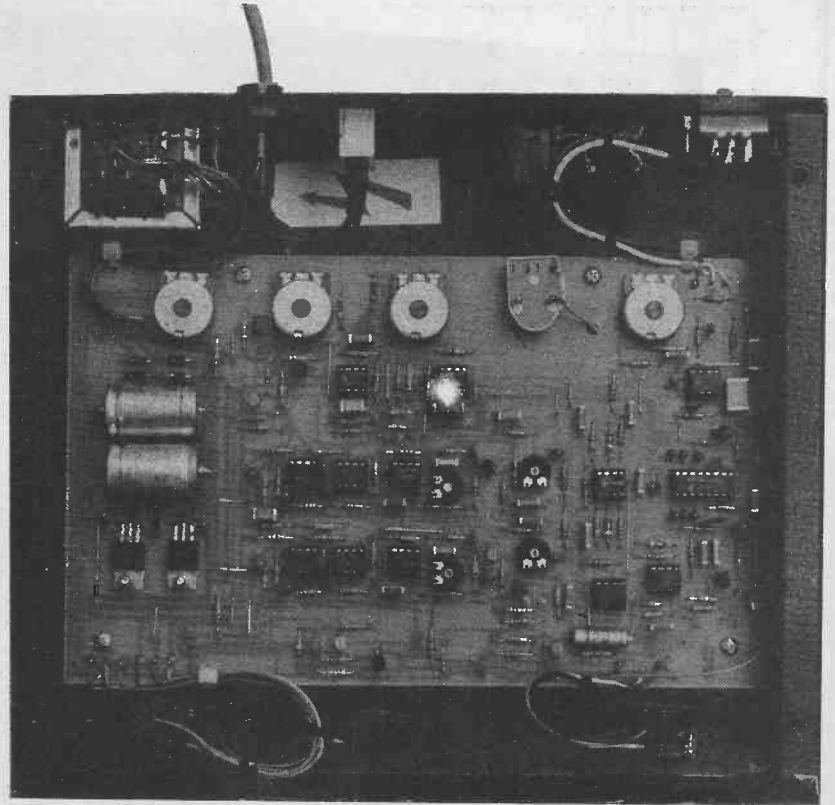

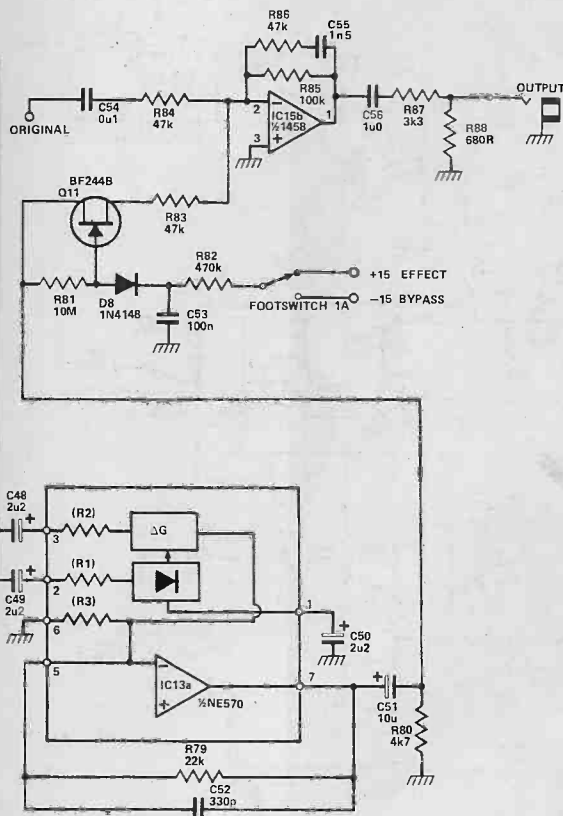

The inside story. Here the PCB has been built and installed in the case with the power supply. Just screw on the base-plate and it's ready to go.

HOW IT WORKS

The input amplifier (Fig.9) is a low noise Op. Amp device, the RC4558 (IC11, pins 1,2,3). With SW2 closed the input impedance is 10 k and the first stage gain is +26 dB. With SW2 open circuit, the input impedance is 110 k and the gain is +6 dB. IC11, pins 5,6,7 forms a pre-emphasis circuit that is used to enhance the higher frequencies of the input signal (Fig.4). A de-emphasis circuit (IC15, pins 1,2,3) corrects the frequency response at the output and in doing so attenuates unwanted high frequency noise generated by the delay line and the compressor. After pre-emphasis the signal is filtered by a 10 kHz 4 pole lowpass filter (IC12) to eliminate aliasing effects that can be caused by the delay line. A compressor/expander system has been employed to improve the overall noise performance (Fig.5). This ensures that the delay lines are always driven with a relatively large signal and that when there is no input signal, the output noise from the delay lines is expanded downwards thus rendering it inaudible. A simple overload detector circuit (Q10) is used to indicate the onset of distortion.

The delay lines are clocked by high frequency VCOs, IC1,2 and IC4,5. The VCO is a simple triangle/square wave relaxation oscillator running at about 45 kHz. The current into pin 5 of the CA3080 determines the oscillation frequency and this current is modulated by the slow oscillator

IC7. Audio signals are fed into the analogue delay lines (IC3,6), the delay time being determined by the relationship,

Delay time = $512 / \text{clock frequency}$, which in this case is about 12 ns. The outputs of the two delay lines are prefiltered by R10,C6 and R24,C16; then mixed together and filtered by a 10 kHz lowpass filter, IC15, pins 5,6,7. The signal is then expanded by the NE570 chip after which it is mixed with the original signal at IC15, pins 1,2,3, having first passed through a 'silent' analogue switch (Q11) which is ON when the effect is selected and OFF when bypassed. The modulation oscillator operates over two frequency ranges, one selected by the chorus speed control; the other by the vibrato speed control. IC7 is a low frequency triangle/square wave relaxation oscillator. When the chorus mode has been selected the modulation waveform is a sine wave, being generated by IC8, pins 1,2,3. This signal is routed via switch Q4 to the high frequency VCO driving delay line A, whilst delay line B is disabled by Q3 which shunts the audio signal to ground. A simple LED control circuit Q7,8,9 indicates whether the unit is bypassed or in either the chorus or vibrato mode as well as indicating the modulation speed.

A standard two rail power supply provides a regulated +15 V at 70 mA and -15 V at 30 mA from two voltage regulators IC9,10.

BUYLINES

A complete kit of parts for the Black Hole choraliser is available from Powertran Electronics. A single delay machine costs £57.30 and a dual delay machine £68.80 (prices include VAT and post). See Powertran's advert elsewhere in this issue for their full address.

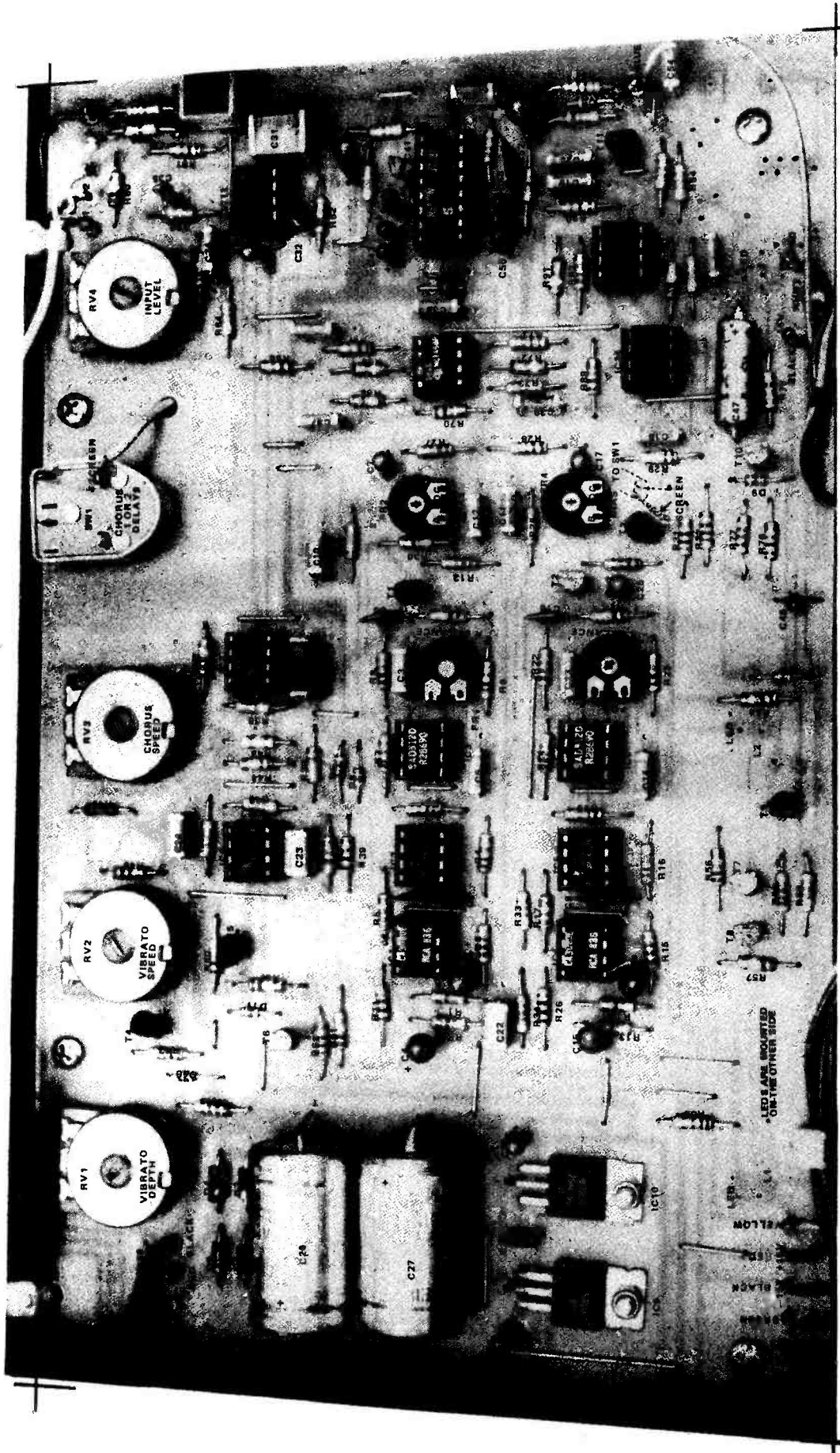


Fig.10. Component overlay. Double check the orientation of ICs, diodes and electrolytic capacitors.

PARTS LIST

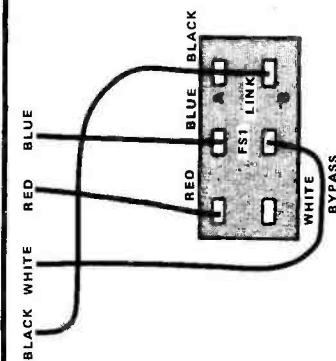
[illegible]

Fig.12. Wiring plan for Footswitch 1.

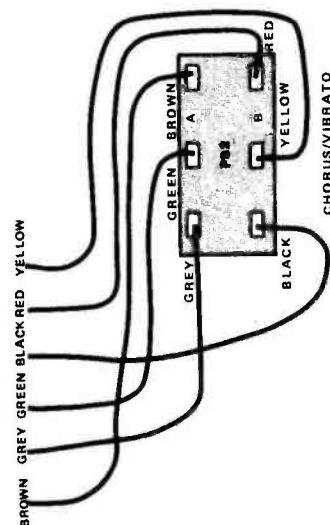


Fig.14. Connections from Footswitch 2 to the PCB.

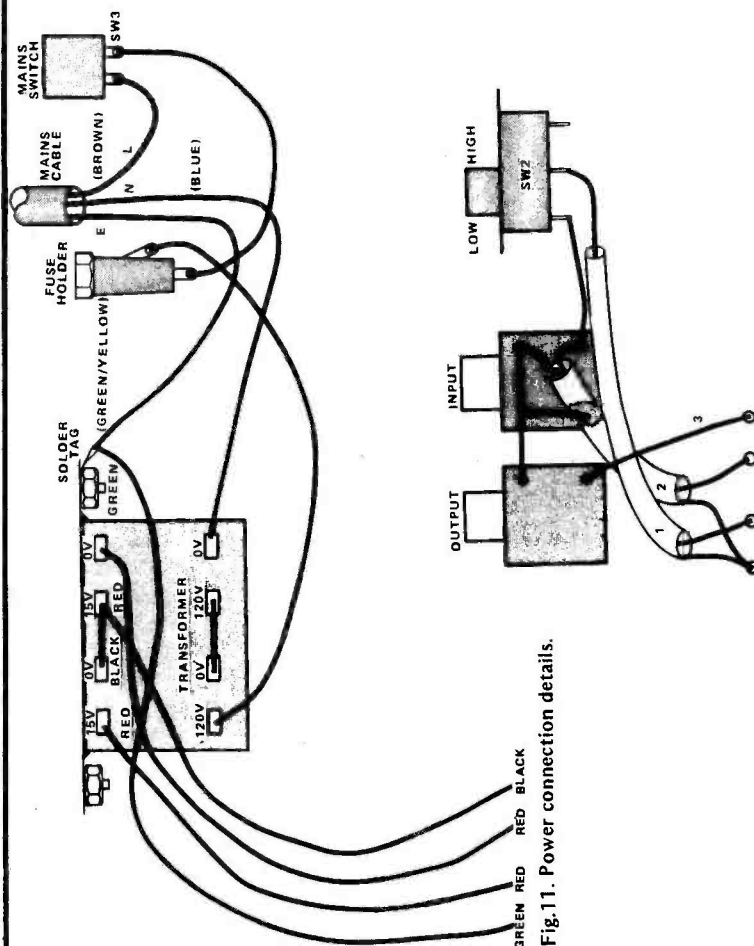


Fig. 13. Input and output connections to PCB.

1999

A FUTURE HISTORY

Cross our palms with silver and see the future unfold. Beware of imitations. This is no guesstimate of what *might* happen – this *is* the future.

Using our very own time machine, a closely guarded secret of the ETI project team, we dispatched a team of reporters to 1999. They brought back stories of a world where World War III is history and robots are causing real problems.

Illustrated in full colour, ETI 1999 is a must for every future historian. Find out what tomorrow holds for you now!





£ 1.50

Plus 30p postage and packing.

Send your cheque/P.O. to

**Sales Office (Specials), Modmags Ltd,
145 Charing Cross Road,
London, WC2H 0FE**

London, WC2H 0EE

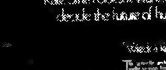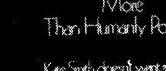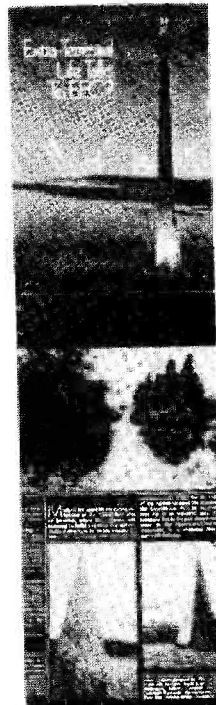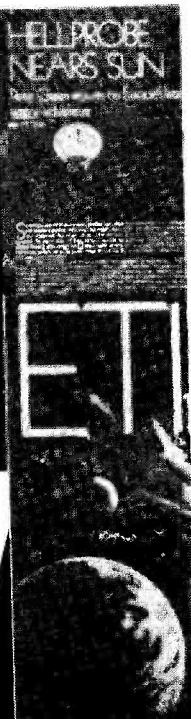

More
Than Humanly Possible

Kate Smith doesn't want robots to decide the future of humanity.

1980-1981

10. *Journal of the American Medical Association*, 273:1033-1034, 1995

...the world's largest...

for the 1990s. The 1990s are expected to be a period of rapid growth for the U.S. economy, and the U.S. government is expected to increase its spending on defense. This is expected to lead to a significant increase in the demand for defense-related services, and this is expected to lead to a significant increase in the demand for defense-related personnel. This is expected to lead to a significant increase in the demand for defense-related personnel.



A Range of Performance from... ...HAMEG




PERFORMANCE AND RELIABILITY
ARE THE SEALS FIRMLY STAMPED
ON THE COMPLETE HAMEG RANGE
AND IT IS A COMPLETE RANGE

HM307	Single Trace DC-10MHz Plus Built-in Component Tester	£149
HM312	Dual Trace DC-20MHz, 5mV/cm, Full X-Y, 30MHz Trigger, Plus TV Trigger	250
HM412	Dual Trace DC-20MHz, 2mV/cm, X-Y, 40MHz Trigger, Plus Sweep Delay	350
HM512	Dual Trace DC-50MHz, 5mV/cm, X-Y, 70MHz Trigger Sweep Delay, Plus Single Shot, Sweep Delay and After Delay Trigger	580
HM812	Dual Trace as per HM512, Plus Storage, Automatic Storage and Variable Persistence	1325

Prices UK List ex VAT

For FULL DETAILS and
DISTRIBUTOR LIST
Contact

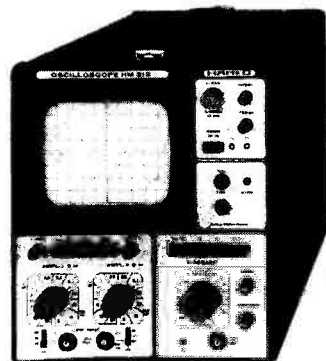Hameg Ltd.,
74-78 Collingdon St.,
Luton,
Beds.
LU1 1RX.



Tel: (0582) 413 174

TRIACS

400V Plastic Case (Texas)

3A	49p	16A	90p
8A	58p	20A	165p
12A	85p	25A	190p
6A with trigger			80p
8A isolated tab			65p
Diac			18p

24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up
to 1kW on and off at preset
times once per day. Kit
contains AY-5-1230 IC,
0.5" LED display, mains
supply, display drivers,
switches, LEDs, triac, PCBs
& full instructions.

CT1000K Basic Kit	£14.90
CT1000KB with white box (56 x 131 x 71mm)	£17.40
Ready Built	£22.50

MINI KITS

These KITS form useful subsystems which may be
incorporated into larger designs or used alone. Kits
include PCB short instructions and all components.

TEMPERATURE CONTROLLER/THERMOSTAT
Uses LM3911 IC to sense temperature (80°C max.)
and triac to switch heater. PCB (4 cm sq.) poten-
tiometer, plus all other components included with
instructions.

500W £3.20 1KW £3.50
SOLID STATE RELAY
Ideal for switching motors, lights, heaters etc. from
logic. Opto isolated with zero voltage switching.
Supplied without triac. Select the required triac from
our range. £2.60

BAR/DOT DISPLAY
Displays an analogue voltage on a linear 10-element
LED display as a bar or single dot. Ideal for
thermometers, level indicators etc. May be stacked to
obtain 20 to 100 element displays. Requires 5-20V
supply. £4.75

**BURST FIRE/PROPORTIONAL TEMPERATURE
CONTROLLER**
Based on the TDA1074 Zero Voltage Switch this kit
contains all the components required to make a
"burst fire" power controller or a "proportional
temperature" controller enabling the temperature of
an enclosure to be maintained to within 0.5°C.
1.5KW £5.25 3KW £5.55

DIGITAL VOLTMETER/ THERMOMETER KIT



Based on the ICL7106. This kit
contains a PCB, resistors, pre-
sets, capacitors, diodes, IC and
0.5" liquid crystal display.
Components are also included
to enable the basic DVM kit to
be modified to a Digital Ther-
mometer, using a single diode

as the sensor. Requires a 3mA 9V supply
(PP3 battery) £20.75

LEDs

LEDs	
0.1" Red	8p
0.1" Green	12p
0.1" Yellow	12p
0.2" Red	9p
0.2" Green	12p
0.2" Yellow	12p
0.2" clips	3p
Rectangular Red	18p
Rectangular Green	20p
Rectangular Yellow	21p

DISPLAYS




DL304 Red 0.3" c.c. pin com- patible with DL704	70p
DL307 Red 0.3" c.c. pin comp	70p
DL707	70p

DL847 Red 0.8" (pin comp DL747) c.c.	£1.80
DL850 Red 0.8" c.c. (pin comp DL750)	£1.80
DL727 Dual 0.5" c.c. Red	£1.50

LIGHTING CONTROL KITS

Directly replace conventional light switch and control
up to 300W of lighting. No mains rewiring. Insulated
touchplates. Easy to follow instructions.

TD300K TOUCHDIMMER. Single touchplate with
alternate action. Brief touch switches lamp on and
off, longer touch dims or brightens lamp. Neon lamp
helps find the switch in the dark. £6.50
**TDE/K Extension kit for TD300K for 2-way switch-
ing etc.** £1.50
TD300K — TOUCHSWITCH & DIMMER. Single
touchplate, small knob controls brightness. £5.50
TS300K — AUTOMATIC. Single touchplate. Time
delay variable 2 secs. to 3 1/2 mins. £4.30
LD300K — LIGHTDIMMER KIT £2.90

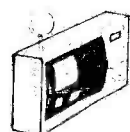

INFRA RED REMOTE CONTROL

If you've got the ideas, we've got the
hardware. Hundreds of uses in the
home, shop, business or industry.
Our range of ICs and components for
Infra-Red remote control enable you
to build controllers for applications
ranging from heating to Hi-Fi to toys
to garage door openers.

Up to 16 channels with three analo-
gue outputs, low component
counts and large tolerance of clock
frequency eliminate the need for
crystals or coils. The systems offer
high noise immunity, reliability and
low cost.

LD271 IR Emitting Diode	36p
SFH205 Photodiode Detector	95p
SL480 I.C. Pulse Amplifier	1.40
SL490 Keyboard Controlled Encoder/Transmitter	2.40
ML922 10-channel Receiver + 3 Analogue Outputs	4.20
ML928 16-channel Receiver (4 latched binary outputs)	1.40
Data sheets (per device)	0.05

These ICs can also be used with
ultrasonic or radio links, depending
on range, cost and speed of opera-
tion. For more details why not give us
a ring



MINI TRANSFORMERS



Standard mains
primaries 240V a.c.
100mA secondaries
6.0-6V 80p
9.0-9V 85p
12.0-12V 80p

D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	38p

Soldercon Pins 50p/100

BOXES

Moulded in high impact ABS. Supplied
with lids and screws. Black or white



82 95 x 71 x 35mm	65p
93 115 x 95 x 37mm	78p

RESISTORS

ZENER DIODES

400mW 3 3V-30V	8p
1 3W 7.5-27V	15p

1/4W 22ohm-10M Pack of 10 (one value)	10p
10 Packs (10 values)	80p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 3% P&P. MAIL ORDER — CALLERS WELCOME
BY APPOINTMENT



TK Electronics

(ETI) 106 STUDLEY GRANGE ROAD
LONDON, W7 2LX. TEL: 01-579 9794



MARPLIN

ELECTRONIC SUPPLIES



SOLDER


A high quality standard solder by Erskin Multicore. Ideal for miniature components 22swg. 1/4kg reel, about 163 metres. Order as FY70M Price £8.50



MINIATURE TRANSFORMERS

Good quality mains transformers to BS415. 6V type: secondaries 0-6V at 500mA + 0-6V at 500mA.

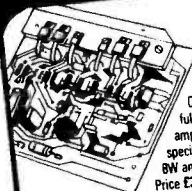Order as WB06G Price £2.63
9V type: secondaries 0-9V at 500mA + 0-9V at 500mA. Order as XWB11M Price £3.40
12V type: secondaries 0-12V at 250mA + 0-12V at 250mA. Order as WB10L Price £2.63
15V type: secondaries 0-15V at 200mA + 0-15V at 200mA. Order as WB15R Price £2.63



AMP KITS

Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications.

8W amp kit: Order as LW36P Price £3.83
50W amp kit: Order as LW35Q

Price £13.73
150W amp kit: Order as LW32K Price £14.89



LIQUID CRYSTAL DISPLAY

High quality 3 1/2 digit 12.7mm (1/2 inch) high figures. Display has centre colon for use in 12 hour clocks and decimal points, plus and minus signs and overflow indicator for use in panel meters.

Order as FY89W Price £8.89



SIREN


A small, but penetrating siren operating on 12V DC (1.2A) Dia. 75mm. Order as YB25C Price £9.81



MCKENZIE POWER SPEAKERS

High quality, high power speakers. 12in. 50W 8Ω Order as X079L Price £19.60

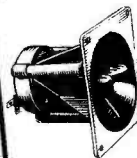12in. 50W 16Ω Order as X080B Price £19.60
12in. 80W 8Ω Order as X081C Price £26.82
12in. 80W 16Ω Order as X082D Price £26.82
15in. 150W 8Ω Order as X083E Price £57.80
15in. 150W 16Ω Order as X084F Price £57.80



PIEZO HORN TWEETER

Very simply added to any speaker system up to 100W rms. No crossover required. Distortion < 1%. Order as WF09K Price £5.27



20,000 OHM/VOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +22dB. Complete with test leads, battery and instruction leaflet. Order as YB83E Price £13.70

MIC STAND

Quality microphone stand extends to 1.5m. Boom arm 1m long adjustable. Stand: Order as XB45Y Price £12.71
Boom: Order as XB46A Price £11.25



SOLDERING IRONS & KITS

Antex CX iron. 17W miniature. Order as FY62S Price £5.25
Antex X25 iron. 25W. Order as FR12W Price £4.88
CX iron with stand in presentation pack. Order as FY68Y Price £5.89
X25 iron with stand in presentation pack. Order as FY69A Price £6.89



CLOCK MODULE

Module requires only transformer and two push switches to operate 4-digit, 0.7in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue. Order as XL14Q Price £8.41



QUICK-CHARGE RECHARGEABLE CELL

1.2V. Size AA(HP7). Fully recharged in 5 hours with 150mA. Capacity: 450mAh. Will last for at least 500 full charge/discharge cycles. Change to quick charge cells now! Order as LR74R Price £1.49

POCKET MULTIMETER

Amazing value 4,000 ohms per volt DC jewelled moving coil meter. Ranges: DC volts 5, 25, 250, 500; AC volts 10, 50, 500, 1,000; DC amps 0 to 0.25mA, 0 to 250mA; Resistance 0 to 600k ohms; Decibels -10 to +22dB. Size only 3 1/2 x 2 1/4 inches. Complete with test leads, battery and instructions. Order as FL60Q Price £8.75



REVERBERATION SYSTEM

The 'concert hall' sound in your living room. Driver module: Order as XB85G Price £6.14
Requires + and - 15V 20mA power supply (ready built) suitable for Driver Module. Order as YL17T Price £4.73
Spring line with 3 sec. reverb time: Order as X106J Price £5.43
Spring line with 7 sec. reverb time: Order as XB84F Price £11.13



KEYBOARDS

High quality keyboards with hard-wearing sloping fronted plastic keys. With keys mounted on nylon bushed steel levers 49-note C to C.

Order as XB15R Price £26.42
61-note C to C. Order as XB16S Price £32.33
With keys pivoted on a hard-wearing moulded fulcrum. 49-note C to C. Order as XB17T Price £21.87




MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 0.5, 5, 50, 500mA, 10A; Resistance 5k, 50k, 500k, 5M, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet. Order as YB87U Price £39.30




TURNTABLES

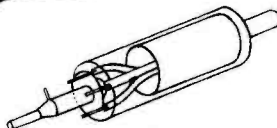Autochanger complete with stereo ceramic cartridge and circuit to make a complete low-cost record player ideal for the young pop fan. Order as XQ00A Price £18.48
Single-play rim-drive turntable with stereo ceramic cartridge. Order as XB23A Price £28.19
Single-play belt-drive turntable 'S' shaped tone arm. Order as XB25C Price £30.63



LASER TUBE

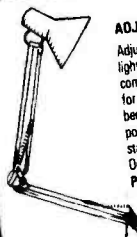A helium-neon 0.5mW laser tube. Full details on page 262 of our catalogue. Order as XL11M Price £124



ADJUSTABLE LAMP

Adjustable to get a bright light on miniature components. With bracket for clamping or bolting to bench or wall. Shade and position fully adjustable and stable. Finished in white. Order as XY25C Price £12.96

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until June 15th 1980. Export customers deduct 13% and export postage will be charged extra at cost.

Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER

MARPLIN

ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex S86 8LR. Telephone: Southend (0702) 554155
Shop: 284 London Road, Westcliff on Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000

RAVEN ON

As the chip industry experiences problems in maintaining its rate of growth Dave Raven explains why and casts a glance at bubble memories.

In complete contrast to most manufactured goods integrated circuit pricing has remained on a steady, decreasing spiral. There is, however, a school of thought which sees this rapidly coming to an end.

With the ever increasing effects of inflation, which is not of course exclusive to the UK, the end of the manufacturers experience learning curve is in sight. The cost of producing linear devices is already said to be rising in the States and signals indicate that digitals will soon follow. This stems from a theory which says that every time accumulated experience doubles, costs and, therefore, prices go down by about 25 per cent. With the pressure from increasing demand for ICs, manufacturers have more than doubled accumulated experience every year, which pushed prices downwards. This theory has apparently proved valid in the industry for many years.

In effect, what is being suggested is that if, from the inception of the IC industry, 10 million devices have been sold by the end of a given year, it would have to sell 10 million devices the following year in order to lower prices by as much as 25 per cent. The following year 20 million devices must be sold to achieve another 25 per cent reduction. Clearly a point must be reached where this rate of growth could not be maintained. The suggestion is that the time has now arrived.

Accumulated shipments of Integrated Circuits reached 11.4 billion units in 1978. During 1979 the total sales of ICs was expected to reach about 5 billion units. If it is assumed that the United States IC industry ships 6.5 billion devices in 1980, it will have taken two years to double accumulated shipments. Therefore, if the theory holds true the price of ICs will have dropped by an average of 25 per cent. Inflation, however, over the two year period is going to more than offset the 25 percent price declines and could even exceed this. Technically, the digital integrated circuits have a more favourable price outlook than linear, since it is still possible to shrink more circuitry into a silicon slice. Designers are, however, experiencing increasing difficulties with the physical limitations posed by one millionth of a metre gate lengths and the effects of stray capacitance and in addition the demands being made on chip manufacturers for a host of new consumer products which appear each year.

To illustrate some of the technical difficulties that have to be overcome in producing 1 micron lines, it is best to explain the techniques that can be used to produce these. The cheapest method is to use photolithography, which is well established for device fabrication. Using a procedure called 'float off' it is possible to define very narrow channels which are chemically etched and a metal is evaporated through the channel producing a very narrow line. The problems that can arise, however, are shown in the photographs and are not easily overcome even with the very sophisticated manufacturing techniques in use today.

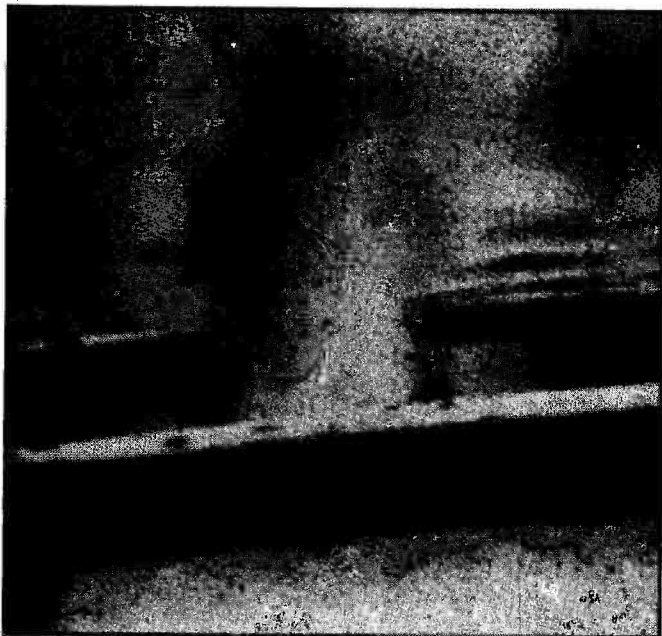


PHOTO 1: an etched channel before deposition of metal to complete the gate.

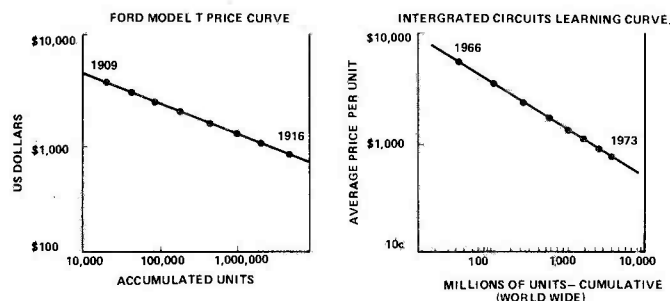


Fig.1. Similarities between price trends for the Model-T Ford and integrated circuits.

The first photograph shows the etched channel before metal is deposited. Distance between the overhang is approximately two microns. The second photograph illustrates the metal deposited through the channel. Photograph three is an example of what can go wrong when the edges of the overhang break down, causing an electrical short. Each ledge is approximately 1.5 microns. This example is somewhat crude in present day technology. However, it serves to show quite clearly the mechanical effects of fabricating devices using these very tiny dimensions.

Electron beam lithography is improving the yield of integrated circuits plus increasing the chip density, thus overcoming many of the earlier problems. Once again, however, this equipment is not cheap and will further increase the already heavy capital investment required. The author of a recent article in an American device technology magazine produced comparisons between the product-