


electronics today

INTERNATIONAL SEPTEMBER 1980 60p

ISSN. 0142-7229

PROJECTS FOR ALL!

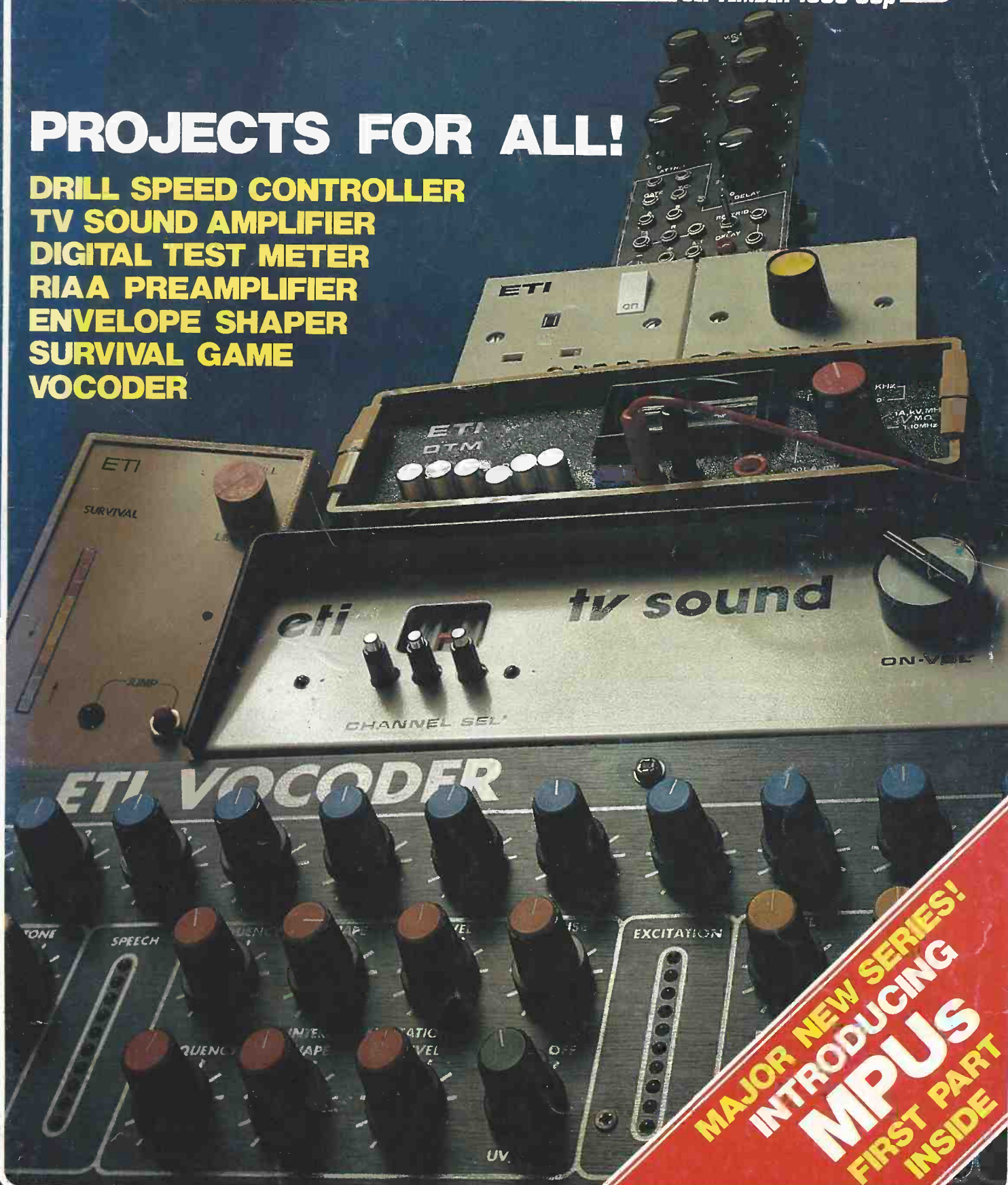DRILL SPEED CONTROLLER
TV SOUND AMPLIFIER
DIGITAL TEST METER
RIAA PREAMPLIFIER
ENVELOPE SHAPER
SURVIVAL GAME
VOCODER



MAJOR NEW SERIES!
INTRODUCING
MPUS
FIRST PART
INSIDE

...NEWS...PROJECTS...MICROPROCESSORS...AUDIO...

8K ON BOARD MEMORY!

5K RAM. 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

KANSAS CITY

low error rate tape interface.

PSI COMP 80
Z80 Based powerful
scientific computer
design as published
in
WIRELESS WORLD



Cabinet size 19.0" x 15.7" x 3.3". Television not included in price

2 MICROPROCESSORS

Z80 the powerful CPU with 158 instructions, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10^{-99} to 9×10^{99} to 8 figures plus 2 exponent digits.

EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

1K MONITOR

resident in EPROM.

SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.

COMPLETE KIT
NOW ONLY
£225 + VAT

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete. Included in the PSICOMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board. 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer. 2K Basic and 1K monitor in EPROMs and, of course, wire, nuts, bolts, etc.

KIT ALSO AVAILABLE AS SEPARATE PACKS

For those customers who wish to spread their purchase or build a personalised system the kit is available as separate packs eg. PCB (16" x 12.5") £43.20. Pair of keyboards £34.80. Firmware in EPROMS £30.00. Toroidal transformer and power supply components £17.50. Cabinet (very rugged, made from steel, really beautifully finished) £25.50. P.S. Will greatly enhance any other single board computer including OHIO SUPERBOARD for which it can be readily modified. Other packs listed in our FREE CATALOGUE.

PSI COMP 80 Memory Expansion System

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3 8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion socket is made via a ribbon cable.

Mother board:

Fibre glass double sided plated through hole P.C.B. 8.7" x 3.0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug £39.90

8K Static RAM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" £12.50
Set of components including IC sockets, plug and socket but excluding RAMs £11.20
2114L RAM (16 required) £5.00
Complete set of board, components, 16 RAMS £89.50

8K ROM board

Fibre glass double sided plated through hole P.C.B. 5.6" x 4.8" £12.40
Set of components including IC sockets, plug and socket but excluding ROMs £10.70
2708 ROM (8 required) £8.00
Complete set of board, components, 8 ROMs £78.50

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!
POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

THIS MONTH'S FRONT COVER FEATURE!
★ **ETI VOCODER** ★



Panel size 19.0" x 5.25". Depth 12.2".

14 CHANNELS!
NOISE GENERATOR!
SLEW RATE CONTROL!

2 OSCILLATORS!
VOICED/UNVOICED DETECTOR!
LED PPM METERS!

COMPLETE KIT ONLY £195 + VAT

Kit includes FREE foot control and test oscillator!

Like all our kits the ETI VOCODER really is complete — fully finished metal work, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc. — even a 13A plug!

MANY MORE KITS
ON PAGE 8

POWERTRAN

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until October 31, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m. - 12 noon, 1-4.30 p.m. Monday-Thursday.



Vocoder ETI excitation p.58



Testing Time p.79

electronics today

SEPTEMBER 1980 VOL 9 No 9 INTERNATIONAL

FEATURES

- | | |
|--------------------|--------------------------------------|
| NEWS | 7 The first and best right here. |
| HEAD AMP DESIGN | 15 Matching your moving coil. |
| CURRENT AFFAIRS | 23 Conducive reading this. |
| MICRO BASICS | 28 A potted computer history. |
| SPOT DESIGNS | 34 Tested circuits for all. |
| AUDIOPHILE | 39 It's music to your ears. |
| RAVEN ON | 44 This one'll leave you speechless. |
| DESIGNERS NOTEBOOK | 48 An attenuated Project Editor. |
| TECH TIPS | 53 We leave it up to you. |

PROJECTS

- | | |
|------------------------|---------------------------------------|
| VOCODER | 58 Orchestrate your vocals. |
| DRILL SPEED CONTROLLER | 69 Holy smoke! |
| TV SOUND TUNER | 73 Sound and vision. |
| DIGITAL TEST METER | 79 Are your digitals up to scratch? |
| SURVIVAL GAME | 87 It's do or die on this one. |
| ENVELOPE SHAPER | 93 Shape your keyboards. |
| RIA A PREAMP | 98 Pure magnetism. |
| FOIL PATTERNS | 102 The nitty-gritty of our projects. |

INFORMATION

- | | |
|-------------------|--------------------------|
| NEXT MONTHS ETI | 14 Look out for October. |
| NEXT MONTH'S CT | 31 Fill your RAMs here. |
| CLOCK RADIO OFFER | 41 Time for a tune. |
| BOOK SERVICE | 85 A tome for the home. |
| ETIPRINTS | 105 PCBs galore. |

OVERSEAS EDITIONS

- AUSTRALIA : Roger Harrison
Editor
- CANADA : Halvor Moorshead
Editor
- GERMANY : Udo Wittig
Editor
- HOLLAND : Anton Kriegsman
Editor



Member of the
Audit Bureau
of Circulation

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5

- | | |
|----------------------|-----------------------------|
| Ron Harris B.Sc. | Editor |
| Ian Graham B.Sc. | Assistant Editor |
| Tina Boylan | Editorial Assistant |
| Diego M. Rincon | Art Director |
| Paul Edwards | Drawing Office Manager |
| Ray Marston | Project Editor |
| Christopher Surgenor | Group Advertisement Manager |
| Steven Rowe | Advertisement Manager |
| T.J. Connell | Managing Director |

PUBLISHED BY DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road, WC2
Argus Distribution Ltd. (British Isles)
12-18 Paul Street, London
Gordon & Gotch Ltd. (Overseas)
QB Limited, Colchester

PRINTED BY

Electronics Today is normally published on the first Friday in the month preceding cover date.

©MODMAGS LTD 1980: All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine, contents, but the publishers cannot be held responsible for errors legally. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription Rates : UK £10 including postage. Airmail and other rates upon application to ETI Subscriptions Service, PO Box 35, Bridge Street, Hemel Hempstead, Herts.

Britain's first com computer kit.

The Sinclair ZX80.

£79.95

Price breakdown
ZX80 and manual: £69.52
VAT: £10.43
Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews...you've heard the excitement...now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home...PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour): *everything!*

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done; connect it to your TV...link it to an appropriate power source*...and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVED and LOADED on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:

- **Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.**
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions. USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.


Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines.

And Benchmark tests show that the ZX80 is faster than all other personal computers.

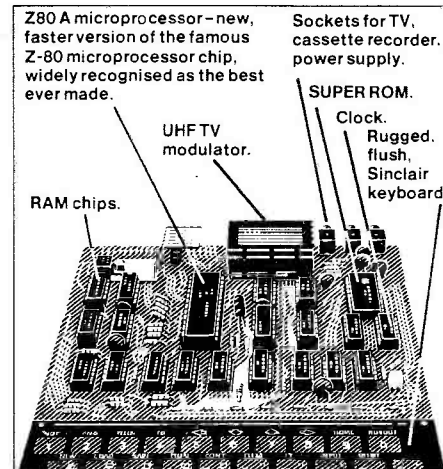No other personal computer offers this unique combination of high capability and low price.




plete



ZX80 software – now available!

See advertisements in Personal Computer World, Electronics Today International, and other journals.

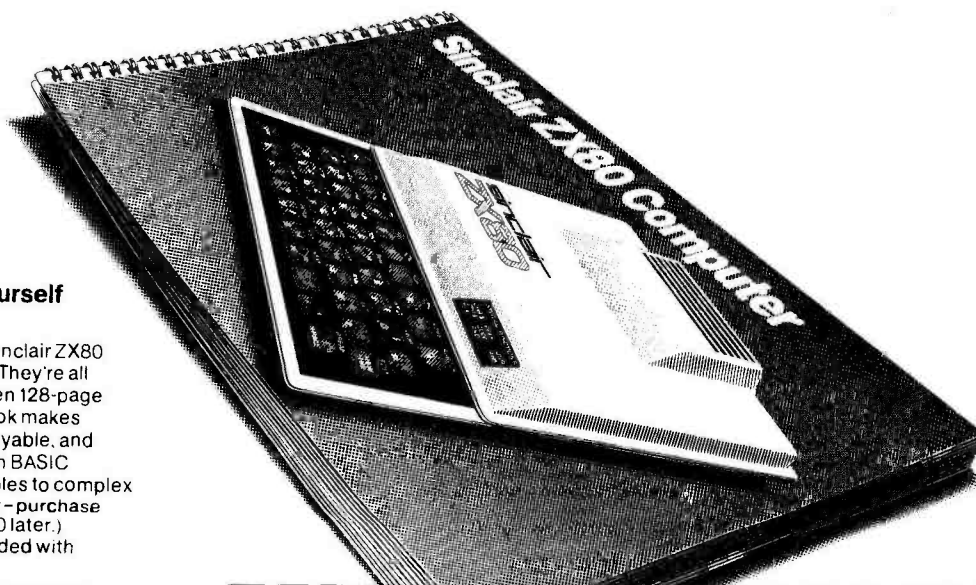New dedicated software – developed independently of Science of Cambridge – reflects the enormous interest in the ZX80. More software available soon – from leading consultancies and software houses.



The Sinclair teach-yourself BASIC manual.

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled and complete with mains adaptor, for only £99.95.

Demand for the ZX80 is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

sinclair

ZX80

Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ETI SEPTEMBER 1980

ORDER FORM

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.
Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor	£79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor	£99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated)	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes)	12.00	
	RAM Memory chips – standard 1K bytes capacity	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer)	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense.

TOTAL £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____
Please print

Name: Mr/Mrs/Miss _____

Address _____

ETI/9/80

TTLs by TEXAS		74290 150p 4020 100p	9301 160p 74S00 80p	74S114 120p	TRANSISTORS		BFR40 25p	TIP31A 58p	2N3553 240p	40409 85p	10A 400V 200p	
7400 11p	74293 150p 4021 110p	9302 175p 74S01 80p	74S115 120p	AC126 25p	BFR41 25p	TIP31C 82p	2N3554 240p	40410 85p	10A 400V 200p	ZENERS	2.7V-33V 400mW 1W 15p	
7401 12p	74294 150p 4022 120p	9303 315p 74S02 80p	74S116 120p	AC127/8 20p	BFR42 25p	TIP31D 82p	2N3555 240p	40411 85p	10A 400V 200p			
7402 13p	74295 150p 4023 27p	9304 315p 74S03 80p	74S117 120p	AC128 25p	BFR43 25p	TIP31E 82p	2N3556 240p	40412 85p	10A 400V 200p	TRIACS		
7403 14p	74296 150p 4024 20p	9305 315p 74S04 80p	74S118 120p	AF116 50p	BFR44 25p	TIP31F 82p	2N3557 240p	40413 85p	10A 400V 200p	PLASTIC		
7404 14p	74297 150p 4025 20p	9306 315p 74S05 80p	74S119 120p	AF117 50p	BFR45 25p	TIP31G 82p	2N3558 240p	40414 85p	10A 400V 200p	DIODES		
7405 18p	74298 150p 4026 20p	9307 315p 74S06 80p	74S120 120p	AD149 70p	BFR46 25p	TIP31H 82p	2N3559 240p	40415 85p	10A 400V 200p	BY127 12p	3A 400V 60p	
7406 18p	74299 150p 4027 50p	9308 315p 74S07 80p	74S121 120p	AD150 70p	BFR47 25p	TIP31I 82p	2N3560 240p	40416 85p	10A 400V 200p	BY128 12p	3A 400V 60p	
7407 38p	74300 150p 4028 80p	9309 315p 74S08 80p	74S122 120p	AD151 70p	BFR48 25p	TIP31J 82p	2N3561 240p	40417 85p	10A 400V 200p	BY129 12p	3A 400V 60p	
7408 17p	74301 150p 4029 100p	9310 315p 74S09 80p	74S123 120p	AD152 70p	BFR49 25p	TIP31K 82p	2N3562 240p	40418 85p	10A 400V 200p	BY130 12p	3A 400V 60p	
7409 19p	74302 150p 4030 200p	9311 315p 74S10 80p	74S124 120p	AD153 70p	BFR50 25p	TIP31L 82p	2N3563 240p	40419 85p	10A 400V 200p	BY131 12p	3A 400V 60p	
7410 19p	74303 150p 4031 200p	9312 315p 74S11 80p	74S125 120p	AD154 70p	BFR51 25p	TIP31M 82p	2N3564 240p	40420 85p	10A 400V 200p	BY132 12p	3A 400V 60p	
7411 20p	74304 150p 4032 180p	9313 315p 74S12 80p	74S126 120p	AD155 70p	BFR52 25p	TIP31N 82p	2N3565 240p	40421 85p	10A 400V 200p	BY133 12p	3A 400V 60p	
7412 20p	74305 150p 4033 180p	9314 315p 74S13 80p	74S127 120p	AD156 70p	BFR53 25p	TIP31O 82p	2N3566 240p	40422 85p	10A 400V 200p	BY134 12p	3A 400V 60p	
7413 20p	74306 150p 4034 295p	9315 315p 74S14 80p	74S128 120p	AD157 70p	BFR54 25p	TIP31P 82p	2N3567 240p	40423 85p	10A 400V 200p	BY135 12p	3A 400V 60p	
7414 40p	74307 150p 4035 115p	9316 315p 74S15 80p	74S129 120p	AD158 70p	BFR55 25p	TIP31Q 82p	2N3568 240p	40424 85p	10A 400V 200p	BY136 12p	3A 400V 60p	
7415 40p	74308 150p 4036 120p	9317 315p 74S16 80p	74S130 120p	AD159 70p	BFR56 25p	TIP31R 82p	2N3569 240p	40425 85p	10A 400V 200p	BY137 12p	3A 400V 60p	
7416 27p	74309 150p 4037 115p	9318 315p 74S17 80p	74S131 120p	AD160 70p	BFR57 25p	TIP31S 82p	2N3570 240p	40426 85p	10A 400V 200p	BY138 12p	3A 400V 60p	
7417 27p	74310 150p 4038 120p	9319 315p 74S18 80p	74S132 120p	AD161 70p	BFR58 25p	TIP31T 82p	2N3571 240p	40427 85p	10A 400V 200p	BY139 12p	3A 400V 60p	
7418 27p	74311 150p 4039 120p	9320 315p 74S19 80p	74S133 120p	AD162 70p	BFR59 25p	TIP31U 82p	2N3572 240p	40428 85p	10A 400V 200p	BY140 12p	3A 400V 60p	
7419 27p	74312 150p 4040 120p	9321 315p 74S20 80p	74S134 120p	AD163 70p	BFR60 25p	TIP31V 82p	2N3573 240p	40429 85p	10A 400V 200p	BY141 12p	3A 400V 60p	
7420 27p	74313 150p 4041 80p	9322 315p 74S21 80p	74S135 120p	AD164 70p	BFR61 25p	TIP31W 82p	2N3574 240p	40430 85p	10A 400V 200p	BY142 12p	3A 400V 60p	
7421 40p	74314 150p 4042 80p	9323 315p 74S22 80p	74S136 120p	AD165 70p	BFR62 25p	TIP31X 82p	2N3575 240p	40431 85p	10A 400V 200p	BY143 12p	3A 400V 60p	
7422 22p	74315 150p 4043 80p	9324 315p 74S23 80p	74S137 120p	AD166 70p	BFR63 25p	TIP31Y 82p	2N3576 240p	40432 85p	10A 400V 200p	BY144 12p	3A 400V 60p	
7423 22p	74316 150p 4044 80p	9325 315p 74S24 80p	74S138 120p	AD167 70p	BFR64 25p	TIP31Z 82p	2N3577 240p	40433 85p	10A 400V 200p	BY145 12p	3A 400V 60p	
7424 30p	74317 150p 4045 80p	9326 315p 74S25 80p	74S139 120p	AD168 70p	BFR65 25p	TIP31AA 82p	2N3578 240p	40434 85p	10A 400V 200p	BY146 12p	3A 400V 60p	
7425 30p	74318 150p 4046 80p	9327 315p 74S26 80p	74S140 120p	AD169 70p	BFR66 25p	TIP31AB 82p	2N3579 240p	40435 85p	10A 400V 200p	BY147 12p	3A 400V 60p	
7426 30p	74319 150p 4047 100p	9328 315p 74S27 80p	74S141 120p	AD170 70p	BFR67 25p	TIP31AC 82p	2N3580 240p	40436 85p	10A 400V 200p	BY148 12p	3A 400V 60p	
7427 30p	74320 150p 4048 55p	9329 315p 74S28 80p	74S142 120p	AD171 70p	BFR68 25p	TIP31AD 82p	2N3581 240p	40437 85p	10A 400V 200p	BY149 12p	3A 400V 60p	
7428 30p	74321 150p 4049 55p	9330 315p 74S29 80p	74S143 120p	AD172 70p	BFR69 25p	TIP31AE 82p	2N3582 240p	40438 85p	10A 400V 200p	BY150 12p	3A 400V 60p	
7429 30p	74322 150p 4050 48p	9331 315p 74S30 80p	74S144 120p	AD173 70p	BFR70 25p	TIP31AF 82p	2N3583 240p	40439 85p	10A 400V 200p	BY151 12p	3A 400V 60p	
7430 30p	74323 150p 4051 48p	9332 315p 74S31 80p	74S145 120p	AD174 70p	BFR71 25p	TIP31AG 82p	2N3584 240p	40440 85p	10A 400V 200p	BY152 12p	3A 400V 60p	
7431 30p	74324 150p 4052 80p	9333 315p 74S32 80p	74S146 120p	AD175 70p	BFR72 25p	TIP31AH 82p	2N3585 240p	40441 85p	10A 400V 200p	BY153 12p	3A 400V 60p	
7432 30p	74325 150p 4053 80p	9334 315p 74S33 80p	74S147 120p	AD176 70p	BFR73 25p	TIP31AI 82p	2N3586 240p	40442 85p	10A 400V 200p	BY154 12p	3A 400V 60p	
7433 30p	74326 150p 4054 150p	9335 315p 74S34 80p	74S148 120p	AD177 70p	BFR74 25p	TIP31AJ 82p	2N3587 240p	40443 85p	10A 400V 200p	BY155 12p	3A 400V 60p	
7434 30p	74327 150p 4055 125p	9336 315p 74S35 80p	74S149 120p	AD178 70p	BFR75 25p	TIP31AK 82p	2N3588 240p	40444 85p	10A 400V 200p	BY156 12p	3A 400V 60p	
7435 30p	74328 150p 4056 135p	9337 315p 74S36 80p	74S150 120p	AD179 70p	BFR76 25p	TIP31AL 82p	2N3589 240p	40445 85p	10A 400V 200p	BY157 12p	3A 400V 60p	
7436 30p	74329 150p 4057 135p	9338 315p 74S37 80p	74S151 120p	AD180 70p	BFR77 25p	TIP31AM 82p	2N3590 240p	40446 85p	10A 400V 200p	BY158 12p	3A 400V 60p	
7437 30p	74330 150p 4058 135p	9339 315p 74S38 80p	74S152 120p	AD181 70p	BFR78 25p	TIP31AN 82p	2N3591 240p	40447 85p	10A 400V 200p	BY159 12p	3A 400V 60p	
7438 30p	74331 150p 4059 135p	9340 315p 74S39 80p	74S153 120p	AD182 70p	BFR79 25p	TIP31AO 82p	2N3592 240p	40448 85p	10A 400V 200p	BY160 12p	3A 400V 60p	
7439 30p	74332 150p 4060 135p	9341 315p 74S40 80p	74S154 120p	AD183 70p	BFR80 25p	TIP31AP 82p	2N3593 240p	40449 85p	10A 400V 200p	BY161 12p	3A 400V 60p	
7440 17p	74333 150p 4061 135p	9342 315p 74S41 80p	74S155 120p	AD184 70p	BFR81 25p	TIP31AQ 82p	2N3594 240p	40450 85p	10A 400V 200p	BY162 12p	3A 400V 60p	
7441 70p	74334 150p 4062 135p	9343 315p 74S42 80p	74S156 120p	AD185 70p	BFR82 25p	TIP31AR 82p	2N3595 240p	40451 85p	10A 400V 200p	BY163 12p	3A 400V 60p	
7442 70p	74335 150p 4063 135p	9344 315p 74S43 80p	74S157 120p	AD186 70p	BFR83 25p	TIP31AS 82p	2N3596 240p	40452 85p	10A 400V 200p	BY164 12p	3A 400V 60p	
7443 112p	74336 150p 4064 135p	9345 315p 74S44 80p	74S158 120p	AD187 70p	BFR84 25p	TIP31AT 82p	2N3597 240p	40453 85p	10A 400V 200p	BY165 12p	3A 400V 60p	
7444 112p	74337 150p 4065 135p	9346 315p 74S45 80p	74S159 120p	AD188 70p	BFR85 25p	TIP31AU 82p	2N3598 240p	40454 85p	10A 400V 200p	BY166 12p	3A 400V 60p	
7445 112p	74338 150p 4066 135p	9347 315p 74S46 80p	74S160 120p	AD189 70p	BFR86 25p	TIP31AV 82p	2N3599 240p	40455 85p	10A 400V 200p	BY167 12p	3A 400V 60p	
7446 63p	74339 150p 4067 450p	9348 315p 74S47 80p	74S161 120p	AD190 70p	BFR87 25p	TIP31AW 82p	2N3600 240p	40456 85p	10A 400V 200p	BY168 12p	3A 400V 60p	
7447 63p	74340 150p 4068 27p	9349 315p 74S48 80p	74S162 120p	AD191 70p	BFR88 25p	TIP31AX 82p	2N3601 240p	40457 85p	10A 400V 200p	BY169 12p	3A 400V 60p	
7448 80p	74341 150p 4069 27p	9350 315p 74S49 80p	74S163 120p	AD192 70p	BFR89 25p	TIP31AY 82p	2N3602 240p	40458 85p	10A 400V 200p	BY170 12p	3A 400V 60p	
7449 80p	74342 150p 4070 27p	9351 315p 74S50 80p	74S164 120p	AD193 70p	BFR90 25p	TIP31AZ 82p	2N3603 240p	40459 85p	10A 400V 200p	BY171 12p	3A 400V 60p	
7450 80p	74343 150p 4071 27p	9352 315p 74S51 80p	74S165 120p	AD194 70p	BFR91 25p	TIP31BA 82p	2N3604 240p	40460 85p	10A 400V 200p	BY172 12p	3A 400V 60p	
7451 17p	74344 150p 4072 25p	9353 315p 74S52 80p	74S166 120p	AD195 70p	BFR92 25p	TIP31BB 82p	2N3605 240p	40461 85p	10A 400V 200p	BY173 12p	3A 400V 60p	
7452 17p	74345 150p 4073 25p	9354 315p 74S53 80p	74S167 120p	AD196 70p	BFR93 25p	TIP31BC 82p	2N3606 240p	40462 85p	10A 400V 200p	BY174 12p	3A 400V 60p	
7453 17p	74346 150p 4074 25p	9355 315p 74S54 80p	74S168 120p	AD197 70p	BFR94 25p	TIP31BD 82p	2N3607 240p	40463 85p	10A 400V 200p	BY175 12p	3A 400V 60p	
7454 17p	74347 150p 4075 25p	9356 315p 74S55 80p	74S169 120p	AD198 70p	BFR95 25p	TIP31BE 82p	2N3608 240p	40464 85p	10A 400V 200p	BY176 12p	3A 400V 60p	
7455 17p	74348 150p 4076 107p	9357 315p 74S56 80p	74S170 120p	AD199 70p	BFR96 25p	TIP31BF 82p	2N3609 240p	40465 85p	10A 400V 200p	BY177 12p	3A 400V 60p	
7456 17p	74349 150p 4077 107p	9358 315p 74S57 80p	74S171 120p	AD200 70p	BFR97 25p	TIP31BG 82p	2N3610 240p	40466 85p	10A 400V 200p	BY178 12p	3A 400V 60p	
7457 17p	74350 150p 4078 27p	9359 315p 74S58 80p	74S172 120p	AD201 70p	BFR98 25p	TIP31BH 82p	2N3611 240p	40467 85p	10A 400V 200p	BY179 12p	3A 400V 60p	
7458 17p	74351 150p 4079 27p	9360 315p 74S59 80p	74S173 120p	AD202 70p	BFR99 25p	TIP31BI 82p	2N3612 240p	40468 85p	10A 400V 200p	BY180 12p	3A 400V 60p	
7459 17p	74352 150p 4080 27p	9361 315p 74S60 80p	74S174 120p	AD203 70p	BFR100 25p	TIP31BJ 82p	2N3613 240p	40469 85p	10A 400V 200p	BY181 12p	3A 400V 60p	
7460 17p	74353 150p 4081 27p	9362 315p 74S61 80p	74S175 120p	AD204 70p	BFR101 25p	TIP31BK 82p	2N3614 240p	40470 85p	10A 400V 200p	BY182 12p	3A 400V 60p	
7461 17p												

DIGEST

Booking Up

Bernard Babani (Publishing) Ltd of The Grampians, Shepherds Bush Road, London W6 7NF have brought out a brand new catalogue of Radio and Electronics books which they publish. They cover such subjects as Electronics, Semiconductors, Computers, Television, Radio, Hi-fi, etc. Whether you are a hobbyist, engineer, designer or student, they have something for you. The catalogue is free, just send them a reasonably large stamped addressed envelope and you will receive your copy by return.

Power Cuts On The Way

In 1968 your 20 inch colour telly using 90° deflection would have consumed over 200 W. Now, the figure is around 65 W. A new development from Finland will further reduce that to about 40 W.

The system, which results in a reduction of about 40% in power consumption, has been incorporated in the Salora G Series of portable colour sets. The design is basically a 90% efficient couple between the power supply and picture tube using an induction transfer system. The resultant cool running improves reliability and extends operational life.



The G Series, with its 16, 20 and 22 inch models, will operate from a standard 60A/hour 12 V battery for 15 hours, or from mains for as long as you pay your bills.

All the models feature automatic electronic tuning, fine

tuning and memory plus add-on options for remote control, 12 V battery and video frequency interface unit.

Salora products are available in the UK from Salora (UK) Ltd, 25A Techno Trading Estate, Swindon SN2 6EZ.

Computer Aided Yacht Race

This year the 1980 Observer Single Handed Transatlantic Yacht Race is being aided by a computer-based system. Known as the Argos system, each of the yachts involved in the race has an on-board transmitter which emits a signal picked up by two satellites regularly crossing the Atlantic. These signals are then rebounded to earth for decoding and processing. The information is fed via Toulouse in France to a CII Honeywell Bull computer in Paris and then is further processed by a Micral Computer in the Paris offices of Europe 1 radio sta-

tion. A Benson drafting machine on line to this computer is then able to give a graphic representation of the yachts' positions. This information is used by the radio station for its coverage of the race and also allows the race organisers to keep a constant eye on the progress of each yacht. This means increased safety for the race, as Coastguards can be immediately notified if they are in difficulty. After the disasters which occurred during last year's Fastnet race, this system will hopefully increase the safety factor in open sea racing.

EMP — The Govt. Speaks

Your Ref.....

HOME OFFICE,

QUEEN ANNE'S GATE,

LONDON, SW1H 9AT

Our Ref.....

27. 7. 1980

The Under Secretary of State desires to acknowledge the receipt of your letter of the 27. 6. 80 which is receiving attention.

This is the entire text of the replies we have received to date from the vast machinery of the British government. Receiving attention? We shall keep plugging away though, and report any sensible answers we do manage to obtain. Meanwhile what are your views on the subject of EMP? Let's hear about them.

Powering Down

Every piece of electrical and electronic equipment needs a power supply of some sort. Larsen Sweeney's latest forecast of the use of power supplies in Europe up to 1986 reports a general downtrend. Not only is the general power supply business slowing down, but, in particular, newer supply systems, eg switching regulated and switched mode, are also feeling the pinch. This is largely a result of a slowdown in new product design and development.

The report warns that British power supply designers are at a distinct disadvantage in this marketplace and many will not

survive the recession. Their competitors in West Germany, France, Sweden and Japan are supported financially by their respective governments, but the British companies are on their own.

The 243 page Larsen Sweeney report covers 16 European countries and 34 power supply product groups, including sections on marketing, the industry, the end user and distributors. Every home should have one. You'll have to raid the piggy bank, though. 'Power Supply In Europe To 1986' will set you back £695. Beat the rush... send your life savings now to Larsen Sweeney Publications Ltd, P O Box 36, Maidstone, Kent.

Vetting VDUs

If your work involves reading data from a telly screen (operating a computer terminal, for instance) you may occasionally wonder if it affects your eyesight, especially if you go home every night with a splitting headache.

The twin evils of radiation and eyestrain have attracted some attention with respect to VDU usage. For this reason the VDU Eye Test (VET) Advisory Group was set up to devise a test package for VDU users. Their final report has now been published as a 12 page booklet.

The Group found 'that no significant hazard from X-ray, ultra-violet, visible or RF radiation has been detected' in modern VDU design. Moreover, the

Group found no evidence that VDU use could cause eyestrain. We consulted a practising Ophthalmic Optician who told us that normal use of the eyes cannot cause damage.

The report did, however, list several factors that could cause discomfort, which the layman might call eyestrain. These included the posture of the VDU user and the working environment.

The Group concluded that VDUs can be used safely, if designed and intalled with proper attention to the user's ergonomic requirements. Where there is intensive use of VDUs, the user's eyesight should be checked with the test recommended in the report.


If you would like a copy of the VET Advisory Group's report, write to Tom Stewart, Butler Cox & Partners Ltd, Morley House, 26-30 Holborn Viaduct, London EC1A 2BF.

TRANSCENDENT DPX

DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER

Another superb design by synthesizer expert Tim Orr — published in Electronics Today International

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic strong sounds.

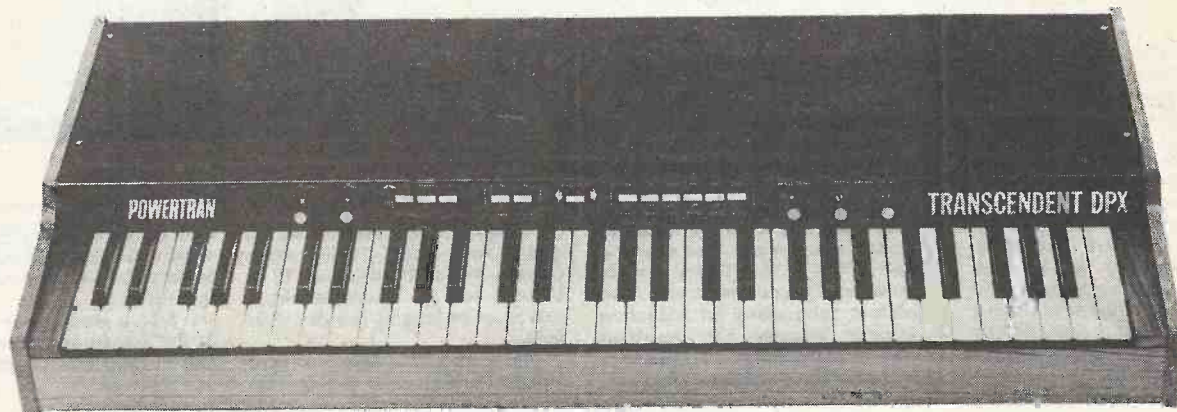

Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

COMPLETE KIT ONLY £299 + VAT

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects. As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.)

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

POWERTRAN

MANY MORE KITS ON PAGE 110 MORE KITS AND ORDERING INFORMATION ON INSIDE FRONT COVER

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an effective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.


The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

**COMPLETE KIT ONLY
£168.50 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



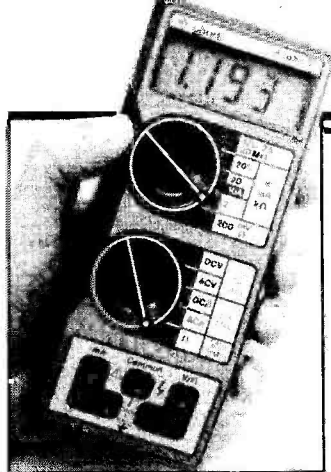Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)



Metering Your Multis

The Alpha V is the latest and smallest hand-held digital multimeter from Gould Instruments. It has a 3½-digit liquid crystal display with 25 measuring ranges covering the five basic functions of DC voltage, AC voltage, DC current, AC current and resistance. It has a maximum reading of 1999 and maximum resolution of 100 µV. Range and function selection is by two rotary switches on the clearly coded front panel. The multimeter is powered by a 9 V carbon zinc or alkaline battery (PP3 or equivalent), the latter giving a typical life of 200 hours. There is a battery low indicator provided by the display, which shows 'BAT' when less than 10% of useful battery life remains. The case is of high-impact ABS plastic and the display is shock mounted behind a polycarbonate plastic window. Accessories supplied with the basic instrument include standard red and black test leads, battery and handbook. The cost is £85.00 (plus VAT) from Gould Instruments Division, Roebuck Road, Haina

Anti Car Theft


Maywood Security Services Ltd. is marketing a method of deterring vehicle thieves. A mobile service is offered which involves abrading the vehicle registration number on every window of a car, caravan, commercial vehicle or boat. This means that in order to mask the identity of a stolen car the thieves must replace all of its windows. The abrading process takes about five minutes at a cost of about £5 per vehicle (quantity discounts may be given). Maywood Security Services Ltd are operating as a franchise for Safecar and they will quite happily call at your place of work or home. This method has received the support of police crime prevention officers throughout the country who have to deal with some 350,000 vehicle thefts a year. The address is Maywood Security Services Ltd, Peake House, 232 High Street, Harlington, Hayes, Middlesex, UB3 5DS. They cover North West, West and South West London.

Status Symbols

Raindirk of Downham Market Norfolk are now supplying the Status range of audio equipment. Their Status 500 power amplifier delivers 250 W per channel into 8R, using power MOSFET output stages. The Status 20 Stereo Control Unit is a rack-mounting system with a modular disc replay amplifier that can be remotely located, three band equaliser with continuously variable turn-over frequencies, built-in headphone amplifiers and external mains power supply. The range will soon also include a parametric equaliser. You can get more information on the Status 500 and the rest of the Status range from Raindirk Ltd, Downham Market, Norfolk.

Sharp Shapes

Sharp Corporation are now marketing an alternative to conventional tubular LEDs. They are designed for flush fitting to front panels and are currently offered in the form of round 'point' indicators, equilateral and isosceles triangles, square and flat sections, all in three different sizes, (3, 4, and 5 mm) and three different colours — red, yellow and green. The shapes make good function indicators and the 'squares and flats' can be stacked to form bar graphs. For 1,000 pieces the price is between 5p and 10p each depending on the size, shape and colour. They are available from CRP Electronics Ltd, 13 Hazelbury Crescent, Luton, LU1 1DF.

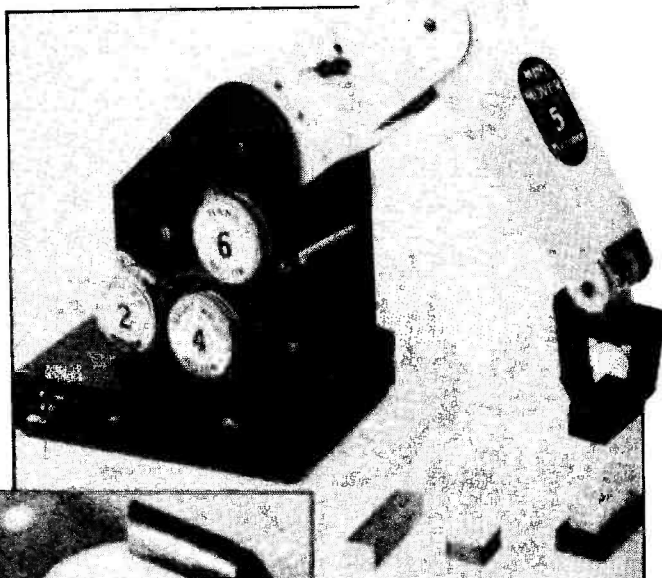

Defence Ministries and may become an industry standard.

Aimed at managers, engineers and programmers, ICS's 'Computerised Robots' course will pinpoint where the new breed of 'intelligent' robots can be used to increase productivity and streamline production.

Japan is currently the major employer of robot labour with 6,000 in use (40,000 if you include the simplest automata). The USA has 3,500 while Europe has only 2,000. If computer companies enter the robotics market, it is estimated that there could be 200,000 robots in use by 1990 in the USA alone with over 35% of all production in robot 'hands' by the turn of the century. As the increasing use of robot labour changes the face of society, all we will need is a machine that enjoys living in it.

You can get more information on the course programme from Dr David C Collins, ICS Publishing Co Ltd, Pebblecoombe, Tadworth, Surrey.

Robot School

Integrated Computer Systems Inc. have announced details of their new courses in 'ADA' and 'Computerised Robots'. 'ADA', a new high level computer language, has been developed by the US Department of Defence in co-ordination with European

Small is Beautiful

A miniature hi-fi system is now available from Mitsubishi Electric, called 'System 4'. It delivers 50 W per channel, both channels driven into 8R and it measures 27W x 42.4H x 27cmD. The four units consist of the M-A04 Power-amp, M-P04 pre-amplifier, M-F04 AM/FM Tuner and the M-T04 front-loading Cassette Deck which is metal tape compatible. Their latest speaker system is also available. A 50 W 8R two way infinite baffle speaker, the SS 630E, retails at £115.00 for the pair. Frequency response is 60 Hz to 22 kHz and dimensions are 305W x 544H x 257mmD.




Don't buy a digital watch until you read this report

There are so many digital watches on the market, with varying functions, that the average person is bound to feel somewhat confused.

A new survey of the electronic watch industry has been produced to clarify this confusion and to give an unbiased and objective answer to the many questions that are constantly being raised.

by Trevor Raven.
C.Eng. AMBIM. MIERE

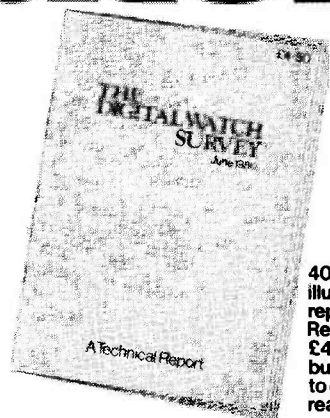

40 page
illustrated
report.
Retail price
£4.50
but just £1
to our
readers.

- * How accurate are electronic watches?
- * Who makes Seiko's?
- * What is the importance between brand names?
- * Is solar power worth the extra money?
- * What are the most important features in a watch?
- * When will prices stop falling?


The survey answers all of these questions and tells you what to look for in a quartz watch; how they work; why the prices vary so much; what the future holds.

SPECIAL OFFER

Send today for this technical report, plus news of a unique Metac offer to beat all special offers.

Complete the coupon below and send it FREEPOST (no stamp required) and we will post, Same Day Despatch, the technical report giving you all you need to know about electronic watches and details of our special offer.

Which is the best watch?

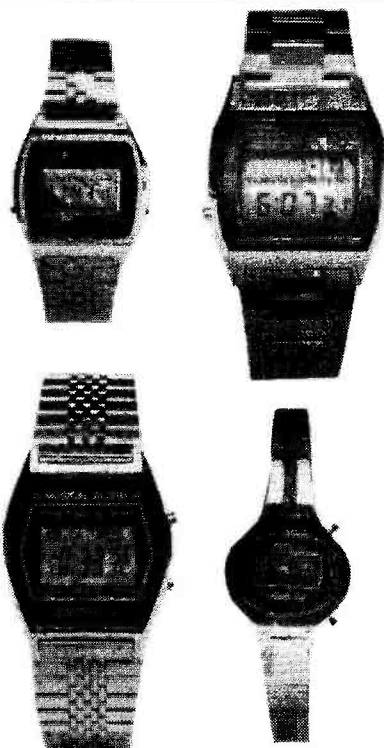

These four watches are very different in price, durability and functions. How would you choose between them?

This unbiased and objective report helps you to make this decision and gives you a deeper insight into the rapidly changing and exciting world of the micro-chip.


For your copy of the report complete and return the coupon to: Metac Electronic & Time Centres, 24-hour Despatch Centre, FREEPOST, 47A High St., Daventry, Northants.

Name	_____
Address	_____

E19

110 projects in every book!

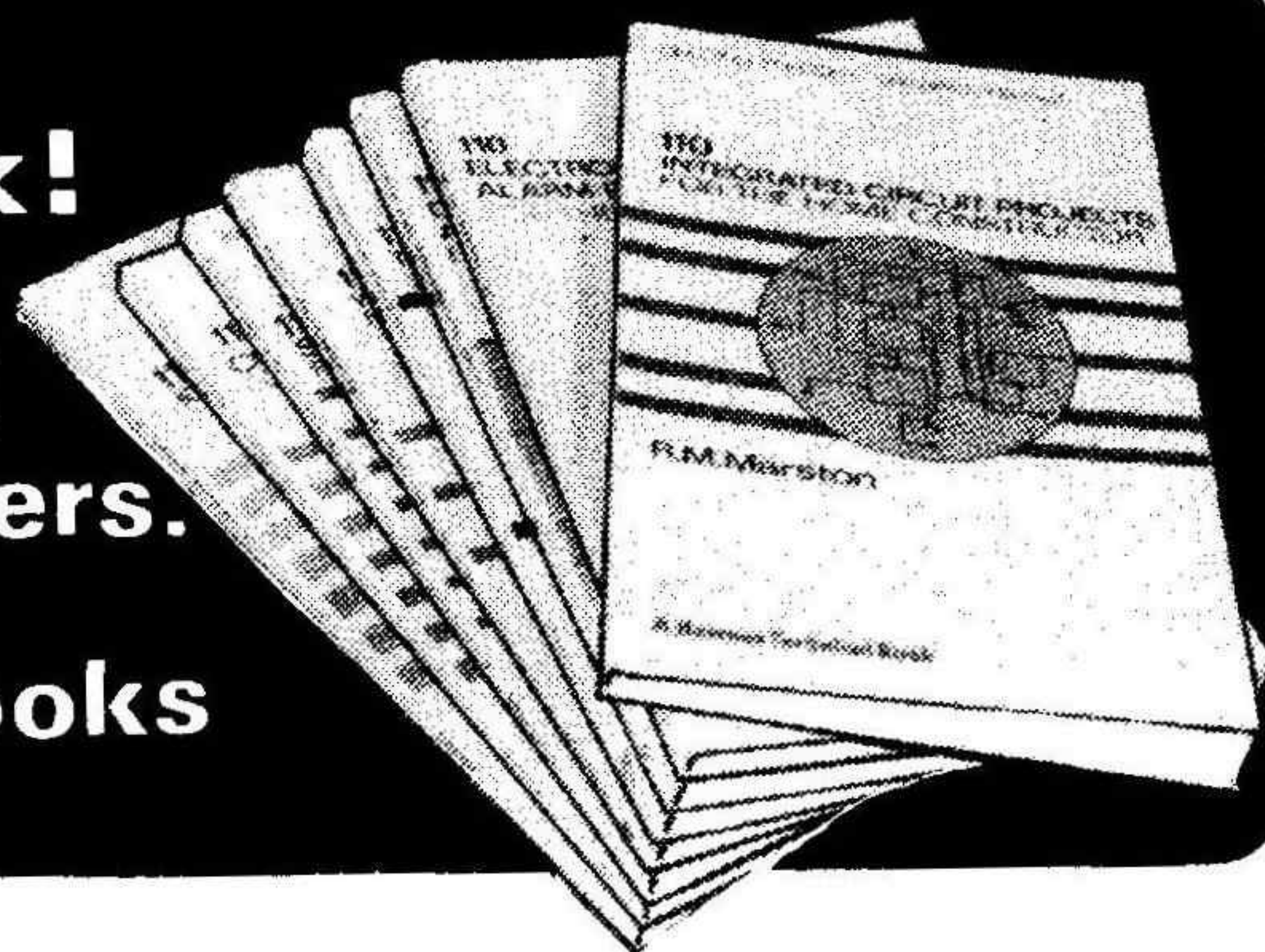The '110' books have been acclaimed by enthusiasts, students and engineers. Each contains 110 different circuit applications. Use them as project books or as source books for circuit ideas.



110 CMOS Digital IC Projects for the Home Constructor
R. M. MARSTON 0 408 00216 6 £3.95

110 Electronic Alarm Projects for the Home Constructor
R. M. MARSTON 0 408 00269 7 £3.95

110 IC Timer Projects for the Home Constructor
JULES H. GILDER 0 408 00480 0 £3.95

110 Integrated Circuit Projects for the Home Constructor –
Second Edition
R. M. MARSTON 0 408 00309 X £3.95

110 Operational Amplifier Projects for the Home Constructor
R. M. MARSTON 0 408 00153 4 £3.95

110 Semiconductor Projects for the Home Constructor –
Second Edition
R. M. MARSTON 0 408 00322 7 £3.95

110 Thyristor Projects using SCRs and Triacs
R. M. MARSTON 0 408 00074 5 £3.95

110 Waveform Generator Projects for the Home Constructor
R. M. MARSTON 0 408 00353 7 £3.95

Available from your bookshop or in case of difficulty direct from the publishers.


Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

ELECTRONIC GAMES


ATARI

SPECIAL
PRICE

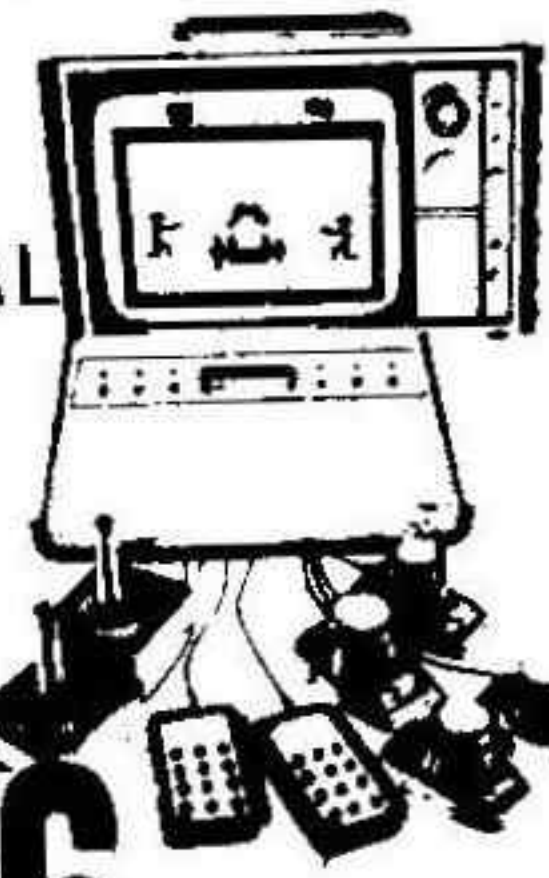


£86 + VAT

SPACE INVADERS

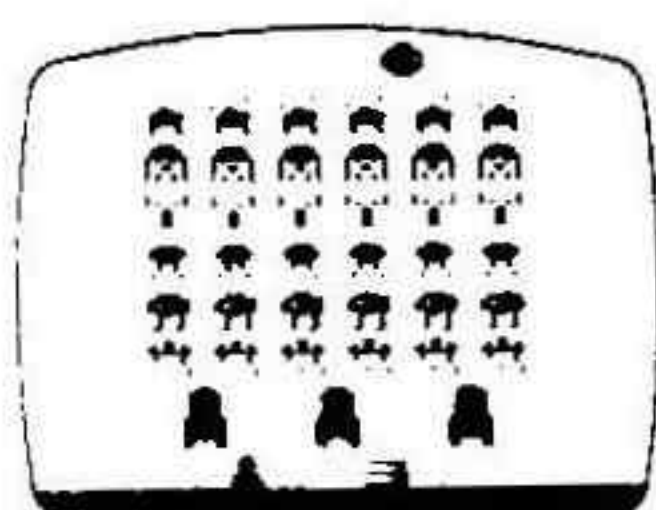

HAND HELDS + CARTRIDGES
ATARI - ACETRONIC
PRINZTRONIC
RADOFIN - DATABASE etc.
We keep a full range!
Send for cartridge lists stating which
machine you own.

INTELLIVISION MATTEL

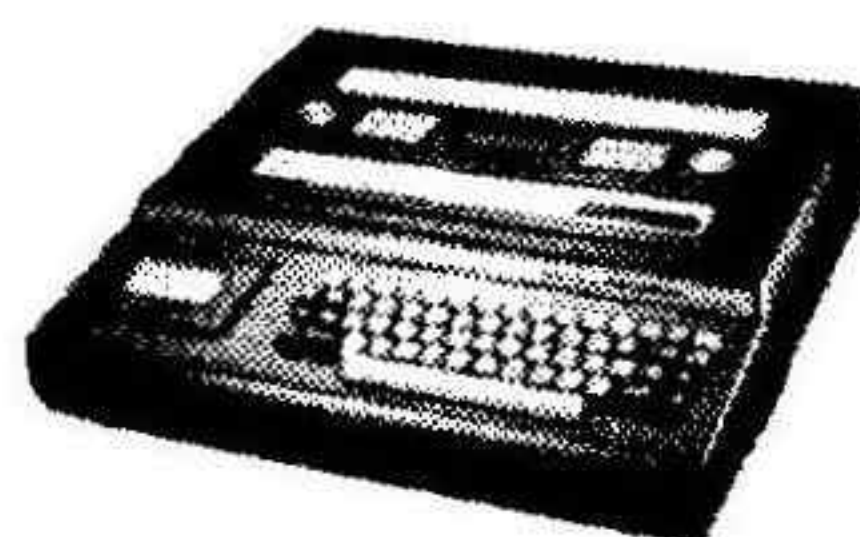

£173.87 + VAT

Available August 1980
This is the most advanced TV
game in the world.
Expandable
next year into a full
microcomputer.
COLOUR CATALOGUE
AVAILABLE WITH
DETAILS ON ALL THE
CARTRIDGES

BRIDGE


COMPUTER



- ★ Plays 1/2/3 or 4 Hands
- ★ Problem Mode
- ★ Audio Feedback
- ★ Instant Response
- ★ Auto scorekeeping

DRAUGHTS

COMPUTER

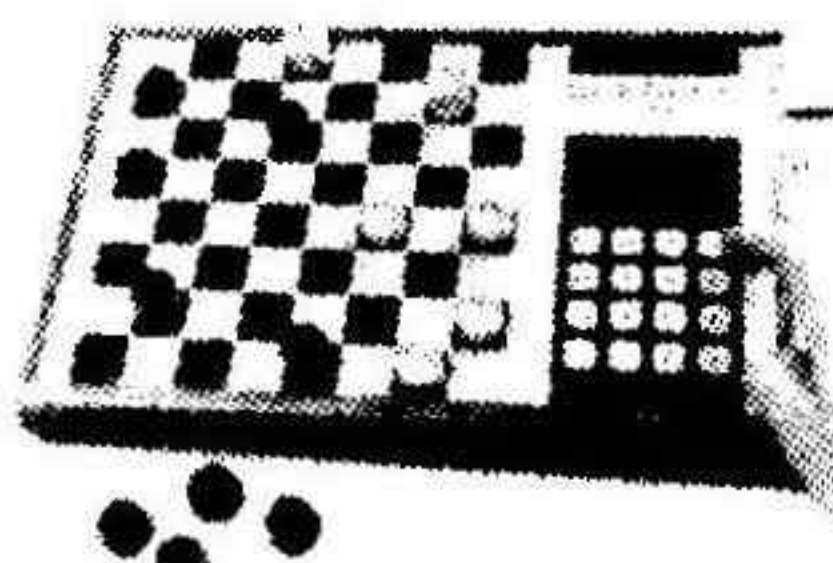

- ★ Solves Problems
- ★ Rejects illegal moves
- 2 level machine
£43 + VAT
- 4 level machine
£77.78 + VAT

CHESS




Send for further details.

COMPUTERS

NEW RANGE
AVAILABLE
AUGUST 1980
We specialise in
computer chess
machines & stock
over 13 different
models from
£20 to £300

BACKGAMMON

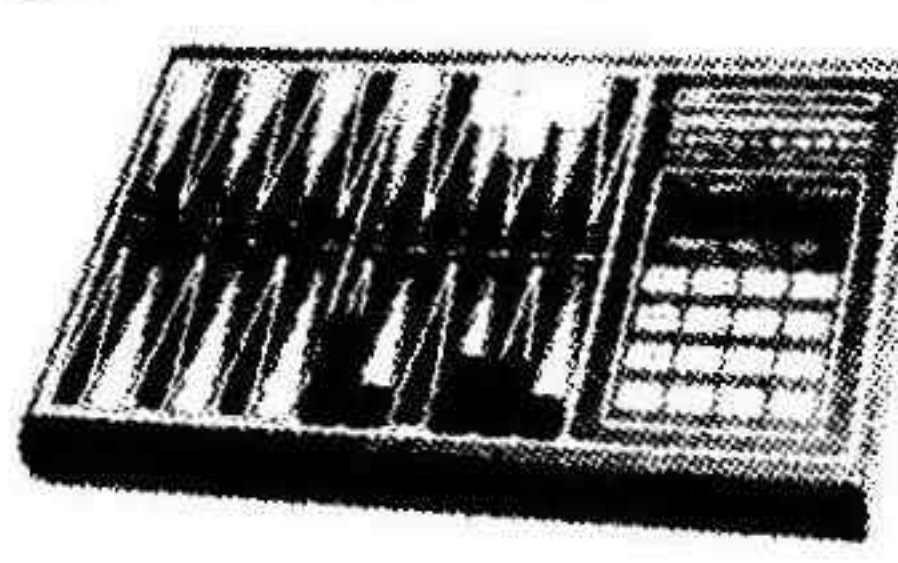

From £38 to £108. Send for further details.

COMPUTERS

OMAR 1
OMAR 2
CHALLENGER
GAMMONMASTER

LEISURE

- ★ CHEAP TV GAMES
- ★ TELEPHONE ANSWERING MACHINES
- ★ AUTO DIALERS
- ★ CALCULATORS
- ★ DIGITAL WATCHES
- ★ PRESTEL
- ★ HAND HELD GAMES

TELETEXT



RADOFIN
TELETEXT
Add on Adaptor

£199 + VAT

27 TUNE
DOOR
BELL
£17.13
+ VAT



FREE CATALOGUE


For a free copy
of our 32 page
catalogue, send
a 12p stamp to
Silica Shop Ltd
or Telephone
01-301 1111

MAIL ORDER SERVICE - Free postage & Packing
TELEPHONE & MAIL ORDERS - accepted on:
Access ★ Barclaycard ★ American Express ★ Diners Club
CALLERS WELCOME - at our shop in Welling - Demonstrations daily
Open from 9am-5pm Mon-Sat (9am-1pm Wed)
GUARANTEE - Full 12 months + After Sales Support!
We have comprehensive brochures on all products. Please let us know what you are interested in and we will send you detailed brochures AND our own
32 page catalogue covering most games on the market.

SILICA SHOP
SILICA SHOP LTD., Dept. ET19
102 Bellegrave Road
Welling, Kent DA16 3QF
Tel: 01-301 1111

3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC

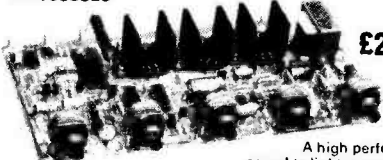

£29.90

A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

3 CHANNEL SOUND/LIGHT

LB31000SL




£21.40

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

2/4/8 CHANNEL CHASER

LB81000LC

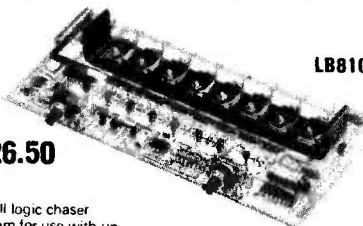


£26.50

An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

4 CHANNEL SEQUENCER

LB41000LS

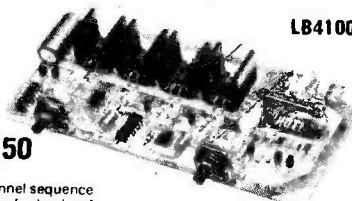


£17.50

A 4 channel sequence generator for banks of lamps up to 1,000V per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

1 AND 3 CHANNEL DIMMERS

LB31000LD

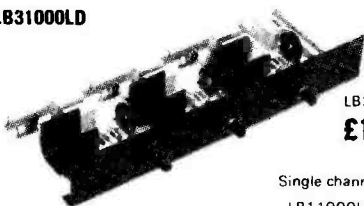

LB31000LD £14.70

Single channel version LB11000LD £6.70

Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders —

LB31000LD (no pots) £13.50 Sliders 75p each.

LB250




£39.50

ROPE LIGHTS/DRIVER

LB41000LC-S

£22.70

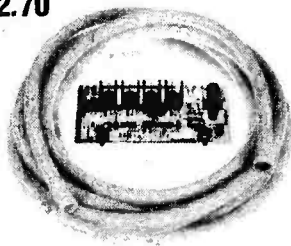

24 feet ropes
Red/Yellow
Blue/Green


ROPE LIGHTS
£51.75

A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control.

STEREO DISCO MIXER/PREAMP

LBPA3

M — Magnetic
C — Ceramic

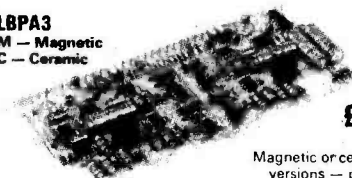

£30.70

Magnetic or ceramic deck versions — please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/ tone controls/ mic. mixer/ tones/ mic. auto fade over decks/ and P.F.L. The unit can be used with either LB10V/150/250 and respective supplies.

Full set of pots — £8.63 Sliders — £11.21

LBPA2
£17.20

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots £2.74, sliders £5.23.

LBPA1
£19.50

A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots £3.27, sliders £4.49.

3-WAY ACTIVE CROSSOVER

LBACO1
£17.90




LBPSU1
£6.20

Bass/mid/treble active crossover with stage booster! Available with crossover points of 20W or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1.

LBRLD1
£5.70

A de-thump unit for use with any LB power amps.

PIEZO
HORNS
£5.75
P/P 50p

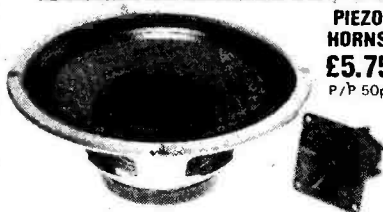


CELESTION LOUDSPEAKERS (8ohms)

G12-65 (12 inch 65W) £20.70 P/P £1.70	G12-100 (12 inch 100W) £26.45 P/P £1.70	G12-125 (12 inch 125W) £46.00 P/P £2.00
--	--	--

POWER SUPPLIES

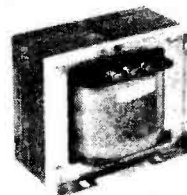A range of rugged power supply units to complement our amps.



LB250PS

LB25PS £11.20 P/P £1.20	LB100PS £14.70 P/P £1.40	LB150PS £18.00 P/P £1.40	LB250PS £24.50 P/P £1.70
-------------------------------	--------------------------------	--------------------------------	--------------------------------



L & B



PROFESSIONAL ENGINEERING BY
PROFESSIONALS

ELECTRONIC MODULES

45 Wortley Road, West Croydon, Surrey
CRO 3EB. Tel. 01-689 4138

- 1) You need a module
- 2) It must be reliable
- 3) It must be competitive
- 4) Its performance must be simply excellent
- 5) Its finish must be outstanding
- 6) You require a connection and circuit diagram
- 7) You require L & B

Each module is manufactured from the highest quality components, and fully tested and guaranteed for 12 months.

All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.O./registered cash/Barclaycard or Access number. C.O.D. service £1 extra. For the new Autumn catalogue send 50p.


POWER AMPLIFIERS

Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to 4 ohms).

25W R.M.S.	100W R.M.S.	150W R.M.S.	250W R.M.S.
20Hz to 60K 0.07% THD 960B S/N LB25	5Hz to 25K 0.1% THD 1100B S/N LB100	5Hz to 25K 0.1% THD 1100B S/N LB150	5Hz to 25K 0.1% THD 1100B S/N LB250
£11.20	£18.20	£26.50	£39.50


Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

PCB FOIL PATTERNS

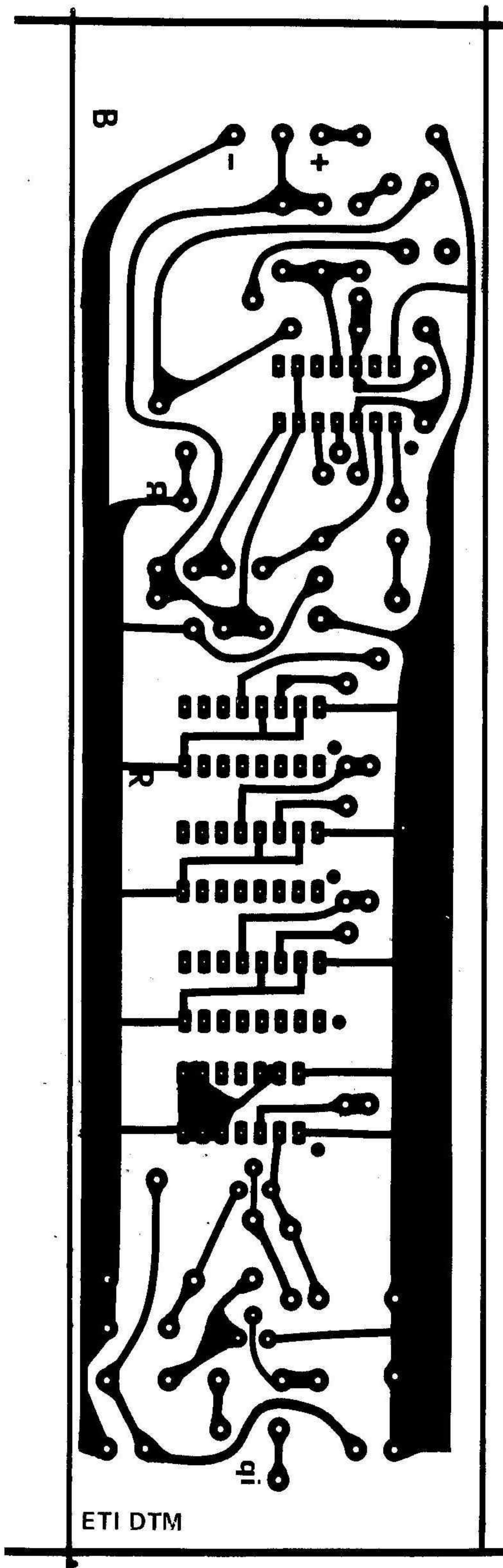


Left: Foil pattern for PCB board B, from the ETI Digital Test Meter project.

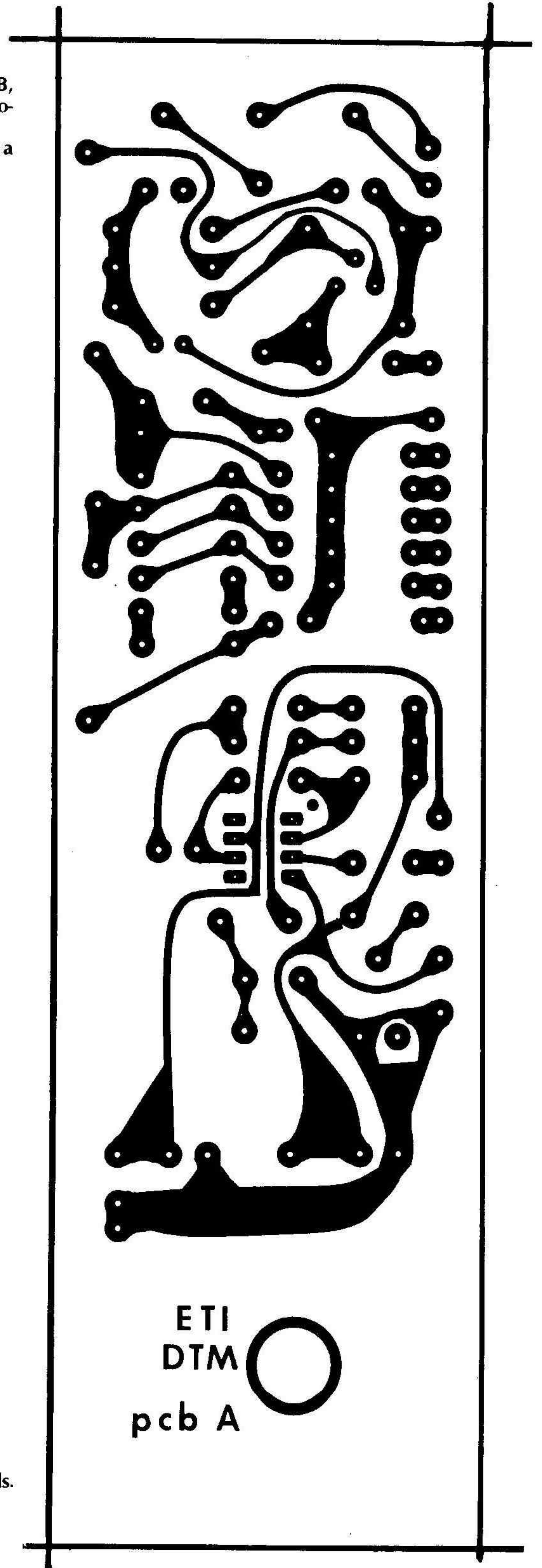Note that this project comprises a total of three boards.




Right: The second of the DTM boards.

ETI DTM
SWITCHING BOARD

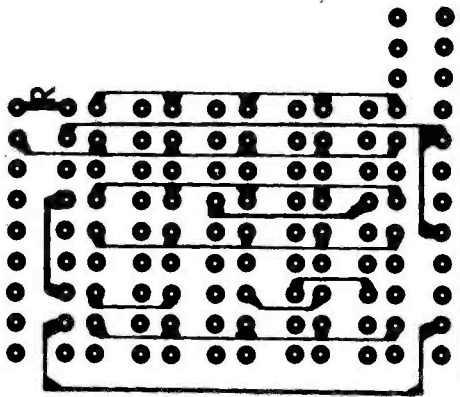


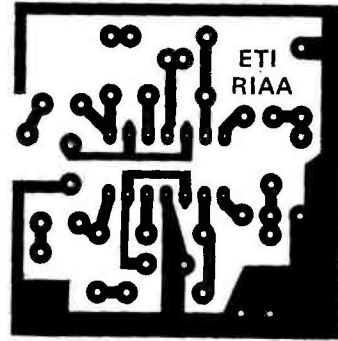Above: The switching board for the DTM project.




Above: The RIAA preamp foil pattern. The board is intended to be mounted inside existing equipment and space maybe left for fixing.

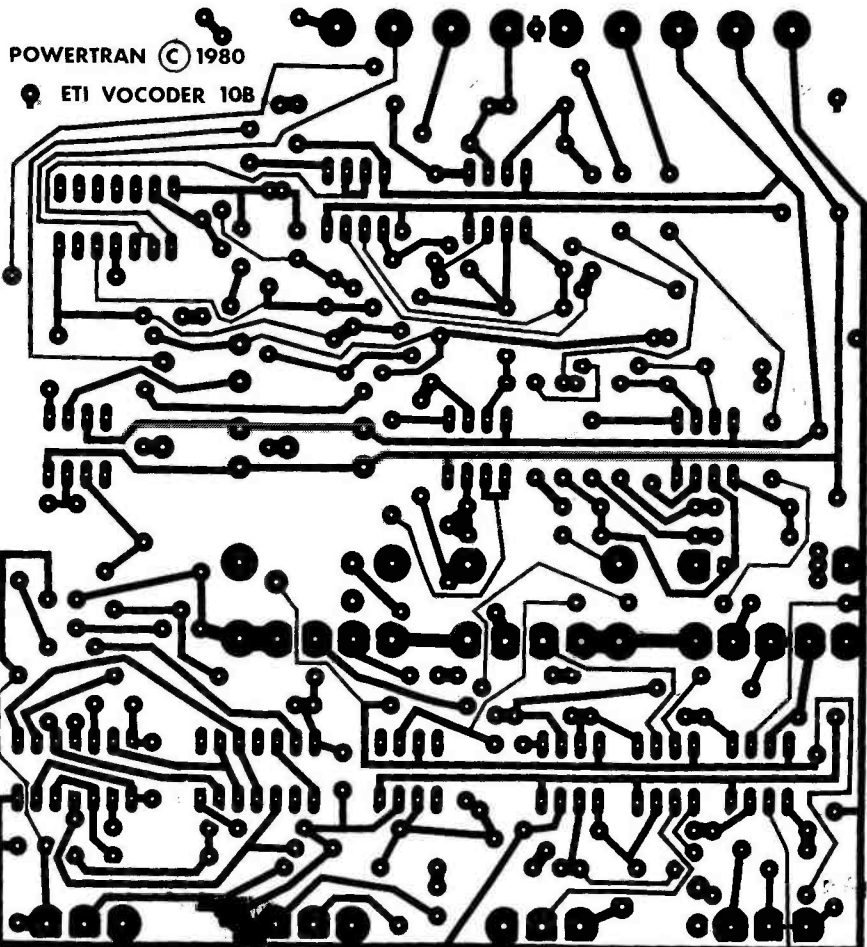
Below: Vocoder board B. The large PCB is not shown here as it is too large to go on the page. An SAE to Modmags will secure a copy.




ETI
SPEED
CONTROL

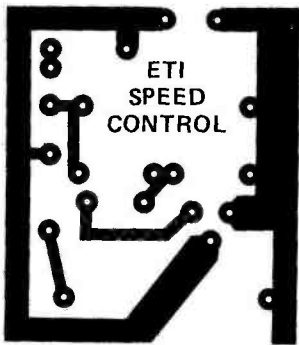

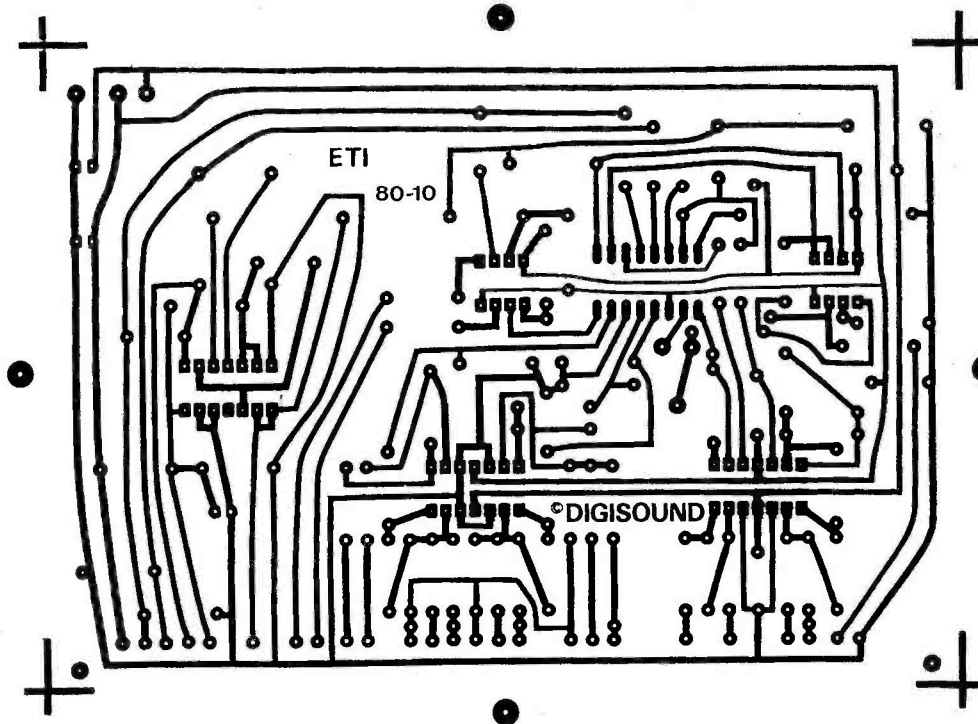
Above: The Drill Speed Controller PCB. Construction is not critical here and other methods may be employed. Take care with the PCB as mains voltage will be present.



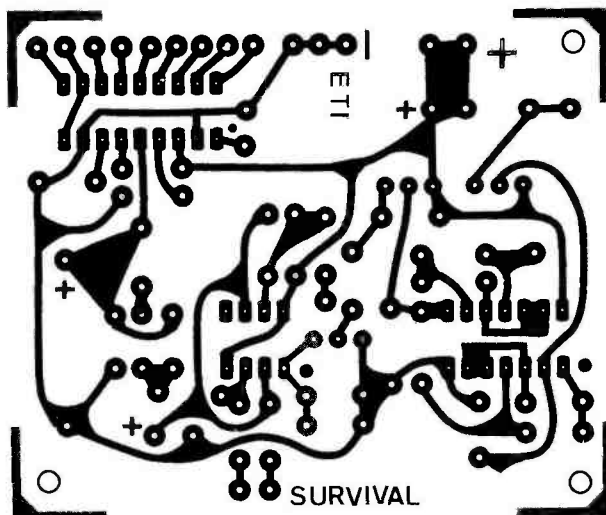Above: Project 80 board for this month's module. Note that copyright exists on the board and firms may not reproduce the PCBs for sale.



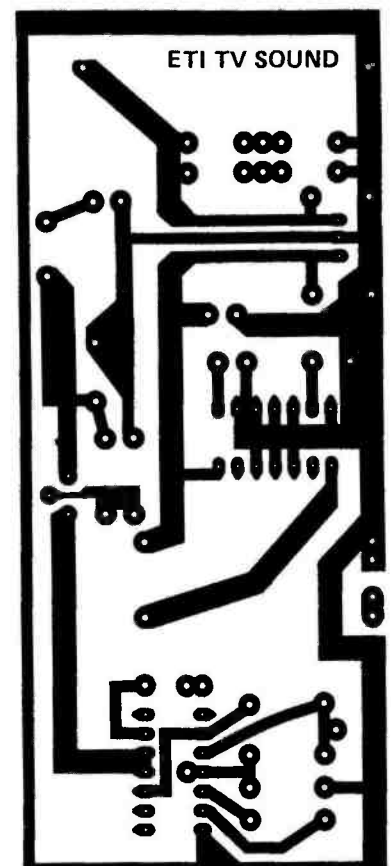Above: Foil pattern for the SURVIVAL game. This has been designed to fit the specified case.
Right: The monitor amplifier board for the TV Sound Tuner. This circuit is an optical extra to aid tuning and setting up.



ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).


PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

038	Buffer Moving Coil Preamp Process Controller	Jan 80	040B	ETI 80 -- PSU Tuning Fork Filter Coin Toss	Feb 80	042B	Touch Dimmer, Battery Charger RC Guardian (Top,Bottom)162	Apr 80
039A	Hum Filter Logic Probe	Dec 79	041A	ETI Audiophile ETI VCA Signal Trace ETI HC Electromyogram	Mar 80	043	IR60 preamp, Receiver, PSU, Servo Tester, VU-PPM	May 80
039B	Long Period Timer Rain Alarm Touch Switch Flash Trigger Pseudo Random Noise Gen	Dec 79	041B	VCM Heater Controller	Mar 80	044A	IR60 Function Board (Top & underside) Control Circuit, Line Transmitter, Tape Response Meter Ohmmeter	June 80
039C	Function Generator	Dec 79	042A	300W Amp Module	Apr 80	044B	FM receiver PSU & Monitor Amp Drum Synth (function board)	June 80
040A	ETI 80 -- VCO and VCLFO	Feb 80	033	Fuel Level Monitor, Alarm, Screen Controller Dynamic Noise Reducer	Sep 79			

HOW IT WORKS

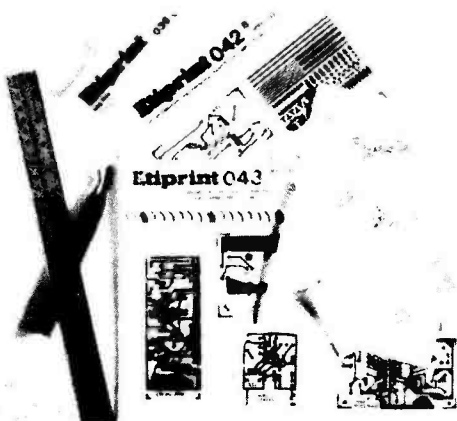

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ETIPRINTS



BUY LINES

ORDER TODAY

Send a cheque or PO (payable to ETI Magazine) to

ETI PRINT, ETI MAGAZINE 145 Charing Cross Road,
London WC2H 0EE.

Price £1.20p.

<p>MOTORS. 1.5V Model motors 22p. Sub. min. 'Big inch' 115V DC 3 rpm motor 32p. Replacement 8 track 12V DC motors 55p. Geared motor motors, 2 1/2 rpm, 75p. 115V AC 4 rpm motor 95p. Cassette motors, 5-8V DC ex. equip. 70p. 9V DC Cassette motors 95p. 6V Cassette motors, new standard jap. type £1.25.</p>	<p>RECORDING TAPE. Low noise mylar, supplied unboxed: 7" 1200' £1.00, 7" 1800' £1.75, 10" 3500' £5.00. JACKSONS C604 50 PF variable tuning condensers. Standard 1/4" spindle. 50p each.</p>	<p>SPECIAL OFFER DEC TYPE BREAD-BOARDS. Micro DEC "A" with 2 16 pin DIL carriers £3.95. Micro DEC "B" with 2 integral 16 pin DIL carriers £3.95. Both breadboards approximately half original selling price.</p>	<p>MOTOROLA PIEZO ELECTRIC TWEETERS</p>  <p>3" direct radiating type £3.85 3.5" flush mounting super horn £4.50</p> <p>PIEZO TWEETERS, require no crossover, and can be used with systems up to 100 watts. Frequency response 3.8 to 28KHz.</p>	<p>TRANSFORMERS. All 240V DC primary (postage per transformer is shown in brackets after price). MINIATURE RANGE 6-0-6V 100ma, 9-0-9V 75ma, 12-0-12V 50ma all 75p each (15p). 12V 200ma 75p (15p). 0-5 280ma £1.20 (20p). 6V 500ma £1.10 (22p). 12V 2A £2.35 (45p). 12V 4A £2.85 (45p). 15-0-15V 1A £2.25 (45p). 30-0-30V 1A £2.85 (54p). 20-0-20V 2A £3.65 (54p). 0-12-15-20-30V 2A £4.75 (54p). 20V 2.5A £2.35 (54p).</p>	<p>KRT101 M/METER. 1,000 opv. 1KV AC/DC Volts. 150ma DC current. Resistance 0-2.5k. 0-100K. £4.35.</p>
<p>BUZZERS. Miniature solid state type. 33x17x15mm. 70db at 3 feet 15ma drain, operates 4-15V DC 75p each. LOUD 12 volt buzzer 50x30mm 63p. Carriers 12V DC Miniature alarm sirens £7.65. 12V DC SIREN, all metal rotary type, high pitched wail, £8.50. Rotary alarm siren, 12V DC, red plastic unit with mounting bracket, 68x75mm, £4.50.</p>	<p>TOOLS. SOLDER Sucker, good suction, teflon nozzle. £4.99. Side cutters 5" £1.45. Pliers 5" £1.45. NEON DRIVER 8" LONG 50p. MIYAMA 16 pin IC test clip £1.85. 5 PIECE precision screwdriver sets, individual handles. £1.05. JUMPER TEST LEAD SETS 10 pairs of leads with insulated crabs each end 90p. CRIMPING TOOL, a combination type for crimping red, blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, insulated, handles, only £2.30.</p>	<p>COPPER LAMINATED PRINTED CIRCUIT BOARD. Fibreglass Single Sided type (approx. 2mm thick) 150x95mm 40p. 200x90mm 55p. 250x145mm 65p. Double-sided Fibreglass 1mm thick. 180x135mm 45p. PAXOLIN BASED TYPE (2mm thick). 180x135mm 40p. 280x200mm 50p.</p>	<p>RANK ARENA stereo cartridge preamplifier modules, suitable for magnetic cartridges, now, supplied with connection details. £1.95.</p>	<p>PROJECT BOXES. Sturdy ABS black plastic boxes with brass inserts and lid. 75x56x35mm 65p. 95x7x35mm 75p. 115x9x37mm 87p.</p>	<p>MMS M/METER. 2,000 opv. 1KV AC/DC Volts. 100ma DC. Resistance 0-10K. 0-1 MEG. £5.50.</p>
<p>RELAYS. 2 types both operate on 12V DC, sealed plastic cased types. 1-350 ohm with 2 make 5 amp contacts 75p. 2-1,000 ohm with 2 changeover 1 amp contacts 75p.</p>	<p>MICROPHONES. Min. Tie pin. Oni, uses dead aid battery (supplied) £4.95. Low cost condenser ECM105 Omni, 600ohms, on/off switch standard jack plug £2.95. EM507 Condenser, uni, 600ohms, 30-18kHz, highly polished metal body. £7.95. DYNAMIC stick microphone dual imp., 600ohms or 20K. 70-15kHz, attractive black metal body. £7.75. EM506 Condenser, cardioid, uni, 600ohms or 50K, heavy chromed copper case. £12.95. DYNAMIC P.A. Mike, mobile radio etc., thumb switch 50k imp. £3.75. CASSETTE replacement microphone with 2.5/3.5 plugs. £1.35. INSERT crystal replacement 35x10mm 40p. GRUNDIG Electret inserts, with built in FET preamp 3-6V DC. £1.00.</p>	<p>TAPE HEADS. Mono cassette. £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. BSH MM 1330 1/2 track 50p. BSR SRP90 1/4 track £2.10. TD10 dual head assembly 2 heads both 1/2 track R/P with built in erase £1.25.</p>	<p>FINNED HEATSINKS. Supplied undrilled: 4mm thick. 27mm high. 75x124mm 60p. 150x124mm 95p. Smaller version 2.7mm thick. 75x108mm 48p. TRANSISTOR SOCKETS T05 or T018 9p each. T03 type 15p each.</p>	<p>VERO HAND HELD BOX. White ABS. 24in x 3.7 in tapered, with screws 68p each.</p>	<p>YN360 M/METER. 20,000 opv. 1KV AC/DC Volts. 250ma DC. 4 resistance ranges in 20 Meg. also has built-in transistor tester with leakage and gain ranges £12.50.</p>
<p>SPECIAL OFFER SEMICONDUCTORS. 2N5082 SCRs 18p. BX504 opto isolator 25p. CA3130 95p. TBa800 50p. TDA1151 25p. 741 22p. 723 35p. NE555 24p. AD161 2/70p pair. 2N3055 38p. IN4005 10 for 35p. BD238 28p. BD438 28p. 741S 35p. 2N414 75p. TL305 alpha numeric display £2.50. MAX3A 3mm LED displays 45p. Min. LDRs 30p. LEDs 0.2" CLEAR 15p. GREEN 12p. RED 10p. Infra-red clear LED 30p. MPU131 PUTs. 40V, 200ma. 375mW 15p. 2N3773 £1.70. Texas R1038 (103) Power trans. 50p. TAG4443 SCR 45p.</p>	<p>LED VU METERS. Utilise sophisticated logic control circuit with adjustable rise and decay times via external capacitor. Spec: Response -20Hz in 100kHz. Tolerance within ±10%. operates on 12-15V DC. 62mm long, 54mm high. MONO VERSION £8.95 STEREO VERSION £18.95</p> 	<p>SWITCHES. Sub. min. Toggles. SPST 8x5x7mm. 42p. DPDT (8x7x7) 55p. DPDT Centre off (12x11x9mm) 77p.</p> <p>PUSH SWITCHES (16x6mm), red top, push in make 15p each, push on break version black vinyl 17p each.</p> <p>SLIDE SWITCHES all DPDT 15x8x12mm 13p. 16x11x9mm 13p. 22x13x8mm 13p. 22x13x8 centre off 14p. Multipole slider double action (12 tags) 29x9x11mm 25p.</p> <p>ROTARY SWITCHES (water) 3P4W. 4P3W. 2P5W and 1P12W all 35p each.</p>	<p>ALUMINIUM PROJECT BOXES. 18 S.W.G. with fitted lid and screws. AB1 3x2x1 52p. AB2 4x3x1.5in 62p. AB3 4x3x2in 66p. AB4 6x4x2in 74p. AB5 6x4x3in 92p. AB6 8x6x2in £1.05. AB7 8x6x3in £1.25.</p>	<p>CLIFF CLICKTEST. 13 amp mains connector. Ideal for workshop, etc., provides rapid and safe mains connection. Tough moulded case and lid with neon indicator and fuse. £5.15.</p>	<p>TMK500 M/METER. 30,000 opv. 1KV AC/DC Volts. D.C. current to 12 amps. Resistance to 60 meg in 4 ranges. also has built-in buzzer for continuity testing. £20.95.</p>
<p>NEW STOCK ITEM - We are now stocking Expo mini hand-held drills, these are a precision British-made tool, ideal for P.C. board drilling, model makers etc. They operate on 12V DC. Drill kit supplied in plastic hinged case, with drill and 21 accessories, drills, sanders, reamers, buffers, etc. complete kit only £14.25. Drill only £7.25. Drill stand to suit vertical drill press £12.95 (postage 65p).</p>					

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for illustrated lists.

PROGRESSIVE RADIO
31 CHEAPSIDE, LIVERPOOL L2 2JD
ALL ORDERS DESPATCHED BY RETURN POST

WEST HYDE CASES FOR E.T.I. PROJECTS

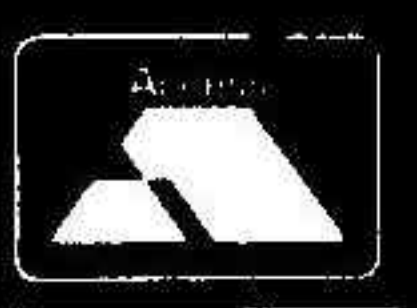

Bench Amplifier (August 1979) Order Code WEC 801
 Audiophile Pre-Amp (October 1979) Order Code CL2 CDL
 Audiophile Power Amp (October 1979) Order Code CL2 CGL
 Audiophile PSU (October 1979) Order Code CL2 AEL
 Pinball Wizard (November 1979) Order Code TEK 364
 Points Controller (December 1979) Order Code BOC 680
 Moving Coil Pre-Amp (January 1980) Order CL2 ADJ
 Synthesiser Project Order Code TEK A23G
 Stereo Image Co-ordinator (July, 1980). Order Code CL2 CDJ.

**PLEASE ASK FOR OUR FREE
80-PAGE CATALOGUE AND PRICE LIST**

THE BIGGEST SELECTION OF CASES IN EUROPE

WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED, UNIT 9, PARK STREET INDUSTRIAL ESTATE, AYLESBURY, BUCKS. TEL 0296 20441

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail.

After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

Book 1 Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.

Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.

Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.

Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.

DESIGN OF DIGITAL SYSTEMS £12.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.



Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.


THE ALGORITHM WRITER'S GUIDE £4.00

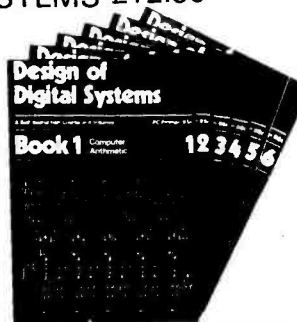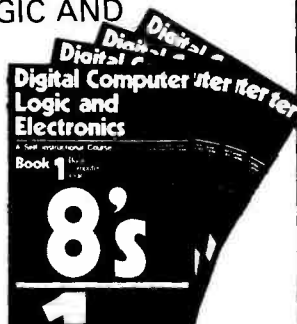explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.



Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.

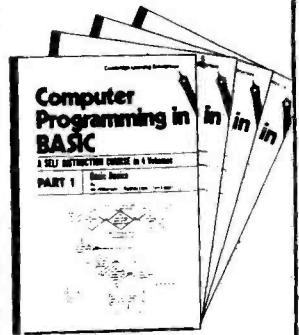

COMPUTER PROGRAMMING IN BASIC £9.00

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL £4.40

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

GUARANTEE - No risk to you

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

....Digital Computer Logic & Electronics @ £7.00

....Design of Digital Systems @ £12.50

....Algorithm Writer's Guide @ £4.00

....Computer Programming in BASIC @ £9.00

....BASIC Handbook @ £11.50

....A.N.S. Cobol @ £4.40

FOUR WAYS TO PAY:

1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)

2) A bank draft, in sterling on a London bank (available at any major bank)

3) Please charge my Access/M.Ch. ☐ Barclay/TrustC/Visa ☐ Am. Exp. ☐ Diners ☐

4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service

Card No. Signed
THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL:
Eur. N.A.F. Mid.E. add 1/3 to price of books; Jpn. Aus. N.Z. Pcf. add 1/2; elsewhere add 1/2

Name

Address

U.K. Delivery: up to 28 days

Cambridge Learning, Unit 14 Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR England.

Reg. in Eng. No. 1328762

Marshall's

**A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582**
Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.
108A Stokes Croft, Bristol.

CAPACITORS:

Mullard Ceramic 63v range
1pF to 10,000pF E 24 range
all at £0.06 each
Siemens Ceramic 63v B37448/9
.01: .022: .033: .047mF @ £0.06
.068: .1mF @ £0.08: .22mF @
£0.11
CSF High Voltage Ceramic Discs
Prices £0.07 to £0.18 Range
100pF to 10,000pF
Voltage range up to 6Kv.
See catalogue for details.
Comprehensive range Siemens
Layer Polyester Caps: .001 to
3.3mF
Prices £0.07 to £0.63.
See catalogue for details.
Large range of Mullard/Siemens
Electrolytic Axial/Radial
Capacitance values 1.0mF to
10,000mF
Voltage ranges 25v: 40v: 63v:
100v:
Prices and types as catalogue
Also Mullard C280; Siemens
B32231/4 and B32110. All prices
net + VAT and postage/packaging.

TOOLS BAHCO

Side Cutter with Bezel.
Side Cutter without Bezel.
End Cutter without Bezel.
Vero Metal Shears.
Other items as catalogue.

BOXES & CASES

See catalogue for full range.
Aluminium boxes 13 sizes.
Rexine Covered boxes 7 sizes.
NEW RANGE TMEC CASES
Send S.A.E. for details & types
Price range, £14.04 to £17.00
ABS PLASTIC BOXES
3" x 2 1/4" x 1 3/8"
3 3/4" x 2 3/4" x 1 3/8" Prices as
4 1/2" x 3 3/4" x 1 1/2" catalogue
8" x 4 3/4" x 3"
BAZELLI INSTRUMENT CASES
5 sizes.
Miscellaneous hardware
including
Vero Board: Superstrips:
Vero Breadboard.
Vero boxes (see catalogue for
full range).
Card Frames: Flip-top boxes:
etc etc.

1980 CATALOGUE

U.K.: 65p post paid
Europe 85p post paid
Rest of World £1.25
post paid
Mail order: 01-624 8582

TTL see catalogue for full range

SN7400N	£0.14	SN7491AN	£0.54
SN7401N	£0.14	SN7492N	£0.31
SN7402N	£0.14	SN7493N	£0.32
SN7403N	£0.14	SN7494N	£0.80
SN7404N	£0.14	SN7495N	£0.55
SN7405N	£0.15	SN7496N	£0.34
SN7406N	£0.34	SN7497N	£1.80
SN7407N	£0.26	SN74100N	£1.10
SN7408N	£0.15	SN74107N	£0.21
SN7409N	£0.16	SN74118N	£0.76
SN7410	£0.15	SN74119N	£1.20
SN7411N	£0.15	SN74121N	£0.25
SN7412N	£0.20	SN74122N	£0.48
SN7413N	£0.28	SN74123N	£0.42
SN7414N	£0.47	SN74124N	£0.53
SN7416N	£0.22	SN74125N	£0.40
SN7417N	£0.22	SN74141N	£0.50
SN7420N	£0.15	SN74145N	£0.64
SN7423N	£0.16	SN74148N	£1.05
SN7425N	£0.19	SN74150N	£0.79
SN7426N	£0.19	SN74151N	£0.55
SN7427N	£0.19	SN74153N	£0.55
SN7430N	£0.15	SN74154N	£0.90
SN7432N	£0.17	SN74155N	£0.60
SN7437N	£0.21	SN74157N	£0.59
SN7438N	£0.21	SN74160AN	£0.70
SN7440N	£0.15	SN74161AN	£0.70
SN7441AN	£0.52	SN74162AN	£0.70
SN7442N	£0.40	SN74163AN	£0.70
SN7445N	£0.66	SN74164N	£0.80
SN7446AN	£0.48	SN74165N	£0.80
SN7447AN	£0.48	SN74167N	£1.20
SN7448N	£0.45	SN74174N	£0.80
SN7450N	£0.15	SN74175N	£0.63
SN7451N	£0.15	SN74176N	£0.74
SN7453N	£0.15	SN74177N	£0.73
SN7454N	£0.15	SN74180N	£0.70
SN7460N	£0.15	SN74181N	£1.65
SN7470N	£0.26	SN74182N	£0.83
SN7472N	£0.24	SN74184N	£1.29
SN7473N	£0.25	SN74185AN	£1.10
SN7474N	£0.25	SN74186N	£1.35
SN7475N	£0.31	SN74188AN	£1.84
SN7476N	£0.26	SN74189N	£2.26
SN7480N	£0.39	SN74190N	£0.74
SN7481N	£0.71	SN74191N	£0.79
SN7482N	£0.65	SN74192N	£0.79
SN7483N	£0.60	SN74193N	£0.79
SN7484N	£0.95	SN74196N	£0.74
SN7485N	£0.70	SN74197N	£0.74
SN7486N	£0.25	SN74198N	£1.09
SN7489N	£1.66	SN74199N	£1.09
SN7490AN	£0.33		

KNOBS & SWITCHES

Big selection as catalogue
Also Resistors; Presets; Pots;
Opto; Semiconductors etc.

SOLDERING EQUIPMENT

IRONS-ANTEX
15 watt C15 £3.95
15 watt CCN £4.20
17 watt CX17 £4.20
25 watt X25 £4.20
Stand £1.50

DESOLDERING TOOL
Solder £6.50

SINCLAIR INSTRUMENTS

Digital Multimeter
PDM35 £ 34.50
DM235 £ 52.50
DM350 £ 72.50
DM450 £ 99.00
Digital Frequency Meter
PFM200 £ 49.80
Low Power Oscilloscope
SC110 £139.00

CRIMSON ELEKTRIK HI FI MODULES

CE608 Power Amp £18.26
CE1004 " " £21.30
CE1008 " " £23.91
CE1704 " " £30.43
CE1708 " " £30.43
CPS1 Power Unit £16.96
CPS3 " " £20.43
CPS6 " " £26.09
CPR1 Pre Amp £29.57
CPR1S Pre Amp £38.70
All prices + VAT + postage/
packaging

RUN YOUR HOME BY REMOTE CONTROL

How many times have you considered building a remote control project for the home but were put off by the dozens of ICs, special coils, lenses and other hard to get components, not to mention the need for a well equipped lab. To set the unit up T.K. ELECTRONICS have changed all that. Three ICs can build a sophisticated system that requires only a capacitor and resistor to set the clock frequency (which can drift by up to 20% without affecting performance). Control radios, hi-fi (including bass, treble and volume), lighting, toys, garage doors, etc. Still not convinced? then look at the prices!

LD271	IR Emitting Diode	36p
SFH205	Photodiode Detector	95p
SL480	IC Pulse Amplifier	£1.40
LA490	Keyboard Controller Encoder / Transmitter	£2.40
ML922	10-channel Receiver & 3 Analogue Outputs	£4.20
ML926	16-channel Receiver (4 Momentary binary outputs)	£1.40
ML928	16-channel Receiver (4 latched binary outputs)	£1.40
	Data sheets (per device)	5p


These ICs can also be used with ultrasonic and radio links, depending on range, cost and speed of operation. For more details, why not give us a ring — or send s.a.e. We will be pleased to advise you.

NEW KIT + + + NEW KIT + + + NEW

If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel ON/OFF infra red transmitter and receiver. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a preamplifier, bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be built into all kinds of equipment from lamps to tape recorders. The minimum range is 20 feet. A suitable box for the receiver is available if required.

ONLY **£12.00**

MINI TRANSFORMERS

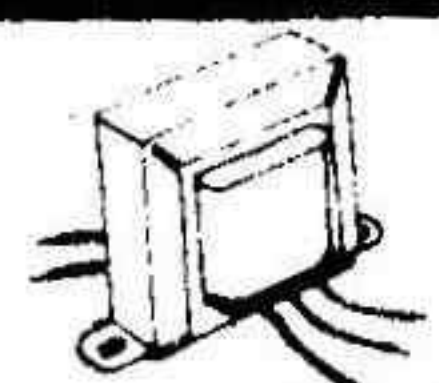

Standard mains
primaries 240V a.c.
100mA secondaries
6.0 6V
9.0 9V
12.0 12V

80p
85p
90p

D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	36p

TKs SPECIAL OFFERS OF THE MONTH

Orders must be received by 30/9/80

5X TIC 106D 5A/400 V SCR	£1.75
5X TIC 206D 3A/400 V TRIAC	£2.00
5X TIC 226D 8A/400 V TRIAC	£2.50
10X RECTANGULAR Green LED	£1.75
10x Rectangular Yellow LED	£1.75
5X 78 L1S 12V 100mA A regulator	£1.10
5X 7805 5V 1A regulator	£2.25

CT4000 CLOCK/APPLIANCE TIMER KIT

The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay Kit (MK2). The kit includes a PCB, keyswitches, I.C. 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.

£25.25



Size: 10 x 12 x 4.5 cms.
Colour: Black.

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

DL1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.60**
DL21000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**
Optional Opto Input DLA1 **60p**

INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp.	19p
AY-5 1230/2 Clock/Timer	£2.60
AY-3 1270 Thermometer	£4.50
ICL7106 DVM (LCD drive)	£8.20
LM377 Dual 2W Amp.	£7.00
LM379S Dual 6W Amp.	£1.45
LM380 2W Audio Amp.	£3.50
LM382 Dual low noise Preamp.	80p
LM386 250mW low voltage Amp.	£1.00
LM1830 Fluid Level Detector	75p
LM2907 f-v Converter (8 pin)	£1.50
LM2917 f-v Converter (14 pin)	£1.40
LM3909 LED Flasher/Oscillator	£1.60
LM3911 Thermometer	55p
LM3914 Dot/Bar Driver	£1.20
MM74C911 4 digit display controller	£2.10
MM74C915 7 segment BCD converter	£2.50
MM74C926 4 digit counter with 7 seg. o/p	£6.50
S566B Touchdimmer	96p
S9263 Touchswitch 16-way	£4.50
SN76477 Complex Sound Generator	£2.50
TBA800 5W Audio Amp.	£4.85
TBA810AS 7W Audio Amp.	£2.52
TDA1024 Zero Voltage Switch	58p
TDA2020 20W Audio Amp.	85p
ZN1034E Timer	£1.20
All ICs supplied with data sheets.	£2.85
Data Sheets only 5p each device	£1.80

MINI KITS

These Kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/THERMOSTAT
Uses LM3911 IC to sense temperature (80°C max), and triac to switch heater. **500W £3.20** **1KW £3.50**

MK2 SOLID STATE RELAY
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**


MK3 BAR/DOT DISPLAY
Displays an analogue voltage on a linear 10-element LED display as a bar or single-dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER
Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. **1.5KW £5.25** **3KW £5.55**

MK5 MAINS TIMER
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW **£4.50**

D.V.M. THERMOMETER KIT

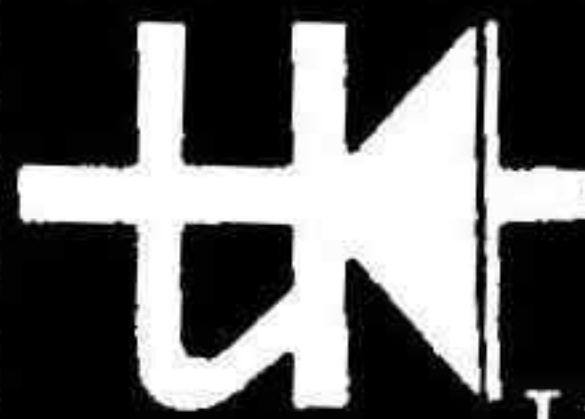Based on the ICL7106. This kit contains a PCB, resistors, presents, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA9V supply (PP3 battery). **£20.75**



All components brand new and to specification. Add V.A.T. AT CURRENT RATE TO ABOVE PRICES PLUS 35p P & P Mail Order Callers welcome by appointment

VISA



T.K. ELECTRONICS (PE) 106 Studley Grange Road, London W7 2LX Tel 01 579 5794

Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, HANTS. PO3 5B

GIANT 0.8" LED clock display, common cathode, non-multiplexed. With data £3.95 each. **ALARM** clock module with 0.7" LED display. With data £5.99 each. **LIQUID** crystal clock display, 0.7" digits. With data and FREE socket, £5.25 each. **FLUORESCENT** reject calculators. Modern, 10 function with full memory. Most-repairable but no g'sees £2.99 each. **TEN** transistor I.F. transformers. All brand new. May include several types. 55p for 10. **CLOCK CHIP** MM53181 I.C. (has alarm output). Brand new, with data £2.35 each. **POLARIZING** filter, plastic, 0.006" thick. Any size cut from 1 sq. in. to max. size 19" X 250 feet. 3p per sq. inch. **MOMENTARY** (push to 'make') switch. Red cap. 15p each. **SLIDE** switch, 2 pole c.p. 15p each. **TWO** calculator keyboards (not compatible with 4204 calc. chip). 99p the pair. **MULTIMETER CHIP**, MM5330 I.C. to build 4 1/2 digit d.m.m. (needs additional circuitry). With data £3.55 each. **KNOBS**, slider control knobs, fits 5 or 8mm shafts. State colour, 14p each. Rotary control knobs, black (18mm diam) with coloured cap, state colour required. 20p each. Skirted rotary knob, same as rotary control knob above but has 'flared' skirt around base. State cap colour required. 27p each. Colours available, black, red, green, blue, yellow, grey, white. **8 DIGIT** common cathode calculator display, 0.1", multiplexed, with data, 99p each. **LED WRIST-WATCH CHIP** with data, 95p each. **LED WRIST-WATCH DISPLAY** matches above watch chip. With data, 95p each. **NOTE**, the wristwatch chip and display are housed in 'legless flatpack' style package and require some fairly fine soldering. **QUALITY** jack sockets, mono 25p each, stereo 30p each. **LM555** timer I.C. with applications booklet. 25p each. **MEMORIES** 2102 static RAM with data, 99p each. **NORTEC** 4204, 4 function calc. chip. With data, 80p each. **UNTESTED** 0.1" LED displays. 10 single digit displays for 95p. 'U' to test.

Post and packing please add 40p (overseas orders add £1).

For your FREE copy of our latest catalogue please send MEDIUM sized SAE. VAT ADD 15% TO TOTAL COST (INCLUDING POST AND PACKING).

'Cash back' satisfaction guarantee on all items.

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in £3.00 with all symbols for direct application to P.C. board. Individual sheets 30p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8—10—12 T.O.S. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price £1.20.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/2in kit or 1/4in kit. £1.20 complete. State size.

All orders dispatched promptly.

All post paid

Shop and Trade enquiries welcome
Special Transfers made to order

E. R. NICHOLLS
P.C.B. TRANSFERS


DEPT. ET19

46 LOWFIELD ROAD
STOCKPORT, CHES. 061-480 2179

The finest amplification from Crimson Elektrik

LATEST DEVELOPMENTS

CRIMSON ELEKTRIK Power amplifiers are the most sophisticated on the market today. Yet now with the latest issue 5 innovations THEY ARE EVEN BETTER! We have included sonic improvements and developed a unique electronic protection circuit which obviates the need for output fuses. In fact, such fuses can seriously degrade the performance of an amplifier. They can blow under heavy drive conditions — even with non faulty loads (due to thermal fatigue), they can be a time consuming nuisance and even dangerous to replace, but more importantly they are responsible for 'envelope distortion' i.e. dynamic compression of the signal, even fuses in the feedback loop suffer from the first two disadvantages, and the latter to a lesser extent.

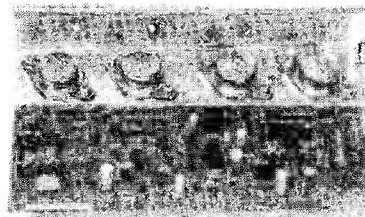

CP3000 POWER AMP MODULE 300 WRMS 4R

BEST VALUE

CRIMSON have an enviable reputation for supplying the best value amplifier kits. You can prove this to yourself by checking out the competition in the following crucial areas: ★ Professional grade phono sockets for ALL signal connections ★ Silver/Gold plated switch contacts ★ Adequate heatsinking for full rated output ★ Available from stock ★ Manufactured by a specialist company with a reputation for friendly and helpful service before and AFTER sale ★ Forms the basis for high quality active loudspeaker systems. Considering the advantages of CRIMSON Kits. Why choose anything else?

SOUND ADVICE

Crimson Amplifiers are versatile and dependable. The new CP3000 will give up to 300 watts into 4 ohms at 0.03% THD and is the obvious choice for P.A. and Disco's requiring the best performance. For Hi-Fi we produce the ever popular pre- and power amp hardware kits which enable our advanced modules to be housed in attractive metalwork and include everything down to the last nut and bolt.

Our Pre-amplifier can be fitted with the moving coil module allowing it to be used with the latest M.C. cartridge (which can now be bought for as little as £30). Write for details, specifications and full price list or send 50p cheque/p.o. for our comprehensive application / users manual.

Space precludes us from publishing all our products and prices, below are just a few examples.

★ Power Amp Modules (single channel)
CE 608 (60 WRMS/8 ohms) £23.10
CE 1708—(170 WRMS/8 ohms) £38.50
CP 3000—(300 WRMS/4 ohms) £58.00
★ 60 + 60 watt stereo pre and power amplifier complete kit £208.86
★ Stereo Moving Coil Pre-Pre Amplifier Module MC1 £28.50
★ 3 Way Active Crossover (single channel) £32.60

Don't forget, Crimson modules are available throughout the country from all branches of Marshalls and Mail order from Badger Sound Services and, of course Crimson Elektrik.

Prices include V.A.T. and post to anywhere in the U.K.



1A Stamford Street, Leicester LE16NL


Telephone (0533) 553508

ATARI CARTRIDGES




Atari Basic Programming. You'll get the basics of computer language and programming. What to say. And how to say it £34.50.

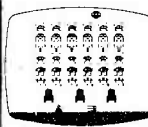Alarm mains units £98.50.
Keyboard controller £11.95
Orders being booked for Human Cannonball and Circus at £15.20.



SPACE INVADERS Game Program. The ultimate Game Programme with 112 game variations including Moving Shields, Zigzagging Laser Bombs, Fast Laser Bombs, Invisible Invaders and 1 & 2 Player Games! This superb cartridge uses the joystick controllers and costs only £27.50 incl. VAT plus 50p Post and Packing. Order Now!

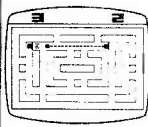Alarm with Space Invaders, call us for a special price.



It's you and your favourite adversary. pursuing one another through bleak big city streets. And blowing each other away with the barokas on your hoods.

The first to blast his opponent twenty-five times is the winner.

So get set for the wildest action since cops discovered robbers. £15.20. Orders now taken.

Slot racers™



GOLF — Now you can play golf at home, even in stormy weather. There are nine tournament-quality holes on Atari's course, each with a designated par. Total par for this course is 36 pars. When playing a one-player game, try to match or beat par. In a two player game, the winner is the player with the least amount of strokes. But swing carefully. There are the usual sandtraps, lakes and trees to avoid. The wrong play may cost penalty strokes. £15.20

ADVENTURE — Adventure plays like the addictive Dungeons and Dragons fantasy role playing board game and includes the added dimension of video. A wicked magician has stolen an Enchanted Goblet and hidden it somewhere in the Kingdom. The object of the game is to rescue the Goblet and replace it inside the Golden Castle where it belongs — no easy task. Three deadly dragons and a black bat hinder your quest, but scattered throughout the Kingdom are objects to help you slay the dragons and outwit the evil magician. £22.50 plus 50p P&P.


Kramer & Co., Dept. ET12, 29 October Place, London NW4.
Tel: 01-203 2473. Telex 888941. Attn.: K7.
Visa, Access, Barclaycard & Company orders accepted. Orders by telephone/telex. Open Mon.-Fri. (Sunday by appointment only).

NEW COMPONENTS

Pack No.	
A10	10 PP3 battery leads. 50p
A30	10 Red or black crocodile clips. 45p
A60	10 Red or black phone plugs. 80p
A61	10 single phono sockets. 70p
A70	10 2.5mm unscreened jack plugs. 80p
A72	10 3.5mm unscreened jack plugs. 80p
A73	10 3.5mm chassis sockets. 80p
A74	10 Standard mono jack plugs. 130p
A75	10 Standard switched jack sockets. 170p
A84	10 5 pin 180° DIN plugs. 120p
A85	10 5 pin 180° DIN chassis sockets. 100p
C10	5 Standard toggle switches SPST. 190p
C20	10 Miniature DPDT slide switches. 130p
C30	10 Miniature push to make switches. 130p
C31	10 Miniature push to break switches. 170p
C40	Pair of ultrasonic transducers. 350p
C50	20 Texas 8 pin sockets. 170p
C51	20 Texas 14 pin sockets. 200p
C52	20 Texas 16 pin sockets. 220p
E10	Resistor kit 10 each value 4.7Ω to 1M. 1/4W type. Total of 650 resistors. 480p
	1/4W 5% carbon resistors. 18p per 20
	Multiples of 20 per value only
E33	10 4.7uF 63V radial electrolytics. 50p
E34	10 10uF 25V radial electrolytics. 50p
E37	10 100uF 25V radial electrolytics. 75p
E44	10 1uF 35V tantalum capacitors. 100p
E50	10 0.01uF Mullard C280 polyester. 50p
E54	10 0.1 Mullard C280 polyester. 50p
F10	10 BC108 transistors. 90p
F15	10 BC184L transistors. 90p
F17	10 BC214L transistors. 90p
F25	10 2N3702 transistors. 80p
F26	10 2N3704 transistors. 80p
F27	10 2N3819 transistors. 190p
F29	10 2N3905 transistors. 300p
F41	4 2N3055 transistors. 200p
F46	5 7805 1A 5V regulators 300p
H10	20 1N4002 rectifier diodes. 75p
H50	20 0A91 signal diodes. 110p
H60	100 1N4148 signal diodes. 180p
H70	5 C1060 4A 400V thyristors. 200p
H75	5 TIC246D 16A 400V triacs. 520p
J10	20 0.2in red LEDs. 170p
J15	50 0.2in red LEDs. 400p
J20	100 0.2in red LEDs 750p
J30	20 0.2in green LEDs. 280p
J50	20 0.2in yellow LEDs. 280p
J80	4 FND500 displays. 350p
K10	5 741 operational amps. 8 pin. 90p
K25	5 LM301A operational amps. 8 pin. 140p
K30	1 LM324 operational amplifiers. 50p
K80	5 CA3140 operational amps. 225p
K90	5 NE555 timers. 110p
M10	8 2114LP memories. 2800p
N5	1 Dado printed circuit board pen. 80p

All prices include VAT. Please add 50p carriage on all orders below £10. Send SAE for our detailed list. Mail order only.

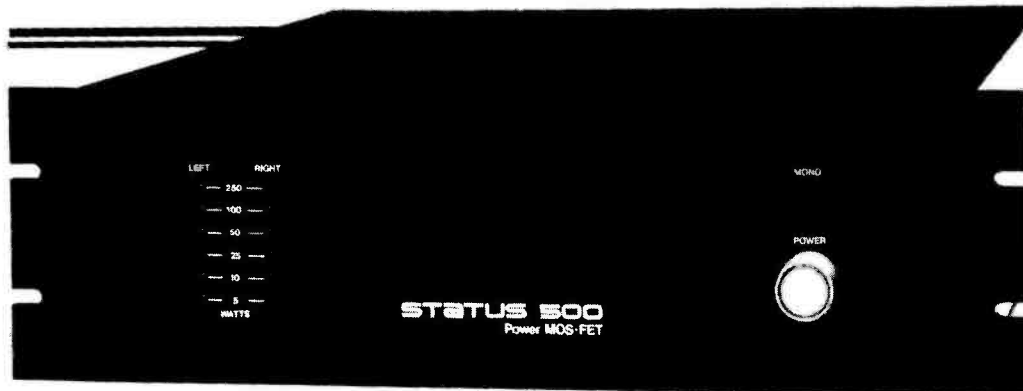RAPID ELECTRONICS
Hillcroft House, Station Road, Eynsford, Kent



Status Symbols

Raindrik of Downham Market Norfolk are now supplying the Status range of audio equipment. Their Status 500 power amplifier delivers 250 W per channel into 8R, using power MOSFET output stages. The Status 20 Stereo Con-

trol Unit is a rack-mounting system with a modular disc replay amplifier that can be remotely located, three band equaliser with continuously variable turn-over frequencies, built-in headphone amplifiers and external mains

power supply. The range will soon also include a parametric equaliser. You can get more information on the Status 500 and the rest of the Status range from Raindrik Ltd, Downham Market, Norfolk.

100 W Power Amp (August)

In Fig.7 on page 67, C1, 2 and 4 are shown the wrong way round. However, they are shown correctly on the component overlay.

In the Power Amplifier Board Parts List on page 68, R15 should be 10R 1W and R16 should be 10R 2W. In the DC Sensing Board Parts List on the same page R7 should be 4k7, R20, 23 are 82k, R18 is 1k0, R26 is 91k and R27 is 5k6. C1,2 and 11 should be 22u 16 V electrolytic and C9, 10 should be carbonate types.

The component overlays on page 69 are correct.


Music To Your Ears

Casio have brought out four new calculators to follow in the footsteps of their Melody Card M-80. They all have eight digits calculating capacity in four functions, with full percent and independent memory. Sliding the mode switch to 'music' converts them to an 11 note instrument for the user to play tunes on the numerals (0-9) and decimal keys.

The ML-720 is credit-card sized and is priced at £17.95. It is powered by two G-8 size batteries which last for 700 hours continuous calculating use. This is extended by an automatic power off function with full memory retention. The ML-860 is slightly bigger with a RRP of £16.95 and uses the larger G-10 batteries which last

almost twice as long as the G-8 type.

For £25.95 you have the choice of the ML-71 and the ML-81 which both tell the time as well. The ML-71 is credit-card size and keeps continuous track of time, with running second display and date and includes a one-tenth second stopwatch feature. It also has an alarm for any preset time of day as well as a countdown timer. The G-10 batteries last about a year. The ML-81 is larger again with the same facilities as the ML-71 plus an independent alarm. The two G-12 batteries last for 14 months continuous operation. All these calculators should be available from dealers soon.

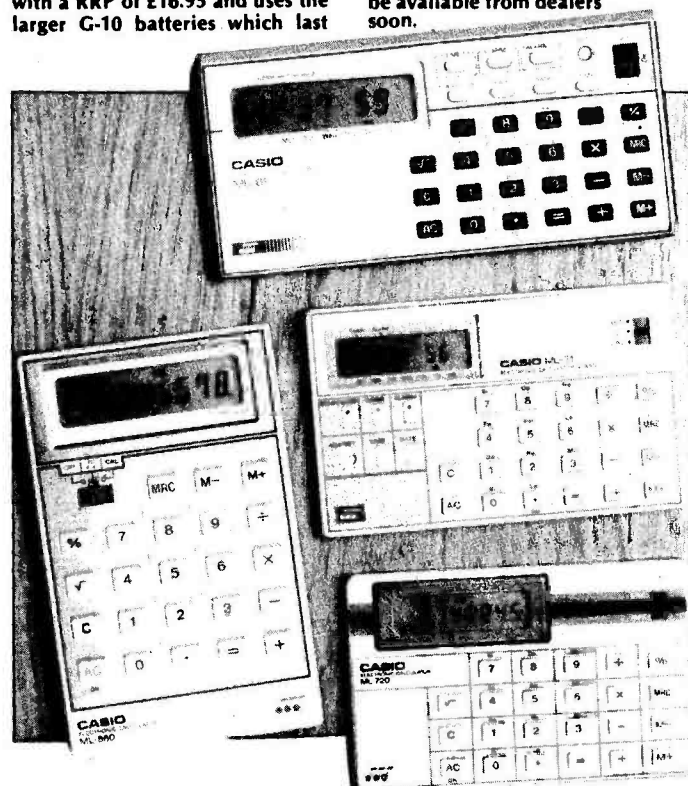


Black Hole (May 1980)

R21, R83 and C10 should be 1k0, 18k and 10nF respectively. A 39k resistor should be connected in series with C40. Cut the appropriate PCB track and solder the resistor across the break. A 1N4148 diode should be connected across each SAD512D input (soldered to the underside of the PCB). Later issue PCBs from Powertran will be suitably modified.

Kit News

TK Electronics' contribution to making legs obsolete should be available in September. It's a touch-controlled light dimmer with single alternate action touch plate. Nothing strange in that, you say. Well, TK have married their touch dimmer with an infra-red remote control system. So, you needn't leave your water bed, with infra-red light controller in one hand and ultrasonic TV controller in the other (and the two will not interfere with each other). TK's TDR300K 300 W Remote Controlled Lightdimmer will probably cost around £10. Watch their adverts in ETI for latest details. Meanwhile TK can supply an infra-red on/off light controller for £12 plus VAT (order model RC500K). A multi-channel infra-red remote control system for models, hi-fi, etc is also available separately.

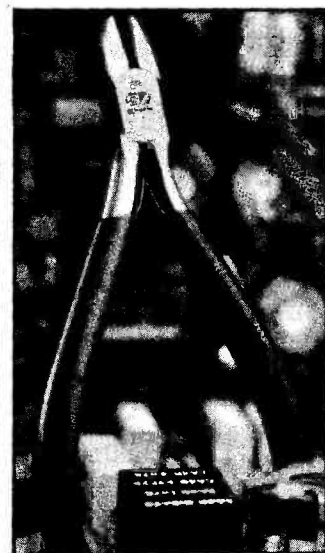Aura Sounds, who pioneered the introduction of Wersi organ kits in the UK, have been appointed marketing agents for Heathkit Electronics. Both companies and you and I come out on top — Heathkit broadens its sales representation, Aura Sounds expands its kit business and Heathkit products are a little more widely available to the likes of you and me.




Hard Wire Side Cutter

A new specialist side cutter for use in the electronics and electrical industries is now available from CeKa. Its hard wearing tungsten carbide tipped cutting edges provide the tool with long working life and cutting capacities of, for example, 0.6 mm on piano wire and 1.6 mm on hard electrode wire. The cutter is 4 1/2" in size and is box jointed for exact location, flush cutting and the prevention of cutting edge overlap. A smooth and controlled action while cutting in sensitive or confined situations is achieved by double leaf return springs. The cutter handles are covered by moulded black PVC grips. In addition to cutting hard wires, CeKa states that use of the side cutters continually on ordinary soft wire will make its working life almost indefinite. The RRP of the CK Precision Side Cutter is £19.40 plus VAT. The address is CeKa Works Ltd, Pwllheli, Gwynedd, North Wales.

MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

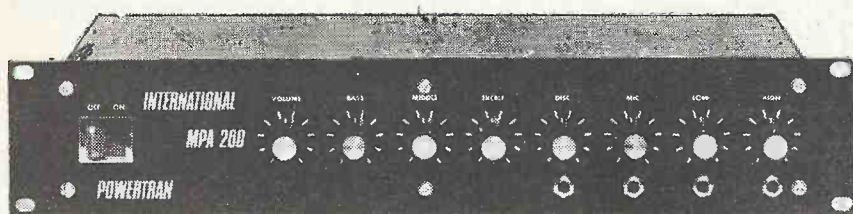

Panel size 19.0" x 3.5". Depth 7.3"

**COMPLETE KIT
ONLY**


£49.90 + VAT!

**MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!**

CHROMATHEQUE 5000 5 CHANNEL LIGHTING EFFECTS SYSTEM

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

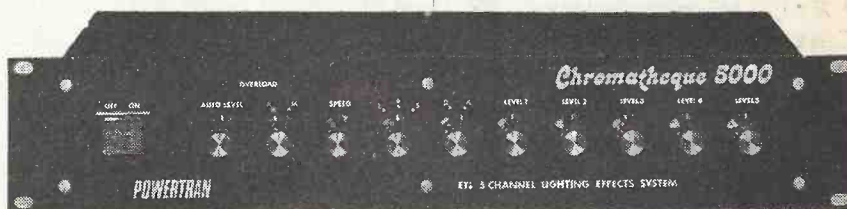Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!



Panel size 19.0" x 3.5". Depth 7.3"


COMPLETE KIT

ONLY

£49.50 + VAT!

POWERTRAN

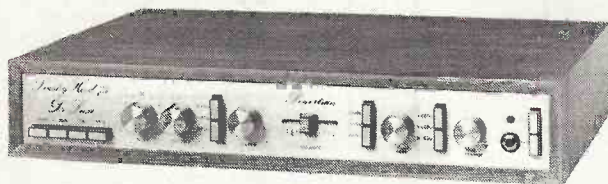
**SYNTHESIZER KITS ON PAGE 8. MORE KITS AND ORDERING
INFORMATION ON INSIDE FRONT COVER.**



**DE LUXE EASY TO BUILD LINSLEY HOOD
75W STEREO AMPLIFIER £99.30 + VAT**

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.

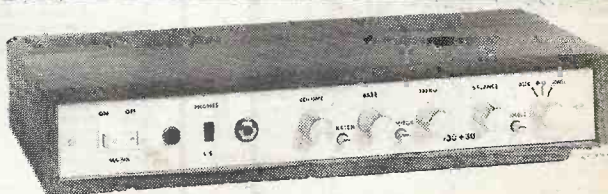All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



T20 + 20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30 + 30) is also available for £38.40 + VAT.

MATCHING TUNERS — See our FREE CATALOGUE!

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!

BLACK HOLE

**MUSIC EFFECTS DEVICE — AS FEATURED
IN ELECTRONICS TODAY INTERNATIONAL!**

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 + VAT (single delay line system)

De Luxe version (dual delay line system) also available for **£59.80 + VAT**

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



REMOTE CONTROL. 32-channel ultra-sonic infra-red transmitter I.C. (SL490) £2.85 each. 32 channel receiver IC.s (ML928+ML929) £3.60 pair. Complete data/projects booklet add 50p. P&P 25p. Datapad Developments, 81 Cholmeley Road, Reading, Berks.

POWERTRAN TRANSCENDENT DPX built to high professional standards available for only £350. Package includes swell pedal, handbook and "Anchor" tuition course. Phone High Wycombe (0494) 36923 (office hours).



**C
C
T
V

C
A
M
E
R
A**

£110.00
+ VAT (£16.50)

+ P/P £3.45 (inc. VAT)
Optional extra manual
£6. Total £129.95

BEST OFFER EVER

**Camera Kit, Lens,
Vidicon & Modulator**

CROFTON

Tel: 01-891 1923 For full details

VHF/FM TRANSMITTER KIT. New silicon chip design means low price (beats anyone else) and better performance. Very small — ideal bug etc. Fully tuneable 88-108 MHz. Instructions etc. all included. INTRODUCTORY OFFER £2.45 + 30p P&P (unlicensable). M. Henry, Dept. ET1, 30 Westholme Gardens, Ruislip.

TRANSCENDENT 2000. Synthesizer. Fully set up and in perfect working order. Must sell, hence £200 only. Phone Worcester 354450 (evenings or weekends).

BOOKS BOOKS BOOKS — Large range of electronics books in stock. Send s.a.e. for list. Servio Radio, Dept ET1 10, 156-8 Merton Road, Wimbledon SW19 1EG.

A SUPERB VALUE STEREO POWER AMPLIFIER OFFER • Stabilised PSU: 2N 3055 output • Stereo 60 watt RMS; IC Preamp. Case includes, controls volume, selector etc., din output/inputs for magnetic pick-up/microphone (3.mv) + Tuner + Tape/Aux. 26 transistors — 2 IC Screened Douglas Transformer, 240 V AC mains lead. NEW—TESTED—DATA £19.95 (inclusive). KLIFCO ELECTRONICS, 1 REGENT ROAD, ILKLEY, W. YORKSHIRE LS29 9EA.

MSF TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, self-setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto, GMT / BST and leap year, also parallel BCD output and can record when an event occurs, receives Rugby time signals, 1000Km range, ACCURACY, £54.80.
60KHZ RUGBY RECEIVER, as in MSF Clock, serial data output, built-in antenna, £15.70.
V.L.F. 7 EXPLORE 10-150KHz Receiver £13.70.
Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (TJ) Old School Lane, Milton, Cambridge

BRAND NEW COMPUTER POWER SUPPLIES: —250v. 400mA. —12v. 2A. +30v. 400mA. +12v. 500mA. and +5v. at a staggering 12A!! Admirably Engineered Units. £35 + £3.50 carr/insurance. Sold tested and working but without guarantee. Payment with order to: J. Wright, 27 Broomhill Drive, Glasgow G11 7AB.

NUCLEAR RADIATION MONITOR. Essential for the survivor of a nuclear attack. Measures up to 100 rads/hour. S.a.e. details: Ray, Nucleonics, 13 Rosemead Gardens, Brentwood CM13 1HZ.

INTENSIVE COURSES IN

BASIC AND PASCAL

including hands on mini-computer operation

These intensive courses are intended to instruct from minimal knowledge to an operational capability of computer programming. Courses are fully residential, allowing maximum time for instruction and programming.

BASIC — Weekends from Friday Evening to Sunday Afternoon.

PASCAL — Weekdays Monday Morning to Friday Afternoon inclusive.

For further details, dates available, fees
Phone (0401) 43139, or write

CLEVELAND BUSINESS SERVICES
(Dept. ET1-2), Cleveland House
Routh, North Humberdale HU17 9SR

MAIL ORDER ONLY

DELTA TECH & CO.

62 NAYLOR ROAD, LONDON, N20 0HN

Please add 35p for P&P

RESISTORS (5% £12)

10 Ohms to 10Mohms 1.5p

PRESETS (.15W HORIZONTAL) 7p

100 Ohms to 2 Mohms

POTENTIOMETERS (1/4W)

Linear & Log Scales

4.7KOhms to 2.2Mohms

VEROBARDS (.1" COPPER)

2.5" x 5" 55p

3.75" x 5" 65p

ZENER DIODES (400mW)

5V6 5p* 9V1 8p

2V7 to 33V 8p

POLYSTYRENE CAP (50V)

10 pF to 1000 pF 5p

CERAMIC CAP (50V)

33 pF to 4700 pF 3p

POLYESTER CAP (100V)

1 nF to 68 nF 6p

100 nF 150 nF 7p

220 nF 330 nF 9p

470 nF 11p 680 nF 13p

1uF: 18p 2.2uF: 22p

3.3uF: 15p* 4.7uF: 15p*

ELECTROLYTIC CAP (uF/V)

1/25 to 47/25: 6p 68/25: 10p/35 8p

150/25: 8p 160/25 4p*

220/25: 10p 470/25: 9p*

640/16: 5p* 1000/10: 5p*

1000/25: 22p 200/12: 6p*

1500/25: 12p* 2200/6.3V 10p*

OPTO/ELECTRONIC

2N5777 55p

OC71 65p

ORP12 70p

DL704 110p

DL707 110p

0.125" & 0.2"

LEDs:

Red 10p

Green 13p

Yellow 13p

0.125" Clip 3p

0.2" Clip 4p

BRIDGE

RECTIFIERS

W02M 20p

W06M 30p

1A/50V 22p

1A/100V 27p

1A/200V 32p

1A/400V 34p

2A/50V 40p

2A/100V 42p

2A/200V 48p

2A/400V 55p

THYRISTOR

2N5064 *12p

VOLTAGE

REGULATORS

7805 65p

7812/15 65p

7818/24 65p

7905 75p

7912/15 75p

7918/24 75p

DIL SOCKETS

8 pin *7p

14 pin *9p

16 pin *10p

18 pin 16p

22 pin 20p

24 pin 21p

28 pin 25p

40 pin 35p

OIOOES

BY127 12p

OA47 8p

OA91 *6p

OA200 6p

OA202 9p

1N916 5p

1N4148 4p

1N4001/2 4p

1N4003 5p

1N4004/5 6p

1N4006/7 8p

1N5400 13p

1N5401 14p

1N5402 15p

1N5404 16p

LINEAR

CIRCUITS

709-8 28p

710-14 35p

741-8 20p

747-14 50p

748-8 35p

CA3018 70p

CA3028A 85p

CA3046 50p

CA3080E 75p

LF351N 44p

LF356N 85p

LM301AN 30p

LM308N 55p

LM318N 120p

LM318H 120p

LM324N 57p

LM339N 52p

LM348N 90p

LM377N 175p

LM380N 90p

LM381N *120p

LM382N *90p

LM1310N 115p

LM1458 *35p

LM3900N 50p

LM3909N 75p

MC1496P 80p

NE531 110p

NE555 22p

NE556 *45p

NE566 140p

SN76115 *80p

TBA641B 200p

TBA800 75p

TBA810S 110p

ZN414 100p

ZN1034E 220p

CMOS AE

*4000 16p

4001B 18p

4002 15p

4006B 70p

4007 *17p

4008 80p

4009 40p

4010 44p

4011B 15p

4012 20p

4013B 35p

4014 80p

4015B 75p

4016 44p

4017 55p

4018 80p

4019 45p

4020B 95p

4021 85p

4022 *70p

4023 22p

4035 107p

4041 75p

4042 70p

4043/4 88p

4047 92p

4048 55p

4049 35p

4050B 44p

4066 50p

4069 *16p

4070B 20p

4071/2 20p

4073 20p

4081/2 20p

4086 80p

4088 80p

4090 100p

4511B *70p

4516/8 100p

4520/8 100p

TTL

7400/1 14p

7402/3 14p

7404/5 16p

7406 23p

7407 25p

7408/9 17p

7410 13p

7411/2 17p

7413 21p

7414 45p

7416 20p

7417 25p

7420 15p

7421 30p

7422 26p

7427 20p

7428 28p

7430 16p

7432 20p

7437 14p

7438 18p

7440 13p

7441 52p

7442 32p

7443 60p

7444 100p

7445 64p

7446 65p

7447A 45p

7472 19p

7473 *16p

7474 *17p

7475 26p

7476 20p

7480 32p

7485 80p

7486 18p

7490 *22p

7491 57p

7492 30p

7493 *20p

7494 50p

7495

CLASSIFIED

RATES

1-3 insertions £6 per scc
4-11 insertions £5.50 per scc
12 insertions £5.00 per scc
23p per word (Min. 20 words)
Box No. of application

All advertisements in this section must be pre-paid
Closing Date:- 1st Fri. month preceding publication

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE.

TEL: 01-437 1002 Ext. 26

MODULAR SENSOR SYSTEMS

SPEED SENSOR £10.95
FLOW SENSOR £13.65

Signal processing/display systems:

Gal/Hr PCB and 4 digit display without case requires 5V DC 400 cycles input time base £34.80
L/Hr PCB and 4 digit display without case requires 5V DC 320 c/sec time base input £35.95
RPM Complete system in case with reset. 12V DC power supply £29.95
Total Galls Complete system in case. 12V DC power supply £44.75
Total Litres
MPG, Km/L
or L/100 Km

All above prices include VAT, p&p UK. These systems are ideally suitable for automotive and other speed/flow measurement projects.

ENVIROSYSTEMS LTD.

Hampfell Road, Grange-over-Sands, Cumbria LA11 6BE
Telephone: 044 84 4233/4

Clips onto logic I.C. to show 16 bits

DIGISCOPE

● Switch selects CMOS or TTL levels
● 5-15V working
● 16 LED display

£27.40 complete - or send for data:

J. E. Sinclair & Co (F1)
82 Plumstead Common Road
London SE18 3RE

MK14 CORNER. Interface Board, includes flag driven mains relays, LED Indicators for all Serial I/O, D/A and single step chips, and prototype area; also suitable for other Micro-computers; PCB and circuit £3.95. Replace calculator display with 1/2" FND 500s; PCD, filter, instructions £1.95. Ready-built replacement keyboard £11. Useful notes on MK14 75p. Rayner, "Kismet", High Street, Colnbrook, Bucks.

DO YOU TRANSMIT AUDIO SIGNALS OVER CABLE CIRCUITS?

We manufacture a full range of interface equipment for transmission of audio signals over private wire of telephone circuits, from Narrow Band STD systems (300Hz-3.4kHz) up to Wide Band Music Circuits.

PARTRIDGE ELECTRONICS

(A. C. Partridge Ltd.)

56 Fleet Road, Benfleet, Essex

Tel: (STD 03745) 3256

We also manufacture audio mixers and sub-assemblies

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components
Full range of HE printed circuit boards, normally ex-stock, same day despatch at competitive prices.
P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Alfac range of etch resist transfers, and other drawing materials for p.c. boards.


Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES

MASONS ROAD
STRATFORD-ON-AVON
WARWICKS, Tel. 4879

CIRCUIT DESIGN. Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

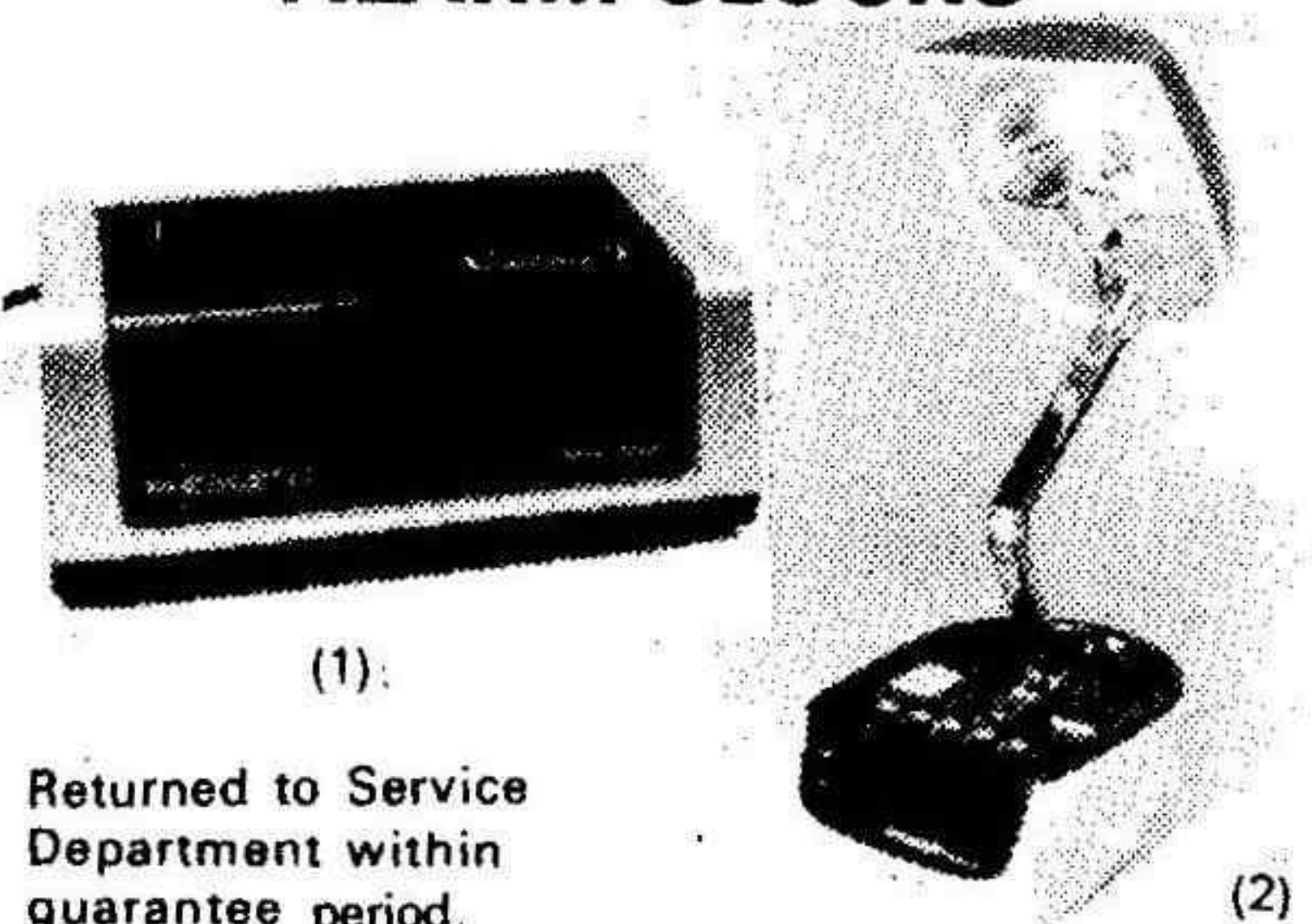BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

1. With alarm repeat. S.R.S.P. of £17.00. Offered at £3.95, inc. VAT, or 3 for £9.95, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00. Offered at £7.95 inc. VAT each, or 3 for £19.95 inc. VAT.

These will be sold as received from our customers with the existing fault(s) and without guarantee. U.K. only

Discounts available on large bulk purchase.

PRESCOTT CLOCK & WATCH CO. LTD.

PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No
100 ALARM TRIGGER MODULE. 100% Solid State. Battery operation. Pos. & Neg. Rings. N/C for 4-wire contacts. N/O for Mats, etc. One Amp Switching Capacity. Only £9.95
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT + matching magnet £1.10
220 Surface 4-wire MAGNETIC REED CONTACT £1.60
240 PRESSURE MAT. Standard size 4-wire 30"x15" £2.20
250 PRESSURE MAT. Stair size 4-wire 23"x6 1/2" £1.73
260 VIBRATION DETECTOR. Pendulum type in Ivory Case with contacted Lid + self-adhesive backing. Adjustable sensitivity £3.50
360 SIX INCH UNDER DOME BELL £9.95
390 BEST QUALITY BELL HOUSING. PVC coated metal, not to be confused with the cheaper decoy covers. Fully signwritten with our Centurion Insignia £9.50
400 DECOY P.V.C. BELL COVER £6.50

Note: All equipment operates on 12 Volts DC.
710 SCOOP OFFER SMOKE ALARMS. Self-contained ionisation Type (1.5% obscuration) with low battery warning at the UNREPEATABLE PRICE of only £8.75 While Stocks Last!!!
Terms: Add 15% VAT to Prices + 40p Postage & Packing.



No Minimum Order.
Access telephone orders welcome on: 0484-35527 or send S.A.E. for Full List to:

CENTURION ALARMS & ELECTRONIC SALES, Dept. ETI, 265 Wakefield Road, Huddersfield, W. Yorks HD5 9BE

LARGEST STOCKS ANYWHERE sheets, and manuals. Service sheets only £1 + s.a.e. Sole suppliers of the famous TV Repair Systems. Complete Diagram Collection. Mono TV/Washing Machines/Col. TV/etc., in huge binders, only £13.50 each. SAE brings newsletter bargain offers, quotes: G.T., 76 Church Street, Larkhall, Lanarkshire (0698) 883334.

200 COMPONENTS £4. 100 diodes 85p. 150 caps £1.50. 100 resistors 85p. All mixed. Lists 15p. Sole Electronics (ETI), 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

TRANSCENDENT DPX Polyphonic Synthesizer, fully working, mint condition, professionally constructed. Save approximately £100 on kit and construction costs! For sale, £299. Telephone: 0282 35680 (Burnley).

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries - you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (ETI6)

11 Percy Avenue, Ashford, Middx. TW15 2PB

BARGAIN PACKS

£1 + 25p P.P. ea

Best quality NEW components at silly prices
Wolwyn, Plessey, Wima, Pye, Sprague, etc

50 x 4.7µF/10V Tub Tantalum
50 x 0.1µF/100V Radial Polyester
20 x 0.22µF/250V Radial Polyester
80 x 0.01µF/400V Axial Polyester
10 x 16µF/450V Tag and Lytics
15 x 32µF/150V Tag and Lytics
20 x 1000µF/10V Wire and Lytics
5 x 10µF/100V Metal Film
2 x 4500µF/25V Screw Term Computer-grade Lytics
6 x 50µF Jackson Variable - Screwdriver adj.
40 x BC107 OR BC109 OR BC170. New - leads crimped short - but usable.
40 assorted high capacity polystyrene between 1n5 and 47nF.
30 assorted axial - WIMA type between 1µF and 4.7µF.
200 assorted 1/4W low noise Metal Oxide resistors.
5 x 1µF/350V at 70°C Tub Paper - suitable electronic ignitions, etc.
Full refund if not delighted

T. SCOTT, 37 Regent Street, Rowhedge, Essex

TRANSFORMERS MANUFACTURED to specification, many popular types ex-stock. Fast turn around on volume production. Send enquiries to Louth Transformers, Queen Street, Louth, Lincs. Tel: (0507) 606436.

TRANSCENDENT 2000 SYNTHESISER. Fully operational, with foot pedal and reverb unit, must sell, £160. Phone Colchester (0206) 211309, evenings.

MAPLIN DISCO UNIT, only needs light unit fitting. Unit tested and used twice, fan cooled heatsinks. Very robust case. Offers around £180. Also Maplin Organ MESS 1/2/3/4. All PCBs finished and working (unit built and disassembled owing to moving house). Two 61-note keyboards, 13-note pedalboard, rotating base speaker unit, drawbars and stop tabs, reverb. Offers please. Tel: 01-445 8336.

ADAM HALL

Cabinet & Flightcase Fittings, fretcloths, coverings, handles, castors etc., Jacks & sockets, Cannons, Bulgins, reverb trays, Emular compression drivers, AKG mics, Celestion speakers, ASS glassfibre horns.

Send 30p postal order for illustrated catalogues to:
ADAM HALL (E T SUPPLIES)
Unit B, Charlton Court
Grainger Road, Southend-on-Sea
Essex SS2 5BZ

ZX80 GAME. Ingenious and challenging 1-2 player game of capture for 1K ZX80. Fully documented. Send £1.50 to HINDLE, 139 Penrhyn Road, Sheffield, S11 8UP.

SPEED — VERSATILITY — ECONOMY



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers, to carry out work on:—
*P.C.B. REPAIRS *ANALOGUE BREADBOARDING *SIMPLE LOGIC WIRING *COMPLEX INTERCONNECTING OF MICROS AND MEMORIES.

EURO INTROKIT £14.84. PROJECT INTROKIT £8.27. PENCIL WITH LOADED BOBBIN £2.44. WIRE DISTRIBUTION STRIPS—GLUE FIX 20/pkt 6" LONG £2.80. ADHESIVE 0-36/TUBE. PRESS FIX 20/pkt 2" LONG £2.92. SINGLE EUROCARD HIGH DENSITY 3 PLANE (36x16 PIN DILS) £4.50. DOUBLE EUROCARD, WITH CAPACITY OF 84x16 PIN DILS £7.25. PROJECT CARD HIGH DENSITY S-SIDED 20x14 PIN DILS £2.85. BOBBINS - BLUE 4/pkt £2.12 GREEN 4/pkt £2.12 PINK 4/pkt £2.12 GOLD 4/pkt £2.12. 1 OF EACH COL. £2.20. TINNED COPPER WIRE 4/pkt £2.12. RECOMMENDED SOLDERING IRON FOR ROADRUNNER HOBBYIST £4.80.

Please add 40p for p&p + 15% VAT to all orders.

FOR FURTHER INFORMATION
ON ROADRUNNER PRODUCTS
SEND LARGE S.A.E. TO:—

T.J. BRINE ASSOCIATES,

116 Blackdown Rural Industries
Haste Hill, Haslemere, Surrey

**TRS 80
SOFTWARE
NOW
AVAILABLE**

**CROFTON
ELECTRONICS
LIMITED**

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD Tel: 01-891 1923

50Hz SUPERBOARDS

BRITISH MODEL

NOW FROM £159.95

+ 1/3 VAT + P&P

Fully built, set up and tested
Accessories, software metal cases, etc.

AUTHORISED dealer back-up

C.T.S., 1 Higher Calderbrook
Littleborough, Lancs.
Tel. Littleborough 79332
any time

CB CITY

PROUDLY PRESENT

NEW

ACCESSORIES CATALOGUE SHOWROOM

Telephone:

ALDERSHOT

0252 318141

Monday-Saturday

9 a.m.-6 p.m.

(NO RIGS)



ADVERTISEMENT INDEX

ACORN COMPUTERS	32	I.L.P.	20 & 21
AJD DIRECT SUPPLIES	100	INTERFACE COMPONENTS	68
ALTEK INSTRUMENTS	97	KEELMOOR LTD	77
AMBIT INTERNATIONAL	26	KODE SERVICES	46
AUDIO ELECTRONICS	90	KRAMER & CO	109
AURA SOUNDS	35	LASCAR ELECTRONICS	52
BAYDIS	68	LB ELECTRONICS	76
BK ELECTRONICS	72	L&B ELECTRONICS	101
B.N.R.S.	43	MAPLIN	116
BUTTERWORTHS	100	MARSHALLS	108
CLACULATOR SALES & SERVICE	97	METAC	10
CAMBRIDGE LEARNING ENTERPRISES	107	MICRO CIRCUITS	42
C.B. CITY	113	MICRO-PRINT LTD	68
CHILTMead	78	MITRAD	47
CHROMASONICS	67	MOUNTAINDENE	45
CLEF PRODUCTS	99	E. R. NICHOLLS	109
CODESPEED	109	NIC MODELS	52
COMMODORE	71	POWERTRAN	2, 8 & 110
COMP. COMP. COMP	114 & 115	PROGRESSIVE RADIO	106
CRIMSON ELEKTRIK	109	RAPID ELECTRONICS	109
CROFTON ELECTRONICS	52	J. W. RIMMER	43
C.S.C.	33	R.T.V.C.	22
CYBER ELECTRONICS	76	SAFGAN ELECTRONICS	91
DELTA TECH & CO	111	SCIENCE OF CAMBRIDGE	4 & 5
DISPLAY ELECTRONICS	38	SILICA SHOP	100
DORAM ELECTRONICS	56	SPECIAL PRODUCTS DISTRIBUTORS	91
DOVE ELECTRONICS	46	C. N. STEVENSON	92
E.D.A.	46	SURETRON	13
ELECTRONIC MAIL ORDER	68	SWANLEY ELECTRONICS	57
ELECTROVALUE	92	TANGERINE	36 & 37
ENVIRO SYSTEMS	99	TECHNOMATIC	6
GMT ELECTRONICS	97	TEMPUS	84
GREENBANK	51	TIMEDATA LTD	76
GREENWELD	90	TK ELECTRONICS	108
HAMEG LTD	70	TRANSAM COMPONENTS	27
HAPPY MEMORIES	76	T&T ELECTRONICS	92
HENRY'S RADIO	57 & 86	WATFORD ELECTRONICS	12 & 13
I.C.S.	91	WEST HYDE DEVELOPMENTS	106
		WILMSLOW AUDIO	43

BITS & BYTES

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes	10 for £4.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Discs 5 1/4" Hard and Soft Sector	£3.50
Floppy Disc Library Case 5 1/4"	£3.50
Verocases for Nascom 1 & 2 etc.	£24.90
Keyboard Cases	£9.90

MEMORY UPGRADES

16K (8 x 4116) £29.90 + VAT

4K Compukit (8 x 2114)
£29.90 + VAT

EPROM 2716 £12.50 + VAT


COMP PRO MIXER

Professional audio mixer that you can build yourself and save over £100.

6 into 2 with full equalization and echo, cve and pan controls.

All you need for your own recording studio is a stereo tape or cassette recorder.

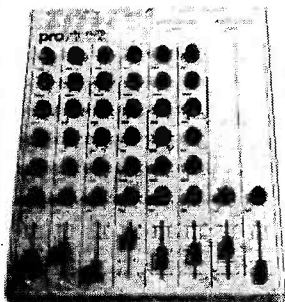This superb mixer kit has slider faders, level meters and additional auxilliary inputs.



Only **£99.90**
plus VAT for
complete kit

Plus FREE
power
supply
valued at
£25.00

Ideal for
DISCOS STAGE MIXING
HOME STUDIOS AND MANY
OTHER APPLICATIONS

NEC SPINWRITER

only
£1490
+ VAT



NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel, giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds. 55 characters per second bidirectional printing — with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.



HITACHI PROFESSIONAL MONITORS

9" — **£129**
12" — **£199**

● **Reliability** Solid state circuitry using an IC and silicon transistors ensures high reliability. ● **500 lines horizontal resolution** Horizontal resolution in excess of 500 lines is achieved in picture center. ● **Stable picture** Even played back pictures of VTR can be displayed without jittering. ● **Looping video input** Video input can be looped through with built-in termination switch. ● **External sync operation** (available as option for U and C types) ● **Compact construction** Two monitors are mountable side by side in a standard 19-inch rack.

RRP
£540



only


£399
+ VAT
**ANADEx
DP8000**

Super Quality — Low cost printer. Tractor Feed with full 96 ASCII character set. Accepts RS232C at baud rates between 100 and 9600 and Parallel Bit data. Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, Compukit etc.



THE NEW ANADEx DP9501

A PROFESSIONAL PRINTER

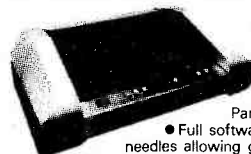

- Bi-directional printing
- Up to 220 chars/line with 4 print densities
- 500 char buffer
- RS232C and Centronics
- Parallel interface built in
- Full software control of matrix needles allowing graphics capability
- 200 chars/sec ● Adjustable width tractor feed.

All this for only **£895** + VAT.

COMPUPHONES


**YOU NEED NEVER MISS AN
IMPORTANT CALL AGAIN
TWO CORDLESS TELEPHONE
SYSTEMS — DIRECT FROM USA**



THE ALCOM

only **£147** + VAT

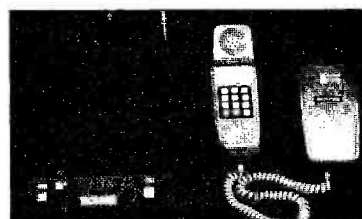
Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling — Bleeps when call arriving — Nicad rechargeable batteries. Charger in base unit.



THE BOHSEI

only **£125** + VAT

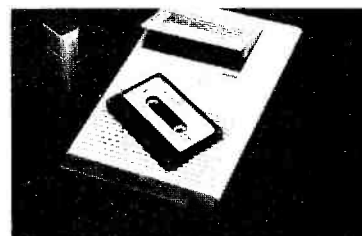Base station connects to your telephone line. Remote handset stylishly designed in red — Push button dialling comes complete with charger unit for batteries in handset.



LOW COST TELEPHONE ANSWERING MACHINE

only
£99.95
+ VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

COMMERCIAL ● EXPANDABLE ● COMPLETE TRS 80 - MODEL II



This new unit from the world's most successful micro company is now available immediately with software.

The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another 1/2 million extra characters including the disc operating system. More disc expansion is now available.

The Model II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic.

A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation.

Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can operate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

64K 1-Disk Model II **£1995.00** + VAT
RRP £2250.00

1 DISK EXPANSION Room for 3


500K per Drive gives total
of 1.5M Byte — 1 Drive plus Cabinet **£799** + VAT

CP M2	£95.00
CIS COBOL	£400.00
C BASIC	£75.00
M BASIC	£155.00
FORTRAN	£220.00
WORDSTAR	£255.00



COMING SOON

26 megabyte
Hard Disc
multi-user
DOS

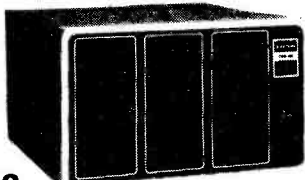

**WE USE THIS
MACHINE IN OUR BUSINESS**

NOBODY CAN GET NEAR OUR PRICES EXCEPT OUR CUSTOMERS



COMMERCIAL • EXPANDABLE • COMPLETE TRS 80 • MODEL II

EXTENDED
WARRANTY BY
COMPUKARE

This new unit from the world's most successful micro company is now available immediately with software.

The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another 1/2 million extra characters including the disc operating system. More disc expansion is now available.


The Model II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic.

A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation.

Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can operate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

COMING SOON

26 megabyte
Hard Disc
multi-user
DOS

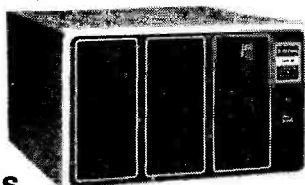

WE USE THIS
MACHINE IN OUR BUSINESS

64K 1-Disk Model II **£1995.00** - VAT
RRP £2250.00

1 DISK EXPANSION


Room for 3

500K per Drive gives total
of 1.5M Byte — 1 Drive plus Cabinet **£799** + VAT

CP/M2	£95.00
CIS COBOL	£400.00
C BASIC	£75.00
M BASIC	£155.00
FORTRAN	£220.00
WORDSTAR	£255.00

COMPUKIT UK101

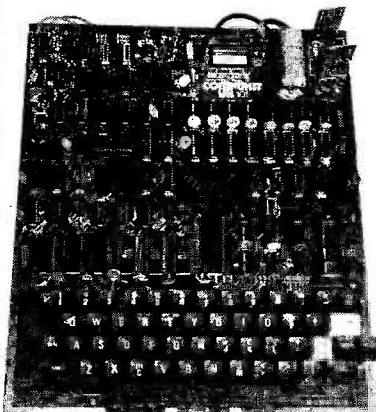EUROPE'S FASTEST SELLING
ONE BOARD COMPUTER



- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape Interface on board.
- ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for CompuKit expansion **£8.50** + VAT

Build, Understand and Program your own
Computer for only a small outlay

KIT ONLY **£179** + VAT
NO EXTRAS NEEDED

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programmes. By pressing the C key the world of Basic is open to you. This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use. Because of the enormous volume of users of this kit we are able to offer a **new reduced price of £179** + VAT

Available ready assembled, tested & ready to go **£229** + VAT

NEW MONITOR FOR COMPUKIT UK101

- In 2K Eprom 2716
- Allows screen editing
- Saves data on tape
- Flashing cursor
- Text scrolls down **£22.00** + VAT

BITS & BYTES

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes	10 for £4.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Discs 5 1/4" Hard and Soft Sector	£3.50
Floppy Disc Library Case 5 1/4"	£3.50
Verocases for Nascom 1 & 2 etc.	£24.90
Keyboard Cases	£9.90

FOR THE COMPUKIT

Assembler/Editor	£14.90
Screen Editor Tape	£5.90

Game Packs

1. Four Games	£5.00
2. Four Games	£5.00
3. Three Games 8K only	£5.00
Space Invaders	£5.00
Chequers	£3.00
Real Time Clock	£3.00
Case for CompuKit	£29.50

All Prices exclusive VAT

EXTENDED
WARRANTY BY
COMPUKARE

We give a full one
year's warranty
on all our products.

We now have in stock
demonstration models of the
Atari 800 and Texas 99/4.
COME AND SEE THEM

SPECIAL OFFER

We will part exchange your Sinclair ZX80
for any of our products.

Refurbished ZX80's—fully guaranteed **£69.90**
(Supply dependant upon stocks). + VAT



We have one of the largest collections of Computer Books under
one roof, along with racks of software for the PET and TRS80.

COME AND SEE FOR YOURSELF

NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really
get hooked. As featured in ETI. Has also 4 other pinball games
and lots of options. Good kit for up-grading old amusement
games.

MINI KIT — PCB, sound & vision modulator, memory chip
and de-code chip. Very simple to construct. **£14.90** + VAT
OR PCB **£2.90** MAIN LSI **£8.50** Both plus VAT



COMP SHOP
"Europe's Largest Discount
Personal Computer Store"

Please add VAT to all prices — including delivery. Please make cheques and postal orders payable to
COMPSHOP LTD., or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or
AMERICAN EXPRESS number.

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G

Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday

Close to New Barnet BR Station — Moorgate Line.

★ **NOW in IRELAND** at: 80 Marlborough St., Dublin 1. Tel: Dublin 749933

★ **COMPSHOP USA**, 1348 East Edinger, Santa Ana, California, Zip Code 92705.
Telephone: 0101 714 5472526



COMP COMPUTER
COMPONENTS

(Part of the CompsShop Ltd. Group)



STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____



MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS
 DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/
 P.O. or BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL
 INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY
 WELCOME. P & P ADD 40p TO ALL ORDERS UNDER £10. OVERSEAS ORDERS
 POSTAGE AT COST. AIR/SURFACE ACCESS ORDERS WELCOME.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground / BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

ELECTRONIC CAPACITORS: (Values are in μ F) 500V: 10 50p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8p; 10, 15, 22, 11p; 32, 47, 50, 12p; 63, 100, 27p; 50V: 50, 100, 220, 25p; 470, 77p; 1000, 60p; 40V: 2, 3, 3.3, 8p; 100, 12p; 2200, 3300, 85p; 4700, 98p; 35V: 10, 33, 7p; 330, 470p

32p: 100x, 10y, 47, 100 8p; 160, 220, 250, 15p; 470 25p; 640, 1000 35p; 1500, 400 2200; 425p
330p: 77p; 4700 85p; 16V, 10, 47, 7p; 100, 125, 8p; 220, 330, 140, 470, 20p; 1000, 1500, 330, 2200
36p: 10V, 100, 7p; 640, 12p; 1000, 16p
TAG-END TYPE: 450V: 100 μ F 180p; 70V: 4700, 1000, 185p; 64V: 3300 150p; 2500 110p; 50V: 4700
150p; 3300 135p; 2200 99p; 40V: 4700 130p; 4000 92p; 3300 88p; 2500 90p; 30V: 4700 110p; 25V:
15000 195p; 6400 120p; 4700 100p; 3300 85p; 2200 80p.

POLYESTER CAPACITORS: Axial lead type.
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n **8p**; 18n **10p**; 22n, 33n **11p**; 47n, 68n **14p**; 100n 17p
 150n, 220n **22p**; 330n, 470n **41p**; 680n **48p**; 1 μ F **64p**; 2 μ **82p**.
160V: 10nF, 12n, 39n, 100n, 150n, 220n **11p**; 330n, 470n **19p**; 680n, 1 μ F **22p**; 2.2 μ F **32p**; 4.7 μ F **36p**.
1000V: 10nF, 15n **20p**; 22n, 22n **26p**; 100n **38p**; 470n **53p**; 1 μ F **175p**.

POLYESTER RADIAL LEAD CAPACITORS: 250V: 10n, 15n, 22n, 27n 5p ; 33n, 47n, 68n, 100n 7p ; 150n 10p ; 220n, 330n 13p ; 470n 17p ; 680n 19p ; 1 μ 22p ; 1 μ 5 30p ; 2 μ 2 34p .	COMPUTER ICs 2102 125 2102-2 225
--	---

TANTALUM BEAD CAPACITORS	POTENTIOMETERS: Rotary, Carbon,	2112-2	250
35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68,	Track, 0.25W Log & 0.5W Lin. 470 Ω ,	2114-450n	298
1K, 2K, 5K, 10K, 20K, 50K, 100K.	680 Ω , 1K Ω & 2K Ω (linear only) Single,	2114-300n	398
		270R	408

1-0p, 2.2μF, 3-3, 4-7, 25V; 10, 20V;	600V; 100V 2 200V (small) 10V; 20V	29p	2708
6u8, 16V; 2u2, 4u7, 10 15p.	Gang	29p	27108
18V; 22u 28p, 47, 100 50p. 220 80p;	5KΩ-2MΩ Single Gang Log & Lin.	29p	4116
10V; 15u, 22u, 33, 24p; 100u 35p;	5KΩ-2MΩ Single Gang D/P Switch	89p	4047
	5KΩ-2MΩ Single Gang Log & Lin.	89p	4052

6V: 47 μ , 68, 100 28p; 3V: 100 20p.	5K1-2M1 Double Gang Log & Lin	85p	6502	99p
	Wire Wound Single Turn 1 Watt		6503	85p
	200 20K Ω	105p	6504	78p
			6505	85p

0-015, 0-02, 0-04, 0-05, 0-056 μ F	7p	SLIDER POTENTIOMETERS	6520	521
0.1 μ F, 50p, 50V: 0.47 μ F	12p	0-25W log and linear values 60mm	6522	821
CERAMIC CAPACITORS 50V		5K Ω -500K Ω single gang	6532	1050
		10K Ω -500K Ω dual gang	6551	1150
			80p	
			80p	

Range: 0.5pF to 10,000pF	4p	Self Stick Graduated Bezels	33p	6800	804
0.015 μ F, 0.022 μ F, 0.033 μ F	5p			6810	364
0.047 μ F 5p, 0.1 μ F, 0.2 μ F	7p	PRESET POTENTIOMETERS		6821	504
	12p	0.1W 500 Ω - 5M Ω Miniature Vertical		6850	484

SILVER MICA	(Values in pF) 3-3, 4-7,		
6-8, 10, 12, 18, 22, 33, 47, 50, 68, 75,			
82, 85, 100, 120, 150, 220	11p each		
250, 270, 300, 330, 360, 390,			

470, 600, 800, 820	16p each	Cermet, Precision, multturn, 0.75V/4in	81LS95	13
1000, 1200, 1800, 2000	26p each	100Ω-100KΩ	81LS96	13
POLYSTYRENE CAPACITORS:			81LS97	14
		RESISTORS — Erie make 5% Carbon	8251	70

10pF to 1nF 22p	1.5nF to 47nF 10p	MINIATURE TYPE TRIMMERS	2.5-6pF; 3-10pF; 10-40pF 22p
------------------------	--------------------------	-------------------------	-------------------------------------

5-25pF; 5-45pF; 60pF; 88pF	30p	1/4W 2.20-4.7M E24	2p	1p	8T97N	15
COMPRESSION TRIMMERS		1/2W 2.20-4.7M E12	2p	1p	AY-3-1015	550
3-40pF; 10-80pF; 25-190pF	30p	1W 2.20-10M E12	5p	4p	AY-5-1013	39
		2% Metal Film 100-1M	8p	4p		

100-500pF 45p	400-1250pF 58p	1% 0.5W 510-1M E24 8p	6p	AY-5-2376	82
GAS & SMOKE DETECTORS		100+ price applies to Resistors of each type not mixed values.		DM8123	19
TGS 812 & 813 415p:		Socket 30p		MC1488	9
				MC1489	9

JACKSONS VARIABLE CAPACITORS		DIODES		BRIDGE RECTIFIERS		MC14411	102
OILICON		BA102		(plastic case)		MC14412	152
100/300pF	205	0.2 365pF with slow				MK4027-2	47
		motion Drive				MK4027-3	47

500pF	250p	0.0208/176	350p	AA119	18	1A/50V	20	MM427-3	35
6.1 Ball Drive	 with slow		AAZ15	15	1A/100V	22	MM4027-4	35
4511/DAF	145p	motion drive	410p	BY100	24	1A/200V	25	MM5208D	TB
		motor drive		BY126	12	1A/400V	29	MM8116N	TB

Dial Drive 4103	C804-5pF: 10, 15	BY127	12	1A/600V	34	MR4118-4	209
6:1/36:1	775p	25: 50pF	250p	CRO33	157	2A/50V	35
Drum 54mm	56p	100, 150pF	335p	OA9	50	2A/100V	44
0:1.365pF	325p	'L' 3x310pF	725p	QA47	12	2A/100V	44
						SFF96364E	105

002 2 365pF	395p	00-3x25pF	550p	0A70	12	2A/200V	48	SFC71301	82
RF CHOKES				0A79	15	2A/400V	53	SFS80102	20
1mH 4.7 10 22 33 47 100 200 470				0A81	15	2A/600V	85	TMS2516	95
				0A81	15	4A/100V	72	TMC2716	115

750, 1mH, 2.5, 5, 10	30p each	OA85	15	4A/400V	78	TMS2710	115
43mH, 100	60p each	OA90	8	6A/100V	73	TMS4027	32
		OA91	8	6A/200V	78	TMS4035	25
		OA95	8	6A/400V	85	TMS4039	25

VEROBORD	0.1	0.15	0.1	OA200	9	8Y164	56	TMS4045	72
	(copper clad)		(plain)	OA202	9	VM18	DIL 50	TNS4047	108
2½ x 3¼"	58p	51p	42p	IN914	4			TMS6011	36
2½ x 5"	68p	62p	—	IN916	4			Z80 CPU 1 2.5M	88

3 3/4 x 3 3/4"	88p	—	—	IN4001/2	5	ZEMER	Z80A CPU4M	109
3 3/4 x 5"	77p	86p	65p	IN4003	6	Range: 2V7 to	Z80 CTC	58
2 1/2 x 17"	204p	—	—	IN4004/5	8	39V 400mW	Z80A CTC	72
2 3/4 x 17"	264p	228p	—			8p each	Z80A CTC	72

3 1/4 x 1 1/2"	204p	224p	IN4006/7	7	Range: 3V3 to 33V, 1.3W	280 P10	66
4 3/4 x 1 7/8"	345p	—	IN4148	4	15p each	Z80A P10	72
Pkt. of 36 pins	22p	VQ: Board	IN5404	17			
Pin insertion tool	140p	DIP Board	IS44	20			

LINEAR ICs

Spot face cutter 105p.	Veroblock 324p	IN5401 13	Thyristors	702	75
		IN5402 14	IA/50V 37	709 14 pin	38
VERO WIRING PEN		IN5406 18	IA/100V 42	709C 8 pin	35
Plus Spool 325p		IN5408 20		710	67

1lb bag Anhydrous 196¢ + 35¢ P&P	NOISE	IA/200V	47	733	98
		IA/400V	55	741 8 pin	17
		5A400V	39	747C 14 pin	78
		5A600V	43	7482 2	78

DALO ETCH RESIST PEN + spare tip 78p	25J	180	8A300V	48	748C 8 pin	36
	VARICAPS		8A500V	58	753 8 pin	185
			8A600V	85	810	158
COPPER CLAD BOARDS			12A100V	88	9400CJ	390

Fibre	Single-sided	Double-sided	SRBP	6A102	25	12A100V	42	AY-1-0212	595
Glass	Single-sided	Double-sided	9.5" x 8.5"	BB105B	40	12A300V	59	AY-1-1313A	660
6" x 6"	90p	110p	95p	BB106	40	12A500V	92	AY-1-1320	311
				MVAM2	185	12A800V	120	AY-1-5050	180

6" x 12" 150p	195p	MVAM115	140	BT106	150	AY-1-5051	150
OIL PLUGS (Headers)				BT116	150	AY-1-5721/6	210
14 pin 35p;	16 pin 40p			C106D	38	AY-3-1270	844
21 pin 35p;	23 pin 35p			TIC44	22		

24 pin 85p; 40 pin 295p		TRIACS		TIC45 25		AY-3-1350 795	
Soldercon pins 100 60p; 500 275p.		3A200V 49		2N4444 140		AY-3-8500 395	
DIL SOCKETS		3A400V 50		2N5064 35		AY-3-8910 855	
EDGE						AY-5-1224A 735	

(TEXAS) Low Wire	CONNECTORS:	8A100V	54	DIAC		AY-5-1230	450
Prof. Wrap	(Double type)	8A400V	64	ST2	25	AY-5-1315	590
8pin		8A800V	108	75108	350	AY-5-1317A	630
10p	.1						
25p	.156						

14pin	12p	36p	2x10 way	—	86p	12A100V	60	75150	140	AS-53500	510
16pin	13p	46p	2x15 way	—	99p	12A400V	70	75154	150	AY-53507	410
18pin	16p	52p	2x18 way	115p	120p	12A800V	115	75450	80	AY-53600	1090
20pin	22p	65p	2x22 way	130p	135p	16A100V	110	75454	80	AY-540070	850

22pin	25p	70p	2x25 way	149p	180p	16A400V	105	75451	75	AY-5-8100	73
24pin	30p	78p	2x30 way	170p	—	16A800V	195	75454	224	CA3011	11
28pin	35p	85p	2x36 way	184p	—	25A500V	235	75491	89	CA3012	15
36pin	105p	—	2x42 way	212p	—	25A800V	195	75492	94	CA3014	15

30pin	—	100p	2x40 way	210	—	250000	100	CA3014	15
40pin	40p	100p	2x43 way	232p	—	T28000	120	CA3018	6

AC125	35	BC182L	10	BF180	38	MPF104	36	TIS46	45	2N2224	20	2N4922	85
AC126	25	BC184L	10	BF184	25	MPF105	36	TIS47	45	2N2227	48	2N4922	125
AC127	22	BC187	25	BF185	25	MPF106	40	TIS49	47	2N2230	48	2N5135	21
AC128	9	BC192	9	BF191	11	MPF107	25	TIS88	60	2N2368	21	2N5136	21
AC141	27	BC212L	9	BF196	12	MPSA06	24	TIS90	30	2N2369A	15	2N5138	20
AC142	28	BC213	9	BF197	12	MPSA55	29	UC191	32	2N2476	120	2N5172	25
AC176	25	BC213L	9	BF198	16	MPSA55	29	UC734	50	2N2483	28	2N5179	60
AC178	26	BC214	9	BF199	29	MPSA56	28	ZTK107	11	2N2484	30	2N5180	38
AC188	26	BC214L	10	BF200	40	MPSA56	28	ZTK108	11	2N2492	50	2N5191	70
AC17	60	BC237	14	BF204	24	MPSU06	50	ZTK300	13	2N2505	50	2N5305	20
AC19	60	BC238	15	BF2448	60	MPSU52	65	ZTK300	13	2N2646	48	2N5308	20
AC19	60	BC307B	14	BF2545	30	MPSU55	65	ZTK301	16	2N2784	55	2N5457	32
AC20	53	BC308	16	BF2564	50	MPSU56	60	ZTK302	20	2N2904	24	2N5458	32
AC21	60	BC327	12	BF2568	45	MPU131	45	ZTK303	25	2N2905A	22	2N5459	32
AC22	60	BC328	15	BF257	35	OC26	170	ZTK304	17	2N2906	22	2N5485	35
AC28	60	BC337	12	BF258	35	OC28	120	ZTK314	24	2N2907	22	2N5777	45
AC29	30	BC338	12	BF259	35	OC36	130	ZTK341	28	2N2908A	22	2N6388	128
AC41	60	BC44	30	BF274	42	OC36	130	ZTK500	15	2N3011	24	2N6109	50
AD149	75	BC461	30	BF451	35	OC41	125	ZTK501	15	2N3020	33	2N5879	140
AD161	42	BC477	35	BF436	35	OC42	48	ZTK502	17	2N3053	19	2SD234	50
AD162	42	BC516	38	BF337	32	OC43	55	ZTK503	15	2N3054	85	3N128	112
AF114	75	BC517	35	BF694	40	OC44	55	ZTK504	25	2N3058	48	3N140	112
AF115	60	BC547	10	BF546	35	OC45	55	ZTK504	25	2N3108	32		
AF116	75	BC548	10	BF593	25	OC70	40	ZTK550	25	2N3252	38		
AF117	95	BC549C	15	BF440	25	OC71	35	40311	60	2N3302	26		
AF118	95	BC556	15	BF441	24	OC72	40	40313	125	2N3441	140		
AF139	40	BC557	10	BF479	24	OC74	50	40315	68	2N3442	140		
AF178	75	BC558	15	BF480	24	OC75	45	40316	85	2N3653	14		
AF186	50	BC559	15	BF481	24	OC76	36	40317	65	2N3702	10		
AS221	60	BC590	80	BF489	65	OC77	75	40320	70	2N3703	10		
BC107	10	BCY35	50	BFX81	45	OC82	50	40324	91	2N3704	10		
BC107B	12	BCY39	78	BFX84	26	OC83	48	40326	52	2N3705	10		
BC108	10	BCY40	48	BFX85	28	OC84	45	40327	62	2N3706	10		
BC108B	12	BCY42	14	BFX86	28	OC140	110	40347	80	2N3707	10		
BC108C	12	BCY45	50	BFX87	28	OC170	85	40348	106	2N3			

**Telephone
orders now
accepted
(£10 min.)**

CA3019	70	MC1312PQ	195	TBA820	70	7442	71	74157	75	1121	195	LS91	125
CA3020	188	MC1458	45	TBA820Q	280	7443	120	74359	185	1123	340	LS92	75
CA3022	70	MC1495	350	TBA950Q	220	7444	116	74160	99			LS93	75
CA3028A	80	MC1498L	92	TCA2700Q	270	7445	116	74161	99			LS95	115
CA3035	235	MC1596	226	CA3965	120	7446	132	74162	99			LS96	180
CA3036	115	MC3302	150	TD1004	290	7447	98	74163	99	74500	60	LS107	45
CA3043	175	MC3340P	120	TD1008	310	7448	99	74164	120	504	73	LS109	75
CA3045	365	MC3360P	120	TD1022	575	7449	120	74165	120	S132	380	LS110	60
CA3046	71	MC3401	135	TD1024	1050	7451	20	74166	155	S130	360	LS113	65
CA3048	124	MC3403	135	TD1090	290	7453	20	74167	240	S138	250	LS114	45
CA3059	175	MC3405	150	TD2020Q	320	7454	20	74170	230	S158	524	LS122	70
CA3075	213	MEM780	205	TD2030	300	7460	20	74172	420	S188	210	LS123	95
CA3078A	63	MC6040	97	TD061CP	54	7470	41	74173	120	S159	180	LS124	180
CA3081	190	MK50398	635	TD062CP	125	7473	40	74175	82	S195	795	LS126	60
CA3082	190	MC55303	125	TD063CP	125	7474	31	74176	105	S194	195	LS127	60
CA3089E	215	MM5507	1275	TL75	45	7475	40	74178	90	S241	195	LS132	95
CA3090AQ	375	MM57160	620	TL702CP	90	7475	56	74177	90	S262	895	LS136	65
CA3123E	150	MM555	890	TL704CN	140	7476	41	74178	149	S287	325	LS138	70
CA3130	90	NE51	80	TL081CP	42	7480	55	74179	155	S408	90	LS139	90
CA3140	48	NE515	10	TL082CP	96	7481	120	74180	90	S472	325	LS140	110
CA3160	95	NE518	10	TL083CP	96	7482	120	74181	280	S470	115	LS147	210
ICL706	795	NE544	185	LO8ACN	120	7483	94	74182	85	S475	825	LS148	175
ICL7107	975	NE555	22	UAA170	150	7484	113	74184	145			LS151	95
ICL8038CC	340	NE556	55	UAA180	150	7485	121	74185	145			LS153	85
ICL8211A	150	NE560	325	XR2266	750	7486	33	74188	299	LS00	13	LS155	95
ICM7205	1150	NE561	395	ZN414	95	7489	215	74190	135	LS01	13	LS156	85
ICM7215	1050	NE528	410	ZN423	185	7489	87	74191	135	LS02	15	LS157	75
ICM7216AJ	1950	NE564	135	ZN424	135	7490	85	74192	135	LS03	15	LS158	85
ICM7217A	1950	NE565A	120	ZN425	415	7492	59	74193	135	LS04	20	LS160	120
ICM7217C	1950	NE566	160	ZN1034E	200	7493	59	74194	105	LS05	23	LS161	95
ICM7217A	790	NE567V	170	ZN1040E	685	7494	95	74195	198	LS08	23	LS162	110
ICM7224	785	NE570	375			7495	75	74196	120	LS09	23	LS163	100
ICM7227A	885	NE571	420			7496	95	74197	90	LS10	20	LS164	110
ICM7555	89	RC4136D											

ETI SEPTEMBER 1981

ETI NEXT MONTH

October issue on sale September 6th - Don't miss out order your copy today.

FM Radio Control

In the course of the past year you've seen all the others produce radio control projects. You've also seen them make a right mess of the idea!

Next month ETI presents the definitive FM, easy-to-build, every-home-should-have-one, radio control. We won't spin it out over 10000 issues either, our circuit is sufficiently refined for us to be able to present full details in one issue!

If you're at all intrigued by controlling things at a distance ETI October is *the* place to be.

Fuzz Sustain

Brilliantly innovative project to please all of the guitarists, all of the time. This nifty little box can provide a really rich fuzz sound and/or a *true* sustain. We stress the 'true' because there have been some attempts to pass off things which are decidedly second-rate before now. As usual ETI gets it right! Inexpensive, ingenious and simply magnificent are words which could well apply to this our latest musicians project!

Don't miss it lest your plectrum gets lonely!

Circuits Circuits And More Circuits

Spot Designs is our new 'tried and tested' circuits features. All the ideas presented have been built and proven — so it is not surprising that this is already a popular new addition to ETI. Next month we're presenting six pages of this top-class ideas material, in response to the many requests to increase the size of the feature.

This is a 'special' one-time only offer so don't get left out circuitless!

Universal Cassette Interface

Into micros? Then ETI has something a little bit special for you next month — a tape interface with switchable baud rate and flexible I/O. It can be run with any system and any tape machine (within reason) and offers all the benefits of being able to save programs on tape at a ridiculous price! Miss this and your fingers will undoubtedly drop off typing!

Einstein Relatives

Yep. The feature you said we would *never* do. A clear easily understood explanation of the Special Theory of Relativity. This is the topic that those smug little physicists are always telling us humans we can never hope to comprehend. Well we can. Just read ETI next month and see for yourself.

Also Appearing

Taking part in next month's production we also have: a Bench Amp for the experimenter; a review for the HP-41C alpha-numeric calculator; an audio signal generator; a flash trigger for quick-off-the-mark photographers plus, of course, all our usual brilliant regulars. It's got to be worth the mere 60p we ask in exchange!

Articles mentioned herein are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

HEAD AMPLIFIER DESIGN

If you've taken the plunge into moving coil cartridges and you're looking around for a head amplifier, Andy Sykes of Videotone explains how you can design your own.



For those of you not yet smitten by the all consuming Hi-Fi bug, a 'Head Amplifier' is not the latest tool for psychologists. The term is borrowed from the telecommunications industry where a preamplifier sited at the mast head is sometimes used to boost the received RF signal in areas of poor signal strength.

Over the past five years there has been a tremendous upsurge of interest in new methods of extracting the musical information from the depths of the record groove. Along with this has come a re-appraisal of the relative merits of the moving coil and moving magnet pickup cartridges. Each has a great deal to recommend it and we should start by comparing the two, albeit briefly.

The principle of operation is the same, ie a current is induced in a coil by a (relatively) moving magnetic field. In the moving magnet type it is, as the name suggests, the magnet that moves because it is mounted on the opposite end of the cantilever to the stylus.

Mass Tendencies

This system works well, but the mass of the magnet/stylus assembly has a nasty tendency to resonate within or just above the audio band. With careful design this effect can be minimised, but some colouration of the sound still occurs. Another problem is that the high impedance of the cartridge, due to the high number of turns required to achieve a usable output, also causes matching problems, lending to high fre-

quency losses in the signal lead capacitance.

Despite all this, excellent results are achievable for a moderate cost and it worth noting that the most competitive area for moving magnet cartridges is between £15 and £25.

Role Playing

Recent developments in technology, however, have made possible an effective reversal of the roles of magnet and coil, neatly overcoming the problems just mentioned, as it is now the coil which moves, inside a static magnetic field. (it is only fair to mention at this point that Ortofon have been producing very underrated moving coil cartridges for many years and are generally considered to be the pioneers of the field). The coil can be made very light, reducing the resonance problem and the output impedance is low due to the small number of turns used, which cures the lead losses.

All is not quite sweetness and light, however, as the system brings its own set of problems, which can be summarised as:

1. Low output — 150uV nominal
2. Very low source impedance
3. Expensive to manufacture

These problems can be overcome at a price, however, and if it is perfection for which you strive, the moving coil cartridge can be considered the best method of transferring data from the record to your ears at present. It is interesting to note that most of the current batch of professional Hi-Fi reviewers use a moving coil cartridge against which others are judged. ➔

Coming Up in the World

A step up device is required to match the low output impedance of the cartridge and to raise its meagre output to a point comparable with the universal moving magnet input or amplifier at approximately 5 mV. One way to achieve this is by the use of a matching transformer similar to those used with low impedance microphones. This solution, however, brings in problems such as secondary load matching, third harmonic distortion, frequency response limitations and hum pickup, all of which require careful and thus expensive design to overcome successfully. An active amplifier is a more cost effective (the watchword of the eighties) solution and has the added advantage of being within the design capabilities of the home constructor.

Design Criteria

The criteria to be considered in the design of such a preamplifier are primarily noise, frequency response and distortion.

If we consider a general MC (Moving Coil) cartridge with an output of 150 mV, source impedance of 10 Ω , and frequency response of 20 Hz to 25 kHz, a matching head amp would have to have at least the following characteristics to achieve Hi-Fi standards:

1. Gain x30 for nominal 4.5 mV output into 47k
2. Signal to noise ratio better than 60 dB
3. Distortion less than 0.05%
4. Overload factor better than 40 dB
5. Frequency bandwidth better than 20 Hz to 20 kHz

The input impedance should theoretically be the same as the cartridge source impedance for maximum power transfer, but it has been argued that MC cartridges work best into loads somewhat higher than this, as it reduces the power dissipation in the (cartridge) coil. Manufacturers differ widely in their recommendations for input impedance, but values between 100 Ω and 470 Ω are most commonly quoted. These values are normally determined by audition, but in my experience strict adherence to the recommended value is by no means as important as one is lead to believe, the differences in sound being more likely due to circuit variation than to mismatch. A good general purpose design *should*, therefore, be suitable for all MC cartridges.

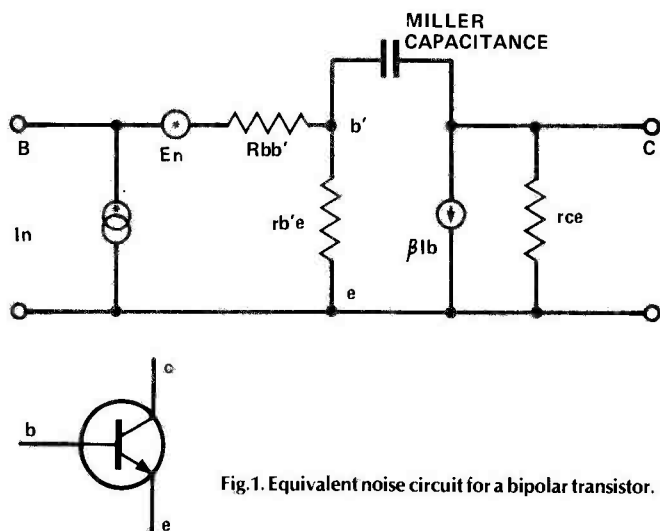


Fig.1. Equivalent noise circuit for a bipolar transistor.

Noise Model

Noise can be thought of as an additional voltage appearing at the input of an amplifier, the ratio between this voltage and the input signal voltage being the measured signal to noise ratio. It is assumed in this model that all noise introduced by the amplifier is added to this input noise voltage and that subsequent amplification of both signal and noise takes place equally and noiselessly. If we wish to achieve a signal to noise ratio of better than 60 dB, this implies an equivalent input noise voltage of around 150 nV. As a comparison, a moving magnet input stage with a signal to noise ratio of 80 dB would have an input noise level of 450 nV and only the very best amplifiers ever achieve anything like this kind of noise figure.

There are three main sources of noise in a transistor amplifier; thermal noise, flicker noise and shot noise. The first two are common to all electronic components, both active and passive, whereas the last is produced in active devices only. Without getting too bogged down in semiconductor physics, shot noise is caused by random fluctuations in the diffusion of minority carriers at the base/emitter junction of the transistor and also by recombination effects within the base region.

Suffice it to say that this type of noise is proportional to the emitter current flowing through the transistor (or diode) and is broadband. Flicker noise is present in semiconductors, resistors and thin metal films, and is produced by skin effects in the surface of the conducting regions of the device. The noise level depends upon the material, but is typically proportional to I^2/f , where I is the current flowing, and is thus often called $1/f$ noise. Thermal noise is, as the name suggests, produced by thermal agitation within the component material and is again broadband in character and proportional to the temperature of the device. The level of noise can be calculated from the equation

$$e^2 = 4KTBR$$

where e = generated noise voltage
 K = Boltzman's constant
 B = frequency bandwidth over which to noise is measured
 T = temperature in degrees Kelvin
 R = the resistance value

Armed with this knowledge, the potential noise generated by any component used in our proposed head amp can be measured and steps taken to reduce its contribution to the total noise produced by the circuit.

In general there are four ground rules which should be followed to help achieve good performance.

1. Choose low noise components
2. Pay careful attention to transistor biasing arrangements
3. Keep resistor values as low as possible
4. Pay careful attention to avoid the pickup of external noise sources

Couldn't be simpler could it?

Low noise types of resistors are metal oxide, close tolerance metal glaze, or thick film. Avoid the use of large electrolytics as the (inevitable) leakage currents generate noise. Tantalum or polycarbonate types are best for the higher capacitance values and polystyrene or silver mica the best cost/size/noise level compromise for lower values. PTFE is the best of all, however, but tends to be on the expensive side. The noise levels produced by transistors are normally obtained from the manufacturer's data and there are several factors to be considered.

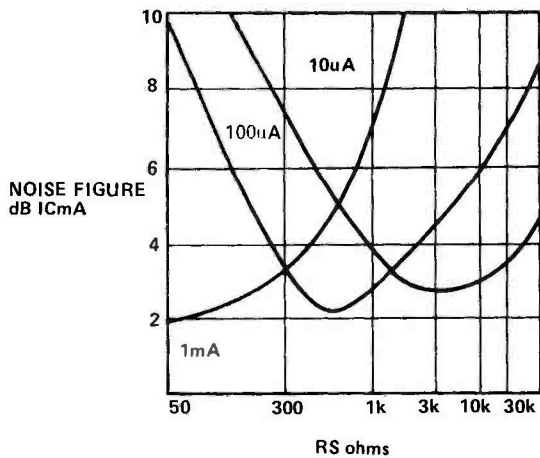


Fig.2. Noise curves for the BC413.

Equivalent Thinking

If we refer to the equivalent circuit for a transistor in common emitter configuration shown in Fig.1, and then consider the various noise sources contained within this circuit, a mathematical expression for the total noise generated can be derived. The exact form of this equation requires far too much deep thought for us to deal with it in detail here, but note that both noise voltage and noise current terms would be involved. It is also immaterial because transistor manufacturers are kind enough to measure it for us and provide noise versus frequency, and noise versus source resistance plots which take the general form shown in Fig.2.

The overall noise level is dependent upon the collector current flowing and for the lowest noise there is an optimum source resistance.

For use in our head amplifier this should ideally be the same as the source impedance of a moving coil cartridge, about 10R, but due to the need to optimise other parameters it is more likely to be between 1k and 10k for a typical audio low noise transistor. This is because the vast majority of uses for these devices involve higher source impedances, ie 47k and the manufacturers do not see sufficient market to justify the production of a special low noise, low source resistance type, except, that is, for the ever-industrious Japanese.

A Nipponese semiconductor firm recently introduced the answer to the head amp designers dreams with a range of low noise transistors with optimum source resistances as low as 2R!

This ability to cobble up a special device to order, where no standard model is adequate, is one reason why the Japanese rule the audio kingdom.

Phenomenal

All is not yet lost, however, as there are two phenomena which may be used to advantage when designing a low noise amplifier with standard components. The first is that some medium power transistors exhibit better noise figures when driven from a low source resistance than normal low noise, low level types. This is mainly due to the need to keep r_{bb} low (see Fig.1) in order to obtain good h_{fe} figures when operating at relatively high collector currents (values between 1mA and 10mA are common), which tends to rule out battery operation.

This brings the additional problem of the mains supply, of which more later. Suitable transistors for this type of use are 2N4405 or BC361, both of which have been successfully used in commercial designs.

The second possible answer is the use of a parallel transistor stage. This is where several transistors are wired in parallel, obvious really isn't it? The main advantage of which lies in the fact that in common emitter mode the base/emitter junctions are in parallel and thus the noise currents and voltages produced by each transistor are summed together, see Fig.3. The basic rule for Communications Engineers considering the noise levels of their systems is that noise signals from several separate sources, feeding into a common input, add by power.

Therefore, the total noise voltage for our parallel stage will be given by the equation $E_{nt} = E_n/N$ where N is the number of transistors. Similarly the total noise current will be given by $I_{nt} = NI_n$. Now the best noise source resistance for a transistor is given by $R_o = E_n/I_n$ and so for our parallel stage this is $R_{ot} = E_{nt}/I_{nt} = R_o/N$. R_{ot} is thus dependent upon the number of transistors used in parallel, the greater the number used the lower the best source resistance becomes.

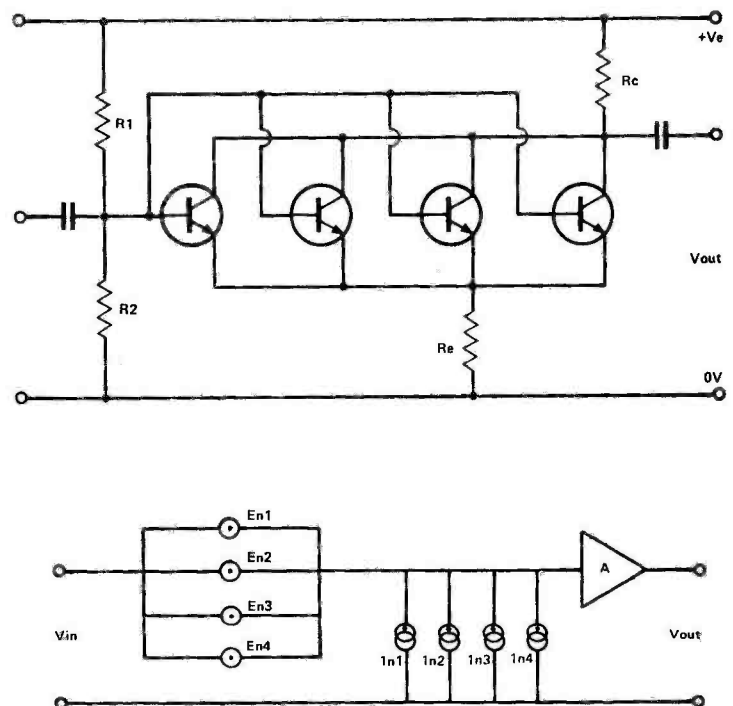


Fig.3. Noise model of parallel stage.

Let us now consider a typical low noise transistor with a best source resistance of 2k to be used with an MC of source impedance 10R. The number of parallel transistors required for the best match is given by $2000/10 = 200$. This is clearly impractical for reasons of cost, the physical space required and, more important, the high value of Miller capacitance that would result. As can be seen from Fig.1, the Miller capacitance introduces feedback between the collector and base of the transistor and is the factor which limits the high frequency response. It would be a major problem if this many transistors were used. In practice eight transistors seems to be the best compromise and is the number most commonly used. Even so it is important to choose a transistor with both a low best source resistance and a good F_t if good results are to be obtained. The F_t of a transistor is the frequency at which the gain becomes unity and should be in the region of 200 MHz. Suitable types for this type of use are BC413, BC415, BC337, 2N4148.

Circuit Options

So much for the theory, we come now to consider the options open to us, in terms of the circuit configurations, which may achieve the required specifications for our Head Amplifier. Something to remember here is that any biasing components used will also add to the noise. Take a standard common emitter circuit, for example, with feedback to counteract thermal changes as shown in Fig.4. The noise voltages produced by R1, R2 and R3 all contribute to the overall noise of the stage. The base bias resistors are particularly important as their noise voltages are effectively in parallel with the input signal and will be amplified by such. The contributions of these biasing components can be reduced by decoupling as shown in Fig.5. The biasing under DC conditions remains the same, but the equivalent noise circuit is as shown.

Note that only the noise associated with R3 will contribute to the input noise and this may be made low in value reducing the thermal noise from this component.

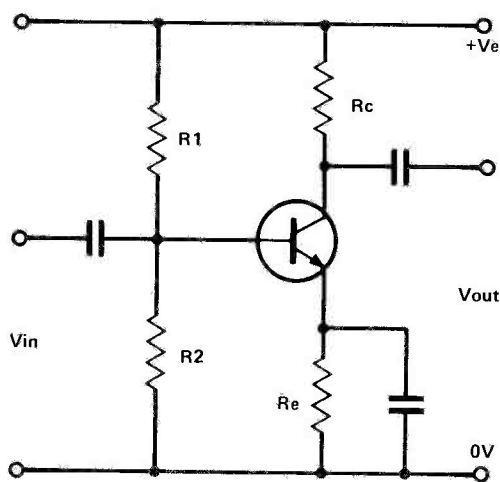


Fig. 4. A standard common emitter circuit.

These examples serve to illustrate the principle because a single stage circuit is unsuitable for use as a high quality Head Amp. The main reasons for this are the variations in gain due to the spread of H_{fe} values in any transistor type and the relatively high values of distortion which are produced. Some form of feedback is required to stabilise and reduce both these parameters and, in general, at least a two stage circuit must be used to produce an acceptable performance.

Controversial Distortion

There is no "best" circuit but there are, as always, some points to bear in mind. In order to reduce the distortion to an acceptably low level, a fair amount of feedback is required and care should be taken to avoid Transient Intermodulation Distortion (TID). This particular form of distortion has proved to be somewhat difficult to define rigorously and there is not an inconsiderable amount of controversy as to exactly what it is and how to avoid it.

Nevertheless it is generally accepted that TID is reduced by ensuring that any amplification stage has a greater gain bandwidth than the stage preceding it. TID also depends on the amount of overall feedback applied around the circuit and careful design of each individual stage to control the amount of harmonic distortion produced will reduce the amount of overall feedback required and hence reduce the circuit susceptibility to TID.

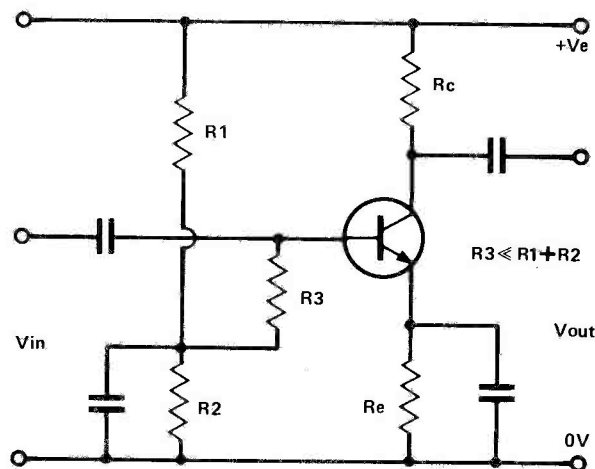


Fig. 5. Low noise base bias circuit.

Breakthrough

The frequency response of the design is also important for two reasons. Apart from the obvious need to keep it wide enough to encompass the whole audio band (traditionally 20 Hz to 20 kHz), it also plays a part in the circuit's susceptibility to Radio Breakthrough. This is a problem because of the high sensitivity of the front end coupled as it is to what is in effect a tuned circuit made up of the cartridge inductance and the input capacitance. My extensive, but completely unintentional, researches into this subject have shown that the two most popular sources of RF interference are Radio 4 at 200 kHz and the local Police/Fire/Ambulance/Taxi Services at anything between 90 and 120 MHz, though the latter is normally only a problem if the offending transmitter is passing close to your Hi-Fi. So, don't put your new moving coil set-up in the front room, folks, if you live on a busy road. The installation of a Mu metal garden gate and front door might also help (for explanation of Mu metal see Hums). Another potential source of RF comes from Citizen's Band transmitters on 27 MHz. But as we all know these are illegal in this country and so nobody really uses them, they just install them in their cars for show.

The offending RF signal is normally received by the first stage acting as a simple diode detector and can be tackled by careful attention to earthing and by the provision of RF filters in the input and supply lines. The input loading capacitor provides good RF decoupling only if a type with good high frequency characteristics is used. Ferrite beads on the input connecting leads can also be used to increase their inductance.

Breakthrough occurring from supply line pickup requires further decoupling to eliminate it. Large electrolytics have a substantial impedance at high frequencies and so should be shunted by a capacitor with better characteristics. A 100n ceramic is suitable here and a small inductor in the supply line is also good practice.

Passing the Buck

Another method of avoiding breakthrough is to make the bandwidth of the head amp wide enough to include any potentially troublesome frequencies. A bandwidth of, say 10 MHz, would include most national AM stations and any signal picked up would simply be amplified without being detected and passed into the main amplifier. This is known as "passing the buck" in the trade and relies upon the better RF rejections characteristics of the RIAA equalisation stage.

And so to Details

A typical two stage amplifier is shown in Figs. 6 and 7. These are of the common emitter/emitter follower and common emitter/common emitter types respectively and serve as good examples of typical designs. Both circuits are direct coupled and have overall negative feedback to set the required gain and reduce distortion.

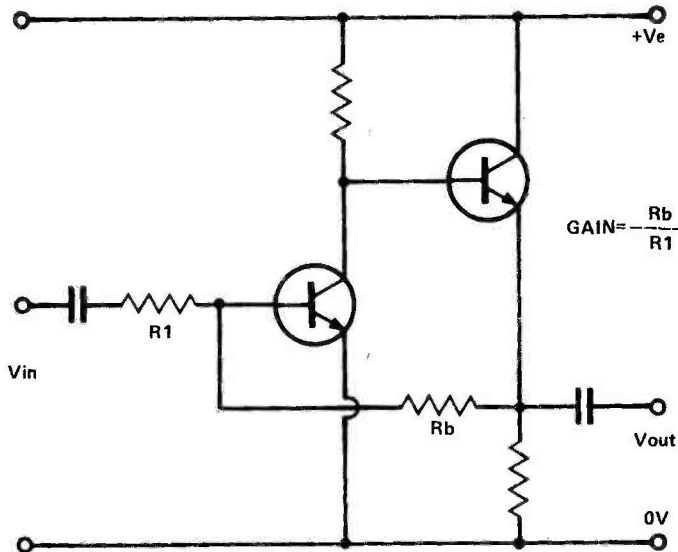


Fig. 6. Common emitter/emitter follower amplifier configuration.

The effect of temperature on biasing is also minimised and note that the low noise method of biasing is used in Fig. 7. To reduce noise to a minimum the feedback components should be kept as low in value as possible, preferably around the 1-10R mark, though this is only practicable in the latter circuit as R1 in Fig. 6 is also the input impedance presented to the cartridge and thus should be somewhere near 100R.

This resistor is in series with the base of the first transistor, however, and as this is probably near to the best source resistance for this stage, assuming the use of parallel transistors, can provide a trade-off with the noise contributed by the relatively high values of the feedback components.

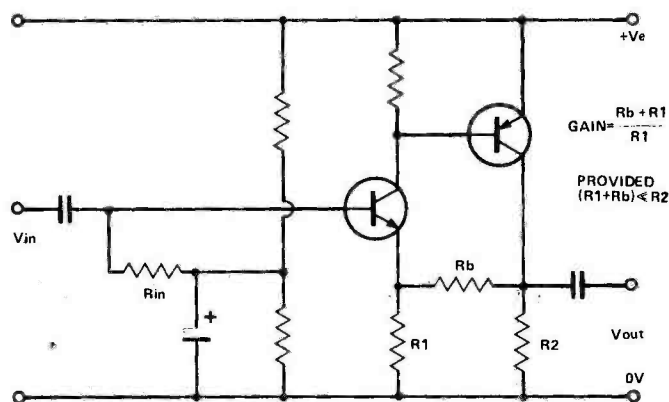


Fig. 7. Common emitter/common emitter amplifier configuration.

When using low feedback resistor values make sure that there is sufficient drive capability in the circuit. A feedback resistance of 10R in Fig. 7, for example, will require a drive of 100 mA for a 1V swing and would, therefore, require the use of a medium power transistor in the second stage.

This component may also contribute its fair share of noise and some degree of experimentation will be required to reach the best compromise.

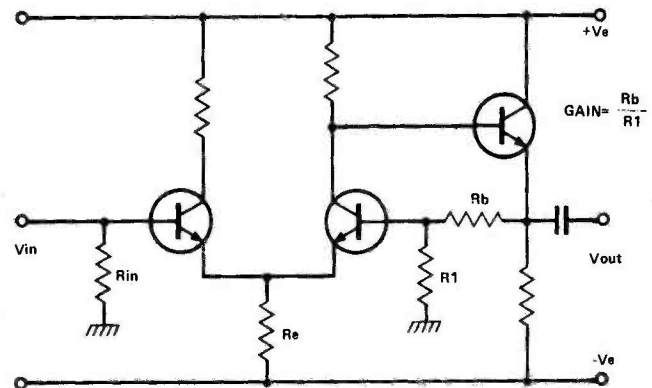


Fig. 8. Differential input circuit.

Redundant Capacitor

A differential input stage as shown in Fig. 8 may be used to great effect. The input is referenced to signal earth, eliminating the need for an input capacitor. The resistance to supply-borne interference and hum is also greater with this kind of configuration and can be further improved by replacing Re with a constant current generator.

This is just as well because the need for a differential supply makes battery operation expensive and somewhat impractical.

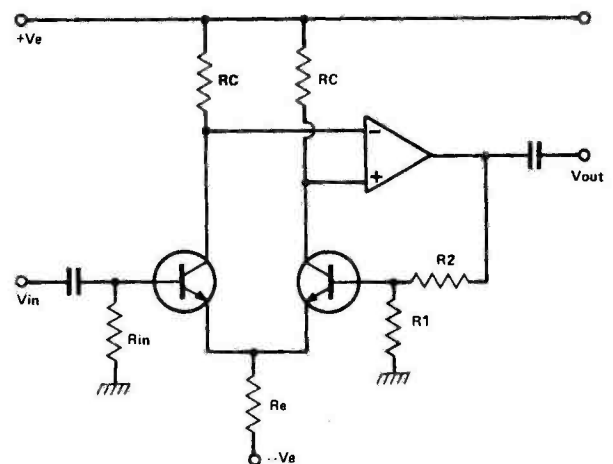


Fig. 9. Differential input with op amp.



A second gain stage may be added to increase the amount of feedback applied and so reduce distortion. This may be another differential stage or even an operational amplifier (Fig. 9).

This latter option may suffer a noise penalty due to the inherent noise output of the op amp but there are some good low noise types now available, such as the TDA1034N and TL071.

Next month we bring Andy Sykes' dissertation to a close with Part 2 of all you need to know about head amplifier design.

ETI


Simply ahead...

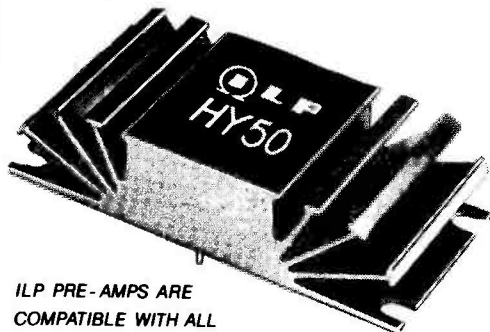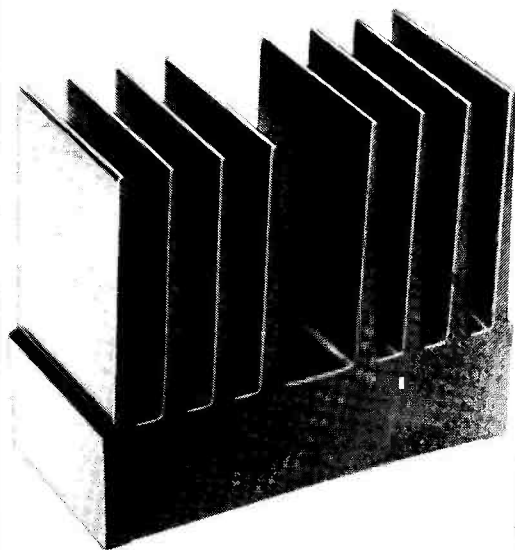

ILP PRE-AMPS ARE
COMPATIBLE WITH ALL
ILP POWER AMPS AND PSUs

POWER AMPLIFIERS

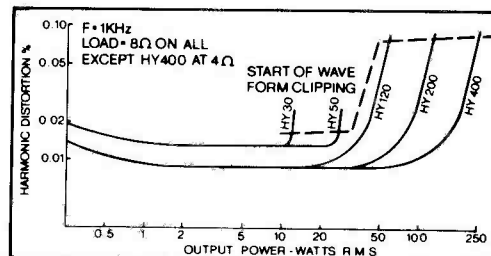ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pickups, tuners, etc. using digital or analogue sound sources.



Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	100dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	100 dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100 dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100 dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100 dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4 Ω - ∞

Input sensitivity - all models 500 mV

Input impedance - all models 100K Ω

Frequency response - all models 10Hz - 45KHz -3dB

POWER SUPPLY UNITS



ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and are in two basic forms — one with circuit panel mounted on conventionally styled laminated transformer, for PSU 30 and 36 — in the other, for larger PSUs, ILP toroidal transformers are used which are half the size and weight of laminated equivalents, are more efficient and have greatly reduced radiation.

PSU 30 \pm 15V at 100mA to drive up to 12xHY6 or 6xHY66 **£4.50 + £0.68 VAT**

THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS

PSU 36 for 1 or 2 HY30s **£8.10 + £1.22 VAT**

PSU 50 with toroidal transformer for 1 and 2 HY50s **£9.75 + £1.46 VAT**

PSU 60 with toroidal transformer for 1 HY120 **£9.75 + £1.46 VAT**

PSU 70 with toroidal transformer for 1 or 2 HY120s **£13.61 + £2.04 VAT**




PSU 90 with toroidal transformer for 1 HY200 **£13.61 + £2.04 VAT**

PSU 180 with toroidal transformer for 1 HY400 or 2xHY200 **£23.02 + £3.45 VAT**



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.


this time with two new pre-amps

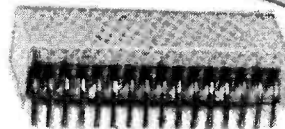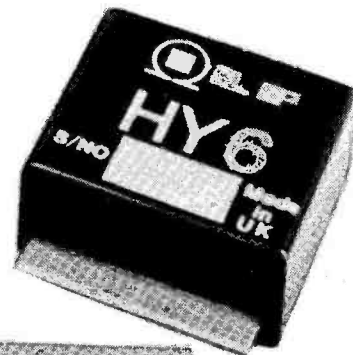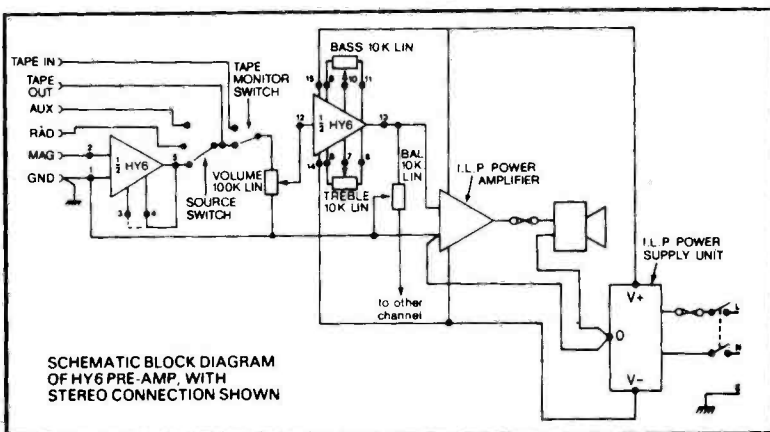

HY6 mono HY66 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers – HY6 for mono operation, HY66 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

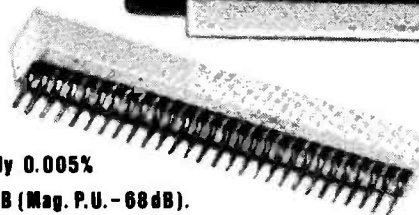Sizes – HY6 – 45 x 20 x 40 mm HY66 90 x 20 x 40 mm Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity – Mag. PU – 3mV; Mic – selectable 1–12mV All others 100mV Tape O/P – 100mV Main O/P – 500mV; Frequency response – D.C. to 100KHz – 3dB.



HY6 mono
£5.60
+ VAT 84p

HY66 stereo
£10.60
+ VAT 1.59

Connectors included

B6 Mounting Board
78p + 12p VAT

B66 Mounting Board
99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90dB (Mag. P.U. – 68dB).
- HIGH OVERLOAD FACTOR – 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 V to ± 50 V.

NO QUIBBLE
5 YEAR GUARANTEE
7 DAY DESPATCH ON
ALL ORDERS
BRITISH DESIGN AND
MANUFACTURE
FREEPOST SERVICE
see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope – we pay postage on all letters sent to us by readers of this journal.



ELECTRONICS LTD.

FREEPOST 4 Graham Bell House, Roper Close,
Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 Telex 965780

Please supply
..... Total purchase price £
I enclose Cheque ☐ Postal Orders ☐ International Money Order ☐
Please debit my Access/Barclaycard Account No.
NAME
ADDRESS
Signature

NEW CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

* EASY TO BUILD * 5 PUSH BUTTON TUNING * MODERN STYLING DESIGN * ALL NEW UNUSED COMPONENTS * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B. * INCORPORATES SUPPRESSION CIRCUITS



£10.50 p&p £1.75

The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue.

The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia.

The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

CONSTRUCTORS PACK 7A
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

£1.95 Per Pack, p & p £1.00.
Pack 7A may only be purchased at the same time as Pack 7.

NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

A FEATURED PROJECT IN PRACTICAL ELECTRONICS

R T V C

323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.
21 E HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm
Closed Thursday

NEW 12+12

AMPLIFIER KIT

An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free Size 9 1/4" x 8 1/4" x 4" approx. with kit. **£13.95** p&p £2.55

TWO WAY SPEAKER KIT To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/4" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65.

Available only to first time purchasers of the 12 + 12 kit.

50WATT MONO DISCO AMP

£30.60
p&p £3.20

Size approx 13 1/4" x 5 1/4" x 8 1/4"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

NOW AVAILABLE

30 + 30 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/4" x 3 1/4" x 10" approx. **£32.90** p&p £3.30

Mullard AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK

SEE OUR PRICES

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £5.00** p&p £1.10

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **illus. OUR PRICE £7.65** p&p £1.15

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/4" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p £1.70 **£4.05**

R T V C

323 EDGWARE ROAD, LONDON W2
21 E HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers.
ALL PRICES INCLUDE VAT AT 15%.
All items subject to availability. Price correct at 8/7/80 and subject to change without notice.
All enquires Stamped Addressed Envelope.
NOTE: Persons under 16 years not served without parent's authorisation.

£76.00 p&p £4.00
100 WATT MONO DISCO AMP

Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx woofer with rolled surround. 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance.

£18.25
Per stereo pair p&p £4.20

BSR P200

Belt drive chassis turntable unit, semi-automatic, cueing device. p&p £3.00
Shure M75 6 Magnetic Cartridge to suit. **£7.95**



BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **OUR PRICE £12.25** p&p £2.75

PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. **UNBEATABLE OFFER AT BUYER COLLECT ONLY.**

BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00. **OUR PRICE £11.95** p&p £2.50

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

CURRENT AFFAIRS

We seem to take for granted that circuits work, but why is it that conductors, semi-conductors and insulators do just what their names imply? A.S. Lipson takes us step by step through the whys and wherefores of atomic structure.

Most of us are reasonably familiar with what electricity is — the movement of electrons through a conductor. But there are some things that we tend to take for granted. For instance, why is it that some materials, like metals, conduct easily, whereas others — insulators — don't, and still others — semiconductors — seem to be somewhere in the middle; conducting, but not as well as metals? In order to find out why, we'll first have to learn something about atomic structure.

First Theory

Essentially, the atom consists of a central, very small positively-charged lump called the nucleus, surrounded by negatively charged electrons. Many books — particularly old ones — tend to give the impression that the electrons are just like little planets orbiting a sun (the nucleus) and that the atom is like a miniature solar system. This is *wrong*. Electrons do not behave just like little billiard balls, or little solid lumps. It is in fact more accurate (although not quite so simple) to visualise the electrons in an atom as being spread out 'charge clouds' around the nucleus, with most of this charge being concentrated at specific distances from the nucleus. The comparison between the two points of view is made in Fig.1.

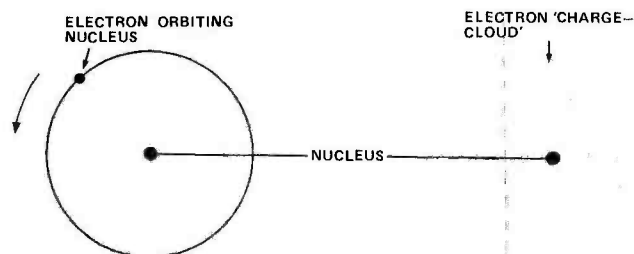


Fig.1. A hydrogen atom according to (a) The 'Solar System' model (b) The 'Charge Cloud' model.

The electrons within an atom can have different energies. If they obtain more than a specified amount of energy (for any particular type of atom), then they can actually break free from the atom. It is clear that the more energy a particular electron has within an atom, the less energy that electron will need to have added to it in order for it to break away from the atom; in other words, the easier it will be for that electron to escape.

Conduction and Insulation

But what has all this to do with conduction of electricity? In metals, some of the outer electrons present have quite high energies within their atoms and, in a solid lump of metal, one or two electrons from each atom are more or less free of their own atoms, although they are held into the metal as a whole. The positively charged ions left when electrons are removed from atoms are packed closely together and, in between them, the free electrons move about at random, (acting as a sort of 'atomic glue'). This negative charge attracts the remaining positive charge on the ions, and holds the whole thing together. (See Fig. 2.) The charge-clouds of all the free electrons join together, and form what is often known as an 'electron sea'. Because of this structure — the way that they are held together — metals can conduct electricity. Why?

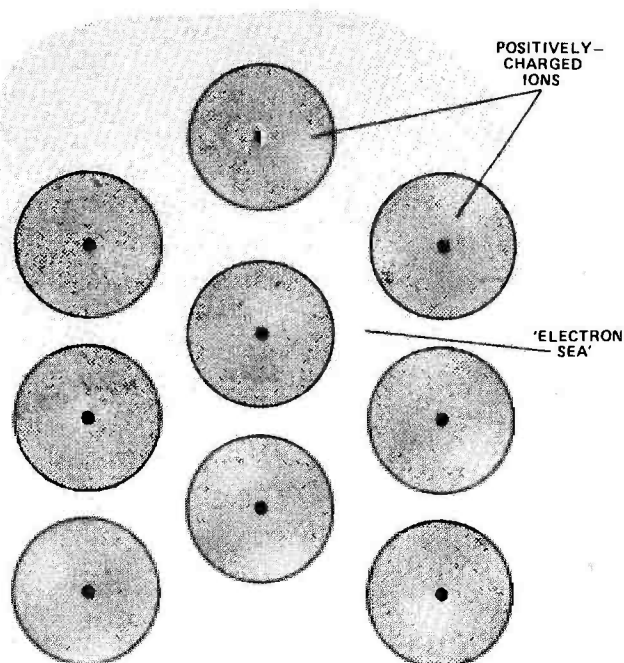


Fig.2. The structure of a metal. Positively charged ions are surrounded by an electron 'Charge Cloud'.

Because of all those free electrons, which aren't held by any particular atom, only by the metal as a whole. They are so loosely attached that if you apply a potential difference across the metal, they can drift along under its influence, and so cause a current to flow. In insulators, on the other hand, the electrons are held much more tightly by the atoms, there is no 'electron sea', and the atoms are bonded together by other means. Consequently, if a potential difference is applied, the electrons are unable to break free from their atoms, and so no current can flow. Our problem is thus solved — we now know how electrical current is conducted in metals, and why it isn't in insulators. Or do we? This theory was widely accepted for some time, and in fact it's still accepted as being broadly true, but there are just one or two things it doesn't explain. Semiconductors, for instance? And why should metals hold their electrons less tightly than non-metals? Our theory is obviously incomplete.

The New Approach

It was the physicists (naturally...) to the rescue. So we must once again return to the atom.

In the first decades of this century, a startling new branch of physics — Quantum Mechanics — made its debut. This was the work of several men, including Einstein, Heisenberg and Schrodinger. One of the first results Quantum Mechanics produced was embodied in a conclusion that Niels Bohr published in 1913. This was that, contrary to what had previously been assumed, the electrons within an atom could not have just any energy level, but could only exist at certain set energy levels. (See Fig. 3a.) This was a radical departure from what had been believed up until then, but it has been proved and is now unquestioned by physicists.

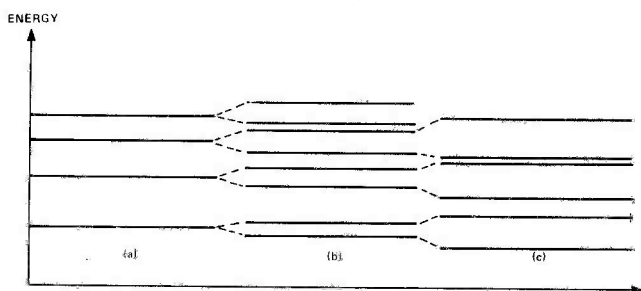


Fig.3a. The electrons within atoms can exist only at set levels. b) When two atoms interact with each other, their energy levels are split. c) In a solid, millions of atoms all interact with each other, and the energy levels are split into so many 'sub-levels' that they behave like continuous bands.


So electrons in atoms can only exist at certain set energy levels. But if you get more than one atom together, the situation changes again — energy levels are split. If, for example, you put two atoms close together, and then look at what has happened to a particular energy level in each atom, you will find that, in one atom, it has shifted up fractionally, in the other atom, it has shifted down slightly. The two atoms act as though the single energy level has been split into two (See Fig. 3b), one very slightly higher than the other. In a solid, where there are millions of atoms all together, the energy levels are split into so many 'sub-levels', all very close in energy, that they act like continuous bands. (Fig. 3c.) In a solid, instead of

there being several separate energy levels at which the electrons can exist there are, instead, several energy 'bands', within which electrons can have a whole range of energy levels. Between these bands however — and this is the important bit — there are still 'forbidden gaps'; energy ranges in which electrons cannot exist because there are no allowable energy levels present. So how does all this help us to understand electrical conduction? Patience... We're just coming to that...

Electron Distribution

The way a material behaves electrically, whether it acts as a conductor or an insulator or whatever, depends on the arrangements of its energy bands, and the way that the electrons are distributed within them. The energy bands of a) a conductor, b) an insulator and c) a semiconductor are shown in Fig. 4. Firstly we will deal with the conductor. The energy bands shown in Fig. 4a are fairly typical of a material like copper. As in any material, the lower energy bands tend to fill up with electrons more easily than the higher energy bands, and consequently, they contain all the electrons that they can possibly hold. There is then a 'forbidden gap' of energies, and above this is another band — known as the conduction band. This band, unlike those below it, is not full, but is capable of holding more electrons than it in fact does. An electron in this band is relatively loosely held by this atom and so it requires only a very small amount of energy, which can be obtained from an applied potential difference to raise it to a higher energy *but still within the conduction band*.

It can now drift along within the metal under the influence of the potential difference. Thus, in a metal, which has either a partially-filled conduction band (eg. copper) or an empty conduction band which overlaps a full energy band, (as in magnesium) it is possible for current to flow quite easily. So far, so good. What about insulators? The energy-band theory can also explain the behaviour of non-conducting materials (Fig. 4b). In such substances, there are still full energy bands at the lower energy levels, but the conduction band is empty. In other words in insulators, electrons do not normally exist with enough energy to be in the conduction band. And it is only in this conduction band that electrons are free enough to take part in a flow of electrical current. If it were possible to get the electrons out of the lower energy bands into the conduction band then these materials could conduct electricity, but in order for that to happen electrons would have to cross the forbidden gap, and the energy required to make them do this is much more than can be supplied by a normal potential difference. In terms of eV (the eV, or 'electron-volt', is a measure of energy which atomic physicists find it convenient to work with, 1 eV being the energy picked up by an electron in passing through a potential difference of 1 volt), the forbidden gap in insulators is normally about 5 eV, hence, under normal circumstances, insulators do not carry electricity.

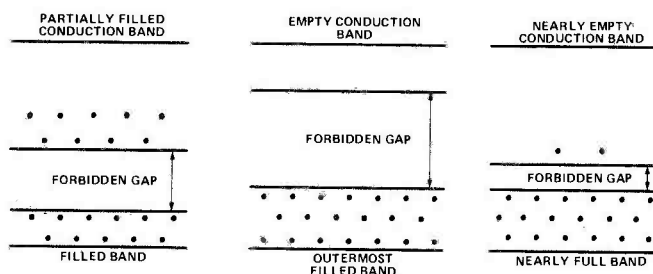

What About Semiconductors?

Semiconductors are really an 'in-between' case. Like insulators, very pure semiconductors such as silicon or germanium have empty conduction bands when the temperature is 'absolute zero' (about minus 273°C), separated from the other energy bands by a forbidden gap. At normal temperatures the conduction bands are not completely empty. Why? Because in semiconductors the forbidden gap is much smaller than in insulators — about 1 eV. It is so much smaller, in fact, that at normal temperatures, the vibration of the atoms in the semiconductor is sufficient to give enough energy to a few electrons to reach the conduction band. Eventually they fall back to the lower energy bands — but more electrons are entering the conduction band all the time, so eventually a balance is struck, with the number of electrons entering the conduction band in any period of time being equal to the number falling back. At normal temperatures, therefore, there are always just a few electrons in the conduction band of a semiconductor, and so it is able to conduct electricity. Though it conducts less well than a metal, since there are far fewer electrons in the conduction band.

But That's Not All.....

There is, however, another means by which a semiconductor can carry electricity. Every time an electron leaves a lower energy band for the conduction band, it leaves an electrically neutral space where there was previously some negative charge. These neutral spaces, surrounded by negatively-charged electrons, can behave almost like a positively charged particle, and when a potential difference is applied, this 'hole' as it is called travels in the opposite direction to that of the electrons. To understand how this happens, imagine a row of chairs, with someone sitting in each of them except the one at the end. (Fig.5) If the first person in the row moves into the empty chair, the next person moves into the chair left empty by the first person, and so on, the 'space' where no one was sitting appears to move in the opposite direction to the people, and that's exactly how it works with 'holes' in semiconductors. While it appears that the hole is moving in one direction, carrying positive charge, what is really happening is that the electrons in the lower energy bands are travelling in the other direction, carrying negative charge, and are moving into the spaces left by electrons which have gone into the conduction band.

Conclusion

Therefore, in a semiconductor, there are two types of charge carriers involved in the conduction of electricity; electrons and 'holes'. Various experiments indicate that in germanium, for example, about one third of all the current is carried by the 'holes'!

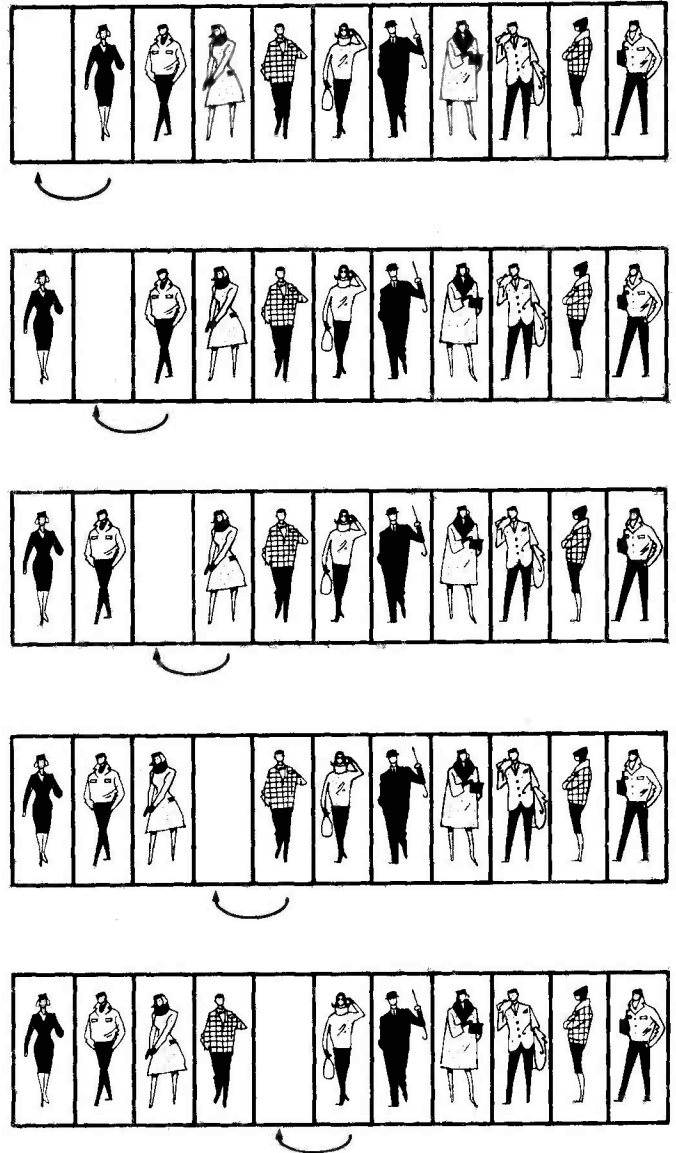



Fig.5. As each person moves into the space next to them, it appears that the gap moves in the other direction. In the conduction band this is an electrically neutral space where there was previously a negative charge. These 'holes' can behave almost like a positively charged particle when a potential difference is applied this 'hole' moves in the opposite direction to the electrons.

Fig. 4. Comparison of the forbidden gap position and magnitude in the three basic types of material. Far left: a conducting substance. The lower energy bands are full of electrons and the forbidden gap is easily bridged by sufficiently energetic electrons which then enter the conduction band. Center: insulators. Note the empty conduction band and the wide forbidden gap in which there are no permissible energy levels. On the right: semiconductor materials in which the energy gap is around 1 eV and at room temperature sufficient energy is imparted by heat action to allow some electrons to cross the gap into the conduction band.

You will remember that, in semiconductors, electrons reach the conduction band because of the vibration of the atoms. This fact is quite important. At higher temperatures the atoms vibrate more, and so more electrons (and 'holes') are available for conduction purposes. To the extent that above about 100°C for germanium, and 150°C for silicon, the conduction is no longer really under control, and so devices like transistors, which use semiconductors, have to be kept below these temperatures, if they are to remain reliable during operation. The fact that silicon is useful as a semiconductor at higher temperatures than germanium, was the major reason for the increased use of silicon rather than germanium devices!

ETI

Complete Audio/Tuner Kits

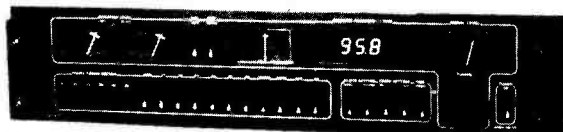

Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules£171.35 inc.

Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching HMOSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit£178.25 inc. Carr. £5.

Preamplifier

More features and facilities, thanks to DC switching and control design.


Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/outs. 2 low pass, 2 high pass active filters, genuine volume related loudness, 10B channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N+, THD -75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

Semiconductors

Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST


CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TD44420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.95	TDA1220	1.61	KB4413	2.24
TBA120S	1.15	TDA1083	2.24	KB4417	2.53
KB4406	0.80	TDA1062	2.24	MC3357P	3.16

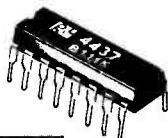

SL1610	1.84	SL1626	2.80
SL1611	1.84	SL1630	1.86
SL1612	1.84	SL1640	2.17
SL1613	2.17	SL1641	2.17
SL1620	2.50	SL6600	4.31
SL1623	2.80	SL6640	3.16
SL1624	3.77	SL6690	3.68
SL1625	2.50	MC1496	1.44

VARIACAP DIODES.....

A section from our PL:			
BA102	0.35	16:1 ratio AM tuning	
BB204	0.41	KV1215 9v triple	2.93
BB105	0.41	KV1211 9v dual	2.01
BB109	0.31	KV1225 25v triple	3.16
MVAM2	1.93	BB212 9v dual	2.25

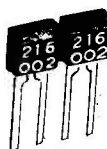

POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).

2SK133 120v N-ch 100W MOSFET £6.33 2SJ48 Pch complement £6.33

2SK135 160v N-ch 100W MOSFET £7.29 2SJ50 Pch complement £7.39

PA101B Kit for 100W MOSFET PA less heatsink £16.10. (£23 inc heatsink/bkt)

ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OKI

KB4445 - 4 channel dig.prop. FM TX IC, 30mW out (amplifiable) -£2.30 inc

KB4446 - 4/5 ch. dig. prop FM RX IC, Suits KB4445 or RCME syst. £2.65.

KB4445/6 pair: £4.75. New 8 page data sheet 35p + SAE. More RC ICs in list

CMOS, LPSNTTL, TTL, MPU:

Listings in the new pricelist.

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

Coming Soon.....

Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here.

SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX. OP. 0.2uV basic sensitivity in HF. Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

CATALOGUES 60p ea. all three for £1.60
PRICES SHOWN HERE INCLUDE VAT
POST/PACKAGE CHARGE NOW 35p

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5. Callers welcome

ambit
INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

Radio/Audio/Communications Modules

LW-MW-SW-SW DC tuned and switched

91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands MW/LW: £15.58 +1SW £16.73

VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output

944378-2
£26.45



Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

Various digital frequency displays

The World's largest range of receiver DFM's is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility - 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



Components

Crystal Filters

Most popular types are available - ex stock, and in quantity.

10.7MHz	25kHz Channel spacing 8pole	£16.67
	12½kHz ..	£17.82
	2.4kHz SSB	£19.78
	Monolithic dual roofing filter	£2.30
34.5MHz	1.3dB loss, 80dB stopband HF first filter in synth. RX	£36.80
RC XTALS	FM pairs (no spilt)	£3.74
	AM pairs	£3.57
USB/LSB	Xtals for 10.7SSB filter	£2.88 ea



Piezo Sounders


The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz) The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)



Keyboard switches and caps

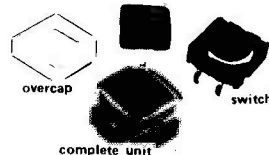From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCM81101 is shown here, with the KT5 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCM81101 : 17p, KT5 : 16p - or 29p/pair



LCD CLOCKS

Clocks use 1.5v at 15uA only.

LCD DVM

DVM 9v/1mA

CM161:	7mm LCD 12/24hr, alarms etc	£11.44 each
CM172:	13mm, 12hr, alarms, timer etc	£14.32 each
CM174:	13mm, 12hr, min/sec stopwatch	£14.32 ea
DVM 176:	ICM7106 based LCD 3½digit	£22.36 each



WHAT'S NEW at AMBIT

NEW PRICELIST/SHORTFORM:-

28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :

£1.50 each - or free with pairs of HMOS and the PA101B

Everything you should know about HMOSFET devices theory and applications.

CWO PLEASE Commercial M/A terms on application. Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt

Parts 1-3 AMBIT catalogues 60p ea, or £1.60 the lot.

'TUSCAN' FROM TRANSAM



Take a step up to your next Computer!

THE CONCEPT

How many ways are there to build an S100 system? Not many, and all expensive. TUSCAN changes all that.

Five S100 boards on one single board—just for starters. Plus five extra slots for future expansion.

What a combination! Z80 and S100 with the TRANSAM total package of system and applications software.

How do we do it? Our prices start at £195 and you can build up in easy stages to a fully CP/M compatible disc based system. Something to think about!

THE HARDWARE

The first Z80 single board computer with integral S100 expansion. British designed to the new IEEE (8 BIT) S100 specification, the TUSCAN offers total system flexibility. A flexibility available now.

The board holds the equivalent of a Z80 cpu card, 8k ram, 8k rom video and I/O cards with 5 spare S100 expansion slots and offers a price/performance ratio which is hard to beat.

Just compare our price with a commercial S100 ten slot motherboard with this specification.

THE SOFTWARE

TUSCAN offers the user the choice of system monitor, editor, resident 8k basic, resident Pascal compiler or full CP/M disk operating system. All options are upwards

compatible and fully supported with applications software. Both 5¼" and 8" drives are supported in double density.

THE PACKAGE

TUSCAN is available in kit form or assembled. With several hardware and software options to suit your requirements and budget. Attractive desk top case also available holds 2 x 5¼" Drives.

TRANSAM

NOBODY DOES IT BETTER!


Send to Transam Components Ltd., 59/61 Theobalds Road, London WC1

I am interested in the TUSCAN Z80 based single board computer with S100 expansion and enclose a S.A.E. for further details.

Name _____

Address _____

Telephone _____

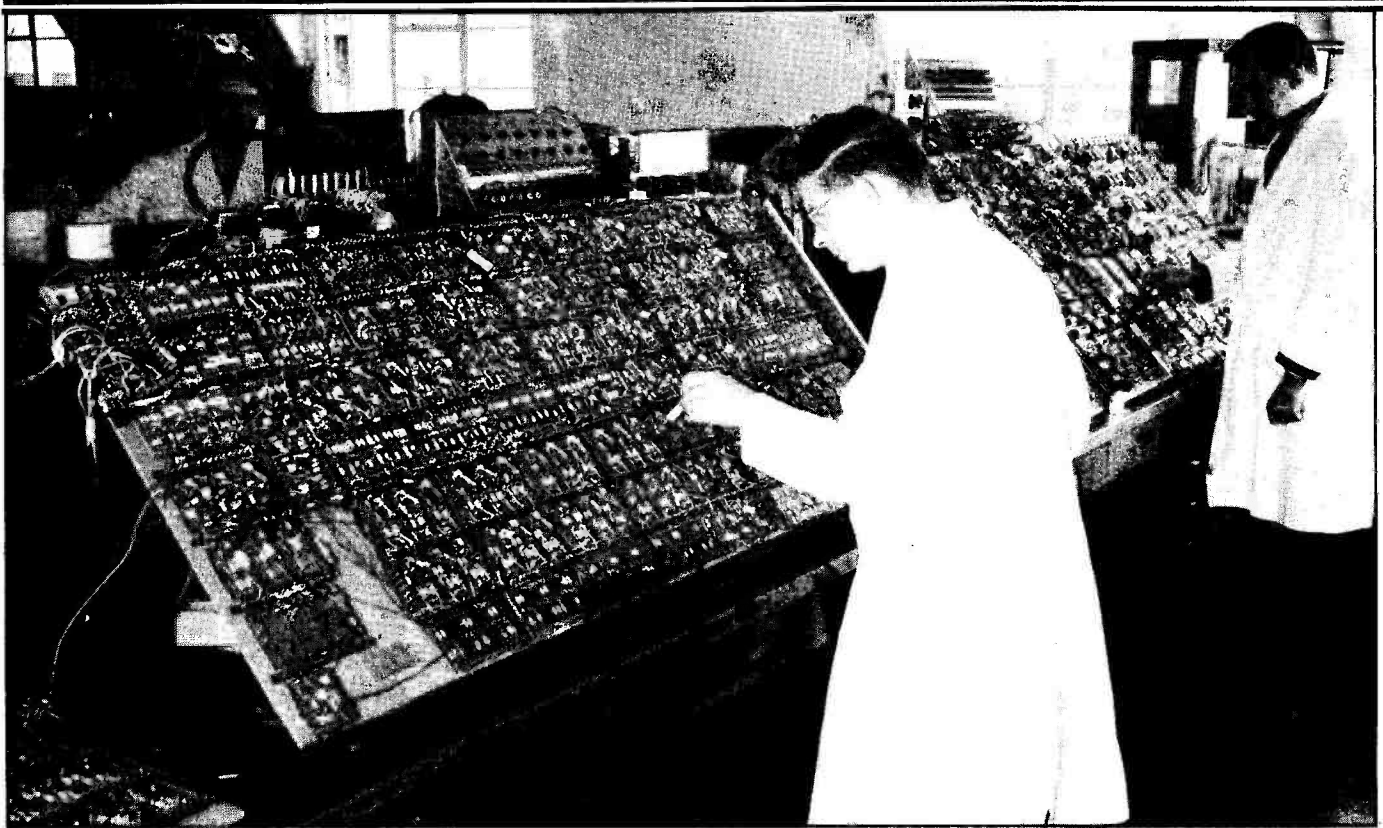

MICROBASICS

Since the demise of Microfile, we felt it was time to initiate another on-going publishing situation computingwise. Henry Budgett kicks off the first instalment of this great new hardware series with a potted history of the technology

Almost without fail we read in some publication or other that the age of computers is upon us. Whilst this statement is unquestionably true it is well worth looking back at the developments that have resulted in this proliferation of computers and computer-based systems. There is a popular temptation to attempt to baffle readers with science and technical terms in articles like this and this has led to an almost 'cult' image being foisted upon the industry, whereas, in reality, we should be trying to do exactly the opposite. It is to this end that I will attempt to define and explain each piece of terminology as it is reached. It is also the reason that I have chosen to begin the series at the beginning rather than to look at just the current darling of the media, the microprocessor.

Three Wise Men

In taking a look over our shoulders at the names associated with the very early computers we find that three stand out as veritable beacons. Taking them in chronological order, for no better reason than simplicity, we first meet Blaise Pascal. Born in the seventeenth century in France he made a considerable impact on the field of mathematics at that time. His father was a tax collector and the sight of him spending many hours adding figures stimulated Blaise to produce a

mechanical engine that would remove the drudgery. The basic design worked, no mean feat in itself, and enjoyed a limited commercial success. Its main drawbacks were that it could only add or subtract (and only one of those at a time). The Pascaline, as it was called, is still in use today recording the mileage travelled in your car and its improved successor which was capable of multiplication survived until the first electronic calculator sent it to the scrap heap. If you are fortunate enough to have one lying in a corner it is worth the trouble to take its lid off and reveal the guts. Remember as you look that this was invented when the Industrial Revolution was still in the future and there were no facilities for making accurate mechanical parts, a problem that was to cause our next innovator to fail.

Inventor With A Difference

Charles Babbage began in a similar manner to Pascal. He was also a child prodigy in the field of mathematics and soon began to find fault with the tables of logarithms being published. It was to the end of producing a machine for calculating these tables that Babbage began his life's work. It was fortunate that he was a wealthy man because despite a Government grant of some £17,000 and eleven years work he finally

abandoned his Difference Engine. Despite this failure his thoughts on automated mathematical machines were still active and he conceived the Analytical Engine that was to eventually ruin him. This idea was to incorporate all the essentials of the Difference Engine but with the magic ingredient of being programmable. The original specification of the machine was that it could perform mathematical operations to order on data provided.

At this instant the concept of computers as we know them today was born. The 'Engine' even incorporated most of the elements found in modern electronic machines. However the theory was not matched by the practice. The inability to make precision parts once again spelled doom and Babbage died aged 80 with not much left to his name except a pile of cogs and wheels. His son did manage to put together a working model, which can today be seen in the Science Museum, London.

Herman The Wise

Less than twenty years later our third individual, Herman Hollerith, forged the final link in the chain of events with his Tabulator. Designed as an entry in a competition to find a system that could analyse the results of the 1890 American census it harnessed the newly developed power source, electricity. Hollerith's machine completed the census in record time and made its inventor a very rich man. Indeed, the company he founded, IBM, is probably the largest mainframe computer producer in the world.

This combination of electricity and advanced mechanics was by no means an ideal solution. In the case of the 'Tabulator', it was designed for one specific job and could not be easily changed. This was not the programmable tool conceived by Babbage. It is interesting to note that, just as Babbage had looked toward the punched cards used by weavers to control their looms, so Hollerith used similar cards to record the census information on. These cards are still in use today in many computer rooms (some things never change!).

The Electronic Age


Just as the application of electrical energy brought Hollerith's 'Tabulator' the success it did, so it spurred on the development of the wide variety of electronic circuits based around the thermionic valve. By the time of the second World War there were many potential challengers for the title of the first computer but they all shared one common characteristic. The development of electronic switching had resulted in the universal adoption of the binary number system. The reason is simple, you can easily turn something on or off and hence create a binary code, but it is obviously much harder to turn something off or on in nine discrete steps. If Pascal or Babbage had designed their systems around binary mathematics instead of the conventional decimal they would have simplified their problems ninefold and the world may even have been introduced to the steam powered computer. Having taken the step to binary, computers never looked back and giants such as Colossus, ENIAC and ACE were born. Each of these was the descendent of the 'Analytical Engine' in that it could be programmed to do any logical task, within reason, and consisted of a number of basic elements, as in today's computers.

In much the same way as the transition from mechanical to electrical occurred, these early computers were replaced by pure electronic devices based on the newly invented transistor. The thermionic valve was an unreliable object, slow in operation and costly in terms of power consumption and space. Indeed, the processing capabilities of most of today's microprocessors greatly exceed the facilities offered even thir-

ty years ago. The advent of the transistor produced the 'second generation' of computers. A 'generation' in computer terms is generally defined as a tenfold decrease in size with a tenfold increase in processing throughput at a tenth of the original cost. As the transistor became the descendent of the valve, so the chip or integrated circuit became the descendent of the transistor. In those days, some ten to twelve years ago, the first integrated devices consisted of perhaps a half dozen transistors on a single chip of silicon. Rapid advances were made and soon a new kind of computer was born.

The Minis

Just as the Mini car revolutionised the way the world looked at motoring so the minicomputer changed the face of computers. Up till the advent of the integrated circuit there had been only 'computers', now there were 'mainframes' and 'minis'. These two were rigidly divided into sectors of operation, the mainframes were used for serious purposes, the minis were 'toys' used in research. Among the names of companies who were to make their fortunes producing minis was DEC, probably still the world leader. Soon the mini was to be found everywhere from research labs to classrooms and their spread was due simply to the fact that they were small, cheap and relatively easy to use. They were even built into pieces of equipment like machine tools. Indeed it is fair to say that the mini paved the way for the micro, although the actual distinctions between them have been rapidly eroded.

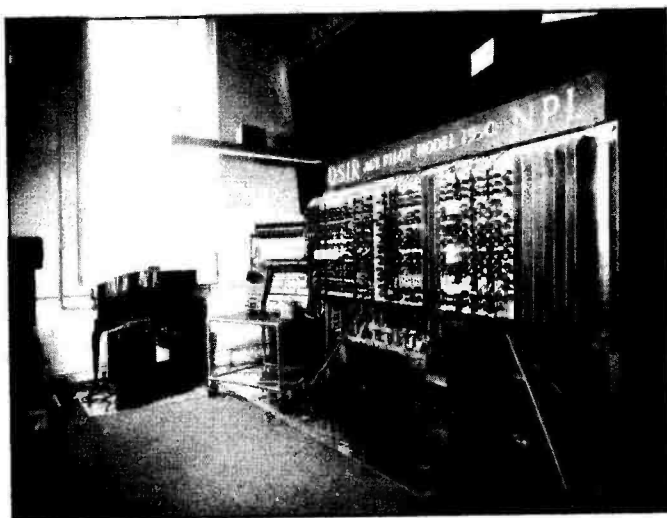

The pilot model of the National Physical Laboratory's ACE, one of the first computer giants (Crown copyright).

Firms involved in the business of integrated circuit production tend to follow a natural progression in the devices that they make. First off the production line come the standard logic elements, the AND OR type gates, and once the production of these is running at a profitable level they attempt to squeeze a little more onto the slab of silicon. As soon as this stage is proved they take another leap forward and so on. In the terminology this is a progression from SSI (Small Scale Integration) with about 10-20 actual devices on the 'chip' through MSI (Medium Scale Integration) which has a dozen or so gates (rather than discrete elements) up to LSI (Large Scale Integration) which is taken as being greater than 100 gates on the chip. At this stage of the game we are still talking about complex TTL type packages, the next jump is to VLSI which, believe it or not, stands for Very Large Scale Integration. We are now in the realm of memory devices and microprocessors.

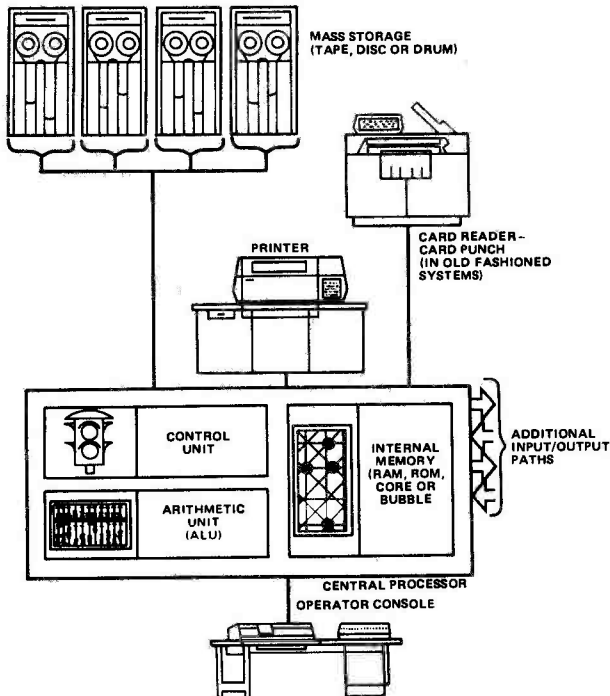


Fig.1. Block diagram of a computer system.

Common Concept


If we take a look at Fig.1 we can see a generalised block diagram of a computer. What kind of computer is not important; they all have the same functional blocks within them, be they micro or mainframe. The common misconception is that the "mighty chip" is a computer, far from it. Your average microprocessor still needs all the memory circuits, control circuits, mass storage devices and other components that even the old valve machines needed; they are merely smaller. The very first microprocessor came about in 1971 simply because it was realised that it would be possible to make a device of that complexity on a single chip. The device was called the 4004 and the company that made it was Intel. More on the micro next month — first some explanation on the basic building blocks of computers.

Eye Oh

The five fundamental elements of any digital computer are:- the ALU or Arithmetic Logic Unit, the control unit, the store or memory and the input and output devices. Taking these in the reverse order we have the input and output devices, often abbreviated to the I/O. Obviously the machine must be able to communicate with the outside world and vice versa, so the most common form of I/O is the Visual Display Unit or VDU. This has, to a very large degree, replaced the old-fashioned Teletype, a special electric typewriter often called a TTY, and is totally silent in operation, which is a welcome change from the racket the earlier device made. Other forms of I/O device are printers, for producing typed copy, plotters for producing graphical output or in the most esoteric cases digitisers and speech synthesisers.

The function of the I/O was simply to enable the user of the computer to load information for processing into the computer and to be able to get the answers back. Quite apart from this information there is the requirement of the computer programmer who wishes to put in information that will instruct the computer to perform certain operations. This, the program, is stored in the memory and of this vital component

there are two types; general purpose memory and off-line or backing memory. The general purpose memory is made up of a large number of bistable elements manufactured in either magnetic or semiconductor materials. In the context of the micro we often refer to these as the user memory. The backing memory is generally of a mass storage type like magnetic tape in one of several forms or magnetic discs or drums. Whilst the computer may have immediate access to some few thousand

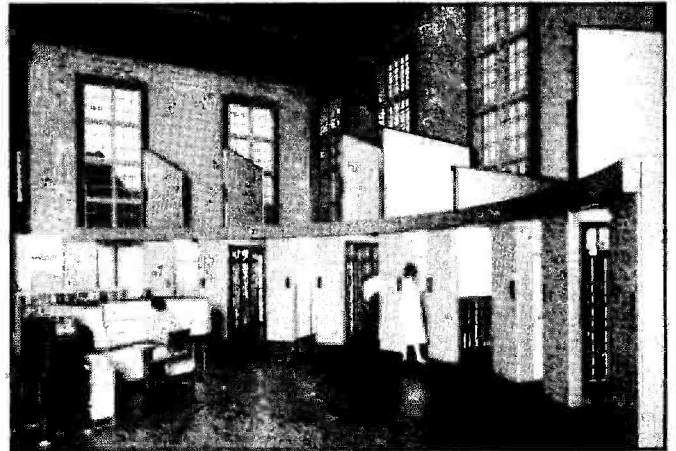

The business end of NPL's ACE computer, used to develop sophisticated mathematical techniques.

storage elements in the user memory, it can often store a few million elements in the backing stores. We will discuss the various types of memory in much greater detail at a later date — only the concept is important at this stage.

The control unit performs the task of making sure that all the various bits of the computer are working in the correct order. It would not be a very efficient machine that had to pause for information because it gave priority to looking after a printer and left the user waiting. The basis of all the control signals is a clock, in fact a very accurate oscillator circuit running at several million cycles per second. This is the heart of the machine and almost without exception all the functions within the computer are locked or synchronised to it.

The one remaining piece of the jigsaw is the ALU. This exists solely to perform arithmetic operations on the elements that are fed to it. Some of these elements are recognised as being instructions, others are simply information which is to be processed according to the previously received instructions. All this takes place at the level of binary signals, that is, each separate piece of information is represented by a pattern of logical ones or logical zeros and this is commonly called 'machine code'. Indeed, at this level of operation the computer is only aware of two groups of patterns — those which correspond to the defined set inside the machine, its "instruction set" in computer parlance, and those patterns which do not match this set which must be data.

To Pastures New

That's the end of this month's offering. In the next part our concentration will lock on to the microprocessor itself and just what goes on inside that little lump of silicon. Those with a wish to pursue the hardware angle in books, might be interested in the following recommended texts on the subject: Introduction To Digital Computer Design by Woollons, published by McGraw Hill. Consumers Guide to Personal Computing and Microprocessors by Frieberger & Chew, published by Hayden.

ETI

computing today

What to look for in the October issue
on sale September 12th.

FOX AND HOUNDS

CT goes rural again, and not down the pub either. Amid scenes of pink clad men thundering across open country, the sounds of baying hounds, demure ladies in full dress and beaming fresh air we find a curious creature called the fox. No blood shed here, this must be the only festival where the fox can actually beat his pursuers at their own game. Turn on all your cunning and see how long you last against the hunters.

Once again our reviewers have brought home an exclusive. This time it's an all British machine featuring the first implementation of the new 10K BASIC from Microsoft. How does the machine rate in terms of value against the established favourites like Apple and NASCOM? Read our expose in the October issue and make your choice.

MIGHTY MICKON

BUSINESS BRAINS

The trend in small business machines these days is to pack all the necessary whizz into a neat desk-top package. Are these really computers or just super-intelligent VDUs? Our reviewer goes to the superbain, a prime example of the breed, by the horns and attempts to wrestle the facts from within its cool grey exterior.

In the third part of our mammoth survey of computers and equipment we turn our attention to VDUs. Once again we present the facts and figures in clear and concise form to allow you to make the best decision. Don't miss it, it's the only one there is.

BUYER'S GUIDE

SPACEWAR

Not just another version of Star Wars but a real wargame simulation with tactical and strategic positioning. James T might find this a harder match than those Klingons he seems to have so much trouble with.

Unique in concept - the home computer that grows as you do! New! - The Acorn Atom

£120 An outstanding personal computer kit

plus VAT and p&p.



Also available
ready-built
£150
plus VAT and p&p


The ATOM - a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now - tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!

The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom.

The standard ATOM kit includes:

- Full sized QWERTY keyboard ● Rugged polystyrene case
- Fibreglass PCB ● 2K RAM ● 8K ROM ● 23 integrated circuits
- Full assembly instructions including tests for fault-finding. (Once built, connect it to any domestic TV and power source)
- Power requirement: 8V at 800 M.A. ATOM power unit available.

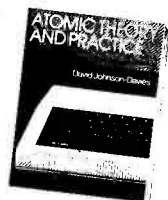See coupon. PLUS FREE MANUAL written in two sections - teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.



The ATOM concept

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMs may be linked to each other - or to a master system with mass storage/

hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally. So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

The ATOM hardware includes:

- Memory from 2K to 12K RAM on board (up to 35K in case)
- 8K to 16K ROM (two 4K additions) ● 6502 processor ● Video Display allows high resolution (256 x 192) graphics and red, green and blue output ● Cassette Interface - CUTS 300 baud
- Loudspeaker allows tone generation of any frequency
- Channel 36 UHF Modulator Output ● Bus output includes internal connections for Acorn Eurocard.

The ATOM software includes:

- 32-bit arithmetic ($\pm 2,000,000,000$) ● High speed execution
- 43 standard/extended BASIC commands ● Variable length strings (up to 256 characters) ● String manipulation functions
- 27 32-bit integer variables ● 27 additional arrays ● random number function ● PUT and GET byte ● WAIT command for timing ● DO-UNTIL construction ● Logical operators (AND, OR, EX-OR) ● LINK to machine-code routines ● PLOT DRAW and MOVE.



ACORN COMPUTER

4a Market Hill,
CAMBRIDGE CB2 3NJ

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Please send me the following items:

Quantity	Item	Item price inc. VAT+p&p	TOTALS
	ATOM KIT 8K + 2K (MIN)	@ £140.00	
	ATOM ASS 8K + 2K (MIN)	@ £174.50	
	ATOM KIT 12 + 12K (MAX)	@ £255.00	
	ATOM ASS 12 + 12K (MAX)	@ £289.50	
	1K RAM SFTS	@ £11.22	
	4K FLOATING POINT ROM	@ £23.30	
	PRINTER DRIVE 6522 VIA	@ £10.35	
	Buffer (LS 244)	@ £3.17	
	MAINS POWER SUPPLY (1.5 amps)	@ £10.20	
	TOTAL		

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £
Please debit my Access/Barclaycard No.

Signature

Name (Please print)

Address

Telephone No.

Registered No: 1403810. VAT No: 215 400 220

ET1/9/80



THREE FOR FREE FROM CSC

Electronics by Numbers
Projects No 7, No 8, No 9



Available from selected stockists ELECTRONICS BY NUMBERS No. 7 DIGITAL DICE

Roll the dice — the electronic way! The digital dice gives you an instant score randomly chosen from 1 to 6, every time you press the button. No losing this under the table!


No. 8 QUIZ MASTER

Play your own 'Sale of the Century'! Up to four contestants pit their wits; the first one to get the answer lights up his 'win' light, and stops anybody else from having a go.

No. 9 MOVING TARGET GAME

Test your reactions! A moving 'line of light' travels along from left to right, over and over again. You've got to 'fire' at just the right moment to score a hit. Fun for all the family!

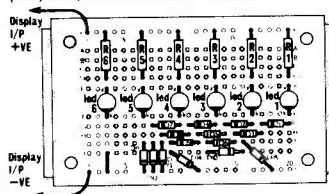Want to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph;



You will need: One EXP 300 or EXP 350 breadboard, 15 silicon diodes, 6 resistors, 6 Light Emitting Diodes.


Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components, connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

For full detailed instructions and layouts of Projects, 7, 8 and 9, simply take the coupon to your nearest CSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you missed projects, 1, 2 and 3, or 4, 5 and 6, please tick the appropriate box in the coupon.


PROTO-BOARDS

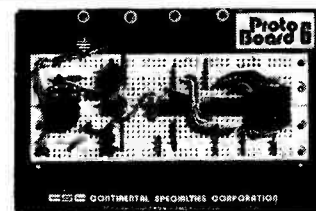The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT £9.20

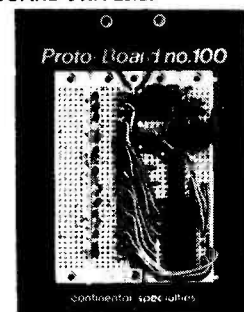

PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80

EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B

EXP 325 £1.60 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars



EXP 350 £3.15 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.




EXP 300 £5.75 The most widely bought bread-board in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.




EXP 600 £6.30 Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.



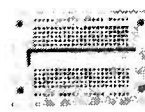EXP 650 £3.60 Has -6" centre spacing so is perfect for MICROPROCESSOR applications.



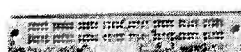EXP 4B £2.30 Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

THE CSC 24 HOUR SERVICE TELEPHONE (0799) 21682

With your Access, American Express, Barclaycard number and your order will be in the post immediately

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) LTD Dept. 9PP
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682 Telex: 817477

IT'S EASY WITH C.S.C. TO RECEIVE YOUR FREE COPY OF PROJECTS 7, 8 and 9

Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

For immediate action

The C.S.C. 24 hour, 5 day a week service. Telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN DIP	UNIT PRICE INC P&P @ 15% VAT	Qty req
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.48	
EXP 300	550	6	£ 7.76	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	

PROTO-BOARDS	CONTACT	IC CAPACITY 14 PIN DIP	UNIT PRICE INC P&P @ 15% VAT	Qty req
PB6	630	6	£11.73	
PB100	760	10	£14.72	

NAME.....

ADDRESS.....

I enclose cheque/P.O. for £.....
Debit my Barclaycard, Access, American Express card No.

Expiry date.....


If you missed project No's 1, 2, 3, 4, 5, and 6, tick box. ☐

For Free catalogue tick box ☐

C.S.C. (UK) Ltd. Dept. 9PP, Unit 1 Shire Hill Industrial Estate Saffron Walden Essex CB11 3AQ

Tel: Saffron Walden (0799) 21682. Telex: 817477

SPOT DESIGNS

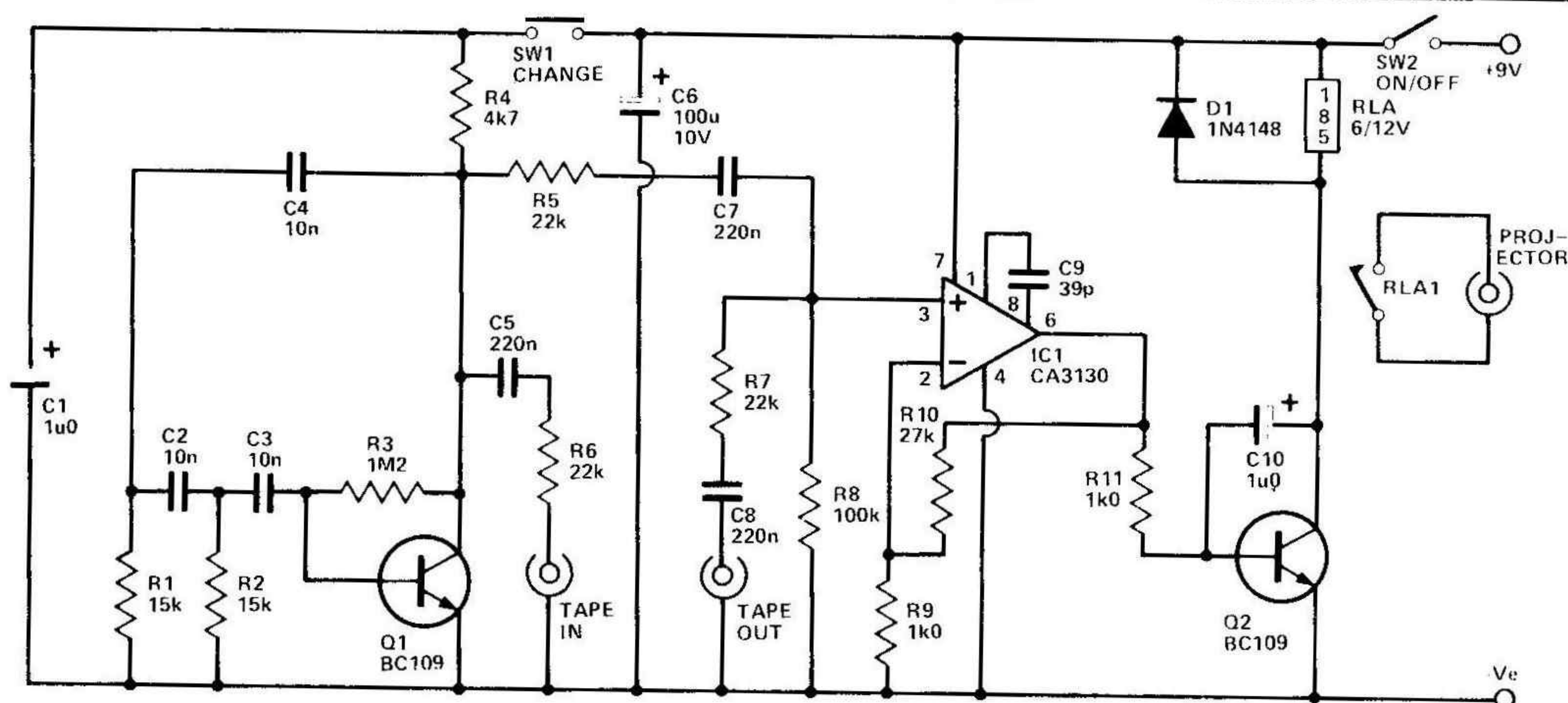

Slide/Tape Synchroniser

With the aid of a tape recorder and a slide tape synchroniser it is possible to obtain programmed slide changing with an automatic projector. By using a synchroniser and a stereo tape deck or recorder it is possible to have music and a commentary recorded on one channel and signals to give automatic slide changes at the appropriate points on the other channel.

A slide/tape synchroniser has two sections; a tone generator and an electronic switch. The tone generator is used to record short bursts of tone onto the tape at the points where slide changes are required. The electronic switch is fed with the tone burst output of the tape recorder and closes a pair of relay contacts for the duration of each burst. The relay contacts are, of course, used to control the automatic slide change mechanism of the projector. Usually the output of the tone generator is coupled to the input of the electronic switch, so that operating the tone generator causes the relay contacts to close. This is useful when recording a tape. With the projector loaded with slides, the synchroniser connected to the projector, the output of the tone generator fed to one input of the recorder and the music/commentary signal ready to be fed to the other input, the tape is inserted. Then the music and commentary are recorded and the tone generator is operated at the appropriate times so that the slides are changed and the tone bursts are recorded onto the tape. If the tape is then rewound, the slide magazine is brought back to its starting point and the tone burst output of the tape recorder is fed to the input of the electronic switch, replaying the tape should give the slide show with accompanying sound track and automatic slide changing. The operator only has to start the tape at the beginning of the show and stop it at the end.

A similar technique is used when using the unit as a program-

med slide timer, the only difference being that there is no soundtrack to bother with.

The tone generator uses Q1 in a straightforward phase shift oscillator operating at about 500 Hz, although the exact operating frequency is not of great importance. It is merely necessary to use one at which the recorder is capable of operating reasonably well. The output from the collector of Q1 is coupled to the tape recorder by DC blocking capacitor C5 and resistor R6. The latter attenuates the output. R6 also ensures that the oscillator cannot be so heavily loaded that it ceases functioning. SW1 is a non-locking, push to make switch. It is briefly pressed to connect the supply to the tone generator and produce the tone bursts.


The tone generator is based on operational amplifier IC1, which is used in the non-inverting mode. Its voltage gain is set at about 28 by R9,10 and R8 biases the non-inverting input to the negative supply rail. R5,7 form a simple passive mixer at the input of IC1, so that it can be fed from either the tone generator or from the output of the tape recorder without the need for any changeover switching. The output of IC1 is used to drive common emitter amplifier Q2, which has the relay coil and protective diode D1 as its collector load. Normally IC1's output is low and Q2 is cut off, but in the presence of an input tone the output of IC1 goes strongly positive on positive going half cycles. C10 integrates these pulses so that Q2 is continuously switched on in the presence of an input tone and the relay is energised. The relay contacts then close and operate the slide change mechanism of the projector.

The current consumption of the unit is only about 500 μ A, but rises to around 40 mA during the brief periods when the relay is activated. The relay can be any type having a 6/12 V coil with a resistance of about 185R or more, provided it has at least one set of normally open contacts of adequate rating.

Clipping Monitor

When using an amplifier at virtually its full output power there is a risk of "clipping" occurring. The amplifier is overdriven to the point where output peaks are flattened because the amplifier simply cannot provide a high enough output voltage. The distortion caused by clipping is often quite severe and readily apparent, but this is not always the case. It is not uncommon for the tweeters in loudspeakers to burn out due to overloading caused by clipping producing strong high frequency signals!

The circuit relies on the fact that with less than about 2 V applied to a LED it will not pass any significant current and will fail to light up. If the voltage applied to the LED is only marginally increased above 2 V, the LED avalanches, a heavy current flows and it glows brightly. R1 is adjusted so that the voltage applied to LED1 via current limiting resistor R2 is just sufficient to cause D1 to glow quite brightly when the amplifier is driven into clipping.

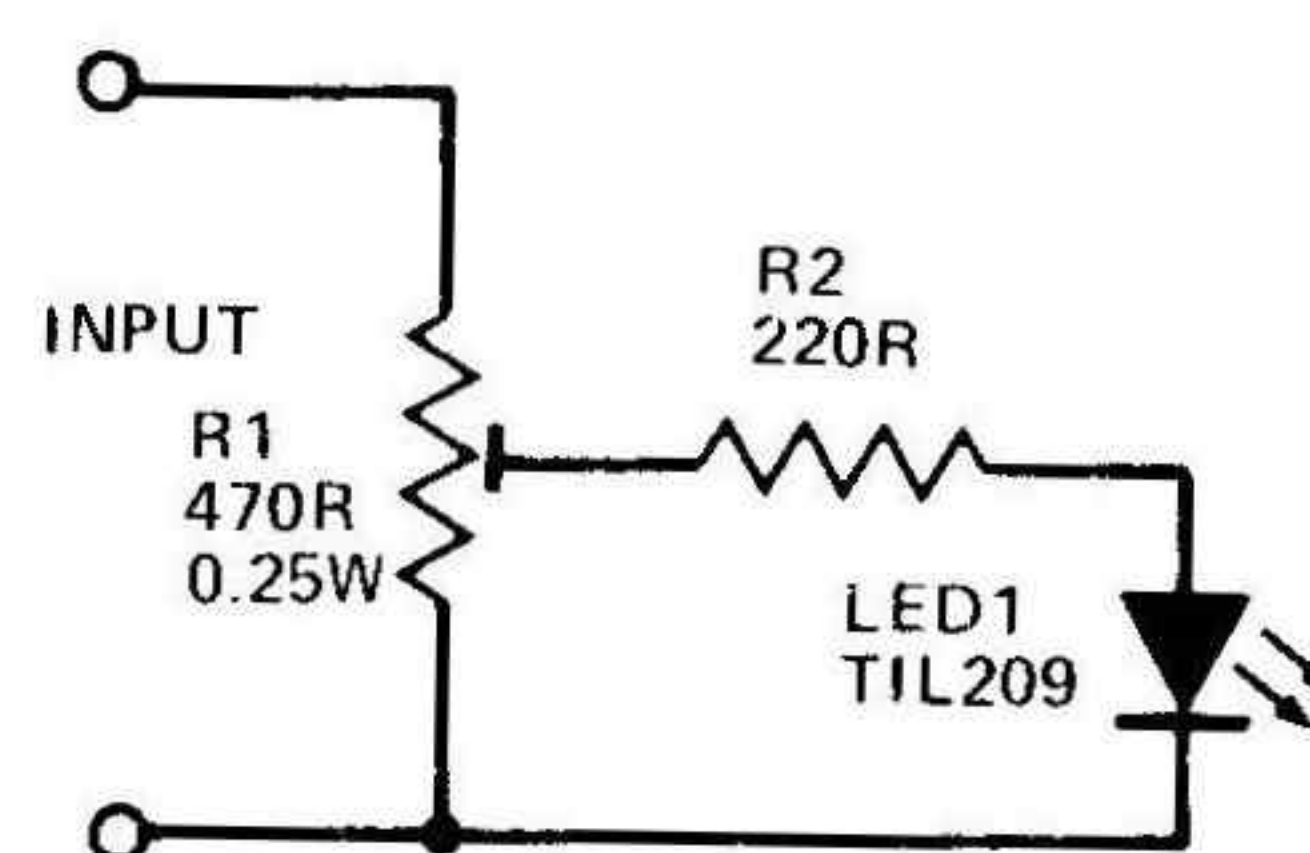


With the amplifier driven just below the clipping threshold there is just enough voltage applied to the circuit to cause LED1 to visibly glow, although it does so at less than full brightness. If the amplifier is driven significantly below the clipping level there will be insufficient voltage fed to D1 to cause it to conduct and it will not light up.



WERSI

at AURA SOUNDS

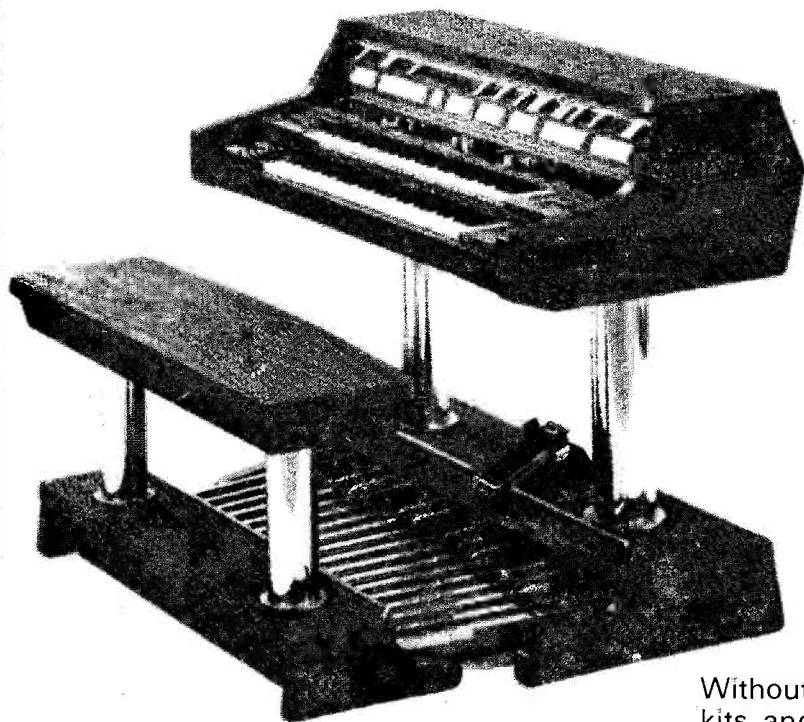

Tomorrow's Electronic Organ Kit is Here

POSSIBLY A NEW NAME TO YOU, BUT KNOWN IN OVER 25 COUNTRIES FOR THE SUPERIOR INSTRUMENTS WHICH THIS GERMAN COMPANY PRODUCE.

See us at 'RECRO '80', Leamington Spa, 1st-8th August. It's a great day out for all the family plus the opportunity to see the whole WERSI range demonstrated live.

WERSI is the first kit producing company applying the latest achievements of the space age technology.

This has decisive effects on the technical and musical quality of WERSI'S electronic organs for the do-it-yourselfer.

The application of modern integrated circuits, so called ICs, simplifies the organ construction considerably. A single IC may replace up to 10,000 conventional electronic components.

In addition, ICs save a lot of space and they are extremely reliable devices.

WERSI, however, went a step farther yet. IC's which were not available on the open market, were developed for specific purposes by WERSI engineering. They are being produced by the most highly reputed IC manufacturers in the world. The result: economical electronic organs with the most up-to-date techniques and unsurpassed musical capabilities.

Without doubt the most comprehensive kits and the most up-to-date designs available today. Just consider a few of the features:

- Precision Master Generator, using MOS-LS1.
- Integrated electronic keying in 1²L technology.
- Unique — All switch functions are programmable.
- Even the smallest organ has drawbars in addition to fixed stops.
- Craftsman-made cabinets available in five veneers.
- Ready-made wiring harnesses eliminate errors.

WERSI MAKES DO-IT-YOURSELF CONSTRUCTION EASIER THAN EVER BEFORE AT A FRACTION OF THE PRICE OF THE FULLY ASSEMBLED WERSI RANGE. GET THE FACTS NOW.

AURA SOUNDS 14-15 Royal Oak Centre, Brighton Rd., Purley, Surrey. Tel: 01-668-9733
and at 17 Upper Charter Arcade, Barnsley, W. Yorks Tel: Barnsley (0226) 5248.



**Send now
for the
104 page
full-colour
catalogue.**

Please send me the full colour WERSI catalogue, price lists and supporting literature (weighing 1 lb!) I enclose a cheque/p.o. for £1.00.

Name.....

Address.....


Send to Aura Sounds (ET13), 14/15 Royal Oak Centre, Brighton Rd., Purley, Surrey.

'MICRON'

from

- FULLY BUILT,TESTED,and housed in ATTRACTIVE CASES
- 6502 based microcomputer
- VDU alpha numeric display
- Powerful monitor TANBUG
- 8K RAM
- 32 parallel I/O lines
- 2 TTL serial I/O lines
- 1 serial I/O port with RS232C, 20mA loop and 16 programmable Baud rates
- Four 16 Bit counter timers
- 300/2400 Baud filenameed cassette interface
- Data bus buffering
- Memory mapping control
- 71key ASCII Keyboard,including numeric keypad
- Includes power supply
- Also includes the first
- * 10K MICROSOFT BASIC *
- available in the UK.
- All the usual BASIC commands
- Integer and real numbers
- Integer and real arrays
- Intrinsic functions ABS,INT,RND,SGN,SIN, SQR,TAB,USR,ATN,COS,EXP,LOG,TAN.
- User defined functions
- READ and DATA statements
- Dump and load programs for cassette recorders
- Program editing command
- String function for text I/O
- BASIC can call user machine-code sub routine
- User machine-code interrupt handler interfaces with BASIC

£395
inc.VAT,P&P

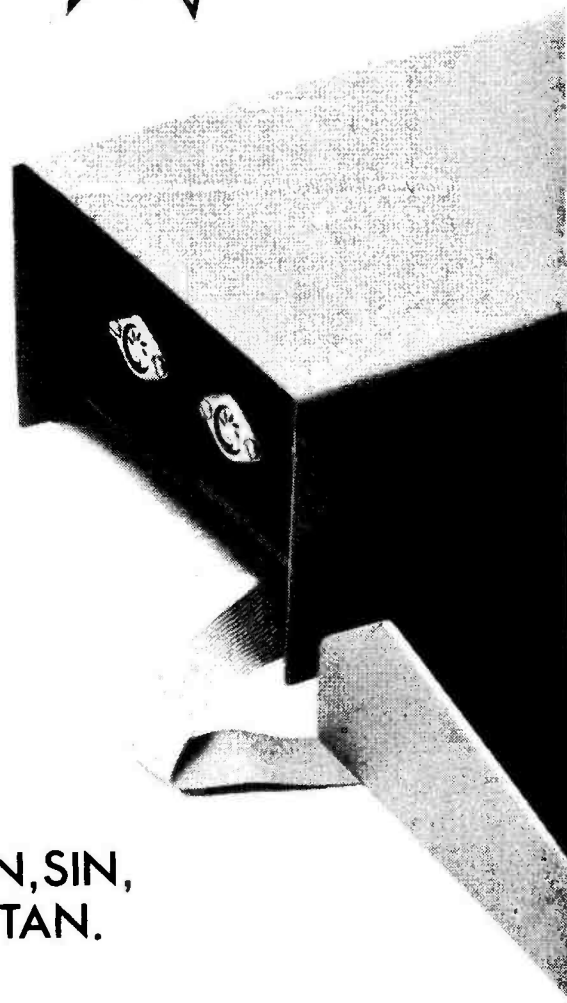

TANGERINE

Available soon!

TANRAM - 40K Bytes on one board!
12 slot SYSTEM MOTHERBOARD,
supports 277K Bytes
SERIAL & PARALLEL I/O boards
High Definition COLOUR GRAPHICS



For comprehensive
details send 12p stamp to:-
Tangerine Computer Systems Ltd.
Forehill, Ely, Cambs. Tel: (0353)3633

Name

Address

.....

.....



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30

THE CHIPS ARE DOWN
MOSTEK, INTEL, NEC, MOTOROLA
I.C. PRICES SLASHED!

A massive purchase of brand new "state of the art" data processing equipment enables us to offer the following chips at never, and we mean never to be repeated prices.


8085A	Central Processor	£11.99
8155C	256x8 Static Ram	£8.95
8253C	Programmable Interval Timer	£8.95
8255A	Programmable Peripheral Interface	£9.95
8259A-8	Programmable Interrupt Control	£4.75
8755A	2Kx8 Eprom 16 I/O Lines	£34.50
MC6850P	ACAI	£3.75
2652	MPCC Comms. Controller	£24.00
2102 1K	Static 650ns Rams 8 for	£5.25
1702	256x8 Eprom	£3.75
5101L-1	256x4 Static Ram 450ns	£4.95

And Remember All Chip Prices Include V.A.T.

All above I.C.s are brand new or removed from new unused socketed P.C.B.'s. Eproms supplied washed.

All full spec. and guaranteed

DATA DYNAMICS 390 ASCII PRINTERS

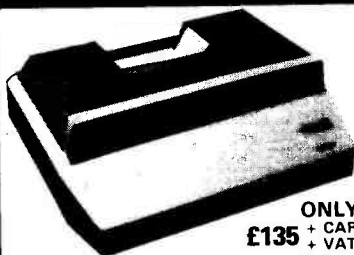

ONLY
£135 + CAR
+ VAT

An advantageous purchase enables us to offer you these superb condition quality printers at a fraction of their original cost. The 390 is a standard Teletype printer housed in a soundproof case. Standard features such as 80 columns, 20ma/RS232 interface and 110 Baud enable direct connection to your M.P.U. Supplied in excellent condition and guaranteed in working order.

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed. 50 + BAG £2.95 100 + BAGS £5.15

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex-equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages 110 V.A.C. (£5.05 + pp 55p) OR 240v A.C. £6.15 + pp 65p. DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2"

ELECTRONIC
COMPONENTS
& EQUIPMENT

66%
DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's., P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kls £ 4.75+pp £1.25 5kls £ 6.75+pp £1.80
10kls £11.75+pp £2.25 20kls £19.99+pp £4.75

★	ROM & RAM STAR OFFERS	★
	4116 16K DYNAMIC RAMS 200ns 8 for £28.50	
	2716 2Kx8 SINGLE RAIL EPROMS £10.25 each	
	2716 2Kx8 3 RAIL EPROMS £8.50 each	

★ **SHUGART SA800** ★
8" Floppy Disk Drives
as new £225.00 + VAT

SUPERVALUE P.C.B. SPECIAL

Another great buy. Board contents include 62 Digital I.C.'s all located in 14 pin D.I.L. sockets. Original cost over £90, our price only £4.95 + PP 65p.

OPTO SMASH!

TIL 302/MAN 77 segment LED readout common anode direct drive (via resistors) from 7447 I.C. 10 each
TIL 119/OC72 Darlington opto isolator 3 for £1.00.
TIL305 0.3 7 x 5 matrix LED alphanumeric readouts £3.75 each.
PHOTO TRANSISTOR
Fairchild FPT-100 NPN silicon 30v 25ma. 4 for £1.00.

DISPLAY I.C. AND TRANSISTOR BARGAINS NEVER CHEAPER

All I.C.'s and Transistors by well known manufacturers and fully guaranteed. No fall outs. Comprehensive data on I.C.'s 15p per type.
2N4351 N channel MOS FET
2N4352 P channel MOS FET.
60p each £1.00 per pair.

HIGH VOLTAGE NPN POWER
SWITCHING TRANSISTORS BVcbo 600v BVceo 500v BVebo 15v 1c 5 amps
Pc 125 watts HFE 60 typ ft 2.5 mhz ideal invertors, etc. T03 £1.60 each 4 for £5.40.
BF258 NPN 250v @ 200ma 45p each 3 for £1.08.
I.R. BS801 2.5 amp 100v bridge rec. P.C. mount long leads 35p each 4 for £1.08.

IN4998 4 amp 100v P.C. mount diodes long leads 14p each 10 for £1.10.
LM309K + 5v 1.2 amp regulator £1.10 each 6 for £5.35.
AGFA C10 computer grade cassettes complete with library cases 68p each, 10 for £5.50.
IN4004 SD4 1 amp 400v diodes 7p each 18 for £1.00.
I.R. 12 amp BRIDGE RECS. 400 volt £1.25 each.

POWER DARLINGTON SCOP! MJ1000 NPN 60v 90w 8 amps T03 85p each
2N6385 NPN 80v 100w 10 amps T03 £1.25 each
LM4030 NPN 60v 150w 16 amps T03 £2.25 each

DECADE 0-9 THUMBWHEEL SWITCHES. Stackable, gold plated contacts, dim. 33 x 43 x 8 mm. 90p each, 10 for £5.50.

Miniature Continental Series 12VDC 4c/o plug in relays £1.30 each.

Greenpar 500 BNC Chass. socket single hole fixing 65p

C90 Audio Cassettes screw type construction 45p each 3 for £1.00.

Bulbs 24v 14 watt white frosted S.B.C. 8 for £1.00.

Bulbs 12v 100 watt clear, base similar S.B.C. 45p each.

S.B.C. Bulb Holders All steel cad. plated panel mount easily fixed via nut and round hole, ideal disco displays, scoreboards, etc. 4 for £1.10.

VMOS VMEI Siliconix T03 power FET 0.60v, DC-200 mhz will drive direct from CMOS etc. £1.50 each, full date 30p.

Heavy Duty Flat Insulated Earth Braid 100-200 amp braided tinned copper in heavy clear PVC sheath 50p per metre. £6 for 15 metres + PP £1 per 15 metres.

BULGIN miniature 6 way male chassis mount socket and matching free plug 60p each, 2 for £1.10.

Red L.E.D.'s full spec. 0.2 14p each, 10 for £1.25.

Red L.E.D.'s 0.125 10p each 10 for 80p.

Dynamic Stick Mics 6000 with built in on/off switch complete with lead and min. jack plug £1.15 each. 10 for £10.00.

T05 HEATSINKS "Thermalloy" black anodised press on aluminium finned type 18p each. 8 for £1.00.

STOP PRESS

Just arrived. Teletype
ASR33, ASC11, 80 Column printers
complete with keyboard and
8 bit paper tape punch and
reader. New low price
£235.00 + carr & VAT
PHONE FOR MORE DETAILS.

BARGAINS GALORE!

In our walk round Warehouse
NOW open Monday to Saturday 9.30-5.30

FREQUENCY	CASE
100 KHZ	HC6/U
1.00 MHZ	HC6/U
2.00 MHZ	HC6/U
2.50 MHZ	HC6/U
5.00 MHZ	HC6/U
8.00 MHZ	HC6/U
10.00 MHZ	HC6/U
11.20 MHZ	HC6/U
20.00 MHZ	HC6/U
33.333 MHZ	HC6/U
UART Xtal 3B 40 KHZ	
S&E for latest XTAL stock list.	

PRICE	£2.95
£2.75	
£2.35	
£2.35	
£2.25	
£2.25	
£2.25	
£2.25	
£2.25	
£2.50	
£1.75	
£2.80	

no time to test price of only

£20.00 + P.P. £1.60
SUPER Cased VERSION Same as above spec. but housed in attractive two tone moulded, free standing case. Unit also includes an all TTL parallel to serial converter (no details) etc.

£27.50 + P.P. £1.85

OROIDAL TRANSFORMERS

HP 240v pri. sec. 2 x 30v @ 4 amps 2 x 18v @ 1 amp £11.00 + p.p. £1.95 dimensions 4 1/2" x 2 1/2"
PR 240v pri. sec. 15 0 15 @ 2 amps dimensions 3" x 2 1/2" £4.95 + p.p. 99p
TM 240v/110v pri. sec. 15 0 15 8vA dimensions 2 1/2" x 1" £1.95 + p.p. 30p
All voltages measured off load.

Plugs, Sockets & Connectors Cannon 'D' Range

Ways	Plug	Socket
9	£1.03	£1.26
15	£1.17	£2.01
25	£1.72	£2.58
37	£2.35	£4.14
50	£2.90	£5.46

25 way ex-equip. plug or socket £1.25

Edge connectors, gold plated

0.1 DS	85 way	£3.99
0.1 DS	45 way	£2.45
0.15 DS	56 way	£3.25
0.156 DS	36 way	£2.00

All connectors easily cut to size

1000's of other connectors in stock

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

HOW TO GET HERE

Victoria, London
Bridge or Holborn
Viaduct to
Thornton Heath.
1 minute from
Thornton Heath
Station.

POWER SUPPLY UNITS

5 VOLT 2.5/8 AMP TTL Made for TTL this compact ex computer systems unit features a 10 amp transformer. DC outputs of 5 volts @ 2.5 amps and 7.5 volts @ 5 amps are available. The 5v output is fully regulated and smoothed with electronic current limiting. May be easily modded for 5 volts @ 7-8 amps. Sold complete with circuit, believed working but untested. £8.25 + £1.60pp.

5 VOLT 3 AMP Ex computer systems, complete on one small chassis, features full regulation and crowbar over voltage protection.
£8.50 + pp 80p

PRINTERS

CENTRONICS 101A 132 column
Matrix printer, serial/parallel input £525 + VAT
DATA PRODUCTS 300-1100 L.P.M. 80 column
Barrel printer, standard T.T.L. parallel interface £650 + VAT
Many other printers available from £45.00

KEYBOARDS

★ 76 KEY ASCII CASED ★

At last a coded 76 key ASCII keyboard at the right price. Housed in an attractive light grey case, this unit was originally made for ICL for use in airport reservation systems so only the BEST parts were used. It has everything, we think, to meet your most exacting requirements, numeric keypad, upper and lower case, cursor controls, single 5 volt rail, serial and parallel data outputs, plus eight LEDs mounted on the case. Supplied with circuits, believed brand new, but may have minor scratches on cases.

Only **£43.50** + £1.60pp

★ LOW PRICE CHASSIS ★



A special bulk purchase enables us to offer the above keyboard at a lowest ever price. 49 coded keys encoded into a direct TTL compatible 7 bit output. Features such as delayed strobe, 5 volt D.C. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector, at a secondhand

price of only

£20.00 + P.P. £1.60
no time to test price of only

£27.50 + P.P. £1.85

OROIDAL TRANSFORMERS

HP 240v pri. sec. 2 x 30v @ 4 amps 2 x 18v @ 1 amp £11.00 + p.p. £1.95 dimensions 4 1/2" x 2 1/2"
PR 240v pri. sec. 15 0 15 @ 2 amps dimensions 3" x 2 1/2" £4.95 + p.p. 99p
TM 240v/110v pri. sec. 15 0 15 8vA dimensions 2 1/2" x 1" £1.95 + p.p. 30p
All voltages measured off load.

Plugs, Sockets & Connectors Cannon 'D' Range

Ways	Plug	Socket
9	£1.03	£1.26
15	£1.17	£2.01
25	£1.72	£2.58
37	£2.35	£4.14
50	£2.90	£5.46

25 way ex-equip. plug or socket £1.25

Edge connectors, gold plated

0.1 DS	85 way	£3.99
0.1 DS	45 way	£2.45
0.15 DS	56 way	£3.25
0.156 DS	36 way	£2.00

All connectors easily cut to size

1000's of other connectors in stock

ELECTRONICS


Dept. E.T.I. 64-66 Melfort Rd., Thornton Heath, Surrey.
Telephone 01-689 7702 or 01-689 6800

MAIL ORDER INFORMATION

Unless otherwise stated all prices inclusive of VAT. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 40p per order. Bona Fide account orders minimum £10.00. Export and trade enquiries welcome. Orders dispatched same day where possible. Access and Barclaycard Visa welcome.

AUDIOPHILE

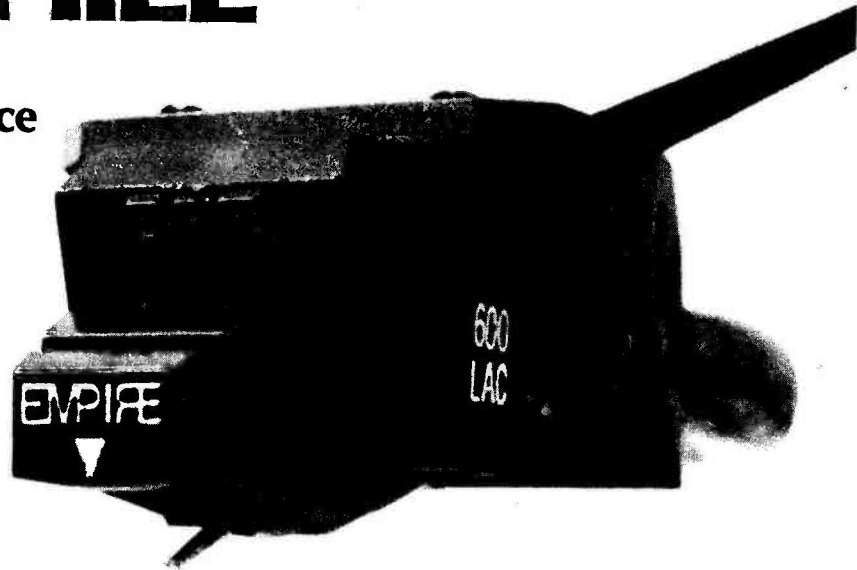Empire's new Dynamic Interface series comes under scrutiny this month and Ron Harris has some second thoughts on metal tape tests.



After last month's highly physical encounter with the JVC AX9 and its 37lbs of muscle rending weight, I decided to cheat the truss a little longer and return to the realm of the phono cartridge — where weight is measured in grams and a man (and his assets) can feel comfortable in their work.

A friend of mine — yes, even editors have friends — has for some time been muttering darkly about Empire cartridges being the best thing since the Big Bang. But after they managed to ignore my pleas for an EDR-9 when last I lined up the cantilevers I had all but given them up as a figment of his lurid imagination.

However, with the dawning of a new day — and the shuffling arrival of our geriatric postman — was delivered unto me a small brown parcel, containing not one but two Empire cartridges. Once more I am forced to revise my model of the Universe. Wrong again.

Having beaten off my friends grasping, avaricious little paws and refused all offers to kidnap Felicity Kendal in return for the contents of the box, I found myself confronted by the new Dynamic Interface series in the form of its 600LAC and 400TC manifestations.

Right then, into battle, SME raised against the fall of night and the howling of the wolves (i.e. neighbours).

Empire Strikes Back

These cartridges use a moving-iron principle to generate their millivolts, inherently more linear than the more common moving magnet. The top two in the range, the 600LAC and the 500ID also employ an 'internally dampened' cantilever to overcome the mechanical h.f. resonance at around 18 kHz.

Other innovations include a cantilever composed of an Aluminium alloy with Boron deposited into it, reduced tip mass and 'two position locking' for the stylus assembly to ensure that it is correctly located.

Benefits claimed are flatter frequency response due to close control of resonance, reduced IM distortion, increased trackability (sorry Shure!), good hum rejection and reduced record wear. In fact everything short of the power of regeneration. Maybe that comes with next year's model.


The basic engineering concept of these cartridges differs from the 'norm' in that here the coils and magnets are fixed in place within the body, a hollow iron armature is attached to the cantilever and generates the output in the coils by moving within the field from the three magnets situated next to them.

Unusual is Empire's use of two 'front' magnets to linearise the field through the pole pieces and coils, which also act to reduce hum pickup. Field strength is effectively concentrated in the gap where the armature is in motion. Empire say this also reduces microphonics (susceptibility to outside vibration).


Inside Story

The 600LAC features the inertially dampened tuned stylus (IDTS) system, Empire's scheme to defeat h.f. resonance. This employs an assembly *INSIDE* the cantilever, consisting of elastomer ring and iron piecework, which provides an antiphase resonance at the critical point to produce a much flatter "twin peak" overall response around resonance.

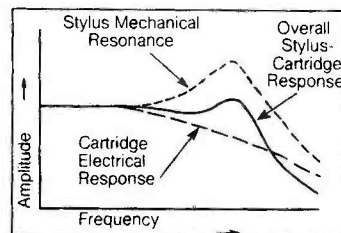
The diagrams explain this better than any combination of letters and spaces.



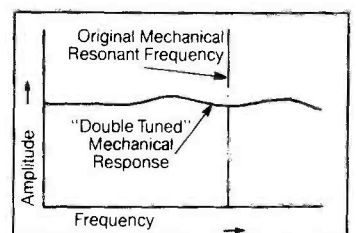Frequency response of a conventional stylus assembly.




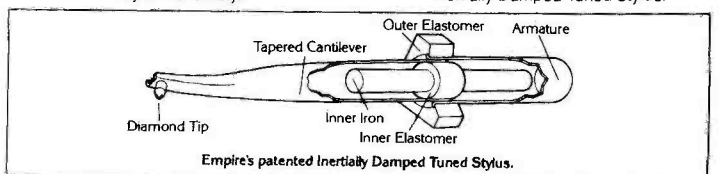Frequency response using Empire's patented Inertially Damped Tuned Stylus.



Empire's patented Inertially Damped Tuned Stylus.

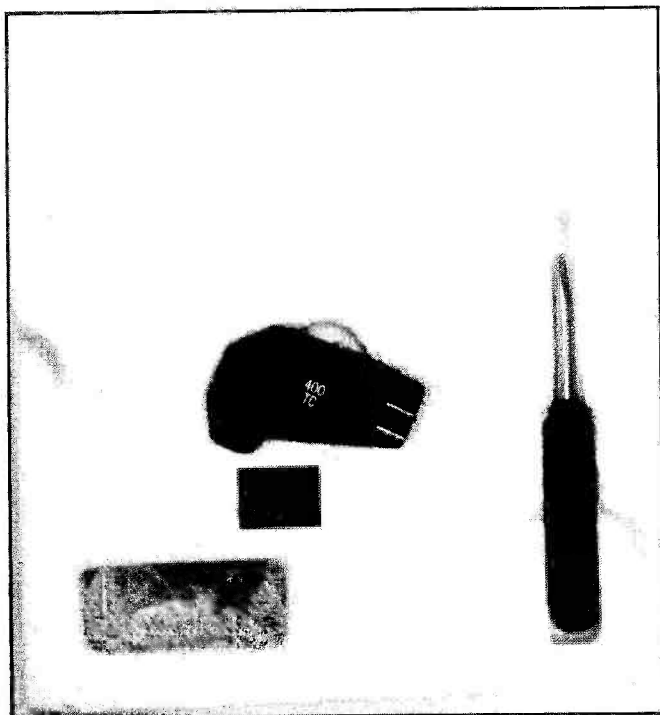
Says it all better than words — Empire's IDTS system.



The 400TC pickup reclining in its box awaiting the moment of truth and the SME. All the DI range are physically similar and are distinguished by the colour of the stylus carriers. In the case of the 400TC this is an extremely lurid red.

LAC stands for 'Large Area of Contact' and implies that lower record wear should be expected from the 600LAC than from a normal elliptical or spherical point. Under high-power magnification a very high order of finish was revealed on our sample, confirming the manufacturer's claim of having paid special attention to stylus polish. Such care would manifest itself in better preservation of those irreparable grooves and lower surface noise.

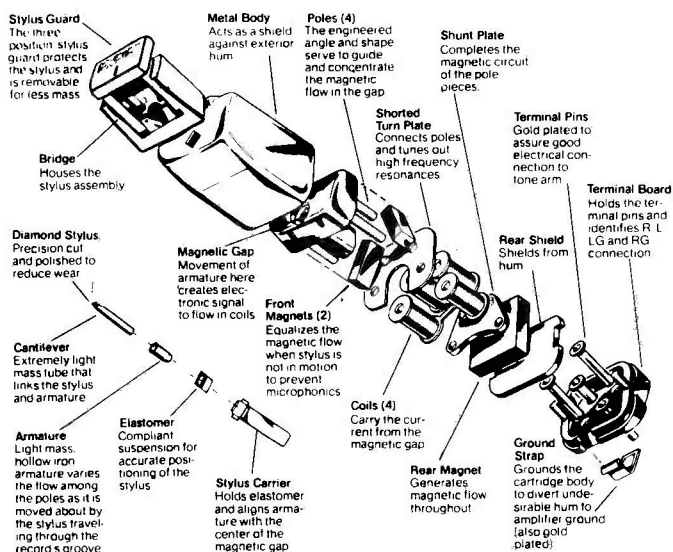The 400TC has the tapered cantilever of its more expensive brethren, and a lower tip mass than most units in this price range. The 400TC retails at around £30 and the 600LAC at



An exploded view of an Empire cartridge. Note the use of two small magnets ahead of the main assembly. This is to concentrate and linearise field strength in the region around the moving iron element.

about £75 — both in very competitive areas indeed. Good performance is not a bonus here, merely a basic requirement for (commercial) survival.

Packet In?

One immediate disappointment must be the presentation of the cartridges. Both arrive wedged into a block of polystyrene, along with fixing hardware and mandatory screwdriver. Outer packaging is a simple cardboard sleeve. Whilst one can applaud the avoidance of expensive trappings that do nothing to enhance performance, surely this is going a little too far — especially at the £80 or so of the 600LAC?

Indeed, the overall appearance of the cartridges themselves does not manifest the overtly confident engineering that one gets from something like a Shure or an Ortofon. Not that they are anything but well made — please don't go thinking that Audiophile is casting needless aspersions! The company offer a two year guarantee on all the range as proof of their confidence in the product. It is certainly not misplaced, I think.

Sound Evidence

After the measurements had been taken and the lab stool vacated for a more comfortable armchair, the 600LAC was auditioned mounted in the inevitable SME series III pickup arm — still the Rolls Royce of its field. Comparison was drawn against the Ortofon/SME 30 H and Coral MC81 (moving coil) units.

Whatever the criteria the 600LAC is a good cartridge. Its sound is characterised by a solid bass and a forward presentation. Treble is very well extended and smooth. Resonances are well controlled, so that damping is certainly effective audibly. The Empire works well with any type of music, but undeniably adds a certain amount of 'life' of its own that is most exciting with rock.

At times I could detect a slight 'edge' on difficult, heavily modulated passages although tracking was always impeccable and the 600LAC was never tricked into mistracking. It has a great deal of the sparkle and transparency of the best cartridges around, but loses out in the mid-range where it is a little veiled when judged absolutely. Nonetheless all hi-fi is a compromise of some sort or other, and this pickup gives away less to perfection than most. Good value, I thought.

Onto the 400TC, which was compared against the Shure M97E and Goldring G900 IGC reference. In a straight A-B comparison the Empire betters the Shure, but falls short of the more refined G900 IGC. It does offer very good returns on the £30 investment required to secure its services, however.

Like the 600LAC, the sound is forward in nature and projects the music outwards from the loudspeakers. Presentation is confident with a good low frequency performance and very smooth top end. As long as speakers are chosen to complement the distinctive style this Empire would be a worthy addition to any system in the £400-£600 price range.

In fact the 400TC is close enough to the 600LAC to make me wonder what place exists for the 500ID, a model that sells for £45 and sits between the two in the Empire range.

Conclusions

Overall then, two good units well placed to succeed and which should be added to shortlists for audition at the friendly neighbourhood dealers. Good features common to both were an insensitivity to surface noise, extended bass and smooth treble. Well worth a listen.

I can see Empire gathering quite a following for this new

Model	600LAC	400TC
1 Frequency Response Bandwidth	6Hz - 50,000Hz	7Hz - 34,000Hz
2 Frequency Response	20Hz - 28,000Hz $\pm 1\frac{1}{4}$ dB	20Hz - 20,000Hz ± 2 dB
3 Tracking Force Range	1 to 2 grams	$\frac{3}{4}$ to 2 grams
4 Recommended Tracking Force	1 $\frac{1}{2}$ grams	1 $\frac{1}{4}$ grams
5 Separation @ 200Hz	21 dB	20 dB
@ 1kHz	30 dB	28 dB
@ 5kHz	20 dB	20 dB
@ 12.5kHz	17 dB	16 dB
6 I.M. Distortion @ 3.54 cm/sec	0.1%	0.15%
@ 14.5 cm/sec	0.4%	0.5%
7 Stylus Shape and Size	LAC	0.2 x 0.7 mil bi-radial
8 Cantilever	Boron vaporized, inertially damped, tapered Aluminum alloy	Tapered Aluminum alloy
9 Effective Tip Mass	0.6 mg	0.6 mg
10 Compliance (Dynamic)	20 x 10 ⁻⁶ cm/dyne	20 x 10 ⁻⁶ cm/dyne
(Static)	28.5 x 10 ⁻⁶ cm/dyne	23 x 10 ⁻⁶ cm/dyne
11 Tracking Ability @ 300Hz	17.9 cm/sec	17.9 cm/sec
@ 1kHz	38 cm/sec	32 cm/sec
12 Channel Balance	within 1.0 dB	within 1.0 dB
13 Vertical Tracking Angle	20°	20°
14 Output @ 1kHz @ 3.54 cm/sec	4.0 mV	3.8 mV
15 Number and Type of Magnets	2 Samarium Cobalt, 1 Indox V	2 Samarium Cobalt, 1 Indox V
16 Load Resistance	47k Ohms	47k Ohms
17 Capacitance	150 pF	150 pF to 400 pF (350 pF optimum)
18 Hum Sensitivity @ 60Hz	0.34 μ V/A/m	0.5 μ V/A/m
19 Total Weight	5.3 grams	5.3 grams
20 Stylus Replacement No. & Color	S600LAC (Black)	S400TC (Red)

How about this for a set of specs? Empire are certainly unafraid to lay it all out in black and white. On test no significant differences were discovered. Hum susceptibility was not tested — you'll note that they have specified this at 60 Hz. Damn colonials again is it not? Tracking weight ranges are sensibly specified and I found that the lower values worked well.

range of cartridges without too much difficulty, and I can think of no higher praise than to comment that while auditioning the 600LAC I was in no hurry to return to the familiar tones of my reference unit.

Tape Measures

Up-cock on the measurement front it seems. Many moons ago I reviewed the TCK 55 II from Sony and in doing so apparently discovered that said machine would not function to the best of its considerable ability with Sony tapes. Metal variety, anyway. Since then Sony have made a valiant effort to completely bury me in cassettes, on the principle that the one I had was a bad sample and all others will work.

After clambering out from under the little plastic boxes and clearing a space to work, I sat down to do a retest with some other examples of their metallic machinations. Lo and behold. Better frequency response and improved linearity. Suspicious editorial mind begins to dream up fiendish Japanese plots to "fix" results. Is Audiophile having its statistics interfered with?

A strong desire for impartiality, together with a fair helping of cowardice led me to pack off the TCK 55 II and all its little metal ammunition for independent testing once more. I neglected to tell the engineer concerned about the initial discrepancy on a particular tape type, just to see if he'd turn it up independently. Come to think of it, those Samurai warriors polishing their swords outside my door may have slipped my mind too — still I probably imagined it.

It would appear from a consideration of both our results that there was something wrong with the tape rather than the machine, after all. That probably clears Sony Tape Recorders Ltd off my back, but enrages Sony Cassette Production 1921 Ltd, or some other such edifice.

(Maybe it is no coincidence that everyone in my train compartment this morning was of oriental extraction and carried a long and curved thin brown paper parcel. Anyone know the Japanese for: "Me given up reviewing hi-fi, taken up knitting instead"?)

ETI

ETI SPECIAL OFFER!

3-wave band alarm clock radio at a price that won't alarm you.

£21.95

special magazine offer (inc p&p)



Every aspect of this beautifully designed electronic alarm clock radio has been carefully thought out. From the superb sound quality and immaculate white housing to the dark face which gives clear and easy reading of the time.

And at approximately £8 cheaper than conventional shop prices it also makes a superb gift.

WAKE TO MUSIC OFF THE ALARM

Unlike so many alarm clock radios you can actually choose how you want to be woken up by the insistent alarm tone or by soothing music.

And in case you feel the need for an extra few minutes in bed there's even a repeatable 9-minute snooze button.

Once the alarm or music has been activated you

can simply touch the snooze sensor for another undisturbed, warming 9-minutes under the covers before you are woken again.

Similarly, the music snooze sensor can be set before you get into bed so that you can be gently serenaded into sleep before the radio automatically cuts itself off.

NO FEAR OF POWER FAILURE

So many alarm clock radios let you down because they are totally dependent upon a constant supply of electric power.

But not this one.

The advanced Hanimex design has even incor-

porated a stand-by battery feature which automatically takes over to power the internal electronic clock and to keep the correct time and alarm setting accurate.

To: Modmags Ltd., (Sales Office)
145 Charing Cross Road,
London WC2H 0EE

I enclose £ for alarm clock radios.

Name

Address

PRIME COMPONENTS LOW PRICES

Also our micro chips are at micro prices. Don't be fooled by low prices. We do not offer for sale, surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT. Please refer to "Ordering Information" before ordering. Official orders from Schools, Colleges, Universities and Gov. Authorities accepted.

DTL	4040	99p	MEMORIES	CPUS
930	55p	4041	2114 300NS	275p
935	65p	4042	4116 200NS	300p
937	55p	4043	4116 150NS	395p
944	55p	4044	4315 (4Kx1) CMOS	795p
946	55p	4045	450NS	995p
957	55p	4046	BS14 4K (1Kx4) CMOS	795p
962	55p	4048	RAM450NS	
969	90p	4049		
		4050		
		4051		

7400	4052	69p	EPROMS	
7400	11p	4053	1702A	450p
7401	12p	4054	2708 45V NS	425p
7402	12p	4055	2716 5V 450 NS	995p
7403	13p	4056	2532 32K 450 NS	2995p
7404	17p	4059		
7409	18p	4060		
7410	16p	4063		
7412	18p	4066		
7513	28p	4067		
7420	16p	4068		
7430	18p	4071		
7432	25p	4070		
7440	16p	4071		
7442	68p	4072		
7448	75p	4073		
7473	32p	4076		
7474	32p	4077		
7475	40p	4078		
7480	35p	4081		
7492	50p	4085		
7493	45p	4086		
7496	45p	4089		
74121	35p	4093		
74123	45p	4094		
74154	90p	4096		
74157	55p	4098		
74162	45p	4099		
74125	50p	4501		
74195	100p	4503		
74196	100p	4504		
74283	140p	4505		
74290	120p	4506		
74365	90p	4507		
74366	90p	4508		
		4510		
		4512		
		4514		
		4515		
		4516		
		4518		
		4520		
		4521		
		4526		
		4527		
		4528		
		4529		
		4532		
		4533		
		4538		
		4543		
		4556		
		4559		
		4569		
		4572		
		4584		
		4585		
		4586		
		4590		
		45107		
		45123		
		45125		
		45132		
		45138		
		45151		
		45153		
		45155		
		45161		
		45163		
		45164		
		45168		
		45174		
		45175		
		45195		
		45221		
		45244		
		45251		
		45252		
		45253		
		45255		
		45257		
		45259		
		45263		
		45266		
		45273		
		45274		
		45275		
		45276		
		45277		
		45278		
		45279		
		45280		
		45281		
		45282		
		45283		
		45284		
		45285		
		45286		
		45287		
		45288		
		45289		
		45290		
		45291		
		45292		
		45293		
		45294		
		45295		
		45296		
		45297		
		45298		
		45299		

7400	4052	69p	EPROMS	
7400	11p	4053	1702A	450p
7401	12p	4054	2708 45V NS	425p
7402	12p	4055	2716 5V 450 NS	995p
7403	13p	4056	2532 32K 450 NS	2995p
7404	17p	4059		
7409	18p	4060		
7410	16p	4063		
7412	18p	4066		
7513	28p	4067		
7420	16p	4068		
7430	18p	4071		
7432	25p	4070		
7440	16p	4071		
7442	68p	4072		
7448	75p	4073		
7473	32p	4076		
7474	32p	4077		
7475	40p	4078		
7480	35p	4081		
7492	50p	4085		
7493	45p	4086		
7496	45p	4089		
74121	35p	4093		
74123	45p	4094		
74154	90p	4096		
74157	55p	4098		
74162	45p	4099		
74125	50p	4501		
74195	100p	4503		
74196	100p	4504		
74283	140p	4505		
74290	120p	4506		
74365	90p	4507		
74366	90p	4508		
		4510		
		4512		
		4514		
		4515		
		4516		
		4518		
		4520		
		4521		
		4526		
		4527		
		4528		
		4529		
		4532		
		4533		
		4538		
		4543		
		4556		
		4559		
		4569		
		4572		
		4584		
		4585		
		4586		
		4590		
		45107		
		45123		
		45125		
		45132		
		45138		
		45151		
		45153		
		45155		
		45161		
		45163		
		45164		
		45168		
		45174		
		45175		
		45195		
		45221		
		45244		
		45251		
		45252		
		45253		
		45255		
		45257		
		45259		
		45263		
		45266		
		45273		
		45274		
		45275		
		45276		
		45277		
		45278		
		45279		
		45280		
		45281		
		45282		
		45283		
		45284		
		45285		
		45286		
		45287		
		45288		
		45289		
		45290		
		45291		
		45292		
		45293		
		45294		
		45295		
		45296		
		45297		
		45298		
		45299		

7400	4052	69p	EPROMS	
7400	11p	4053	1702A	450p
7401	12p	4054	2708 45V NS	425p
7402	12p	4055	2716 5V 450 NS	995p
7403	13p	4056	2532 32K 450 NS	2995p
7404	17p	4059		
7409	18p	4060		
7410	16p	4063		
7412	18p	4066		
7513	28p	4067		
7420	16p	4068		
7430	18p	4071		
7432	25p	4070		
7440	16p	4071		
7442	68p	4072		
7448	75p	4073		
7473	32p	4076		
7474	32p	4077		
7475	40p	4078		
7480	35p	4081		
7492	50p	4085		
7493	45p	4086		
7496	45p	4089		
74121	35p	4093		
74123	45p	4094		
74154	90p	4096		
74157	55p	4098		
74162	45p	4099		
74125	50p	4501		
74195	100p	4503		
74196	100p	4504		
74283	140p	4505		
74290	120p	4506		
74365	90p	4507		
74366	90p	4508		
		4510		
		4512		
		4514		
		4515		
		4516		
		4518		
		4520		
		4521		
		4526		
		4527		
		4528		
		4529		
		4532		
		4533		
		4538		
		4543		
		4556		
		4559		
		4569		
		4572		
		4584		
		4585		
		4586		
		4590		
		45107		
		45123		
		45125		
		45132		
		45138		
		45151		
		45153		
		45155		
		45161		
		45163		
		45164		
		45168		
		45174		
		45175		
		45195		
		45221		
		45244		
		45251		
		45252		
		45253		
		45255		
		45257		
		45259		
		45263		
		45266		
		45273		
		45274		
		45275		
		45276		
		45277		
		45278		
		45279		
		45280		
		45281		
		45282		
		45283		
		45284		
		45285		
		45286		
		45287		
		45288		
		45289		
		45290		
		45291		
		45292		
		45293		
		45294		
		45295		</



Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS - CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD - DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMANS - HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS - KEF - LOWTHER - McKENZIE - MISSION - MONITOR AUDIO - MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS - RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNOY - VIDEOTONE - WHARFEDALE.

WILMSLOW AUDIO

SWAN WORKS, BANK SQUARE
WILMSLOW, CHESHIRE SK9 1HF

Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF
DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI
AND COMPLETE SPEAKERS.

POWERFETS

Some day all power transistors will be made this way!

	CHAN	VDS max V	ID max A	PDISS max W	RDSON Type Ω	Case	Price
BD512	P	60	1.5	10	1(3.5)	T0202	85p
BD522	N	60	1.5	10	2.5	T0202	80p
VMP4	N	60	2.0	25	2.0	380-50E	1250p
VN10KM	N	60	0.5	1.0	4.0	T092†	55p
VN64GA	N	60	12.5	80	0.3	T03	750p
VN67AF	N	60	2.0	15	2.0	T0202	75p
2SJ49	P	140	7.0	100	1.0	T03	395p
2SK134	N	140	7.0	100	1.0	T03	395p

†1/p protected four selection: VN/VM. 96-page Design Cat. 20p. Heat clips/sink T0202 12p, T092 8p, T03 35p.

MANUFACTURERS/DESIGNERS. We will be stocking Powerfets by IR, TI and Inter-sil as well as by Hitachi, ITT and Siliconix. We can advise you on applications and type selection, supply samples and quantities.

REMEMBER Powerfets need virtually no drive current, switch in nanoseconds, and are 2nd breakdown free, etc. etc.

CA3080E DAC08 DM2502 LM3900 LM3915 MC3401 NE529 NE555 SAD1024 SD532 TL081 TL082 2102 4001B 4011B 4013B 4016B 709 710 733 741 78L05/12	70p 250p 555p 43p 280p 30p 145p 25p 1050p 30p 29p 55p 80p 17p 17p 40p 40p 15p 25p 50p 18p 29p	HI-FI ON TWO CHIPS HA12017 (Preamp 0.001% distortion 83dB S/N in phono application) 99p HA1397 (Poweramp 20 watts in 8Ω) 0.02% distortion (typ) 195p Both with data and circuits. POWERFET AMPLIFIER. High power designs offering very low distor- tions. Complete component set. *80 watt (†THD 0.008%) £8.95 *120 watt (†THD 0.004%) £16.85 (with circuits) *into 8Ω †at all powers and all audio frequencies. LED VU/PPM METER Complete component set. Dis- plays positive and negative peak levels, and average levels simultaneously on 10 LEDs, with 3dB resolution. With 10 reds £6, with 7 green, 1 yellow and 2 red £6.40.	SCOPE TRACE DOUBLER P.C.B. Built. C/W shift, chan select, choprate controls and instructions. Useful dis- play from DC to 10MHz. Runs from 9v battery £9.95 VCA High quality design offers attenuation from 0dB to -90dB S/N 90dB, THD 0.01%, B.W. DC to 100KHz. Complete component set and circuit £2.50. Volt controlled pan-pot. Spec. as above. Complete component set and circuit. £3.25. 2μS ADC chip set (DAL08, DM2502, NE529) with data £9 HA1388 (Power amps. 18w from car battery). With data 195p.
--	--	---	---

30p post and packing. Mail order only to

J. W. RIMMER 148 Quarry Street
Liverpool L25 6HQ
Tel. 051-428 2651

Technical enquiries to: 367 Green Lanes, London N4 1DY
Telephone 01-800 6667

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

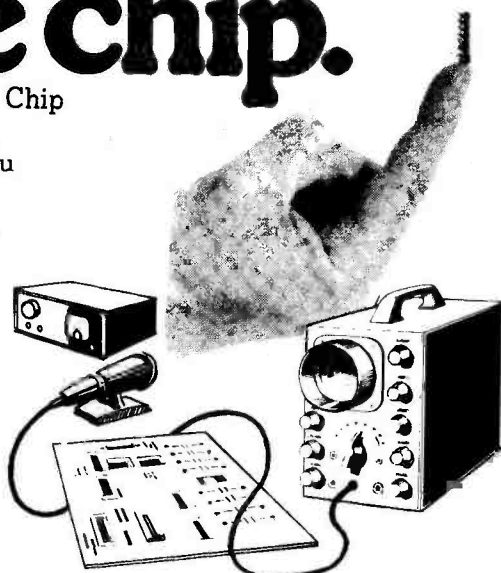- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



ENQUIRY Please send me FREE brochure on: <input type="checkbox"/> Pract. Electronics Name: <input type="text"/> Address: <input type="text"/> BLOCK CAPS PLEASE	I am interested in: <input type="checkbox"/> PRACTICAL ELECTRONICS <input type="checkbox"/> COMPUTER TECHNOLOGY <input type="checkbox"/> OTHER SUBJECTS (Please state your interest)	
	BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL 4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS. ETI/9/813	

RAVEN ON

Dave Raven of Metac Electronics chats about chips that answer back and discusses display developments.

Speech synthesis and voice recognition are techniques which are rapidly changing the interface between humans and their machines. Until now we have been content to read from a visual display or listen to pre-recorded non-intelligent voices which merely pass on information.

Today, however, it is possible to incorporate a human voice which is not a recording and can appear intelligent by varying its responses to the inputs received from humans or data produced by a machine. If, in the past, a colleague was seen listening or talking to a car, calculator, microwave oven or television set, he would most likely be advised to visit a psychiatrist at the earliest opportunity. But now thanks to new devices and computer software technologies, behaviour such as this will become commonplace.

Speak & Spell

The first consumer product which truly contains speech synthesis and which is on the market is Speak & Spell, developed by Texas Instruments. Working with a pair of 128-kilobyte read-only memories and a special version of TI's TMS1000 8-bit microcomputer, the silicon chip can produce a total of 200S of sound for a vocabulary of over 200 words. However, it is capable of accessing up to 2.1 megabytes of memory. Since the speech generator uses memory at a maximum rate of only 1200 bits per second, it could be designed to speak for as long as 30 minutes. The novelty value of Speak & Spell does not wear off quickly as may be imagined and from the reactions of my own young children, it was a clear favourite over other electronic games they have been shown. The word games and spelling tests produced a new angle for creating an interest from children in learning and I also found it quite compulsive myself.

Prior to the breakthrough by Texas Instruments in speech synthesis, earlier products which have surfaced over the last decade have been quite cumbersome and certainly more expensive. Now, with rapid advances taking place in large scale integrated circuits — both analogue and digital — and developments in signal processing, it is realistic to expect a flood of new consumer and industrialised products entering the markets.

Vocal Chips

The techniques used to design speech synthesis circuits are split into three different methods — formant synthesis, linear predictive coding and waveform digitisation with compression. Linear predictive coding is the technique chosen by Texas Instruments for their Speak & Spell Game. The chips which are incorporated represent an integrated circuit model of the vocal tract. Basic to the model is the linear predictive coding technique (LPC) which provides feedback values or coefficients for a digital lattice filter on the synthesiser chip. This linear filter mimics the major resonant modes of the vocal cavity in the human vocal tract. A microprocessor then performs the calculations to derive the filter coefficients. The third chip is a word-storage read-only memory that holds the speech parts broken into four parameters — voicing, pitch, amplitude and frequency. From this information a complex software algorithm manipulates the sound parameters to create the speech synthesis.

Swings And Roundabouts

There are advantages and disadvantages with each of the three speech synthesis techniques mentioned here since they can vary considerably in the quality of speech provided, the amount of data required to achieve acceptable quality and the cost of memory for storing speech data. The technique that is normally chosen depends upon the application for which it is required.

Products using formant synthesis are currently being included in a number of hobbyist computers, among them the TRS80 home computer and PET, as well as in medical and business applications.

During recent years probably one of the most misunderstood pieces of consumer electronic technology has been the liquid crystal display. I well remember an article appearing in ETI which quoted some very out of date information on the life of liquid crystal displays (LCD), and for years after, I experienced worried customers quoting this article back to me about the unreliable life-time of the display.

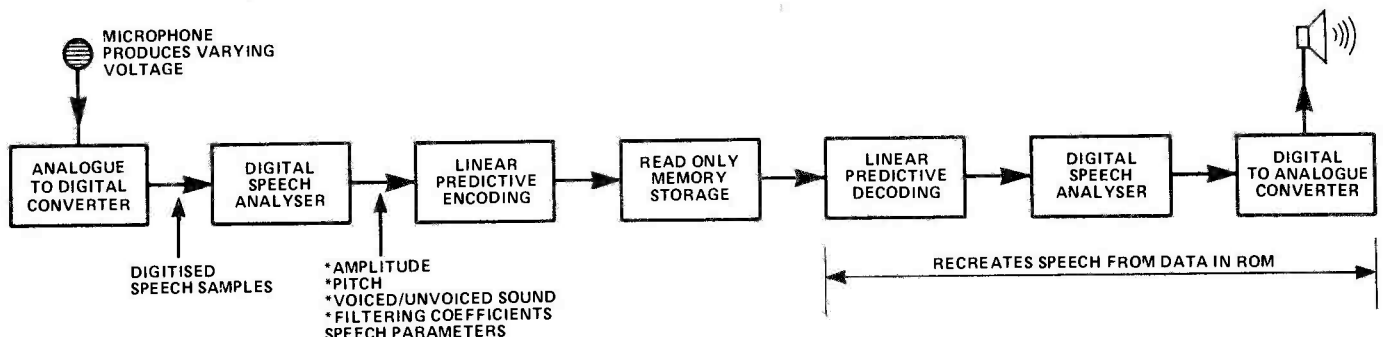


Fig.1. A block diagram showing the elements of a speech synthesiser chip.

They were of course referring to displays which appeared back in history during the very early seventies and it has been my experience that the LCD is probably one of the most reliable display forms currently available. I stuck my neck out in 1976 in an article published in ETI predicting that LCD would win the day over LED, (Light Emitting Diode) remember, and I propounded the reliability of this technique back in those dark days. Well, they say that the good always win and there is little doubt that LCDs have stood the test of time.

Physical Contact

Recent advances in the synthesis (that word keeps appearing this month) of new liquid crystalline materials have made it possible to manufacture plastic sealed LCDs having very long operating lives. This new technique permits economical production of large area displays and at the same time improves the performance of multiplexed addressing. Thus, these new displays are capable of handling an ever-increasing amount of information in alphanumeric or quasi-analogue form. One of the major problems facing designers in their attempts to increase the amount of information which can be displayed, is how to make physical contact with each segment of the display. This is also a problem for chip designers who are restricted by the amount of space for lead-outs. One solution which is getting around this difficulty is by reducing the number of outside contacts to a display, especially when the display has more than 40 separately addressable segments. This can be achieved by means of a technique known as time-multiplexed addressing, in which appropriate segments are connected together to form a group and are sequentially addressed by means of a

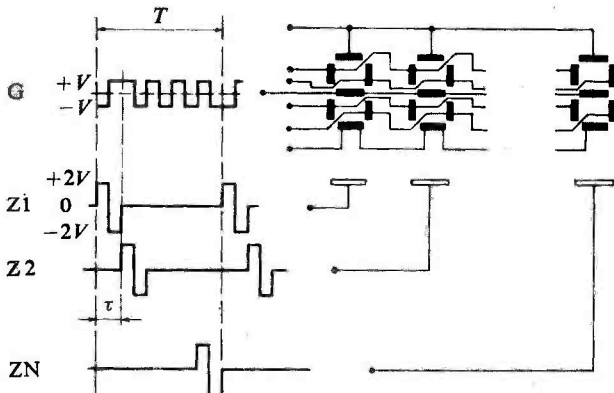


Fig.2. The principle of time-multiplexed operation. The selection interval for each digit, Z1 to ZN, is cyclically repeated at intervals of T. Only the driving signal for segment G is shown.

rear electrode consisting of several parts. Direct addressing of the LCD is presently employed in most watches and other measuring instruments which means there is a direct connection between each display element and a corresponding contact in the driving electronics, which is usually an integrated circuit. This addressing technique, whilst resulting in lots of connections, does have its advantages, since it affords much more freedom with respect to driving voltages and operating temperatures than do other addressing systems. For a directly addressing display it is easy to increase the driving voltage to obtain a display which is readable over a wide range of viewing angles.

ETI

CALCULATORS

SCIENTIFIC

***SPECIAL OFFER**
TEXAS T159 together with PC100C
(Complete as manufacturer's specifications)
£305.00

TEXAS/HP Accessories available	
*TEXAS T159 (Card prog 960 prog steps of 100 mem)	£156.50
*TEXAS T158 (Key prog 480 steps of 60 mem)	£80.00
*TEXAS PC100C (Printing Unit for T158/159)	£165.00
*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes/50 Prog Steps)	£26.00

For your Texas T158/59 Calculator
ELECTRICAL ENG. MODULE
LEISURE (GAMES) MODULE
STRUCTURAL ENG. MODULE
NOW AVAILABLE

*TEXAS TI PROGRAMMER (Hexadecimal Oct)	£46.50
*TEXAS T151/iii (10 mem 32 Prog Steps Stat/Sci)	£28.50
TEXAS T150 LCD (Sci/Stat. 2 Con Mem)	£23.00
TEXAS T125 LCD (Sci/Stats)	£17.00
TEXAS T53 (Sci. 32 Prog Steps-Coa Mem +80 Prog List Applications book)	£25.00

Make more of your
Texas T158/59 Calculator
MATH/UTILITIES MODULE

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

Module includes:

Prompter, Alpha Messages, Printer Formatting, Superplotter, Sorting, Data Arrays, Data Packing, Prime Factors, Hyperbolic Functions, Gamma / Factorial, Random Numbers, Normal Distribution, Interpolation, Roots of a Function, Minimax, Romberg Integration, Differential Equations, Discrete Fourier Series, Calculator Status, Variable Arithmetic, Module Check.	
*TEXAS T158 with Maths/Utilities	£90.00
*TEXAS T159 with Maths/Utilities	£186.50
*TEXAS T158 with Applied Statistics	£80.00
*TEXAS T159 with PC100C & Applied Statistics	£325.00

SUMMER SALE

*TEXAS T159 Calculator (complete as manufacturer's spec. master module, charger, etc.) PLUS statistics module and extra set of 40 Blank Prog. Cards with wallet, etc.
ONLY £180

NEW TEXAS T158C*

*Continuous program facility on all 480 Program steps/60 mem even when calculator switched off	£78.50
*TEXAS T158C (complete plus Applied Stats. Module)	£98.00
*TEXAS T158C + PC100C	£228.00

FREE while stocks last with every purchase of HP 32E or HP 33E

BATTERY HOLDER WITH RECHARGABLE BATTERY** Normally costs £10.38	
*HP33E (8 mem Pro Sci/Stand)	£50.75
*HP33C (as above but con. mem.)	£68.50
*HP32E (advanced SC1 with stand)	£40.50

*HP34C (Sci Prog 20 Mem)	£85.00
*HP67A (K Prog 224 Steps 26 Mem)	£173.00
*HP97A (Fully prog with Printer)	£384.35
HP41C (the newest calculator from HP)	£173.48
HP41C Card Reader/Printer etc. Modules	Now in stock
CASIO FX8100 (10 dig Sci/Sta. Stop Watch / Alarm)	£27.73
CASIO FX501P (Sci. LCD Prog. 128 Steps 11 Mem)	£47.50
CASIO FX502P (Sci. LCD Prog 256 Steps. 22 Mem)	£65.00

LEXICON LANGUAGE TRANSLATOR

*With 6 Lang. Module — French / Italian / German / Spanish etc.)	£120.00
Ring Translator	£120.00

NOW IT'S YOU AGAINST 'COMPUTERS'

CHESS CHALLENGER '77' (7 Levels of game)	£78.50
CHESS CHALLENGER 'VOICE' (10 Levels — beginner to Master Plus) The strongest Prog yet in this series — twice as fast as the other challengers. A microprocessor with 128,000 to 160,000 bits of read only Mem. Over 8000 bits of Random Access Mem. Teaches opening & end game solutions. Plays against itself. Solves book problems etc — and in addition IT SPEAKS. Complete with Deluxe playboard, hand carved men with magnetised base plus Deluxe carry case	£170.00
SARGON. The most advanced chess game yet with ad on module availability for other games (Our price inc. FREE rechargeable battery pack)	£242.60
Super System 3 (as recommended by ETI)	£134.75

Alarm TV games £98.50 inc. VAT

LEARNING AIDS

TEXAS DATAMAN (Number Games-Table learning etc. 5/10 yrs)	£18.00
TEXAS SPELLING B (Spelling Games ideal 5/10 years)	£22.50
TEXAS SPEAK AND SPELL (for older children 8/13 years)	£39.95

IDEAL FOR STUDENTS

ALL WITH LCD DISPLAY

TEXAS T120 (Jun Sci + Con Mem)	£13.00
TEXAS T135 (Sci/Stat C Mem)	£17.00
TEXAS T138 (Sci/Con Mem-Pola Rec Cony Dec Deg conv / Deg Min Sec)	£19.95

GOODS FULLY GUARANTEED PRICES EXCLUDE VAT (ADD 15%)

Company / Hospital and Government orders accepted by phone

Barclaycard / Visa / Access accepted by phone

TEL. 01-455 9823

EXPORT ORDERS WELCOMED

Air Freight / Air Post Delivery

Quotations on request

MOUNTAINDENE

22 Cowper St., London, EC2

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation is even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built-in static timing light, 4-way function light and security changeover switch. Will work all over the country.

Fits all 12v negative earth vehicles with coil/distributor ignition up to 8 cylinders.

The kit comprises of: 12V 400mA/1.5A D.C. Die pressed case. Ready to fit, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. ET1/9
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

(inc. V.A.T. and P.P.)

QUANTITY REQ'D.

I enclose cheque/P.O. for

X5KIT £16.95

ACCESS OR BARCLAY CARD No.

£
Cheque No.

Send SAE if brochure only required.

QUESTION?

1. Is your hobby home computing or electronics?
2. Do you understand the application of IC's, Transistors, Diodes, etc?
3. Have you used or applied analogue or digital techniques?
4. Are you applying TTL Logic to your home computer?
5. Are you programming your home computer using simple software techniques?

If the answer is YES to any of these questions then why not consider turning your hobby into a career — applying your knowledge to servicing electronic equipment ranging from basic terminals and data processing machines through to advanced micro-processor systems.

We will train you through to advanced technology at the company training school, fitting the individual in at their own level.

We have vacancies over the whole of the U.K. especially in the London area, with the successful applicants working from home, usually in a radius of no more than 60-70 miles.


We supply all tools and test equipment, plus a company car which is available for private use.

If you are interested, then why not contact **Mr. C. Marklew on 0249 813771** to discuss your own career opportunities in confidence, or write to:

KODE SERVICES LIMITED

Station Road, Calne, Wiltshire

HAWK Interlocking Touch Switch Systems

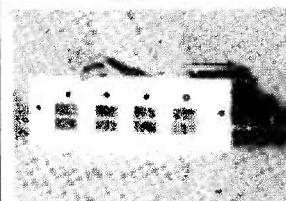

Here is the 4 channel system complete; showing the front panel, the circuitry, and the ribbon cable connecting the two.

Have you ever made a quality project, for which you needed interlocking switches, but all that was available was an unreliable, unsightly and electrically noisy mechanical switch?

You can now get an **electronic switch, touch-operated**, with L.E.D. displays to indicate which channel has been selected, and incorporating totally reliable solid state relays to perform the switching.

There are three options available: 2 channel; 4 channel; and 6 channel. On each channel there are 2 sets of relay contacts acting in parallel, so that stereo signals may be switched — for example, when selecting between the tuner, deck, tape, or auxiliary inputs to an amplifier using the 4 channel unit.

The units are supplied as easy to assemble kits, every kit containing:—

- ★ ALL the necessary components, including a high quality p.c.b. and I.C. sockets
 - ★ An attractive ready assembled front panel — comprising wipe clean stainless steel touch plates on a heat resistant white plastic base, which is pre-drilled for easy mounting on the front panel of your project; complete with
 - ★ LEDs above each switch plate to indicate which channel has been selected (the brightness of these may be adjusted)
 - ★ Complete easy to follow assembly instructions
 - ★ Full technical information
- Some of the special features are:—
- ★ Operation from a single supply rail, from 3V-18V
 - ★ Current consumption only 20mA
 - ★ It is IMPOSSIBLE to switch on more than one channel at a time — if more than one switch plate is touched either none or only one channel will be selected
 - ★ EXTREMELY long life — far longer than that of mechanical switches
 - ★ The HAWKTM range are the ONLY interlocking touch switch systems that the home enthusiast can buy as complete systems

Please note: the solid state relays used are C.M.O.S. 4016 and the limits of these devices must be observed.

Please send to M _____ at (address) _____

Number _____ 2 channel units @ £3.99 ea. Add 25p _____

Number _____ 4 channel units @ £5.99 ea. P/P per _____

Number _____ 6 channel units @ £7.99 ea. _____

Total remittance enclosed _____ Cheque/P.O. No. _____

OR Please send me the technical information only (enclose s a e.) ☐ tick box

DOVE ELECTRONICS TEL: BRISTOL (0272) 48401


4A Harcourt Road, Redland, Bristol BS6 7RG

**SPECIAL
OFFER**



MITRAD CHRONO QUARTZ WATCH/TIMER

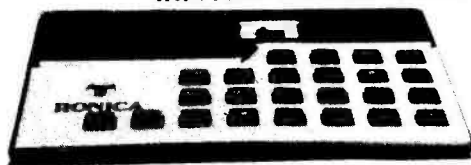Multi-function watch and stop-watch timer **ONLY £20.95 (+ p&p)**
with **FREE** Slimline 'Credit Card' Calculator (our usual price £7.95)



MITRAD CHRONO

Unique neckband/lapel/pocket watch and timer with large easy-to-read liquid crystal display.

1. WATCH

Shows the time in hours, minutes and seconds. Press a button and it shows the day, date and month.

2. TIMER

Accurate to 1/100th second stop-watch function. Shows elapsed time in hours, minutes, seconds and 1/100ths of seconds. Also records lap times in the middle of timing the overall event. Maximum capacity 24 hrs.

Overall dimensions of the timer are approximately 3 1/8 x 2 1/8 x 1 1/16in (79 x 66 x 17mm) so that it fits comfortably into the palm of the hand with the lap/reset and start/stop push buttons perfectly positioned for operation by thumb and forefinger. In tough, impact resistant, black case.

GUARANTEED. MONEY BACK IF NOT DELIGHTED

The Mitrad Chrono Quartz Timer is fully guaranteed for 1 year. And if you are not completely satisfied, just send it back within 10 days and we'll refund your money. Instructions for use included.

SLIMLINE 'CREDIT CARD' CALCULATOR

Hardly any bigger than an ordinary credit card. Has liquid crystal display; addition, subtraction, multiplication, division, square root and memory facilities.

Usually £7.95 but ABSOLUTELY FREE
with every Mitrad Chrono Quartz Timer

TRADE DISCOUNT

Trade discount is available for quantity orders of the Quartz Timer only. Prices are:

5-10	11-15	16-50
£13.95	£13.10	£12.65

Prices are exclusive of VAT (15%) which should be added. Post and packing for all trade orders is £1.50, which includes insurance. Please do not use the coupon for trade orders.



MITRAD
68-70 High Street,
Kettering,
Northants.
Tel: 0536 522024

MITRAD To MITRAD, 68-70 High Street,
Kettering, Northants.

Please send me: QTY Price inc VAT & £1.05 p&h

MITRAD Chrono Quartz Timer

Total value of my order £

I enclose my cheque/postal order

Or debit my Access Card No.

SIGNATURE

NAME (Mr/Mrs/Ms)

ADDRESS

Allow 28 days for delivery.

BLOCK LETTERS PLEASE

DESIGNER'S NOTEBOOK

ETI project editor Ray Marston devotes this month's 'Notebook' to the rather unglamorous but vital subject of passive attenuators.

One of the most important types of artillery in the design engineer's armoury of 'vital weapons' is the apparently simple passive circuit known as the 'attenuator'. Naturally, these apparently simple weapons are full of nasty little surprises and have a tendency to explode in the face of the unwary designer. This month's 'Notebook' is devoted to a brief discussion of the subject.

Attenuators

Attenuators are used to reduce an awkward value input or output signal to a lower and more convenient level. The simplest example of a practical attenuator is the 'pot' circuit of Fig.1, which may be used as a volume control in an audio system or as an output level control in a simple audio generator, etc.

The input signal to the pot attenuator is connected across the total resistance chain and the output is taken from the pot slider. Note that the pot effectively comprises an upper ($R1$) and a lower ($R2$) resistive arm, thus forming a basic 'L'-type attenuator and that the degree of attenuation is determined by the ratio of lower arm resistance divided by the total resistance.

The precise amount of attenuation provided by a pot is generally of little importance and the control is usually left uncalibrated. If a precise amount of attenuation is required, a simple switched potential divider network of the type shown in Fig.2 may be used. It is important to note, however, that this circuit is designed to feed into an *infinite* impedance, or at least one that is very large compared to the total resistance of the divider chain.

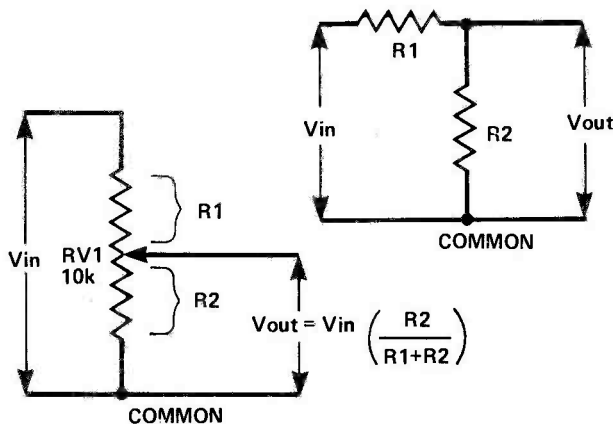


Fig.1 A simple 'pot' attenuator, as used for a volume control or an uncalibrated output level control (left) is a common version of the 'L' attenuator (right).

Design Tips

The first step in designing an attenuator of the Fig.2 type is to decide what its input impedance or total resistance is to be. Next, the values of the individual resistors are determined. Here the design is carried out in a simple sequence of logical steps, there being as many steps as there are attenuator switched positions. In each of these steps, the circuit is considered to consist of an upper and a lower half only. An example will help clarify matters.

Assume (as in our example) that the total resistance is to be 10k and that two attenuation positions (excluding unity) are required and are $\div 10$ and $\div 100$. The values for the greatest amount of attenuation are always determined first, so for $\div 100$ the lowest arm must contain 1/100th of the total resistance, or 100R. This gives the value for $R3$ and leaves the remaining 9900R in the 'upper' ($R1 + R2$) arm.

The values for the $\div 10$ position are next calculated and it is found that 1k Ω is needed for the 'lower' arm. In this case, however, the 'lower' arm consists of $R2 + R3$, but as $R3$ is already known to be 100R, $R2$ must be 1k Ω - 100R = 900R. The upper arm, $R1$, must obviously contain the remaining 9k Ω of the 10k chain.

This simple design procedure may be expanded up to give as many attenuator steps as are required for a particular application.

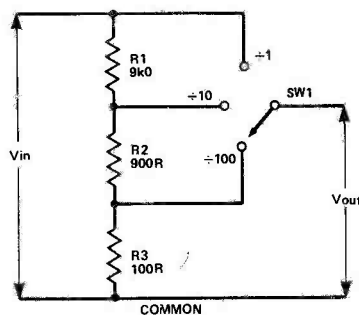


Fig.2 The method of designing this simple switched attenuator is explained in the text.

It should be noted that the simple attenuator circuit of Fig.2 is only accurate at low frequencies or when moderately low values of resistance are used. At high frequencies, stray capacitance will shunt the values of all resistors and may significantly reduce their values and thus the accuracy of the attenuator. This effect is particularly acute when high value resistors are used: a mere 2pF of stray capacitance represents a reactance of about 800k at 100 kHz and will have a very significant shunting effect on any resistor with a value greater than a few tens of kilohms.

Compensation

This problem can readily be overcome by shunting all resistors with correctly chosen values of capacitance, as shown in Fig.3.

Here, each resistor of the chain is shunted with a fixed capacitor, the reactance values of capacitance being in the same ratios as the resistive arms of the attenuator. The highest reactance (smallest capacitance) is connected to the largest resistor and typically has a value in the range 15 to 50pF, the value being large enough to 'swamp' strays but small enough to present an acceptably high impedance to input signals.

This 'compensated' type of attenuator is invariably used in 'scopes' and various other types of high frequency test gear, as shown in the typical circuits of Figs.4 and 5. Once again, note that the compensated attenuator is intended to feed into a high impedance load.

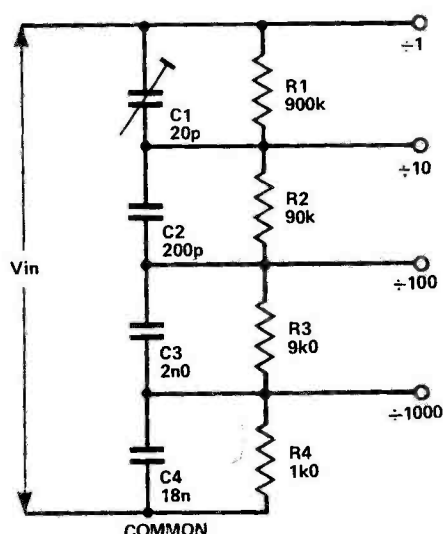


Fig.3 A method of providing frequency compensation (to give a wide frequency response) to a simple attenuator network.

Pot Pitfalls

At this point in our discussion it may have dawned on you that, because of the effects of stray capacitance, there can be certain pitfalls in using pots in some types of circuit. Suppose, for example, that you have designed an audio amplifier with a beautifully flat frequency response but have, in a moment of madness, fitted it with a 500k volume control. You will (hopefully) not be unduly surprised to consequently find that, at low volume settings, stray capacitance of a few picofarads across the upper arm of the pot causes the amplifiers treble response to be boosted by several dB at 12 kHz or so!

Again, suppose that you have designed a superb LF sine/square generator which produces square waves with rise and fall times of a mere 50 nS or so, but have fitted the beast with a simple 10k pot as an output level control. Naturally, you will not be surprised to find that the few picofarads of strays across the upper arm of the pot acts as a reactance of only a couple of thousand ohms to your fast rise and fall time signals and consequently causes your square waves to appear incredibly 'spiky' at low amplitude settings.

Both of the above problems can be solved or minimised by using pots with sensible low resistance values, bearing in mind the effects of strays at the operating frequencies in question.

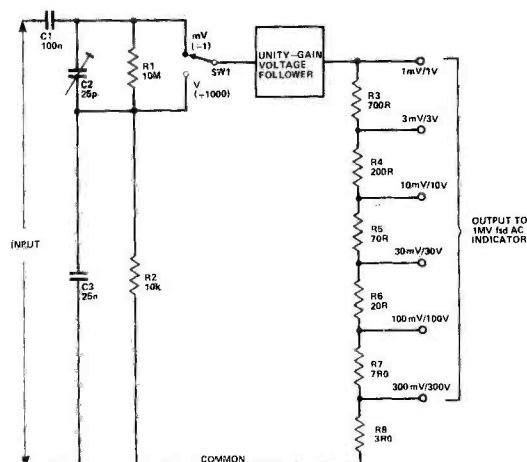


Fig.5 Typical attenuator sections of an AC millivoltmeter;

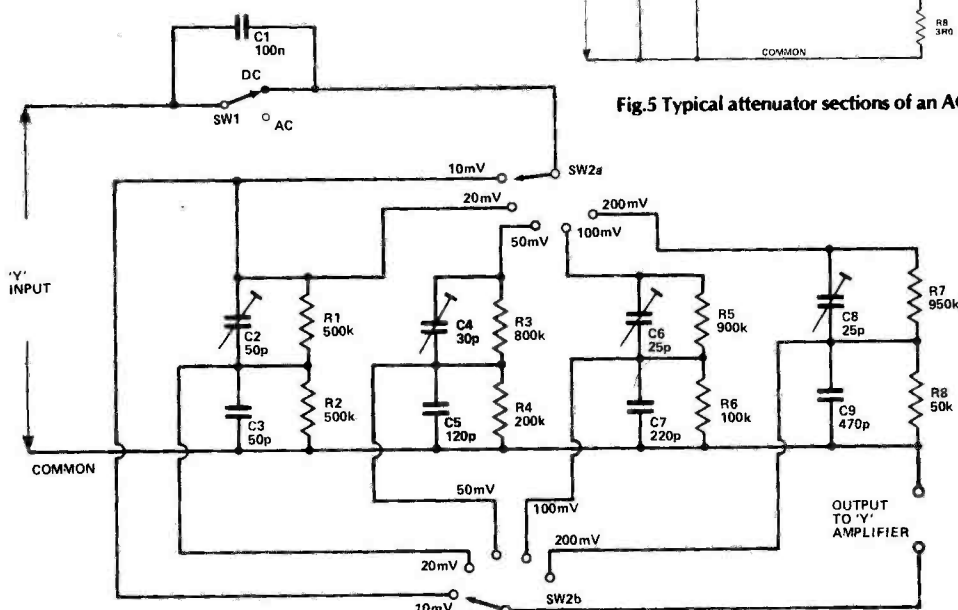


Fig.4 Section of a typical 'scope' Y amplifier attenuator.

Matched-Resistance Attenuators

Often, an attenuator is needed to feed into and/or from a fixed load of some kind, in which case the simple potential divider types of circuit discussed above are of little use. Instead, one of the many versions of the so-called matched-resistance attenuator must be used. Two of the most popular attenuators of this type are shown in Fig.6, together with their basic design formulae. Note that these formulae are valid only when the attenuators are correctly terminated at each end.

The 'T'-type attenuator is a perfectly simple design and several sections can readily be cascaded to form variable attenuator networks, as shown in the practical circuit of Fig.7. Here, the attenuation can be varied from 0 dB to 60 dB in 20 dB steps by switching individual sections into or out of the circuit.

The π attenuator sections cannot be directly cascaded, as is made clear in Fig.8. Nevertheless, sections can be cascaded in modified form to produce a ladder attenuator network, the most popular of all attenuator types.

Looking at Fig.8, you can see that if three individual π sections are wired in cascade (Fig.8a) their adjacent R2 sections connect in parallel to give an impedance of $P/2$ (Fig.8b) while the two R2 end sections have impedances of P . If an external load, R_L , is simply switched to the different outputs of the cascaded π attenuator sections (Fig.8c) the load will clearly see impedances of roughly half of the correct value and so be severely mismatched. To put things right, the formula for the component values of the ladder network of Fig.8c are re-jigged as shown.

The ladder attenuator of Fig.8c is very widely used in AF and RF signal generators. Figure 9 shows the practical circuit of a fully variable 600R attenuator that can be used in sine/square generators, etc. The odd resistor values (correct within 2%) can be made up by wiring pairs of resistors in series or parallel.

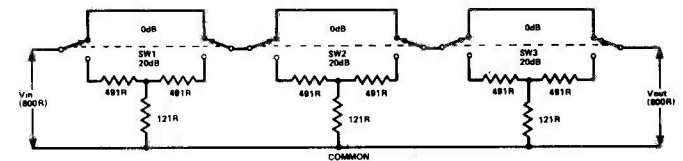


Fig.7 Three identical 20 dB 600R 'T' attenuators cascaded to make a 0-60 dB switched attenuator unit.



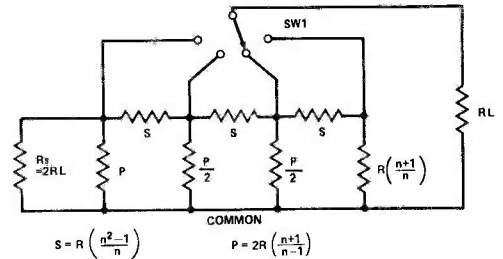
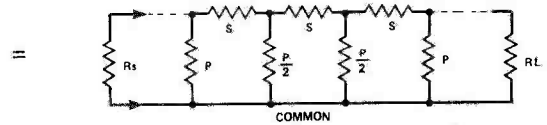
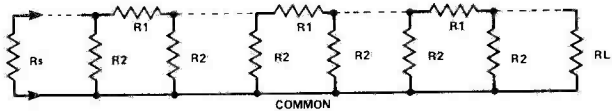


Fig.8 The ladder attenuator (c) is a development of the basic π attenuator (a and b).

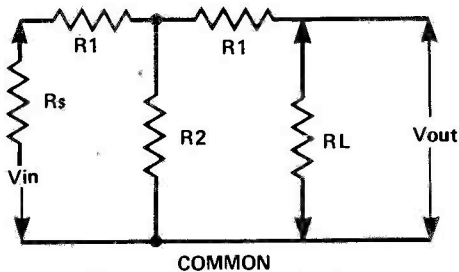

'T' - TYPE ATTENUATOR
 $R1 = R \left(\frac{n-1}{n+1} \right)$ $R2 = R \left(\frac{2n}{n^2-1} \right)$

Fig.6 Two popular types of matched-resistance attenuator.

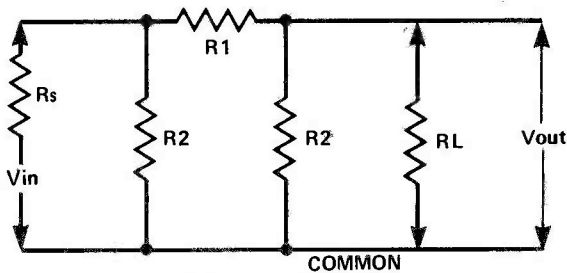

' π ' - TYPE ATTENUATOR
 $R1 = R \left(\frac{n^2-1}{2n} \right)$ $R2 = R \left(\frac{n+1}{n-1} \right)$

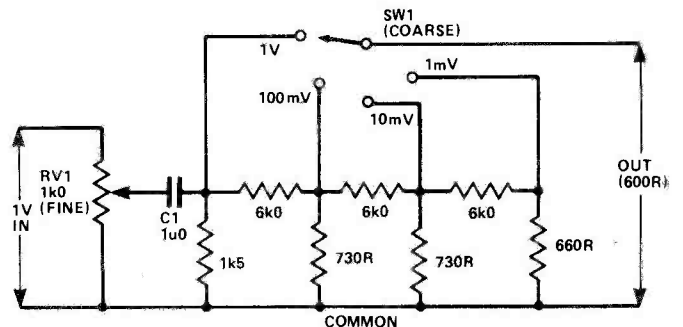


Fig.9 Practical 600R output attenuator network for a modern sine/square generator. RV1 gives fine control. SW2 gives coarse control.

Greenbank

Greenbank Electronics
(Dept T9E) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel. 051-645 3391)




TERMS. VAT. CWO. Cheques etc payable to Greenbank Electronics and crossed.
Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 35p
(+5p VAT = 35p) per order. Export: NO VAT but add 35p (Eire). 75p (Europe) and
£2.50 elsewhere. Access. Barclaycard. Visa. telephoned orders accepted.
(Polys. universities. gov't depts. etc can telephone their orders for immediate
despatch on account.)



UV EPROM ERASERS

UV 140, UV 141

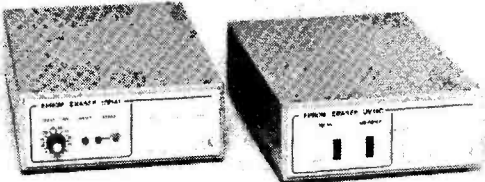

Two easy to use units designed for both the professional and amateur UV-prom user

Features

- Can erase up to 14 proms.
- Special short wave ultraviolet beam
- Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life)
- Sliding tray carries proms on conductive foam
- Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
- "Mains On" and "Tube On" indicators
- Smart textured case
- Complete instructions supplied

Supplied complete with mains plug and flex

Model UV141. Price £77.70

Also available without timer as

Model UV140. Price £61.20

Tex Microsystems "EPROM" UV ERASER



A low cost alternative to the above erasers (UV 140/141) claimed by the manufacturer to erase up to 32 chips in 15-30 mins. This is the cheapest eraser we have seen. The unit has no timer, power switch or safety interlock switch. The user places up to 32 chips into loose conducting foam in the erasure tray (16 along the base, 8 on each side). The chips are held in place by the UV tube which sits in the tray. (Unlike the UV 140/141, no special precautions have been taken to prevent the seepage of UV light, but the manufacturers state that "Incident light from this device is quite safe at distances above 12 inches".)

EPROMT Eraser: Price £35.56

5204/2708 PROGRAMMING SERVICE: £7.50 each prom. (Price does not include prom, we accept handwritten / typed source code — must be hexadecimal).

PROM WASHING SERVICE: 50p each prom

NEW COMPUTER BOARDS

The following computer boards have been added to the range for use with the Z80 (114x203mm fibreglass with gold plated edge connector).

- IP2 8 line opto isolated input board **£9.40**
- OP2 8 line relay output board **£9.40**
- SIO RS232 serial interface board **£9.40**
- MXD2 16K dynamic ram board **£9.40**

SPECIAL OFFER

(Subject to stocks)

No monthly accounts for these prices:

- 2114 (450ns) — 1Kx4 **£2.99 £22.40**
- 2708 (450ns) — 1Kx8 **£5.25 £39.60**
- 2516/2716 (450ns) — 2Kx8 single 5v **£12.00 £88.00**
- 4116 (250ns) — 16Kx1 Dynamic **£3.99 £30.40**

CMOS

These cut prices for Amateur Users and Export. Note: industrial users — quantity prices available. Mostly Motorola. RCA

4000 18p	4042 80p	4095 £1.97	4110 £3.55	4531 £1.45
4001 25p	4043 90p	4096 £1.97	4111 £10.72	4532 £1.30
4002 25p	4044 90p	4097 £5.98	4112VP £1.93	4534 £5.60
4006 95p	4045 £2.63	4098 £1.92	4115V £5.24	4536 £3.69
4007 18p	4046 £1.10	4099 £2.00	4122 £5.66	4537 £26.10
4008 80p	4047 £1.71	4100 £1.92	4133 £12.30	4538 £1.20
4009 40p	4048 77p	4101 £1.69	4135V £5.40	4539 97p
4010 50p	4049 45p	4102 £3.67	4137 £3.81	4541 £1.19
4011 25p	4050 49p	4103 £3.67	4138 £3.81	4543 £1.80
4012 18p	4051 80p	4104 £1.85	4141 £3.33	4543 £4.38
4013 50p	4052 80p	4105 £1.85	4142 £4.41	4552 £14.85
4014 84p	4053 80p	4106 92p	4143VP £1.20	4553 £4.50
4015 84p	4054 £2.18	4107 £1.28	4144VP £1.20	4554 £1.38
4016 45p	4055 £2.55	4108 £7.54	4501 £6.95	4555 78p
4017 80p	4056 £2.55	4109 £1.28	4501 25p	4556 25p
4018 89p	4059 £9.23	4110 £3.00	4502 £3.06	4557 £3.06
4019 45p	4060 £2.10	4114 £1.77	4503 70p	4558 £1.25
4020 90p	4062 £10.00	4160 £1.54	4505 £5.71	4559 £4.38
4021 £1.10	4063 £1.90	4161 £1.54	4506 50p	4560 £2.50
4022 £1.00	4066 55p	4162 £1.54	4507 55p	4561 81p
4023 27p	4067 £7.21	4163 £1.54	4508 £2.90	4562 £5.60
4024 50p	4068 27p	4164 £1.54	4510 99p	4563 £1.50
4025 27p	4069 27p	4165 £1.54	4511 £1.50	4568 £2.38
4026 £3.25	4070 30p	4182 £1.90	4512 80p	4569 £2.50
4027 50p	4071 25p	4182 £2.41	4514 25p	4572 40p
4028 84p	4072 25p	4183 £2.41	4515 30p	4580 £4.77
4029 99p	4073 25p	4184 £3.27	4516 £1.10	4581 £2.62
4030 72p	4075 25p	4208 £7.84	4517 £4.46	4582 £1.14
4031 £4.31	4076 £1.07	4257 £2.31	4518 £4.46	4583 90p
4032 £2.63	4077 25p	4180 90p	4519 80p	4584 90p
4033 £2.63	4078 25p	4161 90p	4520 £1.00	4585 £1.27
4034 £2.00	4081 25p	4162 90p	4521 £2.50	4597 £2.44
4035 £1.10	4082 25p	4163 90p	4522 £1.11	4598 £2.98
4037 £1.99	4085 £1.35	4174 90p	4526 £1.08	4599 £8.95
4038 £1.20	4086 £1.35	4175 £1.15	4527 £1.30	4700 £1.75
4039 £2.78	4088 £1.91	4176 £1.15	4528 £1.30	
4040 £1.00	4089 £1.91	4177 £1.15	4529 £1.30	
4041 £1.59	4094 £2.50	4178 £1.15	4530 70p	

74C

74C00 28p	74C75 57p	74C163 £1.15	74C303 57p	74C925 £5.01
74C02 28p	74C83 £1.34	74C164 £1.08	74C304 57p	74C926 £5.01
74C04 28p	74C86 £1.34	74C165 £1.08	74C305 57p	74C927 £5.01
74C06 28p	74C89 £4.62	74C173 93p	74C306 57p	74C928 £5.01
74C08 28p	74C90 89p	74C174 93p	74C307 57p	74C929 £17.90
74C10 28p	74C93 89p	74C175 93p	74C308 57p	74C930 £17.90
74C11 28p	74C95 £1.08	74C192 £1.15	74C309 £1.69	80C95 85p
74C14 28p	74C107 £1.27	74C193 £1.15	74C310 £1.69	80C96 92p
74C16 28p	74C150 £3.81	74C194 £1.15	74C311 £1.69	80C97 92p
74C18 28p	74C151 £2.95	74C211 £1.41	74C312 £1.45	80C98 92p
74C20 28p	74C152 £3.81	74C245 £2.98	74C315 £1.15	82C19 £6.20
74C22 28p	74C153 £3.81	74C245 £2.98	74C316 £1.15	82C29 £2.90
74C24 28p	74C154 £3.81	74C245 £2.98	74C317 £1.15	82C30 £2.90
74C26 28p	74C155 £3.81	74C245 £2.98	74C318 £1.15	82C31 £2.90
74C28 28p	74C156 £3.81	74C245 £2.98	74C319 £1.15	82C32 £2.90
74C30 28p	74C157 £2.29	74C245 £2.98	74C320 £1.15	82C33 £2.90
74C32 28p	74C158 £2.29	74C245 £2.98	74C321 £1.15	82C34 £2.90
74C34 28p	74C159 £2.29	74C245 £2.98	74C322 £1.15	82C35 £2.90
74C36 28p	74C160 £1.49	74C245 £2.98	74C323 £1.15	82C36 £2.90
74C38 28p	74C161 £1.49	74C245 £2.98	74C324 £1.15	82C37 £2.90
74C40 28p	74C162 £1.15	74C245 £2.98	74C325 £1.15	82C38 £2.90

MODULATORS

- UM111: E36 UHF Ch-36 Vision Modulator £2.50
- UM121: UHF Ch-36 Vision Modulator wide bandwidth (for computers etc) £4.70
- UM123: FM Sound Sub-carrier Modulator £2.50

SWITCH

MODE PSUs


- AC 5221S 5V/10A £69.90
- AC 5221S 5V/5A 12V/1A — 12V/1A — £69.90
- AC 5421S 5V/20A £99.20
- AC 5421S 5V/10A 12V/2A — 12V/2A — £126.50



MICROPROCESSORS

COMPUTER BOARDS		6800 MPU	6800	6805	INTERFACE
114 x 203 mm through-hole		6800 MPU		8115/95 5/7.8	£1.40
Gold plated edge connector.		6800 MPU		£2.75	50p
Buffered SC/MPI CPU £9.40		6810 (128 x 8 RAM)		75492	92p
SC/MPI Protoboard £9.40		6810 (128 x 8 RAM)		75492	£3.95
280 CPU card £9.40		6820, 6821 PA		£3.08	£2.64
VDU 'A' unit £9.90		5805 ACIA		8176/8178	£2.64
VDU 'B' x 4 £9.90		MC6880		IL74	48p
VDU 'G' x three £9.40					
EPROM Programmer		6502		CRT Controller:UARTs	
[27084] £9.40		6520 PS2 PA		Thompson CSO F9 1963/64	£11.50
4k PROM board [52044]		6522		AV-5-1013 UART FR 1602	£4.00
£9.40		6522		AV-5-1013A	£4.70
				AV-5-1014A	£5.60
				AV-5-1015	£5.60
8k PROM board [27084]		CMOS		CH-10A1	KEYBOARD
£9.40		COSMAC CDP 1802E			
2k RAM board [10124] 1k		COSMAC CDP 1802C		CHAR. GEN. KEYBOARD	
2k RAM board [10124] 1k		CDP 1864		ENCODER	
£9.40				MM 66760	£9.75
8k RAM board [21144] 1k		STATICS (Mostly 450ns)		RD 3025 (50w Uppercase)	£16.90
£9.40		2101-256 x 4		RD 3678 CAB/ENF	£4.27
8k RAM board [21144] 1k		2112-256 x 4		AV-2376	£9.75
8k RAM board [21144] 1k		2112-256 x 4			
8k RAM board [21144] 1k		2112-256 x 4			
8k RAM board [21144] 1k		2112-256 x 4			
8k RAM board [21144] 1k		2112-256 x 4			

MONITORS MONITORS MONITORS

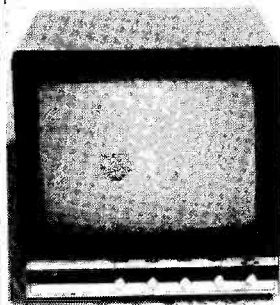

Uncased from 3" to 12"
Cased from 5" to 20"

Semi professional or
professional available
from stock.

Monitor PCB's including
Transformers and Tubes
also in stock.

Phone or write for
details.

CROFTON ELECTRONICS

Crofton Electronics Limited
35 Grosvenor Road, Twickenham, Middx.
Tel: 01 891 1513

HAND HELD GAMES

Supersonic Mastermind	£21.00
Galaxy Invaders	£22.95
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
"DIGITS (like Mastermind)	£14.95

ALL GAMES HAVE SOUND EFFECTS EXCEPT

ATARI video computer £138

SPACE INVADERS CART	£29.95
STAR CHESS T.V. Game	£63.35
DATABASE Prog. T.V. Game	
NEW £89.95	
CHESSMATE 8 Level	NEW £59.95
CHESS CHALLENGER 7	£99.00
CHESS CHALLENGER 10	£160.00
VOICE CHALLENGER	£219.00
CHECKER CHALLENGER 2	£54.00
CHECKER CHALLENGER 4	£90.00
ZODIAC Astrology Computer	
NEW £29.95	
Snooze Alarm	£14.90
EL-MAC 5MHz Scope	£139.90
RADAT 10MHz Scope	£169.00

The latest from the U.S.A. PINBALL WIZARD

★ Still available ★
Featured in Nov. issue of E.T.I
Home TV Game — B.W. Kit
Basic Kit **£28.90**
Contains everything except box and controls
Box & Controls — **£6.50**. Mains Adaptor — **£3.90**
Play 7 games with 4 options on each game
4 Pinball games 2-Basket, 1-Breakout
Versatile car alarm kit **£18.90**
See review in Hobby Electronics November
CHROMA CHIME 24 tune door chimes kit **£10.75** Built **£15.95**
C.B. Aerials and Accessories

COMPUTERS — Home, Business etc.

PET 8K	£458.85
PET 16K	£573.85
SORCERER 16K	£861.35
SORCERER 32K	£918.85
SUPERBOARD II 4K	£180.00
UK 101 Kit 4K	£226.85
Built 4K	£286.35
TRS80 Level 2 16K	£409.40
5 1/4" Floppy Drive	£271.40
Dual Drive	£506.00
NASCOM 2 Kit	£339.25
HEATH WH89	£1,805.00
HEATH WH14 Printer	£586.50
Softy Kit	£115.00
Softy Built	£138.00
Intelligent EPROM Programmer	
Sharp Software	
PRINTERS DISCS . BOOKS	

S.a.e. Enquiries. Please allow up to 21 days for delivery. All prices inc. of VAT.



N.I.C.

61 BROAD LANE, LONDON N.15 4DJ
Day 01-808 0377; Eve 01-889 9736



3 1/2 DIGIT LCD MULTI- METER KIT


Build the Practical Electronics handheld DMM. This superb product offers professional precision with extended battery life. Five function operation (AC and DC VOLTS, AC and DC CURRENT, RESISTANCE) with ability to check diodes. 0.5" LCD display with 'Battery Low' warning. Auto-polarity, Auto-zero. Full protection against transients and overloads with ability to withstand mains on any range. 0.5% basic DC accuracy and 15 different ranges. It measures AC/DC voltages from 0.1mV to 500V. AC/DC current from 0.1µA to 2A. Resistance from 0.1Ω to 2MΩ. 200 hour battery life.

The Kit contains all parts needed to construct the multimeter plus assembly instructions, battery and test leads.

We also offer a calibration service (£5.00 + VAT) and a trouble-shooting and calibration service (£7.50 + VAT). Various other component parts are also available as listed.

The multimeter is also available fully assembled and calibrated at a cost of £39.70 + P&P + VAT.

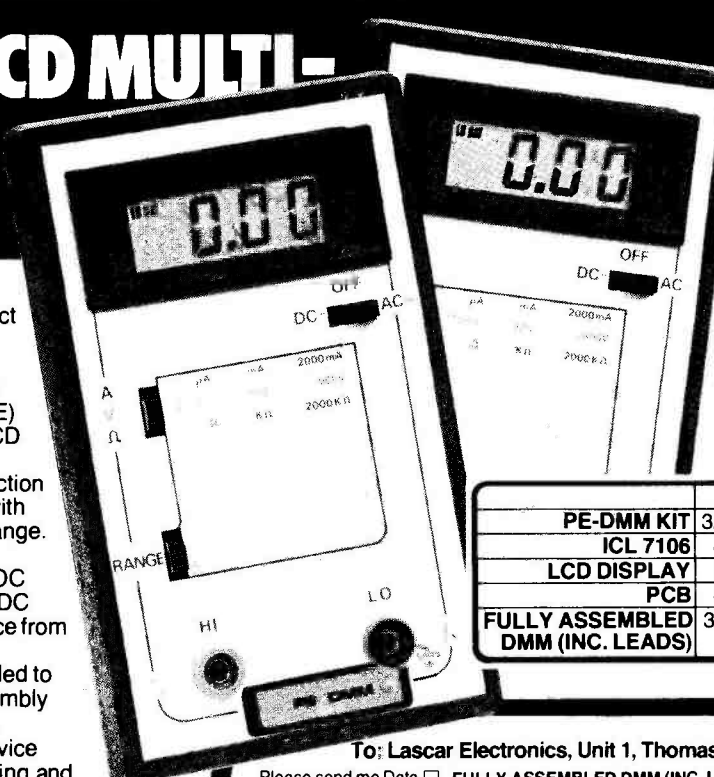Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.



NEW

FEATURED AS A PROJECT IN PRACTICAL ELECTRONICS

	£	P & P	VAT	TOTAL
PE-DMM KIT	32.95	1.00	5.09	39.04
ICL 7106	8.95	0.50	1.42	10.87
LCD DISPLAY	7.95	0.50	1.27	9.72
PCB	4.95	0.50	0.82	6.27
FULLY ASSEMBLED DMM (INC. LEADS)	39.70	1.25	6.14	47.09

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data ☐ FULLY ASSEMBLED DMM (INC. LEADS) £47.09 ☐

PE-DMM KIT £39.04 ☐ ICL 7106 £10.87 ☐ LCD DISPLAY £9.72 ☐ PCB £6.27 ☐


Name _____

Address _____

Tel No _____

I enclose cheque/P.O. value _____

TECH TIPS

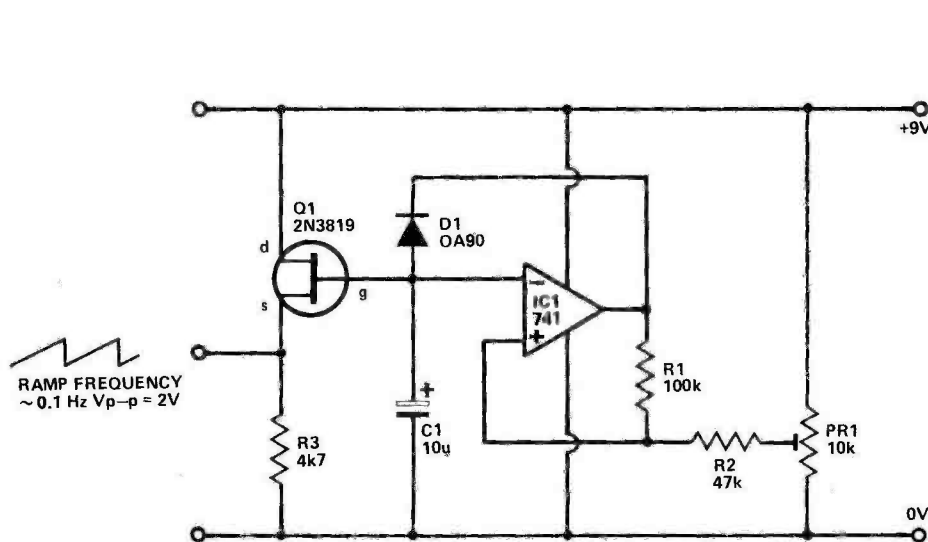

VLF Ramp Generator

C. Malloy, Whitby.

It is always satisfying to exploit the otherwise unwanted property of a device — the reverse bias current of a leaky germanium diode, in this circuit. This reverse saturation current is typically a few microamps for the OA90 and is relatively constant over 2-10 V. This constant current is used to linearly charge the capacitor in the relaxation oscillator built around the 741.

When the diode becomes forward biased the capacitor is rapidly discharged by the limited output current of the op-amp. Frequencies below 0.01 Hz are possible, though measures may have to be taken to improve the linearity of the ramp.

PR1 allows some degree of DC offset of the ramp and the source follower (Q1) reduces the loading on the capacitor which tends to degrade the ramp's linearity. For the same reason tantalum (ie low leakage) types should be used for large values of C3. Linearity can be further improved by the use of a FET input op-amp such as the 3140.

The frequency can be made variable by using the FET constant current generator shown in Fig. 2, which should replace the diode, D1. With RV1 at 100k the current will be about 30 uA and roughly inversely proportional to RV1. This constant current generator needs a voltage of about 3 V to function well. This may require an increased power supply. However, the resulting linearity is excellent, especially with the suggested FET input op-amp.

Car Radio Suppressor



L. Marks, Lancs.

This circuit will suppress mains-borne interference every time the car drives over a buried power line. It may also be used for suppressing ignition HT by a modification to the following equation:

$$f_c = \frac{1}{2\pi R_1 C_1}$$

where $R_1 = \frac{1}{2}R_2$, $C_1 = \frac{1}{2}C_2$.

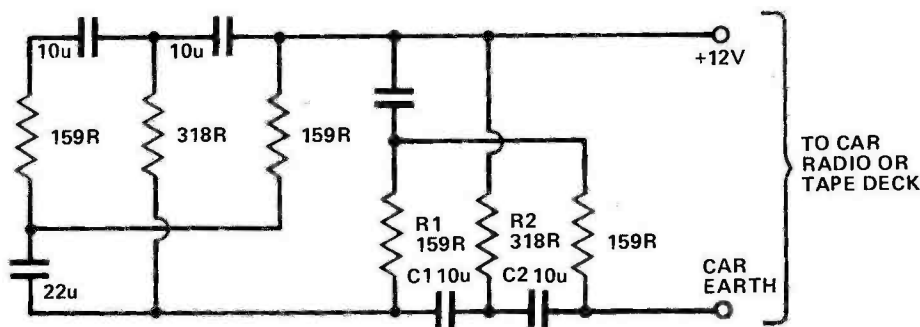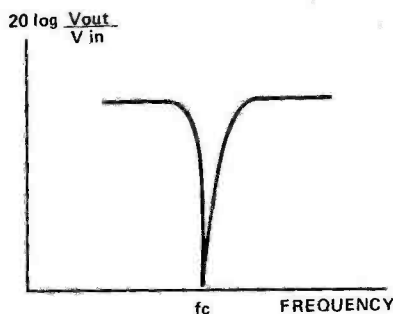The circuit works as a band reject notch filter.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

Parametric Equaliser


C.E. Read, Norwich

The parametric equaliser offers six bands of tone control separated by an octave in frequency, each frequency band being selected by the six position rotary switch.

Potentiometer RV1 permits the selected frequency band to be boosted or cut by 12 dB. The filter is particularly ideal for use with a guitar to modify and enhance the tonal qualities of the instrument.

For example, the 500 Hz setting with cut gives a hollow funky sound, whilst the 500 Hz setting with boost gives an overdriven valve amplifier, the raunchy sound favoured by many rock guitarists, but without the unpleasant muddy, harsh sound resulting from boosting the entire audio frequency spectrum.

	FREQ (Hz)	C2 (pF)	C3 (pF)
a	125	47000	4700
b	250	22000	2200
c	500	12000	1200
d	1k	5600	560
e	2k	2700	270
f	4k	1500	150

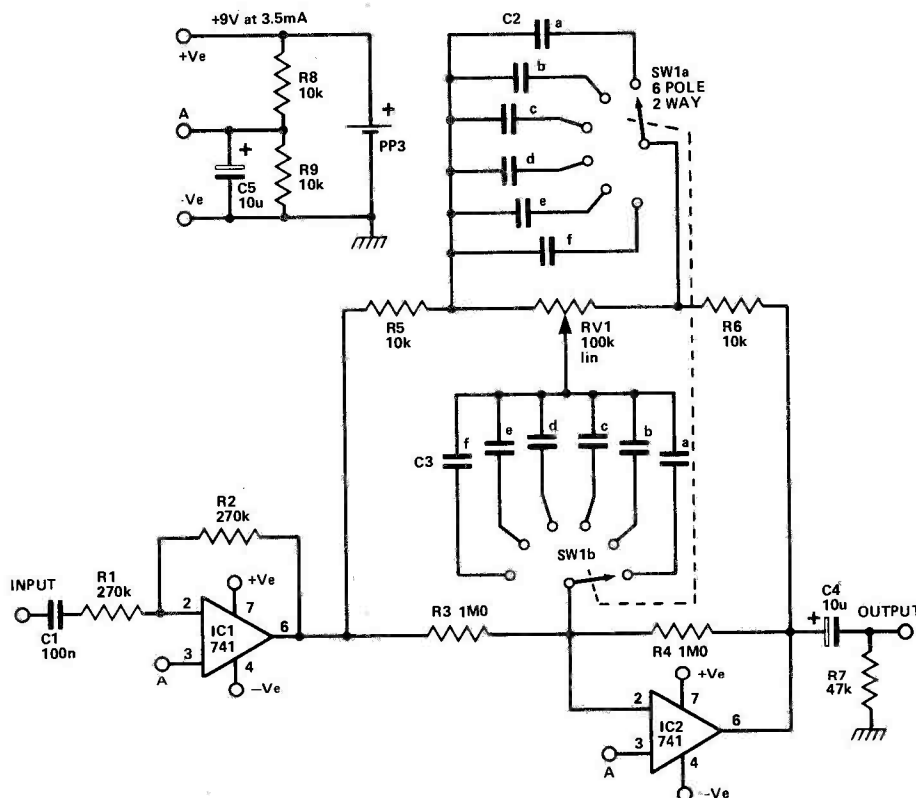

PCBs From Film

I. Parker, Bath.

There is no doubt that the most professional method to produce printed circuit artwork is by the photographic method. Unfortunately this involves the use of expensive cameras and complex enlarging systems.

However, the amateur can use this simple cheap method that produces equally good results.

Take the printed circuit artwork (from the back of ETI) to a commercial


printers and ask them to make an overhead transparency copy of it. This looks like an ordinary photocopy but instead of being printed onto paper the image appears on transparent film. Lay this on top of a piece of presensitised PCB (obtainable from most electronic retailers), use bulldog clips or adhesive tape to make sure of good contact. Then expose to sunlight for about half an hour, spray the board with the developer (following instructions carefully) and then etch the board in a normal solution of Ferric Chloride.


Ni-Cad Charger

J. Grainger, Rugby

This circuit makes use of the new constant current LEDs which are now available for about 50p (Radio spares). These devices pass a constant current of about 15 mA for applied voltages in the range 2-18 V and will also block up to 18 V peak in the reverse direction. Furthermore, they may be paralleled directly to give any multiple of 15 mA and, of course, they light up to give an indication that they are working.

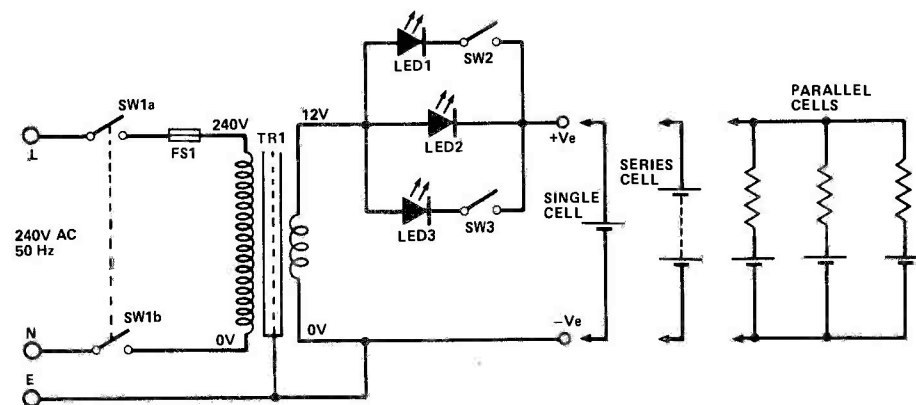The circuit shown will charge a single cell at 15, 30 or 45 mA, or cells in series up to the supply voltage limit (about 14 V). If it is desired to charge cells at less than 15 mA, several cells may be paralleled using suitable sharing resistors, which should drop about 10 V at the cell current. The LEDs will be damaged if the peak voltage of the supply exceeds 18 V (13 V RMS).



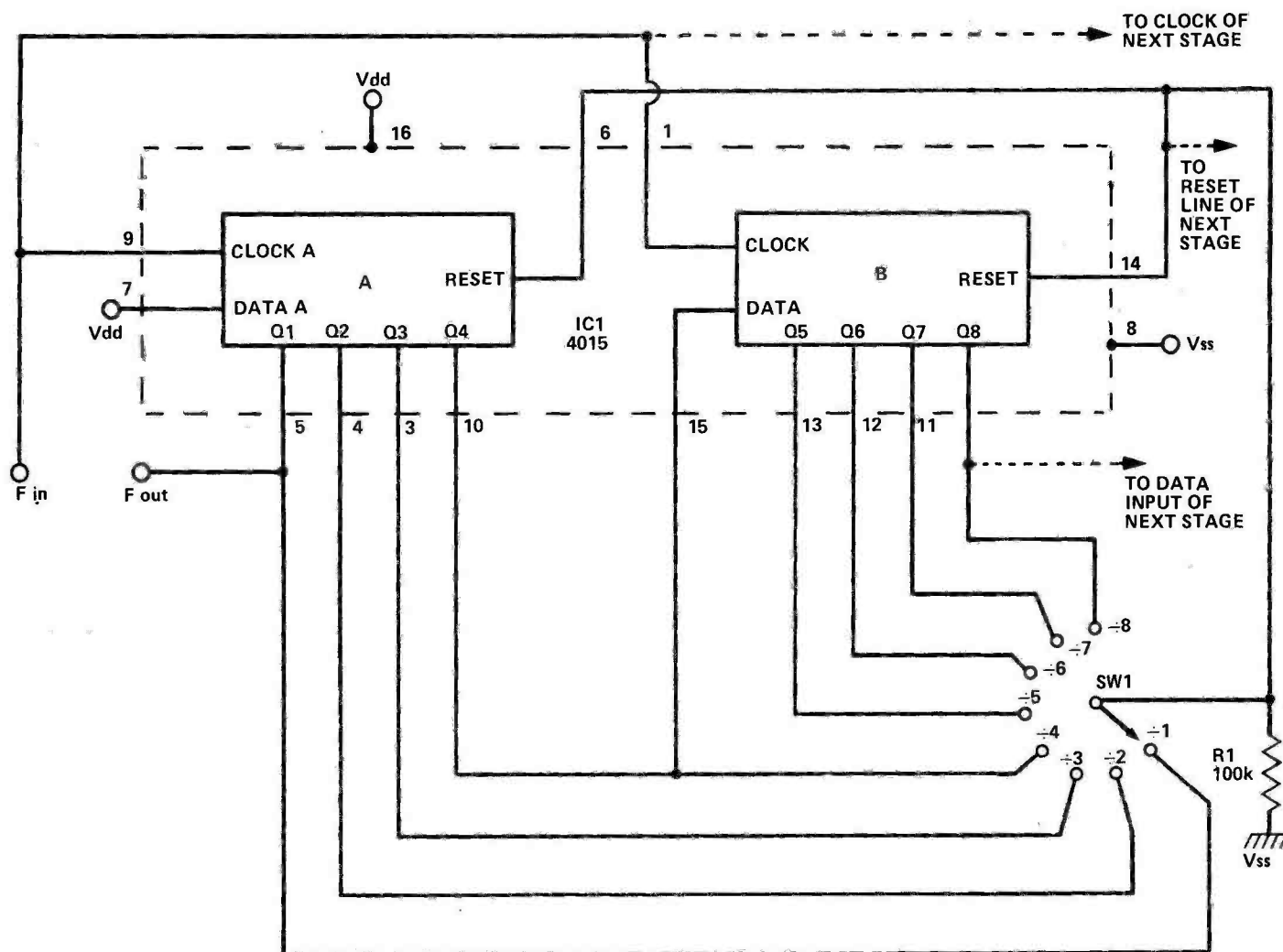

Burglar Alarm

P.N. Durrant, Chester.

The original circuit was developed as a car burglar alarm, but it could be used as a digital combination lock or, with slight modifications — removing counter 2 — a home burglar alarm.

A suitable 4 or 5 digit code is selected and, via a BCD switch wired to the appropriate latches of the 74118. Unused numbers commoned to the reset latch. Switch common is earthed through a push-button. Each is selected and entered by pressing the "enter" button. An incorrect number resets the latch. If the code is right then the unit is all reset and the relay is pulled in. The alarm is now disarmed.

If the code latch is reset a "0" appears at point A, counter 1 starts to count until it reaches eight, which sets the first RS latch, arming the

detector latch.


A digital "0" from the detector switches resets the latch and starts counter 2, which allows a set time to elapse before RLA drops out and the alarm sounds.

Since originally designed for cars without external reset, the final delay was included to allow the owner to enter and reset before the alarm was activated. Therefore the oscillator is set to the fastest time the code can be set.

To arm the unit a noncode number is set in. This leaves enough time to leave the car before the unit is armed. I used an illuminated push-button and connected it to show when the counter had reached its reset point. This also has the advantage of showing the thief that your system is all go.


The power supply must be quite heavily smoothed as the unit was found to be quite sensitive to the noise found in car electrics. The coding switch was a thumbwheel type, since it fitted the holes already in the vehicle it was designed to be used in. A touch type keyboard could be substituted, but an enter button must also be fitted.

The whole unit can be built using CMOS, especially if it is required to run from a separate supply from the main battery. The relay is a reed type holding in a larger multicontact relay with its many enabling and disabling uses in a car. It will also operate many anti-theft devices in the home. A slow code input and 5 S clock acts as a reaction timer, which could be embarrassing after a "liquid lunch".

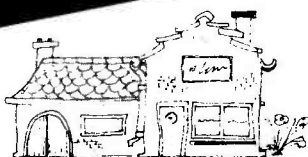

HOME

- Steam train and whistle (80019). Simulates the sound on steam and whistle £6.50
Clap switch (79026). You clap your hands and the light comes on £6.60
Elekdoorbell (79095). Program your own signature £22.00
Touch dimmer (78065). Room lighting controlled by single touch £6.80
TV sound modulator (9925) £3.75
Simple sound effects (79077) £5.70
Electronic nuisance (80016) £3.85
Ultrasonic transmitter (audio) (79510) £7.65
Ultrasonic receiver (audio) (79511) £9.95
DJ killer (79505) £8.80
Quiz master (79033) £6.50
Variable fuzz-box (9984) £6.55
Ioniser (9823). Produces a high concentration of negative ions £9.55
Oscillographics (9979). Random displays patterns on your oscilloscope £11.25
Cackling egg timer (9985). Times your egg, then clucks like a hen! £7.20
Pools forecaster (79053). Weighs up the odds and could win you a fortune £8.15
Loudspeaking telephone amplifier (9987). Amplifies signal without direct connection £11.50
Sensitive lightmeter (9886). Light measurement using silicon photodiode £12.55
Nicaid charger (79024). Automatically prevents over charge of cells £15.20
Proximity detector (9974). Detects movement in a room (electric field change) £9.80
Central alarm (9950). Master station slave station £10.85
Alarm unit £3.10
Touch tuning FM preselect unit (79519). With digital display £17.50
Talk funny (80052). Deliberate electronic distortion of speech and music signals using a single IC, the 2206 £9.60
Colour generator (80027). Using coloured light for an effective display £19.70
Pools predictor (79053) £8.15

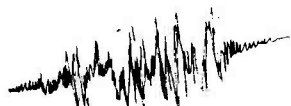

HIGH FREQUENCIES

- Aerial amplifier (80022). Improves the sensitivity of an existing receiver specify VHF/UHF £5.45
UHF/VHF modulator (9976). Generates a carrier for TV signals £6.25
Mini shortwave receiver (9920). Interesting introduction to SW radio £6.95
FM IF strip (78087). Using the CA 3189 limiter demodulator IC £13.05
Stereo decoder (79082). Compatible with the FM IF strip £15.10
Digital tuning scale (80021). A sophisticated digital frequency indication £46.30
Ohm aerial (80076 1 + 2). A practical shortwave aerial for 1.8-30MHz £10.30

Buying one of our PROJECT PACKS will save you the frustration of tracking down those elusive components that hold up the completion of your project. Our packs include Printed Circuit Board, all the components listed in the article together with sockets and solder. Cases, knobs, etc., can be supplied as extra items if required. Ask for more information!

MUSIC


- Chorosynth (80060). A cheap mini-synthesizer £57.90
Elektor vocoder (80060). The first vocoder designed to be built from a kit with excellent features. It has 10 channels £162.50
Front panels for vocoder per channel £1.25
Analog reverberation unit (9973). Kit with 1 SAD 1024 £27.70
Piano. Excellent kit of an electronic piano with three voices.
Master tone oscillator/generator £37.00
Octave PCB (9914) £18.75
Filter PCB (9981) £16.50
Power supply (9979) £19.05
Digital reverberation unit main board £67.20
Extension boards £46.30

NEW - NEW

- ★ **Battery protection (80109)**. Forgetting to turn off the headlights need no longer be a motorist's nightmare. This project is designed to monitor the battery voltage and switch off the lights automatically in all kinds of motor vehicles £5.15
★ **Transistor ignition (80084)**. A system which combines the most significant advantages of other systems including the conventional system! £20.45
★ **Intelligent wiper delay (80086)**. This wiper delay only needs to be told once what is required of it. It will then carry out your orders until you change them, which you can at any time, instantly £15.85
★ **Active car aerial (80018-1 + 2)**. If there is one place to use a good aerial it is in a car £13.85
★ **Stop thief! (80087)**. There are all sorts of systems for protecting cars, but this one is unusual: it is deception, rather than protection £4.20
★ **Battery voltage indicator (80101)**. Only a few components are needed to obtain an optional indication of the battery condition: a single lamp that changes colour as the battery goes into the danger area £6.85
★ **Pest Poster (80130)**. An electronic insect repellent. Confuses mosquitos with high pitch tone £2.35
★ **Morse Trainer (80072)**. Can be preset to generate the morse alphabet for tuition purposes. Morse key required £11.00
★ **Luxury Transistor Tester (80077)**. Not only checks that the device is functional but displays HFE group £15.54

NEW CATALOGUE

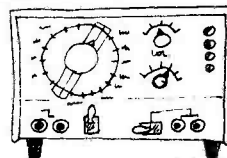Send 40p for our new catalogue giving details of our project packs and component range.



MEASURING

- Digital thermometer (80045)
LCD display (supplied without relay) £28.95
LED display (supplied without relay) £23.20
Relay (two pole changeover) £2.45
AC millivoltmeter (79035). FET input meter circuit and audio generator £6.30
Universal digital meter (79005). Digital replacement for pointer instruments £14.85
Precision timebase (9448). Generates a precision 1 Hertz pulse £13.10
Power supply for timebase £5.40
Universal timebase (78100). Crystal controlled timebase £18.70
1/4 GHz counter (9887 1 + 2 + 3 + 4). Excellent kit count up to 250 MHz £98.15
Minicounter (9927). 1KHz 4 digit display £27.70
Audio analyser (9932). An analyser which can point the deficiencies in a particular audio chain or environment £14.80
Spot sinewave generator (9948). Programmable sinewaves with less than 0.0025% THD £12.95
Simple function generator (9453). Sine, square and sawtooth outputs £27.70
Sinewave generator (79019). Always sinewaves when you need them £8.90
TV scope basic version (9968 1/5). Produces display up to 1 KHz on TV £34.50
TV scope advanced version (9969 1/3). Converts basic scope to 100KHz bandwidth £48.25
Digiscope (9926) £32.35
Digifard (79088). A digital capacitance meter with a wide range £25.10
Gate dipper (79514). Checks the resonant frequency of a circuit £16.00

AUDIO

- Equaliser (9832). Single channel audio equaliser with slidepots £17.70
with turnpots £15.60
with preset pots £13.95
UAA180 LED meter (9817). A two-channel display meter with LEDs £13.00
Peak programme meter (9860). For use with UAA180 LED meter to give stereo audio display £13.00
Luminant (9949 1 + 2 + 3). A novel LED audio level indicator £20.70
Parametric equaliser (9897).
filter section (9897-1) £6.45
Tone control section (9897-2) £5.20
Audio analyser (9932). An analyser which can pinpoint the deficiencies in a particular audio chain or environment £14.80
Preconsonant (9954). A high-performance amplifier £5.75
Consonant (9945). A complete audio control preamplifier £34.85
Toppreamp (80031). Mini preamplifier for Topamp or any other Hi-Fi poweramp £34.30
Topamp (80023). Hybrid audio power amplifier with OM 931 (output 30 watt) £18.50
with OM 961 (output 60 watt) £33.40
Stentor (79070). A portable amplifier ideally suited for PA £30.00
Assistentor (79071). A preamp for use with Stentor £7.00
Elektornado (9874). A 2 x 50 watt or single 100-watt power amplifier £19.50
Electret microphone preamp (9866). Compact design that fits into the mike £4.85

HOW TO ORDER:



Send a cheque or postal order to **DORAM ELECTRONICS LTD.**, Fitzroy House, Market Place, Swaffham, Norfolk, PE37 7QH. All our prices include V.A.T. Please add 40p for postage and packing.

Office hours: Monday-Friday, 9 a.m. to 5 p.m.
Telephone Swaffham (0760) 21627. Telex 817912.



AT BLINKIN' LAST! COLOURBOARD II

THE NEW 50HZ COLOUR VERSION OF OHIO SCIENTIFIC'S SUPERBOARD II IS HERE AND LIKE A TON OF BRICKS DOWN CRASHES THE PRICE OF STANDARD SUPERBOARD II.

50HZ UK BLACK AND WHITE SUPERBOARD II

£159.95 + 15% VAT POST FREE
COLOURBOARD II £205 + 15% VAT




THE UNIQUE SPECIAL
OFFER YOU CAN'T RESIST

- ★ If bought with superboard or colour board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT.
- ★ Modulator and power supply kit £7.95 (£11), 4K extra ram £20 (£24), Case £23 (£26), Cassette recorder £13 (£15), Super Print 800 MST printer £399 (£399), Colour conversion board for Superboard II £45 (£46).


WE CAN CONVERT YOUR SUPERBOARD TO COLOURBOARD, SEND A SAE FOR DETAILS

SINCLAIR PRODUCTS

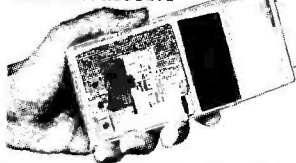

PEM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95, Microvision TV £89, mains adaptor £8.88, PDM35 £34.23, mains adaptor £4.20, case £2.07, DM350 £76.70, DM450 £102.17, DM235 £55.55, Accessories for all 3 models — rechargeable batteries £7.99, mains adaptor/charger £4.20, case £8.90, Enterprise prog calculator £19.95, New SC110 10MHz oscilloscope £144.95, TG105 pulse generator £87, Bench frequency counter £150.

COMPUTER GAMES

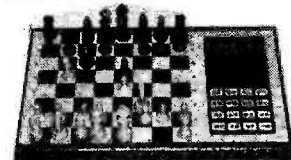

New Sensory Chess Challenger 8 £109, Chess challenger 7 (illustrated) £75, Chess champion 6 £49.95, Checker challenger 2 £39, Star Chess £62, Grandstand video entertainment computer £79.95, Videocarts £12.60, Philips G7000 Videopak home computer £139, Video paks £12.95, Atari Videocomputer £129, Cartridges £14.85 (except chess £43.95 and backgammon £33.95).


SWANLEY ELECTRONICS

Dept. E71, 32 Goldsall Road, Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. List 27p post free. Overseas customers deduct 13%. Official credit orders welcome.

TV GAMES

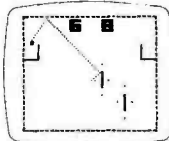AY-3-8500 chip £3.00, Kit £4.26, Stunt cycle AY-3-8760 chip £8.14, kit £4.95, 10 game paddle 2 AY-3-8600 chip £5.95, kit £7.03, Modified shoot kit £5.28, Colour generator kit £9.05.



MAINS TRANSFORMERS

6-0 6V 100ma 80p, 1 1/2 £2.60, 9-0 9V 75ma 80p, 1a £2.40, 2a £3.94, 12-0 12V 100ma 89p, 1a £2.90, 15-0 15V 1a £3.15.

JC12 and JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 watts £2.08, JC20 10 watts £3.54.

CONTINENTAL SPECIALITIES

PRODUCTS
EXP300 £8.61, EXP350 £3.62, EXP325 £1.84, EXP650 £4.14, EXP48 £2.64.

STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. TTL computer supplies 5V 2A £3.13 (£7.44), 5V 4A £5.12 (£12.60), 8-way types 3/4V/6/7 1/2/9/12/15/18V 100ma £1.84 (£2.60), 1A £3.30 (£5.50), 2A £5.60 (£9.84), Variable voltage models 2-18V 100ma £1.84 (£2.60), 1-30V 1A £3.30 (£5.75), 1-30V 2A £5.60 (£12.10).

PRINTED CIRCUIT MATERIALS

PC etching kits — economy £2.42, standard £4.76, 40 sq ins pcb 45p, 1 lb FeCl £1.50, Etch resist pens — economy 50p, dolo 84p, Drill bits 1/32" or 1mm 34p, Etching dish 92p, Laminate cutter £9.20.

BI-PAK AUDIO MODULES

AL30A £4.53, PA12 £8.31, PS12 £1.75, T538 £2.70, S450 £27.90, AL60 £5.62, PA100 £19.24, SPM80 £5.26, BMT80 £6.06, Stereo 30 £23.94, AL80 £8.56.

2114

Full spec, memory chips
Low current, 300NS
Only £3.45

COMPONENTS

IN4148 0.0p, 1N4002 3.1p, 723 14 dil 33p, NE555 8 dil 24p, 741 8 dil 18p, bc547, bc549, bc182, bc184, bc212, bc214, bc548 5.5p, tip31c, tip32c 36p, tip41c 40p, bd132 27p, plastic equiv bc722 4.5p, fuses 20mm x 5mm cartridge .15, .25, .5, 1, 2, 3, 5Amp quickblow 2p, resistors 5% 1/4W £12 10R to 10M 1p, 0.6p for 50+ of one value, polyester capacitors 160V 015, .068mf 2.5p, .1mf 4.0p, .01mf 3.0p, .022, .033mf 3.3p, .047mf 4.0p, .15, .33mf 4.9p, .47mf 8.0p, polystyrene capacitors £12 63V 10 to 1000pf 3p, 1n2 to 10n 4p, ceramic capacitors 50V £6 22pf to 47n 2p, electrolytic capacitors 50V 5, 1, 2mf 6p, 25V 5, 10mf 6p, 16V 22, 33mf 6p, 47, 68mf 3.5p, 100mf 7p, 330, 470mf 9p, 1000mf 11p, zeners 400mw £24 2V7 to 33V 7p, preset pots subminiature 0.1W horiz or vert 100 to 4M 7p, potentiometers 1/4W 4K7 to 2M2 log p lin single 28p, dual 71p, 1/4" red LEDs 9.7p, ic sockets 8 dil 8.7p, 14 dil 10.1p, 16 kit 12p.

BATTERY ELIMINATORS

3-way types with switched output and 4 way multi pack — 3/4V/6V 100ma £2.67, 6/7 1/2/9V 300ma £3.14, 100ma radio types with press-switch connectors 9V £3.77, 6V £3.77, 4 1/2V £4.99, 6 + 6V £4.99, 4 1/2 + 4 1/2V £4.99, cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £3.57, fully stabilized type 3/6/7 1/2/9V 400ma £8.80, car converters 12V dc input, output 7 1/2V 300ma £1.19, output 3/4 1/2/6/7 1/2/9/12V 800ma £2.75.


BATTERY ELIMINATOR KITS

100ma radio types with press-switch connectors 4 1/2V £1.49, 6V £1.49, 9V £1.49, 4 1/2 + 4 1/2V £1.92, 6 + 6V £1.92, 9 + 9V £1.92, cassette type 7 1/2V 100ma with din plug £1.49, heavy duty 13-way types 4 1/2/6/7 1/2/8 1/2/11/13/14/17/21/25/28/34/42V 1A £5.52, 2A £8.80, car converter input 12V dc, output 6/7 1/2/9V 1A stabilized £1.35.

S-DECS AND T-DECS

S-Dec £3.79, T-Dec £4.59, 16 dil adaptor £2.31.

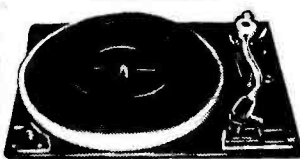EX-STOCK FROM US
**J.V.C. BELT DRIVEN
TURNABLE**
WITH STEREO MAGNETIC
AUDIO TECHNICA
CARTRIDGE



LIST PRICE OVER £50

J.V.C. Turntable supplied complete with Audio Technica AT10 stereo magnetic cartridge.

- * Belt driven
- * 'S' shaped tone arm.
- * Modern design
- * Full size 12" platter.
- * Calibrated counter balance weight (0-3 grms).
- * Anti-skate (bias) device.
- * Size — 12 1/4" x 15 1/4" (approx)

AT ONLY

LIMITED STOCKS **£25.99**

PLUS VAT £3.89 Post £2 50

GEC HIGH QUALITY STEREO

10 + 10 watt AMPLIFIER
WITH AM/FM STEREO TUNER
IDEAL FOR THE HOME

A cancelled export order brings you this offer from the world-famous firm of G.E.C.

AM/FM stereo Tuner Amplifier
Ready built. Comprising of a tuner/pre-amp. board and separate power supply/power amp. board with wiring diagram.
Rotary Controls: Tuning, on/off volume, balance, treble, bass, Stereo Beacon indicator.
Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), L.W., M.W., S.W.

Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.

Frequency Response: 60Hz-20KHz within ± 3dB.
Tape Sensitivity: Output — typically 150 mv. Input — 300 mv for rated output.

Disc Sensitivity: 100 mv (ceramic cartridge)
Radio: FM (VHF) 87.5MHz-108MHz.
Long Wave 145KHz-265KHz.
Medium Wave 520KHz-1620KHz.
Short Wave 5.8KHz-16MHz.
Size: Tuner — 2 1/2" x 15in, x 7 1/2" in. Power Amp — 2in. x 7 1/2" in, x 4 1/2" in.

LOW
PRICE
OFFER



ON/OFF BALANCE, TREBLE, BASS, MONO TAPE Phono AFC FM LW MW SW Tuning. Volume

Fully Guaranteed Ex-Stock

SUITABLE
SPEAKERS
IN CABINETS

PAIR
10 WATTS

£19.95
INC.
VAT

POST
£2.50 Pair

ONLY
£19.95
+ VAT £2 99
CARRIAGE £2 50

5 + 5 Watt Car Stereo Amplifier made for Motorola

- * WITH pre-amplifier and M. & Long wave assembly.
- * Supplied as two built and tested units.
- * R.F. and I.F. stereo preamplifier and radio 4 x 2 x 1 1/4".
- * 5 + 5 watt stereo amplifier 12/14 volt 4 x 2 x 1 1/4"
- * Complete with circuit, data and connection diagrams.
- * Limited quantity available, ex-stock.

BRAND NEW
Only £5 + VAT
+ VAT
Post 50p

EX-
MOTOROLA

EX-MOTOROLA

CAR STEREO CASSETTE MECHANISM

- * Front loading 12 volt transistorised
- * Speed & Voltage control
- * Ex-equipment — Tested O.K.
- * Takes standard C60 cassette

ONLY **£7.50**
INC VAT
POST 80p



Henry's

Phone (01) 723 1008/9
404 Edgware Road, London W2, England I.E.D.




PRD M25 Professional capacitor boom-arm microphone by Eagle.
A graceful 60 cm boom-arm capacitor studio microphone using a cardioid capsule. A high standard of finish for in-vision use and yet robust enough to withstand long periods between maintenance. Supplied complete with 1 red and 1 black windshield and 6 metres of twin screened cable terminating at the microphone end in an XLR connector.
Impedance: 600 ohms (floating). Response: 20-18,000 Hz. Sensitivity: — 70 dBV.
Cable: 6 metres two conductor shielded. Connector: XLR 3-11C, Battery type: HP7.

LIST PRICE
£37 40
OUR PRICE
£19.95
inc VAT
POST £1 50

VOCODER

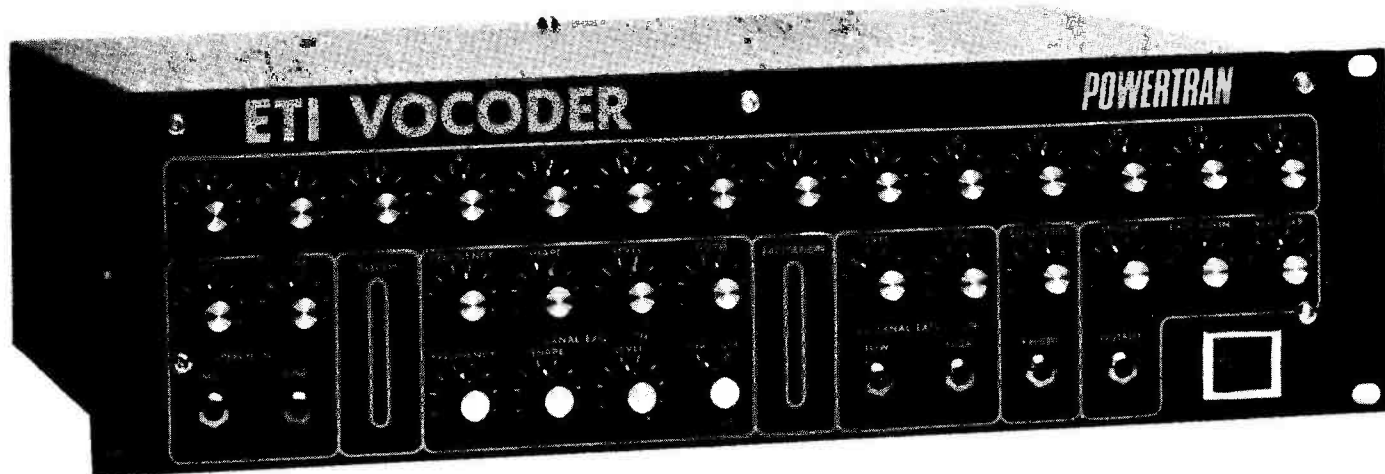Change sex or orchestrate yourself (same thing, really) with the ETI Vocoder, designed by Richard Becker of Powertran.



A vocoder could be simply defined as a device which will, in real time, superimpose the spectral characteristics of one signal upon another. To leave it at that, however, would result in many a yawn and a few skipped pages. In fact vocoders are anything but boring! Put speech and the output of an instrument into a vocoder and the instrument, not the operator, appears to be doing the talking or singing! Use the internal excitation oscillators, change the frequency and the speaker suddenly changes sex. Use the noise generator and there is whispering in the breeze. Use the output of a cassette deck and the London Symphony Orchestra recites the Karma Sutra! Just a few of the possibilities!

Human speech is built up from two basic components — the sound from the vocal chords which buzz when air is passed over them and the sound of air rushing past the teeth. These sounds are used to produce voiced and unvoiced speech respectively. By opening and closing the mouth and the nasal cavity, and by moving the tongue, thereby adjusting the resonances, the basic sounds are modified in amplitude and harmonic content. If the variations in amplitude and harmonic content can be analysed and applied to suitable electronic control circuitry then the basic sounds of speech can be substituted for by almost anything and this is just what a vocoder does.

The first part of a vocoder is a spectrum analyser producing control signals which are a measure of the strength of the speech signal in each of the frequency bands (14 in this design). The substitution (excitation) signal is also split into a number of frequency bands (using identical filters to those used for analysis) and each of these signals is passed through a voltage controlled amplifier whose gain is determined by the control signals. The sum of the outputs of these amplifiers is the vocoder output.


The system

The speech signal, after passing through the pre-amplifier and tone control stages, is separated into 14 bands by bandpass filters, a low pass filter and a high pass filter. The bandpass filters are double tuned that is to say each of the two stages has a slightly different resonant frequency. The effect of this is to broaden the band of accepted frequencies and give the response curve a flattened top. A high Q makes the filters cut off rapidly out of the pass bands.

The envelope followers consist of an active full wave rectifier and a low pass filter, the output of which is the control signal for the synthesiser section. The control signal passes through a sample and hold stage which is used to freeze the music, by means of a footswitch, at any required point of articulation. The stage is also used for slewing rate control which smooths out the control signals for slower and smoother changes in spectral balance and amplitude resulting in speech being changed into singing or chanting.

Holy Responses

In the synthesis section there is a filter bank identical to that of the analysis section. Voltage controlled amplifiers modulate the outputs of these with the control signals from the analysis section. The outputs are then summed to produce the output signal. Alternate channel outputs are inverted since there is a change in phase as a signal is swept through the resonant frequency of the filter. Therefore, at the midpoint between adjacent bands phase cancellation will occur producing deep holes in the overall frequency response. By having adjacent channels outputs inverted with respect to each other there is addition instead of subtraction at the midpoints.

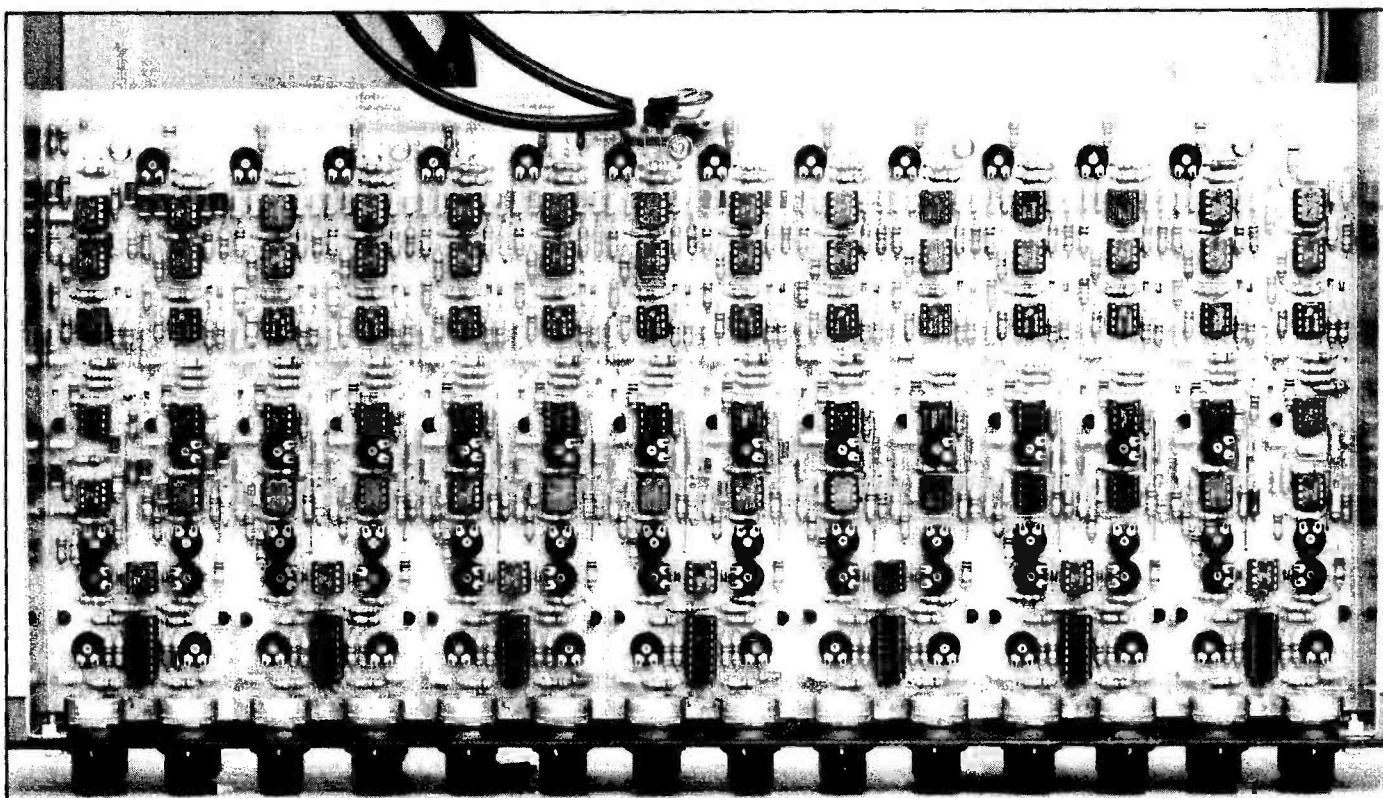

The analysis/synthesis board occupies the front half of the case. All the potentiometers are PCB mounting for ease of construction. The Power Supply Unit (to be described next month) is a respectable distance away, mounted on the rear panel.

SPECIFICATION

14 channel: Filters — 4th order with bandpass filters at $\frac{1}{3}$ octave spacing.

LED Bar Display PPMs for both speech and excitation.

Speech input: amplifier:

mic input: sensitivity 1 mV

mic input: impedance 100k

line input: sensitivity 500 mV

line input: impedance 10k

tone control: ± 6 dB Treble boost — Bass cut/Bass Boost - Treble cut.

excitation input amplifier:

low input: sensitivity 10 mV

low input: impedance 100k

high input: sensitivity 500 mV

high input: impedance 10k

tone control: ± 6 dB Treble boost-Bass cut/Bass boost-Treble cut

Internal excitation:

pseudo-random counter noise generator

2 oscillators — range: 15 Hz-250 Hz

pulse width: fully variable

Slew rate control: 100:1 range. FREEZE by footswitch

Voice/unvoiced detector:

AGC on noise generator to follow excitation signal



Output amplifier:

mixing controls for vocoder, speech bypass and external excitation bypass

Output level: 1V



The internal excitation board.

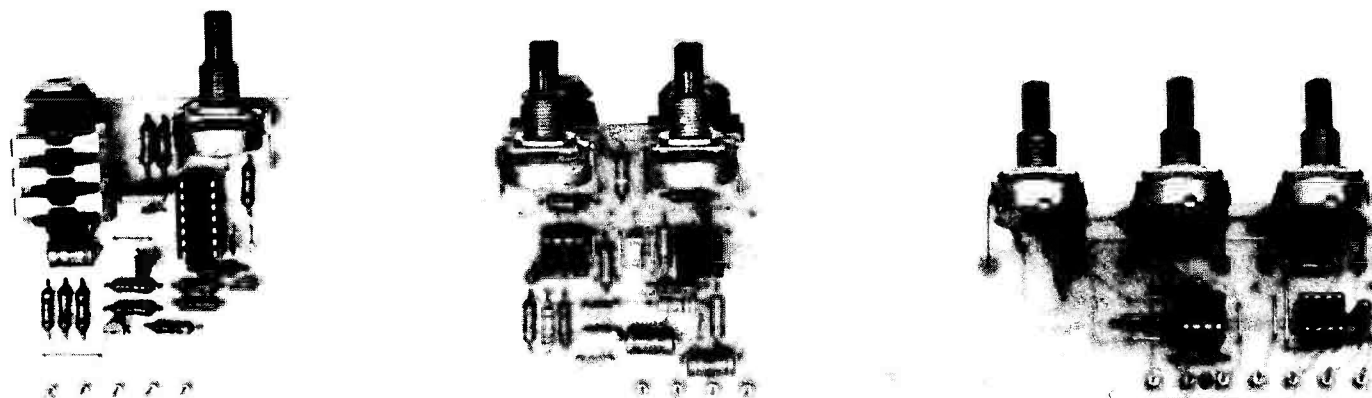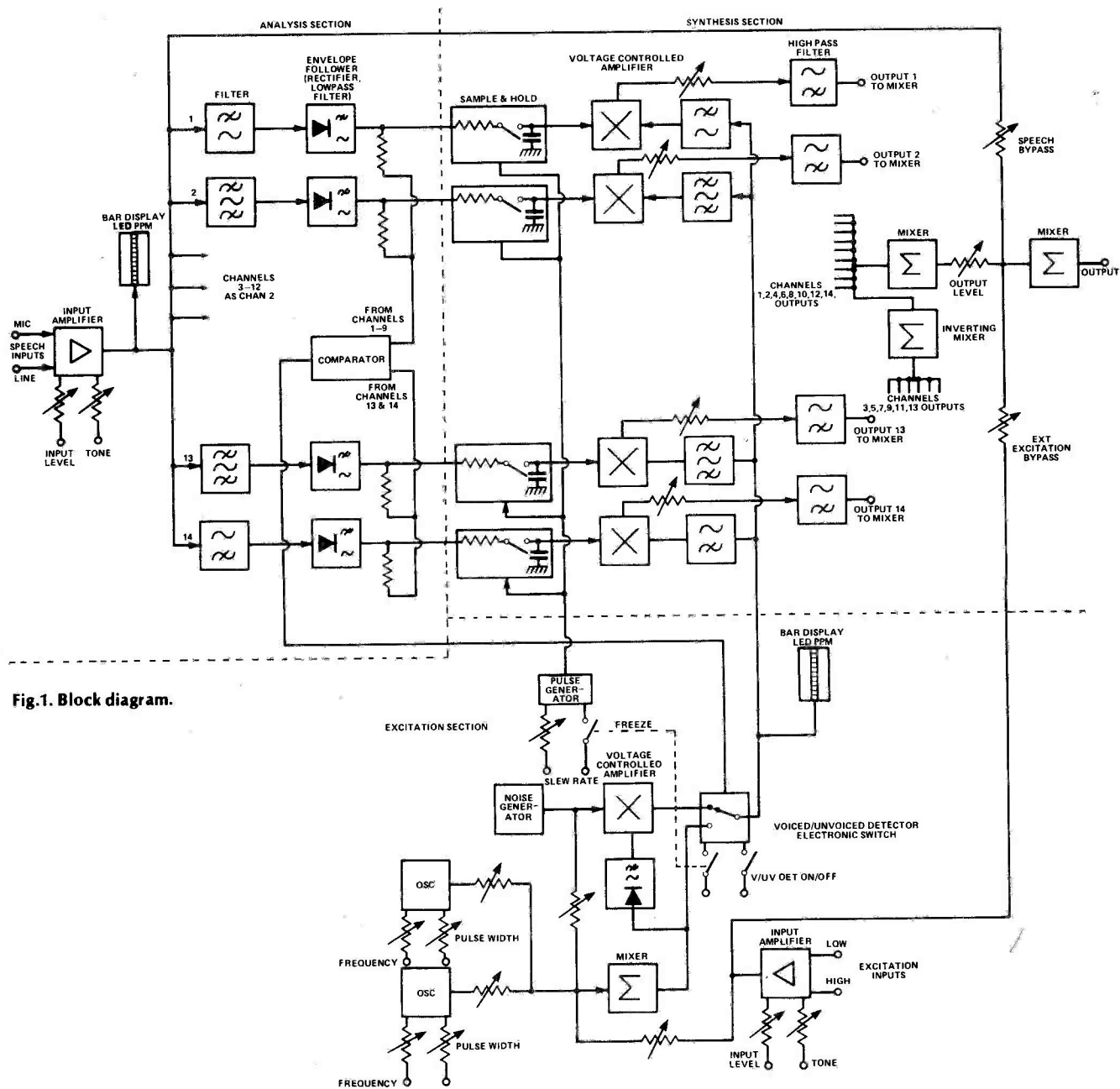

Details of the smaller boards devoted to slew rate control (left), input amplifier (middle) and output amplifier (right) will be given in the concluding part of the Vocoder project next month.

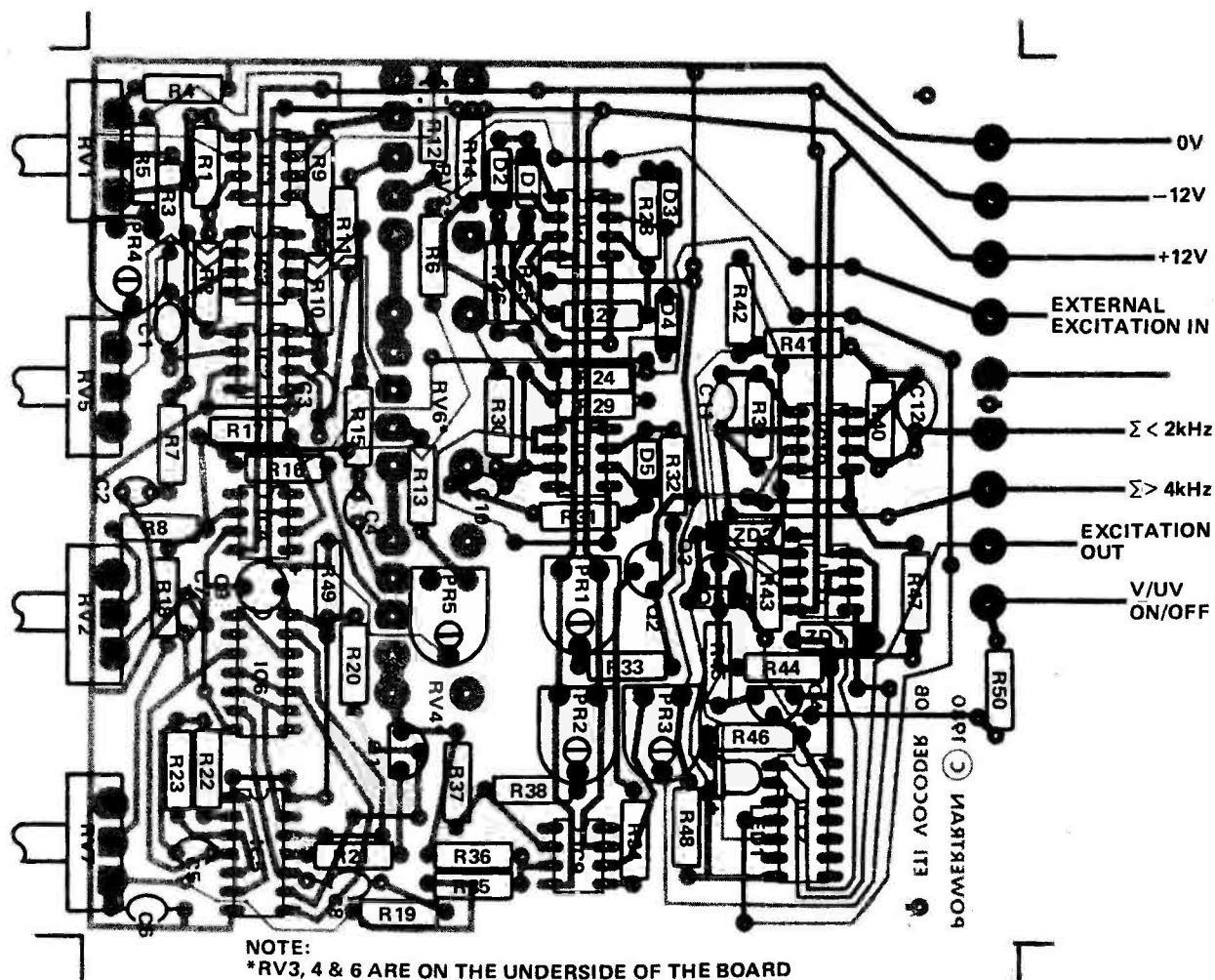


Fig.2. Component overlay of the internal excitation board.

PARTS LIST

RESISTORS — ALL 2% METAL OXIDE

R1,9,29,34,40,44,45,50	10k
R2,10	5k6
R3,11	18k
R4,12	560R
R5,13	11k
R6,8,16,18,35,39,43	47k
R7,15	150k
R14,30,42	1M
R17	100k
R19	15k
R20,24,25,26,27,28	4k7
R21,32	22k
R22	330k
R23	27k
R31	3k9
R33,38	470k
R36,37,46	1k5
R41,47,48	1k
R49	3k3

POTENTIOMETERS

RV1,2,5,7	10k logarithmic
RV3,4,6	10k logarithmic
PR1,2	100k preset
PR3	220k preset
PR4,5	2k2 preset

CAPACITORS


C1,3	100n polyester
C2,4	10n ceramic
C5	220p ceramic
C6	33n polyester
C7	100p ceramic
C8	10n polyester
C9	10u 16V tantalum
C10	100n polycarbonate
C11	220n polycarbonate
C12	1u0 polycarbonate

SEMICONDUCTORS


IC1,2,7,10,11	1458
IC3,8	TL082 or LF353
IC4	741
IC5	4006
IC6	4030
IC9	CA3080
IC12	4016
Q1,3	BC182L
Q2,4	BC212L
ZD1,2	5V1 Zener
D1-D6	1N4148
LED 1	TIL209

MISCELLANEOUS

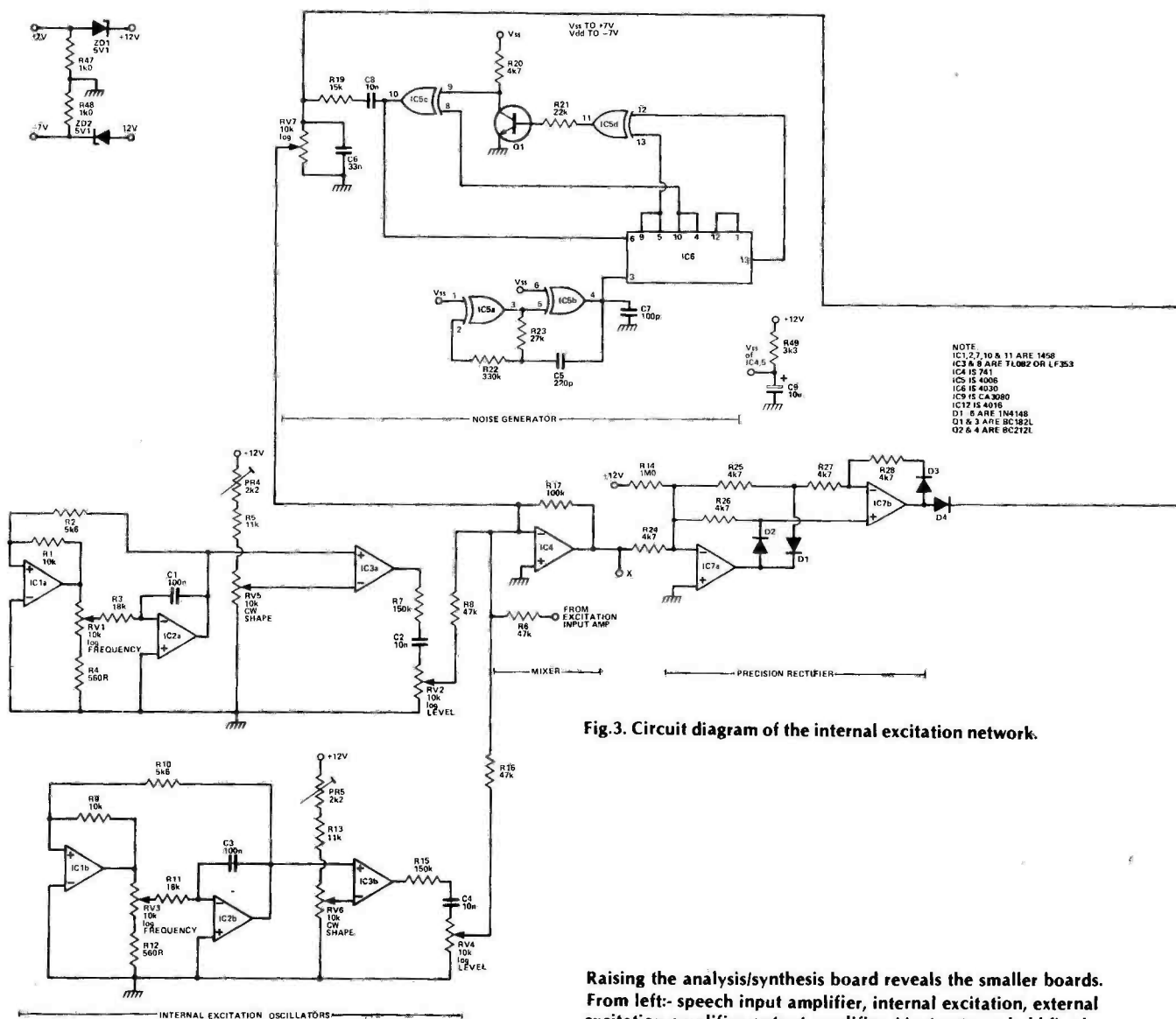9 way connector and pins, IC sockets, terminal pins, rotary on/off switch.



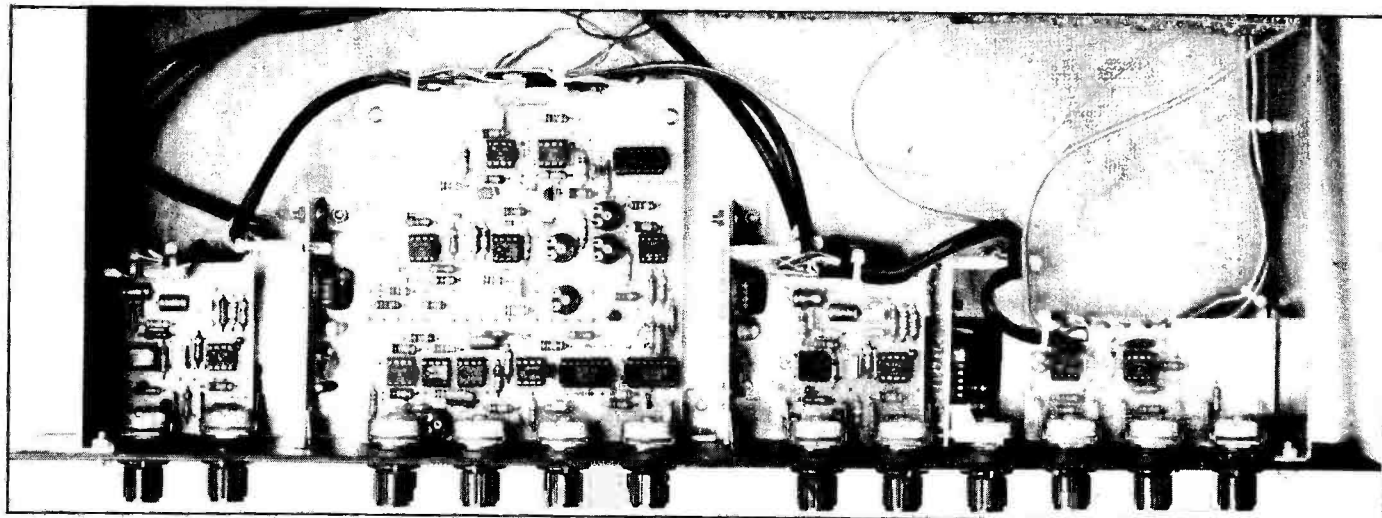Raising the analysis/synthesis board reveals the smaller boards. From left:- speech input amplifier, internal excitation, external excitation amplifier, output amplifier. Most pots are held firmly on their PCBs by pot mounting frames.



HOW IT WORKS

IC1, 2 form a pair of relaxation oscillators. IC2 is an integrator driven by the output of IC1. C1 is charged until it reaches about one third of the supply line voltage when the Schmidt trigger (IC1) changes state and C1 starts discharging until it reaches about one third of the supply line voltage in the opposite direction, making IC1 change state again. The output of IC2 is a triangular waveform which is compared with an adjustable DC voltage by IC3 to produce a pulse output of adjustable mark/space ratio. The outputs of the two oscillators are mixed with the external excitation and the noise by IC4.

The noise generator is a pseudo-random counter. IC5a,b form an oscillator operator at about 40 kHz. This clocks IC6, which is an 18 stage shift register with feedback applied round it via IC5c, d and Q1. The output of IC5c is a complex pulse train, which, when filtered by C8, R19, C6 has the characteristics of random noise with a very even frequency response.

The key part of the voiced/unvoiced detector is the comparator IC11a, which compares the levels of the speech components over 4 kHz with those below 2 kHz. It is not necessary to use separate filters for this purpose as the control signals at the outputs of IC3 of the analysis section contain the necessary information and these are summed by IC10a, b before comparison. When voiced speech is present IC11a goes low, Q3 turns off, its collector goes high and the analogue switch IC12b is opened allowing the output of IC4 to pass to the synthesis section. To match the noise level to that of the excitation from IC4 there is AGC. IC7a is a full wave rectifier peak detector which is buffered by IC8a. IC8b and Q2 are a voltage to current converter to provide a control current for the OTA IC9 through which the noise is passed.


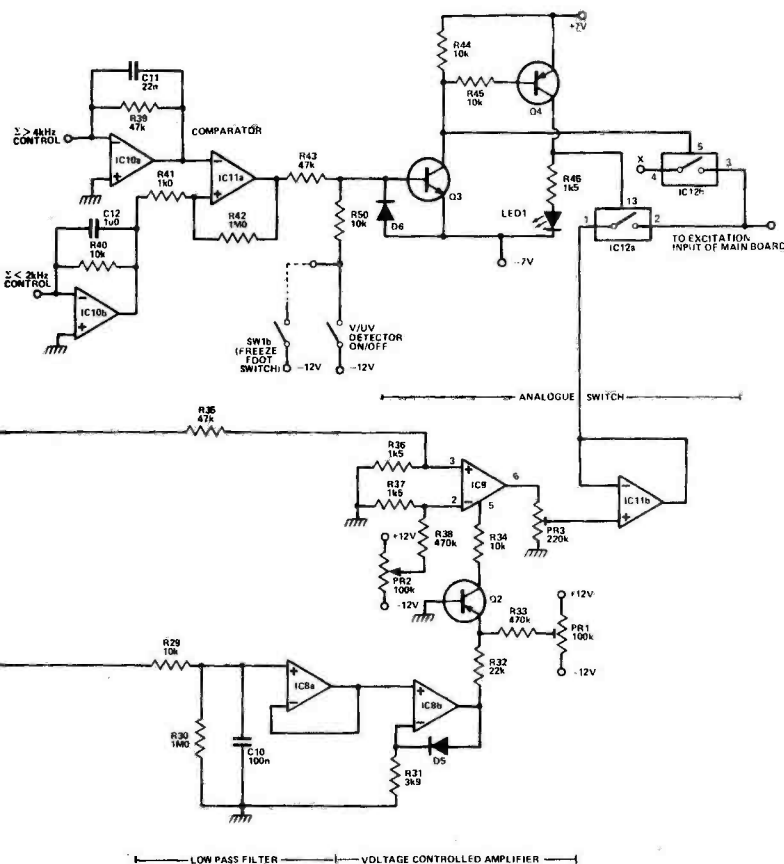


Fig.4.(below) Filter frequency response curves.

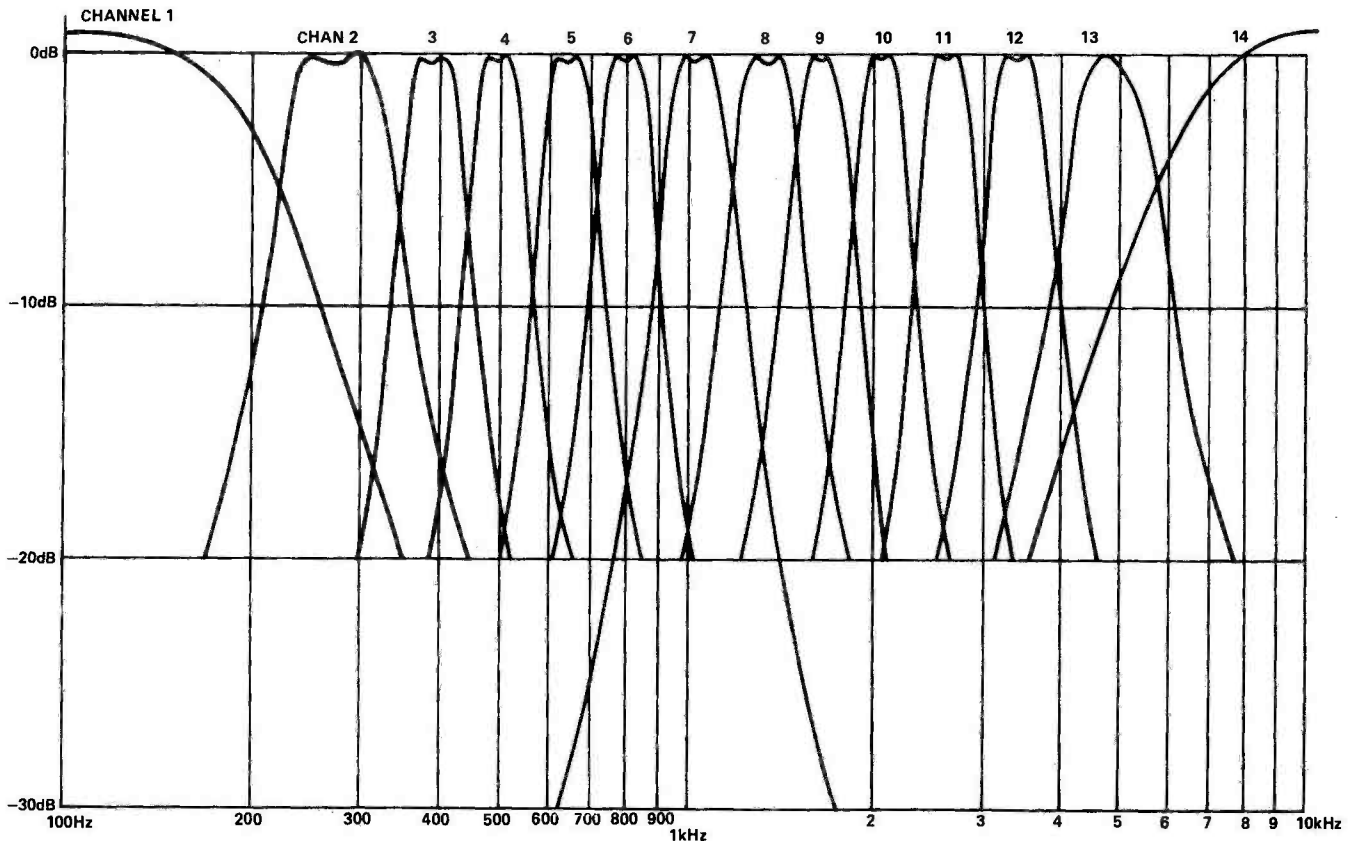

Powertran Electronics, Portway Industrial Estate, Andover, Hampshire, are supplying a complete kit of parts for this project at £195.00 plus 15% VAT. Delivery by Securicor is £2.50 extra. Everything is included in the kit down to the last nut and bolt. They even give you a 'Freeze' footswitch and a test oscillator for setting it up!

Next month we conclude the Vocoder project with constructional details of the remaining boards and power supply, with notes on setting up and use.

IC1 in channels 2-13 is the analysis bandpass active filter. PR1 adjusts the first section in relation to the second. When correctly set up there is an overall voltage gain of 10. In channels 1, 14 IC1 is a low pass filter and a high pass filter respectively. IC2 rectifies the signal to demodulate it to convert it into a control signal for the VCA. IC3 is an active low pass filter with a cut off frequency of 200 Hz or one fifth of the frequency of the bandpass filter, whichever is the higher.

R14 takes the output of IC3 out for analysis by the voiced/unvoiced detector. IC4 is the slewing rate controller, Q1 and R15 acting as a variable resistor which, in conjunction with C7, forms an RC network adjusting the slewing rate of the stage. Being a FET Q1 could, on its own, be used as a variable resistor by simply varying the VGS, but there are 14 of them to control simultaneously and without careful selection they would not track together. To deal with this Q1 is used instead as a switch which is turned on and off by a 1 kHz pulse signal of variable width. C7 is then charged and discharged at a rate dependent on the duty cycle of the pulse

IC5 and Q2 form a voltage to current converter, the gain of which is set by PR2 to compensate for variations in gain in IC6. For correct operation IC5's input must never go negative. To ensure that it doesn't, a bias voltage is applied via R15. This voltage together with the combined offset voltages of IC1-5 is nulled out by PR3.

IC6 is an OTA (operational transconductance amplifier), which could have been our old friend the CA3080, but a better device, the LM13600 is now available. It achieves very low distortion by having linearising diodes at the input. Bias current for these is supplied by R28. The gain is controlled by the current supplied to pin 1. The output of the OTA is taken to a volume control RV1 from where it goes back into IC6 to a buffer stage before being taken out via C12 and R30 to a virtual earth mixer. C12 and R30 serve as a high pass filter to remove breakthrough of the control signal. The excitation or music signal is applied to the OTA via IC7 which is a filter identical to that of IC1.

CHAN	PR1,5	R1,21	R2,22	R3,23	R4,24	R5,25	R6,26	R7	R12,13	C1,3,8,10	C2,4,9,11	C12	IC1,7
1	—	10k	10k	2k0	220R	10k	10k	4k7	68k	47n	150n	220n	TL082/LF353
2	2k2	2k0	82k	24k	910R	110k	110k	4k7	47k	68n	68n	47n	1458
3	1k0	6k2	180k	47k	560R	220k	220k	4k7	30k	39n	39n	33n	1458
4	1k0	6k2	180k	47k	430R	220k	220k	4k7	24k	33n	33n	27n	1458
5	1k0	6k2	180k	47k	430R	220k	220k	3k6	18k	27n	27n	22n	1458
6	1k0	6k2	180k	47k	430R	220k	220k	3k0	15k	22n	22n	18n	1458
7	1k0	6k2	180k	47k	560R	220k	220k	2k4	12k	15n	15n	15n	1458
8	1k0	6k2	180k	47k	560R	220k	220k	1k8	12k	12n	12n	12n	1458
9	1k0	6k2	180k	47k	510R	220k	220k	1k5	12k	10n	10n	10n	1458
10	1k0	6k2	180k	47k	470R	220k	WIRELINK	1k2	12k	8n2	8n2	8n2	TL082/LF353
11	1k0	6k2	180k	47k	430R	220k	WIRELINK	1k2	12k	6n8	6n8	6n8	TL082/LF353
12	1k0	6k2	180k	47k	560R	220k	WIRELINK	1k2	12k	4n7	4n7	4n7	TL082/LF353
13	2k2	2k0	82k	24k	1k1	110k	110k	1k2	12k	3n3	3n3	4n7	1458
14	—	13k	43k	2k0	220R	43k	13k	1k2	12k	1n0	1n0	4n7	1458

64

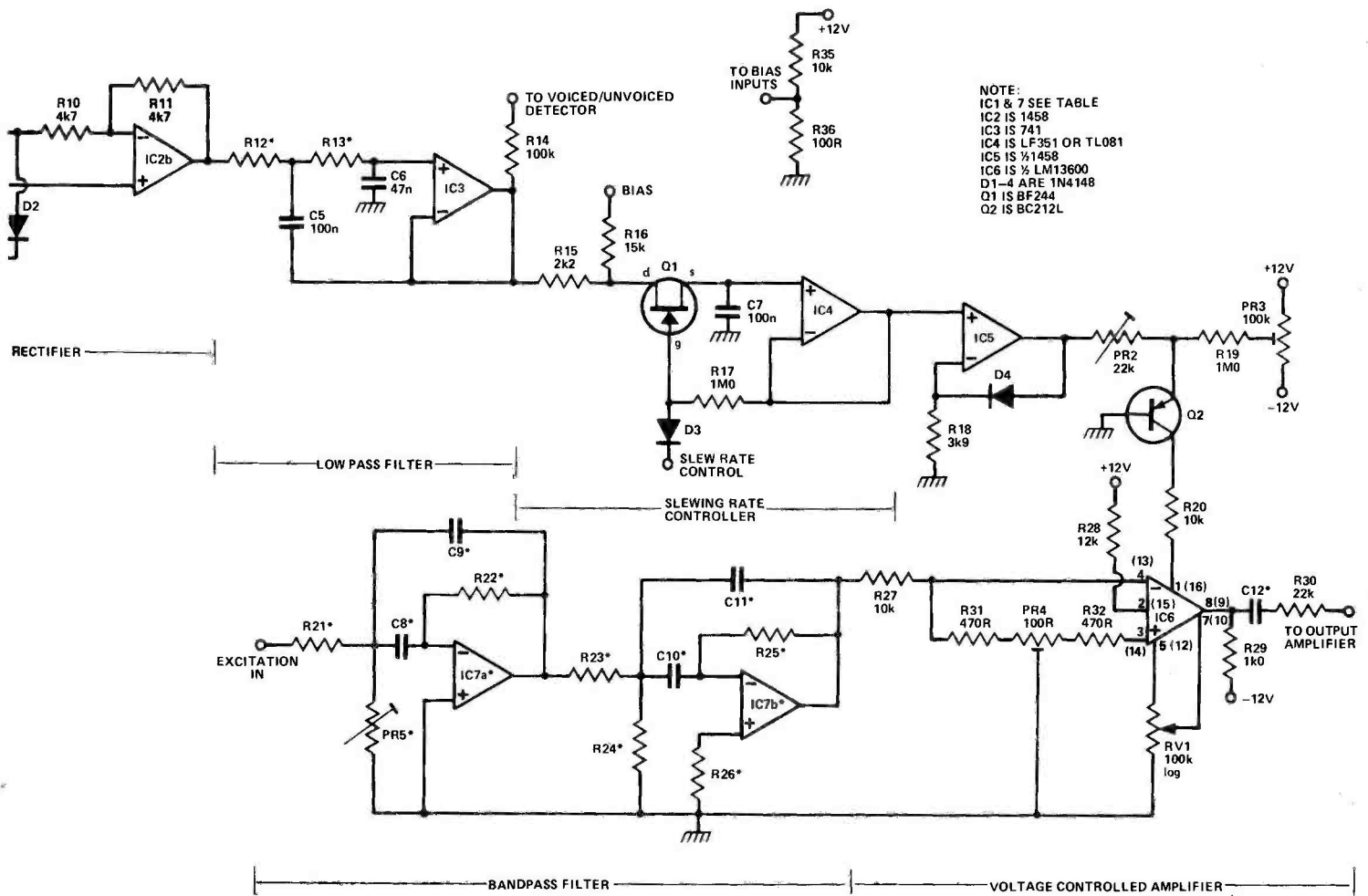


Fig.5a(above). Circuit diagram of analysis/synthesis section.

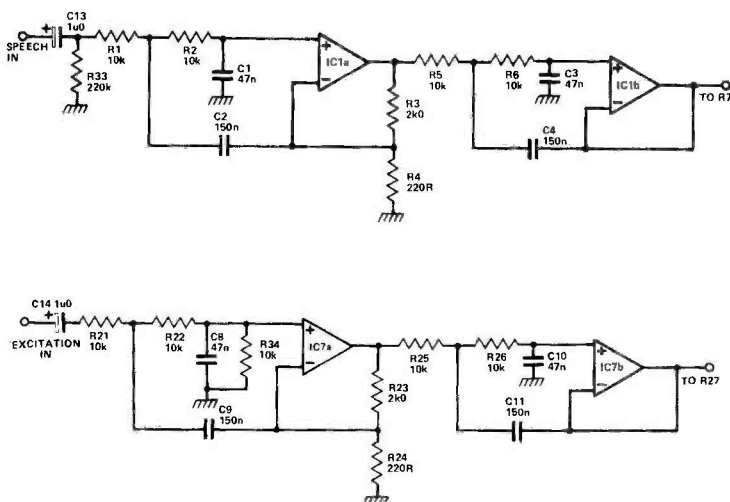


Fig.5b. In channel 1 band pass filters are replaced by the low pass filters shown above.

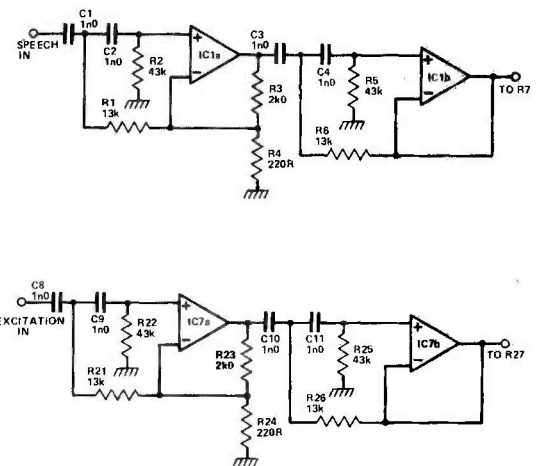


Fig.5c. In channel 14 band pass filters are replaced by the high pass filters above.

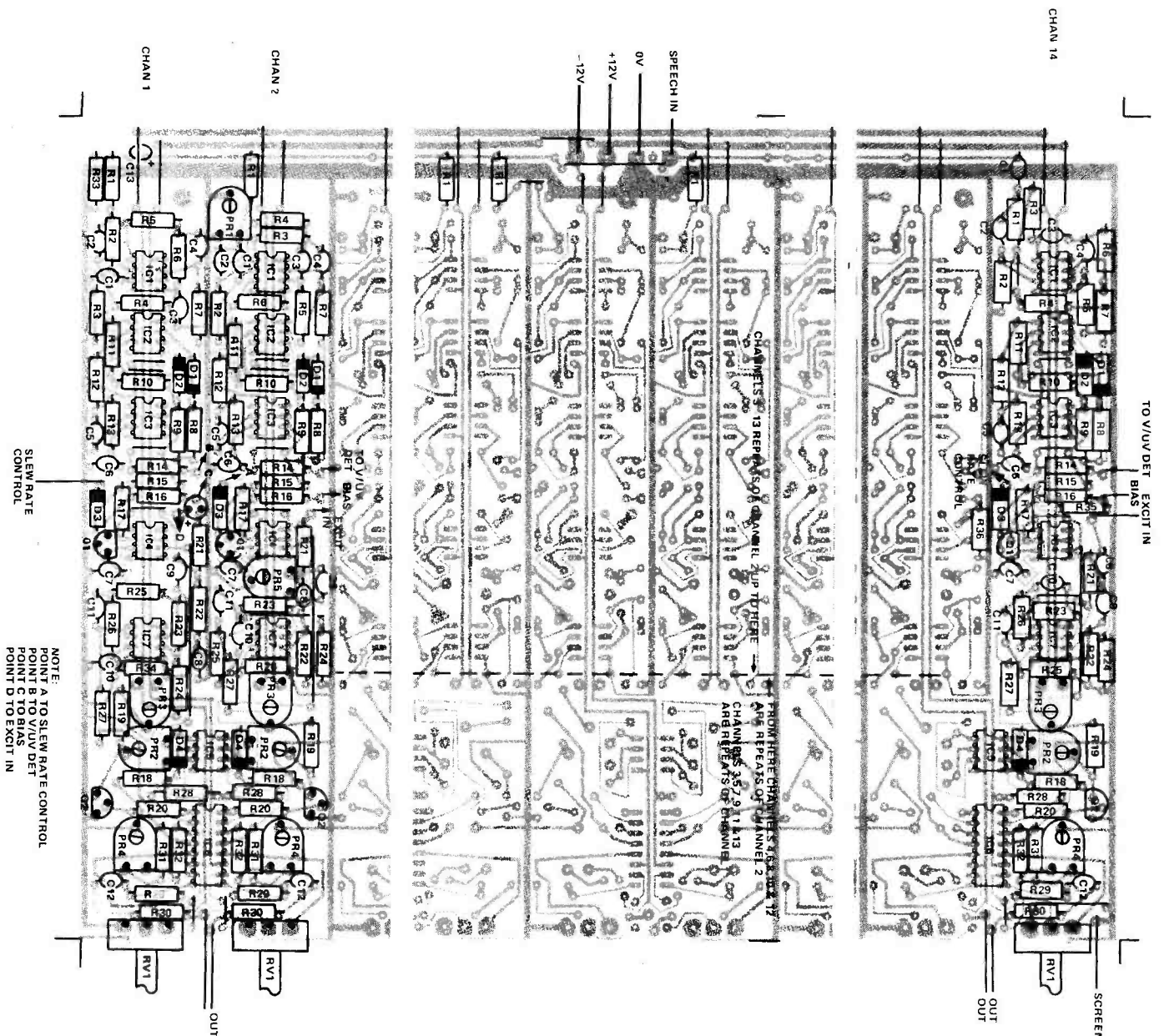


Fig. 6. Component overlay of the analysis/synthesis section. We haven't shown the whole board, as the channels are very similar. The three parts of the board (above) show channels 1, 2 and 14 and the power connections in the middle.

PARTS LIST

PARTS COMMON TO ALL CHANNELS

RESISTORS ALL 2% METAL OXIDE

R1-7, 21-26	see Table 1
R8,9,10,11	4k7
R12,13	see Table 1
R14	100k
R15	2k2
R16	15k
R17,19	1M
R18	3k9
R20,27	10k
R28	12k
R29	1k
R30	22k
R31,32	470R

POTENTIOMETERS

RV1	100k logarithmic
PR1,5	see Table 1
PR2	22k preset
PR3	100k preset
PR4	100R preset

CAPACITORS

C1-4,8-12	see Table 1
C5,7	100n polycarbonate
C6	47n polycarbonate

SEMICONDUCTORS

IC1,7	see Table 1
IC2,5*	1458
IC3	741
IC4	TL081 or LF351
IC6*	LM13600

D1-4	1N4148
Q1	BF233C
Q2	BC212L
*only 1/2 of IC used in each channel	

PARTS SPECIFIC TO CHANNEL 1

R33,34	220k
C13,14	1u0 tantalum

PARTS SPECIFIC TO CHANNEL 14

R35	10k
-----	-----

PARTS SPECIFIC TO CHANNEL 13

R36	100R
-----	------

MISCELLANEOUS

IC sockets, 4 way connector, connector pins.

CHROMASONIC electronics

56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON N10 3HN
TELEPHONE 01-883 3705, 01-883 2289

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS

PETS

2001-8N (8K RAM)

£399

2001-16N (16K RAM) **£499**

2001-32N (32K RAM) **£599**


**ALL WITH NEW KEYBOARD
AND GREEN SCREEN**

PERIPHERALS

Service & Assistance available.

Interfaces available are:

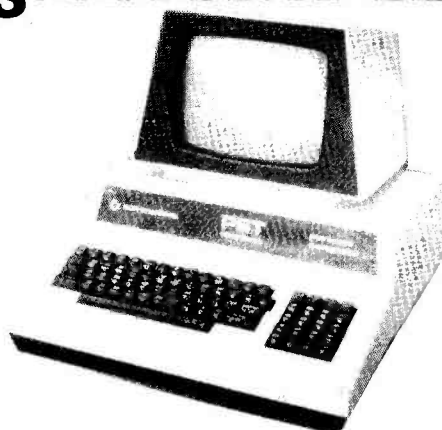X-Y Plotters, Analogues to Digital Converter external cassette deck suitable 16 channel interfaces. Bi-directional interfaces etc.



FOR ALL PETS **£55**

UK101

NEW LOW PRICE

£179 IN KIT FORM

£229 READY BUILT & TESTED


£249 COMPLETE IN CASE

No extras required 8x2114 **£22.50**

- ★ Free sampler tape
- ★ Full Querty keyboard
- ★ 8K basic
- ★ Ram expandable to 8K on board (4K inc)
- ★ Kansas City tape interface

**ASSEMBLER
EDITOR
TAPE
£14.95**

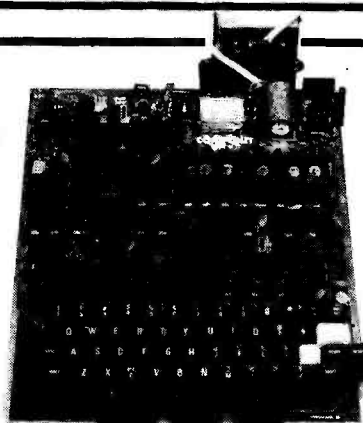★ NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL **£22.00**



MEMORY

D.RAMS	£	p
4027	2.75	
4050 (350NS)	2.35	
4060 (300NS)	2.39	
4116	4.35	

S. RAMS	£	p
2102A	1.09	
2102A2	1.09	
2112A	2.25	
21L02	.98	
2114-4045	2.95	
4035	1.07	
4044-5257	6.93	

BULK PURCHASE	£	p
8.2114	22.50	
8.4116	29.95	
8.21L02	7.00	

BULK PURCHASE	£	p
16 2114	39.95	
16 21L02	13.00	
32 21L02	25.00	
64 21L02	45.00	

EPROMS

2708	4.95
2716 (5v)	13.95
2532	39.95

ROMS

2513 (UC)	5.95
2513 (LC)	5.95

CPUS

6502	9.50
8080	4.75
9900	25.95
6800	5.90
Z80	8.95

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.75
8T28	1.75
8T95	1.57
8T96	1.57
8T97	1.50
8T98	1.57

BAUD RATE GENS

MC14411	8.75
MM5307	8.75

UARTS

AY-5-1013	3.45
AY-3-1015	3.98
MM5503	4.75
6011	3.55

LATEST STOP PRESS AND PRICE LIST

Send sae or phone for up-to-date **PRICES** of all our range of items stocked

CASES

Available for
U.K. 101, Superboard
Nascom,
Appx. DIM. 17" x 15"
435 x 384 mm

PRICE £24.50

P. packing £1.50.

TAPES

Unique stackable tape
storage unit. Interlocking
drawers.
45 drawers each containing 2
C12 tapes

10 drawers **£9.50**
5 drawers **£5.25**
Single drawer **£1.10**

MEMORY EXPANSION KIT

Suitable for UK101, Superboard
expansion using 2114's each board
has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£99.95**
- ★ 16K kit **£139.90**

PRINTERS

TX-80 £395

EPSON TX-80 £395

Dot-matrix printer with Pet
graphics Interface: Cen-
tronics parallel, options: PET,
Apple and serial.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard. (Min. tel order £5). Trade and export enquiries welcome, credit facilities arranged.



Interface Components

ALL PRICES ARE EXCLUSIVE OF VAT

TRANSISTORS			REGULATORS		
AC128	15p	BCY71	12p	7805	57p
AC187K	30p	BCY72	12p	7815	57p
AC188K	30p	BF179	25p	7815	57p
AC17	90p	BF183	25p	7824	57p
AD149	55p	BF200	29p	7905	140p
AF127	35p	BF336	33p	7915	140p
AS217	120p	BFX30	32p	7915	140p
AU113	150p	BFX86	26p	7918	140p
BC107	7p	BFX88	22p	7924	140p
BC108	7p	BFY50	13p	LM320T5	149p
BC108A	7p	BFY51	13p	LM320T8	149p
BC108C	7p	BFY64	28p	LM320T15	149p
BC136	15p	BFY90	56p	LM320T18	149p
BC140	28p	BSX19	80p	LM340T5	74p
BC141	30p	BSY95A	16p	LM340T8	74p
BC142	25p	BU204	149p	LM340T15	74p
BC143	28p	BU208	150p	LM340T18	74p
BC147	6p	OC29	89p		
BC147B	6p	OC43	50p		
BC149	7p	2N696	15p		
BC149C	7p	2N930	20p		
BC159	9p	2N1132	19p		
BC160	35p	2N1304	40p		
BC167A	10p	2N1613	12p		
BC178	12p	2N1711	15p		
BC179	12p	2N2217	20p		
BC182	8p	2N2219A	20p		
BC182L	9p	2N2221	18p		
BC183	9p	2N2368	15p		
BC183L	9p	2N2369	14p		
BC184L	9p	2N2894A	20p		
BC186	20p	2N2904	15p		
BC212	9p	2N2904A	15p		
BC212L	9p	2N2905	15p		
BC213B	9p	2N2906	15p		
BC327	13p	2N2926Y	10p		
BC328	13p	2N2926O	10p		
BC337	16p	2N2926R	10p		
BC338	11p	2N3442	102p		
BC440	32p	2N3702	8p		
BC547	9p	2N3704	8p		
BC548	9p	2N3705	8p		
BC550	14p	2N3708	8p		
BC558	12p	2N3709K	8p		
BCY33	99p	2N3866	35p		
BCY34	99p	2N3906	10p		
BCY39	229p	2N4058	12p		
BCY58	16p	2N4427	60p		
BCY70	12p	Add VAT			

DIODES			TRIACS		
AA119	10p	4A 400V	54p		
BA154	9p	4A 600V	60p		
BA156	9p	6A 400V	60p		
IN4001	4p	6A 600V	66p		
IN4002	4p	8A 400V	66p		
IN4003	5p	8A 600V	72p		
IN4005	5p	10A 400V	72p		
IN4006	6p	10A 600V	84p		
IN4007	6p	15A 400V	108p		
IN4148	5p	15A 600V	126p		
IS44	3p	with internal trigger diac			

OPTO		
Leds		
125 Red	8p	
125 Green	12p	
125 Yellow	12p	
2 Red	10p	
2 Green	10p	
Displays		
704	110p	
741	160p	
747	160p	
750	160p	

BRIDGE RECTIFIERS		
50V	100V	200V
4A 45p	52p	60p
4A 52p	60p	68p
6A 60p	68p	75p
6A 60p	88p	90p
25A 105p	125p	150p

RETAIL SHOP AND MAIL ORDER
WE STOCK A WIDE RANGE OF
 ★ Semiconductors ★ Resistors ★ Capacitors ★ Soldering
 Irons ★ tools ★ VERO products ★ OK Machine Tool Co.
 Products ★ Microcomputers ★ Peripherals including
 Nascom, PET, Sharp.
 ★ Large range of Microcomputer books

INTERFACE COMPONENTS LIMITED
OAKFIELD CORNER, SYCAMORE ROAD, AMERSHAM, BUCKS HP6 6SU
TELEPHONE: 02403 22307. TELEX: 837788
 Write, telephone or call. Access or Barclaycard accepted

VALVE BARGAINS

ANY 5-80p, 10-£1.50, 50-£6.
 Your choice from the following: ECC82, EF80, EF183, EF184, EH90, RCF80, PCF802, PCL82, PCL85/805, PL504, PY800, PY88, PFL200.

COLOUR TV VALVES. PL508-PL509/519 — PY500/A-PL802. All tested 65p each.

100-MULLARD C280/C281 CAPACITORS. Values from .01uf to 1.5uf 250V/W. Our choice. Good mixed selection. Price per 100 £2.

SIGNAL INJECTORS with (Pre-set) variable AF, which emits RF Harmonics into the UHF band. Protected up to 300 volts DC. Complete with leads £5.70 each.

All prices include VAT at 15% P&P per order 30p. S.A.E. for Leaflets. Access Cards accepted.

AERIAL AMPLIFIERS

Aerial Amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 — For Mono or Colour this is tunable over complete UHF television band.

B11 — For Stereo or Standard VHF / FM Radio.

B12 — For VHF Television Band 1 & 3.

All Amplifiers are complete and ready to use.
 Battery type PP3 or 8v to 18v DC, next to the set type fitting. **Prices £5.70 each.**

ELECTRONIC MAILORDER LTD.

62 Bridge Street, Ramsbottom, via Bury, Lancs.
 Tel. RAMS 3036

TANGERINE

Build your own Computer Kits,
 available from **£79.35**

Assembled and tested from £90.85

S.a.e. or telephone

MICRO-PRINT LTD.

21 Bankhouse Road, Hanford
STOKE-ON-TRENT
 (0782) 657893

for advice / assistance and Order Forms
 Prices include V.A.T. Post and packing extra.

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
 Multimeters - Semi Conductors - Timers - Safeblocc

Minimum & Sub Miniature			
Volts	Milli-amps	Ref. Price	P&P
3-0.3	200	238 2.55	.65
0.6-0.6	1A 1A	212 2.95	.70
9-0.9	100	13 2.25	.65
0.9-0.9	330 330	235 2.10	.65
0.8-0.8-9	500 500	207 2.70	.70
0.8-9-0.8-9	1A 1A	208 3.80	.70
0-15-0.15	200 200	236 2.10	.65
0-20-0.20	300 300	214 2.70	.85
20-12-0-12-20	700(DC)	221 3.45	.85
0-15-20, 0-15-20	1A 1A	206 4.55	1.00
0-15-27, 0-15-27	500 500	203 4.00	.85
0-15-27, 0-15-27	1A 1A	204 6.05	1.00

12 AND/OR 24 VOLT			
12v	24V	Ref. Price	P&P
0.5	0.25	111 2.25	.70
1.0	0.5	213 2.70	.85
2	1	71 3.20	.85
4	2	18 4.00	.85
6	3	70 5.55	.90
8	4	108 7.40	1.15
10	5	72 8.20	1.15
12	6	116 8.80	1.15
16	8	17 10.80	1.25
20	10	115 13.80	1.45
30	15	187 16.80	1.45
60	30	226 33.30	1.75

30 VOLT (Pri. 220-240V)			
Sec. 0-12-15-20-24-30V	Ref. Price	£	P&P
0.5	112	2.80	.85
1.0	79	3.55	.85
2.0	3	5.55	1.00
3.0	20	6.25	1.15
4.0	21	8.55	1.15
5.0	51	9.55	1.15
6.0	117	11.05	1.15
8.0	88	14.30	1.45
10.0	89	16.55	1.45

50 VOLT (Pri. 220-240V)			
Sec. 0-19-25-33-40-50V	Ref. Price	£	P&P
0.5	102	3.55	.85
1.0	103	4.55	1.00
2.0	104	7.25	1.15
3.0	105	8.55	1.15
4.0	106	10.80	1.25
6.0	107	15.05	1.45
8.0	118	20.15	1.65
10.0	119	24.05	2.15

60 VOLT (Pri. 220-240V)			
Sec. 0-24-30-40-48-60	Ref. Price	£	P&P
0.5	124	3.80	.85
1.0	126	5.55	1.00
2.0	127	7.50	1.15
3.0	125	11.05	1.25
4.0	123	12.30	1.45
5.0	40	14.10	1.55
6.0	120	17.55	1.55

AUTO TRANSFORMERS

Input / Output Tapped 0-115-210-240V

VA (Watts)	Ref. No.	Price	P&P
20	113	2.60	.85
75	64	4.05	.85
150	4	5.55	1.00

Input / Output Tapped 0-115-210-220-240V

VA	Ref. No.	Price	P&P
300	53	10.05	1.15
500	67	10.80	1.45
1000	84	18.55	1.55

Also 1500/2000/3000VA

MAINS ISOLATING (Centre Tapped & Screened)

Pri: 120/240V Sec: 120/240V

VA (Watts)	Ref. No.	Price	P&P
60	149	6.55	1.00
100	150	7.55	1.25
200	151	11.05	1.25
250	152	13.25	1.45
350	153	16.25	1.55
1000	156	37.05	3.15

Please add VAT at 15%
 Barclaycard and Access facilities
 available
 Trade and Education Welcome

BAYDIS 7a William Street
 Herne Bay, Kent
 Herne Bay 64586

DRILL SPEED CONTROLLER

Keep your electric drill under control with this handy circuit... cheap and simple.

This circuit enables you to control the speed of any appliance that uses a 'universal' motor-drills, sanders, polishers, etc. Only a few components are required and this circuit is just about the simplest that can be built from discrete components. Don't let that put you off though! You get full-wave control from zero to full speed. Who could ask for more?

Construction

We built our unit on its PCB into a standard plastic switch-box and fitted the speed control onto a plastic blanking plate. No heatsink was used on the prototype and one will probably not be required for intermittent use.

Warning

Remember that when running an appliance at low speeds, the efficiency of the cooling fan normally built onto the motor-shaft will be severely reduced. This may result in your motor burning out, so remember to allow the windings to cool when running for an extended period or simply run the appliance at full speed off-load for a short while.

There are no special points to watch with this circuit. A PCB design is given, though any method of construction may be employed. Note that 400 V polypropylene capacitors were used in the prototype as these are better able to withstand connection to the AC mains. Despite its simplicity, this circuit will provide a smooth, wide-range control and amply repays the little effort involved in its construction.

BUYLINES

All the necessary components should be readily available from your usual suppliers. See mail order suppliers advertising in this issue. The polypropylene capacitors are available from Electrovalue Ltd, 28 St Judes Road, Englefield Green, Surrey TW20 0BH.

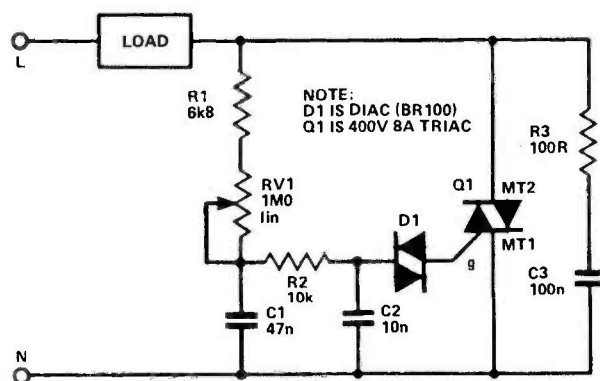
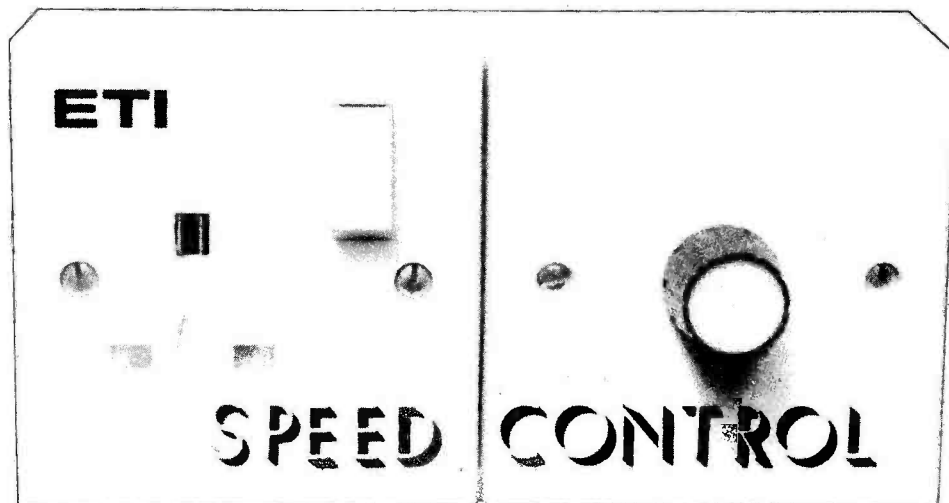


Fig.1. Circuit diagram.

HOW IT WORKS


The essential feature of the circuit is triac Q1. This bi-directional electronic switch controls power flow through the load. This can be any 'universal' motor as may be found powering an electric drill, polisher, etc. The resistor-capacitor combination R3, C3 comprise a snubber network which prevents spurious switching effects in the triac. The triac is turned on when the current flow in its gate — MT1 junction exceeds a certain value. Direction of current flow is unimportant, though there will be a small difference in the sensitivity of the triac, and the device will switch on for both cycles of the alternating mains waveform.

The resistor-capacitor network built with R1, 2, RV1, C1, 2 cause an alternating waveform at mains frequency to appear at the 'hot' end of C2. Adjustment of RV1 controls the phase of this signal with respect to the mains input. When the voltage across C2 exceeds about 30 V, current will flow in the gate circuit of the triac, turning it on. It remains on until the applied mains voltage falls to zero. It then remains off until re-triggered. Dissipation in the triac is low as it is only ever either fully on or fully off and a heatsink is unlikely to be required.

PROJECT: Drill Speed Controller

(Left) The PCB fits snugly into a standard plastic switch box and the speed control is mounted on a plastic blanking plate. A switched power socket completes the picture.

Fig.2 (bottom left). Component overlay

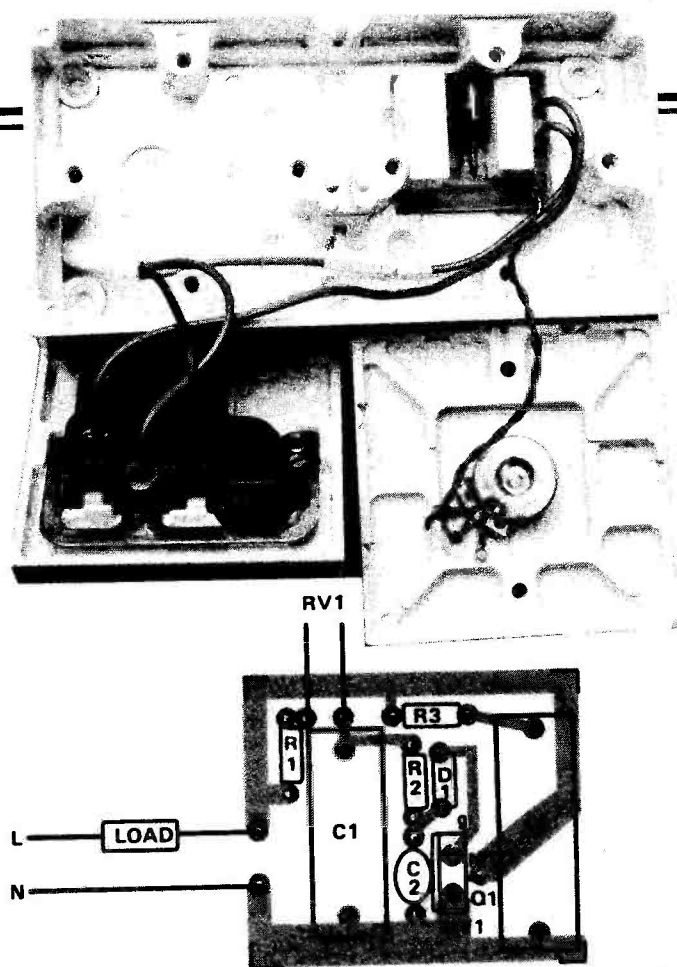

PARTS LIST

Resistors

R1	6k8
R2	10k
R3	100R

Potentiometer

RV1	1M0 linear
-----	------------

Capacitors

C1	47n 400 V AC polypropylene
C2	10n polyester
C3	100n 400 V AC polypropylene

Semiconductors

Q1	8 A 400 V triac
D1	Diac (BR100 or equiv.)

Miscellaneous

Case, PCB, Power Outlet, etc.

ETI

A Range of Performance from... ...HAMEG




PERFORMANCE AND RELIABILITY
ARE THE SEALS FIRMLY STAMPED
ON THE COMPLETE HAMEG RANGE
AND IT IS A COMPLETE RANGE

HM307	Single Trace DC-10MHz Plus Built-in Component Tester	£ 149
HM312	Dual Trace DC-20MHz. 5mV/cm. Full X-Y. 30MHz Trigger. Plus TV Trigger	250
HM412	Dual Trace DC-20MHz. 2mV/cm. X-Y. 40MHz Trigger. Plus Sweep Delay	350
HM512	Dual Trace DC-50MHz. 5mV/cm. X-Y. 70MHz Trigger Sweep Delay. Plus Single Shot. Sweep Delay and After Delay Trigger	580
HM812	Dual Trace as per HM512. Plus Storage. Automatic Storage and Variable Persistence	1325

Prices UK List ex VAT

For FULL DETAILS and
DISTRIBUTOR LIST
Contact

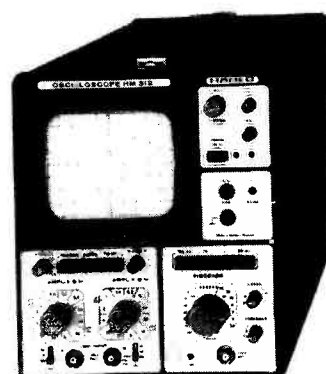Hameg Ltd.,
74-78 Collingdon St.,
Luton,
Beds.
LU1 1RX.



Tel: (0582) 413 174

ETI SEPTEMBER 1980

Buy a microcomputer for under £1,000 and you could be on your own! Unless it's a Commodore PET.



Commodore produce Britain's number one microcomputer. But we don't stop there. We also insist on providing comprehensive support throughout our national dealer network.

Our dealers can examine your needs and demonstrate which hardware and software will suit you best. Their trained engineers are always at hand and a 24-hour field maintenance service is available. Your local dealer can tell you more about the following Commodore Services.

The Commodore PET

The Commodore PET computer range covers everything from the self-contained unit at under £500 to complete business systems at under £2,500.

Commodore Business Software and Petpacks

Our software range covers hundreds of applications. Business software includes Sales and Purchase Ledgers, Accounting, Stock Control, Payroll, Word Processing and more. In addition over 50 Petpacks are available covering such titles as Strathclyde Basic Tutorial, Assembler Development System, Statistics, plus our Treasure Trove and Arcade series of games.

Commodore Approved Products

Compatible products of other manufacturers with Commodore's mark of approval are also available.

Commodore Courses

Commodore offer a range of residential training courses and one day seminars. An excellent start. And when you have installed your system the PET User's Club Newsletter can keep you informed of new ideas and latest developments.

LONDON AREA

Adda Computers Ltd.
W5. 01-579 5845
Advanced Management Systems.
EC2. 01-638 9319
Byteshop Computerland.
W1. 01-636 0647
C.S.S. (Business Equipment) Ltd.
E8. 01-254 9293
Capital Computer Systems.
W1. 01-636 3863
Centralex-London Ltd.
SE13. 01-318 4213
Cream Microcomputer Shop.
HARROW. 01-863 0833
Da Vinci Computer Shop.
EDGWARE. 01-952 0526
L & J Computers.
NW9. 01-204 7525
Home and Business Computers.
E12. 01-472 5107
Merchant Systems Limited.
EC4. 01-353 1464
Metyclean Ltd.
SW1. 01-828 2511
Micro Computation.
N14. 01-882 5104
Micro Computer Centre.
SW14. 01-878 3206
Sumlock Bondain Ltd.
EC1. 01-250 0505
Sumlock Bondain Ltd.
EC4. 01-626 0487
T.L.C. World Trading Ltd.
WC2. 01-839 3894
TOPS TV LTD.
SW1. 01-730 1795

HOME COUNTIES

G.M. Marketing.
ANDOVER. 750922
HSV Microcomputers.
BASINGSTOKE. 62444
MMS Ltd.
BEDFORD. 40601
Elex Systems Ltd.
BRACKNELL. 52929
DDM Direct Data Marketing Ltd.
BRENTWOOD. 229379
Amplicon Micro Systems Ltd.
BRIGHTON. 562163
RUF Computers (UK) Ltd.
BURGESS HILL. 45211
T & V Johnson (Microcomputers
Etc) Ltd. CAMBERLEY. 20446
Cambridge Computer Store.
CAMBRIDGE. 65334
Wego Computers Ltd.
CATERHAM. 49235
Dataview Ltd.
COLCHESTER. 78811
Southeast Systems Ltd.
HASTINGS. 426844
Alpha Business Systems.
HERTFORD. 57423
Brent Computer Systems.
KINGS LANGLEY. 65056
Isher-Woods Business Systems.
LUTON. 416202
South East Computers Ltd.
MAIDSTONE. 681263
Micro Facilities Ltd.
MIDDLESEX. 01-979 4546
J.R. Ward Computers Ltd.
MILTON KEYNES. 562850
Sumlock Bondain (East Anglia) Ltd.
NORWICH. 26255
T & V Johnson (Microcomputers
Etc) Ltd. OXFORD. 721461
H.S.V. Microcomputers.
SOUTHAMPTON. 22131
Super-Vision.
SOUTHAMPTON. 774023
Xitan Systems Ltd.
SOUTHAMPTON. 38740
Stuart R Dean Ltd.
SOUTHEND-ON-SEA. 62707
The Computer Room.
TUNBRIDGE WELLS. 41645
Orchard Electronics.
WALLINGFORD. 35529

Petafect Ltd.
WOKING. 63901
Oxford Computer Systems.
WOODSTOCK. 811976

MIDLANDS AND SOUTH HUMBERSIDE

Byteshop Computerland.
BIRMINGHAM. 622 7149
CPS (Data Systems) Ltd.
BIRMINGHAM. 707 3866
Camden Electronics.
BIRMINGHAM. 773 8240
Computer Services Midlands Ltd.
BIRMINGHAM. 382 4171
Catlands (Computers) Ltd.
BURTON-ON-TRENT. 812380
Ibek Systems.
COVENTRY. 86449
Jondane Associates Ltd.
COVENTRY. 664400
Davidson-Richards Ltd.
DERBY. 366803
Caddis Computer Systems Ltd.
HINCKLEY. 613544
H.B. Computers.
KETERING. 83922
Taylor-Wilson Systems Ltd.
KNOWLE. 6192
Machize Ltd.
LEAMINGTON SPA. 312542
Office Computer Techniques Ltd.
LEICESTER. 28631
Lowe Electronics.
MATLOCK. 2817
Betos (Systems) Ltd.
NOTTINGHAM. 48108
Byteshop Computerland.
NOTTINGHAM. 40576
Keen Computers Ltd.
NOTTINGHAM. 583254
Tekdata Computing.
STOKE-ON-TRENT. 813631
Systems Micros.
TELFORD. 460214
McDowell Knaggs & Associates.
WORCESTER. 427077

YORKSHIRE AND NORTH HUMBERSIDE

Ackroyd Typewriter & Adding
Machine Co. Ltd. BRADFORD. 31835
Allen Computers.
GRIMSBY. 40568
Microware Computers Ltd.
HULL. 562107
Microprocessor Services.
HULL. 23146
Holdene Ltd.
LEEDS. 459459

South Midlands Communications Ltd.
LEEDS. 782326
Yorkshire Electronics Services Ltd.
MORLEY. 522181
Computer Centre (Sheffield) Ltd.
SHEFFIELD. 53519
Electronic Services.
SHEFFIELD. 668767
Hallam Computer Systems Ltd.
SHEFFIELD. 663125

NORTH EAST

Dyson Instruments.
DURHAM. 66837
Curry & Maughan.
GATESHEAD. 774540
Wards (Office Supplies) Group.
GATESHEAD. 605915
Elfton Ltd.
HARTLEPOOL. 61770
Fiddes Marketing Limited.
NEWCASTLE. 81517
Newcastle Computer Services.
NEWCASTLE. 615325
Format Micro Centre.
NEWCASTLE. 21093
Tripoint Associated Systems
Consultants Ltd.
SUNDERLAND. 73310

SOUTH WALES AND WEST COUNTRY

Radan Computational Ltd.
BATH. 318483
Computer Corner.
BAYSTON HILL. 4250
Bristol Computer Centre.
BRISTOL. 23430
C.S.S. (Bristol) Ltd.
BRISTOL. 779452
T & V Johnson (Microcomputers
Etc) Ltd. BRISTOL. 422061
Sumlock Taddon Ltd.
BRISTOL. 26685
Sigma Systems.
CARDIFF. 34869
Office and Business Equipment
(Chester) Ltd. DEESIDE. 817277
A.C. Systems.
EXETER. 71718
Micro Media Systems.
NEWPORT. 59276
J.M. Computer Services Ltd.
NEWQUAY. 2863
Devon Computers.
PAIGNTON. 526303
J.A.D. Integrated Services.
PLYMOUTH. 62616
Business Electronics.
SOUTHAMPTON. 738248
Computer Supplies (Swansea).
SWANSEA. 290047

NORTH WEST AND NORTH WALES

Tharstern Ltd.
BURNLEY. 38481
B + B (Computers) Ltd.
BOLTON. 26644
Preston Computer Centre.
PRESTON. 57684
Catlands (Computers) Ltd.
WILMSLOW. 527166

LIVERPOOL

Aughton Microsystems Ltd.
LIVERPOOL. 548 7788
B.E.C. Computers.
LIVERPOOL. 263 5738
Rockcliff Brothers Ltd.
LIVERPOOL. 521 5830

MANCHESTER AREA

Byteshop Computerland.
MANCHESTER. 236 4737
Computastore Ltd.
MANCHESTER. 832 4761
Cytek (U.K.) Ltd.
MANCHESTER. 872 4682
Executive Reprographic Ltd.
MANCHESTER. 228 1637
N.S.C. Computer Shops Ltd.
MANCHESTER. 832 2269
Sumlock Electronic Services
(Manchester) Ltd.
MANCHESTER. 834 4233
Professional Computer Services Ltd.
OLDHAM. 624 4065
D. Kipping Ltd.
SALFORD. 834 6367
Automated Business Equipment Ltd.
STOCKPORT. 061 432 0708

SCOTLAND

Holdene Microsystems Ltd.
EDINBURGH. 668 2727
Microcentre.
EDINBURGH. 556 7354
Aethrol Consultancy Services.
GLASGOW. 641 7758
Byteshop Computerland.
GLASGOW. 221 7409
Robox Ltd.
GLASGOW. 221 5401
Mac Micro.
INVERNESS. 712203
Thistle Computers.
KIRKWALL. 3140

IRELAND

Softech Ltd.
DUBLIN. 784739
Medical & Scientific Computer
Services Ltd. LISBURN. 77533

To: Commodore Information Centre,
360 Euston Road, London W1 3BL. 01-388 5702

Please send me further information about the Commodore PET.

Name

Position


Address

Intended application

Do you own a PET? YES ☐ NO ☐

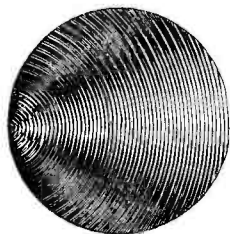 **commodore**


This list covers dealers participating in our advertising



B.K. ELECTRONICS


A SOUND CHOICE

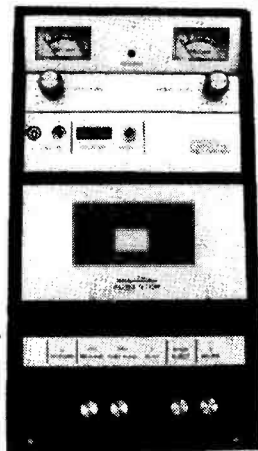★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY




6 piano type keys

STEREO CASSETTE TAPE DECK ASSEMBLY. Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. For horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. **Features:** Pause control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual level controls, twin mic, input sockets, AC erase system, LED record indicator. (Separate power amplifier required.) **Input Sensitivity:** 6 MV (with level control set at max). **Input Impedance:** 47 kOhms. **Output Level:** To both left and right hand channels 150 MV. **Output Impedance:** < 10k. **Signal to noise ratio:** 45 dB nominal. **Power Supply Requirements:** 12V AC at 300mA. **Connections:** All connections to the unit are via a wander lead terminated with a nine pin plug (socket provided). **Dimensions:** Top panel — 1 1/2 in x 6 1/2 in. Mechanism fits through a cut out 5 1/4 in x 10 1/4 in. Clearance required under top panel 2 1/4 in. Supplied complete with circuit diagram etc. **Price £30.50** plus £2.50 postage and packing. Suitable mains 12-volt transformer, **£3.00.**

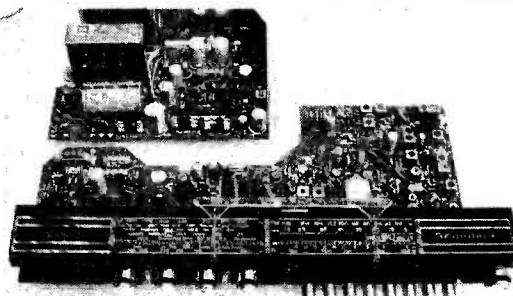

GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc, AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3 dB.


Tape Sensitivity: Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz — 108MHz. Long wave 145kHz — 108kHz. Medium wave. 520kHz — 1620kHz. Short wave. 5.8MHz — 16MHz. **Size:** Tuner — 2 1/4 in x 15 in x 7 1/2 in approx. Power amplifier — 2 in x 7 1/2 in x 4 1/2 in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £21.50** plus £2.50 postage and packing.

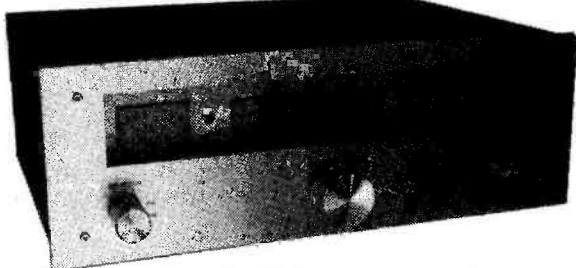

SCOTT AM/FM STEREO TUNER MODEL 516. This Scott tuner is one of the top American makes and is offered at a very realistic price. **Features:** ★ FM tuning range 87.5 to 108 MZ ★ AM tuning range 535 to 1605 kHz ★ Usable FM sensitivity 6.2dBF 2.2μV ★ 300 ohm & 75 ohm Aerial inputs for FM ★ Signal strength tuning meter ★ Stereo beacon indicator ★ Ferrite aerial for AM ★ Mute switch, 10 diodes, 9 transistors and 3 ICs. **Size:** Height 5in, Width 14 1/2 in, Depth 12in. Silver front panel. Black body. Modern stacking format. Suitable for 240-volt 50Hz AC operation. **Price £40.50** plus £2.50 postage and packing.

PIEZO ELECTRIC TWEETERS — MOTOROLA

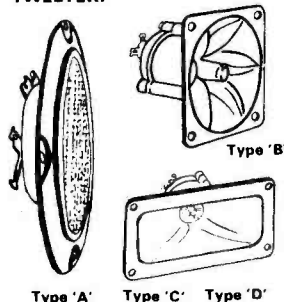Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.75 each;**
Type 'B' 3 1/2 in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.60 each.**
Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £6.20 each.**
Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £9 each.**
Post and Packing, all types, 15p each (or SAE for Piezo leaflets).



JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge. ★ 'S' shaped tone arm. ★ Belt driven. ★ Full size 12in platter. ★ Precision calibrated counterbalance weight (0.3 grms.) ★ Anti-skate (bias) device. Nylon thread weight. ★ Damped cueing lever. ★ 240V AC operation, (50Hz). ★ Cut-out template supplied. **Size — 12 1/4 in x 15 1/4 in (approx).** **Price £29** plus £2.50 postage and packing.

DE-SOLDERING PUMP



This de-soldering pump made to a very exacting specification is ideal for the removal of small components from printed circuit boards, etc. Comes complete with spare PTFE tip. **£5.30** post free.


B.S.R. P163 BELT-DRIVEN TURNTABLE

This famous B.S.R. turntable is ideal for both disco and hi-fi use where a more rugged unit is required.

★ 'S' shaped tone arm
★ Belt driven
★ Slide-in cartridge carrier
★ Calibrated styli pressure gauge
★ Calibrated anti-skate device
★ Damped cueing lever
★ 240v. 50Hz AC operation
Size approx. 11 1/4" x 13 1/4" £22.00 + £2.50 P/P. Suitable magnetic cartridge type TTC/J2203.
Price £4 post free. (Also available separately)

LOUDSPEAKER

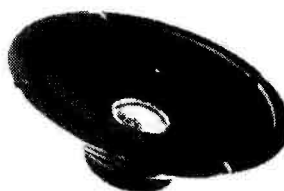High quality full range 8" loudspeaker. 10 watts RMS. 8OHM. Rolled surround with aluminium centre dome.
Price £3.75 each + 75p Postage and Packing each.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.

Access and Barclaycard accepted

TV SOUND TUNER

Enjoy high quality TV sound with this unit, using pre-aligned commercial modules for simple construction.



The BBC frequently 'simulcasts' the sound channel of some of its television music presentations. As well as providing stereo, this gives a dramatic improvement in sound quality. In fact TV sound is transmitted with frequency modulation and can provide good quality (though in mono). The weak link in the system is the TV audio stage and small loudspeaker.

This unit enables you to feed a high quality TV audio signal into your hi-fi; so you will not have to chip your speakers from their concrete columns or mount the TV in the fireplace (even though the chimney does provide an excellent ventilating system!) Use of ready built and aligned modules makes the project very easy to build and it is not expensive!

Tuner Control

An ELC1043 varicap tuner and IF board are bought separately (see 'buylines') and assembled. A handful of other components mount on our PCB and provide power supplies and an optional monitor amp. The varicap tuner is controlled by a single tuning voltage of 0-30 V. We used a surplus push-button station selector unit but any source of a stable voltage may be pressed into service. If you are really up to date, you can even tune the system with your home computer.

Construction

The tuner mounts directly on the IF board. All the holes are there, as well as quite a few spares, though you will need to enlarge the holes for the screening can lugs. Two resistors set the AGC voltage and a capacitor filters the tuning voltage. Be

careful when dealing with the IF board not to disturb any of the adjustments. Remember the units are pre-aligned.

To The Manor Borne

We had our board running within an hour but then it failed mysteriously. Manor quickly sorted us out and sent us away with strict warnings about playing football with the board! Remember that the TV signal comes in on a wing and a prayer at a few hundred MHz and even the IF operates at 38 MHz so show it some respect.

Construction of the PSU and amplifier PCB is straightforward. Take special care to connect the screening braids as shown to avoid hum pick-up. When the unit is assembled into its case, with an aerial connected, a station should be tuned in. A slight buzz may be present. This can be nulled out by adjusting the tuning control whilst making slight adjustments to the quad coil. This is preadjusted and should not need to be moved more than a turn to compensate for the effects of added stray capacitance from the case, etc.

Home Programming

Two versions of the tuner front-end are available. They are interchangeable. Our prototype used the cheaper GI device and we were unable to make any comparison with the more expensive Mullard unit. You pay your money and you takes your choice. Whichever you choose, this project will reward you with quality TV sound. We cannot help with the programmes . . .



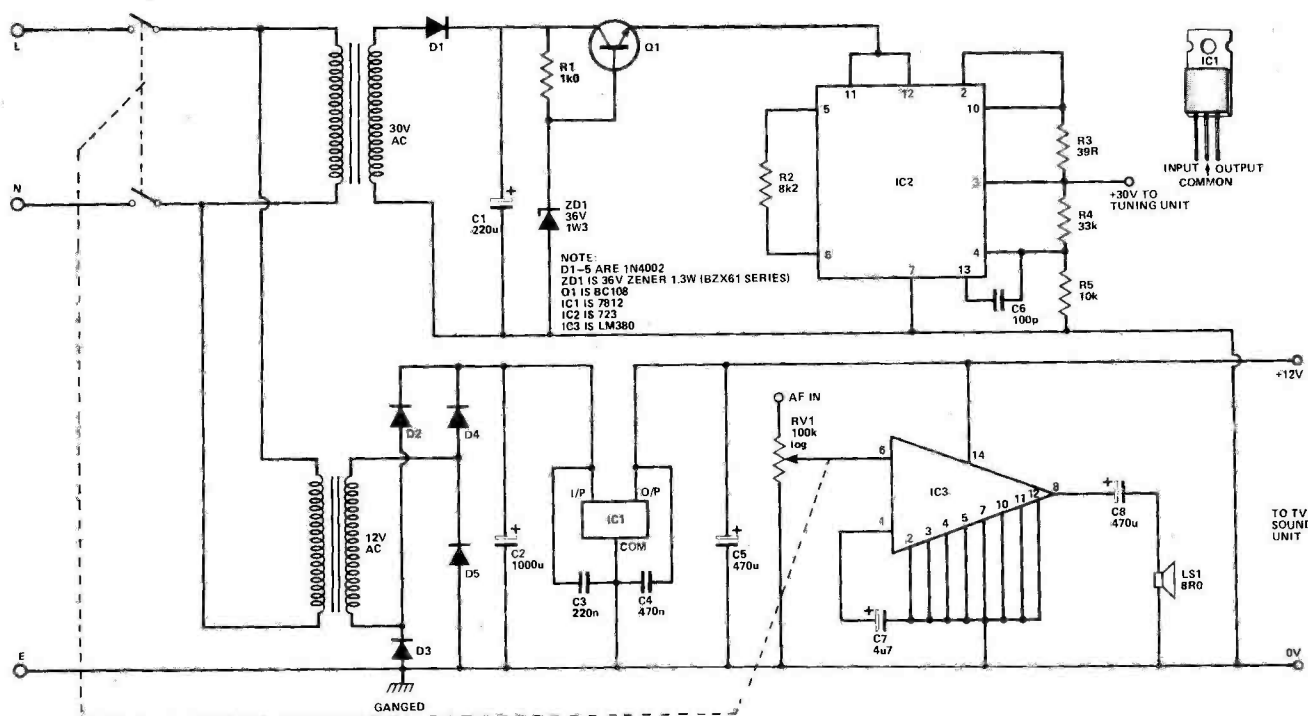


Fig.1. Circuit diagram.

HOW IT WORKS

The TV signal is converted from its UHF carrier frequency down to a more manageable 38 MHz intermediate frequency (IF) by the varicap tuner module ELC1043. 'Varicap' refers to the variable capacitance diodes which replace mechanical tuning capacitors in the front end. The capacitance of the diodes varies according to the reverse bias voltage applied to them. All diodes exhibit this effect but varicap diodes are optimised for operation as capacitors. A relatively high voltage is required and an extra 30 V supply is generated (channels 21 to 34 can be tuned with 0 to 12 V supply).


The output from the tuner module is coupled to the IF stage via a 1n0 capacitor. Our unit came with the capacitor mounted in place — a small disc ceramic is fine. The two cans on the IF sub-assembly are Philips G8 colour receiver modules. Their output is coupled to the TAA570 detector via a 6 MHz ceramic filter which removes the video signal but passes the 6 MHz FM sound carrier. Keep your wiring away from this area of the board. If you touch a finger to the ceramic filter you will hear a variety of AM broadcast stations come booming through! The audio output is coupled via a 1uF electrolytic capacitor.

Note that a video signal is available from the IF board. Although it has a reasonable level — around 1V0 peak-to-peak — you will need to buffer the signal before attempting to use it. Refer to the G8 service manual for suitable circuitry.

Both the tuner and IF board are supplied pre-aligned. A 100nF capacitor is added to the board to filter any track noise from the tuning control and two resistors are used to preset the AGC for optimum gain. A TAA570 detects the sound signal and produces an AF output of a volt or so. This signal will drive your hi-fi directly or via a resistive divider if the amplitude is too high. We incorporated a simple monitor amplifier in our design.

The power supply is quite conventional. A 30 V AC winding is half wave rectified producing a DC voltage of about 43 V. This is pre-regulated by the circuitry around Q1 to reduce the supply below the 40 V absolute maximum required by IC2. This is a 723 regulator chip connected to provide a stable nominal 30 V supply for the station control unit which feeds the tuning voltage to the TV front end.

Output current is limited to about 20 mA though in normal operation only about 1 mA or 2 mA will be drawn. A 12 V AC winding is rectified and regulated with a 7812 IC regulator. This supplies the IF board (about 100 mA) and an on-board monitor amplifier — the LM380. If you do not require an amplifier then omit RV1, IC3, C7,8 and the loudspeaker. Note that IC1 runs rather warm and should have a small heatsink fitted. Although we used a surplus TV station selector unit, any multiturn pot(s) may be pressed into service. 100k units work well.

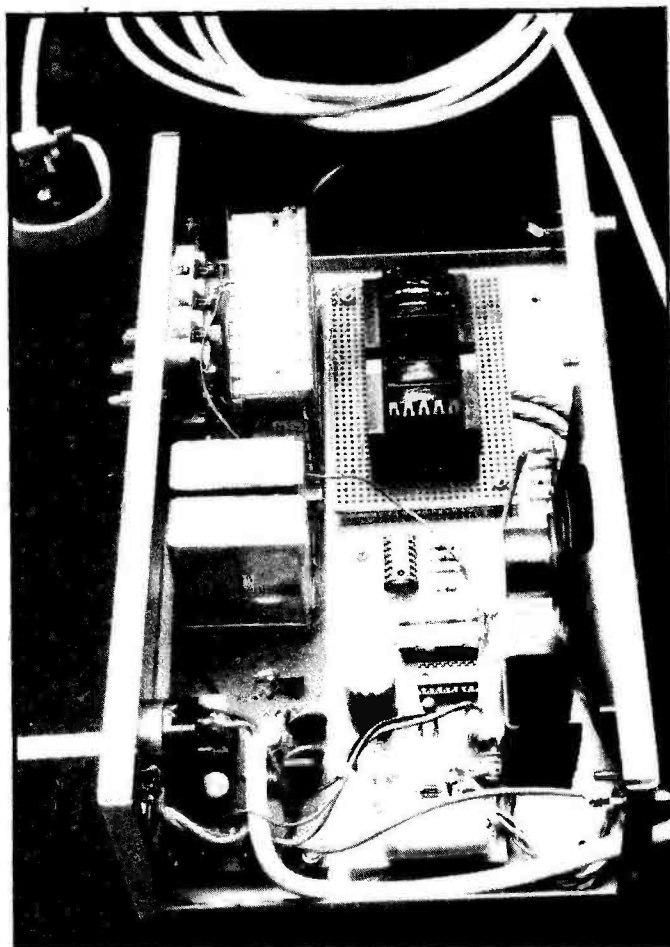

The ready-built IF sub-assembly fits along the front of the case, with our monitor amp behind.

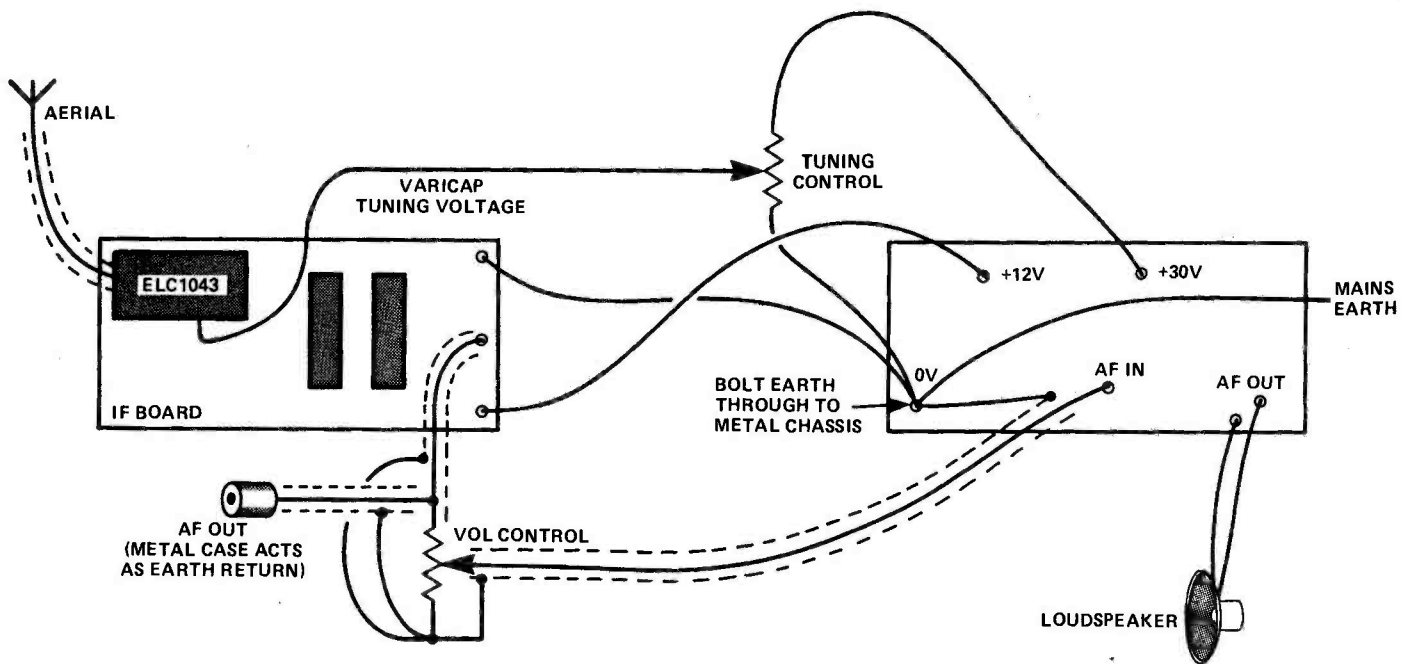


Fig. 2. Connections between our amplifier and the ready-made IF board.

PARTS LIST

Resistors All 1/4W 5%

R1	1k0
R2	8k2
R3	39R
R4	33k
R5	10k

one 6k8 and one 2k2 resistor are required to set the AGC level.

Potentiometer

RV1	100k log.
-----	-----------

Capacitors

C1	220u 63V electrolytic
C2	1000u 25V electrolytic
C3	220n polyester
C4	470n polyester
C5,8	470u 25V electrolytic
C6	100p ceramic
C7	4u7 tantalum

one 100n capacitor is required to filter the tuning voltage.

Semiconductors

IC1	7812
IC2	723
IC3	LM380
Q1	BC108
D1-5	1N4002
ZD1	36V zener 1.3W (BZX61)

Miscellaneous

12V transformer, 30V transformer, heatsink, loudspeaker, varicap tuner, IF board, case.


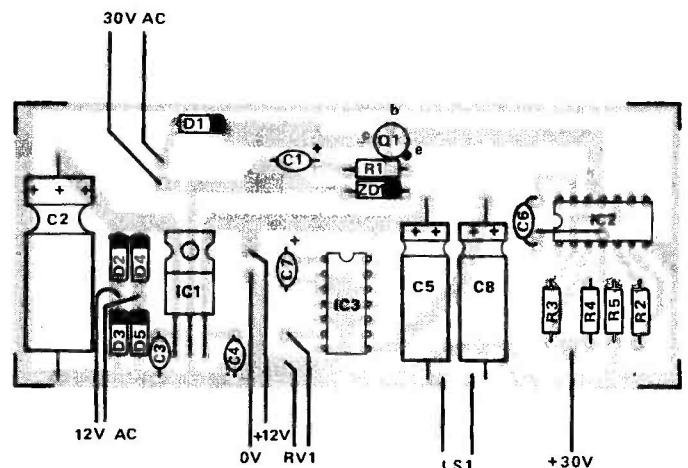


Fig. 3. Component overlay.

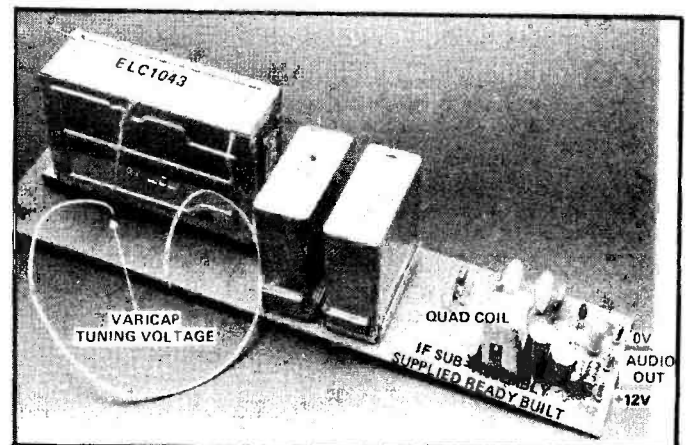

The UHF tuner mounted on the IF sub-assembly.

BUYLINES

The ELC1043 varicap UHF tuner and IF sub-assembly are available from:
 Manor Supplies,
 172 West End Lane,
 London NW6.
 Tel: 01-794 8751.
 They can also supply a suitable push-button station control unit.

Happy Memories

4116 200ns	£3.95	4116 150ns	£5.50
2114 200ns	£3.95	2114 450ns	£3.45
2708 450ns	£4.95	2716 5 volt	£10.95

MEMOREX mini discs soft sectored
£19.95 per ten with free library case


WE'VE MOVED

All prices include VAT, 30p postage on orders below £10
Access and Barclaycard
All orders to:

Dept. ETI
HAPPY MEMORIES
Gladestry, Kington
Herefordshire HR5 3NY
Telephone (054422) 618

NASCOM OWNERS

MICROPROCESSOR CASE

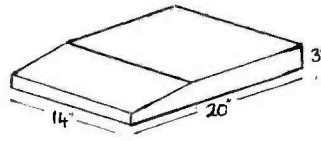

£22 + VAT

AT LAST... A Case you don't have to lever your Micro into. Made from 16 Gauge Aluminium, strong enough to support a Monitor and Cassette. Enough space for Keyboard, P.S.U. Mainboard AND two Expansion Boards (Can also be used for other type Micros., etc.).

Send cheques or POs for £25.30 to:

CYBER ELECTRONICS CO. LTD.
Pavement Square, Addiscombe, Croydon CR0 6RD
(Trade enquiries welcome)

ASCII CODED KEYBOARD £47.15

Designed for ease and accuracy of use, with 60 keys arranged in stepped rows, auto repeat and 2-key rollover. UC and LC ASCII coding. S.a.e. for data.

THE ZX80 MAGIC BOOK £4.75

15 plus programs including Hammurabi, Animals and Othello. Programming tips. Hardware notes. Memory extension circuit.

ZX80 I/O and Memory Boards. S.a.e. for details

All prices inclusive of VAT, p&p

TIMEDATA Ltd.

57 Swallowdale, Basildon, Essex

TTL
CMOS
74LS
LEDS

LB ELECTRONICS

LINEAR
RAMS
EPROMS
SURPLUS

TELEPHONE:
UXBRIDGE 55399

PCB OFFERS

(1A) 100 bit shift register PCB, 115mm x 94mm containing 9x 7491, 6x 7496 and 1x 7441. Terrific bargain 85p. p&p 30p.
(1C) PCB 215mm x 290mm 12xTMS 3122J (or sim.) Hex 32-bit Shift Reg. + 39 ICs £2. + 50p p&p (limited stocks).

MPU CORNER

2122 (200ns), £3. 2114 (450ns) £4.50.
1702 £2.50. 2708 (400ns) £4.50.
74125 for £1 + p&p 25p
MK 1002P (dual 128 bit Shift Reg) 35p.
LM711CH (Voltage Comparator) 30p.
MM5240 Character Generator + Data 2560 Bit (64 x 8 x 5) £3.50, p&p 25p.
(All Full Spec)

2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 25p
International rectifier **SOLID STATE RELAY** type A2402. Out. put 240 VAC 2.5 amps input 90-240 VAC/45-200 VDC £6.00 p/p 25p.

D TYPE CONNECTORS

15 Way wirewrap plugs only 75p.
25 Way ribbon plugs £1.20.
25 Way sockets (solder) £1.00.
50 Way skt (wirewrap) £1.65.
50 Way skt £1.45, p&p 25p.

COVERS

37 Way 80p. (plastic) p/p 25p.

DISPLAYS

HP 5082 4 digit DIL display full spec £1.50 each p&p 25p. Large quantities POA
MAN 727 7 seg CC £1.25 p&p 25p
Burroughs Paraplex 9 Dig. + skt and bezel £1.00, p&p 25p
LED 3 Digit DIL 55p, p&p 25p.
Bowmar 9 digit 1in LED with red bezel. (As used in calculators) £1.00 + 25p p&p

SUPERSAVER

Ribbon Cable Headers 16 DIL Jermyn, gold plated, with cover 45p, p&p 25p.

SUPERSAVER 2

Tantalum Capacitors 25 volt. 4.7 uF. 14 for £1.00, p&p 25p.

SUPERSAVER 3

PRICE SMASH FND 500 .5in. LED displays, full spec £50p each, p&p 25p, large quantities POA

SUPERSAVER 4

HYBRID SYSTEMS DAC 371-B 8 Bit. DIL packaged, ideal MPU users with data. £2.95, p&p 25p

SUPERSAVER 5

Battery eliminator **GVDC 200MA 240VAC** input ideal for calculators, radios, etc., give away price 95p each. Large quantities P.O.A.

SUPERSAVER 6

RS 338-383 Miniature Decade Thumbwheelswitch. £1.65, p&p 25p

SUPERSAVER 7

SN74116 Dual 4 Bit latch 75p, p&p 25p.

SN7418 Arithmetic Logic Unit, 80p, p&p 25p

SN74194 4 Bit Register, 50p p&p 25p.

SN74198 8 Bit Shift Register, 75p p&p 25p

SUPERSAVER 8

ITT 4cx 250b brand new full spec £7.50 each p/p 25p.

SUPERSAVER 9

4 digit 7 segment DIL lead displays 4 for £1.50 p/p 25p

SUPERSAVER 10

9 way male/female connector. ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, 35p, p&p 25p.

SUPERSAVER 11

STAR OFFER. Dynamic hand microphone 200 ohm with lead and 5 pin plug. £1.25 (unrepeatable) p&p 30p.

SUPERSAVER 12

TMS 3128NC Static shift register. £1.50, p&p 25p.

SUPERSAVER 13

PL259 (UHF) Elbow Connectors. 50p each, p&p 25p

SUPERSAVER 14

MPU pcb containing 808A, 2708, 2114 x 24 (all socketed) plus 74TTL/LS etc., sorry no circuit diagrams £28.50 each p/p £1.00.

SUPERSAVER 15

5K multivolt trim pots. PCB mounting, per box of 14 £2.50, p&p 25p.

SUPERSAVER 16

Yet another star bargain. Astec UM111E36 modulator 65p each, p/p 25p.

LEDs (Full spec).

TIL209, red 10p. 0.2in, red 12p. 0.2in, green 28p. 0.2in, yellow 28p.

RL54 red Axial lead. 15p. P&p on all above 25p.

VERNITON Ceramic filters type FM4 10.7MHz 45p, p&p 25p.

TRANSISTORS, 80236 40p, BC183L 10p, BF195 10p, SGS 2N3055 30p, p&p on all 25p.

TBA 810S, with data, 85p. 4-way DIL switches, 75p. MC1303 Dual Stereo preamp with data, £1.25. 7in. Nylon cable ties 100 for £1.50. All p&p 25p.

NEW SN76477 (Yes, back in stock). Sound Generator IC (Train, plane, explosion, laser gun etc.), with data £3.25, p&p 25p.

PCB KEYBOARD, 65mm x 82mm, 18 key Clickers less key tops, ideal Hexadecimal use 35p, p&p 25p.

CAPACITOR SCOOP, 1,600uF at 10v. 160uF at 25v. Axial lead. 2 dozen for £1 + 25p p&p.

PAPST min-fans 80mm x 80mm (approx) 220V 50Hz Brand new £8, p&p £1 (limited stocks).

Pewec Boxer. As above but 115v at £4.50 + p&p.

IEC mains chassis plug 75p suitable socket 35p. p&p 25p.

GIVEAWAY

22 pin low profile dill socket, gold plated
12p EACH
p&p 25p

WE STOCK PETS

8K version £599. SAE for the PET SORCERER software lists at discount prices.
We can also offer a 48-hour repair service for out of warranty PETs. Telephone for details PET edge connector 40x04 £1.40 each p&p 25p.

IC HOLDERS (Low-profile)

8 DIL 12p 14 DIL 15p
16 DIL 17p 18 DIL 20p
22 DIL 28p 24 DIL 35p
28 DIL 45p All p&p 35p

WE STOCK a vast range of TTL, CMOS some 74LS. MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers)

RELAYS

ITT 700 ohm Single pole changeover. 45p. BANOR resettable double pole changeover 12V £1. Both p&p 25p.

CIRCUIT BREAKERS

4450v AC 65v DC 0.5A 50p; ditto 7A 80p, p&p 25p.

ALLEN KEYS, 7/16in 5p; 12 for 50p; p&p 25p.

ASR33 (with tape punch reader), generally overhauled. £185.00 inc. of VAT.

Centronics secondhand printers, various types (o/h), phone for your requirements.

MEMOREX 651 dual disk drives complete with power supplies and format electronics (sorry, no data as yet), £350 each inc. of VAT.

Recordall telephone answering machines (GPO) line matching

transformer removed) sold as is from £2 to £10 depending on condition. Fitted with very nice standard cassette deck. With circuit diagrams. SORRY BUT FOR CALLERS ONLY.

Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

FOR THE PROFESSIONAL USER. CP Clare Keyboard switches with buttons (blank) 65p each p&p 25p.

Gould PMA 47/10 015V 3A Brand new 45p p&p £3.50. Many more in stock but in small numbers. Please phone for requirements.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTISEMENTS. PHONE BEFORE ORDERING.

**SURPLUS STOCKS
PURCHASED
FOR CASH**

LB ELECTRONICS
11 HERCULES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND

All enquiries s.a.e. please

New retail premises, now open Mon, Thurs Fri, and Sat, 9.30-6.00. Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 Opposite Master Brewer.



**UXBRIDGE
55399**

All components full spec

1

GENTS QUARTZ LCD, 5-function. Hours, minutes, secs, month, date, backlight.
ONLY £4.95

2

GENTS QUARTZ LCD. SAME AS 1 - Alternative style.
ONLY £4.95

3

QUARTZ LCD Slim Chronograph. 11-function. Hours, mins, secs, 6 digit-month, date, day of week, 1/100 sec stopwatch, split and lap modes, backlight.
ONLY £7.95

4


QUARTZ LCD ALARM. 6 digit, hours, mins, secs, day, date. 24-hour alarm with on/off indicator.
ONLY £8.95

5

QUARTZ LCD Alarm/Chronograph. 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split and lap modes, 12 and 24 hour alarm.
ONLY £12.95

We don't believe you can find better value combined with quality, than these - our special introductory prices. Compare the savings we offer and order now.

①

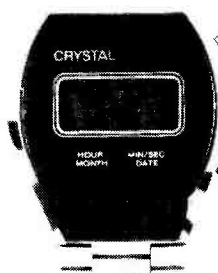

②



③




6

QUARTZ LCD Musical Multi-Alarm/Chronograph. 6-digit. Hours, mins, secs, day, date, 1/100 second stopwatch, split and lap modes, 24 hour alarm, dual time zone.
ONLY £13.45

14 CREDIT CARD CALCULATOR. Very slim with standard 4 functions plus memory, percentage and square root. Complete with a mock leather wallet with credit card pocket.
ONLY £6.95

13 BELTIME 29F. Alarm/Chrono. Advanced and accurate, this watch has 8 time functions, 4 alarm functions and 17 chronograph functions. Complete with backlight and stainless steel bracelet.
ONLY £19.95

④

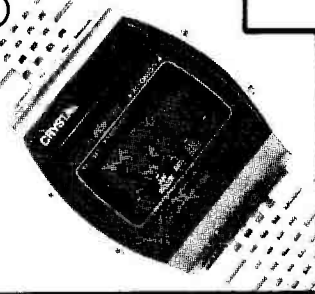

⑤



⑥



7

SINCLAIR PROGRAMMABLE SCIENTIFIC CALCULATOR


Genuine programmable model using micro processor technology, this amazing device is more like a computer than a calculator. Complete with programme library book containing approx. 370 programmes for ELECTRONICS, MATHS, PHYSICS, ENGINEERING ETC. Limited quantity available.

ONLY £7.95
+ 75p carriage.

12

GENTS ANALOGUE QUARTZ. Conventional display, accuracy normally associated with digital watches. Automatic calendar, elegant and robust.
ONLY £19.95

⑦

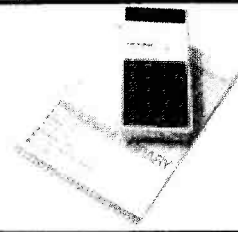

⑧




8

LADIES QUARTZ LCD. 5-function as Gents No. 1. Available with black or white face.
ONLY £5.95

11

LADIES QUARTZ LCD SAME AS 10. Alternative "Round" shape. Available in gold or silver colour.
ONLY £8.95

⑫

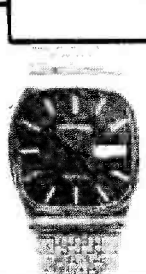

⑬



9

LADIES QUARTZ LCD. SAME FUNCTIONS AS 8. - Alternative style. Available with black or white face.
ONLY £5.95

All watches have fully adjustable, matching stainless steel straps, and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required.

All products carry a Full 7-Day Money-Back Reassurance, plus 12-Month Guarantee. Prices include VAT

10

LADIES QUARTZ LCD. 5 functions. Dress Style. Functions same as 1. Available in gold or silver colour.
ONLY £8.95

⑭



Send stamped addressed envelope for Colour Brochure of 120 other bargains.

DEELMOOR LTD

78 CASTLE STREET,
MELBOURNE, DERBY,
DE7 1DY

Please send me items..... (list numbers)

I enclose cheques/P.O.s for £.....

NAME.....

ADDRESS.....

Please add 35p P/P per item

ETI 4

OLIVETTI PRINTER & KEYBOARD type Te 300
with PUNCH & READER. Upper case ASCII with V24 Interface. 240
volt operation.
£125 each

**INFRA RED IMAGE
CONVERTER type 9606 (CV 144)**
1 3/4" diameter. Requires single low current 3KV to 6KV supply.
Individually boxed. With data
£12.50 each P&P 75p Infra Red Lamps also advertised

**STEPPING
MOTORS**
200 steps — 20 oz./in. torque.
12/24 volt input, 4 wire.
£12 each P&P £1.50

**STEPPING
MOTORS**
200 steps. 20 oz./in. torque.
120 volt operation, 3 wire.
£4 each P&P £1.50

**709 DIL 14 PIN
OPERATIONAL AMPLIFIERS**
at **8p each**
100 off 25% discount

MINIATURE KEYBOARD
Push contacts, marked 0-9 and A-F and 3
optional function keys. **£1.75 ea. P&P 65p**

BLUE THERMAL PAPER
430ft. roll, 8 1/2" wide
£2 per roll. P&P £1.75

**CONVERT THIS UNIT TO A
SUPER BATTERY
CHARGER**

Attractive green ministry quality case with
removable top & bottom plates — heavy
duty power switches—high powered resist-
ors to control current — good quality centre
mounted Amp Meter — strip of wing nut
terminals on front panel which can be used
for connecting leads.

ALL THIS FOR £3.50. P&P £2
FOUR UNITS FOR £12. Carriage £5.

STEPPING MOTORS
North American Philips. 5 volt
3.3 amp operation. 2 wire. PPS
0-200 revs per min. 0-250 used.
Tested.
£16 each P&P £1.50

STEPPING MOTORS
6/12 position with additional where the
rotor is coils. Device can be used as a tacho.
Diagram supplied. Will actually work on 5
volts, 12/24 recommended.
**£1.50 each P&P 75p or 5 for £5 p&p
£1.50.**

RXs 770R used **£100**
730/10 used **£85**
Limited quantity only

**MUST CLEAR
POLARAD SPECTRUM
ANALYSER**
5" Display. These are supplied with STU 2
plug-in 1 to 45 GHZ.
£85 each

**LARGE QUANTITY OF PHOTOMULTI-
PLIERS**
all with information. British approx. 2" window **£2 ea.** British approx. 5" window **£3.50 ea.** American approx. 2" window **£4 ea.** Special American version by RCA **£6 ea.**
P&P all photomultipliers **£1.50 ea.**

BC172	5p	MC4001	15p	TIS92	10p	BC337	8p
82Y8447	10p	MC4012	15p	TIS93	10p	BC327	8p
82Y8813V	10p	MC4020	75p	2N3704	5p	BC251	8p
2N3006	5p	74C20	25p	2N5447	5p	BC171A	5p
1N4305	5p	74C08	25p	2N5449	5p	8FT60	5p
BZX79C12	10p	74C10	20p	2N3053	15p	4013	30p
BC212B	5p	MC4049	35p				
SN76550	10p						
IC 7451	10p						

REGULATORS — att at **45p each.** MC7805, 7812 7815, 7912, 7915.
MC1498L 70p.
16 pin DIL Socket 10p, 14 pin DIL Socket 8p
LED type TIL 209 Red with holder 10p each
SLOTTED OPTO SWITCH supplied with data — normally over £2 OUR PRICE 75p each
ROCKER SWITCHES 2 pole c/o — 15p each
Spring Action Terminals — normally over 30p ea. OUR PRICE 15p each
TOROIDAL TRANSFORMER 0.115V-230V Input 13.5V — 0 — 13.5V rated 8VA output **£1.70 each P&P 75p**
Sub-min TRANSFORMER 0.120-240V Input 12V-0.12V rated 4VA Output 75p each P&P 50p.
L.E.D.s
Standard White 12p, Standard Yellow 15p, Small White 8p.

TRANSISTOR INVERTER
115V AC, 1.7amp Input. Switching is at
20KHZ. Output windings from Pot Core.
Can be rewound to suit own purpose or unit
can be broken for host of components.
Circuit supplied.
£1.25 each P&P £2

KEYBOARD PAD
Size 3 x 2 1/2 x 2" high with 12 Alma Reed
Switches. Blue keys marked in green 0-9
and a star with one blank.
£4 each P&P £1
or **5 for £15 P&P £2**

RXs 770R Mk. II
940
24V INVERTOR VERSION
SPECIAL GOVT. QUALITY

**VER FEW
OF THESE
£175
EACH**
VGC

We still have a large quantity of
**TEST GEAR, OSCILLOSCOPES,
SIGNAL GENERATORS ETC.,
and they are priced to move.**
Callers welcome or write or Better Still PHONE for details
**REMEMBER WE WILL
CONSIDER OFFERS**

**MAGNETOS
NEW BOXED**
Originally for 14 cyl-gipsy
Very adaptable
£4.75 each

**TANTALUM BEAD
CAPACITORS.** 4.7uf
25V. 10 off £1; 100 off
£7.50.
TEXAS Low Profile 40 pin
IC Sockets **45p each.**
**SMALL TRANS-
FORMER.** 240V Input
Output 2 windings 12V &
24V 1 amp. **£2 each.**

SO SIMPLE — SO SAFE
Fit a push button CIRCUIT
BREAKER Small compact
3 ratings 0.8 1.8 &
10AMP State which one
when ordering **75p each.**

AMP METER 2 1/2" dia.
Scaled 0-60. Basic 75MV
FSD. Complete with external
60AMP Shunt. **£2.50
each. P&P £1.50.**

DIODES
All new full spec. devices. IN3063; BAX 13;
IN4148; IS44. 100 off **£1.50 — 1,000 off
£10.**

VARIACS EX Equipment Good condition 8 Amps **£25 ea.**
20 Amps **£35 ea.**
Some 3 phase available. Please enquire

CRYSTALS
19.2KHZ FLAT METAL CASE — **50p each.**
10 MHZ BTG **50p each.**

LOUD HAILERS
Transistorised hand held — no leads — standard internal
batteries supplied. Howl switch
£20 each. P&P £2

TRANSFORMERS Standard Mains input
Secondary outputs
8KV 0.125A **£15 ea.**
3340V 0.66A with matching 40H Choke **£30 the pair**
3KV 50MA **£8 ea.** 4 Volts 250 Amps **£10 ea.**
18KV 30MA **£60.**
22.5KV 110MA **£50 ea.** 5KV 300MA **£15.**
60KV 0.0713A **£150.** 12KV 30MA **£20.**
MULTI PURPOSE MAINS TRANSFORMER 4 windings each
winding 0.10 110 125 at 48A **£15 ea.**
425V 50HZ 2 Wire input. Output 8.5KV 2.55KVA. Could be
run on 240V at 1/2 rating **£15 ea.**
STEP DOWN ISOLATING TRANSFORMER Input 220 250V
5KHZ Output 115V 1.8KVA BRAND NEW. These are very
conservatively rated **£20 ea.**
CAPACITORS
2uf 5KV **£4 ea.** 0.5 mfd 10KV **£4 ea.**
0.5 mfd 5KV **£4 ea.** 8 mfd 2.5KV **£4 ea.**
CARRIAGE on these units will be charged at cost

INFRA RED QUARTZ LAMPS. 230V 6/20 Watts. Size 1.3" x 1/2" x 1/2" **£1.50.**
BRIDGE RECTIFIER. 2 Amp **50p ea.**
PHOTODIODE DETECTOR 4" by leads **25p ea.**
AMPHENOL 1/2 way chassis mount edge connectors 0.8
spacing **15p ea.**
1 F.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre
offset) **60p ea.**
FANS. 115V 1.4 Watts. Size 3 x 3 x 1 1/4" BRAND NEW
£4.50 ea. Secondhand **£2.50 ea.**

Miniature MOTORS 12V with geared wheel (8 teeth 3 1/8" dia)
Size 1 1/4" x 1/2" dia New 30p ea.
MOTOR 12V DC with pulley and integral semiconductor. Speed
Control New **£1 ea.**
LEDEX ROTARY SOLENOIDS. 115V DC No switch assembly
15p ea.
DIAMOND H CONTROLS ROTARY SWITCH. Single pole
10 way Printed Circuit Mount New 10p ea.
DELAY LINE. 50 nanosecs. 3 connections ground in out. Size 2
x 7 1/8 x 1 1/8" New 25p ea.
PULSE TRANSFORMER. Sub min Size 1 1/2" x 5 1/8 x 1 1/8"
Secondary centre tapped New 20p ea.
MOTOR by Inland Motor Corp. DC High Torque. Reversible.
Usable torque at 5V. Max voltage 24V **£2.50 ea. P&P £2**
REMO TV TYPE MULTIPLIER. Two high voltage outputs and
focus **£1 each.**
DON'T TAKE CHANCES. Use the proper EHT CABLE 10p per
metre or £7.50 per 100 metre drum. P&P £1.
MOTOR by Eastern Air Devices Inc. 125V reversible with threaded
shaft (10 teeth 1 1/2" dia) Size 2 1/4" x 2 1/4" dia **75p ea. P&P £1**
PHOTOGRAPHIC LAMPS. Power 230V 500 watt. Screw cap
75p ea. Box of 12 **£5.50. P&P £1.50**
MYSTERY IC PACK. Some 40 pin — good mixture — all new
devices 25 ICs for £1. P&P 50p. You find out what they are and
we will buy the information from you
VACUUM PUMPS — TRAPS, ETC. Send for list
DECOUPLING CAPACITORS. 0.05mfd 10V. 0.01mfd 0.1mfd
50V. 0.047mfd 250V. All values 100 for £1.
E.H.T. CAPACITORS 500pF 8KV 20p each.
10-WAY MULTI COLOUR RIBBON CABLE. New 40p per
metre. 10 metres for £3.
GEC UHF 4-button tuner **£1.50 each.**
CENTAUR 115V FANS 4 1/2" x 1 1/2" **£4.50 ea.**
EX-USED equipment tested 60p each.
POTTER & BRUMFIELD TIMER RELAY. 115V AC. Heavy
duty 7 pole c/s with 2 second delay. Change R & C for different
timing 50p each.
SPEAKERS 2" x 1 1/2" 50 ohms 0.2W. New 40p each.
RAPID DISCHARGE capacitors 8mfd 4kV **£5 each. P&P £2**
BIG INCH Motor. 110V AC 3 rpm 500 cycle. Very small 50p
each.
CONTACTORS. Heavy Duty 24V DC 5 make **£1 each.**
GEC UHF VHF 4-button tuner **£2 each.**
DIGITAL 24-HOUR CLOCK with built in alarm as used in Braun
Digital clocks. Silent ringing. Large illuminated numerals. At
least 50p ea. **ONLY £3.75 each.**
931A PHOTO MULTIPLIER on stainless steel container with
window and built in resistor network. **£2 each. P&P £1**
SILVER CONTROL 500W. Leg Simple tank. Complete with
switch. Length 3 1/2" **25p each.**
RANCO 250V 18A THERMOSTATS with Control knobs
mounted on 3/8" x 1/2" base **£2.50 each.**
SOLID STATE UHF TUNERS. 40 x 1 1/2" **£1 each.**
BRAND NEW blue wax. 40m for £1.
5in SOLID RUBBER RINGS 1 1/2" thick. Keep the kids out

(log) happy 4 for £1. P&P £1.50
TRANSFORMERS
AUTO 240V input 115V 1 Amp output **£1.25 each.** P&P £1.25
240V input. Soc. 6V 1.86A 8kw. Size 2 1/2" x 2 1/2" Good
quality **£1.50 ea. P&P £1**
240V input Soc. 12V 0.92A Size 2 1/2" x 2 1/2" Good quality
£1.50 ea. P&P £1
240V input 12V 100MA Size 60 x 40 x 42mm **50p each.**
240V input. Soc. 12V 0.12V 50MA Size 53 x 45 x 40mm **£1
ea.**
115V input. Soc. 5V 250MA Size 1 1/2" x 1 1/2" x 1 1/2" 2 for
50p.
SEMICONDUCTORS 1N4005 — 5p; 1N4003 — 3p.
At 5p each:
3BC147; BC148B; BC157; BC158; BC237; BF197; OA90;
OA81; BA154; BA243
At 25p each: TIP31; TIP41A; 2N5196; AF139; 2TX341;
BY127 10p; BF181 20p; BD239 40p; BD241 40p; MA343AT
40p; BD228 50p; BD233 8; BD234 Comp Pair 25W — 80p per
pr. at 50p each.
REGULATOR TBA265 8 to 20V in — 5V out 100MA TQ5 Con
50p each BF256C 20p. TV AMPLIFIER TBA 120 20p each.
Integrated Circuits

7453	5p	74H74	12p	75325	£1
7454	5p	74H51	7p	SN15862	4p
7402	12p	74538	10p	MC4028	69p
7476	20p	74502	12p	7417	14p
7495	35p	74154	70p	7441	40p
74122	12p	74C02	18p	74C86	50p
74C00	17p	74C04	18p	74C161	24p
		74C74	18p		

MOTOROLA DUAL in Line 6 pin Opto Coupler 30p each. Gold
plate tester version 50p each.
EPROMS 2708 **£5.50 each.**
TELEPHONES 706 style black or grey **£5.50 each.** 746 style
black or grey **£7.50 each.** Older style black **£2.50 each.** P&P
£1.50 per telephone.
Honeywell humidity controllers 50p each.
THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in
plastic relay case. Standard 7 pin base. Switch delay 50p each.
MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3 way
10p each.
VARIACS. 2 amp Standard 240 volts **£10 each.** P&P £2
ELECTROSTATIC VOLTMETERS. 7.5KV **£8 each.** P&P £1.50
Other ranges available. Please enquire
TRIMMERS. Sub min 0.25 to 1.25pF to 10k 4pF 7 to 45pF All
at 5p each.
CROWN replacement MOTOR for IBM GOLFBALL TYPEWRITER
115V 50HZ 1350 rpm **£4.50 ea.** P&P £2
SMITHS encapsulated transistorised AUDIBLE WARNING
DEVICES 4V 12V Can be driven from 1T1 **65p each.**

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1 — where P&P not stated please use own discretion — excess refunded. CARRIAGE ALL UNITS
5p. P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMHEAD LTD

NORWOOD ROAD, READING

TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with Spoked Wheel)

DIGITAL TEST METER

This unique and modestly priced piece of test gear uses the very latest 3½ digit LCD DVM module and acts as a combined 25-range digital multimeter and a 5-range digital frequency meter. It's another 'first' from ETI.

Two of the most useful pieces of modern electronic test gear are the Digital Multimeter (DMM) and the Digital Frequency Meter (DFM). These instruments are highly accurate, rugged and can be used in any attitude (vertical, horizontal, upside down, etc). Trouble is, they tend to be a bit expensive; a decent pair of such instruments costs about £200.

We have overcome the price by producing a unique 30-range digital instrument that acts as a combined 25-range DMM and 5-range DFM. We've decided to call this new instrument a Digital Test Meter, or DTM. Our DTM is designed around the very latest 3½ digit liquid crystal digital voltmeter module (thereby simplifying construction), is powered from two 6 V battery supplies and typically gives several months of operation from a single battery set.

The AV (alternating voltage) ranges of the DTM are frequency compensated; they are typical responses that are flat within 1% to 40 Hz or to within 1 dB to 120 kHz.

The resistance indicating section of the DTM uses a ratiometric measurement technique and a test voltage of about 300 mV maximum, thereby enabling in-circuit resistance measurements (such as a resistor in parallel with a semiconductor junction) to be made without forward biasing in-circuit junctions. The DTM is provided with an independent facility (via a specific test terminal) for testing semiconductor junctions.

The frequency meter section of the unit can be used to measure frequencies in the range 10 Hz to 1.999 MHz. The input impedance of the section is roughly 200 kΩ and signal levels in the approximate range 10 mV to 100 V can be accepted.


The DTM is provided with a built-in precision 1V2 DC reference, which can be used for basic calibration of the DC and DV ranges. Resistance calibration is automatically established by built-in standard resistors. The instrument must be compared with external standards to calibrate the basic AC, AV and frequency ranges.

Accuracy

The basic 3½ digit DVM module used in the DTM is intended to read 100 mV full scale, with 100% over-range capability (giving a maximum reading of 199.9mV). The basic module is capable of reading with an accuracy that is within 0.1% (one digit, or 100 µV) of full scale, once it has been initially calibrated against a suitable reference standard.

In practice, all other ranges of the DTM are obtained by feeding inputs to the DVM module via resistive potential dividers, current ranging resistors and resistance standards.

In our prototype DTM we've used 1% resistors in all pertinent positions, thus giving the completed instrument an overall accuracy of 1% which we consider to be adequate for most practical purposes. If you want higher accuracy,

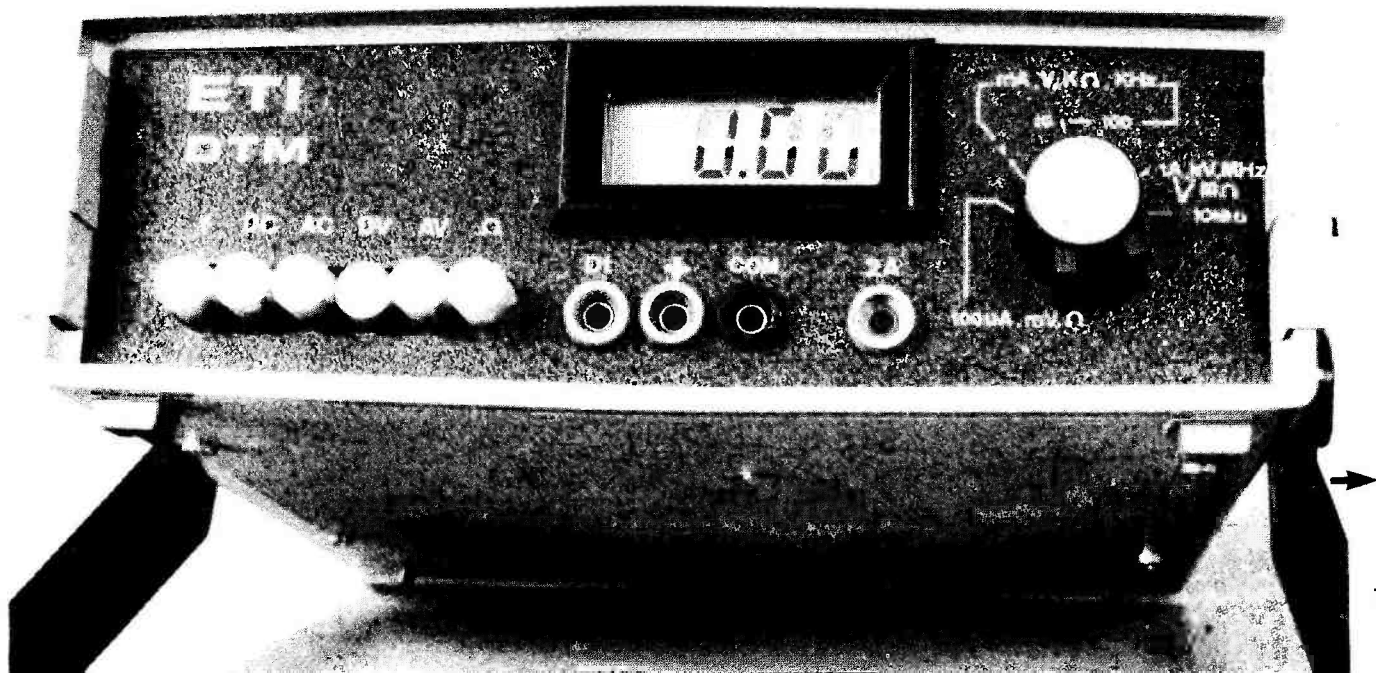

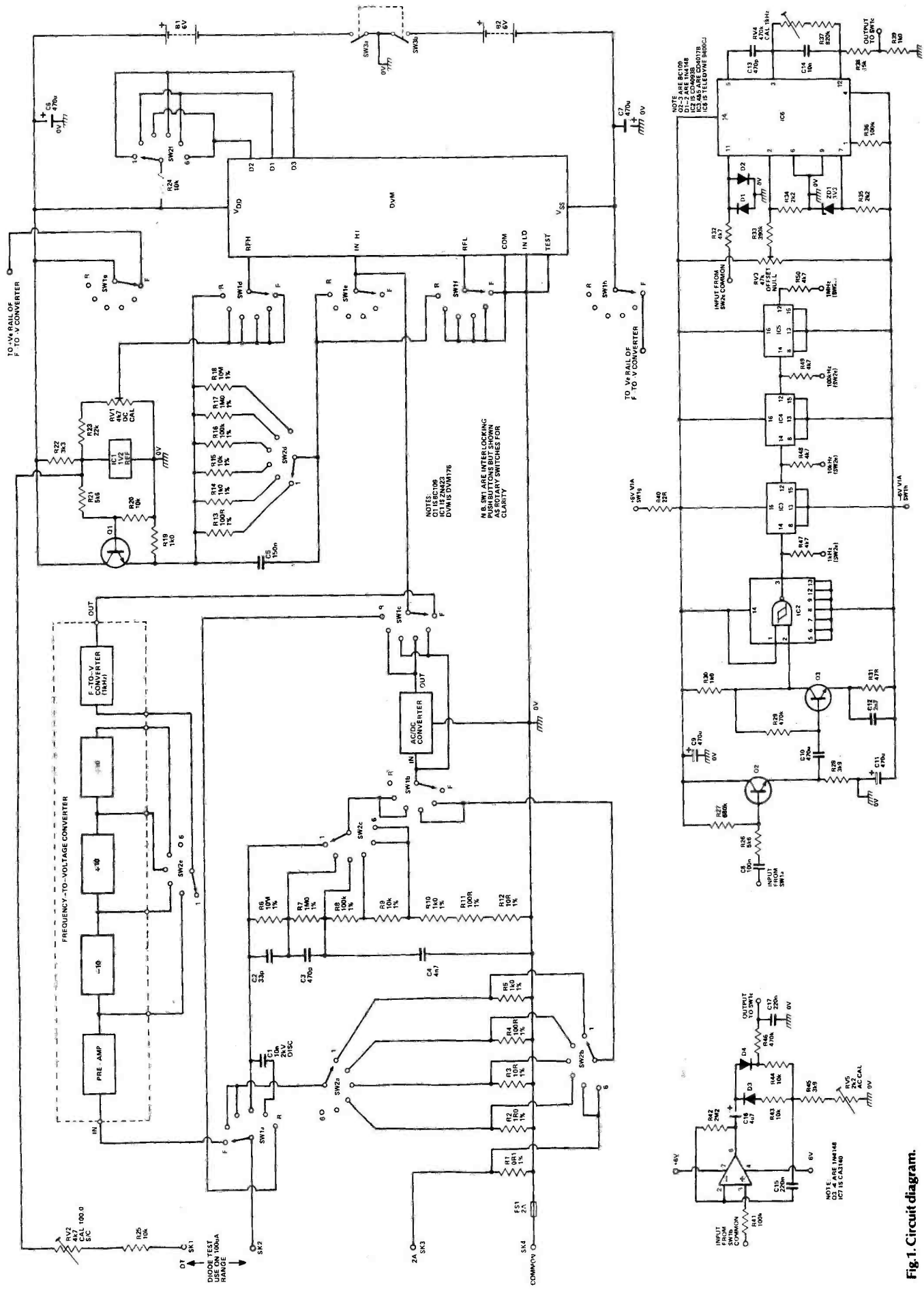


Fig. 1. Circuit diagram.

HOW IT WORKS

The heart of the DTM is a DVM 176M Rev C 3½ digit liquid crystal DVM module, available from Ambit International. This module has a built-in voltage reference and is intended to be powered from a single 9 V battery. The complete module (including the readout) typically draws only 1 mA of current and is intended to read 100 mV DC full scale with 100% over-range capability (giving a maximum reading of 199.9 mV).

In our particular application we need, for various reasons, to power the module from a split 12 V (6-0-6) battery supply; which makes it necessary to ignore the module's built-in voltage reference, and supply it with a reference voltage from an external source. IC1 and the RV1-R23 divider are used for this purpose.

In the completed DTM, voltage ranging is obtained by feeding inputs to the DVM module via the R6-R12 potential divider network. AC voltage ranging is obtained by feeding inputs to the DVM module via the same potential divider (which is frequency compensated via C2-C3 and C4) and via a precision AC/DC converter (designed around IC7).

Current ranging is obtained by feeding the test current through the appropriate one of the R1 to R5 ranging resistors and monitoring the voltages that they generate. In the DC mode, the generated voltages are fed directly to the input of the DVM module. In the AC mode, they are fed to the module via the AC/DC converter.

Frequency indication is obtained by feeding input signals to the DVM module via a precision frequency-to-voltage converter. The f-to-v converter has a basic range of 10 Hz to 1,999 kHz and frequency ranging is achieved by feeding input signals to the converter via switch-selected decade divider networks.

Resistance measurements are made by disconnecting the external reference from the DVM module and connecting the test resistor in series with the appropriate one of the R13 to R18 ranging resistors and powering the combination with a few hundred millivolts DC (via the IC1-Q1 network). The voltage of the ranging resistor is monitored at the reference-input terminals of the DVM module and the voltage of the unknown resistor is monitored at the module's signal input terminals. The DVM module compares the ratios of the two voltages (and thus the ratios of the resistors) and gives a readout that is interpreted directly in terms of resistance.

This 'ratimetric' system of resistance measurement has two distinct advantages. First, maximum test voltages of only a few

hundred millivolts are applied to the unknown resistor, thereby causing in-circuit resistance measurements to be made without disturbing semiconductor junctions to become forward biased. Second, the accuracy of measurement is independent of the energising voltage and is determined solely by the accuracy of the ranging resistors, thus eliminating calibration problems. Our circuit measures resistances of 0R1 to 19.99M in six ranges.

In the DTM, multi-pole switch SW1 is used to select the mode of operation and SW2 is used for range selection. SW2 sets the decimal point of the display to a position appropriate for the selected range.

The DTM has a facility for testing semiconductor junctions. To use this facility, the unit is switched to the 100uA range in the DC mode and the test device is connected between the DT+ and + terminals of the instrument. The DT+ terminal is energised from the built-in 1V2 source via RV2 and R25 and the resulting device current is read out by the DVM module. Open circuit devices give a reading of zero. Short circuit devices give a reading of 100.0. Good silicon junctions give a forward reading of roughly 60.0.

The AC/DC converter section of the instrument is designed around IC7, which is connected as a precision rectifier. The gain of the circuit can be pre-set, for calibration purposes, via RV5. The output of the converter is integrated by the R46, C17 network and by an additional network that is incorporated in the DVM module.


Frequency to voltage conversion input test signals are fed to high-impedance (roughly 200k) input buffer Q2 via safety resistor R26 and are then amplified by Q3 and converted to square waves at the input frequency via IC2. The resulting square waves are then divided down by decade dividers IC3 to IC5.

The heart of the converter is IC6 which, quite simply, is a dedicated precision frequency-to-voltage converter chip, in which the input signal is fed to pin 11 via R32 and a proportional analogue voltage appears at the junction of R38-R39. In our application, the IC is configured to cover the basic range of 10 Hz to 1,999 kHz. Frequency calibration can be set via RV4 and offset nulling (zero output for zero input) can be achieved via RV3.

Frequency ranging of the complete converter circuit is obtained by feeding the input of IC6 from an appropriate point in the IC2-IC5 network via SW2e. Thus, on the 1kHz range IC6 is fed directly from the output of IC2; on the 1MHz range, IC6 is fed from the output of IC5.

self-tapping screws and 1/8 inch spacers into studs moulded into the base of the case.

Make up PCB A as shown in the overlay, taking special care over the construction. Note that 1% resistors are used in the range-determining positions. Fit Veropins in all appropriate positions on the board, to facilitate wiring interconnections. Make up the power supply (+6 V, 0 V and -6 V) connections to the board via SW3.

Make up the following interconnections to the DVM module, noting that the module is a MOS device and can be damaged by static charges; VSS to -6 V and VDD to +6 V on PCB A. Connect COM, IN LO and TEST together and connect to the 0 V power supply line. Connect the 0 V line to the instrument's common input terminal via FS1. Connect RFL to the common terminal of SW1f. Connect RFH to the common terminal of SW1d. Connect IN HI to the common terminals of SW1c and SW1e. 

you'll have to locate a source of supply of ultra-precision resistors.

Construction of the unit presents a bit of a challenge, due to the complexity of the interwiring. Construction needs to be tackled in a methodical manner, with the unit being given a functional check at the end of each building stage. The following building sequence is recommended.

DV Ranges & AV Ranges

Gather all hardware together (switches, battery pack, sockets, fuse holder and the DVM module and bezel) and secure them in their final positions in the instrument case. On our prototype, we've used a bank of push-button switches for SW1 (mode selection) and a rotary switch for SW2 (range selection). On/off switch SW3 is mounted on the rear of the instrument. SW1 is mounted on a small PCB and fixed, via

SW2 RANGES	SW1 MODE SETTINGS					
	f	DC	AC	DV	AV	R
1	—	100uA	100uA	100mV	100mV	100R
2	1kHz	1mA	1mA	1V	1V	1kΩ
3	10kHz	10mA	10mA	10V	10V	10k
4	100kHz	100mA	100mA	100V	100V	100k
5	1MHz	1A	1A	1kV	1kV	1MΩ
6	—	1A	1A	1kV	1kV	10M

Table 1. SW2 range details for the six meter functions.

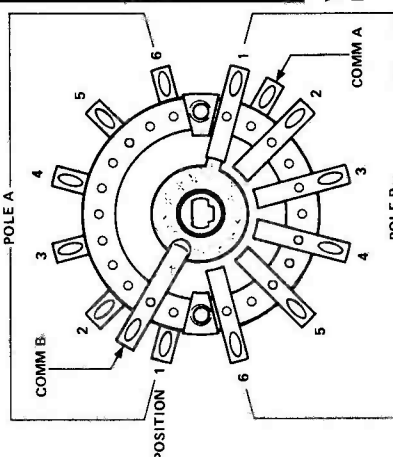


Fig.2. The wiring of SW2 (above) can become a veritable jungle if you're not careful. Lock yourself away from all distractions for half an hour and work round each pole in turn.

Refer to the main circuit diagram and make the following connections. Wire up SW1d and make the connection to RV1 slider on PCB A. Wire up SW1f and make the connection to COM terminal on the DVM module. Trace the DV (direct voltage) path through the circuit and make the appropriate connections as follows. From SK2 to SW1a common; from SW1a DV to R6 and from the R6-R12 chain to the 1 to 6 pins of SK2c; from SW2c common to SW1b DV/AV; from SW1b common to SW1c DV and AC; from SW1c common to SW1e common and to the IN HI terminal of the DVM module.

With all the above connections made, double check the wiring and then switch the unit on. Short the instrument's input terminals and check that the DTM reads 000 on all ranges in the DV mode. Switch to the 1 V range, connect the unit's input terminal (SK2) to SK1 and trim RV1 to obtain a reading of 1V2 (1200). The unit is now approximately calibrated (within 5%) on all DV ranges. Remove the connection from SK1 and check that the unit is functional on all DV ranges.

If you have access to a precision DV source or to an accurate DMM, you can precisely calibrate the DTM by switching it to the 100 mV DV range, connecting a known input test voltage (100-199 mV) and adjusting RV1 for a correct reading.

Decimal Pointing

Refer to the main circuit diagram and make the connections from +6 V to SW2f common via R24 and from the SW2f range pins to the D1, D2 and D3 terminals on the DVM module. Switch the DTM on, on the DV ranges, and check that the decimal point appears in sensible positions on each range (eg 100 mV reads 100.0 on the 100 mV range or 100 on the 1 V range).

Refer to the main circuit diagram and trace the AV (alternating voltage) path, making additional connections as appropriate, as follows. From SK2 to the top of R6 via SW1a and C1; from the output of the R6-R12 chain to SW1b via SW2c; from SW1b common to R41 of the AC/DC converter on PCB A and to the DV and DC pins of SW1c; from R46 of the converter on PCB A and to the DV and DC pins of SW1c common to IN HI on the DVM module.

When the above connections are complete, set the unit to the 100 mV AV range, connect a 1 kHz sine wave of known amplitude (100-199 mV) to the input of the DTM and adjust RV5 for a correct reading. Switch the unit to the 1 V range, increase the input signal to a sensible value and check the frequency response of the instrument. The response should be virtually flat from 20 Hz to 40 Hz; if necessary, the value of C2 can be padded up slightly to obtain the required response. Check that the unit is functional on all other AV ranges.

DC Ranges & AC Ranges

Refer to the main circuit diagram, trace the DC (direct current) circuit path (via R1-R5), add all appropriate switching connections and then give the unit a functional check on all DC ranges.

Refer to the main circuit diagram, trace the AC (alternating current) circuit path, add any appropriate switching connections and give the unit a functional check on all AC ranges.

Resistance Ranges

Refer to the main diagram again, trace the resistance measuring circuit (via R13-R18 and SW2d, SW1d-SW1e-SW1f and from the IN HI pin of the DVM module to SK2 via SW1c

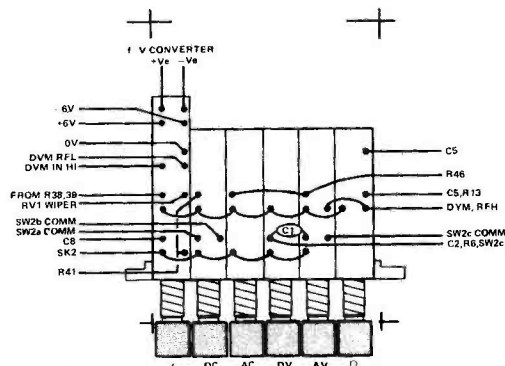


Fig.3. The mode switch assembly fits on its own PCB (above).


and SW1a) and make all appropriate connections. Give the unit a functional check on all ranges by connecting appropriate test resistors to the DTM test terminals.

Note that, due to the low-voltage ratiometric resistance measuring technique used in this instrument, the readout tends to jitter somewhat when used to test resistors with values in excess of 200k or so. This tendency can be minimised by keeping test leads as short as possible, to avoid hum pickup.

Make the connection from R25 (on PCB A) to Diode Test Socket SK1. Short SK1 to SK2 and adjust RV2 for a reading of 100.0 on the 100 uA DC range. Remove the short and check that a reading of 00.0 is obtained. Connect a silicon diode between the two sockets and check that a reading of about 60.0 is obtained in the forward direction and 00.0 in the reverse.

Frequency Ranges

Construct the frequency-to-voltage converter circuit on PCB B and make its supply connections via SW1g (+6 V) and SW1h (-6 V) and the supply common line. Make the input connection to the PCB from SW1a and the output connection to SW1c. Wire up SW2e as shown, noting that a 4k7 resistor is connected directly to each of the 1kHz, 10

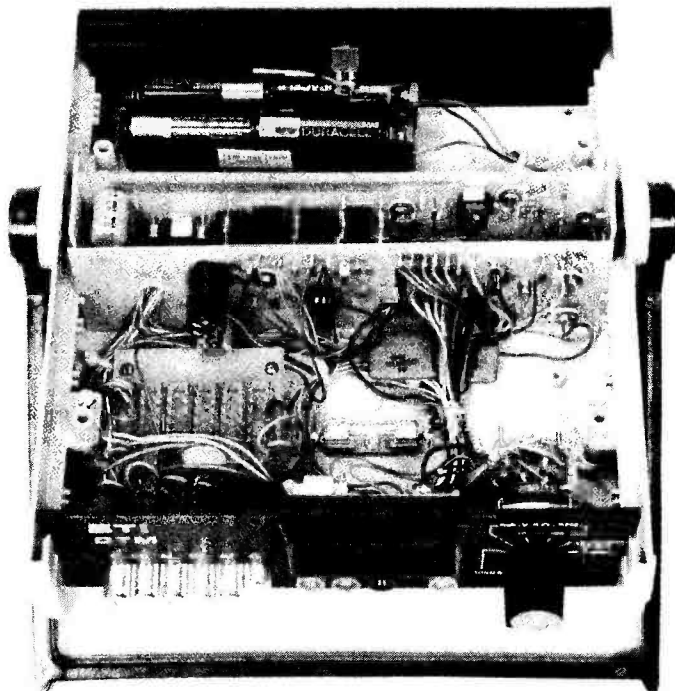

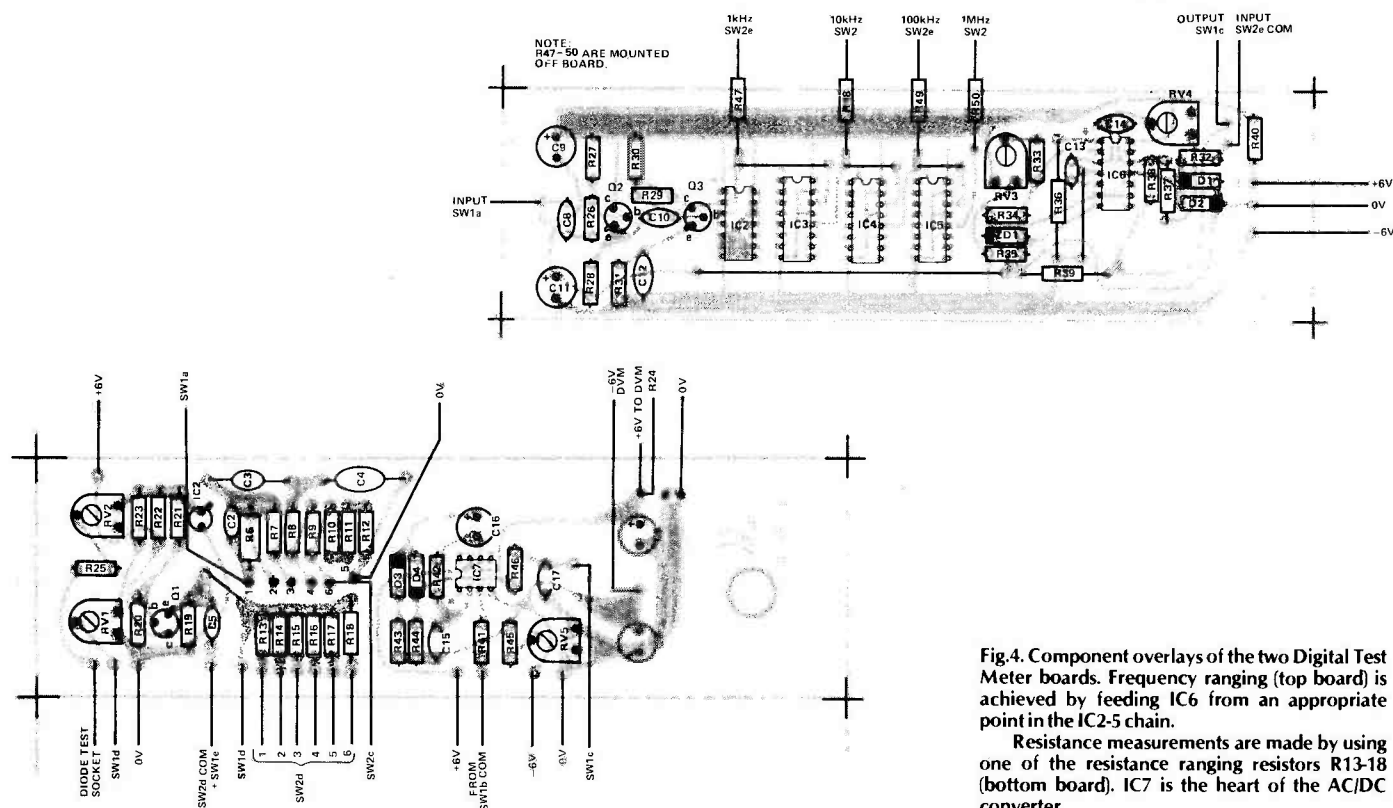


Fig.4. Component overlays of the two Digital Test Meter boards. Frequency ranging (top board) is achieved by feeding IC6 from an appropriate point in the IC2-5 chain.

Resistance measurements are made by using one of the resistance ranging resistors R13-18 (bottom board). IC7 is the heart of the AC/DC converter.

PARTS LIST

Resistors 1/4W 5% unless specified

R1	0R1 1/2W 1%
R2	1R0 1/2W 1%
R3,12	10R 1/2W 1%
R4,11,13	100R 1/2W 1%
R5,10,14	1k 1/2W 1%
R6,18	10M 1/2W 1%
R7,17	1M 1/2W 1%
R8,16	100k 1/2W 1%
R9,15	10k 1/2W 1%
R19,30,39	1k
R20,24,25,43,44	10k
R21,26	5k
R22	3k3
R23	22k
R27	680k
R28,45	3k9
R29,46	470k
R31	47R
R32,47,48,49,50	4k7
R33	390k
R34,35	2k2
R36,41	100k
R37	820k
R38	15k
R40	22R
R42	2M2

Potentiometers

Rv1,2	4k7 miniature horizontal preset
Rv3	47k miniature horizontal preset
Rv4	470k miniature horizontal preset
Rv5	2k2 miniature horizontal preset

Capacitors

C1	10n 2kV ceramic disc.
C2	33p silver mica
C3	470p silver mica
C4	4n7 silver mica
C5	150n polycarbonate
C6,7,9,11	470u 16v electrolytic, PCB type.
C8	100n polycarbonate
C10	470n polycarbonate
C12	2n7 ceramic
C13	470p ceramic
C14	10n polycarbonate
C15,17	220n polycarbonate
C16	4u7 electrolytic, PCB type

Semiconductors

DVM	176M Rev. C.
IC1	Zn423
IC2	4093B
IC3,4,5	4017B
IC6	9400CJ
IC7	CA3140
Q1,2,3	BC109
D1-4	IN4148

Miscellaneous

SW1a, 8 pole change over interlocking push button	
SW1b,c,d,e, 6 pole change over interlocking push button	
SW2a-f, 2 pole 6 way wafers (3 off) rotary switch	
SW3, DPDT miniature toggle	
SK1-4, 4 mm banana sockets	
2 off, 4 section battery holders for HP7	
1 off, 1 1/4" fuse & holder chassis fixing or similar	
1 off, winged knob	
Case (see buylines)	

kHz, 100 kHz and 1 MHz output pins of PCB B, with the connections to SW2e made via these resistors.

When construction is complete, switch to the 1 kHz range in the 'f' mode, short the unit's input terminals and adjust RV3 for zero reading on the meter. Remove the input short, connect a 1 kHz input signal and adjust RV4 for a reading of 1.000 on the meter. Finally, check that the DTM is functional on all other frequency ranges.

BUYLINES

Watford Electronics have agreed to supply a full kit of parts for the ETI DTM.

Our Case for this project was obtained from OK Machine and Tool. (Order as CH23 Tan) Phone 0703-610944.

Ambit International Supply the DVM176 Rev. C.

Our condolences to purchasers of ZEON Hong Kong watches — ZEON have gone into voluntary liquidation

Yet another reason for paying a little more for QUALITY, RELIABILITY AND CONTINUING SERVICE

Our best selling alarm chronograph is now available from stock again

**CASIO
81QS-35B
ALARM
CHRONO**

RRP £34.95

**ONLY
£29.95**



Solid stainless steel, mineral glass. Water resistant. 5-YEAR BATTERY. Hours, minutes, seconds, day and date, month and year. 12 or 24-hour display. 24-hour alarm, hourly chimes. Stopwatch from 1/100 second to 7 hours; net, nap and 1st and 2nd place times.


Something to sing about with twelve programmed melodies!

**CASIO
ML90**

**MELODY
MAKER**

RRP £21.95

**ONLY
£19.95**

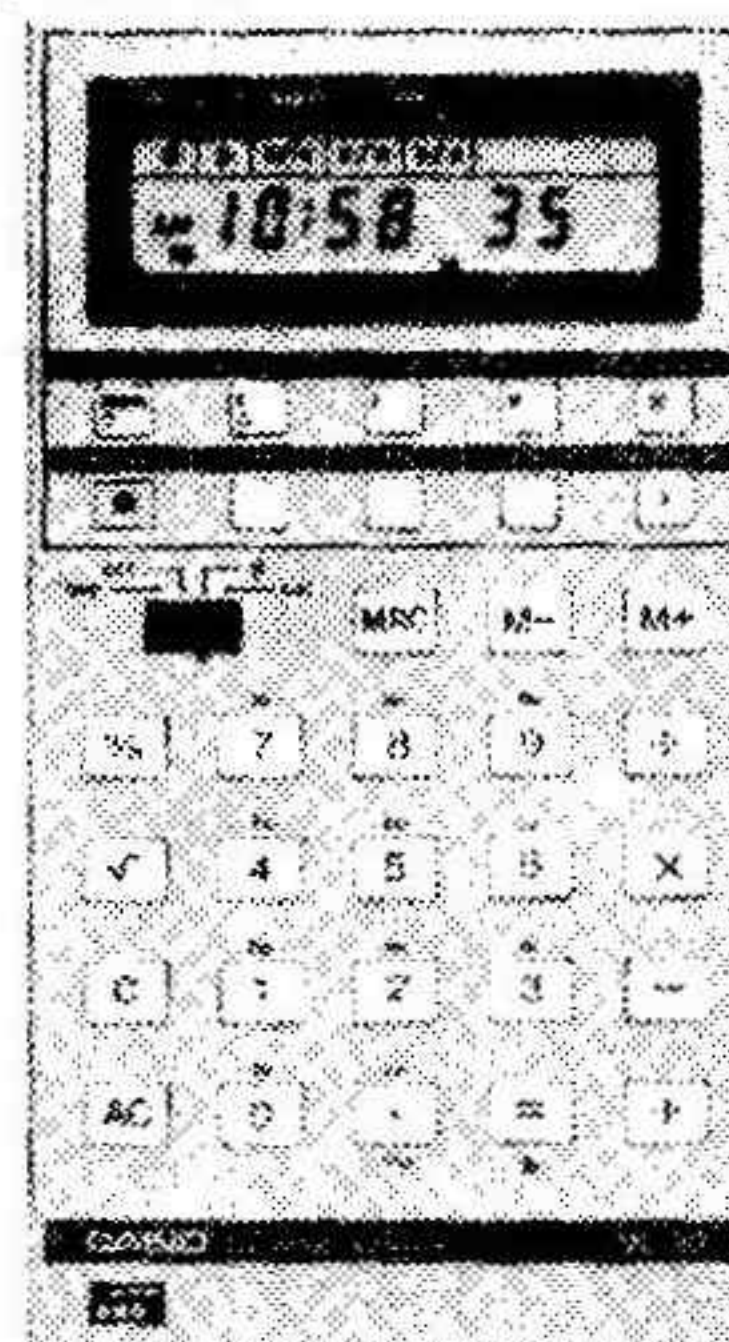

Clock, hourly chimes, calendar to 1999. Alarm 1: 7 different melodies, changing daily, a fixed melody or buzzer. Alarm 2: a fixed melody or buzzer. Date memory 1: "Happy Birthday". Date memory 2: "Wedding March" or "Drinking song". On December 24/25 plays "Jingle Bells". Calculator with 11-note keyboard, full access memory, square roots, %, 7/32 x 2 1/2 x 4 1/2 inches. Wallet. 1 year batteries.

You asked for a metal version of the best selling C-80. Here it is!

**CASIO
C-801**

Watch
Calculator
Stopwatch
Dual time
RRP £34.95

**ONLY
£29.95**



Finger touch keyboard. Hours, minutes, seconds, am/pm and day. Day, date, month calendar pre-programmed to 2009. Professional 24-hour stopwatch, measuring net, lap and first and second place times to 1/100 second. Dual time (24 hour). 8 digit calculator. Backlight. Water resistant chrome plated case with stainless steel bracelet.

C-80 Black resin cased version £24.95

NEW CASIO CHRONOGRAPHS

F-300



**ONLY
£12.95**

110QS-37B



**ONLY
£17.95**

Hours, minutes, seconds, am/pm, day and date. Automatic four year calendar. 1/100 second chronograph to 12 hours, measuring net, lap and first and second place times. Backlight, 2-year lithium battery. Water resistant case. Mineral glass.

F-300 Rugged, lightweight resin case
110QS-37B Chrome plated, S/S bracelet

We PROMISE TO BEAT any sensible lower advertised prices ON THE SPOT if the advertiser has stocks AND you get Casio's guarantee from us!

OTHER STAR BUYS

Watches
F-8C 8 digits. Resin. **Now only** £8.95
F-200 Sports chrono. Resin £10.95
95QS-36B 1/100 sec. 12/24 hr. Solid s/s £19.95
Alarm chronographs
F-80 1/10 sec. Resin. S/s trim £19.95
83QS-41B 1/10 sec. S/s jacket £22.95
83QGS-41B Gold plated version £29.95
81QS-40B As 81QS-35B but chrome £22.95
81QGS-35B Gold plated version £34.95
Casio ladies' watches. 11 models, many with stopwatch and dual time. From £12.95

Calculators
MC-34
HR-10
Scientifics
FX-81 £12.95. **FX-100** £15.95. **FX-330** £15.95
FX-8100
FX-7100
FX-501P
FX-502P
FA-1
Master pack software kit (RRP £17.95)
Free of charge with FX-501P or FX-502P

SUMMERTIME SPECIAL OFFERS

FREE on request with order

With any purchase made from this section before September 30th 1980 **GENTLEMAN'S DIGITAL WATCH** with comprehensive display and long life battery from world famous manufacturer. **Value around £12.** An ideal working watch for you or a present for someone else.

Offers subject to availability.

WATCHES with chronograph (stopwatch)
95QS-42B 12/24 hr Dual time. S/S jacket £17.95
56QS-38B Digi/ana. Timer. chrome £24.95
C-80 Calculator. Dual time £24.95
Alarm chronographs with hourly chimes
81QS-40B As 81QS-35B but chrome £24.95
83QS-41B 1/10 sec. S/S jacket £24.95
79QS-39B 1/10 sec. full calendar. Chrome £29.95

CALCULATORS
AQ-2200 £19.95. **MQ-12** £19.95

Musical: **ML-82** £19.95. **ML-71**, **ML-81** £22.95.
Ultra slim scientific: **FX-3200** £21.95.

FREE ON REQUEST WITH ORDER

With any purchase made from this section before September 30th, 1980.
From world famous manufacturer:
GENT'S DIGITAL WATCH, around £17
or **LADY'S DIGITAL WATCH**, around £15
or **CALCULATOR/CLOCK**, around £17

Offers subject to availability

WATCHES
56QS-50B Digital/analogue. Chronograph. Timer. Solid stainless steel £34.95
79CS-51B Universal calendar alarm chrono with chimes, tone control. Solid s/s £39.95
59CS-33B Ultra slim dress watch with alarm £44.95
Scientific calculator: **FX-8000**. Stopwatch. 2 alarm timers £31.95

SEIKO

100m WATER RESISTANT
SUITABLE FOR SWIMMING ETC



DFT 030/038

**ALARM
CHRONOGRAPH**

100m WATER
RESISTANT

**ONLY
£49.95**

Hours, minutes, seconds with alpha day and date on upper display; and day, date, month calendar. Alarm and hourly chimes. COUNT-DOWN ALARM. Stopwatch from 1/100 second to 12 hours; net, lap and 1st and 2nd place times on double display.

DER 028 SOLAR ALARM CHRONOGRAPH

With weekly alarm, interval timer, 7-year battery.
100m water resistant

£69.95

RETURN OF POST SERVICE

Postal and telephone orders received before 4.00 p.m. will normally be despatched the same day by FIRST CLASS POST.

Send your order by **FREEPOST** (2nd class post — no stamp required). Please phone urgent orders or use first class mail.

ILLUSTRATED CATALOGUE

Casio and Seiko products. Send 25p to: **TEMPUS** (Information and Service Centre), 19-21 Fitzroy Street, Cambridge CB1 1EH.

PRICE includes VAT, P&P. Send your Company Order, Cheque or P.O. or phone your ACCESS or B'CARD number to:

TEMPUS

Tempus (Dept. ETI)
FREEPOST, 164-167 East Road
Cambridge CB1 1BR. Tel. 0223 312866

ETI BOOK SERVICE

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to **Electronics** Squires £3.75
 Beginners Guide to **Transistors** Reddihough £3.75
 Beginners Guide to **Integrated Circuits** Sinclair £3.75
Understanding Electronic Circuits Sinclair £4.60
Understanding Electronic Components Sinclair £4.60
 Beginners Guide to **Radio** King £3.75
 Beginners Guide to **Audio** Sinclair £3.75

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00
Video Cookbook £7.00
TTL Cookbook £7.55
The Basic Cook £4.00 inc. p/p
IC Converter Cookbook £9.50

APPLICATIONS

Fire and Theft Security Systems B. Weis £2.15
How to Build Electronic Kits Capel £2.65
110 Electronic Alarm Projects R. M. Marston £4.45
110 Semiconductor Projects for the Home Constructor R. M. Marston £4.45
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £4.45
110 Thyristor Projects Using SCRs R. M. Marston £4.45
110 Wave Form Generator Projects R. M. Marston £4.45

COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72-page book £12.00
Beginners Guide to Computers and Microprocessors with Projects C. Adams £6.05
Basic Computer Games Ahl £6.05
Basic for Home Computers A self-teaching guide, B. Albrecht £6.15
Illustrating Basic D. Alcock £3.75
Intro to Microprocessors Aspinall £6.55
Z-80 Microcomputer Handbook W. Barden £7.75
How to Program Microcomputers W. Barden £7.25
Introduction to Microcomputers and Microprocessors A. Barna £8.60
Microprocessors in Instruments and Control R. J. Bibbero £13.00
Basic Basic J. S. Coan £7.80
Advanced Basic J. S. Coan £7.30
Getting Acquainted with Microprocessors L. Frenzel £7.25
Beginners Guide to Microprocessors C. M. Gilmore £4.90
Beginners Guide to Home Computers Grossworth £4.50
Beginning Basic R. E. Gosling £4.75
Microprocessor Programming for Computer Hobbyists N. Graham £7.15
Miniprocessors from Calculators to Computers Heiserman £5.00
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.40
Basic Programming J. G. Kemeny £7.25
Microprocessor Systems Design E. Klingman £17.00
Intro to Microprocessors Leventhal £17.00
Microprocessors — Technology, Architecture & Applications D. R. McGlynn £10.55
Interactive Computing with Basic Monro £4.25
Basic with Style P. Nagin £4.25
Software Design for Microcomputers Ogdin £7.20
Microcomputer Design Ogdin £7.25
Microcomputer Base Design Peatman £5.70
Hands on Basic with a PET Peckham £9.55
Basic — A hands on method Peckham £6.95
6800 Software Gourmet Guide and Cookbook Scelbi £8.90
8080 Software Gourmet Guide and Cookbook £8.90
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.35
8080/8085 Software Design Titus £7.60
57 Practical Programs & Games in Basic Tracton £6.65
Microcomputer Primer M. Waite £6.50
Your Own Computer Waite £1.60
Microprocessor/Microprogramming Handbook Ward £6.20

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £7.15
Practical Digital Design Using ICs J. Greenfield £16.00
Designing With TTL Integrated Circuits Texas Instruments £9.35
How To Use IC Circuit Logic Elements J. Streater £3.80
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £4.45
Understanding CMOS Integrated Circuits R. Melen £4.15
Digital Electronic Circuits and Systems R. M. Morris £4.50
MOS Digital ICs G. Flynn £5.25

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.50
Working with the Oscilloscope A. Saunders £4.25
Servicing with the Oscilloscope A. King £6.65
Radio Television and Audio Test Instruments King £7.00

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.45
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £4.45
Designing With Operational Amplifiers Burr Brown £19.00
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.55

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.65
Digital Signal Processing Theory & Applications L. R. Rabiner £24.40
Electronic Communication Systems G. Kennedy £8.75
Frequency Synthesis. Theory & Design Mannasewitsch £25.00
Principles of Communication Systems H. Taub £8.40

THEORY

Introduction to Digital Filtering Bogner £10.60
Transistor Circuit Design Texas Instruments £9.75
Foundations of Wireless Electronics M. G. Scroggie £5.60

REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner £34.50
Electronic Components M. A. Colwell £2.90
Electronic Diagrams M. A. Colwell £2.90
International Transistor Selector T. D. Towers New update £10.20
International FET Selector T. D. Towers £4.35
International Op-Amp Linear IC Selector Towers £7.65
Radio Valve and Semiconductor Data A. M. Bell £4.00
Radio, TV and Audio Technical Reference Amos £30.40

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair £3.55
Integrated Electronics J. Milman £8.20
Practical Solid State DC Supplies T. D. Towers £6.40
Practical Triac/SCR Projects for the Experimenter R. Fox £2.35
Printed Circuit Assembly Hughes & Colwell £2.90

Fallen behind recent advances?
 Just starting out?
 Need a decent reference book?
ETI Book Service provides an easy way of getting your hands on the right title.

nascom-2**MICRO-COMPUTER**FREE 16k B
RAM Board
FREE POWER
SUPPLY

Ex-stock

only £335

+ VAT
Full after sales
service

Z80A 8 bit. This will run at 4 Mhz but is selected between 2/4/Mhz.

On-board, addressable memory. 2K
2K Monitor — Nas-sys 1. 1K Video RAM
(MK 4118). 1K work space/User RAM
(MK 4118) (8K Microsoft Basic)
(MK 3600 ROM) (8K Static RAM/2708E)**Microprocessors** Z80A. 8 bit CPU. This will run at 4MHz but is selectable between 2/4 MHz. This CPU has now been generally accepted as the most powerful, 8 bit processor on the market.**INTERFACE****Keyboard** New expanded 57 key Licon solid state keyboard especially built for Nascom. Uses standard Nascom, monitor controlled, decoding. T.V. The tv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T.V.**I.O.** On-board UART (Int. 6402) which provides serial handling for the on-board cassette interface or the RS232/20mA teletype interface.

The cassette interface is Kansas City standard at either 300 or 1200 baud. There is a link option on the NASCOM-2. For 2400 Baud.

The RS232 and 20mA loop connector will interface directly into any standard teletype.

The input and output sides of the UART are independently switchable between any of the options —

i.e. it is possible to have input on the cassette and output on the printer.

P/O There is also a totally uncommitted Parallel I/O (MK 3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls.**Documentation** Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic.**Basic** The Nascom 2 contains a full 8K Microsoft Basic in one Rom chip with additional features like DEEK, DOKE, SET RESET for simple programming.**TANGERINE**
COMPUTER SYSTEMS"MICRON" the latest line
in superb products£375.00
inc. VAT
BRITISH
DESIGN

- 6502 based microcomputer
- VDU alpha numeric display
- Powerful monitor TANBUG
- 8K RAM
- 32 parallel I/O lines
- 2 serial I/O lines
- RS 232 C/20mA loop, with 16 programmable Baud rates
- Four 16 Bit counter timers
- CUTS cassette recorder interface
- Data bus buffering
- Memory mapping control
- 71 Key ASCII Keyboard, including numeric keypad and with auto repeat
- Including metal cabinets for both keyboard and modules
- Including power supply
- 10K Microsoft BASIC
- All the usual BASIC commands
- Integer and real numbers
- Integer and real arrays
- Intrinsic functions ABS, INT, RND, SGN, SIN, SQ, TAB, USR, ATN, COS, EXP, LOG, TAN.
- User defined functions
- READ and DATA statements
- Dump and load programs for cassette recorders
- Program editing command
- String function for text I/O
- BASIC can call user machine-code sub routine
- User machine-code interrupt handler interfaces with BASIC

MICROPROCESSOR BOARD (NASCOM 2)
4MHz Z80 CPU; TV or Video + 1200 baud
Kansas City + Serial RS 232 printer
Interfaces; Keyboard; 128 character ASCII
plus 128 Graphics in 2 x 2K ROM; free
16-way parallel port; 8K BASIC; NAS SYS
operating monitor. £280 built and tested.**Firmware & MOS ICs**Zeap Assembler (4, 1Kx8 EPROMS) £50
Nas Pen text editor (2, 1Kx8 EPROMS) £30**Expansion boards (in kit form)**

16K RAM £127.50 ● 32K RAM £175.00

48K RAM £220.00

High Resolution Programmable Graphics £90


Colour Board Kit £140

High Resolution Colour add on £37.50

NASCOM PRODUCT LIST + VAT

I/O board kit less I/O chips	45.00
UART + BAUD rate generator + crystal for I/O board	16.00
CTC — MK3882 multiple interrupt driven clock generator for I/O board	8.25
P/O — MK3881 + interconnect for I/O board	8.50
P/O interconnect only (for I/O board)	3.80
Econographics kit for additional 128 characters (N1 only)	30.00
2708/2716 Programmer suitable for N1 and N2 under NAS-SYS	£20.95 plus VAT
Nascom 19" rack mounting card frame for N1 and N2	32.50
Nas-DA disassembler 3 EPROM for Nas-sys	37.50
MK36271 8K BASIC in 8K x 8 ROM	40.00
Naspen VS in 2 EPROM	30.00
Nas-sys monitor in 2 EPROM	25.00
Nasbug T2 1 x EPROM	12.50
Nasbug T4 2 x EPROM	25.00
Tiny Basic 2 x EPROM	25.00
Super Tiny Basic 3 x EPROM	37.50
Super Tiny Basic upgrade 1 x EPROM	12.50
Tape Software	
ZEAP 1.2 tape and documentation for N1	30.00
ZEAP 2 tape and documentation for Nas-sys	30.00
8K BASIC tape and documentation for N1	15.00
MEMORIES Discounts 10% for 4, 15% for 8, 20% for 16	
MK3880 (Z80) for N1	7.50
MK3880-N4 (Z80A) for N2	7.95
MK4116 16K x 1 dynamic RAM	7.50
MK4027 4K x 1 dynamic RAM	2.25
2102 1K x 1 static RAM	1.00
4118 1 K x 8 static RAM	12.75
Unprogrammed 2708	7.50
Unprogrammed 2716	19.95
IM6402 UART	4.50
2114 1K x 4 Static RAM	3.95
8080A	5.25

Ideal for NASCOM — PET — TRS80 — TRITON

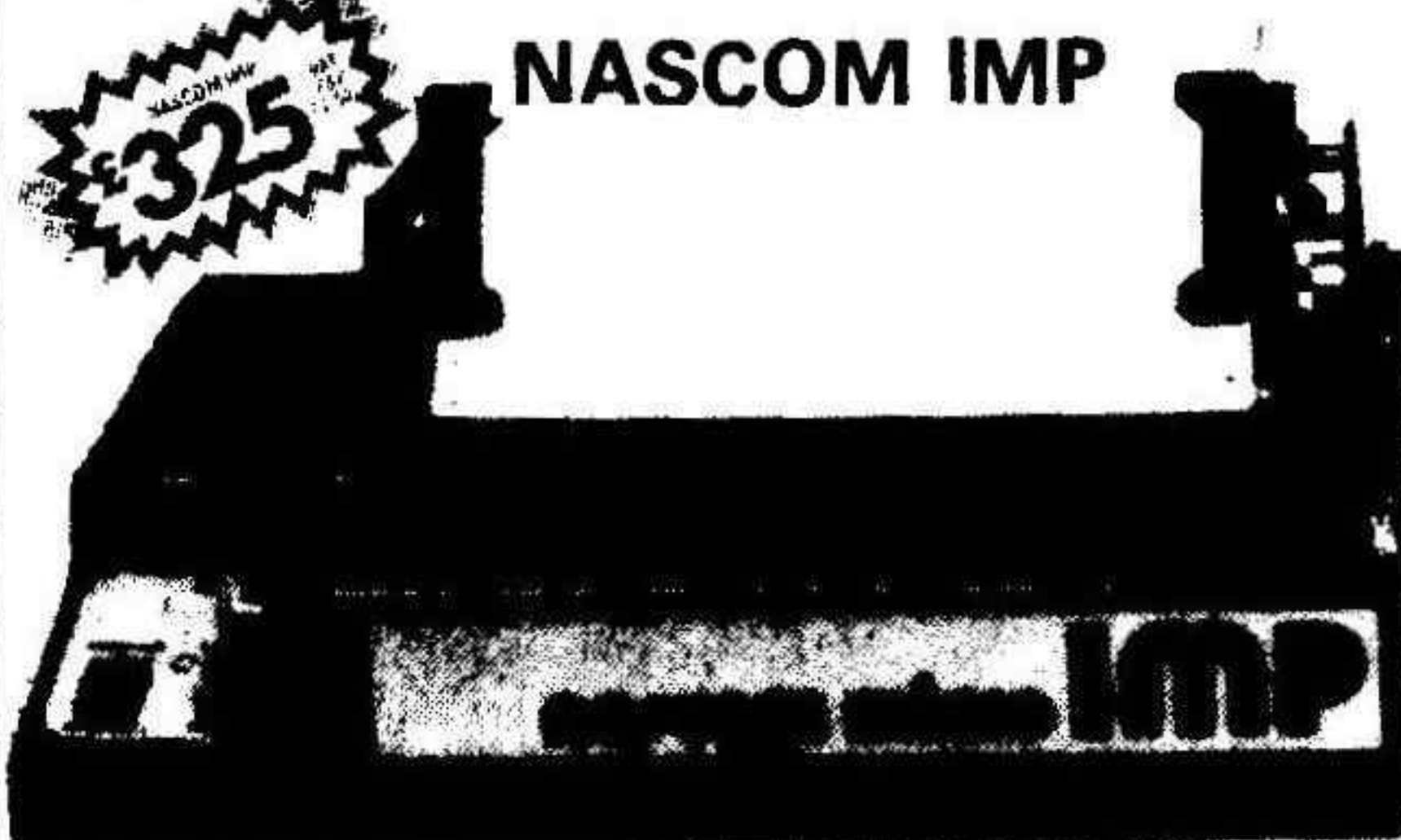
NASCOM IMP**PLAIN PAPER
£325 PRINTER**Fully built and
housed in a
stylish enclosure
for just £325 plus VAT.

INTERFACES WITH ALL MICRO COMPUTERS

The Nascom IMP (Impact Matrix Printer) features

- 60 lines per minute. 80 characters per line.
- Bi-directional printing. ● 10 line print buffer.
- Automatic CR/LF. 96 character ASCII set (including upper/lower case, \$, £). ● Accepts 8 1/2" paper (pressure feed). ● Accepts 9 1/2" paper (tractor feed). ● Tractor/pressure feed. Baud rate from 110 to 9600. ● External signal for optional synchronisation of baud rate.

IDEAL FOR WORD PROCESSING

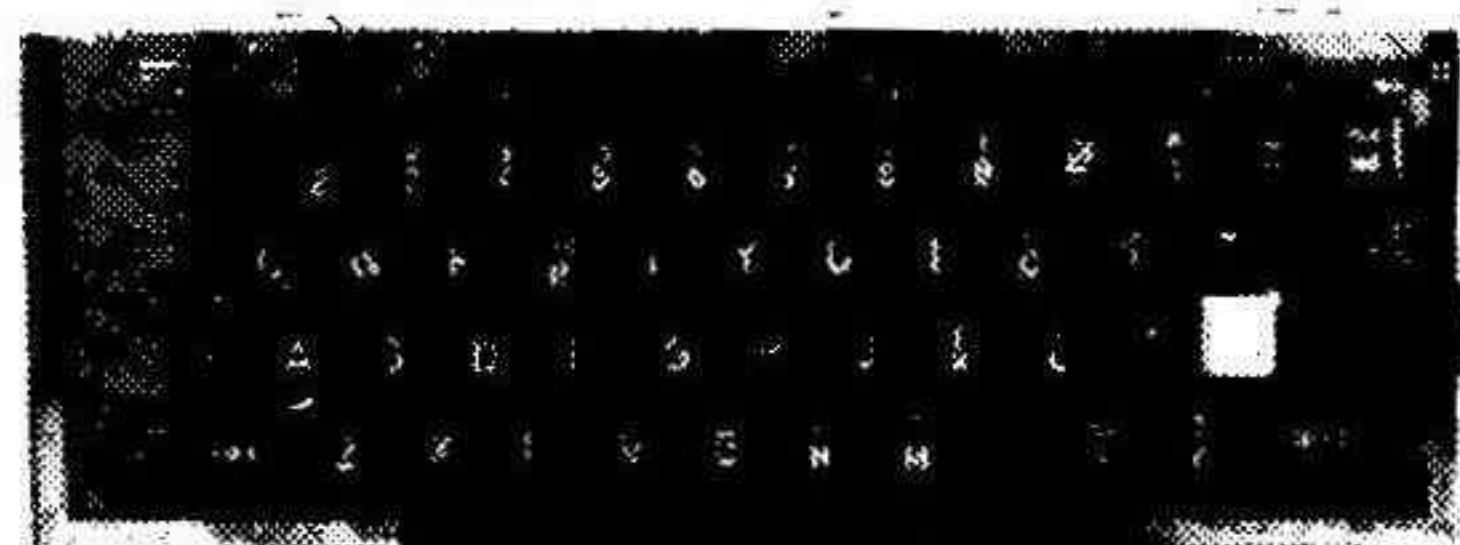COMPUTER KEYBOARDS

TASA 56 key touch sensitive keyboard. All ASCII characters including control keys. Parallel output with strobe. Shift lock. Keys coded in 3 colours to indicate function. 18 V DC at 35 mA. 15" x 6.25" x 0.385" thick. Black resin encapsulated.

49.50 + VAT

STAR DEVICES MK III 71 keytouch sensitive keyboard. With numeric pad. All ASCII characters including control keys. Auto key repeat. Parallel output with strobe. Shift lock with indicator LED. Built in 'beeper' with level control. 5V DC at 300mA 15" x 7" x 1.25". Grey case with white keys on blue.


48.50 plus VAT

CARTER 57 key ASCII keyboard. Conventional key board. 128 ASCII characters including control keys. Parallel output with strobe. Shift lock. + 5 V and -12 V DC. 12" x 5.5" x 1.5". Black keys with white legends.

39.34 + VAT.

FERRANTI — "SIZE 14 x 6 x 3" SLOPING FRONT" 55 Key ASCII Coded in steel case. Complete with Plug and Cable with circuit to convert to T.T.L. levels.

In good condition at only £25 + VAT, P/P £2.50

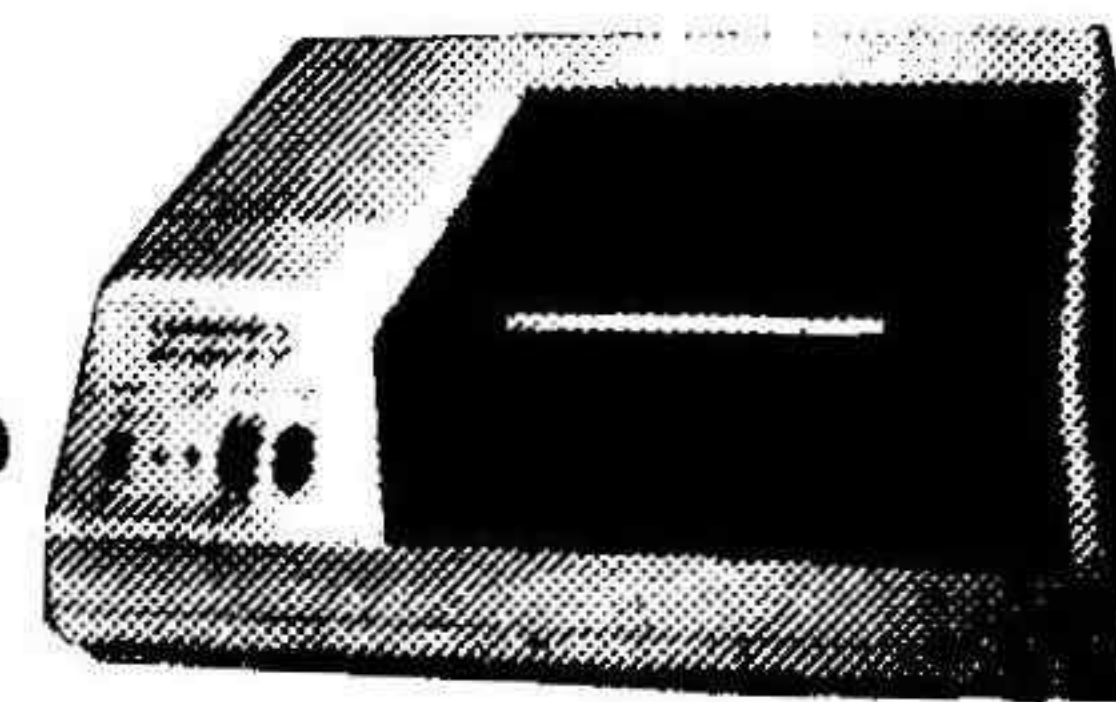CENTRONICS QUICK PRINTERList
Price
£459
incl.
VATOUR
PRICE
plus
VAT**EXCLUSIVE TO HENRY'S
50% OFF MAKER'S PRICE £195**

for: Software selectable 20, 40 and 80 column using 120mm aluminium-ised paper. 1 roll supplied. 150 lines per minute.

TANDY, PET, NASCOM Centronics parallel data interface for Nascom, Tandy, etc.

240 volt mains input. ASCII character set Paper feed, and on/off select switches

'BELL' signal Weight 10lbs

Size: 13" x 10 1/2" x 4 1/2"

New, boxed and fully guaranteed

POST PAID Price £195.00 + VAT

See **COMPUTING TODAY** Recommendations
MARCH/MAY ISSUESFull ASCII keyboard (built) £49.00 plus VAT
The ASCII keyboard includes a numeric keypad and ribbon cable connector. Cabinet available at £20.00 plus VAT.

We have produced a mini-rack which accepts MICROTAN 65 and TANEX, it has an integral power supply, just plug it into the mains and away you go! Finished in Black/Tangerine/Brushed aluminium, it gives your mini-system the professional finish. £43.00 plus VAT

TANGERINE

LONDON STOCKISTS

Microtan 65 Kit, Incl. VAT £79.35
Microtan 65 Assembled, £90.85Tanex (min. con) Kit, Incl. VAT £49.45
Tanex Assembled Incl. VAT £60.95
Lower case pack. Incl. VAT £10.90
Chunky Graphics Pack, Incl. VAT £7.50
20 Way Keypad Incl. VAT £11.50
Mini-mother board Incl. VAT £9.95
Complete Tangerine range available

SEND FOR COMPLETE COMPUTER BROCHURE FREEPOST TO ADDRESS BELOW

London Tangerine and National
Nascom Distributor
Export Orders deduct VAT, but add 5% carriage
Official Export & Educational Orders welcome
Our Telex 262284 Mono Ref. 1400 TransonicsADD VAT
15%
TO YOUR
ORDER
EXCEPT
WHERE
STATED**HENRY'S**

Computer Kit Division

404 Edgware Road, London, W2, England I.E.D.
01-402 6822

SURVIVAL GAME

A highly addictive but infuriating game. Escape from the tyrannical machine if you can. Naturally, the game has sound effects, LED readouts and a skill level control.


Survival is a small hand-held game in which the contestant pits his wits against those of the machine. The machine is a tyrannical device, dedicated to enslaving you by repeatedly making threatening gestures towards you (indicated by a brief flash of a LED as the threat is unleashed). When a threat is made you can either submit, by doing nothing, or you can defy the tyrant by pressing a JUMP button and trying to escape up a flight of steps (indicated by a vertical column of ten LEDs).

To escape, you must press the JUMP button only when the threat LED is on. Each time you make a successful jump, you move a discrete amount towards the top of the steps and eventual escape (indicated by a pulsed WIN sound as the top LED of the column illuminates). If you make a single wrong move while on the steps, however, the tyrant will instantly strike you (indicated by a 'bleep' sound) and send you tumbling back down to the bottom of the steps. Alternatively, if you submit to the threats (by doing nothing) the tyrant will slowly lure you down from your perilous perch.

An Evening's Work

The machine makes a threatening move once every second or so, but the actual threat lasts for only a fraction of this time. The game is provided with a SKILL level control, which enables the threat duration (and thus the escape time) to be varied from over 200 mS to less than 50 mS. At the lowest skill level, it is possible to escape from the tyrant in only four to five successful moves. At the top skill level, between thirty and forty successful moves are needed to ensure escape. The escape 'steps' are exponentially weighed, so that climbing becomes progressively more difficult with each move.

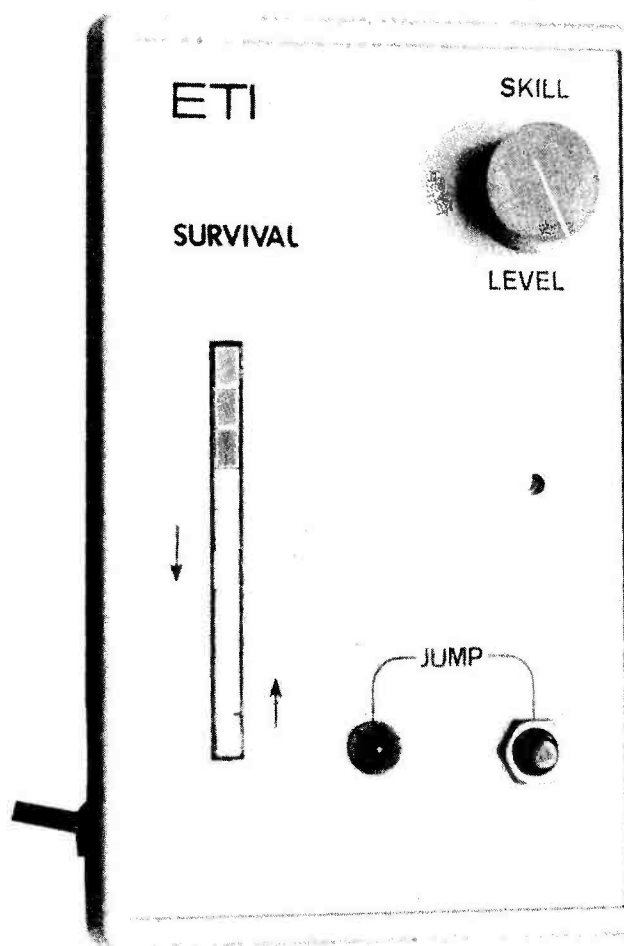The SURVIVAL game is designed around three ICs and three transistors, is reasonably inexpensive to build and is powered from a single 9V battery. The project can be built in one or two evenings.




Construction

Construction of this project should present few problems if the overlay is followed with care. Note that IC3 is a CMOS device and should be mounted in a suitable socket.

When construction of the PCB is complete you can either make temporary connections to the eleven LEDs and the transducer, etc and give the unit a functional check, or you can dive in and fit the whole shebang in a suitable box and give the unit a functional check afterwards. If you decide on the latter approach, note that the unit typically consumes some 30-40 mA and should ideally be powered from a PP7 or larger battery, but that our own prototype is in fact powered (or under-powered!) from a PP3.

It is advisable, before completing the interwiring, to functionally check the performance of each of the eleven LEDs used in the unit.

When construction is complete, switch the game on and check that LED 11 flashes briefly once every second or so and that the flash duration can be varied by RV1. You can check the action of C4 and the ten-LED read-out circuit by temporarily shorting the top of R8 to the positive supply line, in which case the LEDs in the column should sequentially illuminate and the WIN alarm (a pulsed tone) should sound when the upper LED (LED 10) turns on. Finally, remove the temporary short and press PB1 when LED 11 is off, checking that the column of LEDs turn off and a brief tone is generated. Your game is then complete and ready for use.

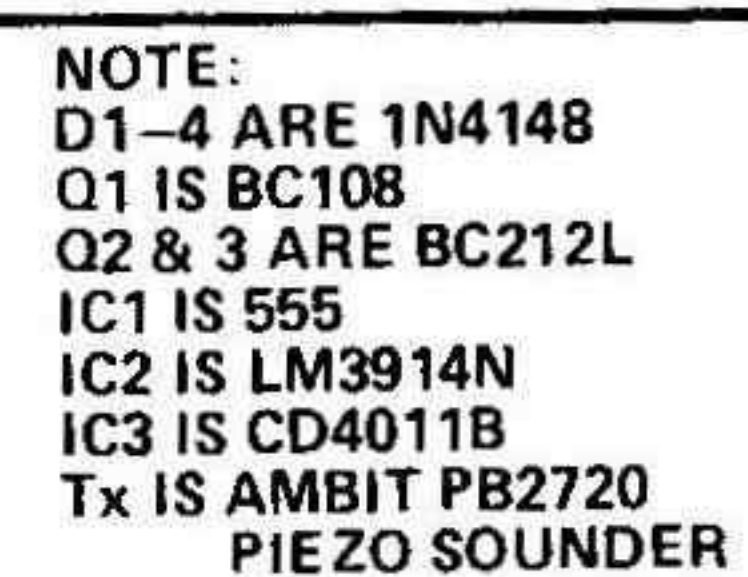

NOTE:
D1-4 ARE 1N4148
Q1 IS BC108
Q2 & 3 ARE BC212L
IC1 IS 555
IC2 IS LM3914N
IC3 IS CD4011B
Tx IS AMBIT PB2720
PIEZO SOUNDER


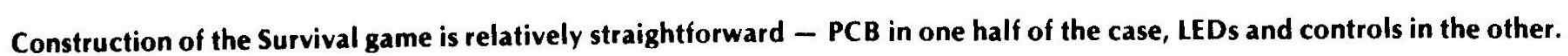


Fig.1b. The sound effects generator consists of two gated astable multivibrators. The game just isn't complete without it.

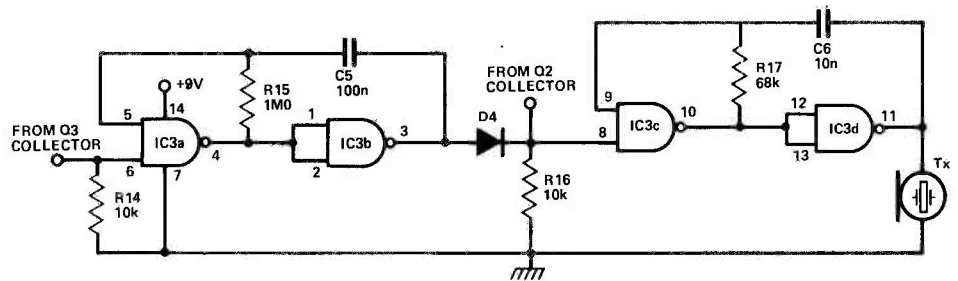

HOW IT WORKS

The basic operating principle of the game is quite simple. IC1 is a low frequency (less than 1 Hz) astable; its output switches alternately between the low (zero) and high (+9 V) states, driving LED 11 on whenever the output is high. The idea of the game is to close PB1 whenever LED 11 is on, thereby causing C4 to slowly charge up via R8, but to ensure that PB1 is open whenever LED 11 is off, thereby preventing C4 from rapidly discharging via R9 and D2. The voltage of C4 is monitored by a LED voltmeter (IC2 and ten LEDs) and the game is won when C4 charges to roughly half supply voltage (LED 10 on). IC3 is used as a sound effects generator and produces a brief tone whenever C4 goes into the discharge mode or a pulsed tone when the game is won.

The operation of the IC1 astable is slightly unusual. Here, C2 alternately charges (LED 11 on) via R1-D1-RV1-R3 in parallel with R2 and discharges (LED 11 off) via R2 only, thereby producing a non-symmetrical output waveform in which LED 11 is on for a shorter period than it is off. The on/off ratio is variable via RV1, which thus acts as a Skill Level control.

The pin 1 ('ground') terminal of IC1 is taken to the 0V line via the base-emitter junction of Q1, shunted by R4 and C3. Whenever C4 is inadvertently discharged by closing PB1 at the wrong time, the capacitor discharges through this junction and turns Q1 on,

thereby causing Q2 to turn on and activate the IC3c-IC3d half of the sound-effects generator circuit.

Capacitor C4 charges slowly in the exponential mode via R8 when PB1 is correctly closed and discharges rapidly via R9 and D2 when PB1 is incorrectly closed. The capacitor discharges very slowly via R10 when PB1 is open. The C4 voltage is monitored by LED voltmeter IC2, which drives a line of ten LEDs in the 'dot' mode. The voltmeter is programmed (via R11) to read full scale (LED 10 on) when C4 is charged to approximately half supply volts and is offset by approximately 600 mV via D3. The base-emitter junction of Q3 is wired in series with LED 10, causing Q3 to turn on and activate the IC3a-IC3b half of the sound effects generator when LED 10 turns on (game won).

The sound effects generator is made up of two gated astable multivibrators. IC3c-IC3d act as a fast (1 kHz or so) astable which directly drives a piezo transducer or sounder and is gated on via Q2 collector whenever PB1 is incorrectly closed. IC3a-IC3b act as a slow (a few Hertz) astable which is activated via Q3 collector when LED 10 turns on and pulses the fast astable on and off to produce a distinctive pulsed-tone GAME WON sound.

The entire circuit is powered from a 9 V battery. The circuit typically consumes some 30-40 mA, so this battery needs to be a PP7 or larger size.

PARTS LIST

Resistors all 1/4W 5%	
R1,11,14,16	10k
R2	220k
R3	33k
R4	100R
R5,6	4k7
R7	820R
R8	12k
R9	120R
R10	330k
R12	470R
R13	1k2
R15	1M0
R17	68k
Potentiometer	
RV1	470k
Capacitors:	
C1,4	220u electrolytic axial
C2	4u7 electrolytic
C3,5	100n polycarbonate
C6	10n polycarbonate
Semiconductors:	
IC1	NE555
IC2	LM3914
IC3	4011B
Q1	BC108
Q2,3	BC212L
D1-D4	1N4148
LED 1-10	TIL 220 or square LEDs
LED 11	TIL 220 standard red 0.2"
Miscellaneous	
PB1	momentary push button
SW1	SPST miniature toggle
B1	PP3
Tx1	transducer (See buylines)
Ceramic resonator	
Case (See buylines)	

BUYLINES

All components used in the ETI Survival game are common types and should present no problems.

The case for this project can be obtained from OK Machine & Tool Ltd. Phone: 0703-610944. Order as Series HP colour tan. Ambit International are stockists for the transducer.

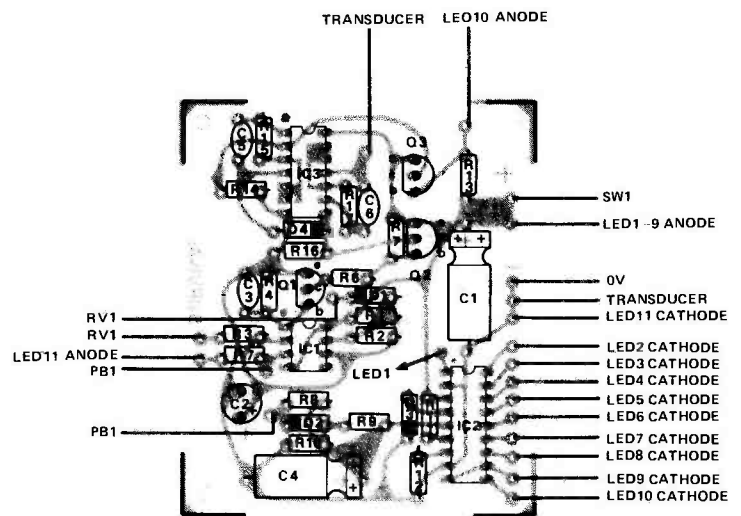


Fig.2. Component overlay. Lots o' LED leads to lace up — there's nothing to it.

AUDIO AND TEST EQUIPMENT CENTRE

Telephone your order with Access and Barclaycards or send cheque with order.



LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm

HAMEG • TRIO • LEADER • SINCLAIR • LASCAR • LEVELL • CSC

Test Equipment now in stock—send large s.a.e.

SCOPE—(UK P/P £2.50 ea.)
HM 307-3 10MHz single beam with Component Tester 170.00
HM 312-8 20MHz dual trace 287.50
HM 412-4 20MHz sweep delay dual trace 402.50
SINCLAIR 10MHz Miniscope. P/S 4.00, Nicads 7.95, Case 8.80 152.50
PROBES x1/x10 12.95, x10 10.50, x1 8.50, x100 16.95.

FREQUENCY COUNTERS

OPTO 7010A 9 digit, 600MHz Portable, 0.1Hz Resolution with NICADS £162.50
MAX 50 50MHz 6 digit pocket counter £1.00
MAX 100 100MHz 8 digit portable counter £8.75
MAX 550 550MHz 6 digit pocket counter £108.00
500 MHz Prescaler for max 50 or max 100 40.00
PFM200 Sinclair 200MHz Pocket Counter 8 digit £4.50
OPTIONAL P/S 4.00, Connector Pack PFM200 £9.95
c7216R, 10MHz, 8 Digit Panel Mounting £5.80
c7218R, 150MHz version £8.25

DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit LED 56.50
PDM35 Sinclair Pocket 3 1/2 digit LED 36.50
HM 310 Sinclair 3 1/2 digit with 10 amp range 107.95
DM450 Sinclair 4 1/2 digit (30kV Probes 15.95, P/S 4.00, DM Nicads 7.95, Cases 8.80)
M1200 Bench Portable 3 1/2 digit LED Resolution 1µA/0.1mv/0.01ohm SPECIAL PRICE NOW £59.50
LMM100 Lascar 3 1/2 digit 2A LCD Bench 0.1% £6.50
LM2001 Lascar 3 1/2 digit 2A LCD Hand 0.1% £1.70
LM200 Lascar 3 1/2 digit 2A LCD Economy 0.5% £4.40
ME502 3 1/2 digit 10e LED plus transistor tester £43.95

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges (TM3 AC volts only), some with AC current, etc. *

TM11 incredible 120 Range Electronic Multi-meter £172.50
TM38 AC Micro voltmeter 3MHz > 4 Megohm (large scale) £46.75
TM3A AC Micro voltmeter 3MHz > 4 Megohm £49.50
3607R 100k/volt* 23 Range (plus transistor checker), Large scale £34.95
7080 20k/volt 26 Range, Large scale £28.95
7081 50k/volt 36 Range Multi-meter, range doubler £19.95
NH55 2kv 10 Range Multi-meter £9.95
NH56 20k/volt 22 Range Popular Multi-meter £10.95
LT101 1k/volt 12 Range Pocket Multi-meter £5.95
VN300TR 20k/volt 19 Range Multi-meter plus transistor check £13.95
AT205 50k/volt 21 Range Multi-meter £24.95
AT1 2k/volt 12 Range Multi-meter Deluxe £7.95
TMK500 30/volt 23 Range Multi-meter, with case £22.95
AT1020 20/volt 19 Range Multi-meter with transistor tester Deluxe £16.95
AT2050 50k/volt 18 Range Deluxe Plus transistor checker £28.50
AT210 100k/volt* 21 Range Multi-meter Deluxe £29.95

AVO 8s and a large range of replacement test leads in stock

GENERAL EQUIPMENT

SE250 Signal Injector 4.95
TE7 Signal Tracer AF/RF 9.95
SWR60 SWR/Power Meter 13.95
DR810 36 Value Resls. Box 3.95
RP124 0/24V 0/1 amp P/S Stabilised 42.50
RP324 3 amp version 54.00
RP230N 0/30v 0/1 amp, P/S Twin Meters 85.00
TR1000 Transistor checker in/out circuit 11.95
MOD43 Signal injector 8.95
C3022 Transistor/Diode Checker 19.95
3101 Clamp Meter Q1 1k ohm, 0/150/300/600 AC volts 0/300 amp 32.95
SWR40/8 SWR & FS Meter 10.50
SWR10 SWR Meter 10.95
MS319 2x100 Watt Audio Watt Meter 13.95
550V Megohm Meter 500 Megohms 51.00
2 1/2 Amp Variable transformer 21.95

DRILLS AND DRILL KITS

9 to 12 volt Operated 1/4" max. SMALL DRILL with collets 7.25
MEDIUM DRILL with 3 collets 10.50
SMALL DRILL with 20 drills/tools 14.95
MEDIUM DRILL with 20 drills/tools 17.95
MAINS Eliminators 9.95
VARIABLE Speed 13.95
12 volt 1/4" Heavy Duty Drill 12.50
MAINS DRILL with tool set 21.95

TV SOUND

High quality TV sound from your Hi-Fi. Simply plug into aerial socket of your FM tuner. £8.50 (UK P&P 50p).

GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges £92.00
TG162D TG152Dm (with meter) 113.85
TG200 Series RC Oscillators Sine/Square output, 1Hz-1MHz 12 Ranges £49.50
TG200D TG200Dm (with meter) 124.20
TG200Dmp (meter & fine control) 149.50
4001 Digital Pulse Generator 0.5Hz-5MHz 155.25
4001 Digital Pulse Generator 0.5Hz-5MHz 105.00
2001 Function Generator-Sine/Square/Triangle/TTL £66.00
SG2030 (RF) 6 bands 250kHz-300MHz 49.95
6052 PAL VHF/UHF Colour Bar Generator 250.00
AG761 (Audio) sine 19Hz-220Hz square 19Hz-100kHz £1.00
ARF300 (RF-Audio) 18Hz-200MHz £78.50

PROTO BOARD IN STOCK

KITS PR 6.20, PR 100 11.80.
SEPARATES EXP300 5.95, EXP600 6.50, EXP350 3.45, EXP650 3.95

LOGIC PROBES AND MONITORS

LT2000 Economy Probe 10MHz 9.95
LM1 Monitor circuit powered 33.00
LP1 Probe 10MHz 35.50
LP2 1.5MHz 20.50
16 Pin IC test clip 1.95

PIEZO HORN TWEETERS


Up to 100 watts each. No x-over reqd. Only 4.95 each. Flared Horns 6.50
Midrange Flared Horns 9.50 (UK Post Free)

SPECIAL BULK PURCHASE

EE 10+10 watt Tuner/Amplifier. MW/LW/SW/Stations Fk. Supplied as two aery to connect leads. £21.95 P&P £1.50

IN STOCK NOW

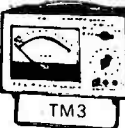Large range of speakers and kits, public address equipment, microphones, mixers, security systems, intercomms, ham equipment. See catalogue



FREE CATALOGUE

SEND STAMPED (117p UK) ADDRESSED ENVELOPE (MIN 9 1/2 x 6 1/2) FOR YOUR COPY NOW

PRICES CORRECT AT 1/7/80

AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724 3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W. 1.

GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT @ 15% — just add 40p post

HAVE YOU GOT YOUR COPY OF THE AMAZING GREENWELD CATALOGUE YET????

WHY NOT?? — LOOK AT ALL THESE FEATURES:

- * 60p Discount Vouchers
 - * Quantity Prices for bulk buyers
 - * Bargain List Supplement
 - * Reply paid envelope
 - * Priority Order Form
 - * VAT inclusive prices
- Also included is the NEW VERO catalogue, normally 40p on its own!!
ALL THIS FOR JUST 40p + 35p post!!!
Can you resist such an offer???

SLIDER POT SCOOP!!!

Made by Pihar, types PL40CP & PL60C. Siftly prices for superb goods!!
PL40CP — 69x16x9mm. 40mm slide length. 220R, 2k2 or 10k lin only. Prices (any mix): 1-24 20p; 25-99 17p; 100+ 14p.
PL60C — 84x10x7mm, 60mm slide length. 5k, 10k, 22k and 100k log. only. Prices (any mix) 1-24 25p; 25-99 22p; 100+ 17p.

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia x 20mm 70p.
Z402 Miniature type buzzer, 6, 9 or 12V. only 22x15x16mm. Very neat 53p.
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only £1.
A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage reqd 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied £1.50
WB92 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket 85p.
WB90 DiD Reed relay SPCO 2-4-10V. 200R coil. Only £2.20.
FSRA60 relay, 2 x 10A contacts. 1M, 18. Coil is 250R, and rated 60V ac, but works on 12-24 DC. Solid Encapsulation with screw terminals makes it ideal for car use. £1.20.

REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.
SPEC: Output voltage 0-28V
Output current 20mA-2A
Source impedance 0R1
Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only £6.75

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low price!! Almost all are marked with type number — almost all are full spec. devices. Some have bent leads. Over 30 different types have been found by us including BC184/212/238/307/328. BF196/7. 2TX107/8/9/342/450/550. etc. Only available as a mixed pack at £3 per 100. £7 per 250. £25 per 1000.

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES

K001 50V ceramic disc capacitors. 5%, 10 of each value 22pF to 1 000pF total 210. £3.69.
K002 Extended range 22pF to 0.1µF. 330 values £5.53.
K003 Polyester capacitors. 10 each of these values. 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £8.07.
K004 Mylar capacitors min 100pF type 10 each all values from 1 000pF to 10 000pF Total 130 for £4.05.
K007 Electrolytic capacitors 25V working small physical size. 10 each of these popular values. 1, 2.2, 4.7, 10, 22, 47, 100µF Total 70 for £3.59.
K008 Extended range, as above, also including 220, 370 and 1000µF. Total of 100 for £8.05.
K021 Miniature carbon film 5% resistors CR25 or similar. 10 of each value from 10R to 1M. E12 series Total 610 resistors £6.15.
K022 Extended range. Total 850 resistors from 1R to 10M £8.50.
K041 Zener diodes 400mW 5% BZY88 etc. 10 of each value from 2.7V to 36V. £24 series. Total 280 for £16.37.

TM4030 RAM

4096 bit dynamic RAM with 3000ns access time 470ns cycle time, single low capacitance high level clock i/p. fully TTL compatible: low power dissipation. Supplied with data £2.75.

COMPONENT PANELS

Z525 Contains 11 800mA 60V 2N5061 SCRs, 11 6V8 diodes, 11 1N4004 diodes plus Rs, Cs, etc. Only £1.
74 Series ICs — Gates and complex logic. 20 assorted ICs on panels £1; 100 ICs £4.
Z527 2x6V reed relays, 8x25030 or 25230 6x400V reeds, plus Rs. Only 50p.
Z531 Trimpot Pack — Ex-computer panels with 20 mixed value multi-turn types £1.00.

VEROCASE SALE!!!

Only one size left now — these have sold very fast — if you want a 1/2 price case like 75 3008, only in GREEN, order one now!!
21051 180x120x85mm £2.30.

P.C. ETCHING KIT Mk IV

The best value in etching kits on the market — contains 100 sq ins copper clad board, 1lb Ferric Chloride, Etch resist pen, abrasive cleaner, 20 miniature drill bits, etching dish and instructions. All for £4.95.

BULK SUPPLIES

All new full spec. devices. Prices are for a minimum of 100 of any one device and exclude VAT, which must be added at 15%. Minimum order value from this section is £10+VAT+post. VAT receipt on request.

RESISTORS

Min. 1/4W 5% carbon film 1R-10M (10% over 1M), all £8.00/1,000.
The following values only at £3.80/1,000, per value 47R, 82R, 18R, 39R, 56R, 220R, 1k, 4k7, 18k, 33k, 39k, 47k, 220k, 390k, 560k, 680k, 820k.

MIN. PRESETS

0.1W miniature type, open construction. All values from 100R to 1M, vertical or horizontal mounting. All at £0.42.
The following values only at .03: 470R, 470RH, 500RH, 1kH, 1k5H, 2kV, 2k2H, 2k5H, 4k7H. Also some Pihar enclosed type at .042: 150RV, 200RH, 2kV.

POTS

5k lin: 100k lin; 220k lin; 500k log; 1M lin. All with std. bush and spindle. £1.14.

ELECTROLYTIC CAPS

2.2/25 R	.028	47/63 R	.045
2.2/63 A	.032	100/63 A	.020
4.7/10 R	.022	100/35 R PC	.035
4.7/25 R	.028	220/16 A	.055
4.7/50 R	.034	220/25 R	.065
10/16 R	.030	220/70 A	.075
10/25 R	.032	330/50 A	.075
10/25 R PC	.022	330/100 A	.085
10/50 A	.035	470/16 R	.060
10/50 A	.040	470/100 RC	.150
10/100 R	.042	1000/40 A	.230
15/40 A	.030	1000/63 A	.280
22/10 R	.021	2200/10 R	.080
22/25 A	.026	2200/25 A	.280
22/25 R	.027	2200/40 RC	.350
22/63 A	.040	3300/10 A	.090
33/16 A	.022	3300/25 A	.180
47/6 A	.015	4700/10 A	.100
47/25 A	.032	4700/25 RC	.250
47/35 R	.038	4700/40 RC	.35
47/40 A	.045	10000/15 RC	.250

R=radial leads R PC=short radial
A=axial leads L leads for PC mounting
RC=tag ended can

POLYESTER CAPS

01	400V	C296	.025
015	250V	C280	.025
022	400V	C280	.026
068	250V	Advance	.025
22	250V	C280	.035
22	250V	Advance	.035
22	100V	Minicap	.035
47	250V	C280	.05
47	160V	C296	.04
1.0	250V	C280	.055
1.5	63V	Filmcap	.065
2.2	160V	Filmcap	.08
3.3	100V	Wima MKS	.195
4.7	100V	Wima MKS	.235
4.7	100V	Wima MKS	.285

POLYSTYRENE CAPS

22pF	125V 5%	£8/1000	1.5/35 .06
27pF	125V 5%	£8/1000	3.3/25 .18
1500pF	125V 10%	£14/1000	10/25 .15
8200pF	125V 10%	£18/1000	

MINIATURE CERAMIC CAPS

Thompson/CSF miniature type in the following values
3.9pF 4.7pF, 22pF, 33pF, 47pF, 47pF, 68pF, 82pF, 100pF, 560pF, 2700pF. All 5% except 10%, 1020%.
Prices: up to 82pF £7/1000
100pF £9/1000
560pF £5/1000
2700pF £9/1000
Samples on request (see please).
Mullard min. ceramics:
33pF 5% 100V £7/1000
330pF 2% 100V £8/1000
330pF 10% 100V £13/1000
Siemens min. ceramics:
330pF 5% 63V £7/1000
022uF 53V £14/1000
Lemco 047uF 63V £16/1000


SEMICONDUCTORS

741, 12, 555, 19, 7401, 08, 7405, 09, 741, 74, 21, 4001, 17, 4011, 17, 51 signal diodes like 1N4148 by Ticon bandolered sets of 10k £80 (1k £10), 1N4002 £25/k, 1N4006 £34/k, 1N4007 £36/k, Ge signal diode DK14 £20/k, SCRs, 2P4M (C106D) 4A 400V, 26, 2N5060, 8A 30V, 15, CR201 1A 200V, 18.
See last month's advert. for transistors; send s.a.e. for latest bulk buyers list.

If you need a little vice — consult the

VICE SQUAD

DREMEL D-VICE

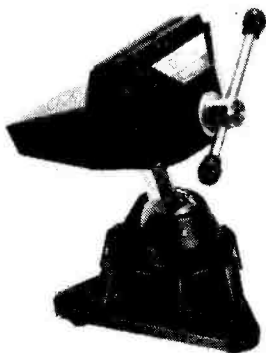

2214. Bench mounting screw down Base — multi position vice $2\frac{1}{2}$ " jaw opening.



2218. Handy clamp available for converting 2214 to completely portable tool for easy attachment to bench or table top.

2221. Combination vice and clamp.

VACU-VICE

Vacuum Base ensures instant easy hold and release on smooth non-porous surfaces.

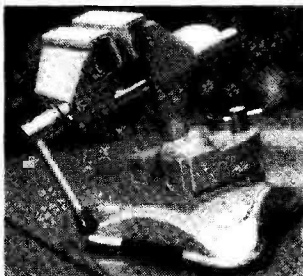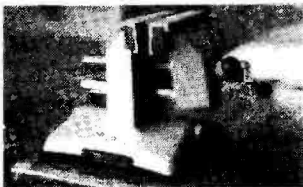Models 300 & 400 have full 3" jaw opening and include rubber slide on jaws for handling delicate work.



PROFESSIONAL TOOLS for the workshop, home laboratory or on-site use

Literature and prices on request

Special Products Distributors Limited

(Dept. ETI) 81 Piccadilly, London W1V 0HL

Tel: 01-629 9556

Cables: Spiroird, London W1


Telex: 265200 (Answerback RACEN)

SAFGAN ST-45

High-quality low-cost single trace Oscilloscope that is simply — SUPERIOR. Compare us and see.

Price at £137*

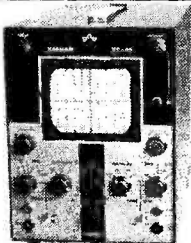● 10mv/div ● 5MHz ● BRITISH
● ONE YEAR GUARANTEE



ST-45 SPECIFICATION VERTICAL SYSTEM

Sensitivity 10mv/div 5v/div in 9 cal. steps
Bandwidth (3dB)
DC Coupled DC 5MHz
AC Coupled 5Hz-5MHz
Risettime 70µsec
Input Impedance 1MΩ + 22 PF approx. (for all ranges 500 for 10mv/div
Input Coupling AC CND DC
Input volts: 400V max.
Accuracy + 5%

HORIZONTAL SYSTEM

Time base speeds
50ms/div 1µsec/div in 15 cal. steps with
X5 Multiplier to 250msec/div and X5
Expansion to 200nsec/div
External — X sensitivity 1v/div
External — X Bandwidth 500KHz
Accuracy + 5%

ACCESSORIES

Passive Probe switched (X1, REF. × 10)
100MHz bandwidth £11.50 + VAT.
BNC to 4mm Socket Adaptor £2.95 + VAT

TRIGGER

Internal 0.5 div (20Hz-2MHz), 1 div (2MHz-5MHz)
External 100mv (20Hz-2MHz), 200mv (2MHz-5MHz)
Bright Line Auto
Trace free runs in absence of signal
Trigger Level selects triggering point
Trigger (+ve and (-ve slope selection

FRONT PANEL

Black-Silver-White-ST-45-S The Silver Scope
Black-Gold-White-ST-45-G The Gold Scope.

GENERAL

Blue display graticule ruled 8 x 10 div (6.4cm x 8cm).
Power consumption 10VA approx.
Mains selection 200v-220V-240V rms (40Hz-60Hz)
Size: H. 215mm; W. 165mm; D. 280mm.
Weight 10lbs 4.5kg approx.
Case aluminium with black pvc finish and black handle, scratch-resist front panel, black control knobs, black feet and tilt bar.

Safgan Electronics Ltd.

56 Bishops Wood, St. Johns
Woking, Surrey, GU1 3QB

Educational and Government
Institutions official orders
accepted.

ORDERS TO: SAFGAN ELECTRONICS LTD.

56 Bishops Wood, St. Johns, Woking
Surrey GU21 3QB or Tel: Woking 66836

Please send me ☐ ST-45 ☐ Probe ☐ Adaptor

I enclose PO/Cheque ☐ (Goods + 15% VAT + £3.00 p&p)

Name

Address

* Ex VAT UK A80 ETI

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to your outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide in Electronics

Name

Address


Age

ICS

To ICS, Dept. Y265, Intertext House,
London SW8 4UJ
or telephone: 01-622 9911
(all hours)

ELECTROVALUE

FOR COMPONENTS THAT COUNT

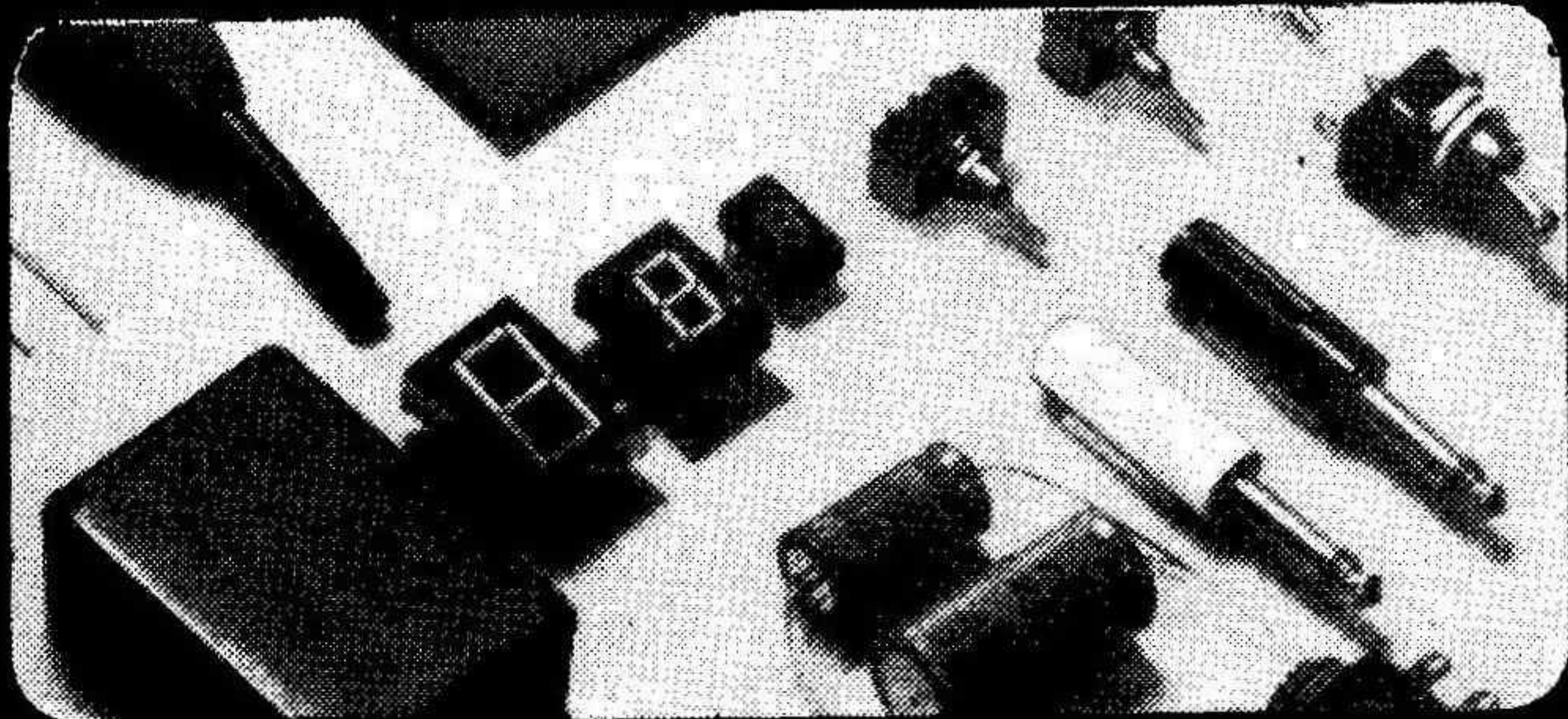

SIEMENS
SEMI-CONDUCTOR
CAPACITORS
FERRITES

NASCOM
MICRO COMPUTERS
AND
ANCILLARIES

VERO
BOARDS
CASES &
KITS

ISKRA
RESISTORS

RADIOHM
POTENTIOMETERS

BREADBOARDS
SOLDER TOOLS

OPTO-ELECTRONICS

SWITCHES

CATALOGUE 10

**ALL GOOD PROJECTS START WITH CATALOGUE 10
IT'S FREE FOR THE ASKING**

128 pages packed with almost everything everyone wants. There are attractive discounts and free postage in UK on orders £5.75 and upwards.


ELECTROVALUE LTD. HEAD OFFICE (Mail Orders)

28(H) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: Egham 33603. Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4945.

BOMB PROOF POWER!

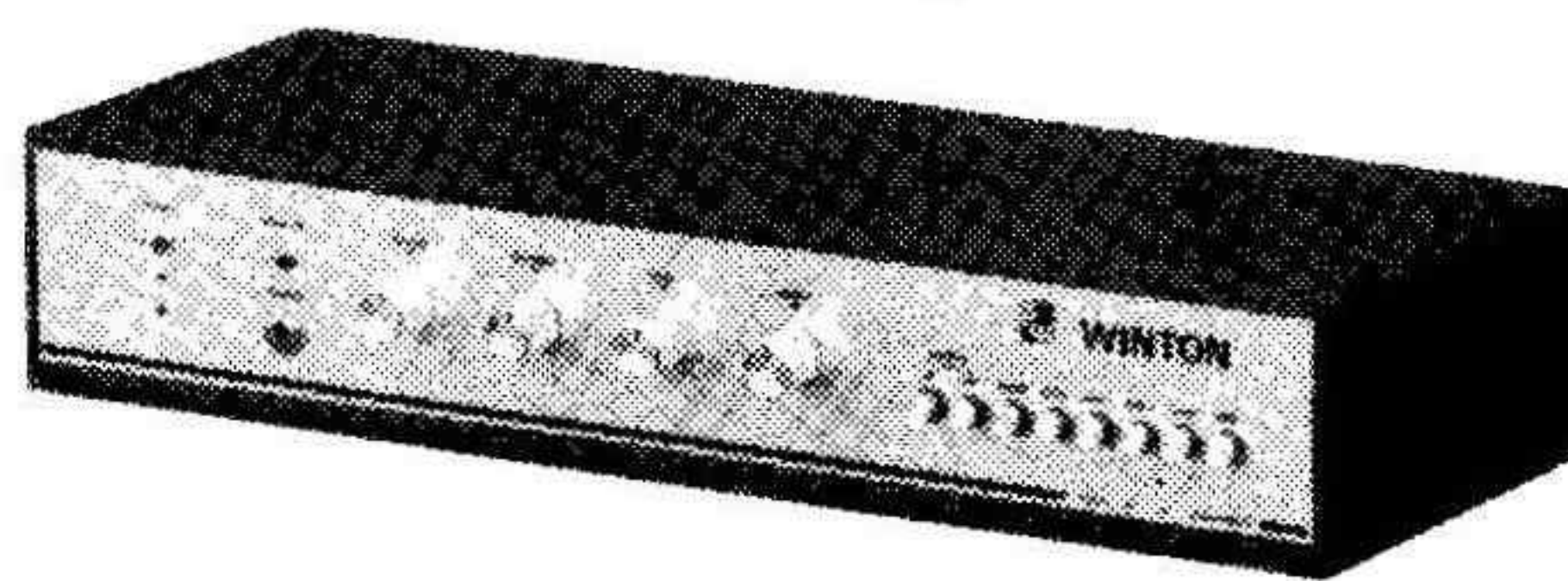

The **WINTON** is still the **OUTSTANDING KIT ACHIEVEMENT** of the decade. Using POWER MOS-FETs in the OUTPUT STAGE it provides 50 + 50 WATTS at less than 0.1% distortion over the **whole** audio band.

The Power MOS-FETs we use are practically 'Bomb Proof' without the need for distortion introducing protection devices, or as some coyly name them "Thermal Overload Cutouts." Our MOS-FETs don't suffer from thermal runaway or secondary breakdown as ordinary transistors do.

Requiring around twenty hours to build you finish up with an amplifier which is equal to, or better than ready-built designs costing upwards of £600, and you have the enormous satisfaction of having built it yourself.

A 12p stamp will bring you the full details or better still, send your cheque for the best amplifier kit around. POWER MOS-FETs RULE, O.K.

COMPLETE KIT of all parts necessary to build the P.W. WINTON **£133.50**

Order with complete confidence (C.W.O. only please) from:

T. & T. ELECTRONICS (Dept. E)
Green Hayes, Surlingham Lane, Rockland St. Mary
Norwich NR14 7HH. Telephone 05088 632

PRICE INCLUSIVE OF V.A.T. & CARRIAGE
Callers by appointment only

STEVENSON Electronic Components

STEVENSON

AT LAST! OUR NEW 1980/81 CATALOGUE IS NOW AVAILABLE.

Our new catalogue is just packed with components. It contains 100 illustrated pages detailing over 3000 line items. These include:

Amplifier modules	Connectors	Meters
Books	Desoldering tools	Ni-cad cells
Breadboards	Drills	Op-amps
Cabinets	Etching equipment	Rams
Cables	Heatsinks	Resistors
Capacitors	IC sockets	Switches
CMOS	Knobs	Tools
Crossovers	Mains Transformers	Triacs

Included with our catalogue you will receive:

- a reply paid envelope for your first order.
- a mail order form to facilitate rapid despatch
- a 50p discount voucher to be used against mail order purchases over £10.00.

Available now by post from the address below at a cost of **50p**

Due to stock and administrative problems over the last few months, the quality of our service had suffered considerably. These problems have now been resolved and we are confident that we can now offer the quality of service we had been accustomed to. We wish to convey our apologies to any customers who have been inconvenienced.

All prices include VAT. Please add 50p carriage on orders below £15. Contact our sales office with your requirements on: **01-464 5770**



OPTO

Red	0.125in.	0.2in.	
Green	TIL209	TIL220	10p
Yellow	TIL211	TIL221	16p
Clips	TIL213	TIL223	16p
	3p	3p	
DISPLAYS			
DL704	0.3in CC		130p
DL707	0.3in CA		130p
FND500	0.5in CA		100p

TRANSISTORS

AC127	25p	BC547	8p	TIP30C	70p
AC128	25p	BCY71	18p	TIP2955	65p
AD161	40p	BD131	35p	TIP3055	60p
AD162	40p	BD132	35p	ZTX107	12p
BC107	10p	BD139	35p	ZTX108	12p
BC108	10p	BD140	35p	ZTX109	12p
BC109	10p	BFX29	25p	ZTX300	14p
BC147	9p	BFX84	26p	ZTX500	15p
BC178	16p	BFY50	23p	2N3053	25p
BC182	10p	BFY51	23p	2N3055	55p
BC182L	10p	MJ2955	98p	2N3702	9p
BC184	10p	TIP29C	60p	2N3703	9p
BC184L	10p			2N3704	9p
BC212	10p	DIODES		2N3819	22p
BC212L	10p	1N914	4p	2N3905	10p
BC214	10p	1N4001	4p	2N5777	50p
BC214L	10p	1N4006	7p		
		BZY88 series	8p each	1N4148	3p
				1N4002	5p
				1N5401	14p

LINEAR

741	18p	LM324	52p	MM57160	650p
747	70p	LM339	55p	NE531	140p
748	40p	LM348	100p	NE555	23p
7106	850p	LM377	170p	NE556	60p
CA3046	70p	LM378	230p	NE567	120p
CA3080	75p	LM381	140p	RC4136	100p
CA3130	100p	LM382	120p	TBA800	80p
CA3140	60p	LM386	90p	TBA810	110p
LF347	170p	LM387	120p	TDA1022	630p
LF351	45p	LM1458	40p	TL081	45p
LF353	90p	LM1830	180p	TL082	85p
LF356	95p	LM3900	60p	TL084	125p
LM301A	30p	LM3909	72p	XR2206	390p
LM318	85p	LM3911	120p	ZN414	80p
		LM3914	320p	ZN425E	475p
		LM3915	320p		

PACKS

Specially designed packs intended for development work at a considerable saving.


Low resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 530p each
Low resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 875p each
Presets. Pack of 5 of each value from 100ohms to 1 Megohm. a total of 65 presets. 390p each.
LED's. Pack containing 10 of each colour LED 0.2 size. Total of 30 Led's + clips. 450p each
Zeners. Pack of 5 of each value from 2U7 to 33V. A total of 130 zeners. 880p each.

CMOS

4001	25p	4025	25p	4072	25p
4002	25p	4026	150p	4081	30p
4006	95p	4027	50p	4082	30p
4007	25p	4028	90p	4085	85p
4011	30p	4029	110p	4093	80p
4013	45p	4040	110p	4095	110p
4015	85p	4042	85p	4510	90p
4016	48p	4046	110p	4511	100p
4017	80p	4048	60p	4518	90p
4018	90p	4049	50p	4520	110p
4020	110p	4050	50p	4527	165p
4022	100p	4052	80p	4528	100p
4023	25p	4060	120p	4532	125p
4024	60p	4066	63p	4543	170p
		4068	25p	4583	80p
		4069	25p	4585	115p
		4070	25p		
		4071	25p		

SKTS

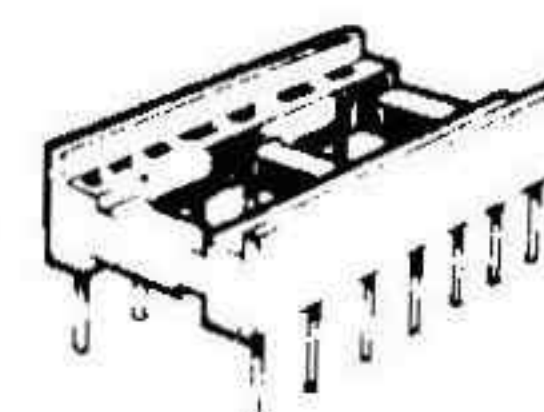Low Profile Texas
8 pin 9p 22pin 20p
14pin 11p 24pin 22p
16pin 12p 28pin 26p
18pin 16p 40pin 38p
20pin 18p



SWITCHES

TOGGLE
Standard SPST 40p DPDT 55p
Miniature SPDT 80p DPDT 90p
Subminiature SPST 65p DPDT 85p
SLIDE Standard DPDT 17p. Miniature 16p each.
PUSH Push to make 16p. Push to break 22p.


TTL

7400	15p	7447	65p	74123	50p
7401	15p	7448	65p	74125	60p
7402	15p	7472	35p	74126	60p
7404	16p	7473	38p	74132	70p
7406	38p	7474	36p	74141	95p
7408	22p	7475	40p	74145	90p
7410	18p	7476	40p	74150	120p
7413	35p	7483	80p	74154	110p
7414	56p	7485	80p	74157	80p
7420	16p	7486	35p	74164	120p
7427	30p	7490	45p	74165	120p
7430	30p	7492	55p	74174	100p
7432	35p	7493	45p	74175	95p
		7494	70p	74190	100p
		7495	70p	74191	100p
		7496	70p	74192	100p
		74121	45p	74196	100p

76 College Road, Bromley, Kent BR1 1DE.

ENVELOPE SHAPER

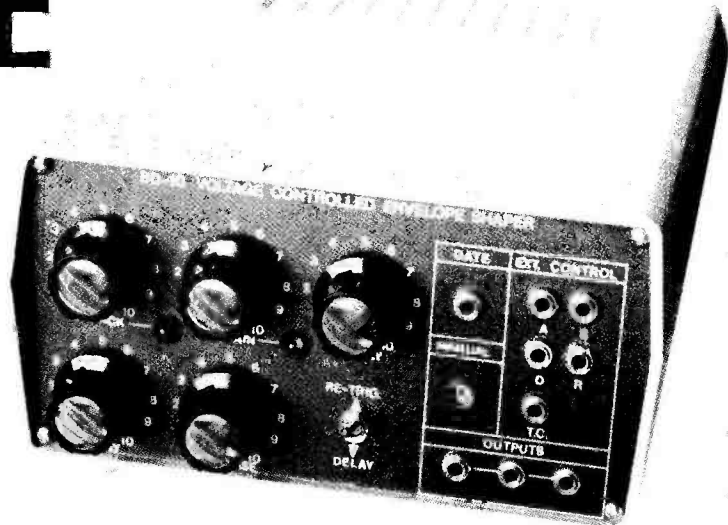Is it Mantovani or a Project 80 synthesiser? You can't tell the difference with this VCES designed by R.C. Blakey



Conventional ADSR envelope generators are adequate for most practical purposes since they are capable of providing a reasonable simulation of the amplitude envelopes of many musical instruments. The Project 80 Voltage Controlled Envelope Shaper (VCES) is provided for those who wish to obtain more realistic simulation or to obtain dynamic control over envelope shape. It is also a useful tool for innovative synthesis. The design incorporates the following features; bending of the standard exponential attack, decay and release curves to other shapes; alteration of attack, decay and release times by an external voltage thus allowing the envelope to be altered in proportion to the note played; the use of non linear sustain; built-in timer for re-triggering to create dual peak envelopes and also the generation of a delayed AD envelope.

Design and Application

The VCES is based on the CEM 3310 Voltage Controlled Envelope Generator produced by Curtis Electromusic Specialties. While it is well suited for use as a conventional ADSR envelope generator for both monophonic and polyphonic synthesisers the facilities provided on chip also make it ideal for configuring a complex envelope generator. The attack (A), decay (D), and release (R) parameters have a scale sensitivity of 60 mV/decade (18 mV/octave) while sustain level (S) is linearly proportional to the voltage applied to pin 9. To facilitate generation of complex shapes each of the four inputs has been buffered by an op amp configured as a summer and our standard 0 to +10 V control voltages allow the A, D and R times to be varied from 2 mS to greater than 20 S. Likewise for the sustain input a voltage of 0 to +10 V varies the sustain level from 0 to 100% of the peak attack voltage which has also been normalised to +10 V.

The A, D and R responses follow an exponential curve. These characteristic curves may easily be altered in this design by taking a proportion of the output from the module and feeding it back to the appropriate input for the attack curve. The greater the amount of feedback the more convex the response and, although the overall time constant will increase, this may be adjusted over a wide range with the manual control provided. If the output is inverted prior to feedback then the attack curve will become concave in shape. Some of these curves are closer approximations to

conventional instruments while others offer some novel responses. The shape of the decay curve, or the release curve, may be similarly altered and thus the VCES offers virtually unlimited scope for generation of envelope shapes. The use of low frequency waveforms to modify the time constants is also practical but setting up to obtain useful results is quite time consuming. Two attenuators, with or without inversion, are provided and the 80-5 Processor module may be used for distribution and attenuation when more complex patching is required.

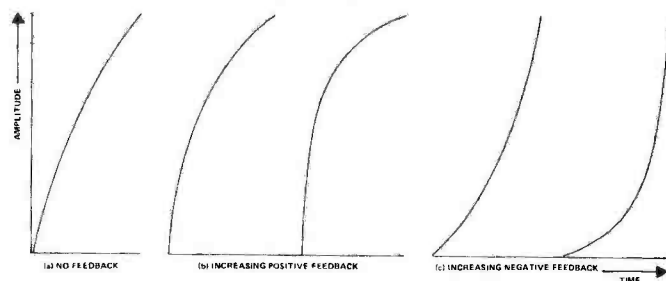


Fig.1. The effect of feedback on the attack response.

Tremolo

The sustain level also has provision for external control and one application is to apply a low frequency waveform to this input in combination with an attenuator and perhaps the manual control to produce a varying sustain. If this envelope is now used to control a VCA the effect is a tremolo only during the sustain part of the note. In the design both the upper and lower levels of the sustain control have been clamped for protection.

Another application for voltage control of envelope shape is the automatic alteration of the time constants or sustain level while the instrument is being played.

Time and Time Again

A simple timer has been incorporated in the design which allows re-triggering, or initial trigger delay, for periods up to about 2.5 S. The effect of re-triggering is to produce an envelope with two peaks, which is a transient effect exhibited by a number of conventional instruments. Often, however, as such instruments reach their peak output the

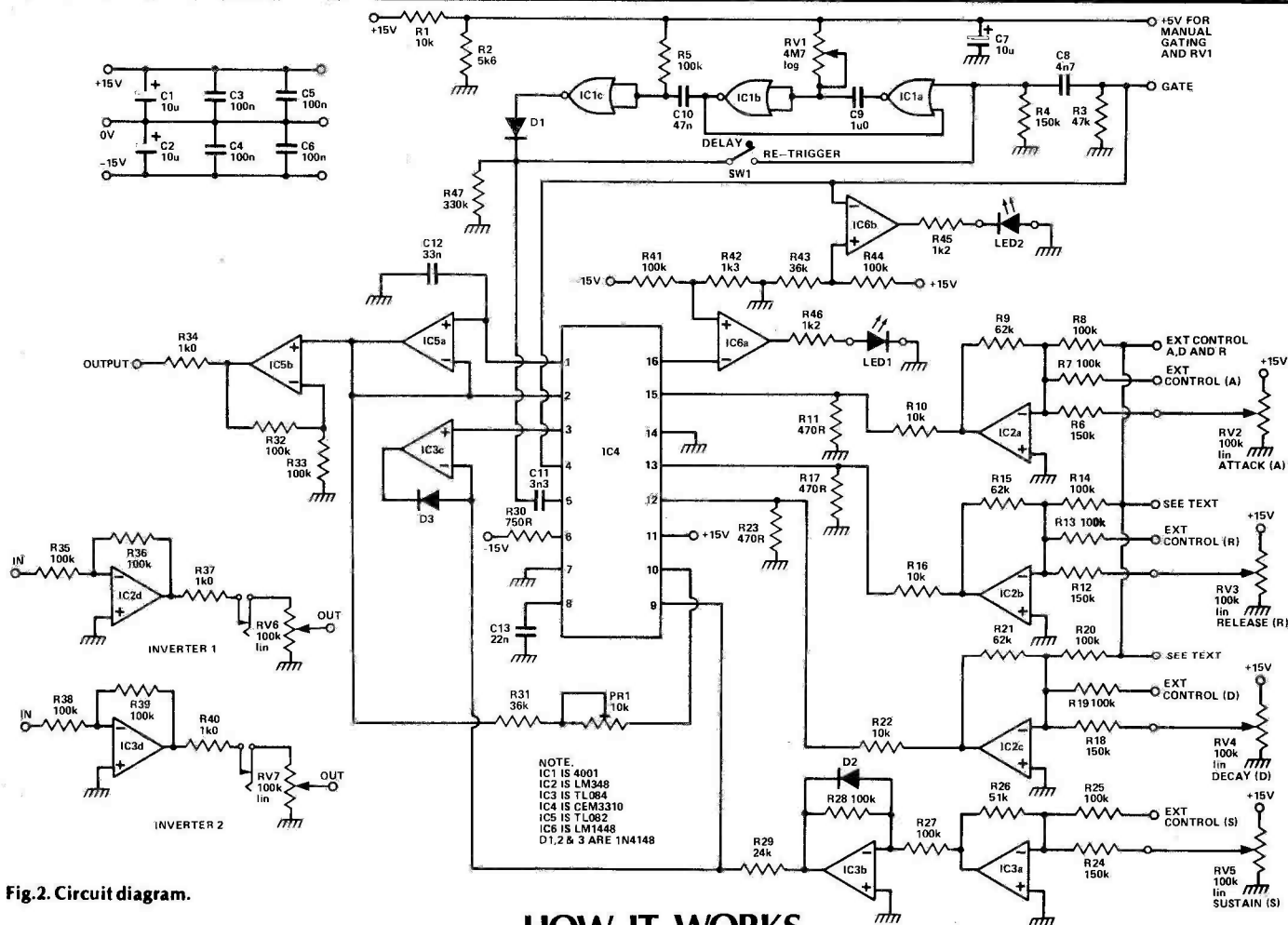


Fig.2. Circuit diagram.

HOW IT WORKS

The attack, decay and release control inputs (pins 15, 12 and 13 respectively) have a control sensitivity of 18 mV/octave and a 10k/470R attenuating network is placed ahead of these inputs. The time constants of the attack, decay and release curves are determined by $R_x C_x$ times the exponential multiplier, $\exp(-V_c/V_T)$; where R_x is $R31$ plus part of $PR1$; $C_x = C12$; V_c = the control voltage at the appropriate pin; and $V_T = kT/q$. The values of R_x and C_x have been chosen to minimise errors and to retain the very low voltage feedthrough which is a feature of the CEM 3310. With the values used an increasing negative voltage at the 10k/470R attenuator will increase the time constant and a voltage from 0 to about -5V6 will give a range of 2 ms to 20 S for each time control input. To obtain both external and manual control of the time constants an inverting summer with a nominal gain of 0.62 has been placed ahead of the attenuating resistors; in the case of the attack control, using IC2a and associated resistors R6 to R9 ahead of attenuator R10/R11. Thus increasing positive voltages up to +10 V will now give the same control range. R7,8 are for external control voltages while RV2 via R6 provides manual control over the same range. R8 is connected with R14 (release control) and R20 (decay control) such that an external voltage applied to R8 will simultaneously change all three time constants.

Sustain level on the CEM 3310 is determined by the voltage at pin 9 and a voltage from 0 to +5 V will change the sustain level from 0 to 100% of the peak attack voltage. To obtain both manual and external control of sustain and retain the control polarity this input is preceded by IC3a and IC3b configured as two inverting summers with an overall gain of 0.5. Thus 0 to +10 V at R25 will produce the 0 to 100% sustain level control. Manual control is obtained with RV5 and R24. If the sustain voltage were to exceed the peak attack to 100% sustain level control. Manual control is obtained with RV5 and R24. If the sustain voltage were to exceed the peak attack voltage then the envelope will ramp up to this higher voltage level with undesirable results. Pin 3 of the CEM 3310 outputs the peak attack voltage and so the sustain level and pin 3 are connected to IC3c arranged as a precision peak follower to prevent the aforementioned situation.

The output buffer within the CEM 3310 (pin 2) has adequate drive capability for most applications but in this design it may be used to drive several inputs and overloading of the buffer will result in a loss of performance. The internal buffer has been bypassed by IC5a and the output increased to the Project 80 standard of +10 V by a non inverting amplifier, IC5b, which has a gain of two.

The attack output pin (pin 2) provides a voltage of between -0V4 and -1V2 only during the attack phase to provide a visual indication of the attack phase using LED 1. Pin 16 is connected to IC6a arranged as a comparator. IC6b is also a comparator and will turn on LED 2 when a gate voltage is present.

The CEM 3310 requires both gate and trigger pulses to generate an ADSR envelope. The 80-10 module is designed to operate with a gate voltage of +5 V and the trigger is generated by differentiating the gate pulse using C8 and R4 which is then applied to pin 5 via C11 (SW1 closed). To obtain the re-triggering and delay facilities IC1a and IC1b are used to form a monostable. The time delay is determined by the charging time of C9 via RV1 and when the voltage on C9 exceeds the threshold voltage of IC1b its output will go low and reset the monostable. IC1c is used to generate a second trigger pulse whose short duration is determined by the time required to charge up C10, to the threshold voltage level, via R5. With SW1 closed two trigger pulses are therefore generated when RV1 provides sufficient resistance to produce a noticeable delay. With SW1 open only the delayed trigger pulse is presented to pin 5 of IC4, which will allow it to operate in an AD mode.

To operate the CEM 3310 from ± 15 V supplies it is necessary to place a series current limiting resistor on the negative supply line to pin 6. The value of R20 has been chosen to comply with the general equation $R_{EE} = (V_{EE} - 7.2)/0.010$. For the timer a nominal +5 V is derived from the voltage divider formed by R1,2 since power supply to IC1 is not critical. These latter components may be changed to suit other gate voltages.

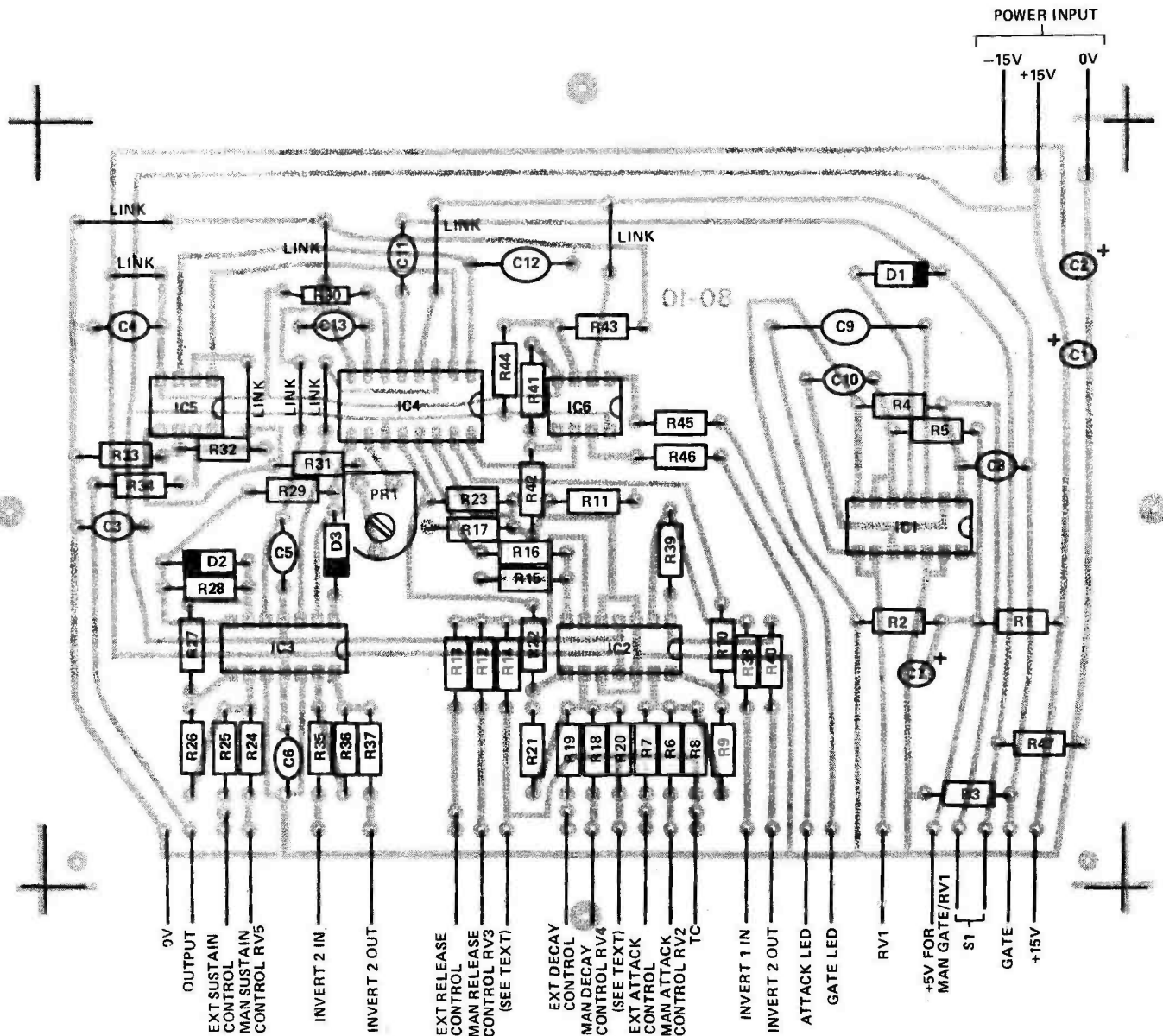


Fig.3. Component overlay

PARTS LIST

Resistors, 1/4w, 5% carbon film unless specified.

R1	10k
R2	5k6
R3	47k
R4,6,12,18,24	150k
R5,7,8,13,14,19,20,25,27, 28,32,33,35,36,38,39, 41,44	100k
R9,15,21	62k
R10,16,22	10k 1% metal film
R11,17,23	470R 1% metal film
R26	51k
R29	24k
R30	750R
R31,43	36k
R34,37,40	1k0
R42	1k3
R45,46	1k2
R47	330k

Potentiometers

PR1	10k carbon
RV1	4M7 logarithmic
RV2,3,4,5,6,7	100k linear

Capacitors

C1,2,7	10u 25 V PCB electrolytic
C3,4,5,6	100n polyester
C8	4n7 polycarbonate
C9	1u0 polyester
C10	47n polyester
C11	3n3 polycarbonate
C12	33n polycarbonate
C13	22n polyester

Semiconductors

IC1	4001B
IC2	LM248N
IC3	TL084CP
IC4	CEM3310
IC5	TL082CP
IC6	LM1458N
D1,2,3	1N4148
LED 1	Red LED
LED 2	Green LED

Miscellaneous

SW1	SPST sub-miniature toggle switch
PCB, case, etc.	

sound alters due to the presence of noise and complex waveforms in the transient. A better simulation of this effect is obtained by using two envelope generators, two sound sources, a dual VCA and mixing the outputs from the latter together. In this example the VCES timer is in the delay mode and will initiate an AD envelope when the trigger occurs. It should be noted that only AD envelopes are practical in the delay mode since if the sustain level is above zero the voltage will ramp up to the set level when the gate pulse is received.

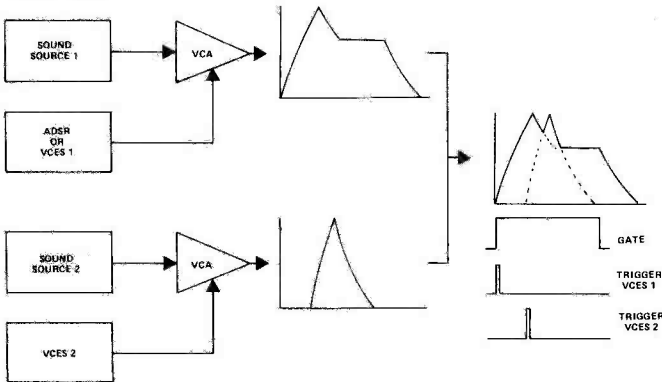


Fig.4. Patch for obtaining realistic transient effects.

Construction

In common with other Project 80 modules the Voltage Controlled Envelope Shaper may be panel mounted or installed in a Teka Alba A23G case. The latter, however, does not have sufficient panel area to neatly accommodate all of the facilities provided. In the cased module illustrated we have omitted the two inverters and controls RV6 and RV7.


The panel markings for the inverters are -, + and A1 (or A2) with the latter being associated with the attenuating potentiometer RV6 (or RV7). Taking Inverter 1 as the example: R35 is wired to the jack socket marked - at the connection which makes contact with the jack plug; the output of the inverter (R37) is wired to the jack socket marked + but to the connection disabled when a jack plug is inserted, whereas the other connection on this socket is wired to RV6; finally the wiper of RV6 is wired to the make connection on the A1 jack socket. This allows a jack plug into the - socket to access the inverter and the output is obtained at A1, with attenuation when required. For non-inverted voltages which require attenuation these are obtained via the + socket with the output at A1.

One external control of attack, decay and release times is commoned and accessed on the PCB at R8. This allows all three time constants to be altered simultaneously and is connected to jack socket marked TC, denoting time constants. If required, however, the constructor may obtain two independent controls for each time constant by cutting the PCB tracks that join up the inputs of R8, R14 and R20. PCB connections are provided at R14 and R20 to cater for this modification.

The module may be manually gated by connecting a push-to-make switch from the +5 V line to the gate input.

Calibration and Testing

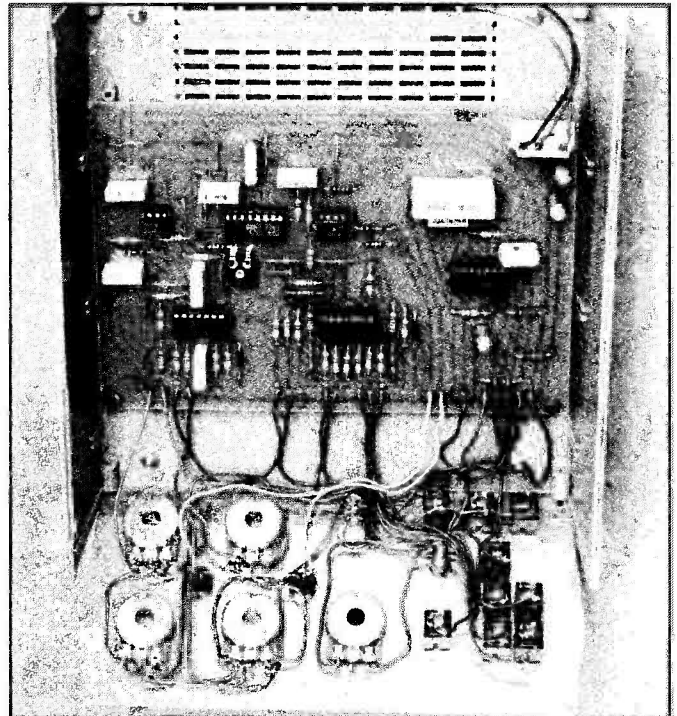The attack, decay and release manual controls are numbered 0-10 for reference purposes since once external voltages are applied a time calibration becomes meaningless.



Tackle the control wiring methodically, otherwise you're in for a case of the wiring jungles.

PR1 allows more than one module to have the same time constants for a given input voltage. For precise calibration a triggered timing device is required but in most instances the following technique is adequate. Set PR1 to mid-position and connect a voltmeter between ground and the junction of R6 and R9. Turn RV2 until a voltage of -5V6 is obtained. Set all other control pots to zero. Gate the module manually and time the attack time as shown by the attack LED being on. The manual push button is held down until the LED goes off. Gate the unit several times to allow all components to stabilise for this long attack time and then commence adjusting PR1 to give an attack time of 20 S.

Note that the gate LED is only on while the manual button is depressed. Next set the attack time for a short duration, switch to re-trigger mode, turn RV1 fully clockwise and manually gate the module and keep push button held down until the test is complete. The attack LED should come on when the button is first depressed and again about 2.5 S later when the unit re-triggers. Keep settings the same but put the switch into delay mode. In this test the attack LED should come on about 2.5 S after manually gating the unit. Finally connect the output to a VCO which is in turn connected to an audio amplifier and set the attack, decay, sustain and release controls to about mid-position. Gate the module and release the push-button when a steady note is obtained. The test is a simple means of checking that the A,D,S and R functions are all operational. The functioning of the inverters may also be checked in the same way by putting the output from the VCES through the inverters without attenuation prior to the VCO. In this test the envelope will be inverted, that is, the frequency starting high, decreasing, holding steady and then finally going high again.

BUYLINES

An 80-10 Voltage Controlled Envelope Shaper module kit (PCB plus components) is available for the inclusive price of £19.20 from Digisound Limited, 13 The Brooklands, Wrea Green, Preston, Lancs. PR4 2NQ.

CALCULATORS

ALL EQUIPMENT FULLY GUARANTEED
so order with confidence and PAY NO MORE

PROGRAMMABLE CALCULATORS



FX 501P 10+2 digit, 128 step, 11 memories	£43.43
FX 502P 10+2 digit, 256 step, 22 memories	£60.83
FA1 Adaptor cassette interface	£17.35
MASTERPACK 150+ programmes on tape with manual	
FX 501P + FA1 + Masterpack	
FX 502P + FA1 + Masterpack	
TEXAS TI51 111 32 step 10 memory	£25.17
TEXAS TI53 Lcd 32 step constant memory	£22.57
TEXAS TI57 50 step 8 memory	£23.44
TEXAS TI58 480 step 60 memory	£58.22
TEXAS TI58C as above with prog retention	£73.87
TEXAS TI59 960 step 100 memory mag card	£150.39
TEXAS PC100C Printer for 58/59C/59	£138.48
TEXAS PC100C IF ORDERED WITH 58/59C/59	£130.39
INCLUDES: - rechargeable battery pack/adaptor/charger	

PROGRAMME LIBRARIES FOR TI58/59C/59

MATHS/UTILITIES, APPLIED STATS, ELECTRICAL ENGINEERING	£22.57
LEISURE	£33.00
SURVEYING, STRUCTURAL ENGINEERING	£54.74
PC 100C PAPER ROLLS, 10 OFF	£19.09
BATTERY PACKS state model or BP number	£6.04

SCIENTIFICS 8 DIGIT Lcd

CASIO FX68	£16.48
CASIO FX81	£11.26
CASIO FX330	£13.87
CASIO FX2600	£18.48
CASIO FX7100	£20.83
SHARP EL503	£11.26
TEXAS TI25 or TI35	£16.48
TEXAS TI50	£19.96

SCIENTIFICS 10 DIGIT Lcd

CASIO FX100	£13.00
CASIO FX510	£16.48
CASIO FX3200	£18.22
CASIO FX5000 10 MEM	£24.30
SHARP EL5806 (8+2)	£15.61
SHARP EL5808 (8+2)	£13.87
SHARP EL5812	£16.48
NATIONAL NS108	£15.61

TEXAS TI42 M.B.A. 32 step 12 memory finance/stats	£35.81
TEXAS TI PROGRAMMER	£43.43
TEXAS TI44 Lcd constant memory statistical	£25.17
TEXAS LITTLE PROFESSOR	£11.26
TEXAS DATAMAN	£17.35
TEXAS SPEAK AND SPELL	£38.22


CLOCK CALCULATORS

CASIO MQ8 micro card watch in leather case	£17.35
CASIO PW81 hourly chime/alarm	£13.00
CASIO ML71 card version of ML81 with 1 alarm	£19.09
CASIO AQ1500 day/date/stopwatch	£13.87
CASIO AQ2200 hourly chime/alarm/calendar/stopwatch	£17.35
CASIO MQ12 card version of above	£17.35
CASIO L50 new 12 pre-programmed tunes	£17.35
TELEPHONE ANSWERING MACHINES twin cassette	£147.78

PRICES EXCLUDE V.A.T. PLEASE ADD 15% POST & PACKING FREE

CALCULATOR SALES & SERVICE

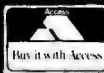Arrow Works, Arrow Road, Redditch B98 8NN
Tel. Redditch (0527) 43169



BUILD YOUR OWN METAL DETECTOR VLF/TR VCO/TR IB/TR BFO...



Shadow VLF/TR. Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nails, bottle caps, even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.

The head is thermally and capacitively shielded. 4 modes: deepseeking VLF plus 3 TR discriminating ranges. Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI.

Complete kit now only £87.67 inc. VAT & post!

Individual parts: Search head £21.33 PCB £6.80 Case £5.33 Adjustable shaft assy. £5.10. LM393 £1.12. Manual (gives more info. than ETI article — and extra function) £1.12. All inc. VAT & post! (Other parts also available separately)

Shadow TR/IB (illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. **Complete kit £33.60 inc. VAT and Post.**

Shadow TR/VCO. An advanced version of the TR/IB. Use as a sensitive 18 machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. **Kit price £38.67 inc. VAT and Post.**

Matching stereo headphones for all Shadow models £5.85 inc. VAT and Post

Beginners BFO model. A very detailed assembly manual and pre-wound coils make this an ideal first project. Simple high efficiency circuit. Full size (not a toy) but weighs only 300gms (10.5ozs) with battery! **FREE STETHOSCOPE HEADSET** with every order. **ALT3 kit: £15.60 inc. VAT and Post.** Padded high Z headphones £5.45 inc. VAT.

Shell Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions £14.45 inc. VAT and Post.

ALTEK

(ETI), 1 Green Lane
Walton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please. Phone (093 22) 44110 anytime!

Freeport A
Birmingham
B19 1BR
ELECTRONICS
021-233-2400

FREEPOST ON ORDERS
VAT INCLUSIVE PRICES
ADD 30p P&P
24 HR PHONE ANSWERING SERVICE

ALL PRICES IN PENCE EXCEPT WHERE OTHERWISE STATED

C-MOS		3.3V/5V		LINEAR										SEMICONDUCTORS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
HEF4001	1	HEF4004	109	HEF4012	127	CA3046	84	95V14	5	BC182L	1	HEF4002	110	HEF4013	128	CA3090E	77	1N4001	5	BC184	2	HEF4003	111	HEF4014	129	CA3100	78	95V15	6	BC185	3	HEF4004	112	HEF4015	130	CA3101	79	1N4002	5	BC186L	4	HEF4005	113	HEF4016	131	CA3102	80	95V16	7	BC187	5	HEF4006	114	HEF4017	132	CA3103	81	1N4003	5	BC188	6	HEF4007	115	HEF4018	133	CA3104	82	95V17	8	BC189	7	HEF4008	116	HEF4019	134	CA3105	83	1N4004	7	BC190	8	HEF4009	117	HEF4020	135	CA3106	84	95V18	9	BC191	9	HEF4010	118	HEF4021	136	CA3107	85	1N4005	7	BC192	10	HEF4011	119	HEF4022	137	CA3108	86	95V19	10	BC193	11	HEF4012	120	HEF4023	138	CA3109	87	1N4006	8	BC194	12	HEF4013	121	HEF4024	139	CA3110	88	95V20	11	BC195	13	HEF4014	122	HEF4025	140	CA3111	89	1N4007	8	BC196	14	HEF4015	123	HEF4026	141	CA3112	90	95V21	12	BC197	15	HEF4016	124	HEF4027	142	CA3113	91	1N4008	9	BC198	16	HEF4017	125	HEF4028	143	CA3114	92	95V22	13	BC199	17	HEF4018	126	HEF4029	144	CA3115	93	1N4009	9	BC200	18	HEF4019	127	HEF4030	145	CA3116	94	95V23	14	BC201	19	HEF4020	128	HEF4031	146	CA3117	95	1N4010	10	BC202	20	HEF4021	129	HEF4032	147	CA3118	96	95V24	15	BC203	21	HEF4022	130	HEF4033	148	CA3119	97	1N4011	10	BC204	22	HEF4023	131	HEF4034	149	CA3120	98	95V25	16	BC205	23	HEF4024	132	HEF4035	150	CA3121	99	1N4012	11	BC206	24	HEF4025	133	HEF4036	151	CA3122	100	95V26	17	BC207	25	HEF4026	134	HEF4037	152	CA3123	101	1N4013	11	BC208	26	HEF4027	135	HEF4038	153	CA3124	102	95V27	18	BC209	27	HEF4028	136	HEF4039	154	CA3125	103	1N4014	12	BC210	28	HEF4029	137	HEF4040	155	CA3126	104	95V28	19	BC211	29	HEF4030	138	HEF4041	156	CA3127	105	1N4015	12	BC212	30	HEF4031	139	HEF4042	157	CA3128	106	95V29	20	BC213	31	HEF4032	140	HEF4043	158	CA3129	107	1N4016	13	BC214	32	HEF4033	141	HEF4044	159	CA3130	108	95V30	21	BC215	33	HEF4034	142	HEF4045	160	CA3131	109	1N4017	13	BC216	34	HEF4035	143	HEF4046	161	CA3132	110	95V31	22	BC217	35	HEF4036	144	HEF4047	162	CA3133	111	1N4018	14	BC218	36	HEF4037	145	HEF4048	163	CA3134	112	95V32	23	BC219	37	HEF4038	146	HEF4049	164	CA3135	113	1N4019	14	BC220	38	HEF4039	147	HEF4050	165	CA3136	114	95V33	24	BC221	39	HEF4040	148	HEF4051	166	CA3137	115	1N4020	15	BC222	40	HEF4041	149	HEF4052	167	CA3138	116	95V34	25	BC223	41	HEF4042	150	HEF4053	168	CA3139	117	1N4021	15	BC224	42	HEF4043	151	HEF4054	169	CA3140	118	95V35	26	BC225	43	HEF4044	152	HEF4055	170	CA3141	119	1N4022	16	BC226	44	HEF4045	153	HEF4056	171	CA3142	120	95V36	27	BC227	45	HEF4046	154	HEF4057	172	CA3143	121	1N4023	16	BC228	46	HEF4047	155	HEF4058	173	CA3144	122	95V37	28	BC229	47	HEF4048	156	HEF4059	174	CA3145	123	1N4024	17	BC230	48	HEF4049	157	HEF4060	175	CA3146	124	95V38	29	BC231	49	HEF4050	158	HEF4061	176	CA3147	125	1N4025	17	BC232	50	HEF4051	159	HEF4062	177	CA3148	126	95V39	30	BC233	51	HEF4052	160	HEF4063	178	CA3149	127	1N4026	18	BC234	52	HEF4053	161	HEF4064	179	CA3150	128	95V40	31	BC235	53	HEF4054	162	HEF4065	180	CA3151	129	1N4027	18	BC236	54	HEF4055	163	HEF4066	181	CA3152	130	95V41	32	BC237	55	HEF4056	164	HEF4067	182	CA3153	131	1N4028	19	BC238	56	HEF4057	165	HEF4068	183	CA3154	132	95V42	33	BC239	57	HEF4058	166	HEF4069	184	CA3155	133	1N4029	19	BC240	58	HEF4059	167	HEF4070	185	CA3156	134	95V43	34	BC241	59	HEF4060	168	HEF4071	186	CA3157	135	1N4030	20	BC242	60	HEF4061	169	HEF4072	187	CA3158	136	95V44	35	BC243	61	HEF4062	170	HEF4073	188	CA3159	137	1N4031	20	BC244	62	HEF4063	171	HEF4074	189	CA3160	138	95V45	36	BC245	63	HEF4064	172	HEF4075	190	CA3161	139	1N4032	21	BC246	64	HEF4065	173	HEF4076	191	CA3162	140	95V46	37	BC247	65	HEF4066	174	HEF4077	192	CA3163	141	1N4033	21	BC248	66	HEF4067	175	HEF4078	193	CA3164	142	95V47	38	BC249	67	HEF4068	176	HEF4079	194	CA3165	143	1N4034	22	BC250	68	HEF4069	177	HEF4080	195	CA3166	144	95V48	39	BC251	69	HEF4070	178	HEF4081	196	CA3167	145	1N4035	22	BC252	70	HEF4071	179	HEF4082	197	CA3168	146	95V49	40	BC253	71	HEF4072	180	HEF4083	198	CA3169	147	1N4036	23	BC254	72	HEF4073	181	HEF4084	199	CA3170	148	95V50	41	BC255	73	HEF4074	182	HEF4085	200	CA3171	149	1N4037	23	BC256	74	HEF4075	183	HEF4086	201	CA3172	150	95V51	42	BC257	75	HEF4076	184	HEF4087	202	CA3173	151	1N4038	24	BC258	76	HEF4077	185	HEF4088	203	CA3174	152	95V52	43	BC259	77	HEF4078	186	HEF4089	204	CA3175	153	1N4039	24	BC260	78	HEF4079	187	HEF4090	205	CA3176	154	95V53	44	BC261	79	HEF4080	188	HEF4091	206	CA3177	155	1N4040	25	BC262	80	HEF4081	189	HEF4092	207	CA3178	156	95V54	45	BC263	81	HEF4082	190	HEF4093	208	CA3179	157	1N4041	25	BC264	82	HEF4083	191	HEF4094	209	CA3180	158	95V55	46	BC265	83	HEF4084	192	HEF4095	210	CA3181	159	1N4042	26	BC266	84	HEF4085	193	HEF4096	211	CA3182	160	95V56	47	BC267	85	HEF4086	194	HEF4097	212	CA3183	161	1N4043	26	BC268	86	HEF4087	195	HEF4098	213	CA3184	162	95V57	48	BC269	87	HEF4088	196	HEF4099	214	CA3185	163	1N4044	27	BC270	88	HEF4089	197	HEF4100	215	CA3186	164	95V58	49	BC271	89	HEF4090	198	HEF4101	216	CA3187	165	1N4045	27	BC272	90	HEF4091	199	HEF4102	217	CA3188	166	95V59	50	BC273	91	HEF4092	200	HEF4103	218	CA3189	167	1N4046	28	BC274	92	HEF4093	201	HEF4104	219	CA3190	168	95V60	51	BC275	93	HEF4094	202	HEF4105	220	CA3191	169	1N4047	28	BC276	94	HEF4095	203	HEF4106	221	CA3192	170	95V61	52	BC277	95	HEF4096	204	HEF4107	222	CA3193	171	1N4048	29	BC278	96	HEF4097	205	HEF4108	223	CA3194	172	95V62	53	BC279	97	HEF4098	206	HEF4109	224	CA3195	173	1N4049	29	BC280	98	HEF4099	207	HEF4110	225	CA3196	174	95V63	54	BC281	99	HEF4100	208	HEF4111	226	CA3197	175	1N4050	30	BC282	100	HEF4101	209	HEF4112	227	CA3198	176	95V64	55	BC283	101	HEF4102	210	HEF4113	228	CA3199	177	95V65	56	BC284	102	HEF4103	211	HEF4114	229	CA3200	178	95V66	57	BC285	103	HEF4104	212	HEF4115	230	CA3201	179	95V67	58	BC286	104	HEF4105	213	HEF4116	231	CA3202	180	95V68	59	BC287	105	HEF4106	214	HEF4117	232	CA3203	181	95V69	60	BC288	106	HEF4107	215	HEF4118	233	CA3204	182	95V70	61	BC289	107	HEF4108	216	HEF4119	234	CA3205	183	95V71	62	BC290	108	HEF4109	217	HEF4120	235	CA3206	184	95V72	63	BC291	109	HEF4110	218	HEF4121	236	CA3207	185	95V73	64	BC292	110	HEF4111	219	HEF4122	237	CA3208	186	95V74	65	BC293	111	HEF4112	220	HEF4123	238	CA3209	187	95V75	66	BC294	112	HEF4113	221	HEF4124	239	CA3210	188	95V76	67	BC295	113	HEF4114	222	HEF4125	240	CA3211	189	95V77	68	BC296	114	HEF4115	223	HEF4126	241	CA3212	190	95V78	69	BC297	115	HEF4116	224	HEF4127	242	CA3213	191	95V79	70	BC298	116	HEF4117	225	HEF4128	243	CA3214	192	95V80	71	BC299	117	HEF4118	226	HEF4129	244	CA3215	193	95V81	72	BC300	118	HEF4119	227	HEF4130	245	CA3216	194	95V82	73	BC301	119	HEF4120	228	HEF4131	246	CA3217	195	95V83	74	BC302	120	HEF4121	229	HEF4132	247	CA3218	196	95V84	75	BC303	121	HEF4122	230	HEF4133	248	CA3219	197	95V85	76	BC304	122	HEF4123	231	HEF4134	249	CA3220	198	95V86	77	BC305	123	HEF4124	232	HEF4135	250	CA3221	199	95V87	78	BC306	124	HEF4125	233	HEF4136	251	CA3222	200	95V88	79	BC307	125	HEF4126	234	HEF4137	252	CA3223	201	95V89	80	BC308	126	HEF4127	235	HEF4138	253	CA3224	202	95V90	81	BC309	127	HEF4128	236	HEF4139	254	CA3225	203	95V91	82	BC310	128	HEF4129	237	HEF4140	255	CA3226	204	95V92	83	BC311	129	HEF4130	238	HEF4141	256	CA3227	205	95V93	84	BC312	130	HEF4131	239	HEF4142	257	CA3228	206	95V94	85	BC313	131	HEF4132	240	HEF4143	258	CA3229	207	95V95	86	BC314	132	HEF4133	241	HEF4144	259	CA3230	208	95V96	87	BC315	133	HEF4134	242	HEF4145	260	CA3231	209	95V97	88	BC316	134	HEF4135	243	HEF4146	261	CA3232	210	95V98	89	BC317	135	HEF4136	244	HEF4147	262	CA3233	211	95V99	90	BC318	136	HEF4137	245	HEF4148	263	CA3234	212	95V100	91	BC319	137	HEF4138	246	HEF4149	264	CA3235	213	95V101	92

RIAA PREAMP

Fit a magnetic cartridge to your stereo system with our economical pre-amp design

Ceramic or crystal cartridges have found wide application in lo to mid-fi stereo systems. Manufacturers like them because they are cheap. As they have a high output level (100mV-2V) no preamp is required enabling a simple and economical system to be readily assembled. Of course, the disadvantage is that the quality of reproduction reflects the cost.

The next step up the hi-fi ladder is the use of a magnetic cartridge. However, you cannot simply plug one in. Magnetic cartridges have a comparatively low output level and their playback response coupled with all the jiggery-pokery that goes into the manufacture of a record results in a very squeaky sound.

Stylish Motion

Ceramic and magnetic cartridges are distinguished by their different responses to the movement of the stylus as it follows the fluctuations of the groove. A ceramic transducer produces an output proportional to the deflection amplitude of the stylus, whereas the output of a magnetic cartridge reflects the rate of change (velocity) of the stylus. Recordings could be made in either a constant velocity or constant amplitude (against frequency) mode. Each has its advantages. In fact a combination of the two is used in an attempt to get the best of both worlds and a standard was set out by the Record Industry Association of America (RIAA — get it?).

Ideal Response

Our graph shows the RIAA playback equalisation curves with the ideal response shown dotted and what you actually get indicated with a solid line. With a 0 dB reference at 1 kHz, it can be seen that the response ranges over nearly +20 dB between 20 Hz and 20 kHz, a scale of 100 to 1. The high gain at low frequencies means that care must be taken to avoid mains hum pick up and screened connecting cables are essential.

Two into One

The preamp and equalisation are neatly combined in one circuit. Our design utilises a single chip from National which features dual amplifiers with an internal resistor matrix. Use of the internal resistors enables an RIAA response to be achieved with just a few components. The unit exhibits a gain of 46 dB (200) at the 0 dB reference frequency of 1 kHz and may be powered from any 10-14V supply. Current consumption is around 16 mA maximum.

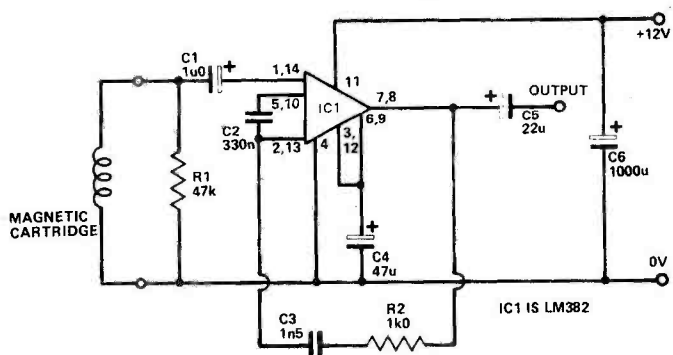
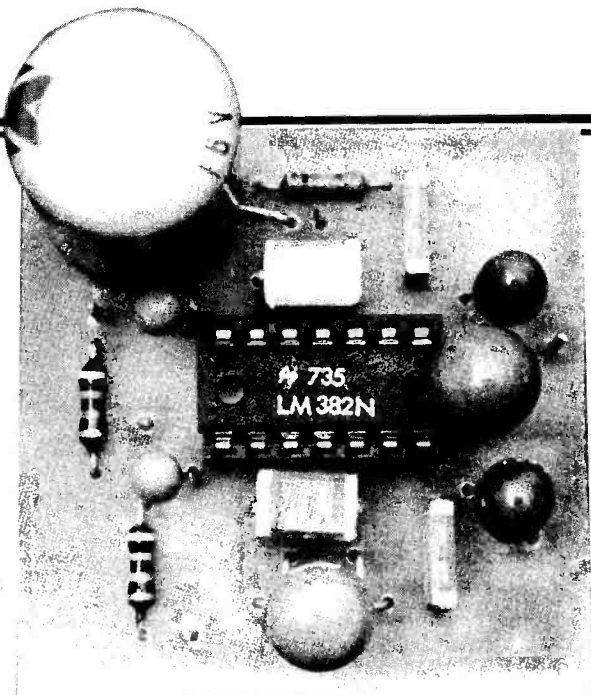


Fig.1. Circuit diagram.

HOW IT WORKS

The desired RIAA frequency response is achieved through the use of a resistor-capacitor network in the feedback loop of an op-amp. Use of an internal resistor matrix in the LM382 chip enables a very simple practical circuit to be used. The circuit is absolutely conventional. A 12 V supply was chosen as the LM382 is characterised for operation in automobiles and its output is biased to 6 V.

The circuit offers a gain of 46 dB (200x) at the RIAA 0 dB reference frequency of 1 kHz. As the output of a typical magnetic cartridge is in the range 2-7 mV, this should result in a preamp output of around 1 V, an ideal level for the 'line' input of most amps. A 47k resistor at the input provides the standard cartridge load and a single 1,000 uF capacitor is used for overall supply decoupling.

Note that the integrated circuit pins are identified for the left and right channels with pairs of numbers on the circuit diagram. Also that all components except IC1 and C6 are duplicated on the component overlay.


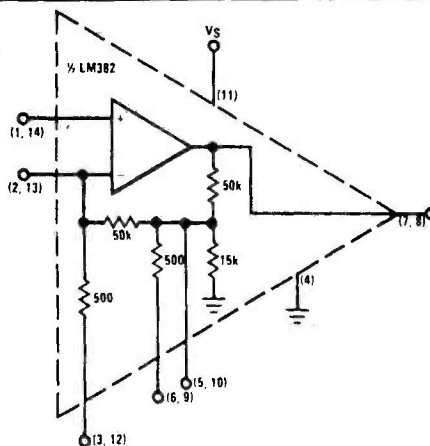


Fig.2. Internal structure of the LM382.

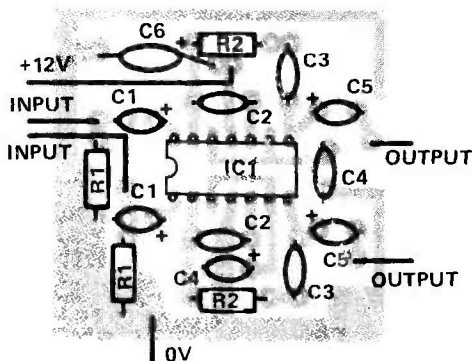

PARTS LIST


Resistors	
R1	47k
R2	1k0
Capacitors	
C1	1u0 tantalum
C2	330n polyester
C3	1n5 polyester
C4	47u tantalum
C5	22u tantalum
C6	1000u electrolytic
Semiconductor	
IC1	LM382

BUYLINES

No problems here. All the components should be readily available from your usual suppliers.

The LM382 can be obtained from Watford Electronics & Delta Tech and Co.

Fig.3.(left) Component overlay.
Fig.4.(below) RIAA playback equalisation curve.

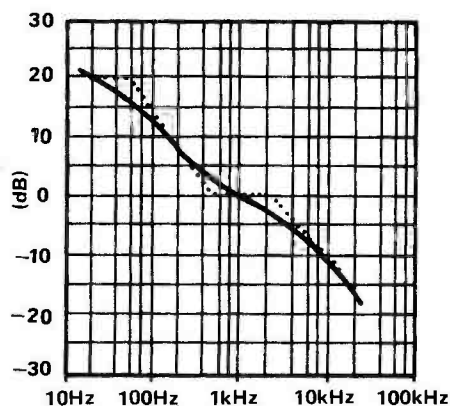

Construction

Use of a printed circuit board is recommended for this project. If you use another method of construction, ensure that connecting leads are kept short and locate the decoupling capacitor close to the supply pins of the integrated circuit. The unit may be assembled into a metal case for good screening. Once assembled, just connect your cartridge to the inputs and connect the outputs to your amp, either directly to the 'line' input or via the passive tone controls if you have them. Then put on your favourite disc and relax and enjoy it.

ETI

CLEF KITS



High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS

Six and 7 1/4 Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design. Build this widely acclaimed professional instrument, for either Domestic or Stage use, from our top quality Component kits.

SIX OCTAVES— £207

7 1/4 OCTAVES— £232

P. E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT— £169

Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits.

P.A.'s — SPEAKERS — CABINETS

Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)

16 Mayfield Road, Bramhall, Cheshire SK7 1JU. 061 439 3297

NEW — ELECTRONIC ROTOR

Two-speed organ rotor simulator plus a three-phase chorus generator on a single PCB (8" x 5"). Kit includes all components — IC sockets throughout — mains operation and stereo headphone driver PCB. Easily integrated with existing organ. Component kit £89.00.

KEYBOARDS

We believe that we have located the best manufacturer of square front Keyboards, as used in our Kits, and can also supply Keyswitch hardware including the industry standard soft plated contact springs.

49 NOTE C-C £23.80

73 NOTE F-F £37.00

88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE

We are specialists in Electronic Piano Manufacture and can build your Piano for you — see lists.

INFORMATION

Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T. carriage & Insurance.

VISITS

Are welcome by appointment, otherwise Mail Order Only.

EXPORT

Enquiries welcome — in Australia please contact JAYCAR (Sydney).

FUEL ECONOMY in kit form



FUELSTRETCHER, the leading UK in-car petrol computer, now available in kit form to save £££££'s from start to finish.

You have a choice from two kits:

FSX20 gives accurate instantaneous digital mpg readings to obtain maximum fuel economy. Standard features include choice of two update frequencies, automatic clear down under idling and owner calibration facility.

FSX10 gives a digital gallons used reading to allow determination of total fuel and average mpg.

Kits are complete with all necessary components and comprehensive instructions. All components guaranteed for 12 months, full technical back-up services available.

ENVIROSYSTEMS LTD., Dept. ETI
Hampfell Road, Grange-over-Sands, Cumbria, LA11 6BE.
Tel: 044 84 4233/4

Name

Address

Phone your order with Access or Barclaycard

	inc. VAT & p&p.	Qty Rqd.	I enclose cheque/
FSX20	£47.50		POs for £
* PI option	£65.90		Cheque No.
FSX10	£34.80		* Petrol Injection