

#### **8K ON BOARD MEMORY!**

5K RAM. 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

#### 2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

#### **GRAPHICS!**

64 character graphics option — includes transistor symbols! Only £18 20 extra!

MEMORY MAPPED
high resolution VDU circuitry using discrete
TTL for extra flexibility. Has its own 2K
memory to give 32 lines for 64 characters.

#### **KANSAS CITY**

low error rate tape interface.

PSI comp 80 **Z80 Based powerful** scientific computer design as published in WIRELESS WORLD



**EFFICIENT OPERATION** 

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

2 MICROPROCESSORS
Z80 the powerful CPU with 15B instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, ', squares, the last exponentials trie functions inverse etc.

cruncher. Functions include +, -, ', squares, roots, logs exponentials, trig functions, inverses etc. Range 10 99 to 9 x 1999 to 8 figures plus 2 exponent

RESIDENT BASIC with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

**1K MONITOR** resident in EPROM

SINGLE BOARD DESIGN Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB

COMPLETÉ KIT **NOW ONLY** £225 + VAT

Cabinet size 19.0"x15.7"x3.3" Television not included in price

The kit for this outstandingly practical design by John Adams published in a series of articles in Wireless World really is complete. Included in the PSICOMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board. 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer. 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.

KIT ALSO AVAILABLE AS SEPARATE PACKS
For those customers who wish by agreed their purchase or hold a persentiated cystims the kill is available as
apparted packs on POS [16" x 12-5"] 643-20. Peir of keybearde 534-80. Firmwere is EPROMS 530-00.
Tervital Insustemer and power supply components E17-60, cabinal party ragged, made from steel, really
beautifully flatished E28-30. P.S. Will greatly sebance only albert single beard computer including OHIO
SUPPREADRAD for which is case to readily medified. Other packs latisful are FREE CATALOGUE.

#### **PSI COMP 80 Memory**

#### **Expansion System**

Expansion up to 32K all inside the computer's own cabinet!

By carefully thought out engineering a mother board with buffers and its own power supply (powered by the computer's transformer) enables up to 3.8K RAM or 8K ROM boards to be fitted neatly inside the computer cabinet. Connections to the mother board from the main board expansion realist is mediative. socket is made via a ribbon cable

Mother board:

Fibre glass double sided plated through hole PCB 8.7" x 3.0" set of all components including all brackets, fixing parts and ribbon cable with socket to connect to expansion plug £39.90

POWERTAL

8K Static RAM hoard Fibre glass double sided plated through hole P C B 5.6" x 4 8" £12.50 Set of components including IC sockets, plug and socket but excluding RAMs £11.20 £114L RAM (16 required) £5.00 Complete set of board. components. 16 RAMS

£89.50

Fibre glass double sided plated through hole PCB 56"x 48" £12.40
Set of components including IC sockets, plug and socket but excluding ROMs £10.70
2708 ROM (8 required) £6.00 ROM board

Complete set of board, components, 8 ROMs £68.50 ETI VOCODER ★ AND THE RESERVE OF THE PERSON OF THE PERSON

COMP 80



Panel size 19.0" x 5.25". Depth 12.2"

14 CHANNELS! **NOISE GENERATOR! LED PPM METERS! SLEW RATE CONTROL!**  2 OSCILLATORS! VOICED/UNVOICED **DETECTOR!** 

#### COMPLETE KIT ONLY £195 + VAT

#### Kit includes FREE foot control and test oscillator!

Like all our kits the ETI VOCODER really is complete — fully finished metal work, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc. — even a 13A plugIKits also available as separate packs — See our Free Catalogue.

# OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SP103NM

(STD 0264) 64455


PRICE SINGUITY: Order with commonage ingespective or any price changes we will honour in this advertisement until February 28th, 1981. If this month's advertisement is mentioned with your order Errors and VATI rate changes excluded. EXPORT ORDERS: No WAT. Postage charged at actual gost plus of handling and

tva i inclusive per sit. SALES COUNTER: If you prefer to collect kit from the factory, callet Seles Counter. Open 9 a.m.-12 noon, 1-4.30 p.m. Monday, Thursday.

U.K. ORDERS. Subjecting 15% surcharge for VAT. No charge is made for carriage.

MANY MORE KITS ON PAGE 8

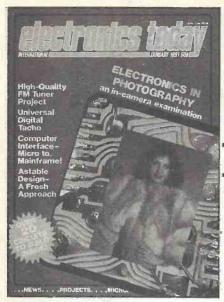SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50



Watch the birdie p.88

# IANUARY 1981 VOL 10 NO

#### **FEATURES**

DIGEST MICROBASICS 17

9 New news is good news Monitoring programs

SPOT DESIGNS

And a couple of other spots 27 Sound seasonal ideas

AUDIOPHILE \*29 I/O INTERFACE

43 Computer talk

**READERS SURVEY** 

ASTROLOGUE 54 Win The Spaceflight Directory 57 Audience participation

DESIGNER'S NOTEBOOK 72 555 astables


88 Watch the LED birdie

SLR ELECTRONICS TECH TIPS

96 Circuits from your very own selves

**ELECTRONICS TOMORROW 102** See-SAW filters

# **PROIECTS**

 

LED TACHO 49 Light up your revs

AUDIOPHILE FM TUNER 62 Spot the tuning POLYSYNTH 77 The makings of a motherboard


FOIL PATTERNS 110 Rub down foils

### **INFORMATION**

NEXT MONTH'S ET! 15 What's in February

BINDERS 19 Issue protection ETIPRINTS 109 Rubbing down PCBs

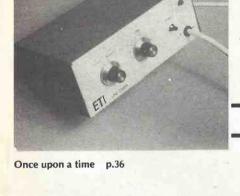COME AND JOIN US 112 Calling all camera operators





Spot the tuning p.62



The hi-fi supermarket p.29

### EDITORIAL AND ADVERTISEMENT OFFICE 145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5

Ron Harris B.Sc. lan Graham B.Sc. Tina Boylan

Paul Wilson-Patterson

Editor Assistant Editor

Paul Edwards Christopher Surgenor Steven Rowe

Roy Perryment I.J. Connell Managing Director

**Editorial Assistant** Group Art Editor Paul Edwards Drawing Office Manager Ray Marston Project Editor

Group Advertisement Manager A directisement Manager Advertisement Representative

OVERSEAS **EDITIONS** and their

AUSTRALIA - Roger Harrison CANADA - Halvor Moorshead

**EDMORS** 

GERMANY - Udo Wittig **HOLLAND** - Anton Kriegsman

ABC

Member of the Audit Bureau of Circulation



PUBLISHED BY DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road, WC2 Argus Press Sales & Distribution Ltd. 12-18 Paul Street, London Gordon & Golen Ltd (Overseas)

PRINTED BY QB Limited, Colchester COVERS PRINTED BY Alabaster Passmore

Electronics Today is normally published on the first Friday in the month preceding cover date. ...... © MODMAGS LTD 1980. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any vanations affecting price or availability whichmay occur after the publication has closed for press. ..... Subscription Rates UK £10 including postage. Airmail and other rates upon application to ETI Subscriptions Service, PO Box 35, Bridge Street, Hemel Hempstead, Herts.

# Why the Sinclair ZX80 is Britain's best-selling

**Built: £99.**95

Including VAT, post and packing, free course in computing, free mains adaptor.

Kit: £79.95

Including VAT, post and packing, free course in computing.

This is the ZX80. A really powerful, full-facility computer, matching or surpassing other personal computers at several times the price. 'Personal Computer World' gave it 5 stars for 'excellent value'. Benchmark tests say it's faster than all previous personal computers.

Programmed in BASIC – the world's most popular language – the ZX80 is suitable for beginners and experts alike. And response from enthusiasts has been tremendous – over 20,000 ZX80s have been sold so far!

#### Powerful ROM and BASIC interpreter

The 4K BASIC ROM offers remarkable programming advantages:


- \* Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. A cursor identifies errors immediately.
- \* Excellent string-handling capabilitytakes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison).
- \* Up to 26 single dimension arrays.
- \* FOR/NEXT loops nested up to 26.
- \* Variable names of any length.
- \* BASIC language also handles full Boolean arithmetic, condition expressions, etc.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- \* Timer under program control.
- \* PEEK and POKE enable entry of machine code instructions.
- \* High-resolution graphics.
- \* Lines of unlimited length.
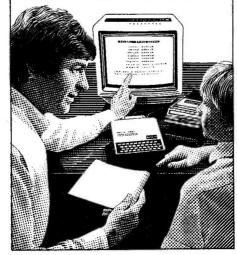
#### Unique RAM

The ZX80's 1K-BYTE RAM is the equivalent of up to 4K BYTES in a conventional computer—typically storing 100 lines of BASIC.

No other personal computer offers this unique combination of high capability and low price.





The ZX80 as a family learning aid. Children of 10 years and upwards are quick to understand the principles of computing—and enjoy their personal computer.

# The Sinclair teach-yourself BASIC manual

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book (free with every ZX80). The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs.

#### Kit or built-it's up to you

In kit form, the ZX80 is pleasantly easy to assemble, using a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9V DC nominal unregulated. If not, see the coupon.

Both kit and built versions come complete with all necessary leads to connect to your TV (colour or black and white) and cassette recorder. Plug in and you're ready to go. (Built versions come with mains adaptor.)

ETI JANUARY 1981

# personal computer.

# Now available for the ZX80... New 16K-BYTE RAM pack



Massive add-on memory. Only £49.95,

The new 16K-BYTE RAM pack is a complete module designed to provide you – and your Sinclair ZX80 – with massive add-on memory. You can use it for those really long and complex programs – or as a personal database. (Yet it can cost as little as half the price of competitive add-on memory for other computers.)

For example, you could write an interactive or 'conversational' program to show people what your ZX80 can do. With 16K-BYTES of RAM, they could be talking to your computer for hours!

Or you can store a mass of data – perhaps in a fairly simple program – such as a name and address list, or a telephone directory.

And by linking a number of separate programs together into one giant, but modular, program, you can achieve the same effect as loading several programs at once.

We're also confident that it won't be long

before you can buy cassette-based software using the full 16K-BYTE RAM. So keep an eye on the personal computer magazines – and brush up your chess perhaps!

The RAM pack simply plugs into the existing expansion port on the rear of the ZX80. No wires, no soldering. It's a matter of seconds and you don't need another power supply. You can only add one RAM pack to your ZX80 – but with 16K-BYTES who could want more!

#### How to order

Demand for the ZX80 exceeds all other personal computers put together! So use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt—and we have no doubt that you will be.

# sinclair zx80

Science of Cambridge Ltd.

6 Kings Parade, Cambridge, Cambs., CB2 1SN. Tel: 0223 311488.

To: Science of Cambridge, FREEPOST 7, Cambridge CB2 1YY.

Remember: all prices shown include VAT, postage and packing. No hidden extras, Please send me:

Qty	Item	Code	Item price	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	02	79.95	
N	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor.	01	99.95	
	Mains Adaptor(s) (600 mA at 9V DC nominal unregulated).	03	8.95	
	16K-BYTE RAM pack(s)	18	49.95	
	Sinclair ZX80 Manual(s). (Manual free with every ZX80 kit or ready-made computer).	06	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense.

TOTAL: £

l enclose a cheque/postal order payable to Science of Cambridge Ltd for  $\pounds$  —Please print

Name: Mr/Mrs/Miss

Address -

FREEPOST - no stamp needed.

ET1/1

10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 23 330n 13p; 470n 17p; 680n 19p; 1 μ 22P; 1 μ 5 30p; 2 μ 2 34p, 27 34p, 27 35v; 0.1 μ 6, 0.22, 0.33, 0.47, 0.68, 1.0 μ, 2.2 μ 6, 33, 4.7, 25V; 10, 20V, 6μ 8, 16V; 2 μ 2 4μ 7, 100 50p, 220 80p; 16V; 2 μ 2 4μ 7, 100 50p, 220 80p; 16V; 2 μ 2 4μ 7, 100 50p, 220 80p; 5K0.2 MΩ Single Gang Log & Lin. 29p 5K0.2 MΩ Single Gang D/P Switch 69p 65 5K0.2 MΩ Single Gang B/P Switch 69p 65 5K0.2	EED. ORDERS SSH/CHEQUE/ EDUCATIONAL PORT INQUIRY SEAS ORDERS  ad otherwise, all d Football Ground. y, Ample Free Car  5p; 63V: 0.47, 1.0, 00. 220, 25p; 470, 00. 220, 25p; 470, 00. 40p; 2200, 45p; 0, 1500, 30p; 2200  110p; 50V: 4700, 1500, 30p; 2200  110p; 50V: 4700, 1500, 30p; 2200  110p; 50V: 4700, 1500, 30p; 2500  1144350n 295  1144450n 296  1144350n 296  1144350n 296  114450n 396  114450n 296  114450n 296  114450n 396  114450n 396  114450n 396  114450n 396  11450n 396  11450n 396  11450n 396  11450n 396  115650 350  115650 350	TRANSI  AC125 35 AC126 25 AC127 25 AC127 25 AC127 25 AC127 25 AC141 30 AC176 28 AC188 30 AC176 28 AC188 70 ACY18 70 ACY20 75 ACY22 60 ACY27 75 ACY22 75 ACY22 75 ACY22 75 ACY22 175 ACY21 75 ACY	BC1821 10 BC1831 10 BC1841 10 BC1861 20 BC186 30 BC187 26 BC212 10 BC2121 10 BC2121 10 BC213 10 BC214 10 BC213 11 BC214 10 BC213 11 BC214 10 BC213 11 BC214 10 BC213 11 BC214 10 BC215 11 BC214 10 BC237 14 BC307 14 BC337 15 BC38 15	BF154 25 BF158 25 BF167 29 BF177 25 BF177 25 BF177 25 BF177 25 BF178 30 BF179 35 BF180 38 BF180 38 BF180 38 BF180 38 BF180 38 BF185 38 BF186 38 BF186 38 BF196 12 BF197 12 BF198 16 BF198 12 BF198 12 BF198 16 BF198 12 BF198 16 BF198 12 BF198 16 BF1	MJE340 54 MJE370 100 MJE371 100 MJE371 100 MJE371 100 MJE371 100 MJE321 95 MJE2255 99 MJE2255 99 MJE2255 90 MJE3055 70 MPF102 66 MPF103 36 MPF105 36 MPF105 36 MPF106 40 MPF106 36 MPF101 36 MPF105 36 MPF101 36 MPF105 36 MPF101 36 MPF105 36 MPF101 36 MPS010 55 MPS010	TIP120 90 TIP121 99 TIP122 99 TIP122 99 TIP141 120 TIP147 120 TIP147 120 TIP147 120 TIP148 45 TIS59 50 TIS44 45 TIS59 50 TIS43 32 TIS46 45 TIS59 50 TIS47 55 TIS91 32 UC734 65 TIS91 32 UC734 65 TIS91 32 UC734 65 TIS91 32 TIX107 11 ZTX108 12 ZTX109 12 ZTX109 12 ZTX109 12 ZTX109 12 ZTX109 12 ZTX109 12 ZTX300 13 ZTX301 15 ZTX301 15 ZTX302 16 ZTX301 15 ZTX302 18 ZTX301 15 ZTX303 19 ZTX301	2N2905A 26 2N2907 26 2N2907 26 2N2907 26 2N2928G 10 2N3011 28 2N3020 45 2N3053 26 2N3054 58 2N3055 48 2N3055 48 2N3055 48 2N3055 10 2N3702 10 2N3702 10 2N3702 10 2N3705 10 2N3706 10 2N37	2N5459 36 2N5485 36 2N5777 45 2N5879 190 2N6027 32 2N6388 150 2S0234 75 3N128 112 3N140 112 40311 60 40313 130 40316 95 40317 60 40320 60 40323 60 40324 100 40324 100 40326 60 40327 70 40348 120 40368 43 40368 43 40369 50 40368 43 40369 70 40408 70 40408 70 40408 70 40408 70 40560
6V: 47 μ. 68, 100 28p; 3V: 100 20p.  MYLAR FILM CAPACITORS 100V: 0,001, 0,002, 0,005, 0,01 μF 69 0,015, 0,02, 0,005, 0,056 μF 7p 0,1 μF, 9p. 50V: 0,47 μF  CERAMIC CAPACITORS 50V Mange: 0,56 ft 0,10,000 μF 0,015 μF, 0,022 μF, 0,033 μF 0,047 μF 5p. 0,1 μF, 0,2 μF 7p 0,047 μF 5p. 0,1 μF, 0,2 μF 7p 3ILVER MICA (Values in pF) 33, 47, 50, 88, 75, 52, 85, 100, 120, 150, 220 11p each 250, 270, 300, 330, 360, 390, 169, 220 120, 100, 120, 150, 220 120, 150, 80, 75, 100, 120, 150, 220 120, 200, 200, 24, 7MΩ Vert.  POLYSTYRENE CAPACITORS: 1000, 120, 150, 150, 470, 600, 800, 820 20  MINIATURE TYPE TRIMMERS 2.56pF, 31 10pF: 10-40pF 2p, 100, 150, 150, 150, 150, 150, 150, 150	522 650 530 1350 531 1350 532 850 545 1450 551 850 592 2572 800 700 910 360 - 821 500 821 500 821 500 821 500 821 1500 825 485 825 485 825 485 825 485 825 485 825 485 825 825 825 825 825 825 826 825 825 827 826	8C1443 30 8C14478 19 8C14478 19 8C14488 19 8C1489 19 8C1489 19 8C153 27 8C1554 27 8C1554 17 8C1558 10 8C1558 10 8C1658 10 8C1670 15 8C1677 15 8C1677 15 8C1677 15 8C1678 10 8C1688 10 8C1688 10 8C1671 11 8C177 15 8C177 11 8C177 11 8C177 11 8C177 11 8C177 12 8C188 10 8C1688 10 8C177 10 8C188 10 8C18	BD1331 48 BD1332 48 BD1333 60 BD135 40 BD136 40 BD137 40 BD137 40 BD138 40 BD140 40 BD144 19 BD145 175 BD1265 110 BD206 110 BD	BPY52 23 BPY53 32 BPY55 32 BPY56 32 BPY64 35 BPY71 20 BFY91 120 BFY91 120 BSX26 34 BSX26 34 BSX28 34 BSX28 34 BSX28 34 BSX28 34 BSY95A 25 BU105 170 BU205 200 BU205 200 BU205 190 BU205 200 BU205 200 B	TIP29A 36 TIP29C 60, TIP29C 60, TIP30C 47 TIP30A 48 TIP30B 50 TIP30C 58 TIP31A 55 TIP31B 48 TIP31C 50 TIP31B 48 TIP31C 50 TIP31B 48 TIP31C 50 TIP31B 48 TIP3	2N1307 65 2N1308 68 2N1613 30 2N1670 150 2N1670 150 2N1670 295 2N2217 45 2N22184 45 2N22204 26 2N22204 26 2N22204 25 2N22204 25 2N22204 25 2N22204 25 2N22369 48 2N23694 50 2N2489 27 2N2489 27 2N24	2N4234 48 2N42264 24 2N42266 15 2N42289 18 2N4314 68 2N44400 18 2N4487 80 2N4889 75 2N4889 75 2N4891 175 2N49921 55 2N49921 55 2N5139 22 2N5139 22 2N5139 28 2N5179 45 2N5180 45 2N5180 45 2N5180 45 2N5180 24 2N5489 38 2N5489 38 2N54	400p 2718-50v 650p 4116 299p IM6402 (UART) 380p MM1702AQ 295p  Telephone orders by Access now accepted (£10 min.) LS76 45 LS78 50 LS83 106 LS85 30 LS85 30
100/200pf   250p   25	K4027.4   350   C     M8116N	A3048	14 MC1494 14 MC1495 13 MC1495 13 MC1495 13 MC1495 13 MC1495 15 MC3302 90 MC3302 15 MC3302 15 MC3307 15 MC3307 15 MC3307 15 MC3307 16 MC3403 16 MC3403 16 MC3403 17 MC3	900 TBA69000 3500 TCA965 992 TDA10040 992 TD	250 7444 10 290 7445 10 290 7445 10 290 7446 13 310 7447 7 575 7448 7 575 7448 7 575 7448 7 320 7451 2 320 7451 2 320 7454 2 320 7454 2 320 7454 2 320 7454 2 320 7454 2 320 7457 3 320 7457 3 321 7457 3 321 7457 3 322 7457 3 323 7457 3 324 7457 3 327 7458 3 328 7458 3 32	6	74185 349 741121 325 74122 325 748S 60 504 73 5138 240 5138 240 5138 240 5138 240 5138 240 5138 240 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5188 210 5287 328 5288 210 5287 328 5472 1150 5247 5150 5472 1150 5475 1250 5472 1150 5475 1250 5475 1250 5475 1250 5476 1250 5	LS90

# WATFORD ELECTRONICS

#### **COMPUTER CORNER**

• SUPERBOARD II Ready-built and tested
Only £150
• PSU 5V/3A (for above incl. RF Modulator) £25
• 610 Expansion Board (8K RAM) expandable to
£150 CHALLANGER 1P (Superboard cased with P)

PExtra 4K RAM (8x2114)
Plastic Case Black, fits UK101 Superbuard, £25 NASCOM lies piece, mo 200 column Hugh Performance Impact Printer. Ideal for PET. NASCOM, UK 101, Superboard, TRSB0 etc. only £325 y VIDEO GENILE based on TRSB0, Utilises 280, 12K level II Basic 15K RAM incl. Cassette Deck STRINGY FLOPPY. Combines economy of Cassette with speed & reliability of DISC (incl. 20 £169 waters)

SOFTY. Intelligent SPROM Programme nects directly to TV. Develop, copy, Burn EP

Ready-built & tested Ready-built or tested
PSU for above (Built)

9 UHF Modulators 6MHz

UHF Modulators 8MHz

9 KEYPADS 4 x 4 matrix

9 Full ASCII coded 56 Key Keyboard Mod. 78 6 £40

\$ 10x C12 Cassettes in Rack £5.50 (P&P is extra on all items) Call in at our shop for Demo. or write in for leaflets.

SWITCHES TOGGLE: 2A, 250V SPST 33 DPST 34 DPDT

4 pole on/off SUB-MIN TOGGLE SP changeover 60p SPST on / off 54p SPDT biased off 105p DPDT 6 tags 75p DPDT centre off 88p DPDT centre off 145p Push to break 20p SLIDE 250V: 1A DPDT 1A DPDT c/over ½A DPDT 4 pole 2-way 4 pole 2-way 24p PUSH BUTTON DPDT Black Body Red, Blue, Grn., Yell. SRL Latching 125p SRM Momentary 125p

MINI. Non Locking Push to Make 15p Push Break 25p DIL SWITCHES (SPST) 4 way 85p; 6 way 95p; 8 way 115p.

ROTARY: Make your own multiway Switch. Adjustable Step Shafting Assembly. Accommodate up to 6
Waters 65p
Mains Switch DPST to fit 45p
Waters 1 pole / 12 way. 2p / 6 able Stop Shafting Assembly. Accommunate of the Wafers of Stammans Switch OPST to fit Break Before Make Wafers 1 pole / 12 way. 2p / 6 way. 3p / 4 way. 4p / 3 way. 6p / 2 way 56p Arman Synacr and Streen FOTARY: (Adjustable Stop) 1 pols / 2 to 12 way. 4p / 2p / 2 to 6 way. 3 pole / 2 to 4 way. 4p / 2b / 2 to 3 way. 4 pole / 2 to 4 way. 4 pole /

'D' CONNECTORS (Cannon type)

Plugs Sockets Covers
ay 95p 128p
ay 135p 195p
ay 198p 284p
ay 290p 398p

**CRYSTALS** 100KHz 455KHz MHz .008M 395 392 323 362 362 323 195 290 323 425 323 200 323 392 28MHz 6MHz 8MHz 8432MHz 4576MHz .2768M .57954M .000MHz 4.000MHz 4.032MHz 4.433619M 5.0MHz 5.185M 5.24288M 6.0MHz 6.0MHz 6.5536M 7.680M 8.0MHz 8.08333M 8.867237M 9.375M 10.0MHz 10.7MHz

95p; 8 way 115p. 3/way

TRANSFORMERS (Malins Prim. 220-240V)
6-0 6V; 9-0.9V; 12-0-12V 100mA 95p
3VA: 0-6 V0 8V (PCB mounting) 12V. 3A
15V. 3A
15V. 3A 15V. 25A 15V. 25A
12V. 3A: 15V. 25A 15V. 25A
12V. 5A 12V. 5A; 15V. 4A 15V. 4A; 20V. 3A
20V. 3A
24VA: 6V. 1.5A 6C.1.5A: 9V. 1.3A 9V. 1.3A; 2V. 1.3A
2V. 1A 12V. 1A; 15V. 8A 15V. 8A
12V. 1A
12V. 1A; 15V. 1A; 15V. 3A
15V. 3A
12V. 1A
12V. 1A; 15V. 3A
15V. 3A
12V. 1A
12V. 1A; 15V. 3A
15V. 3A
12V. 1A
12V. 1A
15V. 1A
12V. 1A
15V. 1A
16V. 1A
1

**VOLTAGE REGULATORS** 

ALUM. BOXES

METERS FSD 60x46x 35mm 0-50μA 0-100μA 0-500μA 0-1mA 0-1mA 0-50mA 0-10mA 0-50mA 0-10mA 0-50mA 0-24 0-25V 0-25V 0-50V AC 0-300V AC 4x4x11/2" 4x234x11/2" 4x51/4x11/4" 4x5½x1½" 100 4x2½x2" 80 5x4x2" 107 6x4x2" 110 7x5x2½" 185 8x6x3" 185 10x7x3" 240 10x4¼x3" 228 10x22" 228 12x5x3" 12x8x3" "VU" 445p each

PANEL

4½x3½x1½" 0-50μΑ 0-100μΑ 0-500μΑ **595p each** 

8.0MHz 392 8.08333M 362 8.867237M 362 9.375M 323 10.0MHz 323 10.7MHz 392 12MHz 392 14.31818M 362 8.432M 323 10.0MHz 323 10.0MHz 323 20.0MHz 323 10.00MHz 323 100.00MHz 323 ETI Projects: Parts available for: Digital Test Meter, DM900, 60W Amplifier System. Send SAE plus 5p

TO3 7805 7812 7815 7818 145p 7818 T0220 7805 7812 7815 7818 7824 Plastic Ca 60p 60p 60p 60p 60p 60p 
 100mA
 7092
 Plastic Casing

 5V
 78L05
 30p
 79L05

 6V
 78L62
 30p
 30p

 8V
 78L82
 30p
 30p

 12V
 78L12
 30p
 79L12

 15V
 78L15
 30p
 79L15
 65p LM300H LM305H LM309K LM317K LM323K LM325N LM326N 170p 140p 135p 350p 550p 240p 240p

18 7 Segment Displays
18 7 Segment Displays
30 Tik307 675
30 Tik312.3" CA 105
40 Tik313.3" CC 105
55 Tik322.5" CC 115
75 DL704.3" CC 99
10 DL707.3" CA 99
225 DL747.6" CA 180
8" Grange CA 250
55 FND357 Red 120
FND357 Red 120
FND357 Red 120
FND358 Green CA 150
85 6" Green CA 255
45 .3" E1 Red CA 150
3" Til Red CA 150
3" Til Red CA 150 segments 15400 OCP71 ORP12 ORP61 2N5777

ISOLATORS TIL111/2 TIL111/ TIL117 95

DVM176 LCD 3½ Digits LCD 4 Digits LCD 6 Digits 350 135 135 135 136 130 LS373 LS374 LS375 LS377 LS378 LS379 4054 4055 4056 4057 4059 4060 4061 4063 4066 4067 4068 4069 4071 4072 4073 120 115 790 750 950 1250 480 850 280 570 1050 850 999 350 350 969 960 1600 4500 71800 3200 8882 900 1300 215 215 4200 3310 3300 3315 1855 1856 665 665 90 LS384 LS385 LS386 LS390 LS393 LS395 4075 4076 4077 4078 4081 4082 4085 4086 4093 4094 4095 4096 4098 4099 4160 4161 4162 4163 4174 350 750 28 105 65 75 48 325 85 98 84 225 220 250 90 415 90 90 LS669 LS670 LS673 LS674 CMOS
4000 14
4000 14
4000 15
4006 86
4007 19
4008 76
4009 40
4010 48
4011 18
4012 24
4013 43
4014 80
4015 82 4041 4042 4043 4044 4045 4046 4047 4048 4049 4050 4051 4052 4053 4510 4511 4512 4513 4514 4515 4516 4517 4518 4519 4002 4006 4007 4008 4009 4010 4011 4012 4013

MUSICA **BUILD THE WORLD FAMOUS** CHROMA-CH

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

\* Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware

★ Texas Instruments TMS 1000 microcomputer

★ Comprehensive kit manual with full circuit details

\* Ready drilled and legended PCB included

Plays 24 well-known tunes including: Star Spangled Banner; William Tell Overture,

Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful. plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time



TMS 1000N

STEP OF MP0027A Micro-computer chip available separately

if required. Full 24 tune spec device fully guaranteed. This angue chip can be used not only for electronic door chimes but for other projects requeng musical couput. Car Horns. Musical Boxes. Alarms.

Amusement Machines. Public Address etc. \$4.95

ALL CHROMATRONICS PRODUCTS SUPPLET WITH MONEY BACK GUARANTEE PLEASE AS ASSAULT AS A PROPUNE FOR THE CONTRACT OF THE CONTRACT O

Please send me TO:CHROMATRONICS, RIVER WAY, HARLOW, ESSEX Telephone: (0279) 418611 

I enclose cheque / PO value £ or debit my ACCESS/BARCLAYCARD account no.

CHROMATRONICS

ETI 1/81

#### **RANSCENDENT 2000** SINGLE BOARD SYNTHESIZER

as a constructional article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid team cabinet, filter sweep The kit includes fully finished metalwork, fully assembled solid team cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal film), and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

COMPLETE KIT ONLY £168.50 + VAT!



Cabinet size 24:6" x 15.7" x 4.8" (rear) 3.4" (front)

# TRANSCENDENT POL

TRANSCANTANT PINYSYATA

SYNTHESIZER

# AS FEATURED IN THIS ISSUE!

#### COMPLETE KIT from £320 + VAT

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready-built equipment costing thousands of pounds. This latest addition to the famous Transcendent family is a 4 octave (transposable over 7 octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes. An add-on unit permits expansion up to 8 voices. Each voice is a complete synthesizer in itself with 2 VCOs, 2 ADSRs, 1VCA and 1 VCF. Being voltage controlled all voices can be adjusted simultaneously by master controls yet their own pitch and gate signals mean each voice can be operated independently from the keyboard.

Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards plug into PCB mounted sockets. The kit includes fully finished metallwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or 0.5% and 0.1% metal film), nuts, bolts, etc. Complete kit with 1 voice £320, 2 voices £368, 4 voices £464, expansion unit to extend to 8 voices £295 (all prices subject to V.A.T.). A mere fraction of what you would have to pay for a ready-built comparable instrument!

# TRANSCENDENT DPX

#### **MULTI-VOICE SYNTHESIZER**

Another superb design by synthesizer expert Tim Orr published in **Electronics Today International** 

PIECHTRAN

COMPLETE KIT ONLY £299 + VAT!



Cabinet size 36.3" × 15.0" × 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or read sound—fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard and brass as so as so the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrator comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus / ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects. As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer

As the system is dosed on organization of organization of organization of the composing etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

Solid took cobinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plugl

#### MANY MORE KITS ON PAGE 115. MORE KITS AND ORDERING INFORMATION ON INSIDE FRONT COVER

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.

# DIGEST


# Hitachi MAGic

Historii have developed an experimental colour video camera combined with a video tape, recorder — provisionally christened the 'MAG Camera'. Using high density recording techniques, the combination is little bigger than an 8 mm cine camera. The cassette, using ¼" tape, is almost as small as an audio cassette and allows two hours of recording/playback. The complete unit weighs only 2.6 kg, including a rechargeable battery pack. Watch this space for news on development of the MAG Camera.

Hitachi have also launched a new portable VHS video recorder. The VT 7000 is one of the lightest in the world — just 5.9 kg. All the controls are of feather touch 'IC logic' operation, with a remote control facility. The recorder can be linked up with the VT TU 70 video tuner, which also doubles as an AC power source/charger for the recorder.

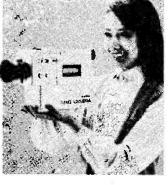If you don't feel like getting up for a bowlful of breakfast telly, you can amuse yourself in bed with Hitachi's new K 2300 portable monochrome set combined with a quartz clock. The set has a 4½" tube and receives both VHF and UHF. Its






four way power source means that the K 2300 can be used virtually anywhere — bedroom (mains/battery), car, caravan, garden or Santa's grotty (sorry) grotto.

(sorry) grotto.
The quartz clock can be used to switch the TV on or off, so you can use it as a snooze switch at night and a telly alarm in the morning. Also featured is an audio output socket, so that sound recordings can be made (naughty).

Now what about the pound notes? The VT 7000 is £579, the VT TU 70 £159 and the K 2300 £115. All prices include VAT.

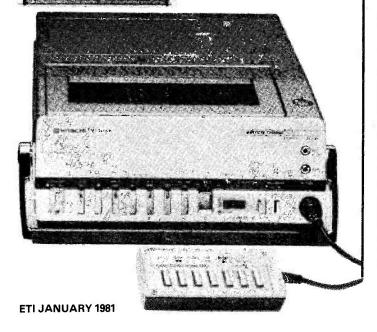Hitachi's new MAG camera (top) combines video camera and recorder. The K2300 portable telly (left) is also an alarm clock. Their new VHS video recorder (below) is one of the lightest portables available.




# Welsh Chip Shop

Within the next year construction work is to begin on the first Inmos large scale production facility in Newport, Gwent. Production of advanced very large scale integrated semiconductor devices for worldwide distribution should begin in 1982. Inmos is a subsidiary of the National Enterprise Board.
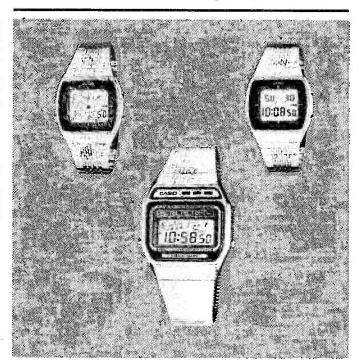
# **Ace Move**

Business must be booming in Bately — Ace Mailtronix Ltd has moved into larger premises at 3a Commercial Street, Batley, West Yorks. WF17 5HJ. The Ace component catalogue, listing approximately 1,000 items, is available for 30p (refundable on orders above £5) to mail order customers. If you're passing through Batley (as one does), call into Ace and collect your copy free.



# Anne O'Log Watches

Poor old Anne O'Log died a death when digital watches took off, but now she's in demand again. Casio's new AA81 is a digital watch with hands — nothing strange in that, you may say. However, the AA81 has no moving parts. It's all done with LCDs.

The display offers a choice of digital hours, minutes and seconds plus day and date (automatic calendar) OR hours and minutes on 'hands' plus digital seconds. There is also a wristful of extra features — stopwatch (to 1/100th of a second), daily alarm with variable tone pitch and count-down alarm/timer up to 60 minutes.

The Casio M12 doesn't have a hand in sight. Its speciality is playing tunes — a different one for every day of the week, if you feel the need. Its repertoire includes 'Happy Birthday',

Wedding Bells' and 'Jingle Bells' for those special days in the year. It will also play the Big Ben chimes every hour.

The digitial display shows hours, minutes, seconds, AM/PM (or 24 hour clock), month, date and day (not all at once, of course). When it's sounding off, a musical stave magically appears on the display as the melody is played. AND the M12 features a countdown alarm/stopwatch function.

The Casio AA81 with chrome case, stainless steel bracelet and 18 month lithium battery costs £34.95. The AA83 (same features with stainless steel case and bracelet) costs £49.95 and the AA81G (gold plated) costs £54.95. The M12 costs £26.95 with resin case and strap or you can buy the same watch packaged in a stainles steel case and bracelet for £34.95 (the M1200). Casio's recommended retail prices are the maximum you can expect to pay, so shop around for bargains.

# PRACTICAL ELECTRONICS PROJECT 125 WATT POWER AMP KIT

Max. Output power Operating voltage (DC) t nads

50-80 Max 4-16 ohms Frequency response Measured at 100 watts 25 Hz-20kHz Sensitivity for 100 watts 400mV @ 47K Typical T.H.D. @ 50 watts 4 ohms load 205 x 90 and 190 x 36 mm

**SPECIFICATIONS** 

125 watt RMS

Dimensions The P.E. power amp kit is a module for high power applications -disco units, guitar amplifiers, public address systems and even high power domestic systems.

The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, the

output stage uses four 115 watt transistors normally only two would be used, result, a high powered rugged unit The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use, supplied with all parts and circuit diagrams.

9.50 plus f 1 00 p&p 125 watt power amp kit

ACCESSORIES AUCESSORIES
Suitable L.S. coupling electrolytic £1.00 plus 20p p&p

Suitable Mains Power Supply Unit **£7.50** plus £2.75 p&p. sufficient for one power amp

**PRACTICAL ÉLECTRONICS OCTOBER ISSUE** 



### DIY STEREO BARGAIN PACKS FEATURING FAMOUS BUILT MULLARD PREAMP MODULES



In easy to build form C.B.s backprinted, etched and drilled ready to use

**BUILD A 12 WATTS PER CHANNEL STEREO AMPLIFIER** ACCESSORIES AND L.S. KIT EXTRA (not available separately)

DIY PACK 1 2 x power amp kits LP1182/ preamp module, suitable for ceramic and auxiliary inputs.

DIV PACK 2 2 x nower amp kits LP1184 preamp module suitable for magnetic ceramic and auxiliary inputs

QIY SPEAKER KIT Two 8" x 5" approx. 4 ohm bass.

£6.00 plus £1.10 p&p

£3.50 plus £1.70 p&p

DIY ACCESSORIES Mains transformer smoothing capacitor rectifier 4 x slider controls, for base, treble and volume

£3.00

ACCESSORIES: Available only at time of purchase of Bargain Packs

# 12 + 12 WATT AMPLIFIER

KIT NOTE: for use with 4 to 8 ohms speakers.

With up-to-the-minute features To complete you just supply screws, connecting wire and solder. Features include din sockets for ceramic cartridge, microphone, tape or tuner Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp nodule, plus 2 power amplifier assembly kits and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kt.

Size 9%" x 8%" x 4" approx. £13.95

for use with 4 to 8 ohms speakers.

**BSR** chassis record deck with manual set down and return, complete with stered . ceramic cartridos

£8,50 plus £2.75 p&p when purchased with amplifier. Available separately £10.50 plus £2.75 p&p 8" SPEAKER KIT. 2 Phillips 8" approx. speakers. £4,75 per

stereo pair plus £1.50 p&p when purchased with amplifier. Available separately £6.75 plus £1.50 p&p

EREO MAGNETIC PRE-AMP CONVERSION KIT all components including P.C.B. to convert your ceramic input on the 12 + 12 amp to magnetic. when purchased with kit featured above. £4.00 separately inc p&p



BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rom spindle adaptor ideally suited for home or disco use.

£12.25 OUR PRICE plus £2.75 p&p



#### PHILLIPS RECORD PLAYER DECK GC037



Hi Fi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acquistic feedback, Complete with 6P401 stereo magnetic cartridge-LIMITED STOCK UNBEATABLE OFFER AT

£27.50 complete plus £2.75 p&p

# OFFER!

SAVE MONEY by purchasing 12 + 12 amp kit, BSR record deck and speaker kit together for only

# **PRACTICAL ELECTRONICS** CAR RADIO KIT

(Constructors pack 7)



- Easy to build \*5 push button tuning
- Modern styling design \* All new unused components
- 6 watt output \*Ready etched & punched P.C.B.
- \* Incorporates suppression circuits

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching retary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia

The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

Complete with instructions.

#### **CONSTRUCTORS PACK 7A**

Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete £1.95 per pack, p&p £1.00 Pack 7A may only be purchased at the same time as Pack 7

NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p. FEATURED PROJECT IN PRACTICAL ELECTRONICS



#### 30 + 30 WATT STEREO AMPLIFIER **BUILT AND TESTED**

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14%" x 10" approx.

READY TO PLAY £32.90 plus g3 30 n&r



#### 323 EDGWARE ROAD, LONDON, W.2 21E HIGH STREET, ACTON W3 6NG ACTON. Mail Order only. No callers.

ALL PRICES INCLUDE VAT AT 15%

All items subject to availability. Price correct at 1.11.80 and subject to change without notice

For further information send for instruction booklet 20p plus stamped addressed envelope

Persons under 16 years not served without parent's authorisation

BARGAIN OFFER!!



#### ARISTON PICK UP

Ariston pick-up arm manufactured in Japan. Complete with headshell Listed price over £30.00

#### **100 WATT** MONO DISCO **AMPLIFIER**

Brushed aluminum, fascia and rotary controls Size approx 14" x 4" x 1014. Five vertical slide controls, master volume, tape leverl, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level

76.00 Output 100 watts RMS 200 watts peak. plus £4.00 p&p

#### **50 WATT MONO DISCO AMPLIFIER**

Size appox 13%" x 5¼" x 6¾", 50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls

fitted with integral push-pull switches. Independent bass and treble controls and master volume

plus £3.20 p&p



Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers goods despatched to mainland and in Jerus and Indiana and in Jerus and Indiana and In



as included FREE with December issue of PRACTICAL ELECTRONICS

It's work-bench size for keeping alongside your favourite journal for instant reference to stock and technical data.



With more to choose from than ever - all the items you have learned to depend on being obtainable from Electrovalue PLUS MANY NEW ONES to bring Catalogue '81 bang up to date. The V.A.T. inclusive price list that goes with it will hold for at least 4 months before the next one is issued.

Yes - you will enjoy dealing with Electrovalue - prices are keen - service is tops.



Write, phone or call if you haven't yet got Catalogue '81 - and you will receive yours by return. (We pay postage).

AND YOU GET BONUS DISCOUNTS AND FREE U.K. POSTAGE TOO, WHEN YOU BUY FROM ELECTROVALUE.

ELECTROVALUE LTD. (Dept. ETI), 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 OHB. Telephone: (STD 0784) (London 87) 33603 Telex: 264475.

	Please send me my FREE COPY OF ELECTROVALUE CATALOGUE '81.
1	Name
1	Address
1	near the state of

# Rapid Electronics

Guaranteed same day D
-----------------------

Quality Product

Wast Stocks

Free Catalogue

Competitive Prices

Pack			Pack		
A10	10 PP3 battery leads	50p	FII	10 BC 108 trans.	90p
A72	10 3.5mm jack plugs	80p	F26	10 2N3704 trans.	80p
A73	10 3.5mm jack sockets	80p	F27	10 2N3819 trans.	190p
A74	10 Std. jack plugs	130p	H11	20 1N4002 diodes	75p
A75	10 Std. jack sockets	170p	H50	20 0A91 diodes	110p
A84	10 5 pin 180 DIN plug	120p	H60	100 1N4148 diodes	180p
A85	10 5 pin 180 sockets	100p	H70	5 C106D thyristors	200p
C20	10 Min. slide switch	130p	J10	20 0.2in, red LEDs	170p
C30	10 Push to make sw.	130p	J15	50 0.2in, red LEDs	400p
C31	10 Push to break sw.	170p	J20	100 0.2in. red LEDs	750p
C40	Pair Ultrasonics	350p	J30	20 0.2in. green LEDs	280p
C32	Submin. SPST toggle	60p	J50	20 0.2in. yellow LEDs	280p
C33	Submin. DPDT toggle	80p	J80	4 FND500 CC displays	350p
C50	20 Texas 8 pin sockets	170p	K5	5 741 op amps.	900
C51	20 Texas 14 pin sockets	200p	K40	1 LM324 op amp.	50p
C52	20 Texas 16 pin sockets		K 20	5 CA3140 op amps.	225p
E10	Resistor kit. 10 ea valu	e IW	K85	5 NE555 timers	110p
LIU	4.7Ω 1M.650 resistors	480p	L8	5 4011 CMOS	130p
E34	10 10u 25V radial elec	50p	L9	4013 CMOS	40p
E37	10 100u 25V radial	75p	Lii	4017 CMOS	75p
E44	10 lu 35V tantalum	100p	L19	4049 CMOS	45p
E54	10 0.1 C280 polyester	50p	M 20	Dalo pen	80p

For quality components at competitive prices by return of post Rapid Electronics must be your first choice!

All prices include VAT. Please add 50p postage and packing Send SAE for our complete catalogue.

Rapid Electronics Limited Hilleroft House, Station Road, Eynsford, Kent

# **DISCO LIGHTING** KITS!!!

First class constructional projects, c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

£9.90 LK3 £15.50

3 channel sound-to-light. 300 w/channel 1v - 100w input

2kW slider dimmer suitable for clubs/pubs A professional unit c/w **FACE PLATE** 

3 channel 3kW £17.90 zero voltage firing 200mV - 100 watts input.

1K4 £16.50

4 channel 4kW

audio - forward/reverse auto - two speed ranges. Suitable case for

LK 1/2/4 £3.50 100w spots ES or BC £1.50. Coloured pigmy lamps 65p.

8m rope lights



Carriage on above 70p

UNREPEATABLE HI-FI BARGAIN 3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

★ 64" linen surround bass unit

★ 5" mid-range unit

★ 3" tweeter

★ 3 way crossover, fixing screws & baffle

★ 20 watts handling capability.

Full instructions provided

Must be heard to be believed!!

£10.50 or 2 kits for £20 Carr. £1 per kit

# SAXON ENTERTAINMENTS (ETI)

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS. (01) 684 8007

Order by phone - Access/Barclaycard/C.O.D. Open Mon. - Sat. 9am - 5pm.

# NEW TUSCAN S100

A Z80 based S100 Computer System.

TUSCAN main board. The heart of the system with Z80, video, Ram, Rom, and I/O plus five S100 slots for expansion.

Professional case will house the complete system\_ Two keyboard options -

Hinged lid for easy access-

Stylish finish ideal for office or home

Available in Kit Form or Assembled.

Houses two 5¼ " drives for a compact business system

NASCOM PRODUCT LIST + VAT I/O board kit less I/O chips 45.00 UART + BAUD rate generator + crystal for I/O

Econographics kit for additional 128 characters (N1 only)

Nascom 19" rack mounting card frame for N1 and N2 for N1 and N2 Nas-DA disassembler 3 EPROM for Nas-sys 37.50 32.50

MK36271 8K BASIC in 8K x 8 ROM Naspen VS in 2 EPROM 30.00

Naspen VS in 2 EPROM
Nas-uvs monitor in 2 EPROM
4 Games Tape
Nasbug T4 2 x EPROM
Tiny Basic 2 x EPROM
Super Tiny Basic 3 x EPROM
Super Tiny Basic upgrade 1 x EPROM
Taps Software 25.00 £8.50 25.00 25.00

ZEAP 2 tape and documentation for NAS-SYS 8K BASIC tape and documentation for N1 15.00

The Henelec controller card plugs direct into a Z80

Pine Henelec controller care plugs direct into a 2-w
P10 and controls up to 3 double-sided mini-floppy
drives giving a maximum 480K system.
 General Purpose FDC control software for
simple DOS or for CPM.
 Simple DOS aftware for NASCOM 1/2 under

OR ROM CB10S for CPM on NASCOM 1/2
 incorporating the major NAS SYS features Maximum 60K CPM system

New Mid prom supplied to 127.7-FM
TWO SYSTEMS

SIM-DOS "Roppy Tape Recorder" with 1 drive PSU firmware, etc.

Double sided £390 plus VAT

CPM System with 1 drive, double sided PSU

£450 plus VAT

THE HENELEC DISK SYSTEM FOR NASCOM and any other Z80 8080 Microcomputer with an uncommitted P10

ISKS

● New MD prom supplied for N2/CPM

firmware, etc.

• Additional Drives with PSU

**MICRO-KIT** na/com-2 COMPUTER WITH IMPROVED 16k B RAM Board POWER SUPPLY £29.50

options available

A range

of firmware

only £335

Full after sales

16K RAM £140

Firmware & MOS ICs Software Zeap Assembler (4, 1Kx8 EPROMS) £50 Nas Pen text editor (2, 1Kx8 EPROMS) £30 Expension boards (in kit form) ● 32K RAM £175.00 48K RAM £210

EPROM CARD (NASCOM compatable) KIT. Suitable for 16 x 2708 or 16 x 2716 or mixed 1 x NASCOM 8k BASIC ROM £55.00. BASIC programmers aid. elf locating tape £14.95.

#### NASCOM-1

NASCOM-1

12" x8" PCB carring 5LSI MOS packages, 16 1K MOS memory packages and 33 TTL packages. There is on-board interface for UHF or unmodulated video and cassette or teletype. The 4K memory block is assigned to the operating system and video display leaving a 1K user RAM. The MPU is the standard 280 which is capable of executing 158 instructions including all 8080 code.

Built price £140 + VAT.



NASCOM

£325 PRINTER

Fully built and housed in a stylish enclosure

. 525 for just £325 plus VAT.
INTERFACES WITH ALL MICRO COMPUTERS

INTERFACES WITH ALL MICHO COMPOTERS

The Nascom IMP (Impact Matrix Printer) features

80 characters per line.

80 characters per line.

80 characters per line.

90 to line print buffer.

Automatic CR/LF.

96 character ASCII set (including upper/lower case, \$, £).

Accepts 8½" paper (tractor/pressure feed. Baud rate from 110 to 9600.

External signal for optional synchronisation of baud rate.

IDEAL FOR WORD PROCESSING

ex-stock

On Demonstration NOW

KITS from

£1481.00

£235 + VAT

Complete Business System 48K. Two 5" drives

All components

available separately.

# COMPUTER SYSTEMS

# "MICRON"

the latest line in superb products on demonstration from vour London stockist EX-STOCK £395.00 inc. VAT BRITISH DESIGN

- 6502 based microcomputer
- VDU alpha numeric display
- . Powerful monitor TANBUG
- **8K RAM**
- 32 parallel I/O lines
- 2 serial I/O lines
- RS 232 C/20mA loop, with 16 programmable Baud rates
- Four 16 Bit counter timers
- **CUTS** cassette recorder interface
- Data bus buffering
- Memory mapping control
- 71 Key ASCII Keyboard, including numeric keypad and with auto repeat
- Including metal cabinets for both
- keyboard and modules
- Including power supply 10K Microsoft BASIC

#### ONLY £29.95 + VAT Add Post £1 50. \$COOP **Professional ASCII Kevboards**



The 'APPLE' Computer Keybo

- 52 key 7 bit ASCII coded Positive strobe + 5V 12V Full ASCII characters

- Full ASCI Indiracties
  Parallel output with strobe
  Power light on control
  National mm 5740 chip. TTL output
  Superbly made. Size 12x5.5x1. Sins.
  Black keys with white ledgens
  Escape, shift, return and reset keys

Complete with circuit and data. Ideal for use with

Complete with circuit and data. Ideal for use with Tangerine, Triton, Tuscan, Apple and most computers, Ex stock from HENRY'S This is definitely the BEST BUY. Supplied Brand New in manufacturer's original jacking (anti-static). Just post remittance total £35.95 (incl. VAT and Post)

#### **CENTRONICS QUICK PRINTER**



OUR PRICE plus VAT

£195

#### **EXCLUSIVE TO HENRY'S** 50% OFF MAKER'S PRICE

List

for:
Software selectable 20, 40 and 80 column using 120mm aluminiumised paper. 1 roll supplied.

NASCOMECentronics parallel data interface for Nascom, Tandy, etc.

240 volt mains input. ASCII character set Paper feed, and on/off select switches

ELL' signel Weight 10lbs Size: 13" x 10;" x 4;". 'BELL' signal

> MONITORS New and Reconditioned FROM £35

Microtan 65 kit Microtan 65 assembled Lower case option Graphics option 20 way keypad Full ASCII keyboard Taney kit

£69 00 79 00 9.48 6.52 Tanex assembled Tanex assembled
Tanex (expanded)kit
Tanex (expanded)assmbld
Serial 1/O option 10.00 49.00 Tanram kit Tanram assembled 44.00 Tanram (expanded)assbld 190.00

106.50 116.50 12.87 ANCER. LONDON STOCKISTS

MPS1 power supply Mini Mother board Mini Rack

10K extended Microsoft in ROM .....£39.00 10K extended Microsoft

in EPROM . . . . . 49.00

SEND FOR COMPLETE COMPUTER BROCHURE FREEPOST TO ADDRESS BELOW

MEMORIES Discounts 10% for 4, 15% for 8, 20% for 16. ADD VAT.

MK 3880 (NZ80) MK 3880-N4 (Z80A) MK 4116 16K x 1 dy RAM MK 4027 4K x 1 dy RAM 2102 1K x 1 static RAM 4118 1K x 8 static RAM

7.50 7.96 4.50 2.25 1.00 12.76

43.00

2708 2716 IM6402 UART 2114 1K x 4 static RAM 8080A

12.50 4.50 2.95 5.25





HENRY'S

Computer Kit Division

404 Edgware Road, London, W2, England I.E.D.

Landon W2, England I.E.D.

Mono Ref.
1400 Transonics 01-402 6822

# ELECTRONICS TOMORROW

SPECTRAL OUTPUT INPUT DATA **Dave Raven of Metac Electronics reports** on the development and applications (FOCAL LENGTH) of Surface Acoustic APERTURE 1 Wave devices. ACOUSTO-OPTIC BRAGG CELL COLLIMATION RF INPUT Fig. 1 An integrated optical spectrum analyser incorporating an acousto-C)COPYRIGHT MODMAGS Ltd optic Bragg cell. MPLIFIE MIXER LOCAL OSCILLATOR

t was at HMS Vernon (the Royal Navy's experimental station at Portsmouth) that wireless staff produced the first "Tuned Shunts" receiving circuit at the beginning of the 1900s. Ever since there has been an increasing demand for higher frequency tuners, filters and delay lines. Surface acoustic wave (SAW) devices have been with us now for over 10 years and are in common use for colour television receivers. They can be incorporated in bandpass filters for radio-frequency receivers, TV intermediate-frequency amplifiers and frequency synthesisers. Others serve as dispersive delay lines in linear frequency-modulated chirp radar, microscan receivers, as tapped delay lines in biphase-coded waveform generators and correlators and as convolvers with memory and programmable matched filters. Most of the applications for SAW devices occur in the high-frequency range. Crystal and LC filters both overlap the bandwidth and frequency range of SAW filters.

However, in the frequency region of 30 to 500 MHz and bandwidth range of 0.1% to 30% only SAW filters simultaneously offer reproducibility, reliability, low cost, selectivity and small size. The techniques used for producing SAW devices are similar to other solid-state devices so that low cost and high repeatability can be achieved. Once the mask has been designed, filters from one production to the next can be easily produced with identical characteristics. On the other hand, LC and discrete crystal filters require laborious tuning procedures.

# **Under The Surface**

Until recently most SAW devices were fabricated on two particular substrate materials, lithium niobate and ST-cut quartz. Lithium niobate can achieve a large coupling coefficient but it has poor temperature stability. Frequency shifts are — 90 parts per million per °C. So it is used mostly for wider fractional bandwidth devices. A reasonable range of bandwidths is from 3% to 50% of centre frequency.

Quartz has a zero temperature coefficient at room temperature, but a low coupling coefficient. Minimum loss filters can be fabricated for bandwidths below 4%. Wide band devices are less desirable in quartz due to the much higher insertion loss. The physical constraints of the size of the substrate rule out filters at low frequency. A filter with a 100 MHz centre frequency, 40 dB side lobes, and a 0.1% bandwidth would require a four inch long substrate.

# Thin Films

When comparing the fabrication of SAW devices to other solid-state devices, it should be pointed out that single crystal piezoelectric materials are not as easily produced in the same manner as, say, silicon slices for microchip production. The surface states of these materials are critical and, to enable cheaper volume production of SAW devices, development work is being carried out to produce thin film piezoelectric material. Research at Nottingham University in the Department of Electrical and Electronic Engineering is being carried out on

producing thin film piezoelectric materials. One such material, zinc oxide, is of particular interest.

In addition to producing SAW devices it is possible to exploit both the optical and piezoelectric properties of zinc oxide. Work at Nottingham on producing thin film material using silicon with a layer of zinc oxide sputtered onto the surface has further shown that high quality device structures can be produced. Suggested applications are integrated optical spectrum analysers, acoustically scanned image devices, convolvers with surface controlling junctions and storage correlators. One other piezoelectric material which showed promise was gallium arsenide. Work has been carried out to produce a tapped delay line and, incorporated on the same slice, a field effect transistor which could be modulated by the surface acoustic wave.

# **Integrated Optics**

The development of electro-optical components is a major new area for thin film technology and during the next 10 years integrated optics will become as familiar as integrated electronic circuitry. Once again it is at the materials stage that most of this work is taking place and it will be largely determined by the fabrication techniques and suitable film structures. It has been known for some time that techniques normally used in the production of electronic devices can also be used to form optical waveguides and components. The waveguiding is based on the creation of a localised region having a higher refractive index than the surrounding medium, leading to modes of propagation in which the light undergoes total reflection at each interface. Here once again, gallium arsenide is a promising material for the development of integrated optics and, as with attempts to combine an acoustic device with an electrical one, gallium arsenide fulfills the vast majority of requirements for optical circuits, in the emission and detection of light as well as modulation and guiding. Further, it should be possible to integrate the optics and electronic circuitry.

# **The Generation Game**

Integrated optics can best be described as a kind of secondgeneration optical fibre telecommunications. The first generation employs multimode fibres and electroluminescent diodes. The evolving field of integrated optics combines singlemode fibres with laser diodes to increase information handling capacity, with control also at the optical level. The basic building blocks for an integrated optical circuit have reached an advanced state of development, where complete circuits are being attempted.

As always in high technology, a major role for integrated optics is seen in electronic warfare. An integrated RF spectrum analyser is used to detect RF pulsed signals from a dense signal spectrum. A leading application of integrated optics is in coherent optical signal processing. One approach to an integrated optical spectrum analyser incorporates most of the techniques discussed throughout the article, a piezoelectric zinc oxide transducer and integrated optics. A radio frequency signal is mixed with a coherent optical-signal carrier in a device known as an acousto-optic Bragg cell. The heterodyned RF signal is converted by a transducer into a surface elastic wave that travels through the Bragg cell. The wave alters the refractive index, producing a grating effect that deflects the optical beam. An array of photo detectors provides individual responses for each frequency—resolution cell.

SAW devices and integrated optics promise some very exciting developments in the next decade and once again it demonstrates how important and closely related the whole subject of physics is to electronics.

# IDEAL FOR XMAS **COMPUTER CHESS** CHESS CHALLENGER "7" (7 Levels of game) SARGOM. The most advanced chess game yet with add on module availability for other games (Our prices lee, File rechargedate bettery pack) Super Bystem 3 (as recommended by ETI) £134.75 CHESS TRAVELLER £527 SENSORY CHALLENGER 8. The latest Chess Computer from America now in stock SENSORY CHALLENGER 'VOICE'. The updated and more sophisticated version of the popular Voice' Challenger P.O.A. \* SPECIAL OFFER TEXAS T159 together with PC100C (Complete as manufacturer's specification £305 TEXAS/HP Accessories available a steps of 100 mem) \*TEXAS T150 (Card prog 950 prog steps of 100 mem) \*TEXAS T150 (Key prog 480 steps of 50 mem) \*TEXAS PC100C (Printing Unit for T158/159) \*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes/50 Prog Steps) T.V. GAMES ES2 PHILIPS console complete with all controls plus game cartrige MOST GAMES CARTRIDGES AVAILABLE P.O.A. MTEXAS TI PROGRAMMER (Hexadecimal Oct) \*\*TEXAS TIST /M (10 mem 32 Prop Steps Stat / Sci) \*\*TEXAS TIST /M (10 mem 32 Prop Steps Stat / Sci) \*\*TEXAS TIST LCD (Sci / Stat / Z Con Meme) \*\*TEXAS TIST LCD (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / Stat / Z Con Meme) \*\*TEXAS TIST (Sci / S Con Meme) \*\*TEXAS TIST (S Con M LEARNING FUN GAMES TEXAS DATAMAN (Number Games-Table learning etc. 5/10 yrs) TEXAS SPELLING B (Spelling Games ideal 5/10 years) TEXAS SPEAK AND SPELL (for older children 8/13 years) LANGUAGE TRANSLATORS £110 £88 Make were of year Texas T181/89 Calculator MATHS //19 Calculator MATHS //19 Calculator MATHS //11117188 MODULE If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines. Module includes \*TEXAS T188 with Maths / Utilities \*TEXAS T188 with Maths / Utilities \*TEXAS T188 with Applied Statistics \*TEXAS T188 with PC100C & Applied Statpucs **CORDLESS TELEPHONES** £120,95 The most up-to-data models from ANSWER PHONES from SINCLAIR/THANDAR METERS All prices in this section include VAT. SC110 £145.25; PFM200 £52.30, PDM36 £32.90; TM362 £55.80, TM35 £112.30, TM356 £86.40, TF200 £186, TG105 £86, 50, TF200 £148.50, TF800 £43 (Prescaler increases PFM200 up to 800MHz), DM235 £55, DM350 £78.50, DM450 £102. WONTER BALE RTEXAS T180 Calculator (complete as manufacturer's spec. master module, charger, etc). PLUS stabilities module and extra set of 40 Blank Prog. Cards with weller, stc. Only £190 #TEXAS TISSC Continuous program facility on sit 480 Program steps/60 mem even when calculator switched off #72.60 #7EXAS TISSC (complete plus Applied Stats, Module) #7EXAS TISSC - PC100C #228.60 eTEXAS T188C (complete plus Applied Stats, Module) eTEXAS T188C + PC100C #14P33E (8 mem. Pro Sci / Sta) ... #14P33C (as above but con. mem) #14P33E (Advanced Sci with Statis £80.50 £83.00 £173.00 £384.35 £167.43 #HP34C (Sci Prog 20 Mem) #HP97A (K Prog 224 Steps 26 Mem) #HP97A (Fully prog with Printer) #HP91C (the prog with Printer) HP91C Card Reader/Printer etc. Modules IDEAL FOR STUDENTS

TEXAS T120 (Jun Sci + Con TEXAS T135 (Sci/Stat C Men

GOODS FULLY GUARANTEED PRICES EXCLUDE VAT (ADD 15%)

Company / Hospital and Government orders accepted by phone

TEL. 01-455 9823

MOUNTAINDENE

22 Cowper St., London, EC2

elcome. Air Freight/Air Post Delivery. Quotations on request

£13.00 £17.00

# THE REMOTE CONTROL



STORY

ONCE UPON A TIME



if you wanted to control any equipment remotely you had to buy a dozen logic ICs, chase around the shops for crystals and expensive ultrasonic transducers and then spend a few deays getting the unit to work. Then one day TX began stocking a new system. You seguind was one IC, a couple of translatiors, resistors and a keyboard for her transmitter and a couply ICS who were capacitors for the receiver, to give you up to 16 on /off (digital) outputs of 10 and 10 to 10 and 10 a

LD271 IR Emitting Diode	.36	ML926 16-channel receiver 4	
SFH205 Photodiode Detector	.95	momentary binary outputs	1.40
SL480 IC Pulse Amp.	1.70	ML928 16-channel receiver, 4	1.40
SL490 32 Command Encoder /		latched binary outputs	1.40
transmitter	2,40	ML929 16-channel receiver, 4	
ML922 10-channel receiver		latched binary outputs	1.40
± 3 analogue outputs	4.20		

DEST/ ML925. A decoder designed for model/toy control, providing a 2-speed drive moto: and three position latched steering system or a vabicle with momentary action steering and a third motor, eg. gun turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc.

2.10

To make things EVEN EASIER, we have designed several new kits.—

MK6 — Simple Infre Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 90 battery.

MK7 — Infre Red RECEIVER, Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240Vac, but can be modified for use with 5 to 15V dc supplies and transistor or

switch loads up to SUUW at 240Vac, but can be modified for us with a to 159 to supplies and info supplies.

Special Price\* MK6 and MK7 together. Order as RC500K

Special Price\* MK6 and MK7 together. Order as RC500K

MK8 — Coded infra Red TRANSMITTER, Based on the SL490, the kit includes 2 IR LEDs, measures only B321.3 cms and requires a SV (PF3) battery.

MK3 — 4 Way KCYB0ARD. For use with the MK8 kit, to make a 4-channel remote control transmitter.

MK10 — 15 Way KCYB0ARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML926 or Min 926 receiver (MK12) kit.

MISJ26 of MISJ28 receiver (MI L) Rt.

MK12 — 16 Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or of remotely. Outputs may be lacked or momentary, depending on whether the MISZ6 or MISS8 is specified. Includes its own mains supply. 11.98

Now you can buy all the components you require for your infra red system or complete kits from one supplier, at unbestable prices, and live happily



#### CT4000 CLOCK/APPLIANCE TIMER KIT

The CT4000 has been designed to preset the state (on or off) of four outnots at four times per day for up to 7 days in advance lenabling the unit to control tape recorders, appliances, central heating, lights, let. The times are so to a 0.1" high red LED display by means of a krybbard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V for mains loads use our Solid State Helay Kit (MKZ). The kit includes a PCB, keyswitches, LC 4 digit LED display, transformer, plus all other components and a sprean printed and drilled box which can also accommodate up to 4 des a PUD, neyson s s all other components and a can also accommodate up to 4 Size 10 - 12 - 4.5 cms Colour, Black. spread LED display, transformer, spread printed and drilled box which can Solid State Relay Kits. £25.25



#### 24HR, CLOCK/APP, TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day Kit contains AY 5-1230 IC, 0.5° LED display, mains supply, display drivers, switches, LEDs, trac, PCBs, & full instructions.

CT1000K Basic Kit

£14.90

£22.50

CT1000KB with white box (56/131 × 71mm) £17.40

### LIGHTING CONTROL KITS

Directly replace conventional light switch and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.

10 300K 100UCHDIMMER. Single touchplate with alternare action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp, helps find the switch in the dark.

TDE/K Extension kit for T0300K for 2-way switching, etc. 200


TSA300K TIME DELAY TOUCHSWITCH Turns off after preset delay (2 secs., to 3 1/2 min

£4.30 £3.20 1.D3DOK Conventional Lightdimmer
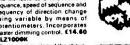
#### **DISCO LIGHTING KITS**

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto solated audio input. DL 1000X

DL 1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates meater dimming control. £14.60 DL21000K



D12100eX
A lower cost version of the above, festuring undirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum.



#### DIGITAL VOLTMETER/ THERMOMETER KIT



Based on the ICL 7106 This kit contains a PCB, resistors, presert, appactors diodes, L and 0.5" figure drapt display Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode at the sensor. Requires a 3ma A 9V supply (PP3 battery)

# MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kit include PCB, short instructions and all com-

ponents.
MK1 TEMPERATURE CONTROLLER/

THERMOSTAT
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater 1KW £4.

MK2 SOLID STATE RELAY
Ideal for switching motors, lights heaters etc.
from logic. Opto-isolated with zero voltage
switching. Supplied without triac. Select the
required triac from our range.

E2.60
MKS BAR/ DOT DISPLAY

MKS BARZ DOT DISPLAY

Osplays an analogue voltage on a linear 10element LEO display as abar or single dot Ideal for
thermometers. level indicators etc. May be
stacked to obtain 20 to 100 element displays.
Requires 5.20V supply. £4.75

MKA PROPORTIONAL TEMPERATURE
CONTROLLER
Based on the TDA1024 Zero voltage switch this
kit may be wired to form a burst five power
controller or a proportional temperature
controller or a proportional temperature
controller enabling the temperature of an enclosure to be maintained to within 0.5 C.

MKS MAINS TIMER

MK5 MAINS TIMER
Based on the ZN 1034E Timer IC this kit will switch
a mains load on (or off) for a preset time from 20
minutes to 35 hours. Longer or shurrer periods
may be realised by minor component changes
Maximum load it.W. £4.50

#### **TRIACS**



400	V Plastic	Case (T	ex <b>as</b> )
3A	49p	16A	95p
8A	58p		
12A	85p		
6A wil	h trigger		80p
8A iso	lated tab		65p
Diac			18p

#### AND NOW A DIMMER THAT MAKES TOUCH DIMMERS OBSOLETE

Two years ago TK Electronics launched a touchdimmer kit, the T0300K, which made knob controlled dimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW. TK have designed a touch dimmer kit with an Infra

a touch dimmer kit with an Infra
Red Remote control enabling you to
switch and control the brightness
of your lights from the comflight
of your armchair etc. (as well as manually by touching the frontplate
or by using the TDE /K extension kii)
As with all our kits, these come complete with all components
including REI suppression, frontplate, a neon to help you find the switch
in the dark and a neat box for the transmiter. The plastic toughtale has
no metal pads to touch ensuring complete safety and enabling the plate to
be covered with a decorative finish to
blend with your from decor.

8 17

We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.

in two years time in two years time everyone will be selling te to remote control dimmers but you can have your TDR300K kit NOW for only £14.30 for the dimmer unit and £4.20 with transmitter.

£14.30 for the dimmer unit and £4.20 for the transmitter.

For the more athletic of you the T0300K is still available at £6.50 and the T0E/K at £2.00 DON'T FORGET to add 40p P&P and 15% VAT to your total purchase

#### INTEGRATED CIRCUITS

555 Timer	21p
741 Op Amp	19p
AY-5-1224 Clock	€2.60
k/Timer	£4.50
ometer	€8.20
D drive)	£7.00
	£1.45
	£3.50
Amp	80p
noise Preamp	€1.00
	75p
	£1.50
	£1.40
rter (1.4 pin)	£1.60
ner / Oscillator	60p
neter	£1.20
	€2.10
	€8.50
ment-BCO converter	96p
it counter with 7 seq of	/p £4.50
ner	£2.50
h 16-way	€4.85
	€2.52
	68p
	£1.00
	€1,20
	£2.85
	£1.80
ih data sheets	
	741 Dp Amp AV-5-1224 Clock k/Timer Dutrive) Dutrive) Amp Amp Dose Preamp w voltage Amp et Oetector riter (14 pm) ret / Oxfoliator leter (14 pm)

#### MINI TRANSFORMERS

**LEDs** 

Standard mains primaries 240V a.c. 100mA secondaries 6-0-6V

#### DISPLAYS



DL304 Red 0.3" c.c. pin compatible with DL704 DL307 Red 0.3" c.a. pin compatible with DL707 75p DL727 Dual 0.5" c.a. Red £1.50

# **CMOS**

19p
199
18p
26p
20p
54p
24p
90p
€1.80
£1.80

#### D.I.L. I.C. SOCKETS

8 pin 14 pin	8p	18 pin 28 pin	17p 24p 36p
16 pin Soldercon Pins	14p	40 pm	50p/100

CAPACITORS

6p 6p 7p 7p 7p 7p 12p

5p 5p 6p 7p 12p 8p 10p 14p 15p 24p 34p

16V

10V

Polyester 250V

Tantalum (bead) 35V 0.1 0.1 0.22 0.47

10

0.002 0.033 0.047 0.068

0.1

63V

25V

25V

#### BOXES

Moulded in high impact ABS. Supplied with lids and screws, Black.

82 95 x 71 x 35mm
83 115 x 95 x 37mm
95n



RESISTORS

#### ZENER DIODES

400mW3 3V-30V 1 3W 7 5 27V

1/4W 10ohm-10M E12 Pack of 10 (one value) 10p 10 Packs (10 values) 80p

#### **VOLTAGE REGULATORS**



Available in 5V, 12V & 15V 78L series 100mA pos 79L series 100mA neg. 78 series 1A pos. £1.80

#### RECTIFIERS

1N4001 IA/50V	4p
1N4004 1A/400V	6p
1N5401 3A/50V	8p
1N5404 3A/400V	10p
1A 50V Bridge	19p
1A 400V Bridge	22p
3A 50V Bridge	48p
3A 400V Bridge	58p
(Bridge rectifiers are miniature PCB me	ounting types)

#### VMOS POWER FETS

VN10KM 0.5A/60V (TO92) VN66AF 2A/60V (TO220) 52p 88p

#### **TRANSISTORS**

BC108	Bp	BFY50	20p
BC182	8p	TIP31A	40p
BC182L	8p	TIP32A	40p
BC212	9p	2N3055	45p
BC212L	9p	2N3442	90p
BC337	18p	2N3819	20p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER — CALLERS WELCOME BY APPOINTMENT



TK Electronics (ETI), 11 BOSTON ROAD LONDON W7 3SJ. 01-579 9794

10 R 22 R 33 R 47 R 100 R 220 R 1000 R 47 A 100 A 220 A

33 10V 6.3V

100 3V

1.000pF 2.200pF 4.700pF 10.000pF

5p 5p 6p 8p 11p 14p 20p 8p 8p 12p




# 8 Watt Audio Amplifier


Using a modern audio power amplifier IC, it is easy to produce an amplifier giving several watts of output with quite good quality. This amplifier is based on the TDA2006 and gives about 8 W RMS into an 8R speaker, or 12 W when using a 4R load. At most output powers the distortion is typically only a fraction of one percent, but it does rise significantly at higher output levels.

The TDA 2006 is in many ways like an operational amplifier, but it has a class B power output stage. In this circuit it is used in the inverting amplifier mode with R1 and R2 forming a potential divider that biases the non-inverting input to half the supply voltage. C1 filters out hum and noise which might otherwise be coupled from the supply lines to the non-inverting input via the bias circuit. The inverting input is biased by R4 and together with R3 this resistor forms a negative feedback circuit, which sets the voltage gain and input impedance of the amplifier. As would be the case with an operational amplifier, the voltage gain is equal to R4 divided by R3 and the input impedance is equal to R3. With the values shown this gives a voltage gain of 27 times and an input impedance of 100k. However, within reason these figures can be modified by changing the values of R3 and R4. RV1 is the volume control and does of course shunt the input impedance of the circuit as a whole (down to as little as 50k with the specified values).

As the TDA2006 has a supply ripple rejection ratio of 50 dB, it is not essential to use a very well smoothed supply, but it is important that the device's 30 V maximum supply voltage rating is not exceeded. The maximum average supply current is a little over 500 mA when using an 8R speaker and about 800 mA when using a 4R load. The TDA2006 should be mounted on a substantial heatsink, but has thermal shutdown circuitry, which protects it against overheating. It also incorporates output current limiting circuitry.

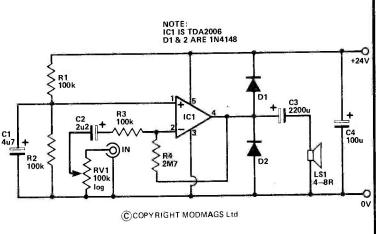


# The facts of the case

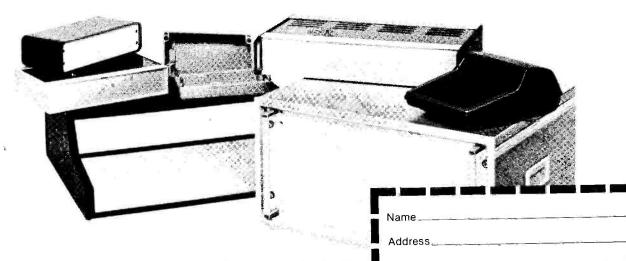

West Hyde have one aim in life, to provide a practical solution to the problem of electronic packaging. The fact of the matter is that we have an ideal case for almost every project featured in this magazine. In this advertisement it is impossible to show you our whole range of nearly 1,000 different instrument cases, or our extensive collection of tools and accessories. Please complete the coupon and, in turn, we will send you our free 80-page catalogue and price list.

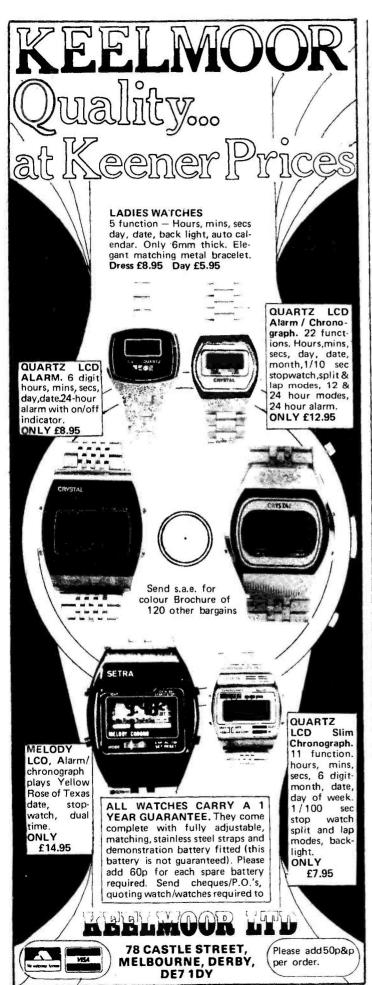**WEST HYDE** 

West Hyde Developments Limited, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks., HP20: 1ET Telephone: Aylesbury (0296) 20441/5



# 3 CHANNEL SOUND/LIGHT

LB31000SLC

£32.70



#### 3 CHANNEL SOUND/LIGHT



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.


#### 2/4/8 CHANNEL CHASER



£28.00

An all logic chaser system for use with up to 8 channels at 1,000 wats each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

#### **4 CHANNEL SEQUENCER**

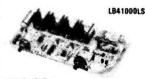

£19.20

A 4 channel sequence generator for banks of lamps up to 1 000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

#### 1 AND 3 CHANNEL OIMMERS

1831000LD 1831000LD £16.20 Single channel version

LB11000LD £7.20

Power dimmer units for theatre/stage applications up to 1,000W per channel with on board suppressing. The unit is also available without rotary pots for use with sliders —

LB31000LØ (no pots) £15.00 Sliders 75p each.

#### ROPE LIGHTS/DRIVER LB41000LC-S £24.20



24 feet ropes Red/Yellow Blue/Green

ROPE LIGHTS £45.40

A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound-light effect. The unit will control up to 10 ropes with chase speed and trigger level control.

# Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months

months
All prices shown are VAT inclusive. Please include
50p post/packing except where individually
stated. To mail order, send cheque/P.O./
registered cash or Access number. C.O.D. service
£1 extra. For the new Autumn catalogue send 50p
(Full spec. shown).

# STEREO DISCO MIXER/PREAMP

£33.70

Magnetic or ceramic deck

All the requirements of a stereo disco preamp on one board. Lett and right deck mixerations controls/mic. mixer/tones/mic. auto fade over deck/and P.F.L. The unit can be used with either LB\$00/150/250

Full set of pots — £8.63

#### LPBA2 £17.20

A four channel mixe and tone stage for mics guitars, etc. Can be used with any LB amps. Set of pots £2.74. £19.50

A stereo hi-fi preamp and tone stage for mag, p.u./tape/tuner, etc. Set of pots £3.27.

#### 3-WAY ACTIVE CROSSOVER



Bass/mid/treble active crossover with stage boaster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1 (1 or 2).

#### **POWER AMPLIFIERS**

Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to

26W R.M.S. 100W R.M.S.| 150W R.M.S.| 250W R.M.S. 20Hz to 60K 0.07% THD 96DB S/N LB25 5Hz to 25K 0.1% THD 0.1% THO 110DB S/N 110DB S/N LB100 LB15D 5Hz to 25K 0.1% THD 1100B S/N LB250

£11.20 £19.70 £29.20 £43.50

Note all models are available with aither 500mV or 775mV sensitivity. Please state when ordering.



LBRLD1 £6.20

A de-thump unit for use with any LB power amps.

#### **POWER SUPPLIES**

182593 L8100P8 L8166P8 £11.20 £16.20 £19.00 P/P £1.40 P/P £1.40 P/P £1.40 P/P £1.20



#### **CELESTION LOUDSPEAKERS** (B ohms)

G12-85 G12 inch 85W) G12 inch 100W) G10 inch 50W) G12 inch 100W) G10 inch 50W) G10 inc

#### **NEW - MINI MODULES - NEW**

NEW — WIRT WUDULGS— NEW Ingeniously designed mini pre-amplifier building blocks for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct not your pain. LBMM 1723-45.
LBMM3 Pre-amp for mics, guilters etc.
LBMM4 Pre-amp for mics, guilters etc.
LBMM3 Bass/hoost/cut for either LBMM1/2/3/4/5.
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5.
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5.

LBPSU1 ± 15V supply for up to 12 modules LBPSU ± 15V regulated for up to 50 modules MM1 £4.60; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £5.70; PSU1 £7.20; RPSU £14.50.

Mini Module Discount, Any types between 10 and 24 (quantity) -- 20% 25 + -- 30%.



🗉 L & B

**ELECTRONIC MODULES** PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon, Surrey CRO 3EB. Tel. 01-689 4138

# THE ZX80 COMPANION

#### Second Edition—THE MONITOR REVEALED

This best-selling Sinclair ZX80 manual has now been extended to include a detailed explanation of the monitor, routines and entry points. Send £10 cheque / P.O. to:

#### LINSAC 68 Barker Road, Middlesbrough Cleveland TS5 5ES

Send s.a.e. for latest catalogue of ZX80 programs - games, educational and utilities - in lower-priced packages.

Also available: ZX80 Monitor Listing

# TV SOUND TUNER **ETI SEP 80 PROJECT**

All parts available / send for list

ALSO

No. 1 for Teletext Kits TV Spare Parts and Components

Callers welcome at Shop Premises

# MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD TELEPHONE: 01-794 8751

Near West Hampstead Jubilee & British Rail Stations

Mass full a

\*\*\*\*\*\*\*\*\*\* SPECIAL OFFER

LED ALARM CLOCK MODULE with bright 0.7" LED display and s output. Just add mains transformer and time setting switches for operation special price of £4.99 whilst stocks last, With data sheet. Cat. No. 205. rational clock. At the

\*\*\*\*\*\*\*\*\*\*

SOUND EFFECTS MODULE Brand new, designed for 'Spaceman' toy, itsess 5 audio / visual programs. Requires 80 nm spaker (not supplied), 88p. Cat. No. 108.

SIMULATED LASER CANNON for spaceman toy. LEO on moulded 6" lead with mini jack plug. Fits socket on Sound Effects Module Only 20p each of Supplied on Supplied College 10 and 10 a

CONTROL OF STATE OF S

each. DIODES 1N3470, 4p each or 25 for 50p. 1N4003, 5p each. 1N4148, 3p each. 1N4151, 5p

each or 10 for 35p.; Pageschot 25 for abp. HAVO3, 5p each TNA143, 5p each TNA151, 5p.
CALCULATOR CONTROL OF A 10 for and constant. Not compatible with our calc. kybts, With data and calculator circuit, 30p, Cat. No. 408
MIGHT ORANGE DISPLAY 3 digit, 7 segment gas discharge display. 0.25" high digits. With data, only 35p each. Cat. No. 310.

Untested Items

FLUORESCENT CALCULATORS Manufacturers rejects. Most repairable but no guarantees.
10 function with full memory. With 'repairing calculator' into £2,50. Cat. No. 107.

LED DISPLAYS (untested — no guarantees) 10 seven segment LED displays. 0.127" digits. common cathode. 10 for \$9p. Cat. No. 311.

POST AND PACKING PLEASE ADD 40p (OVERSEAS ORDERS ADD £1)


LOTS MORE GOODIES IN OUR CATALOGUE, SEND MEDIUM SIZED SAE FOR YOUR FREE COPY

SATISFACTION GUARANTEED ON ALL ITEMS OR FULL CASH REFUNDED

VAT PLEASE ADD 15% TO THE TOTAL COST OF YOUR ORDER (INCLUDING POST AND PACKING).
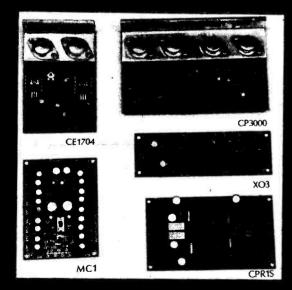
# the Professionals

Crimson modular audio amplifiers feature: \*Low values of transient and steadystate distortions \*Envelope distortion (below 500 Hz) less than 0.05% \*con-board electronic protection \*P.C.B. pin and edge connector termination \*Full range of complimentary components, i.e. P.S.U.'s, heatsinks etc. available from Crimson.



The Crimson range of amplifier modules are built to very high standards and have earned an enviable reputation in every field to which they have been applied. The boards come ready built and tested (guaranteed for two years) and can be used to advantage where high quality signal amplification is required. The power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge mode. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are catered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is basically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also onboard is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and gives the required boost for low output moving coil type cartridges. External components required are potentiometers for volume and balance, switches for signal routing and a regulated ±15V D.C. power source (REG1). Complimenting this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

Numerous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Power amplifier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review, August 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietory flight cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in Wireless World October/November 1980. Further details of how to use the modules are contained in the Users/Application Manual available at £0.50.

SP	ECIF	ICA	TIO	NS	

.,,,,										17
CE 608	38		CPS1	50mm	30V/uS	110dB	775mV	0 0035%	1 5Hz 50Khz ( 3dB)	80 · 120 · 25
CE1004	44	70	CPS3	100mm	30V145	110dB	775mV	0 0035%	1 5Hz 50Khz i 3dB+	80 - 120 - 25
CE 100B	65		CPS3	100mm	30V/u5	110dB	775my	0 0035%	1 5Hz 50Khz ( 3db)	BO - 120 - 25
CE 1704	85	121	CPS6	(50mm FM)	30VAuS	110dB	775mV	0 0035%	1 5Hz 50Khz ( 3dB)	80 · 120 · 25
CE1708	125		CPS6	150mm FM1	30V A.S	110dB	776mV	0 0035%	1 5Hz 50Khz 1 3dB1	80 - 120 - 25
CP3000		250	CPS6	FM2	JUVAUS	110dB	775mV	0.0035%	1 5Hz 50Khz ( 3dB)	161 - 102 - 35
CPANS	Output	17mV	REG1		3VAIS	70ctB	2 8mV RMS	0 008%	20Hz 20KHz	138 - 80 - 35
MC1(S)	Output	2mV	BEGI			65dB	70uV 150	0.008%	20Hz 20Khz	80 - 120 - 35
VO2 VO3	Dutnut	775 250Year	BEG1		9V 115	90dB	775mV	0.01%	C over points ore set	150 50 20
*Power	output i	batour s	WRM	S and is a	ven for	two m	odules run	off the sa	me power supp	bly. Higher
	Outputi	3 quotou	• • • • • • • •	o und is g				T . ID C		, ,
DOWNER	are obtai	nablaifuei	na on	n madulie r	C P	l I oriti	usina a stabi	ilised P. 5	· U	

PRICES	HELD	FROM	AAY-	-TOFE	B '80
Power Amplifier	Modules	Power Supply	Modules	Heat	sinks
CE 608	£21 00	CPS1(80VA)	£19.50	50mm	1 1 70
CE1004	E24 50	CPS21150VA1	£23 50	100mm	f2 70
CE1008	127 50	CP\$6 (250VA)	130 00	150mm	13 50
CE1704	£35 00	REG1	t 9 30	FM1	t'36 00
CE 1708	f35 00	186	12 50	FM2	142 00
Pre Amplifue	Modules	Active Cros	tovers	Hard	ware

re-Amplifier	Modules	Active C	Crossovers	Hardware	,
PR1	/34 00	XO2	£ 19 00	Po: Amp	139
PAIS	(44 50	XO3	128 35	Power Amp	138
IC1	£26.00	MU1	t 7 50	Thermal Curouts	11
CIS	137 00				


BARCLAYCARD

(1.00 extra +( mort i 100)



9 CLAYMILL ROAD, LEICESTER LE47JJ, ENGLAND, Tel 0533 761920 Telex 34694 Chanco G CRIMLEK

ETI JANUARY 1981

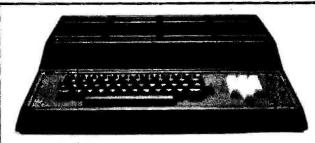

# MICROTYPE MODEL 3 CASE

Ready cut for SUPERBOARD/UK 101, NASCOM 2 and blank for HOMEBREWS

Produced in black ABS Plostic, complete with fixings and instructions, space for PSU, expansion, force feed fan, numeric pad and additional keys.

£24-50 + p&p + VAT



# NPS1 NUMERIC PAD

for SUPERBOARD/UK101 only

A 0-9 numeric pad in kit form, complete with switches, caps, PCB, plug and socket, cable and

£11-95 + p&p + VAT

Please send me a Model 3 case at £29.90 inc.

My micro is .

Please send me a NPS1 numeric pad for my Superboard/ UK101 at £14.32 inc.

Please send me your full literature. I enclose SAE.

(Please enclose your name and address with cheque or P/O)



# /ICROTY

PO BOX 104 HEMEL HEMPSTEAD HP2 7QZ



# Wilmslow **Audio**

# THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATA-LOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMANS HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS KEF - LOWTHER - MCKENZIE - MISSION - MONITOR AUDIO MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNOY VIDEOTONE - WHARFEDALF

# WILMSLOW AUDIO

35/39 CHURCH STREET WILMSLOW, CHESHIRE

Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI AND COMPLETE SPEAKERS.



# SPACE **INVADERS**



HAND HELDS + CARTRIDGES ATARI - ACETRONIC - PRINZTRONIC RADOFIN - DATABASE etc

We keep a full range! Send for cartridge lists stating which machine you own

MAIL ORDER SERVICE

# SION MATTEL

**AUGH** 



£173.87 + VAT

Available August 1980 This is the most advanced TV

game in the world. Expandable next year into a full microcomputer. COLOUR CATALOGUE AVAILABLE WITH DETAILS ON ALL THE CARTRIDGES

RIDGE

Problem Mode

Audio Feedback

Instant Response

Auto scorekeeping

COMPUTER

Plays 1/2/3 or 4 Hands

COMPUTER

Solves Problems Rejects illegal moves

2 level machine £43 + VAT

4 level machine

£77.78 + VAT

TELEPHONE & MAIL ORDERS accepted on Access \* Barclaycard \* Access ran Express \* Diners Club
CALLERS WELCOME – at our shop in Welling — Demonstrations daily
Open From 9am-5pm Mon-Sa: — (9am-1pm Wed)



Send for further details.

#### COMPUTERS

**NEW RANGE** AVAILABLE AUGUST 1980 We specialise in computer chess machines & stock over 13 different models from £20 to £300

# KGAMMON



OMAR 1 OMAR 2 CHALLENGER GAMMONMASTER

From £38 to £108. Send for further details.

## COMPUTERS



# LEISURE

- \*CHEAP TV GAMES
- \* TELEPHONE ANSWERING MACHINES
- **AUTO DIALLERS**
- \* CALCULATORS
- **DIGITAL WATCHES**
- PRESTEL
- \* HAND HELD GAMES

# altigy aylah

SILICA SHOP LTD., Dept. ETI.1 1-4 The Mews, Hatherley Road Sidcup, Kent, DA14 4DX

Tel: 01-301 1111

GUARANTEE - Ful 12 months - After Sales Support We have comprehensive brochures on all products. Please, et us know what you like into 32 page catalogue covering most games on the market.

# CATALOGUE For a free copy

FREE

of our 32 page catalogue, send a 12p stamp to Silica Shop Ltd Telephone or Telephone

CEEFAX

Add on Adaptor

£173 + VAT

RADOFIN TELETEXT

24-TUNE

DOOR

BELL

£13.65

+ VAT

100

108

# ETIPRINTS

ETIPRINTS offer you the easy way to produce high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

etiprints are made from our original artwork ensuring a neat and accurate board. We thought Etiprints were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

#### PARTS LIST

040A	ETI 80 VCO/VCLFO	Feb 80		Speed Control	
040B	ETI 80 PSU Tuning Fork Hi-Lo Filter	Feb 80	047C	DTM Switching Board RIAA Preamp ETI 80 Envelope Shaper	Sep 80
	Coin Toss			TV Sound Survival	
041A	Audiophile Driver Amp VCA Signal Tracer Heater Controller Main Board Electromyogram	Mar 80	048A	Sustain/Fuzz Box Flash Trigger FM Radio Control Receiver: (Top side)	Oct 80
041B	ETI 80 VCM Heater Controller Sensor	Mar 80		(Bottom side) FM Radio Control Transmitter	
046A	ETI 80 Dual VCA 100 W Power Amplifier	Aug 80	048B	Vocoder Siew Rate Control Vocoder Output Amp Vocoder Input Amp	Oct 80
046B	Capacitance Meter US Alarm BGM 100 W Amplifier	Aug 80		Vocoder PSU Vocoder LED PPM Display	
	Logic Tester 100 W Power Amp		048C	Cassette Interface ETI 80 Monitor Amp	Oct 80
047A	Digital Test Meter	Sep 80	049	AF Generator	Nov 80
047B	Vocoder Internal Excitation	Sep 80		Multi-Option Board Space Invasion PSU	

#### = BUYLINES =

Sheets for Sep 79, Dec 79, Jan 80 and April - July 80 are temporarily out of stock.

Earlier ETIPRINT sheets are available.

Send a cheque for PO (payable to ETI) for £1.20 per sheet with details of the project for which you require an ETIPRINT, and the month and year of publication to:

ETIPRINTS, ETI, 145 Charing Cross Road, London WC2H 0EE.

#### =HOW IT WORKS ==

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!





# **Pocket Printer**

animex have launched what they believe to be the smallest and most versatile print and display calculator in the world. The Micro 1226T features a 12 digit green display plus full print-out capability in a 140 x 72.4 x 23.5 mm package weighing only 260 g.

# Ultrasound

A new series of matched, low-cost ultrasonic transducers from Impectron are small, light and highly sensitive. They offer excellent performance in applications such as industrial control and intruder detection systems.

The EFR-OCB25K5 and EFR-RCB25K5 are transmitter and receiver respectively, with a nominal centre frequency of 25 kHz. Sensitivity is around -60 dB/V/uBar with mini-

It uses standard 38 mm thermal paper from its own paper store or from a larger paper holder. The keyboard includes a fully addressable four key memory, percentage key, item count key and single and double zero input key. Print-out speed is 1.8 lines per second.

mum bandwidth of 3 kHz. Overall dimensions are 1" long (body length 0.37") by 0.95" diameter for both transducers.

Their internal construction incorporates a compound vibrator (ceramic chip plus conical aluminium resonator) providing sensitivity and bandwidth.

Delivery is ex-stock and application notes for designers are available from Impectron Ltd, Foundry Lane, Horsham, W Sussex RH13 5PX.



# **Crystal Clear**

Ambit International's four new Acompact modules combine a data decoder and LCD display for only £19.95. Two versions (DM180) DM181), based on the ICM 7211, provide simultaneous decoding and display from multiplexed BCD inputs. Hex or Code B displays are also available. Power consumption is 3V5 to 6 V at typically 20 uA in either four or 3½ digit formats.


All the modules measure 60 x 30 x 7 mm (12.5 mm LCDs with integral incandescent backlighting) and can be supplied with a panel mounting bezel. For further details contact Ambit International. 200 North Service Road, Brentwood, Essex CM14 4SG.

Beckman Instruments' new model 740 and 742 large area LCDs feature as standard pin connectors bonded to the display. The connectors are also available separately.

The 740 features six digits (½" high) with colons and decimal points in a 2.75" x 1.2" package. The 742 offers eight digits, also ½" high with colons and decimal points, in a 3.7" x 1.2" package.

Power consumption is very low — 50 uW for the 740. Both models offer a wide operating voltage range (3-20 V RMS) and are compatible with available CMOS drive circuits.

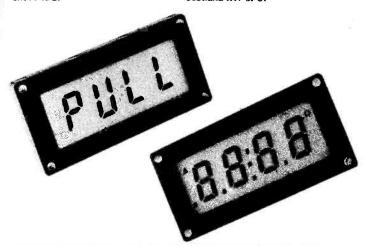For further information contact Beckman Instruments Ltd, Queensway, Glenrothes, Fife, Scotland KY7 5PU.



Ambit International (above) and Beckman (below) displaying themselves.



# Autel


EMIDATA and Autelca Ag, the Swiss pay-phone manufacturer, have got together to produce a new pay-phone credit card system. When the customer buys a card, its magnetic strip is pre-coded with an agreed credit value (a number of time units).


To pay for a call you simply insert the card in a slot in the telephone. Its value is displayed on a digital read-out and reduced unit-by-unit at the appropriate rate during the carl. When you hang up, the card is returned coded with its reduced value. If the value should fall to zero




during a call, the card is returned and the display flashes for a few seconds before automatic disconnection. The card is then disposed of and a new one purchased.


# PCB FOIL PATTERNS

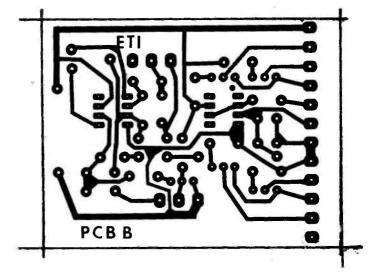

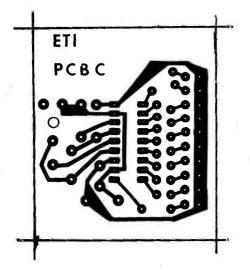


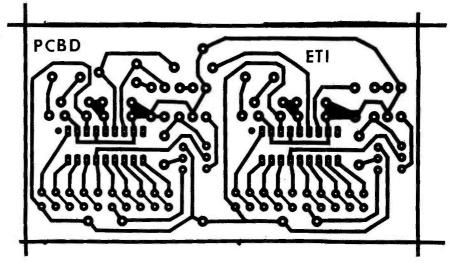The FM Tuner boards B (above), C (left) and D (below).




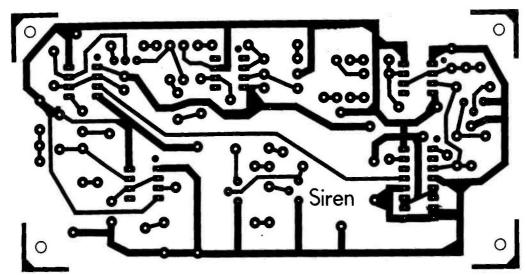


(Above) Multi-Option Siren.

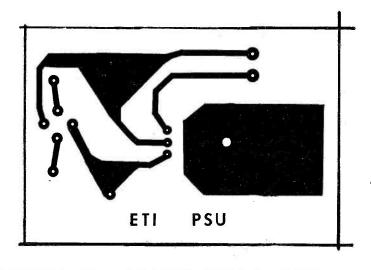


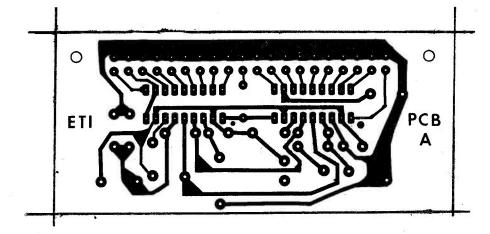
The FM Tuner PSU (above), switch assembly board (right) and PCB A (below).



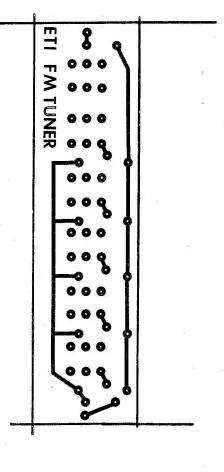

(Below) LED Tacho.

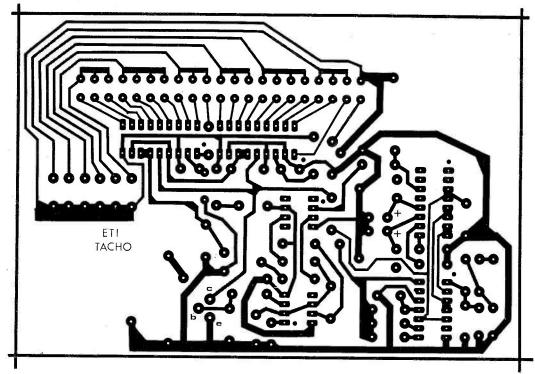

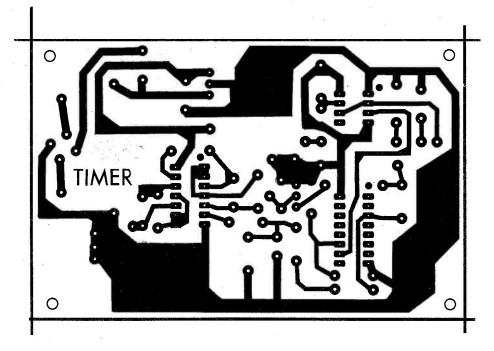

(Above) Universal Timer.



**ELECTRONICS TODAY INTERNATIONAL HOBBY ELECTRONICS COMPUTING TODAY VIDEO TODAY** 

MM Design & Print, one of London's youngest and most progressive graphics agencies, urgently requires an experienced process camera operator for its rapidly expanding magazine and publicity work. There will be an opportunity for the right person to get involved in other aspects of production.

An attractive salary is offered, depending on age and experience.

If you're young, eager to learn and don't mind hard work, then ring Diego Rincón on 01-437 1002.

#### PARNOON ELECTRONICS LTD.

Dept. No 22, 44 Paddock Mead, Harlow, Essex CM18 7RR, Tel: 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range  $\pm$  51/10 tolerance. High quality resistors made under strictly controlled conditions by automatic ma and colour coded.

£1.00 per hundred mixed. (Min 10 per value) £8-50 per thousand mixed. (Min 50 per value) Special stock pack 60 values. 10 off each £5-50

DIODES: IN4148 3p each. Min order quantity – 15 items

£1.60 per hundred

**DIL SWITCHES:** Gold plated contact in fully sealed base – solve those programming problems. 4 Way **86p** each, 6 Way **£1·00** each, 8 Way **£1·20** each,

DIL SOCKETS: High quality, low profile sockets. 8 pin - **10p.** 14 pin - **13p.** 16 pin - **15p.** 18 pin - **19p.** 20 pin - **25p.** 22 pin - **29p.** 24 pin - **35p.** 28 pin - **39p.** 40 pin - **57p.** 

ALL PRICES INCLUDE V.A.T. & POST & PACKING -MIN ORDER - U.K. £1 00. OVERSEAS £5 · CASH WITH ORDER PLEASE

#### Electronic Kits for the Thrifty!

Build 50 Interesting Projects on a P.C. Chassis with surplus components from your

### EXPERIMENTER'S PRINTED CIRCUIT KIT

Contents: 4 small boards to suit the enclosed designs. Etching Powder, Resist Paint, Solvent, Degreaser and Etching Instructions: also 50 Circuit Diagrams, Chassis Plans and Layouts for simple Crystal Sets, Transistor Radios, Transmitters, Amplifiers, Intercoms, Radio Control, Metal Detector, Photoelectric and Ultrasonic Alarms, "Perpetual Motions", Light-Beam Telephone Instruments, Testers, Gadgets, etc. You can build at negligible cost with "Surplus" or reclaimed parts and transistors you already have. Price: £1,70. Postage and Packing 30p.

#### PHOTOELECTRIC KIT

A kit of basic parts to build a simple I.R.-sensitive Photoelectric Switch. Contents: Phototransistor, Transistors, Diode, Resistors, Connector, Latching Relay, Chassis Board, Case, Screws and full instructions.

Price £4.50 Postage and Packing 50p

A kit of parts to build an I.R. folded-beam Projector and Receiver to suit the above kit. Contents: 2 Lenses, 2 Mirrors, 2 45-deg, blocks, Infra-Red Filter, Lampholder, Building Plans, Price £3.70. Postage and Packing 30p, Both kits together make an Invisible-Beam

# EXPERIMENTAL ELECTRONICS 335 Battersea Park Road, London, 5W11 4SL Send s.a.e. for full details of all kits and circuits

# PROTON ELECTRONICS

		_	~						
7400 7401	12p 13p	74L504 74L510	16p 21p	LINEAR LM 301 A-8 555 556	25p 21p 58p	BC109C BC147/8 BC149 BC159	10p 7p 7p 8p	TIP30 2N3054 2N3055	38p 49p 40p
7402 7403 7404 7405 7408 7410 7414 7428 7442	13p 13p 14p 16p 16p 16p 50p 40p 52p	4000 4001 4002 4006 4007 4011 4012 4014 4016	15p 15p 15p 75p 18p 19p 18p 65p 42p	709-14 710-14 741-8 747-14 748-8 723-14 CA3046 CA3080 CA3140	29p 38p 17p 50p 35p 35p 55p 75p	BL158 BC182/3 BC184 BC212/3 BC214 ZTX214 BC327 BC327 BC328 BC337	8p 8p 8p 8p 8p 16p 14p	DIOD IN914 IN4148 IN4001 IN4004 IN4005 IN4007 IN5401	3p 2p 4p 5p 5p 7p 14p
7475 7476 7485 7490 7493 7494	36p 38p 99p 35p 36p 76p	4017 -4024 4030 4035 4043 4044	69p 50p 50p 95p 90p 80p	LM3900 MC1310P MC1458 TBA800 TBA810	48p 110p 40p 80p 85p 33p	BC338 BC547 BC557 BCY70/71 BLY72 BD131/2	14p 9p 9p 13p 13p 35p	0A91 0PT DL704 FND500	110p 95p
74100 74121 74151 741500 741502	110p 32p 69p 15p 16p	4047 4051 4066 4069 4085/6	95p 78p 55p 20p 70p	TL081 TL082 TRANS BC107/8 BC109	60p	BD135/6 BD139/40 BFY50151 BFY52 AD161/2	38p 35p 19p 19p 40p	Red Green Yellow Clips	.2" 10p 13p 13p 4p

0.5W Res. Carb. Film 51. E12 range 10Ω-10m 1½p, Polyester Caps 0.015-0.068 4p, 0 1-0 33 0.47 8p, 0.68 8p, 1.0 13p,
All Full Spec. Gueranteed, C.W.O. 30p P&P. Mail order only

70 BRIGGS FOLD ROAD, EGERTON, BOLTON BL7 98Q

#### THE ZX80 MAGIC BOOK £4.75

For machines with 1.3K RAM. New edition 3 contains 20 plus programs including one which allows you to make music with your ZX80, and games such as Moon Lander, Hammurabi, Othello, Hexpawn and Animals. Also sections on How it Works, Plotting, Using USR, Converting other BASICS, and Hardware Notes including circuits for static and dynamic memory extensions and I/O.

#### 23 + 23 WAY ZX80 EDGE CONNECTOR. £3 MICROPROCESSOR POWER SUPPLY. £29.30

Cased, assembled and tested. 240V AC input. Stabilised outputs + & - 12V @ 350mA total, +5V@ 1A.

# ASCII KEYBOARD. £39 inc. VAT, P&P

Brand new, assembled and tested. 60 keys arranged in typewriter style stepped rows, auto repeat function, UC + LC  $\infty$ ded, S.A.E. FOR DETAILS.

ALL PRICES INCLUDE UK DELIVERY & 15% VAT

# TIMEDATA LTD.

57 Swallowdale, Basildon, Essex

# **ADVENTURES** with ELECTRONICS



A complete Kit, including S-Dec, wire & bettery, for the 16 projects described in Tom Duncan's book 'Adventures in Electronics' published by John Murrey. No soldering. Adopted for class use in many schools: and a welcome gift for ages 11 upwards.

With book, £21.69

Without book 521.69

Without book, £19.84

Clear pictorial instructions for making the following: RAIN DETECTOR, INTERCOM, MORSE BUZZER, BURGLAR ALARM, 3 TYPES OF RADIO, PARKING LIGHT, FLASHING LAMP, ELECTRONIC ORGAN, METRONOME, SIREN, TIMER, COUNTER, FIRE ALARM.

#### ADVENTURES WITH MICROELECTRONICS

A similar Kit including 'Bimboard' and Integrated Circuits. Suitable for the complete beginner, or those who have already enjoyed 'Adventures with Electronics'.

With book, £33.11 Without book, £31.11

Conversion Kit: With book, £26.90 Without book, £24.90 Cash or cheque with order, please, to

LAB UNILAB LTD. Clarendon Blackburn, BB1 9TA, Eng Telephone (0254) 57643 UNILAB LTD. Clarendon Road, Blackburn, BB1 9TA, England.

Prices include carriage and VAT and are correct at time of going to press.

MAIL ORDER ONLY		OPTO/	4041	85p	7473	+18p	AC151		BD121/3	75p	TIP36A 200	
		ELECTRONIC	4042	80p	7474	+25p	AC153		BD124	81p	TIP36B 210	
DELTA TECH & (	חי	2N5777 <b>55p</b>	4043/4			<b>★25</b> p	AC176		BD131/2	40p	TIP41A 60 TIP42A 60	
I UELIA IEUΠ α U	JU.	OCP71 65p			7476	30p	AC187/8		BD135 to BD140	40p	TIP2955 70	
		ORP12 <b>80p</b>	4048		7480	32p	AC187K AD149	30p ★50p	BF178	30p	TIP3055 +30	
62 NAYLOR ROAD, LONDON,		DL704 110p	4049		7485 74B6	80p	AD161/2		BF 179	19p	ZTX107/8 12	
	usive Prices	DL707 110p	4050B			±25p	AF114	30p	BF180	34p	ZTX109 12	
Please add 35p for P&		0.125" & 0.2"	4068/9		7490	57p	AF124	35p	BF181	8p	ZTX300/1 14	P
CERAMIC CAP (BOV)	NE555 <b>26</b> p	LEDs:	4070B/1		7492/3	30p	AF125/6	35p	BF183	34p	ZTX302/3 18	
33 pF to 4700 pF 4p	NE556 <b>*45</b> p	Red 13p	4072/3		7494	50p	AF127	35p	BF184/5	25p	ZTX304 23	
POLYSTYRENE CAP (50V)	NE566 140p	Green 16p	4081/2	26p	7495	40p	AF139	40p	BF194/5	12p	ZTX311 18	
10 pF to 1000 pF 5p POLYESTER CAP (100V)	SN76115N *80p TBA641B 200p	Yellow 16p	4086		7496	37p	AF239	44p	8F196/7	12p	ZTX500/1 15 ZTX502 20	
1 nF to 68 nF 6p; 100 nF 150 nF 8p; 220	TBA800 75p	0.125" Clip <b>3p</b> 0.2" Clip <b>3p</b>	4510	100p		200p	BC107/B	10p	BF19B BF200	10p	ZTX502 20 ZTX503 17	
nF 9p; 330 nF 10p; 470 nF 11p; 680 nF	TBA 810S 110p	0.2 Clip <b>Op</b>	4511B		74100 74105	60p	BC109 BC117	10p 23p	BF224B	14p	ZTX504 24	
12p; 1uF 14p; 1.5 uF 16p; 2.2 uF 20p;	ZN414 90p	DIL SOCKETS	4516/8 4520/8		74105	22p	BC140	20p	BF 244B	*22p	2N696/7 20	
3.3uF 15p*; 4.7uF: 15p*	ZN1034E 220p	8 pin <b>*8p</b>	17L	. oup	74109	34p	BC142/3	30p	BF25B	26p	2N698 20	
		14 pin <b>★9p</b>	7400/1	16p	74110	40p	BC147/8	10p	BF259	40p	2N706 14	
ELECTROLYTIC CAP (uF/V)	DIODES	16 pin <b>★10p</b> 18 pin <b>16p</b>	7402/3	16p	74118	84p	BC149	10p	BFR39	30p	2N914 20	
1/25 to 47/25 <b>6p</b> ; 68/25 <b>7p</b> ; 100/35, 150/25 <b>8p</b> ; 160/25; <b>5p</b> *; 200/12;	OA47 <b>8p</b>	22 pin <b>20p</b>	7404/5	16p	74121	25p	BC157#8	12p	BFR40	20p	2N918 38 2N1302/3 38	
6p: 250/12 7p: 220/25 10p; 470/25.	OA91 7p	24 pin <b>21p</b>	7406	18p	74122	30p	BC159	12p	BFR79	32p 20p	2N1302/3 38 2N1304 38	
500/30 10p*: 470/40 mini 15p;	OA200 <b>6p</b>	28 pm <b>25p</b>	7407	25p	74123	50p	BC167	14p	BFRBO BFX29	25p	2N1306 30	
640/16: <b>8p</b> : 1000/10 <b>8p</b> *: 1000/25	OA202 9p 1N916 5p	40 pin 35p	740B	22p	74125/6 74132	42p 65p	BC169C BC171	13p 10p	BFX84	25p	2N1308 3	
24p: 1500/25: 24p+; 2200/6.3 10p+	1N916 <b>5p</b> 1N4148 <b>4p</b>	THEFT	7409	13p	74141/5	46p	BC171	6p	BFX85/6	20p	2N1613 28	
ZENER DIODES (400mW)	1N4001/2 4p	THYRISTOR C106D 40p	7410	13p	74150	85p	BC177/8	16p	BFX87/8	25p	2N1711 13	
2V7 to 33V 8p	1N4003 <b>5p</b>	(4A/4000V)	7411/2	21p	74151	65p	BC179	16p	BFX88	25p	2N1B93 2	
VEROBOARDS (.1" copper)	1N4004/5 <b>6p</b>	(42740001)	7414	45p	74153	43p	BC1828	10p	BFY50/1	20p	2N2217 10	
2.5" x 5" 65p	1N4006/7 8p	CMOS AE	7416	20p	74154	66p	BC1B2L	*8p	BFY52	22p		3р
3.75" x 5" 75p RESISTORS (5% E12)	1N5400 <b>13p</b>	4000 <b>16</b> p	7417	25p	74155	46p	BC183B	10p	BRY39	50p		3p 7p
10 Ohms to 10 Mohms 1.5p	1N5401 14p	4001B <b>20p</b>	7420	*14p	74156	42p	BC184	10p	BSX19	12p 22p		5p
PRESETS (.15W HORIZONTAL)	1N5402 <b>15p</b> 1N5404 <b>16p</b>	4002 16p 4006B 75p	7421	30p	74157 74160	36p	BC186 BC187	25p 15p	BSX20 BU205	150p		Вр
100 Ohms to 2 Mohms 7p	1110404 100	4007 <b>*16p</b>	7422	26p	74160	55p	BC207/9	13p	BU 20B	210p	2N2904/5 2	1p
POTENTIOMETERS (1/4W)	BRIDGE	4008 65p	7427	28p	74162/3	60p	BC212	10p	MJ2955	110p		1p
Linear & Log Scales	RECTIFIERS	4009 <b>42p</b>	7430	16p	74164/5	56p	BC212L	*8p	MJE340	52p		Dр
4K7 to 2M2 33p	WO2M <b>20p</b>	4010 <b>48p</b>	7432	28p	74166	95p	BC213L	10p	MJE2955	110p		Оp
LF356N 85p	W06M <b>30p</b>	4011B <b>20p</b>	7433	38p	74173	110p	BC214	10p	MJE3055	80p		0р 5р
LINEAR LM301AN 30p	1A/50V 22p	4012 <b>25</b> p	7437	14p	74174/5	55p	BC214L	*8p	MPF102 MPF104/5	45p 40p	2N3442 14	
TOO O	1.5A/75V <b>22p</b> 1A/200V <b>32p</b>	4013B 45p 4014/5B 80p	7438	18p	74176/7	70p 35p	BC238	18p	MPF10475	45p	2N3702 to	.,
LIVIS TON 120P	1A/400V 34p	4014/38 <b>440</b>	7440	13p	74180 74181	80p	BC261B BC301/3	32p	MPSA06	26p		10
710-14 350 LM318H 120p LM324N 570	2A/100V 40p	4017 <b>70p</b>	7441 7442	52p	74182	45p	BC328	17p	MPSA56	26p	2N3772 *8	
747-14 <b>50p</b> LM339N <b>52p</b>	2A/400V 55p	401B 85p	7443	60p	74190	50p	8C33B	17p	MPSU06	60p	2N377.3 <b>25</b>	
748-8 35p   M348N 90p	3A/100V 55p	4019 <b>50p</b>	7444	100p	74191	90p	8C461	40p	OC28/35	92p		1p
CA3018 70p LM377N 175p	3A/600V 65p	4020B 100p	7445	64p	74192/3	50p	8C477	35p	TIP29	40p		0p
CA3028A 85p LM3BON 90p		4021/2 <b>95</b> p	7446	65p	74194	70p	BC478	20p	TIP29B	42p		0р 5р
CA3046 50p LM381N +120p	VOLTAGE	4023 <b>22p</b>	7447A	50p	74195	68p	BC479	23p	TIP30	40p 42p		5p
CA3054 40p LM382N 120p CA3080E 75p LM1310N 115p	REGULATORS	4024B <b>55</b> p 4025 <b>20</b> p	744B	52p	74196	78p	8C547/8	12p	TIP30B	+30p		Sp Sp
CONTRACT OF	7805 <b>70p</b> 7812/15 <b>70p</b>	4025 <b>20p</b>	7450	10p	74197 74198	45p	BC549	12p	TIP31A	40p		5p
CA3130E 90p LM1458N *40p LM3900N *50p	7812/15 <b>70p</b> 7818/24 <b>70p</b>	4027 30p	7451/3	13p 10p	74198	90p	BC557/8 BC559	14p	TIP33	65p		Op
CA3090AQ LM3909N 75p	7905 <b>80p</b>	4029 <b>90p</b>	7454 7460	13p	TRANSIST		BCY70	18p	TIP33C	70p	2N6027 3	0p
*200p MC1496P 80p	7912/15 <b>80p</b>	4030 55p	7470	20p	AC126/7	22p	BCY71/2	18p	TIP34A	75p	3N128 5	0p
LF351N 44p NE531 120p	7918/24 80p	4035 11 <b>0</b> p	7472	19p	AC128	20p	BD115	58p	TIP35B	200p	2N5459 <b>4</b>	0p
	25p 7473	16p 1N4005 4	.5p ZD5V			15p	160uF/	25V 3p	CA3090A	ú 70p		P
1017	40p 7490	23p 1N4007	Sp ZD9V		TIP31	A 22	640uF/	16V 3p	SN76115		33uF/40V 4	
25 PCS 4007A 13P 4017A 4011B 15P 7420			Op BF24		TIP30	55 <b>22</b>	1uF poly	, 8р	680nF po	ly 7p	MANY MOI	IE
EACH TOTAL					_	_						113

**ETI JANUARY 1981** 

# **CLEF KITS**

High Quality Electronic Musical Instruments under the pe struments under the personal supervi sion of Specialist Designer A. J BOOTHMAN.

U

#### **JOANNA 72 & 88 PIANOS**

Six and 7¼ Octave Electronic Pianos with unique Touch Sensitive Action as used in the P. E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. Build this widely acclaimed professional instru-ment, for either Domestic or Stage use, from our top quality Component kits.

SIX OCTAVES - £207.00 7% OCTAVES - £232.00

#### P.E. STRING ENSEMBLE

The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impress-

COMPONENT KIT - £169.00 Back up TELEPHONE advice is available from the designer to supplement the clear instructions included with the above Kits

#### P.A.s - SPEAKERS -CABINETS

Units can be supplied to add to the Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

#### P.E. MASTER RHYTHM

A User Programmable Rhythm Generator for up to 24 selectable patterns on Eight tracks. Three in-strumentation settings select from twelve instruments, and sequence operation gives up to 16 Bar pattern

COMPONENT KIT-£79.00

#### **ELECTRONIC ROTOR**

Two-speed organ rotor simulator plus a three-phase chorus generator. Easily integrated with existing organ.

COMPONENT KIT £89.00.

#### KEYBOARDS (SQUARE FRONT)

49 NOTE C-C £23.80

73 NOTE F-F £37.00

88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

#### **BUILDING SERVICE**

We are specialists in Electronic Piano Manufacture and can build your Piano for

#### INFORMATION

INFORMATION
Please send S.A.E quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & insurance.

#### Showroom: 44a Bramhall Lane South

Enquiries welcome — in Australia please contact JAYCAR (Sydney).

### CLEF PRODUCTS (ELECTRUNICS) LIMITED

(Dept. E.T.I.), 16 Mayfield Road, Bramhall, Cheshire, SK7 1JU, 061-439 3297



MIGTORS. 1.5V Model motors 22P. Sub. min.
'Big inch' 115V DC 3 rpm motor 32p.
Replacement 8 truck 12V DC motors 55p.
115V AC 4 rpm motor 95p. 9V GC Casatte
motors 95p. 6V Casaatte motors. new

BIJZZERS. Ministers solid state type. 2 voltages available. 6 or 12 vdc 75g sach. LUDO 12 volt bazzer 50×30ms 50p. Cartars 12Y OC Minister atoms frans 17.85. 12Y OC SARRI. all metal rolary type. Minj pitched wall. Ed. 50. Rebary atoms sizes. 12Y OC. red plastic unit volta mounting bracket. 68 × 75mm 14.50.

RELAYS. 2 types both operate on 12V OC, sealed plastic cased types. 1—350 ohm with 2 make 5 amp contacts 75p. 2—1,000 ohm with 2 changeover 1 amp contacts 75p.

SPECIAL OFFER SEMICOMDUCTORS. 285062 SCRs 18, 8X504 apto isolator 25g, CA3130 95g, CA3200 45g, TOA1151 25g, 731 CA3200 45g, MS55 25g, RS55 25g, RS56 25g, RS56 25g, RS56 25g, RS66 25g, RS

NEW STOCK ITEM — We are now stocking to mind hand-hold drills, these are a practised british-made tool, ideal lar P.C. beard drilling, madel maters atc. They prevail no 12 '00 C. Orill kit supplied in plantic hinged case, with drill and 21 accessories, cliffle, sanders, realmers, buffer, stc. complete kit only £14.25. Orill only £12.25 orill or £12.95 [postage 659].

S.W.R./RELDSTRENGTH + POWER METRES. S.W.A. 1: to 1:3. R.F. power B-100 watts frag. range 1.5 MHZ to 144 MHZ.1 52 Å: MPTEMMCE PLZ56 terminations stre 8"× 2"× 2" 19.85. JACK SOOIS COO4 50 PF variable tening condessors. Standard W aglodia. 50p cach.

TOOLS, SOLDER Sector, good ancilos, teles nazris, E4 99 Side cettors 5° E1 45, Piezo 5° E1 45, MEDON DANIES PE 1016 59, BRITAMIA 16 pie 10 E33 city E1 25, 5° PIECE precision acceredirers rais, individual headles, E1 05, JUMPER TEST LEAD SETS 10 pairs of leader with insalable crecs each eef 50, CAMPPING TOOL, accombination byte for crimoling real this and prilow terminations also incorparates a wire criminar for acceptance and wire cetter insulation.

MAICH OPPHONES. Min. The pin. Oai. uses deal aid battery (supplied \$4.95. Low cast some terms to Conference COM 105 Danie. (Dishburt. on/off south. Dishburt. on/off south. Dishburt. on/off south. Dishburt. on/off south. Oail political world being £7.95. EMBTOP share one dishburt on the pin. (2.95. EMBTOP share one dishburt on the pin. (2.95. EMBTOP share one dishburt. Oail off share one dishburt. Oail off share one dishburt. Oail off share of the pin. (2.95. EMBTOP share) of the pin. (2.95. EMBTOP consequence of the pin. ETZ.25. EMMON Castesser. Cartisle. Ins. GOODsheer of Sol. barry chromod Copper Case, Et2.95. DYNAMON P.A. Miks, mobile rolle oct. thanh which Sols inp. E3.75. CASSETTE replacement microphone with 25.73.5 plage [1.35. INSERTA Crystel replacement 35×10m 40p. GRUNDING Floring in Control of the Control of Castes Castes



EED VU METERS. Utilities applicational logic control circuit with adjustable rise and decay these via autoraal capacitar-Speciares — 200 may be a 12-150 OC. 82mm logs. Stome logs. 100 Meters 100 Met

SPECIAL OFFEN DEC TYPE BREAD-BOARDS. Micro DEC "A" with 2 16 pin Oil carriers 63.95. Approximately built original saffing price.

SUMPLUS P.C. BOARD with 15 C106 B CR.'s 4 read relays, 22 sambored transisters, various diedes, resisters, etc. £3.10.

COPPER LAMINATED PRINTED CIRCUIT BOARD. Fibreglass Single Sided type (apprais. Zum Bitch) 150/150m 40p. 2001/30mm 55p. Doeble-sided Fibreglass Imm blick, 180x135mm 45p. PAKOLIN BASED TYPE: (Zum Riick). 180x135mm 40p. 2801/200mm 50p.

TAPE MEADS. Mone casselle, £1.75. Stereo casselle £3.90. Stendard 8 track stereo £1.95. BSH MM 1330 ½ track 50p. BSR SRP90 ½ track £2.10. Told dual head assembly 2 heads both ½ track R/P with built in erase £1.25.

SWITCHES, Sub. min. Toggies. SPS1 8×5×7mm. 42p. DPOT [8×7×7] 55p OPOT Centre off [12×11×9mm] 77p.

PUSH SWITCHES (16×6mm), red top push in make 15p each, push on breat version black vinyl 17p each.

SLIDE SWITCHES all OPOT  $15\times8\times12$ mm 13p,  $16\times11\times9$ mm 13p,  $22\times13\times8$ mm 13p,  $22\times13\times8$  centre off 14p, Multipale strider double achea [12 tags]  $29\times9\times1$ mm 25p.

ROTARY SWITCHES (water) 3P4W, 4P3W 2P6W and 1P12W all 35p each.

10 pin D.I.I. SWITCHES paly 42s exch. RIBBON CABLE 8-way single core minia-ture 22p per metre.

INCADS. AA size 1.2 volts 500ma E1.10

MOTOROL & PLEZO ELECTRIC TWEETERS



PIEZO TWEETERS, require no crossover and can be used with systems up to 100 writs. Frequency response 3.8 to 28KHz.

SUPER HORN variou, flush flunge 311".

BANK ARENA stereo cartridge pream-ptifier modules, suitable for magnetic cartridges, new, supplied with connection details, £1.95.


FINNED HEATSIMKS. Supplied undrilled 4mm thick. 27mm high. 75×124mm 60p. 150×124mm 95p. Smaller version 2.7mm hick. 75×108mm 48p. TRANSISTOR SOCKETS 108 or 1018 9p sach. 103 type

Atuminium Project Boxes. 18 S.W.C. with fitted lid and acrews. AB1 3x2x+1 5cp. AB2 4x3x+1.5in 62p. AB3 4x3x2in 66p. AB4 6x4x2in 74p. AB5 6x4x3m Ep. AB5 8x6x2in El.D5. AB7 8x6x3in El.Z5.

ANTEX SOLDERING IRONS. All 240V AC. Model & 15 watts €3.95. Model ICX 17 watts €3.95p. ST3 SOLDERING IRON STAND, suits all Antex Irons

TRANSDUCERS, REC/SENDER 40KH7

 TRAMSFORMERS, All 240V OC grimmy [nathage per Iranalarmer is abeum in trackets where price], MIRISTANIE RAMSE 50-6V (100m.; 9-6-W 15m.; 12-6-12V 50m.; 1179; ach; 150.) 127 (20m.; 150.) 127 (20m.; 150.) 128 (45); 120.0 128 (45); 130.0 130V IA 12.25 (45); 130.0 130V IA 12.25



PROJECT BUXES. Sturdy ABS black plastic bears with brass imagers and lid. 75×56×35mm 65p 95×7×35mm 75p 115×9×37mm 87p.

VERO HAND HELD BOX, White ABS. 24in × 3.7 in tapered, with scraws 68p each.

VERO POTTING PLASTIC Boxes with lid and screws 70×50×20mm, black, 43p

35 WATT RMS STEREO SPEAKER SYSTEM. Wester. Squawker. Two ster (controlled) in black heavy alloy cabinets. 74"×4½"×4" C35.75 pair P&P £1.95.

SPECIAL OFFER DEMAGNETIZER. Ourved probe type, suitable for reet or cassette machines, operates on 240V AC only £1.95.

POWER SUPPLIES. Switched type plugs into a 13 amg socket has 3-4, 5-6, 7-5 and 9 volts 0 c out at either 100 or 400ma switchable £3-45. HC244R stabilitand power supply 3-6-7,5-94 OC at 400ma, has polarity suppry 3-6-7.5-9V DC at 400ms, has polarity reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current \$5.50.



KRT101 M/Meter, 1.000, opv. IKV AC/DC Velts, 150ma DC current, Rusist-ance D-2.5k, D-100K, £4.35.



NH55 M/METER, 2.000 spv (KV AC/DC Volts, 100ma DC., Rusistance O-10K, 0-1 MEG, E5.50.



YN 360 M/METER. 20.000 apv., IKV AC/OC Volts, 250ma DC. 4 rasist-ance ranges to 20 Mag. also has built in transistor tester with leakage and lester with leakage and gain ranges £12.50.

HANDY BENCH VICE, 1"-iaw opening £2.95. 6" MOTORISED ALARM BELLS, 65mA, 8848 E7.95.

IC CAR STEREO CASSETTE PLAYERS, 3 wells per channel cutput. HO eutput imp., antestop mechanism (Japanesa) E12.50.

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown, VAT inclusive prices. S.A.E. for illustrated lists.


# PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL L2 2JD ALL ORDERS DESPATCHED BY RETURN POST
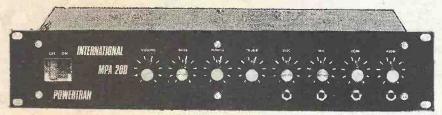
# MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs; controls, wire, etc. — compfete down to the last nut and bolt.



Panel size 19.0" x 3.5". Depth 7.3"

COMPLETE KIT ONLY £49.90 + VAT!

**MATCHES THE CHROMATHEQUE 5000** PERFECTLY!


# **CHROMATHEOUE** 5000

**CHANNEL LIGHTING** EFFECTS SYSTEM

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!


COMPLETE KIT ONLY £49.50 + VAT!

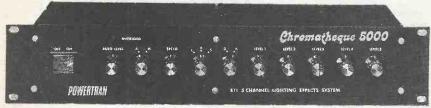

Panel size 19.0" x 3.5", Depth 7.3"
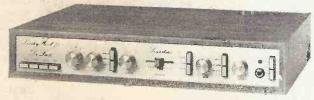
# PIWFKIR

SYNTHESIZER KITS ON PAGE 8. MORE KITS AND ORDERING INFORMATION ON INSIDE FRONT COVER.



#### DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £85.00 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%

All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



#### T20 + 20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for £38.40+VAT.

MATCHING TUNERS — See our FREE CATALOGUE!

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!

#### **MUSIC EFFECTS DEVICE — AS FEATURED** IN ELECTRONICS TODAY INTERNATIONAL!

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a spacey feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 +VAT (single delay line system)

De Luxe version (dual delay line system) also available for £59.80 + VAT

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



# GREENWEL

443A Millbrook Road Southampton SO1 OHX

All prices include VAT @ 15% — just add 40p post

### THE SPECTACULAR 1981 GREENWELD

#### **Component Catalogue**

Bigger and better than ever!!!

- 60p discount vouchers
- First Class reply paid envelope
- Free Bargain List Priority Order Form
- VAT inclusive prices
- Quantity prices for bulk buyers
- ★ Free Data Sheet

SEND 75p FOR YOUR COPY NOW!!

#### **BUY A COMPLETE RANGE OF** COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST, VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors. 5%, 10 of each value 22pF to 1,000pF, total 210, £3.69. K002 Extended range 22pF to 0.1 μF, 330 values

\$5.53. K003 Polyester capacitors, 10 each of these values 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47μ, 110 altogether for £5.07. K004 Mylar capacitors, min 100V type 10 each all values from 1.000pF to 10.000pF. Total 130 for £4.08.

for £4.05.

K007. Electrolytic capacitors 25V working small physical size. 10 each of these popular values 1, 2, 4.7, 10, 22, 4.7, 100, P. Total 70 for £3.59.

K008. Extended range, as above, also including 220. 470 and 1000µF. Total of 100 for £6.05.

K021. Miniature carbon film 5% resistors CR25 or similar. 10 of each value from 10R to 1M. E12 series. Total 610 resistors £6.15.

K022. Extended range. Total 850 resistors from 1R to 10M £8.50.

K031. Zener forders 400 ref. \$56.878.8 pt. 10.

K031. Zener forders 400 ref. \$56.878.8 pt. 10.

IR to 10M £8.50.
KQ41 Zener diadas 400mW 5% BZY88, etc. 10 of each value from 2.70 to 36V. E24 series. Total 280 for £16.37.
NEW KQ51 LED's — 10 each red, green & yellow 3mm & 5mm, with clips. Total 60 LED's for each

### **BUZZERS, MOTORS**

BUZZERS, MOTORS
& RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia X 20mm 856.
Z402 Miniature type buzzer, 6.9 or 12V. only
Z7x 15x 16mm. very neal 65p
Z450 Miniature 6V DC motor. high quality type
32mm dia X 25mm high, with 12mm spindle.
Only 61.
A372 Auditle Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage read 4-18V. Can also be driven direct from TTL or CMOS. Module size
45x21x12mm Comprehensive data supplied 61.50
W3932 Heavy Duty 12V relay ideal for the control of the control of

E1.50 W892 Heavy Duty 12V relay, ideal for car use— single 15A make contact. Coil 25R in sealed metal can with mounting bracket 85p. W890 Dit, Reed relay SPCO 2.4-10V, 200R coil. Ook E2.20 Only £2.20.

Ony £2.20.
FSRA60 Letching relay, 2 × 10A contacts, 1M, 18. Coil is 250R, and rated 60V ac, but works on 18.24 DC. Solid Ecapsulation with screw terminals makes it ideal for use. £1.20.

#### **REGULATED PSU PANEL**

Exclusive Greenweld design — better spec, than anything on the market being offered at the price. Penel 110×82×33mm high contains all components including bindge rectifier and smoother acpactors. Ready built and tested — just add that penel of the price of the pric

SPEC Output voltage 0-28V Output current 20mA-2A Source impedance OR1 Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only £7.75

#### 1N4004 & 6 DIODES

Special purchase of 1A rects, Russian made Packed in boxes of 300, £8.50 per box 4 boxes £30.00; 10 boxes £75.00

#### DISC CERAMICS

0.22uF 12V 9mm dia. Ideal for decoupling 100 for £2.75; 1000 £20.00.
0.05uF 12V 15mm dia. 100 £1.50; 1000 £12.00. Pack of disc ceramics, assorted values and voltages — 200 for £1.00

#### **TRANSFORMERS**

Mains primary, 50V 20A sec. £20.00, Mains pri 110V 15A sec £30.00; 20A £40.00.

#### SLIDER POT SCOOP!!!

Made by Phier, types PL40CP & PL60C Silly proes for supering goods! PL40CP & PSx1 5x 4mm, 40mm side length 270R, 2x2 or 10x in print, Proces (any mix) 1.24 20p; 25-99 17p; 110x 14p; PL60C— 84x10x7mm, 60mm side length, 5k, log only. Prices 1.24 25p; 25-99 22p; 100+17p.

CALC CHIPS 60p!!!

New full spec. supplied with data. Type MK50321
— full function inc memory. Only 60p

DISPLAYS
8 and 9 digit 7-segment bubble type for above chips — most have minor faults, dud segment, etc. Mixture of 2 or 3 different types with data. 5 for £1.00

NICADS
Ex-equip size C approx. £1 each; 10 for £8.00

Z525 Contans 11 800mA 50V 2N5061 SCRs, 11 6W8 zenes, 11 1N4004 diodes plus Rs, Cs. etc. Only £1. 2529 74 Series ICs — Gates and complex logic, 20 asstd. ICs on panels £1; 100 ICs £4. 2527 2 X8V zenef x-1. 2529 74 Senes ICs — Gates and complex logic, 20 asstd. ICs on panels £1; 100 ICs £4. 2527 2×6V reed relays 6×25030 or 2S230 6×400V rects, plus Rs. Only 50p.

#### TTL, LINEAR, OPTO

All new full spec — Fairchild / SGS:
TTL: 5400, 5401, 5402, 5403, 3404, 5405, 5410, 5421, 5430, 5450, 6451, 5453, 6460
— All 12p es. 5470, 5472, 5474, 5475, 5476, 5480, 5486, 5490, 54107, 54121, 54122 — all 20p es. 5482, 54126 — 40p es. Others (74S, 1476 R/J 1) (76E feliased)

an zupea. 949, 54126 – 40 pes. Umers (745, H) on B/I. 12 (SAE please). LINEAR: 9665 or 9666, 7 x 50V Darlingtons in 60 DIL 609, 75452 or 4 dual parilyh driver 70p; XK1444 7 CMOS P-channel buffers, 15V 16 DIL

24p.
OPTO: Isolators, FCD831 60p; TIL115/118
60p; FPE100/106 Infrared LED £2.50; FND847
7 seg 0.8" CA £2.00; FND850 CC £2.00. (Data on request for linear & opto devices).

#### **VEROBLOC BREADBOARD**

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC Blocs can be joined together. Bus strips on X & Y axls — total 360 connexion points for just £4.15.

#### **BULK SUPPLIES**

All new full spec, devices. Prices are for a minimum of 100 of any one device and exclude VAT, which must be added at 15%. Minimum order value from this section is £10+VAT+post. VAT receipt on request.

Min. WW 5% carbon film 18-10M (10% over 1M), all £6.09/1,000. The following values only at £3.50/1,000; per value 4R1, 882, 188, 398, 568, 220R, 18, 487, 188, 33k, 39k, 47k, 220k,390k, 560k, 680k, 690k, 680k, 6

#### MIN PRESETS

O 1W miniature type, open construction. All values from 100R to 1M, vertical or horizontal mounting. All at .042.

The following values only at .03: 470RV, 470RH, 500RH, 18H, 185H, 2kV, 2k2H, 2k5H, 4k7H, Also some Piher enclosed type at .042: 150RV, 200RH, 2kV.

POTS
5k lin, 100k lin; 220k lin; 500k log; 1M lin, All with std. bush and spindle, .14. ELECTROLYTICS-PC RADIAL LEAD

#### mm pitch. Value / Voltag

0.47/50	-022	47/40	.026
1/50	.024	100/16	022
2.2/50	.024	100/40	.027
4.7/25	.022	220/63	048
10/16	.021	330/25	.048
10/40	.023	1000/16	.06
22/25	.023	2200/40 #	.32
47/25	.025	*8mm 16mm	
Minihau Balu			

#### Minibox Polyesters Value/Voltage/Pitch

Tolder Tollage	· · · · · · · · · · · · · · · · · · ·		
1/100/7.5	.024	.033/250/10	.028
068/250/10	.024	.22/100/15	.036
022/400/10	.024	.33/100/15	.046
01/630/7.5	022	47/100/15	052
01/100/7.5	022		

**ZENERS.** 400mW 5% **2**V4 3V6 **4V7** 6V2 6V8 7V5 8V2 11V 1**2**V 14V 18V 24V, All at **.03** 

	LED	's		TANT BE	ADS
3mm yellaw 3mm green	80.	5mm yellow 5mm green 3mm clips 5mm clips	.09	1.5/35 3.3/25 10:25	.06

MINIATURE CERAMIC CAPS
Thompson/CSF miniature type in the following

values
3. 9pf, 4.7pf, 22pF, 33pF, 47pF, 47pF, 68pF,
3. 9pf, 100pf, 560pF; 2700pF†, All 5 % except
10.2, 120.6
10.2, 120.6
10.20
10.20
10.20
10.20
10.2 £9/1000 £5/1000 £9/1000

Samples on request (sae please).

Mullard min. ceramics: 33pF 5% 100V 330pF 2% 100V 3300pF 10% 100V €7/1000 £8/1000 £13/1000 Stettner min. ceramics 330pF 5% 63V 022uF 63V Lemco 047uF 63V £16,1000

SEMICONDUCTORS
741 .12. 555.19: 7401.08: 7405.09: 74L74
.21. 4001.17: 4011.17: 51 signal diodes like lik4 148 by Tion bandeliered reels of 10k £80 (1k 10): IN4002 £25/k: IN4006 £34/k: IN4007 £36/k: Ge signal diode Dk.14 £20/k: SCRs 2P4M (C1060) 4A 400V .26: 2N5060 .BA 30V .15 CR201 IA 200V .18

Send sae for latest bulk buyers list.


ALL EQUIPMENT NEW, BOXED AND FULLY GUARANTEED Order with confidence and pay no more

		and the second s
PROGRAMMABLE SCIENT	IFIC	
Casio FX501P		£46.95
Casio FA1 Adaptor-Cassette Int	terface , ,	, , £19.95
Casio FX501P with FA1		£64.95
Casio FX502P with FA1		£84.95
Texas *T159		£176.95
Texas PC100C		£176.95
Sharp EL5101 16 Digit		
Sharp EL5100 24 Digit		£56.95
SPECIAL OFFER	Texas T158C with PC	
OI ECIAL OITEN	Texas T159 with PC10	00C <b>£350.00</b>
	Includes mains adapto	r/charger
TEXAS ACCESS	ORIES in stock e.g. Libi	raries, etc.
Maths/Utilities, Applied Stats		
Surveying, Structural Engineer		
PL100C Rolls 10 off		
Battery Packs. State model or I		
T		ELECTRICATE SOCIETY

### **QUALITY WITH FULL GUARANTEE**

 Texas T1 Programmer
 £51.95

 Texas T151 111
 £28.95

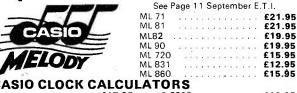

CHOID OFFICE CHECOFY	710N3	
MQ6 £17.95 AQ1600 new model £15.95	AQ <b>22</b> 00	
CASIO SCIENTIFICS	eta	

8 DIGIT	10 DIGIT	
FX68 £1	18.95 FX100£1	4.95
FX81 £1	13.95 FX510£1	8.95
FX330£1		
FX2600 £1	18.95 National NS108 £1	7.95

ALL PRICES NOW INCLUDE V.A.T., POST AND PACKING \* Cheque with order or C.O.D. 75p. Extra up to £100 FREEPOST NO STAMP NEEDED. S.A.E. WITH ENQUIRIES PLEASE

CALCULATOR SALES & SERVICE, Redditch, Words, FREE POST **R98 OBB** 

# MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p EACH POSTAGE 15p PER PACK UP TO FOUR PACKS **FIVE OR MORE POST FREE BUY SIX PACKS AND GET A SEVENTH PACK FREE!** 

MN1, 300 1/4-watt Resistors pre-formed

MN1. 300 ¼-watt Resistors pre-tormed for P&C Mtg.
MN2. 200 ¼ & ½-watt Resistors.
MN3. 100 1 & 2-watt Resistors.
MN4. 50 Wirewound Resistors.
MN5. 100 metal oxide Resistors. 1%, 2% and 5%.
MN6. 12 asstd. potentiometers.
MN7. 25 asstd. skeleton pre-set Resistors.

MN8. 50 asstd. Electrolytic Capacitors.
MN9. 100 asstd. Ceramic Capacitors. Pite, disc, tub and monolythic etc MN10. 100 mixed capacitors Polyester, Polystyrene, Metallised, Radial and Axial

MN11. 20 asstd. Silver Mica Capacitors.
MN12. 8 Tantalum Bead Capacitors

(useful values). MN13, 20 asstd. Transistors, BC, 2N

Saries + Power etc. MN14. 40 IN4148 Diode

MN15. 5 Light Sensitive Devices. MN16. 20 min. wire-ended Neons MN17. 2 12-volt Relays. Ex nearly new

MN18. 3 Encapsulated Reed Relays. 9-12v. coil, d.-pole and t.-pole.
MN19. 2 24-volt Relays. Ex nearly new

MN20, 1 240-110 to 12-volt, 100ma Transformer MN21. 1 240-110 to 24-volt 100ma

MN22. 8 .2" Led s with clips, 4 red, 2 vellow, 2 green

MN23. 116 asstd. screws, nuts, washers, self-tappers etc.
MN24. 100 asstd. small springs.

MN25. 50 asstd. pop rivets.
MN26. 50 asstd. insulated crimps.
MN27. 200 items, grommets, spacers, cable markers. plastic screws, sleeving, tie wraps etc. MN28. 20 asstd fuses 11/4" 20mm etc.

MN29. 75mts equipment, wire, asstd. colours and sizes.

MN30. 3 x 2m length. 3 core, mains

MN31. 12 asstd. trimmer capacitors, compression film. Air-spaced etc.
MN32. 15 30pF Beehive trimmers.

MN33. 20 coil formers, ceramic, plastic,

MN33. 20 con formers, sostalling, read relay etc.
MN34. 25 min. glass reed switch.
MN35. 10 asstd. switches, toggle, slide,

MN36. 10 ex equipment panel lamps (no MN37. 10 asstd. audio connectors. Din

phono etc.

MN38. 1 PCB with triac control IC data

MN39. 1 oscillator PCB loads of components. (no data).

MN40. 50 Polystyrene capacitors. MN41. 10 asstd. T.T.L. I/Cs. MN42. 10 BC107 Transistors.

MN43. 10 BC108 Transistors.
MN44. 10 Screwfix S.P.C.O. min. slide

# CHORDGATE LTD.

75 FARINGDON ROAD, SWINDON, WILTS TEL: SWINDON (0793) 33877

RETAIL SHOP AT ABOVE ADDRESS

PLEASE QUOTE NO. OF PACKS WHEN ORDERING



# Video **Monitors** for CCTV or

Character Display

P4(White) P31(Green) and P39 (Green, Long Persistance) available as standard.

# Monitor Drive Boards

for OEM's available

for both 90° and 110° Tubes.

PHONE OR WRITE FOR DETAILS



# **CROFTON ELECTRONICS**

35 Grosvenor Road, Twickenham Middlesex TW1 4AD.

Telephones: 01 891 1923/1513

#### HAND HELD GAMES

Supersonic Mastermind	£21.00
Galaxy Invaders	£22.95
Mattel Soccer	£21.50
ENTERPRISE 4 in 1	£24.95
3 Games and calculator in one	
*Electronic Mastermind	£12.90
U.F.O. Master Blaster	£24.95
Amaze-A-Tron maze game	£18.95
Touch Me by ATARI (like Simon)	£26.95
Football (two players)	£24.95
ZAP missile game	£11.95
*DIGITS (like Mastermind)	£14.95
Space Invaders	
ALL GAMES HAVE SOUND E	
EVCEDT .	

#### The latest from the U.S.A.

#### PINBALL WIZARD

★ Still available ★
Featured in Nov. issue of E.T.I.
Home TV Game — B/W Kit

Basic Kit **£28.90** 

Contains everything except box and controls

Box & Controls -- £6.50. Mains Adaptor

Play 7 games with 4 options on each

game 4-Pinball games 2-Basket, 1-Breakout

Versatile car alarm kit . . . . £18.90 See review in Hobby Electronics November

CHROMA CHIME 24 tune door chimes kit £10.75 Built £15.95
C.B. Aerials and Accessories

# **ATARI** video

£99.95 computer ..., Sargon 2.5 Chess Super System 3 Chess SPACE INVADERS CART £29.95 STAR CHESS T.V. Game £63.3!
DATABASE Prog. T.V. Game

#### **COMPUTERS** — Home. Business etc.

Videogenie System 16k	£368.00
PET 8K	£458.85
PET 16K	€573.85
CODOFFER A CH	€861.35
SORCERER 32K	
UK 101 Kit 4K	
Built 4K	
	£409.40
	£271.40
Dual Drive	£506.00
NASCOM 2 Kit	£339.25
. HEATH WH89	
	£586.50
Softy Kit	£138.00
Softy Built	
Intelligent EPROM Progr	rammer
1 Sharp Software	
PRINTERS : FLOPPY	DISCS : BOOKS

S.a.e. Enquiries. Please allow up to 21 days for delivery. All prices inc. of VAT.





# Buy at with Access UNIT 5

Day 01-808 0377; Eve 01-889 9736

### **OHIO SCIENTIFIC SUPERBOARDS** WITH 32 x 32 DISPLAYS



CHEAPO EXPANSION OFFER
Buy a 610 expansion board with 8K ram on board and space for another 16K for £159 + 15% and get a free 5V 2A power kit and any extra ram you want for £3.50/K + 15% buy a minifoppy + case + power supply + 2 copies dos for £275 + 15% with the 610 and we will do the extra ram for £2/K + 15% (up to 16K).

Announcing the new 50Hz guard band models with 1.5MHz clocks giving 50% more speed, a full 32 x 32 display and a multi-speed tape

interface.

BLACK AND WHITE £159 + 15% post free

COLOUR VERSION £225 + 15% VAT

THE UNIQUE SPECIAL OFFER YOU CANNOT RESIST

OTHER TOU CANNOT RESIST
If bought with Superboard these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Guard band kit £0 (£8). Modulator and power supply kit £1 (£25). 4K extra ram £20 (£24). Display expansion kit, approx. 30 lines × 54 characters. £16 (£20). Case £23 (£26). Colour conversion board kit £35 (£45) or built £65 (£65). Cassetter excurder £14 (£16). C£6MON improved monitor rom poa. Extended monitor (tape) £20 (£20). Assembler / Editor £25 (£25). Word processor £10 (£10).

#### TV GAMES

1v GAMES AY-3-8550 chip £4.00, kit £5.26. Stunt cycle AY-3-8765 chip + kit £20.95. 10 game paddle 2AY-3-8600 chip £5.95, kit £7.03. Modified shoot kit £5.28. Col-our generator kit £9.95.



MAINS TRANSFORMERS 6.0-6V 100ma 96p, 1½a £3.32. 9-0-9V 75ma 96p, 1a £3.08, 2a £4.93. 12-0-12V 100ma £1.20, 1a £3.70. 15-0-15V £3.98.

JC12 and JC20 integrated circuit audio amplifier chips with data and printed circuits. JC12 6 watts £2.50. JC20 10 watts £3.54.

#### CONTINENTAL SPECIALITIES

PRODUCTS

EXP300 £6.61. EXP350 £3.62. EXP325 £1.84.

EXP650 £4.14. EXP4B £2.64.

STABILIZED POWER KITS
TTL computer supplies 5v 2a £8.38. 5v 4a £14.16.
8-way types 3/4½/6/7½/9/12/15/18v 100 ma.
£3.12. 1a £8. 2a 1£12.11. Variable voltage models
2.18v 100ma £3.12, 1-30v 1a £8.30. 1-30v 2a
£14.82.

#### PRINTED CIRCUIT

MATERIALS
PC etching kits: economy £2.92, standard £5.26, 40
sq in pcb 50p. 1 lb FeC1 £1.70. Etch resist pens:
economy 50p, dalo 90p, drilb bits 1/32nd in or 1mm
35p. Etching dish 92p. Laminate cutter £1.30.

BI-PAK AUDIO MODULES AL30A £4.53. PA12 £9.31. PS12 £1.75. T538 £2.90. S450 £27.90. AL50 £5.62. PA100 £19.24. SPM80 £5.26. BMT80 £6.36. Stereo 30 £24.14.

COMPUTER GAMES
New Sensory Chess Challenger 8 £119. Chess Challenger 7 £79. Chess Champion 6 £49.95. Checker Challenger 2 £33. Star chess £62. Atari Video computer £107. Cartridges £14.85 (except chess £43.95, backgammon £33.95 and space invaders £27.50).

S-DEC AND T-DECS S-Dec £3.79, T-Dec £4.59, 16 dil adaptor £2.31.

COMPONENTS

1N4148 0.9p. 1N4002 3.7p. 2114 memory chips, low current 300ns £3.45. 723 14 dil 36p. NE555 8 dil 7p. 741 8 dil 20p. bc 547. bc548, bc182, bc184, bc212, bc214, 6.1p. tip 32c 43p. tip41c 48p. bd132 32p. Fusso 20mm x 5mm carridge 15, 25, 5, 1, 2, 3, 5a quackblow 2p. Resislors, 5% ½W £12 10R to 10M 1.5p. 0.8p for 50-4 of ner value. Polyester capacitors 160v. 015. 068mf, 2.6p. 047. 1mf 4p. 01mf 3p. 022. 033mf 3.3p. 15, 22, 33mf 4.9p., 47mf 6p. Polystyrene capacitors £12 63v 10 to 1000pf 4p, 1nž to 10 n5 p. Ceramic capacitors 50V £6 p. 25v 5. 10mf 6p, 16v 2, 33mf 6p, 76 68mf 5p, 25v 5. 10mf 6p, 16v 22, 33mf 6p, 76 68mf 5p, 25v 5. 10mf 6p, 16v 22, 33mf 6p, 76 mf 6p; 16v 22, 33mf 6p, 76 mf 7p, 330 470mf 3p. 1000mf 11p. Zeners 400mW £24 2v7 to 33v 7p. Preset pots subministure 0.1W horiz or vert 100 to 2Mz 8p. Potentiometers ½W 4X7 to 2M2 single 29p. dual 71p, ½\* red LE0s 11p. 15 sockets 8 dil 8.7p, 14 dil 10.1p, 16 dil 12p.

**BATTERY ELIMINATORS** BATTERY ELIMINATORS
3-way types with switched output and 4-way multi jack:
3/4½/fb 100ma £2.99, 6/7½/fb 300ma £3.50.
100ma radio types with press-stud connectors 9v
£4.77, 6v £4.77, 4½v £4.77, 9 + 9V £5.99, 6 + 6v
£5.99, 4½ + 4½v £5.99. Cassette recorder mains unit
7½v, 100ma with 5 pin din plug £4.77, £1½ y stabilised type 3/6/7½/g 400ma £7.15. Car converters 12v
dc input, output 7½v 300ma £1.19; output 3/4½/6/7½/9/12v 800ma £3.04.

#### **BATTERY ELIMINATOR KITS**

100ms radio types with press-studs connectors 4½v £1.64, 6v £1.64, 9v £1.64, 4½ + 4½v £2.30, 6 + 6v £2.30, 9 + 9v £2.30, Cassette type 7½v 100ms with din plug £1.64. Heavy duty 13-way types 4½v67/78½v11/13/14/17/21/25/23/34/42 1a £6.32, 2æ £10.86. Car convener input 12v dc, output 67/39 v1 Astabilised £1.62.

#### SINCLAIR PRODUCTS



SC110 10MHz oscilloscope £144.95. PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, adaptor £6.88. PDM35 £34.23, adaptor £4.20, case £2.07. DM350 £85.21, DM450 £109.11, DM235 £59.95. Accessories for all 3 models: rechargeable batteries £7.99, mains adaptor £4.02, case £8.90. Enterprise prog calculator £19.95. TG105 £87. TF200 £150.

#### PRINTERS



The best value in matrix printers and a fantastic cheapo offer to boot. OKI Microline 80 (allustrated): £359 + 15% 8ASE 2 8008 (new improved version at the 800MST) £359 + 15%. BASE 2 850 Model price by secret quotation only. Anacom 150 £899 + 15%. Buy any of the above and we will supply an interface kit and word processor program for Superboard for only £1.

#### THE NEW OHIO SERIES 2 CHALLENGER CIP




Program selectable 24 x 24 or 12 x 48 displays, Sound, music and voice output. 8K ram expandable to 32K. 8K basic. We dare not publish our cheap price for fear of being gunned down in the street by desperate rivals. Send a highly obaque see for a stunning quote from the masters of cheapo and freebie trading. We also stock the CTPMF Sense 2 disc version. Again, secret quotations
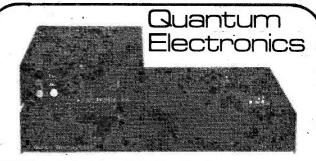
# SWANLEY ELECTRONICS Dept. ETI, 32 Goldsel Rd., Swanley, Kent BR8 8EZ

Telephone Swanley 64851. Please add 40p postage. Prices include VAT unless stated. Lists 27p post free Overseas customers deduct 13%. Official credit orders welcome.






ve, must be the most cost-effective pre-amp available, catering for auxiliary, 2 or 3 head tape and providing a perfect match for any cartridge, moving coil or magnetic, by using our unique low-cost matching card to define the sensitivity and cartridge loading. Prudent choice of components and elegant circuitry give outstanding objective and subjective performance (see Popular Hi-Fi August). The module used in the objective and subjective performance (see Popular Hi-Fi August). The module used in the 102 is available separately, as are suitable mains supplies and moving coil head amp/modules. There are two matching stereo power amp kits which are supplied with built and tested circuit boards, requiring only straightforward assembly and point to point wiring. The new ready-built 'D' versions feature separate d.c. supplies for each channel and other refinements which elevate their performance into the super-fi class but which are not incorporated in the kits. Our power amp modules and supplies below enable an amp of high specification to be constructed.

\* COMING SOON: ACTIVE CROSSOVERS \* 102 pre-amp: module only £63.50; built £92.00

45W channel: kit, P2, £100.50; built, 202D £151.00 110W/channel: kit, P4, £126.00; built, 204D £185.00

#### **POWER AMP MODULES AND SUPPLIES**



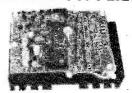

M1504, 1508 £35.79. M3003 £50.28. M854 £26.00. M3008 £53.96. M4002, 5004 £82.60\*

#### 6 NEW MODULES ★ NOW UP TO 500W r.m.s.!

We offer a wide range of modules to suit virtually any application with an honest specification unbeatable at the price. They are available in both the popular medium duty "L' bracket format for up to 300W r.m.s. (M3008, MS6.8ohms) and also in high dissipation versions using various heatsink combinations. Correct choice of modules allows reliable continuous operation at up to 500W r.m.s. (M5004. 1786, 4ohms) without premature cut off or the need for external circuitry. Matching toroidal power supplies with single and deuble d.c. sections are available. Exemplary specifications include l.h.d. less than .01% at 1kHz; 30 V/µS slow rate; moise below 1100B; integrity protected against overload and high d.c. output offset; stable into any load.

#### **★ EXCELLENT TRADE PRICES ★**

### **NEW DELUXE SPEAKER KITS**







£89.00



£159.00



PRICES PER PAIR INC. BAFFLES

Have you wondered why the existing sources of speaker kits offer a bewildering choice of systems, particularly combinations of 200mm bass unit and tweeter? Don't they know which ones are best? If so, why bother with the rest! Well we have sorted out these super kits which ones are best? If so, why bother with the rest! Well we have sorted out these super kits so you can order in confidence, knowing you get our full endorsement of their performance and value. The kits incorporate professionally finished front baffles with the drive units already mounted so all the fiddly work is done for you. All that is left to do is to make a simple box. Crossover networks, foam and terminals are included. Systems 1 and 2 use a 200mm bass and 25mm dome tweeter from Son Audax, System 2 being a reflex design that we enthusiastically recommend. System 3 is a competitive 3-way 1.8 using Seas bass and mid with a Son Audax tweeter, cleverly incorporating a stand at the bottom of the enclosure, as does System 4, undoubtedly the best kit on the market, using a Volt 250mm bass driver with a 250mm ABR on the rear baffle (also supplied), a modified Peciless mid and Son Audax tweeter. We will also be retailing selected drive units at competitive prices, e.g. Son Audax 200mm bass, 20825.4 £13.50; 25mm tweeter. HD100D25. £9.00.

All our prices **include** V.A.T. and delivery. Export no problem — please send for a specific quote by return. All equipment can be wired for 110V mains. Please send a large S.A.E. or dollar bill for our full information and review reprints.

SWEDEN: BLN LJUD Hi-Fi, SÖDRA KASERNGATAN 14 B, S291 33 KRISTIANSTAD U.S.A.: OX DISCO, BOX 123, CLAYMONT, DELAWARE 19703 8 ALBION STREET, LEICESTER. Tel. 546198

#### **RATES**

1-3 insertions £7 per scc 4-11 insertions £6.50 per scc 12 insertions £6 per scc 24p per word (min. 15 words) Box No. of application

All advertisements in this section must be pre-paid

Closing Date: 1st Fri. month preceding publication

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO: ETI CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE.

TEL: 01-437 1002

#### TELEPHONE ANSWERING MACHINES,

Super Phones, Radio Phones, etc. Ring C.W.A.S. 0274 682674.

150 ASSORTED RESISTORS £1. 100 assorted capacitors £1, 100 IN4148 £1. P. and P. 20p. S.a.e. lists of components, mikes, meters. Dept. T, D.B. Products, 1 Holly Tce., York, YO1 4DS

#### Earn £20-£100 p.w. in your spare time

by introducing the revolutionary new Flip-Caller telephone to your friends. Features micro-chip controlled push-button dialling and memory recall. Sells itself. Generous commission. For details write to Dept. ETI

IDL SUPERPHONE P.O. Box 31, Twickenham TW2 5RL



#### COLOUR MODULATOR

- R G B inputs, PAL/UHF output Unflimited colour combinations TTL etc interface details supplied 1000's already in use!

KIT: only £12

Built & Tested: only £18

please add VAT at 15% to all prices Barclay/Access orders accepted by telephone



Dower House, Billericay Road

STUART

SYSTEMS Ltd

Dower House, Billericay Road

Herongate, Brentwood.

SYSTEMS Ltd

Delephone: Brentwood (0277) 810244

**BURGLAR ALARM** Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

£99 SYNTHESISER DIY. Professional results, easy-build. S.a.e. Dewton, 254 Ringwood Road, Ferndown, Dorset BH22

CIRCUIT DESIGN, Prototype construction? Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write\_A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346)

# SHARP COMPUTERS

NEW LOW PRICES
Pocket Computer PC1211, complete with cassette interface. CE 121 £108.95.
MZ80 Computer 2DK £504.85-48K £573.85
MZ80 P3 Line Printer £585.50. MZ80FD Disc Drive MZ80 I/O Expansion Interface £109.25.

**ELKAN ELECTRONICS** 28 Bury New Road, Prestwich Manchester M25 8LD

# TTL CMOS TALS LEDS

# ECT

#### PCB OFFERS

(1A) 100 bit shift register PCB, 115mm × 94mm containing 9 × 7491, 6 × 7496 and 1 × 7441. Terrific bargain 85p, p&p 30p.

Data General Nova 3 PCB 4K
memory £40 each + £2 p&p
MPU CORNER

2122 (200ns), £3. 2114 (450ns)

Texas Instruments. 2716 single rail. Brand new. Full spec. £6.95 each p&p 25p. 2708 (400ns)

MK 1002P (dual 128 bit Shift Reg) 35p. LM711CH (Voltage Comparator)

30p.

(All Full Spec)
2526 Character Generator (64 × 9 × 9) £2.95 + data & p&p 25p.
MM5240 AA/J Character Generator £3.50 + data. p/p

International rectifier SOLID **STATE RELAY** type A2402. Output 240 VAC 2.5 amps input 90-240 VAC/45-200 VDC £6.00

D TYPE CONNECTORS

9 Way: sockets (solder) 55p.
15 Way: wirewrap plugs only 75p.
50 Way: skt (wirewrap) £1.65.
50 Way: kt £1.45, p&p 25p.
25 Way Male to Female with covers plus minimum 1 metre of cable (12 way) £4.00 each p/p

catie (12 mg, 35p, 25 Way plug (solderail), 25 Way socket £1.20 aach.
COVERS
25 Way: 75p (plastic), p&p 25p.
37 Way: 90p (plastic), p&p 25p.
DISPLAYS

DISPLAYS

HP 5082 4 digit DIL display full spec £1.50 each, p&p 25p, Large quantities POA.

MAN 72 7 seg CC £1.25, p&p

**ETI JANUARY 1981** 

MAN /2 / seg CC £1.25, p&p 25p. Burroughs Panaplex 9 Dig. + skt and bezel £1.00, p&p 25p. LED 3 Digit DIL 55p, p&p 25p. Bowmar 9 digit .1 in LED with red bezel. (As used in calculators). £1.00 + 25p p&p

#### SUPERSAVER 1

Ribbon Cable Headers 16 DIL Jermyn, gold plated, with cover 45p, p&p 25p. Ansley Header plugs. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing

type). p/p 25p.
Ansley I/O Header plugs. .1in
26 Way 65p, 26 Way (rightangled) 85p. 40 Way £1.00 p/p

**SUPERSAVER 2** 

SUPERSAVER 2
Tantalum Capacitors 25 volt. 4.7
uF, 14 for £1.00, p&p 25p.
SUPERSAVER 3
PRICE SMASH FND 500 .5in.
LED displays, full spec 50p each,
p&p 25p, large quantities POA.
SUPERSAVER 5
Battery aliminator, BVDC

Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p. SUPERSAVER 6

RS 338-383 Miniature Decade Thumbwheelswitch. £1.65, p&p

SUPERSAVER 7 SN74116 Dual 4 Bit letch 75p,

p&p 25p SN7418 Arithmetic Logic Unit, **80p,** p&p 25p. SN74194 4 Bit Register, **50p** p&p

25p. SN74198 8 Bit Shift Register, **75p** 

SN74198 8 Bit Shift Register, 75p p&p 25p.
SUPERSAVER 8
ITT 4cx 250b brand new full spec £7.50 each p&p 25p.
SUPERSAVER 9
5 digit 7 segment DIL LED \_11" displays 4 for £1.50 p./p 25p.
SUPERSAVER 10

SUPERSAVER 10
9 way male/female connector,
ELCO 8129, 0.1 inch pitch, goldplated PCB mounting, ideal for
bussing two PCBs together.
Super value, 35p, p&p 25p.
SUPERSAVER 11
74LS266 50p, 74LS245 £2.40.
74LS240 £1.00. 74S260 35p.
P&P on all above 25p.

#### **SUPERSAVER 12** TMS 3128NC Static shift register,

£1.50, p&p 25p. **SUPERSAVER 14** 

Recording Designs Ltd digital cassette deck. 50-100 Baud RS232 240V input. A professional superb deck. £58.00, p&p £2.00.

SUPERSAVER 15
5K multiturn trimpots, PCB mounting, per box of 14 £2.50, p&p 25p.

SUPERSAVER 16 Qmax chassis punch 1¼" £3.25, p&p 45p.

LEDs (Full spec.)
TIL209, red 10p. 0.2in, red 12p.
0.2in. green 28p. 0.2in, yellow

28p. RL54 red Axial lead. 15p. P&P on all above 25p.
VERNITRON Ceramic filters type
FM4 10 yMHz 45p, p&p 25p.
TRANSISTORS, BD236 40p,

BC183L 10p, BF195 10p. TBA 810S, with data, 85p, 4-way Dil switches, 75p. MC1303 Dual Stereo preamp with data, £1.25.
7in. Nylon cable ties 100 for £1.50. All p&p 25p.
NEW SN76477 (Yes, back in

stock). Sound Generator IC (Train plane, explosion, laser gun, etc.) with data £3.25, p&p 25p.
PCB KEYBOARD, 65mm ×

82mm, 18 key Clickers less Key tops, ideal Hexadecimal use 35p, p&p 25p. CAPACITOR SCOOP. 1.600uF

at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 + 25p p&p. MINI FANS 80mm × 80mm 115v. Brand new. £4.50

+ £1.00 p&p.
IEC mains chassis plug **75p** suitable socket **35p**, p&p 25p.

GIVEAWAY 22 pin low profile dil socket, gold plated. 12p EACH

SURPLUS EPROMS LINEAR RAMS Just arrived. ITT 2082 Data Just arrived. ITT 2082 Data Modem. Brand new and boxed, with manual. 600/1200 Beud. Data Modem to CC ITT. V24/ RS232C. Channel centre frequencies 1300 and 1700Hz (600 Beud) or 1300 and 2100Hz (1200 Baud). Synchronous or asynchronous operation over 2 or 4 wire, switch or dedicated lines, built in self and lines test functions. Some of the best functions. Some of the best equipment we have ever obtained. £115.00 each, p&p £3.00. (Fraction of original

IC H	OLDERS	(Low-prof	ile)
8 Dil	12p	14 Dil	15p
16 Dil	17p	18 Dil	20p
22 Dil	28p	24 Dil	35p
28 Dil	45p	All p&up	35p

WE STOCK a vast range of TTL, CMOS, some 74LS. MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

#### RELAYS

Banor resettable double pole changeover 12V £1. Both p&p 25p.

CIRCUIT BREAKERS 4450v AC 65v DC 0.5A 50p; ditto 7A 80p, p&p 25p. ALLEN KEYS, 7/16in 5p; 12 for

50p; p&p 25p. ASR33 (with tape punch reader). generally overhauled. £185.00 inc. of VAT.
CENTRONICS 101A Dot Matrix

printer. Fully overhauled. 165 char/sec. £450.00 inc. VAT. Carriage at cost. As above dual headed 300 char/sec £650 inc.

C.P.U. TYPE 10660. These devices are brand new, supplied with comprehensive, data sheet for experimental use or hang them on your Christmas tree! 4 for £1, p&p 25p.

**UXBRIDGE 55399** ICL POWER SUPPLY (exchange units) 240V AC input. Output +24V at 2 amps DC, -24V at 2 amps DC (adjustable to 12V) +5V at 4 amps DC -100V DC and 6.3V AC. £12.00. Callers only.

**TELEPHONE:** 

Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as

shown per item.

FOR THE PROFESSIONAL

USER. CP Clare Keyboard
switches with buttons (blank) 65p

switches with buttons (blank) 65p each pkp, 25p.
BURROUGHS keyboard, 96 key station. On-board crystal and TTL. Brand new and boxed.
500mm × 190mm. At the time of advert no data. No keytops at Clare pender. Reed tches. Bargain £12.00 each, Reed p&p £1.50.
PLEASE DO NOT ORDER GOODS

FROM OLD ADVERTS. PHONE BEFORE ORDERING

**SURPLUS STOCKS** SURPLUS STOCKS
PURCHASED
FOR CASH

LB ELECTRONICS
11 HERCIES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND
All enquiries s.a.e. please

Felephone answering machine service out of business hours. New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays, Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.

ALL PRICES INCLUSIVE OF VAT

UXBRIDGE 55399

All components full spec

#### **MICROS**



21114 21114L 221142 22376 2516(5v) 2532 2508 4027 4116 4027 4116 57109 57161 6011 6011 6011 6011 602 6502 6502 6502 6532 6546 6802 6802 6802 6802 6802 6802 6802 680	23.45 3.75 11.55 12.95 12.95 12.95 14.95 12.95 1	81998 SC/MP2 8080 80886 8155 81LS96 81LS96 81LS97 81LS98 81LS98 81LS98 8212 8212 8212 8251 8253 8255 8257 8259 8678 8259 8678 8259 8678 8259 8678 878 878 878 878 878 878 87	1.80 9.85 5.49 11.85 89.00 11.80 12.80 1.30 1.30 2.45 2.50 4.95 4.95 10.95 4.95 11.96 12.80 1.30 2.45 2.50 4.95 10.95 4.95 10.95 2.95 10.95 2.95 10.95
MC1489 MC14881 MC14411 1702 2101 2102 2111 2112 2114 2114 2142 2376 2513 2516(5v) 2532 2708	3.75 10.40 11.50 6.50 13.95 29.00 6.50	74S287 74S288 74S471 74S472 74S474 8T26 8T28 8T95 8T97 8T98 SC/MP2 8080 8086 8154 8155 81LS95	9.95 5.49 11.95 89.00 11.50 12.50 1.30

#### SOFTWARE

CP/M®

DISK WITH MAN Available on 8" IBM format 6

Ò	5% for TUSCAN
TCL SOFT TCL Disc Bi TCL Pascal	£120/£9
MICROSO	CT

0			CAFEICAE
Basic-80			
Basic Compiler			
Fortran-80			
Cobol-80			£325/£15
Edit 80			£45/£10
Macro 80			£75/£10
MICROPRO			

Word Star£	255/£15
Word-Star/Mail-Merge £	315/£15
Data Star£	1 <b>95/£</b> 25
Word-Master	£75/£15

DIGITAL	R	Ц	Б	E	ρ	V	R	C	н	4	
CP/M 1-4											£75/£18
CP/M 2-2											£95/£18
MAC				,							.£55/£10
SID			,								£45/£10
OTHERS											
KISS											£190/£15
CHINED C	0.0	2	r								C125/C15

	LIBUILIO
SUPER SORT	1 £125/£15
CBASIC 2	£75/£10
Z80 Dev Pack	£50/£12
ZSID	£60/£7
POSTMASTE	R£85/£10
MEDIA	
5% S/Sided D	/D£3.50
" per 10	£29.50
8" S/Sided D/	D £4.50
	£35.00
C12 Data Cass	ettes 50p
CIZ Data Cass	

#### MAIL ORDER TEL & MAIL OF





#### 74LS00

LS00 LS01 LS02 LS03 LS04 LS05 LS08 LS09 LS10 LS11 LS12 LS13 .S14

LS366 LS367 LS368 65 65 180 180 180 185 215 85 140 196 270 230 140 196 150 106 270 LS378 LS379 LS386 LS390 LS395 LS396 LS396 LS396 LS447 LS447 LS490 LS668 LS669 LS669

74XX 74CXX LINEARS Many other types in stock. Tel for details

# **VE HAVE MOVE**

TO OUR NEW CENTRAL LONDON SHOWROOM 59/61 THEOBALDS RD, WC1 TUBE HOLBORN.

#### FLOPPY DISK DRIVES



We sell all you need cased or un-cased. Cables & connectors. Brand

new fully guarar	nteed.
	Price
Single 5 % Drive	£195
Single 8" SA800	£395
Dual 51/4 PSU	£59
Dual 8" PSU	£76
Dual Cabinet & PSU 1x8"	£565
Dual 8" Drive Unit	£945
Dual 51/4 Drive Unit	£440

# A Z80 based S100 Computer

Single board will hold up to 8K RAM, 8K ROM, Video interface Z80 processor — I/O and cassette interface. 5 spare \$100 expansion sockets for memory/disc ex-pansion. System monitor, resident BASIC or CP/M system option. All com-ponents available separately or ready-built NEW LOW PRICES

TUSCAN MAIN BOARD KIT ONLY £235 + VAT SAE FOR DETAILS



SINGLE BOARD

**PERSONAL** 

COMPUTER

### **VIDEO TERMINAL**



24x80 display Pentland Video Terminal full features professional

NEW LOW PRICES

terminal. Full details on request Price £595

# S100 CARDS



16K STATIC KIT with no RAM(2114) £ 62 " 8K RAM " £109 " 16K RAM " £157 ASSM £ 82 £130 £178 £ 48 8K static (16x2114 chips)

BAK DYNAMIC (4116) with 16K RAM with 32K RAM with 48K RAM £149 £189 £165 £205 £245 £229 with 64K RAM £269 £ 16K upgrade 8x4116 £ 16/32K EPROM CARD £285

Without EPROMs 2708/2516 £63 £ 89 FDC DOUBLE DENSITY Double Density for 51/4 or 8" Drives £ -£195

# ALL OUR PRICES EXCLUDE VAT & P/P VAT

QUALITY FOR £ 425



Uses any paper roll, fanfold single sheets, 96 character ASCII, 7 x 7 dot matrix, 50 CPS, RS232 or parallel 1/O.

#### **OK TOOLS**

Full range of wire wrapping accessories & boards & dip jumpers etc. Visit our showroom or send for our catalogue. VERO

# \$100 prototyping boards and full range of accessories.

BOOKS Complete range of microcomputer books and magazines on sale in our showroom.

# CATALOGUE AVAILABLE

Catalogue evallable. Send 50p & S.A.E. (A4 size).


9090 BASED SINGLE BOARD system with EUROCARD **EXPANSION** 

Complete Kit Incl. PSU/Case/Keybd Expansion Motherboard Kit 8K (2114) RAM Card Kit 8K (2708) ROM Card Kit Expandable up to CP/M Disc System. SAE for


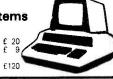
#### TCL PASCAL FOR PET & CP/M systems

Put Pascal on your PET now Pascal conversion ROM Pascal manual Complete package including compiler



Insulation/Piercing
Ribbon/Cables
I/OHEADER PLUG

10 way £2.20 20 way £3.40 26 way £4.00 34 way £4.80 40 way £5.40 50 way £6.50

10 way £1.60 20 way £2.30 26 way £2.70 34 way £3.30 40 way £3.75 50 way £4.60 60 way £6.00



ttoldlitten.		Zero Inser Force Soci	
DIP SV	vitches		£4.95
4 way	£1.20	24 way	
7 way	£1.75	40 way	£6.00 :
8 way	£1 80	D-Type	
DIP	Plugs	25W Male	£2.80
14 D!I	f 65	2EIA/ Enmala	C3 00

8 way DIP Pluge 14 DIL € £ .65 £2.20 £3.60 24 DIL 40 DII

DIL SOCKETS

	Low	Wire
	Prof	Wrap
8pin	10p	26p
14pin	12p	35p
16pin	13p	42p
18pin	16p	60p
20pin		90p
22pin		
24pin		65p
28pin		90p
		1.10p
40pin	-up	i.iup

25W Cover Edge Edge Connectors

2x 6 way	- 1.75	PRI
2x12 way	- 3.00	Grev
2x10 way	- 2.00	10 .65
2x15 way	- 3.20	14 90
2x18 way	- 3.50	16 1.20
2x22 way	3.203.65	20 1.40
2x25 way	3.60	26 1.60
2x30 way	4 15	34 2 40
2x36 way	4.753.90	40 2.80
2x40 way	5.00	503,30
2x43 way	5.504 60	60 4.00
100000-1-1		

insulation Piercing
Edge Connectors
vay £3.60 40 way £5.30
vay £4.00 50 way £6.00 20 way £3.60 26 way £4.00 34 way £4.60 25W Female £3.80

# £2.80 Insulation Piercing £3.80 DIP Plugs £1.80 14 way DIP Plug £ 16 way DIP Plug £ 24 way DIP Plug £

£1.30 £1.50 £2.80 Ribbon Cable PRICE/M Coloured
10
14
16
20
26
34
40
50
4 90 1.20 1.40 1.60 2.40 2.80 3.30 4.00 5.50

# CRYSTALS FOR MICROS

3.00	4.00MHz	2.70	10.00MHz	2.70
3.00	4.43MHz	1.00	10.7MHz	2.70
3.70	5.0MHz	2.70	16,00MHz	2.90
3.60	6.0MHz	2.70	18.00MHz	2 90
3.50	6.144MHz	2.70	18.432	2.90
3.00	7.0MHz	2.70	36MHz	2.90
1.50	7.168MHz	2.50	48.0MHz	2.70
3.05	8.00MHz	2.70	100MHz	2 90
2.70				
	3.00 3.70 3.60 3.50 3.00 1.50 3.05	3.00 4.43MHz 3.70 5.0MHz 3.60 6.0MHz 3.50 6.144MHz 3.00 7.0MHz 1.50 7.168MHz 3.05 8.00MHz	3.00 4.43MHz 1.00 3.70 5.0MHz 2.70 3.60 6.0MHz 2.70 3.50 6.144MHz 2.70 3.00 7.0MHz 2.70 1.50 7.168MHz 2.50 3.05 8.00MHz 2.70	3.00 4.43MHz 1.00 10.7MHz 3.70 5.0MHz 2.70 16.00MHz 3.70 5.0MHz 2.70 18.00MHz 3.50 6.144MHz 2.70 18.432 3.00 7.0MHz 2.70 36MHz 1.50 7.168MHz 2.50 48.0MHz 3.05 8.00MHz 2.70 10.0MHz 2.70 10.0MHz 2.70 10.0MHz 3.05 8.00MHz 2.70 10.0MHz 3.05 8.00MHz 2.70 10.0MHz 3.05 8.00MHz 3.05 8.

59/61 THEOBALDS RD LONDON WC1 TEL: 406 5240/2113 TELEX 444198.

# PRINTED **CIRCUITS**

### HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components Full range of HE printed circuit boards normally existock, same day despatch at competitive prices

Boards to individual designs Resist-coated epoxy glass laminate for the d.i y. man with full processing instructions (nounusual chemicals required)

Alfac range of etch resist transfers, and other drawing materials for pic boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES MASONS ROAD STRATFORD-ON-AVON

WARWICKS, Tel. 4879

ZX80 SPACE INTRUDERS-zap the intruders as they attempt to land, £4. Movies-7x8 character pictures displayed in rapid movement, gives animation effect, £3. Both are continuous programs with no loss of T.V. Sync. Inclusive prices for listing and details, or send s.a.e. for list of all ZX80 Specials to-K. Macdonald, 26 Spiers Close, Knowle, Solihull B93 9ES.

#### XMAS PRESENT FOR ZX80 OWNERS.

Stockmarket, Hangman with unlimited words, day of week, nim and others. 7 programs on cassette for £5, or send s.a.e. for list. -Cadsoft, 24 St. James Street, Cheltenham,

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.75 sq. ft. Post/ packing 60p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.



#### ADAM HALL

Cabinet & Flightcase Fittings, fretcloths. coverings, handles, castors etc., Jacks & sockets, Cannons, Bulgins, reverb trays, Emilar compression drivers, AKG mics, Celestion speakers, ASS glassfibre horns.

Send 30p postal order for illustrated catalogues to:
ADAM HALL (E T SUPPLIES)
Unit B, Charlton Court
Grainger Road, Southend-on-Sea
Essex SS2 5BZ

### LAMP STRINGS

Kit LS-1. Each Kit contains: 200 Lamps (50 each Red, Blue, Yellow, Green). 200 Pre Cut Leads, 400 Sleeves plus Instructions

Easy to Construct. Ideal for

#### DISCOS, SHOPS, DISPLAYS, XMAS DECORATIONS ETC.

£10.00 S-1 c/w Instructions SL-1 100 Spare Lamps (25 each colour) .....£5.75

Prices include VAT and P&P

#### J& HASSOCIATES LTD.

The Maltings **Station Road** Sawbridgeworth, Herts Tel: 0279-723156 Telex: 81675 JLamps-G

Trade Enquiries Invited

A SUPERB VALUE STEREO POWER AMPLIFIER OFFER • Stabilised PSU; 2N 3055 output ● Stereo 60-watt RMS: ● I.C. Preamp. Case includes, controls volume, selector etc., din output/inputs for magnetic pick-up/microphone (3.mv) + Tuner + Tape/Aux. 26 transistors — 2 IC Screened Douglas Transformer, 240V AC mains lead. New—tested—data £19.95 (inclusive).— Klifco Electronics, 1 Regent Road, Ilkley, W. Yorkshire LS29 9EA.

ZX80 BUILT BY SINCLAIR. Complete with manual and power supply. Cost £110, only £85. Must sell because of new Micron. — Phone Geoff Peach, evenirigs, 01-804 0642 (Enfield)

NASCOM OWNERS - 16 gauge Aluminium Console, will support portable T.V. or monitor. Enough space inside for 3A PSU, CPU Board and two expansion boards. Size 14" x 20" x 3" with sloping front for keyboard. Price includes keyboard cut-out, rubber feet, carry handle. Send cheques or P.O.s for £25.30 to — Cyber Electronics Co. Ltd., Pavement Square, Addiscombe, Croydon CRO 6RD. Tel. 01-651 0388, any time.

#### **DIGITAL WATCH BATTERY** REPLACEMENT KIT



These watches all require battery These watches all require battery topwer cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screw-driver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement hatteries. then supply replacement batteries
you lit them. Begin now. Send
for complete kit and get into a
fast-growing business. Prompt

**BOLSTER INSTRUMENT CO. (ET20)** 

11 Percy Avenue, Ashford, Middx. TW15 2PB



STABILISED POWER SUPPLIES. Variable 5-15V, 1A, Encased, Require leads, £8, Mains Transformers 9-21V. 10A. £6. Used room thermostats £1. P.&P. £1.50 per item.—D. Hingston, 12 Meadow Lane, Westbury, Wilts. Tel. 823726.

GENTLEMAN SEEKS MANUFACTURER for two patented inventions: Electronic football pools forecaster and electronic chord finder, Box No. 202, ETI, 145 Charing Cross Road, London, WC2H OEE.

**NUCLEAR RADIATION MONITOR. Es**sential for the survivor of a nuclear attack. Measures up to 100 rads/hour. S.a.e. details: Ray Nucleonics, 13 Rosemead Gardens, Brentwood CM13 1HZ.

PROGRAMMING, SINGLE/TRIPLE RAIL UVEPROMs. £3/1K. 2516 (2716) 2708, 2532, 2758, 2508, 2704. Petron Electronics, Dept. E, 1 Courtlands Road, Newton Abbot, Devon, TQ12 2JA.

U.V. EPROMS, 1024 x 8 type 2708. Full specification devices, with data. £3.50 each, four or more only £3.25. Post free. S.A.E. for details. Box No. 203, ETI, 145 Charing Cross Road, London WC2H OEE.

# CENTURION

**BURGLAR ALARM EQUIPMENT** AT UNBEATABLE VALUE JUST LOOK!

Order No

100 ALARM TRIGGER MODULE. 100% Solid State. Battery operation. Pos. & Neg. Rings. N. C for 4-wire contacts. N/O for Mots. etc. One Amp Switching Capacity Only. £9.95.
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT— &1.50.
220 Surface 4-wire MAGNETIC REED CONTACT— &1.50.
220 Surface 4-wire MAGNETIC REED CONTACT— &1.50.
220 PRESSURE MAT. Standard size 4-wire 30"x16" £1.73.
260 VIBRATION DETECTOR, Pendulum type in Ivory Case with contacted Lid 4-self-adhesive backing. Adjustable sensitivity £3.50.
380 SIX INCH UNDER DOME BELL.
390 BEST OUALITY BELL HOUSING. PVC coated metal, not to be confused with the cheaper decry covers. Fully signwritten with our Centurion Insignia. 400 DECOY P.V.C. BELL COVEN
NEW TWO-TONE U.S.A. POLICE SOUNDERS, complete with
reathermof hor £14.50 weatherproof horn
SOUNDER PCB Module, only
WEATHERPROOF Louspeaker, 8 ohm horn, only Note. All equipment operates on 12 Volts DC. Terme: Add 15% VAT to Prices + 60p Postage & Packing No Minimum Order.
Access telephone orders Welcome on:
0484-35527 or send
5.A,E. for Full List to:
CENTURION ALARMS & ELECTRONIC SALES, Dept. ETI, 265 Wakefield Road, Huddersfield, W. Yorks HD5 9BE.

# **PANELS**

Give your project the professional finish it deserves. Blend in with existing equipment with these tough 2mm thick anodised aluminium fascia panels, matt black or brushed silver finish. Stock sizes:  $44 \times 16$  cm £4.75,  $35 \times 15$  cm £4.25, 30 × 12 cm £3.90. Other sizes available in quantity to order. Prices incl. c.w.o.

#### PROJECT FINISHERS

P.O. Box 2, Buntingford, Herts

#### TIME EXACT?

MSF CLOCK is ALWAYS CORRECT-never gains or MSF CLOCK is ALWAYS CORRECT—never gains or loses, self-setting at switch-on. 8 digits show Date, Hours, Minutes and Seconds, auto. GMT/BST and Leap Year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, ABSOLUTE TIME, £54.80.
V.L.F.? EXPLORE 10-150KHz, Receiver, £13.70.
60KHz. RUGBY RECEIVER, as in MSF Clock, serial data and audio outputs, £15.70.
Each fun-to-build kit includes all parts, printed circuit.

Each fun-to-build kit includes all parts, printed circuit case, instructions, postage, etc., money-back assurance, so GET one NOW.

nce, so GET one NOW.

CAMBRIDGE KITS

45 (TN) Old School Lane, Milton, Cambridge

# C.B.S.

If you are in Business and considering an application of a Minicomputer or Microproces sor based System and are a little confused why not attend one of our courses

- Microcomputer Application BUSINESS
- Microcomputer Application ENGINEERING AND CONTROL
- Programming in BASIC INTRODUC-O. ТІОЙ
- Programming in BASIC ADVANCED

We are an independent consultative organisation specialising in business and engineering application, prepared to recommend systems when required and provide full software and programming support.

Courses are available for individual or group instruction, and may be arranged to suit your specific applications.

For full details and dates available write or

#### CLEVELAND **BUSINESS SERVICES**

**Cleveland House** Routh, Near Beverley North Humberside HU17 9SR Tel: Leven 0401-43139

#### SPEED - VERSATILITY - ECONOMY



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUMNER is used by hobbylsts, students, technicians, designers and engineers, to carry out work on:—P.C.B. REPAIRS \*ANALOGUE BREADBOARDIMS \*SIMPLE LOGIC WIRING \*COMPLEX INTERCONNECTING OF MICROS AND MEMORIES

AND MEMORIES.

EURO INTROXIT £16.70. PORJECT KIT £8.18.

MINIKIT (A) £7. PENCIL WITH LOADED OSE BOBBIN £2.81 WITH T.C.W. BOBBIN £2.76. STRIPS. GLUE FIX 20.7 PKT. 6" LONG £3.20. HIGH DENSITY GLUEFIX 20.7 PKT. 6" LONG £3.20. PRESS FIX 20.7 PKT. £3.20. SINGLE HIGH DENSITY D-SIDED EUROCARD £5.18. SINGLE SIDED £3.80. DOUBLE HIGH DENSITY D-SIDED EUROCARD £8.60. PROJECT CARD £2.50. BOBBINS: BLUE 4/PKT. £2.12. GREEN 4/PKT. £2.12. GOLD 4/PKT. £2.12. INK 4/PKT. £2.12. OF EACH-COLOUR £2.20. TINNED COPPER 2/PKT. 60.96. AD 150 PKT. 22.7kT. £0.96. ADHESIVE £0.41. SOLDERING IRON
420°C £5.52. REPLACEMENT WELLER TIPS — PTAA8
430°C £1.40. PTAA9 480°C £1.40.
Please add 40p for P&P + VAT to all orders
FOR FURTHER INFORMATION ON

ROADRUNNER PRODUCTS SEND LARGE S.A.E. TO

J. BRINE ASSOCIATES FREEPOST, Haslemere, Surrey GU27 3BL



TELEPHONE ANSWERING MACHINE. Build your own for under £10 plus any Cassette Recorder. Send £3 for circuit and plans. S. D. Cross, 24 Thorney Road, Streetly, Sutton Coldfield, West Midlands.

**DIGISCOPE DS2 LOGIC MONITORS. 16** channel CMOS/TTL, £27.40. Free leaflet: J. E. Sinclare & Co., 82 Plumstead Common Road SE18 3RE

# £1 BARGAIN PACKS All packs £1 each; any 12 for £10. Post 25p. All

top-grade new com PC1 12 BC107 PC2 14 BC108 - no rubbish PC10 15 0.1/35V tants PC10 15 0.1/35V tants PC11 14 3mm red LEDs PC12 12 5mm red LEDs PC13 8 741 PC14 6 555 PC3 12BBC109 PC4 3 2N3055 PC5 7 BFY51 PC6 16 BC182 PC7 60 1N4148

PC15 15 12V zeners PC16 100 1k ¼W 5% Rs PC8 25 1N4003 Send S.A.E. for 8-page list/enquiries. Mail only.
PC ELECTRONICS, 1 Thombill, Romany Road
Whiteparish, Salisbury, SP5 2SD

EFFECTS UNITS FOR GUITAR, Keyboards and vocals. A.D.T. Chorus £44.25. Flanger £36.75. Phaser £27.75. Fuzz-Overdrive £21.75. Echo-Analog Delay £48.75. For details send S.A.E. to Druzyc-Taylor Electronics, 148 Coventry Road, Warwick, CU34 5HL. Tel: (0926) 499300.

FREQUENCY COUNTER TIMER, 1Hz-50MHz £60 ono. Teletext Decoder Bk/w display, not remote control. Plugs into aerial £100 o.n.o. Crawley, Sussex 884606.

U.K. AIRPORT FREQUENCIES LIST. £1. U.K. coast station frequencies list £1. PLH Electronics, 20 Vallis Road, Frome, Somer-

PARAPHYSICS JOURNAL. Russian / Czech translations. Autogenics (self-training) improves vitality. Psychotronic Generators, UFOs, contacting extraterrestrials, Kirklianography, telelinesis, levitation, gravity lasers. S.A.E. 4x9": Paralab, Downton, Wilts.

# **ETI ADVERTISEMENT INDEX**

ć	AITKEN BROS	86
	ALTEK INSTRUMENTS	42
	AMBIT INTERNATIONAL	53
	AMBIT INTERNATIONAL AUDIO ELECTRONICS 14, 28 & AURA SOUNDS	42
	AURA SOUNDS	85
	RAYDIS	22
	BI-PAK SEMICONDUCTORS	48
	BI-PAK SEMICONDUCTORS BK ELECTRONICS	71
	BNRSBOSS INDUSTRIAL	41
	BOSS INDUSTRIAL	47
	BUTTERWORTHS	76
	CALCULATOR SALES & SERVICE 1	116
	CAMBRIDGE LEARNING	69
	CASTLE ELECTRONICS	16
	CHILTMEAD	61
	CHORDGATE 1	116
	CHROMASONICS 46 &	47
	CHILTMEAD CHORDGATE CHROMASONICS 46 & CHROMATRONICS	7
	CLEF PRODUCTS 1	14
	CONFEREN	0.7
	COMP, COMP, COMP . 122 & 1	23
	CRIMSON ELEKTRIK 1	07
	COMP, COMP 122 & 1 CRIMSON ELEKTRIK 122 & 1 CROFTON ELECTRONICS 1	17
	L.S.C	39
	DELTA TECH & CO 1	13
	DISPLAY ELECTRONICS	40
	DORAM ELECTRONICS	75
	EDA	33
	ELECTRONIZE DESIGN	42
	ELECTRO SUPPLIES	60
	ELECTROVALUE 1	00
	ELECTROVALUE	12
	GENERAL NORTHERN MICROCO	M-
	PUTERS	
	GREENBANK	87
(	GREENWELD 1	16
	HAPPY MEMORIES	60
	HEATH ELECTRONICS	86
١	HENRY'S RADIO 52.60.1	01
ĺ	ics	93
1	ICS	70
ì	KEELMORE LTD 1	06
i	KEELMORE LTD 1 LB ELECTRONICS 1	19

INICIALITADEY
L&BELECTRONICS 106
L & B ELECTRONICS 106 LINSAC 107
MACI IN ZAND 27
MANOR SUPPLIES 107
MANOR SUPPLIES 107 MAPLIN 124
MARSHALLS 52
MARLIN       124         MARSHALLS       52         MAYWARE LTD       70         MICROCIRCUITS       99
MICROCIRCUITS 99
MICRODIGITAL 14
MICROTYPE 108
MINKITS 70
MINIM AUDIO 93
MITRAD 34 & 35
MOUNTAINDENE 103
NIC MODELS 117
PARNDON ELECTRONICS 112
T. POWELL 93
T. POWELL 93 POWERTRAIN 2, 8 & 115
PROGRESSIVE RADIO 114
PROGRESSIVE RADIO 114 PROTON ELECTRONICS 113 QUANTUM ELECTRONICS 118
QUANTUM ELECTRONICS 118
RAPID ELECTRONICS 100
J. W. RIMMER 76
J. W. RIMMER
R.T.V.C 10
SAXON ENTERTAINMENTS 100
SAXON ENTERTAINMENTS 100 SCIENCE OF CAMBRIDGE 4 & 5
SILICA SHOP 108
SIIDFTDON SVSTEMS 110
SWANLEY ELECTRONICS 117
SWANLEY ELECTRONICS 117 TANGERINE 94 & 95
TECHNOMATIC 26
TEMPUS 56
TIMEDATA 113
TK ELECTRONICS 104
TIMEDATA
UNILAB 113
VIDEOTONE
WATFORD ELECTRONICS 6 & 7
WEST HYDE DEVELOPMENTS 105 WILMSLOW AUDIO 108
WILMSLOW AUDIO 108

#### **NEW REDUCED PRICES** 8K £399 16K £499 VAT 32K £599

RRP £795 for 32K

Very popular for The PEDIGREE PETS home & busine 8K Microsoft Basic in ROM 8K Pet 32K & 16K, with home & business new improved keyboard. All with green screen

Cassette Deck £55 extra Full range of software available

Interface PET IEEE — Centronics Parallel
Decoded £77.00 + VAT

### NOW IN STOCK **SUPER 80 COLUMN PET**

only £825 + VAT

#### PECIAL GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only £299 + VAT Interface Cards £49

Full Pet Graphics including cables. Ready to go. EX-STOCK.

Interfaces with APPLE, PET, EXIDY, TRS80, COMPUKIT and NASCOM.

# NASCOM 2 DISC DRIVES Add a powerful, double density, mini floppy disc to your Nascom system. your Nascom system. Disc Controller Card (includes Nasbus 6 S100 interface Will-control 4 Drives. CPM operating system. Extended Disc Basic Est. Power supply included One Disc System - £499 + VAT Additional Disc Unit - £299 + VAT

#### **NASCOM 2 GAMES TAPE**

featuring Space Invaders and Android Nim, Re-numbering program and other goodies!

£7.50 + VAT

### NEC SPINWRITER

only £1490 + VAT



NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel, giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds. 55 characters per second bidirectional printing — with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.



### TEAC DISK DRIVES

- TEAC FD-50A has 40 tracks giving 125K. Bytes unformatted single density capacity. The FD-50A can be used in gouble density recording
- mode.
  The FD-50A is Shugart SA400 interface compatible.
  Directly compatible with Tandy TRS80 expansion interface. Also interfaces with Video Genie, SWTP, Heathkit,
- North Star Horizon, Superbrain, Nascom, etc, etc.
  Address selection for Daisy chaining up to 4 Disks.
  Disks plus power supply housed in an attractive grey

Disk Drive £389 + VAT Disk Drive £225 + VAT

#### **COMP POCKET COMPUTER GREATEST BREAKTHROUGH**

£99.90 + VAT

YET

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

● Programs in BASIC ● "QWERTY" Alphabetic Keyboard ● 1.9K Random Access Memory ● Long Battery Life.

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24-character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing hatteries. Automatic statement compaction squeezes every batteries. Automatic statement compaction squeezes every batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

Program Program Each £13.95 Real Estate F8.95 Business Statistics Business Financial Personal Financial £10.95 £10.95 £10.95 Civil Engineering £13.95 £13.95 £13.95 £8.95 Aviation Math Drill



**ACULAB FLOPPY** TAPE
The tape that behaves

like a disc, for TRS-80 LEVEL 2.

Hard Disc

multi-user

DOS

only £169 + VAT

Connects directly to TRS-80 Level 2 Keyboard. Operating and file handling software in ROM, 8 commands add 12 powerful functions to Level 2 BASIC.

#### YOU NEED NEVER MISS AN IMPORTANT CALL AGAIN TWO CORDLESS TELEPHONE SYSTEMS - DIRECT FROM USA



#### THE ALCOM

only £147 + VAT

Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling — Bleeps when call arriving — Nicad rechargeable batteries. Charger in base unit



#### **LOW COST TELEPHONE ANSWERING MACHINE**

£99.95

Microprocessor controlled answering machine. Plug into your pitone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

# 26 megaioyte 4444444 # 0 E

1 DISK

**EXPANSION** 

Room for 3

500K per Drive gives

total of 1.5M Byte - 1 Drive

plus Cabinet £799 + VAT

COMMERCIAL . EXPANDABLE . COMPLETE TRS 80 · MODEL II COMING

TRS 80 • MODEL II

This new unit from the world's most successful micro company is now available immediately with software.

The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another ½ million extra characters including the disc operating system. More disc expansion is now available.

The Model'II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic.

A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation.

Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can op-rate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

64K 1-Disk Model II £1995.00 VAI

BRP £2250.00

CP/M2 £95.00 CIS COBOL £400.00 FORTRAN £220.00 WORDSTAR £255.00 C BASIC £75.00 M BASIC £155.00

£12.50 + VAT **EPROM 2716** 

**WE USE THIS** MACHINE IN OUR BUSINESS



Fully converted to UK T V Standard Comes complete with easy to follow manuals UK Power Supply Casseste Leads Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available.

Interface to Centronics Parallel for TRS80 £75.00 + VAT

only **£295** - VAT **TRS80** Expand your TRS80 by 32K Memory on board **EXPANSION** INTERFACE Centronics parallel port Disk controller card. Real time clock. Requires Level If Basic. Interface for 2 cassette decks. complete

with power supply







Super Quality — Low cost printer. Tractor Feed with full 96 ASCII character set. Accepts RS232C at band rates between 100 and 9600 and Parallel Bit data.

Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, Compukit etc.



 Bi-directional printing Up to 220 chars/line with 4 print densities ● 500 char buffer

 RS232C and Centronics Parallel interface built in Full software control of matrix

needles allowing graphics capability

200 chars/sec • Adjustable width tractor feed.

All this for only £895 + VAT.

#### THE ATARI VIDEO COMPUTER **GAMES SYSTEM**

Atari's Video Computer System [83,00] now offers more \* than 1300 different game variations and options in twenty Game Program<sup>TM</sup> cartridges! Most Cartriages only £13.90 + VA

Prices may vary with special editions Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar,, Video Divmpics, Outlaw, Basketball Hunt & Score\*, Space War, Sky Diver, Air Sea Battle, Codebreaker\*, Miniature Golf.

\*Keyboard Controllers - £16.90 + VAT Extra Paddle Controllers
- £14.90 + VAT SPACE INVADERS NOW IN STOCK £25

# EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

★ 6502 based system — best value for money on the market. ★ Powerful 8K Basic — Fastest around ★ Full Owerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then this is the machine for you.

40 pin Expansion Jumper Cable for Compukit expansion £8.50 + VAT

Build, Understand and Program your own Computer for only a small outlay.

KIT ONLY £179 + VAT NO EXTRAS NEEDED

Available ready assembled, tested & ready to go £229 + VAT

#### **NEW MONITOR FOR COMPUKIT UK101**

In 2K Eprom 2716 ● Allows screen editing
 Saves data on tape
 Flashing cursor
 Text scrolls down
 £22.00 + VAT

#### FOR THE COMPUNIT

Assembler/Editor	£14.90	1. Four G
Screen Editor Tape	£5.90	2. Four C

All Prices exclusive VAT

	Super S	
Game Packs		
£5.00	Chequer	
£5.00	Real Tin	
£5.00	Case for	
	£5.00	

Super Space Invaders (8K)	£6.50
Space Invaders	£5.00
Chequers	£3.00
Real Time Clock	£3.00
Case for Compukit	£29.50



#### HITACHI **PROFESSIONAL MONITORS**

9" - £129 £99.95 12" - £199 £149

 Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability.
 500 lines horizontal resolution
 Horizontal resolution in excess of 500 lines is resolution Horizontal resolution in excess of 500 lines is achieved in picture center. • Stable picture Even played back pictures of VTR can be displayed without jittering. • Looping video input Video input can be looped through with built-in termination switch. • External sync operation (available as option for U and C types) • Compact construction Two monitors are mountable side by side in a standard 19-inch rack.

#### **MEMORY UPGRADES**

16K (8 x 4116) £29.90 +VAT 4K Compukit (8 x 2114) £29.90 +VAT

#### **ENGLISH COLOUR TV/ AMERICAN NTSC** COLOUR MONITOR

Suitable for Apple, Atari and Texas 99/4 £295 +VAT

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes	10 for £4.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Discs 5¼" Hard and Soft Sectored	€3.50
Floppy Disc Library Case 5¼"	£3.50
Verocases for Nascom 1 & 2 etc.	£24.90
Keyboard Cases	£9.90

#### SPECIAL OFFER

We will part exchange your Sinclair ZX80 for any of our products.

Refurbished ZX80's—fully guaranteed £69.90 (Supply dependant upon stocks).

We have one of the largest collections of Computer Books under one roof, along with racks of software for the PET and TRS80.

Come and see for yourself.

# TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinbáll games and lots of options. Good kit for up-grading old amusement

games.

MINI KIT — PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct. £14.90 + VAT and de-code chip. Very simple to construct. £14.9

OR PCB £2.90 MAIN LSI £8.50 Both plus VAT



#### WE ARE NOW STOCKING THE APPLE II EUROPLUS AT REDUCED PRICES



16K £599 32K £649 48K £659

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too ecause of built-in features like:

because of built-in features like:

BASIC — The Language that Makes Programming Fun.

High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays. Sound Capability that Brings Programs to Life. Hand Controls for Games and Other Human-Input Applications. Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package. Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a comblete, ready-to-run computer. Just connect it to a video

complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.



SHOWROOM & **SALES CENTRE AT** 

311 Edgware Road, London W2. Telephone: 01-441 2922

We give a full one year's warranty on all our products.

5,60

# SPECIAL-ONCE IN A LIFETIME OFFER!

16K £399 32K **£449** ≸ 48K £499

RRP f740

**EXIDY** SORCERER

For Personal or Business Use.
32K or 48K memory. 8K Microsoft Basic in ROM. D Cassette I/O, RS232 I/O. Parallel I/O (Centronic Expansion available through optional extra S Motherboard. 69 Key keyboard including 16 key numeric pad.

"Europes Largest Discount Personal Computer Stores

Please add VAT to all prices - including delivery. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

#### MAIL ORDER AND SHOP:

14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station — Moorgate Line).
Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G

#### **NEW WEST END SHOWROOM:**

311 Edgware Road, London W2. Telephone: 01-262 0387

OPEN - 10am - 7pm - Monday to Saturday

# IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933

\*\*COMPSHOP USA, 1348 East Edinger, Santa Ana, California, Zip Code 92705.
Telephone: 0101 714 5472526















# Compu-copy


R ank Xerox's new baby, the Xerox 9700, offers the first direct link between computers and the xerographic process. From a digital input, the 9700 can simultaneously produce a business form and the computer-generated text to go on the form.

The input data can be received on-line from an IBM mainframe or off-line via nine-track magnetic tape. Laser technology converts this data into the selected typeface. At the same time, the standard letter or form is called from memory and the two combined, using the same process, printing on both sides of the paper at the rate of two copies per second. Output on A4 paper can be vertical or horizontal, as necessary.

A variety of standard type sizes and faces are available, but the 9700 can also print company logos, signatures and any other shape that can be converted into a digital code using the 90,000 dots per square inch printing format.

Graham Clark, Managing Director of Rank Xerox (UK), said that he hoped to see 100 of the 9700s installed in the UK within three years. Xerox believe a 9700 installation to be feasible in applications where computer technology is linked to a demand for more than 700,000 high quality prints per month.

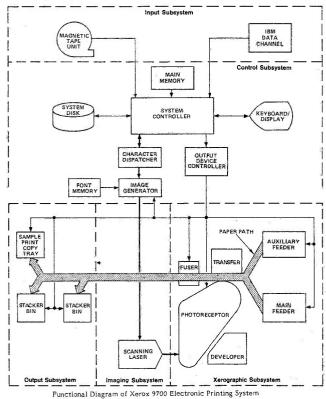
The system will be available with a range of software for sale, lease or rental, a 24 hour service support and free operator training from January 1st 1981. The minimum sale price will be £184,650 and rental options from £5,900 per month-(including 700,000 impressions).



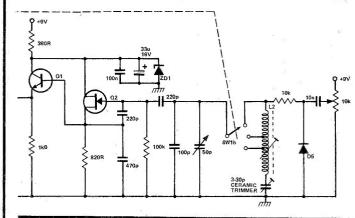
# OOPS Tech-Tips

ast month you may have noticed that the circuit diagram for the Direct-Conversion Receiver made a

brave attempt to escape off the edge of the page. We've reprinted the offending end of the diagram, which also shows the values of the capacitors in parallel with ZD1 and a recommended change to the capacitor in series with coil L2.



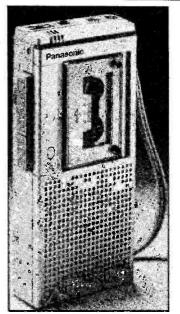

# **Micro-Taping**

panasonic Business Equipment has announced the introduction of the Panasonic RN-Z01, a new low-priced, mains/battery, two-speed microcassette recorder. Features include one-touch recording with cue and review controls, which allow the tape to be rewound or played on to locate a particular piece of recording. There is also a 'follow-up' feature, which lets you start recording during playback without having to stop the recorder first.


The RN-Z01 measures only 14.25 x 64 x 2.58 cm, weighs only 270 g, is fully compatible with the Panasonic RN-195 transcription machine and comes complete with a cassette and carrying case for only £49.42 plus VAT. It is only available through distributors of Panasonic Business Equipment. For details of local stockists contact Panasonic Business Equipment Ltd, 9 Connaught Street, London W2.

# **Colour Tuning**

Mitsubishi Electric have introduced a new FM/LW/MW tuner, the DA-F630, with an unusual method of tuning indication. When you tune into a mono station, the scale illumination changes from white to orange. When you tune into a stereo station it changes from white to green. As soon as you let go of the tuning control, a locking circuit automatically engages to prevent drift.

The front panel features softtouch switching for MW, LW, FM, muting/mode and power, a five-LED signal strength indicator and a single tuning LED.

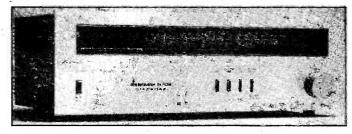Sensitivity (FM stereo, 40 kHz dev) is 16 uV, S/N (stereo, 40 kHz unweighted) is 70 dB, THD (stereo, 1 kHz, 40 kHz dev) is 0.4% and frequency response is 40 Hz to 15 kHz (± 3 dB). The DA-F630 measures 42.4 x 14 x 25 cm.





\*includes delivery within Mainland U.K. \*includes 12 months guarantee. \* tested before despatch


\*bona fide official orders welcome

Prices.	Nett	VAT	Total
MZ 80k Computer 48k RAM	460.00	69.00	529.00
MZ 801/0 Interface unit	82.00	12.30	94.30
MZ 80 FD Dual Disk Drive	650.00	97.50	747.50
MZ 80 P3 Printer	430.00	64.50	494.50
CP/M Operating System	200.00	30.00	230.00
PC 1211 Pocket Computer	82.00	12.30	94.30
CE 121 Cassette Interface	12.00	1.80	13.80
ledger and stock control available fr	ee with full s	ystem pu	rchases.

I enclose cheque	e/P.O. for:
Access	5224
Barclaycard	4929
Name	
Address:	
	Post Code
Goods required	
24 Hour - 7 [	Day ANSAPHONE SERVICE on 051-236 0707
(a) (b)	BARCACOR S
CRA	COMPANY
AILERS	Mail Orders to:
25 BRUNSWICH LIVERPOOL L2	OPJ. FREEPOST (No stamp required)
25 BRUNSWICH	STREET, Mail Orders to: MICRODIGITAL LIMITED FREEPOST (No stamp required)

# **QUALITY DOES NOT HAVE** TO COST VERY MUCH! INCLUDE

# BECKER Hi-Fi Speakers

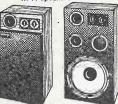

# VAT All models multi-speaker systems

With controls, attractive woodgrain finish.

RMS ratings for 8 ohm.

10.35 10" 3 speaker system 35 watts 23"

× 13" × 10½" €79.95 pair

12.45 12" 4 speaker system 45 watts

26½" × 14½" × 11" €89.95 pair

12.60 12" 4 speaker system 60 watts

26½" × 14½ × 11" €115.95 pair


15.90 15" 5 speaker system 90 watts 28"

× 17½" × 11½" €135.95 pair

(UK c) €5.45 pair).

■ Demoestration to callers.

On Demonstration to callers.

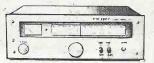

# **SCOTT T516 STEREO** FM/AM TUNER

HIGH QUALITY STEREO FM/AM TUNER BY SCOTT OF USA.

Overall size 5" x 141/2" x 12". Brand new and fully guaranteed at a special low price. (C/P £1.55)

£38.95 On demonstration for catters.




# JVC BELT DRIVE TURNTABLE

JVC TURNTABLE WITH FREE AUDIO TECHNICA AT 100 STEREO CARTRIDGE.

- 'S' shaped tone arm ★ Belt drive ★ 12" Platter ★ Calibrated counter-balance
- weight
   ★ Anti-static device

£29.95 (C/P £1.55)

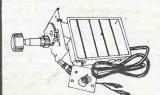

# TV SOUND FROM YOUR HI-FI

High quality TV sound converter plags into aerial socket of your FM tuner. 9 volt battery operated (battery not supplied). Nothing to look at . . . but just listen

On Demonstration for callers.
(As reviewed in 'Popular Hi-Fi July 1979) £8.50



1000's SOLD





Professional sound hi-fi speaker kits with high sensitivity (89-92dB). Extended frequency response (223 50-20kHz. 253 35-25kHz). Designed and made in Scandinavia to the highest quality. All supplied with complete cabinet plans, tweeters/ crossovers/leads etc. \* On Demonstration to

- ★ Hi-Fi 223, 30/45 watt 3 speaker 8" system
- \* Hi-Fi 253. 60/100 watt 3 speaker 8" system

  £34.50 pair

  £34.50 each

  Hi-Fi 403. 60/100 watt 3 speaker 10" system
- E44.50 each
  Hi-Fi 603. 80/150 watt 3 speaker 12" system
  E64.50 each

(UK C/P £2.50) COMPLETE RANGE OF SEAS CHASSIS SPEAKERS ETC ALWAYS IN STOCK ALSO STOCKISTS FOR AUDAX, GOODMANS, KEF, PEERLESS ETC.

# **PIEZO TWEETERS**





Clean sound, very low distortion tweeters. No crossover required. Suitable up to 100 watts — more in series.

- n series.
  Mid-range horn for disco/pa/groups ...
  Z Tweeter horn for hi-fi/disco/pa ..... £6.95 £4.40 £3.50 3 Popular hi-fi and disco ..... C/P 50p (up to 4 items)
- STEREO ACCESSORIES
- 1987 Hi-Fi Frequency Equaliser .... £49.95
- APM 200 Peak programme meter (twin scale)
   S39.95

   MS3219 Twin Scale audio output meter £12.95

   MC350 Tape echo chamber £58.95

# **FREE CATALOGUE**

Large range of speakers/stereophones/mixers/PA equipment etc - and much morel Plus huge range of test equipment.
ALL PRICES INCLUDE VAT SEND LARGE 171/2p SAE ALL PRICES CORRECT AT 1,12.80 E&OE

# ELECTRONICS Cubegate Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564 OPEN 9-6 Mon-Sat

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS OR CALL IN AND SEE FOR YOURSELF





# **IR Beam Alarm**

Our IR Beam Alarm features a dual beam IR link. The two beams, a few inches apart, must be broken simultaneously to activate the alarm. So, you won't have any false-triggering problems when a fly lands on the transmitter or receiver. Mind you, if you are visited by the East Lothian formation fly ensemble, you've got problems. The link will operate over 10m range and could form the basis of a comprehensive house alarm system.

# **Digital Designers' Circuit** Supplement

Only 10 years ago, relatively simple digital circuits occupied acres of boards bristling with components. Now, very often, there's a single, special-purpose chip to do it all. Even if there isn't, a microprocessor can handle most contingencies. So. digital designers face increasingly complex problems as more and more functions are condensed into chip-size logic. Tim Orr's Digital Designers' Circuit Supplement starts you off on the road to making sense of it all.

# **Drum Sequencer**

If you need a lot of banging in your life (perhaps you're a musician), try your hand at the ETI Drum Sequencer. It's designed in two distinct sections. The drum effects unit will simulate high/low tom-tom and bass and snare drum voices, manually triggered by, say, a loudspeaker sensor. The clever bit is the sequential programmer, which will reproduce the drum rhythm of your choice from the effects unit.

# **Crystal Calibrator**

If you need a frequency standard for calibration purposes anywhere in the 100 Hz to 1 MHz range, then you need the February issue of ETI. Our Crystal Calibrator lets you determine the frequency of an unknown crystal or produce an accurate calibration signal for setting up and test applications — a useful piece of test gear.

# **SPL** Meter


For the first time in a UK electronics magazine, ETI features an accurate, calibrated Sound Pressure Level Meter design based on a special-purpose, but modestly priced, precision microphone insert.

Use it to check absolute values of sound level or loudness at home or work — Crossroads at 96dB can damage your health! Use it to set up the graphic equaliser in your hi-fi system - check that sound levels at all frequencies are equal in your deep-pile, luxuriously upholstered, sound absorbing penthouse. Build the ETI SPL Meter at a fraction of the cost of commercial units

# **Stethoscope**

ETI February also features our engineers' stethoscope design. This useful instrument can be used in a variety of engineering applications to check for faults in moving parts pistons in cylinders, for example.

> The ETI Roulette game the home casino.

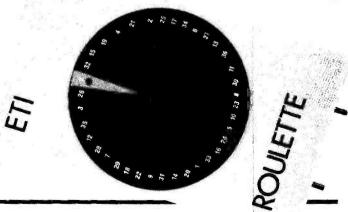

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

Now out of twelve years' experience in electronics and communication comes the South Coast's own Computer Centre Choose from our wide range of micro-computers and support material. Ideally suited to the hobbyist about to enter the fascinating world of computers. Personal callers or mail order welcome

Nascom 2-£225 . Comprehensive starter system that grows with you Powerful Z80A 57 KeyLicon solid-state keyboard. TV or monitor On board UART (6402) Parallel 1/0 with 16 lines. Kit fully documented. 8K microsoft basic in ROM

Nascom Imp-£325. Plain paper with standard specification eatures: 60 lines/minute Bidirectional printing Baud rate 110-9600

Nascom 1—£125 Kitform —£140 readybuilt. Full range of Nascom accessories are normally held in stock Detailed specification and full list available

00





Microtan 65-£69 6502 1K Tanbug. microprocessor. 1K user RAM. Full TV display. 20-way keypad. £10.00

Tanex-£43 7K RAM, 6K RAM, 8K microsoft basic 32 parallel 1/0 lines.
2 serial. 1 x 20mA serial.
Cassette interface and motherboard. System Rack

£49 in black/tangerine brushed aluminium. Full Ascii keyboard with numeric keypad. £56.35. Cabinet available at £20

Optional lower case pack—£9.48 Chunky Graphics Pack—£6.52

£69

# COMMODORE PET

Everything has been said about PET A full range of accessories and software (both games and business) is held in stock

8K Small Keyboard: £399.00 8K Large Keyboard: £425.00 16K: £499.00 External Cassette: £55.00







Apple 16K video output only—£895.00. Disc drive without controller—£299.00. Disc drive with controller—£349.00. 16K add-on—£89.00. CARDS: Prototype/hobby card—£15.00. Parallel Printer Interface Card—£104.00. Communications Card—£130.00.

High-speed serial Interface Card—£113.00. Pascal Language System - £299.00.

Epsom T80 Printer: £349.00

+ FREE £695

# SHARP

MZ80-Sharp's dynamic entry into microcomputers Floppy disc units plus printer now available

Dual Discs: £715.00 Printer: £475.00



# video genie ryztem

BASIC language Easy-to-use Easy-to-use BASIC language means that programmes are easily written for specific applications. Many pre-recorded programme tapes are available. TRS80 software compatible. Great scope for the home, introducing the whole family to the computer age.

9" Monitor only £85.00 Epsom 80 Printer £349.00



# SALE OF DEMONSTRATION EQUIPMENT

Centronics 779 with stand was £995.00 now £699.00 Computhink 800K Dual Disc was £1145.00 now £695.00 32K PET was £695.00 now £599.00 16K Apple 11 was £695.00 now £599.00 All items sold with warranty.

# BOOKS

Basic Computer Game—£5.50. Instant Basic—£7.20. Pet Revealed—£10.00 Library of Pet Subroutines—£10.00. Your First Computer—£5.95. Guide to Basic Programming—£8.85. Basic Basic—£6.50. Advanced Basic—£6.00. Programming Z80—£8.95. 6520 Applications Book—£7.95. And lots more. Programming Z80—£8.95. 6520 Applications Book—£7. Send for full list of microcomputer and electronics books.



Media C12 Cassettes—£5.00 for 10.  $10 \times 514''$  mini floppy discs—£25.00 Kybe or Memorex. Listing paper—£15 per box, 2000 sheets  $11 \times 912''$ .

Printers: Commodore 3022, Epsom 80, Anadex DP8000, Qume. Service: Full service and spares for all equipment. Microprocessor components 6502, Z80A, 2716, 2114, etc., etc. Large range of CMOS, TTL, Linear, Transistors, Capacitors, Sockets, Rectifiers, LEDs, Resistors—full list available. Monitors: Range of direct import U.S. monitors 12" b/w £139.95. 12" green/black £149.95. Hitachi 12" £197, 9" £127. Under development—IEEE Intelligent Interface for Nascom, IEEE Controller, to operate Nascom or Commodore discs. Delivery January 1981

ALL PRICES—ADD 15% VAT. DELIVERY: POSTAGE/PACKING WILL BE NOTIFIED BARCLAYCARD AND ACCESS ORDERS TAKEN BY PHONE

7 CASTLE ST., HASTINGS, EAST SUSSEX TN34 3DY Shop hours 0900 to 1730 Mondays to Saturdays

Telephone: Hastings (0424) 437875 Personal callers welcome

# **MICROBASICS**

'Speak to me only with thine software'. Henry Budgett discusses the monitor program that ties together the hardware from previous Microbasics.

f, at this point in the series, you feel that you have got yourself a real microcomputer, then think again. What you have is a collection of hardware that will process, store and transmit data but it has not yet been told how it should do it. Whilst the average person will usually be working in a high level language such as BASIC the actual CPU can only undertand binary numbers. Quite apart from the Interpreter that translates the high level language instructions into the appropriate binary codes there has to be a piece of software called the monitor.

The name 'monitor' is synonymous with the operating system in bigger machines and performs the same tasks as the front panel used to in the days when computers had pretty lights and knobs all over them. The term 'software front panel' is still used in some literature to imply something special.


# **Monitoring The Situation**

Before we take a detailed look at one particular monitor and what it does it is necessary to understand the tasks that should be done first. The monitor must be aware of the size and location of the memory, the location of the I/O devices and, most important of all, how to start everything up in the right way.

If we have informed the computer of these facts by writing a short machine code routine and a look-up table that details the various devices and their functions, we can now proceed.

We will assume that our microprocessor is being driven by an ASCII keyboard and that it will display the information on a TV screen. How does the monitor know when a key has been hit on the keyboard? The usual procedure is to operate under interrupts. This is done by causing a special bit in the CPU's status word to be set whenever a key is pressed. The monitor is continually looking at this bit, even if it's doing something else, and when it detects it, whatever is currently happening is suspended and the I/O port that caused the interrupt to occur is examined. It knows which one this is by means of a wonderful device known as the interrupt vector. It can now read the value of the key that was pressed.

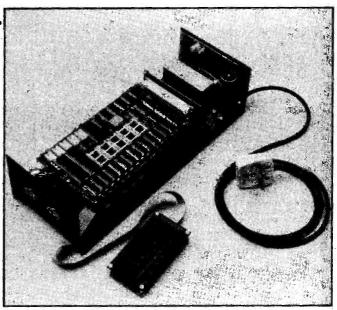What the monitor does with this piece of information depends on the type of monitor that you have. Some are very complex and allow all manner of special things to be done in the way of machine code programming. The one I am going to take a close look at is a good example of the kind of complexity that you can achieve within a very small space.



Microtan 65 with TANBUG and XBUG.

# **Bugging Your Micro**

For historical reasons monitors are generally given BUG as part of their name. TANBUG is the standard monitor supplied with the Microtan 65 computer and, along with its enhancement XBUG, is the basis of the rest of this article.

TANBUG is rather special in that you can plug in either a simple Hex keypad or a full ASCII keyboard and it will detect which one is being used. For the sake of simplicity, assume that the ASCII keyboard is used. As soon as the machine is reset by means of the hardware switch, the internal hardware reset vector jumps straight into the start of the monitor. Being polite, 'user friendly' to use the jargon, the monitor announces its existence and gives you a character on the screen known as a prompt. Within the context of a monitor, the prompt and the cursor can be regarded as the same unless an error has occured and then a '?' is displayed.

Before we can run any programs we first have to write them and thus we need a means of getting information into the memory and changing it if necessary. This is achieved by the M <addr > command which opens the specified address and displays its contents on the screen followed by a prompt. We can now type in the code that we require to replace that currently stored, step back to the previous location, step forward to the next location or go back to the monitor by pressing respectively ESC, LF or CR. These apparently meaningless mnemonics are ESCape. Line Feed and Carriage Return respectively and are interrupted in various ways by the monitor. Let us assume that you have written a program into the memory of your micro using the monitor and that you now wish to run it. In the case of TANBUG simply type 'G < addr > CR'. This tells the CPU to load the CPU's program counter with the specified address, to load the stack pointer with the beginning of the stack area in RAM and to start obeying the instructions. Clever stuff.

# **Doing It Slowly**

The trouble with programs written in machine code is that they tend to run extremely quickly. We can slow them down by writing delay loops but we can also use a monitor command which gives us single steps. Keying S sets the process into one-step-at-a-time mode. After each step has been processed the program stops and goes back to the monitor with a full display of the CPU's registers. You can execute the next step by keying P for proceed. It must be noted that a program step is not just the contents of one address but the complete instruction such as 'jump to address A000'.

Because the main cause of programs crashing is the wrong interpretation of information in the registers, the monitor allows you to adjust their values in much the same way as you can alter the contents of the memory. Even more common than that is the occasional 'bug' that lurks within the code and only jumps out at obscure times. We can catch this by setting a trap for it called a breakpoint. We generally know where the bug comes from but we don't know what causes it to appear so we set the breakpoint to the relevant position in the program and leave it running. When the bug appears and takes the trapped route it trips the breakpoint and this causes a complete printout of all the registers allowing you to find the reasons for its sudden emergence. With the TANBUG monitor you can set up to eight different traps, allowing bug catching on a lavish scale.

# **Display Your Contents**

Keeping track of the program in the depths of the memory is made easy by having a list command. This allows you to display memory contents on the screen in a regular format, making the checking and copying on to paper easy. As the final option in the TANBUG repertoire, we can calculate offsets. Because it is quicker to tell a program to jump back ten steps rather than to tell it the absolute address, there is a relative jump command which allows you to move up to 127 steps in either direction. To use this, merely key in the address of the jump command, the address you wish to get back to and CR. The monitor then gives you the HEX value for the relative jump.

# **Saving The Day**

The basic Microtan 65 is equipped with only 1K of RAM and out of this must be taken the stack requirements for the CPU and the monitor, the 512 bytes of video RAM and some working space. The user is left with about 430 bytes for his programs although it is possible to use the video RAM area to some extent. Because of this limited area it was not thought necessary to include any cassette storage capability on the CPU card; there isn't any space left anyway! Once one enters the realms of expansion with the TANEX card, cassette I/O is essential and the enhanced monitor package, XBUG, supplies this and more.

XBUG is packaged in a 2K EPROM and gives the user three extra functions. These are cassette handling, a line-by-line assembler and a line-by-line translator. The latter two are almost unique and, at this price level, give the system a distinct

edge.

The cassette-handling software allows the saving and loading of named files as well as the verification of saved files against the memory at two speeds. The slow CUTS (Computer Users Tape Standard) 300 baud speed is generally used for important system files, and for any back-up copies because the recordings made are inherently less prone to corruptions. That

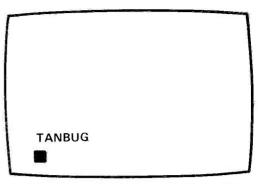


Fig 1. The monitor announces itself to the world and 'prompts' the user to do something. The **1** is replaced by a '?' in the event of an error.

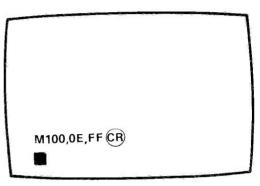


Fig 2. Typing M100 CR opens the specified location and reveals the current value 0E. We have replaced this with FF and closed the location but we could have stepped forward or back through memory by using other commands.

L0400,3 CR 0400 A2 FF 9A E8 86 17 20 B7 0408 A0 0F 20 73 FE 88 10 A9 0410 20 8D E0 03 A9 00 85 00

Fig 3. The monitor will list the program from any given address in blocks of eight bytes per line for up to 256 lines. Here we have selected three.

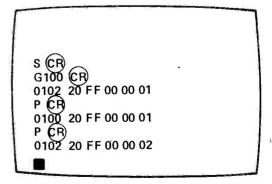


Fig 4. By setting the monitor to operate in single steps, we can inspect the contents of each register in the CPU after each step before proceeding with the P command. The registers are; next address to be executed, CPU status value, low byte of the stack pointer, index X register value, index Y register value and the accumulator value.

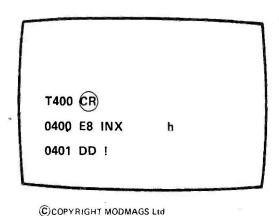


Fig 5. Using the assembler, we define the starting address and the current memory value is displayed. We have overwritten this by keying INX which has been translated into its correct Hex code and the assembler has stepped to the next location in memory. The prompt symbol "!" is used to identify the fact that you are in the assembler mode and the 'h' to the extreme right is the ASCII character that corresponds to the Hex code. This acts as a check.

is not to say that the fast speed, of approximately 2400 baud, is unreliable — one generally uses this for the convenience of loading programs quickly; a program takes eight times longer to load using the CUTS format. The manual gives the setting up information in two programs which should be tried at each tape speed. I use a manual level control tape recorder which also allows the tape speed to be varied slightly, but the system works perfectly on virtually any cassette recorder. The reason that I chose a rather more expensive machine is not because I've got money to burn, but because I receive programs for a wide variety of machines and sometimes the speeds or recording settings vary, hence the need to be able to adjust my system to that of the person who is supplying the tape.

# **Interpretations Supplied**

As mentioned earlier the XBUC monitor is equipped with a simple assembler and dis-assembler. This allows the budding machine code programmer to use assembly language mnemonics rather than the actual Hex codes. The mnemonics are effectively one step towards high level language programming. They allow the programmer to think in logically sounding 'words' rather than in specific Hex codes.

Given a starting address and the appropriate commands, the assembler will convert the op-code and its associated operands into the proper Hex codes. It is quite intelligent too; most common errors are trapped before they can be entered.

As a direct complement to the assembler there is a lineby-line translator, which converts the stored Hex into the more meaningful assembly language mnemonics. It is called a 'lineby-line' system because it needs to know the correct start or else it will try to convert Hex data into assembly language mnemonics. In some cases you can have enormous fun disassembling a program to reveal another program which, according to the translator, is complete nonsense! Don't get me wrong, I'm not criticising the limited capability of the translator but rather pointing out that, for a 2K package, it packs one heck of a punch. The nearest equivalent system that I can recall is one supplied with the Rockwell AIM 65 and that takes about 2K on its own just to give an equivalent assembler.

# The Next Step

Nowadays the almost universal introduction to high level language programming is through BASIC. With a language like this, a new piece of software is required — the Interpreter. This is, if you like, equivalent to the mnemonic assembler in that it converts the 'English' of the BASIC commands into the Hex code that the CPU needs. To avoid wasteful repetitions of the code, the BASIC will use routines that are already written in the monitor, the cassette-handling routines for example.

This use of standard routines allows the BASIC programmer to call machine code programs from this BASIC program. This is often done to speed execution of a program or to perform a repetitive chore. On my system there is no 'Clear Screen' command in BASIC, so I have a standard machine code routine for this stored in memory, which I call as reauired.

# A Close Encounter

I hope to be taking a very close look at one specific computer in the next two episodes. As yet the computer hasn't arrived, but with luck next month will see the first part. The reason for taking a look at a complete computer is to try to explain the systems aspect, ie how all the bits and pieces fit together, rather than continue to inspect the individual elements.

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately twelve issues and is attractively bound and blocked with the ELECTRONICS TODAY INTERNATIONAL logo.

Price U.K. £3.95 including postage, packing and V.A.T., overseas orders add 30p. Why not place your order now and send the completed coupon with remittance to:-

E STREET, 0686 nent of order.

	LONDON W8 7SZ: Tel: 01-727 0686 Please allow 3/4 weeks for fulfillment of order
	it's easy
E	Easibind Ltd.,4 Uxbridge St., London,W87S Nat. Giro No. 5157552.
	Order Form ELECTRONICS TODAY INTERNATIONAL
	for binders
100	Years required
i e	Name
<b>E</b> V	Address
	www.comacarararararararararararararararararara
0 0	Date

# he range grows

New Profile Amplifiers- Two New Series CHILL CHILD CHILD


Advantageous to have a laster slew rate. Towar, what where it is not a control of the state of t CHOOSE AN I.L.P MOSFET POWER AMP when it is

£33.46 + £5.02 Price & Signal/Noise Ratio DIN AUDIO 100dB Rise Time STE Slew Rate 20V/µs 20V/µS Distor-tion Typical at 1KHz 0.005% 0.005% 60W into 4-8Ω into 4-80 Output Power RIMS 120W MOS120 M0S200 Model

CHOOSE AN I.L.P BIPOLAR POWER AMP Where power and price are first consideration while maintaining optimism performance with hi-fiquality maintaining optimism performance with hi-fiquality maintaining optimism performance with hi-fiquality and wide choice of models. From domestic hi-fi to disco and P.A., Jorinstrumentamplification, there is considered. A., Jorinstrumentamplification, there is baseles, we have encapsulated Bipolars within our New


Profile extrusions with their computer-vertified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and withour newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distor- tion Typical at TKHz	Siew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT	
HA30	15W into 4-8Ω	0.015%	15V/µs	Sµs	100dB	£6.34 + 95p	in the second
HY60	30W into 4-8Ω	0.015%	15V/µs	Sus	100dB	£7.24 + £1.09	
HY120	60W into 4-80	0.01%	15V/µs	Sus	100dB	£15.20 + £2.28	- 1
HY200	1:20W into	0.01%	15V/µs	Sus.	100dB	£18.44 + £2.77	
HY400	240W into	0.01%	157/µs	Suc	100dB	£27.68 + £4.15	

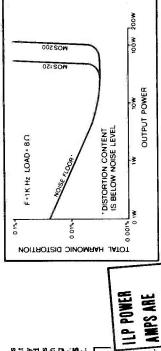

ENCAPSULATED FOR THERMAL AMPS ARE

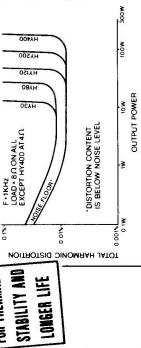Load impedance both models Input impedance both models  $100K\Omega$   $4\Omega$ -  $\infty$  Input sensitivity both Frequency response both models models 500mV



Load impedance all models  $4\Omega$  - $\infty$  Input impedance all models  $100K\Omega$  Input sensitivity all models 800mV Frequency response all models  $15H_{\rm E} < 0KH_{\rm E} - 3dB$ 

# THE NEW PROFILE EXTRUSIONS

The introduction of standard heatsink extrusion for all III. Power amplifiers achieves many advantages:—Research shows they provide optimum thermal dissipation and stability. Solved shoulders allow easy mounting, standardisation enables ustokeepour prices competitive. Surfaces are matt black, anodised for lower thermal conductivity. Extrusions vary in size according to module number.





NO OUIBBLE 5 YEAR GUARANTEE S

BRITISH DESIGN AND MANUFACTURE 7.DAY DESPATCH ON ALL ORDERS

FREEPOST SERVICE

\*

WITH ALL

10

advanced audio modules. Their improved characteristics Active Tone Control circuits provide ±12dB cut and boost.

Inputs Sensitivity - Mag. PU. -3mV: Mic - selectable
1-[2mV: All others 100mV. Tape O/P - 100mV: Main O/P -HY6 (mono) and HY66 (stereo) are new to I.L.P's range of and styling ensure their being compatible with all I.I.P power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polanty. Full assembly instructions are provided Mounting boards are available as below.

500mV: Frequency response - D.C. to 100KHz - 3dB. HY6 mono £5.60 + 84p VAT Connectors included

366 Mounting Board for one HY66 99p + 15p VAT 86 Mounting Board for one HY6 78p + 12p VAT HY66 stereo £10.60+£1.59 VAT Connectors included

DISTORTION TYPICALLY S/N RATIO — 90dB (Mag. P.U. — 68 dB)

SCHEMATIC BLOCK DIAGRAM OF HYG PRE AMP, WITH STEREO CONNECTION SHOWN

ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING QUALITY CONNECTORS

NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v • 38 dB overload margin on Mag. P.U.

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

**TEN YEARS OF PLANNED** 971-1980 PROGRESS

> £4.50 + 0.68p VAT £8.10+£1.22 VAT £9.75+£1.46 VAT

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made invourownfactory. Thisthese. L. Prowersupplyunits are space-saving, more efficient and their better overall design helpsenormostly when assembly building. All models in the range are compatible with all LL.P amps and pre-amps with types to match whatever LL.P.

When, in 1971, Jan L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this me whitning is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructions as the modules to build with. The range grows brigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why with existing ones) are wen past crawing there.

BRITAIN'S FASTEST GROWING MODUME SUPPLIERS

£13.61 + £2.04 VAT £14.75 + £2.21 VAT £23.02 + £3.45 VAT £24.20 + £3.63 VAT

**PSU180** for use with 1 HY400 or 2 HY200 PSU185 for use with 1 or 2 MOS200

PSU95 for use with 1 MOS200

PSU90 for use with I HY200

PSU75 for use with 1 or 2 MOS120 PSU65 for use with 1 MOS120 PSU70 for use with 1 or 2 HY120's

£13.61 + £2.04 VA7 £13.61 + £2.04 VAT

£9.75 + £1 £9.75 + £1

ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
 PSU50 for use with 1 or 2 HY60's

**PSU60** for use with 1 HY 120

PSU30 ±15V at 100mA to drive up to 12 x HY6 or 6 x HY66 ■ THE FOLLOWING WILL ALSO DRIVE I.L. P PRE-AMPS

PSU36 for use with 1 or 2 HY30's

	1
	:
	Please supply
	:
3	:
CIZIE	:
2	:
S	1
>	:
5	
9	÷
<b>-</b>	
7	3
CANTERBURY	÷
ر	:
<u>`</u>	1
3	i
2	
2	:
Z.	1
Ş	
LECTRONICS LID	
3	Y
3	d
4	St.
3	ø.
	88
10: I.L.	<u> </u>
	-

chase price £	al Money Ord
	I enclose Cheque ☐ Postal Orders ☐ International Money Ord
	ue 🗌 Postal Ord
	I enclose Cheq

TO ORDER Send cheque or money order payable to I.L.P Electronics Indand crossed Or pay by ACCESS or BARCLAY CARD Cash payments must be in regalatered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

When ordering or writing about IL.P products, you do not need to stamp the envelope, Mark it TREPOST plus the code shown in the address below. We pay the postage for you.

Freepost facility

\*

Order

Please debit my Access/Barclaycard Account No.

ADDRESS NAME

Signature

Telex 965780

Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.


Telephone (0227) 54778 |Technical (0227) 64723

FREEPOST 4

ELECTRONICS
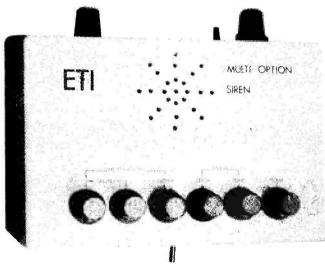
# MULTI-OPTION SIREN

Warbles, bleeps, rising tones, falling tones and key-shifted tones, with or without vibrato — just a few of the near-infinite variety of sounds generated by our Multi-option Siren. Design by Ray Marston. Project development by Steve Ramsahadeo.



This design has a total of seven variable controls plus six switch-selectable operating modes and can generate such a vast range of different sounds that it is quite difficult to adequately give a written impression of the full capabilities of the project.

The heart of the unit is a tone generator that can have its operating frequency varied over virtually the full audio range by a single tone control. The frequency of this tone generator can also be modulated by either or both of two more generators, the first of these being a vibrato square wave oscillator. Both the vibrato rate and vibrato depth can be varied by individual controls. Thus, a little bit of fast vibrato imposes a 'buzz' sound on the tone, while lots of slow vibrato produces a sound like that of a tinkling piano key.

The second frequency-modulation generator is a very-low-frequency (VLF) oscillator that can produce either a pulse or a ramp waveform. Two mod shape controls allow the rise and fall times of the ramp or the on and off times of the pulse to be independently varied over a wide range to produce a wide variety of frequency-modulation waveforms. The depth of modulation is fully variable by a mod depth control.

Thus, with lots of symmetrical VLF ramp modulation applied, the circuit produces a 'wailing' American police-car sound without vibrato, or the sound of a repeatedly scaled (up and down) piano when lots of slow vibrato is applied. With a little bit of symmetrical VLF pulse modulation applied, the circuit produces the familiar 'dee-dah' British police-car sound without vibrato, or the alternate sounds of the repeated hammering of one piano key followed by the similar hammering of a different key when lots of slow vibrato is applied. The circuit can, of course, generate a virtually infinite variety of sounds between these extremes.

# **Gating Facilities**

In addition to all the above sound generating facilities we've provided the ETI Siren with a number of gating functions. The gate is driven by the VLF oscillator and can be used

to disable the audio output signal during either the leading or the trailing part of the VLF waveform or on alternate VLF-generator cycles. To gain an insight into the functional effect of this gating facility, imagine that the siren controls are set to produce a symmetrical VLF ramp waveform with lots of mod depth and no vibrato.

With the gating circuit turned off, the siren produces the familiar wailing sound. With leading gating applied the siren repeatedly produces a 'peeow' or falling tone sound followed by a blank period. With trailing gating the siren repeatedly produces a 'wheep' or rising tone sound followed by a blank period. With alternate gating the siren repeatedly produces a wail sound followed by a blank period of equal length.

Thus, the gating facility effectively trebles the variety of sounds that our siren can produce — and three times a 'near-infinite variety of sounds' should be enough to satisfy anyone!

The Multi-option Siren circuit needs a 12 V supply, which can be derived either from batteries or from the mains via a suitable supply circuit.

All components are mounted on a single PCB to ease construction. Begin by inserting all low profile components, ie wire links and sockets, followed by resistors, diodes, capacitors and transistors, observing the orientation of all polarised components. Fit the ICs last, taking care when handling the CMOS 555.

If you decide to use the recommended Vero case, drill all the holes to accommodate the potentiometers, switches and loudspeaker vent. Fix the loudspeaker in the upper half of the case and hold it in place with a few drops of the ever faithful Super-glue. The PCB must be centralised, so that the two battery holders can be placed either side. To enable the holders to fit in this way the battery connectors are not used. The power connections are soldered directly onto the studs, so take care not to apply excessive heat. A piece of insulating tape can then be stuck across the connections to stop interference with the front panel.

After a visual check, you will now be able to produce a variety of sound effects that will span the galaxy; yes, you too can have the best battery-powered bird caller in the land.

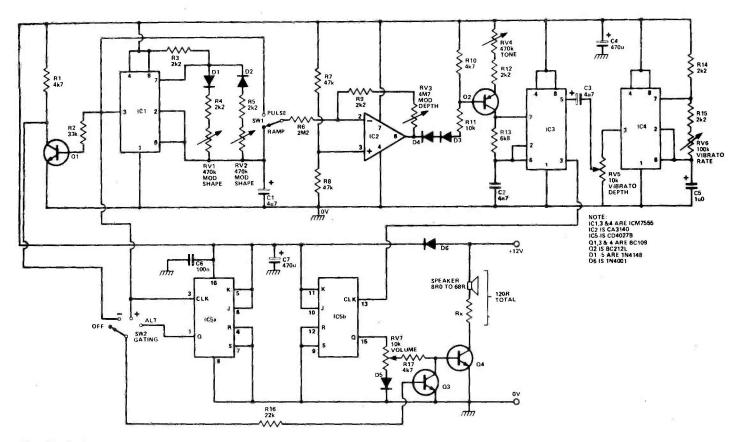


Fig.1 Circuit diagram.


# **HOW IT WORKS**

The heart of the project is the tone generator designed around IC3. This is a fairly conventional 555-type astable, except that C2 charges via R13 and the constant current generator formed by Q2 and its associated resistor and diode networks. Normally, the output of IC2 (feeding D4) is at half-supply volts, so Q2 base is at a couple of volts below the positive supply value. The operating frequency of IC3 is variable via tone control RV4. The output (pin 3) of the IC3 tone generator is divided-by-two to provide a symmetrical waveform (via IC5b) and the resulting audio signal is fed to the speaker via Q4-R17 and volume control RV7.

IC4 is wired as a perfectly conventional 555 type astable and is used as a vibrato generator, with its square wave output being used to frequency modulate the IC3 tone generator via pin 5. The vibrato rate is variable via RV6 and the vibrato depth is variable via RV5.

IC1 is also wired as a 555-type astable, but in this case the charge and discharge times of C1 are independently varied by RV1 and RV2 respectively and the circuit operates at a very low frequency (VLF). The output of the VLF oscillator can be used to frequency-modulate tone-generator IC3 via IC2 and constant-current generator Q2, the pin 3 output being used to provide pulse modulation and the C1 output to provide ramp modulation. The depth of modulation can be varied by mod depth control RV3, which enables the gain of IC2 to be varied from near-zero (RV3 = zero) to approximately x2 (RV3 = 4M7).

The square wave (pin 3) output of the VLF oscillator can also be used to synchronously gate the audio output signal of the siren on and off via Q3. When this transistor is driven to saturation (by a high bias to R16) it kills the input signal to amplifier Q4. If R16 is driven directly from pin 3 of IC1, the audio signal is killed (gated off) when the VLF output is high. If R16 is driven from the collector of inverter Q1, the audio signal is killed when the VLF output is low. If R16 is driven from the output of divide-by-two flip-flop IC5a, the audio signal is killed on alternate VLF cycles.

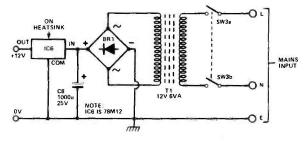


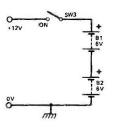



Fig.2 Alternative battery and mains power supply options.
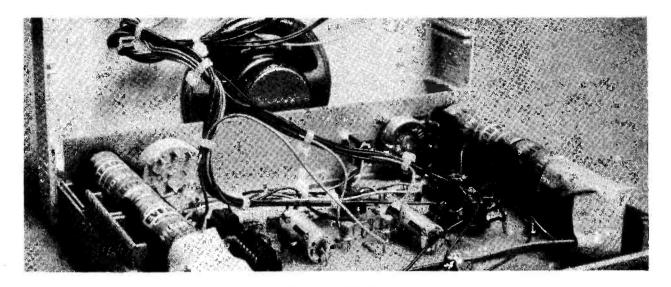
# BUYLINES

There should be no problem in obtaining any of the components used in the ETI Siren. All should be available from mail order suppliers advertising in this issue. If you have trouble obtaining a 68R loudspeaker, Technomatic should be able to help.



		P/	ARTS LIST	
	Resistors all 1	4W 5%	C3	4u7 63 V electrolytic PCB type
1	R1,10,17	4k7	C4,7	470u 25 V axial electrolytic
1	R2	33k	C5	1u0 63 V electrolytic PCB type
	R3,4,5,9,12,		C6	100n polyester Mullard C280
1	14,15	2k2		
L	R6	2M2	Semiconduct	
1	R7,8	47k	IC1,3,4	ICM7555
	R11	10k	IC2	CA3140
Ĭ.	R13	6k8	IC5	4027B
1	R16	22k	Q1,3,4	BC109
1			Q2	BC212L
	Potentiomete	ers	D1-5	1N4148
	RV1,2,4	470k linear	D6	1N4001
1	RV3	4M7 linear		
1	RV5	10k linear	Miscellaneou	us
1	RV6	100k linear	SW1.3	DPST miniature toggle
ł	RV7	10k logarithmic	SW2	1 pole 4 way rotary switch
1	K 1 /	1011 10 8	LS1	68R
1	Capacitors			tery holders (HP7 type) (2 off)
1	C1	4u7 35 V tantalum		rder code 202-21037L)
	C2	4n7 ceramic	Knobs to suit	
			KINDS to suit	(0.011)

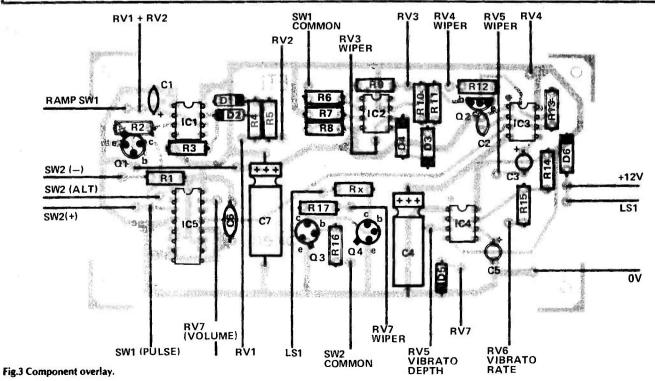

24

ETI

# YOU CANNOT BUY CHE YOU CAN ONLY OFF LA FOR YOUR MONEY LA

Introduces DIRECT SELLINGthe Ultimate **Discount** 







20 00000

MU 25 C





£25

MOVING MAGNET £7.28 S100 555SX 555E £14.22 S101 666E £32.48 S200

AGE FROM VIDEOTONE



# **HEAD AMP**

£51.75 H300 £24.75 T100

# **HEADSHELLS**

£6 £7 £4



The complete fully reviewed range of Videotone Speakers which dominate within their class. Now at lowest ever prices. GB2

D 100 £38 Minimax 11 £44 GB<sub>3</sub> £50 £60 GBS £207 D 93 £40






£29.30

£22.25

£17.39
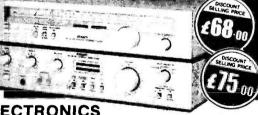
# **TURNTABLES**

£69.00 Sansui SR222 Mk2 £64.00 JVC LA 11 £140.00 JVC SLQ 3



This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

30 watt amp MC input SA4130	£75.00
Stereo Tuner ST4120	£68.00
Cassette full features SC3200	£98.00
50 Watt amplifier WA7700	£77.00
20 Watt amplifier LA2020	£58.00



# SEND FOR OUR ATEST FREE BROCHURE

AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly on to you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your specific of the consumer protection packages are help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require.
We carry out our own servicing and are dedicated to giving Value for Money. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. Remember, you have 21 days trial period on all products. That is andcastle the measure of our confidence Managing Director



# HEADPHONES

£12.65 HP 90 Headphone £9.69 HP 80 Headphone

Superbly made with top flight performance.



DEOT

ALL PRICES INCLUDE VAT



lease send me your Direct Selling Brochure and li	st of sales outlets.
ame	
ddress	
	ETI 1/81

TTLs by TEXAS 74290 150p 4020 100p 7400 11p 74293 150p 4021 110p 74500 60p .74298 200p 4022 100p 7401 12p .74365 100p 4023 27p	93 SERIES         74S SERIES           9301'         160p         74S00         60p         74S114'         120p           9302         175p         74S04         60p         74S124'         300p           9308         316p         74S05         75p         74S132'         160p           9310         275p         74S03         75p         74S133'         75p	TRANSISTORS         BFR40         25p         TIP30A         48p           AC126         25p         BFR41         25p         TIP30C         60p           AC127/8         20p         BFR79         25p         TIP31C         58p           AC175         25p         BFR80         25p         TIP31C         62p	2N3055
7402 12p 74366 100p 4024 50p 7403 14p 74367 100p 4025 20p 7404 14p 74368 100p 4026 130p 7405 18p 74390 200p 4027 50p 7406 36p 74390 200p 4028 84p 7407 36p 74490 225p 4029 100p 7408 17p 7449 58FRIES 4030 55p	9310 275p 74508 75p 745133 75p 9311 275p 74510 60p 745138 225p 9312 180p 74520 60p 745139 225p 9314 185p 74530 60p 745157 250p 9314 185p 74532 90p 745174 250p 9321 225p 74537 90p 745174 250p 9321 255p 74537 60p 745194 350p	AC187/8 25p BFR81 25p TJP32A 68p AF116 50p BFX29 40p TJP32A 68p AD149 70p BFX30 34p TJP33A 99p AD161/2 45p BFX86/7 30p TJP33A 99p AU107 200p BFX86/7 30p TJP33A 115p BC107/8 11p BFX88 30p TJP34A 115p BC1097 11p BFX88 30p TJP34A 225p	2M3584 250p   40364   120p   25A 400V 400p   120p   25A 400V 400p   120p   25A 400V 400p   120p
7408 17p 74Ls SERIES 4030 55p 7409 19p 74LSO0 14p 4031 200p 7410 15p 74LSO2 16p 4034 200p 7411 24p 74LSO3 18p 4035 110p 7412 20p 74LSO3 18p 4035 110p 7413 30p 74LSO4 16p 4036 295p 7413 30p 74LSO5 25p 4039 295p	9334 <b>360</b> p 74574 <b>90</b> p 74524 <b>450</b> p 9358 <b>250</b> p 74585 <b>300</b> p 745260 709 9370 <b>300</b> p 74586 <b>180</b> p 745373 <b>500</b> p 9374 <b>200</b> p 745112 <b>120</b> p 745374 <b>500</b> p	SC117   20p   BFY50   30p   TIP35C   290p   SC147/8   9p   BFY51/2   30p   TIP36A   270p   SC149   10p   BFY56   33p   TIP36C   340p   SC157/8   10p   BFY90   90p   TIP41A   65p   C159   TIP41C   78p   TIP41C   TIP4C   TIP	283819   25p   40673   75p   283820   50p   40841   90p   TRIACS   283823   70p   40871 / 2 100p   PLASTIC   283866   90p   DIODES   3A 400V   70p   709
7414 40p 741508 22p 4040 100p 74C14 90p 74L509 21p 4041 80p 7416 27p 74L510 20p 4042 80p 7417 27p 74L511 40p 4043 90p 7420 17p 74L513 40p 4044 90p	LINEAR I.Cs	BC169C         12p         BSX19:20         ZOP         TIP42A         70p           BC172         12p         BU104         225p         TIP42C         22p           BC177:18         17p         BU105         190p         TIP54         160p           BC182:13         10p         BU108         250p         TIP120         120p           BC182:3         10p         BU108         250p         TIP122         130p           BC184         11p         BU326         180p         TIP122         130p           TIP12         130p         TIP12         120p         TIP12         120p	2M3993/4 18p 57/2 65 8500 88p 8A 4000 75p 2M4037 65p 0A47 9p 8A 5000 95p 12A 4060 12p 0A81 15p 12A 5000 88p 2M4061 12p 0A89 15p 12A 5000 105p 12A 5000 115p
7422 22p 74LS20 20p 4047 100p 7423 34p 74LS21 40p 4048 55p 74LS27 38p 4049 45p 74LS27 38p 4050 45p 74LS27 32p 4050 45p 74LS27 34p 34LS22 27p 4051 80p 8051	AY3-8912 A 560p MC3340P 120p MK50398 750p AY5-124A 240p MK50398 750p AY5-1317A 775p MM57160 620p AY5-40070 520p NE551 150p CA3019 80p NE555 20p	BC187         30p.         BU180A120p         TpP147         130p           BC212/3         11p.         BU265         200p         TlP2955         78p           BC214         12p.         BU208         200p         TlP4055         70p           BC237         15p.         BU406         145p         TlS43         45p           BC327         16p.         E300         50p         TlS93         30p	2N4123/4 27p OA91 9p 15A 500V 130p 2N4125/6 27p, OA95 9p 12800D 130p 2N44217 90p OA200 10p 2N4427 90p 1N914 4p 1N915 7p THYRISTORS
7428 360 741537 300 4052 800 7430 170 741538 380 4053 800 150 4054 300 741547 750 4055 1250 7433 400 741547 750 4055 1250 7437 350 74155 240 4056 1350 7438 350 74155 300 4059 6000	CA3046 70p NE556 70p CA3048 225p NE562B 425p CA3080E 72p NE564 420p CA3086 48p NE565 130p CA3089E 225p NE566 155p CA3089AQ 375p NE567 140p	EC338         15p         E310         50p         ZTX300         13p           BC481         36p         MJ2501         225p         ZTX500         15p           BC477/8         30p         MJ2955         30p         ZTX502         18p           BC516/7         40p         MJ3001         225p         ZTX502         18p           BC547B         16p         MJE340         50p         ZM57A         250p	245089   27p   104148   4p   14 900   70p   275172   275   276
7440 17p 741573 50p 4066 115p 7441 70p 741574 57p 4063 120p 7442A 60p 741575 36p 4066 50p 7443 112p 741576 45p 4067 450p 7444 112p 741583 70p 4068 27p 7445 100p 741585 80p 4069 20p 20p	CA3130E 90p NE571 425p CA3140E 50p NE5534A 250p CA3160E 100p RC4136 120p CA3161E 140p S566B 270p CA3162E 450p SADT024A 1250p	BC54BC         9p         MJE2955         100p         2N5B5         36p           BC549C         18p         MJE3055         70p         2N697         25p           BC557B         16p         MPF102         45p         2N5B8         45p           BC559C         18p         MPF10374         40p         2N706A         30p           BC77172         22p         MPF10576         40p         2N708         30p           BC77172         22p         MPS6531         50p         2N918         45p	NS296 Sp   NS404 / 7 19p   15A 400V 180p   10p   15A 400V 180p   10p   15A 400V 180p   10p   10p
7445A 839 741856 40p 4070 30p 7447A 75p 741850 40p 4071 25p 7445A 80p 741859 2 70p 4072 25p 7450 17p 741858 610p 4072 25p 7450 17p 741858 110p 4075 25p 7451 17p 741856 110p 4075 25p 7453 17p 7418107 45p 4076 107p	CA3189E 300p SFF96364 1100p CA3280 160p SL490 400p FX209 750p SP8515 750p FX209 750p TA72Uo 140p CL7106 860p TAA621 275p	BO131/2         50p         MPS6534         50p         2N930         18p           BO135/6         54p         MPSA06         30p         2N131/236p           BO139/6         54p         MPSA12         50p         2N131/236p           BO140         60p         MPSA12         50p         2N1511/3         25p           BO140         60p         MPSA13         50p         2N1711/1         25p           BO232         95p         MPSA20         50p         2N2102         70p           BO232         95p         MPSA42         50p         2N2160         350p	2N5485   44p   36 regs   30   22p   2N4444   140p   2N5060   34p   2N5060   34p   2N5060   34p   2N5064   160p   2N5064   160p   2N5064   160p   2N5063   300p   2N5065   300p   3N5065   3N50
7454 17p 74L5109 80p 4081 27p 7460 17p 74L5112 40p 4082 27p 7470 36p 74L5113 90p 4086 72p 7472 30p 74L5114 45p 4089 160p 7473 34p 74L5122 80p 4093 70p	CLR038   300p   TBA641B11   300p   TBA651   200p   200p   TBA651   200p   200	B0233         75p         MPSA43         30p         2N2219A         30p           B02345         85p         MPSA56         32p         7N222A         30p           B0241         70p         MPSA70         50p         2N2369A         25p           B0242         70p         MPSU06         63p         2N2484         30p           B0756         200p         MPSU07         60p         2N2646         45p           B7200         32p         MPSU45         90p         2N2646         45p           B7200         32p         MPSU45         90p         2N290475         30p	2N6109 325p 1A 50V 19p SPEAKERS 2N6107 65p 1A 100V 20p Syre 2N61247 190p 1A 400V 25p 2yr 64R 80p 2N6294 130p 1A 600V 30p 2yr 8R 80p 2N6290 65p 2A 50V 30p 2r 8R 90p 2N6292 65p 2A 100V 35p 1yr 8R 90p
7475 38p 74LS124 180p 4095 95p 7476 32p 74LS125 50p 4096 95p 7480 50p 74LS126 50p 4097 340p 7481 100p 74LS132 60p 4098 120p 7482 84p 7481 30p 4099 200p	LM311 70p TCA22U 350p LM318 200p LM319 225p LM324 45p TDA1008 320p LM339 75p TDA1010 225p LM339 75p TDA1010 225p	BF244B         35p         MPSU65         78p         2N2906A         30p           BF256B         70p         OC28         130p         2N2907A         30p           BF257B         32p         OC35         130p         2N2928         9p           BF259         36p         11P29A         40p         2N3928         9p           BF839         25p         11P29C         55n         2N3053         30p           BF839         25p         11P29C         55n         2N3054         65p	2SC1172 150p 2A 400V 45p 3N128 120p 3A 200V 60p 3N140 120p 3A 600V 72p 3N140 120p 3A 600V 72p 5MHz UHF 375p 3N201 110p 4A 400V 100p 8MHz UHF 375p 3N201 110p 4A 400V 100p
7483a 90p 7415136 55p 40100 220p; 7484 100p 7415138 65p 40101 132p 7485 110p 7415139 75p 40101 180p 7486 34p 7415145 120p 40103 180p 7489 210p 7415147 220p 40104 99p; 7490A 30p 7415148 175p 40105 120p 7491 80p 7415151 80p 40106 90p	UM358P SOP TDA1024 120p TDA10348 250p TDA10348 250p TDA10348 250p TDA10348 250p TDA2002V 325p UM381AN. 180p TDA2002V 325p UM386 95p TDA2020 45p	2101.4L 400p Z80P10 600p 2102.2L 120p Z80AP10 700p 21078 500p Z80ACTC 700p 2111.4 400p Z80ACTC 700p 2112.4 300p Z80ADATT £15	LOW PROPILE DIL BOCKETS BY TEXAS   8 pin \$ 9p 18 pin 18p 24 pin 24p 14 pin 10p 20 pin 20p 28 pin 30p 16 pin 11p 22 pin 22p 40 pin 40p 27 pin
7492A 45p 74LS153 80p 40107 60p 17493A 35p 74LS154 200p 40108 470p 74934 84p 74LS155 80p 40109 100p 17495A 70p 74LS155 90p 40110 300p 7496 65p 74LS156 80p 40114 250p	IM709 36p 1L072/82 75p 1L072 130p 1L072 350p 1L074 130p 1L072 350p 1L074 110p 1L0723 100p UAA170 175p 1M741 18p 1UNNS118 220p	2114-21 450p 4027-3 375p 4044 900p 4116 350p 41184 £1200 1M6402 450p MS402 450p	WIRE WRAP SOCKETS BY TEXAS           .8 pin         25p         18 pin         50p         24 pin         70p           .14 pin         35p         20 pin         60p         28 pin         80p           16 pin         40p         22 pin         65p         40 pin         100p
74100 130p 74LS160 90p 4503 70p 14107 34p 74LS161 75p 4507 55p 74109 55p 74LS162 140p 4508 290p 74LS163 100p 4510 99p 74LS163 100p 45110 99p 14118 130p 74LS164 90p 4511 120p 1	LM 748 35p UNN6184 320; LM 748 35p UNN2003 100p LM 2917 250p XR2206 300p LM 300 70p ZM 140 20 225p	5101 400s 6810 328s CHARACTER 68201 400s 82516 328s 3257ADC 990p 71301 700p R0.3:2513.U.C. 500p R0.3:2513.U.C. 500p	SUBMINIATURE   SWITCHES   SWITCHES   IRONS
74119 210p 74IS165 140p 4512 80p 74120 110p 74IS165 180p 4514 250p 74121 34p 74IS173 110p 4515 300p 74122 48p 74IS174 100p 4515 110p 74123 60p 74IS175 100p 4518 100p 100p 100p 100p 100p 100p 100p 10	LM3919 70p ZN427E 135p LM3911 130p ZN425E 400p LM3914 225p ZN427E 750p LM3915 226p ZN427E 750p	745188 225p 745387 350p 7453470 650p 7453471 650p 7455171 650p 745571 650p 32.7688412 250p	DPDT (centre off) 85p Push to make 15p Break 25p Push latching SPCO SLIDE OPDT 18b  C CXYZES 180p SLIDE OPDT 18b  C CXYZES 180p
74126 60p 74L5190 100p 4521 250p 74128 75p 74L5191 100p 4526 108p 74132 75p 74L5192 100p 4527 100p 74136 75p 74L5193 100p 4528 100p 74137 50p 74L5193 100p 4528 100p 74137 50p 74L5195 140p 4532 140p 74141 50p 74L5196 120p 4534 550p	1A +ve' —ve 5V 7805 60p 7905 65p 12V 7812 60p 7912 65p 15V 7815 60p 7915 70p 18V 7818 60p 7918 70p	CPUs 100KHz 300p 1600 1200p 200KHz 370p 1802CE 750p 1 0MHz 320p 1500 1 008MHz 350p 1 8432MHz 325p 1 8432MHz 325p	ROCKER SPST   28p   CCN   200p   WAFER   1P/12W   45p   49   45p
74142 200p 74LS197 90p 4536 3756 74145 90p 74LS221 120p 4538 120p 74147 190p 74LS241 175p 4543 180p 74148 150p 74LS241 175p 4553 320p 74150 130p 74LS242 170p 4556 72p	24V 7824 60p 7924 70p 10UmA TO 92 5V 78L05 30p 79L05 70p 12V 78L12 30p 79L12 70p 15V 78L15 30p 79L15 70p OTHER REGULATORS 78HGKC 600p	6802 950p 3.25760MHz 325p 6809 220 3 276MHz 300p 8080A 450p 3 579MHz 175p 8085A 1100p 4 194MHz 290p 1 4 194MHz POA	2.5×3.75" 25 75 75 75 75 75 75 75 75 75 75 75 75 75
74153 70p 74LS244 150p 4569 250p 74154 120p 74LS245 250p 4572 40p 74155 90p 74LS247 140p 4583 110p 74156 90p 74LS251 140p 4583 90p 74157 70p 74LS253 90p 4585 150p	LM309K 135p 78H05KC 550p LM3177 200p 78MGT2C 135p LM323K 500p 79H6KC 600p LM723 37p, 11.497 300p OFTO-ELECTRONICS	TM59980A £20 4 43MHz 125p 280A . 650p 6 0MHz 300p 6 144MHz 300p 1702A 500p 7 0MHz 300p 2708 450p 7 168MHz 300p 27164 (510) 9 00MHz 300p 27164 (510	TRAMSFORMERS   Pkt of 100 pins   50p   pinm 220 / 240y   5 0 6 100 mm 90p   90-9 15 mm 95p   90-9 13 mm 9 330p   2 wire species   18p   2 wire species   2
74159 1900 7415257 900 4724 2500 74150 1000 7415258 1800 40097 900 74161 1000 7415259 1800 14411 11000 74162 1000 7415269 1600 14412 11000 74163 1000 7415267 1000 14413 11000 74164 1200 7415273 1700 14433 11000 74164 1200 7415279 909 14500 7000	OCP71 90p ORP61 120p ORP12 120p TL78 55p OPT0-ISOLATORS 16D74 130p TIL111 90p MCT26 100p TIL112 90p	2716 (+5V)   27   8 00MHz   300p   2532   225   8 867MHz   300p   2732   225   10.00MHz   310p   10.70MHz   350p   16.00MHz   350p   16.	0.127 2A 410p + combs 370p 15-0.15 1A 325p Combs 7p EDGEBOARD CONNECTORS 0.158" PITCH 2 x 10 way 85p 2 x 22 way 135p
74165 130p 74LS288 90p 14599 290p 74166 120p 74LS288 160p INTERFACE LC; 74167 200p 74LS323 400p AD536A £13 74170 240p 74LS324 200p AD561J 1400p 74LT32 450p 74LS348 200p AD7524 600p 74LT33 120p 74LS365 48p DM8123 175p	MCS2400 190p TiL116 90p LEDS 0 125 0 22" TiL32 55p TiL220 Red 16p TiL211 Gr 20p TiL222 Gr 18p TiL211 Gr 20p TiL228 Red 22p	3245 450p 18.00MHz 300p 6522 650p 18.432 350p 18.432 350p 6820 375p 26.690MHz 350p 6821 340p 27.145MHz 325p	2 x 15 way 100p 2 x 25 way 160p 2 x 18 way 120p  COUNTERS 74C925 550p MC4024 325p MC4024 MC4
74174 90p 74LS367 70p DMB131 375p 74175 85p 74LS368 100p DP8304 450p 74176 90p 74LS373 150p DS8835 250p 74177 90p 74LS374 150p DS8836 150p 74178 160p 74LS375 120p DS8836 225p	TIL212 Ye 25p Rectangular LEDs (R. G. Y) 30p NS65881 570p TIL311 600p	6850 300p 48.0MH, 300p 55.5MH 400p 116.0MH; 350p 8205 320p 8212 2225	CM7216B   2000p   10116   70p   10231   350p
74181 160p 74LS378 140p MC1489 75p 74182 90p 74LS390 120p MM69174 C13 741844 150p 74LS393 120p 25510 350p 74185 150p 74LS399 200p 75107 160p 74186 500p 74LS345 140p 75110 375n	DISPLAYS         TIL312/3         110p           3015F         200p         TIL321-12         130p           DL704         140p         TIL331-12         130p           DL707 Red         140p         7750/60         200p           FND357         120p         ORIVERS           FND500         110p         9368         250p	8216 200p 8224 270p 8226 250p 8228 521p 8251 470p 8251 470p 8253 1000p 4116 (200ns)	£2.00 7805/7812 £5/10 £4.00 7905/7912 £6/10 £5.00 (Above prices for one value) £2.50
74198 325p 7415870 4000p 75150 175p 74190 120p 4000 SERIES 75154 175p 74191 120p 4000 15p 75182 230p 74192 100p 4000 22p 75322 300p 74193 100p 4002 20p 75324 375p	FND507 110p 9370 300p MAN3640 175p UDN6118 320p MAN4640 200p UDN6184 320p BOOKS by TEXAS Understanding	9255 480p 8257 800p 8257 8259 800p Programming service	P&P and VAT extra for 2716 available by appointment or by mail.  HANDOR TEST EQUIPMENT
74195 95p 4007 20p 75361 3006 74196 95p 4008 80p 75365 200p 74197 80p 4009 40p 75451:2 72p 74198 150p 4010 50p 75451:2 72p 74199 150p 4011 40p 8126 160p	Power Semiconductor Data Book (600 pages) £4.50 Chers: TTL ( CMOS £3.00 Microproces:	23.50 EXP300 E578p DM2 Communications System (EXP350 EXP350 315p DM2 EXP350 EXP350 BM3 E	35 Digital Multimeter £50 50 Digital Multimeter £69 52 Hand Held DMM £48 0 Frequency Meter £145
74721 160p 4012 25p 8728 250p 74251 140p 4013 50p 8165 180p 74259 250p 4014 84p 8197 180p 74278 290p 4015 84p 811595 120p 74279 110p 4016 45p 811596 140p 74283 140p 4017 70p 811530 140p	Software Design for Microprocessors (400 pages) £11.00 The Great Int'l Maths on Keys (208 pages) £3.50 Understanding Microprocessors (240	Op P&P on each book (NO VAT)	25 Pulse Generator £81 P&P £2.50 per item + VAT  OS, Linears, Memories, etc. and can normally offer
74283 140p 4017 70p 81LS97 120p 74284 360p 4018 89p 81LS98 140p 74285 360p 4019 45p 9602 220p	pages) £3.50 Understanding Solid State Electronics (240 pages) £3.50  Please add 30p P&P & VAT 15	ex-stock deliveries. We welcome inquiries for buyers	OMATIC LTD

NEW RETAIL SHOP 367 Edgware Road, W2 Open: 9.30—5.30

Government, Colleges, etc. Orders accepted

CALLERS WELCOME

TECHNOMATIC LTD.

17 BURNLEY ROAD, LONDON NW10
(2 minutes Dollis Hill tube station) (ample street parking)
Tel: 01-452 1500/01-450 6597 Telex: 922800)


# **CW Filter**

ne of the most desirable features of a communications receiver is a set of really good IF filters for the various modes of modulation. Presumably due to the expense and complexity of such circuitry, this is lacking in many sets. In such cases it is often possible to obtain a worthwhile improvement in performance by using an audio filter with a response tailored to suit the required mode of reception. A filter of this type is of most help for CW (Morse) reception, where only a very narrow bandwidth is needed. In fact, an infinitely narrow bandwidth is the theoretical ideal, since the CW signal is just a single frequency! In practice, a bandwidth of a few hundred Hertz is necessary, since it is very difficult to tune to a signal and stay accurately tuned to it with a narrower bandwidth.

The circuit uses an integrated circuit audio amplifier (TDA2006) in the non-inverting mode, with R2 and R3 being used to bias the non-

inverting input. C4 to C7, R4,5 and PR1 form a T-notch filter, which provides frequency selective negative feedback over IC1. R4 and R5 also bias the inverting input of the device. A T-notch filter allows most frequencies to pass readily, but at and close to its operating frequency it gives a high level of attenuation. Thus, in this case it gives virtually 100% negative feedback and only about unity voltage gain at most frequencies. However, at its operating frequency there is little feedback and high voltage gain. This gives the required narrow passband.

PR1 controls the bandwidth of the filter and a fairly flat response will be obtained at maximum resistance. Decreasing its resistance gives a sharper and narrower response, but too low a resistance will give an unusably sharp response. The circuit might even start to oscillate. R1 attenuates the input signal to a level that gives roughly unity gain at the centre of the passband, but the exact voltage gain depends on the setting of PR1. The output can be fed to low, medium, or high impedance headphones, or a loudspeaker. Current consumption is about 15 mA.

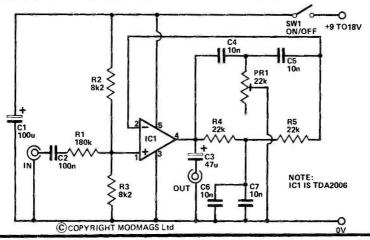

J. DIMM A THROUGH! If you want an Autoranging Auto Unit Display, 3½ digit l ve got to hand it to you! Incredible

latest professional state-of-the-art 31/2-digit DMM - at really old-Introducing the fashioned prices! From just an unbelievable £39.95 inc. VAT, plus £1.15 p&p!

imV, 100µA and 0.10 resolution!

6200

- Measures AC voltage to 600V!
- Measures DC voltage to 1000V!
- Measures resistance
- to 2 Megohms!
- Low power Ohm ranges!
- # Displays mV, V and mA!
- 0.8% accuracy!
- \* Zero adjustment!
- # 3 other models too!

This one-off price is so unbelievably low because the A D converter and display are custom-built. This is a genuine, no corners cut top-spec DMM, that gives you all the features above and 200 hrs continuous battery life on the 312-digit LCD display, auto 'Batt' warning; pair of test leads batteries, spare fuse and 6 months' guarantee! This offer can't last for ever, so buy now Remember, a DMM

in the hand

# Plus three other DMMs in the range!

6220 As the 6200, plus 10 Amp

ONLY £49.95 inc VAT! AC DC measurement' ONLY £64.95 inc. VAT! 6100 With Continuity check'

6110 As 6100, plus 10 Amp AC DC measurement Add £1 15 p&p please

ONLY £74.95 inc. VAT

I believe voi	.i Planca	cond ma	the I	MM.		marked
1 DEBEAE ACK	I LIEUSE	seno me	THE L	71111	(1)	HIGHNOCK

6200 (a £41.10 each inc VAT, p&p Total price £. 6220 (a £51.10 each, inc VAT, p&p Total price £ \_6100 (a £66.10 each, inc VAT, p&p Total price £ 6110 (a £76.10 each, inc VAT, p&p Total price £

Total cash cheque enclosed & Cheques payable to

Maclin-Zand Electronics Ltd., please 38 Mount Pleasant, London WCIX 0AP Tel 01-278 7369 01-837 1165



ACCESS orders taken. Please write card no. and signature.

ACCESS NO Name

Signed To: Maclin-Zand Electronics Ltd., 38 Mount

Pleasant, London WCIX 0AP For overseas orders, please

add £5 to cost of total order package. 4 EF

- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- CALL IN AND SEE FOR YOURSELF


• ALL MODELS ON DISPLAY

● RETAIL - MAIL ORDER EXPORT INDUSTRIAL

OPEN SIX DAYS A WEEK

# ALL PRICES INCLUDE VAT



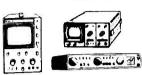

A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace.

Mains and battery/mains portables.

Many on demonstration.

DUAL TRACE (UK c/p etc £3.50)

SINGLE TRACE (UK c/p etc £2.50) Hm 307-3 10mHZ, 5mV, 6 × 7cm display plus CO1303D 5mHZ, 10mHZ, 7 × 7cm display £109.25

SC110 10mHZ Battery portable, 10mV 3.2 × 2.6cm display (Optional case £8.80, Nicads £7.95. Mains unit £4) £149.95 **LB0512A** 10mHZ, 10mV, 5" display **CS1559A** 10mHZ, 10mV, 5" display V151 15mHZ 1mV, 5" display £195.50 £198.50 £241.50

OPTIONAL PROBES (ALL MODELS) X1 £6.50, X10 £8.50, X100 £12.95, X1-X10 £10.95

All Scopes now with Free Probe(s)

£76.95

HAMEG TRIO LEADER SINCLAIR HITACHI

CS1562A 10mHZ, 10mV, 5" display CS1575 5mHZ, 5" 1mV display £227.00 £270.00 **CS1576** SIMZ, 5 MIV display **£270.00 Hm312-8** 20mHZ, 5mV, 8×10cm display **£253.00 CS1566A** 20mHZ, 5mV, 5" display **£323.15 LBO 3085** 70mHZ 2mV 5 × 6.3cm display.

Battery/mains Portable, built in Nicads £482.00 Hm412-4 20mHZ, 5mV, 8 × 10cm display plus sweep Delay £399.50 £455.40

sweep Delay £31
C\$1577A 30mHZ, 2mV, 5" display £41
C\$1830 30mHZ, 2mV, 5" display plus sweep £5 £507.15

delay Hm512-8 50mHZ, 5mV, 10 × 8cm display. £667.00 £294.00

V152 15mHZ 1mV (5mV), 5" display
V152 15mHZ 1mV, 5" display
V302 30mHZ 1mV, 5" display £325.60 £447.35 V550 50mHZ 1mV 10 × 8cm £799.25

Delay sweep + 3 channel display

# GENERATORS (UK c/p £1.75)





TRIO • LEADER • CSC SINCLAIR . LEVELL

# RF

SG402 100KHZ - 30mHZ with AM modulation £64.40 SG16 100kHz-100mHZ (300mHZ on £56.50 SG2030 250KHZ - 100mHZ low cost range ARF 300 18HZ-200mHZ £46.95

**PULSE** 

2001 1HZ-100KHZ Function £86.00 TG105 5HZ-5mHZ 4001 0.5HZ-5mHZ £92.50 £105.00 A range of Signal Generators to cover Audio, RF and Pulsing. Mains operated (TG series Battery).

**AUDIO** (All sine/square) **AG202A** 20HZ – 200KHZ **LAG26** 20HZ – 200KHZ £65.55 £69.00 AG203 10HZ-1mHZ sine/square

AG120A 10HZ-1mHZ £137.00

LEVELL ('M' with Meter) 152 SERIES 3HZ - 300KHZ Sine/ Square

200 SERIES 1HZ-1mHZ Sine/Square TG152D £92.00 £113.85

TG152DM TG200D TG200DM £149 50 TG200DMP £155.25

F56 50

£86.50

# SWR/FS AND **POWER METERS**



Range in stock covering up to 150mHz and up to 1 K watt power, PL259 sockets. Also 250 UHZ Grid Dipmeter SWR9 SWR 5 3 – 150mHz SWR9S SWR/Power meter 31/2 – 150mHz 0 – 1000 watts 110 SWR/Power 1½ – 144mHZ 11/2 - 144mHZ 0/10/100 watts 171 As 110 Twnn meter plus F/S £14.50 Plus large range of BNC/PL259/etc leads/plugs/adaptors/connectors always

in stock, 176 SWR/Power/FS 1½2-144mHZ, 5-50 watt. Plus 25-40mHZ AC match KDMS Grid Dip 1½2-250mHZ

£4.50 £5.95 £6.95

# A range of LED and LCD Seach and Hand DMM's bettery operated with optional Micada. All supplied DIGITAL MULTIMETERS KAISE • SINCLAIR • LASCAR • THURLBY BENCH PORTABLES (UK c/p £1.00

low cost range audio and RF





t opon jetraj (BB) conquerter

HAND HELD (UK post etc. #5p)

TM352 31/2 Digit LCD plus 10 ADC and Hfe checker £54.95 PDM35 31/2 Digit 16 range LED (no AC current)
ME502 31/2 Digit LED plus 10A £32.95 DC and Hfe checker LM2001 3½ Digit LCD 2 amp £43.95

AC/DC 0.1% £51.70 6200 31/2 Digit LCD 0.2A AC/DC, £39.95 Auto range 6220 As 6200 plus 10A AC/DC 6100 As 6200 plus Cont. test/range hold £59.95

£74.95

DM235 3½ Digit LED 21 ranges, 0.5% AC/DC 2A DM350 3½ Digit LED 34 ranges AC/DC 10A TM353 31/2 Digit LCD AC/DC 2 TM351 31/2 Digit LCD AC/DC 10

£107.95 LM100 31/2 Digit LCD AC/DC 2 DM450 41/2 Digit LED 34 ranges £107.95 AC/DC 10 amp (DM series options, Carry case £8.80, Nicads £7.95, Mains adapte £4.00)

# MULTIMETERS (UK post etc 75p)



KRT101 1K/Volt 10 range pocket ATM1/LT1 1K/Volt 12 range pocket NH55 2K/Volt 10 range pocket
AT1 2K/Volt 12 range pocket de luxe
NH56 20K/Volt 22 range pocket
VN360TR 20K/Volt 19 range pocket
ST.95 plus hfe test AT1020 20K/Volt 19 range de luxe £13.95

£16.95 plus hfe test 7081 50K/Volt 36 range plus 10 amp TMK500 30K/Volt 23 range plus 12A

DC/Cont. test AT20 20K/Volt 21 range de luxe plus 10A DC and 5KV DC £21.50 £21.95 AT205 50K/Volt 21 range de luxe plus

10A DC 524.95
7080 20K/Volt 26 range large scale, 10A DC 7080 50K/Volt 18 range de luxe

£28.50 plus hfe test

AT210 100K/Volt 21 range de luxe plus 12A AC/DC £29.95 360TR 100K/Volt 23 range plus het checker and AC/DC 10 amps £34.95

# CHOOSE FROM THE UK's LARGEST SELECTION

# FREQUENCY COUNTERS



Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.

6110 As 6100 plus 10A AC/DC



HAND HELD (UK post etc #5p)

PFM200 20HZ to 200mHZ 8 Digit LED MAX50 100HZ to 50mHZ 6 Digit LED MAX550 30KHZ to 550mHZ 6 Digit LED £54 50 £61.00 £106.00

BENCH PORTABLES (UK c/p £1.00) MAX100 8 Digit LED 5HZ to 100mHZ TF200 8 Digit LCD 10HZ to 200mHZ 7010A 9 Digit LED 10HZ to 600mHZ £89.00 £158.95 £169.00 TP600 600mHZ Pre-Scaler for TF200 £41.00 200SPC 6 Digit 100mHZ LED built into 0.002 HZ £437.00 to 5.5mHZ pulse generator

CSC SINCLAIR OPTO ELECTRONICS

# LOGIC PROBES MONITORS

Logic probes indicating high/low etc states that acopes can miss, all circult powered for all IC's. LP3 50 mHZ logic probe LP1 10 mHZ logic probe LP2 1½ mHZ logic probe LP35.50 LMI Logic monitor £33.00

LMI Logic monitor LDP076 50 mHZ logic probe £51.00 Also in stock range of Protoboard kits and breadboards.

MINI DRILLS AND KITS

(9-12 Volt 1/4" chucks)

Small Drill plus 3 collets
Medium Drill plus 3 collets
Medium Drill plus 20 tools
Medium Drill plus 20 tools
Medium Drill plus 20 tools

113.95 Medium Drill plus 20 too Mains Drill Mains Drill plus 20 tools

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export — prices on request ■ All prices correct at 1.12.80 E & OE ■ All prices include V.A.T

Cubegate 301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724-3564

OPEN SIX DAYS A WEEK



FREE CATALOGUE

Send large SAE (17%p UK) Schools, Companies, etc. free on request.

# **AUDIOPHILE**

It's almost time for Rudolph the red-nosed guinea pig (everyone's had to economise) to drag his sleigh across your roof. If you haven't sent your letter to Santa yet, Ron Harris offers a few sound suggestions.

t's that time of the year again, is it not? Out with the plastic holly, stale booze and cast-iron fruit cake. At work everyone goes around smiling and saying "cheers" too often, all the time checking people over with hungry eyes to see who is gonna grab who at this year's booze-up. Goodwill to all men and all that.

Another quaint little custom widely practised in some social circles is that of spending money that doesn't exist upon things which are totally unnecessary and giving them away to people who don't want them anyway, in return for which you are guaranteed to receive several pieces of ultra-modern junk yourself. Sheer unadulterated lunacy really.

Why not change things this year? As you are most unlikely to get Felicity Kendal, regardless of who you ask (I've written to Santa seven years running with no luck, so far — why should you be any different, eh?), something remotely hi-fi might make the pain and heartache of disappointment a little less hard to bear. Now, unless you're friends with a few dozen Arab Sheiks it is also unlikely that, on the morning of the 25th, you will awaken to find a neatly packaged Meridan, SME or Linn sat sitting beneath the Woolies tree . . .

Audiophile this month is dedicated to providing a few dozen or so ideas for additions and improvements to hi-fi systems of all denominations that are financially feasible, be it your intention to give or to receive. It is *especially* more blessed to give when you can afford it.


# **Format For Mats And Things**

A glance at any audio emporium will show you that there are more than just a few accessories and gadgets to choose from these days and it would have been totally impossible to cover them all; by the time we published this, someone would have released a hundred more. Beside which, not all the vended items can even remotely meet their manufacturer's claims. I've been very selective, therefore, about which items to include. If you don't find a particular item here, that in itself is no condemnation. However, everything which is included, is recommended!

There is in addition a 'special' section for what I think are 'special' items and these are written up in more detail than the rest. Prices appended to each are typical prices you can expect to pay in the shops, inclusive of VAT. It might be an idea to leave this article lying around with certain items heavily ringed in flourescent yellow, or something. Alternatively be direct and hit a few friends over the head with it — you never know, as well as broken bones you might just get a stylus cleaner or two.

Items appear in no particular order of merit or anything else.


(Oh yes, Merry Thingy and all that.)

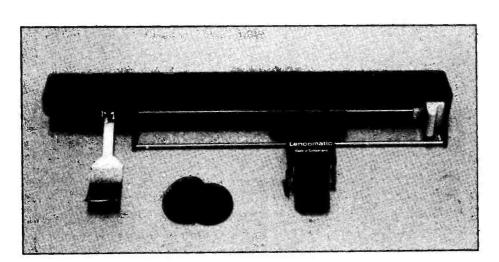

Above the Lencomatic record cleaner. This is the most unusual of the hordes of tracking cleaners around the shops these days. Rather than fit it to the deck on a nice plain, ordinary, boring pillar it attaches to the perspex lid and that evil looking tongue rests on the spindle to locate the device! There is a little carbon-fibre brush and a large pad on the business end. Perfect for lazy people or those who wish to aspire to such heights of inaction. The only drawback is the somewhat odd appearance. Price: £8.93.




Above: Discguard. I'm always suspicious of things to spray onto records, but this seems harmless enough — if I can overcome the hidebound conservative attitude that the less stuff I put under the stylus, the less will end up stuck all over it! Discguard is a permanent anti-static treatment which is undetectable audibly (we tried it!) and greatly reduces the LP's ability to attract dust. Price:-£4.50.

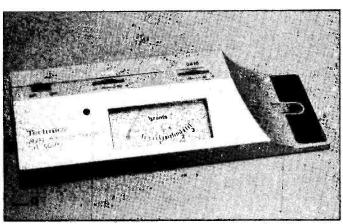


Above: Technics SH-50P1 stylus pressure gauge. A long way from little weights this. A strain gauge measures the downforce present and reads out the tracking weight on a meter. It is accurate to about 0.1g if set-up properly — a reference weight is provided — and looks very very flashy in use. Just the thing to impress the neighbours — and yourself! I like this idea — how about a digital version eh, Technics? Price:- £17.95.



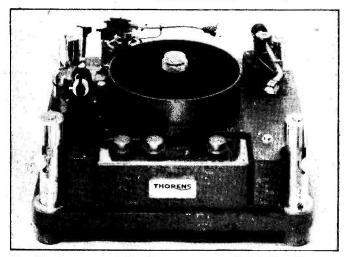Above: Turntable mats are a favourite tune-up these days and these are consequently a large number of them around. This is one of the newest. The Metrocare has a very high surface tension — VERY high. It grips an LP like a Scotsman grips his drink and thus provide an excellent bond. Price:- £16.75.




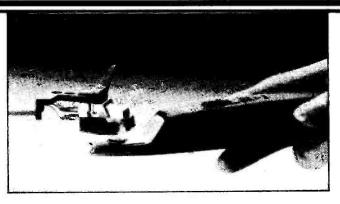The ultimate accessory? The Thorens Reference deck, built with no compromise whatsoever to price. It weighs 90 kgs, claims to possess unmeasurable rumble and w/f at 0.02%, is a subtle  $620 \times 360 \times 510$  mm in size. The chassis is aluminium cast, filled with iron grain. In other words it is very big, very heavy, and very expensive (circa £4,000). Supposed to sound pretty good too.




Above (and below!): Now this has got to be the Idea Of The Year! Without passing any comments — and you mucky minded lot out there can keep quiet too — this is a vibrating stylus cleaner from Audio Technica. There is a pad at the end, attached to a vibrator within the body of the device. You lower the stylus onto the pad and leave it alone for a few seconds. The clever little widget meanwhile proceeds to shake all the muck off the stylus!

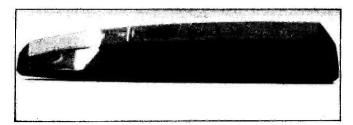
Ingenious in the extreme and it works superbly. Sheer magic. Never in the field of human grooves has so much been cleaned so well by so little. There is a bottle of cleaner supplied to deal with really bad cases of encrustation. Thoroughly and totally recommended. Every home should have two. Price:- £9.95.




Not all turntable mats are designed to be anti-resonance à là the Metrocare. This Goldring is primarily anti-static and is composed of carbon fibres to provide a leak-path to earth for the charge present on the LP.

Price:- £3.90.

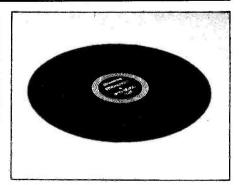

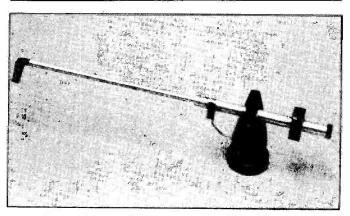

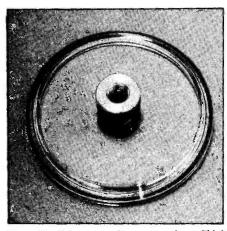
Above: the Exstatic carbon fibre sweep arm. Of all the millions of Dust-Bug descendents available this is my favourite. It looks very classy indeed and does the job better than most. An earthing lead is provided to form a conductive path to ground static encountered in mid-sweep and the counterweight provides playing weight adjustment to optimise tracking. Price:- £8.40.



Above: the Metrocare anti-resonance clamp. This is formed of clear perspex with a brass center. The idea being that it is fitted over the spindle atop your records, to clamp them firmly onto the mat, thus dewarping warps and supressing resonance. Used together with a good turntable mat the clamp can offer a worthwhile improvement in sound quality, especially in the bass. Price:-£4.54

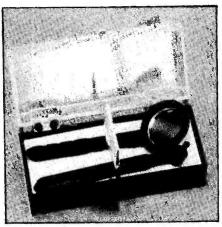
Below: a neat little notion this. As the cleaning tape passes the heads, it rotates a cunningly placed rotary magnet which simultaneously de-magnetises them. The magnet is moved away automatically within the cassette by the spooling action.





Above: a smallie-but-goodie. Just the thing to buy with the change from an LP! The Exstatic stylus care kit only costs 90p and will earn that back with the first wipe of the brush! Go on — you know it makes sense. Make a good present for the person that bought your Des O'Connor Greatest Hits last year. If he plays that sort of stuff, SOMEONE better take care of his stylus and quick!


Price:- £0.90.

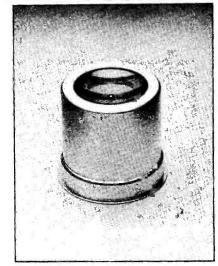

Above: Triple Checker! Well, it is. A record weight, spirit level and 45 RPM adaptor all in one. That little ball bearing you can see lurking under the glass rolls around in a shallow dish to indicate how level the deck is (inaudibly I might add) and the thing is so heavy no warp will dare defy it! The Triple Checker comes from Goldring and costs;

Price:- £6.00



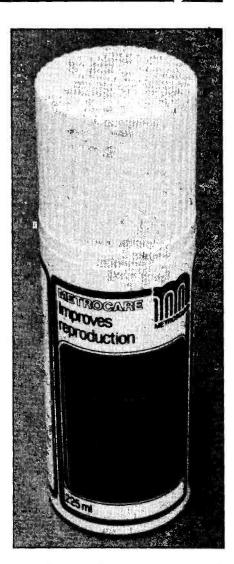

Above: do you suffer from dirty, ingrained, groove dust? Do your records lack that new-look sparkle? Are your highs too low and your lows distorted? Give your LPs a face-lift with the Metrocare Rejuvenating Fluid!

This is literally applied like a face-pack from


This is literally applied like a face-pack from the bottle, being smeared across the surface and allowed to dry into a thin plastic film. This is then peeled away, taking most of the gunge with it!

Price: £4.24.

Below and left: the Exstatic record brushes. Both consist of carbon fibre bristles, with the wiper possessing a pad down the centre for better dust collection. Both come with a stand.

Prices:- £6.00 and £7.50 (super).



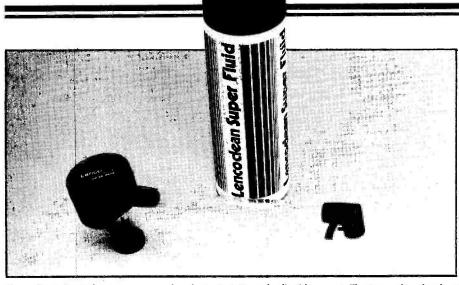

Above: how about playing your record under water? Or under liquid anyway. The Lencoclean has been around a long time and continues to have its followers. It is a wet-playing system, which means that the arm (filled with fluid) tracks ahead of the stylus, dispensing a band of liquid into the groove. Any matter present is held in suspension when the stylus arrives and has minimal effect. No more snap, crackle and pop. No more static. Quiet backgrounds guaranteed.

The penalty to be paid is that once used, always used. Dry playing becomes impossible because the mud in the grooves has to be suspended else it gathers around the stylus somewhat rapidly. As I said, the system has a lot of followers and works superbly. It is up to you whether you take the plunge!

Price:- £5.93.



Left and below: TDK make two head demagnetisers, one very pretty cassette unit (left) which is fully automatic and absolutely beautiful! The conventional unit below (not to scale!) is designed for reel-to-reel mainly and is superbly constructed.

Price:- £11.25 (cassette) £21 (reel-to-reel).




Above: the tracking cleaner for automatic record players. It attaches to the headshell. From Metrocare at Price:-£1.68.




Above: the renamed Spectra mat. Dumpa it is called now apparently, but it is still one of the very best of the turntable mats to be purchased working well on a wide range of decks.

Price:- £19.80.

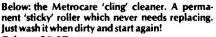

Price: £5.87.

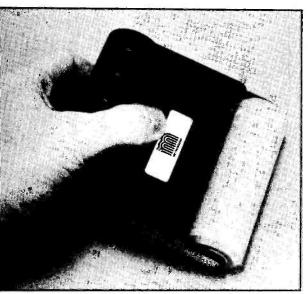

# Offers On Offer

The ETI switchboard has glowed red in the night since we ran our hi-fi system offer a couple of issues back. The most oft asked questions were whether the equipment was purchasable separately and where it could be heard.

The answers are yes — prices below — and at Videotone's showroom in Crofton Park Road (see advert in this issue). We chose the system for its sound vs price performance and if you make the trip to Videotone you'll see what we mean. Take a copy of ETI along and you can buy at the prices quoted below. But be quick about it as time, tide and stock levels wait for no man!

 ST 4120 tuner
 £55 + £3 p&p

 ST 4130 amplifier
 £50 + £3 p&p

 SC 3200 cassette deck
 £75 + £3 p&p

(reduced again from £88. Too good to our readers we are!)

GB2 loudspeakers (pair) £45 + £7 p&p

Incidentally, since Audiophile uses a Coral MC81 quite extensively as a reference, Videotone are prepared to let ETI readers buy one at a good discount on normal prices. An MC81 and H300 head-amp will cost you £44.50 and £45.00 respectively instead of £48.87 (+ p&p) and £51.75 (+ p&p). Add a quid to each for postage as usual and tell them ETI sent you!

# **TRANSFORMERS**

Panel Meters, Bridge Rectifiers, Power Supply Units Multimeters - Semi Conductors - Timers - Safebloc

IVIGICIIII	arata - 20	71111	CU	IIUU	CLOIS - TH	Hets -	Satebloo	
Minimum & Sub	Miniature				50 VOLT			
	Milli- A	ef. P	rice		Sec: 0-19			
		lo.		P&P		Ref.	Price	
Volts			_		Amps	No.	£	P& P
3-0-3	200 2:	38 2	.60	.70	0.5	102	3.60	.90
0.6, 0.6	1A 1A 2	12 3	.00	.75	1.0	103	4.60	1.05
9-0-9	100	13 2	.30	.70	2.0	104	7.30	1.20
0.9, 0.9		35 2		.70	3.0	105	8.60	1.20
0-8-9, 0-8-9		07 2		.75	4 0	106	10.85	1.30
0-8-9, 0-8-9		08 3		.75	60	107	15.10	1.50
0-15, 0-15		36 2		.70	8.0	118	20.20	1.70
0-20, 0-20		14 2		.90	10.0	119	24.10	2.20
			.50	.90	60 VOLT			
0-15-20, 0-15-20				1.05	Sec: 0-24			
0-15-27, 0-15-27		03 4		.85	Amos	Ref. No.	Price	P& P
0-15-27, 0-15-27		U4 E	D.TU	1.05	0.5	124	3.85	.90
12 AND/OR 24 V	VOLT			- 1	1.0	126	5.60	1.05
Pri: 220-240 Volts	3				2.0	127	7.55	1.05
Amps	Pr	ice		- 3	3.0	125	11.10	1.30
12v 24V	Ref. £		PS	P	4.0	123	12.35	1.50
0.5 0.25		.30		75	5.0	40	14.15	1.60
1.0 0.5		.75		90	6.0	120	17.60	1.60
2 1	71 3	.25		90			RMERS	1.00
4 2	18 4	.05	. 1	85			ped 0-115-21	0-240V
6 3	70 5	.60		95	VA		Price	0-2-01
8 4		.40		20		Ref.		
10 5	72 8	.25		20	(Watts)		£	P&P
12 6	116 8	.85		20	20 75	113 64	2.65	.90
16 8		.85	1.3		150	4	4.10	.90
20 10		.85		50	Input/O		5.60	1.05
30 15		.85	1.5		0-115-21			
60 30	226 33	.35	1.8	80	300	53	10.10	1.20
30 VOLT (Pri: 22	20-240V)				500	67	10.10	1.50
Sec: 0-12-15-20-					1000	84	18.60	1.60
Ref.	Price						/3000VA	1.00
Amos No.	£		P& F				NG (Centre	Tapped &
0.5 112	2.85		.90		Screened	1)	•	
1.0 79	3.60		.90		Pri. 120/			20/240V
2.0 3	5.60		1.05		VA.	Ref.	Price	
3.0 20	6.30		1.20		(Watts)	No.	£	P&P
4.0 21	6.60		1.20		60	149	6.60 7.60	1.05 1.30
5.0 51	9.60		1.20	) ]	100	150	11.10	
6.0 117	11.10		1.20	)	200	151	13.30	1.30 1.50
8.0 88	14.35		1.50		250	152	16.30	1.60
10.0 89	16.60		1.50	)	350	153	37.10	3.20
		_	_		1000	156	37.10	3.20
Please a	add VAT at 1	5%			-		7a William	n Ctront

JUMP TO IT!

BAYDIS

Barclaycard and Access facilities

available Trade and Education Welcome 7a William Street


Herne Bay 64586

Herne Bay, Kent

Climb aboard the breadboarding bandwagon with CSC's new WK-1 wire jumper kit - just what you've always wanted to make breadboarding easier and quicker than ever before. Here, in one neatly compartmented box, are all those different lengths of insulated hook-up wire you need - 25 pieces of each, in 14 lengths ranging from 0.1 inch to 4 inches. What's more, the CSC kit make your job even easier by colour-coding all the different lengths and providing a quarterinch length at each end with the insulation stripped off and bent through 90°. So CSC jumper wires come ready to plug straight into your quick-test sockets, bus strips or breadboard system. No more fiddling around with wire cutters, strippers or pliers - everything you need in one box. Take the plunge right now by filling in the CSC coupon.

CSC (UK) Ltd., Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: (0799) 21682. Telex: 817477.

-	Jumper Kit	£5.00 Nett.	
			Please deduct £1 postage from each additional order
i enclas	e cheque/P	O for £	
or debr	my Barcla	ycard, Acce	ess, American Express card
	·		r
			Exp. date
or Tel:	(0799) 216	82 with yo	ur card number and your order
will be	in the post	immediatel	٧.
NÂME			
MAINE			
ADDRI	223		
AUDIII			
	IAL SPECIA, NES C	OPPORATION	
CONTINEN			
CONTINEN		, Carlot Co.	FREE catalogue tick box
CONTINEN		4	FREE Catalogue tiek box t
CONTINEN			FREE Catalogue tick box t.
	ntal Specialt	es Corporatio	2
Contine	ntal Specialt	es Corporatio	on (UK) Limited, Dept. 9RR e, Saffron Walden, Essex CB11 3AQ.

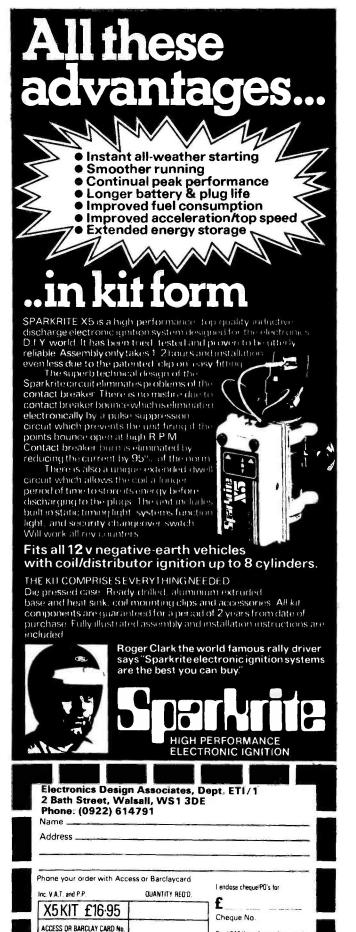

Send SAE if brochure only required.

The premier mail order house specialising in quality products and superior after-sales care.

# **SEIKO QUARTZ** LCD MEMORY-BANK CALENDAR WATCH

# SPECIAL PRICE ONLY £29.95

plus 85p p&p. Usually £89 or over.

- Displays hour, minute, second, month, day of the week and date in 12 hour indication - or 24 hour at the touch of a button.
- Button touch also displays month and year and dates for a designated month with Sunday dates flashing.
- Stores dates in memory up to 11 ahead, flashes 'MEMO' on designated dates.
- Illuminated time and calendar display.
- Display flashes when battery nears life end.
- Stainless steel case and wrist strap (adjustable).

In presentation case with instructions.

# **A LIFETIME** WATCH AT A **BARGAIN-OF-A-**LIFETIME PRICE

Full refund if not completely satisfied.

Mitrad, 68-70 High Street, Kettering, Northants. Tel: 0536 522024

This is a representative selection from the collection of guaranteed leading make and own brand watches offered through Mitrad's 7 day distribution system and backed by Mitrad's own service organisation. For complete product range, ring or write for catalogue.

Trade price list available for

bulk orders.



<b>.</b>	MD610 watch(es) at £17.80 inc p&p  Seiko Quartz watch(es) at £30.80 inc p&p	MD607 watch(es) at £10.80 inc p&p  MD608 watch(es) at £16.35 inc p&p
n / I enclose che	MD605 watch(es) at £12.80 inc p&p e of my order £ eque/PO or debit my Access/Barclaycard No	
d / Address	Signat	41.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.1.



**MD609** Gentleman's **super slim** flag date alarm. Only 4mm case thickness. Continuous display of hours, minutes, seconds and day; optional display of date, month, year. 24 hour alarm, alarm mode indication. Back light. Infinitely adjustable stainless steel strap. Very latest technology.

£10.95 + 85p p&p

MD610 Gentleman's dual time melody alarm chrono. Only 5mm case thickness. Continuous display of hours, minutes, seconds plus date and mode indications. 'Running horse' chrono to 1/10 sec, 12 hour alarm plays 30 seconds of 'Yellow Rose of Texas'. Infinitely adjustable stainless steel strap.

£16.95 + 85p p&p

MD605 Ladies musical alarm chrono. Continuous display of hours, minutes, seconds; optional display of day, date, month. Auto calendar. Chronograph with lap timing facilities, to ½10 sec. 24 hour alarm plays 30 seconds of Beethoven's 'Fur Elise'. Back light. Infinitely adjustable stainless steel strap.

£11.95 + 85p p&p

MD606 Ladies five function fashion LCD watch with 3 year battery. Continuous display of hours and minutes, with month/date and date/seconds available. Auto calendar. Only 6mm case thickness. Back light. Infinitely adjustable stainless steel strap.

£9.95 + 85p p&p

MD607 Ladies slim 'sugar coated' dress watch. Continuous display of hours and minutes; optional display of month and date. Auto calendar. Back light, Integral watch and strap. In gold or silver finish.

£9.95 + 85p p&p

MD608 Gentleman's musical alarm chrono. Continuous display of haurs, minutes, seconds, plus day indication. Also month and date. Chronograph with lap timing facilities, to ½ sec. 24 hour alarm plays 30 seconds of Beethoven's 'Fur Elise' or can be set to awaken to a single note. Back light. Infinitely adjustable stainless steel strap.

£15.50 + 85p p&p

# UNIVERSAL **TIMER**

Our two-range (1-10 and 10-100 min) timer has excellent stability and produces a 30 S pulsed alarm sound

at the end of each timing period.

The unit is mains powered, can switch 15 A mains loads and can give either make or break timing operation.

Design by Ray Marston. Project development by Steve Ramsahadeo.


ost analogue (pot controlled) long-period timers published in hobby magazines use a 555 one-shot IC and a large electrolytic capacitor as their main timing elements. Unfortunately, conventional electrolytic capacitors have very wide tolerances (typically -50% to +100%) and suffer from relatively large and unpredictable leakage currents. Consequently, these simple circuits cannot be relied upon to give accurate or repeatable timing periods or to give periods significantly exceeding 15 minutes or so.

Our ETI Universal Timer gets away from the conventional design approach, with its inherent disadvantages, by using an astable clock generator and a divide-by-8192 CMOS counter as its main timing elements, the astable period being controlled by a pot and a highly stable polyester capacitor. Consequently, our timer has excellent accuracy and stability and can fully span the 1 min to 100 mins timing range in two switch-

selected decade ranges.

Our timer has a few other unusual features. It is mains powered and has a relay-switched mains output lead that can be used to feed power to external loads (heaters, lamps, etc); the relay can switch mains currents of up to 15 A and a mode switch enables the timer to give either make or break timing operations of the external loads.

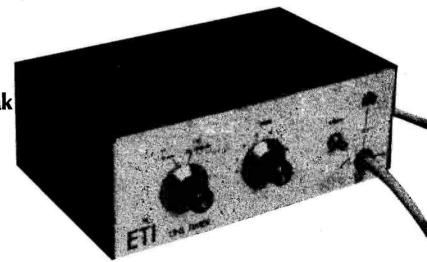Timing operations are initiated by a push-button start switch and a pulsed-tone alarm sounds for 30 S to give an audible warning on the completion of each timing cycle. The unit has a variety of practical uses in the home, workshop, darkroom, etc.



# Construction

Most of the circuitry (with the exception of T1, the relay, the switches and pot) is mounted on a single PCB, the construction of which should present few problems. Note that IC1-3 (CMOS types) should be mounted in suitable sockets and voltage regulator IC4 needs to be fitted with a small heat-

When construction is complete, fit the PCB in a suitable case, together with the mains transformer and the heavy-duty relay (which MUST be fitted in the specified socket) and proceed with the interwiring. Take special care over the interwiring of the relay contacts and SW2 and the mains connections. Finally, drill a small hole (roughtly 4 mm) in the top of the case, bond the PB-2720 acoustic transducer below it and connect it to the rest of the circuitry.

# **Testing**

When the unit is complete, give it a functional test as follows. First, connect the unit to the mains and check that its neon indicator illuminates when SW2 is set to TIMED BREAK position and turns off when SW2 is set to TIMED MAKE. Now set RV1 to its minimum position, set SW1 to the '1-10 min' range and firmly operate PB1. Check that the neon immediately changes state, indicating that the relay has turned on and

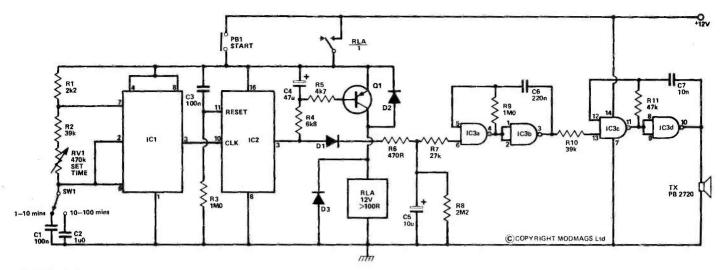


Fig.1 Circuit diagram.

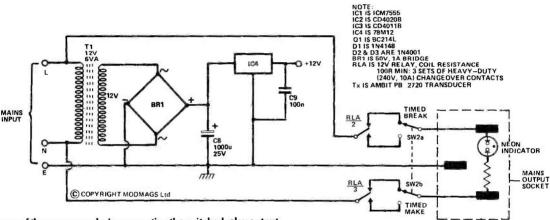


Fig. 2 Circuit diagram of the power supply, incorporating the switched relay output.

the timing period has begun; also check that the relay turns off again at the end of the timing period (roughly one minute) and that the acoustic alarm operates and generates a pulsed-tone signal for roughly 30 S when the timing period is complete.

# \_BUYLINES

Most of the components used are readily available from suppliers advertising in this issue. In case of difficulty, Watford Electronics can supply the relay specified.

# **HOW IT WORKS**

The circuit comprises four main blocks, these being an astable clock generator (IC1), a multi-stage binary divider (IC2), a relay driver (Q1) and a gated alarm-call generator (IC3), all powered from a 12 V regulated line provided by IC4.

The clock generator is designed around IC1, a CMOS version of the 555 timer. The chip is wired in the astable mode and generates clock signals with periods variable over the 7.3 mS to 732 mS range via RV1 and SW1. The output of IC1 is used to clock the multi-stage CMOS binary counter designed around IC2, which is effectively wired in the 'divide-by-8192' mode; the output (pin 3) of this counter is normally low but goes high on the arrival of the 8192nd clock pulse.

The output of IC2 is used to drive relay RLA on via Q1 and to gate on the alarm-call generator (IC3) via the D1-R6-C5-R8-R7 network. This generator comprises a fast astable (IC3c-IC3d) and a slow astable (IC3a-IC3b). The slow astable is gated on by a momentary high output from IC2 and then gates the fast astable on and off at a rate of about 2 Hz.

The alarm-call generator part of the circuit is permanently connected to the 12 V supply lines, but the IC1-IC2-Q1 parts of the circuit are only connected to the supply rails when PB1 or relay contacts RLA/1 are closed. The complete circuit functions as follows.

Timing operations are initiated by momentarily closing PB1, thereby connecting the supply to the IC1-IC2-Q1 circuitry. As PB1 is closed, a reset pulse is fed to pin 11 of IC2 via C3 and causes the counter's registers to set to zero, driving the output of IC2 low. As IC2's output goes low it drives Q1 and the relay on via R4-R5, thereby causing contacts RLA/1 to close and maintain the supply to the circuitry once PB1 is released.

As soon as PB1 is closed, IC1 starts to oscillate and generate clock pulses, which are then counted by IC2. On the arrival of the 8192nd clock pulse the output of IC2 switches high, turning Q1 and the relay off and causing contacts RLA/1 to open and break the supply connections to IC1-IC2-Q1. The timing sequence is then complete.

C4 imposes a slight turn-off delay on Q1, so that the output of IC2 remains high for 100 mS or so before the relay turns off. This brief high period is sufficient for the IC2 output to fully charge C5 via D1 and R6, thereby activating the IC3 alarm-call generator, which produces an audible pulsed-tone signal in the PB-2720 transducer. Once the relay has turned off, the charge on C5 slowly leaks away via R8 until, after about 30 S, insufficient charge remains to gate IC3a on, at which point the alarm-call generator turns off. The entire operating sequence is then complete.


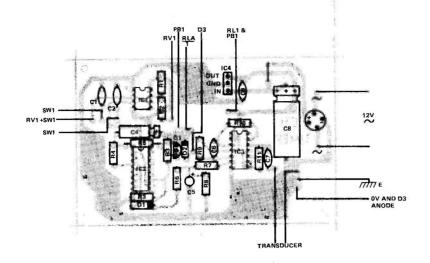


Fig.3 Component overlay.

Resistors all 1/4	W 5%	Semiconduct	ors
R1	2k2	IC1	ICM7555
R2,10	39k	IC2	CD4020B
R3,9	1M0	IC3	CD4011B
R4	6k8	IC4	78M12 or 7812
R5	4k7	Q1	BC214L
R6	470R	BR1	50 V, 1 A bridge rectifier
R7	27k	D1	1N4148
R8	2M2	D2,3	1N4001
R11	47k		
Potentiometer	1		
RV1	470k Linear	Miscellaneou	ıs
Capacitors		SW1	1 pole rotary switch
C1,3,9	100n polycarbonate	SW2	DPDT toggle 15 A 240 V
C1,3,9 C2	1u0 polycarbonate	PB1	momentary push button
C4	47u 25 V axial electrolytic	Tx1	transducer PB 2720
C5	10u 63 V electrolytic PCB type	RLA	12 V coil resistance > 100R. 3 pole changeove
C6	220n polycarbonate		contacts rated at 240 V, 10 A and 11 pin relay
C7	10n polycarbonate		base 15 A rated (see Buylines).
C8	1000u 25 V axial electrolytic	T1	12 V, 6 VA

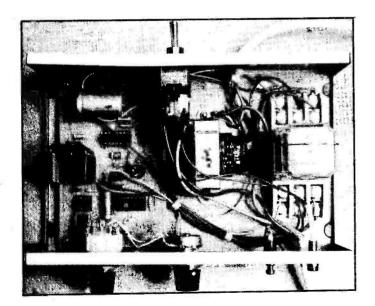

Construction is fairly straightforward. IC4 needs a small heatsink and CMOS ICs 1-3 should be mounted in sockets.

# **Calibration**

Once the unit is functioning correctly, you can proceed with the scale calibration. The obvious (and very time consuming) way to do this is to check the timing periods obtained by varying RV1 against a stop watch, by trial and error, until suitable RV1 calibration points are found.

# **Alternatively**

If you have access to a reasonably accurate 'scope, a far easier way to calibrate the timing scale is to directly measure the period of the IC1 clock waveform, noting that a period of 7.32 mS corresponds to a timing period of precisely one minute. Thus, 1 min = 7.32 mS, 5 mins = 36.6 mS, 10 mins = 73.2 mS, etc.

The upper timing range of SW1 is approximately a decade up on the lower range, so a single calibration scale can serve for both ranges. The tracking accuracy of the two ranges depends on the relative accuracies of C1 and C2 and will typically be within 10% if good polyester components are used. If you want precise tracking, you can achieve it by replacing C2 with a 820nF polyester capacitor and then padding its value up by trial and error, until precise coincidence of the '5 min' and '50 min' points is obtained on the two range scales. **FTI** 

# HREE FOR FRE Electronics by Numbers Projects No 7, No 8, No 9

Available from selected stockists **ELECTRONICS BY NUMBERS** No. 7 DIGITAL DICE

Roll the dice - the electronic way! The digital dice gives you an instant score randomly chosen from 1 to 6, every time you press the button. No losing this under the table!


# No. 8 QUIZ MASTER

Play your own 'Sale of the Century'! Up to four contestants pit their wits, the first one to get the answer lights up his 'win' light, and stops anybody else from having a go.
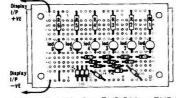
# No. 9 MOVING TARGET GAME

Test your reactions! A moving 'line of light' travels along from left to right, over and over again. You've got to 'fire' at just the right moment to score a hit. Fun for all the family!

Went to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph;



You will need; One EXP 300 or EXP 350 breadboard, 15 silicon diodes, 6 resistors, 6 Light Emitting Diodes.

Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components. connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

For full detailed instructions and layouts of Projects, 7, 8 and 9, simply take the coupon to your nearest CSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you missed projects, 1, 2 and 3, or 4, 5 and 6, please tick the appropriate box in the coupon.


# PROTO-BOARDS

The ultimate in breadboards for the minimum of cost: Two easily assembled kits



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips

# PROTO-BOARD 6 KIT £9.20

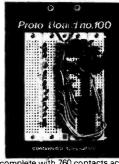

PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy

PROTO-BOARD 100 KIT £11.80

# EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP

EXP 325 £1.60 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



EXP 350 £3.15 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars



EXP 300 £5.75 The most widely bought bread-board in the UK With 550 contact points, two 40 point



bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.

EXP 600 £6.30 Most MICROPROCESSOR projects in magazines and educational books. are built on the EXP 600.



EXP 650 £3.60 Has -6"centrespacing so is perfect for MICROPROCESSOR applications



EXP 4B £2.30 Four more bus-bars in "snap-on" unit



The above prices are exclusive of P&P and 15% VAT.

# THE CSC 24 HOUR SERVICE TELEPHONE (0799) 21682

With your Access, American Express, Barclaycard number and your order will be in the post immediately

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) LTD Dept. 9PP Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Tel: Saffron Walden (0799) 21682 Telex: 817477

II'S EASY	WITH C.S.C.———
TO RECEIVE YOUR FREE	COPY OF PROJECTS 7, 8 and 9
the coupon	For immediate action

Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate

box(es) the breadt	order Will			
EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN DIP.	UNIT PRICE INC	Qty req.
EXP 325	130	1	£ 2.70	
EXP 360	270	3	£ 4.48	
EXP 300	550	6	£ 7.76	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus Bar	£ 5.00	
EXP 48	Four 40 Point Bus-Bars		£ 3.60	

ROTO-BOARDS			
PB5	630	6	£11.73
PB100	760	10	£14.72

C.S.C. (UK) Limited, Dept. 9PP, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Tel: Saffron Walden (0799) 21682 Telex: 817477

Telep Ameri	hone	24 hour, 5 day a week service. 0799 21682 and give us your Access, kpress or Barclaycard number and your in the post immediately
INC VAT	Qty req.	NAME
)		ADDRESS
3		
5		16 g g 15 g g g g g g g g g g g g g g g g
9		
0		l enclose cheque/P.O. for £ Debit my Barclaycard, Access,
0		American Express card No
		Expiry date
		If you missed project No's
3		1, 2, 3, 4, 5, and 6, tick box.

For Free catalogue tick box

**ETI JANUARY 1981** 



NOW OPEN MONDAY-SATURDAY

9.30-5.30

2716 EPROM 5v Rail 2716 EPROM 3 Rail ... £8.50 2708 EPROM ..... £4.95

4116 16k x 1 200ns 2114L-31k x 4 300ns .. 8 for £22.50 2102L-31k x 1 650ns ... 8 for £5.50

.. 8 for £27.50

ock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U's sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

# **TELETYPE ASR33** I/O TERMINALS



Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry. RS232 serial interface, 110 baud. 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.

Options: Floor stand £12.50 + VAT Sound proof enclosure £25.00 + VAT


# **ICL TERMIPRINTER** 300 BAUD TERMINALS



£325 + CAR

Made under licence from the world famous GE Co Made under licence from the world famous GE Co. The ICL Termiprinter is a small attractive unit with so many features it is impossible to list them in the space available! Brief spec. as follows; RS232 serial interlace, switchable baud rates 110, 150, 300, (30 cps), upper and lower case correspondence type face, standard paper, almost silent running, form feed, electronic tab settings, suited for word processor applications plus many more features. Supplied in good condition and in working order. Limited quantity.

# SCOOP PURCHASE 9" VIDEO MONITORS

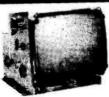

ONLY £57.50 VAT

Made by the famous MOTOROLA CO. The 9° video monitor type XM226-16 is a self contained unit featuring a quoted bandwidth of 10Hz to 10MHz with 800 lines resolution bandwidth of 10Hz to 10MHz with 800 lines resolution at 1th screen center. The printed circuit board and power transistors are both plug-in for ease of servicing. All controls are easily accessible from the rear. By connection of any 7551 composite video signal and 129 of... you have a professional monitor to do any MPUICCTV

system proud!
Supplied BRAND NEW complete with £57.50 + VAT Specialist carriage and insurance £7.50 + VAT

# **EX STOCK** SOFTY

SOFTWARE DEVELOPMENT SYSTEM, INVALUABLE TOOL FOR DESIGNERS, HOBBYISTS ETC.

Enables "open heart surgery" on 2708, 2716, etc, Blows, Copies, Reads EPROMS or emulates EPROM/ROM IN-SITU whilst displaying contents off ROM/RAM on a domestic TV receiver. A host of other features.

Write or phone for more details.

£115 + VAT & CARR PSU £20 + VAT

You'll never regret buying a SOFTY!

# **EQUIPMENT CASES**



GIVE YOUR M.P.U. A HOME ONLY £9.95

Superb professional fully enclosed, made for the G.P.O. to the highest standard, offered at a fraction of their original cost they feature aluminium sides, hinged removable front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand new may have minor scuff marks/scratches due to bad storage. Dimensions 16°D × 6 % "H × 14 %" W

# **MAKE YOUR COMPUTER TALK!!!** VIA OUR EX-GPO MODEM UNITS

Well, not exactly talk, but communicate over a standard dial-up G.P.O. the with any other modem. The modem unit 2A is housed in an attractive hibr glass case measuring only 15 w x 13 d x 5 h, inside are the electronics and mains power supply which enable serial duplex data communication between terminal/computer etc. at any speed up to and in excess of 250 baud (300 at a push). Made to the most stringent, exacting specification for the G.P.O. These units feature Modular plug in P.C.B.'s, internal test points, Standard tone frequencies, Configureable to terminal or computer end, Auto unattended answer, RS232/V34 interface on standard 25 way '0' socket, etc., supplied complete with dapsy, at a fraction of their original cost at only

nal cost at only

£55.00-64.50 CARR

NOTE: Units believed working, but untested, unguaranteed. Per mission may be required for connection to G.P.O. lines.

# **SEMICONDUCTOR** 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new, full spec, with manufacturers markings, fully guaranteed 50 + BAG £2.95 100 + BAGS £5.15

Keep your equipment Cool and Reliable with our tested ex-equipm "Muffin Fans" almost silent running and easily mounted. Available Muffin Fans' almost silent running and easily mounted. Available in wo voltages. 110 V.A.C. £5.05+pp 90p OR 240v A.C. £6.15+pp 00p DIMENSIOMS 42 x 42 x 13 .

# ELECTRONIC COMPONENTS & EQUIPMENT



Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's., P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices!
Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kds £ 4.75+pp £1.25 10kds £11.75+pp £2.25

5kls £ 6.75+pp £1.80 20kls £19.99+pp £4.75

# LED DIGITAL ALARM CLOCK MODULE

\*12 HOUR \*50/60 HZ \*LARGE DISPLAY
The same module, NATIONAL MA1012, \* 100's OF USES used in most alarm clock/radios on the used in most alarm clock/radios on the market today, the only difference is our price! GIANT ½" LED characters give extremely clear viewing and readability. All electronics are self-contained on a P.C.B. measuring only 3"x 1½". By addition of a few switches and 5/16 volts A.C. you have a multi-function alarm clock at a mere fraction of cost. Decree of functions

function alarm clock at a mere fraction of cost. Dozens of functions include sooze timer, am-pm, alarm set, power fail indicators, flashing seconds cursor, modulated alarm output, dimmer control, etc, etc, seconds cursor, mounted that at only £5.25

suitable transformer for mains operation £1.75

# Save Over £1200!! Logabax DZM180 High Speed **Matrix Printers**

Matrix Printers
This must be one of our greatest bulk saving deals this year. This fabulous printer is listed at over £1800 and judging by the quality workmanship we are not surprised. The Logabax DZM180 Matrix printer, capable of printing up to 132 characters per line on any size (via variable tractor unit) sprocket fed fartfold paper. A precision matrix head utilising ruby bearings gives exceptionally clear uniform legible characters via standard ribbon. Mary other leatures include internal buffer, for high throughput, in excess of 180 characters per second, software controlable form and tab functions, standard TTL parallel interface, etc. etc. nterface, etc. etc. Supplied brand new and boxed at only

£599.00 plus VAT\*

\*Carriage — please enquire for specific quote.

# THE "MULTIVOLT" MULTI RAIL P.S.U.

This has got to be the power supply to end all your M.P.U./LAB supply requirements Recently made by the famous "WIER" CO Ltd to the highest professional specifications. With an original cost of over £200 the supply features every possible form of protection, full regulation, over voltage and current limit and just look at these outputs, it may have been made to your specifications!

+ 5 V at 12 Amps

+ 30 V at 2 Amns 12 V at 2.5 Amos + 5 V at 4.5 Amps 9 V at 1 Amp

you agreet then order now whilst stocks last.
Supplied BRAND NEW at only

£59.99 CARR & INSUR. £6.75 complete with diagrams.

# **BRAND NEW** 8" FLOPPY DISK DRIVES

. £245+carr+VAT DRI 7100 £300 + carr + VAT **DRI 7200** 

# 5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S. U. we have managed to secure a large quantity of ex-computer systems P.S. U.'s with the following spec.; 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12' x 5' x 3'. The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply effective 5v @ 7 amp supply.
Supplied complete with circuit at only £10.95 + £1.75pp.

Supplied complete with circuit at only £10.95 + Believed working but untested, unguaranteed

# **KEYBOARDS** ★ LOW PRICE CHASSIS



lowest ever price 49 coded keys encoded into a direct TTL compatible 7 bit output Features such as delayed strobe, 5 voli D.C. single rail operation and rollower protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector at a secondhand

"no time to test"

£20.00 + P.P. £1.60

SUPER CASED VERSION Same as above spec, but housed in attractive two tone moulded, free standing case. Unit also includes an all TTL parallel to serial convertor (no details) etc

£27.50 + P.P. £1.85

# TOROIDAL TRANSFORMERS

PR 240v pri. sec. 15 0 15 @ 2 amps dimensions 3" x 2½" £4 95+pp 99p TM 240vil 10v pri. sec. 15 0 15 0vA dimensions 2} x 1 £1 95+pp 30p All voltagas measurad off load.

# Plugs, Sockets & Connectors Cannon 'D' Range

-		
Ways	Plug	Socket
9	£1.03	£1.26
15	£1.17	£2.01
25	£1.72	£2.58
37	£2.35	£4.14
50	62.90	£5.46


25 way ex-equip. plug or socket £1.25

 Edge connectors, gold plated 0.1" DS 0.1" DS 40 way £2.45 £3.99 85 way 0.15°DS 0.156DS £3.25 £2.00 16DS 36 way
All connectors easily cut to size
1000's of other connectors ex stock



Dept. E.T.I. 64-66 Melfort Rd., Thornton Heath Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800

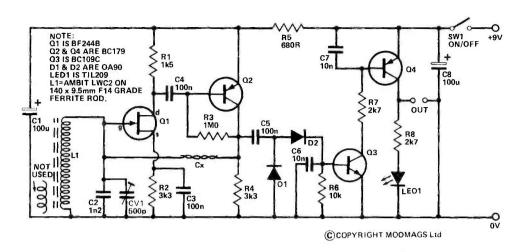**INFORMATION** Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 50p per order. Bona Fida account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.



# 60 kHz Time Receiver

his receiver gives reception of the atomic clock time signals This receiver gives reception of the atomic control of transmitted by the Rugby MSF transmitter on 60 kHz. At this very transmitted by the Rugby MSF transmitter on 60 kHz. At this very low radio frequency it is not necessary to use a superhet. A ferrite aerial is used with L1, an ordinary LW broadcast band aerial coil, and the relatively high tuning capacitance of C2 and C3 is used to reduce the resonant frequency to the appropriate figure. The receiver is tuned by CV1 and by adjusting the position of L1 on the ferrite rod.

The output of L1 is direct-coupled to a straightforward common source JFET stage and this in turn feeds a simple common emitter stage. Due to the relatively low frequency involved these can both provide good voltage gain without using tuned circuit loads. The collector

of Q2 is in-phase with the gate of Q1 and if necessary, "twisted pair" Cx can be used to provide regeneration between these two points to boost the sensitivity of the set.

The output from Q2's collector is coupled by C5 to a simple diode modulator circuit which consists of D1, D2, C6 and R6. When the 60 kHz carrier is present a strong DC bias is produced across R6, but this potential quickly decays during the gaps in the carrier (the 1 S markers and other signals are modulated onto the carrier wave in the form of brief pauses in the signal).

Thus Q3 is switched on when the carrier is present, so that Q4 is in turn switched on, giving a high output and causing LED 1 to light up. In the absence of the carrier wave Q3, Q4 and LED 1 all switch off and the output of the receiver goes low.

When initially adjusting the set it is helpful to monitor the output of the detector using a crystal earpiece connected across R6.



- Understanding circuit diagrams.
   Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. Special educational Mini-

  - Computer supplied ready for use. Self Test program exercise.
- Services of skilled tutor available.

# MASTER THE REST


- Radio Amateurs Licence. ◆ Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators Digital Meters etc.

FR	Name	PRACTICAL ÉLECTRONICS  COMPUTER TECHNOLÓGY
E	Address	OTHER SUBJECTS pease staticy per interest!
_	BLOCK CAPS OUT ASI	
BB	ITISH NATIONAL BADIO	& ELECTRONICS SCHOO

# SPECIAL PURCHASE



# OF TOP QUALITY **LCD MULTIMETERS**

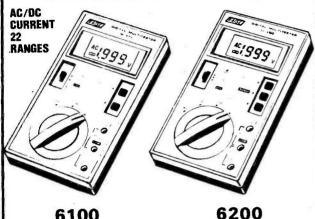

# **CHOOSE FROM FOUR MODELS**

- 31/2 digit autoranging (volts / ohms)
- 200 hours battery life (2 pencells)
- 10 amp AC/DC (6220 & 6110) \* 1000v DC 600v AC 200mA AC/DC (6200 &6100)
- Range hold facility (6100 & 6110) ×
- Unit and range sign (6110 & 6220)
- Continuity buzzer (6100 & 6110)

# RESOLUTION

100 µVDC. 1 mVAC 10 µA AC/DC 0.1 oHM 10 mA on 10A, AC/DC

6100

# **OTHER FEATURES** (ALL MODELS)

Low power OHms Range Zero Adjust key Battery Warning In circuit resistance test Size 155 x 85 x 28mm. 250g.

- \* All prices include batteries / leads
- and UK Vat (UK c/p 65p)
  Order by Post or Telephone with Barday or Access

# **ACCURACY** 6100/6110

0.5% DC Volts 1% DC Current

2% AC Current

0.5% Resistance

# 6200/6220

0.8% DC Volts 1.3% DC Current

4% AC Current

0.8% Resistance

6200 £39.95

6220 **£49.95** 

6100 £59.95

6110 £74.95

# OR CALL IN AND SEE FOR YOURSELF

Prices correct at 1.12.80 E&OE

OPEN 9-6 SIX DAYS A WEEK Cubegate Limited

# AUDIO ELECTRONICS

Or debit Barclay / Access No.

301 EDGWARE ROAD, LONDON, W2 1BN

TELEPHONE 01 724 3564







From Mr/ Mrs /iMiss	Ref.	
(Block capitals please)		-
Address	- 4 1 1	2 6
Please supply Qty. Models	8076	
I/We enclose (incl. 65p post)	5 5 E + 15	
Cha /PO value		
CHQ/FO value		
	Address  Please supply Qty. Models  1/We enclose (incl. 65p post)	Address Please supply Qty. Models  1/We enclose (incl. 65p post)

# **BUILD YOUR OWN METAL DETECTOR** VLF/TR VCO/TR IB/TR BFO ...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for



Individual parts: Search head £21.33 PCB £6.80 Case £5.33 Adjustable shaft assy, £5.10. LM393 £1.12, Manual (gives more info; than ETI article — and extra function) £1.12, AR inc. VAT & post! (Other parts also available separately)

edow TR/18 (illustrated). A true transmit receive/induction balance detector at a budget price for one who doesn't need discrimination. Waterproof and thermally insulated search head. Good skirlyt, Built-n peaker and headsa jeck. Complete kit £33.80 inc. VAT and Post.

Shadow TR/VCD. An advanced version of the TR/IB. Use as a sensitive 1B machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and, enabling detection of negative, high permability anomalises. Kit price 25.6-97 inc VAT and Post.

s for all Shadow models FS.SS inc. VAT and Post

Shell Kit. Consists of the (hard to find) hardwere items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions £18.48 inc. VAT and Post.

# ALTEK (ETI), 1 Green Lane Walton-on-Thames Surrey

# ELECTRONIC IGNITION SAVES PETROL

More and more new cars use electronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.

TOTAL ENERGY DISCHARGE gives all the

- Peak Performance—higher output voltage.
  Improved Economy—consistent high ignition performance.
  Better Starting—full spark power even with low battery.
  Accurate Timing—prevents contact wear without 'contactless' errors.
  Smooth Performance—immune to contact bounce effects.

SUPER HIGH POWER SPARK-31/2 times the energy of ordinary C.D. systems.

OPTIMUM SPARK DURATION—to get the very best performance and economy with today's lean carburettor settings.

DESIGNED IN RELIABILITY—with the 'ultimate insurance' of a changeover switch to rt instantly to standard ignition.

# TECHNICAL DETAILS

HIGH EFFICIENCY INVERTER. A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4

SUPPRB DISCHARGE CIRCUIT. A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the

SOPHISTICATED TRIGGER CIRCUIT. This circuit removes all unwanted s caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

# IN MONEY-SAVING KIT FORM at £14.85 and P. & P.

All you need is a small soldering iron and a few basic tools - everything else is supplied easy-to-follow instructions

FITS ALL 6/12-volt NEGATIVE EARTH cars

# **ELECTRONIZE DESIGN**

2 Hillside Road, Four Oaks Sutton Coldfield, West Midlands, 874 4DQ Phone 021-308 5877

I/O INTERFACE

Computers share a common failing with man (and woman) — they use a variety of different languages and dialects. This design by Clive Cartlidge lets the Compucolor II talk to a whole new family of computers.

The interface described here was originally built to allow a Compucolor II microcomputer to be connected to any one of four "mainframes" at North Staffordshire Polytechnic. The mainframes in question were a GEC 4082, an HP 2000E, an ICL 2960 and an ICL 2904; both of the latter machines being front ended by 7502 processors. After construction, however, it became obvious that the device had a much wider appeal and could be used in a variety of applications where bit length and parity changes were necessary.

This device was required to overcome the problem that the Compucolor II transmits and receives eight bit characters from its R\$232 port, whereas the mainframes mentioned above all transmit and receive seven bits with an even parity bit added.

The UART is an LSI sub-system which accepts binary characters from either a terminal or a computer and transmits/receives this character with appended control and error detecting bits. All characters contain a start bit, five to eight data bits, one or two stop bits and either an even/odd or a no parity bit. This is all hard wire selectable on the UART together with an operating speed of up to 30 kbaud.


# The UART Receiver

The UART requires a clock signal 16 times the designed baud rate. Initialisation is performed by applying a reset pulse to pin 21. This sets the Data Available flag, pin 19, to a logic 0. Reception of data starts when the serial input signal changes from a marking state (logic 1) to a spacing stage (logic 0). This condition constitutes a start bit and it is valid if the serial input line continues to be at logic 0, when centre sampled, eight clock pulses later. If this is not the case, however, and the serial line has returned to logic 1 when sampled, the start bit verification process will be reset. After a genuine start bit has been received and verified by the process above, data bits, parity bit if used and stop bits are received.

On receiving parity and stop bits, the receiver will compare the transmitted parity and stop bits with the 'expected' pattern and indicate any errors by changing the parity error flip-flop and/or the framing error flip-flop to a logic 1.

When a full character has been received, internal logic examines the 'Data Available' line to see if data has been read out. If the line is at a logic 1, the receiver will assume that data has not been read out and the over-run flip-flop will be set to logic 1, indicating an over-run error. If 'Data Available' is set to logic 0, the receiver will assume that data has been read out.

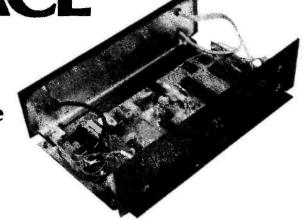After the Data Available line goes to logic 1, indicating a character has been received, the receiver shift register is ready to accept the next character and has one full character time to remove the first character received.



# The Transmitter

The same clock signal may be used for the transmitter as for the receiver. The external reset pulse is also common. When this is applied the 'Transmitter Buffer Empty', End of Character and the Serial Output lines of the device are driven to logic 1. Data occurring on the Data Input lines, pins 26-33, is strobed into the device by a pulse on pin 23, the Data Strobe. Once this has occurred, the Transmitter Buffer Empty (TBMT) flag goes to a logic 0, indicating that a character is being transmitted and the device is unable to accept further characters until this flag returns again to logic 1. The device is double buffered and so when the TBMT flag returns to logic 1, one full character time is available for loading the next character without any loss in transmission speed.

Data transmission is initiated with the transmission of a start bit, data bits, parity bit if required and stop bits. When the last stop bit has been on the line for one bit time, the End of Character flag will go to a logic 1 indicating that a new character is ready for transmission.


# **Control bits**

The number of bits per character (five through eight) together with a parity bit (odd, even or none) and one or two stop bits can be selected by strapping appropriate pins on the UART to logic 1 or logic 0. These selections apply to both the receiver section and transmitter of the chip.
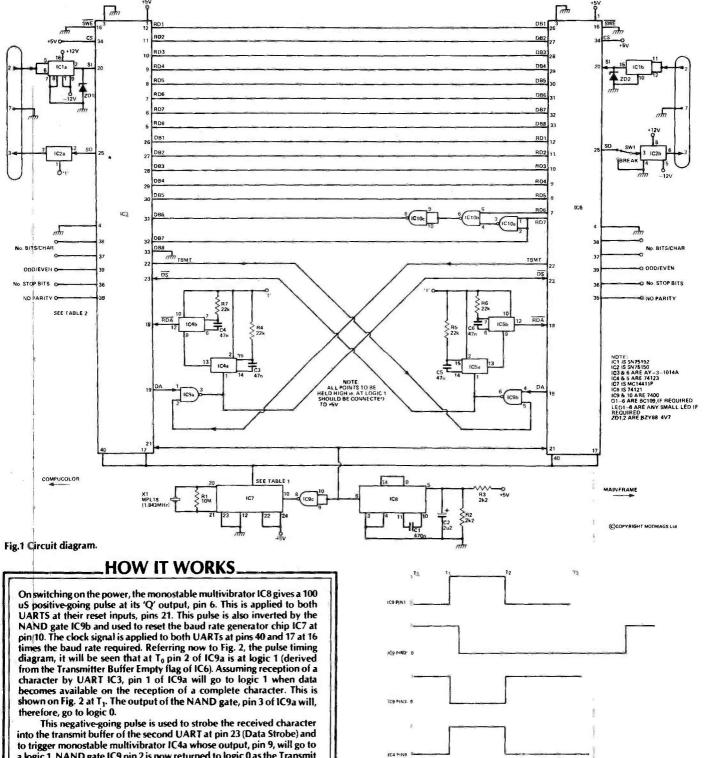
# **Code Converter**

One particular problem encountered when using this interface was that most of the logging-in data received from the mainframes was in lower case ASCII code. While most terminal devices would simply display this as upper case, the Compucolor II treats lower case code as graphics display information. This difficulty is overcome by the NAND gate code converter (IC10). The circuit's logical function simply drops bit six when bit seven is set to a logic 1, effectively converting lower case code to upper case before it emerges from the interface.

A second problem was encountered when using the device with the HP 2000 Basic system. This was the need for a break key. Break not being a valid ASCII character, it cannot be implemented through the UART. This is easily cured by fitting a push button switch on to the computer side of the interface as shown.



to trigger monostable multivibrator IC4a whose output, pin 9, will go to a logic 1. NAND gate IC9 pin 2 is now returned to logic 0 as the Transmit Buffer Empty flag of UART IC6 will be driven to logic 0, having been filled' with a character. The time delay shown on the diagram is due to chip propagation which proves ample in the design shown. After a timing delay in the first monostable set by timing components C3 and R4, pin 9 on IC4b goes to logic 0 (T2 on the timing diagram). Pin 12 on IC4 follows it and this signal is used to reset the Data Available flag on UART IC3. At this stage, once the Transmitter Buffer Empty line of UART IC6 has returned to logic 1, the circuits are back in their original

states and ready to accept the next character.

This description also applies to characters flowing through the interface in the opposite direction. IC1 and IC2 are both dual level converter chips which convert RS232 levels (usually  $\pm$ 12 V) to TTL levels of 0 V and 5 V.

Fig.2 Pulse timing diagram.

# **BUYLINES**

Most of the components required can be ordered from suppliers advertising in this issue. In case of difficulty, advertisers specialising in computer hardware may be of assistance.

The variable regulator (RC4149D) is a Radiospares component — RS No. 306-011.


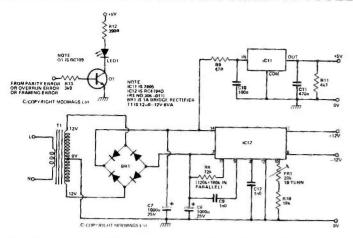


Fig.3 Circuit diagram of the power supply and LED indicators if required.

	1/4 W 5% unless otherwise stated
R1	10M
R2, 3	2k2
R4, 5, 6, 7	22k
R8	72k (120k + 180k in parallel)
R9	47R 2 W
R10	18k
R11	4k7
R12	390R (six if required)
R13	3k9 (six if required)
Potentiomete	er
PR1	20k 10-turn preset
Capacitors	
C1, 11	470n polyester
C2	2u2 35 V tantalum
C3, 4, 5, 6	47n ceramic
C7, 8	1000u 25 V axial electrolytic
C9, 12	1n0 ceramic
C10	100n ceramic
Semiconduct	
IC1	75152
IC2	75150
IC3, 6	AY-3-1014A
IC4, 5	74123
IC7	MC14411P
IC8	74121
IC9, 10	7400
IC11	7805
IC12	RC4194D
Q1	BC109 (six if required)
ŽD1, 2	BZY88 4V7
BR1	1 A bridge rectifier
LED1	0.2" LED (six if required)
Miscellaneou	5

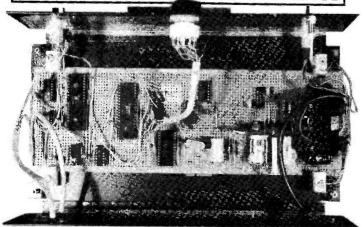

The method of construction is not critical. The author's board is shown above.

Pin No.	Function	User Ba	aud
1	F4	Rate	
1 2	F1 F3	9600	
3	F5	4800 2400	
4	F7	1200	
5	F8	600	
6	F10	200	
7	F9	300	
8	F11	150	
9	F14	75	
10	Reset		
11	NC		
12 13	Ground F13	100.0	
14	F13	109.9 134.5	
15	F6	1800	
16	F4	3600	
17	F2	7200	
18	F15	921.61	кНz
19	F16	1.843 M	
20	Crystal		
21	Crystal		
22	rate select		
23 24	rate select		
-	+5 V		
Table 1 MC 14411P ni	n connections	and clos	k spands
			n specus
Pins 35	Logic 0	Logic 1	
39 39	Parity Odd parity	No parii	
3 <del>9</del> 36	Odd parity One stop bit	Even pa	
30	One stop bit	Two sto	p bits
Character	Pin 37	Pin 38	
Lengths			
5 bits 5 bits	Logic 0	Logic 0	
7 bits	Logic 0	Logic 1	
8 bits	Logic 1 Logic 1	Logic 0	
Table 2.	Logic 1	Logic 1	
	connections (	1(3.6)	
1 Vcc Pc 2 NC	ower Supply (+	-5 V)	
3 Groun	d		
the same of the sa	ed Data Enabl	-	RDE
	ed Data Bits	e	(RD8-RD1)
13 Parity	Error		(PE)
	g Error		(FE)
15 Over r	un		(OR)
16 Status	Word Enable		SWE
17 Receiv	er Clock		(RCP)
	Data Available		RDAV
	vailable		(DAV)
20 Serial I 21 Externa			(St)
	al Reset <u>uitte</u> r Buffer Er	nntv	(XR)
23 Data S	trobe	npty	(TBMT)
	Character		DS (EOC)
25 Serial (	Dutput		(SO)
	it inputs		(DB1-DB8)
	Strobe		(CS)
35 No Par	ity		(NP)
36 Numbe	er of stop bits		(TSB)
37-38 Numbe	er of bits per ch	naracter	
39 Odd/Ev	en parity selec	ct	
40 Transm	itter Clock		(TCP)

Table 3.

AY-3-1014A pin connections.

# electronics

ARCHWAY, LONDON N19 5RD - 50 vards from Archway Station & 9 Bus Routes TELEPHONE: 01-263 9493/01-263 9495

# YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS

8N 8K RAM - £399 16N 16K RAM - £499 32N 32K RAM £599 CASSETTE DECK - £55

> 343K Twin Floppy Disk £695





COMPLETE 32K SYSTEM £1789

(NORTHERN LINE) ARCHWAY STATION

NEW 32K with 80 col Screen Twin Disk Drive 950K

All with new keyboard and green screen

FRICTION FEED PRINTER £375 **Tractor Feed Printer** 





£825 £895

# MEMORY EXPANSION KIT

Suitable for UK101, Superboard expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- \* 8K kit

£89.95 £122.96

★ 16K kit

★ Printed Circuit Board

£29.95

★ 40 pin-40 pin header plug

£8.50

UPPER HOLLOWAY STATION LMR & ER

JUNCTION ROAD

NEXT DOOR

ARCHWAY A1

ROAD

ST. JOHNS

VIDEO GENIE VIDEO GENIE based on TRS80



Utilises Z80, 12k level II Basic, Integral Cassette Deck, UHF O/P 16k RAM.

all TRS80 features

# CASES-

Available for UK101. Superboard, Nascom. Appx. DIM 17" x 15" 435 x 384 mm

**PRICE £24.50** Post & Packing £1.50

# -UK101 P.P.I

Built & tested. Interfaces TX80 Printer direct. Can be programmed to operate relays, motors, various other peripherals CENTRONICS COMPATABLE"

Plugs into IC socket. LED binary display fully documented.

£29.95

# PRINTERS-



# **EPSON TX-80** £349

Dot-matrix printer with Pet graphics interface: Centronics parallel and serial: Pet and Apple compatible.

£179 IN KIT FORM £229 READY BUILT & **TESTED** 

£255 COMPLETE IN CASE

4K Expansion (8x2114) NOW ONLY £18.00

No extras required

- ★ Free sampler tape
- ★ Full Qwerty keyboard
- ★ 8K basic
- ★ Ram expandable to 8K on on board (4K inc)
- \* Kansas City tape interface
- NEW MONITOR ALLOWS FULL EDITING & ★ NEW MONITUR A CURSOR CONTROL



Please add VAT 15% to all prices. Postage on computers: printers and cassette decks charged at cost, all other items P&P 30p Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome credit facilities arranged





# NEW SHOP & SHOWROOM NOW OPEN

Telephone: 01-263 9493/01-263 9495

# UK101 SOUND

Sound Generator and combined parallel in out port kit containing P.C.B., AY-3-8910. 6820 PIA. Fully documented and demo tape. £29.95. AY-3-8910 £8.50.

# UK101 SOFTWARE

	£
Space Invaders	6.50
Real Time Clock	5.00
Chequers	3.00
Othello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10xC12 Blank Tapes	4.00

# -- MEMORY-

D.RAMS	£р
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	3.95

# **S.RAMS** 2102A

2102A	1.30
2102A2	1.69
2112A	2.75
2114/4045	2.75
4035	1.07
4044-5257	6.93
6810	3.50

# **BULK PURCHASE**

8x2114	18.00
8x4116	27.50
16x2114	34.00

# CPUs

Z80 2.5Meg	7.95
Z80A 4Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

# EPROMs

2708	4.25
2716 (5v)	6.95
2532	29.95

# = SUPPORT CHIPS=

Z80 CTC	5.95
Z80A CTC	6.95
Z80 P10	5.95
Z80A P10	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
9224	2.75
8228	
8251	4.95
8253	£9.75
8255	4.50
TMS9901	13.16
TMCOOOS	11 10

# -ROM-

2513 (UC)	5.95

# BUFFERS .

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	£1.50
8T97	1.50
8T98	1.50

# I.C. SOCKETS

TMS9904 (74LS362)

1.C. SOCKE 13	
D.I.L.	W/W
.09	.25
,11	.35
.12	.42
.16	.50
.20	.62
.22	.65
.24	.70
.30	.80
_	.99
.40	1.10
	.09 .11 .12 .16 .20 .22 .24

# BAUD RATE GENS


MC14411	8.75
MM5307	8.75

# -UARTS-

AY-5-1013	3.95
AY-3-1015	4.75
MM5303	4.75
TMS6011	3.55

SEND S.A.E. FOR COMPLETE PRICE LIST OR PHONE 01-263 9493
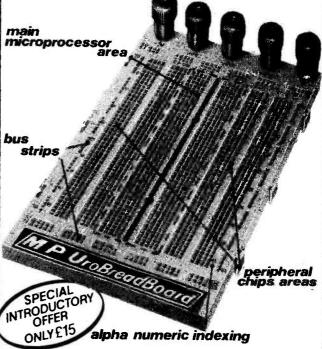
# If you're into MICROPROCESSORS then they should be into an M P UroBreadBoard



- \* MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- \* Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- Power Bus Strips on all sides
- \* 5 incoming turret Power Terminals
- \* Component Support Bracket included
- \* Over 1400 contact points
- \* Alpha-Numeric column and row indexing
- \* Eurocard size (160mm x 100mm)
- \* Slots onto all BIMBOARDS
- Non-Slip rubber backing
- \* Ideal for schools and colleges
- \* Long life, <10m.ohms, nickel silver contacts

The PROFESSIONALS breadboard that BEGINNERS can start on

# BOSS INDUSTRIAL MOULDINGS LTD

2 Herne Hill Rd, London SE24 OAU, England Telephone 01-737 2383 Telex 919693 Cables & Telegrams: LITZEN LONDON SE24

Please send me ........ MPUroBreadBoard(s) at the special, limited period, introductory offer price of £15.00.

This price includes VAT & PP, is applicable from Sept 1 1980 but please add 15% for Overseas Orders, make cheques/P.O. payable to BOSS Industrial Mouldings Ltd and allow 10 days for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £....

	_		,		•	_		•		٠.	-	•	٠.	•	•••	•••	•••	••••	•••	•••	•••	•••	•••	•••	••		
Name .	,		ė		1		¥	18	78								ysh"	46	4		ı	÷				iya.	
Company																											
Address																											

Telephone Number . . . . . . . . . . . . . . . . ETI 1/81



SEMICONDUCTORS SEND YOUR ORDERS TO DEPT. ETI1. PO BOX 6, WARE, HERTS. VISIT OUR SHOP AT: 3 BALDOCK ST., WARE, HERTS. TEL 0920 3182. TELEX: 817861

#### **AUDIO MODULES EXPERIMENTOR BREADBOARDS SILICON RECTIFIERS** FROM • • **AMPLIFIERS** 3 Amp IN5400 50V IN5401 100V IN5402 200V IN5404 400V IN5406 600V IN5407 800V IN5408 1000V 3 watt Audio Amplifier Module 22-32v supply 5 watt Audio Amplifier Module 22-32v supply 7-10 watt Audio Amplifier Module 22-32v No soldering breadboards. Simply plug components in and out of letter number identified. £5.51 supply 15-**25 watt Audio Amplifier Module 30-50v** Nickel-silver contact holes. Start small and simply snap-AL60 supply 35 watt Audio Amplifier Module 40-60v supply 50 watt Audio Amplifier Module 50-70v supply 125 watt Audio Amplifier Module 50-80v supply £6.81 £10.67 £17.38 £25.91 lock boards together to build a breadboard of any size 1 Amp IN4001 50V IN4002 100V IN4003 200V IN4004 400V IN4005 600V IN4006 800V IN4007 1000V 10 Amp IS10/50 50V £0.05 £0.05 £0.07 £0.08 £0.09 £0.10 All EXP Breadboards have two bus-bars as an integral £0.21 £0.24 £0.26 £0.40 £0.48 £0.58 £0.69 £0.79 IS10/50 50V IS10/100 100V IS10/200 200V IS10/400 400V IS10/600 600V IS10/800 800V IS10/1000 1000V IS10/1200 1200V part of the board. If you need more than two buses, simply snap on 4 more bus-bars with the aid of an EXP STEREO PRE-AMPLIFIERS 48 EXP 325 The ideal breadboard for 1 chip circuits Supply voltage 22-32v input sensitivity 300mv suit: AL10/AL20/AL30 PA12 £9.63 Accepts 8, 14, 16 and up to 22-pin Supply voltage 24:36vinputs:- Tape, Tuner, Mag P U., Sutt: AL60/AL80 Supply voltage 35:70v inputs:- Tape, Tuner, Mag P.U., Sutt: AL80/AL120/AL250 ONLY £1.84 1.5 Amp ISO15 50V ISO20 100V ISO21 200V ISO23 400V ISO25 600V ISO27 800V ISO27 1000V 30 Amp IS30/50 50V IS30/50 50V IS30/100 100V IS30/200 200V IS30/400 400V IS30/600 600V IS30/600 800V IS30/1000 1000V IS30/1200 1200V IC's £20.30 £0.10 £0.11 £0.12 £0.14 £0.16 £0.18 £0.23 £0.28 48mm (1.9") £0.64 £0.79 £1.06 £1.43 £2.02 £2.23 £2.65 £3.31 EXP 350 270 contact points with two 20-point bus-ONLY £3-62 MONO PRE-AMPLIFIERS bars. 91mm (3.6") MM100 Supply voltage 40-65v inputs: Mag, P.U., Tap Microphone Max. output 500miv Supply voltage 40-65v inputs: 2 Guitars, Microphones Max. output 500mv EXP 300 550 contacts with two 40-point bus-£14.29 ONLY £6-61 bars. 152mm (6.0") £14.29 EXP 650 For Micro-processors. **ONLY £4.14** 60 Amp 1S70/50 50V 1S70/100 100V IS70/200 200V **POWER SUPPLIES** £0.86 £0.96 £1.38 91mm (3.6") ONLY £2-65 24v Supply suit 2 · AL10, 2 · AL20, 2 · AL30 & PA12/S,450 33v Stabilised supply - suit 2 · AL60, PA100 to 15 watts EXP 4B More bus-bars. PS12 152mm (6.0") £1.90 EXP 600 As EXP 300 but accepts 24 pin DIL and **THYRISTORS** £5.57 ONLY £7-25 SPM120/45 45v Stabilised supply – suit 2 · AL60 PA100 to 25 watts SPM120/55 55v Stabilised supply – suit 2 · AL80 PA200 600ma Volts No. 10 THY600/10 20 THY600/20 30 THY600/30 50 THY600/10 100 THY600/10 200 THY600/400 TO 48 Case Price £0.55 £0.59 £0.66 £0.71 7 amp Volts No. 50 THY7A/50 100 THY7A/100 200 THY7A/200 400 THY7A/400 600 THY7A/600 800 THY7A/800 TO 18 Case £7.34 152mm (6.0") Price £0.17 £0.18 £0.23 £0.25 £0.29 £0.44 £0,51 All EXP 300 Breadboards mix and match with 600 €7.34 series £7 34 **ANTEX IRONS** £4.37 1943 15 watt quality soldering iron with MISCELLANEOUS 10 amp T Volts No. 50 THY10A/50 100 THY10A/100 200 THY10A/200 400 THY10A/400 600 THY10A/600 800 THY10A/800 bit £4.88 TO 48 Case Stereo Magnetic Cartridge Pre-Amplifier-input 3.5 mv Output 100mv Stereo FM Tuner Supply Voltage 20-30v-Varicap runed Complete 7 wart per Channel Stereo Amplifier Board – includes amps, pre-Price £0.59 £0.66 £0.71 £0.81 £1.14 £1.40 1947 Replacement element for 1943 MPA30 £2.18 1 amp Volts No. 50 THY1A/50 100 THY1A/100 200 THY1A/200 400 THY1A/400 600 THY1A/600 800 THY1A/800 TO 66 Case £3.76 1944 Iron coated bit 3/32" for 1943 £0.53 Price £0.30 £0.32 £0.37 £0.44 £0.52 £0.67 \$ 450 1945 fron coated bit 1/8" for 1943 £0.53 1946 Iron coated bit 3/16" for 1943 STEREO30 £0.53 amp, power supply, front panel, knobs etc – requires 2050 Transformer 1948 18 watt iron with iron coated bit £4.59 1952 Replacement element for 1948 £2.18 TO 48 Case Price 0 £0.62 00 £0.67 00 £0.71 00 £0.89 00 £1.04 watt 12 max. - Siren Alarm Module 5 watt 12v max. - Siren Alarm Mod 10 channel mono-graphic equalise complete with sliders and knobs 1949 Iron coated bit 3/32" for 1948 £0.53 Volts No. 50 THY16A/50 100 THY16A/100 200 THY16A/200 400 THY16A/400 600 THY16A/600 800 THY16A/800 1950 Iron coated bit 1/8" for 1948 £0.53 £26,45 3 amp Volts No. 50 THY3A/50 100 THY3A/100 200 THY3A/200 400 THY3A/400 1951 Iron coated bit 3/16" for 1948 Variable regulated stabilised power supply 2-30v 0-2 amps TO 66 Case £0.53 £8.74 Price £0.32 £0.35 £0.38 £0.48 1931 X25 25 watt iron, ceramic shaft and another **TRANSFORMERS** shaft of stainless steel to ensure strength £4.88 €1.60 Replacement element for 1931 £1.84 30 amp T Volts No. 50 THY30A/50 100 THY30A/200 200 THY30A/200 400 THY30A/400 600 THY30A/600 1.7 amp 35v suit SPM80 2 amp 55v 750m A 17v suit PS 12 1.5 amp 0.45v-55v suit SPM120/45, SPM120/55v 2 amp 0.55v-65v suit SPM120/55, SPM120/65v 1932 Iron coated bit 1/8" for 1931 TO 94 Case £0.57 Price £1.38 £1.64 £1.87 £2.06 £4.03 1933 Iron coated bit 2/16" for 1931 1934 Iron coated bit 3/32" for 1931 £0.57 SK1 soldering Kit - contains 15 watt soldering £5.98 £1.21 TO 66 Case 2041 Price £0.41 £0.52 £0.58 £0.66 iron with 3/16" bit plus two spare bits, a reel of Volts No. 50 THY5A/50 100 THY5A/100 200 THY5A/200 400 THY5A/400 600 THY5A/600 800 THY5A/800 No. BT101/500R BT102/500R BT106 BT107 BT108 2N3228 2N3525 BTX30/50L BTX30/400L C106/4 BT116 solder, heat-sink and a booklet 'How to 1 amp 0-20v suit Stereo 30 150mA 15-0-15v suit SG30 Solder £6.38 1939 ST3 iron stand made from high grade bakelite ACCESSORIES chrom plated steel spring, suit all models -Teak Cabinet suit Stereo 30, 320 · 235 · 81 mm Teak Cabinet suit STA15 425 · 290 · 95mm includes accommodation for six bits and two sponges to keep the iron bits clean £1.86 5 amp TO Volts No. 400 THY5A/400P 600 THY5A/600P 800 THY5A/800P TO 220 Case Front Panel for PA100 & PA200 Front Panel for Date of PA100 & PA200 Front Panel for Date of PA100 & PA200 Kit of parts including Teak Cabinet, chassis sockets, knobs to build 15 watt stereo 1724 Model MLX as X25 iron but 12 volts CASES AND BOXES VERO plastic case box. These boxes consist of top and bottom sections which include fixings points for horizontal mounting PC boards/chassis plates, the two sections are held together by four screws which enter through the base and are concealed by plastic feet. No. Length Width Height Price 170 140mm 40mm 205mm £6.35 £22.94 **VEROBOARD** ZENER DIODES 400 mw (Bzy88) D007. Glass encapsulated range of voltages available. 1-3v, 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-8v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v. neid to and are No. 170 171 172 2.5" 5" .1 copper 2.5" 3.75" .1 cons Price £4-35 £4-85 £6-30 40mm 75mm 110mm 140mm 140mm 140mm 205mm 205mm 1w 1.5w Plastic and metal encapsulated. Range of voltages available. 1.3v. 2.2v. 2.7v. 3.3v. 3.9v. 4.3v. 4.7v. 5.1v. 5.6v. 6.2v. 6.8v. 7.5v. 8.2v. 9.1v. 10v. 11v. 12v. 13v. 15v. 16v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v. 47v. 51v. 68v. 72v. 75v. 82v. 91v. 100v. INSTRUMENT CASES in two ed top Length 8in 11in 10w Metal stud type S010 case. Range of voltages available. 1 3v. 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-6v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 16v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v **METAL FOIL CAPACITOR PAKS** from bright alli, with helf inch deep ALUMINIUM BOXES made construction each box complete 16204 – Containing 50 metal foil capacitor like Mullard C280 series – Mixed values ranging from 01uf – 2-2uf, Complete with identification sheet No. 159 160 161 162 163 164 165 166 Width 21in 4in 21in 4in 21in 21in 5in 6in 4in Price £0.98 £0.98 £0.98 £1.10 £0.98 £0.67 £1.54 £1.98 £1.32 TRIACS **BRIDGE RECTIFIERS** 2 amp volts 100 200 400 SILICON 1 amp Type No 50v RMS BR 100v RMS BR 200v RMS BR 400v RMS BR TO5 case 10 amn Price Type 10-23 50 rms 1000 rms 1000 rms 1000 rms 1000 rms 1000 rms SILICON 2 amp TOS case No. Price TR12A/100 £0-36 100 TR12A/200 £0-59 200 TR12A/400 £0-82 400 TR110A/100 £0-88 TR110A/200 £1-06 TR110A/400 £1-29 10 amp SLOPE front aluminium boxes with black viny sides & aluminium back, top & front - strong or SILICON 25 amp 400 volts 100 200 400 TR110A/400P £1.29 SILICON 10 amp TR16A/100 £0-59 TR16A/200 £0-70 DIACS TR16A/400 £0-88 BR100 £0-23 D32 £0-23 No. Price Type BR10/50 £1-50 50v RMS BR10/200 £1-70 200v RMS 2 in 5 in 2 in 12 in 3 in 8 in 2 in 7 in 4 in 16 in 4 in 11 in 50v RMS 200v RMS BR25/50 £1.90 BR25/200 £2.20



All prices include VAT. Add 50p post per order — Just quote your Access or Barclaycard number. Terms. Cash with order, cheques. POs. payable to Bi-Pak at above address. Access and Barclaycard also accepted.

GIRO A. C No 3887006



## LED TACHO

A unique two-range tacho that gives an analogue RPM display on a bar of 21 LEDs. The display flashes to indicate an alarm condition when the RPM exceed a preset limit. Design by Ray Marston. Project development by Steve Ramsahadeo.

he ETI Tacho/Alarm is an all solid-state project. It displays engine speed in analogue form (like a conventional tacho) as an illuminated section of a line of 21 LEDs. The length of the illuminated section is proportional to the engine speed, so that half of the scale is illuminated at half of full-scale speed, and so on. In other words, the display is in bar rather than dot form.

The Tacho/Alarm can be used with virtually any type of multi-cylinder petrol engine. It has two speed ranges, each of which can be calibrated by a preset pot to give any full-scale speed range required by the individual owner. Our prototype is calibrated to give full scale readings of 10,000 RPM and 1,000 RPM on a four-cylinder, four-stroke engine. The lower range is of great value when adjusting the engine's ignition and carburation for recommended tick-over speeds. The upper range has adequate resolution (500 RPM per step in our case).

A unique feature of our product is the provision of a visual over-speed alarm facility, which causes the LED display to rapidly flash on and off when the RPM exceed a preset level; the tacho continues to indicate the actual RPM under the alarm condition. Tachos are normally placed directly in front of the driver in sports/racing cars, so this visual alarm system is a highly effective 'attention getter' in such vehicles.

The unit is designed for use only on vehicles fitted with 12 V electrical systems. It can be used with conventional or capacitor-discharge (CD) ignition systems and is wired into the vehicle with three connecting leads. It can be used on vehicles fitted with either negative or positive earth electrical systems.

#### Construction


The complete unit, including the 21 LED display, is mounted on a single PCB. Take care over the construction, paying special attention to the following points:

(1) Our prototype uses a display comprising a linear row of 21 square LEDs, mounted horizontally on the PCB. You may prefer to use a semicircular display of LEDs, in which case you can mount the display on a separate board of your own design, with suitable connections to our board. In either case confirm the polarity and functioning of each of the 21 LEDs, by connecting in series with a 1k0 resistor and testing across a 12 V supply, before wiring into place on the PCB. Note that the LED colours can be mixed, if required.

If you use the same display form as our prototype, bend and adjust the LED leads so that each LED slightly overhangs the edge of the PCB when soldered into place.

(2) Seven link connections are made on the PCB. Also note that the external connections to the unit (0 V,  $\pm$  ve and CB) are made via solder terminals (Veropins).

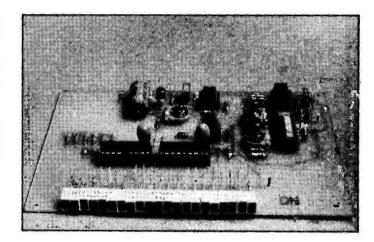(3) Range-changing is achieved via a three-pole two-way



switch. On our prototype we've used a DIL slide switch, mounted directly on the PCB, for this purpose. Some readers may prefer to mount this switch off-board.

(4) Note that the values of C2 and C3 must be chosen to suit the engine type and full-scale RPM ranges required (see the conversion graph). Our prototype, calibrated to read 10,000 RPM and 1,000 RPM on a four-cylinder four-stroke engine, uses C2 and C3 values of 22nF and 220nF respectively.

When the construction is complete, connect the unit to a 12 V supply and check that only LED 1 illuminates. If all LEDs illuminate, suspect a fault in the wiring of IC1.

#### **Calibration**

The unit can be calibrated against either a precision tachometer or against an accurate (2% better) audio gennerator that gives a square wave output of at least 3 V peak-to-peak. The method of calibration against an audio generator is as follows.

Connect the tacho to a 12 V supply and connect the square wav. output of the audio generator betweeen the 0 V and CB terminals of the unit. Check against the conversion graph to find the frequency needed to give the required high range full-scale RPM reading on the type of engine in question and feed this frequency into the tacho input. Switch SW1 to its high range (10,000 RPM on our prototype) and adjust PR1 for full-scale reading. Now set the generator to the alarm frequency and adjust PR3 so that the display flashes. Recheck both adjustments.

Now switch SW1 to its low range (1,000 RPM on our prototype), set the required full-scale frequency and adjust PR2 for a full-scale reading on the tacho. Note that the alarm facility is inoperative on this range.

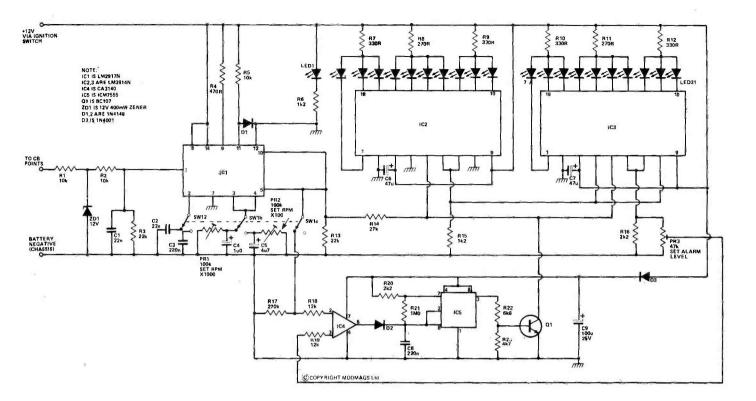


Fig. 1 Circuit diagram.

#### HOW IT WORKS

The ignition signal appearing on a vehicle's contact-breaker (CB) points has a basic frequency that is directly proportional to the RPM of the engine. Our tacho works by picking up the CB signal, extracting its basic frequency, converting the frequency to a linearly-related DC voltage and then displaying this voltage (and thus the RPM) on a line of 21 LEDs. The basic tacho can thus be broken down, for descriptive purposes, into an input signal conditioner section, a frequency-to-voltage converter section and a LED voltmeter display section.

The input signal conditioner section comprises R1-R2-R3-ZD1-C1. The CB signal of a conventional ignition system consists of a basic RPM-related rectangular waveform that switches alternately between zero and 12 V, onto which various ringing waveforms with typical peak amplitudes of 250 V and frequencies up to 10 kHz are superimposed. The purpose of the input signal conditioner is to cleanly filter out the basic rectangular waveform and pass it on to the F-to-V converter. It does this first by limiting the peak amplitude of the signal to 12 V via R1 and ZD1 and then filtering out any remaining high frequency components via R2-R3-C1. The resulting clean signal is passed on to the input (pin 1) of IC1.

IC1 is a frequency-to-voltage converter chip with a built-in supply voltage regulator. The operating range of the IC is determined by the value of a capacitor connected to pin 2 and by a timing resistor and smoothing capacitor connected to pins 3-4. In our application, two switch-selected presettable ranges are provided. The DC output of the IC is made available across R13 and is passed on to the high-impedance input terminals of the IC2-IC3 LED voltmeter circuit via series resistor R14. R14 is essential to the operation of the alarm section of the tacho.

IC2 and IC3 are LED display drivers. Each IC can drive a chain of 10 LEDs, the number of LEDs illuminated being proportional to the magnitude of the IC's input signal. Put simply, the ICs act as LED colleges

In our application, the two LM3914 ICs are cascaded in such a way

that they perform as a single 20-LED voltmeter with a full-scale range of 2V4. This full-scale value is determined by precision voltage references built into the ICs. The full-scale reference voltage (2V4) is generated across R16 and PR3. The configuration of our voltmeter is such that it gives a bar display, in which LEDs 1 to 11 are illuminated at half-scale or LEDs 1 to 21 are illuminated at full-scale. R7 to R12 are wired in series with the display LEDs to reduce the power dissipation of the two ICs. LED 1 is permanently illuminated so that the RPM display does not blank out completely when the engine is stationary with the ignition turned on.

The alarm section of the tacho is fairly simple. IC4 is wired as a voltage comparator with a stable reference voltage fed to its non-inverting (pin 3) input from PR3 and with an RPM-related voltage fed to its inverting (pin 2) input from R13 via SW1c. The output of IC4 is used to enable or disable astable multivibrator IC5 and the output of IC5 is used to enable or disable the inputs to the IC2-IC3 voltmeter via Q1 and R14.

At low engine speeds (below the alarm level) the input of IC4 is driven high, thereby disabling the IC5 astable by preventing C8 from discharging. Under this condition the output of IC5 is driven low, cutting off Q1 and enabling the tacho circuit to operate in the normal way.

At high engine speeds (at or above the alarm level) the output of IC4 is driven low, thereby enabling the IC5 astable to operate at a rate of roughly 2 Hz and alternately drive Q1 on and off. In the moments that Q1 is cut off, the tacho operates in the normal way, but in the moments that Q1 is driven on its collector pulls the pin 5 input terminals of IC2 and IC3 to near-zero volts and thereby effectively blanks the LED displays. The LEDs flash rapidly under the alarm condition, but continue to indicate RPM values.

The alarm point can be set in any position on the tacho scale by PR3. SW1c is used to disable the alarm section when the tacho is set to its low(1,000 RPM in our prototype) range. Note that the power supply to the alarm is decoupled from the main supply by D3 and C9.

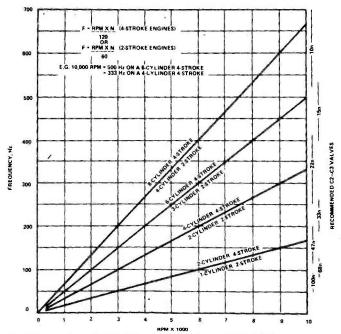


Fig. 2 Conversion graph to determine the values of C2 and C3.

#### Installation

The completed unit can either be mounted in a special cut-out in the vehicle's instrument panel or (preferably) can be assembled in a home-made housing and clipped on top of the instrument panel. In either case try to fit some kind of light shield to the face of the unit, so that the LEDs are shielded from direct sunlight.


To wire the unit into place, connect the supply leads to the tacho via the vehicle's ignition switch and connect the unit's CB terminal to the CB terminal on the vehicle's distributor. Note that the unit can be fitted to vehicles using either positive or negative earth systems.

The lower range of the tacho is of great value when adjusting the engine for correct tick-over. It is thus advantageous to arrange the tacho housing so that it can be easily dismounted from the instrument panel.

#### BUYLINES\_

All components used in the LED Tacho are common types and should present few problems. The dual-in-line slide switch is stocked by the major mail order companies that advertise in this issue.

Resistors all 1/4 W	/ 5%	C3,8	220n polycarbonate
R1,2,5	10k	C4	1u0 35 V tantalum
R3,13	22k	C5	4u7 35 V tantalum
R4	470R	C6,7	47u 16 V tantalum
R6,15	1k2	C9	100u 25 V electrolytic
R7,9,10,12	330R		
R8,11	270R	Semiconductors	
R14	27k	IC1	LM2917N
R16,20	2k2	IC2,3	LM3914
R17	270k	IC4	CA3140
R18,19	12k	IC5	ICM7555
R21	1M0	Q1	BC107
R22	6k8	ZD1	BZY88 12 V
R23	4k7	D1,2	1N4148
Potentiometers		D3	1N4001
PR1,2	100k miniature horizontal preset	LED1-21	Red, square type.
PR3	47k miniature horizontal preset	Miscellaneous	
Capacitors		SW1	4-pole 2-way dual-in-line slide switch
C1,2	22n polycarbonate	PCB, case.	

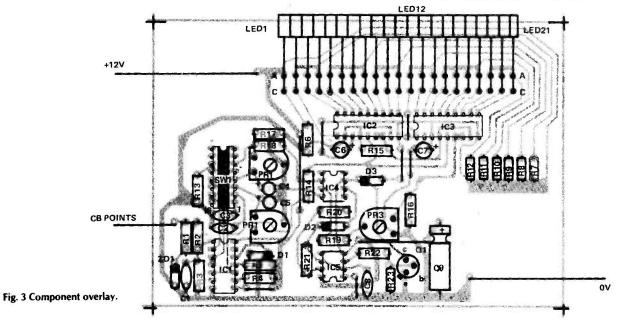

ETI

#### enter the computer age video genie system

12K MICROSOFT BASIC 16K RAM, UHF MODULATOR INTERNAL CASSETTE

**SECOND CASSETTE** 

**80 COLUMNS** 

**MACHINES** 

INTERFACE

- **70 LINES PER MINUTE**
- **GRAPHICS CHARACTERS** INTERFACES TO MOST





ACCESS AND BARCLAYCARD ACCEPTED

100's OF PROGRAMS AVAILABLE TRS-80 LEVEL II SOFTWARE

#### GENERAL NORTHERN MICROCOMPUTERS

46 Middle Street, Blackhall Hartiepool, Cleveland Tel: Peterlee (0783) 863871 7 SEMMENT DISPLAYS NEWLETT-PACKARD High Efficiency "eitre bright" bei incb. red. Common mode type SOR: 7850 (etniker to 01707). Common Catheda version 5002-7853 (aimitar to 91,704). OND PRICE BRAND NEW E1. Set of six of aither type. Ell incl. YAT.

FAMICONLS FID 10 0.25" Mini rod 7 segment display. Common sunde, 50p 5 for £2.5

LP1171 & LP1179 MODULES MULLARD UPIT71 and UPIT78 trains heart and 6 contents which form the heart of quality ARTH tears. Fall medium long-wave and WHF coverage. Hery he used as the heart of aposity partiable or buser. Supply 84 of 15mA output 70mV of 20K. Pair CS.78.

Supply WHT OATA.

UPITS7 Medican 8 Lang Wave Tonor, medick-baser 52.50 LP1185 Varican CS.80

+ WITH pre-amplifier and fit. 8 Long Were examply.

\* With pre-amplifier and fit. 8 Long Were examply.

\* Supplied as two boilt and lessed writs.

\* R.T. and LF. steroe prompilifier and radio 4 x 2 x 1".

\* Unified exactly

\* 5 + 5 with starce amplifier 12/14 wit 4 x 2 x 1".

\* Complete with circuit, data and connection diagrams.

\* Limited quantity available, ex-stock.

EX-MOTOROLA Only CS. Post 50p

PRO RES Professional capacitor beam-arm microphone by Eagle.

A preced 85 on beam-arm capacitor studie increphone sales a cardial capacit. A high standard of finish
for in-statem sand of traduct momphs to withstand long profess below and retracting complete
with I red and 1 Mack windshield and 6 metras of fivile acrossed cable terminating of the microphase and is £19.95 cessacter. sence: 600 dems (flesting), Response: 20-18,000 Hz. Sensettivity: — 79 dBV. Cable: 6 maires dector ablaided. Conneccion: XUI 3-116. Battery type: HP7.

THE COMMON THE COMMON

MAMS TRANSFORMERS ON 200/250V to put

Туре	Current	Size	Price
12¥	100m/s	1%x1%x1%	€8.95
12¥	500m/s	1%x1%x1%	£1.35
6-0-6	300m/A	2x2x2	£1.50
124	2 amps	3x21/2x21/2	€2.95
8-20V	1 amp		€2.50
12-20V	1 ama		£2.50
14-D-14V	1.5 amp		£2.50
12V	1 amp		€2.50
	Size 6x5x5	cm. Postage 50 <sub>1</sub>	e each

2W MM. W/W YOL. CONTROLS 108-47K. 10 for £6

10 TURM POTS. 478-100K. 10 far £17.50

INULLARD TRANSO, IC notice amplified RGA GA3000, Fit if £1.50, ar F2 56 BUZDS TEXAS, C1.50 mm. 10 for £12. BUZDS TO3 Texas TV power transisters, 10 for £15. 190 for ETZE.

ETZELLARD AD161-AD162. Matched pair 80p, 10 pairs ES.
100 pairs ESS.

Carless of 800 pairs EZSO EX-STOCK.

S or 12 volts TRAAE23 ATES voltage rapploters 50p oc.
100m/msys [TD09] pair 10 CA.30.

CAJSOO RCA POSITIVE VARIABLE 5 volt 100m cmp variable.
18-244 90p oc.
TEXAS 10 WATT, IC, Amp SS170016 5-5in package E1.25. 10
br E18.

n. BEB (14 pla DRL) IC TY sexad asspirier-detector by AYES on Mt. other parts. Complete with data. 68p. 10 far ES, 100

STEREO CASSETTE TAPE HEAD. High quality rapid meet for meet machines record/replay with mounting brack XRPS (X24RP 18). V track. Roc./Play modern inp. XRPSID (X24RP 18). V track Rocer/ Play two inp. XRPSID (X24RP 18). V track rares for XRP series REF1 (X254RP 18). V track rares for XRP series REF1 (X254RP V track Properties). The Series REF1 (X254RP V track Properties). The Series REF1 (X254RP V track Properties).

GX12 E387 Ernen 875 shins 2mA GX20 E382 Ernen 90 shins 10mA Mitathiux Tape Meade 14 Track AMS Erne KKS-T with Me-weld screen WKS-T with Me-weld screen





404 Edgware Road, London, W2, England 01-723 1008/9

## **Marshall's**

A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA Industrial Sales: 01-328 1009

Mail Order: 01-624-8582-24hr, service Asio estat shous 325 Edaware Road, London W.2 40 Crickhemord Bradway, Edindon NW2-85 West Regent 54 - Grasgow 108A Stokes Croft, Bristol

We now supply the extremely reliable and cost conscious LEADER range of

testgear.
SINGLE TRACE OSCILLOSCOPES LBO 510A 5" 4MHz 20mV LBO 512A 5" 10MHz 10mV LBO 513A 5" 10MHz 10mV LBO 507A 5" 20MHz 10mV DUAL TRACE OSCUL OSCOPES LBO 308S 3" 20MHz 2mV LBO 508A 5" 20MHz 10mV LBO 520A 5" 35MHz 5mV LNO 514 5" 10MHz 5mV T.V : RADIO TEST GLAR LSG 16 Signal Generator LSG 231 FM Stereo Signal Generator LCG 392U PAL B Partern Generator £169.00 AUDIO TEST GEAR AGO 125 Teacher
LAG 26 Autho Generator
LAG 190A Autho Generator
LOM 170 Distortion Meter
LFM 39A Wow/Flutter Meter (Din)
LFM 39A Wow/Flutter Meter (Din)
LFM 24040 Tester
LAG 125 Low Distortion Autho Generator £249 00 GENERAL TEST GEAR LCR 740 LCR Bridge
LTC 906A Transistor Checker
LVT 72 Fel Transistor Checker
LTC 907 Transistor Checker
LAT 47 Attenuator
LAT 45 Attenuator
LFG 1300 Sweep/Function Generator £ 135.00 £ 190.00 £ 139.00 £ 135.00 £ 75.00 £ 299.00 AMATEUR RADIO OM 815 DIP Meter
IM 870A Antenna Imperance Meter
IM 880 RF Power Meter
IM 880 SWR/Wait Meter
AC 895 Antenna Coupler
AC 895 Antenna Coupler
AC 897 Antenna Coupler

Please send large SAE for special catalogue. All prices exclusive VAT/carriage.

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.



Lots of old friends, but also many new products including leader test gear, Crimson Hi Fi Modules, Rechargeable NI Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc. Available by post, UK 75p post paid: Europe 95p post paid: Rest of world £1.35 post paid.

#### SINCLAIR INSTRUMENTS Digital Multimeter

PDM35 £ 34.50 " DM235 £ 52.50 " DM350 € 72.50 " DM450 £ 99.00

Digital Frequency Meter PFM200 £ 49.80

Low Power Oscilloscope

SC110 £139.00

NEW

TF200 Frequency Meter

£145 00

TGF105 Pulse Generator

£ 85.00

#### CRIMSON ELEKTRIK HIFI MODULES

CE608 Power Amp £20.09 CE1004 £23.43 CE1008 £26.30 CF 1704 £33.48 17 37 CE1708 £33.48 CPS1 Power Unit £19.52 CPS3 £23.52 CPS6 £30.00 CPR1 Pre Amp £32.17 CPR1S Pre Amp £42.52 All Prices + VAT + postage/ packaging

Don't forget! We also carry an impressive range of semi-conductors, passive components, electro mechanical components, tools etc

#### AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

The color   1-10				py (with an S	AE please). Par	t 4 of the cat	alogue is une c			ed version of pt.17.
1.000				TTL N and LSN			74LS169 2.00	VARICAP	TRANSISTORS	
Carrier   Carr				7400N 0-13			7417UN 2.30 7415170 2.00			
1.58					7446N 0.94				BC 238 0.08	
1.50			KB4420B 1.09							
Finds										22P, 27P, 33P, 47P
1900   1.0							74177N 0.78			
1988   1989			KB4432 1.95							
1979   9.66   1984   1.15   24,000   1.25										INU, 2N2, 3N3, 4N70.06
Diday   1.68										
Figure   1.00					74LS54 0-24	74LS126 0.44	74185N 1.34		BC546 0.12	1000.22000.09
1978   1.75			KB4441 1.35							
Miles   1.00										10N,100N0.16
HARDON D. 1.00 NROSCHE J. 2-26 74619 0.24 7470 0.38 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470 0.39 7470 0.40 7470					7470N 0.28				BC639 0.22	
SMANCE 1.65 SMANO 3.75 74150 0.22 741671 0.38 741401 2.65 741600 0.09 50041 0.00 50041 0			NE5044N 2.26						DOM: 1 775 0 10	IND SOLDER IN0.09
Michael   1.60   Septim   2.01   74   74   74   74   75   74   74   74										
NESSAN 0-106 SIS-316 2-00 744281 0-24 74405 0-17 74405										
RESPON D. S. BIAGO S. 172   7412   0.29 7400   0.89 74	NE555N	0.30		74LS10 0.24		74144N 3.12				
Misself   1.09	NE556N		SL6600 3.75							
Misself   4.29   50.70   2.15   74180   0.38   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   74181   0.18   0.18   74181   0.18   0.18   74181   0.18   0.18   74181   0.18   0.18   74181   0.18   0.18   74181   0.18   0.18   74181   0.18   0.18   74181   0.18   0.									2SD760 0.45	
## ## ## ## ## ## ## ## ## ## ## ## ##	NES64N									POLYESTER (GENERAL)
NESTOR   1.85   PRESIDENT   1.75   74   180   0.30   74   74   74   74   74   74   74   7	NE565N		1CL8038CC 4.50							
SEAZES   1.28   INJ.   1.21   1.29   74.17   0.30   74.89   1.04   74.15   0.44   74.15   0.44   74.15   0.45										
TROMODING 1.48   MAIL 122   1.15   74280   74780   742										
MATORIE 0.64 MALES 1.45 76250 0.45 74250 0.4	TBA651	1.81		7420N 0.16	74LS85 0.99		74LS365 0.49	IN5402 0-15		20mm LEAD SPACING
WATING   0.65			HA11225 1.45			74154N 0.96				
MATING 0.59   MATING 2   1.95   7428   0.22   74785   0.10   74157   0.10   0.00   74157   0.10   0.00   74157   0.10   0.00   0										
LAYARD 0.27 MAJAH 1.20 74279 0.27 74289 0.35 74285 0.36 742839 0.40 74289 1.40 74289 1.40 74289 0.35 74285 0.3	uA710PC	0.59		. 7423N 0.27	74LS90 0.90	74156N 0.80	7413374 1.80			
NATATION 0.70								6A/200V 0.75	2SJ 48 3.00	
WATERSON   0.36							74LS393 1.40	-		
WASSISSESSESSESSESSESSESSESSESSESSESSESSES				7428N 0+35	74LS92 0.78					
PRECUMENT   1.00						74160N 0.82	TOKO COILS A	ND FILTERS		
TURNAGO 0.75 TURNAGO 1.75 TURNA							SEE THE EXTE	NSIVE SECTION		
TUMANG 1.60 SAALOS 3.75   74LS32 0.24   74LS95 0.15   74LS95 0.25   74LS			& SYNTHESISER ICS					RICE LISTS AND		
TENIORS 2-11 SAALDSS 3-15 14-178 O-40 A999 U-50 7415-8 0-92 THE TENIORS 1-15 SAALDSS 3-15 14-178 O-40 A999 U-50 7415-8 0-92 THE TENIORS 1-15 SAALDSS 3-15 14-178 A999 U-50 7415-8 0-92 THE TENIORS 1-15 THE TENIOR	TCA940E	1.80	SAA1056 3.75	74LS32 0.24		74LS162 1.30	I.	DINDUCTORS		
TRAILS 5 1.45	TDA1028					74163N 0.92		with the blue was put your was been been select		
TINIDIO 2 1.95   LR1232   19:00   7440N 0.17   744810 0.18   74481 0.10   10041-33m1 0.19   10041-33m1									SMALL SIGNAL	
TRAIO72 2-69   LRI242 19.00   74LS40 0.24   74L99N 0.63 74L950   1.05	TDA1062								RF DEVICES	
TOALORS 1.05	TDA1072		LN1242 19.00			74165N 1.05		0.19		TANTALUM BEAD CAPS
TOALIGOG 3.05 M95522 11.30 741.542 0.99 741.1N 0.68 100M181 series 120M1-1.59 0.55 M95527 7.85 10M156 2.00 M95528 7.85 4044 0.20 M1562 0.05 M95528 0.75 M1562 0.05 M95528 0.75 M1562 0.05 M95528 0.05 M1562 0.05 M95528 0.05 M1562 0.05								0.33		
HAL137   1-20						7416/N 2.50		S		
TABLE   1.00	HA1137	1.20	MSM5525 7.85				120mH-1.5H	0.55		
TIAN 220 1.40 MS55271 9.75 4049 1.70 1.80 1.70 1.80 1.70 1.80 1.70 1.70 1.70 1.70 1.70 1.70 1.70 1.7				4043 0.85		(i)		ER .		
MI-130					VOLTAGE REGULA	TORS	PB2720	0.44		ALLIMAN EL COTROL VILOS
IMA1307   1.55	LM1303				1 79				BF395 0.18	
NC1300   1.20			ICM7107CP 9.55			CRYSTAL FIL	TER PRODUCTS	LEDs		
MC1500   1.20							POLE TYPES: 1 5			
HA1370 1-90 SP8647 6.00 4051 0.65 78SUTEZ 1.75 79SUGEC 6.00 4051 0.56 78SUTEZ 1.75 79SUGEC 6.00 4775 1.00 450 79SUGEC 6.00 4051 0.56 78SUGEC 6.00 40					78Lseries 0.35					
NA   198   2-75   95-990   198   1	HA1 370	1.90								
MC190  1.55   mM4015   4.45   4066   0.56   7230N   0.65   10022D 2.48HZ SSB 17.20   3MH GN CLEAR   0.16   3MH GNED   0.16   3MH GN CLEAR   0.16   3MH CLEAR										47/100.09
SLIGE   1.60   HD  2009   6.00   4068   0.25   L200   1.95   HF  FIFTHER:   SMPL STRIPER:   360   36							KHZ SSB 17.20 3			
SLI611P 1.60	SL1610P						LIJA LUIV.			
Silicia   1.80	SI1611P					B34F8A 34.5				
Sil620P   2.17   CMOS 4000 SERIES   4072   0.20   LM337MP   1.48   No splits available   2.17   Sil621P   2.17   4001   0.17   4075   0.20   MICROMARKET   3rd OT 30pF H2SU 1.65   SMM ORA CI   0.29   Sil625P   2.17   4002   0.23   4077   0.20   8080A/2   7.50   3rd OT 30pF H2SU 1.65   SMM ORA CI   0.29   Sil626P   2.44   4008   0.80   4078   0.20   8212   2.30   Sil626P   2.44   4008   0.80   4078   0.20   8212   2.30   Sil626P   2.44   4008   0.80   4093   0.78   8216   1.95   Sil640P   1.89   4010B   0.58   4093   0.78   8216   1.95   Sil640P   1.89   4010B   0.58   4093   0.78   8224   3.50   Pairs FM   3.25   Pa						RADIO CONTE				100/63,470/16,
SLI621P   2.17   4001			CMOS 4000 SERIES				available!	MM YELLOW 0.18		1000 0 5 170 60 0 00
SLI623P 2.24 4000 0.17 4076 0.90   SLI623P 2.17 4002 0.23 4000 0.17 4076 0.90   SUBJESSE 2.17 4002 0.23 4077 0.20 8080A/2 7.50   SUBJESSE 2.17 4008 0.80 4078 0.20 8212 2.30   SUBJESSE 2.14 4008 0.80 4078 0.20 8212 2.30   SUBJESSE 2.14 5.50   SUBJESSE 2.14 5.50   SUBJESSE 2.15   SUBJESS	SL1621P			4073 0.20	MICROMARKET					
SIL626P 2.44 4008 0.80 4078 0.20 8212 2.30 3rd OT 30pF HC25U 1.65 2.5 x SMM GRA 0.24 3.10 0.69 SIL630P 1.62 4009 0.58 4093 0.78 8216 1.95 PM TX :- FWINTER RED 0.56 JT76 0.65 JMM TNFR RED 0.56 JT76 0.65 JMM TNFR RED 0.56 JMM TNFR RED 0.55 JMM TNFR RED 0.56 JMM TNFR RED 0.55 JMM TNFR RED 0.56 JMM T	SL1623P	2.24			WICHUMARKET					3300/250.69
Silidade   2.44   4008	SI.624C				8080A/2 7.50	AM/FM RX:-				1000/1000.88
SIL630P   1.62   4009   0.58   4082   0.20   8214   3.50   5M   NNFR RED 0.56   J176   0.65   AIAL   (HORIZ. MOJNT)					8212 2.30		F HC25U 1.65	2.5 X SMM ORA 0.24	J310 0.69	
SIL641P 1.89 4011Ae 0.20 4175 0.95 8224 3.50 Pairs FM 3.25 IR OPT CPUR 1.44 40673 38X51 0.49 10763.00 4012 0.55 4506 0.51 8255 5.40 ULNZ242A 3.05 4013 0.55 4510 0.99 ULNZ242B 1.00 4015 0.95 4510 0.99 6810 5.95 10000 0.70 4016 0.52 4512 0.98 6810 5.95 100000 0.70 4016 0.52 4512 0.98 6810 5.95 100000 0.70 4016 0.52 4512 0.98 6810 5.95 100000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 10000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000 0.70 4016 0.52 4512 0.98 6810 5.95 10000000 0.70 4016 0.52 4512 0.98 6810 5.95 10000000 0.70 4016 0.52 4512 0.98 6810 5.95 10000000 0.70 4016 0.52 4512 0.98 6810 5.95 100000000000 0.70 4016 0.52 4512 0.98 6810 5.95 1000000000000000000000000000000000000	SL1630P	1.62	4009 0.58	4082 0.20	8214 3.50				J176 0.65	
Same   California   Californi	SL1640P									
TAX-2020   3.00   4012   0.55   4506   0.51   8255   5.40     Sept   5.40     Sept   5.40     Sept   5.40     Sept   5.40     Sept										
UIN2242A 3.05 4013 0.55 4510 0.99 UIN2283B 1.00 4015 0.95 4511 1.49 6800P 7.50 CRYSTALS 3.5 digit 9.45 38K60 0.58 M27680 0.75 A23080E 0.70 4016 0.52 4512 0.98 6810 5.95 32.768 MEZ 2.70 5 digit 8.95 8960 0.75 A23080E 1.84 4017 0.80 4514 2.55 6820 7.45 100MHz 3.85 A23080E 1.40 4020 0.93 4520 1.09 6852 4.85 1.00 A25102 0.90 4521 2.36 6852 4.85 1.00 A25102 0.90 4522 1.49 MC2708 7.50 4.000MHz 2.00 MXEMS (SIBL1=MIDLOB) CA3140E 0.46 4023 0.17 4529 1.41 2114 6.50 4.194 4.994 2.20 4.20 4.20 4.20 4.20 4.20 4.20 4.2	TDA2020									33/160.09
CA3080E 0.70 4015 0.52 4512 0.98 6810 5.95 32.768 kHz 2.70 5 digit 8.95 8951 0.70 1000/16	ULN2242A	3.05	4013 0.55	4510 0.99	( uom 2 50	CHVCTALE		3.5 digit 9.45	SK60 0.58	47/25,100/160.10
CA3089E 1.84 4017 0.80 4514 2.55 6820 7.45 100CHZ 3.85 (A3090AC) 3.35 4019 0.60 4518 1.03 6850 4.90 6850 4.85 1.00HZ 3.00 1.0MHZ 3.00 1.0M	ULN2283B									
CA31990AQ 3.35								digit 8.95		
CA3130E 1.40 4020B 0.93 4520 1.09 6852 4.85 1.00Ftz 3.00 3.2766Mtz 2.70 4020 0.82 4521 2.36 4022 0.90 4522 1.49 MC2708 7.50 4.000Mtz 2.00 4.000Mtz 2.000Mtz 2.00 4.000Mtz 2.000Mtz 2.					6850 4.90	455kH2	5.00			1000/35,4700/160.45
CA3130T 0.90 4022 0.90 4522 1.49 MC2708 7.50 4.000MHz 2.00 MIXEMS (SHL1=MIXOR) CA3140E 0.46 4023 0.17 4529 1.41 2114 6.50 4.194 J9MHz 2.30 SHL1=MIXOR) CA3189E 2.20 4024 0.76 4539 1.10 4027 5.78 6.5536MHz 2.10 SHL1=8.1-200MHz 4.55 CM161. MC3357P 2.35 4025 0.17 4549 3.50 2102 1.70 10.0MHz 2.50 SHL1=8.1-200MHz 4.55 SHL1=MIXOR) MC3357P 2.35 4025 0.17 4549 3.50 2102 1.70 10.0MHz 2.50 SHL1=8.1-200MHz 4.55 CM161. MIXEMS (SHL1=MIXOR) SHL1=1-200MHz 4.25 CM161. MIXEMS (SHL1=MIXOR) CA3130T 2.30 SHL1=MIXOR) 0.25W, 5W EL2 CARRON 1c/m-1.00.02 0.25W, 5W EL2 C	CA3123E	1.40	4020B 0.93	4520 1.09	6852 4.85		0.00			1000/500.58
CA3140E 0.46 4023 0.17 4529 1.41 2114 6.50 4.19439412 2.30 SBL1 1-500412 4.25 CABON 10.60425 2.20 4024 0.76 4539 1.10 4027 5.78 6.5536412 2.10 SBL1 1-500412 4.55 SBL1-8 1.1-200412 4.5	CA3130E				MC2708 7 50				-	RESISTORS
CA3189E 2.20 4024 0.76 4539 1.10 4027 5.78 6.5536MEI2 2.10 SELIL-8 1-200MEI2 4.55 CM161 Miniature clock, 12/24 hr., alarm, 12-100MEI2 9.25 SRAI 5-500MEI2 9.25 SRAI 5-							2 20		LCD Module	0.25W, 5% EL2 CARBON
NC3357P 2.35 4025 0.17 4549 3.50 2102 1.70 10.0MHz 2.50 SBL1-x 10-1000Mtz 5.75 Miniature clock, 12/34 hr., alarm, 10.005 Mrs 2.50 SBL1-x 10-1000Mtz 5.75 Miniature clock, 12/34 hr., alarm, 10.05 Mrs 2.50 SBL1-x 10-1000Mtz 5.75 SRAI 5.500Mtz 8.45 12/34 hr., alarm, 10.05 SRAI 1.500Mtz 9.25 SRAI 1.500Mtz 13.35 SRAI 1.500Mtz 13.35 SRAI 1.500Mtz 9.25 SRAI 1.500Mtz 13.35 SRAI 1.500Mtz 9.25 SRAI 1.500Mtz 9.25 SRAI 1.500Mtz 13.35 SRAI 1.500Mtz 9.25 SR					4027 5.78	6.5536MHz	2.10 SHL1-8			1chm=10M0.02
IM3900N 0.60 4026 1.80 4554 1.53 2112 3.40 10.69938Hz 2.50 SRAI 5-5008Hz 8 455 12/22 hr., alarm, 12/24			4025 0.17	4549 3.50	2102 1.70	10.0MHz	2.50 SBL1-X	19-1000MHZ 5.75	Miniature clock,	
LA3914N 2.80 4029 1.00 4566 1.59 HM4716 4.50 10.245Mdrz 2.50 SRAIH 5-500Mtz 11.35 backlight Air for 9.95 100mm TYPE 100mm	1M3900N	0.60					4 50			
No.										
HSH400 0.80 4035 1.20 4569 3.03 11.52MHz 2.50 HORIZ CERMET PRESETS 100MHz 3.00 11.52MHz 3.00 11.52MHz 3.00						10.7MHz	3.00 SRA3			
KB4406 0.60 4040 0.83 4572 0.30 100MHz 3.00	KB4400		4035 1.20	4569 3.03	1		2.50			HORIZ CERMET PRESETS
KB44LZ 1.95 4V4Z 0.03 4505 1.10	KB4406					1 TOOMH2	7.00 1			lk, 10k0.27
	KB4412	1.95	4042 0.85	4585 I.10						

Please send an SAE with all enquiries. Access/Barclayod (min £5 please) Callers welcome PRICES EXCLUDE VAT - PLEASE ADD 15%\*
Postage 35p per order. CWO please. (\*UK only)

ambit

CWO PLEASE: Commercial MA terms on application. Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.


INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

CATALOGUES
2 & 3....60p ea
4.......75p
(4 inc. rev. ofpart 1)
ALL PARTS:

.....£1.75.....

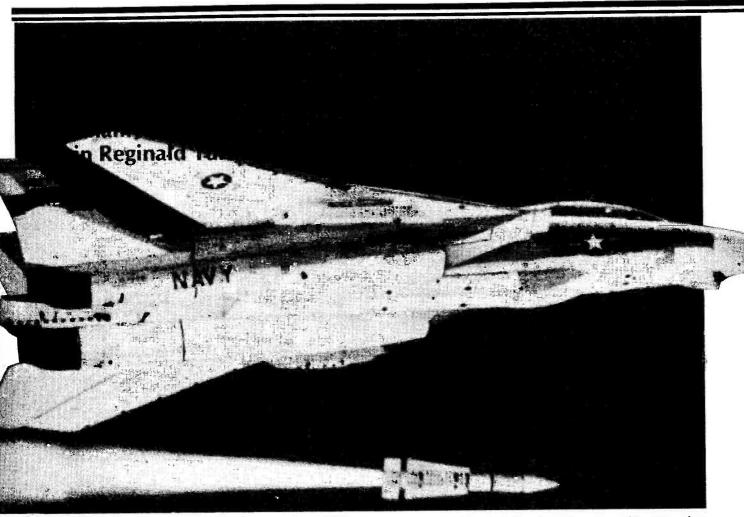

he cause of the Ariane rocket accident in May 1980 has been found. As I reported in October's Astrologue, the second test flight of the European launcher lasted only two minutes. The vehicle broke up in flight and exploded.

Extensive tests, simulation and examination of wreckage recovered from the sea were necessary to narrow down the range of hypotheses and eventually reproduce on the test-stand the behaviour of the faulty engine.

It was proved that the cause of the engine failure was not external to the engine itself, or due to a foreign body present at ignition or an acoustic 'ground efect' during lift-off.

Accident investigators have found that the failure was due to combustion instability at high frequency (above 2 kHz) in one of the four first stage engines 5.75 S after ignition. The vibration lasted only 0.3 S, but it was so violent that it abruptly altered the characteristics of the fuel injector. Damage to the injector destroyed the engine 64 S after ignition, starting a propulsion bay fire, which destroyed the vehicle 108 S after lift-off.

#### **Fuel Injection**

The fuel injector is a very complex element of the rocket design. It is used to deliver almost 250 kg of fuel and oxidant to the combustion chamber through nearly 1,000 orifices. Its failure was probably due to slight variations in component manufacture, although the injectors behaved normally in nearly 200 engine development tests. To resolve the problem, injector manufacturing tolerances are to be altered and injectors will be selected by static firings on the engine test-stand.

The third Ariane vehicle should be equipped with the new injectors and ready for launch by the end of March 1981, if

Trials of the improved AIM-54C Phoenix missile continue. This US Navy photo shows an engineering development model being fired from an F-14 Tomcat fighter at the Pacific Missile Range. Once again, the new model, teamed with the Hughes' AWG-9 RADAR fire control system, behaved perfectly, passing well within the lethal distance of the drone target. The Phoenix is regarded as one of the world's most technologically advanced tactical missiles.

testing proceeds satisfactorily. The fourth and last test flight would then be scheduled for June 1981. The first operational launch could take place in October.

#### **AWOL Satellite**

Late last year, RCA's multi-million dollar Satcom III satellite disappeared 14.5 S into the 28 S apogee kick motor burn (to place the satellite in geostationary orbit). A study of the incident has suggested two possible causes.

If, when the motor fired, the exhaust cone broke, hot gases would have melted the back end of the satellite, destroying the communications equipment. Alternatively, if, after the motor fired, the solar array was deployed prematurely, suffering structural damage due to thrust, a total power loss would ensue. As exhaust overheating was observed prior to loss of contact, the review board has opted for the first alternative.

In addition to the cost of the launch and hardware involved, RCA may lose a further \$20 million in expected revenue. However, the venture was insured for around \$77 million

In the meantime, Satcom III's customers can use 11 transponders on another satellite (Comstar D-2) for \$40,000 per transponder — the same as the Satcom usage charge. Comstar D-2's full charge is normally \$70,000 per transponder. RCA will launch a replacement satellite in June 1981.



#### In Print

Reginald Turnill has been covering spaceflight since the Soviet-US missile race in the post-war years, which developed into the race to land a man on the moon. He reported for the. BBC on every manned spaceflight from Gagarin to the joint Apollo-Soyuz mission in 1975, including the first moon landing. His wealth of first-hand knowledge of the major space

projects reflects in his authoritative writing on the subject. In nearly 400 pages. The Observer's Spaceflight Directory updates and augments the smaller Observer's books on manned and unmanned spaceflight. It includes sections on space programmes in 14 countries, tabulations of manned and unmanned flights and blow by blow accounts of satellites and launch vehicles from Oscar to Skylab and Surveyor to the Space Shuttle. Soviet projects are also covered extensively.

#### **Prize Day**

You can win a copy of this magnificent handbook by trying your hand at our simple, free entry competition. All you have to do is complete the crossword by solving the cryptic clues. Most of them offer two means of arriving at the solution and most are fairly simple.

When you've solved all the clues (here's the nasty bit), give each letter of the alphabet a number (A-1, B-2, .... Y-25, Z-26), add up the numerical value of all the solutions, write that number in the space provided on the coupon and send your entry to:

ASTROLOGUE CROSSWORD.

ETI,

145 Charing Cross Road,

London WC2H 0FF

Closing date for entries — January 31st 1981.

If you don't win the competition, you can get hold of your own copy of The Observer's Spaceflight Directory by Reginald Turnill, published by Frederick Warne, for £7.50 from any good bookshop.

#### CROSSWORD CLUES -

#### Across

- Messenger of the Gods, first in line from the Sun. (7)
- Car step seen through prisms, (7)
- One of those returned from the Moon in a rocket. (4)
- Such a wing on a variable geometry aircraft. (5) Major or minor, a friend of Goldilocks. (4)
- In Scorpio and in plant a resistor. (7
- Benny's friends in the sky send out streams of gas
- Getting up and down shortly giving lots back. (4)
- Getting on course for the Moon initially in fast limousines. (3)
- Initiatives 4: Neil Armstrong 2, giving support. (4) Imitates Bonny and Sam. (4) Troubled SOS in grim for first Mercurial Gemini

- National Oceanic and Atmospheric Administration.
- Peenemunde led to Saturn for him. (5) Join Oriental take-off for one. (4)
- The seriousness of the downward pull. (7)
- Enterprise will never be this, Columbia. (7)

#### Down

- The Vikings headed here and returned in express ramjets. (4)
- Company trek carrying a payload. (6) Plane turn about vertical axis way back. (3)
- In part, it's unlikely to provide a shining example. (3)
- Propulsive force through American street. (6) Shepard or Bean in a Lancaster bomber. (4)
- Liberty Bell did this, we hear five accross the channel. (4)
- Geostationary Operational Environmental Satellite leaves. (4)
- At Los Angeles south missile. (5)
  Pasadena's famous laboratories tenth, sixteenth and twelfth. (3)
- So, point to call for help. (3)
- A damp reception for astronauts partly due to phase angle. (3)
- The French southern Launch Escape System. (3)
- French place of departure for Ariane. (6) Graduate back with credit for nebula. (4)
- Brief moment on our satellite. (4) Scheme and French celestial body. (6)
- Southern seaman only coming out at night. (4)
  Narrow beam fired by futuristic gun. (3)
- Nameless aircraft alias airborne crockery. (3)

1	2				3		4			5	6
7				8		77		9	10		
	<b>\</b>		11			12		1. 3			
13		14							15		16
			4		17		T				
18	19		-	20				21	22	23	
			24				Γ				
25											26
27				28	29		30		31		
			_3								
32					-	1	33				

NAME		111	2.5				25	- 41			y 20	*		8 y	g.		O.	٠.	y 1	- 1			,	e: •	. 4	*1	. 4		
ADDRESS				г.	, .	4 4	9.									i o		. "	- 4-			4	;			٠	. v		
	( 6 )		• 15			8.2	 ds: J	4.5	20 10		X 3		*(			2 5	-8			r	> 1*		4	• -0		61	4 0	1 4	
	5 1 1	7.			ę ·	4 5			. ,	- 4	9 1			2. 1	9		-1%	,51 °				ŵ	W.	4 -		161	4. 19		
NUMERICAL	VA	LU	E		ν.	- /-	. 7				4 .						ě.			\$ 1	. ,	si	w .	V 1346	2 1		2 1	. 4	

ETI


#### Now you can have LINEAR REGRESSION at your fingertips!

With the FX-3500P, Casio's new low-cost programmable scientific. An abundance of built-in functions, including Linear Regression. Prov. price: UNDER £30.
 
#### THE ULTIMATE WATCHES

\* STAR BUY FOR 1980 \*
Our best selling watch





#### **12 MELODY ALARM** CHRONOGRAPHS

Hours, minutes, seconds, am-pm, 12 or 24 hour. Day, date and month auto calendar.

Alarm. 7 melodies, one for each day of the

week. Hourly time signal. With "Big Ben" type

Date memory. Select either "Wedding March' or 'Trinklied' to be played.

Birthday and Christmas Memory.

Countdown alarm. From 1 second to 1 hour.

After zero count continues positively.

rtch. 1/10 second to 1 hour. Net, lap.

Picturesque moving display of notes played Light. Lithium, Glass. Water-resistant cases.

M-12 Resin, s/s trim, M-1200 all s/s 9.0 mm





£19.95

£32.50

#### LCD ANALOGUE/ DIGITAL

Alarm Chronograph with countdo Analogue. Independent hours and minutes with synchronous digital seconds. Dual time

Digital. Hours, minutes, seconds, day and

Stopwatch. 1/100 second to 12 hours. Net lap and 1st and 2nd place. Start/stop and 10 minute signals

Alarm. For 30 seconds with carousel display.

Countdown Alarm. Normal and net times to 1 hour with amazing "Star Burst" flashing

Time Signal. Half-hourly and hourly chimes. Tone control. Lithium battery. Light. Water-resistant case. 8.65mm thick. Mineral glass.

AA81 Chrome plated AA81G gold plated AA82 stainless steel

AA83 Dress watch, s/s



£29.95

£49.95

£39.95

£29.95

#### for around 40 functions **100 METRE WATER** RESISTANT

Alarm chronographs with countdown Amazing 5-year lithium battery life, Hours,

Amazing 5-year lithium battery life. Hours, minutes, seconds, am/pm, day, date and month. 12 or 24 hour. Time is always visible regardless of display mode.

Stopwatch. 1/100 second to 1 hour. Net.lap, and 1st and 2nd. Start/stop signal, 10 minute signal.

Alarm. Sounds for 30 seconds.

Countdown Alarm. Normal and net times to 12 hours. Start/stop and 10 minute signals. Times signal. Half-hourly and hourly chimes.

Time signal. Half-hourly and hourly chimes.
W-100. All resin. W-150B All s/s. W-150C
(not illustrated) s/s case/resin strap. £29.95

A250. As above but with standard water-resistant case

\$220. As above but with dual tune in lieu of alarms and chimes

F300 Sports Chronograph (right). 8 digits, hours, minutes, seconds, date and day indicator, 1/100 second stopwatch; net, lap and 1st and 2nd place times, to 12 hours. Resin case, s/s trim. Water-resistant. Glass. Light.

£17.95 110QS-37B Metal version

F81 Alarm Chronograph (far right). 8 digit dsplay of hours, minutes, seconds, am/pm and date. 24-hour alarm, hourly chimes, 1/10 second stopwatch to 12 hours; net, lap, 1st & 2nd place. Resin case/strap. Water resist. Mineral glass. Nightlight.

83Q8-41B. S/s jacket version £19.95







£24.95

£25.00

£12.95

£15.95

OTHER CASIO WATCHES Remember we will BEAT lower prices by 5%

OTHER CASIO WAI CHES Remember we will be A I lower prices by 5% 8 digit besic watches. F7C £8.95. 111QS-348 £14.95. Chronographs. 95QS-36B £19.95. 56QS-38B Digital/analogue £14.95. Calculator/Chronographs. C80 £24.95. C801 £29.95. Adam chronos. 81QS-35B all s/s £29.95. 83QGS-41B. Gold plated. £29.95. 81QQS-35B Gold plated £29.95. 79QS-39B calendar. £29.95. 79CS-51B Calendar. all s/s £39.95

#### LADIES' MODELS with stopwatch or dual time.

87QGL-13B gold plated £24.95. 87QL-13B chrome £16.95. Other ladies' models from £10.95 to £34.95.

Ladies' Alarm Watches. Hourly chimes, calendar LA550 all s/s £24.95, LA551, chrome £19.95 Details on request.

\* Providing the advertiser has stocks and we make a small profit!

CHRISTMAS POST Our return of post service means that orders received by 18th December should reach you in time for Christmas, subject to availability

#### **RETURN OF THE SUPERCALCS!**

★ NEW MODEL! FX-6100

Clock. Hours, minutes, seconds, am/pm.

Alarm. Alarm signal at pre-set time.

Hourty chimes. Every hour, on the hour. Easily switched

vn alarm. (Repeater time).


Stopwards. Normal, nepeater time; Stopwards. Normal, net, and lap times to 1/100 second. Calculator. 39 scientific functions. True algebraic logic. 5 level parenthesis, cube roots, standard deviations, R-P and P-R coordinate conversions, sexagesimal conversions, full

memory, %
Approx. 14 months on 2 penlight batteries (AA type). 34 x

3 x 5%inches. (RRP £22.95). £19.95

FX-7100. Card version of above with kiss-touch keys. 3/16 x 2% x 3%. (£27.95). **£24.95** 

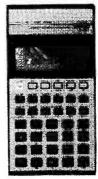**FX-8100.** Specifications as above plus permanently programmed calendar (1976-1999), day, date, month and year. Also has hyperbolics.  $\frac{1}{2}$  x 2 $\frac{3}{2}$  x 5 $\frac{1}{2}$ . £24.95



#### CASIOTONE KEYBOARDS

★ NEW MODEL! CT-301 Domestic Keyboard
Polyphonic playing of 14 instruments plus 16 rhythm voices. Dimensions, etc are similar to the CT-201. Woodgrain only. Provisional price; under £300.

CT-201. 29 polyphonic instruments over 4 octaves, 4-sound memory function. 3 x 331/2 x 9%. Weight 15 lbs. Integral amplifier and speaker. AC only. (£285) **£245** 

#### THE SPACE INVADERS ARE BACK!



This time right in your pocket. An action-packed speed game that will give you hours of skilful entertainment and chair-gripping excitement. Never another dull spare moment. Also an 11-note melody calculator, preprogrammed "When The Saints Go Marching In". Full receipts. Also accept memory, %. Auto power-off facility.


MG-880 (left)

£10.95 (£12.95)

MG-770 (right) Kiss touch

keys. 5/32x3¾x2⅓

£12.95 (F14 95)

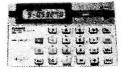

#### 12 PRE-PROGRAMMED MELODIES

Clock, calendar, 11-note melody maker, calculator, square roots, %. Alarm 1; 7 tunes, one for each day. Alarm 2; a fixed tune. Hourly chimes. Date memories; 4 anniversary

MQ-1200 (below). Desk or bedside. Built-in speaker, Volume control. Nightlight. Powered by three AA size batteries. 19/16x 6 x 2¾ inches.

£19.95 100

BEAT lower prices by 5%

M L-90 (right) Kiss keys Stopwatch 7/32 x 2½ x 4½"

£19.95

(£22.95)

Other Casio calculators, P.O.A. Remember, we will



ALARM CHRONOGRAPHS FROM £37.50 SEIKO



£37.50

DFT 048 (left) Alarm, countdown alarm hourly chimes, stopwatch to 1/100 second, net, lap, 1st & 2nd.

DFT 038 100 metre water-resistant ver-

£49.95

DER 048 Solar powered (right). Weekly programmable alarm, 16-hour interval count-down alarm timer, hourly chimes, 1/100 cond stoowatch DER 018 100 metre water-resistant ver-

£69.95



£52.50

DUO DISPLAY Analogue / digital watches from £57.50

Send 25p for our illustrated catalogue of latest Casio and Seiko products. Offers are subject to availability

Price includes VAT and P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAY-CARD number to



Dept. ETI, FREEPOST 164-167 East Road, Cambridge CB1 1DB Tel: 0223 312866

# ETI READER SURVEY

Time for the big one again — our annual nationwide survey of ETI readers. It's your chance to say what you think of us and do your bit to influence what we publish.

All you have to do is fill in the questionnaire overleaf and consign it to its fate at the hands of the Royal Mail. Even now we're preparing for office life to grind to a halt as thousands of questionnaire-laden pigeons start arriving.

Your replies are read and your comments noted. They all go towards shaping ETI in the eighties.

ETI Survey,
Modmags Ltd.,
145 Charing Cross Road,
London WC2H 0EE.

Please rate the following articles on a scale of 1 (awful to 9 (brilliant). If you didn't read the feature, please score 0.

16) Which of ETI's special offers did you purchase in the past year?

	SCORE	SCORE READ	SCANNED	SCANNED COMMENTS?
FM TUNER				
LED TACHO				
MULTI-OPTION SIREN				
POLYSYNTH				
UNIVERSALTIMER				
<b>ELECTRONICS TOMORROW</b>				
I/O INTERFACE				
DESIGNER'S NOTEBOOK				
MICROBASICS				
ASTROLOGUE				
TECH TIPS				
SLR ELECTRONICS				
SPOT DESIGNS				
DIGEST				
AUDIOPHILE				

Asterisk the single best feature in your estimation.

in addition please make any comments you would like to in the space provided. (Go on — don't be shy!)

ISSUE ISSUES

2) Do you consider yourself a regular reader?

Yes/No

If yes - how long?

Six months or less/1 year/2 years/3 years/longer.

If you've been a reader for longer than a year, how does ETI now compare with ETI a year ago? Circle appropriate comment.

Much better Slightly better No different Slightly worse Much worse Oh my God!

How long do you keep your past copies of ETI? 1 month 6 months

4

1 year 6 months

longer

Other (please specify) Advertisement Impulse buy How did you become a reader of ETI? Friend's copy By accident

6) How many people read your copy?

**PROJECTS** 

Have you ever built a project from ET1? If yes which did you construct in the last year — please list

These are personal questions which you may find objectionable. Please feel free to tell us to mind our business in that case. Answering them would help us greatly, however, and your co-operation would be appreciated. All info treated strictly as statistics and in confidence.

Yes/No Yes/No Yes/No (a) Approx. how many times in the last year have you ordered goods from a mail order com-Atrocious 20) Have you ever purchased goods from mail order advertisements in ETI? 19) Do you find the advertisements in ETI useful when purchasing goods? Bad Is there anything you'd like to see appear as an offer in ETI? If yes, please specify 17) Have you ever bought any goods from ETI mail order? If yes how was the service you received? Never Any problems? (Please specify below) 18) Do you read advertisements in ETI? Frequently Occasionally Neither ADVERTISING 21) If so:-

(b) How many mail order companies have you used during that period? 22) Approx. how much have you spent on electronics in the last year?

23) Approx. how much of this amount was spent as a direct result of seeing an advertisement in ET1? AUDIO 24) Do you own a stereo system?

Yes/No 26) Approx. how much do you spend annually on audio equipment? 25) If yes, how much did your present system cost?

28) Do you own or rent a videocassette recorder? 27) Please list your present system VIDEO

Yes/No 29) If not, do you intend owning or renting a VCR within the next year?

Yes/No

Yes/No 劉) Do you own a home computer or microprocessor system? 31) If yes, how much did it cost? HOME COMPUTING

32) Did you buy it through:(a) Recommendation by other/shop
(b) Article in ETI/other magazine
(c) Advertisement in ETI/other magazine.
Delete where not applicable.

Yes/No

READER PROFILE

es/No es/No es/No our in-	9) Is there anything you would especially like to see as a project in ETI?  10) In general, if there is a kit available for a project would you purchase that rather that assembling the components yourself?  11) Do you construct using PCBs?  11) Do you construct using PCBs?  12) In general again, do projects constructed from ETI work first time?  12) In general again, do projects constructed from ETI work first time?  13) Please read the list of topics below and indicate how you think coverage of them measur up in the appropriate box  About right  Rould cover   Total ignored from ETI work first time?  Should cover   Total ignored from ETI work first time?  Should cover   Total ignored from ETI work first time?	in ETI?  ou purchase that rath  lime?  Should cover  more in future		(Male/Female/Undecide al income (if in full time emp ar job title? d any of these credit cards? d any of these credit cards? d Access Americ of Level "A'Level 'O'Level "A'Level ut like about ETI? stions for improvement? stions for improvement? stions for with ETI scorin rscale of 100 with ETI scorin	can Express can Express can Express ication? onc sthe Bad Guys!) ng 50, please rate READ SOMETIMES	HNC if necessary	NEVER
tr would you purchase that rether than 39 What is your job title?  Yes/No Yes/No 37 Do you hold any of these credit cated? Yes/No 39 To you hold any of these credit cated? Yes/No 39 To what level was you in full time selection? ONC HNC Degr Stratume?  Yes/No 39 To what level was you in full time selection?  What do you like about ETI?  40 and dislike?  41 Any suggestions for improvement?  42 Any comments to make? [Please include separate sheet if necessary!]  43 The competition. (Otherwise known as the Bad Guys!)  Any comments to make? [Please include separate sheet if necessary!]  43 The competition. (Otherwise known as the Bad Guys!)  Any comments to make? [Please include separate sheet if necessary!]  43 The competition. (Otherwise known as the Bad Guys!)  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make? [Please include separate sheet if necessary!]  Any comments to make any comme	9) Is there anything you would especially like to see as a project in ETI?  Please specify.  10) In general, if there is a kit available for a project would you purchase that rather that assembling the components yourself?  11) Do you construct using PCBs?  If yes, do you etch your own?  If yes, do you etch your own?  12) In general again, do projects constructed from ETI work first time?  SUBJECTIVE MATTER  13) Please read the list of topics below and indicate how you think coverage of them measur up in the appropriate box  About right Should cover Should cover I Total now ignores in future in future in future in future in forces.	in ETI?  ou purchase that rath  lime?  Should cover  more in future		ar income (if in full time emp r job title? d any of these credit cards? d any of these credit cards? d Access Americ of Level A'Level 'O' Level A'Level 'A' Level 'O' Level A'Level 'A' Level 'O' Level A'Level 'A' Level 'O' Level A'Level 'A' Level 'A' Level '	can Express can Express can Express ication? ONC it be separate shee sthe Bad Guys!) READ SOMETIMES	HNC if necessary	NEVER
treatine of them rether than 36) What is your job title?  Yes/No Yes/No Yes/No Yes/No Sin Do you hold any of these credit cards? Yes/No Sin Do you hold any of these credit cards? Yes/No Sin Do you hold any of these credit cards? Yes/No What do you like about ETI?  40) and dislike?  41) Any auggestions for improvement?  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition (Otherwise known as the Bad Guys!)  43) The competition of 100 with ETI sooring 50, please rise the competition against u Wheten State and	10) In general, if there is a kit available for a project would you purchase that rather the assembling the components yourself?  11) Do you construct using PCBs?  14) Bo you construct using PCBs?  15) In general again, do projects constructed from ETI work first time?  16) Please read the list of topics below and indicate how you think coverage of them measure up in the appropriate box  17) About right  18) Should cover and future in future	ou purchase that rath time?  Should cover more in future		d any of these credit cards? d Access Americ d Access Americ d Were you in full time edu 'O' Level 'Ike about ETI? stions for improvement? stion. (Otherwise known as tition. (Otherwise known as tition. (Otherwise known as tition.)	cation? ONC of separate sheets the Bad Guys!) READ SOMETIMES	HNC tif necessary the competit	n aga
Vea/No Yea/No You think coverage of them measures ow you think coverage of them measures and distilked Year I Totally Yea/No You think coverage of them measures and distilked Year I Totally Yea/No You think coverage of them measures and distilked Year I Totally Yea/No You think coverage of them measures and distilked Year I Totally Yea/No You think coverage of them measures and distilked Year I Totally Yea/No You think coverage of them measures and distilked Year I Totally Yea/No You think coverage of them measures and distilked Year I Totally Yea/No Year I Totally Yea/No Year I Totally Yea/No Yea/No Yea/No Year I Totally Yea/No Yea/No Yea/No Yea/No Yea/No Yea/No Yea/No Yea/No Yea/No No Yea/No No Yea/No No No Yea/No No No Yea/No No No No Yea/No No No No Yea/No No N	11) Do you construct using PCBs?  14) Do you construct using PCBs?  15) In general again, do projects constructed from ETI work first time?  16) Please read the list of topics below and indicate how you think coverage of them measurup in the appropriate box  About right Should cover Total now in future in future ignored.	time?  Ak coverage of them m Should cover more in future		d any of these credit cards?  d Access Americ vel were you in full time edu 'O' Level 'A' Level 'Ike about ETI? like? stions for improvement? stions for improvement? stions (Otherwise known as tition. (Otherwise known as tition.)	can Express ication? ONC de separate shee s the Bad Guys!} ig 50, please rate SOMETIMES	HNC tif necessary	n aga
Work first time?  Yes/No  CSE  O'Loval  Si) To what level were you in full time aducation?  O'Loval  Si) What do you like about ETI?  Ow you think coverage of them measures  40and dislike?  41) Any suggestions for improvement?  42) Any comments to make? [Please include separate sheet if necessary])  43) The competition. (Otherwise knowned separate sheet if necessary)]  ABDIO CONSTRUCTOR  REGULAR  SOMETIMES  On an arbitrary scale of 100 with ETI scoring 80, please rate the competition against u  NIDEO  TELEVISON  VIDEO  COMPUTING  PRACTICAL WIRELESS  PRACTICAL ELECTRONICS  PRACTICAL WIRELESS  PRA	verage of them nuld cover	verage of them nuld cover		rel were you in full time edue 'O' Level 'A' Level 'A' Level 'A' Level 'A' Level like? like? stions for improvement? stions for improvement? stions (Otherwise known as tition. (Otherwise known as scale of 100 with ETI scoring REGULAR	ide separate shee sthe Bad Guys!) READ SOMETIMES	HNC if necessary	n aga
38) What do you think coverage of them measures  40)and dialite?  41) Any suggestions for improvement?  42) Any comments to make? (Please include separate sheet if necessary!)  43) The competition. (Otherwise known as the Bad Guys!)  43) The competition of 100 with ETI scoring 50, please rate the competition against u  ABDIO CONSTRUCTOR  RECULAR  R	SUBJECTIVE MATTER  13) Please read the list of topics below and indicate how you think coverage of them measur up in the appropriate box  About right less in future more in future ignore.	Should cover more in future		like?  stions for improvement?  stions for improvement?  ents to make? (Please includ tition. (Otherwise known as tition. (Otherwise known as	de separate sheels the Bad Guys!) 1950, please rate	t if necessary the competit	On against u
Attocious	SUBJECTIVE MATTER  13) Please read the list of topics below and indicate how you think coverage of them measur  up in the appropriate box  About right Should cover Total  now less in future more in future ignored.	Should cover more in future		stions for improvement? ents to make? (Please includ tition. (Otherwise known as scale of 100 with ETI scorin REGULAR	de separate sheers the Bad Guys!) g 50, please rate READ SOMETIMES	t if necessary	on against u
41) Any suggestions for improvement?  42) Any comments to make? (Please include separate sheet if necessary))  42) Any comments to make? (Please include separate sheet if necessary))  43) The competition. (Otherwise known as the Bad Guys)]  On an arbitrary scale of 100 with ETI scoring 50, please rate the competition against u  REQUIAR  REQUIAR  REQUIAR  REQUIAR  REACTICAL COMPUTING  COMPUTIERS WORLD  TELEVISION  VIDEO  COMPUTIER AGE  PRACTICAL ELECTRONICS  PRACTICAL ELECTRONICS  PRACTICAL ELECTRONICS  PRACTICAL ELECTRONICS  COMPUTIER WORLD  PRACTICAL ELECTRONICS  PRACTICAL ELECTRONICS  COMPUTIER WORLD  PRACTICAL ELECTRONICS  COMPUTIER WORLD  PRACTICAL ELECTRONICS  COMPUTION TO COMPUTI	About right Should cover Should cover now less in future	Should cover more in future		stions for improvement? ents to make? (Please includ tition. (Otherwise known as scale of 100 with ETI scorin REGULAR	de separate shees the Bad Guys!} ng 50, please rate READ SOMETIMES	t if necessary the competit	on against u
43) The competition. (Otherwise known as the Bad Guys!)  On an arbitrary scale of 100 with ETI scoring 60, please rate the competition against u  READ  REGULAR  REGLES  REGULAR  REGULAR  REGULAR  REGULAR  REGULAR  REGULAR  REGUL	PROJECTS		On an arbitrary	tition. (Otherwise known as scale of 100 with ETI scorin	s the Bad Guys!) ng 50, please rate READ SOMETIMES	the competit	on against u
t we can present in ETI. What is your in-  On an arbitrary scale of 100 with ETI scoring 50, please rate the competition against u  REGULAR REGULAR SOMETINE  WINELESS WORLD  TELEVISION  VIDEO  PRACTICAL COMPUTING  COMPUTER AGE  PRACTICAL ELECTRONICS  COMPUTING TODAY  HOBBY ELECTRONICS  COMPUTING TODAY  WHAT VIDEO  FTI  Thank you for your time and patience!  Astrocious  Name			On an arbitrary RADIO CONST	scale of 100 with ETI scorin	ng 50, please rate READ SOMETIMES	the competit	on against u
On an arbitrary scale of 100 with ETI scoring 50, please rate the competition against u  READ READ READ REGULAR SOMETIMES UNIFICAL COMPUTEN  WIRELESS WORLD TELEVISION VIDEO PRACTICAL WIRELESS PRACTICAL W	FEATURES		On an arbitrary	REGULAR	ng 50, please rate	the competit	on against u
REGULAR SOMETIMES USED TO NEVER	HOME COMPUTING		RADIO CONST	REGULAR	READ SOMETIMES	USED TO	NEVER
RADIO CONSTRUCTOR   SOMETIMES   USED TO   NEVER	AUDIO		RADIO CONST		SOMETIMES	USED TO	NEVER
t we can present in ETI. What is your insis should we place on each?  UMBER NOW LET'S HAVE MORE  Yes/No	EQUIPMENT REVIEWS		RADIO CONST	DI CATOLI			
t we can present in ETI. What is your insis should we place on each?  UMBER NOW LET'S HAVE MORE  Ves/No	SPACE FACT			Y			
t we can present in ETI. What is your insis should we place on each?  UMBER NOW LET'S HAVE MORE  Ves/No	SCIENCE FICTION		WIBEI ESC WO	00000			
t we can present in ETI. What is your insis should we place on each?  UMBER NOW LET'S HAVE MORE  Ves/No	GENERAL SCIENCE		WINELESS WO	ארם			
t we can present in ETI. What is your insis should we place on each?  UMBER NOW LET'S HAVE MORE  Ves/No	MILITARY ELECTRONICS		IELEVISION				+
t we can present in ETI. What is your insis should we place on each?  UMBER NOW LET'S HAVE MORE  Ves/No	ANY OTHER (CRECIEV)		VIDEO				+
is should we place on each?  UMBER NOW LET'S HAVE MORE  Yes/No  Atrocious Non-existent			PRACTICAL CC	OMPUTING			
UMBER NOW LET'S HAVE MORE  Ves/No  Atrocious  Non-existent		1000		GE			
UMBER NOW LET'S HAVE MORE	(3) More specifically, there are many types of project we can present in E.I. What is your interest in these examples, and what sort of emphasis should we place on each?	resent in EII. What is e place on each?		IRELESS			
Atrocious Non-existent	WON GEARING TOOL	F	 [	ECTRONICS			
Yes/No Yes/No Atrocious Non-existent		-	T	MPUTER WORLD			
Ves/No Atrocious Non-existent	SOUND EFFECTS		ELEKTOB				
Yes/No Atrocious Non-existent	GAMES		EVERYDAY ELE	CTRONICS			
Yes/No Atrocious Non-existent	MUSIC		COMPUTINGT	ODAY			
Yes/No Atrocious Non-existent	AUDIO		HOBBY ELECTR	RONICS			
Yes/No Atrocious Non-existent	BIOFEEDBACK		VIDEO TODAY				
Yes/No Atrocious Non-existent	MOTORING		WHAT VIDEO				
Yes/No Atrocious Non-existent	COMPUTING		ETI				
Atrocious Non-existent				our time and patiencel			
Atrocious Non-existent			ĸ				
Tibosof and doction and hope to below	Atrocions		Name				
	intered when dealing	an dealing with us below	Address				

	READ			01410
REGULAR	ILAR SOMETIMES	USED TO	NEVER	MALING
RADIO CONSTRUCTOR				
WIRELESS WORLD				
TELEVISION				
VIDEO				
PRACTICAL COMPUTING				
COMPUTER AGE				
PRACTICAL WIRELESS				
PRACTICAL ELECTRONICS				
PERSONAL COMPUTER WORLD				
ВУТЕ				
ELEKTOR				
EVERYDAY ELECTRONICS				
COMPUTING TODAY				
HOBBY ELECTRONICS				
VIDEO TODAY				
WHAT VIDEO				
				2

### SPECIAL OFFERS

#### **TO LAUNCH OUR** MAIL ORDER DEPT.

SEMI CONDUCTORS: 2N2222A 8 for £1,2N6385 50p,2N506115p, EMI CONDUCTORS: 2N.2222A 8 for £1,216368 \$40,218366 113p, BC182 (TO5) 15 for £1, BC212L (TO5) 15 for £1, BC714L (TO5) 15 for £1, BF245 fet 20p, BU208 £1.50, MJE340AT 50p, 741 (8 pin DIL) 8 for £1, 555 5 for £1, 723 Reg. 25p, Dual 741 30p. EXTRA SPECIAL LIMITED OFFERS: 2708 450ns £3.50, 8080A £3, EM4402 (4k Static Ram) £2.

Ram) £2.

RESISTORS: Carbon Film ¼w 5% £3/1000 Our Mix. Metal Oxide ½w 2% £2/Our Mix. Rectangular Presets (W/W and Cermet) 10/£1 Our Mix. Wirewounds 2w, 4w, 6w, 10w, 40/£1 Our Mix.

CAPACITORS: 100 Disc Ceramid (40 values) £1.50, 100 μ f 63 volt Radial 12p each 15/£1, 1μf 100 volt Radial Polyester 20p. Can Electrolytic. 680 μ f 63 volt 25p, 10,000 μ f 25 volt £1, 3300 μ f 63 volt £1, 4700 μ f 63 volt £1.50, 1200 μ f 25 volt 75p. Computer Type, 1000 μ f 160 volt £1.50, 1500 μ f 100 volt £1.50, 1100 μ f 100 volt £1.50, 1100 μ f 25 volt £1.25, 21000 μ f 40 volt £2, 47000 μ f 25 volt £2.

MISC ITEMS: Parks of 9 Slide Switches 50p. 10 Clear Mains Neons £1.

MISC ITEMS: Pack of 9 Slide Switches 50p, 10 Clear Mains Neons £1, 1" Pitch Edge Connectors Double sided 43 way £1, 48 way £1.50, 500R Ten Turn Pots £1, 15 Turn Dials £1.50, 16 way Low Profile i/c Sockets 10/£1, 7 way DIL Switch 80p.

All prices include VAT. Please add 30p P&P. Large S.A.E. for List

#### ELECTRO SUPPLIES

MAIL ORDER DEPT. (Callers please phone first) mess Mill, Shawclough Road sterfoot, Rossendale, Lancs. Waterfoot, Rossens

(Open 6 days) 6A Todd Street (next to Victoria Stn.)

### Happy Memories

£3.45 2114 200ns 4116 200ns £2.95 £7.95 £2.95 2716 5 volt 2114 450ns 2708 450ns £4.75

MEMOREX SOFT-SECTORED MINI-DISCS for PET, TRS-80, etc. Supplied in Free Library Case £19.95 per 10

Low Profile I.C. Sockets by Texas Pins ..... 8 14 16 18 20 22 24 28 40 

Memory Upgrade Kits for Apple, 2020, TRS-80, etc. . . . . . from £30 please phone

Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened.

ALL PRICES INCLUDE V.A.T. POSTAGE FREE ON ORDERS OVER £10, OTHERWISE ADD 30p.

Access and Barclaycard Welcome

**HAPPY MEMORIES** Dept. ETI

Gladestry, Kington Herefordshire HR5 3NY Telephone (054422) 618

Recommended for: Civil

#### AVOID DANGER from RADIATION WITH OUR RADIATION DETECTOR

#### **General Information:**

Pocket dosimeters provide an accurate, reliable and immediate method of measuring the integrated dose of radiation received by those exposed to ionising radiation. The dose may be read at any time and in any place, providing a source of light is available

Principle:

The dosimeter is an ionisation chamber type using a quartr fibre electroscope as the indicating element. A microscope is used to project the image of the moving quartz fibre element on to a graticule scale. The quartz fibre is mounted on a wire electrode, which in turn is supported by a high quality insulator. When the instrument is charged, positive charges distribute themselves over the wire electrode and quartz fibre causing the fibre to bend away from the electrode. The fibre will take up a position depending on the amount of charge on the system.

When the surrounding air in the ionisation chamber is ionised negative ions will be attracted to the positively charged electrode thereby reducing its charge. The resulting fibre movement will be related directly to the quantity of radiation producing the ionisation. The fibre movement can thus be calibrated directly in roentgen units and the rate of movement of the fibre will be proportional to the roentgens received per unit time

#### Construction:

The microscope, electroscope and ionisation chamber are housed in an outer skin which may be of brass or aluminium. At one end of the rubular case is fixed a charging assembly, and at the other an eye-piece window

Each dosinteter is provided with protective end cap translucent window so that the cap need not be removed for reading.

Dosimeters meet vibration drop, salt spray. humidity, water immersion and temperature tests


 BE PREPARED, EVERY HOME SHOULD HAVE ONE

> YOU CAN'T SEE IT **HEAR IT** FEEL IT BUT YOU CAN DETECT IT

> > **WILL READ X-RAY** & GAMMA RADIATION
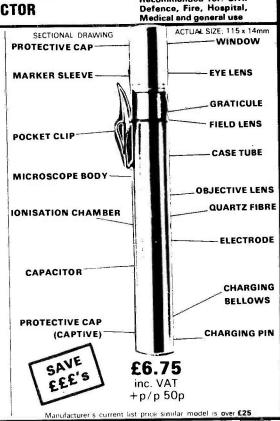
#### Features:

- THESE UNITS WILL READ **AUTOMATICALLY THE AMOUNT OF** RADIATION IN THE AIR
- THIS INSTRUMENT IS ONLY A LITTLE LARGER THAN A FOUNTAIN
- CLIPS ON TO YOUR TOP POCKET
- WEIGHT LESS THAN 3 0Z.
- CONTAINS THREE LENSES
- FULLY CHARGED, TESTED AND **GUARANTEED**
- BRITISH DESIGN AND MANUFAC-TURE, RUGGED CONSTRUCTION
- MANUFACTURER'S LIST PRICE OF SIMILAR MODEL IS OVER £25
- BUY NOW WHILST STOCKS AVAIL-ABLE. DELIVERY BY RETURN POST





#### HENRY'S

**TELEX 262284 REF. 1400 Mail Order Division** 404 Edgware Road, London W2, England I.E.D.



Supplied complete with Data and Information on radiation and detectors.

All units are checked and tested just prior to despatch by first-class mail in proper protective packing.

VIEW THRU LENS



TEKTRONIX STORAGE OSCILLOSCOPE. Type 434, as new. 12 months' warranty £1,950. TEKTRONIX OSCILLOSCOPE. Type 647, with 10A2 and 3B11 £500 TEKTRONIX STORAGE OSCILLOSCOPE. Type 564 with 3A6 and 3B4 £350.
TELEQUIPMENT STORAGE DSCILLOSCOPE, Type DM53A £285.
TELEQUIPMENT OSCILLOSCOPE, Type 032 Portable, mains/ 6275.
HAMBEG OSCILLOSCOPE. Type 512 DB. 50MHZ £350.
TELEQUIPMENT OSCILLOSCOPE. Type S54A SB 10MHZ. £190.
SE LASS OSCILLOSCOPE. Type S54D S100.
ADVANCE OSCILLOSCOPE. Type OS1000 DB 15MHZ. £250.
TEXTRONIX OSCILLOSCOPE. 547 with 1A1 plug-in Duai TB. 50MH
TEXTRONIX OSCILLOSCOPE 547 with 1A1 plug-in Duai TB. 50MH
TEXTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2B67
£300. ADVANCE OSCILLOSCOPE. Type OS1000 DB 15MHZ. £250. TEKTRONIX OSCILLOSCOPE 547 with 141 Juggin Dual TB. 50MHZ. £375. TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2867 10MHZ. £300.
TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2867 10MHZ. £300.
TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2867 10MHZ. £300.
TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2867 10MHZ. £300.
TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2867 10MHZ. £300.
TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2867 10MHZ. £300.
MARCONI FM SIG. GEN. Type TF10668 65. £285.
G. B. E. BRADLEY LTO. R.F. MILLIVOLTMETER. Type 112 £75
ADVANCE A.C. VOLTMETER. Type WM77E £80
MARCONI WAVE ANALYSER. TF2330. Good condition. £150
AVO R.F. SIG. GEN. Model HF135. £75
MARCONI SUDE RANGE R.C. OSCILLATOR. TF1370. £95.
MARCONI SENSITIVE VALVE VOLTMETER. TF2600. £50.
MARCONI SENSITIVE VALVE VOLTMETER. Type 670. £255.
MARCONI SENSITIVE VALVE VOLTMETER. Type 12650. £50.
MARCONI SENSITIVE VALVE VOLTMETER. Type 10MHZ. £150
AIRMEC SIGNAL GENERATOR. Type 204 AM /FM 320MMZ £150
AIRMEC SIGNAL GENERATOR. Type 204 AM /FM 320MMZ £150
AIRMEC SIGNAL GENERATOR. Type 704 AM /FM 320MMZ £150
WAYNE KERR UNIVERSAL BRIDGE. Type 120 B250
MARCONI UNIVERSAL BRIDGE. TYPE 1508 £100
SOLARTRON THUS RMS VOLTMETER. TYPE 1708 ED 1018 £50
BAK AUTOMATIC VIBRATION EXCITER CONTROL. Type 1018 £50
MARCONI UNIVERSAL BRIDGE. TYPE 1750 MT 1019 £50
MARCONI UNIVERSAL BRIDGE. TYPE 1750 £150
MARCONI RBS UMBALANCEU STANDARU ATTENDATUR DUCHM. DN) 0942/00
645
STODDART AIRCRAFT Radio Interference and Field Intensity Meter, type
NM-52A 375-1000MHz (2 pieces) 6235
MARCONI SIGNAL GENERATOR. Type TR8018 685
RBS DIRECT CAPACITANCE METER (S0
BBK HETERODYNE VOLTMETER (RECEIVER) Type 2005 6250
MARCONI VARIABLE ATTENDATOR. TF(1)73A/2S 640
MARCONI DOUBLE PULSE GENERATOR. Type TF1400/S 650
RADIOMETER (COPENHAGEN) WAVE ANALYSER. Type FRA 2CT3a 680

SOLARTRON DIGITAL VOLTMETER. Type LM1867 £75
HEWLETT PACKARD DIGITAL RECORDER. Type 50508 £50
HATFIELD PSOPHOMETER. Type DRG 657167A £50
AOVANCE DUAL STABILISED D.C. SUPPLY PP3., 0-30V 1A £25
MARCONI COUNTER FREQUENCY METER TF1417/2 with 10-500MHZ
Countery LF2400 The Pair £60. Convenor TF2400. The Pair £50.

PORTURE MONITOR MODEL PM-52T (5in screen) As new £55

HEWLETT PACKARD POWER SUPPLY 6214A. 0-12V, 0-1.2A, new, boxed. 485.

M.P. TRIPLE OUTPUT POWER SUPPLY 6236A, 0-6V, 0-2.5A/0-20V, 0-0.5A, new boxed £175.

M.P. OC. POWER SUPPLY 62098, 0-320V, 0-0.1A, new boxed, £140.

T.O.A. ELECTRONICS LTD Electronic Polyrecorder EPR.2T Mains £120.

THE JAMES KING COMPANY FS-1100T FREGUENCY STANDARD £50.

MARCONI CARRIER DEVIATION METER. Type 1593 D £50.

SOLARTRON PULSE GENERATOR. Type 6107 D £100.

MI SANDERS LEVELLING AMPLIFIER. Type 6587 £175.

SCOPEX OSCILLOSCOPE. Type 4010 D8 10MHZ £170.

ADVANCE OSCILLOSCOPE. Type 4010 D8 10MHZ £175.

COSSON OSCILLOSCOPE. Type 105240 D8 10MHZ £175.

COSSON OSCILLOSCOPE. Type 6501 D8 10MHZ £175.

COSSON OSCILLOSCOPE. Type 1051 D8 10MHZ £175.

TELEQUIPMENT OSCILLOSCOPE. Type 108 10 MHZ £170.

TELEQUIPMENT OSCILLOSCOPE. TYPE 100 10 MHZ £170.

TELEQUIPMENT OSCILLOSCOPE. TYPE 100 11 MHZ £170.

TELEQUIPMENT OSCILLOSCOPE. TYPE 100 H.P. TRIPLE OUTPUT POWER SUPPLY 6236A, 0-6V, 0-2.5A/0-20V,

HEWLETT PACKARD DISPLAY 143A with 1424A Sampling Timebase and 1411A Sampling Vertical Amplifier. Up to 4GHZ Large Display. £350. H.P. MEMORY DISPLAY 5480B with 5486A Control TB and 5488A Y 1411A Sampling Vertical Amplifier. Up to 4GHZ Large Display. 2550.

H.P. MEMORY DISPLAY 5480B with 5486A Control TB and 5488A Y System. £275

System. £275

New Memory Display 5480A with 5486A Control TB and 5485A two channel input. £225.

R\$5. UP TEST RECEIVER 0.9-2.7GHZ 8N1524 £150

EDDVSTONE RECEIVER. Type 990S 250-850MHZ. £450

R\$5. UHF TEST RECEIVER. BN1523 280-940 MHZ. £450

R\$5. UHF TEST RECEIVER. BN1523 280-940 MHZ. £120

R\$6. UHF STS TRECEIVER. BN1523 280-940 MHZ. £120

R\$7. UP TEST RECEIVER. BN1523 280-940 MHZ. £120

R\$6. UHF STS TRECEIVER. BN1521 SUPEC. Type 15818 £175

MARCONI YELL STS TREST NO IC. £100

DAVE AF ANALYSER. Type 1461A. £30

DAWE AF ANALYSER. Type 1461A. £30

DAWE AF ANALYSER. Type 1461A. £30

DAWE AF ANALYSER. Type 1461A. £30

GERROLD SWEEP FREQUENCY GENERATOR. Model 602 £40

TELONIC SWEEP FREQUENCY GENERATOR. Type 5090. Case damaged hence £50

MARCONI VALVE VOLTMETER. Type 171300. £15

SOLARTRON DIGITAL VOLTMETER. Type 11420.2. £30

VIOEO CIRCUITS LTD TUBE TESTER. Type V33. £30

LABGAR COLOUMMATCH £35 PATTERN GENERATOR. Type CM6004-F6

R\$ & LAIND SEED HERVY CONCENTERN EMERATOR. Type CM6004-F6

R\$ & LAIND SEED HERVY CONCENTS TO THE \$100 MS TANALY SEED TO THE SET SEED TO THE TYPE TO THE SET SEED PG, E30

B & K BEAT FREQUENCY OSCILLATOR. Type 1014. £175

B & K AUDIO FREQUENCY SPECTROMETER. Type 2112. £225

ADVANCE OSCILLOSCOPE. Type OS1000A. DB 20MHZ. £300

#### JUST IN TORODIAI TRANSFORMER

INAUSE OTIVE IN 1915 I

TANTALUM CAPACITORS — all at 10p each 22mfd 6V; 39mfd 10V; 22mfd 35V; 1mfd 35V.

#### **TANDY TRS 80**

IANUT INS 6U
Level 2 Microprocessor System comprising
of Display. Keyboard with processor and
16K memory; Expansion Interface with 32K
additional memory; two Floppy Disk Drives;
Tandy Printer; manuals, books, disks, etc—
including Updated DOS Disks. Hardly used.
EXCEPTIONAL CONDITION. Will separate

**THE LOT £1,600** 

#### **INFRA RED IMAGE CONVERTER Type 9606** (CV 144)

1 % in diameter. Requires single low current 3KV to 6KV supply individually boxed. With

£12.50 each Infra Red Lamps also advertised

#### **GARRARD DIRECT DRIVE TURNTABLE MOTORS**

Made in Japan. With internal electronic speed control. 24 volt. Connections sup-

£3.50 each, P&P £1.50

#### **EX-MINISTRY SOLID** STATE **400 HZ INVERTOR**

28 VDC input. 115V output. Size 7 x 2½ x 15in approx. Connection details supplied. £18 each. P&P £2

#### TRANSISTOR INVERTOR

115V AC 1.7 Amp Input. Switching is at 20Khz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied. £1.25 each. P&P £2

#### CONVERT THIS UNIT TO A

#### **SUPER BATTERY CHARGER**

Attractive green ministry quality case with removable top and bottom plates - heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for £3.50. P&P £2. Four units £12. Carriage £5

#### STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts. 12/24 recommended. £1.50 each P&P-75p or 5 for £5 P&P £1.50.

#### STEPPING MOTORS

200 Steps. 20 oz/in. torque, 12/24 vi £12 each. P&P £1.50 volt input 4-wire

KEYBOARD PAD
'' high with 12 Alma Reed Switches Blue Size 3x21/2x2 keys marked in green 0-9 and a star with one blank £4 each, P&P £1, or 5 for £15 P&P £2.

#### MINIATURE KEYBOARD

ts, marked 0-9 and A-F and 3 optional function keys. £1.75 each. Push conta

CRYSTALS Flat metal cas

TALS 50p ea stal case — 19.2KHZ; 844.8KHZ; B7G — 10MHZ.

LOUDHAILERS. Transistorised hand-held. no leads. Standard internal batteries supplied. How! Switch. £20 ea. P&P £2 IMFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 13½" × ½" dia. £1.50 ea. 240V 1650 Watts. Size 22¾" x ½" dia. £3

BRIDGE RECTIFIER. 2 Amp 50p ss.
PHOTODIODE DETECTOR 4" fly leads, 25p ss.
AMPHENOL. 17-way chassis mount edge connectors 0.1
spacing, 15p ss.
I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre

I.E.C. Standard MAINS LEAD. Moulded (3 vertical that pins centre offset) 60p es.
FANS. 115V 13 Watts. Size  $3/4 \times 3/4 \times 1/5$ " BRAND NEW.
£4.60 es. Secondhard £2.50 es.
DELAY LINE: 50 nanosecs. 3 connections — ground-in-out Size 2 × 7/16 ×5/16" New 25p es.
Ministure MOTORS 12V with geered wheel (8 teeth 3/16" die).
Size 1/4 × ½" dis. New 30p es.
MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New £1 es.

Control. New £1 ea.

LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly,

**SOME TEKTRONIX 500** range oscilloscopes

ngle Trace Plug-ins. Working. From £100. Phone for details

DIODES All new full spec. devices IN3063 BAX 13. 1S44, 1N4148; 1N3470; 1N4151.

100 off £1.50, 1,000 off £10

DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New 10p se. 100 for £7.50 Puls E TRANSFORMER. Sub min. Size ½ x 57.16 x ½". Secondary centre tapped. New 20p se. MOTOR by Infland Motor Corp. DC High Torque. Reversible. Usable torque at 5V. Max voltage 24V £2.50 se. P&P £2. REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus £1 sext. REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus, £1 each.

DON'T TAKE CHANCES. Use the proper EHT CABLE, 10p per metre or £7.50 per 100 metre /drum, P&P £2.

PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap 75p ea. Box of 12 £5.50, P&P £1.50.

RAPID DISCHARGE capacitors Bmid 4kV £5 each. P&P £2.

WYSTERY IC PACK. Some 40 pin — good mixture — all new devices. 25 ICs for £1. P&P 50p.

VACUUM PUMPS — TRAPS, £TC. Send for Irst.

DECOUPLING CAPACITORS

0.05mld 10V; 0.01 mfd; 0.047mld 250V, 33K, 330pf. All values. 100 for £1.50.

EHT. Canacitor 500df 8KV 20n each.

D.Obm61 10V; 0.01md; 0.04 /mid 250V; 33K, 330pf. All values 100 for €1.50.

E.H.T. Capacitor 500pf 8KV 20p sech.

E.H.T. Capacitor 500pf 8KV 20p sech.

Oway MULTI COLDUR R18B0N CABLE. New 40p per metra. 10 metres for £3.

GEC UHF 4 button tuner £1.50 each.

CENTAUR 115V FANS 4½ × 4 × 1½" £4.50 ea.

EX-USED equipment, tested, 50p sech.

CONTACTORS. Heavy Duty 24V DC 5 make £1 sach.

GEC UHF/VHF 6-button tuner £2 each.

GEC UHF/VHF 6-button tuner £2 each.

DIGITAL 24-HOUR CLOCK with built-in alarm as used in Braun Digital clocks. Silent running, large illuminated numerals. AC mains. Size 5½ × 2½ × 2½". ONLY £3.78 each.

B31A PHOTO MULTIPLIER £2 each. R8P £1

RANCO 250V 18A THERMOSTATS with Control knobs calbrated 55-200 degree €2.50 each.

SOLID STATE UHF TUNERS. 30 acs £1 each.

SALDER CONTROL 500K Log. Single track. Complete with knob. Length 3½". 25p each.

TRAMSFORMERS.

knob. Length 31/2". 2 TRANSFORMERS TRAMBÉRMERS .

AUTO 240V input .15 V. 1 Amp output £1.25 asch. P&P £1.25.

240V input. Soc. 6V. 1.86A. Size 2½ × 2 × 2". Good quality £1.50 as. P&P £1.

240V input boc. 12V 0.92A. Size 2½ × 2 × 2". Good quality. £1.50 as. P&P £1.

240V input 12V 100MA. Size 60 × 40 × 42mm. 50p asch.

240V input .30c. 12V-0.12V 50MA. Size 53 × 45 × 40mm. £1.

240V input. Soc. 12-0.12V 50MA. Size 53 × 45 × 40mm. £1.

115V input. Soc. 5V 250MA. Size 1 11/6 × 1.5 × 1%" 2 for 115V input. Sec 10-0-10V 1A Size 2½ × 2 × 2", 2 for £1.50, SEMICONDUCTORS 1N4005 - 5p; 1N4002 - 3p.

SEMICURDUCTORS 1N4005 - 5g; 1N4002 - 3p.
At 5p each:
8C147, BC148B, BC157, BC15B, BC237, BF197, OA90, OA81,
BA154, BA243.

At 25p seech:
TP91, TP41A, 2N5E96, AF139, 2TX341
BY127 10p. BF181 20p; BD239 40p; BD241 40p; MA343AT
40p; BD228 50p; BD233 8 BD234 Comp Pair 25W — 80p per

pr. at 50p sech. REGULATOR TBA625 8to 20V in — 5V out 100MA T05 Con. 50p sech BF256C 20p. TV AMPLIFIER TBA 120 20p sech.

Integrate	d Circuits				
7453	5p	74H74	12p	75325	£1
7451	5p	74H51	7p	SN15862	40
7402	12p	74538	10p	MC4028	69p
7476	20p	74502	12p	7417	140
7495	35p	74154	70p	7441	40p
74122	12p	74C02	16p	74C86	50p
74C00	17p	74C04	18p	74C161	24p
		74C74	180		

MOTOROLA DUAL in Line 6 pin Opto Coupler 30p each. Gold

MOTORULA BUAL In Line or prince countries.

EPROMS 2708 £5.50 each.

EPROMS 2708 £5.50 each.

SMITHS encepsulated transistorised AUDIBLE WARNING DEVICES 4V-12V Can be driven from TTL \$5p each.

ELECTROSTATIC VOLTMETER, 7 5KV £8. ea. P&P £1 50. Other ranges available — please enquire.

TRIMMERS: Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. All an each.

at 6p each.
HONEYWELL humidity controllers 50p each.
THYRISTOR TIMER. Solid State. 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay 50p each.
MINIATURE PC MOUNT SLIDE SWITCH. Single pole 3-way

10p each.
4 D1G17 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits Good brilliance at 1.5V. 15 connections 22.80 each. Some E.H.T. Transformers and Capacitors available. Please

Enquire
TELEPHONES 706 style black: grey or blue £5.50 ea; 746 style
black or grey £7.50. Older style black £2.50 each, Discoloured
grey 706 £4 ea P&P £1.50 per telephone.
DC \$ERVO MOTOR 110V 2.5Amp continuous. Oouble shaft.
Brand new. 4 wire. 4 brush £25 ea. Plus carriage.
PC Mount POTS. Wire wound with knob 200 ohm & 100hm. 10p

MIN. RELAY 24V. 2 pole c/o. Brand new. 75p each.
TIME DELAY RELAY 0.1 to 10 secs. 115V AC. DPDT. £5 each.
CAPACITORS at 5p each. 0.1ut 400V. Small rec. block PC
Wount German class; 3300pt; 220n(250V. 0.01 m/d 150V.
INSERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brend new wrapped 75p each. or 10 for £6.

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or 500 ohm. Tested. £25 each or 5 for £100.

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1 — where P&P not stated please use own discretion — excess refunded. £5 CARRIAGE ON ALL UNITS. P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

NORWOOD ROAD, READING

**TELEPHONE NO. READING 669656** 

(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel"



The heart of this unusual FM stereo tuner project is a ready-built type 7254 tuner module available from Ambit International. This module has built-in varicap diodes and is tuned by an externally applied DC voltage. It requires a mere handful of external components, plus a regulated 12 V power supply, to make a ready-to-run tuner unit with switch selection of muting, AFC and mono/stereo functioning. The audio output of the module (about 200 mV RMS) can be fed directly to the input of any stereo audio preamp.

#### Construction


We strongly recommend that you build up the individual units of this project one at a time and interconnect and test them on the open bench before fitting the full set of modules (with or without the optional 'extras') into the final case. Start off by building the power supply unit and check that a stable 12 V is available at the output of IC1.

Next, refer to the basic wiring and interconnection diagram and temporarily wire up the 7254 module as shown,
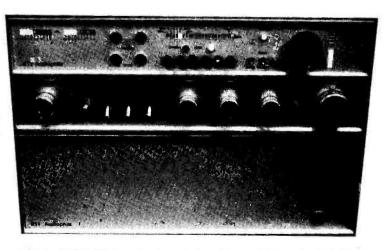
#### **Spot the Tune**

In our Audiophile tuner unit we've provided the basic 7254 module with switch-selected tuning either with one of four preset pots for fixed station selection, or with a 10-turn pot for normal manual tuning. As an optional extra, you can also tune with a special search-and-lock circuit which automatically locates and locks on to strong FM broadcast stations. This circuit is provided with 'search' buttons that can be used to rapidly find the approximate location of a wanted station or reject an unwanted station.

We've designed our FM tuner to cover the 87.5 MHz to 104.5 MHz frequency range, with tuning indication provided on a linear 20-LED frequency scale. We've also provided the unit with a 10-LED signal-strength meter and with an optional stereo audio level indicator with 10 LEDs on each channel. The completed 'full option' unit is exceptionally attractive, with lots of fixed and moving lights, and gives a very impressive performance in the automatic 'search-and-lock' mode.



The Audiophile FM Tuner has been designed to match the Audiophile 4000 preamp and power amplifier (featured in ETI October 1979).

connecting the following components in place: R1, R2, R3, LED 1, SW1, SW2, SW3, SW4, PR1 to PR4, RV1, R4, R5. Note that on our prototype unit we used six interlocking push buttons (including one for the 'automatic' tuning mode) to make SW4 and mounted them on their own PCB, together with multi-turn preset pots PR1-4. Connect the unit to the 12 V power supply, connect an antenna (a few feet of wire should be adequate) and connect the audio outputs of the module to a preamp/power amplifier combination.

Switch the unit on, turn SW4 to position five (manual tuning), SW1 (muting) on, SW2 (AFC) off, SW3 (mono/stereo) to mono and check that the unit can be tuned with RV1. Check that interstation noise is suppressed to a reasonable level when mute switch SW1 is on. If necessary, trim the 100k pot on the 7254 module to obtain satisfactory muting. Check that the unit is functional in the four preset positions of SW4. Finally switch SW3 to the stereo mode and check that LED 1 turns on when a stereo station is tuned in and that stereo noise is not excessive. If necessary, trim the 10k pot on the 7254 to obtain the

correct stereo operation.


Now make up the 20-LED frequency scale on PCB 'A'. Note that this board uses square LEDs, mounted horizontally. Fit the LEDs in place with great care, ensuring that their front faces are all in line and overhang the edge of the PCB by the thickness of the front panel of your proposed tuner case. When construction is complete, make the connections to the power supply and to pin 1 of the 7254 module. Switch on and adjust PR2 to set 1V75 between point 'A' and ground. Check that the frequency scale can be fully scanned via RV1 in the manual tuning mode, noting that the PCB is fitted upside down in the final tuner case, so that the display moves to he right with increasing tuning voltage and frequency.

#### Signal Strength Meter

Next, build up the optional LED signal strength meter on PCB 'C', noting that R39 is mounted on the underside of the PCB and that square LEDs are again used. In this instance the LEDs are mounted vertically on the PCB and special care must be taken to establish the LED heights, as follows. Make a mock-up of the signal strength meter section of your final front panel, complete with a cut-out for the 10-LED display, temporarily fit the PCB in its final 'fixed' position behind the front panel, push the two end LEDs into position on the PCB with their faces flush with the front of the panel and then solder into place. Now fix the remaining eight LEDs in place, using a straight edge across the two end LEDs to give the correct height adjustment. When construction is complete, connect the unit to the power supply and to the 7254 module, scan the band in the manual mode and adjust PR3 so that the lowest signal strength LED is barely on with the weakest of input signals; you'll find that only the lowest three to seven LEDs illuminate under most signal conditions.
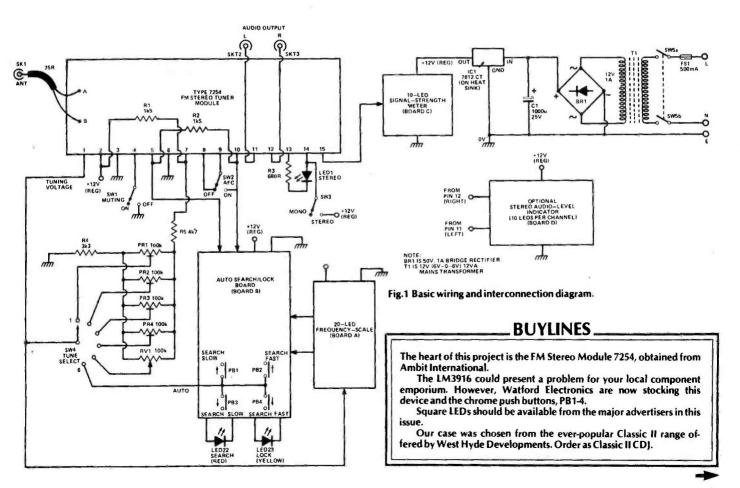
#### **Auto Search And Lock**

The search and lock circuit is an optional 'extra' and requires some care in setting up. Construct the PCB as shown in the overlay, taking care to use good quality (low leakage) tantalum components in the C7 position. Temporarily remove the link from the completed PCB, connect the board into the tuner circuit, TURN THE AFC OFF (SW2), turn SW4 to auto position and switch the unit on. Check that the frequency scale can be scanned up and down using the fast and slow search buttons (PB1-4) and that a selected station remains in tune for a



reasonable time (at least a minute) when the buttons are released. If all is well, insert the link on the PCB.

Switch SW4 to the manual tuning position, tune upwards (with RV1) towards a reasonably strong station and very carefully adjust PR2 so that the search LED (LED 22) is normally on, but turns off and switches lock LED 23 on just as the signal strength indicator goes past its peak reading position. Repeat the action several times, checking that the lock LED acts as an effective 'optimum tuning' indicator.

Now switch SW4 to the auto tuning position, drive the tuning scale fully to the left with the PB4 fast left button and then release PB4. The circuit will now start slowly scanning up the band (to the right), looking for a strong station. When a suitable station is located, the circuit will scan fractionally past the peak signal strength position and then lock on, driving on LED 23. The search LED will subsequently give an occasional flash as a correction pulse is generated to maintain correct tuning. If necessary, trim PR2 very slightly to obtain the same action.



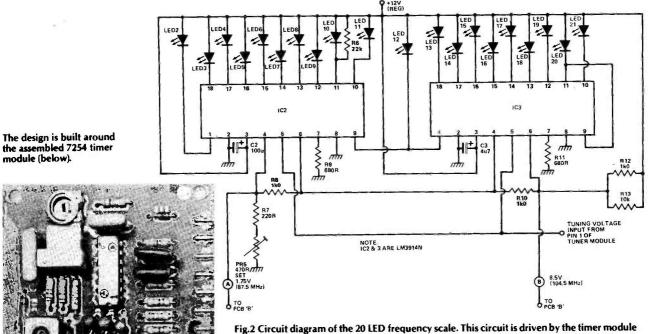


Fig.2 Circuit diagram of the 20 LED frequency scale. This circuit is driven by the timer module (with its ancillary components) and so the component numbering follows on from the module.

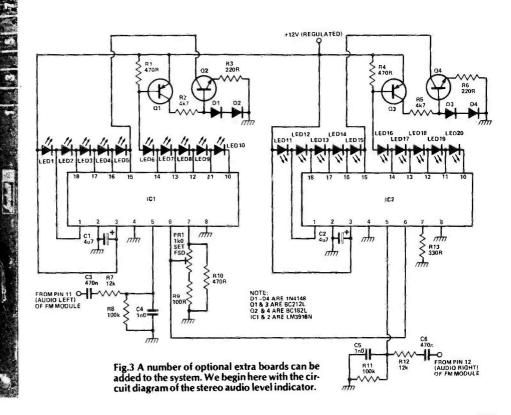

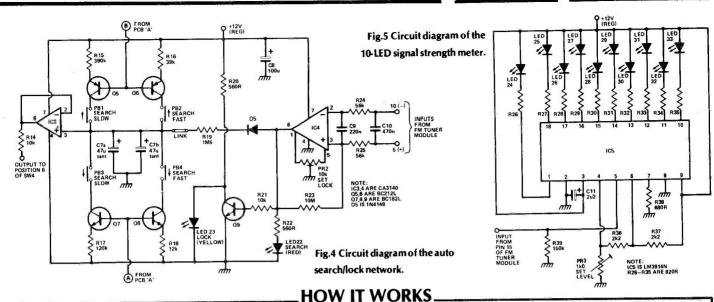

The heart of the ETI Audiophile FM Tuner is a ready-built type 7254 FM stereo tuner module with built-in varicap diodes, designed to be tuned with an external DC voltage applied to pin 1. In our application this tuning voltage can be derived from the 12 V regulated power supply line via the R1-R5-PR1-to-PR4-RV1-R4 potential divider or via an auto search-and-lock board. In either case, we use a 20-LED 'voltmeter' circuit to monitor the pin 1 voltage and to thus act as an effective frequency or tuning scale.

The 7254 tuner module has a number of useful output pins. Pin 7 includes an AFC voltage which can be used (via the tuning potential divider) to hold stations on-tune. A voltage proportional to the tuned signal strength is generated at pin 15 and is used in our circuit to drive a 10-LED indicating meter. Tuning meter 'nulling' signals are generated between pins 5 and 10 and are used in our application to control an automatic search-and-lock circuit. Decoded stereo output signals are available at pins 11 and 12 and can be used to drive an optional stereo audio-level indicator as well as for feeding audio signals to an external preamp power amplifier combination. The 20-LED frequency scale is simply an expanded scale LED voltmeter circuit designed around two series-connected LM3914 bargraph ICs operated in the 'dot' mode. The lower and upper limits of the voltmeter scale are determined by fixed reference voltages fed to pin 4 of IC2 (1V75) and pin 6 of IC3 (8V5) respectively via the PR6-R7-R8-R10-R12-R13 potential divider. The input to the voltmeter is fed to pin 5 of the two ICs from the pin 1 tuning voltage of the FM tuner module. This voltage is directly proportional to the tuned frequency, so the voltmeter acts as an effective tuning

The 10-LED signal strength meter is also an expanded scale LED voltmeter designed around an LM3914 bargraph IC, but in this case the IC is operated in the 'bar' mode. The lower and upper limits of the voltmeter scale are determined by fixed reference voltages fed to pins 4 and 6 respectively of the IC. The input voltage to the meter is derived from the pin 15 'signal-strength' output of the FM tuner module.

The stereo audio-level indicators take the form of a pair of virtually identical 10-LED voltmeters with semi-log scales. Each voltmeter is designed around an LM3916 bargraph IC, a VU-scaled version of the LM3914. The full-scale sensitivity of the meters is set at a few hundred millivolts peak (to suit individual tastes) by preset PR1 and audio inputs are fed to pin 5 of each IC from the outputs of the 7254 tuner module via a simple filter network. The audio signals are AC-coupled and the meters respond to the positive halves of the waveform only.

The LEDs are connected to the LM3916 ICs in a most unusual manner in this particular application. The actual ICs are operated in the 'dot' mode, with only one output being low at any moment of time, but the LEDs are connected to each IC in two series-connected groups of five and produce a 'bar' form of display. The purpose of this configuration is to provide current conservation. In a normal 'bar' display, if all 10 LEDs are on and each LED consumes 10 mA, the total current consumption is 100 mA. In the configuration shown in the diagram the currents of each group of five LEDs pass through the series-connected LEDs, so that the circuit consumes a total of only 20 mA when all 10 LEDs are on and consuming 10 mA each.

To understand the operation of the circuit, let's take the example of IC1, remembering that only one output pin can be low at any moment. If pin 1 is driven low by an audio output signal, LED 1 goes on and draws (say) 10 mA from the supply. If pin 18 goes low, series-

connected LEDs 1 and 2 both go on and each passes the same 10 mA of current. Similarly, if pin 15 goes low, series-connected LEDs 1-5 all go on and each passes the total of 10 mA that flows into pin 15 of the IC. If pin 14 goes low only LED 6 is turned on by the IC and passes 10 mA into the chip. This current flows via R1 and Q1 base, however, so Q1 conducts and turns on constant-current generator Q2, which, in turn, draws 20 mA (say) through the whole of the series-connected LED 1 to LED 5 'bar'; six LEDs are thus driven on under this condition and the circuit consumes a total of 20 mA. Similarly, if pin 10 goes low the whole LED 6 to LED 10 'bar' is driven on by the chip and the LED 1 to LED 5 'bar' is driven on by the constant-current generator, so all 10 LEDs are on and the circuit consumes a total of only 20 mA.

The search circuit is quite simple. To understand its operation, assume that the link is broken. Capacitor(s) C7 is a low-leakage tantalum type and is used to store a tuning voltage that can be fed to pin 1 of the 7254 tuner module via the IC3 high-impedance unity-gain buffer amplifier and via SW4. Transistors Q5 to Q8 are all wired as low-level constant-current generators and can be used to charge or discharge C7 via 'search' buttons PB1 to PB4 and thus scan the frequency band of the tuner module. When the buttons are released, C7 tries to store the tuning voltage, but in practice the voltage slowly leaks away via the capacitor imperfections and the operating frequency of the tuner very slowly decays downwards. The 'lock' section of the circuit is driven from the pin 5 and pin 10 outputs of the 7254 module. These pins are intended to drive an analogue tuning meter. If you connect a sensitive volt or current meter between these pins in the polarity shown (it is recommended that you do so to check circuit operation) you'll find that the meter will normally give a positive reading, but that the reading will null or go slightly negative when the 7254 module is precisely tuned to a reasonably strong broadcast station. In our circuit, the pin 5 and 10 outputs of the tuner module are fed to voltage comparator IC4 via a simple filter network in such a way that the IC4 output goes high when a station is not present or is off-tune, but switches low when a reasonably strong station is correctly tuned. Thus, when a station is not present the high output of IC4 slowly charges C7 via R19 and D5 and causes the 7254 tuning voltage to slowly increase as the module 'searches' for a station. Under this condition search LED 22 is driven on via R22. Q9 is also driven on via R21 and turns lock LED 23 off. When a reasonably powerful station is located and correctly tuned the output of IC4 switches low, so C7 is no longer charged via R19. D5 is back-biased under this condition, so C7 does not discharge back into IC4. Simultaneously, LED 22 and Q9 are disabled and lock LED 23 is driven on via R20. Once a station is 'locked' in this manner, C7 very slowly discharges via leakage currents, so the tuning voltage slowly decreases. As soon as a station goes fractionally off-tune, however, the IC4 output switches momentarily high and generates a brief 'correction' or 're-charge' pulse which brings the C7 tuning voltage back up to the correct value. This action is indicated by a brief flash of LED 22.

Note in the IC4 comparator circuit that a small amount of hysteresis is provided by R23. Also note that the trip point of IC4 can be varied over a narrow range with PR2, to compensate for slight offsets in the pin 5 to 10 outputs of the 7254 module and allow correct locking to be obtained. If a circuit fails to lock correctly, it may be that the offset of these outputs is excessive. This effect may be overcome by wiring a shunt resistor (value determined by experiment) between the relevant pins of the tuner module.

-


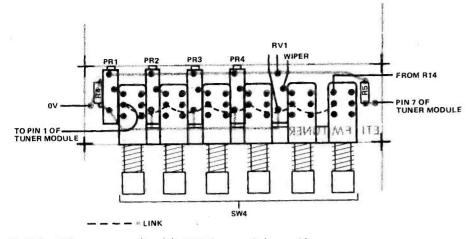


Fig.6 (above) Component overlay of the SW4 six-way switch assembly.

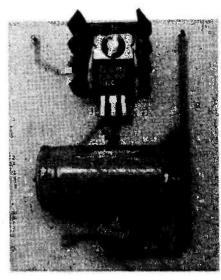

The power supply board — couldn't be simpler.

## ANGLÉ BRACKET PCB

Fig.7 (above) Component overlay of the LED tuning scale.

## +12V 12V AC Ø/P

Fig.8 (above) Component overlay of the PSU. And this is how the whole jigsaw goes together (below).

#### PARTS LIST.

and Tuning Scale
¼ W 5%
1k5
680R
3k3
4k7
22k
220R
1k0
10k

**Potentiometers** 

PR1-4 PR5 100k 3/4 in. 20-turn cermet preset 470R miniature horizontal preset

100k 10 turn linear RV1

Capacitors

1000u 25 V electrolytic 100u 16 V electrolytic PCB type 4u7 35 V tantalum C1 C2 **C3** 

Semiconductors

7812 IC1 LM3914N IC2,3 50 V 1A bridge rectifier TIL209 BR1

LED 1 square LEDs (yellow) **LED 2-21** 


Miscellaneous

6-0-6 12 VA transformer SW1-3

SPDT miniature toggle 2 pole changover interlocking push button (6-way SW4

assembly)

SW5 DPDT miniature toggle (optional)
7254 FM module (see Buylines), PCB 'A', fuse and holder, phono sockets (X2).

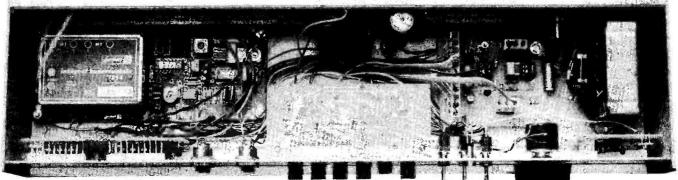

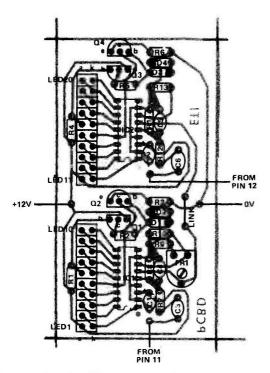


Fig.9 Component overlay of the stereo audio level indicator.

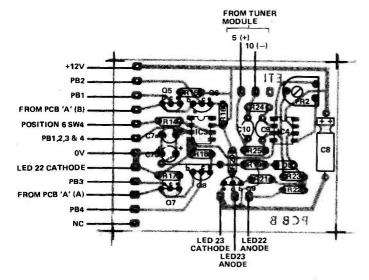


Fig.10 Component overlay of the auto search-lock network.


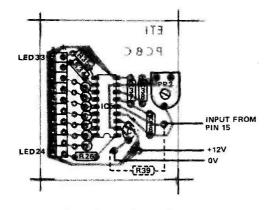


Fig.11 Component overlay of the signal strength meter.

Stereo audio leve	lindicator
Resistors all 1/4 W	504
R1,4,10	470R
R2,5	4k7
R3,6	220R
R7,12	12k
R8,11	100k
R9	100R
R13	330R
Potentiometers PR1	1k0 miniature horizontal preset
Capacitors	
C1,2	4u7 35 V tantalum
C3,6	470n polycarbonate
C4,5	1n0 polycarbonate
Semiconductors	
IC1,2	LM3916N (see Buylines)
Q1,3	BC212L
Q2,4	BC182L
D1-D4	1N4148
LED 1-20	square LEDs (red)
Miscellaneous PCB 'D'	
Auto search/lock	
Danista all 1/14/	EQ
Resistors all ¼W	
R14,21	10k
R15	390k
R16	39k
R17	120k
R18	12k
R19	1M5
R20,22	560R
R23 R24,25	10M 56k
Potentiometers PR2	10k miniature horizontal preset
_	
Capacitors	49 46 3/4
C7a,b	47u 16 V tantalum
C8	100u 25 V electrolytic
C9 C10	220n polycarbonate 470n polycarbonate
Semiconductors	
IC3,4	CA3140
Q5,6	BC212L
Q7,8,9	BC182L
D5	1N4148
LED 22,23	T1L209
Miscellaneous	
PB1-4 PCB 'B'.	momentary push buttons (see Buylines)
Signal Strength M	eter
Resistors all 1/4 W	5%
R26-35	820R
36,37	2k2
R38	680R
R39	150k
Potentiometers PR3	1k0 miniature horizontal preset
Capacitors	2.025.14
C11	2u2 35 V tantalum
Semiconductors C5	LM3914N
C5	LM3914N
Semiconductors IC5 LED 24-33 Miscellaneous	LM3914N square LEDs (green)

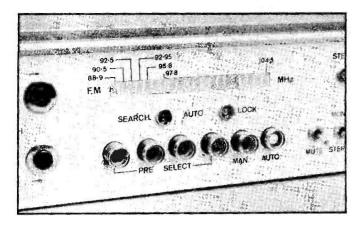

The tuning scale is mounted above the switch assembly, which takes care of manual and auto timing. The search and lock indicators can also be seen.

When using the auto search-and-lock facility, note that the circuit always scans (searches) to the right and will only fully lock on to signals of reasonable strength (it may temporarily lock to weak signals). To rapidly locate a required station, the search buttons may be used to set the tuning scale slightly to the left of the known position. The search buttons can also be used to unlock from an unwanted station. Also note that the AFC facility must be turned off when the auto search-and-lock circuit is in use.

#### **Stereo Audio Level Indicator**

The stereo audio level indicator is an optional item and gives an attractive visual indication of the tuner's audio output signals. The circuit is built on PCB 'D' and uses 10 square LEDs on each channel. These LEDs are mounted vertically on the PCB, their heights being adjusted in the same way as for the signal strength indicator board. When construction is complete, wire the unit into place (connect its 0 V rail directly to the power supply common terminal) and give the unit a functional check. PR1 (on PCB 'D') is simply adjusted so that the display does not run off the scale when strong peak audio signals are present.

#### **Casing The Tuner**

When all of the modules have been fully tested on the open bench they can be fitted together in a suitable cabinet, noting that all supply connections must be taken directly to the power supply module (to avoid hum loops, etc.). If you decide to use the 'Classic II' case that we have used in our prototype, note the following constructional points.

The 'Classic II' case is provided with PCB mounting slots and these are used to hold the power supply and the signal strength and audio level boards in place. The basic 7254 tuner module, the SW4 PCB, the search-and-lock board (PCB 'B') and mains transformer T1 are all mounted on the case baseplate with '4' inch stand-off pillars. The tuning scale (PCB 'A') is mounted on the front panel with angle brackets that are epoxied to the rear face of the panel.

## **SUBSCRIPTIONS**

ETI 1980 . . . . . available from your newsagent every month.

Forget to buy it this month? Or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £10.00 we'll send you twelve issues of ETI. To claim your years' supply of ETI, send your PO or cheque direct to

ETI Subscriptions MAP Publications PO Box 35 Bridge Street Hemel Hempstead Herts.



#### **CAMBRIDGE LEARNING**

#### **SELF-INSTRUCTION COURSES**

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's -soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail.

After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND **ELECTRONICS £7.50** 

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw No mathematical beginner. knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.



Everyone can learn from it students, engineers, hobbvists.

housewives, scientists. Its four A4 volumes consist of:

Book 1 Binary, octal and decimal number systems; conversion between number systems;
conversion of fractions; octal decimal conversion tables.

Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to

Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input

gates.

Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift

#### DESIGN OF DIGITAL SYSTEMS £13.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic finally circuits and to understanding of calculator and



computer design.

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication

and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Fig flogs; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive—OR feedback counters; random access memories (RAMs) and read only memorics (ROMs).

memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and

#### Flow Charts and Algorithms are the essential logical procedures used in all computer programming

and mastering them is the key to success here as well as being a priceless tool in all administrative areas -presenting safety regulations, government legislation, office procedures etc.

#### THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

#### GUARANTEE No risk to you.

If you are not completely satisfied, your money will be refunded upon return of the books in good condition.

**CAMBRIDGE LEARNING LIMITED, UNIT 17** RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS., PE18 4BR, ENGLAND

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice)

Please allow 28 days for delivery in U.K.

TELEPHONE: ST. IVES (0480) 67446

#### Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the debugging, program, documentation. Harder problems are provided with a series of hints so you



never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.

#### COMPUTER PROGRAMMING IN BASIC

Book1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF....THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR....NEXT, RESTORE; debugging; arrays; bubble sorting; TAB

Book 4 Advanced BASIC; subfoutines; string variables; files; complex programming;

#### THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

#### A.N.S. COBOL £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

	DFR		7 N C
IIK	ארוו	FL 11	T IVI

Please send me the following books:  Digital Computer Logic & Electronics @ £7.50  Design of Digital Systems @ £13.50  Algorithm Writer's Guide @ £4.00  Computer Programming in BASIC @ £10.00  BASIC Handbook @ £11.50  ANS COBOL @ £5.90  Your Bookist (Free)  I enclose a *cheque/PO payable to Cambridge Learning Ltd. for £ (*delete where applicable)  Please charge my:
*Access/American Express/Barclaycard/Diners Club/Eurocard/Visa/ Masterchange/Trustcard
Credit Card No
Signature
Name,
Address
**************************************
Cambridge Learning Limited, Unit 17, Rivermill Site FREEPOST, St. Ives, Huntingdon, Cambs PE18 4BR, England. (Registered in England, No. 1328762)



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types thich they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers

30 <sub>va</sub>	70mm dia. × 30m Weight 0.45 Kg (+£1.00)	E4.71	160 <sub>v</sub>	110mm dia. × 4 ■ Weight 1.8 Kg (+£1.4	0mm <b>£8.88</b> 0p.p. + £1.54 VAT)
1X010	SECONDARY RMS VOLTS R	SECONDARY MS CURRENT 2.50	<b>TYPE</b> 5X012	SECONDARY RMS VOLTS 12+12	SECONDARY RMS CURRENT 6.66
1X011 1X012 1X013 1X014 1X015 1X016 1X017	9+9 12+12 15+15 18+18 22+22 25+25 30+30	1.66 1.25 1.00 0.83 0.68 0.60 0.50	5X013 5X014 5X015 5X016 5X017 5X018 5X028	15+15 18+18 22+22 25+25 30+30 35+35 110	5.33 4.44 3.63 3.20 2.66 2.28
50va	80mm dia. x 35mi Weight 0.9 Kg (+ £1.10 r	£5.19	5X029 5X030	220 240	0.72 0.66
2X010 2X011 2X012	6+6 9+9 12+12	4.16 2.77 2.08	225	110mm dia. x 4 Weight 2.2 Kg (+£1.5	E10.59 (p.p.+£1.81 VAT)
2X013 2X014 2X015 2X016 2X017 2X028 2X029 2X030	15 + 15 18 + 18 12 + 22 25 + 25 30 + 30 110 220 240	1.66 1.38 1.13 1.00 0.83 0.45 0.22 0.20	6X014 6X015 6X016 6X017 6X018 6X026 6X028 6X029 6X030	18 + 18 22 + 22 25 + 25 30 + 30 35 + 35 40 + 40 110 220 240	6.25 5.11 4.50 3.75 3.21 2.81 2.04 1.02 0.93
80 <sub>va</sub>	90mm dia. x 30mr Weight 1 Kg (+£1.20 p.	£5.76 p. +£1.04 VAT)	300v	110mm dia. x5 ■ Weight 2.6 Kg	<sup>0mm</sup> £12.27
3X010 3X011 3X012 3X013 3X014 3X015 3X016 3X017 3X028 3X029 3X030	6+6 9+9 12+12 15+15 18+18 22+22 25+25 30 110 220 240	6.64 4.44 3.33 2.66 2.22 1.81 1.60 1.33 0.72 0.36 0.33	7X016 7X017 7X018 7X026 7X025 7X028 7X029 7X030	(+£1.6) 25+25 30+30 35+35 40+40 45+45 110 220 240	6.00 5.00 4.28 3.75 3.33 2.72 1.36 1.25
120va	90mm dia. x 40mm Weight 1.2 Kg (+£1.30 p.	£6.72		140mm dia.×6 ■ Weight 4 Kg (£1.70	£16.35 (p.p. + £2.71 VAT)
4X011 4X012 4X013 4X014 4X015 4X016 4X017 4X028	9+9 12+12 15+15 18+18 22+22 25+25 30+30	6.66 5.00 4.00 3.33 2.72 2.40 2.00	8X017 8X018 8X026 8X025 8X033 8X028 8X029 8X030	30 + 30 35 + 35 40 + 40 45 + 45 50 + 50 110 220 240	8.33 7.14 6.25 5.55 5.00 4.54 2.27 2.08
4X029 4X030	220 240	0.54		TOROIDAL TR VARANTEED FO	

#### **CHOICE OF 3 PRIMARY INPUTS**

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

follows: (secondaries can be connected in series or paramer)
For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

\* CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility. (U.K. only).

Simply address envelope to FREEPOST to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Lid or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £l extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.



TRANSFORMERS

A division of I.L.P. ELECTRONICS LTD.

FREEPOST T4 GRAHAM BELL HOUSE ROPER CLOSE

**CANTERBURY CT2 7EP** 

Phone (0227) 54778 Technical (0227) 64723 Telex 965 780

#### CAR ENTERTAINMENT BARGAINS

Show us that you could have purchased for less within one month of your purchase and we will refund the difference!

 STEREO CASSETTE/RADIO.
 MW and Stereo FM radio and Stereo
 Cassette Player, 8 watts per channel, lockable fast forward and autoston lockable fast forward and autostop.
Includes fitting kit and FREE
SPEAKERS. Sold elsewhere for up
to £85 (believe it or not). OUR!
PRICE £45 (+ £1.50 post). (For
negative earth cars only).





● PYE 7-CHANNEL STEREO GRAPHIC EQUALISER/ BOOSTER AMPLIFIER. 17 watts R.M.S. per channel. Frequency response 20Hz to 30,00Hz. ± 12dB cut/boost on each channel. Complete with fitting kit. You would pay at least £45 elsowhere. OUR PRICE £28 (+ £1.20 met) £1.20 post).

SUITABLE SPEAKERS FOR EQUALISER. Adjustable angle, shelf-mounting, power handling 30 watts max. OUR PRICE £16 per pair £1.20 post).





ELECTRIC ANTENNA. Wing mounting, including switch and fitting kit. OUR PRICE £10 (+ £1.20

PLEASE NOTE: These goods are ready built units. All goods guaranteed one year. 10-day money back offer on all undamaged goods. Goods ex-stock at time of going to press. Send SAE for details

#### MINIKITS ELECTRONICS LTD.

88H Hainault Road, Leytonstone, London E11 1EH

#### MC-3L+FORMULA 4 MkIII®

The best value in state-of-the-art pickup



Geometry optimised for 12" LP Discs Stevenson, 'Wireless World,' May & June, 1966

> The only variable mass damped arm for high or low compliance Styli.

Reviewed by John Borwick - Feb. '79 Gramophone.





MC-2C MOVING COIL CARTRIDGE T24 Universal

Transformer, the quietest best step-up avail-

#### NEW

High Output Moving Coil Cartridge MC-3L.

No step-up required.


Super-polished special line contact nude diamond stylus for maximum information retrieval

REVIEWED BY REG. WILLIAMSON, SEPT. '79 'HI-FI FOR PLEASURE' and GEOFF GILES DEC. '79 'PRACTICAL
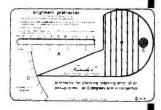
#### Alignment Protractor Mk. II

Improve your stereo image. Enables correct setting of all pick-up arm and cartridge combinations. Measures tracking accuracy over entire disc surface with Steveson zero error points for minimum distortion

Devised by Percy Wilson M.A., Original 'Hi-Fi News' Review avail-



MAYWARE LTD. (Dept. ET1) P.O. Box 58, Edgware, Middlesex HA8 9UH Tel: 01-958 9421



## - William and the state of the same

#### 6 piano type keys

## thondal B.K. ELECTRONICS thondal A SOUND CHOICE



#### **★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS** A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY

STEREO CASSETTE TAPE DECK ASSEMBLY. Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. Features: Pause, control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual record, level controls, secondary inputs for twin microphones. Input Sensitivity: 6 MV (with level control set at max). Input Impedance: 47 kOhms. Output Level: To both left and right hand channels 150 MV. Output Impedance: < 10k. Signal to noise ratio: 45 dB nominal. Power Supply Requirements: 12V AC at 300M/A. Connections: All connections to the unit are via a wander lead terminated with a nine pin plug (socket provided). Dimensions: Top 111/2 in x 61/2 in. Mechanism fits through a cut out 5% in x 101/2 in. Clearance required under top panel 21/4 in. Supplied complete with circuit diagram etc. Price £30.50 plus £2.50 postage

and packing. Suitable mains 12-volt transformer, £3.00.

NEW RANGE QUALITY POWER LOUDSPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hifd and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons Specification and Price:-

15" 100 watt. Impedance 8ohm 50 oz. magnet. 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Res-ponse to 2.5KHz. Sensitivity 97d8. Price £32 eech. £2.00 Packing and Carriage each


12" 100 watt. Impedance 8 ohm. 50 oz. magnet. 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. PTICE £23.70 each. £2.00 Packing and Carriage each.

8" 50 watt. Impedance 8 ohm. 20 oz. magnet. 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. Price £8.90 each. £1.00 Packing and Carriage each.

#### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put i series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH

TWEETER

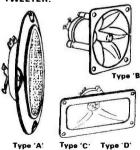


Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. Price (Type 'A') £3.45 each. Type 'B' 31/2in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**Type 'C' 2in x 5in wide dispersion

horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**Type 'D' 2in x 6in wide dispersion

horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. Price £6.90 each.

Post and Packing, all types, 15p each

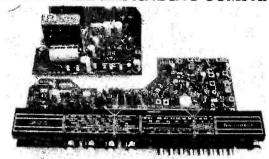

GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. Note: Circuit diagram and interconnecting wiring diagrams supplied. Rotary Controls: Tuning, on/off volume, balance, treble, bass. Push-button controls: Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. Frequency Response: 60Hz-20kHz within ± 3dB

Tape Sensitivity: Output - typically 150 mV. Input - 300 mV for rated output. Disc Sensitivity: 100mV (cer-23/4 in x 15 in x 71/2 in approx. Power amplifier — 2in x 7 1/2in x 41/2in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price** £23.50 plus £2.50 postage and fack-

JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

\* 'S' shaped tone arm.

★ Belt driven.

\*Full size 12in platter.\*

\* Precision calibrated counterbalance weight (0-3 arms )

\* Anti-skate (bias) device. Nylon thread

weight. ★ Damped cueing lever.

★ 240V AC operation, (50Hz). \* Cut-out template supplied.

Size — 12¾ in x 15¾ in (approx).

Price £28.50 plus £2.50 postage and



**AVAILABLE EX STOCK** PHONE (0702) 527572 or large s.a.e. for leaflets etc.

#### FIRE ALARM CENTRAL CONTROL UNIT (S.T.C.) Ideal for Fire or Burglar Alarm Systems

Responds to normally open or closed

- switches (or smoke detectors etc.) Complete with an internal EXIDE lead acid accumulator (dry charged) as a back-up for mains failure. This is trickle charged
- \* 6v-2 amp output for Fire/Burglar alarm,
- ★ Re-set button for silencing Fire/Burglar
- # Internal buzzer which sounds if re-set button ★ Internal buzzer which sounds if re-set button if pressed until initiating switch is cleared.
   ★ Wall mounting, complete with red case, approx. 11" x 7½" x 4".
   ★ 240 x 4C operation.
   Price £18.50 + £3 postage and packing.

#### LOUDSPEAKER

High quality full range 8" loudspeaker. 15 watts RMS 8 ohm. Rolled surround with aluminium centre dome

Price £3.75 each + 75p Postage and





**B.K. ELECTRONICS** 

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★SAE for current lists. ★Official orders welcome. ★All prices include VAT. ★Mail order only. ★All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by **prior** appointment, please phone 0702-527572.



## **DESIGNER'S NOTEBOOK**

Ray Marston devotes this month's Notebook to a discussion of special applications for 555 or 7555 astable circuits.

he old-fashioned 555 timer, or its modern CMOS counterpart, the ICM7555, can readily be used as a highly stable and cost-effective astable multivibrator. Usually, the device is merely used to generate simple square waves, but in practice it is readily capable of performing some fairly fancy tricks: it can, for example, be used to generate useful ramp and sine waveforms and can be gated on and off in a variety of ways.

#### Gating The 555/7555 Astable

The 555/7555 astable can be gated on and off in a variety of ways, to produce a variety of output waveforms. Figure 1 shows the basic connections and the equivalent circuit of the standard 555/7555 astable, it is necessary to understand the operation of this basic circuit in order to appreciate the action of the various gating methods. In the following discussions, a

12 V supply rail is assumed in all circuits.

The first point to note about the Fig. 1 equivalent circuit is that the IC contains a three-resistor potential divider, two voltage comparators, a flip-flop, a transistor and an output buffer. The divider ratios are such that one-third of the supply voltage (ie. 4 V) is set on the lower comparator and two-thirds of the supply voltage (ie. 8 V) is set on the upper comparator. The circuit action is such that, in each operating cycle, C1 first charges up to 8 V through R1-R2, at which point the upper comparator activates the flip-flop and turns the pin 7 transistor on; the transistor then discharges C1 through R2 until the C1 voltage falls to 4 V, at which point the lower comparator activates the flip-flop and turns the pin 7 transistor off, causing C1 to recharge through R1-R2. The operating cycle is then complete and repeats ad infinitum. A ramp waveform with an amplitude that swings between 4 V and 8 V is generated across C1 and a rectangular waveform is generated at output pin 3.



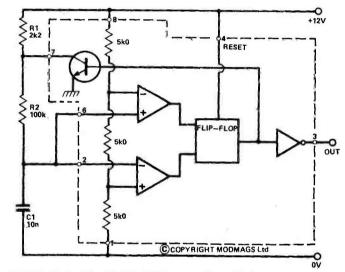


Fig.1b Equivalent circuit of the 555-type astable multivibrator.

The conventional way of gating the 555/7555 astable is with the pin 4 reset terminal, as shown in Fig. 2. When this pin is pulled to ground (by a 1k0 resistor), the flip-flop output is driven high, thus discharging C1 through R2 and the transistor and also driving the pin 3 output low. The resulting circuit waveforms are shown in the diagram. Note that, when the astable is gated on, the first half cycle is considerably longer than the succeeding half cycles. Also note that, when the astable is first gated off, the C1 voltage takes a substantial time to decay to zero. The pin 3 output is zero under the off condition.

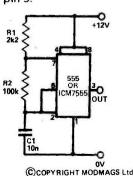

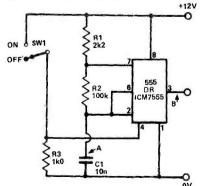

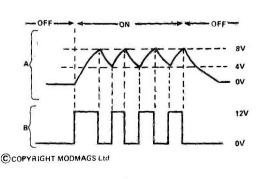


Fig.1a Basic circuit of the 55-type astable multivibrator.

Fig.2 Conventional way of gating the 555 astable, with resultant waveforms.

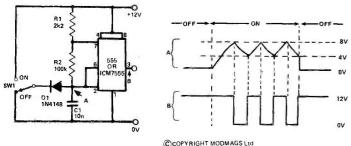


Fig.3 Basic method of gating the 555 astable using C1, with resultant waveforms. Note that the period of the first half-cycle is longer than that of the succeeding half-cycles.

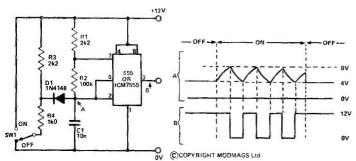


Fig.4 Modification of the C1 gating scheme, giving constant-period half-cycles.

#### **Alternative Methods**

One alternative method of gating the 555/7555 is shown in Fig. 3. Here, when the circuit is gated on, D1 is back-biased and the astable operates in the normal way, but when the circuit is gated off D1 shorts out C1 and pulls point A to ground; in practice, of course, SW1 can be replaced by an electronic switching waveform (the output of a CMOS gate, etc.) Note in this circuit that, when the astable is gated on, the first half cycle is again considerably longer than the succeeding half cycles, but that the C1 voltage falls abruptly to zero at gate-off. Also note that the pin 3 output is high in the off state.

Figure 4 shows how the above circuit can be modified so that the duration of the first half cycle is almost equal to that of the succeeding half cycles. This is achieved by choosing the R3-R4 values so that the C1 voltage is only a fraction below 4 V (one-third of supply volts) under the off condition. A substantially different set of waveforms can be obtained by choosing the R3-R4 values so that the C1 voltage is a fraction below 8 V (two-thirds of supply volts) under the off condition, as shown in Fig. 5.

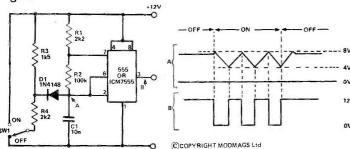


Fig.5 This slight modification of the C1 gating scheme produces a considerable change in the circuit output waveforms.

It should be appreciated that the 555/7555 astable can only oscillate if its timing capacitor (C1) is free to swing between the 4 V and 8 V switching levels. This simple fact makes it possible to voltage-gate the astable by using the circuit of

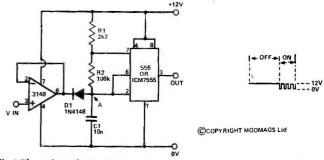


Fig. 6 The voltage-controlled astable produces an output only when  $V_{LV}$  exceeds two-thirds supply (8 V in this example).

Fig. 6. Here, the circuit produces output waveforms only when the input voltage exceeds 8 V. The circuit can be made to trigger at other levels by giving the op-amp an appropriate voltage gain factor.

Finally, an alternative method of gating the 555/7555 astable is shown in Fig. 7. Here, the circuit is gated off by driving the C1 voltage above 8 V by D1. A feature of this circuit is that its 'B' output is low under the off condition.

#### **Asymmetrical Astables**

The basic 555/7555 astable generates near-symmetrical output waveforms, provided that R2 is large relative to R1 (giving near-equal C1 charge and discharge time constants). Figures 8 to 10 show alternative methods of generating non-symmetrical waveforms. In Fig. 8, C1 charges through R1-R2 but discharges through R2 in parallel with R3-D1, to produce the waveforms shown. In Fig. 9, C1 charges through R1 and R2 in parallel with R3-D1, but discharges through R2 only; this circuit is useful for providing narrow output pulses at the 'B' terminal.

Finally, in Fig. 10, C1 charges through R1-R3-D2 and discharges through D1-RV1-R1-R2, to produce narrow output pulses at the 'B' terminal. This circuit is useful for generating variable-frequency constant-width pulses.

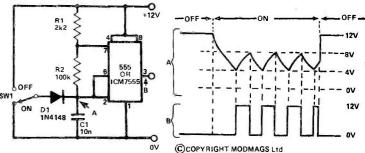


Fig.7 This C1 gating scheme produces a 'B' output that is low in the off condition.

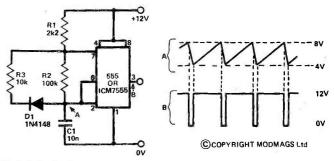


Fig.8 A method of producing a non-symmetrical fixed-ratio from the 555 astable.

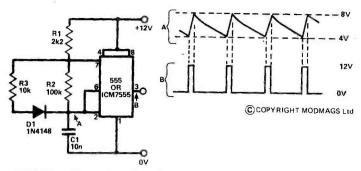


Fig.9 Alternative method of producing a non-symmetrical fixed-ratio output from the 555 astable.

#### 555/7555 Sine Wave Generation

Figure 11 shows how a sine wave signal can be obtained from a 555/7555 astable. Here, the symmetrical ramp waveform of C2 is buffered by Q1 and then AC coupled to the R1-R2-D1-D2 divider/limiter network. This network attenuates the ramp signal and then non-linearly removes the ramp's positive and negative peaks, to produce a sine-shaped waveform of about 1 V peak-to-peak amplitude at the output terminal. The distortion level of the resulting sine wave is typically of the order of 3% and its frequency can be varied from a few cycles per minute to several hundred kilohertz by suitable choice of the C2 value.

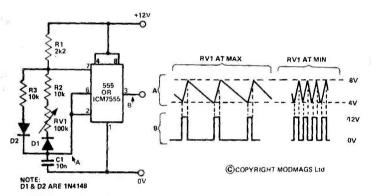


Fig. 10 A method of producing a non-symmetrical variable-ratio output from the 555 astable.

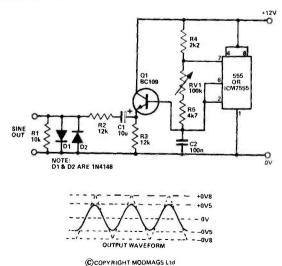


Fig.11 A 555 sine-wave generator with a range of 83 Hz to 1.4 kHz (via R1).

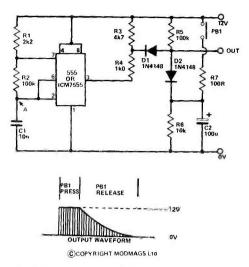


Fig. 12 A method of amplitude-modulating the pin 3 output of the 555 astable in music and sound generator applications.

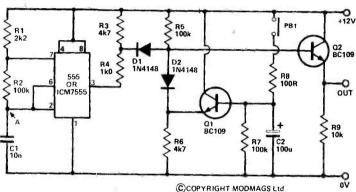


Fig. 13 A modification of the Fig. 12 circuit to give extended decay times and a buffered output.

#### **AM Output**

Figure 12 shows how the pin 3 square wave output of the 555/7555 astable can be amplitude-modulated to produce the typical attack-hold-decay envelope of a simple musical instrument or of a special-effects sound generator. The heart of the unit is the diode AND gate, or mixer, formed by D1-D2-R5. One input of this gate is fed from the output of the astable via R3-R4 and the other from across R6. The basic action of this gate is such that (ignoring the diode volt drops) its output amplitude is equal to the lesser of the two inputs.

Thus, when D1 is fed with the square wave output of the astable, the peak output of the unit will be zero when the R6 voltage is zero, or 5 V when the R6 voltage is 5 V, etc. In our circuit, R6 is shunted by electrolytic capacitor C2. Thus, when PB1 is pressed, a large voltage is applied to R6 and a large-amplitude square wave output is available. When PB1 is released, the R6 voltage and the square wave output amplitude decay exponentially to zero (with a time constant of R6-C2), as shown in the diagram. The R3-R4 network is used to apply a slight offset bias to the rectangular input waveform, to ensure a full cut-off of the output waveform after PB1 is released.

Finally, Fig. 13 shows how the above circuit can be modified to give extended display times (via emitter follower Q1) and a buffered audio output (via emitter follower Q2).



DORAM ELECTRONICS LTD

Fitzroy House, Market Place, Swaffham, Norfolk, PE37 7QH.

TEL:(0760) 21627 TELEX 817912 VAT Reg: 324 5604 75

Projects for beginners	PROJECT PACKS	
Clap switch (79026) Responds from a hand clap to so Simple Sound effects (79077) Strange noises from a Pools predictor (79053) An analogue computer that	a very simple circuit, loudspeaker included. t may win you a fortune. duces very strange results when fed with a human voice. ound of steam and whistle. pise, but only in the dark!	£6.60 £5.70 £8.15 £9.60 £2.35 £6.50 £3.85 £7.20
New projects		21.20
Melody Maker (80502) An electronic musical bo LCD Counter (80117) Simple to construct freque Linear Thermometer (80127) Simple but effective Precision Power Unit (80514) Produces accurate	ox that can play 27 tunes with organ or piano-like quality. ency display for AM and FM bands. ve meter reading thermometer using a diode as sensor. e reference voltages at presetable current limits up to 2 Amps. o signals on tape with operation of two slide projectors.	£23.50 £41.20 £13.45 £48.65 £46.50
Audio projects	p.ojestela	240.30
Top-preamp (80031) Mini all IC preamplifier for use v	s Philips modules for high fidelity performance. Two power levels:	£34.40
Stentor (79070) A high power portable amplifier for PA Assistentor (79071) A preamplifier designed for Sten	OM931 (output 30 OM961 (output 60 A use ntor which can also be used as a speech compressor for radio transmission onstruction to suit your equalisation requirements. Filter section (9897-1)	Watt) £33.40 £30.00 £7.00 £6.45
Elektornado (9897) A single board design that can be UAA180 LED meter (9817) A two channel voltage dis Peak Programme Meter (9860) To be used with UAA Audlo Analyser (9932) An analyser that can pin point Stereo dynamic Preamp (80532) A low noise high qu STAMP (80543) Super tiny amplifier with up to 1 Watt Consonant (9945) A high quality audio control amplifii Preconsonant (9945) A preamplifier for the disc input Luminant (9949) A two channel LED display designed	v180 LED meter to give PPM display. It the deficiences in an audio chain. It will be consequent to the deficience of the consequent to the consequent to the Consequent.	£5.20 £19.50 £13.00 £3.70 £14.80 £5.20 £3.75 £34.65 £5.75 £20.70
Car projects		220.10
Car Battery Charger (79517) Reliable and safe charger Transistor Ignition (80082) The most significant adversariation (80102) Direct warning of high oil tem Intelligent Wiper Delay (80086) Can be set to produce Battery Protection (80109) Automatically switches of Battery Voltage Indicator (80101) LEDs indicate the Active Car Aerial (80018) Improves the sensitivity of A	antages of other systems combined in one. iperature. State long or short dipstick required. be delayed wipes at any predetermined interval. fif the head lamps of a parked car. be condition of your battery.	£21.70 £20.45 £11.25 £15.85 £5.15 £6.85
Music projects	waste in adio reception in your car.	£13.85
Chorosynth (80060) A cheap mini synthesizer. Send Elektor Vocoder (80060) The first Vocoder designed the Analogue Reverberation Unit (9973) Uses a SAD102 Guitar Preamp (77020) With three tone controls.	to be built in kit form 10 Channel modular construction	£57.90 £162.50 £27.70 £6.50
Projects for the home		20.00
Touch Dimmer (78065) Room lighting controlled by a loniser (9823) Produces a high concentration of negat Loudspeaking telephone amplifier (9987) Amplifies Proximity Detector (9974) Detects by electric field characteristics.	tive ions. without direct connection	£6.80 £9.55 £11.50 £9.80
Our Project Packs include the electron	nic components the BCR applicate and coldents are	46

Our Project Packs include the electronic components, the PCB, sockets and solder together with assembly instructions. Cases, knobs etc can be supplied as extra items if required. This is only part of our wide range of projects. See our catalogue for details of other projects that we can supply. You can also ring our number between 12.30 p.m. and 1.30 p.m. any weekday for a recorded announcement of any new items we have available. Send 40<sub>D</sub> for catalogue

#### **HOW TO ORDER**

Send a cheque or postal order to DORAM ELECTRONICS LTD or write or ring with your Access account number. All our prices include VAT. Overseas customers please deduct 15%. Please add 40p to your order for postage and packing. An answering service is qualiable to take answering service is available to take your orders outside our normal office hours. Mail Order service a de boer company

Buy it with Access

NAME
ADDRESS

#### **DIGITAL VOLTMETER MODULE**



Fully built and tested, ONLY

- \* Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- \* Requires only single supply between 7 & 12 volts (220mA)
- High accuracy +0.1% +1 digit
- Large bright 0.43" high efficiency displays
- \* 4 readings per second sampling rate
- Size only 41 x 95 x 10mm
- \* Supplied with full data & applications information

This brand new, quality module manufactured by Autona Limited (who are one of the U.K's largest module manufacturers) means you can build accurate test equipment, multimeters, thermometers, etc. easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature

Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50pp. & p.= £14.24) now to:-

Dept. ET14 RISCOMP LIMITED 21 Duke Street **Princes Risborough** Bucks, HP17 OAT

BUCKINGHAMSHIRE'S NEW **ELECTRONICS CENTRE** 8 miles off the M40 50 minutes from London Telephone: (084 44) 6326



EX-STOCK DELIVERY



#### **POWERFET AMPLIFIERS**

Some day all power amps will be made this way!

Very high quality 80 watt and 120 watt designs (by Hitachi) offering wide bandwidths and very low distortions. Both are conservatively rated and can be used with supplies up to ±70V. One P.C.B. serves both designs, and an 80 watt unit can be upgraded by the simple addition of components.
All units come with substantial heatsink/mounting brackets.

PFA80 80w into 8Ω (Vs = ± 50V) †THD ≤ 0.008%. S/N 120dB. PFA120 120W into 8Ω, (Vs =  $\pm$  55V), †THD  $\leq$  0.005%. S/N 120dB.

KIT £18.85, BUILT £20.85

KIT £11.95. BUILT £13.95 KIT £18.85. BUILT £20. ffrom 1W to rated output at all audio frequencies. PFA120. recommended for 4\Omega loads.

45v.0.45v, 300Va Toroidal Transformer £15 (£2 p&p)

	CHAN	VDS- max V	ID max A	PDISS max W	Price	CA3045 70p CA3080E 70p CA3086 55p	2114 4001B 4007
BD512	P	60	1.5	10	85p	CA3140E 45p	4011B
80522	N	60	1.5	10	80p	DACOBEN 250m	4013B 4016B
VMP4	N	60	2.0	25	1250p	DM2502 555p	4069
VN10KM	1 N	60	0.5	1.0	55p	LM3900 43p	709
VN64GA	N	60	12.5	80	750p	MC3401 30p NE529 145p	710 733
VN67AF	.N	60	2.0	15	75p	NE555 25p	741
2SJ49	P	140	7.0	100	340p	SAD1024	78L05
2SK134	N	140	7.0	100	.340p	1050p TL081 29p	78L12 781705
	-				J	TL082 65p	781712

1/p protected. †our selection. VN/VM 120-page Design Cat. **45p.** Heat clips/sink T0202 **12p.** T092 **8p.** T03

35p. HI-FI ON TWO CHIPS

HI-FI ON TWO CHIPS
HA12017 (Preamp 0.001%
distortion 83dB S/N in phono
application) 80p. HA1397
(Poweramp 20 watts in 80;
0.02% distortion (typ) 195p.
Both with data and circuits.
VCA High quality design offers
attenuation from 0dB to
-90dB. S/N 900B, THD
0.01%, B.W. DC to 100KHz.
Complete component set and Complete component set and circuit £2.50.

1.C. Sockets (low prof.).
8 pin 10p, 14 pin 12p, 16 pin 13p.
Low noise Resistor set 10 off each E1P. value from 10R to 10M 730, 16W, 5% CF resistors 6500.

tors 650p.

SCOPE TRACE DOUBLER P.C.B.

P.C.B.

Built. C/W shift, chan select, choprate controls and instructions. Useful display from DC to 10MHz. Runs from 9v battery €9.95

2μS ADC chip set (DACO8, DM2502, NE529) with data £9. HA1388 (Bridge amp, 18w from car battery). With data 195p. Heatsink for HA1388/1397

148 Quarry Street Liverpool L25 6HQ Tel. 051-428 2651

Technical enquiries to 367 Green Lanes, London N4 1DY. Telephone. 01-800 6667 Overseas ordors. Payment in sterling £1.00 p&p

## 110 projects in every book!!

The '110' books have been acclaimed by enthusiasts, students and engineers. Each contains 110 different circuit applications. Use them as project books or as source books for circuit ideas.



110 CMOS Digital IC Projects for the Home Constructor R. M. MARSTON 0 408 002 16 6

110 Electronic Alarm Projects for the Home Constructor R. M. MARSTON 0 408 00269 7

110 IC Timer Projects for the Home Constructor JULES H. GILDER 0 408 00480 0 £3.95

110 Integrated Circuit Projects for the Home Constructor -Second Edition

R. M. MARSTON

0 408 00309 X

£3.95

110 Operational Amplifier Projects for the Home Constructor R. M. MARSTON 0 408 00 153 4 £3.95

110 Semiconductor Projects for the Home Constructor Second Edition R. M. MARSTON 0 408 00322 7 £3.95

110 Thyristor Projects using SCRs and Triacs R. M. MARSTON 0 408 0074 5 £3.95

110 Waveform Generator Projects for the Home Constructor R. M. MARSTON

Available from your bookshop or in case of difficulty direct from the publishers.



## **POLYSYNTH**

Part 2: This month we continue the Polysynth project with details of the motherboard and control boards. Design and development by Tim Orr



olyphonic portamento has been provided by using a voltage controlled slew limiter for each pitch voltage (Fig. 10.11). The slew rate is controlled by the lanc current and the timing capacitor  $C_B$ .

Slew Rate = 
$$I_{ABC}$$
 $C_B$  VS<sup>-1</sup>

An LM13600 OTA is used to charge and discharge C<sub>B</sub>. The OTA is contained in a feedback loop of two op-amps to reduce the differential offset voltage change between the input and the output. The circuit generates a voltage change of about 100 uV over its full range of 0 to -4V at all slew rate settings.

With the portamento pot fully clockwise, the pitch of the notes will not be noticeably slewed. As the pot is rotated anticlockwise the slew limiting will become very obvious. At its slowest rate, a four octave transition will take about 2 S.

#### **Volume Control**

The audio outputs from all voices are mixed into IC13, Fig. 10. This is a voltage controlled amplifier. With the master volume control anticlockwise the output will be fully off.

#### Pitch Bend

The pitch bend joystick is shown in Fig.12. Note that the offset lever has to be cut short to avoid fouling the pitch bend plate. This lever is adjusted so that with the joystick in the centre, the voltage on the pot wiper is zero.

#### **Panel Boards**

SP10 3NM

Board PS5 generates all the common synthesiser parameters and PS6 the individual parameters. Most of the panel controls merely generate DC voltages. However, there are three modulation oscillators which are used to produce VCO vibrato, VCF sweep and pulse width modulation of the VCO square wave output. Note that the pulse width modulation pots(RV2.4) are dual function.

Clockwise they are connected to the modulation oscillator and anticlockwise they produce a manual control ranging from one-to-one square wave to a very thin pulse. In the centre of the pot movement there is a mechanical 'click'.

A pseudo-random noise source (IC5,6) with a low frequency boost has also been included as a sound source. Boards PS5 and PS6 connect to PS4 via preformed 12" flexible jumper links. Make certain that these links are clamped to the boards with self-adhesive ribbon cable clamps, as these will take the strain of the cables as they are flexed.

#### **BUYLINES**

Powertran Electronics can supply a complete kit of parts for each option of the Transcendent Polysynth

£320 1 voice £368 2 voices £464 4 voices

4 voice expansion kit All prices are exclusive of VAT. Powertran Electronics, Portway Industrial Estate, Andover, Hants

Note: The price of the 4 voice expansion kit was shown incorrectly last

£295


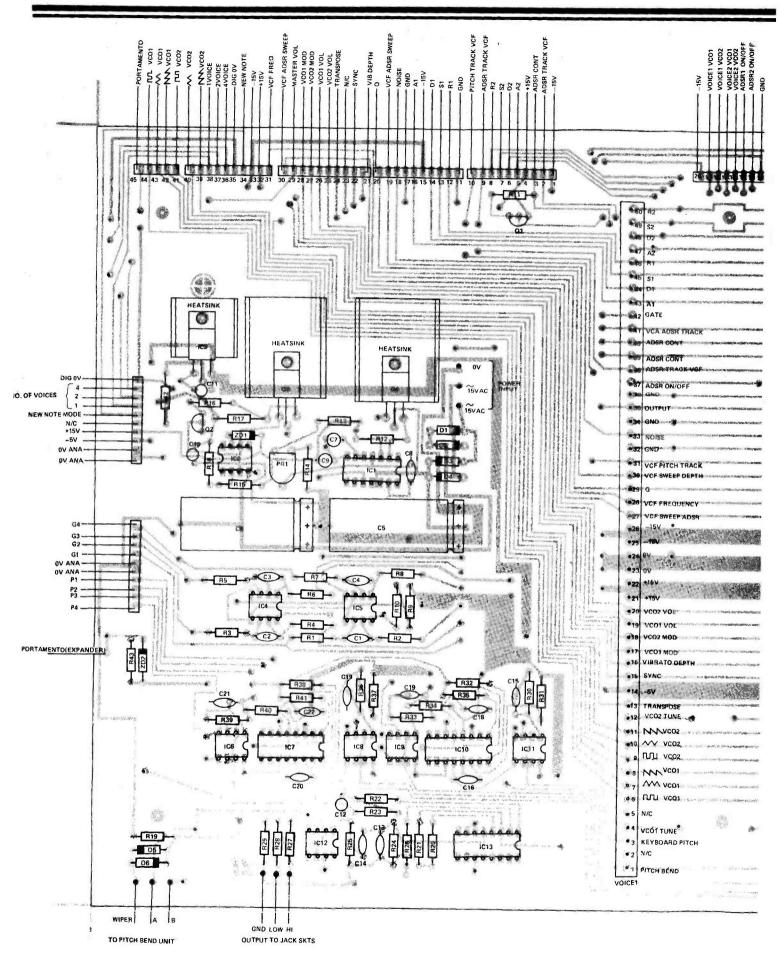


Fig.1 Component overlay of the motherboard (PS4). The circuit diagram was published last month.

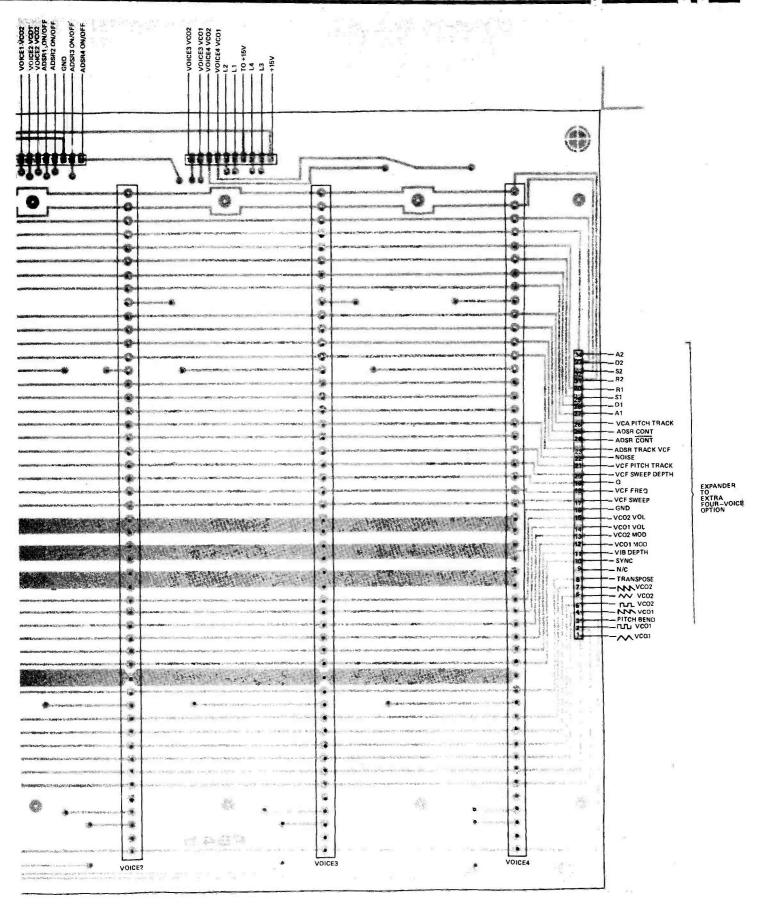

#### PARTS LIST: PS4

Resistors all ¼ W 5%	unless otherwise stated	C8	330p ceramic	
R1,3,5,7	1M0	C13		
R2,4,6,8	1k5	C14,16,18,20,22	1n0 polycarbonate	
R9	1k2	C15,17,19,21	220n polycarbonate	
R10,26,30,33,36,39	15k	C13,17,19,21	470p ceramic	
R11,32,35,38,41	100k	C		
R12,17	1R0 2 W	Semiconductors'	· · ·	
R13	12k 2% metal oxide	IC1	723 (DIL)	
R14	10k 2% metal oxide	IC2,12	741	
R15,18	10k 0.5% metal film	IC3	7905	
	TOR U.5 76 metal film	IC4,5	1458	
R16,20,21,27,29,31,	110	IC6,8,9,11	LF353	
34,37,40	1k0	IC7,10,13	LM13600	
R22,23,25	22k	Q1,2	BC212L	
R19,24,28	10k	Q3	TIP30A	
R42	100R 1 W	Q4	TIP29A	
R43	270k	ZD1	10 V	
- 1		ZD2	5V1	
Potentiometers		D1,2,3,4	1N4002	
RV33	10k linear (single axis joystick)	D5,6	1N4148	
PR1	10k cermet preset	,-		
Capacitors		Miscellaneous		
C1,2,3,4	1n0 ceramic		Dil sockets 14 nin Dil socket 2 aff 16 min n	
C5,6	2200u 25 V electrolytic	PCB PS4, 8 off 8 pin DIL sockets, 14 pin DIL socket, 3 off 16 pi sockets, 2 off heatsinks (RS 401-964 or equivalent), TV5 heatsink		
C7,9,10,11,12 10u 16 V tantalum		necting pins, self-adhesive clips.		

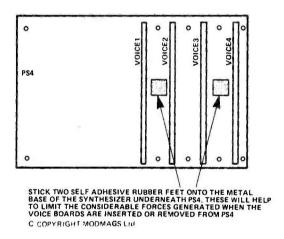


Fig.2 Plugging in the voice boards could damage the motherboard if it is not cushioned as shown.

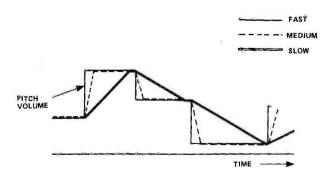


Fig.3 The effect of variable slew limiting (portamento) on pitch voltage.

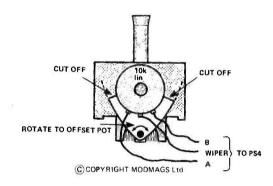


Fig.4 Mechanical details of the joystick pitch bend control.


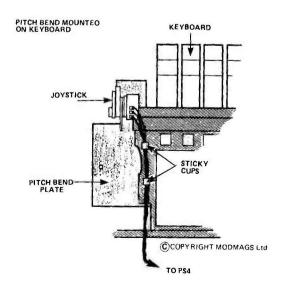


Fig.5 Mounting the joystick pitch bend control (RV33) on the end of the keyboard.

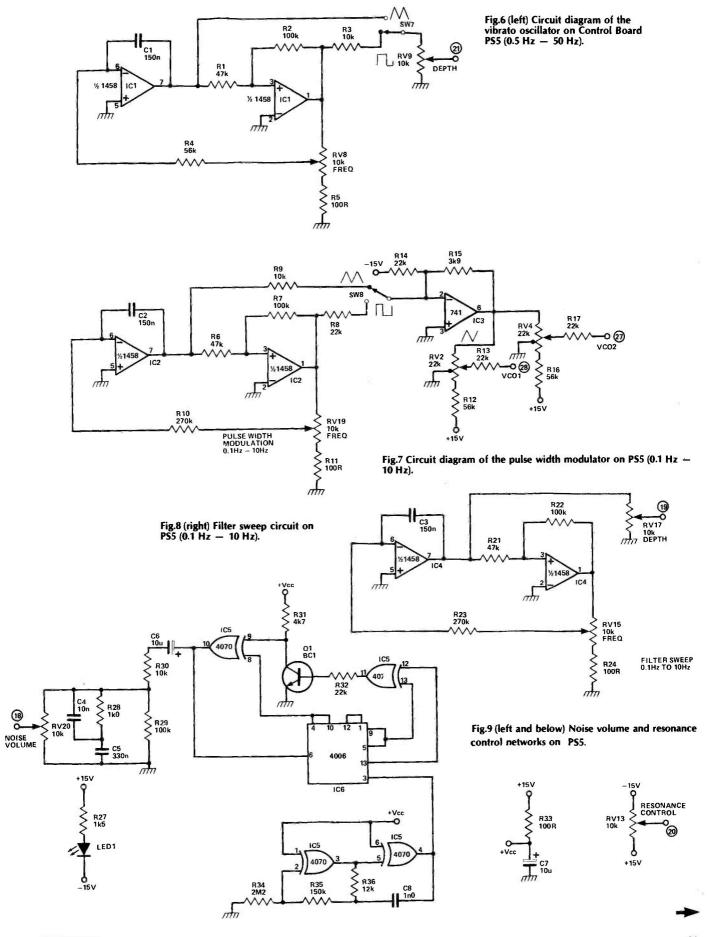



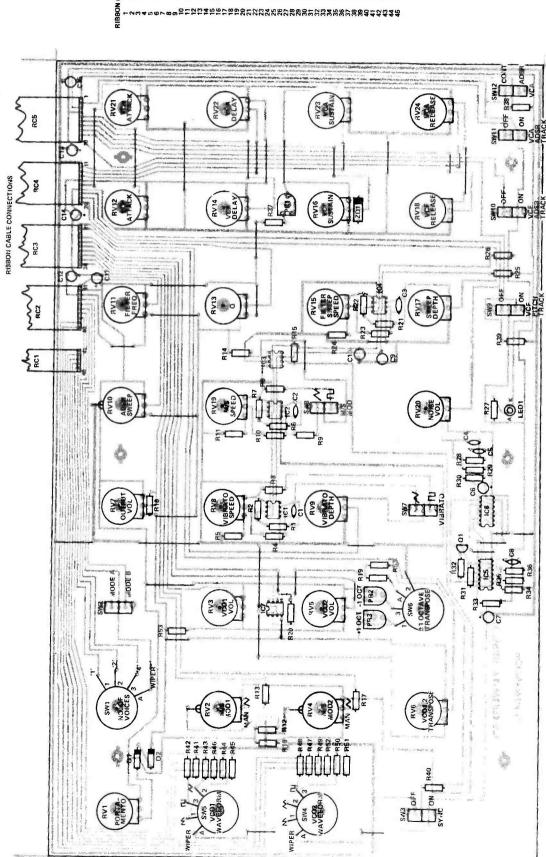


Fig.10 Component overlay of control board PS5.

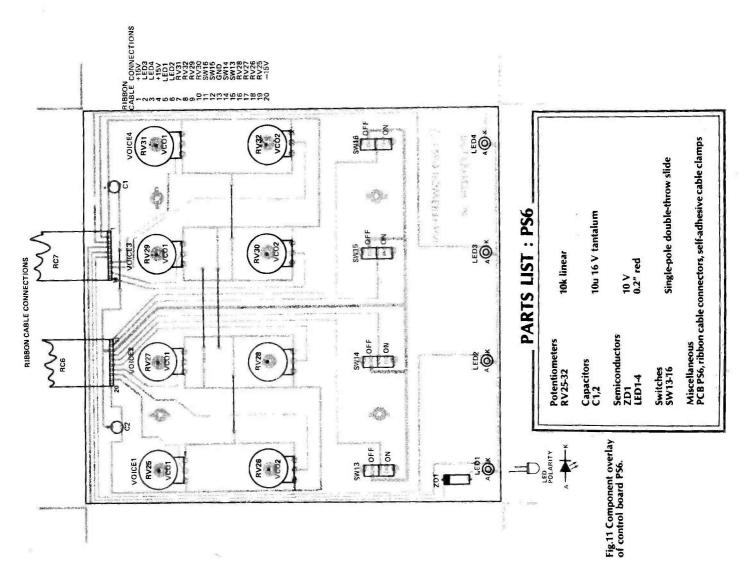


Resistors all 1/4 W 5% unless otherwise stated	,29,38,40-52 6 6 4,17,32 4,17,32	Potentiometers RV1,8,15,19,20 RV2,4,10 RV2,4,10 RV3,6,5,7,9,11,13, 16,17,23 16,17,23 17,13, 19,11,13, 10, preset RV12,14,18,21,22,24 10, preset RR2,3 150n polycarbonate C4,2,3 10n polycarbonate C5,2,3,2,4,2,4,2,4,2,2,2,4,2,2,2,2,2,2,2,2	nductors s	SW4.5,6. 4-pole 3-way rotary SW4.5,6. 4-pole 3-way rotary Miscellaneous PCB PS5, connectors, self-adhesive clips
Resisto	R. 1,5,21 R. 3,9,30 R. 3,9,30 R. 5,11,2 R. 6,13,1 R. 16,23 R. 16,2	Potenti RV2,4,7 RV2,4,1 16,13,6,9 RV12,1 PR1 PR2,3 Capaci CC1,2,3 C4	Semicol Semicol 1C1,2,4 1C3,7 1C6 1C6 1C7 1C1,2,4 1C7 1C7 1C7 1C7 1C7 1C7 1C7 1C7 1C7 1C7	SW4,5 SW4,5 Miscel PCB PS

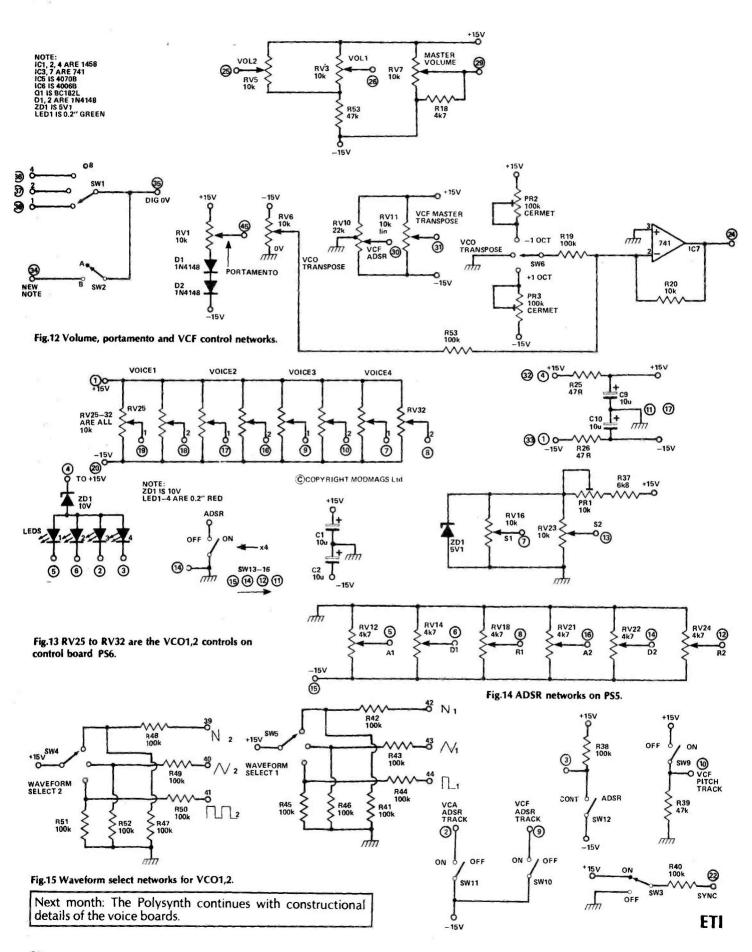



Aura Sounds are the first company to successfully market Wersi Organs and Kits in the United Kingdom. Operating from modern Showrooms, we offer a complete, unique evening and weekend telephone support advice. We pride ourselves on our friendly and individual service. We market Wersi products because we feel they are simply the best, both in terms of quality and reliability. These factors, together with a fresh approach, are what have made Wersi one of the leading organ manufacturers in the world today. AURA SOUNDS AND WERSI — THE WINNING COMBINATION. Illustrated below are just a few of the wide range of organs in stock.

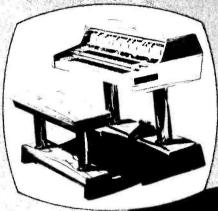

#### The SATURN W3T.

The ultimate transportable organ, featuring sophisticated rhythm unit and built-in WERSI Voice. 30 or 61 note Keyboards and 30 pedals.

## The COSMOS W5S

The baby of the range, a great instrument at a great price. There are many optional extras and Cosmos can be easily assembled at home by the average handyman.



Our Birmingham Showroom opens mid-November. See Wersi organs and Heath hobbykits at:

1729 Coventry Road, Sheldon (midway between the City and Airport)





The HELIOS. For home or professional use. Available as a transportable model with various options including 25-pedal clavier.

#### The GALAXY.

The top model of the range with 3 full manuals and a 30 note pedalboard. For looks and sound, the effects are first class.



### **IMPORTANT**

AURA SOUNDS have just been appointed marketing agents for the range of Heath Electronic Kits in the U.K. This exciting range of 'up-market' Kits makes AURA SOUNDS, more than ever before, the company to come to for advice and product choice.

AURA SOUNDS 14-15 Royal Oak Centre, Brighton Road, Purley, Surrey. Telephone 01-668 9733 and at 17 Upper Charter Arcade, Barnsley, West Yorks. Telephone (0226) 5248 THE PROFESSIONALS

Please send me the 104 page colour WER	SI	catalogue
plus the NEW HEATHKIT BROCHURE	&	price lists
Lenclose a cheque/P.O. for £1.00		

Name\_\_\_\_

Address

Send to Aura Sounds Ltd. 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.

ETI.1.8



## AITKEN BROS.

35 High Bridge, Newcastle upon Tyne Tel: 0632 26729

## thandar **Test Equipment from Sinclair Electronics**



#### PDM35 DIGITAL POCKET MULTI-METER

INTELEM LED DISPLAY. DC volts (4 ranges) 1mV to 1000V. AV volts 1v to 500v. DC current (6 ranges) 1nA to 200mA. Resistance (5 ranges) 10 to 20MEGO. £39.95. AC adaptor £4.25. Padded carrying case £1.95. MN1604 Battery £1.28. Size 157x76x32mm.



PFM200 frequency meter. LED display. Range 20Hz to 200MHz. Accessories as for PDM35. Size 157x76x32mm. £57.95.



## **DM235 BENCH-PORTABLE DIGITAL**

MULTIMETER

INICLINICLEN
LED display. DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1mV to 750V. DC current 1μa to 1000MA.
Resistance (5 ranges) 1Ω to 20MEGΩ. £60.98. Carrying case £8.95. AC Adaptor/Charger £4.25. Rechargeable battery pack £8.95. Size 255x148x40mm.



#### DM350 & DM450. BENCH-PORTABLE **DIGITAL MULTIMETERS**

DM350 3½ digit LED display £83.95. DM450 4½ digit LED display £114.95. Both provide six functions in 34 ranges. DC voltage 10 μV to 1200V (100 μV on DM350). AC voltage 100 μV to 750 v. DC current 1nA to 10A. AC current 1nA to 10A. Resistance 10mQ to 20mQ (100 mQ on DM350). Carrying case £8.95. AC adaptor / charger £4.25. Rechargeable battery pack £8.95. Size 255x148x40 mm.



## SC110 LOW POWER PORTABLE

OSCILLOSCOPE
The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided, including Bright line and Auto with TV line and frame filtering. £159.85.



#### **TF200 FREQUENCY METER**

LCD display. The TF200 measures frequencies from 10Hz to 200MHz with a resolution of at least 1 ppm (typically better) across the whole measurement range. £166.75.



#### **TG105 PULSE GENERATOR**

The TG 105 is a mains operated 5Hz to 5MHz pulse generator with independent TTL and 50Ω variable outputs. Period and pulse width are each selected by a 6 position range switch rolus vernier control. £98.75.



#### **CALSCOPE SUPER 6 £186.30**

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 my/cm and wide time base range from 1 us to 100 ms/cm. Full specification to request. Professional scopes you can afford.



CALSCOPE SUPER 10 £251.85.
A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of builf-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request.

Please write or phone for illustrated brochure giving full technical specifications, for any of the "thander" products.





Education Establishment Orders Accepted PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER ALL PRICES INCLUDE POSTAGE AND VAT

## Greenbank

Greenbank Electronics (Dept T1E) 92 New Chester Road, New Ferry Wirrsl, Menseyside L62 5AG (Tel: 051-645 2391)



CMOS

18p 25p 25p 25p 25p 25p 25p 40p 40p 40p 45p 88p 45p 89p £1.10 27p 27p £2.25

90p 90p 74p E4.31 £1.31 £2.63 £2.00 £1.10

£1.99 £1.20

28p 28p 28p 28p 90p 28p 28p 28p 95p £1.43 57p 59p

74C

74C00 74C02

74C04

74CD8

74C10 74C14

74C20 74C30 74C32 74C42 74C48 74C73 74C74

TERMS, YAT. CWO. Cheques etc psyable to Greenbank Electronics and creased. Add VAT to all prices at 15% except where stated otherwise. Pest etc: [UK 35p] + 5p VAT = 40p) per order. Export: NO VAT but and 35p [Erre]. 75p [Eurepe] and [E2.50 otsewhere. Access, Barclaycard. Visa, telephonal orders accepted. [Polys, universities, govi depts, etc can telephone their orders for immediate despatch on accessed.]

hose cut prices for Amateur Users and Export, Note: industrial users —

£1.97

£1.97 £1.97 £5.98 £1.92 £2.00

£1.92 £1.69 £3.67 £3.67 £1.85 £1.85

92p £1.28 £7.54 £1.28 £3.00 £1.77 £1.54 £1.54 £1.54 £1.54 £1.54 £1.90 £1.90 £1.90 £1.90 £1.90 £1.90 £1.90

98p 98p 98p 98p 90p £1.15 4161 4162 4163 4174 4175

E1.15 E1.08 E1.08 93p 93p 93p E1.15 E1.15 E1.15 E1.46 E1.41 E2.98 E1.79 E1.79 79p

40104 40105

4194 4408 4409

74C163 74C164 74C165 74C173 74C174 74C175 74C192 74C193 74C290 74C221 74C221 74C245 74C373 74C374 74C902

80p 90p 90p 52.63 £1.10 £1.71 77p 45p 80p 80p 80p 52.55 £2.55 £2.55 £2.22 £2.10 £10.00 £1.80 £2.72 £2.72 £2.72 £7.21

27p 27p 30p 25p 25p 25p 25p 25p

29p 29p 27p 27p 27p E1.35 E1.35 E2.91

80p £2.50

57p £1.34 £1.34 67p £4.62 89p £1.08 £1.27 £3.81 £2.55 £3.81 £2.55 £3.81 £2.49 £1.49 £1.15

74C76

74C83 74C85 74C86 74C89 74C90 74C93 74C93 74C95 74C107

740150

74C151 74C154

74C157 74C160

74C161 74C162

4410 4411 4412VP

4422 4433

4451

140000

740909 740910 740911

740912

740914 74C915 74C918 74C921 74C922 74C923 £8.55 £10.72

£10.72 £14.93 £3.66 £12.30 £3.60 £3.61 £3.61

23.93 24.41 25.95 23.14 25.95 25.71 50p 25.71 50p 22.65 22.6

57p 57c. £7.53 57p £1.00 £1.69 £7.45 £7.39 £1.45 £1.10 £17.07 £3.78



£1.45 £1.30 £5.80 £3.69 £26.10 £1.20 97p £1.19 £1.435 £14.85 £1.38 £14.85 £1.38 £1.38 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50

40p £4.77 £2.62 £1.14

90p 90p £1.27 £2.44 £2.98 £5.95 £1.75

85p 92p 85p 92p £6.20

£2.90 £2.90

£1.85 £1.60 £2.12

E1.84 E2.15

86p E2.30 E2.31 E2.16 E2.15 E2.76 E1.50 E1.44 E1.80 E1.82 E1.82 E2.48

740925

82C19 88C29 88C30

## QUARTZ

SOLDERCON PINS 100 **50**p 1000 63 95

DII SOCKETS 6/14/16 pis 10p/12p/13p 18/20/22 pin 18p/28p/25p 10p/20p/20p 24/28/40 pin 30p/40p/50p 24 pin Textool lever type zero insertion force £8.50

43 way, 0,1" pitch, wire wrap, polarizing slot pin 37 Single sided [1×42] £3.11 Double sided [2×42]£4.10

(All Mind dips)
CA 3130E
CA 3140E
UA 741 (Texas) 84p 35p 22p

LED DISPLAYS

LIQUID CRYSTAL

CLOCK CHIPS AY-5-1224A MK 50253 MK 50366 £2.60 £5.50 £6.50

SIX DECADE COUNTERS NK 50395/6/7 NK 50306/9 £9.80 £7.50

		20.40
32.758KHz		256"×1" (pack of 5) 74
(Watch)	€3.23	2%"×3%" 53
60 KHz	£9.95	2½"×5" 62
100.9 KHz	£3.62	21/4"×17" £1.5
200.0 KHz	£3.92	3%"×3%" 62
204.8 KHz	£3.92	3%"×5" 86
262.144 KHz	€3.92	3%"×17" £2.4
307.2 KHz	£3.92	4,7"×17.9" £3.1
312.5 KHz	£3.92	0.1" Plainboard
455.0 KHz	£4.95	(no stries)
1.000 IMz	E3.62	3%"×2%" 31
1.808 MHz	€3.92	34"×5" 51
1.280 MHz	£3.92	34"×17.0" £1.5
1.5 MHz	₹4.25	Terminal plas E1.50/5
1.8 MHz	£4.25	V-0 OFF tword £1.1
1.8432 MHz	£3.62	DIP brandbaard 62.5
2.000 MRz	£3.62	Suet face cutter 83
2.097152 MHz	€3.23	Pin insertion tool £1.3
2.4578 Imiz	£3.82	1 th most can use 1.1.
2.500 MHz	£3.92	
2.58250 MHz	£3.62	SOLDERCON PINS
3.800 MHz	£3.62	100 50p 1000 £3.9
3.2768 MHz	£3.23	
3.579545 MHz	£1.95	
3.93216 MHz	£1.92	DIL SOCKETS
4.000 994z	£2.90	8/14/16 pis
4.032 MHz	£3.23	10p/12p/13
4.096 MHz	£3.23	18/20/22 pla
4.194304 MHz	£3.23	10p/20p/25
4.433619 MHz	£1.25	24/28/40 pin
4.608 MHz	£3.23	38p /40p /50
4.800 MHz	£3.23	24 pla Taxtool lover ty
4.9152 MMz	£1.23	zoro insertion force ES.S
5.000 MHz	£3.23	
5.0688 NHz	£3.23	EDGE CONNECTORS
5.0000 MMZ	C3.23	EDGE COMMECIONS

C3.23 C3.20 C3.92 C3.92 C3.92 C3.23 C3.23 C3.23 C3.23 C3.22 C3.23 C3.92 C3.92

5.120 MHz
5.105 MHz
5.000 MHz
6.000 MHz

20.1134 MHz

24.0 MHz 26.690 MHz

26,690 MHz 27,0 MHz 27,145 MHz 27,648 MHz 38,6666 MHz 48,000 MHz 100,000 MHz 116,900 MHz

FORE COMMECTORS

99p £2.00 £1.80 £1.20 DL-704E DL-727E/728E DL-747E/750E FHID 500/560

4×0.5" Digits 40 pin Dil. £9.95

## **SWITCH MODE PSUs**



AC 52218 59/10A 62 52218 59/5A 129/1A -129/1A, -59/0.1A 62 52218 59/5A 129/1A -129/1A, -59/0.1A 62 54218 59/10A 129/2A -129/2A -59/0.1A 62 6128.50 AC 52218 5V/10A AC 92218 5V/5A, 12V/1A, —12V/1A, —5V/0.1A

OPEN CARD SWITCH MODE PSU
FULLY ASSEMBLED P.Cs. CARD 197 x 108 x
52mm. Outputs +5V/6A. -5V/0.5A. +12V/
1A. -12V/17ype AC9251

## **UV 140, UV ERASER**



Two easy to use units designed for both the professional and teur UV-prom user

Can erase up to 14 proms.

Special short wave ultraviolet tube.
Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life).
Sliding tray carries proms on conductive foam.

Sliding tray carries proms on conductive foam.
Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
"Mains On" and "Tube On" indicators.
Smart textured case.
Complete instructions supplied.
Supplied complete with mains plug and flex

Model UV141. Price £77.70

Also available without timer as

Model UV140: Price £61.20

#### TEX MICROSYSTEMS "FPROMPT" UV ERASER



A low cost alternative to the above erasers (UV 140 / 141) claimed by the manufacturer to erase up to 32 chips in 15:30 mins. This is the cheapest eraser we have seen. The unit has no timer, power switch or safety interlock switch. The user places up to 32 chips into loose conducting foam in the erasure tray (15 along the base, 8 on each side). The chips are held in place by the UV tube which sits in the tray. (Unlike the UV 140 / 141, no special precautions have been taken to prevent the seepage of UV light, but the manufacturers state that "Incident light from this device is quite safe at distances above 12 inches".) (Dimensions - 325 x 64 x 38mm)

EPROMPT ERASER Price £33

#### MODULAR COMPUTER SYSTEM CARDS

A range of 'International' (114 x 203mm) size cards which may be purchased individually as desired, or to build up a complete system. Further details available on request. All boards are epoxy glass with gold plated edge plug. VDU A, B, G (ser of 3) £27.20 £9.40 MAXD-2 16K of 4116

PRM-2 4K of 5206

PRM-2 4K of 5206

PRM-2 4K of 5206

PRM-2 5406

PRM-

74LS20 74LS21 74LS26 74LS27 74LS28 74LS30 74LS32 74LS33 74LS33

74LS374 74LS375 74LS377 74L 96p 76p E1.70 96p 96p 76p 96p £1.28 E1.70 £3.50 £1.90 £1.90 £1.90 £1.40 £1.42 £1.42 £1.42 £1.45 £1.45 £1.45 £1.22 £1.23 £1.24 £1.24 £1.24 £1.24 £1.24 £1.24 £1.24 £1.24 £1.24 £1.26 £2.29 £2.29 £3 £1.50 74LS 153
74LS 154
74LS 156
74LS 156
74LS 160
74LS 161
74LS 162
74LS 163
74LS 173
74L 74L863 74L873 74LS245 74L8247 46p 41p 74LS378
74LS384
74LS384
74LS380
74LS393
74LS395
74LS396
74LS396
74LS396
74LS447
74LS447
74LS490
74LS669
74LS670 74LS01 74LS74 741.8248 741.8251 741.8251 741.8253 741.8255 741.8256 741.8261 741.8266 741.8267 741.8273 741.8273 741.8283 741.8290 741.8293 741.8293 741.8293 741.8324 741.8325 741.8325 741.8325 741.8327 48p 40p £1.15. £1.18. 43p 88p £1.04. 89p £1.16. £1.18. 44p 70p £1.80. 60p 95p 85p £1.08. £1.73. 74LS76 74LS78 741883 741885 741886 741890 741891 741892 741893 741895 741896 7418107 7418109 90p £1.38 £1.14 75p £2.28 £1.05 £1.05 £1.05 £1.05 £1.05 £1.40 £1.30 £1.30 £1.30 £1.30 £1.30 £1.30 £1.20 £1.30 £1.30 £1.30 £1.30 74LS132 74LS136 74LS136 74LS139 74LS145 74LS147 74LS147

741574

## FLOPPY DISK CONTROLLER BOARD

This is used in conjunction with 'Kemitron' Z80 boards to interface to hwin single density S758' 'floppy disks. It is not available as a bare board, but only built and testicless circuit diagram.

To run CP/M on the system a serial interface (e.g. SIO board) to some sort of VDU or terminal is required, and 32K of RAM (e.g. two MXD2 boards). The M2B-3 board has facilities for power on jump and a 'boot prom to load the CP/M operating system from the disk. Boot PROM (2708).

## T.V. MONITOR P.C.B. for OEM users

This is we assembled P.C.B. size 130 x 190mm, which yee odd to your own 12"/14" black and white C.R.T. (90 days a. 20mm dis. nack), to obtain a T.Y. munitor at modest cast. (Regrettably we cannot supply the C.R.T. at process.)

Preset controls, contract, brightness, etc., are included, and the only injusts needed are 15 volts = 10% AC at 1.5 Amps and 1 Volt pk-pk composite video inject.

63.50
63.50 €33,50

## **KEYBOARD CASES**

## DOT MATRIX PRINTER

#### DAISYWHEEL PRINTER

High quality printer for use with word processing packages running under CP/M, 45 characters per second RS-232 interface. (Check stock position before ordering.) Qume Sprint 5 Model 45/RO £1495.00

#### **FUROCARD 19" CARD FRAME**

Kit at 2 and plates + angles, 2 froat and 2 roar his bara, guide location strips.

Accessories
Cart guides speck of 10]
Earscard Plag (BA way DIM 41612)
Earscard Pla E27.47

## **MICROPROCESSORS**

DYNAMICS MK 4116 18K 200s €2.75 UV ERASABLES
5204 (512 x 8) £9.95
2788 1K x 8 £3.50
2716/2516 2K x 8 single 5v
25.95
26.95 £19.95 £5,95 £9,95 £19,95 £3,25 £3,75 £3,50 £22,30 £4,85 £2,64 0019 6810 (128 × 8 RAM) 68410 (128 × 8 RAM) 8820, 6821 PIA 6845 5204/2708/2518 Programming Service E7.50/E7.50/ E19.80 each prom. (Price does not lactade prom. Wa accept handwrither/types source code — must be besedeclass). 6845 8850 ACIA

SC/MP 11 RAM 1/0 PROM WASHING SERVICE 50p each prom SC/MP II (4MHz) Hrs 8154 Ram I/O €9.40

UV PROM ERASER
UV140 £5
UV141 £7
EPROMPT £61,20 £77,70 £33,00 UNTERFACE 81LS95/6/7/8 1488 (R\$232) 75491 LED driver 75492 2N425 6725/8728 STATICS IM 450mS) 2102-1K x 1 2111-256 x 4 2112-256 x 4 2114/4045-1Kx 4 E1.20 E2.25 E2.25 £1.40 8 x 2114

11.74

CRT Controller: Uarts -5-1013 £4.00 -5-1013A £4.70 -3-1014A £5.60 -3-1075 £5.60

CHAR. GEN. KEYBOARD ENCODER

EMCODER

MK 2302 E15.29

RC-3-2513 [5w Uppercase] C6-90

DM 8678 CAB/BWF E14.27

AY-5-2376 E3-75

FIRMWARE ZMON for ZBO (1 x 2700) E14.95 2K Tiny BASIC for ZBO (2 x 2708) 4K RML res us. E49.50 4K RML RM for SC/RP (4 x 2708) E49.95

| IK Various, her SC/MP | 1x 724.95 | IK Various, her SC/MP | 1x 724.95 | Closscriptive leaflet available on above, find SW4, 5] | IK Closter Junior | 1x2708| | IN Closter Junior | 1x270

UHF MODULATORS
UNTITL ED Virios medislater.
T.V. game or cheap computer type
2.2.80
UN1231 E38 Wide handwidth.
Camputer VDU type, par. 422,00
UN1231 E38 Wide handwidth.
Camputer VDU type.
UN1232 E38 Wide handwidth.
Camputer VDU type.
UN1232 E38 Cambined wide
handwidth virios medislater orth
intercarrier sound. Nigh price.
EN.25
VOLTABE REGULATORS

MOSTAGE REGULATORS

75p E1.06 97p E1.06 E5.61

VOLTAGE CONVERTER

# SLR ELECTRONICS

The humble 35 mm SLR camera has changed a great deal in recent

years. Ian Graham investigates one aspect of electronics in photography, the development of camera

electronics.

he point and shoot' phenomenon was for many years associated with cheaper non-reflex cameras, designed to be idiotproof, with ease of film loading and exposure in mind. Now, however, most manufacturers have at least one automatic SLR(single lens reflex) model in their range.

The 35 mm SLR is the most popular and versatile camera type in use today. It's versatile, because a typical SLR offers a range of interchangeable lenses and matched add-ons — motor-drive, power winder, electronic flash, bulk film pack, databack, etc. Further, because the viewfinder shows the image seen through the lens, the effect of any lens can be seen immediately — the photographer sees what the film 'sees'.

## **Meter Manual**

In a manual TTL (through the lens) meter, light passes through the lens and is reflected by a mirror up to a prism at the top of the camera and out through the viewfinder eyepiece. Photocells mounted on the prism measure the brightness of the incoming light. Film speed and, typically, shutter speed are preset by the photographer. Adjusting the aperture of the lens causes a needle visible in the viewfinder to move towards a + (over exposure) or a - (under exposure). When the needle is central, the film will be exposed correctly when the shutter release is pressed.

However, this system cannot be used to operate an automatic system. It's easy to see why. You switch on the meter and compose your picture. The automatic meter selects the appropriate shutter speed (in an aperture priority system). When you press the shutter release, the mirror up, it is not seeing the view through the lens any more. The end result is a wrongly exposed film. The answer is to provide some means of storing or remembering the meter measurement during the exposure. One method involves the use of a capacitor to store the meter



control voltage.

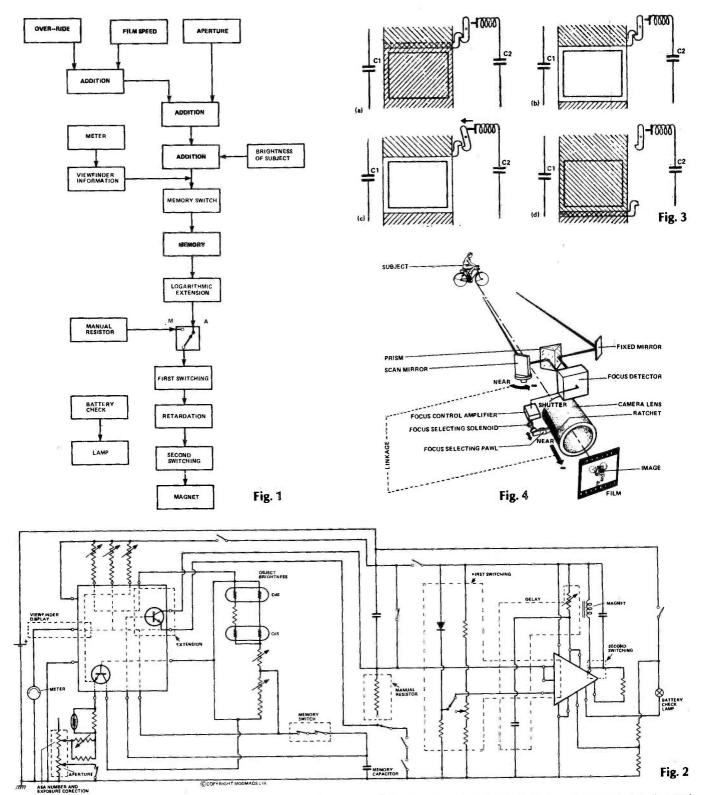


Fig. 1 Block diagram of the manual/automatic exposure control employed by the Minolta XE-1.

Fig. 2 Circuit diagram of the exposure control system used by the Minolta XE-1.

Fig. 3 Mamiya's moving coil electronic shutter consumes a tenth the power of electromagnetic systems. In addition, the consumption remains constant whatever the shutter speed. Up to 100,000 exposures can be made with one 6 V silver oxide cell. (a) The shutter is closed. The moving coil energising capacitor (C2) is normally charged. Current is not flowing. (b) The first blind moves, opening the shutter when the shutter release button is pressed. The exposure time control capacitor (C1) begins to charge. The latch holds back the second

blind. The charge time of C1 is determined by the shutter speed. (c) The instant of exposure. When C1 reaches a preset voltage, C2 discharges, energising the moving coil. This releases the second blind. (d) The second shutter blind moves, closing the shutter. C2 charges in a very short time, consuming very little power—ready for the next exposure.

Fig. 4 Konica developed the first self-focusing camera — the C35 AF. Light from the subject passes through two windows on the front of the camera on to two mirrors, one fixed and one moveable. When the shutter release is pressed, the moveable mirror turns until the two images coincide on the focus detector. A focusing control signal is then used to focus the lens correctly — all within 80 ms.

## **Direct Measurement**

The Olympus OM-2 uses TTL metering, but its SBC (Silicon Blue Cell) sensors face the film, and so they measure the light actually reaching the film emulsion during the exposure. This makes the memory device used in other cameras obsolete. The OM-2's system doesn't have to remember its light reading, because the reading is taken during the exposure itself. Its advantage is that it can compensate for changes in light levels after the beginning of the exposure. By eliminating a memory device power consumption is reduced.

Also, in flash photography, the sensors can follow the flash intensity as it increases in fractions of 1/10,000 S and cut off the camera's flash unit when the correct exposure is reached. Of

course, a dedicated flash system is needed.

The OM-2 manages to combine centre and average exposure weighting. At high shutter speeds (over 1/60 S) the light level reading is taken from the shutter curtain. Its reflective coating pattern produces a centre-weighted reading. At lower speeds (below 1/15 S) the measurement is made directly from the whole film surface.

## Logarithms

The shutter speed settings follow the simple geometric progression 1 S, ½ S, ¼ S, ... 1/250 S, 1/500S, 1/1000 S. If, for ease of calculation, we start with a meter circuit output of 0V1 and double it for each successive stop on the shutter speed dial, by the time we reach the last speed setting, the output voltage would be:

$$0V1 \times 2^{10} = 102V4$$

Because of the size, weight and expense of batteries, no camera can use a 100 V supply.

The answer is logarithmic compression of the voltage steps, so that the maximum power requirement is given by:

$$0V1 \times 10 = 1 V$$

In practice, most of the cameras available now derive their supply requirements from a single 6  $\,\mathrm{V}\,$  silver oxide cell or two 1V5 silver oxide cells.

## Metering

One exception is the Konica FS-1, powered by four alkaline-manganese penlight cells. However, the FS-1 is no ordinary camera. It looks much the same as any other, except for the lack of a wind-on lever. It doesn't need one — it has its own built-in power winder, yet the combination is smaller and much lighter than a conventional SLR plus add-on winder.

The four size AA cells power the winder and camera electronics. The obvious advantage is that the photographer need carry only one spare set of batteries. Normally camera and winder batteries are not interchangeable.

## **Processing**

The FS-1 employs a digital CPU (Central Processing Unit) together with support ICs to take care of light measurement, exposure calculation and motor control to provide total electronic control. The tiny CPU manages to pack in more than 1100 gates and 250 transistors, impossible to fit inside a camera just a few years ago.

Information from the Gallium Arsenide Phosphide photocell about the light level is compared with preset values for film speed and shutter speed to compute the appropriate aperture (f/stop). This analogue value is converted to a digital input for the f/stop register. The aperture information is also displayed in the viewfinder.

The Pentax M.E. Super has a wind-on lever, but no shutter

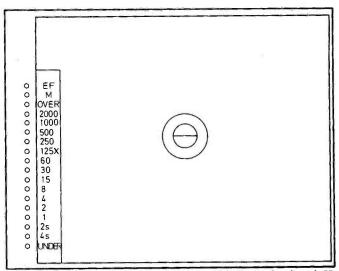


Fig. 5 The Pentax ME Super displays data by means of a three-colour line of LEDs. At 1/60 S and above, the speed selected by the camera will turn on the appropriate green LED. If you see green, it's OK to shoot. If the camera selects 1/30 S or below, the LED lit is yellow, warning you that, although the exposure is correct, there is a danger of blur due to camera shake. At each end of the scale there is a red LED to indicate under or over exposure. If exposure compensation is being used, a red EF LED comes on. Manual operation is similarly shown (green LED).

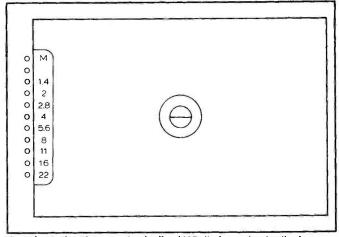


Fig. 6 The Konica FS-1 uses a simple all-red LED display to give details of aperture selected, under/over exposure, battery check, flash ready and manual mode.

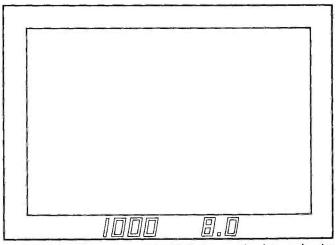


Fig. 7 The Canon A-1's alphanumeric LED display gives the photographer data on just about all the camera's functions — aperture, shutter speed, under/over exposure, flash ready, manual mode, B setting, out of range and operating error. There's even an automatic brightness control to match the display brightness to that of the image in the viewfinder.

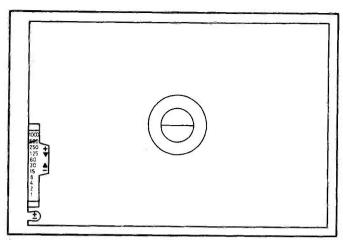


Fig. 8 The Olympus OM-2's bright viewfinder display shows the shutter speed by means of a needle on a scale. Information about under/over exposure, flash ready, exposure compensation, etc is also shown. When you switch to manual, the shutter speed scale disappears and you are left with the conventional needle display described earlier. When the camera is switched off, the viewfinder display disappears completely.

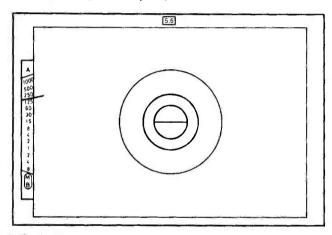


Fig.9 Like the OM-2, the Nikon FE's display of shutter speed is a needle-onscale type. The Silicon Photodiodes used in the FE are filtered to match the spectral response of the human eye.

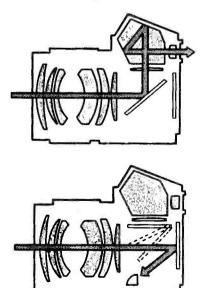


Fig. 10 With the mirror in the down position (top), the Nikon FE looks much the same as any other camera, but when the mirror flips up (above) a light reading is taken directly from the film plane.

speed dial. In manual mode, shutter speeds are selected by pressing one of two buttons on the top of the camera — one causes the shutter speed selected to increase one LED at a time, the other causes it to decrease, until the desired speed is reached.

## Multi-mode

Up to now I have been describing cameras using either shutter speed priroity or aperture priority. But, it is possible to have both. In fact, the Canon A-1 has no less than five automatic programmes:

- 1. Shutter speed priority useful for action photography.
- 2. Aperture priority useful if you know that your subject is not going to get up and run away.
- 3. Stopped down with the meter reading the light entering the lens, accessories which don't couple directly to the camera electronics can be used.
- 4. Programmed the camera decides the shutter speed and aperture.
- 5. Flash using a flashgun which couples directly to the camera electronics, automatic flash photography is possible.

The viewfinder alphanumeric LED display gives a complete run-down on just about everything. The A-1's self-timer allows selection of a 2 S or 10 S delay. As the timer is completely electronic, it can be cancelled at the touch of a button, unlike most mechanical self-timers.

The A-1 and the Nikon FE (an aperture priority model) both have a memory lock facility. Suppose you are photographing your loved one (or wife) against a bright window. Click — and there you have an interesting silhouette. The meter has exposed the film for the bright window, not for the subject.

With the A-1 and FE, you can take a correct exposure reading from the subject's face, turn on the memory lock and take the picture. The meter will 'remember' the correct exposure until the lock is turned off.

## **Screen Data**

The information displayed in the viewfinder and the method of display varies enormously from camera to camera. Some give full alphanumeric data on everything. Others rely on a very simple three-LED system — red, green, red meaning under-exposed, correct and over-exposed (manual TTL system).

Typically, slight pressure on the shutter release button switches the meter on. Some cameras still use an on/off switch mounted on the camera body. If yours does, remember to switch it off! The first-pressure type is foolproof, even with an absent-minded photographer to contend with. Table 1 is a quick guide to a few popular automatic mode 35 mm SLRs, giving details of the camera's electronic systems. It is by no means exhaustive and is not intended to be used as a buyers' guide.

The space available for components and PCBs inside the camera is severely limited. Nowadays the circuitry is commonly mounted on and in flexible, paper-thin, plastic film PCBs, which can be wrapped round the familiar shape of the major features of the camera under the thin metal skin. The flexible tracks greatly reduce the number of flying leads and solder joints necessary. The fewer connections, the less chance there is of a broken wire or a dry joint.

## Finally . . .

The microprocessor is only now beginning to make an impression on amateur photography, so the camera is probably at the simple four-function pocket calculator stage. Look what has happened to calculators in a very few years — LCD displays, programmable, sound effects, talking displays, etc. It will be interesting to watch how the designers transfer this kind of technology to cameras.

		ior		Table. 1 A comparison of SLRs with automatic pr		used by some popular 35 mn
Carneto	Model	Viewinder Information	Studies	, Auto transi	e weet	<i>Qonet</i>
Canon	A-1	A-LED Aperture Shutter Speed Manual Override Flash Ready B Setting Over/Under Exposure Out of Range Operating Error	EHC	Aperture Priority Shutter priority Pre-Programmed Stopped Down Flash	TTL SPL) Centre Weighted Full aperture	6 V Silver Oxide Cell
Fujica	AX-5	LED Aperture Exposure Mode Over/Under Exposure Battery Check	EHC	Aperture Priority Shutter Priority Pre-Programmed Stopped Down Flash	TTL SPD Centre-Weighted Full Aperture	6 V Silver Oxide Cell
Konica	FS-1	LED Aperture Flash Ready Over/Under Exposure Manual Override Automatic Mode Battery Check	EVM	Sharrer Priority	TTL GaAsP Centre Weighted Full Aperture	Four Alkaline- Manganese Cells
Minolta	XG9		FHC .	Aperture Priority	CdS Centre Weighted Full Aperture	Two 1V5 Silver Oxide Cells
Nikon	FE.	Shutter Speed Scale Aperture/Meter Needle	ĖVM	Aperture Priority	TTÎ SPD Centre-Weighted Full Aperture	Two 1V5 Silver Oxide Cells
Olympus	OM-2N	Exposure Index (Manual) Shutter Speed (Auto)	EHÇ	Aperture Priority	TTL ST SPD: 1- CdS Centre-Weighted Tull Aperture	Two 1V5 Silver Oxide Cells
Pentax	ME Super	Aperture Shutter Speeds Exposure LEDs Over/Under Exposure Flash Ready	EVM	Aperture Priority	TTL GPD Centre-Weighted Full Aperture	Two 1V5 Silver Oxide Cells
P			KE	Y:		
		Viewfinder Information Shutter	E — el H — h V — vo C — cl	ectronic orizontal ertical loth	-D	
		Meter	SPD — GaAsP CdS —	metal Through The Lens Silicon Photodiode — Gallium Arsenic Cadmium Sulphide Gallium Photodio	le Phosphide e	

#### **IONISER KIT**

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels like fresh ocean air, pure crisp and wonderfully refreshing.

All parts P.C.B. and full instructions £10. A suitable case including front panel, neon switch, etc. Available at £8 extra.

#### H.E. KITS

Car Booster ZD50 £18; Multi Option Siren ZD36 £10.50; Car Equaliser ZD52 £13.30; Envelope Generator ZD20 £11.79; R/C Speed Controller ZD3 £9.60; White Noise Effects Unit ZD18 £16.85; Track Cleaner ZD12 £7.75; Drill Speed Controller ZD21 £7.

All Hobby Kits supplied cases except ZD3. All kits contain components as specified plus Texas I.C. sockets where required. Also connecting wire. Special introductory offer to E.T.I. readers, a pack of nuts, bolts, washers, self-cutting, self-tapping screws supplied with each kit.

## **SPECIAL OFFERS**

Texas/I.T.T. 1N4148, 100 for £1.50. Fairchild FLV ISO Red '2 LEDs 10 for £1; 100 for £7.50. Mullard Computer Electrolytics S/T 21,000 U.F. 40V £3.50 £1.50 Daly Electrolytic Capacitors 2000 µ F. 100V 10 for **50p** I.T.T. BCY 72 Transistors leads pre-formed Varicap Tuners ELC1042 £6.00 Varicap Tuner ELC 1043 £6.00 Philips Scope Tube 5" CV2191/DG-13-2 £10.00 Thorn-Sylvannia Scope Tube 5" SE5J £17.50 (Callers only) Toshiba 12" TV Tube 310GAB4 £12.50 (Callers only)

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra orders. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of Kits.

## T. POWELL

306 ST. PAUL'S ROAD HIGHBURY CORNER, LONDON, N.1. TELEPHONE: 01-226 1489

Access / Visa accepted Shop hours: Mon. to Fri. 9-5.30. Sat. 9-4.30

# TELEVISION SOUND IS GOOD!

Yes it's true—but you'll need to listen through a Minim Television Sound Tuner to be convinced. Music, wildlife, even the news suddenly comes to life when you can hear all the detail that you expect from High Fidelity equipment.

Connect the Minim Television Sound Tuner to the amplifier or music centre or listen directly on headphones so as not to disturb others.

Further information will only cost you 12p — stamp out poor television sound!

Name

Minim Audio Limited, Lent Rise Road, Burnham, Slough SL1 7NY. Tel: Burnham 63724

## **Minim Audio**

make a note of our name!

AIN	-c65
TRAIN	CCE
-0 3°	Electronics
Television	ICS h
in Radio,	helped thousa of ambitious per

helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics – now it can be your turn.
Whether you are a newcomer to the field or already working in the industry. ICS can provide you with the specialised training so essential

Personal Tuition and Guaranteed Success

The expert and personel guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

#### **City and Guilds Certificates**

to success.

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians Radio, T.V. Electronics Technicians Radio Amateurs Electrical Installation Work

#### Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

#### Other Career Courses

A wide range of other technical and professional courses are available including GCE.

			ï
West -	To ICS, Der London SW	ot. Z263, Intert /8 4UU	ex
Name Address _		· · · · · · · · · · · · · · · · · · ·	

ICS

To ICS, Dept. 265C, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

Age .



'MICRON' may sound small - but we all know that it's much larger than an atom!

The un-beatable features of Microtan 65 and Tanex have been brought together to give you Micron, a ready built and tested computer of outstanding value. Fully supported by comprehensive documentation, Micron represents an ideal starting point in personal computing. We've taken a full O.E.M. licence for Microsoft Basic, which means that you'll have the support of the most popular Basic available, (as used on PET, APPLE, TANDY etc.). If you want to expand Micron there's no problem, just move into the system rack and choose from the range of Microtan modules. Read the information, study what the magazines have to say about us and compare what we have to offer with other systems, then we feel sure that you'll be convinced that we've produced an excellent product.

- FULLY BUILT, TESTED AND CASED.
- 6502 BASED MICROCOMPUTER.
- O VDU ALPHA NUMERIC DISPLAY.
- 8K RAM.
- 32 PARALLEL I/O LINES.
- 2 TTL SERIAL I/O LINES.
- ●1 SERIAL I/O PORT WITH RS232/20mA LOOP, AND 16 PROGRAMMABLE BAUD RATES.
- 300 / 2400 BAUD FILENAMED CASS. INTERFACE.
- DATA BUS BUFFERING.
- MEMORY MAPPING CONTROL.
- 71 KEY ASCII KEYBOARD, INCLUDING NUMERIC KEYPAD.
- POWER SUPPLY INCLUDED.


# TANGERINE

Forehill Works
Forehill Ely Cambs England Tel: (0353)3633

#### SOFTWARE

- 10K EXTENDED MICROSOFT BASIC.
- ALL THE USUAL BASIC COMMANDS.
- INTEGER AND REAL NUMBERS.
- INTEGER AND REAL ARRAYS.
- INTRINSIC FUNCTIONS: ABS, INT, RND SGN, SIN, SQR, TAB, USR, ATN, COS, EXP, LOG, TAN.
- USER DEFINED FUNCTIONS.
- READ AND DATA STATEMENTS.
- DUMP AND LOAD PROGRAMS.
- PROGRAM EDITING COMMAND.
- STRING FUNCTION FOR TEXT I/O.
- BASIC CAN CALL MACHINE CODE SUB-ROUTINE.
- USER MACHINE CODE INTERRUPT HAND-LER INTERFACES WITH BASIC.
- O XBUG.
- DATA CASSETTE FILE HANDLING IN BASIC

## microtan 65

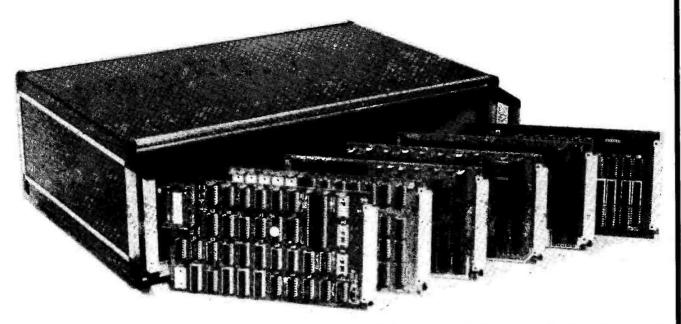

The Microtan system is rapidly becoming accepted as the ultimate approach to personal computing. Start with Microtan 65, a 6502 based single board computer, and expand to a powerful system in simple and in-expensive stages. The Microtan system is a concept and not an afterthought, this means expansion is easy and very efficient! Unlike many other systems, you'll find it difficult to outgrow Microtan, and you won't be wasting your money on a product that will only last you a few months! When you are ready to expand, Tanex is waiting. The features offered by Tanex are tremendous, and you can start into them for just £49.45! Cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, memory mapping and a further 1K of RAM are standard. From thereon expansion is simple, just plug in extra integrated circuits to get yourself 8K of RAM, a further 16 I/O lines and two more counter timers a serial I/O line with RS232/20mA loop and full modem control, XBUG - a firmware package containing cassette file handling routines, plus a line-by-line assembler (translator) and dis-assembler, PLUS 10K EXTENDED MICROSOFT BASIC, a suped-up version of the Basic as used by major manufacturers such as Apple, Tandy and Nascom, NO OTHER LOW COST MICROCOMPUTER OFFERS YOU THIS SUPERB PACKAGE. O.K. so you want more memory, try Tanram for size! Upto 40K bytes on one board starting for as little as £50.60. RAM freaks will be pleased to hear that our system mother board offers page memory logic which will support 277K Bytes, satisfied? To house these beautiful modules you can choose between our mini-rack (as used on Micron), which accepts Microtan and Tanex, or our system rack pictured above. The system rack will support 12 modules. What are these extra modules? Well for starters there's a couple of I/O modules, parallel and serial offering upto 128 I/O lines organised as 16 8 bit ports and 8 serial I/O ports respectively. Shortly we'll be introducing high definition (256x256) colour graphics, A to D and D to A modules, IEEE 488 Bus interface, a PROM programmer, disc controller and TANDOS - a 6502 CPM system. So there's plenty to keep you busy. Send for more details, and find out how you can get started ALL PRICES QUOTED INCLUDE V.A.T. for just £79.35!

## AIM 65, KIM 1, SIM 1 USERS- READ ON!

We have produced a T.V. interface module which simply connects to the expansion socket of your computer and produces a display of 16 rows by 40 characters! Of even more interest will be our Buffer module, which allows you to expand into our system rack, giving you access to the full range of Microtan modules.

3 100		
Please underline the	information	required.
AIM T.V. INTERFACE.	MICROTAN	SYSTEM
NAME:	**	
ADDRESS:	Section 1988	<del>or and the second of the seco</del>
PLEASE ENCLOSE 12p S	STAMP. THANK	YOU.
TELMOL LINGLOSE 120 3	TARG . CHANK	100.

# TECH TIPS

## **Click Eliminator Auto Threshold**


#### S.P. Cobbold, Cambridge

This circuit is designed to increase the versatility of the 'ETI Click Eliminator'. It automatically adjusts the threshold level for greater sensitivity during extended quiet passages, while

reducing the sensitivity during peak transient levels.

The left and right channels are added and amplified by the

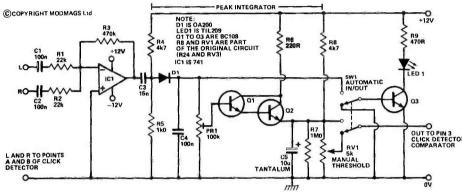operational amplifier IC1, which largely cancels the antiphase signals of the click. C1 and C2 decouple any DC offset voltage from the input amplifiers. D1 and C4 hold the peak level of the higher frequency audio signals and pass this to C5 through Q1 and Q2, giving a rise time of



approximately 3 mS and a hold time of the order of 5 S. No buffer is required for C5 as the comparator of the click detection circuit has a JFET input. R4 and R5 bias the peak integrating section to give a minimum of approximately 0V5 on C5 when the preset PR1 is adjusted for optimum click detection. This adjustment is best performed using a badly scratched record (borrow a friend's if necessary) and setting PR1 to the point where the loudest click is just removed from a section of loud music.

Q3 and LED1 give a visual indication of operation by changing from dull to bright with the music signal when switched to automatic.

It can be seen from the rise and hold times of the peak integrator that large transients in the middle of a quiet passage (eg a cymbal crash) may cause a single inappropriate click detection before the integrator charges up. Conversely, a series of clicks in very rapid sucession may be ignored. However, I have found these two faults far more acceptable than the severe distortion caused by repeated spurious click detection when unexpectedly high transient levels pass the manually set threshold.

## **Shop Doorbell**

## R. Gamester, Chesham

This unit was designed to give a remote indication of a shop door opening. The bell rings once as the door opens and a flashing LED indicates that the door is open. To prevent the unit being repeatedly triggered, a time


delay operates from the closing of the door for a period of 20-30 S, during which time the LED is constantly illuminated.

When the door opens, C2 charges quickly through D1 and IC2b turns Q2 on. The oscillator (IC2d) is running and interrupts the LED by switching Q1 on

When the door is closed the

oscillator is stopped, leaving Q1 on. This gives a constant indication until C2 discharges through R3, PR1 and R4.

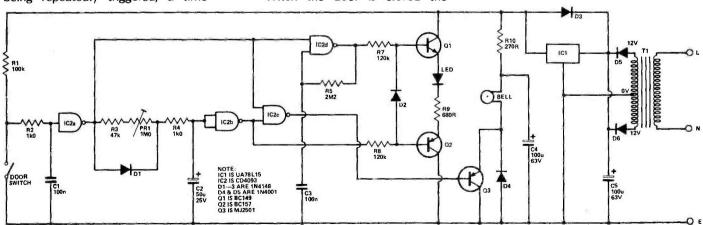The bell is a standard 3 V vibrator type and is powered by C4, this being discharged through the armature by Q3. IC2c generates the drive pulse, its duration being the charge time of C2.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright, Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

# Simple Combination Lock

## M.D. Chapman, Sale

Although this circuit uses surprisingly few components, the unit provides up to nine code elements and a billion-toone chance of random operation.


The first nine outputs of the decade counter (IC1) are fed via the diode OR gates (one for every different number used in the code) to the selected switches. As shown on the circuit diagram the combination sequence is 123412341. However, both the numbers and the sequence can be

modified by rewiring the output diodes (D1-9) to different switches. To change the number of active code switches (ie. numbers 1234 in this case), you will have to either remove or add to the number of diode OR gates.

Operation is very simple. As the counter sequences through its outputs 0-9 it provides a logic 1 to one of the four diode OR gates, thereby making one of the active switches live. When this live switch is pressed it provides the clock pulse to increment the counter one step. This, then, provides a logic 1 to the next OR gate, making the next digit in the code live, which in turn, when pressed, provides the next clock pulse and so on until the counter reaches its tenth output. Once output

nine goes high it turns on Q1, therebyswitching the relay and desired load. Since only one of the outputs is high at any one time, only one of the keys will move the counter and, should any dud key (ie. keys 567890 in this case) be pressed, this will reset the counter to zero, making guesswork ineffectual.

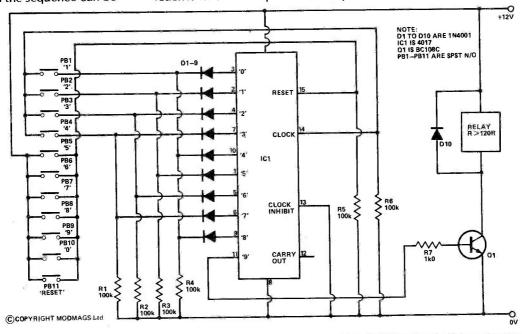When selecting the code sequence, it is worth remembering that in order to maintain a nine element code the effect of switch bounce should be minimised by avoiding the use of any number consecutively, ie. codes such 123343222. However, if necessary, the clock input can be debounced to allow such a sequence.



## **5 V TTL Supply**


#### D. McIntyre, Camberley

The circuit shown was designed to eliminate expensive accidents with TTL caused by inadvertently turning up the knob on the (heavily smoothed) train controller normally used as a bench PSU. It is provided with crowbar protection just in case, though.

Power Darlington Q3 is biased to just over 5 V by ZD1 and Q2 (this does not have to be a Darlington, although the output will not be as stable if it is not). Any change in output voltage is sensed by Q2 and it adjusts ZD1's reference level accordingly. Any change in input voltage is adjusted by normal zener operation. The output level may be set using PR2 and it will

remain fairly stable ( $\pm 0V5$ ) for a change in input from 8 V to 12 V. If, for some reason, the output voltage should rise above the preset level to, say, 6 V, SCR1 will be triggered and the

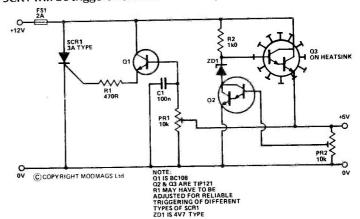fuse will blow. This trigger level may be set by PR1. C1 reduces the (extreme) sensitivity to noise. SCR1 is not critical, but it should be capable of sinking the required current.




## Accenting Metronome

P. Hill, London

The circuit consists of a clock generator determining the beat and a monostable producing the accent.

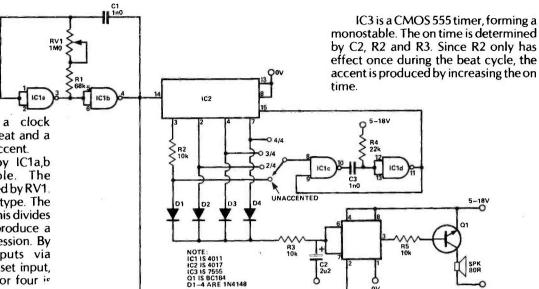
The clock is formed by IC1a,b configured as an astable. The frequency or tempo is adjusted by RV1. C1 must be a non-polarised type. The clock pulses are fed to IC2. This divides and decodes the clock to produce a high at each output in succession. By feeding one of the outputs via monostable IC1c,d to the reset input, division by one, two, three or four is possible, thus selecting the beat.



## **Contact Breaker**
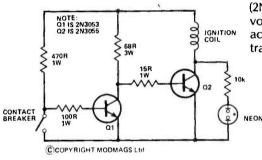
## E. P. Young, Plymouth

The contact breaker carries a mere 25mAwhen the ignition coil is charging up for the induction of high voltage to produce a spark in the spark plug. Further, without the induced EMF across the CB from the primary winding of the ignition coil, the life of the CB will be greatly increased.



A cheaper power transistor (2N3055) is chosen instead of the high voltage type. A neon bulb is used across collector-emitter to protect the transistor from a high induced EMF.

## Simple VCR


#### S. Draper, Sudbrooke

This circuit is a simple voltage-controlled resistor, which may be used in a variety of applications (it was originally designed as a portion of a voltage-controlled envelope generator). It has two big advantages over the often-used FET type circuit—a large control range (10,000:1) and a predictable voltage-current characteristic.

The voltage differential between terminals A and B is amplified and converted to a current by OTA IC1, the gain of which is controlled by the current flowing into it at pin 5. The resulting current is fed to current multiplier IC2, which multiplies it by a factor of R<sub>X</sub>/R<sub>y</sub> and feeds it to terminal B. This means that the current flowing into or out of terminal B is proportional to the voltage difference between terminals A and B and to the control current generated by voltage-current converter IC3.


The formula for the circuit resistance is as follows:
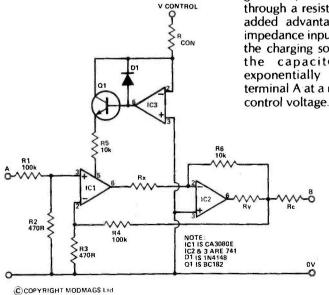
$$R = \frac{200R_{CON}R_{Y}}{19.2V_{CON}R_{X}} + Rc$$



This means that with a constant applied voltage, the output current will be proportional to the control voltage and the effective resistance is inversly proportional to same.

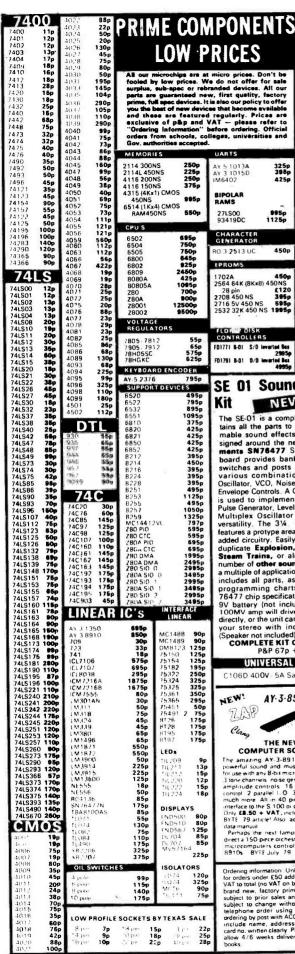In circuits such as an envelope generator, where a capacitor is charged through a resistor, this circuit has the added advantage of having a high impedance input and so does not load the charging source. In this example, the capacitor would charge exponentially to the voltage on terminal A at a rate determined by the control voltage.



PRIME COMPONENTS NEW, LOW, LOW PRICES ON MEMORIES

MEMORIES	1+	50+		prime, full spec. s	nd fully	guerant	eed!				
2114 L 450 NS	225p	200p	175p	EPROMS	1+	50+	100+	LINEARS	1+	50 +	100+
2114 L 300 NS	250p	225p	195p	2708 450 NS	395p	375p	350p	ICL 7106 CPL	575p	625p	475
4116 150 NS	375p	350p	325p	2716 Single 5V				LCD 106 31/2-digit			
4116 200 NS Ceramic 6514 (TC 5514P) 1kx4		225p	195p		595p	550p	495p	LCO Display NE 555P	18p	625p	475; 16;
CMOS RAM 450NS	550p	625p	495p			1695p	1495p		33p	30p	28

NEW EXCITING, ENTERTAINING SOFTWARE FOR THE APPLE II and APPLE II PLUSII

ASTEROIDS IN SPACE!!!!

If you liked 'Inveders' you'll love ASTEROIDS IN SPACE!!!!

spaceship is travelling in the middle of a shower of asteroids. Blast the asteroids with lasers, but beware — BIG ASTEROIDS FRAGMENT INTO SMALL ASTEROIDS I The Apple game pout to rotate your spaceship, lire its laser gun, and give it thrust to propel it through endless space. From time to time, soc, you'll encounter an allen spaceship whose mission is to DESTROY YOU, so you'd better destroy it first! High resolution graphics and sound effects add to the arcade-like excitement this program generates.

RUNS ON ANY APPLE II WITH AT LEAST 32K AND ONE DISK DRIVE! ON DISKETTE ONLY

## FROM INTERSIL ICL 7660 Voltage Converter

The Intersil ICL7660 is a monolithic MAXCOMOS power supply circuit which offers unique performance advantages over previously available devices. The ICL766D performs the complete supply voltage conversion from positive to negative for an input range of +1,5V to +1

FEATURES

All are identical and equivalent types - we reserve the right to

All are identical and equiversity substitute any make. 256 bit (32x8) 16-pin tri-state MB7051 / 27509 / 7603 / 5600 / 6331 / 745288 / 825123 256 bit (32x8) 16-pin open collector 3959 MB7056 / 27508 / 7602 / 5600 / 6330 / 745188 / 82523 3959 MB7052 / 74S287 / T8P14S10 / 93427 / 82S129 / 7611 8301

Coative Outputs
Supplies
Inexpensive Negative Supplies
Oate Acquisition Systems

Oate Acquisition Systems 1K (256x4) 16-pin open collector MB7057 / 74S387 / TBP14SA10 / 93417 / 82S126 / 7610 / 6300 395p 6300 2K (512x4) 16-pin tri-state MB7053 / 93446 / B2S131 / 7621 / 6306 2K (512x4) 16-pin open collector ' MB7058 / 93436 / 82S10 / 7620 / 6305 495 4950 MB7058 / 93436 / 82510 / 7620 / 6305 4K (1024x4) 18-pin tri-state MB7122 / 745476 / 93453 / 825137 / 7643 / 6353 / 27533 / 3625 / 5626

## SE 01 Sound Effects NEW

995p 1125p

450p

The SE-01 is a complete kit that con-The St-O1 is a complete kit that con-nains all the parts to built a program-mable sound effects generator. De-signed around the new Texas Intru-ments SN76477 Sound Chip, the board provides banks of MINI DIP board provides banks of MINI Dis-switches and posts to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator Level Comparator and Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3½ x 3 PC Board features a protype area to allow for user added circuitry. Easily programmed to duplicate Explosion, Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100MV amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results!
(Speaker not included).

COMPLETE KIT ONLY £14.99

P&P 67p + VA

#### UNIVERSAL SCR

C106D 400V 5A Sale

30p



#### COMPUTER SOUND CHIP

COMPUTER SOUND CHIP

The mazing AV.3-8910 is a lantastically powerful sound and music generator perfect for use with any Bibli micro processor. Contains 3 tone channels noise generator 3 channels of amplitude control 2 patielle 1.0 3 D A conveners plus much more. Alt in 40 pm DIP Super-easy to interface to the 5 100 or other Busses. Only £8.50 + VAT, including FREF reprint of BYTE 79 article 1/los and 47 25 for 60-page date manual.

Perhaps the next famous composer will not direct a 150 perce orchestra but rather a tito of microcomputers controlling a bank of AY 3 8910s. BYTE July 79

Ordering information. Unless otherwise stated for orders under £50 add 50p p&p. Add 15% VA Grand to VAT on books, All devices to VAT or the VAT or books, All devices to VAT or the VAT or books, All devices subject to change without notice. Minimum letephone order using ACCESS is £10. If ordering by post with ACCESS, include name, address and card no, written cleanty. Please allow 4/6 weeks delivery on books.

## NEW

#### SUPER MUSIC MACHINE KIT!

AT LAST — an offereible kit that can be PROGRAMMED TO PLAY ANY 2006 OR SROUP OF SUNGS! instead of a sightmere of numerous ICs and special separative Bapeter Rolls. The SUPER NUMER CANCENT CASE S SPECIAL MASK PROGRAMMED COMPUTER CHIP are CHOS again and the supposter oranged FPROM. The 2706-2718 paris about SCI Visionies and rolling plated and acressed PC based on all AL composents occupy the PROMISE AND ADMINISTRATION OF THE PROGRAMMENT OF THE PRO

Fig. 17096.5:
\*\*Rapic kit contains 25 shart bases in the main C/
\*\*Plan before a stirred 1008 for up to 1,000 18096 NOTES per ROBM (ROM is not included)
\*\*Plan before a stirred 1008 for up to 1,000 18096 NOTES per ROBM (ROM is not included)
\*\*Operation to 120 AC or 120 DC @ 2000ab. (Using mits at 270 C and with optimate) ROM requires 8V bias battery, not included.
\*\*Town that also be power will drive to be it is then penaleurs are bern apeators (not included).
\*\*PLET TIME previous steps sequentially through all times.
\*\*Times antices can be write imper solected or beard is destinated to take 100 p willches.
\*\*TIMES AUTHOR OF BOUTEMP or as to adoptable.
\*\*STEP-INC VIOLINE SEQUENCES can be authorized reportions of taxes address to provide for multiple deerhall applications.
\*\*STEP-INC TIME PROVINCES Can be authorized reportions of taxes address to provide for multiple deerhall applications.
\*\*STEP-INC TIME PROVINCES Can be authorized reportions of taxes address to provide for multiple deerhall applications.
\*\*STEP-INC TIME PROVINCES CAN BOOK with popular and classical times readily available. Sand SAE far list and prices.
\*\*OMNY EVE.75 for basic kit (ples pdg 60p)

## STEREO! S100 SOUND **COMPUTER BOARD!**

At last, an S-100 Board that unleashes the full power of two unbelievable General Instruments AY-3-8910 NMOS Computer sound ICs. Allows you, under total computer control, to generate an infinite number of special effects for games or any other program. Sounds can be called in BASIC, ASSEMBLY LANGUAGE, etc.

KIT FEATURES

KIT FEATURES

\* Two GI Sound computer ICs (AY3-8910)

\* Four parallel I/O ports on Board

\* Uses on Board audio Amps or your STEREO

\* On Board proto typing are and an are an encluded

\* PC Board is stoldermasked, silk screened with gold contacts

\* Easy, quick and fun to build, with full instructions

\* Uses Programmed I/O for maximum system flexibility

\* Both BASIC and ASSEMBLY language programming examples are included

COMPLETE KIT ... ONLY ESS-96, includes 60 page data Manual

BARE BOARD ... ONLY EZS-00, includes 60 page data Manual

AY3-3-810 chip special price with purchase of BARE BOARD (2 chips) £15. SOFTWARE: SCL is now available! Our Sound Command Language makes writing Sound Effects programs a SNAPI. SCL also includes routines for Register-Examine-Modify, Memory-Examine-Modify and Play-Memory. SCL is available on CP/M compatible Diskette or 2708/2716 Diskette - £19.95, 2708 — £14.96, 2716 — £24.95. Diskette includes the source. EPROMS are ORG at E000H.

MEVA 6809 S-100 SINGLE-BOARD COMPUTER

## Meets IEEE S-100 Standard!

## RS - 232 Handshake rtS — 232 Handshakel Selectable BAUD Rates! Manual includes: 11" × 7" Schematic, Parts List, User Notes, Software Listings and MORE!

Wises Motorola's Powerful MC6809 CPUI \*
4K, 8K, 16K ROM! \*

ACIA, PIA, 8080 Simulated I/O!

Bareboard only £49! (plus £1 p&p) CPU (6809) £24.50!

ADSMON: Monitor (2716) £251 COMPLETE BOARD ASSEMBLED AND TESTED, ONLY £250! (plus £2 p&p)

#### Autoranging, Auto Unit Display, 3½-digit LCD DMM for ONLY £39.95 inc. VAT!

The nationally advertised 6200, giving 200mA AC / DC current measurement. AC voltage to 750V (DC to 100VV), 100,4 resolution and 0.1 0 hms — 2 Megohms. Accuracy is 0.8% and it displays mV. V and mA. You won't lind a cheaper 0MM with these learners. AND batteries, test leads, spare fuse and one year guarantee are INCLUDED in the low, inc. VAT price of just



Dept. ET15, 4 Meeting Street, Appledore, Nr. Bideford, North Devon EX39 1RY. Tel. Bideford (02372) 79507. Telex: 8953084.