

electronics today

ISSN. 0142-7229

INTERNATIONAL

APRIL 1981 65p



MAKE YOUR OWN ELECTRONIC MUSIC!

Four superb projects inside

- DRUM SYNTHESISER/RHYTHM GENERATOR
- VISUAL SOUND ANALYSER
- SYNTHESISER MODULE
- GUITAR NOTE EXPANDER

PLUS Electronics in Boats
First Steps In Programming
Pickup Cartridge Principles
Low Resistance Meter Project

**BIGGER BETTER VALUE
THAN EVER!**

***OVER 25 CIRCUITS TO BUILD!
*SIX DIY PROJECTS *OVER 110 PAGES**

NEWS... PRO

MICROPROCESSORS... AUDIO...

TRANSCENDENT POLYSYNTH

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready built equipment costing thousands of pounds. Designed by synthesizer expert Tim Orr and being featured in this issue of Electronics Today International, this latest addition to the famous Transcendent family is a 4 octave (transposable over 7 1/2 octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes. Whereas conventional synthesizers handle only one at a time.

The basic instrument is supplied with 1 voice and up to 3 more may be plugged in. A further 4 voices may be added by connecting to an expander unit, the metalwork and woodwork of which is designed for side by side matching with the main instrument. Each voice is a

complete synthesizer in itself with 2 VCOs, 2 ADSRs, a VCA and a VCF (requiring only control voltages and a power supply, the voice boards are also suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to ensure consistency between the voices.

Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plugs and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2% metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

EXPANDABLE POLYPHONIC SYNTHESIZER



COMPLETE KIT

ONLY

£320 + VAT

(Single voice)
Plug in extra
Voices - Kit price £32 + VAT
(£46 + VAT if ordered with kit)

Cabinet size 31.1" x 19.6" x 7.6" rear 3.4" front

Kit also available as separate packs

Item	Price	Pack	Description	Price	Pack	Description	Price
ADSR IC CEM 3310	£4.00	POLY 1	Pair of PCB's for multiplex control K B contacts	£9.50	POLY 14	PCB for VOICE boards	£6.80
VCO IC CEM 3340	£6.00	POLY 2	IC's, IC sockets, Rs, Cs, for master control	£8.20	POLY 15	Printed circuit board for VOICE PCB	£4.80
0.1% 25 ppm M.F. Res	£0.50	POLY 3	Superior quality keyboard	£32.25	POLY 16	PCB for plug in voices	£8.20
0.5% 25 ppm M.F. Res	£0.25	POLY 4	Contacts & bus bars	£12.00	POLY 17	Rs, Cs, potentiometer connectors for one voice	£16.30
30 ppm multilayer ceramic cap	£0.50	POLY 5	Double sided plated through PCB for digital control & pitch gate generator	£17.25	POLY 18	IC's, IC sockets, diodes for one voice	£27.50
ICs and details of all packs in our FREE CATALOGUE		POLY 6	Rs, Cs, heat sink for fitting to Pack 5	£10.50	POLY 19	Transformer 0.120 240 17.0 17 0.7.7	£6.30
		POLY 7	IC's IC sockets, diodes for fitting to Pack 5	£31.30	POLY 20	Printed control	£3.90
		POLY 8	Double sided mother board (for plug in voices)	£18.90	POLY 21	Main parts eg jack sockets, knobs, mains switch etc	£13.00
		POLY 9	Rs, Cs, connectors for mother board	£14.10	POLY 22	Ribbon cable, ribbon cable connectors, mains cable	£8.45
		POLY 10	IC's IC sockets, Trs, heat sinks for mother board	£13.10	POLY 23	Fully finished metalwork and fixing parts	£25.60
		POLY 11	PCB for master controls (left of section marked VOICES)	£18.80	POLY 24	Solid teak cabinet	£25.80
		POLY 12	ICs, IC sockets, diodes Trs, Rs, Cs for master control PCB	£9.30		Total cost for individually purchased packs for single voice instrument	£355.15
		POLY 13	Pots, Switches for master control board	£11.80		Complete kit for 4 voice expander including connectors	£295.00
						All prices VAT exclusive.	

POWERTRAN

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!
POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until May 31st, 1981. If this month's advertisement is cancelled with your order. Errors and VAT rate changes included.


EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and postal discountation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage fees at current rates if changed.

SECURICOR DELIVERY: For the express service (to be arranged separately) £2.50 V.A.T. included per kg.

SALES COUNTER: If you prefer to collect kit from the factory call at Sales Counter, Open Hours: 12 noon - 1.4.30pm Monday-Thursday.


MANY MORE KITS ON PAGE 8

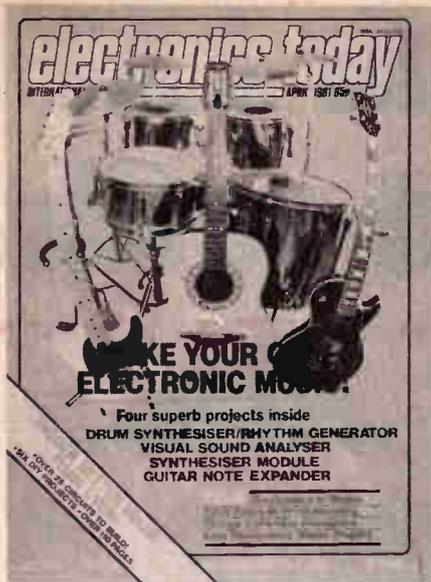


Our thanks to Music Bank, 6 Erskine Road, London NW3, who provided the facilities for our cover photograph



Double dose of drumming p.75

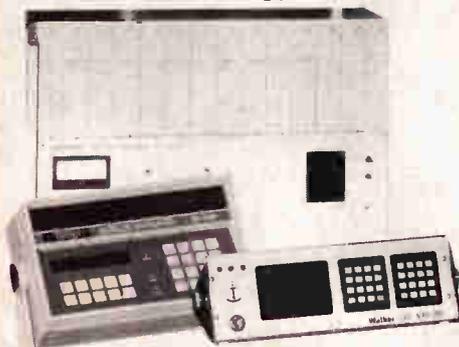

All at sea p.28

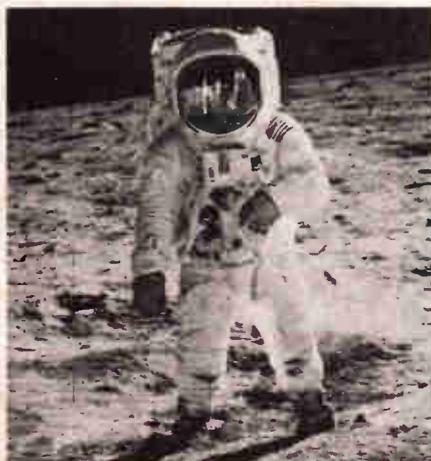

Interplanetary pix p.71

electronics today

APRIL 1981 VOL 10 NO 4 INTERNATIONAL

FEATURES

DIGEST	8	Read all about it
KIT REVIEW	17	Touch dimmer tested
ELECTRONICS IN BOATS	28	Boat Show reviewed
TECH TIPS	35	Readers' circuits
PICKUP PRINCIPLES	44	In the groove
MICROBASICS	55	Programming programmers
DESIGNER'S NOTEBOOK	66	CMOS safety
ASTROLOGUE	71	Aeronautics and artwork
AUDIOPHILE	82	The Reviewer's Return
SPOT DESIGNS	88	Tried and tested circuits
THE LEPTONS	91	A subatomic story

PROJECTS

VSCA	21	Audio display
LOW-OHM METER	40	Measure miniscule resistances
MUSICAL BOX	50	Shake it all about
NOISE GENERATOR	59	A Project 80 module
DRUM MACHINE	75	Sound design
GUITAR NOTE EXPANDER	95	Stretch your strings
READER'S DESIGNS	100	Caravan lights checker
FOIL PATTERNS	104	Board meeting

INFORMATION

EXHIBITION	10	We're coming to Bristol
NEXT MONTH'S ETI	15	What are we going to do next
BOOKS	27	Our technical book service
SUBSCRIPTIONS	63	Advance booking
ETIPRINTS	102	Give yourself a rub-down

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.

Ron Harris B.Sc.
Peter Green
Tina Boylan
Paul Wilson-Patterson
Paul Edwards
Ray Marston
Steven Rowe
Sally Holley
T.J. Connell

Editor
Assistant Editor
Editorial Assistant
Group Art Editor
Drawing Office Manager
Project Editor
Advertisement Manager
Advertisement Representative
Managing Director

OVERSEAS EDITIONS and their EDITORS
AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsman



Member of the Audit Bureau of Circulation



PUBLISHED BY Modmags Ltd., 145 Charing Cross Road, London WC2H 0EE
DISTRIBUTED BY Argus Press Sales & Distribution Ltd. 12-18 Paul Street, London EC2A 4JS (British Isles)
PRINTED BY QB Limited, Colchester
COVERS PRINTED BY Alabaster Passmore

Electronics Today is normally published on the first Friday in the month preceding cover date. © MODMAGS LTD 1981. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. Subscription Rates: UK E11 including postage. Airmail and other rates upon application to ETI Subscriptions Service, Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE.

Why the Sinclair ZX80 is Britain's best-selling

Built: £99.95

Including VAT, post and packing, free course in computing, free mains adaptor.

Kit: £79.95

Including VAT, post and packing, free course in computing.

This is the ZX80. A really powerful, full-facility computer, matching or surpassing other personal computers at several times the price. 'Personal Computer World' gave it 5 stars for 'excellent value'. Benchmark tests say it's faster than all previous personal computers.

Programmed in BASIC – the world's most popular language – the ZX80 is suitable for beginners and experts alike. And response from enthusiasts has been tremendous – over 20,000 ZX80s have been sold so far!

Powerful ROM and BASIC interpreter

The 4K BASIC ROM offers remarkable programming advantages:

- * Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- * Unique syntax check. A cursor identifies errors immediately.
- * Excellent string-handling capability – takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison).
- * Up to 26 single dimension arrays.
- * FOR/NEXT loops nested up to 26.
- * Variable names of any length.
- * BASIC language also handles full Boolean arithmetic, condition expressions, etc.
- * Randomise function, useful for games and secret codes, as well as more serious applications.
- * Timer under program control.
- * PEEK and POKE enable entry of machine code instructions.
- * High-resolution graphics.
- * Lines of unlimited length.

Unique RAM

The ZX80's 1K-BYTE RAM is the equivalent of up to 4K BYTES in a conventional computer – typically storing 100 lines of BASIC.

No other personal computer offers this unique combination of high capability and low price.



The ZX80 as a family learning aid. Children of 10 years and upwards are quick to understand the principles of computing – and enjoy their personal computer.

The Sinclair teach-yourself BASIC manual

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book (free with every ZX80). The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs.

Kit or built – it's up to you

In kit form, the ZX80 is pleasantly easy to assemble, using a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9V DC nominal unregulated. If not, see the coupon.

Both kit and built versions come complete with all necessary leads to connect to your TV (colour or black and white) and cassette recorder. Plug in and you're ready to go. (Built versions come with mains adaptor.)

ETI APRIL 1981

personal computer.

Now available for the ZX80... New 16K-BYTE RAM pack

Massive add-on memory. Only £49.95.

The new 16K-BYTE RAM pack is a complete module designed to provide you – and your Sinclair ZX80 – with massive add-on memory. You can use it for those really long and complex programs – or as a personal database. (Yet it can cost as little as half the price of competitive add-on memory for other computers.)

For example, you could write an interactive or 'conversational' program to show people what your ZX80 can do. With 16K-BYTES of RAM, they could be talking to your computer for hours!

Or you can store a mass of data – perhaps in a fairly simple program – such as a name and address list, or a telephone directory.

And by linking a number of separate programs together into one giant, but modular, program, you can achieve the same effect as loading several programs at once.



We're also confident that it won't be long

before you can buy cassette-based software using the full 16K-BYTE RAM. So keep an eye on the personal computer magazines – and brush up your chess perhaps!

The RAM pack simply plugs into the existing expansion port on the rear of the ZX80. No wires, no soldering. It's a matter of seconds and you don't need another power supply. You can only add one RAM pack to your ZX80 – but with 16K-BYTES who could want more!

How to order

Demand for the ZX80 exceeds all other personal computers put together! So use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

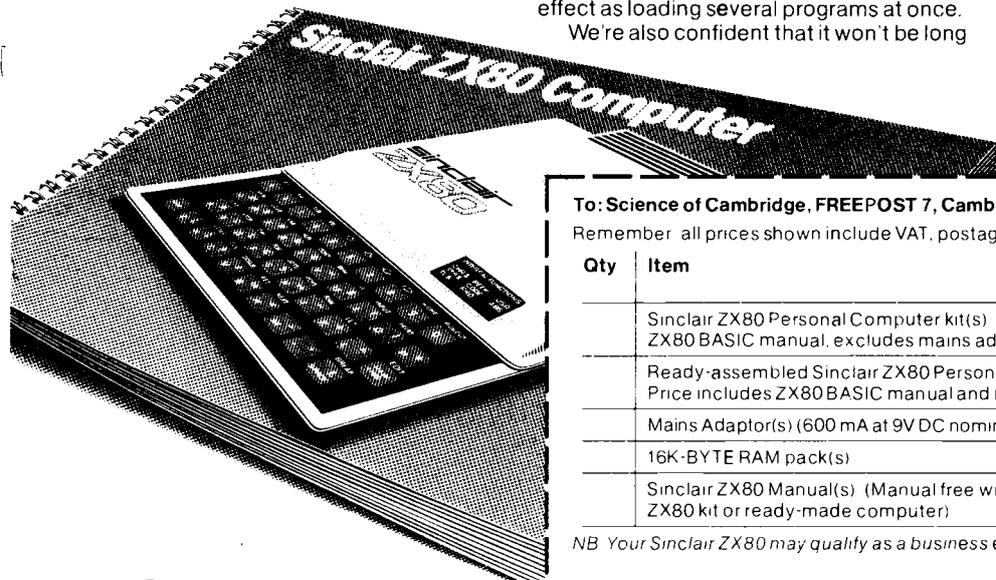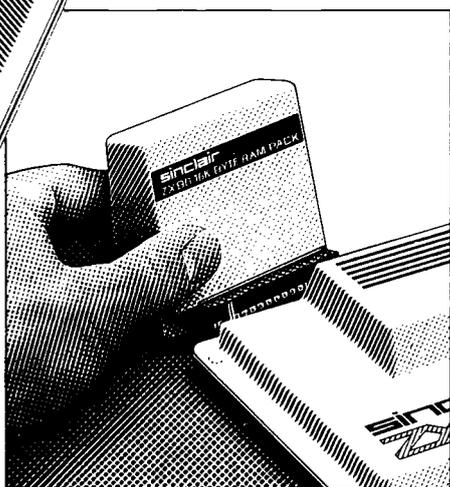

To: Science of Cambridge, FREEPOST 7, Cambridge CB2 1YY.

Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me:

Qty	Item	Code	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s) Price includes ZX80 BASIC manual, excludes mains adaptor.	02	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s) Price includes ZX80 BASIC manual and mains adaptor	01	99.95	
	Mains Adaptor(s) (600 mA at 9V DC nominal unregulated)	03	8.95	
	16K-BYTE RAM pack(s)	18	49.95	
	Sinclair ZX80 Manual(s) (Manual free with every ZX80 kit or ready-made computer)	06	5.00	

NB Your Sinclair ZX80 may qualify as a business expense

TOTAL: £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____

Please print

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed.

ET104

sinclair ZX80

Science of Cambridge Ltd.

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ETI APRIL 1981

WATFORD ELECTRONICS

COMPUTER CORNER

SUPERBOARD II Series II Ready built and tested 50Hz. No Flicker Incl Manuals and Programme Cassette **£149**
POWER SUPPLY 5V (3A incl RF Modulator) for Superboard II (Ready-built and tested) **£20**
4K RAM (8 x 2114) **£14**
610 EXPANSION BOARD 8K RAM (Expandable to 24K) Ideal for Superboard, UK101, etc **£150**
MICROTYPE CASE III, Black ABS case ideal for Superboard, UK101, NASCOM etc **£25**
VIDEO GENIE based on TRS80 Utilises Z80 12K level II BASIC. 16K RAM. 64 x 48 Video Display, incl Cassette Deck **£288**
SOUND UNIT for above (ready fitted) **£15**
LOWER CASE for above (ready fitted) **£35**
ACULAB FLOPPY with Waters **£174**
EXPANSION BOX with RS232C **£199**
S100 16K Memory **£95**
S100 32K Memory **£135**
SUPERPRINT 800, 80 column Low Cost Impact Printer. 9 1/2" paper width. Tractor / Friction Feed inputs for RS232, 20mA Loop, IEE-488. Centronics parallel all standard **£295**

EPSON TX-80B Dot Matrix, Tractor Feed **£295**
EPSON TX-80 Dot Matrix, Friction Feed **£295**
SEIKOSHA G780A Uni-hammer, 80 Column, Impact Graphic, Dot Printer **Only £225**
SOFTY, Intelligent EPROM Programmer, Ready built and tested **£120**
SOFTY in kit form **£100**
SOFTY POWER SUPPLY (ready built) **£20**
TEX EPROM Eraser **£33**
UV141 EPROM Eraser with timer **£77**
KEYBOARD 756 Full ASCII coded **£39**
KEYPAD 4 x 4 matrix (Reed switches) **350p**
STACK PACK 10 x C12 High Grade Cassettes incl the unique stackable drawers and labels **£25p** (p&p on the above items is extra)

SWITCHES TOGGLE 2A, 250V SPST 33p DPDT 44p 4 pole on/off 54p	SLIDE 250V: DPDT 1A 14p DPDT 1A c/off 15p DPDT 2A 15p 4 pole 2-way 24p	ROTARY (Adjustable Stop) SWITCHES 1 pole / 2 to 12 way, 2 pole / 2 to 6 way, 3 pole / 2 to 4 way, 4 pole / 2 to 3 way 45p ROTARY: Mains DP 250V 4A on/off 50p ROTARY: Make your own multiway switch. Sharing Assembly Has adjustable stop. Accommodates up to 6 wafers 90p WAFERS: (Break before Make) 1 pole / 12 way, 2p / 6 way, 3p / 4 way, 4p / 3 way, 8p / 2 way 60p Mains DP Switch 250V / 2A to fit 45p Spacers 4p; Screen 8p
SUB-MIN TOGGLE SPST on/off 54p SPDT c/over 60p SPDT c/off 85 SPDT biased both ways 105 DPDT 6 tags 75p DPDT centre off 88p DPDT biased both ways 145p DPDT 3 positions on/on/off 185p 4 pole 2 way 205p	PUSH BUTTON 6A with 10mm Button SPDT 89p DPDT 145p SPDT 99p DPDT 145p Mini Non Lock Push to Make 15p Red, Blue, Grn., Push to Break 25p OIL SWITCHES SPST 1 way 85p , 6 way 95p , 8 way 115p ; 10 way 145p	'D' CONNECTORS (Cannon type) Plugs Sockets Covers 9way 95p 125p Ptc 15way 135p 185p 150p 25way 198p 284p 170p 37way 290p 398p 185p

CRYSTALS 100KHz 323 200KHz 370 455KHz 383 1MHz 323 1.008M 395 1.28MHz 392 1.6MHz 323 1.8MHz 323 1.8432MHz 382 2MHz 305 2.4576MHz 382 3.2768M 323 3.57954M 195 4.000MHz 290 4.032MHz 323 4.19430M 170 4.433619M 235 5.0MHz 355 5.185M 323 5.24288M 425 6.0MHz 323 6.144MHz 295 6.5536M 200 6.5536MHz 290 7MHz 290 7.168MHz 290 7.680M 323 8.0MHz 392 8.08333M 392 8.867237M 392 9.375M 323 10.0MHz 323 10.7MHz 323 12.0MHz 392 14.31818M 392 16.0MHz 260 18MHz 323 18.432M 323 20.0MHz 323 26.69MHz 290 27.648M 323 38.8667M 350 48.0MHz 323 100.00MHz 323 116.0MHz 300	TRANSFORMERS (Mains Prim. 220-240V) 0-6-0V 9-0-9V, 12-0-12V 100mA 98p 175p 8VA: 0-6V 0-6V (PCB mounting) 175p 12V-3A, 15V-2.5A 15V-2.5A 220p 12V-4.5V-1.3A 4.5V-1.3A, 6V-1.2A 6V-1.2A, 20V-3A 250p (30p p&p) 20V-3A 250p (30p p&p) 24VA: 6V-1.5A 6C-1.5A 9V-1.3A 9V-1.3A, 12V-1A 12V-1A, 15V-8A 15V-8A, 20V-6A 20V-6A 320p (55p p&p) 50VA: 6V-4A 6V-4A, 9V-2.5A 9V-2.5A, 12V-2A 12V-2A, 15V-1.5A 15V-1.5A, 20V-1.2A 20V-1.2A, 25V-1A 25V-1A, 30V-8A 30V-8A 360p (60p p&p) 100VA: 12V-4A 12V-4A 15V-3A 15V-3A, 20V-2.5A 20V-2.5A, 30V-1.5A 30V-1.5A, 40V-1.25A 40V-1.25A, 50V-1A 50V-1A 820p (74p p&p) (NB p&p charge to be added above our normal postal charge)	ALUM. BOXES WITH LIO 3x2x1" 65 4x2 1/2x2" 85 4x2 1/4x1 1/2" 85 4x2 1/2x2 1/2" 103 4x4 1 1/2" 95 4x4x2 1/2" 100 5x4x2" 95 5 1/2x2 1/2x2 1/2" 130 5 1/2x4 1 1/2" 99 5 1/2x4 2 1/2" 120 6x4x2" 120 6x4x3" 148 7x5x2 1/2" 165 7x5x3" 180 8x6x3" 210	PANEL METERS F80 60x46x 35mm 0-50uA 105 0-100uA 105 0-500uA 105 0-1mA 105 0-5mA 105 0-10mA 105 0-50mA 105 0-100mA 105 0-500mA 105 0-1A 105 0-2A 105 0-25V 105 0-50V AC 105 0-300V AC 105 "VU" 445p each 4 1/2x3 1/2x1 1/2" 105 0-50uA 105 0-100uA 105 0-500uA 105 885p each 7 Segment Displays TIL307 675 TIL312 3" CA 105 TIL313 3" CC 105 TIL321 5" CA 115 TIL322 5" CC 115 DL704 3" CC 99 DL707 3" CA 99 DL747 6" CA 150 B Orange CA 250 FN0357 Red 120 FN5000 115 3" Green CA 150 6" Green CA 215 3 = 1 Red CA 150 3 = 1 Green CA 150
---	--	--	---

VOLTAGE REGULATORS 1A TO3 +ve -ve 5V 7805 145p 7905 220p 12V 7812 145p 7912 220p 15V 7815 145p 18V 7818 145p 1A TO220 Plastic Casing 5V 7805 60p 7905 65p 12V 7812 60p 7912 65p 15V 7815 60p 7915 65p 18V 7818 60p 7918 65p 100mA TO92 Plastic Casing 5V 78L05 30p 79L05 65p 6V 78L62 30p 7.8V 78L82 30p 12V 78L12 30p 79L12 65p 15V 78L15 30p 79L15 65p LM300H 170p LM723 38p LM305H 140p TAA550 50p LM309K 135p TB6258 95p LM317K 350p ZDA1412 150p LM317H 240p 78H05 + 5V-5A 59p LM323K 550p LM325N 240p 78HG + 5V to +25V 65p LM326N 240p 5A 85p LM327 270p 79HG 850p	OPTO LEDs with Clips TIL209 Red 13 TIL211 Grn 17 TIL212 Yel 18 TIL220 2" Red 14 2 Green, Yellow or Amber 18 2" High Bright Red 18 2" Flashing Red 49 2" Red, Green 46 Square LEDs, Red, Green, Yellow 30 LD271 Infra Red 40 SFH205 Detector 90 TIL32 Infra Red 65 TIL78 Detector 75 BARGRAPH Red 10 segments 225 LS400 255 OC7P1 120 ORP12 63 ORP61 85 2N5777 45 ISOLATORS IL74 55 TIL111 2-4 90
--	--

Parts available for ETI Projects	LS245 150 LS247 135 LS248 135 LS249 136 LS251 130 LS253 96 LS257 96 LS258 120 LS259 160 LS261 460 LS266 75 LS273 190 LS275 320 LS279 88 LS280 280 LS283 90 LS290 130 LS293 130 LS295 215 LS298 215 LS299 420 LS300 175 LS302 175 LS320 270 LS323 460 LS324 200 LS325 320 LS326 310 LS327 310 LS346 185 LS347 150 LS348 180 LS352 185 LS353 185 LS365 85 LS366 85 LS367 85 LS368 80	LS373 150 LS374 150 LS375 150 LS377 190 LS378 140 LS379 215 LS384 260 LS385 420 LS386 85 LS390 140 LS393 140 LS395 210 LS396 195 LS398 275 LS399 230 LS445 140 LS447 195 LS490 245 LS492 105 LS498 105 LS499 270 LS5673 750 LS674 860	4016 35 4017 70 4018 76 4019 42 4020 85 4021 90 4022 85 4023 24 4024 60 4025 24 4026 170 4027 45 4028 92 4029 98 4030 55 4031 185 4032 125 4033 175 4034 213 4035 95 4036 275 4037 115 4038 110 4039 299 4040 85 4041 80 4042 70 4043 80 4044 80 4045 175 4046 95 4047 98 4048 65 4049 35 4050 38 4051 86 4052 86 4053 86	4054 130 4055 130 4056 135 4057 2850 4058 575 4060 110 4061 1225 4062 995 4063 120 4066 46 4067 430 4068 26 4069 22 4070 25 4071 25 4072 25 4073 25 4075 23 4076 85 4077 30 4078 28 4081 26 4082 25 4085 90 4086 90 4089 150 4093 55 4094 210 4095 95 4096 95 4097 340 4098 115 4099 150 4100 115 4101 115 4102 115 4169 115 4170 115	4175 120 4194 115 4408 790 4409 790 4410 750 4411 960 4412 1250 4412V 1520 4415F 480 4415V 850 4419 280 4422 570 4432 1050 4435 950 4440 950 4450 350 4451 350 4452 455 4490F 350 4500 450 4501 750 4502 108 4503 65 4506 75 4507 48 4508 280 4510 85 4511 88 4512 94 4513 94 4514 225 4515 225 4516 90 4517 415 4518 90 4519 80 4520 90 4521 210 4522 150 4526 98 4527 125 4528 100 4529 100 4530 90 4531 130 4532 120 4534 510 4536 310 4538 145 4539 120 4541 190 4543 150 4549 395 4553 399 4554 192 4555 85 4556 60 4557 425 4558 174 4559 450 4560 199 4561 104 4562 525 4566 195 4568 299 4569 195 4572 36 4580 495 4581 320 4582 135 4583 105 4584 55 4585 90 4587 330 4588 390 4589 390 46106 99
---	---	--	--	--	--

CMOS

4000 14 4001 14 4002 15 4006 86 4007 19 4008 76 4009 46 4010 50 4011 18 4012 24 4013 43 4014 80 4015 82	4016 35 4017 70 4018 76 4019 42 4020 85 4021 90 4022 85 4023 24 4024 60 4025 24 4026 170 4027 45 4028 92 4029 98 4030 55 4031 185 4032 125 4033 175 4034 213 4035 95 4036 275 4037 115 4038 110 4039 299 4040 85 4041 80 4042 70 4043 80 4044 80 4045 175 4046 95 4047 98 4048 65 4049 35 4050 38 4051 86 4052 86 4053 86	4054 130 4055 130 4056 135 4057 2850 4058 575 4060 110 4061 1225 4062 995 4063 120 4066 46 4067 430 4068 26 4069 22 4070 25 4071 25 4072 25 4073 25 4075 23 4076 85 4077 30 4078 28 4081 26 4082 25 4085 90 4086 90 4089 150 4093 55 4094 210 4095 95 4096 95 4097 340 4098 115 4099 150 4100 115 4101 115 4102 115 4103 115 4104 115 4105 115 4106 115 4107 115 4108 115 4109 115 4110 115 4111 115 4112 115 4113 115 4114 115 4115 115 4116 115 4117 115 4118 115 4119 115 4120 115	4175 120 4194 115 4408 790 4409 790 4410 750 4411 960 4412 1250 4412V 1520 4415F 480 4415V 850 4419 280 4422 570 4432 1050 4435 950 4440 950 4450 350 4451 350 4452 455 4490F 350 4500 450 4501 750 4502 108 4503 65 4506 75 4507 48 4508 280 4510 85 4511 88 4512 94 4513 94 4514 225 4515 225 4516 90 4517 415 4518 90 4519 80 4520 90 4521 210 4522 150 4526 98 4527 125 4528 100 4529 100 4530 90 4531 130 4532 120 4534 510 4536 310 4538 145 4539 120 4541 190 4543 150 4549 395 4553 399 4554 192 4555 85 4556 60 4557 425 4558 174 4559 450 4560 199 4561 104 4562 525 4566 195 4568 299 4569 195 4572 36 4580 495 4581 320 4582 135 4583 105 45
--	--	--	--

DIGEST

OOPS Digital Test Meter

Some constructors of the DTM (September '80) have reported problems with the DVM module blowing. This can be prevented by putting a 10M resistor in series with the IN HI pin of the module.

On page 83 the overlay for the resistance measurement board (bottom overlay) shows the common of R43, R44, R45 and C15 connected to IC7 pin 4. In fact IC7 pin 4 should go only to the -6 V takeoff point and C7 -ve. Cut the PCB track just above R45 (page 80 Fig.1 shows the correct wiring).

Take It Anywhere

New from JVC is the CX N610GB, a 6" VHF/UHF portable colour TV/monitor. This compact unit can be taken anywhere; it is capable of PAL and SECAM TV reception so you can receive programmes in any country that has one of the following TV systems - PAL B, G, or I system and SECAM B, G, D, K, or KI system (both CCIR continental and OIRT standards). The CX 610GB's colour system automatically switches to the broadcast system being used and the corresponding sound IF frequency can then be selected. The set has a newly developed JVC precision in-line picture tube, giving excellent colour pictures, and its highly sensitive swivel antenna ensures good quality

Vocoder


Two of the ICs in the Vocoder (September '80) are listed incorrectly. In the circuit diagram and Parts List for the internal excitation board, IC5 is a 4030 and IC6 is a 4006.

Breadboard 80

In our report on Breadboard 80 (in the February News Digest), our reporter, no doubt overcome by the occasion, said that our celebrity guest was Brian Rix. In fact Mr Rix, a radio amateur, was at the show as a guest of Practical Wireless, to whom we offer our apologies.

reception wherever you are. The flexibility of this unit is further enhanced by a four-way power supply - from the household mains, ordinary batteries, its own rechargeable battery pack or from a 12 V DC car or boat battery.

The CX 610GB can also function as an on-location video monitor when used in conjunction with a colour video camera and portable video recorder. You can even record off-the-air television broadcasts out-of-doors by connecting the CX 610GB to a portable video recorder. The recommended retail price is £259 (including VAT), and further information is available from JVC (UK) Ltd, Eldonwell Trading Estate, Staples Corner, 6-8 Priestley Way, London NW2 7AF.

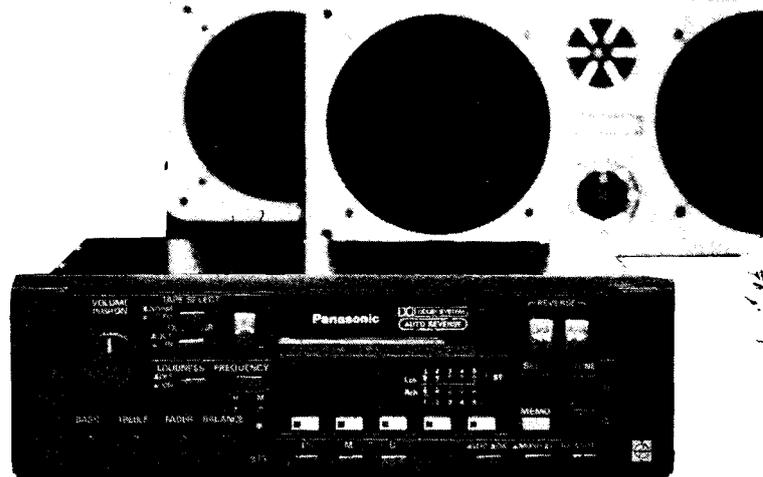


Panasonic Car-Fi

Panasonic has introduced what it believes to be the first full hi-fi stereo car radio/cassette that will fit into a standard DIN size dashboard aperture. The CQ 973 combines microprocessor electronics with full hi-fi specifications and according to Panasonic it is the most advanced in-car system available.

For those of you who can afford the £395.95 price tag, the CQ 973 offers digital frequency readout, three waveband stereo radio, (LW/MW/FM), electronic preset tuning, auto-tune tuning, an auto-reverse cassette player with a Dolby Noise Reduction system, and an output of 100 W. The

radio functions are all push-button controlled, with a total of 15 preset stations (five on each band); as an additional safety feature the driver can also keep his hands on the steering wheel and tune the radio by footswitch. The bright green digital frequency readout also functions as a clock, and at night all the major controls are illuminated.

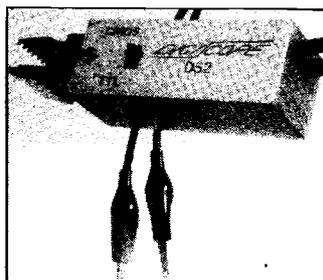The unit is fitted with normal/metal tape selection and both the fast forward and rewind buttons can be locked in. Separate bass, treble and loudness controls are provided. For further information on the CQ 973 and the rest of Panasonic's in-car entertainment range, contact any of Panasonic's authorised dealers.



Logic Monitor

If you're in the business of developing or trouble-shooting digital circuits then you'll be interested in the Digiscope DS2 Logic Monitor. The device simply clips over any 14 or 16 pin DIL logic IC during operation, and indicates the state of each pin, either 0 or 1. Each pin has its state shown simultaneously on a 16-LED display, enabling cir-

cuit action and faults to be traced with ease. The DS2 is powered from either the circuit supply or an external source and draws negligible current from the IC under test, so circuit operation is unaffected. The input threshold is adjustable to suit either TTL or CMOS ICs. The monitor can also be used to check free packages; power is applied to the supply pins and since the DS2 pulls all the inputs high, operation can be checked by grounding the appropriate inputs and observing the effect. The DS2 is housed in a tough aluminium case and is suitable for use in industrial environments; the case is only 1" wide so several ICs may be checked side-by-side simultaneously. There is a range of accessories available including plugs and an extension lead for remote monitoring. The Digiscope DS2 costs £27.40 and further information is available from the manufacturers, J.E. Sinclair & Co., 82 Plumstead Common Road, London SE18 3RE.

Micro Talk

General Instrument Microelectronics have announced the introduction of a new speech synthesis chip, the SP0256. It's a 28 lead LSI device, designed to generate up to 256 discrete sequences of human speech or other complex sounds

stored in its built-in 16K ROM. External expansion can increase the SP0256's repertoire to almost 3825 sequences. Commonly used sounds can be stored once and called from memory when necessary, reducing data storage requirements. Applications envisaged include warning systems, radar, test gear and security systems.

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd.) and featured as a construction article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal film), and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

**COMPLETE KIT ONLY
£168.50 + VAT!**



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

COMING SHORTLY!

1024 NOTE COMPOSER/SEQUENCER — LESS THAN £100



Panel size 19.0" x 5.25". Depth 12.2"

ETI VOCODER

**COMPLETE KIT ONLY
£195 + VAT!**

Kit includes FREE foot control and test oscillator!

Featured as a construction article in **Electronics Today International** this design enables a vocoder of great versatility and high intelligibility to be built for an amazingly low price. 14 channels are used to achieve its high intelligibility, each channel having its own level control. There are two input amplifiers, one for speech either from microphone or a high level source e.g. mixer or cassette deck and one for external excitation (the substitution signal) from either high or low level sources. Each amplifier has its own level control and a rather special type of tone control giving varying degrees of bass boost with treble cut or treble boost with bass cut. The level of the speech and excitation signals are monitored by LED PPM meters with 10 lights — 7 green and 3 red which indicate the level at 3dB steps. There are three internal sources of excitation — a noise generator and two pulse generators of variable frequency and pulse width. Any of the internal sources and the external source can be mixed together. There is a voiced / unvoiced detector which substitutes noise for the excitation signal at the points in speech where the vocal chord derived sounds of the speaker are substituted for by the unvoiced sounds of sibilants, etc. There is a slow rate control which smooths out the changes in spectral balance and amplitude enabling a change of the speech into singing or chanting and other special effects. A foot switch is provided to permit a complete freeze in spectral balance and amplitude whenever required. An LED on this indicates when the freeze is in operation.

An output mixer allows mixing of the speech, external excitation and vocoder output. The majority of the components fit into the large analysis/synthesis board with the rest on 8 much smaller boards with the controls and sockets mounted on them for ease of construction. Connectors are used for the small amount of wiring between the boards. The kit includes fully finished metalwork, professional quality components (all resistors 2% metal oxide) nuts, bolts, etc. — even a 13A plug!

TRANSCENDENT DPX

MULTI-VOICE SYNTHESIZER

Another superb design by
synthesizer expert Tim Orr
published in
Electronics Today International

**COMPLETE KIT
ONLY
£299 + VAT!**



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus / ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

POWERTRAN

**MANY MORE KITS ON PAGE 107. MORE KITS AND ORDERING
INFORMATION ON INSIDE FRONT COVER**

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

COMPUTERS • AUDIO • RADIO • MUSIC • LOGIC • COMPONENTS • CB

HOBBY ELECTRONICS GOES WEST

London has more than its fair share of electronics shows, but we know that electronics enthusiasts are by no means limited to the capital. For that reason the first annual Hobby Electronics Show is to be held in Bristol — centre of the South-West.

What's to see there?

- major electronics component suppliers
- special exhibition offers
- Wales & West schools' electronic project competition (*has your school submitted an entry yet? Available from Hobby Electronics 81)

TICKETS — at the door — ADULT : £1.00. CHILD, STUDENT, OAP : 50p.


GAMES • KITS • TEST GEAR • MAGAZINES • SPECIAL OFFERS • BOOKS

OPEN DAYS :

Friday May 29th : 10am — 7pm • Saturday May 30th : 10am — 6pm • Sunday May 31st : 10am — 4pm

Hobby Electronics BRISTOL EXHIBITION CENTRE '81

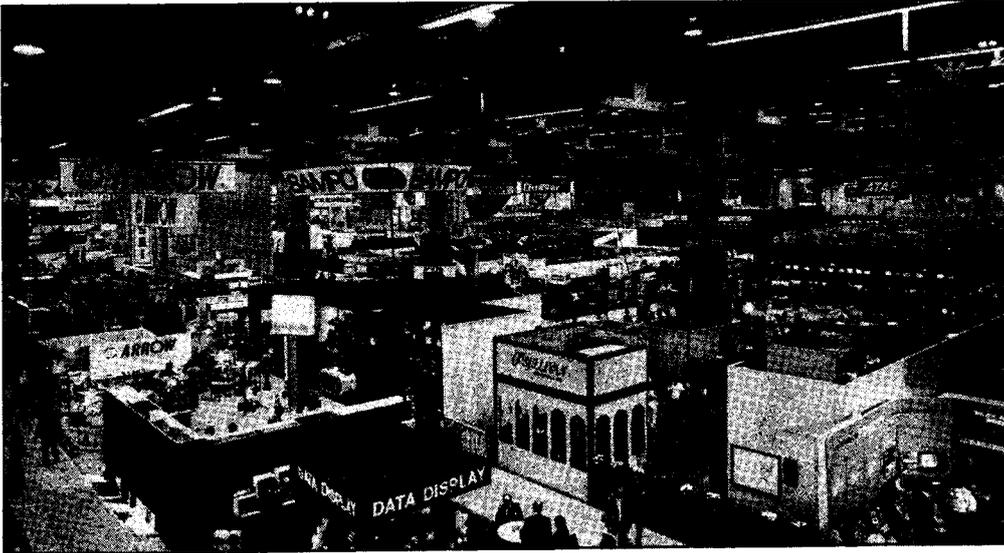Order your tickets now from:
Exhibition Manager,
Hobby Electronics 81,
145 Charing Cross Road,
London WC2H 0EE.



Vegas

The Winter Consumer Electronic Show keeps breaking its own records, and this year's event will be no exception. The Show organisers said that more than 850 exhibitors are showing off their new products at the Las Vegas Convention Centre, up from 757 at last year's Winter Show.

By the end of the year, it seems improbable that anyone will not have heard of the Video Disc. The long wait for the disc to become a functioning reality is over, and by next Winter's CES, close to 25 manufacturers will have a system on the market. The most carefully orchestrated and the most expensive promotion, advertising, and distribution programmes ever seen for an electronic product will forcefeed the video disc message to the American consumers in 1981.

Much of the attention is still focused on the competition between the Philips-made optical laser disc format and the RCA-patented CED

Disc system. Matsushita's VHD system, which will be a later entry into the field, can be expected to buck the other two, benefitting from the publicity about discs created by the optical — CED dogfight.

Another Atari first is their new remote control console which combines sleek, futuristic styling and advanced technology and simply makes the game more enjoyable. Two quick-action remote controllers allow the players to move around the room freely without clumsy controller wires interfering with game action. Now the players can select, play and reset games on this new system without ever having to get up. Fingertip touch controls and LED signals are built into the hand-held remote controllers for game select and game reset options and the combination joystick and pedal controllers respond quickly and easily to the players' touch. Activision also showed some new cartridges they have lined up which are compatible with the Atari system. One is Cen-

tre-court Tennis, which offers everything from lightning-quick serves to breathtaking back-hand

Gerald Chevin




Versatile Video

Supplies of the new Ferguson Videostar VHS Portable video cassette recorder, model 3V24, are soon to become available. The 3V24 is expected to be the most lightweight recorder on the market, weighing in at 5.2 kg. The 3V24 has a microprocessor-assisted, fully electronic logic control cassette deck which can be operated either direct-

ly or by the full remote control unit supplied. The recorder incorporates a new Edit Start Control system for minimising picture break-up between recordings, as well as a picture scan facility which operates at 10 times normal speed, both forward and reverse. Other facilities include still frame, single frame advance and variable slow motion. A new quick-change power pack is supplied giving full recharge in 1½ hours, and there is a choice of two AC power supply/battery charger units available for use with the 3V24.

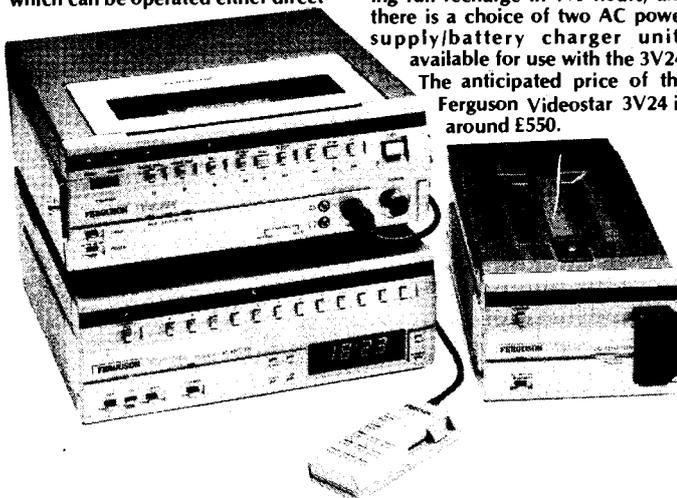The anticipated price of the Ferguson Videostar 3V24 is around £550.



Telly Type

Delpa Systems have just announced their new Video telex which is capable of overcoming many of the inherent problems of ordinary telex machines. The Video telex uses a VDU and so the typing of messages takes half the normal time. The machine offers full correction and editing facilities, including the correction of spelling mistakes and the deletion of lines or paragraphs. It also provides full tabulation which means more attractive layouts, par-


ticularly useful in reports and orders. On existing machines where punch tapes are used, error correcting is extremely awkward and any incoming calls will interrupt the process, but the Video telex does not punch the message until it is 100% correct. The machine can either be used in the telex room or by other staff throughout the office building. Each station costs around £900 and further details can be obtained from Delpa Systems (UK) Ltd, Data Transfer Division, 56 Chiswick High Road, London W4 1SZ.

IMPORTANT NOTICE

Readers have recently confused Electronics Today Limited as being associated with the ownership of our magazine, Electronics Today International. Our magazine is owned by Modmags Limited, part of the Argus Press Holdings Limited Group of Companies.

Electronics Today Limited has advertised in our magazine, as "Metac", but so as to prevent any further confusion we wish to make it clear that Electronics Today Limited is not owned or managed by any member of the Argus Press Holdings Limited Group of Companies.

TTL by TEXAS 7400 11p 74293 150p 4020 110p 7400 11p 74293 150p 4021 110p 7400 11p 74293 150p 4022 110p 7401 12p 74365 100p 4023 27p 7402 12p 74366 100p 4024 50p 7403 12p 74367 100p 4025 20p 7404 14p 74368 100p 4026 130p 7405 18p 74390 200p 4027 50p 7406 36p 74393 200p 4028 84p 7407 36p 74490 225p 4029 100p 7408 17p 74LS SERIES 4030 55p 7409 19p 74LS00 14p 4031 200p 7410 15p 74LS01 14p 4032 200p 7411 24p 74LS03 10p 4035 110p 7412 20p 74LS04 16p 4036 295p 7413 30p 74LS05 25p 4039 295p 7414 40p 74LS08 22p 4040 100p 7415 27p 74LS10 20p 4042 80p 7417 27p 74LS11 20p 4043 90p 7420 17p 74LS13 40p 4044 90p 7421 40p 74LS14 50p 4046 110p 7422 22p 74LS20 20p 4047 100p 7423 34p 74LS21 40p 4048 55p 7425 30p 74LS27 38p 4050 45p 7426 40p 74LS30 40p 4050 45p 7427 34p 74LS32 27p 4051 80p 7428 36p 74LS37 30p 4052 80p 7430 17p 74LS38 38p 4053 80p 7432 30p 74LS42 70p 4054 150p 7433 40p 74LS47 24p 4059 135p 7437 35p 74LS51 30p 4056 135p 7438 35p 74LS55 30p 4059 600p 7440 17p 74LS73 50p 4060 115p 7441 70p 74LS74 27p 4063 120p 7442A 60p 74LS76 36p 4066 50p 7443 115p 74LS76 36p 4066 50p 7444 112p 74LS83 70p 4068 27p 7445 100p 74LS85 80p 4069 20p 7446A 93p 74LS86 40p 4070 30p 7447A 75p 74LS90 40p 4071 25p 7448 80p 74LS92 70p 4072 25p 7450 17p 74LS96 100p 4075 25p 7451 17p 74LS96 100p 4075 25p 7453 17p 74LS107 45p 4076 100p 7454 17p 74LS109 80p 4081 27p 7456 17p 74LS112 40p 4082 27p 7457 36p 74LS113 90p 4086 70p 7472 30p 74LS114 60p 4089 150p 7473 34p 74LS122 80p 4093 70p 7474 30p 74LS123 60p 4094 250p 7475 38p 74LS124 180p 4095 95p 7476 32p 74LS125 50p 4096 95p 7480 50p 74LS126 50p 4099 340p 7481 100p 74LS132 60p 4098 120p 7482 84p 74LS133 30p 4099 200p 7483a 90p 74LS136 55p 4010 220p 7484 100p 74LS138 65p 4010 132p 7485 110p 74LS139 75p 4010 180p 7486 32p 74LS145 120p 4010 180p 7489 210p 74LS147 120p 4010 90p 7490A 30p 74LS148 175p 4010 120p 7491 80p 74LS151 80p 4010 90p 7492A 46p 74LS153 60p 4010 70p 7493A 36p 74LS154 200p 4010 470p 7494 84p 74LS154 200p 4010 470p 7495A 70p 74LS154 200p 4010 300p 7496 65p 74LS157 60p 4011 420p 7497 180p 74LS158 60p 4502 120p 74100 130p 74LS160 90p 4503 70p 74101 34p 74LS161 75p 4507 55p 74109 55p 74LS162 150p 4508 290p 74116 200p 74LS163 100p 4510 90p 74118 130p 74LS164 90p 4511 120p 74119 210p 74LS165 140p 4512 80p 74120 110p 74LS166 180p 4514 250p 74121 34p 74LS173 110p 4515 300p 74122 48p 74LS174 100p 4516 60p 74123 60p 74LS175 100p 4518 100p 74125 75p 74LS181 320p 4520 100p 74126 60p 74LS190 100p 4521 250p 74128 75p 74LS191 100p 4526 108p 74132 75p 74LS192 100p 4527 180p 74136 75p 74LS193 100p 4528 180p 74137 50p 74LS195 140p 4532 140p 74141 50p 74LS196 120p 4534 500p 74142 200p 74LS197 90p 4536 375p 74145 190p 74LS221 120p 4538 120p 74148 150p 74LS240 175p 4543 180p 74150 150p 74LS241 120p 4543 320p 74151A 70p 74LS242 170p 4556 72p 74153 70p 74LS243 170p 4560 200p 74154 120p 74LS244 150p 4569 250p 74154 120p 74LS245 250p 4572 400p 74155 90p 74LS251 140p 4583 110p 74157 90p 74LS251 140p 4584 90p 74159 190p 74LS257 90p 4724 250p 74160 100p 74LS258 160p 4009 70p 74161 100p 74LS259 160p 14411 1100p 74163 100p 74LS266 100p 14413 1100p 74163 100p 74LS273 170p 7553 70p 74164 120p 74LS279 100p 14500 70p 74165 130p 74LS283 90p 14599 290p 74166 120p 74LS298 160p 74167 200p 74LS323 400p AD536A £13 74170 240p 74LS324 200p AD561J 1400p 74172 450p 74LS324 200p AD752A 600p 74173 120p 74LS365 48p DM8123 175p 74174 90p 74LS367 70p DM8131 175p 74175 85p 74LS368 100p DP8304 450p 74176 90p 74LS373 150p DS8834 250p 74177 90p 74LS373 150p DS8834 250p 74178 160p 74LS375 150p DS8838 150p 74180 93p 74LS377 160p MC1488 70p 74181 160p 74LS378 140p MC1489 70p 74182 90p 74LS390 120p MC3446 300p 74184A 150p 74LS399 120p 25510 350p 74185 150p 74LS399 120p 75107 160p 74186 500p 74LS445 200p 75110 325p 74188 325p 74LS670 400p 75114 175p 74190 120p 4000 SERIES 75154 175p 74191 120p 4000 11p 75182 230p 74192 100p 4001 22p 75322 300p 74193 100p 4002 20p 75324 375p 74194 120p 4006 20p 75361 300p 74195 95p 4007 20p 75363 400p 74196 95p 4008 80p 75363 400p 74197 80p 4009 40p 75451 2 72p 74198 100p 4010 20p 75491 2 70p 74199 150p 4011 20p 8126 160p 74201 160p 4012 20p 8126 160p 74251 140p 4013 20p 8126 160p 74252 250p 4014 84p 8195 180p 7427 290p 4015 84p 8195 180p 7427A 110p 4016 84p 8195 180p 7428 140p 4016 84p 8195 180p 7428A 360p 4018 70p 81LS97 120p 7428B 360p 4019 45p 81LS98 140p 7428C 360p 4019 45p 81LS98 140p	93 SERIES 9301 150p 74S00 60p 74S114 120p 9302 175p 74S04 60p 74S124 300p 9308 316p 74S05 75p 74S132 160p 9310 275p 74S08 75p 74S133 75p 9311 275p 74S10 75p 74S138 225p 9312 160p 74S20 60p 74S139 225p 9314 185p 74S30 60p 74S157 250p 9316 225p 74S32 90p 74S174 250p 9321 225p 74S37 90p 74S175 320p 9322 125p 74S64 90p 74S194 350p 9334 30p 74S74 90p 74S241 450p 9368 250p 74S85 60p 74S269 250p 9370 300p 74S86 180p 74S373 500p 9374 200p 74S112 120p 74S374 500p	74S SERIES LM13600 125p LM3712 180p MC1310P 150p MC1458 45p MC1495L 350p MC1496 70p MC33400 120p MC33998 75p LM920 77.5p MM57160 620p NE551 150p NE555 20p NE556 150p NE562B 420p NE564 420p NE565 130p NE566 150p NE567 140p NE571 42.5p NE583A 250p RC4136 270p S5668 270p SAD1024A 1200p SN74877 180p SL490 400p SN74877 180p SP8515 750p TA7205 280p TA821 270p TB641B11 300p TB651 200p TB652 200p TB653 200p TB654 200p TB655 200p TB656 200p TB657 200p TB658 200p TB659 200p TB660 200p TB661 200p TB662 200p TB663 200p TB664 200p TB665 200p TB666 200p TB667 200p TB668 200p TB669 200p TB670 200p TB671 200p TB672 200p TB673 200p TB674 200p TB675 200p TB676 200p TB677 200p TB678 200p TB679 200p TB680 200p TB681 200p TB682 200p TB683 200p TB684 200p TB685 200p TB686 200p TB687 200p TB688 200p TB689 200p TB690 200p TB691 200p TB692 200p TB693 200p TB694 200p TB695 200p TB696 200p TB697 200p TB698 200p TB699 200p TB700 200p	TRANSISTORS BC107 25p BC108 25p BC109 25p BC299 25p BC300 25p	MEMORIES 2102 120p 2103 120p 2107 800p 2111 2 800p 2112 300p 2114 2 800p 4027 3 800p 4044 800p 4116 400p 4118 4 £10 5101 800p 5814 45 £25 74S201 400p 74S212 325p ROM/PROMS 71301 700p 74S188 225p 74S287 250p 74S288 250p 74S471 850p 74S571 650p CPUs 1600 1200p 1903CE 750p 2404A 250p 6502 600p 6802 950p 6809 £16 8008A 32p 80C86 1100p 1N5900A £20 TM59980A £20 Z80 800p Z80A 800p EPROMS 1702A 500p 2N577 480p 2708 £12 (+5V) 2732 £12 2733 £12 SUPPORT DEVICES 3245 800p 3246 800p 6522 800p 6523 800p 6524 800p 6600 800p	TIP30A 48p TIP30C 60p TIP31A 55p TIP31C 62p TIP32A 68p TIP32C 82p TIP33A 90p TIP33C 114p TIP34A 110p TIP34C 160p TIP35A 225p TIP35C 290p TIP36A 270p TIP36C 340p TIP41A 65p TIP41C 78p TIP35C 290p TIP36A 270p TIP36C 340p TIP41A 65p TIP41C 78p TIP39C 270p TIP42A 70p TIP42C 82p TIP5A 160p TIP120 120p TIP122 130p TIP142 130p TIP147 130p TIP2955 78p TIP4055 78p TIP4056 78p TIP4057 78p TIP4058 78p TIP4059 78p TIP4060 78p TIP4061 78p TIP4062 78p TIP4063 78p TIP4064 78p TIP4065 78p TIP4066 78p TIP4067 78p TIP4068 78p TIP4069 78p TIP4070 78p TIP4071 78p TIP4072 78p TIP4073 78p TIP4074 78p TIP4075 78p TIP4076 78p TIP4077 78p TIP4078 78p TIP4079 78p TIP4080 78p TIP4081 78p TIP4082 78p TIP4083 78p TIP4084 78p TIP4085 78p TIP4086 78p TIP4087 78p TIP4088 78p TIP4089 78p TIP4090 78p TIP4091 78p TIP4092 78p TIP4093 78p TIP4094 78p TIP4095 78p TIP4096 78p TIP4097 78p TIP4098 78p TIP4099 78p TIP4100 78p	2N3055 48p 2N3442 140p 2N3553 200p 2N3554 200p 2N3584 250p 2N3643 4 48p 2N3702 3 12p 2N3704 5 12p 2N3706 7 14p 2N3708 9 14p 2N3773 300p 2N3819 25p 2N3820 50p 2N3823 70p 2N3856 90p 2N3902 70p 2N3903 4 18p 2N3905 6 20p 2N4037 65p 2N4058 9 12p 2N4061 2 18p 2N4123 6 27p 2N4401 3 27p 2N4427 90p 2N4466 60p 2N4519 90p 2N4571 90p 2N4574 250p 2N4575 250p 2N4576 250p 2N4668 250p 2N4669 250p
--	---	--	--	---	---	--

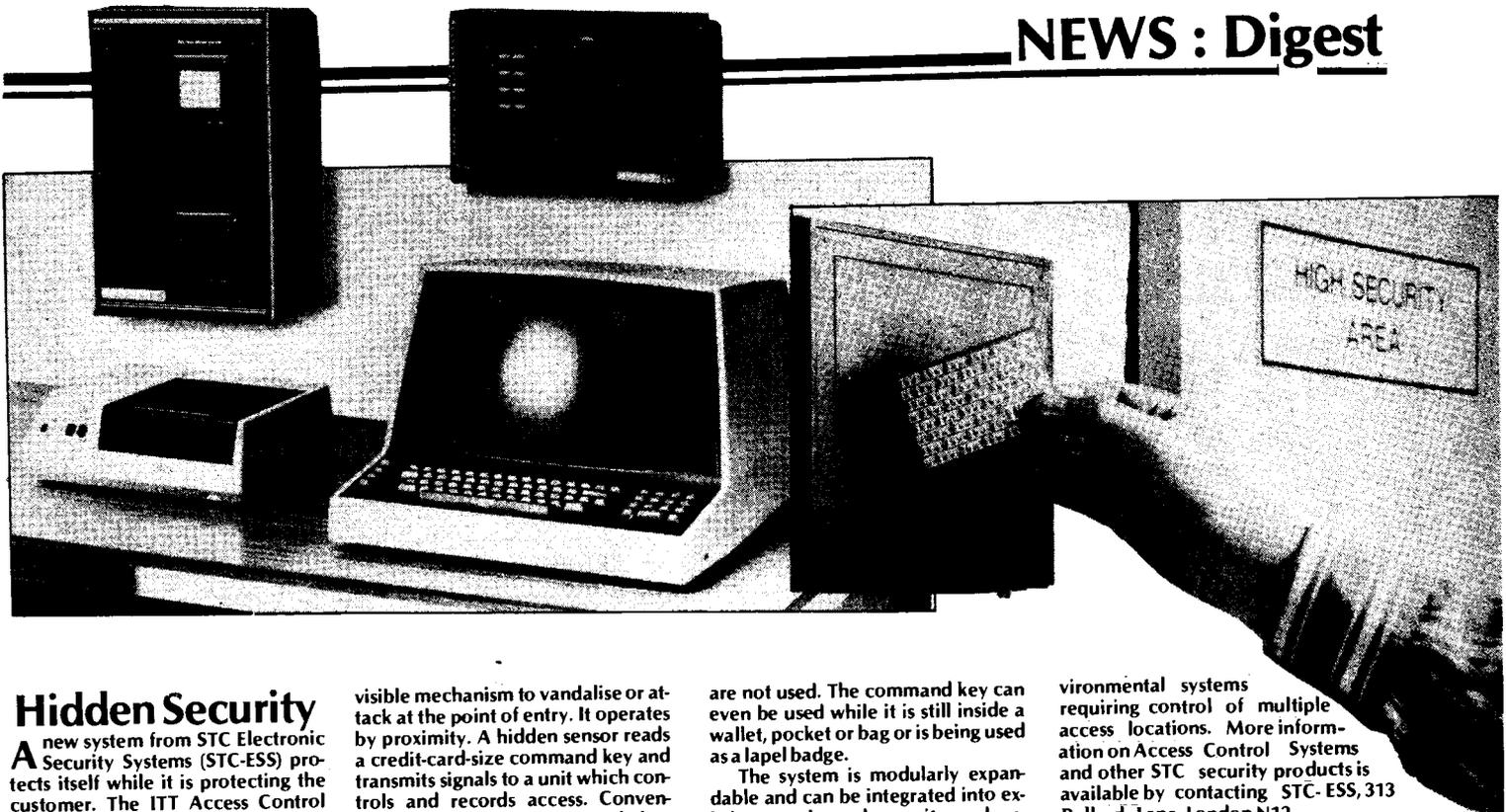

Hidden Security

A new system from STC Electronic Security Systems (STC-ESS) protects itself while it is protecting the customer. The ITT Access Control System, now marketed by STC has no

visible mechanism to vandalise or attack at the point of entry. It operates by proximity. A hidden sensor reads a credit-card-size command key and transmits signals to a unit which controls and records access. Conventional keys, key holes or card slots

are not used. The command key can even be used while it is still inside a wallet, pocket or bag or is being used as a lapel badge.

The system is modularly expandable and can be integrated into existing or planned security and en-

vironmental systems requiring control of multiple access locations. More information on Access Control Systems and other STC security products is available by contacting STC-ESS, 313 Ballards Lane, London N12.

Wire Cutting

If you've ever had an electrical fault in your Rolls, you're only too well aware of the jungle of wires that lurk beneath your bonnet, the colour coding cleverly hidden under years of crud. Ripault of Enfield in collaboration with Liverpool University's Dept. of Electrical Engineering and Electronics have addressed themselves to the sticky problem of cutting down the wiring harness to something a little more manageable.

The prototype has already been installed in a Maxi. It uses 10 m of twin core cable instead of 100 m of 130 separate leads used in the conventional Leyland harness. The wire links a number of electronic control boxes, one core carrying power and

the other digital control signals for the black boxes. Not only does this method cut down enormously the amount and complexity of the vehicle's wiring, but it also eliminates the use of high-current electro-mechanical relays which are subject to contact wear.


The system is designed to meet a B1 specification. Amongst the requirements are that the system should operate under the hostile environment of the engine compartment. That means surviving a temperature range of -40°C to +120°C.

Benefits of the new system include low power consumption, quick and convenient fault diagnosis and easier servicing. A security system could also be built-in.

IC Survival

Winslow Component Systems has introduced a new range of IC sockets designed to be virtually indestructible. The heart of the socket is a new contact featuring an inverted leaf design. This double-sided inverted leaf allows for a certain degree of careless handling when inserting an IC, which also facilitates the use of automatic insertion equipment. It is available in two

versions — the W3200 series, which has tin plated contacts, for the lower cost consumer type applications and the W3300, aimed at the industrial and professional market incorporating tin and gold plated contacts which are totally insulated from surface tracks on double sided PCBs. The W3300 is also 100% anti-wicking. Both versions come in the complete range of contact configurations from 8-40 pins, they are only 0.15" high and are moulded in UL approved glass reinforced polyester.

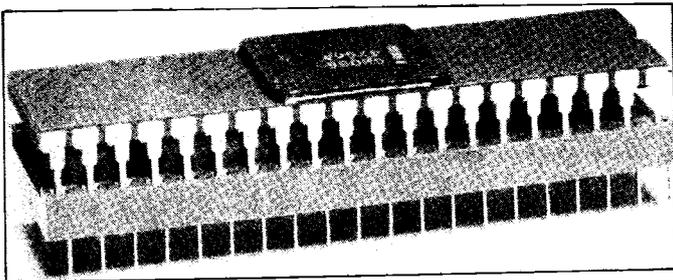


Teach Yourself Video

Have you invested in a video recorder, but haven't yet discovered its full potential? If the sole function of your recorder is to commit 'Crossroads' to tape, a new publication from 'those awfully nice Sony people' might widen your horizons. Their 48 page full colour handbook 'How To Video' is on sale

at their 134 Regent Street showroom in London for 60p (also by post for 90p).

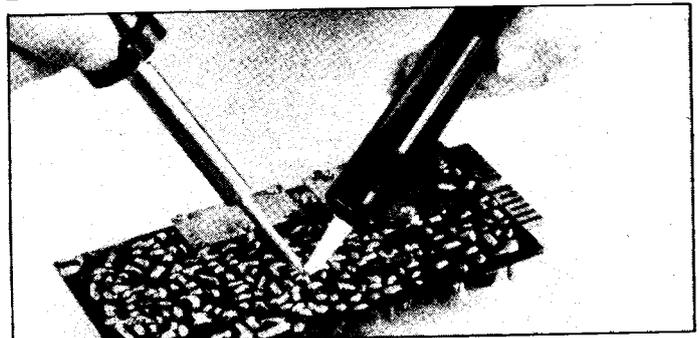Video recorders are very complex electronic devices, but are nevertheless simple to operate. 'How To Video' uses simple, non-technical language and ample illustrations to explain what your recorder is capable of, how to make home movies, the use of sound and lighting and even the creation of professional style, special effects and titling.



Suck It And See

New from OK Machine & Tool (UK) Ltd is the DSP-1 desolder pump. OK claim that it features industrial performance at an economy price. For about £6.00 you can arm your toolkit with this all-metal

device, with an easy-to-replace Teflon tip — self-cleaning on each stroke.

The DSP-1 desolder pump is supplied by OK Machine & Tool (UK) Ltd, Dutton Lane, Eastleigh, Hants SO5 4AA.

April Fair

Keep April 14th to 16th of 1981 free in your diary for the gathering of the clans in the Polytechnic of North London Theatre when the Association of London Computer Clubs hold their second London Computer Fair. For only 75p you can spend a day in North London in the

company of everyone who is anyone in personal computing. In addition to retail stands you can visit seminars, workshops and club stands. There's even a bring and buy sale. If you're within reach of a tube station, you're half way there. The venue, the Polytechnic of North London, is opposite Holloway Road tube station.

- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- CALL IN AND SEE FOR YOURSELF


AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL - MAIL ORDER - EXPORT - INDUSTRIAL
- OPEN SIX DAYS A WEEK

ALL PRICES INCLUDE VAT

SCOPES

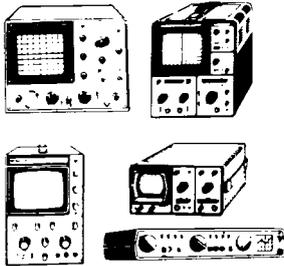A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace. Mains and Battery/Mains Portables. Many on demonstration.



SINGLE TRACE

(UK c/p etc £2.50)

- Hm 307-3 10mHZ, 5mV, 5 x 7 cm display plus component test **£158.78**
£109.25
 CO1303D 5mHZ, 10mHZ, 7 x 7cm display **£158.95**
 SC110 10mHZ battery portable, 10mV 3.2 x 2.6cm display (Optional case **£8.88**, Nicads **£8.83**, Mains unit **£4**) **£190.50**
 *LB0512A 10mHZ 10mV, 5" display **£190.50**
 *CS1559A 10mHZ 10mV, 5" display **£241.50**
 *V151 15mHZ 1mV 5" display

OPTIONAL PROBES (ALL MODELS)

X1 **£6.50**, X10 **£8.50**, X100 **£12.95**, X1-X10 **£10.95**

*PRICE INCLUDES FREE PROBE(S)

HAMEG ● TRIO ● LEADER ● SINCLAIR ● HITACHI


DUAL TRACE

(UK c/p etc £3.50)

- CS1562A 10mHZ, 10mV 5" display **£287.00**
 CS1575 5mHZ 1mV 5" display **£284.00**
 Hm 312-B 20mHZ 5mV B x 10cm display **£253.00**
 CS1566A 20mHZ, 5mV, 5" display **£339.00**
 *LBO 3085 70mHZ, 2mV, 5 x 6 3cm display. Battery/mains. Portable built-in Nicads **£482.00**
 HM412-4 20mHZ, 5mV, B x 10cm display plus Sweep Delay **£399.50**
 CS1577A 35mHZ, 2mV, 5" display **£478.00**
 CS1830 30mHZ, 2mV, 5" display plus sweep delay and delay line - new model **£589.00**
 Hm512-8 50mHZ, 5mV, 10 x 8cm display. Delay Sweep **£867.00**
 *LB0514 10mHZ, 1mV, (5mV) 5" display **£284.00**
 *V152 15mHZ, 1mV, 5" display **£328.00**
 *V302 30mHZ, 1mV, 5" display **£447.35**
 *V550 50mHZ, 1mV, 10 x 8cm Delay sweep + 3 channel display **£799.25**

GENERATORS RF

(UK c/p £1.75)

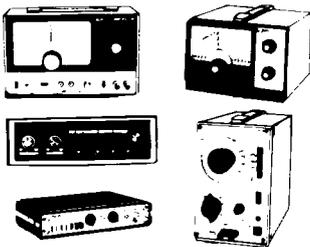

TRIO ● LEADER ● CSC
SINCLAIR ● LEVELL

- SG402 100 KHZ-30mHZ with AM modulation **£68.00**
 LSG16 100KHZ-100mHZ (300mHZ on Harmonics) **£83.25**
 SG2030 250KHZ-100mHZ low cost range **£46.95**
 ARF 300 18HZ-200mHZ low cost range audio and RF **£76.95**

PULSE

- 2001 1HZ-100KHZ (function) **£89.70**
 TG105 5HZ-5mHZ **£92.50**
 4001 0.5HZ-5mHZ **£109.25**
 TT100 (function 10KHZ) **£90.85**

AUDIO

(All sine / square)

- AG202A 20HZ - 200KHZ **£69.00**
 LG26 20HZ - 200KHZ **£73.60**
 AG203 10HZ - 1mHZ sine / sq **£126.75**
 LAG120A 10HZ - 1mHZ **£146.00**

LOGIC PROBES/MONITORS

Logic probes indicating high/low, etc., states that scopes can miss. All circuit powered for all ICs.

LP3 50 mHZ logic probe **£55.95**
 LP1 10 mHZ logic probe **£35.50**
 LP2 1 1/2 mHZ logic probe **£19.95**
 LM1 Logic monitor **£33.00**
 LDP 50 mHZ logic probe with case **£51.00**
 Also in stock range of Protoboard kits and breadboards.

'PRO' MULTIMETERS

- M1200 100K/Volt 30 ranges plus AC/DC 15 amp **£67.00**
 K1400 20K/Volt 23 range large scale **£79.95**
 M1500 20K/Volt 42 range plus AC/DC 10 amp **£53.50**
 (UK c/p £1.20)
 K200 38 range FET 10m ohm input 20HZ to 30mHZ multimeter **£95.00**
 (UK c/p £1.50)

SWR/FS AND POWER METERS




Range in stock covering up to 150mHZ and up to 1K watt power PL259 sockets. Also 250 UNZ Grid Dipmeter.

SWR9 SWR/S 3-150mHZ **£9.50**
 SWR50 SWR/Power meter, 3 1/2-150mHZ 0-1000 watts **£13.95**
 110 SWR/Power 1 1/2-144mHZ 0/10/100 watts **£11.50**
 171 As 110 Twin meter plus F/S **£14.50**
 Plus large range of BNC/PL259/etc leads / plugs / adaptors / connectors always in stock.
 176 SWR/Power/FS 1 1/2-144mHZ 5-50 watt **£16.60**
 KDMG Grid Dip 1 1/2-250mHZ **£38.50**

DIGITAL MULTIMETERS

KAISE ● SINCLAIR ● LASCAR ● THURLBY

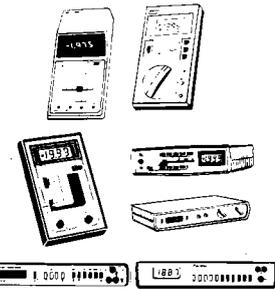A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors some with optional Nicads. All supplied with batteries and leads.



HAND HELD


- TM352 3 1/2 Digit LCD plus 10 ADC and Hfe checker **£54.95**
 TM354 3 1/2 Digit LCD 2A AC/DC **£45.94**
 ME502 3 1/2 Digit LED plus 10A DC and Hfe checker **£43.95**
 LM2001 3 1/2 Digit LCD 2 amp AC/DC 0.1 % **£51.70**
 6200 3 1/2 Digit LCD 0.2A AC/DC. Auto range **£45.95**
 6220 As 6200 plus 10A AC/DC **£55.95**
 6100 As 6200 plus Cont. test./range hold **£69.95**
 6110 As 6200 plus 10A AC/DC **£85.95**
 GL35C 3 1/2 Digit LCD 1A AC/DC with case **£37.50**

BENCH PORTABLES

- (UK c/p £1)
 DM235 3 1/2 Digit LED 21 ranges, 0.5% AC/DC 2A **£60.38**
 DM350 3 1/2 Digit LED 34 ranges AC/DC 10A **£87.38**
 TM353 3 1/2 Digit LCD AC/DC 2 amp **£96.60**
 TM351 3 1/2 Digit LCD AC/DC 10 amp **£113.85**
 LM100 3 1/2 Digit LCD AC/DC 2 amp **£86.50**
 DM450 4 1/2 Digit LED 34 ranges AC/DC 10 amp **£113.85**
 (DM series options. Carry case **£8.86** Nicads **£8.63** Mains adaptor **£4**)


MULTIMETERS

(UK post etc 75p)

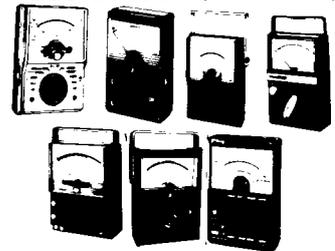

- KRT101 1K/Volt 10 range pocket **£4.60**
 ATM1/LT1 1K/Volt 12 range pocket **£5.98**
 NH55 2K/Volt 10 range pocket **£6.50**
 AT1 2K/Volt 12 range pocket de luxe **£7.75**
 NH56 20K/Volt 22 range pocket **£11.95**
 YN360TR 20K/Volt 19 range pocket plus hfe test **£13.50**
 AT1020 20K/Volt 19 range de luxe plus hfe test **£16.95**
 7081 50K/Volt 36 range plus 10 amp DC **£20.80**
 TR303TR 20K/Volt + 12A DC + Hfe test **£15.95**
 AT20 20K/Volt 21 range de luxe plus 10A DC and 5KV DC **£21.95**
 AT205 50K/Volt 21 range de luxe plus 10A DC **£24.95**
 7080 20K/Volt 26 range large scale, 10A DC plus 5KV AC/DC **£26.95**
 AT2050 50K/Volt 18 range de luxe plus hfe test **£28.50**
 AT210 100K/Volt 21 range de luxe 12A AC/DC **£29.95**
 360TR 100K/Volt 23 range plus hfe cvker and AC/DC 10 amps **£34.95**

FREQUENCY COUNTERS

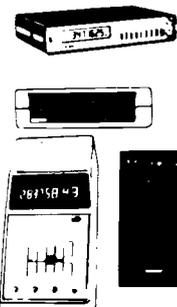

Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.

HAND HELD

- (UK post etc 85p)
 PFM200 20HZ to 200mHZ 8 Digit LED **£52.27**
 MAX50 100HZ to 50mHZ 6 Digit LED **£61.00**
 MAX550 30KHZ to 550mHZ 6 Digit LED **£106.00**

BENCH PORTABLES

- (UK c/p £1)
 MAX100 8 digit LED 5HZ to 100mHZ **£89.00**
 TF200 8 Digit LCD 10HZ to 200mHZ **£166.75**
 7010A 9 Digit LED 10HZ to 600mHZ **£169.00**
 200SPC 6 Digit 100mHZ LED built into 0.002HZ to 5.5mHZ Pulse Generator **£437.00**
 TP600 600mHZ Pre-Scaler for TF200 **£43.13**
 TF040 8 Digit LCD 60mHZ **£126.50**

CSC ● SINCLAIR ● SPC ● OPTO ELECTRONICS

SOLDERLESS BREADBOARD AND KITS

- EXP350 **£3.45**, EXP650 **£3.95**, EXP300 **£5.95**, EXP600 **£6.50**.
 KITS
 PB6 **£9.95**, PB100 **£12.95**, PB101 **£17.95**.

(UK c/p EXPs 30p, Kits 55p)

MINI DRILLS AND KITS

- (9-12 Volt 1 1/2" chucks)
 Small Drill plus 3 collets **£7.25**
 Medium Drill plus 3 collets **£10.50**
 Small Drill plus 20 tools **£14.95**
 Medium Drill plus 20 tools **£17.95**
 Mains Drill **£13.95**
 Mains Drill plus 20 tools **£21.50**

CHOOSE FROM UK'S LARGEST SELECTION

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export - prices on request ● All prices correct at 1.2.81 E & OE ● All prices include VAT



FREE CATALOGUE!
 Send large SAE (17 1/2p UK) Schools, Companies, etc. free on request.

AUDIO ELECTRONICS

Cubegate Limited

OPEN SIX DAYS A WEEK

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

electronics today

INTERNATIONAL

NEXT
MONTH



1024 COMPOSER

This machine will plug into the back of your synthesiser and allow sequences of up to 1024 notes to be played automatically. This Powertran design provides complete control of the starting and finishing points of the sequence, so several shorter tunes may be stored in the memory simultaneously. Both pitch and note length are fully programmable and rests may also be entered.

IR REMOTE CONTROL

As promised last month, we present a five-channel infrared remote control system which will interface with last month's Noiseless Power Switch. The unit has three latching channels (ie push-on, push-off), two non-latching channels, and a range of up to 30 feet. Full constructional details of both the transmitter and receiver will be given.

SOLDERING IRON

A DIY design for a thermostatically-controlled soldering iron that is a must for any serious constructor. If you've ever cursed your unwieldy welding device, you'll be glad to know that with our tiny version your fingers are only 1½" from the bit for precision control. The iron runs from a switched-mode power supply at only 3 V, so it's completely safe for soldering CMOS — with a continuous temperature range up to 500°C, built-in light, interchangeable tips and a price one-fifth of a commercial equivalent, you can't afford *not* to build one.

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

ETI APRIL 1981

TOUCH DIMMER

This project makes light work of lamp dimming. Based on the S566B IC, it provides touch control of brightness and a memory that turns the light on at a pre-determined level. The big difference with this design is that it can be used with the IR remote control and still retain all the normal functions. The remote control unit can operate two of these dimmers.


POWER SWITCH

For those of you who don't need the low noise and high current capability of the Noiseless Power Switch, we're publishing a cheap power switch that will handle a current of 5 A and interface with the IR remote control. Up to three of these switches can be controlled by the IR transmitter.

SONIC HOLOGRAPHY

Surround-sound in your living room! No, your eyes don't deceive you — the speakers are in front of you. No, your ears don't deceive you — sounds to the left of you, to the right, behind and above you. Find out more in next month's ETI.

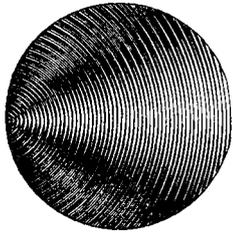LOOK OUT FOR THE
MAY ISSUE ON SALE
APRIL 3rd




thandar
STOCKIST

B.K. ELECTRONICS

A SOUND CHOICE

thandar
STOCKIST

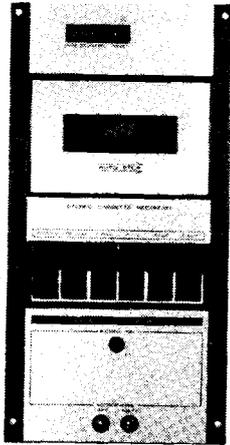★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY




6 piano type keys

STEREO CASSETTE TAPE DECK MODULE.

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record,rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input sensitivity:** 100mV to 2V. **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5½in x 11¼in. Clearance required under top panel 2¼in. Supplied complete with circuit diagram and connecting diagram.

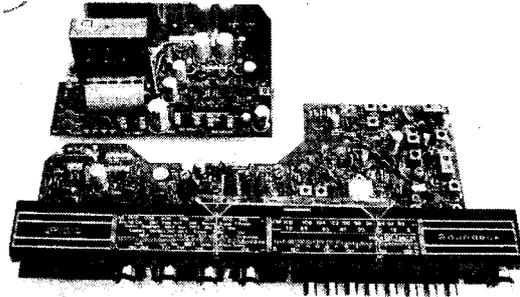Price £25.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) **£3.00.**



GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS.

Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms, 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3dB.


Tape Sensitivity: Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz — 108MHz. Long wave 145kHz — 108kHz. Medium wave. 520kHz — 1620kHz. Short wave. 5.8MHz — 16MHz. **Size:** Tuner — 2¼in x 15in x 7½ in approx. Power amplifier — 2in x 7½in x 4½in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £23.50 plus £2.50 postage and packing.**

NEW RANGE QUALITY POWER LOUSPEAKERS (15", 12" and 8").

These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons.

Specification and Price:—

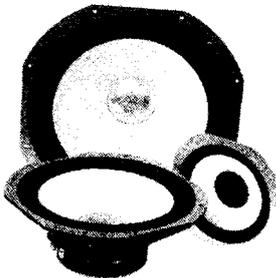15" 100 watt. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.



12" 100 watt. Impedance 8 ohm. 50 oz. magnet. 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

8" 50 watt. Impedance 8 ohm. 20 oz. magnet. 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. **Price £8.90 each.** £1.25 Packing and Carriage each.

PIEZO ELECTRIC TWEETERS — MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover **is not** required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**


Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.45 each.**

Type 'B' 3½in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**


Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**

Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £6.90 each.**

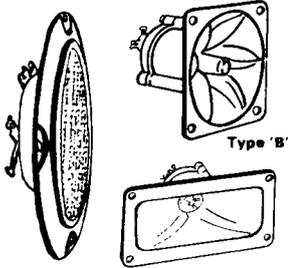Post and Packing, all types, 15p each (or SAE for Piezo leaflets).



Type 'A' Type 'C' Type 'D'

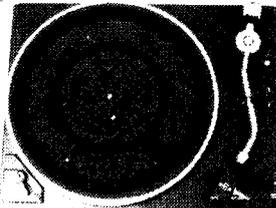


JVC TURNTABLE.

JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

- ★ 'S' shaped tone arm.
- ★ Belt driven.
- ★ Full size 12in platter.
- ★ Precision calibrated counterbalance weight (0.3 grms.)
- ★ Anti-skate (bias) device. Nylon thread weight.
- ★ Damped cueing lever.
- ★ 240V AC operation. (50Hz).
- ★ Cut-out template supplied.
- Size — 12¼in x 15¾in (approx).

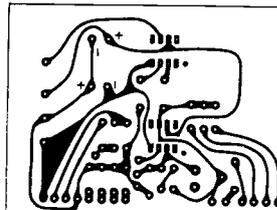Price £28.50 plus £2.50 postage and packing



COPPER LAMINATED PRINTED CIRCUIT BOARD (single sided).

Paxoline based type. Size 15½" x 12¼". Brand new. Still shiny and bright. **£1.25 per sheet.** Post free.

FIRE ALARM CENTRAL CONTROL UNIT (S.T.C.)

Ideal for Fire or Burglar Alarm Systems

- ★ Responds to normally open or closed switches (or smoke detectors etc)
- ★ Complete with an internal EXIDE lead acid accumulator (dry charged) as a back-up for mains failure. This is trickle charged
- ★ 6v-2 amp output for Fire/Burglar alarm, etc
- ★ Re-set button for silencing Fire/Burglar alarm
- ★ Internal buzzer which sounds if re-set button if pressed until initiating switch is cleared.
- ★ Wall mounting, complete with red case, approx. 11" x 7½" x 4"
- ★ 240v AC operation.

LOUDSPEAKER


High quality full range 8" loudspeaker 15 watts RMS 8 ohm. Rolled surround with aluminium centre dome **Price £3.75 each + £1.** Postage and Packing each.



B.K. ELECTRONICS


37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

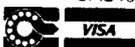★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



KIT REVIEW

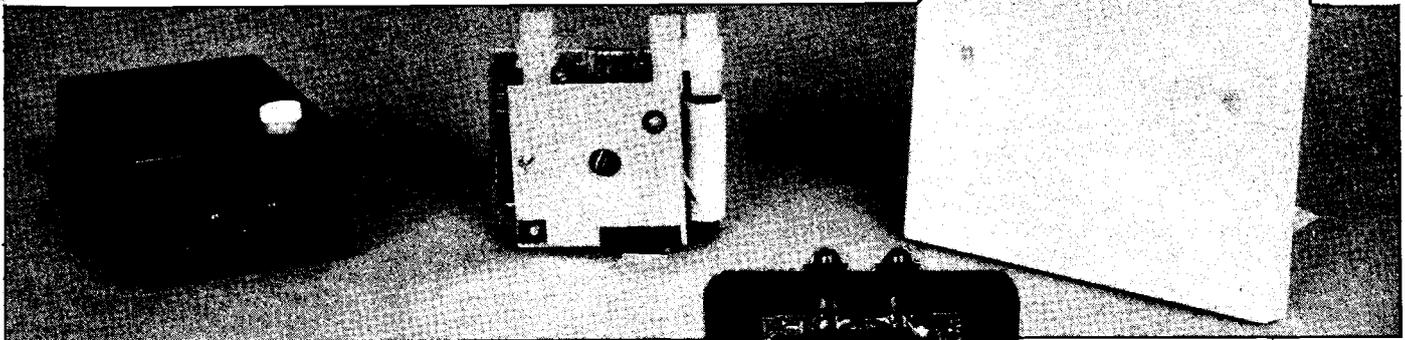There are many adverts about for build-it-yourself electronic kits — everything from door chimes to hi-fi. But do they represent value for money? This new series finds out for you.



This is the first in a new series of articles, designed to look in detail at some of the DIY kits available on the market, particularly those which yield a useful item for the home or car when completed.

We will be paying close attention to ease of construction — which includes a consideration of the clarity of the instruction leaflets provided. Anyone reading this who produces a kit which they feel might be suitable, is asked to ring the editor at our office number and we'll take it from there.

Taking A Dim View!

For our first month we're having a look at TK Electronic's remote controlled light dimmer, which sells for around £20. The kit comprises two separate units, a touch operated light switch and an IR (infra-red) control box. The dimmer can be constructed initially with straightforward touch operation, and the IR option added later.

The dimmer itself uses the 566 IC, which allows for a neat little circuit with 'memory' capability. Turn on the light by touching the plate and it will assume the level of brightness you last set it at. Holding a finger on the plate will cause the level to cycle between maximum and minimum brightness.

To add the IR facility an external photodiode is fitted to the mounting plate (see photo). This then produces full operation from the hand-held unit. The latter is little more than a multivibrator and two IR LEDs. A neat little black plastic box is provided, predrilled, for mounting the controls.

Constructive Thinking


The instructions provided with the kit are well explained, but could be better presented. A separate sheet is included with details of different types of electronic components and some helpful hints on soldering.

These serve as a general construction guide, the detailed building notes for a specific project being pretty sparse. This, together with the very high component density found on the PCB, makes me think that an absolute beginner would find the dimmer a difficult task. As this is a mains circuit, best make a start in electronics elsewhere.


Having said that, anyone who has built a few magazine projects would find the kit relatively simple to put together,



How to connect photo-diode D8 to P.C.B.

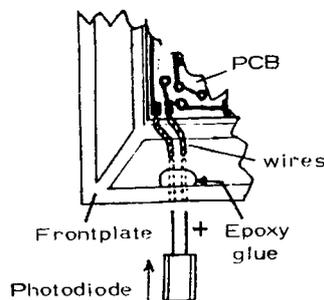

P.C.B. LAYOUT

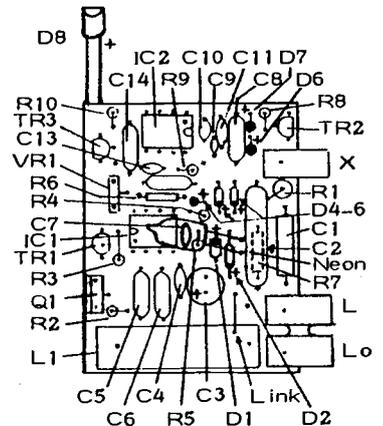

Above left: the assembled transmitter. Note the shaky PCB fittings. Above and right: examples from the well-explained notes. Diagrams are basic, but well thought out. Instructions are generally adequate for the constructor with a little experience.

although care will still be needed in soldering up the PCB, however experienced you may be!

Assembly of the hand controller is very simple indeed, as there are only some eight components involved! The push button is PCB mounted, as are the LEDs. One point about the controller that I did not like was the fact that the LED leads are used to secure the PCB into the box. This means that every time the push button is operated, the leads are stressed unnecessarily. Also the box is a fraction too narrow to admit a PP3 with a battery clip fitted. Thus, it has to be laid along the case which means in turn that it is effectively jammed against the PCB — again putting stress upon the LED leads!

Built And Working

Assembly took about two hours, including the time required to sort out the components initially. No "sillies" manifested themselves from the instructions and the kit was complete as supplied.

Once built the unit functioned first time and the notes provided on installation and use were clear and concise. Take some care with the choice of wiring box you use for mounting the kit, though, as it is fairly deep and will protrude some 35 mm behind the front plate when fitted.

In use the dimmer functioned perfectly at all times, with the photodiode having a good wide acceptance angle. Range is about 30 ft — more than most living rooms I would have thought.

Conclusions


Overall a good design. The circuit is neat and well thought out and the PCB design quite a feat of miniaturisation! However, this does tend to mean that the kit is best suited to someone with some previous constructional experience.

The unit represents reasonable value for money and can be confidently recommended.


RON HARRIS

BUYLINES

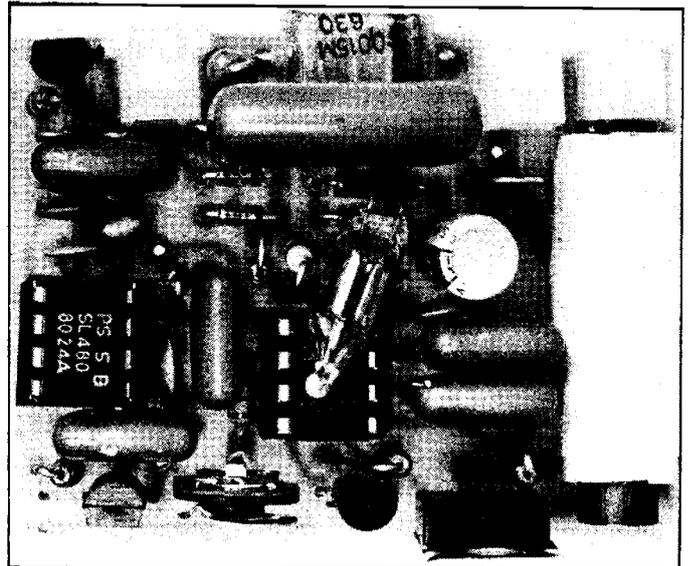TDR300K Touch Dimmer Kit £14.30 + VAT (+ 40p P&P per order),
MK6 Infra-red Transmitter £4.20 + VAT. TK Electronics, 11 Boston
Road, London W7 3SJ. Tel: 01-579 9794.



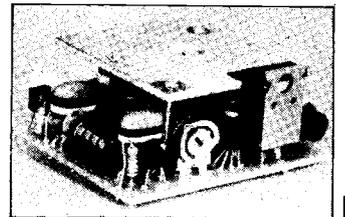Above: the main PCB assembled — note the bulb fitting. This is to ensure that it lines up with the hole in the touch plate, shown fitted (right photo). The board is somewhat crowded in places and care needs to be exercised when soldering.



ETI

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T. V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK — THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

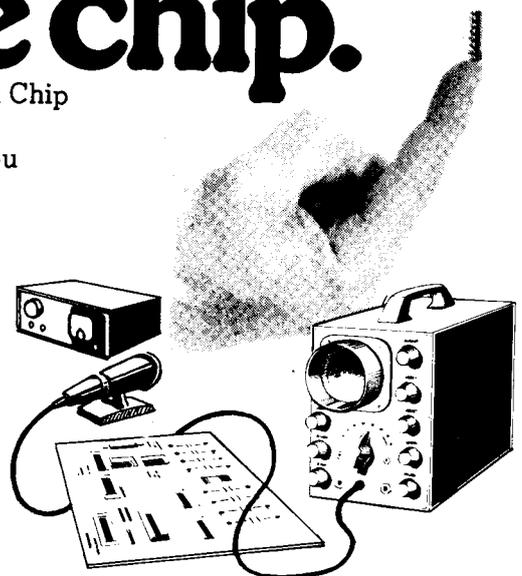- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators — Digital Meters etc.




ENRME	Please send your FREE brochure without obligation to:	Full Name (in block letters)
	Name (in block letters)	PRACTICAL ELECTRONICS
	Address	COMPUTER TECHNOLOGY
	OTHER SUBJECTS

PLEASE PRINT IN BLOCK CAPS PLEASE


BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS. ETI 4/813

You can't beat The System.

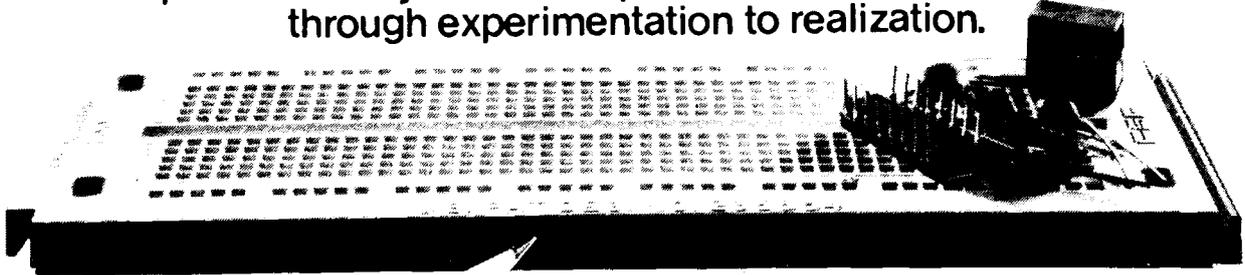
The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard

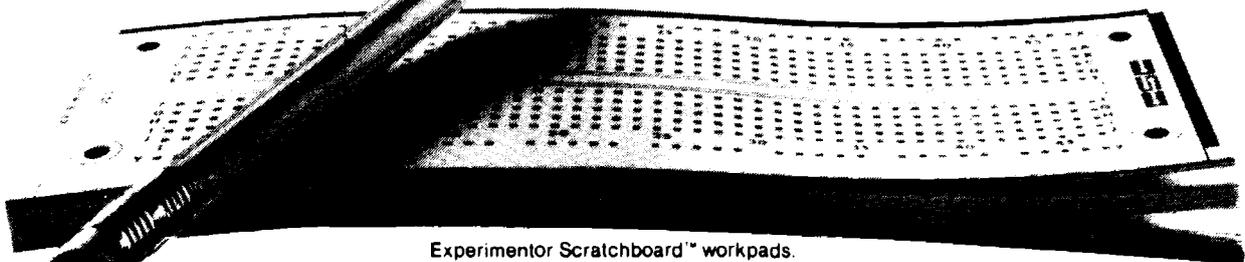

Experimentor Scratchboard™ workpads.

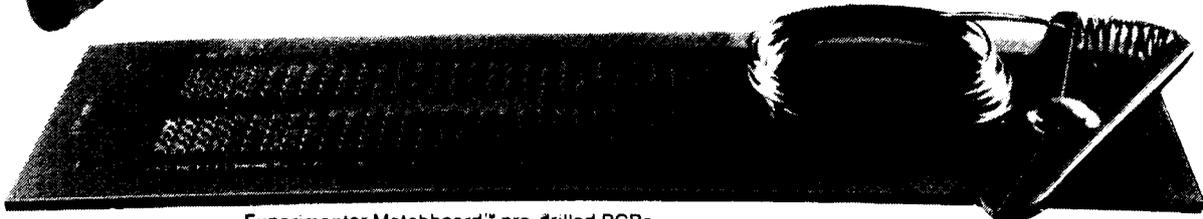

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item * A Matchboard pre-drilled PCB £1.20	2. EXP-302, which includes three items Three 50-sheet Scratchboard workpads £1.50	3. EXP-303, which includes three items Two Matchboards and an EXP-300 solderless breadboard £7.60	4. EXP-304, which includes four items Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad £8.70
---	--	--	--

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited
Dept. 9W Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

GLOBAL SPECIALTIES CORPORATION, DEPT. 9W
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex

Name _____

Address _____

Inc P&P and 15% VAT

1. EXP 300PC £2.25	Qty Reqd	2. EXP 302 £2.58	Qty Reqd
3. EXP 303 £9.90	Qty Reqd	4. EXP 304 £11.15	Qty Reqd

FREE Catalogue tick box
I enclose cheque- PO for
£ _____

Phone your order with Access, Barclaycard or American Express

Card No. _____ Expiry date _____

New from Casio, world leaders in creative technology combined with high quality and reliability

JOIN THE KEYBOARD REVOLUTION!

For everyone music has its own meaning. It is to capture the true values of music that Casio have spent years of research and development efforts. They bring to life beautiful sound experiences never before available. A new generation of tone-true electronic sounds of vivid realism — the composition of a fresh musical system.

By closely analyzing the natural sound variations in the waves and pitches of different instruments, Casio have been able to trace the characteristics peculiar to each traditional instrument. Pitch, timbre and harmonics have been measured, digitalised and stored in electronic chip memory for faithful and exciting reproduction of the clarity and beauty of the originals.

CASIOTONE 401



RRP £345
ONLY £295*

Full polyphonic 8-note playing of 14 instruments and sounds over 4 octaves.

Rhythm accompaniment. 16 different rhythms with full-in auto-rhythm.

Casio Auto Chord. Allows one finger accompaniment. Just press a key with a single finger and play major, minor and seventh chords, with bass accompaniment, automatically. Combines with auto-rhythm for professional sounds.


Vibrato, Delayed vibrato, sustain and hold are incorporated in the at-a-glance, simple to use operational panel. Pitch control makes group tuning easy. Compact 4 1/4" x 3 1/8" x 1 1/2" inches with integral amplifier and speaker. The light weight (28.2lb) allows playing anywhere there is an A.C. socket. Stand £39.

CASIOTONE 301

The same size and basic specification as the 401 above, the 301 does not have Casio Auto Chord or built-in sustain and hold facilities. There are 8 rhythm voices with a variation on each. Weight 27lbs.

£245*

CASIOTONE MT-30

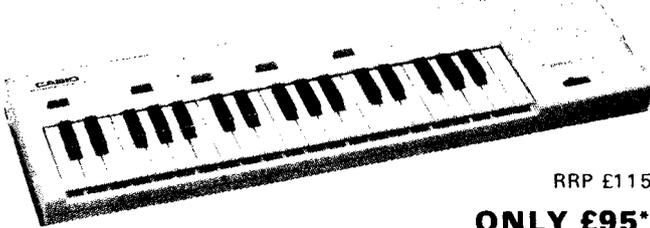

RRP £115
ONLY £95*

Full polyphonic playing of 22 instruments and sounds over 3 octaves. 4-position sound memory lets you switch between pre-selected sounds without pause. Built-in vibrato and sustain functions greatly enhance the overall musical effect. Compact 2 3/4" x 2 1/4" x 6 1/2" inches, with built-in amplifier and loudspeaker. Battery / mains power source and light weight (6lb) allows playing anywhere.


CASIOTONE 201 and M-10

Please telephone for availability.
201: Mains version of the MT-30. 29 instruments over 4 octaves

£245*
£69*

M-10: 4 instruments over 2 1/2 octaves. Battery / mains.

CASIO BQ-1100 BIOLATOR/ WATCH

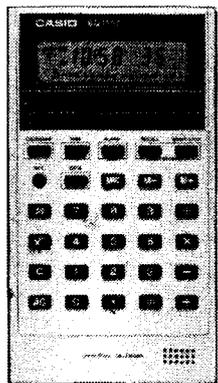

Clock, calendar, 2 alarms, countdown alarm stopwatch, time memory, three date memories, biorhythm and date calculations, calculator

Clock. Hours, minutes, seconds, am/pm, Day/date. Universal calendar. Pre-programmed 1901 to 2099. Day, date, month and year display

Alarm. Two separate alarms. 24-hour system.

Countdown alarm. 1/10 second to 24 hours, or

Stopwatch 1/10 second to 24 hours. Net times, or

Time memory. Dual time facility. 24-hour system.

Calculator. 8 digits. Full memory. Sq roots, %. Date calculations. Any monthly calendar from 1901 to 2099 can be displayed and utilised.

Biorhythm calculations. Forecast your physical, emotional and intellectual performance potential. Chart your peak, ebb and critical days and reschedule to avoid mistakes. Two silver oxide batteries last approx 1 year.

Dims: 1/4 x 2 7/16 x 4 3/8 inches. Leatherette wallet.

ALL THIS FOR ONLY £14.95*


MG-880 SPACE GAME/CALCULATOR

Our best selling calculator. Thousands sold! An action packed speed game that will give you hours of skilful entertainment and chair-gripping excitement. Also an 11-note melody calculator with full memory. %.

KEEP A DATE WITH CASIO

You always wanted a musical calculator with date memories and date/time alarms — HERE IT IS!

UC-365 UNIVERSAL CALENDAR

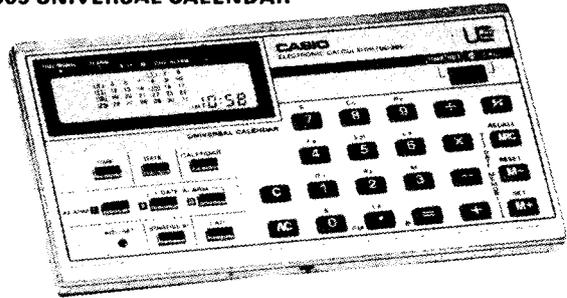

Clock, universal calendar, date memories, daily alarm, 2 daily or date/time alarms, hourly chimes, stopwatch, countdown alarm, time memory, calculator.

Clock display: Hours, minutes, seconds, am/pm, or hours, minutes, full calendar.

Calendar: Pre-programmed from 1901 to 2099. Full month display.

Date memories: Any day or days pre-settable within 12-month period. (Birthdays, etc.)

Alarms: Alarm 1 — Daily alarm Alarm 2 & 3 — Daily alarms or time alarms on pre-set dates. (Pre-programmed melodies or electronic buzzer.)

Stopwatch: 1/10 second to 24 hours; net, lap and first and second place. Or

Countdown alarm: 1/10 second steps, settable in minutes up to 24 hours. Or

Time memory: 24 hour system. The time of any other zone can be stored.

Calculator: Optional musical keys, full memory and percentage.

Two silver oxide batteries last approx. 1 year. RRP £22.95

1/4 x 4 1/2 x 2 1/2 inches. Leatherette wallet with window

£19.95*

UC-360. Card sized version of above. 7/32 x 3 3/8 x 2 3/8 inches

£19.95*

UC-3000. Office desk version. Angled display. 1 1/4 x 4 x 6 1/4 inches

£27.95*

CASIO'S AMAZING NEW FX-3500P


Programmable. Non-volatile memories and stores. Statistical regression and integrals.

38 functional (non-volatile) steps. 2 programme storage capability. Unconditional and conditional jumps. 7 (non-volatile) memories, one independent. 6 constant memories. 18 pairs of parentheses, nestable in 6 levels.

61 built-in functions, including Integrals (Simpson's rule). Linear regression, logarithmic regression, exponential regression and power regression.

Hyperbolics, sexagesimal and co-ordinates conversions. 10 digit mantissa or 10 + 2 exponent. Two silver oxide batteries give approximately 1,000 hours continuous use with power-saving automatic cut-off, with data and memory protection.

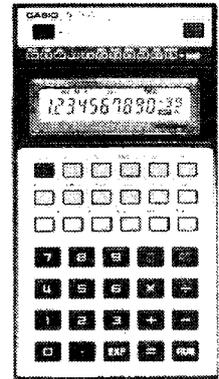Dims: 9/32 x 2 1/8 x 5 1/4 inches. Supplied with leatherette wallet.



ALL THIS FOR ONLY £22.95*

FX-180P. Hand held version without hyperbolics. 2 x AA batteries: 3/4 x 3 x 5/8

£19.95*

FX-2700P. As FX3500P but 8+2; without integrals, regression. 1 programme

£19.95*

FX-8100. Scientific with clock, calendar, alarm, chimes, stopwatch, etc

£24.95*

CASIO'S BEST SELLING WATCHES



AA81



M1200



W150B

LCS ANALOGUE / DIGITAL ALARM CHRONOGRAPH with countdown alarm.

AA-81 chrome, s/s bracelet £29.95. AA-81G. Gold plated £49.95. AA-82. All s/s £39.95.

12 MELODY ALARM CHRONOGRAPHS with countdown alarm. M-12 resin case / strap

£24.95. M1200 all stainless steel £29.95.

100 METRE WATER RESISTANT Alarm chronographs with countdown alarm. W100.

Resin case / strap £19.95. W150C Stainless steel case / resin strap £25.95. W150B

Stainless steel case / bracelet £32.50.

Send 20p (postage) for our illustrated catalogue of Casio and Seiko.

***PRICES**

We will beat any lower advertised price by 5% providing we still make a profit! Just send details and your remittance for the lower amount. Prices include VAT and P&P.


Price includes VAT, P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. ET1, FREEPOST, 164-167 East Road, Cambridge CB1 1DB. Tel: 0223 312866

VISUAL COMPLEX SOUND ANALYSER

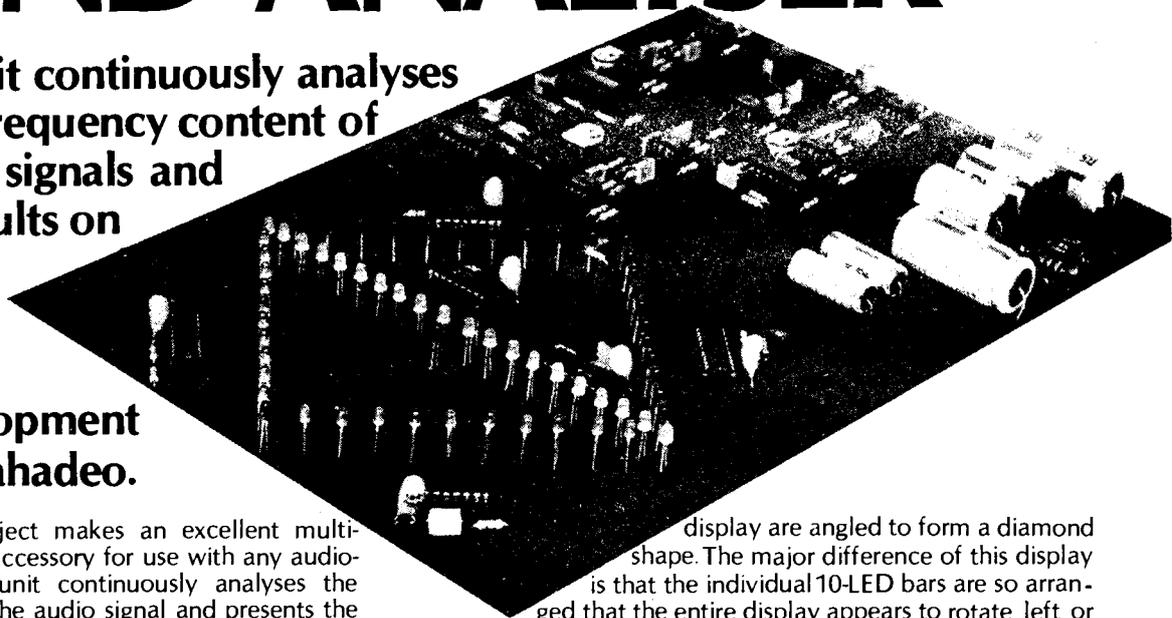This unusual unit continuously analyses the amplitude/frequency content of complex audio signals and presents the results on a multi-colour 60-LED display. Design by Ray Marston. Development by Steve Ramsahadeo.



This very unusual project makes an excellent multi-colour visual display accessory for use with any audio-output system. The unit continuously analyses the complex sound content of the audio signal and presents the results of the analysis, in three colours, on six 10-LED bar displays arranged as a diamond with a diagonal. Naturally, in the presence of music, etc., the displays bounce and sway in sympathy with the analysed contents of the audio signal and present an attractive moving display.

The Visual Complex Sound Analyser display unit is mains powered and receives its audio input signal from the output (speaker) of the system under test. The audio signal is actually analysed in the form of three overlapping audio bands, having nominal 3 dB points of 20 Hz — 120 Hz (red display), 250 Hz — 2 kHz (yellow display), and 2 kHz — 7 kHz (green display). The upper three 10-LED bars each move in 3 dB steps and display the instantaneous signal amplitudes of the three audio bands. The lower three 10-LED bars move in linear steps and display the instantaneous dominant frequencies of the three bands.

The Display

This is a project where the skilled constructor might like to experiment with alternative display-pattern layouts. Our development prototype unit was originally built up on Veroboard and had a display in which the six 10-LED bars were arranged as three parallel 20-LED lines, each representing a specific colour-coded frequency band, with the upper half of the display showing amplitude and the lower half showing instantaneous dominant frequencies. On this unit, the central 'reference' bar (four LEDs) of the display represents zero amplitude/frequency, so that each of the three display lines appears to expand and contract from its central point.

On the final PCB version of the unit we've changed the display to the form shown in the photographs. Here, the display is again in the form of three 20-LED lines, each representing a specific colour-coded frequency band, with the upper half of the display showing amplitudes and the lower half showing dominant frequencies, but in this case the two outer lines of the

display are angled to form a diamond shape. The major difference of this display is that the individual 10-LED bars are so arranged that the entire display appears to rotate left or right in sympathy with the music, rather than simply expand or contract. Thus, on the low-frequency (red) band the two 10-LED bars expand downwards with increasing amplitude/frequency, whereas on the high-frequency (green) band the two 10-LED bars expand upwards under the same condition; the central (yellow) band expands in a downwards direction. If you've got any better ideas, feel free to do your own thing.

Construction

The entire circuit, with the exception of mains transformer T1 and pot RV1, is built up on a single large (12 x 8 inches) PCB. On our prototype we've coated the entire top surface of the PCB with navy-blue flock paper, to enhance the visual appeal of the unit: if you wish to do the same, proceed as follows.

- (1). The PCB uses a fairly large number of bridging links on the top side of the PCB, as well as several long links on the underside; these underside links are facilitated by Veropins (marked on the overlay as A, B, C, etc) pushed through the board from the top side. The underside links are completed by joining A to A, B to B, etc. To start the construction, drill all holes to accommodate the wire links and the Veropins, then insert the links and pins from the component (upper) side of the PCB and solder into place.
- (2). Now coat the entire upper surface of the PCB and the lower side of the flock paper with cow gum, allow ten minutes to set and then press the paper evenly into place and trim the outer edges.
- (3). Next, drill all remaining holes in the PCB and then proceed with the construction in the normal way, taking extra care to observe the polarities of all semiconductor devices (particularly IC17 and IC18) and electrolytic capacitors. Take special care to check the functioning/polarity of all LEDs before soldering them into place and note that the LEDs *must* be of the colours

shown in the circuit diagram. Don't forget to connect the (several) links on the underside of the PCB.

When the construction is complete, double-check all wiring, connect the unit to RV1 and T1 and then switch on. Initially, only the central 4-LED 'bar' should illuminate. Now connect the unit to an audio (music) source and check that the unit is functioning by adjusting RV1 to give a display that behaves in the manner already described.

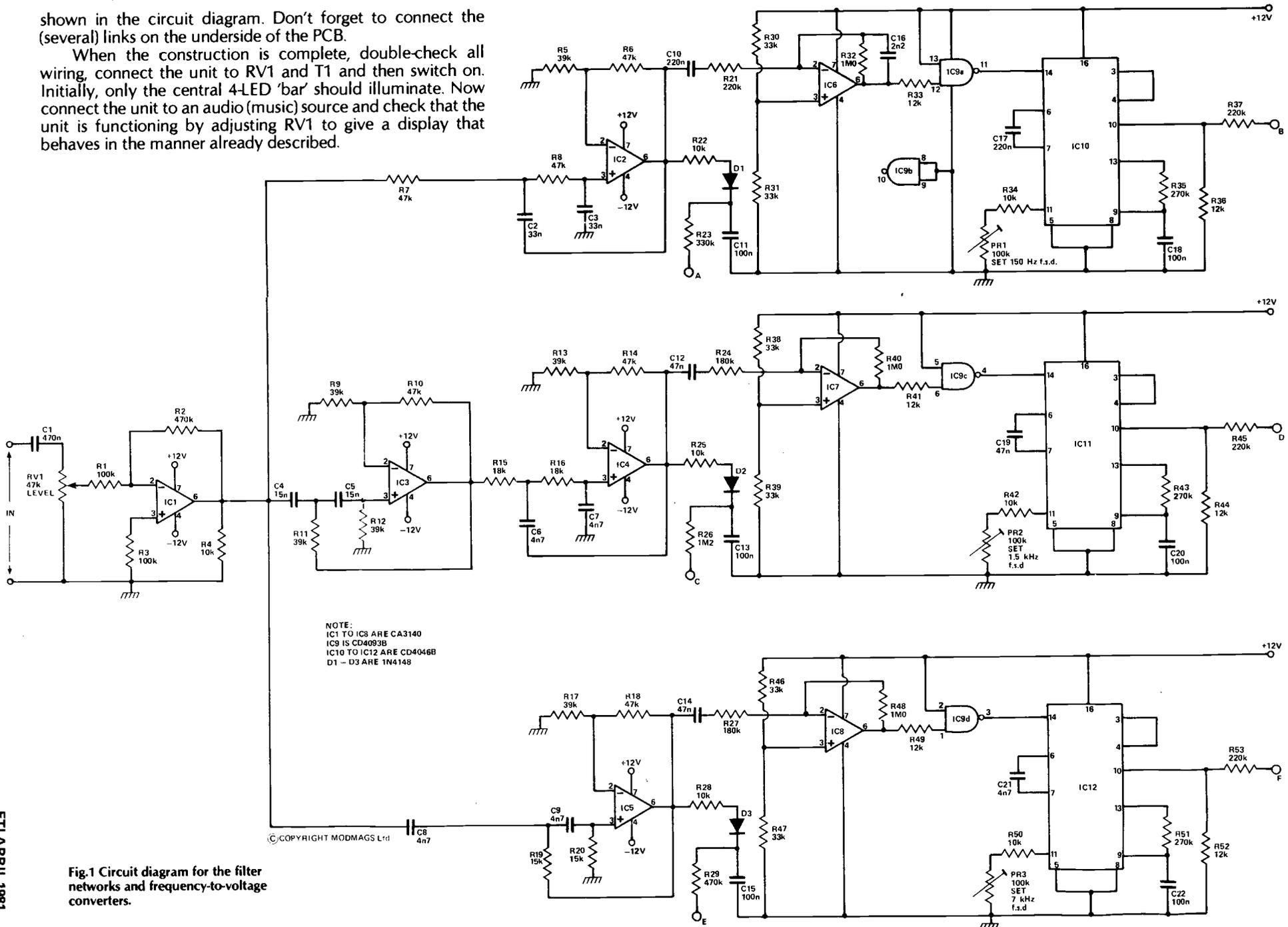


Fig.1 Circuit diagram for the filter networks and frequency-to-voltage converters.

HOW IT WORKS

The audio input signal is fed, after a simple 'level control' (RV1-IC1), to a multiple filter network, which divides the complex input signal into three distinct (but overlapping) bands. The lowest band has an upper 3 dB cut-off frequency of 120 Hz and operates in the low-pass mode (IC2). The middle band operates in the band-pass mode (using high-pass filter IC3 and low-pass filter IC4) and has lower and upper cut-off points of 250 Hz and 2 kHz respectively. The upper band operates in the high-pass mode (IC5) and has a lower cut-off point of 2 kHz.

The output of each filter is peak-detected and filtered by a rapid-charge slow-discharge network (R22-D1-C11-R23-R56, etc) and passes to the input of a 10-LED 'amplitude indication' display. These displays are based on LM3915 dot/bar drivers and give a log display in 10 3 dB steps: they are set, via pins 6-7, to read full scale at 1.2 V. The outputs of the rectifier networks are fed to the inputs of the LM3915 drivers via fixed potential divider networks (R23-R56, R26-R60, and R29-R64), the values of which have been calculated to compensate for differences in the gains of the three sets of filters.

Note that in the LM3915 circuits the ICs are powered from a 12 V supply, but the LED chains are driven from a 24 V supply. The ICs are wired to operate in the 'dot' mode (via pins 9 and 11), but the 10 LEDs in each chain are wired in series; consequently, the LEDs produce a 'bar' display with the LEDs that are on passing a common current. Thus, the LED current consumption is constant, irrespective of whether one or 10 LEDs are turned on.

The low-frequency level indicator (IC13) uses red LEDs, the mid-band indicator (IC15) uses yellow LEDs and the upper indicator (IC17) uses green LEDs. To give an equal brightness to all three colours, the LED drive current of each LM3915 is weighted by the resistor connected to pins 6-7. The red LEDs pass approximately 8 mA, the yellow pass 18 mA and the green pass 25 mA.

The output of each of the three audio filters is also fed to a frequency-to-voltage converter network, and the instantaneous frequency is subsequently displayed on another line of 10 LEDs by LM3914 linear drivers. These drivers are again operated in the dot mode with a bar display and are current-weighted.

Each frequency-to-voltage converter operates as follows. The output of each audio filter is amplified (by IC6, etc) and converted to a square wave by one of the IC9 Schmitt gates. The resulting square wave signal is fed to the input of a phase-locked loop (PLL) circuit (IC10, etc) and compared with an externally set reference frequency (set by C17-R34-PR2, etc). The PLL incorporates a phase comparator and a voltage-controlled oscillator (VCO). The output of the comparator is coupled to the input of the VCO via a simple filter network (R35-C18) and the VCO input voltage is made available, via an internal buffer, at pin 10. As the PLL tries to track the rapidly-shifting input signal, it generates a signal at pin 10 that is proportional to the instantaneous frequency of the input signal (0 V at zero frequency, 12 V at the reference frequency, etc). The output signal of each PLL circuit is fed to the input of its respective LM3914 display driver via a simple potential divider network (R37-R57, etc).

The total of six 10-LED displays are arranged in three pairs, each of a different colour and each displaying the instantaneous amplitude (upper LEDs) and frequency (lower LEDs) of a specified audio band. A bar of four red LEDs is mounted horizontally across the centre of the display, to enable the amplitude and frequency areas of each band to be readily distinguished.

The complete unit uses + 24 V, + 12 V and - 12 V supply rails, each regulated by an IC.

The unit incorporates only three preset controls (PR1, PR2, PR3), which are used to set the full-scale reading of each frequency display (150 Hz, 1.5 kHz and 7 kHz). Figure 5 shows a simple circuit which can be used to generate suitable reference signals when initially calibrating the unit. The circuit is a basic astable, with its frequency determined by the C1-R2-R3-R4 values; the circuit can be easily built on a spare piece of Veroboard.

Fig.2 Block diagram of the complete circuit.



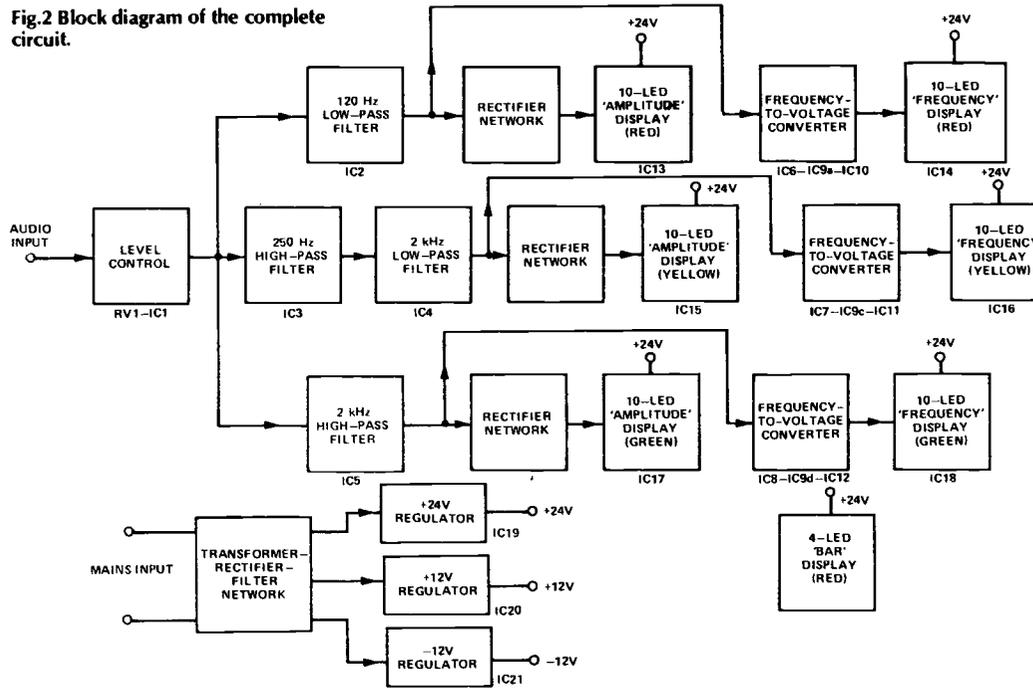


Fig.3 Circuit diagram of the power supply section.

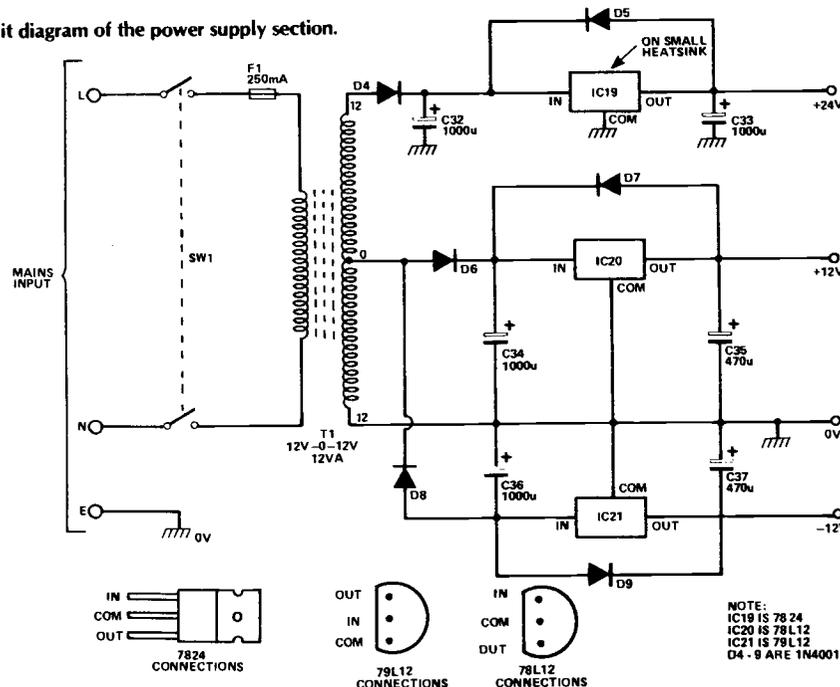


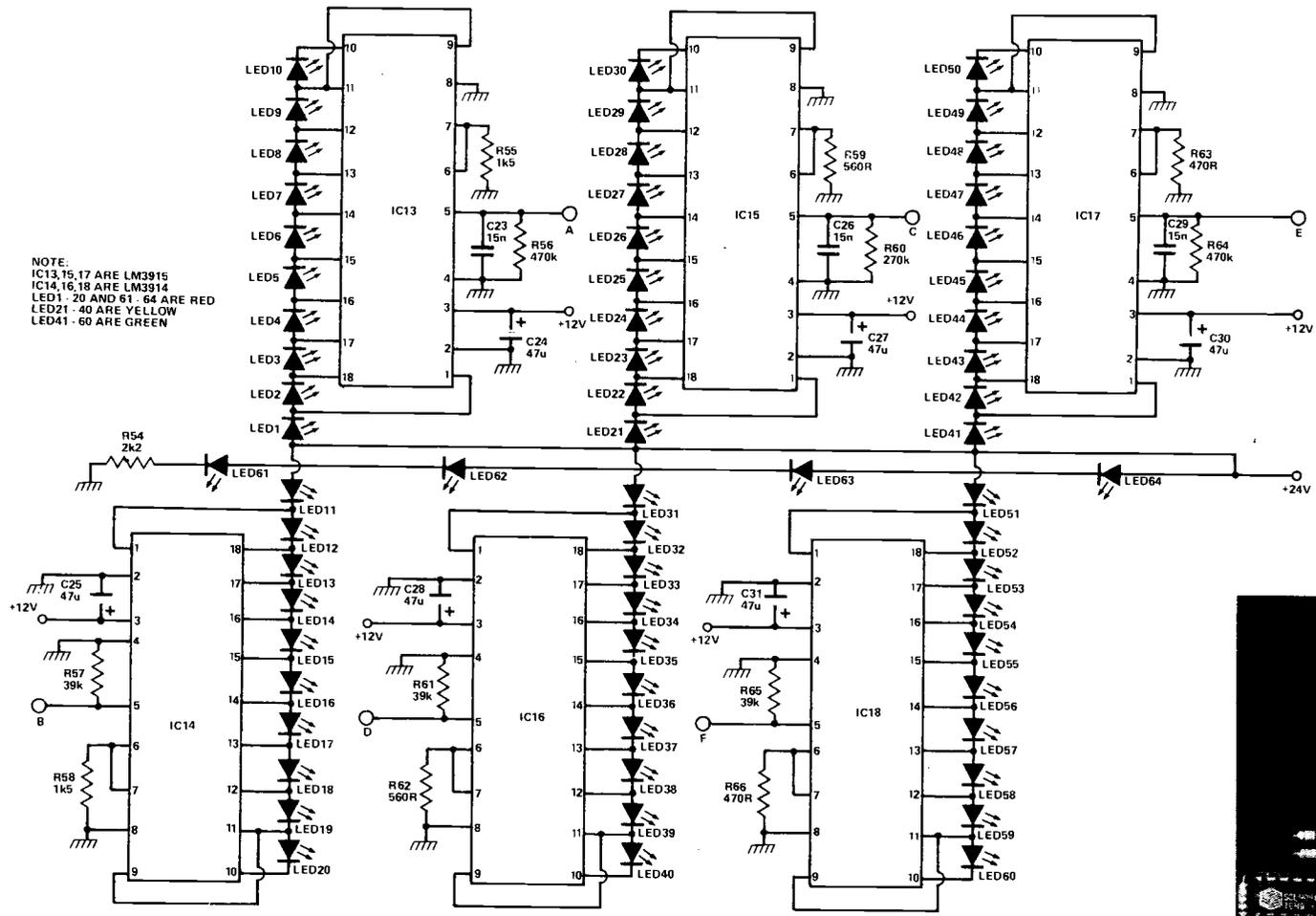

NOTE:
 IC13, 15, 17 ARE LM3915
 IC14, 16, 18 ARE LM3914
 LED1 - 20 AND 61 - 64 ARE RED
 LED21 - 40 ARE YELLOW
 LED41 - 60 ARE GREEN

Fig.4 Circuit diagram of the display circuitry. The three sections at the top display the amplitude, and those below display the dominant frequency, in each of the three bands.

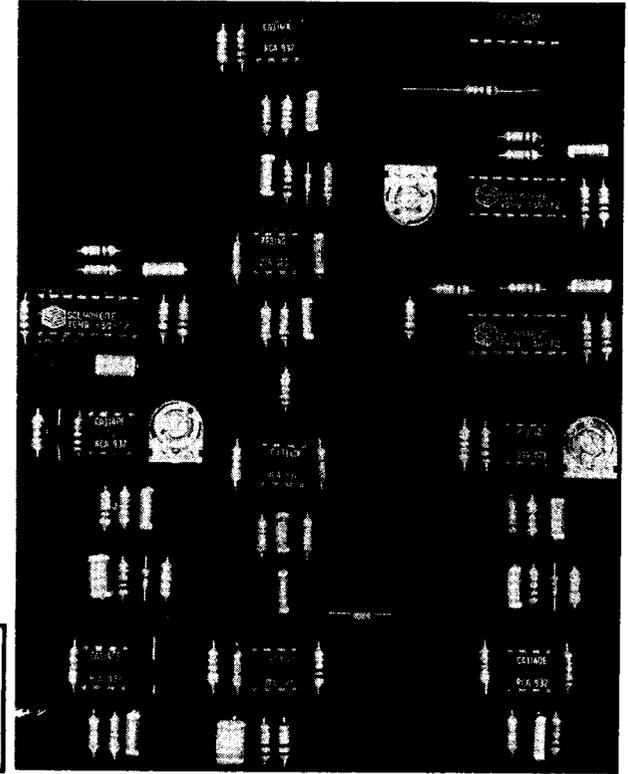Close-up of the filter circuitry (below).



Finally, to correctly calibrate the frequency response of the completed unit, build the simple calibration oscillator (see Fig. 5) on a piece of Veroboard and then use it to set up the full-scale frequency levels of the three frequency bars with PR1, PR2 and PR3.

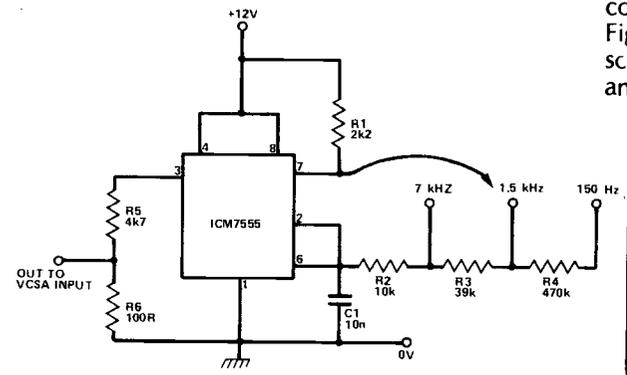


Fig.5 (left) This simple circuit will generate the three frequencies required to calibrate the frequency display.

BUYLINES

All components used in the V.C.S.A. are easily available. In case of difficulty the LM3914 and LM3915 can be purchased from advertisers in this issue. Should you decide to enhance the appearance of your PCB with flock paper then Paperchase Products Ltd., 213 Tottenham Court Road, London W1P 9AF offer a selection of colours.


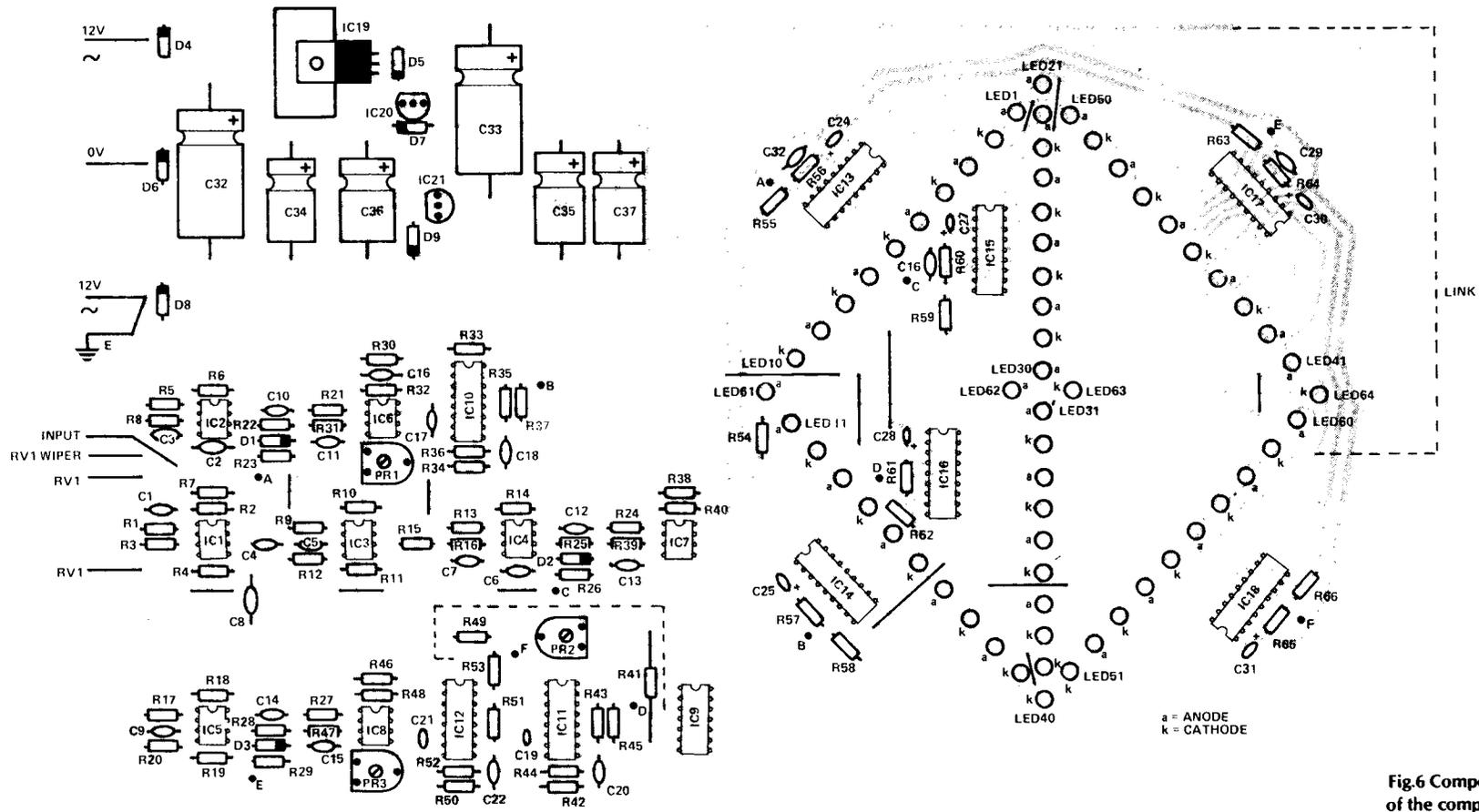


Fig.6 Component overlay of the complete VCSA.

PARTS LIST

Resistors (All 1/4W 10%)	R63, 66	470R	C35, 37	470u 16 V electrolytic
R1, 3	Potentiometers		Semiconductors	
R2, 29, 56, 64	RV1	47k linear	IC1-8	CA3140
R4, 22, 25, 28, 34, 42, 50	PR1, 2, 3	100k miniature horizontal preset	IC9	4093B
R5, 9, 11, 12, 13, 17, 57, 61, 65	Capacitors		IC10, 11, 12	4046B
R6, 7, 8, 10, 14, 18	C1	470n polycarbonate	IC13, 15, 17	LM3915
R15, 16	C2	33n ceramic	IC14, 16, 18	LM3914
R19, 20	C3	33n polycarbonate	IC19	7824
R21, 37, 45, 53	C4, 5, 23, 26, 29	15n polycarbonate	IC20	78L12
R23	C6, 7, 8, 9, 21	4n7 polycarbonate	IC21	79L12
R24, 27	C10, 17	220n polycarbonate	D1-3	1N4148
R26	C11, 13, 15, 18, 20, 22	100n polycarbonate	D4-9	1N4001
R30, 31, 38, 39, 46, 47	C12, 14	47n polycarbonate	LED1-20, 61-64	0.125" Red
R32, 40, 48	C16	2n2 ceramic	LED21-40	0.125" Yellow
R33, 36, 41, 44, 49, 52	C19	47n ceramic	LED41-60	0.125" Green
R35, 43, 51, 60	C24, 25, 27, 28, 30, 31	47u 16 V tantalum	Miscellaneous	
R54	C32, 33	1000u 63 V electrolytic	T1	12-0-12, 12 VA
R55, 58	C34, 36	1000u 25 V electrolytic	SW1	DPDT miniature toggle
R59, 62			F1	250 mA fuse and holder

MICROS

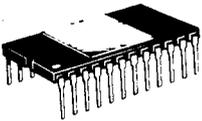

Micros, memory and support

MC1489	85	74S287	2.50
MC1488	85	74S268	2.50
MC14411	11.95	74S471	4.95
MC14412	11.95	74S472	11.95
1702	8.95	74S474	11.95
2101	2.99	8T26	1.80
2102	99	8T28	1.80
2111	2.32	8T95	1.80
2112	2.32	8T97	1.80
2114	3.45	8T98	1.80
2114L	3.75	SC/MP2	9.95
2142	10.40	8080	5.49
2376	11.80	8085	11.95
2513	6.50	8086	89.00
2516(5v)	13.95	8154	11.50
2532	29.00	8155	12.50
2705	8.15	81LS95	1.30
4027	2.95	81LS96	1.30
4116	4.95	81LS97	1.30
4118	14.95	81LS98	1.30
5204	7.95	8212	2.45
57109	12.43	8216	2.50
57161	9.95	8224	2.50
6011	4.95	8228	4.20
6402	4.95	8251	4.95
6502	7.95	8253	10.95
6520	4.50	8255	4.95
6522	7.95	8257	10.95
6532	8.50	8259	11.95
6545	14.95	8678	12.95
6575	14.95	8602	2.20
6800	7.95	95354	10.95
6802	12.49	Z80-2mHz	7.50
6805	19.95	Z80-PIO	6.95
6810	3.95	Z80-CTC	6.95
6821	4.50	Z80-4mHz	8.95
6845	19.50	Z80-PIO	7.50
6850	3.95	Z80-CTC	7.50
6852	5.95	Z8000	120.00
74S00	59	ADC0817	14.47
74S04	3.95	DG300	3.80
74S201	8.95	F8	9.95
74S188	2.50	F8SM1	9.95
74S262	9.95		

74LS00

LS00	13	LS366	85
LS01	13	LS367	85
LS02	16	LS368	85
LS03	15	LS373	180
LS04	20	LS374	180
LS05	23	LS375	180
LS06	23	LS377	180
LS09	23	LS378	185
LS10	20	LS379	215
LS11	32	LS386	85
LS12	32	LS390	140
LS13	40	LS393	140
LS14	40	LS396	180
LS15	40	LS396	180
LS20	24	LS399	275
LS21	32	LS399	230
LS22	40	LS445	140
LS26	48	LS447	185
LS27	48	LS490	150
LS28	48	LS668	105
LS30	24	LS669	105
LS32	30	LS790	270
LS33	39		
LS37	39		
LS38	39		
LS40	28		
LS42	80		
LS47	85		
LS48	120		
LS49	120		
LS51	28		
LS54	30		
LS55	70		
LS63	180		
LS73	40		
LS74	40		
LS75	40		
LS76	45		
LS78	46		
LS83	105		
LS85	105		
LS86	45		
LS90	50		
LS91	125		
LS93	75		
LS95	115		
LS96	180		
LS107	45		
LS109	80		
LS112	80		
LS113	85		
LS114	49		
LS122	70		
LS123	85		
LS124	180		
LS125	80		
LS126	80		
LS132	95		
LS133	30		
LS136	65		
LS139	80		
LS145	120		
LS148	175		
LS151	95		
LS153	85		
LS154	85		
LS156	95		
LS157	78		
LS158	85		
LS160	120		
LS161	95		
LS162	110		
LS163	100		
LS164	115		
LS165	155		
LS166	175		
LS168	210		
LS169	210		
LS170	288		
LS173	105		
LS174	147		
LS175	110		
LS181	285		
LS182	120		
LS191	120		
LS192	125		
LS193	125		
LS194	125		
LS195	120		
LS196	120		
LS202	345		
LS221	120		
LS240	225		
LS241	225		
LS242	225		
LS243	232		
LS244	245		
LS245	280		
LS247	135		
LS248	135		
LS249	135		
LS251	130		
LS253	130		
LS257	115		
LS258	120		
LS259	180		
LS261	480		
LS266	75		
LS273	180		
LS275	180		
LS279	89		
LS290	255		
LS293	180		
LS290	130		
LS293	130		
LS295	215		
LS298	215		
LS299	420		
LS324	200		
LS325	320		
LS326	320		
LS327	315		
LS352	185		
LS353	185		
LS355	85		

FLOPPY DISK DRIVES

We sell all you need cased or uncased. Cables & connectors. Brand new fully guaranteed.

Price

Single 5 1/4 Drive	£195
Single 8" SA800	£395
Dual 5 1/4 PSU	£59
Dual 8" PSU	£78
Dual Cabinet & PSU 1x8"	£565
Dual 8" Drive Unit	£945
Dual 5 1/4 Drive Unit	£440

VIDEO TERMINAL

24x80 display
Pentland Video
Terminal full features
professional terminal. Full details on request
Price **£595**

S100 CARDS

NEW LOW PRICES

16K STATIC	KIT	ASSM
with no RAM (2114)	£ 62	£ 82
" 8K RAM	£ 109	£ 130
" 16K RAM	£ 157	£ 178
8K static (16x2114 chips)	£ 48	

64K DYNAMIC (4116)
with 16K RAM £149 £165
with 32K RAM £189 £205
with 48K RAM £229 £245
with 64K RAM £269 £285
16K upgrade 8x4116 £ 40

16/32K EPROM CARD
Without EPROMs
2708/2516 £63 £ 89

FDC DOUBLE DENSITY
Double Density for 5 1/4" or 8" Drives £ - £195

VAT

ALL OUR PRICES EXCLUDE VAT & P/P

CENTRONICS 737 PRINTER
LETTER QUALITY FOR £425

Uses any paper roll, fanfold, single sheets, 96 character ASCII, 7 x 7 dot matrix, 50 CPS, RS232 or parallel I/O

OK TOOLS
Full range of wire wrapping accessories & boards & dip jumpers etc. Visit our showroom or send for our catalogue.

VERO
S100 prototyping boards and full range of accessories.

BOOKS
Complete range of microcomputer books and magazines on sale in our showroom.

CATALOGUE AVAILABLE
Catalogue available. Send 50p & S.A.E. (A4 size).

WE HAVE MOVED
TO OUR NEW CENTRAL LONDON SHOWROOM
59/61 THEOBALDS RD, WC1 TUBE HOLBORN.

TUSCAN S100
A Z80 based S100 Computer

Single board will hold up to 8K RAM, 8K ROM. Video interface Z80 processor - I/O and cassette interface. 5 spare S100 expansion sockets for memory/disc expansion. System monitor, resident BASIC or CP/M system option. All components available separately or ready-built

NEW LOW PRICES
TUSCAN MAIN BOARD KIT ONLY £235 + VAT
SAE FOR DETAILS

TRITON SINGLE BOARD PERSONAL COMPUTER

8080 BASED SINGLE BOARD system with EUROCARD EXPANSION

Complete Kit incl. PSU/Case/Keybd £286
Expansion Motherboard Kit £ 50
8K (2114) RAM Card Kit £ 97
8K (2708) ROM Card Kit £ 97
Expandable up to CP/M
Disc System SAE for details

TCL PASCAL
FOR PET & CP/M systems

Put Pascal on your PET now
Pascal conversion ROM £ 20
Pascal manual £ 9
Complete package including compiler £120

Edge Connectors S100 £4.00

Insulation/Piercing Ribbon/Cables

I/OHEADER		PLUG	
10 way	£2.20	10 way	£1.60
20 way	£3.40	20 way	£2.30
26 way	£4.00	26 way	£2.70
34 way	£4.80	34 way	£3.30
40 way	£5.40	40 way	£3.75
50 way	£6.00	50 way	£4.60
60 way	£6.50	60 way	£5.00

Zero Insertion Force Sockets

16 way	£4.95
24 way	£6.00
40 way	£9.50

D-Types

25W Male	£2.80
25W Female	£3.80
25W Cover	£1.80

Insulation Piercing Edge Connectors

20 way	£3.60
26 way	£4.00
34 way	£4.60

Insulation Piercing DIP Plugs

14 way	DIP Plug £1.30
16 way	DIP Plug £1.50
24 way	DIP Plug £2.80

DIP Switches

4 way	£1.20
7 way	£1.75
8 way	£1.80

DIP Plugs

14 DIL	£ 65
24 DIL	£ 20
40 DIL	£3.60

DIL SOCKETS (TEXAS)

Low	Wire	2x 6 way - 1.75	
Prof	Wrap	2x12 way - 3.00	
8pin	10p	26p	2x10 way - 2.00
14pin	12p	36p	2x15 way - 3.20
16pin	13p	42p	2x18 way - 3.50
18pin	16p	80p	2x22 way 3.203.65
20pin	22p	90p	2x25 way 3.60 -
22pin	25p	-	2x30 way 4.15 -
24pin	30p	65p	2x36 way 4.753.90
28pin	35p	80p	2x40 way 5.00
40pin	40p	1.10p	2x43 way 5.504.60

Edge Connectors

156	1
156	1

Ribbon Cable PRICE/M

Grey	Coloured	
10	10	90
14	14	1.20
16	16	1.40
20	20	1.60
24	24	2.40
34	34	2.80
40	40	3.30
50	50	4.00
60	60	5.50

CRYSTALS FOR MICROS

32.768KHz	3.00	4.00MHz	2.70	10.00MHz	2.70
100KHz	3.00	4.43MHz	1.00	10.7MHz	2.70
200KHz	3.70	5.0MHz	2.70	16.00MHz	2.80
1.0MHz	3.60	6.0MHz	2.70	18.00MHz	2.90
1.008MHz	3.50	6.144MHz	2.70	18.432	2.90
1.8432MHz	3.00	7.0MHz	2.70	36MHz	2.90
2.00MHz	1.50	7.168MHz	2.50	48.0MHz	2.70
2.45760MHz	3.05	8.00MHz	2.70	100MHz	2.90
3.276MHz	2.70				

TRANSAM

59/61 THEOBALDS RD
LONDON WC1
TEL: 405 5240/2113
TELEX 444198.

TRANSAM

electronics today international BOOK SERVICE

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road London WC2. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires £4.25
Beginners Guide to Transistors Reddihough £4.25
Beginners Guide to Integrated Circuits Sinclair £4.25
Understanding Electronic Circuits Sinclair £5.10
Understanding Electronic Components Sinclair £5.10
Beginners Guide to Radio King £4.25
Beginners Guide to Audio Sinclair £4.25
Understanding Electronics, Warring £4.90

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.65
IC Op-Amp Cookbook £10.00
Video Cookbook £6.50
ITL Cookbook £7.55
The Basic Cook £4.00
IC Converter Cookbook £9.50
Master IC Cookbook Hallmark £7.45

APPLICATIONS

Fire and Theft Security Systems B. Weis £2.15
How To Build Electronic Kits Chapel £3.25
110 Electronic Alarm Projects R. M. Marston £4.95
110 Semiconductor Projects for the Home Constructor R. M. Marston £4.95
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £4.95
110 Thyristor Projects Using SCRs R. M. Marston £4.95
110 Wave Form Generator Projects R. M. Marston £4.95

COMPUTING & MICROPROCESSORS

What is a Microprocessor? 2 cassette tapes plus a 72 page book £10.00
Beginners Guide to Computers and Microprocessors with Projects C. Adams £6.05
BASIC Computer Games Ahl £6.05
BASIC for Home Computers A self-teaching guide B. Albrecht £6.60
Illustrating BASIC D. Alcock £4.25
Troubleshooting to Microprocessors and Digital Logic Goodman £5.90
Z-80 Microcomputer Handbook W. Barden £7.75
How to Program Microcomputers W. Barden £7.25
Introduction to Microcomputers and Microprocessors A. Barna £9.50
Microprocessors in Instruments and Control R. J. Bibbero £13.10
Basic BASIC J. S. Coan £7.40
Advanced BASIC J. S. Coan £6.40
Getting Acquainted with Microprocessors L. Frenzel £7.25
Beginners Guide to Microprocessors C. M. Gilmore £4.90
1001 Things to do with Your Personal Computer Sawusch £6.00
Beginning BASIC R. E. Gosling £4.75
Microprocessor Programming for Computer Hobbyists N. Graham £7.15
Miniprocessors from Calculators to Computers Heiserman £5.35
Microcomputers, Microprocessors, Hardware, Software and Applications J. L. Hilburn £17.40
BASIC Programming J. G. Kemeny £8.20
Microprocessor Systems Design E. Klingman £17.65
Intro to Microprocessors Leventhal £11.00
Microprocessor — Technology, Architecture & Applications D. R. McGlynn £11.30
Interactive Computing with BASIC Monro £4.35
BASIC with Style P. Nagin £4.50
Software Design for Microcomputers Ogdin £8.95
Microcomputer Design Ogdin £7.45
Microcomputer Base Design Peatman £6.10
Hands on BASIC with a PET Peckham £10.50
Complete Microcomputer Systems Handbook £8.75
6800 Software Gourmet Guide and Cookbook Scelbi £9.20
8080 Software Gourmet Guide and Cookbook £9.20
The 8080A Bugbook: Microcomputer Interfacing & Programming P. H. Rony £8.35
8080/8085 Software Design Titus £7.60
57 Practical Programs & Games in BASIC Tracton £6.65
How to Design, Build and Program Your own Working Computer System £7.10
Your Own Computer Waite £2.25
Microprocessor/Microprogramming Handbook Ward £6.20

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £7.25
Practical Digital Design Using ICs J. Greenfield £16.00
Designing With TTL Integrated Circuits Texas Instruments £9.60
How To Use IC Circuit Logic Elements J. Streater £4.85
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £4.95
Understanding CMOS Integrated Circuits R. Melen £4.60
MOS Digital ICs G. Flynn £5.25

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £4.00
Working with the Oscilloscope A. Saunders £4.60
Servicing with the Oscilloscope A. King £7.50
Radio Television and Audio Test Instruments King £8.30

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.45
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £4.95
Designing With Operational Amplifiers Burr Brown £19.65
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.80

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carison £7.65
Digital Signal Processing Theory & Applications L. R. Rabner £24.40
Electronic Communication Systems G. Kennedy £8.75
Frequency Synthesis, Theory & Design Mannassewitsch £25.00
Principles of Communication Systems H. Taub £8.40

THEORY

Introduction to Digital Filtering Bogner £10.60
Transistor Circuit Design Texas Instruments £10.00
Foundations of Wireless Electronics M. G. Scroggie £6.10
Electronic Circuit Design Handbook 4th Edition £16.75
Master Guide to Electronic Circuits Adams £9.25


REFERENCE

Electronic Engineers Reference Book (Ed. 4) L. W. Turner £38.00
Electronic Components M. A. Colwell £3.40
Electronic Diagrams M. A. Colwell £3.40
International Transistor Selector T. D. Towers New update £10.70
International FET Selector T. D. Towers New update £4.60
International Op-Amp Linear IC Selector Towers £8.00
International Microprocessor Selector (NEW) Towers £16.00
Radio, TV and Audio Technical Reference Amos £37.00

MISCELLANEOUS

Electronic Fault Diagnosis Sinclair £4.00
Integrated Electronics J. Milman £8.20
Practical Solid State DC Supplies T. D. Towers £6.50
Practical Triac/SCR Projects for the Experimenter R. Fox £2.35
Printed Circuit Assembly Hughes & Colwell £3.40

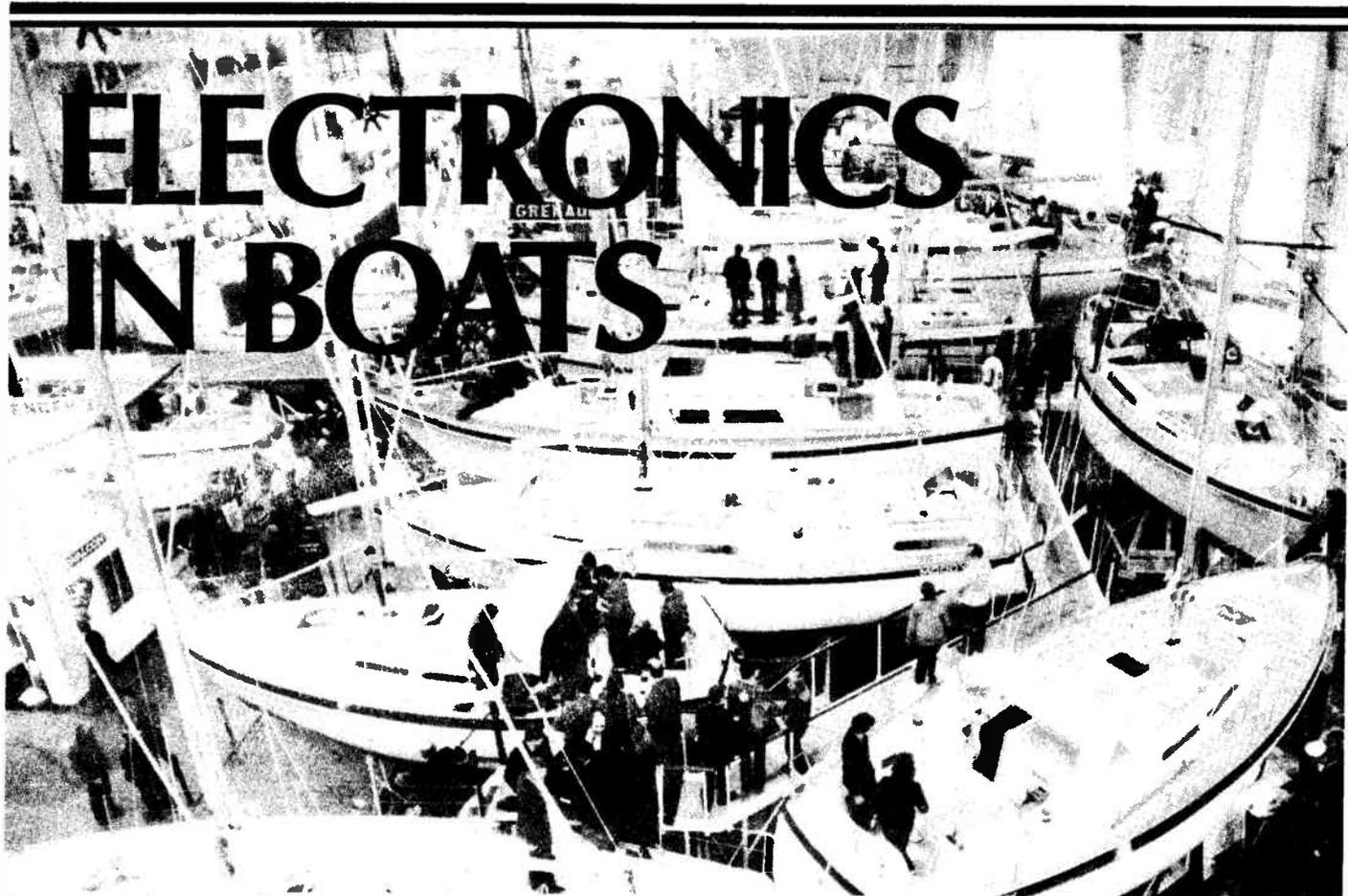Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy way of getting your hands on the right title.



January saw the return to Earl's Court of the International Boat Show. Tina Boylan, (ETI's very own Tiller Girl) and Peter Green went along to see what part electronics plays in boating.

The 27th London International Boat Show brought a brief glimpse of the sunny Caribbean to a frost-bitten and land-locked crowd this January at Earl's Court. It was filled to the gunwales with land-lubbers and sea-goers alike, for the show is not merely aimed at the enthusiast or those of us with money to burn. There are plenty of attractions; gadgets to puzzle over and pleasure craft of every conceivable shape and size fill the huge halls as far as the eye (no offence, Nelson) can see. The whole experience is geared towards sun-baked fantasies and the epitome of luxury.

As you leave the lower halls, however, you find stands with some of the more down-to-earth(?) elements of boating on offer. Waterproof gear, life jackets and a million different types of rope. Proving that there's a lot more to boats than basking in the sun!

Messing About In Boats



Practically a whole floor was given to what interests ETI most — electronic devices. Electronics now plays an extremely important part in sailing the seven seas; the aid it gives to navigation and safety is immeasurable. For although men have successfully managed to sail over quite long distances for thousands of years with little more than the stars to guide them, electronics enables them to navigate far more accurately and has saved hundreds of lives.

Direction finding and measurement of speed are the most rudimentary necessities for sailing. The earliest form of navigation used charts, compasses and the first instrument — the log (literally!), which was a log tied to a rope knotted at equal intervals and dropped over the stern of the boat, the rope being paid

Far left: A small radio direction finder with digital readout of the selected frequency.

Left: A satellite navigation unit.

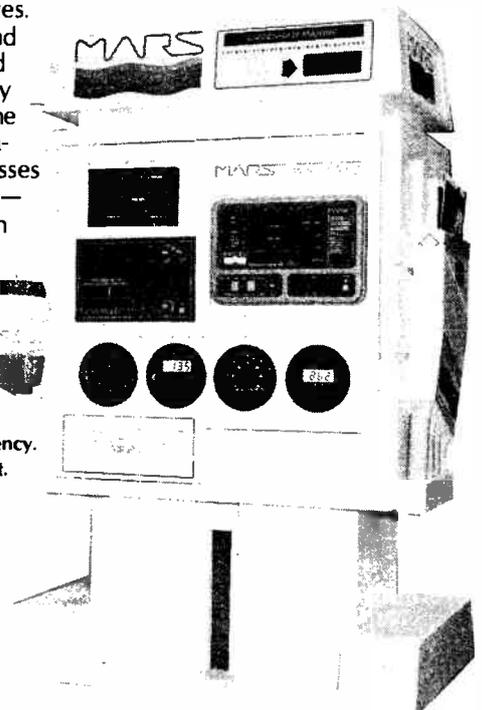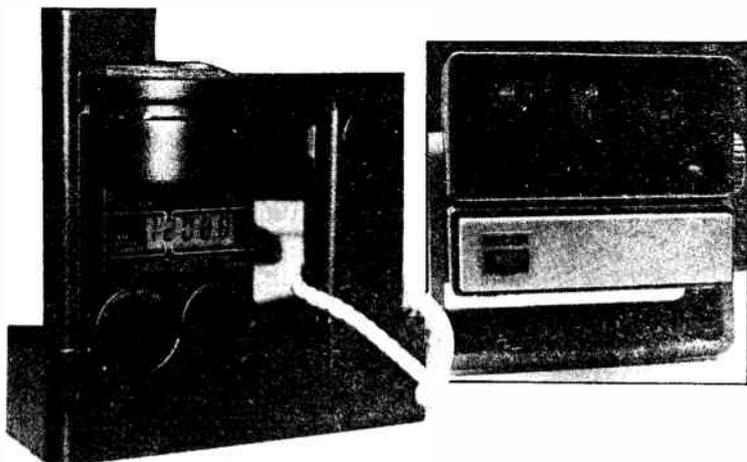Right: A demonstration console for various navigational aids.



out for a known length of time and the knots counted. Calculations would then be made using these three ingredients. The result was always an approximation, as time keeping was not very accurate. In order to solve this problem, during the 17th century the British Admiralty offered a prize of ten thousand pounds for the development of an accurate chronometer. This huge sum was clearly an indication of the importance of such a device. In 1762 horologist John Harrison collected the prize for his design which kept an accuracy of better than two minutes over a six week period — a considerable achievement for the time (groan)!

Today electronic time keeping and calculation are accepted as being both accurate and simple. But electronics in navigation has come a long way from this simple level. Any mechanical instrument can be used in conjunction with electronics and in the case of navigation it is used in three main ways.


Which Way Now?

The first simple method is mainly an offshore aid and is called Radio Direction Finding (RDF). To use this system you must know your approximate position and from your (still indispensable) charts, you then choose three or more transmitting aircraft or marine radio beacons which are in the vicinity of your approximate position. The simplest RDF receivers are operated by manually turning a loop of ferrite antenna until the chosen beacon is heard at minimum strength. Beacon direction is then read off a calibrated scale. A separate sensing antenna must be incorporated to tell whether the beacon is in front of the boat or behind it. Some of the hand-held RDFs, of which there were many at the show, have a built-in compass. Using this it is possible to obtain a fix quickly and the skipper is able to use this on deck, therefore avoiding interference from rigging etc. Headphones are provided on many models for aural identification of very weak signals. When you have read off the bearing of each beacon you plot them on the chart and where the lines cross — X marks the spot, your position has been found! The bearings taken from these fixed stations give a resultant bearing which is usually accurate to within 2°.

The second method of navigation is an essential for any water-going vessel and is the aforementioned log, only somewhat changed in design! The log indicates speed and nautical mileage using a sensor. The simplest form of this is a small impeller monitoring water flow which is mounted through the hull, or over the stern of small boats. As it rotates it pulses a reed or similar switch to provide a suitable signal for subsequent analogue or digital processing and display. This type of sensor is unfortunately liable to clogging by seaweed or flotsam or may be inaccurate due to protrusions from the hull of the boat.

A way round this is to use one of two other electronic systems which have no moving parts. The first of these transmits ultrasonic pulses through the hull into the water and then listens for reflections caused by bubbles or other moving particles under the boat. The frequency of the received signal will differ from the transmitted one because of the Doppler shift and this is proportional to the speed of the water flow. The instrument displays the frequency difference as units of speed. Incorporated circuitry compensates for variations in the speed of sound in water at different temperatures and salinities.

The second and more common device is a hull-mounted electromagnet which creates a magnetic field at right-angles to the motion of the boat, with the lines of flux passing vertically through the hull. Since seawater is conductive, a voltage is induced in the water proportional to the velocity at which the water cuts through the field. There are two small metal studs which protrude through the hull and pick up the voltage — and

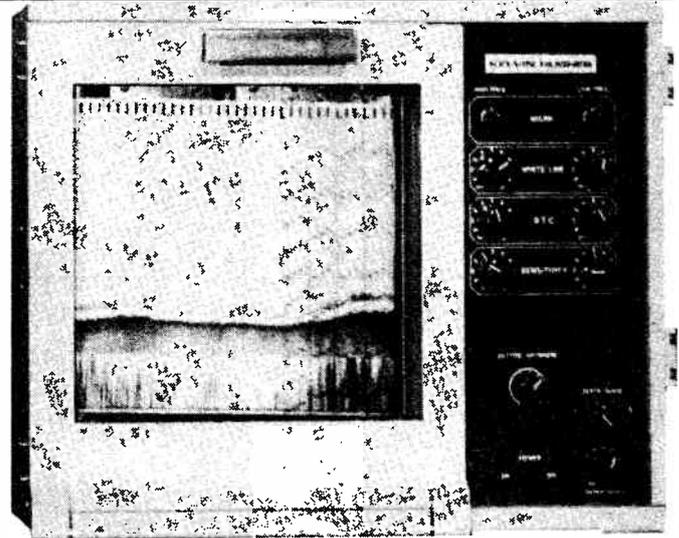

Above: A depth sounder with pen recorder.
Bottom: Another satellite navigation console.

that's all there is to it! With the log to calculate speed and mileage and bearings taken from a compass, this method can be used for dead reckoning navigation out at sea.

Seeing Stars

Satellite navigation is the last and most accurate means of position finding at present. This method is used mostly in large boats and ships as it can be rather expensive to install. As each satellite orbits the earth it transmits a signal on 150 and 400 MHz every two minutes. These signals give its exact orbital parameters, which are frequently updated with information based on observations made by land-based dedicated tracking stations. The satellites can provide information 19 or 20 times in every 24 hours, and, although their passes are not evenly spaced the worst delays are not normally longer than 2½ to 3 hours. Using the most sophisticated type of on-board dual frequency receivers, a positional accuracy of a few metres can be achieved anywhere in the world. Current satellite navigation receivers often incorporate extra features which are capable of predicting the next satellite pass, and have the ability to perform dead reckoning navigation between passes as well as ringing an alarm when the predicted destination is reached.

Sounds Fishy

So now your direction is pretty clear, but there is more information which must be found because you *really* need to know what's around you as well, and particularly what's under you. The open sea is not a swimming pool with a constant depth everywhere, and rivers are not like canals; they have sandbanks and shallows. So next on the list of electronic aids is a depth sounder.



These work by transmitting an impulse and measuring how long it takes to return. Ultrasonic energy is used for this; all types of depth sounder use this principle and only vary in the type of display, output power and frequency.


The display is usually an LED type, and when the acoustic pulse is sent out an LED flashes at the zero mark. When the echo returns another LED flashes on the dial at an angle proportional to the time since the transmit pulse was sent, thus indicating the depth of water below the hull. Apart from indicating the distance of the sea bed, the depth sounder will also pick up the position of shoals of fish, making it a useful aid for fishermen. Many depth sounders incorporate a pen recorder which enables them to return to a particularly good area where shoals have been found before. The depth sounder also makes landing less hazardous in bad weather conditions.

So now you know exactly where you're going. Great. But with the waterways of the world crowded with many different types of vessel, it's rather important that you know where they're going to, otherwise — oops! A collision, and that happens all too frequently!


On The Rebound

As far as hitting other vessels at sea goes, radar is the most effective safeguard available, even for the smallest craft. Radar not only enables you to see other vessels, but can also be used as a navigational aid because coastlines are also visible on it. Most radar sets consist of two main units — a console containing the display circuitry and controls, and a transceiver/scanner unit containing the RF electronics and the rotary antenna. Efficient radar does depend largely upon the height of elevation of the antenna since radar waves are transmitted on a line-of-sight principle. In bad weather this can mean that high waves will deflect the radar signal from a small boat making readings inaccurate. A small boat can also be easily mistaken for a wave by a radar operator on a large vessel, and this point brings us neatly to an associated safety device which is used with radar.

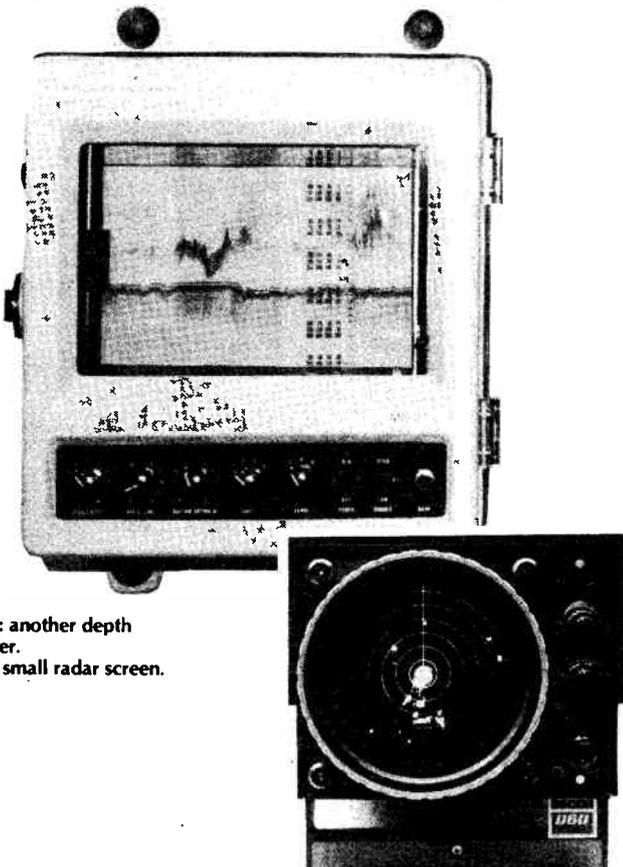A small boat, particularly if it is built of fibreglass or wood, does not reflect radar waves as well as a large vessel or one made of steel or aluminium, which leaves it little hope of being spotted on radar. Luckily there is a device which greatly improves the visibility of a small boat and can be easily fitted.



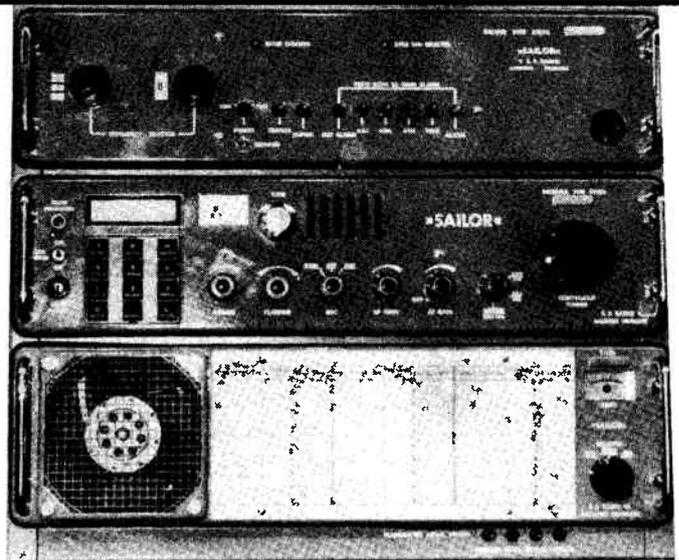Above: another depth recorder.
Right: small radar screen.



Above and left: Two reasons for choosing a small VHF radio telephone. These HF units are fairly bulky and would only suit large craft travelling far out to sea.

The metal radar reflector is masthead mounted and its shape and material make it an effective reflector of radar beams, giving a clear indication of the presence of a small boat on a radar monitor. These do have to be carefully fitted or they can be practically useless.

Steering A Straight Course

Electronics can also be used for steering your course once it is chosen. An 'autopilot' can be used for either power boats or sailing boats. Basically an autopilot is a straightforward servomechanism; the actual heading is compared to the desired course and the error signal is used to drive a servomotor, thus correcting the rudder. A disadvantage with this system is that the swell of waves can affect the autopilot and cause it to continually try to correct the movements of the rudder, however insignificant they may be, so many autopilots have a built-in override mechanism which can be adjusted to compensate for varying sea conditions.

On a sailing boat, steering is far more dependent on wind direction, so an autopilot of the type used in power boats would be next to useless; it would keep a heading regardless of wind change leaving the sails set wrongly, which, at best, would cause the boat to lose speed and at worst could put it into a dangerous situation. So most sailboat autopilots keep the boat on the right heading relative to the wind; these units offer a choice of compass or wind vane to generate the control signal.


Come In Number 44

Even boats equipped with all of the safety features so far mentioned can find themselves running into trouble and in need of communication with rescue services. Or maybe you want to contact someone you wish to speak to (you're half-way across the North Sea when you realise that it's Aunt Maud's birthday and you forgot to send a card...).

British Telecom International, the new telecommunications branch of the Post Office, now operates 12 coastal radio stations in Britain; 11 of these are for medium/short range use, one is for long range. In addition, there is a continually growing network of remotely controlled VHF stations. The coastal stations will deal with any type of message, from ship-to-shore social calls to distress signals — the latter naturally receiving priority at all times — and also broadcast routine weather reports, gale warnings and details of navigational hazards.

handset and a small helical aerial. In an emergency the set can be removed from its installation and used as a walkie-talkie; an obvious advantage if your cockpit is on fire, you've lost your mast and the main aerial with it, or you're sitting in a small rubber dinghy about 20 fathoms above the remains of your yacht! However, in this mode your range will be reduced still further, especially at sea level.

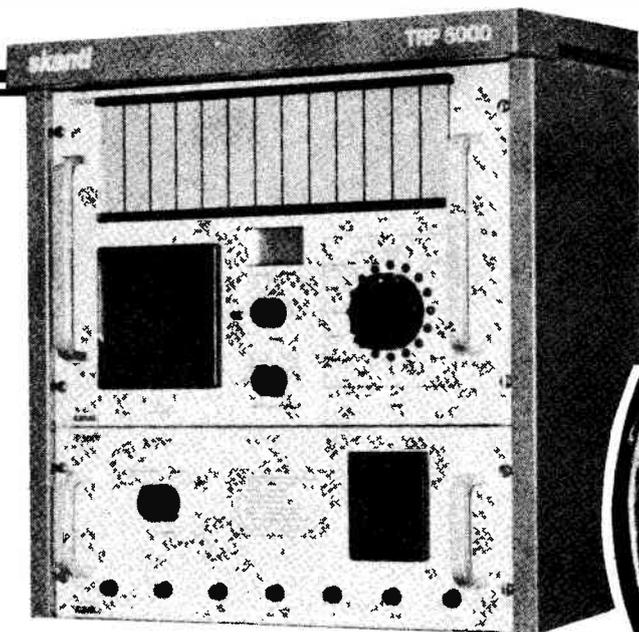Left: This VHF radio telephone features more facilities than the basic models but is still quite compact.



The Art of RT

The VHF radio telephone solves many of the problems that prevent small boat owners from fitting HF equipment and as such is an invaluable aid to safety for pleasure boats. HF radios are generally large and draw a lot of power, sometimes necessitating extra batteries. They are more complex, more prone to interference, more expensive and more difficult to install (aerials are generally loaded whips which require a ground plane). A typical VHF unit, though, is only slightly bigger than a car radio/cassette player and is just as easy to install. Mounting brackets for vertical or horizontal fitting are usually provided, and some types have a mounting flange that allows flush installation in a bulkhead, car dashboard style. After that you simply fit a mast-top aerial, plug into the boat's 12 V supply and you're ready to go.

Models generally offer similar facilities and these are limited to the essentials — on/off switch, volume, squelch and channel selector switch. The VHF frequencies allocated are from 156 MHz to 162 MHz and generally the transceivers will have a selection of a dozen channels in this range. Some models use a frequency synthesiser, so you can only transmit on the frequencies pre-selected by the manufacturer. Others have individual crystals fitted for each channel, and by changing crystals you can pick any set of frequencies that are convenient. All radio telephones should be capable of transmitting on channel 16 — this is the VHF international distress frequency.

Output power ranges from about 10 W to 25 W and often a control is provided to reduce the power output when speaking to a station at close quarters. This may either be in the form of a high/low switch or a continuously variable pot, and prevents unnecessary interference to more distant users.

Simply Simplex

Although there are some duplex channels in the VHF band (ie you may transmit and receive simultaneously, as with a telephone), only simplex transceivers were in evidence at the Show. These require the use of a press-to-talk button on the microphone, a feature well-known to those "good buddies" who have the *other* sort of radio fitted in their cars!

The qualification "in-shore and coastal" is due to the one disadvantage of VHF compared to HF: lack of range. VHF frequencies are not subject to 'skip' via the ionosphere and while this provides immunity from unwanted signals, it does mean that only line-of-sight communication is possible. Even with a mast-top aerial, range is limited to about 20 nautical miles.

A few VHF radio telephones have an optional version which allows completely portable use: the set has a battery pack (rechargeable from the ship's 12 V supply), a telephone

Hand-Held Help

For absolute assurance that an accident at sea will not be compounded by your inability to summon help, a portable distress radio telephone is essential. These units are complete, self-contained HF radio telephones, pre-tuned to one frequency only, the international maritime distress frequency (2182 kHz). Unlike the VHF band, this frequency is not subject to line-of-sight restrictions and is insensitive to aerial height. Typical 'worst-case' transmitting ranges exceed 40 miles; under favourable conditions this can be greatly extended.

A typical distress radio telephone is shock-resistant, waterproof and self-buoyant (radio overboard?!). The controls are kept to an absolute minimum and are designed to be easy to operate even with numbed fingers. Instructions are clearly and concisely printed on the case for the benefit of untrained people. To use the unit, the earth-wire with its lead sinker is thrown into the sea, the telescopic aerial extended fully, and the alarm button pressed for about 20-30 S. This causes a two-tone signal to be transmitted which overrides all other traffic on the 2182 kHz frequency and automatically activates the watch-keeping receivers used by coastguards, rescue services, merchant ships and trawlers. Once you've attracted everyone's attention you can make speech contact with your rescuers.

These units may also be used for 'urgency' calls (without using the alarm button), for direct contact with coastguards and commercial ships in order to obtain medical, meteorological or navigational advice, or to report any less serious damage to your vessel such as engine failure.

It should be pointed out that, especially in the case of VHF sets, there is little point in fitting a radio telephone unless everyone who is aboard the boat has been told where the set is and how to use it. Help is going to be a long time coming if the only man who can use the radio is the one who has just suffered a heart attack, or food poisoning, or been washed irretrievably overboard. For similar reasons, try to get a VHF set with duplex operation. Then anyone unfamiliar with radio procedure is unable to cause, at least, confusion and at worst, fatal delay, by forgetting to press the push-to-talk button.

Be Prepared

So that more or less sums up the wide range of electronic gadgets you will need for your boat, whatever size it may be. Of course, there are still many developments being made in nautical electronics because, unfortunately accidents *do* still happen. One thing visiting the Boat Show can teach you is how important having the right equipment is, and, if you visit next year's Show you too may become hooked on boats for life! **ETI**


SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series



HY120

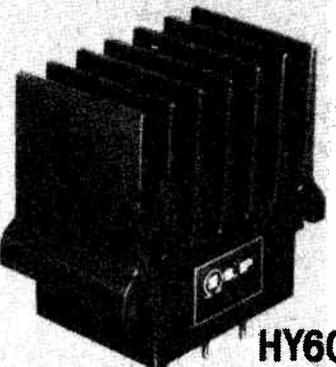

HY60

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR


CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

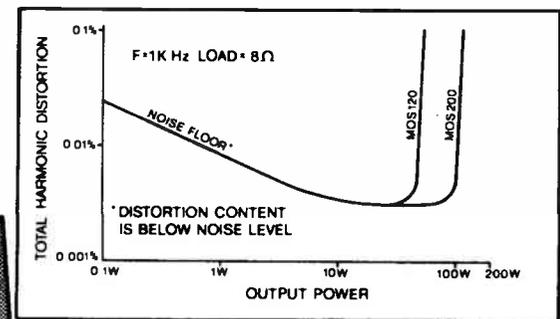
I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE



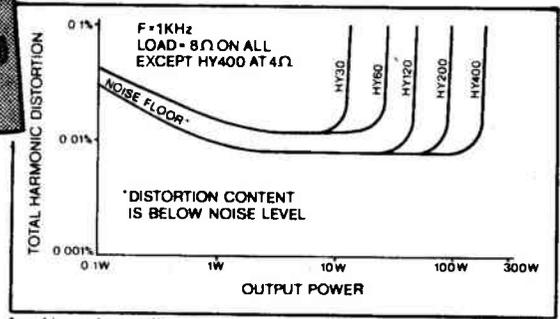Load impedance both models 4Ω-∞ Input impedance both models 100KΩ
Input sensitivity both models 500mV Frequency response both models 15Hz-100KHz - 3dB



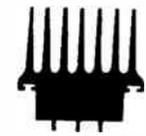Load impedance all models 4Ω-∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages:-
Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive; Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.

NEW PRE-AMPS

HY6 (mono) and **HY66** (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - **HY6** - 45 x 20 x 40 mm. **HY66** - 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity - Mag. PU. - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
HY66 stereo £12.19 + £1.83 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.


- PSU30 ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS
- PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
- PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
- PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ **TO ORDER** Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

COMPATIBLE WITH ALL I.L.P. MODULES

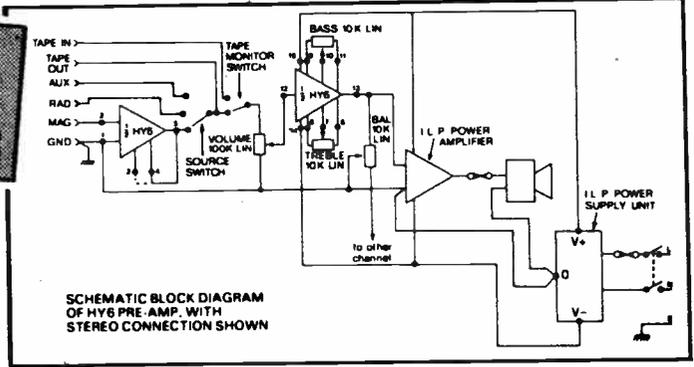

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 v

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply

..... Total purchase price £.....


I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

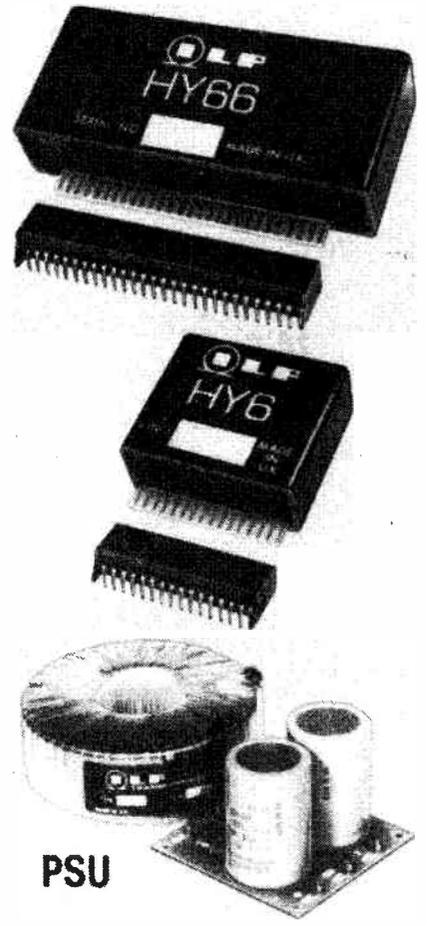

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE

I.L.P. ELECTRONICS LTD.

FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

ALL U.K. ORDERS DESPATCHED POST FREE

Rapid Electronics

Pack No.		50p	Pack No.		45p
A10	10 PP3 battery leads	50p	F331	1 BD139 transistor	45p
A72	10 3.5mm jack plugs	80p	F421	1 MJ2955 transistor	110p
A73	10 3.5mm jack sockets	80p	F43	5 78L05 regulators	180p
A74A	5 Standard jack plugs	80p	F46A	1 7805 regulator	70p
A75A	5 Std. jack sockets	90p	F47A	1 7812 regulator	70p
A84A	5 5 pin 180 DIN plugs	70p	F49A	1 7905 regulator	75p
A85A	5 5 pin 180 DIN sockets	55p	E53	1 LM317T variable reg.	200p
C21	5 Min. slide switches	75p	F54	LM323K 3A 5V reg.	500p
C28	5 Push to make switches	70p	H11	20 1N4002 diodes	75p
C29	5 Push to break switches	90p	H30	2 W005 bridge rectifiers	45p
C50	20 8 pin DIL sockets	170p	H60	100 1N4148 diodes	180p
C51	20 14 pin DIL sockets	200p	H73	2 C106D thyristors	90p
C52	20 16 pin DIL sockets	220p	J5	10 0.2in red LEDs	100p
E10	Resistor kit. 650 resistors 1/4W		J25	10 0.2in green LEDs	150p
-	10 ea value 4.7 to 1M	480p	J45	10 0.2in yellow LEDs	150p
-	Single potentiometers		J70	20 0.2in LED clips	60p
-	5K-1M log in lin	35p	J7	10 0.125in red LEDs	100p
-	Slide potentiometers. 60mm		J27	10 0.125in green LEDs	150p
-	travel. 5K-500K log or lin	65p	J47	10 0.125in yellow LEDs	150p
E26	10 100K min. presets	70p	J72	20 0.125in LED clips	60p
E31	10 1u 63V electrolytics	50p	J75	1 FND500 CC display	100p
E33	10 4u7 63V radial elec.	50p	K5	5 741 op amps.	90p
E34	10 10u 25V radial elec.	50p	K20	5 CA3140 op amps.	225p
E37	10 100u 25V radial elec.	75p	K30	5 LM301A op amps.	140p
E44	10 1u 35V bead tants.	100p	K40	1 LM324 op amps.	50p
E50	10 0.01 C280 polyester	50p	K50	1 LM380 2W amp.	70p
E54	10 0.01 C280 polyester	50p	K75	1 LM3914 LED bar graph	320p
E10	10 BC107 transistors	90p	K85	5 NE555 timers	110p
F11	10 BC108 transistors	90p	K90	1 NE556 timer	50p
F12	10 BC109 transistors	90p	K100	5 TL081 op amps.	175p
F17	10 BC214L transistors	90p	L8	5 4011 CMOS	130p
F27A	5 2N3819 transistors	100p	L9	1 4013 CMOS	40p
F311	1 BD131 transistor	45p	L11	1 4017 CMOS	75p
F312	1 BD132 transistor	45p	L22	1 4049 CMOS	45p

All prices include VAT. Please add 50p postage and packing. Send s.a.c. for our complete catalogue.

Rapid Electronics Limited
Hillcroft House, Station Road, Eynsford, Kent

LANGSTONE ELECTRONICS

38 OUTRAM ROAD, SOUTHSEA, HANTS. PO5 1QZ


TRANSISTORS	DIODES	74 TTL	CMOS	MPUs
AC18/19 15p	AA143/4 10p	7400 12p	4000/1/2 18p	6800 440p
BC107/8/9 22p	OA81/5 10p	7401/2 14p	4008 79p	6802 680p
BC177/8/9 18p	1N914 4p	7404/5 18p	4011/2 18p	6809 1790p
BC182/3/4 8p	1N4001/2 5p	7406/7 28p	4016 39p	6821 230p
BC212/3/4 11p	1N4003/5 5p	7413 28p	4017/8 79p	6840 680p
BCW91/2 30p	1N4006/7 7p	7447 79p	4023/5 18p	6850 230p
BCY70/1/2 17p	1N4148 4p	7450/4 18p	4040 90p	6852 270p
BD135/6 40p	1N5401/2 14p	7473/4 23p	4046 120p	6862 820p
BDY56 200p	1N5404/5 18p	8481/3 88p	4049/50 48p	6875 480p
8F257/8 23p	1N5406/7 18p	7485 110p	4093 79p	6880 130p
8FY50/1/2 23p	Diac 28p	7489 190p	4402/12 38p	6882 270p
BU126 150p		7491 88p	4502 99p	6888 95p
BU208 200p		7493 39p	4510 110p	6889 130p
BUX48 500p		74121 33p	4514 240p	9364 1150p
ME0404 13p	ZENERS	74123 62p	4516/B 99p	
ME1001 10p	0.5W 8p	74145 79p	4528/31 99p	
MEF3819 23p	1.3W 12p	74155/6 89p	4581 185p	MEMORIES
MEU11/12 30p		74164/5 106p	4582 128p	6810 170p
MEU21/2 30p		74182 89p	4510 110p	2114 340p
2N404A 25p	THYRISTORS	74192/3 89p	4584 89p	4116 370p
2N914 17p	0.8A/100V 37p		4585 89p	2708 510p
2N2218/3 23p	1.6A/400V 39p	LINEARS		2716 840p
2N2221/2 23p	4A/400V 47p	355/6/7 80p	CONSUMER	
2N2369A 17p	10A/400V 140p	741 80p	SAJ180 186p	PLUS:
2N2484 30p	25A/400V 620p	301A 30p	SAK115 123p	Resistors
2N2646 48p		324 85p	TAA930 180p	Capacitors
2N2904/5 24p		324 85p	TBA900 196p	Veroblocks
2N2906/7 24p		741 80p	TCA910 95p	Connectors
2N3055 48p	TRIACS	1458 48p	FSM1601 186p	Knobs
2N3702/3 11p	1.6A/400V 47p	309K 120p	TDA1067 190p	Potentiometers
2N3704/11 10p	6A/400V 70p	7805/12 85p	TDE2608 290p	Solder Equip.
2N3819 23p	10A/400V 118p	7805/12 85p	ULN2136 120p	Wire & Cable
2N405B-62 11p	25A/700V 500p	7805/12 85p	ULN2244 260p	
2N5308 28p	40A/700V 600p	555 25p		

NOTE: ALL OUR PRICES INCLUDE VAT

PLEASE RUSH ME YOUR CATALOGUE — FREE!

Name: _____
Address: _____


THE NEW AND UNIQUE VEROBLOC

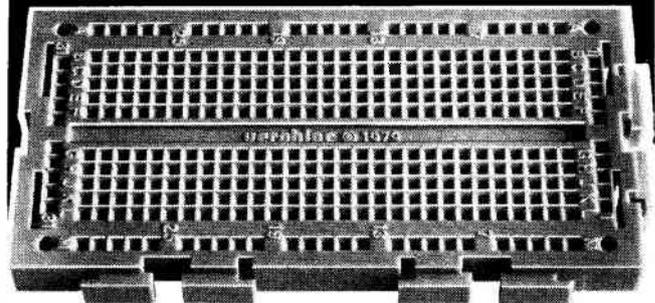

ADDS TO YOUR CAPABILITY

Already used in industry, this solderless breadboard is now available to the hobbyist. Unique because of its universal interlocking facility meaning you no longer need lots of different boards.

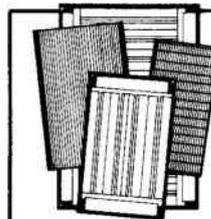Send now for the unique Verobloc.
Order code 200-21092G. £4.16p inclusive.



AND VERO HAVE ADDED TO THEIR TRADITIONAL RANGE OF HIGH QUALITY BOARDS, ALSO EX-STOCK.

No.	Order Code	Description	Size (mm)	Price
1)	10-2845B	Microboard	160 x 100	5.66
2)	10-2846H	Microboard	160 x 233.4	12.41
3)	200-21084E	V-Q Board	147.83 x 73.66	1.65
4)	09-2196L	Veroboard	160 x 100	1.63

Carriage & VAT included.

Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hampshire SO5 3ZR. Tel (04215) 62829

State quantity and order codes required _____

Name _____

Address _____

ET14


I enclose Cheque/PO for £ _____ or debit my Barclay Card/

Access No _____

Exp. date _____

vero

TECH TIPS

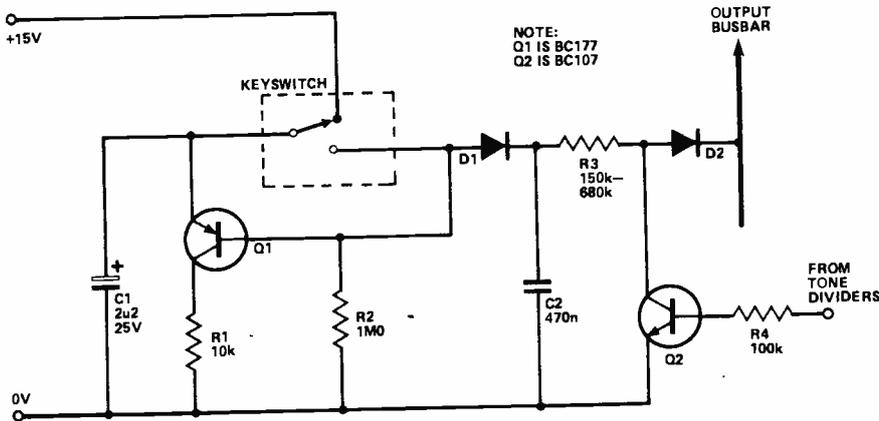

Touch-Sensitive Piano Keying

J. Cozens, York

The circuit is operated by a single-pole change-over key switch. When the key is in the fully released position C1 is held charged from the 15 V rail. Q1 is turned

on by the bias current supplied by R2. When the key is depressed C1 is disconnected from the 15 V rail and starts to discharge through Q1 and R1. When the

key is fully depressed Q1 is turned off and the remaining voltage on C1 then charges up C2 via D1. Both capacitors then discharge via R3. The envelope produced by this decaying voltage is chopped by Q2, driven directly from the tone dividers. Upon the release of the key, C1 is disconnected from the chopper circuit and C2 discharges rapidly via R3, simulating the action of the dampers. D1 is included to prevent C2 discharging through R2 when the key is released and D2 prevents interaction with other keying circuits.

As the voltage remaining on C1 at the completion of a keystroke depends on the key velocity, a degree of touch-sensitivity is obtained with this circuit.

Tuning Fork Mods.

M.L. Duncan, Greenford.

With a few slight modifications to the ET1 Tuning Fork it is possible to use the very cheap and plentiful TV colour crystal tuned to 4.43361875 MHz.


The oscillator circuit output is divided by 2519 giving a frequency of 1760 accurate to one part in 250,000. The division is done by a 4040 in place of the 4020 and the switching giving an alternate 'A' at 445 Hz is eliminated.

A 4013 dual flip-flop is added before the output buffer to give further division by two and four. These outputs are switched before the buffer to give a choice of 'A's at 880 and 440 Hz respectively. The


extra cost of the 4013 is offset by eliminating one of the 4011s.

The diagram shows the altered parts

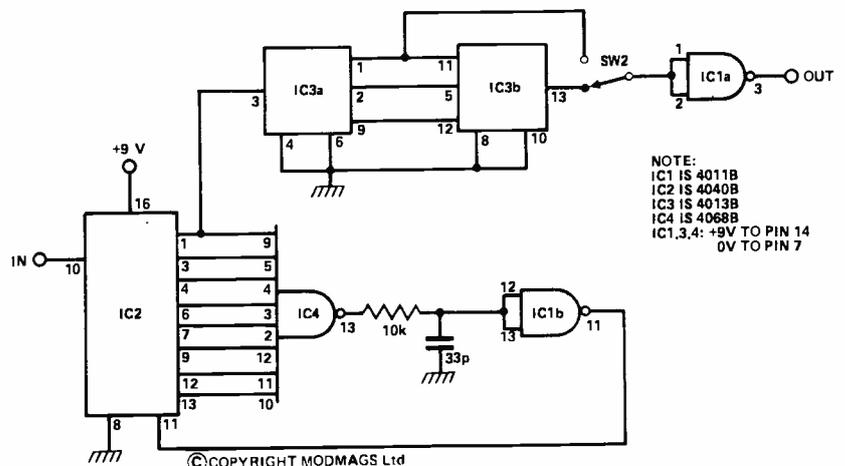of the circuit. The oscillator is retained, using the changed crystal, as is the output circuit from R4 onwards.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

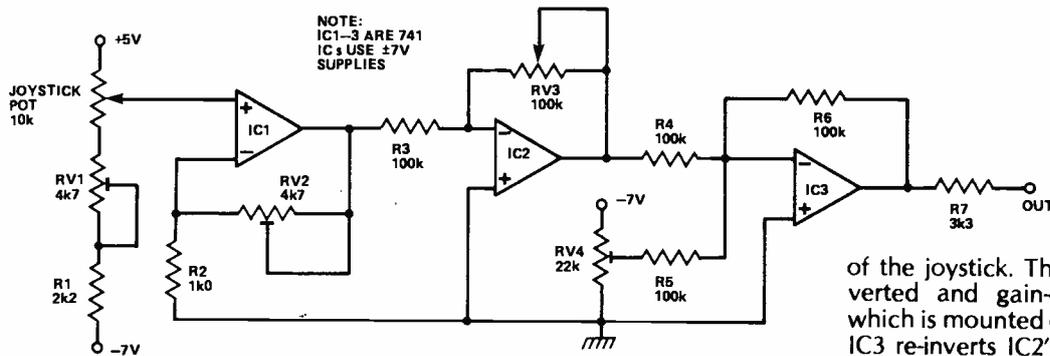

Joystick Control

M. Swale, Cardiff

Having recently built the ETI 4600 synthesiser, I found, to my dismay, that most joystick pots only vary by about 30° at maximum deflection. Consequently, the original circuit for the joystick control, which assumes complete rotation of the joystick pot, will not give the required

5 V swing. The circuit attached will convert a small DC voltage change provided by the joystick into 0-5 V at the output.

Circuit function and setting up is as follows:- RV1 is adjusted so that there is 0 V at the joystick pot wiper. (Note that RV1 and R1 may need to be on the + 5 V side of the joystick pot, depending on the actual pots used in the joystick).

RV2 is then adjusted to give ±2V5 swing at IC1 output with full deflection

of the joystick. This voltage is then inverted and gain-controlled by RV3, which is mounted on the joystick plate. IC3 re-inverts IC2's output and RV4 is adjusted to add 2V5 to the output of IC3. The output then becomes a 0-5 V swing, with 2V5 at the centre point.

This control voltage swing is ideal for use in the 4600 synthesiser since 2V5 into the keyboard modulation input gives no variation in pitch, ie the keyboard pitch can be shifted up and down by an amount dependent on RV3. The power for the circuit can be taken directly from the 4600 PSU.

Improved Speaker Overload Indicator

J. Harrold, Bristol

This circuit is based on a design by J. P. Macaulay, which appeared in Electronics Digest Vol. 1. This one offers an improvement in performance, which is low cost and does not introduce an external DC power supply.

Peaks in music can be very short and may be too fast (or dim) to be seen clearly on a LED if held for their duration only. This circuit uses a monostable to hold a LED on for a set time after triggering by a peak in music.


The voltage at the speaker output terminals is rectified and then passed to

potential divider R2, R3. ZD1 provides 'last ditch' protection for Q1 and IC1 (this method is not suitable if indication of overloads of greater than 50 W is required). Q1 is used as a voltage variable resistor and with ZD2, series pass transistor Q2 and C1, provides a regulated supply. This supply improves the stability of the 3V9 reference potential at the inverting input of IC1 and also provides a stable supply for IC2 and its timing components R8, C2. C1 cannot be placed between 0 V and the collector of Q2 as this would have an adverse filtering effect on high frequency signals. When the voltage across R2 is less than 3V9, the output from comparator IC1 is low (≈1V5) and this voltage is dropped across forward biased red LED 1 (or alternatively any three silicon diodes in

series). Q3 is off and the trigger (pin 2) of IC2 is high. When the voltage across R2 exceeds 3V9, IC1 output goes high and Q3 is turned on, lowering the voltage at IC2 pin 2, triggering the monostable and lighting LED 2 for a period dependent on R8, C2 (about 100 ms with given values). C2 must be a low leakage type (not ceramic). Decoupling of the control voltage (pin 5) by C3 was not necessary in the prototype. R1 protects the amplifier from possible bridge failure. Q1 may be replaced by a fixed resistor appropriate to the input voltage with slight degradation of performance. The value of R3 is given by:

$$R3 = (\sqrt{2PR} - 3.9) \text{ kilohms,}$$

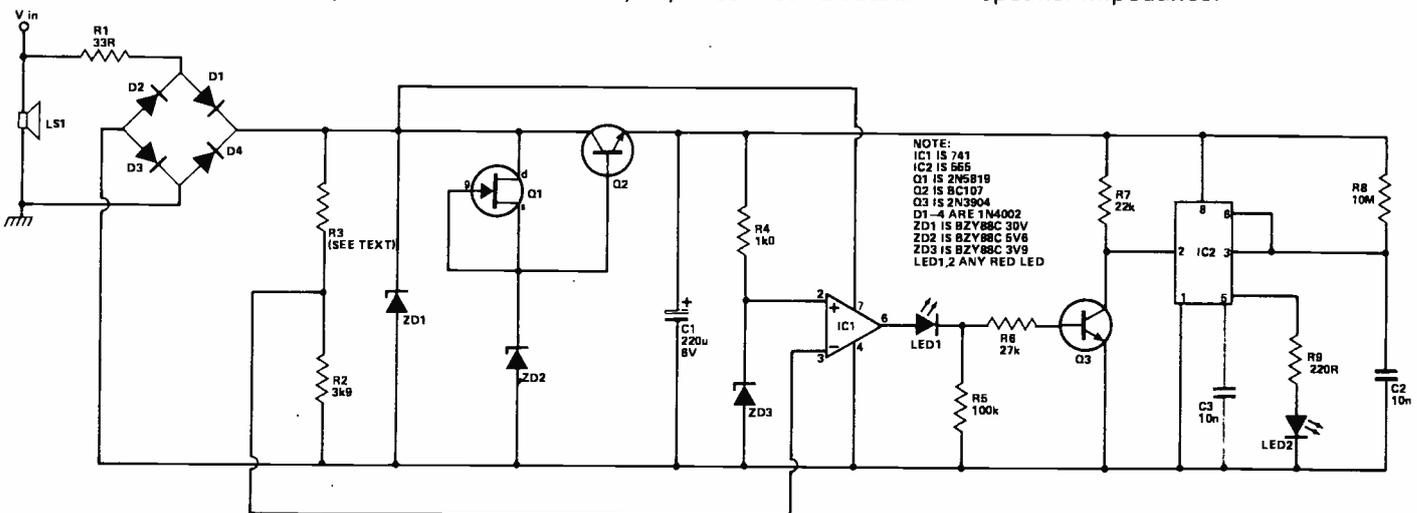where P is the power output and R is the speaker impedance.



©COPYRIGHT MODMAGS Ltd

'Zener-less' Battery Eliminator

P.J. Hunt, Wimborne


Designed as a variable-voltage battery eliminator, this circuit provides a stabilised output without Zener diodes as the reference source. Instead, a V_{be} -multiplier is employed, so that the output voltage may be continuously varied by PR1 over the range 6-10 V.

The V_{be} -multiplier is shown schematically in the inset. Provided that V_{cc} is high enough, the potential across R1 will be about 600 mV for a silicon transistor. The current through R1 can thus be adjusted so that the base current of the transistor may be ignored for practical purposes. In this case, the current through R1 will equal the current

through R2. The potential at point A is thus given by:


$$V = V_{be} \times \frac{(R1 + R2)}{R1}$$

— hence the name V_{be} -multiplier.

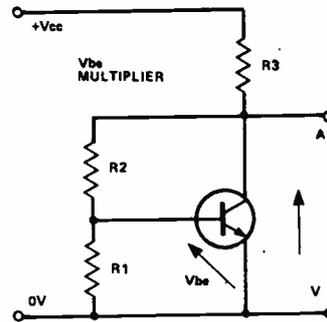


R3 limits the current through the parallel combination of the transistor and R1/R2. Suppose as an example that V_{cc} tries to rise. The potential divider formed by the three resistors will try to raise the voltage across R1. This will tend to increase the collector current and thus increase the potential drop across R3, leading to a stabilising effect at point A. This is a case of voltage-derived series feedback.

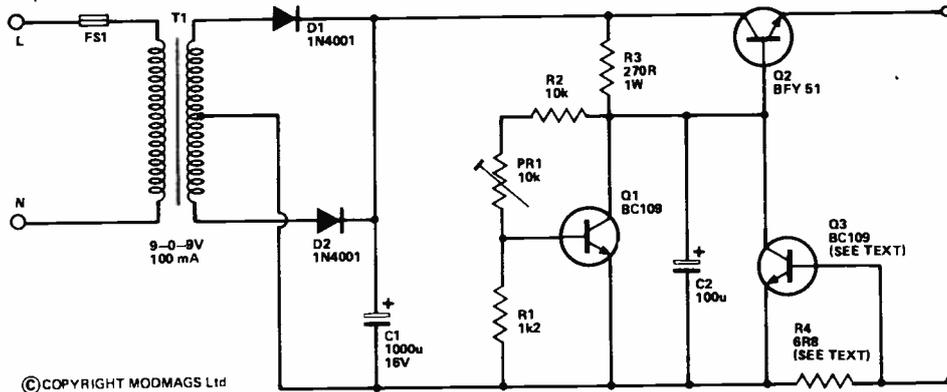In the practical circuit, R3 also provides base current for the series transistor Q2. Q3 and R4 form a current limiter. If the output current exceeds approximately 100 mA, Q3 starts to turn on, reducing the output voltage. If desired, Q3 and R4 may be omitted, in which case R3 may be derated to 1/2 W. The whole unit fits easily inside a PP9 battery case.



© COPYRIGHT MODMAGS Ltd

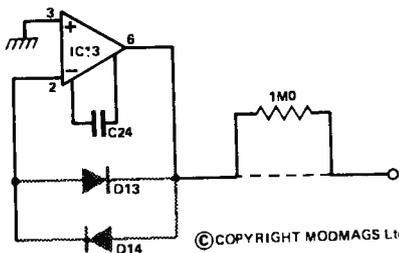


© COPYRIGHT MODMAGS Ltd

Transcendent Pulse Wave Improvement

J.F. Jordan, Cambridge

The pulse wave on the original Transcendent 2000 suffers from a slow falling edge, making LFO modulation of pulse width less effective for chorus sounds and removing the characteristic hollow tone of the square wave.

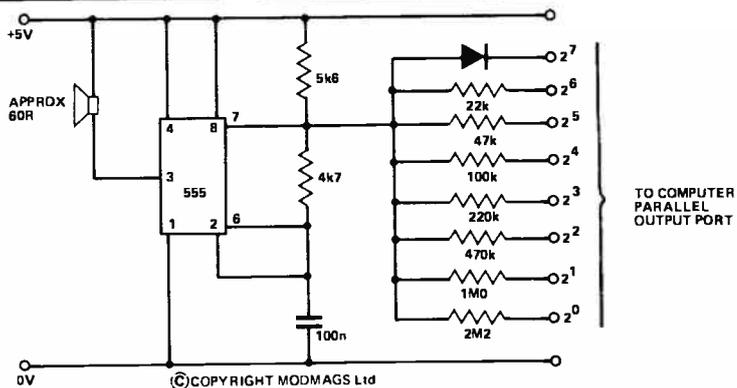This problem can be solved by removing D13 and D14 and inserting a 1M0 resistor across a break in the track from the output of IC13 to SW4. The comparator then operates in open loop mode giving much improved waveform edges.



© COPYRIGHT MODMAGS Ltd

Cheap Micro Music Box

T.M. Tobin, Birmingham

This circuit may be connected to the output port of any micro to generate musical notes over a range of about 1 1/2 octaves. On/off control is provided by the most significant bit and the resistors provide seven bit resolution. Alternative on/off control methods can be used to give eight bit resolution, eg by using the handshake lines, if available.

If the diode is replaced by a resistor, say 10k, it will be found that below a certain output value the voltage at pin 7 is insufficient to charge the capacitor. Thus the sound can be switched off.

The resolution is sufficient to enable values to be found corresponding to tones and semitones throughout the frequency range. Current consumption depends largely on the loudspeaker impedance and is generally low enough for power to be taken directly from the computer. Most constructors will have all the parts required which in any case will cost less than £1.

£395
incl.VAT& P&P



micron

'MICRON' may sound small - but we all know that it's much larger than an atom!

The un-beatable features of Microtan 65 and Tanex have been brought together to give you Micron, a ready built and tested computer of outstanding value. Fully supported by comprehensive documentation, Micron represents an ideal starting point in personal computing. We've taken a full O.E.M. licence for Microsoft Basic, which means that you'll have the support of the most popular Basic available, (as used on PET, APPLE, TANDY etc.). If you want to expand Micron there's no problem, just move into the system rack and choose from the range of Microtan modules. Read the information, study what the magazines have to say about us and compare what we have to offer with other systems, then we feel sure that you'll be convinced that we've produced an excellent product.

- FULLY BUILT, TESTED AND CASED.
- 6502 BASED MICROCOMPUTER.
- VDU ALPHA NUMERIC DISPLAY.
- 8K RAM.
- 32 PARALLEL I/O LINES.
- 2 TTL SERIAL I/O LINES.
- 1 SERIAL I/O PORT WITH RS232/20mA LOOP, AND 16 PROGRAMMABLE BAUD RATES.
- 300 / 2400 BAUD FILENAMED CASS. INTERFACE.
- DATA BUS BUFFERING.
- MEMORY MAPPING CONTROL.
- 71 KEY ASCII KEYBOARD, INCLUDING NUMERIC KEYPAD.
- POWER SUPPLY INCLUDED.


SOFTWARE

- 10K EXTENDED MICROSOFT BASIC.
- ALL THE USUAL BASIC COMMANDS.
- INTEGER AND REAL NUMBERS.
- INTEGER AND REAL ARRAYS.
- INTRINSIC FUNCTIONS: ABS, INT, RND, SGN, SIN, SQR, TAB, USR, ATN, COS, EXP, LOG, TAN.
- USER DEFINED FUNCTIONS.
- READ AND DATA STATEMENTS.
- DUMP AND LOAD PROGRAMS.
- PROGRAM EDITING COMMAND.
- STRING FUNCTION FOR TEXT I/O.
- BASIC CAN CALL MACHINE CODE SUB-ROUTINE.
- USER MACHINE CODE INTERRUPT HANDLER INTERFACES WITH BASIC.
- XBUG.
- DATA CASSETTE FILE HANDLING IN BASIC

TANGERINE
COMPUTER SYSTEMS LIMITED

Forehill Works
Forehill Ely Cambs England Tel: (0353)3633

microtan 65

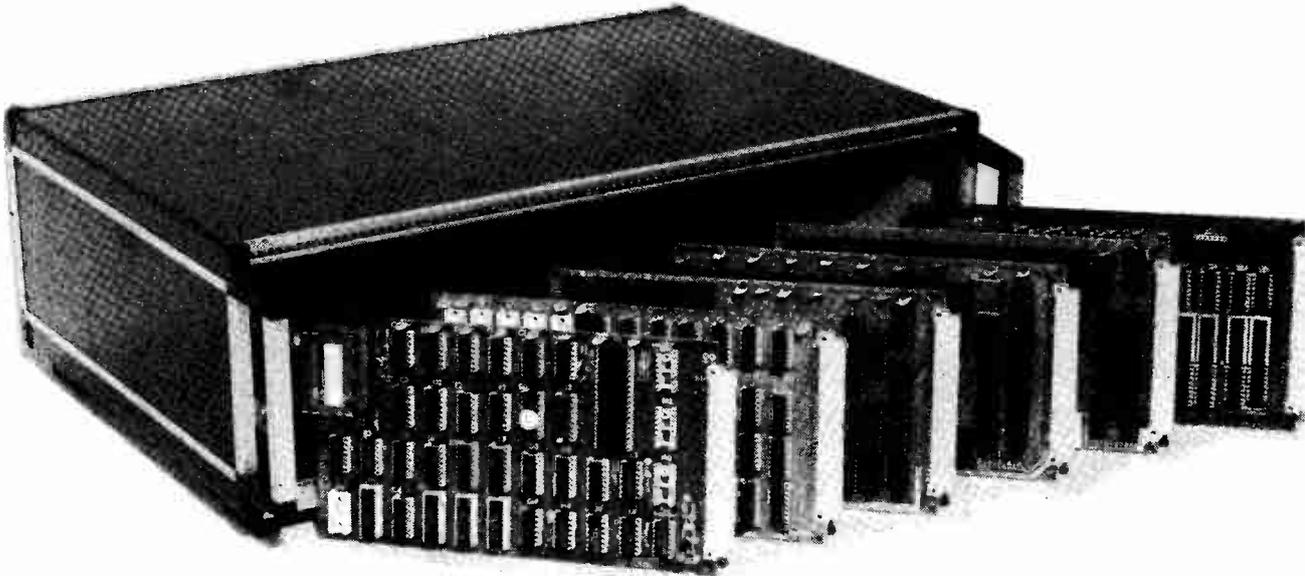

The Microtan system is rapidly becoming accepted as the ultimate approach to personal computing. Start with Microtan 65, a 6502 based single board computer, and expand to a powerful system in simple and in-expensive stages. The Microtan system is a concept and not an afterthought, this means expansion is easy and very efficient! Unlike many other systems, you'll find it difficult to outgrow Microtan, and you won't be wasting your money on a product that will only last you a few months! When you are ready to expand, Tanex is waiting. The features offered by Tanex are tremendous, and you can start into them for just £49.45! Cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, memory mapping and a further 1K of RAM are standard. From thereon expansion is simple, just plug in extra integrated circuits to get yourself 8K of RAM, a further 16 I/O lines and two more counter timers a serial I/O line with RS232/20mA loop and full modem control, XBUG - a firmware package containing cassette file handling routines, plus a line-by-line assembler (translator) and dis-assembler, PLUS 10K EXTENDED MICROSOFT BASIC, a suped-up version of the Basic as used by major manufacturers such as Apple, Tandy and Nascom, NO OTHER LOW COST MICROCOMPUTER OFFERS YOU THIS SUPERB PACKAGE. O.K. so you want more memory, try Tanram for size! Upto 40K bytes on one board starting for as little as £50.60. RAM freaks will be pleased to hear that our system mother board offers page memory logic which will support 277K Bytes, satisfied? To house these beautiful modules you can choose between our mini-rack (as used on Micron), which accepts Microtan and Tanex, or our system rack pictured above. The system rack will support 12 modules. What are these extra modules? Well for starters there's a couple of I/O modules, parallel and serial offering upto 128 I/O lines organised as 16 8 bit ports and 8 serial I/O ports respectively. Shortly we'll be introducing high definition (256x256) colour graphics, A to D and D to A modules, IEEE 488 Bus interface, a PROM programmer, disc controller and TANDOS - a 6502 CPM system. So there's plenty to keep you busy. Send for more details, and find out how you can get started for just £79.35! **ALL PRICES QUOTED INCLUDE V.A.T.**

AIM 65, KIM 1, SIM 1 USERS- READ ON!

We have produced a T.V. interface module which simply connects to the expansion socket of your computer and produces a display of 16 rows by 40 characters! Of even more interest will be our Buffer module, which allows you to expand into our system rack, giving you access to the full range of Microtan modules.

Please underline the information required.

AIM T.V. INTERFACE. MICROTAN SYSTEM.


NAME: _____

ADDRESS: _____

PLEASE ENCLOSE 12p STAMP. THANK YOU. _____

LOW-OHM METER

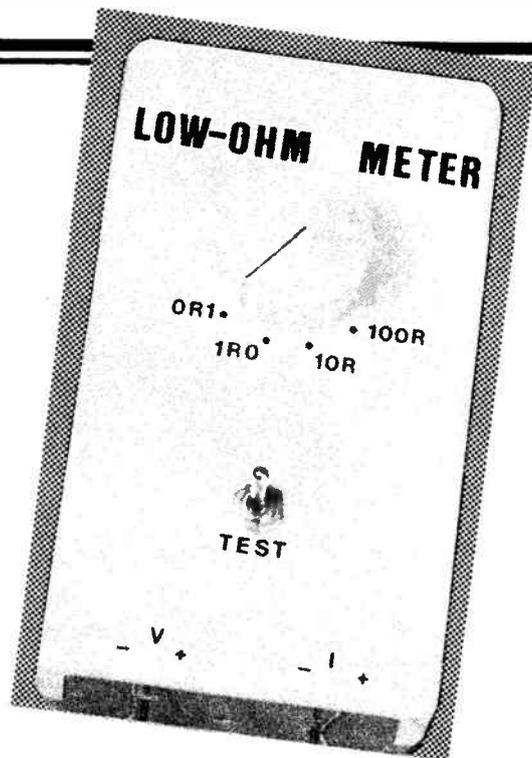Measure resistances from a hundred ohms down to a few milliohms with this accurate four-range meter. It can be built as a self-contained unit or as an adaptor for use with an existing multimeter. Design and development by Ray Marston.



Ever wanted to measure the resistance of a transformer winding or a suspect solder joint, but found that your trusty multimeter wasn't sensitive enough to do the job? If so, our Low-Ohm Meter will solve your problems. It accurately measures resistances from a hundred ohms down to a few milliohms, in four decade ranges, using a precision four-terminal measuring technique that eliminates the effect of connecting leads, etc. from the readings.

Our Low-Ohm Meter contains two fully independent (and independently powered) circuits, these being a multi-range constant-current generator and a DC millivoltmeter with a full-scale sensitivity of 10 mV. The generator is used to apply a fixed test current to the resistor that is being measured, and the voltmeter is used to measure the resultant voltage that is developed directly across the resistor, indicating the true value of the resistor and ignoring the effects of the test leads. This four terminal measurement technique is widely used in precision calibration laboratories.

The Low-Ohm Meter indicates 100 milliohms (OR1) on its most sensitive range, using a test current of 100 mA. Supply battery B1 must be capable of supplying this current without excessive voltage drop; a PP9 type is recommended. The unit consumes power only when TEST switch SW1 is closed. SW1 is a biased switch and is normally open.

Construction

The Low-Ohm Meter can be built as either a self-contained unit, with built-in supply batteries and moving coil meter, or as an adaptor unit for use with an existing multimeter. In this latter instance, use a meter set to its 1 V DC range.

Start the construction by assembling the components on the PCB, as shown on the overlay. If your meter or multimeter has a sensitivity of 100 μ A (10k/V) or better, give R9 a value of 10k. If the sensitivity is 1 mA (1k0/V) or better, reduce the R9 value to twice the ohms-per-volt value of the meter.


When assembling the components, note that PR2 is a multi-turn $3/4$ inch cermet trimmer and that its adjuster spindle overhangs the edge of the PCB; we'll refer to this end of the PCB as the 'front'. Solder four flexible leads to the indicated points at the front of the PCB. Solder Veropins to the other terminal points. Now test-fit the PCB in your chosen case. Drill a small hole in the front of the case, in line with PR2, to accept PR2's spindle and facilitate external 'set zero' adjustments. Drill two additional holes in the case front, to allow passage of the two pairs of 'I' and 'V' leads. You might consider taking the 'I' leads to a pair of quick-connection terminals (push-button loudspeaker type), for easy insertion of the resistor under test. Now drill the top of the case to accept SW1 and SW2 and fit these components into place. Finally, fix the PCB into the case and complete the interwiring to the switches.


Test And Use

When construction is complete, connect the two 9 V batteries to the unit, noting that B1 must be capable of supplying 100 mA, and connect the 'M' terminals to a 1 V DC meter or multimeter. Now short the two 'V' terminals together, close the test switch, and adjust PR2 to obtain a zero reading on the meter.

Next, turn SW1 to the 100R range and connect a 100R resistor (5% or better) across the 'I' terminals. Now connect the 'V' terminals across the test resistor (on the resistor side of the 'I' leads), with like polarities to like (+ to +, etc), close the test switch, and adjust PR1 to obtain a full scale reading on the meter. The unit is now calibrated and ready for use.

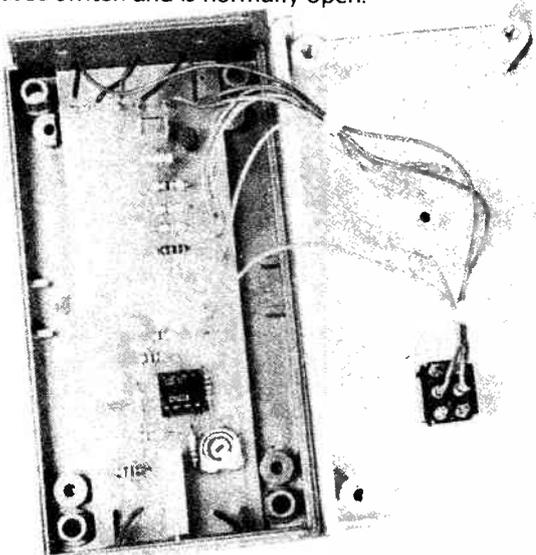The PCB is mounted so that the cermet preset can be adjusted through a hole in the case.



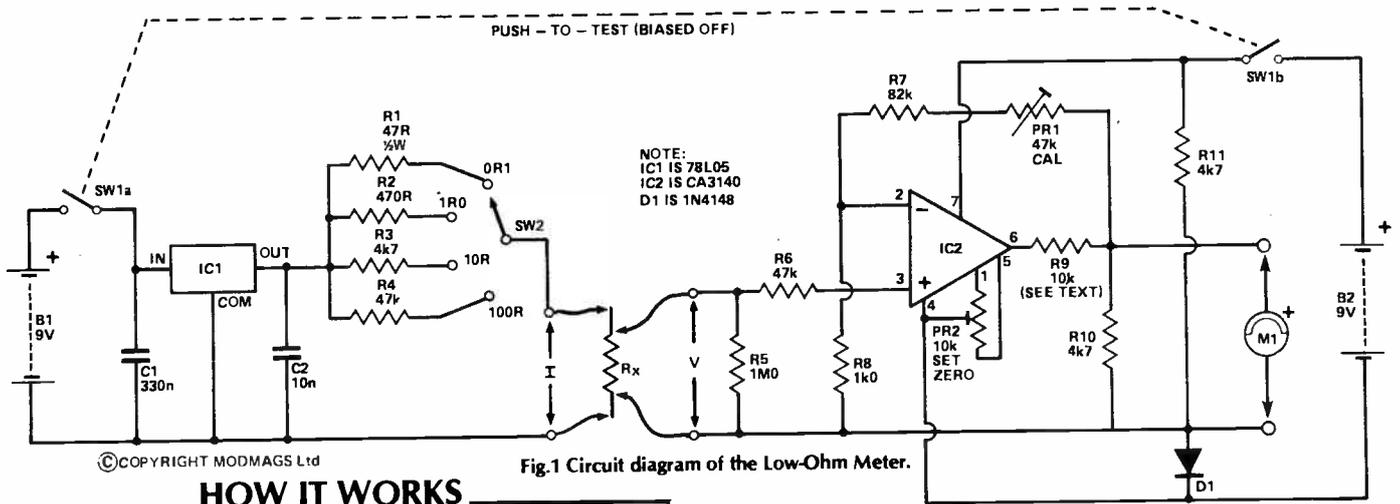

HOW IT WORKS

The constant generator circuit is very simple. IC1 is a 5 V regulator and the output test current (I) is determined by resistor R1 to R4. On each range, the value of the test resistor (Rx) is very low relative to the current-limiting resistor, and the full scale test voltage (10 mV) is very small relative to the 5 volts of the regulator. Consequently, on each range, the test current is virtually independent of the effects of lead resistances, etc: on the most sensitive (100 milliohms) range (I = 100 mA), one ohm of lead resistance will introduce a maximum full-scale error of 2%. A similar lead resistance will introduce an error of only .002% on the 100R (I = 100 uA) range. In practice, therefore, the reading errors are primarily determined by the accuracies of R1 to R4.

The DC millivoltmeter (designed around IC2) is a fairly conventional design. It is based on a CA3140 op-amp, which can respond to DC inputs down to zero volts. To enable the output to go slightly negative (for zero-setting purposes), a -600 mV supply rail is generated by R11 and D1. Resistor R9 is used to limit the maximum voltage to the meter to about 2 V, to eliminate the possibility of meter damage if the unit is incorrectly ranged. The sensitivity of the meter is variable over a limited range by PR1, for calibration purposes (to compensate for test-current errors).

When using the unit, note that the 'I' terminals supply a test current to the resistor being measured, and that the 'V' terminals indicate the voltage developed directly across the resistor. The 'V' terminals must therefore always be connected to the resistor 'inside' the 'I' leads, as indicated by the circuit diagram. When using the meter on its most sensitive (0R1) range, the 'I' leads should be kept as short as possible: on this range, 1R0 of lead resistance will introduce a maximum reading error of 2% on a 100 milliohm test resistance.

PARTS LIST

Resistors (¼W 5%, unless otherwise stated)

R1	47R ½W
R2	470R
R3, 10, 11	4k7
R4, 6	47k
R5	1M0
R7	82k
R8	1k0
R9	10k

Potentiometers

PR1	47k miniature horizontal preset
PR2	10k ¼ inch cermet multiturn preset

Capacitors

C1	330n polycarbonate
C2	10n polycarbonate


Semiconductors

IC1	78L05
IC2	CA3140
D1	1N4148

Miscellaneous

SW1	Miniature 2-pole biased toggle (normally off)
SW2	1-pole 4-way rotary switch
M1	Moving coil meter, 1 V FSD, sensitivity 100 uA or better.

Case, quick-connection terminals.

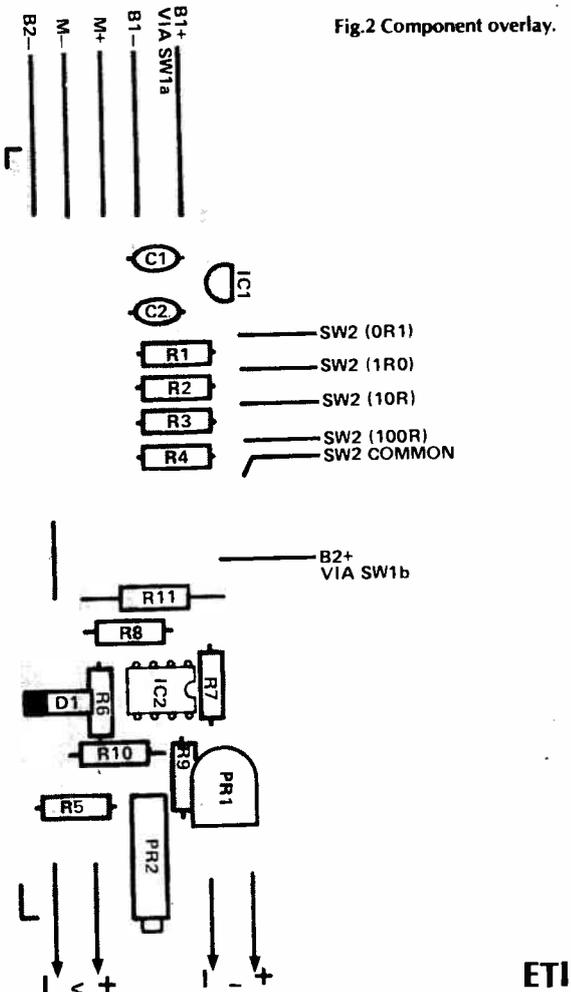

BUYLINES

Absolutely no problems here: all components are readily available

ELECTRO SUPPLIES

TRANSISTORS

8C107	10p	8C237	12p	BF194	12p	BF595	30p	2N3055	45p
8C108	10p	8C337	15p	BF195	12p	BFR40	25p	2N3583	60p
8C109	10p	8C547	10p	BF197	14p	BFY90	50p	2N3702	10p
8C1258	8p	80238	40p	BF245	30p	8UW81A	200p	2N3705	10p
8C149	10p	80239	40p	BF256A	40p	MJE340AT	50p	2N3710	10p
8C154	12p	80371A	30p	BF324	30p	MPF131	25p	2N4061	15p
8C159	9p	80X94	65p	BF469	65p	MPF132	25p	2N4123	10p
8C171	10p	80Y92	120p	BF495	20p	MPU131	25p	2N4125	12p

LINEAR ICs

CA3012	45p	MC1349	90p	TAA320	40p	T0A047D			
CA3080	50p	MC1350	90p	TBA120S	60p	TDA101D	150p	SPECIAL OFFER	
LM324	60p	MC1558	100p	TBA651	100p	TDA117D	75p	AY-5-3507 DVM	
LM741	15p	ME535T	50p	TBA661B	125p	TDA1190	200p	CHIP (with data)	
LM1458	40p	ME555	22p	TBA800	70p	TDA2524	150p	£2.75p (limited	
LM3900	60p	SAJ110A		TBA810S	80p	TDA2541	150p	quantity).	
MC1307	75p	SAS580	100p	TBA820	150p	TDA2560	150p		
MC1310	100p	SAS590	100p	TCA270S	90p	TDA2581	175p		

LOW PROFILE IC SOCKETS

14 pin - 12	100	(150 £10)	35-amp 50-volt Stud Diodes, c/w mounting kit	4 £1
16 pin - 10	100	(130 £10)		
22 pin - 7	100	(100 £10)		
24 pin - 6	100	(70 £10)		
40 pin - 3	100	(40 £10)		

For larger quantities please phone for prices

Semi-conductor Packs. Diodes / Transistors / SCRs / ICs, over 100 items (no rejects) £1.50 each, two for £2

SPECIAL OFFERS

LM1101N (DOLBY B I/C)	£2.50
TDA2020 (20 watt amp)	£2.50
MM57105 (PAL colour TV game I/C)	£2.00
MM53100N (TV clock timer)	£2.00
AY-5-1013 (UART)	£2.00

Prices include VAT, please add 50p P&P

MAIL ORDER DEPT.
(Callers please phone first)
BOWNESS MILL, SHAWCLOUGH RD
WATERFOOT, ROSSENDALE, LANCS
TEL: ROSSENDALE 5556

RETAIL SHOP
(Open 6 days)
6A TODD ST
MANCHESTER
(next to Victoria Stn.)
TEL: 061-834 1185

Counter Intelligence



Only £129-95 plus VAT

High precision, performance, reliability at a very low price. The HFC 60 high frequency counter is based on the very latest LSI technology.

- Bright 8 digit 0.5" LED display.
- Mains input for normal use.
- DC power input, 9-16 volts, for mobile use.
- Tough anodised metal case, neat tilt legs.
- Model HFC 60 - £129.95 plus VAT (60 Mhz).
- Model HFC 600 with high gain X10 UHF pre-scaler extends operation to full 600 Mhz - £159.95 plus VAT.
- Proportional temperature controlled crystal oven available for both models. Supplied fitted or as easy 'add on' £30 extra plus VAT.

Get full details on these and our other models now. Why pay more?



DRALLIM DAVIS ELECTRONICS LTD
Brett Drive, Bexhill-on-Sea, East Sussex TN40 2JR Telephone (0424) 216611 Telex 95285
Agency enquiries invited.

ELECTRONIC GAMES

ATARI



SPECIAL PRICE

£86 + VAT

INTELLIVISION MATTEL



£173.87 + VAT

This is the most advanced TV game in the world. Expandable this year into a full microcomputer. COLOUR CATALOGUE AVAILABLE WITH DETAILS ON ALL THE CARTRIDGES

CHESS



Send for further details.

COMPUTERS

NEW RANGE AVAILABLE AUGUST 1980
We specialise in computer chess machines & stock over 13 different models from £20 to £300

TELETEXT



RADOFIN TELETEXT
Add on Adaptor

£173 + VAT

BRIDGE


COMPUTER



- ★ Plays 1/2/3 or 4 Hands
- ★ Problem Mode
- ★ Audio Feedback
- ★ Instant Response
- ★ Auto scorekeeping

BACKGAMMON

COMPUTERS

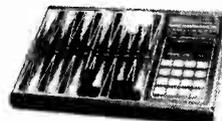

- OMAR 1
- OMAR 2
- CHALLENGER
- GAMMONMASTER

From £38 to £108. Send for further details.

SPACE INVADERS



HAND HELDS + CARTRIDGES
ATARI ACETRONIC, PRINZTRONIC
RADOFIN - OATABASE etc.

We keep a full range!
Send for cartridge lists stating which machine you own.

DRAUGHTS

COMPUTER



- ★ Solves Problems
- ★ Rejects illegal moves
- 2 level machine £43 + VAT
- 4 level machine £77.78 + VAT

LEISURE

- ★ CHEAP TV GAMES
- ★ TELEPHONE ANSWERING MACHINES
- ★ AUTO DIALLERS
- ★ CALCULATORS
- ★ DIGITAL WATCHES
- ★ PRESTEL
- ★ HAND HELD GAMES

SILICA SHOP

SILICA SHOP LTD., Dept. ET1 4
1-4 The Mews, Hatherley Road
Sidcup, Kent, DA14 4DX
Tel: 01-301 1111

FREE CATALOGUE

For a free copy of our 32 page catalogue, send a 12p stamp to Silica Shop Ltd or Telephone 01-301 1111

MAIL ORDER SERVICE - Free postage & Packing

TELEPHONE & MAIL ORDERS - accepted on:
Access ★ Barclaycard ★ American Express ★ Diners Club

CALLERS WELCOME - at our shop in Sidcup - Demonstrations daily
Open from 9am-5pm Mon-Sat. (9am-1pm Wed.)

GUARANTEE - Full 12 months + After Sales Support!


We have comprehensive brochures on all products. Please let us know what you are interested in and we will send you detailed brochures AND our own 32 page catalogue covering most games on the market.

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS		TTL Nand LSN		7442N 1.15		74LS112 0.38		74LS169 2.00		VARICAP TUNING DIODES		TRANSISTORS AUDIO DEVICES		CAPACITORS All 5mm or less spacing	
TBA120S 1.00	KB4413 1.95	7400N 0.13	7444N 1.12	74LS111 0.38	74170N 2.30	BA102 0.30	BC217 0.08	GENERAL 50V							
L200 1.95	KB4417 1.80	74LS00 0.20	7445N 0.94	74LS113 0.38	74LS170 2.00	BA121 0.30	BC239 0.08	22P, 33P, 47P, 68P							
U247B 1.28	KB4420 2.25	74LS01 0.13	7446N 0.94	74LS114 0.38	74LS174 1.20	ITT210 0.30	BC239 0.08	82P, 10P, 15P, 18P, 0.04							
U257B 1.28	KB4423 2.30	74LS02 0.14	7448N 0.56	74LS118 0.83	74LS175 1.10	BB105B 0.36	BC307 0.08	22P, 27P, 33P, 47P							
U267B 1.28	KB4424 1.65	74LS03 0.20	7449N 0.99	74LS120 1.15	74LS176 0.75	BB109 0.27	BC308 0.08	56P, 68P, 82P, 100P, 0.05							
LM301H 0.67	KB4431 1.95	74LS04 0.14	7450N 0.17	74LS122 0.46	74LS177N 0.78	MVM125 1.05	BC309 0.08	150P, 220P, 270P							
LM301N 0.30	KB4432 1.95	74LS05 0.18	7451N 0.24	74LS124 1.75	74LS181 1.65	BB212 1.95	BC413 0.10	330P, 390P, 470P, 0.055							
LM308H 0.96	KB4433 1.52	74LS06 0.28	7452N 0.28	74LS125 0.44	74LS181 3.50	KV121 2.45	BC414 0.11	150, 220, 330, 470, 0.06							
LM308N 0.65	KB4436 2.53	74LS07 0.38	7453N 0.17	74LS126 0.44	74LS183 2.10	KV122 1.95	BC415 0.07	10N (0.01UF), 0.05							
LM339N 0.66	KB4437 1.75	74LS08 0.24	7454N 0.17	74LS128 0.74	74LS184 1.35	KV122 2.75	BC416 0.08	22N, 47N, 0.005							
LM348N 1.86	KB4438 2.22	74LS09 0.24	7455N 0.24	74LS129 0.73	74LS185 1.34	KV125 2.95	BC546 0.12	100N, 220N, 0.005							
LF351N 0.38	KB4441 1.35	74LS09 0.24	7456N 0.17	74LS130 0.60	74LS188 1.10	KV125 2.55	BC550 0.12	MONOLITHIC CERAMIC							
LF353N 0.76	KB4445 1.29	74LS09 0.24	7457N 0.28	74LS132 0.78	74LS192 1.05	KV125 2.75	BC560 0.12	10N, 100N, 0.005							
LM374N 3.75	KB4446 2.75	74LS09 0.24	7458N 0.69	74LS136 0.40	74LS193 1.80	SWITCHING AND PIN DIODES	BC640 0.23	FEDTHRU							
LM380N-14 1.00	KB4448 1.65	74LS09 0.24	7459N 0.33	74LS138 0.60	74LS194 1.05	SHOTTKY DIODES	29C1775 0.18	1N0 SOLDER IN, 0.09							
LM380N-8 1.80	NE5044N 2.26	74LS09 0.24	7460N 0.17	74LS141 0.56	74LS196 1.10	IN6263 0.62	29C1772 0.18	POLYMER (SIPMENS)							
LM381N 1.81	NE5532N 1.85	74LS09 0.24	7461N 0.17	74LS142 2.65	74LS197 1.10	BA182 0.19	25D866A 0.30	10mm LEAD SPACING							
ZN4199C 1.95	SD6000 3.75	74LS09 0.24	7462N 0.28	74LS143 3.12	74LS198 1.50	BA244 0.17	25D668A 0.40	10N, 22N, 33N, 0.01							
NE544N 1.80	SL6270 2.03	74LS09 0.24	7463N 0.32	74LS144 3.12	74LS199 1.60	BA379 0.35	25D648A 0.40	10N, 22N, 33N, 0.01							
NE555N 0.30	SL6310 2.03	74LS09 0.24	7464N 0.32	74LS145 0.97	74LS207 1.08	TDAL061 0.95	25D760 0.45	10N, 22N, 33N, 0.01							
NE556N 0.50	SL6600 3.75	74LS09 0.24	7465N 0.37	74LS147 1.75	74LS215 1.08	SIGNAL DIODES & RECTIFIERS	25D720 0.45	10N, 15N, 22N, 33N, 0.06							
NE560N 3.50	SL6640 2.75	74LS09 0.24	7466N 0.37	74LS148 1.19	74LS215 1.08	IN4148 0.06	25C2546 0.19	47N, 68N, 100N, 0.08							
NE562N 4.05	SL6690 3.20	74LS09 0.24	7467N 0.38	74LS149 1.19	74LS216 1.53	IN4001 0.06	25A1084 0.20	20N LEAD SPACING							
NE564N 4.29	SL6700 2.35	74LS09 0.24	7468N 0.48	74LS150 0.99	74LS217 0.52	IN4002 0.07	25A1085 0.19	220N, 330N, 470N, 0.18							
NE565N 1.00	ICL8038CC 4.50	74LS09 0.24	7469N 0.64	74LS151 0.84	74LS218 0.52	IN4002 0.07	25C2547 0.20	MYLAR							
NE566N 1.60	MSL9362 1.75	74LS09 0.24	7470N 0.28	74LS152 0.84	74LS219 0.52	IN4002 0.07	25C2548 0.20	5mm LEAD SPACING							
NE570N 3.85	MSL9363 1.75	74LS09 0.24	7471N 0.30	74LS153 0.54	74LS223 3.00	IN4002 0.07	25C2549 0.20	10N, 10N, 22N, 33N, 0.08							
SL624 3.28	HAI1221 1.95	74LS09 0.24	7472N 0.28	74LS154 0.96	25C48 3.00	IN4002 0.07	25C2550 0.20	10N, 10N, 22N, 33N, 0.08							
TBA651 1.81	HAI1223 2.15	74LS09 0.24	7473N 0.32	74LS155 1.10	25K134 3.10	IN4002 0.07	25C2551 0.20	20N LEAD SPACING							
UA709HC 0.64	HAI1225 1.45	74LS09 0.24	7474N 0.32	74LS156 0.80	25K135 3.75	IN4002 0.07	25C2552 0.20	220N, 330N, 470N, 0.18							
UA709PC 0.36	HAI2002 1.45	74LS09 0.24	7475N 0.38	74LS157 1.10	25J 50 3.75	IN4002 0.07	25C2553 0.20	POLYSTYRENE							
UA710HC 0.65	HAI2017 0.80	74LS09 0.24	7476N 0.38	74LS158 0.67	BD535 0.52	IN4002 0.07	25C2554 0.20	10P, 15P, 18P, 22P,							
UA710PC 0.59	HAI2402 1.95	74LS09 0.24	7477N 0.38	74LS159 2.10	BD536 0.52	IN4002 0.07	25C2555 0.20	27P, 47P, 56P, 68P, 0.08							
UA711CH 0.66	HAI2411 1.20	74LS09 0.24	7478N 0.38	74LS160 1.30	BD537 0.33	IN4002 0.07	25C2556 0.20	100P, 180P, 220P,							
UA711CN 0.27	HAI2412 1.55	74LS09 0.24	7479N 0.33	74LS161 0.78	BD538 0.33	IN4002 0.07	25C2557 0.20	270P, 330P, 390P, 0.09							
UA714CN 0.70	LF13741 0.33	74LS09 0.24	7480N 0.48	74LS162 1.30	BD165 0.30	IN4002 0.07	25C2558 0.20	470P, 680P, 820P, 0.10							
UA748CN 0.36	SN76660N 0.80	74LS09 0.24	7481N 0.86	74LS163 0.78	BD166 0.31	IN4002 0.07	25C2559 0.20	10N, 1N2, 1N5, 1N8, 0.11							
UA753 2.44		74LS09 0.24	7482N 1.09	74LS164 1.30	SMALL SIGNAL RF DEVICES	IN4002 0.07	25C2560 0.20	2N2, 2N7, 3N3, 3N9, 0.12							
UA758 2.35		74LS09 0.24	7483N 1.64	74LS165 1.04	BF194 0.18	IN4002 0.07	25C2561 0.20	4N7, 5N6, 6N8, 10N, 0.13							
TBA810AS 1.09		74LS09 0.24	7484N 0.69	74LS166 1.30	BF195 0.18	IN4002 0.07	25C2562 0.20	TANTALUM BEAD CAPS							
TBA820M 0.75		74LS09 0.24	7485N 1.20	74LS167 0.92	BF195 0.18	IN4002 0.07	25C2563 0.20	16V: 0.22, 0.33,							
TC9A04E 1.80		74LS09 0.24	7486N 0.58	74LS168 1.30	BF224 0.22	IN4002 0.07	25C2564 0.20	0.68, 1.0, 0.005, 0.18							
TDA1028 2.11		74LS09 0.24	7487N 1.85	74LS169 2.50	BF224 0.18	IN4002 0.07	25C2565 0.20	16V: 2.2, 4.7, 10, 0.19							
TDA1029 2.11		74LS09 0.24	7488N 1.20	74LS170 2.50	BF241 0.18	IN4002 0.07	25C2566 0.20	6V3: 22.47, 0.005, 0.30							
TDA1054 1.45		74LS09 0.24	7489N 2.05	74LS171 0.55	BF241 0.18	IN4002 0.07	25C2567 0.20	10V: 22, 100, 0.005, 0.35							
TDA1062 1.95		74LS09 0.24	7490N 0.33	74LS172 0.55	BF241 0.18	IN4002 0.07	25C2568 0.20	ALUMINUM ELECTROLYTIC RADIAL (VERT. MOUNT)							
TDA1072 2.69		74LS09 0.24	7491N 0.76	74LS173 0.55	BF241 0.18	IN4002 0.07	25C2569 0.20	(uF/voltage)							
TDA1074A 5.04		74LS09 0.24	7492N 0.38	74LS174 1.80	BF241 0.18	IN4002 0.07	25C2570 0.20	1/63, 2/250, 4.7/35							
TDA1083 1.95		74LS09 0.24	7493N 0.78	74LS175 1.95	BF241 0.18	IN4002 0.07	25C2571 0.20	10/16, 15/16, 22/10							
TDA1090 3.05		74LS09 0.24	7494N 0.78	74LS176 1.30	BF241 0.18	IN4002 0.07	25C2572 0.20	33/6.3, 0.005, 0.08							
HAI137 1.20		74LS09 0.24	7495N 0.65	74LS177 1.95	BF241 0.18	IN4002 0.07	25C2573 0.20	22/16, 33/10,							
HAI196 2.00		74LS09 0.24	7496N 0.65	74LS178 1.30	BF241 0.18	IN4002 0.07	25C2574 0.20	47/10, 0.005, 0.09							
HAI197 1.00		74LS09 0.24	7497N 1.85	74LS179 1.30	BF241 0.18	IN4002 0.07	25C2575 0.20	10/63, 22/50, 33/50,							
TDA1220 1.40		74LS09 0.24	7498N 2.05	74LS180 1.40	BF241 0.18	IN4002 0.07	25C2576 0.20	47/16, 100/25, 220/16							
LM1301 0.99		74LS09 0.24	7499N 0.33	74LS181 1.40	BF241 0.18	IN4002 0.07	25C2577 0.20	47/6, 3, 0.005, 0.12							
LM1307 1.55		74LS09 0.24	7499N 0.33	74LS182 1.30	BF241 0.18	IN4002 0.07	25C2578 0.20	100/63, 470/63, 0.23							
MCL310P 1.90		74LS09 0.24	7499N 0.33	74LS183 2.10	BF241 0.18	IN4002 0.07	25C2579 0.20	1000/10, 0.005, 0.18							
MCL330 1.20		74LS09 0.24	7499N 0.33	74LS184 1.35	BF241 0.18	IN4002 0.07	25C2580 0.20	1000/16, 470/63, 0.23							
MCL350 1.20		74LS09 0.24	7499N 0.33	74LS185 1.34	BF241 0.18	IN4002 0.07	25C2581 0.20	1000/63, 2200/16, 0.30							
HA1370 1.90		74LS09 0.24	7499N 0.33	74LS186 0.49	BF241 0.18	IN4002 0.07	25C2582 0.20	3300/25, 0.005, 0.69							
HA1388 2.75		74LS09 0.24	7499N 0.33	74LS187 0.43	BF241 0.18	IN4002 0.07	25C2583 0.20	1000/10, 0.005, 0.88							
TDA1490 1.86		74LS09 0.24	7499N 0.33	74LS188 1.10	BF241 0.18	IN4002 0.07	25C2584 0.20	1000/70, 0.005, 3.00							
MCL496P 1.25		74LS09 0.24	7499N 0.33	74LS189 1.10	BF241 0.18	IN4002 0.07	25C2585 0.20	XAXIAL (HORIZ. MOUNT)							
SLI610P 1.60		74LS09 0.24	7499N 0.33	74LS190 1.05	BF241 0.18	IN4002 0.07	25C2586 0.20	17/25, 4.7/16, 6.4/25							
SLI611P 1.60		74LS09 0.24	7499N 0.33	74LS191 1.10	BF241 0.18	IN4002 0.07	25C2587 0.20	10/16, 0.005, 0.08							
SLI612P 1.60		74LS09 0.24	7499N 0.33	74LS192 1.05	BF241 0.18	IN4002 0.07									

PICKUP PRINCIPLES

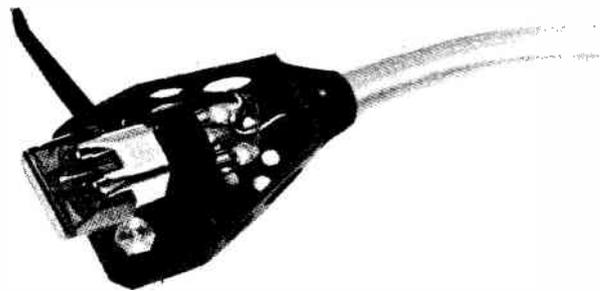

There have been many features on hi-fi in ETI. We have pondered preamplifiers. We have looked at loudspeakers. We have tested turntables. And now — Ron Harris gives you the needle!

The pickup cartridge is the smallest and most oft overlooked component in the hi-fi chain. Much debate has taken place of late as to the what, which and how of turntables and amplifiers. Speakers have also had their day in the centre of the stage, but cartridges — apart from the resurgence of the moving coil a few years back — have simply and quietly gone from strength to strength. Companies such as Goldring, Shure, Ortofon and Empire have continued to add more art to the science of music reproduction without always receiving due attention or accolade.

There have been many variations on the pickup theme. Such divergences as the electret/capacitive cartridge and the almost universal (cheap and cheerful!) piezo-electric are still for sale in most emporiums, but are of little importance to the main hi-fi market. Two main systems dominate; moving magnet and moving coil.

Both are based upon Faraday's laws of electromagnetic induction, which can be briefly, if a little impolitely, summed up as stating that if you move a magnet around anywhere near a coil of wire, you will cause a voltage to appear across that coil. The voltage will bear a direct relationship to the movement.

Elements Of Generation

Before moving on to a consideration of the important parameters and how they affect performance, let's take a look at how each of the systems work:-

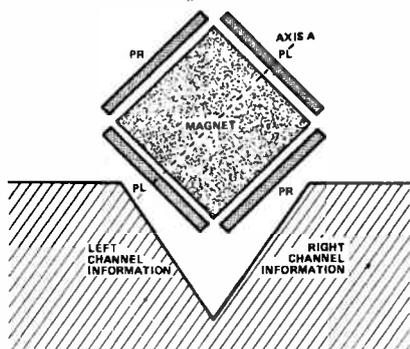


Fig. 1a The mechanical relationship between the pole pieces (which are fixed to the cartridge body), the magnet (which is attached to the stylus), and the record groove wall.

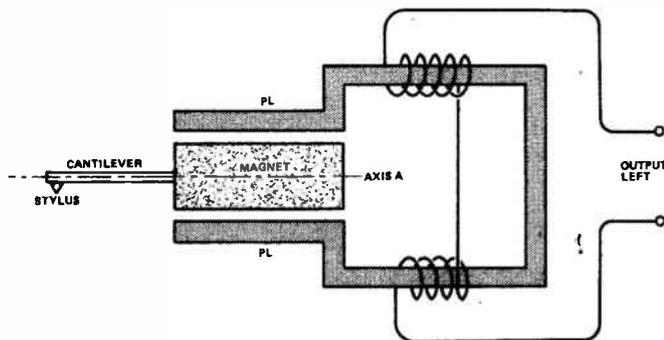


Fig. 1b Axis A can be referred to Fig. 1a to show the positioning of the generator within a moving magnet cartridge.

1/ Moving Magnet And Induced Magnet

Figure 1 shows a very generalised view of a moving magnet cartridge. Figure 1a shows the relationship of magnet to record groove and the position of the pole pieces. Axis A allows the two drawings to be related.

As the stylus follows the groove wall the magnet transcribes a similar path, parallel to PR and at varying distance from PL. A voltage is thus generated in the coil which is directly related to the groove information.

All cartridges must be well shielded from external fields generated by such as mains transformers, as the flux changes are minute and such a field can induce an output comparable to the wanted signal. (Hence that all-too-familiar mains hum.)

The most oft employed variation upon this theme replaces the moving magnets with a single high permeability armature (usually iron). The magnets are fixed within the body, with a resulting drop in mass attached to stylus. A voltage is induced into the coils by the movement of the iron armature within the magnetic field. For this reason the technique is called 'induced magnet' or 'moving iron' and excellent examples are marketed by Ortofon and Empire amongst others.

Output levels are generally around 2-3 mV.

2/ Moving Coil

It may come as a surprise to some of the newer converts to the black arts of hi-fi to know that moving coil cartridges have a longer history than the ubiquitous moving magnet. Originally



Strange looking things, but every home should have one. This particular point is a close-up Van der Hul stylus as employed in the Goldring G900IGC.

developed by Ortofon, their tracking-ability weaknesses and requirement for a step-up device led to their practical extinction a few years ago. However, the birth of the 'esoteric' hi-fi market and the subsequent interest of the Japanese audiophiles, has led to their virtues being prized over their vices once more.

The principle is extremely simple, and is illustrated in very general terms in Fig.2. The magnets are held in a fixed position within the cartridge body and the coils are mechanically linked to the stylus assembly. As the stylus follows the groove modulations the coils move relative to the magnets, thus generating the required signal voltages.

Output is generally lower, of the order of 0.2 mV and an extra amplification stage (step-up device) is required. However, a new generation of cartridges has arisen which utilise a far greater number of windings on the coils and more powerful magnets to generate a higher voltage level, comparable to moving magnet designs. The need for a step-up device is thus eliminated.

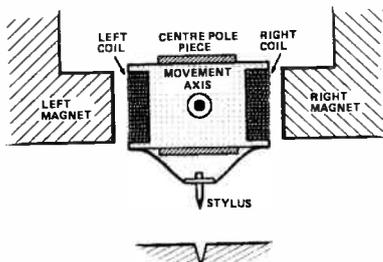


Fig. 2 Moving coil cartridge basics. As the stylus moves the coils, a current is generated within them by the magnetic field from the fixed magnets.

Two By Two

Considering the cartridge to be composed of two separate systems allows the different parameters of each to be evaluated correctly. The two systems are (i) dynamic components:- i.e. stylus, cantilever, pivot and moving generator (ii) static components:- i.e. body, fixed generator elements, electrical connections. If we define the task of the pickup as that of translating the mechanical movements produced at the stylus, by the LP, into an electrical signal for transmission to an amplifier, then we can consider the design requirements for each stage of that translation in turn.

Before proceeding, it should be noted that the pickup cartridge is an integral part of the record playing system as a whole. Many of the design parameters for the cartridge are correctly chosen to optimise the complete system under dynamic condition. In this article we cannot fully explore these interactions, but merely highlight them where they impinge upon the cartridge design directly.

Putting On The Stylus

In order to correctly interpret the record groove, a stylus must remain in contact with the groove wall, and be able to follow each and every modulation. The earliest stylus shape employed was a spherical one, simply because it was easiest to make and required least alignment. This suffered from the disadvantage of an inability to follow the highest frequencies recorded on a disc, because it will get "squeezed out" of the groove once the modulations become shorter than the length of the stylus, measured along the groove.

Elliptical styli were introduced to overcome this by reducing that length and yet maintaining as large an area of contact with the groove wall as possible. Tracking weights had to be lower to prevent record wear increasing significantly, but the modulation tracing (tracking) deficiency of the spherical tip was overcome. Many companies have since attempted to refine this stylus configuration, with varying degrees of success. Only the Shure hyper-elliptical appears to offer any real advantage over the basic design, having an increased tracking ability and better high frequency definition.

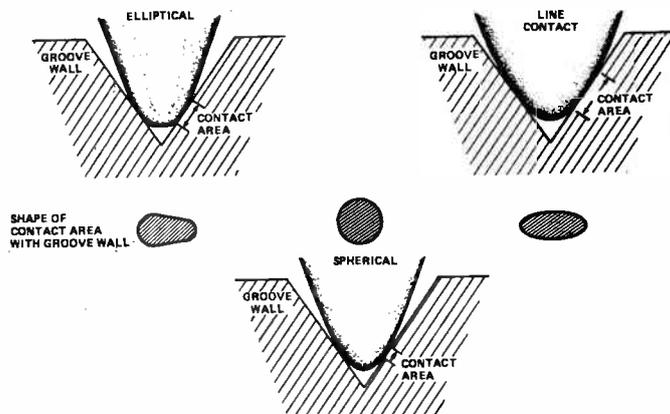


Fig. 3 The three most common stylus profiles and their relative parameters. Note that whilst the elliptical offers a greater tracking ability, its area of contact will generate increased record wear.

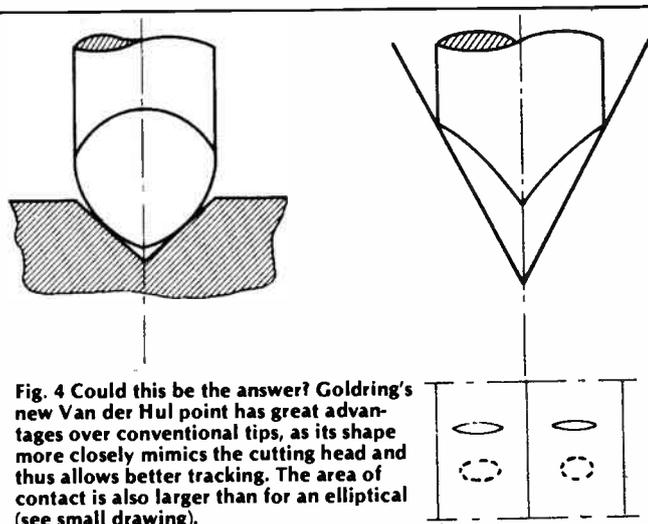


Fig. 4 Could this be the answer? Goldring's new Van der Hul point has great advantages over conventional tips, as its shape more closely mimics the cutting head and thus allows better tracking. The area of contact is also larger than for an elliptical (see small drawing).


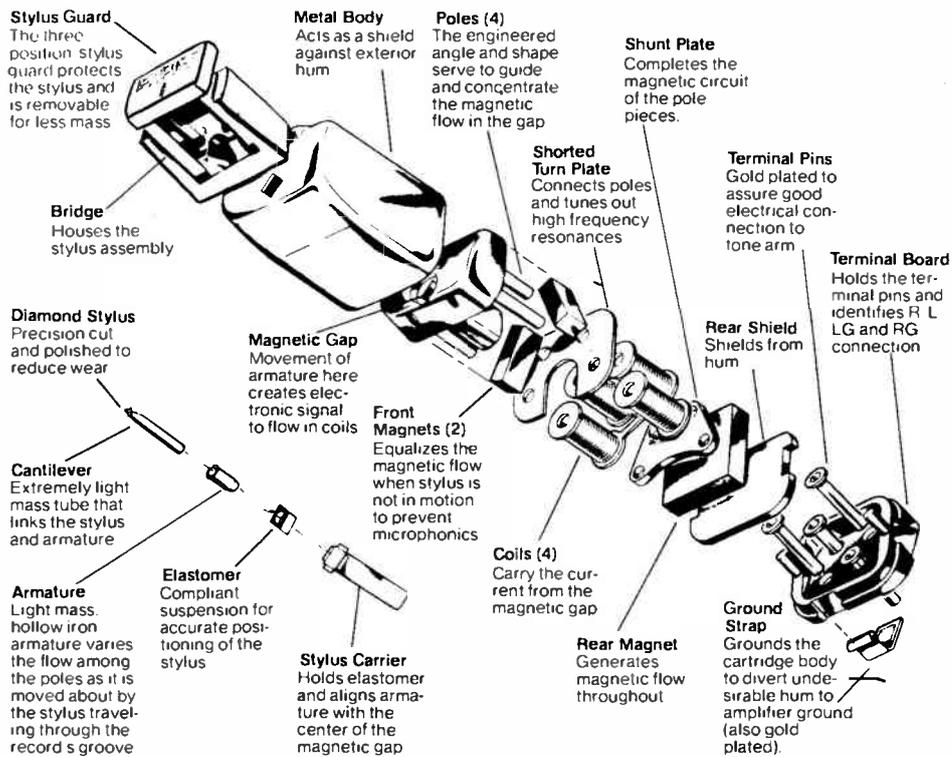


Fig. 5 This exploded view of an Empire induced magnet design gives an indication of the lengths that top manufacturers will go to in order to beat resonances and colourations.

A still later development has been the line-contact stylus, (Shibata) which has attempted to get closer to the shape of the cutter head used in the initial production of the disc — this would obviously allow it to follow the groove more closely than anything else. Contact area would also be increased, with a resultant reduction in record wear. This type has reached its zenith with the introduction of the Goldring G900 IGC cartridge and its Van der Hul stylus. It dramatically improved the performance of the G900 series and would seem, at the moment, to be closer to The Answer than anything else.

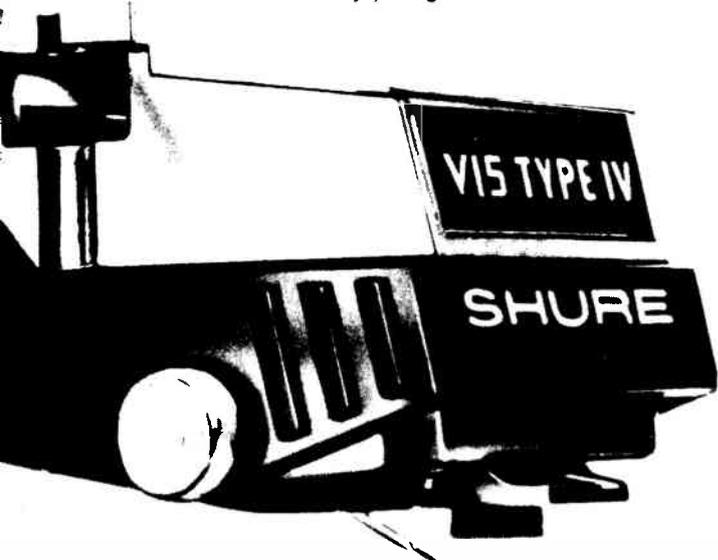

This V15IV attempts to optimise its own working conditions by using a damped, static-conducting 'rider' brush, operating ahead of the stylus. Warp effects are drastically reduced.

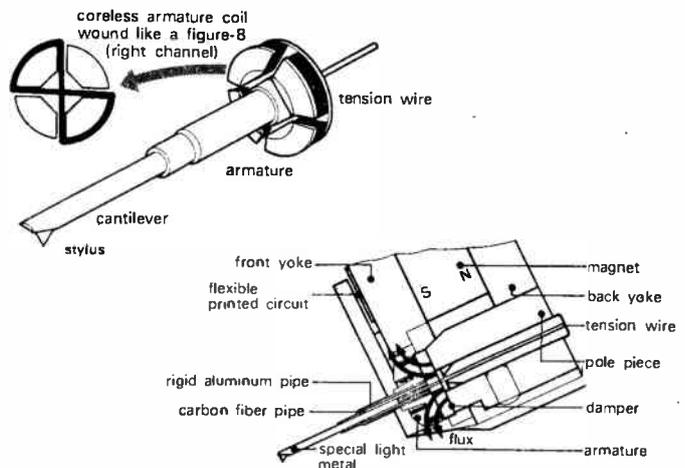


Fig. 6 A cross-section of a Sony moving coil pickup, showing how the coils are miniaturised to decrease the mass of the moving element, thus improving transient behaviour.

Cantilever Leavings

The stylus is joined to the generating element, be it coils or magnetic material, by the cantilever. It should be so attached that it tracks the disc at 20° to the vertical, (vertical tracking angle), since this is the cutting head angle and any deviation from this will be yet another source of distortion. (20° is, in fact, not yet a totally standard figure, but is the most used and best compromise figure we have).

If the cantilever were a totally rigid coupling then the pickup would be just as totally unable to produce a signal from the record, since the stylus would be prevented from moving with the groove. If it were too compliant, then the slightest warp or variation in surface would destroy the unit, with the arm mass inertia bending the cantilever out of shape.

Compliance is thus an important compromise parameter. The higher the compliance the lower must be the arm mass for the correct operation. This is because, like any mechanical system, the two working together will possess a resonant frequency — i.e. they will move easier at one frequency than any other, producing a non-linear response. Since the usable audio band extends approximately from 20 Hz-20 kHz and disc warps generally produce a signal somewhere around 6 Hz the ideal compromise is to place the system resonance between the two.

Combinations of compliance and arm mass are chosen to achieve this aim. Low mass pickup arms score a few points here as mass is easily added to these to 'tune' the resonance to an ideal frequency. If an arm is too heavy for a particular cartridge then there is little that can help — short of a hacksaw! For that reason alone, I tend to favour the SME Series III for all but a couple of cartridges — and those are low compliance, low output, moving coil designs, for which there exist specially designed carriers.

Compliance is normally measured in Compliance Units or CU where $1 \text{ CU} = 1 \times 10^{-6} \text{ cm/dyne}$.

Damping For All

All cartridge cantilevers are 'damped' to some extent, to control the resonances of the system. Some companies eg Ortofon (in the MC30) employ a complex mechanical linkage to overcome both the low frequency resonance and that at around 18 kHz — way at the other end of the spectrum — excited by the interaction between the record itself and the stylus. It is this resonance, and how successfully it is controlled which, more than any other single factor, determines how well a cartridge will audition.

A large number of factors are involved here; the mass of the stylus tip itself, the length of cantilever, compliance, damping of the pivot and the mass seen by the stylus reflected back from the arm through the cantilever, ie the effective mass of the system. It is an unfortunate fact that the better solutions to the problem are all expensive, which is why cartridges continue to cost a comparable amount of money, per ounce, to precious metals.

Generators

In the case of moving magnet designs the requirement for the fixed coils is fairly straightforward. The vast majority of amplifiers carry a 47k input, which is designed to accept these units. This makes electrical matching a fairly simple affair. The greatest source of contention will be the level of capacitance that the cartridge will be subjected to as a load. Too high a value will act as an HF filter and 'dull' the cartridge sound significantly. Too little will subjectively boost the treble, giving increased noise and a harsh brittle sound. Manufacturers always specify a capacitance value at which their unit performs best and this should be rigidly adhered to. Add about 150pF, for arm leads, to the input value of the amplifier and adjust by adding capacitors if necessary — $\pm 15\%$ will generally be close enough.

Some units, such as Grado are uncritical to a great extent, whilst others, eg Goldring, will have their subjective performance jeopardised if the value is not adjusted properly.

Moving coils present a more involved problem. The output here is too low to be connected directly to a conventional pickup, and so too is the impedance, so the step-up device must act as a buffer stage as well as providing the gain needed to allow normal usage. Impedance levels are of the order of 10-40R and as the device is essentially a current generator, noise will be a problem if matching is not precise. Again the easiest way around this is to stick with the manufacturer's recommendations as to which unit performs best with his cartridge.

High-Outputs

The latest generation of moving coil cartridges employ a generator technique which obtains outputs of around 2 mV, allowing their direct connection to a standard input. The coils in these models are generally wound with many more turns of wire to produce a higher voltage from the same magnetic field strength. The impedance is also 'padded' by this technique to improve matching. However, the resultant unit 'gain' has led some companies into problems with hum induction and electrical matching difficulties, despite their precautions.

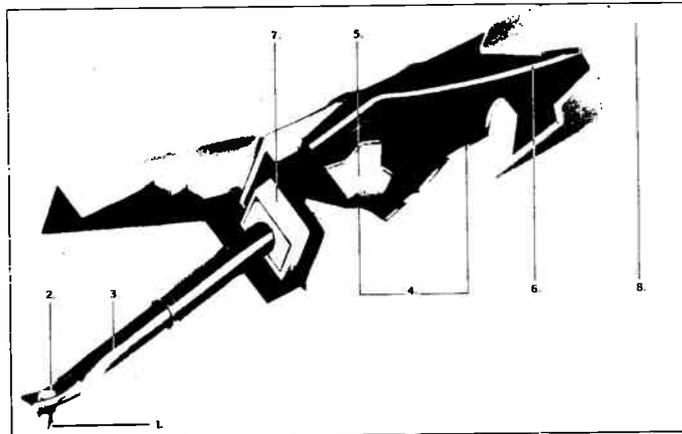


Fig. 7. So you thought cantilevers were simple? Take a look at this Shure version:- 1. Full diamond stone, meticulously shaped and polished, then assembled into an accurately machined mounting. Hyperelliptical in the V15 Type IV; hyperbolic in the M24H; biradial (elliptical) in the V15 Type III, and spherical in the V15 IV-G. 2. Doubly secure mounting — aligned, the diamond is first fitted into its socket, then high-temperature cemented to ensure permanent geometric orientation. 3. Ultra-thin-wall stylus shank — telescoped structure in V15 Type IV for low mass. Beryllium interior control lever in V15 Type III, M24H, M95 Series, M75 Type 2, and M91 Series for rigidity where needed to prevent tracking errors. 4. Viscoelastic suspension block — the efficient "heart" of the bearing which defines the pivot point of the stylus. In the V15 Type IV and M24H, a two-function bearing system separately optimized for high frequencies and for low frequencies. 5. High-energy magnet with electromachined aperture for exact positioning of stylus shank. Pivot location ensures minimal contribution to effective mass of moving system. 6. Precisely adjusted, resonance-free support wire. 7. Pivot control — correct location and function of bearing and support wire ensured. 8. Stylus assembly carrier — placement of stylus assembly relative to pickup coils within cartridge body is optimised. Not so straightforward really, is it?

Ultimo produce perhaps the best known examples of high-output moving coils and they are also renowned for requiring very high capacitive loading, well in excess of the levels normally found in amplifier circuits. *Correctly* loaded, though they possess a very high sound quality and avoid the need (and expense) of a step-up device altogether.

Conclusions

Summarising briefly then, a cartridge has to extract the mechanical information from the record groove without passing on any appreciable vibration to the pickup arm if possible, and translate this into as faithful an electrical signal as possible; it must not be affected by warps or distortions in the vinyl surface; it must be impervious to electrical fields produced by motors, transformers etc and, ideally should be totally insensitive as to which pickup arm it is used in.

Any cartridge which met those requirements could be safely described as perfect, and whilst we are unlikely ever to have such a unit offered for sale, some of the approximations we do have are really incredible engineering achievements when you consider the difficulties involved, — whether you happen to like the sound of them, or not!

ETI

CHROMASONIC electronics



48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD — 100 yards from Archway Station & 9 Bus Routes
 TELEPHONE: 01-263 9493/01-263 9495

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS

PETS & SYSTEMS

8N 8K RAM — £399
 16N 16K RAM — £499
 32N 32K RAM £599
 CASSETTE DECK — £55

343K Twin Floppy Disk
£695

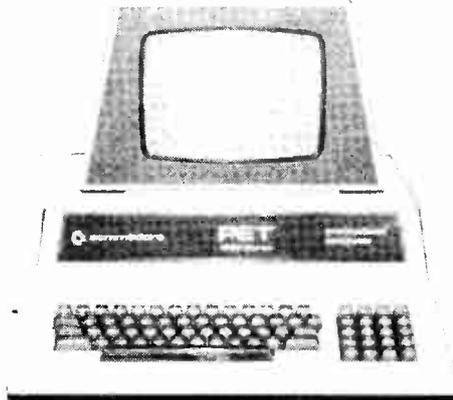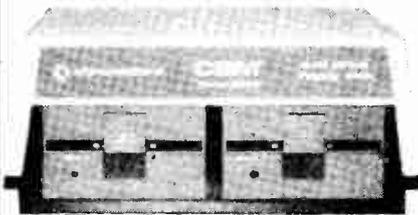

COMPLETE 32K SYSTEM £1789

NEW 32K with 80 col Screen
 Twin Disk Drive 950K **£825**
£896

All with new keyboard
 and green screen

FRICITION FEED PRINTER
£375
 Tractor Feed Printer
£425




MEMORY EXPANSION KIT

Suitable for UK101, Super-board expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£79.95**
- ★ 16K kit **£106.95**
- ★ Printed Circuit Board **£29.95**
- ★ 40 pin-40 pin header plug **£8.50**

NEW SHOP

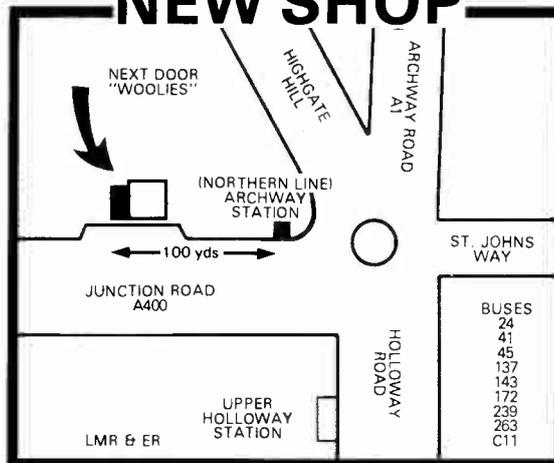

VIDEO GENIE

VIDEO GENIE based on TRS80



Utilises Z80, 12k level II Basic, Integral Cassette Deck, UHF O/P 16k RAM, all TRS80 features

£289

CASES

Available for UK101, Superboard, Nascom. Appx. DIM 17" x 15" 435 x 384 mm

PRICE £24.50
 Post & Packing £1.50

UK101 P.P.I.

Built & tested. Interfaces TX80 Printer direct. Can be programmed to operate relays, motors, various other peripherals "CENTRONICS COMPATABLE" Plugs into IC socket. LED binary display fully documented.

£29.95

U K 1 0 1


£179 IN KIT FORM
£229 READY BUILT & TESTED
£255 COMPLETE IN CASE

4K Expansion (8x2114) NOW ONLY £14.00

- No extras required
- ★ Free sampler tape
 - ★ Full Qwerty keyboard
 - ★ 8K basic
 - ★ Ram expandable to 8K on board (4K inc)
 - ★ Kansas City tape interface
 - ★ NEW MONITOR ALLOWS FULL EDITING & CURSOR CONTROL **£22.00**



PRINTERS

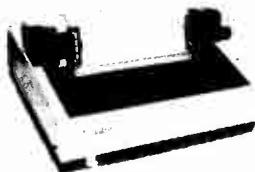

EPSON MX80 £359
EPSON TX80 £295

Dot-matrix printer with Pet graphics interface: Centronics parallel and serial: Pet and Apple compatible.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard. (Min. tel order £5) Trade and export enquiries welcome, credit facilities arranged.



CHROMASONIC electronics

NEW SHOP & SHOWROOM NOW OPEN

Telephone: 01-263 9493/01-263 9495

UK101 SOUND

Sound Generator and combined parallel in out port kit, containing P.C.B., AY-3-8910, 6820 PIA. Fully documented and demo tape. **£29.95.** AY-3-8910 £8.50.

UK101 SOFTWARE

	£
Space Invaders	6.50
Real Time Clock	3.00
Chequers	3.00
Othello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10x12 Blank Tapes	4.00

MEMORY

D.RAMS	£ p
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	3.95

S.RAMS	£
2102A	1.30
2102A2	1.69
2112A	2.75
2114/4045	2.75
4035	1.07
4044-5257	6.93
6810	3.50

BULK PURCHASE	£
8x2114	14.00
8x4116	18.00
16x2114	26.00

Z80 2.5Meg	7.95
Z80A 4Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

EPROMs

2708	4.25
2716 (5v)	6.95
2532	29.95

SUPPORT CHIPS

Z80 CTC	5.95
Z80A CTC	6.95
Z80 P10	5.95
Z80A P10	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
9224	2.75
8228	
8251	4.95
8253	9.75
8255	4.50
TMS9901	13.16
TMS9902	11.18
TMS9904 (74LS362)	8.40

ROM

2513 (UC)	5.95
-----------	------

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	1.50
8T97	1.50
8T98	1.50

I.C. SOCKETS

	D.I.L.	W/W
8 pin	.09	.25
14 pin	.11	.35
16 pin	.12	.42
18 pin	.16	.50
20 pin	.20	.62
22 pin	.22	.65
24 pin	.24	.70
28 pin	.30	.80
36 pin	—	.99
40 pin	.40	1.10

BAUD RATE GENS

MC14411	8.75
MM5307	8.75

UARTS

AY-5-1013	3.95
AY-3-1015	4.75
MM5303	4.75
TMS6011	3.55

SEND S.A.E. FOR COMPLETE PRICE LIST
OR PHONE 01-263 9493

KEELMOOR


Quality... at Keener Prices

LADIES WATCHES

5 function — Hours, mins, secs day, date, back light, auto calendar. Only 6mm thick. Elegant matching metal bracelet. Dress £8.95 Day £5.95

QUARTZ LCD Slim Chronograph. 11 function. hours, mins, secs, 6 digit-month, date, day of week. 1/100 sec stop watch split and lap modes, back-light. **ONLY £7.95**

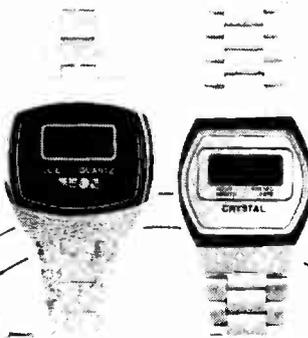QUARTZ LCD ALARM. 6 digit hours, mins, secs, day, date. 24-hour alarm with on/off indicator. **ONLY £8.95**



Send s.a.e. for colour Brochure of 120 other bargains

Send s.a.e. for colour Brochure of 120 other bargains

Send s.a.e. for colour Brochure of 120 other bargains

Send s.a.e. for colour Brochure of 120 other bargains


ALL WATCHES CARRY A 1 YEAR GUARANTEE. They come complete with fully adjustable, matching, stainless steel straps and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required. Send cheques/P.O.'s, quoting watch/watches required to

QUARTZ LCD Alarm / Chronograph. 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split & lap modes, 12 & 24 hour modes, 24 hour alarm. **ONLY £12.95**

KEELMOOR LTD
78 CASTLE STREET, MELBOURNE, DERBY, DE7 1DY
Please add 50p & p per order.

MUSICAL BOX

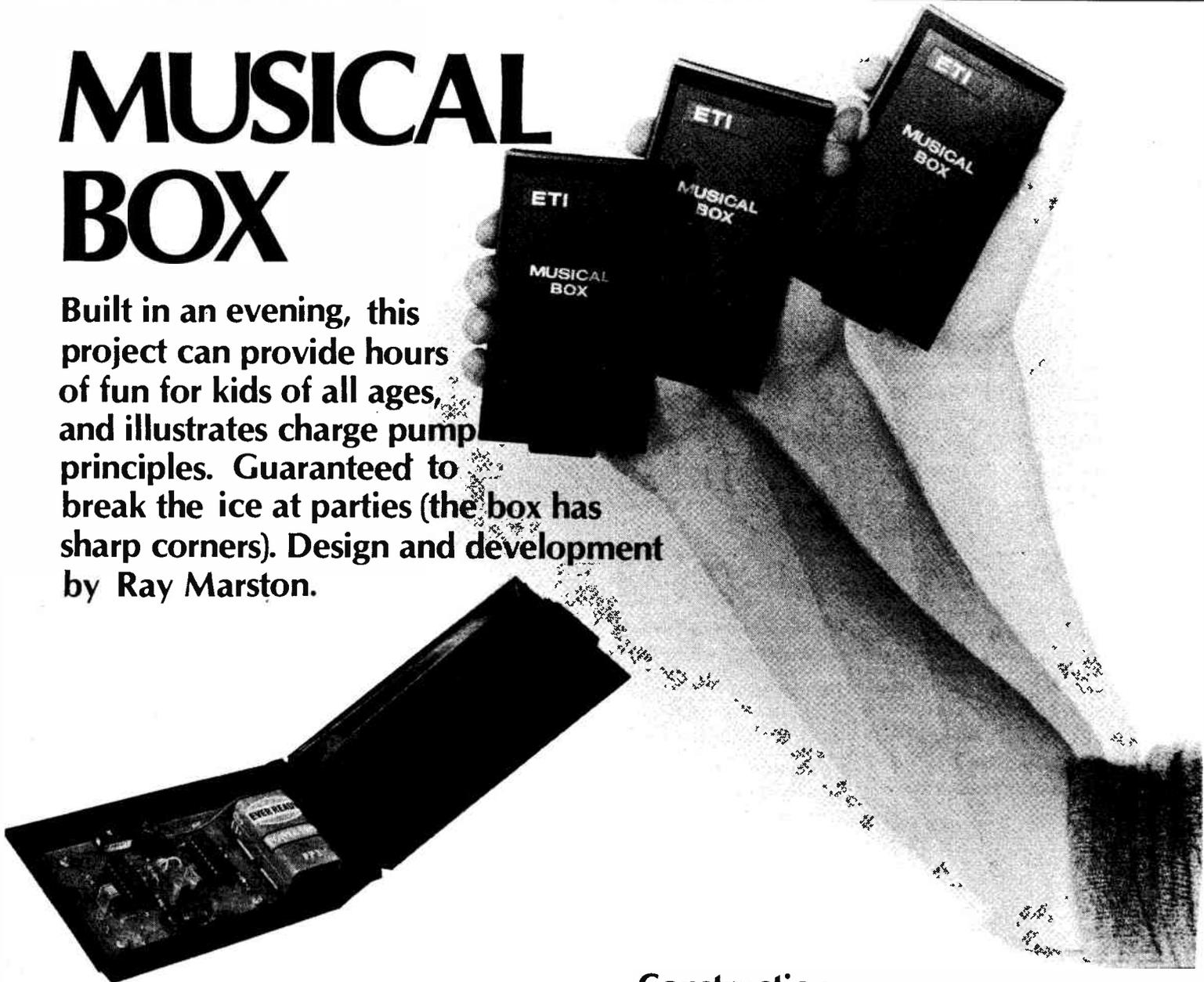Built in an evening, this project can provide hours of fun for kids of all ages, and illustrates charge pump principles. Guaranteed to break the ice at parties (the box has sharp corners). Design and development by Ray Marston.



This neat little novelty project contains a variable-frequency master tone generator and a variable-rate gate oscillator, both activated by a single built-in mercury tilt switch. The output of the tone generator is fed directly to a miniature acoustic transducer (sound generator); the frequency of this generator slowly rises when the tilt switch is open or slowly falls when it is closed. The gate oscillator is used to pulse the master tone generator on and off. Its operating rate is proportional to the switching rate of the tilt switch; the rate decays slowly towards zero when the tilt switch takes up a stable state.

Thus, if the unit is gently tilted downwards, a rising tone is generated; tilt the unit upwards, and a falling tone is produced. Give the unit a gentle shake and the tone will be pulsed on and off at a slow rate. Shake the unit vigorously and the pulse rate will rise to a high value. In all cases, the tone can be increased or decreased by suitably tilting the unit. A whole range of sounds can be produced by shaking and/or tilting the unit.

The unit is housed in a pocket-sized 'flip-top' black case. The unit's on/off switch is mounted directly on the PCB, access to the switch being gained by flipping open the case top. The unit is powered by a single PP3 battery.


Construction

This is a very easy project to build, since all of the circuit's components (including the battery and the acoustic transducer) are mounted directly on a single PCB. The PCB is designed to fit into the Verobox mentioned in the list of components.

When building the unit, note that the two CMOS ICs should be mounted in suitable sockets. Other points to note are that two bridging links are used on the board and that the mercury tilt switch is fixed by soldering it to Veropins (see photograph). On/off switch SW2 is a sub-miniature PCB-mounting type, soldered directly to the board. Don't solder the transducer leads yet.

When construction is complete, fix the acoustic transducer (Tx) to the underside of the PCB (below the large unetched copper area) with double-sided sticky pads. Now pass the transducer leads through the hole near the centre of the board and solder them in place. Fix the PP3 battery in place on the PCB, again using sticky pads. Now fix the completed PCB into the specified case, after first drilling a large hole in the case below the position of the acoustic transducer. Finally, switch the unit on, snap the lid shut, give it a shake, and sit back and enjoy the sounds.

Fig.1 Circuit diagram.

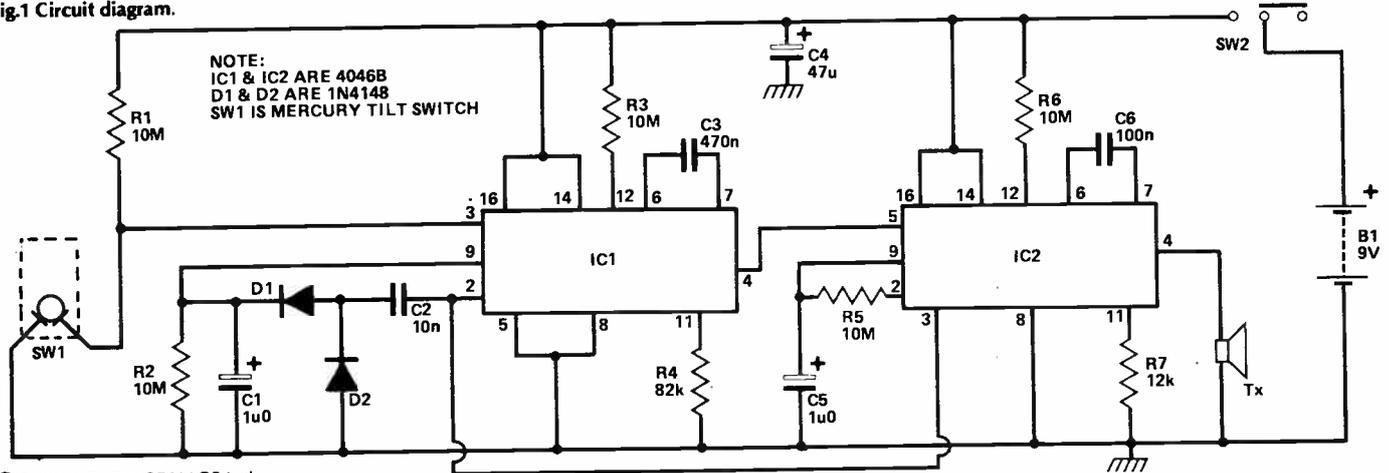

© COPYRIGHT MODMAGS Ltd

HOW IT WORKS

The circuit contains two wide-range voltage-controlled oscillators (VCOs), each built around a 4046B IC, together with a mercury tilt switch and some switch-conditioning circuitry. The two oscillators are basically similar, their frequencies being determined by the input voltage on pin 9 (of the 4046B ICs) and by the values of the capacitors/resistors connected to pins 6, 7, 11 and 12.

The 4046B ICs contain a variety of elements in addition to the VCOs. In our circuit, the most important of these is an EX-OR gate which, in our application, is wired as a simple pulse inverter with its input at pin 3 and its output at pin 2. We use these inverters as part of the switch-conditioning circuitry.

The mercury tilt switch is wired to the input of the built-in inverter (pin 3) of IC1: the output of this inverter (pin 2) is connected to the input of the inverter of IC2. If the tilt switch is opened, these two inverters cause the pin 2 voltage of IC2 to switch to a high value, so C5 starts to charge up via R5, thereby causing the VCO in IC2 to generate a rising tone signal in the acoustic transducer. When the tilt switch closes, pin 2 of IC2 switches low, causing C5 to discharge via R5 and so generating a falling tone.

The inverted switch output of IC1 (pin 2) is also fed to a charge pump circuit (designed around C2-D1-D2-C1-R2), which causes a small amount of charge to be fed to C1 each time that the tilt switch activates. This charge leaks away slowly via R2, so that the mean voltage of C1 is proportional to the rate at which the tilt switch is operated or shaken. The C1 voltage is used to control the VCO frequency of IC1, and the output (pin 4) of this IC is used to gate the VCO of IC2 on and off via pin 5.

Thus, the operating frequency of IC2 is controlled by tilting the mercury tilt switch and the pulse rate is controlled by shaking the switch.

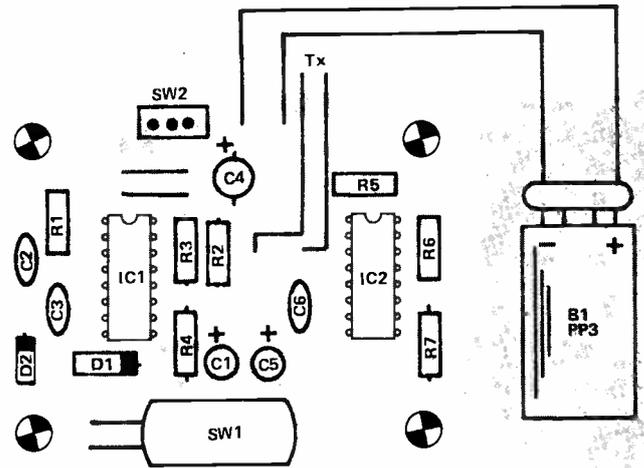


Fig.2 Component overlay for the Musical Box.


PARTS LIST

Resistors (all 1/4 W 5%)	
R1,2,3,5,6	10M
R4	82k
R7	12k
Capacitors	
C1,5	1u0, 16 V electrolytic (PCB-mounting)
C2	10n polyester
C3	470n polyester
C4	47u, 16 V electrolytic (PCB-mounting)
C6	100n polyester
Semiconductors	
IC1,2	4046B
D1,2	1N4148
Miscellaneous	
SW1	mercury tilt switch
SW2	sub-miniature PCB-mounting slide switch
Tx	PB-2720 transducer
Verocase, order no. 202-21317	

BUYLINES

The only unusual components here are the mercury tilt switch and the acoustic transducer. The transducer is available from Ambit International.

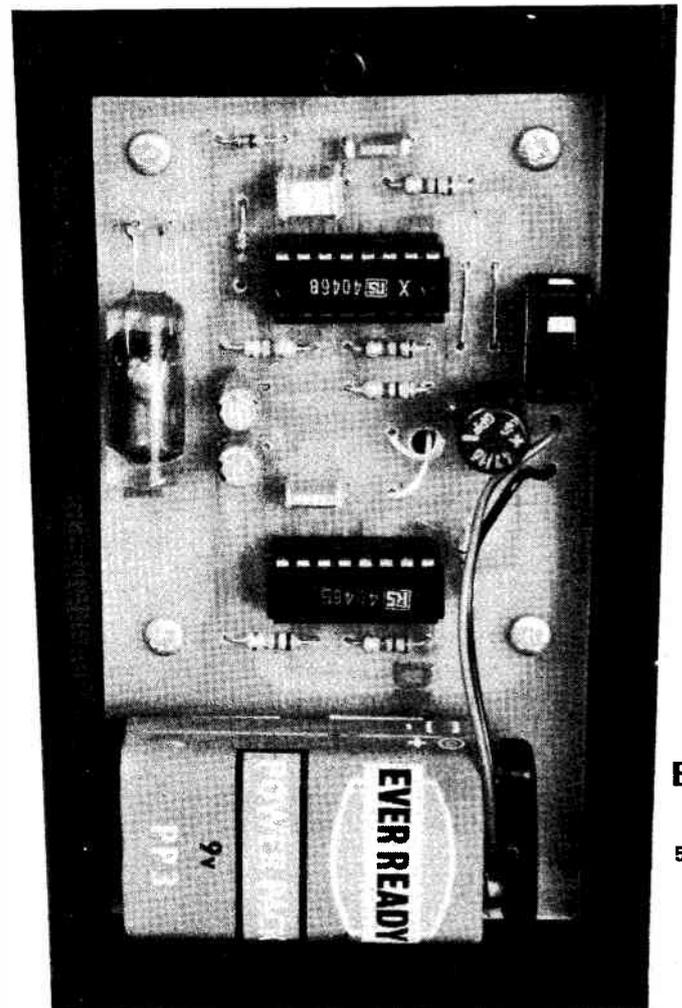The tilt switch used in our prototype is available, to order, from Watford Electronics.



PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
 Special stock pack. 60 values. 10 off each **£5.50**



DIODES: IN4148 3p each. Min order quantity - 15 items.
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
 4 Way **86p** each. 6 Way **£1.00** each. 8 Way **£1.20** each



DIL SOCKETS: High quality, low profile sockets.
 8 pin - **10p**. 14 pin - **13p**. 16 pin - **15p**. 18 pin - **19p**. 20 pin - **25p**.
 22 pin - **29p**. 24 pin - **35p**. 28 pin - **39p**. 40 pin - **57p**.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
 MIN ORDER - U.K. £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

LATEST ADDITION TO OUR RANGE OF AUDIO SIGNAL GENERATORS

MODEL AO 150

Very low distortion unit with frequency meter.

£53 (+ UK VAT). P&P £2.50

Earlier models still available (from **£23**). Send SAE for full lists plus Function Generator, Millivoltmeter, Distortion Analyser, R.F. Signal Generator, etc.

TELERADIO

325 FORE STREET, LONDON N9 0PE
 01-807 3719 Closed Thursdays



IONISER KIT

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels like fresh ocean air, pure crisp and wonderfully refreshing.

All parts P.C.B. and full instructions **£10**. A suitable case including front panel, neon switch, etc. **Available at £8** extra.

H.E. KITS

Car Booster ZD50 £18; Multi Option Siren ZD36 £10.50; Car Equaliser ZD52 £13.30; Envelope Generator ZD20 £11.79; R/C Speed Controller ZD3 £9.60; White Noise Effects Unit ZD18 £16.85; Track Cleaner ZD12 £7.75; Drill Speed Controller ZD21 £7.

All Hobby Kits supplied cases except ZD3. All kits contain components as specified plus Texas I.C. sockets where required. Also connecting wire. Special introductory offer to E.T.I. readers, a pack of nuts, bolts, washers, self-cutting, self-tapping screws supplied with each kit.

SPECIAL OFFERS

Texas/I.T.T. 1N4148, 100 for **£1.50**.

Fairchild FLV ISO Red '2 LEDs 10 for **£1**; 100 for **£7.50**.

Mullard Computer Electrolytics S/T 21,000 U.F. 40V **£3.50**

Daly Electrolytic Capacitors 2000µF, 100V **£1.50**

I.T.T. BCY 72 Transistors leads pre-formed 10 for **50p**

Varicap Tuners ELC1042 **£6.00**

Varicap Tuner ELC1043 **£6.00**

Philips Scope Tube 5" CV2191/DG-13-2 **£10.00**

Thorn-Sylvania Scope Tube 5" SE5J **£17.50** (Callers only)

Toshiba 12" TV Tube 310GAB4 **£12.50** (Callers only)

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra orders. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of Kits.

T. POWELL

306 ST. PAUL'S ROAD
 HIGHBURY CORNER, LONDON, N.1.
 TELEPHONE: 01-226 1489

Access/Visa accepted
 Shop hours: Mon. to Fri. 9-5.30. Sat. 9-4.30

POWERFET AMPLIFIERS AND COMPONENTS



POWERFETS

	CHAN	VDS max V	ID max A	PDISS max W	Price
BD512	P	60	1.5	10	90
8D522	N	60	1.5	10	85
VMP4	N	60	2.0	25	1250
VN10KM	*N	60	0.5	1.0	60
VN64GA	N	60	12.5	80	750
VN67AF	*N	60	2.0	15	80
2SJ49	P	140	7.0	100	340
2SK134	N	140	7.0	100	340

* L/p protected. † our selection. VN/VM 120-page Design Cat. **45p**. Heat clips / sink TO202 **12p**. TO92 **8p**. TO3 **35p**.

COMPONENTS

CA3045	70p	NE555	25p	40163	40p
CA3080E	70p	SAD 1024	1050p	4069	17p
CA3086	55p	TLO81	25p	709	15p
CA3140E	45p	TLO82	55p	710	25p
DAC08EN	250p	2102	80p	733	50p
DM2502	555p	2114	340p	741	18p
HA12017	80p	40018	17p	78L06	29p
HA1397	195p	4007	17p	78L12	29p
LM3900	43p	40118	17p	78M05	39p
MC3401	30p	40138	40p	78M12	39p
NE529	145p				

SCOPE TRACE DOUBLER P.C.B.

Built C/W shift, chan select, choprate controls and instructions. Useful display from DC to 10MHz. Runs from 9v battery. **£9.95**.

2x S.ADC chip set (DAC08, DM2502, NE529) with data £9. HA1388 (Bridge amp, 18w from car battery). With data **165p**.

Heatsink for HA1388/1397 **40p**.

See next month's issue for more on the PFAs or send SAE for details.

Pre-amp PAN 20 (Available March '81)

Taking advantage of Hitachi's ultra-low noise bipolar technology, J. W. RIMMER have produced a state-of-the-art pre-amp board to complement their power amplifiers.

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain/attenuator control (volume control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag. PUs, and space on the board is available for different equalisations. (Tone control + filter circuits available shortly on separate board.)

Specification

B.W 20Hz-30KHz ± 1 dB
 THD 0.003% type

at rated o/p

SNR

85dB (ref. 5mV RIAA)

105dB (ref. 100mV flat)

Vs

Output

Cost

(built board)

less controls)

Power Amp PAN 1397

(Available March '81)

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation, providing high powers from low supply voltages.

Specification

Output power RMS

THD

SNR

Input

Cost

(Built)

Power supply components for 1397. Trans (16-0-16V, 50VA)

£3.95.

Supply board, $\pm 22V$ with above, and anti-thump circuitry. Drives 2 x 1397 **£3.95**.

P&P 75p with PFAs or transformer, otherwise 40p. VAT inc. prices.

PFA120

PFA80/120

The PFA is perhaps the perfect realisation of the classic powerful amp design. The superb P.C.B. allows the use of either one or two pairs of output services, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads.)

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

Specification

Bandwidth PFA80 10Hz-100KHz ± 1 dB

Output power PFA120 100W (Vs $\pm 50V$)

RMS into 8Ω 80W (Vs $\pm 50V$)

T.H.D. $\leq 0.008\%$

from 1w to rated output at all audio frequencies

SNR 120dB

Slew Rate 20V/µs

Gain X22

Rin 30K

Vs max. $\pm 70V$

Cost

(built)

(kit)

£15.95

£13.95

£22.85

£20.85

Simple modification for bridge mode

FROM THE POWERFET SPECIALISTS **J. W. RIMMER**

Mail order only to —
 Technical enquiries


148 QUARRY STREET, LIVERPOOL L25 6HQ. Tel: 051 428 2651
367 Green Lanes, London N4 1DY
01-800 6667

Unique in concept - the home computer that grows as you do!

The Acorn Atom

£120 An outstanding personal computer kit
plus VAT and p&p.

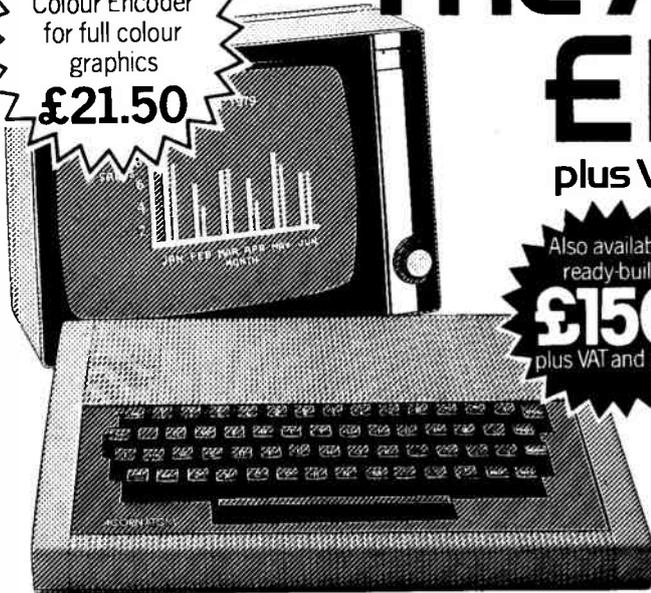NEW!
Colour Encoder
for full colour
graphics
£21.50



Also available
ready-built
£150
plus VAT and p&p

The ATOM – a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now – tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!


*The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom.

The standard ATOM kit includes:

- Full sized QWERTY keyboard ● Rugged polystyrene case
 - Fibreglass PCB ● 2K RAM ● 8K ROM ● 23 integrated circuits
 - Full assembly instructions including tests for fault-finding.
- (Once built, connect it to any domestic TV and power source)

● Power requirement: 8V at 800 M A. ATOM power unit available.

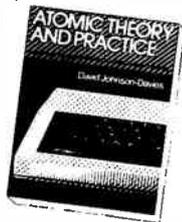See coupon. PLUS FREE MANUAL written in two sections – teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.



The ATOM concept

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMs may be linked to each other – or to a master system with mass storage/

hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally. So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

The ATOM hardware includes:

- Memory from 2K to 12K RAM on board (up to 35K in case)
- 8K to 16K ROM (two 4K additions) ● 6502 processor ● Video Display allows high resolution (256 x 192) graphics and red, green and blue output ● Cassette Interface – CUTS 300 baud
- Loudspeaker allows tone generation of any frequency
- Channel 36 UHF Modulator Output ● Bus output includes internal connections for Acorn Eurocard.

The ATOM software includes:

- 32-bit arithmetic (±2,000,000,000) ● High speed execution
- 43 standard/extended BASIC commands ● Variable length strings (up to 256 characters) ● String manipulation functions
- 27 32-bit integer variables ● 27 additional arrays ● random number function ● PUT and GET byte ● WAIT command for timing ● DO-UNTIL construction ● Logical operators (AND, OR, EX-OR) ● LINK to machine-code routines ● PLOT DRAW and MOVE.



**4a Market Hill,
CAMBRIDGE CB2 3NJ**

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Quantity	Item	Item price inc. VAT+p&p	TOTALS
	ATOM KIT-8K ROM+2K RAM (MIN)	£140.00	
	ATOM ASSEMBLED-8K ROM+2K RAM (MIN)	£174.50	
	ATOM KIT-12K ROM+12K RAM (MAX)	£255.00	
	ATOM ASSEMBLED-12K ROM+12K RAM (MAX)	£289.50	
	1K RAM SETS	£11.22	
	4K FLOATING POINT ROM (inc. in 12K Version)	£23.30	
	PRINTER DRIVE 6522 VIA	£10.35	
	(inc. in 12K version) LS244 Buffer	£3.17	
	COLOUR ENCODER	£21.50	
	MAINS POWER SUPPLY (1.3 amps)	£10.20	
		TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £
Please debit my Access/Barclaycard No.

Signature
Name (Please print)
Address

Telephone No.
Registered No: 1403810. VAT No: 215 400 220



ETI 4/81

THE BI-PAK OPTO SHOW

LEDs

1501	£0.10	TIL209 Red LED .125"
1502	£0.16	TIL211 Green LED .125"
1503	£0.16	TIL213 Yellow LED .125"
1504	£0.10	FLV117 Red LED 2"
1505	£0.16	FLV310 Green LED 2"
1506	£0.16	FLV410 Yellow LED 2"
1507	£0.80	2nd Grade LED pack 10 assorted
1522	£0.12	MIL32 Clear Illuminating Red LED .125"
1523	£0.12	FLV111 Clear Illuminating Red LED 2"
1524	£0.65	COX21 Red Flashing LED
1525	£0.75	COX95 two colour LED

OPTO-ISOLATORS

1515	£0.65	Opto-isolator IL74 Single
1516	£1.16	Opto-isolator ILD74 Dual
1517	£2.10	Opto-isolator ILQ74 Quad

7 SEGMENT LED DISPLAYS

1508	£0.80	BDL307 7 segment LED display 3"
1509	£1.80	BDL527 dual 7 segment LED display 5"
1510	£0.98	BDL707 7 segment LED display 3"
1511	£1.75	BLD747 7 segment LED display 6"
1512	£1.90	BDL727 dual 7 segment LED display 5"

MISCELLANEOUS

1514	£0.60	ORP12 Light Dependent Resistor
1518	£0.60	Photo transistor P20 NPN
1519	£0.26	Photo Darlington MEL11 NPN
1520	£0.40	Photo transistor OCP71 PNP
1526	£0.38	FPE100 Infra Red Emitter
1527	£0.38	COV89 Infra Red LED

BEGINNER'S PAK NO. 1 — 100 TRANSISTORS

A pack of well known transistors, as used in many popular projects. A must for beginners (and very useful to experienced constructors too).

10	BC107/B	TO18	Metal	NPN
10	BC237	TO92	Plastic	PNP
5	BC177/B	TO18	Metal	PNP
5	BC251	TO92	Plastic	PNP
10	BFY51-BC141	TO39	Metal	NPN
5	BC160	TO39	Metal	PNP
5	2N3055	TO3	Metal	NPN
2	BD312/MJ2955	TO3	Metal	PNP
5	TIP29-31	TO220	Plastic	NPN
2	TIP30-32	TO220	Plastic	PNP
10	OC71-76	Germanium	Metal	PNP
5	AC128-188	Germanium	Metal	PNP
5	AC127-187-188	Germanium	Metal	NPN
5	OC44-45	Germanium	Metal	PNP
5	TIS43-UT46	Unijunction	Plastic	
5	2N3819	F.E.T.		
2	MEL11	Photo Transistor Plastic		
2	BD131	TD126	Plastic	NPN
2	BD132	TD126	Plastic	PNP
—	100	TOTAL		

ALL devices — brand new and full spec. as per device coding. Data and lead out details included in pack.
Normal Retail Value £2.3
Our Special Offer Price **£15**

BEGINNER'S PAK NO. 2 — 100 RECTIFIERS, SCRs, TRIACS, DIODES

20	IN4001-IN4007	1amp Silicon Rectifier
20	IN54D1-IN54D7	3amp Silicon Rectifier
20	IN4148	Fast switch diodes Silicon
10	QA200 BAX13-16	General Purpose Diode Silicon
5	C106D	Thyristor 400v TO202 Case
2	10amp Triacs 400v	TO22D Case Isolated Tab
2	4amp Triacs 400v	TO22D Case Non-isolated Tab
10	Assorted 3amp	Thyristors 50-600 volts TO64-TO66
5	Assorted 1amp	Thyristors 50-600 volts TO39 Case
6	QAB1-91	General Purpose Germanium Diodes
—	100	TOTAL

ALL devices brand new and full spec. Data and lead out details included.
Normal Retail Value £17
Our Special Offer Price **£11**

UNTESTED SEMICONDUCTOR PAKS


U1	150 germ Gold Bonded Diodes OA47	£1.00
U2	150 germ Point contact diodes DA81	£1.00
U3	150 Silicon G.P. 200mA Diodes OA200	£1.00
U4	150 Silicon Fast Switch Diodes IN4148	£1.00
U5	25 Stud type Silicon Rectifiers up to 10A	£1.00
U6	10 SCRs 5amp TO66	£1.00
U7	40 Sil Trans NPN TO18 Case BC107/B/9	£1.00
U8	40 Sil Trans PNP TO18 Case BC177/B/9	£1.00
U9	40 Sil Trans NPN TO18 Case 2N706/B	£1.00
U10	40 Sil Trans NPN TO5-39 2N697/2N1711	£1.00
U11	40 Sil Trans PNP TO5-39 2N2905/1132	£1.00
U12	30 Sil Trans NPN TO39 BFY51-BC141	£1.00
U13	30 Sil Trans PNP TO39 BC160-161 etc	£1.00
U14	10 Sil Trans NPN TO3 2N3055	£1.00
U15	10 Sil Trans NPN TO220 TIP29-31-33	£1.00
U16	10 Sil Trans PNP TO220 TIP30-32-34	£1.00
U17	30 Sil Trans NPN TO39 High Vols. BF25B/115	£1.00
U18	40 Sil Trans TO92 BC237/B	£1.00
U19	40 Sil Trans TO92 BC251	£1.00
U20	40 Sil Trans NPN TO92 BC183.4	£1.00
U21	40 Sil Trans PNP TO92 BC257 BC212L	£1.00

Code Nos mentioned above are given as a guide to the type of device in the pack. The devices themselves are normally unmarked.

ELECTROLYTIC PAKS

A range of paks each containing 25 first quality, mixed value miniature electrolytics	
EC1 Values from .47mFD-10mFD	£1.00
EC2 Values from 10mFD-100mFD	£1.00
EC3 Values from 100mFD-1000mFD	£1.00

NEW SHAPE LEDs

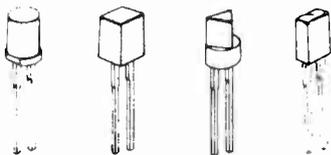

1561	£0.26	3mm Cylindrical LED Red
1562	£0.26	3mm Square LED Red
1563	£0.26	3mm Triangular LED Red
1564	£0.26	5mm Rectangular LED Red
1565	£0.26	5mm Cylindrical LED Red
1566	£0.26	5mm Square LED Red
1567	£0.26	5mm Triangular LED Red
1568	£0.28	3mm Cylindrical LED Green
1569	£0.28	3mm Square LED Green
1570	£0.28	3mm Triangular LED Green
1571	£0.28	5mm Rectangular LED Green
1572	£0.28	5mm Cylindrical LED Green
1573	£0.28	5mm Square LED Green
1574	£0.28	5mm Triangular LED Green
1575	£0.28	3mm Cylindrical LED Yellow
1576	£0.28	3mm Square LED Yellow
1577	£0.28	3mm Triangular LED Yellow
1578	£0.28	5mm Rectangular LED Yellow
1579	£0.28	5mm Cylindrical LED Yellow
1580	£0.28	5mm Square LED Yellow
1581	£0.28	5mm Triangular LED Yellow

CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors	
MC1 40 miniature ceramic capacitors 5 of each value: 22pf, 27pf, 33pf, 47pf, 56pf, 68pf, 82pf	£1.00
MC2 40 miniature ceramic capacitors 5 of each value: 100pf, 120pf, 150pf, 180pf, 220pf, 270pf, 330pf, 390pf	£1.00
MC3 40 miniature ceramic capacitors 5 of each value: 470pf, 560pf, 680pf, 820pf, 1000pf, 1500pf, 2200pf, 3300pf	£1.00
MC4 35 miniature ceramic capacitors 5 of each value: 4700pf, 6800pf, 01uf, 015uf, 022uf, 033uf, 047uf	£1.00

SPEAKERS AND CROSSOVERS

1901	Dome Tweeter 3 1/2" Bohms 50w	£2.20
1902	Dome Tweeter 3" Bohms 20w	£2.60
1903	Flared Horn Tweeter Bohms 30w	£3.80
1904	2 way crossover 15w Bohms	£1.24
1905	2 way crossover 40w Bohms	£2.70
1906	3 way crossover 60w Bohms	£3.50
1907	Plexo Tweeter	£5.20
1914	70mm 80ohm speaker	£1.20
1915	70mm 80hm speaker	£0.95
1916	56mm 80hm speaker	£0.65
1917	2 1/2" 80hm speaker	£0.75
1918	2 1/2" 64ohm speaker	£0.82
1919	5 1/2" woofer 4ohms 10w	£3.90
1920	5 1/2" woofer 8ohms 10w	£3.90
1921	5 1/2" Dual cone wide range Bohms	£5.80
1922	8" Dual cone long throw Bohms 15w	£4.84
1923	8" woofer dual 4 + Bohms rubber edge 20w	£7.80

DIL SOCKETS


1601	8 Pin	0.09	1606	22 Pin	0.24
1602	14 Pin	0.11	1607	24 Pin	0.28
1603	16 Pin	0.12	1608	28 Pin	0.32
1604	18 Pin	0.18	1609	40 Pin	0.38
1605	20 Pin	0.20			

LATE ADDITIONS — HIGH CURRENT AMPS AND SWITCHES

BFT32	£0.60	VCEO	60	VCBO	80	I.C. Max	3A
BFT33	£0.62		80		100		3A
BFT34	£0.65		100		120		3A
BFT37	£0.95		100		120		3A

RPY76A Infra Red Detector **£0.65**

LED CLIPS AND HOUSINGS

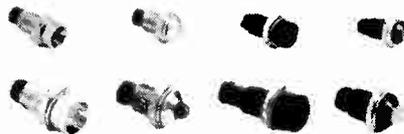

1548	£0.15	LED Plastic clips .125"
1549	£0.18	LED Plastic clips 2"
1550	£0.26	LED Housing (nickel plated) .125" A
1551	£0.22	LED Housing (nickel plated) .125" B
1552	£0.37	LED Housing (matt black) .125" C
1553	£0.31	LED Housing (matt black) .125" D
1554	£0.34	LED Housing (nickel plated) 2" E
1555	£0.28	LED Housing (nickel plated) 2" F
1556	£0.44	LED Housing (matt black) 2" G
1557	£0.36	LED Housing (matt black) 2" H

BULBS AND NEONS

1534	£0.24	LES Bulb 6v 0.36w
1535	£0.24	LES Bulb 6.5v 1w
1536	£0.24	LES Bulb 14v D.75w
1538	£0.24	MES Bulb Round 6v .04A
1539	£0.20	MES Bulb Round 6.5v .15A
1540	£0.20	MES Bulb Round 6.5v .3A
1541	£0.20	MES Bulb Round 12.0v 1A
1542	£0.20	MES Bulb Round 12.0v 2.2w
1543	£0.34	Neon Red Round 240v
1544	£0.34	Neon Red Rectangular 240v
1545	£0.34	Neon Orange Rectangular 240v
1546	£0.34	Neon Green Rectangular 240v
1547	£0.18	MES Battery Holder

CARBON FILM RESISTOR PAKS

These paks contain a range of Carbon Film Resistors, assorted into the following groups:	
R1 80 Mixed 1/4w 100ohms-820ohms	£1.00
R2 80 Mixed 1/4w 1Kohms-8.2Kohms	£1.00
R3 80 Mixed 1/4w 10Kohms-82Kohms	£1.00
R4 80 Mixed 1/4w 100Kohms-1M	£1.00
R5 60 Mixed 1/4w 100Kohms-820ohms	£1.00
R6 60 Mixed 1/4w 1Kohms-8.2Kohms	£1.00
R7 60 Mixed 1/4w 10Kohms-82Kohms	£1.00
R8 60 Mixed 1/4w 100Kohms-1M	£1.00

TANTALUM BEAD CAPACITORS

401	0.1uF 16v	0.11	414	47.0uF 16v	0.55
402	0.22uF 16v	0.11	415	100.0uF 10v	0.55
403	0.33uF 16v	0.11	416	1uF 35v	0.12
404	0.47uF 16v	0.11	417	22uF 35v	0.12
405	0.68uF 16v	0.11	418	33uF 35v	0.12
406	1.0uF 16v	0.11	419	47uF 35v	0.12
407	2.2uF 16v	0.12	420	68uF 35v	0.12
408	3.3uF 16v	0.13	421	1.0uF 35v	0.12
409	4.7uF 16v	0.14	422	2.2uF 35v	0.13
410	6.8uF 16v	0.15	423	3.3uF 35v	0.15
411	10.0uF 16v	0.16	424	4.7uF 35v	0.18
412	22.0uF 16v	0.28	425	6.8uF 35v	0.30
413	33.0uF 16v	0.50	426	10.0uF 35v	0.38

FAIRCHILD/DARLINGTONS

Type	Pol	VCEO	VCBO	I.C.	HFE	Case	£ p.
2N6052	PNP	-100v	-100v	12A	750-18K	TO3	1.50
2N6282	NPN	60v	60v	20A	750-18K	TO3	1.25
MJ3000	NPN	60v	60v	10A	1KM	TO3	1.00
SE9300	NPN	60v	60v	10A	1000	TO22D	0.90
SE9031	NPN	80v	80v	10A	1000	TO22D	0.95
SE9304	NPN	80v	80v	10A	1000	TO3	0.95
SE9305	NPN	100v	100v	10A	1000	TO3	1.00
SE9401	PNP	80v	80v	10A	1000	TO22D	1.10
TIP115	PNP	60v	60v	2A	1K	TO22D	0.40
TIP117	PNP	100v	100v	2A	1K	TO22D	0.60
TIP120	NPN	60v	60v	5A	1K	TO22D	0.60
TIP121	NPN	80v	80v	5A	1K	TO22D	0.65
TIP122	NPN	100v	100v	5A	1K	TO22D	0.68
TIP126	PNP	80v	80v	5A	1K	TO22D	0.70
TIP127	PNP	100v	100v	5A	1K	TO22D	0.72

POWER SUPPLIES

137	AC-DC Adaptor 6.7v, 9 & 12 volts	3.50
138	DC-DC Adaptor 6.7v, 9 volts	2.70

CABINETS

139	Teak 30 Case	7.00
140	Teak 60 Case	9.50

Access and Barclaycards accepted — just telephone our Orderline — Ware (STD 0920) 3182. All prices exclude V.A.T., add 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak at address below.

BI-PAK

SEMICONDUCTORS
Dept. E.T.I. 4, P.O. BOX 6, WARE, HERTS.
Tel: Ware (STD 0920) 3442. Telex: 817861.
Giro No. 3887006.
Visit our shop at: 3 Baldock St, Ware, Herts.

BARCLAYCARD

VISA

Buy it with Access

MICROBASICS

Having dealt with the hardware, Microbasics now takes a look at its use. Programmers aren't born, they're . . . programmed? A.P. Stephenson explains how.

Programming entails far more than the mechanical mastery of the BASIC language. However cunning you are with the IF/THENS, however nifty with the FOR loops, however subtle with ON GOTOs and however flashy your attack on the keyboard, you can remain in a time-wasting rut unless all this brilliance is tempered with self-discipline.

The media in general and the American TV slush programs in particular would have us believe that programmers have an IQ of three figures and walk about with glazed eyes and swollen brains. This is absolute codswallop. The primary attribute required of a programmer is patience. The secondary attribute is a strong sense of method.

A programmer must also have compassion. Consideration for the poor wretch who must use the program afterwards is not always taken as seriously as it should be. Rather paradoxically, this compassion should also be directed inward. A month or so can elapse between the start and finishing date of even moderately sized programs, at the end of which the details of the structure seem to be indelibly printed in the mind. . . a dangerous and often entirely false assumption. A year after writing it, scrutiny of the listing may fail not only in recalling to mind how the thing works but in many cases may not even be recognised as one's own work! Superficially, this would appear to be unimportant. It worked when I wrote it so why the hell does it matter if I can't understand it now? This is a comforting philosophy if the program was perfect, complete, covered all possible variations and was immune to constructive criticism. The probability of this is about as remote as finding a farmer who confesses to making a profit. In truth, any program will eventually reveal annoying deficiencies or omissions with the result that modifications are reluctantly forced upon the original masterpiece. It is at this time that the programmer may wish a little more care had been taken in the original version. A few more REMarks, perhaps, or a few less purposeless GOTOs all over the place. . . in short, a little more compassion.

A programmer must also be willing to learn from others. To put it more bluntly, you must not be afraid to cheat a little by indulging in controlled plagiarism. Programs in magazines should be studied for novel twists, clever little short cuts or elegant new solutions to old problems. Most 'inventions' are ninety-nine per cent other peoples' ideas, plus perhaps a few additions or rearrangements. The same applies to programs.

For example, the well known trick used in the PRESS ANY KEY TO CONTINUE situation:

```
200 GET K$: IF K$ = "" THEN 200
```

must have been invented by somebody and yet we all use it at times. But this is obvious you might say. So is the safety pin now, but the 'inventor' is alleged to have made a fortune. There is of course a respectable middle of the road approach between blatant stealing of an entire program (perhaps with a few pathetic attempts at disguise by changing the names of a few variables) and complete avoidance of all previous ideas.

A programmer should be familiar with the programming language. This should be self-evident but surprisingly is not always the case. It is easy to become hooked on a small subset of the language and neglect some of the keywords because they

are difficult to understand. The string handling keywords LEFT\$, RIGHT\$, MID\$ AND STR\$ are particularly neglected in BASIC and even subscripted variables are sometimes shunned. Before embarking on any ambitious project, any weaknesses in this area should be patched up by re-reading the manual and practising at the keyboard. Learning to program is like learning to play the piano. You practice difficult exercises even if they sound boring.

Last but certainly not least, a programmer must be dedicated. Once a program has been started, whatever difficulties arise, it must be finished. Shelving a program because it becomes difficult is disgraceful, pretending it was due to the usual 'lack of time' is worse. Unfortunately, it takes some time before you acquire an instinct for assessing the 'complexity potential' of a given programming project. However dedicated, it is no good carrying on if the project turns out to be beyond your capabilities. There is a balanced midway approach between dedication and pigheadedness which can only come with experience.

Before Sitting At The Keyboard

Serious works on programming have traditionally sneered at the thought of 'writing' a program at the keyboard. The correct approach, we are told, is to first draw the flowchart and then the coding on paper. . . only then should we sit at the keyboard. Whilst agreeing with the general principle, it is a little hard to stick rigidly to such idealistic advice. In the days when the main (or usually the only) peripheral was the printer and the keyboard was operated under time-sharing disciplines it was too expensive on paper and computer time to monopolise the keyboard for trial-and-error programming techniques. In the modern era of the personal computer the situation is easier and the advice can be taken less literally. However, it is advisable to scribble out a rough flowchart outlining the strategy to be employed before the bout of keyboard bashing.

Regarding flowcharts in general, there appears to be a growing doubt as to their usefulness in some quarters. It has even been suggested that most programmers write the program *first* and the flowchart *afterwards* just to please the academic Establishment. In other words the flowchart is used to explain how the program was designed rather than as a prelude to the actual design. The structure of a flowchart is beginning to show basic changes. A new idea entirely is superseding the old scheme. Thus, the flow in the new flowchart is from left to right with progressively more detailed levels of 'explanation' beneath. If you are experienced, the first left — right level is sufficient without assistance from lower levels. An idea of the difference between the old and the new can be gained by examining Fig.1 and Fig.2.

Deeper levels of even greater detail can be shown if desired. This leads on to the idea of structured programming which is a set of rules and regulations which advanced programmers are now expected to use when they are part of a team. Anyone interested should buy a book on the subject if they want to get with it! ➔

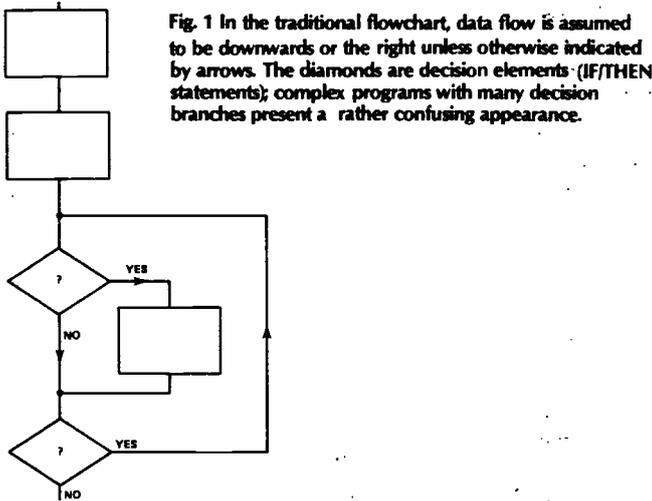


Fig. 1 In the traditional flowchart, data flow is assumed to be downwards or the right unless otherwise indicated by arrows. The diamonds are decision elements (IF/THEN statements); complex programs with many decision branches present a rather confusing appearance.

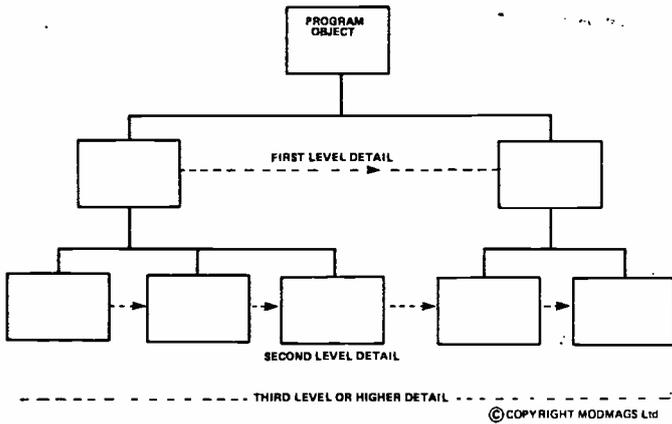


Fig. 2 In the modern flowchart, flow is only from left to right (the arrows shown are normally omitted). The different levels of detail simply 'explain' how the level above is programmed. If you are clever, the crude first level is sufficient to understand the program structure; the second level merely explains more fully how the first level works.

Back to earth again. Get hold of a folder, preferably a loose leaf ring binder, and collect vital pieces of information such as POKE numbers and codes, hex to decimal conversion tables, an abridged BASIC keyword list, the memory map (and in particular, the screen memory map), cuttings from magazine articles etc. etc. But watch the Parkinson syndrome. The binder can get fatter and fatter and particular information more and more difficult to locate as the collection grows. Be ruthless and periodically spit out the muck which, in this sense, means anything you now KNOW.

One final piece of advice... have some scrap paper and a pencil by the side of you. Once you get locked-on to a computer keyboard, it becomes an effort of will to get up and search for a pencil. Consequently you will try to memorise GOTO line numbers and almost certainly forget them once the listing scrolls back.

Starting At The Keyboard

Rule 1. Always have a blank (or rubbish) tape in the cassette, fully rewound, and another by the side. As soon as a reasonable segment of the program has been entered and roughly proved, get it onto tape and rewind it again. Then place the other tape in the cassette and continue with another segment and then tape it. The reason for this advice is based on the following possible hazards:

- a. another member of the household or workshop, unac-

quainted with the volatile properties of RAM may suddenly decide to unplug the PET in order to use the iron!
 b. the current segment you are working on has been the subject of an improvement... but a bug shows up and you get lost. Frantic efforts to remember the pre-modified version to get back to safety often fail miserably.

Under these conditions the advantage of a "fall-back" tape is obvious. By continually swapping the tapes as the program progresses, each one being a proven update of the last, much frustration can be avoided without the expensive assistance of the psychiatrist.

Rule 2. Risking the charge of advertising, PET owners should save up and get the PROGRAMMER'S TOOLKIT. This is without doubt the most useful aid to programming the PET you are ever likely to meet. Once you have used it, it appears to be indispensable. No more ragged line number sequences. No more endless searches to discover which variables have been used and which haven't. The ability to append subroutines to programs on tape is a joy to behold and operate. All this at seemingly lightening speed and idiot-proof in operation. (This should bring me a crate of whisky at Christmas).

One word of advice regarding the RENUMBERING facility. Avoid renumbering too many times during program development. This is not due to any technical reason but to the erasure of previously memorised GOTO line numbers. The TOOLKIT changes all the GOTO and THENs accordingly but it doesn't change your memory with it! As far as possible, renumber after the last bug has been hurled out of the system.

Developing The Program

There are no rules... just keep pegging away until you have 'finished'. To finish a program is perhaps the most elusive of all the arts. The elusive nature is seldom due to unexpected difficulties in the actual programming. It is a self-inflicted elusiveness resulting from, on the one hand a growing confidence, and on the other a dissatisfaction with the original terms of reference. The original moderate aim gathers momentum and the 'end' is pushed further and further away, the number of lines grow and grow, the number of variables increase, the facilities offered are increased until the bomb bursts with a polite but spine chilling message... "OUT OF MEMORY ERROR IN LINE 2.597E25".

The moral from all this can be summed up in one sentence: Decide the aim, stick to it, write it, debug it, test it, save it and switch off.

Testing The Program

After the crude bugs have been cleared and the programmer is satisfied with it, the real testing should now begin. It is necessary to enlist the aid of an independent guinea pig with no prior knowledge of computer keyboards. The luckless individual should be persuaded (or forced) to sit down and operate the program. Signs of consternation should be noted and the offending message from the screen should be earmarked for amendment. It is an astounding law of nature that if the message... "PRESS ANY KEY TO CONTINUE" meets the eye of certain guinea pigs, their diabolical little finger will jab at the STOP or the SHIFT LOCK keys; this in spite of there being about seventy other keys to assault. If you subsequently change this to PRESS SPACE BAR, the very size of the thing seems to make it transparent to the gaze and the eyes will be seen to oscillate wildly as they search for a key marked "SPACE BAR". The air usually becomes charged with emotion, sarcasm is freely interchanged between programmer and guinea pig, at times even escalating to full scale military activity. It is all very disappointing and sad for anyone trying to become a programmer. But don't let that discourage you.

ETI

Self Instruction Courses from Cambridge Learning

They're faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction — you know that you are learning and without mindless drudgery. With a good self-instruction course you become the world's best teacher.

MICROCOMPUTERS ARE COMING— RIDE THE WAVE! LEARN TO PROGRAM!

MILLIONS OF JOBS ARE THREATENED, BUT MILLIONS MORE WILL BE CREATED

LEARN BASIC

The language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest, and computer games.



COMPUTER PROGRAMMING IN BASIC (CPB) 4 Vols. £10.00

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.
Book 2 High- and low-level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.
Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK (BHB) £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL (ANS) £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here, as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

THE ALGORITHM WRITER'S GUIDE (AWG) £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

JOIN THE DIGITAL REVOLUTION!

DESIGN OF DIGITAL SYSTEMS (DDS) 6 Vols. £13.50

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers




BOOK 1 *Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems. BOOK 2 OR and AND functions; multiple-input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic. BOOK 3 Half, full, serial, and parallel adders; subtraction; processors and ALU's; multiplication and division. BOOK 4 Flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters; ROMS and RAMS. BOOK 5 Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address de-coding. BOOK 6 CPU; memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems.*

Digital calculators and watches came in during the 1970's. Soon you will see digital cash cards, telephones, car instruments, and TV messages from your friends.

DIGITAL COMPUTER LOGIC AND ELECTRONICS (DCL) 4 Vols. £7.50

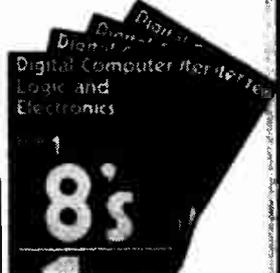A course covering the material in *italics* on the left, but at a slower pace. (4 vols)



GUARANTEE — No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition within 28 days. Our free booklist is sent with each order.

CAMBRIDGE LEARNING LTD. (Registered in England No. 1328762)
Unit 11, Rivermill Site, FREEPOST, St. Ives, HUNTINGDON, Cambs PE17 4BR. Phone 0480 67446

To: Cambridge Learning Ltd., Unit 11, Rivermill Site, Freeport, St. Ives, Huntingdon, Cambs. PE17 4BR

Order Form

PLEASE SEND: Quantity

CPB (£10.00)	<input type="checkbox"/>
BHB (£11.50)	<input type="checkbox"/>
ANS (£5.90)	<input type="checkbox"/>
AWG (£4.00)	<input type="checkbox"/>
DDS (£13.50)	<input type="checkbox"/>
DCL (£7.50)	<input type="checkbox"/>

THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE, AIRMAIL: Europe, North Africa, Middle East, add ½ to price of books. Japan, Australia, New Zealand, Pacific Islands add ¾. Elsewhere add ½.

U.K. Delivery: up to 28 days (or send 50p per course for 1st class post.)

Name

Address

.....

.....

.....

FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire)
- 2) A bank draft in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/American Express/Barclaycard/Diners Visa/Mastercharge/Trustcard

Card No

Expiry Date

Signed

Or phone us with these credit card details on 0480 67446 (24 hour ansafone service)

SPRING IS HERE

AND MEN'S THOUGHTS TURN TO...
**OUR AMAZINGLY LOW PRICED
SPECIAL OFFERS!?!**

Closing date 31 4 81

Don't forget P&P and V.A.T. to your order

6 x 555	£1.00	LEDs 0.2"	15 x BC182	£1.00
6 x 741	90p	10 each red green yellow	15 x BC212	£1.00
IC Sockets	£1.00	LM3915 + 10-element LED display	4 x C1060	£1.00
15 x 8 pin	£1.00	Liquid Crystal Display 3 1/2 x 5" digits, d.r.l.	6 x CD4011 C MOS	£1.00
12 x 14 pin	£1.00	2 x TIC226D 8A/400V Triacs	2 x 7805	£1.35
10 x 16 pin	£1.00	2 x TIC236D 12A/400V Triacs	2 x 7812	£1.00
8 x 18 pin	£1.00		2 x 7815	£1.00
6 x 22 pin	£1.00			

* BONUS * Further 5% discount if you buy the lot (£24.76 + VAT)

REMOTE CONTROL COMPONENTS AND KITS



LD271 IR Emitting diode	.36	ML926 16-channel receiver 4 momentary binary outputs	1.40
SF4205 Photodiode Detector	.90	ML928 16-channel receiver, 4 latched binary outputs	1.40
SL480 IC Pulse Amp	1.70	ML929 16-channel receiver, 4 latched binary outputs	1.40
SL490 32 Command Encoder/transmitter	2.40	Clip-on Plastic Reflector for IR LEDs, increases range	.20
ML922 16-channel receiver + 3 analogue outputs	4.20		

NEW ML925 A decoder designed for model/toy control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg. gun turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. **2.10**

To make things EVEN EASIER, we have designed several new kits —
MK6 — Simple Infra Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **4.20**
MK7 — Infra Red RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. **5.00**
* Special Price * MK6 and MK7 together. Order as RC500K. **12.50**

MK8 — Coded Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8x2x1.3 cms and requires a 9V (PP3) battery. **5.90**
MK9 — 4 Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter. **1.90**
MK10 — 16-Way KEYBOARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. **5.40**

MK11 — 10 On-Off Channel IR RECEIVER with 3 analogue outputs (0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply. **12.00**
MK12 — 16 Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. **11.95**
MK13 — 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and -, analogue + and - (3), mute, normalise analogue outputs, and on/standby. **4.35**



24HR CLOCK/APP TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY 5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac PCBs & full instructions.

CT1000K Basic Kit	£14.90
CT1000KB with white box (56:131 x 71mm)	£17.40
Ready Built	£22.50

DIGITAL VOLTMETER/THERMOMETER KIT



Based on the ICL 7106. This kit contains 1 PCB, resistors, presets, capacitors, diodes IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). **£19.50**

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/THERMOSTAT
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 1KW. **£4.**

MK2 SOLID STATE RELAY
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

MK3 BAR/DOT DISPLAY
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER
Based on the TOA1024 Zero voltage switch, this kit may be wired to form a 'burst fire' power controller or a 'proportional temperature' controller enabling the temperature of an enclosure to be maintained to within 0.5°C. 3KW. **£5.55**

MK5 MAINS TIMER
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. **£4.50**

TRIACS

400V Plastic Case (Texas)		
3A TIC206D	49p	
8A TIC206D	58p	
12A TIC236D	55p	
16A TIC246D	95p	
25A TIC2630	190p	
6A with trigger Q4006LT	80p	
8A isolated tab TXAL2268	65p	
Diac	18p	

LIGHTING CONTROL KITS

Directly replace conventional light switch and cord up to 300W of lighting. No messy wiring. Insulated touchplates. Easy to follow instructions.

TO300K TOUCHDIMMER Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. **£6.50**
TOE/K Extension kit for TO300K for 2-way switching, etc. **£2.00**

TSA300K TIMEDELAY TOUCHSWITCH Delay variable from 2 secs to 3 1/2 mins. **£4.30**
LO300K Conventional LIGHTDIMMER **£3.20**

DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

DL 1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.80**

DL21000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Output switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**

Optional Opto Input
DLA1 60p



ARE YOU SITTING COMFORTABLY?

Our new TDR300K Touch Dimmer Kit will ensure that you are. Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter. The complete kit, which includes easy to follow instructions, will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.



In years to come everyone will be selling remote control dimmers, but you can have ONLY TDR300K kit now for ONLY £14.30 for the dimmer unit and £4.20 for the transmitter.



For the more athletic of you, the TD300K Touchdimmer kit is still available at £6.50 and the TDE/K Extension kit, for 2-way switching etc., is £2. DON'T FORGET to add 50p P&P and 15% VAT to your total purchase.

INTEGRATED CIRCUITS

555 Timer	21p
74 Op. Amp	19p
AY-5-1224 Clock	£2.60
AY-5-1230 2 Clock/Timer	£4.50
AY-3-1270 Thermometer (ICL7106 DVM (LCD drive))	£8.20
LM2907 Fv Converter (8 pin)	£1.40
LM377 Dual 2W Amp	£1.45
LM3795 Dual 6W Amp	£3.50
LM380 2W Audio Amp	80p
LM382 Dual low noise Preamp	£1.00
LM386 250mW low voltage Amp	75p
LM1830 Fluid Level Detector	£1.50
LM2907 Fv Converter (8 pin)	£1.40
LM2917 Fv Converter (14 pin)	£1.80
LM3909 LED Flasher/Oscillator	60p
LM3911 Thermometer	£1.20
LM3814 Dot-Bar Driver (Lin)	£2.10
LM3915 Dot-Bar Driver (log)	£2.20
MM74C911 4 digit display controller	95p
MM74C915 7 segment BCD converter	95p
MM74C926 4 digit counter with 7 seg out	£4.50
5568B Touchdimmer	£2.50
SL440 AC powered control	£1.75
SN76477 Complex Sound Generator	£2.52
TBA800 5W Audio Amp	68p
TBA10AS 7W Audio Amp	£1.00
TOA1024 Zero Voltage Switch	£1.20
TDA2020 20W Audio Amp	£2.85
ZN1034E Timer	£1.80

All ICs supplied with data sheets
Data Sheets only 10p each device

MINI TRANSFORMERS

Standard mains primaries 240V a.c.		
100mA secondaries		
6.0-6V	80p	
9.0-9V	85p	
12.0-12V	90p	
Opto Isolated TRIAC MOC 3020 400V	£1.10	

LEDs

0.1" Red	9p
0.1" Green	12p
0.1" Yellow	12p
0.2" Red	9p
0.2" Green	12p
0.2" Yellow	12p
0.2" chips	3p
Rectangular Red 16p	
Rectangular Green 17p	
Rectangular Yellow 17p	
Flat Face Rectangular, Triangular, Arrow-head Square	
Red	17p
Green	20p
Rec. Yellow	20p

DISPLAYS

DL304 Red 0.3" c.c. pin com. compatible with DL704	75p
DL307 Red 0.3" c.c. pin com. compatible with DL707	75p
DL727 Dual 0.5" c.c. Red, four digit multiplexed	£1.50
MP463 0.5" c.c. Red, four digit multiplexed	£2.20

CMOS

4000	17p	4019	42p	4069	19p
4001	16p	4023	22p	4070	19p
4002	18p	4025	21p	4071	18p
4007	17p	4026	£1.30	4077	26p
4011	19p	4027	40p	4081	20p
4012	17p	4028	50p	4093	54p
4013	35p	4040	80p	4501	24p
4015	75p	4049	38p	4511	90p
4016	35p	4050	40p	4514	£1.80
4017	70p	4060	£1.08	4516	£1.80

BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black.

B1 75x6x35mm	65p
B2 95x71x35mm	85p
B3 115x95x37mm	95p

D.I.L. I.C. SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	34p
16 pin	14p	40 pin	36p

Soldercon Pins 50p/100

CAPACITORS

Polyester 250V			
0.01	0.22	5p	12p
0.002	6p	0.33	12p
0.033	7p	0.47	15p
0.047	7p	0.68	18p
0.068	7p	1.0	24p
0.1	7p	1.5	27p
0.15	12p	2.2	31p

Electrolytics A Axial R Radial			
63V 10 R	5p	16V 10 R	5p
2.2 R	5p	22 R	5p
4.7 R	6p	33 R	5p
10 R	7p	47 R	6p
47 R	12p	100 R	8p
25V 22 A	8p	220 R	11p
47 A	10p	470 R	14p
100 A	14p	1000 R	20p
110 A	15p	10V 47 A	8p
470 A	24p	100 A	8p
1000 A	34p	220 A	12p

Tantalum (bead)			
35V 0.1	9p	10V 22 A	20p
0.22	9p	6.3V 33	20p
0.47	9p	0.68	27p
1.0	9p	3V 100	27p
2.2	10p		
4.7	14p		
10	20p		

Ceramic 50V			
100pF	4p	1,000pF	4p
220pF	4p	2,200pF	4p
470pF	4p	4,700pF	4p
		10,000pF	5p

ZENER DIODES

400mW 1/2 10V	8p
3W 7.5 27V	15p

RESISTORS

1/4W 10 ohm-10M, E12 series
Pack of 10 (one value)
10 Packs (10 values)
80p

VOLTAGE REGULATORS

Available in 5V, 12V & 15V versions.
78L series 100mA pos. 26p
79L series 100mA neg. 60p
78 series 1A pos. 52p

LM317T adjustable 1.2V-37V 1.5A **£1.80**

RECTIFIERS

1N4001 1A/50V	4p
1N4004 1A/400V	6p
1N5401 3A/50V	18p
1N5404 3A/400V	10p
1A 50V Bridge	18p
1A 400V Bridge	22p
3A 50V Bridge	11p
3A 400V Bridge	58p

(Bridge rectifiers are miniature PCB mounting types)

V MOS POWER FETS

VN10KM 0.5A/60V (T092)	52p
VN66AF 2A/60V (T0220)	88p

TRANSISTORS

BC108	8p	BFY50	20p
BC182	8p	TIP31A	40p
BC182L	8p	TIP32A	40p
BC212	8p	2N3055	45p
BC212L	8p	2N3442	90p
BC337	18p	2N3819	20p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD 50p P&P and 15% VAT TO TOTAL OVERSEAS CUSTOMERS ADD £1.50 (Europe) £4 (elsewhere) for P&P. Send size for price list and with all enquiries. Cashers welcome 9.30-5.00 (Mon-Fri) 10.00-4.00 (Sat).

TK Electronics
(ETI), 11 BOSTON ROAD
LONDON W7 3SJ. 01-579 9794



NOISE GENERATOR

Despite what the average audiophile will tell you, noise can be useful. This noise generator with sample and hold facility is the basic building block for Project 80 sound effects. Design and development by Charles Blakey.

Noise sources are essential for the synthesis of many sounds. These range from musical instruments, such as pipe organ and percussive devices, to natural sounds like wind, rain and surf, and to man-made sounds such as steam engines, explosions and gunfire. The 80-12 module provides white noise, which has the characteristic hissing sound, pink noise, which is deeper in intensity, and a low frequency noise (sometimes referred to as red noise). The low frequency noise may also be used as a random modulating source.

A sample and hold circuit, also incorporated, allows external sound sources to be sampled and converted into control voltages for, say operating a VCO. The sample and hold unit, therefore, provides a means by which the synthesiser can play itself.

Noisy Networks

In this design white noise is produced by reverse biasing an NPN transistor, since this method produces a wide bandwidth. The main problem with this technique is the low amplitude of the noise and often the need to try several transistors to attain the desired amplitude. This has been largely overcome by using a two stage amplifier, IC1a and IC1b, which allows the overall gain to be varied between about 100 to 5700 times. As an additional safeguard the transistor is mounted in a socket to facilitate trying other devices, should the amplitude prove insufficient. White noise is defined as having equal energy per cycle and pink noise equal energy per octave. To derive the latter requires the white noise to be filtered at -3 dB/octave and, since filters usually have slopes of 6 dB/octave, a 3 dB type has to be approximated. Note that other variations in noise colouration may be obtained by filtering the white or pink noise with Project 80 filters 80-6 or 80-7. The low frequency noise is obtained by low pass filtering the pink noise using a 6 dB/octave filter with a cut-off frequency of about 16 Hz (constructed around IC1d). The white and pink noise outputs will be in the range 5-10 V p-p while the low frequency noise is 10 V p-p.

The sample and hold circuit uses the principle of gating a FET, Q2, on and off and storing the sampled voltage on C16, which is buffered by voltage follower IC5b. FET gating is achieved using a CA3140E, configured as a comparator such that a positive clock pulse will cause it to go high (about 13 V) and allow the signal through to be stored on C16. When the clock pulse is near zero, IC4 will swing to about -14 V and gate the FET off. If the signal being sampled is varying rapidly in amplitude, it is essential that the clock pulse be short otherwise the output will not be in discrete steps but will follow the variations in signal amplitude while the clock pulse is high.

The internal clock in the 80-12 uses a CMOS 555 timer whose sampling rate may be varied from about 1 cycle per 4.5 S to 25 Hz. The pulse width is adjustable and the output from the clock, buffered by IC3, is available for use as, say, a



PROJECT 80 NEWSFLASH: Due to considerations of space and time, the final Project 80 module, a combined effects unit (containing an external Input Interface and Dual Ring Modulator), the system keyboard and the keyboard controller will now be available in a booklet at the end of February. To get your copy send a cheque or postal order for £2.95 (including postage and packing) to: ETI/Project 80, 145 Charing Cross Road, London WC2H 0EE.

synchronising trigger on an ADSR. Provision is made for using an external clock and the pulse output from the 80-2 VCO or 80-3 VCLFO is suitable.

Achieving the desired results depends on the clock rate and the amplitude of the signal being sampled. The latter may be attenuated by RV2. Additionally, when using a VCO as the clock, the pulse width is another variable for special effects.

Construction And Setting Up

Setting up the noise generator is simply achieved by adjusting PR1 to obtain the desired amplitude. This may be done in three ways: (a) using a DMM on the white noise output and adjusting PR1 until a reading of about 1V8 to 3V2 is obtained on the AC range; (b) using an oscilloscope and observing the white noise output while adjusting PR1 to obtain a peak to peak output of 5-10 V; or (c) connecting the output of the low frequency noise at R16 to a DC voltmeter and adjusting PR1 until occasional readings of about -7 V are obtained when observed over a period of a few minutes. With most analogue meters the above readings will be approximately halved. With some transistors it may be possible to obtain the correct amplitude of the white and pink noise by increasing the gain with PR1, but the amplitude of the low frequency noise will be too high. In the latter circumstances the best approach is to try another NPN transistor rather than alter the value of R14.

Only one adjustment is required in the sample and hold section, namely, to adjust PR2 to obtain a short pulse output from the internal clock based on IC2. This adjustment should be made in the following sequence:-

- a) Connect the low frequency noise output to the signal input of the sample and hold with RV2 fully clockwise. →



PIN VIEWS

NOTE:
IC1 LM348
IC2 ICM7555
IC3,4 CA3140E
ICS TL082

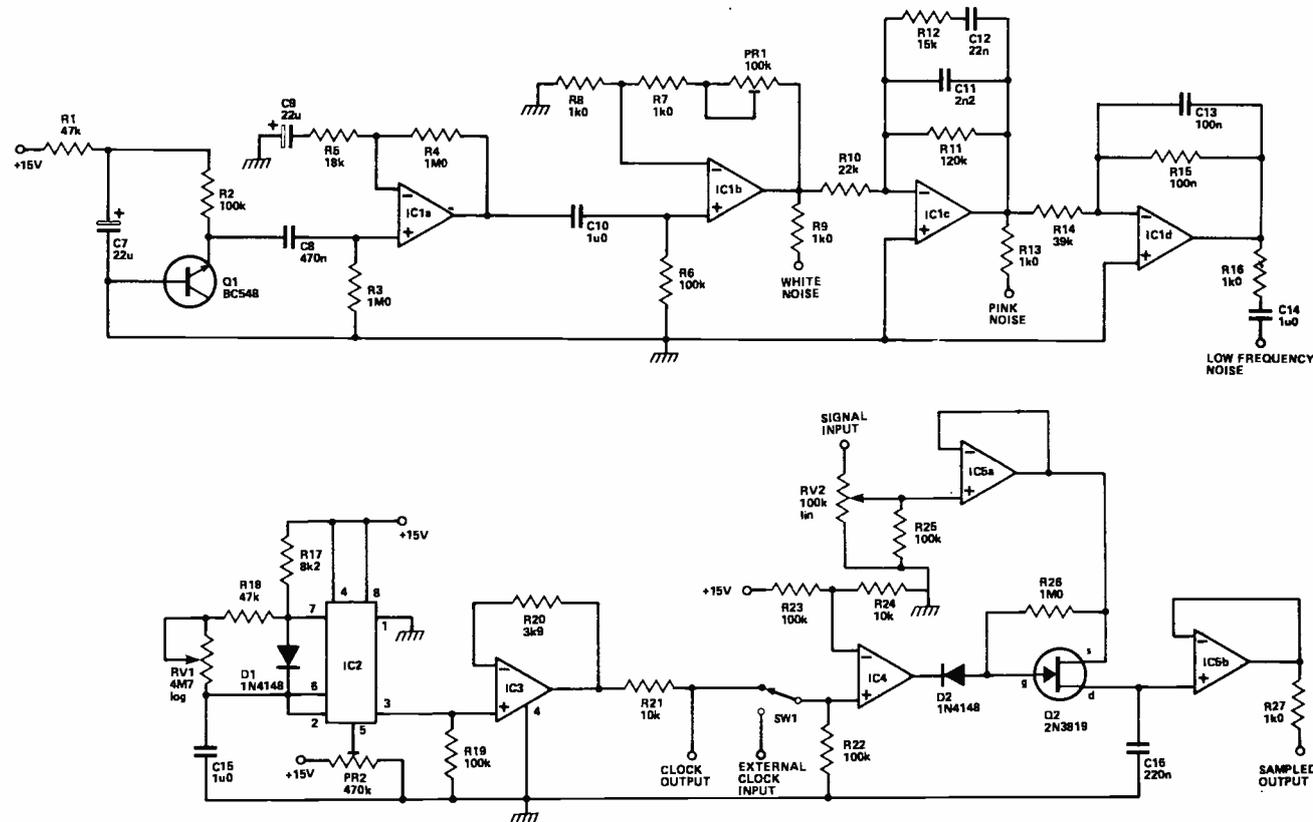
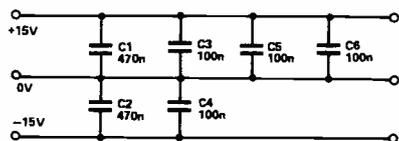


Fig.1 Circuit diagram.

- b) Connect the output of the sample and hold to a VCO with the coarse frequency control set to mid position and one of the waveforms connected to an amplifier.
- c) Set RV1 (clock rate) to about 75% rotation which should give a sampling rate of about 2-3 Hz.
- d) Turn PR2 fully anti-clockwise and switch power on.
- e) After a few seconds delay slowly turn PR2 clockwise until the VCO output starts changing frequency in a step-wise manner.
- f) Finally check that the VCO continues to change step-wise over the full range of the internal clock (RV1) and if necessary turn PR2 further clockwise until this is achieved.

HOW IT WORKS

Reverse biasing the NPN transistor, Q1, will generate noise at its base-emitter junction. The few millivolts of noise at the output of Q1 has to be amplified to the levels required for the synthesiser and this is achieved with two AC coupled non-inverting amplifiers configured around IC1a and IC1b. The gain of IC1a is fixed at about 56 while the gain of the IC1b amplifier may be adjusted from 2 to 102 by means of PR1. The overall gain of the amplifier section may, therefore, be varied from 113 to 5760 times. The amplified white noise is available via R9.

To obtain pink noise it is necessary to filter the white noise by -3 dB/octave and a close approximation over the audio range is obtained with the active filter built around IC1c. R11 and C11 form a first order low pass filter with a cut off frequency of 663 Hz, while R12 and C12 are an augmenting integrator which has an output proportional to the input signal added to an output proportional to the time integral of the input signal. The frequency response of the latter is relatively flat above about 1 kHz and below this frequency the incoming signal is attenuated at a rate of 6 dB/octave. The combination of R11/C11 with R12/C12 achieves the -3 dB/octave response and the pink noise output is available at R13. The low frequency noise is obtained by using a first order low pass filter with a cut off frequency of about 16 Hz and this is obtained with IC1d, R15 and C13 with the output being available via R16 and C14.

In the sample and hold network a signal is applied to the source of FET, Q2, via IC5a configured as a voltage follower and whose signal

input may be attenuated by RV2. When Q2's gate is positive, the signal passes through and the voltage present at the signal input will change the voltage on C16 accordingly. If Q2 is gated off the last voltage on C16 is held, since leakage is kept low by buffering it with a voltage follower based on IC5b. By sampling the input for only very short durations, the voltage on C16, available at R27, will be a series of discrete steps which may in turn be used to control voltage controlled modules. The negative to positive voltage transition for gating Q2 on for sampling is obtained with IC4 configured as a comparator. With a near zero voltage at the non-inverting input of IC4 its output will be close to the negative rail voltage of -15 V and Q2 will be off. When a positive pulse is applied to the non-inverting input then IC4 goes positive (about +13 V) and turns on Q2 so that a sample of the signal voltage can be taken and stored on C16. The internal clock used to turn Q2 on and off via IC4 is based on CMOS 555 timer, IC2. The pin configuration and operational features are the same as a bipolar 555 but the CMOS version has advantages in terms of power consumption and absence of crowbarbing the power supply during the output transition. A conventional astable configuration is used and, while D1 allows a wide range of duty cycle, the main adjustment for the latter is the application of a positive voltage to its control voltage input, pin 5, via PR2. The output of the timer is buffered by IC3 so that it may be used for external synchronisation purposes. The output also goes via an SPDT switch, SW1, to comparator IC4. The switch allows external clock sources to be used.

PROJECT : Noise Generator


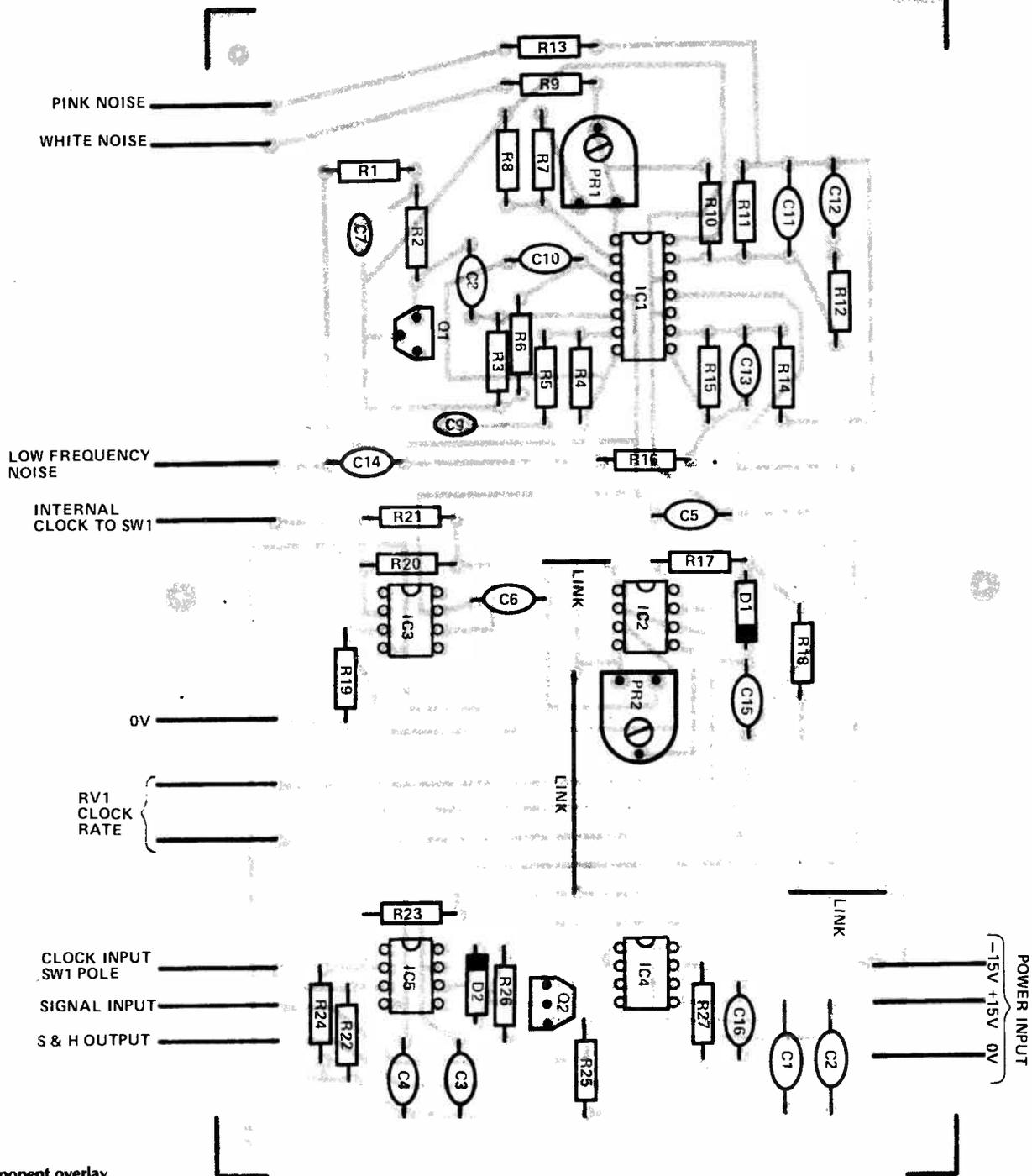
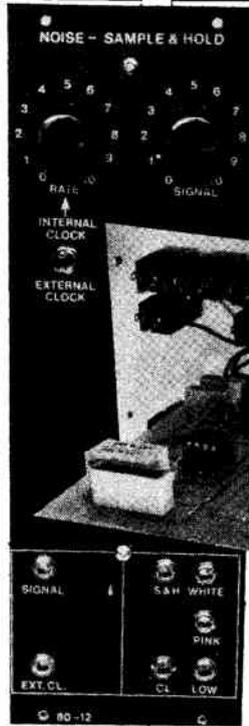


Fig.2 Component overlay


PARTS LIST

Resistors ¼ W 5% carbon	Capacitors		PR1	100k carbon
R1,18	C1,2	470n polyester	PR2	470k carbon
R2,6,15,19,22,23,25	C3,4,5,6,13	100n polyester	Semiconductors	
R3,4,26	C7,9	22µ 25V PCB electrolytic	IC1	LM348N
R5	C8	470n MKH polyester	IC2	ICM7555 IPA
R7,8,9,13,16,27	C10,14,15	1µ0 MKH polyester	IC3,4	CA3140E
R10	C11	2n2 polystyrene	IC5	TL082 CP
R11	C12	22n polycarbonate	D1, 2	1N4148
R12	C16	220n MKH polyester	Q1	BC548
R14			Q2	2N3819
R17	Potentiometers/Trimmers		Miscellaneous	
R20	RV1	4M7 linear	SW1	5PDT miniature toggle
R21,24	RV2	100k linear	Transistor holder	

PROJECT : Noise Generator

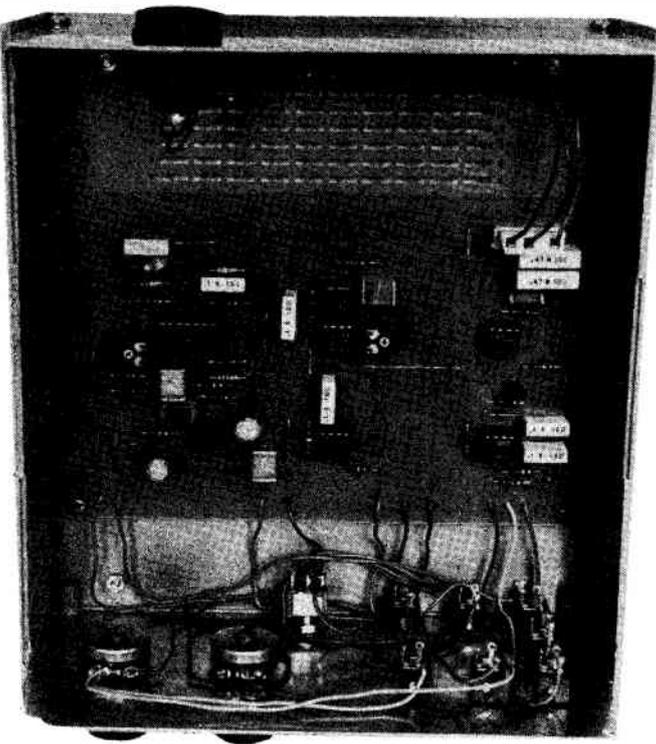

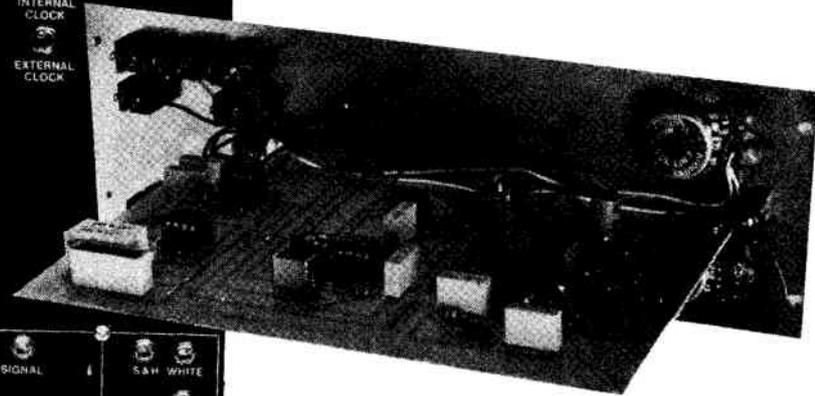Each Project 80 module can be housed in a West Hyde Developments' Teko Alba A23G case (far left) or on a front panel only (left).




All the modules can be mounted on front panels (above) and cased together in one cabinet.

BUYLINES

The 80-12 Noise Generator — Sample & Hold module is available as a kit with PCB and all listed components for £13.17, inclusive of postage and VAT, from Digisound Limited, 13 The Brooklands, Wrea Green, Preston, Lancs. PR4 2NQ.

ETI

The 2001 sweeps the board at only £78*

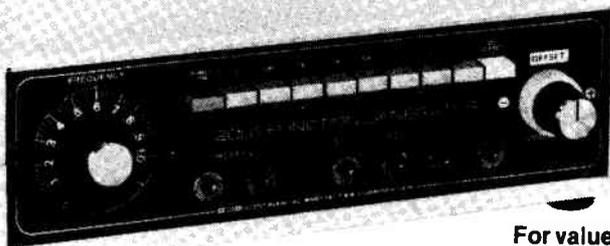

Get all the waveforms you need — 1 Hz to 1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and low-level main outputs.

An applied DC Voltage at the Sweep input can shift the 2001's frequency; or sweep up to 100:1 with an AC signal. A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

For value for money the 2001 sweeps the rest off the board.

For immediate action — The G.S.C. 24 hour, 5 day a week service Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately or just clip out the coupon.

*price excluding P&P and 15% VAT

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited
Dept. 9HH Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex 817477

Global Specialties Corporation (UK) Limited
Dept 9HH Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 2001 Sweepable
Function Generator

£91.43 (inc. P&P
and 15% VAT)

Qty
Reqd.

For FREE catalogue
tick box

Name Address

I enclose PO/Cheque for £..... or debit my
Barclaycard/Access/American Express No exp date

SUBSCRIPTIONS

This year we present a new twelve-part, non-fiction series — ETI 1981 available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £11.00 we'll send you twelve issues of ETI.

To claim your year's supply of ETI, send your PO or cheque direct to :

ETI Subscriptions,
Modmags Ltd,
145 Charing Cross Road,
London WC2H 0EE



**It's easy
to complain
about
advertisements.**

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.
A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

MIGHTY NINETY PACKS

**SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 15p PER PACK UP TO FOUR PACKS
FIVE OR MORE POST FREE
BUY SIX PACKS AND GET A SEVENTH PACK FREE!**

- | | |
|---|--|
| <p>MN1. 300 ¼-watt Resistors pre-formed for P&C Mtg.
MN2. 200 ¼ & ½-watt Resistors.
MN3. 100 1 & 2-watt Resistors.
MN4. 50 Wirewound Resistors.
MN5. 100 metal oxide Resistors. 1%, 2% and 5%.
MN6. 12 asstd. potentiometers.
MN7. 25 asstd. skeleton pre-set Resistors.
MN8. 50 asstd. Electrolytic Capacitors.
MN9. 100 asstd. Ceramic Capacitors. Pte, disc, tub and monolithic etc.
MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.
MN11. 20 asstd. Silver Mica Capacitors.
MN12. 8 Tantalum Bead Capacitors (useful values).
MN13. 20 asstd. Transistors, BC, 2N Series + Power etc.
MN14. 40 IN4148 Diodes.
MN15. 5 Light Sensitive Devices.
MN16. 20 min. wire-ended Neons.
MN17. 2 12-volt Relays. Ex nearly new equip.
MN18. 3 Encapsulated Reed Relays. 9-12v. coil, d.-pole and t.-pole.
MN19. 2 24-volt Relays. Ex nearly new equip.
MN20. 1 240-110 to 12-volt, 100ma Transformer.
MN21. 1 240-110 to 24-volt 100ma Transformer.
MN22. B .2" Led s with clips, 4 red, 2 yellow, 2 green.</p> | <p>MN23. 116 asstd. screws, nuts, washers, self-tappers etc.
MN24. 100 asstd. small springs.
MN25. 50 asstd. pop rivets.
MN26. 50 asstd. insulated crimps.
MN27. 200 items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.
MN28. 20 asstd. fuses. 1¼" 20mm etc.
MN29. 75mts equipment, wire, asstd. colours and sizes.
MN30. 3 x 2m length. 3 core, mains cable.
MN31. 12 asstd. trimmer capacitors. Compression film. Air-spaced etc.
MN32. 15 30pF Beehive trimmers.
MN33. 20 coil formers, ceramic, plastic, reed relay etc.
MN34. 25 min. glass reed switch.
MN35. 10 asstd. switches, toggle, slide, macro etc.
MN36. 10 ex equipment panel lamps (no rubbish).
MN37. 10 asstd. audio connectors. Din phone etc.
MN38. 1 PCB with triac control IC data inc.
MN39. 1 oscillator PCB loads of components. (no data).
MN40. 50 Polystyrene capacitors.
MN41. 10 asstd. T.T.L. I/Cs.
MN42. 10 BC107 Transistors.
MN43. 10 BC108 Transistors.
MN44. 10 Screwfix S.P.C.O. min. slide switches.</p> |
|---|--|

CHORDGATE LTD.

**75 FARINGDON ROAD, SWINDON, WILTS
TEL: SWINDON (0793) 33877**

RETAIL SHOP AT ABOVE ADDRESS

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

L.P. Toroidal

TRANSFORMERS IN A RANGE OF 76 TYPES

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

30VA	70mm dia. x 30mm Weight 0.45 Kg	£4.71 (+£1.20 p.p. + 0.89 VAT)	160VA	110mm dia. x 40mm Weight 1.8 Kg	£8.88 (+£1.80 p.p. + £1.60 VAT)
50VA	80mm dia. x 35mm Weight 0.9 Kg	£5.19 (+£1.30 p.p. + 0.97 VAT)	225VA	110mm dia. x 45mm Weight 2.2 Kg	£10.59 (+£1.90 p.p. + £1.87 VAT)
80VA	90mm dia. x 30mm Weight 1 Kg	£5.76 (+£1.50 p.p. + £1.09 VAT)	300VA	110mm dia. x 50mm Weight 2.6 Kg	£12.27 (+£2.00 p.p. + £2.14 VAT)
120VA	90mm dia. x 40mm Weight 1.2 Kg	£6.72 (+£1.60 p.p. + £1.25 VAT)	500VA	140mm dia. x 60mm Weight 4 Kg	£16.35 (£2.10 p.p. + £2.77 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.90	5X012	12+12	6.66
1X011	9+9	1.66	5X013	15+15	5.33
1X012	12+12	1.25	5X014	18+18	4.44
1X013	15+15	1.00	5X015	22+22	3.63
1X014	18+18	0.83	5X016	25+25	3.20
1X015	22+22	0.68	5X017	30+30	2.66
1X016	25+25	0.60	5X018	35+35	2.28
1X017	30+30	0.50	5X028	110	1.45
2X010	6+6	4.16	5X029	220	0.72
2X011	9+9	2.77	5X030	240	0.66
2X012	12+12	2.08	6X014	18+18	6.25
2X013	15+15	1.66	6X015	22+22	5.11
2X014	18+18	1.38	6X016	25+25	4.50
2X015	22+22	1.13	6X017	30+30	3.75
2X016	25+25	1.00	6X018	35+35	3.21
2X017	30+30	0.83	6X026	40+40	2.81
2X028	110	0.83	6X028	110	2.04
2X029	220	0.45	6X029	220	1.02
2X030	240	0.20	6X030	240	0.93
3X010	6+6	6.64	7X016	25+25	6.00
3X011	9+9	4.44	7X017	30+30	5.00
3X012	12+12	3.33	7X018	35+35	4.28
3X013	15+15	2.66	7X026	40+40	3.75
3X014	18+18	2.22	7X025	45+45	3.33
3X015	22+22	1.81	7X028	110	2.72
3X016	25+25	1.60	7X029	220	1.36
3X017	30+30	1.33	7X030	240	1.25
3X028	110	0.72			
3X029	220	0.36			
3X030	240	0.33			
4X010	6+6	10.00	8X017	30+30	8.33
4X011	9+9	6.66	8X018	35+35	7.14
4X012	12+12	5.00	8X026	40+40	6.25
4X013	15+15	4.00	8X025	45+45	5.55
4X014	18+18	3.33	8X033	50+50	5.00
4X015	22+22	2.72	8X028	110	4.54
4X016	25+25	2.40	8X029	220	2.27
4X017	30+30	2.00	8X030	240	2.08
4X028	110	1.09			
4X029	220	0.54			
4X030	240	0.50			

• I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

• CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility. (U.K. only).

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.



L.P. TRANSFORMERS

A division of I.L.P. ELECTRONICS LTD.

FREEPOST T4 GRAHAM BELL HOUSE ROPER CLOSE

CANTERBURY CT2 1EP

Phone (0227) 54778 Technical (0227) 64723 Telex 96S 780

DIGITAL 24 HOUR CLOCK

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS

AS USED IN BRAUN DIGITAL CLOCKS

MECHANISM WITH ALARM £5.00
MECHANISM & CASE £6.99
Inc. assembly instructions

Assemble it in an evening!

THREE FOR £13.50 | MECHANISMS 10 FOR £39. 100 FOR £300

• AC MAINS
• SIZE 6 3/4 x 2 3/4
Your receipt is a 2-year guarantee

HALF PRICE OFFER

HENRY'S Radio

HENRY'S RADIO
404 EDGWARE ROAD,
LONDON W2 1ED 01-723 1006

EXPORT ENQUIRIES INVITED

DELIVERY FROM STOCK

THE ZX80 MAGIC BOOK £4.75

20 plus programs including one which allows you to make music with your ZX80, and games such as Moon Lander, Hammurabi, Othello and Hexpawn. Also sections on How it Works, Plotting, Using USB, Converting Programs Written in Other BASICS, and hardware notes including circuits for static and dynamic RAM and I/O.

THE ATOM MAGIC BOOK £5.50

Programs to run on your ATOM, including Brickout, Hexpawn, Othello and Space Battle. Also Programming Tips and Hardware Notes.

ASCII CODED KEYBOARD £35 inc. VAT & 9p

Brand new, assembled and tested. 60 keys in stepped rows. Auto repeat. S.a.e. for details.

ALL PRICES INCLUDE UK DELIVERY & VAT

TIMEDATA LTD.

57 Swallowdale, Basildon, Essex



Wilmslow Audio

THE firm for speakers!

SEND 50P FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC, AND DISCOUNT PRICE LIST.

AUDAX - AUDIOMASTER - BAKER - BOWERS & WILKINS
CASTLE - CELESTION - CHARTWELL - COLES - DALESFORD
DECCA - EAGLE - ELAC - EMI - FANE - GAUSS - GOODMAN'S
HARBETH - ISOPHON - I.M.F. - JORDON - JORDAN WATTS
KEF - LOWTHER - MCKENZIE - MISSION - MONITOR AUDIO
MOTOROLA - PEERLESS - RADFORD - RAM - ROGERS
RICHARD ALLAN - SEAS - SHACKMAN - STAG - TANNON
VIDEOTONE - WHARFEDALE.

WILMSLOW AUDIO

35/39 CHURCH STREET
WILMSLOW, CHESHIRE SK9 1AS

Tel. 0625-529599 FOR MAIL ORDER AND EXPORT OF DRIVE UNITS, KITS, ETC.

Tel. 0625-526213 SWIFT OF WILMSLOW)
5 SWAN STREET, WILMSLOW, CHESHIRE SK9 1HF)
FOR HI-FI AND COMPLETE SPEAKERS

DESIGNER'S NOTEBOOK

Certain elementary safety precautions must be taken when handling CMOS ICs or designing CMOS circuits. Ray Marston explains all in this month's 'Notebook'.

Early CMOS ICs earned a reputation for being easily damaged by static electricity, either when being handled or when being soldered into circuit boards, etc. Subsequently, manufacturers tried to overcome this 'fragility' problem by providing the ICs with extensive built-in input and output protection on each gate in each package. These protection networks do a fairly satisfactory job, but provide the design engineer with a few extra problems when designing CMOS circuits. This month's Notebook takes an in-depth look at the subject.

CMOS Protection Networks

CMOS ICs are, by definition, Metal-Oxide Semiconductor devices, in which the input signal is applied to the near-infinite impedance (about 10^{12} ohms) of the metal-oxide gate. Typically, the gate oxide has a breakdown voltage of about 80 V: if a gate oxide break-down does occur, the resultant damage to the device is catastrophic and irreversible. To protect the CMOS against excessive input voltages (particularly arising from static energy), all modern CMOS ICs are provided with extensive built-in protection on all inputs and outputs.

Figure 1 shows the standard protection network that is used on the vast majority of B-series CMOS devices. Here, all diodes marked as 'D1' are used to prevent the input or output from swinging more than 600 mV below the V_{SS} (0 V) rail, and all diodes marked as 'D2' are used to prevent the input or output from swinging more than 600 mV above the V_{DD} (supply positive) rail. D3 is intended to prevent the V_{DD} terminal from swinging negative to the V_{SS} pin (electrostatically) when the device is being handled.

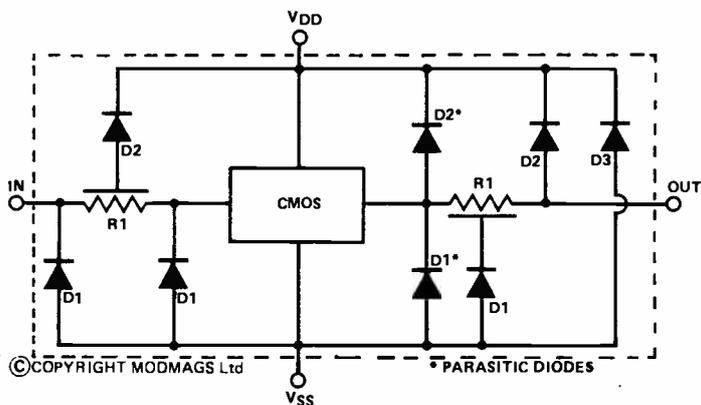


Fig. 1 These are the standard electrostatic-discharge protection networks used on most B-series CMOS ICs. The two diodes associated with the resistors are distributed across the entire resistance, as shown.

There are a couple of minor exceptions to the standard version of the protection network. One of these is the type used on the 4049B and 4050B series of hex buffer/converters which, as shown in Fig. 2, have their inputs free to swing well above the V_{DD} rail. These particular ICs are specifically intended for use in logic-level conversion applications, in which (for example) the input may come from a 12 V CMOS network but the output and the IC supply rail are matched to a 5 V TTL network.

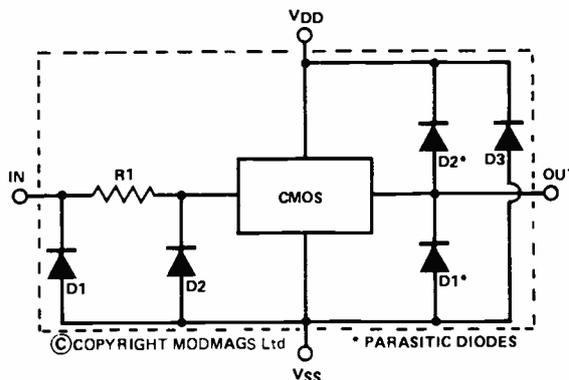


Fig. 2 This protection network is used on the 4049B and 4050B hex buffers. Note that the input is free to swing above the positive supply (V_{DD}) rail.

Another exception is the 4066B type of transmission gate or bilateral switch, and its equivalents. These devices comprise a bilateral electronic switch and a switch-control network. In these circuits, all switch-control networks have the type of input protection shown in Fig. 1, but the switches themselves have the simple protection network shown in Fig. 3.

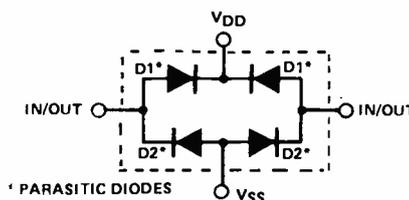


Fig. 3 The 4066B quad bilateral switch has standard B-series protection on its gate control input terminals, but has this simplified form of protection on its 'switch' elements.

Note in Figs. 1-3 that all diodes marked with asterisks are 'parasitic' devices, which just happen to occur fortuitously as an inherent part of the CMOS manufacturing process, while all other diodes are specifically designed into the circuits. Also note that the networks are intended only to give protection

against 'normal' electrostatic discharge voltages. When the networks are subjected to ordinary DC signals, the diodes are liable to burn out if their forward currents exceed 10 mA or so, thereby causing possible catastrophic damage to the IC substrate.

Major CMOS manufacturers such as RCA reckon that an electrostatically charged human body can be approximated by the circuit of Fig. 4, in which the 'body' has an effective capacitance of 100pF and a source resistance of 560R. The manufacturers have carried out extensive tests with this model by charging the 'body' to various voltages and then discharging it (via the 560R series resistor) into different terminal combinations (input, output, V_{SS} , V_{DD}) of CMOS devices to establish worst-case capability figures for the three types of electrostatic-discharge protection networks. It should be noted in these tests that the 560R series resistor acts as a current-limiting voltage dropper, so the voltage actually reaching the CMOS device is far lower than the initial electrostatic voltage.

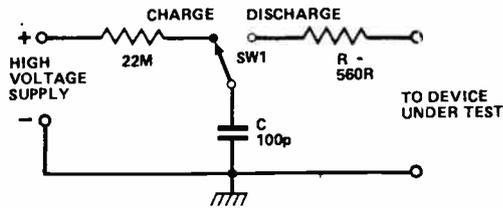


Fig. 4 Manufacturers use this equivalent-body discharge network when evaluating the capabilities of their CMOS protection networks.

The results of the manufacturer's protection capability tests are shown in Fig. 5. As you can see, the standard protection network can withstand a 4 kV electrostatic discharge. A quick calculation shows, however, that this represents a peak protection-diode current of several amps, yet we've already seen that these diodes can withstand DC currents of only 10 mA or so. Puzzled?

PROTECTION NETWORK	WORST - CASE CAPABILITY
STANDARD B-SERIES 4049B AND 4050B 4066B BILATERAL SWITCH	4 kV 1 kV TO 2 kV < 800 V

© COPYRIGHT MODMAGS Ltd

Fig. 5 These are the worst-case capabilities of the three different CMOS protection networks, when tested with the network of Fig. 4.

Up The Junction

Just about the only way of destroying a diode is to literally vaporise its junction, and this can only be done by applying an adequate amount of power for sufficient time for the melting process to take place. Since a junction must inevitably be formed on a substrate, which has a finite mass, all junctions inevitably have a certain amount of thermal inertia and are, in fact, destroyed by energy overloads (power-time product), rather than by simple power overloads.

Consequently, it is quite normal to find that a diode rated at 1 A (for example) can, in fact, withstand brief current surges up to several hundred amps. Similarly, CMOS protection diodes, which have very low DC current ratings (10 mA), can withstand very high levels of surge current (several amps), provided that the surge current duration is very brief. Figure 6 shows the typical surge current capabilities of these protection diodes. Remembering that the 100p — 560R 'human body' equivalent circuit has a time constant of a mere 56 nS, it no longer comes as a surprise to note that these diodes can withstand several amps of peak current from a 4 kV discharge!


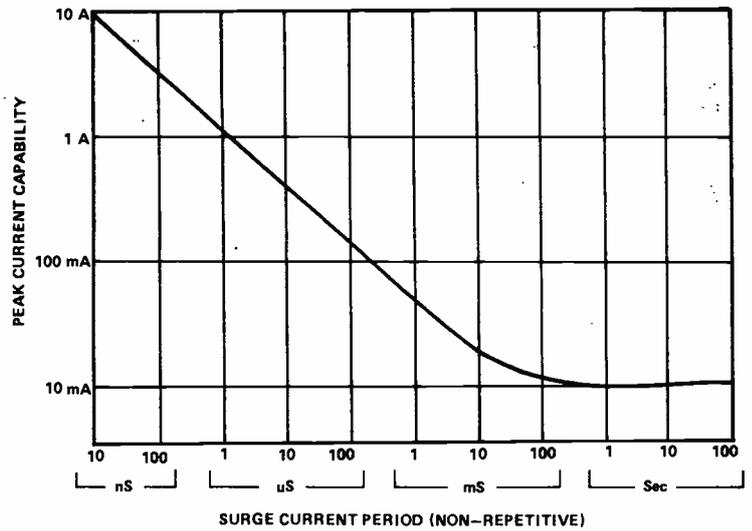


Fig. 6 Typical surge-current capabilities of CMOS protection diodes.

CMOS Circuit Design

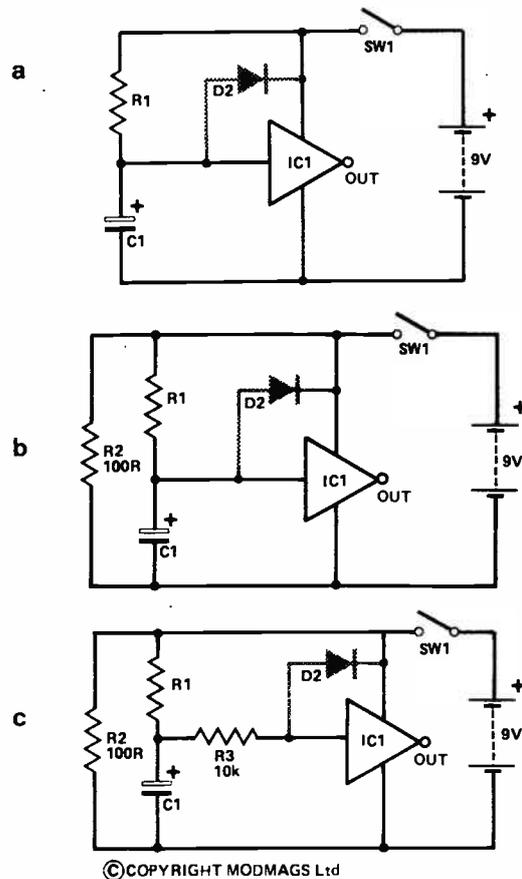By now you will have gathered that you can effectively destroy a CMOS device by simply blowing one or more of its 'protection' diodes with a DC current as low as 10 mA. Consequently, when designing CMOS circuits, precautions must be taken to ensure that excessive diode current cannot flow in the CMOS chips.



© COPYRIGHT MODMAGS Ltd

Fig. 7 Circuits (a) and (c) are safe, but circuit (b) will almost certainly cause a front-end 'blow'. See text for explanation.

CMOS ICs can be 'blown' by excessive signals applied to either the input or the output terminals. If several CMOS stages are cascaded, empirical experience shows that a front-end blow will usually destroy only a single device (because low energy levels are normally involved), but a rear-end (output) 'blow' will often have a ripple effect (because high energy levels are involved) and cause the destruction of all ICs in the chain.

The most common cause of front-end 'blow', and its cure, are illustrated in Fig. 7. Here, a capacitor is connected directly between the IC gate and the 0 V line: when SW1 is closed, the capacitor charges up via R1 and eventually attains the full positive supply potential. When SW1 is opened (to switch the circuit off), C1 tries to discharge via D2, the 'upper' input protection diode of the gate.

In the Fig. 7a circuit, the only discharge path for C1 is via D2 and the IC's supply terminals; consequently the discharge currents will be quite low and the IC will probably suffer no damage. In Fig. 7b, on the other hand, a 100R resistor is connected across the supply terminals, so C1 will try to discharge to ground via D2 and R2, and the resulting 90 mA peak current will almost certainly result in the destruction of the chip. In practice, R2 may well take the form of various resistors and semiconductor devices distributed throughout the total circuit.

Figure 7c shows the cure for the Fig. 7b design problem, a 10k resistor wired in series with the gate to limit the C1 discharge currents to a safe value. Whenever you design CMOS circuits and have to connect a capacitor between a gate and the 0 V rail, always make sure that the capacitor discharge current is limited to a safe value, either by a series gate resistor or by some other factor.

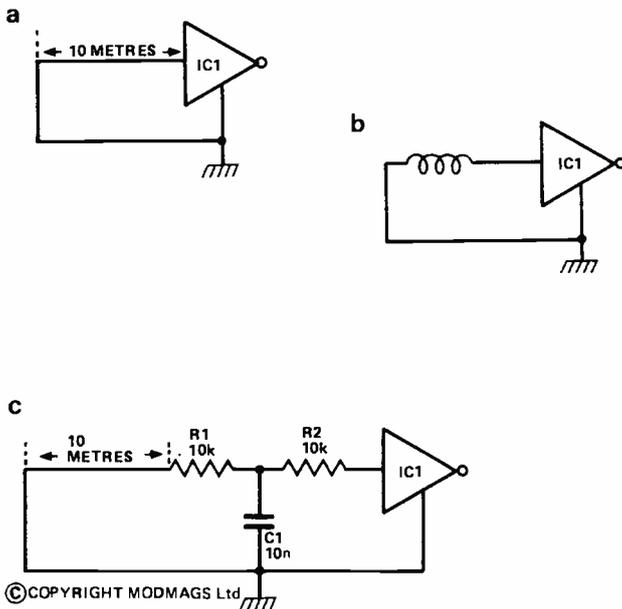


Fig. 8 Long input cables, as in (a), can be equivalent to an inductor (b), and present another front-end blowing hazard. The cure is simple (c).

Figure 8 illustrates another possible cause of front-end 'blowing', and its cure. In Fig. 8a, it seems that the IC's input is safely grounded by the 10 m of input cable (in practice, this cable may go to a low impedance sensor, etc), but in actual fact (Fig. 8b) this cable will inevitably be inductive and can easily pick up unwanted radiation and possibly feed destructive signals to the IC input. Figure 8c shows that the circuit can be rendered safe with a simple filter (R1-C1) and a series gate resistor (R2).

Back-end Blowing

The most common cause of back-end blowing is unexpected back-EMFs (from inductive loads) reaching the CMOS output by breaking through from power-driving circuitry.

Inductive loads, such as relays, can generate surprisingly large back EMFs as their fields collapse at switch-off, as can be proved by connecting a relay in the 'buzzer' mode shown in Fig. 9. Typically, a 12 V relay will generate a back-EMF of about 300 V! If you ever use CMOS to switch a relay or other highly inductive load using a transistor driver, always protect the transistor with a pair of 1N4001 diodes connected as shown in Fig. 10a. If you want to be really safe, you can use another pair of similarly-connected diodes to directly protect the output of the CMOS stage, as shown in Fig. 10b.

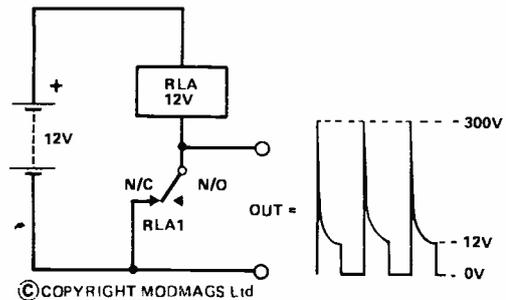


Fig. 9 This 'buzzer' circuit can be used to check the magnitude of the back-EMF from a relay. 300 V is typical!

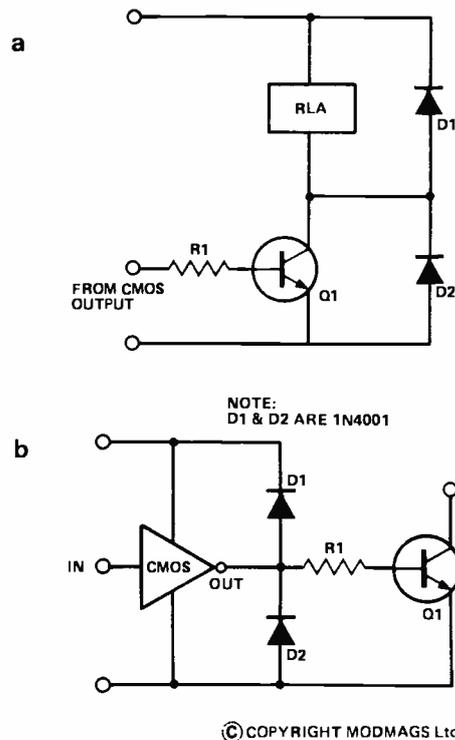


Fig. 10 (a) A transistor relay-driver can be protected with a pair of diodes. (b) The output of a CMOS stage can be given added protection with a similar arrangement.

ETI

DORAM

DORAM ELECTRONICS LTD

Fitzroy House, Market Place,
Swaffham, Norfolk, PE37 7QH.

TEL:(0760) 21627 TELEX: 817912

VAT Reg: 324 5604 75

PROJECT PACKS

Projects for beginners

LCD Converter (80117) Simple to construct display for FM and AM Bands	£41.20
Pools predictor (79053) An analogue computer that may win you a fortune	£8.15
Talk Funny (80052) A ring modulator circuit that produces very strange results when fed with a human voice	£9.60
Pest Pester (80130) An electronic insect repellent	£2.35
Steam train sound effects (80019) Simulates the sound of steam and whistle	£6.50
Electronic Nuisance (80016) Makes an annoying noise, but only in the dark!	£3.85
Cackling Eggtimer (9985) An eggtimer with a difference, it clucks like a hen	£7.20

New projects

200w Disco Power Amplifier (81082)	£20.85
Swinging Poster (81073) Animated poster	£15.20
Minimixer (81068) High quality 5 channel stereo mixer	£37.50
Process Timer (81101) Photographic darkroom timer	£18.20
High Com (81117-1) Telefunken noise reduction system	£49.55

Audio projects

Top-preamp (80031) Mini, all IC preamplifier for use with most power amplifiers	£34.40
Topamp (80031) Hybrid audio power amplifier uses Philips modules for high fidelity performance. Two power levels: OM931 (output 30 watt)	£18.50
OM961 (output 60 watt)	£33.40
Parametric Equalizer (9897) A modular system of construction to suit your equalisation requirements. Filter section (9897-1)	£6.45
Tone section (9897-2)	£5.20

Elektornado (9897) A single board design that can be used as either a single 100 Watt amplifier or two 50 Watt amplifiers

UAA180 LED meter (9817) A two channel voltage display unit	£19.50
Peak Programme Meter (9860) To be used with UAA180 LED meter to give PPM display	£13.00
Audio Analyser (9932) An analyser that can pinpoint the deficiencies in an audio chain	£3.70
Stereo dynamic Preamp (80532) A low noise high quality disc preamplifier	£14.80
STAMP (80543) Super tiny amplifier up to 1 Watt output	£5.20
Melody Maker (80502) An electronic musical box that can play up to 27 tunes	£3.75
	£23.50

Car projects

Car Battery Charger (79517) Reliable and safe charger for all types of lead-acid batteries	£21.70
Transistor Ignition (80082) The most significant advantages of other systems combined in one	£20.45
Dipstick Probe (80102) Direct warning of high oil temperature. State long or short dipstick required	£11.25
Intelligent Wiper Delay (80086) Can be set to produce delayed wipes at any predetermined interval	£15.85
Battery Protection (80109) Automatically switches off the headlamps of a parked car	£5.15
Battery Voltage Indicator (80101) LEDs indicate the condition of your battery	£6.85
Active Car Aerial (80081) Improves the sensitivity of AM and FM radio reception in your car	£13.85

Music projects

Chorosynth (80060) A cheap mini synthesizer. Send for details	£57.90
Elektor Vocoder (80060) The first Vocoder designed to be built in kit form. 10 Channel modular construction	£162.50
Analogue Reverberation Unit (9973) Uses a SAD 1024 which can produce a delay up to 100mS	£27.70
Guitar Preamp (77020) With three tone controls	£6.50

Projects for the home

Touch Dimmer (78065) Room lighting controlled by a single touch	£6.80
Programmable Slide Fader (81002) Mixes audio signals on tape with operation of two slide projectors	£46.50
Fridge Alarm (81024) Audible warning if fridge door is left open	£5.55
Loudspeaking telephone amplifier (9987) Amplifies without direct connection	£11.50
Proximity Detector (9974) Detects by electric field change movement in a room	£9.80

Our Project Packs include the electronic components, the PCB, sockets and solder together with assembly instructions. Cases, knobs etc can be supplied as extra items if required. This is only part of our wide range of projects. See our catalogue for details of other projects that we can supply. You can also ring our number between 12.30 and 1.30 p.m. any weekday for a recorded announcement of any new items we have available.

HOW TO ORDER


Send a cheque or postal order to DORAM ELECTRONICS LTD or write or ring with your Access account number. All our prices include VAT. Overseas customers please deduct 15%. Please add 40p to your order for postage and packing. An answering service is available to take your orders outside our normal office hours. Mail Order service only.

a de boer company



NAME _____

ADDRESS _____
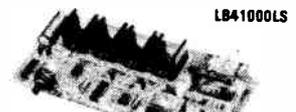
<p>3 CHANNEL SOUND/LIGHT CHASER LB31000SLC £32.70</p>  <p>A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.</p>	<p>STEREO DISCO MIXER/PREAMP LBPA3 M - Magnetic C - Ceramic £33.70</p>  <p>Magnetic or ceramic deck versions - please state</p> <p>All the requirements of a stereo disco preamp on one board, left and right deck mixer/tone controls/mic. mixer/tones/mic. auto fade over decks and P.F.L. The unit can be used with either LB100/150/250</p> <p>Full set of pots - £8.83</p>												
<p>3 CHANNEL SOUND/LIGHT LB31000SL £22.70</p>  <p>All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.</p>	<p>LBPA2 £17.20 A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots £2.74.</p> <p>LBPA1 £19.50 A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots £3.27.</p>												
<p>2/4/8 CHANNEL CHASER LB81000LC £28.00</p>  <p>An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and modula cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.</p>	<p>3-WAY ACTIVE CROSSOVER LBAC01 £17.90</p>  <p>Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01 (1 or 2).</p>												
<p>4 CHANNEL SEQUENCER LB41000LS £19.20</p>  <p>A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.</p>	<p>POWER AMPLIFIERS</p> <p>Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatinks and rugged a/p devices fail operate down to 4 ohms.</p> <table border="1"> <tr> <th>20W R.M.S.</th> <th>100W R.M.S.</th> <th>100W R.M.S.</th> <th>250W R.M.S.</th> </tr> <tr> <td>20Hz to 80K 0.07% THD 980B S/N LB25</td> <td>5Hz to 25K 0.1% THD 1100B S/N LB70</td> <td>5Hz to 25K 0.1% THD 1100B S/N LB100</td> <td>5Hz to 25K 0.1% THD 1100B S/N LB250</td> </tr> <tr> <td>£11.20</td> <td>£19.70</td> <td>£29.20</td> <td>£43.50</td> </tr> </table> <p>Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.</p>	20W R.M.S.	100W R.M.S.	100W R.M.S.	250W R.M.S.	20Hz to 80K 0.07% THD 980B S/N LB25	5Hz to 25K 0.1% THD 1100B S/N LB70	5Hz to 25K 0.1% THD 1100B S/N LB100	5Hz to 25K 0.1% THD 1100B S/N LB250	£11.20	£19.70	£29.20	£43.50
20W R.M.S.	100W R.M.S.	100W R.M.S.	250W R.M.S.										
20Hz to 80K 0.07% THD 980B S/N LB25	5Hz to 25K 0.1% THD 1100B S/N LB70	5Hz to 25K 0.1% THD 1100B S/N LB100	5Hz to 25K 0.1% THD 1100B S/N LB250										
£11.20	£19.70	£29.20	£43.50										
<p>1 AND 3 CHANNEL DIMMERS LB31000LD £16.20</p>  <p>Single channel version LB11000LD £7.20</p> <p>Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders - LB31000LD (no pots) £15.00 Sliders 75p each.</p>	<p>LBRLD1 £6.20</p>  <p>A de-thump unit for use with any LB power amps.</p>												
<p>ROPE LIGHTS/DRIVER LB41000LC-S £24.20</p>  <p>24 feet ropes Red/Yellow Blue/Green</p> <p>ROPE LIGHTS £45.40</p> <p>A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control.</p>	<p>POWER AMP POWER SUPPLIES</p> <table border="1"> <tr> <th>LB26PS</th> <th>LB106PS</th> <th>LB156PS</th> <th>LB256PS</th> </tr> <tr> <td>£11.20 P/P £1.20</td> <td>£16.20 P/P £1.40</td> <td>£19.00 P/P £1.40</td> <td>£26.50 P/P £1.70</td> </tr> </table> <p>FOR GUITAR, P.A. AND DISCO</p> <p>PIEZO HORNS £5.75 P/P 50p</p> 	LB26PS	LB106PS	LB156PS	LB256PS	£11.20 P/P £1.20	£16.20 P/P £1.40	£19.00 P/P £1.40	£26.50 P/P £1.70				
LB26PS	LB106PS	LB156PS	LB256PS										
£11.20 P/P £1.20	£16.20 P/P £1.40	£19.00 P/P £1.40	£26.50 P/P £1.70										
<p>CELESTION LOUSPEAKERS (All standard cone 8 ohms)</p> <table border="1"> <tr> <th>B12-65 (12 inch 85W)</th> <th>G12-100 (12 inch 100W)</th> <th>G10-50 (10 inch 50W)</th> </tr> <tr> <td>£20.70 P/P £1.70</td> <td>£26.45 P/P £1.70</td> <td>£14.70 P/P £1.70</td> </tr> </table> <p>NEW - MINI MODULES - NEW</p> <p>Ingeniously designed mini pre-amplifier 'building blocks' for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.</p> <p>LBMM1 Pre-amp for mics, guitars etc. LBMM2 Mixer for up to 8 LBMM1/2/3/4/5 LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5 LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5 LBMM5 Treble boost/cut for either LBMM1/2/3/4/5 LBPSU1 ± 15V supply for up to 12 modules LBPSU ± 15V regulated for up to 50 modules</p> <p>MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £5.70; PSU1 £7.20; RPSU £14.50.</p> <p>Mini Module Discount: Any types between 10 and 24 (quantity) - 20%. 25+ - 30%</p>	B12-65 (12 inch 85W)	G12-100 (12 inch 100W)	G10-50 (10 inch 50W)	£20.70 P/P £1.70	£26.45 P/P £1.70	£14.70 P/P £1.70	<p>Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.</p> <p>All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order, send cheque/P.O./registered cash or Access number. C.O.D. service £1 extra. For the new Autumn catalogue send 50p (Full spec. shown).</p> <p>Please note: This company has no connection with LB Electronics of Hillingdon.</p>						
B12-65 (12 inch 85W)	G12-100 (12 inch 100W)	G10-50 (10 inch 50W)											
£20.70 P/P £1.70	£26.45 P/P £1.70	£14.70 P/P £1.70											
<p>L & B ELECTRONIC MODULES PROFESSIONAL ENGINEERING BY PROFESSIONALS 45 Wortley Road, West Croydon, Surrey CR0 3EB. Tel. 01-689 4138</p>	<p>POWER AMPLIFIERS</p> <p>Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatinks and rugged a/p devices fail operate down to 4 ohms.</p>												

NEW

TRS 80 MODEL III



The Model III has arrived in the U.K.
★ **NEW FEATURES AVAILABLE** ★

- ★ Upper and Lower Case characters (standard)
- ★ Real Time Clock
- ★ 500 or 1500 Band Cassette
- ★ Parallel Printer Interface (standard)
- ★ Auto Repeat keys
- ★ Flashing Cursor
- ★ New Characters, Greek, Japanese Kana
- ★ Numeric Keypad
- ★ 16, 32 or 48K
- ★ Room for two D.D. Disc Drives & Interface
- ★ 12" VDU

★ All in stylish cabinet.

16K £649 INCLUSIVE

S.a.e. Enquiries. Delivery 4-6 weeks

N.I.C.
Unit 5 61 Broad Lane, London N15
Daytime: 808 0377; evenings: 889 9736

QUESTION?

1. Is your hobby home computing or electronics?
2. Do you understand the application of IC's, Transistors, Diodes, etc?
3. Have you used or applied analogue or digital techniques?
4. Are you applying TTL Logic to your home computer?
5. Are you programming your home computer using simple software techniques?

If the answer is YES to any of these questions then why not consider turning your hobby into a career - applying your knowledge to servicing electronic equipment ranging from basic terminals and data processing machines through to advanced micro-processor systems.


We will train you through to advanced technology at the company training school, fitting the individual in at their own level.

We have vacancies over the whole of the U.K. especially in the London area, with the successful applicants working from home, usually in a radius of no more than 60-70 miles.

We supply all tools and test equipment, plus a company car which is available for private use.

If you are interested, then why not contact **Mr. C. Marklew** on **0249 813771** to discuss your own career opportunities in confidence, or write to:

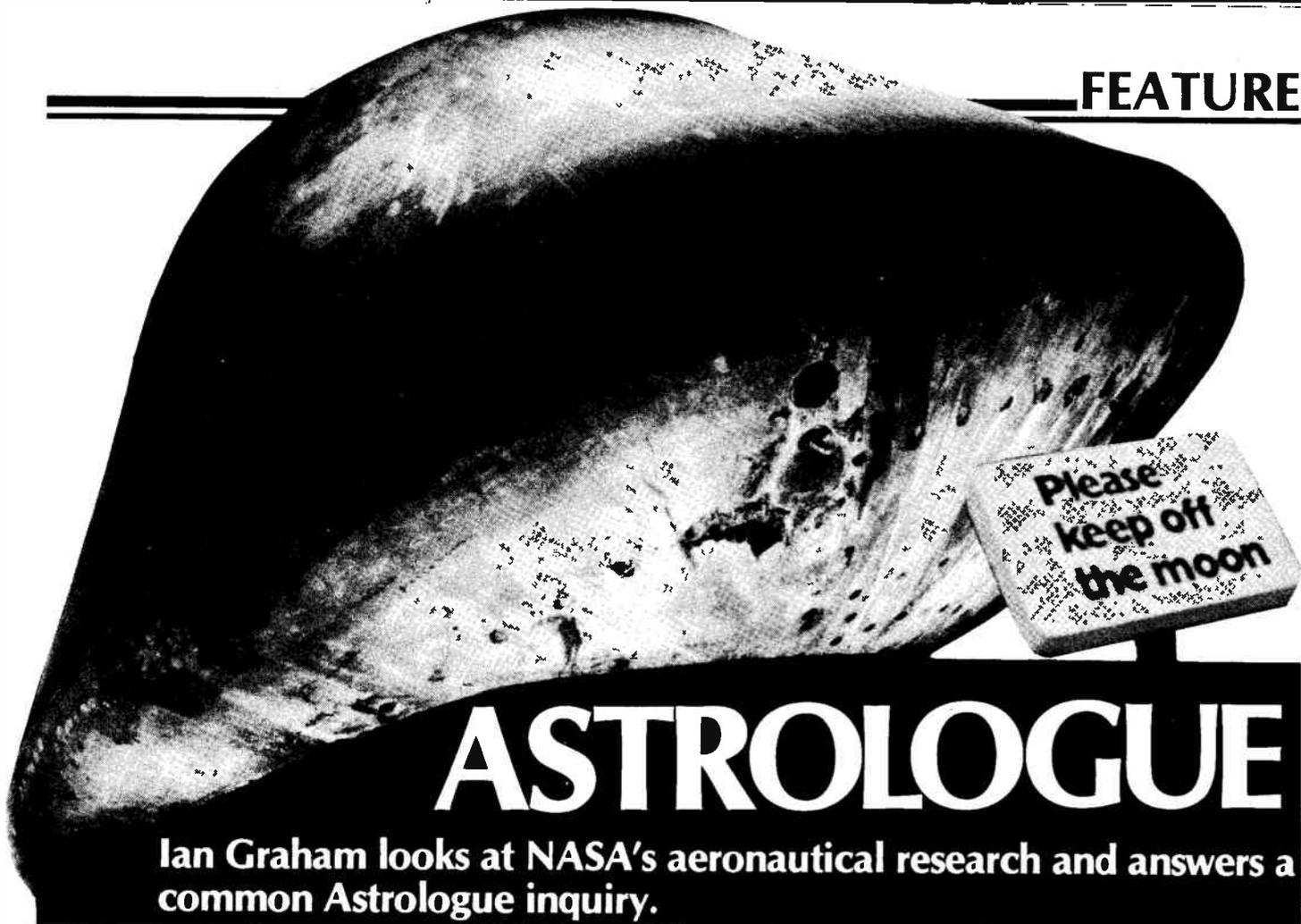KODE SERVICES LIMITED
Station Road, Calne, Wiltshire



ASTROLOGUE

Ian Graham looks at NASA's aeronautical research and answers a common Astrologue inquiry.

Say NASA and most people think of rockets and moonshots. One side of NASA's activities that doesn't hit the headlines is its aeronautical research. The work falls into four categories:

Proof of concept — flying hardware to prove a theory eg the X-series of research aircraft.

Extension of the art — building upon the contemporary state of the art.

Future needs — meeting broad and far-reaching research goals.

Problem solving — trouble-shooting design problems. The research reaches into almost every aspect of aviation — fluid physics, propulsion, materials, structures, electronics and human factors, all of which came together to support the development of safer, environmentally compatible (quieter and pollution-free), fuel-efficient aircraft.

Flying Circus

Testing out the drawing board ideas has brought some weird machinery into existence. The Bell Tilt Rotor Research Aircraft can, as the name implies, tilt its engines vertically and take off like a helicopter. Once off the ground, the rotors tilt forward into the horizontal attitude and, together with the fixed wing, generate lift in the normal way. This programme is aimed at developing more advanced vertical and short take-off and landing aircraft for use in difficult airport areas where long runways and shallow glide paths are impossible. They could also be a regular feature of future 'bus-stop' airports close to city centres.

Pivoting Wings

We naturally expect aircraft to be symmetrical vehicles. The port wing is always swept back at the same angle as the starboard wing. An aircraft with one wing swept forward and one swept back wouldn't fly. Wrong! Several decades ago, NASA's Robert T. Jones tested the idea in a wind tunnel and it worked.

Scepticism and insufficiently advanced technology meant that the aircraft has not been built until now. It even has advantages over conventional first generation supersonic transports, producing a substantially quieter sonic boom. At low speed, the wing is kept at right angles to the fuselage. At high speed, the whole wing pivots up to 60° to reduce drag. In this configuration, the aircraft looks rather like a pair of flying scissors.

HiMAT

Inevitably, NASA is involved in a great deal of military aircraft research. The next generation of fighters must combine very high speeds and manoeuvrability, but remain within the g-forces that a pilot can withstand. To this end NASA has flight tested a scaled down remotely piloted airframe called HiMAT (Highly Manoeuvrable Aircraft Technology). The futuristic airframe is dropped from a modified B-52. The HiMAT pilot stays on the ground and flies the aircraft from the Dryden Flight Research Centre in front of typical fighter cockpit displays. If ground control is lost, an airborne pilot can take over. If both fail, HiMAT automatically flies in circles until control is regained (or its fuel runs out). I hope to look at HiMAT in detail in a future Astrologue.

Windy Caverns

The traditional image of aero research at this level is of a cavernous wind tunnel containing a full-size mock-up of the aircraft. This certainly still goes on, but much more advanced techniques can provide a means of 'flying' the aircraft before it is built. Computer dynamic analysis is still used to predict the behaviour of the new design in flight. A tethered scale model can be 'flown' in a wind tunnel to study the aircraft's behaviour at the limits of its performance. All the data from these studies can be used to program a simulator computer to give crewmen experience in handling the aircraft in potentially dangerous situations before they get off the ground in the real thing. →

Computer analysis, model testing and simulator flights all contribute to the designers' and pilots' understanding of the behaviour of the aircraft in the air. The fourth stage is the acid test — a NASA research pilot must actually strap the strange new machine to his seat and probe the limits of the flight envelope for himself.

Where Can I Get

The most common inquiry I receive in the Astrologue mail is, 'Where can I get slides, posters, photos, etc of astronauts, spacecraft, rockets, the planets ?' I can answer you all by saying Space Frontiers. They will gladly supply sets of slides, postcards, charts, posters, mission badges, T-shirts, video tapes, movies, sound cassettes and replica plaques.

The slide sets cover Mercury, Gemini, Apollo, Skylab, Apollo-Soyuz, Space Shuttle, Mariner, Viking, Pioneers 10 and 11, Voyagers 1 and 2, stars and planets, rockets, storms and weather, space centres, 21st century space colonies and UFOs. They come in everything from five-slide sets at £1.75 to mammoth 80-slide sets at £16. A general set called 'Image of Space' (15 slides), showing an Apollo launch, the Earth from space, Earth-rise over the Moon, Buzz Aldrin on the Moon, UV activity in the Sun, a Skylab spacewalker, etc is available for £5 all inclusive. Quality and presentation are first class.

Science Museum

If you're in London, you can come by a set of Space Frontiers postcards at the Science Museum (nearest tube — South Kensington). 'Men in Space', a six-card set, and 'Man On The Moon', a 12-card set from the Hansen Planetarium in Salt Lake City, are available from the Museum shop.

While you're there it's worth popping into the ground floor 'Exploration' display. The theme is 'the extension of mankind's faculties by artificial means.' This special area is regularly brought up to date. In addition to the third floor space exploration and rocketry display, 'Exploration' features the Apollo 10 Command Module (not a replica — it's the real thing) and a full-size copy of the Apollo 11 Lunar Module.

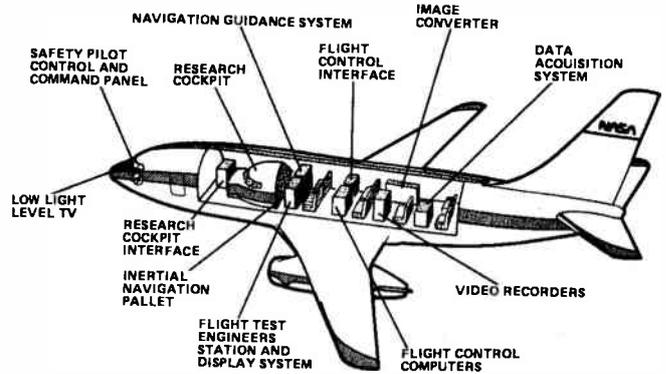
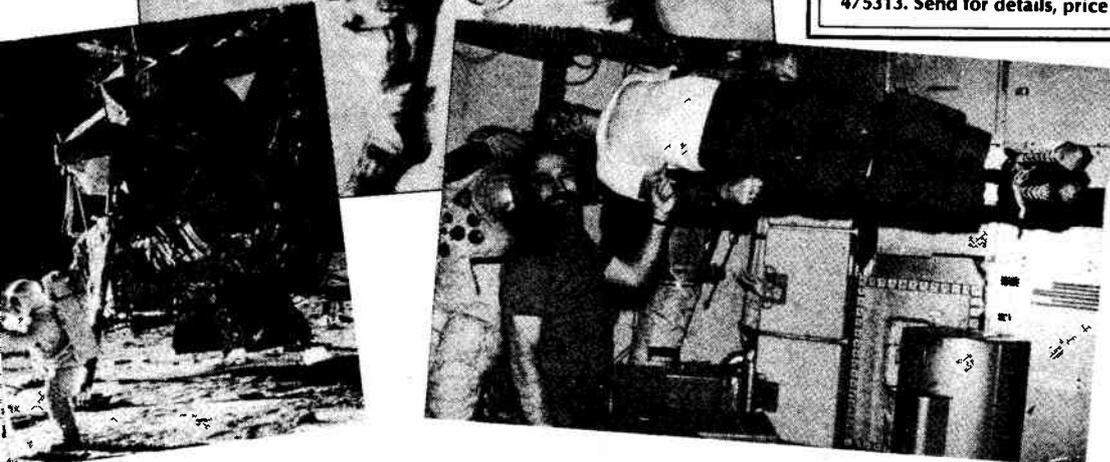
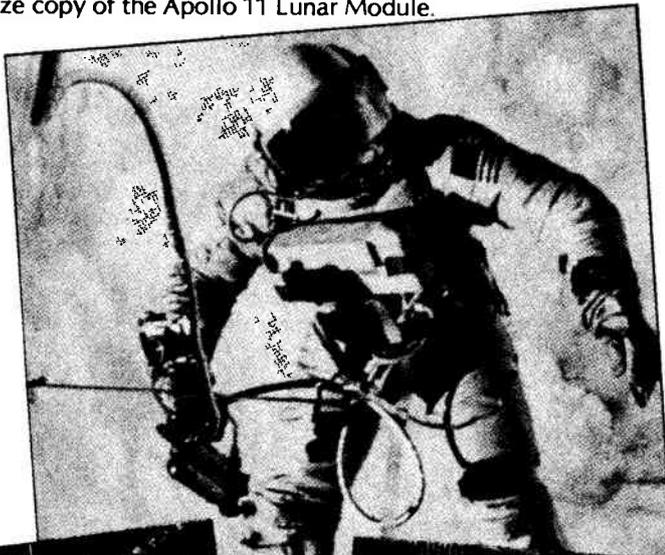


Fig.1 This modified Boeing 737 was used to study flying and take-off/landing routines in bad weather and the use of 'smart' avionics to assist in air traffic control. The Terminal-Configured Vehicle (TCV) can be flown from the research cockpit with the conventional cockpit crew providing a safety back-up. The aim of the programme is to reduce hold-ups at airports due to bad weather, reduce the separation of aircraft on take-off and landing and save fuel by using the most fuel-efficient landing programs. The end result — airlines and airports can substantially cut their losses.

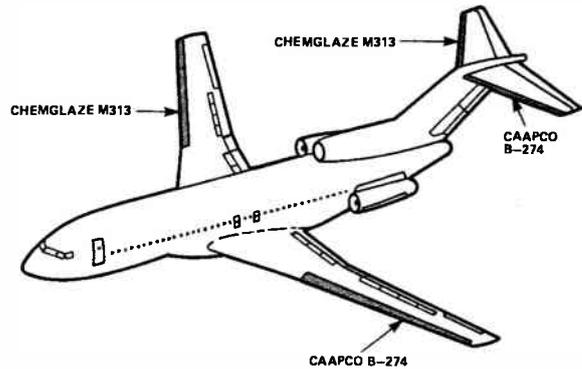


Fig.2 An Air Micronesia Boeing 727 was used to experiment with plastic coatings to reduce skin friction drag on wing and tail surfaces in a tropical environment. Two types of coatings — Chemglaze M313 and CAAPCO B-274 — are being investigated. The location and extent of the coatings on the 727 are shown above. Potential fuel savings from small drag reductions are substantial.

SHORTS

The Arianspace consortium has signed a \$150 million contract with the Columbian government to launch two telecommunications satellites, Satcol 1 and 2, into geostationary orbit in 1984.

The Mark II version of the Skyflash medium range, air-to-air missile has fallen prey to the latest defence cuts. The Mk. II version would have incorporated an improved homing head and electronic counter measures. The Mk I will have to be improved if it is to be a worthwhile weapon in service until the late 1980s.

BUYLINES

All manner of spaceflight memorabilia are available from Space Frontiers Ltd, 30 Fifth Avenue, Havant, Hampshire PO9 2PL. Tel:0705 475313. Send for details, price lists, etc.

Ed White floats in space, the solar wind experiment rises on the moon and supermen exercise in Skylab. Space Frontiers will supply these and many, many more in full colour. Our lead photograph is the Apollo 10 Command Module, now on display in the Exploration section of the Science Museum, South Kensington.

ETI

ETI APRIL 1981

The watches everyone wants at prices everyone can afford.

SENSATIONAL SEIKO OFFER



Three genuine Seiko quartz masterpieces – the world's most wanted watches – at the sort of incredible prices only Mitrad's purchasing power makes possible. (Check at any jewellers and see how much you save).

SEIKO QUARTZ DIGITAL ALARM CHRONOGRAPH/TIMER

Seiko prestige and precision in an elegant gentleman's watch. Exceptionally clear and uncluttered digital presentation give a continuous readout in hours, minutes, seconds, day and date, and with month, day and date calendar. Alarm, with AM/PM indication, sounds twice a second for 10 seconds, then four times a second for 10 seconds. Hourly time signals. 12 hour stopwatch records elapsed time and lap times to 1/100 second. Countdown timer sounds a continuous tone at the end of the selected time. Pushbutton illumination. Water resistant. Hardlex glass. Stainless steel case with black panel. Adjustable stainless steel strap. In presentation box with operating instructions.

SPECIAL OFFER PRICE

ONLY £34.95

plus £1.25 p&p

Trade £26. Add 15% VAT + £1.50 p&p per order. (Minimum order 5 watches, one style or mix of styles)

SEIKO QUARTZ ANALOGUE WATCH

A beautiful, classically styled, ladies watch that combines elegance with the incredible accuracy of Seiko quartz technology. Gold plated case with stainless steel back. Gilt face with clear gold markings. Hardlex glass. Most attractive strap that has the appearance of the fashionable bangle strap, but is so flexible and adjustable that it will fit virtually any wrist – even a small child's. Gold safety chain. In presentation box with setting and care instructions.

SPECIAL OFFER PRICE

ONLY £49.95

plus £1.25 p&p

Trade £41. Add 15% VAT + £1.50 p&p per order. (Minimum order 5 watches, one style or mix of styles)

☎ Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention.

NB. Please do not use the coupon for trade orders.

SEIKO QUARTZ MEMORY BANK CALENDAR WATCH

Inimitable Seiko styling in a gentleman's precision watch. Clear digital presentation provides continuous display of hours, minutes, seconds, month, day and date for optional 12/24 hour cycle. Optional monthly calendar display of month, year and dates for designated month (any month, January 1930 to December 2009). Sunday indication and Sunday dates flashing. Memory bank stores up to 11 dates, displays 'MEMO' and flashes on designated dates. Display flashes as battery life nears end. Pushbutton illumination. Water resistant. Hardlex glass. Stainless steel case with black panel. Adjustable stainless steel strap. In presentation box with operating instructions.

SPECIAL OFFER PRICE

ONLY £27.95

plus £1.25 p&p

Trade £20. Add 15% VAT + £1.50 p&p per order. (Minimum order 5 watches, one style or mix of styles)



MITRAD 68/70 High Street, Kettering, Northants, NN16 8SY. Telephone (0536) 522024

The premier mail order house specialising in quality products and superior after-sales care.

To Mitrad 68/70 High Street, Kettering, Northants.

Please send me

- Seiko Quartz Digital Alarm Chrono. at £36.20 (incl. p&p)
- Seiko Quartz Memory Bank Calendar Watch at £29.20 (incl. p&p)
- Seiko Quartz Analogue Watch at £51.20 (incl. p&p)

Total value of my order £ _____

I enclose cheque/PO made payable to Mitrad

Or debit my Access/Barclaycard No. _____

Signature _____

Name _____

Address _____

(BLOCK LETTERS PLEASE)

Allow up to 28 days for delivery. Full refund if not completely satisfied. Registered in England No. 2554356.

ETI 4/81



Freeport A
Birmingham
B19 1BR
021-233-2400

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MOS (BUFFERED)				LINEAR				SEMICONDUCTORS			
HEF4001	22	HEF4044	105	HEF4512	139	CA3046	84	IN614	5	BC182L	12
HEF4002	22	HEF4046	133	HEF4516	127	CA3080E	77	IN4001	5	BC184	11
HEF4007	22	HEF4047	109	HEF4517	478	CA3130E	99	IN4002	5	BC184L	12
HEF4009	119	HEF4049	57	HEF4519	69	CA3180E	283	IN4004	7	BC212	12
HEF4011	100	HEF4051	87	HEF4520	118	LM301AN	34	IN4148	4	BC214	11
HEF4018	22	HEF4052	90	HEF4521	235	LM339N	78	IN5402	15	BC214L	12
HEF4012	22	HEF4053	90	HEF4528	124	LM339N	104	2N3299	21	BC247	13
HEF4013	57	HEF4066	62	HEF4532	150	LM381AN	198	2N3546	48	BC248	11
HEF4014	105	HEF4067	475	HEF4534	638	LM3900N	75	2N2826G	13	BC249	12
HEF4015	100	HEF4068	22	HEF4539	138	MC3402P	196	2N3053	19	BC257	15
HEF4016	57	HEF4069	22	HEF4585	122	NE531	131	2N3054	35	BC268	15
HEF4017	100	HEF4070	22	HEF4724	214	NE532T	288	2N3055	35	BC270	15
HEF4018	100	HEF4071	23	HEF4077	113	NE588N	28	2N3702	9	BC271	15
HEF4019	58	HEF4072	23	HEF4099	92	NE588N	86	2N3704	9	BC2131	39
HEF4020	112	HEF4073	23	HEF40106	78	NE588N	171	2N3705	10	BD132	39
HEF4021	107	HEF4075	23	HEF40160	149	NE571N	505	2N3713	297	BD139	39
HEF4022	103	HEF4076	130	HEF40192	149	NE571N	505	2N3819	22	BD140	39
HEF4023	22	HEF4077	72			PCA138	148	2N3820	38	BFR80	333
HEF4024	78	HEF4078	23			TBA1205	88	2N3904	9	BFK85	29
HEF4025	22	HEF4081	23			TD10348	230	2N4557	39	BFY50	17
HEF4026	244	HEF4082	23			TD10348	230	2N4559	35	BFY51	17
HEF4027	57	HEF4083	80			TLO81CP	84	40873	88	BRV39	50
HEF4028	89	HEF4086	80			TL064CN	156	BC107	14	BSX20	21
HEF4029	113	HEF4093	63			NEB70N	485	2N3713	297	CL2090	2850
HEF4030	58	HEF4094	219			UA7812CU	78	UA741CT	47	BC108C	18
HEF4031	250	HEF4154	208			UA7815CU	97	BC109	14	TP32	54
HEF4035	138	HEF4507	114			UA7912CU	78	BC109B	19	TP41C	78
HEF4040	107	HEF4505	74			UA7915CU	107	BC109C	19	TP41C	78
HEF4041	94	HEF4508	230			UA78108CS	38	BC148	10	TP2955	75
HEF4042	83	HEF4510	135			UA7812CS	38	BC158	10	TP3056	60
HEF4043	100	HEF4511	157			UA7815CS	38	BC177	17	TI543	38

CAPACITORS				ELECTROLYTIC RADIAL LEADS				ELECTROLYTIC RADIAL LEADS			
Electrolytic Axial				Polyester Radial Leads				Electrolytic Radial Leads			
-10% to +50% Tol.				Dipped Type, C280/282 Style				-10% to +50% Tol.			
Cap 018 + pF				Moulded Type, 10.2mm Pitch				Cap 034 + pF			
1.0	10	28	40	83	100	200	300	400	500	600	83
1.5	10	28	40	83	100	200	300	400	500	600	83
2.2	10	28	40	83	100	200	300	400	500	600	83
3.3	10	28	40	83	100	200	300	400	500	600	83
4.7	10	28	40	83	100	200	300	400	500	600	83
6.8	10	28	40	83	100	200	300	400	500	600	83
10	10	28	40	83	100	200	300	400	500	600	83
15	10	28	40	83	100	200	300	400	500	600	83
22	10	28	40	83	100	200	300	400	500	600	83
33	10	28	40	83	100	200	300	400	500	600	83
47	10	28	40	83	100	200	300	400	500	600	83
68	10	28	40	83	100	200	300	400	500	600	83
100	10	28	40	83	100	200	300	400	500	600	83
150	10	28	40	83	100	200	300	400	500	600	83
220	13	28	40	83	100	200	300	400	500	600	83
330	13	28	40	83	100	200	300	400	500	600	83
470	13	28	40	83	100	200	300	400	500	600	83
680	21	28	40	83	100	200	300	400	500	600	83
1000	25	30	40	83	100	200	300	400	500	600	83
1500	35	39			100	200	300	400	500	600	83
2200	42				100	200	300	400	500	600	83

RESISTORS				SKELETON PRESETS, MINIATURE				SKELETON PRESETS, STANDARD			
Carbon Film, Fixed				0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting				0.1W, E3 Values, 100R-1M, Lin. Horizontal Mount			
0.25W, E24 Values, 100-10M, 5% Tol.				0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting				0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting			
2 each				8 each				11 each			
Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)			
0.5W, E12 Values, 10R-4M7, 10% Tol.				0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mount				0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mount			
3 each				11 each				11 each			
Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)			
Metal Film, Fixed				0.5W, E3 Values, 1K-2M2, Lin.				0.25W, E3 Values, 4K7-2M2, Log.			
0.5W, E24 Values, 5R-1M, 2% Tol.				8 each				39 each			
2.5W, E12 Values, 10R-27K, 5% Tol.				18 each				39 each			
Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)			
Metal Glaze, Fixed				0.5W, E3 Values, 2K2-470, Lin.				0.25W, E3 Values, 1K0-1M0, Log.			
0.5W, E24 Values, 1M-33M, 5% Tol.				18 each				45 each			
Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)				Req RD% 100/100 (Multi 10/Value)			

MAINS TRANSFORMERS				PLASTIC BOXES - BOTS INDUSTRIAL MOULDINGS			
Secondaries may be connected in series or parallel to give wide voltage range				Moulded Box and Base Fitting Flanged Lid			
Primaries 0-220, 240V				ABS Box, CW Brass Bushes, and Lid in Orange			
BVA - Clamp Type Construction				L112 W82 D31			
Approx 18% Regulation F.C. 54, W36, W35				L190 W80 D50			
4-5V, 0-4.5V Secondaries				L190 W110 D80			
0.5V, 0-8V				LBS W56 D28			
0-12V, 0-12V				L111 W11 D42			
0-15V, 0-15V				L181 W86 D53			
0-20V, 0-20V				L182 W113 D81			
20VA - Clamp Type Construction				Diecast Boxes			
Approx 18% Regulation F.C. 70, H48, W48				Diecast Box and Flanged Lid			
4-5V, 0-4.5V Secondaries				Aluminium Box and Lid in Natural Finish			
0.8V, 0-8V				L113 W63 D31			
0-12V, 0-12V				L152 W82 D50			
0-15V, 0-15V				L182 W113 D81			
0-17.5V, 0-17.5V							
0-20V, 0-20V							

VERO ELECTRONICS PRODUCTS				SWITCHES			
2.5" x 5" 1" pitch Veroboard				Miniature Toggle - Honeywell			
3.75" x 5" 1" pitch Veroboard				SPDT C/O/H			
2.8" x 1" 1" pitch Veroboard (S)				SPDT Double Bias To Centre			
3.75" x 5" 1" pitch Plain Board				DPDT			
5.82" x 2.8" 1" pitch V-Q D/B Board				DPDT C/O/H			
Spot Face Cutter				Miniature Push - C & K			
Pin Insertion Tool for .040 type pin				SP Push To Make, Momentary			
DS Pins .040 (100)				SP Push To Break, Momentary			
DS Pins .040 (100)							
Verovare Kit (1-ohm, 2-wire, 25-comb)							
Verovare Combs (25)							
Verovare Wire (2)							

GMT ELECTRONICS PROJECTS			KIT	BUILT UP
FREE-STANDING COMPLETE TELETXT UNIT - FULL SPEC			£199-90	£275-00
TELETXT DECODER BOARD + REMOTE HAND CONTROL			£135-90	£160-00
TELETXT COMPATIBLE TUNER AND P. S. U.			£ 46-90	£ 57-00
TELETXT COMPATIBLE PAL ENCODER + MODULATOR			£ 22-90	£ 35-00
F. E. T. OUTPUT 100W MONO POWER AMPLIFIER MODULE			£ 27-50	£ 35-00
X-BAND DOPPLER RADAR ALARM MODULE - MARK II			£ 35-90	£ 44-00
ONE AMP P. S. U. MODULE (SPECIFY 5 OR 12 VOLTS)			£ 7-50	£ 10-00
SIMULATED INERTIA MODEL TRAIN CONTROLLER			£ 22-50	£ 35-00
SIMULATED INERTIA SLOT RACER CONTROLLER			£ 27-50	£ 40-00
MODEL TRAIN STEAM SOUND SIMULATOR MODULE			£ N/A	£ 5-00

LOW-COST, RUGGED TEMPERATURE CONTROL

HIGH QUALITY

TEMP. GAUGE 0° - 120° C
Remote sensor on 38" capillary, panel mounting dial 55mm. dia.
ONLY £1.85
(Incl. P&P)

16A 240V RANCO THERMOSTAT
Wide control range (low room temp. to over boiling point)
Sensor on 22" capillary. **£2.30**, including control knob.

RANCO THERMAL CUT-OUT 100° C
15A 240V. Sensing coil on 41" capillary. Panel mounting with reset button.

BUY ONE EACH OF ABOVE FOR £4.85

LIGHT DEPENDENT RESISTORS in plastic housing with window. 18" heavy duty lead. Two types - A similar to ORP6. B similar to ORP12. You normally pay well over double for Resistor alone. Either type **30p each** or **£2.35** for 10 (any mix).

DOUBLE ENDED SMITHS BLOWERS
2 output apertures, 53 x 103 mm. Large flange. **Only £5.50**.

SMALL INDUCTION MOTOR (shaded pole), double ended with 3/4" x 3 1/2" shafts, 240V. **£3.25**.

BULGIN STRAIN RELIEF SLEEVE 10 FOR 30p

USEFUL RUBBER GROMMETS. Fit 3/4" hole. **10 for 20p**.

20WATT RESISTOR. 410Ω 5% wire ended. **Only 50p**.

RELAYS BY KEYSWITCH
10A 2-Pole C/O 240V Col.
ONLY 80p
2 for £1.50
5 for £3.50

Panel M.E.S. Bulb Holder. High quality. Red lens. **30p**

BULGIN GLASS FUSES
20 mm 1A Quick Blow
10 for 40p
1" (same size as 13A plug fuse but not to BS1362). Will fit most 1 1/4" chassis mount fuse holders, 10A quick blow. 5A anti-surge, 3A quick blow.
10 (any mix) 40p
100 for £3

GEC CONTACTOR
3 heavy duty normally open contacts 600V 35A. 240V coil.
ONLY £4.50

TOP QUALITY CHROME TOGGLE SWITCHES
2 pole C/O centre off 10A 240V, 80p, 2 for £1.50, 5 for £3.50.
2 Pole make, biased off 2A 240V.
30p. 4 for £1

CAPACITOR, 800V AC, RMS, 0.01 MFD.
30p each

ADD 50p P&P
ORDERS OVER
£2.50 post free

LEM SERVICES
239 RUGBY ROAD
LEAMINGTON SPA CV32 8DY
WARWICKSHIRE

BUILD YOUR OWN METAL DETECTOR

VLF/TR VCO/TR IB/TR BFO...

Pre-aligned search heads — test equipment not required. Literature available in return for SAE. Manuals and parts sold separately: write or phone for price. Export welcome: write for quote.

Shadow VLF/TR. Full specification discriminator, not just ferrous/nonferrous indication. It works by measuring the conductivity of the target; now you can reject nails bottle caps even aluminium foil and ring pull tabs! Full ground effect exclusion over normal or high permeability soils.
The head is thermally and capacitively shielded.
4 modes: deepseeking VLF plus 3 TR discriminating ranges.
Push button "memory" tuning. Performance equals commercial detectors costing £200! As described in ETI.
Complete kit now only £87.67 inc. VAT & post!

Shadow TR/IB. (Illustrated). A true transmit receive/induction balance detector at a budget price for anyone who doesn't need discrimination. Waterproof and thermally insulated search head. Good sensitivity. Built-in speaker and headset jack. **Complete kit £33.60 inc. VAT and Post.**

Shadow TR/VCO. An advanced version of the TR/IB. Use as a sensitive IB machine or switch to VCO mode when the sound changes to a varying pitch, allowing easier use over mineralised ground and enabling detection of negative, high permeability anomalies. **Kit price £38.67 inc. VAT and Post.**

Matching stereo headphones for all Shadow models £6.85 inc. VAT and Post

Shell Kit. Consists of the (hard to find) hardware items, for detectors of your own design. Fully adjustable shaft with handle, search head mouldings (int. diam. 185mm) with hinge assembly, special clips to mount your own control housing (any box is suitable). Completely non-metallic and undrilled. With assembly instructions **£14.45 inc. VAT and Post.**

ALTEK

(ETI), 1 Green Lane
Walton-on-Thames Surrey

Order by post or phone (24 hours). Access & Visa Cards quote number. Callers by appointment only please.
Phone (093 22) 44110 anytime!

DRUM MACHINE

Drums, cymbals, snares and bongos. You can simulate these instruments with this 'double percussion' project. The instruments can be played either manually or automatically using a built-in sequencer. Design by Ray Marston. Project development by Steve Ramsahadeo.



This attractive little musical instrument has two 'percussion simulator' channels. Channel 1 can be used to simulate the sounds of normal drums only: channel 2 can be used to simulate the sounds of all types of drums, including snares, plus metallic percussion sounds such as cymbals, etc. On each channel, the envelope decay times and the basic musical tones, etc., are fully variable using the manual controls, to enable a wide range of percussion sounds to be simulated. The outputs of the two channels are mixed internally and can be fed to an external power amplifier from a single output socket. The complete instrument is powered from a 12 V battery pack.

Play It, Sam

The instrument can either be played manually, automatically, or by a combination of the two methods. In the manual mode, each channel can be played using a small speaker, connected to the channel input: the speaker acts as a 'drum head' transducer and triggers a percussion sound when the cone is tapped with a finger or stick.

The instrument can be played automatically using the built-in eight-step sequencer. Each channel of the sequencer is used to control one of the channels of the percussion

instrument, and can be programmed with a DIL package of eight SPST switches to generate any one of a variety of rhythms. The sequencer can be used in the fully automatic mode, in which it continuously cycles through the eight-step sequence, or can be used in a triggered, or manual initiate, mode in which it runs through a single eight-step sequence each time that an external switch is momentarily closed. The manual initiate facility enables the internally-generated rhythm to be manually synchronised to an external beat (with a foot switch, etc), or to be introduced into the music only in those parts where it is required.


The manual and automatic playing methods operate in the OR mode. In other words, manually-initiated percussion sounds can be played at the same time as the automatically initiated sounds. A particularly attractive way of using the instrument is to play it mainly in the manual mode, but to occasionally bring in a few bars of automatic sequencing with a foot switch, using the manual initiate facility. The unit thus acts as a highly versatile musical instrument.


Construction

The circuitry is built up on two PCBs, a single large board being used to hold all of the components (except the pots and switches) of the main double percussion instrument, and a smaller board being used for the components of the sequencer circuit. The unit uses a good deal of interwiring between the PCB and the total of eleven control pots, etc., so some care is required in the construction.

Start the construction by building up the main PCB, taking the usual care over the component polarities. Use Veropins to facilitate the connections from the PCB to the ten control pots.

When construction of the main PCB is complete, give it a functional check by temporarily connecting the ten pots to the unit, wire a couple of small speakers (impedance not important) to the two input terminals, connect the unit to a 12 V supply and take the output to an external power amplifier. Check that plain drum sounds can be manually generated on channel 1, and all types of percussion sounds from channel 2. Note on channel 2 that Q5 is used as a white noise source (for generating cymbal

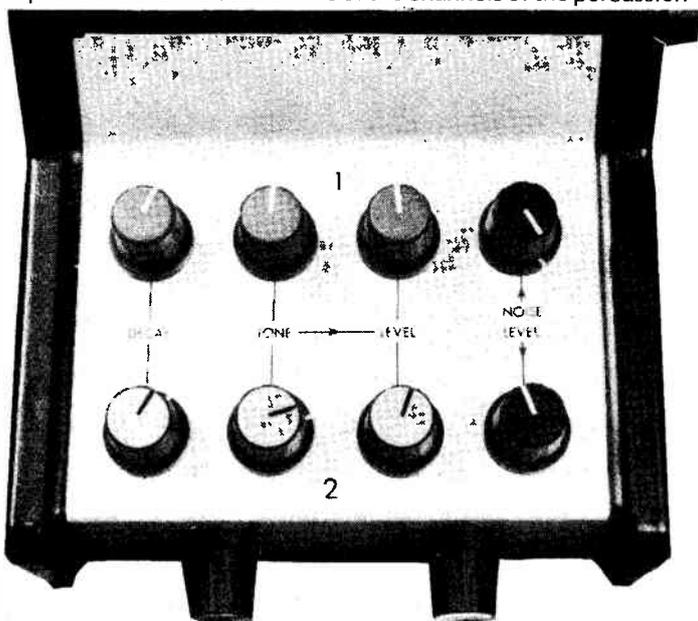

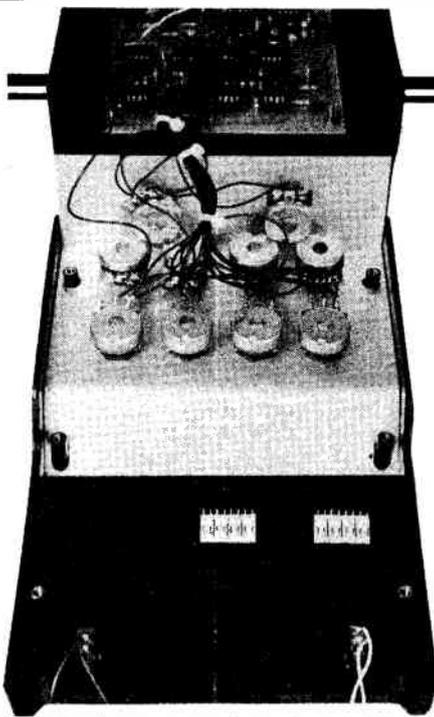

The DIL switches are epoxied to the top of the case as shown here. The sequencer board can then be secured by plugging the DIL sockets onto the exposed pins.

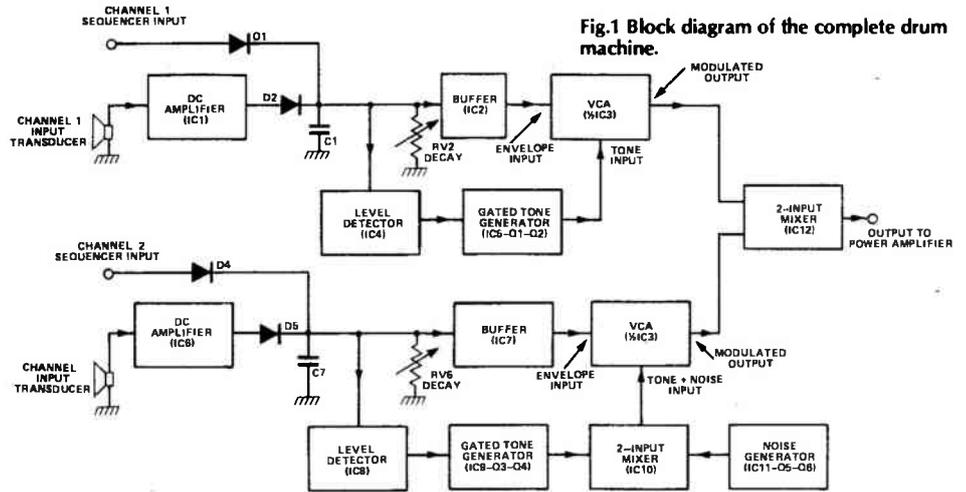


Fig.1 Block diagram of the complete drum machine.

BUYLINES

No unusual components are used in this project, your local emporium should meet your requirements. However, if you experience difficulty in obtaining the NE570, Watford Electronics are stockists of this device.

Collet knobs are available from Electrovalue Ltd. and the case from West Hyde Developments, order as BOC668.

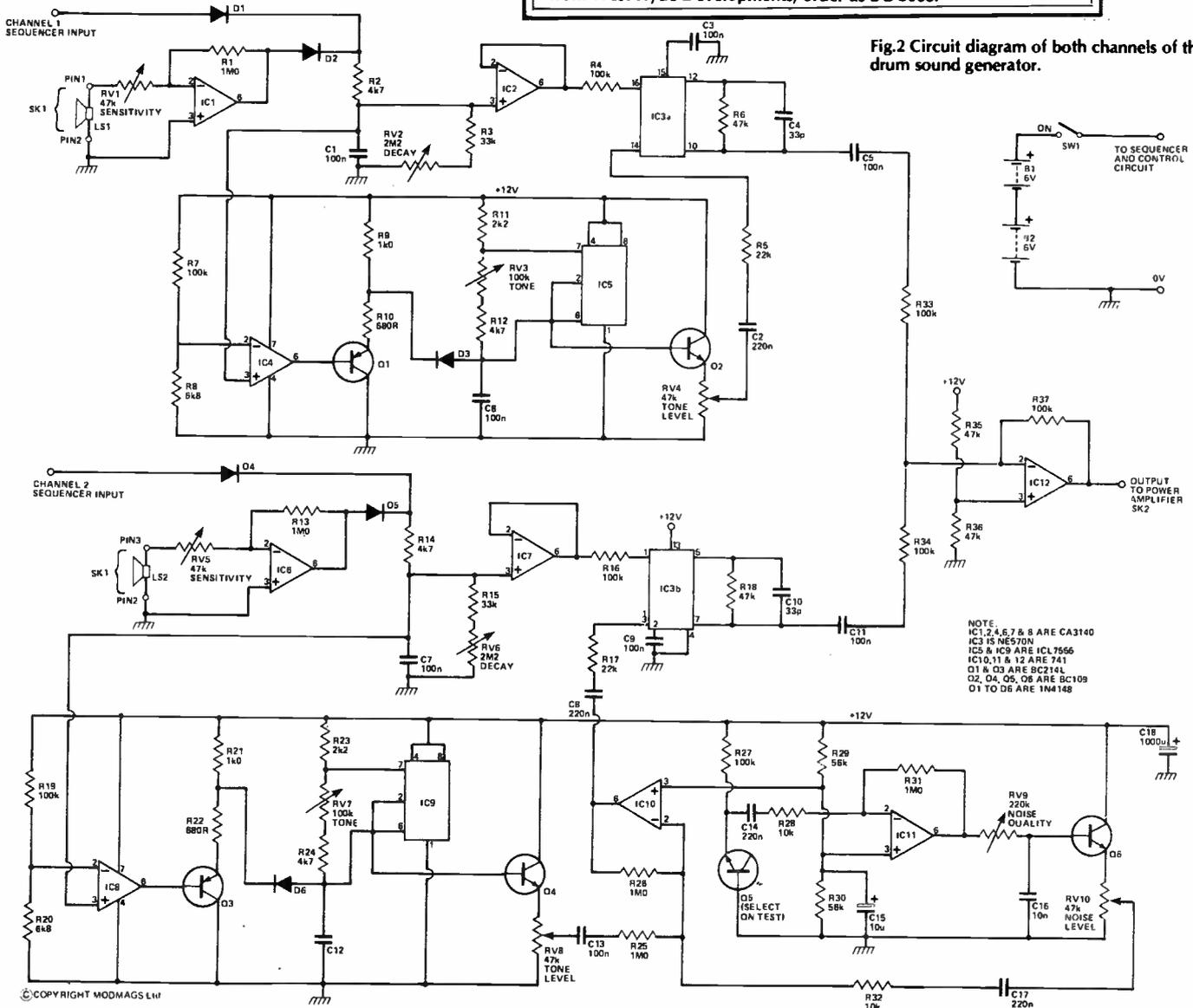


Fig.2 Circuit diagram of both channels of the drum sound generator.

NOTE:
 IC1, 2, 4, 5, 7 & 8 ARE CA3140
 IC3 IS NE570
 IC5 & IC9 ARE ICL7556
 IC10, 11 & 12 ARE 741
 Q1 & Q3 ARE BC174L
 Q2, Q4, Q5, Q8 ARE BC109
 Q1 TO Q6 ARE 1N4148

© COPYRIGHT MODMAGS LTD

HOW IT WORKS

The basic instrument contains two essentially similar channels (see block diagram), each comprising a voltage-controlled amplifier (VCA), a gated tone generator and an envelope generator. The envelope generator produces the characteristic fast-attack/slow-decay modulation waveform of a percussion instrument and can be activated by either an external transducer (a speaker) or the pulse input of an automatic sequencer unit.

The outputs of the two channels are added in a two-input mixer and are made available at a phono socket, where they can be fed to a power amplifier. The channel 1 circuitry produces modulated tone signals only, and can be used to generate a range of simple drum sounds. The channel 2 circuitry incorporates a noise generator and a two-input mixer as well as a tone-generator, and can be used to reproduce all of the sounds of channel 1 plus snare drums, cymbals, etc.

The two channels of the instrument are basically similar, so let's start off with a detailed description of channel 1. When used in the manual mode the instrument is played using an external transducer such as a speaker (LS1), which is connected to the input of high-gain DC amplifier IC1. Each time that the transducer is tapped, the output of IC1 jumps abruptly positive and rapidly charges C1 via D2-R2; C1 then discharges exponentially via R3-RV2, to produce the characteristic fast-attack/slow decay modulation waveform of a percussion instrument. The waveform is then fed to one half of dual VCA IC3 via unity-gain buffer IC2, where it is used to control the gain of the VCA.

Note that the C1 modulation generator can be activated by either the transducer or by a pulse signal fed to C1 via D1-R1 from the independent sequencer circuit (auto mode). The C1 voltage is monitored by comparator IC4, which gates on astable IC5 whenever the C1 voltage exceeds a few hundred millivolts. The astable generates a symmetrical ramp waveform, which is buffered by Q1 and fed to the 'tone' input of VCA via level control RV4. The tone of the astable can be varied over the range 83 Hz to 1.4 kHz with RV3.

Thus, each time the channel is activated (by the transducer or by a sequencer) a modulation waveform is fed to one input of the VCA and a tone signal is fed to the other, to produce a modulated tone signal at output pin 10 of IC3. The signal is fed to one input of two-input mixer IC12. A wide variety of drum sounds can be simulated by suitable adjustment of RV2, RV3 and RV4.

Channel 2 is similar to channel 1, except that the output of the tone generator (from RV8) is fed to the VCA via a two-input mixer designed around IC10. The other input to this mixer is derived from a

noise generator designed around Q5-IC11 and Q6. Here, the reverse-biased base-emitter junction of Q5 is used as a noise source and the noise signal is then amplified by IC11, filtered by RV9-C16 and made available via level control RV10.

The instrument is powered from a 12 V supply, derived from eight 1V5 cells. This supply is also used to power the Auto-Manual Eight-Step Sequencer unit.

The sequencer unit has two output channels, each of which produces a single or repeating sequence of up to eight 5 mS output pulses; the sequencing period can be varied over a wide range by a clock (or 'tempo') generator, and individual pulses can be programmed in or out on each channel with a dual-in-line package of eight SPST switches. The unit is designed to automatically sequence the double percussion instrument.


The unit comprises a clock generator (IC1), a 4017 counter (IC2) and two sets of switch-programmable clock/decoder coincidence detectors (IC1 and D3 to D18). The clock generator is designed around a 555 astable and generates a series of 5mS pulses, with the inter-pulse period variable over a wide range by RV1. The pulses are used to clock IC2.

IC2 is a 4017 counter with ten decoded outputs. These outputs sequentially go high on the arrival of each new clock pulse, with only one output being high at any moment in time. On each channel the decoded 4017 outputs that are required are fed to one side of a two-input AND gate (IC3a-IC3b or IC3c-IC3d) via a bank of diodes and switches, while the 5mS clock pulse is fed to the other side of the AND gate. The programmed sequence of 5 mS pulses are thus generated at the output of each AND gate.


When the unit is operated in the manual mode, the 4017 sequences automatically for the first eight clock pulses and then stops as its '9' output goes high and activates the inhibit pin: the single automatic sequence can be re-initiated by momentarily closing PB1 and thus resetting the 4017, so that the '1' output goes high on the arrival of the next clock pulse. The manual facility enables the sequencer to be manually synchronised to an external beat.

When the unit is operated in the auto mode the reset and inhibit pins of IC2 are shorted together by SW3. This configuration effectively causes the 4017 to see a double clock pulse as the '9' output goes momentarily high, thereby causing the '0' output to go high as the IC resets but then causing the '1' output to go high almost immediately. The net effect of all this is that the sequence repeats continuously when SW3 is set to the auto mode.

Fig.3 Circuit diagram of the eight-step sequencer unit.

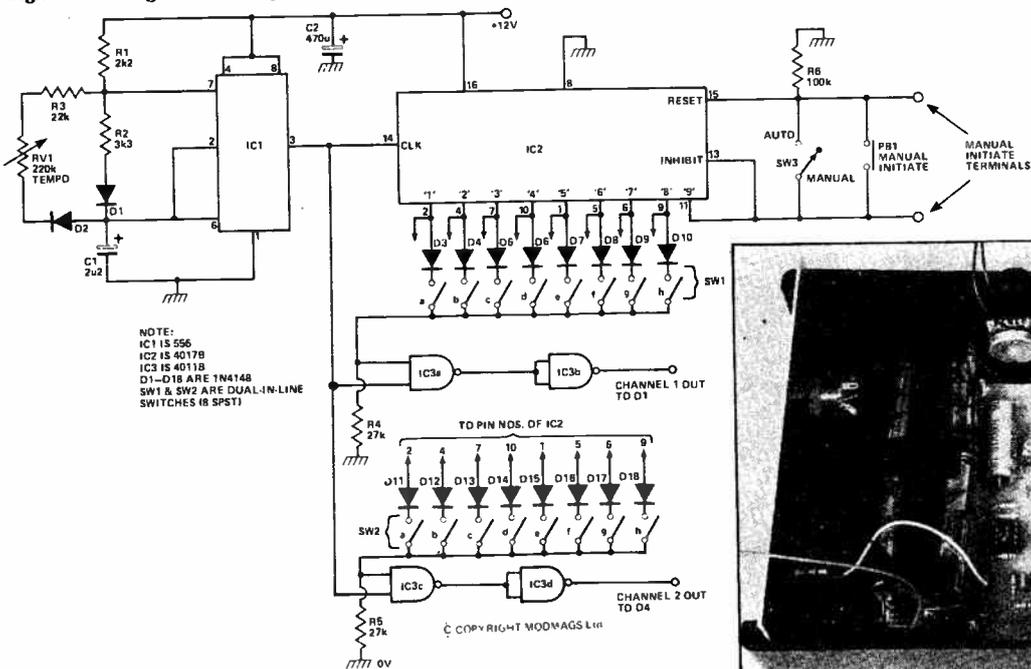

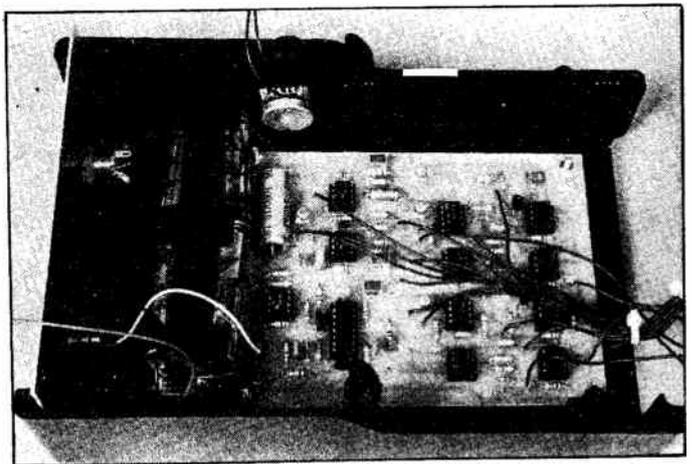Below: the sound generator board and batteries are mounted in the lower half of the case. RV1 (tempo control) can be seen mounted on the side — all other pots are situated on the front panel.



sounds, etc), and may have to be selected on test to produce an adequate noise level.

Proceed next with the construction of the sequencer circuit on the smaller PCB. Note that the two sets of DIL switches MUST be mounted in sockets, and that capacitor C2 is mounted on the underside of the PCB.

You can now proceed with the assembly of the two boards and all other components in the specified case. Note the following points. The large PCB is secured to the base of the case with stand-off pillars: leave sufficient space at the rear of the case to accommodate the battery pack (eight 1V5 cells). The ten percussion-control pots are mounted on the front section of the top half of the case.

The sequencer board is secured to the rear half of the top section of the case by the board's DIL switches, which are epoxied to the case. Proceed as follows.

First, hold the board in position below the case top and very

carefully mark out the precise outlines of the two switches. Now cut two holes in the case top, to allow the switches to pass through the case. Next, remove the switches from their PCB sockets, push them into the holes so that the top faces are flush with the case top and then fix the two switches into place with epoxy or super-glue. When the glue has set, fit the PCB to the switches (and thus the case) by carefully inserting the DIL switches in the sockets. Tempo control RV1 is mounted on the right hand side of the lower half of the case.

Finally, to complete the construction, fit all the remaining switches and sockets into place and complete the interwiring. We recommend that you use jack sockets to connect the two 'drum head' speakers to the unit, configured so that the input pins short out if the speakers are removed.

When using the completed unit, note that, if the 'drum head' speakers are not used, they must be replaced by short circuits, to eliminate the possibility of circuit instability.



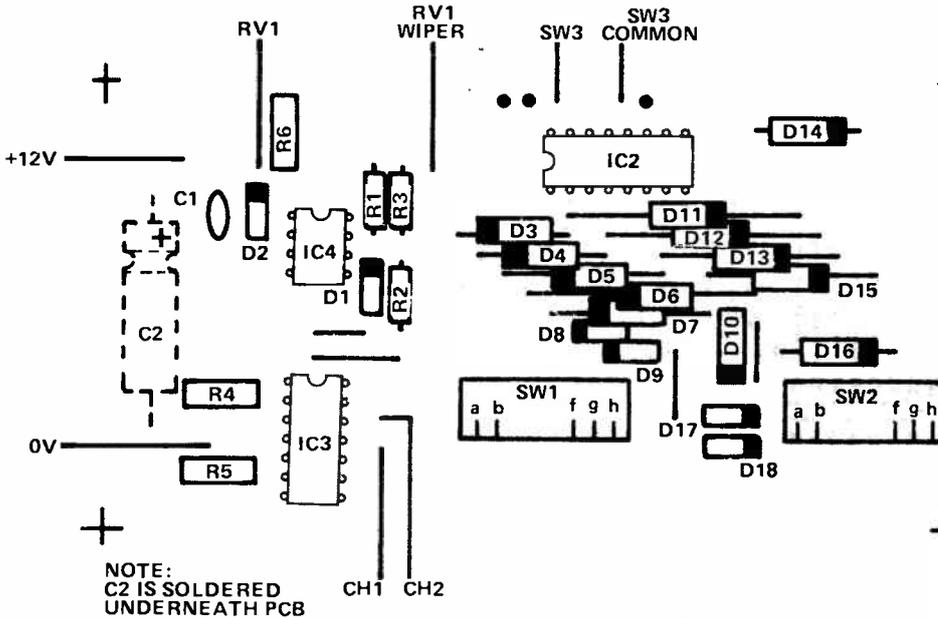
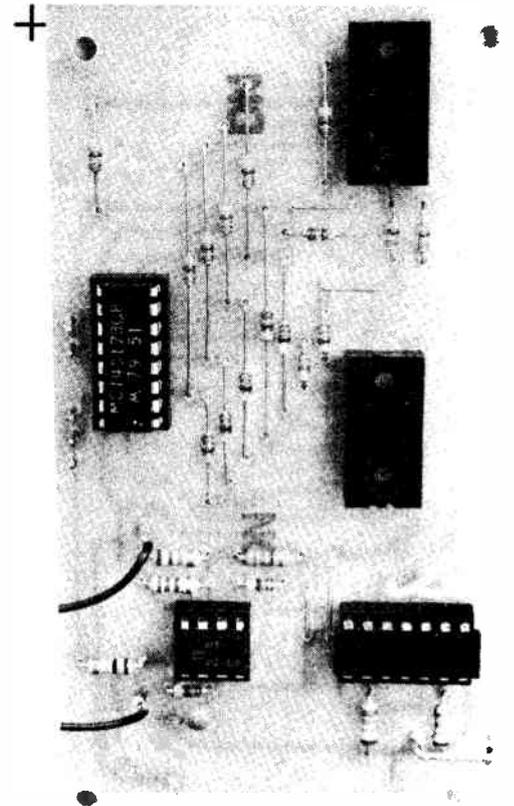


Fig.4 Component overlay for the sequencer board. Note that C2 is soldered underneath the PCB, and an insulated link should be soldered between IC2 pin 8 and the 0 V rail.

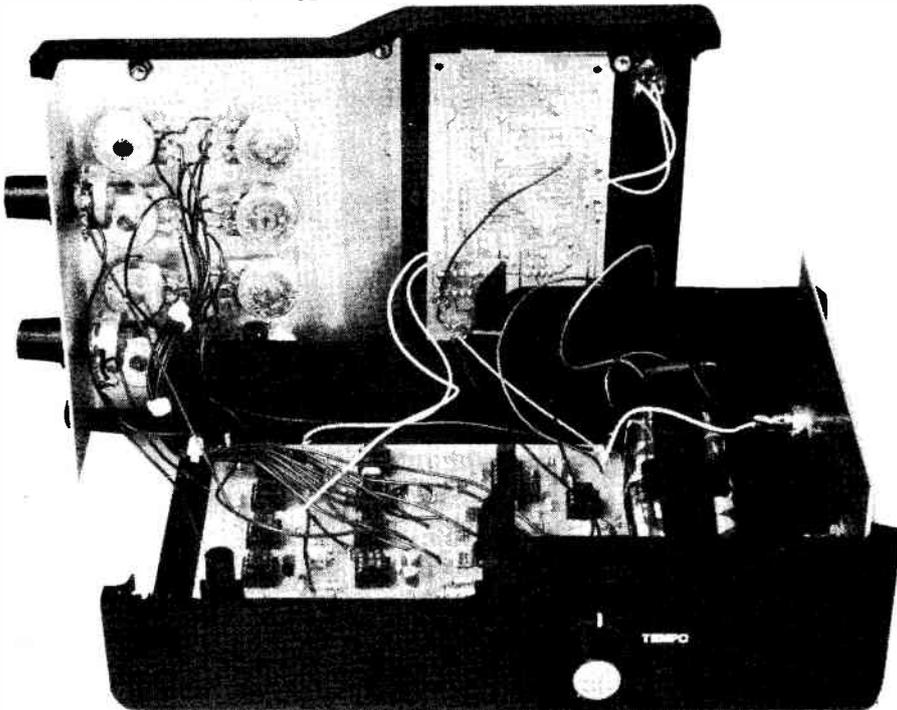Below left: with the case open you can see how the boards and controls are interwired. The sequencer board (below) is secured to the top of the case by pressing the empty sockets onto the pins of the DIL switches.



PROJECT : Drum Machine

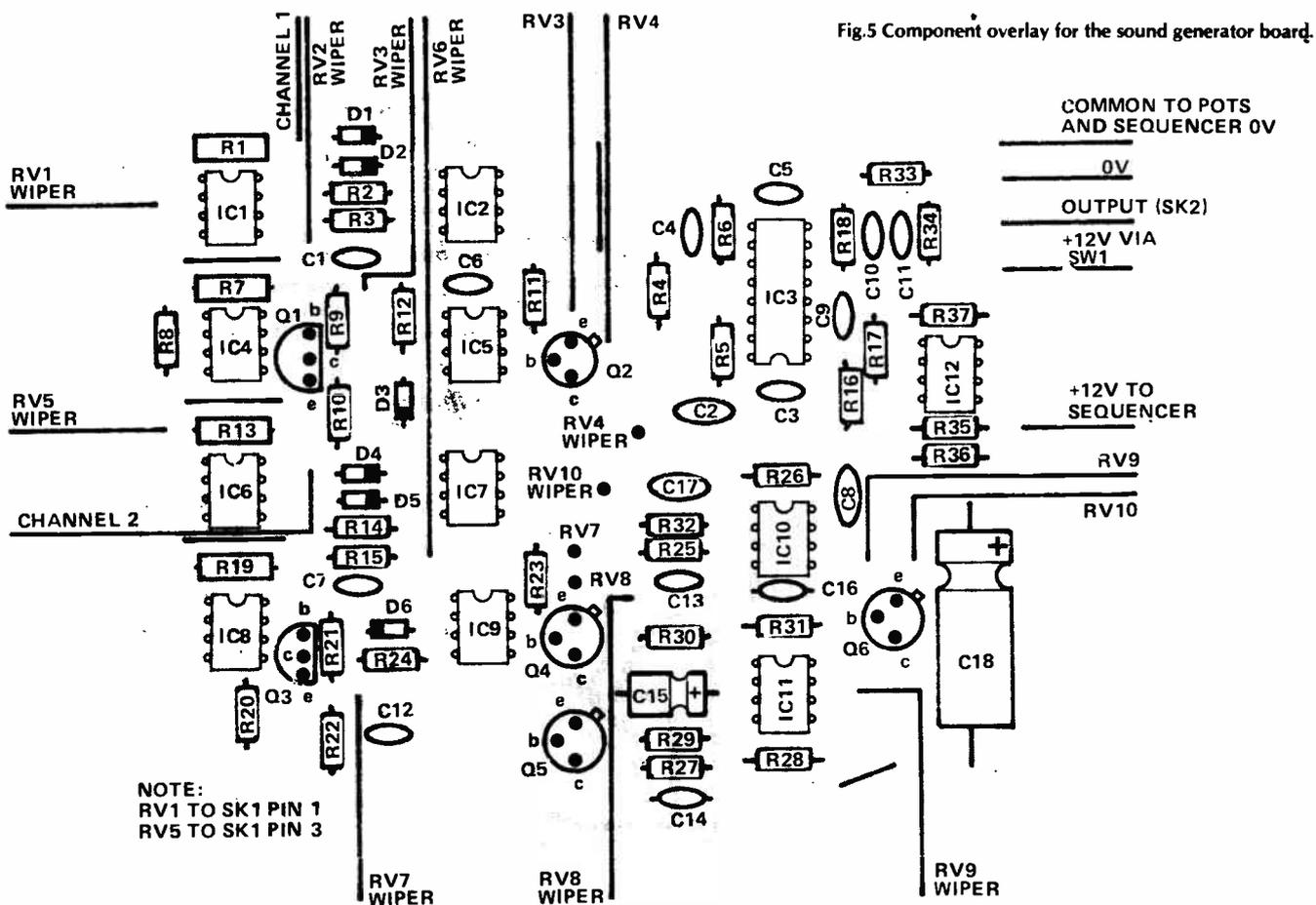

PARTS LIST

CONTROL CIRCUIT

Resistors (all 1/4 W, 5%)

R1,13,25,26,31	1M0
R2,12,14,24	4k7
R3,15	33k
R4,7,16,19,27,33,34,37	100k
R5,17	22k
R6,18,35,36	47k
R8,20	6k8
R9,21	1k0
R10,22	680R
R11,23	2k2
R28,32	10k
R29,30	56k

Potentiometers

RV1,4,5,8,10	47k linear
RV2,6	2M2 linear
RV3,7	100k linear
RV9	220k linear

Capacitors

C1,3,5,6,7,9,11,12,13	100n ceramic
C2,8,14,17	220n polycarbonate
C4,10	33p ceramic
C15	10u 25 V axial electrolytic
C16	10n ceramic
C18	1000u 16 V axial electrolytic

Semiconductors

IC1,2,4,6,7,8	CA3140
IC3	NE570N
IC5,9	7555
IC10,11,12	741
Q1,3	BC214L
Q2,4,5,6	BC109

Miscellaneous

SW1	SPST miniature toggle
SK1	3 pin DIN socket and plug
SK2	phono socket
LS1,2	50 mm loudspeaker
10 off collet knobs, caps and nut covers	
Case (see Buylines)	
2 off HP7- four section battery holders	
8 off HP7 batteries	

SEQUENCER

Resistors (all 1/4 W, 5%)

R1	2k2
R2	3k3
R3	22k
R4,5	27k
R6	100k

Potentiometers

RV1	220k linear
-----	-------------

Capacitors

C1	2u2 35 V tantalum
C2	470u 25 V axial electrolytic

Semiconductors

IC1	555
IC2	4017B
IC3	4011B
D1-D18	1N4148

Miscellaneous

SW1,2	8-SPST dual-in-line lateral switches
SW3	SPST miniature toggle
PB1	momentary push button
1 off collet knob, cap and nut cover	


SAFGAN DT-400 SERIES

DUAL TRACE OSCILLOSCOPES
NEW BRITISH PRODUCTS
FROM £169+VAT

ALL MODELS

- DUAL TRACE
- 5mv/div
- 4" CRT

DT-400 SERIES

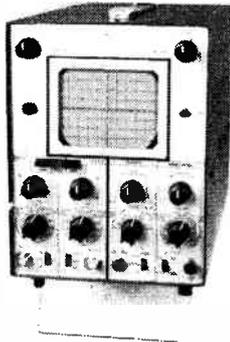

MODELS

DT-410 10MHz £169+VAT
DT-412 12MHz £175+VAT
DT-415 15MHz £188+VAT

SPECIFICATION FOR ALL MODELS

- ★ CH1, CH2; 5mv div - 20V/div in 12 cal steps.
- ★ Bandwidth: 10MHz (DT-410), 12MHz (DT-412), 15MHz (DT-415).
- ★ Time Base; 0.5µs div - 200ms/div in 18 cal steps.
x 5 expansion to 100ns/div.
x 5 multiplier to 1s/div.
- ★ XY facility: matched x = CH1, Y = CH2.
- ★ Trigger: Level Control, ± slope selection.
- ★ Bright Line Auto, Normal, TV Triggering.
- ★ CH1, CH2 0.5div; 100mv External Source.
- ★ Z modulation.
- ★ CAL o/p for probe compensation.
- ★ Graticule blue ruled 8x10div (6.4x8 cm²).
- ★ Size: H 215mm, W 165mm, D 280mm, Weight 4.5kg.

PROBE (X1 - REF - X10) £11.50+VAT

ORDERS TO SAFGAN ELECTRONICS LTD.
56 BISHOPS WOOD, ST. JOHN'S, WOKING
SURREY GU21 3QB. Tel: Woking
69560 or Woking 66836

GOODS + p&p £3.50 or parcel service £6.50 + 15%
LONDON STOCKIST: AUDIO ELECTRONICS. TEL: 01-724 3564

DT400s are designed and manufactured by SAFGAN in England

Lowest Prices Yet!

Memory Chips

Guaranteed quality - Any faulty chips should be returned to us within 12 months of purchase with proof of purchase for replacement by return of post.

4116 and 2114 chips at the same price

4116 dynamic memory chips guaranteed to 200 nanoseconds full cycle time. Suitable for Apple, TRS 80, Nascom, Exidy Sorcerer, Sharp MZ 80K etc (8 chips give 16k bytes of memory).

2114 static memory chips guaranteed to 300 nanoseconds full cycle time. Low power, suitable for Superboard CompuKit, Atom, ZX 80 etc. (2 chips give 1K byte of memory).

No. of Chips	Unit Price	Total Price		
		Nett	Vat	Total
2	1.80	3.60	.54	4.14
8	1.70	13.60	2.04	15.64
24	1.60	38.40	5.76	44.16
100	1.40	140.00	21.00	161.00
500	1.30	650.00	97.50	747.50
1000	1.25	1250.00	187.50	1437.50

Official orders welcome. Post and Packing free:
24 Hr Telephone Credit Card Orders 051-236 0707



Mail orders to:
MICRODIGITAL LIMITED
FREEPOST (No stamp required)
LIVERPOOL L2 2AB



Retail Premises at:
25 BRUNSWICK STREET,
LIVERPOOL L2 0PJ
Tel. 051-227 2535/6/7

MICRODIGITAL

A NEW ADVENTURE IN COOKING! COMPONENTS AND CHIPS FROM

Fast Service

Low Prices

Great Menu

ELECTRONICS

MF	Volts	Dim mm	Price	pp
1500*	100	80 x 25	70p	
2200	40	50 x 25	150p	
3300	25	50 x 25	150p	
3300*	63	115 x 35	80p	
3300*	150	100 x 65	120p	
4700	75	115 x 35	190p	
11000	25	80 x 50	180p	
15000	16	80 x 35	180p	
15000	40	115 x 35	190p	
22000	16	80 x 50	220p	
22000	25	115 x 35	250p	
28000	25	105 x 70	270p	80p
34000	50	145 x 75	350p	80p
64000	40	115 x 75	590p	80p
68000	16	115 x 60	575p	80p
132 000	10	145 x 75	600p	80p
160 000	30	220 x 75	750p	120p

ALL TYPES HAVE SCREW TERMINALS.

*EX-EQUIPMENT TESTED

Pitch	Ways	Price
0.1	17 AC	60p
0.1	36 BC	190p
0.1	45 BC	245p
0.1	54 AC	110p
0.1	85 AC	200p
0.15	12 AC	75p
0.15	25 BC	120p
0.15	56 BC	325p
0.156	12 PET	150p
0.156	28 BC	190p
0.156	36 BC	200p

A SINGLE SIDED B DOUBLE SIDED
C SOLD TAG D WIRE WRAP
ALL GOLD PLATED EASILY CUT TO SIZE

Type	V	A	Case	Price
LM309K	-5	12	TO3 110p	
LM323K	-5	3.0	TO3 599p	
7805	+5	1.0	TO220 50p	
7815	+5	1.2	TO3 110p	
LM723	VAR	-	DL 35p	

Type	N	LS	S
7400	10p	15p	25p
7401	12p	-	-
7402	12p	-	-
7403	14p	15p	16p
7404	14p	15p	-
7405	18p	-	-
7406	32p	-	-
7407	32p	-	-
7408	17p	22p	-
7409	22p	-	-
7410	15p	19p	-
7411	-	-	38p
7412	30p	-	-
7414	50p	-	-
7416	27p	-	-
7417	28p	-	-
7420	17p	19p	18p
7423	30p	-	-
7427	34p	-	-
7428	35p	-	-
7430	17p	20p	-
7432	28p	30p	-
7437	35p	-	-
7438	30p	-	-
7440	17p	15p	-
7441	85p	-	-
7442	55p	-	-
7445	120p	-	-
7447	45p	-	-
7450	17p	-	-
7451	85p	22p	-
7454	17p	23p	-
7470	33p	-	-
7472	28p	-	-
7473	34p	-	-
7474	28p	32p	38p
7475	28p	-	-
7476	35p	-	-
7485	90p	-	-
7486	34p	35p	-
7489	200p	-	-
7490	28p	-	-
7492	50p	-	-
7493	28p	-	-
7495	65p	-	-
7496	60p	-	-
7497	175p	-	-
74100	330p	-	-
74104	45p	-	-

Type	N	LS	S
74107	32p	-	-
74109	50p	-	-
74111	50p	-	-
74112	-	-	90p
74113	-	-	45p
74115	195p	-	-
74118	75p	-	-
74121	28p	-	-
74122	41p	-	-
74123	45p	-	-
74125	53p	-	50p
74128	72p	-	-
74132	68p	-	-
74133	45p	-	-
74147	180p	-	25p
74148	103p	-	-
74150	98p	-	-
74151	80p	-	100p
74153	85p	-	-
74154	98p	-	-
74155	60p	-	-
74157	80p	-	65p
74163	90p	-	-
74163	80p	-	-
74164	120p	-	110p
74166	120p	-	-
74170	235p	-	-
74172	445p	-	-
74173	110p	-	-
74174	85p	-	-
74175	80p	-	100p
74180	52p	-	-
74181	150p	-	-
74182	-	-	90p
74190	85p	-	-
74191	85p	-	-
74193	85p	-	55p
74194	85p	-	-
74197	75p	-	-
74198	140p	-	-
74201	150p	-	-
74266	-	-	95p
74271	235p	-	-
74279	80p	-	-
74283	155p	-	-
74284	400p	-	-
74285	400p	-	-
74298	180p	-	-
74366	95p	-	-
74367	90p	-	-
74390	-	-	140p
74393	195p	-	-

Frequency	Case	Price
19.20KHz	HC6U	300p
38.40KHz	HC6U	400p
100.00KHz	HC6U	300p
110.00KHz	B7C	400p
1.00MHz	HC6U	320p
2.00MHz	HC6U	280p
4.00MHz	HC1B	280p
5.00MHz	HC1B	280p
6.00MHz	HC1B	280p
8.00MHz	HC1B	280p
10.00MHz	HC1B	280p
10.25MHz	HC1B	280p
11.20MHz	HC1B	280p
30.00MHz	HC1B	280p

Case	Price
CA3011	60p
CA3028B	100p
CA3046	85p
CA434	110p
LM301	30p
LM324N	40p
LM3900	50p
MC1408L	40p
MC1458R	45p
NE555	25p
NE556	25p
NE567	165p
TBA673	225p
TLO82	85p
741	15p

A	V	Price
1.5	30	30p
1.5	20	50p
2.5	75	40p
5	100	80p
10	100	150p
12	400	190p

Ways	Plug	Stack	Price
9	103p	120p	
5	117p	201p	
25	172p	258p	
37	235p	414p	
50	290p	545p	

Ways	Price
1103	50p
2101-4	410p
*2114L-3	30UNS
2N3702	8p
2N3703	8p
2N3704	8p
*4116	375NS
2N3771	150p
2N3906	15p
2N4304	20p
2N4351	50p
2N4352	50p
2N5447	10p
2N5449	12p
2N5943	55p
2N5985	125p
ACY19	75p
AD161	40p

Pins	Prices
8	10p
14	14p
16	16p
18	18p
20	20p
24	25p

Ways	Price
2N697	22p
2N689	35p
2N705A	35p
2N1136A	35p
2N2646	45p
2N2904	23p
2N2906	23p
2N2926	7p
2N3053	25p
2N3055H	60p
2N3440	60p
2N3442	120p
2N3702	8p
2N3703	8p
2N3704	8p
*4116	375NS
2N3906	15p
2N4304	20p
2N4351	50p
2N4352	50p
2N5447	10p
2N5449	12p
2N5943	55p
2N5985	125p
ACY19	75p
AD161	40p

Ways	Price
2N697	22p
2N689	35p
2N705A	35p
2N1136A	35p
2N2646	45p
2N2904	23p
2N2906	23p
2N2926	7p
2N3053	25p
2N3055H	60p
2N3440	60p
2N3442	120p
2N3	

TEKTRONIX STORAGE OSCILLOSCOPE. Type 434, as new. 12 months' warranty £1,950.

TEKTRONIX OSCILLOSCOPE. Type 647, with 10A2 and 3B11. £500

TEKTRONIX STORAGE OSCILLOSCOPE. Type 564 with 3A6 and 3B4 £350

TELEQUIPMENT STORAGE OSCILLOSCOPE. Type DM53A £285.

TELEQUIPMENT OSCILLOSCOPE. Type D32. Portable, mains/battery. £275.

HAMEG OSCILLOSCOPE. Type 512 DB. 50MHZ. £350.

TELEQUIPMENT OSCILLOSCOPE. Type 554A. 50 10MHZ. £190.

SELABS OSCILLOSCOPE. Type SM 111 DB 20MHZ. £325.

ADVANCE OSCILLOSCOPE. Type OS1000 DB 15MHZ. £250.

TEKTRONIX OSCILLOSCOPE 547 with 1A1 plug-in Dual TB 50MHZ. £375.

TEKTRONIX OSCILLOSCOPE. Type 561A with 3A1 and 2B67 10MHZ. £300.

TEKTRONIX OSCILLOSCOPE. Type 533A with CA. DB 24MHZ. £140.

HEWLETT PACKARD AC CONVERTER. Type 3461A. £120.

MARCONI FM SIG. GEN. Type TF1068B/6S. £295.

G. & E. BRADLEY LTD. R.F. MILLIVOLTMETER. Type 112 £75

ADVANCE A.C. VOLTMETER. Type VM77E £80

MARCONI WAVE ANALYSER. TF2330 Good condition. £150

AVO R.F. SIG. GEN. Model HF 35. £75

MARCONI WIDE RANGE R.C. OSCILLATOR. TF1370. £95.

MARCONI AM/FM SIG. GEN. Type TF1066/1. £225.

MARCONI SENSITIVE VALVE VOLTMETER. TF2600. £80.

MARCONI SIG. GEN. MK2. TF995A/3/S (CT402) £275.

TEKTRONIX type 1130 SPECTRUM ANALYSER PLUG-IN. (works, slight corrosion) £325

AIRREC SIGNAL GENERATOR. Type 204 AM/FM 320MHZ £150

WAYNE KERR UNIVERSAL BRIDGE. Type B221 £50

ADVANCE R.F. Signal Generator E2 100KHZ-100MHZ £40

ADVANCE VHF MILLIVOLTMETER VM79 (No probe) £50

ADVANCE SIGNAL GENERATOR Type B487 30KHZ-30MHZ £25

COSSOR NOISE LEVEL METER CT48A (Ex-Ministry) £18

S.T.C. ATTENUATOR 0-100DB 600ohm CB

S.T.C. ATTENUATOR 0-100DB 75 ohm E2

AVO VALVE CHARACTERISTIC METER E20

E.M.T. UNIT 230V 50cs 25VA 7 5V £22.50

BRANDENBURG HIGH VOLTAGE GENERATORS 10KV E80

BRANDENBURG HIGH VOLTAGE GENERATORS 30KV E80

VARIACS Ex-equipment Good condition 8 amp £25

VARIACS Ex-equipment Good condition 20 amp £35

CRC GENERATOR TBF6880. Sine/square/Triangle Very good £60

B&K AUTOMATIC VIBRATION EXCITER CONTROL. Type 1018 £50

B&K AUTOMATIC VIBRATION EXCITER CONTROL. Type 1019 £50

MARCONI UNIVERSAL BRIDGE. Type TF688B £100

SOLARTRON TRUE RMS VOLTMETER. Type VM1484 £75

TAYLOR VALVE TESTER. Type 45D £85

ADVANCE LF OSCILLATOR. Type H1E £45

ADVANCE SIGNAL GENERATOR S62B 150KHZ-220MHZ £60

MARCONI UNIVERSAL BRIDGE. Type TF688A £50

TAYLOR METER MODEL 128. £15

R&S SELEKTOM USWY 8N 15221/2 £100

B&K LEVEL RECORDER. Type 2304 £50

RACAL HF SELECTIVE ANALYSER. Type 9056. £375

SCHLUMBERGER AUTO COUNTER. Type FB2602. £150

MARCONI F.E.T. MULTIMETER. Type TF2650 (new) £95

LEVELL MULTIMETER. Type TM111 £50

ICE MULTIMETER SUPERTESTER 680R E15

MARCONI SIGNAL GENERATOR. Type TF144H £225

MARCONI SIGNAL GENERATOR. Type TF801D/1/S £195

MARCONI UNIVERSAL BRIDGE. Type TF1313 £250

RACAL SIGNAL GENERATOR. Type 365A, 1 to 320MHZ AM/FM £175

R&S Z-g DIAGRAM RM3662 300-2400MHZ E85

R&S POLYSEKOP 1 SWOB 42/50 £350

WAYNE KERR COMPONENT BRIDGE. CT375 (B521) £75

R&S UNBALANCED STANDARD ATTENUATOR 500HM. BN18942/50 £45

STODDART AIRCRAFT Radio Interference and Field Intensity Meter. type NM-52A 375-1000MHZ (2 pieces) £325

MARCONI SIGNAL GENERATOR. Type TF801B £85

R&S DIRECT CAPACITANCE METER E50

B&K HETERODYNE VOLTMETER (RECEIVER) Type 2005 £250

MARCONI VARIABLE ATTENUATOR. TF1073A/25 £45

MARCONI DOUBLE PULSE GENERATOR. Type TF1400/S £50

RADIOMETER (COPENHAGEN) WAVE ANALYSER. Type FRA 2CT3a £50

SOLARTRON DIGITAL VOLTMETER. Type LM1867 £75

HEWLETT PACKARD DIGITAL RECORDER. Type 5050B £50

HATHFIELD PHOPHOMETER. Type DRG 657167A £50

ADVANCE DUAL STABILISED D.C. SUPPLY PP3. 0-30V 1A £25

PICTURE MONITOR MOODER PM-527 (Sim screen) As new £55

HEWLETT PACKARD POWER SUPPLY 6214A. 0-12V; 0-1.2A, new, boxed. £85.

H.P. DC POWER SUPPLY 6209B 0-320V, 0-0.1A, new boxed. £140

T.O.A. ELECTRONICS LTD Electronic Polyrecorder EPR-2T. Mains £120

THE JAMES KING COMPANY FB-1100T FREQUENCY STANDARD E50

MARCONI CARRIER DEVIATION METER. Type TF591D £50

SOLARTRON PULSE GENERATOR. Type G01101. 2 £40

MI SANDERS LEVELLING AMPLIFIER. Type 6587 £175

SCOPEX OSCILLOSCOPE. Type 4010 DB 10MHZ £170

ADVANCE OSCILLOSCOPE. Type OS240 DB 10MHZ £175

COSSOR OSCILLOSCOPE. Type CDU150 DB 35MHZ £225

TELEQUIPMENT OSCILLOSCOPE. Type D61 DB 10MHZ £195

HEWLETT PACKARD OSCILLOSCOPE. Type 120B X-Y. From £85

FLUKE DIFFERENTIAL AC/DC VOLTMETER. Model 832A £60

ADVANCE AUDIO SIGNAL GENERATOR. Type H1. Sine/Square £25

R & S TUNABLE INDICATING AMP. BN 12121/2 45-600MHZ £100

MURHEAD WAVE ANALYSER 30-31HZ E50

HEWLETT PACKARD DIGITAL VOLTMETER. Type 3460B £75

WAYNE KERR THERMOMETER. Type LT100 with probe. £50

HATHFIELD RADIO FREQUENCY BRIDGE. Type LE300A/1. £50

SOLARTRON OSCILLOSCOPE. Type CD1400. DB 15MHZ. From £75

HAMEG OSCILLOSCOPE. Type HM412. £250

KNIGHT RF SIG. GEN. KG685 with Sweep Marker Gen. KG687. The Pair £100.

H.P. MEMORY DISPLAY 5480B with 5486A Control TB and 5488A Y System. £275

H.P. MEMORY DISPLAY 5480A with 5486A Control TB and 5485A two channel input. £225.

R&S UHF TEST RECEIVER 0.9-2.7GHz BN1524 £160

EDDYSTONE RECEIVER. Type 9905 25.0-850MHZ. £450

R&S UHF TEST RECEIVER. BN1523 280-940 MHZ. £120

KETHLEY REGULATED HIGH VOLTAGE SUPPLY. Type 241. £250

HEWLETT PACKARD D.C. CURRENT SOURCE. Type 6181B £175

MARCONI XY MEMORY Type TK2214. £140

R&S UHF SIGNAL GENERATOR. BN41022 300-1000MHZ. £80

GPO DATAL TESTER NO C. £100

LEVELL BROADBAND VOLTMETER. Type TM68B. £40.

DAWE AF ANALYSER. Type 1461A. £30

R&S UHF/VHF FREQUENCY METER. BN442 30-3000MHZ £60

R&S UHF MILLIVOLTMETER. BN1091. £70

GERROLD SWEEP FREQUENCY GENERATOR. Model 602 £40

TELEONIC SWEEP GENERATOR. Type SD 3 450-900 MHZ. £75.

H.P. VHF SIGNAL GENERATOR. Type 608D. Case damaged hence £50

MARCONI VALVE VOLTMETER. Type TF1300. £15

SOLARTRON DIGITAL VOLTMETER. Type LM1420. 2. £30

VIDEO CIRCUITS LTD TUBE TESTER. Type V33. £30

LARGE AREA COLOURMATCH 825 PATTERN GENERATOR. Type CM6004. Pp. £20

H. K. BEAT FREQUENCY OSCILLATOR. Type 1014 £175

ADVANCE OSCILLOSCOPE. Type OS1000A. DB 20MHZ. £300

PLEASE CHECK AVAILABILITY BEFORE ORDERING.

FERRET A.T.E.
£650
Phone for details

EDDYSTONE RECEIVERS
Model 770R-AM/FM
£95 each
Model 770R Mk II
£150 each

INFRA RED IMAGE CONVERTER Type 9606 (CV 144)
1 3/4in diameter. Requires single low current 3KV to 6KV supply individually boxed. With data.
£12.50 each
Infra Red Lamps also advertised

VARIAN RUBIDIUM STANDARD Model R20
5mhz, 1mhz, 0.1mhz
£600

EX-MINISTRY SOLID STATE 400 HZ INVERTOR
28 VDC input, 115V output. Size 7 x 2 1/2 x 1 1/2in approx. Connection details supplied.
£18 each. P&P £2

TRANSISTOR INVERTOR
115V AC 1.7 Amp input. Switching is at 20KHz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied.
£1.25 each. P&P £2.

CONVERT THIS UNIT TO A

SUPER BATTERY CHARGER
Attractive green ministry quality case with removable top and bottom panels — heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for **£3.50** P&P £2. Four units £12. Carriage £5.

STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a tachometer. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p
or 5 for **£5 P&P £1.50**.

STEPPING MOTORS

200 Steps. 20 oz/in. torque. 12/24 volt input 4-wire.
£12 each. P&P £1.50

KEYBOARD PAD

Size 3x2 1/2x2 1/2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.
£4 each. P&P £1. or 5 for **£15 P&P £2.**

MINIATURE KEYBOARD

Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 each.**

CRYSTALS 50p each.
Flat metal case — 19 2KHZ. 844.9KHZ. BTG — 10MHZ.

LOUDHAILERS. Transistorised hand-held, no leads. Standard internal batteries supplied. Howl Switch **£20** each. P&P £2

INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 1 3/8" x 1/2" dia. **£1.50** each. 240V 1650 Watts. Size 2 2/8" x 1/2" dia. **£3** each.

BRIDGE RECTIFIER. 2 Amp 50p each.

PHOTODIODE DETECTOR 4" fly leads. **25p** each.

AMPHENOL. 17-way chassis mount edge connectors 0-1 spacing. **15p** each.

E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) **60p** each.

FANS. 115V 13 Watts. Size 3/4 x 3/4 x 1/2" BRAND NEW. **£4.50** each. Secondhand **£2.50** each.

DELAY LINE. 50 nanoseconds. 3 connections — ground-in-out Size 2 x 7/16 x 5/16" New **25p** each.

MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New **£1** each.

LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. **15p** each.

DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New **10p** each. 100 for **£7.50**

SOME TEKTRONIX 500 RANGE OSCILLOSCOPES
with Single Trace Plug-ins. Working.
From **£100.** Phone for details

DIODES
All new full spec. devices IN3063
BAX 13. 1544. 1N4148;
1N3470; 1N4151.
100 off **£1.50.** 1,000 off **£10**

PULSE TRANSFORMER. Sub minf Size 1/2 x 5/16 x 1/4"
Secondary centre tapped. New **20p** each.

REMO TV TUBE MULTIPLIER. Two high voltage outputs and focus. **£1** each.

DON'T TAKE CHANCES. Use the proper EHT CABLE. **10p** per metre or **£7.50** per 100 metres/drum. P&P £2

PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap **75p** each. Box of 12 **£5.50.** P&P £1.50.

RAPID DISCHARGE CAPACITORS Bmf4d 4kV E5 each. P&P £2.

MYSTERY IC PACK. Some 40 pin — good mixture — all new devices. **25 ICs for £1.** P&P 50p

DECOUPLING CAPACITORS
0.05mfd 10V. 0.01mfd. 0.047mfd 250V. 33K. 330pf. All values 100 for **£1.80.**

E.N.T. Capacitor 500pf 8KV 20p each.

10-way MULTI COLOUR RIBBON CABLE. New **40p** per metre. 10 metres for **£3.**

CEC UHF 4-button tuner **£1.50** each.

CENTAUR 115V FANS 4 1/4 x 1 1/2" **£4.50** each.

EX-USED equipment. tested. **60p** each.

CONTACTORS. Heavy Duty 24V DC 5 make **£1** each.

CEC UHF/VHF 6-button tuner **£2** each.

931A PHOTO MULTIPLIER E2 each. P&P £1.

RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degree **£2.50** each.

SOLID STATE UHF TUNERS. 30 acc **£1** each.

BRAND REX blue wire wraps. 30 metres for **£1.** P&P 25p.

SLIDER CONTROL 500K Log. Single track. Complete with knob. Length 3 1/2" **25p** each.

TRANSFORMERS
TYPE 240V input 115V 1 Amp output **£1.25** each. P&P £1.25

240V input. Soc. 6V 1.86A. Size 2 1/2 x 2 x 2". Good quality. **£1.50** each. P&P £1.

240V input. Soc. 12V D.92A. Size 2 1/2 x 2 x 2". Good quality. **£1.50** each. P&P £1.

240V input. Soc. 12V 100V. Size 60 x 40 x 42mm. **50p** each.

240V input. Soc. 12-0-12V 50MA. Size 53 x 45 x 40mm. **£1** each.

115V input. Soc. 5V 250MA. Size 1 1/8 x 1 1/2 x 1 1/4". **2 for 50p.**

115V input. Soc. 10-0-10V1A. Size 2 1/2 x 2 x 2". **2 for £1.50.**

SEMICONDUCATORS
1N4005 — 5p; 1N4002 — 3p.

At 5p each:
BC147, BC148B, BC157, BC158, BC237, BF197, OA90, OA81, BA154, BA243.

At 25p each:
TIP31, TIP41A, 2N5696, AF139, 2TX34
BY127 10p; BF181 20p; BD239 49p; BD241 40p; MA343AT 49p; BD228 80p; BD233 & BD234 Comp Pair 25W — **80p** per pair. at 50p each.

REGULATOR TBA625 8to 20V in — 5V out 100MA **T05** Con. 50p each BF256C 20p.

TV AMPLIFIER TBA 120 20p each.

Integrated Circuits

7453	5p	74511	7p	75325	£1
7451	5p	74538	10p	SN15862	4p
7402	12p	74502	12p	MC4028	60p
7476	20p	74154	7p	7417	14p
7495	35p	74C02	16p	74C86	50p
74122	12p	74C03	16p	74C161	24p
74C01	17p	74C74	16p		

MOTOROLA DUAL in Line 6 pin Opto Coupler **30p** each. Gold plate tester version **50p** each.

EPROMS 2708 **£5.50** each.

SMITHS encapsulated transistorised **AUDIBLE WARNING DEVICES 4V 12V.** Can be driven from TTL **85p** each.

ELECTROSTATIC VOLTMETER. 7.5KV **£5** each. P&P £1.50. Other ranges available in plastic enclosure.

TRIMMERS. Sub min 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. **AH** at 6p each.

HONEYWELL humidity controllers **50p** each.

THYRISTOR TIMER. Solid State 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay **50p** each.

MINIATURE PC MOUNT SLIDE SWITCH. 2 pole 2 way **10p** each.

4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits. Good brilliance at 1.5V. 15 connections **£2.50** each. Some E.H.T. Transformers and Capacitors available. Please enquire.

TELEPHONES 706 style black; grey or blue **£5.50** each. 74b style black or grey **£7.50**. Older style black **£2.50** each. Discoloured grey 706 **£4** each P&P **£1.50** per telephone.

DC SERVO MOTOR 110V 2.5Amp continuous. Double shaft. Brand new 4 wire 4 brush **£25** each. Plus carriage.

PC Mount POTS. Wire wound with knob 200ohm & 10ohm. **10p** each.

MIN. RELAY 24V. 2 pole c/o. Brand new. **75p** each.

TIME DELAY RELAY 0.1 to 10secs. 115V AC. DPDT. **£5** each.

CAPACITORS at 5p each. 0.1uf 400V. Small rec. block PC Mount German class. 3300pf. 220nF250V; 0.01mfd 160V

INSERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brand new wrapped **75p** each. or 10 for **£6.**

TOROIDAL TRANSFORMERS. Input 0-120-240 Volts. Output 0-12V. 0-12V 10VA per winding. Encapsulated — identical to R.S. Components at **£3.90.** OUR SPECIAL PRICE **£5** each. P&P **£1.50.**

TANTALUM CAPACITORS — All at 10p each — 100 off **£7.50.** 22mfd 6V 39mfd 10V. 22mfd 35V. 1mfd 35V

MINIATURE SLIDE SWITCHES. Single pole 2 way **10p** each. 10 off **90p**

HEAVY DUTY RHEOSTAT. 7.5ohm 5.5Amp. Diameter 5". Standard 1/2" shaft **£2.50** each. P&P **£1.50.**


LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or 500 ohm. Tested. **£25** each or 5 for **£100.**

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM VAT £1.50 — where P&P not stated please use own discretion — excess refunded.
£5 CARRIAGE ON ALL UNITS. P&P OR CARRIAGE AND VAT at 15% on total MUST BE ADDED TO ALL ORDERS.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

SHILTHHEAD LTD

NORWOOD ROAD, READING **TELEPHONE NO. READING 669656**
(2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel")

AUDIOPHILE

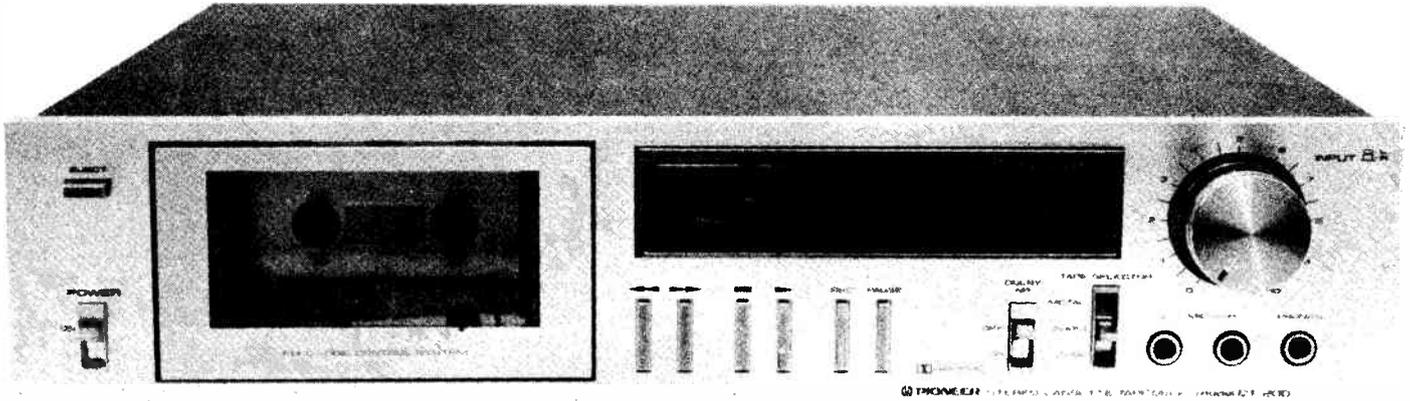

Yes, you read it right. . . Audiophile is back! Ron Harris takes pen in hand again to review a couple of Pioneer tape decks, and enthuses over some old friends.

Right. Put down the trannie radios, pack away the pine needles — Audiophile has returned! That man at the back with the yellow handbag who whispered "Oh gawd, not again" can leave now of his own accord, or be carried out later when the boys get round to landscape his anatomy.

To all my regulars who sorely missed these pages and who wept and wailed their grief to the dawn — thank you. To any tasteless cloth-eared ingrate who thinks I should have stayed away — read on, read on, there is yet hope and charity for such as ye in the halls of the righteous! (ie here. . .).

For my return trick, I'm taking a look at two tape machines from Pioneer's cassette deck range, one from each end: the CTF-1250, which is their flagship design, and the CT-200, an interesting new release at the budget end of the price scale. Thus we shall be all things to all men. . . I think.


Tape For All Seasons

The new CT-200 is a basic, no-nonsense machine intended mainly for the first time hi-fi man who doesn't wish to have to upgrade again in a hurry. It is compact and sports little in the way of excess controls. Normal VU meters are fitted, with no peak indicators. Logic control is employed for the tape transport mechanism and, strangely, Pioneer have opted for captive phono leads on the input/output connectors. Surely a yard of screened lead and a phono plug can't cost less than a plain ordinary panel socket?

Apart from this the CT-200 is distinguished only by its normality! There are no frills and no gimmicks at all. The controls worked impeccably at all times and the meters were fast enough to give reliable results when recording.



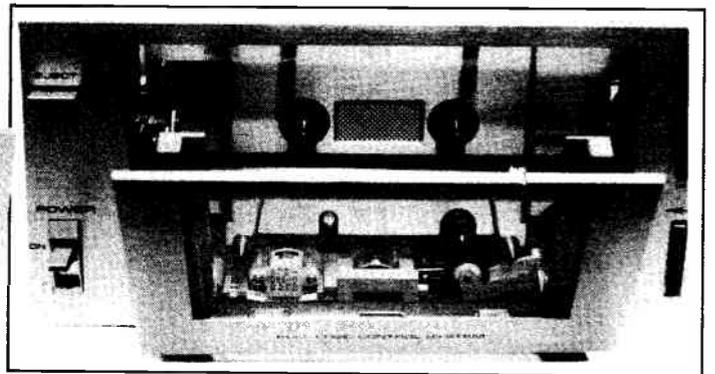As you can see from this detail of the control section of the CT-200, Pioneer have kept it simple. The meters are conventional VU, with no peak indicators, but this should not deter an intended purchase, as they are still pretty good at their jobs! Transport controls are solenoid operated, a plus point at the price.



Unusual is the way in which virtually a whole section of the front panel unhinges to accept a cassette. Can be a little un-nerving the first time, you think something somewhere has dropped off, if you'll pardon the expression!

The heads are easily accessed for cleaning.

The one minor annoyance was the switching 'thump' generated whenever the mains power was interrupted. A small thing, but one which Pioneer should attend to, ASAP.

Resulting Tests

The test bench brought forth no gremlins from the design and a scrutiny of the results will show that good figures were returned on all counts. The signal-to-noise and metal tape figures are particularly impressive for a machine in this price bracket.

Sensitivity was slightly below the spec., at about 80 mV, but this is still a very reasonable figure and one that, together with the input impedance of 90k, should ensure that the CT-200 will work happily with the majority of amplifiers.

Wow and flutter is very well controlled and proved unobtrusive in use. All in all the machine gave a surprisingly good account of itself under test and one which does it credit at the price.

Frequency response : LH tape :-	25 Hz — 14 kHz ± 4 dB
(-20 dB)	CrO ₂ :- 25 Hz — 17 kHz ± 3 dB
	Metal :- 25 Hz — 18 kHz ± 2 dB
	FeCr :- 25 Hz — 18 kHz ± 3 dB
Signal-to-noise Ratio :-	-65 dB
(best result, Dolby on)	
Wow and Flutter :	DIN :- ±0.15%
	WRMS :- ±0.05%
Harmonic Distortion :-	1.2% (0 dB)
Line Sensitivity :-	80 mV
Input Impedance :-	90k

Table 1 — Test Results CT-200

Auditioning

Having duly done my duty with the meters and measures, it was down to the nice part of the job — settling back in a chair and listening to the deck playing coherent music as opposed to all those monotonous tones. Again the CT-200 provided a surprise — put simply, it sounded better than I suppose I'd expected. The sound was clean and sharp, with little trace of the

old 'cassette sound' that was so immediately recognisable a couple of years back. The machine was always detectable against a reference, as would be expected for a £100 deck, but was never anything less than satisfying to listen to.

Overall it represents very good value for money and can be thoroughly recommended. It just goes to show how far budget hi-fi — and tape in particular — has come of late.

Battleship Engineering

The CTF-1250 is a massive machine which is some 16½ x 7½ x 14½ inches in size, and 26 lb in weight. Once more into the truss dear friends, or block up the living room with tape deck...

For all that, the front panel is tightly packed with controls, buttons and things that glow in the night. There is even a control to turn down the brightness of the fluorescent display, lest its brilliance offend thee.

Basically the machine is possessed of full tape optimisation facilities, a digital tape counter, full logic controls which can be operated from the counter, and peak reading meters which can be set to one of three modes.

Rather than waste an issue describing it all in a thousand words, take a look at the photo and diagram, the caption to which should explain the myriad machinations of the machine.


Results Of A Test

Table 2 gives a brief extract from the test results, in a form which can be compared to those for the CT-200. As you can see, there is not the difference you may expect, considering how many more bits of green paper are required to obtain the 1250. Those buttons cost money.


All results are given with the machine optimised for the tape in use. With the system employed here, such a set-up is easy and certainly yields improved results for relatively little effort. The figures are generally 'good' for a cassette deck but are nothing outstanding by any means. The CTF-1250 turned in solid, repeatable performance on all the important parameters.

Listening In

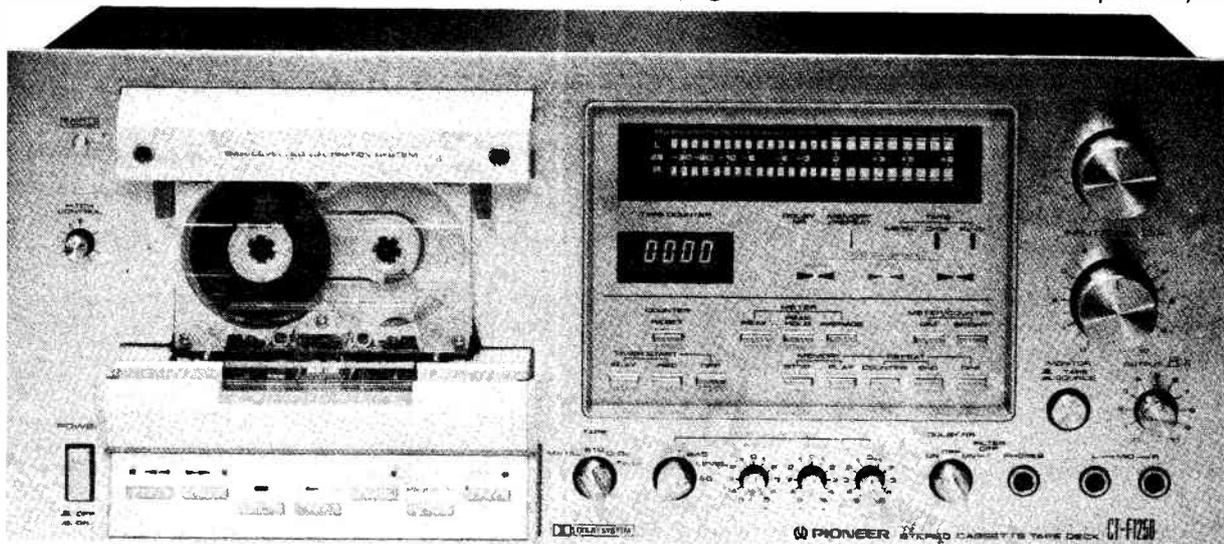Under audition the 1250 proved a difficult machine to live with. No insult intended, it was just well-nigh impossible to stop playing with the controls and *listen* to it! In practice, once a par-



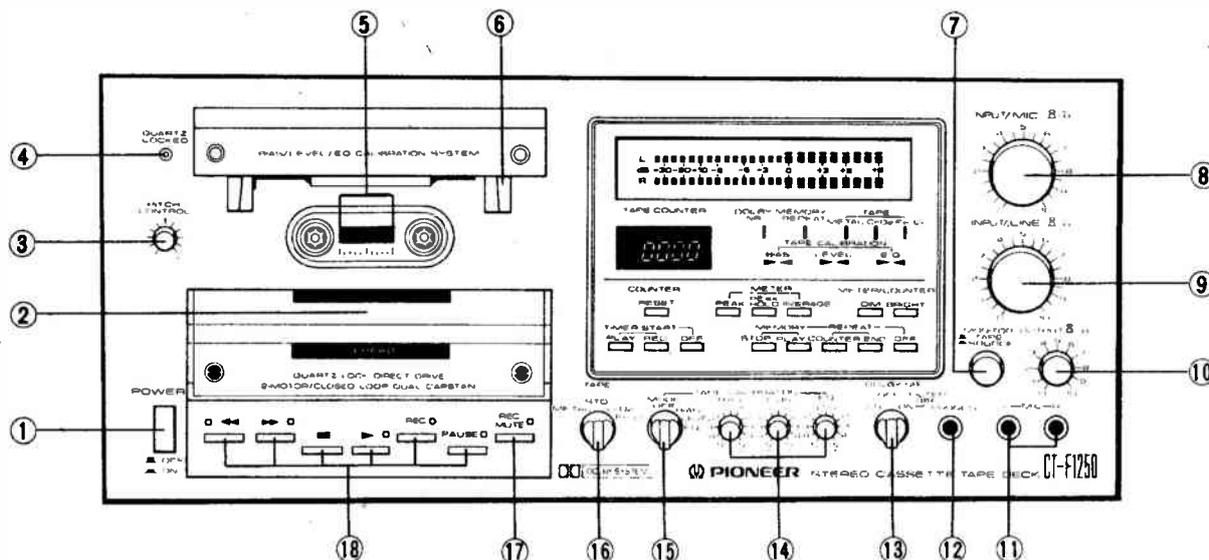The exact opposite of the CT-200 in every way! This is the daunting 1250, Pioneer's tape flagship. Those impressive meters have three modes of operation, peak reading or hold and average.



Rather than attempt to describe the 1250, I've taken the visual approach and stolen this illustration from the Pioneer handbook!

- 1) Mains Power: One fault here is that it is not 'de-thumped'.
- 2) Dust Cover: fits over the heads which would otherwise be very vulnerable. A nice touch this.
- 3) Pitch Control: yes, that's right the speed is quartz locked and can be varied if required.
- 4) PLL Indicator: activates when speed is correctly set.
- 5) Remaining Tape Markers: just the usual backlight to show how much tape is left.
- 6) Tape Guide: accurately machined guide paths to make sure you put the cassette in straight.
- 7) Monitor: standard stuff for a 3-head design, chooses tape or source.
- 8) Mic Level: ganged input control for the front panel jacks.
- 9) Line Input: ditto for the two inputs on the rear panel. Friction linking is a little too strong!
- 10) Output Level: click stopped at 0 dB.
- 11) Mic Inputs: 1/4" jack sockets.
- 12) Headphone Output: provides a healthy output to drive a pair of dynamic phones.
- 13) Dolby Filter: allows use of the NR with/without MPX filtering.
- 14) Tape Calibration: just set the Mode switch to required parameter and adjust the appropriate control until the calibration lights indicate purity. Simple and efficient.
- 15) Mode Control: used with 14.
- 16) Tape Selector: standard choice of four tape types.
- 17) Record Mute: useful for killing ads. when taping from radio etc.
- 18) Solenoid Controls: all transport controls are logic locked and virtually idiot-proof.

ticular brand of tape has been settled on, and the control settings noted, there is little reason to fiddle around at all.

The metering is superb and about the most useful I've encountered anywhere. The sound quality is, again, good, but not as good as can be obtained elsewhere for £450. Some sacrifice has to be made if you want to buy all those lovely facilities.

Best results — regardless of optimisation, strangely enough — were obtained with Maxell tapes and in particular the UDX-II. Sony Metal came a close second, which although providing a cleaner result, showed some signs of treble lift whatever I did to the optimiser.

Frequency response : LH :-	25 Hz — 15 kHz ± 3 dB
(- 20 dB)	CrO ₂ :- 25 Hz — 17 kHz ± 3 dB
	Metal :- 25 Hz — 19 kHz ± 3 dB
	FeCr :- 25 Hz — 16 kHz ± 3 dB
Signal-to-noise Ratio :-	- 66 dB
(best result, Dolby on)	
Wow and Flutter :	DIN :- 0.1%
	WRMS :- 0.03%
Harmonic Distortion :-	0.9% (0 dB)
Line Sensitivity :-	60 mV
Input Impedance :-	50k

Table 2 — Test Results CTF-1250

Sum Summary

Adding it all up, the CTF-1250 comes out as a very crafty compromise; one that will appeal to many. Its sound is not of the ultimate quality, but its facilities and versatility are second to none.

The CT-200 is a well-conceived and well-executed budget deck that offers excellent value for money and an outstanding sound quality for the class.

Audio Updates

At present I'm working on a feature called 'Sonic Holography' for next month's ETI — and if you don't know what that is (S.H. not ETI!) then you're gonna have to buy our next issue, 'cos I ain't gonna tell you now — as part of which I've had the chance to renew my acquaintance with the Gale loudspeakers. I thought that since such opportunities occur but rarely, I'd drop the reader's letters and ramble on about them for a while instead.


Any Port In A Gale?

Few products, especially loudspeakers, can claim to have stood the ravages of time and changing tastes as successfully as the Gale GS401. It is now many years since Ian Gale first unleashed his chrome-end, unconventionally horizontal transducer upon the ears of the world and, if anything, its standing has risen with the passing of the summers.

Infinite baffle enclosure (330 x 605 x 270 mm)
Four unit design (2 x 200 mm; 1 x 100 mm; 1 x 19 mm dome)
Crossover frequency : 475 Hz and 5 kHz
Efficiency : 20 W produces 96 dB at 1 m
Power handling : 40 W — 200 W RMS per channel into 8R amplifiers recommended
Fuse-protected against overload

Table 3 — Specification of Gale GS401A

FEATURE : Audiophile

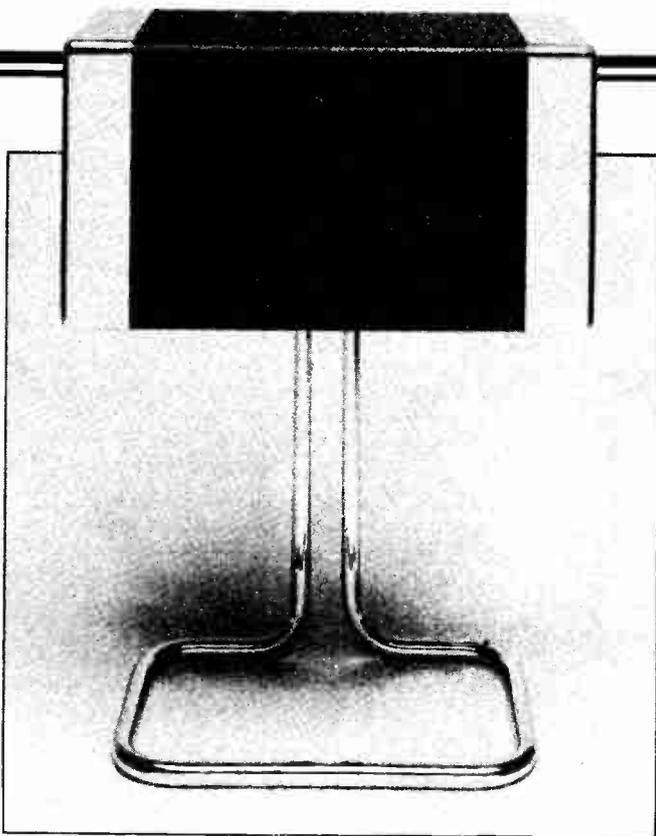

Above: the imposing Gale 401, in chrome livery. The stands are also available in a black finish and personally I prefer it that way!

It is basically a four unit, infinite baffle (sealed box) design of prodigious power handling and excellent imaging. Long before 'phase linearity' gathered unto itself the role of buzzword, the Gales were presenting an essentially phase stable performance, witnessed by the incredible square wave performance. This is one of the few loudspeakers through which such a signal may pass and emerge with some semblance of accuracy.

I had the Gales at home for a period of some weeks and grew to appreciate their virtues more with time. Comparing them to my usual reference — the KEF 105 II — they have a relatively similar approach to music. The 105 has a better defined bass register and a more transparent treble, but the Gales run them mighty close indeed — and at half the price!

Anyone who is about to spread over £400 on the counter for a pair of speakers would be well advised to hold onto the cash until he'd given the 401s a chance to show what they can do. They are more room dependent than most transducers in this league and less coloured than any when set up correctly. Still an outstanding design then, and a lasting credit to their designer.

Trailer

Next month it's back to pickups for a trio of moving coils from Mayware, Ultimo, and Ortofon. I'll also be putting down some words on a new Japanese speaker (shock horror...), the Mitsubishi DS-32B which has been specially designed for non-oriental ears.

ETI

— CLEF KITS —

MASTER RHYTHM

As published in Practical Electronics



KIT. — £79. BUILT — £114

FULLY PROGRAMMABLE TWENTY-FOUR PATTERNS

EIGHT PARALLEL TRACKS

TWELVE INSTRUMENTS

SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

PIANOS

SPECIALISTS SINCE 1972
STAGE & DOMESTIC TYPES



The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

See lists for Cabinets, P.A. & Manufacture.

SIX OCTAVES £207
7½ OCTAVES £232

STRINGS £169

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch plus two-phase Chorus.

ROTOR-CHORUS £89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" p.c.b. Mains P.S.U. included.

KEYBOARDS

Square Front with two hole actuator—easily cut.

49 NOTE—£25; 73 NOTE— £39
88 NOTE—£47

OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates — in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

CLEF PRODUCTS (ELECTRONICS) LIMITED. (Dopt. E.T.T.)

44A BRAMHALL LANE SOUTH, BRAMHALL, STOCKPORT, CHESHIRE SK7 1AH. 061-439 3297

ELECTRONIC IGNITION SAVES PETROL

More and more new cars use electronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.



TOTAL ENERGY DISCHARGE gives all the advantages of the best capacitive discharge ignitions.

- ★ **Peak Performance**—higher output voltage.
- ★ **Improved Economy**—consistent high ignition performance.
- ★ **Better Starting**—full spark power even with low battery.
- ★ **Accurate Timing**—prevents contact wear without 'contactless' errors.
- ★ **Smooth Performance**—immune to contact bounce effects.

PLUS

- SUPER HIGH POWER SPARK**—3½ times the energy of ordinary C.D. systems.
- OPTIMUM SPARK DURATION**—to get the very best performance and economy with today's lean carburettor settings.
- DESIGNED IN RELIABILITY**—with the 'ultimate insurance' of a changeover switch to revert instantly to standard ignition.

TECHNICAL DETAILS

HIGH EFFICIENCY INVERTER. A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4 volts.

SUPERB DISCHARGE CIRCUIT. A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the H.T. system.

SOPHISTICATED TRIGGER CIRCUIT. This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

IN MONEY-SAVING KIT FORM at £14.85 Inc. V.A.T. and P. & P.


All you need is a small soldering iron and a few basic tools — everything else is supplied with easy-to-follow instructions.

FITS ALL 6 / 12-volt NEGATIVE EARTH cars
ELECTRONIZE DESIGN
2 Hillside Road, Four Oaks
Sutton Coldfield, West Midlands, B74 4DQ
Phone 021-308 5877

RADIATION DETECTORS

BE PREPARED WITH THIS DETECTOR

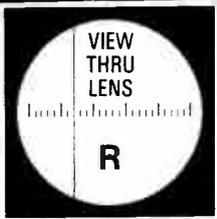Recommended for General use.
CIVIL DEFENCE ● FIRE SERVICES ● MEDICAL



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS.
- UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.
- PRECISION INSTRUMENT, METAL CASED, WEIGHT 2oz.
- CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION.
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

COMPLETE WITH DATA

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.


Standard model 0-5 or 0-50R ONLY

£6.95 inc. VAT
Post & Packing 60p

Be prepared, buy whilst available.

HENRY'S

404 EDGWARE ROAD, LONDON W2 1ED

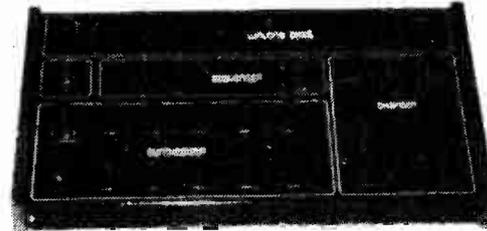

GUITAR
• SYNTH •
KIT.
£199.50

A stunning new concept. Play synthesiser from guitar or virtually any other instrument with no multicore lead problems. Chords, Walking Bass & Sequencer are all programmable by the instrument. Just send £3.60 Cheque or P.O. & we will return the complete description & plans, along with a £3.00 credit voucher to be used with any purchase over £20.00.
2 ARDEN COURT, CHURCH ROAD, CAMPBELL CLARK CABINETS PERRY BARR, BIRMINGHAM. B42 1LF

TV SOUND TUNER ETI SEP 80 PROJECT

All parts available / send for list
ALSO
No. 1 for Teletext Kits
TV Spare Parts and Components

Callers welcome at Shop Premises
MANOR SUPPLIES
172 WEST END LANE, LONDON NW6 1SD
TELEPHONE: 01-794 8751
Near West Hampstead Jubilee & British Rail Stations

TTL CMOS 74LS LEDs

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE
UXBRIDGE 55399

SUPERSALE '81
All full spec. 2114 (450ns) £1.85, p&p 35p. 2708 £2.00 p&p 35p. TEXAS INSTRUMENTS 2716 single rail, full spec. £5.95.

NEW FREEDOM PHONE
The completely portable telephone with intercom and beep paging facility. Range 200 yards £125 + VAT p&p £3.00. Leaflet available on request (not PO). HO certified)

MK 1002P (dual 128 bit Shift Reg) 35p.
LM711CH (Voltage Comparator) 30p.
(All Full Spec)
2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 35p
MM5240 AA/J Character Generator £3.50 + data. p/p 35p.
LEAR SIEGLER dot matrix print head 7 needle £19.50 p/p 50p
ZETTLER low profile PCB relay 30mm x 36mm 4 8/6 9v d.c. 2/2 5 amps a.c. contacts. 85p p/p 35p.

D TYPE CONNECTORS
9 Way sockets (solder) 55p.
15 Way wirewrap plugs only 75p.
50 Way skt (wirewrap) £1.65.
50 Way skt £1.45, p&p 25p.
25 Way Male to Female with covers plus minimum 1 metre of cable (12 way) £4.00 each p/p 35p.
25 Way plug (solder), 25 Way socket £1.20 each.

COVERS
37 Way 90p (plastic), p&p 35p.
9 Way (metal) 60p, 15 Way (metal) 75p, 25 Way (plastic) 65p.
37 Way reduced from 90p to 80p.
50 Way (plastic) 90p.

DISPLAYS
HP 5082 4 digit DIL display full spec £1.50 each, p&p 35p Large quantities POA.
LED 3 Digit DIL 55p, p&p 35p
Bowmar 9 digit 1 in LED with red bezel. (As used in calculators) £1.00 + 35p p&p

SUPERSAVER 1
Ribbon Cable Headers 16 DIL Jernyn, gold plated, with cover 45p, p&p 25p
Ansley Header plugs. PCB mounting. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing type), p/p 35p.
Ansley I/O Header plugs. 1in 26 Way 65p, 26 Way (right-angled) 85p, 40 Way £1.00 p/p 35p.

SUPERSAVER 2
Tantalum Capacitors 25 volt. 4.7 uF. 14 for £1.00, p&p 35p.

SUPERSAVER 3
PRICE SMASH FND 500 5in. LED displays, full spec 50p each, p&p 35p, large quantities POA.

SUPERSAVER 5
Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.

SUPERSAVER 6
EAO KEY SWITCH oblong fascia. 25mm x 18mm (approx. 18mm hole, fixing supplied, brand new with 2 keys. £2.95 p&p 35p.

SUPERSAVER 7
SN74116 Dual 4 Bit latch 75p, p&p 35p
SN74118 Arithmetic Logic Unit, 80p, p&p 35p.
SN74194 4 Bit Register. 50p p&p 35p
SN74198 8 Bit Shift Register. 75p p&p 35p.

SUPERSAVER 8
ITT Act 250b brand new full spec £7.50 each p&p 35p

SUPERSAVER 9
5 digit 7 segment DIL LED 11" displays 4 for £1.50 p/p 35p.

SUPERSAVER 10
9 way male/female connector, ELCO B129. 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value. 35p, p&p 35p.

SUPERSAVER 11
74LS266 50p. 74LS245 £2.40. 74LS240 £1.00. 74S260 35p. P&P on all above 35p.

SUPERSAVER 12
TMS 3128NC Static shift register, £1.50, p&p 35p.

SUPERSAVER 14
Recording Designs Ltd digital cassette deck 50-100 Baud RS232 240V input. A professional superb deck £48.00, p&p £2.00.

SUPERSAVER 15
5K 1/2" multitrack trim pots, PCB mounting, per box of 14 £2.50, p&p 35p.

SUPERSAVER 16
OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1.00, p&p 3 p.

LEDs (Full spec.)
TIL209, red 10p. 0.2in, red 12p. 0.2in green 28p. 0.2in, yellow 28p.
RL54 red Axial lead. 15p.
P&P on all above 35p.
VERNITRON Ceramic filters type FM4 10 yMHz 45p, p&p 35p.
TRANSISTORS, 8D236 40p, 8C183L 10p, BF195 10p,
TBA 810S, with data. 85p, 4-way DIL switches. 75p. MC1303 Dual Stereo preamp with data, £1.25. 7in. Nylon cable ties 100 for £1.50. All p&p 35p.

TMS 4030, 4096 x 1 dynamic RAM 2000 ns removed from PCBs. £1.00 each. 16 for £25, p&p 35p

PCB KEYBOARD, 65mm x 82mm, 18 key Clickers less Key tops, ideal Hexadecimal use 35p, p&p 35p

CAPACITOR SCOOP. 1.600uF at 10v. 160uF at 25v. Axial lead. 2 dozen for £1 + 35p p&p

DON'T KILL YOUR EPROMS.
Augat 24 Way low profile socket. Solid gold pins. A superb socket. Leave your eproms in them for programming or usage to prevent breaking off pins. Only 40p each, p&p 35p.

GIVEAWAY
18 pin low profile dié socket 13p EACH or 8 for £1.00 p&p 35p

Just arrived. ITT 2082 Data Modem. Brand new and boxed, with manual. 600/1200 Baud. Data Modem to CC ITT. V24/RS232C. Channel centre frequencies 1300 and 1700Hz. (600 Baud) or 1300 and 2100Hz (1200 Baud). Synchronous or asynchronous operation over 2 or 4 wire, switch or dedicated lines, built in self and lines test functions. Some of the best equipment we have ever obtained. £115.00 each, p&p £3.00. (Fraction of original cost).

IC HOLDERS (Low-profile)
8 DIL 12p 14 DIL 15p
16 DIL 17p 18 DIL 20p
22 DIL 28p 24 DIL 35p
28 DIL 45p All p&p 35p.

WE STOCK a vast range of TTL, CMOS, some 74LS MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

RELAYS
Banor resettable double pole changeover 12V £1. Both p&p 35p.

JUST ARRIVED - PCB 008 OSCILLATOR Containing 1 NPN transistor, 1 resistor, 1 transformer and PP3 battery connector. 30mm x 20mm (approx) 35p each. 5 for £1, p/p 35p. **PCB 009 1 x CD4069, 1 x CD4011, 5 transistors, 7 capacitors, 12 resistors, 1 diode, 45mm x 55mm (approx). 45p each p/p 35p.**

CENTRONICS 101A Dot Matrix printer. Fully overhauled. 165 char/sec. £450.00 inc. VAT. Carriage at cost. As above dual headed 300 char/sec £650 inc. VAT.

C.P.U. TYPE 10660. These devices are brand new, supplied with data sheet for experimental use 4 for £1, p&p 35p.

ICL POWER SUPPLY (exchange units) 240V AC input. Output +24V at 2 amps DC, -24V at 2 amps DC (adjustable to 12V) +5V at 4 amps DC -100V DC and 6.3V AC. £10.50.

Terms cash with order (official orders welcomed from colleges, etc) All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

FOR THE PROFESSIONAL USER. CP Clare Keyboard switches with buttons (blank) 65p each p&p 35p.

BURROUGHS keyboard, 96 key station. On-board crystal and TTL. Brand new and boxed. 500mm x 190mm. At the time of advert no data. No keytops at all. Clare pender. Read switches. Bargain £12.00 each, p&p £1.50.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING

SURPLUS STOCKS PURCHASED FOR CASH

LB ELECTRONICS
11 HERCIES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND
All enquiries s.a.e. please
Telephone answering machine
service out of business hours.

New retail premises, now open Mon. Tues. Thurs. Fri. and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.

ALL PRICES INCLUSIVE OF VAT

UXBRIDGE 55399
All components full spec.

Dept. ET18, Unit 9/10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165, 01-278 7369. Telex: 8953084 Maclin G.

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to ordering information before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.

NEW, LOW, LOW PRICES ON MEMORIES!!!

Compare our prices before you buy elsewhere! All devices are brand new, factory prime, full spec and fully guaranteed! All prices exclude p&p and VAT. Please refer to Ordering Information before ordering. DON'T DELAY - BUY TODAY - SUCH LOW PRICES DON'T LAST FOR EVER!

STATIC RAMS			
2114L 450 NS	1.24	25.99	100+
2114L 300 NS	195p	175p	150p
2114L 200 NS	225p	195p	175p
4118 250 NS 8K	250p	225p	195p
NEW!!!			
HM6116 16K (2K x 8)	895p	795p	695p
150 NS 24-pin NEW!!!	£19.95	£17.95	£15.95
DYNAMIC RAMS			
4116 200 NS Ceramic	195p	175p	150p

4116 150 NS	375p	350p	325p
HM4864 64K (65K x 1) 200 NS	Single + 5V supply		
16-pin NEW!!!	£29.95	£24.95	£19.95
CMOS RAMS			
5101 1K (256 x 4)			
450 NS	350p	325p	295p
4315 4K (4K x 1) 450 NS	995p		
TC5514P 4K (1K x 4)	495p	450p	395p
450 NS			
HM6116 16K (2K x 8)			
150 NS 24-pin NEW!!!	£19.95	£17.95	£15.95
EPROMS			
2708 450 NS	350p	325p	295p
2716 Single 5V 450 NS	475p	450p	395p
2532 Single 5V 450 NS	£14.95	£12.95	£11.95
2732 Intel-type 450 NS	£14.95	£12.95	£11.95
2564 64K (8K x 8) 450	£99	£95	£90
NS 28-pin			

Ordering information. Unless otherwise stated for orders under £50 add 50p p&p. Add 15% VAT to total (no VAT on books). All devices are brand new, factory prime and full spec and subject to prior sales and availability. Prices subject to change without notice. Minimum telephone order using ACCESS, is £10. If ordering by post with ACCESS, include name, address and card no. written clearly. Please allow 4/6 weeks delivery on books.



DTL

830	55p	74LS112	75p	4042	73p
935	65p	74LS123	63p	4043	86p
937	55p	74LS125	50p	4044	89p
944	65p	74LS126	50p	4045	160p
946	55p	74LS132	79p	4047	99p
947	55p	74LS138	69p	4048	56p
962	55p	74LS139	75p	4049	38p
9099	90p	74LS148	170p	4050	40p
		74LS151	75p	4051	69p
		74LS153	75p	4052	75p
		74LS155	65p	4053	73p
		74LS157	74p	4054	111p
		74LS160	115p	4055	121p
		74LS161	78p	4056	121p
		74LS163	90p	4059	560p
		74LS164	90p	4060	112p
		74LS165	150p	4063	112p
		74LS168	190p	4066	56p
		74LS173	100p	4067	422p
		74LS174	99p	4068	19p
		74LS175	99p	4069	19p
		74LS181	280p	4070	28p
		74LS190	110p	4071	25p
		74LS195	87p	4072	25p
		74LS196	100p	4075	20p
		74LS221	110p	4076	88p
		74LS240	210p	4077	23p
		74LS241	200p	4078	23p
		74LS242	220p	4081	29p
		74LS244	175p	4082	25p
		74LS245	220p	4085	86p
		74LS251	120p	4086	68p
		74LS253	120p	4089	160p
		74LS257	110p	4093	68p
		74LS260	90p	4094	225p
		74LS273	175p	4095	99p
		74LS290	95p	4096	325p
		74LS293	120p	4098	110p
		74LS366	57p	4099	180p
		74LS373	170p	4501	25p
		74LS374	170p	4502	112p
		74LS375	140p	4503	68p
		74LS393	135p	4507	52p
		74LS490	140p	4508	288p
		74LS670	260p	4510	76p

7400

7400	11p	74LS112	75p	4042	73p
7401	12p	74LS123	63p	4043	86p
7402	12p	74LS125	50p	4044	89p
7403	13p	74LS126	50p	4045	160p
7404	17p	74LS132	79p	4047	99p
7409	18p	74LS138	69p	4048	56p
7410	18p	74LS139	75p	4049	38p
7412	18p	74LS148	170p	4050	40p
7513	28p	74LS151	75p	4051	69p
7420	16p	74LS153	75p	4052	75p
7430	18p	74LS155	65p	4053	73p
7432	25p	74LS157	74p	4054	111p
7440	16p	74LS160	115p	4055	121p
7442	68p	74LS161	78p	4056	121p
7446	75p	74LS163	90p	4059	560p
7473	32p	74LS164	90p	4060	112p
7474	40p	74LS165	150p	4063	112p
7476	40p	74LS168	190p	4066	56p
7490	35p	74LS173	100p	4067	422p
7492	50p	74LS174	99p	4068	19p
7493	50p	74LS175	99p	4069	19p
7496	45p	74LS181	280p	4070	28p
74121	45p	74LS190	110p	4071	25p
74123	45p	74LS195	87p	4072	25p
74154	90p	74LS196	100p	4075	20p
74157	55p	74LS221	110p	4076	88p
74122	45p	74LS240	210p	4077	23p
74125	50p	74LS241	200p	4078	23p
74195	100p	74LS242	220p	4081	29p
74196	100p	74LS244	175p	4082	25p
74283	140p	74LS245	220p	4085	86p
74290	120p	74LS251	120p	4089	160p
74365	90p	74LS253	120p	4089	160p
74365	90p	74LS257	110p	4093	68p
74365	90p	74LS260	90p	4094	225p
74365	90p	74LS273	175p	4095	99p
74365	90p	74LS290	95p	4096	325p
74365	90p	74LS293	120p	4098	110p
74365	90p	74LS366	57p	4099	180p
74365	90p	74LS373	170p	4501	25p
74365	90p	74LS374	170p	4502	112p
74365	90p	74LS375	140p	4503	68p
74365	90p	74LS393	135p	4507	52p
74365	90p	74LS490	140p	4508	288p
74365	90p	74LS670	260p	4510	76p

74LS

74LS00	12p	4001	19p	4516	109p
74LS01	12p	4002	19p	4518	99p
74LS02	13p	4006	75p	4520	99p
74LS03	13p	4007	19p	4521	230p
74LS08	20p	4008	80p	4526	105p
74LS10	19p	4009	36p	4527	130p
74LS11	20p	4010	45p	4528	99p
74LS12	30p	4011	24p	4529	140p
74LS13	35p	4012	24p	4531	150p
74LS14	60p	4013	38p	4532	125p
74LS15	38p	4014	70p	4538	150p
74LS20	18p	4015	75p	4543	160p
74LS21	30p	4016	35p	4556	70p
74LS22	38p	4017	75p	4560	225p
74LS26	45p	4018	42p	4572	46p
74LS27	45p	4019	42p	4574	46p
74LS30	18p	4020	88p	4584	79p
74LS32	23p	4021	100p	4585	125p
74LS37	35p	4022	89p		
74LS38	35p	4023	22p		
74LS40	55p	4024	50p		
74LS42	55p	4025	20p		
74LS47	78p	4026	130p		
74LS48	85p	4027	43p		
74LS49	99p	4028	75p		
74LS53	30p	4029	80p		
74LS74	30p	4030	50p		
74LS75	42p	4031	195p		
74LS85	98p	4033	145p		
74LS86	39p	4035	104p		
74LS90	30p	4036	290p		
74LS93	75p	4037	105p		
74LS96	150p	4038	110p		
74LS107	40p	4039	280p		
		4040	99p		
		4041	75p		

LOW PROFILE SOCKETS BY TEXAS

SALE	74LS
8 pin	74LS00
14 pin	74LS01
16 pin	74LS02
18 pin	74LS03
20 pin	74LS08
22 pin	74LS10
24 pin	74LS11
28 pin	74LS12
40 pin	74LS13

KEYBOARD ENCODER

AY 2376	795p
---------	------

SUPPORT DEVICES

6520	325p
6522	625p
6532	625p
6551	825p
6910	350p
6620	360p
6621	325p
6845	£23.50
6850	295p
6852	350p
6853	445p
6854	445p
6855	445p
6856	445p
6857	895p
6858	950p
6859	950p
6860	845p
6862	925p
6869	£19
8086A	£25p
8088A	£10.95
280A CTC	695p
280 DMA	£19.95
280A DMA	£24.95
280S 0-1	£29.95
280A 510-0	£34.95
280S 10-1	£29.95
280A 510-1	£34.95
280S 10-2	£29.95
280A 510-2	£34.95

VOLTAGE REGULATORS

7805-7812	50p
7905-7912	80p
78HOSSC	575p
78HGKC	625p

EPROMS

2708 450 NS	350p
2716 5V 450 NS	475p
2532 32K 450 NS	£14.95
2732 Intel-type	450 NS
2564 64K (8K x 8) 450	£14.95
NS 28-pin	£99
	£95
	£90

UARTS

415 1013A	325p
415 1015D	398p
IM6-021P1	325p

CPU S

6253	625p
6504	750p
6505	750p
6800	845p
6802	925p
6809	£19
8086A	£25p
8088A	£10.95
280A CTC	695p
280 DMA	£19.95
280A DMA	


SPOT DESIGNS

20 W MOSFET Amplifier

Although power MOSFETs were originally only used in super-fi amplifiers, they have fallen in price to the point where they can be given serious consideration for use in any amplifier where an output power of between about 20 W and 100 W RMS is required. This simple design gives good quality results with the level of total harmonic distortion well below 1% at all audio frequencies provided the maximum output power is not exceeded. The maximum output power is a little over 20 W RMS if a 50 V supply is used and approximately 30 W RMS if a 60 V supply is employed with the unit (both are loaded voltages).

The circuit is basically quite conventional with Q2,3 being used as a Darlington pair, common emitter driver stage. The main collector load for this is formed by a constant current generator circuit using Q1 and its associated components. This gives a current of about 6-7 mA in the driver stage. Such a low current is acceptable due to the very high current gain of the complementary source follower MOSFET output devices. PR2 is used to set the appropriate quiescent output current through the output stage and the slightly negative temperature coefficient of the output devices makes any thermal stabilisation here totally unnecessary. R2,3 and PR1 are used to bias the amplifier. No phase or frequency compensation components are needed due to the excellent high frequency performance of the two output transistors.

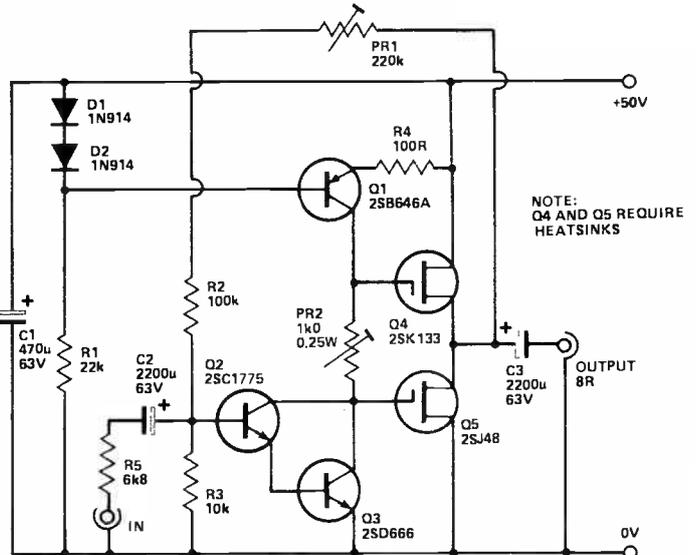Before initially connecting the supply to the circuit, set PR1 at about half maximum resistance. PR1 is then adjusted to give half the supply voltage at Q4 and Q5 source terminals and PR2 is advanced to give the circuit a quiescent current consumption of approximately 100 mA. The circuit has an input sensitivity of about 500 mV into 6k8



for full output. Current consumption is about 800 mA RMS at 20 W RMS output and almost 1 A with an output of 30 W RMS. The transistors are available from Ambit International.


Call Charge Reminder

The idea of this simple circuit is to give the user some idea of the number of units that are being accumulated while a telephone call is in progress. It is not intended to give a readout of the number of units, but instead gives a warning (clicking) sound each time an extra unit is accumulated. This enables a very simple and inexpensive circuit to be used and is effective in that it prevents the user from losing track of time.

A CMOS version of the 555 timer device (the ICM7555) is used as the basis of the unit. Using the CMOS version has the advantage of giving a much lower current consumption (about 100 uA). Before starting to dial the required number the unit is switched to the standby mode using SW1. This connects power to the circuit, but the 555 astable is blocked from operating properly by R1 which holds timing capacitor C2 into a charged state.

When the call is answered, SW1 is switched to the on position and R1 is then disconnected so that the unit is able to function normally. However, the astable cycle does not start at the normal point with C2 charging from zero. Instead, C2 is rapidly discharged to one third of the supply voltage through R11 and IC1 and then starts to charge again. This is important, since the initial cycle of the circuit would otherwise be significantly elongated (an effect that occurs with virtually all astable circuits).

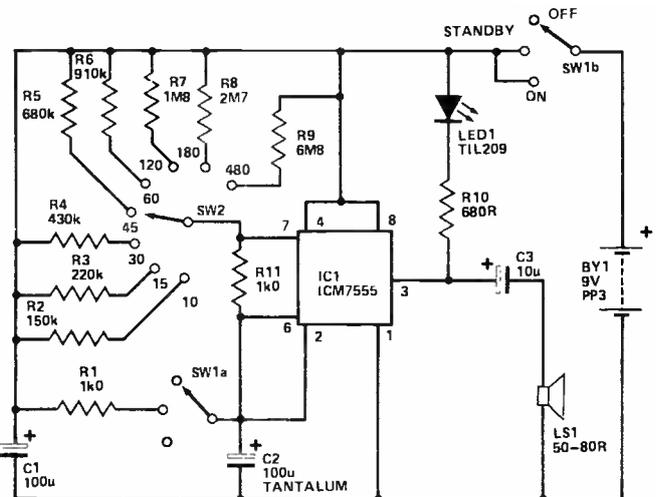The operating frequency of the unit is controlled by SW2 and the series of timing resistors (R2-9). The telephone dialling instructions booklet should be consulted to ascertain the time per unit of the call you are about to make and SW2 is then set to the appropriate time. The output of IC1 is normally high, but at the end of each cycle it briefly



goes low, giving a clicking sound from LS1 and giving a brief flash from optional indicator LED 1. Each click, including the one that occurs as the unit is switched to the on position, indicates an extra unit has been accumulated.

VIDEOTONE

**BUY DIRECT FROM US AND
GET THE SAME HIGH
QUALITY AT LOW PRICES!**




DISCOUNT
SELLING PRICE
£50.00

LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. **NOW AT LOWEST EVER PRICES.**

D100	£38.00
Minimax 11	£44.00
GB3	£50.00
GB2	£60.00
GBS	£207.00
D 93	£40.00

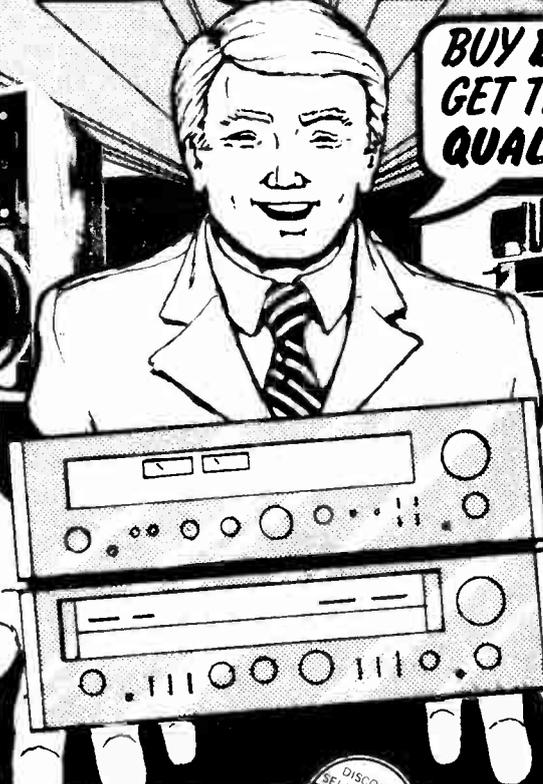

CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL UK's No. 1 Cartridge	MOVING MAGNET
MC 81 £48.87	555SX £7.28
777EX £35.00	555E £14.22
777E £25.00	666E £32.48
HEAD AMP	HEADSHELLS
H300 £51.75	S100 £6.00
T100 £24.75	S101 £7.00
	S200 £4.00

TURNTABLES

Sansui SR222 Mk2	£69.00
Sansui P50S	£69.00

AMPS-TUNER-CASSETTE

30 watt amp MC input SA4 130	£75.00
Stereo Tuner ST 4120	£68.00
Cassette full features SC 4200	£95.00
50 watt amplifier WA7700	£77.00
20 watt amplifier LA2020	£58.00

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.



DISCOUNT
SELLING PRICE
£68.00

DISCOUNT
SELLING PRICE
£75.00

* A MESSAGE FROM VIDEOTONE *

Dear Customer
You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly onto you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving **Value for Money**. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. **Remember, you have 21 days trial period on all products. That is the measure of our confidence.**

Cliff Hardcastle
Cliff Hardcastle, Managing Director.



MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39



HEADPHONES

Superbly made with top flight performance

HP90	£12.65
HP80	£9.69



Quality plus value - always

VIDEOTONE

ALL
PRICES
INCLUDE
VAT

ALL PRODUCTS
ON DISPLAY &
CONTINUOUS
DEMONSTRATIONS

98 CROFTON
PARK ROAD
LONDON SE4
TEL: 01-690 8511/2

SEND FOR OUR LATEST
FREE BROCHURE
AND DETAIL LIST OF LOCAL
SALES OUTLETS IN THE U.K.

NAME _____
ADDRESS _____

ET

Get a great deal from Marshall's

CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48
CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00
CPR 1	Pre Amp	£32.17
CPR 1S	" "	£42.52

ILP HI FI MODULES

Power Amplifiers

HY30	£ 7.29
HY60	£ 8.33
HY120	£17.48
HY200	£21.21
HY400	£31.83

Pre Amplifiers

HY6	£ 6.44
HY66	£12.19

Power Supplies

PSU30	£ 4.50
PSU36	£ 8.10
PSU60	£13.04
PSU70	£13.04
PSU180	£21.34

SINCLAIR INSTRUMENTS

Digital Multimeter

	PDM35	£ 34.50
"	DM235	£ 52.50
"	DM350	£ 72.50
"	DM450	£ 99.00

Digital Frequency Meter

	PFM200	£ 49.80
--	--------	---------

Low Power Oscilloscope

	SC110	£139.00
--	-------	---------

TF200 Frequency Meter

		£145.00
--	--	---------

TGF105 Pulse Generator

NEW		£ 85.00
------------	--	---------

LCD Multimeter

	TM351	£99.00
--	-------	--------

LCD Multimeter

	TM352	£49.95
--	-------	--------

Prescaler

	TP600	£37.50
--	-------	--------

MULTIPLEX NICKEL CADMIUM CELLS

Type S101 (HP4) £0.98

Type SubC (HP11) £1.75

Type SubD (HP2) £1.95

Friwo Chargers for above

Penlight 4: accommodates

1-4 size HP7 £5.50

Combibox FW611: accommodates

HP7, HP11 £13.25

NOTE ALL PRICES NET. EXCLUDING VAT. POSTAGE/PACKING

New


Presensitised PC Boards, Developer. U.V. units.

Toyo miniature Fans 230v AC £9.95

Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95

Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

Just one of the exciting Leader range

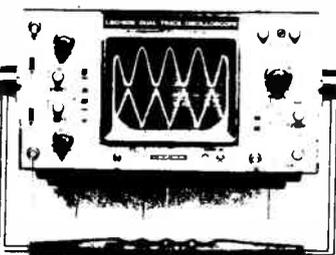

£299 + VAT

LB0508A OSCILLOSCOPE
With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.


A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA.
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr service.

Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2, 85 West Regent St., Glasgow 108A Stokes Croft Bristol.

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

BECKER Hi-Fi Speakers

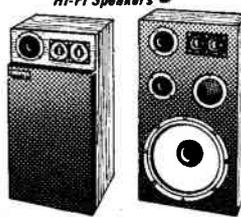


All models multi-speaker systems

With controls, attractive woodgrain finish. RMS ratings for 8 ohm.

12.60 12" 4 speaker system 60 watts 26 1/2" x 14 1/2" x 11" £115.95 pair

15.90 15" 5 speaker system 90 watts 28" x 17 1/2" x 11 1/2" £135.95 pair (UK c/p £12.00 pair)

ON DEMONSTRATION TO CALLERS

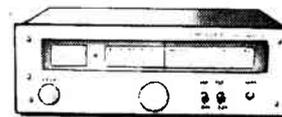

SCOTT T516 STEREO FM/AM TUNER

HIGH QUALITY STEREO FM/AM TUNER BY SCOTT OF U.S.A.

Overall size 5" x 14 1/2" x 12". Brand new and fully guaranteed at a special low price. (C/P £1.55)

£38.95

On demonstration for callers.




JVC BELT DRIVE TURNTABLE

JVC TURNTABLE WITH FREE AUDIO TECHNICA AT100 STEREO CARTRIDGE.

- * S shaped tone arm
- * Belt drive
- * 12" Platter * Calibrated counter-balance weight
- * Anti-static device

Size 12 1/4" x 15 1/4" (C/P £1.55)

£29.95

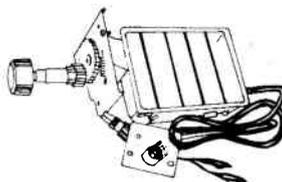

1000's SOLD

TV SOUND FROM YOUR HI-FI

High quality TV sound converter plugs into aerial socket of your FM tuner. 9 volt battery operated (battery not supplied). Nothing to look at... but just listen!

- * Fitted slow-motion drive (UK Post etc. 65p)

On Demonstration to callers.

New model (appearance may differ from illustration)

£8.50



SEAS SPEAKER KITS

8 ohm



Professional sound hi-fi speaker kits with high sensitivity (90-92dB). Extended frequency response (223" 50-20kHz, 253" 35-25kHz). Designed and made in Scandinavia to the highest quality. All supplied with complete cabinet plans, tweeters/crossovers/leads etc. * On Demonstration to callers.

- * Hi-Fi 223, 30/45 watt 3 speaker 8" system £43.50 pair
- * Hi-Fi 253, 60/100 watt 3 speaker 8" system £34.50 each
- * Hi-Fi 403, 60/100 watt 3 speaker 10" system £44.50 each
- * Hi-Fi 603, 80/150 watt 3 speaker 12" system £64.50 each

(UK C/P £2.50)

COMPLETE RANGE OF SEAS CHASSIS SPEAKERS ETC ALWAYS IN STOCK ALSO STOCKISTS FOR AUDAX, GOODMANS, KEF, PEERLESS ETC.

PIEZO TWEETERS



Clean sound, very low distortion tweeters. No crossover required. Suitable up to 100 watts -- more in series.

- 1 Mid-range horn for disco/pa/groups £6.95
- 2 Tweeter horn for hi-fi/disco/pa £5.50
- 3 Popular hi-fi and disco £4.40
- 4 Flat type hi-fi £3.50

On Demonstration to callers.

C/P 50p (up to 4 items)

STEREO ACCESSORIES

- * GE1305 Hi-Fi Frequency Equaliser £62.95
- * APM 200 Peak programme meter (w/in scale) £39.95
- * MS3219 Twin Scale audio output meter £12.95
- * MC350 Tape echo chamber £59.95

FREE CATALOGUE

Large range of speakers/stereophones/microphones/mixers/PA equipment etc -- and much more! Plus huge range of test equipment. ALL PRICES INCLUDE VAT SEND LARGE 20p SAE

PRICES CORRECT AT 1.2.81

AUDIO ELECTRONICS

Cubegate Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND.

TELEPHONE 01-724 3564 OPEN 9-6 Mon-Sat

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS OR CALL IN AND SEE FOR YOURSELF



THE LEPTONS

No, not more aliens for Captain Kirk to deal with, but a family of subatomic particles. Lepton means 'light particle', but some of them aren't, and they may not be made up of quarks either. Confused? So are the particle physicists. A.S. Lipson explains.

Once upon a time, physics was simple (well, nearly...). Subatomic physics especially, seemed to be fairly clear cut. Around the turn of the century, J. J. Thomson had discovered the electron, which carried a negative electrical charge. A few years later, Max Planck had stated the existence of the photon, or 'particle of light'. There was one other particle; the proton, which was positively charged, and had a mass about 1836 times that of the electron. The proton and electron were known to exist within atoms. That was the entire list of subatomic particles, and it looked as though everyone would live happily ever after.

Then things got complicated. In the 1930s and 40s, more particles started turning up, and they have continued to do so to the present day. First there were the neutron and mu-meson. Then there were the pi-mesons, or pions (three different ones!), the Kaons, the positron, the anti-proton, the anti-neutron, the anti-muon, a few different particles called Sigmas, and no less than four variations on a type of particle known as a neutrino (of which we will see more later). . . . The list seemed endless.

Eventually, the physicists managed to start simplifying the situation. It became apparent that many particles — the proton and neutron, for example, might be made up of various combinations of a few even more basic particles — called quarks. Instead of having all those different particles, maybe everything could be explained in terms of just three or four quarks. There was a particular group of particles, however — collectively known as 'leptons' — which did not seem to be made up of quarks. It's these particles which concern us in this article.

Light Matter

The word lepton comes from the Greek word 'lepto', meaning light, since the earliest leptons discovered were particles with relatively little mass. It is now known that not all leptons are light, after all, but the name has stuck.

The first lepton to be discovered was the electron, which has a negative electric charge of 1.6×10^{-19} coulombs, and a mass of 9.1×10^{-31} kg. (It will be convenient for the purposes of this article to refer to particles as having a mass of so many times the mass of the electron, so for the moment we can say simply that an electron has mass 1. Using this scale, a hydrogen atom has a mass of nearly 2000). The next particle to enter our story is the neutron. The neutron is not a lepton, but its relationship with the electron leads us to the next important point — the neutrino.

The neutron is a fairly massive particle; on the electron's scale it has a mass of 1839. It carries no net electrical charge — hence its name. One important feature of the neutron is that, like many particles, it is unstable. An isolated neutron will tend, after an average time of 15 minutes or so, to disintegrate, producing a proton (mass 1836) and an electron. You will notice that, since the neutron carries no charge, when it turns into a positively charged proton, it is necessary that an equal and op-

Particle	Mass (x electron mass)	Charge (in coulombs)	Lifetime	Lepton
Proton	1836	1.6×10^{-19}	Stable	No
Neutron	1839	Zero	About 15 min	No
Electron	1	-1.6×10^{-19}	Stable	Yes
Electron-neutrino	Very small	Zero	Stable	Yes
Muon	207	-1.6×10^{-19}	2.2×10^{-6} S	Yes
Muon-neutrino	Very small	Zero	Stable	Yes
Tau	About 3500	-1.6×10^{-19}	Less than 3×10^{-12} S	Yes
Tau-neutrino	Very small	Zero	Stable	Yes

Table 1. Particles discussed in the article (antiparticles left out for simplicity).

posite charge — the electron — is created at the same time, so that the total charge remains zero. All well and good, then; sometimes a neutron spontaneously changes into a proton and an electron.

Think Of A Particle. . .

Unfortunately, it isn't quite that simple. You see, when this reaction was first observed to happen, physicists weren't too happy with it. It seemed that certain physical laws which had always held before weren't holding any more. But then it was spotted that all the laws *would* be holding, if only there was another particle taking part in the reaction. This particle, although it had never been observed, was christened the 'neutrino', from Italian words meaning 'little neutral one' — since the neutrino, if it existed, would have little or no mass and be electrically neutral. The fact that the neutrino had never been detected was easily explained — all the methods used to detect subatomic particles depended on their having measurable masses and charges. The neutrino had neither. In fact, neutrinos react with other matter very rarely. If a beam of neutrinos was aimed at a concrete slab a light-year thick, by far the majority would get through easily!

You may think it a little bit far-fetched that scientists would actually *invent* a new particle — one that had never been found — just to explain why some physical laws didn't seem to work. Why not just change the laws? Well, all through the history of science, it has invariably turned out that the simplest explanation of a set of events is the correct one. In this case, it was simpler to keep the old, simple set of laws and invent a new particle, than it would have been to invent a whole new set of more complicated laws. This, at least, was how the physicists reasoned, and as it happened, they were right! In 1956, twenty-five years after its original invention, the neutrino was discovered! In fact, it was found that the particle produced when a neutron

turned into a proton and an electron was not a neutrino, but its 'antiparticle', the antineutrino. This, however, was a small point, and the discovery of the actual existence of the neutrino is regarded as a major triumph for theoretical physics, which had predicted its existence all those years before.

So now our family of leptons contains two particles; the electron and the neutrino (and their antiparticles — the 'positron' and the 'antineutrino' respectively). This wasn't the case for long, though. In the late 1930s, another lepton was discovered in cosmic rays high up in the atmosphere. This particle was called the mu-meson, or muon for short. It was given the symbol μ , the Greek letter mu. There are only two real differences between the muon and the electron. Firstly, the muon has a much greater mass, about 207 times that of the electron; and secondly, the muon, like the neutron, is unstable, although on average it has a much shorter lifetime. Under normal conditions, a muon will disintegrate after only about one five hundred thousandth of a second, turning into an electron and producing two neutrinos. Apart from these two differences, however, the electron and muon are strikingly similar. For instance, both carry the same charge, -1.6×10^{-19} coulombs. The anti-muon carries a positive charge of the same magnitude, just as does the anti-electron, or positron. The similarity between the two particles has been puzzling physicists ever since the discovery of the muon. But there's one more thing puzzling them, too. . . .

Identical Twins?

It was found that many of the reactions involving electrons also involved neutrinos. Similarly, many reactions involving muons also involved neutrinos. The neutrinos that reacted along with electrons didn't seem to be the same as those which reacted along with muons. Apparently, there were two types of neutrinos. If you examined a neutrino from a reaction involving an electron, you would find that it could not be made to take part in a reaction involving a muon. Similarly, a neutrino from a muon reaction could not be made to react with an electron. Neutrinos, then, had to be divided into two groups; 'electron neutrinos' and 'muon neutrinos'. What is the difference between the two types of neutrino? The somewhat embarrassing answer (for a physicist) is that, even today, nobody really knows. They are different, but we don't know why. All we do know is that reactions involving electrons tend also to involve electron neutrinos, whereas reactions involving muons tend to involve muon neutrinos. When a reaction involves both electrons and muons, both types of neutrinos are involved. For instance, when a muon turns into an electron, a muon neutrino and an electron antineutrino are produced (see Fig.1b). The two types of neutrinos are like almost-identical twins — you can't tell the difference just by looking at them, but only by looking at the different ways they behave. And, of course, each of the two types of neutrino has its own anti-neutrino, as well.

Three's A Crowd. . . .

As if the situation wasn't already complicated enough, experiments conducted in the last five years or so indicate (wait for it) that there's yet another lepton. This one, called the tau particle (and given the symbol τ — the Greek letter tau) is, again, just like the electron and muon, but with a still greater mass (about 3500 times the mass of an electron — nearly as massive as a molecule of hydrogen! As far as subatomic particles go, this is well into the heavyweight league), and with a still shorter average lifetime before it disintegrates into other particles. As yet, experiments are not conclusive, but it seems that the tau particle also has its own pair of neutrinos — the tau neutrino and the tau antineutrino. Unsurprisingly, these neutrinos refuse to take part in electron or muon reactions, unless a tau particle is also involved.

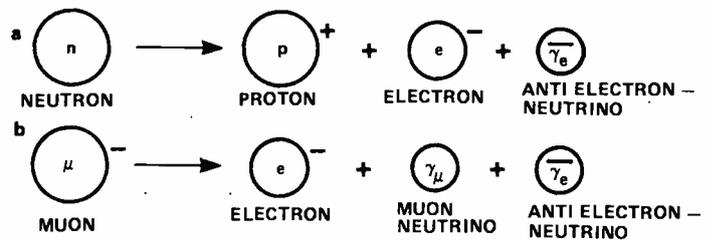


Fig. 1. (a) Neutron turning into proton and electron, giving off anti-neutrino. (b) Muon disintegrating to produce electron, muon-neutrino and anti electron-neutrino.

Any Answers?

So that is the situation at the moment. There are three known leptons which carry electric charge — the electron, the muon and the tau (each also having a positively charged antiparticle) and correspondingly, three sets of a pair of neutrinos — the electron-, muon- and tau-neutrinos, with their antiparticles. There are a lot of questions still to be answered. Are there any more leptons, like the electron, muon and tau, but with still greater masses, and shorter average lifetimes? If there are, do they also have their own neutrinos? And for that matter, what is it that makes, say, a muon neutrino different from a tau neutrino? There's one more major problem too.

A Massive Question

It has been known for several decades now that neutrinos have very little, or perhaps no mass at all. In fact, there has been a tendency among physicists to believe that the latter is the case — that the neutrino has no mass, although this has never been proved. Very recent experiments, however, make it look as though perhaps the neutrinos do have masses after all. If this is so, then physicists may have to rethink a lot of theories. Do neutrinos have mass? We shall just have to wait and see and maybe everyone will live happily ever after.

ETI

CIRCUIT DIAGRAMS/OVERLAYS/ FLOWCHARTS!

Do you require professionally drawn Circuit diagrams, Overlays, Flowcharts etc. drawn from your own designs? MM Design & Print offer a quick, accurate and cheap Technical Illustration and lettering service to readers of ETI. We illustrate anything from a single chip amplifier to a colour television circuit design, with finished artwork supplied to your specification. For further details please ring Paul Edwards, on 01-437 1002/7 extension 29, or write to the address below.



Part of the Modmag Group.

145 Charing Cross Road,
WC2H 0EE

KNOW YOUR ZX80

With LINSAC products for the Sinclair ZX80

THE ZX80 COMPANION



(SECOND EDITION)
LINSAC

NOW ONLY
£7.95

THE ZX80 COMPANION
(Second Edition)
Moulder, Logan and Trotter

ISBN 0 907211 00 3. Price £7.95 incl. UK postage.

This best-selling manual on the Sinclair ZX80 covers ZX80 BASIC, hardware and programs and has a detailed explanation of the ZX80 Monitor, routines and entry points. A routine for generating moving displays is also included.

- Ch.1 - Operating the ZX80
- Ch.2 - Theory of Computers
- Ch.3 - ZX80 BASIC
- Ch.4 - The ZX80 Monitor
- Ch.5 - Construction and Hardware
- Ch.6 - ZX80 Programs
- App.1 - Comparison of Z80 Opcodes and ZX80 Characters.
- App.2 - The BK ROM

For a cassette of ten programs from the Companion add £4.95.

The ZX80 Monitor A complete assembly language listing of the ZX80's 4K Monitor, with annotations. - Price £10.00 incl. UK postage.

Cassette Software

All LINSAC program packs are on single C12 cassettes with printed run instructions. All run on 1K ZX80's unless otherwise stated. Price £7.95 per pack incl. UK postage.

- GAMES PACK 1 - Three Towers, Number Guessing, Mastermind, Sketcher, Murkic, Nim, Symbol Simon.
- GAMES PACK 2 - Nine Lives, The Maze Game, Plain Sailing, OXO, Chinese Puzzle, Tower of Hanoi, Battleships.
- GAMES PACK 3 - (ZK) - Fruit Machine, Four in a Line, Zombies.
- EDUCATION PACK 1 - Maths Drill, Dot Recognition, Musical Notes, Spelling Quiz, Day Finder.
- EDUCATION PACK 2 - Graph Plotter, Prime Factors, Number Base, Bar Charts, Statistics.
- EDUCATION PACK 3 - (ZK) - CAL Quiz Package with three sample data sets.
- UTILITY PACK 1 - Memory Display, Hex Code Monitor, Renumber - Memory Search.

LINSAC 68 Barker Road, Linthorpe, Middlesbrough, Co. Cleveland TS5 5ES

Professional ASCII Keyboards

ONLY £29.95
ADD + VAT
SCOOP £1.50



The 'APPLE' Computer Keyboard

- 52 KEY 7 BIT ASCII CODED
- POSITIVE STROBE. +5V - 12V
- FULL ASCII CHARACTERS
- PARALLEL OUTPUT WITH STROBE
- POWER LIGHT ON CONTROL
- NATIONAL mm 5740 CHIP. TTL OUTPUT
- SUPERBLY MADE. SIZE 12x5.5x1.5ins
- BLACK KEYS WITH WHITE LEDGENS
- ESCAPE. SHIFT. RETURN & RESET KEYS

Complete with CIRCUIT & DATA
Ideally for use with TANGERINE TRITON

Ex-Stock from HENRY'S TUSCAN APPLE & most computers

This is definitely the **BEST BUY**
Supplied **Brand NEW** in manufacturers original jacking (ANTI-STATIC)
Just post remittance total £35.95 (incl. VAT & Post)



Henry's



Computer Kit Division
404 Edgware Road, London, W2, England
01-402 6822

MAIL ORDER ONLY
DELTA TECH & CO.
62 NAYLOR ROAD, LONDON, N20 0HN
Tel: 01-445 8224
Prices include VAT. Add 35p P&P
Minimum Access order £3

SWITCHES	LM3900N *50p	LM3909N *75p	MC1496P *80p	NE531 *120p	NE555 *25p	NE556 *45p	NE566 *140p	SN76023N *120p	SN76115N *80p	TBA6418 *200p	TBA800 *75p	TBA B10S *110p	ZN14 *90p	ZN1034E *220p	
SLIDE 1A/250V DPDT	12p														
TOGGLE 3A/250V DPDT	35p														
ROTARY 2A/250V DPST	35p														
CERAMIC CAP (50V)															
33 pF to 4700 pF	4p														
POLYSTYRENE CAP (50V)															
10 pF to 1000 pF	5p														
POLYESTER CAP (100V)															
1 nF to 68 nF 6p; 100 nF 150 nF 8p; 220 nF 330 nF 10p; 470 nF 11p; 680 nF 7p; 1 uF 7p; 1.5 uF 7p; 2.2 uF 20p; 3.3 uF 15p; 4.7 uF 15p															
ELECTROLYTIC CAP (uF/V)															
1/25 to 47/25 6p; 68/25 7p; 100/35 150/25 8p; 160/25 5p; 200/12 6p; 250/12 7p; 220/25 10p; 470/25 500/30 12p; 470/40 mini 15p; 640/16 8p; 1000/10 10p; 1000/40 24p; 1500/25 24p; 2200/6 3 12p															
ZENER DIODES (400mW)															
2V7 to 33V 8p															
VEROBOARDS (.1" copper)															
2.5" x 5"	65p														
3.75" x 5"	80p														
RESISTORS (5% E12)															
10 Ohms to 10Mohms	2p														
PRESETS (.15W HORIZONTAL)															
100 Ohms to 2 Mohms	7p														
POTENTIOMETERS (1/4W)															
Linear & Log Scales															
4K7 to 2M2	33p														
LINEAR CIRCUITS	LF351N *44p	LF356N *85p	LM301AN *30p	LM308N *38p	LM318N *120p	LM318H *120p	LM324N *57p	LM339N *52p	LM348N *90p	LM377N *175p	LM380N *90p	LM381N *120p	LM382N *120p	LM1310N *115p	LM1458N *40p
709-B	28p														
710-14	35p														
741-B	22p														
747-14	50p														
748-B	35p														
CA301B	70p														
CA3028A	85p														
CA3046	50p														
CA3054N	40p														
CA3080B	78p														
CA3090AQ	200p														
CA3130E	95p														
CA3140E	48p														
4001B	15p	4016A	25p	7473	16p	1N4005	4.5p	ZD5V6	5p	BFY50	15p	CA3090AQ	70p	160 uF/25V	4p
4007A	13p	4017A	40p	7490	23p	1N4007	8p	ZD9V1	5p	TIP31A	22p	SN76115N	50p	640 uF/16V	4p
4011B	15p	7420	13p	OA91	5.5p	1N5404	10p	BF244C	14p	TIP3055	22p	33uF/40V	4p	WO05	16p

TRIACS	4021/2	95p	7446	65p	74194	70p	BCY70	18p	TIP41A	60p
3A/400Vp	4023	22p	7447A	50p	74195	68p	BCY71/2	18p	TIP42A	60p
10A/600Vm	4024B	55p	7448	52p	74196	95p	BD115	35p	TIP2955	70p
30A/600Vm	4025	20p	7450	10p	74197	45p	BD121/3	50p	TIP3055	*30p
DIAC	4027	50p	7451/3	13p	74198	120p	BD124	50p	ZTX107/B	12p
ST2	4028	70p	7454	10p	74199	90p	BD131/2	40p	ZTX109	12p
VOLTAGE REGULATORS	4029	90p	7460	13p			BD135 to		ZTX300/1	14p
7805	4030	55p	7470	20p	TRANSISTORS		BD140	40p	ZTX302/3	18p
7812/15	4035	110p	7472	19p	AC126/7	22p	BF179	19p	ZTX304	23p
7818/24	4041	85p	7473	*18p	AC128	20p	BF180	34p	ZTX500/1	15p
7905	4042	80p	7474	28p	AC153	25p	BF181	8p	ZTX502	20p
7912/15	4043/4	99p	7475	28p	AC176	22p	BF183	34p	ZTX504	24p
7918/24	4047	105p	7476	30p	AC187/B	22p	BF184/5	25p	ZTX506/7	20p
	4048	60p	7480	32p	AD149	40p	BF194/5	12p	2N698	20p
DPTO/ ELECTRONIC	4049	50p	7485	140p	AD161/2	28p	BF196/7	12p	2N706	14p
4050B	40508	50p	7486	18p	AF114	30p	BF198	10p	2N914	20p
2N5777	4066	60p	7490	28p	AF124	35p	BF248	14p	2N918	20p
OC711	4068/9	22p	7491	57p	AF125/6	35p	BF244B	*22p	2N1302/3	35p
ORP12	4070B/1	22p	7492	30p	AF127	35p	BF248	28p	2N1304	35p
DL704	4072/3	22p	7494	50p	BC107/B	10p	BF258	28p	2N1306	30p
DL707	4081/2	26p	7495	40p	BC109	10p	BF259	28p	2N1308	35p
LEDs:	4086	80p	7496	37p	BC140	20p	BFR39	30p	2N1613	25p
0.125" & 0.2"	4510	100p	7497	200p	BC142/3	30p	BFR40	30p	2N1711	13p
Red	4511B	100p	74100	60p	BC147/B	10p	BFR79	32p	2N1893	25p
Green	4516/B	105p	74105	43p	BC149	10p	BFR80	20p	2N2217	18p
Yellow	4520/B	105p	74107	22p	BC157/B	12p	BFX29	25p	2N2219	23p
Rect. Green	TTL		74109	34p	BC159	12p	BFX84	25p	2N2222A	23p
0.125" Clip	7400/1	16p	74110	40p	BC169C	13p	BFX85/6	20p	2N2369	17p
0.2" Clip	7402/3	16p	74118	84p	BC171	10p	BFX87/B	25p	2N2484	25p
DIL SOCKETS	7404/5	18p	74121	25p	BC173	8p	BFY50/1	20p	2N2646	46p
8 pin	7406	16p	74122	30p	BC177/B	16p	BFY52	22p	2N2904/5	21p
14 pin	7407	25p	74123	50p	BC179	16p	BRY39	50p	2N2906/7	21p
16 pin	7408	22p	74125/6	42p	BC182	10p	BSX19	12p	2N2926G	10p
18 pin	7409	13p	74132	65p	BC182L	*8p	BSX20	22p	2N3053	20p
22 pin	7410	13p	74141/5	46p	BC183B	10p	BU205	150p	2N3054	30p
24 pin	7411/2	17p	74150	85p	BC184	10p	BU208	210p	2N3055	45p
28 pin	7413	30p	74151	65p	BC186	25p	MJ2955	110p	2N3442	140p
40 pin	7414	45p	74153	43p	BC187	15p	MJE340	52p	2N3702 to	
CMOS AE	7416	20p	74154	66p	BC207/9	13p	MJE3055	80p	2N3711	11p
4000	7417	25p	74155	46p	BC212	10p	MPF102	45p	2N3772	*70p
4001B	7420	15p	74156	42p	BC212L	*8p	MPF104/5	40p	2N3773	250p
4002	7421	30p	74157	38p	BC213L	10p	MPF106	45p	2N3819	21p
4006B	7422	26p	74160	57p	BC214	10p	OC2B/35	50p	2N3820	40p
4007	7427	20p	74161	55p	BC214L	*8p	TIP29	42p	2N3823	70p
4008	7428	28p	74162/3	60p	BC238	18p	TIP29B	40p	2N3866	65p
4009	7430	26p	74164/5	56p	BC261B	23p	TIP30	40p	2N3903/4	15p
4010	7432	18p	74166	95p	BC301/3	32p	TIP3			

GREENWELD

443A Millbrook Road Southampton SO1 0HX
All prices include VAT @ 15% — just add 40p post

THE SPECTACULAR 1981 GREENWELD Component Catalogue

- Bigger and better than ever!!!
- ★ 60p discount vouchers
- ★ First Class reply paid envelope
- ★ Free Bargain List
- ★ Priority Order Form
- ★ VAT inclusive prices
- ★ Quantity prices for bulk buyers
- ★ Free Data Sheet

SEND 75p FOR YOUR COPY NOW!!

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1.000pF, total 210, £3.99.
K002 Extended range 22pF to 0.1µF, 330 values £5.53.

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ. 110 altogether for £8.97.

K004 Mylar capacitors, min 100V type 10 each all values from 1.000pF to 10.000pF. Total 130 for £6.06.

K007 Electrolytic capacitors 25V working small physical size 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.99.

K008 Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for £8.06.

K021 Miniature carbon film 5% resistors CR25 or similar, 10 of each value from 10R to 1M, £12 series. Total 610 resistors £8.16.

K022 Extended range. Total 850 resistors from 1R to 10M £8.90.

K041 Zener diodes 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for £18.37.

NEW 60x1 LEDs — 10 each red, green & yellow 3mm & 5mm, with clips. Total 60 LEDs for £8.99

BUZZERS, MOTORS & RELAYS

Z401 Powerful 8V DC buzzer, all metal construction 50mm dia x 20mm 89p.

Z402 Miniature type buzzer, 6, 9 or 12V, only 22x15x8mm, very neat 89p.

Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only £1.

A372 Audible Warning device — solid state circuit drives high efficiency transducer to give high output. Voltage range 4-18V. Can also be driven direct from TTL or CMOS. Module size 45x21x12mm. Comprehensive data supplied £1.80

W892 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting brackets 89p.

W890 Oil Reed relay SPCO 2.4-10V, 200R coil. Only £2.20.

FSR480 Latching relay, 2 x 10A contacts, 1M, 18. Coil is 250R, and rated 60V ac, but works on 12-24 DC. Solid Encapsulation with screw terminals makes it ideal for car use. £1.20.

REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: Output voltage 0-28V
Output current 20mA-2A
Source Impedance DR1
Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only £7.75

1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, £8.80 per box, 4 boxes £30.00; 10 boxes £75.00

DISC CERAMICS

0.22µF 12V 9mm dia. Ideal for decoupling. 100 for £2.75; 1000 £20.00.
0.05µF 12V 15mm dia. 100 £1.80; 1000 £12.00. Pack of disc ceramics, assorted values and voltages — 200 for £1.00

TRANSFORMERS

Mains primary, 50V 20A sec £20.00. Mains pri 110V 15A sec £30.00; 20A £40.00.

SLIDER POT SCOOP!!!

Made by Pihar, types PL40CP & PL60C. Silly prices for superb goods!
PL40CP — 69x18x9mm, 40mm slide length. 220R, 2k2 or 10k in only. Prices (any mix): 1-24 20p; 25-99 17p; 100+ 14p.
PL60C — 64x10x7mm, 60mm slide length. 5k. log. only. Prices 1-24 22p; 25-99 22p; 100+ 17p.

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only £7.75 Suitable transformer and pots £6.00 Send SAE for fuller details.

CALC CHIPS 60p!!!

New full spec, supplied with data. 1 type MK50321 — full function inc. memory. Only 60p

£1 BARGAIN PACKS Each pack £1; any 25 packs £22

- K101 16 BC2398 transistors
- K102 15 BC349A transistors
- K103 10 BC546B transistors
- K104 18 BC182B transistors
- K105 50 1N4148 diodes
- K106 18 BC184L transistors
- K107 18 BC213L transistors
- K108 8 2N5080 thyristors, 30V 0.8A TO92 case

- K109 15 BC114 transistors
- K110 4 BD131 transistors
- K111 4 BD132 transistors
- K112 12 3A 100V rects, wire ended
- K113 30 DA002 rects 150V 0.5A
- K114 15 XK8118 (BF241) transistors
- K115 18 SP1218 (2N3702) transistors
- K116 10 MPSL01 NPN 140V TO82
- K117 10 BF450 PNP TV IF amp transistor
- K118 16 ME4101 NPN 60V AF low noise
- K119 10 2N5401 NPN 180V TO92
- K120 6 prs 2S098/2S9496 AF O/P sim to AC128/176

- K121 20 7V5 400mW zeners
- K122 10 VR525 5.25V 2.2W zener
- K123 10 58V 1W zener
- K124 50 02µF disc ceramic
- K125 200 1k 1/4W carbon film resistors
- K126 100 300pF 83V polystyrene preformed caps

- K127 25 47µF 25V axial lead caps
- K128 25 15µF 40V do
- K129 8 AA113 diodes
- K130 25 470V 0.1W presets
- K131 10 VA1088 thermistor
- K132 12 4 7µF 50V bead tants
- K133 20 3 way 5A term blocks
- K134 50 unmarked untested OC71 type transistors

- K135 30 4.7µF 10V radial elec
- K136 4 AC187k transistors
- K137 5 18µF 100V non-polarized caps
- K138 30 1/4" coil former with slug
- K139 40 025µF 50V mylar caps
- K140 30 05 do
- K141 40 0.01µF 400V axial caps (C28B)
- K142 25 wire ended neon std size, 90V
- K143 200 squares mica insulation 25mm sq.
- K144 30 IR5 3W wirewound resistors
- K145 10 1500µF 16V caps — radial PC mntg
- K146 25 330V axial caps
- K147 3 150µF 350V caps — radial PC mntg
- K148 30 transformer former type X228
- K149 12 Ferrite rod type X036
- K150 10 switches type W430

- K151 12 0.125" rad LED's
- K152 10 0.2" rad LED's
- K153 30 105 heat sinks, same as G104
- K154 15 5 pin 180° Din socket, clip fit
- K155 100 metres thin flex (10x2mm length)
- K156 15 1/4" chassis mntg fuseholder
- K157 12 16 pin QIL-QIL IC sockets
- K158 6 SPCO centre off white rocker switches

- K159 20 0.3W presets 500k V with knurled knob
- K161 20 0.3W presets 2k5 V
- K162 20 0.3W presets 2M5 V with knurled knob
- K163 400 15R 1/4W 5% preformed vert mntg resistors
- K164 50 22pF 2% silver mica caps
- K165 20 Sub-mn reed switch, body 20mm long
- K166 100 3300pF 630V polyester PC mntg caps

- K168 50 AA144 diode preformed as above
- K169 30 8V2 400mW zener as K167
- K171 25 11V do
- K173 12 1 5µF 25V tant bead caps
- K174 12 0.47µF 25V tant bead caps
- K175 100 2000pF 21k, 1.25V p/s caps
- K176 24 150R 0.1W vert presets
- K177 24 470R 0.1W horiz presets
- K178 24 470R 0.1W vert presets
- K179 24 2k 0.1W horiz presets
- K180 24 2k 0.1W vert presets
- K181 24 2k2 0.1W horiz presets
- K185 200 1R 1/4W CF preformed R's for horiz mntg, 15mm centres

- K187 18 PE5030 NPN Si TO92 transistors. Vce 35V, Hfe 75
- K188 18 FS44 PNP Si TO92 transistors. Vce 20V, Hfe 300
- K189 30 1N649 600V 0.4A diodes, preformed for H mntg.
- K190 16 BZY85 BV2 250mW zener diodes
- K191 8 BY300/800 'Top Hat' switching diode, 800V 8A
- K192 25 RGP108 100V 1A switching diode

- K193 25 RGP108 100V 1A switching diode
- K194 25 RGP108 100V 1A switching diode
- K195 25 RGP108 100V 1A switching diode
- K196 25 RGP108 100V 1A switching diode
- K197 25 RGP108 100V 1A switching diode
- K198 25 RGP108 100V 1A switching diode
- K199 25 RGP108 100V 1A switching diode
- K200 25 RGP108 100V 1A switching diode

- K201 25 RGP108 100V 1A switching diode
- K202 25 RGP108 100V 1A switching diode
- K203 25 RGP108 100V 1A switching diode
- K204 25 RGP108 100V 1A switching diode
- K205 25 RGP108 100V 1A switching diode
- K206 25 RGP108 100V 1A switching diode
- K207 25 RGP108 100V 1A switching diode
- K208 25 RGP108 100V 1A switching diode

- K209 25 RGP108 100V 1A switching diode
- K210 25 RGP108 100V 1A switching diode
- K211 25 RGP108 100V 1A switching diode
- K212 25 RGP108 100V 1A switching diode
- K213 25 RGP108 100V 1A switching diode
- K214 25 RGP108 100V 1A switching diode
- K215 25 RGP108 100V 1A switching diode
- K216 25 RGP108 100V 1A switching diode

- K217 25 RGP108 100V 1A switching diode
- K218 25 RGP108 100V 1A switching diode
- K219 25 RGP108 100V 1A switching diode
- K220 25 RGP108 100V 1A switching diode
- K221 25 RGP108 100V 1A switching diode
- K222 25 RGP108 100V 1A switching diode
- K223 25 RGP108 100V 1A switching diode
- K224 25 RGP108 100V 1A switching diode

- K225 25 RGP108 100V 1A switching diode
- K226 25 RGP108 100V 1A switching diode
- K227 25 RGP108 100V 1A switching diode
- K228 25 RGP108 100V 1A switching diode
- K229 25 RGP108 100V 1A switching diode
- K230 25 RGP108 100V 1A switching diode
- K231 25 RGP108 100V 1A switching diode
- K232 25 RGP108 100V 1A switching diode

- K233 25 RGP108 100V 1A switching diode
- K234 25 RGP108 100V 1A switching diode
- K235 25 RGP108 100V 1A switching diode
- K236 25 RGP108 100V 1A switching diode
- K237 25 RGP108 100V 1A switching diode
- K238 25 RGP108 100V 1A switching diode
- K239 25 RGP108 100V 1A switching diode
- K240 25 RGP108 100V 1A switching diode

- K241 25 RGP108 100V 1A switching diode
- K242 25 RGP108 100V 1A switching diode
- K243 25 RGP108 100V 1A switching diode
- K244 25 RGP108 100V 1A switching diode
- K245 25 RGP108 100V 1A switching diode
- K246 25 RGP108 100V 1A switching diode
- K247 25 RGP108 100V 1A switching diode
- K248 25 RGP108 100V 1A switching diode



WORTH UP TO £30

FREE WATCH OFFER on all Thandar test equipment

If you are interested in purchasing a hand-held digital multimeter, a bench digital multimeter, a hand-held frequency meter, bench frequency meter, a pulse generator, a function generator, a fully portable brief-case size oscilloscope, a 2" video monitor or even an eprom programmer and obtain a quality watch free of charge then why not take advantage of our special offer.

For purchases of between £39 and £99 we will send free of charge a gold-plated Digital LCD, ultra-slim, five-function watch. For purchases of £100 and over we will send a gold-plated, ultra-slim, analogue watch, as per photograph. Both these watches have leather straps. This watch offer is subject to availability and in any event we will send alternative watches with a retail value of £12 and £30 respectively. YOUR WATCH MAY BE SENT SEPARATELY TO ANY ADDRESS WITHIN THE UK IF REQUIRED.

Hand-held digital multimeters	
PDM 35 L.E.D. hand held DMM	£39.68
TM 354 L.C.D. hand held DMM	£45.94
TM 352 L.C.D. hand held DMM	£57.44

Bench frequency meters	
TF 040 bench frequency meter	£126.50
TF 200 bench frequency meter	£166.75

Bench digital multimeters	
DM 235 L.E.C. digital multimeter	£60.38
DM 350 L.E.D. digital multimeter	£83.38
TM 353 L.C.D. digital multimeter	£96.60
DM 450 L.E.D. digital multimeter	£113.85
TM 351 L.C.D. digital multimeter	£113.85

Pulse Generator	
TG 105 pulse generator	£97.95

Bench Function Generator	
TG 100 function generator	£90.85

Fully Portable Oscilloscope	
SC 110 Oscilloscope	£159.85

2" Video Monitor	
MON 1A 2" Video monitor	£109.25

Eprom Programmer	
PKW 5000 Eprom Programmer	£918.85

All prices include V.A.T. Official orders welcome. Mail order only, or callers at our warehouse by prior appointment. Barclaycard/Access welcome. Cheque/P.O.s, etc., with order. Large s.a.e. for complete Thandar list. All items POST FREE.

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex, SS9 5TY
Tel: Southend 527572

CALCULATORS

All equipment new boxed and fully guaranteed
Price includes V.A.T., Post and Packing

PRICES

ANY CASIO, SHARP OR TEXAS CALCULATOR SENT FOR £1 LESS THAN ANY OTHER ADVERTISED PRICE IN THIS MAGAZINE (subject to stock)

CASIO		
FX501P PROGRAMMABLE	£49.95	
FX502P PROGRAMMABLE	£69.95	
FA1 CASSETTE INTERFACE	£19.95	
FX501P with FA1	£69.95	
FX502P with FA1	£89.95	
FX100 10 DIGIT SCIENTIFIC	£14.95	
FX 68 B digit compact scientific	£18.95	
FX 510 B digit scientific best-seller	£18.95	
FX 7100 credit card scientific clock/alarm	£23.95	
FX 8100 B digit scientific clock/timer/alarm, etc.	£23.95	
BQ 1100 biorthyths	£16.95	

★ NEW		
FX 180P PROGRAMMABLE 38 step	£19.95	
FX 350P PROGRAMMABLE 38 step	£21.95	
FX 270P PROGRAMMABLE 38 step	£18.95	
FX 6100 similar to 8100 less calendar	£19.95	

SHARP		
POCKET COMPUTER 1211 with interface	£106.95	
EL 5101 PROGRAMMABLE 18 digit	£41.95	
EL 5100 PROGRAMMABLE 24 digit	£51.95	

TEXAS INSTRUMENTS		
TI 51-11 PROGRAMMABLE 32 step	£28.95	
TI 57 PROGRAMMABLE 50 step	£27.95	
TI 58 PROGRAMMABLE 480 step	£69.95	
TI 58C as above with constant memory and programme	£78.95	
TI 59 PROGRAMMABLE 980 step	£178.95	
PC 100C printer for TI 58/58C/59	£173.95	
TI PROGRAMMER	£131.95	

(* includes mains adaptor/charger)

LITTLE PROFESSOR	TEXAS ELECTRONIC LEARNING AIDS	
DATAMAN	LETTER LOGIC	£21.95
	SPEAK & SPELL	£39.95

COROLESS PRO FF 3000 up to 600 feet range	£139.95
COROLESS PHONE 4001 up to 500 feet range	£108.95
FLIP PHONE 788 with memory radial, easy to connect at extension	£26.95

MINIATURE V.H.F. P.M. TRANSMITTERS	
MINI MICRON, 50 yards range 100-108 MHz	£14.95
MICRON 2 100 yards range 100-108 MHz	£18.95
MICRON X 1000 yards range 95-115 MHz	£28.95

FULL RANGE OF CASIO, SHARP AND TEXAS CALCULATORS AVAILABLE
SEND P.O., CHEQUE, ACCESS NUMBER OR ADD 75P FOR C.O.D. (up to £100)

CALCULATOR SALES & SERVICE

FREEPOST, REDDITCH, WORCS, B97 4BR

GUITAR NOTE EXPANDER

If you've ever built a conventional fuzz/sustain unit, you may have been disappointed by the harshness of the sound. If so, we present the answer to your problems—soft clipping. Design by Q.A. Rice. Development by Plamen Pazov.

A good number of fuzzbox circuits have appeared in the past which attempt to emulate the sound of an overdriven valve amp; the majority of these look great on a scope but still sound rough. The chief characteristic of valve amps is the way they overload; rounding off the peaks as opposed to transistor circuits which clip off the peaks, producing predominant odd harmonics. FET amps produce overload in a similar way to valve amps, and a cheaper and better (or worse) way to obtain this is to use CMOS gates in the linear mode. Figure 1 shows the overload for a triangular waveform. In the final circuit we have used a very versatile and much under-used CMOS IC, the CD4007 dual complementary pair and inverter. One complementary pair is wired as a second inverter — the two inverters are used as amplifiers and give a combined gain of 60 dB. One of the remaining CMOS FETs is used as a voltage-controlled resistor which can vary between from several megohms to a few hundred ohms. The output of the amplifier is passed to a detector which controls the resistance of the FET, and this is fed back to various parts of the circuit to give the expansion and compression effects. Figure 2 shows the input/output characteristics for the various functions. The compressor is effective over a 30 dB range.

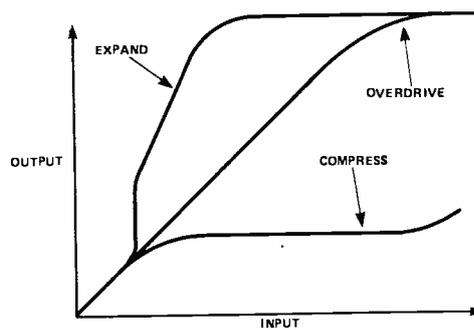


Fig.2 Input/output characteristics for various functions of the effects unit.

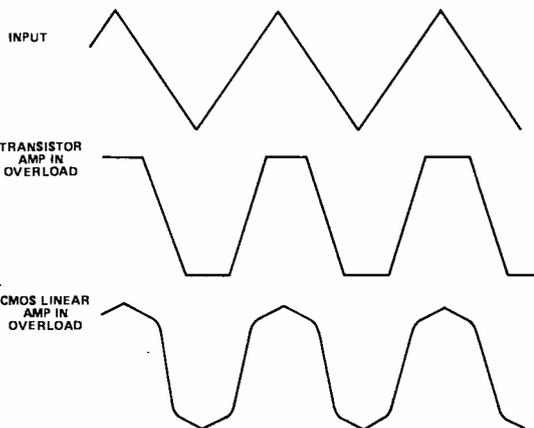


Fig.1 Clipping characteristics for two types of amplifier under overload conditions.


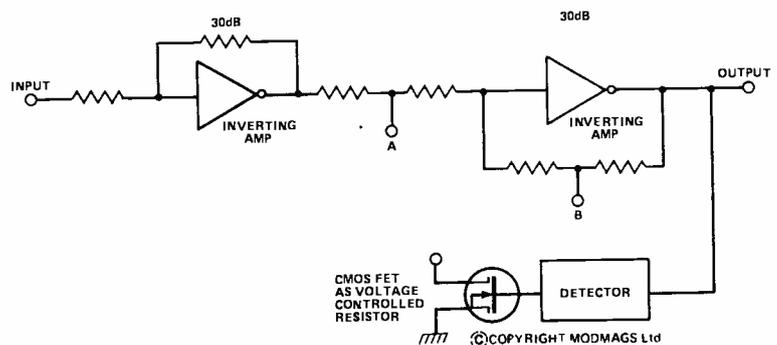


Fig.3 This diagram shows the basic principle of the unit.

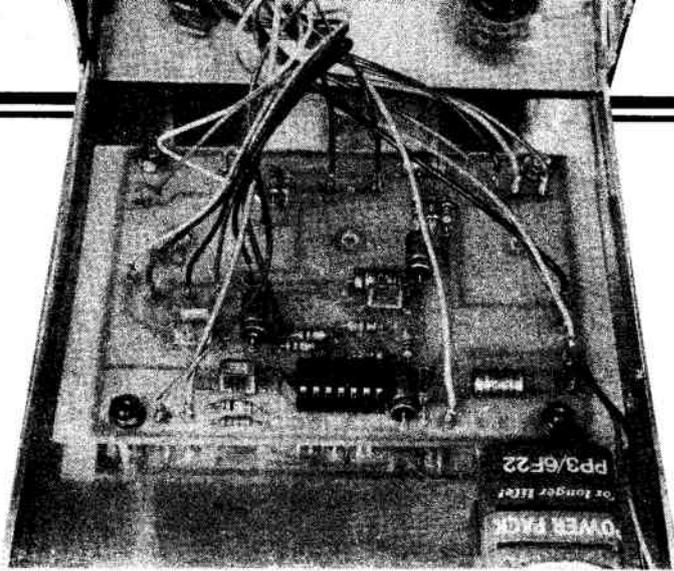

The unit has six functions, as follows:

1. Overall overdrive
 2. Overall compression, for sustaining
 3. High frequency compression, for bass overdrive
 4. Overall expansion, for sustained overdrive
 5. Mid expansion, for mid to high accentuation
 6. High frequency expansion, for high accentuation
- The effect of all these functions is variable, with the exception of overdrive.

Construction

The PCB is designed to accept the control components (SW2 and pots) if PCB-mounting of these components is preferred, to give a very compact construction. For the prototype this was not necessary as we used a custom-built housing (see Buylines). The box comes unpunched so if you want to arrange the controls and sockets differently you can get a drill and do your own thing. If you use a different housing remember that a metal case should be used to maintain proper screening.

We used a volume control with a built-in on/off switch instead of the standard method of using the input jack, as the latter approach produces a 9 V peak back into the source circuit and can cause damage if this circuit is active.

If the guitar has a low sensitivity pickup, it may be necessary to increase the value of R2 accordingly. The unit only consumes 3 mA so the batteries should last quite a while.

HOW IT WORKS

CMOS inverters may be used in the same manner as op-amps in the inverting mode, with the added bonus that they are self-biasing. The input is fed into IC1a, configured as a high gain, high impedance amplifier to give a gain of around 30 dB. This is decoupled and passed through a resistor pair to a second amplifier stage, which has a resistor pair in its feedback (see Fig. 3). If point A is now taken to ground via a resistance, gain is reduced; if this is done to point B, gain is increased. The final output is passed through a detector to give a voltage proportional to the signal level; this voltage is used to control the CMOS FET. If the FET is taken to point A or point B, then the overall gain is proportional to the final output signal. Thus if the output reduces the signal, it is self compressing. If it increases it, the signal is expanded. By making these gain variations frequency-dependant, we can accentuate or subdue the high frequency as required, at various break points to give the effects required. The output signal has to be attenuated to return it to its original level.

PARTS LIST

Resistors (all 1/4 W, 5%)	
R1, 10	100k✓
R2	3M3
R3, 4, 7	4k7✓
R5, 6	150k✓
R8	1M0
R9	470k✓
Potentiometers	
RV1	10k logarithmic
RV2	100k logarithmic with integral switch
Capacitors	
C1	220n polyester
C2, 3, 4, 6, 10, 11	2u2 16 V axial electrolytic
C5	22n polyester
C7	3n3 ceramic or polycarbonate
C8	1n0 ceramic or polycarbonate
C9	10n polyester
Semiconductors	
IC1	CD4007
D1, 2	OA91
Miscellaneous	
SW1	DPDT latching footswitch
SW2	2-pole 6-way rotary switch
SK1, 2	mono jack sockets
Battery-clip (PP3), metal box (see Buylines).	


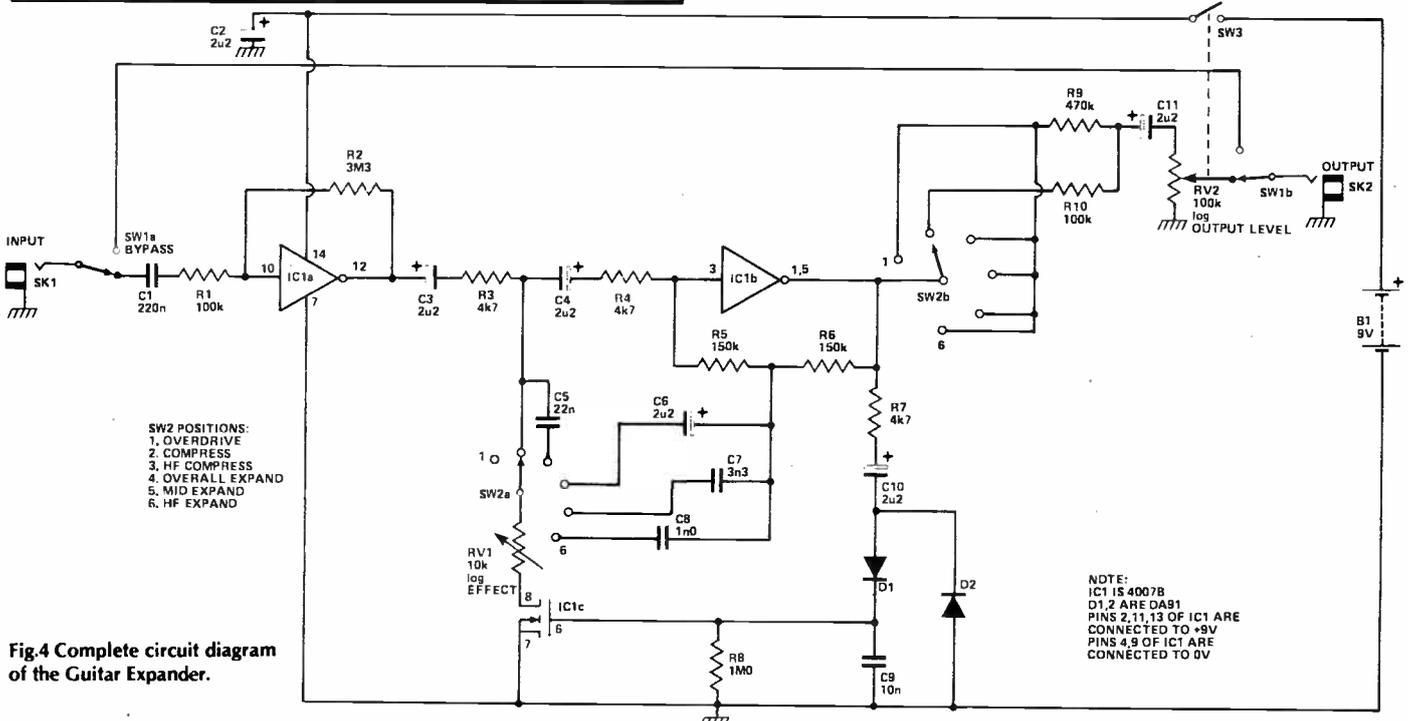
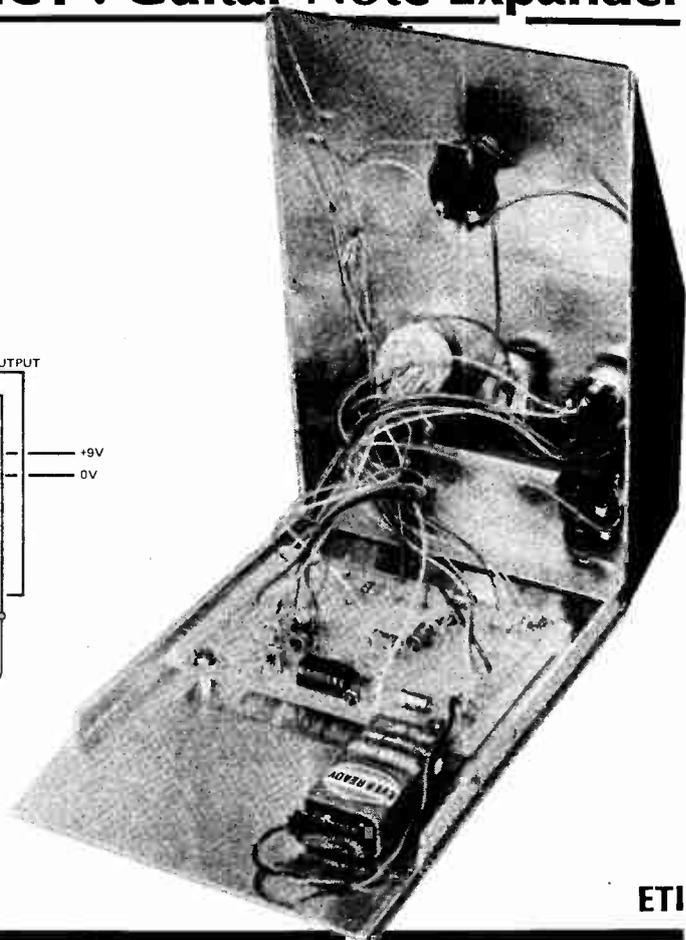


Fig.4 Complete circuit diagram of the Guitar Expander.

PROJECT : Guitar Note Expander

Fig.5 Component overlay.

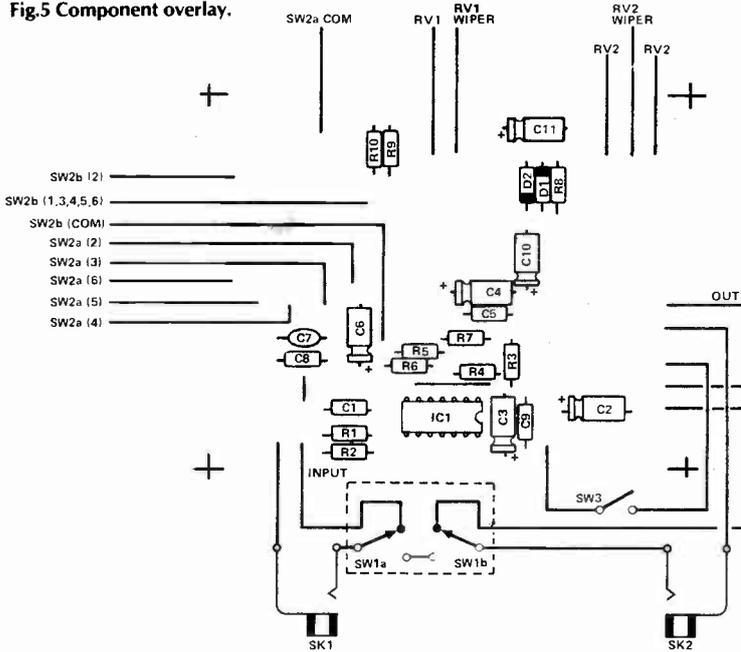

BUYLINES

As mentioned in the text, we have arranged for the construction of a custom case for this project, or indeed any other of your musical projects. H.L. Smith & Co Ltd, 287 Edgware Road, London W2 1BE will supply the box, ref. ETI-1 for the modest sum of £2.00.

All the other components should be readily available from most of the distributors advertising in this issue.

ETI

Join the Professionals...

Crimson modular audio amplifiers feature: ★Low values of transient and steadystate distortions ★Envelope distortion (below 500 Hz) less than 0.05% ★on-board electronic protection ★P.C.B. pin and edge connector termination ★Full range of complimentary components i.e. P.S.U.s, heatsinks etc. available from Crimson.

The Crimson range of amplifier modules are built to very high standards and have earned an enviable reputation in every field to which they have been applied. The boards come ready built and tested (guaranteed for two years) and can be used to advantage where high quality signal amplification is required. The power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge mode. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are catered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is basically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also on-board is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and gives the required boost for low output moving coil type cartridges. External components required are potentiometers for volume and balance, switches for signal routing and a regulated $\pm 15V$ D.C. power source (REG1). Complementing this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

Numerous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Power amplifier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review, August 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietary flight cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in Wireless World October/November 1980. Further details of how to use the modules are contained in the Users/Application Manual available at £0.50.

SPECIFICATIONS

Type	O/Pchms*	O/Pchms*	PSU	H/Sinks	Slew	S/N	Sensitivity	T.H.D. (typ)	F.R.	Size
CE 608	36	70	CP51	50mm	30V/5	110dB	775mV	0.0035%	1.5W/50KHz 3dB	80 120 25
CE1004	44	70	CP53	100mm	30V/5	110dB	775mV	0.0035%	1.5W/50KHz 3dB	80 120 25
CE1008	65	121	CP53	100mm	30V/5	110dB	775mV	0.0035%	1.5W/50KHz 3dB	80 120 25
CE1704	85	121	CP55	150mm FM1	30V/5	110dB	775mV	0.0035%	1.5W/50KHz 3dB	80 120 25
CE1708	125	121	CP55	150mm FM1	30V/5	110dB	775mV	0.0035%	1.5W/50KHz 3dB	80 120 25
CP3000	250	250	CP56	FM2	30V/5	110dB	775mV	0.0035%	1.5W/50KHz 3dB	161 102 35
CPR1 S	Output	775mV	REG1	1V/5	70dB	2.8W/WRMS	0.0035%	20mV/20KHz	138 80 35	
MC1 S	Output	2mV	REG1	1V/5	65dB	70mV/150	0.0035%	20mV/20KHz	80 120 35	
XO2 XO3	Output	775 2500mV	REG1	1V/5	90dB	775mV	0.01%	X over points	150 50 20	

*Power output is quoted WRMS and is given for two modules run off the same power supply. Higher powers are obtainable if using one module per P.S.U. or if using a stabilised P.S.U.

PRICES HELD FROM MAY TO FEB '80

Power Amplifier Modules	Power Supply Modules	Hardware
CE 608	£121.00 (PS1/180VA)	£19.50 50mm
CE1004	£124.50 (PS3/1150VA)	£23.50 100mm
CE1008	£127.50 (PS5/250VA)	£30.00 150mm
CE1704	£135.00 REG1	£19.30 FM1
CE1708	£135.00 TR6	£12.50 FM2

BARCLAYCARD

VISA

Master Charge

Card or write

pro forma

Prices include VAT, P&P to anywhere in the UK. COD £1.00 extra (lim. £100). Export - Pay by Access. Master Charge - Visa. Card or write pro forma.

PLEASE SEND ME MORE DETAILS OF ALL CRIMSON ELEKTRIK AMPLIFIERS

Name _____ Address _____



Crimson Elektrik

9 CLAYMILL ROAD, LEICESTER LE47JJ, ENGLAND. Tel 0533 761920 Telex 34694 Chanco G CRIMLEK

INTRUDER ALARMS

BRANDED INTRUDER ALARMS AT DISCOUNT PRICES FOR LIMITED PERIOD ONLY

Alarm with self-contained siren. Keyed and timed entry, using minimal power consumption on stand-by. With circuit fault indicator, 3 reed switches, 1 pressure mat, wire and full installation instructions. **£36.80**

Siren extension unit to increase range **£11.75**

Self-powered siren (sounds if separately attacked) **£25.00**

Self-powered bell (sounds if separately attacked) **£29.00**

Reed switches (surface) **£1.00**

Reed switches (flush) **£0.90**

Pressure Pad — 27" x 15" **£2.20**

Pressure Pad — 22½" x 6¾" **£1.60**

All above prices inclusive of V.A.T. and postage. Terms: Cash with order. Write to Yale Security Products, Wood Street, Willenhall, West Midlands WV13 1LA. Telephone: 0902 66911. Telex: 338251.

DISCO LIGHTING KITS!!!


First class constructional projects. c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 3 channel sound-to-light. 300 w/channel 1v — 100w input **£9.90**

LK3 2kW slider dimmer suitable for clubs/pubs. A professional unit c/w **FACE PLATE** **£8.90**

LK2 3 channel 3kW zero voltage firing 200mV — 100 watts input. **£17.90**

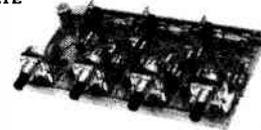
LK4 4 channel 4kW audio — forward/reverse auto — two speed ranges. **£16.50**



ALL KITS C/W circuit, comprehensive instructions & full parts guarantee

Carriage on above 70p

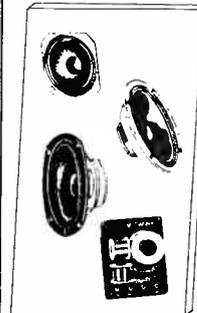Suitable case for LK 1/2/4 **£3.50**
100w spots ES or BC **£1.50**.
Coloured pigmy lamps **65p**.
8m rope lights **£49**



UNREPEATABLE HI-FI BARGAIN

3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

- ★ 6½" linen surround bass unit
 - ★ 5" mid-range unit
 - ★ 3" tweeter
 - ★ 3 way crossover, fixing screws & baffle
 - ★ 20 watts handling capability.
- Full instructions provided
Must be heard to be believed!!

£10.50 or 2 kits for **£20** Carr. **£1** per kit

SAXON ENTERTAINMENTS (ETI)
327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.
(01) 684 8007

Order by phone — Access/Barclaycard/C.O.D.
Open Mon. — Sat. 9am — 5pm.

CASTLE ELECTRONICS


SOUTH COAST MICRO CENTRE

Telephone Hastings (0424) 437875

TANGERINE

microtan 65 **£69**

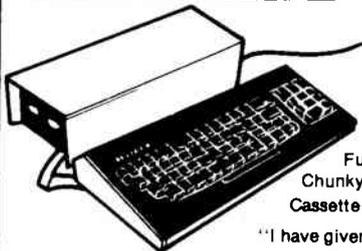Microtan 65 is the most advanced, most powerful, most expandable microcomputer available — it also happens to be the most cost effective.



6502 Microprocessor 1K Tanbug 1K User RAM Full TV Display **£79** (ready-built). 20-way KEYPAD—**£10**. TANEX—**£43**

1K 16 parallel I/O lines. Cassette Interface—1 serial I/O line. 2 x 16 BIT counter timers OPTIONS TK RAM total—32 parallel I/O lines. 4 x 16 BIT counter timers—RS232. 20MA current loop.

10K MICROSOFT BASIC—**£49**

System Rack—**£49** in black/tangerine in brushed aluminium.

Full Ascii Keyboard with numeric pad—**£60.85**. Cabinet available—**£20**. Lower Case option—**£9.48**.

Chunky Graphics Pack—**£6.52**. Tanram Full Memory Expansion to 40K—**£119.00**. Mini Motherboard—**£10.00**.

Cassette with counter—**£21.70**.

"I have given TANGERINE five bonus points for getting just about everything right"—E.T.I. Mag., May 1980.

video genie

WITH

- 16K user RAM plus extended 12K
- Microsoft BASIC in ROM •Fully TRS-80 level II software compatible •Self-contained, PSU, UHF modulator and cassette •Simply plugs into video monitor or UHF TV.

16K **£299**

Expander from **£195.00**

COMMODORE	8K	£399.00
	16K	£499.00
	32K	£649.00
SHARP MZ80	20K	£449.00
APPLE	16K	£599.00
	Epsom Printer	£349.00
plus BOOKS/MEMORIES/SOFTWARE				

ALL PRICES ADD 15% VAT. DELIVERY CHARGES WILL BE NOTIFIED
ACCESS AND BARCLAYCARD ORDERS TAKEN BY PHONE

7 CASTLE ST., HASTINGS, E. SUSSEX TN34 3DY Telephone: Hastings (0424) 437875

SHOP HOURS 0900 to 1730 MONDAY to SATURDAY. PERSONAL CALLERS WELCOME

Greenbank

Greenbank Electronics
(Dept T4E) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel: 051-645 3391)




TERMS, VAT, CWO. Cheques etc payable to Greenbank Electronics and crossed.
Add VAT at all prices at 15% except where stated otherwise. Post etc: UK 40p
(+6p VAT = 46p) per order. Export: NO VAT but add 40p (Eire), E1 (Europe) and
£3.50 elsewhere. Access: Barclaycard, Visa, telephoned orders accepted.
(Polys, universities, gov depts, etc can telephone their orders for immediate
despatch on account.)



QUARTZ

32.768KHz	£3.23	2 1/2" x 1" back of 91 £1.01
60 KHz	£8.95	2 1/2" x 3/4" 73p
100.0 KHz	£3.62	2 1/2" x 5" 79p
200.0 KHz	£3.92	2 1/2" x 1 1/2" £2.51
204.8 KHz	£3.92	3 1/2" x 3 1/2" 85p
262.144 KHz	£3.92	3 1/2" x 5 1/2" 95p
307.2 KHz	£3.92	4 1/2" x 1 1/2" £3.25
312.5 KHz	£3.92	3 7/8" x 1 1/2" £4.25
455.0 KHz	£4.95	0.1" Plainboard
1.000 MHz	£3.62	(no strips)
1.008 MHz	£3.92	3 1/2" x 2 1/2" 52p
1.280 MHz	£3.92	3 1/2" x 5" 79p
1.6 MHz	£4.25	3 1/2" x 1 1/2" £2.11
1.8 MHz	£4.25	Terminal pins £1.50/500
1.8432 KHz	£3.62	V-0 DIP board £1.50
2.000 MHz	£3.62	DIP breadboard £3.50
2.097152 MHz	£3.23	Spot face carrier £1.10
2.4576 MHz	£3.92	Pin location hole £1.02
2.50928 MHz	£3.62	
3.000 MHz	£3.62	
3.2768 MHz	£3.23	
3.579544 MHz	£1.95	
3.93216 MHz	£3.92	
4.000 MHz	£2.90	
4.032 MHz	£3.23	
4.096 MHz	£3.23	
4.194304 MHz	£3.23	
4.433616 MHz	£1.25	
4.608 MHz	£3.23	
4.800 MHz	£3.23	
4.9152 MHz	£3.23	
5.000 MHz	£3.23	
5.0688 MHz	£3.23	
5.120 MHz	£3.23	
5.185 MHz	£3.23	
5.488 MHz	£3.23	
5.625 MHz	£3.23	
6.144 MHz	£3.23	
6.400 MHz	£3.23	
6.5536 MHz	£3.23	
7.000 MHz	£3.23	
7.158 MHz	£3.23	
7.680 MHz	£3.23	
7.86432 MHz	£3.23	
8.000 MHz	£3.23	
8.08333 MHz	£3.62	
8.38860 MHz	£3.23	
8.96727 MHz	£3.23	
9.375 MHz	£3.92	
9.800 MHz	£3.92	
10.000 MHz	£3.23	
10.245 MHz	£3.23	
10.700 MHz	£3.23	
10.92 MHz	£3.92	
11.000 MHz	£3.92	
12.000 MHz	£3.92	
14.0 MHz	£3.23	
14.31818 MHz	£3.92	
16.000 MHz	£3.92	
18.000 MHz	£3.23	
18.432 MHz	£3.23	
20.000 MHz	£3.62	
20.1134 MHz	£3.23	
24.0 MHz	£3.92	
26.680 MHz	£2.10	
27.0 MHz	£3.92	
27.145 MHz	£3.92	
27.848 MHz	£3.92	
38.8666 MHz	£3.23	
48.000 MHz	£3.23	
100.000 MHz	£3.23	
116.000 MHz	£3.23	

UV 141, UV ERASER

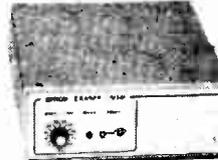

Two easy to use units designed for both the professional and amateur UV-prom user

- Features**
- Can erase up to 14 proms.
 - Special short wave ultraviolet tube
 - Erase time variable between 5 and 50 minutes in 5 minute steps (preventing over exposure which may shorten prom life)
 - Sliding tray carries proms on conductive foam
 - Safety interlock switch prevents the timing circuit from operating and switching on the tube with the tray open.
 - "Mains On" and "Tube On" indicators.
 - Complete instructions supplied.

Model UV 141. Price £77.70

Also available without timer as Model UV 140. Price £61.20

TEX MICROSYSTEMS "EPROMPT" UV ERASER



A low cost alternative to the above erasers (UV 140, 141) claimed by the manufacturer to erase up to 32 chips in 15-30 mins. This is the cheapest eraser we have seen. The unit has no timer, power switch or safety interlock switch. The user places up to 32 chips into loose conducting foam in the erasure tray (6 along the base, 8 on each side). The chips are held in place by the UV tube which sits in the tray (Unlike the UV 140/141, no special precautions have been taken to prevent the seepage of UV light, but the manufacturers state that incident light from this device is quite safe at distances above 12 inches.)

(Dimensions - 325 x 64 x 38mm)

EPROMPT ERASER Price £33

EUROCARD COMPUTER BOARDS

*Custom 80 Modular Z80 Based System. Details in preparation, free on request.

"BIG BOARD" Z80 COMPUTER KIT

We hope this item will be in stock by the time this advert reaches you, but please check to see before sending any money! Features: 64K Dynamic RAM, Floppy Disk Controller, 80 x 24 Char Video output £395, CP/M Disk Operating System to suit. £99.

MODULAR COMPUTER SYSTEM CARDS

A range of 'International' (114 x 203mm) size cards which may be purchased individually as desired, or to build up a complete system. Further details available on request. All boards are epoxy glass with gold plated edge plug

VDU A, B G (set of 3) £27.20
SC/MP P SC/MP CPU £9.40
MPA 7 Buffered SC/MP CPU £9.40
MZB-3 Z80-CPU £9.40
MXA-1 2K of 2102 £9.40
MXA-3 8K of 2114 £9.40
MXD-2 16K of 4116 £9.40
PRM-2 4K of 5204 £9.40
PRM-8 8K of 2708 £9.40
RRM-14 8K of 2516 + 6K of 2114 £9.40
SIO 2 RS-232 (two) £9.40
TPA-2 Tape Interface £9.40
IP-2 Input Port £9.40
OCR B Keyboard Input £9.40
OP-3 Output Port £9.40
PS-2 PROM Programmer £9.40
PSU-A4 Power Supply £9.40
PSU-B 5V Power Supply £9.50
PSU-C 2V Power Supply £9.50
13-slot backboard, can be used with most of the above boards. 13" x 4 1/4" x 1 1/2" £11.50

CMOS

These cut prices for Amateur Users and Export. Note: Industrial users - quantity prices available. Mostly Motorola, RCA

4000 18p	4042 80p	4095 £1.97	4410 £8.55	4531 £1.45
4001 25p	4043 90p	4096 £1.97	4411 £10.72	4532 £1.30
4002 25p	4044 90p	4097 £5.98	4412 12 1/2" £14.53	4534 £5.60
4006 95p	4045 £2.63	4098 £1.92	4415 25.24	4536 £3.60
4007 18p	4046 £1.10	4099 £2.00	4422 £5.66	4537L £26.10
4008 90p	4047 £1.71	4100 £1.92	4433 £12.30	4538 £1.20
4009 40p	4048 77p	4101 £1.69	4435 25.40	4539 97p
4010 50p	4049 45p	4102 £3.67	4450 £3.81	4541 £1.19
4011 25p	4050 49p	4103 £3.67	4451 £3.81	4543 £1.80
4012 18p	4051 80p	4104 £1.95	4461 £3.53	4549 £4.38
4013 50p	4052 80p	4105 £1.85	4462 £4.41	4552 £14.85
4014 84p	4053 80p	4106 92p	4490P £4.20	4553 £4.50
4015 84p	4054 £2.18	4107 £1.28	4490P £3.14	4554 £1.38
4018 45p	4055 £2.55	4108 £7.54	4500 £8.95	4555 79p
4017 90p	4056 £2.55	4109 £1.28	4501 29p	4557 £3.86
4018 95p	4057 £8.23	4110 £3.00	4502 £1.20	4557 £3.86
4019 45p	4058 £2.10	4114 £1.77	4503 70p	4558 £1.25
4020 95p	4059 £10.00	4160 £1.54	4505 £5.71	4559 £4.38
4021 £1.10	4063 £1.90	4161 £1.54	4506 50p	4560 £2.50
4022 £1.00	4066 55p	4162 £1.54	4507 55p	4561 81p
4023 27p	4067 £7.21	4163 £1.54	4508 £2.90	4562 £5.60
4024 79p	4068 77p	4164 90p	4510 99p	4566 £1.59
4025 27p	4069 27p	4165 £3.03	4511 £1.50	4568 £2.38
4026 £3.25	4070 30p	4166 £1.90	4512 80p	4569 £2.50
4027 90p	4071 25p	4192 £2.41	4514 £2.85	4572 40p
4028 84p	4072 25p	4193 £2.41	4515 £3.00	4580 £4.77
4029 99p	4073 25p	4194 £1.96	4516 £1.10	4581 £2.62
4030 74p	4075 25p	4208 £7.54	4517 £4.46	4582 £1.14
4031 £4.31	4076 £1.07	4257 £2.31	4518 £1.00	4583 90p
4032 £1.31	4077 29p	4160 90p	4519 80p	4584 90p
4033 £2.63	4078 29p	4161 90p	4520 £1.00	4585 £1.27
4034 £2.00	4081 27p	4162 90p	4521 £2.50	4597 £2.44
4035 £1.10	4082 27p	4163 90p	4522 £1.41	4598 £2.98
4037 £1.99	4085 £1.35	4174 90p	4526 £1.08	4599 £5.95
4038 £1.20	4086 £1.35	4176 £1.15	4527 £1.00	4700 £1.75
4039 £2.78	4089 £2.91	4194 £1.16	4528 £1.20	4528 £1.20
4040 £1.00	4093 80p	4408 £9.37	4529 £1.30	4530 70p
4041 £1.59	4094 £2.50	4409 £9.37	4530 70p	

74C

74C00 29p	74C01 29p	74C02 29p	74C03 29p	74C04 29p
74C05 29p	74C06 29p	74C07 29p	74C08 29p	74C09 29p
74C10 29p	74C11 29p	74C12 29p	74C13 29p	74C14 29p
74C15 29p	74C16 29p	74C17 29p	74C18 29p	74C19 29p
74C20 29p	74C21 29p	74C22 29p	74C23 29p	74C24 29p
74C25 29p	74C26 29p	74C27 29p	74C28 29p	74C29 29p
74C30 29p	74C31 29p	74C32 29p	74C33 29p	74C34 29p
74C35 29p	74C36 29p	74C37 29p	74C38 29p	74C39 29p
74C40 29p	74C41 29p	74C42 29p	74C43 29p	74C44 29p
74C45 29p	74C46 29p	74C47 29p	74C48 29p	74C49 29p
74C50 29p	74C51 29p	74C52 29p	74C53 29p	74C54 29p
74C55 29p	74C56 29p	74C57 29p	74C58 29p	74C59 29p
74C60 29p	74C61 29p	74C62 29p	74C63 29p	74C64 29p
74C65 29p	74C66 29p	74C67 29p	74C68 29p	74C69 29p
74C70 29p	74C71 29p	74C72 29p	74C73 29p	74C74 29p
74C75 29p	74C76 29p	74C77 29p	74C78 29p	74C79 29p
74C80 29p	74C81 29p	74C82 29p	74C83 29p	74C84 29p
74C85 29p	74C86 29p	74C87 29p	74C88 29p	74C89 29p
74C90 29p	74C91 29p	74C92 29p	74C93 29p	74C94 29p
74C95 29p	74C96 29p	74C97 29p	74C98 29p	74C99 29p

74LS

74LS00 14p	74LS01 14p	74LS02 14p	74LS03 14p	74LS04 14p
74LS05 14p	74LS06 14p	74LS07 14p	74LS08 14p	74LS09 14p
74LS10 14p	74LS11 14p	74LS12 14p	74LS13 14p	74LS14 14p
74LS15 14p	74LS16 14p	74LS17 14p	74LS18 14p	74LS19 14p
74LS20 14p	74LS21 14p	74LS22 14p	74LS23 14p	74LS24 14p
74LS25 14p	74LS26 14p	74LS27 14p	74LS28 14p	74LS29 14p
74LS30 14p	74LS31 14p	74LS32 14p	74LS33 14p	74LS34 14p
74LS35 14p	74LS36 14p	74LS37 14p	74LS38 14p	74LS39 14p
74LS40 14p	74LS41 14p	74LS42 14p	74LS43 14p	74LS44 14p
74LS45 14p	74LS46 14p	74LS47 14p	74LS48 14p	74LS49 14p
74LS50 14p	74LS51 14p	74LS52 14p	74LS53 14p	74LS54 14p
74LS55 14p	74LS56 14p	74LS57 14p	74LS58 14p	74LS59 14p
74LS60 14p	74LS61 14p	74LS62 14p	74LS63 14p	74LS64 14p
74LS65 14p	74LS66 14p	74LS67 14p	74LS68 14p	74LS69 14p
74LS70 14p	74LS71 14p	74LS72 14p	74LS73 14p	74LS74 14p
74LS75 14p	74LS76 14p	74LS77 14p	74LS78 14p	74LS79 14p
74LS80 14p	74LS81 14p	74LS82 14p	74LS83 14p	74LS84 14p
74LS85 14p	74LS86 14p	74LS87 14p	74LS88 14p	74LS89 14p
74LS90 14p	74LS91 14p	74LS92 14p	74LS93 14p	74LS94 14p
74LS95 14p	74LS96 14p	74LS97 14p	74LS98 14p	74LS99 14p
74LS100 14p	74LS101 14p	74LS102 14p	74LS103 14p	74LS104 14p
74LS105 14p	74LS106 14p	74LS107 14p	74LS108 14p	74LS109 14p
74LS110 14p	74LS111 14p	74LS112 14p	74LS113 14p	74LS114 14p
74LS115 14p	74LS116 14p	74LS117 14p	74LS118 14p	74LS119 14p
74LS120 14p	74LS121 14p	74LS122 14p	74LS123 14p	74LS124 14p
74LS125 14p	74LS126 14p	74LS127 14p	74LS128 14p	74LS129 14p
74LS130 14p	74LS131 14p	74LS132 14p	74LS133 14p	74LS134 14p
74LS135 14p	74LS136 14p	74LS137 14p	74LS138 14p	74LS139 14p
74LS140 14p	74LS141 14p	74LS142 14p	74LS143 14p	74LS144 14p
74LS145 14p	74LS146 14p	74LS147 14p	74LS148 14p	

READER'S DESIGNS

CARAVAN LIGHTS CHECKER

A project that will pay for itself in the first ticket from the police that you don't collect. Submitted by Graham Packer of Soutergate.

Many ETI readers, besides boring the pants off their neighbours with dreary electronics, are just as anti-social when it comes to cluttering up the highways with their sluggish caravans. Now that they (and their caravans) are in hibernation until summer, the time is at hand to reach for soldering iron and component catalogue and make amends.

Most caravans receive their power supply and lighting signals by way of a multiway plug and socket, terminating on a 'choc-block' terminal strip under the front seat/bed. This is where the 'guts' of the project goes. The cable is merely chopped and the large plastic box inserted. The display unit can be mounted anywhere that is visible from the driving mirror and double sided tape (the thick foamy kind) may be used to hold it on the wardrobe or side of the kitchen unit.

For once, no complicated electronics; just the most basic of electromagnetic devices, the relay, albeit in its more refined form of the reed insert. These reeds, originally developed for electronic telephone exchanges, need about 20 to 50 ampere turns to pull them in. The current drawn by a caravan sidelight, brakelight or indicator lamp can be found by calculation (or just asking people) and the correct number of turns wound around the reed.

Reed inserts may be obtained from a number of sources and be of dubious vintage. Therefore, it's best to wind on 40 or 50 turns of 22 swg insulated wire and check them out first with the test circuit shown.

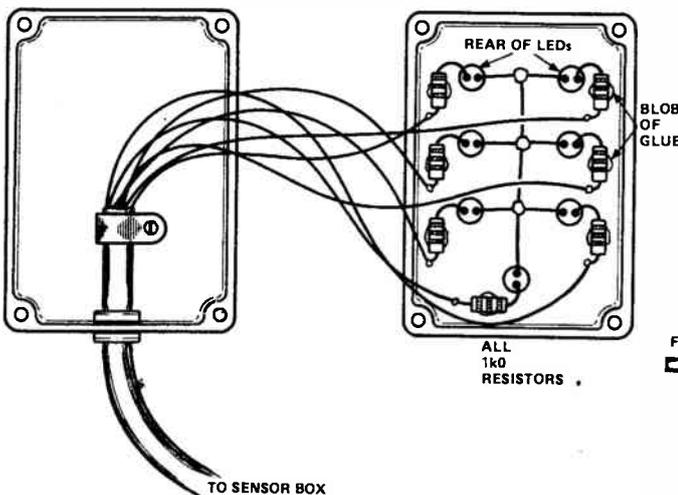


Fig. 1 Construction details of the display box.

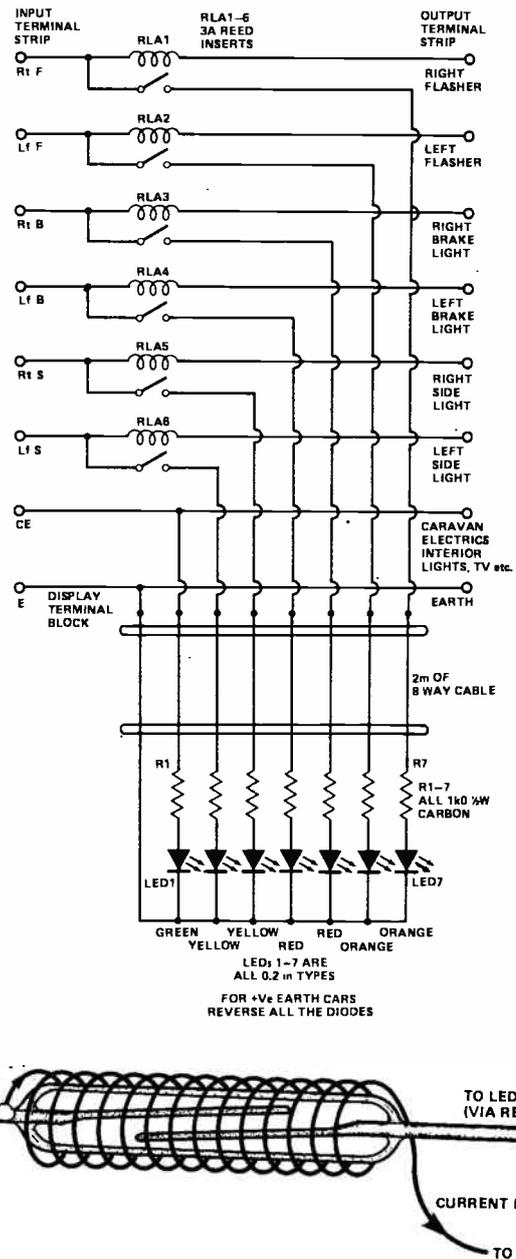


Fig. 2 Circuit diagram with relay assembly/wiring details.

Fig. 3 Construction details of the sensor box.


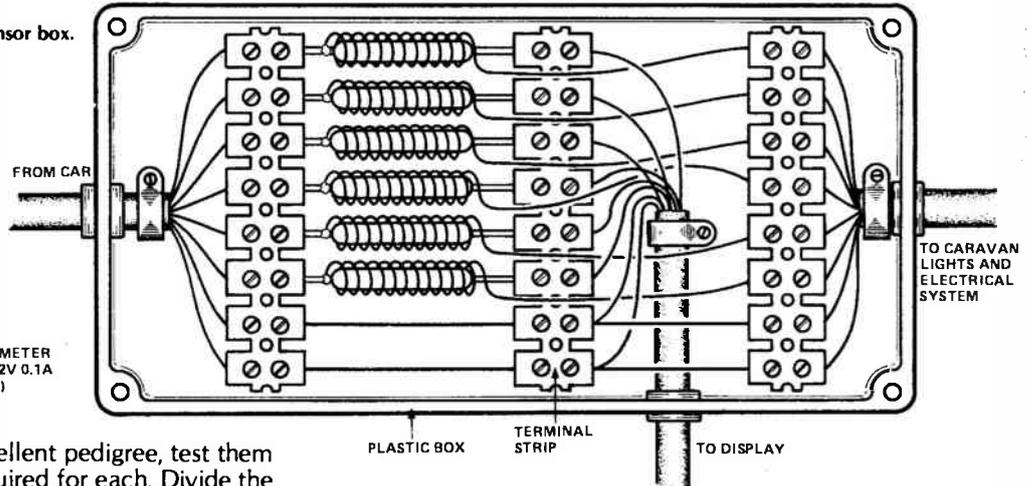


Fig. 4 This simple circuit can be used to check out reed relays.

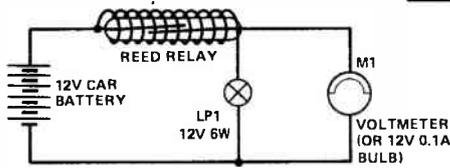

If the reeds do not have an excellent pedigree, test them and decide how many turns are required for each. Divide the ampere turns by the current to be drawn and there's the number you need. Add 25% for luck. As a rule of thumb, 6 W sidelights need about 40 turns in two or three layers, or 20 turns if they are fore and aft. You could put separate current sensors in each line and make your caravan look like a mobile Blackpool Illuminations! Brake and indicator lights need only 12 turns.

Solder one end of a length of 20 swg insulated wire to one end of a reed and wind carefully along its entire length. Be careful not to break the glass as it will slice into your fingers with the greatest of ease. Hold the reed in your left hand with the loose end of wire pulled taut by your little finger and apply cyanoacrylate (Superglue). Two days later it should be possible to remove the completed current sensing relay from your hand!

Install the reeds between the two choc-blocks as shown in the diagram by holding the terminal blocks on a flat surface to ensure that no twisting action takes place when the assembly is finally installed in its box. Cyanoacrylate may now be used to mount the complete assembly in its box. Complete the wiring and install in your beloved behemoth.

The green 'power-on-to-the-caravan' light only consumes 15-20 mA and as long as the caravan is being pulled daily (as it would be on holiday) the overnight drain is negligible.

A complete kit of parts, including solder and superglue is available from Packer Communications, Bridge End Barn, Soutergate, Cumbria LA17 7TW for £12.75 including post and VAT.

ETI

OSCILLOSCOPES

How to use them - How they work · by Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models is available. But which is the right scope for a particular application? Which features are essential, which not so important? What techniques will get the best out of the instrument?

Ian Hickman, experienced in both professional and hobbyist electronics, has written this book to help all oscilloscope users - and potential users. After introducing basic principles for readers new to the subject, he explains in detail the features of typical simple and advanced real-time oscilloscopes, plus accessories such as probes and cameras. He advises on how to choose and operate scopes, and how to avoid common pitfalls; he also describes special-purpose instruments, from small portable scopes to storage scopes and spectrum and logic analysers. Finally, to give readers a better understanding of how oscilloscopes work, he explains the principles of the cathode-ray tube and basic scope circuitry.

NEW BOOK

Illustrated with many photographs and two-colour diagrams, the book will appeal to everyone who needs to know about oscilloscopes, from the school student to the graduate, from the hobbyist to the technician.

Available from your local bookseller or in case of difficulty from the Publisher.

BROADEN YOUR SCOPE NOW!

Cut out this coupon and return it to Patricia Davies, Marketing Manager, at the address below.

Please send me copy/copies of Oscilloscopes by Hickman: 0 408 00472 X Illustrated paperback, 128 pages (216 x 138mm) at £3.45 each.

I enclose a cheque/PO for £ _____ in total payment

From _____

Address _____

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

ETIPRINTS

ETIPRINTS offer you the easy way to produce high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

PARTS LIST

040A	ETI 80 VCO/VCLFO	Feb 80	Speed Control		
040B	ETI 80 PSU	Feb 80	DTM Switching Board		
	Tuning Fork		RIAA Preamp		
	Hi-Lo Filter		047C	ETI 80 Envelope Shaper	Sep 80
	Coin Toss			TV Sound	
041A	Audiophile Driver Amp	Mar 80		Survival	
	VCA		048A	Sustain/Fuzz Box	Oct 80
	Signal Tracer			Flash Trigger	
	Heater Controller Main Board			FM Radio Control Receiver:	
	Electromyogram			(Top side)	
041B	ETI 80 VCM	Mar 80		(Bottom side)	
	Heater Controller Sensor			FM Radio Control	
046A	ETI 80 Dual VCA	Aug 80		Transmitter	
	100 W Power Amplifier		048B	Vocoder Slew Rate Control	Oct 80
046B	Capacitance Meter	Aug 80		Vocoder Output Amp	
	US Alarm			Vocoder Input Amp	
	BGM 100 W Amplifier			Vocoder PSU	
	Logic Tester			Vocoder LED PPM Display	
	100 W Power Amp		048C	Cassette Interface	Oct 80
047A	Digital Test Meter	Sep 80		ETI 80 Monitor Amp	
047B	Vocoder Internal Excitation	Sep 80	049	AF Generator	Nov 80
				Multi-Option Board	
				Space Invasion PSU	

BUYLINES

Sheets for Sep 79, Dec 79, Jan 80 and April - July 80 are temporarily out of stock. Earlier ETIPRINT sheets are available.

Send a cheque for PO (payable to ETI) for £1.20 per sheet with details of the project for which you require an ETIPRINT, and the month and year of publication to:

ETIPRINTS,
ETI,
145 Charing Cross Road,
London WC2H 0EE.

HOW IT WORKS


Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ETIPRINTS

The **SENSATIONAL** CROFTON Offer

9" metal cased monitors
at the lowest price ever –
£48.50 plus VAT and
P & P.

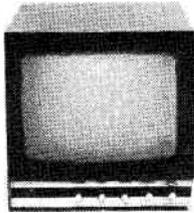P4 phosphor standard.
P31 and P39 available
at an extra £11.50 total.



Sony colour camera type
2010P only £375.00 total
including VAT and P & P.
12v operation IV
composite video out,
adapter box and
modulator available for
£25.00 total when
purchased with camera.
Normally £69.50.



Ask for Crofton Mail
Order Catalogue.



All major credit cards accepted.

All items subject to availability. The above prices include VAT
Carriage will be charged at cost

Phone or write to

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middx TW1 4AD.

Tel: 01-891 1923/1513

MICROPROCESSORS, MEMORIES, TTL

MICROPROCESSORS

Z80 CPU	6.84
Z80 CTC	4.75
Z90 PIO	4.75
Z80 SIO-0	20.11
Z80 SIO-1	20.11
Z80 SIO-2	20.11
Z80 DART	13.44
Z80 DMA	17.62
Z80A CPU	8.23
Z80A CTC	5.78
Z80A PIO	5.78
Z80A SIO-0	24.17
Z80A SIO-1	24.17
Z80A SIO-2	24.17
Z80A DART	21.02
Z80A DMA	21.02
6800	3.82
6802	5.74
6809	18.94
6810	1.43
6821	1.93
6840	5.87
6850	1.95

TTL

74LS 04	0.21
74LS 05	0.21
74LS 08	0.20
74LS 09	0.21
74LS 10	0.20
74LS 11	0.21
74LS 12	0.21
74LS 13	0.41
74LS 14	0.71
74LS 15	0.21
74LS 20	0.20
74LS 21	0.21
74LS 22	0.21
74LS 26	0.27
74LS 27	0.21
74LS 28	0.25
74LS 30	0.20
74LS 32	0.20
74LS 33	0.25
74LS 37	0.25
74LS 38	0.25
74LS 40	0.20
74LS 42	0.56
74LS 47	0.58
74LS 49	0.86
74LS 51	0.20
74LS 54	0.21
74LS 55	0.21
74LS 73	0.30
74LS 74	0.27
74LS 75	0.42
74LS 76	0.30
74LS 83	0.76
74LS 86	0.26
74LS 90	0.52
74LS 91	1.13
74LS 92	0.56
74LS 93	0.55
74LS 95	0.68
74LS109	0.36
74LS112	0.36
74LS113	0.36
74LS114	0.36
74LS122	0.63
74LS123	0.81
74LS124	1.49
74LS125	0.41
74LS126	0.41
74LS132	0.71
74LS136	0.41
74LS138	0.56
74LS139	0.56

TTL

74LS145	1.06
74LS151	0.49
74LS153	0.49
74LS155	0.70
74LS156	0.70
74LS157	0.50
74LS158	0.56
74LS160	0.61
74LS161	0.61
74LS162	0.61
74LS163	0.61
74LS164	0.71
74LS174	1.06
74LS175	0.84
74LS181	2.10
74LS190	0.85
74LS191	0.85
74LS192	0.97
74LS193	0.97
74LS194	0.58
74LS195	0.58
74LS196	0.96
74LS197	0.96
74LS221	0.90
74LS240	1.41
74LS242	1.19
74LS243	1.19
74LS244	1.18
74LS245	1.69
74LS247	0.57
74LS248	1.05
74LS249	1.05
74LS251	0.64
74LS253	0.64
74LS258	0.56
74LS259	1.61
74LS273	1.37
74LS279	0.51
74LS283	0.63
74LS293	0.73
74LS366	0.54
74LS367	0.54
74LS368	0.54
74LS373	1.11
74LS374	0.70
74LS375	0.70
74LS377	1.37
74LS378	1.03
74LS379	0.78
74LS386	0.41
74LS390	0.96
74LS393	0.85

MOS MEMORIES

2708 1kx8	
450ns	3.25
2716 2kx8	
450ns	5.75
2114 1kx4	
200ns	2.50
4027 4kx1	
200ns	1.65
4116 16kx1	
150ns	2.95
4116 16kx1	
200ns	2.50

8-BIT CONVERTERS

ZN425E(A/D)	3.50
ZN427E(A/D)	6.28
ZN426E(D/A)	3.00
ZN428E(D/A)	4.78
ZN429E(D/A)	2.10
Data Converter Handbook	1.00

TTL

74LS 00	0.20
74LS 01	0.21
74LS 02	0.20
74LS 03	0.20

All devices brand new, full spec. and fully guaranteed. Please add 15% VAT (and 50p post and packing on orders under £10). All orders despatched by return of post. E.&O.E.

Computer Co. Ltd., Hewitt House
Northgate Street, Bury St. Edmunds
Suffolk IP33 1HQ

Tel: (0284) 701321 Telex: 817682

MIDWICH



68
LARGE
PAGES

The larger
Catalogue
that means

FREE POSTAGE
IN U.K.

ADDITIONAL
DISCOUNTS

KEEN PRICES

GUARANTEED
SATISFACTION

GOOD STOCKS

We pay postage

Semi-Conductors • I.C.s • Opto-
devices • Rs and Cs in great variety
• Pots • Switches • Knobs •
Accessories • Tools • Materials •
Connectors


ELECTROVALUE

**FREE
FOR THE
ASKING**

ELECTROVALUE LTD. (Dept. HE4) 28 St. Jude's Road, Englefield Green, Egham, Surrey
TW20 0HB Telephone: (STD 0784) (London 87) 33603. Telex: 264475


PCB FOIL PATTERNS

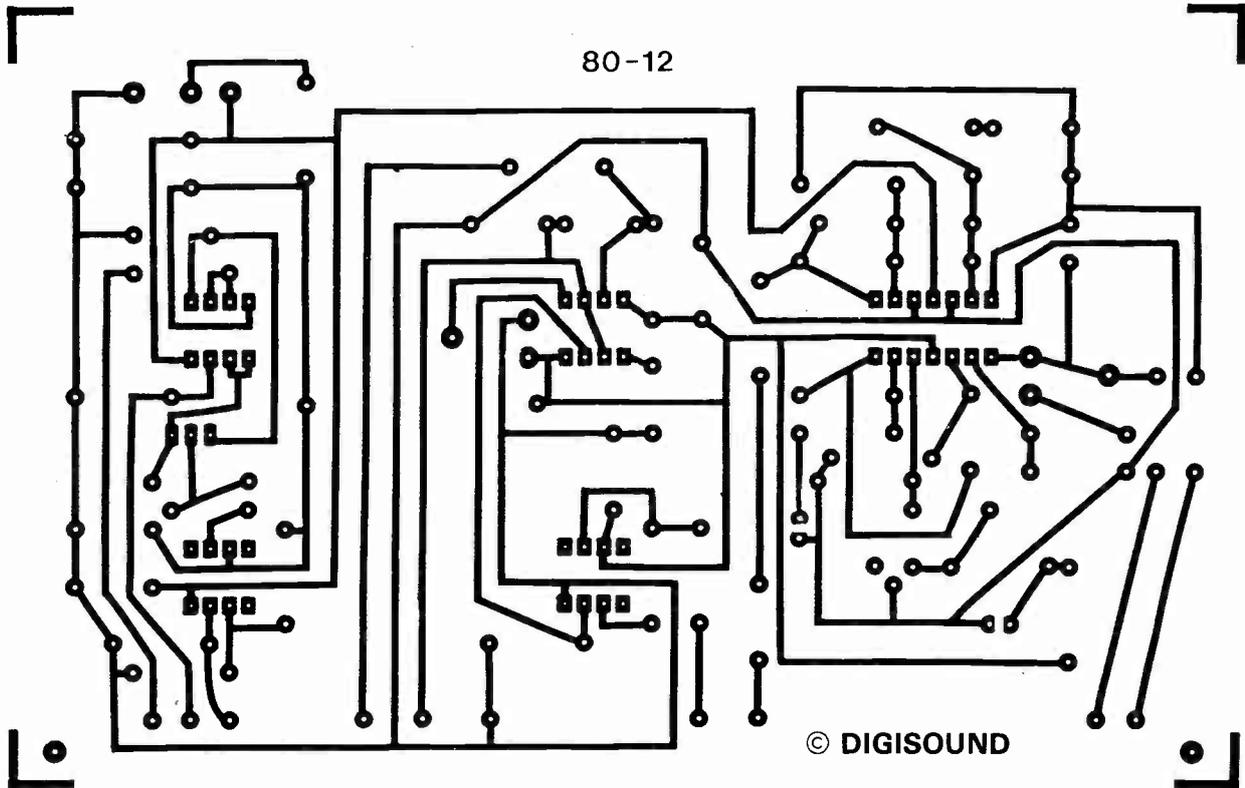
Please note that the foil pattern for the VCSA is too large to go into the magazine. A large SAE will secure a photocopy.





Above: Foil pattern for this month's Project 80 module. Note that Digisound hold the copyright on this board and firms may not reproduce the PCBs for sale.

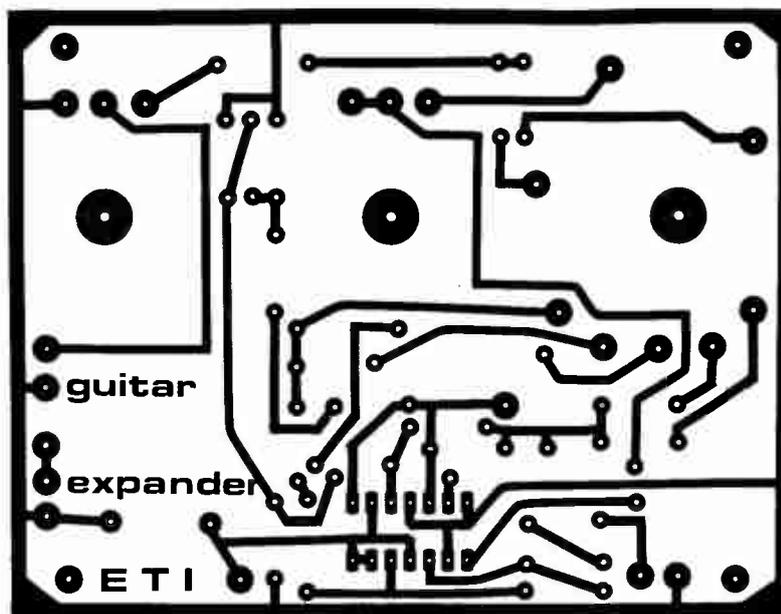Right: Foil pattern for the guitar expander.




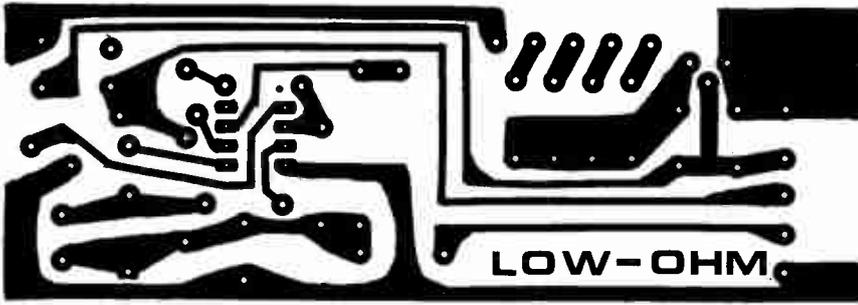

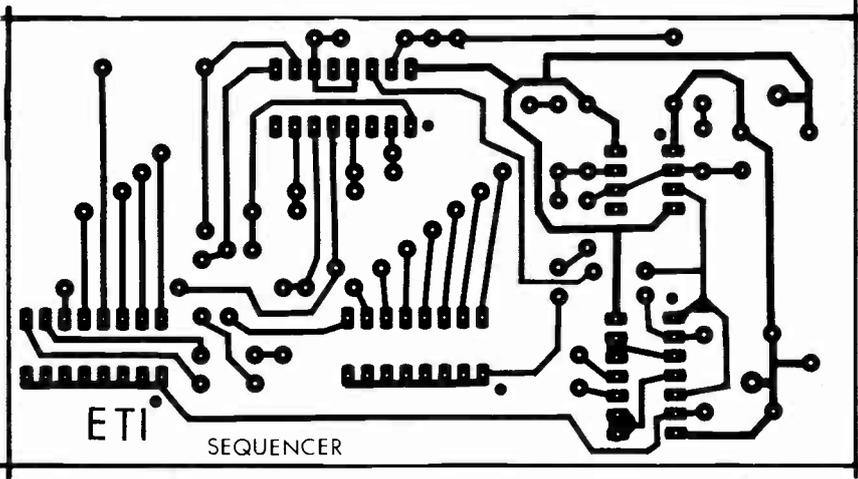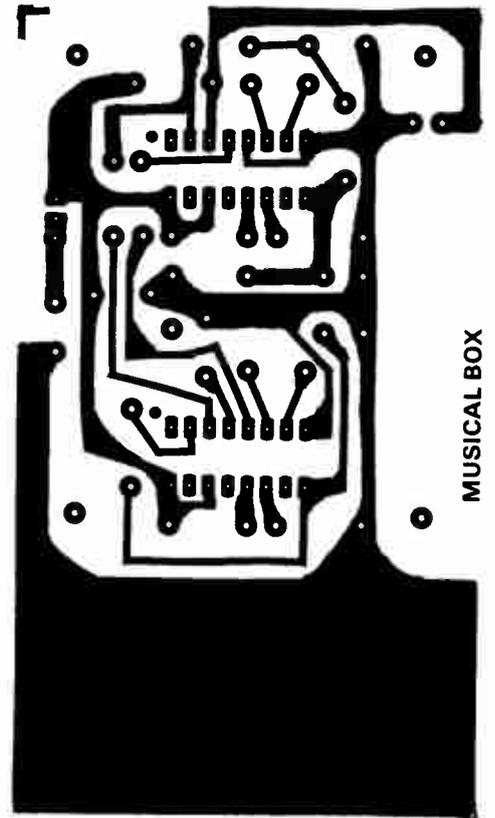Above: The Low-ohm Meter foil pattern.
Right: Musical Box PCB — this has been designed to fit into the specified case.



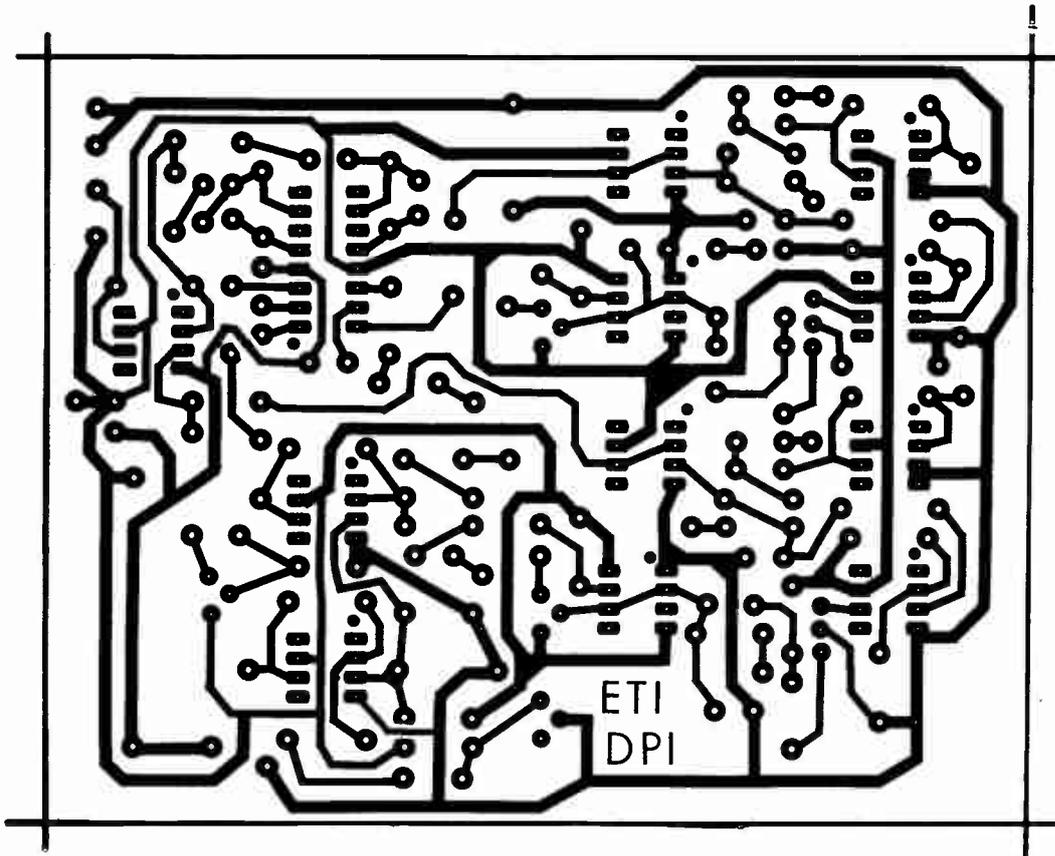Above and below: The two foil patterns for the ETI Drum Machine.



HAMEG

OSCILLOSCOPES

Top Performance
In Every Range



HM 307

HM 307 £138

Y: Bandwidth DC-10MHz (-3dB) • Sensitivity 5mV-20V/cm (±5%)
X: Timebase 0.2s-0.2µs/cm (±5%) • Triggering 2Hz-30MHz (3mm)
Built-in component tester • Calibrator • Screen 6x7cm • 1kV

HM 312 £220

Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 5mV-20V/cm (±3%)
X: Timebase 0.2s-40ns/cm incl. x5 Magn. • Trig. 3Hz-30MHz (4mm)
Dual trace • X-Y Operation • Calibrator • Screen 8x10cm • 2kV

HM 412 £350

Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 2mV-20V/cm (±3%)
X: Timebase 2s-40ns/cm incl. x5 Magn. • Trig. DC-40MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Sweep delay • Overscan, Trigger, Delay indications • Trigger filter
Z-Modulation • Calibrator • Graticule illumination • 2kV

HM 512 £580

Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/cm (±3%)
X: Timebase 5s-20ns/cm incl. x5 Magn. • Trig. DC-70MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Reset • Overscan, Trigger, Ready, Delay indications
var. Hold-off • Z-Modulation • Graticule illumination • 12kV

HM 812 £1,458

Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/div. (±3%)
X: Timebase 5s-20ns/div. incl. x5 Magn. • Trig. DC-70MHz (0.5div.)
Dual trace analog storage with var. Persistence and Auto-Storage
Algebr. addition • X-Y Operation • Screen 8x10div. (7.2x9cm)
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Overscan, Trigger, Ready, Delay, AS indications
var. Hold-off • Z-Modulation • X-Guard circuit • Calibrator • 8.5kV



HM 812
Storage

For more information
contact:

HAMEG LTD. 74-78 Collingdon Street LUTON
Bedfordshire LU1 1RX Telephone (0582) 413174 Telex 825484

Prices U. K.
List Ex. VAT

Happy Memories

4116 200ns	£2.25	2114 200ns	£2.95
2114 450ns	£2.20	2716 5 volt	£5.25
2708 450ns	£3.95		

MEMOREX SOFT-SECTORED MINI-DISCS for
PET, TRS-80, etc. Supplied in **Free Library Case**
£19.95 per 10

Low Profile I.C. Sockets by Texas

Pins	8	14	16	18	20	22	24	28	40
Pence	10	11	12	16	17	20	21	28	37

Memory Upgrade Kits for Apple, 2020, TRS-80,
etc. **from £18** please phone

Quantity prices available on request. Government
and Educational Orders welcome. Trade accounts
opened.

**ALL PRICES INCLUDE V.A.T. POSTAGE FREE ON
ORDERS OVER £15, OTHERWISE ADD 30p**

Access and Barclaycard Welcome

HAPPY MEMORIES

Dept. ET1
Gladestry, Kington
Herefordshire HR5 3NY
Telephone (054422) 618

OWO SCIENTIFIC NEW SUPERBOARD 3



The special offer of the century (only Swanley could do it!) — for just £188 we will supply Superboard 3 with a free power supply and modulator kit and our free guard band kit (a brilliant breakthrough in itself for this kit extends the display to 32 x 32, gives 1200 and 300 Baud tape speeds, increases the computing speed by 50% and converts the display to 50Hz for flicker free viewing). Guard band kit is also supplied separately for £10. 4K extra ram £18.95. Case £27. Cassette recorder £17. Cognon improved monitor rom £29.80. Assembler/editor tape £25. Word processor program £10. Display expansion kit 30 lines x 54 characters for Superboard 2 (Not 3) £20. Cheapa memory expansion offer — Buy a 610 expansion board with 8K ram on board and space for another 16K for £159 and get a free 5V 4A power kit and any extra ram you want for £3/K. Buy a minifloppy disc drive + case + power supply + DOS to £275 and we will do the extra ram for £2/K (max. 16K). New Series 2 Challenger C1P — cheapa 4K version £202. Ohio 8K version (illustrated) £259.

PRINTERS



Buy any of the below and get a free interface kit and word processor programme for UK101 or Superboard 2 — OKI Microline 80 (illustrated) £329. Base 2 800MST £299. Saikoshi GP80 £225.

MEMORY CHIPS
2114 450ns £2.15. 4116 200ns £2.83. 4027 £1.30. All low current.

★ SINCLAIR PRODUCTS

Sinclair products only are all post free. SC110 Oscilloscope £139. Adapter £4. Rechargeable batteries £7.95. X1 probe £8.95. X10 probe £9.95. Carry case £8.50. PFM200 £54.50. Adapter £4. Case £1.73. connector kit £11.27. PDM 35 £32.95. adapter £4. case £1.73. DM235 £86.50. DM350 £78.50. DM450 £107.95. adapter £4. case £8.80. rechargeable betts £7.95. Microvision TV £69. adaptor £8.88.

★ BATTERY ELIMINATORS

3-way type 6/7½/9V 300ma £3.50. 100ma radio types with press studs 9v £4.95. 9+9v £8.25. Car converter 12v input. output 3/4½/5/7½/9v 800ma £3.04.

★ BATTERY ELIMINATOR KITS

100ma radio types with press-studs 9v £1.79. 9+9v £2.50. Stabilized 8-way types 3/4½/6/7½/9/12/15/18v 100ma £3.12. 1 Amp £8.30. Stabilized power kits 2-18v 100ma £3.12. 1-30v 1A £8.50. 1-30v 2A £15.30. TTL and computer supplies 5V stabilized 1½A £9. 3A £12. 6A £20. 12v car converters 6/7½/9v 1A £1.62.

★ TV GAMES

Stunt cycle chn + kit £20.95. AY-3-8800 + kit £12.95. AY-3-8550 + kit £9.26.

★ PRINTED CIRCUIT MATERIALS

PCetching kit: economy £3.42. standard £6.78. 40 sq ins pcb 50p. 1 lb FeCl3 £2.20. Etch resist pans: economy 50p. delo 90p. Drill bits 1/32" or 1mm 30p. Etching dish 92p. Laminata cutter £1.30.

★ BI-PAK AUDIO MODULES

AL30A £4.53. PA12 £9.31. PS12 £1.75. T53B £2.90. S450 £27.90. AL60 £5.62. PA100 £19.24. SPM80 £5.26. BMT80 £5.36. Stereo 30 £24.14. AL80 £3.56.

★ COMPONENTS

1N4148 1.5p. 1N4002 3.7p. NE555 8 dit 26p. 7418 dit 20p. bc182. bc184. bc212. bc214. bc547. bc549 8.1p. Resistors 5% ¼W E12 10R to 10M 1.5p. 0.9p for 50+ of one value. Polyester capacitors 150v 01.5. 068ml 2.9p. 047. 1mf 4.4p. 01mf 3.3p. 022. 033mf 3.7p. 15. 22. 33mf 5.4p. 47mf 6.6p. Polystyrene capacitors E12 63V 10 to 1000pf 4p. 1n2 to 10n 5p. Ceramic capacitors 50v EB 22pf to 47n 2.5p. Electrolytic capacitors 50v 5. 1. 2mf 8p. 25V 5. 10mf 6p. 16v 22. 33mf 8p. 47mf 5p. 100mf 7p. 330. 470mf 9p. 100mf 11p. ZENERS 400mw E24 2v7 to 33v 7p. Preset pots subminiature 0 1W horiz or vert 100 to 2M2 8p. ic sockets B dit 8.7p. 14 dit 10.1p. 16 dit 12p.

SWANLEY ELECTRONICS

Dept. ET1, 32 Goldcol Rd, Swanley, Kent, BR8 5EZ
Telephone Swanley 64851. Please add 45p postage, except on Sinclair products. Add VAT except on sections marked with a ★ which already include it. Late 27p post free. No VAT on overseas orders which are welcomed. Official orders welcome.

CHROMATHEQUE 5000 5 CHANNEL LIGHTING EFFECTS SYSTEM



Panel size 19.0" x 3.5".
Depth 7.3"

**COMPLETE KIT
ONLY
£49.50 + VAT!**

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

**COMPLETE KIT
ONLY
£49.90 + VAT!**

**MATCHES THE
CHROMATHEQUE 5000
PERFECTLY!**


Panel size 19" x 3.5". Depth 7.3"



Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

SP2-200 2-CHANNEL 100W AMPLIFIER

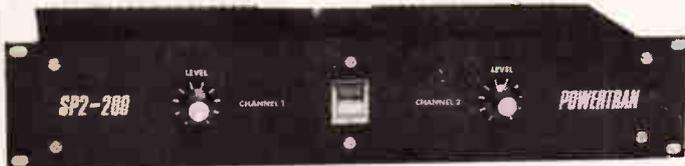

Panel size 19.0" x 3.5". Depth 7.3"

NEW!

**COMPLETE KIT
ONLY
£64.90 + VAT!**

The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new design uses two of these amplifier sections powered by separate power supplies fed from a common toroidal transformer. Input sensitivity is 775mV. Power output is 100 rms into 8 ohms from both channels simultaneously. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt!

POWERTRAN

**SYNTHESIZER KITS ON PAGE 8. MORE KITS AND ORDERING
INFORMATION ON INSIDE FRONT COVER.**



**DE LUXE EASY TO BUILD LINSLEY HOOD
75W STEREO AMPLIFIER £85.00 + VAT**

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!

All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.



T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for **£38.40 + VAT**.
MATCHING TUNERS — See our FREE CATALOGUE!

BLACK HOLE CHORALIZER

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls. LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 + VAT (single delay line system)

De Luxe version (dual delay line system) also available for **£59.80 + VAT**

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)



HIGH POWER MODULE KITS

125 WATT MODEL **£10.50** plus £1.15 p&p (Illustrated)

200 WATT MODEL **£14.95** plus £1.15 p&p


SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response measured at 100 watts 25Hz-20KHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1%
 Dimensions 205 x 90 and 190 x 36 mm
 The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components. result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the

aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions

ACCESSORIES

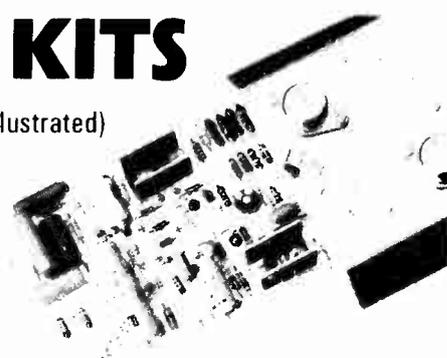Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p
 Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p
 Suitable Mains Power Supply Unit for 125W model **£7.50** plus £3 15 p&p
 Suitable Twin Transformer Power Supply for 200W model **£13.95** plus £4 00 p&p



MULLARD LP1183 STEREO PREAMP

FREE! Original listed price over £5 00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.

PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)



2 WAVE BAND MW LW
 * Easy to build * 5 push button tuning
 * Modern styling design * All new unused components
 * 6 watt output * Ready etched & punched P.C.B.
 * Incorporates suppression circuits * Now with tape input sock.

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale with matching rotary control knobs, one, combining on/off volume and tone control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

£10.50

Complete with instructions
CONSTRUCTORS PACK 7A plus £2 00 p&p
 Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete **£1.95** per pack, p&p £1 15




30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx

READY TO PLAY **£32.90** plus £3 80 p&p

HI FI STEREO AMPLIFIER MODULES

- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. £1.95 plus 70p p&p
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. £4.95 plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit. £3.95 plus £1 15 p&p
- Matching power supply kit with transformer. £3 00 plus £1 96 p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. £1 70 plus 80p p&p.
- Complete with application notes

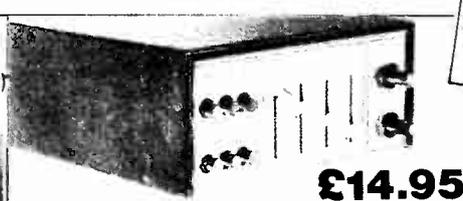

10+10 WATT STEREO AMPLIFIER KIT

£14.95 plus £2 90 p&p

- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier module
- Attractive black vinyl finish cabinet. Size 9" x 8 1/2" x 3 1/4" approx
- Converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit

SPECIFICATIONS

Suitable for 4 to 8 ohms speakers
 Frequency response 40Hz — 20KHz
 Input Sensitivity P.U. 150mV Aux. 200mV Mic. 1.5mV
 Tone controls Bass ± 12db @ 60Hz
 Treble ± 12db @ 10KHz
 Distortion -1% typically @ 4 watts
 Mains supply 220 250 volts 50Hz

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge **£8.50** plus £3 15 p&p when purchased with amplifier. Available separately **£10.50** plus £3 16 p&p

8" SPEAKER KIT 2 8" approx twin cone domestic use speakers. £4.75 per stereo pair plus £1 70 p&p when purchased with amplifier. Available separately **£6.75** plus £1 70 p&p

STEREO MAGNETIC PRE-AMP CONVERSION KIT

All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p



323 EDGWARE ROAD LONDON W2
 21E HIGH STREET, ACTON W3 6NG

ACTON. Mail Order only. No callers. ALL PRICES INCLUDE VAT AT 15%. All items subject to availability. Price correct at 5.2.81 and subject to change without notice. For further information send for instructions 20p plus stamped addressed envelope. NOTE: Goods despatched to mainland and N. Ireland only. Persons under 16 years not served without parent's authorisation. RTVC LTD. reserve the right to alter, update or improve their products without notice.



STEREO DISCO PREAMPLIFIER

matching above modules, suitable for twin deck mixing with P.F.L. output and Mic/Tape input. Ready built, ready to play with circuit diagram and application notes to suit our power module kits. **£21.95** plus £1 72 p&p

100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls. Size approx 14" x 4" x 10". Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **£76.00** plus £4 60 p&p

50 WATT MONO DISCO AMPLIFIER

Size approx 13 1/2" x 5 1/4" x 6 1/4". 50 watts rms 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches independent bass and treble controls and master volume.

£30.60 plus £3 68 p&p

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use.

£12.25 OUR PRICE plus £3 16 p&p. Size approx 13" x 11"

PHILIPS RECORD PLAYER DECK GC037

Hi-Fi record player deck 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge—LIMITED STOCK. UNBEATABLE OFFER AT **£27.50** complete plus £3 16 p&p

NEXT MONTH. NEXT MONTH. NEXT MONTH. NEXT MONTH. NEXT MONTH.

Hobby Electronics

Look for the April issue.
You can't afford to miss it!

Anatomy Of The Space-Shuttle

A special HE report on the forthcoming NASA Space-Shuttle launch. We investigate what the technical problems have been, why it's overdue, and give you a timetable running up to the launch and beyond

Tremolo

Just the effect you want for your guitar to complement the Fuzzbox in the March issue, although it will work with any electronic musical instrument. Simple-to-build, even simpler-to-use yet it won't burn a hole in your pocket

Russian Roulette

A novelty game designed to eliminate the players — without any mess whatsoever

----- STOP PRESS ----- STOP PRESS ----- STOP PRESS -----
- COMPETITION - STOP - NEXT MONTH'S ISSUE OF HOBBY ELECTRONICS
- STOP - PROMOTING THE UNITED NATION'S INTERNATIONAL YEAR OF
THE HANDICAPPED PERSON - STOP - QUERY - DO YOU THINK YOU CAN
DESIGN AN ELECTRONIC AID TO HELP A HANDICAPPED PERSON - STOP -
ANY ELECTRONIC AID - SOLID-STATE, COMPUTER PROGRAM, EVEN VALVE
- ANY ELECTRONIC AID - STOP - ANY HANDICAP - STOP - PRIZES TO
WIN - STOP
----- STOP PRESS ----- STOP PRESS ----- STOP PRESS -----

High Fidelity Comes To HE

Announcing a special audio project for HE: a hi-fi, high-power amplifier system which you can tailor according to your budget by making use of our special-offer kits. We start with the pre-amplifier in the April issue. This pre-amp requires *no wiring* except for the leads to the power supply! You can use it with your own amplifier too

Windscreen Washer Alarm

For the motorist who's fed up with cleaning his windscreen by hand because his washer bottle has run dry. As soon as the fluid drops below a predetermined level a 're-fill me' alarm is displayed

Plus:

News, views and info on CB, circuits, recent developments in electronics — everything for the electronics enthusiast and hobbyist — things you can't afford to miss. Get It!

Items mentioned here are those planned, but unforeseen circumstances may affect the actual contents.

PC WHOLESALE

1 THORNHILL, ROMSEY ROAD
WHITEPARISH, SALISBURY SP5 2SD

All good new full spec — prices are for minimum 100 any one type. Minimum Order £10 + 50p post. No VAT. SAE for full list.

AC130	.14	NC's	19482	.22
AC170	.14	40010	18	.22
AD101/2	.45	40110	.10	100
BC107	.37	40120F	.20	16493
BC108	.36	4017A	.35	140
BC109C	.36	4025A	.12	100
BC114	.35	4025A	.30	19480
BC147/A/1	.35	4040	.25	100
BC171/2	.35	4080	.30	100
BC177	.37	4080	.12	100
BC182D	.045	45110	.50	CAPACITORS
BC182L	.34	490140	.50	crapped lead
BC2120	.045	51140A	1.30	PCB mktg.
BC237/A/1	.36	2700 450m	2.80	0.47/50
BC300	.36	741	.12	1/20
BC320	.37	555	.17	2.2/20
BC327/0	.37			4.7/25
BC441	.18			47/10
BC481	.20	LEP's		10/10
BC567/A/1	.36	3000 red	.25	10/40
BC568	.36	yellow	.22/25	.225
BC569	.36	green	.22/25	.224
BC570	.36	grey	.22/25	.223
BC571	.36	5000 red	.200	47/40
BC572	.36	yellow	.200	100/10
BC573	.36	green	.200	100/25
BC574	.36	grey	.200	100/40
BC575/2	.13	Claps	.02	220/40
BC100	.36			1000/10
BC100	.36			2200/40
BC100	.36	Zeners. 400mW		.320
TP2300	.46	254 300 407 500 602		
TP2300	.45	600 700 802 901 110		
2N1132	.10	12V 14V 15V 24V. All m		
2N1711	.10	.33.		
2N2000	.12			
2N2040	.34			
2N2040M	.045			
2N2050	.15	800000		
2N2065	.30	104140	.02	
2N2700/A	.045	1k	.012	
2N2810	.14	10k	.000	
2N2841	.17	100k	.013	
40073	.45	100k	.000	


£1 BARGAIN PACKS

All packs £1 each; any 12 for £10. Post 25p. All top-grade new components — no rubbish.

PC1 12 BC107	PC9 10 TO3 sockets
PC2 14 BC108	PC10 15 0.1/35V tantal
PC3 12BBC109	PC11 14 3mm rad LEDs
PC4 3 2N3055	PC12 12 5mm rad LEDs
PC5 7 8F51	PC13 8 741
PC6 16 BC182	PC14 8 555
PC7 60 1N4148	PC15 15 12V zeners
PC8 25 1N4003	PC16 100 1k ¼W 5% Rs

Send S.A.E. for B-page list/enquiries. Mail only.
PC ELECTRONICS, 1 Thornhill, Romsey Road
Whiteparish, Salisbury, SP5 2SD

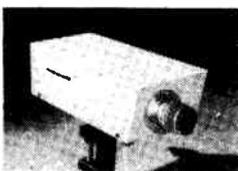AMAZING ELECTRONICS PLANS. Lasers; Super-powered cutting rifle, pistol, light show, ultra-sonic force fields, pocket defence weapon, giant tesla, satellite T.V. Pyrotechnics, 150 more projects. Catalogue 75p. From: Plancentre, St. John's Street, Bridgenorth, Shropshire.



CCTV CAMERA

£126.50 + P&P £3.45 (inc. VAT)
Total £129.95

BEST OFFER EVER
Camera Kit, Lens,
Vidicon & Modulator

CROFTON

Tel: 01-891 1923 For full details

SHARP miz-BOOK

and PC1211 Computers at
LOWEST PRICES!!
With lots of FREE PROGRAMS

KING PIN COMPUTERS
PO Box 40, Stovenage, Herts.
SGA ZNF

Tel. Stev. (0438) 59677, up to 9 p.m.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

BURGLAR ALARM EQUIPMENT. Wide selection at competitive prices. Sae for price list. A. Barton (ETI), 27 Gunville Road, Newport, I.O.W.

GOULD OS253 OSCILLOSCOPE. 18 months old £300. Phone Sheffield (0742) 339073 after 6.30 weekdays.

GOLD UNDER YOUR FEET? Special purchase C-Scope VLF/TR750 Metal Detectors. Normal price £84.90, 2 year guarantee. £59.90 including carriage. (0634) 250625.

AN UNBEATABLE KLIFCO OFFER. Quality Stereoamplifier chassis + Free Stereo Magnetic Pick-up. P.C.B. + Data £10.50. 60+60 watt (RMS) protected; 3Ω min 0.03% THD; 12-50V working, din sockets + controls; selector, V/C etc. Tested. 1 Regent Road, Ilkley LS29 9EA.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components
Full range of HE printed circuit boards normally ex-stock. same day despatch at competitive prices
P.C Boards to individual designs
Resist-coated epoxy glass laminate for the diy man with full processing instructions (no unusual chemicals required)

Alfac range of etch resist transfers and other drawing materials for p.c boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASON'S ROAD
STRATFORD-ON-AVON
WARWICKS, Tel. 4879

COLOUR MODULATOR

- RG B inputs, PAL/UFH output
- Unlimited colour combinations
- TTL etc interface details supplied
- 1000's already in use!

KIT: only £12 Built & Tested: only £18

— please add VAT at 15% to all prices
— Barclay/Access orders accepted by telephone

WILLIAM STUART SYSTEMS Ltd

Dower House, Billericay Road
Herongate, Brentwood,
Essex CM13 3SU.
Telephone: Brentwood (0277) 810244

C.B.S.

If you are in Business and considering an application of a Minicomputer or Microprocessor based System and are a little confused why not attend one of our courses.

- Microcomputer Application — BUSINESS
- Microcomputer Application — ENGINEERING AND CONTROL
- Programming in BASIC — INTRODUCTION
- Programming in BASIC — ADVANCED

We are an independent consultative organisation specialising in business and engineering application, prepared to recommend systems when required and provide full software and programming support.

Courses are available for individual or group instruction, and may be arranged to suit your specific applications.

For full details and dates available write or phone:

CLEVELAND BUSINESS SERVICES


Cleveland House
Routh, Near Beverley
North Humberstone HU17 9SR
Tel: Leven 0401-43139

SHARP POCKET COMPUTERS

PC 1211 Pocket Computer with CE121 Cassette Interface £105.95
Printer Cassette Interface CE122 £59.95
The CE122 combines the functions of printer and cassette interface.
PC 1211, complete with CE122 Printer/Cassette Interface £152.00
Free Papermate Pen with all orders. All prices include 15% VAT and U.K. delivery.
ELKAN ELECTRONICS, 28 Bury New Road
Prestwich, Manchester, M25 8LD

ZX80 'LIVE ACTION' SOFTWARE. Top quality games at unbeatable prices: BREAKOUT (1K) £4; SPACE INTRUDERS (2K) £4. Also MOVIES (2K plus), 7x8 character pictures displayed in rapid rotation giving animation effect £3 — No hardware modification whatsoever. Written in machine code without loss of T.V. synchronisation. SOUNDS INCREDIBLE? — YES, but it's true. Reviews say the ZX80 can't be used for continuous live action ARCADE type games — WELL IT CAN — WE'VE DONE IT — SEEING IS BELIEVING — Send cheques or P.O.'s for program listing (or S.A.E. for list of all software) to: MACRONICS (K. Macdonald), 26 Spiers Close, Knowle, Solihull, B93 9ES.

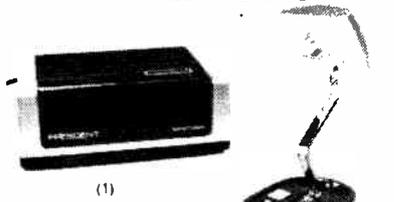BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period (2)
1. With alarm repeat. S.R.S.P. of £17.00. Offered at £3.95, inc. VAT or 3 for £9.95, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00 Offered at £7.95 inc. VAT each, or 3 for £19.95 inc. VAT
These will be sold as received from our customers with the existing fault(s) and without guarantee U.K. only
Discounts available on large bulk purchase
PRESCOTT CLOCK & WATCH CO. LTD.
PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

SPEED — VERSATILITY — ECONOMY



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers, to carry out work on—

• P.C.B. REPAIRS • ANALOGUE BREADBOARDING • SIMPLE LOGIC WIRING • COMPLEX INTERCONNECTING OF MICROS AND MEMORIES.

EURO INTROKIT £16.70. PROJECT KIT £8.18.
MINIKIT (A) £7. PENCIL WITH LOADED QSE BOBBIN £2.81 WITH T.C.W. BOBBIN £2.76. STRIPS: GLUE FIX 20/PKT 6" LONG £3.20. HIGH DENSITY GLUEFIX 20/PKT 6" LONG £3.20. PRESS FIX 20/PKT £3.20. SINGLE HIGH DENSITY D-SIDED EUROCARD £5.18. SINGLE SIDED £3.80. DOUBLE HIGH DENSITY D-SIDED EUROCARD £8.60. PROJECT CARD £2.50. BOBBINS: BLUE 4/PKT. £2.12. GREEN 4/PKT. £2.12. GOLD 4/PKT. £2.12. PINK 4/PKT. £2.12. 1 OF EACH COLOUR £2.20. TINNED COPPER 2/PKT. £0.96. ADHESIVE £0.41. SOLDERING IRON 420 C £5.52. REPLACEMENT WELDER TIPS — PTAAB 430 C £1.40. PTAAB 480 C £1.40.

Please add 40p for P&P + VAT to all orders
FOR FURTHER INFORMATION ON
ROADRUNNER PRODUCTS SEND
LARGE S.A.E. TO:

T. J. BRINE ASSOCIATES
FREEPOST, Haslemere, Surrey GU27 3BL

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (ET23)
11 Percy Avenue, Ashford, Middx. TW15 2PB

PRE-WAR ONWARD VALVES, wireless (S.W.s included). S.A.E. 100 transistors £5. Bargains list 15p. — Sole Electronics, ET1, 37 Stanley Street, Ormskirk, Lancs.

FM MINI TRANSMITTERS 88-108 MHz, 150 yard range. Money back (before/after assembly). Guaranteed. Kit £2.65 + 25p P&P. P. Faherty, 37 College Drive, Ruislip, Middx.

SN76477 sound generator plus data	160p
XR2206 tone decoder plus data	270p
MM57160 STAC timer	500p
ZN425E D to A converter	380p
NE555 timer	15p
2708 450nS EPROM	300p
TBA800 5W audio amplifier	70p
NE567 tone decoder	100p
LM13600 dual transconductance amp.	120p
LM387 low noise preamp plus data	130p
LM386 power amplifier	80p
LM377 dual 2w. amplifier	150p
LF351 operational amplifier	40p
LF353 dual LF351	80p
TDA1022 delay line	500p
7805 or 7812 TO220 regulator	50p
7905 or 7912 TO220 regulator	60p
Metal film 1/4w. 1% resistors 51Q to 300K. E24 series	4p
Siemens polyester capacitors 0.01, 0.022, 0.047, 0.1	9p
Pack 50 each 6BA nuts, washers, 1/2" screws	50p
Pack 50 each 4BA nuts, washers, 1/2" screws	70p
Connecting cable single strand, 1 metre of eight different colours, total 8 metres	30p
As above but 5 metres each colour, total 40m.	140p
Light duty stranded 10/0 1mm, 8 colours	4p metre
Extra flex. 55/0.1, red or black	12p metre
Twin cable, speaker type	10p metre
Single screened cable	15p metre
Twin individually screened	20p metre
Min. 3-core mains cable, 2.5A	22p metre

All prices exclude V.A.T. Please add 40p carriage. All brand new components.

J. NELSON 203 HIGH STREET
LONDON, S.E.13

MICROTYPE

READY CUT CASE FOR SUPERBOARD, UK101, NASCOM 2, (ALSO AVAILABLE WITH BLANK KEYBOARD FOR HOMEBREW, NASCOM 1, ETC.)

PRODUCED IN BLACK ABS PLASTIC, COMPLETE WITH SCREWS AND INSTRUCTIONS SPACE FOR EXPANSION, FORCE FEED FAN, NUMERIC PAD AND ADDITIONAL KEYS ONLY £24.50 + £1.50 P&P + VAT.
SEND CHEQUES OR P.O.'S FOR £29.90 TO:
MICROTYPE, P.O. BOX 104, HEML, HEMPSTEAD, HERTS, HP2 7QZ
SAE FOR DETAILS DEALER & OEM ENQUIRIES WELCOME

B.U.F.O.R.I.N. BUFORIN UFO Research Network urgently need investigators in all parts of Britain. For more details, send 10p and s.a.e. to — The BUFORIN, Upper Grange Farm, Old Dalby, Melfon Mowbray, Leicestershire.

SYNTHESISER 4600 for sale. Full constructional data, professionally built. Calibrated, tuned and tested. Excellent finish, beautiful condition, £750 ono. Tel: Letchworth 04626 76951 after 6pm.

POWER SUPPLIES, new, guaranteed. Many types cased and uncased. Write Petron Electronics, 1 Courtlands Road, Newton Abbot, Devon.

BUILD A 12 into 2 mixer for £100. Details £3.50. P.O. to Mr J. A. Lovatt, Flat 5, 36 William Ave., Margate, Kent.

POWERTRAN D.P.X. Polyphonic Synthesiser fully built and tested, perfect working order, £350 ono. Phone Leeds 450586/8. Ext. 38. (Flat F3).

CB SPARES

Japanese original transistors and integrated circuits.

Largest selection in Britain at very low prices.

Write or phone for free list.

McLaughlin Electronics
44 Carlisle Road
Londonderry
N. Ireland BT48 6JW

Tel: (0504) 65002

Mail Order Protection Scheme

If you order goods from mail order advertisers in this magazine and pay by post in advance of delivery, this publication *Electronics Today International* will consider you for compensation if the advertiser should become insolvent or bankrupt, provided

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication *Electronics Today International* explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1800 per annum for any one advertiser so affected and up to £5400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures has not been complied with, at the discretion of this publication *Electronics Today International*; but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc., received as a result of answering such advertisements). Classified advertisements are excluded.

ADAM HALL

Cabinet & Flightcase Fittings, Trasluths coverings, handles, castors etc. Jacks & sockets. Cannons, Bulgins, reverb trays, Emilar compression drivers, AKG mics, Celestion speakers, ASS glassfibre horns

Send 30p postal order for illustrated catalogues to
ADAM HALL (E T SUPPLIES)
Unit B, Charlton Court
Grainger Road, Southend-on-Sea
Essex SS2 5BZ

EXACT TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60kHz atomic time signals, built-in antenna, 1000Km range, ABSOLUTE TIME, £54.80.
V.L.F.7 EXPLORE 10-150KHz, Receiver £13.70.
60KHz RUGBY RECEIVER, as in MSF Clock, serial data output, built-in antenna, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc. money back assurance so GET your NOW.

CAMBRIDGE KITS
45 (TR) Old School Lane, Milton, Cambridge

MK 14 KITS. Keyboard £12.80. 1/2" display £12.80. 4K memory board, fitted 1K £20.82. Ditto fitted 4K £43.47. 16 bit LED board £11.41. Mother board £9.34. Cassette interface £8.21. 5v, 1.5A power supply, less transformer £7.55. Super VDU interface £39. New monitor £14.95. VDU monitor PROM (5v) £14.95. Pico-2 basic PROM (5v) £14.95. Mk 14 book £5.95. Secondhand Mk 14 £37. Catalogue 80p. Full price list — send SAE. Post 80p. Redditch Electronics, 21 Ferney Hill Ave., Redditch, Worcs. B97 4RU. Tel: (0527) 61240 evenings.

TELEPHONE ANSWERING MACHINE. Build your own for under £10 plus any cassette recorder. Send £3 for circuit and plans. S. D. Cross, 24 Thorney Road, Streetly, Sutton Coldfield, West Midlands.

DOUBLE SIDED COPPER CLAD Fibreglass Board. 1/2p/sq. inch. Please state size. Maximum size 12" x 12". Minimum order £1. P&P 60p. Also complete P.C.B. service. H.C.R. (Chelmsford), 1 Bankside, off New Street, Chelmsford.

FORMANT SYNTH, integral case, reverb, phaser, etc. Less one VCO, all working. £450. Tel: (0670) 513567.

100 IN4148 £1, 150 Resistors £1, 100 Capacitors £1. P&P 25p. S.A.E. lists. Dept. T. D.B. Products, P.O. Box 8, York YO1 1FT.

BUDGET MICRO BITS:

- 1K Extra Memory Kit for Mk. 14's..... £8.54
- Decoding logic kit for Mk. 14 address to full 16 lines..... £2.81
- 4k Static Memory block kit..... £30.95
- Address and Data buffers with memory control logic kit..... £18.70

TREMORRAN DATA SYSTEMS
Tors Park, Infracombe, N. Devon

WANTED. Electronic components and test equipment. Good prices given. Q Services, 29 Lawford Crescent, Yatley (0252) 871048, Camberley, Surrey.

VIDEO MUSIC



The amazing Videograph, as featured recently in Electronics Today International, links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically-minded, a square-wave signal generator is built-in, permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

DIY KIT ONLY £33.95

Case & Controls £15.95
or READY BUILT £69.95

All prices include VAT and postage

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD
Telephone: Brentwood (0277) 810244

DIGITAL VOLTMETER MODULE



Fully built and tested, ONLY **£11.95+VAT**

- ★ Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- ★ Requires only single supply between 7 & 12 volts (220mA)
- ★ High accuracy +0.1% + 1 digit
- ★ Large bright 0.43" high efficiency displays
- ★ 4 readings per second sampling rate
- ★ Size only 41 x 95 x 10mm.
- ★ Supplied with full data & applications information

This quality module manufactured by Autona Limited (one of the U.K.'s largest module manufacturers) means you can build accurate test equipment, multi-meters, thermometers, etc., easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.


Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50p p. & p. = £14.24) now to:

Dept. ET14, RISCOMP LIMITED
21 Duke Street, Princes Risborough
Bucks. HP17 0AT
Telephone (084-44) 6326

Retail shop callers welcome



EX-STOCK DELIVERY

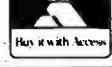

ADVERT INDEX

Acorn Computers.....	53	Langstone Electronics.....	34
Altek Instruments.....	74	LB Electronics.....	86
Ambit International.....	43	L & B Electronics.....	70
Audio Electronics.....	14 & 90	LEM Services.....	74
Bi-Pak Semiconductors.....	54	Linsac.....	93
BK Electronics.....	16 & 94	Manor Supplies.....	86
BNRS.....	18	Maplin.....	116
Butterworths.....	101	Marshall's.....	90
Calculator Sales & Service.....	94	Micro Circuits.....	87
Cambridge Learning.....	57	Microdigital.....	80
Campbell Clark Cabinets.....	86	Midwich Computers.....	103
Castle Electronics.....	98	Mitrad.....	73
Chiltmead.....	81	NIC Models.....	70
Chordgate Ltd.....	63	Parndon Electronics.....	52
Chromasonics.....	48 & 49	T. Powell.....	52
Clef Products.....	85	Powertran.....	2, 8 & 107
Comp Comp Comp.....	114 & 115	Rapid Electronics.....	34
Crimson Elektrik.....	97	J. W. Rimmer.....	52
Crofton Electronics.....	103	R.T.V.C.....	108
Delta Tech & Co.....	93	Safgan Electronics.....	80
Display Electronics.....	65 & 80	Saxon Entertainments.....	98
Doram Electronics.....	69	Science of Cambridge.....	4 & 5
Drallim Davis Electronics.....	42	Silica Shop.....	42
Electronize Design.....	85	Swanley Electronics.....	106
Electro Supplies.....	42	Tangerine.....	38 & 39
Electrovalue.....	103	Technomatic.....	12
GMT Electronics.....	74	Teleradio.....	52
Greenbank.....	99	Tempus.....	20
Greenweld.....	94	Timedata.....	64
G.S.C.....	19 & 62	TK Electronics.....	58
Hameg Ltd.....	106	Transam Components.....	26
Happy Memories.....	106	Vero Electronics.....	34
Henry's Radio.....	64, 86 & 93	Videotone Ltd.....	89
I.C.S.....	7	Watford Electronics.....	6 & 7
I.L.P.....	32, 33 & 64	Wilmslow Audio.....	64
Keelmore.....	49	Yale Security.....	98
Kode Services.....	70		

PROGRAMMING, UV. Eproms, most types, 1 & 3 rail. £3/1K. Dept. E, Petron Electronics, 1 Courtlands Road, Newton Abbot, Devon.

WANTED

Test equipment, valves, tubes and scrap electronics.

Reasonable prices paid. Distance no object (UK mainland only).

FRG General Supplies
Unit 3, Longhill Industrial Estate
March, Cambridgeshire
PT15 8NQ

Tel: March (03542) 58614
or 01-404 5011
Telex: 24224 Quote Ref. 3165

ELECTRIFY YOUR SALES! • CLASSIFIED ADVERTISEMENT

1	2	3
4	5	6
7	8	9
10	11	12
13	14	15

Please place my advert in: **Electronics Today International**
(Delete as applicable) **Hobby Electronics**

Advertise nationally in Electronics Today International/Hobby Electronics. Simply print your advertisement in the coupon here (left), indicating which magazine you require. Or telephone for more information.

Name

Address

Tel. No. (Day)

Send, together with your cheque to:
Jenny Naraine, ETI/HE,
145 Charing Cross Rd., London WC2H 0EE.
Tel: 01-437 1002 Ext. 50.

Learn more about our products - Send £1 & S.A.E. for 1981 Spring Catalogue

NEW REDUCED PRICES

8K **£399**
 16K **£449** + VAT
 32K **£499**
 RRP £795 for 32K



The PEDIGREE PETS Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen.

Cassette Deck **£55** extra. Full range of software available.

Interface PET IEEE - Centronics Parallel
 Decoded **£77.00** + VAT

EXTENDED WARRANTY BY COMPUKARE

We give a full one year's warranty on all our products.

SPECIAL SCOOP GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only **£299** + VAT



Interface Cards for Apple, Pet, TRS80, Nascom and CompuKit - **£49** + VAT

Full Pet Graphics including cables. Ready to go. **EX-STOCK.**

EXTENDED WARRANTY BY COMPUKARE

NASCOM 2 DISC DRIVES

Add a powerful, double density, mini floppy disc to your Nascom system.

- Disc Controller Card (includes Nasbus 6 S100 interface)
- Will control 4 Drives.
- CPM operating system.
- Extended Disc Basic Compiler.
- Power supply included



One Disc System - **£499** + VAT
 Additional Disc Unit - **£299** + VAT

EXTENDED WARRANTY BY COMPUKARE

NASCOM 2 GAMES TAPE

featuring Space Invaders and Android Nim, Re-numbering program and other goodies!

£7.50 + VAT

EXTENDED WARRANTY BY COMPUKARE

NEC SPINWRITER

only **£1350** + VAT



NEC's high quality printer uses a print "thimble" that has less diameter and inertia than a daisy wheel, giving a quieter, faster, more reliable printer that can cope with plotting and printing (128 ASCII characters) with up to five copies, friction or tractor fed. The ribbon and thimble can be changed in seconds. 55 characters per second bidirectional printing - with red/black, bold, subscript, superscript, proportional spacing, tabbing, and much, much more.

EXTENDED WARRANTY BY COMPUKARE

TEAC DISK DRIVES



- TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.
- The FD-50A can be used in double density recording mode.
- The FD-50A is Shugart SA400 interface compatible.
- Directly compatible with Tandy TRS80 expansion interface.
- Also interfaces with Video Genie, SWTP, Heathkit, North Star Horizon, Superbrain, Nascom, etc., etc.
- Address selection for Daisy chaining up to 4 Disks.
- Disks plus power supply housed in an attractive grey case.

Single Disk Drive **£225** + VAT Double Disk Drive **£389** + VAT

EXTENDED WARRANTY BY COMPUKARE

COMP POCKET COMPUTER GREATEST BREAKTHROUGH YET

£99.90 + VAT



COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

- Programs in BASIC • "QWERTY" Alphabetic Keyboard • 1.9K Random Access Memory
- Long Battery Life.

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24-character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

EXTENDED WARRANTY BY COMPUKARE

FANTASTIC FOR FILE HANDLING ACULAB FLOPPY TAPE

The tape that behaves like a disc, for TRS-80 LEVEL 2.

only **£169** + VAT



The Aculab Floppy Tape for the TRS-80 and Video Genie is a highly reliable digital storage system that provides many of the advantages of floppy disks at less cost. Automatic debounce routine for the Level 2 keyboard. Connects directly to TRS-80 Level 2 Keyboard. Operating and file handling software in ROM. 8 commands add 12 powerful functions to Level 2 BASIC.

EXTENDED WARRANTY BY COMPUKARE

THE VIDEO GENIE SYSTEM

Ideal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.

EG3000 Series

WITH NEW EXTRA KEYS!

16K £289 + VAT

- 16K user RAM
- plus extended 12K Microsoft BASIC in ROM
- Fully TRS-80 Level II software compatible
- Huge range of software already available
- Self contained, PSU, UHF modulator, and cassette
- Simply plugs into video monitor or UHF TV
- Full expansion to disks and printer
- Absolutely complete - just fit into mains plug.

The Video Genie is a complete computer system, requiring only connection to a domestic 625 line TV set to be fully operational; or if required a video monitor can be connected to provide the best quality display. 51 key typewriter style keyboard, which features a 10 key rollover. Supplied with the following accessories: • BASIC demonstration tape; • Video lead; • Second cassette lead; • Users manual; • BASIC manual; • Beginners programming manual. Write-useful programs in the BASIC computer language yourself.

VIDEO GENIE EXPANSION BOX NOW IN SHOP

EXTENDED WARRANTY BY COMPUKARE

only **£325** + VAT



TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals, UK Power Supply, Cassette Leads, Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go. Full Range of Software Available

Interface to Centronics Parallel for TRS80 **£75.00** + VAT

only **£295** + VAT

Expand your TRS80 by 32K

32K TRS80 EXPANSION INTERFACE

32K Memory on board
 Centronics parallel port
 Disk controller card
 Real time clock. Requires Level II Basic. Interface for 2 cassette decks, complete with power supply.

EXTENDED WARRANTY BY COMPUKARE

YOU NEED NEVER MISS AN IMPORTANT CALL AGAIN TWO CORDLESS TELEPHONE SYSTEMS - DIRECT FROM USA



THE ALCOM only **£147** + VAT

Base station connects to your telephone line. Remote handset clips to your belt and gives you push-button dialling - Bleeps when call arriving - Nicad rechargeable batteries. Charger in base unit.



LOW COST TELEPHONE ANSWERING MACHINE only **£99.95** + VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

EXTENDED WARRANTY BY COMPUKARE

COMMERCIAL EXPANDABLE • COMPLETE TRS 80 • MODEL II

64K 1-Disk Model II

£1995.00 + VAT

RRP £2250.00



The Model III is now in our showroom

This new unit from the world's most successful micro company is now available immediately with software. The basic unit comes complete with 64 thousand characters (bytes) of Memory. The built in 8" Floppy disc adds another 1/2 million extra characters including the disc operating system. More disc expansion is now available.

The Model II is a complete unit with a full keyboard including a numeric pad and 12" screen which gives 24 lines of 80 characters. The computer is supplied with both the disc operating system and the Level III Basic.

A full self test routine is written into the power up procedure to eliminate incorrect operation. Both serial and parallel expansion sockets are standard. A printer is a plug-in operation.

Both hardware and software necessary to talk to a mainframe are included. Terminal usage is very possible. With the addition of CPM2 you can operate with COBOL, FORTRAN, MBASIC, CBASIC in which languages are many other applications packages i.e. accounting, payroll stock etc.

CP/M2	£95.00	M BASIC	£155.00
CIS COBOL	£400.00	FORTRAN	£220.00
C BASIC	£75.00	WORDSTAR	£255.00

EXTENDED WARRANTY BY COMPUKARE

COMP PRO MIXER

Professional audio mixer that you can build yourself and save over £100.

Only **£99.90** plus VAT for complete kit. Plus FREE power supply valued at **£25.00**



FULL RANGE OF ACCESSIT AUDIO ADD-ONS

EXTENDED WARRANTY BY COMPUKARE

NOBODY CAN GET NEAR OUR PRICES EXCEPT OUR CUSTOMERS

RRP £540 only **£399** - VAT
ANADEX DP8000
 Super Quality — Low cost printer Tractor Feed with full 96 ASCII character set — Accepts RS232C at baud rates between 100 and 9600 and Parallel Bit data
 Attaches either directly or through interfaces to Pet, Apple, TRS80, Sorcerer, Nascom, Compukit etc.

THE NEW ANADEX DP9500 and DP9501 A PROFESSIONAL PRINTER

- Bi-directional printing
- Up to 220 chars/line with 4 print densities
- 500 char buffer
- RS232C and Centronics Parallel interface built in
- Full software control of matrix needles allowing graphics capability
- 200 chars/sec
- Adjustable width tractor feed.

DP9500 — ONLY **£795** + VAT
 DP9501 — ONLY **£845** + VAT

THE ATARI VIDEO COMPUTER GAMES SYSTEM **£83.00** + VAT

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!

Most Cartridges only **£13.90** + VAT
 Prices may vary with special editions Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle, Codebreaker*, Miniature Golf.

Extra Paddle Controllers — **£14.90** + VAT
 Keyboard Controllers — **£16.90** + VAT
SPACE INVADERS NOW IN STOCK £25

NEW TV GAME BREAK OUT

Has got to be one of the world's greatest TV games. You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for upgrading old amusement games

MINI KIT — PCB, sound & vision modulator, memory chip and de code chip. Very simple to construct **£14.90** + VAT
OR PCB **£2.90** MAIN LSI **£8.50** Both plus VAT

WE ARE NOW STOCKING THE APPLE II AT REDUCED PRICES

16K **£599**
 32K **£649**
 48K **£659** + VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:

- BASIC — The Language that Makes Programming Fun.
- High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays.
- Sound Capability that Brings Programs to Life.
- Hand Controls for Games and Other Human-Input Applications.
- Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package.
- Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER
COMPUKIT UK101

- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape Interface on board.
- ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for Compukit expansion **£8.50** + VAT

Build, Understand and Program your own Computer for only a small outlay **KIT ONLY £179** - VAT **NO EXTRAS NEEDED**

Available ready assembled, tested & ready to go **£229** + VAT

NEW MONITOR FOR COMPUKIT UK101

- In 2K Eprom 2716
- Allows screen editing
- Saves data on tape
- Flashing cursor
- Text scrolls down

£22.00 + VAT
Special Bonus SAVE £22. New Super Monitor inc. in each kit or sold separately for **£22** + VAT.

FOR THE COMPUKIT	Game Packs	Super Space Invaders (8K)	£8.50
Assembler/Editor £14.90	1. Four Games £5.00	Space Invaders	£5.00
Screen Editor Tape £5.90	2. Four Games £5.00	Chequers	£3.00
All Prices exclusive VAT	3. Three Games 8K only £5.00	Real Time Clock	£3.00
		Case for Compukit	£29.50

HITACHI PROFESSIONAL MONITORS

9" — ~~£129~~ **£99.95**
 12" — ~~£199~~ **£149**

- Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability.
- 500 lines horizontal resolution Horizontal resolution in excess of 500 lines is achieved in picture center.
- Stable picture Even played back pictures of VTR can be displayed without jittering.
- Looping video input Video input can be looped through with built-in termination switch.
- External sync operation (available as option for U and C types)
- Compact construction Two monitors are mountable side by side in a standard 19-inch rack.

ENGLISH COLOUR TV/ AMERICAN NTSC COLOUR MONITOR

Suitable for Apple, Atari and Texas 99/4 **£295** + VAT

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes	10 for £4.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Discs 5 1/4" Hard and Soft Sector	£3.50
Floppy Disc Library Case 5 1/4"	£3.50
Verocases for Nascom 1 & 2 etc.	£24.90
Keyboard Cases	£9.90

MEMORY UPGRADES

16K (8 x 4116) **£29.90** + VAT
 4K Compukit (8 x 2114) **£29.90** + VAT

SPECIAL OFFER

We will part exchange your Sinclair ZX80 for any of our products.

Refurbished ZX80's — fully guaranteed + VAT
 Refurbished MicroAces — **£69.90** + VAT
 (Supply dependant upon stocks).



We have one of the largest collections of Computer Books under one roof, along with racks of software for the PET and TRS80. **Come and see for yourself.**

NOW OPEN

OUR NEW SHOWROOM & SALES CENTRE AT
 311 Edgware Road,
 London W2.
 Telephone: 01-262 0387

APPLE DISC II

Disc with Controller **£349** + VAT
 Additional Drives **£299** + VAT

- Powerful Disk Operating Software Supports up to 6 drives
- Name Access to Files for Ease of Use
- BASIC Program Chaining to Link Software Together
- Random or Sequential File Access to Simplify Programming
- Dynamic Disk Spare Allocation for Efficient Storage
- Individual File Write-Protection Eliminates Accidental File Alterations
- Loads an 8K Byte Binary Image in 6.5 sec. (1.2 sec. in Pascal)
- Storage Capacity of 116 Kilobytes (143K Bytes with Pascal) on Standard 5 1/4" Diskettes
- Powered Directly From the APPLE (Up to 6 Drives) for Convenience and High Reliability
- Packaged in Heavy-Duty, Colour-Coordinated Steel Cabinet

A SELECTION OF APPLE INTERFACES ARE NOW AVAILABLE AT OUR NEW SHOWROOM.

Delivery is added at cost. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number. **CREDIT FACILITIES ARRANGED** — send S.A.E. for application form.

MAIL ORDER AND SHOP
 14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station — Moorgate Line).
 Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G
OPEN (BARNET) — 10am - 7pm — Monday to Saturday
NEW WEST END SHOWROOM.
 311 Edgware Road London W2 Telephone: 01-262 0387
OPEN (LONDON) — 10am 6pm — Monday to Saturday

- ★ IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933
- ★ **COMP SHOP USA**, 1348 East Edinger, Santa Ana, California, Zip Code 92705. Telephone: 0101 714 5472526

COMP SHOP "Europe's Largest Discount Personal Computer Stores"

COMP COMPUTER COMPONENTS (Part of the Compshop Ltd. Group)

Logos: BARCLAYCARD, VISA, AMERICAN EXPRESS, DINERS CLUB INTERNATIONAL, COMP SHOP INTERNATIONAL, WOODGATE ACCESS.

Make it for a Song!



The New **Maplin in Matinée**

Amazing Value For Only £299.95 + £99.50 for cabinet if required.

Easy to build. Latest technology — means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain. Sustain on both manuals, and pedalboard. Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money. Full construction details in *Electronics & Music Maker* magazine.



The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't afford to be without.



Post this coupon now for your copy of our 1981 catalogue price £1. Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons. I enclose £1.25.

Name _____

Address _____

ET1481

MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554 155. Sales (0702) 552911.

Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
Both shops closed Mondays.

Catalogue now on sale in all branches of WHSMITH  Price £1.00

