

electronics today

ISSN. 0142-7229

INTERNATIONAL

OCTOBER 1981 65p

HIGH QUALITY, LOW COST, DIY SPEAKER

Build your own
domestic monitor
for a fraction of
the price!

PLUS

- ★ Engineer's Guide to BASIC
- ★ Laser Testing For Hi-Fi
- ★ Ring Modulator For Voice Effects




NEW
SERIES INSIDE!

Choosing and using
robots in Britain




FM-MAINS
REMOTE CONTROL
SYSTEM!

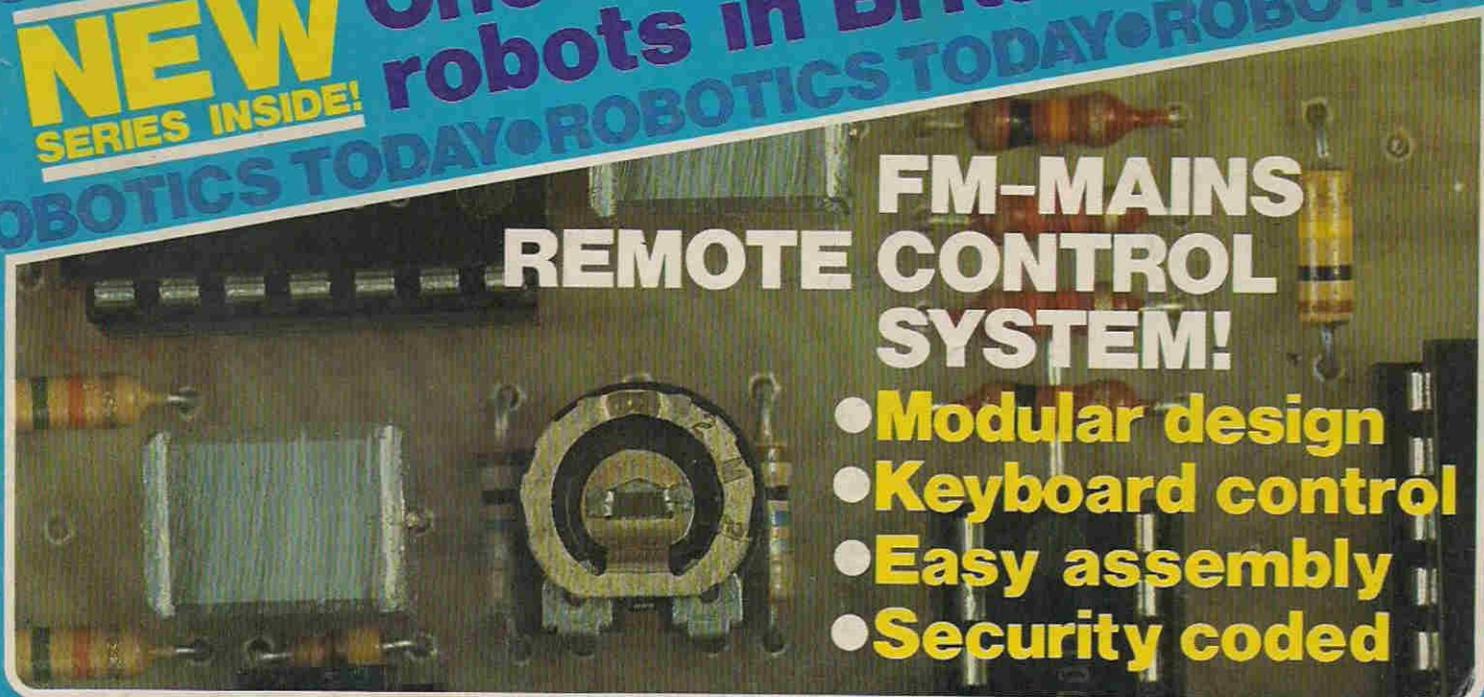- Modular design
- Keyboard control
- Easy assembly
- Security coded



...NEWS... PROJECTS... MICROPROCESSORS... AUDIO...

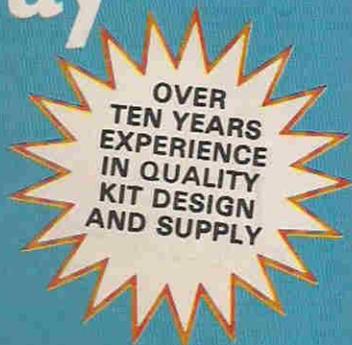Much more than just kits quite simply the best way to make music ...



Powertran have been designing and manufacturing high-quality electronic kits for more than a decade. Thousands have been purchased and assembled by constructors throughout the UK and world-wide. Many of our regular clients have built the entire range — several times! A Powertran kit makes an excellent gift for the electronics enthusiast; and is a gift that, when constructed, may be given again.

Our reputation rests on these unshakeable foundations — we use the most imaginative and ingenious designers; we use high grade components subjected to rigid quality control; our kits are complete, even screws and wire are included; we take care with packing and despatch; our instructions are clear and always fully comprehensive ... and if that weren't enough we back it up with our money-back guarantee. Powertran care and your skill gives you that something special.

Among the most popular of our kits are the fabulous 'Transcendent' range of synthesisers. Designed by the expert in the field, Tim Orr, and featured in Electronics Today International — those kits represent the zenith in both constructional ingenuity and musical performance. Thanks to our fully illustrated, carefully diagrammed 30 pages plus of constructional notes the 'Transcendent' range is comfortably within the capability of most enthusiasts. A great many 'first time builders' have completed them without difficulty and are justifiably pleased with the results.



TRANSCENDENT POLYSYNTH — brilliant design work and high technology components give the home constructor a machine of such versatility and range, equalled only by factory-made units costing thousands of pounds. Despite the advanced electronics the kit is mechanically simple with minimal wiring and ribbon cable connectors. Solid teak cabinet, fully finished metalwork — a 100% complete kit to give totally professional result.
COMPLETE KIT £320 (+ VAT)
Team the Polysynth with the new matching 4 voice expander
COMPLETE KIT £295 (+ VAT)

TRANSCENDENT DPX — a versatile 5 octave keyboard. The two audio outputs can be used simultaneously to give harpsichord and piano/honky-tonk or reed and strings/brass both fully polyphonic. To add more excitement there is a chorus/ensemble unit with strong or mild effect switching. The DPX is an advanced design — yet care, and our superb construction manual, make it a kit for every enthusiast.
COMPLETE KIT £299 (+ VAT)

TRANSCENDENT 2000 — a 3 octave keyboard yet with all the design ingenuity and thorough engineering that makes a superb and versatile machine. Quality teak cabinet and quality components throughout — complete down to the 13 amp plug. Buy it — build it — then plug-in and play it! A truly professional sound.
COMPLETE KIT £168 (+ VAT)

1024 COMPOSER — one of our latest designs. The Composer controls the synth, with a sequence of up to 1024 notes or equal selection of shorter sequences. Mains powered and with trickle-charged battery to preserve programme after switch-off.
COMPLETE KIT £89.50 (+ VAT)

... write or phone for NEW 40 page '81/82 catalogue — FREE!




PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until Nov 30th, 1981, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.
SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m.-12 noon, 1-4.30p.m. Monday-Thursday.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

MORE SUPERB KITS INSIDE
THE BACK COVER OF
THIS ISSUE

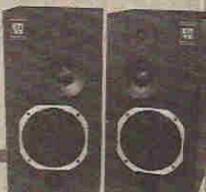INTERNATIONAL
HIGH QUALITY,
LOW COST, DIY
SPEAKER




PLUS




Home-built hi-fi p.22



Commands by cable p.56

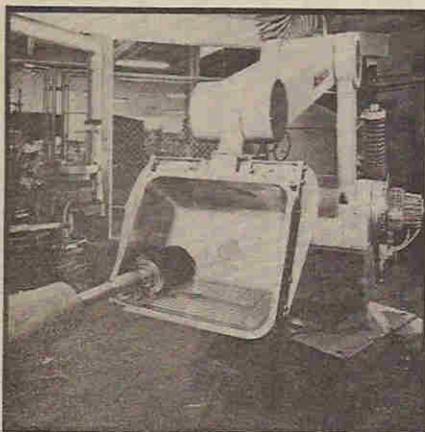

The new workers p.72

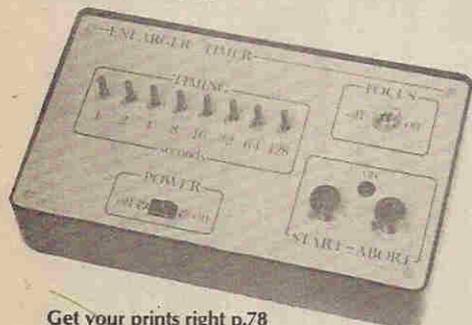

Get your prints right p.78

OCTOBER 1981 VOL 10 NO 10

INTERNATIONAL

FEATURES

- | | | |
|---------------------------|----|----------------------------------|
| DIGEST | 8 | News from both sides of de fence |
| LASERS IN HI-FI | 17 | Loudspeakers and light-sabres? |
| DESIGNER'S NOTEBOOK | 31 | Makes batteries last longer |
| dbx NOISE REDUCTION | 40 | Something for music lovers |
| TECH TIPS | 50 | All your own work |
| SPOT DESIGNS | 52 | Tried and tested circuits |
| ENGINEER'S GUIDE TO BASIC | 63 | Learn to speak the language |
| ROBOTICS TODAY | 72 | New technology = new series |
| CASIO FX-602P | 83 | A miniature mathematical marvel |

PROJECTS

- | | | |
|--------------------------|----|--|
| V3 LOUDSPEAKER | 22 | Build a pair and your ears will love you |
| MICROPOWER PENDULUM | 37 | Treat your clock to a cheap tick-tock |
| ROBOT ARM | 43 | The Armdroid assembled |
| FM MAINS REMOTE CONTROL | 56 | Make your wiring work for you |
| MICROPOWER THERMAL ALARM | 68 | Tiny temperature tester |
| ENLARGER TIMER | 78 | How fast is your enlarger? |
| SOUND BENDER | 88 | Wonderfully warped waveforms |
| FOIL PATTERNS | 94 | A copper communion |

INFORMATION

- | | | |
|------------------|----|---------------------------------|
| BREADBOARD '81 | 10 | We're a lot of exhibitionists |
| NEXT MONTH'S ETI | 15 | Forthcoming attractions |
| BOOKS | 29 | Our technical library |
| ETI PCB SERVICE | 54 | Build better with bought boards |
| BINDERS | 97 | Help stamp out naked ETIs |

Due to lack of space, Audiophile has been held over until next month.

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.
Telex 8811896.

Ron Harris B.Sc.
Paul Wilson-Patterson
T.J. Connell

Editor
Group Art Editor
Managing Director

Peter Green
Tina Boylan
Judith Jacobs

Assistant Editor
Editorial Assistants

Alison Lilly
Paul Edwards
Ray Marston

Assistant Art Editor
Drawing Office Manager
Project Editor

OVERSEAS
EDITIONS
and their
EDITORS

AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsman



Member of the
Audit Bureau
of Circulation

PUBLISHED BY Modmags Ltd., 145 Charing Cross Road, London WC2H 0EE
DISTRIBUTED BY Argus Press Sales & Distribution Ltd.
12-18 Paul Street, London EC2A 4JS (British Isles)
PRINTED BY QB Limited, Colchester
COVERS PRINTED BY Alabaster Passmore



Electronics Today is normally published on the first Friday in the month preceding cover date. © MODMAGS LTD 1981. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. Subscription Rates: UK £11.25 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR46AR.



THE AX-210 IS OUT OF THIS WORLD

THE WORLDS MOST VERSATILE WATCH

CASIO AX-210

Multiple Display LCD Analogue/Digital

ANALOGUE display of time plus:

- *Digital time display, 12 or 24 hour system.
- *Digital date, month and year, plus day flag.
- *Full month calendar display, current month.
- *Full month calendar display, next month.
- Auto-calendar pre-programmed to the year 2029.

Dual time modes

- *ANALOGUE display of local time plus digital second time zone, 12 or 24 hour system.

Alarm mode

- *ANALOGUE time with digital "Alarm Set Time", 24 hour system, AM/PM and "alarm on" indicators.
- *Buzzer for 20 seconds or select "Dixie Land", "Green Sleeves" or "My Darling Clementine".

Hourly time signal

- *Chimes at noon. Easily switched on or off.

Countdown alarm timer mode

- *Amazing ANALOGUE display, plus digital countdown. Normal and net times from 1 to 60 minutes with automatic retrieval of pre-entered time.

Stop watch mode

- *ANALOGUE countup, with digital timing of net, lap and first and second place times from 1/100 second to 1 hour. Confirmation signal.

Easy setting of times and alarm with forward and backward stepping, and rapid run facility. Dims: 9.25 x 35 x 36mm approx. Mineral glass. Long life lithium battery. +/-15secs/month.



RRP (34.95)
ONLY £29.95



100 METRE WATER RESISTANT WATCHES WITH C/D ALARM AND STOPWATCH



W150
£24.95*



W150C
£21.95*



W100
£19.95

Time and auto calendar, alarm, hourly chimes, countdown alarm timer with repeat memory function, stopwatch. Time is always on display, regardless of mode. Stainless steel.

THESE SPACE INVADERS WILL ALARM YOU

CA90 (LEFT)
£19.95*




CA901 (RIGHT)
£29.95*



Time and auto calendar, calculator, alarm, hourly chimes, stopwatch, dual time. DIGITAL SPACE INVADER GAME.

CASIO'S MOST AMAZING WATCHES EVER

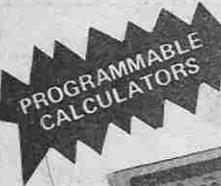


POWERFUL HIGH SPEED FX702P COMPUTER USING BASIC LANGUAGE



CASIO
FX702P
(RRP £134.95)
ONLY £119.95

LCD scrolling display of alpha/numeric (dot matrix) characters. Input can be varied from 1680 programme steps with 26 independent memories, to 80 programme steps with 226 memories. (All retained when switched off). Up to 10 programmes can be stored (P0 to P9). Subroutine: Nested up to 10 levels. FOR-NEXT looping: Nested up to 8 levels. Straightforward programme debugging by tracing. Editing by moving cursor. 55 built-in scientific and statistical functions, including regression analysis and correlation coefficient, can be incorporated in programmes. Programme/data storage on cassette tape via optional FA-2 (available soon). Optional FP-10 mini printer, PLUG-IN ROM MODULES, available soon. Two lithium batteries give approx. 200 hours' continuous operation, with battery saving Auto Power Off after approx. 6 minutes' non-use. Dimensions: 17 x 165 x 82mm (9/16 x 6 1/2 x 3 1/4"). Weight: 180g (6.3oz.).

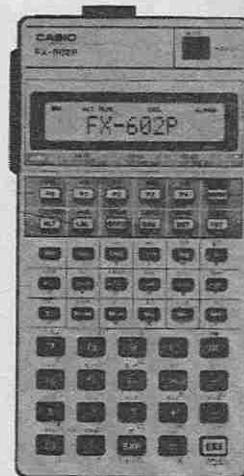

CASIO FX602P
(RRP £84.95)
ONLY £74.95

- *LCD alpha/numeric (dot matrix) scrolling display (86 types).
- *Variable input capacity from 32 functional program steps with 88 independent memories, to 512 steps with 22 memories.
- *Memory and program retention when switched off.
- *Up to 10 pairs unconditional jumps (GOTO). Manual jump.
- *Conditional jumps and count jumps. Indirect addressing.
- *Up to 9 subroutines. Nesting possible up to 9 levels.
- *50 built-in scientific functions, all usable in programmes.
- *PAM (Perfect Algebraic Method) with 33 brackets at 11 levels.
- *Ultra high speed calculations.
- *Program storage on cassette tape using optional FA-1.
- *Compatible with FX-501/2P.
- *2 lithium batteries. Approx 660 hours continuous use.
- *Battery saving Auto Power Off
- *Only 9.6 x 71 x 141.2mm. 100g.

PRICE includes VAT and P&P. Send your company order, cheque, PO or phone your Access or Barclaycard number to

TEMPUS


LEADING CASIO DISTRIBUTOR

Dept. ETI/10
164/167 East Road, Cambridge CB1 1DB
Telephone: 0223 312866

THE KEYBOARD REVOLUTION

CASIOTONE POLYPHONIC KEYBOARDS With built in Amplifier and Loudspeaker.

CASIOTONE MT-30

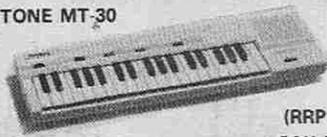

(RRP £115.00)
ONLY £95.00

22 instruments over 3 octaves. 4-position sound memory. Battery or mains. O/P jack. Dims: 2½ x 22½ x 6½". 6lb.

CASIOTONE 202




(RRP £325.00)
ONLY £275.00

"Son of success... The two harpichords demonstrate the Casiotone's talent for sparkling crystal clear tones... Even more impressive is the clav..." (Melody Maker).

49 instruments over 4 octaves. 4 voice memory function with push button selection. 3 vibrato settings and sustain. Pitch control. O/P jacks. AC only. 3½ x 34½ x 11½". 15.8lbs

CASIOTONE 301

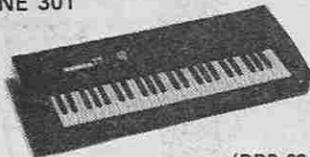

(RRP £245.00)
ONLY £199.00

14 instruments over 4 octaves. 8 x 2 rhythm accompaniments. Vibrato and delayed vibrato. Start/stop, synchro start, tempo control tempo indicator, and rhythm volume. Pitch control. AC only. O/P jacks. 4½ x 31½ x 12½". 27lbs.

CASIOTONE 401




(RRP 345.00)
ONLY £295.00

As 301 plus following: 16 rhythm accompaniments, with fill-in. Casio Auto Chord for one finger or auto accompaniment. Plays major, minor and 7th chords with bass. Balance control, C.A.C. lever, chord lever, memory lever and octave switch. Dimensions as 301. Weight 28.2lb.

BECOME AN INSTANT MUSICIAN NO EXPERIENCE NECESSARY

The success story of 1981. Hundreds sold already! As featured on "Tomorrow's World".

CASIO VL-TONE (VL-1) Electronic Musical Instrument and calculator

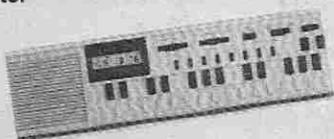

(RRP 39.95)
ONLY £35.95

VL-1 records and plays back up to 100 notes as a melody. ONE KEY PLAY or AUTO PLAY of Piano, Violin, Flute, Guitar and Fantasy, or create your own unique sounds with A.D.S.R. 10 built-in AUTO RHYTHMS and TEMPO CONTROL. LCD digital readout of notes and tempo Also a calculator. Battery powered with memory and programme retention. Integral amplifier/speaker. Output jack. With song book. Dimensions: 1½ x 11½ x 3".

Send 20p for illustrated catalogue of selected casio and seiko products.

LCD DIGITAL MULTIMETERS

ALL PRICES INCLUDE VAT

WHILE STOCKS LAST!


MODEL 6110

3½ Digit LCD featuring 23 ranges with volts/ohms autorange, unit and sign indicators, 10 amp AC/DC, battery warning, low power ohms ranges. Range hold and continuity buzzer. Fuse protected. Resolution 0.1mV DC, 1mV AC, 10 microamp, 0.1ohms. Supplied with battery and leads.

Fitted top quality rotary switch.

Was £85.95 as advertised by us

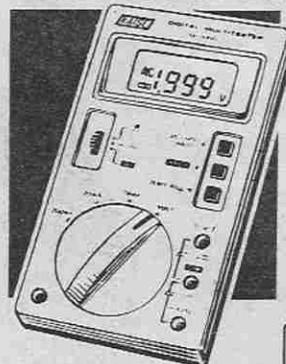Now **£59.95** post paid.
plus free carry case.



■ LIMITED OFFERS
WHILST STOCKS LAST
■ ORDER BY POST OR
PHONE IN WITH
BARCLAY - VISA -
ACCESS - TRUST
CARDS.

RANGES

AC/DC Current - 20mA/200mA/10 amp.
DC Voltage (auto) - 200mV/2V/
20V/200V/1000V.
AC Voltage - 2V/20V/200V/600V.
Resistance (auto) - 200/2K/20K/
200K/2000K ohm.

ALSO AVAILABLE MODEL 6220


As 6110 but without range hold and continuity buzzer. Only two AC/DC 200mA/10 amp ranges i.e. 22 ranges. Was £55.95. Now **£42.95** post paid.

AUDIO ELECTRONICS

Cubegate Limited

OPEN SIX DAYS A WEEK • CALL IN AND SEE FOR YOURSELF

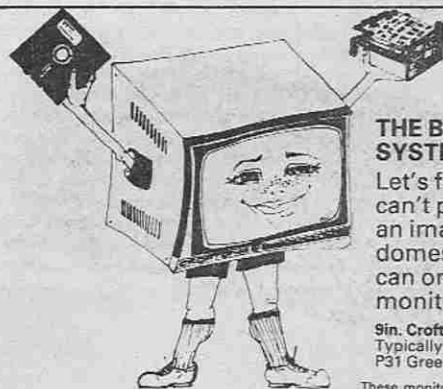301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564
ALSO AT HENRY'S RADIO, 404/406 EDGWARE ROAD, LONDON W2



THE BODY OF ANY SYSTEM

Let's face it - you can't produce as crisp an image on a domestic TV as you can on a Crofton monitor.

9in. Crofton Monitors
Typically P4 White.....£84.97
P31 Green.....£79.32

These monitor and Shugart prices are dependent upon sterling/dollar conversion rates. Phone us for up-to-date prices.

SHUGART FLOPPY DISK DRIVES

No case. No power supply.
SA 400 5¼in. S.S.S.D.£149.05
SA 450 5¼in. D.S.S.D.£283.31
SA 800 8in. S.S.S.D.£340.52

FLOPPY DISKS - BOXES OF TEN

Single-sided 35/40 Track£26.45
Double-sided 35/40 Track 5¼in.£37.95
Single-sided 77 Track£41.40
Double-sided 77 Track 5¼in.£47.15
Single-sided 8in.£40.25

IKEGAMI 12in. MONITORS

P4 White£171.50
P31 Green£184.97

2/3in. FULLY INTERLACED C.C.T.V. CAMERAS£149.00

ALL THE ABOVE PRICES INCLUDE V.A.T. AND CARRIAGE




ALL MAJOR CREDIT CARDS
ACCEPTED: Small surcharge



CROFTON ELECTRONICS LTD.

35 Grosvenor Road, Twickenham, Middx, TW1 4AD
01-891 1923/1513

DIGEST

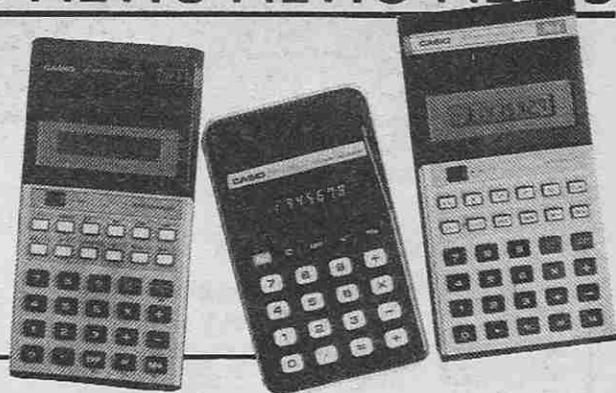

Cover Up!

Smiths Industries Time Controls, manufacturers of time switches, are introducing a special protective cover for their 'European' range of products. The new cover is made of a resilient waterproof combination of metal and plastic, and is designed to be mounted integrally to the 'European' time switch models without either adhesives or major installation requirements. It has been developed as a protective device, thus making the time switch range equally suitable for both interior and external, home or commercial use. The tough plastic will not only protect the time switch from inadvertent knocks but will also keep it waterproof in situations like exterior walls. The cover also has a sealing arrangement to prevent the setting being tampered with, particularly by children, although it is not difficult to remove when time adjustments need to be made. The European time switches are very popular and feature quartz driven motor and battery reserve which allows for up to 150 hours of supplementary power in the event of power failure. Sixty minute, 24 hour and 7 day versions are available. The cover will fit any of the range and is available from leading electrical appliance outlets and wholesalers throughout the UK. Prices for the timeswitches themselves vary from £11.81 to £35. Smiths Industries Time Controls, Waterloo Road, Cricklewood, London NW2 7UR.

Elementary My Dear Watson

As many education authorities are now allowing and even encouraging the use of calculators, Casio are attempting to help bridge the gap for youngsters between using the simple four-function calculator and its scientific counterpart. They have launched two models which they describe as 'elementary' — the FX5 and the FX7. The FX5 has a 'scientific' layout giving access to fractions, roots, pi, percentages, square, reciprocal, change-sign, parenthesis (three levels) and independent memory. The FX7 also incorporates sine, cos, tan and log functions, while introducing the concept of exponents. There is an LCD display on both models and batteries are the readily available AA size. The recommended prices are: FX5 £10.95, FX7 £12.95 and they should be available from any Casio dealer, but in case of difficulty contact Casio Electronics Co Ltd, 28 Scrutton Street, London EC2A 4TY.

Something In The Air


In recent years it has become necessary to monitor precisely the meteorological environment around nuclear power stations, and to this end Frazer-Nash of Hershham, Surrey, has supplied several sets of windspeed and direction monitoring equipment to the Central Electricity Generating Board, including the recent commissioning of a wind monitoring system at the Wylfa Power Station in North Wales. The MK 5B system installed there uses advanced digital and analogue techniques to process the signals from windspeed and direction sensors, mounted at different heights on a remotely sited tower. Signals from the sensors, displayed at the remote site on a meter panel are transmitted to the main electronics cabinet in the Power Station Administrative Building. A second cabinet is for lightning protection and has self-test facilities which allow system testing from the tower site or from the cabinet itself. The wind systems are manufactured to licensed designs of the British Meteorological Office and can be used to upgrade earlier Met Office approved systems. MK 5B systems are designed to use lightweight cables over long distances from the sensors, thus reducing installation and maintenance costs. Telemetry can be supplied to transmit readings via standard PO telephone lines or radio links. For further details of wind monitoring systems contact Frazer-Nash (Electronics) Ltd, The Old Forge, Pleasant Place, Hershham, Walton-on-Thames, Surrey.

TV Game Comeback

TV games are currently having an incredible resurgence of popularity in this country after a massive drop in demand over the past few years. Hong Kong's TV games shipments to Britain have risen by 260% in the first quarter of this year, effectively making us their biggest market — even overtaking West Germany, the former largest market. Exports to the third largest market, the USA, also rose by 1,047%, thus giving a total export rise for Hong Kong of 112%.

Disc Shooting

Thorn EMI Video Programmes Ltd has now begun to commission programme material purpose-made for the new VHD Videodisc System. Among the first productions to be launched in June 1982 will be 'Great British Fishing' which features the well-known footballer and amateur angler Jack Charlton. The material is designed to exploit the data retrieval facilities offered by the VHD system. The fishing programme runs for two hours and covers several angling locations including coarse, game and sea fishing, all under the expert guidance of Chris Dawn, Features Editor of 'Angling Times'. The programme will also include a 'data section' — individual frames of information, accessible at the touch of a button, to provide background knowledge of each location featured, details of local accommodation, fishing rights, travel guides and information on other local attractions, tackle suppliers, local angling records and so on.

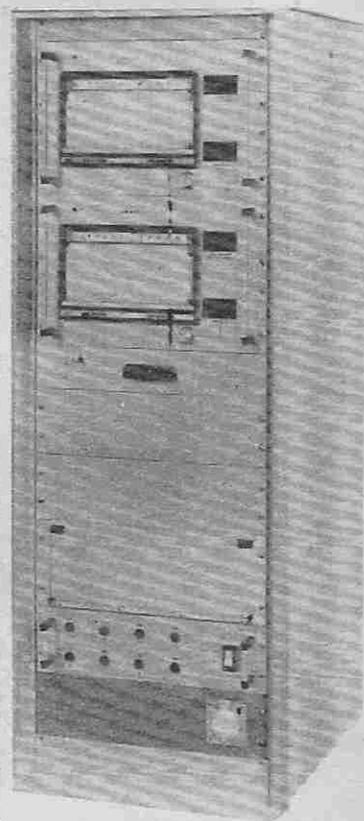

MICROCOMPUTER COMPONENTS

LOWEST PRICES - FASTEST DELIVERY

Device	Price	Device	Price	Device	Price	Device	Price	
MEMORIES								
NEW LOW PRICES								
CPUs		2114 L 200ns		74LS49	0.59	CMOS 4000		
6502	4.95	1+	1.28	74LS51	0.14	'B' SERIES		
6800	3.70	(LOW POWER)		74LS54	0.15	4000	0.12	
6802	5.11	25+	1.19	74LS55	0.15	4001	0.13	
6803	11.80	25+	1.19	74LS73	0.20	4002	0.13	
6809	11.95	2114 L 300ns		74LS74	0.17	4006	0.60	
8085A	5.50	1+	1.28	74LS75	0.28	4007	0.17	
Z80 CPU	4.00	(LOW POWER)		74LS76	0.20	4008	0.55	
Z80A CPU	4.82	FOR ACORN		74LS78	0.24	4009	0.28	
		ETC.		74LS83	0.50	4010	0.28	
		25+	1.19	74LS85	0.70	4011	0.14	
		2708 450ns		74LS86	0.18	4012	0.17	
SUPPORT CHIPS		1+	1.99	74LS90	0.30	4013	0.33	
6520	3.15	25+	1.85	74LS91	0.80	4014	0.58	
6522	4.95	2716 450ns		74LS92	0.35	4015	0.58	
6532	7.95	1+	2.49	74LS93	0.34	4016	0.28	
6821	1.74	(single +5v)		74LS95	0.44	4017	0.45	
6840	4.20	25+	2.37	74LS109	0.25	4018	0.58	
68488P	9.11	2532 450ns		74LS112	0.25	4019	0.29	
6850	1.70	1+	5.50	74LS113	0.25	4020	0.58	
6862	6.91	25+	5.31	74LS114	0.25	4021	0.60	
6871A1T	18.70	2732 450ns		74LS122	0.39	4022	0.62	
6875L	4.18	1+	5.43	74LS123	0.55	4023	0.17	
6880	1.07	25+	5.24	74LS124	1.00	4024	0.38	
6887	0.80	4116 150ns		74LS125	0.28	4025	0.16	
8212	1.70	1+	1.15	74LS126	0.28	4026	0.99	
8216	1.70	25+	1.06	74LS132	0.45	4027	0.30	
8224	2.45	4116 200ns		74LS136	0.28	4028	0.55	
8228	3.95	1+	0.80	74LS138	0.34	4031	1.65	
8251	3.95	25+	0.72	74LS139	0.37	4033	1.60	
8253	7.95	4118 200ns		74LS145	0.75	4035	0.72	
8255	3.95	1+	3.90	74LS148	0.90	4040	0.57	
AY-3-1015	3.90	25+	3.23	74LS151	0.34	4041	0.69	
AY-5-1013	3.45	6116 200ns		74LS153	0.35	4042	0.54	
AY-5-2376	6.95	1+	10.95	74LS155	0.39	4043	0.59	
MC1488	0.64	2k x 8	25+	9.95	74LS156	0.38	4044	0.64
MC1489	0.64	8264 200ns		1+	12.00	74LS157	0.34	
MC14411	6.94	1+	12.00	74LS158	0.36	4046	0.68	
MC14412	7.99	64k x 1	25+	11.00	74LS160	0.39	4047	
RO-3-2513L	7.70	74LS161		0.39	4048	0.54		
RO-3-2513U	7.70	REGULATORS		74LS162	0.39	4049	0.30	
Z80 CTC	4.00	7805	0.50	74LS163	0.39	4050	0.30	
Z80A CTC	4.00	7812	0.50	74LS164	0.47	4051	0.59	
Z80 DMA	11.52	7905	0.55	74LS165	0.99	4052	0.68	
Z80A DMA	9.99	7912	0.55	74LS166	0.84	4053	0.59	
Z80 DART	7.18	CRYSTALS		74LS173	0.70	4054	1.20	
Z80A DART	7.18	1 MHz	3.00	74LS174	0.54	4055	1.20	
Z80 PIO	3.78	1.8432 MHz	2.50	74LS175	0.54	4060	0.89	
Z80A PIO	3.78	2.4576 MHz	2.50	74LS181	1.30	4063	0.95	
Z80 SIO-0	13.95	4 MHz	1.65	74LS190	0.55	4066	0.34	
Z80 SIO-1	13.95	DIL SOCKETS		74LS191	0.55	4068	0.17	
Z80 SIO-2	13.95	8 pin	0.07	74LS192	0.69	4069	0.17	
Z80A SIO-0	13.95	14 pin	0.09	74LS193	0.59	4070	0.19	
Z80A SIO-1	13.95	16 pin	0.09	74LS194	0.39	4071	0.19	
Z80A SIO-2	13.95	18 pin	0.15	74LS195	0.39	4072	0.19	
		20 pin	0.17	74LS196	0.58	4073	0.19	
CRT CONTROLLERS		22 pin	0.21	74LS197	0.65	4075	0.17	
9364AP	5.94	24 pin	0.23	74LS221	0.60	4076	0.60	
9365	62.90	28 pin	0.25	74LS240	0.89	4077	0.22	
9366	62.90	40 pin	0.29	74LS241	0.89	4078	0.24	
6845	9.50	74LS SERIES		74LS242	0.79	4081	0.14	
		74LS00	0.11	74LS243	0.79	4082	0.19	
DATA CONVERTERS		74LS01	0.11	74LS244	0.79	4085	0.63	
ZN425E	3.50	74LS02	0.12	74LS245	0.89	4086	0.69	
ZN426E	3.00	74LS03	0.12	74LS247	1.34	4093	0.39	
ZN427E	6.28	74LS04	0.13	74LS248	1.00	4502	0.23	
ZN428E	4.78	74LS05	0.13	74LS249	0.68	4507	0.39	
ZN429E	2.10	74LS06	0.13	74LS251	0.39	4508	1.90	
ZN432	28.09	74LS08	0.13	74LS253	0.39	4510	0.60	
ZN433	22.59	74LS09	0.13	74LS257	0.44	4511	0.49	
ZN440	56.63	74LS10	0.13	74LS258	0.38	4512	0.60	
ZN450E	7.61	74LS11	0.14	74LS259	0.38	4514	1.49	
		74LS12	0.15	74LS261	1.90	4515	1.49	
		74LS13	0.22	74LS266	0.23	4516	0.75	
CONVERTER H'BOOK	1.00	74LS14	0.44	74LS273	0.90	4518	0.40	
DATA CONVERTER KIT	29.95	74LS15	0.13	74LS279	0.34	4519	0.28	
		74LS16	0.12	74LS283	0.44	4520	0.69	
		74LS17	0.14	74LS290	0.56	4521	1.49	
		74LS18	0.14	74LS293	0.45	4522	1.20	
		74LS19	0.18	74LS365	0.34	4526	0.70	
		74LS20	0.14	74LS366	0.34	4527	0.89	
		74LS21	0.19	74LS367	0.34	4528	0.70	
		74LS22	0.12	74LS368	0.34	4532	0.89	
		74LS23	0.14	74LS373	0.74	4541	1.39	
		74LS24	0.16	74LS374	0.74	4543	0.99	
		74LS25	0.16	74LS375	0.47	4553	2.90	
		74LS26	0.16	74LS377	0.89	4555	0.49	
		74LS27	0.13	74LS378	0.69	4556	0.54	
		74LS28	0.34	74LS386	0.28	4585	0.98	
		74LS29	0.39	74LS390	0.59			
		74LS30	0.60	74LS393	0.58			

OFFICIAL ORDERS WELCOME - QUANTITY DISCOUNTS AVAILABLE

MIDWICH COMPUTER COMPANY LTD.
HEWITT HOUSE,
NORTHGATE STREET
BURY ST. EDMUNDS
SUFFOLK, IP33 1HQ
Tel: (0284) 701321

ALL PRICES EXCLUDE POST AND PACKING (50p ON ORDERS UNDER £10) AND V.A.T.

ALL ORDERS DESPATCHED ON DAY OF RECEIPT WITH FULL REFUND FOR OUT OF STOCK ITEMS IF REQUESTED.

CREDIT CARD ORDERS WELCOME (ACCESS AND VISA) - 24 HOUR TELEPHONE SERVICE



MUSICAL MICRO 24 TUNE DOOR BELL

BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

- ★ Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware
- ★ Texas Instruments TMS 1000 microcomputer
- ★ Comprehensive kit manual with full circuit details

ONLY £11.95
+ 75p p&p
UK ONLY

Ready built version also available. Special offer price **£15.95** incl. p&p.

Plays 24 well-known tunes including: Star Spangled Banner, William Tell Overture, Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful, plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

TMS 1000N 

-MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output

Car Horns Musical Boxes Alarms
Amusement Machines Public Address etc

£4.95 (UK only)
or 3 for **£12.50** incl. p&p.

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-10 DAYS FOR DELIVERY

Please send me:
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.
NAME _____
ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____


Signature _____
CHROMATRONICS

Components

Greater Capacity


Compstock's family of electrolytic capacitors are designed to meet the requirements of power supply circuits in consumer and industrial applications. The Type M series of aluminium electrolytic capacitors,

from National Panasonic, is available in values ranging from 220-22,000 μ F, -10% +50%, and with working voltage ratings up to 500 V DC. Operational temperature ranges vary between -25°C to +85°C according to the working voltage rating, and the series exhibits good DC leakage characteristics. The Type M capacitor is constructed with a vinyl-insulated aluminium can and an annular, chassis mounting clip (for two hole mounting) at the base, which incorporates industry standard solder-slot terminations. Further information from Compstock Electronics Ltd, Compstock House, London Road, Stanford-le-Hope, Essex SS17 0JU.

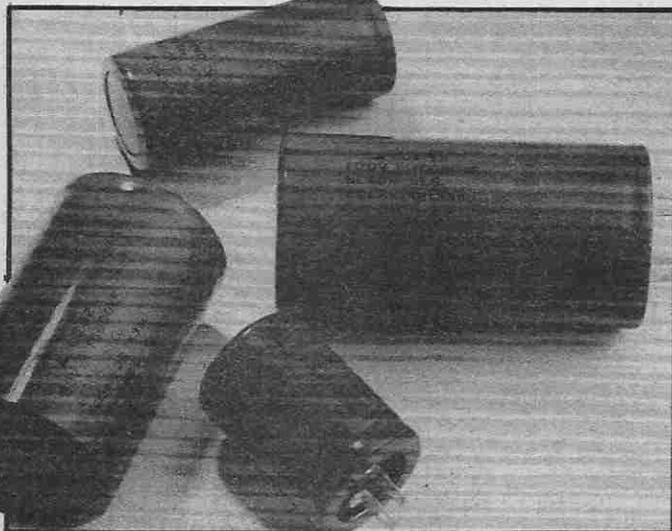


Try It First

For all you eager circuit builders out there BOSS Industrial Mouldings Ltd have launched an upgraded range of their Bimboard Designer Prototyping systems. The new Bimconsole has either one, two or three individual Bimboards mounted on a 15° sloping front panel with a triple rail power supply. Each Bimboard comprises a central breadboarding area in which 47 horizontal rows of 5 interconnected sockets are set either side of a central channel on a 2.54 mm matrix, together with integral bus strips running up each side for power carrying etc. The Bimboard will accept .3" and .6" pitch DIL packages as well as resistors, transistors, diodes, capacitors etc, which can be easily plugged in. It incorporates a fixed 5 V DC at 1 A supply, and independently adjustable positive and negative rails ± 5 V to ± 15 V DC at 0.5A supplies, all brought out to top panel terminals that simultaneously accept 4 mm plugs and stripped wires. 220-240 V AC, 50-60 Hz mains input is via an IEC plug and socket with a screwdriver-release fuse holder providing 500 mA anti-surge protection. Full details on the Bimboard are available from BOSS Industrial Mouldings Ltd, 2 Herne Hill Road, London SE24 0AU.

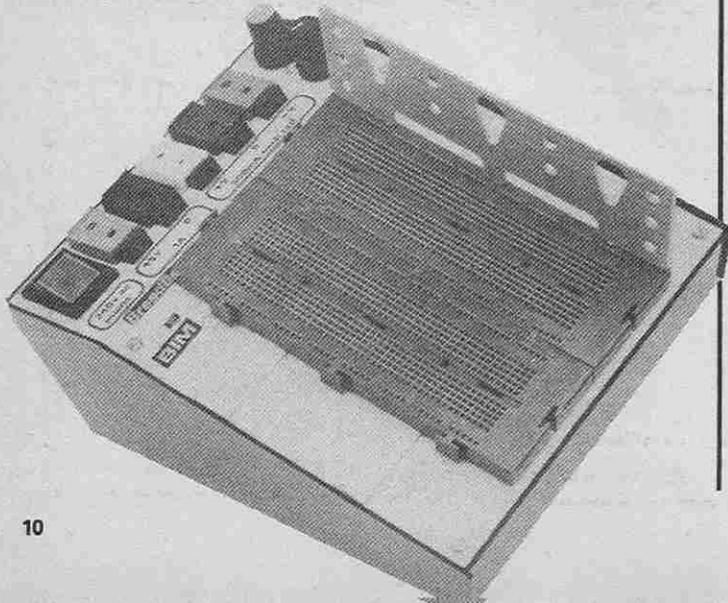

Light Entertainment

From Cetronic Ltd come the RC80 and RC120 Rectilinear Lighting Faders for use in the control of lighting for theatres, concert halls, auditoriums, discos etc. Their working life is greater than 100,000,000 operations and they are designed within a rigid insulated frame; the resistance and collector tracks are made from hard-wearing conductive plastic for long life and smooth operation plus the advantages of very low noise level, good linearity, low residual voltage, almost infinite resolution and high traverse speed. They are available with electrical travel of 8 mm (1 W) and 120 mm (2 W) at 10K nominal resistance. Both models incorporate stand off terminals for easy PCB mounting. For details of suppliers and prices contact Cetronic Ltd, Hoddesdon Road, Stanstead Abbots, Ware, Herts SG12 8EJ.

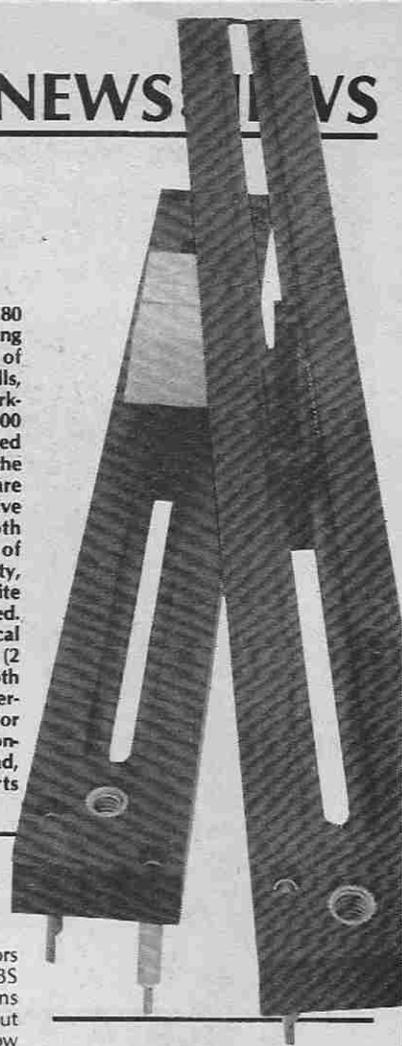

Capacitor Catalogue


A 10-page catalogue of capacitors has been published by RBS Capacitors Ltd, and it contains everything you need to know about their 125°C to 300°C high and low voltage ceramic, chip and mica capacitors. The booklet is illustrated with photos, diagrams and tables. Methods of installation are described and instructions, theory and

parts numbering are explained in clear language. For further details contact RBS Capacitors Ltd, Orchard Works, Vencourt Place, London W6.



IC Sockets

The TI C69 range of screw-machined integrated circuit sockets is now available from BA Electronics. They provide a high level of performance in multiple insertion applications. The low-profile sockets have tin-plated pins for solder-tail assembly, with four-leaf gold-plated beryllium-copper contacts for good electrical performance. Sockets are available with from 6 to 64 pins. Further details are available from BA Electronics Ltd, Millbrook Road, Yate, Bristol BS17 5NX.

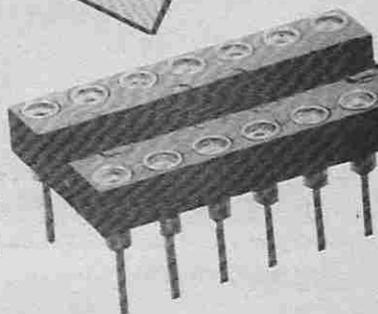


THE EXHIBITION FOR THE ELECTRONICS ENTHUSIAST

COMPUTERS • AUDIO • RADIO • MUSIC • LOGIC • TEST GEAR • CB • GAMES • KITS

Wednesday 11th November 10 a.m.-6 p.m. Thursday 12th November 10 a.m.-8 p.m.

Friday 13th November 10 a.m.-6 p.m. Saturday 14th November 10 a.m.-6 p.m.

Sunday 15th November 10 a.m.-4 p.m.

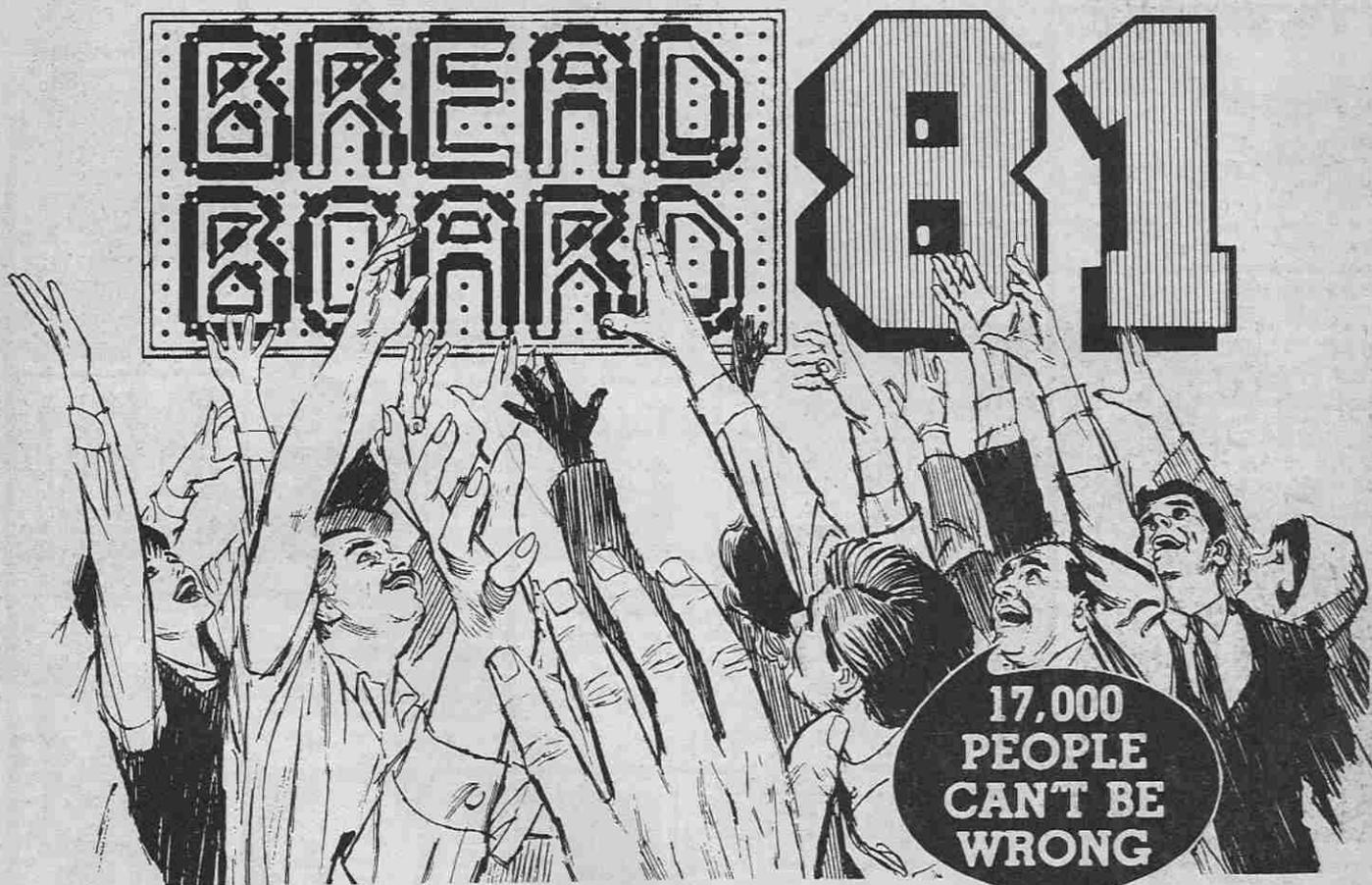

COMPONENTS • DEMONSTRATIONS • SPECIAL OFFERS • MAGAZINES • BOOKS

Any one of the 17,000 people who thronged the RHS for the Breadboard exhibition last year will need no introduction to this year's premier show for the electronics enthusiast. They already know all about the demonstrations, bargain sales, bookstalls, games, kits, computers and music machines to be found at BREADBOARD 81. They could name you all the leading companies who were there to see — and to buy from, at fantastic prices.

Even those lucky 17,000 would be surprised to hear that this year we've **improved** BREADBOARD still further! More stands, more demonstrations and wider gangways to make it all easier to enjoy!

BREADBOARD 81 is the place to be from November 11th to 15th at the RHS Hall. Why not come and find out for yourself how much you missed last year? We can promise plenty to see and do at BREADBOARD 81.

Close to Victoria Station and NCP car parking facilities.

Cost of entry will be £2.00 for adults and £1.00 for children under 14 yrs and O.A.P.s.
ORGANISED BY MODMAGS LTD., 145 CHARING CROSS ROAD, LONDON WC2H 0EE.

ROYAL HORTICULTURAL SOCIETY'S
NEW HALL, GREYCOAT STREET,
WESTMINSTER, LONDON S.W.1.

To avoid queuing, advance tickets will be available from
Advance Tickets BB '81.
Modmags Ltd, 145 Charing Cross Road,
London WC2H 0EE.

Special Advance Booking Price

Adults £1.75 Children under 14 yrs and O.A.P.s 80p

Please send tickets @ £1.75 tickets @ 80p

To:.....

.....

.....

.....

I enclose PO/cheque for f.....

Advance tickets **MUST** be ordered **BEFORE** 20th October 1981.

32 TUNES DOORCHIME/BURGLAR ALARM

This doorchime is powered from 9V d.c. source, and has battery back-up facility. It has an automatic tune advance facility and single or dual play options at 3 selectable speeds. A built-in burglar alarm circuit allows construction of a NORMALLY CLOSED alarm system, two bell pushes can be connected, each playing different tunes.

£9.95 + 95p P&P

DUAL TIME COUNTDOWN ALARM CHRONO

This superb watch has all the features one would ever need. It has selectable 12/24-hr. display, count-down timer/alarm, dual time zone, chronograph with lap time facility, 24-hr. alarm with 5 min. snooze facility, back light fully adjustable stainless steel bracelet and we are offering it at our incredibly low price.

£8.95 + 50p P&P

FLUORESCENT PORTABLE LIGHT

A very useful battery-operated high-power fluorescent light for use in the car or for camping. Uses 8" C size cells and it has a socket for 12V DC input for use in the car. Power consumption is 6 watts. New circuit makes batteries last longer.

£4.95 + 95p P&P

WALKIE TALKIES WITH AM RADIO

These walkie talkies have AM radio built into them. Other features include Morse Code key, volume control and telescopic antenna. Frequency 49MHz. AM. Range approx. 16th mile.

£21.95 per pair + £1.95 P&P

SEARCH 2 WALKIE TALKIES

These are good quality walkie talkies made by GENERAL ELECTRIC CO. Features include Morse Code key and colour code telescopic antenna. Frequency 49MHz. AM. Range approx. 16th mile. Price elsewhere £19.95. Our price

£12.95 per pair + £1.95 P&P

MINI COM WALKIE TALKIES

These are very neat and very small walkie talkies, they will fit in your pocket. Ideal gift for all ages. Frequency 49MHz. AM. Range approx. 16th mile. Our price per pair is

£10.95 + 95p P&P

CB/TV1-FM/AIR-PB-WB PORTABLE RADIO

This is a specialist receiver and it covers frequency bands which are not available on ordinary receivers. It covers 54-176MHz and also receives 40 channel CB. It has volume and squelch controls.

£14.95 - £1.25 P&P

HANDHELD SPACE INVADERS

A superb game, provides endless fun for children and adults alike. WARNING: THIS GAME CAN SERIOUSLY EFFECT YOUR PAST-TIME! It gives you 90 seconds to hit enemy craft. The sleeping time and 4 digit score is constantly displayed. Score is decremented if you hit a friendly ship or if enemy missile penetrates your defence.

£10.95 + 75p P&P

FM WIRELESS MICROPHONE

This high quality Electret microphone can be tuned to transmit in the range 88-95MHz FM. It can be received on any FM receiver, the range depends on the sensitivity of the receiver. Uses one penlight battery which fits inside the microphone. Ideal for parties, discos and clubs.

£8.95 + 50p P&P

LADY'S SUGAR COATED WATCH

Beautifully styled lady's LCD watch with matching bracelet. Functions includes: hours, mins, secs, month, date and back light. Super value for money. Its available in chrome or gold colour.

£5.95 + 50p P&P

SLIM PENDANT WATCH

This watch is beautifully designed as a slim pendant and comes complete with a 26in. long neck chain. The functions include: hours, minutes, seconds, day, month and 4-year auto calendar. Comes in gold colour and is ideal for day and night wear.

£6.95 + 50p P&P

LADY'S 6-DIGIT MUSICAL ALARM

This watch plays Beatles song "Yesterday". It displays hour, mins, secs and date. It has a melody test button, back light and a musical snooze alarm. Comes in gold or chrome colour.

£10.95 + 75p P&P

SILENT ALARM/POCKET PAGER

This is an individually coded 4 watt radio transmitter and pocket pager receiver. It has a range of 2 miles. It can be used to protect your vehicle or a property and can also be used for paging. Power requirement for transmitter is 12V D.C.

£89.95 - £2.95 P&P

MINI LCD DESK CLOCK

This is a very versatile desk clock with large (15mm high) digit LCD. Functions include hours, mins, secs, month and date.

£7.95 + 75p P&P

BICYCLE BURGLAR ALARM

40 channel C.B. receiver and AM radio. All in one.

£19.95 + 95p P&P

AM/FM STEREO RADIO

This is a lightweight 2-band receiver with hot time facility to let you know what is going on around you. It comes complete with stereo headphones and a carrying case. You can wear it on your belt or carry it on your shoulder.

£19.95 + £1.95 P&P

Car coffee maker **£3.95** + 75p P&P
 Lady's 5-function LCD watch **£3.95** + 50p P&P
 Gents 5-function LCD watch **£3.95** + 50p P&P
 Bicycle horn with police/fire/ambu **£3.50** + 75p P&P
 Bicycle radio AM **£4.95** + 75p P&P
 AM/FM/air band pocket radio **£6.95** + 75p P&P
 Slim pen watch **£6.95** + 50p P&P

RAPIDE REACTOLITE SUNGLASSES

These photochromatic sunglasses get darker as the sun gets brighter, and are crystal clear in the shade. These are available in strong metal frames in silver, gold or black colour. These come complete with a carrying case. The suggested retail price is £12.95, but we are offering them at a very special price of

£4.95 + 75p P&P

SUPERSPEED AIR PUMP

Plug this high speed piston compressor to your car's cigarette lighter socket and you can inflate tyres, air beds, dinghys or footballs. It comes complete with rubber hose and locking valve, high pressure and cone adaptors.

£10.95 + 95p P&P

CLAPPER SONIC CONTROL CAR

This sports car can be controlled by clapping your hands or by blowing a whistle. It goes straight or backs in circular path, either of these motions can be commended by hand clapping. Provides lots of fun for all the family. Ideal gift for ages 3 and over.

£6.95 + 95p P&P

RADIO CONTROLLED PORSCHE 928

This 1/16 scale model is a beautifully designed car. It has forward, reverse, stop, turn right and turn left controls. The hand set operates on 27MHz and has a telescopic antenna. Its ideal gift for children over 6 years.

£24.95 + £1.95 P&P

CAR ELECTRIC AERIAL

Add a little luxury to your car by installing this motorised car aerial. Can be installed in any car or truck with 12V supply. It is an excellent value for money and is an ideal gift.

£8.95 + £1.25 P&P

TELEPHONE ANSWERING SYSTEM WITH REMOTE CONTROL

You will never miss that important phone call with this machine. You can call your number from any telephone and with the remote control bleeper check to see if any calls have been recorded. You can then erase or retain the messages. It comes complete with microphone, cassette, remote control bleeper and adaptor. We are offering this system at a very low introductory price. Elsewhere it is being sold for £149.

£95.95 + £2.90 P&P

QUARTZ TRAVEL ALARM CLOCK

This is a very versatile alarm clock, you can use it in the car, in the kitchen or as a desk top clock. Large (1cm character size) display makes it easy to read from a distance. It has 4-year auto calendar, backlight, AM/FM indicator and alarm on indicator.

£7.95 + 75p P&P

17 PC MINI SOCKET SET

This triple chrome plated, rust proof metric set consists of 5" reversible ratchet handle, 5" cross bar, 5" flexible handle, 2" extension bar, 6" extension bar, 11 sockets (6 PT) 4, 4.5, 5, 5.5, 6, 7, 8, 9, 10, 11, 12mm. All this comes in a neat little metal case.

£3.95 + £1.20 P&P

SMOKE DETECTOR FIRE ALARM

This early warning smoke detector can detect the fire at its early stages, and give those extra vital minutes to save life. At our offer price you could put one in each room. If you buy four, we will give you one free. Each unit comes complete with a battery. (Please note that all units are tested before despatch in case of malfunction, our liability is limited to the replacement of alarm unit.)

£8.95 + 75p P&P (P&P for more than three units is £2.50)

CAR STEREO PLAYER WITH AM/FM-MPX RADIO

This compact, quality product is designed to provide you with exceptional listening pleasure. The features include: AM/FM dial-in-door, local, distance attenuator switch for better stereo reception, AM/FM indicator, FM stereo indicator, Fast forward and eject button for cassette, balance, volume and tone controls.

£29.95 + £1.90 P&P
 Suitable speakers £5.00 per pair + 55p P&P

TALKING ALARM CLOCK/STOPWATCH

This "Sharp" Talking Clock is a "state-of-the-art" product. On pressing the button it announces the time. At the preset alarm time a musical alarm is played and again the time is announced. It has 5 mins. snooze facility. Also has a useful timer and speaks time elapsed every 1 min., 5 mins, or 30 mins., whichever is selected in the stopwatch mode it announces the elapsed time at preset intervals or on pressing of a button at any time it is an ideal gift, especially useful for blind people. Overall size is 11.4 x 6 x 2.2cms.

£39.95 + £1.95 P&P

AKHTER INSTRUMENTS LTD.
 11-15 BUSH HOUSE
 HARLOW, ESSEX CM18 6NS
 Tel. 0279 723452

PHONE YOUR BARCLAYCARD OR ACCESS NUMBER FOR IMMEDIATE DESPATCH 24-hour service

GUARANTEE: All our products are guaranteed for a period of 1 year. We also offer a 10-day money back guarantee. (If you are not completely satisfied with our product, then return within 10 days in same condition as you received it.) All our products are fully tested before despatch.



ACTing Up!

Hitachi are launching a follow-up to their successful ACT-01 bookcase hi-fi system called (surprise, surprise) the ACT-02. The system comprises of four main separate units — amplifier, tuner, cassette deck and speakers — each miniaturised and with brushed aluminium fascias. The amp and tuner measure only 230 mm wide by 74 mm high and, when placed on top of one another, come to the same height as the cassette deck. The amp has an output

of 25 W per channel with no more than 0.3% total harmonic distortion. It has five LED power output meters per channel. The tuner receives FM, medium wave and long wave and has a flywheel coupled tuning knob and LED tuning indicators for spot-on station selection. For good clear, clean FM, the front end features a dual gate MOSFET. The cassette deck accepts metal, normal and C₆₀ tapes. It has the Hitachi self-programme search system which lets you skip backwards and forwards to find your favourite track. There is also a recording mute function for editing as you record, microphone mixing with volume control, Dolby noise reduction and an air damped ejection system. The speaker enclosures contain a 12 cm woofer and a 5 cm tweeter. The ACT costs £349 complete and further information about it can be obtained from Hitachi dealers.

Happy Answer

Do you get irritated when you make a phone call and the only answer you get is the droning voice of one of those dratted answering machines? Well, GMTC are attempting to lower a lot of blood pressure levels by launching their 'Happy Answer Message Cassettes'. They carry six hilarious (?) singing messages, written, produced and recorded by Mitch Murray who is renowned for hits like 'Bonnie & Clyde', 'You Were Made For Me' and

'I Like It'. The idea of the tape is to put the caller in the right frame of mind for putting his message on the end of the tape. All too often people just mutter expletives and put the phone down — equally irritating for the recipient! The Happy Answer Message Cassettes are £2.50 each from all GMTC stockists including Harrods, Dickins & Jones, Alders and branches of W H Smith and Rymans, or by mail order from their showroom at 15 Newman Street, London W1. Telephone orders on 01-580 3647.

Audio Yearbook

Studio Sound's Pro-Audio Yearbook 1981, edited by Angus Robertson, is the second of a series of reference books for the professional audio and video markets. It's a massive hardbacked effort, running to 624 pages of information for the professional recording and broadcasting industries. The contents are arranged in two parts. The first consists of 71 alphabetically sequenced sections on equipment and services ranging from 'Amplifiers, Power' through 'Engineers, Freelance and Consultant' and 'Links, Radio' to 'Turntables, Pick-up Arms and Cartridges'. The coverage is exhaustive; the only glaring omission seems to be the area of professional sound reinforcement speaker systems. Curiously, synthesisers are included; these are normally considered to be musical instruments rather than sound equipment. Within each section the information is presented in a highly condensed fashion yet with sufficient detail to allow comparison between the makes and models on offer. Prices, in pounds sterling or US dollars, are quoted for most items to permit cost comparison. The first part also contains useful reference material; a list of pro-audio dealers around the world, international power supply standards, and a 'Jargon' chapter (which inexplicably contains many terms from television and even one or two from the print industry). The second, smaller, part consists of a series of indexes to companies and subjects mentioned in the first part, plus a list of international pro-audio manufacturers and distributors giving an address, telephone and telex number and a contact name for each. The Pro-Audio Yearbook will be a useful tool for anyone purchasing professional grade equipment. The inclusion of every aspect of pro-audio — recording, radio, television and film sound — means that much of its content will be irrelevant to any one user; presumably the size of the individual markets did not permit separate publications for each specialisation. In any case it could be argued that there is sufficient overlap in both equipment and services to justify the all-in approach. The retail price of £19.50 should not deter the professional sector but will almost certainly discourage amateur or casual interest. The Pro-Audio Yearbook 1981 is available from specialist bookshops, pro-audio dealers or by mail order from the Special Projects Dept, Link House Magazines (Croydon) Ltd, Link House, Dingwall Avenue, Croydon CR9 2TA. Post and packaging charges are £1.10.

Ron Keeley

System A

Here are a few more cartridges and the recommended input module for the preamplifier. If you have a cartridge that isn't shown here or in the July '81 issue send us an SAE and we'll let you know which module is suitable.

Ortofon VMS 20E	E
Ortofon MC10	C
Stanton 680 EE	E
Entre 1	C
Rega 100	E
Coral MC88	E
Dynavector 10X II	E
Dynavector 20A II	E
NAD 9000	E
Technics EPC 205C	E
Reference Spectre	B
Koetsu	C
Grado FTE + 1	G
Bang & Olufsen MMC20CL	E

Safe Bet

GMTC is a company which has only been operating for a year and has now taken on the sole agency of what they think will be a real winner — a safe with no keys! The GMTC Elsafe has already been featured on Tomorrow's World and Pebble Mill and has full approval from insurance companies like Lloyds of London. The cabinet is fitted with an electronically controlled panel which replaces the conventional keys and it offers one million combinations which can be changed every time the safe is locked. If someone doesn't know the combination and tries to open it, it will automatically cease to function after three attempts. Even if the right combination is then used, it will not open for another 30 minutes. The cabinet can be fastened to the floor with interior bolts and it has emergency batteries in case of power failure. The Elsafe measures 35.6 x 46.5 x 53.6 cm and retails at £450 including VAT. Further information from GMT Company, 15 Newman Street, London W1.

GMTC ELSAFE
(SECURITY CABINET)

Defence Digest

This new regular feature is devoted to defence electronics, its equipment techniques and application. Defence remains one of the largest growth areas in UK industry, with much of the real innovation and investment taking place there.


Defence Digest will thus act as a news (and views) section, containing up-to-date information and explanation of some of the happenings in the different sectors of the defence industry.

Companies with information and articles for these columns are invited to submit them direct to Defence Digest at our editorial address. Indeed, anyone with anything to say on the subject, be it information or opinion, is a potential contributor and should not refrain from putting pen to paper.

Sky Flash For Sweden

The British Aerospace Dynamics Group has taken up an option valued at £11 million to supply a further quantity of Sky Flash air-to-air missiles to FMV (Forsvarets Materielverk), Sweden, to arm the Swedish Air Force's Saab Viggen JA37 all-weather fighter. FMV has also identified options for further quantities of missile. Sky Flash has been successfully integrated with Viggen and to date all firings have been effective. British Aerospace is the prime contractor for Sky Flash.

Major sub-contractors include Marconi Space and Defence Systems for the advanced monopulse radar seeker and EMI Electronics Ltd for the radar proximity fuse. Sky Flash is the most advanced product of its type in production and affords a highly effective capability against modern air threats. It has a proven performance against both subsonic and supersonic targets flying from high, down to very low altitudes. Sky Flash is in service on Royal Air Force Phantom aircraft and will also arm the Tornado F2 Air defence variant. It has also been successfully fired from the General Dynamics F16 fighter.

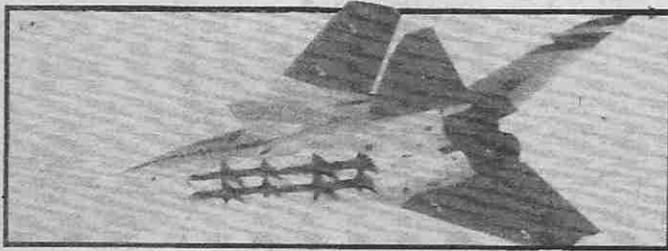


Marconi Success

A series of trials, sponsored by the Royal Navy, has enabled Marconi Radar Systems Ltd to demonstrate the effective use of millimetric radar to further improve the GWS25/Seawolf anti-missile system's performance against low-level targets. The trials were carried out at one of the Royal Navy's firing ranges, and included seven successful 'live' firings of Seawolf against small and large targets close to the sea surface. Using a derivative of the DN181 Blindfire radar, on the same mount as the Seawolf type 910 tracker radar, the trials showed that the tracking of such targets as sea-skimming anti-ship missiles flying a few feet above the surface is considerably improved, therefore ensuring the probability of successful engagement by the Seawolf missile. At present this low-angle tracking is carried out by a television system. Now the DN181 gives an all-weather, round-the-clock capability. The DN181 was developed by Marconi Radar's sister company, Marconi Space and Defence Systems Ltd, and is used with the successful Rapier missile system. Marconi is the overall ship system contractor for GWS25/Seawolf; British Aerospace for the missile, and Vickers for the launcher.

Surveillance System For The Forces

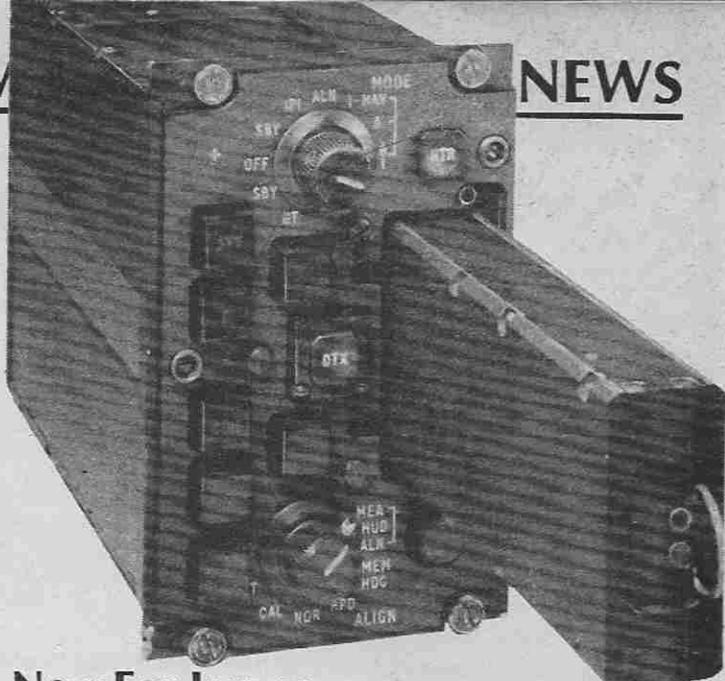A new range of technically advanced radio surveillance and monitoring equipment is available from MCL (Marlborough Communications Ltd) the British telecommunications equipment company specialising in HF frequency management, electronic warfare surveillance systems, and related communications fields. The new



New For Jaguar

The Ferranti FIN 1064 inertial navigation system is to re-equip the RAF Jaguar aircraft. The picture shows the program loading unit in position in the inertial navigation control unit. This program loading unit is first programmed by flight planning staff, and includes the flight program, navigation information for

the sortie, weapon status and any other relevant tactical information. The PLU, which contains a printed circuit board instead of a tape cassette, is then inserted into the control unit by the pilot or ground crew and the data automatically and quickly transferred to the FIN 1064 computer in the aircraft.

Sunburgh Radar For CAA

After a two-year leasing period, the Civil Aviation Authority have purchased outright the Marconi Radar installation at Sunburgh in the Shetlands. The total cost is estimated to be £1/3 million. Marconi Radar Systems Ltd is a GEC Marconi Electronics company. The radar is one of the S600 series of transportable radars and has provided cover support for helicopters and oil-related air traffic serving the offshore oil industry in the North of Scotland. An S1061 L-band (23 cm) squintless feed antenna together with an S2011 transmitter/receiver provide good range performance against small targets such as helicopters and light aircraft, while circular polarisation and the S7100 Digital Signal Processor ensure a crisp, low 'clutter' display in the adverse weather conditions often experienced in the Shetlands. The company said of this latest order, 'the installation was carried out in record time — just five months from receipt of order the system was designed, assembled, containerised, transported to the Shetlands and commissioned ready for service — and in two years of operation we have been able to provide a quick response specialist back-up service so that a reliable operation has been maintained'.

range of equipment called COMINT is for use by all three armed services: Army, Navy and Air Force and can be used in airborne, shipborne, land tactical and in fixed site locations and will be installed as a system by MCL's engineers to suit the user's requirements. The system is designed and developed by SciComm Inc of Garland, Texas, leading specialists in this field, and it will be exclusively supplied by MCL. The Royal Air

Force is currently using SciComm ELINT surveillance systems with MCL providing technical support. The picture shows Phil Derry (right), Marketing Director of MCL, discussing customer requirements for COMINT with Ray Urban May, Vice President Marketing of SciComm Inc who designed and developed the range of equipment.

Dart Gyroscope For Texas

The British Aerospace Dynamics Group Dart gyroscope produced at Stevenage has been selected by Texas Instruments for their Paveway III low-level laser guided bomb. The dart will be part of the digital guidance and control system to increase operational flexibility. The Dart is a miniature two-axis rate gyroscope giving high performance for low weight and size. The Paveway program has gained a reputation for one bomb — one target, and Paveway II has been in high volume production for several years, being the principal weapon of its category in the USAF inventory.


**NEXT
MONTH**

electronics today

INTERNATIONAL

FREE NEXT MONTH 100 CIRCUIT SUPPLEMENT

Yet again ETI brings you more of everything! Next month we're giving away a designer's dream — 100 circuits from the ever-fresh pen of Tim Orr. They will cover all aspects of electronics from audio to digital and will come with full design notes to facilitate their adaptation to your particular requirement. Other magazines make a full issue out of such as this, but not ETI. We're giving them away free with *five* constructional projects — including a superb Music Processor, truly the final word in effects units, an exposé on the GPO plans for 'free' communications, an explanation of FTL travel. . . plus our usual super features and news. Why buy anything else when you *could* have the best?

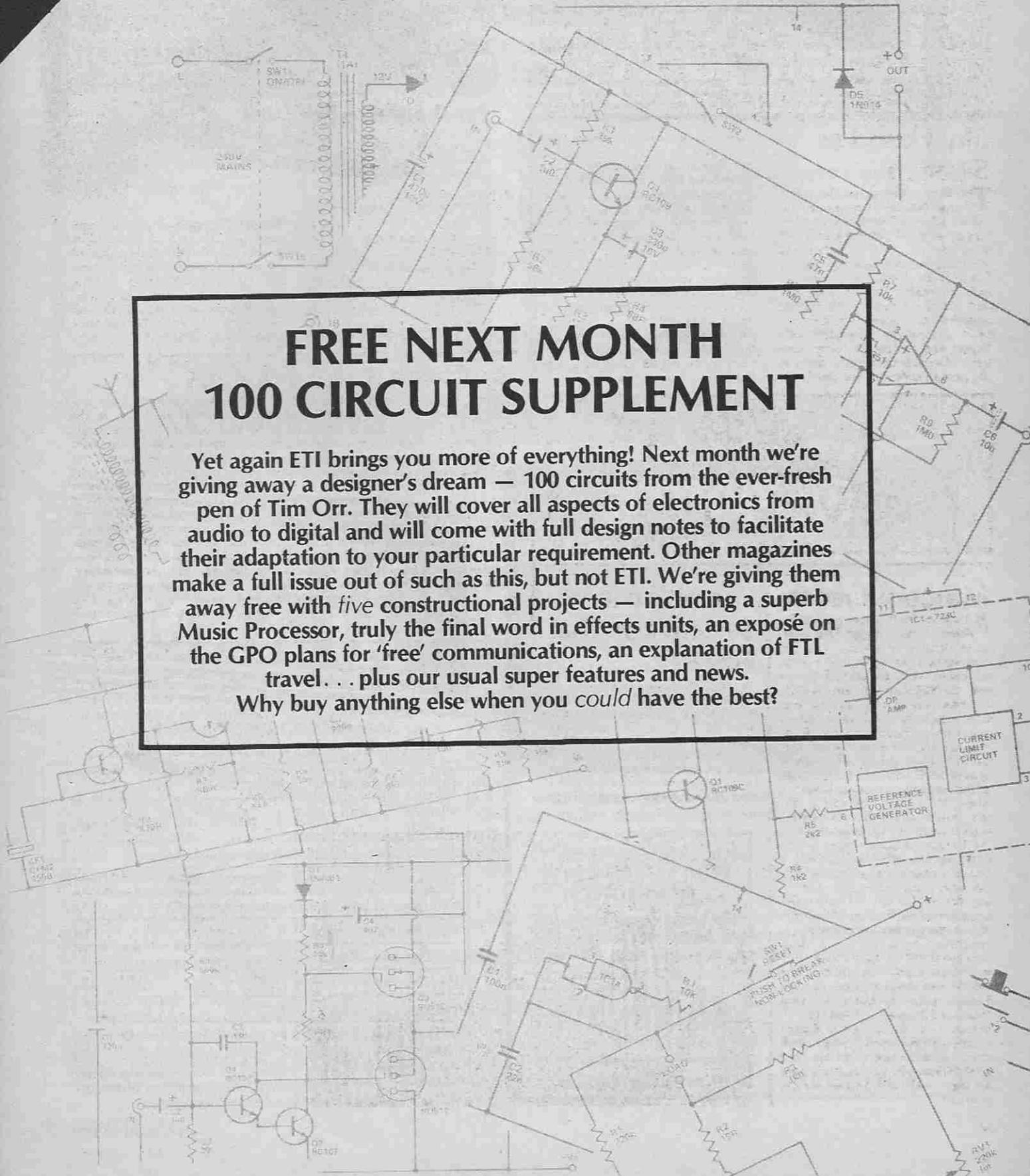

EXCITING OFFERS!

DIGITAL VOLTMETER MODULE

Fully built & tested



ONLY
£11.95
+VAT

- Positive and negative voltages with an FSD of 999mV which is easily extended.
- Requires only single supply 7 - 12V.
- High overall accuracy $\pm 0.1\% + 1$ digit.
- Large bright 0.43" (11mm) LED displays.
- Supplied with full data and applications information.

Using this fully built and calibrated module as a basis now means that you can easily build a wide range of accurate equipment such as multimeters, thermometers, battery indicators, etc. etc. at a fraction of the cost of ready-made equipment. Full details are supplied with each module showing how to easily extend the voltage range and measure current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, universities, the P.O. and many companies.

Temperature Measurement £2.15 +VAT

An easily constructed kit using an I.C. probe providing a linear output of 10mV/°C over the temperature range from -10°C to +100°C. The unit is ideal for use in conjunction with the above DVM module providing an accurate digital thermometer suitable for a wide range of applications.

Power Supply £4.95 +VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V providing current levels of up to 250mA each. The unit is ideally suited for powering the DVM and the Temperature Measurement module.

ULTRASONIC ALARM MODULE

Fully built & tested

ONLY
£10.95
+VAT



Range adjustable from 5' - 25'

A really effective fully built module which contains both ultrasonic transmitter and receiver, together with the necessary circuitry for providing the appropriate delays and false alarm suppression. Using this module with a suitable 12V power supply and relay unit such as that shown, a really effective though inexpensive intruder alarm may be constructed. The module, which is supplied with a comprehensive data sheet, is easily mounted in a wide range of enclosures. A ready drilled case, together with all the necessary hardware, is available below.

Power Supply & Relay Unit £3.95 +VAT

Incorporating a stabilised 12V supply and a s.p.c.o. relay with 3A contacts, this unit is designed to operate in conjunction with the above ultrasonic unit. Fully built and tested, its compact size makes it ideal for constructing the smallest of units.



Hardware Kit £3.95 +VAT

A suitable ready drilled case together with the various mounting pillars, nuts and bolts, and including a mains switch and 2mm sockets designed to house the ultrasonic alarm module, together with its associated power supply. This hardware kit provides an ideal solution for assembling the economical alarm system. Size 153mm x 120mm x 45mm



In addition to the above a wide range of competitively priced electronic components is stocked. Please telephone your specific requirements.


- V.A.T. must be added on all items.
- Shop hours 9 - 5.30 (Weds. 9 - 1)
- ex-stock delivery on all items.
- Units on demonstration, callers welcome.
- Post and packing charge 50p per order.
- S.A.E. with all enquiries please.

RISCOMP LIMITED

Dept.: E.T.I.1
21 Duke Street,
Princes Risborough, Bucks.
Tel: Princes Risborough (084 44) 6326

MEMOTECH

48K MEMORY EXTENSION FOR THE ZX81

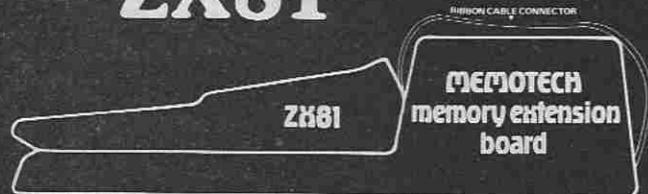

The **MEMOTECH** memory extension board will allow the ZX81 to run 48K Basic programs which may include up to 16K of assembly code.

The **ZX81** sits on a custom built case which contains the **MEMOTECH** memory and a power supply which not only supplies power to the **MEMOTECH** memory, but also to the ZX81.

The **MEMOTECH** memory board has a fully buffered control-data-address bus with PCB 40 way header plug. All leads are provided.

The **MEMOTECH** memory costs:
£109.00 + 15% VAT in kit form. £129.00 + 15% VAT ready assembled. Please make cheques payable to **MEMOTECH**. Delivery in two weeks from receipt of order.

MEMOTECH, 103 Walton Street, Oxford.

INTRUDER ALARMS

BRANDED INTRUDER ALARMS AT DISCOUNT PRICES FOR LIMITED PERIOD ONLY

Alarm with self-contained siren. Keyed and timed entry, using minimal power consumption on stand-by. With circuit fault indicator, 3 reed switches, 1 pressure mat, wire and full installation instructions. **£36.80**

Siren extension unit to increase range **£11.75**

Self-powered siren (sounds if separately attacked) **£25.00**

Self-powered bell (sounds if separately attacked) **£29.00**

Reed switches (surface) **£1.00**

Reed switches (flush) **£0.90**



Pressure Pad — 27" x 15" **£2.20**

Pressure Pad — 22½" x 6¾" **£1.60**

All above prices inclusive of V.A.T. and postage. Terms: Cash with order. Write to Yale Security Products, Wood Street, Willenhall, West Midlands WV13 1LA. Telephone: 0902 66911. Telex: 338251.

LASERS IN HI-FI

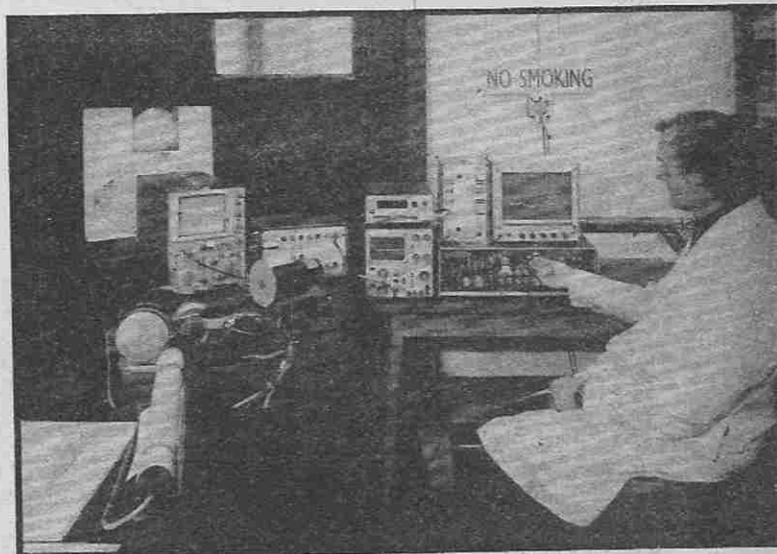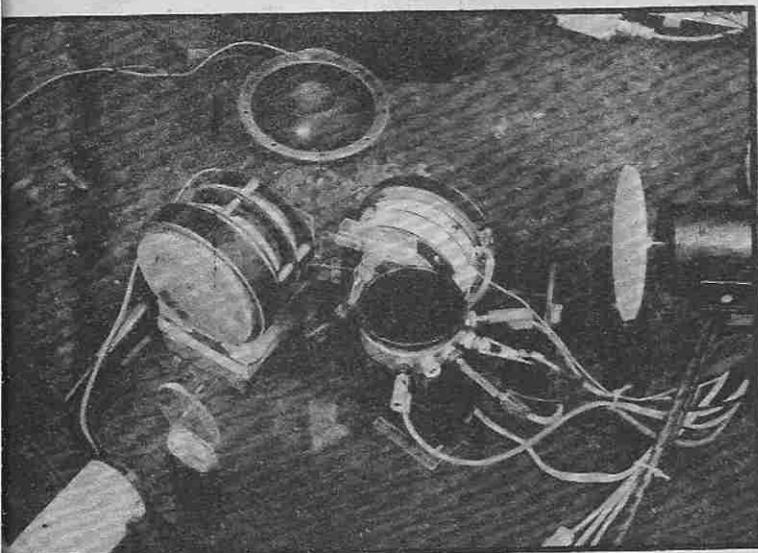Laser technology is making a bid to replace the cartridge in your pickup arm, but it's already been in use for many years at the other end of the hi-fi, helping to develop better speakers. Peter Green takes a look at developments in the Wharfedale labs.



Designing loudspeakers is a complex business. Sound engineers trying to bridge the gap between theory and practice are faced with the tricky problem of investigating exactly how a speaker cone vibrates at frequencies across the audio band and at any point on the surface. Ten years ago the use of laser holography techniques was applied to speaker development by Wharfedale (yes folks, it's British); techniques which provide the design team with a 'contour-line' map of the vibration of a speaker cone.

Typical holograms obtained with this technique are shown in the centre row of Fig. 1. The contours provide a typical guide to the manner and degree of vibration suffered by the cone at the moment the hologram was taken, but although this technique is a good one it has a number of disadvantages. Complicated vibration patterns give intricate contours which require much interpretation; furthermore, there are no helpful little numbers printed on the contours as in an ordinary map so it's not possible to tell whether the vibrations are convex or concave in nature. This makes it difficult to judge what remedy should be applied to counter the resulting sound distortion, so that the analysis becomes an art rather than a science; it also takes time, and in research and development time often means a great deal of money. What is needed is a quick way of producing a three-dimensional view of the actual 'hills' and 'dales' of the terrain, rather than a 2-D map.

To overcome these problems two new laser techniques have been developed by Wharfedale's senior acoustic engineer, Dr Peter Fryer. They are based on the Laser Doppler Velocimeter concept pioneered at the Government's Atomic Energy Research Establishment at Harwell, together with work done at Southampton University. The equipment used was entirely designed and built by Wharfedale for a small fraction of the cost of commercially available (and inferior) sensors, using the excellent engineering rule of never re-inventing the wheel.

The sensing circuit uses an ordinary FM radio set, and when you need a scanning mirror system, what else would a loudspeaker company build it from but loudspeaker voice coils?

Take A SCALP

The basic technique uses a Scanned Laser Probe, or SCALP, and in just 15 minutes it can provide an exact 3-D picture of the vibration of the whole surface of the speaker cone when a single frequency is fed into it. The signal from SCALP corresponds to both the amount and direction of the cone surface vibration at the point of reflection of the laser light, and thus gives a clearer and more accurate representation than holography requiring a minimum of interpretation. Alternatively a Frequency Slice Plot (FRESP) can be made, which shows on one plot the 3-D behaviour of the speaker cone in one plane over the complete range of audio frequencies. Until now this complete vibration-frequency signature has been impossible to obtain.

The SCALP process is basically quite simple and is shown diagrammatically in Fig. 3. Laser light passes through a beam splitter and emerges as two equally bright beams travelling at right angles to one another. One of these, the reference beam, falls onto a rapidly rotating disc whose speed is such that the frequency of the reflected laser light is Doppler-shifted by 10.7 MHz — the intermediate frequency of the IF strip inside an FM radio. The other beam (the sensing beam) is reflected from two mirrors and then onto the speaker under test. The two reflected beams, reference and sensing, return back along their original paths and meet again at the beam splitter. Half of each of them is sent into a new beam which falls onto a photocell.

This output beam is composed of light-half of which is at the original frequency and half of which has been frequency-shifted by the disc. The two components beat together at the photocell and produce a steady 10.7 MHz electrical signal

which is fed into the appropriate part of an FM radio just as if it had been picked up by a radio aerial. With no audio signal being fed to the test speaker the FM radio will output a steady DC level, showing the speaker to be stationary.


Light . . . Music . . . Action

Suppose now that a single frequency is fed to the speaker. During the first part of the vibration cycle the speaker is moving




forwards — the reflected laser light is shifted upwards in frequency by an amount that depends on the velocity of the cone. Thus the beat frequency at the photocell is altered and the FM radio output increases by a corresponding amount. When the speaker is moving away from the beam splitter the frequency of the sensing beam is reduced and so the radio output drops. Thus the output of the radio indicates both the amount and the direction of the speaker cone movement — phase information that the hologram would have lost has been preserved.

BAD

Fig. 1 Laser studies of loudspeakers.

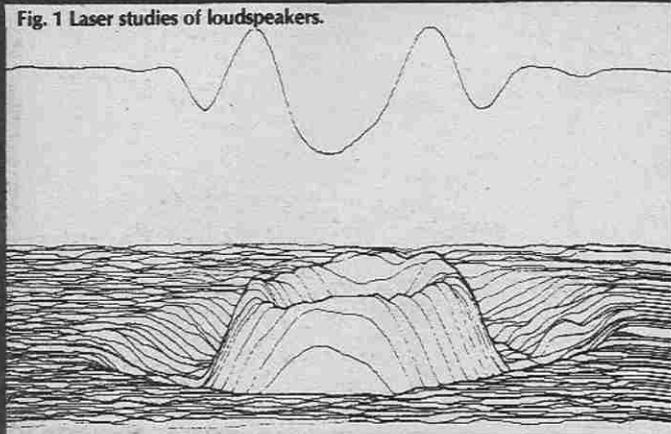

NOT SO BAD

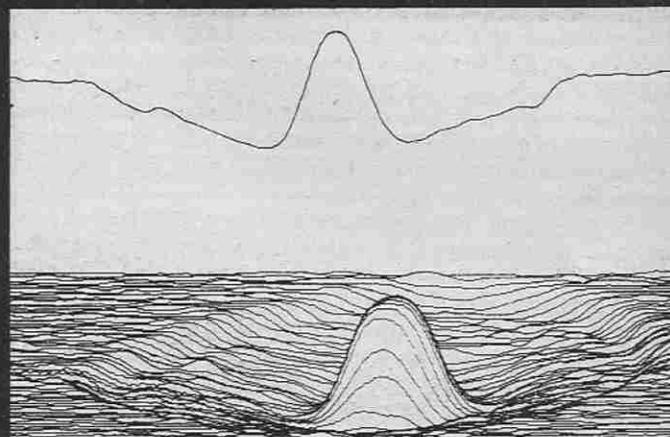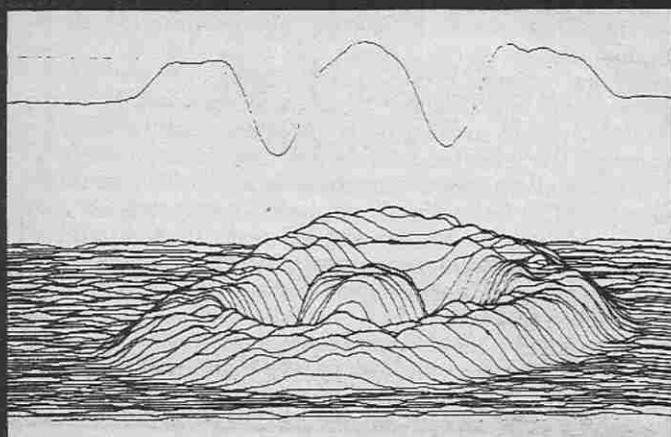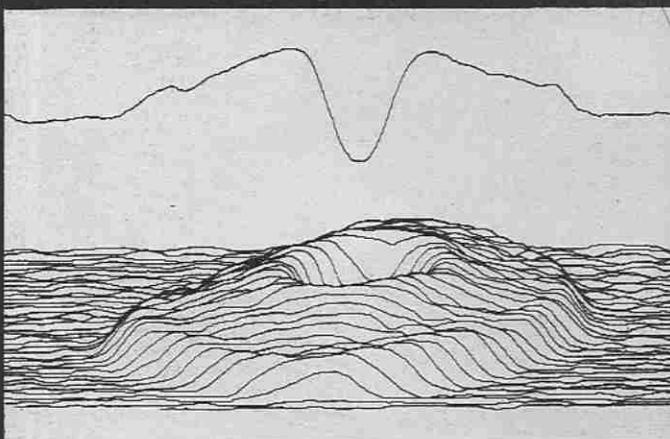







The two mirrors in the path of the sensing beam are attached to loudspeaker voice coils. One of these is connected to the voltage from the 3-D plotter which scans the X-Y plotter across the page, the other to the voltage which scans up the page. Hence the sensing beam is scanned across the cone and at any point on the plot the movement of a corresponding point on the speaker is preserved in the form of a 3-D plot of the speaker vibration. Typical results of laser plotting are shown in the top row of Fig. 1.

FRESP — Son Of SCALP

FRESP is similar to SCALP, but in this case the vertical scanning mechanism is turned off. Thus each curve plotted is of the same horizontal slice across the middle of the loudspeaker. Instead of moving the laser beam by a small amount vertically for each separate trace, the frequency being fed to the speaker is changed between traces starting at the highest frequency and moving down in small steps to the lowest frequency.

BETTER

OK

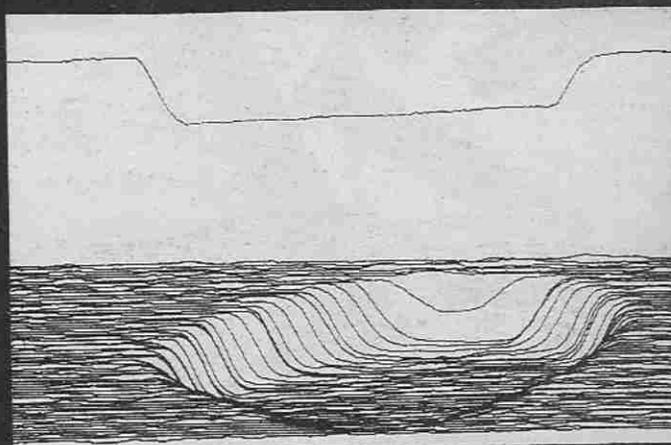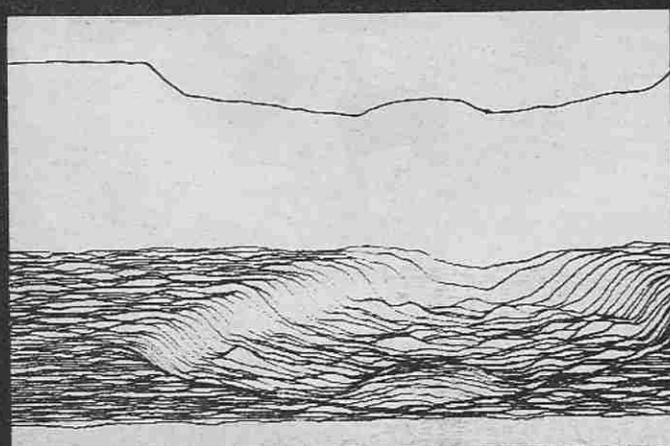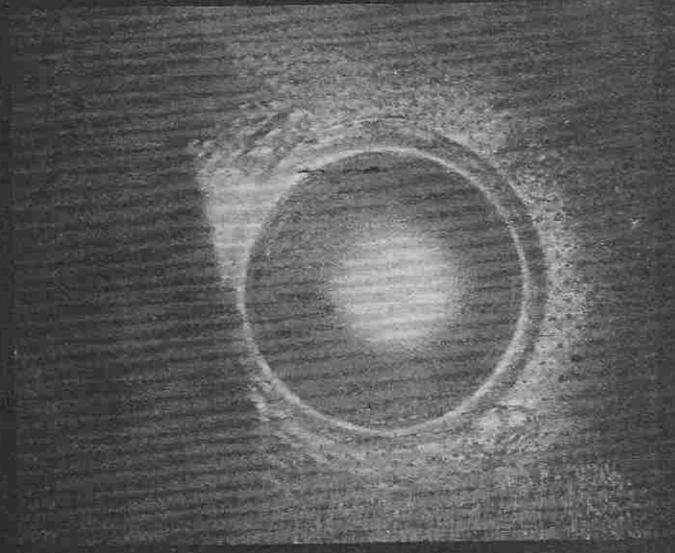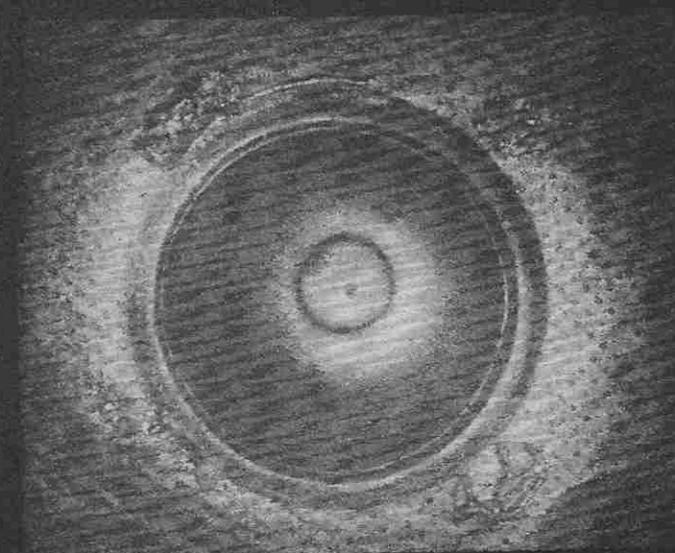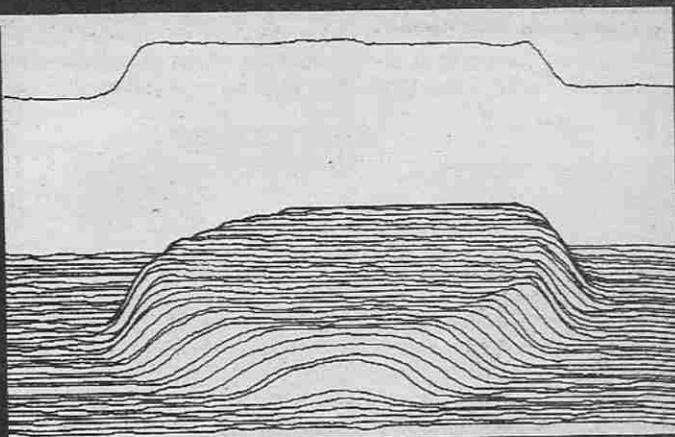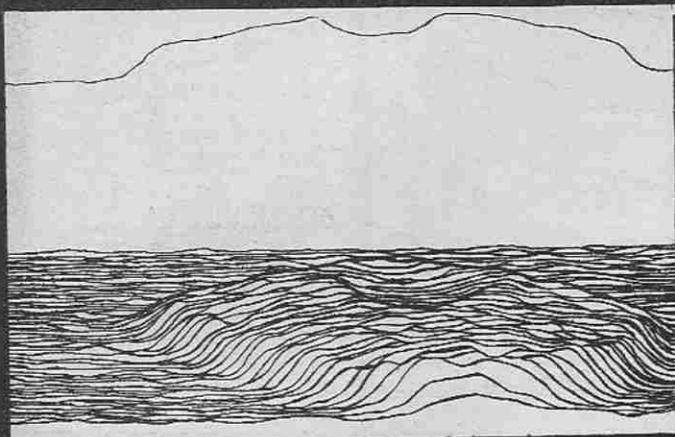

This results in a plot having the same width from top to bottom (the width of the central slice through the speaker) instead of the circular representation of SCALP. Each separate curve now represents the behaviour of this slice at a different frequency. FRESF gives a complete resonant history of vibration of the cone slice between any two frequency limits, the curves being plotted in 3-D and with added horizontal and vertical perspective to aid visibility.

The Plot Thickens

FRESF may also be plotted in a different manner; instead of each curve being a slice across the middle of the speaker for a single frequency, the axes are both turned through 90°. Each curve is then a complete frequency sweep at a single point on a line across the middle of the speaker; each curve represents the behaviour of the cone at all frequencies, albeit at slightly different points across the width. This change in vision angle can

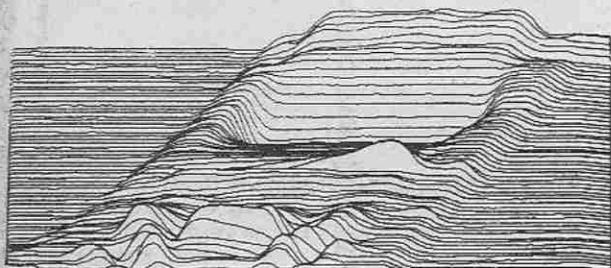


Fig. 2 This FRESF plot pinpoints regions which may benefit from a more detailed SCALP analysis. For example, the odd hump at about 500 Hz is probably worth investigating.

often allow faults to be more clearly seen which could have been hidden behind other features in the normal FRESF.

Furthermore, both FRESF and SCALP can easily be drawn with the phase of the display changed. Peaks in the original display become troughs and vice versa, especially useful where the true depth of very deep 'holes' are masked by the 'foreground' of the plot, as in the 'BAD' example of Fig. 1. The out-of-phase plots along the bottom of Fig. 1 show how this reversal makes holes into peaks and allows their true 'depth' in relation to the rest of the curve to be judged. A powerful tool, then, and one which will keep Wharfedale at the forefront of loudspeaker design.

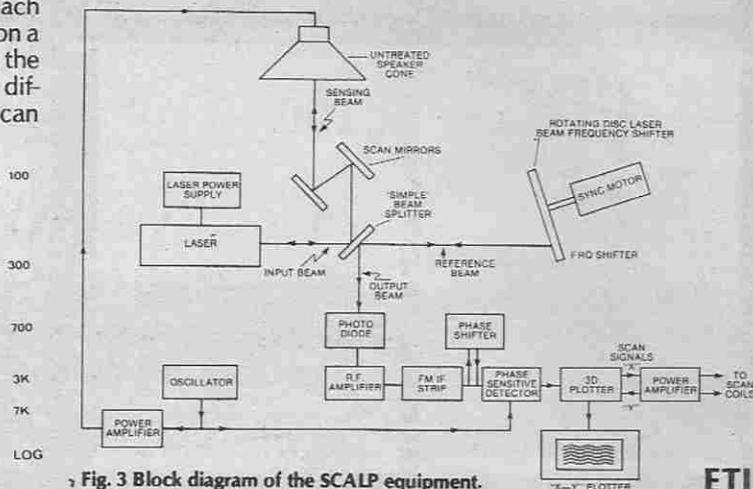


Fig. 3 Block diagram of the SCALP equipment.

ETI

Elliott Electronics Ltd.,
Leicester 0533-553293

F. Blakley & Sons Ltd.,
Heywood 0706-65087

F.P. Tools Ltd.,
Motherwell 069-65672

Horizon Electronics Ltd.,
Glastonbury 0458-33600

Ibis Electronics Ltd.,
Wokingham 0734-791171


Batvale Marketing Ltd.,
Ely 0353-778320
Ely 0353-778756
(24 hours)

For
your
FREE
Catalogue
Send 30p to cover P&P

NEW DISTRIBUTORS WANTED

Quality Two Part DIN 41612
& Min 'D' Connectors.

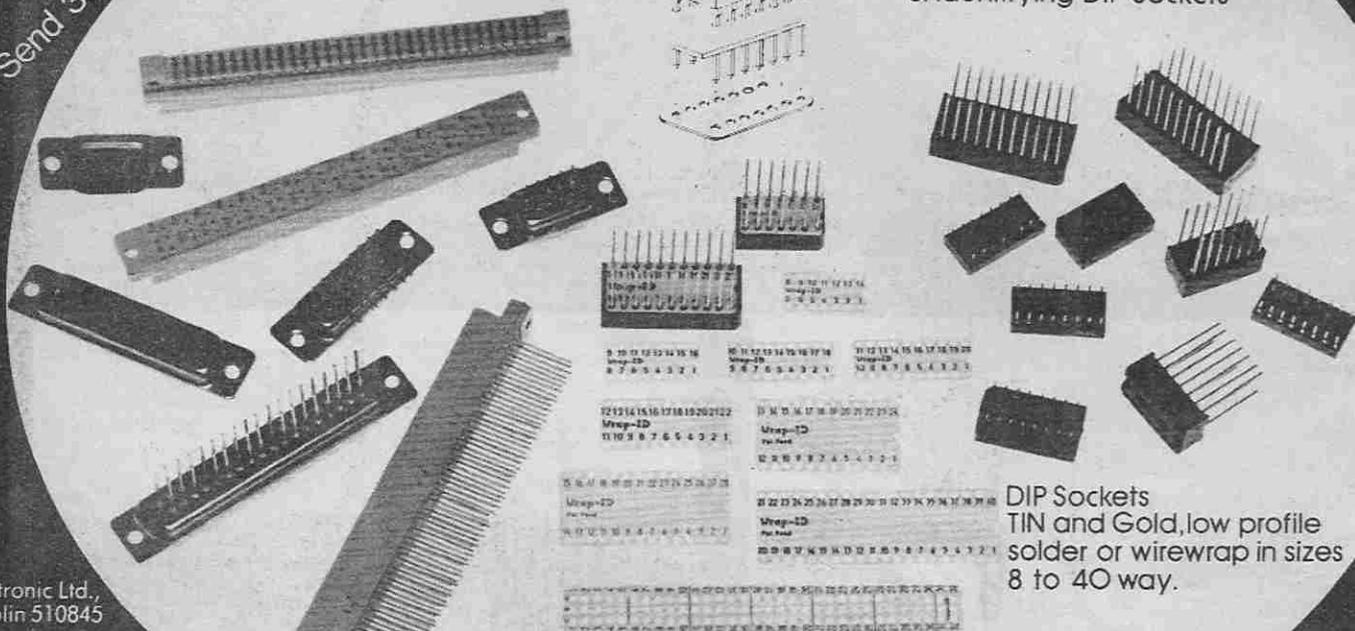Wrap ID Eliminate Errors
for instant locking-numbering
& identifying DIP Sockets



DIP Sockets
TIN and Gold, low profile
solder or wirewrap in sizes
8 to 40 way.

Neltronic Ltd.,
Dublin 510845

Cobbies Ltd.,
London. 01-699-2282

Microdigital Ltd.,
Liverpool. 051-227-2535

Electronica CG Ltd.,
Manchester. 061-788-0656

Spectron Electronics (Manchester) Ltd.,
Salford. 061-834-4583

Jee Distribution Ltd.,
Middlesex. 01-897-3429

Watford Electronics Ltd.,
Watford. 0923-37774

Technomatic Ltd.,
London. 01-452-1500

Transam,
London. 01 405 5240
A. Marshall (London) Ltd.,
London. 01-624-0805

Interface Components Ltd.,
Amersham. 02403-22307
New Bear Computing Store Ltd.,
Newbury. 0635-30505

ELECTROWARE*

DUTTON LANE EASTLEIGH SO5 4AA TEL(0703)610944/5

AVAILABLE FROM ALL LEADING ELECTRONIC DISTRIBUTORS

BI-PAK BARGAINS

"IRRESISTIBLE RESISTOR BARGAINS"

Pak No.	Qty.	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/2 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.
*Quantities approximate, count by weight.

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty.	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 22pf-390pf	£1
SX19	100	Mixed Ceramics 470pf-.047uf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-100mfd.	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240°, Inline 3-6 Pin, Speakers, Phono Jack, Stereo and Mono, etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

SX26	3 Pks.	of 6 pin 240° DIN Plugs and Chassis Sockets	50p
SX27	1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket.	30p	
SX28	4 Phono plugs and 2 dual phono connectors.	30p	
SX29	1 x 2.5mm Plug to 3.5mm Socket adaptor.	20p	
SX30	1 x 3.5mm Plug to 2.5mm Socket adaptor.	20p	
SX31	1 x 3.5mm Plug to Phono Socket adaptor	20p	



SX32	1 x Standard Jack Plug to Phono Socket adaptor.	25p
SX33	1 x Toggle Switch SPST Miniature. 125v 10A	40p
SX34	1 x Toggle Switch SPDT Miniature. 125v 10A	40p
SX35	1 x Rocker Switch SPDT Miniature. 240v 5A	40p
SX36	1 x Right Angle Mono Jack Plug	15p
SX37	20 pieces. 1.2 & 4mm-plugs and sockets (Banana). Matching colours and sizes.	£1
SX50	10 Assorted Switches: Toggle, Slide, Rocker, Push button.	£1

Guarantee

Satisfaction or your money back has always been BI-PAK's GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received.

SX40	250 Silicon Diodes—Switching like IN4148 DO-35. All good—uncoded. Worth double our price. 45v 75mA.	£1.25
SX41	250 Silicon Diodes—General Purpose. Like OA200/202, BAK13/16. Uncoded. 30-100v 200mA, DO-7.	£1.25

SX44	10 5A SCR's T064. 3 x 50v. 3 x 100v. 2 x 200v. 2 x 400v. Super value less than 1/2 price.	£2
SX45	10 5A SCR's T066. 2 x 50v. 2 x 100v. 4 x 200v. 2 x 400v. All coded. Brand new. a giveaway at	£2



SEMICONDUCTORS FROM AROUND THE WORLD

100 A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices.

Guaranteed Value over £10 at Normal Retail Price



£4.00 yours for only Data etc. in every pak. Order No. SX56

BI-PAK'S OPTO BARGAIN OF THE YEAR!

Valued at over £10—Normal Retail—we offer you a pak of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow and Clear. 7 Segment Displays both Common Cathode and Common Anode PLUS bubble type displays—like DL-33. Photo Transistors—similar to QCP71 Photo Detectors—like MEL11-12. This whole pak of 25 devices will cost you just

£4.00 AND we guarantee your money back if you are not completely satisfied. FULL data etc included. Order No. SX57.

MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours.	£1
SX58	25 Assorted TTL Gates 7400 Series. 7401-7460.	£1
SX59	10 Assorted Flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX61	25 Assorted Potentiometers, Rotary, Dual, etc.	£1
SX62	40 Assorted Pre-Sets Hor/Vert etc.	£1

STILL MORE!

SLIDER POTENTIOMETERS

SX63	5 x 470 ohms Lin	SX67	5 x 47k Lin
SX64	5 x 1k Lin	SX68	5 x 47k Log
SX65	5 x 22k Lin	SX69	5 x 100k Lin
SX66	5 x 22k Log	SX70	5 x 1 meg Lin

All at 50p per pak.
SX71 50 BC108 "Fallouts". Manufacturers out of spec on valts or gain. You test.
SX72 A mixed bundle of Copper clad Board, Fibre glass and paper. Single and double sided. A fantastic bargain. £1

BARGAINS

SX42	20 small .125 Red LED's	£1
SX43	10 Rectangular Green LED's. 2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages all coded. New.	£1
SX47	4 Black Instrument Knobs—winged with pointer 1.1" Standard screw. Fit size 29 x 20mm.	50p
SX48	5 Chrome knobs standard push fit. 15mm	50p
SX49	20 Assorted Slider Knobs. Black/Chrome, etc.	£1

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back up diagrams with each module.

Specification:
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 kHz—3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%
BI-PAK'S giveaway price

£2.25 each

You could not Build one for this price.

BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a BI-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send 75p plus 25p p&p.

£1 FREE PAK

Get a £1 FREE PAK. Orders over £10 excluding VAT. Choose £1 Pak free (or 2 x 50p) add it to your order and save even more money. This offer only applies to this advertisement.

This offer only applies to this advertisement

IC SOCKETS

The lowest price ever.

The more you buy the cheaper they come!

Pin	10 off	50 off	100 off
8	75p	£3.00	£5
14	80p	£3.25	£5.50
16	80p	£3.25	£5.50
16°	80p	£3.25	£5.50

Quilled



SX52	6 Black Heatsink will fit TO-3 and TO-220. Ready drilled. Half price value	£1
------	--	----

SX53	1 Power finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design. pre drilled. TO-3 Size 45mm square x 20mm high.	40p
------	---	-----

SX54	TO-66 size. 35mm x 30mm x 12mm.	35p
------	---------------------------------	-----

SX55	1 Heat Efficiency Power Finned Heatsink. 90mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices	£1.50 each
------	--	------------

SX38	100 Silicon NPN Transistors—all perfect. Coded mixed types with data and eqvt. sheet. No rejects. Real value	£2.50
------	--	-------

SX39	100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt. sheet. No rejects. Fantastic value	£2.50
------	---	-------

MULLARD. AS2 17 PNP.	Germ TO-3 Power Trans.	60 VCB 8A	32 VCE 30W	20 VEB H/c 30min	Pass Replacement for AD130/131/140/149 OC25/26/28/35 2N3613/14/17/2N1533
----------------------	------------------------	-----------	------------	------------------	--

Great Value at 65p each or 2 for £1.




BI-PAK

Send your orders to Dept ET10, BI-PAK PO BOX 6 WARE HERTS. SHOP AT 3 BALDOCK ST WARE HERTS. TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS. BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GYRO 388 7006 ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



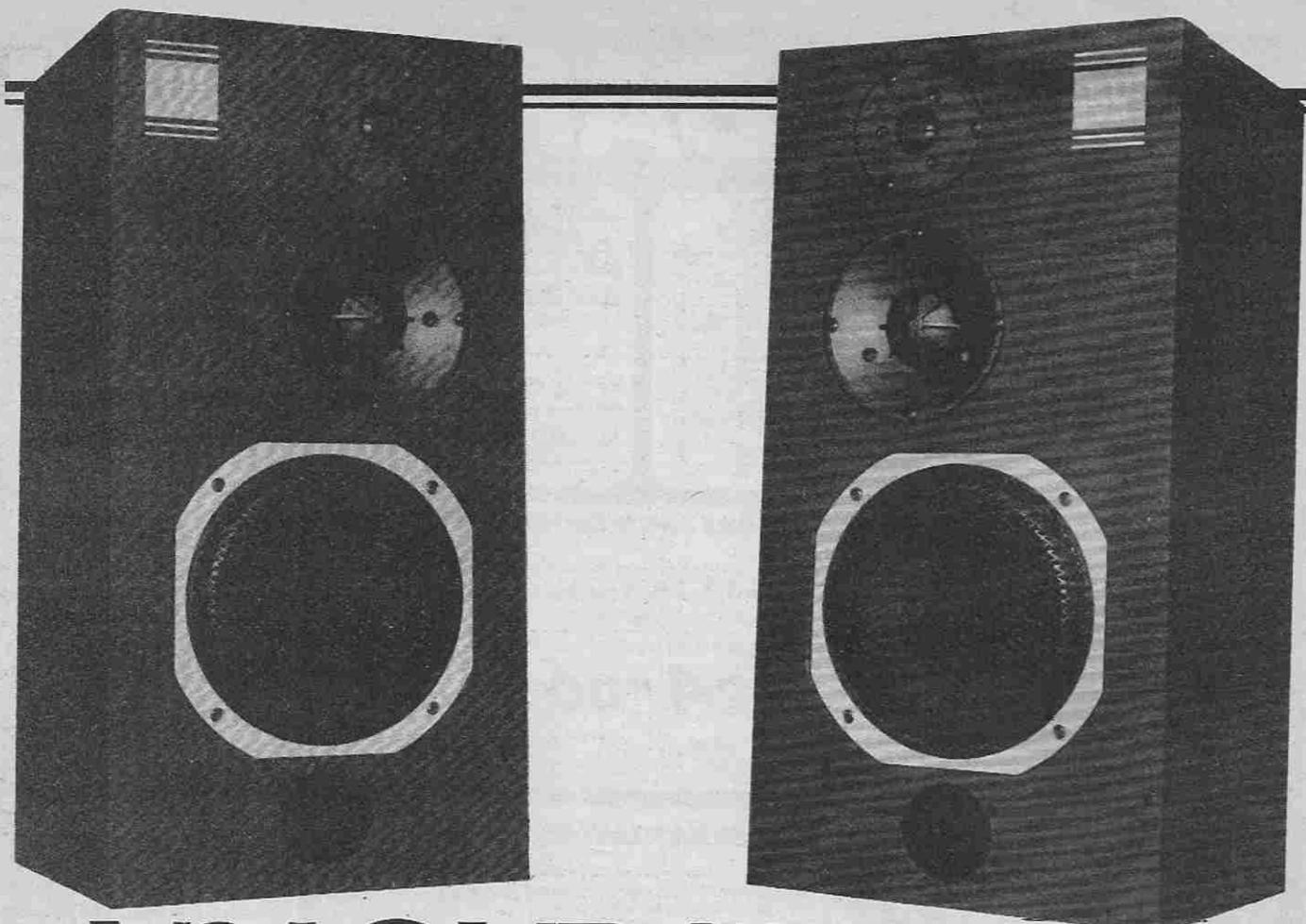Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total. Postage add 50p per Total order



V3 LOUDSPEAKER

As always, ETI delivers the best in DIY hi-fi. These high quality, high power speakers will make your music sound good and your living room look good. Design and development by David Lyth.

The V3 loudspeaker system is a three unit design using a Volt 8" bass driver and a Philips dome midrange and tweeter; crossover points are 700 Hz and 5 kHz. A reflex enclosure is employed, constructed from 19 mm high-density chipboard with the units mounted in a mirror image configuration. A grille baffle is not necessary for other than aesthetic reasons because the driver units incorporate either a grille or similar structure protecting the 'software'. However, extensive research has revealed that small fingers can get at the midrange dome which will result in a recessive sound balance. Beware!

The V3 is a medium efficiency system with a wide frequency response and is capable of high power handling, especially in the bass. Distortion and colouration are very low and the smooth response gives good tolerance of aggressive or edgy material.

The cabinet uses high-density chipboard 19 mm thick and is simple to construct, with panels coming economically from standard sheet

sizes. All the drive units are rebated and some care is necessary to get a good fit, although plywood could be used for the front panel to make this task easier.

Reflex Action

Reflex enclosures have been the subject of much controversy in the past because some designs work well and some are appallingly bad. The problem lies in the design itself and the approach taken here is to use tables generated by A. N. Thiele, an Australian. Thiele likened the combination of bass unit and enclosure to an electrical filter and used synthesis techniques from this field to build up tables enabling the designer to choose a cabinet to suit a particular drive unit. Knowledge of various drive unit parameters is necessary — for example, Q_T , V_{AS} , F_S . The system response options are those shown by Butterworth or Chebyshev high pass filters — Fig. 3 shows some characteristics.

However, the Thiele alignments are not the final solution to the design problem. The responses available (with the exception of the QB3) are flat down to the -2 dB point (give or take a ripple) and a correctly aligned system would show this response under free field or anechoic conditions. But who sits around listening to ideal electrical filters hanging 30 m above a field? Your private life is none of my concern, but I have found that when a pair of loudspeakers are listened to in an average sized room the bass response can sound unbalanced. This is because they are not 'looking' into omnidirectional space but seeing rather less than this depending on the wavelength of the sound reproduced and system-room positioning. There is a dramatic difference between the bass response of a system held in the middle of a room and that when placed in a corner. This is similar to the variation when going from true free field conditions to a listening room, and it is necessary to modify the 'correct' response to compensate for the bass

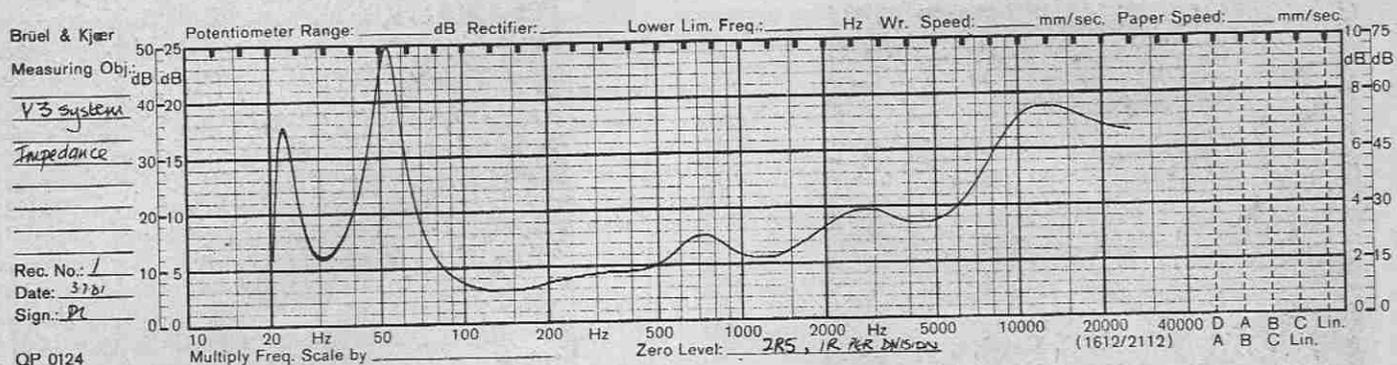


Fig. 1 Impedance curve for the V3 Loudspeaker.

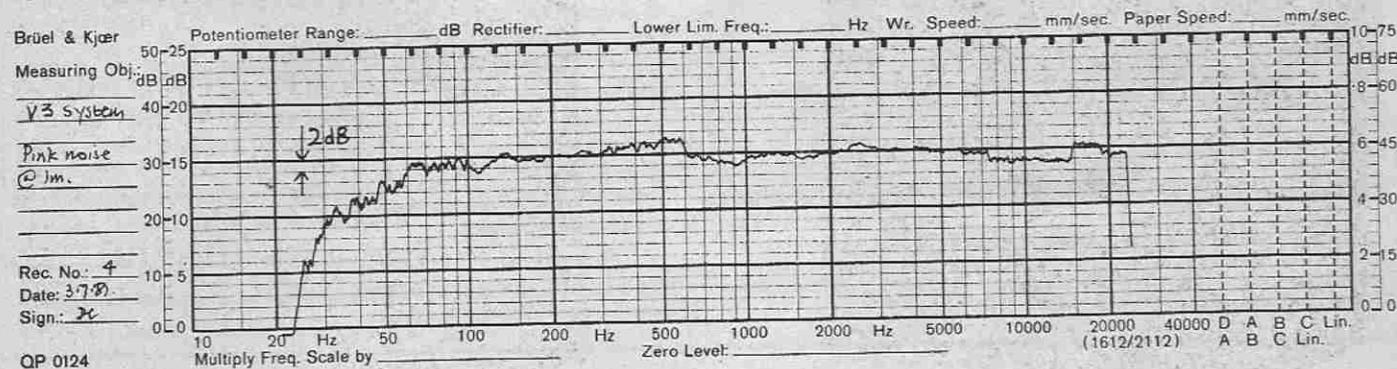


Fig. 2 Frequency response of the V3.

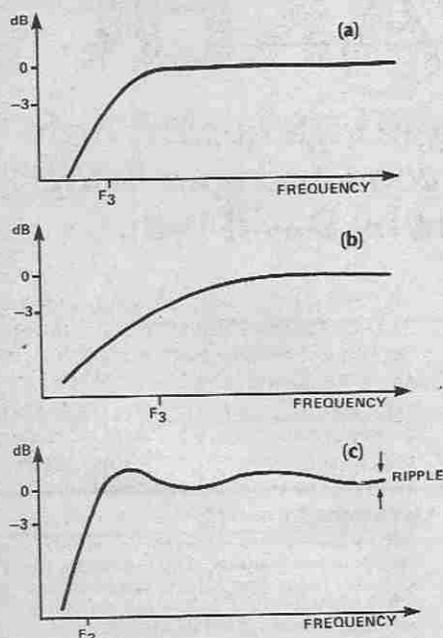


Fig. 3 Butterworth B4 response (a); Quasi-Butterworth response (b); Chebyshev C4 response (c).

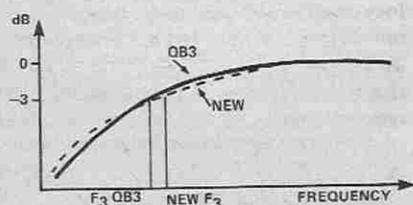


Fig. 4 The response of the V3 speaker compared to the Thiele QB3, showing the improvement in the bass.

boost provided by the room so that very deep bass is maintained but overemphasis of middle and upper bass is avoided.

This means that we want a flat response in the room and not in free field conditions. The Thiele alignment that most closely approaches our desired free field response is the QB3. Initial work showed that a fairly small cabinet (volume about 29 litres) produced good results but there was still an overemphasis of middle bass in an average sized room. Enlarging the cabinet by 30% and reducing the reflex tuning frequency to 30 Hz gave a dramatic improvement, the bass output sounding even and with an excellent lower octave. In a way the obvious has occurred ie "a good big 'un will always beat a good little 'un". Excellent transient response is maintained and this is fundamentally due to the large magnet fitted to the B220 bass unit. Nevertheless the Thiele approach was an excellent starting point for the design. Figure 4 shows the effective improvement in the bass response. The system was always used on stands 250 mm high with free space underneath, placed with its back against a wall and kept out of corners.


Middle And Upper Class

A midrange dome was selected

because domes have a fundamental advantage over coned units of the same size — their break up modes occur at higher frequencies. As the alternative to a 50 mm dome would have been a 75 mm cone unit, this means that the dome will operate with more diaphragm control to a rather higher frequency. The tweeter has a soft dome as opposed to the midrange's pulp dome, and incorporates a diffuser.

The midrange and tweeter have very smooth responses with low colouration and distortion. These two units are offset from the centre of the cabinet so that the pair are mirror imaged on the two speakers. This improves stereo imaging, mainly by reducing edge diffraction which is a major cause of poor stereo.

The worst case for diffraction is when the tweeter, for example, is mounted equidistant from the three nearest cabinet edges. Re-radiation will then take place at the same frequency for each edge and this will cause a discontinuity in the frequency response. By offsetting the unit the diffraction is smeared and reduced to insignificant levels. Elimination of the grille also helps because there is no grille baffle standing proud of the cabinet to present an obstacle to the surface sound wave, thus worsening diffraction. The only real argument for a grille is aesthetic and then a foam grille is the best solution.

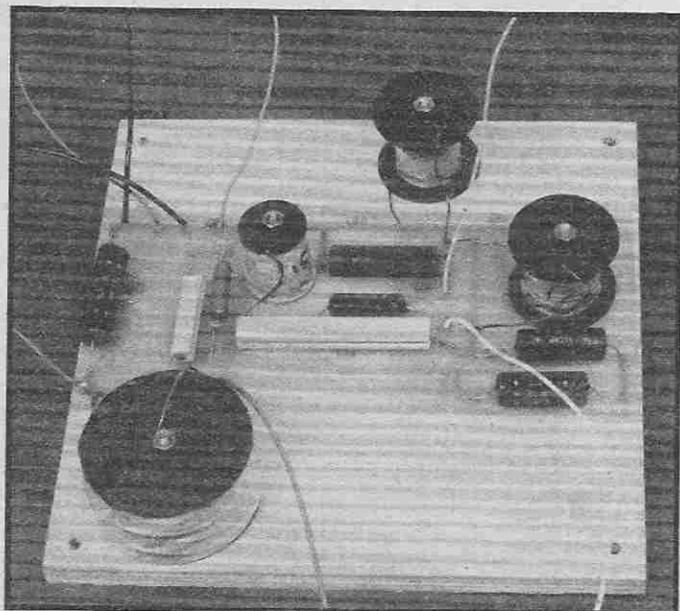

After the components have been soldered to the PCB, the crossover board is secured to a plywood panel using the choke fixing bolts. To get the choke connecting leads the right length, you'll have to cut access holes beneath the PCB pads so you can solder the wires last.

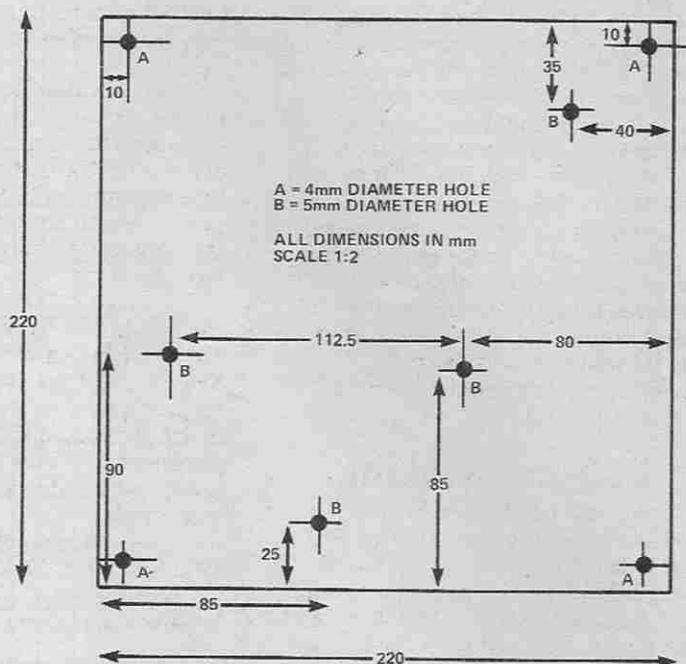


Fig. 5 This diagram shows the drilling positions for the choke and mounting screwholes on the crossover panel.

The Crossover

This uses air cored chokes exclusively because these have a better ability to pass transients than ferrite cored chokes, which can momentarily saturate on high power peaks. The chokes are well spaced to prevent any flux linkage between them. There are two 40uF capacitors feeding the midrange so that their combined voltage rating is great enough to prevent possible failure under high power drive.

The crossover is constructed on a PCB which is attached to a wooden crossover board by clamping it beneath the chokes which are bolted through with brass screws. The wire used should have a 6 A rating.

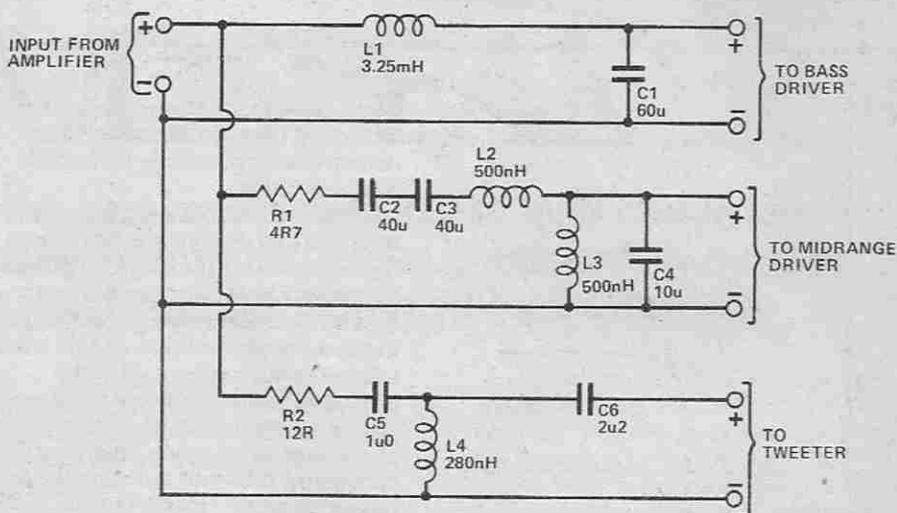


Fig. 6 Circuit diagram of the crossover.

Listening Tests

During the design of the V3 there were constant trips made between listening rooms and the test equipment in order to make modifications to the crossover or cabinet. Comparisons were made with the Yamaha NS1000M, Gale GS401A, KEF 105 II and Popular Hi-fi Boxers: each of these systems had particular strong points and it was a design aim to approach the low colouration and discrimination of these designs. Listening was done with material ranging from choral works through to heavy rock. The cabinets were set so that the dome units were on the inside of the pair. A front grille was never used and connection was by screened twin lead with the screen connected to the inner core, thus

HOW IT WORKS

The crossover uses second order filters throughout, except for the high pass tweeter section which is third order. The values diverge from those of the text book because the load presented by the drivers is not a constant resistance. Apart from the impedance rise at resonance for the midrange, all units exhibit a rising impedance characteristic over their possible operational range because of the voice coil inductance. This is compensated for in the low pass section feeding the bass driver by using a larger shunt capacitor than calculations show.

The band pass filter used for the midrange also includes a little response shaping in its function. The midrange unit has an impedance rise at its resonant frequency (which lies one octave below the crossover point) and to control this the shunt choke of 0.5mH is appreciably

smaller than calculated. This is because the normally rising impedance characteristic of a high pass filter below the crossover point prevents amplifier damping from controlling a resonance in this area — this is the case with the Philips unit. By using the lowest possible value choke next to the unit that did not upset frequency response or drop overall system impedance it is possible to give the unit a degree of damping by simulating a low impedance drive around resonance. The net result is better control and increased power handling. This consideration dictated the choice of the lower crossover point.

The upper crossover point is chosen to match the radiation characteristics of the units as closely as possible and to provide the best integration. The tweeter is also attenuated to match levels.

making twin flex. If there is a magic in speaker cables, apart from common sense, then the greater surface area of the screen should reduce skin effect, the only thing that would have a deleterious effect on the electrical transmission — 13 A twin cable would probably do just as well, however.

Ancillary equipment tried varied from moving coil cartridges to moving magnets with either valve or a high-powered transistor amplifier. The end result justifies the time and effort and the V3 stands very favourable comparison with systems costing £400 upwards per pair.

Cabinet Making


You will need the following: 24 + 1½" x No. 8 self-tapping screws and screw sink No. 8 — 1" long; flexible Plastic Padding, sandpapers, electric drill, jig saw, chisels, 7/32" drill bit, and wood glue. Butt joints are used throughout — providing reasonable care is taken this will provide a satisfactory cabinet. Rebates or internal battens are only necessary where high strength is required, which is not the case with a domestic system.

Internal battens, or a least small blocks, may be useful in helping to locate the side panels.

An important consideration when cutting the panels is to allow the edge of a panel to stand slightly proud (0.5 mm) of the mating panel surface when assembled so that the step produced can be sanded back — at the very least this should be tolerated for.

When it comes to rebating the unit the best plan is to cut the basic mounting hole and rest a unit in this. Draw round the outside edge and rebate to suit the flange thickness — it is not necessary to allow for any gasket thickness. It is more pleasing to the eye if the unit stands slightly proud rather than sub-flush.

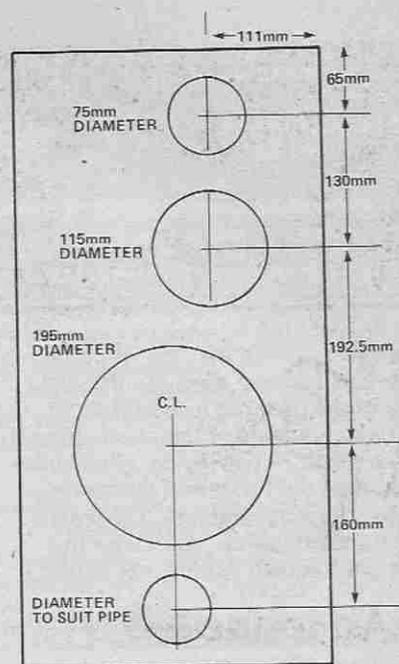The midrange and tweeter are secured by No. 6 x 19 mm pan head self-tapping screws. The bass unit is heavier and requires 2BA x 1" screws



FRONT PANEL (RHS SPEAKER) SHOWING BASIC CUTOUTS FOR UNITS.

PLASTIC PIPE IS 95mm INTERNAL DIAMETER AND 180mm LONG.

CUTOUT ON REAR PANEL FOR TERMINALS IS 30mm x 12mm.

BAF SIZE IS 1 SQUARE METER x 25mm THICK.

SCREWS SHOULD NOT BE MORE THAN 150mm APART.

Fig. 8 Template for the front baffle. The dimensions are important, so cut carefully!

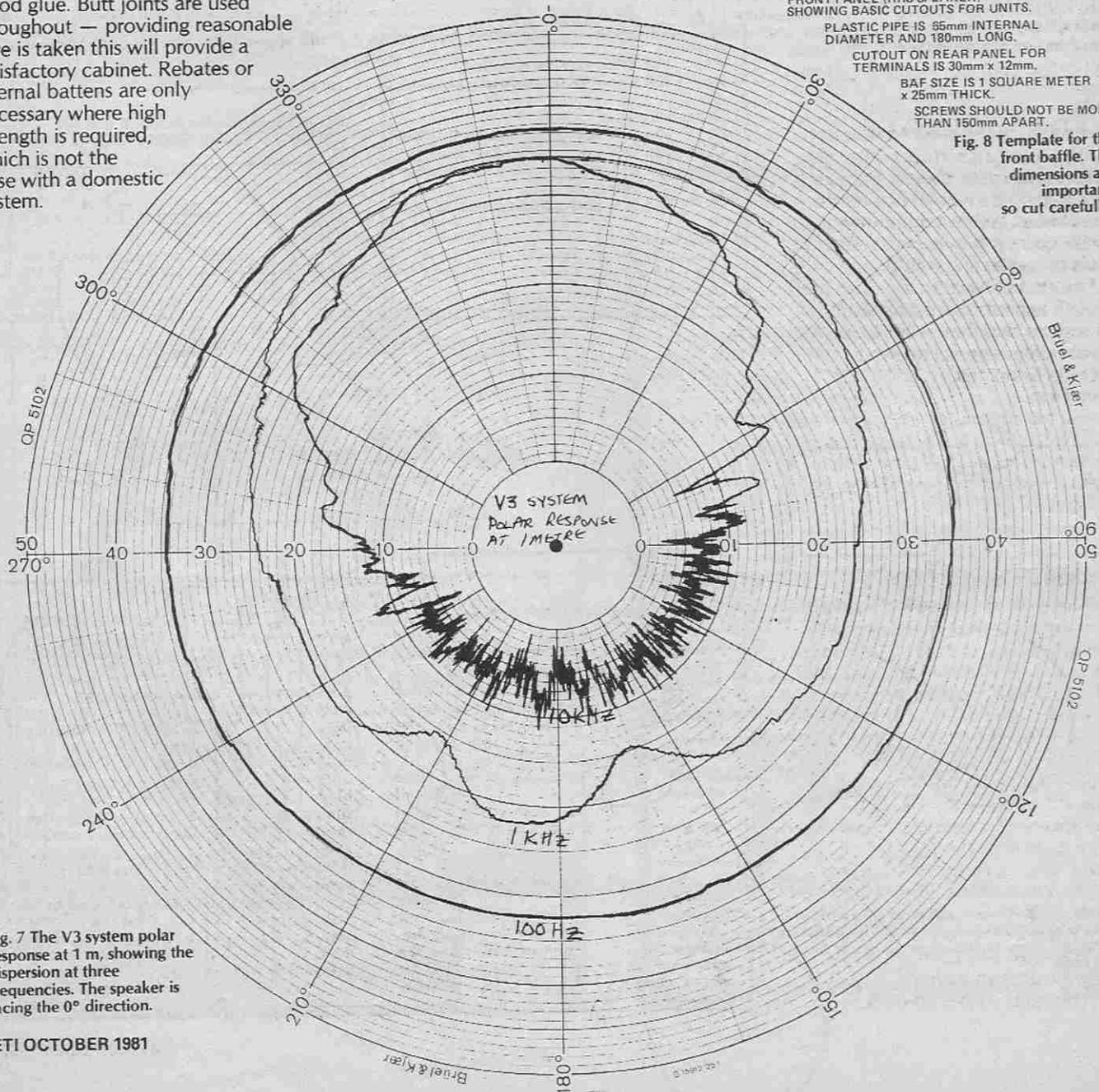


Fig. 7 The V3 system polar response at 1m, showing the dispersion at three frequencies. The speaker is facing the 0° direction.

TECHNICAL SPECIFICATION

Frequency Range	30 - 20,000 Hz
Frequency Response	60 - 20,000 Hz \pm 3 dB
Impedance	8R
Amplifier Requirement	25 W - 150 W
Efficiency	1 W for 82 dB at 1 m
Reflex Tuning	30 Hz
Crossover Frequencies	700 Hz and 5 kHz
Size	600 mm x 300 mm x 300 mm

WOOD CUTTING LIST

2 off 600 mm x 300 mm for front and back
 2 off 262 mm x 300 mm for top and bottom
 2 off 262 mm x 562 mm for sides
 1 off 220 mm x 220 mm for crossover board
 All panels are 19 mm high-density chipboard except for the crossover board, which is 12 mm plywood.

with T-nuts — use the 7/32" drill for these and hammer the T-nut into the back of the panel so it seats flat.

The mounting of the plastic tube is easy enough — you simply glue it into the hole at the bottom of the baffle, leaving the inner end free. The length of this pipe is critical, as it tunes the resonant frequency of the enclosure.

An Inside Job

The electrical assembly is straightforward. The completed PCB is bolted to a wooden board which is then glued and screwed onto the back panel of the cabinet — here it will give some extra panel damping. The BAF wadding is distributed about the cabinet such that the vent end is not obstructed and all surfaces other than the front panel are covered. Enough BAF is specified to allow for some to be positioned in the centre of the cabinet where it is at its most effective for stopping standing waves.

Ensure that leads to the drive units do not sit against the cabinet walls or drive units where they might buzz. Air leaks are definitely not allowed.

Good listening!

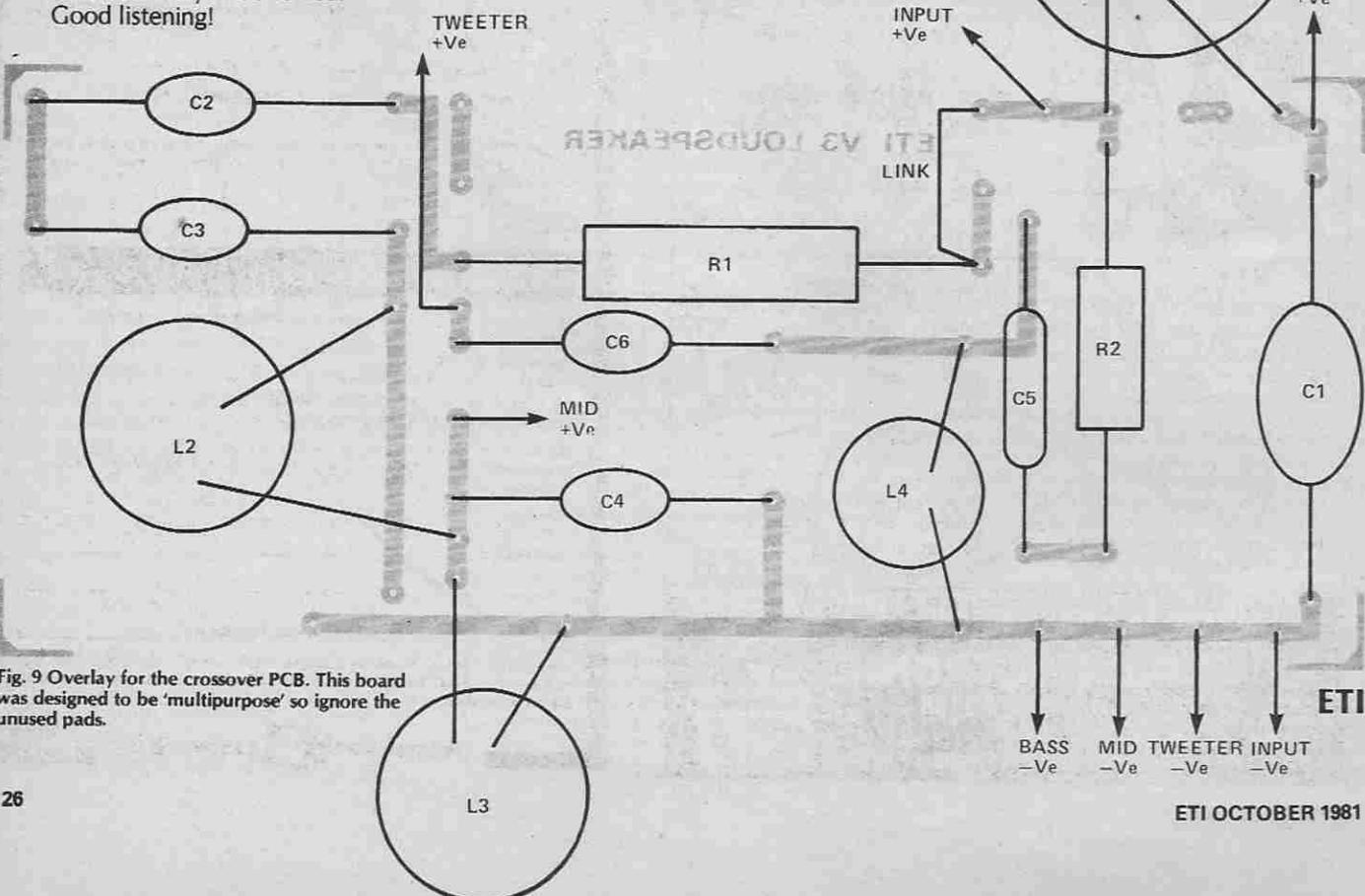


Fig. 9 Overlay for the crossover PCB. This board was designed to be 'multipurpose' so ignore the unused pads.

BUYLINES

A kit of parts comprising all the drive units, all the crossover components including the PCB, BAF wadding, T-nuts and 2BA screws, terminal panel and gaskets is available from Volt Loudspeakers Ltd, 88-90 Grays Inn Road, London WC1X 8AA. The cost of a set of parts for one pair of V3 speakers is £189.75 including VAT and carriage. Note that the woodwork is not included in the kit, although Volt can provide this too for an extra charge. Contact them for details.

PARTS LIST

Resistors	
R1	4R7 10%, 17 W wirewound
R2	12R 5%, 7 W wirewound
Capacitors	
C1	60u 50 V non-polarised electrolytic
C2,3	40u 50 V non-polarised electrolytic
C4	10u 50 V non-polarised electrolytic
C5	1u0 polyester
C6	2u2 50 V non-polarised electrolytic
Inductors	
L1	3.25mH (No. 17)
L2,3	0.5mH (No. 12)
L4	0.28mH (No. 15)


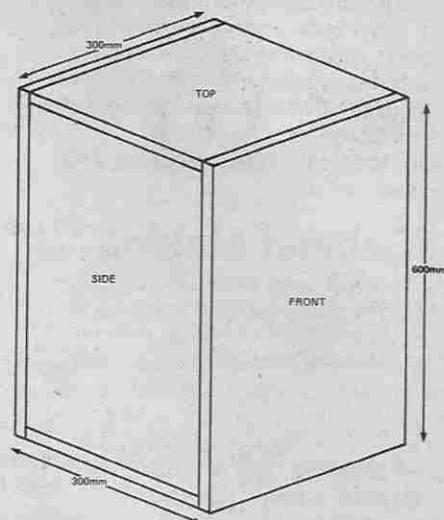


Fig. 10 This is how the panels fit together — if you did your sawing right!

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

BECKER Hi-Fi Speakers

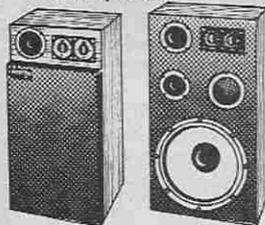

All models multi-speaker systems

With controls, attractive woodgrain finish RMS ratings for 8 ohm.

New improved models.


12.60 12" 4 speaker system 60 watts (90 watts peak) 26 1/2" x 14 1/2" x 11" **£99.95 pair**

15.90 15" 5 speaker system 90 watts (130 watts peak) 28" x 17 1/2" x 11 1/2" **£135.95 pair**

ON DEMONSTRATION TO CALLERS

Collection only
Usually a selection of good value Hi-Fi speakers in stock - please call in.

TV SOUND FROM YOUR HI-FI (Mk III)

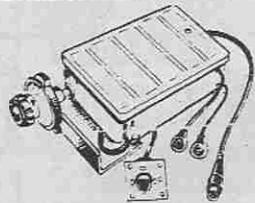

High quality TV sound converter plugs into aerial socket of your FM tuner 9 volt battery operated (battery not supplied). Nothing to look at... but just listen!

★ Fitted slow-motion drive (Mk III) (UK Post etc. 65p)

On Demonstration for callers to 301 Edgware Road

£11.50

PUBLIC ADDRESS AMPLIFIERS AND SPEAKERS



TA770 40 Watt 240v AC OR 12v DC 4 Inputs **£62.50**

TA660 60 watt 240v AC OR 24v DC 5 Inputs **£98.50**

TA306 30 watt 240v AC OR 12v DC 3 Inputs **£42.50**

CP2 10/20 watt 12v DC 2 Inputs **£27.60**

HORNS 8 watt **£4.95**; 15 watt **£8.95**

25 watt **£15.50**; 40 watt **£19.50**

Also Range of Megaphones in Stock

UD130Hz 600/50k Dual PA-Disco mic. **£7.95**

DS255 Deluxe version **£12.95**

ECM1026 600 ohm Mini Lapel mic. **£6.95**

Just 3 of 30 types in stock.



MIXER AND GRAPHICS

GX1307 10 x 10 Channel Stereo Graphic Equaliser Plus 4 Channel Stereo Mixer

£115.00

MC350R Tape Echo Chamber **£59.95**

DE1 Electronic Echo Chamber **£69.95**

SM1000 4 Channel Stereo Mixer (battery operated) **£18.95**

SM500 5 Channel Stereo Disco Mixer Cabinet mounting **£49.95**

SM3000 5 Channel Stereo Mixer **£31.95**

MS3219 Twin 100 watt Audio Output Meter **£12.95**

3019 6 Range Sound Level Meter **£22.95**

PIEZO TWEETERS



Clean sound. Very low distortion tweeters. No crossover required. Suitable up to 100 watts - more in series.

1 Mid-range horn for disco/pa/groups **£6.95**

2 Tweeter horn for hi-fi/disco/pa **£5.50**

3 Popular hi-fi and disco **£4.40**

4 Flat type hi-fi **£3.50**

UK Post Free

On Demonstration to callers.

NEW books from Prentice-Hall and Sams

Prentice-Hall books

Electronic Design with Off-the-Shelf Integrated Circuits
Z. H. Meiksin and Philip C. Thackray

Now available in paperback, this practical handbook gives step-by-step instructions on how to build complex electronic equipment and systems with readily available integrated circuits.
£5.55 Paperback 384 pages 13-250274-7

How to Get More Out of Low-Cost Electronic Test Equipment
Robert Genn, Jr.

This fully illustrated paperback edition of a 1979 publication covers such equipment as multimeters and inexpensive oscilloscopes.
£4.85 Paperback 208 pages 13-408690-2

Practical Troubleshooting Techniques for Microprocessor Systems
James Coffron

The author describes troubleshooting techniques for 8-bit microprocessors, and covers circuits utilizing the 8080, 8085, Z-80 and 6800.
£13.95 Hardback 256 pages 13-694273-3

Pb Video/Computers
Hb How to Select, Mix and Operate Personal Computers and Home Video Systems
Charles J. Sippl and Fred Dahl

For amateurs and experts alike, this clearly-written book discusses the capabilities of the integrated video terminal which lies at the heart of the computer/video communications revolution.
£11.15 Hardback 246 pages 13-941856-3
£5.55 Paperback 13-941849-0

Sams books

Digital Counter Handbook
Louis E. Frenzel, Jr.

Covering both electronic and mechanical counters, this practical book pays special attention to digital-counter test and measuring instruments.
£7.10 Paperback 264 pages 672-21758-9

Practical Solid-State Circuit Design; 2nd Edition
Jerome E. Oleksy

The second edition of this popular book has been expanded to include IC devices and functional blocks—miniature systems on single chips that can be programmed to specific needs.
£5.80 Paperback 216 pages 672-21787-2

SCRs and Related Thyristor Devices
Clay Laster

A clear, thorough guide to the thyristor family, this book covers silicon controlled rectifiers (SCRs), triacs, diacs, unijunction transistors and other devices.
£7.50 Paperback 136 pages 672-21806-2

Prices are correct at the time of going to press but may be subject to change.

Book Orders

These books can be ordered from your bookseller or in case of difficulty from

**Department 30,
Prentice-Hall International,
66 Wood Lane End, Hemel Hempstead,
Hertfordshire HP2 4RG, England.**

Please mark the number of books you wish to order in the boxes besides each title and return the advertisement to the address above with your payment.

Name _____

Address _____

Prentice/Hall  International

ET110

ORDER BY POST (OR PHONE) OR CALL IN

ALL PRICES INCLUDE VAT



Cubegate Limited

AUDIO ELECTRONICS

301 Edgware Rd. London W2 1BN

Tel: 01-724 3564

Also at Henrys Radio 404 Edgware Rd. W2

FREE
Catalogue
send large
20p SAE

Rapid Electronics

Hillcroft House
Station Road
Eynsford Kent

COMPONENT KITS

1/4W Resistor Kit. Contains 10 of each value from 4.7Ω to 1M (total of 650 resistors). 480p each.
Ceramic Capacitor Kit. Contains 5 of each value from 22pF to 0.01μF (total 135 caps.). 370p each.
Polyester Capacitor Kit. Contains 5 of each value from 0.01μF to 1μF (total 65 caps.). 575p each.
Nut and Bolt Kit. Total 300 items 140p each.
 25 6BA 1/4in. bolts 50 6BA washers 50 4BA nuts
 25 6BA 1/2in. bolts 25 4BA 1/4in. bolts 50 4BA washers
 50 6BA nuts

LINEAR

*741	15	*LM301A	25	LM3900	50	*SN7477	150
CA3080	70	LM318	85	LM3909	70	TBA800	80
*CA3130	75	*LM324	40	LM3911	120	TBA810	95
CA3140	45	LM339	50	*LM3914	200	*TL081	30
*CM7555	80	LM380	80	*LM3915	200	TL082	70
LF351	45	LM381	120	LM3800	120	*TL084	90
LF353	85	LM382	120	*NE555	17	XR2206	300
LF356	90	LM387	120	NE556	55	ZN414	100
		LM1458	40	*RC4136	60	*ZN425E	350

CMOS

*4001	13	*4017	45	4028	80	*4066	35	4082	25
4002	25	4018	75	4040	85	4068	25	*4093	43
*4007	18	4020	85	4046	100	*4069	18	4510	85
*4011	14	*4023	25	4047	100	4070	25	*4511	65
*4013	30	*4024	40	*4049	30	*4071	18	*4518	70
4015	80	*4025	18	*4050	30	*4072	18	4520	90
*4016	30	*4027	35	4060	105	*4081	18	*4528	75

SWITCHES

7400	11	7406	26	7427	28	7447	48	7475	38
7401	11	7408	15	7430	15	7448	50	7476	30
7402	12	7410	14	7432	25	7454	16	7483	50
7403	14	7413	24	7437	27	7472	25	7485	75
7404	14	7414	35	7442	40	7473	28	7486	25
7405	17	7420	15	7446	60	7474	25	7489	180

RESISTORS

Carbon film 1/4W 5% 4.7Ω to 10M. Sold in packs of 10 per value. 10p per pack.
 Potentiometers. Preset miniature horizontal 100Ω to 1M. 7p. Rotary 5K-1M Log or Lin. *28p. Slide. 5K-500K Log or Lin. 60mm travel. 63p.
 Mixer type control knobs to suit above pots. Available in red, black, green, grey, yellow and blue. For rotary pots. 16p. Slide pots 12p.

DIODES

1N4001 4p 400mW
 *1N4002 3p zeners
 1N4006 7p
 *1N4148 2p

HARDWARE

5 PP3 battery connectors 30p
 5 red or bl. croc. clips 30p
 22mm solid alum. knob 36p
 28mm solid alum. knob 48p
 Red or black probe clip 35p
 Magnetic earphone + plug 18p
 Crystal earphone + plug 44p
 Pr Ultrasonics 350p
 Red or amber panel neon 45p
 20 way ribbon cable 120p/m
 TO5 or TO18 sink 15p
 TO220 heatsink 28p
 Min push to break sw. 15p
 Submin. toggle DPDT 50p
 20mm panel fuseholder 25p
 909 100mA transformer *65p
 Dale pen 100p
 64mm 64 ohm speaker *70p
 *10 metres 22swg solder *60p

VERO

Size 0.1 matrix
 2.5 x 1in. 22p
 2.5 x 3.75in. 75p
 2.5 x 5in. 85p
 3.75 x 5in. 95p
 VQ Board 160p
 Veropins per 100
 Single sided 50p
 Double sided 60p
 Spotface cutter 105p

CONNECTORS

DIN	Plug	Socket	Jack	Plug	Socket
2 pin	9p	9p	2.5mm	10p	10p
3 pin	12p	10p	3.5mm	*7p	*9p
5 pin	13p	11p	Standard	*12p	*15p
Phono	10p	12p	Stereo	24p	25p

Our new extended 38 page catalogue now contains an even wider range of components. Simply send 42p in stamps for your copy.
FREE with orders over £5

CAPACITORS

Polyester. Radial leads. 250V. C280 type. *0.01, 5p; 0.015, 0.022, 0.033, 6p; 0.047, 0.068 7p; *0.1, 5p; 0.15, 0.22, 9p; *0.47, 10p; 1.0, 22p.
 Electrolytic. Radial leads
 0.47/63V, 7p; 1/63V, *2/63V, *4/7/63V, *10/25V, 5p; 22/25V, 47/25V, 8p; *100/25V, 6p; 220/25V, 14p; 470/25V, 22p; 1000/25V, 30p.
 Tantalum bead
 0.1/50V, 0.22/50V, 0.33/50V, 0.47/50V, 12p; *1/50V, 10p; *2/25V, 12p; *4/7/25V, 15p; *10/25V, 18p.
 Polystyrene 5%. 10p to 1000p 6p each; 1500p to 4700p 8p each; 6800p to 0.01 μF each.

TRANSISTORS

AC128	25	*BC182L	8	*BF244B	18	ZTX108	12
AC176	25	*BC184L	7	BFX29	25	ZTX300	14
AD161	40	BC122L	10	BFY51	23	2N2369	17
AD162	40	*BC214L	8	*BFY52	18	2N2646	45
BC107	10	*BC478	20	MJ2955	100	2N3053	23
*BC108	8	BC547	10	TIP31A	45	2N3055	50
*BC108C	10	BC548	10	TIP32A	45	*2N3702	6
BC109	10	BC549	10	TIP41A	60	*2N3704	6
BC109C	12	BD131	35	TIP42A	60	2N3819	15
BC148	8	BD132	35	TIP2955	60	2N3904	10
BC178	18	BD139	35	TIP3055	55	*2N3905	6
BC179	18	BD140	35	*ZTX107	9	*2N5459	18

SOCKETS

8-pin 7p
 14-pin 9p
 16-pin 10p
 18 pin 15p
 100 Soldercon pins 45p

REGULATORS

*78L05	25	*7905	50
78L12	30	*7912	45
78L15	30	7915	65
*7805	45	LM723	40
*7812	45	*LM317T	99
7815	60	*LM322K	350

OPTO

*3mm, red 7p
 *3mm green 12p
 *3mm yellow 14p
 *5mm red 8p
 *5mm green 12p
 5mm yellow 14p
 *FND500 70p

CABLES

20 metre pack of connecting cable. 2m each 10 colours. 75p
 Lightweight screened 12p/m
 Standard screened 16p/m
 Stereo screened 23p/m
 4 core screened 45p/m
 Min. mains 3 core 23p/m

The Rapid Guarantee ★ Same day despatch ★ Competitive prices
 ★ Top quality components ★ In-depth stock

New Bear

2708 £1.99 2716 £2.99
 4116 £1.99 4027 £0.45
 SFF96364 £8.00 6821 £3.10
 6402 £5.00 6800 £4.99
 80 0.1" Pitch edge connector £2.30
 (NASCOM & 77/68)

SEND/PHONE FOR EXTENSIVE
special offer
 LISTS
 74LS, 6800, 6502, Z80, 6809
 CONNECTORS, CRYSTALS, SWITCHES,
 DISK DRIVES, MEMORIES

"LOW PRICES"

Fast Delivery

40 BARTHOLOMEW STREET, NEWBURY, BERKS.
 (0635) 30505. PLEASE ADD V.A.T., P. & P. 30p
 BARCLAYCARD, ACCESS & OFFICIAL ORDERS
 WELCOME.

D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts. Sanded base. Ideal for programming. 6-position at less than half manufacturer's price. ONLY 75p Will fit into 14-pin dill socket. Ten at 65p ea.; per 100 55p ea.	HONEYWELL PROXIMITY DETECTOR Integral amplifier. 8v. D.C. £3.50 PHOTO CONDUCTIVE CELL £1.25. High-power CdS cell; 500mW. for control circuits. Resistance 600 ohm to 4K. Max. volts 240. Size 1/2 x 1/2in. RIBBON MICROPHONE with pre-amp. on chassis, £1.75.	MULLARD MODULES LP1171 IF Strip Front end LP1186 vancap LP1157 Med. & Long Tuner £5.00	ULTRA SONIC TRANSDUCERS 40K/C. Complete on 18in. screened cable. £1.75 each; pairs £2.55. ULTRA SONIC TRANSMITTER. Complete unit (uncased requires 1.5V) £3.25. FOSTER DYNAMIC MICROPHONES. 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
U.H.F. MODULATORS Latest type, adjustable, ideal for computers. Size 3x2 1/2 x 1 inch Only £2.95 In screened case	LM380 Amplifier 75p LM318N Hi-Slew Op. Amp. £1.50 LM323K 5v. 3-amp. reg. £3.80 LM310N Volt. Follower Amp. £1.20 LM311H High Perf. Volt. Comparator. £1.00 LM384N 5-watt Amp. £1.20 LM393N Dual Comparator 60p	CRYSTALS COLOUR TV 4 433619 mc/s £1.25 Miniature type sealed 7905 Voltage Regulator 1 amp TO220 Negative - Motorola 80p	CHIPS 2102 450 n/s £1.00 2114 300 n/s £1.75 2115 300 n/s £1.50 2732 450 n/s £7.50
MONSANTO Half-inch + 1 Display High Intensity £1 each set of 4 £3.50 Common anode 14 Pin Dill Package	STEREO CASSETTE TAPE HEADS Quality replacement for most recorders with mounting plate. Record/Replay £2.80 MARRIOTT TAPE HEADS Quarter track Type XRPS18 Record/Replay (each) £2.00 XRPS26 Record/Replay (each) £3.00 XES11 Erase (each) £1.00	HEWLETT-PACKARD DISPLAYS HIGH EFFICIENCY AND VERY BRIGHT Only £1.00 each Set of 5 for £5 Half-inch red common cathode wall. replace DL707. 14-pin Dill.	EX-MOTOROLA 5 + 5-WATT CAR STEREO AMPLIFIERS WATT CAR STEREO AMPLIFIERS Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in) with circuit and data. Only £5 pair. Includes pre-amp.
BRIDGE RECTIFIER 800 PIV 35 amps 1/2x1/2x1/2in. £3.50	RECHARGEABLE BATTERIES VARTA 36 volts DEAC. M/AAH 225 £1.90 DRYFIT 6-volt 4.5 amp. £7.50 XJAL FILTER 10.7mc/s. 12.5dB separation. 1/2x1/4x1 inch £7.00 100K/S + 1 meg 3-pin 12.00	"CHERRY" ADD-ON KEYPAD LIST PRICE £22.00 OUR PRICE £7.50 - V.A.T.	A compact 12-button keypad suitable for use with Cherry Keyboard to extend its functions plus four extra keys. Supplied brand new with data. A 3 x 4 non-encoded single mode keyboard in sloped format.

QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated).
 DELIVERY from stock - All post paid. Please add V.A.T. EXPORT enquiries invited.
TELEX 262284
 Transonics
 Mono 1400

Henry's

01-723 1008/9
 404 EDGWARE ROAD, LONDON W2 1ED

electronics today international BOOK SERVICE

How to order: Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Modmags Sales Office, 145 Charing Cross Road, London WC2. All prices include P&P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires £4.50
Beginners Guide to Transistors Reddihough £4.50
Beginners Guide to Integrated Circuits Sinclair £4.50
Beginners Guide to Radio King £4.50
Beginners Guide to Audio Sinclair £4.50
Introducing Amateur Electronics Sinclair £4.50
Understanding Electronic Circuits Sinclair £5.10
Understanding Electronic Components Sinclair £5.10

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filter Cookbook £11.30
IC Timer Cookbook £7.65
IC Op Amp Cookbook £10.70
TTL Cookbook £7.55
MC 6809 Cookbook Carl D. Warren £5.30
PLL Synthesiser Cookbook Kinley £5.85
8085A Cookbook Titus £10.05

APPLICATIONS

How To Build Electronic Kits Chapel £3.25
110 Electronic Alarm Projects Marston £5.25
110 Semiconductor Projects for the Home Constructor Marston £5.25
110 Integrated Circuit Projects for the Home Constructor Marston £5.25
110 Thyristor Projects Using SCRs Marston £5.25
110 Waveform Generator Projects Marston £5.25
99 Practical Electronic Projects Friedman £4.20

COMPUTING & MICROPROCESSORS

What is a Microprocessor 2 cassette tapes plus a 72-page book £10.00
Beginners Guide to Computers and Microprocessors with projects £6.05
Basic Computer Games Ahl £6.05
Basic for Home Computers Albrecht £6.60
Illustrating Basic Alcock £4.25
Troubleshooting Microprocessors and Digital Logic Goodman £5.90
Z-80 Microcomputer Handbook £7.75
Microprocessors in Instruments and Control Bibbero £13.10
Basic Basic Coan £7.25
Advanced Basic Coan £6.40
1001 Things to do with your Personal Computer Sawusch £6.00
Microcomputers, Microprocessors, Hardware, Software and Applications Hilburn £17.40
Microprocessor Systems Design Klingman £18.80
Introduction to Microprocessors Leventhal £11.25
Microprocessor Technology, Architecture and Applications £11.30
Basic with Style Nagin £4.50
Microcomputer Design Ogdin £7.45
Hands on Basic with a Pet Peckham £11.95
6800 Software Gourmet Guide and Cookbook Scelbi £9.20
8080 Software Gourmet Guide and Cookbook Scelbi £9.20
The 8080A Bugbook Rony £8.35
8080/8085 Software Design Titus £7.60
How to Design, Build and Program your own Working Computer System £7.10
Your Own Computer Waite £2.25
Microcomputer Interfacing Handbook A/D & D/A £6.35
Crash Course in Microprocessors Frenzel £12.40
Musical Applications of Microprocessors Chamberlain £17.50
The Pascal Handbook Tiberghien £11.35
50 Basic Exercises Lamotier £9.50
Learning Basic with the Sinclair ZX80 £4.95
Microprocessors for Hobbyists Coles £4.25
Introduction to Microcomputer Programming Sanderson £5.25
Microprocessors and Microcomputers for Engineering Students and Technicians Woolland £5.95
Using CP/M - Self Teaching Guide Ashley Fernandez £6.95
Digital Counter Handbook Frenzel £8.40
33 Challenging Computer Games for TRS80-Apple-Pet Chance £5.75
How to Build Your Own Working Robot Pet Dalesta £5.75
Microprocessor and Digital Computer Technology £16.00
Guidebook to Small Computers Barden £4.20
How to Debug Your Personal Computer Huffman £6.30
How to Troubleshoot and Repair Microcomputers Leuk £6.30
6809 Microcomputer Programmes and Interfacing with Experiments Staugaard £10.20
Wordprocessors Programmed. Training Guide with Practical Application £ Digital Circuits and Microcomputers Johnson £9.75
Experiments in Artificial Intelligence for Small Computers £5.60

LOGIC

Designing with TTL Integrated Circuits Texas Instruments £10.95
How to Use IC Circuit Logic Elements Strater £4.85
110 CMOS Digital IC Projects for the Home Constructor Marston £5.25
Digital ICs - How They Work and How to Use Them Barber £16.30
Electronic Design with Off the Shelf ICs Meikson £6.30
Getting Acquainted with the IC Turner £4.20

TEST INSTRUMENTS

The Oscilloscope in Use Sinclair £4.00
How to Get More Out of Low-cost Electronic Test Equipment Genn £5.50

OP-AMPS

Applications of Operational Amplifiers Graeme £9.20
110 Operational Amplifier Projects for the Home Constructor Marston £5.25
Designing with Operational Amplifiers Burr Brown £26.50
Design of Op-Amp Circuits with Experiments £6.80
Operational Amplifiers. Design and Applications Tobery £8.95
Op-Amp Handbook Hughes £15.50

COMMUNICATIONS

Digital Signal Processing. Theory and Applications Rabiner £24.40
Electronic Communication Systems Kennedy £8.95
Principles of Communication Systems Taub £8.40

THEORY

Introduction to Digital Filtering Bognor £12.25
Transistor Circuit Design Texas Instruments £10.95
Electronic Circuit Design Handbook Design of active filters, with experiments: Berlin £6.80

REFERENCE

Electronic Engineers Reference Book Turner £41.00
Electronic Components Colwell £4.00
Electronic Diagrams Colwell £4.00
International Transistor Selector Towers £10.70
International FET Selector Towers £4.60
International Op-Amp Linear IC Selector Towers £8.00
International Microprocessor Selector Towers £16.00
Dictionary of Audio - Radio and Video Roberts £16.00
Dictionary of Electronics Amos £16.00
Dictionary of Electrical Engineering Amos £16.00
Dictionary of Telecommunications Amos £16.00
Giant Book of Electronic Circuits Collins £5.75
World Radio/TV Handbook Vol. 35 1981 £10.50
How to Build Electronic Projects Malcolm £6.45
Modern Electronic Circuit Reference Manual Marcus £33.50

GENERAL ELECTRONICS

Electronic Fault Diagnosis Sinclair £4.00
Printed Circuit Assembly Hughes and Colwell £4.00
Electronic Musical Instruments Crowhurst £4.25
Electronic Music Synthesisers Horn £4.60
Videocassette Recorders. Theory and Servicing McGinty £10.50
Practical Electronic Maths. Velay and Dulin £6.95
Electronic Circuits. Discrete and Integrated Schilling, Belove £7.25
Electronic Troubleshooting Handbook Genn £5.60
Experimenters Guide to Solid State Electronic Projects Barber £5.60
Practical Handbook of Solid State Troubleshooting Genn £11.00
Practical Solid State Circuit Design Oleksy £7.00
The Art of Electronics Horowitz £14.10
Complete Guide to Reading Schematic Diagrams Douglas Young £5.60

Fallen behind recent advances?

Just starting out?

Need a decent reference book?

ETI Book Service provides an easy way of getting your hands on the right title.

TTLs by TEXAS				74LS SERIES				9301 SERIES				74S SERIES				74S114				TRANSISTORS				BFR40				TIP300				3N141				6A 50V			
7400	30p	74LS00	12p	4023	20p	9301	160p	74S00	60p	74S124	300p	AC126	25p	BFR41	25p	TIP30C	48p	2N3442	140p	3N141	110p	6A 50V	80p																
7401	11p	74LS01	14p	4024	40p	9302	175p	74S01	60p	74S132	160p	AC127B	20p	BFR79	25p	TIP31A	52p	2N3553	240p	3N201	110p	6A 100V	100p																
7402	12p	74LS02	14p	4025	20p	9306	316p	74S02	75p	74S133	75p	AC176	25p	BFR80	25p	TIP31C	52p	2N3584	250p	3N204	120p	6A 400V	120p																
7403	14p	74LS03	14p	4027	32p	9310	275p	74S03	75p	74S138	225p	AC198	10p	BFR81	25p	TIP32A	52p	2N3633	48p	40290	250p	10A 400V	200p																
7404	14p	74LS04	15p	4028	60p	9311	275p	74S04	60p	74S139	225p	AF116	50p	BFX29	40p	TIP32C	82p	2N3702/2	12p	40296/1/2	75p	25A 400V	400p																
7405	18p	74LS05	15p	4029	75p	9312	160p	74S05	60p	74S157	250p	AD149	70p	BFX30	34p	TIP33A	90p	2N3706/1/4	14p	40408	90p	ZENERS																	
7406	21p	74LS06	16p	4030	40p	9314	165p	74S06	60p	74S163	300p	AD161/2	45p	BFX34/5	40p	TIP33C	114p	2N3708/9	12p	40410	100p	2.7V-33V																	
7407	27p	74LS07	16p	4031	40p	9316	225p	74S07	90p	74S174	250p	AU107	200p	BFX36/7	30p	TIP34A	114p	2N3773	300p	40411	300p	400mW	9p																
7408	16p	74LS10	15p	4034	180p	9322	150p	74S10	90p	74S175	320p	BC107/8	13p	BFX38	50p	TIP34B	160p	2N3819	25p	40594	120p	1W	15p																
7409	15p	74LS11	25p	4035	80p	9324	360p	74S11	90p	74S241	450p	BC119	10p	BFX40	90p	TIP35A	68p	2N3820	50p	40595	120p																		
7410	15p	74LS12	25p	4036	285p	9334	360p	74S12	90p	74S242	450p	BC147/8	9p	BFY51/2	30p	TIP35C	290p	2N3833	70p	40599	120p																		
7411	20p	74LS13	25p	4037	285p	9368	250p	74S13	90p	74S260	70p	BC149	10p	BFY56	33p	TIP36A	270p	2N3866	90p	40871/2	100p																		
7412	20p	74LS14	45p	4038	285p	9370	300p	74S14	180p	74S373	400p	BC157/8	10p	BFY56	33p	TIP36C	340p	2N3902	700p																				
7413	25p	74LS15	45p	4039	55p	9374	200p	74S15	120p	74S374	400p	BC158/9	12p	BFY56	33p	TIP41A	65p	2N3903/4	18p																				
7414	35p	74LS16	20p	4040	55p							BC159/12	11p	BFY56	33p	TIP41C	70p	2N3905/6	20p																				
7414	35p	74LS17	20p	4041	55p							BC160/12	11p	BFY56	33p	TIP42A	70p	2N3907	85p																				
7415	25p	74LS18	18p	4042	70p							BC172	12p	BU104	225p	TIP42C	82p	2N4061/2	18p																				
7416	25p	74LS19	18p	4043	70p							BC177/8	17p	BU105	190p	TIP54	160p	2N4123/4	27p																				
7417	17p	74LS20	18p	4044	70p							BC179	18p	BU108	255p	TIP120	120p	2N4125/6	27p																				
7420	17p	74LS21	18p	4045	70p							BC182/3	10p	BU109	225p	TIP122	130p	2N4143/3	27p																				
7421	30p	74LS22	18p	4046	70p							BC187	30p	BU180A	120p	TIP142	130p	2N4227	90p																				
7422	20p	74LS23	18p	4047	70p							BC212/3	11p	BU205	250p	TIP144	130p	2N4247	90p																				
7423	22p	74LS24	40p	4050	27p							BC214	12p	BU208	200p	TIP255	78p	2N5087	27p																				
7425	28p	74LS25	40p	4051	80p							BC227	16p	BU208	200p	TIP4055	70p	2N5089	27p																				
7426	30p	74LS26	40p	4052	80p							BC327	16p	BU208	200p	TIS93	30p	2N5172	27p																				
7427	25p	74LS27	40p	4053	80p							BC338	16p	E300	50p	ZTX108	12p	2N5191	90p																				
7428	30p	74LS28	40p	4054	80p							BC341	36p	E308	50p	ZTX109	12p	2N5194	90p																				
7430	15p	74LS29	20p	4055	120p							BC347/8	30p	E310	50p	ZTX500	18p	2N5236	55p																				
7432	25p	74LS29	20p	4056	120p							BC348	36p	MJ2501	225p	ZTX502	18p	2N5236	55p																				
7433	27p	74LS29	20p	4059	500p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7434	27p	74LS29	20p	4060	90p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7435	27p	74LS29	20p	4060	90p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7436	30p	74LS29	20p	4063	100p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7437	30p	74LS29	20p	4063	100p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7440	17p	74LS29	20p	4066	120p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7441	70p	74LS29	20p	4067	400p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7442A	50p	74LS29	20p	4068	18p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7445	60p	74LS29	20p	4069	18p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7446A	95p	74LS29	20p	4070	18p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7447A	45p	74LS29	20p	4071	18p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7448	45p	74LS29	20p	4072	18p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7450	17p	74LS109	30p	4073	20p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7451	17p	74LS112	34p	4075	20p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7453	17p	74LS113	30p	4076	60p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7454	17p	74LS114	30p	4077	16p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7456	17p	74LS114	30p	4078	16p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7457	17p	74LS114	30p	4078	16p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7470	36p	74LS123	50p	4086	72p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7472	30p	74LS124	120p	4089	150p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7473	30p	74LS125	30p	4093	40p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7474	23p	74LS126	30p	4094	150p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7475	30p	74LS132	45p	4095	95p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7480	50p	74LS136	30p	4097	340p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7481	100p	74LS138	36p	4098	90p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7482	70p	74LS139	36p	4099	120p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7483A	45p	74LS145	70p	4098	90p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7484	100p	74LS147	160p	4097	120p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7485	90p	74LS149	160p	4097	120p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7486	25p	74LS151	70p	40102	180p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7489	210p	74LS153	60p	40103	180p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7490A	30p	74LS154	200p	40106	50p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7491	60p	74LS155	40p	40109	100p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7492A	30p	74LS156	40p	40163	100p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7493A	30p	74LS157	40p	40163	100p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7494	50p	74LS158	36p	40174	90p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7495A	50p	74LS160	40p	40175	100p							BC349	36p	MJ2505	225p	ZTX504	30p	2N5401	50p																				
7496	45p	74LS161	40p	40193	120p							BC34																											

DESIGNER'S NOTEBOOK

Ray Marston looks at some unique micropower monitor and oscillator circuits which give years of continuous operation from a battery supply.

Analogue alarm-type monitor circuits have a variety of practical applications in the home and in industry. Such circuits may be used to monitor temperature, light, sound or voltage levels and activate an alarm or relay when preset levels are exceeded. The trouble is, such circuits almost invariably draw fairly high quiescent currents and have to be mains-powered, since they would otherwise flatten a supply battery after only a day or two of continuous operation. This month's Notebook looks at ways of designing micropower versions of such monitors, which will give years of continuous operation from a single supply battery.

Conventional Checking

Figure 1 shows the circuit of a conventional precision temperature monitor, which operates a relay when the temperature of TH1 rises above a value preset by PR1. Here, R1 and R2 are wired as one half of a Wheatstone bridge and apply a fixed reference voltage to the non-inverting terminal of voltage comparator IC1; NTC thermistor TH1 and PR1 are wired as the other half of the bridge and feed a temperature-dependent voltage (which falls with increasing temperature) to the inverting terminal of the comparator. In use, PR1 is adjusted so that the bridge is very slightly unbalanced at the desired alarm temperature, thus driving the output of IC1 high when the temperature reaches or exceeds the preset level and actuating the relay via VFET Q1. Note that the action of this circuit can be reversed, so that it acts as a precision under-temperature switch or monitor, by simply transposing the positions of TH1 and PR1.

An outstanding advantage of the Fig. 1 circuit is that, because TH1-PR1-R1-R2 are bridge-configured, the trip point of the circuit is not influenced by variations in the supply voltage, and the design thus gives true 'precision' operation. A major disadvantage of the circuit is that it draws a quiescent current of about 5 mA and will flatten a PP9 battery after less than two

days of continuous operation. In actual fact, however, the circuit does not (logically) need to be continuously powered, for the following reason.

Micropower Sampling Techniques

The Fig. 1 circuit monitors the temperature continuously and thus draws continuous power. In reality, however, temperature is a slowly varying parameter and thus does not need to be monitored continuously; instead, it can be efficiently monitored by briefly inspecting or sampling it only once every second or so. If the sample periods are very brief (say 300 μ s) relative to the sampling interval (1 s) the mean current consumption of the monitor can be reduced by a factor equal to the interval/period ratio (eg a factor of 3300) by using the sampling technique; for example, the 5 mA consumption of the Fig. 1 circuit can be reduced to a mean value of a mere 1.6 μ A. The sampling technique thus enables micropower monitor designs to be implemented.

Figure 2 shows the basic circuit of a micropower or sampling version of the precision temperature monitor, which operates the relay when the TH1 temperature rises above a preset value but which draws a mean quiescent current of only a few microamps. The TH1-PR1-R1-R2-IC1 monitor network is almost identical to that of Fig. 1, but instead of being continuously powered it is powered by a sample pulse generator and Q1. Note that the output of IC1 is fed to temporary memory store R4-C1 via D1, and that the memory store operates the relay via VFET Q2.

Thus, if the TH1 temperature is below the trip level when the sample pulse arrives, IC1 output will remain low and no

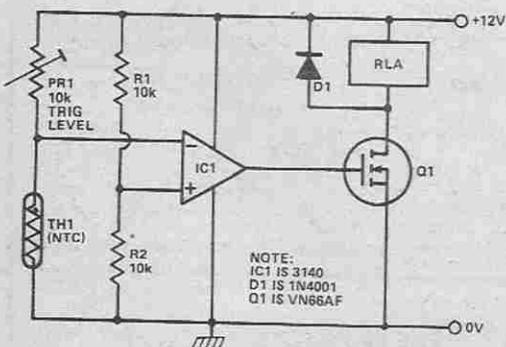


Fig. 1 This over-temperature alarm consumes a quiescent current of about 5 mA and will flatten a PP9 battery in under two days.

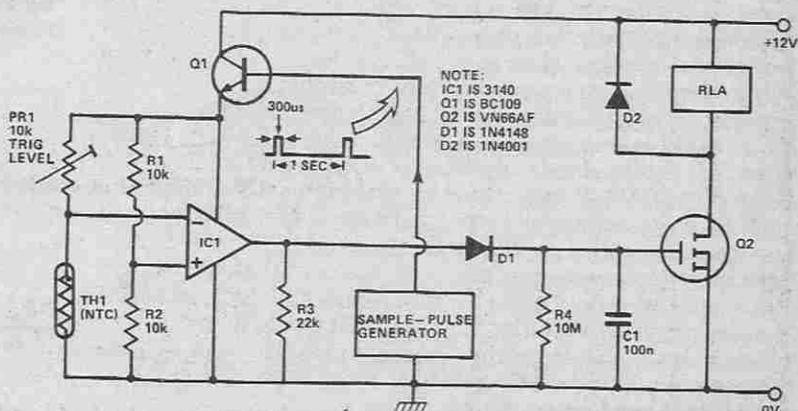


Fig. 2 This micropower or sampling version of the circuit consumes a mean quiescent current of only a few microamps and gives years of operation from a PP9.

charge will be fed to C1, so Q2 and the relay will be off. If the TH1 temperature is above the trip level when the sample pulse arrives the IC1 output will switch high for the duration of the pulse and thus rapidly charge C1 up via D1, driving the relay on via Q2; the C1 charge will then easily hold the relay on until the arrival of the next sample pulse.

The Fig. 2 circuit, then, illustrates the basic principles of the micropower sampling technique. In reality, the sampling interval used (and thus the reduction in mean power consumption) will depend on the specific application. If, for example, you wish to monitor the temperature of a large vat, which has massive thermal inertia, you can happily use sampling intervals of several minutes and thus run the monitor with only nanoamps of current. If, on the other hand, you wish to monitor transient changes in light or sound levels with minimum durations of 100 ms, you may have to use a 50 ms sampling interval and a 1 ms sample pulse, in which case the mean current consumption of your circuit will be reduced by a factor of 'only' 50!

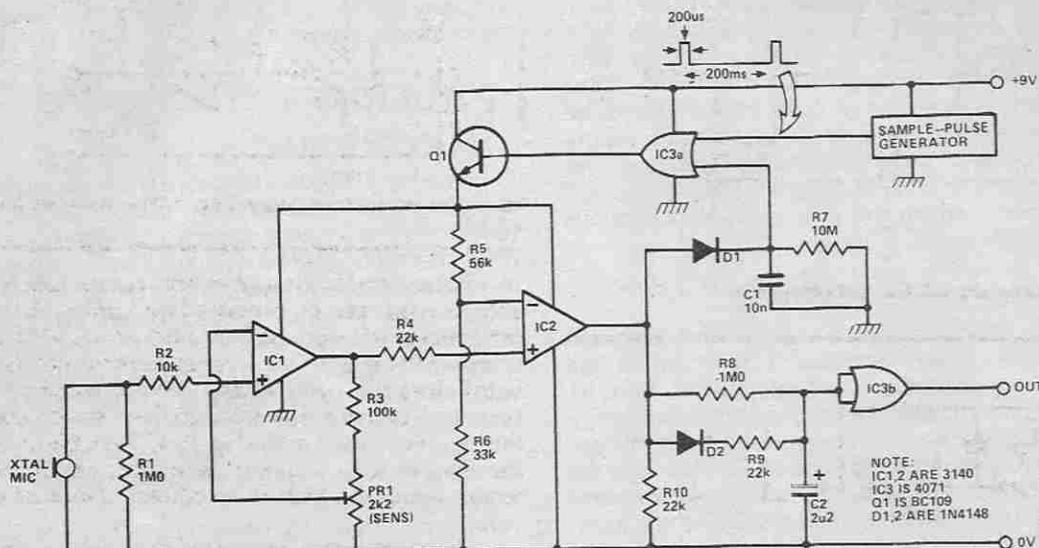


Fig. 3 This micropower 5 kHz tone-signal monitor consumes less than 10 uA of stand-by current.

In some cases you may have to slightly modify the operating principle of the sampling circuitry to obtain the desired micropower operation. Figure 3, for example, shows the basic circuit of a micropower 5 kHz tone-signal monitor which consumes a quiescent current of under 10 uA and in which the monitored tone signals have minimum durations of 250 ms. Thus, the sample pulse generator is designed to produce a minimum pulse width of 200 us so that it can 'capture' at least one full 5 kHz tone cycle, and the sampling interval is set at 200 ms so that part of a tone burst will always be captured. The sampling circuitry thus gives a 1000:1 reduction in monitor current consumption. The Fig. 3 circuit is designed to produce a high output when it receives a tone burst that is greater than a preset amplitude and duration, and operates as follows.

A crystal microphone is used to monitor the tone signals and has its output fed to the input of variable-gain amplifier IC1; this IC is a CA3140 op-amp and its input terminal is grounded by R1-R2, so it produces an output that is equal to an amplified and positively rectified version of the input signal. This is fed to the input of non-inverting voltage comparator IC2, which thus produces a high output when the tone signal amplitude exceeds a value preset by PR1. The IC1-IC2 circuit would normally consume about 6 mA, but in this design is sampled by a 200 us pulse once every 200 ms via OR gate IC3a and Q1 and thus consumes a mean current of only 6 uA.

If no output is produced from the monitor during the 200 us sampling period, the circuit will simply send another sample pulse 200 ms later. If, however, an output is produced during the

200 us sample period the resulting output pulse will be captured by D1-C1-R7 and use to fully connect the supply to the IC1-IC2 monitor circuitry via OR gate IC3a and Q1: the circuit will then temporarily operate in the conventional mode in which the 5 kHz input tone burst produces a train of square wave output signals from IC2. These signals are then 'conditioned' by D2-R8-R9-C2 and IC3b, which produces a high output only if the signals are continuously present for at least 50 ms. The sampling and conditioning circuitry thus gives very high overall immunity to false triggering by transient signals and other glitches.

Looking again at the Fig. 2 and 3 circuits, it is obvious that if the sampling systems is to be truly efficient, the actual sample-pulse generator must itself consume negligible current, and this immediately makes us think of using a CMOS oscillator in this position. Unfortunately, however, conventional CMOS oscillators are not good enough for the sampling application, so some rather special designs are called for. Let's look at this subject.

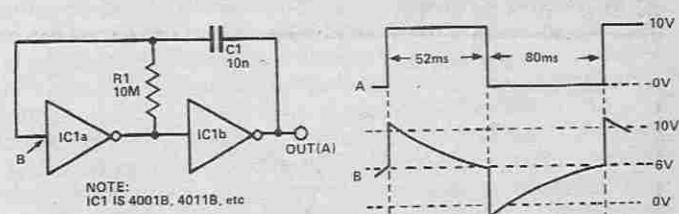


Fig. 4 This standard CMOS astable consumes 12 uA at 6 V, 75 uA at 10 V.

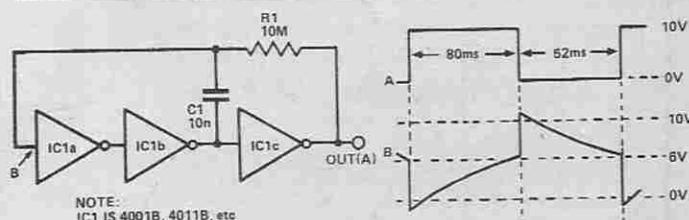


Fig. 5 This ring-of-three CMOS astable consumes 12 uA at 6 V, 75 uA at 10 V.

CMOS Oscillators

Figures 4 and 5 show the circuits and waveforms of a standard and a ring-of-three B-series astable respectively. Note that each of these circuits has a period of 132 ms and consumes a

mean current of 12 μ A from a 6 V supply or 75 μ A from a 10 V supply. Also note that both circuits use a 10M timing resistor, so these relatively high current-consumption levels are clearly attributable to the actual CMOS chips and not to the timing networks.

The Fig. 4 and 5 astable circuits are designed around modern B-series buffered CMOS chips: even higher current-consumption figures are obtained if old-fashioned A-series unbuffered chips are used in the designs. A-series chips are no longer readily available, but you can simulate them by using a 4007UB dual complementary pair plus inverter chip (see Fig. 6). Figure 7 shows how to connect a 4007UB so that it acts like an unbuffered ring-of-three astable; note in this case that the circuit consumes 280 μ A from a 6 V supply or 1.6 mA from a 10 V supply.

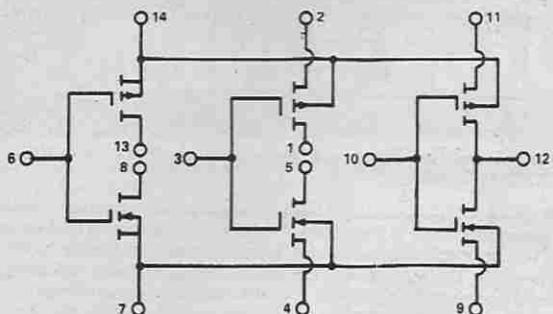


Fig. 6 Functional diagram of the 4007UB dual complementary pair and inverter.

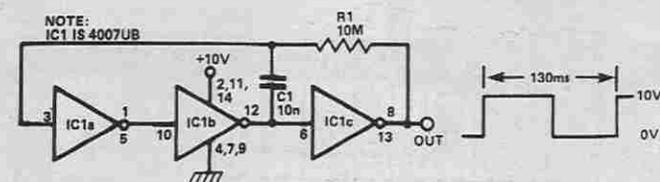


Fig. 7 This 'unbuffered' version of the ring-of-three astable consumes 280 μ A at 6 V, 1.6 mA at 10 V.

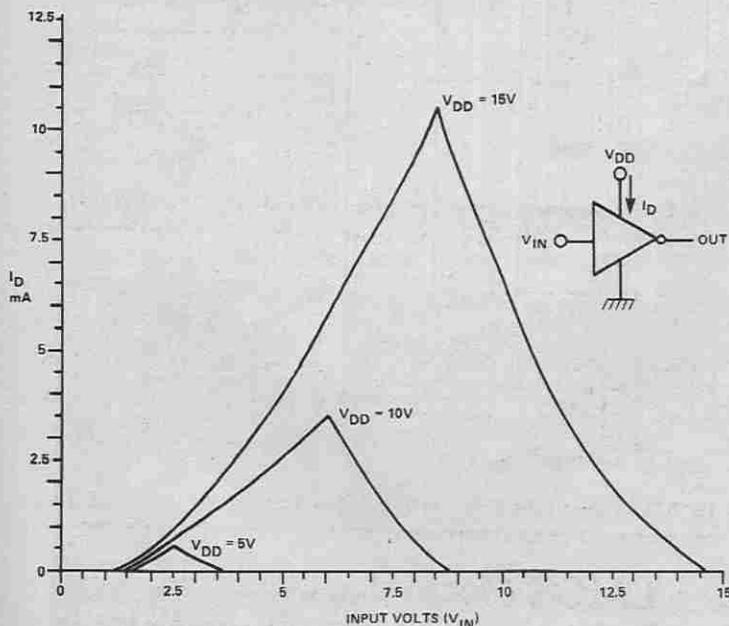


Fig. 8 Typical current and voltage transfer characteristics of a CMOS inverter stage (4001, 4007, 4011 etc).

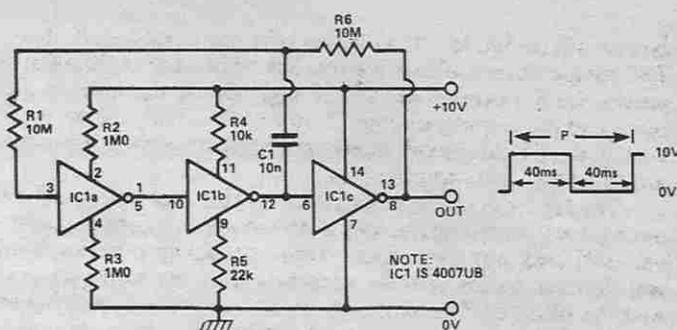


Fig. 9 This micropower ring-of-three symmetrical astable consumes 8 μ A at 10 V, or 1.5 μ A at 6 V.

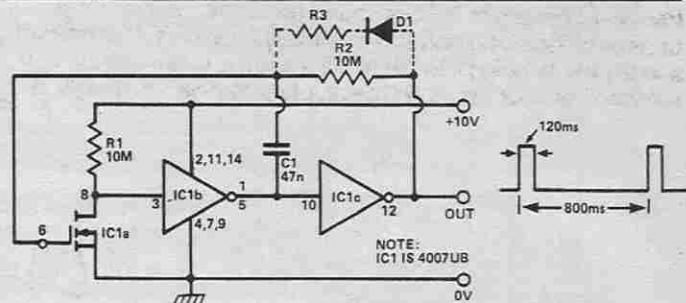


Fig. 10 This asymmetrical ring-of-three astable consumes 5 μ A at 10 V, 2 μ A at 6 V.

The reason for the high current consumption of the Fig. 4, 5 and 7 circuits can be explained by looking at the typical current/voltage transfer characteristics of a CMOS inverter stage, as shown in Fig. 8. As the inverter is driven into its 'linear' region both halves of its complementary MOS stages are driven on and fairly high currents flow through these stages. Looking back at the basic waveform of the Fig. 4 and 5 astables, you can see that the input of IC1a is almost permanently driven into the linear region, hence the high mean current consumptions of the circuits.

Now that we've discovered the cause of the high current consumption of the conventional CMOS astable, it is a fairly easy matter to solve the problem and come up with a useful micropower CMOS astable design, as shown in Fig. 9. Here, the 4007UB IC is configured as a ring-of-three astable, but current-limiting resistors are wired in series with its IC1a and IC1b stages, to limit its 'linear mode' currents to very low levels. The resulting circuit consumes a mere 1.5 μ A at 6 V or 8 μ A at 10 V and produces a symmetrical output waveform, although the frequency stability of the circuit is not particularly good, with the period varying from 200 ms at 6 V to 80 ms at 10 V.

Figure 10 shows how to wire the 4007UB as an asymmetrical ring-of-three astable that consumes 2 μ A at 6 V or 5 μ A at 10 V. The circuit produces a 120 ms pulse once every 800 ms: the pulse width of the circuit can, if desired, be reduced below the 120 ms value by shunting R2 with a diode-resistor series combination, as shown dotted by R3-D1 in the diagram; the R3 value determines the pulse width. Note that this circuit has the desired characteristics of the sample pulse generator that we are looking for.

Figure 11 shows a practical example of the modified version of the Fig. 10 circuit. In this case the circuit produces a 300 μ s pulse once every 900 ms and consumes 2 μ A at 6 V or 4.5 μ A at 10 V. In the diagram the output is shown feeding directly to a PB-2720 acoustic transducer, which thus produces a repetitive 'tick-tick' sound: this circuit can usefully be fixed to a lamp or other object, so that the object can easily be sound-located in the dark, or by the blind.

The current consumption of the Fig. 11 circuit can be even further reduced by simply wiring a 22k resistor between pin 2 or the 4007UB and the positive supply line, as shown in Fig. 12. This

MASTER ELECTRONICS NOW!

The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

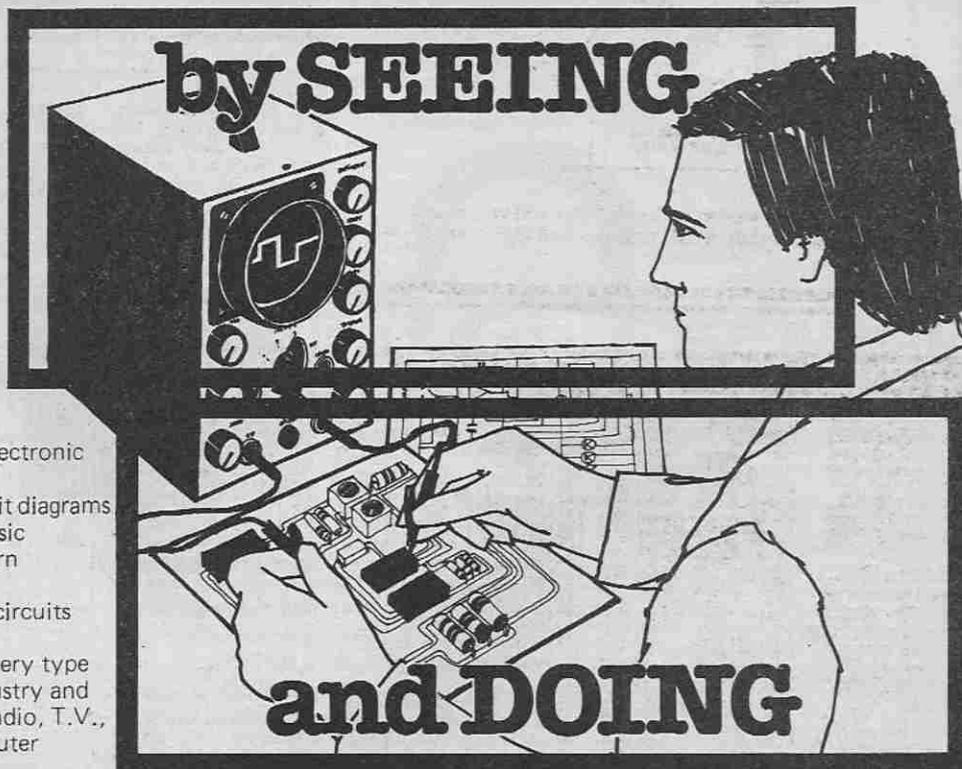

New Job? New Career? New Hobby? Get into **Electronics Now!**

FREE!

COLOUR BROCHURE



Please send your brochure without any obligation to

I am interested in:

ETI/10/820

NAME _____

COURSE IN ELECTRONICS as described above

ADDRESS _____

RADIO AMATEUR LICENCE

MICROPROCESSORS


LOGIC COURSE

OTHER SUBJECTS _____

POST NOW TO:

BLOCK CAPS PLEASE

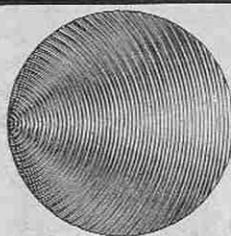British National Radio & Electronics School Reading, Berks. RG1 1BR.




APPROVED
thandar
STOCKIST

B.K. ELECTRONICS

A SOUND CHOICE

APPROVED
thandar
STOCKIST

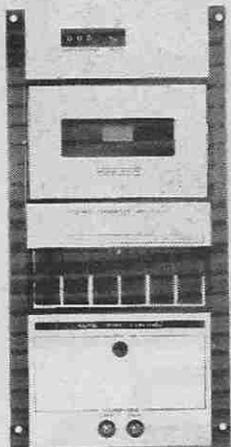★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



6 piano type keys

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price:-

15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz. magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohm, 20 oz. magnet, 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone and black protective grill. **Price £8.90 each.** £1.25 Packing and Carriage each.

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.45 each.**



Type 'B' 3 1/2in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**

Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**

Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £6.90 each.**

Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

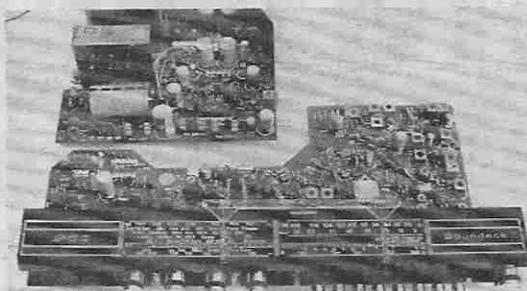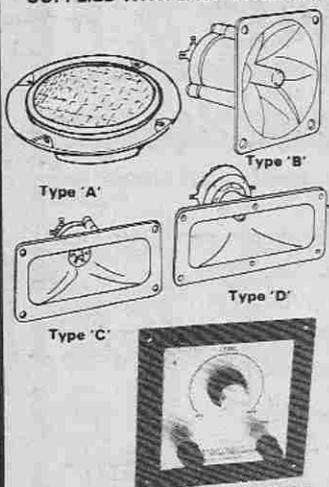Piezo Level Control/Loudspeaker Terminals. Combines two spring-loaded loudspeaker terminals, wire wound potentiometer and resistor network. All mounted on a smart brushed aluminium plate. Fits neatly through a 3" x 3" cut out on rear of speaker cabinet. **Price £2.99 + 20p postage and packing.**



GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3dB.

Tape Sensitivity: Output - typically 150 mV. Input - 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz - 108MHz Long wave 145kHz - 108kHz. Medium wave. 520kHz - 1620kHz. Short wave. 5.8MHz - 16MHz. **Size:** Tuner - 2 3/4" x 15in x 7 1/2 in approx. Power amplifier - 2in x 7 1/2 in x 4 1/2 in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £23.50 plus £2.50 postage and packing.**

JVC TURNTABLE. JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

- ★ 'S' shaped tone arm.
- ★ Belt driven.
- ★ Full size 12in platter.
- ★ Precision calibrated counterbalance weight (0-3 grms.)
- ★ Anti-skate (bias) device. Nylon thread weight.
- ★ Damped cueing lever.
- ★ 240V AC operation, (50Hz).
- ★ Cut-out template supplied.
- Size - 12 3/4 in x 15 3/4 in (approx).
- Price £28.50 plus £2.50 postage and packing.**



Matching 3-way loudspeakers and crossover

Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover


Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring-loaded loudspeaker terminals and recessed mounting panel.

Price £19.95 per kit + £2.50 postage and packing. Available separately, prices on request.

12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz. magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. **Attractive blue cone with aluminium centre dome.**

Price £16.49 ea + £2.50 P&P.

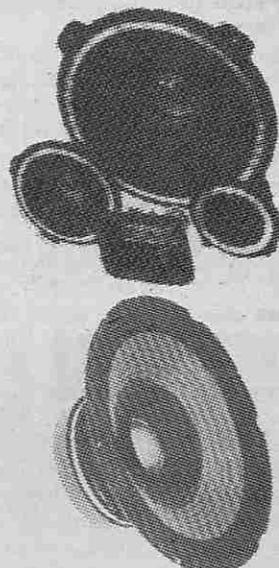

B.K. ELECTRONICS


37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



MICROPOWER PENDULUM

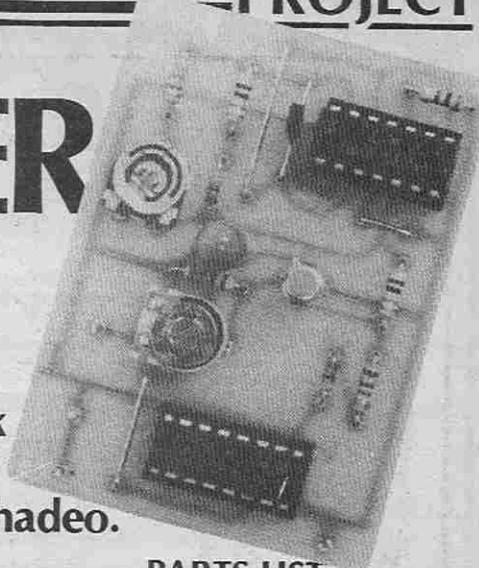Add a 'tick-tock' sound to your electronic clock with this amazing little module. Design by Ray Marston. Project development by Steve Ramsahadeo.



Modern electronic clocks are inexpensive and highly accurate devices, but lack the comforting 'tick-tock' sounds of old-fashioned mechanical timepieces. The 'tick-tock' sound of a clock confers two particular advantages. First, its rhythmic sounds are soothing and tend, at night, to help induce sleep; second, the sounds help the owner to easily locate the clock in a darkened room.

The little module described on this page enables you to add a 'tick-tock' sound to virtually any electronic clock. The unit consists of a low frequency micropower oscillator and divider circuit that has its output fed to a PB-2720 ceramic transducer, which generates the 'tick-tock' sounds. The unit can be operated from any supply in the range 4V5 to 12V; its total current consumption varies from 1 μ A at 4V5 to 5.5 μ A at 12 V. To put it another way, the unit will give a couple of years of continuous operation from a PP3 battery!

Construction

The complete circuit (other than the transducer) is built up on a small PCB and construction should present no problems. Note that three jumper links are used on the board and that C2 is a tantalum component. The use of mounting sockets for IC1 and IC2 is advised.

When construction is complete, fit the PB-2720 transducer in place and simply connect the unit to a battery and check that the tick-tock sound is generated. The tick-tock rate can be varied by PR1 and the volume by PR2: if you can't get the tick-tock rate low enough for your particular application, increase the C1 value to 100n.

The complete module can be powered from the existing clock supply rails (if they are in the 4V5 to 12 V range) or from its own PP3 battery. No on/off switch is needed in the supply line, since the current consumption is so low.

HOW IT WORKS

Circuit operation is quite simple. IC1 is configured as a special micropower oscillator (see this month's edition of Designer's Notebook) and produces a 300 μ s pulse at pin 12 roughly once every second; the rate can be varied over a limited range by PR1. This pulse is fed to the PB-2720 acoustic transducer via emitter follower Q1 and volume control PR2, and is also fed to the clock terminal of IC2, a 4017B divider chip. The 4017B is configured in the divide-by-two mode and its action is such that pin 2 switches between ground and supply voltage on alternate clock cycles.

Note that pin 2 of IC2 is connected to the base of emitter follower Q1 via R6 and D2. Thus, on the arrival of the 'tick' clock pulse pin 2 is high, so D2 is reverse biased and virtually the full clock pulse is fed to Q1 base (via R5), producing a loud 'tick' sound from the PB-2720. On the arrival of the 'tock' clock pulse, however, pin 2 of IC2 goes low and pulls R6 to ground via D2 so that R5-R6 act as a potential divider, thus causing only two-thirds of the clock pulse to reach Q1 base, and generating a softer 'tock' sound in the PB-2720. This process repeats ad infinitum.

Note that although the mean current consumption of the unit is only in the microamp range, the peak pulse currents feeding the ultra-efficient PB-2720 acoustic transducer may have amplitudes of several milliamps; the transducer thus produces 'tick-tock' sounds that are (if desired) clearly audible at a considerable range.

BUYLINES

There should be no problems obtaining any of the components used in the Pendulum. The PB-2720 transducer is available from Ambit International. The PCB for this project can be obtained from our PCB service — see page 54.

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)

R1	10M
R2,5	10k
R3	4M7
R4	100k
R6	22k

Potentiometers

PR1	4M7 miniature horizontal preset
PR2	22k miniature horizontal preset

Capacitors

C1	47n ceramic
C2	47 μ 16 V tantalum

Semiconductors

IC1	4007UB
IC2	4017B
Q1	BC109
D1,2	1N4148

Miscellaneous

TX1	PB-2720
PCB	(see Buylines); battery (4V5-12 V).

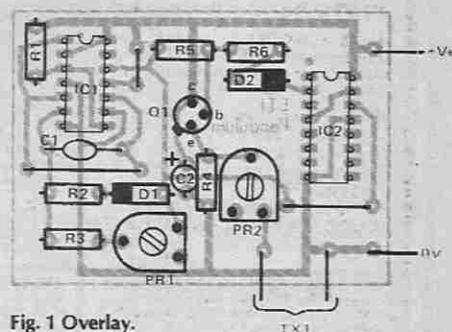


Fig. 1 Overlay.

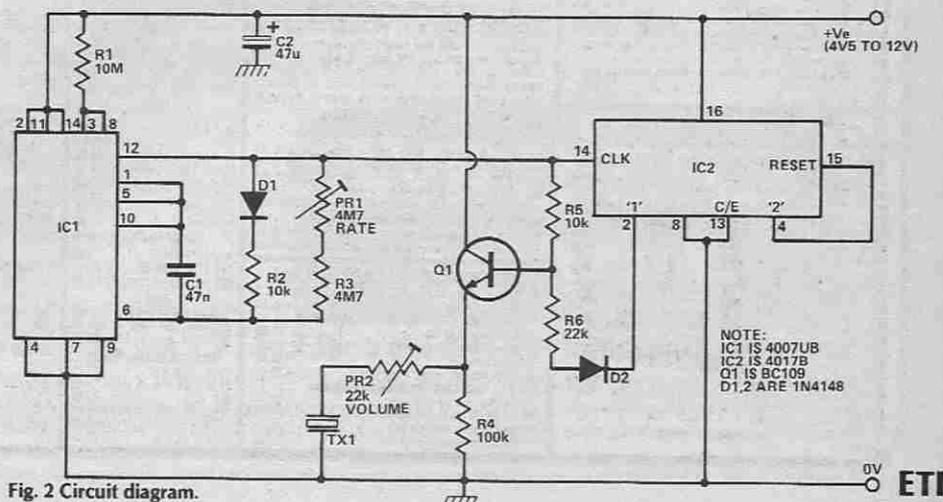


Fig. 2 Circuit diagram.

Greenbank

Greenbank Electronics
(Dept. T10E) 92 New Chester Road, New Ferry
Wirral, Merseyside, L62 5AG
(Tel: 051-645 3391)

TERMS, VAT, C.W.O. Cheques etc payable to Greenbank Electronics and crossed.
Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 40p
(+5p VAT = 45p) per order. Export: NO VAT but add 40p (Eire), E1 (Europe) and
£3.50 elsewhere. Access: Barclaycard, Visa, telephoned orders accepted.
(Polys, universities, gov depts. etc can telephone their orders for immediate
despatch on account.)



Offered as an alternative to the well-established International Size Computer Cards.

NEW EUROCARD 280 COMPUTER BOARDS CUSTOM 80 SYSTEM

★ 1 ★ SINGLE BOARD COLOUR VDU Teletext format, 24 lines of 40 characters, upper case/lower case/pixel graphics/flashing characters. Contiguous or Non-Contiguous, single/double height characters. Memory mapped. On board modulator for use with TV set (b/w or colour).

Full kit of parts £74.55 Order as CUSTOM 80 VDU KIT

★ 2 ★ KEYBOARD PORT. A circuit board for connection of ASCII keyboard, interrupt driven, uses powerful 280 mode 2 vectored interrupts. Includes 1K RAM, space for 2K ROM (both of which can be switched using software).

Full kit of parts £49.25 Order as CUSTOM 80 KBP KIT

★ 3 ★ CPU powerful high-speed 280A processor, operates at full 4MHz. Can insert wait states when requested. Halt indicator, pulsed reset permits use with dynamic RAMs, 5 output buffers connect to BUS (NOT ADD ON!).

Full kit of parts £43.22 Order as CUSTOM 80 CPU KIT

★ 4 ★ MOTHERBOARD KIT. 10 slot backboard (kit includes 5 DIN 41612 Eurocard sockets type 64/96 using rows a and c). Provision for ±5V and ±12V, incorporates two daisy chain lines for interrupt priority and bus priority. Kit price includes the following: PCB, 2 mounting rails, 5 DIN 64/96 sockets, fixings for up to 10 sockets, and fixings to fit rails to card frame, and documentation.

Kit of parts £34.09. Order as CUSTOM 80 MICRO BUS KIT.

★ 5 ★ 32K DYNAMIC RAM. This board uses 280 refresh. 32K of 4116s can be located on 4K boundaries. 20 Decoded address lines decoded for 1M byte (1024K bytes). Note full kit of parts (includes all memory devices) £65. Order as CUSTOM 80 RAM KIT

All kits of parts include full instructions, circuit diagrams, components and ic sockets, nuts, bolts, washers and Eurocard plug and card front where appropriate.

★ 6 ★ SOFTWARE. Powerful CSYS operating system and De-Bug package fits in sockets on KBP circuit board; requires minimum of 1K ram, comprehensive instructions included. A fully commented listing is available at extra charge.

CSYS FIRMWARE £24

CSYS LISTING £5. (only available to purchasers of CSYS firmware)

COMING SOON: Dual CUTS tape interface, selectable baud rates.

IN DEVELOPMENT: Floppy DISK interface.

S.a.e. for free leaflet.

CMOS

These cut prices for Amateur Users and Export.
Note: Industrial users - quantity prices available.
Mostly Motorola, RCA


4000	18p	4042	80p	4095	£1.97	4411	£10.72	4532	£1.30
4001	25p	4043	90p	4096	£1.97	4420P	£14.93	4534	£5.60
4002	25p	4044	90p	4097	£5.98	4425V	£5.24	4536	£3.60
4006	90p	4045	£2.63	4098	£1.92	4427	£5.56	4537L	£26.10
4007	18p	4046	£1.10	4099	£2.00	4433	£12.30	4538	£1.20
4008	80p	4047	£1.10	4100	£1.92	4435V	£5.40	4539	97p
4009	40p	4048	77p	4101	£1.69	4450	£3.81	4541	191p
4010	50p	4049	45p	4102	£3.67	4461	£3.93	4543	£1.80
4011	25p	4050	49p	4103	£3.87	4463	£4.41	4545	£4.38
4012	18p	4051	90p	4104	£1.54	4467	£4.20	4552	£14.45
4013	50p	4052	80p	4105	£1.85	4469P	£4.20	4554	£1.50
4014	84p	4053	80p	4106	99p	4470	£5.95	4554	£4.58
4015	84p	4054	£2.18	4107	£1.28	4501	29p	4555	78p
4016	45p	4055	£2.55	4108	£7.56	4502	£1.20	4556	72p
4017	80p	4056	£2.55	4109	£1.28	4503	78p	4557	£2.52
4018	80p	4057	£3.23	4110	£3.00	4504	£5.71	4558	£1.25
4019	45p	4058	£2.10	4111	£1.77	4505	50p	4559	£4.38
4020	99p	4059	£1.00	4112	£1.54	4507	55p	4560	£2.50
4021	£1.10	4063	£1.00	4113	£1.54	4508	£2.90	4561	81p
4022	£1.00	4066	55p	4114	£1.54	4510	99p	4566	£1.99
4023	27p	4067	£7.21	4115	£1.54	4511	99p	4566	£1.99
4024	79p	4068	27p	4116	£1.54	4512	80p	4568	£2.38
4025	27p	4069	27p	4117	£1.54	4513	80p	4569	£2.50
4026	£3.25	4070	30p	4118	£5.03	4513	£2.11	4569	£2.50
4027	50p	4071	25p	4119	£2.41	4514	£2.65	4572	40p
4028	84p	4072	25p	4120	£2.41	4515	£3.00	4580	£4.77
4029	90p	4073	25p	4121	£2.41	4516	£1.10	4582	£1.14
4030	74p	4074	25p	4122	£3.27	4517	£4.46	4583	90p
4031	£4.31	4075	£1.10	4123	£3.27	4518	£1.00	4584	90p
4032	£1.31	4077	29p	4124	£1.00	4520	£1.00	4585	£1.27
4033	£2.63	4078	29p	4125	£1.00	4521	£2.50	4597	£2.44
4034	£2.00	4081	27p	4126	99p	4522	£1.11	4598	£2.98
4035	£1.10	4082	27p	4127	99p	4523	£1.11	4599	£6.85
4036	£1.99	4083	£1.35	4128	99p	4527	50p	4700	£1.75
4037	£1.20	4084	£2.31	4129	£1.15	4528	£1.20	1CM7038A	£4.25
4038	£2.78	4085	£2.91	4130	£1.15	4529	£1.30		
4040	£1.00	4093	90p	4131	£3.57	4530	70p		
4041	£1.59	4094	£2.90	4132	£3.57	4531	£1.45		

74C

74C00	29p	74C16	£1.15	74C24	57p	74C32	£5.99
74C01	29p	74C17	£1.15	74C25	57p	74C33	£5.99
74C02	29p	74C18	£1.15	74C26	57p	74C34	£5.99
74C03	29p	74C19	£1.15	74C27	57p	74C35	£5.99
74C04	29p	74C20	£1.15	74C28	57p	74C36	£5.99
74C05	29p	74C21	£1.15	74C29	57p	74C37	£5.99
74C06	29p	74C22	£1.15	74C30	57p	74C38	£5.99
74C07	29p	74C23	£1.15	74C31	57p	74C39	£5.99
74C08	29p	74C24	£1.15	74C32	57p	74C40	£5.99
74C09	29p	74C25	£1.15	74C33	57p	74C41	£5.99
74C10	29p	74C26	£1.15	74C34	57p	74C42	£5.99
74C11	29p	74C27	£1.15	74C35	57p	74C43	£5.99
74C12	29p	74C28	£1.15	74C36	57p	74C44	£5.99
74C84	29p	74C100	£1.15	74C108	57p	74C116	£5.99
74C85	29p	74C101	£1.15				

OHIO SCIENTIFIC COMPUTERS

Our prices are so low we dare not print them! Special offer: Superboard 3 + free Cegmon monitor **poa**. Superboard 3 + free power supply, modulator and guard band kits **poa**. Series 2: Challenger **poa**. Power supply kit **£11.95**. Modulator **£3.50**. Guard band kit **£10**. 4K extra ram **£10.90**. Case **£27**. Cegmon **£22.50**. Wemon **£19.95**. Assembler/Editor tape **£25**. Word processor program **£10**. Display expansion kit for Superboard 2 series 1 only **£14**. Centronics interface kit **£10**. 810 expansion board **poa**. Cased minifloppy disc drive with DOS and psu **poa**. Cassette recorder **£19**. Colour adaptor board built **£65**.

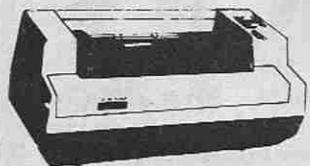VIDEO GENIE £289**PRINTERS**

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard:

Epson MX70 **£259**. Epson MX80T **£359**. Epson MX80F/T1 **£399**. Epson MX80F/T2 **£449**. Epson MX100 **£575**. OKI Microline 80 **£299**. OKI Microline 82A **£399**. OKI Microline 83A **£699**. OKI Microline 82 **£399**. OKI Microline 83 **£699**. Centronics 737 **£395**. Seikosha GP80A **£199**.

TV GAMES*

AY-3-8600 + kit **£12.98**. AY-3-8550 + kit **£9.26**.

SWANLEY ELECTRONICS

Dept. ETI, 32 Godsel Road, Swanley
Kent BR8 8EZ
Tel: Swanley (0322) 64851

SINCLAIR PRODUCTS*

Sinclair products only are all post free. SC110 Oscilloscope **£158.95**, adaptor **£5.69**, rechargeable batteries **£8.63**, x1 probe **£9.78**, x10 probe **£11.50**, carry case **£8.86**. PFM200 **£57.27**, adaptor **£5.69**, case **£3.45**, connector kit **£11.27**. PDM35 **£32.95**, adaptor **£5.69**, case **£3.45**. DM225 **£80.98**. DM350 **£87.38**. DM450 **£136.85**, adaptor **£5.69**, case **£8.86**, rechargeable batts. **£8.63**. Microvision TV **£89**, adaptor **£5.95**. TM352 **£54.95**. TM354 **£46.95**.

BATTERY ELIMINATORS*

3-way type 6/7.5/8V 300ma **£3.50**. 100ma radio types with press studs 9V **£4.95**. 9-9V **£6.25**. Car converter 12V input, output 3/4.5/6/7.5/9V **£8.04** **£3.04**.

BATTERY ELIMINATOR KITS*

100 ma radio types with press-studs 9V **£1.79**, 9-9V **£2.50**. Stabilised 8-way types 3/4.5/6/7.5/9/12/15/18V 100ma **£3.12**. 1 Amp **£8.50**. Stabilised power kits 2-15V 100ma **£3.12**. 1-30V 1A **£8.50**. 1-30V 2A **£15.30**. TTL and computer supplies 5V stabilised 1.5A **£9**, 3A **£14**, 6A **£22**. 12V car converters 6/7.5/9V 1A **£1.62**.

SHARP COMPUTERS


M280K 20K **£418**, 36K **£440**, 48K **£460**. PC1211 **£82**.

**BI-PAK AUDIO MODULES***

AL30A **£4.35**. PS12 **£9.31**. PS12 **£1.75**. T536 **£2.90**. S450 **£27.90**. AL60 **£5.82**. PA100 **£19.94**. SPM80 **£5.26**. BMT80 **£6.36**. Stereo 30 **£23.14**. AL80 **£8.56**.

VIC 20 COMPUTERS

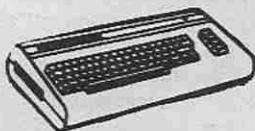Our prices are the lowest yet. Ring for a quote.



Postage **£3.50** on computers, **£4.50** on printers and 45p on other orders. Lists 27p post free. Please add VAT to all prices except those sections marked with a * which already include it. Overseas and credit official orders welcome.

Quality support for; ATOM**ZX80 ACTION !**

2 games per cassette - for only **£4!!**

**ZX80
ZX81**

Flicker-free action games for your ZX80.

Only 1K RAM needed, and the original (4K) ROM.

Cassette C80A: **BRKOUT** ----- **ACK-ACK** **£4-**

Cassette C80B: **SHELL GAME** ---- **INVADERS** **£4-**

The ZX80 Magic Book

** WITH 8K ROM / ZX81 SUPPLEMENT **

Games programs, computer music, converting programs written in other BASICs. Improving the picture, RAM and I/O circuits, and much more. **£4.75**

Getting Acquainted with your ZX81

A Tim Hartnell masterpiece. **£4.95**

23+23 WAY ZX80/81 EDGE CONNECTOR SOCKET **£3.50**

ATOM CASSETTES ; £5 each

CAAA: **BREAKOUT + CUPBALL + 3D MAZE + SIMON 2**

CAAB: **PINBALL + LETTERS + SPACEWAR + DRIVE**

Both tapes need 1K VDU + 5K text RAM

The ATOM Magic Book

A wealth of games and other programs; storing speech in your ATOM, converting programs written in other BASICs, tape recording hints, plus many other useful hardware and software tips. **£5.50**

16/32K ATOM RAM Boards

from **£59.50**

Single Eurocard, can fit inside Atom's case. Built & tested. Also suitable for other 6502/6800 computers. Bare PCB only **£23**. S.a.e. for further details

ALL PRICES INCLUDE U.K. P&P + VAT WHERE APPLICABLE

TIME DATA Ltd.

57 Swallowdale, Basildon, Essex

Look out for Wireless World's striking front cover.

Editorial now includes electronics, radio, audio, video and computing.

**FREE THIS MONTH**

Exclusive reprint of Arthur C. Clarke's 1945 article on satellite broadcasting.

PLUS

Hi-Fi Article—how to distinguish between amplifier and loudspeaker sound.

Micro Article—how to connect microprocessors to other electrical/electronic equipment.

Many other regular articles including world of amateur radio, news of the month, circuit ideas, new products and job opportunities.

wireless world

Electronics • Television • Radio • Audio

October issue out now only 70p.



dbx NOISE REDUCTION

Overshadowed by Dolby despite its theoretical superiority, the dbx noise reduction system now seems poised to take the hi-fi market by storm. Peter Green was at the press launch and this is what he heard.

Until now it has been impossible to listen to music at home with anything like the quality of the original. However much you spend on your hi-fi, however low the distortion figures, however carefully you tend your records and however diligently you clean your tape heads, you cannot get away from the twin evils of surface noise and restricted dynamic range.

Surface noise is caused by the limited quality of the recording medium itself. Imperfections and inhomogeneity in the particles that make up the tape coating generate the familiar hissing we know and hate; the roughness of the vinyl surfaces of record grooves produces its share of hissing and pops. Surface noise also affects dynamic range. During a live performance it is possible for sound pressure levels to momentarily hit 120 dB during music transients; however, background noise levels in the audience can easily range from 30 to 50 dB and so this simplistic treatment indicates that live music has a perceived dynamic range of about 70 to 90 dB. Unfortunately a good cassette recorder has a dynamic range of only about 45 dB, while a conventional vinyl record is not much better at 55 dB. Recording engineers have to compress the signal by a factor of 2:1 so that the loudest passages are below the level that causes tape saturation or distortion, and the quietest passages are above the level of tape hiss or record surface noise (see Fig. 1). This squeezing of the signal into a restricted dynamic range makes the music sound flat, unexciting and unrealistic. You know it's a recording.

D Versus d

The noise reduction system that established a virtual monopoly in the world hi-fi market of the seventies was Dolby B, a system that reduced high frequency noise (the most objectionable kind) by boosting high frequencies on recording and attenuating them on playback, thus also reducing the noise added in the recording process.

dbx decided to tackle the other problem — restricted dynamic range. Since sounds have to be compressed to be recorded on tape or disc, a system that allowed 1:2 expansion on playback would recreate the range of the original performance (Fig. 2). This idea is quite old but difficult to apply, because the expander and compressor must track each other (be exactly complementary), especially on transients — this in turn requires accurate detection of the signal. The difficulties in this and the way that dbx overcame them are described later, but the important point is that when the recorded signal is ex-


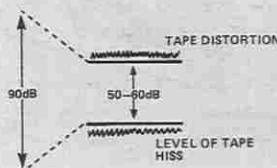


Fig. 1 (left) When recording tapes or discs, engineers monitor the signal and turn the level up or down ('gain riding') to avoid distortion or hiss. This compression greatly reduces the dynamic range to an absolute maximum of about 60 dB.

Fig. 2 (right) By introducing 2:1 compression on recording, then accurately and automatically reversing the process on playback, the dbx noise reduction system reclaims the original dynamic range. As a bonus, tape hiss becomes inaudible.

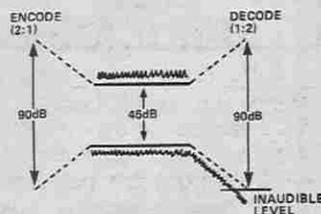

panded the tape noise drops below the level of audibility. dbx have killed two birds with one stone, together with an assortment of sacred cows; for example, they recommend that you use chromium dioxide rather than metal tapes, because it's pointless to pay extra money for an improvement of 2 to 3 dB when the system itself is giving you an extra 30 dB across the whole frequency range.

Paths Of Glory

Figure 3 shows the block diagram of a Type II dbx noise reduction system for domestic use (the Type I system has certain differences in the turnover frequencies of the filters to suit professional situations). The encoder and decoder each have two paths — the signal and detection paths.

The music signal to be recorded first goes through a band pass filter to remove unwanted out-of-band components. Type II values are 30 Hz to 100 kHz, Type I are 22 Hz to 27 kHz. The lower limit is there to prevent subsonic noise from underground trains, traffic vibrations and the like from being recorded; the upper limit prevents pick-up of CB and other interference. The Type I value is much lower because studios often have very long leads which are more susceptible to pick-up. The signal passes through a pre-emphasis network that boosts high frequencies and helps to overcome tape modulation noise (which is caused by uneven magnetisation due to tape inconsistency), and into the voltage-controlled amplifier. The VCA is linear in dB with control voltage to make things simpler later on; it compresses the signal by a 2:1 ratio.

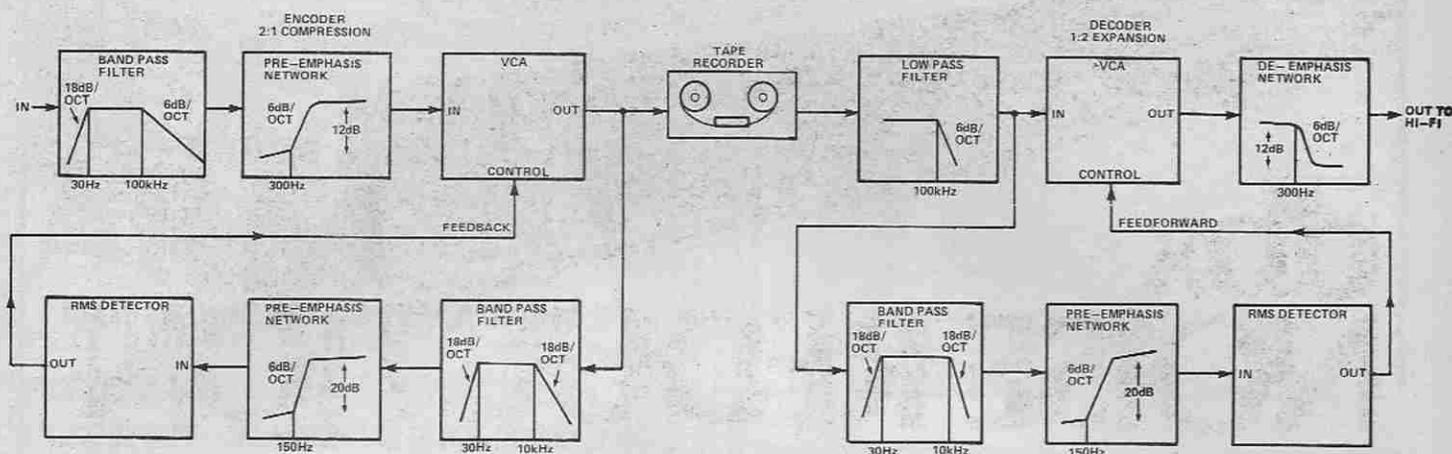


Fig. 3 Block diagram of the Type II dbx noise reduction system.

The output of the VCA is passed to the tape recorder, and also into the detector section. The first stage is a band pass filter which has a slope of 18 dB/octave above 10 kHz, so that the detector 'takes less notice' of high frequencies. Next comes another pre-emphasis network, this time to increase the compression of the signal at high frequencies and avoid the possibility that the pre-emphasis in the signal path will cause high-frequency tape saturation. The RMS detector converts the AC signal into a DC voltage proportional to the level in dB; since the VCA also follows this law the whole system is linear in dB.

Mirror, Mirror

The encoder is a compressor with negative feedback; the higher the signal level the greater the gain reduction. The decoder must be a mirror image to give the correct tracking and recovery of the original performance, so it is configured as a feedforward system acting as a 1:2 expander. The importance of this is that if the tape recorder is considered to be 'transparent', the VCA control voltage in the decoder is being derived from exactly the same signal as that for the encoder VCA. The detector path in the decoder is identical to the one already described — band pass filter, pre-emphasis network, RMS detector — and so the control signals will also be identical (to within component tolerances). The decoder VCA has its control polarity reversed and gives a complementary gain change to that of the encoder; the de-emphasis network reverses the effect of the encoder pre-emphasis to restore a flat overall frequency response. It's interesting to note that this flat system response is due solely to the mirror-image nature of the signal processing — the frequency responses of encoder and decoder are complementary, but not flat.

Because a high value of loop gain (40 dB) is employed in the decoder, a low pass filter is needed at the input to prevent high-frequency oscillation caused by capacitive coupling. This keeps the system stable.

RMS detectors have been used because tape recorders aren't perfect, or 'transparent' — they introduce huge amounts

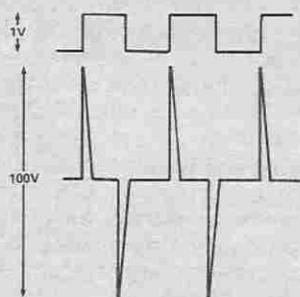


Fig. 4 Phase shift can have dramatic effects on the shape of waveforms!
ETI OCTOBER 1981

of phase shift. This is not noticeable to the ear, but the effect of passing a 1 V peak-to-peak square wave through a 90° phase shift filter is shown in Fig. 4; cheaper and simpler detectors such as peak or averaging types would not give identical outputs for the two waveforms and the mirror-imaging would be lost. An RMS detector is the only one that will give the same output level for both.

Silence Is Golden

If anyone feels that the working of the system is hard to understand, rest assured that a practical demonstration isn't. The press showing started with a hiss comparison using blank unencoded tape, first with no noise reduction, then Dolby B, Dolby C and finally dbx. Hiss was still significant with the two Dolby systems, although the improvement was noticeable — but when the dbx cut in, nothing could be heard except the gasps of amazement from hardened journalists. No hiss whatsoever! Listening to extracts from discs and tapes was a revelation; for the first time in my life I could shut my eyes and believe the orchestra was really there. I heard musicians fingering their instruments, I heard someone on the record sniff, and the music appeared out of a silent background — it was real!

Naturally the impact dbx has on the market will depend on how many encoded discs and tapes they can release, and how quickly. But several major cassette deck manufacturers (eg Technics, Trio, Teac, Yamaha, Marantz) are fitting dbx alongside Dolby in some of their models, and Dolby must be thinking hard about their next move. (At ETI we're thinking about how nice a review model would be, hint, hint!) With approximate RRP's of £120 for the Model 222 (for two head tape decks) and £170 for the Model 224 (three head decks), a dbx noise reduction system could be the best upgrade you'll ever make.

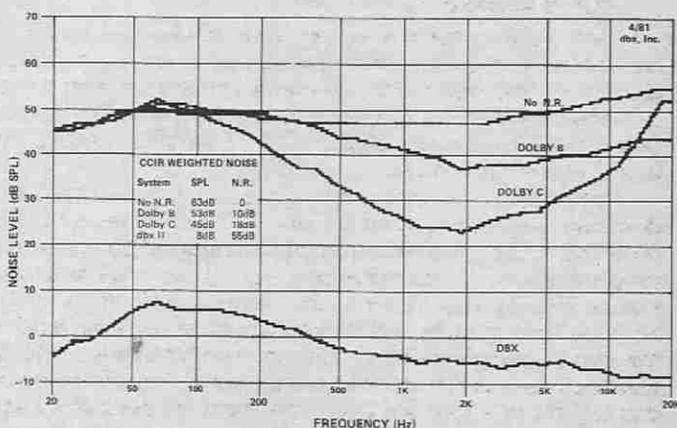


Fig. 5 A comparison graph of noise reduction systems, issued by dbx.

ETI

SUPER VALUE PACKS AND COMPONENTS

P1. 50 Ass. Electrolytics Caps. 80p	P 9 20 High Voltage Discs. 1KV-8KV. 27pf-470pf 80p
P2. 80 Polyester, Polycarbonate, Polypropylene 80p	P10 18 High Voltage Discs 1KV-8KV 1000pf-01uf 80p
P3. 100 Small Cer. Discs 80p	P11 10 20mm in line fuse holders 80p
P4. 80 Square Cer. Plates 80p	P12 10 5 pin din chassis sockets 80p
P5. 50 Polystyrene Caps. 5.6pf-3900pf 80p	P13 150 Axial 1/4 watt resistors 80p
P6. 45 Polystyrene Caps. 4700pf-047uf 80p	P14 5 100K Multitone trimmers for Thorn Varicap tuners 80p
P7. 20 Silver Mica 5.6pf-220pf 80p	P15 One of each Tant Bead Cap. as listed below. Qty. 20. £3.50
P 8 18 Silver Mica 270pf-0047uf 80p	

DIODES 1N4001: .04p. 1N4002: .04p. 1N4003: .04p. 1N4004: .05p. 1N4005: .05p. OA90: .08p. OA91: .06p.

TANT BEAD CAPACITORS

1/35v .22/35v .33/35v .47/35v .68/35v 1/35v 10p each	
2.2/16v 3.3/16v 4.7/16v 12p	4.7/35v 6.8/25v 14p
6.8/35v 15p	10/16v 16p
22/16v 25p	33/10v 25p
100/16v 50p	47/16v 50p
Polystyrene Caps. from .03p	Low Voltage discs from .03p
Silver Mica from .10p	Etc. etc. Lists enclosed with first order or S.A.E.

Post and packing add .20p per pack or .20p on orders for components only. Orders over £5.00 post free. VAT inclusive. C.H.J. SUPPLIES, 4 STATION ROAD, CUFFLEY, HERTS. Tel: 01-440 8959

STOP PRESS MAPLIN ROAD SHOWS

DEMONSTRATION OF MATINÉE ORGAN AND ATARI PERSONAL COMPUTER

Friday 25th September Grainger Room Newcastle Centre Hotel New Bridge Street, Newcastle-upon-Tyne	Saturday 26th September Rosebery Room Grosvenor Centre Hotel Grosvenor Street, Edinburgh	Sunday 27th September Ullswater Room Portland Hotel 3 Portland Street Piccadilly Gardens Manchester
--	---	---

Tuesday 29th September The Riverside Suite Hotel Nelson Prince of Wales Road Norwich	Monday 28th September The Malvern Suite Birmingham Centre Hotel New Street Birmingham
---	--

For further details telephone **MAPLIN 0702 554155**

ETCH RESIST TRANSFER

KIT SIZE 1:1

Complete kit 13 sheets 6in. x 4 1/2in. £3, with all symbols for direct application to P.C. board. Individual sheets 30p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Leads and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8-10-12 T.O.5 Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

MAIL ORDER PC BOARD

2" x 8" 12 pieces for	£1.00 post 50p
3" x 8" 7 pieces for	£1.00 post 50p
4" x 8" 6 pieces for	£1.00 post 50p
6" x 8" 4 pieces for	£1.00 post 50p
8" x 8" 3 pieces for	£1.00 post 50p

Some double-sided, same price also 3/32" ss

PLAIN PAXOLIN INSULATION BOARD

1/32" 4" x 8" 10 pieces for	£1.00 post 50p
1/16" 4" x 8" 6 pieces for	£1.00 post 50p

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black or white. Size of sheet 12" x 9". Price £1.20.

GRAPHIC TRANSFERS WITH SPACE ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12" x 9" contains capitals, lower case and numerals 1/4" kit or 1/4" kit. £1.20 complete. State size.

All orders despatched promptly. All post paid

Shop and Trade enquiries welcome. Special Transfers made to order

E. R. NICHOLLS

P.C.B. TRANSFERS

DEPT. ETI.10, 46 LOWFIELD ROAD
STOCKPORT, CHESHIRE. 061-480 2179

TTL
CMOS
74LS
LEDS

LB ELECTRONICS

LINEAR
RAMS
EPROMS
SURPLUS

TELEPHONE:
UXBRIDGE 55399

SUPERSALE '81
All full spec. 2114 (450ns) £1.50, 8 of £1.40 each. P&P 35p. 2708 £2 p&p 35p. TEXAS INSTRUMENTS 2716 single rail full spec. £3.80. ITT 4116 (200ns) £1.35, 8 for £1.15 each. Texas 4116 (250ns) £1, p&p 35p.
PORTABLE DATA TERMINAL. Transdata 305 thermal portable printer. Built-in acoustic modem, 80 columns, 94 characters, upper and lower. ASCII 100, 110, 300 Baud. V24 interface, supplied fully working £185. Weight 22lbs - carriage at cost. Leaflet, s.a.e.
MK 1002P (dual 128 bit Shift Reg) 35p.
UA710DC 14 dil 22p, 6 for £1, p&p 30p. (All Full Spec)
2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 35p.
MM5240 AA/3 Character Generator £3.50 + data. p/p 35p.
LEAR SIEGLER dot matrix print-head, 7 needle. £19.50 p/p 50p.
ZETTLER low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.5amps a.c. contacts. 85p p/p 35p.

D TYPE CONNECTORS
9 Way: sockets (solder) 55p.
15 Way: wirewrap plugs only 75p.
15 Way Plugs 85p.
15 Way Sockets 70p.
50 Way Plug £1.65
50 Way: skt (wirewrap) £1.65.
50 Way: skt £1.45, p&p 25p.
25 Way plug (solder/call), 25 Way socket £1.50 each.

COVERS
37 Way: 90p (plastic), p&p 35p.
9 Way (metal) 60p, 15 Way (metal) 95p, 25 Way (open metal) 85p, 37 Way reduced from 90p to 80p. 50 Way (plastic) 90p.

DISPLAYS
HP 5082/7414.4 digit DIL display full spec £1.50 each, p&p 35p. Large quantities POA.
LED 3 Digit DIL 55p, p&p 35p.

HP5082/7650 .4" cc, left and right decimal point, high brightness (unmarked), only 50p, 12 for £5, p&p 35p.

SUPERSAVER 1
Ribbon Cable Headers 16 DIL Jermyn, gold-plated, with cover 45p, p&p 25p.

Ansley Header plugs. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing type) p/p 35p.

Ansley I/O Header plugs PCB Mounting 1in 26 Way 65p, 26 Way (right-angled) 85p, 40 Way £1 p/p 35p. SUPERSAVER 2
Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.

SUPERSAVER 3
PRICE SMASH FND500 .5in. LED displays, full spec 50p each, p&p 35p, large quantities POA. **SUPERSAVER 5**
Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.

SUPERSAVER 6
EAO KEY SWITCH oblong fascia, 25mm x 18mm (approx. 18mm hole), fixing supplied, brand new with 2 keys. £2.95 p&p 35p.

SUPERSAVER 7
SN74116 Dual 4 Bit latch 75p, p&p 35p.
SN74118 Arithmetic Logic Unit, 80p, p&p 35p.
SN74194 4 Bit Reg 50p p&p 35p.
SN74198 8 Bit Shift Register, 75p p&p 35p.

SUPERSAVER 8
ITT 4cx 250b brand new full spec £7.50 each p&p 35p.

SUPERSAVER 9
5 digit 7 segment DIL LED .11" displays 5 for £1.50 p/p 35p.

SUPERSAVER 10
9-way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, 35p, p&p 35p.

SUPERSAVER 11
74LS266 50p. 74LS245 £2.40. 74LS240 80p. 74S260 35p. P&P on all above 35p.

SUPERSAVER 12
CHROME CAPPED KNOBS 18mm dia. 1/4" spindle, Shaft 18mm long. 12 for £2.00. FREE POSTAGE.

SUPERSAVER 14
BOX FANS 115V 50/60Hz. 120mm x 120mm. New. £4.50. P/P £1.00.

SUPERSAVER 15
5K 3/4" multiturn trimmots, PCB mounting, per box of 14 £2.50. As above 1K and 50K, p&p 35p.

SUPERSAVER 16
OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1, p&p 35p.

SUPERSAVER 17
VU METER 48mm x 50mm approx. overall size. Face size 50mm x 28mm approx. Brand new. £1.15 p&p 30p. (Sent at purchaser's risk).

SUPERSAVER 18
PCB AMP (LM380). Unused. 65mm x 95mm approx. 9-12V DC. £1.35 p&p 35p.

SUPERSAVER 19
10 DIGIT (Red). LED display. (.122in. digit size). With built-in driver chip and built-in lens magnifier. Data sheet supplied. Brand new. £2.50 p&p 35p.

SUPERSAVER 20
4 1/2in. JUMPER LEAD. 16 DIL header to 16 DIL header. 95p p&p 30p.

SUPERSAVER 21
2 1/2in. JUMPER LEAD. 14 DIL header to 14 DIL header. 65p p&p 30p.

SUPERSAVER 22
1lb reel of solder 18 SWG 64/36 alloy £6.50 p&p 90p.

A SUMMER GIVEAWAY. 280 P/O. Only £3.75 p&p 35p. MC1489 Brand new 46p each. Large quantities P.O.A. p&p 30p.

NICADS AA SIZE - 500 MAH 1-25v rechargeable 50 milliamp 12-15 hours. £1.44, P&P 35p.

TMS 4030, 4096 x 1 dynamic RAM 200 ns removed from PCBs. 65p each. 16 for £6, p&p 35p.

GPO LINE MATCHING TRANSFORMER. With 12V reed relay etc. removed from equipment. £1 + 40p p&p.

CAPACITOR SCOOP. 1.600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 - 35p p&p.

DON'T KILL YOUR EPROMS. Augat 24 Way low profile socket. Solid gold pins. A superb socket. Leave your eproms in them for programming or usage to prevent breaking off pins. Only 40p each, p&p 35p.

GIVEAWAY 18 pin low profile dil socket 13p EACH or 8 for £1

AUGAT IC SOCKETS
(The best available)

16 Dil 20p	24 Dil 40p
18 Dil 25p	40 Dil 55p
20 Dil 30p	p&p 35p.

WE STOCK a vast range of TTL, CMOS, some 74LS, MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

NEW LINES
GUEST (gold plated) IC test clip. 40 way, 28 way £4.50 per pair. P/P 50p.

REG PCB (less components), 5V 1 amp, 12V 1 amp and heatsink (60mm x 90mm). Brand new, £1.00. Heatsink only, 55p. P/P 35p.

NEC FIP4B13 4 digit glass display (green with centre colour) and plus and minus sign, only £1.35. P/P 30p.

PL259 SOCKET CHASSIS MOUNT. 50p p&p 30p.

TRANSFORMERS 012, 024 1 amp £2.50, P&P 50p. 012.5 0.92 amp £2.50, P&P 50p.

TTL SALE 7410 9p, 7413 18p, 7416 18p, 7490 28p, 74155 45p, 74174 60p, 74181 £1, 74284 28p, 74285 £2.25. P&P 35p.

WHY PAY POUNDS? - Just arrived Amphenol 36-way plug and socket (used) to fit all your printer. Only £2.75 per pair. P/P 35p.

Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

BURROUGHS keyboard, 96 key station. On-board crystal and TTL. Brand new and boxed. 500mm x 190mm. At the time of advert no data. No keytops at all. Clare pender. Reed switches. Bargain £12 each, p&p £1.50.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.

SURPLUS STOCKS
PURCHASED FOR CASH

LB ELECTRONICS
11 HERCULES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND

All enquiries s.a.e. please
Telephone answering machine service out of business hours.

New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.

ALL PRICES INCLUSIVE OF VAT
UXBRIDGE 55399
All components full spec.

ROBOT ARM

Part 2 of the Armdroid project gives the complete constructional details of the electronics. System concept by Ron Harris. Realisation and development by Ajit Channe, Nick Ouroussoff and Andrew Lennard.

This month we give the Parts Lists and overlays for the Armdroid, plus a few things we have to point out. A large number of supply decoupling capacitors are required on the interface board — for clarity these were not shown on last month's circuit diagram, but they appear as C2-14 in Fig. 3. Figure 3 also includes two extra resistors which experience has shown to be necessary

On the motor driver board, there are four spare pads to the left of each IC4. These may be used to directly connect control signals from the outputs of the latches on the interface board, if direct computer control of the stepper coils is desired as mentioned last month.

Finally, Colne Robotics are continuing development work on the gripper, and invite suggestions for alternative designs. If you think you've got a good idea (some possibilities are mentioned in Robotics Today this month), get in touch with Colne at the address given in Buylines last month. If they like your proposal they're prepared to do the development and engineering work and pay the inventor a royalty. Over to you!

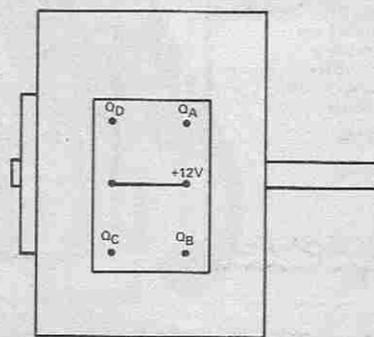
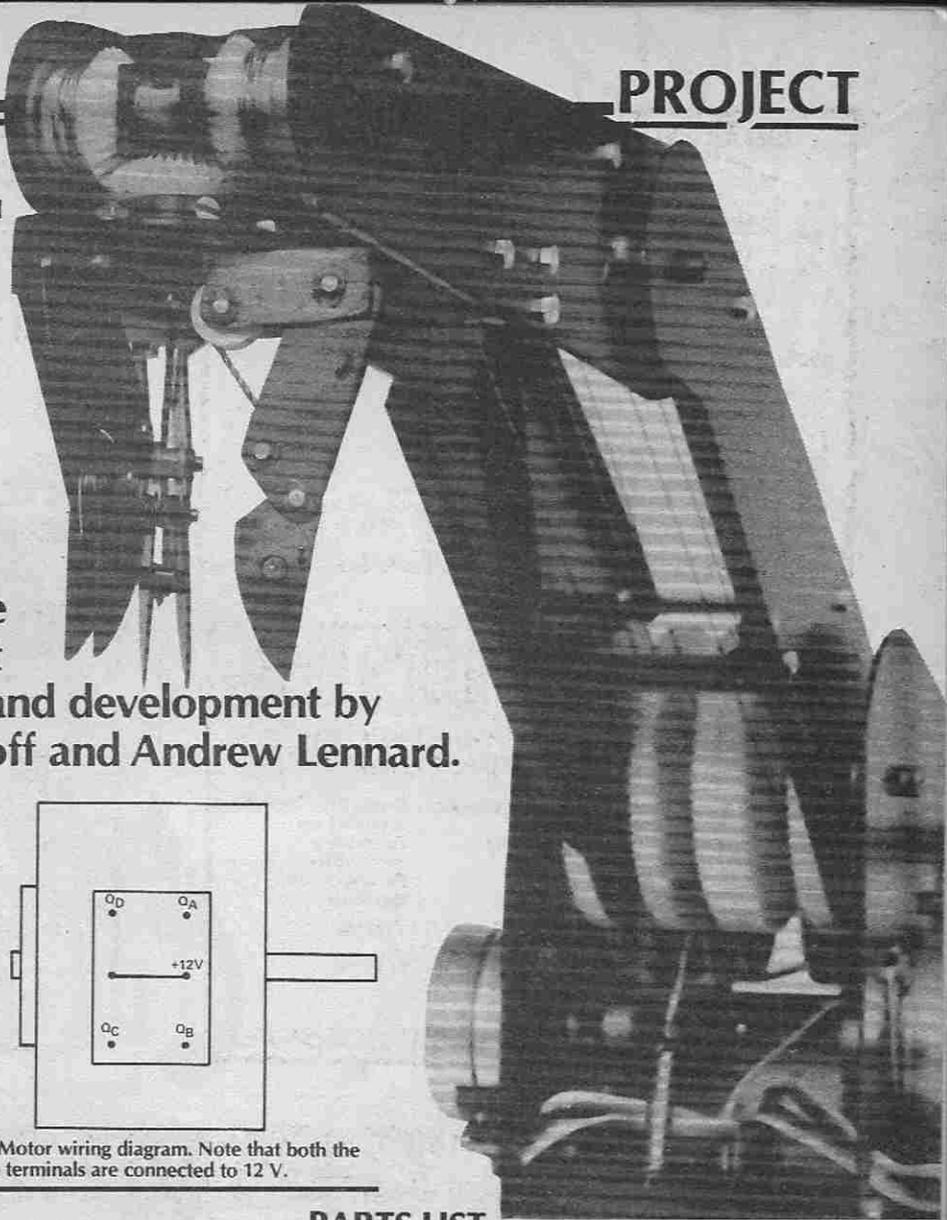


Fig. 1 Motor wiring diagram. Note that both the centre terminals are connected to 12 V.

PARTS LIST

POWER SUPPLY

Resistors (all 1/4 W, 5%)

R1 4k7

Capacitors

C1,2 4700u 25 V axial electrolytic

C3,4 1u0 35 V tantalum

C5 220n polyester

Semiconductors

IC1 78H12

IC2 7805

BR1 200 V, 6 A bridge rectifier

TS1 240 V AC transient suppressor

Miscellaneous

SW1 mains switch

T1 12 V, 50 VA


LP1 12 V, 50 VA

LP1 neon lamp

FS1 1 A fuse

Heatsink (drilled for T03 case)

Fig. 2 Overlay for the PSU. Note that IC1 requires a heatsink.

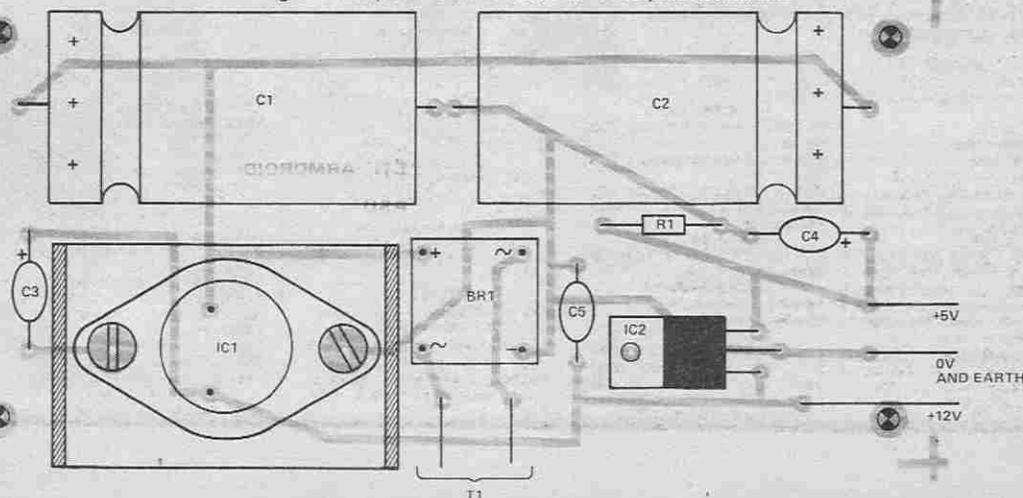

WIN £100!
2nd PRIZE £25
3rd PRIZE £10

ROBOT PROGRAM COMPETITION FREE ENTRY!

Here's a chance for all you would-be robotists and programmers to earn yourselves £100!

In order to encourage the wider use of our first robot, ETI is offering a cash prize of one hundred pounds for the best program submitted which enables the Armdroid to be used with any of the following computers:

- Commodore PET — any model
- Tangerine MICRON
- Sharp MZ-80K
- Tandy TRS-80 Model III
- Superboard (expanded)
- Video Genie
- Apple/ITT 2020
- NASCOM
- Acorn Atom

Any memory size may be used, but we would suggest that a minimum of 8K is accepted. (The routine takes nothing like this amount of space incidentally!)

Entries must include a full listing and tapes are *ONLY* acceptable for PET and Sharp. Any other undocumented entries supplied on tape will be disqualified.

Group entries are quite acceptable, but it must be made clear who is to receive the cheque in the event of success, be it school, club or individual.

Handwritten entries will be considered, although presentation will play a part in deciding the competition, so typed entries (and printed listings) are to be preferred.

Closing date is October 31st 1981 and the winners will be announced as soon as possible after that date.

Send to: **Armdroid Competition, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.**

RULES

1. The entry must allow the Armdroid to be both keyboard controlled and to execute a series of actions under program control.
2. Programs for the TRS-80 Model I are not eligible for consideration, although they may be submitted to ETI and Computing Today as articles in the normal manner.
3. Entries arriving with a postmark of November 1st or later will not be eligible for judging.
4. All entries become the property of Modmags Ltd upon submission and no correspondence concerning the competition will be entered into. Any entries published in the magazine will be paid for at the usual rates.
5. The judges' decision shall be considered final by the contestants.



PROJECT : Robot Arm

PARTS LIST

INTERFACE BOARD

Resistors (all 1/4 W, 5% except where stated)

R1	1k Ω
R2,13	10k
R3-8	2k Ω resistor network
R9-11	1k Ω
R12	15k

Capacitors

C1	100p polystyrene
C2-14	10n ceramic

Semiconductors

IC1,2	74LS125
IC3	74LS04
IC4	74LS123
IC5	74LS366
IC6	74LS138
IC7-12	74LS175

Miscellaneous

SW1-6 SPST microswitches
0.1" 10-way edge connector (one off); four-way PCB plug and socket connectors (six off).

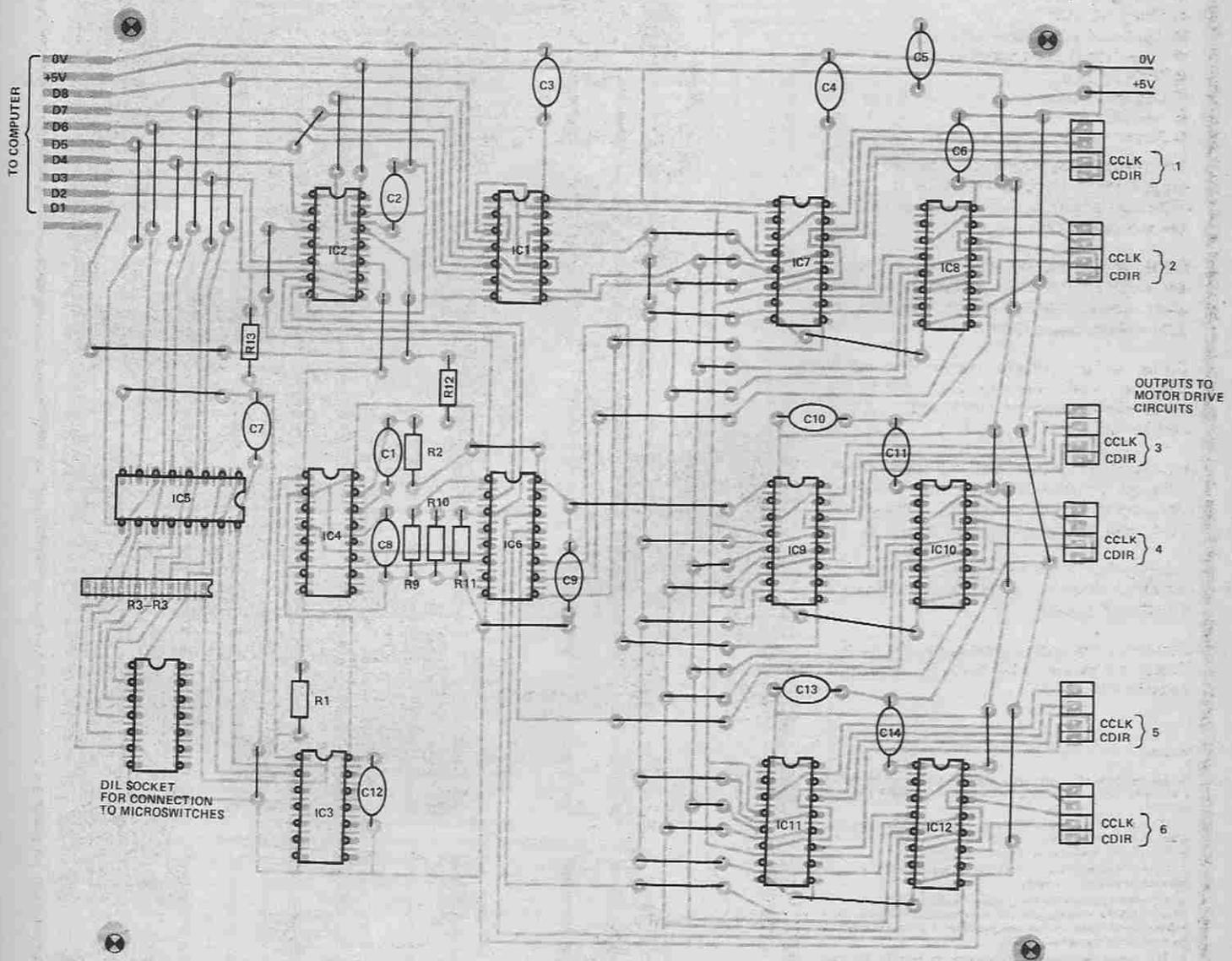
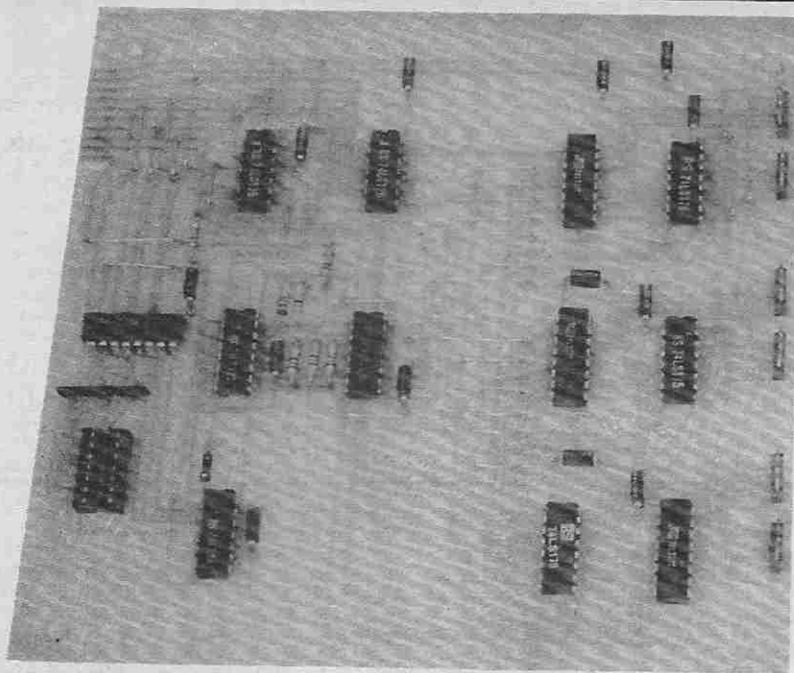


Fig. 3 Interface board overlay. The connection to the computer port will depend on your particular machine.

PROJECT : Robot Arm

PARTS LIST

MOTOR DRIVER

(For one channel only — six sets required except where stated)

Resistors (all 1/4 W, 5%)

R1	10k (one off)
R2,3	10k
R4	39k (one off)
R5	68k (one off)
R6	100k

Potentiometer

PR1 100k miniature vertical preset (one off)

Capacitors

C1 10n ceramic (one off)
C2 100n ceramic (one off)

C3 10n ceramic

Semiconductors

IC1	CD4551 (three off)
IC2	CD4013
IC3	CD4070
IC4	CD40109
IC5	VQ1000CS
IC6	555 (one off)

Miscellaneous

SW1 SPDT toggle (one off)
SW2,3 SPST push-button
MTR1 12 V stepper motor
0.1" 16-way edge connector (one off); four-way PCB plug and socket connectors (three off); 25-way terminal block (one off).


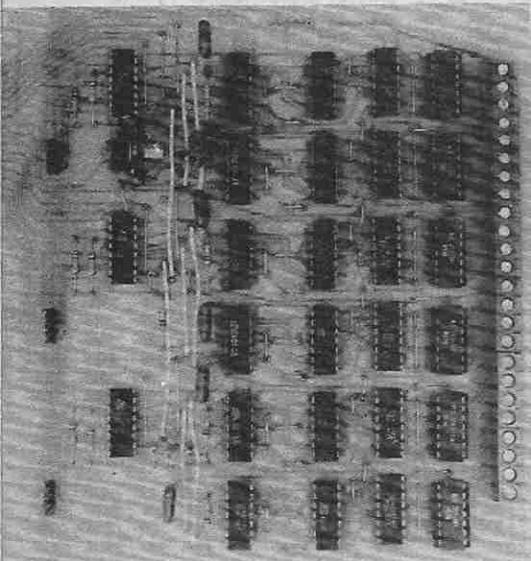


Fig. 4 Overlay for the motor driver board. Points A-A, B-B, . . . , F-F are linked by lengths of insulated wire; normally points G-G are also linked so that the manual override switch (SW1) controls the CMOS switches in all six channels. However, if it is required to provide a separate override for each pair of channels, pads are provided at pin 9 of each IC1 for the extra pull-down resistors.

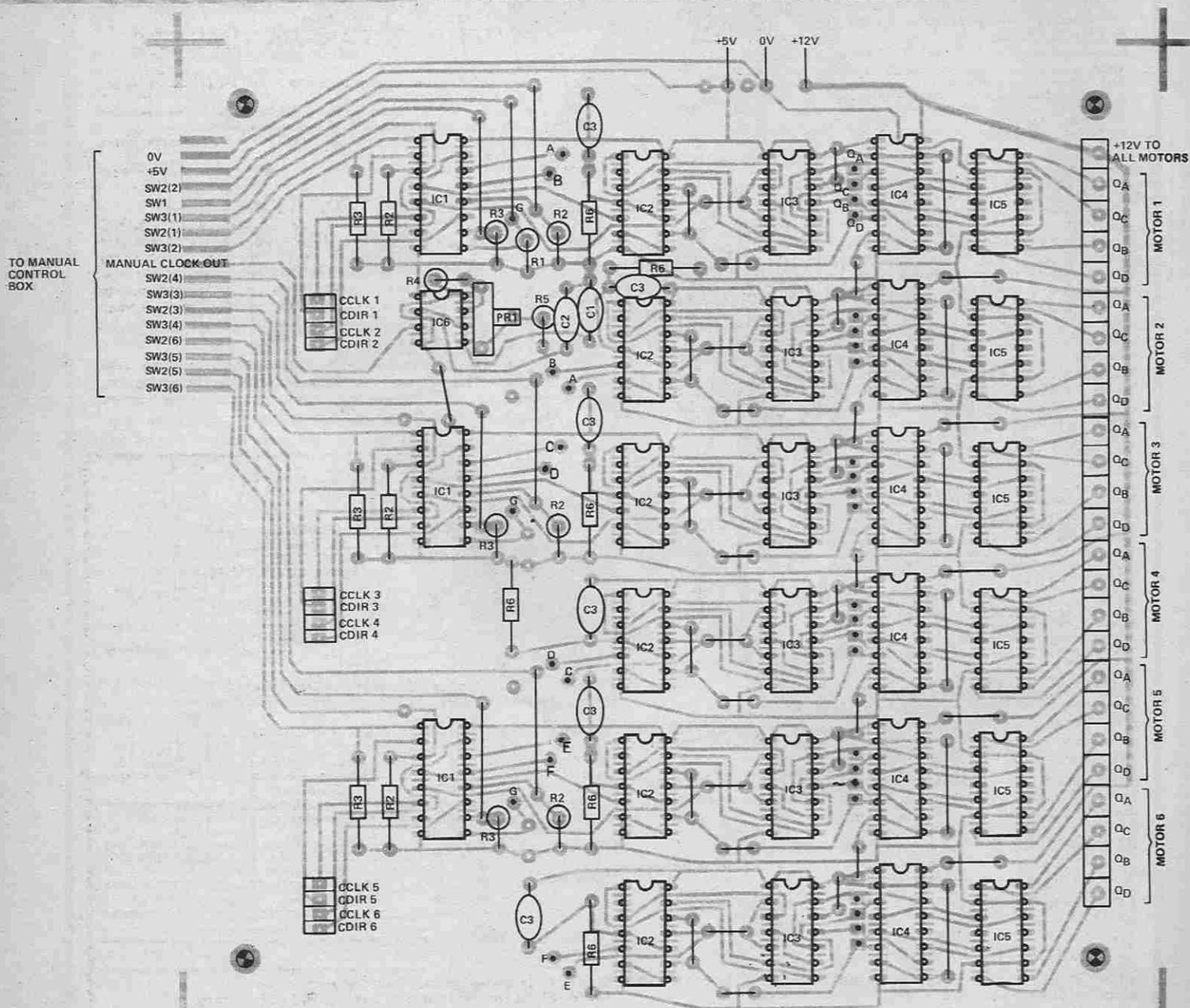

ETI

ETI OCTOBER 1981

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail.

After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £8.50

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

Book 1 Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.

Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.

Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.

Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters, shift registers; half-adders.



Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.



COMPUTER PROGRAMMING IN BASIC £10.50

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET, errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

A.N.S. COBOL £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

DESIGN OF DIGITAL SYSTEMS £14

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.


Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

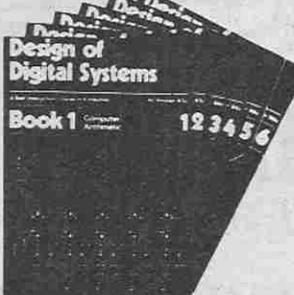Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

GUARANTEE No risk to you.

If you are not completely satisfied, your money will be refunded upon return of the books in good condition.

**CAMBRIDGE LEARNING LIMITED, UNIT 17
RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON,
CAMBS., PE17 4BR, ENGLAND.
TELEPHONE: ST. IVES (0480) 67446**

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice).

Please allow 28 days for delivery in U.K.

ORDER FORM

Please send me the following books:

-Digital Computer Logic & Electronics @ £8.50
-Design of Digital Systems @ £14.00
-Algorithm Writer's Guide @ £4.00
-Computer Programming in BASIC @ £10.50
-BASIC Handbook @ £11.50
-ANS COBOL @ £5.90
-Booklist (Free)

I enclose a cheque/P.O. payable to Cambridge Learning Ltd. for £..... (* delete where applicable)

Please charge my:

*Access/American Express/Barclaycard/Diners' Club/Visa/Mastercharge/Trustcard

Exp. date Credit Card No.....

Signature.....
Telephone orders from credit card holders accepted on 0480 67446 (Amsafone).

Overseas customers (incl. Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, Unit 17, Rivermill Site
FREEPOST, St. Ives, Huntingdon, Cambs., PE17 4BR, England
(Registered in England, No. 1328762)

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 20p PER PACK UP TO FOUR PACKS
FIVE OR MORE POST FREE
BUY SIX PACKS AND GET A SEVENTH PACK FREE!

MN1. 300 ¼-watt Resistors pre-formed for P&C Mtg.
MN2. 200 ¼ & ½-watt Resistors
MN3. 100 1 & 2-watt Resistors
MN4. 50 Wirewound Resistors.
MN5. 100 metal oxide Resistors. 1%, 2% and 5%.
MN6. 12 asstd. potentiometers.
MN7. 25 asstd. skeleton pre-set Resistors.
MN8. 50 asstd. Electrolytic Capacitors.
MN9. 100 asstd. Ceramic Capacitors. Pile, disc, tub and monolithic etc.
MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.
MN11. 20 asstd. Silver Mica Capacitors.
MN12. 8 Tantalum Bead Capacitors (useful values).
MN13. 20 asstd. Transistors. BC, 2N Series + Power etc.
MN14. 40 IN4148 Diodes.
MN15. 5 Light Sensitive Devices.
MN16. 20 min. wire-ended Neons.
MN17. 2 12-volt Relays. Ex nearly new equip.
MN18. 3 Encapsulated Reed Relays. 9-12v. coil, d-pole and t-pole.
MN19. 2 24-volt Relays. Ex nearly new equip.
MN20. 1 240-110 to 12-volt, 100ma Transformer.
MN21. 1 240-110 to 24-volt 100ma Transformer.
MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green.

MN23. 116 asstd. screws, nuts, washers, self-tappers etc.
MN24. 100 asstd. small springs.
MN25. 50 asstd. pop rivets.
MN26. 50 asstd. insulated crimps.
MN27. 200 items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.
MN28. 20 asstd. fuses. 1¼" 20mm etc.
MN29. 75mts equipment, wire, asstd. colours and sizes.
MN30. 3 x 2m length, 3 core, mains cable.
MN31. 12 asstd. trimmer capacitors, compression film. Air-spaced etc.
MN32. 15 30pF Beehive trimmers
MN33. 20 coil formers, ceramic, plastic, reed relay etc.
MN34. 25 min. glass reed switch.
MN35. 10 asstd. switches, toggle, slide, micro etc.
MN37. 10 asstd. audio connectors, Din, phone etc.
MN38. 1 PCB with triac control IC data inc.
MN39. 1 oscillator PCB loads of components. (no data)
MN40. 50 Polystyrene capacitors.
MN42. 10 BC107 Transistors.
MN43. 10 BC108 Transistors.
MN44. 10 Screwfix S.P.C.O. min. slide switches.
MN58. 2xCA723 Voltage Regulator
MN64. 5 Press to make min. switches.
MN65. 3 BF245 FETS.

CHORDGATE LTD. Dept. A

75 FARINGDON ROAD, SWINDON, WILTS
 TEL: SWINDON (0793) 33877
 RETAIL SHOP AT ABOVE ADDRESS

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

ELECTRONIC IGNITION SAVES PETROL

More and more new cars use electronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.



TOTAL ENERGY DISCHARGE gives all the advantages of the best capacitive discharge ignitions:

- ★ **Peak Performance**—higher output voltage.
- ★ **Improved Economy**—consistent high ignition performance.
- ★ **Better Starting**—full spark power even with low battery.
- ★ **Accurate Timing**—prevents contact wear without 'contactless' errors.
- ★ **Smooth Performance**—immune to contact bounce effects.

PLUS

SUPER HIGH POWER SPARK—3½ times the energy of ordinary C.D. systems.
OPTIMUM SPARK DURATION—to get the very best performance and economy with today's lean carburettor settings.
DESIGNED IN RELIABILITY—with the 'ultimate insurance' of a changeover switch to revert instantly to standard ignition.

TECHNICAL DETAILS

HIGH EFFICIENCY INVERTER. A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4 volts.

SUPERB DISCHARGE CIRCUIT. A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the H.T. system.

SOPHISTICATED TRIGGER CIRCUIT. This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

IN MONEY-SAVING KIT FORM at £14.85
Also MOTORCYCLE TWIN OUTPUT KIT at £22.94

Plus £1 UK P&P

All you need is a small soldering iron and a few basic tools — everything else is supplied with easy-to-follow instructions.

FITS ALL 6/12-volt NEGATIVE EARTH VEHICLES
ELECTRONIZE DESIGN



2 Hillside Road, Four Oaks
 Sutton Coldfield, West Midlands, B74 4DQ
 Phone 021-308 5877



The WORLD of RADIO & ELECTRONICS

AMBIT INTERNATIONAL



CONCISE PARTS CATALOGUE

OUT NOW!

AMBIT'S NEW CATALOGUE

In an attempt to collate and organize our burgeoning ranges of 'stock' components (now over 7000 line items), we have at last produced a 'concise' 80 page parts catalogue to supplement the popular 'Tecknowledgy' series of 'wordy' applications catalogues, which now lists a wide range of basic components - as well as our unique RF and Communications components. The *World of Radio and Electronics* contains everything the informed electronics user needs, at prices which we guarantee will match the lowest on the market for equivalent product.

Prices appear on the page alongside the part numbers, and the catalogue is now updated quarterly - available either direct from here (60p all inc) or at most newsagents and bookstalls where you can find electronics publications. So as well as all the 'run-of-mill' items like resistor, capacitors, hardware, solder etc - you now have the first genuinely complete parts source for the radio, communication, electronics, computer user.

Ambit International
 200, North Service Road,
 Brentwood,
 Essex CM14 4SG

Lost in the Hi Fi Jungle?

Phone Wilmslow 526213

for an expert guide to the territories of:

A&R **Dual** **MISSION** **PIONEER**

AIWA HITACHI OPTONICA Sansai

Plus

ARISTON • AKAI • B & W • CELESTION • GRADO • JR KEF • MONITOR AUDIO • NAGAOKA • ORTOFON ROGERS • THORENS • TRIO • VIDEOTONE

The Excellent New CJ-55 TURNTABLE

Sensible advice from expert staff

3 years guarantee on Hi Fi

Service Department on Premises

Very competitive prices

SWIFT
OF WILMSLOW

5 Swan Street, Wilmslow,
Cheshire Telephone 0625 526213




Now the time can tell you! . . .

New — from Silicon Speech Systems (a Powertran subsidiary) — the first ever easy-to-build kit that will give a whole new meaning to the 'speaking clock'! Electronics and quartz technology combine to enable you to construct a talking timepiece that is interesting to build — fun to have!

Full instructions make this a kit with equal appeal to the beginner or experienced constructor.

ONLY £29.95 includes VAT and Post & Pkg.

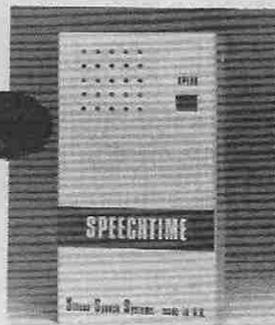- Accurate to a minute a year
- Adjustable voice pitch
- Grained stainless-steel case
- Pocket size — approx. 5in. x 2½in. x 1in.
- Useful in the home or office



Silicon Speech Systems

(A Powertran Subsidiary)



PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS., SP10 3NM
TELEPHONE ORDERING FOR ACCESS CUSTOMERS IS NOW AVAILABLE —
RING ANDOVER (0264) 64455; PLACE YOUR ORDER AND JUST QUOTE YOUR CARD NUMBER

CASIO

WHAT WILL THEY THINK OF NEXT?



FX 100
£15.95



FX 310
£17.95



FX 330
£15.95



FX 510
£18.95



FX 68
£18.95



FX 6100
£18.95



FX 7100
£23.95



FX 8100
£23.95
CASIO 601P
£51.95



FX 180P
£18.95



FX 200P
£17.95



FX 2700P
£18.95



FX 3500P
£21.95



FX 502P
£61.95



FX 602P
£71.95

CASIO FA 1 ADAPTOR CASSETTE INTERFACE for 501P, 502P, 601P, 602P

FA1 £19.95

TEXAS INSTRUMENTS

TI 51-111.....	£29.95	TI 57.....	£26.95
TI 58.....	£57.95	TI 58C.....	£68.95
TI 59.....	£121.95	PC 100C printer for 58/58C/59.....	£148.95

SHARP EL 5101 16 digit alpha/numeric £41.95 EL 5100 24 digit alpha/numeric £51.95
Pocket Computer PC1211 £91.95 CE121 Cassette Interface £15.95
CE122 Printer/Cassette Interface £71.95

FULL RANGE OF CASIO SHARP AND TEXAS INSTRUMENTS AVAILABLE. S.A.E. WITH ENQUIRIES PLEASE

SEND CASH, CHEQUES, P.O., etc., PAYABLE TO C.S.S. — OR QUOTE ACCESS NUMBER ON ORDERS OVER £30 ONLY. C.O.D. AVAILABLE AT EXTRA CHARGE OF £1.50 UP TO £250

CALCULATOR SALES & SERVICE



FREEPOST (no stamp required) REDDITCH, WORCS. B98 0BR
Telephone (0527) 43169

TECH TIPS

Audio Link Modifications

T. Bennett, Hazel Grove

Referring to the circuit information offered by T.P. Hopkins in the June Tech Tips Special for a Bidirectional Audio Link, a closer inspection of the circuit will reveal several omissions, some of which the amateur constructor may find difficult to rectify. There are no biasing components shown (to provide balance); the voltage rails are not shown; and DC blocking capacitors are not shown — it won't work without them. I enclose a drawing of a circuit with these features which I constructed in order to test the rejection — this was measured at 50 dB.

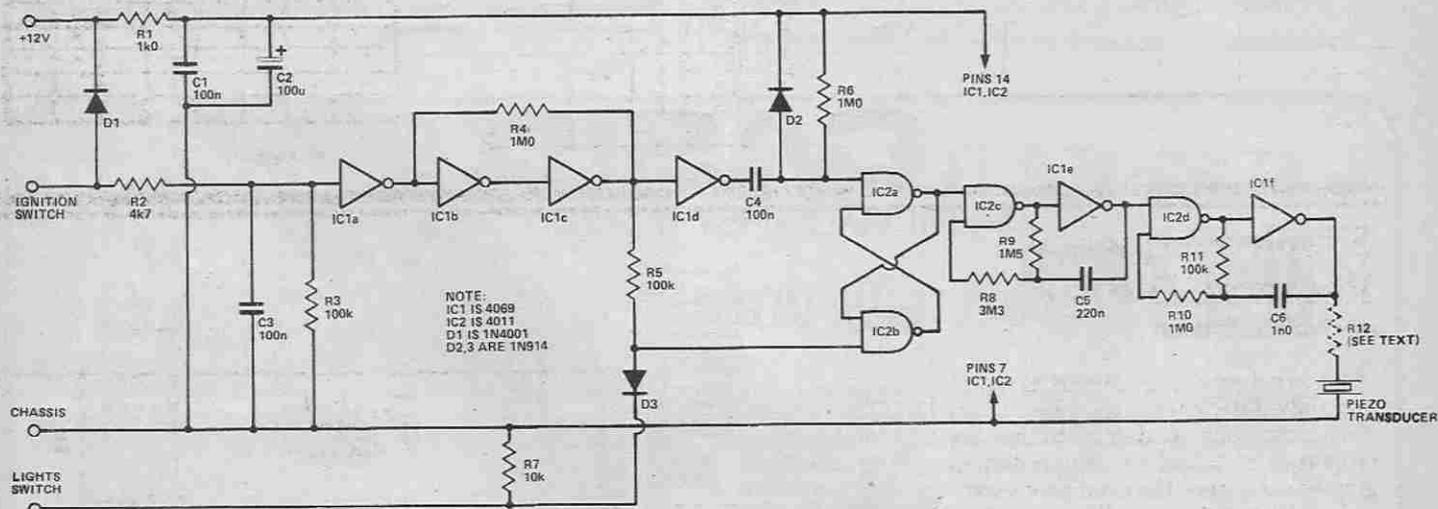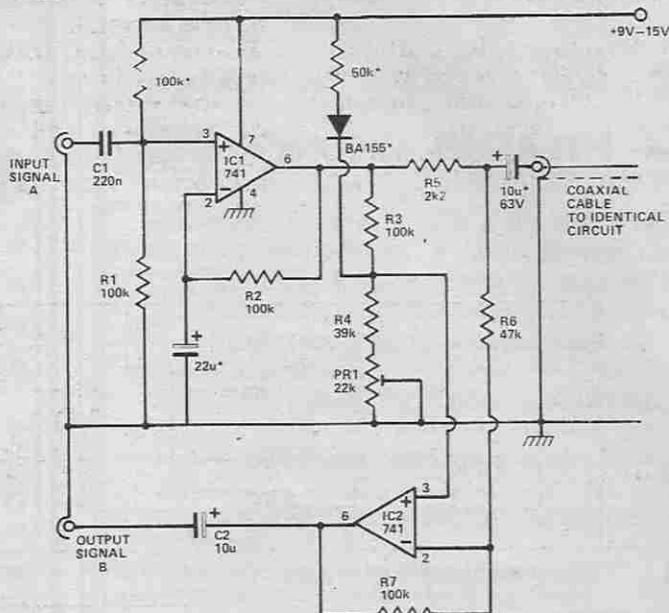

Car Lights Warning

A.M. Tucker, Dorchester

This circuit gives an audible warning if the car lights are left on when the ignition is switched off. If necessary, the lights can be switched off and then on again, and the alarm will be cancelled.

Operation is as follows: the ignition switch is connected to buffer IC1a, Schmitt trigger R4-IC1b-IC1b and inverter IC1d. R1-C1-C2 and R2-C3 are

filters. If the lights are on and the ignition is switched off, a negative pulse is applied through C4 to IC2b and the junction of R5 and D3 goes high, causing the flip-flop to change over. This enables the slow oscillator IC2c-IC1e (approximately 1.3 Hz), which pulses the (approximately) 4 kHz oscillator IC2d-IC1f, causing audible bleeps in the piezo-electric transducer. If the lights are off, the input to IC2a is held low via D3 and R7, inhibiting the oscillators. D1 and D2 deal

with unwanted transients, while R12 is chosen to give the required warning level.

The circuit can be adapted for positive earth vehicles by reversing the diodes and electrolytic capacitor, reversing the connections to pins 7 and 14 of the ICs, and substituting a 4001 NOR IC for the 4011 NAND IC. With this modification, there may be a short bleep when the ignition is switched off and the lights are not on.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

Seven Channel Lightshow

J. McCauley, Dundalk

When used with an audio input this circuit gives a very effective display, using seven 75 W coloured spot lamps for disco work or smaller 'pygmy' bulbs when used as an addition to a home audio system. Alternatively the 7447,

which is a display driver, can drive seven LEDs directly.


As can be seen from the truth table there are 16 different arrangements for the sequence of switching. This helps give the impression that the bulbs are randomly switched. The operation of the circuit is as follows.

The 555 timer is connected here as a VCO with the control voltage on pin 5 derived from the audio input via the FET input buffer circuit. The variable length

pulses from the VCO are then used to clock the 7493 which is connected here as a binary counter.

The outputs from the 7493 are then decoded by the 7447 decoder (BCD to seven-segment). The outputs from this IC are used to trigger the SCRs, thus turning on the appropriate lights.

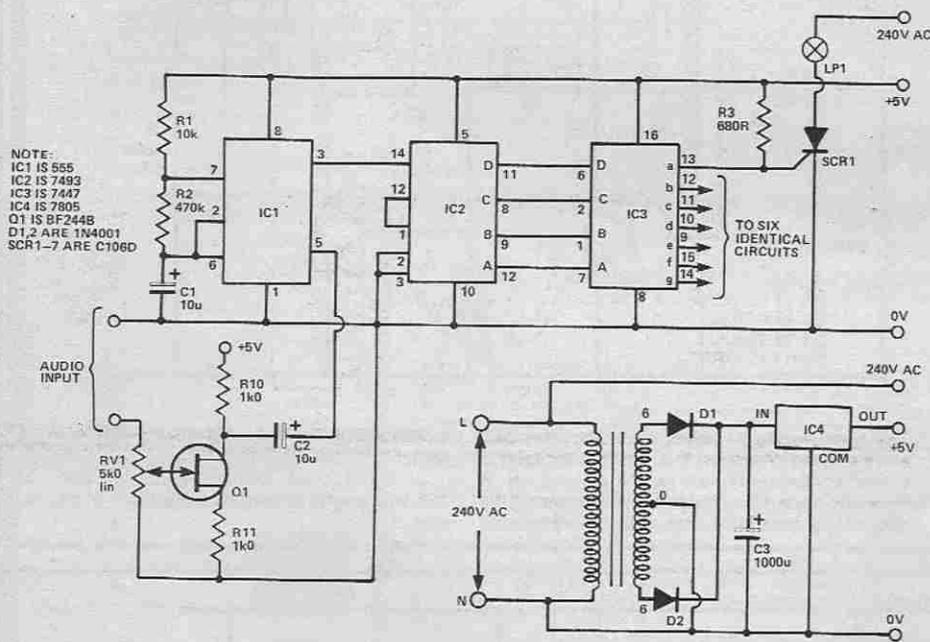All that is necessary to operate the circuit is adjustment of the input level control (RV1) to give the best visual display. When switching low power loads ie 75 W, RFI suppression circuitry should not be required; however, with greater loads (absolute max 750 W per channel) such circuitry will be necessary.




COUNT	LP1	LP2	LP3	LP4	LP5	LP6	LP7
0		X	X	X	X	X	X
1					X	X	
2	X			X		X	X
3	X				X	X	X
4	X	X			X	X	
5	X	X			X	X	X
6	X	X	X	X	X		
7					X	X	X
8	X	X	X	X	X	X	X
9	X	X			X	X	X
10		X	X	X		X	X
11				X	X	X	X
12	X	X			X		
13	X	X		X	X	X	X
14	X	X	X	X	X		
15							

X = LAMP LIT

Simple Frequency Response Display

M. Harrison, London

This circuit was originally designed to test audio filter circuits, but has several other uses such as demonstrating the properties of tuned circuits, or testing graphic equalisers. The circuit consists of a low-frequency oscillator with a triangular wave output which is used to frequency modulate a VCO, while also being fed to the X input of a 'scope' (the signal is about 2 V peak-to-peak, so further amplification may be needed for some 'scopes'). The VCO output is passed to the Y input through the filter under test. This gives a display of output level against frequency, with the frequency decreasing from left to right. SW1 sets the frequency range of the display, and RV1 sets the scanning speed; it is adjusted to give a good display, and does not affect the actual shape of the display. As well as being simple this circuit is cheap, the 76477 only costing about £2. Q1 and Q2 are any NPN silicon transistors with a reasonable gain, for example BC108.

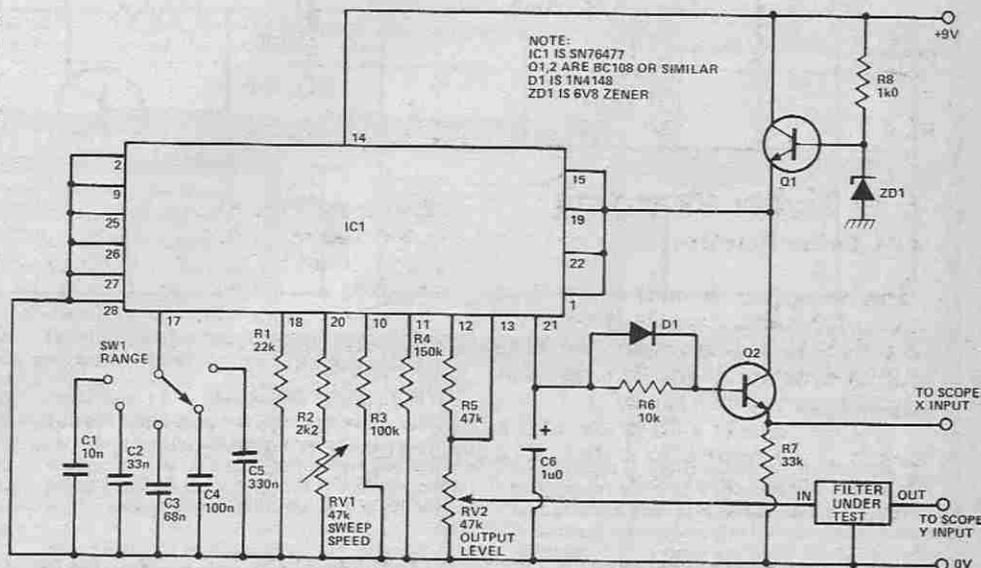

NOTE:
IC1 IS 5N76477
Q1,2 ARE BC108 OR SIMILAR
D1 IS 1N4149
ZD1 IS 6V8 ZENER


SPOT DESIGNS

Light-activated Switch

Most light-operated switches are designed to respond to the ambient light level so that some item of equipment is switched on or off at a certain light level. This circuit is somewhat different in that it is designed to respond to mains-powered lighting, rather than to some ambient light level. It could, for example, be used with a bedroom TV set, to automatically switch the set off when a bedside lamp was switched off. No doubt there are other applications for a circuit of this type.


The difference between mains lighting and natural light which is exploited in this circuit is that mains lighting is modulated at the 50 Hz mains frequency whereas natural lighting is fairly stable. LDR1 and R1 are connected as a potential divider across the supply lines, and in the presence of natural lighting only, the output voltage from this network will change only gradually. On the other hand, mains lighting will vary in intensity at 50 Hz, causing the resistance of LDR1 to vary in sympathy and producing a 50 Hz output signal from the potential divider.

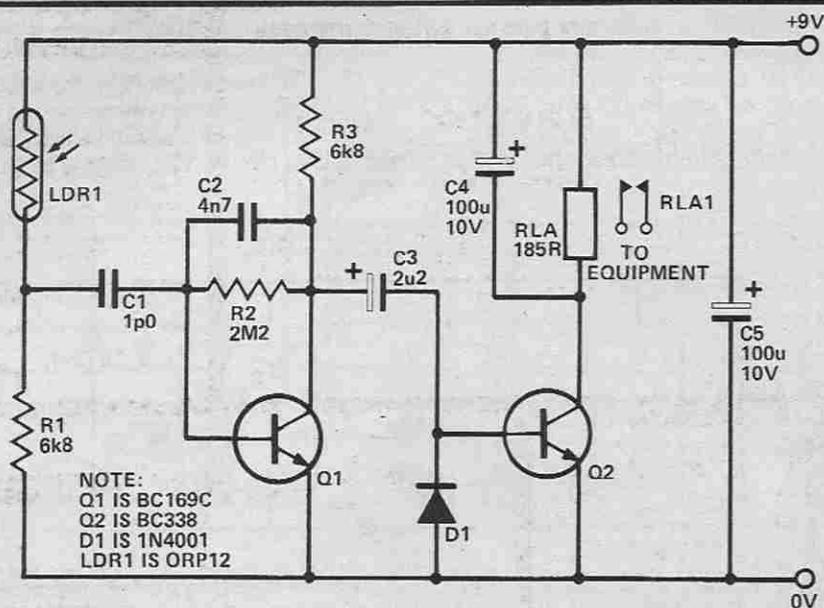This signal is coupled by C1 to the input of a high gain common emitter amplifier which uses Q1 in a standard configuration. C2 reduces high frequency noise that could otherwise upset the operation of the unit. The amplified signal at Q1's collector is coupled by C3 to the base of Q2, and the latter is switched on by positive half-cycles.



This gives a series of pulses across the relay coil, and these are integrated by C4 so that the relay is closed continuously, not pulsed on and off. A normally-open relay contact is used to control the external equipment (or a normally-closed type if

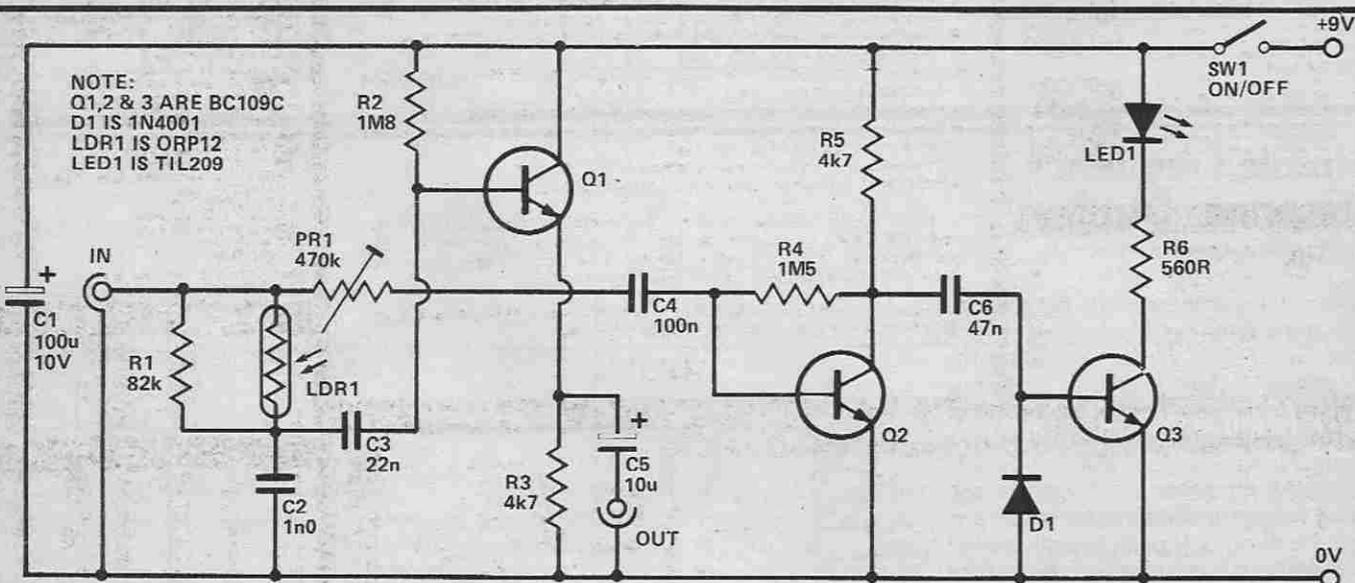is necessary for the controlled equipment to switch on when the mains lighting is switched off). Avoid strong natural lighting on LDR1 as this will greatly reduce the sensitivity of the circuit.



Dynamic Noise Limiter

A dynamic noise limiter (DNL) is primarily intended for use with a cassette recorder to process the output when playing a cassette that has not been encoded by a noise reduction unit of some kind, and therefore gives a comparatively poor signal-to-noise ratio. The DNL gives a degree of treble cut at low signal levels, with a subsequent improvement in the signal-to-noise ratio. At higher signal levels the treble cut is gradually lifted, and is practically eliminated at the highest

levels. This gives reduced signal-to-noise ratio, but this is not noticeable as the main signal masks the noise.

The parallel impedance of R1 and LDR1 together with C2 forms a low-pass filter. The output from this filter is taken to the output socket via emitter follower buffer stage Q1, and the high input impedance of this stage ensures that loading effects do not impede the performance of the filter.

Some of the input signal is coupled to the base of Q2 via PR1 and C4, and a greatly amplified signal appears at Q2's collector. This is coupled to the base of Q3 by C6, and Q3 will be switched on during positive signal peaks of suitably high amplitude. This causes LED1 to light up, and since


it is directed at LDR1 (which should be shielded from the ambient light), the impedance of the latter falls. This reduces the high frequency attenuation of the filter and gives the required lifting of the treble cut at high signal levels. The fast attack and relatively slow decay times of LDR1 ensure that it responds to the average light output of LED1 and not to individual light pulses, so that the required circuit action and low distortion are obtained.

The unit will operate with input signal levels from about 50 mV RMS to over 1 V RMS, and it should therefore match the output signal of any cassette recorder or deck. PR1 is given the highest resistance setting that provides full treble lift at the peak signal level.

Team Up With **TK** Electronics

for top-quality components, innovative kits
FAST SERVICE AND LOW, LOW PRICES

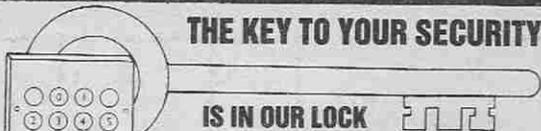Prices do not include V.A.T. Add 50p P. & P. + 15% V.A.T. to total. Overseas customers add £1.50 (Europe), £4 (elsewhere). Access and Barclaycard welcome. Send s.a.e. for price list and with enquiries. Shop open: 9-5 (Mon.-Fri.), 10-4 (Sat.)
11 BOSTON ROAD, LONDON, W7 3SJ
Tel: 01-579 9794/2842



If you have problems with people tampering with your car, electrical and electronic equipment, or if you are just in a habit of forgetting your door keys, we have just the kit for you.

Our ELECTRONIC LOCK KIT includes a 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is pre-wired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7 x 6 x 3 cms. Power consumption is 40uA at 5V, to 15V, d.c.

At only **£10.50** + V.A.T., it will make a smaller hole in your pocket than a bunch of keys!

LOCK ICs	
LS7220 with SAVE memory	£2.75
LS7225 with latched and momentary outputs and a tamper output	£2.80
Data only	.10

DVM/THERMOMETER KIT

£13.50
VAT

Based on ICL7106 DVM chip and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter - only a few additional switches and resistors required (details supplied) or make a sensitive digital thermometer (-50°C to 150°C) reading to 0.1°C. The basic kit has a sensitivity for full scale of 200mV, automatic polarity and runs from a 9V PP3 battery.

DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1kW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

DL1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.60**

DL2100K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**
Optional Opto Input
DLA1 **60p**

TRIACS

400V Plastic Case (Texas)	
3A TIC206D	49p
8A TIC226D	58p
12A TIC236D	85p
16A TIC246D	95p
25A TIC283D	190p
5A with trigger Q4006LT	80p
8A isolated tab TXAL226B	55p
Diac	18p
Opto Isolated Triac	
MOC3020 0.6A/400V	

REMOTE CONTROL COMPONENTS AND KITS

LD271 IR Emitting Diode	.36	ML927 16-channel Receiver, 4 Momentary Binary Outputs	1.40
SF4205 Photodiode Detector	.90	ML928 16-channel Receiver, 4 Latched Binary Outputs	1.40
SL480 IC Pulse Amp	1.70	ML929 16-channel Receiver, 4 Latched Binary Outputs	1.40
SL490 32-command Encoder/Transmitter	2.40	Clip-on Plastic Receiver for IR LEDs, increases range	.20
ML922 16-channel Receiver + 3 Analogue Outputs	4.20		
ML926 16-channel Receiver, 4 Momentary Binary Outputs	1.40		

ML925. A decoder designed for model/toy control, providing a 2-speed drive motor and three-position latched steering system or a vehicle with momentary action steering and a third motor, e.g. gun, turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc.

KITS ★★★★★ KITS ★★★★★ KITS ★★★★★ KITS

MK6 - Simple Infra-Red TRANSMITTER. A pulsed infra-red source which comes complete with a hand-held plastic box. Requires a 9V. battery.	£4.20
MK7 - Infra-Red RECEIVER. Single channel, range approximately 20ft. Mains powered with a triac output to switch loads up to 500W, at 240V, a.c. but can be modified for use with 5-15V, d.c. supplies and transistors or relay outputs.	£9.00
MK8 - Coded Infra-Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8 x 2 x 1.3 cms. and requires a 9V (PP3) battery.	£5.90
MK9 - 4-way KEYBOARD. For use with MK8 kit.	£1.90
MK10 - 16-way KEYBOARD for use with MK8 kit, to generate different codes for decoding by the ML928/926 receiver (MK12 kit).	£11.95
MK11 - 10 on/off channel IR RECEIVER with 3 analogue outputs (0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC, includes its own mains supply.	£12.00
MK12 - 16-channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which, with further interface circuitry, such as relays, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply.	£11.95
MK13 - 11-way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and -, analogue + and - (3), mute, normalise analogue outputs, and on/standby.	£4.35

YOU MUST HAVE BETTER THINGS TO DO

than getting up to switch lights on when it gets dark. Our Lamp Dimmer Kit with INFRA-RED REMOTE CONTROL will enable you to switch the lights on or off, and set the brightness, at a push of a button without leaving your armchair, waterbed, etc. Not only will you save time but it has also been estimated that the savings in shoe leather and carpet wear alone would pay for this unit in approximately 1.3697 years or more!! This unit has, of course, considerable practical uses, especially for the old, infirm and disabled. It works like a conventional dimmer, enabling you to switch the lights on or off, or to dim to whatever brightness you require, by touch or remotely using the hand-held infra-red transmitter. When assembled, it fits into a plaster depth box to replace your conventional switch or dimmer with no rewiring. TDR300K Dimmer Kit **£14.30**, and MK6 Transmitter Kit **£4.20**.

We also still sell our highly-popular TD300K Touch Dimmer Kit at **£7.00** and the LD300K rotary-controlled Dimmer Kit at only **£3.50** (plus V.A.T. to above prices).

All kits contain all necessary components and full assembly instructions. You only need a soldering iron, cutters and a few hours.



NOT JUST ANOTHER CLOCK

but a PROGRAMMABLE TIMER KIT which can run your central heating, burglar alarm, lighting, tape-recorder/radio and lots more. Designed to control four mains outputs independently, switching these on and off on selected days and times in a seven-day cycle.

Features include:

- ★ 0.5in. LED 12-hour display
- ★ Day of week, a.m./p.m. and output status indicators
- ★ Zero Voltage Switching Outputs
- ★ 50/60Hz mains operation
- ★ Battery back-up saves stored programmes and continues time keeping during power failures (battery not supplied)
- ★ Display blanking during power failure to conserve battery power
- ★ 18 programme time sets
- ★ Powerful "Everyday" function enabling output to switch every day but use only one time set
- ★ Useful "sleep" function - turns on output for one hour
- ★ Direct switch control enabling output to be turned on immediately or after a specified time interval
- ★ 20-function keypad for programme entry
- ★ Programme verification at the touch of a button

To control your central heating, for example (including different switching times at weekends), just connect it to your system, programme it, set it and forget it. The clock will do the rest. There has never been a clock capable of so much at this price.

CT5000K Timer Kit (includes all components, assembly and programming instructions, and an attractive black case)

£45.00

INTEGRATED CIRCUITS

555 Timer	21		
556 Dual 555 Timer	40		
AD590 Constant Current Temperature Sensor	2.75		
AY-5-1224 Clock	2.60		
AY-6-1230 Clock/Timer	4.50		
AY-3-1270 Thermometer	8.20		
CA3160 Transconductance Op Amp	.72		
CA3130 CMOS Op. Amp.	.75		
CA3140 CMOS Op. Amp.	1.43		
ICL7106 DVM (LCD drive)	7.00		
ICM6555 CMOS 555 Timer	.79		
LM377 Dual 2W. Amp.	1.45		
LM3795 Dual 6W. Amp.	3.50		
LM380 2W. Audio Amp.	.80		
LM382 Dual low-noise Pre-Amp.	1.00		
LM386 250mW. Low Voltage Amp.	.75		
LM1830 Fluid Level Detector	1.50		
LM2917 F-V Converter (14-pin)	1.60		
LM3909 LED Flasher/Oscillator	.60		
LM3911 Thermometer	1.20		
LM3914 Dot/Bar Driver (linear)	2.10		
LM3915 Dot/Bar Driver (log.)	2.20		
LS7220 Electronic Combination Lock with "Save" feature	2.75		
LS7225 Electronic Combination Lock with tamper output	2.60		
MM74C911 4-digit display controller	6.50		
MM74C915 7-segment BCD Converter	.96		
MM74C926 Counter/7-seg. output	4.50		
S5868 Touchdimmer	2.50		
SL440 A.C. Power Control	1.25		
SL441 Burst Fire Controller	1.75		
SN76447 Complex Sound Generator	1.75		
TBA800 5W. Audio Amp.	.68		
TBA810AS 7W. Audio Amp.	1.00		
TMS1121 Clock/7-day Timer	8.50		
Data for TMS1.121	.50		
TDA1024 Zero Voltage Switch	1.20		
TDA2020 20W. Audio Amp.	2.85		
TDA4290 D.C. Controlled, Base, Treble and Volume Pre-Amp.	1.98		
TL081 J-FET Op. Amp.	.37		
TL082 Dual J-FET Op. Amp.	.60		
TL084 Quad J-Fet Op. Amp.	1.00		
ZN414 A.M. Radio	.98		
ZN1034E Timer	1.80		

Most ICs supplied with Data Sheet
Data Sheets only - per device

MEMORIES & MICROS

2114	1.35	Z80A CPU	5.00
2708	2.25	M6802P	5.50
2716	2.65	8035L	8.00
2732	7.80	Z80A CTC	4.00
4116	1.40	Z80AP10	4.00
6810	1.40	6850P	1.85
6821P	1.85	6852P	3.00

CMOS

4000	.1	4019	.38	4069	.18
4001	.14	4023	.22	4070	.24
4002	.14	4025	.18	4071	.22
4007	.14	4026	1.05	4077	.24
4011	.15	4027	.40	4081	.22
4012	.17	4028	5.00	4093	.45
4013	.35	4040	.68	4801	.24
4015	.70	4049	.30	4511	.65
4016	.30	4050	3.00	4514	1.80
4017	.65	4060	.90		

TTL 74LS

LS00	.12	LS38	.16	LS126	.29
LS01	.12	LS40	.14	LS132	.44
LS02	.13	LS42	.40	LS160	.40
LS03	.13	LS47	.42	LS161	.40
LS04	.14	LS51	.15	LS162	.40
LS05	.15	LS54	.15	LS163	.40
LS06	.15	LS55	.15	LS164	.50
LS09	.15	LS73	.20	LS165	1.05
LS10	.14	LS74	.18	LS166	.85
LS11	.15	LS75	.27	LS173	.72
LS12	.15	LS76	.21	LS174	.52
LS14	.27	LS85	.64	LS191	.58
LS14	.48	LS86	.18	LS192	.85
LS15	.15	LS90	.32	LS193	.65
LS20	.14	LS93	.37	LS196	.65
LS21	.15	LS95	.48	LS197	.65
LS22	.15	LS107	.24	LS219	.34
LS26	.18	LS109	.24	LS365	.34
LS27	.15	LS112	.24	LS366	.34
LS30	.14	LS113	.24	LS367	.34
LS32	.15	LS114	.24	LS368	.34
LS37	.17	LS123	.51		


MINI TRANSFORMERS

Standard mains primaries 240V a.c. 100mA secondaries	
6-0-6V	80p
9-0-9V	85p
12-0-12V	90p
1A, 9-0-9V	210p

LEDS

0.1in. Red	9p
0.1in. Green	12p
0.1in. Yellow	12p
0.2in. Red	9p
0.2in. Green	12p
0.2in. Yellow	12p
0.2in. Clips	3p
Rectangular Red	15p
Rectangular Green	15p
Rectangular Yellow	17p
Flat Face rectangular, Triangular, Arrowhead or Square	17p
Red	17p
Green	20p
Rec. Yellow	20p

MICROS

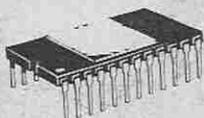

Micros, memory and support

MC1489	86	74S287	2.60
MC1488	86	74S288	2.60
MC14411	11.96	74S471	4.96
MC14412	11.96	74S472	11.96
1702	6.96	74S474	11.96
2101	2.99	8126	1.80
2102	3.99	8128	1.80
2111	2.32	8195	1.80
2112	2.32	8197	1.80
2114	3.46	8198	1.80
2114L	3.75	SC/MP2	9.96
2142	10.40	8080	6.49
2376	11.60	8085	11.96
2513	6.60	8086	89.00
2516(5v)	13.95	8154	11.60
2532	29.00	8155	12.60
2708	6.60	81LS95	1.30
4027	2.96	81LS96	1.30
4116	4.96	81LS97	1.30
4118	14.96	81LS98	1.30
5204	7.96	8212	2.46
57109	12.43	8216	2.50
57161	4.96	8224	1.80
6011	6.96	8228	4.20
6402	4.96	8251	4.96
6502	7.96	8253	10.96
6520	4.60	8255	4.96
6522	7.96	8257	10.96
6532	8.60	8259	11.96
6545	17.50	8678	12.96
6576	14.96	8602	2.20
6800	7.96	96384	10.96
6802	12.49	Z80-2mHz	7.50
6809	19.96	Z80-P10	6.96
6810	3.96	Z80-CTC	6.96
6821	4.96	Z80-4mHz	8.96
6845	19.60	Z80-P10	7.60
6850	3.96	Z80-CTC	7.50
6852	5.96	Z8000	120.00
74S00	69	ADDC0817	14.47
74S04	66	DG300	3.60
74S201	3.96	FB	9.96
74S188	2.60	F8SM1	9.96
74S262	9.96		

SOFTWARE

DISK WITH /MAN
CP/M⁺ MANUAL

Available on 8" IBM format & 5 1/4" for TUSCAN & TRITON

TCL SOFTWARE

TCL Disc Basic	£55/£9
TCL Pascal	£120/£9

MICROSOFT

Basic-80	£165/£15
Basic Compiler	£195/£16
Fortran-80	£205/£15
Cobol-80	£325/£15
Edit 80	£45/£10
Macro 80	£75/£10

MICROPRO

Word Star	£255/£15
Word-Star/Mail-Merge	£315/£15
Data Star	£195/£25
Word-Master	£75/£15

DIGITAL RESEARCH

CP/M 1.4	£75/£18
CP/M 2.2	£95/£18
MAC	£55/£10
SID	£45/£10

OTHERS

KISS	£190/£15
SUPER SORT 1	£125/£15
C BASIC 2	£75/£10
Z80 Dev. Pack	£50/£12
ZSID	£60/£7
POSTMASTER	£85/£10

MEDIA (DYSAN)

5 1/4" S/Sided D/D	£4.20
per 10	£37.00
8" S/Sided D/D	£4.90
per 10	£43.00
C12 Data Cassettes	50p

MAIL ORDER

TEL & MAIL ORDERS ACCEPTED

BARCLAYCARD
VISA

COMPUTER SYSTEMS

TUSCAN S100 A Z80 based S100 Computer

All Tuscans have built-in expansion interface, full RS232 serial I/O. Spare parallel output port (Centronics) IEEE 8BIT S100 expansion. Powerful Z80 processor and are expandable to full CP/M system.

DESIGNED & BUILT IN BRITAIN

- 16K Tuscan starter kit (inc. P.S.U. & keyboard) £299
- 16K Home Computer assembled & cased £499
- 24K single drive CP/M system (assembled) £999
- 60K twin drive CP/M business system £1449

Also available with double sided drives for 8" and 5 1/4" systems. The Tuscan builds to meet all requirements, 5 spare S100 slots for your plug in boards. Full details on the Tuscan and peripherals is given in our new computer systems catalogue - also see our Software catalogue.



AND SPARES

74LS00

LS001	13	LS164	115
LS01	13	LS165	156
LS02	15	LS166	176
LS03	16	LS168	210
LS04	23	LS169	210
LS05	20	LS170	286
LS08	23	LS173	106
LS09	23	LS174	147
LS10	20	LS175	110
LS11	32	LS181	286
LS12	32	LS190	120
LS13	40	LS191	120
LS14	76	LS192	126
LS15	40	LS193	126
LS16	40	LS194	126
LS19	24	LS196	126
LS21	32	LS196	126
LS22	40	LS202	346
LS26	48	LS221	120
LS27	46	LS240	226
LS28	48	LS241	226
LS30	24	LS242	232
LS32	30	LS243	232
LS33	39	LS244	226
LS37	39	LS245	310
LS38	39	LS247	136
LS40	28	LS248	136
LS42	80	LS249	136
LS47	86	LS251	130
LS48	120	LS253	130
LS49	120	LS257	116
LS51	25	LS258	120
LS54	30	LS259	180
LS55	70	LS261	450
LS563	150	LS266	76
LS73	40	LS273	180
LS74	48	LS275	320
LS75	48	LS279	88
LS76	45	LS280	250
LS83	106	LS283	190
LS85	106	LS290	130
LS86	46	LS293	130
LS90	50	LS296	216
LS91	126	LS288	216
LS93	76	LS299	420
LS95	115	LS324	200
LS96	180	LS325	320
LS107	46	LS326	320
LS109	75	LS327	316
LS112	80	LS352	186
LS113	85	LS353	186
LS114	49	LS355	86
LS122	70	LS366	86
LS123	96	LS367	86
LS124	180	LS368	86
LS125	80	LS373	180
LS126	80	LS374	180
LS132	96	LS375	180
LS133	30	LS377	199
LS136	56	LS378	186
LS138	70	LS379	216
LS139	90	LS386	86
LS145	120	LS390	140
LS148	175	LS393	140
LS151	96	LS395	210
LS153	86	LS396	199
LS156	96	LS398	276
LS156	96	LS399	230
LS157	76	LS445	140
LS158	86	LS447	196
LS160	120	LS490	160
LS161	96	LS668	106
LS162	110	LS669	106
LS163	100	LS670	270

S100 CARDS

NEW

64K STATIC EPROM

Brand new board, takes 2S16 eproms and/or 2k and 8 static CMOS RANS. 150ns access time, ultra low power consumption

Memory kit asm £153 £162
64/16K board £153 £162
64/32K £248 £257
64/48K £343 £352
64/64K £438 £447

Memory upgrades £50/8K
OEM & Dealer enquiries welcome

FDC DOUBLE DENSITY

Double Density for 5 1/4" or 8" Drives £ - £195

FLOPPY DISK DRIVES

We sell all you need cased or uncased. Cables & connectors. Brand new fully guaranteed.

Price
Single 5 1/4 Drive £155
Single 8" SA800 £365
Dual 5 1/4 PSU £49.50
Dual 8" PSU £76
Dual Cabinet & PSU 1x8" £665
Dual 8" Drive Unit £1125
Dual 5 1/4 Drive Unit.. £440

CATALOGUE AVAILABLE

Three new catalogues now available covering the main areas of computing

- Hardware systems
- Software
- Spares

Catalogues are 40p each or all 3 for £1 - free to companies and Govt. bodies when ordered on official letterhead.

TCL PASCAL

A British Pascal Compiler
Ideal Educational Language
Runs on several machines.
Educational discounts
Available for Multi-User
Departments
Officially approved Commodore product

PET
PET 80 COLM.
RML 380Z



TUSCAN SUPERBRAIN
Price £120. 1 off

Edge Connectors S100

£4.00



DIP Switches	15 way	£4.95
4 way	24 way	£6.00
7 way	40 way	£9.50
8 way		

D-Types

25W Male	£2.80
25W Female	£3.80
25W Cover	£1.80

Edge Connectors

1	156
2x 6 way	1.75
2x12 way	3.00
2x10 way	2.00
2x15 way	3.20
2x18 way	3.50
2x22 way 3.203 65	20 1.40
2x25 way 3.60	26 1.60
2x30 way 4.15	34 2.40
2x36 way 4.753 90	40 2.80
2x40 way 5.00	50 3.30
2x43 way 5.504 60	60 4.00

Insulation Piercing Ribbon/Cables

10 way	£2.20	10 way	£1.60
20 way	£3.40	20 way	£2.30
26 way	£4.00	26 way	£2.70
34 way	£4.80	34 way	£3.30
40 way	£5.40	40 way	£3.75
50 way	£6.00	50 way	£4.60
60 way	£6.50	60 way	£5.00

Insulation Piercing Edge Connectors

20 way	£3.60	40 way	£5.30
26 way	£4.00	50 way	£6.00
34 way	£4.60		

DIP Plugs

14 DIL	£.65
24 DIL	£2.20
40 DIL	£3.60

DIP SOCKETS (TEXAS)

Low Wire	2x 6 way - 1.75
Prof Wrap	2x12 way - 3.00
8pin 10p	26p 2x10 way - 2.00
14pin 12p	35p 2x15 way - 3.20
16pin 13p	42p 2x18 way - 3.50
18pin 16p	60p 2x22 way 3.203 65
20pin 22p	90p 2x25 way 3.60
22pin 25p	— 2x30 way 4.15
24pin 30p	65p 2x36 way 4.753 90
28pin 35p	90p 2x40 way 5.00
40pin 40p	1.10p 2x43 way 5.504 60

Insulation Piercing DIP Plugs

14 way	DIP Plug	£1.30
16 way	DIP Plug	£1.50
24 way	DIP Plug	£2.80

Ribbon Cable PRICE/M

Grey	Coloured		
10	65	10	90
14	90	14	1.20
16	1.20	16	1.40
20	1.40	20	1.60
26	1.60	26	2.40
34	2.40	34	2.80
40	2.80	40	3.30
50	3.30	50	4.00
60	4.00	60	5.50


CRYSTALS FOR MICROS

32.768KHz	3.00	4.00MHz	2.70	10.00MHz	2.70
100KHz	3.00	4.43MHz	1.00	10.7MHz	2.70
200KHz	3.70	5.0MHz	2.70	16.00MHz	2.90
1.0MHz	3.60	6.0MHz	2.70	18.00MHz	2.90
1.008MHz	3.50	6.144MHz	2.70	18.432	2.90
1.8432MHz	3.00	7.0MHz	2.70	36MHz	2.90
2.00MHz	1.50	7.168MHz	2.50	48.0MHz	2.70
2.45760MHz	3.05	8.00MHz	2.70	100MHz	2.90
3.276MHz	2.70				



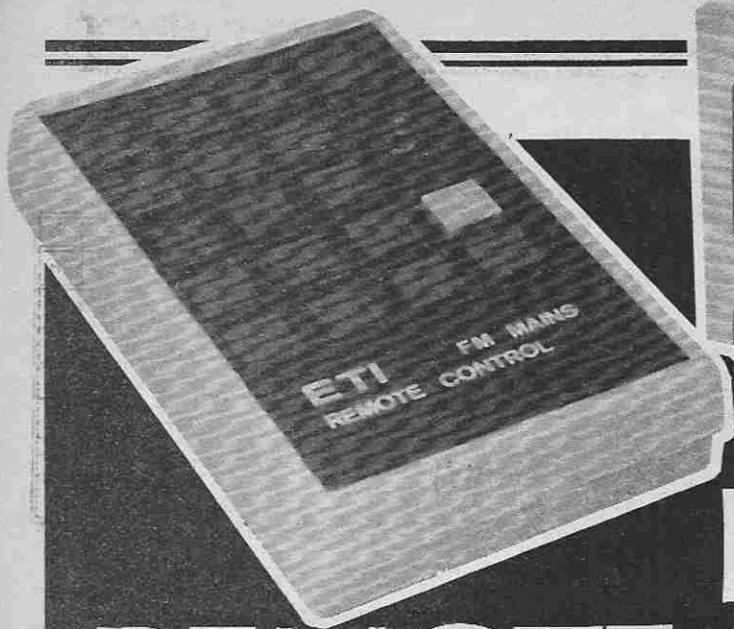DEPT. ET101
59/61 THEOBALDS RD.
LONDON WC1
TEL: 405 5420/2113
TELEX 24224. REF: 1422
ALL PRICES EXCLUDE VAT





FM MAINS REMOTE CONTROL

Control your home without leaving the comfort of your armchair with this cunning system that sends instructions down the mains. Project development by Steven Ramsahadeo.

Remote control on a small scale is fairly simple to implement, these days — ETI has published many circuits on this topic. These have ranged from simple ultrasonic on/off switches, to 'dedicated' hard-wired systems such as the Beast train controller, to general purpose, multifunction infra-red devices. The disadvantages of these systems were that their use was restricted to one room, with the exception of the Beast; but then you want to control model trains from another room?

Remote control over a reasonable distance needs a rethink about the methods available. Infra-red and ultrasound are both out; light only travels in straight lines, and an ultrasonic system that could operate throughout the house would need an impossibly powerful transmitter — even if you left all your doors open! Radio control is also out of the question, since it may only be lawfully used to operate models, not to mention the interference and bandwidth problems that would occur if everyone started using such a system.

It seems that the only choice left is to run lengths of cable to all the devices that need to be controlled, and use electrical control signals. All that money for expensive copper wire, all the work involved in laying the cable runs beneath floorboards and plaster, all the redecorating; this idea doesn't seem to have much going for it either.

Send A Cable

Fortunately, almost every home in the UK already has a suitable distribution system installed; the mains supply. This network links all the rooms in the house (and probably the shed and garage too), is hidden from sight and yet has access points exactly where you want them — at the appliances you wish to control. A single transmitter can be plugged in to a power socket anywhere in the house and superimpose control data onto the 50 Hz mains using radio frequency FM signals. These signals will be picked up by any receivers that are also connected to the mains, and after suitable decoding the selected appliance can be made to turn on or off.

Such a system was first discussed in our House Wiring feature in the June 80 ETI. At that time we postulated a six bit data word that could address any one of the 16 different devices and convey up to four different instructions; RF filters (with a suitable voltage/current rating) were to be fitted in the feeder lines to the house wiring to prevent interaction with a neighbour's system.

The design presented here takes a somewhat different approach. Suitable inductors for the filter network are not available, so the interference problem has been tackled by using a nine bit data word. Four bits define one of 16 system or house codes, with each house in a street on

the same mains phase choosing a different code. Another four bits define one of 16 appliances, with the final bit being the on/off command. Your receiver modules are all set to the same house code, but different appliance codes; thus you can switch appliances individually but not trigger receivers in neighbouring houses.

Pressing Matters

In general, two key closures are required to send an instruction with this system. First press and release the key corresponding to the appliance you wish to control, then press either the on or off key. After a quarter of a second or so (the time taken to transmit the complete data word plus its synchronisation bits), the relay in the chosen unit will change state, operating the microswitch. The system of mains switching has been chosen to provide isolation, and the SW1/RLA assemblies will be made available by the kit supplier (see Buylines). Naturally the number of bits means that data must be transmitted serially, and the system requires information to be latched, combined into a single data word, synchronised to the mains zero-crossing points... a lot of circuitry which results in the use of the ubiquitous chip, in this case two custom-designed ICs which will only be available from the source mentioned in Buylines.

Once latched into one or other state, the receivers will not switch over unless they receive a specific

command or are disconnected from the mains (receivers always assume the off state on power-up). This means you can unplug the transmitter to move it around the house without upsetting any of the slave modules. Using a switched 13 A socket (the switch being wired in parallel with the microswitch) allows manual override of the slave module.

Some RFI may be picked up on radios during operation of the transmitter but this only lasts for the duration of the keypress and will cause no problems.

Construction

Construction of the transmitter should present few problems. The PCBs are specifically designed to fit in a small hand-held enclosure (see Buylines). The case comes apart in two sections; the keypad is fixed in the top half and the control circuit in the other half. These are connected with a short length of ribbon cable and two 14-way header plugs terminated at each end.

We recommend the use of our PCBs, especially for the keypad which is a double-sided board.

Start construction by assembling the 18 push-buttons and LED1 on the top side of the PCB (side A). The 14 pin header socket is mounted on the opposite side and is soldered approximately 2 mm above the surface of the board, allowing just enough space to solder the tracks on this side. Note that wherever corresponding tracks are found above and below a pad, both sides should be soldered to complete the connection. When the keypad is built make a visual check for any solder bridges or dry joints; if all is well you can begin construction of the control circuit. Assemble all components according to the overlay, observing the orientation of the semiconductor devices and electrolytic capacitor. There are two points to note here; C3 is bent at right angles to lie flat on the PCB (as shown by the photographs), and rubber or PVC sleeving should be used to insulate the mains connection on the PCB.

As there is very little height available the best way of securing the control circuit PCB is by double-sided sticky pads. To give a professional appearance a grid can be cut out from a self-adhesive aluminium sheet to match the keypad, which can then be stuck to the front of the case. The keypad is held in place by a few drops of Superglue at each corner. When doing this it is worth checking that there is adequate clearance between the header socket and C3. This step

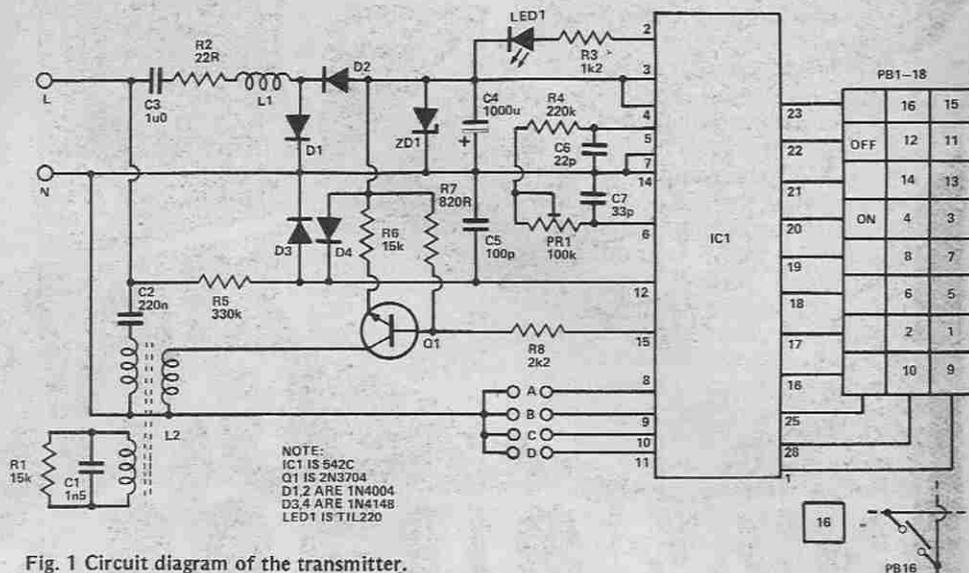


Fig. 1 Circuit diagram of the transmitter.

HOW IT WORKS

TRANSMITTER

The transmitter is built round a customised IC with 16 system codes (selectable by wire links to pins 8-11) and a separate code for addressing up to 16 remote slave modules in your home or office. The system codes are necessary to allow you to switch lights or appliances attached to the slave modules on or off without activating slave modules being operated by neighbours.

The keyboard matrix is scanned at 3.8 kHz; when a key is pressed its code is combined with the system code. Multiple key connection is controlled by the IC. The single digital message is then sent to the transmitter section which generates 120 kHz signals to pulse-position modulate the AC line. The digital code serial output has to be synchronised to the 50 Hz AC signal, so the chip incorporates a zero-crossing detector. The message, now synchronous with the mains waveform, is clocked a bit at a time on the zero crossing of the wave. It contains nine bits of information; a four bit system code and a five bit matrix (keyboard function) code. Each message is transmitted in true and in inverted form on successive half-cycles of the AC waveform. A logic 1 bit consists of three 1 ms bursts of 120 kHz signal at 200 us after the zero crossing of each phase. A logic 0 bit is indicated by no signal for that half-cycle. To synchronise the receivers with the transmitter a trigger code of three successive logic 1 bits followed by a logic 0 bit is used. The

complete message takes 11 full AC cycles (220 ms) to complete.

The line attachment is made by a transformer (L2) and capacitive coupler (C2). The transmission can range down the wiring on the domestic side of your electrical system and is bounded by the Electricity Board's transformer. This gives the possibility of controlling slave modules in a number of houses as there can be six or seven on each transformer — hence the system or house code.

The power supply for the circuit comes from C3, R2 and L1 all in series. The mains is rectified negatively by D2, with shunt diode D1 providing DC restoration. The supply voltage, regulated by ZD1, is stored on C4. The timing signal is limited by R5; it is clamped in the positive direction by D4 connected to the common line, and in the negative direction by D3 connected to the negative side of the power supply. This produces an 18 V square wave. C5 is provided to eliminate high frequencies from this section, such as the 120 kHz transmissions.

C2 isolates one side of the transmitter coil from the mains and thereby allows the coil to produce signals across the mains. Q1 provides the drive signals; R7 and R8 set the drive level to the transistor, while emitter resistor R6 provides stabilisation. The oscillator components are R4-C6-C7-PR1, the latter component setting the frequency.

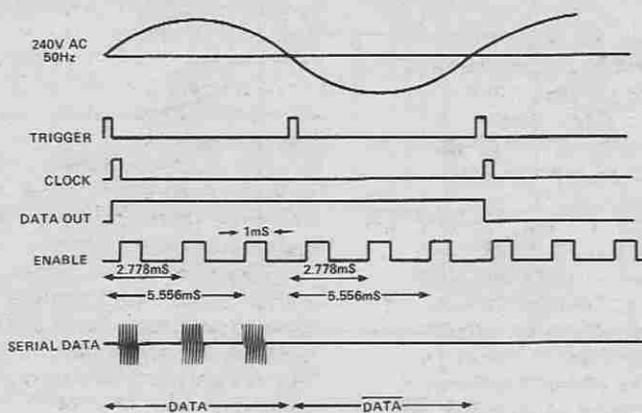


Fig. 2 The timing diagram for the transmitter signals.


should only be done when the system has been fully tested.

The most practical method of housing the receiver unit is in an MK double surface-mounting box (see Buylines). This particular box accepts two single 13 A sockets (only one used) enabling the PCB to fit in the left side and the switch mechanism on the right beneath the 13 A output socket.

No problems should be encountered in constructing the receiver PCB provided you follow the same precautions as for the transmitter. The board is mounted on three 1/4" spacers. The mains lead can be passed through any one of the 'knockouts' located around the edge of the box. Heavy gauge wire (ie 13/0.2) should be used to connect the switch mechanism and the 13 A output socket.

The appliance module, which is supplied as a ready built unit, is fixed on the blanking plate. The connections are passed through a small hole and terminated at the points indicated on the receiver PCB.

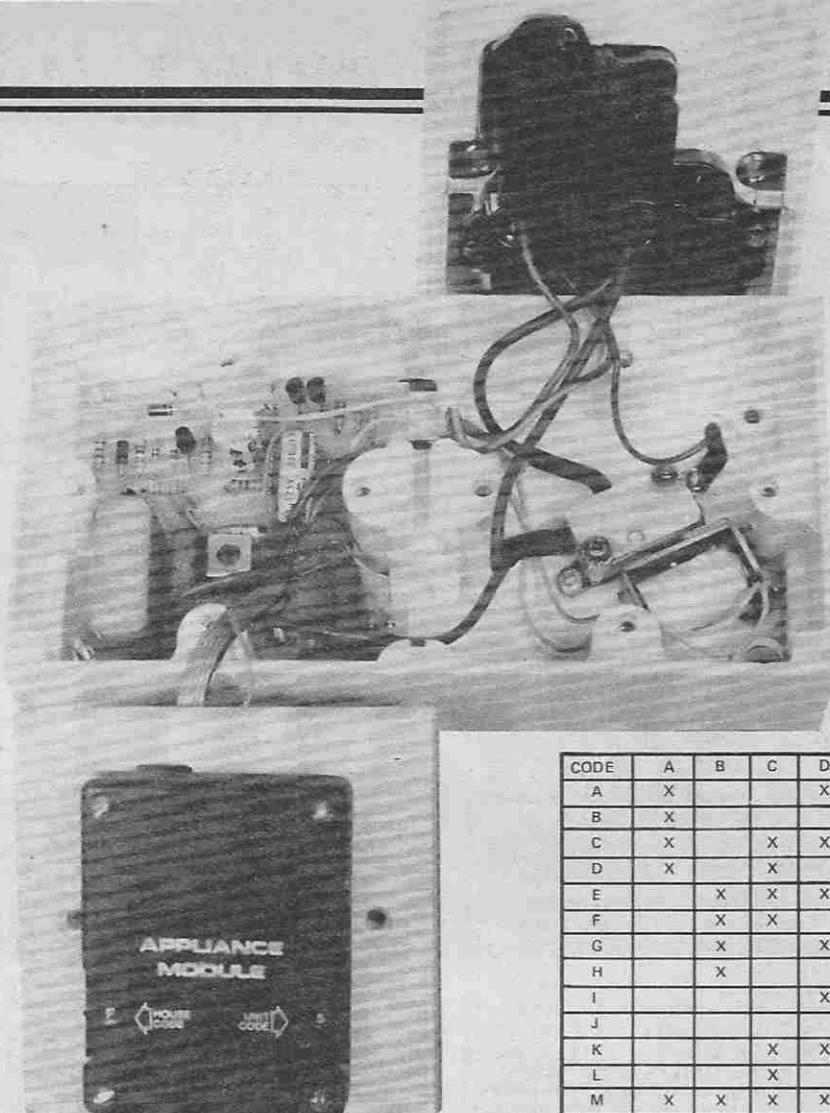Setting up the system is a matter of adjusting the presets in the transmitter and receiver so that the frequency of the clock oscillator is 120 kHz. Range of the system should be good enough for any practical purposes — the prototype unit was able to consistently switch a light on and off when the transmitter was in a bedroom and the receiver was in a shed at the end of a 100' garden.



Inside the receiver. The PCB fits in one half of the box, the switch/relay mechanism in the other.

CODE	A	B	C	D
A	X			X
B	X			
C	X		X	X
D	X		X	
E		X	X	X
F		X	X	
G		X		X
H		X		
I				X
J				
K			X	X
L			X	
M	X	X	X	X
N	X	X	X	
O	X	X		X
P	X	X		

Fig. 3 System code selection table. X means insert a link on the transmitter board (Fig. 6).


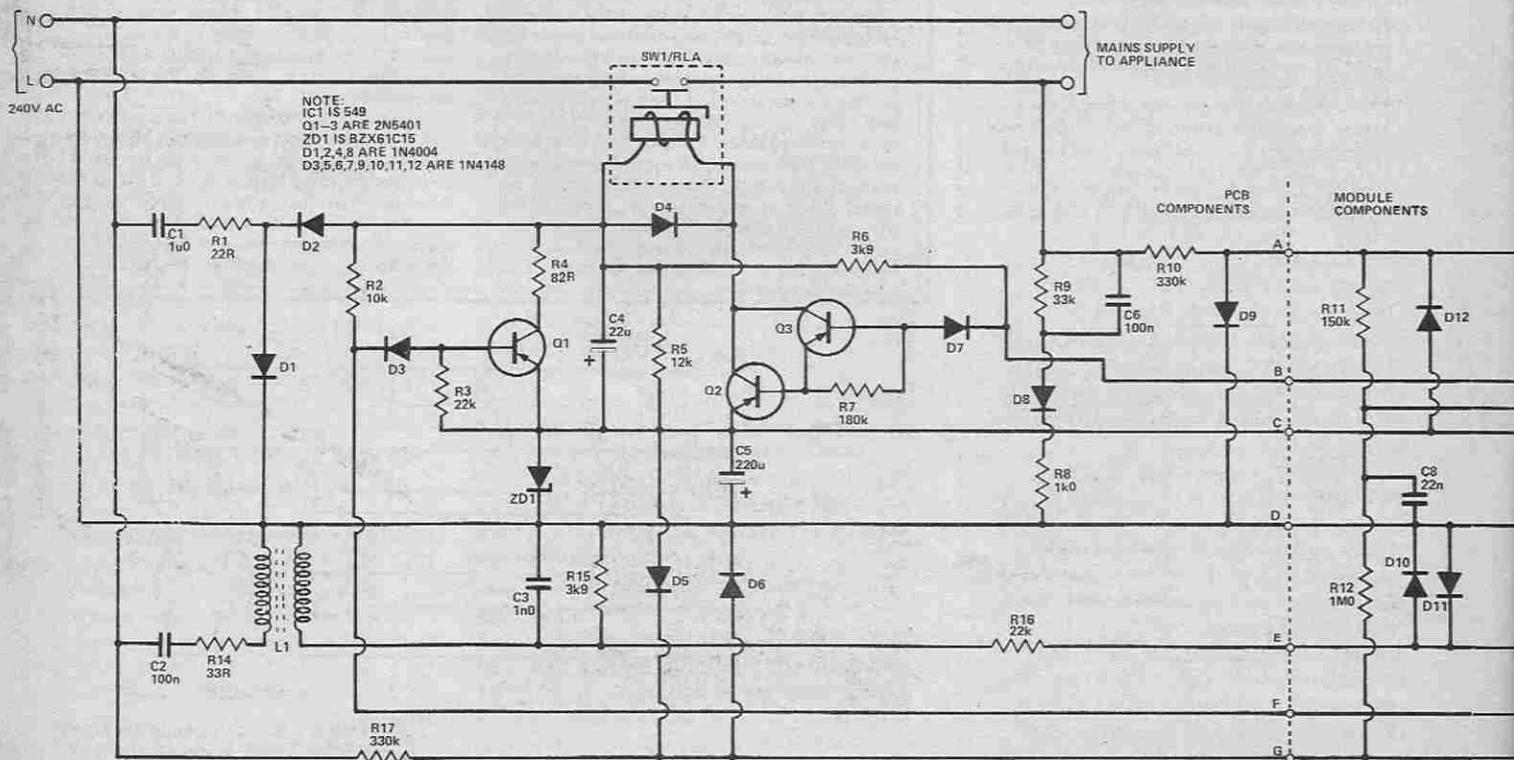


Fig. 4 Circuit diagram of the receiver. Components to the right of the dotted line are supplied ready-mounted on the appliance module.

PROJECT : Mains Remote Control

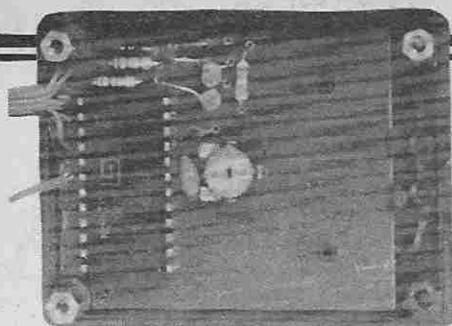

HOW IT WORKS

RECEIVER

As with the transmitter, a tuned circuit is connected across the mains; signals are picked up by L1 via R14 and mains isolation capacitor C2. The coil is tuned by C3 and R15; its output is clipped by D10,11 and capacitively coupled by C7 into the receiver chip (IC1). Once again synchronisation to the mains is provided by a resistor (R17), the signal being clamped to the 15 V negative supply and the common line by D5 and D6 respectively. The oscillator components are R13-C9-C10-PR1.

Two rotary hexadecimal switches code the receiver in the same way as the transmitter — SW2 selects the channel number and SW3 the device number.

The power supply is similar to that of the transmitter. D2 rectifies the mains with D1 providing the shunt path for R1-C1. Normally Q1 is turned on and connects the very negative supply section (ie D2 anode) to C1 and ZD1, which smooth and regulate the supply to the IC. The Darlington pair Q2-Q3 are turned off, and hence RLA is off and no power is supplied to the appliance via SW1. R5 ensures that C4 is discharged.

When IC1 detects a valid 'turn-on' signal, it momentarily switches the control line to the base of Q1 high, turning the transistor off. This action rapidly charges C4; shortly afterwards IC1 switches on the Q2-Q3 Darlington, so that RLA is connected between the regulated and unregulated supply rails and turns on. C4 discharges rapidly through the relay and the Darlington, giving a switch-on boost that makes sure the relay pulls in. SW1 is now closed and the load is energised. A 'turn-off' signal causes IC1 to switch off the Darlington, cutting the drive to the relay — D4 is connected across the relay to suppress voltage spikes.

R8-R9-C6-D8 provide a low impedance supply to the positive side of C1-ZD1 when SW1 is closed, to help hold the relay in. R10 feeds a clipper circuit that senses when the switch is closed or the socket has a load in it.

PARTS LIST

TRANSMITTER

Resistors (all 1/4 W, 5% except where stated)

R1,6	15k
R2	22R 1/2W
R3	1k2
R4	220k
R5	330k
R7	820R
R8	2k2

Potentiometer

PR1	100k miniature horizontal preset
-----	----------------------------------

Capacitors

C1	1n5 polystyrene
C2	220n 250 V AC polyester
C3	1u0 400 V radial polyester
C4	1000u 25 V axial electrolytic
C5	100p ceramic
C6	22p ceramic
C7	33p ceramic

Semiconductors


IC1	542C
Q1	2N3704
D1,2	1N4004
D3,4	1N4148
LED1	TIL220

Miscellaneous

PB1-18	push-button switches
L1	150uH
L2	Toko 1A1011
14 pin DIL plug (one off); ribbon cable; case.	

BUYLINES

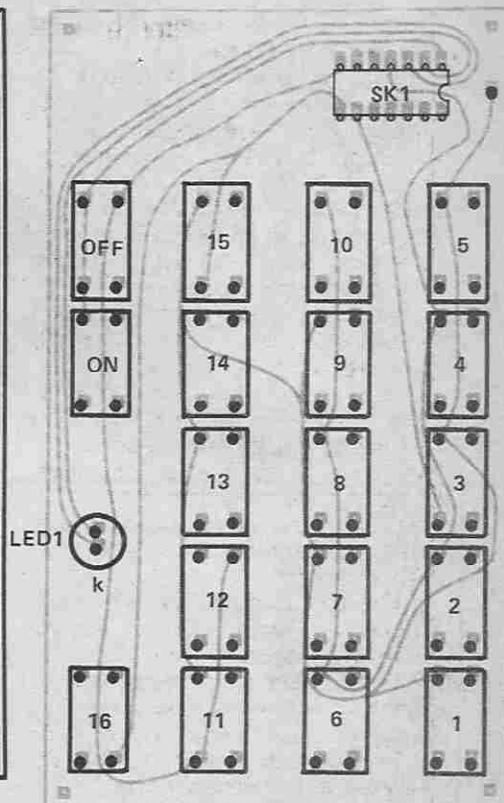A kit of parts for the FM Mains Remote Control System is available from Rockway Ltd, 1 Station Road, Twickenham, Middlesex TW1 4LL (telephone 01-892 7044). The kit contains one transmitter unit and two receiver units and costs £99 plus VAT and carriage. The receiver units will also be available separately.



NOTE:

k = CATHODE
● = THROUGH-BOARD LINK

Fig. 5 Overlay for the keypad. Note that SK1 is mounted underneath the board, and that all component pins are soldered on both sides of the double-sided board.



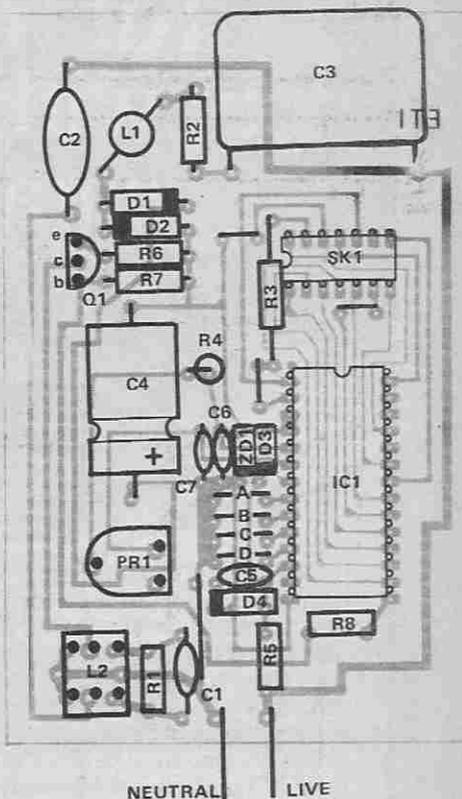
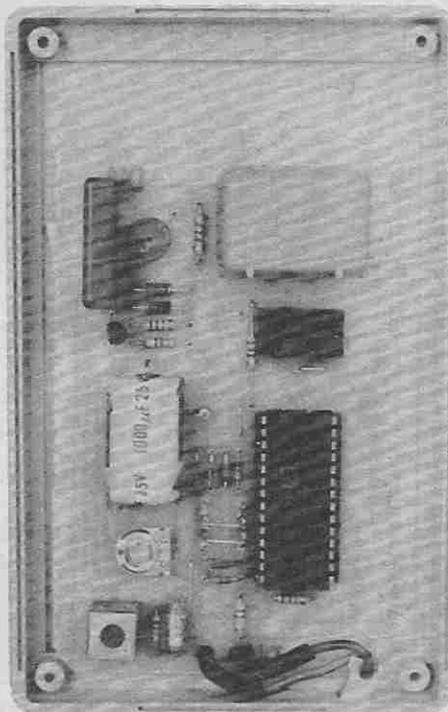


Fig. 6 Overlay for the transmitter board. Make links A, B, C, D as shown in Fig. 3.

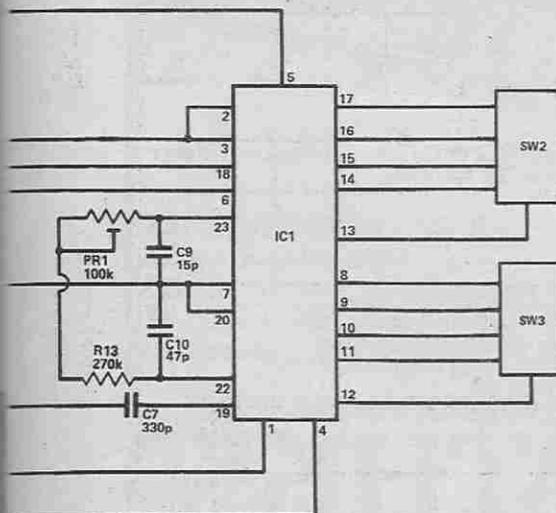DANAVOX ARE ALWAYS COMING UP WITH SOUND IDEAS.



**STETOCLIP
JUNIOR 60
HEADSET**

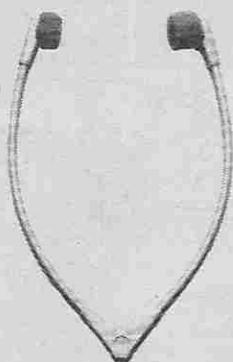

**STETOCLIP
LIGHTWEIGHT
HEADSET**




**SENIOR
STETOCLIP
HEADSET**



**STETOCLIP
GEMINI
HEADSET**



**STETOMIKE
HMT 808**

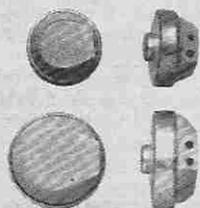


**STANDARD &
SUB-MINOR
EARPHONES**




**PLASTIC
EARHANGERS**




**DANAMIC FIDELITY
EARSET**

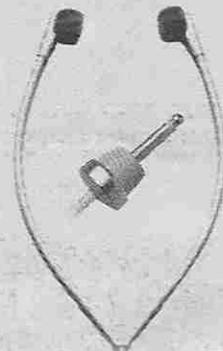

**STETOTUBE
HEADSET &
SOUND PLUG**

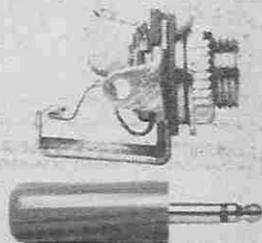

**2,5mm 3,5mm
JACK PLUGS &
SOCKETS**

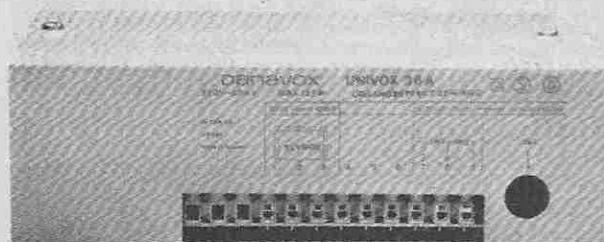

INDUCTIVE LOOP AMPLIFIER TYPE 36A



**FIELD STRENGTH
TESTER FSI**



**SUBMINIATURE
SWITCHES**



**DANASOUND
HEADSET**

The Danavox policy has always been one of constant improvement. Our refinement, development and research has enabled us to offer an advanced range of components and accessories for dictation machines, tape recorders, tele-communications, hearing aids and electro-acoustic equipment. All our products are built with care and precision. And all carry the Danavox guarantee.

For more information about any Danavox product, contact John Carter.

Danavox

DANAVOX (Gt. Britain) Ltd.,
1 Cheyne Walk, Northampton. NN1 5PT
Tel: (0604) 36351 Telex 312395

FOR A SOUND DIAGNOSIS...

New CLEAN N CHECK is a unique and complete cassette machine maintenance pack.

The patented *Drive Analyser will check in seconds the drive mechanism of your cassette machine to locate faults which can lead to damage and breakdown.

If the Drive Analyser shows no fault, then you can confidently use the tape head and capstan cleaning solutions provided to ensure optimum performance.

Proper maintenance of any machine should consist not only of cleaning, but also of checking the mechanism.



The Clean-n-Check pack contains

- Head cleaning solution.
- Capstan cleaning solution.
- Cotton buds and holder.
- Drive analyser cassette with indicator registering as faulty/normal/service required soon, on play/rewind/FFwd functions of your cassette player.

The check drive analyser is presently being used by growing numbers of hi-fi service organisations.

Clean-n-Check™

"Because good sound...sounds good!"

TO: TECHNOLOGY RESOURCES LTD, Dept 654
HENDON ROAD, SUNDERLAND SR9 9XZ.

Please send me CLEAN-N-CHECK packs
@ £4.50 each (incl. p&p). Total enclosed: £

NAME:

ADDRESS:

(Allow 14-21 days delivery. 28 day money back guarantee)
Registered in England No 1428994

This model is not suitable for use with car cassette players. ETI.10.81

HAMEG

OSCILLOSCOPES

Top Performance
In Every Range



HM 307

HM 307

£ 138

Y: Bandwidth DC-10MHz (-3dB) • Sensitivity 5mV-20V/cm (±5%)
X: Timebase 0.2s-0.2µs/cm (±5%) • Triggering 2Hz-30MHz (3mm)
Built-in component tester • Calibrator • Screen 6x7cm • 1kV

HM 203

£ 220

Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 5mV-20V/cm (±3%)
X: Timebase 0.2s-40ns/cm incl. x5 Magn. • Trig. 3Hz-30MHz (5mm)
Dual trace • X-Y Operation • Calibrator • Screen 8x10cm • 2kV

HM 412

£ 350

Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 2mV-20V/cm (±3%)
X: Timebase 2s-40ns/cm incl. x5 Magn. • Trig. DC-40MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Sweep delay • Overscan, Trigger, Delay indications • Trigger filter
Z-Modulation • Calibrator • Graticule illumination • 2kV

HM 512

£ 580

Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/cm (±3%)
X: Timebase 5s-20ns/cm incl. x5 Magn. • Trig. DC-70MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot + Reset • Overscan, Trigger, Ready, Delay indications
var. Hold-off • Z-Modulation • Graticule illumination • 12kV

HM 812

£ 1,458

Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/div. (±3%)
X: Timebase 5s-20ns/div. incl. x5 Magn. • Trig. DC-70MHz (0.5div.)
Dual trace analog storage with var. Persistence and Auto-Storage
Algebr. addition • X-Y Operation • Screen 8x10div. (7.2x9cm)
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Overscan, Trigger, Ready, Delay, AS indications
var. Hold-off • Z-Modulation • X-Guard circuit • Calibrator • 8.5kV



HM 812
Storage

For more information
contact:

Prices U. K.
List Ex. VAT

HAMEG LTD. 74-78 Collingdon Street LUTON
Bedfordshire LU1 1RX Telephone (0582) 413174 Telex 825484

ENGINEER'S GUIDE TO BASIC

Despite the various alternatives, BASIC is still the most universally accepted programming language; unfortunately there are almost as many dialects as there are machines. This new series by Stewart Fleming will help you pick your way through the programming jungle.

The purpose of this series of articles is two-fold: to provide the reader with a detailed introduction to the BASIC language (where we will look at the syntax or 'grammar' of the language and illustrate this with lots of interesting applications); and to provide a reference manual of the differences between the versions of BASIC as offered by some of the better-known microcomputer manufacturers together with an indication of the capabilities and limitations of the hardware concerned.

The reader will therefore be able to use this manual:

- to learn BASIC
- to help him decide which BASIC (and possibly which equipment) is most suitable for his proposed application. Thus we hope the articles will be particularly helpful to the first-time microcomputer buyer.
- as an aid in implementing on one machine a BASIC program which has been written for another machine.

Using The Articles

We hope then that this introduction to BASIC will be useful both to the absolute beginner and also to the more advanced programmer. Very little prior knowledge will be assumed of the reader and we will explain any technical terms as we go along.

The articles can be treated as a complete course in BASIC: they will cover all the important features of the language in a simple and concise way. Alternatively they can be used as a reference manual. We have included a section on the general principles of computer operation, and, if you are completely new to computing, it is suggested that you read this first — so that you will understand some of the 'whys' as well as the 'hows' of BASIC programming.

Finally we hope that the applications described will be both interesting and helpful and will be useful to you as models on which to base your own applications. Perhaps you will also be encouraged to come up with your own more elegant and efficient solutions (there will be a short section on programming 'style' and structured programming later on).

The best way to learn BASIC programming is by doing it! If at all possible, get hold of a microcomputer, and work through the illustrations and examples yourself on the computer. By the time you've got to the end of the series you should have a really good grasp of the BASIC language and of its potential applications.

Computer Operation

The way in which microcomputers and most minicomputers are organised (their 'architecture') is different from the organisation of the large computers ('mainframe' computers as they are called). This is partly because of differences in the way

the main functional units of the computer (the CPU, memory and the peripherals together with their interface units) are constructed and used and partly because of differences in the way these items are connected together using sets of communicating wires known as 'highways' or 'buses'. The statements which follow concerning microcomputers will therefore not all necessarily be true of the large computers (although the general principles of computer operation will still apply).

Figure 1 is a block diagram showing the main features of a microcomputer. The MPU (Microprocessor Unit) may be further subdivided into functional components as shown in Fig. 2.

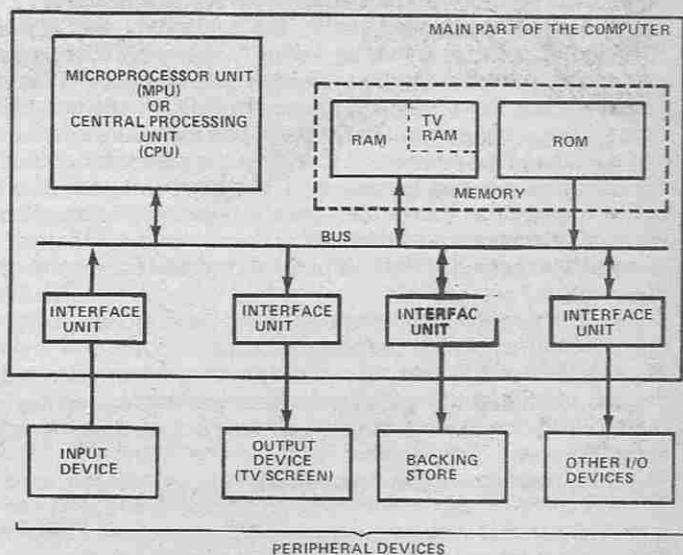


Fig. 1 Block diagram showing the hardware of a microcomputer.

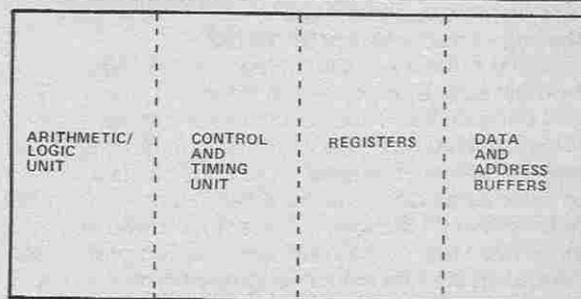


Fig. 2 The functional elements contained in the block marked Microprocessor Unit in Fig. 1.

Programs And Data

The purpose of a computer is to carry out instructions or operations on data that has usually been entered via an input device, and to communicate the results produced to the outside world. A variety of different instructions (the instruction set) will be available and by arranging for a sequence of instructions to be obeyed, or 'executed', one after the other, the computer may be used to perform tasks as diverse as the solution of a complicated mathematical equation and the control of the lighting and heating of a house. A set of instructions to perform a particular task is called a computer program. In all computing, therefore, there are just two types of items that are stored and used within the computer. These are:

- program instructions
- the data which the program instructions are to use.

With this in mind, we can now describe briefly the components of a microcomputer.

Down Memory Lane

Both program instructions and data are stored in the computer's memory. Actually, the very first computers that stored their program instructions internally — EDSAC and EDVAC (1943-1944) kept their instructions and data in separate memory areas — the so-called 'Harvard' architecture — but this was quickly replaced by the idea of a 'shared' memory introduced in 1945 by John von Neumann.

The computer's memory consists of locations, each of which can hold either a program instruction or an item of data (or part of an instruction or item of data). Each of these locations has a unique address — a number used to identify a particular location. Thus, if we have a 32K store ($1K = 2^{10} = 1024$) the addresses may be 0 to 32767. Memory comes in two types: ROM (Read Only Memory) and RAM (Random Access Memory).

We may deposit any valid instruction or data item into a RAM location (this is known as writing to memory), or we may get a copy of the information stored in a RAM location (this is called reading from memory). By contrast, ROM can be used only for the reading operation. ROM is used to hold instructions and data that are a permanent feature of the computer system. This information can be accessed but never altered. ROM holds, among other things, the 'operating system' — a program which is permanently resident within the computer, and which controls the running of the computer and certain fixed items of data.

In the context of microprocessors, the functions of an operating system will include the following:

- control over the selection and operating of input/output devices and file handling (this includes screen editing and interfacing with the screen control electronics and keyboard decoder)
- provision of error correction routines
- the calling of subroutines and programs as and when required. (Note that with some microcomputers, eg the PET, the BASIC interpreter is permanently stored in memory; in others, such as the Research Machines 380Z, the compiler has to be loaded by the operating system under user control)
- sending messages to the user
- obeying instructions sent by the user.

There is often a particular area of RAM dedicated for use by the main output device — the TV screen (also known as the CRT — Cathode Ray Tube). Each location in the TV, or video, RAM is associated with a particular part of the screen. This is an example of memory mapping. By altering the data items stored in the video RAM, different characters or graphics symbols are made to appear on the screen. The actual conversion of data in the video RAM to screen information is accomplished using the TV control electronics (which in some microcomputers works independently of the rest of the microcomputer) and which has been represented as an interface unit in Fig. 1. The control elec-

tronics actually accesses an area of ROM containing coded information needed to represent each of the different characters and symbols on the TV screen.

Processor Processes

The Central Processing Unit (CPU) is the part of the computer that takes the program instructions from store and obeys (or 'executes') them. Once an instruction has been obeyed, the CPU fetches the next instruction from store and executes that. Program instructions can be broadly classified as follows:

Load/Store These instructions transfer data from registers within the CPU to the memory and vice versa. (A register is an electronic device capable of storing an item of data — the glossary will give a more precise definition.) This family of instructions will also include those that move data between CPU registers, or put particular items of data into CPU registers.


Arithmetic/Logical/Shift These instructions perform operations on data held in registers within the CPU and in memory locations. A typical operation would be the addition of two numbers, one of which is assumed to be in a special CPU register called the Accumulator, the other number being in the memory address specified in the instruction. The result of the addition is put back into the accumulator. The Arithmetic/Logic Unit (ALU) carries out these operations.

Jump/Branch These are instructions to alter the normal sequence in which program instructions are executed.

Input/Output These instructions handle the input of information from peripherals and the output to peripherals.

The CPU, then, actually covers quite a lot of separate items. It includes the Control Unit (the part which actually fetches instructions from memory), decodes the instruction (decides which separate operations have to be carried out in order to obey the instruction), and sends the appropriate signals to the different parts of the computer. (The term 'microprogramming' — a method used by some control units to generate these signals — has absolutely no connection with the subject of this series which is the programming of microcomputers!) The process of fetching and executing program instructions is, in fact, all that computers ever do.

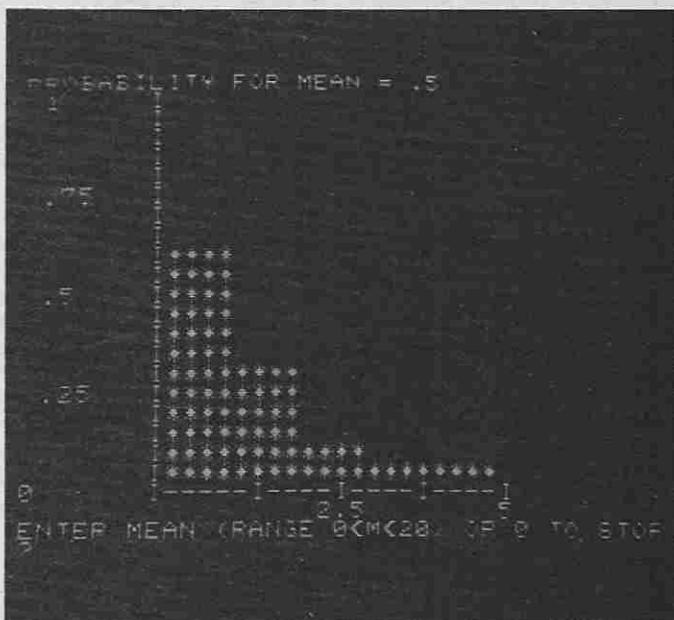As already mentioned, the CPU also has electronic circuitry known as the Arithmetic Logic Unit where arithmetic and



The program listed in Fig. 5 plots the Poisson distribution and gives this result on the screen of a PET computer. For a mean of 0.5 the graph peaks close to the y-axis at a fairly high value. ...

other operations on data are carried out. Another component of the CPU is the series of registers — internal memory locations which may be quickly accessed, and which are used to contain data and addresses which are needed by the CPU. The data and address buffers indicated in Fig. 2 are used to hold data 'in transit' between the CPU and the external memory address stored in the buffer.

Finally, in Fig. 2 the timer has been included as part of the CPU. The function of the timer is to send a steady stream of voltage pulses to the rest of the CPU and to other devices also. These pulses are used for controlling the timing of computer operations.

On The Periphery

A peripheral is any external device connected up to the

main part of the computer. (The computer here is taken to consist of the CPU, memory and any interface units). Examples are the keyboard, TV screen, floppy disc drive, cassette, graph plotter, strain gauge, light dimmer, robot and so on. The connection between peripheral and computer is normally via an interface unit. The purpose of the interface unit is to act as a 'go-between', thereby ensuring that the voltage levels and the form in which data is represented in the peripheral can be made compatible with those of the computer. Standards for interface units have been set; the RS-232-C, IEEE-488 and the self-styled Centronics interface are some examples.



Fig. 3 BASIC or other high level program instructions cannot be executed until they are compiled or interpreted into a form the MPU can understand — machine code.

Bus Conductors

The bus is a set of wires connecting all the components of the microcomputer, together with the rules about which wire is to carry which item of information. Some wires carry data, some carry addresses (or locations) and some carry control information (eg indicating whether the CPU is reading or writing the data item).

Storage

The programs that we have been talking about so far are nothing like BASIC or FORTRAN or the other 'English-like' languages. They are in machine code — ie the instructions are stored in locations consisting of eight or 16 electronic 'switches' that are either on or off. This sequence of on or off switches can be represented to us as '1s' and '0s' — a 1 corresponding to on and 0 corresponding to off. Each instruction will have its own unique pattern of 0s and 1s. The individual 0s and 1s are bits and a collection of eight bits is a byte.


Similarly, data is stored as a set of bits — normally one byte per character. Thus the number '3' and the letter 'A' will both have their own code or bit-pattern. Copies of these bit-patterns can be moved from one register or memory location to another under the control of the CPU regardless of whether the pattern represents program instructions or data. When an instruction is to be obeyed, it is read from its location in memory into a register in the Control Unit. The Control Unit then decodes the pattern of 0s and 1s in this register and takes the appropriate actions as already described — thereby executing the instruction.

High-Level Languages


We have seen that there are only two types of item — program instructions and data. A set of program instructions consisting of 0s and 1s is a machine code program. These are the only programs that are ever executed.

A high-level program, such as a BASIC program, will never actually be executed by the computer. It will be used as data by a special machine code program called a compiler or an interpreter which produces, as output, corresponding machine code instructions which will be stored away (in RAM or on an external storage device) and may be subsequently run or executed.

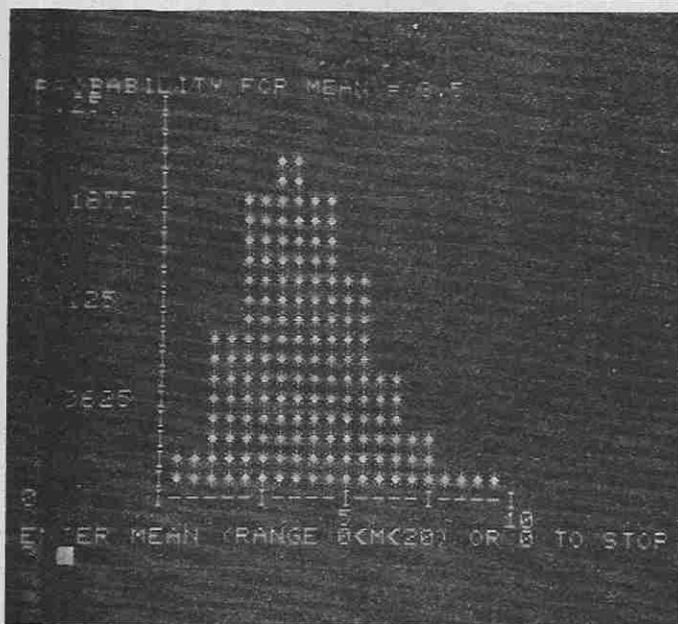The difference between a compiler and an interpreter is that the compiler converts the high-level language program into machine code all in one go, whereas the interpreter converts high-level language instructions to machine code one at a time as the program is being executed. The versions of BASIC that we will be looking at are all interpreted.



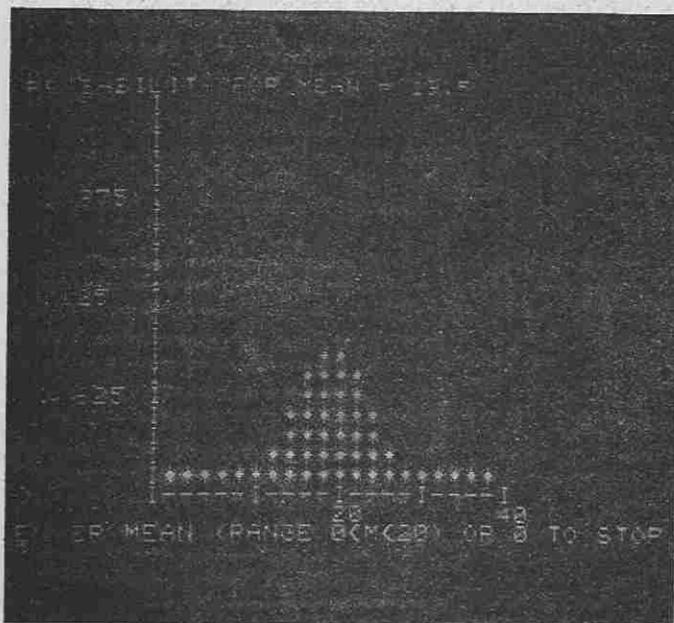... but as the mean increases (here it's 3.5), the peak shifts towards the right and its value decreases, the axis scales automatically changing to suit...



... until at a mean of 19.5 this squat symmetrical shape is obtained. Once again the x and y scales have 'auto-ranged' their values to accommodate the graph in the screen area.

BASIC instructions are stored over several bytes. The details vary from microcomputer to microcomputer, but Fig. 4 is representative. The compressed BASIC text uses 'tokens' to represent keywords, eg "P" means "PRINT". The link contains an address used by the interpreter in the sequencing of program instructions; it indicates where to find the start of the next line of BASIC text.

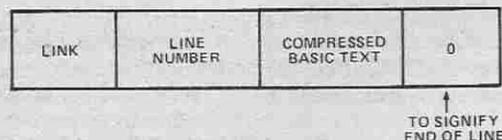


Fig. 4 BASIC programs are generally stored in the microcomputer memory in a form such as this.

For each BASIC instruction, a series of machine-code instructions — known as a subroutine — will be executed. Once these instructions have been obeyed, the next BASIC instruction is interpreted. BASIC, when interpreted rather than compiled, takes longer to execute, but the program can be stored in less memory.

Commands And Statements

Basic instructions are of two types: commands and statements. Commands specify some action which is to be performed on a program; eg the execution of the program or the listing of program statements. Statements specify operations to be performed by the program, or provide information relevant to the program.

Both commands and statements may omit line numbers: normally, commands do not have them, but statements do. (A statement with line numbers is called a program statement; if it doesn't it is called a direct statement). When using direct

statements, the computer is rather like a super-calculator — statements are executed as soon as they are keyed-in.

We are now in a position to look briefly at a typical BASIC program.

Program Notes

Figure 5 is an example of a complete BASIC program. It plots a graph of the Poisson distribution, a function used in statistics. Details of this distribution can be found in most statistics books; if you're interested, the formula is

$$Pr(x) = \frac{m^x \cdot e^{-m}}{x!}$$

where m is the mean of the distribution. The program uses a restricted subset of BASIC and should work for most 'floating-point' versions of the language. Ways of implementing such a program in 'integer' BASIC will be discussed in later issues. If your microcomputer supports floating-point BASIC, you should try running this program (it was actually tested using a PET). Note that there may be slight problems with some machines because of different screen formats — for example, the top nine lines will be lost on a TRS-80 because its screen is only 16 lines deep, not 25.

Those of you who are familiar with BASIC and have a detailed knowledge of a particular version would probably write a rather different program to this, but this example nevertheless illustrates how quite attractive results can be obtained using just a few BASIC keywords: DIM, REM, PRINT, INPUT, FOR...NEXT, IF...THEN, STOP, END and RUN and the functions EXP, INT, LOG and TAB. These will be explained fully in later issues. We will also be discussing the variations that can occur in different versions of BASIC, and looking at BASIC programming structures and techniques, programming style, and the conversion of programs from one version of BASIC to another.

```

100 DIM B$(20,20),A(40)
110 PRINT "POISSON DISTRIBUTION PROGRAM"
120 PRINT "===== "
130 PRINT
140 PRINT "ENTER MEAN (RANGE 0<M<20) OR 0
    TO STOP"
150 INPUT M
160 IF M=0 THEN STOP
170 IF M>=20 THEN 140
179 REM **CALCULATE POISSON PROBABILITIES**
180 LET Z=1
190 LET A(1)=20*EXP(-M)
200 LET Y=A(1)
210 FOR X=2 TO 40
220 LET A(X)=(A(X-1)*M)/(X-1)
229 REM **WORK OUT VERTICAL RANGE*****
230 IF A(X)<Y THEN 250
240 LET Y=A(X)
250 NEXT X
260 LET Y=INT(Y)+1
269 REM **WORK OUT HORIZONTAL RANGE*****
270 FOR X=1 TO 40
280 IF A(X)<Y/20 THEN 300
290 LET Z=X
300 NEXT X
309 REM **WORK OUT VERT. AND HORIZ. SCALES**
310 LET V=0.4*(Y+INT(4/Y))-0.2
320 LET W=2*(2-INT(LOG(Y)/LOG(2)))
330 LET H=0.4*(Z+INT(4/Z))-0.2
340 LET H=2*(2-INT(LOG(H)/LOG(2)))
349 REM **INITIALISE ARRAY*****
350 FOR C=1 TO 20

```

```

360 FOR B=1 TO 20
370 LET B$(C,B)=" "
380 NEXT B
390 NEXT C
399 REM **ENTER VALUES TO ARRAY*****
400 FOR X=1 TO 20
410 LET Q=INT(V*A(INT((X-1)/H)+1)+0.5)
420 IF Q=0 THEN 460
430 FOR J=1 TO Q
440 LET B$(J,X)="*"
450 NEXT J
460 NEXT X
469 REM **PRINT GRAPH AND VERTICAL AXIS**
470 PRINT "PROBABILITY FOR MEAN =" ;M
480 FOR K=20 TO 1 STEP -1
490 IF INT(K/5)<K/5 GOTO 520
500 PRINT K/(20*V);TAB(7);"I";
510 GOTO 530
520 PRINT TAB(7);"I";
530 FOR J=1 TO 20
540 PRINT B$(K,J);
550 NEXT J
560 PRINT
570 NEXT K
579 REM **PRINT HORIZONTAL AXIS*****
580 PRINT "0      I-----I-----I-----I-----I"
590 PRINT TAB(17-INT(0.99-INT(10/H)+10/H));
    10/H;TAB(27);20/H
600 GOTO 140
610 END

```

Fig. 5 This simple example program should run on most microcomputers. ETI

ALWAYS A CHANGING RANGE OF OSCILLOSCOPES, COMPUTERS, TERMINALS, ETC.

- Item No.
- 1 TEKTRONIX STORAGE OSCILLOSCOPE type 549 with 1A1 - 30MHZ £425
 - 2 TEKTRONIX DUAL TRACE OSCILLOSCOPE type 581A with type 82 plug-in, 85 MHz £246
 - 3 TELEQUIPMENT OSCILLOSCOPE type D54, DB 10MHZ, Brand new £225
 - 4 TELEQUIPMENT OSCILLOSCOPE type D51A, Dual Trace 10MHZ £225
 - 5 SCOPEX OSCILLOSCOPE type 4D10, Dual Trace 10MHZ £170
 - 6 PHILIPS FM STEREO GENERATOR type PM6456, Separate L&R Signals Carrier Freq 100MHz +/- 1%, RF O/P 3mV pk-pk £150
 - 7 ADVANCE DIGITAL MULTIMETER ALPHA II, DC/AC £30
 - 8 MARCONI STANDARD SIGNAL GENERATOR type TF144H 10KHZ-72MHZ £195
 - 9 HEWLETT PACKARD DC CURRENT SOURCE 6181B £168
 - 10 SCHUMBERGER AUTOMATIC COUNTER type FB2602 DC-50MHZ £135
 - 11 DECCA (KORTING) COLOUR BAR GENERATOR type 82515 £125
 - 12 SIEMENS FREQ METER 450-1000 MHZ £175
 - 13 HEWLETT PACKARD AUDIO OSCILLATOR type 204B £120
 - 14 HEWLETT PACKARD AC VOLT METER type 400E £125
 - 15 AVO MULTI METER type 71 £35
 - 16 KEITHLEY ELECTROMETER type 800A £50
 - 17 MARCONI WIDE RANGE OSCILLATOR TF1370, 10KHZ-10MHZ £90
 - 18 RACAL H.F. SELECTIVE ANALYSER type 9056 £350
 - 19 HEWLETT PACKARD POWER SUPPLY type 6214A 0-12V; 0-1.2A, NEW £85
 - 20 TINSLEY FREQUENCY SELECTIVE DETECTOR AMPLIFIER type 5710 £25
 - 21 PITMAN ELECTROMETER type 437 £50
 - 22 COUTANT DIGITAL VOLT METER type CDV 200A £40
 - 23 VERNER DOUBLE PULSE GENERATOR type TSA 628 £50
 - 24 MARCONI AM/EM MODULATION METER type TF2300, 4MHZ-1GHZ £375
 - 25 BRANDENBURG HIGH VOLTAGE METER 0-30KV type 88M £50
 - 26 RANK ABENA E.H.T. METER 0-30KV £40
 - 27 WEIR MINIREG POWER SUPPLY type 401-1, 0-30V; 0-1.5A £30
 - 28 MARCONI (SANDERS) MICROWAVE POWER METER type 6598 with probe £225
 - 29 RHODE & SCHWARZ INDUCTANCE METER LRT, 0N6100 £25
 - 30 E.M. WAREHAM DC LOG CONVERTOR type S12 £25
 - 31 ADVANCE DIGITAL MULTIMETER type DMM2 £90
 - 32 FARNELL DIGITAL MULTIMETER type DM131 £90
 - 33 FEEDBACK FUNCTION GENERATOR type FG600 Sine/Square/Triangle £100
 - 34 GRIFFIN SIGNAL GENERATOR & AMPLIFIER 1HZ-100KHZ £150
 - 35 MARCONI TUNABLE REJECTION FILTER type TF2334 £110
 - 36 TEKTRONIX SAMPLING PLUG-IN type 1S1 £200
 - 37 BRADLEY DC SIGNAL GENERATOR type 123 £80
 - 38 FLUKE VOLT METER type 623 £50
 - 39 MUIRHEAD WAVE ANALYSER type K-134-A £65
 - 40 PHILIPS COMPARTOR 278KHZ £40
 - 41 SOLARTRON/SCHUMBERGER COMPUTING VOLT METER type JM1776 £60
 - 42 HEWLETT PACKARD DIGITAL VOLT METER type 3440A £55
 - 43 RACAL AUTO FREQUENCY CONVERTOR type 803R 500MHZ £30
 - 44 AVO UNIVERSAL BRIDGE type 7 £80

- 45 PSI - RMS VOLTMETER type A1301 £80
- 46 STODDART RADIO INTERFERENCE & FIELD INTENSITY METER type N-M52A £140
- 47 MARCONI (SANDERS) LEVELLING AMPLIFIER type 6587 £250
- 48 MARCONI DISPLAY OSCILLOSCOPE type TF2212 £100
- 49 BRANDENBURG PHOTOMULTIPLIER POWER SUPPLY 472R, 0-2KV £150
- 50 KEITHLEY REGULATED HIGH VOLTAGE SUPPLY type 241 £225
- 51 BRANDENBURG PHOTOMULTIPLIER POWER SUPPLY 0-2500 Volts £125
- 52 GENERAL RADIO type 1360B Microwave Oscillator 1.7-4.1 GHz £250
- 53 GENERAL RADIO type 1142A Frequency/Discriminator Meter 0-1.5MHZ £200
- 54 GENERAL OSCILLATORS types 1209C, 1209L, 1215C with Power Unit type 1289A, 50-900 MHz £245
- 55 BRADLEY MULTIMETER TYPE CT4719 £75
- 56 BEMEX CROSSMATCH/DOT GENERATOR UHF/VHF £30
- 57 ADVANCE AC TRANSISTORISED VOLTMETER TYPE VM78 £18
- 58 RACAL FREQUENCY COUNTER type 836 32MHZ £50
- 59 FARNLEY SINE/SQUARE OSCILLATOR £45
- 60 CROPTIC THERMO COUPLE POTENTIOMETER type P-4-E £35
- 61 E.M.T. WOW & FLUTTER METER £75
- 62 MARCONI OUTPUT POWER METER type TF893 £25
- 63 RHODE & SCHWARZ NOISE GENERATOR SKTU BN4151/2/60 3-1000MHZ £125
- 64 RHODE & SCHWARZ STANDARD SIG GENERATOR AM/FM, SDAF BN41023/2 £125
- 65 TAYLOR SIGNAL GENERATOR type 82A, 4-120MHZ AM/FM £85
- 66 TAYLOR RF SIGNAL GENERATOR type 68A/M MK2 £85
- 67 ADVANCE Q METER type T1 100KHZ-100MHZ £40
- 68 ADVANCE PULSE GENERATOR type PG5002D £40
- 69 ADVANCE WAVE VOLTMETER type VM79, No probe £25
- 70 AIRMEC MILLIVOLT METER type 301 £25
- 71 TAYLOR VALVE TESTER type 45D £80
- 72 HEWLETT PACKARD UHF SIGNAL GENERATOR type 612A 450-1200MHZ £175
- 73 MOSELEY X-Y RECORDER type 2D-2, As is £120
- 74 B & K LEVEL RECORDER type 2305, 50dB Potentiometer, Brand new with accessories £950
- 75 B & K LEVEL RECORDER type 2305 £275
- 76 MARCONI AM SIGNAL GENERATOR type TF801D/8S 10-485 MHZ £150
- 77 MARCONI UHF SIGNAL GENERATOR type TF1060 £150
- 78 RACAL UNIVERSAL COUNTER TIMER CT488 (SA540 with SA545), As is £45
- 79 SOLARTRON PULSE GENERATOR type GO.1101.2 £40
- 80 RACAL DIGITAL FREQUENCY METER SA520, As is £10
- 81 RACAL DIGITAL FREQUENCY METER type 806R 32MHZ £35
- 82 AVO TRANSISTOR ANALYSER type TA £40
- 83 MUIRHEAD DECADE OSCILLATOR type D-890-A £65
- 84 DAVE STROBOLIGHT type 1201E £25
- 85 HUNTS CAPACITOR ANALYSER & RESISTANCE BRIDGE type CRB3 £45
- 86 AVO TRANSISTOR TEST SET type CT1537 £45
- 87 ADVANCE STABILISED POWER UNIT type PP1 0.600V; 300MA £40

A MUST FOR THE COMPUTER OR VIDEO MAN

CONRAC 14" MONITOR. Solid-state - sync - plus video input sockets. Not cased. Used but tested. **£35 each. Carriage £5**
Other monitors available including colour. Please enquire.
PLEASE CHECK AVAILABILITY BEFORE ORDERING

CREED MODEL 75

Printer with keyboard. Late model. Still the cheapest way to get a printout from your microprocessor. Basic data ad connections supplied. Used, good condition. **ONLY £25 each.**
RECEIVE ONLY. £18 each

MINIATURE VARIAC 0.6 AMP

In an attractive Blue Case with Carrying Handle. Size 10 1/4 x 6 1/4 x 6 1/2". With 20 good quality screw terminals with integral 4mm socket giving multiple voltage and current outputs.
New condition. Individually Boxed. **£15 each. P&P £2**

RADAR AERIALS

Rotary, complete with Waveguide Couplers. These are brand new, Ministry boxed. Very impressive. Dish diameter 27 inches. **£85 each. Carriage £5**

EX-MINISTRY MASTS 40ft. HEAVY DUTY

With guys, etc. In transit case **£50 each. Carriage £5**

SINE & SQUARE WAVE AUDIO GENERATOR type TE22, 20HZ- 200KHZ. Portable. As new.

ONLY £55 each P&P £3

INFRA RED IMAGE CONVERTER Type 9606 (CV 144)

13 1/4in. diameter. Requires single low current 3KV to 6KV, supply individually boxed. With data. **£12.50 each**
Infra Red Lamps also advertised

TRANSISTOR INVERTOR

115V AC 1.7 Amp Input. Switching is at 20KHz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied. **£1.25 each. P&P £2.**

COSSOR VDU with KEYBOARD

80 characters x 13 lines; 600/1200 baud; RS232; standard 240 volts input; screen size 9 inches.
Very good condition. Tested. Limited quantity.
£70 each. Carriage at cost.

CONVERT THIS UNIT TO A SUPER BATTERY CHARGER

Attractive green ministry quality case with removable top and bottom plates - heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for **£3.50. P&P £3.** Four units **£12. Carriage £6.**

STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a tach. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.
£1.50 each P&P 75p
or 5 for **£5 P&P £1.50.**

STEPPING MOTORS

200 Steps. 20 oz/in. torque, 12/24 volt input 5-wire **£12 each. P&P £1.50**

KEYBOARD PAD

Size 3x2 1/2" with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank. **£4 each. P&P £1, or 5 for £15 P&P £2.**

MINIATURE KEYBOARD

Push contacts, marked 0-9 and A-F and 3 optional function keys. **£1.75 each.**

DIODES

All new full spec. devices IN3063; BAX 13; 1S44; 1N3470; 1N4151. 100 off **£1.50, 1,000 off £10**

CRYSTALS 50p each
Flat metal case - 19.2KHZ; 844.8KHZ; B7G - 10MHZ

PULSE TRANSFORMER Sub min. Size 1/2 x 5/16 x 1/4". Secondary centre tapped. **New 20p ea.**

REMO TY TYPE MULTIPLIER. Two high voltage outputs and focus. **£1 each.**

DON'T TAKE CHANCES. Use the proper EHT CABLE. 10p per meter or **£7.50 per 100 metre drum.** P&P £2.

PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap. 75p ea. Box of 12 **£5.90. P&P £1.50.**

INFRA RED QUARTZ LAMPS. 230V 620 watts. Size 13 1/2" x 1/8" dia. **£1.50 ea. 240V 1650 watts. Size 23 3/4" x 1/2" dia. £3 ea.**

BRIDGE RECTIFIER. 2 Amp 50p ea.

PHOTODIODE DETECTOR 4" fly leads. **25p ea.**

AMPHENOL. 17-way chassis mount edge connectors 0.1 spacing. **15p ea.**

I.E.C. Standard MAINS LEAD. Moulded 13 vertical flat pins centre offset. **60p ea.**

FANS. 115V 13 watts. Size 3 1/4 x 3 1/4 x 1 1/2". BRAND NEW. **£4.50 ea. Secondhand £2.50 ea.**

DELAY LINE. 50 nanosecs. 3 connections - ground-in out. Size 2 x 7/16 x 1/8". **New 25p ea.**

SOME TEKTRONIX 500 RANGE OSCILLOSCOPES

with Single Trace Plug-ins. Working.
From **£100.** Phone for details

GENERAL PURPOSE OSCILLOSCOPE TECH TYPE TO-2

Single beam. Size approx 6x7x9 3/4in.
Weight 7lbs.
Ideal for the beginner or school user.
ONLY £49.50 each P&P £3

MULTIMETER Russian type 4324.

AC/DC volts; AC/DC current; ohms, etc.
Brand new, boxed.
£12.50 each. P&P £2.50.

METROHM INSULATION AND CONTINUITY TESTER 500 volts

Portable, Battery Operated, Standard P.P.7 (Battery not supplied). Complete with carrying case.
As new **£40 each**
Used but good condition **£25 each. P&P £3.**

MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New **£1 ea.**

LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. **15p ea.**

DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New **10p ea. 100 for £7.50.**

RAPID DISCHARGE capacitors 8mfd 4KV **£5 each. P&P £2.**

DECOUPLING CAPACITORS 0.05mfd 10V; 0.01mfd; 0.047mfd 250V; 33K, 330pf. All values. **10c for £1.50.**

E.H.T. Capacitor 500pf 8KV 20p each.

10-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10 metres for **£3.**

GEC UHF 6-button tuner **£1.50 each.**

CENTAUR 115V FANS. 4 1/2 x 2 1/2 x 1 1/2". **£4.50 ea. Ex-equipment, tested 60p each.**

CONTACTORS. Heavy Duty 24V DC 5 make **£1 each.**

GEC UHF/VHF 6-button tuner **£2 each.**

931A PHOTO MULTIPLIER **£2 each. P&P £1.**

RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degrees C **£2.50 each.**

SOLID STATE UHF TUNERS. 39MHZ. **£1 each.**

BRAND REX blue wire wraps. 30 metres for **£1. P&P 25p.**

TRANSFORMERS

AUTO 240V input 115V. 1 Amp output **£1.25 each. P&P £1.25.**

240V input. Soc. 6V, 1.86A. Size 2 1/2 x 2 1/2". Good quality **£1.50 ea. P&P £1.**

240V input. Soc. 12V 0.92A. Size 2 1/2 x 2 1/2". Good quality. **£1.50 ea. P&P £1.**

240V input 12V 100MA. Size 60 x 40 x 42mm. 50p each.

240V input. Sec. 12-0-12V 50MA. Size 1 1/2 x 1 1/2 x 1 1/4". 2 for 50p.

115V input. Sec. 5V 250MA. Size 1 1/2 x 1 1/2 x 1 1/4". 2 for 50p.

115V input. Sec. 10-0-10V 1A. Size 2 1/2 x 2 1/2 x 2 1/2". 2 for 50p.

SEMICONDUCTORS 1N4005 - 5p; 1N4002 - 3p.

At 5p each:
8C147, 8C157, 8C158, 8C237, BF197, 0A90, 0A81, BC1488, BA154, BA243.

At 25p each:
TIP31, TIP41A, 2N5636, AF139, 2TX341, BY127, 10p, BF181, 20p, BD239, 49p, BD241, 40p; MA343AT, 49p; BD228 50p; BD233 & BD234 Comp Pair 25V - 80p per pr. at 50p each.

REGULATOR TBA626 8 to 20V in - 5V out 100MA T05 Con. 50p each BF256C 20p.

TV AMPLIFIER TBA 120 20p each.

MOTOROLA DUAL in Line 6-pin Opto Coupler **30p each.** Gold plate tester version **50p each.**

ELECTROSTATIC VOLTMETER. 7.5KV **£8 ea. P&P £1.50.** Other ranges available - please enquire.

TRIMMERS. Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. All at 6p each.

HONEYWELL humidity controllers **50p each.**

THRYSITOR TIMER. Solid State. 15 secs adjustable (reset) in plastic relay case. Standard 7-pin base. Series delay **50p each.**

MINIATURE PC MOUNT SLIDE SWITCH. 2 pole 2 way 10p each.

4 DIGIT 7 SEGMENT per digit plus a figure one to the left plus a centre minus sign to the left of the figure one with decimal places between digits. Good brilliance at 1.5V. 15 connections **£2.50 each.**

Some **E.H.T. TRANSFORMERS** and **CAPACITORS** available. Please enquire.

TELEPHONES 706 style black; grey or blue **£5.50 ea.**; 746 style black or grey **£7.50.** Older style black **£2.50 each.** Discarded only **706 £4 ea. P&P £1.50 per 10 ea.**

DC SERVO MOTOR 110V 2.5 Amp continuous. Double shaft. Brand new. 4 wire 4 brush **£18 ea.** Plus carriage.

PC Mount POTS. Wire wound with knob 200 ohm & 10 ohm. **10p ea.**

MINI. RELAY 24V. 2 pole c/o. Brand new. **75p each.**

TIME DELAY RELAY 0.1 to 10 secs. 115V AC. DPDT. **£5 each.**

CAPACITORS at 5p each. 0.1uf 400V. Small rect. block PC Mount German class; 3300pf; 220nf 250V; 0.01mfd 160V. INSERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality). Ex-Min. Brand new without 75p each, or 10 for **£6.**

TOROIDAL TRANSFORMERS. Input 0-120-240 Volts. Output 0-12V; 0-12V; 10VA per winding. Encapsulated - identical to R.S. Components at **£8.90. OUR SPECIAL PRICE £5 ea. P&P £1.50.**

TANTALUM CAPACITORS - All at 10p each - 100 off **£7.50.** 22mfd 8V; 33mfd 10V; 22mfd 35V; 1mfd 35V.

MINIATURE SLIDE SWITCHES. Single pole 2 way 10p each.

HEAVY DUTY RHEOSTAT. 7.5ohm. 5.5Amp. Diameter 5". Standard 1/4" shaft **£2.50 each. P&P £1.50.**

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm or 500 ohm. Tested **£25 each** or 5 for **£100.**

MINIMUM ORDER **£3 VALUE OF GOODS.** MINIMUM P&P **£1.50** - where P&P not stated please use own discretion - excess refunded.
£5 CARRIAGE ON ALL UNITS. P&P OR CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS.
CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.
BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMHEAD LTD

NORWOOD ROAD, READING
TELEPHONE NO. READING 669656
(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

MICROPOWER THERMAL ALARM

This over- or under-temperature alarm consumes a mere 3.5 μ A of quiescent current, yet the alarm delivers 1 W of peak audio power. Design by Ray Marston. Development by Steve Ramsahadeo.

Precision temperature alarms have a variety of practical uses in the home: they can be used to indicate ice conditions in the loft, over-temperature conditions in the greenhouse or fire conditions in any part of the building. Trouble is, all conventional systems draw quiescent currents of several milliamps and will flatten a PP9 battery after less than two days of continuous operation. Yuck!

ETI's new Micropower Thermal Alarm system can be used as either an over- or under-temperature alarm; it is specifically designed to overcome the battery flattening problem using the principles described in this month's Designer's Notebook.

Construction

The entire circuit, other than the thermistor, speaker and battery, is mounted on a small PCB and construction should present few problems. Note, however, that the circuit uses some high-value resistors, so take care to keep the board clean during and after assembly; when construction and testing is complete, you can coat the entire circuit with varnish, to exclude the shunting effects

of moisture and dirt.

The circuit is designed to work with a negative-temperature-coefficient (NTC) thermistor that has a resistance in the range 1k Ω to 10k Ω at the desired alarm temperature; the VA1066S is suitable for use at all 'normal' temperatures. TH1 and PR1 can be

configured to give either over or under-temperature alarm operation; with the connections shown in the circuit diagram, the unit acts as an under-temperature (ice warning, etc) alarm; for over-temperature operation, simply transpose the TH1 and PR1 positions using the links provided on the PCB. In

HOW IT WORKS


The circuit comprises three main sections, these being a thermal switch (TH1-PR1-R1-R2 and IC1), a sample pulse generator (IC2 and Q1), and an alarm generator (IC3 and Q2). The thermal switch circuit is quite conventional: TH1-PR1-R1-R2 are wired as a simple bridge across the inputs of voltage comparator IC1. The action is such that the output of IC1 is normally low (at 0 V) but switches high when the TH1 temperature falls below a value preset by PR1 (the circuit can be made to give over-temperature switching by transposing the TH1 and PR1 positions). If this conventional circuit were powered from a continuous DC source, it would draw several milliamps of quiescent current.

The sample pulse generator is designed around IC2, which is configured as a special micropower oscillator (see this month's edition of Designer's Notebook) and produces a 300 μ s pulse at pin 12 roughly once every second. This pulse is used to connect power to the IC1 thermal switch circuitry via emitter follower Q1, thus reducing its mean current consump-

tion by a factor of 3000 relative to the 'normal' DC value. Thus, if the TH1 temperature is above the preset alarm level on the arrival of the sample pulse, the IC1 output (pin 6) will be low and no charge will be fed to C1 via D1, but if the temperature is below the preset level the output of IC1 will switch high for the duration of the sample pulse, rapidly charging C1: the C1 charge is used to activate the IC3 alarm generator circuitry.

IC3a-IC3b are connected as a gated 6 Hz astable, with the output fed to the input of 1 kHz gated astable IC3c-IC3d; IC3d has its output fed to an external speaker via VDET power amplifier Q2. Thus, when the C1 voltage is zero, the two IC3 astables and Q2 are cut off and the alarm generator circuitry consumes zero quiescent current, but when the C1 voltage is high the 6 Hz astable is gated on and pulses the 1 kHz astable on and off, generating a powerful pulsed-tone alarm signal in the speaker. The supply to the major sections of the circuit is decoupled from LS1/Q2 transients by D3 and C3.

Fig. 1 Circuit diagram of the Micropower Thermal Alarm. The points A-D can be linked so as to provide either over- or under-temperature sensing.

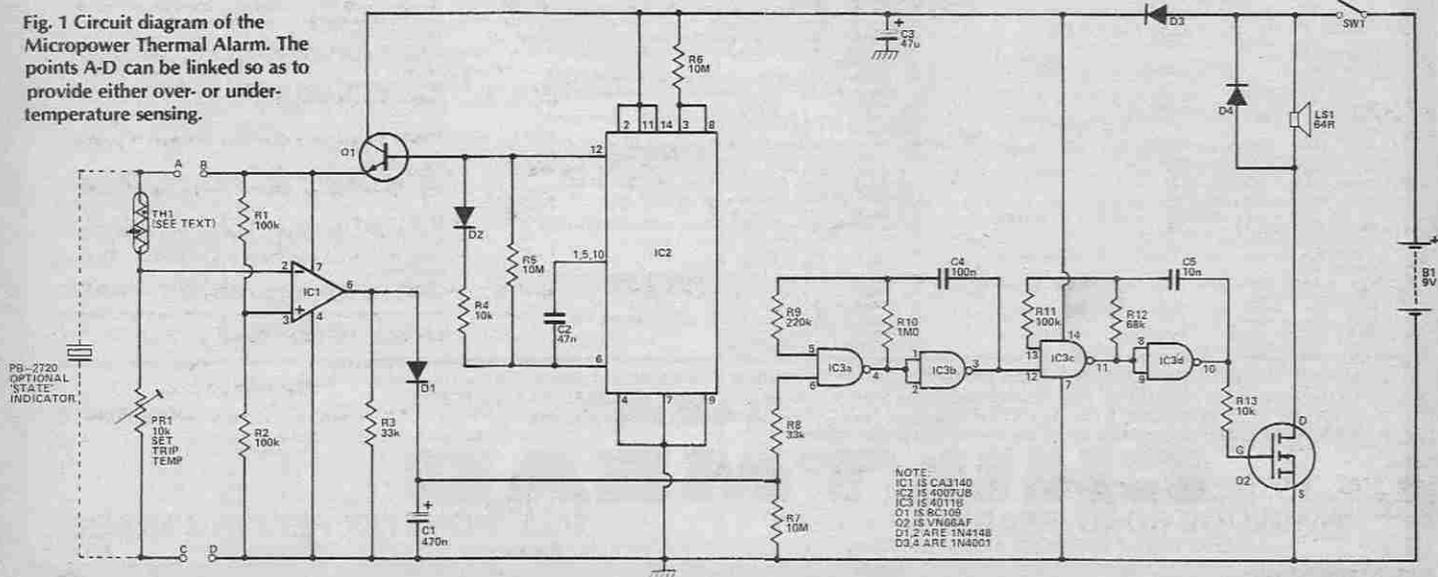

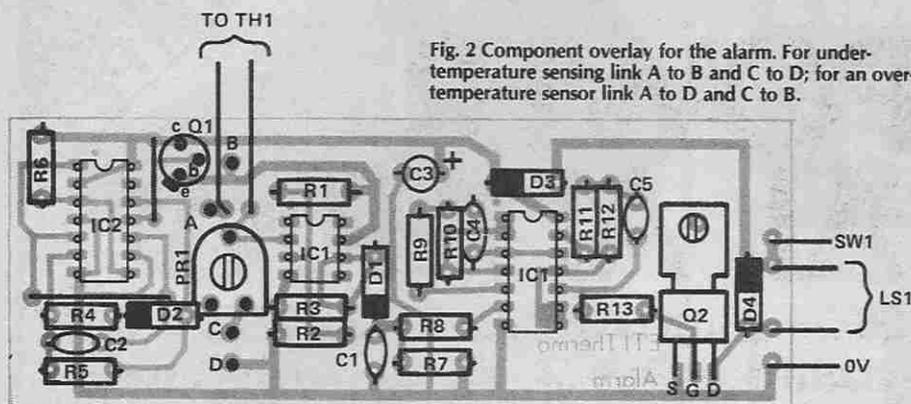


Fig. 2 Component overlay for the alarm. For under-temperature sensing link A to B and C to D; for an over-temperature sensor link A to D and C to B.

PARTS LIST

Resistors (all 1/4 W, 5%)

R1,2,11	100k
R3,8	33k
R4,13	10k
R5,6,7	10M
R10	1M0
R12	68k

Potentiometers

PR1	10k miniature horizontal preset
-----	---------------------------------

Capacitors

C1	470n 16 V tantalum
C2	47n ceramic
C3	47u 16 V tantalum
C4	100n ceramic
C5	10n ceramic

Semiconductors

IC1	CA3140
IC2	4007UB
IC3	4011B
Q1	BC109
Q2	VN66AF
D1,2	1N4148
D3,4	1N4001

Miscellaneous

TH1	VA1066S
SW1	SPST miniature toggle
LS1	64R loudspeaker
TX1	PB-2720 (optional)
PCB	(see Buylines)

BUYLINES

TH1 and Q2 are available from Electroval. Technomatic stock the 64R loudspeaker. All the other components are readily available from our regular advertisers. See page 54 for details of our PCB service.

practical use, the thermistor is mounted remote from the PCB.

When construction of the unit is complete, fit the speaker and battery in place and give the unit a functional check by adjusting PR1 so that the alarm activates; then back-off PR1 so that the alarm turns off again (after a few seconds delay). Finally, raise (or lower) the TH1 temperature to the desired alarm value and then trim PR1 so that the alarm activates.

If desired, a PB-2720 acoustic transducer can be wired between

points A and C of the circuit to act as a state indicator. This transducer will generate an audible click once every second when the circuit is working correctly, and adds only a fraction of a microamp to the total current consumption of the unit.

ETI

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
30VA 70 x 30mm 0.45 Kg Regulation 18%	1X010	6-6	2.50	£4.48 - 0.87p P/P - 0.80p VAT
	1X011	9-9	1.66	
	1X012	12-12	1.25	
	1X013	15-15	1.00	
	1X014	18-18	0.83	
	1X015	22-22	0.68	
	1X016	25-25	0.60	
1X017	30-30	0.50		
50VA 80 x 35mm 0.9 Kg Regulation 13%	2X010	6-6	4.16	£4.93 - £1.10 P/P - 0.90p VAT
	2X011	9-9	2.77	
	2X012	12-12	2.08	
	2X013	15-15	1.66	
	2X014	18-18	1.38	
	2X015	22-22	1.13	
	2X016	25-25	1.00	
2X017	30-30	0.83		
2X028	110	0.45		
2X028	220	0.22		
2X030	240	0.20		
80VA 90 x 30mm 1 Kg Regulation 12%	3X010	6-6	5.64	£5.47 - £1.43 P/P - £1.04 VAT
	3X011	9-9	4.44	
	3X012	12-12	3.33	
	3X013	15-15	2.66	
	3X014	18-18	2.22	
	3X015	22-22	1.81	
	3X016	25-25	1.60	
3X017	30-30	1.33		
3X028	110	0.72		
3X028	220	0.36		
3X030	240	0.33		
120VA 90 x 40mm 1.2 Kg Regulation 11%	4X010	6-6	10.00	£6.38 - £1.43 P/P - £1.17 VAT
	4X011	9-9	6.66	
	4X012	12-12	5.00	
	4X013	15-15	4.00	
	4X014	18-18	3.33	
	4X015	22-22	2.72	
	4X016	25-25	2.40	
4X017	30-30	2.00		
4X018	35-35	1.71		
4X028	110	1.09		
4X028	220	0.54		
4X030	240	0.50		
160VA 110 x 40mm 1.8 Kg Regulation 8%	5X011	9-9	8.89	£8.44 - £1.43 P/P - £1.48 VAT
	5X012	12-12	6.66	
	5X013	15-15	5.33	
	5X014	18-18	4.44	
	5X015	22-22	3.63	
	5X016	25-25	3.20	
	5X017	30-30	2.66	
5X018	35-35	2.28		
5X026	40-40	2.00		
5X028	110	1.45		
5X028	220	0.72		
5X030	240	0.66		

Also available at Electroval, Maplins, Marshalls, Technomatic and Watford Electronics.

I.L.P. TRANSFORMERS

INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
225VA 110 x 45mm 2.2 Kg Regulation 7%	6X012	12-12	9.38	£10.06 - £1.73 P/P - £1.77 VAT
	6X013	15-15	7.50	
	6X014	18-18	6.25	
	6X015	22-22	5.11	
	6X016	25-25	4.50	
	6X017	30-30	3.75	
	6X018	35-35	3.21	
	6X026	40-40	2.81	
	6X025	45-45	2.50	
	6X028	110	2.04	
6X029	220	1.02		
6X030	240	0.93		
300VA 110 x 50mm 2.6 Kg Regulation 6%	7X014	18-18	8.33	£11.66 - £2.01 VAT
	7X015	22-22	6.82	
	7X016	25-25	6.00	
	7X017	30-30	5.00	
	7X018	35-35	4.28	
	7X026	40-40	3.75	
	7X025	45-45	3.33	
7X028	50-50	3.00		
7X028	110	2.72		
7X029	220	1.36		
7X030	240	1.25		
500VA 140 x 60mm 4 Kg Regulation 4%	8X017	30-30	9.33	£15.53 - £2.05 P/P - £2.64 VAT
	8X018	35-35	7.14	
	8X026	40-40	6.25	
	8X025	45-45	5.55	
	8X033	50-50	5.00	
	8X042	55-55	4.54	
	8X028	110	4.54	
8X028	220	2.27		
8X030	240	2.08		
625VA 140 x 75mm 5.0 Kg Regulation 4%	9X017	30-30	10.41	£21.54 - £2.20 P/P - £3.56 VAT
	9X018	35-35	8.32	
	9X026	40-40	7.81	
	9X025	45-45	6.94	
	9X033	50-50	6.25	
	9X042	55-55	5.68	
	9X028	110	5.68	
9X029	220	2.84		
9X030	240	2.60		

IMPORTANT: Regulator references - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage

See our adverts, also on pages 90 & 91

I.L.P. TRANSFORMERS (a division of I.L.P. ELECTRONICS LTD.)
FREEPOST T4, GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY, CT2 7EP
Phone (0227) 54778 - Technical (0227) 64723 - Telex 965 780

NOW 95 TOROIDAL TYPES FROM 30VA TO 625VA

★★ I.L.P. TOROIDALS ★★

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Induced hum is reduced by a factor of ten. I.L.P. toroidals cost virtually the same as the older types which they are rapidly replacing. Now increased production capacity means even lower prices. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. GUARANTEED 5 YEARS.

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel). For 110V Primary insert 0 in place of "X" in type number. For 220V Primary (Europe) insert 1 in place of "X" in type number. For 240V Primary (U.K.) insert 2 in place of "X" in type number. Example: 50VA 240V 6+6V 4.16A=22010.

- ★ CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.
- ★ FREEPOST FACILITY (U.K. only). Simply send your order in envelope marked FREEPOST to address below. NO STAMP REQUIRED.
- ★ TO ORDER Enclose Cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd. or quote your ACCESS OR BARCLAYCARD account number. VAT must be included with U.K. order. To pay C.O.D. add £1 extra to TOTAL value of order.

GOODS DESPATCHED WITHIN 7 DAYS OF RECEIPT OF ORDER

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply Transformer(s)..... No.(s).....

..... Total purchase price £.....

I enclose Cheque Postal Orders International Money Order

Debit my Access/Barclaycard Account No.....

NAME.....

ADDRESS.....

Signature.....

ETI10

Has seven years of success gone to our heads?



NEW IMPROVED

MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

POPULAR HI-FI

"Switching to the Minimax' from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." **Comparative test OCTOBER 1975.**

HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" **JANUARY 1975.**

PRACTICAL HI-FI & Audio

"The depth, clarity and openness of sound produced is quite astonishing". **JUNE '75**

WHAT HI-FI

"... the ability of the Mini-

max to take a lot of power and still sound good could be decisive" — **Comparative test, APRIL 1977.**

PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". **JANUARY 1981.**

Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms.
Frequency Response: 80Hz — 20KHz±5dB.
Finish: natural teak, veneer with black frets.
Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.
Weight: 4.1 Kgs (9 lbs) each.

ONLY £69.95 A PAIR

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

VIDEOTONE


98 CROFTON PARK ROAD
LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. ET10

NAME _____

ADDRESS _____

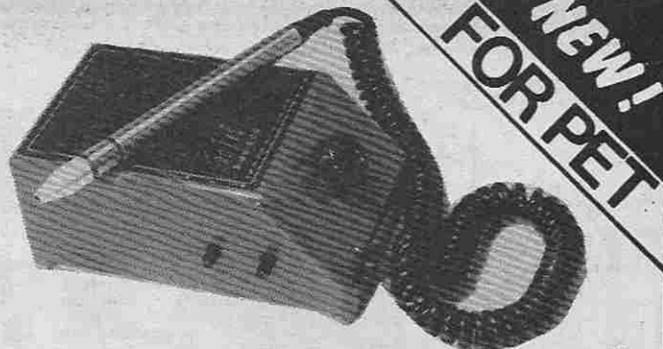

**NEW!
FOR PET**

Not just a light pen but a complete data entry and processing system for your PET. It can offer a much faster, more convenient and often better alternative to the keyboard in almost any program. In fact any task involving human participation in the office, lab or classroom can be carried out faster and with fewer errors. (Especially if you can't touch type!). Typical applications include: data input and selection, word processor enhancement, graphics handling, fast program writing and editing, computer assisted design, games etc. etc. This system is very easy to use. All complicated machine code is out of sight in a plug in ROM — just point the pen and touch the tip! The hardware includes a stainless steel light pen with precision optics, programmable touch switch and retractable cable. The 'pen-rest' houses the control electronics (including CB2 sound) which simply plugs into the USER PORT. The firmware supports both pic and track modes, auto cursor movement (better than repeat keys for editing!), single key instant screen reverse, high resolution (1 x 2 pixels) if needed, Coordinates and screen address returned as BASIC variables. All this and more is fully explained and documented in the comprehensive manual. There is not enough room in this ad to list all its features but literature is available on request. To order just send a cheque or phone (anytime) quoting your credit card number.

ALTEK (ETI) 1 Green Lane
Walton-on-Thames Surrey

Order by post or phone (093 22) 44110 ... 24 hours
Access or Visa accepted. ... Callers by appointment
Selected dealers needed in U.K. and overseas. ETI

£170 + VAT

Happy Memories

Part type	1 off 50-99	100 up
4116 200ns.....	1.00	.90 .80
4116 250ns.....	.90	.80 .70
2114 200ns Low power.....	1.30	1.20 1.10
2114 450ns Low power.....	1.25	1.15 1.05
4118 250ns.....	3.95	3.25 2.95
6116 150ns CMOS.....	8.75	8.25 7.95
2708 450ns.....	2.40	2.25 2.15
2716 450ns 5 volt.....	2.65	2.40 2.20
2716 450ns three rail.....	7.40	7.00 6.75
2732 450ns Intel type.....	5.40	4.95 4.65
2532 450ns Texas type.....	5.40	4.95 4.65
Z80A-CPU	£5.25	Z80A-PI0 £4.75
		Z80A-CTC £4.75

Low profile IC sockets:
Pins 8 14 16 18 20 22 24 28 40
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5 inch SSDD £17.00 5 inch DSDD £23.60
8 inch SSSD £22.95 8 inch SSDD £28.85
8 inch DSDD £34.75

74LS series TTL. Large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 30p post & packing to orders under £15 and VAT to total

Access & Barclaycard welcome.
24-hr. service on (054 422) 618

Government and Educational orders welcome, £15 minimum

Trade accounts operated, 'phone or write for details
Prices are still tending to drop, 'phone for a quote before you buy

Happy Memories (ETI), Gladestry, Kington
Herefordshire HR5 3NY. Tel: (054 422) 618 or 628

CLEF ELECTRONIC MUSIC

MASTER RHYTHM

As published in Practical Electronics



KIT. — £79. BUILT — £119

FULLY PROGRAMMABLE
TWENTY-FOUR PATTERNS

EIGHT PARALLEL TRACKS

TWELVE INSTRUMENTS

SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

PIANOS

SPECIALISTS SINCE 1972
STAGE & DOMESTIC TYPES



The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufacture.



SIX OCTAVES £217
7 1/2 OCTAVES £244

STRINGS £179

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch plus two-phase Chorus.

ROTOR-CHORUS

£89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" p.c.b. Mains P.S.U. included.

KEYBOARDS

Square Front with two hole actuator—easily cut.

49 NOTE £28.75; 61 NOTE £38
73 NOTE £47; 88 NOTE £57

OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates — in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM


CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E.T.I.)
44A BRAMHALL LANE SOUTH, BRAMHALL,
STOCKPORT, CHESHIRE SK7 1AH. 061-439 3297

sabtronics

An entire range of low-cost high-performance instruments



* 861QA 600 MHz
FREQUENCY METER

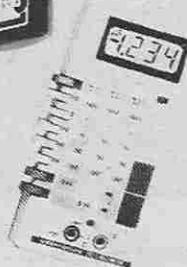

* 2037A L.C.D. HAND HELD
DMM WITH TEMPERATURE

- 2010A 3 1/2 DIGIT L.C.D. DMM
- 2015A 3 1/2 DIGIT L.C.D. DMN
- 2035A 3 1/2 DIGIT L.C.D. HANDHELD DMM
- 8110A 100 MHz 8 DIGIT FREQUENCY METER
- 8610B 600 MHz 9 DIGIT FREQUENCY METER
- 8000B 1 GHz 9 DIGIT FREQUENCY METER
- 5000A 200 KHz FUNCTION GENERATOR
- LP-1 10 MHz LOGIC PROBE

* ALSO AVAILABLE IN KIT FORM

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices — no-one can beat our price/performance ratio.

sabtronics

"Making Performance Affordable"


Full colour illustrated brochure and price list from:
BLACK STAR LTD, 9a Crown Street, St. Ives, Cambs. PE17 4EB
Tel: (0480) 62440. Telex: 32339



ATOM OWNERS LOOK OUT

There are DODGEMS about!

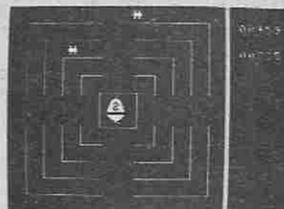Dodgems is just one of the brand new games packs from Acorn, the manufacturers of your Atom. You have to steer your car around the lanes collecting points. But beware! There's a computer controlled car programmed on a collision course. If you survive the game gets faster. Also in Games Pack 6 are Simon and Amoeba.



GET THE BEST—FORGET THE REST

All Acornsoft games are designed and produced by the manufacturers of the Atom. Trust the manufacturer to get the very best out of his product. Realistic sound effects, great graphics and colour too!

GAMES PACK 1

Asteroids Shoot them before they crash into you. Lists ten best scores. Program 4K, graphics 6K.

Sub Hunt Command a destroyer tracking a submarine, find its position and destroy it. Program 1K, graphics 1/2K, needs floating-point.

Breakout Score points knocking bricks from wall. Ball has two changes of angle and speed. Program 3K, graphics 1-2K. COLOUR

GAMES PACK 2

Dogfight Two-player game; each player controls a plane and tries to shoot down his opponent without crashing. Program 4K, graphics 6K.

Mastermind Guess the computer's code before the computer guesses yours; program 3K, graphics 1/2K.

Zombie Land on Zombie island; try to lure all the zombies into the swamp. In desperation jump into hyper-space! Program 3K, graphics 1/2K. COLOUR

GAMES PACK 3

Rat Trap Move your rats without colliding with the trails left. Entangle your opponent before he entangles you! High-speed rat action-replay. Program 4K, graphics 6K.

Lunar Lander Land a spacecraft on a lunar crater; altitude velocity, fuel and drift. Program 1K, graphics 1/2K.

Black Box Deduce the position of four invisible objects in the Black Box by firing rays at them. Program 4K, graphics 1/2K.



GAMES PACK 4

Star Trek Classic computer game; rid the universe of Klingons. Short and long-range scans, galactic map, phasers, photon torpedoes, shields etc. Program 5K, graphics 2K.

Four Row Take turns in placing marbles on the board; the first to get a line of four wins. Program 5K, graphics 6K. COLOUR

Space Attack Repel the invasions of earth and avoid being hit by the gunner ships. Becomes progressively harder with each invasion. Program 3K, graphics 6K.

GAMES PACK 5

Invaders The most popular video game, with invaders, flying saucers, shelters, and full sound effects. Program 5K, graphics 6K.

Wumpus Wander in caves inhabited by the Wumpus. Find and shoot him before he eats you. Pits and bats make things harder. Program 2K, graphics 1/2K.


Reversi Reversi, or Othello played with counters that are black one side and white on the other; Program 3K, graphics 1/2K. COLOUR

GAMES PACK 7

Green Things An alien life-form has invaded your space-craft; discover a way of destroying it with the weapons available on the ship. Program 5K, graphics 2K. COLOUR

Ballistics Take turns in firing shells at the other player, taking into account the wind and shape of the hill. Program 3K, graphics 6K, needs floating-point.

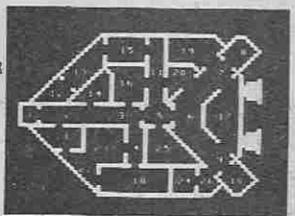Snake Grow yourself a snake by guiding it towards digits which it eats. Program 2K, graphics 1/2K.




ORDER TODAY!

Just send a cheque or money order. Only £11.50 per pack including VAT and post and packing. State which packs you want.

Or ring 0223 316039 or 01-930 1614 quoting your Access or Barclaycard number. Allow 14 days for delivery. Or if you think you can wait for more details just write to

Acornsoft Limited, 4a Market Hill, Cambridge.

ACORNSOFT TAKE GAMES SERIOUSLY

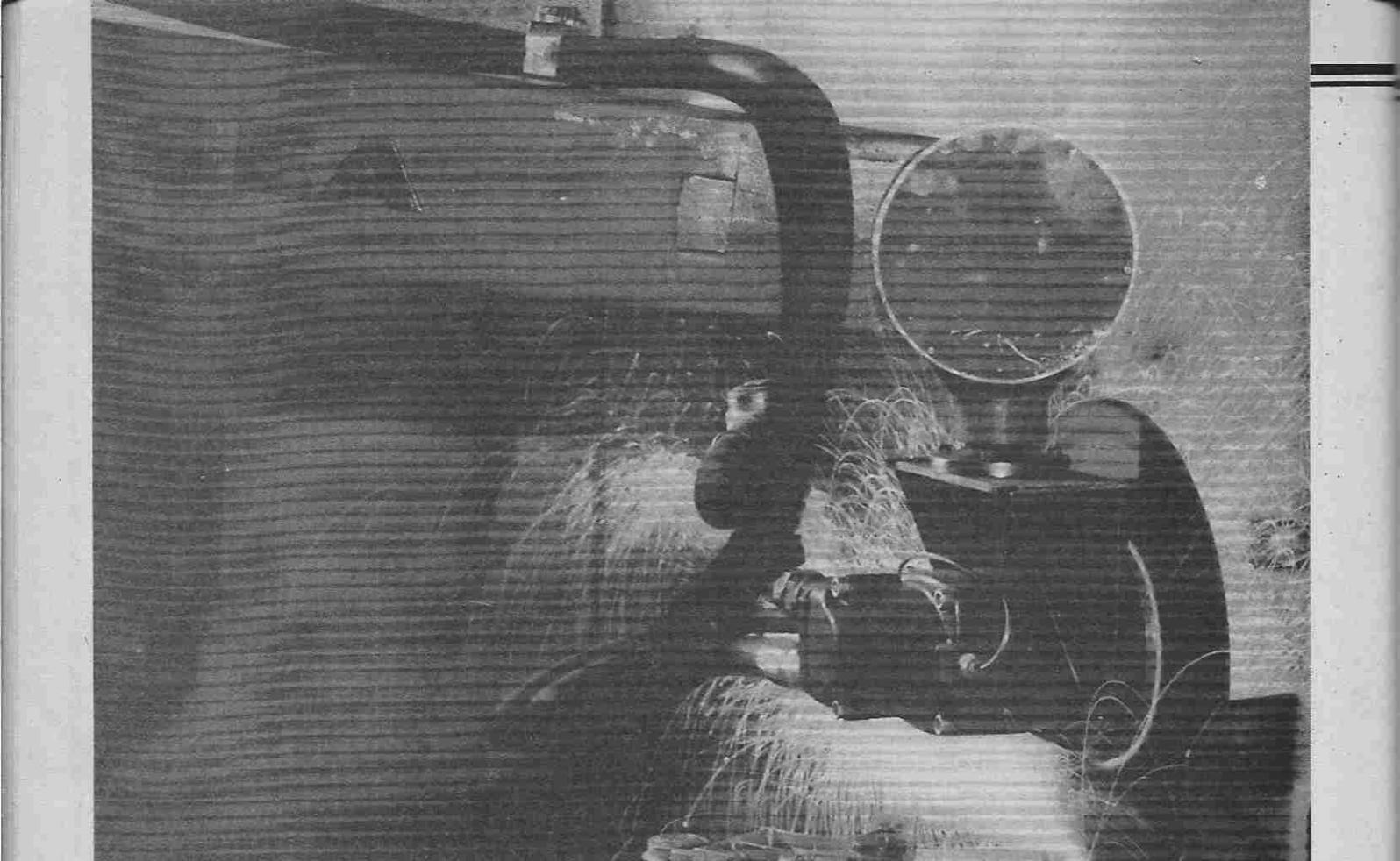

ROBOTICS TODAY

As readers must now be aware, we at ETI are convinced that robotics has a major role to play in the industrial development of this country — hence this new series. To start us off, Martyn Paradise of Robotec looks at procedures involved in the application of robots in industry.

Initial contacts between ourselves and companies wishing to use robots are often by direct mailing approach, followed by telephoning. Occasionally, exhibitions such as the recent Automan '81 exhibition at Brighton, where interest was greatly increased over the previous exhibition in 1979, result in contacts.

Generally, customers fall into two categories, those who want to use robots in their production facilities, but don't have a particular area to try first; and those who have decided upon an application and want help to implement a robot system.

The first type of customer requires a visit by us to 'look around' and assess the situation. From this visit, one or more areas where a robot may be feasible are highlighted. Simple quick feasibility studies of each possible application are then carried out in conjunction with the customer. It may be that the feasibility studies show that some other type of automation is

required, such as dedicated assembly machines, instead of a flexible robot system.

The second type of customer, who has a definite project in mind, needs careful vetting because often the proposed application may be too arduous for the robot selected, or insufficient funds have been allowed for development costs or the project is only economic, producing a suitable repayment, if the single robot can make a sweeping change to the production processes presently used. For instance, one prospective customer wished to justify one robot project by making it do the work of five manual operators spaced over a distance of 40 ft. The poor robot was expected to whizz back and forth along a track from one work station to the next like a demented yo-yo.

As a general rule, assume that one robot can do the work of one complete human operator, and that one small assembly-type robot can do the work of one human arm and hand.

This new series will provide a stage upon which our readers may display their robotics achievements. It is intended to cover the practical application of robots in Britain today, be it at hobbyist level or in industry.

Readers in either category are invited to write to the editor of ETI, detailing their experiments, projects, application or usage of robotics. Any articles published will be paid for at commercial rates. It is also hoped to run an 'Ideas Forum' wherein readers can exchange views and ideas but that depends upon the response of our readers — you!

Write to: THE EDITOR, ETI MAGAZINE, 145 CHARING CROSS ROAD, LONDON WC2H 0EE and mark your envelope "Robotics Today".

Feasibility Studies

In the initial quick studies above, how did we arrive at a decision as to whether a production process warranted a robot? Basically, a five point approach can be adopted for selection:

- 1) Types and range of components, and loads to be handled or worked on.
- 2) The cycle time required (or available) to carry out the work task.
- 3) The accuracy/repeatability of positioning of the robot to allow it to handle the components correctly.
- 4) Work envelope — ie, the work area required by the robot to carry out the task; height, length and breadth. This may be constrained by the physical environment of the work situation.
- 5) Costs and economics. This is an area where an otherwise ideal application falls down; after all, most companies are in business to make a profit, not a loss, and if expensive modern technology does not produce greater efficiency or save costs then there is not much point in using it.

To put some rough figures to each of the five points above, a robot may be viable if the following limits are acceptable.

- 1) Loads and components vary from a few grammes to 100-150 kg. Often the batch size of individual components is more important than the component size, ie how long does a particular specification of component run on a production line in the proposed application? If it is constantly changing, by how much does it change; is there a family of similar components that can be run one after the other? If the component is constantly changing then the time taken to retool the robot for each new

component may be significant and each part may require a separate gripper, making tooling costs very high.

2) Cycle times required should be between 5-8 s minimum and upwards; although shorter times are becoming available, particularly for assembly robots.

3) An accuracy/repeatability of less than 0.004", and generally $\pm 0.016" - 0.050"$.

4) A work envelope, as described above, that can vary from the range of a man's arm and hand, upwards to that of a complete man moving in a 6-8 ft circle.

5) If the project can pay for itself over a 2-3 year period on a first project, then it is usually viable. A typical robot installation may cost £20,000 — £70,000 in total including any other hardware required. Individual project costs and economics can vary from one company to the next, and it is not simply that the robot may save an operator's wages when installed. The robot does not take holidays and always works at a steady pace. The robot may not need any heat or light although when a completely darkened automatic warehouse was tried a few years ago, the few human operators left in the system insisted on lights being put back in, as they were disconcerted by objects being suddenly discharged out of the 'night' from unexpected directions.

Guarding may be simplified, needing to protect the human operators from the complete system instead of from individual machines. Another cost saving might be shown in the robot's greater consistency; it doesn't have a Monday morning or a Friday night, although problems have occurred with some of the robots that we have worked on that begin to make one wonder.

If from the five points above, a robot system seems feasible, more detailed studies and trials can proceed, to look at the actual operations that the robot needs to carry out and the design of the gripper and the tooling necessary. Some type of modelling of the proposed application is a good idea. We use simple physical 1/10th scale models as well as engineering drawings to aid analysis of the project. Models allow the possible variations and movements of the robot to be quickly understood and observed, something that is not always easy for many people when trying to understand movements in three dimensions.

Selection And Design

Once we know what the robot is expected to do, we can select the 'ideal' robot for the job and design and build the gripper and tooling to suit. The choice of robot may be constrained

Arc welding by robot. The device is one from ASEA Ltd.



by particular preferences towards hydraulic or electric operation; country of manufacture; delivery time; previous track record; and promised after-sales service; as well as the direct costs of installation and running.

The gripper and tooling is the area of a robot project where the most problems occur and often where the smallest amount of money is allocated for development. A robot is no good unless it has a gripper and tooling to allow it to do the job it was bought for; or if its interfaces don't allow it to talk to the outside environment.

The aim of the gripper design is to produce the simplest mechanism to carry out the required tasks. After all, the gripper has to be at least as reliable as the robot to which it is fitted and work day in and day out without attention.

The most common types of grippers use some type of pincer action to hold a component, similar to the action of the human thumb and forefinger. Obviously the mechanical 'thumb' and 'forefinger' may be stronger, wider and thicker than the human counterpart and peculiarly shaped to hold the limited range of components to be handled.

Power to move the gripper (open and close it, for instance) is commonly pneumatic, as compressed air is normally available in factories and a wide range of actuators and valves are available off the shelf. Hydraulic power can also be used, particularly with hydraulic robots.

Magnetic grippers for handling ferrous objects, vacuums for handling glass sheets and cardboard boxes, and electric motors for driving geared jaws are some other types of gripper power that can be tried, although the straight mechanical type is often preferred because of its reliability and simplicity.

The design and development of the gripper may take several months depending on its complexity and any problems that occur with components and hardware used.

Other Interfaces And Hardware

Once the gripper, when mounted on the robot, can carry out the sequence of operations as required by the application, the remaining interfaces need developing. These include electrical interfaces, to connect the solenoid valves of the pneumatic gripper to the robot control system (eg simple relays); also inputs from microswitches and proximity sensors to detect the opening and closing of the gripper jaws and operation of other equipment such as lathes, presses, and conveyors, in order to tell the robot that a component is ready for handling.

Opening of the safety gates also needs monitoring, so that any ingress by human operators into the work area of the robot can be detected and the robot stopped.

Programming

Most industrial robots use a cable-mounted teach box to allow the programmer to instruct the robot. The robot is moved from one position to the next in the required sequence of operations, and each position and operation is stored in the robot's memory. For certain spraying and welding robots, it is possible to teach the robot by holding the spray gun attached to the robot head and leading it through the required cycle.

For complex palletising and handling programs requiring very fine movements, programming can take several days at the initial trial and development stage, followed by further time during installation and commissioning.

All preliminary programming and trials should always be carried out away from the final production area, if only because the problems that always occur during development of a robot system will be spotted and picked on by the sceptics who always seem to abound when new ideas are tried. Everyone has met him — he's the type who doesn't offer help until you've had a go, then says "If I were you I would have done this or that". It is always easier to look backward, than to look forward and anticipate problems.

Final Installation


Putting the robot and its associated hardware into the production environment is the final stage, and includes checking all the safety interlocks between the robot and the outside world, final programming and any last minute modifications to the gripper and tooling.

Often a new robot application will be run at half its designed speed to allow it to 'bed-in' and to test the operation of the system over a period of weeks; after this the tooling may be checked for wear and general conditions, and then the speed of the system will be gradually increased up to the designed limit.


Our thanks to ASEA for providing the photographs.

Suggested Reading

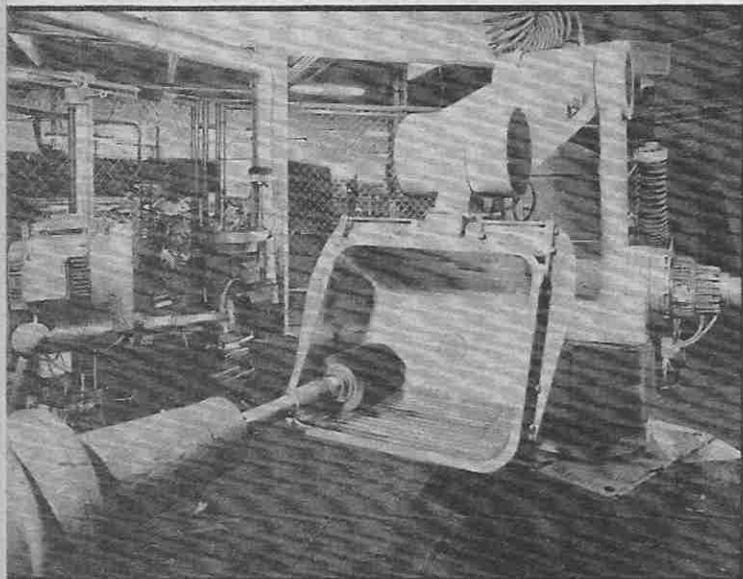Assembly Automation and The Industrial Robot — both quarterly magazines published by IFS (Publications) Ltd, 35-39 High Street, Kempston, Bedford MK42 7BT.



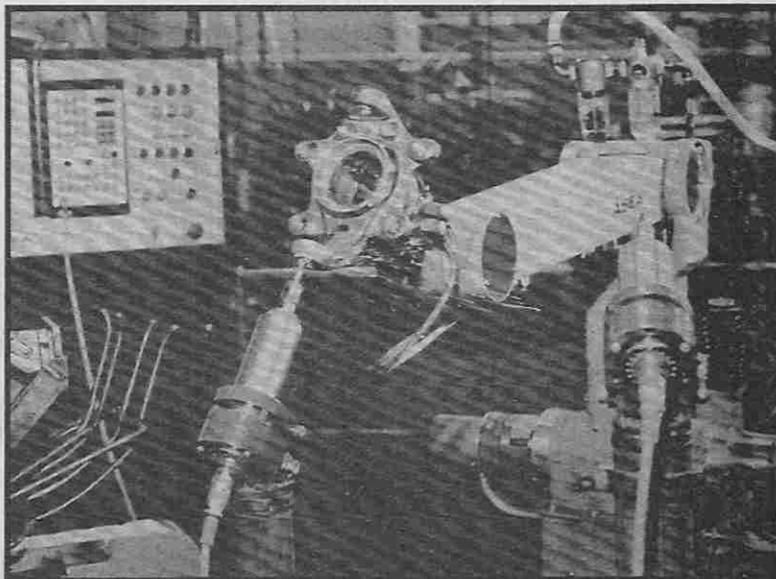Polishing stainless steel kitchen sinks. The ASEA IRb-60 robot picks up the sinks and guides them against the buffing wheels which are attached to fixed spindles.



De-burring a guide-spindle housing after machining. The IRb-6 robot picks up the items and guides them against rotary files.

NEW

PRACTICAL ELECTRONICS - STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF-System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagrams and instructions.



SPECIAL OFFER! TUNER KIT PLUS:


- Matching I.C. 10+10 Stereo Power amplifier kit (usually £3.95 + £1.15 p&p)
- Mullard LP1183 built preamp. suitable for magnetic/ceramic and auxiliary inputs (usually £1.95 + 70p p&p)
- Matching power supply kit with transformer (usually £3.00 + £1.95 p&p)

- Matching set of 4 slider controls complete with knobs for bass, treble and volumes (usually £1.70 + 80p p&p)

£21.95 plus £3.80 p&p.

ONLY

£17.95 plus £2.50 p&p.

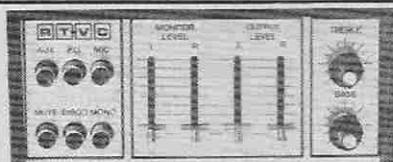

STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/4" x 3 3/4" (approx)
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner, Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with the kit.

£14.95 Plus £2.90 p&p.

SPECIFICATIONS: Suitable for 4 to 8 ohm speakers. Frequency response 40Hz - 20KHz. P.U. 150mV. Aux. 200mV. Mic. 1.5mV. Tone controls Bass ± 12 db @ 60Hz. Treble ± 12 db @ 10KHz. Distortion 0.1% typically @ 8 watts. Mains supply 220 - 250 volts 50Hz.

STEREO MAGNETIC PRE-AMP CONVERSION KIT Includes FREE Magnetic cartridge with diamond styli. All components including p.c.b. to convert your ceramic input on the 10-10 to magnetic. Only available with 10+10 amp. **£2.00** includes p&p.

8" SPEAKER KIT Two 8" twin cone domestic speakers. **£4.75** per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately **£6.75** plus £1.70 p&p.

PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II

2 WAVE BAND MW -- LW

- Easy to build
- 5 push button tuning
- Modern design
- 6 watt output
- Ready etched and punched PCB
- Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics March issue. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 organic filter type pre-aligned and assembled, and a Bird pre aligned push button tuning unit.

£10.50 Plus £2.00 p&p.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.). available as a kit complete. **£1.95**/pack. Plus £1.15 p&p.




HIGH POWER AMPLIFIER MODULES

READY BUILT OR IN KIT FORM

	KIT	BUILT
125 WATT MODEL	£10.50 Plus £1.15 p&p	£14.25 Plus £1.15 p&p.
200 WATT MODEL	£14.95 Plus £1.15 p&p	£18.95 Plus £1.15 p&p


SPECIFICATIONS: Max. output power (RMS) 125 watts 200 watts. Operating voltage (DC) 50 - 80 max. 70 - 95 max. Loads 4 - 16 ohms 4 - 16 ohms. Frequency response measured @ 100 watts 25Hz - 20KHz 25Hz - 20KHz. Sensitivity for 100 watts 400mV @ 47K 40mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms 0.1% 0.1%. Dimensions (both models) 205 x 90 and 190 x 36mm. The P.E. power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of

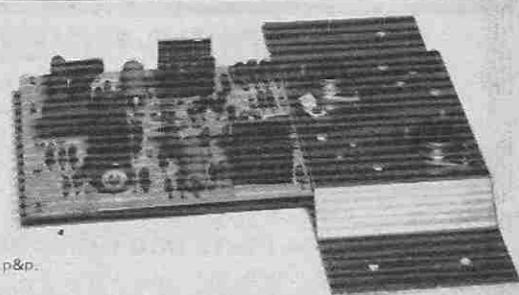

generously rated components, result a high powered rugged unit. The PC Board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES:

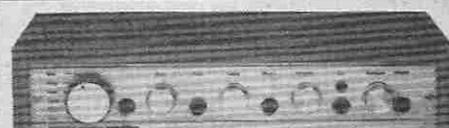- Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p.
- Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p.
- Suitable mains power supply unit for 125W model **£7.50** plus £3.15 p&p.
- Suitable Twin transformer power supply for 200W model **£13.95** plus £4.00 p&p.



30+30 WATT STEREO AMPLIFIER


Viscount IV unit in teak simulate cabinet, silver finished rotary controls and pushbuttons with matching fascia, mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30+30 watts RMS, 60+60 watts peak. For use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx. **£32.90** Plus £3.80 p&p.

PHILIPS BELT DRIVE RECORD PLAYER - DECK GC037

(Size: 15 1/2" x 12 1/2" approx.) HiFi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge.

LIMITED STOCK.

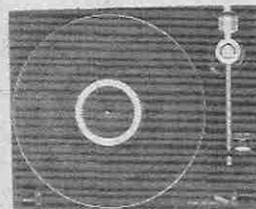
UNBEATABLE OFFER AT **£27.50** COMPLETE Plus £3.16 p&p.



MONO MIXER AMPLIFIERS



50 WATT Six individually mixed inputs for two pick ups (Cer. or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux inputs. Size: 13 1/2" x 6 1/2" x 3 1/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use. **£39.95** Plus £3.70 p&p.

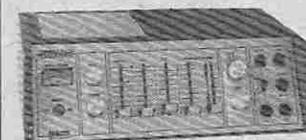**100 WATT**

Brushed Aluminium fascia and rotary controls. Size: approx. 14 1/2" x 4" x 10 1/2". Five vertical slider controls, master volume, tape level, mic level, deck level, PLUS INTERDECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PFL) lets YOU hear the next disc before fading it in. VU meter monitors output. 100w RMS output (200w peak). **£76.00** Plus £4.60 p&p.



CALLERS ONLY
323 Edgware Rd, London W2. Tel: 01-723 8432.
Open 9.30am - 5.30pm. Closed all day Thursday.
Persons under 16 not served without parents authorisation.
ALL PRICES INCLUDE VAT AT 15%.

MAIL ORDER ONLY
21E HIGH STREET, ACTON, W3 6NG.
Note: Goods despatched to UK postal addresses only.
For further information send for instructions 20p plus stamped addressed envelope.

All items subject to availability. Prices correct at 1/10/80 and subject to change without notice. RTVC Limited reserve the right to update their products without notice.

NEW!

OFFICIAL POWERTRAN KIT REPAIR AND ASSEMBLY SERVICE

Circolec (EGS) are delighted to announce their new OFFICIAL Powertran repair and assembly service for electronic kits, we can supply you any kit ready built and tested (see Powertran advert in this issue). Either buy direct from us or through Powertran. Full details on request.

All Powertran kits are now served and repaired efficiently by our experienced engineers. Simply send your faulty unit to us carefully packed together with details of problems and we will do the rest.

ASSEMBLY PRICES EXAMPLES:

1024 Composer £50 + VAT: Vocoder £120 + VAT.

Prices include postage but Securicor delivery available at extra cost.

ALL GAMES STILL AVAILABLE AT THE BEST PRICES!

CIRCOLEC

1 FRANCISCAN ROAD, TOOTING, LONDON SW17
Tel: 01-767 1233

**TV SOUND TUNER
ETI SEP 80 PROJECT**

All parts available / send for list

ALSO

**No. 1 for Teletext Kits
TV Spare Parts and Components**

Callers welcome at Shop Premises

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD
TELEPHONE: 01-794 8751

Near West Hampstead Jubilee & British Rail Stations



Just 50p will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits...

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

- * Lowest prices — Largest stocks *
- * Expert staff — Sound advice *
- * Choose your DIY HiFi Speakers in the comfort * of our listening lounge. (Customer operated demonstration facilities)
- * Ample parking *
- * Access - Visa - American Express accepted *



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



**MAIL ORDER ONLY
DELTA TECH & CO.
62 NAYLOR ROAD, LONDON, N20 0HN
Tel: 01-445 8224**

Prices include VAT. Add 35p P&P

MINIMUM ACCESS ORDER £4

Discounts on items marked *

10 off 5%, 20 off 10%, 40 off 20%

S.A.E. for special offers

C.W.O. for discounts



Table listing various electronic components such as CERAMIC CAP, POLYSTYRENE CAP, POLYESTER CAP, ELECTROLYTIC CAP, SWITCHES, RESISTORS, POTENTIOMETERS, VEROBORDS, ZENER DIODES, TRANSFORMER, OPTO ELECTRONICS, BRIDGE RECTIFIERS, and THYRISTORS with their respective prices.

Table listing electronic components including DIL SOCKETS, TRIACS, DIODES, VOLTAGE REGULATORS, and THYRISTORS with their respective prices.

Table listing electronic components including ICL8038CC, NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

Table listing electronic components including NE555, NE562, NE564, NE565, NE566, NE567, LM100C, LM1301AN, LM308N, LM311, LM318H, LM318N, LM324N, LM339N, LM348N, LM377N, LM380N, LM381N, LM382N, LM386N, LM733, LM1310N, LM1458N, LM1930, LM2217, LM3390N, LM3391N, LM3392N, LM3499N, LM3500N.

WHY PAY MORE FOR YOUR MEMORIES — MICRO — LINEAR PRODUCT

COMPARE OUR PRICES

PART	DESCRIPTION	PRICE
TMS2516JL	Single supply 16K Eprom	£2.25
TMS2532JL	Single supply 32K Eprom	£6.00
TMS4116-15JL	16K Static Ram	£1.00
TMS9900JL	16 Bit CPU	£29.50
MC6800P	8 Bit CPU	£3.25
MCM2114C30	1K Static Ram 300ns	£0.90
MCM2114C30	As above (Low Power) 300ns	£0.90
MCM2114C45	1K Static (Low Power) 450ns	£0.88
UA741CP	Linear Amplifier	£0.12
TL062BCP	Bifet Op Amp	£0.35
LM324P	Quad Op Amp	£0.21
LM358P	Dual Op Amp	£0.20
LM393P	Dual Diff Comparators	£0.26

Package Type: JL Ceramic; P+C Plastic

All parts by leading manufacturers full spec and fully guaranteed
Despatch by return post

Terms of Business:

Cash/Cheque/POs with order

Prices listed are exclusive of VAT. Add 15% to total cost including post and packing

All orders under £20 add 50p post and packing

SHEBMAN ELECTRONICS

45 HANWORTH ROAD
SUNBURY ON THAMES, MIDDLESEX
Phone: SUNBURY ON THAMES 89469

Texas Instruments invented... the integrated circuit and the Pocket Guide

TTL £3.50

Volume One Digital Integrated Circuits.

A concise summary - logic and pin assignments - of all TTL semiconductor devices currently available from Texas Instruments, the world's largest manufacturer.

LINEAR & INTERFACE £2.50

Volume Two Professional Linear.

A detailed description of all Texas Instruments Linear and Interface integrated circuits (including second-source). Pin-out guides, device characteristics and complete support information are included.

Together these Pocket Guides make the complete reference to advanced bipolar integrated circuits from Texas Instruments.

To obtain your copies complete the order form and send together with your cheque or postal order (payable to Texas Instruments Ltd) to:

Texas Instruments Ltd, PO Box 50,
Market Harborough, Leics.



Please send me
Quantity _____ copies of the
TI Pocket Guide Volume I (TTL)
@ £3.50 each, total £ _____
Quantity _____ copies of the
TI Pocket Guide Volume II (Linear & Interface)
@ £2.50 each, total £ _____
I enclose cheque _____ to the value (add £1.50 p&p per
order) of £ _____ in payment.
Name _____
Company name (if any) _____
Address _____

ET01

Send completed forms to Texas Instruments Ltd, PO Box 50,
Market Harborough, Leics.


Texas Instruments invented the integrated circuit, the
microprocessor, and the microcomputer.
Being first is our business.

TEXAS INSTRUMENTS
LIMITED



B.K. ELECTRONICS A SOUND CHOICE FACTORY FRESH THANDAR TEST EQUIPMENT BY SINCLAIR

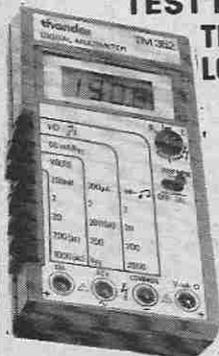The very latest TM352 HAND LCD DIGITAL MULTIMETER



- ★ 1/2" 3 1/2 digit display.
- ★ DC and AC volts.
- ★ DC current.
- ★ Resistance and diode check.
- ★ Audible continuity check.
- ★ hFE measurements.
- ★ Latest push-button controls for ease of operation.

DC voltage 200mV, 2V, 20V, 200V, 1000V.
AC voltage 200V and 1000V.
DC current 200µA, 2mA, 20mA, 200mA, 10A.
Resistance, diode check and continuity test 2KΩ,
20KΩ, 200KΩ, 2000KΩ.
hFE measurement 0-1000.
Power requirement 9V (PP3 battery).
Price **£56.00** (including test leads and battery).
Carry case **£3.45**.

SC110 FULLY PORTABLE OSCILLOSCOPE

The new Thandar SC110 represents a breakthrough in oscilloscope development. The
Full-sized performance SC110 is less than 2" thick and weighs
under 2lb., yet it retains the standard
features of a bench oscilloscope.

- ★ 10MHz bandwidth.
- ★ 10mV per div. sensitivity.
- ★ Full trigger facilities are provided,
including brightline and auto.,
with TV line and frame filtering.
- ★ Runs on ordinary HP11 (four)
batteries.

Basic price **£157.00**. Optional
extras: AC adaptor **£5.69**, re-
chargeable batteries **£8.63**, X1
probe **£9.78**, X10 probe **£11.50**,
carrying case **£8.86**.



★ All genuine Thandar accessories.


All prices include V.A.T. Official orders welcome. Mail order only, or callers by
prior appointment. Barclaycard/Access welcome. Cash/cheque, etc., with order.
Large s.a.e. for complete Thandar list. Government and Educational Estab-
lishments official orders welcome.

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex, SS9 5TY
Tel: Southend 527572

ENLARGER TIMER

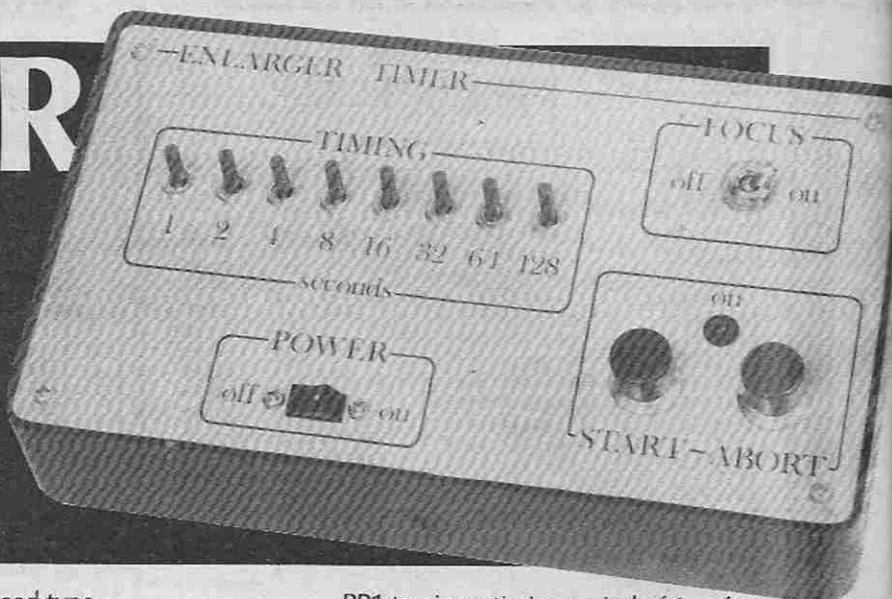At last — an enlarger timer designed for the photographer by a photographer. Design and development by Tony Alston.



Most enlarger timers use either potentiometers or rotary switches for time period selection; however, both these methods suffer from some drawbacks. First the potentiometers, although inexpensive, are generally difficult to line up with a timing mark especially under darkroom conditions, and also tend to wear out after long usage. The rotary switch overcomes the alignment problem but the timing period range is normally limited to the number of click stop positions — mostly 12 ways, maximum 18 ways. The ETI Enlarger Timer does not suffer from either of these problems; it uses only eight toggle switches in conjunction with the 2240 programmable timer IC to offer a wide range of accurate and easily selected timing periods ranging from one second to 4 minutes 15 seconds in one-second steps.

This flexibility is due to the programmable eight bit counter, oscillator and control flip/flop featured within the timer IC. Having set the time base to 1 s using PR1, R4 and C2, each single switch (SW1-8) will give the basic timing periods of 1, 2, 4, 8, 16, 32, 64 and 128 s; by switching in more than one switch, any combination of timing periods can be achieved as previously mentioned.

Construction

As can be seen from the photographs, all switches and push-buttons are mounted on the front panel together with the LED indicator. Suitable mains input and output sockets such as Bulgin miniature mains type are mounted on the rear case panel, input nearest the transformer, output (for the enlarger) by the PCB. The PCB design will enable an easier and neater assembly, but make sure to orientate components D1-D5, Q1, IC1, C2, C3 and LED1 as shown in the overlay diagram. Note that C2 must be

a tantalum bead type.

Once all the components are mounted on the PCB and the switches, LED1, sockets and transformer are wired to the board, make sure that the panel assembly does not foul the transformer or the relay when fitted to the case.

Setting Up

This couldn't be easier; having checked all connections, connect the timer to the mains and the enlarger to the unit. First put switches SW1-8 and SW10 in the off positions, put SW9 (on/off switch) in the on position, operate focus switch SW10 and the enlarger lamp will light. Switch SW10 to the off position. Adjustment to the timing range can now be made; switch SW1 only (1 s switch) to on and adjust

PR1 to give a timing period of 1 s after PB1 (start) is pushed — a stopwatch or digital watch is ideal for this.

Using The Timer

Switch on SW9 (on/off switch) and power will be applied to the circuitry. SW10 can be used for focusing the enlarger; cancel SW10 once this is done. Select the timing period required using a combination of SW1-8, push PB1 and the enlarger lamp timing cycle will commence; after this period the timer will stop/reset. LED1 will be on during timing period as a visual indication. If cancellation of a timing period is needed press PB2 which will abort and reset the timer. If any interference from RLA/2 is experienced, fit a 100n 600 V capacitor as marked on the circuit and overlay diagrams (C4).

HOW IT WORKS

The heart of the ETI Enlarger Timer is the 2240 programmable timer IC which features a time base oscillator, programmable eight bit counter and a control flip-flop that can be used in monostable or astable mode. Here it is used in the monostable mode.

On application of a positive pulse to pin 11 (trigger) via PB1 and R1, the timing cycle is started. The trigger input activates the time base oscillator, enables the counter section and sets the counter outputs low from their normally high state. This switches on Q1 and activates RLA for the time duration as set by the SW1-8 combination. The timing sequence is completed when a positive pulse is applied to pin 10 (reset) via R3 from the output bus, disabling the time base and counter sections and returning the counter outputs to a high state.

The duration of the timing cycle T_o is given as:

$$T_o = nT = nRC \text{ seconds}$$

(R in ohms, C in farads)

where $T (= RC)$ is the time base period as set by the timing components at pin 13 (PR1, R4 and C2) and n is an integer in the range of $1 \leq n \leq 255$ as determined by the combination of counter outputs (pins 1-8) via SW1-8 to the output bus. The time base

as set by PR1, R4 and C2 is 1 s.

The binary-counter outputs are the open collector type and can be shorted together to the common pull-up resistor R6. Thus the time delays associated with each counter input can be added together; for example, if pin 6 is connected by SW6 to the output bus the duration of the timing cycle, T_o , is 32T. (T is 1 s as previously stated). Similarly, if pins 1, 5, and 6 are all connected to the output bus via their appropriate switches SW1, SW5 and SW6 the total time delay is 49T (1 + 16 + 32). In this manner the timing cycle can be programmed to be from 1 s to 255 s (four minutes 15 s) in 1 s steps by proper choice of switches SW1-8.

The enlarger lamp is powered from the AC outlet socket and receives its current via the RLA/2 contacts for the duration of the selected timing period. An LED is incorporated as a visual indicator; it is switched on by RLA/1 and remains on for the timing period. Manual cancellation is provided for by PB2 which applies a positive pulse to pin 10; this can be used at any point in the timing period. SW10, the focusing switch, overrides the RLA/2 contact regardless of the output state of IC1 thus enabling the enlarger to be focused.

The power supply consists of T1, D2-D5 and C3 which provides smoothing.

PARTS LIST

Resistors (all 1/4 W, 5%)

R1,2,6	10k
R3	47k
R4	33k
R5	22k
R7	1k5

Potentiometer

PR1	22k miniature horizontal preset
-----	---------------------------------

Capacitors

C1	10n disc ceramic
C2	22u 16 V tantalum
C3	1000u 25 V axial electrolytic
C4	100n 600 V mixed dielectric

Semiconductors

IC1	uA2240CP
-----	----------

Q1	2N3702
----	--------

D1	1N4148
----	--------

D2-5	1N4001
------	--------

LED1	0.2" red LED
------	--------------

Miscellaneous

PB1,2	momentary action push-button
-------	------------------------------

SW1-8	SPST miniature toggle
-------	-----------------------

SW9	SPST 240 V 3 A miniature rocker
-----	---------------------------------


SW10	SPST 240 V 3 A toggle
------	-----------------------

RLA	12 V DPDT PCB-mounting, 205R coil (see Buylines)
-----	--

Transformer (12 V, 250 mA or similar); AC outlet socket (Bulgin type); PCB (see Buylines); mains lead; case to suit (see Buylines).

BUYLINES

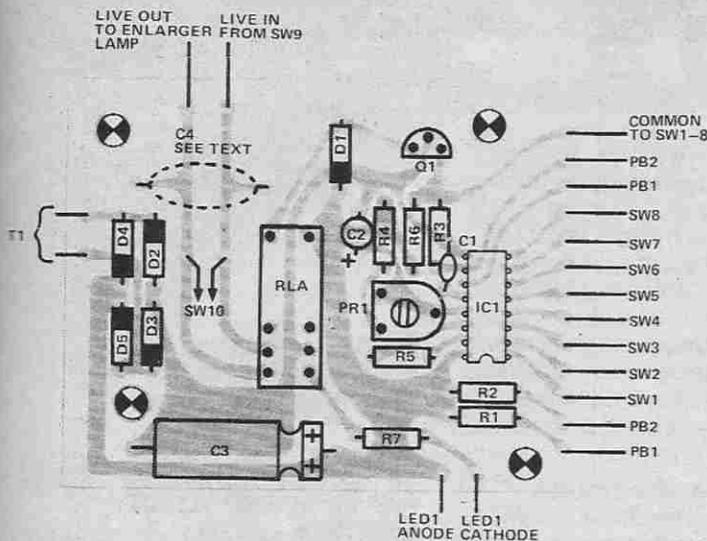Most of the components used in this project can be easily obtained for component retailers or mail order firms. IC1 is available from Technomatic and the relay is from Watford Electronics. The case we used is from Tandy, order no. 270-627; and if you don't want to make your own PCB from the foil pattern at the back of the magazine, then take a look at the advert for our PCB Service on page 54.



(Left) Inside the prototype, showing the neat layout and tidy wiring.


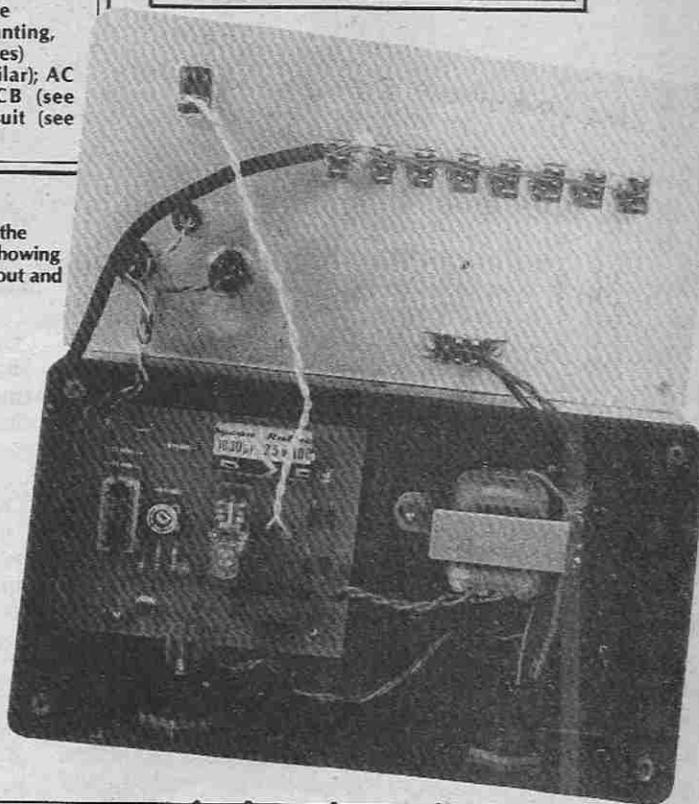


Fig. 1 Component overlay of the ETI Enlarger Timer.

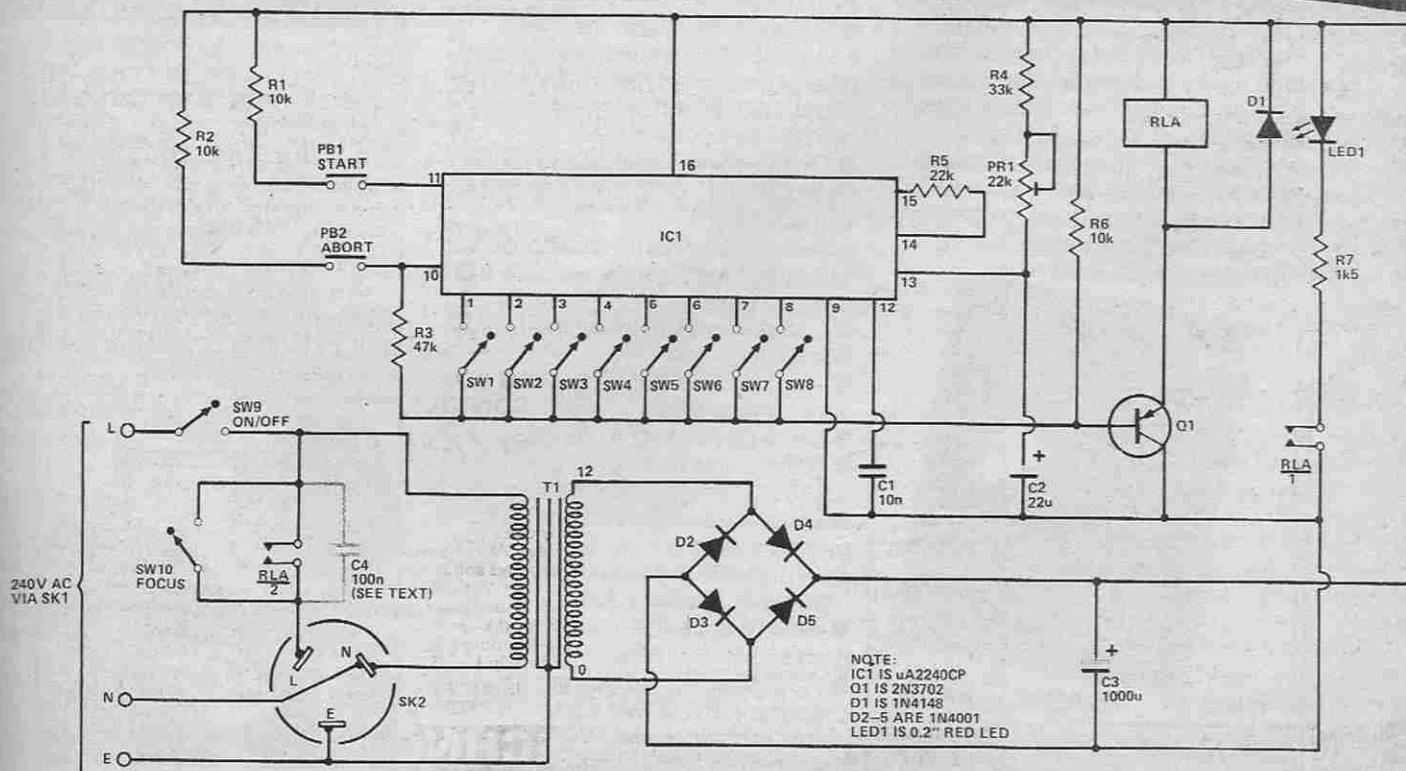

NOTE:
IC1 IS uA2240CP
Q1 IS 2N3702
D1 IS 1N4148
D2-5 ARE 1N4001
LED1 IS 0.2" RED LED

Fig. 2 Complete circuit diagram of the timer. C4 may be necessary to suppress switching noise from the relay contacts.

Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!


Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

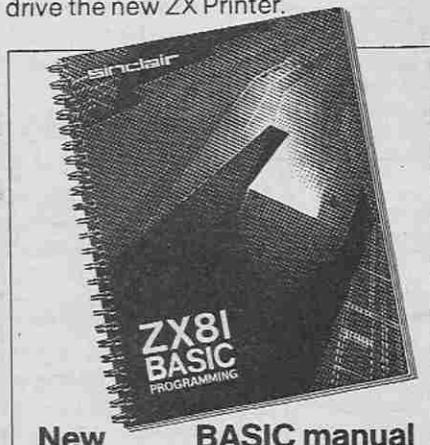And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

Kit: £49.⁹⁵

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



puter-



Available now - the ZX Printer for only £49.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumeric and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.

Qty	Item	Code	Item price £	Order Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

*Please charge to my Access/Barclaycard/Trustcard account no.

*Please delete/complete as applicable.

Please print.

Name: Mr/Mrs/Miss

Address:

FREEPOST - no stamp needed. Offer applies to UK only.

ETI 10

sinclair ZX81

3 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: (0276) 66104 & 21282.

LONDON'S
TEST EQUIPMENT
CENTRES

AUDIO ELECTRONICS

Retail • Mail Order • Industrial • Educational • Export

OPEN SIX DAYS A WEEK • CALL IN AND SEE FOR YOURSELF

ALL MODELS
ON DISPLAY
ALL PRICES INCLUDE VAT



TRIO OSCILLOSCOPES

Range of mains operated Scopes with 5" displays, triggered sweep (UK c/p £3.50)

DUAL TRACE

CS1562A 10 MHz, 10 mV, 1 micro sec.	£267.95
CS1560A II 15 MHz, 10mV, 0.5 micro sec.	£341.55
CS1566A 20 MHz, 5mV, 0.5 micro sec.	£363.40
CS1577A 35 MHz, 2mV, 0.1 micro sec.	£523.25
CS1830 Mk II 30MHz, 2mV, 0.2 micro sec. (fitted delay line)	£626.75
CS1575 5 MHz, 1mV, 0.5 micro sec. Multi display Audio scope.	£312.80

SINGLE TRACE

CS1559A 10 MHz, 10mV, 1 micro sec. 5" display Triggered sweep (UK c/p £3.50)	£251.85
CO1303D 5 MHz, 10mV, low sweep for observation below 1 Hz and up to 450 MHz, 75mm display (UK c/p £2.00)	£124.20

Optional probes - all models.
X1 £8.50 X10 £10.50 X1-X10 £12.95 X100 £16.95



THANDAR - SINCLAIR

Reliable low cost portable instruments, bench models all 25.5 x 15 x 5cm. Generators mains operated rest battery (supplied). UK c/p Hand models 65p, bench £1.15

DIGITAL MULTIMETERS (3 1/2 digit LCD)

TM354 Hand held, DC 2A, 2m ohm, 1mV - 1000V DC, 500V AC	£45.94
TM352 Hand held, DC 10A, Hfe test, Continuity test	£57.44
TM353 Bench, 2A AC/DC, 1000V AC/DC, 20M ohm, Typical 0.25%	£96.60
TM351 Bench, 10A AC/DC, 1000V AC/DC, 20M ohm, Typical 0.1%	£113.85

FREQUENCY COUNTERS (8 Digit)

PFM200 Hand held LED, 200 MHz, 10mV (600 MHz with TP600)	£57.27
TF040 Bench LCD, 40 MHz, 40mV (400 MHz with TP600)	£126.50
TF200 Bench LCD, 200 MHz, 10-30mV (600 MHz with TP600)	£166.75
TP600 600 MHz + 10 Prescaler 10 mV	£43.13

GENERATORS (All bench models) mains operated
TG100 Function 1 Hz-100 KHz, Sine/SQ/Triangle/TTL £90.85
TG102 Function 0.2 Hz-2 MHz, Sine/SQ/Triangle/TTL £166.75
TG105 Pulse, 5 MHz-5 Hz (200ns-200ms) various outputs £97.75


OSCILLOSCOPE (Bench model low power portable)
10 MHz 2" trace, 10mV, 0.1 micro sec. All facilities, Model SC110 £159.85
(Rechargeable battery pack £8.63, AC adaptor/charger £5.69)

OPTIONAL ITEMS

Carry case (bench only) £8.84 AC Adaptors (state model) £5.69



MULTIMETERS

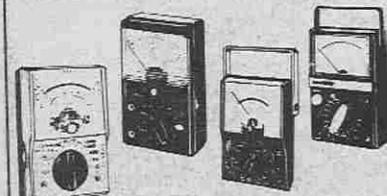

(UK c/p 65p or £1.00 for two)
CHOOSE FROM UK'S LARGEST RANGE

KRT101 10 range pocket 1K/Volt	£4.50
KRT100 12 range pocket 1K/Volt	£5.50
NH55 10 range pocket 2K/Volt	£6.50
AT1 12 range pocket Deluxe 2K/Volt	£7.75
ST5 11 range pocket 4K/Volt	£8.50
YN360TR 19 range plus Hfe Test 20K/Volt	£11.95
NH56 22 range pocket 20K/Volt	£13.50
ST303TR 21 range plus Hfe Test 20K/Volt	£15.95
KRT5001 16 range - range double 50K/Volt	£16.50
AT1020 19 range Deluxe plus Hfe Test 20K/Volt	£16.95
ETC5000 As KRT5001 plus colour scales 50K/Volt	£17.95
7081 18 range - range double 10A DC 50K/Volt	£20.85
TMK500 23 range, Plus 12A DC Plus Cont. Buzzer 30K/Volt	£22.75
AT205 21 range Deluxe 10A DC 50K/Volt	£25.75
C7080 26 range large scale 10A DC, 5KV AC/DC 20K/Volt	£27.50
AT210 23 range Deluxe 12A AC/DC, 100K/Volt	£31.00
360TR 23 range Large scale 10A AC/DC Hfe Test 50Meg ohm, 1KV AC/DC 100K/Volt	£34.95

CLAMP-ON-METERS INSULATION TESTERS



Multi-range clamps all with resistance range, carry case & leads. Also digital and DC clamp in stock (UK c/p 75p)

ST300 300A 600V 9 ranges	£25.95
ST310 300A 600V 9 ranges	£29.95
K2602 150A, 600V, AC 7 ranges	£35.95
*K2606 300A, 600V, AC 8 ranges	£44.00
K2803 300A, 600V, AC 9 ranges	£53.95
K2903 900A, 750V, AC 9 ranges	£77.50
K2103 1000A, 750V, AC 9 ranges	£95.00

*Optional temperature probe £13.80

ELECTRONIC INSULATION TESTERS

Battery operated complete with carry case (UK c/p £1.00)

YF500L 500V/100Meg. Plus 0-100 ohm	£55.00
K3103 600V/100Meg. Plus 0-2.6K ohm	£95.00
K3106 500V & 1000V, 1000 & 2000Meg	£104.00
K4101 Earth resistance tester	£136.50
M500 Hand cranked insulation tester 500V/100Meg.	£67.50

CROTECH OSCILLOSCOPES

Range of Portable Scopes mains and battery operated. Plus special features (UK c/p £3.00)

3030 Single trace 15 MHz, 5 mV, 0.5 micro sec. Plus built in component tester, 95mm tube	£166.75
3131 Dual trace 15 MHz, trig to 35 MHz, 5mV, 0.5 micro sec, 130mm tube, plus component tester.	£264.50
3034 Battery-mains dual trace 15 MHz, trig to 20 MHz, built in Nicads, 5mV, 0.5 micro sec. (Eliminator charger optional £28.75)	£356.50

Also Available 3033, single trace 3034 3035, 130mm 3030 3337, dual 30 MHz, 130mm (Optional Probes all models - see Trio above)

3033, single trace	£293.25
3035, 130mm	£189.75
3337, dual 30 MHz, 130mm	£408.25



LOGIC PROBE



(UK c/p 45p)
Leader LDP076 50 MHz
10MEG ohm, 10n Sec. with carry case £56.90

DIRECT READ HV PROBE




(UK c/p 65p)
0/40KV: 20K Volt £18.40

OSCILLOSCOPE PROBE KITS

(UK c/p 50p per 1 to 3)
Available BNC plug or Banana
X1 £8.50 X10 £10.50
X1-X10 £12.95
Also X100 (BNC only) £16.95

TRIO GENERATORS

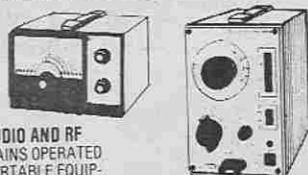

AUDIO AND RF MAINS OPERATED PORTABLE EQUIPMENT (UK c/p £1.10)

SG402 6 range RF 100 KHZ - 30 MHz ± 1.5. INT/EXT. MOD. 100 mV o/p Variable	£88.00
AG202A Matching 4 range Audio, 20 Hz - 200 KHZ Sine Square. Distortion 0.5-1% Variable o/p to 10V	£78.20
AG203 5 band 10 Hz - 1 MHz, Sine/Square, 0.5dB deviation, Distortion Max. 0.1% Switched Alternator & variable.	£126.50

ALSO IN STOCK Newtronics 200P & 200SPC 0.002 Hz 5.5 MHz Generators (200 SPC with 100 MHz counter)

PROFESSIONAL MULTIMETERS



(UK c/p £1.50) All featuring AC/DC Volts/Current & Ohms ranges

M1500 43 range 20K/Volt: AC/DC 10A	£53.50
M1200 30 range 100K/Volt: AC/DC 15A 200 Meg ohm.	£67.50
K1400 26 range large scale 20K/Volt: 10A AC/DC, 20 Meg ohm: 5kV AC/DC	£79.95
K200 39 range 10 Meg ohm input, 25 Hz-1 MHz	£95.00

OPTIONS Cases: M 1500 & 1200 £16.50; K1400 £19.00
Temperature Probe for K1400 £13.80

THURLBY DIGITAL MULTIMETER



4 1/2 Digit, 0.05% 7 Function LCD
Made to exacting standards in UK
30 ranges: 1200V DC, 750V AC, 10A AC/DC, 32 Meg ohm. Also includes frequency measurement to 4 MHz and 4 KHz output.
Price is with batteries, test leads and mains adaptor. (optional carry case £20.45)

£171.00
UK c/p £1.00

CALLERS WILL ALWAYS FIND A RANGE OF LOW COST TEST EQUIPMENT, ACCESSORIES, TOOLS, IRONS AND BOARDS IN STOCK. ALSO SPECIAL OFFERS FOR CERTAIN EQUIPMENT WHICH WILL VARY FROM TIME TO TIME

PRICE CORRECT AT TIME OF PREPARATION E & OE.
ALL PRICES INCLUDE VAT.
CHOOSE FROM UK'S LARGEST RANGE

ALL PRICES INCLUDE VAT

AUDIO ELECTRONICS

Cubagate Limited
301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564
ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2

OPEN SIX DAYS A WEEK • CALL IN AND SEE FOR YOURSELF

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order



FREE CATALOGUE!

Send large SAE (20p UK)
Schools, Companies, etc. free on request.

PROGRAMMABLE SCIENTIFIC CALCULATOR

CASIO FX-602P

CASIO FX-602P

Those clever Casio people have done it again. This calculator? — computer? — puts real programming power in your pocket. With Ron Harris on keyboards.

With the advent of the Sharp PC1211 BASIC computer, there are those who have questioned the need to produce programmable calculators at all. With a handheld computer, programmable to do almost anything except make the tea, why bother with a calculator — which has no string handling at all and is necessarily limited in its memory space? The argument rounds off, usually, with the surmise that with the continued plummet in memory cost, it won't be long before 8K handheld machines are available, with all the power of the earlier personal computers.

This may all be true, but somehow I think it will take a little longer than the optimistic programmer fraternity would have us believe.

Even if we all awoke from our slumbers with the dawn tomorrow to find some friendly faerie people had left a handheld TRS-80 under our pillows — with or without stealing our teeth in payment — there will remain a place in the universe for the calculator. After all, working out the electricity bill or last month's overdraft hardly requires an electronic brain the size of a planet, now does it?

Everyday, mundane computations are more readily accomplished at the push of a button, without the need of recourse to an all-singing, all-dancing, all-branching computing marvel. Theirs is a loftier realm.

Casio Diversions

Having gone to all this trouble to justify the existence of the calculator, I must say that this FX-602P from Casio is a brave attempt at totally blurring the distinctions between calculator and computer. It has string handling, of a sort, GOSUB and

GOTO commands, a facility to swop memory against program steps, and the option to save programs on tape.

Normally it has 512 program steps and 22 memories. This can be varied up to 32 program steps and 88 memories. As you can see memories cost more than one step apiece. As with its predecessor, the FX-502 (see ETI February 80 issue), the 602 can be hooked up to a tape machine via the FA-1 adaptor.

Rather than me spend large numbers of words explaining what the 602 will do, take a look at the keyboard diagrams given herein, as these show all the keys and their functions more clearly than my prose could illustrate them.

Alpha Modes

The main difference between the 602 and its predecessors is the ability to input and use alphanumeric strings both in the program — usually as prompts or result indicators — or simply to live up routine calculations.



Each character is made up on a 7 x 5 dot matrix on the LCD display. Each 'dot' is in fact a small rectangle and imaginative use of this matrix by Casio has given a good clear display with a versatile character set.

As Before . . .

As with the 502, this new machine uses different 'modes' of operation to allow programming and debugging. Mode 1 is the 'RUN' mode and Mode 2 the 'WRITE' mode, which, when selected, lists up the available programs (from a selection of 10) and the number of steps left for use.

It is curious that selecting 'WRITE' mode is in itself con-

FA 1 connector

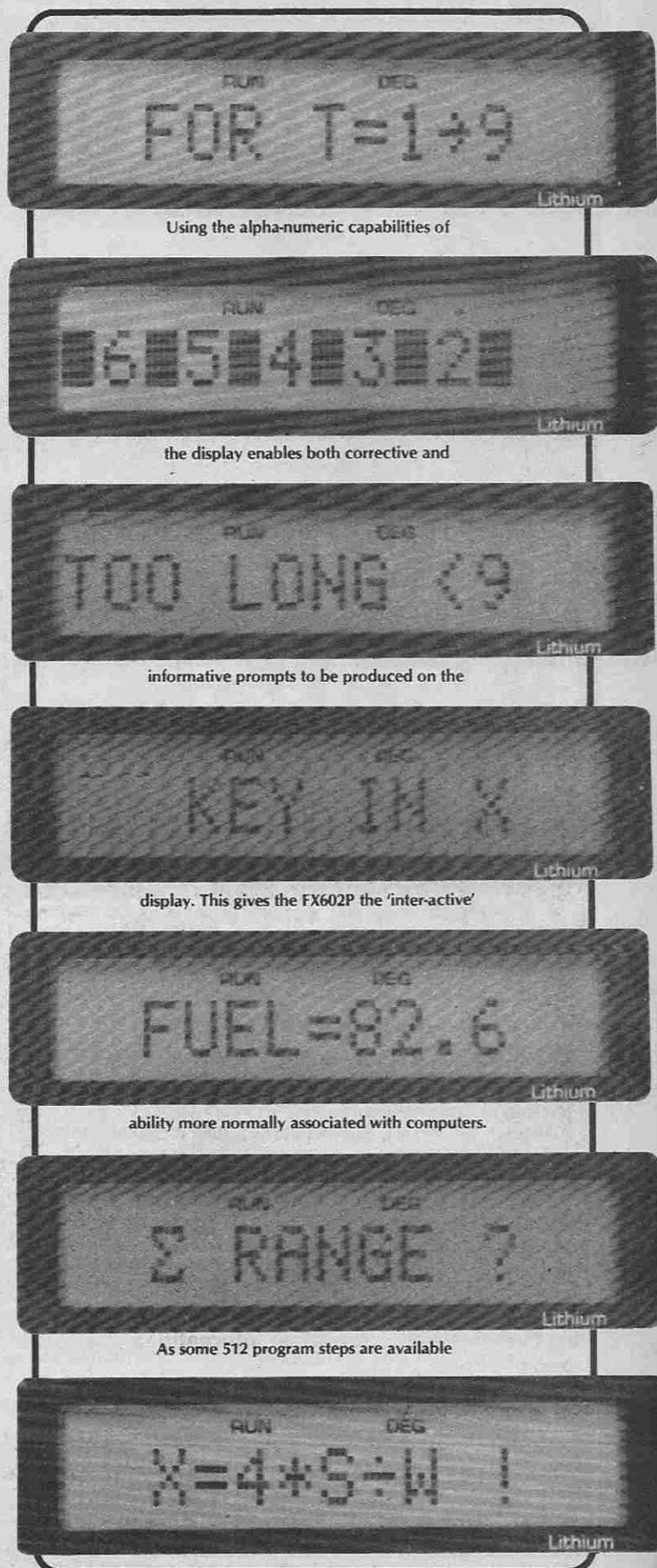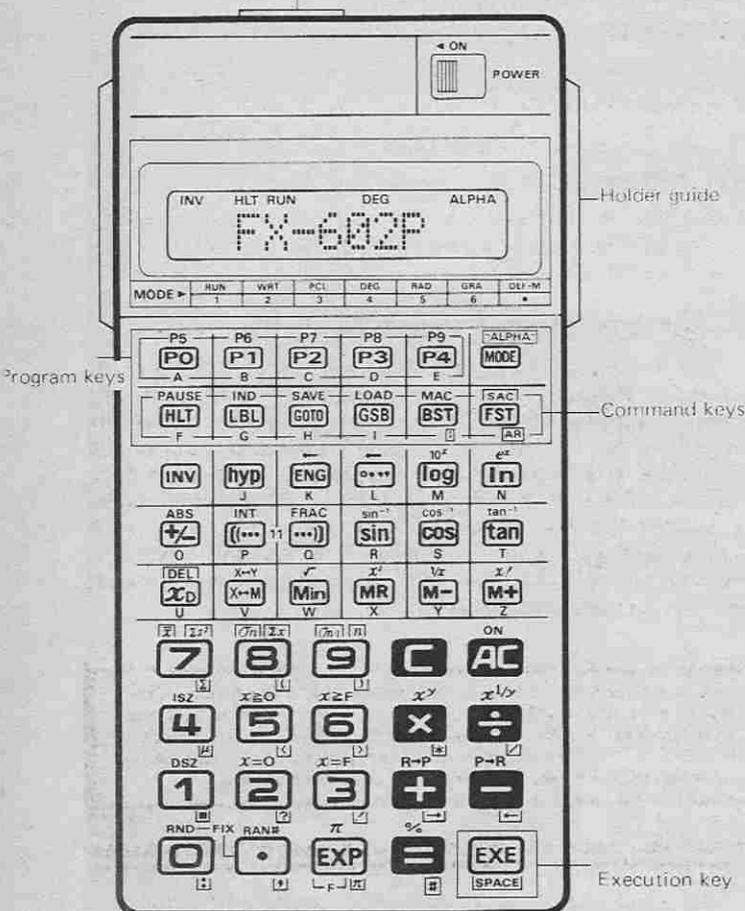

A close-up of the FX602P keyboard when used in the programmable mode. The top two rows of keys control program 'call' and mode selection. Most of the functions of the FX602P can be read off from the keys themselves.

Note that the alpha characters are accessed by mode 'alpha' and then keying in each letter as written under the appropriate keys. The display will automatically scroll across to the left if you exceed the capacity. Under program control this means you could use the 602P to leave messages. "Dinner in the oven" maybe?

sidered a step. Effectively then, since each 'select' uses up a step, 512 are never quite available!

Other 'modes' employ either 'grads' or 'rads' in place of degrees for scientific calculation and will, no doubt, be of inestimable service to someone, somewhere.

Standard deviation is a 'standard' key function, as are 11 levels of parenthesis and a random number generator. It's possible to select (FIX) the number of decimal places in the random number to suit various applications. Percentages too can be obtained from a single keystroke.

All the information stored in program or data memories is retained, even with the 602 switched off. It takes only a two-key operation to clear the entire store, so care must be exercised here.

Under Program

When running a program, the 602 is capable of conditional branching, ie 'goto line XX if X > 0' etc, or a simple GOTO command which is employed in conjunction with sets of 'LABELS'. These the user keys in — they occupy a single program step each. In addition, other programs can be called as subroutines from a main control program. All very versatile.

The 'Alpha' mode allows you to insert strings of letters and/or symbols into the program at any stage desired. This can

Using the alpha-numeric capabilities of

the display enables both corrective and


informative prompts to be produced on the

display. This gives the FX602P the 'inter-active'

ability more normally associated with computers.

As some 512 program steps are available

FEATURE : Casio FX-602P

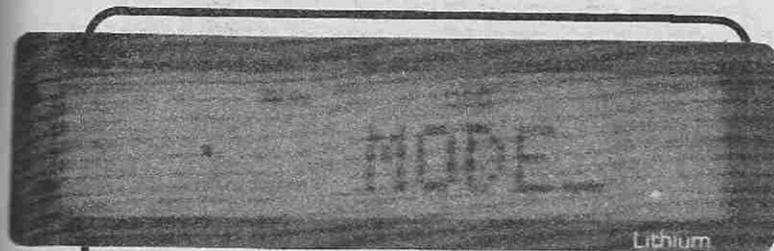

for use some very comprehensive software

Lithium



can be developed. Alpha-strings are permissible

Lithium



within the program execution at any point.

Lithium

be used as a prompt, for example

"KEY IN FUEL"

"KEY IN DISTANCE"

"AVE. MPG = 24.2"

or as indicators to answers or complex key routines requiring the user to keep track of a string of numbers, perhaps in a standard deviation calculation.


Calculated Expense -

All this will cost you around £74, which includes a comprehensive program library — although this contains mainly scientific applications and says much about the market in which Casio expect to sell the FX-602P. There can be no doubt at all that the 602P is good value indeed for its price and it duly takes its place at the top of the list of programmable calculators. I could find nothing to criticise in its operation of facilities and can only recommend it to anyone seeking a powerful portable machine, which has comprehensive control over memory and data space.


You can obtain the FX-602P from Tempus, 164-167 East Road, Cambridge CB1 1DB, for the princely sum of £74.95 including VAT and p&p. The FA-1 adaptor to allow storage of programs on tape will cost you £19.95. The basic program library is supplied with the calculator. Our thanks to Tempus for lending us the review machine.

ETI

TWO SIDES TO YOUR SUCCESS FROM VERO

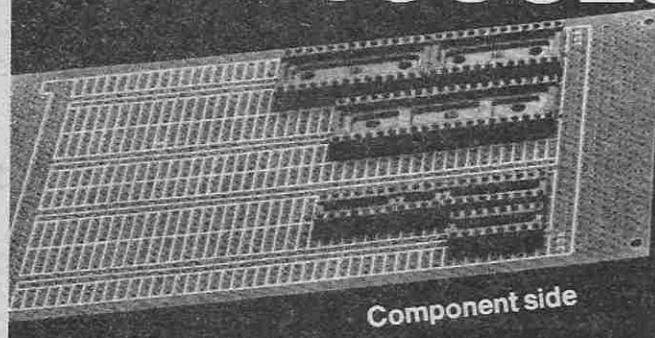

Component side

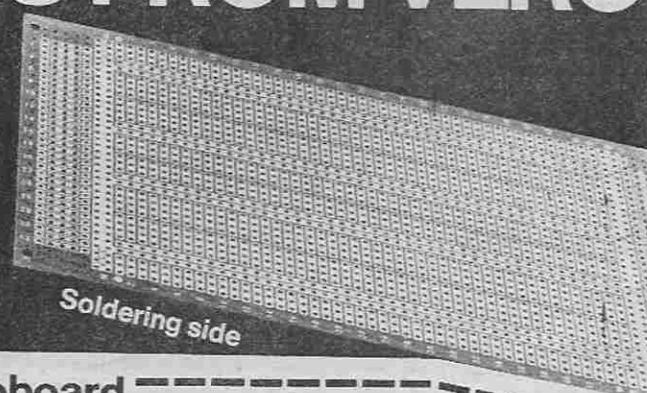

Soldering side

The Low Cost Eurocard Size Microboard

Fully Compatible with indirect connectors and Card Frames to the latest international specifications.

Accepts any Integrated circuit package — allows high packing density.

Screen Printed with 'island' pattern for ease of use — ideal for solder and wire wrap applications.



Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hampshire SO5 3ZR. Tel (04215) 62829

PLEASE SUPPLY QTY.	ORDERCODE	DESCRIPTION	SIZE	PRICE
	200-22271B	MICROBOARD	160 x 100mm	£3.47 each (including VAT & carriage)
	200-22270E	MICROBOARD	160 x 233mm	£5.47 each

Name: _____

Address: _____

Postal Code: _____

My Access/Barclay No. is: _____ Signed _____

ELECTROVALUE

74LS00 Series

00	14p	153	77p
02	14p	155	94p
04	16p	156	94p
05	23p	157	60p
08	20p	161	78p
10	19p	163	90p
11	20p	164	90p
14	58p	165	75p
20	18p	166	165p
30	21p	173	100p
32	22p	174	85p
37	24p	175	94p
38	35p	191	90p
42	59p	193	90p
47	89p	195	87p
51	25p	196	90p
73	30p	197	85p
74	30p	221	110p
75	44p	240	165p
76	30p	241	165p
85	80p	242	142p
86	38p	243	142p
90	44p	244	145p
92	59p	245	203p
93	57p	252	85p
107	40p	253	90p
112	38p	257	75p
123	82p	259	160p
125	45p	266	31p
126	42p	273	130p
132	60p	279	76p
136	42p	299	295p
137	110p	367	56p
138	64p	368	55p
139	70p	373	150p
145	120p	374	150p
148	165p	378	84p
151	77p	393	85p

MEMORIES Prime stock

2114	£2.40	2708	£3.00
4118	£7.90	2508	£3.50
4116(200nS)	£1.50	2516	£3.50

(All prices above are net)
2508 and 2516 are single rail

Z80 Series

Z80 2.5 MHz	£5.00	Z80 PIO 4 MHz	£6.00
Z80A 4 MHz	£6.00	Z80 CTC	£6.00
Z80 PIO 2.5 MHz	£5.50	6402 UART	£4.50

(All above prices are net)

SPECIAL OFFER FROM ELECTROVALUE

25 x 4116 each £1.30 net (32.50 n)

LOOK OUT FOR CATALOGUE 82

FREE with Practical Electronics Nov. issue

ORDERING

POSTAGE 40p on orders under £5.00
DISCOUNTS (Not on items marked Net or N)
5% on orders over £20.00
10% on orders over £50.00

Add VAT at 15% to total value of order in U.K.

ELECTROVALUE LTD. DEPT. ET110, 29 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB
Phone Egham 33603 (STD 0784) (London 87). Telex 264475
Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945

SPECIAL OFFERS

FUSE HOLDERS 20MM CHASSIS MOUNTING

10 for only	30p
100 for only	£2.50
1000 for only	£20.00

FUSE HOLDERS DOUBLE 20MM CHASSIS MOUNTING

10 for only	50p
100 for only	£4.00
1000 for only	£30.00

ASSORTED PACKS SELF-TAPPING, SELF-CUTTING SCREWS. 2lb. weight, approx. 700 items (U.K. only) £3.00

WIRE-WOUND RESISTORS BY V.T.M.

5K 9 watts 5%

10 for	50p
100 for	£3.00
1000 for	£20.00

ASSORTED IFs BY TOKO, etc., 10 for £50p
I.T.T. LEVER SWITCHES, 8 pole c.o., batch £1.00
HOOK-UP WIRE WITH PLUGS AND SOCKETS, very useful for TV Engineers 60p
TEXAS I.T.T. 1N4148, 100 for £1.50
MULLARD MATCHED PAIR AD161/162 50p

MULLARD POT CORES

LA3 100-500KHz	75p
LA4 10-30 KHz	£1.00
LA5 30-1000 KHz	£1.00
LA7 < 10 KHz	£1.00
Also LA13	£2.00

RELAYS 24V 3 C.O. HD 11-pin plug-in £1.50
A.E.I. MOTORS TYPE BP 1303/B, 100-125V S.P. 60 cycles, h.p. 3 watts, r.p.m. 1550 £3.50
FAIRCHILD FLV150, red, 2 LEDs, 10 for £1.00, 100 £8.65.

PLEASE NOTE ALL PRICES INCLUDE POST AND V.A.T.

IONISER KIT ZT13

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. This result? Your air feels like fresh ocean air, pure, crisp and wonderfully refreshing. All parts PCB and full instructions, £12.50. A suitable case including front panel, neon switch, etc. Available at £10.50.

T. POWELL

Dept. E.T.I.
Advance Works
44 Wallace Road, London, N.1
Tel: 01-226 1489

HOURS: Mon.-Fri. 9-5.30 p.m.
Sat. 9-4.30 p.m.



Minimum Telephone Orders: £5
Minimum Mail Order: £1

GREENWELD

443A Millbrook Road Southampton SO1 0HX
All prices include VAT @ 15% - just add 40p post

AMAZING!

COMPUTER GAMES

PCBs FOR PEANUTS!!

A bulk purchase of PCBs from several well known computer games including Battleships, Simon, Logic 5 and Starbird enable us to offer these at incredible low prices:

"STARBIRD"
Gives realistic engine sounds and flashing laser blasts - accelerating engine noise when mode is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt. clip (needs PP3 battery). Only £2.95 - 2 for £5. For details of other games, send SAE.

COMPONENT PANELS

A504 Black case 50x50x78mm with octal base. PCB inside has 24V reed relay, 200V 7A SCR, 4x6A 200V relays, etc. 60p.
2529 74 Series ICs - Gates and complex logic, 20 asstd ICs on panels £1, 100 ICs £4.
2527 2x6V reed relays. 6x25030 or 25230. 6x400V reeds, plus Rs. Only 50p.
2535 RAM panel - 36 2102A, 4 static RAM's, also 28 other chips inc. 7x LS75, 4x 74368, 3x 74180, etc. Only £5.
Z536. As above but extra 15 74LS chips £6.

LINEAR, OPTO

TIL311 Hexadecimal display with decoder, 0-9 and A-F. With data £3.50.
AD563KD D-A converter. Only £3.50.
FN5220 2 digit 1/2" 7-seg. display on PCB, CC. With data £1.50. 7-seg. displays: FND380, 501, all 50p; 530, 847, 850, all £1.50. Regs. TO3 cases: 7824 120p; 7885 100p; 7808 100p; 7812 100p; 78CB 230p. Others on B/L 13.
Op-Amps: uA4136 130p; uA776 145p; uA777 30p; uA318 245p.
Isolators: FCD831, IL15, TIL118, all 60p.

CAPACITOR BARGAINS

2200uF 100V cans 77 x 35mm dia. 75p; 10 - £5.50.
220uF 10V axial 5p; 100 £2.30; 1,000 £16.
40V - 100uF 275V 102 x 44mm dia. 75p; 10 £5.50.
200uF 350V, 100+100+50uF 300V can. 75 x 44mm dia. 40p; 10 - £3; 100 - £20.
100uF 25V axial, £3 - 100.

SUMMER CLEARANCE

Bulk Buyers Sale!!!

All prices 100+ one type. Add 15% VAT

Send SAE for full list

AC176	14p	BC547B	5p	BSY95A	61/2p
AD161/2	45p	BC548	5p	BU407	60p
BC107	7p	BC549	5p	PBC108	41/2p
BC108	6p	BC556A	6p	PN109	5p
BC109	7p	BC557A	6p	TIP30	22p
BC109C	8p	BC559	6p	TIP31A	17p
BC114	5p	BCY71	11p	TIP41A	28p
BC115	5p	BCY72	10p	TIP42A	29p
BC117	6p	BC131	18p	TIP42C	33p
BC119	14p	BD132	18p	TIP295S	46p
BC125	6p	BD133	18p	TIP305	45p
BC133	14p	BD137	20p	TIS43	20p
BC141	16p	BD138	20p	2N1132	16p
BC143	16p	BD139	16p	2N1171	18p
BC147	5p	BD140	20p	2N1893	16p
BC148	5p	BD221	35p	2N2369	12p
BC149	5p	BD222	35p	2N2894	12p
BC153	5p	BD246	30p	2N2904	16p
BC169	5p	BD278	28p	2N2926Y	41/2p
BC172	5p	BD525	24p	2N2928R	41/2p
BC182B	41/2p	BD526	24p	2N3011	14p
BC183	41/2p	BD543	30p	2N3055	30p
BC183L	4p	BD686A	45p	2N3638A	7p
BC209	7p	BF173	13p	2N3642	6p
BC212	41/2p	BF181	15p	2N3645	8p
BC214L (T05)	BF184	14p	2N3654	9p	
BC237B	4p	BF194	51/2p	2N3703	41/2p
BC238B	5p	BF195	51/2p	2N3704	41/2p
BC239B	5p	BF196	51/2p	2N3705	41/2p
BC252	7p	BF197	51/2p	2N3706	41/2p
BC256	6p	BF198	51/2p	2N3710	41/2p
BC307	6p	BF244	18p	2N4062	5p
BC308B	5p	BF257	15p	2N4124	7p
BC309	5p	BF258	20p	2N4400	5p
BC317	5p	BF259	20p	2N4403	6p
BC318B	5p	BF324	13p	2N4410	6p
BC319B	5p	BF355	18p	2N4418	8p
BC320	7p	BF394	51/2p	2N5193	20p
BC321B	5p	BF414	7p	2N5226	7p
BC326	7p	BF450	91/2p	2N5305	8p
BC348	7p	BF451	9p	2N5401	17p
BC351	14p	BF457	27p	2N5447	6p
BC413	5p	BF474	17p	2N5551	10p
BC441	19p	BF504	15p	2N5831	20p
BC461	20p	BFY51	13p	2N5858	7p
BC485B	6p	BFY52	13p	2N6121	16p
BC486A	6p	BFY64	15p	2N6290	40p
BC546B	6p	BSX20	13p	40673	45p

4 TERMINAL REGS

uA78MG in power mini-dip case 5-30V at 12A £1.
uA79MG Negative version of above £1.20.
Only 4 extra components required (50p extra) to make a fully variable supply! Data supplied.

1W AMP PANELS

A011 Compact audio amp intended for record player on panel 95x65mm including vol control and switch, complete with knob. Apart from amp circuitry built around LM380N or TB4820M, there is a speed control circuit using 5 transistors. 9V operation, connection data supplied. ONLY £1.50.

VU METERS

V006. Very attractive 55x48mm scaled 20 to 5dB, 250uA movement. Only £1.75 or £3 pr.

OP-AMP PSU KIT

A198. All parts + instructions to make a 50mA +15.0, -15V supply from mains input. Only £1.95

COPPER CLAD BOARD

K522. All pieces too small for our etching kits. Mostly double sided fibreglass. 250gm (approx. 110 sq ins) for just £1.

JOB LOT OF COMPONENTS

9,500 1N4006; 10,000 033/50; 22,000 10pF/50; 15,000 22/12; 11,000 270pF/50; 15,000 68pF/50. 30,000 various resistors. Total 112,500 components for £350 inc VAT & carr.

12 VOLT INDICATORS

Ideal for light chasers, etc. Miniature 12V 75mA wire ended lamps in yellow, red, green, blue and clear. 10p each. 20 each colour, total 100 for £5.50. 100 clear only £4.50.

EPROMS

INTEL 2716-1	£3.00
FAIRCHILD 2708	£3.00
T.I. 2516-45	£3.00

THE SPECTACULAR 1981 GREENWELD Component Catalogue

- ★ Bigger and better than ever!!!
- ★ 60p discount vouchers
- ★ First Class reply paid envelope
- ★ Free Bargain List
- ★ Priority Order Form
- ★ VAT inclusive prices
- ★ Quantity prices for bulk buyers
- ★ Free Data Sheet

SEND 75p FOR YOUR COPY NOW!!

ODDS AND ENDS

Transformer, mains in, 1770V 10mA out £2.50.
W847 PCB mntg. relay 11 x 33 x 20mm. 37R 5-10V SPDC 3A 99p.
901A5 Pickering DLL relay 500R, SP make. 3.7-10V, ex-equip. on PCB, 75p.
X905 140 x 10mm ferrite rod with LW and MW windings, 46p.
K520 Switch pack - 20 different, rocker, slide, rotary, toggle, push, micro, etc. Only £2.
K521 Heatshrink pack - 5 diff. sizes, each 200mm, 50p.
10M 1/2W 5% CF Resistors - pack of 200, £1.
40W amp PCB + CCT + layout, £1. All parts to make, £3.50.
1% 1/2W Rs - 111k, 333k, 500k, 900k, 950k. All 10p/25p.

TV TEST GEAR

Wobulators, Calibration Gens., Modulators, Sync. Generators, Encoders, Converters, etc. All cheap. SAE List.

VDU CRTs


Approx. 250" 12" and 15" 110" tubes available for callers only. All £15 each.

CHROMASONIC electronics

48 JUNCTION ROAD, ARCHWAY LONDON N19 5RD — 100 yards from Archway Station & 9 Bus Routes
 TELEPHONE: 01-263 9493/01-263 9495

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPUTERS

PET

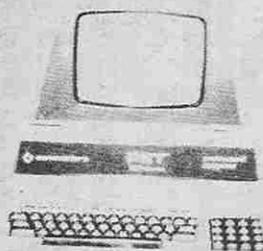

4008 8K RAM
 4016 16K RAM
 4032 32K RAM
 4040 Dual Drive Disk
 4022 80 column
 tracks feed.
 3023 80 column
 friction feed.
 C2N Cassette Unit.

For the business man we stock the 8000 range inc 8032 and 8050 with daisy wheel printers coming soon.

PHONE FOR MOST COMPETITIVE PRICES WORD PROCESSING AND 32K SYSTEMS PHONE FOR DETAILS

UK101

UK101 Kit inc 8K memory £125
 Ready Built inc 8K memory £175
 Complete in case £199
 4K Expansion 8x2114 £14
 Memory Expansion Kit 8K £79.95
 Memory Expansion Kit 16K £106.95
 Parallel Printer Interface £29.95
 Sound generator plus
 PIO kit £29.95
 Cases £24.50

NEW

Chromasonics Sound Kit £24.95
 Colour Kit £84.95

Inc. Demo Tape & Full Documentation. Send for details.

DOWN
IN PRICE

V
I
C
2
0

VIDEO GENIE



£279 EG3003

Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features. Simply plugs into monitor or UHF TV. With V.U. Meter.

PARALLEL PRINTER INTERFACE INC CABLE £33.00
 CHROMASONICS PROGRAMMABLE SOUND KIT £24.95
 SOUND KIT (FITTING EXTRA) £7.00
 LOWER CASE KIT (FITTING EXTRA) £27.50
 COLOUR KIT (FITTING EXTRA) £34.95
 EXPANSION BOX WITH/WITHOUT RS232 £215/£185
 16K/32K RAM BOARD £94/£129

NEW GENIE AVAILABLE SOON.

APPLE

APPLE II PLUS

48K Machines £595
 Disk Drive with Controller £349
 Disk Drive without Controller £299
 Graphic Tablet £460
 Colour Card £107



Accessory cards, Software
 All available — Phone for Details

PRINTERS



INTERFACES AND CABLES FOR APPLE II, PET, TRS80, RS232, UK101, SHARP SUPERBOARD ALL AVAILABLE.

EPSON MX80 £359

Dot-matrix printer with Pet graphics interface. Centronics parallel and serial. Pet and Apple compatible. True bidirectional, 80 cps.

EPSON MX80 FT/1 £399

Dual single sheet friction and tractor feed, 9 wire head, true descenders.

EPSON-MX FT/2 £449

An FT/1 with high resolution graphics.

EPSON MX70 £259

Tractor feed, 7 wire head, high resolution graphics.

SEIKOSHA GP80A £199

Dot matrix 5x7, 80 columns, 30 cps graphics, double width characters.

JUST PHONE FOR FURTHER DETAILS

MONITORS

Green Monitor £99.00
 MONI 9" (illust) B&W £82.00
 Hitachi professional monitors
 9" Black & White £99.95
 12" Black & White £149.00



VIC 20

Colours

24 total. 8 for characters, 8 for border, 16 for screen mixed as you wish. Basic colours on program keys are black, white, red, blue, light blue, green, yellow and purple.

Sound

3 Tone Generator for music, "White Noise" Generator for language and sound effects. Each Generator gives 3 octaves. Reproduction is through TV speaker.

Character/Line Display

22 Characters by 23 lines, 64 ASCII characters, pet-type graphic character set.

Keyboard

DIN typewriter keyboard with 8 programmable function possibilities via 4 special function keys. Colours are directly addressable from the keyboard.

Peripherals/Accessories

VIC Datacassette with special interface to guarantee high reliability read/write quality (PET/CBM compatible).

Price only £165.00.
 Cassette recorder £34.75 6
 sample programmes.



TANTEL

PRESTEL BY TANTEL
 COMMUNICATIONS AT YOUR FINGERTIPS
 FOR BUSINESS & HOME. UP TO DATE INFO

180,000 pages of information on Travel, News, Investment, Holidays, Hotels Etc., Etc.

£170

TANTEL IS POST OFFICE APPROVED. SEND FOR DETAILS.
 DEMONSTRATION AVAILABLE AT OUR SHOWROOM.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard (Min. tel. order £5). Export enquiries welcome. Official orders welcome.





SOUND BENDER

This neat little ring modulator has a built-in wide-range sine/triangle modulation oscillator and a 'pan pot' output mixer, but can be built (less the case) for under £10. Design by Ray Marston. Development by Steve Ramsahadeo.

One of the most popular types of cheap sound-effects units is the so-called 'ring modulator' or four-quadrant multiplier. These units have two inputs, one being a voice or music audio signal and the other being a simple sine or triangle oscillator waveform: the output of the unit is equal to the product of the two instantaneous signal amplitudes. In other words, the oscillator effectively amplitude-modulates the voice/music signal, to give some very interesting changes in the apparent signal content of the original voice/music material.

The ETI Sound Bender is a fully self-contained version of the popular ring modulator circuit. Naturally, however, our project has few special features. First, it has a built-in modulation oscillator that can span the frequency range 3 Hz to 5 kHz using a

single control pot and which can produce either sine or symmetrical-triangle output waveforms. Second, the actual ring modulator is based on a precision four-quadrant multiplier circuit that is integrated into the oscillator chip; the multiplier balance is externally adjustable, enabling the unit to be used either as a 'sound bender' or as a simple sine/triangle audio generator. Finally, the unit incorporates a two-channel audio mixer in its output stage, which enables the original and modulated audio signals to be mixed in any desired ratio (ranging from 'all original' to 'all modulated') by a single pan-pot type control.

Our unit is designed to operate from nominal audio input signal levels of about 100 mV RMS or greater and can simply be interposed between the output of the preamplifier and the

input of the main amplifier of an existing audio system. The unit is battery powered by a stack of eight 1V5 cells and typically consumes about 12 mA.

Construction

The ETI Sound Bender is a fairly simple project and construction should present very few problems. Build up the PCB as shown by the overlay, noting the use of 16 Veropins to facilitate the circuit interwiring, then fit the PCB into a suitable case and complete the interwiring to the off-board components, noting that the two halves of RV4 are contra-connected. On our prototype unit the four control pots are fitted on the unit's front panel and the two switches and the input/output terminals are fitted on the

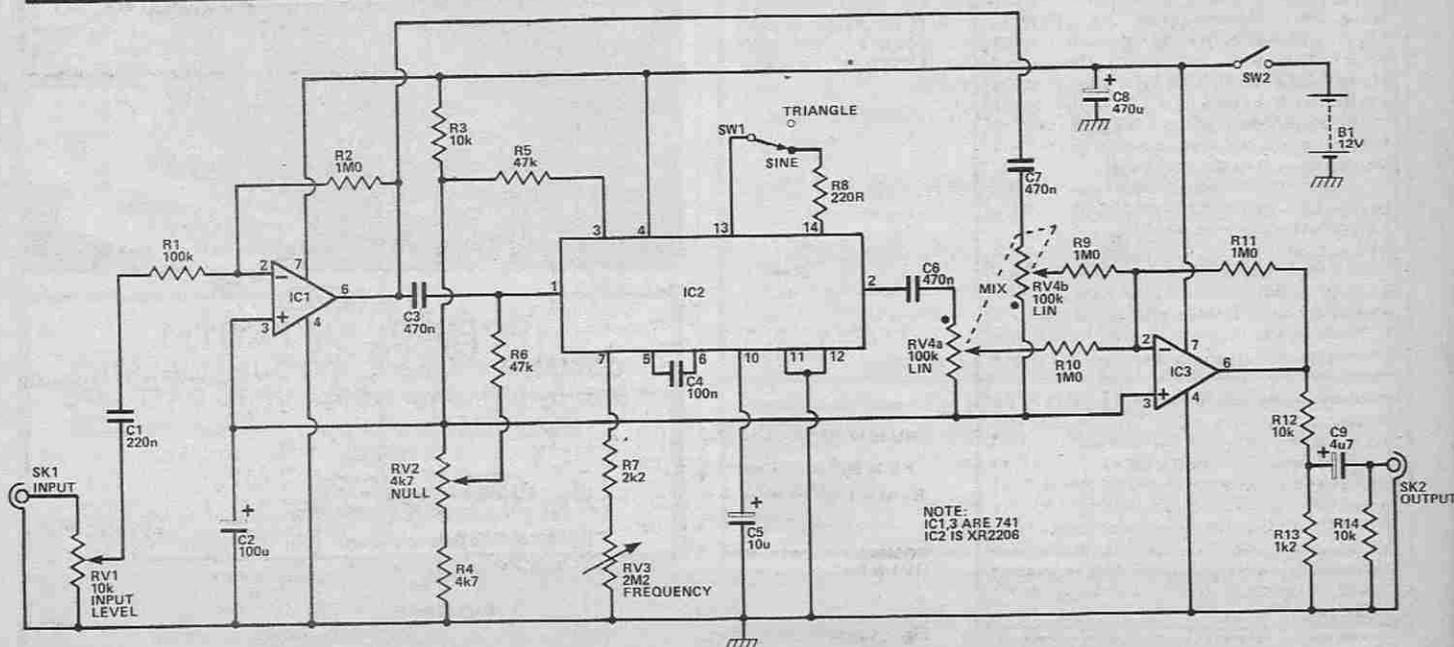


Fig. 1 Complete diagram of the ETI Sound Bender.

rear panel. As you can see from the photographs, the circuitry and battery pack make a fairly tight fit in the specified case.

The unit is very easy to use. Simply connect the output to an audio power amplifier/speaker combination, adjust RV2 (null) for zero output tone, then connect a voice or music input signal and see how the sound can be 'bent' using the frequency and mix controls. Level control RV1 is simply adjusted to give good sensitivity without amplitude limiting (clipping).

To use the unit as a simple audio generator, turn the input level control down and set the mix control (RV4) to give a 'modulation only' output, then adjust null control RV2 to give the desired output signal amplitude. RV3 then acts as the frequency control and SW1 gives selection of either sine or triangle output waveforms.

BUYLINES


There are no unusual components used in this project — the XR2206 should be available from most major mail order companies advertising in this issue. The case used can be obtained from Watford Electronics or OK Machine and Tool Ltd — order as CM5-125. The PCB is available from our PCB service as advertised on page 54.

HOW IT WORKS

The heart of this unit is IC2, an XR2206 function generator chip that incorporates a wide-range sine/triangle waveform generator and a precision four-quadrant multiplier within a single package. The output of the waveform generator is internally connected to one input of the multiplier, and the other input of the multiplier is accessible at pin 1: the output is available at pin 2.

In our application, the generator can produce either sine or symmetrical-triangle waveforms, depending on the setting of SW1, and its frequency (determined by C4-R7-RV3) can be varied over the range 3 Hz to 5 kHz via RV3. The pin 1 input of the multiplier is biased by RV2, which is normally adjusted to balance the multiplier so that it produces zero output when zero signal input is applied to pin 1.

The audio input signal is applied across RV1 and a fraction of this signal is tapped off and applied to $\times 10$ amplifier IC1. The output of IC1 splits into two paths, with one path passing to one input of two-channel audio mixer IC3 via RV4b, and with the other path passing to the input (pin 1) of IC2, which has its output (pin 2) taken to the other input of the IC3 mixer via RV4a. Note that mix controls RV4a and RV4b are contra-connected, so that they control the mixing action in 'pan pot' fashion, giving a final output from IC3 that ranges from 'all original signal' to 'all modulated signal' in the extreme settings of RV4. The output amplitude of IC3 is divided by 10 (by R12-R13), so that the final output signal has an amplitude roughly equal to that of the input signal feeding IC1, thereby giving the Sound Bender a good overall signal-to-noise ratio.

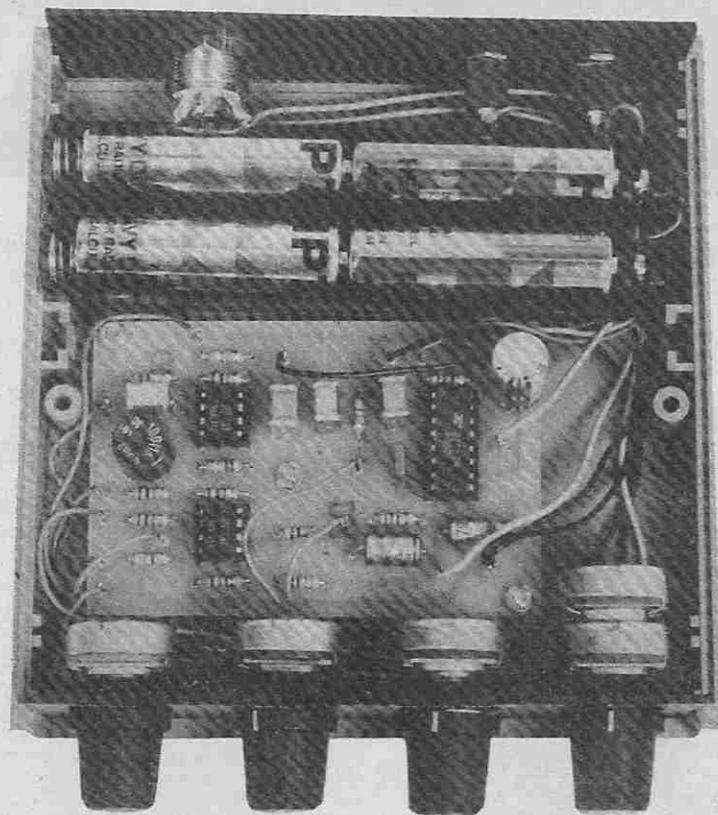

Everything does fit in the case specified, but only just!

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)		C2	100u 16 V PCB electrolytic
R1	100k	C3,6,7	470n polycarbonate
R2,9,10,11	1M	C4	100n ceramic
R3,12,14	10k	C5	10u 25 V axial electrolytic
R4	4k7	C8	470u 16 V PCB electrolytic
R5,6	47k	C9	4u7 16 V axial electrolytic
R7	2k2	Semiconductors	
R8	220R	IC1,3	741
Potentiometers		IC2	XR2206
RV1	10k linear	Miscellaneous	
RV2	4k7 linear	SW1,2	SPDT miniature toggle
RV3	2M2 linear	SK1,2	phono sockets
RV4	100k dual linear	PCB (see Buylines);	four-section HP7 battery holders (two off).
Capacitors			
C1	220n polycarbonate		

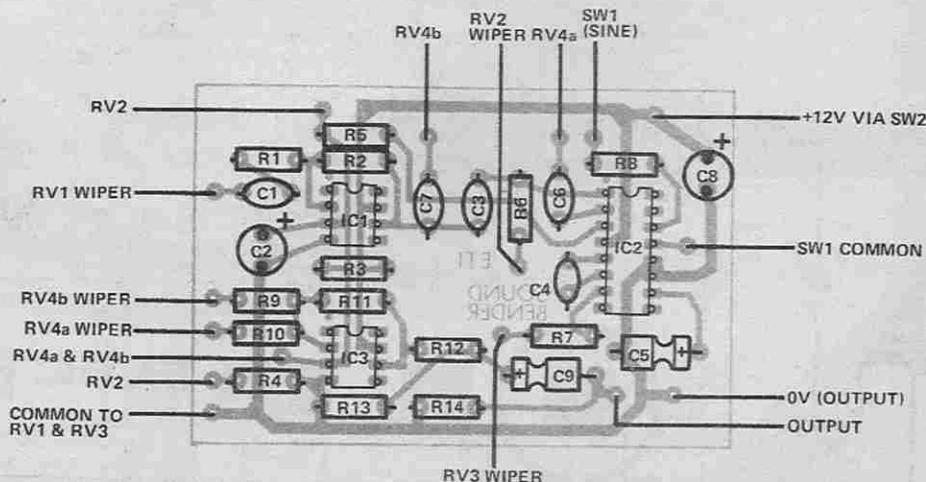



Fig. 2 Component overlay.

20 POWER AMPS

19 FUNCTIONAL MODULES

DAWN

POWER UP TO 480 WATTS RMS SINGLE CHANNEL

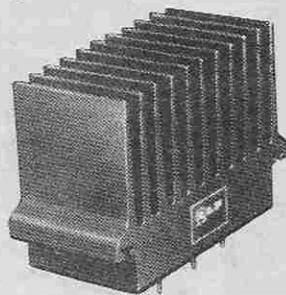

AMPLIFIER WITH HEAT-SINK

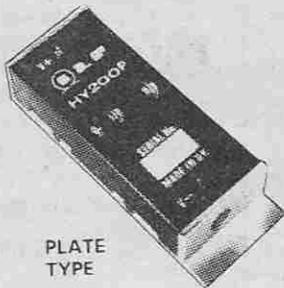


PLATE TYPE



PSU

Which amplifier?

I.L.P. Amplifiers now come in three basic types, each of which is available with or without heatsink. Having decided the system you want (home hi-fi (models HY 30, 60 or 120 for example), super quality hi-fi with extra versatility (MOS120, MOS200) or Disco PA/Guitar (HD120, HD200 or HD400) you will then decide whether amplifiers housed within their own heatsinks or plate amplifiers for bolting to a metal chassis will suit. With choice such as this and a brilliant new range of I.L.P. functional modules to choose from you now have the chance to build the finest audio system ever offered to the constructor.

BIPOLAR Standard, with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts-rms	DISTORTION		SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
		T.H.D. Typ at 1kHz	I.M.D 50Hz/7kHz 4:1											
HY30	15w 4-8Ω	0.015%	<0.006%	-18±20	76x68x40	240	£7.29	£1.09						
HY60	30w 4-8Ω	0.015%	<0.006%	±25±30	76x68x40	240	£8.33	£1.25						
HY120	60w 4-8Ω	0.01%	<0.006%	±35±40	120x78x40	410	£17.48	£2.62	HY120P	120x26x40	215	£15.50	£2.33	
HY200	120w 4-8Ω	0.01%	<0.006%	±45±50	120x78x50	515	£21.21	£3.18	HY200P	120x26x40	215	£18.46	£2.77	
HY400	240w 4Ω	0.01%	<0.006%	±45±50	120x78x100	1025	£31.83	£4.77	HY400P	120x26x70	375	£28.33	£4.25	

Protection: Load line, momentary short circuit (typically 10 sec) Slew rate: 15V/μs Rise time: 5μs
S/N ratio: 100db Frequency response (-3dB): 15Hz-50kHz
Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω/100Hz)>400

HEAVY DUTY with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts-rms	T.H.D. Typ at 1kHz	I.M.D 50Hz/7kHz 4:1	SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
HD120	60w 4-8Ω	0.01%	<0.006%	±35±40	120x78x50	515	£22.48	£3.37	HD120P	120x26x50	265	£19.84	£2.98	
HD200	120w 4-8Ω	0.01%	<0.006%	±45±50	120x78x60	620	£27.38	£4.11	HD200P	120x26x50	265	£23.63	£3.54	
HD400	240w 4Ω	0.01%	<0.006%	±45±50	120x78x100	1025	£38.63	£5.79	HD400P	120x26x70	375	£34.28	£5.14	

Protection: load line, PERMANENT SHORT CIRCUIT (ideal for disco group use should evidence of short circuit not be immediately apparent)
The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs. as for standard types.

MOSFET Ultra-Fi, with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts-rms	T.H.D. Typ at 1kHz	I.M.D 50Hz/7kHz 4:1	SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
MOS120	60w 4-8Ω	<0.005%	<0.006%	±45±50	120x78x40	420	£25.88	£3.88	MOS120P	120x26x40	215	£23.32	£3.50	
MOS200	120w 4-8Ω	<0.005%	<0.006%	±55±60	120x78x80	850	£33.46	£5.02	MOS200P	120x26x80	420	£28.53	£4.28	
MOS400	240w 4Ω	<0.005%	<0.006%	±55±60	120x78x100	1025	£45.39	£6.81	MOS400P	120x26x100	525	£38.91	£5.84	

Protection: Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).
Ultra-Fi specifications:
Slew rate: 20V/μs Rise time: 3μs S/N ratio: 100db Frequency response (-3dB): 15Hz-100kHz
Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω/100Hz)>400

POWER SUPPLY UNITS			PRICE	VAT
MODEL NO.	FOR USE WITH			
PSU30	15V combinations of HY6-66 series to a maximum of 100mA or one HY67 The following will also drive the HY6-66 series except HY67 which requires the PSU30.	£4.50	£0.68	
PSU36	1 or 2 HY30	£8.10	£1.22	
PSU50	1 or 2 HY60	£10.94	£1.64	
PSU60	1 x HY120, HY120P, HD120, HD120P	£13.04	£1.96	
PSU65	1 x MOS120, 1 x MOS120P	£13.32	£2.00	
PSU70	1 or 2 HY120, HY120P, HD120, HD120P	£15.92	£2.39	
PSU75	1 or 2 MOS120, MOS120P	£16.20	£2.43	
PSU90	1 x HY200, HY200P, HD200, HD200P	£16.20	£2.43	
PSU95	1 x MOS200, MOS200P	£16.32	£2.45	
PSU180	2 x HY200, HY200P, HD200, HD200P or 1 x HY400, 1 x HY400P, HD400, HD400P	£21.34	£3.20	
PSU185	1 or 2 MOS200, MOS200P, 1 x MOS400, 1 x MOS400P	£21.46	£3.22	

All models except PSU30 and PSU36 incorporate our own toroidal transformers.

FP480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by I.L.P. for use with any two power amplifiers of the same type to double the power output obtained and will function with any I.L.P. power supply. In totally sealed case, size 45 x 50 x 20mm, with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%.
Price: £4.79 + 72p V.A.T.

I.L.P. ELECTRONICS LTD.
FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP
Telephone (0227) 54778 (Technical (0227) 64723) Telex 965780
Available also from MARSHALLS, TECHNOMATIC, WATFORD ELECTRONICS and certain other selected retailers.

GOODS BY MAIL ORDER DESPATCHED WITHIN 7 DAYS

OF A NEW ERA



Which modules?

In launching eighteen different units all within amazingly compact cases to help make complete audio systems using I.L.P. power amplifiers, we bring the most exciting, the most versatile modular assembly scheme ever for constructors of all ages and experience. Study the list - see how these modules will combine to almost any audio project you fancy - and remember *all I.L.P. modules are compatible with each other*, they connect easily. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm. They are so reliable that all I.L.P. modules carry a 5 year no quibble guarantee.



MODEL NO.	MODULE	DESCRIPTION/FACILITIES	CURRENT REQUIRED	PRICE	VAT
HY6	MONO PRE AMP	Mic/Mag. Cartridge/Tuner/Tape/Aux + Volume/Bass/Treble	10mA	£6.44	£0.97
HY7	MONO MIXER	To mix eight signals into one	10mA	£5.15	£0.77
HY8	STEREO MIXER	Two channels, each mixing five signals into one	10mA	£6.25	£0.94
HY9	STEREO PRE AMP	Two channels mag. Cartridge/Mic + Volume	10mA	£6.70	£1.01
HY11	MONO MIXER	To mix five signals into one + Bass/Treble controls	10mA	£7.05	£1.06
HY12	MONO PRE AMP	To mix four signals into one + Bass/Mid-range/Treble	10mA	£6.70	£1.01
HY13	MONO VU METER	Programmable gain/LED overload driver	10mA	£5.95	£0.89
HY66	STEREO PRE AMP	Mic/Mag. Cartridge/Tape/Tuner/Aux + Volume/Bass/Treble/Balance	20mA	£12.19	£1.83
HY67	STEREO HEADPHONE	Will drive headphones in the range of 4Ω - 2KΩ	80mA	£12.35	£1.85
HY68	STEREO MIXER	Two channels, each mixing ten signals into one	20mA	£7.95	£1.19
HY69	MONO PRE AMP	Two input channels of mag. Cartridge/Mic + Mixing/Volume/Treble/Bass	20mA	£10.45	£1.57
HY71	DUAL STEREO PRE AMP	Four channels of mag. Cartridge/Mic + Volume	20mA	£10.75	£1.61
HY72	VOICE OPERATED STEREO FADER	Depth/Delay	20mA	£13.10	£1.97
HY73	GUITAR PRE AMP	Two Guitar (Bass/Lead) and Mic + separate Volume/Bass/Treble + Mix	20mA	£12.25	£1.84
+HY74	STEREO MIXER	Two channels, each mixing five signals into one + Treble/Bass	20mA	£11.45	£1.72
+HY75	STEREO PRE AMP	Two channels, each mixing four signals into one + Bass/Mid-range/Treble	20mA	£10.75	£1.61
+HY76	STEREO SWITCH MATRIX	Two channels, each switching one of four signals into one	20mA	To be announced	
+HY77	STEREO VU METER DRIVER	Programmable gain/LED overload driver	20mA	£9.25	£1.39

The modules are encapsulated and include latest design high quality clip-on edge connectors.

For easy mounting we recommend B6 Mounting board for modules HY6 - HY13 78p + 12p. V.A.T.

B66 Mounting board for HY66 - HY77 99p + 13p. V.A.T.

All I.L.P. modules include full connection data.

I.L.P. Products are of British Design and Manufacture.

All the above modules operate from -15V minimum to +30V maximum higher voltages being accommodated by use of dropper resistors. HY67 can only be used with the PSU 30 power supply unit.

Ready September may be ordered now

Now turn to our ad. on page 69

TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. If sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order. When ordering, U.K. customers must include the appropriate V.A.T. as shown.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED.

ALL WITH I.L.P.'S 5 YEAR NO QUIBBLE GUARANTEE

To: I.L.P. ELECTRONICS LTD, ROPER CLOSE CANTERBURY CT2 7EP

Please supply.....

Total purchase price £.....

I enclose Cheque / Postal Orders / International Money Order

Please debit my Access/Barclaycard Account No.....

NAME.....

ADDRESS.....

Signature.....

ALL U.K. ORDERS DESPATCHED POST FREE

ETI/10

RECEIVING YOUR ORDER

RADIATION DETECTORS

BE PREPARED VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture
Tested and fully guaranteed. Ex-stock delivery.

Henry's 01-723 1008/9

404 EDGWARE ROAD, LONDON W2 1ED

10 OUT OF 10.— IT'S ELEKTRIK!

- Who's amplifiers sound **audibly** superior?
- Who supplies the BBC, IBA, top loudspeaker manufacturers international recording studios etc?
- Which power amplifier modules feature high speed, electronic protection, virtually zero TIM, negligible THD, 110dB S/N ratio, and a range of power outputs from **60-300 WRMS**?
- Which amplifiers are **guaranteed** unconditionally stable thermally, electrically and mechanically?
- Whose reputation for back-up, service and **friendly** advice is second to none?
- Who makes amplifiers OEM capable of driving motors, magnets, vibrators etc?
- Who offers a complete hi-fi kit amplifier at **half** the cost of any comparable units?
- Who also specialise in **active** amplification?
- Who offers a complementary range of ancillary equipment such as heatsinks, bridge drivers and toroidal power supplies etc?
- Who is the **leading** name in innovative and proven amplification?


A **Crimson Elekrik**

If you would like further details on our complete range send a 7" x 10" sae + 50p cheque or PO for our comprehensive users/application manual to:
CRIMSON ELEKTRIK, (ETI), 9 CLAYMILL ROAD, LEICESTER LE4 7JJ. Telephone 0533-761920 Telex 34694 CRIMLEK

TTL	74157 45p	4069 16p	LS109 30p	BF194-7 10p	MEMORIES
7400 11p	74160 54p	4061 22p	LS123 60p	BF259 32p	2102 105p
7402 11p	74161 54p	4062 22p	LS125 44p	BF337 38p	2114-3 195p
7403 14p	74164 54p	4511 55p	LS126 44p	BU205 120p	4116-3 210p
7404 14p	74174 70p	4518 45p	LS157 35p	BU228 150p	2708 210p
7407 24p	74175 70p	4520 65p	LS160 45p	TIP31/2A 40p	2716 375p
7410 14p	74350 180p	4543 115p	LS161 45p	2N3055 44p	
7413 25p	74383 180p	4555 40p	LS164 45p		OPTO
7414 30p			LS174 50p		DL704 95p
7416 25p			LS175 50p		DL707 95p
7420 14p	CMOS-8	74LS	LS221 64p		DL747 150p
7426 22p	4002 12p	LS00 12p	LS221 64p	DIGIDES	
7430 15p	4006 80p	LS02 14p	LS290 110p	1N914 4p	
7441 55p	4011 14p	LS03 14p	LS293 110p	1N4001/4 6p	LEDs
7442 34p	4012 18p	LS04 15p		1N4006 7p	Green, Red
7447 45p	4013 33p	LS10 15p	LINEAR	1N5401/4 14p	Small 12p
7451 16p	4016 29p	LS12 15p	CA3130 30p	1N5407 24p	Large 15p
7454 16p	4017 50p	LS13 30p	LM303A 27p	W005 20p	
7473 25p	4023 19p	LS14 40p	LM311 70p	W01 30p	REGS. TO-220
7474 25p	4024 39p	LS20 15p	LM381A 160p	W04 36p	7805 55p
7486 25p	4027 27p	LS26 18p	741C-8 18p		7812/5 60p
7490 26p	4029 75p	LS30 18p	NE555 22p		7905/12/5 60p
7492 35p	4040 60p	LS42 36p	NE566 60p	DIL SOCKETS	VEROBOARDS
7495 30p	4046 70p	LS47 72p		Low Profile	Copperclad 0.1"
74107 26p	4048 28p	LS51 15p	TRANSISTORS	8 pin 8p	2.5" x 3.75" 73p
74109 35p	4050 28p	LS54 15p	AC127/8 25p	14 pin 9p	2.5" x 5" 83p
74121 28p	4051 62p	LS73 25p	BC107/9 10p	16 pin 10p	3.75" x 3.75" 83p
74123 35p	4052 62p	LS74 25p	BC147/8 9p	18 pin 16p	5" x 3.75" 95p
74141 45p	4053 62p	LS90 34p	BC157/8 9p	20 pin 18p	3.75" x 17" 326p
74151 40p	4055 95p	LS92 42p	BC184 9p	24 pin 20p	4.7" x 17" 426p
74153 40p	4056 85p	LS93 38p	BC214 9p	28 pin 24p	
		LS107 35p	BD131/2 40p	40 pin 32p	

MAIL ORDER, CWO Add 25p P&P, VAT 15%. Many more items in stock. Send SAE for full price list. 10% DISCOUNT ON ORDERS OVER £20

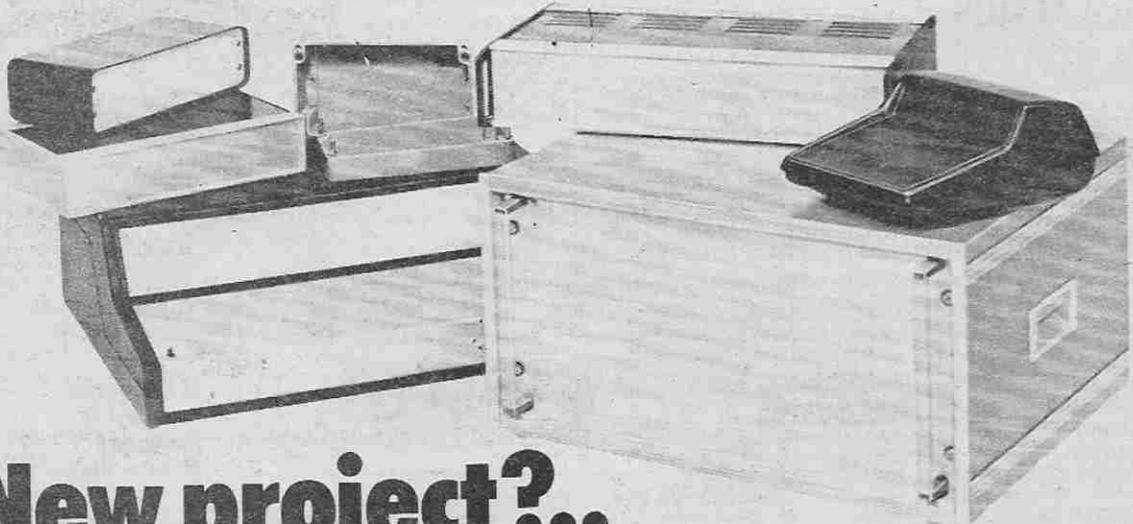AUDIO VIDEO SERVICES
19 GALS WORTHY AVENUE
ROMFORD RM6 4PX. 01-599 6680



New project?..

If you're about to start on a new project, you're no doubt looking for the right enclosure. With around 1,000 different cases and 250,000 case parts currently in stock, we must be your number one choice. Why not send for our free catalogue.

**Specify West Hyde-
we've a good case for it!**
WEST HYDE

West Hyde Developments Limited
Unit 9, Park Street Industrial Estate, Aylesbury, Bucks.
Telephone: (0296) 20441. Telex: 83570 W HYDE G.

Month	Project	Case
January 1981	Audiophile FM Tuner	CL2 CDJ
February 1981	Sound Pressure Level Meter	BOC 709B
March 1981	Crystal Frequency Calibrator	BOC 434
April 1981	Drum Synthesiser	BOC 668
May 1981	Noise Generator	TEK A2 3G
	Temp. Controlled Iron	BBA 1016
	IR Remote Control	SAM 006
		SAM 001
June 1981	Antenna Extender	BOA 115
	Drill Speed Controller	SAM 006
July 1981	Super Dice	BOC 450G
September 1981	LAB TSU	SWF 222X

Written or telephone orders accepted from Access and Barclaycard holders.



NEW POWER DIMMING MODULES

- ★ Fully isolated
- ★ Multi channel common wiring lines
- ★ Master dimming over banks
- ★ Remote override
- ★ Dead "kill" and "all on"
- ★ Low voltage feed lines
- ★ Common neutral or live outputs

Power Dimming Modules

A range of isolated digitally controlled dimming modules, complete with panels. Each type requires connection to the supply/reference board.

Slave power controllers (SPC)
Controls up to 1000W via the slider.
RFI suppressed/fused.

Slave power unit (SPU)
Controls up to 1000W via a logic signal from a remote slave.

Master controllers (MC)
Will master dim from 1 to a bank of 20 SPC units.

Remote slaves (RS) - (Preset)
Will override an SPC at a remote location to the main system.

Supply/reference board
Provides the necessary supply voltages and signals to all units. Facilities for "Kill" and "all on". Supplies up to any combination of 50 modules.

SPC	£11.90
SPU	£9.90
MC	£7.20
RS	£8.50
Supply	£28.20


SPECIAL DISCOUNTS

Are available on power dimmers. Total your order up and deduct:

£100 to £199	20%
£200 to £299	25%
£300+	30%

3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC £32.70

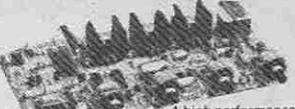

A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti-interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 50Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

STEREO DISCO MIXER/PREAMP

LBPA3
M - Magnetic
C - Ceramic



Magnetic or ceramic deck versions - please state. All the requirements of a stereo disco preamp on one board, left and right deck mixers/controls/misc. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with either LB 100/150/250.
Full set of pots - £8.63

2/4/8 CHANNEL CHASER LB81000LC



£28.00
An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

PROGRAMMABLE - 8

£114.90

P/P INS
£1.50



Complete with blue panel/white letters

- ★ 8 channel 400W each
- ★ 15, 32, 64, 128 patterns
- ★ Automatic program recycle
- ★ Adjustable cue on/off speed
- ★ Optically isolated, suppressed
- ★ Either common Neutral or live lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be replayed in the stored order, with control over the cycle on and off time. At the end of the program the system re-cycles to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although removing the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following night's performance. The module obviously provides unlimited effects and is a must for all serious lighting shows.



MULTI - 4

£54.90

The Multi-4 is a comprehensive sound and chase module, offering a wide range of forward, reverse or random effects, with additional sound modulation facilities. Modes of operation are set on control pots which act as electronic switches. The unit has a wide speed range and will accept virtually any sound level input. The Multi-4 also provides monitor circuits for LED driving. The triac outputs may be used to drive up to 4000W of lighting or up to 70 metres of rope lights.

Attractive blue panels with white letters, complete with LED monitors, knobs and mains illuminated switch.

£9.70

L & B ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon Surrey CR0 3EB. Tel. 01-589 4138

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months. All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.O./Registered cash/Barclaycard or Access number. C.O.D. service £1 extra. For further information send a s.a.e. stating which model. PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

3-WAY ACTIVE CROSSOVER LBAC01

£17.90

Bass/mid/treble active crossover with stage booster. Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01. (1 or 2).

3 CHANNEL SOUND/LIGHT LB31000SL

£22.70

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

MICRO TIMES

19 Mill St., Bideford, North Devon EX39 2JR, England
Telephone Bideford (023 72) 79798

INTRODUCING CMOS AND TTL

see below for micro prices



CMOS	THYRISTORS	VOLTAGE REGULATORS	74LS	TTL
4001 12p	C106D 28p	7805 5V 53p	74LS00 14p	74LS01 14p
4002 12p		7805 5V 58p	74LS02 13p	74LS02 13p
4006 98p		7812 12V 58p	74LS03 13p	74LS03 13p
4007 60p		7812 12V 58p	74LS04 14p	74LS04 14p
4008 60p		78L05 5V 29p	74LS08 13p	74LS08 13p
4010 38p		78L12 12V 29p	74LS14 14p	74LS14 14p
4011 12p		500mA 500mA	74LS16 14p	74LS16 14p
4012 18p		79M12 12V 62p	74LS17 14p	74LS17 14p
4013 33p		79M05 5V 62p	74LS18 14p	74LS18 14p
4014 60p		723 32p	74LS20 14p	74LS20 14p
4015 62p			74LS21 14p	74LS21 14p
4016 28p			74LS22 14p	74LS22 14p
4017 53p			74LS23 14p	74LS23 14p
4018 58p			74LS24 14p	74LS24 14p
4019 38p			74LS25 14p	74LS25 14p
4020 85p			74LS26 14p	74LS26 14p
4023 38p			74LS27 14p	74LS27 14p
4024 38p			74LS28 14p	74LS28 14p
4025 14p			74LS29 14p	74LS29 14p
4026 1.28			74LS30 14p	74LS30 14p
4027 35p			74LS31 14p	74LS31 14p
4028 52p			74LS32 14p	74LS32 14p
4029 70p			74LS33 14p	74LS33 14p
4030 48p			74LS34 14p	74LS34 14p
4031 1.95			74LS35 14p	74LS35 14p
4040 66p			74LS36 14p	74LS36 14p
4042 66p			74LS37 14p	74LS37 14p
4044 60p			74LS38 14p	74LS38 14p
4046 74p			74LS39 14p	74LS39 14p
4047 78p			74LS40 14p	74LS40 14p
4048 44p			74LS41 14p	74LS41 14p
4049 27p			74LS42 14p	74LS42 14p
4050 66p			74LS43 14p	74LS43 14p
4051 80p			74LS44 14p	74LS44 14p
4052 60p			74LS45 14p	74LS45 14p
4056 1.50			74LS46 14p	74LS46 14p
4060 86p			74LS47 14p	74LS47 14p
4063 1.18			74LS48 14p	74LS48 14p
4066 38p			74LS49 14p	74LS49 14p
4068 18p			74LS50 14p	74LS50 14p
4069 15p			74LS51 14p	74LS51 14p
4070 22p			74LS52 14p	74LS52 14p
4071 18p			74LS53 14p	74LS53 14p
4075 20p			74LS54 14p	74LS54 14p
4077 22p			74LS55 14p	74LS55 14p
4078 20p			74LS56 14p	74LS56 14p
4081 18p			74LS57 14p	74LS57 14p
4093 42p			74LS58 14p	74LS58 14p
4503 65p			74LS59 14p	74LS59 14p
4510 65p			74LS60 14p	74LS60 14p
4511 51p			74LS61 14p	74LS61 14p
4518 70p			74LS62 14p	74LS62 14p
4520 70p			74LS63 14p	74LS63 14p
4560 2.20			74LS64 14p	74LS64 14p
4572 30p			74LS65 14p	74LS65 14p

50p OFF VOUCHER

When £5 plus order of CMOS, TTL or LINEAR is placed. Return Voucher with order. VWS

LOW PROFILE DIL SOCKETS	ENCODER/TRANSMITTER	RECEIVER/DECODER	SOUND EFFECTS GENERATOR	LINEAR ICs
40 pin 30p	LM1871 £1.90	LM1872 £1.90	SN76477N £1.75 ea.	NE555 17p
28 pin 26p	LM1871 £1.90	LM1872 £1.90	LM1871 £1.90	NE556 48p
24 pin 24p	LM1871 £1.90	LM1872 £1.90	LM1872 £1.90	RC4136 85p
22 pin 22p	LM1871 £1.90	LM1872 £1.90	LM1873 £1.90	LM301AN 28p
18 pin 18p	LM1871 £1.90	LM1872 £1.90	LM1874 £1.90	LM311P 45p
16 pin 16p	LM1871 £1.90	LM1872 £1.90	LM1875 £1.90	LM318 1.45
14 pin 12p	LM1871 £1.90	LM1872 £1.90	LM1876 £1.90	LM324N 42p
8 pin 9p	LM1871 £1.90	LM1872 £1.90	LM1877 £1.90	LM339N 40p
	LM1871 £1.90	LM1872 £1.90	LM1878 £1.90	LM348N 78p
	LM1871 £1.90	LM1872 £1.90	LM1879 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1880 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1881 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1882 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1883 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1884 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1885 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1886 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1887 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1888 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1889 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1890 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1891 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1892 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1893 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1894 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1895 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1896 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1897 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1898 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1899 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1900 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1901 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1902 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1903 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1904 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1905 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1906 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1907 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1908 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1909 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1910 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1911 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1912 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1913 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1914 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1915 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1916 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1917 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1918 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1919 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1920 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1921 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1922 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1923 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1924 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1925 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1926 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1927 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1928 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1929 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1930 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1931 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1932 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1933 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1934 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1935 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1936 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1937 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1938 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1939 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1940 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1941 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1942 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1943 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1944 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1945 £1.90	
	LM1871 £1.90	LM1872 £1.90	LM1946 £1	

PCB FOIL PATTERNS

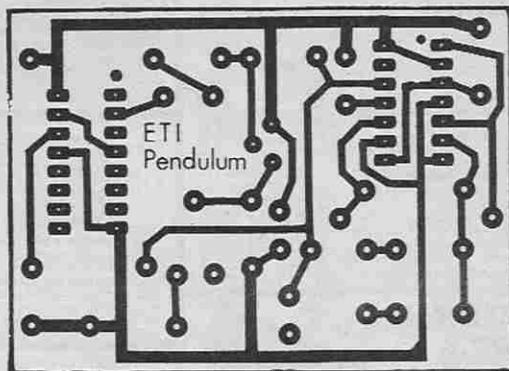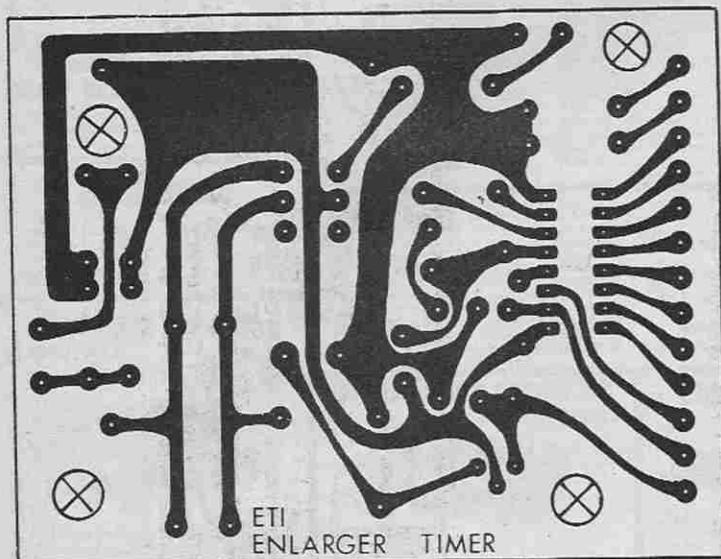

Above: the PCB for the Micropower Pendulum.

Left: the Enlarger Timer foil pattern.

SUBSCRIPTIONS

This year we present a new twelve-part, non-fiction series — ETI 1981 available from your newsagent every month.


Forget to buy it this month, or is your newsagent sold out?

Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £11.25 we'll send you twelve issues of ETI.


To claim your years' supply of ETI, send your PO or cheque direct to :

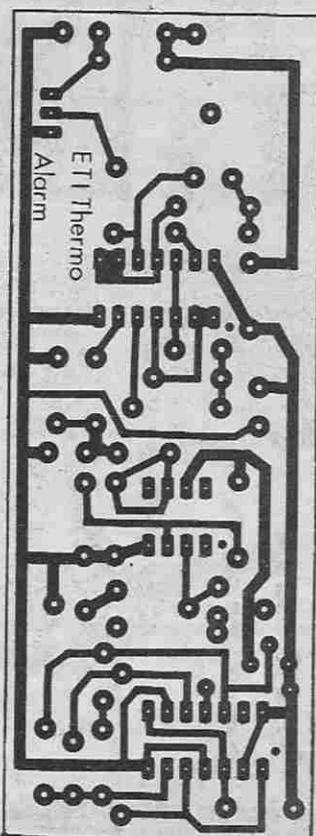ETI Subscriptions Department,
513 London Road,
Thornton Heath,
Surrey CR4 6AR.
Tel: 01-684 3157.






Above: the Micropower Thermal Alarm PCB.

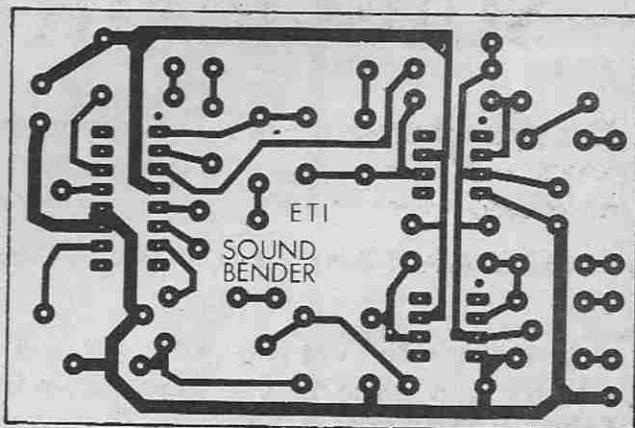

Above: foil pattern for the Sound Bender.

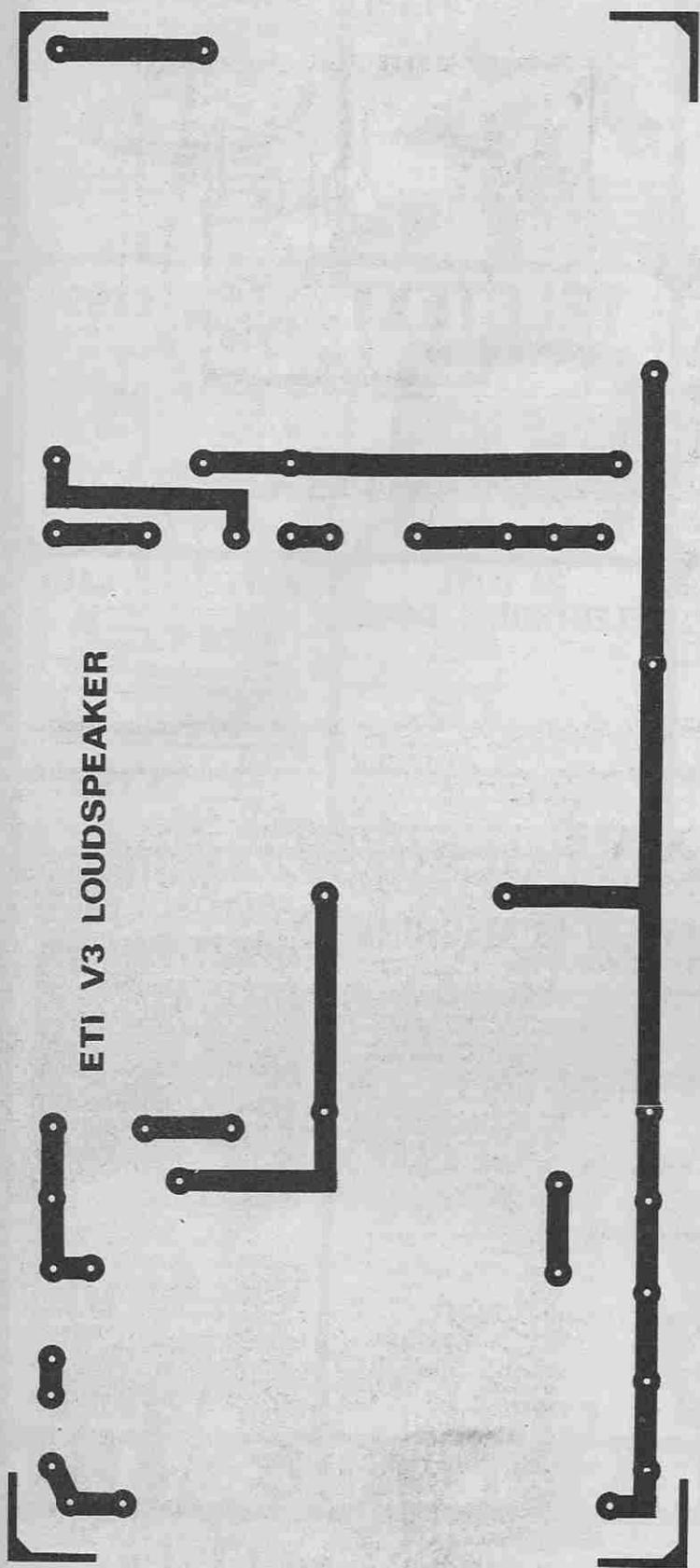Left: The crossover PCB for the V3 loudspeaker.



ET1 V3 LOUDSPEAKER

ETI

The loudspeaker board is copyright and may not be reproduced by commercial manufacturers. Due to lack of space this month, the foil patterns for the FM Mains Remote Control System will be published in the next issue.


ELECTRONIC GAMES

COLOUR CARTRIDGE T.V. GAME



SEMI-PROGRAMMABLE T.V. GAME
+ 4 Cartridges + Mains Adaptor
Normal Price £73
NOW REDUCED TO: £39.50
inc. VAT

DATABASE T.V. GAME

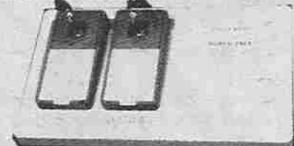


FULLY PROGRAMMABLE CARTRIDGE T.V. GAME
14 Cartridges available
Normal Price £87.86
NOW REDUCED TO: £59
inc. VAT



ATARI T.V. GAME

The most popular T.V. Game on the market with a range of over 40 cartridges including SPACE INVADERS with over 112 games on one cartridge.
£95.45
inc. VAT

SPACE INVADERS

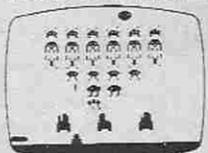

Hand-held Invaders Games available £19.95
+ Invaders Cartridges available to fit ATARI RADOFIN ACETRONIC PHILIPS G7000
+ Cartridges also available for MATTEL TELENG/ROWTRON/DATABASE/INTERTON

CHESS COMPUTERS



MANY UNITS ARE COVERED BY THE EXCLUSIVE SILICA SHOP 2 YEAR GUARANTEE

We carry a range of over 15 different Chess computers:
Electronic Chess £29.95
Chess Traveller £39.95
Chess Challenger 7 £79.00
Sensory 8 £119.00
Sensory Voice £259.00
SPECIAL OFFERS:
VOICE CHESS CHALLENGER
Normal Price £245 NOW £135.00
SARGON 2.5/BORIS 2.5
Normal Price £273.70 NOW £199.95
All prices include V.A.T.

TELETEXT




ADD-ON ADAPTOR £199

THE RADOFIN TELETEXT ADD-ON ADAPTOR

Plug the adaptor into the aerial socket of your colour T.V. and receive the CEEFAX and ORACLE television information services.
THIS NEW MODEL INCORPORATES:
• Double height character facility
• True PAL Colour
• Meets latest BBC & IBA broadcast specifications
• Push button channel change
• Unnecessary to remove the unit to watch normal TV programmes
• Gold plated circuit board for reliability
• New SUPERIMPOSE News Flash facility

SPEAK & SPELL

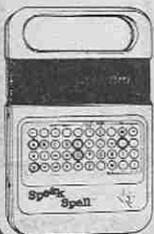

Normal Price £49.95
NOW REDUCED TO: £39.50
inc. VAT

Teach your child to spell properly with this unique learning aid. Fully automatic features and scoring. Additional word modules available to extend the range of words.

ADDING MACHINE OLYMPIA HHP 1010



Normal Price £57.21
NOW REDUCED TO: £34
inc. VAT

Uses ordinary paper!
No need to buy expensive thermal paper!
Fast adding PRINTER. CALCULATOR. 2 lines per second. 10 digit capacity.
Uses normal adding machine rolls. Battery or mains operated.
Size 9 1/4" x 4 1/2" x 2 1/2"
(Mains adaptor extra)


24 TUNE ELECTRONIC DOOR BELL



Normal Price £19.70
NOW REDUCED TO: £12.70
inc. VAT

Plays 24 different tunes with separate speed control and volume control. Select the most appropriate tune for your visitor with appropriate tunes for different times of the year!

MATTEL T.V. GAME

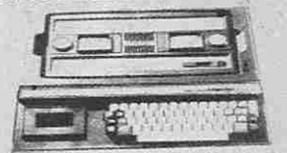

The most advanced T.V. game in the world 20 cartridges available. Add on KEYBOARD coming soon to convert the £199.95 inc. VAT MATTEL to a home computer with 16K RAM fully expandable and programmable in Microsoft Basic. Other accessories will be available later in the year.

HAND HELD GAMES EARTH INVADERS



These invaders are a breed of creature hitherto unknown to man. They cannot be killed by traditional methods — they must be buried. The battle is conducted in a maze where squads of aliens chase home troops. The only way of eliminating them is by digging holes and burying them.
£23.95
inc. VAT


THE OLYMPIA — POST OFFICE APPROVED TELEPHONE ANSWERING MACHINE WITH REMOTE CALL-IN BLEEPER

This telephone answering machine is manufactured by Olympia Business Machines, one of the largest Office Equipment manufacturers in the U.K. It is fully POST OFFICE APPROVED and will answer and record messages for 24 hours a day. With your remote call-in bleeper you can receive these messages by telephone wherever you are in the world. The remote call-in bleeper activates the Answer/Record Unit, which will at your command repeat messages, keep or erase them, and is activated from anywhere in the world, or on your return to your home or office. The machine can also be used for message referral, if you have an urgent appointment, but are expecting an important call, simply record the phone number and location where you can be reached. With optional extra beepers (£13 each) this facility can be extended to colleagues and members of the family. Using a C90 standard cassette you can record as many as 45 messages. The announcement can be up to 16 seconds long and the incoming message up to 30 seconds long.



The machine is easy to install and comes with full instructions. It is easily wired to your junction box with the spade connectors provided or alternatively a jack plug can be provided to plug into a jack socket. Most important, of course, is the fact that it is fully POST OFFICE APPROVED. The price of £135 (inc. VAT) includes the machine, an extra-light remote call-in bleeper, the microphone message tape, A.C. mains adaptor. The unit is 9 1/4" x 6" x 2 1/2" and is fully guaranteed for 12 months. The telephone can be placed directly on the unit — no additional desk space is required.
£135
inc. VAT

PRESTEL VIEWDATA

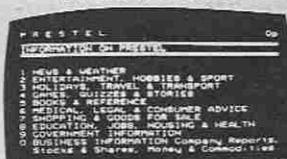


The ACE TELCOM VDX1000 Prestel Viewdata adaptor: simply plugs into the aerial socket of your television and enables you to receive the Prestel Viewdata service in colour or black & white.

Features:
— Simplified controls for quick, easy operation.
— Special graphics feature for high resolution.
— State-of-the-art microprocessor controller.
— Standard remote telephone keypad with Prestel keys 'A' - 'H'.
— Auto dialler incorporated for easy Prestel acquisition.
— True PAL colour encoder using reliable IC chroma filter and data line incorporated for minimum picture interference maximum fidelity.
— Includes convenient TV - Prestel switchbox.
— Easily connected to standard home or office telephone lines.
— Fully Post Office approved.

SPECIAL PRICE £228.85
inc. VAT


HAND HELD GAMES GALAXY 1000

GALAXY 1000

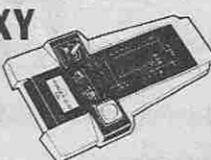

The 2nd generation Galaxy Invader. The invaders have re-grouped and have a seemingly endless supply of spacecraft whilst the player's arsenal is limited to just 250 missiles to be launched from 3 missile stations. You have to prevent the invaders landing or from destroying your home defences.
£19.95
inc. VAT


FOR FREE BROCHURES - TEL: 01-301 1111

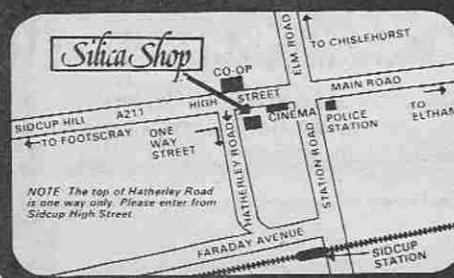

For free illustrated brochure and reviews on our range of electronic games, please telephone 01 301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESSCARD/INCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48hr. delivery service available.
— CALLERS WELCOME. Demonstrations daily at our Sidcup shop open from 9am-6pm Monday-Saturday Early Closing Thursday 1pm - Late Opening Friday 8pm - 2 Year GUARANTEE - All goods are covered by a full year's guarantee. Many are further covered by our exclusive Silica Shop 2 year Guarantee.
— MONEY BACK UNDER TAKING. If you are unsatisfied with your purchase and return it within 7 days, we will give you a full refund.
— AFTER SALES SERVICE. Available on all machines out of guarantee.
— COMPETITIVE PRICES. We are never knowingly undersold.
— HELPFUL ADVICE. Available on the suitability of each machine.
— CREDIT FACILITIES. Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
— PART EXCHANGE SCHEME. Available on second hand machines.
— CREDIT CARDS WELCOME. Access: Barclaycard, Diners Club, American Express.

SILICA SHOP LIMITED ET1081

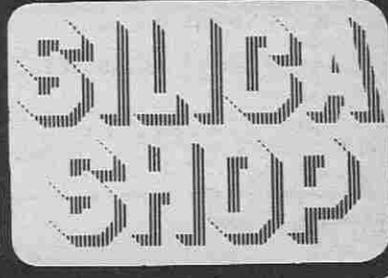1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX
Telephone: 01-301 1111 or 01-309 1111



IT'S A DOGS LIFE!

Mighty mongrel strikes again!



Stop your powerful pooch carving up your carefully collected ETIs with his canine choppers and live in hardback harmony with a profusion of precious project books by armour-plating your archives.

Invest in an ETI binder. You know it makes sense. You can have any colour you like as long as it's black.

Price U.K. £3.95 including postage, packing and V.A.T., overseas orders add 30p. Why not place your order now and send the completed coupon with remittance to:-

EASIBIND LTD., 4 UXBRIDGE STREET, LONDON W8 7SZ. Tel: 01-727 0686

Please allow 3/4 weeks for fulfillment of order.

it's easy with EASIBIND

Easibind Ltd, 4 Uxbridge St, London, W8 7SZ.

Nat. Giro No. 5157552.

Order Form

ELECTRONICS TODAY INTERNATIONAL

I enclose p.o./cheque value

for binders

Years required

BLOCK LETTERS PLEASE

Name

Address

Date

Registration No. 307469



ETI PROJECT KITS FROM MAGENTA ELECTRONICS LTD

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.T.I. Projects. We supply carefully selected sets of parts to enable you to construct E.T.I. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.T.I. which includes the project - you will need to order the instruction reprint as an extra 45p each.

Reprints available separately 45p each + p&p 40p

MAINS AUDIO LINK, Sept. '81	£49.98
LAB PSU, Sept. '81. Less case	£37.98
WATCHDOG HOME SECURITY SYSTEM, Aug. '81	£43.33
Rechargeable battery	£20.98 extra
HEARTBEAT MONITOR, Aug. '81	£26.26
HANDCLAP SYNTHESIZER, Aug. '81	£29.98
FLASH SEQUENCER, Aug. '81. Less flash sockets	£35.65
SMART BATTERY CHARGER, July '81	£31.98
WAH PHASE, June '81. Less pedal	£13.44
LED JEWELLERY, June '81. Cross	£2.47
Spiral	£7.20
Star	£9.41
ALIEN ATTACK, Jan. '81	£19.76
ANTENNA EXTENDER, June '81	£21.68
MINI DRILL SPEED CONTROLLER, June '81	£25.13
DIGITAL CLOCK, May '81 (round leds)	£43.97
CARAVAN LIGHTS CHECKER, April '81, less glue	£10.16
GUITAR NOTE EXPANDER - ETI, April '81	£16.47
DRUM MACHINE, April '81	£65.94
MUSICAL BOX, April '81	£12.54
ENGINEERS STETHOSCOPE, Mar '81	£19.19
SOUND PRESSURE LEVEL METER, Feb. '81	£45.75
PULSE GENERATOR, Feb. '81 less case	£35.33
Case extra	£27.47
INFRA RED ALARM, Feb. '81	£54.98
UNIVERSAL TIMER, Jan. '81	£31.77
MULTI-OPTION SIREN, Jan. '81	£26.91
LED TACHO, Jan '81. Less case	£34.77
4 INPUT MIXER, Dec. '80	£19.77
BENCH AMPLIFIER, Dec. '80	£23.95
MUSICAL DOORBELL, Dec. '80	£11.61

AUDIO TEST OSCILLATOR, Nov. '80	£18.30
RIAA PRE-AMP (stereo), Nov. '80	£6.83
2W POWER AMP, Nov. '80	£6.09
METRONOME, Nov. '80	£5.98
LIGHT SWITCH, Nov. '80	£8.54
TOUCH BUZZER, Nov. '80	£6.11
SUSTAIN/FUZZ BOX, Oct. '80	£24.99
CASSETTE INTERFACE, Oct. '80. Less case	£11.57
ULTRASONIC BURGLAR ALARM, Aug. '80	£26.82
CAPACITANCE METER, Aug. '80	£20.26
CMOS LOGIC TESTER, Aug. '80	£10.97
SIGNAL TRACER, Mar. '80	£11.98
TUNING FORK, Feb. '80	£14.82
ACCENTUATED BEAT METRONOME, Jun. '79	£17.90
CLICK ELIMINATOR, April '79 less case	£46.57
Case extra	£14.98
GUITAR EFFECTS UNIT, April '79	£14.78
COMPLEX SOUND GENERATOR, Oct. '78. Less case	£21.97
TELEPHONE BELL EXTENDER, Oct. '78. Less speaker	£16.47
Horn speaker extra	£6.83

The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

The INSTRUCTOR is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the INSTRUCTOR and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk. 2. Circuits are built on a plug in Eurobreadboard. Kit is available with or without the breadboard. INSTRUCTOR COMPONENT PACK: Including Eurobreadboard £27.85; or less Eurobreadboard £21.65.

INSTRUCTOR COURSE NOTES AND OPERATING INSTRUCTIONS - EXTRA £2.96

MAGENTA ELECTRONICS LTD.

ET5, 135 HUNTER STREET, BURTON-ON-TRENT, STAFFS. DE14 2ST
0283-65435. 9-5 MON.-FRI. MAIL ORDER ONLY

ALL PRICES INCLUDE VAT
ADD 40p P&P TO ALL ORDERS

Irish Republic & B.F.P.O. Europe deduct 10% from prices shown. Payment must be in sterling.



Accepted Barclaycard (Visa) orders accepted by phone or post.

1981 ELECTRONICS CATALOGUE

KITS
ICs
TRANSISTORS
CAPACITORS

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery. Send 70p in stamps or add 70p to your order.


TOOLS
RESISTORS
HARDWARE
CASES

404 EDGWARE RD. LONDON, W2 1ED TEL: 01-402 6822

TANGERINE • TANGERINE • TANGERINE • TANGERINE • TANGERINE

MICROTAN 65

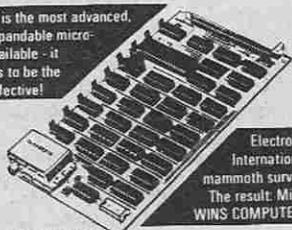Microtan 65 is the most advanced, powerful, expandable micro-computer available - it also happens to be the most cost effective!



Electronic Today International held a mammoth survey of kits. The result: Microtan 65 WINS COMPUTER CLASS!

MICROTAN 65 CONTENTS

High quality, plated thru hole printed circuit board, solder resist and silk screened component identification. 6502 microprocessor. 1K monitor TANBUG. Now with 'V' Bug. 1K RAM for user programme, stack and display memory. VDU alphanumeric display of 16 rows by 32 characters. MICROTAN 65 system file hinder. 136 page, bound, users hardware/software manual with constructional details and sample programmes. Logic and discrete components to fully expand MICROTAN 65.

The MICROTAN 65 kit has won widespread acclaim for its superb presentation. We pay attention to detail!

KIT FORM £69.00 + £10.35 V.A.T., total £79.35

MICROTAN 65 ASSEMBLED AND TESTED

Specification as above, but assembled and fully bench tested by ourselves. **£79.00** + £11.85 V.A.T., total £90.85

MICROTAN 65 OPTIONS

LOWER CASE PACK

Two integrated circuits which connect into locations on MICROTAN allowing 128 displayable characters. **£9.48** + £1.42, total £10.90

GRAPHICS PACK

Five integrated circuits which connect into locations on MICROTAN allowing the display of chunky graphics (64 x 64 pixels). What are chunky graphics? Well, imagine a piece of graph paper with 64 squares vertically and 64 squares horizontally, a total of 4096. Each square can be made black on white. **£6.52** + V.A.T. 98p, total £7.50

20 WAY KEYPAD

Inexpensive means of getting up and running. Uses 'Schoeller' key-switches, and connects to MICROTAN through a 16 pin D.I.L. plug on ribbon cable. Black anodised enclosure, with TANGERINE legends, finishes off what must be the best value for money keypad available. Available assembled and tested. **£10.00** + V.A.T. £1.50, total £11.50

*Space Invaders game (for use with keypad only) **£15.22** + V.A.T. £2.28 total £17.50

POWER SUPPLIES

MPS 1: Input 120 or 240V AC. Output 5 Volts at 3 Amps Regulated. MPS 1 will power both MICROTAN and TANEX fully expanded. Built on the same size printed circuit board as MICROTAN etc. Available as a fully built and tested unit. **£23.00** + V.A.T. £3.45, total £26.45

X MPS2 +5V 6A. +12V. -5 and -12V switch mode system PSU **£69.13** + V.A.T.

MINI-SYSTEM RACK

We have produced a mini-system rack which accepts MICROTAN 65, TANEX and our mini-mother board. It has an integral power supply, just plug it into the mains and away you go! Finished in TANGERINE/BLACK, it gives your system the professional finish. Front panel access for I/O cables. **AVAILABLE AS AN ASSEMBLED UNIT.** **£43.00** + V.A.T. £6.45, total £49.45

FULL SYSTEM RACK

For the man that has everything! 19 inch wide system rack which accepts: MICROTAN 65, TANEX, TANRAM, SEVEN FURTHER EXPANSION BOARDS, TANDOS and THE SYSTEM POWER SUPPLY. Available in many formats, e.g. Individual front panels, full width hinged front panel, back panel with or without connectors. **£49.00** + V.A.T. £7.35, total £56.35

NEW PRODUCTS

NOW AVAILABLE

HIGH DEFINITION COLOUR GRAPHICS CONTROLLER CARD **£90.85** incl. V.A.T. **£120.00** - V.A.T.

SERIAL I/O CARD (From) **£58.00** - V.A.T.
PARALLEL I/O CARD (From) **£47.50** - V.A.T.
ROM CARD (BUILT) LESS ROM **£47.50** - V.A.T.
AIM-KIM INTERFACE CARD **£59.00** - V.A.T.
SERIAL I/O KIT **£17.25** incl. V.A.T.

SYSTEM MOTHER BOARD WITH 4 SOCKETS FOR SYSTEM RACK **£39** - V.A.T.
SYSTEM MOTHER BOARD WITH 12 SOCKETS FOR SYSTEM RACK **£55** - V.A.T.
32K RAM CARD **£115** - V.A.T.
32K ROM CARD (LESS CHIPS) **£54.65** incl. V.A.T.

MICRON COMPUTER

FULLY BUILT, TESTED, and housed in ATTRACTIVE CASES.




£395 inc. V.A.T. P&P

6502 based microcomputer. VDU alpha numeric display. Powerful monitor TANBUG. 8K RAM. 32 parallel I/O lines. 2 TTL serial I/O lines. Four 16 Bit counter timers. Cassette interface. Data bus buffering. Memory mapping control. 71 key ASCII keyboard, including numeric keypad. Includes power supply. Also includes the first '10K MICROSOFT BASIC' available in the U.K. All the usual BASIC commands.

TANRAM

Available now tanram - 40K Bytes on one board. Single board of bulk memory offering 7K Static RAM (2114), and 32K Dynamic RAM (4116). Onboard refresh is totally transparent to CPU operation and is unaffected by normal DMA's. TANRAM fully expands the available address space of the 6502 microprocessor. MICROTAN, TANEX and TANRAM together provide 16K RAM, 48K RAM, and 1K I/O - that's a lot of memory and a lot of I/O! Built and tested. **TANRAM ASSEMBLED.**

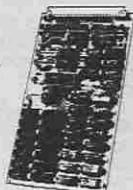

40K RAM CARD WITH 16K DYNAMIC RAM £76 - V.A.T.

CONTENTS: High quality plated thru hole printed circuit board, solder resist and silk screened component identification. Full complement of I.C. sockets for maximum expansion 64 way D.I.N. edge connector. 1K RAM (2114). Data bus buffering. TANRAM users manual.

EXTRA RAM: 1K STATIC (2114) **£2.95** each. 16K DYNAMIC (4116) **£1.50** each.

MEMORIES EXPAND YOUR SYSTEM WITH OUR TANGERINE APPROVED CHIPS.

Discounts 10% for 4, 15% for 8, 20% for 16.
2102 1K x 1 Static RAM **80p** IM 8402 UART **£4.50**
2708 **£3.50** 2114 1K x 4 Static RAM **£2.95**
2716 **£6.50** 8080A **£5.00**
MK 4116 16K x 1 Dynamic RAM **£1.50** 4118 1K x 8 Static RAM **£7.50**
All plus V.A.T.

MONITORS (PROFESSIONAL) RECONDITIONED AND NEW - FROM £35.00 to £129.95

CENTRONICS Ideal for Tangerine PRINTERS

CENTRONICS P.I. **£150** + V.A.T.
SHEIKHSA **£199** + V.A.T.
Model 730 **£350** + V.A.T.
Model 737 **£395** + V.A.T.



NEW MICROTANTEL POST OFFICE APPROVED PRESTEL - VIEWDATA

• FULL COLOUR GRAPHICS • MICROTAN OWNERS CAN COMMUNICATE WITH EACH OTHER • CAN STORE PRESTEL • CAN BE USED AS AN EDITING TERMINAL • CAN BE INTERFACED WITH PET, APPLE etc.

£170 + V.A.T.

Just connect to the serial socket of any colour or black and white domestic T.V. receiver and to your Post Office installed jack socket and you are into the exciting world of PRESTEL. Via simple push button use, you are able to view 170,000 pages of up to the minute information on many services, order goods from companies - all this without leaving your armchair!

TANEX £43.00

Minimum Config Kit

+ V.A.T. £6.45, total £49.45

CONTENTS


High quality plated thru hole printed circuit board, solder resist and silk screened component identification. I.C. sockets for maximum expansion. 64 Way D.I.N. edge connector. 1K RAM, cassette interface, 16 parallel I/O lines, a T.T.L. serial I/O port, two 16 bit counter timers, data bus buffering, memory mapping, logic and discrete components for maximum expansion. TANEX users manual.

TANEX (Minimum configuration) Assembled £53.00 + V.A.T. £7.95, total £60.95



TANEX EXPANSION

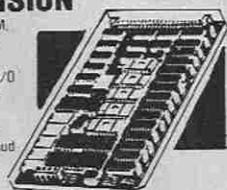Expanded TANEX offers: 7K RAM, locations for 4K EPROM (2716), locations for 10K extended MICROSOFT BASIC, 32 parallel I/O lines, two TTL serial I/O ports, a third serial I/O port with RS232/20mA loop, full modem control and 16 programmable baud rates, four 16 bit counter timers, cassette interface, data bus buffering, and memory mapping.



EXPANDED TANEX KIT (Excludes ROM, XBUG and BASIC) £89.70 + V.A.T. £13.46, total £103.16

EXPANDED TANEX ASSEMBLED £99.70 + V.A.T. £14.96, total £114.66

OPTIONS TO FULLY EXPANDED TANEX IN SIMPLE INEXPENSIVE STAGES.

10K Extended MICROSOFT BASIC in EPROM (with manual) **£48.00** + V.A.T. £7.35, total £55.35

Extra RAM: 1K (2 x 2114) **£5.20** + V.A.T. 78p, total £5.98

SERIAL I/O KIT **£10.26** + V.A.T. £1.60, total £11.86

6522 VIA **£8.00** + V.A.T. £1.20, total £9.20

XBUG **£17.35** + V.A.T. £2.60, total £19.95

AS YOU CAN SEE THE PRICES OF OUR EXPANSION COMPONENTS ARE VERY, VERY COMPETITIVE!

TANGERINE DISC SYSTEM

Z8 CONTROLLER CARD **£150.00** - V.A.T.
DOUBLE SIDED DOUBLE DENSITY DRIVE **£215.00** - V.A.T.
CP/M DISK OPERATING SYSTEM **£80** + V.A.T.



71 KEY ASCII KEYBOARD £56.34 + V.A.T.

NO EXTRAS NEEDED. Uses gold crosspoint keys. Includes numeric keypad and ribbon cable. Available as fully assembled and tested. **SUPER METAL CABINET IN TANGERINE/BLACK £20.00** + V.A.T. £3.00, total £23.00



PROFESSIONAL ASCII KEYBOARDS Ideal for Tangerine

£29.95 - V.A.T.

- 52 key 7 bit ASCII coded
- Positive strobe +5V-12V
- ASCII characters
- Parallel output with strobe
- Power light on control
- Chip by General Instrument (G.I.) TTL output



- Superbly made
- Size 13 x 5.5 x 1.5 ins.
- Black keys with white ledgers
- Escape shift return & reset keys
- Control repeat & bell keys
- Complete with DATA

ADD-ON KEYPAD

A compact 12 button keypad suitable for use with above keyboard to extend its functions plus four extra keys. Supplied brand new with data. A 4x4 non-encoded single mode keyboard.

LIST PRICE **£22.00** OUR PRICE **£7.95** - V.A.T.

PLUS MANY NEW EXCITING PRODUCTS IN DEVELOPMENT AUTOMATICALLY AVAILABLE FROM US WHEN RELEASED BY OUR PRINCIPALS TANGERINE LTD

All products are available from stock. FULLY GUARANTEED - BUY WITH CONFIDENCE. BRITISH DESIGN & MANUFACTURE AND ON DEMONSTRATION IN OUR COMPUTER DEPT.

SEND FOR FREE BROCHURE

TANGERINE • TANGERINE
Stockist Enquiries on headed notepaper to: **COMPUTER KIT LTD.** (Principal Distributors in U.K.)
11/12 Paddington Green, London, W2, Tele: 01-723 5095 Telex 262284 Ref. 1400 TRANSONICS
All orders pre-paid and official advertised here and elsewhere in this magazine by TANGERINE to be forwarded DIRECTLY to **COMPUTER DEPT., 11/12 PADDINGTON GREEN, LONDON W2**

CIRCUIT DIAGRAMS/OVERLAYS/ FLOWCHARTS!


Do you require professionally drawn Circuit diagrams, Overlays, Flowcharts etc. drawn from your own designs? MM Design & Print offer a quick, accurate and cheap Technical Illustration and lettering service to readers of ETI. We illustrate anything from a single chip amplifier to a colour television circuit design, with finished artwork supplied to your specification. For further details please ring Paul Edwards, on 01-437 1002/7 extension 29, or write to the address below.




Part of the Modmag Group

145 Charing Cross Road,
WC2H 0EE

D.I.Y. EFFECTS PEDAL CASES

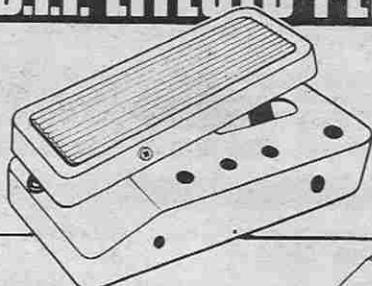

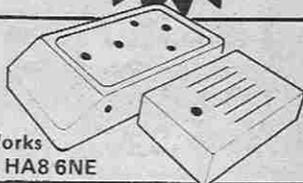AS
FEATURED IN
JUNE ISSUE OF
ELECTRONICS
TODAY
WAA-PHASE CASE
ONLY £7.48
+ £1.25 postage
and packing!



VARIOUS CASES AVAILABLE -
SEND FOR LIST AND PRICES

SOLA SOUND LTD. Unit 6, Leto Works
off Mead Road, Edgware, Middlesex HA8 6NE

PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film: E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
 Special stock pack: 60 values. 10 off each **£5.50**

DIODES: IN4148 3p each. Min order quantity - 15 items.
£1.60 per hundred


DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
 4 Way **86p** each 5 Way **£1.00** each. 8 Way **£1.20** each.

DIL SOCKETS: High quality, low profile sockets.
 8 pin - **10p**. 14 pin - **11p**. 16 pin - **12p**. 18 pin - **19p**. 20 pin - **21p**.
 22 pin - **23p**. 24 pin - **25p**. 28 pin - **27p**. 40 pin - **42p**.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
 MIN. ORDER - U.K. £1.00. OVERSEAS £5. CASH WITH ORDER PLEASE

The Finest Amplifiers deserve the Finest Kits

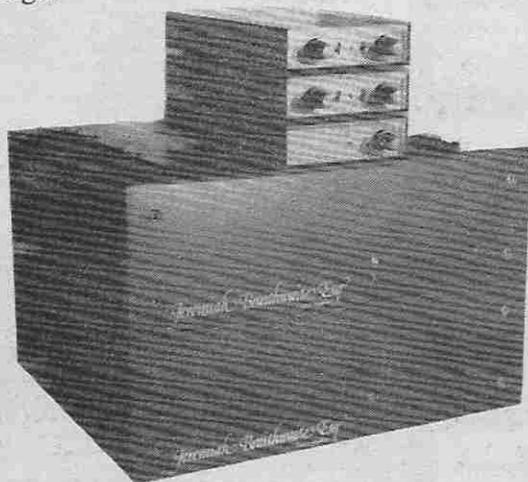The Electronics Today System A, designed by Stan Curtis comprises two monophonic Class A Power Amplifiers and a modular pre-amplifier of such superlative performance that they stand comparison with commercial products in any price range.



Braithwaite KITS

- ★ are approved by the designer
- ★ use the finest quality components
- ★ offer a unique "get you out of trouble" service and full technical support.
- ★ offer a unique post-assembly testing service

Complete Kits
 (Part Kits available)
 Pre-Amplifier £76.90
 Mono Power-Amplifier £221.95
 including VAT (carriage extra).

Details and price list from:

Braithwaite KITS

215, High Street, Offord Cluny,
 Huntingdon, Cambs. (0480) 811659

Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD.
KINGSGATE HOUSE
KINGSGATE PLACE
LONDON NW6 4TA.
MAIL ORDER 01-824 8582 24HR SERVICE
INDUSTRIAL SALES 01-328 1005

ALSO RETAIL SHOPS AT
325 EDGWARE ROAD, LONDON W2 01-723 4242
85 WEST REGENT STREET, GLASGOW, 041-332 4133

WE TAKE ACCESS - AMERICAN EXPRESS - BARCLAYCARD CARD - DINERS

PLEASE ADD POSTAGE/PACKING 60p UNLESS STATED
ALSO 15% VAT ON TOTAL - ALL ITEMS ON THIS
ADVERTISEMENT SPECIALLY SELECTED FOR EX-STOCK
DELIVERY.

RECHARGEABLE NICKEL CADMIUM BATTERIES & CHARGERS

TYPE	VOLTS	AV. CAP.	PRICE
S101 (HP7)	1.25	0.5AH	£1.13
Sub C (HP11)	1.25	1.2AH	£1.91
Sub D (HP2)	1.25	1.2AH	£2.14
Penlight 4 Charger for 1-4 HP7			£5.50
Combibox FW61 Charger for HP7, HP11, HP2			£14.40

CAPACITORS

SIEMENS LAYER 837880 2mm		SIEMENS LAYER 837861 2mm		SIEMENS ELECTROLYTIC AXIAL	
001	10	015	50.00	47/100	15
002	10	022	50.00	10/100	15
003	10	033	50.00	10/100	15
015/250	0.15	0.22	50.00	47/100	15
0.22/250	0.22	0.33	50.00	100/25	20
0.33/250	0.33	0.47	50.00	100/25	20
0.47/250	0.47	0.68	50.00	100/25	20
0.68/250	0.68	1.0	50.00	100/25	20
1.0/250	1.0	1.5	50.00	100/25	20
1.5/250	1.5	2.2	50.00	100/25	20
2.2/250	2.2	3.3	50.00	100/25	20
3.3/250	3.3	4.7	50.00	100/25	20
4.7/250	4.7	6.8	50.00	100/25	20
6.8/250	6.8	10	50.00	100/25	20
10/250	10	15	50.00	100/25	20
15/250	15	22	50.00	100/25	20
22/250	22	33	50.00	100/25	20
33/250	33	47	50.00	100/25	20
47/250	47	68	50.00	100/25	20
68/250	68	100	50.00	100/25	20
100/250	100	150	50.00	100/25	20
150/250	150	220	50.00	100/25	20
220/250	220	330	50.00	100/25	20
330/250	330	470	50.00	100/25	20
470/250	470	680	50.00	100/25	20
680/250	680	1000	50.00	100/25	20
1000/250	1000	1500	50.00	100/25	20
1500/250	1500	2200	50.00	100/25	20
2200/250	2200	3300	50.00	100/25	20
3300/250	3300	4700	50.00	100/25	20
4700/250	4700	6800	50.00	100/25	20
6800/250	6800	10000	50.00	100/25	20
10000/250	10000	15000	50.00	100/25	20
15000/250	15000	22000	50.00	100/25	20
22000/250	22000	33000	50.00	100/25	20
33000/250	33000	47000	50.00	100/25	20
47000/250	47000	68000	50.00	100/25	20
68000/250	68000	100000	50.00	100/25	20
100000/250	100000	150000	50.00	100/25	20
150000/250	150000	220000	50.00	100/25	20
220000/250	220000	330000	50.00	100/25	20
330000/250	330000	470000	50.00	100/25	20
470000/250	470000	680000	50.00	100/25	20
680000/250	680000	1000000	50.00	100/25	20
1000000/250	1000000	1500000	50.00	100/25	20
1500000/250	1500000	2200000	50.00	100/25	20
2200000/250	2200000	3300000	50.00	100/25	20
3300000/250	3300000	4700000	50.00	100/25	20
4700000/250	4700000	6800000	50.00	100/25	20
6800000/250	6800000	10000000	50.00	100/25	20
10000000/250	10000000	15000000	50.00	100/25	20
15000000/250	15000000	22000000	50.00	100/25	20
22000000/250	22000000	33000000	50.00	100/25	20
33000000/250	33000000	47000000	50.00	100/25	20
47000000/250	47000000	68000000	50.00	100/25	20
68000000/250	68000000	100000000	50.00	100/25	20
100000000/250	100000000	150000000	50.00	100/25	20
150000000/250	150000000	220000000	50.00	100/25	20
220000000/250	220000000	330000000	50.00	100/25	20
330000000/250	330000000	470000000	50.00	100/25	20
470000000/250	470000000	680000000	50.00	100/25	20
680000000/250	680000000	1000000000	50.00	100/25	20
1000000000/250	1000000000	1500000000	50.00	100/25	20
1500000000/250	1500000000	2200000000	50.00	100/25	20
2200000000/250	2200000000	3300000000	50.00	100/25	20
3300000000/250	3300000000	4700000000	50.00	100/25	20
4700000000/250	4700000000	6800000000	50.00	100/25	20
6800000000/250	6800000000	10000000000	50.00	100/25	20
10000000000/250	10000000000	15000000000	50.00	100/25	20
15000000000/250	15000000000	22000000000	50.00	100/25	20
22000000000/250	22000000000	33000000000	50.00	100/25	20
33000000000/250	33000000000	47000000000	50.00	100/25	20
47000000000/250	47000000000	68000000000	50.00	100/25	20
68000000000/250	68000000000	100000000000	50.00	100/25	20
100000000000/250	100000000000	150000000000	50.00	100/25	20
150000000000/250	150000000000	220000000000	50.00	100/25	20
220000000000/250	220000000000	330000000000	50.00	100/25	20
330000000000/250	330000000000	470000000000	50.00	100/25	20
470000000000/250	470000000000	680000000000	50.00	100/25	20
680000000000/250	680000000000	1000000000000	50.00	100/25	20
1000000000000/250	1000000000000	1500000000000	50.00	100/25	20
1500000000000/250	1500000000000	2200000000000	50.00	100/25	20
2200000000000/250	2200000000000	3300000000000	50.00	100/25	20
3300000000000/250	3300000000000	4700000000000	50.00	100/25	20
4700000000000/250	4700000000000	6800000000000	50.00	100/25	20
6800000000000/250	6800000000000	10000000000000	50.00	100/25	20
10000000000000/250	10000000000000	15000000000000	50.00	100/25	20
15000000000000/250	15000000000000	22000000000000	50.00	100/25	20
22000000000000/250	22000000000000	33000000000000	50.00	100/25	20
33000000000000/250	33000000000000	47000000000000	50.00	100/25	20
47000000000000/250	47000000000000	68000000000000	50.00	100/25	20
68000000000000/250	68000000000000	100000000000000	50.00	100/25	20
100000000000000/250	100000000000000	150000000000000	50.00	100/25	20
150000000000000/250	150000000000000	220000000000000	50.00	100/25	20
220000000000000/250	220000000000000	330000000000000	50.00	100/25	20
330000000000000/250	330000000000000	470000000000000	50.00	100/25	20
470000000000000/250	470000000000000	680000000000000	50.00	100/25	20
680000000000000/250	680000000000000	1000000000000000	50.00	100/25	20
1000000000000000/250	1000000000000000	1500000000000000	50.00	100/25	20
1500000000000000/250	1500000000000000	2200000000000000	50.00	100/25	20
2200000000000000/250	2200000000000000	3300000000000000	50.00	100/25	20
3300000000000000/250	3300000000000000	4700000000000000	50.00	100/25	20
4700000000000000/250	4700000000000000	6800000000000000	50.00	100/25	20
6800000000000000/250	6800000000000000	10000000000000000	50.00	100/25	20
10000000000000000/250	10000000000000000	15000000000000000	50.00	100/25	20
15000000000000000/250	15000000000000000	22000000000000000	50.00	100/25	20
22000000000000000/250	22000000000000000	33000000000000000	50.00	100/25	20
33000000000000000/250	33000000000000000	47000000000000000	50.00	100/25	20
47000000000000000/250	47000000000000000	68000000000000000	50.00	100/25	20
68000000000000000/250	68000000000000000	100000000000000000	50.00	100/25	20
100000000000000000/250	100000000000000000	150000000000000000	50.00	100/25	20
150000000000000000/250	150000000000000000	220000000000000000	50.00	100/25	20
220000000000000000/250	220000000000000000	330000000000000000	50.00	100/25	20
330000000000000000/250	330000000000000000	470000000000000000	50.00	100/25	20
470000000000000000/250	470000000000000000	680000000000000000	50.00	100/25	20
680000000000000000/250	680000000000000000	1000000000000000000	50.00	100/25	20
1000000000000000000/250	1000000000000000000	1500000000000000000	50.00	100/25	20
1500000000000000000/250	1500000000000000000	2200000000000000000	50.00	100/25	20
2200000000000000000/250	2200000000000000000	3300000000000000000	50.00	100/25	20
3300000000000000000/250	3300000000000000000	4700000000000000000	50.00	100/25	20
4700000000000000000/250	4700000000000000000	6800000000000000000	50.00	100/25	20
6800000000000000000/250	6800000000000000000	10000000000000000000	50.00	100/25	20
10000000000000000000/250	10000000000000000000	15000000000000000000	50.00	100/25	20
15000000000000000000/250	15000000000000000000	22000000000000000000	50.00	100/25	20
22000000000000000000/250	22000000000000000000	33000000000000000000	50.00	100/25	20
33000000000000000000/250	33000000000000000000	47000000000000000000	50.00	100/25	20
47000000000000000000/250	47000000000000000000	68000000000000000000	50		

THE POWERFET AMPLIFIER



PFA 80
(100W plus into 8Ω)

Elegant Simplicity
Advances in high technology should make life simpler. A cluttered power amplifier board may well perform superbly but its busy elaboration is an indication that its design is pushing the limit of its component technology.
There are now many first class bipolar power amps on the market. All of them are complex and consequently expensive. Any additional improvements in the areas where they are weak (e.g. H.F. distortion) can only be obtained with yet further complexity and cost.
Only a new technology can provide the sort of "quantum jump" in component performance necessary to reduce the clutter on the board, reduce the cost and make the highest fit once more affordable.

Powerfets

So far 29 semiconductor manufacturers have invested in this new technology. Clearly powerfets are something special.

Their enormous power gains eliminate conventional drive circuitry in power amps, permitting delightfully simple designs. Their freedom from secondary breakdown and their tendency to shutdown when thermally overstressed, result in inherently stable and destruction-proof output stages, not needing protection circuitry. And perhaps best of all, their lack of charge storage make them fast and responsive, producing amplifiers of wide bandwidth and low distortion even at high frequencies.



Power Supply Components available

The PFA is perhaps the perfect realisation of the classic powerfet amp design. The superb PCB allows the use of either one or two pairs of output devices, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads).

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.


Specification	PFA80	PFA120
Bandwidth	10Hz	100KHz - 1dB
Output Power	80W (Vs - 50V)	120W (Vs - 55V)
R.M.S. into 8Ω		
THD (20Hz - 20KHz) (KHz at rated output)	≤ 0.008%	≤ 0.005%
SNR	0.004% typ	0.002% typ
Slew Rate	120dB	> 20V/μS
Gain	X22	X22
Rin	3K	3K
Vs max	-70V	-70V
Cost (built)	£15.95	£22.85
(kit)	£13.95	£20.85 P. & P. 75p

Power Amp PAN 1397

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation, providing high powers from low supply voltages.

Specification

Output power RMS	20W into 8Ω at ±22V
THD	20W into 4Ω at ±19V
SNR	0.02% at 1KHz 1W to 12W
Input	90dB
Cost (Built)	£5.80 (P. & P. 40p)

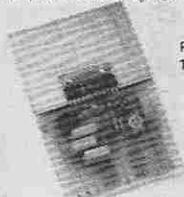

PAN 1397

PSU 101

Main transformer for above: 17-0-17V 50VA £3.95 (P. & P. £1)

Pre-amp PAN 20

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain attenuator control (VOL - control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag. Plus and space on the board is available for different equalisations.

Specification

B.W.	20Hz-30KHz - 1dB
THD	0.003% typ
at rated o.p.	
SNR	85dB (ref. 5mV RIAA)
Vs	105dB (ref. 100mV full - 20V)
Output	1V (clips at - 20dB)
Cost (built board less controls)	£4.75 (needed for stereo) (P. & P. 40p)

THE POWERFET SPECIALISTS J. W. RIMMER

Mail order only to:


Dept. E&MM/9, 148 Quarry Street, Liverpool L25 6HQ.

Telephone: 051-428 2651

Technical enquiries:

367 Green Lanes, London N4 1DY. Tel: 01-800 6667

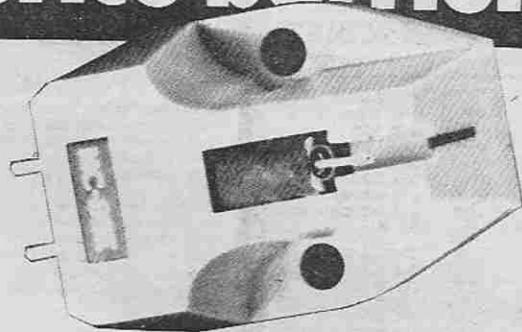A moving coil cartridge that breaks the price barrier!



the new MC88E from CORAL

The new MC88E represents a breakthrough in high output moving coil cartridges. No step-up device or amp is required and it is available at a sensational price of only £39.95.

The high output voltage of 2.5mV does away with the need for a head amplifier or step-up transformer, which add to the expense of using most previous moving coil cartridges.

We can't emphasise enough, just how advanced the technology that has produced this breakthrough is - a miniaturised and specially shaped armature; unique coil winding technique; a magnet that is so compact,

yet generating high magnetic flux density; compliance of 17 cu's. The result is a cartridge with flat frequency response over the super wide range of 20Hz - 40KHz, removing the distortion caused by certain frequencies, which can be found in many conventional cartridges. Coral's considerable experience in moving coil cartridges has enabled them to offer the ultimate in quality and performance at this incredibly low price.

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

VIDEOTONE

98 CROFTON PARK ROAD
LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. ET10

NAME _____

ADDRESS _____



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30


RAM AND EPROM NEW LOW VAT INCLUSIVE PRICES

2716 5v Rail	£6-00	4116	200 NS 16KX1 DYN.	8 for £19-95
2716 3 Rail	£7-50	2114L-3	300 NS 1KX4 ST.	8 for £22-50
2708 450 NS	£4-50	2102L-3	650 NS 1KX1 ST.	8 for £ 5-50
2708 Ex Equip	£2-25	TMS4030JL	300 NS 4KX1 DYN	8 for £ 9-95

All devices full spec. and guaranteed. Bulk enquiries welcome.

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

TELETYPE ASR33 I/O TERMINALS

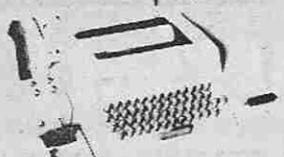

From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT
Sound proof enclosure £25.00 + VAT

ICL TERMIPRINTER 300 BAUD TERMINALS



PRICES REDUCED

ONLY £295 + CAR + VAT

Made under licence from the world famous GE Co. The ICL Termiprinter is a small attractive unit with so many features it is impossible to list them in the space available! Brief spec. as follows: RS232 serial interface, switchable baud rates 110, 150, 300, (30 cps), upper and lower case correspondence type face, standard paper, almost silent running, form feed, electronic tab settings, suited for word processor applications plus many more features. Supplied in good condition and in working order. Limited quantity.

MPU EXPERIMENTORS +5v-12v-12v-24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 180mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:
+5v @ 2 amps DC +12v @ 800 ma DC
-12v @ 800 ma DC +24v @ 350 ma DC
and if that's not enough a fully floating 5v output @ 50 ma DC which may be sensed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 340v AC mains input. They are ex-GPO and may have minor scratches on the front panels, they are sold untested but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!


HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd. to a "no cost spend" spec for the GPO, the Modem 12 is a synchronous Modem for use on DATEL 2412 services, or other data links. Many features include: switchable V28 modulation, 2400 baud full duplex 600/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication, CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc.
£185.00 + £9.50 carriage + VAT.
*Permission may be required for connection to PD lines.

PERTEC

PERTEC TAPE DRIVES
7 track 6840 — 75-25 £175.00 + VAT
9 track 6840 — 9-25 £295.00 + VAT
Phone for more details

EQUIPMENT CASES

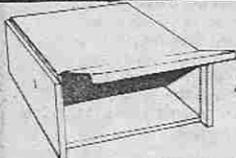

GIVE YOUR M.P.U. A HOME ONLY £9.95 + 1.85 pp

Superb professional fully enclosed, made for the G.P.O. to the highest standard, offered at a fraction of their original cost they feature aluminium sides, hinged removable front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand new may have minor scuff marks/scratches due to bad storage. Dimensions 16" D x 6 1/2" H x 14 1/2" W

NATIONAL MA1012 LED CLOCK MODULE

★ 12 HOUR
★ ALARM
★ 50/60 HZ

The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only Suitable transformer £1.75. £5.25

MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those unnerving hang ups and data glitches, fit one now and cure your problems! Suppression Devices SDS A10 5 amp £6.95
Corcom Inc F1900 30 amp £13.95 + pp £1.00

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex-equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages. 110 V.A.C. £5.05 + pp 90p OR 240v A.C. £6.15 + pp 90p DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2"

ELECTRONIC COMPONENTS & EQUIPMENT

66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kds £ 4.75 + pp £1.25 5kds £ 6.75 + pp £1.80
10kds £11.75 + pp £2.25 20kds £19.99 + pp £4.75

SAVE OVER £1400

THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232/V24 serial interface - 7 xtal controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in Z800 eproms easily reconfigured for custom fonts etc.

All this and more, not refurbished but BRAND NEW At Only £525 + VAT + carriage and ins. £18.00 + VAT
OPTIONAL EXTRAS ★ Lower case £25.00 ★ 16K buffer £30.00 ★ Second tractor for simultaneous dual forms £85.00 ★ Logabax maintenance, P.O.A.

MAJOR SAVINGS HARD DISK DRIVES

Another major purchase allows us to bring you the professional technology of hard disk drives at a price you can now afford. Just imagine absolutely masses of correct data transferred or saved on your system by the time your finger leaves the carriage return key!! All drives offered are made to the highest professional standard by the DRE Co., perhaps the largest of UK OEM peripheral manufacturers. All components are batch selected to obtain the utmost reliability and after having run two series 30 and a 4000 drive continuously 24 hours a day for over a year without a single read/write error we can most certainly vouch for the quality.

DIABLO/DRE series 30. Fully refurbished this 2.5 MB drive accepts 2315 exchangeable (via removing top cover) disk cartridges. Sectoring is a feature of the disk pack and may range from 8-48. Fully DEC RK05, Nova, Texas, system compatible. Requires +5 — 15v DC Supply. Series 30 Drive £475 + VAT Series 30 Front Loader £695 + VAT
DC Power Supply for 2 series 30's £125 + VAT
DRE 4000 B Series. Model 4044. Technology at its finest, this drive currently manufactured by DRE features 10 MB's of on line storage split into two disk platters. 1, 5 MB fixed and 1 top load 5 MB type 5440 exchangeable cartridge. Features DC drive motor, built in air conditioning system, write protect, mains powered, etc. Supplied Brand New and Boxed complete with Manual and Rack Slides.
Fully Ampex, Hawk, Wango, Nova compatible.
Manufacturers current price £3100, our price £1495 — VAT.

*For DEC compatibility or alternate sectoring please enquire. Xylogics DECLSI 11 controller for 4 S30 or 2 4000 drives £850 + VAT Newton Labs S100 controller for 4 S30 or 2 4000 £625 + VAT Controller for TRS80, PET, APPLE, price to be announced.
NEW 2315 12 sector disk packs £40 + VAT
NEW 5440 any sector packs £48 + VAT
ORDER NOW!! These prices may never be repeated. Specialist carriage S30 £15.00 + VAT 4000 £20 + VAT.

ELECTRONICS

Dept. ETI, 64-66 Melfort Road, Thornton Heath
Croydon, Surrey - Tel: 01-689 7702 or 01-689 6800

MAIL ORDER INFORMATION

Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00 Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bona Fide company orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

EX STOCK SOFTY EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. FSU £20 + £1.80 carr. + VAT.
Write of phone for more details.

9" VIDEO MONITORS

Ex-composite 9" Motorola Video Monitors 75 Ω composite input, tested but unguaranteed. £39.99 + £7.50 carriage + VAT. Complete with circuit.

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, diodes, linear, I.C.'s, triacs, diodes, bridge rect., etc. etc. All devices guaranteed brand new full spec with manufacturers markings, fully guaranteed. 50+ bag £2.95 100+ bag £5.15
TTL 74 Series
A gigantic purchase of an "access the board" range of 74 TTL series I.C.'s enables us to offer our 100+ mixed "monthly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy, fully guaranteed all I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.50

RCA FULLY CODED ASCII CASED KEYBOARDS



IDEAL - TANGERINE, OHIO ETC.

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. £43.95
VP611 Same as VP601 with numeric pad. £54.95
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. £84.26
VP616 Same as VP606, with numeric pad, Plug and cable for VP601, VP611 £2.25
Plug for VP606, VP616 £2.10
Post, Packing and Insurance. £1.95
ORDER NOW OR SEND FOR DETAILS.

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply.
Supplied complete with circuit at only £10.95 + £1.75 pp. Believed working but untested, unguaranteed.

GUITAR/P.A. MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50; 80 watt £44; 200 watt £68; 100 watt twin channel, sep. treble/bass per channel, £85; 80 watt £52; 200 watt £78; 100 watt four channel, sep. treble/bass per channel, £75; 200 watt £98; slaves 100 watt £34, 200 watt £60; 250 watt £70; 500 watt £140; fuzz boxes, great sound £12; bass fuzz £12.90; overdrive fuzz with treble and bass boosters £22; 100 watt combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £38; twin channel £115; bass combo £118; speakers 15in, 100 watt £36; 12in, 100 watt £24; 60 watt £16; microphone Shure Unidy 8 £28; 3-Channel sound/light £26.

Send cheque/P.O. to:
WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield
Cheshire. Tel: 061-308 2064

SHARP POCKET COMPUTERS

CE122 Printer/Cassette Interface £74.95
PC1211 Pocket Computer £91.95
CE121 Cassette Interface £14.95
CASIO CA-90 Watch/Calc/Game £19.95

PC1211 Software, S.A.E. details.
All prices include 15% V.A.T. and U.K. delivery

ELKAN ELECTRONICS, 28 Bury New Road
Prestwick, Manchester, M25 8LD

DO YOU TRANSMIT AUDIO SIGNALS OVER CABLE CIRCUITS?

We manufacture a full range of interface equipment for transmission of audio signals over private wire of telephone circuits, from Narrow Band STD systems (300Hz-3.4kHz) up to Wide Band Music Circuits.

PARTRIDGE ELECTRONICS

(A. C. Partridge Ltd.)

56 Fleet Road, Benfleet, Essex
Tel: (STD 03745) 3256

We also manufacture audio mixers and sub-assemblies

KEYBOARD FOR ZX81. Full-size keyboard kit for ZX80 and ZX81, £19.95. Keyboard connector, £1.95. ZX80/81 connector, £2.95. 24-line in/out port, £14.50. Motherboard, £10.44. P. & P. 40p under £10, 80p over £10. S.a.e. for details. - Redditch Electronics, 21 Ferney Hill Avenue, Redditch, Worcs., B97 4RU.

BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

1. With alarm repeat. S.R.S.P. of £17.00. Offered at £3.95, inc. VAT, or 3 for £9.95, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00. Offered at £7.95 inc. VAT each, or 3 for £19.95 inc. VAT.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

U.K. only

Discounts available on large bulk purchase.

PRESCOTT CLOCK & WATCH CO. LTD.

PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

CLASSIFIEDS

ETI RATES
1-4 Insertions £9.00 per scc
5-11 Insertions £8.00 per scc
12+ Insertions £7.00 per scc
30p per word (min 12 words)
Box No. £2.00
Closing date 1st Friday in month preceding publication.

HE RATES
1-3 Insertions £5.00 per scc
4-11 Insertions £4.50 per scc
12+ Insertions £4.00 per scc
18p per word (min 15 words)
Box No. £1.50
Closing date 2nd Friday in month preceding publication.

Classified Advertisements must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

STEREO HEADPHONES

Economy Grade £7.95
Standard Grade £11.95
Hi-Fi Grade £24.95

inc. lead, 1/4in. dia stereo plug and P&P
Cheshire Micro Des. 66 Close Lane,
Alsager, Stoke-on-Trent

CONVERT ANY TV into large screen oscilloscope. External unit plus into aerial socket. Circuit and plans £3 (SAE details). - J. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

PARAPHYSICS JOURNAL (Russian translations); Psychotronic Generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9". Paralab, Downtown, Wilts.

HALF PRICE components, switches, coils, etc. S.a.e. for lists - Gaze Electronics Ltd., 132 Gladstone Street, Darlington, Co. Durham.

ELECTRONIC MUSICAL EFFECTS. Custom-built selection of electronic effects and instruments to suit individual specification. E.g.: Delay Units, Synthesizers, Phasers, etc. GEI, 6 The Sparlings, Kirby-le-Soken, Essex. Phone Frinton (02556) 77342.

BURGLAR ALARM Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

COPPER CLAD BOARD DOUBLE-SIDED FIBRE-GLASS: - 1,000 sq. inches of assorted sizes £6,800 sq. inches of assorted sizes £5,600 sq. inches of assorted sizes £4 and 400 sq inches of assorted sizes £3. Postage free. Also complete P.C.B. services. H.C.R. (Chelmsford), 1 Bankside, off New Street, Chelmsford.

AMAZING ELECTRONICS PLANS. Lasers; Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue 75p. - From Plancentre, 16 Mill Grove, Bilbrook, Codsall, Wolverhampton.

VHF/FM TRANSMITTER KIT. New IC design means low price and better performance. Very small - ideal bug etc. . . . Receive on domestic radio (VHF 88-108MHz). Instructions etc. all included. Only £3.00 inc. P&P. unlicensable). M. Henry, Dept. ETI, 30 Westholme Gardens, Ruslip.

T. & J. ELECTRONICS COMPONENTS - Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

TRANSCENDENT DPX. Piano/strings, assembled ready to go. £325 o.n.o. Tel. Andrew 0904 86377 (evenings).

HAVE YOU SEEN THE GREEN CAT?
1000s of components (C.B., Radio & Electronic), Aerials, Plugs, SWR Meters & Accessories, Audio, Hi-Fi, Experimental devices. In fact anything electronic at unbelievably low prices. Something for everyone. Send 25p, cheque, P.O., and RECEIVE FREE GIFT.
MYERS (Dept. ETI), 12 Harper Street, Leeds LS2 7PE.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices

P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Full range of etch resist transfers and other drawing materials for p.c. boards.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASON ROAD
STRATFORD-ON-AVON
WARWICKS, Tel. 4879

MK. 14 ACCESSORIES. S.a.e. for price list. - Redditch Electronics, 21 Ferney Hill Avenue, Redditch, Worcestershire, B97 4RU.

WANTED. Electronic components and test equipment. Good prices given. Q Services, 29 Lawford Crescent, Yately (0252) 871048, Camberley, Surrey.



CCTV CAMERA

£126.50 + P&P £3.45 (inc. VAT)
Total £129.95

BEST OFFER EVER
Camera Kit, Lens,
Vidicon & Modulator


CROFTON

35 GROSVENOR ROAD
TWICKENHAM, MIDDX.

The Complete Infra Red Burglar Alarm System

for Domestic & Commercial use

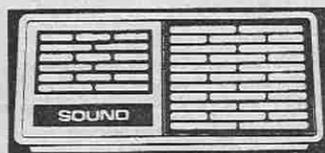Designed to specifically detect body heat and motion



Introductory Offer
£32.50+VAT
(including P and P)

Ideal for Caravans
Yachts
Shops

F D Kendall & Co
256 A/B Lewisham High St
London SE 13

- Piercing alarm
- Horizontal Aiming Control
- 9V. Battery Powered (Battery not included)
- Normal—Delay—Walk Test Function Switch
- Remote Alarm Terminal Controls
- Low Battery Warning Signal
- 9V. D.C. Adaptor Socket

3-INCH 30 OHMS 1.5-watt loudspeakers, square frame, suitable metronome project, etc., 70p each; 50p p. & p. per order. Cheques, p/os to — Afdec Electronics Ltd., 17c London Street, Basingstoke, Hants.

WE BUY surplus electronic components, PCB's, etc., for cash. Tel: (0703) 785862.

BARGAINS FOR THE QUARTZ ELECTRONIC HANDYMAN BRANDED QUARTZ ALARM CLOCKS

ORIENT/PRESIDENT JAPANESE

KIENZLE/PRESIDENT GERMAN



Returned to Service Department within guarantee period

- (1) Recommended price when perfect £12.95. To facilitate repair 5 offered for £11.95 inclusive of VAT
- (2) Recommended price when perfect £12.95. To facilitate repair 5 offered for £11.95 inclusive of VAT

These will be sold as received from our customers with the existing fault(s) and without guarantee.

UK ONLY

Discounts available on large bulk purchases.

PRESCOTT CLOCK & WATCH CO. LTD.

Prescott House, Humber Road, London NW2 6ER

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (ET28)

11 Percy Avenue, Ashford, Middx. TW15 2PB

PRE-PACKED SCREWS, Nuts, Washers, Solder Tags, Studding. Send for price list. A1 Sales (ETI), P.O. Box 402, London SW6 6LU.

CROFT ALARM EQUIPMENT. Send S.A.E. for free list or cheque or P.O. for £14.60 for our burglar alarm module to: Croft Alarms, Box 89 Stockport SK5 7ER

DIGITAL WATCH SPARES. Standard parts for all LCD watches. Send SAE for full list. Profords, Copners Drive, Holmer Green, Bucks.

ZX80/ZX81 PROGRAMMABLE CHARACTER GENERATOR. Just plugs in. Built and cased £34.50. Kit £29.95. Colour to follow. Edge connector £2.50. Memory, sound, keyboard. UK101/Superboard P.C.G. P.O.A. Resistors 3/4p. S.a.e. for details. Haven Hardware, 4 Asby Road, Asby, Workington, Cumbria.

MICROTAN 65. Superb game for single board users with keypad. Road Race features a winding road, scoring, time limit, accelerator and obstacles. Documented listing £2; also Mastermind £2. J. R. Wallace, 16 Kirkleatham Lane, Redcar, Cleveland.

PRINTED CIRCUIT BOARDS designed. Realistic prices. Manufactured/delivered assembled or unassembled. Quick delivery on one-offs or multiples. Complete artwork/silk screening service. Enquiries to — Bertal Designs, 66 Harwood Close, Arnold, Nottingham. Tel. Nottm. 202049.

OFFICIAL POWERTRAN KIT BUILDERS AND REPAIRERS. Let the official Powertran kit specialists build or repair your kit for you. All work guaranteed and undertaken by professionals. Fast service (see our display advert. elsewhere). — Phone 01-767 1233 for details or please write to Circolec, 1 Franciscan Road, Tooting, London, S.W.17.

PROGRAMMING UV. EPROMS, SPECIAL OFFER, £2.50/1K ALL INCLUSIVE. Quote ref. SO29. — Petron Electronics, 1 Courtlands Road, Newton Abbot, Devon.

STUDIO HIRE

8-TRACK STUDIO INCLUDING SYNTHESISERS, FREE TEA and a handy musician/engineer, £20 per 6-hour session. Ideal for composers, synth'players, etc.

For full details catch DAVE on WAT-FORD 39347.

SPEED - VERSATILITY - ECONOMY



WIRING SYSTEM

SPEED UP YOUR WIRING TECHNIQUE AND OBTAIN A LOW COST, PROFESSIONAL RESULT USING THE MOST VERSATILE MANUAL WIRING SYSTEM AVAILABLE.

For further information write to: — T.J. BRINE ASSOC., FREEPOST, HASLEMERE, SURREY, GU27 3BL. (TE) 0428 53850.

ASK ABOUT OUR INTRODUCTORY OFFER!

35 LEDS (RED) £5

AEG 5mm matched, full spec.

Inc. P&P, VAT and Clips

Mail order only

COVE COMPONENTS

58 Southwood Road

Cove, Farnborough

Hampshire GU14 0JJ

2114-L2

PRICES DOWN

Brand new, full spec., 200ns LOW POWER STATIC RAM

Prices slashed due to huge response to previous offer. New inclusive prices

1	8	24
£1.50	£1.45	£1.35

P&P 40p for order under £20

INTELLIGENT COMPUTING ELECTRONICS

5 Dryden Court, Kennington Estate

Kennington, London SE11

Tel: 01-735 1488

ZX81 FLICKER-FREE GAMES. 6 on cassette, £3 (or s.a.e. details). — Kerr, Dept. ETI, 29 Chadderton Drive, Unsworth, Bury, Lancs.

CLOSE ENCOUNTERS GROUP. Personal introductions/dances, parties, talks, social events. Meet interesting, attractive people. All areas. — Tel. (Liverpool) 051-931-2844 (24 hours).

ELECTRIFY YOUR SALES! • CLASSIFIED ADVERTISEMENT

1	2	3
4	5	6
7	8	9
10	11	12
13	14	15

Please place my advert in: Electronics Today International (Delete as applicable) Hobby Electronics

Advertise nationally in Electronics Today International/Hobby Electronics. Simply print your advertisement in the coupon here (left), indicating which magazine you require. Or telephone for more information.

Name

Address

Tel. No. (Day)

Send, together with your cheque to:
Jenny Naraine, ETI/HE,
145 Charing Cross Rd., London WC2H 0EE.
Tel: 01-437 1002 Ext. 50.

BARGAIN OFFER

Massive clearout of electronic components. Ideal for home constructors, experimenters and beginners

2lb Box £2.00 plus £1.50 P&P
10lb Box £10.00 plus £2.50 P&P
Prices include VAT. Money back if not satisfied on goods returned within 14 days.

Send your order to:

HARRISON BROS
PO Box 55
Westcliff-on-Sea
Essex S50 7LQ

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4.

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices include P&P and VAT

Orders under £2 please add 20p.

SAE for List of Copper and Resistance Wires. Dealer enquiries welcome

ZX81 16K

BRAND NEW INTERACTIVE GRAPHICS

DRAGON MAZE - An exciting game of skill ... £5.95
PLANETIDS - Blast through the asteroids ... £3.95
LAP RECORD - Random circuit car racing ... £3.95
SCROLL - Rolling large text display ... £2.95
Introductory offer: £12.95 all four listings.

MACRONICS, 26 Spiers Close, Knowle, Solihull
B93 9E5

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, RIGHT TIME, £62.80.
V.L.F.7 EXPLOTE 10-150KHz, Receiver £16.50.
60KHz RUGBY RECEIVER, as in MSF Clock, serial data and audio outputs, £17.90.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (TX) Old School Lane, Milton, Cambridge

ADAM HALL

Cabinet & Flightcase Fittings, fretcloths coverings, handles, castors etc. Jacks & sockets. Cannons. Bulbins, reverb trays. Emular compression drivers. AKG mics. Celestion speakers. ASS glassfibre horns.

Send 30p postal order for illustrated catalogues to

ADAM HALL (E T SUPPLIES)

Unit B, Charlton Court
Grainger Road, Southend-on-Sea
Essex S52 5BZ

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac 'light-sensitive lacquer' - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

CENTURION BURGLAR ALARM EQUIPMENT. Send s.a.e. for free list or a cheque/p.o. for £5.95 for our special offer of a full-sized decoy bell cover. To: Centurion, Dept. ETI, 265 Wakefield Road, Huddersfield, West Yorkshire. Access and Barclaycard. Telephone orders 0484 35527.

ETI PCB'S
Buy it with Access
BARCLAYCARD

**MAIL ORDER ONLY
SEND S.A.E. FOR
DETAILS**

**GROFFON
ELECTRONICS
LIMITED**

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD · Tel: 01-891 1923

EPROM PROGRAMMING £2.50/K (Your chip) including erasure, +50p p+p+ins. Fast turnaround. Reductions for repeat orders, modifications etc. S.A.E. enquiries: SEAMIST S.S.D., 45 Oak Street, Fakenham, Norfolk.

COMPUTER GRAPPLER BAGS. Bag 1 contains: 16 x 4116 (200ns.) or equivalent; 2 x 2716 (350ns); 8 x 16-pin I.C. Sockets; 8 x 14-pin I.C. Sockets; 1 x LS244; 1 x LS240; 10 x Misc. LSTTL chips. Bag 2: 8 x 2118; 8 x 16-pin I.C. Sockets. All bags £15 + 60p carr./insur-ance. All components are brand new, or removed from brand-new boards; full spec. Payment with orders to - J. Wright, 27 Broomhill Drive, Glasgow, G11 7AB.

KLIFCO RETURN AN.AD No. 5. Simply return + £4.95 for any package amplifier, 10/30/60W. + T03-3in. heatsink + pot + data. - 1 Regent Road, Ilkley, LS29 9EA.

OSCILLOSCOPE repair and calibration. Quick service, competitive rates. W.I.R. Electronics. 01-367 6816.

WANTED

Test equipment, valves, tubes and scrap electronics.

Reasonable prices paid. Distance no object (UK mainland only).

FRG General Supplies
Unit 3, Longhill Industrial Estate
March, Cambridgeshire
PT15 8NQ

Tel: March (03542) 56614
or 01-404 5011
Telex: 24224 Quote Ref. 3165

BUILD A 12 into 2 mixer for £100. Details £3.50. P.O. to Mr J. A. Lovatt, Flat 5, 36 William Ave., Margate, Kent.

TELEPHONE ANSWERING MACHINES, Super Phones, Radio Phones, etc. Ring C.W.A.S. 0274 682674.

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture
Tested & fully guaranteed.
Ex-stock delivery

£6.95 inc. VAT
Post & Pack 60p

Ideal for the experimenter
COMPLETE WITH DATA

HENRY'S

404 EDGWARE ROAD, LONDON W2 1ED

PROCEEDINGS UNDER SECTION 23 OF THE PATENTS ACT 1949

(as amended by the Patents Act 1977)

NOTICE OF INTENTION TO PRESENT A PETITION TO THE HIGH COURT OF JUSTICE CHANCERY DIVISION PATENTS COURT IN THE MATTER OF THE PATENTS ACT 1949 AND IN THE MATTER OF LETTER PATENT NO. 1,141,071 Dated 29th March, 1966 and entitled "Power Supply Circuit for Continuous Wave Magnetron" granted to ADVANCE TRANSFORMER COMPANY a corporation of the State of Illinois of 2950 North Western Avenue, Chicago, Illinois, United States of America.

NOTICE IS HEREBY GIVEN that it is the intention of the said ADVANCE TRANSFORMER COMPANY to present a Petition to the Patents Court, High Court of Justice, praying that the term of the said Letters Patent be extended under Section 23 of the Patents Act 1949 as amended. AND NOTICE IS FURTHER GIVEN that on Monday the 23rd day of November 1981 at 10.30 o'clock in the forenoon or so soon thereafter as Counsel may be heard the said PETITIONERS intend to apply to the Court for fixing a date of hearing of the Petition and other Directions.

NOTICES OF OPPOSITIONS TO THE Petition must be lodged not less than seven days before the date mentioned at the Chancery Registrar's Office, Royal Courts of Justice, Strand, London WC2A 2LL. Documents requiring service upon the said Petitioners pursuant to Order 103 Rules 3 to 7 of the Rules of the Supreme Court 1979 should be served at the offices of the undersigned Solicitors of the said Petitioners.

DATED THIS 7th day of August 1981.

Bird & Bird
2 Gray's Inn Square, London WC1R 5AF
Solicitors for the Petitioners

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

To ICS, Dept. Z263, Intertext House,
London SW8 4UU

Name

Address

Age

ICS

To ICS, Dept. M265, Intertext House
London SW8 4UJ
or telephone 01-622 9911 (all hours)

ADVERTISEMENT INDEX

Acorn Computers	71
Akhter Instruments	12
Altek Instruments	70
Ambit International	34 & 48
Audio Electronics	7, 27 & 82
Audio Video Services	92
Bi-Pak Semiconductors	21
BK Electronics	36 & 77
Black Sar Ltd.	71
B.N.R.S.	35
Braithwaite Kits	99
Calculator Sales & Service	49
Cambridge Learning	47
Chiltmead	67
C.H.J. Supplies	42
Chordgate Ltd.	48
Chromasonics	87
Chromatronics	9
Circolec	76
Clef Products	71
Crimson Elektrik	92
Crofton Electronics	7
Danavox	61
Delta Tech. & Co.	76
Display Electronics	102
Electronize Design	48
Electrovalue	86
Greenbank Electronics	38
Greenweld Electronics	86
Hameg Ltd.	62
Happy Memories	70
Heath Electronics	60
Henry's Radio	28, 92 & 98
ILP Electronics	69, 90 & 91
LB Electronics	42
L & B Electronics	93
Magenta Electronics	97
Manor Supplies	76
Maplin	42 & 108
Marshalls	100
Memotech Ltd.	16
Micro Times	93
Midwich Computers	9
Newbear Computing	28
E. R. Nicholls	42
OK Machine & Tool	20
Parndon Electronics	99
T. Powell	86
Powertran Electronics	2 & 107
Prentice-Hall International	27
Rapid Electronics	28
J. W. Rimmer	101
Riscomp Ltd.	16
R.T.V.C.	75
Shebman Electronics	77
Silica Shop	96
Silicon Speech Systems	49
Sinclair Research	80 & 81
Sola Sound	99
Swanley Electronics	39
Swift of Wilmslow	49
Technology Resources	62
Technomatic	30
Tempus	6 & 7
Texas Instruments	77
Timedata Ltd.	39
TK Electronics	53
Transam Components	55
Vero Electronics	85
Videotone	70 & 101
Watford Electronics	4 & 5
West Hyde Developments	92
Wilmslow Audio	76
Wireless World	39
Yale Security Products	16

Much more than just kits quite simply the best way to make music ...

WORLD
LEADERS IN
ELECTRONIC
KITS

The smart contemporary styling of the 'black-boxes' contain the easy-to-build advanced electronics that produce everything from high grade amplification to complex lighting effects. These units are among the finest of their kind available and combine, as do all the Powertran kits, constructional ingenuity with high grade performance capability.

The finest materials and components are used throughout and the easy-to-follow fully illustrated and diagrammed manuals make building as pleasurable as operating.

Each unit can, of course, perform its independent function — but if it is compatible with its fellows (same cabinet sizes and the same quality and professional finish) to enable you to assemble an impressive bank of wholly controllable power.



MPA 200 — a 100W amplifier with professional finish and performance at an exceptionally low price. Adaptable inputs mixer accepts a variety of sources. Straightforward construction — an excellent beginners kit. **COMPLETE KIT £49.90 (+ VAT)**

CHROMATHEQUE 5000 — 5 channel lighting effect system. Sound to light, strobe to music level, random or sequential effects — each channel handles up to 500W yet minimal wiring is needed with our single-board design. **COMPLETE KIT £49.50 (+ VAT)**

ETI VOCODER — 14 channel for maximum versatility and high intelligibility: each channel has independent level control. 2 input amplifiers — for speech/external excitation — each with level control and tone control. The Vocoder is a superb machine capable of infinite variety of operation. Construction with our easy to follow, comprehensive builders' manual — is challenging yet within the scope of most enthusiasts. **COMPLETE KIT £195 (+ VAT)**

SP2 200 — 2 channel 100W amplifier. Two of the rugged, reliable and economic amplifiers from the MPA200 are fed by separate power supplies from a common toroidal transformer. Fully finished metalwork, fibreglass PCBs, controls, wire — everything you need to make this powerful unit. **COMPLETE KIT £64.90 (+ VAT)**



DJ90 STEREO MIXER — a versatile new mixer with 2 stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Auto planning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulation — everything ... yet still under £100! (Our console below shows the mixer neatly teamed with a Chromatheque and SP2 200) **COMPLETE KIT £97.50 (+ VAT)**



Money Back Guarantee — If you are not completely satisfied with your Powertran Kit return it in original condition within 10 days for full refund.

Free Soldering Practice Kit — To assist the beginner we will supply, on request with your first kit order, a free soldering practice kit with useful tips and illustrations.

Component Packs — All our kits are available as separate packs (e.g. PCB component sets, hardware sets etc). Prices in our FREE catalogue.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

MORE KITS AND FULL ORDER
DETAILS INSIDE FRONT
COVER

STOP PRESS

MAPLIN ROAD SHOWS

Friday 25th September
Grainger Room
Newcastle Centre Hotel
New Bridge Street,
Newcastle-upon-Tyne

Saturday 26th September
Rosebery Room
Grosvenor Centre Hotel
Grosvenor Street
Edinburgh

Sunday 27th September
Ullswater Room
Portland Hotel
3 Portland Street
Piccadilly Gardens
Manchester

Monday 28th September
The Malvern Suite
Birmingham Centre Hotel
New Street
Birmingham

Tuesday 29th September
The Riverside Suite
Hotel Nelson
Prince of Wales Road
Norwich

For further details
phone 0702 554155



in SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



in HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

make it easy...

The Maplin Matinée

Amazing value for only £299.95 plus £99.50 for cabinet if required (carriage extra)

Easy to build, superb specification.

Comparable with organs selling for up to £1,000. For full construction details refer to Electronics & Music Maker.



with MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911

by MAIL ORDER

A fast service
You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **maplin** your first choice for components every time!

Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____

ET11081