


Electronics today

ISSN. 0142-7229

INTERNATIONAL

NOVEMBER 1981 ONLY 65p

★ FREE INSIDE ★
★ CIRCUIT SUPPLEMENT ★

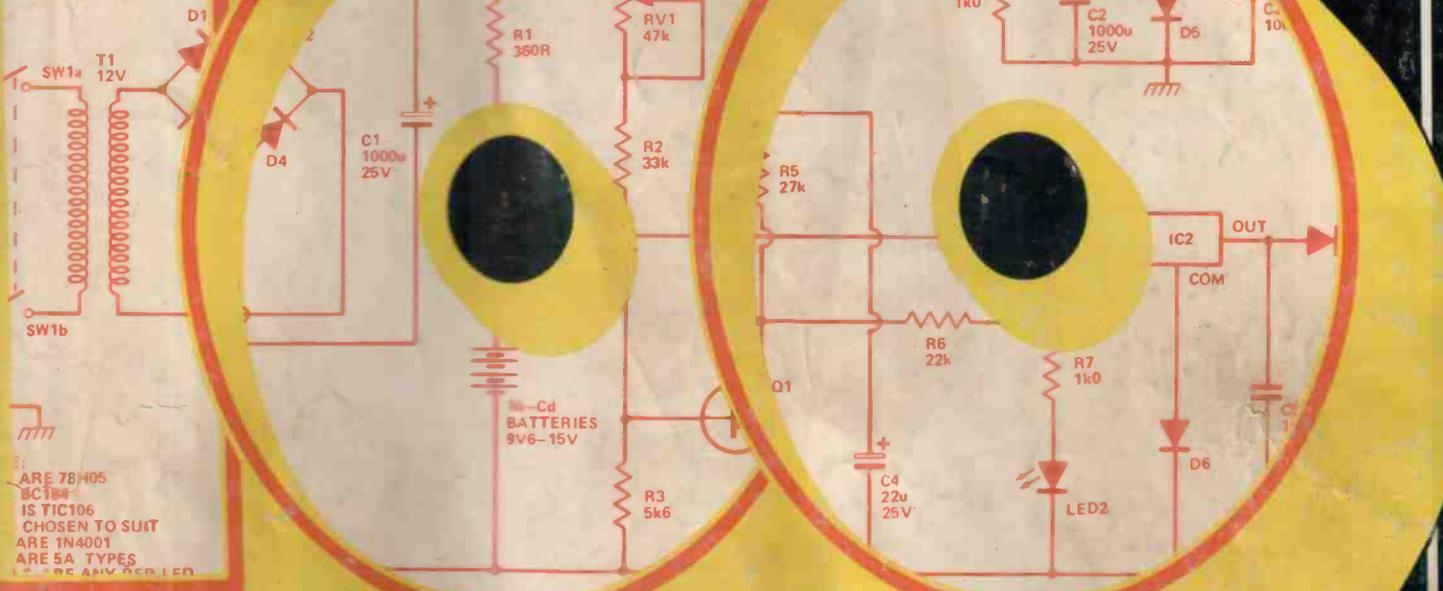

ARE 78405
BC184
IS TIC106
CHOSEN TO SUIT
ARE 1N4001
ARE 5A TYPES
ARE ANY REQUIRED

NEW DESIGNS TO TRY!

PLUS

ROBOTICS AND SENSOR TECHNIQUES

DIY MUSIC PROCESSOR TO BUILD

VOICE-OVER UNIT FOR DJs

BETTER VALUE THAN EVER!
OVER 120 PAGES
OF ELECTRONICS
INSIDE!

AUDIO....COMPUTING....MUSIC...RADIO....ROBOTICS...

Much more than just kits quite simply the best way to make music ...

OVER
TEN YEARS
EXPERIENCE
IN QUALITY
KIT DESIGN
AND SUPPLY

Powertran have been designing and manufacturing high-quality electronic kits for more than a decade. Thousands have been purchased and assembled by constructors throughout the UK and world-wide. Many of our regular clients have built the entire range — several times! A Powertran kit makes an excellent gift for the electronics enthusiast; and is a gift that, when constructed, may be given again.

Our reputation rests on these unshakeable foundations — we use the most imaginative and ingenious designers; we use high grade components subjected to rigid quality control; our kits are complete, even screws and wire are included; we take care with packing and despatch; our instructions are clear and always fully comprehensive ... and if that weren't enough we back it up with our money-back guarantee. Powertran care and your skill gives you that something special.

Among the most popular of our kits are the fabulous 'Transcendent' range of synthesisers. Designed by the expert in the field, Tim Orr, and featured in Electronics Today International — those kits represent the zenith in both constructional ingenuity and musical performance. Thanks to our fully illustrated, carefully diagrammed 30 pages plus of constructional notes the 'Transcendent' range is comfortably within the capability of most enthusiasts. A great many 'first time builders' have completed them without difficulty and are justifiably pleased with the results.



TRANSCENDENT POLYSYNTH — brilliant design work and high technology components give the home constructor a machine of such versatility and range, equalled only by factory-made units costing thousands of pounds. Despite the advanced electronics the kit is mechanically simple with minimal wiring and ribbon cable connectors. Solid teak cabinet, fully finished metalwork — a 100% complete kit to give totally professional result.
COMPLETE KIT £320 (+ VAT)
Team the Polysynth with the new matching 4 voice expander
COMPLETE KIT £295 (+ VAT)

TRANSCENDENT DPX — a versatile 5 octave keyboard. The two audio outputs can be used simultaneously to give harpsichord and piano/honky-tonk or reed and strings/brass both fully polyphonic. To add more excitement there is a chorus/ensemble unit with strong or mild effect switching. The DPX is an advanced design — yet care, and our superb construction manual, make it a kit for every enthusiast.
COMPLETE KIT £299 (+ VAT)

TRANSCENDENT 2000 — a 3 octave keyboard yet with all the design ingenuity and thorough engineering that makes a superb and versatile machine. Quality teak cabinet and quality components throughout — complete down to the 13 amp plug. Buy it — build it — then plug-in and play it! A truly professional sound.
COMPLETE KIT £168 (+ VAT)

1024 COMPOSER — one of our latest designs. The Composer controls the synth, with a sequence of up to 1024 notes or equal selection of shorter sequences. Mains powered and with trickle-charged battery to preserve programme after switch-off.
COMPLETE KIT £89.50 (+ VAT)

... write or phone for NEW 40 page '81/82 catalogue — FREE!



PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until Dec 31st, 1981, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed. Cheques, Barclaycard, Access accepted.


SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.
SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m.-12 noon, 1-4.30p.m. Monday-Thursday.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

MORE SUPERB KITS INSIDE
THE BACK COVER OF
THIS ISSUE

12/11/81

G-L DREW 011 47147

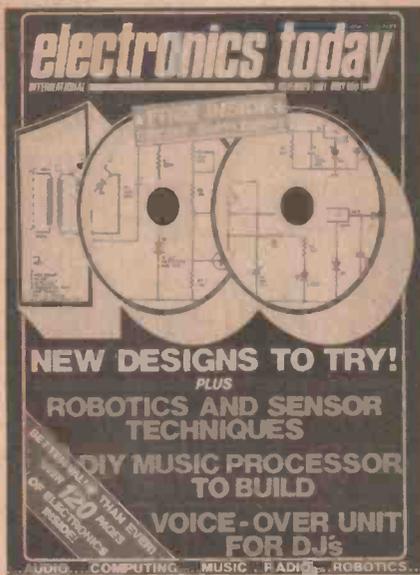

24 pages of goodies p.50

electronics today

NOVEMBER 1981 VOL 10 NO 11 INTERNATIONAL

FEATURES

- | | | |
|---------------------------|----|--------------------------------|
| DIGEST | 10 | Nothing but the news |
| TELECOM TURNROUND | 19 | What's yellow and dangerous? |
| FASTER-THAN-LIGHT TRAVEL | 32 | Faster than a speeding photon. |
| ENGINEER'S GUIDE TO BASIC | 45 | Part 2 delves into data |
| 100 CIRCUIT SUPPLEMENT | 50 | Circuits delivered by the ton |
| AUDIOPHILE | 81 | Pages of Alpages |
| ROBOTICS TODAY | 88 | The editor muses about mobiles |

PROJECTS

- | | | |
|--------------------|-----|----------------------------------|
| VOICE-OVER UNIT | 26 | It's the disco duck |
| MUSIC PROCESSOR | 38 | Fabulous four-fold effects |
| PHONE BELL SHIFTER | 78 | Personalise your phone — legally |
| CAR ALARM | 94 | A new twist to an old idea |
| FOIL PATTERNS | 101 | The other side of our projects |

INFORMATION

- | | | |
|-------------------------|-----|------------------------------------|
| BREADBOARD '81 | 9 | Social event of the year |
| NEXT MONTH'S ETI | 17 | The delights of December |
| BOOKS | 37 | Curl up with a good one |
| SUBSCRIPTIONS | 43 | Sign up for a year |
| PCB SERVICE | 76 | Buy one of our etchings |
| ELECTRONICS — IT'S EASY | 84 | You can't keep a good special down |
| BINDERS | 117 | Bound backnumbers last longer |




New choices from Telecom p.19



For fading DJs p.26



Effects unit extraordinaire p.38

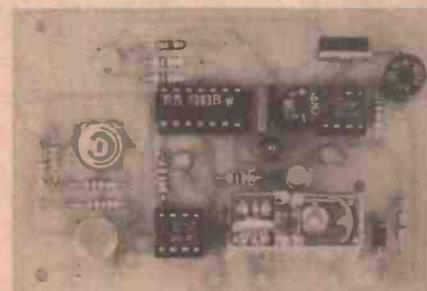

Drive thieves away p.94

ETI NOVEMBER 1981

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.
Telex 8811896.

Ron Harris B.Sc.
Alan Griffiths
Paul Wilson-Patterson
T.J. Connell

Editor
Advertisement Manager
Group Art Editor
Managing Director

Peter Green
Tina Boylan
Judith Jacobs
Alison Lilly
Paul Edwards
Rory Holmes

Assistant Editor
Editorial Assistants

Assistant Art Editor
Drawing Office Manager
Project Editor

PUBLISHED BY
DISTRIBUTED BY
PRINTED BY
COVERS PRINTED BY

Argus Specialist Publications Ltd.,
145 Charing Cross Road, London WC2H 0EE
Argus Press Sales & Distribution Ltd.
12-18 Paul Street, London EC2A 4JS (British Isles)
QB Limited, Colchester
Alabaster Passmore

OVERSEAS
EDITIONS
and their
EDITORS

AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsman



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. © Argus Specialist Publications Ltd 1981. All material is subject to worldwide copyright protection. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press. □ Subscription Rates. UK £11.25 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

SWITCHES

TOGGLE: 2A, 250V. SPST 33p DPDT 44p... SUB-MIN TOGGLE SPST on/off 54p SPDT c/over 60p...

DIL SWITCHES

(SPST) 4 way 70p; 6 way 85p; 8 way 90p; 10 way 145p. (SPDT) 4 way 190p... ROTARY SWITCHES: (Adjustable Stop type) 1 pole/2 to 12 way; 2p/2 to 6 way; 3 pole/2 to 4 way; 4p/2 to 3 way 45p...

VEROBOARD 0.1in

2 1/2 x 3 1/4" clad plain 150p 73p 52p... 2 1/2 x 5" 83p... 3 3/4 x 3 3/4" 83p... 3 3/4 x 5" 95p 79p... 3 3/4 x 17" 326p 211p... 4 1/4 x 17" 426p... Pkt. of 100 pins 50p... Spot face cutter 118p... Pin insertion tool 162p...

PLUGS & SOCKETS

JACK 2.5mm (plastic) 8p Plug Socket In-line 10p... Metal 15p 8p 10p... 3.5mm (plastic) 10p 15p 12p... Metal 16p 10p 18p... 1/4in Mono Plastic 15p 20p 15p... Metal 36p 14p 30p... Vinyl Stereo 22p 24p 22p... Plastic 36p 20p 39p... DIN 2 pin 8p 6p 14p... 3 pin 13p 10p 15p... 4 pin 16p 12p 15p... 5 pin 13p 12p 15p... BANANA 1mm 9p 9p... 2mm 13p 13p... 3mm (wander) 11p 11p... 4mm 13p 14p... CO-AXIAL (TV) Plastic 10p 16p 8p... Metal 19p 20p 40p... UHF Connectors (50Ω-CB) Plug PL259 40p; Reducer 14p; Socket SO239 Round Chassis 40p; Socket SO239 Square Panel 38p... BULGIN ICTAL 250V-6A/pin Plug P551 199p; Socket 68p... IEC 3 pin 250V/6A Plug, chassis mounting 40p; Socket, free hanging 70p; Socket, with 2 metre lead 150p... ZERO INSERTION FORCE DIL SOCKETS 24 way 650p; 28 way 820p; 40 way 975p...

PANEL METERS

FSD 60x46x35mm 0-50uA 95p... 0-100uA 10p... 0-500uA 10p... 0-1mA 0-5mA 20p... 0-10mA 20p... 0-50mA 20p... 0-100mA 20p... 0-500mA 20p... 0-1A 0-1A 20p... 0-2A 20p... 0-2.5V 20p... 0-50V AC 20p... 0-300V AC 20p... "VU" 445p each... 100KHz 290... 200KHz 370... 455KHz 383... 1MHz 300... 1.008M 395... 2.28MHz 392... 1.6MHz 323... 1.8MHz 323... 1.8432MHz 300... 2MHz 305... 2.4576MHz 300... 2.6144MHz 240... 3.57954M 150... 3.6864MHz 300... 4.000MHz 300... 4.032 290... 4.19430M 200... 4.433619 120... 5.0MHz 240... 5.195M 300... 5.24288M 240... 6.0MHz 240... 6.144MHz 240... 6.5536MHz 200... 7MHz 200... 7.168MHz 290... 7.680M 200... 8.0MHz 200... 8.08333M 362... 8.828237M 240... 9.375M 323... 10.0MHz 240... 10.7MHz 270... 12MHz 290... 14.31818M 320... 16.0MHz 275... 18MHz 240... 18.432M 240... 19.968MHz 240... 20.0MHz 323... 20.8333M 362... 26.69MHz 240... 27.145MHz 240... 27.648M 320... 38.6667M 290... 48.0MHz 270... 100.00MHz 323... 118.0MHz 300...

RELAYS

REED, Encapsulated, Single Pole, 5W Normally Open, 200mA, 50V DC... RL12 700Ω 6V to 9V 120p... RL13 1KΩ 9V to 12V 120p... RL14 1KΩ 12V to 18V 120p... RL15 3KΩ 18V to 30V 135p... Single Pole, Change Over... RL16 1KΩ 4V to 10V 295p... RL17 1KΩ 9V to 12V 295p... Double Pole, Normally Open... RL18 350Ω 9V to 12V 200p... Miniature, enclosed, PCB mount. Our RL6 series... RL6-91 170Ω coil, 7V5 to 12V DC; 380V/6A AC; 1300VA/50W 210p... RL6-111 170Ω coil, 8V-14V; 250V AC 5A 220p... RL6-114 740Ω coil, 17V5-29V 250V/5A AC 222p... CONTINENTAL Cradle Type Relays. Miniature Plug-in relays. 110V DC; 12V AC, 2A/DC; 2.5A AC 30W/100VA. 2 pole c/over 185Ω; 6V-18V. RL201 180p... RL202 180p... 4 pole c/over 9V to 18V; 185Ω. RL211 220p... High Power "Heavy Duty" PCB Mounting, Cradle type. S.P.C.D. Power Gain 1-8000 380V AC/16A; 3.5k VA, 6 to 19V; 190Ω 295p...

FERRIC CHLORIDE

1 lb bag Anhydrous 195p + 50p P&P... ULTRASONIC TRANSDUCER 40KHz 395p pr... DIL SOCKETS (TEXAS) Low Prof. Wire Wrap 8pin 8p 25p... 14pin 10p 35p... 16pin 10p 42p... 18pin 16p 52p... 20pin 22p 60p... 22pin 25p 70p... 24pin 25p 70p... 28pin 28p 80p... 36pin 30p 99p... D CONNECTORS (Cannon type) Pins Plugs Sockets Covers 9way 9p 125p 145p... 15way 135p 198p 150p... 25way 198p 284p 170p... 37way 290p 398p 185p... EDGE CONNECTORS: (Double type) 2x10 way -1 156... 2x15 way -1 135p... 2x18 way 140p 145p... 2x22 way 160p 165p... 2x25 way 180p 175p... 2x30 way 199p... 2x36 way 235p... 2x40 way 265p... 2x43 way 280p... COPPER CLAD BOARDS Fibre Single Double S.R.B.P. glass sided sided 9.5" x 8.5" 6" x 6" 90p 95p... 6" x 12" 150p 195p... DIL SOCKETS (Cannon type) Pins Plugs Sockets Covers 9way 9p 125p 145p... 15way 135p 198p 150p... 25way 198p 284p 170p... 37way 290p 398p 185p... Soldercon Pins 100 pins 70p... 500 pins 220p...

CRYSTALS

100KHz 290... 200KHz 370... 455KHz 383... 1MHz 300... 1.008M 395... 2.28MHz 392... 1.6MHz 323... 1.8MHz 323... 1.8432MHz 300... 2MHz 305... 2.4576MHz 300... 2.6144MHz 240... 3.57954M 150... 3.6864MHz 300... 4.000MHz 300... 4.032 290... 4.19430M 200... 4.433619 120... 5.0MHz 240... 5.195M 300... 5.24288M 240... 6.0MHz 240... 6.144MHz 240... 6.5536MHz 200... 7MHz 200... 7.168MHz 290... 7.680M 200... 8.0MHz 200... 8.08333M 362... 8.828237M 240... 9.375M 323... 10.0MHz 240... 10.7MHz 270... 12MHz 290... 14.31818M 320... 16.0MHz 275... 18MHz 240... 18.432M 240... 19.968MHz 240... 20.0MHz 323... 20.8333M 362... 26.69MHz 240... 27.145MHz 240... 27.648M 320... 38.6667M 290... 48.0MHz 270... 100.00MHz 323... 118.0MHz 300...

PIEZO TRANSDUCERS

Type PB-2720 75p... BUZZERS, miniature, solid-state 6V; 9V & 12V 70p... LOUDSPEAKERS Miniature, 0.3W; 8Ω. 2in, 2 1/4in, 2 1/2in, 3in 2 1/2in 40Ω, 64Ω or 80Ω 80p... WANDER MIKE The new Radio microphone that transforms your FM radio into a cordless PA System. Just tune-in your radio on to 90MHz, turn on the Wander Mike and you have instant high quality sound reproduction, PA System. Has a range of 100 feet +. Also supplied is a 5-metre cable with jack plug, should you wish to use it as a standard microphone. Ideal for singers, musicians, conferences, lectures, discos, clubs etc. ONLY £39.50... SPEAKING CLOCK Complete Kit of parts available for this clock. Only £37.50...

DIL PLUGS

14pin 44p... 16pin 49p... 24pin 88p... 40pin 250p... Double ended DIP Jumpers 14pin 18pin 40pin 6in 185p 205p 300p 465p... 12in 195p 215p 315p 490p... 24in 215p 235p 350p 540p... 36in 230p 250p 375p 595p... AMPHENOL PLUGS IEEE 675p Centronics I/O 657p

JUMPER LEADS (Ribbon Cable Assembly)

Single ended DIP Jumpers 24 Inches 14 pin 145p; 16 pin 165p; 24 pin 240p; 40 pin 385p... Double ended DIP Jumpers 14pin 18pin 40pin 6in 185p 205p 300p 465p... 12in 195p 215p 315p 490p... 24in 215p 235p 350p 540p... 36in 230p 250p 375p 595p... AMPHENOL PLUGS IEEE 675p Centronics I/O 657p

TRANSFORMERS

Prim. 240V 6.0-6V; 9.0-9V; 12.0-12V 100mA 98p... PCB mounting, Miniature, Split Bobbin 3VA; 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p... 6VA; 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p... Standard Split Bobbin type: 6VA; 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A; 2x15V-0.25A 270p... 12VA; 2x4.5V-1.3A; 2x6V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 275p (35p p&p)... 24VA; 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 320p (60p p&p)... 50VA; 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 400p (60p p&p)... 100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).

VOLTAGE REGULATORS

+ve metal case -ve 1A TO3 5V 7805 145p... 12V 7812 145p... 15V 7815 145p... 18V 7818 145p... 1A TO220 Plastic Casing 5V 7805 50p... 12V 7812 50p... 15V 7815 50p... 18V 7818 50p... 24V 7824 50p... 100mA TO92 Plastic Casing 5V 78L05 30p... 6V 78L62 30p... 8V 78L82 30p... 12V 78L12 30p... 15V 78L15 30p... CA3085 95p... LM3048 170p... LM309KP 99p... LM309H 170p... LM309M 140p... LM309K 35p... LM317K 130p... LM317H 280p... LM323K 550p... LM325N 240p... LM326N 240p... LM327 270p... LM723 35p... TAA550 50p... TBA625B 75p... TOA1412 150p... 78H05 + 5V/5A 50p... 78H6 + 5V to +25V 5A 650p... 79HG-2.25V to 24V 5A 800p... IC TEST CLIPS. Professional quality. Gold plated contacts. 8 pin 450p; 14 pin 275p; 16 pin 290p; 18 pin 595p; 20 pin 699p; 22 pin 795p; 24 pin 845p; 28 pin 925p; 36 pin £12; 40 pin £13... ANTEZ SOLDERING IRON C-15W 480p; CX17W 430p; CCN-15W 440p; CX25W 445p... Spare tips, assorted sizes 50p... Spare Elements 210p... Iron stand with sponge 160p... SOLDER (Multicore) 18SWG 75p... Size 5 Dispenser 360p... Size 12 Reel 75p... 22SWG 360p... PC115 Dispenser 100p... Size 10 Reel 360p...

OPTO ELECTRONICS

LEDs with Clips TIL209 Red 13... TIL211 Grn. 17... TIL212 Yel. 18... TIL220 2" Red 14... 2" Green/Yellow or Amber 18... 0.2" Bi colour Red/Green 85p... Green/Yellow 65p... 0.2" Tri colour Red/Green/Yellow 85p... Square LEDs, Red, Green, Yellow, 30p... LD271 Infra Red 46... SFH205 Detector 91... TIL32 Infra Red 58... TIL78 Detector 60... BARGRAPH, Red 10 segments 225... LS40C 255... OCP71 120... ORP12 86... ORP61 85... 2N6777 45... ISOLATORS IL74 TIL111/2/4 50... 7 Segment Displays TIL307 875... TIL312 3" CA 105... TIL313 3" CC 105... TIL321 5" CA 115... TIL322 5" CC 115... DL704 3" CC 99... DL707 3" CA 99... DL747 6" CA 180... .8" Orange CA 250... FND357 Red 125... FND500 115... 3" Green CA 150... 3" Red CA 215... 3" 1 Red CA 150... 3" 1 Green CA 150... DVM176 1885... LCD 3 1/2 Digits 675... LCD 4 Digits 750... LCD 6 Digits 850... NEON with resistor, push fit. 250V mains Round, Red or Amber 95p... Rectangular, nut fixing Red, Amber, Green 30p... Reflective Optical Switch 296p... Slotted Optical Switch 186p...

COMPUTER CORNER

POWER SUPPLY 5V/5A Ready-built and tested £20... 4K RAM (8 x 2114) 790p... MICROCASE, Impact resist. ABS, ivory top, brown base. Very attractive. Specially designed to fit UK101 Superboard, Nascom and uncut for home-brewed micros £26... VIDEO GENIE based on TRS80. Utilises 280 12K level II BASIC, 16K RAM, 64 x 48 Video Display, incl. Cassette Deck £275... SOUND UNIT for above (ready fitted) £15... LOWER CASE for above (ready fitted) £35... SOFTY-2. The complete Microprocessor development system for Engineers & Beginners. New powerful instructions. Accepts any 24-pin 5V single rail EPROMS. Supplied fully built, tested and enclosed in a black ABS case. Also included is an encapsulated plug-in type Power Supply £169... VIC 26. Commodore's highly acclaimed and long awaited Microcomputer. Connects directly to any colour TV set. Sound reproduced through TV Speaker (Music, Language and other sound effects). Has PET type Graphics. Standard PET Basic £165... TEX EPROM Eraser £33... UV141 EPROM Eraser with timer £77... KEYBOARD 756 Full ASCII coded £39... KEYPAD 4x4 matrix (Reed switches) 350p... UHF Modulator ASTEC 6MHz 280p... UHF Modulator ASTEC 8MHz 450p... EPSON TX-80B Dot Matrix, Tractor Feed £239... EPSON TX-80 Dot Matrix, Friction Feed £239... SEIKOSHA GP80A Uni-hammer, 80 Column, Impact Graphic, Dot Printer Only £195... P&P on the above items is extra. Call in at our retail shop for a demonstration on any of the above products. Be satisfied before you buy.

WATFORD'S BOOKSHOP CORNER

TEXAS TTL Data Book (Revised Edition) 680p... TIL Cook-Book 750p... European CMOS DataBook (Comprehensive) 750p... CMOS Cook-Book 750p... Personal Computer Book 695p... Illustrating BASIC 390p... BASIC with Style 540p... A Bit of BASIC 640p... Advanced BASIC 790p... BASIC Computer Games 550p... More BASIC Computer Games 550p... Some Common BASIC Programs 1150p... Practical BASIC Programs 1250p... 6502 Software Design 900p... 6502 Application Book 960p... Programming the 6502 (C202) 1165p... Programming & Interfacing the 6502 1100p... 6502 Assembly Language Programming 1350p... 6802 Assembly Language Programming 1250p... 6809 Assembly Language Programming 1530p... Practical Intro to PASCAL 550p... Using CP/M: A self teaching guide 810p... 8080A/8085 Assembly Lang. Programming 1375p... Z80 Instruction Handbook 430p... Z80/8080 Assembly Lang. Programming 715p... Z80 Microcomputer Handbook 825p... 8080/Z80 Assembly Lang. Techniques 925p... Programming the Z80 (C280) 1230p... Z80 Assembly Language Programming 1485p... Intro to TRS-80 Graphics 760p... TRS80 BASIC - A self teaching guide 790p... ZX80 Pocket Book 520p... 30 Programs for the Sinclair ZX80 700p... Making the most of your ZX80 790p... 32 BASIC Programs for the PET Computer 1435p... PET & the IEEE 488 Bus (GP1B) 1200p... PET Graphics 1200p... Some Common Basic Programs/PET 1100p... PET/CBM Personal Computer Guide 1200p... PET Revealed 1100p... Library of PET Subroutines 1000p... Apple II Users' Guide 1200p... Practical Intro to PASCAL 550p... PASCAL with Style 600p... Programming in PASCAL (revised) 800p... CRT Controller Handbook 600p... CP/M Handbook 995p... Microprocessor Interfacing Technique 1120p... S-100 Bus Handbook 1100p... Writing Interactive Compiler & Interpreters 1340p... Please add 55p P&P charge on books... No VAT on books

TRANSFORMERS

Prim. 240V 6.0-6V; 9.0-9V; 12.0-12V 100mA 98p... PCB mounting, Miniature, Split Bobbin 3VA; 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p... 6VA; 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p... Standard Split Bobbin type: 6VA; 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A; 2x15V-0.25A 270p... 12VA; 2x4.5V-1.3A; 2x6V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 275p (35p p&p)... 24VA; 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 320p (60p p&p)... 50VA; 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 400p (60p p&p)... 100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).

VOLTAGE REGULATORS

+ve metal case -ve 1A TO3 5V 7805 145p... 12V 7812 145p... 15V 7815 145p... 18V 7818 145p... 1A TO220 Plastic Casing 5V 7805 50p... 12V 7812 50p... 15V 7815 50p... 18V 7818 50p... 24V 7824 50p... 100mA TO92 Plastic Casing 5V 78L05 30p... 6V 78L62 30p... 8V 78L82 30p... 12V 78L12 30p... 15V 78L15 30p... CA3085 95p... LM3048 170p... LM309KP 99p... LM309H 170p... LM309M 140p... LM309K 35p... LM317K 130p... LM317H 280p... LM323K 550p... LM325N 240p... LM326N 240p... LM327 270p... LM723 35p... TAA550 50p... TBA625B 75p... TOA1412 150p... 78H05 + 5V/5A 50p... 78H6 + 5V to +25V 5A 650p... 79HG-2.25V to 24V 5A 800p... IC TEST CLIPS. Professional quality. Gold plated contacts. 8 pin 450p; 14 pin 275p; 16 pin 290p; 18 pin 595p; 20 pin 699p; 22 pin 795p; 24 pin 845p; 28 pin 925p; 36 pin £12; 40 pin £13... ANTEZ SOLDERING IRON C-15W 480p; CX17W 430p; CCN-15W 440p; CX25W 445p... Spare tips, assorted sizes 50p... Spare Elements 210p... Iron stand with sponge 160p... SOLDER (Multicore) 18SWG 75p... Size 5 Dispenser 360p... Size 12 Reel 75p... 22SWG 360p... PC115 Dispenser 100p... Size 10 Reel 360p...

OPTO ELECTRONICS

LEDs with Clips TIL209 Red 13... TIL211 Grn. 17... TIL212 Yel. 18... TIL220 2" Red 14... 2" Green/Yellow or Amber 18... 0.2" Bi colour Red/Green 85p... Green/Yellow 65p... 0.2" Tri colour Red/Green/Yellow 85p... Square LEDs, Red, Green, Yellow, 30p... LD271 Infra Red 46... SFH205 Detector 91... TIL32 Infra Red 58... TIL78 Detector 60... BARGRAPH, Red 10 segments 225... LS40C 255... OCP71 120... ORP12 86... ORP61 85... 2N6777 45... ISOLATORS IL74 TIL111/2/4 50... 7 Segment Displays TIL307 875... TIL312 3" CA 105... TIL313 3" CC 105... TIL321 5" CA 115... TIL322 5" CC 115... DL704 3" CC 99... DL707 3" CA 99... DL747 6" CA 180... .8" Orange CA 250... FND357 Red 125... FND500 115... 3" Green CA 150... 3" Red CA 215... 3" 1 Red CA 150... 3" 1 Green CA 150... DVM176 1885... LCD 3 1/2 Digits 675... LCD 4 Digits 750... LCD 6 Digits 850... NEON with resistor, push fit. 250V mains Round, Red or Amber 95p... Rectangular, nut fixing Red, Amber, Green 30p... Reflective Optical Switch 296p... Slotted Optical Switch 186p...

COMPUTER CORNER

POWER SUPPLY 5V/5A Ready-built and tested £20... 4K RAM (8 x 2114) 790p... MICROCASE, Impact resist. ABS, ivory top, brown base. Very attractive. Specially designed to fit UK101 Superboard, Nascom and uncut for home-brewed micros £26... VIDEO GENIE based on TRS80. Utilises 280 12K level II BASIC, 16K RAM, 64 x 48 Video Display, incl. Cassette Deck £275... SOUND UNIT for above (ready fitted) £15... LOWER CASE for above (ready fitted) £35... SOFTY-2. The complete Microprocessor development system for Engineers & Beginners. New powerful instructions. Accepts any 24-pin 5V single rail EPROMS. Supplied fully built, tested and enclosed in a black ABS case. Also included is an encapsulated plug-in type Power Supply £169... VIC 26. Commodore's highly acclaimed and long awaited Microcomputer. Connects directly to any colour TV set. Sound reproduced through TV Speaker (Music, Language and other sound effects). Has PET type Graphics. Standard PET Basic £165... TEX EPROM Eraser £33... UV141 EPROM Eraser with timer £77... KEYBOARD 756 Full ASCII coded £39... KEYPAD 4x4 matrix (Reed switches) 350p... UHF Modulator ASTEC 6MHz 280p... UHF Modulator ASTEC 8MHz 450p... EPSON TX-80B Dot Matrix, Tractor Feed £239... EPSON TX-80 Dot Matrix, Friction Feed £239... SEIKOSHA GP80A Uni-hammer, 80 Column, Impact Graphic, Dot Printer Only £195... P&P on the above items is extra. Call in at our retail shop for a demonstration on any of the above products. Be satisfied before you buy.

WATFORD'S BOOKSHOP CORNER

TEXAS TTL Data Book (Revised Edition) 680p... TIL Cook-Book 750p... European CMOS DataBook (Comprehensive) 750p... CMOS Cook-Book 750p... Personal Computer Book 695p... Illustrating BASIC 390p... BASIC with Style 540p... A Bit of BASIC 640p... Advanced BASIC 790p... BASIC Computer Games 550p... More BASIC Computer Games 550p... Some Common BASIC Programs 1150p... Practical BASIC Programs 1250p... 6502 Software Design 900p... 6502 Application Book 960p... Programming the 6502 (C202) 1165p... Programming & Interfacing the 6502 1100p... 6502 Assembly Language Programming 1350p... 6802 Assembly Language Programming 1250p... 6809 Assembly Language Programming 1530p... Practical Intro to PASCAL 550p... Using CP/M: A self teaching guide 810p... 8080A/8085 Assembly Lang. Programming 1375p... Z80 Instruction Handbook 430p... Z80/8080 Assembly Lang. Programming 715p... Z80 Microcomputer Handbook 825p... 8080/Z80 Assembly Lang. Techniques 925p... Programming the Z80 (C280) 1230p... Z80 Assembly Language Programming 1485p... Intro to TRS-80 Graphics 760p... TRS80 BASIC - A self teaching guide 790p... ZX80 Pocket Book 520p... 30 Programs for the Sinclair ZX80 700p... Making the most of your ZX80 790p... 32 BASIC Programs for the PET Computer 1435p... PET & the IEEE 488 Bus (GP1B) 1200p... PET Graphics 1200p... Some Common Basic Programs/PET 1100p... PET/CBM Personal Computer Guide 1200p... PET Revealed 1100p... Library of PET Subroutines 1000p... Apple II Users' Guide 1200p... Practical Intro to PASCAL 550p... PASCAL with Style 600p... Programming in PASCAL (revised) 800p... CRT Controller Handbook 600p... CP/M Handbook 995p... Microprocessor Interfacing Technique 1120p... S-100 Bus Handbook 1100p... Writing Interactive Compiler & Interpreters 1340p... Please add 55p P&P charge on books... No VAT on books

TRANSFORMERS

Prim. 240V 6.0-6V; 9.0-9V; 12.0-12V 100mA 98p... PCB mounting, Miniature, Split Bobbin 3VA; 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p... 6VA; 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A 270p... Standard Split Bobbin type: 6VA; 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A; 2x15V-0.25A 270p... 12VA; 2x4.5V-1.3A; 2x6V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 275p (35p p&p)... 24VA; 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 320p (60p p&p)... 50VA; 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 400p (60p p&p)... 100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).


VOLTAGE REGULATORS

+ve metal case -ve 1A TO3 5V 7805 145p... 12V 7812 145p... 15V 7815 145p... 18V 7818 145p... 1A TO220 Plastic Casing 5V 7805 50p... 12V 7812 50p... 15V 7815 50p... 18V 7818 50p... 24V 7824 50p... 100mA TO92 Plastic Casing 5V 78L05 30p... 6V 78L62 30p... 8V 78L82 30p... 12V 78L12 30p... 15V 78L15 30p... CA3085 95p... LM3048 170p... LM309KP 99p... LM309H 170p... LM309M 140p... LM309K 35p... LM317K 130p... LM317H 280p... LM323K 550p... LM325N 240p... LM326N 240p... LM327 270p... LM723 35p... TAA550 50p... TBA625B 75p... TOA1412 150p... 78H05 + 5V/5A 50p... 78H6 + 5V to +25V 5A 650p... 79HG-2.25V to 24V 5A 800p... IC TEST CLIPS. Professional quality. Gold plated contacts



World's most powerful

**BASIC pocket computer
CASIO FX-702P**

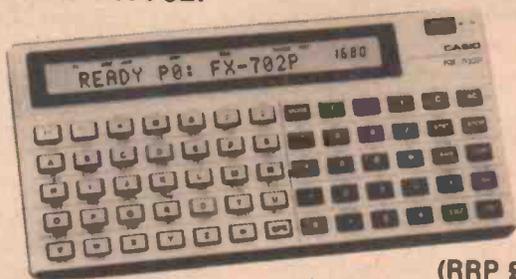

(RRP £134.95)
ONLY £119.95

High speed computer using BASIC language, with program/data storage on cassette tape via optional FA-2 adaptor.

AVAILABLE SOON: Plug in ROM program modules and FP-10 Mini Printer for program/data printout.

LCD dot matrix scrolling display. Input can be varied from 1680 program steps, with 26 independent memories, to 80 program steps with 226 memories, plus text display memory (string and string manipulations), all with power back-up. Up to 10 program storage.

Subroutines: 10 levels. FOR NEXT looping, 8 levels.

Debugging by tracing. Editing by moving cursor.

55 built-in functions including **Regression Analysis** and **Correlation Coefficient** all usable in programs. Program/data storage on cassette tape. Two lithium batteries give approximately 200 hours continuous use, with Auto Power Off after 6 mins disuse.

Dimensions: 17 x 165 x 82mm. (1/8 x 6 1/2 x 3 1/4). Weight 180g (6.3oz).

FX-602P Advanced programmable. Up to 512 steps **£74.95**
Plus **FREE Professional Programmable Pack** (RRP £12.95)

NEW! **FX-3600P** 38 program steps **£22.95**



World's most versatile

**alarm chronograph watch
CASIO AX-210**



(RRP £34.95)

ONLY £29.95

10 alternative displays
Over 60 useful functions

ANALOGUE display of time plus:

- * Digital time display, 12 or 24 hour system.
- * Digital date, month and year, plus day flag.
- * Full month calendar display, current month.
- * Full month calendar display, next month.

Auto calendar pre-programmed to the year 2029.

Dual time modes

* **ANALOGUE** display of local time, plus digital second time zone, 12 or 24 hour system.

Alarm mode

* **ANALOGUE** time with "Alarm Set" digital time, 24 hour system. AM/PM and "alarm on" indicators. Buzzer for 20 seconds, or select "Dixieland" "Green Sleeves" or "My Darling Clementine".

Hourly time signal "Big Ben" chimes at noon. Easily switched on or off.

Countdown alarm timer mode

* **Amazing ANALOGUE** display, plus digital countdown. Normal and net times from 1 to 60 minutes with automatic retrieval of pre-entered time.

Stopwatch mode

* **ANALOGUE** countup, with digital timing of net, lap and first and second place times from 1/100 sec to 1 hour. Confirmation signal.

Easy setting of times and alarm with forward and backward stepping and rapid run facility. Dimensions: 9.25 x 35 x 36mm approx. Mineral glass. Long life lithium battery. Accuracy ± 15 seconds/month.

CASIO PROGRAMMABLES

With power back-up for memories and programs

NEW FX-602P

LCD dot matrix scrolling display. 32 to 512 program steps. 22 to 88 memories. 33 parentheses, 11 levels. Editing by cursor.

Jumps.
9.6 x 71 x 141.2mm.
100g.

(RRP £84.95) **£74.95**

Plus **FREE Professional Programming Pack** (RRP £12.95)



THESE SPACE INVADERS WILL ALARM YOU

Casio's most amazing watches ever!

CA90 (left)

£19.95*

CA901 (right)

£29.95



Time and auto calendar, calculator, alarm, hourly chimes, stopwatch, dual time.

DIGITAL SPACE INVADER GAME.

CLAIRVOYANT CALCULATOR

Fortune Teller, Matchmaker, Calendar and Alarm Clock

CASIO FT-7



(RRP £18.95)

ONLY £16.95

Predictions of individual fortunes (Health; Gambline/Investment, Business and Love) or the compatibility between two persons on any given day.

6 digit clock. Auto calendar pre-programmed from 1901 to 2099. Daily alarm and hourly chimes can be easily switched on or off. Calculator with full memory, %. One year battery life (2 x LR44).

7.9 x 114 x 56.5mm (1/4 x 4 1/2 x 2 1/4"). 58g (2oz). With wallet.

NEW FX-3600P

Up to 38 steps and 2 programs, plus 7 memories, 18 parentheses, 6 levels. 61 functions, including **Integrals & Regression Analysis**. Long life **Lithium** battery.

8.7 x 71.5 x 134mm. 64g.
(RRP £25.95) **£22.95**




NEW MG-885

"Game II" and calculator. Full memory and % plus 3 level digital space invader game.

(RRP £12.95) **£10.95**

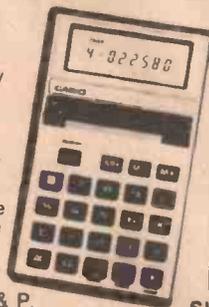The highly successful MG-880 calculator/game plus **FREE** cubik puzzle
ONLY £10.95




Delivery normally by return of post. Prices include VAT and P & P. Send your cheque, P.O. or phone your ACCESS of B'CARD number to:

SHORT FORM CATALOGUE
Available October
14p stamp appreciated

TEMPUS

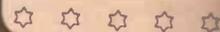THE LEADING U.K. REPRESENTATIVE,
Dept. REW/11,
164/167 East Road, Cambridge, CB1 1DB
Tel: 0223 312866





MUSICAL MICRO 24 TUNE DOOR BELL



BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

- ★ Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware
- ★ Texas Instruments TMS 1000 microcomputer
- ★ Comprehensive kit manual with full circuit details

Ready built version also available. Special offer price **£15.95 incl. p.&p.**

Plays 24 well-known tunes including:

Star Spangled Banner, William Tell Overture, Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful, plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

TMS 1000N



—MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output.

Car Horns Musical Boxes Alarms
Amusement Machines Public Address etc

£4.95

or 3 for £12.50 incl. p.&p.

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____

or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

MICROCOMPUTER COMPONENTS

LOWEST PRICES - FASTEST DELIVERY

| Device | Price | Device | Price | Device | Price | Device | Price |
|-----------------------|-------|---------|-------|------------|-------|--------|-------|
| MEMORIES | | | | | | | |
| NEW LOW PRICES | | | | | | | |
| CPUs | | 74LS49 | 0.59 | CMOS 4000 | | | |
| 6502 | 4.95 | 74LS51 | 0.14 | 'B' SERIES | | | |
| 6800 | 3.70 | 74LS54 | 0.15 | 4000 | | | 0.12 |
| 6802 | 5.11 | 74LS55 | 0.15 | 4001 | | | 0.13 |
| 6803 | 11.80 | 74LS73 | 0.20 | 4002 | | | 0.13 |
| 6809 | 11.95 | 74LS74 | 0.17 | 4006 | | | 0.60 |
| 8085A | 5.50 | 74LS75 | 0.28 | 4007 | | | 0.17 |
| Z80 CPU | 4.00 | 74LS76 | 0.20 | 4008 | | | 0.55 |
| Z80A CPU | 4.82 | 74LS78 | 0.24 | 4009 | | | 0.20 |
| | | 74LS83 | 0.50 | 4010 | | | 0.28 |
| | | 74LS85 | 0.70 | 4011 | | | 0.14 |
| | | 74LS86 | 0.18 | 4012 | | | 0.17 |
| | | 74LS90 | 0.30 | 4013 | | | 0.33 |
| | | 74LS91 | 0.80 | 4014 | | | 0.58 |
| | | 74LS92 | 0.35 | 4015 | | | 0.58 |
| | | 74LS93 | 0.34 | 4016 | | | 0.28 |
| | | 74LS95 | 0.44 | 4017 | | | 0.45 |
| | | 74LS109 | 0.25 | 4018 | | | 0.58 |
| | | 74LS112 | 0.25 | 4019 | | | 0.29 |
| | | 74LS113 | 0.25 | 4020 | | | 0.58 |
| | | 74LS114 | 0.25 | 4021 | | | 0.60 |
| | | 74LS122 | 0.39 | 4022 | | | 0.62 |
| | | 74LS123 | 0.55 | 4023 | | | 0.17 |
| | | 74LS124 | 1.00 | 4024 | | | 0.38 |
| | | 74LS125 | 0.28 | 4025 | | | 0.16 |
| | | 74LS126 | 0.28 | 4026 | | | 0.99 |
| | | 74LS132 | 0.45 | 4027 | | | 0.30 |
| | | 74LS136 | 0.28 | 4028 | | | 0.55 |
| | | 74LS138 | 0.34 | 4031 | | | 1.65 |
| | | 74LS139 | 0.37 | 4033 | | | 1.60 |
| | | 74LS145 | 0.75 | 4035 | | | 0.92 |
| | | 74LS148 | 0.90 | 4040 | | | 0.57 |
| | | 74LS151 | 0.34 | 4041 | | | 0.69 |
| | | 74LS153 | 0.35 | 4042 | | | 0.54 |
| | | 74LS155 | 0.39 | 4043 | | | 0.59 |
| | | 74LS156 | 0.38 | 4044 | | | 0.64 |
| | | 74LS157 | 0.34 | 4045 | | | 1.65 |
| | | 74LS158 | 0.36 | 4046 | | | 0.68 |
| | | 74LS160 | 0.39 | 4047 | | | 0.68 |
| | | 74LS161 | 0.39 | 4048 | | | 0.54 |
| | | 74LS162 | 0.39 | 4049 | | | 0.30 |
| | | 74LS163 | 0.39 | 4050 | | | 0.30 |
| | | 74LS164 | 0.47 | 4051 | | | 0.59 |
| | | 74LS165 | 0.99 | 4052 | | | 0.68 |
| | | 74LS166 | 0.84 | 4053 | | | 0.59 |
| | | 74LS173 | 0.70 | 4054 | | | 1.20 |
| | | 74LS174 | 0.54 | 4055 | | | 1.20 |
| | | 74LS175 | 0.54 | 4060 | | | 0.89 |
| | | 74LS181 | 1.30 | 4063 | | | 0.95 |
| | | 74LS190 | 0.55 | 4066 | | | 0.34 |
| | | 74LS191 | 0.55 | 4068 | | | 0.17 |
| | | 74LS192 | 0.69 | 4069 | | | 0.17 |
| | | 74LS193 | 0.59 | 4070 | | | 0.19 |
| | | 74LS194 | 0.39 | 4071 | | | 0.19 |
| | | 74LS195 | 0.39 | 4072 | | | 0.19 |
| | | 74LS196 | 0.58 | 4073 | | | 0.19 |
| | | 74LS197 | 0.65 | 4075 | | | 0.17 |
| | | 74LS221 | 0.60 | 4076 | | | 0.60 |
| | | 74LS240 | 0.89 | 4077 | | | 0.22 |
| | | 74LS241 | 0.89 | 4078 | | | 0.24 |
| | | 74LS242 | 0.79 | 4081 | | | 0.14 |
| | | 74LS243 | 0.79 | 4082 | | | 0.19 |
| | | 74LS244 | 0.79 | 4085 | | | 0.63 |
| | | 74LS245 | 0.89 | 4086 | | | 0.69 |
| | | 74LS247 | 1.34 | 4093 | | | 0.39 |
| | | 74LS248 | 1.00 | 4502 | | | 0.23 |
| | | 74LS249 | 0.68 | 4507 | | | 0.39 |
| | | 74LS251 | 0.39 | 4508 | | | 1.90 |
| | | 74LS253 | 0.39 | 4510 | | | 0.60 |
| | | 74LS257 | 0.44 | 4511 | | | 0.49 |
| | | 74LS258 | 0.38 | 4512 | | | 0.60 |
| | | 74LS259 | 1.15 | 4514 | | | 1.49 |
| | | 74LS261 | 1.90 | 4515 | | | 1.49 |
| | | 74LS266 | 0.23 | 4516 | | | 0.75 |
| | | 74LS273 | 0.90 | 4518 | | | 0.40 |
| | | 74LS275 | 0.34 | 4519 | | | 0.28 |
| | | 74LS283 | 0.44 | 4520 | | | 0.69 |
| | | 74LS290 | 0.56 | 4521 | | | 1.49 |
| | | 74LS293 | 0.45 | 4522 | | | 1.20 |
| | | 74LS365 | 0.34 | 4526 | | | 0.70 |
| | | 74LS366 | 0.34 | 4527 | | | 0.89 |
| | | 74LS367 | 0.34 | 4528 | | | 0.70 |
| | | 74LS368 | 0.34 | 4532 | | | 0.89 |
| | | 74LS373 | 0.74 | 4541 | | | 1.39 |
| | | 74LS374 | 0.74 | 4543 | | | 0.99 |
| | | 74LS375 | 0.47 | 4553 | | | 2.90 |
| | | 74LS377 | 0.89 | 4555 | | | 0.49 |
| | | 74LS378 | 0.69 | 4556 | | | 0.54 |
| | | 74LS386 | 0.28 | 4558 | | | 0.98 |
| | | 74LS390 | 0.59 | | | | |
| | | 74LS393 | 0.59 | | | | |

OFFICIAL ORDERS WELCOME - QUANTITY DISCOUNTS AVAILABLE

MIDWICH COMPUTER
COMPANY LTD. DEPT ET1/1
HEWITT HOUSE,
NORTHGATE STREET,
BURY ST. EDMUNDS,
SUFFOLK, IP33 1HQ
Tel: (0284) 701321

PLEASE SEND SAE (20p) FOR FULL PRICE LIST.

ALL PRICES EXCLUDE POST AND PACKING (50p ON ORDERS UNDER £10) AND V.A.T.

ALL ORDERS DESPATCHED ON DAY OF RECEIPT WITH FULL REFUND FOR OUT OF STOCK ITEMS IF REQUESTED.

CREDIT CARD ORDERS WELCOME (ACCESS AND VISA) - 24-HOUR TELEPHONE SERVICE

THE EXHIBITION FOR THE ELECTRONICS ENTHUSIAST

COMPUTERS • AUDIO • RADIO • MUSIC • LOGIC • TEST GEAR • CB • GAMES • KITS

Wednesday 11th November 10 a.m.-6 p.m. Thursday 12th November 10 a.m.-8 p.m.

Friday 13th November 10 a.m.-6 p.m. Saturday 14th November 10 a.m.-6 p.m.

Sunday 15th November 10 a.m.-4 p.m.



COMPONENTS • DEMONSTRATIONS • SPECIAL OFFERS • MAGAZINES • BOOKS

Any one of the 17,000 people who thronged the RHS for the Breadboard exhibition last year will need no introduction to this year's premier show for the electronics enthusiast. They already know all about the demonstrations, bargain sales, bookstalls, games, kits, computers and music machines to be found at BREADBOARD 81. They could name you all the leading companies who were there to see — and to buy from, at fantastic prices.

Even those lucky 17,000 would be surprised to hear that this year we've **improved** BREADBOARD still further! More stands, more demonstrations and wider gangways to make it all easier to enjoy!

BREADBOARD 81 is the place to be from November 11th to 15th at the RHS Hall. Why not come and find out for yourself how much you missed last year? We can promise plenty to see and do at BREADBOARD 81.

Close to Victoria Station and NCP car parking facilities.

Cost of entry will be £2.00 for adults and £1.00 for children under 14 yrs and O.A.P.s.

ORGANISED BY ARGUS SPECIALIST PUBLICATIONS LTD., 145

CHARING CROSS ROAD, LONDON WC2H 0EE.

ROYAL HORTICULTURAL SOCIETY'S
NEW HALL, GREYCOAT STREET,
WESTMINSTER, LONDON S.W.1.

To avoid queueing, advance tickets will be available from
Advance Tickets BB '81,
ASP Ltd, 145 Charing Cross Road,
London WC2H 0EE.

Special Advance Booking Price

Adults £1.75 Children under 14 yrs and O.A.P.s 80p

Please send tickets @ £1.75 tickets @ 80p

To:.....

.....


.....

.....

I enclose PO/cheque for £..... (make payable to ASP Ltd.)

Advance tickets **MUST** be ordered **BEFORE** 20th October 1981.

DIGEST

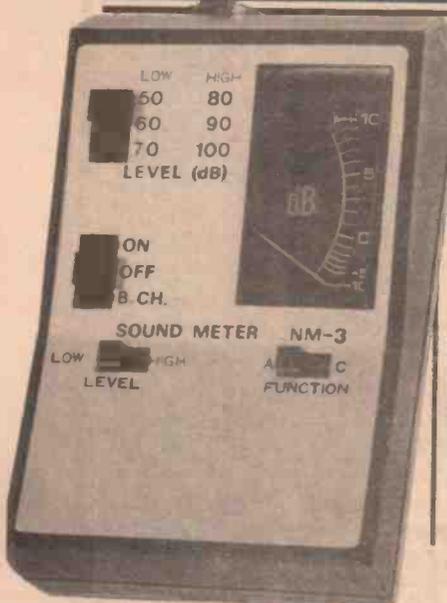

Level Sound

A new Sound Level Meter is now available from B.K. Electronics. Its a very useful gadget, essential for checking conformance of sound levels to legal and medical requirements, and to correct sound distribution with regard to sound pressure level and frequency response in theatres, conference auditoriums and discotheques etc — as well as to direct sound pressure levels and frequency characteristics of loudspeakers, not to mention correcting setting of professional and domestic graphic equalisers, etc. The Sound

Chess Choice

Vulcan Electronics Ltd have launched three chess computers simultaneously and in conjunction with the major international manufacturer SciSys. The range has been endorsed by the World Chess Federation FIDE, and each of the three offer a different form of high technology which makes them the most advanced chess computers seen in this country. The Chess Champion Mark V is an up-market chess computer and is more powerful than the average home computer as well as being the strongest micro chess computer yet developed. It retails at £249 which is about half the normal price for such an advanced model. The Super System IV offers a free conventional chessboard and pieces for its price of £119 and is very near to the Mark V in terms of sophistication. It uses the standard co-ordinate system of chess notation with an LCD display for each move. Accessories are also available, including an LCD electronic chessboard and a separate printer. Executive Chess is a hand-held model with a price tag of £89.95 and can be battery or mains operated. It has advanced technical features and makes a good 'second' chess computer for the travelling chess enthusiast. Further information on the computers is available from Vulcan Electronics, 45 South Street, Bishop's Stortford, Herts.



Level Meter incorporates two switched weighting networks 'A' and 'C', built-in condenser microphone, battery check facilities, 150 hour battery life and a measuring range of 40-110 dB in six steps. The weighting networks are thus: 'A' weighting incorporates a filter which simulates the response of the human ear and is useful for checking general environmental sound levels; 'C' weighting filter provides a flat response and is used for direct sound pressure measurement. The unit is available direct from B K Electronics for £33 including VAT, at 37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY.

Changing Names

Don't get too confused — the publishers haven't done a moonlight flit — It's just that we've changed our name! We are now called ARGUS SPECIALIST PUBLICATIONS LTD so can you make any cheques for our company payable to A.S.P. Ltd, in future. The reason for the change? Well, our offices are in Soho, and our former name, 'Modmags', seemed to attract a lot of men to our office in dirty raincoats, complaining about the content of our magazines!



Breaker 19!

If you've got a taste for CB, then CB now has a taste for you! The world's first restaurant for Citizens' Band enthusiasts has just opened in Princes Street, London W1. The Eyeball Bistro offers a wide choice of sensibly priced meals and drinks, as well as having the unique feature of enabling CBers to listen into their favourite channels while they eat (once CB is made legal, of course!) There is a powerful receiver behind the bar and speakers at each table will allow the customers to listen while they eat. There will also be a display of the latest CB equipment for customers to test or even buy there and then. Dishes on the menu have been given names using CB slang and here are a few mouth-

watering examples: a Home Office Special is a prawn cocktail, while Old Smokey (the term for the police) is slices of smoked ham served with a slice of pineapple, a Low Gain Fruit Platter is a tropical fruit salad with ice sorbet or cottage cheese topping. Drinks, both alcoholic and non-alcoholic, have names in the same style. Among them is the Good Buddy cocktail — Southern Comfort, pineapple juice and lime; or the Eyeball Special, a blend of advocaat, white rum, cherry brandy and pineapple juice. The aim of the bistro is to enable CBers to meet each other in person after having chatted over the airwaves. So if you want to pop along for an 'eyeball', make sure you get a 'good copy' on the address: The Eyeball Bistro Club, 2 Princes Street, London W1, phone 01-629 8516.

Watch This!


If you're sick of digital watches, how about taking a look at this watch from Casio. Its all analogue, but with a difference. It's fully electronic and has no moving parts. It uses LCD and has conventional hours, minutes and sweep seconds hands. The Model AN8GL is designed to be attractive and fashionable, face colour matches the synthetic strap. Hour positions are marked by standard Roman numerals and all the time settings and adjustments are handled by two buttons, keeping the compact gold-plated watch case simple and uncluttered. The display shows hour and minute hands, and seconds indication is by a third sweep hand or as a series of marks on the face edge to show accumulated seconds. Accuracy is to within 15 seconds a month. RRP is £27.95, but products of this type are often sold cheaper. Further information can be obtained from Casio Electronics Co Ltd, 28 Scrutton Street, London EC2A 4TY.




Components

Illuminations

Perdix Components Ltd announce a new range of illuminated push-button switches which offer a very low profile (29 mm) and three types of illumination — LED full face, LED spot and filament lamp styles. Actuation is either momentary or latching and the switches are offered with three types of contact and choice of side or double pole configurations. The contacts are designed with a precision snap mechanism and have a life of around 2,000,000 operations. For ease of mounting a range of mounting barriers are also available. For

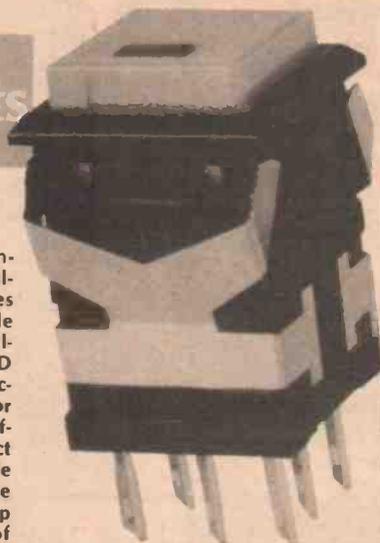


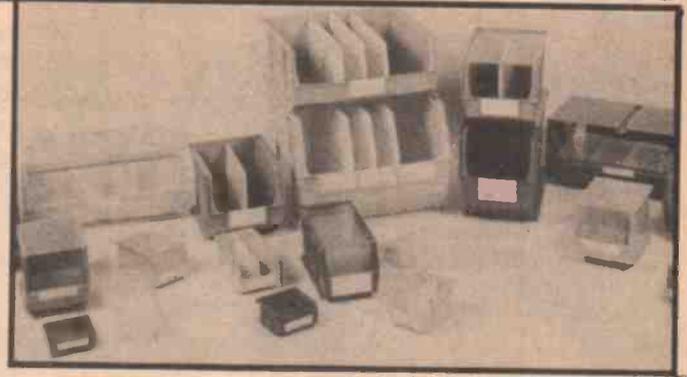further details contact: Perdix Components Ltd, 98 Crofton Park Road, London SE4.



Self-contained

Linvar Ltd are announcing their range of 'Linbin' containers, suitable for small parts storage, materials handling, display equipment and work centres. Linvar manufacture 20 types of container, all of which fit into the Linvar louvred panel. They are all manufactured from a high density anti-static polypropylene and are available in eight colours. They have identification cards, can be sub-divided and have lids attached, resulting in their selection by the Design Council. Further details can be obtained from: Linvar Ltd, Barkby Road, Leicester, LE4 7LL.

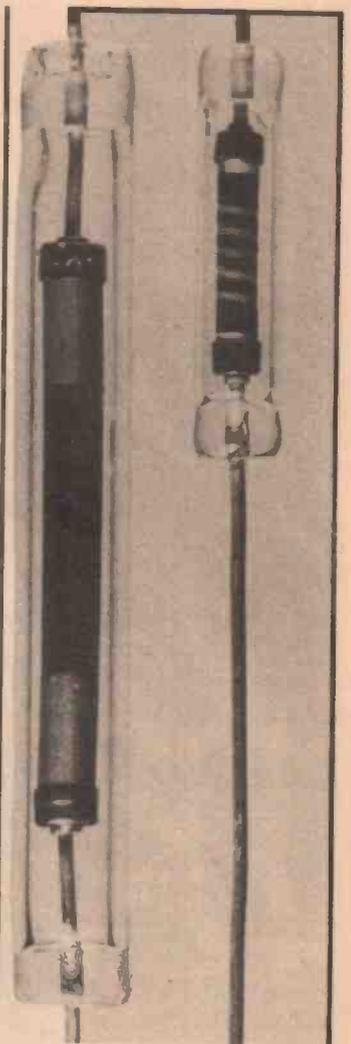


A Case In Point

Hot off the press and available for immediate delivery is the new comprehensive spring catalogue from West Hyde Developments. In this catalogue you will find many new products which have been added to their current range. These include a complete series of optoelectronics components from Mentor, together with a selection of high quality computer terminal enclosures from Bopla. The catalogue is also presented in a new easy to read, three-column format. For further information contact West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks, HP20 1ET.

Resist Them!

A series of high resistance, high voltage resistors, encased in a hermetically sealed glass envelope and believed to be the smallest of their type currently available, comes from Rhopoint Ltd. They are designed to meet the requirements of professional and laboratory applications and provide rugged stable high resistance elements unaffected by the environment. The ultra stable 'High Megohm' HR series from Component General Inc has a resistance range from 10^6 ohms to 10^{14} ohms. Operating voltages of up to 5 kV can be handled and in the event of a voltage overload, its non-spiral construction merely results in arcing across the terminals, leaving the element undamaged and immediately re-usable. The HR series includes the HR600 resistors with body dimensions of 0.562×0.110 ", maximum voltage of 1000 V and a power rating of $\frac{1}{8}$ W and the HR1250 with body dimensions of 1.25×0.156 " and a 5 kV voltage handling and $\frac{1}{4}$ W rating. Each resistor is processed for high reliability and performance. The resistance element is an inorganic film deposited on a ceramic rod and the element is hermetically sealed in a glass envelope with all exposed areas fire-polished and annealed. Protection of the element is ensured by filling the envelope with dry gas and coating the resistor with silicone to reduce surface leakage due to water absorption. For further information on all Rhopoint resistors contact them at Delta House, 118 Station Road East, Oxted, Surrey RH8 0AY.

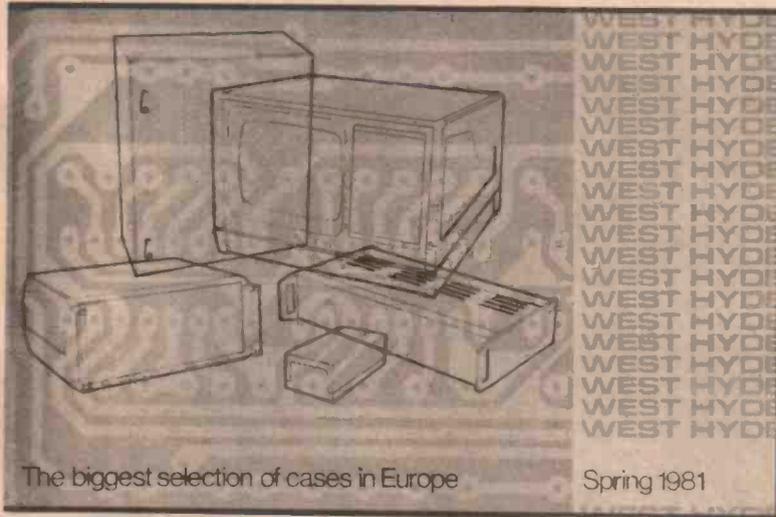

The biggest selection of cases in Europe

Spring 1981

Solder Power

Multicore Solders of Hemel Hempstead have just introduced Xersin IPC30, a multi-purpose compound containing solder powder for making a printed circuit and soldering it with just one material. This process, using screen printing or stencilling methods, provides a protective coating of copper laminate, thus ensuring good solderability. Xersin IPC30 acts as an etch-resist, surface preservative, flux and solder, and enables a seven-stage process to be reduced to just two

stages. It eliminates the need for separate applications of etch-resist remover, surface preservative, flux and solder, and the subsequent cleaning of single-sided PCBs. Multicore developed Xersin using pure chemicals instead of natural rosin as the basis for a flux, these being environmentally safer and not needing removal after soldering. This makes Xersin particularly suitable for short production runs or prototypes. Further information can be obtained from Multicore Solders Ltd, Maylands Avenue, Hemel Hempstead, Herts HP2 7EP.



EXCITING OFFERS!

DIGITAL VOLTMETER MODULE

Fully built & tested



ONLY
£11.95
+VAT

- Positive and negative voltages with an FSD of 999mV which is easily extended.
- Requires only single supply 7 - 12V.
- High overall accuracy $\pm 0.1\% + 1$ digit.
- Large bright 0.43" (11mm) LED displays.
- Supplied with full data and applications information.

Using this fully built and calibrated module as a basis now means that you can easily build a wide range of accurate equipment such as multimeters, thermometers, battery indicators, etc. etc. at a fraction of the cost of ready-made equipment. Full details are supplied with each module showing how to easily extend the voltage range and measure current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, universities, the P.O. and many companies.

Temperature Measurement £2.15 +VAT

An easily constructed kit using an I.C. probe providing a linear output of 10mV/°C over the temperature range from -10°C to +100°C. The unit is ideal for use in conjunction with the above DVM module providing an accurate digital thermometer suitable for a wide range of applications.

Power Supply £4.95 +VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V providing current levels of up to 250mA each. The unit is ideally suited for powering the DVM and the Temperature Measurement module.

ULTRASONIC ALARM MODULE

Fully built & tested

ONLY
£10.95
+VAT



Range adjustable from 5' - 25'

A really effective fully built module which contains both ultrasonic transmitter and receiver, together with the necessary circuitry for providing the appropriate delays and false alarm suppression. Using this module with a suitable 12V power supply and relay unit such as that shown, a really effective though inexpensive intruder alarm may be constructed. The module, which is supplied with a comprehensive data sheet, is easily mounted in a wide range of enclosures. A ready drilled case, together with all the necessary hardware, is available below.

Power Supply & Relay Unit

£3.95 +VAT

Incorporating a stabilised 12V supply and a s.p.c.o. relay with 3A contacts, this unit is designed to operate in conjunction with the above ultrasonic unit. Fully built and tested, its compact size makes it ideal for constructing the smallest of units.



Hardware Kit £3.95 +VAT

A suitable ready drilled case together with the various mounting pillars, nuts and bolts, and including a mains switch and 2mm sockets designed to house the ultrasonic alarm module, together with its associated power supply. This hardware kit provides an ideal solution for assembling the economical alarm system. Size 153mm x 120mm x 45mm



In addition to the above a wide range of competitively priced electronic components is stocked. Please telephone your specific requirements.

- V.A.T. must be added on all items.
- Shop hours 9 - 5.30 (Weds. 9 - 1)
- ex-stock delivery on all items.
- Units on demonstration, callers welcome.
- Post and packing charge 50p per order.
- S.A.E. with all enquiries please.



RISCOMP LIMITED

Dept. E.T.I. 2.
21 Duke Street,
Princes Risborough, Bucks.
Tel: Princes Risborough (084 44) 6326

INTRUDER ALARMS

BRANDED INTRUDER ALARMS AT DISCOUNT PRICES FOR LIMITED PERIOD ONLY

Alarm with self-contained siren. Keyed and timed entry, using minimal power consumption on stand-by. With circuit fault indicator, 3 reed switches, 1 pressure mat, wire and full installation instructions. **£36.80**

Siren extension unit to increase range **£11.75**

Self-powered siren (sounds if separately attacked) **£25.00**

Self-powered bell (sounds if separately attacked) **£29.00**

Reed switches (surface) **£1.00**

Reed switches (flush) **£0.90**

Pressure Pad — 27" x 15" **£2.20**

Pressure Pad — 22 1/2" x 6 3/4" **£1.60**

All above prices inclusive of V.A.T. and postage. Terms: Cash with order. Write to Yale Security Products, Wood Street, Willenhall, West Midlands WV13 1LA. Telephone: 0902 66911. Telex: 338251.

MEMOTECH

48K MEMORY EXTENSION FOR THE ZX81



The MEMOTECH memory extension board will allow the ZX81 to run 48K Basic programs which may include up to 16K of assembly code.

The ZX81 sits on a custom built case which contains the MEMOTECH memory and a power supply which not only supplies power to the MEMOTECH memory, but also to the ZX81.

The MEMOTECH memory board has a fully buffered control-data-address bus with PCB 40 way header plug. All leads are provided.

The MEMOTECH memory costs: £109.00 + 15% VAT in kit form. £129.00 + 15% VAT ready assembled. Please make cheques payable to MEMOTECH. Delivery in two weeks from receipt of order.

MEMOTECH, 103 Walton Street, Oxford.

Defence Digest

This new regular feature is devoted to defence electronics, its equipment techniques and application. Defence remains one of the largest growth areas in UK industry, with much of the real innovation and investment taking place there.

Defence Digest will thus act as a news (and views) section, containing up-to-date information and explanation of some of the happenings in the different sectors of the defence industry.

Companies with information and articles for these columns are invited to submit them direct to Defence Digest at our editorial address. Indeed, anyone with anything to say on the subject, be it information or opinion, is a potential contributor and should not refrain from putting pen to paper.





Minehunting

A labelled plan display and associated FM1600B computer suite which forms part of the Ferranti Mine Counter Measures Control System is shown here undergoing final test and inspection in a special commissioning

area at Cairo Mill in Lancashire. The first two of these systems has already been accepted by the Royal Navy and are at sea in the 'Hunt' class minehunters HMS Brecon and HMS Ledbury. (They feature wholly Glass Reinforced Plastic (GRP) hulls). The Control System pictured and another from the same order are destined for installation on board minehunters HMS Cottismore and HMS Chattistock, at present being built.

Rangefinder

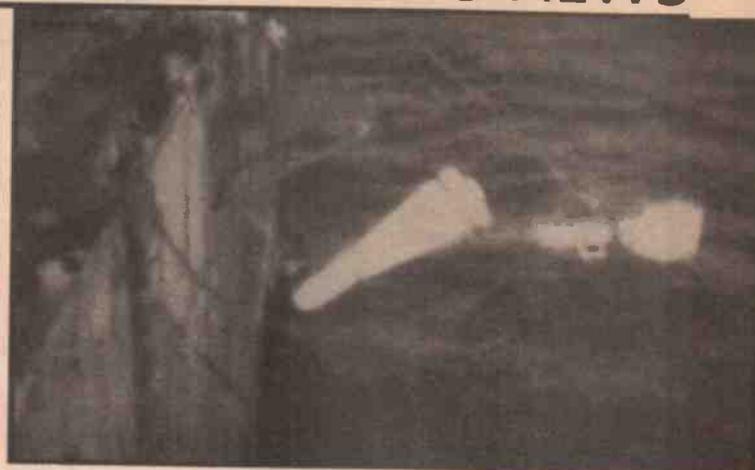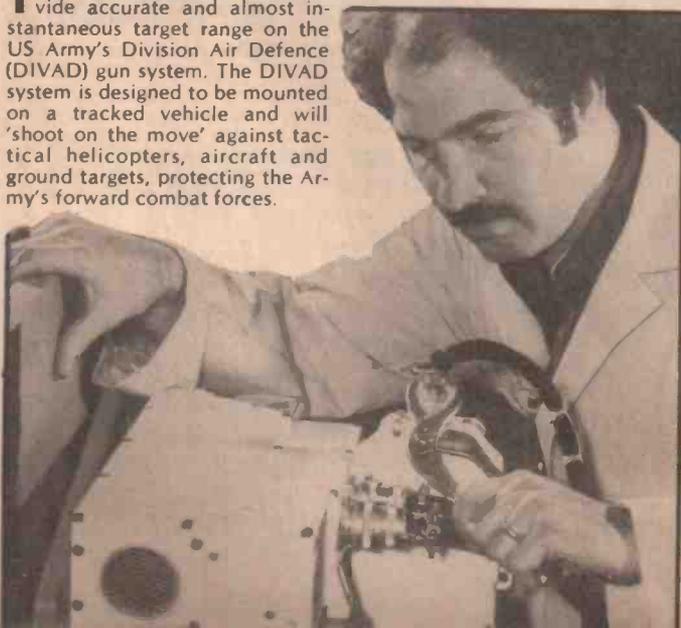
This laser rangefinder will provide accurate and almost instantaneous target range on the US Army's Division Air Defence (DIVAD) gun system. The DIVAD system is designed to be mounted on a tracked vehicle and will 'shoot on the move' against tactical helicopters, aircraft and ground targets, protecting the Army's forward combat forces.



Rocket Missile

The AGM-65 Maverick is the US Air Force's versatile rocket-propelled air-to-surface missile designed for launching from tactical aircraft against hardpoint targets such as field fortifications, bunkers, tanks, armoured personnel carriers, parked aircraft and radar or missile sites. New versions will expand the use of Maverick to the US Marine Corps and the Navy. Mavericks currently operational are the television-guided AGM-65A and the longer range TV-guided AGM-65B. They carry an electro-optical seeker in the nose which produces a TV image on cockpit display. Two other guidance systems currently in development to give the missile day-or-night capability are an im-

aging infra-red seeker, and a laser-seeking system. The Maverick delivers a warhead with a forward-firing conical shaped charge designed for high penetration, and can be launched at various ranges and speeds. The picture shows the new AGM-65E laser guided version of the missile as it neared the side of the target ship Ozark and then penetrated its hull before detonating. Launched from a US Air Force F-4 the mission was intended as a test of the missile's new 300-pound class penetrator/blast warhead's effectiveness against naval targets. The missile guided itself to a laser spot illuminated by a laser designator. The missile then penetrated through the hull of the former US Navy minesweeper, causing it to sink.

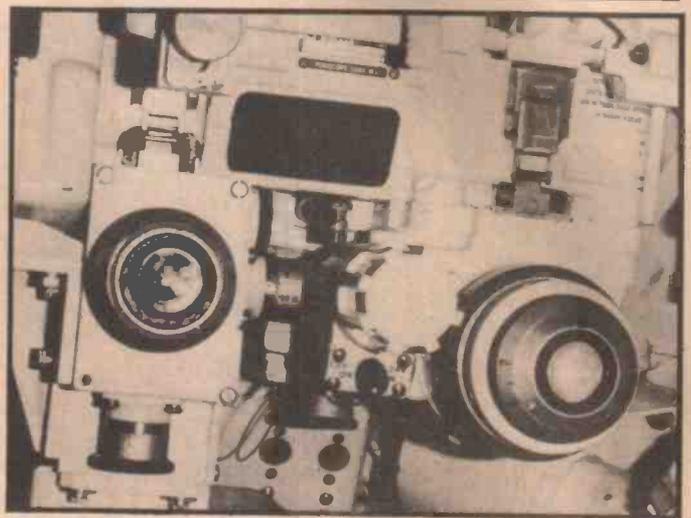

Tank Telescope

The Ferranti Type 521 laser body assembly has been designed by the Company's Electro-optics Department to replace directly the existing Day Body Assembly in the M32 Gunner's Periscope, usually installed in M48 and M60 main battle tanks. The system gives a 'times 8' sighting telescope and laser ranging with a readout of target range in the eyepiece. The type 521 can be interfaced directly with a fire control computer, by displaying an offset aiming mark in the eyepiece. This is all achieved without internal modification to the M32 Head Assembly which

need not even be removed during the replacement of the existing day assembly. The picture shows it installed in a Type M48A5 tank during field trials. The heart of the 521 is the Ferranti Type 520 laser range-finder, and advanced third generation NdYAG laser. The aim of achieving a single correct range to the target is met by first having a very narrow emitted beam divergence (typically 0.4 milliradians), and second, providing flexible receiver electronics that can be optimised to particular climatic and tactical situations. The Type 520 is packaged in a pre-aligned, plug-in module for ease of maintenance.

BI-PAK BARGAINS

"IRRESISTIBLE RESISTOR BARGAINS"

| Pak No. | Qty. | Description | Price |
|---------|------|---|-------|
| SX10 | 400 | Mixed "All Type" Resistors | £1 |
| SX11 | 400 | Pre-formed 1/4-watt Carbon Resistors | £1 |
| SX12 | 200 | 1/4 watt Carbon Resistors | £1 |
| SX13 | 200 | 1/4 watt Carbon Resistors | £1 |
| SX14 | 150 | 1/2 watt Resistors 22 ohm-2m2 Mixed | £1 |
| SX15 | 100 | 1 and 2 watt Resistors 22 ohm-2m2 Mixed | £1 |

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects. Quantities approximate, count by weight.

"CAPABLE CAPACITOR PAKS"

| Pak No. | Qty. | Description | Price |
|---------|------|---|-------|
| SX16 | 250 | Capacitors Mixed Types | £1 |
| SX17 | 200 | Ceramic Capacitors Miniature Mixed | £1 |
| SX18 | 100 | Mixed Ceramics 22pf-390pf | £1 |
| SX19 | 100 | Mixed Ceramics 470pf-047uf | £1 |
| SX20 | 100 | Assorted Polyester/Polystyrene Capacitors | £1 |
| SX21 | 60 | Mixed C280 type capacitors metal foil | £1 |
| SX22 | 100 | Electrolytics, all sorts | £1 |
| SX23 | 50 | Quality Electrolytics 50-100mfd | £1 |
| SX24 | 20 | Tantalum Beads, mixed | £1 |

Quantities approximate, count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°, 240°. Inline 3-6 Pin, Speakers, Phono, Jack, Stereo and Mono, etc. etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

| | | | |
|------|--------|---|-----|
| SX26 | 3 Pcs. | 6 pin 240° DIN Plugs and Chassis Sockets. | 50p |
| SX27 | 1 x | Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket. | 30p |
| SX28 | 4 | Phono plugs and 2 dual phono connectors. | 30p |
| SX29 | 1 x | 2.5mm Plug to 3.5mm Socket adaptor. | 20p |
| SX30 | 1 x | 3.5mm Plug to 2.5mm Socket adaptor. | 20p |
| SX31 | 1 x | 3.5mm Plug to Phono Socket adaptor. | 20p |



| | | | |
|------|------------|---|-----|
| SX32 | 1 x | Standard Jack Plug to Phono Socket adaptor. | 25p |
| SX33 | 1 x | Toggle Switch SPST Miniature. 125v 10A | 40p |
| SX34 | 1 x | Toggle Switch SPDT Miniature. 125v 10A | 40p |
| SX35 | 1 x | Rocker Switch SPDT Miniature. 240v 5A | 40p |
| SX36 | 1 x | Right Angle Mono Jack Plug. | 15p |
| SX37 | 20 pieces. | 1.2 & 4mm plugs and sockets (Banana). Matching colours and sizes. | £1 |
| SX50 | 10 | Assorted Switches Toggle Slide, Rocker, Push button. | £1 |

Guarantee

Satisfaction or your money back has always been BI-PAK's GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received.

| | | | |
|------|-----|---|-------|
| SX40 | 250 | Silicon Diodes—Switching like IN4148 DO-35 All good—uncoded. Worth double our price 45v 75mA. | £1.25 |
| SX41 | 250 | Silicon Diodes—General Purpose like OA200/202 BAX13/16 Uncoded 30-100v 200mA DO-7. | £1.25 |



| | | | |
|------|-------|---|----|
| SX44 | 10 5A | SCR's T064 3 x 50v, 3 x 100v, 2 x 200v, 2 x 400v. Super value less than 1/2 price. | £2 |
| SX45 | 10 5A | SCR's T066 2 x 50v, 2 x 100v, 4 x 200v, 2 x 400v All coded. Brand new, a give away! | £2 |



SEMICONDUCTORS FROM AROUND THE WORLD

100

A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices.

100

Guaranteed Value over £10 at Normal Retail Price

£4.00

yours for only

Data etc. in every pak. Order No. SX56



£1 FREE PAK

Get a £1 FREE PAK. Orders over £10 excluding VAT. Choose £1 Pack free (or 2 x 50p) add it to your order and save even more money. This offer only applies to this advertisement.

This offer only applies to this advertisement.

BI-PAK'S OPTO BARGAIN OF THE YEAR!

Valued at over £10—Normal Retail—we offer you a pack of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow and Clear. 7 Segment Displays both Common Cathode and Common Anode PLUS bubble type displays—like DL-33 Photo Transistors—similar to OCP71 Photo Detectors—like MEL11-12. This whole pack of 25 devices will cost you just

25

£4.00

25

AND we guarantee your money back if you are not completely satisfied. FULL data etc. included.

Order No. SX57.



IC SOCKETS

The lowest price ever.

The more you buy the cheaper they come!

| | | | |
|-----|--------|--------|---------|
| Pin | 10 off | 50 off | 100 off |
| 8 | 75p | £3.00 | £5 |
| 14 | 80p | £3.25 | £5.50 |
| 16 | 80p | £3.25 | £5.50 |
| 16" | 80p | £3.25 | £5.50 |

Quilted *



BARGAINS

| | | | |
|------|----------|--|-----|
| SX42 | 20 small | 125 Red LED's | £1 |
| SX43 | 10 | Rectangular Green LED's 2 | £1 |
| SX46 | 30 | Assorted Zener Diodes 250mw-2 watt mixed voltages all coded. New | £1 |
| SX47 | 4 | Black Instrument knobs—winged with pointer 1/2" Standard screw. Fit size 29 x 20mm | 50p |
| SX48 | 5 | Chrome knobs, standard push fit. 15mm | 50p |
| SX49 | 20 | Assorted Slider Knobs Black/Chrome, etc. | £1 |

MORE BARGAINS!

| | | | |
|------|-----------|--|----|
| SX51 | 60 metres | PVC covered Hook up wire single and stranded. Mixed colours. | £1 |
| SX58 | 25 | Assorted TTL Gates 7400 Series, 7401-7460 | £1 |
| SX59 | 10 | Assorted Flip Flops and MSI TTL | £1 |
| SX60 | 20 | Assorted Slider Potentiometers | £1 |
| SX61 | 25 | Assorted Potentiometers, Rotary, Dual, etc. | £1 |
| SX62 | 40 | Assorted Pre-sets Hor/Vert etc. | £1 |

STILL MORE!

SLIDER POTENTIOMETERS

Plastic 40mm Travel Mono
 SX63 5 x 470 ohms Lin SX67 5 x 47k Lin
 SX64 5 x 1k Lin SX68 5 x 47k Log
 SX65 5 x 22k Lin SX69 5 x 100k Lin
 SX66 5 x 22k Log SX70 5 x 1 meg Lin

| | | | |
|------|---|---|----|
| SX71 | All at 50p per pack. | 50 BC108 "Fallouts". Manufacturers out of spec. on volts or gain. You test. | £1 |
| SX72 | A mixed bundle of Copper clad Board, Fibre glass and paper. Single and double sided. A fantastic bargain. | £1 | |

6 Black Heatsink will fit TO-3 and TO-220. Ready drilled. Half price value.

| | | |
|------|---|------------|
| SX52 | 6 Black Heatsink will fit TO-3 and TO-220. Ready drilled. Half price value. | £1 |
| SX53 | 1 Power Finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre drilled. TO-3 Size 45mm square x 20mm high. | 40p |
| SX54 | TO-66 size 35mm x 30mm x 12mm. | 35p |
| SX55 | 1 Heat Efficiency Power Finned Heatsink 90mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices. | £1.50 each |

| | | |
|------|---|-------|
| SX38 | 100 Silicon NPN Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Real value. | £2.50 |
| SX39 | 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Fantastic value. | £2.50 |

| | | |
|---------------------|------------------------|----------------------|
| MULLARD ASZ 17 PNP. | Germ TO-3 Power Trans. | Pos. Replacement for |
| 60 VCB 8A | 32 VCE 30W | AD130/131/140/149 |
| 20 VEB Hfe 30mn | | 0C25/26/28/35 |
| | | 2N3613/14/17/2N1533 |

Great Value at 65p each or 2 for £1.

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification
 ● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz—3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price

£2.25 each

You could not Build one for this price.



BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional who could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a BI-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send 75p plus 25p p&p.

BI-PAK

Send your orders to Dept ETI/11 BI-PAK PO
 BOX 6 WARE HERTS
 SHOP AT 3 BALDWIN ST WARE HERTS
 TERMS CASH WITH ORDER SAME DAY DISPATCH ACCESS
 BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182 GIRO 388 7006
 ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 50p per Total order.

ELECTROVALUE CATALOGUE

82

(Ready mid October)

**Improved . . . updated and
a real money saver**

Your instant link with today's forward trends in electronic progress, your chance for quick delivery of the components you'll need for 1982 projects — plus of course, Electrovalue's vast and dependable stocks of basics — resistors, capacitors, semi-conductors, pots, connectors, meters, hardware and a massive variety of items well arranged for swift reference. In our new catalogue, computing takes far more pages, and there is a sense of urgency and service throughout to help you when ordering.

Send 70p for your copy of Catalogue 82 by return. A reclaim voucher allows you to deduct 70p when ordering goods £10 or more.

When sending for Catalogue 82 please mark CAT. 82 clearly on top left corner of envelope.

This year it's better than ever!

DISCOUNTS

(On all items except some quoted NET or N)
5% on orders over £20
10% on orders over £50

FREE POSTAGE

in U.K. on orders £5 upwards
V.A.T. Chargeable on U.K. orders at prevailing rate (15%)

ELECTROVALUE LTD., Dept. PW10, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone 33603 (STD 0784: London — 87). Telex: 264475.
Northern Branch (personal shoppers only) — 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4945.

To: ELECTROVALUE LTD., 28 ST. JUDE'S ROAD, englefield green, EGHAM, SURREY TW20 0HB.

Please send me copies of Catalogue 82 at 70p for which I enclose £.


NAME
ADDRESS

ETI/11

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

BECKER Hi-Fi Speakers

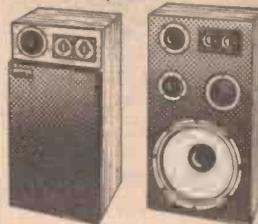

All models multi-speaker systems

With controls, attractive woodgrain finish RMS ratings for 8 ohm.


New improved models.

12.60 12" 4 speaker system 60 watts (90 watts peak) 26 1/2" x 14 1/2" x 11" £99.95 pair

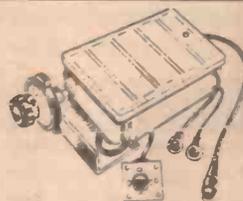15.90 15" 5 speaker system 90 watts (130 watts peak) 28" x 17 1/2" x 11 1/2" £135.95 pair

ON DEMONSTRATION TO CALLERS

Collection only
Usually a selection of good value Hi-Fi speakers in stock — please call in.



TV SOUND FROM YOUR HI-FI (Mk III)

High quality TV sound converter plugs into aerial socket of your FM tuner 9 volt battery operated (battery not supplied). Nothing to look at . . . but just listen!

★ Fitted slow-motion drive (Mk III)
(UK Post etc. 65p)

On Demonstration for callers to 301 Edgware Road.

£11.50

PUBLIC ADDRESS AMPLIFIERS AND SPEAKERS

TA770 40 Watt 240v AC OR 12v DC 4 Inputs £62.50

TA660 60 watt 240v AC OR 24v DC 5 Inputs £98.50

TA306 30 watt 240v AC OR 12v DC 3 Inputs £42.50

CP2 10/20 watt 12v DC 2 Inputs £27.60

HORNS 8 watt £4.95: 15 watt £8.95

25 watt £15.50: 40 watt £19.50

Also Range of Megaphones in Stock

MICROPHONES

U0130Hz 600/50k Dual PA-Disco, mic. £7.95

DS255 Deluxe version £12.95

ECM1026 600 ohm Mini Lapel mic. £6.95

Just 3 of 30 types in stock.



MIXER AND GRAPHICS

GX1307 10 x 10 Channel Stereo Graphic Equaliser Plus 4 Channel Stereo Mixer £115.00

MIC350E Tape Echo Chamber £75.00

DEI Electronic Echo Chamber £18.95

SM1000 4 Channel Stereo Mixer (battery operated) £49.95

SM500 5 Channel Stereo Disco Mixer Cabinet mounting £31.95

SM3000 5 Channel Stereo Mixer £12.95

MS3219 Twin 100 watt Audio Output Meter £22.95

3019 6 Range Sound Level Meter

GE1305 10 Channel Stereo Graphic Equaliser

SEAS SPEAKER KITS 8 ohm



Professional sound hi-fi speaker kits with high sensitivity (89-92dB). Extended frequency response (223'50-20kHz: '253' 35-25 kHz). Designed and made in Scandinavia to the highest quality. All supplied with complete cabinet plans. Tweeters/crossovers/leads etc.

★ Hi-Fi 223. 30/45 watt 3 speaker 8" system £43.50 pair

★ Hi-Fi 253. 60/100 watt 3 speaker 8" system £34.50 each

★ Hi-Fi 403 60/100 watt 3 speaker 10" system £44.50 each

★ Hi-Fi 603 80/150 watt 3 speaker 12" system £64.50 each

(UK C/P £7.50 per pair)

On Demonstration to callers.

PIEZO TWEETERS



Clean sound. Very low distortion tweeters. No crossover required. Suitable up to 100 watts — more in series.

1 Mid-range horn for disco/pa/groups £8.95

2 Tweeter horn for hi-fi/disco/pa £5.50

3 Popular hi-fi and disco £4.40

4 Flat type hi-fi £3.50

UK Post Free

On Demonstration to callers.

ORDER BY POST (OR PHONE) OR CALL IN

Cubegate Limited

AUDIO ELECTRONICS

301 Edgware Rd. London W2 1BN

Tel: 01-724 3564

Also at Henrys Radio 404 Edgware Rd. W2

ALL PRICES INCLUDE VAT

FREE
Catalogue
send large
20p SAE

electronics today

INTERNATIONAL

NEXT
MONTH

CROSSOVER NETWORKS

Crossover filters play an enormously important part in the quality of the sound you get from your loudspeaker; they must be precisely designed to suit the characteristics of the drive units, the enclosure and even the power amplifier being used. This article gives some insight into the modern approach to crossover design from the people who ought to know — KEF Electronics. It's bad news for suck-it-and-see home designers.

ALCOHOMETER

An entertaining little gadget for those readers who, like the ETI staff, have a certain fondness for the products of fermentation. This crystal-locked reaction timer will give a digital display of your steadily deteriorating reflexes as you imbibe at your local hostelry; although an accurate indication of your sobriety, or lack of it, isn't possible (despite our repeated attempts at calibration), it should prove to you that alcohol affects your co-ordination and doesn't really mix with driving. Alternatively you could play the new game we've invented in the office, where a group of people sit round a table with the tippie of their choice and an Alcohometer. The first person has a drink, tests his reaction time, places the Alcohometer back on the table and passes the bottle to his left. The winner is the last person still able to find the table.


COMPONENT TESTER

This handy little piece of test gear will tell you all you need to know about your semiconductors. Designed with simplicity of use in mind, it will test transistors, diodes, LEDs and standard op-amps (eight pin DIP). Any transistors, small signal or power, may be tested, and if you plug them in the wrong way round this unit lets you know; once the leads are sorted out it tells you whether the polarity is NPN or PNP. If the transistor is OK the box beeps at you, with a frequency that depends on the gain — shorted and open-circuit devices are also indicated. Similar information is provided for diodes and LEDs; polarity, short, open-circuit or OK. Op-amps are checked for adequate gain. Build one next month and you'll wonder how you ever lived without it.

BODYWORK CHECKER

Is your body in good condition? Can you be sure it will stand up under stress, or will it collapse if you ask too much of it? Don't worry, we're not getting personal — it's your car we're concerned about. ETI fearlessly probes behind the paintwork to discover how much of your vehicle is metal and how much is plastic filler. The ETI Bodywork Checker is a small, easy-to-use unit; you simply run its sensor over the bodywork and two LEDs indicate whether it's GOOD or BAD. The prototype was tested on a fleet of lorries and quite a few of the drivers got upset at the results. An invaluable aid to the second-hand car buyer.

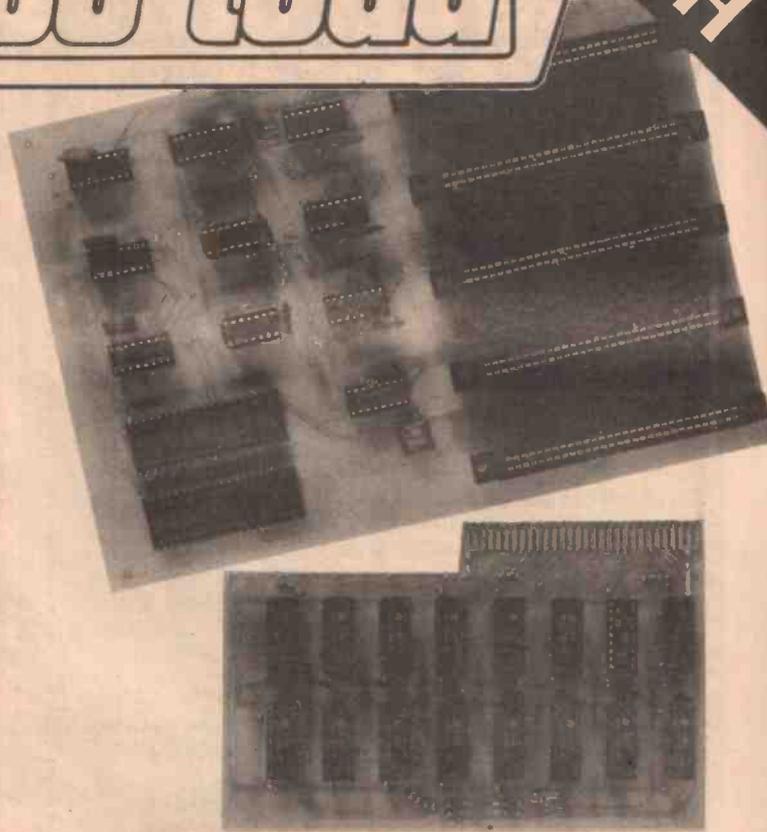Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.



UNIVERSAL MEMORY EXPANSION

Have you got a home computer? Then the chances are it's based on the 6502, one of the most popular microprocessors in current use. Are you poor, starving, and trying to decide which piece of furniture to burn first this winter to keep warm (just like us)? Then the chances are your computer has fairly limited capabilities — 8 to 16K of memory, say, and no peripherals. Next month we can change all that with a universal expansion system at a price that won't give your bank manager apoplexy.

The system consists of a motherboard (containing the decoding circuitry) and smaller plug-in boards which you insert into multi-way sockets on the motherboard. The first article will give full constructional details of the motherboard and an 8K RAM module — in the coming months we'll present other modules, including an EPROM card, programmable sound generator, parallel I/O card and a low cost disc interface. You decide which modules to fit, and where; you customise your computer to suit your own requirements. For ease of construction and a professional finish, good quality double-sided plated-through PCBs will be available, as well as complete kits of parts. This is the age of computing — make the most of it with ETI.

**LOOK OUT FOR
THE DECEMBER ISSUE
ON SALE NOVEMBER 6th**

TELECOM TURNROUND

The British Telecommunications Bill becomes law this autumn. Tina Boylan investigates its implications for the poor Buzby-berated consumer.

The Post Office has been running Britain's telecommunications since their inception. British Telecom (BT) is the name of the subsidiary responsible for this aspect of our country's communications and has total responsibility for approving, supplying, installing and monitoring all equipment for use in the UK. This effectively gives them a total monopoly, which infringes both UK and EEC law. This situation has brought about the necessity for new regulations governing communications in Britain.

Liberalisation

On 21st July 1980, the Secretary of State for Industry, Sir Keith Joseph, announced a proposal for relaxing the BT monopoly. Part of his statement included:

"We are going to allow people more freedom to use British Telecommunications circuits to offer services to third parties which are not currently provided by British Telecommunications, for example in the data processing field. I expect this change to lead to a significant growth in information, data transmission, educational and entertainment services provided over telephone circuits and to the emergence of new business. I have also decided to commission an *independent economic assessment* of the implications of allowing complete liberalisation of what are commonly referred to as value added network services"

The 'independent economic assessment' referred to in the speech was started in September 1980, after the Department of Industry commissioned Professor Michael Beesley to undertake it and it is his report, completed in January 1981, which constitutes the basis of the British Telecommunications Bill which is due to become law at the end of November this year.

In order to compile the report certain terms of reference were used viz:

To examine the scope for, and means of realising, profitable leasing of the network to users who would have unrestricted use of the capacity to provide services, taking account of:

- a) the need for such arrangements to operate to the benefit of the consumer;
- b) the effect of such arrangements on BT's present pricing structure and profitability.

During the course of the three month study, evidence was heard from many organisations and individuals, both in the UK and abroad, where communications networks are run differently.

Findings

British Telecom put the case that there should *not* be freedom to resell, because of estimated losses in revenue from

British Telecommunications Bill
(AS AMENDED ON REPORT)

ARRANGEMENT OF CLAUSES
PART I

NEW CORPORATION FOR THE PROVISION OF
TELECOMMUNICATION AND DATA PROCESSING SERVICES

The Corporation
The Corporation.

Powers and duties of the Corporation

2. Powers of the Corporation.
3. General.
4. General.



The range of telephone attachments currently available from British Telecom.

trunk calls being diverted to leased lines. They also believe that resale would deny the advantages of what they consider to be their *natural* monopoly, and that competition would ultimately increase costs.

Another of their arguments was that design standardisation and compatibility would cause problems. However, the Beesley report refutes these arguments stating that prospective losses which BT has estimated are exaggerated, particularly as they do not account for the price rises recently announced, which are effective from November 1981. The arguments over standardisation and compatibility were also considered to be easily solvable.

Although BT is constrained through Government policy on prices and investment (which is in itself economically incompatible with freer competition) it was still decided that even with these constraints maintained there would be a net profit from resale.

From the consumer's point of view, evidence was gained from European countries and the United States that liberalisation of voice services and development of highly advanced data transmission are closely connected. For example, the USA is the most liberal of all the countries surveyed and is also the farthest ahead in the non-voice data services. Its projected rate of development in the next few years is also expected to exceed that of the larger European countries.

British Telecom also felt that royalty payments would help to decrease their losses, but this suggestion was rejected by the report because of the conditions it would impose on the lessee.

Instead tariffs would be set by BT alone, which would not discriminate between customers according to whether they intend to resell circuit capacity. In any case, if allegations are made against BT of discriminatory treatment they would be referred to the Department of Industry for independent assessment.

Here On In

The findings of the report and the subsequent Bill seem quite straightforward, but in real terms how will they be implemented? What effect has the Bill already had on interested parties, and what is already being done behind the scenes at British Telecom?


In the area of data transmission, things are already happening fast, as various companies jostle for position in a race that they consider has been neglected by BT in the past. An example of this keen attitude is shown by a consortium formed by the companies of Cable and Wireless, British Petroleum and Barclays Merchant Bank. This triumvirate aim to establish a new service called 'Mercury', which they hope to start just as soon as the new liberalisation comes into effect.

Mercury will be based on a system of fibre optic networks employing Inter-City trunk routes throughout the UK. The optical fibres will be laid alongside existing British Rail Inter-City railway tracks, using their existing ducts. The advantage of this is that no planning permission will be needed to lay the new links. The service uses bit-streams of 64 kilobits compared with 9.6 KB for conventional copper cable transmission. Each stream can be subdivided into separate voice channels, allowing nearly 1,000 phone calls to be carried down each hair-thin strand of glass. They can also be used as wideband circuits for very fast data transfer speeds.

Once the transmissions have left the railways they will be transferred by microwave (eventually satellite transmissions will be used over distances greater than 400 Km) and then (hopefully) will be interfaced to BT's PSTN (Public Switched Telephone Network) using the proposed leased private lines.



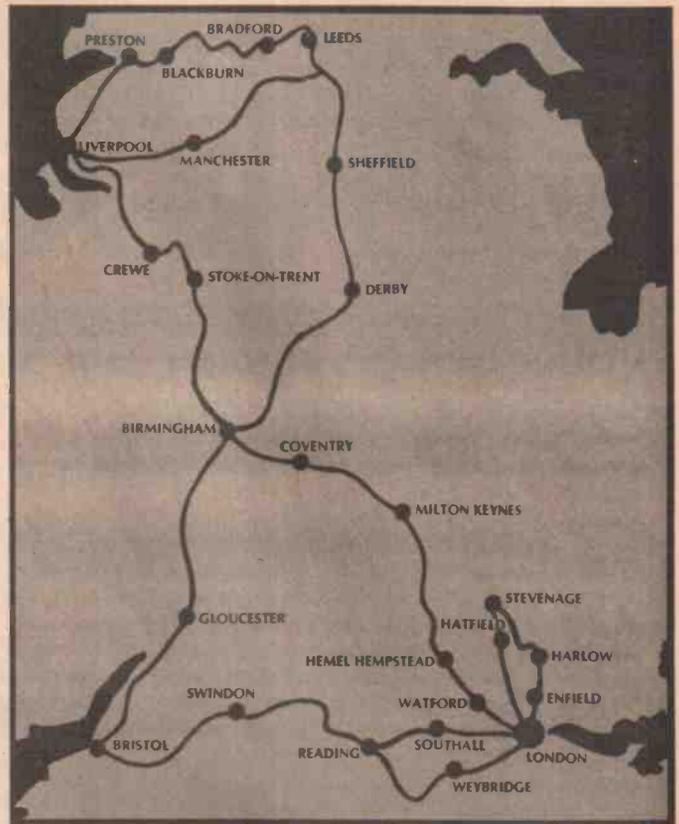One of the new range of office telephones soon to be available from British Telecom.



A map of England showing the proposed Mercury network.

If's And But's

The consortium of the three companies hope to have their service running by mid 1983, but this timescale greatly depends on BT's willingness to implement the Bill speedily. The chances are that they will procrastinate, only partly because of difficulties in the administration needed to allow a successful and smooth transition into competition. Not surprisingly BT are aggrieved that a system like Mercury will 'cream off' the lucrative trunk network traffic, which currently subsidises the loss-making local networks. British Telecom also allege that Mercury will slow down their change to the new 'System X' exchanges, which will take over from the present Strowgers which have been in existence since 1920.

Mercury, however, will undoubtedly supply a better service in an area where existing services *do not* reflect the latest technology; increased prices *do not* reflect improved services; very high speed data transmission is *simply not* available and new circuits or re-routes are *not available* at short notice.

The consortium must also have a licence from the Home Office to use microwaves before the end of the year so that they can begin to order apparatus and fibre. So far this licence is not forthcoming.

It would be unfair to judge BT too harshly in the light of the Mercury project without also mentioning their plans for fibre-optic links, for they too will be converting their trunk networks during this decade, though their projections are slightly less optimistic. They estimate that by 1990 over half the UK long distance network will be fibre optic. They also stress that any benefits to private operators using fibre optics are due to their own research and investment in this area.

The Mercury consortium are also testing a plan to use laser and microwave communications between specific buildings over short distances in the London area. Again licences are needed before these can be used, and again British Telecom are setting up plans for their own rival network on the same lines. These will effectively become secondary networks in the large cities of the UK.

Nearer Home

In our everyday contact with British Telecom changes will also occur, mostly in the supply of equipment from other companies.

The range of telephones currently on offer from BT includes models from outside manufacturers, including some foreign ones. These models are included because BT considers that they conform to their current standards and specifications. Once the Bill is made law, BT is determined that there will not be a 'free for all' in the supply of any and all types of telephone attachment. BT is, at the moment, negotiating terms and standards for the supply of telephones, as well as organising an independent body to monitor them.

It is expected that immediately after the Bill is passed at the end of November, BT itself will administer this aspect until a purpose-designed body can be initiated. It is not expected that this body, which will probably be part of the BEAB (British Electro-Technical Approval Board) or the BSI (British Standards Institution) will be in existence until early next year, when they will take over from BT.

Even with these integration plans imminent, not all the new equipment will become immediately available. The Department of Industry Consultative Committee on Telecommunications recommends the phasing in of new equipment over a period of about three years. This is in order to create an orderly transition into the competitive environment, where new suppliers as well as BT itself will have an opportunity of researching new products as well as improving the old ones over this transitional period.

The phasing is expected to follow roughly this pattern;

Phase 1, First Year

- Internal wiring
- Jack plugs (and hence sockets)
- Telephone handsets, based on 'special range' specification, and intelligent telephones
- Explosive atmosphere telephones
- Telephone answering machines
- Modems and, where appropriate, multiplexors
- Callmakers (ie repertory diallers)
- Flexibility switches and patching frames
- Network management systems

Phase 2, Second Year

- Lift telephones
- Weather telephones
- Multiterminal telephones
- Trunk barring devices
- Bells
- Diversion switches
- Flexibility, fallback devices
- Teleprinters
- Radiophones
- Radio paging receivers
- House exchange systems (Keyphones)
- Key and lamp units
- Call diversion equipments
- Alarms using PSTN
- Specialist telephones (eg for the handicapped)
- Loud speaking telephones

Phase 3, During Third Year

- Conference telephones
- Cordless telephones
- Private payphones
- Private meters
- Private branch exchanges (including ancillary equipment such as automatic call distributors, or other items where they arise)
- Private Telex branch exchanges
- Facsimile machines
- Other interconnect equipment (eg control and processing equipment for radiophone services)
- Error detection units
- Autosender
- Broadcast units

British Telecom is obviously concerned that any future standards for equipment supplied for use in conjunction with their apparatus will give the consumer the highest quality of transmission and reliability.

Stepping Up

But why is all this closely monitored standardisation necessary, you might think? Any why this 'orderly transition' business? After all, it is already quite easy to obtain telephones which are *not* BT approved in high-street shops throughout the UK, and there does not appear to be any problem getting them wired in.


Telecom is aware of this problem, but until now has tended to turn a blind eye to it. This may be because there is no legislation which allows them to prevent this equipment being sold, their only power is to prevent you using it on their lines.

Or is it?

British Telecom, in association with the Newspaper Publishers' Association have, until now, effectively prevented any advertising of illegal equipment such as answering machines and private telephones. They have managed to do this partly because, in order to advertise it, there would have to be a warning included saying that it was not suitable for connection to the UK system. Doing this would render the advertisement invalid, so the association agreed not to accept any advertising from them.

If equipment is bought from an illegal supplier and the impression is given that it can be connected, then action can be taken through the Trading Standards Officers under the Trades Descriptions Act by BT, or by the purchaser himself under the Sale of Goods Act. BT's only effective power is to withdraw the telephone service after 48 hours if they find an illegal telephone in your possession and you refuse to disconnect it.

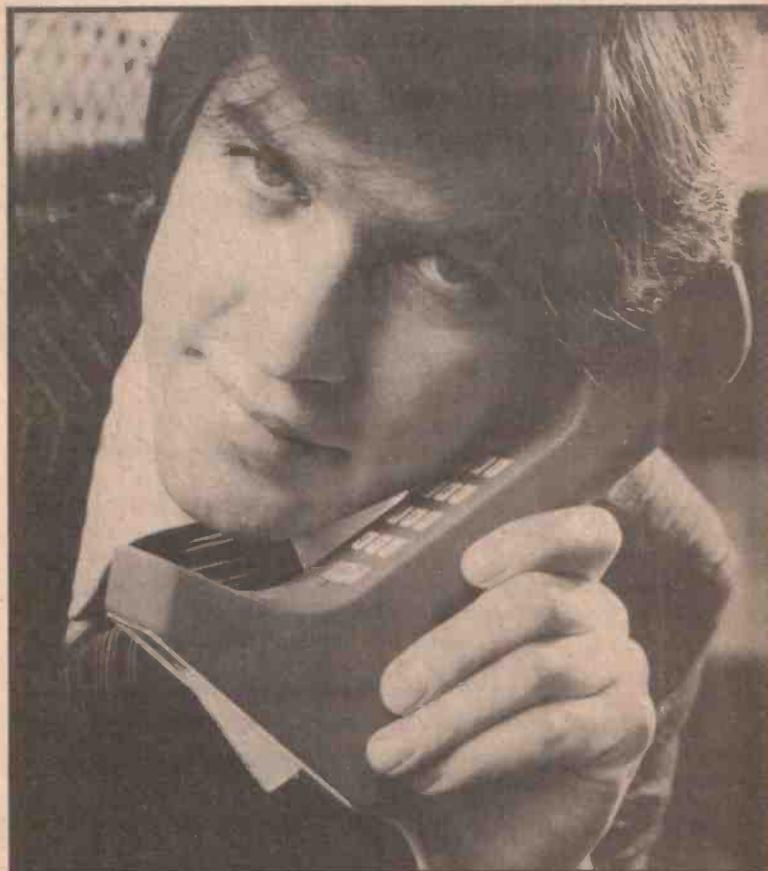Recently BT has decided to enforce their (limited) powers strongly over these illegal phones. In a directive to their employees as well as free pamphlets for the public (you may



One of the new range of British Telecom hand-held phones.

have had one with your telephone bill) they emphasise the risks to their staff of coming into contact with wrongly connected apparatus as well as the damage it can do to the network, even though there is no evidence to back up this assumption. It also emphasises that once the Bill is law, customers will not be allowed to connect apparatus without their approval. They also stress the point once more of the importance of 'orderly transition'.

Despite the fact that illegal suppliers cannot advertise their products, BT itself is investing £100,000 in advertising in the Daily and Sunday newspapers — some might describe this as saturation advertising — maybe BT is more than a little worried about what will happen once the flood gates of reform have been opened.

All Sewn Up

British Telecom is currently experiencing some very bad publicity, and the public is in uproar about what can only be considered to be inconsistencies in their policy. The first storm of protest was towards the end of August, when price increases due to start at the end of November were announced. Some of these effectively totalled 115%. Coincidentally the Bill is to be made law at exactly this time. Approximately two weeks later it was announced that BT's profits for the year totalled £180.7 million (the figure was described by the Government as lower than expected).

A BT spokesman, when asked to comment about the Bill and its effects, pointed out that it was not BT's idea, but something the Government had decided although BT had to put it into action. Perhaps with the General Election only three years away, BT are hoping to stall liberalisation plans long enough to see a Labour Government in power. They, after all

are not quite so keen on free enterprise as the Conservatives. With a few delays here and there, perhaps the third stage of their integration plan will not even have started when the Election comes round, and afterwards may not need to be started at all.

It seems only time and experience will tell how smoothly and quickly we will get our improved telecommunications network, and hopefully the consumer will not be the last party considered in the legal wrangles which are bound to ensue whatever happens.

The Newspaper Publishers Association Limited.
 6 BOUVERIE STREET
 LONDON EC4Y 8AY
 TELEPHONE: 01-583 8132

ADVERTISING DEPARTMENT

REPORT on a Meeting with Post Office Telecommunications,
 1980

Thursday

Three
 Mr M
 Mr J
 Chair
 Sect
 adv
 Mr
 Of
 m
 t
 d
 t

Use British Telecom Certified Attachments



This pamphlet explains why apparatus attached to telephone exchange lines is certified by British Telecom and why uncertified apparatus should not be used by the public.

It also explains the way in which certification would change under the Government's current proposals and suggests remedies available to users who feel they have been misled.

Why telephone apparatus is certified by British Telecom

This ensures:

- Technical compatibility with our complex network of switching, signalling and transmission equipment.
- Minimum risk of causing injury to our staff or damage to the system.
- Other users' lines are not subjected to interference.
- Connection arrangements.

computing today

NOVEMBER 1981
 ISSN 0142-7210
 70p

ON T' TELLY

The domesticated television set is no longer the simple device of Baird's dreams. It doubles up as a personal computer terminal, video games display and home movie projection system. To add to its workload there is the Teletext information system, the first of the two main information networks that we'll be taking a look at over the next couple of months. How the system has developed over the last five years and what its future is likely to be are just two of the topics to be covered in the next issue of CT.

A CRACKING SUCCESS?

Triumph Adler's new small system, the Alphatronic, certainly looks to be a winner on paper. It has inspired a number of software houses to produce business oriented packages for it but it could also fit into the serious personal market too. Our reviewer has been using the system for an extended period and reveals his discoveries about its strengths and weaknesses as a machine for serious use.

YOUR FIRST BYTE?

Judging by the amount of correspondence we receive from people who read the magazine but who don't yet own computers, there seems to be a need for an introductory series to computer programming. Starting next month we present just such a series which, in catering for the complete novice, will introduce simple programming techniques plus a few clever tricks for the more advanced computerist.

SPEAK UNTO ME

Some months ago we reported on the National Semiconductor's DIGITALKER system. There are now several complete systems that use this chip set for low-cost speech synthesis, and next month's Special Report takes a look at one such unit produced by a new British company. The unit has plug-in compatibility with one of the most popular personal computers as well as having optional interfaces for many of the other machines on the market.

MASTER ELECTRONICS NOW!

The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

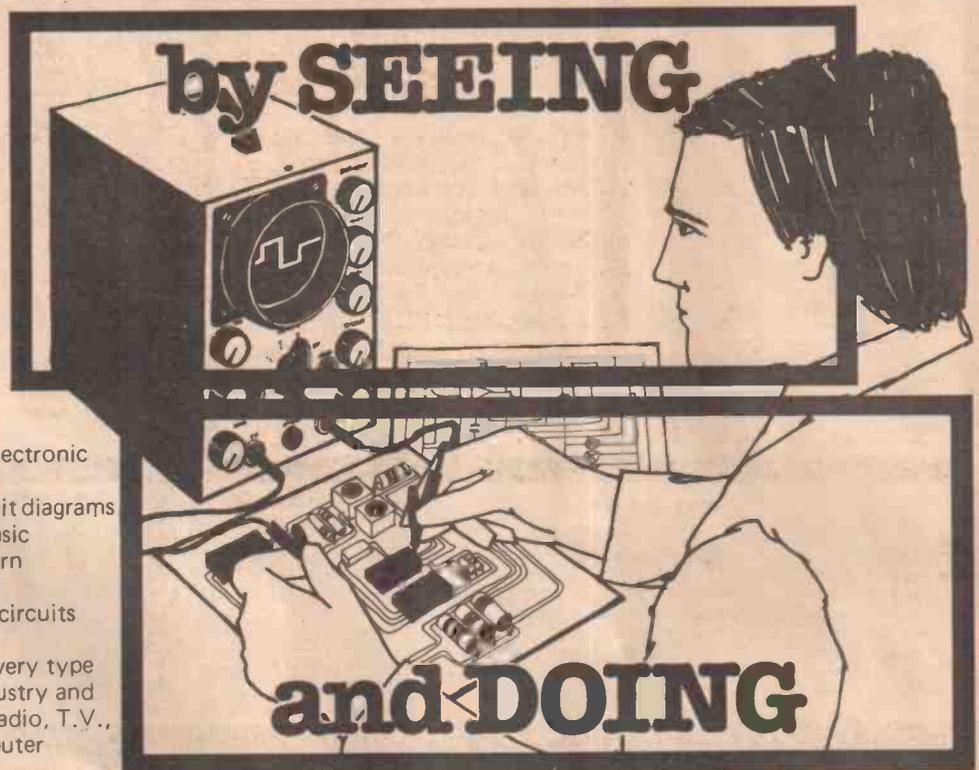

New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE



POST NOW TO:

Please send your brochure without any obligation to

I am interested in:

ET1/11/820

NAME _____

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

ADDRESS _____

OTHER SUBJECTS _____

BLOCK CAPS PLEASE _____

British National Radio & Electronics School Reading, Berks. RG1 1BR.



This disco project automatically fades the music down when the DJ talks into his microphone, then gently restores the music level when the chatting is finished. Design by Ray Marston. Development by Steve Ramsahadeo.

VOICE-OVER UNIT

A minor hassle facing the disco DJ is that whenever he needs to make a mid-music announcement, he has to go through a fiddly procedure of first turning down the music level and raising the microphone level at the start of the announcement, and subsequently reducing the microphone level and restoring the music signal when the announcement is complete. ETI's new Voice-over Unit is designed to overcome this trifling little problem.

Our stereo voice-over or ducking unit is an inexpensive mains-power project that is meant to be fitted ahead of the main power amplifier system. The unit has a pair of music input and output terminals, plus a microphone input socket, and its action is such that the microphone signal passes directly through the unit but the amplitude of the music signal is controlled by the amplitude of the microphone signal. When the microphone signal is below a preset threshold value, the music signal passes directly through the unit but when the microphone signal exceeds the threshold value the music signal amplitude is automatically reduced or ducked to a preset level, so that the DJ's voice signal automatically overrides the music.

The switching action of our unit is such that the music signal is faded down smoothly but rapidly as soon as an adequate microphone signal is applied, but returns to its original level relatively slowly (over a period of a few seconds) once the microphone input is removed, thereby giving a smooth

fade-over action. The unit is provided with only two front-panel controls, these being the microphone sensitivity pot, which controls the unit's switching level, and a ducking level pot, which enables the music attenuation level to be preset to any desired value.

The music input levels to the unit should have nominal peak-to-peak values of about 1 V maximum. The microphone input signal also needs a peak-to-peak value of about 1 V nominal, so the microphone signal to the unit will probably have to be taken from a simple preamplifier circuit or be tapped off from an existing preamplifier.

Construction

Before starting the actual construction, check that the PCB slides comfortably into the locating slots that are moulded inside the specified case and, when all is well, proceed with the assembly of the electronic components on the PCB, noting the use of Veropins to facilitate the off-board interwiring.

Next, drill the front panel to accept control pots RV1 and RV2 and LED1 and the set of four input/output (music) sockets, then fit these components into place and wire them to the PCB.

At this stage, temporarily connect mains transformer T1 to the PCB and give the complete unit a functional test, noting that all inputs need nominal amplitudes of 1 V peak-to-peak. Check that the microphone signal effectively passes directly

through the system: check that the music signals pass directly through the system when no microphone signal is present, but duck down to a preset level (adjustable by RV2) when a strong microphone signal is applied. When correct functioning is confirmed, complete the construction as follows.

First, drill a hole in the side of the case to accept the microphone input socket, taking care to allow clearance for the PCB, then wire the socket to RV1. Next, test-bolt transformer T1 into the rear of the case, taking care to scrape the black anodising away from the case below the transformer fixing lugs (to allow a good ground connection). Now complete the transformer connections to the PCB, connect a mains lead to the transformer (taking care to ensure that adequate insulation is provided) and bolt the transformer firmly into place. Finally, drill a hole in the rear panel to allow passage of the mains lead, then screw the front and rear panels into place. The construction is then complete and the unit is ready for use at your next disco session.

BUYLINES

The NE570 can be obtained from Watford Electronics. The case used in the prototype is a Sink Box, available from West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks (order as Sink Box 150K). See our PCB Service advert on page 76 if you don't want to etch the board yourself.

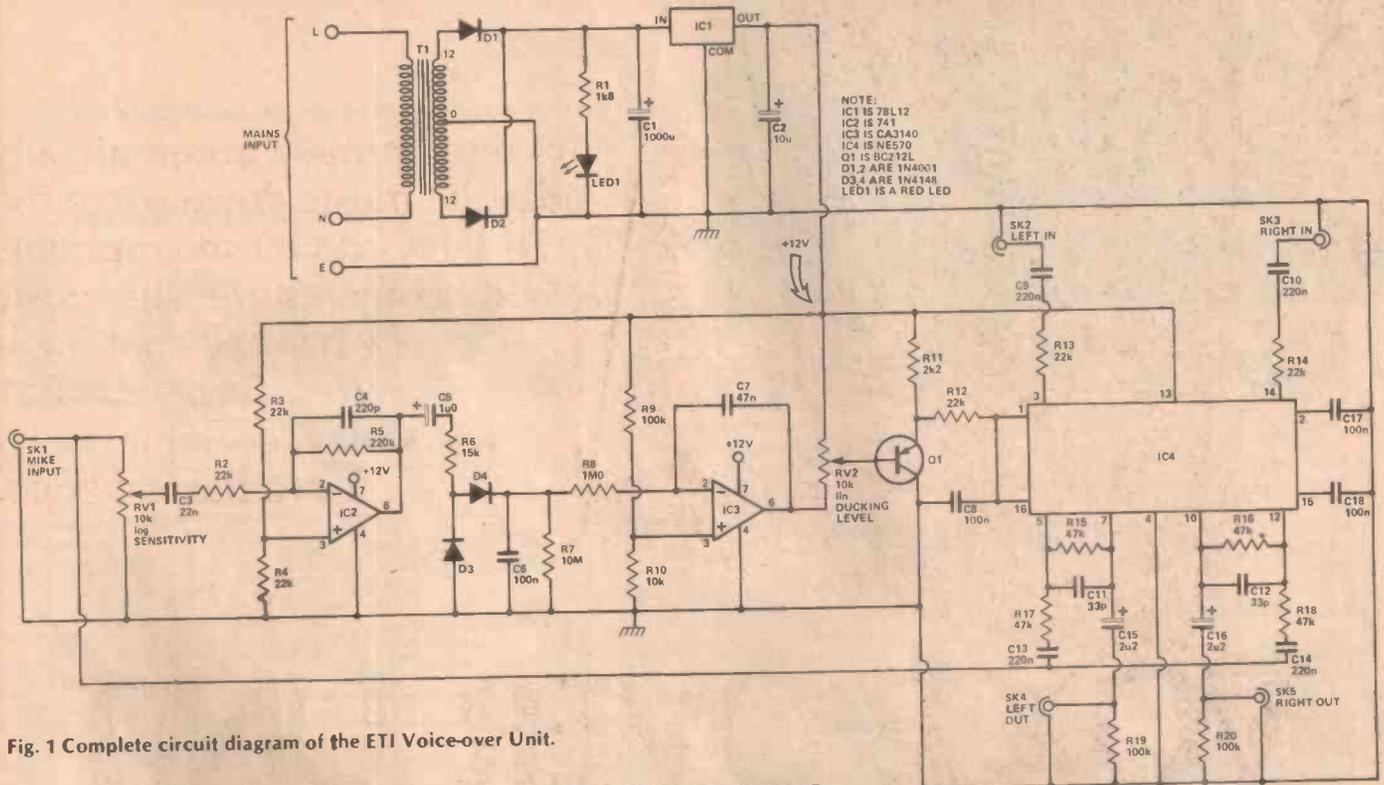


Fig. 1 Complete circuit diagram of the ET1 Voice-over Unit.

HOW IT WORKS

The heart of this unit is IC4 (NE570), which can be regarded as a dual voltage-controlled amplifier. Basically, each half of this chip contains a voltage-controlled variable-gain cell with its output fed to the outside world via a built-in inverting op-amp stage. The gain-cell control voltages are connected to pins 1 (left) and 16 (right) via R12, and the AC (music) input signals are connected to pins 3 (left) and 14 (right); the gain-cell outputs are available at pins 5 (left) and 12 (right) and the op-amp inputs and outputs are available at pins 5 and 7 (left) and 12 and 10 (right) respectively. In our application, the built-in op-amps are each used as two-channel audio mixers, which use the gain-cell outputs as one input and the microphone signal as the other input, and the gains of the gain-cells are controlled from the microphone input signals via the IC2-IC3-Q1 network.

The overall basic circuit action is such that, when no microphone input signal is present, Q1 is cut off and almost the full supply-rail voltage is applied to R12, so the gain-cells each give an overall gain of a few dB to the music signals, which appear at full volume at the two output terminals of IC4. When a high


and continuous microphone signal is present, however, Q1 is driven to saturation and its emitter is pulled down to near-zero volts: under this condition the music signal is reduced to -80 dB but the microphone signal is unattenuated, so only the microphone signal appears at the output. In practice, the actual ducking or music-attenuation level can be fully varied by RV2, so the music and microphone signals can be mixed if required, and the microphone-derived gain-control voltage is arranged to give a fade-over, rather than a switching action, with a simple integrating network, as follows.

The microphone signal is fed to sensitivity control RV1 and is then passed on to speech-bandwidth (350 Hz to 3.5 kHz) amplifier IC2, which has a mid-band gain of 20 dB and is DC-biased for single-supply operation by R3-R4. The AC output signal of IC2 is then effectively peak-detected by the R6-D3-D4-C6-R7 dual-time-constant (quick charge, slow discharge) network and the resulting DC signal is applied to one input of IC3 via R8. IC3 is wired as a voltage comparator, with a fixed reference of 1V1 applied to its non-inverting terminal and with the DC input signal applied

to its inverting terminal via the R8-C7 integration network. This causes the op-amp output to swing linearly (rather than switch abruptly) from one state to the other during the transition period. The output of IC3 is fed to ducking level control RV2 and a proportion of the resulting DC voltage is tapped off from the slider, buffered by emitter follower Q1, and used to provide the DC control voltage to IC4.

The net action of the IC2-IC3-Q1 network is such that the output of IC3 is driven high in the absence of a microphone signal, or low in the presence of a strong microphone signal. When a strong microphone signal first becomes available, the peak detection circuitry rapidly activates IC3, and the IC3 output swings smoothly from the high to the low level, with a time constant of roughly 100 ms (due to R8-C7). When the microphone signal is subsequently removed the output of IC3 swings back to the high level with a time constant of a few seconds (controlled by R7-R8-C7), thus giving a slow fade-back of the music signal.

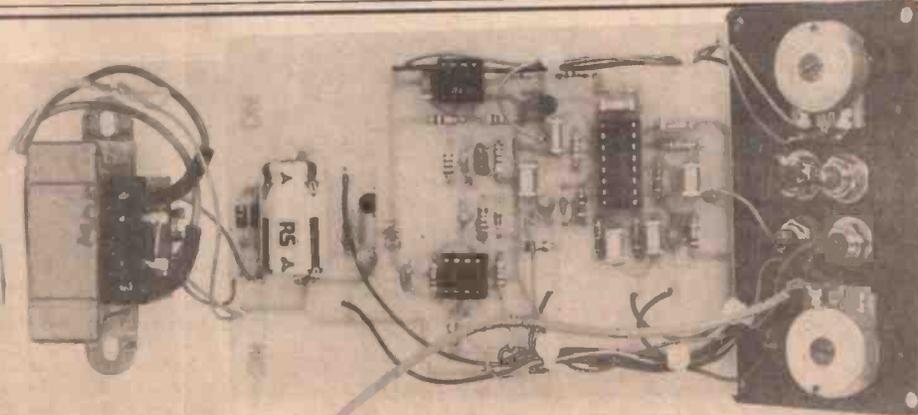The entire stereo voice-over circuit is powered from a single-ended 12 V supply derived from the mains by T1-D1-D2-C1 and voltage regulator IC1.



We've pulled everything out of the Sink Box for this photograph, which shows how the interwiring is made.

The Logic Probes

Spend Less

Test More



LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

£31.00*

Model LP-3 illustrated



LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,


replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £11-92)

£18.00*

Model LP-3 illustrated

*price excluding P.&P. and 15% VAT

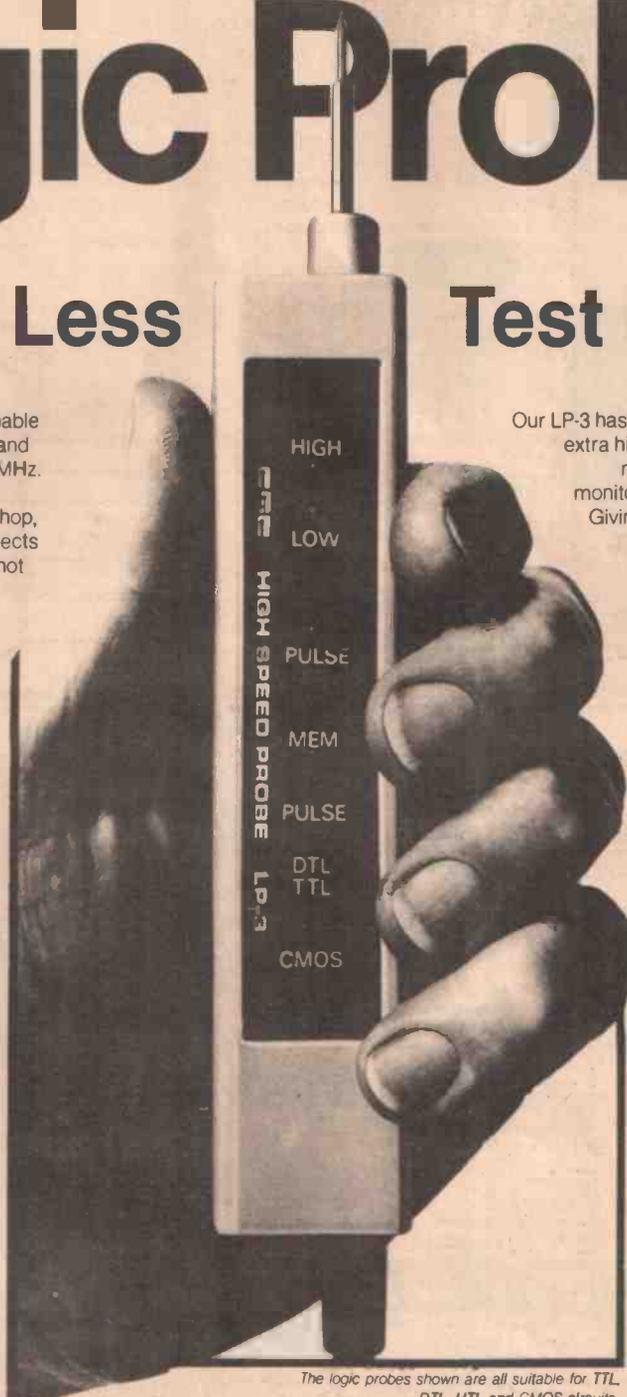

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

£49.00*

Model LP-3 illustrated

The New Pulser DP-1

The Digital Pulser: another new idea from G.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

£51.00*

Model LP-3 illustrated

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 911
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

G.S.C. (UK) Limited, Dept. 911 Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

Prices include P.&P. and 15% VAT

| | | | | | | | | | | | | | | |
|------|--------|-----|------|--------|-----|------|--------|-----|------|--------|-----|-------|--------|-----|
| LP-1 | £37.38 | Qty | LP-2 | £22.14 | Qty | LP-3 | £58.08 | Qty | DP-1 | £60.38 | Qty | LPK-1 | £14.86 | Qty |
|------|--------|-----|------|--------|-----|------|--------|-----|------|--------|-----|-------|--------|-----|

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour, 5 day a week service.

Telephone (0799) 21682 and give us your Barclaycard, Access, American Express
number and your order will be in the post immediately.

For FREE catalogue
tick box

20 POWER AMPS

19 FUNCTIONAL MODULES

DAWA

POWER UP TO 480 WATTS RMS SINGLE CHANNEL



AMPLIFIER WITH HEAT SINK

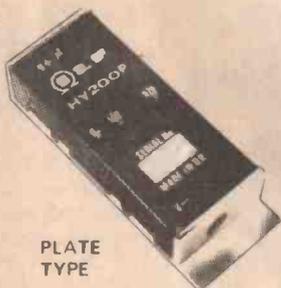


PLATE TYPE



PSU

Which amplifier?

I.L.P. Amplifiers now come in three basic types, each of which is available with or without heatsink. Having decided the system you want - home hi fi (models HY30, 60 or 120 for example), super quality hi fi with extra versatility (MOS120, MOS200) or Disco PA Guitar (HD120, HD200 or HD400) you will then decide whether amplifiers housed within their own heatsinks or plate amplifiers for bolting to a metal chassis will suit. With choice such as this and a brilliant new range of I.L.P. functional modules to choose from you now have the chance to build the finest audio system ever offered to the constructor.

| BIPOLAR Standard, with heatsinks | | | | | | | | | | Without heatsinks | | | | |
|----------------------------------|------------------------|--------------------|----------------------|------------------------|------------|--------|--------|-------|--------------|-------------------|--------|--------|-------|--|
| MODEL NUMBER | OUTPUT POWER Watts rms | DISTORTION | | SUPPLY VOLTAGE TYP/MAX | SIZE mm | WT gms | PRICE | VAT | MODEL NUMBER | SIZE in mm | WT gms | PRICE | VAT | |
| | | T.N.O. Typ at 1kHz | I.M.O. 60HZ 7kHz 4:1 | | | | | | | | | | | |
| HY30 | 15w 4 8Ω | 0.015% | <0.006% | -18-20 | 76x68x40 | 240 | £7.29 | £1.09 | | | | | | |
| HY60 | 30w 4 8Ω | 0.015% | <0.006% | -25-30 | 76x68x40 | 240 | £8.33 | £1.25 | | | | | | |
| HY120 | 60w 4 8Ω | 0.01% | <0.006% | -35-40 | 120x78x40 | 410 | £17.48 | £2.62 | HY120P | 120x26x40 | 215 | £15.50 | £2.33 | |
| HY200 | 120w 4 8Ω | 0.01% | <0.006% | -45-50 | 120x78x50 | 515 | £21.21 | £3.18 | HY200P | 120x26x40 | 215 | £18.46 | £2.77 | |
| HY400 | 240w 4Ω | 0.01% | <0.006% | -45-50 | 120x78x100 | 1025 | £31.83 | £4.77 | HY400P | 120x26x70 | 375 | £28.33 | £4.25 | |

Protection: Load line, momentary short circuit (typically 10 sec) Slew rate: 15V/μs Rise time: 5μs
S/N ratio: 100db Frequency response: 3dB: 15Hz-50kHz
Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω 100Hz) >400

| HEAVY DUTY with heatsinks | | | | | | | | | | Without heatsinks | | | | |
|---------------------------|------------------------|--------------------|----------------------|------------------------|------------|--------|--------|-------|--------------|-------------------|--------|--------|-------|--|
| MODEL NUMBER | OUTPUT POWER Watts rms | T.N.O. Typ at 1kHz | I.M.O. 60HZ 7kHz 4:1 | SUPPLY VOLTAGE TYP/MAX | SIZE mm | WT gms | PRICE | VAT | MODEL NUMBER | SIZE in mm | WT gms | PRICE | VAT | |
| HD120 | 60w 4 8Ω | 0.01% | <0.006% | -35-40 | 120x78x50 | 515 | £22.48 | £3.37 | HD120P | 120x26x50 | 265 | £19.84 | £2.98 | |
| HD200 | 120w 4 8Ω | 0.01% | <0.006% | -45-50 | 120x78x60 | 620 | £27.38 | £4.11 | HD200P | 120x26x50 | 265 | £23.63 | £3.54 | |
| HD400 | 240w 4Ω | 0.01% | <0.006% | -45-50 | 120x78x100 | 1025 | £38.63 | £5.79 | HD400P | 120x26x70 | 375 | £34.28 | £5.14 | |

Protection: load line, PERMANENT SHORT CIRCUIT (ideal for disco group use should evidence of short circuit not be immediately apparent). The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs. as for standard types.

| MOSFET Ultra-Fi, with heatsinks | | | | | | | | | | Without heatsinks | | | | |
|---------------------------------|------------------------|--------------------|----------------------|------------------------|------------|--------|--------|-------|--------------|-------------------|--------|--------|-------|--|
| MODEL NUMBER | OUTPUT POWER Watts rms | T.N.O. Typ at 1kHz | I.M.O. 60HZ 7kHz 4:1 | SUPPLY VOLTAGE TYP/MAX | SIZE mm | WT gms | PRICE | VAT | MODEL NUMBER | SIZE in mm | WT gms | PRICE | VAT | |
| MOS120 | 60w 4 8Ω | <0.005% | <0.006% | -45-50 | 120x78x40 | 420 | £25.88 | £3.88 | MOS120P | 120x26x40 | 215 | £23.32 | £3.50 | |
| MOS200 | 120w 4 8Ω | <0.005% | <0.006% | -55-60 | 120x78x80 | 850 | £33.46 | £5.02 | MOS200P | 120x26x80 | 420 | £28.53 | £4.28 | |
| MOS400 | 240w 4Ω | <0.005% | <0.006% | -55-60 | 120x78x100 | 1025 | £45.39 | £6.81 | MOS400P | 120x26x100 | 525 | £38.91 | £5.84 | |

Protection: Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).
Ultra-fi specifications:
Slew rate: 20V/μs Rise time: 3μs S/N ratio: 100db Frequency response: 3dB: 15Hz-100kHz
Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω 100Hz) >400

| POWER SUPPLY UNITS | | | |
|--------------------|--|--------|-------|
| MODEL NO | FOR USE WITH | PRICE | VAT |
| PSU30 | 15V combinations of HY6 66 series to a maximum of 100mA or one HY67 The following will also drive the HY6 66 series except HY67 which requires the PSU30. | £4.50 | £0.68 |
| PSU36 | 1 or 2 HY30 | £8.10 | £1.22 |
| PSU50 | 1 or 2 HY60 | £10.94 | £1.64 |
| PSU60 | 1 x HY120 HY120P HD120 HD120P | £13.04 | £1.96 |
| PSU65 | 1 x MOS120 1 x MOS120P | £13.32 | £2.00 |
| PSU70 | 1 or 2 HY120 HY120P HD120 HD120P | £15.92 | £2.39 |
| PSU75 | 1 or 2 MOS120 MOS120P | £16.20 | £2.43 |
| PSU90 | 1 x HY200 HY200P HD200 HD200P | £16.20 | £2.43 |
| PSU95 | 1 x MOS200 MOS200P | £16.32 | £2.45 |
| PSU180 | 2 x HY200 HY200P HD200 HD200P or 1 x HY400 1 x HY400P HD400 HD400P | £21.34 | £3.20 |
| PSU185 | 1 or 2 MOS200 MOS200P 1 x MOS400 1 x MOS400P | £21.46 | £3.22 |

All models except PSU30 and PSU36 incorporate our own toroidal transformers.

FP480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by I.L.P. for use with any two power amplifiers of the same type to double the power output obtained and will function with any I.L.P. power supply. In totally sealed case, size 45 x 50 x 20mm, with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%.
Price: £4.79 + 72p. V.A.T.

I.L.P. ELECTRONICS LTD.
FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP
Telephone (0227) 54778 (Technical (0227) 64723) Telex 965780
Available also from MARSHALLS, TECHNOMATIC, WATFORD ELECTRONICS and certain other selected retailers.

GOODS BY MAIL ORDER DESPATCHED WITHIN 7 DAYS

OF A NEW ERA



Which modules?

In launching eighteen different units all within amazingly compact cases to help make complete audio systems using I.L.P. power amplifiers, we bring the most exciting, the most versatile modular assembly scheme ever for constructors of all ages and experience. Study the list - see how these modules will combine to almost any audio project you fancy - and remember *all I.L.P. modules are compatible with each other*, they connect easily. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm. They are so reliable that all I.L.P. modules carry a 5 year no quibble guarantee.



| MODEL NO. | MODULE | DESCRIPTION/FACILITIES | CURRENT REQUIRED | PRICE | VAT |
|-----------|-----------------------------|---|------------------|-----------------|-------|
| HY6 | MONO PRE AMP | Mic/Mag. Cartridge/Tuner/Tape/Aux + Volume/Bass/Treble | 10mA | £6.44 | £0.97 |
| HY7 | MONO MIXER | To mix eight signals into one | 10mA | £5.15 | £0.77 |
| HY8 | STEREO MIXER | Two channels, each mixing five signals into one | 10mA | £6.25 | £0.94 |
| HY9 | STEREO PRE AMP | Two channels mag. Cartridge/Mic + Volume | 10mA | £6.70 | £1.01 |
| HY11 | MONO MIXER | To mix five signals into one + Bass/Treble controls | 10mA | £7.05 | £1.06 |
| HY12 | MONO PRE AMP | To mix four signals into one + Bass/Mid-range/Treble | 10mA | £6.70 | £1.01 |
| HY13 | MONO VU METER | Programmable gain/LED overload driver | 10mA | £5.95 | £0.89 |
| HY66 | STEREO PRE AMP | Mic/Mag. Cartridge/Tape/Tuner/Aux + Volume/Bass/Treble/Balance | 20mA | £12.19 | £1.83 |
| HY67 | STEREO HEADPHONE | Will drive headphones in the range of 4Ω - 2KΩ | 80mA | £12.35 | £1.85 |
| HY68 | STEREO MIXER | Two channels, each mixing ten signals into one | 20mA | £7.95 | £1.19 |
| HY69 | MONO PRE AMP | Two input channels of mag. Cartridge/Mic + Mixing/Volume/Treble/Bass | 20mA | £10.45 | £1.57 |
| HY71 | DUAL STEREO PRE AMP | Four channels of mag. Cartridge/Mic + Volume | 20mA | £10.75 | £1.61 |
| HY72 | VOICE OPERATED STEREO FADER | Depth/Delay | 20mA | £13.10 | £1.97 |
| HY73 | GUITAR PRE AMP | Two Guitar (Bass/Lead) and Mic + separate Volume/Bass/Treble + Mix | 20mA | £12.25 | £1.84 |
| †HY74 | STEREO MIXER | Two channels, each mixing five signals into one + Treble/Bass | 20mA | £11.45 | £1.72 |
| †HY75 | STEREO PRE AMP | Two channels, each mixing four signals into one + Bass/Mid-range/Treble | 20mA | £10.75 | £1.61 |
| †HY76 | STEREO SWITCH MATRIX | Two channels, each switching one of four signals into one | 20mA | To be announced | |
| †HY77 | STEREO VU METER DRIVER | Programmable gain/LED overload driver | 20mA | £9.25 | £1.39 |

The modules are encapsulated and include latest design high quality clip-on edge connectors.

For easy mounting we recommend B6 Mounting board for modules HY6 - HY13 78p + 12p. V.A.T.

B66 Mounting board for HY66 - HY77 99p + 13p. V.A.T.

All I.L.P. modules include full connection data.

I.L.P. Products are of British Design and Manufacture.

All the above modules operate from 15V minimum to 30V maximum - higher voltages being accommodated by use of dropout resistors. HY67 can only be used with the PSU 30 power supply unit.

† Ready September - may be ordered now

Now turn to our ad. on page 85

TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. If sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order. When ordering, U.K. customers must include the appropriate V.A.T. as shown. PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED.

ALL WITH I.L.P.'S 5 YEAR NO QUIBBLE GUARANTEE

To: I.L.P. ELECTRONICS LTD, ROPER CLOSE CANTERBURY CT2 7EP

Please supply.....

Total purchase price £.....

I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.....

NAME.....

ADDRESS.....

Signature.....

ALL U.K. ORDERS DESPATCHED POST FREE

ET1/11

OF RECEIVING YOUR ORDER

FASTER- THAN- LIGHT TRAVEL

Captain Kirk used it, the *Nostromo* needed it, and the Empire couldn't exist without it. But A.S. Lipson, light-sabre in one hand and phaser in the other, lays waste to the plots of countless space operas.

One of the most popular themes chosen by science fiction writers is that of the Galactic Empire. The scene is thus; centuries in the future, man has spread out through the galaxy, colonising planets in other star systems, and has built up an empire, simultaneously solving the problem of overpopulation on Earth. But the stars are all an awfully long way away — even the relatively close ones. If a light year is the distance light travels in a year (and light travels at about 299,793,000 metres per second, or, if you prefer, 186,000 miles per second — fast enough to circle the equator seven and a half times in one second!), so even the nearest star is nearly four and a half light years away. The distances from us of the 10 nearest stars are given in Table 1.

TABLE 1

| Star | Distance In Light Years |
|--------------------------|-------------------------|
| Proxima Centauri | 4.3 |
| Alpha Centauri (A and B) | 4.4 |
| Barnard's star | 5.9 |
| Wolf 359 | 7.6 |
| HD 95735 | 8.1 |
| Sirius (A and B) | 8.6 |
| UV Ceti (A and B) | 8.9 |
| Ross 154 | 9.5 |
| Ross 248 | 10.3 |
| Epsilon Eridani | 10.8 |

As you can see, the stars seem uncomfortably far away. If we start to consider stars at the far side of the galaxy, we find that we are talking about distances of the order of 80,000 light years! The problem with such unimaginably great distances, of course, is that travelling them takes rather a long time. If we are to colonise the stars, then either we need to develop some means of travelling faster than light, or our astronauts are going to get either very bored or very dead on the way to wherever they're going.

Conversation Stopper

Even supposing that we could overcome the problem of boredom, there would still be a communication problem. Supposing you wish to talk to old Aunt Ethel at Alpha Centauri (say); once you've said 'hello' over the radio, it's another 4.4 years before Aunt Ethel will hear you, because radio signals travel at

the same speed as light, and Alpha Centauri is 4.4 light years away. It takes the same time for the reply to get back. All in all, it takes nearly nine years to get a reply, even from the nearest star systems! This is clearly no way to run a conversation. The same problem also operates with any interstellar communication. Radio, light, or anything slower, just isn't fast enough for the sort of communication needed for our new Galactic Civilisation. Unfortunately, we don't have anything faster.

So what's the big problem? We can just let the boffins get on with it, and they can invent us a faster-than-light (FTL) drive! Or can they...?

Speed Limit

There is, of course, a slight snag (nothing's ever *that* easy). In 1905, a gentleman by the name of Albert Einstein published a paper laying down the foundations of what is now known as Special Relativity. Among the many interesting results of special relativity is the following — it is impossible to accelerate any body to the speed of light, let alone beyond. You can get close; in big particle accelerators, electrons have been made to move at more than 99.99% of light velocity — but never quite 100%. This obviously creates a slight problem with our ideas about interstellar travel, and unfortunately, there is now relatively (oh, dear) little doubt that Einstein's results are correct. They are among the most thoroughly tested conclusions in the history of physics, and so far no-one has been able to fault them. There have been one or two occasions when people *thought* that they'd proved Einstein wrong, but it always turned out that they had mucked up their experiments, or misinterpreted their readings. So far Einstein seems quite safe.

While destroying most of our hopes of an FTL drive, relativity also provided us with a partial solution to our problems. You remember that one of the reasons we wanted a faster-than-light drive in the first place was to reduce the length of time that our travellers would have to spend on the journey, and hence reduce not only the boredom of such voyages, but also the amount of food needed (not forgetting little things like oxygen, as well). Well, we may not need a faster-than-light drive after all! Because according to relativity theory, when you travel at high velocities, time starts to do funny things. Measured by an observer on Earth, time on a fast-travelling spaceship appears to have slowed down. (A more detailed treatment of this is really the province of another article, so we won't go into it very thoroughly.) If someone was to set off in a

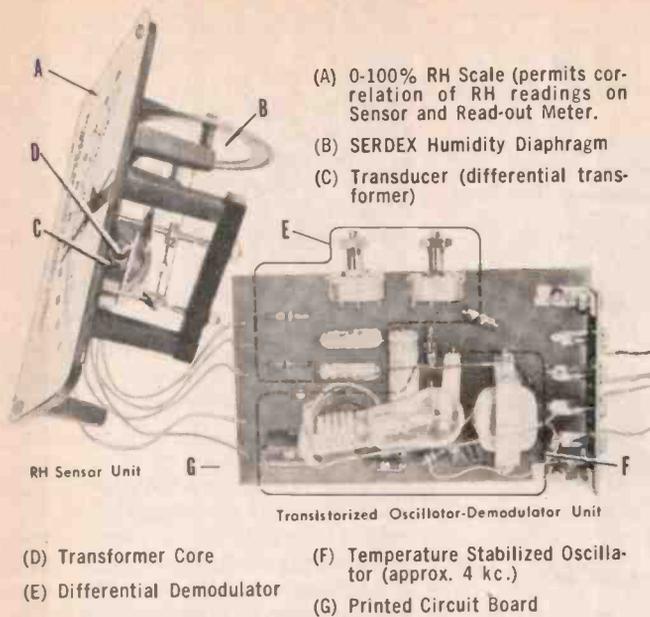


Fig. 2. Operation of this SERDEX humidity sensor is based upon a hygroscopic animal membrane forming a diaphragm.

RELATIVE EQUILIBRIUM MOISTURE (rem or em) — in the paper industry, it is the ability of the fibres to lose or absorb water (the sorption process) that decides the shrinkage, tearability, etc. Equilibrium will eventually occur between the air humidity and the paper content. To make it clear that it is the paper moisture content that is stated, em is quoted. Hence a lower em than RH means the paper takes in moisture.

LIMITATIONS OF DEW POINT MEASUREMENT

Not all moisture measurements make direct use of the dew point phenomena but it is instructive to consider the limitations of the process for the effects are present in most procedures.

THE KELVIN EFFECT — In 1870, Lord Kelvin arrived at the conclusion that the vapour pressure over a concave liquid surface is less than that over a plane surface of the same material. Water condensing on a surface forms droplets which produce a curved interface surface with the surrounding vapour. It has not been an easy matter to prove Kelvin's theory, for the effect is small, but convincing electron microscope studies of evaporating lead, carried out at Imperial College in London, have shown it to be true for lead and gold. The Cambridge Systems Company of Massachusetts have estimated the depression in dew point temperature due to 30 μm drops size condensation as 0.005K. Few people would find the Kelvin effect error a problem.

THE RAOULT EFFECT — In 1887 Raoult produced a law governing the

RELATIVE HUMIDITY, RH for short — this expresses the amount of water vapour present, compared with the maximum that could be at the temperature of interest. (The quantity of water vapour present would only apply for a stated temperature). RH is expressed as a percentage. For example, a dry day in the summer could be as low as 20% whereas when it is actually raining, it rises to 100%. The need for this relative unit occurs because many processes do not depend upon the absolute water content, but on the amount that could be absorbed or liberated from the air. RH is probably the most commonly used unit outside of process control areas.

moisture can be taken up so the bulb is not cooled at all. (The same reason is why evaporative air coolers do not give as much cooling in humid weather). This concept is used in the wet-and-dry bulb hygrometer.

MIXING RATIO — the ratio of weight of water vapour to dry carrier gas.

POUNDS/KILOGRAMS PER HOUR — this expresses the absolute amount of water vapour supplied per hour. For example, heat treatment of metals requires knowledge of the water content in the furnace as this controls the carburizing process reaction rate.

PARTS PER MILLION, PPM — this expresses the water content by virtue of the weight of water, PPM_W or its volume, PPM_V , so it is either the ratio of the partial pressure of the water vapour to the total pressure, or else the PPM_V value multiplied by the ratio of the molecular weights of water to the other gas to yield the first value. Care is needed to define which is intended, for both units are dimensionless, and appear the same unless qualified with a (by weight) or (by volume) statement.

WET BULB TEMPERATURE (no accepted abbreviation exists) — if a thermometer has its sensing area wetted with water (usually with a saturated wick) and air is passed rapidly over it, the thermometer reads a value less than that of an identical dry thermometer by an amount depending upon the relative humidity. If the air is 100% saturated, no more

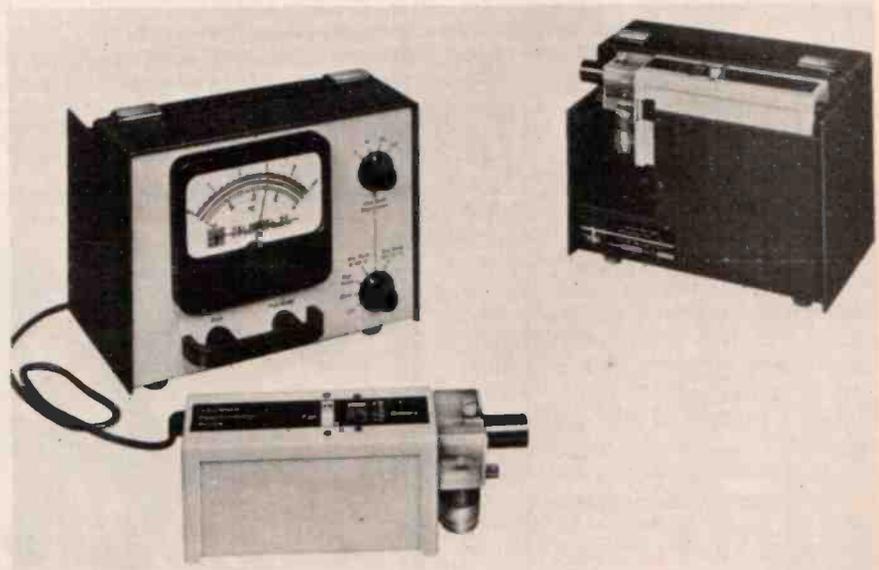


Fig. 3. The Yellow Springs Instrument Co. aspirated psychrometer. The righthand view shows the unit packed for transportation. Thermistors are used as temperature sensors.

Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

Kit: £49.⁹⁵


Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.

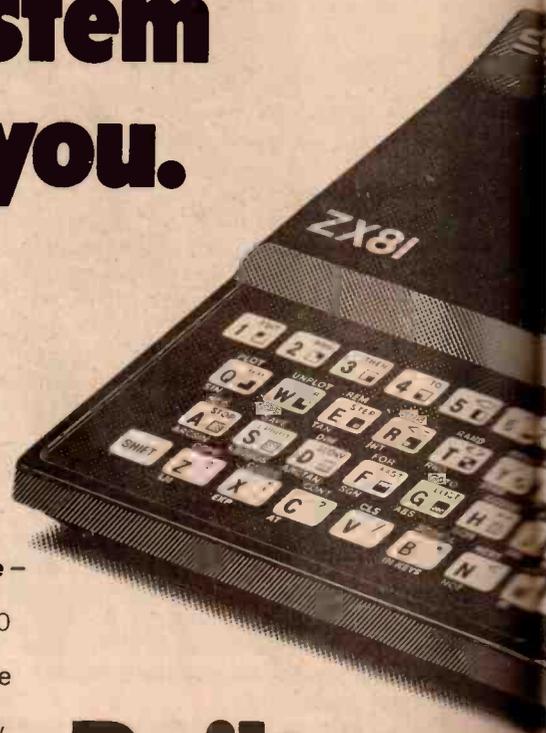

Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



Computer-



Available now - the ZX Printer for only £49.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha- numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.

| Qty | Item | Code | Item price £ | Order Total £ |
|-----|---|------|-----------------|---------------------|
| | Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor. | 12 | 49.95 | |
| | Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor. | 11 | 69.95 | |
| | Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated). | 10 | 8.95 | |
| | 16K-BYTE RAM pack. | 18 | 49.95 | |
| | Sinclair ZX Printer. | 27 | 49.95 | |
| | 8K BASIC ROM to fit ZX80. | 17 | 19.95 | |
| | Post and Packing. | | | 2.95 |

Please tick if you require a VAT receipt

TOTAL £

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

*Please charge to my Access/Barclaycard/Trustcard account no.

*Please delete/complete as applicable

Please print.

Name: Mr/Mrs/Miss

Address:

FREEPOST - no stamp needed. Offer applies to UK only.

ET1 11

sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: (0276) 66104 & 21282.

electronics today international BOOK SERVICE

How to order; Make cheques payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, Sales Office, 145 Charing Cross Road, London WC2. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS

Beginners Guide to Electronics Squires £4.50
Beginners Guide to Transistors Reddihough £4.50
Beginners Guide to Integrated Circuits Sinclair £4.50
Beginners Guide to Radio King £4.50
Beginners Guide to Audio Sinclair £4.50
Introducing Amateur Electronics Sinclair £4.50
Understanding Electronic Circuits Sinclair £5.10
Understanding Electronic Components Sinclair £5.10

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filter Cookbook £11.30
IC Timer Cookbook £7.65
IC Op Amp Cook Book £10.70
TTL Cookbook £7.55
MC 6809 Cookbook Carl D. Warren £5.30
PLL Synthesiser Cookbook Kinley £5.85
8085A Cookbook Titus £10.05

APPLICATIONS

How To Build Electronic Kits Chapel £3.25
110 Electronic Alarm Projects Marston £5.25
110 Semiconductor Projects for the Home Constructor Marston £5.25
110 Integrated Circuit Projects for the Home Constructor Marston £5.25
110 Thyristor Projects Using SCRs Marston £5.25
110 Waveform Generator Projects Marston £5.25
99 Practical Electronic Projects Friedman £4.20

COMPUTING & MICROPROCESSORS

What is a Microprocessor 2 cassette tapes plus a 72-page book £10.00
Beginners Guide to Computers and Microprocessors with projects £6.05
Basic Computer Games Ahl £6.05
Basic for Home Computers Albrecht £6.60
Illustrating Basic Alcock £4.25
Troubleshooting Microprocessors and Digital Logic Goodman £5.90
Z-80 Microcomputer Handbook £7.75
Microprocessors in Instruments and Control Bibbero £13.10
Basic Basic Coan £7.25
Advanced Basic Coan £6.40
1001 Things to do with your Personal Computer Sawusch £6.00
Microcomputers, Microprocessors, Hardware, Software and Applications Hibern £17.40
Microprocessor Systems Design Klingman £18.80
Introduction to Microprocessors Leventhal £11.25
Microprocessor Technology, Architecture and Applications £11.30
Basic with Style Nagin £4.50
Microcomputer Design Ogdin £7.45
Hands on Basic with a Pet Packham £11.95
6800 Software Gourmet Guide and Cookbook Scelbi £9.20
8080 Software Gourmet Guide and Cookbook Scelbi £9.20
The 8080A Bugbook Rony £8.35
8080/8085 Software Design Titus £7.60
How to Design, Build and Program your own Working Computer System £7.10
Your Own Computer Waite £2.25
Microcomputer Interfacing Handbook A/D & D/A £6.35
Crash Course in Microcomputers Frenzel £12.40
Musical Applications of Microprocessors Chamberlain £17.50
The Pascal Handbook Tiberghien £11.35
50 Basic Exercises Lamotier £9.50
Learning Basic with the Sinclair ZX80 £4.95
Microprocessors for Hobbyists Coles £4.25
Introduction to Microcomputer Programming Sanderson £5.25
Microprocessors and Microcomputers for Engineering Students and Technicians Wooland £5.95
Using CP/M - Self Teaching Guide Ashley Fernandez £6.95
Digital Counter Handbook Frenzel £8.40
33 Challenging Computer Games for TRS80-Apple-Pet Chance £5.75
How to Build Your Own Working Robot Pet Dalesta £5.75
Microprocessor and Digital Computer Technology £16.00
Guidebook to Small Computers Barden £4.20
How to Debug Your Personal Computer Huffman £6.30
How to Troubleshoot and Repair Microcomputers Leuk £6.30
6809 Microcomputer Programmes and Interfacing with Experiments Staugaard £10.20
Wordprocessors Programmed. Training Guide with Practical Application £
Digital Circuits and Microcomputers Johnson £9.75
Experiments in Artificial Intelligence for Small Computers £5.60

LOGIC

Designing with TTL Integrated Circuits Texas Instruments £10.95
How to Use IC Circuit Logic Elements Stratel £4.85
110 CMOS Digital IC Projects for the Home Constructor Marston £5.25
Digital ICs - How They Work and How to Use Them Barber £16.30
Electronic Design with Off the Shelf ICs Meikson £6.30
Getting Acquainted with the IC Turner £4.20

TEST INSTRUMENTS

The Oscilloscope in Use Sinclair £4.00
How to Get More Out of Low-cost Electronic Test Equipment Genn £5.50

OP-AMPS

Applications of Operational Amplifiers Graeme £9.20
110 Operational Amplifier Projects for the Home Constructor Marston £5.25
Designing with Operational Amplifiers Burr Brown £26.50
Design of Op-Amp Circuits with Experiments £6.80
Operational Amplifiers. Design and Applications Tobery £8.95
Op-Amp Handbook Hughes £15.50

COMMUNICATIONS

Digital Signal Processing. Theory and Applications Rabiner £24.40
Electronic Communication Systems Kennedy £8.95
Principles of Communication Systems Taub £8.40

THEORY

Introduction to Digital Filtering Bognor £12.25
Transistor Circuit Design Texas Instruments £10.95
Electronic Circuit Design Handbook Design of active filters, with experiments: Berlin £6.80

REFERENCE

Electronic Engineers Reference Book Turner £41.00
Electronic Components Colwell £4.00
Electronic Diagrams Colwell £4.00
International Transistor Selector Towers £10.70
International FET Selector Towers £4.60
International Op-Amp Linear IC Selector Towers £8.00
International Microprocessor Selector Towers £16.00
Dictionary of Audio - Radio and Video Roberts £16.00
Dictionary of Electronics Amos £16.00
Dictionary of Electrical Engineering Amos £16.00
Dictionary of Telecommunications Amos £16.00
Giant Book of Electronic Circuits Collins £5.75
World Radio/TV Handbook Vol. 35 1981 £10.50
How to Build Electronic Projects Malcolm £6.45
Modern Electronic Circuit Reference Manual Marcus £33.50

GENERAL ELECTRONICS

Electronic Fault Diagnosis Sinclair £4.00
Printed Circuit Assembly Hughes and Colwell £4.00
Electronic Musical Instruments Crowhurst £4.25
Electronic Music Synthesizers Horn £4.60
Videocassette Recorders. Theory and Servicing McGinty £10.50
Practical Electronic Maths. Veley and Dulin £6.95
Electronic Circuits. Discrete and Integrated Schilling, Belove £7.25
Electronic Troubleshooting Handbook Genn £5.60
Experimenters Guide to Solid State Electronic Projects Barber £5.60
Practical Handbook of Solid State Troubleshooting Genn £11.00
Practical Solid State Circuit Design Oleksy £7.00
The Art of Electronics Horowitz £14.10
Complete Guide to Reading Schematic Diagrams Douglas Young £5.60

Fallen behind recent advances?

Just starting out?

Need a decent reference book?

ETI Book Service provides an easy way of getting your hands on the right title.

MUSIC PROCESSOR



We're pretty generous people here at ETI. We don't just give you an echo unit, or a phaser, or a flanger, or a chorus unit — this project has got the lot! Design by Ray Marston. Development by Steve Ramsahadeo.

The ETI Music Processor is designed to add any of four switch-selected effects to any musical or audio signal, these effects being double-tracking (mini-echo), auto-double-tracking or ADT (mini-chorus effect), phasing and flanging. None of these effects can be claimed as unique; it is, however, pretty rare to be able to get all four effects from a single unit. The unique feature of our unit, however, is the way in which its scanning circuit works.

In conventional ADT, phasing and flanging units a low-frequency oscillator is used to scan the selected effect up and down the audio band, and in all the commercial units that we've seen this oscillator simply free-runs so that, for example, a phaser unit phases continuously and thus eventually tends to produce a rather tedious musical effect. Our unit is different, because the scan oscillator can be operated in one of three basic modes — manual scan, one-shot scan, or free-run scan. In the first two of these modes the scanning can be initiated by either a push-button or a foot switch, and in each of the three modes a range of four different scan speeds are available.

A Passing Phase

Because of the unusual scanning generator used in our unit the processor produces the kinds of

operating effects that all musicians dream of. Suppose, for example, that you are using the unit as a phaser in the one-shot scanning mode; in this case your musical instrument will normally play straight through the unit with no special effects being added. As soon as you want to add the phasing effect to a musical passage you simply press the scan button or the foot switch once, at which point the unit will noiselessly switch over (using built-in electronic switches) to the phasing mode until one complete phase-down/phase-up scan cycle is complete, and then revert to the straight-through mode.

A similar effect is obtained in the manual scan mode, except that the unit scans down only while the scan button or foot switch is held closed and scans back up again as soon as the button/foot switch is released. A red LED illuminates if the unit reaches a self-imposed limit in the scan-down mode, and a green LED illuminates when the scanner reaches its upper limit and returns to the straight-through or normal mode of operation.

Similar kinds of action occur when the processor is used in the ADT and flanging modes, with special effects being imposed on the music only when the scanning action is initiated by the press button or foot switch. When the scanner is used in the free-running mode, of course, the special effects are imposed continuously, as in a conventional unit, and when the unit is

used in the simple double-tracking (echo) mode the scan generator is switched out of circuit and the echo is permanently present.

MP Use

The complete processor unit is mains-powered, contains a total of 10 ICs, and is easy to use: the music signal (with a nominal peak-to-peak amplitude of at least a few hundred millivolts) is simply connected to the unit's input, and the output of the unit is then taken to a suitable power amplifier. The desired musical effects and scan speed and mode are then selected by panel-mounted switches and the input level is adjusted by RV1 so that straight-through operation is obtained with minimal distortion. When the unit is used in the double-tracking and ADT modes, the echo depth can be varied with RV2: when the unit is used in the flanging mode, the flanging level or depth is varied with RV3.

The complete unit can, if desired, be used to add the specified effects to virtually any audio signal source. The unit does, however, generate a small amount of RFI, and if it is to be used with a radio or tuner-derived audio signal it may be necessary to fit the unit into a well screened metal case, to avoid interference; the unit is provided with a simple RF input filter (activated by a slide switch) that is intended for use with radio-derived input signals.


Construction

There should be no problems in the construction of this project provided you follow the overlay carefully, paying particular attention to the orientation of the electrolytic capacitors and semiconductor devices. All components are mounted on a single PCB except for R24 and C7, which are hardwired between SK1 and SW3.

Start construction by assembling the power supply components. Be sure to insulate the mains terminals on the PCB and SW5 with rubber or PVC sleeving. When this section is built, connect a voltmeter across the output and check you get a reading of 15 V. The remainder of the circuit can now be built.

The Music Processor project is not particularly difficult to build: the circuit does, however, incorporate a couple of preset pots and access to a scope and an audio generator is desirable when adjusting one of these components, so that optimum phasing effects can be obtained.

To adjust PR1, connect a DC voltmeter between PR1 slider and the +15 V rail and then adjust PR1 for a reading of precisely 5 V. To adjust PR2, switch the unit to the double-tracking mode, set RV2 (echo depth) to mid value, and apply a 1 kHz (nominal) sine wave signal of about 1 V peak-to-peak to the unit's input. Use a scope to monitor the two signals on the inputs of R46 and R47 and then adjust PR2 until the magnitudes are equal.

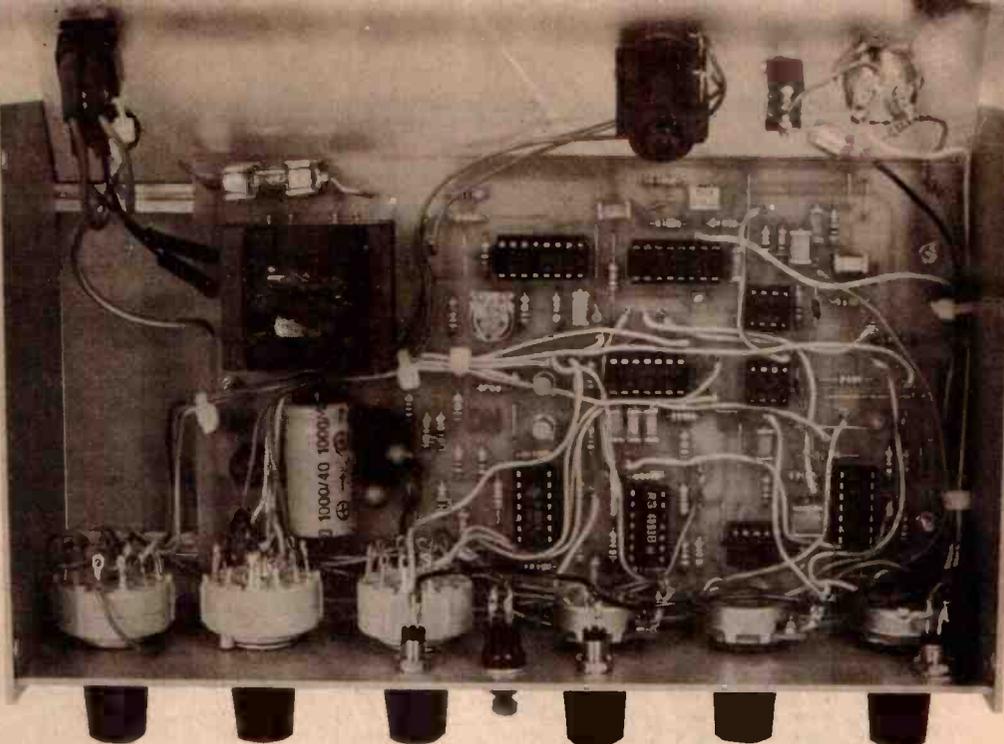

Inside the Music Processor. It may look as if we had an accident with a plate of spaghetti, but you shouldn't have any problems if you follow the overlay methodically.

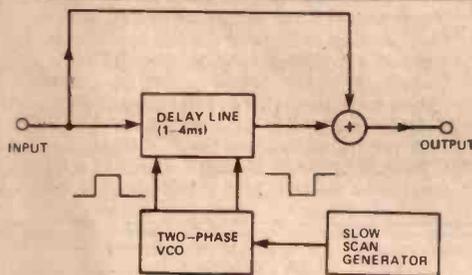


Fig. 3 With a shorter delay time the Fig. 2 circuit becomes a phaser.

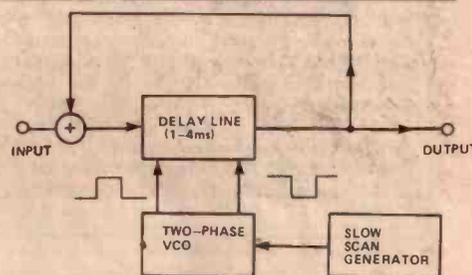


Fig. 4 This configuration of the circuit elements causes flanging.

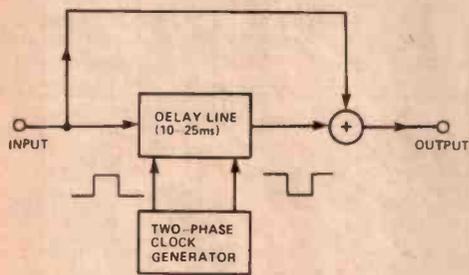


Fig. 1 Block diagram of the double-tracking or echo circuit.

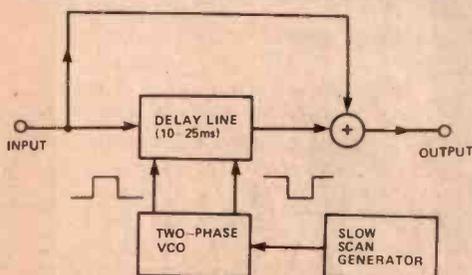


Fig. 2 Block diagram of the auto-double-tracking or mini-chorus circuit.

HOW IT WORKS

BASIC PRINCIPLES

The ETI Music Processor uses a number of basic circuit elements, such as a CCD delay line, a VCO, a couple of audio mixers and low pass filters and a special slow scan generator to implement the effects that are available from the unit. In each of the four basic operating modes of the unit (double-tracking, ADT, phasing and flanging), these elements are configured by electronic switches to give the desired mode of circuit operation. Figures 1 to 4 show the four basic configurations of the unit.

Thus, in the basic double-tracking mode (Fig. 1) the delay line is clocked by a fixed-frequency two-phase generator to give an overall delay in the range 10-25 ms. The audio input signal splits two ways as it enters the unit, one path going directly to one input of an audio mixer and the other going to the remaining mixer input via the delay line. Consequently, the output of the mixer consists of two identical audio signals that are time-displaced by a fixed amount, thus giving a simple echo or double-tracking effect.

The ADT (automatic double-tracking) circuit of Fig. 2 differs from that of Fig. 1 in that the fixed-frequency two-phase clock generator is replaced by a two-phase VCO (voltage controlled oscillator) that can have its frequency (and thus the delay time of the line) varied using a slow scan generator. The ear perceives the audio output signals of this circuit as two distinct signals with a variable time-displacement, this being the so-called 'chorus' effect.

The phasing circuit of Fig. 3 differs from the ADT circuit only in that the VCO frequency is speeded up to give line time-delays in the range 1-4 ms. The effects of this time-delay reduction are quite dramatic; the ear no longer perceives the unit's output as two distinct signals. As the direct and delayed signals are added together in the audio mixer, those signal components that arrive in anti-phase tend to self-cancel, introducing a series of notches throughout the audio frequency band (ie a comb filter). With 1 ms delay the notches are spaced 1 kHz apart, and with 4 ms delay they are spaced 250 Hz apart. These phase-induced notches are relatively shallow (about 20 dB deep), but introduce a pleasing acoustic effect as they are swept up and down through music signals by the slow scan generator.

The flanging circuit of Fig. 4 differs from the phasing circuit in that the audio mixer is placed ahead of the delay line, and part of the delayed signal is fed directly back to one input of the mixer. The consequence of this configuration is that in-phase signal components arriving at the mixer tend to add together regeneratively, introducing a series of comb-like peaks in the audio frequency response. The amplitude of these peaks depends on the degree of feedback and can be made very steep. These phase-induced peaks introduce very powerful acoustic effects as they are swept up and down through a music signal via the slow scan generator.

HOW IT WORKS

THE MAIN CIRCUIT

The main circuit of the unit contains all of the elements described above, except for the slow scan generator. Here, IC5 is the CCD delay line, IC6 is the VCO or clock generator, IC4 and IC8 are two-input audio mixers and IC7 is a low pass amplifier. Input signals are applied to the unit via level control RV1; the unit's clock generator produces a certain amount of RFI, and R24-C7 can be used to prevent this RFI feeding back to the input terminal when the unit is used with a radio music source. ICs 3 and 9 are used in the circuit as voltage-controlled electronic mode selector switches.

In the double-tracking mode, switches IC3d, IC9b and IC9c are open and IC9a is closed. In this case one half of the input signal is fed directly to the R46 side of audio mixer IC8 and the other half is fed to the R47 side of the IC8 mixer via low pass (22 kHz) mixer IC4, delay line IC5, and low pass amplifier IC7. The IC6 clock generator operates at a fairly low frequency, with its rate determined by C15 and the series values of R37 and RV2; the scan generator input is disabled by IC9b, and the second input of mixer IC4 is disabled by IC3d.

Table 1 shows the states of the IC3 and IC9 switches (which are DC-controlled by SW4) in the different operating modes of the circuit. Note here that IC3d and IC9a are activated automatically by the scan generator circuitry (provided they haven't been overridden by SW4), and that these switches are closed when scanning is in progress. Also note that, when the unit is used in the flanging mode and IC3d is closed, the R35-R36-D5-D6-D7-D8 network is used to

automatically limit the magnitude of feedback signals from RV3 to R34, so that flanging does not attain uncontrolled levels.

From Table 1 and the above information, the reader should have little trouble in figuring out the precise methods of circuit operation in the other modes. Note that IC9c controls the coarse speed range of the VCO, and IC9b enables or inhibits the input from the scan generator circuit.

THE SCAN GENERATOR CIRCUIT

The scan generator circuit provides a ramp waveform to the input of the VCO and provides control signals to IC3d and IC9a of the main circuit. When the circuit is used in the manual and one-shot modes the scanning is initiated by closing either PB1 or an external foot switch; the circuit action is such that the IC3d and IC9a switches of the main circuit are normally opened and music signals are played straight through the unit (via the delay line) without any special effects being imposed, but as soon as a scan is initiated these two switches are activated by IC2b and special effects are imposed for the duration of the scan.

The operating theory of the scan generator circuit is fairly involved. IC1a is an op-amp integrator circuit and is DC-biased at half-supply volts by R4-R5. In our application, the circuit is used as a ramp waveform generator and its timing action is controlled by R6, capacitors C1 to C3 and by the DC voltage on the R7-R8 junction; normally, this voltage has a value of 5 V but switches to 10 V when PB1 or IC3c are closed. Thus, the output of IC1a (which

feeds the VCO input of the main circuit via IC9b) is normally at +10 V, but starts to ramp down towards +5 V as soon as the R7-R8 junction is pulled high by PB1 or IC3c. As soon as the R7-R8 junction is allowed to switch to +5 V, the IC1a output starts to ramp back towards +10 V again.

The IC1a circuit has four ramp speeds available, which are controlled by switching in different total values of integrating capacitance using SW1. In the fastest ramping speed, only 68n of capacitance (C3) is used; in the next speed, 136n (C2 + C3); in the third speed 218n (C1 + C3) and in the slowest speed 286n (C1 + C2 + C3).

The output of IC1a is fed to inverting amplifier IC1b, which has a DC voltage gain slightly greater than unity, and the output of IC1b is fed to the inputs of non-inverting voltage comparators IC1c and IC1d. IC1c is referenced to +10 V; IC1d is referenced to +5 V and has its output inverted by IC2a. The circuit action is such that the output of IC1c switches high whenever the IC1a ramp generator reaches or exceeds the scan-down limit, and the output of IC2a switches high whenever IC1a is not ramping or whenever it reaches or exceeds the scan-up limit; these two states are indicated by LED2 and LED1 respectively.

IC2c-IC2d is a simple bistable circuit, which can be set by a positive pulse applied across R16 or reset by a positive pulse fed to D4; the output of the bistable is used to control switch IC3c. The reset signal of the bistable is derived from the output of IC1c; the set signal is derived from PB1 or from the output of IC2a, depending on the operating mode (selected with SW2) of the

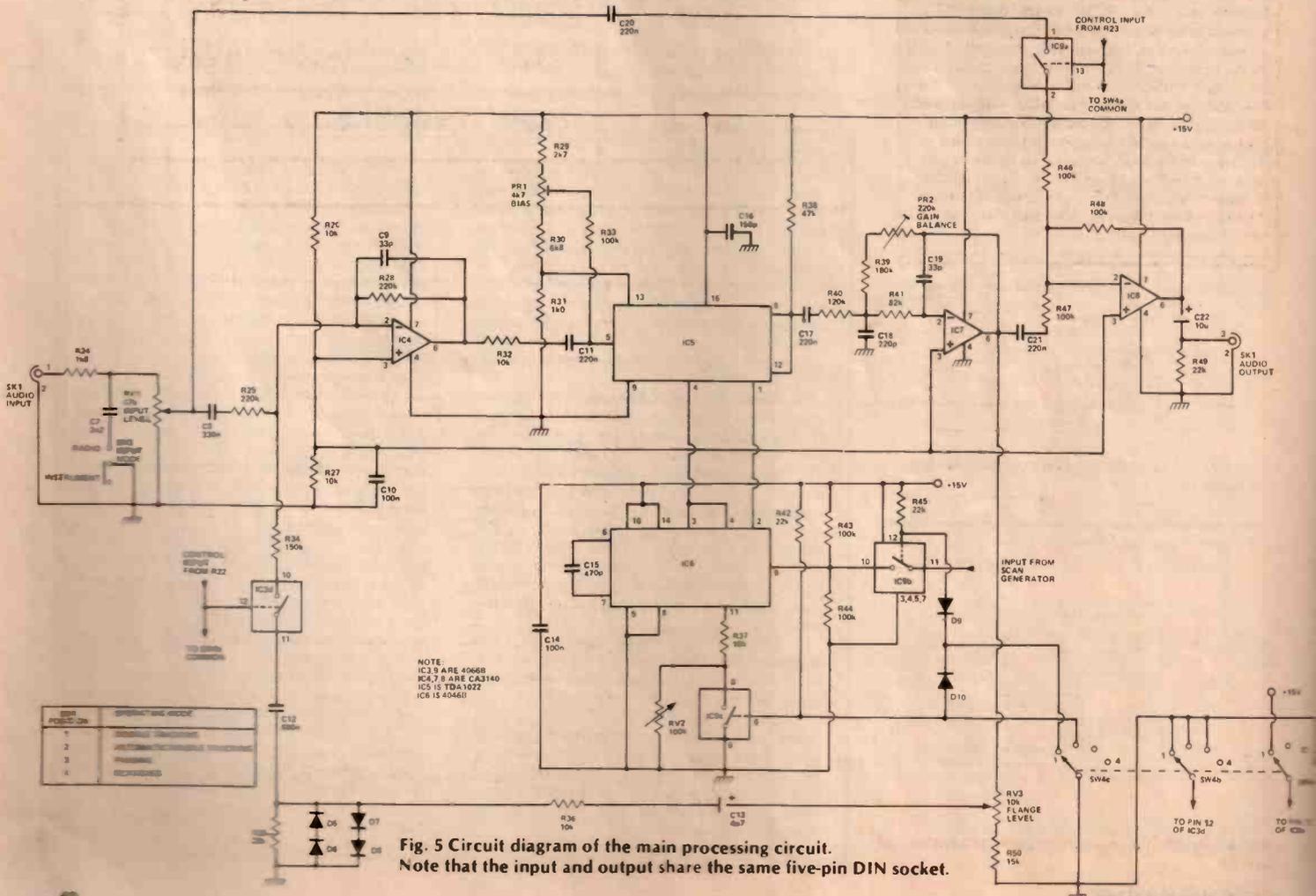


Fig. 5 Circuit diagram of the main processing circuit. Note that the input and output share the same five-pin DIN socket.


PROJECT : Music Processor

scan generator. The output of IC2a is also used to control IC3d and IC9a (in the main circuit) via 10 ms delay/inverter network R19-C6-R20-IC2b and R22 and R23. The overall action of the generator in each of the three different operating modes is as follows.

MANUAL SCAN. In this mode of operation the scanning is entirely controlled by PB1 (or the external foot switch) and the unit simply gives a scan-down action when PB1 is closed, or a scan-up action when PB1 is open. The scan limits are indicated by LEDs 1 and 2; switches IC3d and IC9a receive 'close' control signals when scanning is in progress and 'open' signals when scanning is not in progress. SW4a and SW4b determine whether or not these control signals are acted upon.

ONE-SHOT SCAN. In this mode of operation the output of PB1 is used to feed a set signal to bistable IC2c-IC2d and the input of the IC1a ramp generator is controlled from the bistable output via IC3c. When PB1 is momentarily closed the bistable output is switched high, causing IC3c to close and initiate a ramp-down action; ramp-down is maintained until the scan-down limit is reached. At this point the bistable is reset by IC1c output, causing IC3c to open; the ramp generator then scans back up to the full extent, at which point the one-shot circuit action is complete. IC3d and IC9a are again controlled from the output of IC2b throughout the one-shot action.

FREE-RUNNING SCAN. In this mode of operation the set input of the bistable is controlled from the output of IC2a, the reset input is controlled from the output of IC1c, and the scanning action is controlled from the bistable output via IC3c. The action is such that IC1a ramps down (IC3c closed) until the scan-down limit is reached, at which point the bistable is reset. IC3c then opens and IC1a ramps up until the scan-up limit is reached, at which point the bistable is set again via IC2a output and IC3c closes again, initiating another ramp-down action; this process continues ad infinitum. Note that, because of the delay action of R19-C6-R20 and IC2b, the IC3d and IC9a control signals are continuously maintained when the scan generator is used in the free-running mode.

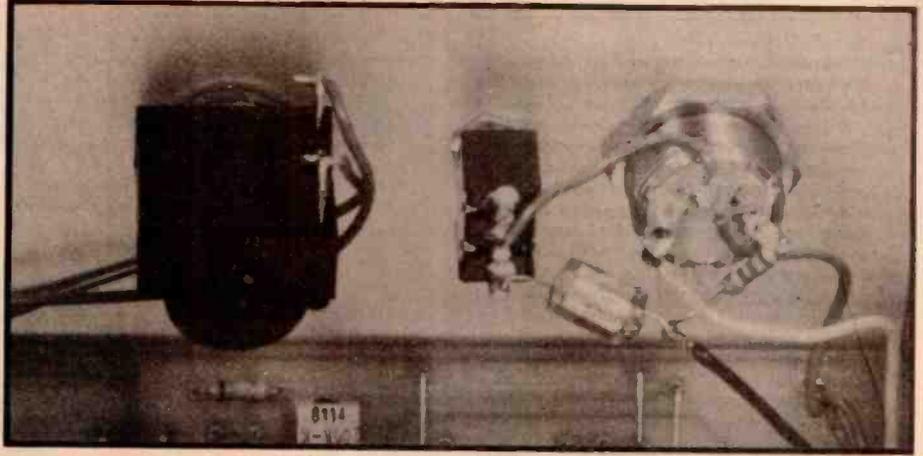

A detail shot showing how C7 and R24 are mounted. SK1 is on the right, and one end of R24 is soldered to pin 1 (input). The other end of the resistor is soldered to C7 and a wire which goes to RV1 on the front panel. The remaining wires on SK1 are ground (pin2) and output (pin 3). Closing SW3 connects the capacitor to ground to filter RFI at the input. If an external footswitch is to be used, it may be plugged into the mono jack socket on the left of the picture.

TABLE 1

| OPERATING MODE | SWITCH STATES | | | |
|-----------------|---------------|--------|--------|--------|
| | IC9a | IC9b | IC3d | IC9c |
| Double Tracking | Closed | Open | Open | Open |
| ADT | Closed | Closed | Open | Open |
| Phasing | Closed | Closed | Open | Closed |
| Flanging | Open | Closed | Closed | Closed |


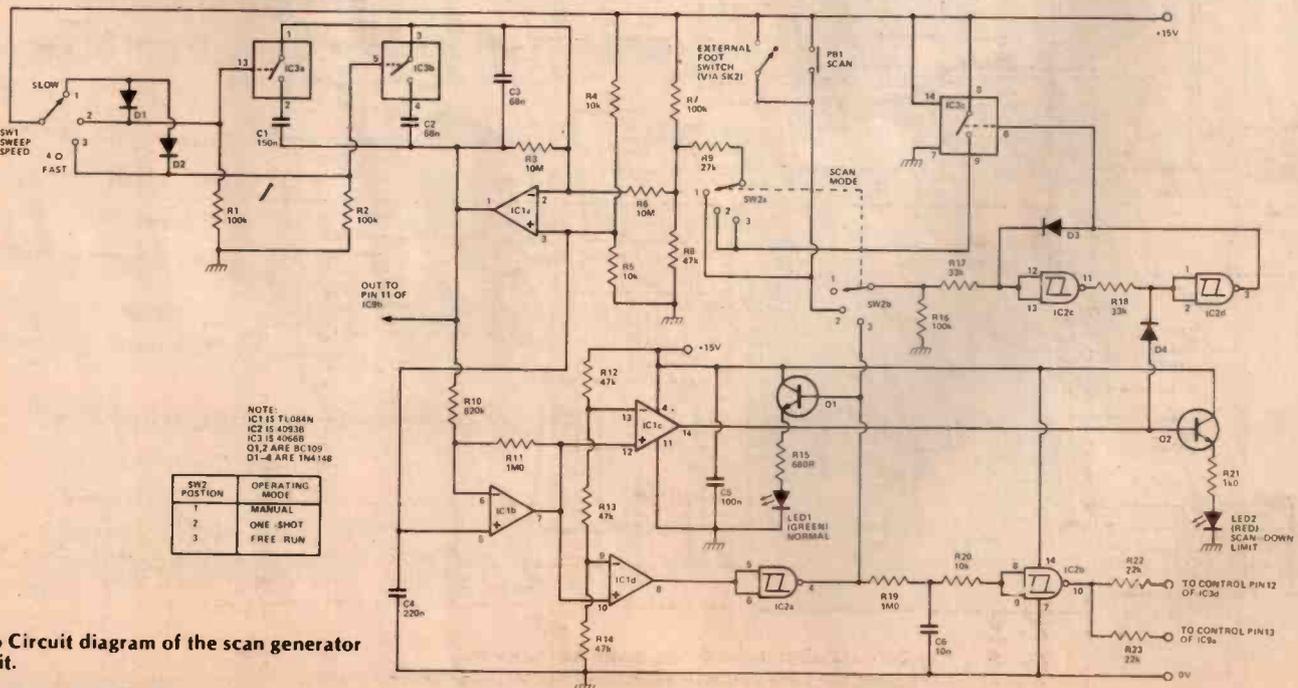


Fig. 6 Circuit diagram of the scan generator circuit.

BUYLINES

Nothing particularly out of the ordinary for this project; most of the components are available from the normal outlets. In case of difficulty, Technomatic and Watford Electronics stock the TL084N, Electrovalue and Watford stock the PCB-mounting transformer, and C23 can be obtained from Electrovalue. The case we used (order no. CL2 ADJ) can be obtained from West Hyde Developments for a retail price of £12.94 including postage and packing. The PCB can be purchased from our PCB Service (see advert on page 76).

Fig. 7 Component overlay of the ETI Music Processor. There's a great deal that fits on the board, and a great deal that doesn't, so take time and care over construction. Note the large number of 'blob and arrow' symbols; some of these represent wiring to off-board components, some are point-to-point connections on the PCB. The latter blobs are the lettered ones; link A to A, B to B and so on. Remember that R24 and C7 are mounted directly on SK1 and SW3.

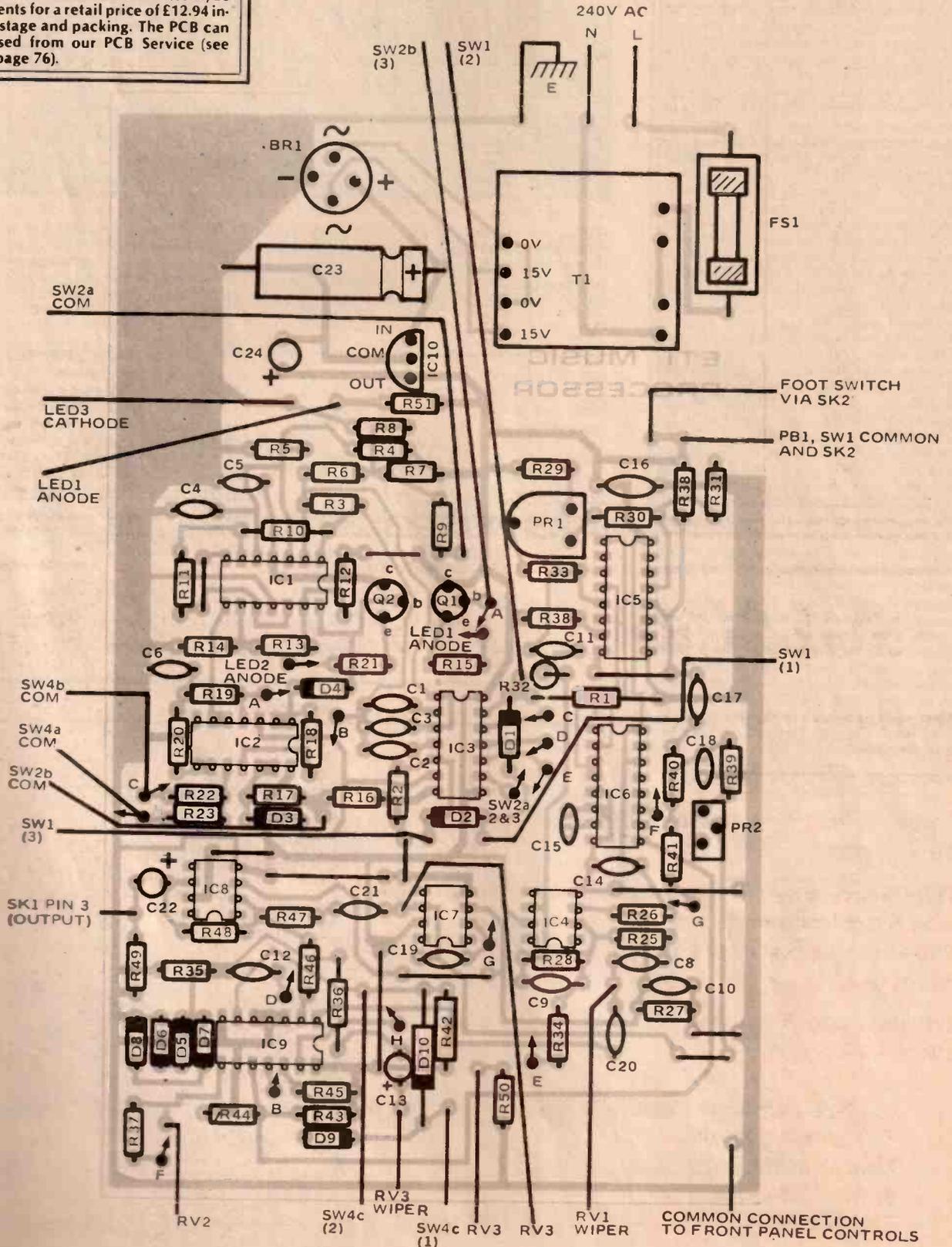

PROJECT : Music Processor

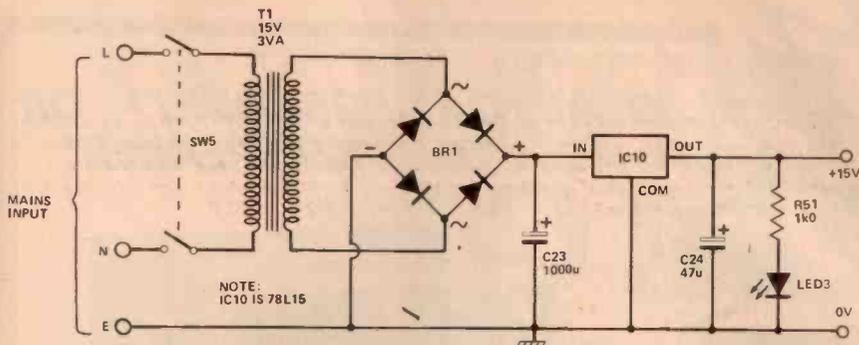


Fig. 8 Circuit diagram of the power supply for the project.

| | |
|----------|-------------------------------|
| 20,21 | 220n polycarbonate |
| C5,10,14 | 100n polycarbonate |
| C6 | 10n polycarbonate |
| C7 | 2n2 polystyrene |
| C8 | 330n polycarbonate |
| C9,19 | 33p ceramic |
| C12 | 680n polycarbonate |
| C13 | 4u7 35 V tantalum |
| C15 | 470p ceramic |
| C16 | 150p ceramic |
| C18 | 220p ceramic |
| C22 | 10u 35 V tantalum |
| C23 | 1000u 40 V axial electrolytic |
| C24 | 47u 16 V tantalum |

PARTS LIST

Resistors (all 1/4 W, 5%)

| | |
|---------------|------|
| R1,2,7, | |
| 16,33, | |
| 43,44, | |
| 46,47,48 | 100k |
| R3,6 | 10M |
| R4,5,20,26, | |
| 27,32,36,37 | 10k |
| R8,12,13, | |
| 14,38 | 47k |
| R9 | 27k |
| R10 | 820k |
| R11,19 | 1M0 |
| R15 | 680R |
| R17,18 | 33k |
| R21,31,51 | 1k0 |
| R22,23,35,42, | |
| 45,49 | 22k |
| R24 | 1k8 |
| R25,28 | 220k |

Resistors (continued)

| | |
|-----|------|
| R29 | 2k7 |
| R30 | 6k8 |
| R34 | 150k |
| R39 | 180k |
| R40 | 120k |
| R41 | 82k |
| R50 | 15k |

Potentiometers

| | |
|-----|---------------------------------|
| RV1 | 47k logarithmic |
| RV2 | 100k linear |
| RV3 | 10k linear |
| PR1 | 4k7 miniature horizontal preset |
| PR2 | 220k miniature vertical preset |

Capacitors

| | |
|-----------|--------------------|
| C1 | 150n polycarbonate |
| C2,3 | 68n polycarbonate |
| C4,11,17, | |

Semiconductors

| | |
|---------|---------------------------|
| IC1 | TL084N |
| IC2 | 4093B |
| IC3,9 | 4066B |
| IC4,7,8 | CA3140 |
| IC5 | TDA1022 |
| IC6 | 4046B |
| IC10 | 78L15 |
| Q1,2 | BC109 |
| BR1 | 50V, 1 A bridge rectifier |
| D1-10 | 1N4148 |
| LED1 | 0.125" green LED |
| LED2,3 | 0.125" red LED |

Miscellaneous

| | |
|-----|---------------------------------------|
| T1 | 15-0-15 3 VA PCB-mounting transformer |
| SW1 | 1-pole 4-way rotary switch |
| SW2 | 2-pole 4-way rotary switch |
| SW3 | SPDT miniature toggle switch |
| SW4 | 3-pole 4-way rotary switch |
| SK1 | five pin DIN socket |
| SK2 | 1/4" mono jack socket |

SUBSCRIPTIONS

This year we present a new twelve-part, non-fiction series — ETI 1981 available from your newsagent every month.

Forget to buy it this month, or is your newsagent sold out?


Why worry when ETI gets to the shop? Sit back and wait for it to come to you. Take out an ETI Subscription. For only £11.25 we'll send you twelve issues of ETI.

To claim your years' supply of ETI, send your PO or cheque direct to :


ETI Subscriptions Department,
513 London Road,
Thornton Heath,
Surrey CR4 6AR.
Tel: 01-684 3157.



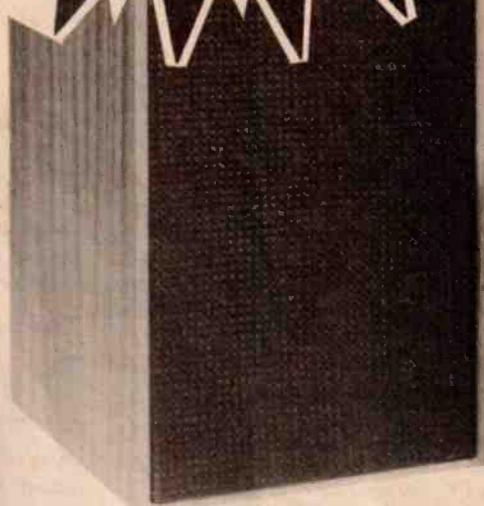**ETI READER
OFFER!
VIDEOTONE
D100 LOUDSPEAKERS
ONLY
£29.95 inc VAT
Save over
25%**



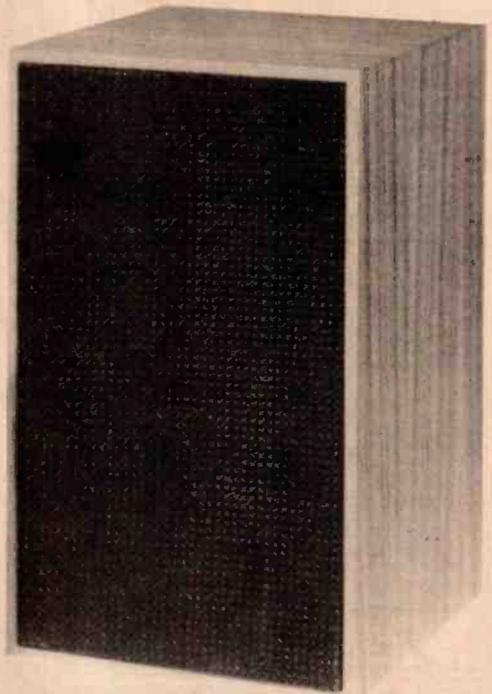**IDEAL FOR UPGRADING — OR
AS A 'SECOND SPEAKER'**



TYPICAL SPECIFICATION

Recommended Amplifier Power: 10-25 watts RMS per channel. In general they need between 8 & 10 watts RMS per channel for every 1000 cu.ft. of room space. Impedance: 4-8 ohms. Frequency Response: 90 Hz-18 KHz \pm 5 dB. Finishes: Real teak or walnut veneer with black frets. Size: 7 3/4" deep, 6 1/2" wide, 11" high. Weight: 3.5 Kg. (7lb. 9oz.) each 8 Kg. (17lb. 8oz.) per pair/packed.

The highly acclaimed D100 loudspeaker is an ideal 'second speaker' for use in the dining room, bedroom — or anywhere else you need music! It is diminutive in size, but has a *big* sound! Using versions of the 'Minimax 2' drive units — but in a slightly larger cabinet (still less than 8" x 7" x 11" !!!) the D100 provides a truly hi-fi performance at a lo-fi price.

This reader offer is an unrepeatable opportunity — at an unrepeatable price — to add this amazing little speaker to your system. The sound quality is outstanding; the mid-range being clear and detailed and the bass response exceptional for the size. Colouration is particularly low in this design and as a consequence the D100 sounds much larger than it actually is! There is no trace of that 'small-box' sound that bedevils many competitive designs.

The power handling is high, up to 50 W programme — which makes the D100 an ideal match for a "micro" system — or indeed any system where size is an important consideration.

At this price can you afford not to have a pair?

To ETI Loudspeaker Offer,
145 Charing Cross Road,
London WC2.

Please send me pairs of D100 speakers at £29.95 per pair, plus £2.95 p&p per pair.
I enclose a cheque/PO made payable to Modmags for £



ORDER BY POST WITH
BARCLAYCARD/ACCESS,



4 9 2 9

5 2 2 4

Please debit my account

Signature:

Tick choice of veneer: Teak Walnut

Name (CAPITALS)

Address (CAPITALS)

Please note that the offer applies to UK mainland only; allow 28 days for delivery.

ENGINEER'S GUIDE TO BASIC

Computing is all about data - numbers to be processed, constants for calculations, strings for the manipulation of groups of characters. Stewart Fleming looks at the various methods of data storage, the limitations that these cause, and how the problems may be overcome.

In this second article an attempt will be made to describe the types of data item that can be handled by BASIC programs, and then to classify BASIC instructions, statements and commands according to their function. Throughout the series comparison will be made between different BASICs and we will describe how particular operations may be effected in different versions of the language. We will also look at some of the ways in which floating-point operations may be carried out using integers and strings only. The topics covered will be illustrated by complete examples, even if this means occasionally 'jumping ahead' a little.

BASIC allows three main types of data: integers, floating-point numbers and strings. For each of these types a code is used to convert the item to be represented into a collection of bits which may be stored and moved around within the computer. Let's look at the three types one by one.

Integers

These are the positive and negative whole numbers including zero. The positive sign, +, is optional when representing the positive numbers or zero both in ordinary arithmetic and in BASIC — thus -37, 42, +42, -0, 0 and +0 are all integers. Computers allow only a subset of the integers — often -32768 to +32767. This is a result of the binary representation of integers within the computer. The binary system is the two's number system — thus using two eight-bit bytes, say:

$$5_{10} = 101_2 = \underbrace{(0000000000000101)}_2$$

1st byte 2nd byte

The subscript after the numbers indicates which base we are counting in.

Negative integers will be represented in a variety of ways. A common one is the 'two's complement' method in which the negative number is represented by the corresponding positive binary number in which the 0s have been converted to 1s and vice versa (a process known as inversion) and 1 added to the result.

$$\text{Hence } -5_{10} = (111111111111010 + 1)_{2\text{'s complement}}$$

$$= (111111111111011)_{2\text{'s complement}}$$

(Carrying out this process again on the number just formed gives us the original positive number, as the reader can readily verify.)

The left-hand bit is considered to be a sign bit — 0 means positive and 1 negative. It follows that the largest positive two-

byte integer is

$$0111111111111111_2 = 2^{15} - 1 = 32767_{10}$$

and the largest negative one is

$$1000000000000000_2 = -2^{15} = -32768_{10}$$

(as can be verified by inverting the bits and adding one.)

Another method of representing negative numbers known as the 'one's complement' method simply inverts the bits of the corresponding positive number. This time the range will be -32767 to +32767 (one less than the 2's complement system) and there will be two ways of representing zero:

$$+0_{10} = (0000000000000000)_2$$

$$-0_{10} = (1111111111111111)_{1\text{'s complement}}$$

A third way is the 'sign and modulus' method where the most significant bit (the left-most bit) is taken as a sign bit (0 = positive, 1 = negative). Thus:

$$+5_{10} = (0000000000000101)_2$$

SIGN BIT MODULUS

$$-5_{10} = (1000000000000101)_2$$

Mention should be made of Acorn Atom BASIC which uses four bytes for each integer and therefore has a much larger integer range than most BASICs. Acorn BASIC also allows the representation of integers in the hexadecimal notation (base 16) provided the number is preceded by the hash (#) symbol. Hexadecimal uses the digits 0 to 9, and also the letters A to F for the numbers 10 to 15. An example of a number in hexadecimal is

$$3F_{16} = (3 \times 16 + 15)_{10} = 63_{10}$$

This would be represented in Acorn BASIC by #3F.

The Real Thing

Real numbers are all the numbers that may be represented in decimal notation. (Note, however, that some real numbers — including e and π — would require an infinite series of decimals and hence are not strictly representable). The integers are representable in decimal notation and are therefore included in the real numbers. Examples of real numbers are: 0.25, -73.420, 5.0, 5, 0.33333.

FEATURE : Guide To BASIC Part 2

bounded by single quotes. Acorn BASIC gets round this by representing a single quotation mark within a string by two quotation marks, thus

"IT"'S A KNOCKOUT"

In certain instances (eg in conjunction with a DATA statement) the surrounding quotes may be omitted.

How Long . . .

The length of a string is the number of characters contained within it. A string of length zero is known as a null string, and the maximum length that a string can take may vary between machines, but is usually 255. Each character occupies one byte of storage in memory, and is represented by a numeric code which is usually a superset of the ASCII (pronounced as in Arthur) code (American Standard Code for Information Interchange). Thus, for example,

A = 01000001, = 65₁₀

BASICs will also store a start address (the address of the first character) for any string that occurs within a BASIC program or that is created by a BASIC program, together with some additional information such as the length of the string.

Some BASICs store an 'end-of-string' character as part of the string. Acorn BASIC, for example, adds the 'return' character (ASCII code 13) to its strings, but this is not included in any length-of-string calculations. Some of the characters within a string may be used by BASIC to carry out operations such as editing the screen — these are known as control characters — and others may be used to display particular shapes on the screen (graphics characters). More about them later.

Data Selection

Although there are three types of data item available, integers, floating-point numbers and strings, not all BASICs use all three. PET BASIC does, and stores numbers as integers rather than floating-point wherever possible. Research Machines' BASIC has only strings and floating-point numbers, while Acorn and Apple both offer BASICs with just integers and strings. With the Acorn, the user can purchase an extension ROM that gives him floating-point facilities; the Apple user can purchase a different version of BASIC stored on disc.


We will now consider ways in which floating-point operations may be implemented using an integer BASIC. Possible approaches are:

- writing BASIC subroutines to convert real numbers stored as strings into a decimal floating-point representation which uses the integers 0-9 only, to carry out arithmetic operations on these numbers, and to convert them back. (Such a program, written in Acorn BASIC, is listed in this article. This program will be described fully, and the algorithm it uses discussed, in the next article, which will also deal with structured programming and thus enable the routines to be written in any BASIC supporting integers and strings.)

- writing the subroutines in assembly language or machine code, thereby speeding up the arithmetic operations.

However, if the user requires a lot of floating-point numbers and operations in his applications, he would be well advised to choose a BASIC better suited to his purpose.

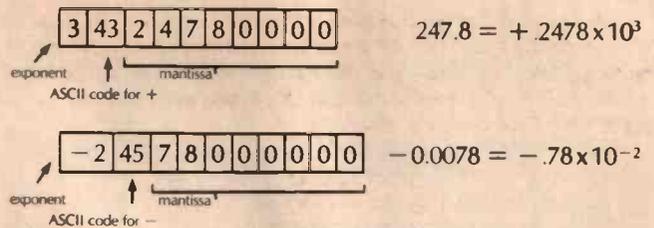The program listed here works for real numbers up to 10 characters long, but not in scientific notation. Numbers are stored to a precision of eight decimal digits. The addition subroutine will register an overflow condition if addition produces a sum greater than 9999999999999999, or less than -9999999999999999. The program stores its floating-point numbers in the following format:



Sample runs of the program look like the examples below, with the user entries in bold type and the computer responses in medium.

```
> RUN
ENTER FIRST NUMBER
?56.3
ENTER SECOND NUMBER
?- 4.7
ANSWER IS + 51.600000
ENTER FIRST NUMBER
?66666666666666666666
ENTER SECOND NUMBER
?55555555555555555555
OVERFLOW
>
```

Constants And Variables

Numbers and strings which occur 'as themselves' within a BASIC program are known as constants. Numbers and strings may also be represented symbolically using variables. Variables will be the subject of a later article, but for now, a BASIC variable is a name which represents and identifies an area of storage containing a valid string or number. We may conceptually view the variable as a box containing a value.



In this example the variable X has the value 3.5, though at a later stage it may contain a different value — hence the term 'variable'. The BASIC programmer can thus refer to values by symbolic names, and is freed from the task of keeping track of the specific memory locations where his data is stored.

Classified Items

We have already classified BASIC instructions as being either statements or commands (see last month) — broadly speaking, statements are operations to be performed by a program and commands are operations to be performed on a program. In addition, all BASICs offer built-in programs known as functions which carry out useful specific operations on strings and/or numbers. For example, we might have functions to work out the length of a string, or to calculate the tangent of an angle.

So we may classify the items that may occur within BASIC or will be accepted by BASIC as:

- constants
- variables
- commands
- statements
- functions and operators (operators include +, -, /, =, > etc)

Commands may be further classified as creating or modifying programs (eg NEW); executing programs (eg CLEAR, RUN); or storing and retrieving programs (eg LOAD). Statements may be classified as assignment (eg LET); definition (eg DEF FN); control (eg IF . . . THEN); input/output (eg PRINT); graphics (eg SET, PLOT); memory reference (eg PEEK, POKE). During the remainder of this series we will be looking at each of these areas.

A Last Word

Last month's program can be vertically compressed to fit on a smaller screen (eg TRS-80) by inserting the lines

341 LET V=V/2

342 LET W=10

and rewriting

480 FOR K=W TO 1 STEP -1

There was also a small factual error which crept in — the early computers with a 'Harvard' architecture were ENIAC and Mark 1.

```

100 GOSUB 1140
110 PRINT "ENTER FIRST NUMBER"
120 Z=5; GOSUB i
130 PRINT "ENTER SECOND NUMBER"
140 Z=8; GOSUB i
150 $O="Z4=Z5+Z8"; GOSUB a
160 Z=4; PRINT "ANSWER IS"; GOSUB p
170 GOTO 110
180 END
189 REM **STRING TO F-P NO.*****
190i INPUT $ZZ(Z)
200 LET $X=$ZZ(Z)
209 REM **WORK OUT SIGN*****
210 IF CH$X < >45 AND CH$X < >43 THEN YY(Z*10+1)=43;
GOTO 240
220 YY(Z*10+1)=CH$X
230 $X=$X+1
240 $W=$X
249 REM **WORK OUT EXPONENT AND ELIMINATE DECIMAL
POINT*****
250 LET M=LEN(X)
260 FOR I=1 TO LEN(X)
270 IF CH$X < >46 THEN GOTO 300
280 LET M=M-1
290 GOTO 320
300 LET $X=$X+1
310 NEXT I
320 LET $W+M=""
330 LET $W+LEN(W)=$X+1
339 REM **ELIMINATE LEADING ZEROS*****
340 FOR I=1 TO LEN(W)
350 IF CH$W < >48 THEN GOTO 380
360 LET $W=$W+1
370 M=M-1
380 NEXT I
390 YY(Z*10)=M
399 REM **PUT MANTISSA IN ARRAY*****
400 FOR I=2 TO 9
410 S=CH$W
420 LET S=S-48
430 IF S < 0 THEN S=0
440 YY(Z*10+I)=S
450 LET $W=$W+1
460 NEXT I
470 RETURN
478 REM **F-P NO. TO STRING*****
479 REM **TEST FOR ZERO*****
480p IF YY(10*Z+2)=0 THEN $ZZ(Z)="0."; GOTO 630
489 REM **FIND SIGN OF NUMBER*****
490 IF YY(10*Z+1)=43 THEN $ZZ(Z)="+"; GOTO 510
500 $ZZ(Z)="-"
509 REM **APPEND LEFT DIGITS*****
510 IF YY(10*Z) < =0 THEN $ZZ(Z)+LEN(ZZ(Z))="0."; GOTO 560
520 FOR I=2 TO YY(10*Z)+1
530 IF I > 9 THEN $ZZ(Z)+LEN(ZZ(Z))="0."; GOTO 550
540 $ZZ(Z)+LEN(ZZ(Z))=$UU(YY(10*Z+I))
550 NEXT I
559 REM **APPEND DECIMAL POINT*****
560 $ZZ(Z)+LEN(ZZ(Z))="."
569 REM **APPEND RIGHT DIGITS*****
570 IF YY(10*Z)+2 > 9 THEN $ZZ(Z)+LEN(ZZ(Z))="0."; GOTO 620
580 FOR I=YY(10*Z)+2 TO 9
590 IF I < 2 THEN $ZZ(Z)+LEN(ZZ(Z))="0."; GOTO 610
600 $ZZ(Z)+LEN(ZZ(Z))=$UU(YY(10*Z+I))
610 NEXT I
620 PRINT $ZZ(Z)
    
```

```

630 RETURN
639 REM **WORK OUT NUMBERS TO BE ADDED*****
640a DIM KK(2)
650 L=0
660 IF CH$O < 48 OR CH$O > 57 THEN GOTO 690
670 S=CH$O
680 KK(L)=S-48; L=L+1
690 $O=$O+1
700 IF L < 3 THEN GOTO 660
708 REM **ADDITION OF F-P NOS.*****
709 REM **INITIALIZE ARRAYS*****
710 FOR I=1 TO 39
720 RR(I)=0
730 SS(I)=0
740 TT(I)=0
750 NEXT I
759 REM **PUT NOS. IN RR AND SS*****
760 FOR I=0 TO 7
770 RR(20-YY(10*KK(1))+I)=YY(10*KK(1)+I+2)
780 SS(20-YY(10*KK(2))+I)=YY(10*KK(2)+I+2)
790 NEXT I
799 REM **TAKE 9'S COMPLEMENT WHERE NECESSARY*****
800 IF YY(10*KK(1)+1)=43 THEN GOTO 840
810 FOR I=0 TO 39
820 RR(I)=9-RR(I)
830 NEXT I
840 IF YY(10*KK(2)+1)=43 THEN GOTO 880
850 FOR I=0 TO 39
860 SS(I)=9-SS(I)
870 NEXT I
879 REM **ADD RR AND SS AND PUT RESULT IN TT*****
880 C=0
890 FOR I=39 TO 0 STEP -1
900 TT(I)=SS(I)+RR(I)+C
910 IF TT(I) > 9 THEN TT(I)=TT(I)-10; C=1; GOTO 930
920 C=0
930 NEXT I
939 REM **PERFORM END-AROUND CARRY*****
940 FOR I=39 TO 0 STEP -1
950 TT(I)=TT(I)+C
960 IF TT(I) < 10 THEN GOTO 990
970 TT(I)=TT(I)-10; C=1
980 NEXT I
989 REM **TEST FOR OVERFLOW*****
990 IF TT(0) < >0 AND TT(0) < >9 THEN PRINT "OVERFLOW";
STOP
999 REM **TEST FOR SIGN. TAKE 9'S COMPLEMENT IF
NECESSARY*****
1000 IF TT(0)=0 THEN YY(10*KK(0)+1)=45; GOTO 1050
1010 FOR I=0 TO 39
1020 TT(I)=9-TT(I)
1030 NEXT I
1040 YY(10*KK(0)+1)=45
1049 REM **WORK OUT MANTISSA*****
1050 FOR I=0 TO 39
1060 IF TT(I) < >0 THEN GOTO 1080
1070 NEXT I
1080 FOR J=0 TO 7
1090 IF I+J > 39 THEN YY(10*KK(0)+2+J)=0; GOTO 1110
1100 YY(10*KK(0)+2+J)=TT(I+J)
1110 NEXT J
1119 REM **WORK OUT EXPONENT*****
1120 YY(10*KK(0))=20-I
1130 RETURN
1139 REM **INITIALIZE ARRAYS*****
1140 DIM YY(99), RR(39), SS(39), TT(39), O(15)
1150 DIM UU(9)
1160 FOR N=0 TO 9; DIM B(1); UU(N)=B; NEXT N
1170 $UU(0)="0"; $UU(1)="1"; $UU(2)="2"
1180 $UU(3)="3"; $UU(4)="4"; $UU(5)="5"
1190 $UU(6)="6"; $UU(7)="7"; $UU(8)="8"; $UU(9)="9"
1200 DIM ZZ(9), X(19), W(19)
1210 FOR N=0 TO 9
1220 DIM J(19)
1230 ZZ(N)=J
1240 NEXT N
1250 RETURN
    
```

Program 1. Performing floating-point addition in Acorn Integer BASIC.

THE POWERFET AMPLIFIER



PFA 80
(100W plus into 8Ω)

Powerfets

So far 29 semiconductor manufacturers have invested in this new technology. Clearly powerfets are something special.

Their enormous power gains eliminate conventional drive circuitry in power amps, permitting delightfully simple designs. Their freedom from secondary breakdown and their tendency to shutdown when thermally overstressed, result in inherently stable and destruction-proof output stages, not needing protection circuitry. And perhaps best of all, their lack of charge storage make them fast and responsive, producing amplifiers of wide bandwidth and low distortion even at high frequencies.

Elegant Simplicity

Advances in high technology should make life simpler. A cluttered power amplifier board may well perform superbly but its busy elaboration is an indication that its design is pushing the limit of its component technology.

There are now many first class bipolar power amps on the market. All of them are complex and consequently expensive. Any additional improvements in the areas where they are weak (e.g. H.F. distortion) can only be obtained with yet further complexity and cost.

Only a new technology can provide the sort of "quantum jump" in component performance necessary to reduce the clutter on the board, reduce the cost and make the highest fit once more affordable.



Power Supply Components available

The PFA is perhaps the perfect realisation of the classic powerfet amp design. The superb PCB allows the use of either one or two pairs of output devices, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads).

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

| Specification | PFA80 | PFA120 |
|--|----------------|-----------------|
| Bandwidth | 10Hz | 100KHz - 1dB |
| Output Power | 80W (Vs - 50V) | 120W (Vs - 55V) |
| R.M.S. into 8Ω | | |
| THD (20Hz - 20KHz) (KHz at rated output) | ≤ 0.008% | ≤ 0.005% |
| SNR | 0.004% 1vp | 0.002% 1vp |
| Slew Rate | 120dB | > 20V μS |
| Gain | X22 | X22 |
| Rin | 3K | |
| Vs max | 70V | |

| Cost (built) (kit) | £15.95 | £22.85 | P. & P. 75p |
|--------------------|--------|--------|-------------|
| | £13.95 | £20.85 | |

Power Amp PAN 1397

A high quality 20W power amp board based on the HA 1397. Easily modified for bridge operation, providing high powers from low supply voltages.

Specification

| | | |
|------------------|-------------------------|----------|
| Output power RMS | 20W into 8Ω at 22V | PAN 1397 |
| | 20W into 4Ω at 19V | |
| THD | 0.02% at 1KHz 1W to 12W | |
| SNR | 90dB | |
| Input | 100mV into 50K | |
| Cost (built) | £5.80 (P. & P. 40p) | |



PAN 1397

PSU 101

Mains transformer for above 17.0 17v 50VA £3.95 (P. & P. £1)

Pre-amp PAN 20

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain attenuator control (vo₁ - a control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag PUs and space on the board is available for different equalisations.

Specification

| | |
|----------------------------------|---|
| B.V. | 20Hz - 30KHz - 1dB |
| THD | 0.003% 1vp |
| at rated o.p. | |
| SNR | 85dB (ref. 5mV RIAA) |
| Vs | 105dB (ref. 100mV 10Hz - 20V) |
| Output | 1V (clips at - 20dB) |
| Cost (built board less controls) | £4.75 2 (modified for stereo) (P. & P. 40p) |

THE POWERFET SPECIALISTS

J. W. RIMMER


Mail order only to:
Dept ETI/11, 148 Quarry Street, Liverpool L25 6HO.

Telephone: 051-428 2651

Technical enquiries:

367 Green Lanes, London N4 1DY. Tel: 01-800 6667

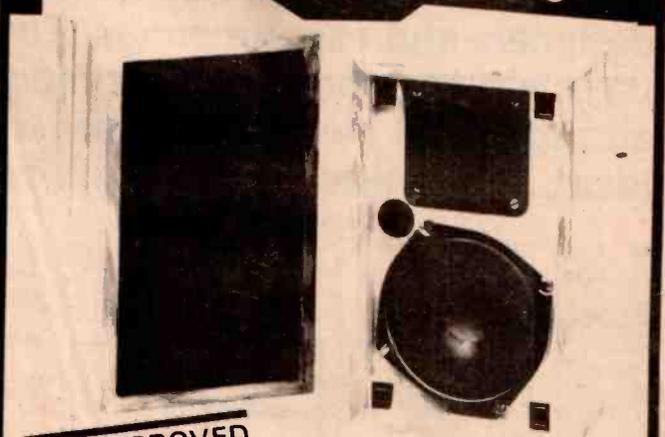Has seven years of success gone to our heads?



NEW IMPROVED

MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

POPULAR HI-FI

"Switching to the Minimaxes" from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." Comparative test OCTOBER 1975.

HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" JANUARY 1975.

PRACTICAL HI-FI & Audio

"The depth, clarity and openness of sound produced is quite astonishing". JUNE '75

WHAT HI-FI

"... the ability of the Mini-

max to take a lot of power and still sound good could be decisive" - Comparative test, APRIL 1977.

PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". JANUARY 1981.

Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms. Frequency Response: 80Hz - 20KHz ±5dB.

Finish: natural teak, veneer with black frets.

Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.

Weight: 4.1 Kgs (9 lbs) each.

ONLY £69.95 A PAIR

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

VIDEOTONE 98 CROFTON PARK ROAD LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4.

ET11


NAME _____

ADDRESS _____

100 CIRCUIT

A circuit bonanza in our latest supplement — 100 circuits for designers and experimenters. Tim Orr has been labouring long into the night to produce this comprehensive reference work, covering all aspects of electronics from analogue to digital. If you're stuck for ideas, this is the place to look first.


1 Precision VCO

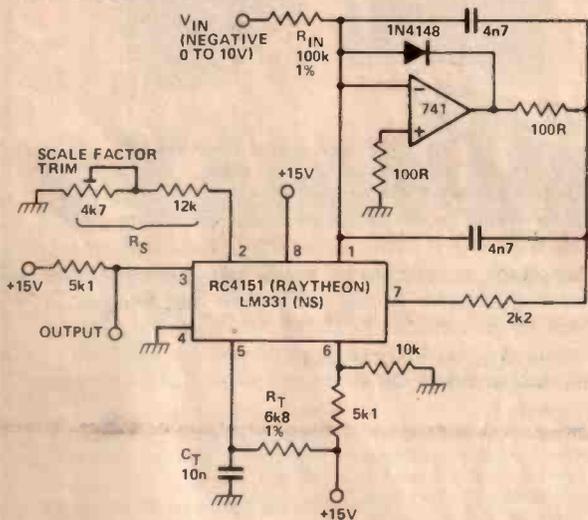

$$F = (-V_{IN}) / (2.09 \times (R_S / R_{IN}) \times 1 / (R_T C_T)) \text{ Hz}$$


Maximum frequency = 10 kHz
 Linearity = 0.05%
 Response time = 10 us
 Op-amp powered from ± 15 V

2 Triangle/Square Wave Oscillator

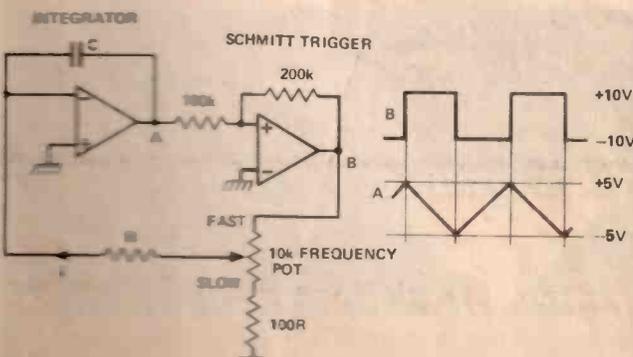


Output frequency $F = (\text{pot fraction}) / 2RC$
 Pot fraction can be 0.1 to 1/100, giving a 100 to 1 range from the pot
 Suitable frequency range = 0.01 Hz to 50 kHz
 Run op-amps from ± 12 V

3 Low Dissipation Regulator

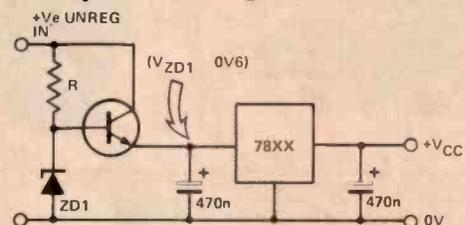



Using an external transistor to reduce the input voltage and power dissipation to a safe level.

4 Basic Op-amp Building Blocks

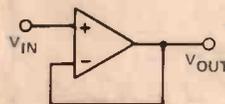



Voltage follower/buffer
 Input must have a DC path to ground

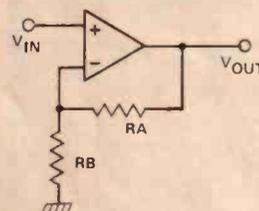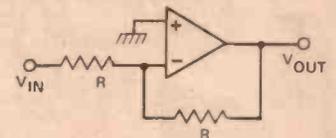Inverter
 Voltage gain = -1
 input impedance = R



Non-inverting amplifier
 Input must have a DC path to ground
 Voltage gain = $(R_A + R_B) / R_P$

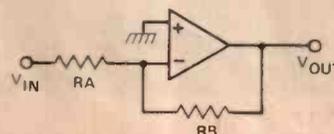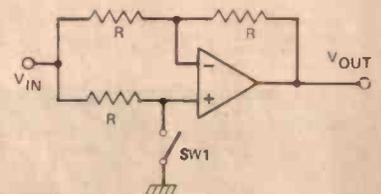
Inverter/non-inverter amplifier
 Voltage gain = +1 with SW1 open
 Voltage gain = -1 with SW1 closed



Inverting Amplifier
 Voltage gain = $-R_B / R_A$
 Input impedance = R_A


SUPPLEMENT

5 Audio Power Amp

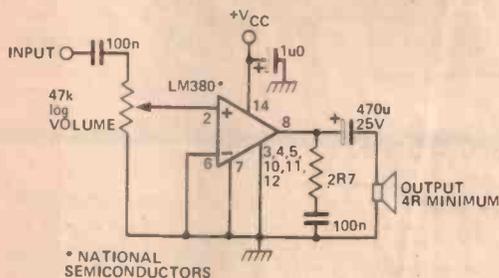

* NATIONAL SEMICONDUCTORS
 Voltage gain (fixed) = x 50 (34 dB)
 +V_{CC} range = +8 V to +22 V
 Typical quiescent current = 7 mA
 Output power = 2W5 (with speaker = 8R, heatsink fitted)

6 Linear VCO

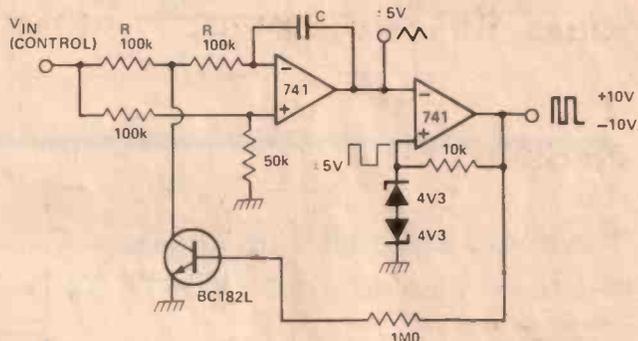


Triangle and square wave outputs

$$\text{Output frequency } F = (1.667 \times 10^{-7} \times V_{IN})/C \text{ Hz}$$

If $C = 1n0$ and $V_{IN} = 10V$, then $F = 1.66 \text{ kHz}$

Changing both R's from 100k to 10k will increase F by x 10

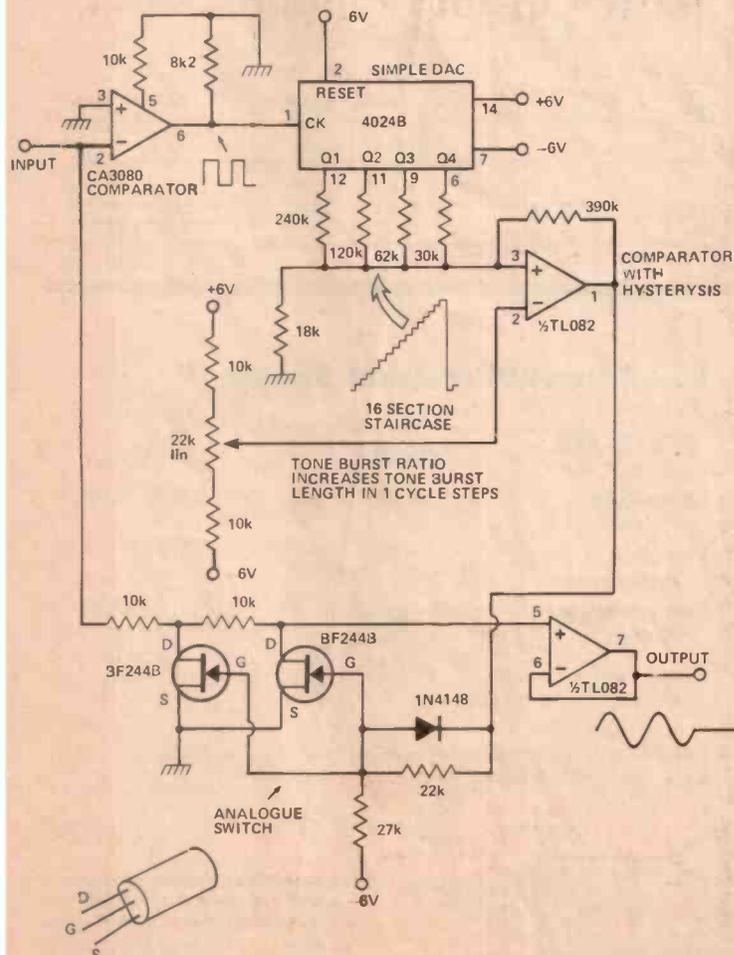
For low frequencies use TL081 op-amps
 Frequency range 0.1 Hz to 10 kHz




8 Variable Length Tone Burst Generator

Input is a sinewave or any other periodic waveform, maximum level $\pm 2V$, maximum frequency 100 kHz
 Output is a tone burst variable from one cycle on, 15 cycles off to 15 cycles on, one cycle off
 All devices powered from $\pm 6V$

7 Two Chip VCA

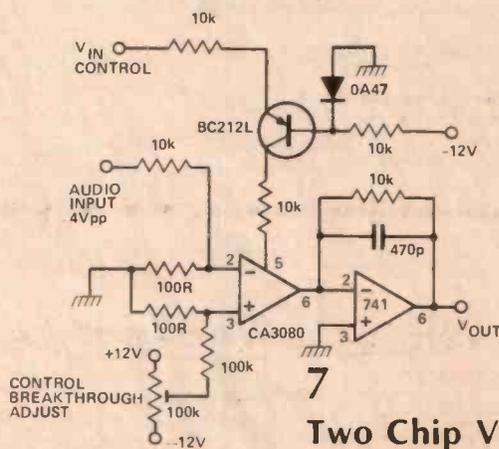


9 Digital Clock

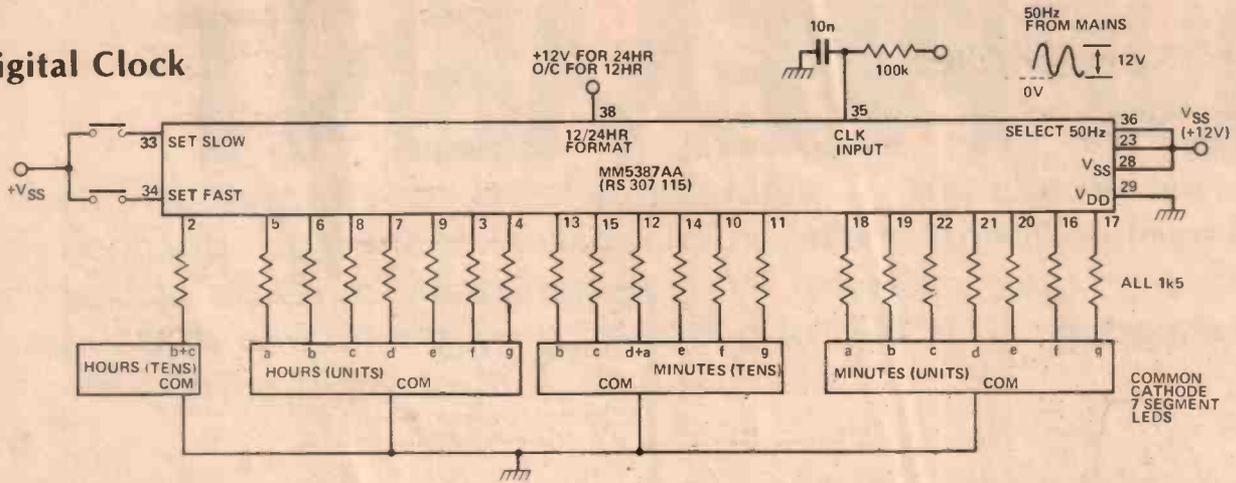

10 Keyboard Encoder And Display

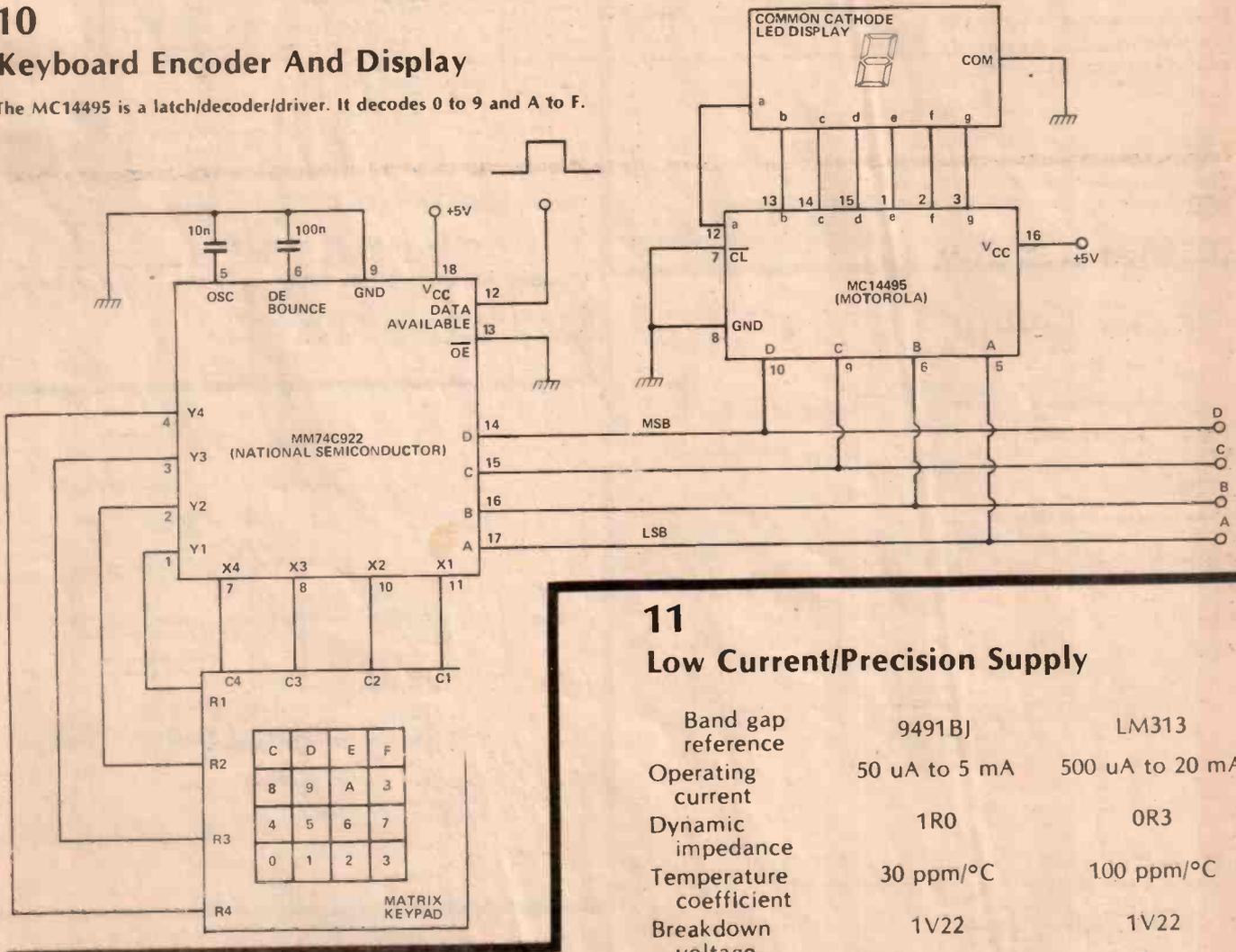
The MC14495 is a latch/decoder/driver. It decodes 0 to 9 and A to F.



11 Low Current/Precision Supply

| | | |
|-------------------------|---------------|-----------------|
| Band gap reference | 9491BJ | LM313 |
| Operating current | 50 uA to 5 mA | 500 uA to 20 mA |
| Dynamic impedance | 1R0 | 0R3 |
| Temperature coefficient | 30 ppm/°C | 100 ppm/°C |
| Breakdown voltage | 1V22 | 1V22 |

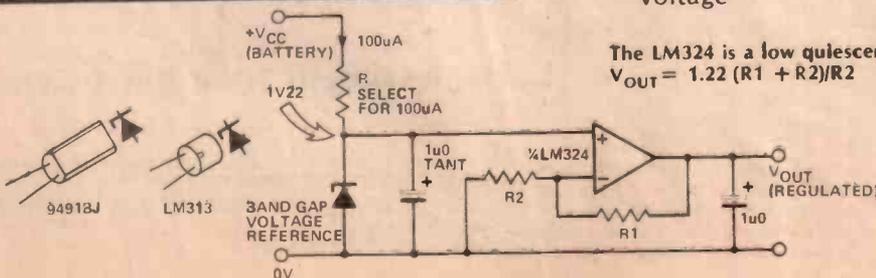The LM324 is a low quiescent current, ground sensing op-amp
 $V_{OUT} = 1.22 (R1 + R2)/R2$




Very useful for battery equipment where only low current and low voltages are available. Also used as voltage references in DVM units.


12 Switched Capacitor Filter

The R5604 contains three $\frac{1}{2}$ octave, 6 pole Chebyshev band pass filters. The centre frequencies are determined by the relationship $\frac{F_{CLK}}{135}$, $\frac{F_{CLK}}{108}$, $\frac{F_{CLK}}{86.5}$.


Maximum centre frequency = 10 kHz

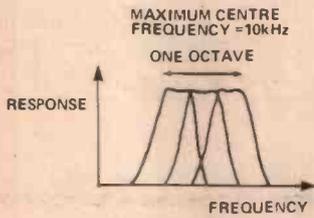


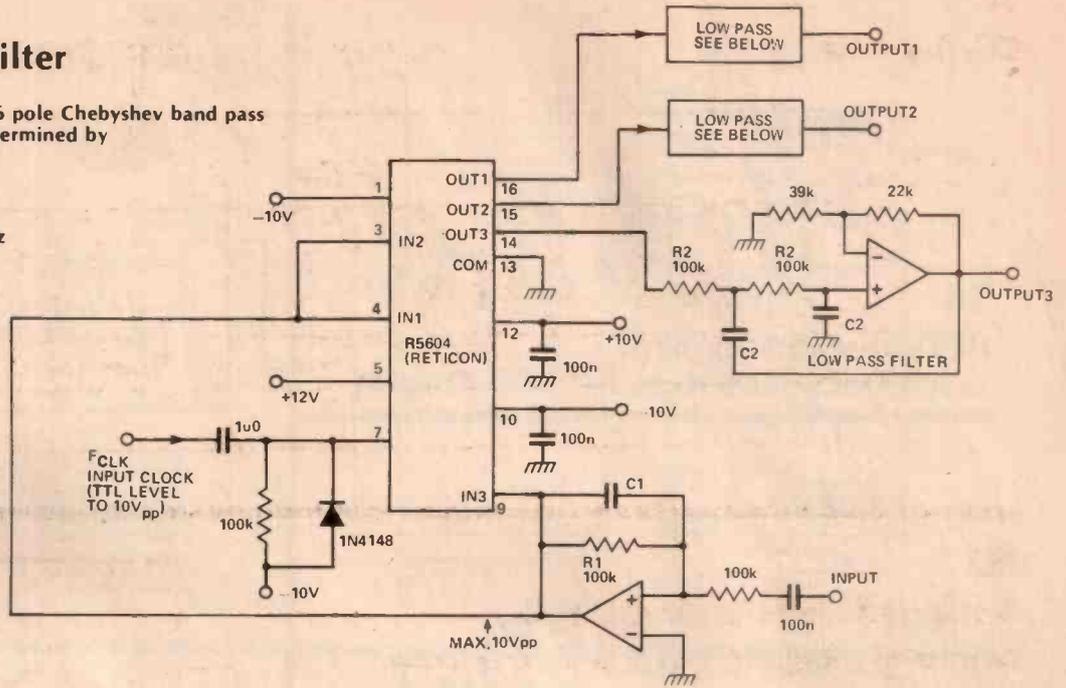
Frequency response of one device. To obtain lower octaves, merely divide input clock frequency by factors of 2.



13 3½ Digit LCD DVM

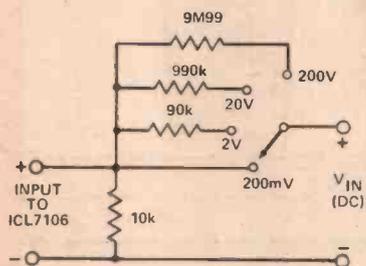


DC voltage inputs

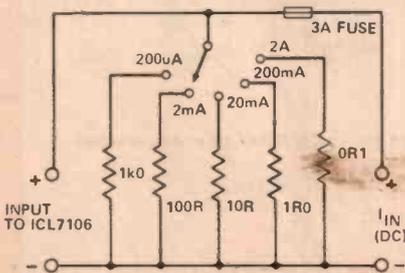
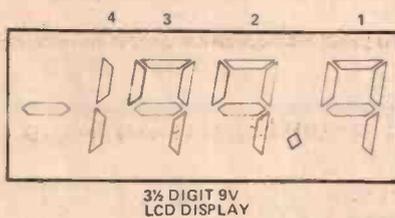


DC current inputs

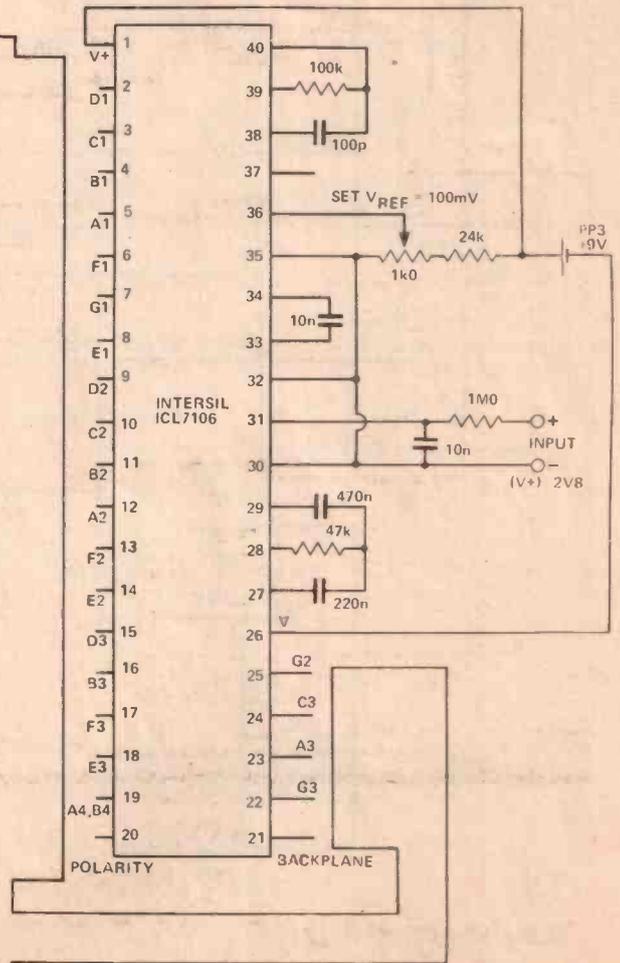Input voltage range = ± 200 mV
 Quiescent current = 0.8 mA
 Common mode input range = $(V+) - 0V5$ to $(V-) + 1V$
 Decimal point must be driven externally by EXORing the decimal point data with the backplane strobe



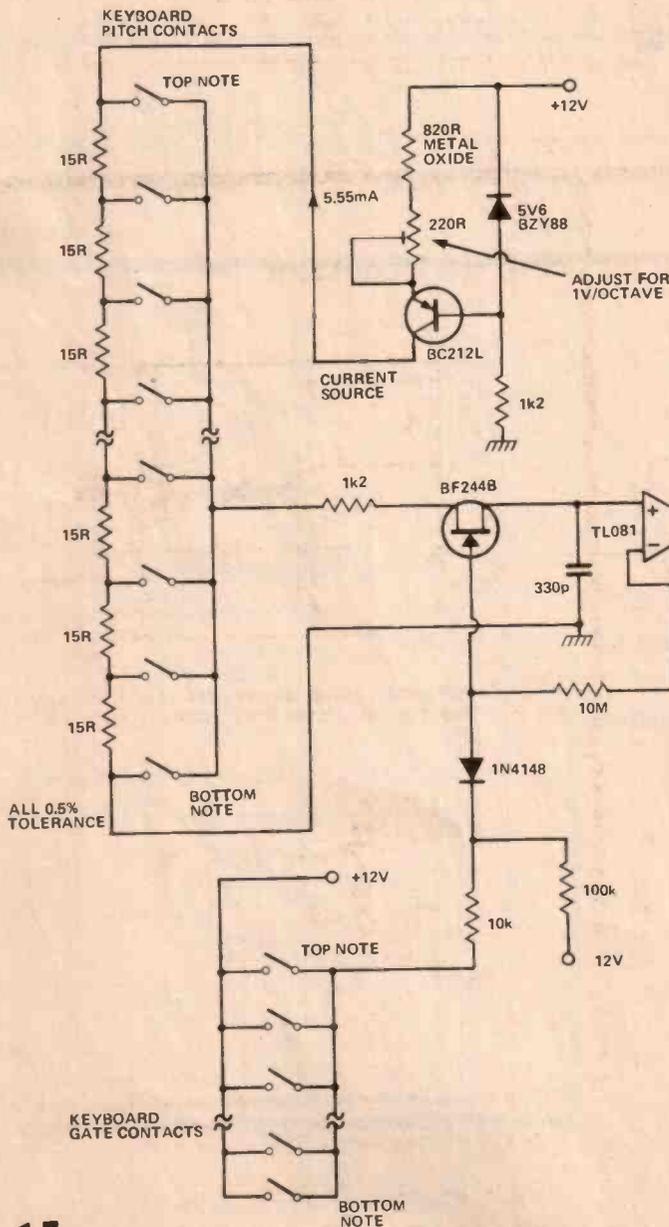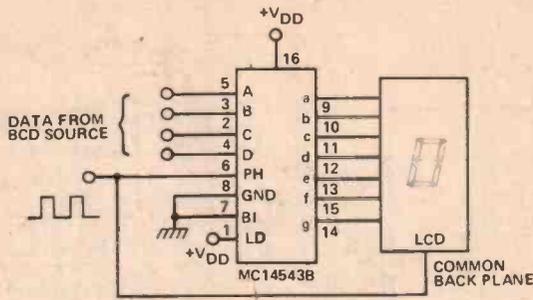
14 BCD-to-seven-segment Latch/Decoder/Driver for LCD Display




15 Keyboard Unit

Adjust the keyboard contacts so that the pitch contacts make before the gate contacts

16 Magnetic Field Detector

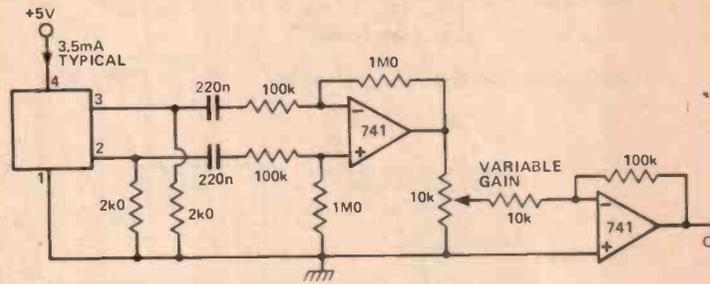


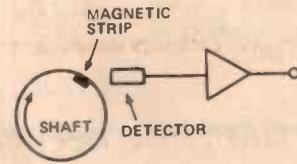Circuit is AC-coupled
The linear Hall effect IC is the 6345S2 (RS 304 267)
Maximum gain = +40 dB
Detector sensitivity = 7.5 mV to 10.6 mV/mT
Detector frequency response = DC to 100 kHz



Circuit can be used as a tachometer

17 Linear VCO (Ramp Waveform)

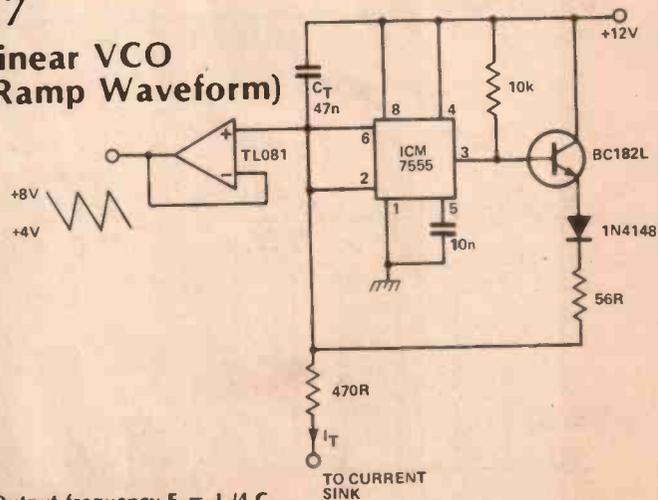

Output frequency $F = I_T / 4 C_T$

If $I_T = 1\text{mA}$, $C_T = 47\text{n}$, then $F = 5.3\text{kHz}$


18 Fast VCO

Oscillation frequency $F = I_T / 3C_T$ Hz


If $I_T = 2$ mA, $C_T = 330$ p, then $F = 2$ MHz

Alter C_T to increase F

Maximum frequency = 10 MHz

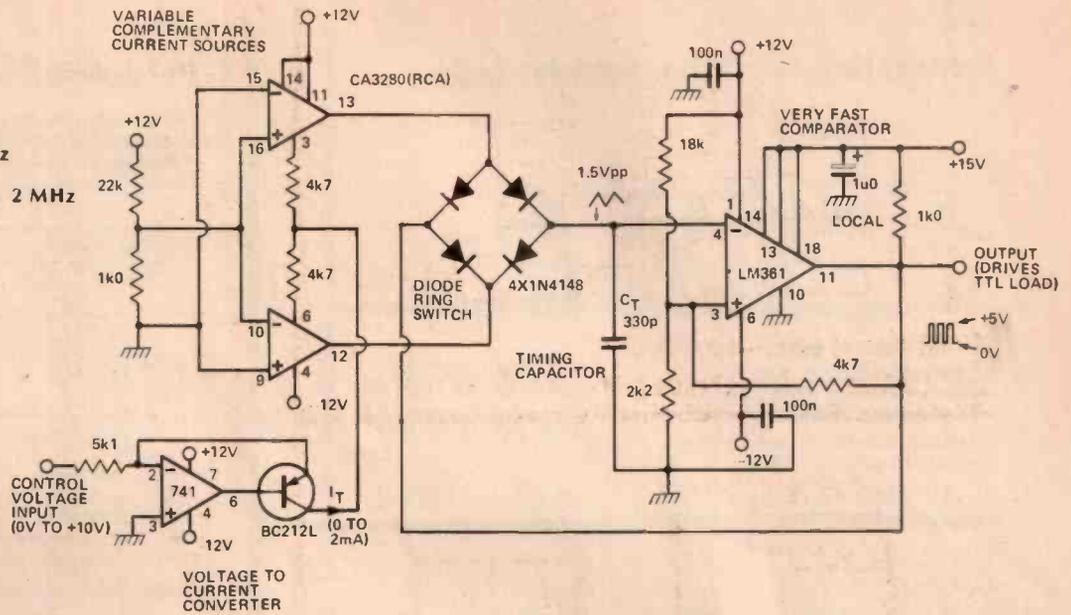

19 Precision Full Wave Rectifier

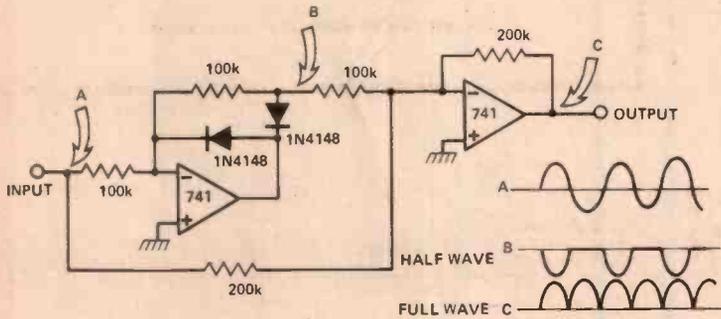


20 Band Pass Active Filter

$$F_c = 1/2\pi C\sqrt{R_A + R_B}$$

$$Q = 1/2\sqrt{R_A/R_B}$$


$$\text{Gain} = 2Q^2$$

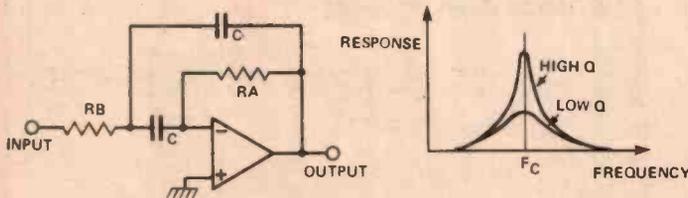


$$F_c = 1\text{kHz}, C = 15\text{n}$$

| RA | RB | Q | GAIN |
|------|------|-----|--------|
| 10k6 | 10k6 | 0.5 | x 0.5 |
| 21k2 | 5k3 | 1.0 | x 2.0 |
| 42k4 | 2k65 | 2.0 | x 8.0 |
| 84k8 | 1k32 | 4.0 | x 32.0 |

21 Battery Regulator

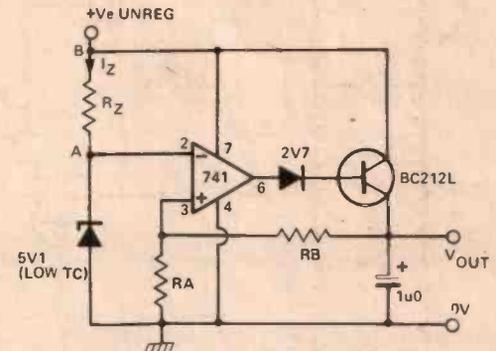

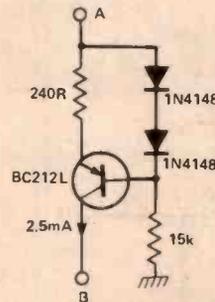A very low dropout voltage can be obtained by allowing Q1 to saturate. This gives maximum lifetime on battery power.



Better regulation can be obtained by replacing R_Z with this 2.5 mA current source. However, the unregulated supply rail must not drop below $(5V_1 + 1V_2) = 6V_3$

Select R_Z for an I_Z of about 2.5 mA

$$V_{OUT} = 5V_1 \times (R_A + R_B) / R_A$$


Minimum $V_{OUT} \sim 6V$

Dropout voltage = $V_{CE}(Q1 \text{ saturated}) \sim 0V_3$

Keep I_{OUT} less than 50 mA

22

Generating Negative Supply Rails

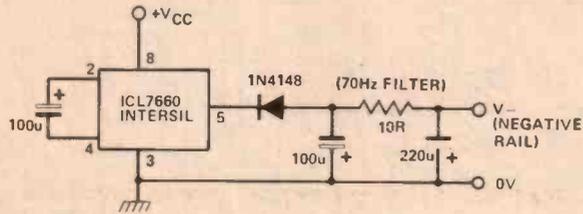


$V_- = (+V_{CC} - 0V7)$
 Typical efficiency = 98%
 Quiescent current = 170 μ A
 $+V_{CC}$ range = 3 to 10 V
 Maximum output current = 40 mA
 Output resistance = 55R


23

Low Impedance Source Preamp

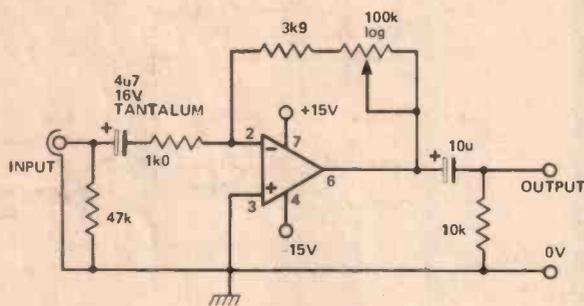Very low input noise
 Input noise = 4 nV/\sqrt{Hz}
 Equivalent input noise voltage = 0.56 μ V_{RMS} (20 kHz bandwidth)
 Input impedance = 1k Ω (suitable for microphone)



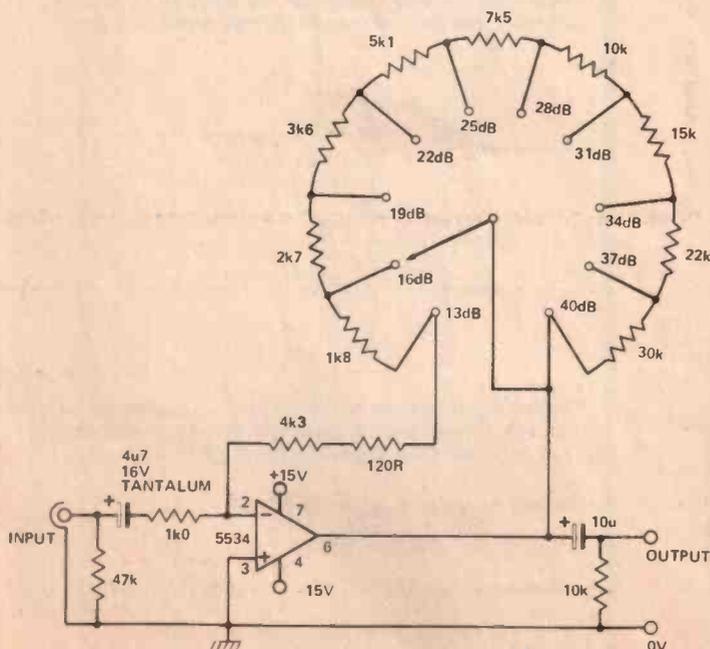Variable gain; x 3.9 to x 100 (12 dB to 40 dB)




Switched gain; 3 dB steps


24

Precision Power Supplies

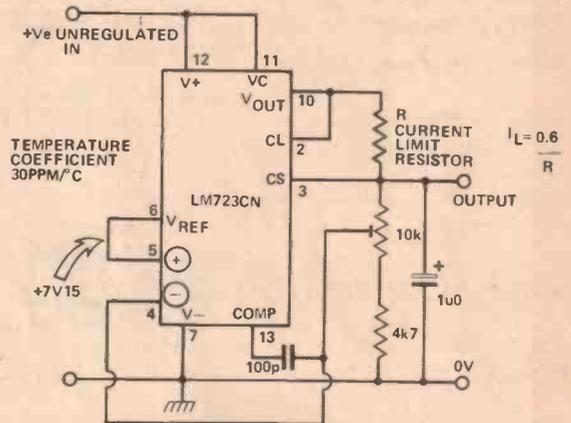723 general specifications:
 Maximum input voltage = 40 V
 Maximum current output = 150 mA
 Output voltage range = 2 to 37 V



Adjustable +7 V to +21 V

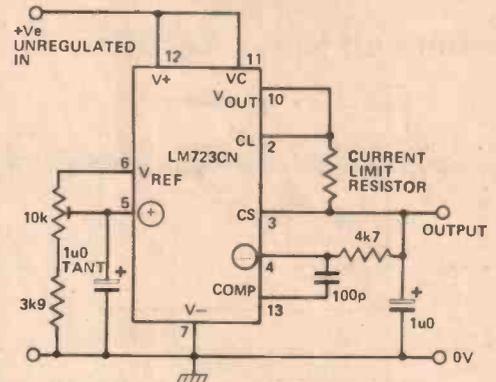


Adjustable +2 V to +7 V

25


True RMS Measurement

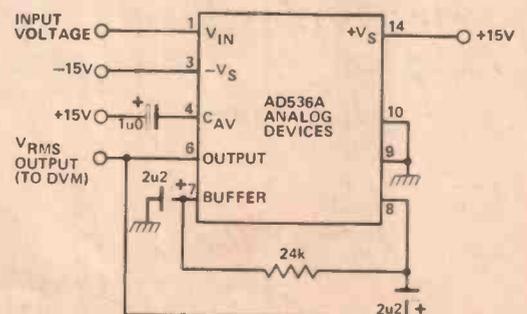Input voltage 7 V_{RMS} maximum
 Bandwidth: 300 kHz, V_{RMS} > 0V1
 Error of 1% for a crest factor of 7
 Quiescent current = 1mA
 60 dB range




30

Schmitt Triggers

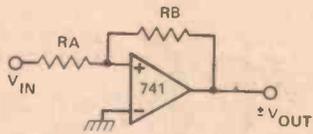


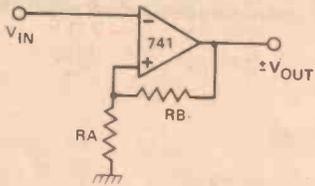Non-inverting; input hysteresis levels = $\pm(RA/RB) \times V_{OUT}$



Inverting; input hysteresis levels = $\pm(RA/(RA + RB)) \times V_{OUT}$

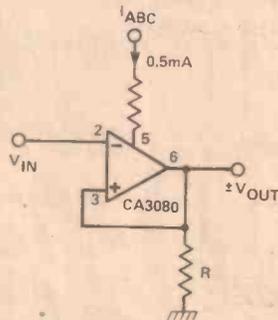Note that V_{OUT} depends on the supply voltage and the individual op-amp




Transconductance type; input hysteresis levels = $\pm V_{OUT}$; $V_{OUT} = R \times I_{ABC}$

R can be replaced by two 1N4148 diodes back-to-back

32


Mains Power Supply Unit

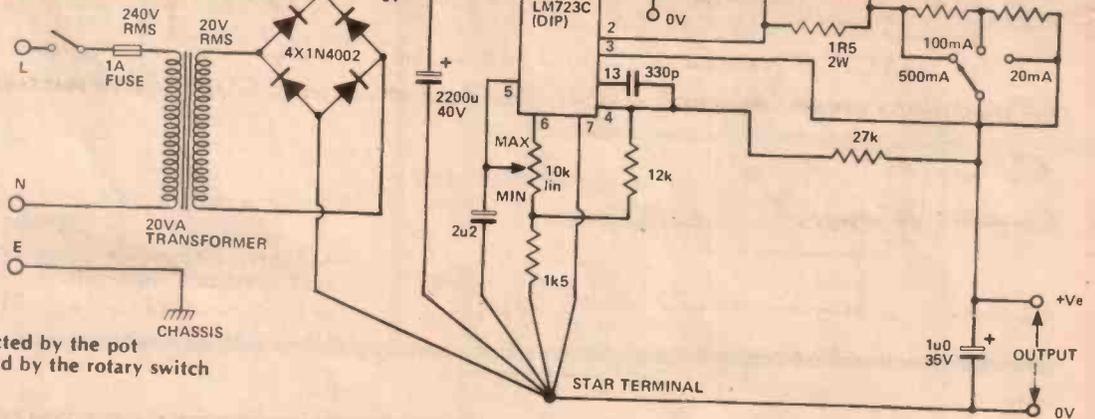

Variable output voltage is selected by the pot
Variable current limit is selected by the rotary switch
Output voltage is 0 to +20 V

31

Fast Oscillator

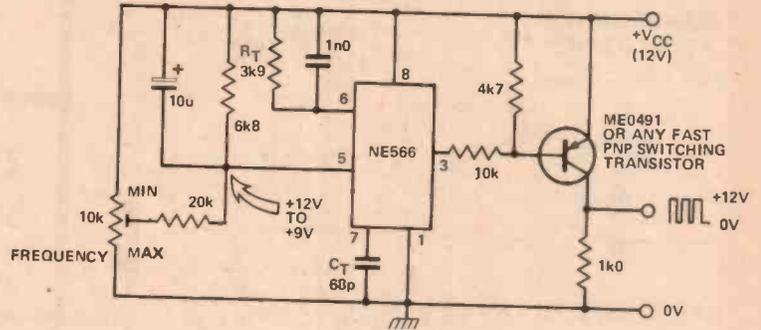


Bias voltage on pin 5, $V_B = \frac{1}{4} V_{CC}$ to V_{CC}

V_B gives a 10 to 1 control range


Typical frequency = 1 MHz

33

Standard Eight-bit DAC

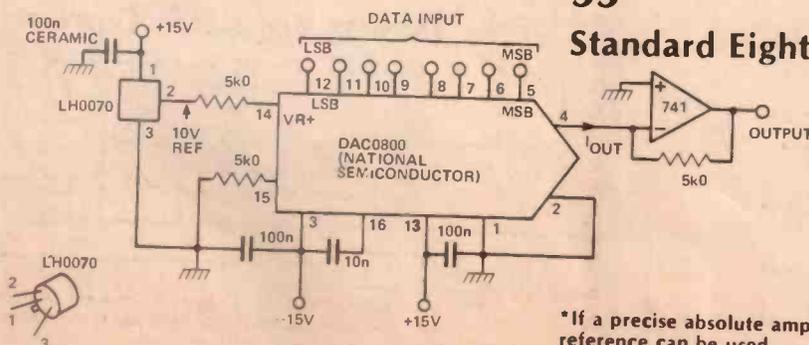

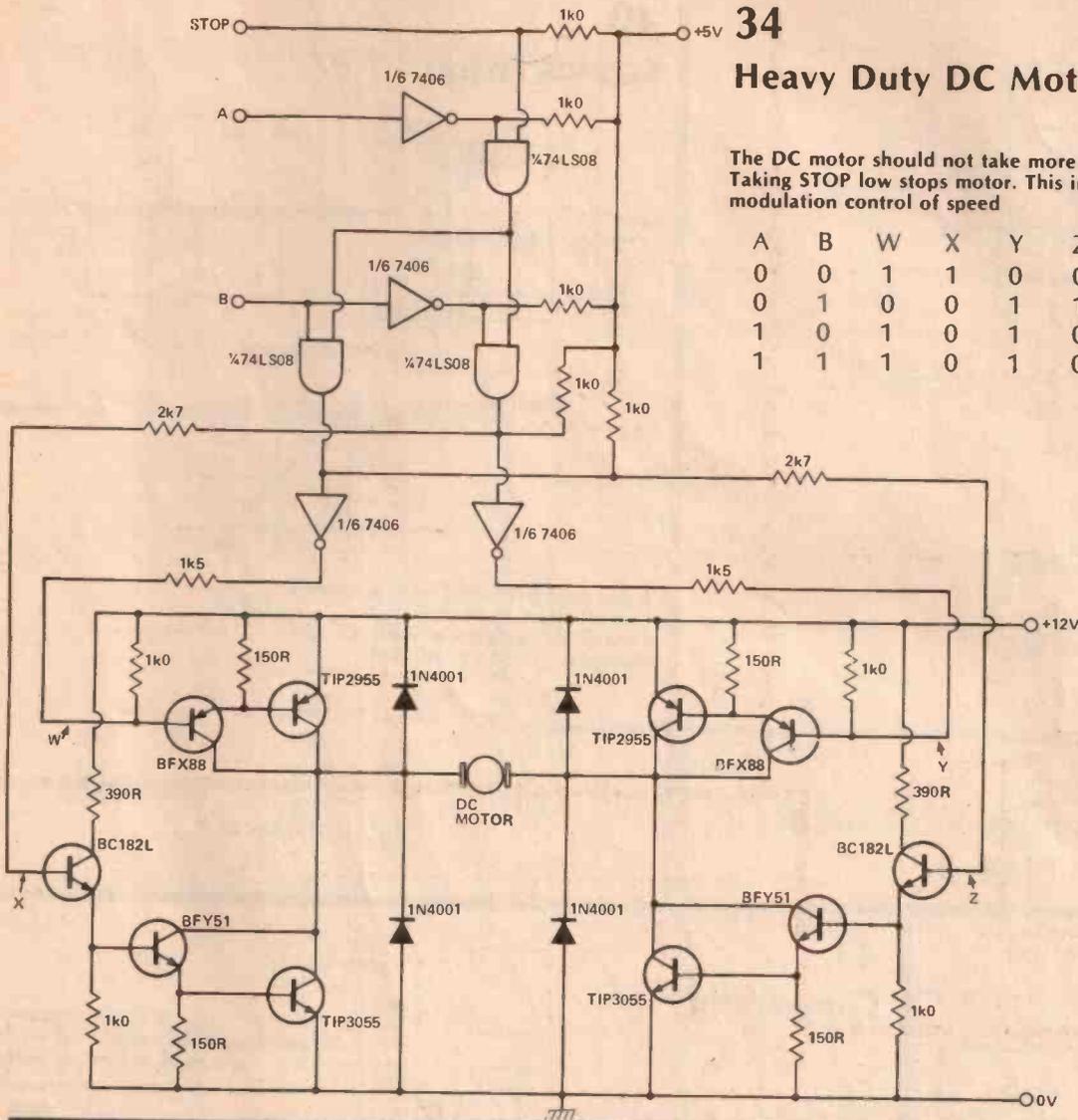*If a precise absolute amplitude is not needed, then a zener diode reference can be used



34 Heavy Duty DC Motor Control


The DC motor should not take more than 3 to 4 A continuous current Taking STOP low stops motor. This input can be used for mark/space modulation control of speed

| A | B | W | X | Y | Z | |
|---|---|---|---|---|---|---------|
| 0 | 0 | 1 | 1 | 0 | 0 | REVERSE |
| 0 | 1 | 0 | 0 | 1 | 1 | FORWARD |
| 1 | 0 | 1 | 0 | 1 | 0 | OFF |
| 1 | 1 | 1 | 0 | 1 | 0 | OFF |


35 Current Mirrors

If $\beta = 100$, $I_2/I_1 = 0.98$


*Matched transistors with the same β

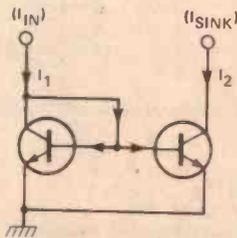

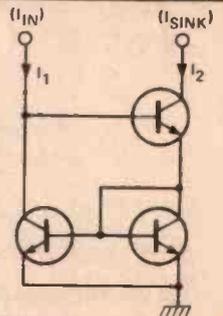This improved mirror gives a better I_2/I_1 performance with lower values of β . Also the I_{SINK} current sink has a much higher output slope resistance.




36 Increasing Regulator Voltages

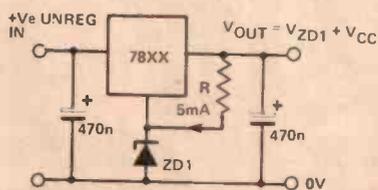



Increasing the output voltage using a zener diode.

37 Increasing Regulator Currents

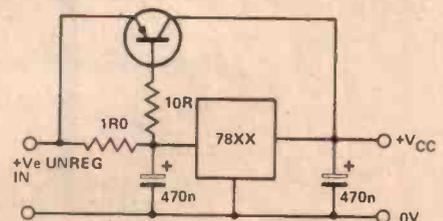

Using a bypass transistor to increase the output current drive. The first 600 mA flows through the regulator, the rest via the external transistor.

38 Rumble Filter

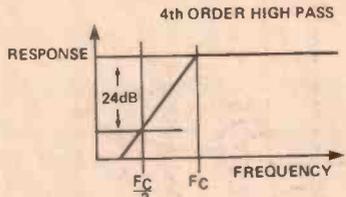
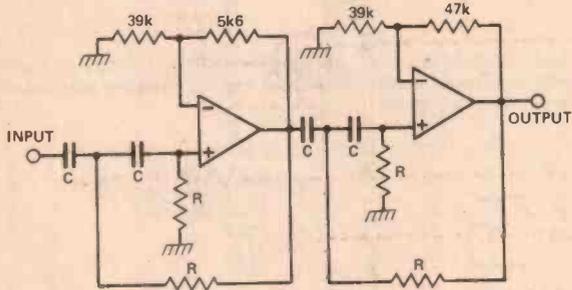


Roll-off slope = 24dB/octave
 Overall voltage gain = x 2.6 (8.3 dB)
 Op-amps are 741's or RC4558

| F_c | C | R |
|--------|------|-----|
| 25 Hz | 100n | 62k |
| 50 Hz | 100n | 30k |
| 100 Hz | 100n | 15k |
| 200 Hz | 100n | 7k5 |

(5% tolerance)

40 Scratch Filter

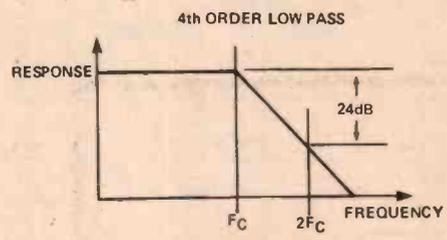
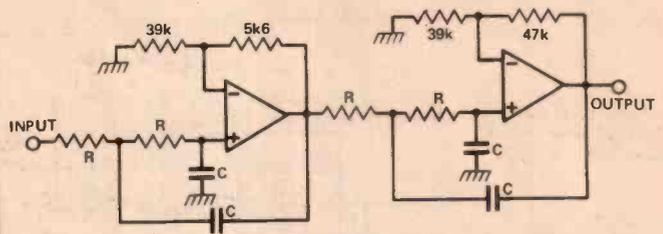


Input must have a DC path to ground
 Roll-off slope = 24 dB/octave
 Overall voltage gain = x 2.6 (8.3 dB)
 Op-amps are 741's or RC4558



| F_c | C | R |
|---------|-----|-----|
| 10 kHz | 1n5 | 10k |
| 7.5 kHz | 1n5 | 14k |
| 5 kHz | 1n5 | 20k |

(5% tolerance)

39 Monostables

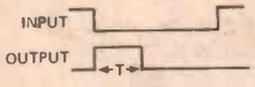
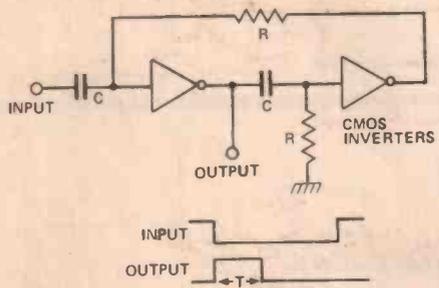


CMOS inverters
 $T = 1.38RC$
 Keep R greater than 47k

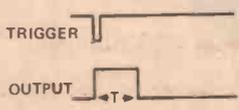
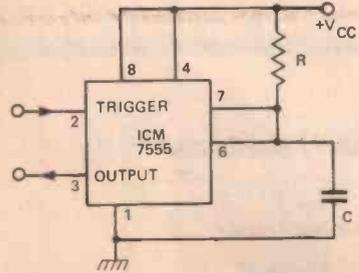


CMOS 555
 $T = 1.1RC$

41 Comparators

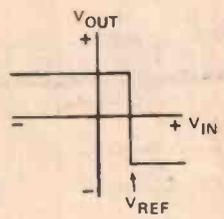
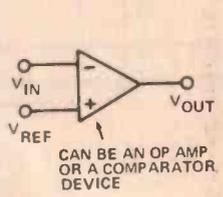


Response of a simple comparator

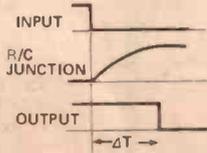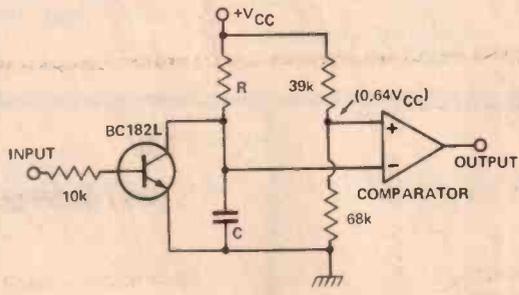

Time delay generator; $\Delta T = RC$

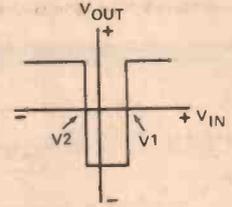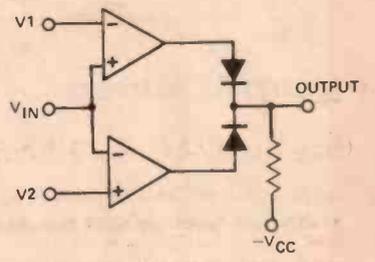Window comparator
 V1 and V2 can be defined by resistors
 or can be set by any voltage
 Note that V1 must be more positive
 than V2






Standard comparators
 LM311 single
 LM339 quad
 LM361 very fast single
 LM3914 linear 10-section
 LM3915 log 10-section

42

Triangle To Sine Wave Converter

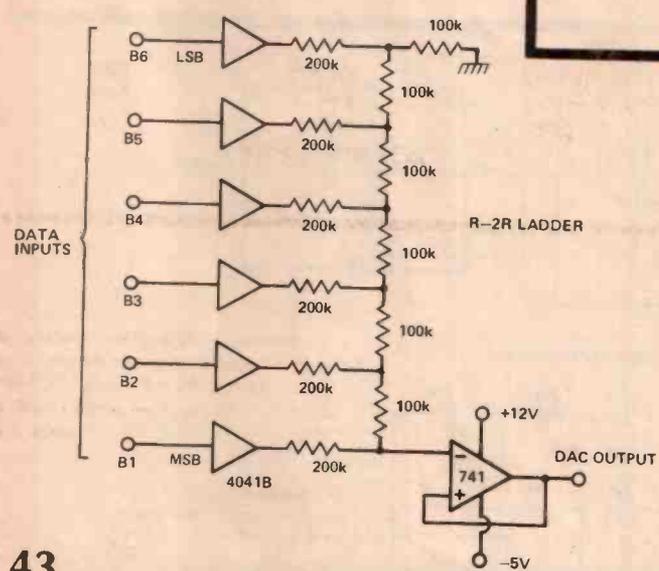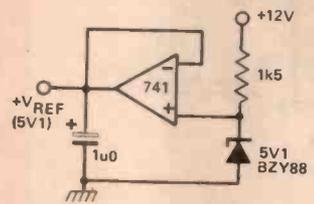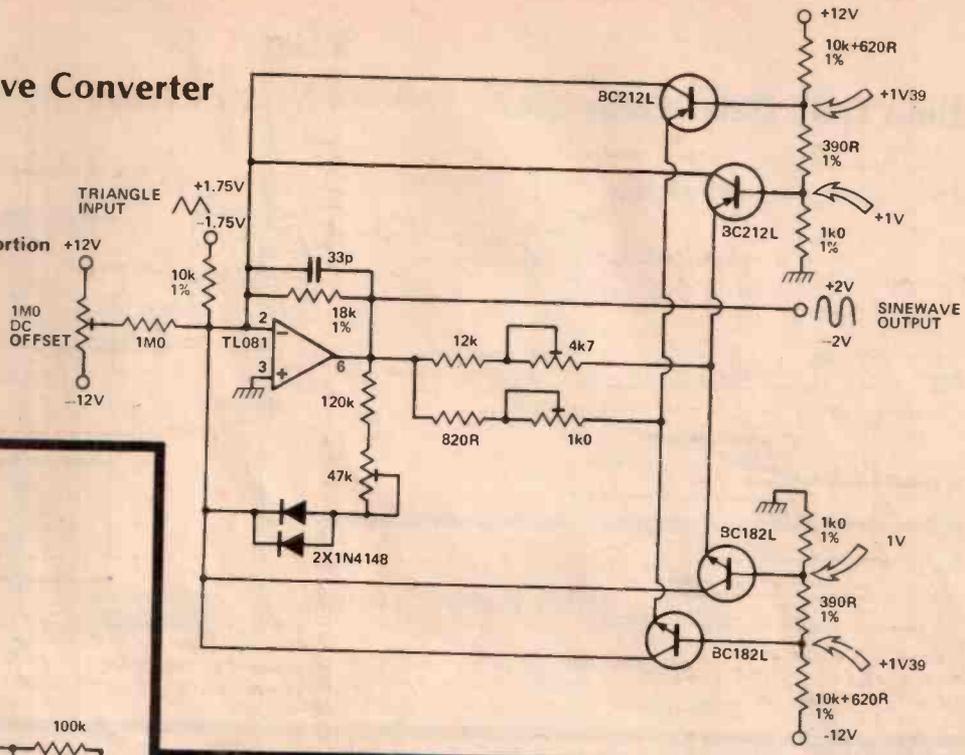Adjust all presets for minimum distortion
 Typical THD = 1%
 Best THD = 0.5%






43

Six-bit DAC — 10-bit Precision

Buffers powered from 0 V and +V_{REF}
 Resistors in ladder need 0.1% tolerance
 DAC output has 64 steps

44

50 Hz Notch, Variable Q

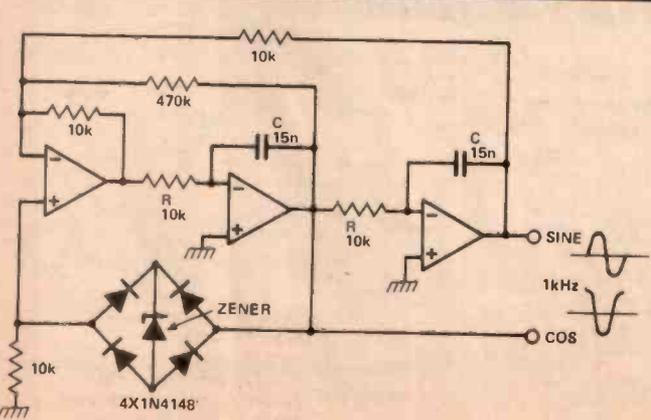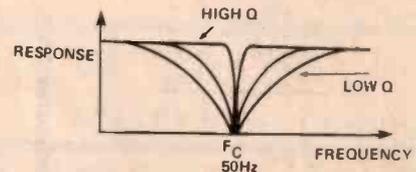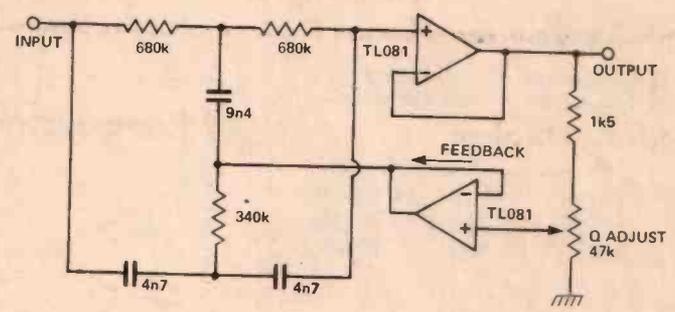

45

Dual Integrator Oscillator

Quadrature outputs (ie sine and cosine)



$$\text{Output frequency } F = \frac{1}{2\pi RC} \text{ Hz}$$

To change frequency, change both R's or both C's.
 Maximum frequency ~ 20 kHz
 Minimum frequency ~ 0.016 Hz using C = 1μ0, R = 10M, and TL081 op-amps
 Oscillation amplitude = 2x(zener voltage + 1V2) V_{pp}

46

Multiple Time Delay Generator

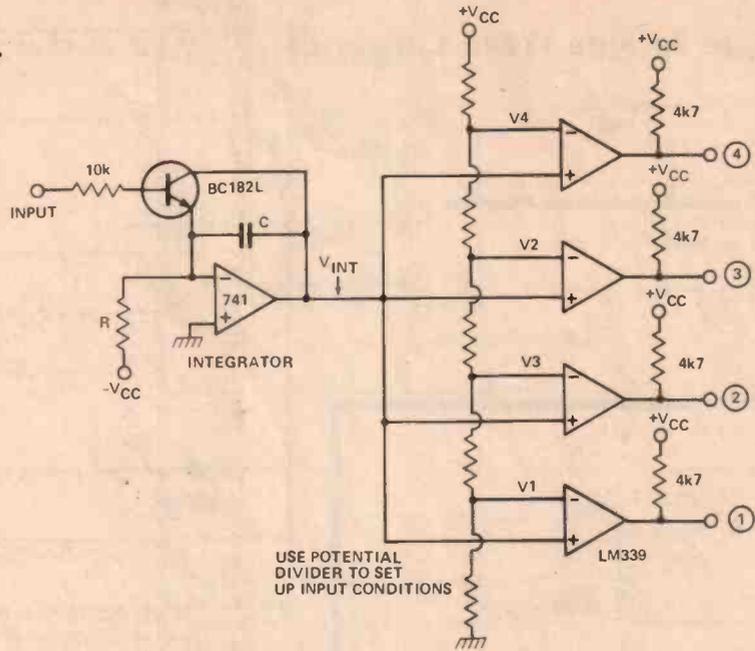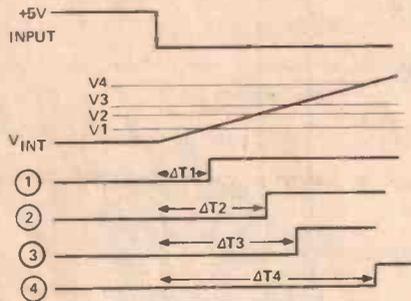Ramp rate = $-(-V_{cc}/CR)$ volts per second



47



Low Pass Active Filters

Inputs must have a DC path to ground


$$F_c = \frac{1}{2\pi RC}$$

2 pole roll-off = -12 dB/octave
4 pole roll-off = -24 dB/octave

| R | C | F _c |
|------|-----|----------------|
| 107k | 15n | 100 Hz |
| 10k7 | 15n | 1 kHz |
| 10k7 | 1n5 | 10 kHz |

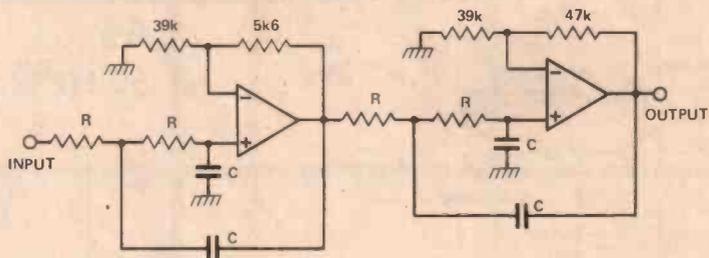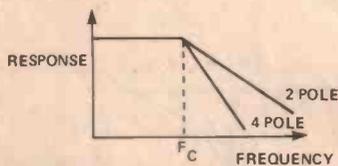

4 pole Butterworth

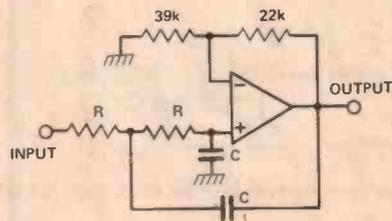


2 pole Butterworth

48

Inverting Peak Voltage Detector

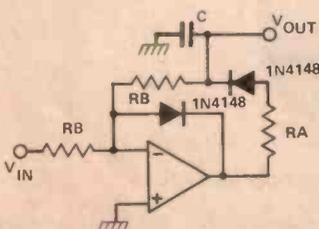Attack time constant = C.RA
Decay time constant = C.RB



This circuit works well at high frequencies


49

Non-inverting Peak Voltage Detector

Input must have a DC path to ground

Keep RA greater than 1k0 to avoid dumping large currents to ground via C

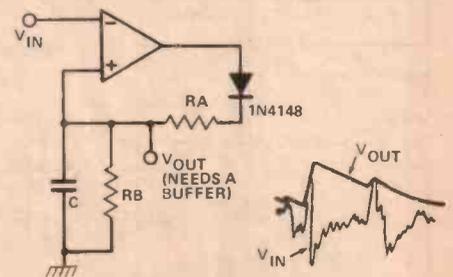Attack time constant = C.RA
Decay time constant = C.RB



This circuit is not suited for high frequency operation

50


High Pass Active Filters

$$F_c = \frac{1}{2\pi RC} \text{ Hz}$$


2 pole roll-off = +12 dB/octave

4 pole roll-off = +24 dB/octave


| R | C | F _c |
|------|-----|----------------|
| 107k | 15n | 100 Hz |
| 10k7 | 15n | 1 kHz |
| 10k7 | 1n5 | 10 kHz |

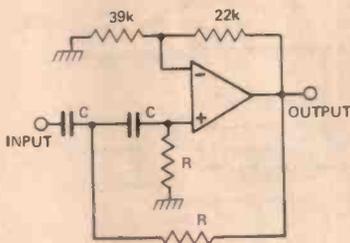

2 pole Butterworth

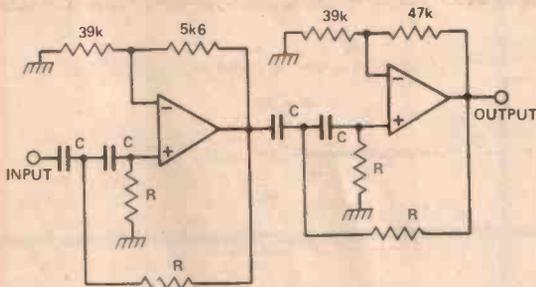


4 pole Butterworth

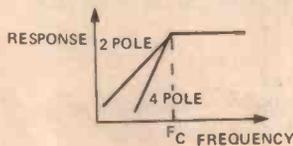

52


Bass And Treble Tone Control

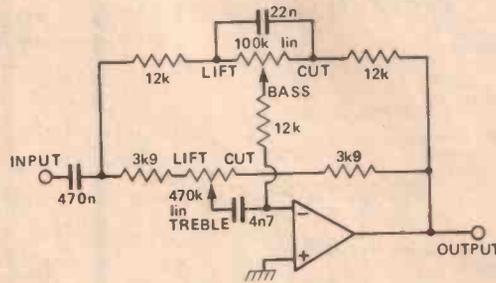


53

Active Notch Filter

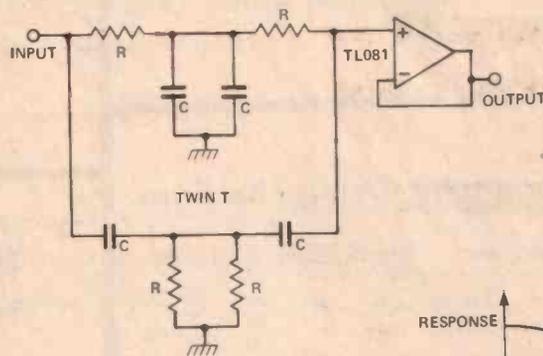The two R's in parallel represent R/2
The two C's in parallel represent 2C
For 50 Hz, R = 680k, C = 4n7 (a hum remover)




$$F_c = \frac{1}{2\pi RC}$$

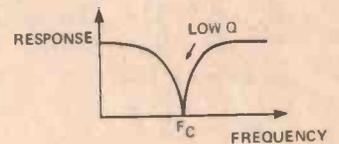


51

Double Tuned Band Pass

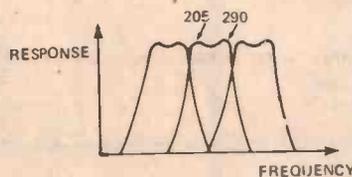Filter section has been designed for one octave spacing. To alter the components for the other octaves, scale the resistors or the capacitors, ie changing C to 7n5 increases the filter frequency by one octave.




Typical filter bank response

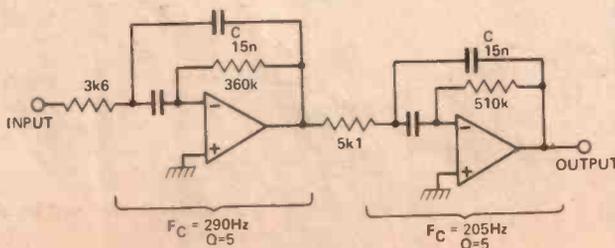

54


Middle Tone Control

Input must have a DC path to ground

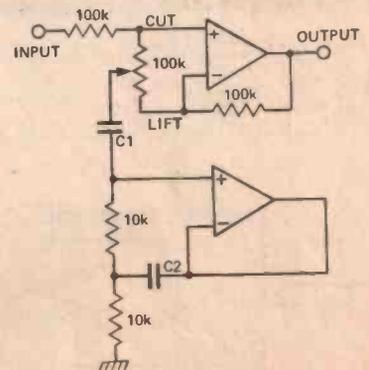

55


Switch Debouncing Using Schmitt Triggers

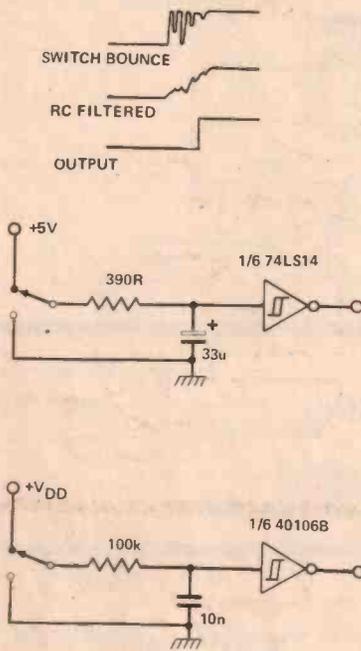

56

Switch Debouncing Using Flip-flops

| Flip-flop using NOR gates | | | | Flip-flop using NAND gates | | | |
|---------------------------|---|---|-----------|----------------------------|---|---|-----------|
| S | R | Q | \bar{Q} | S | R | Q | \bar{Q} |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |

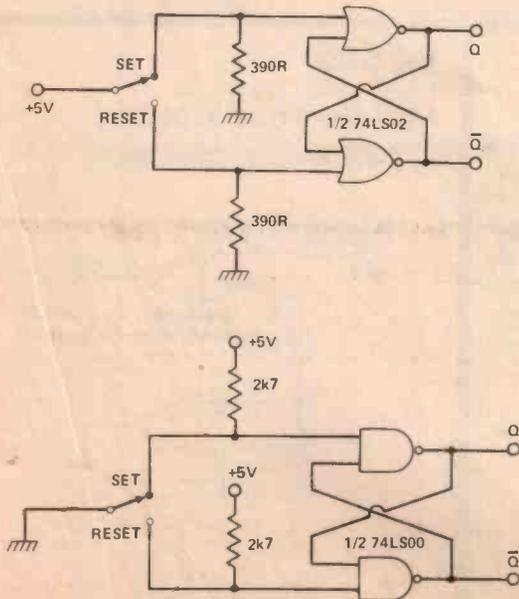


57

Log Converter

V_{OUT} changes by 1 V for every octave change of the I_{IN} current

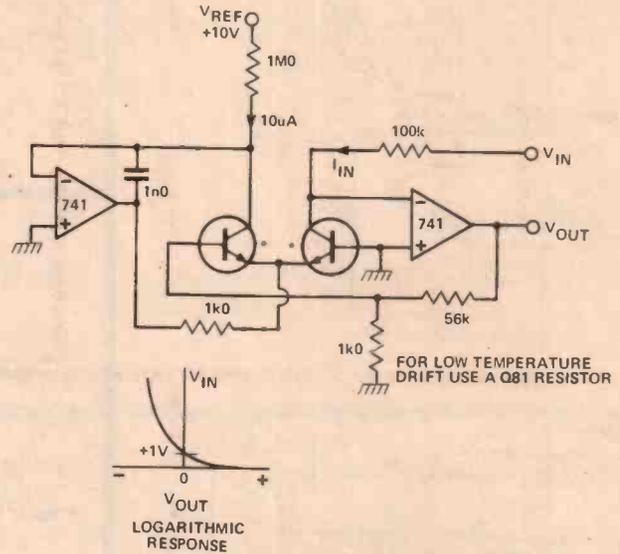
*The matched transistors can be two BC212L in thermal contact, or a dual transistor (LM394), or part of an array (CA3046)



58

Antilog (Exponential) Converter

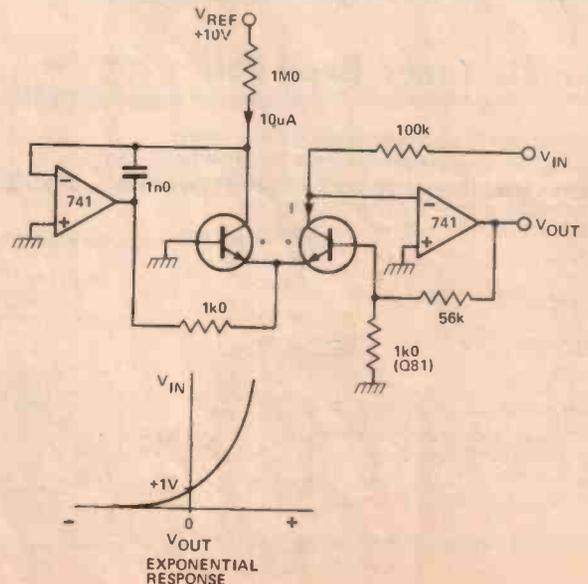
$V_{OUT} = I \times 100k$
 The current I doubles for every 1 V increase of V_{IN}
 When $V_{IN} = 0$ V, $I = 10 \mu A$



59

Low Voltage Power Amp

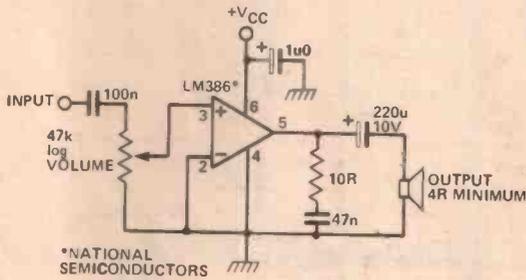
Voltage gain (fixed) = x 20 (26 dB)
 +V_{CC} range = +4 V to +12 V
 Typical quiescent current = 4 mA (suitable to PP3 use)
 Output power = 0W7 (if +V_{CC} = 9V, speaker = 8R)
 THD = 10%



61

Staircase Generator

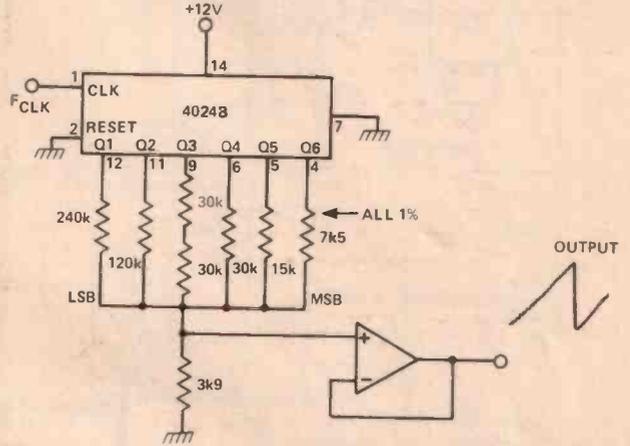Output frequency $F = F_{CLK}/64$
 Staircase is made up of 64 steps





60

5 A Regulator

LM338 parameters:
 Maximum input/output difference = 35 V
 Maximum output current = 5 A
 Ripple rejection = 85 dB
 Thermal resistance, junction to case = 1°C/W

$$V_{OUT} = 1.25 (R1 + R2)/R1$$

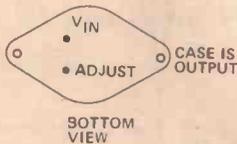
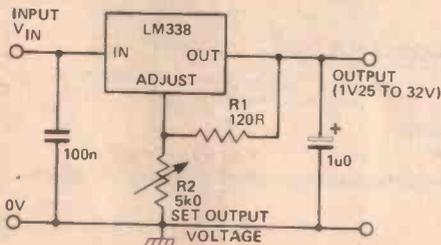
$$P_{DISS} = I_{OUT}(V_{IN} - V_{OUT}). \text{ Use a heatsink.}$$



62

Notch Filter (Hum Remover)


Notch frequency = $1/2 \pi RC$

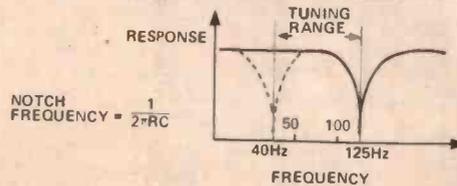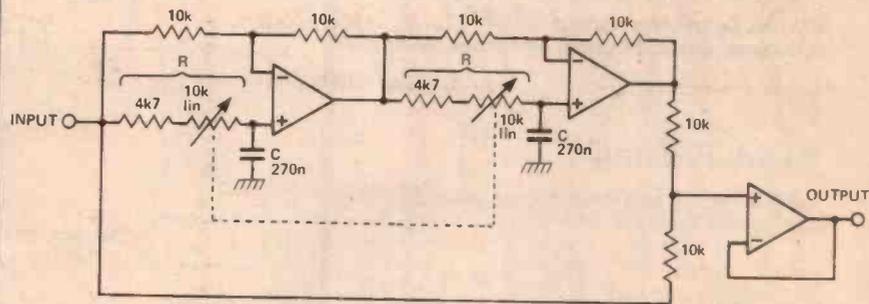

63


Graphic Equaliser

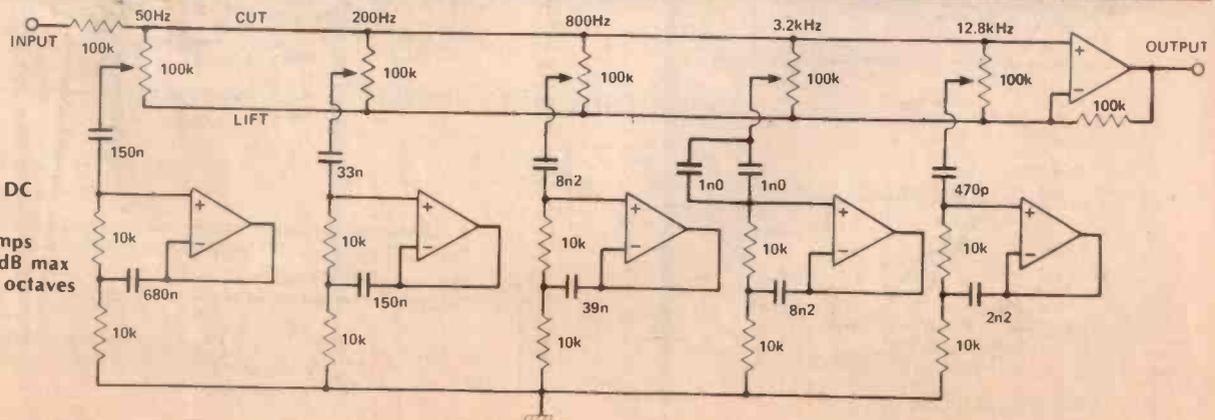Input must have a DC path to ground
 Use 741's for op-amps
 Cut and lift = 13 dB max
 Filter spacing = 2 octaves




64

Exponential Current Sink

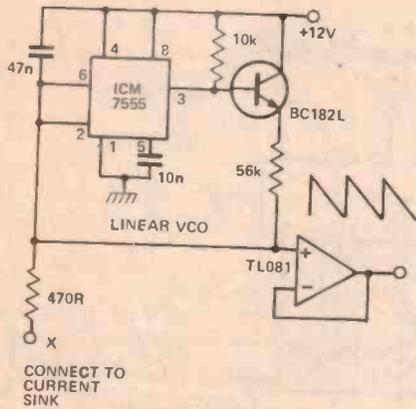

CONNECT TO CURRENT SINK


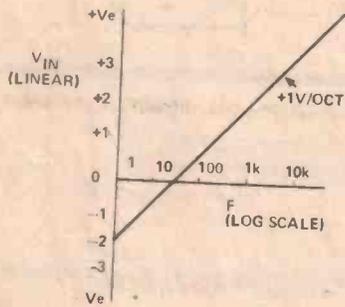


Frequency response of a linear VCO driven by an exponential current sink


65

RIAA Preamp

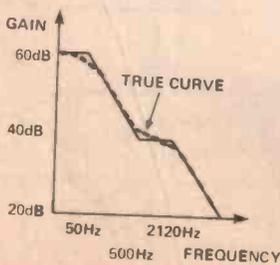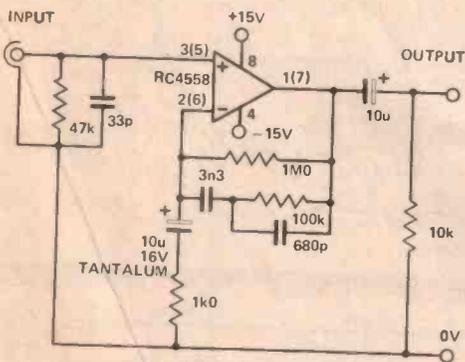Suitable for use with magnetic cartridge
Use RC4558 for low noise




RIAA playback curve

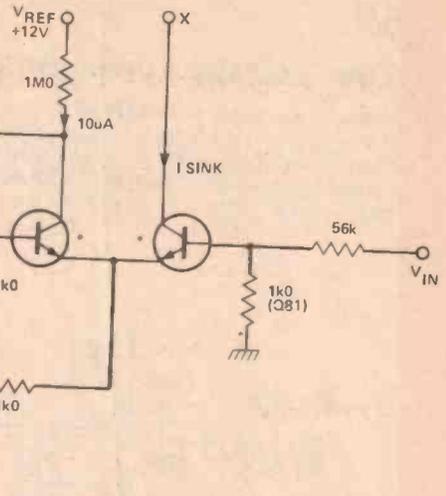

*Matched transistors in thermal contact

66

Exponential Current Source




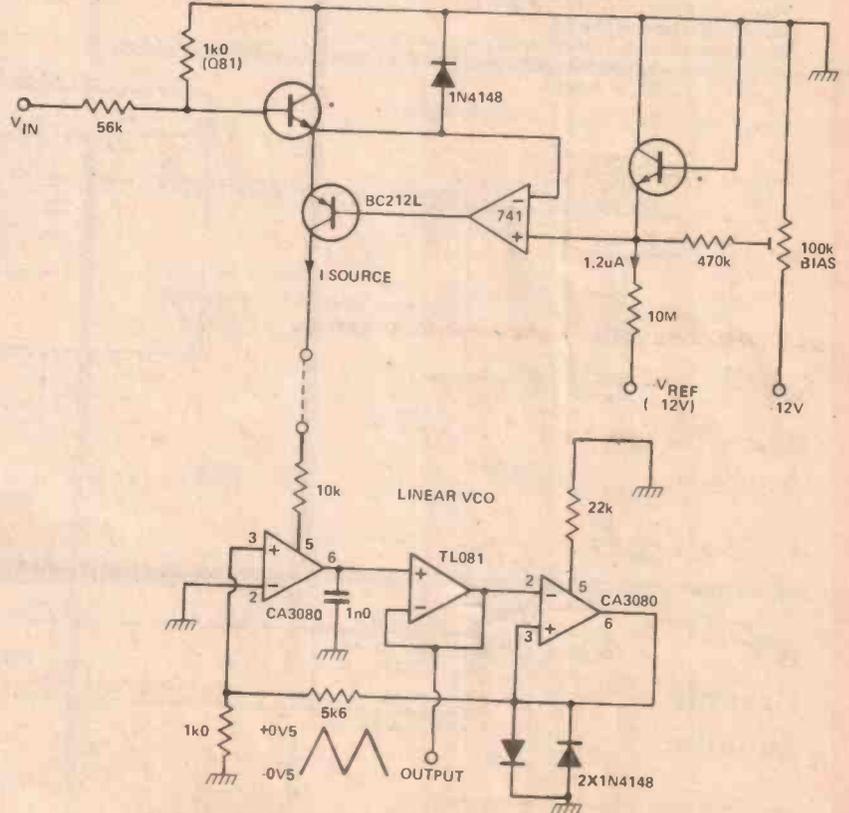


An exponential current source can be used to drive a linear VCO. The VCO then has a 1 V/octave response

Devices all powered from ± 12 V


*Matched transistors in thermal contact

67 Voltage-to-current Converters

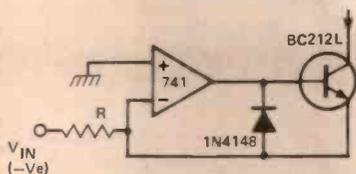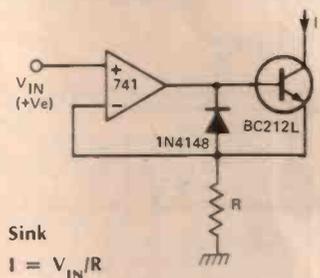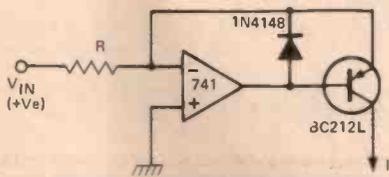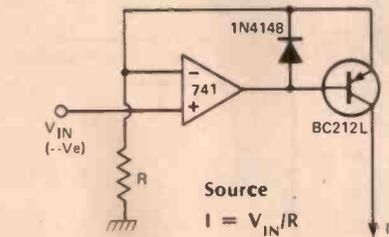

68 Wien Bridge Sine Wave Oscillator

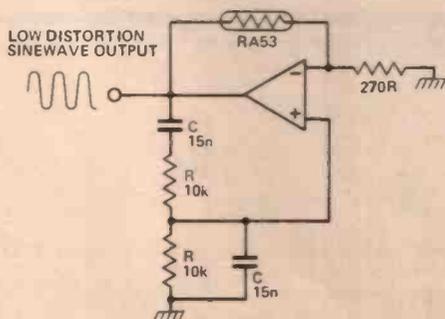
Output frequency $F = \frac{1}{2\pi RC}$ Hz



The RA53 is a negative temperature coefficient thermistor; it sets A_v to 3 for stable oscillation.


69 Frequency-to-voltage Converter

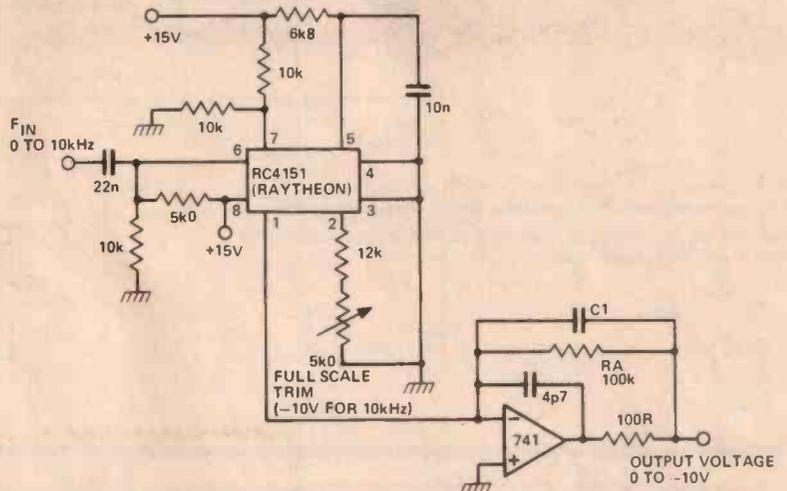With $C1 = 100n$, ripple is 100 mV
Response time = $RA.C1$
If $RA = 100k$, $C1 = 100n$, response time = 10 ms




70 Eight-bit ADC

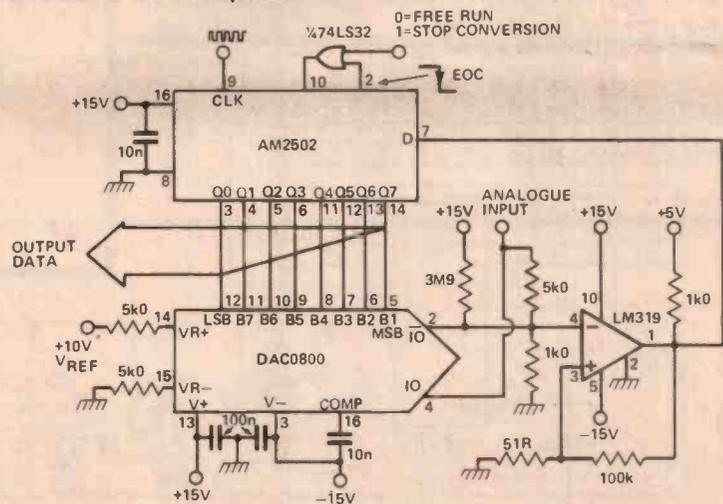This circuit uses an eight-bit DAC plus a successive approximation register.
Conversion time 9 clock periods



71 Electronic Shutdown

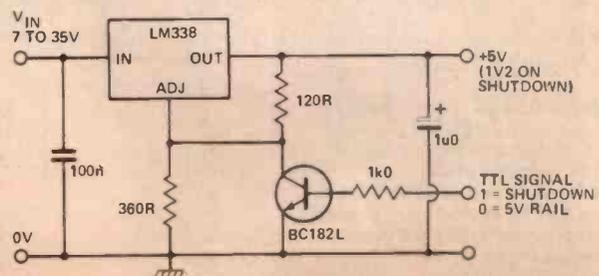


72

State Variable Filter

$$F_c = \frac{1}{2\pi RC} \text{ Hz}$$


Gain = Q
Q and F_c are independently variable. F_c may be tuned with a double gang pot (for R). Q factors as high as 100 may be obtained. All responses track with frequency.

| R | C | F_c |
|------|-----|--------|
| 107k | 15n | 100 Hz |
| 10k7 | 15n | 1 kHz |
| 10k7 | 1n5 | 10kHz |

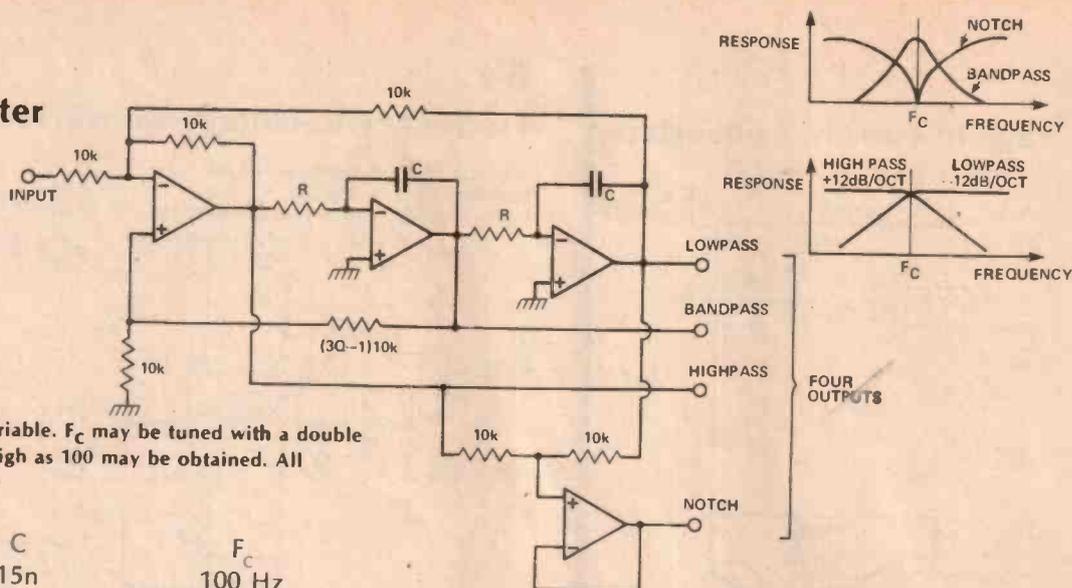


73

FET Audio Switching

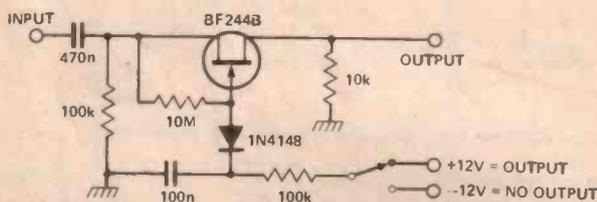


74

LDR Audio Switching

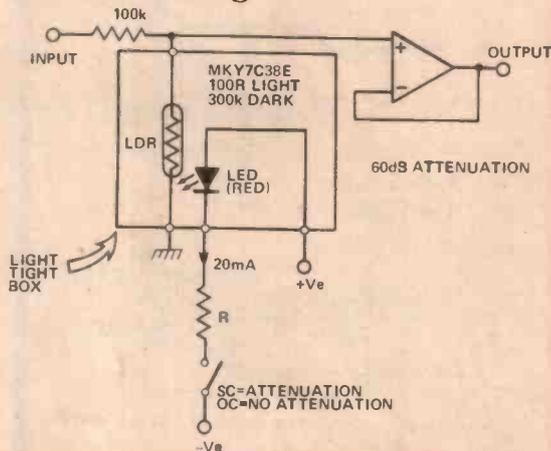

PUSH-TO-MAKE SWITCH CONTACTS

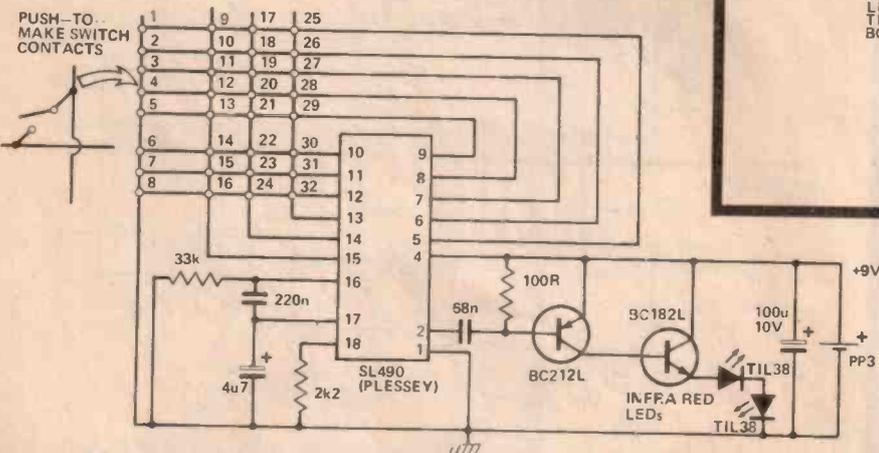

75

Infra-red Transmitter


Standby current = 6 uA
Operating current = 8 mA
32 commands (five-bit code)

76

Infra-red Receiver


Plessey receiver chip range

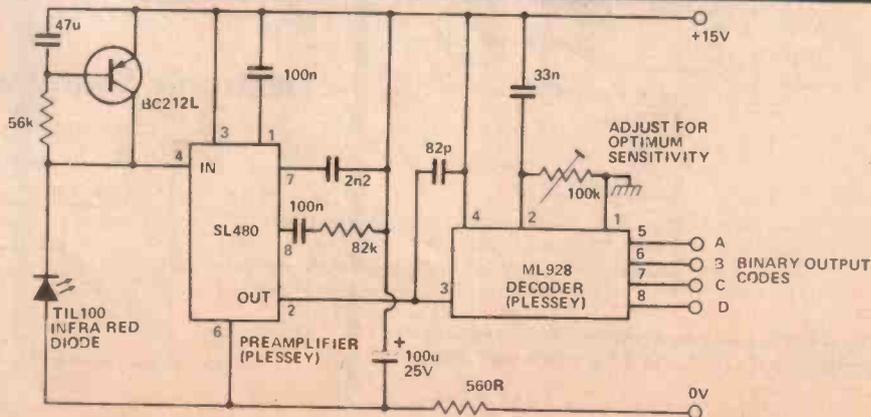- ML928 codes 1 to 16 latched
- ML929 codes 17 to 32 latched
- ML926 codes 1 to 16 momentary
- ML927 codes 17 to 32 momentary
- ML920 20 outputs and three analogue channels
- ML922 10 outputs and three analogue channels
- ML923 16 outputs and one analogue channel
- ML924 five bit code output
- ML925 multifunction for toys



77

Function Generator

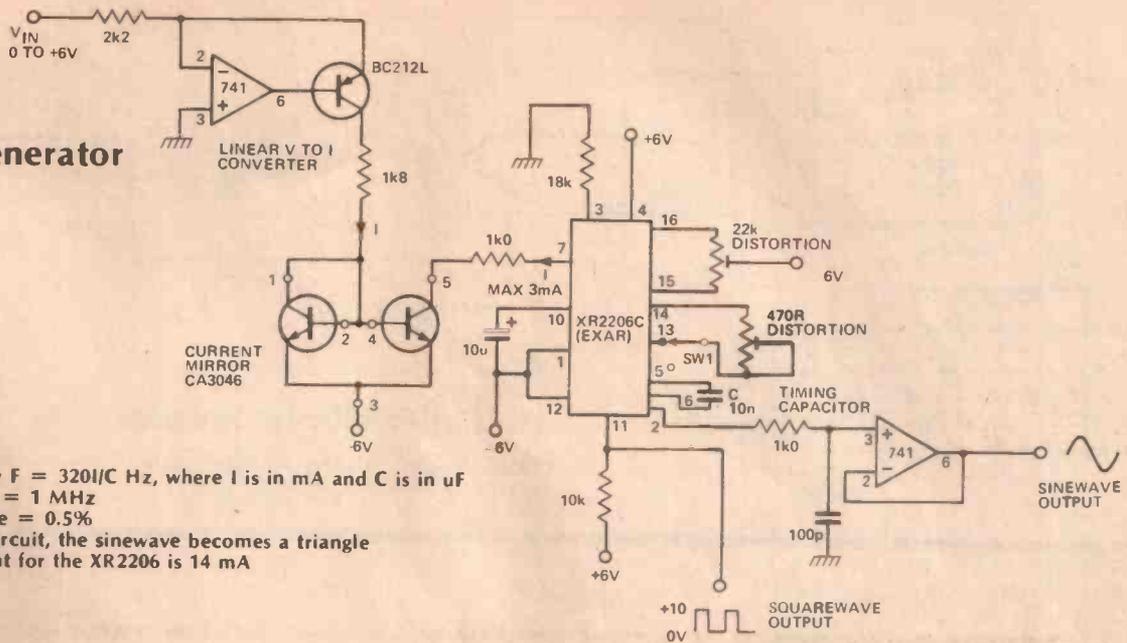


Oscillation frequency $F = 320I/C$ Hz, where I is in mA and C is in μF
 Maximum frequency = 1 MHz
 Best THD of sinewave = 0.5%
 When SW1 is open-circuit, the sinewave becomes a triangle
 Typical supply current for the XR2206 is 14 mA

78

Analogue Delay Line


Delay time $\Delta T = 512 / (\text{clock frequency} \times 4)$
 Signal bandwidth (F_c) \leq clock frequency/6

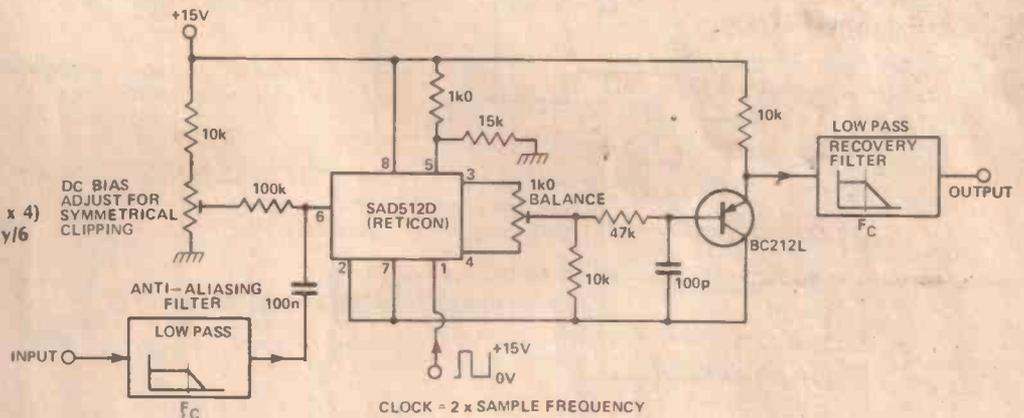If clock frequency = 60 kHz
 $\Delta T = 512 / (60,000 \times 4) = 2.13$ ms
 Bandwidth = 10 kHz




79

Voltage Regulators

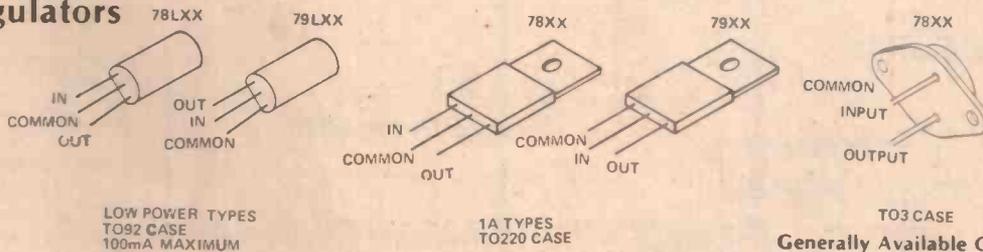


78XX series
 +5V
 +12V
 +15V
 +18V
 +24V


79XX series
 -5V
 -12V
 -15V
 -18V
 -24V

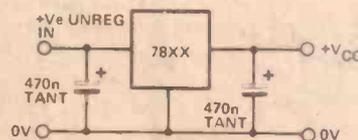

Generally Available Output Voltages

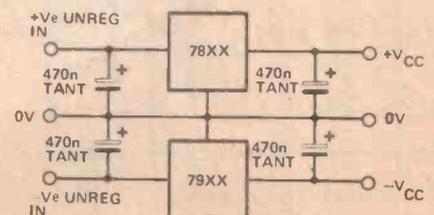


Refer to manufacturer's information for maximum input voltage. Typically this is 25 V for 5 V devices and 35 V for all others. Regulators need about 2 V difference between the unregulated rail and the output rail. Less than this, and the output rail will collapse. Note that the power dissipated in the regulator $= I_{OUT}(V_{UNREG} - V_{CC})$. This can be several watts, and so sufficient heatsinking must be used.

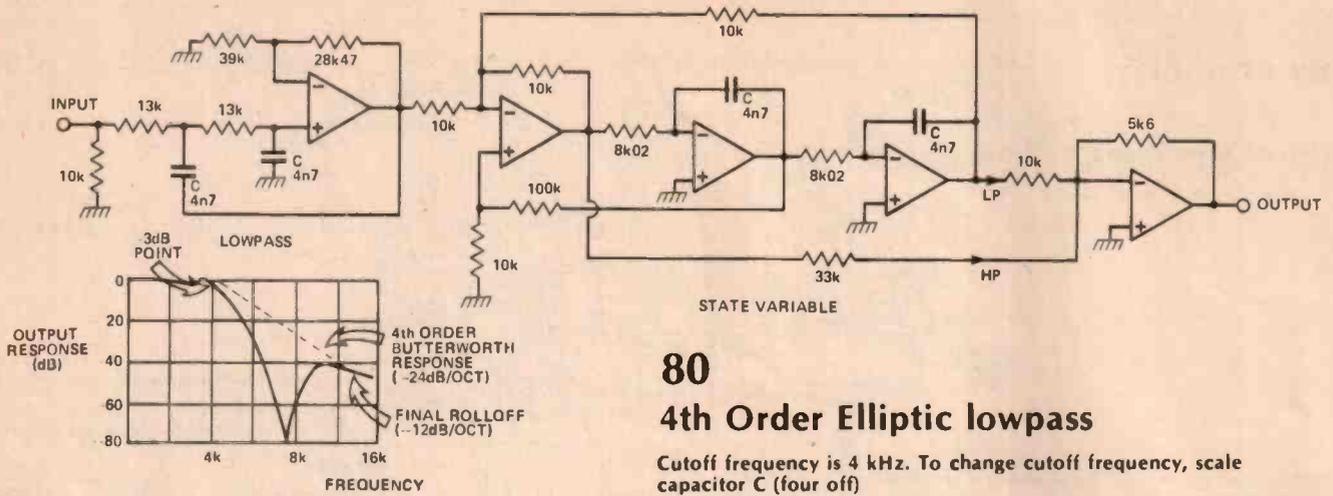

80 4th Order Elliptic lowpass

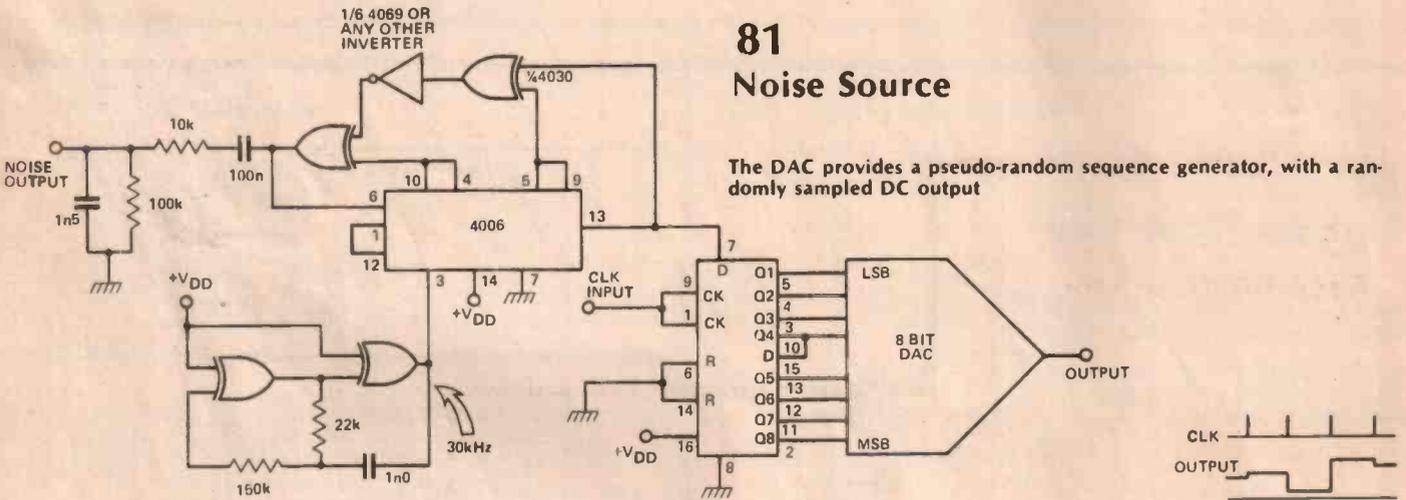
Cutoff frequency is 4 kHz. To change cutoff frequency, scale capacitor C (four off)



81 Noise Source

The DAC provides a pseudo-random sequence generator, with a randomly sampled DC output


82 Fuzz Unit For Guitar

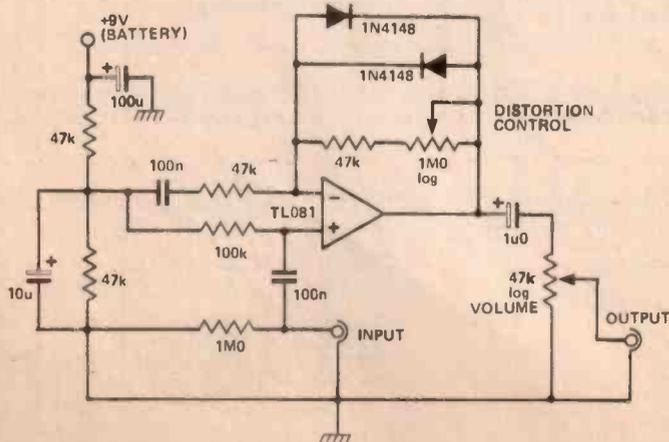

The battery can be switched on via the jack socket (a stereo jack can be used).

83 LED Flasher

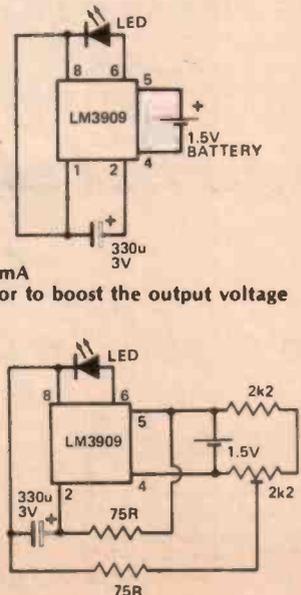1 Hz flash rate
Average current drain = 0.32 mA
Circuit uses the timing capacitor to boost the output voltage





Variable flash rate 0 to 20 Hz

84


Data Multiplexer

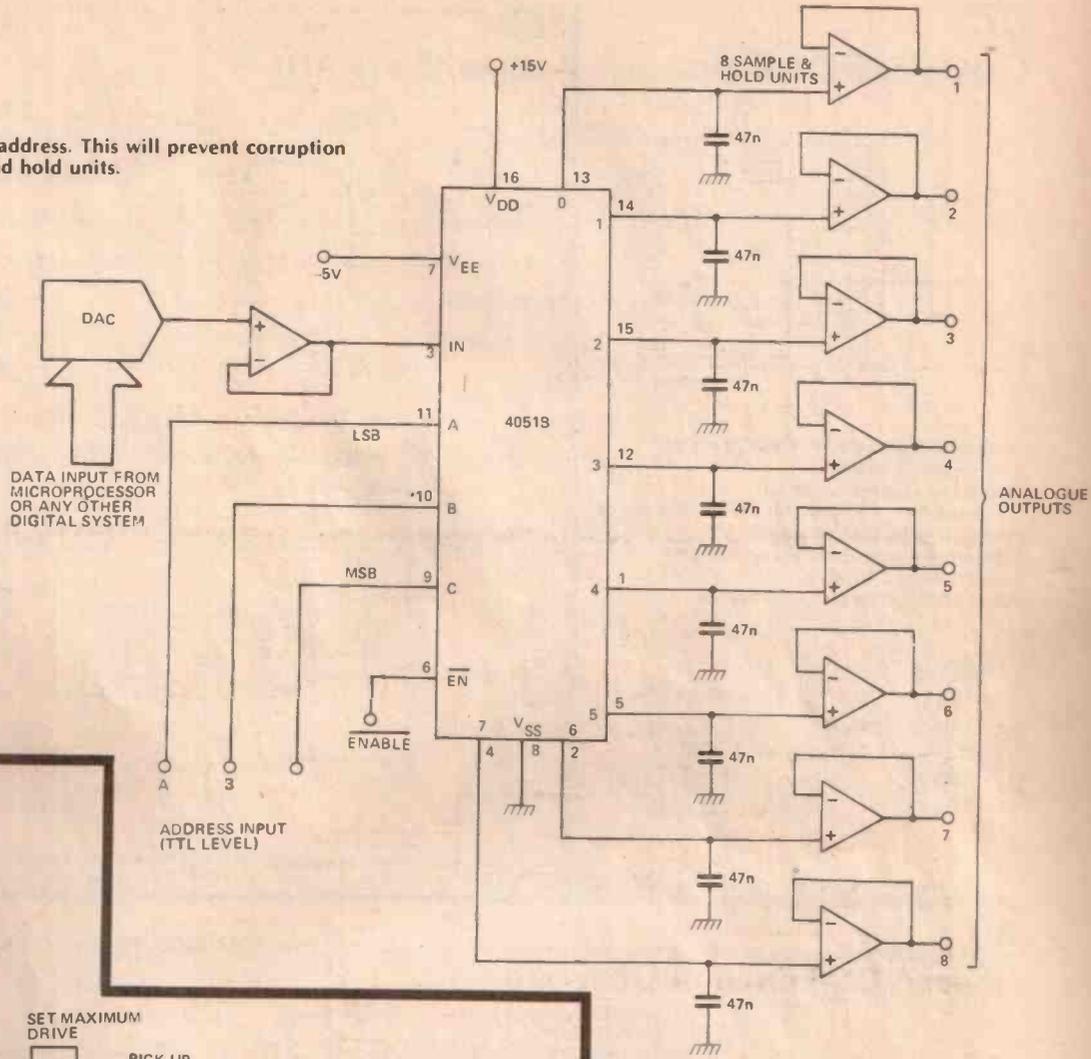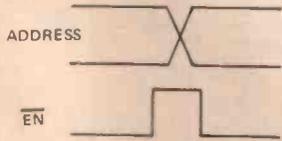Take \overline{EN} high when changing the address. This will prevent corruption of the data held on the sample and hold units.
All TL081 powered from $\pm 12V$



85


Reverberation Unit

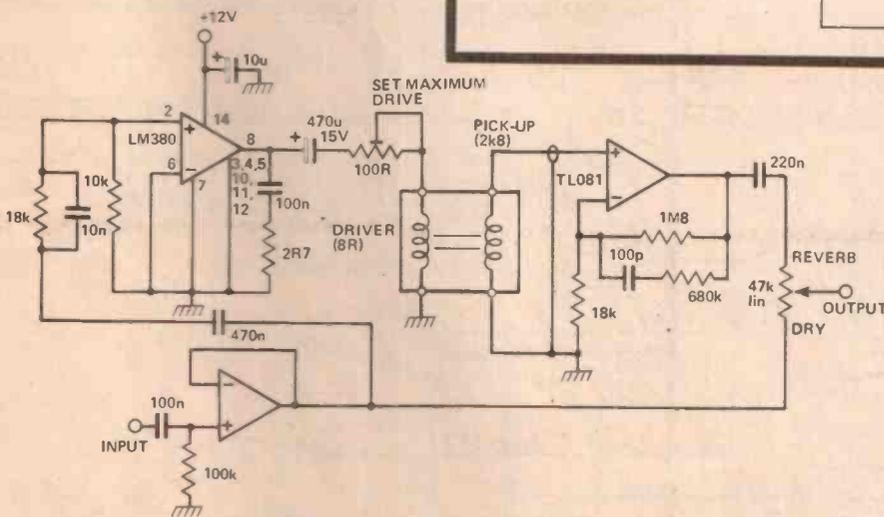


86

LED Peak Program Meter

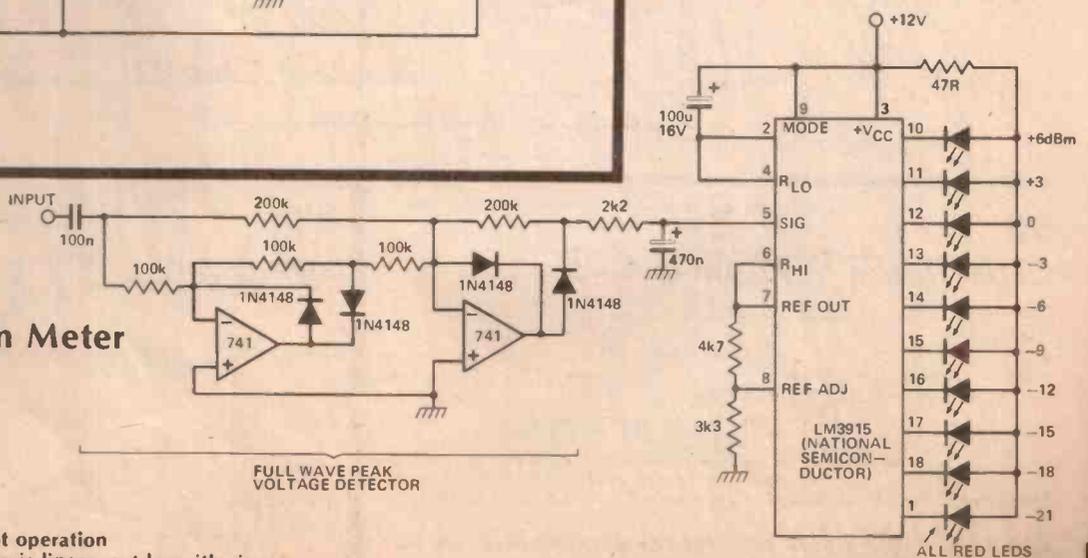Leave pin 9 open circuit for dot operation
If an LM3914 is used the display is linear, not logarithmic





87 CMOS 555 Oscillator

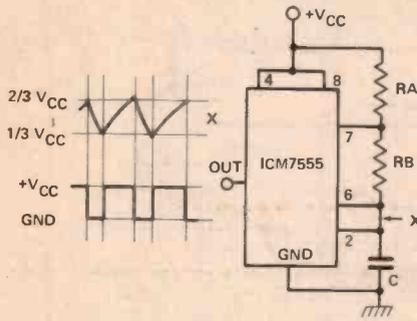

Output frequency $F = 1.46 / (C(RA + RB))$
 C in farads, R in ohms
 Quiescent current $\sim 120 \mu A$
 Input current $\sim 50 \text{ pA}$ (this allows the use of resistors up to 10M in value)
 Frequency range 0.001 Hz to 500 kHz
 Supply range 2 to 18 V
 Rise and fall time (pin 3) = 40 ns


| RA, RB | C | F |
|--------|----------|---------|
| 10M | 10u TANT | 7.3 mHz |
| 1M | 1u0 | 0.73 Hz |
| 100k | 100n | 73 Hz |
| 10k | 10n | 7.3 kHz |
| 10k | 1n0 | 73 kHz |

88 Logarithmic ADC

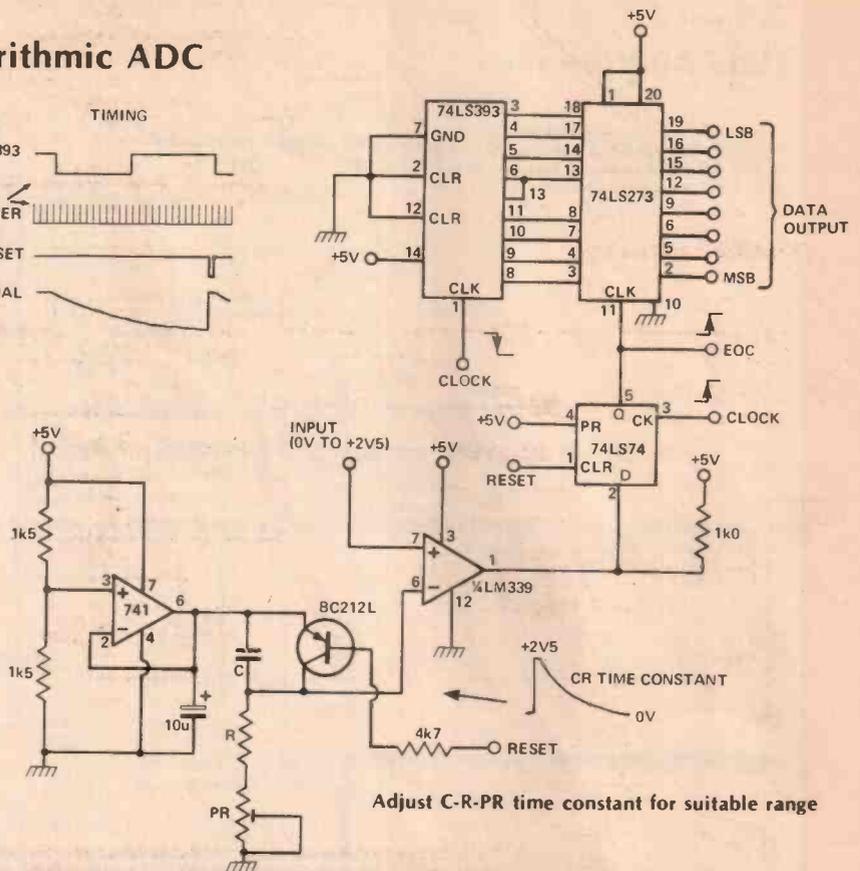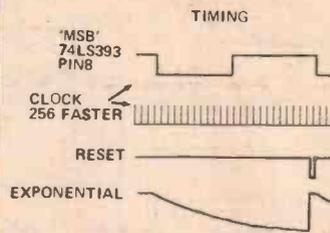

Adjust C-R-PR time constant for suitable range

89 Linear VCO/Function Generator

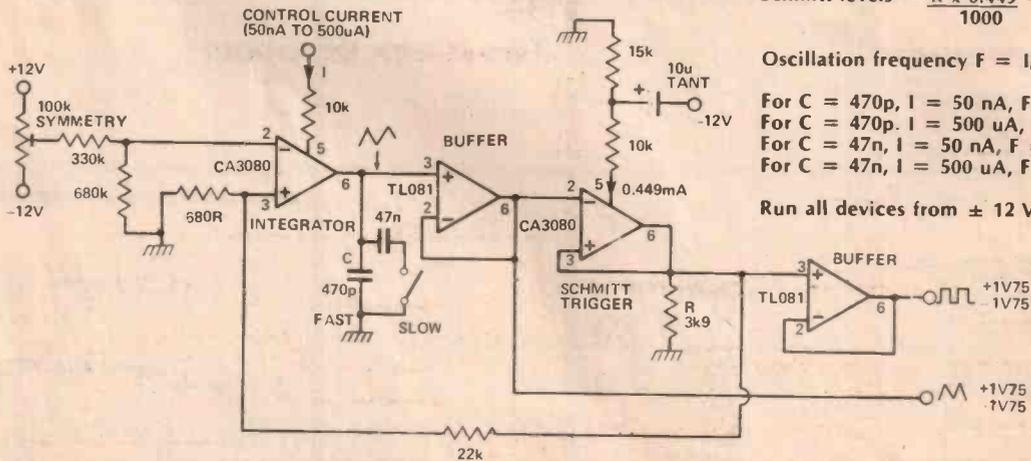


$$\text{Schmitt levels} = \frac{R \times 0.449}{1000} = 3.9 \times 0.449 = \pm 1V75$$

$$\text{Oscillation frequency } F = 1 / (C \times 4 \times 1.75) = 1/7C \text{ Hz}$$

For C = 470p, I = 50 nA, F = 15 Hz
 For C = 470p, I = 500 uA, F = 150 kHz
 For C = 47n, I = 50 nA, F = 0.015 Hz
 For C = 47n, I = 500 uA, F = 150 Hz


Run all devices from $\pm 12 \text{ V}$

90 Capacitance Multiplier

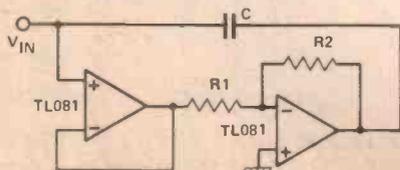

The input looks like a capacitor C_{IN} where $C_{IN} = C(R1 + R2)/R1$
 Circuit can be used to synthesise large capacitors (NB equivalent in impedance, not energy storage)

91 Slew Limiter

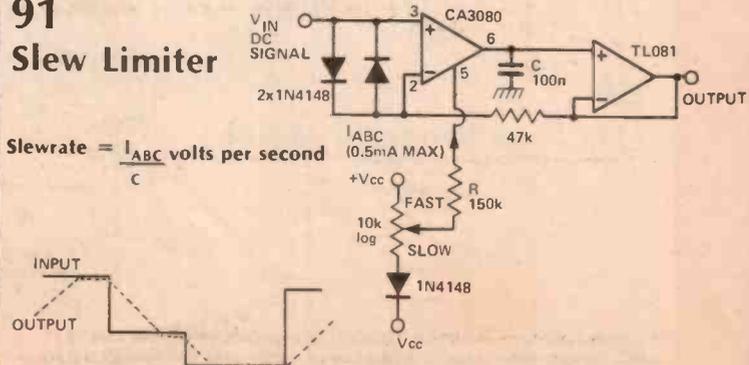


$$\text{Slewrates} = \frac{I_{ABC} \text{ volts per second}}{C}$$



95

Monolithic Sample And Hold

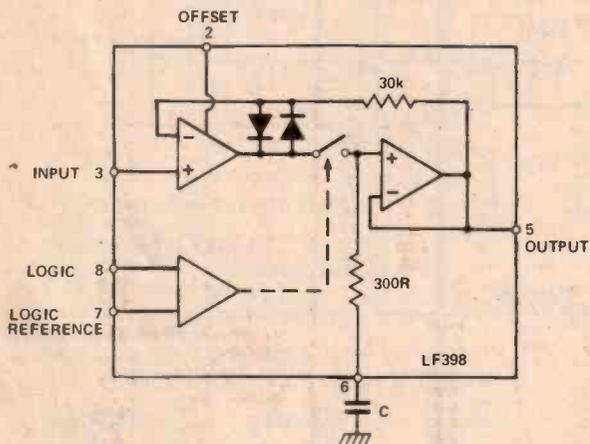
Logic high = sample
 Logic low = hold
 Logic reference = TTL or CMOS



Use a printed circuit guard ring (connected to the output voltage) around the hold capacitor

96


Op-amp Oscillator

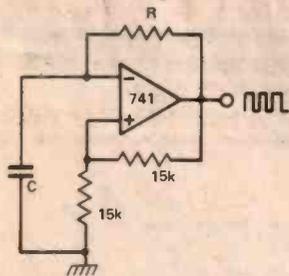

$$F \sim \frac{1}{RC} \text{ (rule of thumb)}$$

97

TTL Oscillator

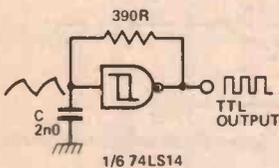


Vary C to change frequency
 Do not increase the size of the 390R resistor

Frequency range = 1 Hz to 1 MHz

98

TTL Ring Oscillator

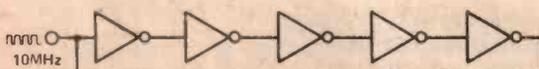


$F = 1/(5 \times \text{propagation delay})$
 For TTL inverters (74LS04) total propagation delay = 20 ns

99

FET Sample And Hold

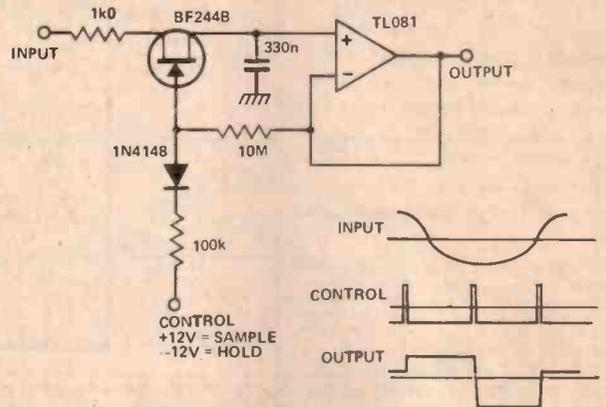Control = +12 V; sample
 Control = -12 V; hold




Use a printed circuit guard ring (connected to the output voltage) around the hold capacitor

100

4016 Sample And Hold

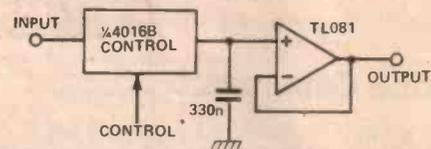
Control = +V_{CC}; sample
 Control = -V_{CC}; hold
 -V_{CC} < signal voltage < +V_{CC}
 +V_{CC} - (-V_{CC}) ≤ 15 V



Use a printed circuit guard ring (connected to the output voltage) around the hold capacitor

101

Battery Eliminator

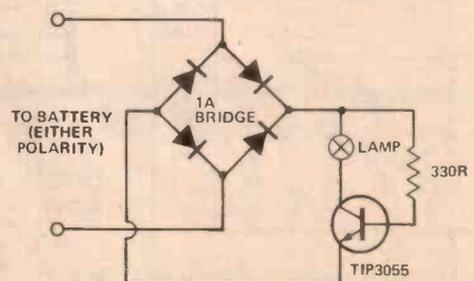

A free bonus!
 Lamp glows to show circuit is in operation
 Lamp goes out when battery has been eliminated
 Patent applied for

CAMBRIDGE LEARNING

Self Instruction Courses

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency, with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, and clear documentation.

BOOK 1 Computers and what they do well: READ, DATA, PRINT, powers, brackets, variable names, LET, errors, coding simple programs. BOOK 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF, THEN, GO TO; limitations of computers, problem definition. BOOK 3 Compilers and interpreters, loops, FOR...NEXT, RESTORE, debugging, arrays, bubble sorting, TAB. BOOK 4 Advanced BASIC; subroutines; strings, files; complex programming, examples; glossary.

Also **THE BASIC HANDBOOK (BHB) £14.50** An encyclopaedic guide to the major BASIC dialects. A must if you use other peoples' programs. New completely revised edition

and: **ALGORITHM WRITER'S GUIDE (AWG) £4.00** Communicate by flow chart! Learn to use Yes/No questions for: procedures, system design, safety, legislation etc.

Understand Digital Electronics

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers.

BOOK 1 *Decimal Octal, hexadecimal, and binary number systems and conversion between number systems, negative numbers, complementary systems.* BOOK 2 *OR and AND functions, multiple input gates, truth tables; De Morgan's Laws; canonical forms; logic conventions, Karnaugh mapping, three state and wired logic.* BOOK 3 *Half, full, serial, and parallel adders, subtraction, processors and ALUs, multiplication and division.* BOOK 4 *flip flops; shift registers, asynchronous synchronous, ring, Johnson, and exclusive OR feedback counters, ROMS and RAMS.* BOOK 5 *Structure of calculators; keyboard encoding; decoding display data; register systems, control unit; PROM; address de coding.* BOOK 6 *CPU; memory organisation character representation, program storage, address modes, input/output systems, program interrupts, interrupt priorities, programming, assemblers; computers; executive programs, operating systems.*

DIGITAL COMPUTER LOGIC & ELECTRONICS. (DCL) £8.50

A course covering the material in italics above, but at a slower pace. (4 vols)

GUARANTEE - No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition.

CAMBRIDGE LEARNING LIMITED, UNIT 18, RIVERMILL SITE, FREEPOST, ST IVES, HUNTINGDON PE17 4BR

| | | | |
|-------------------|-----|----------|----------|
| PLEASE SEND ME: - | CBP | (£10.50) | Quantity |
| | BHB | (£14.50) | |
| | AWG | (£4.00) | |
| | DDS | (£14.00) | |
| | DCL | (£8.50) | |

FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M Ch Barclay/Trustic/Visa Am. Exp. Diners
- 4) Or phone us with these credit card details (0480) 67446 (ansaphone) 24 hour service.

Expiry date.....
Card No..... Signed.....

THESE PRICES COVER THE COST OF SURFACE MAIL WORLOWIDE. AIRMAIL: Eur. N.Af. Mid.E. add 1/2 to price of books: Jpn. Aus. N.Z. Pctc add 1/2; elsewhere add 1/2

Name.....
Address.....

Cambridge Learning Limited, Unit 18, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England. U.K. Delivery: up to 28 days

Reg. in Eng. No. 1328762

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safeloc

| Minimum & Sub Miniature | | | |
|-------------------------|------------|----------|-------------|
| Volts | Milli-amps | Ref. No. | Price £ P&P |
| 3-0-3 | 200 | 238 | 2.60 70 |
| 0 6 0 6 | 1A 1A | 212 | 3.00 75 |
| 9-0-9 | 100 | 13 | 2.30 70 |
| 0 9 0 9 | 330 330 | 235 | 2.15 70 |
| 0-8-9 0-8-9 | 500 500 | 207 | 2.75 75 |
| 0-8-9 0-8-9 | 1A 1A | 208 | 3.85 75 |
| 0-15 0-15 | 200 200 | 236 | 2.15 70 |
| 0-20 0-20 | 300 300 | 214 | 2.75 90 |
| 20-12-0 12-20 | 700(DC) | 221 | 3.50 90 |
| 0-15-20 0-15-20 | 1A 1A | 206 | 4.60 1 05 |
| 0-15-27 0-15-27 | 500 500 | 203 | 4.05 85 |
| 0-15-27 0-15-27 | 1A 1A | 204 | 6.10 1 05 |

| 17 AND/OR 24 VOLT Pri 220-240 Volts | | | |
|--|------|------|-------------|
| Amps | 24V | Ref. | Price £ P&P |
| 0 5 | 0 25 | 11 | 2.30 75 |
| 1 0 | 0 5 | 213 | 2.75 90 |
| 2 | 1 | 71 | 3.25 90 |
| 4 | 2 | 18 | 4.05 85 |
| 6 | 3 | 70 | 5.60 95 |
| 8 | 4 | 108 | 7.40 1 20 |
| 10 | 5 | 72 | 8.25 1 20 |
| 12 | 6 | 116 | 8.85 1 20 |
| 16 | 8 | 17 | 10.85 1 30 |
| 20 | 10 | 115 | 13.85 1 50 |
| 30 | 15 | 187 | 16.85 1 50 |
| 60 | 30 | 226 | 33.35 1 80 |

| 30 VOLT (Pri 220-240V) Sec 0-12-15 20-24-30V | | | |
|---|----------|---------|------|
| Amps | Ref. No. | Price £ | P&P |
| 0 5 | 112 | 2.85 | 90 |
| 1 0 | 79 | 3.60 | 90 |
| 2 0 | 3 | 5.60 | 1 05 |
| 3 0 | 20 | 6.30 | 1 20 |
| 4 0 | 21 | 6.60 | 1 20 |
| 5 0 | 51 | 6.60 | 1 20 |
| 6 0 | 117 | 11.10 | 1 20 |
| 8 0 | 88 | 14.35 | 1 50 |
| 10 0 | 89 | 16.60 | 1 50 |

| 50 VOLT (Pri 220-240V) Sec 0-19-25-33-40-50V | | | |
|---|----------|---------|------|
| Amps | Ref. No. | Price £ | P&P |
| 0 5 | 102 | 3.60 | 90 |
| 1 0 | 103 | 4.60 | 1 05 |
| 2 0 | 104 | 7.30 | 1 20 |
| 3 0 | 105 | 8.60 | 1 20 |
| 4 0 | 106 | 10.85 | 1 30 |
| 6 0 | 107 | 15.10 | 1 50 |
| 8 0 | 118 | 20.20 | 1 70 |
| 10 0 | 119 | 24.10 | 2 20 |

| 60 VOLT (Pri 220-240V) Sec 0-24-30-40-48-60 | | | |
|--|----------|---------|------|
| Amps | Ref. No. | Price £ | P&P |
| 0 5 | 124 | 3.85 | 90 |
| 1 0 | 126 | 5.60 | 1 05 |
| 2 0 | 127 | 7.55 | 1 20 |
| 3 0 | 125 | 11.10 | 1 30 |
| 4 0 | 123 | 12.35 | 1 50 |
| 5 0 | 40 | 14.15 | 1 60 |
| 6 0 | 120 | 17.60 | 1 60 |

| AUTO TRANSFORMERS Input Output Tapped 0-115-210-240V | | | |
|---|----------|---------|------|
| VA (Watts) | Ref. No. | Price £ | P&P |
| 20 | 113 | 2.65 | 90 |
| 75 | 64 | 4.10 | 90 |
| 150 | 4 | 5.60 | 1 05 |

| Input/Output Tapped 0-115-210-240-240V | | | |
|---|----------|---------|------|
| VA (Watts) | Ref. No. | Price £ | P&P |
| 300 | 53 | 10.10 | 1 20 |
| 500 | 67 | 10.85 | 1 50 |
| 1000 | 84 | 18.60 | 1 60 |

Also 1500 2000 3000VA

MAINS ISOLATING (Centre Tapped & Screened) Sec 120 240V

| VA (Watts) | Ref. No. | Price £ | P&P |
|------------|----------|---------|------|
| 60 | 149 | 6.60 | 1 05 |
| 100 | 150 | 7.60 | 1 30 |
| 200 | 151 | 11.10 | 1 30 |
| 250 | 152 | 13.30 | 1 50 |
| 350 | 153 | 16.30 | 1 60 |
| 1000 | 156 | 37.10 | 3 20 |

Please add VAT at 15%
Barclaycard and Access facilities available
Trade and Education Welcome

BAYDIS 7a William Street
Herne Bay, Kent
Herne Bay G458E

MIGHTY NINETY PACKS

**SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 20p PER PACK UP TO FOUR PACKS
FIVE OR MORE POST FREE**

BUY SIX PACKS AND GET A SEVENTH PACK FREE!

- MN1.** 300 1/4-watt Resistors pre-formed for P&C Mtg
- MN2.** 200 1/4 & 1/2 watt Resistors
- MN3.** 100 1 & 2-watt Resistors
- MN4.** 50 Wirewound Resistors
- MN5.** 100 metal oxide Resistors 1%, 2% and 5%
- MN6.** 12 asstd potentiometers
- MN7.** 25 asstd skeleton pre-set Resistors
- MN8.** 50 asstd Electrolytic Capacitors
- MN9.** 100 asstd Ceramic Capacitors Pile disc, tub and monolithic etc
- MN10.** 100 mixed capacitors Polyester, Polystyrene Metallised, Radial and Axial types
- MN11.** 20 asstd Silver Mica Capacitors
- MN12.** 8 Tantalum Bead Capacitors (useful values)
- MN13.** 20 asstd Transistors BC, 2N Series + Power etc
- MN14.** 40 IN4148 Diodes
- MN15.** 5 Light Sensitive Devices
- MN16.** 20 min wire-ended Neons
- MN17.** 2 12-volt Relays Ex nearly new equip
- MN18.** 3 Encapsulated Reed Relays, 9-12v coil d pole and 1 pole
- MN19.** 2 24-volt Relays Ex nearly new equip
- MN20.** 1 240-110 to 12-volt 100ma Transformer
- MN21.** 1 240-110 to 24-volt 100ma Transformer
- MN22.** 8 2" Led s with clips, 4 red, 2 yellow, 2 green
- MN23.** 116 asstd screws nuts washers self-tappers etc
- MN24.** 100 asstd small springs
- MN25.** 50 asstd pop rivets
- MN26.** 50 asstd insulated crimps
- MN27.** 200 items grommets, spacers cable markers, plastic screws, sleeving tie wraps etc
- MN28.** 20 asstd fuses 1/4" 20mm etc
- MN29.** 75mts equipment wire asstd colours and sizes
- MN30.** 3 x 2m length 3 core, mains cable
- MN31.** 12 asstd trimmer capacitors, compression film Air-spaced etc
- MN32.** 15 30p Beehive trimmers
- MN33.** 20 coil formers, ceramic plastic, reed relay etc
- MN34.** 25 min. glass reed switch
- MN35.** 10 asstd switches, toggle, slide, micro etc
- MN37.** 10 asstd audio connectors Din, phono etc
- MN38.** 1 PCB with triac control IC data inc
- MN39.** 1 oscillator PCB loads of components, (no data)
- MN40.** 50 Polystyrene capacitors
- MN42.** 10 BC107 Transistors
- MN43.** 10 BC108 Transistors
- MN44.** 10 Screwfix S P C O min slide switches
- MN58.** 2xCA723 Voltage Regulator
- MN64.** 5 Press to make min. switches
- MN65.** 3 BF245 FETS.

CHORDGATE LTD. Dept. A
75 FARINGDON ROAD, SWINDON, WILTS
TEL: SWINDON (0793) 33877
RETAIL SHOP AT ABOVE ADDRESS

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

NEW

PRACTICAL ELECTRONICS - STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagrams and instructions



SPECIAL OFFER! TUNER KIT PLUS:


- Matching I.C. 10+10 Stereo Power amplifier kit (usually £3.95 + £1.15 p&p)
- Mullard LP1183 built preamp, suitable for magnetic/ceramic and auxiliary inputs (usually £1.95 + 70p p&p)
- Matching power supply kit with transformer (usually £3.00 + £1.95 p&p)

- Matching set of 4 slider controls complete with knobs for bass, treble and volumes (usually £1.70 + 80p p&p)

£21.95 plus £3.80 p&p.

ONLY

£17.95 plus £2.50 p&p.

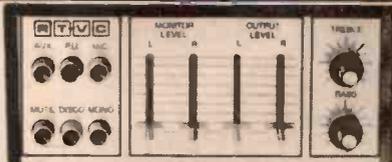

STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/4" x 3 1/4" (approx)
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with the kit.

£14.95 Plus £2.90 p&p.

SPECIFICATIONS: Suitable for 4 to 8 ohm speakers. Frequency response 40Hz - 20KHz. P.U. 150mV. Aux. 200mV. Mic. 1.5mV.

Tone controls

Bass +12db @ 60Hz
Treble +12db @ 10KHz
0.1% typically @ 8 watts
220 - 250 volts 50Hz

Distortion
Mains supply

STEREO MAGNETIC PRE-AMP CONVERSION KIT Includes FREE Magnetic cartridge with diamond styli. All components including p.c.b. to convert your ceramic input on the 10+10 to magnetic. Only available with 10+10 amp. **£2.00** includes p&p.

8" SPEAKER KIT Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately £6.75 plus £1.70 p&p.

PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II

2 WAVE BAND MW - LW

- Easy to build
- 5 push button tuning
- Modern design
- 6 watt output
- Ready etched and punched PCB
- Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics March issue. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output (neg. ground) and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

£10.50 Plus £2.00 p&p.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" approx.) available as a kit complete. **£1.95/pack.** Plus £1.15 p&p.

HIGH POWER AMPLIFIER MODULES


READY BUILT OR IN KIT FORM

| | KIT | BUILT |
|----------------|-----------------------|-----------------------|
| 125 WATT MODEL | £10.50 Plus £1.15 p&p | £14.25 Plus £1.15 p&p |
| 200 WATT MODEL | £14.95 Plus £1.15 p&p | £18.95 Plus £1.15 p&p |

SPECIFICATIONS:

| | 125 W Model | 200 W Model |
|---|--------------------------|--------------|
| Max. output power (RMS) | 125 watts | 200 watts |
| Operating voltage (DC) | 50 - 80 max. | 70 - 95 max. |
| Loads | 4 - 16 ohms | 4 - 16 ohms |
| Frequency response measured @ 100 watts | 25Hz - 20KHz | 25Hz - 20KHz |
| Sensitivity for 100 watts | 400mV @ 47K | 40mV @ 47K |
| Typical T.H.D. @ 50 watts, 4 ohms | 0.1% | 0.1% |
| Dimensions (both models) | 205 x 90 and 190 x 36mm. | |

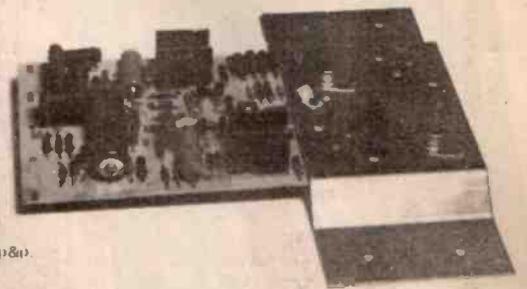The P.E. power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of



generously rated components, result, a high powered rugged unit. The PC Board is back printed, etched and ready to drill for ease of construction and the aluminum chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES:

- Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p.
- Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p.
- Suitable mains power supply unit for 125W model **£7.50** plus £3.15 p&p.
- Suitable twin transformer power supply for 200W model **£13.95** plus £4.00 p&p.




30+30 WATT STEREO AMPLIFIER

Viscount TV unit in teak simulate cabinet, silver finished rotary controls and pushbuttons with matching fascia, mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30+30 watts RMS, 60+60 watts peak. For use with 4 to 8 ohm speakers. Size: 14 1/2" x 10" approx. **£32.90** Plus £3.80 p&p.

PHILIPS BELT DRIVE RECORD PLAYER - DECK GC037

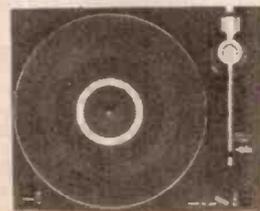(Size: 15 1/2" x 12 1/2" approx.) HiFi record player deck, 2 speed, damped curing, auto shut off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge.




LIMITED STOCK.


UNBEATABLE OFFER AT **£27.50**

COMPLETE Plus £3.16 p&p.

MONO MIXER AMPLIFIERS

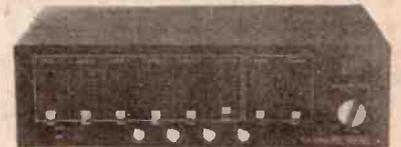

50 WATT Six individually mixed inputs for two pickups (Cer. or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux inputs. Size: 13 1/2" x 6 1/2" x 3 1/2" approx. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use. **£39.95** Plus £3.70 p&p.

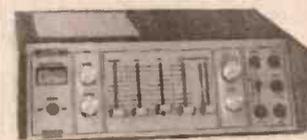

100 WATT Brushed Aluminium fascia and rotary controls. Size: approx. 14 1/2" x 4 1/2" x 10 1/2". Five vertical slider controls, master volume, tape level, mic level, deck level, PLUS INTERDECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre face level controls (PFL) lets YOU hear the next disc before fading it in. VU meter monitors output. 100w RMS output (200w peak). **£76.00** Plus £4.60 p&p.



CALLERS ONLY

323 Edgware Rd, London W2. Tel: 01-723 8432. Open 9.30am - 5.30pm. Closed all day Thursday. Persons under 16 not served without parents authorisation.

ALL PRICES INCLUDE VAT AT 15%.

MAIL ORDER ONLY

21E HIGH STREET, ACTON, W3 6NG.

Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope.

PHONE BELL SHIFTER



If you want to customise your phone without incurring a visit from the British Telecom heavies clutching their wirecutters, then this is the project for you. Design by Ray Marston. Development by Steve Ramsahadeo.

A unique feature of our Phone Bell Shifter project is that it uses a micropower signal-sampling technique (as described in last month's Designer's Notebook) to detect the presence of a ringing signal and then automatically switch the unit into the full-power mode. Because of this technique, the unit draws a quiescent current of a mere 7 μ A, thus giving up to two years of continuous operation from a single PP9 supply battery.

The Phone Bell Shifter project is provided with two preset pots plus a normal volume control, and is simple to set up and use. The acoustic pickup transducer (which forms the input of the unit) is simply placed underneath the telephone body (below the bells) and the sensitivity of the unit is then initially adjusted by one preset to give the desired trigger action when the phone rings: once this pot has been initially set, it requires no subsequent adjustment.

Construction

All of the major electronics of this project (except the input transducer

and the output speaker) are built into a single Verobox, which also houses the PP9 supply battery, and construction should present very few problems. A number of high value resistors are used in the circuit, so extra care should be taken to ensure that moisture and contaminated grease are not allowed to shunt down the effective values of these components; when PCB construction is complete and the circuit has been tested, the board should be given a coating of varnish to prevent the ingress of moisture.

When the PCB construction is complete, fit the PCB and the PP9 battery into the recommended Verobox and complete the interwiring to RV1, SW1 and the input and output sockets. Fit the specified speaker in a second Verobox and then connect it to the input of the main unit.

To set the unit up initially, simply adjust sensitivity control PR1 so that the unit's alarm activates when the phone bells ring, and then adjust PR2 so that the alarm volume does not fall to zero when the main volume control is turned fully down.

A major problem with the present-day British telephone system is that all bell-type phones generate virtually identical ringing sounds, thereby creating all sorts of problems. In the home, for example, while watching TV you'll often hear a phone ring and instantly leap to your feet to answer the call, only to find that the ringing sound comes from a phone in the TV programme. Similarly, when you are relaxing in the garden on a summer's day, or when you have wandered into a neighbouring office at work, you'll often hear a distant phone ring and will not know if the call is intended for you or a neighbour.

The ETI Phone Bell Shifter project is designed to overcome these identification problems by giving your phone its own distinctive sound. The project consists of a sophisticated five IC circuit; its input is provided by an inexpensive transducer, acoustically coupled to the phone body to detect the ringing of the phone bells, and its output is taken to an external 15R speaker from a built-in alarm-tone generator. A distinctive pulsed-tone alarm sound is generated which is synchronous with the detected phone bell signal. The speaker is connected to the output of the unit using twin flex, and can either be placed near the phone (so that the unit acts as a phone identifier) or can be placed at a remote location (so that the unit acts as a phone bell extender).


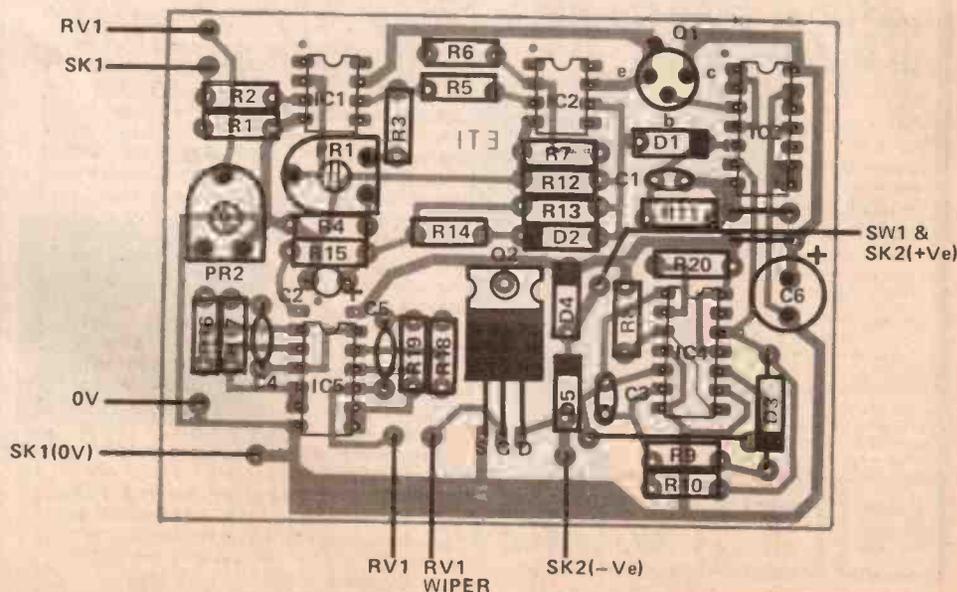


Fig. 1 Component overlay.

Fig. 2 Circuit diagram for the Phone Bell Shifter.

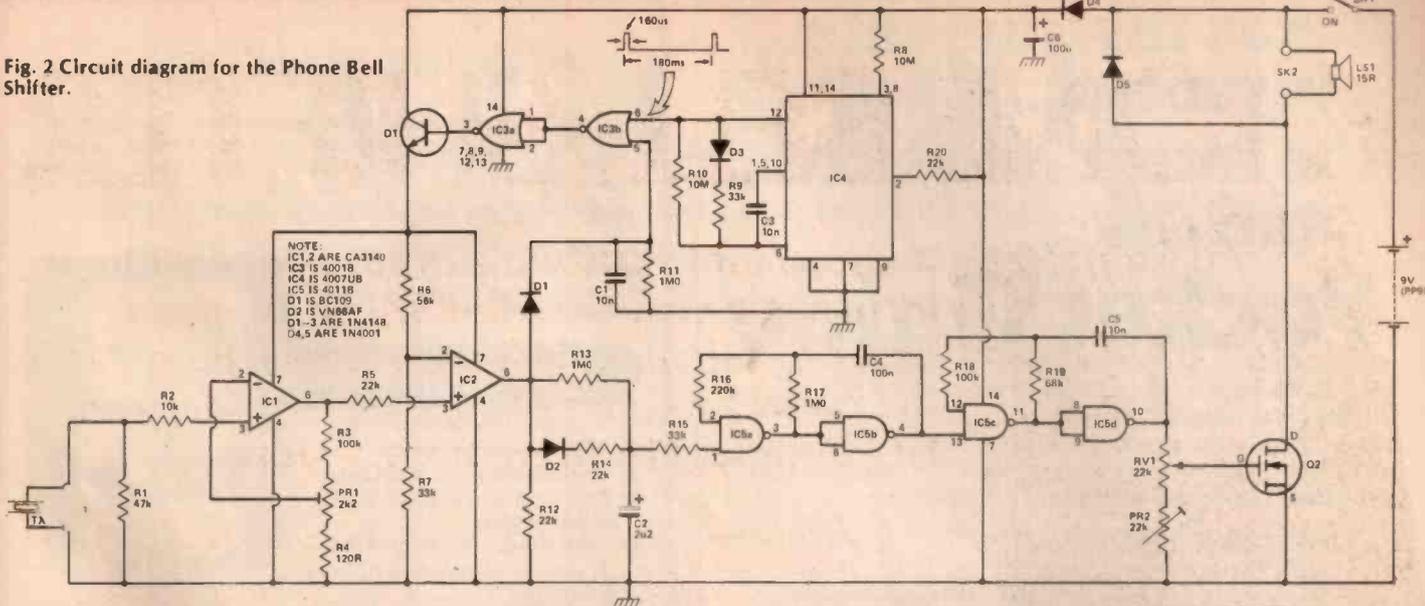

HOW IT WORKS

First ignore the effects of the signal-sampling circuitry and assume that Q1 is replaced by a short-circuit, so that supply power is continuously applied to IC1 and IC2.

The acoustic pickup device used in the circuit is a PB-2720 transducer, which is placed under the phone body, below the bells. This transducer has a poor low frequency response, but is quite sensitive to the high frequency (3 to 5 kHz) overtones of the phone bell. The output of the transducer is applied directly to the input of non-inverting variable-gain amplifier IC1.

Although the input of IC1 is DC-grounded by R1-R2, the CA3140 op-amp used in this position is able to respond to input signals all the way down to 0 V; consequently, the output of this op-amp (pin 6) corresponds to an amplified but positively half-wave rectified version of the input signal. This signal is fed to the input of non-inverting voltage comparator IC2, which is reference-biased at about 3 V by R6-R7.

Thus, the overall action of the IC1-IC2 circuit is such that the output of IC2 is normally low, but changes into a series of 3-5 kHz square waves in the presence of bell-ring input signals. These square wave signals are processed by the R13-D2-R14-C2 dual-time-constant integrating network, so that a high DC voltage (6 V) is developed across C2 in the presence of a true ring signal, and this voltage is used to activate the IC5 alarm-tone generator circuitry. Note that, because of the integrating action of D2-R14-C2, the input signal must be sustained for greater than 50 ms to initiate a high switching action in IC5, so the circuit has excellent immunity to transient signals caused by physically banging the telephone body or PB-2720 transducer. Similarly, because of the actions of R13-C2, the IC5 alarm circuit does not turn off until several hundred milliseconds after the bell-ring input has been removed, and thus gives a single continuous action from a double (ringing) input signal.

The IC5 oscillator circuitry is quite simple. IC5a-IC5b is a low-frequency gated astable (about 6 Hz), with its output fed to the input of 1 kHz gated astable IC5c-IC5d. The output of the 1 kHz astable is fed to the input of VFET Q2 via volume control pot RV1, and Q2 uses the external 15R speaker as its drain load. In the absence of an input signal (from C2) the two astables and Q2 are cut off and the circuit consumes virtually zero standby current; in the presence of a high signal from C2 the low frequency astable activates and pulses the 1 kHz astable on and off at a 6 Hz rate,

thereby producing a pulsed tone in the 15R speaker.

Note that the supply to the major sections of the Phone Bell Shifter circuitry is decoupled from speaker/Q2 transients by D4 and C6.

In this circuit, IC5 and Q2 consume virtually zero quiescent current, but the IC1-IC2 ring detector stages would, if continuously powered from a 9 V supply, consume a quiescent current of about 4 mA and would thus flatten a PP9 battery in less than two days of continuous running. To overcome this problem and vastly extend the battery life, we use a signal-sampling technique in which a micropower oscillator network (IC4-IC3-Q1) is used to feed pulses of supply power to the IC1-IC2 ring detector circuit and simultaneously check the output of the detector for signs of such a signal; if a signal is detected, the circuitry then applies full power to IC1-IC2, so that the signal can be fully processed. The sampling pulses are only 160 µs wide and are repeated every 180 ms; consequently the mean power consumption of the detector circuit is reduced by a factor of 1125, to a mere 3.5 µA. The micropower oscillator network also consumes a running current of 3.5 µA so the total quiescent current of the entire Phone Bell Shifter circuit works out at 7 µA, thus giving up to two years of continuous running from a single PP9 supply battery.

IC4 is a special-purpose micropower oscillator circuit, designed around a 4007UB dual complementary pair plus inverter CMOS chip: a full description of this oscillator was given in the October edition of Designer's Notebook. The output pulses of IC4 are fed to one input of the IC3a-IC3b OR gate and then passed on to emitter follower Q1, which consequently connects supply power to the IC1-IC2 ring detector circuitry for 160 µs once every 180 ms. Simultaneously, the output of IC2 is peak-detected (inspected) during the sampling period and the resulting signals (if any) are stored in C1 and fed to the second input of the IC3 OR gate. Consequently, if a bell-ring signal is absent during the sampling period, the output of IC2 will be low and zero voltage will appear across C1, so another sample pulse will be applied 180 ms later. If, on the other hand, a bell-ring signal is present during the sampling period, the output of IC2 will switch high and store a high voltage on C1, thereby taking the second input of the IC3 OR gate high. This causes Q1 to turn fully on, so that the supply is semi-permanently connected to IC1-IC2 and the input signals may be fully processed.

PARTS LIST

Resistors (all 1/4 W, 5%)

| | |
|-------------|------|
| R1 | 47k |
| R2 | 10k |
| R3,18 | 100k |
| R4 | 120R |
| R5,12,14,20 | 22k |
| R6 | 56k |
| R7,9,15 | 33k |
| R8,10 | 10M |
| R11,13,17 | 1MΩ |
| R16 | 220k |
| R19 | 68k |

Potentiometers

| | |
|-----|---------------------------------|
| RV1 | 22k logarithmic |
| PR1 | 2k2 miniature horizontal preset |
| PR2 | 22k miniature horizontal preset |

Capacitors

| | |
|--------|----------------------------|
| C1,3,5 | 10n ceramic |
| C2 | 2u2 16 V tantalum |
| C4 | 100n ceramic |
| C6 | 100µ 16 V PCB electrolytic |

Semiconductors

| | |
|--------|--------|
| IC1,2 | CA3140 |
| IC3 | 4001B |
| IC4 | 4007B |
| IC5 | 4011B |
| Q1 | BC109 |
| Q2 | VN66AF |
| D1,2,3 | 1N4148 |
| D4,5 | 1N4001 |

Miscellaneous

| | |
|--|-------------------------------------|
| SW1 | SPST miniature toggle |
| LS1 | 15R 2 W, 5" x 3" elliptical speaker |
| SK1,2 | phono socket |
| TX1 | PB-2720 |
| Case for electronics (Verobox order no. 202-21391A; case for speaker (order no. 202-21030K). | |

BUYLINES

LS1 might prove a little difficult to obtain from your local component emporium, but Watford Electronics have agreed to supply the speaker on request. The VMOS transistor (Q2) is available from Electrovalue, and Ambit International are stockists for the PB-2720. The PCB can be obtained from our PCB Service — see page 76 for details.

Texas Instruments invented.... the integrated circuit and the Pocket Guide

TTL £3.50

Volume One Digital Integrated Circuits.

A concise summary - logic and pin assignments - of all TTL semiconductor devices currently available from Texas Instruments, the world's largest manufacturer.

LINEAR & INTERFACE £2.50

Volume Two Professional Linear.

A detailed description of all Texas Instruments Linear and Interface integrated circuits (including second-source). Pin-out guides, device characteristics and complete support information are included.

Together these Pocket Guides make *the* complete reference to advanced bipolar integrated circuits from Texas Instruments.

To obtain your copies complete the order form and send together with your cheque or postal order (payable to Texas Instruments Ltd) to:

Texas Instruments Ltd, PO Box 50,
Market Harborough, Leics.



Please send me

Quantity _____ copies of the
TI Pocket Guide Volume I (TTL)

at £3.50 each, total £ _____

Quantity _____ copies of the
TI Pocket Guide Volume II (Linear & Interface)

at £2.50 each, total £ _____

I enclose cheque _____ to the value (add £1.50 p&p per
order) of £ _____ in payment.

Name _____

Company name (if any) _____

Address _____

ET02

Send completed forms to Texas Instruments Ltd, PO Box 50,
Market Harborough, Leics.

Texas Instruments invented the integrated circuit, the
microprocessor, and the microcomputer.

Being first is our business.

TEXAS INSTRUMENTS
LIMITED




Now the time can tell you! . . .

New - from Silicon Speech Systems (a Powertran subsidiary) - the first ever easy-to-build kit that will give a whole new meaning to the 'speaking clock'! Electronics and quartz technology combine to enable you to construct a talking timepiece that is interesting to build - fun to have!

Full instructions make this a kit with equal appeal to the beginner or experienced constructor.

ONLY £29.95 includes VAT and Post & Pkg

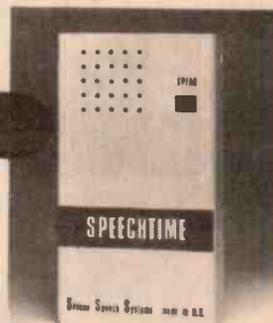- Accurate to a minute a year
- Adjustable voice pitch
- Grained stainless-steel case
- Pocket size - approx. 5in. x 2½in. x 1in.
- Useful in the home or office
- A perfect gift to give to the enthusiast
- Or, why not build one as a present for someone else?



Silicon Speech Systems

(A Powertran Subsidiary)

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS., SP10 3NM

TELEPHONE ORDERING FOR ACCESS/BARCLAYCARD
CUSTOMERS AVAILABLE -

RING ANDOVER (0264) 64455; PLACE YOUR ORDER AND
JUST QUOTE YOUR CARD NUMBER

SPECIAL OFFERS

FUSE HOLDERS 20MM CHASSIS MOUNTING

10 for only 30p
100 for only £2.50
1000 for only £20.00

FUSE HOLDERS DOUBLE 20MM CHASSIS MOUNTING

10 for only 50p
100 for only £4.00
1000 for only £30.00

ASSORTED PACKS SELF-TAPPING, SELF-CUTTING SCREWS. 2lb. weight,
approx. 700 items (U.K. only) £3.00

WIRE-WOUND RESISTORS BY V.T.M.

5K 9 watts 5%

10 for 50p
100 for £3.00
1000 for £20.00

ASSORTED IFs BY TOKO, etc., 10 for 50p
I.T.T. LEVER SWITCHES, 8 pole c.o., boxed £1.00

HOOK-UP WIRE WITH PLUGS AND SOCKETS, very useful for TV Engineers
..... 60p

TEXAS/I.T.T. 1N4148, 100 for £1.50
MULLARD MATCHED PAIR AD161/162 50p

MULLARD POT CORES

LA3 100-500KHz 75p
LA4 10-30 KHz £1.00
LA5 30-1000 KHz £1.00
LA7 < 10 KHz £1.00
Also LA13 £2.00

RELAYS 24V 3 C.O. HD 11-pin plug-in £1.50

A.E.I. MOTORS TYPE BP 1303/B, 100-125V S.P. 60 cycles, h.p. 3 watts, r.p.m.
1550 £3.50

FAIRCHILD FLV150, red, .2 LEDs, 10 for £1.00, 100 £8.65.

PLEASE NOTE ALL PRICES INCLUDE POST AND V.A.T.

IONISER KIT ZD13

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. This result? Your air feels like fresh ocean air, pure, crisp and wonderfully refreshing. All parts PCB and full instructions, £12.50. A suitable case including front panel, neon switch, etc. Available at £10.50.

T. POWELL

Dept. E.T.I.
Advance Works
44 Wallace Road, London, N.1
Tel: 01-226 1489

HOURS: Mon.-Fri. 9-5.30 p.m.
Sat. 9-4.30 p.m.



Minimum Telephone Orders: £5
Minimum Mail Order: £1

AUDIOPHILE

A first look at a new name to the tape market and a mention for a useful gadget to keep it clean! Ron Harris reports on the Alpage AL-300.

I hate summer. All that lousy sunshine and hot weather. The main problem is that people expect you to get outdoors and enjoy being roasted to death slowly. Sounds very lemming-like, if you ask me, all this rushing off to the sea every time the sun shines.

Hi-fi tends to become an anti-social undertaking too — even if, like me, you resolutely refuse to burn to death with a smile and prefer to remain enthroned in your lounge with Tchaikovsky caressing the speakers. But they won't leave you alone, not even then. Hot weather means open windows and open windows mean 100 dB of music escaping into the wide world outside — and that means neighbours banging on doors because you woke them from their sun-drenched stupor on the back lawn.

Oh for the joys of winter, with icy rain sleeting against the windows (closed), a warm glow in the hearth (the cat got too close to the electric fire and burst into flames), a glass of brandy in the hand and the sweet sounds of music gently filling the room... until the roof leaks, water pours in and short circuits the amp which explodes violently, taking out the speakers and impaling you in the armchair with pieces of flying speaker cone.

Is there nought to life save adversity in the face of perfection?

Record Time


Avoiding the sunshine this month paid some dividends, in that I came across two superb new LPs which can be totally recommended for content and recorded quality. The old 'Rickie Lee Jones' album has long been a demonstration standard and now the new LP, called 'Pirates', could well go the same way. The guitars and vocals are outstandingly reproduced and will get better as your system improves. The content is much more jazz orientated than the earlier offering, which undoubtedly puts off as many people as it endears.

The better of the two, however, has to be the new Stevie Nicks album, 'Belladonna'. To start with the woman has an amazing voice and is devastatingly attractive. The kind of beauty for which men would kill, merely to earn a smile and a softness in the eye. Nothing to do with the music, I know, but

The record has a truly excellent vocal recording and is very well detailed. The balance is slightly bright, which will show up any hardness inherent in the system, as the LP itself is never hard-sounding. If you want a system test for detail and clarity then this is it. I suspect that if you frequent hi-fi shops as a hobby (plastic mac optional) you'll be hearing more of this particular album in future.

Alpage AL-300

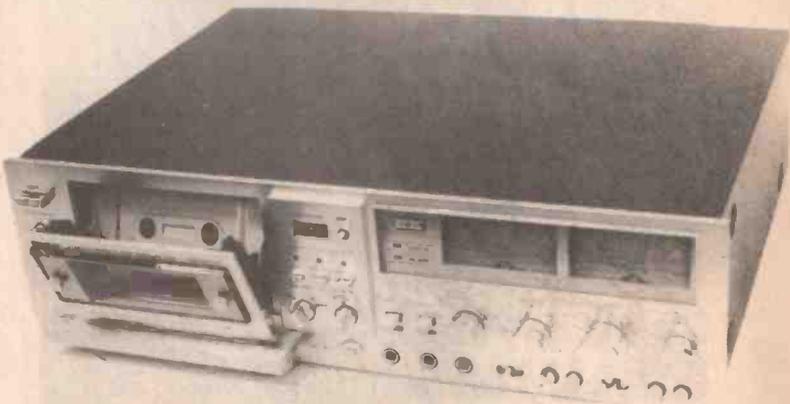Couple of issues ago now I mentioned the new range of



Above: The Alpage AL-300 in all its glory, the top line machine in Shure's range of three.

Below: The front panel block on the Alpage AL-300 detaches to form a corded remote control.



Left: The stunning and sensuous Stevie Nicks, as she appears on the cover of her new album.



tape decks from Shure Electronics, entitled *Alpage*, promising more details to follow. When, they've arrived! Herein one review of the AL-300 cassette deck, the top-line machine in the present range of three.

Among its many attributes it boasts variable bias and Dolby, which work in conjunction with the metering. This itself is switchable from peak reading to average. More common facilities include metal-tape capability, off-tape monitoring and auto play/rewind. Record mute is there, for those who can suss out how to use it.

Transport control is solenoid operated and the front panel block detaches to form a (corded) remote control. There is also a pitch control for altering replay speed slightly — useful if you're slow of hearing or wish to make sure that your 46 minute LP will fit onto a 45 minute side. With a small variation in pitch it is most unlikely that anyone would ever notice that the music is playing slightly fast.

Variable Everything

Dolby B has been so widely accepted that hardly anyone bothers to question it any more. With the new surge of interest in noise reduction systems — Dolby C, HX, dbx, etc etc some points are now being raised.

Variable Dolby (allowing optimisation of level) can bring audible benefits. With Dolby B the signal passing through the record circuits has to have identical response to, and be at the same level as, the signal in the replay deprocessors.

Failure to achieve this will mean that tapes replaying at a higher level will sound bright and edgy, and less sensitive tapes dull and lacking in treble.

The *Alpage* AL-300 has a built-in test oscillator, operable at 400 Hz and 10 kHz. The former frequency is used to align the Dolby processors, by recording the calibration tone and setting up the replay level on the meters. Worthwhile if you're searching for the 'nth' degree of audible quality.

As to the benefits of variable bias these can be clearly heard if you're mad enough to deliberately set up a tape wrongly and record the same piece of music again, only this time correctly.

Insufficient bias will cause LF and MF distortion and make the tape prone to 'dropouts' as the signal is not securely imprinted upon the tape.

Too much bias and the HF end of the spectrum disappears at great speed whereupon severe compression becomes apparent. All very nasty overall.

Since brands of tape vary so much in quality, manufacturers of tape decks thought it worthwhile to include 'fine-tuning' of bias-level to offset the usual 'type-select' switch found adorning front panels the world over.

The *Alpage* facility is thus a justifiable and useful addition.

Head Of The Class

One possible problem with the newer tape formulations, metal and ferrichrome, is their requirement for much higher levels of bias than had hitherto been required. Earlier designs of deck used record heads that had a small gap and were prone to 'saturate' under the level of bias required for these tapes.

It is thus reassuring (to me anyway — if I hadn't told you about it you wouldn't have worried, would you?) to note that the *Alpage* has a reasonable margin of safety in the design and that no trace of head problems was encountered. This is a sound design all round.

The bias levels seemed to have been well selected and were as 'right' as they could be for the overall settings. The 'chrome' option gave very good results, for example, with Maxell XLIIS and TDK SA, even without optimisation.

A useful table is provided in the pigeon-Japanese-English manual listing out a wide range of tape types and the recommended settings. Apart from this, though, the book is down to the usual standards of these productions — ie pretty dire. *Alpage* are no worse than most others, but with section headings like "A 4-step switch applicable to a metal tape being now talked about", they sure as hell ain't any better!

Tested Results

The outcome of the bench tests proved most satisfactory with the AL-300 giving a creditable account of itself. The metal tape response proved particularly extended, running from 22 Hz to 21,000 Hz ± 3 dB, beyond which it dived into the bottom of the graph paper.

Signal to noise (with Dolby in) on UDXLIIS proved to be a respectable 65 dB, good but not quite up to spec. Still, God alone knows how the inscrutable East derive some of their figures — and He probably works for Matsushita Electronics nowadays anyway.

Without Dolby, S/N fell to a wholly irrelevant 54 dB.

Rest of the figures (taken with Maxell XLIIS and TDK metal tapes):

| | | |
|-----------------------------------|---|--|
| THD (record to replay): | 0.75% at 1 kHz, Dolby level | |
| FREQUENCY RESPONSE (± 3 dB): | 22-21000 Hz Metal 30-18500 Hz FeCr 25-18000 Hz CrO ₂ 40-15000 Hz Normal | } After optimising bias and Dolby levels |
| WOW AND FLUTTER (WRMS): | 0.03% | |
| INPUTS: | 0.25 mV/500R (Microphone) 120 mV/47k (Line) 0.15 mV/k (DIN) | |
| OUTPUTS: | 1 V/47k (Line) 2 mW/8R (Headphone) | |
| SIZE: | 435 (W) x 120 (H) x 300 (D) mm | |
| PRICE: | around £290 - £300 | |

A very good set of figures, these, and for the price asked in return, very good value for money. I have had my hands on machines costing a great deal more, from better known names, that have not performed to this standard. There is little to pick up on here, save maybe that the response is decidedly restricted on the cheaper tape types, regardless of how much the user may play with the tuning.

Metal and 'high-bias' types, however, gave better than expected results.



The unfamiliar controls in the bottom right-hand corner operate the built-in test oscillator for those of you who like to squeeze the last drop of perfection out of your system.



Last minute news, hot from the postman, is of Wharfedale's new DIY Speakercraft range, including treble, mid-range and bass drivers and crossover networks.



IT'S THAT YOUNG DEVIL JENKINS ON ABOUT LOWERING THE MODULUS OF ELASTICITY OF AIR... IS HE SENDING ME UP AGAIN STAN??!

In Use

As you must expect by now, the Alpage AL-300 did not disgrace itself under listening tests any more than it did sat sitting in the middle of a test bench. Despite the optimisation system — which produced audible improvements in most brands of tape, at least at the top end — the AL-300 did seem to favour some manufacturers' wares. Maxell XLIIS gave consistently superior results to any other similar mixture and TDK metal outperformed all rivals. These two were thus employed for the listening tests.

In both cases the sound was clearer and sharper with these tapes, than with competitive productions and a smoother high frequency was evident. This would tend to suggest bias requirements were well met — but with 'adjustable' bias how could this be?


Anyway the AL-300 is a top class cassette deck, regardless of the vagaries of tape types. It gave consistently good results with a nicely 'open' sound, free of any of the dreaded 'cassette compression' which occurs with some designs. The bass response is very good, if a little on the full side of neutral. Treble is well extended and clean.

About the only real complaint is that it is damned difficult no, let's not be polite — impossible is a better word — to get at the heads and rollers to clean them. To do so one must first heave off the door — a procedure which is studiously ignored throughout the manual. Tsk tsk.

Summary

A well-designed cassette machine with a particularly versatile recording facility that offers audible improvements with most tape types. The head circuitry is especially well done and should guarantee good results from the AL-300 in a wide range of applications.

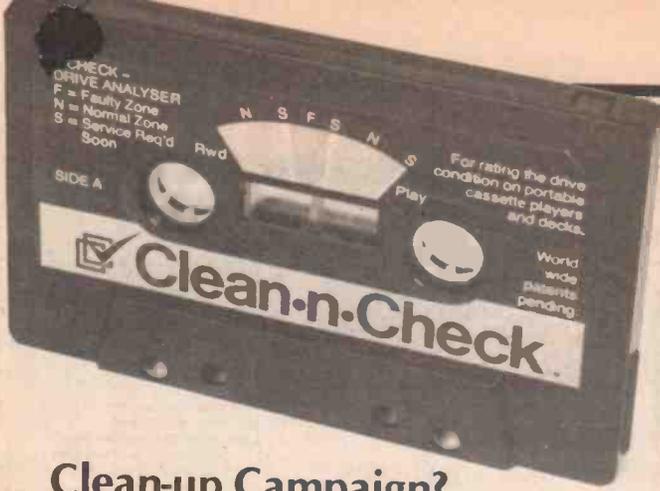All in all, the Alpage offers excellent return for the asking price.



Clean-up Campaign?

While rambling on about tape and associated machinery, it seems like a good time to mention a clever little gadget which drifted across my desk recently. It is endearingly entitled 'Clean and Check'. Not a bad title in light of the fact that this describes its function in life perfectly.

After all, you can't fit 'A-device-for-checking-drive-belt-tensions-and-motor-operation-and-cleaning-both-the-heads-and-rollers-which-comes-complete-in-one-neat-little-box-which-opens-in-two-directions-just-to-confuse-you' all onto a cassette case now, can you? Sensible marketing, that.

One half of the package is a cassette body which contains a belt connecting the two hubs together. Once it is placed in the machine and the machine is started, the belt comes under tension moving a pointer across a scale to indicate the state of health of the drive system. Clever and effective.

The other half is a clean-up set, consisting of two bottles of cleaning fluid: one for the heads and another to take care of the rubber rollers etc. Cotton swabs are provided for applying the magic liquids to those important little places in the machinery.

Trying It Out

The cleaning mixtures proved most efficient in de-filming rollers on the aging machines we tried it on. The head cleaner too did its job without complaint and seemed as good as any other chemical brew I've wiped across bits of metal in the past.

The drive checker, I can only say, seems a great idea — I didn't have any dying drive systems to prove it on, but the belt responds to change in tension quite well. The idea is so obvious once someone tells you about it, you wonder why no-one has thought of it before.

A neat little package. Good value at £4.50 all inclusive. Every home should have one.

Available from Technology Resources Ltd, Dept 654, Hendon Road, Sunderland SR9 9XZ.

ETI



IT LIVES AGAIN!

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.


Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics — It's Easy**. Originally a long-running series in Electronics Today International, **Electronics — It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenomenally successful publication is available again, in its third reprint. **Electronics — It's Easy** is a comprehensive and simply-written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics — It's Easy** by mail order using the coupon below. Make cheques or postal orders payable to ASP Ltd; alternatively you may pay by Access or Barclaycard.

Send to: Sales Office (Specials),
 Argus Specialist Publications Ltd,
 145 Charing Cross Road, London WC2H 0EE.
 Please send me copies of Electronics —
 It's Easy. I have enclosed £. (£4.95 each
 including p&p).

NAME
 ADDRESS

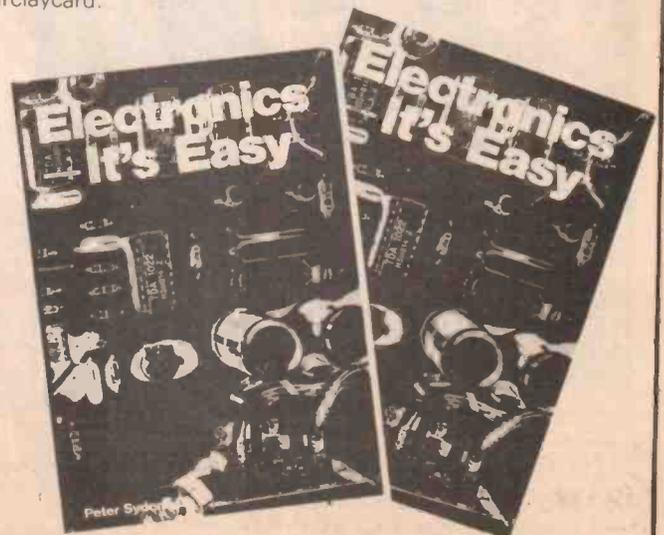Please debit my account
 My Access/ Barclaycard No. is
 Signature



RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture

Tested and fully guaranteed. Ex-stock delivery.

Henry's

01-723 1008/9

404 EDGWARE ROAD, LONDON W2 1ED



FREE RECHARGE SERVICE AFTER PURCHASE

£6.95

inc VAT Post & Pack 60p

COMPLETE WITH DATA

PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.

£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)

Special stock pack: 60 values, 10 off each £5.50

DIODES: IN4148 3p each. Min order quantity - 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each.

DIL SOCKETS: High quality, low profile sockets.
8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN. ORDER - U.K. £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

CLEF ELECTRONIC MUSIC

MASTER RHYTHM

As published in Practical Electronics



KIT. - £79.

BUILT - £119

- FULLY PROGRAMMABLE TWENTY-FOUR PATTERNS
- EIGHT PARALLEL TRACKS
- TWELVE INSTRUMENTS
- SEQUENCE OPERATION

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.


PIANOS

SPECIALISTS SINCE 1972 STAGE & DOMESTIC TYPES



The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

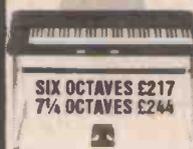Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufacture.



SIX OCTAVES £217
7 1/2 OCTAVES £244

STRINGS £179

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch plus two-phase Chorus.

ROTOR-CHORUS £89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" p.c.b. Mains P.S.U. included.

KEYBOARDS

Square front with two hole actuator - easily cut.

49 NOTE £28.75; 61 NOTE £38
73 NOTE £47; 88 NOTE £57

OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates - in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dopt. E.T.I.)
44A BRAMHALL LANE SOUTH, BRAMHALL,
STOCKPORT, CHESHIRE SK7 1AH. 061-439 3297

| TYPE | SERIES No. | SECONDARY RMS Volts | CURRENT | PRICE |
|---|------------|---------------------|---------|--|
| 30VA 70 - 30mm 0.45 Kg Regulation 18% | 1X010 | 6 - 6 | 2.50 | £4.48 - 0.87p P/P - 0.80p VAT |
| | 1X011 | 9 - 9 | 1.66 | |
| | 1X012 | 12 - 12 | 1.25 | |
| | 1X013 | 15 - 15 | 1.00 | |
| | 1X014 | 18 - 18 | 0.83 | |
| | 1X015 | 22 - 22 | 0.68 | |
| | 1X016 | 25 - 25 | 0.60 | |
| 2X010 | 30 - 30 | 0.50 | | |
| 50VA 80 - 35mm 0.9 Kg Regulation 13% | 2X010 | 6 - 6 | 4.16 | £4.93 - £1.10 P/P - 0.90p VAT |
| | 2X011 | 9 - 9 | 2.77 | |
| | 2X012 | 12 - 12 | 2.08 | |
| | 2X013 | 15 - 15 | 1.66 | |
| | 2X014 | 18 - 18 | 1.38 | |
| | 2X015 | 22 - 22 | 1.13 | |
| | 2X016 | 25 - 25 | 1.00 | |
| 2X017 | 30 - 30 | 0.83 | | |
| 2X028 | 110 | 0.45 | | |
| 2X029 | 220 | 0.22 | | |
| 2X030 | 240 | 0.20 | | |
| 80VA 90 - 30mm 1 Kg Regulation 12% | 3X010 | 6 - 6 | 6.64 | £5.47 - £1.43 P/P - £1.04 VAT |
| | 3X011 | 9 - 9 | 4.44 | |
| | 3X012 | 12 - 12 | 3.33 | |
| | 3X013 | 15 - 15 | 2.66 | |
| | 3X014 | 18 - 18 | 2.22 | |
| | 3X015 | 22 - 22 | 1.81 | |
| | 3X016 | 25 - 25 | 1.60 | |
| 3X017 | 30 - 30 | 1.33 | | |
| 3X028 | 110 | 0.72 | | |
| 3X029 | 220 | 0.36 | | |
| 3X030 | 240 | 0.33 | | |
| 120VA 90 - 40mm 1.2 Kg Regulation 11% | 4X010 | 6 - 6 | 10.00 | £6.38 - £1.43 P/P - £1.17 VAT |
| | 4X011 | 9 - 9 | 6.66 | |
| | 4X012 | 12 - 12 | 5.00 | |
| | 4X013 | 15 - 15 | 4.00 | |
| | 4X014 | 18 - 18 | 3.33 | |
| | 4X015 | 22 - 22 | 2.72 | |
| | 4X016 | 25 - 25 | 2.40 | |
| 4X017 | 30 - 30 | 2.00 | | |
| 4X018 | 35 - 35 | 1.71 | | |
| 4X028 | 110 | 1.09 | | |
| 4X029 | 220 | 0.54 | | |
| 4X030 | 240 | 0.50 | | |
| 160VA 110 - 40mm 1.8 Kg Regulation 8% | 5X011 | 9 - 9 | 8.89 | £8.44 - £1.43 P/P - £1.48 VAT |
| | 5X012 | 12 - 12 | 6.66 | |
| | 5X013 | 15 - 15 | 5.33 | |
| | 5X014 | 18 - 18 | 4.44 | |
| | 5X015 | 22 - 22 | 3.63 | |
| | 5X016 | 25 - 25 | 3.20 | |
| | 5X017 | 30 - 30 | 2.66 | |
| 5X018 | 35 - 35 | 2.28 | | |
| 5X026 | 40 - 40 | 2.00 | | |
| 5X028 | 110 | 1.45 | | |
| 5X029 | 220 | 0.72 | | |
| 5X030 | 240 | 0.66 | | |

Also available at Electrovalve, Maplins, Marshalls, Technomatic and Watford Electronics.



FREEPOST T4, GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY, CT2 7EP
Phone (0227) 54778 - Technical (0227) 64723 - Telex 965 780

I.L.P. TRANSFORMERS

INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

| TYPE | SERIES No. | SECONDARY RMS Volts | CURRENT | PRICE |
|---|------------|---------------------|---------|---|
| 225VA 110 - 45mm 2.2 Kg Regulation 7% | 6X012 | 12 - 12 | 9.38 | £10.06 - £1.73 P/P - £1.77 VAT |
| | 6X013 | 15 - 15 | 7.50 | |
| | 6X014 | 18 - 18 | 6.25 | |
| | 6X015 | 22 - 22 | 5.11 | |
| | 6X016 | 25 - 25 | 4.50 | |
| | 6X017 | 30 - 30 | 3.75 | |
| | 6X018 | 35 - 35 | 3.21 | |
| | 6X026 | 40 - 40 | 2.81 | |
| | 6X025 | 45 - 45 | 2.50 | |
| | 6X028 | 110 | 2.04 | |
| 6X029 | 220 | 1.02 | | |
| 6X030 | 240 | 0.93 | | |
| 300VA 110 - 50mm 2.6 Kg Regulation 6% | 7X014 | 18 - 18 | 8.33 | £11.66 - £1.73 P/P - £2.01 VAT |
| | 7X015 | 22 - 22 | 6.82 | |
| | 7X016 | 25 - 25 | 6.00 | |
| | 7X017 | 30 - 30 | 5.00 | |
| | 7X018 | 35 - 35 | 4.28 | |
| | 7X026 | 40 - 40 | 3.75 | |
| | 7X025 | 45 - 45 | 3.33 | |
| 7X023 | 50 - 50 | 3.00 | | |
| 7X028 | 110 | 2.72 | | |
| 7X029 | 220 | 1.36 | | |
| 7X030 | 240 | 1.25 | | |
| 500VA 140 - 60mm 4 Kg Regulation 4% | 8X017 | 30 - 30 | 8.33 | £15.53 - £2.05 P/P - £2.64 VAT |
| | 8X018 | 35 - 35 | 7.14 | |
| | 8X026 | 40 - 40 | 6.25 | |
| | 8X025 | 45 - 45 | 5.55 | |
| | 8X033 | 50 - 50 | 5.00 | |
| | 8X042 | 55 - 55 | 4.54 | |
| | 8X028 | 110 | 4.54 | |
| 8X029 | 220 | 2.27 | | |
| 8X030 | 240 | 2.08 | | |
| 625VA 140 - 75mm 5.0 Kg Regulation 4% | 9X017 | 30 - 30 | 10.41 | £21.54 - £2.20 P/P - £3.56 VAT |
| | 9X018 | 35 - 35 | 8.92 | |
| | 9X026 | 40 - 40 | 7.81 | |
| | 9X025 | 45 - 45 | 6.94 | |
| | 9X033 | 50 - 50 | 6.25 | |
| | 9X042 | 55 - 55 | 5.68 | |
| | 9X028 | 110 | 5.68 | |
| 9X029 | 220 | 2.84 | | |
| 9X030 | 240 | 2.60 | | |

IMPORTANT: Regulator references All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

See our adverts, also on pages 30 & 31

NOW 95 TOROIDAL TYPES FROM 30VA TO 625VA

★★ I.L.P. TOROIDALS ★★

We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Induced hum is reduced by a factor of ten. I.L.P. toroidals cost virtually the same as the older types which they are rapidly replacing. Now increased production capacity means even lower prices. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. GUARANTEED 5 YEARS.

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel).

For 110V Primary insert 0 in place of "X" in type number. For 220V Primary (Europe) insert 1 in place of "X" in type number. For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example: 50VA 240V 6+6V 4.16A=22010.

- ★ CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.
- ★ FREEPOST FACILITY (U.K. only). Simply send your order in envelope marked FREEPOST to address below. NO STAMP REQUIRED.
- ★ TO ORDER Enclose Cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd. or quote your ACCESS OR BARCLAYCARD account number. VAT must be included with U.K. order. To pay C.O.D. add £1 extra to TOTAL value of order.

GOODS DESPATCHED WITHIN 7 DAYS OF RECEIPT OF ORDER

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply Transformer(s) No.(s)

Total purchase price £

Enclose Cheque | Postal Orders | International Money Order | Debit my Access/Barclaycard Account No.


NAME
ADDRESS

Signature

|ETI11

CASIO

WHAT WILL THEY THINK OF NEXT?

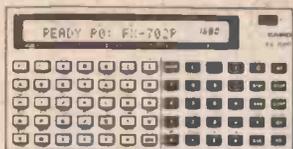

FX-702P

- Display capacity for 20 alpha-numeric characters.
- High utility variation of program steps and data memories.

ONLY £115.95
FAZ interface available soon.
FP10 printer unit available soon.



FX 330
£15.95



FX 510
£18.95



FX 68
£18.95



FX 6100
£18.95



FX 7100
£23.95



FX 8100
£23.95

CASIO 601P
£51.95



FX 180P
£18.95



FX 200P
£17.95



FX 2700P
£18.95



FX 3500P
£21.95



FX 502P
£61.95



FX 602P
£71.95

CASIO FA 1 ADAPTOR CASSETTE INTERFACE for 501P, 502P, 601P, 602P

FA1 £19.95

TEXAS INSTRUMENTS

| | | | |
|-----------|---------|-------------------------------|---------|
| TI 51-111 | £29.95 | TI 57 | £26.95 |
| TI 58 | £57.95 | TI 58C | £68.95 |
| TI 59 | £121.95 | PC 100C printer for 58/58C/59 | £148.95 |

SHARP EL 5101 16 digit alpha/numeric £41.95 EL 5100 24 digit alpha/numeric £51.95
Pocket Computer PC1211 £91.95 CE121 Cassette Interface £15.95
CE122 Printer/Cassette Interface £71.95

FULL RANGE OF CASIO SHARP AND TEXAS AVAILABLE. S.A.E. WITH ENQUIRIES PLEASE


SEND CASH, CHEQUES, P.O., etc., PAYABLE TO C.S.S. - OR QUOTE ACCESS NUMBER ON ORDERS OVER £30 only. C.O.D. AVAILABLE AT EXTRA CHARGE OF £1.50 UP TO £250

CALCULATOR SALES & SERVICE


FREEPOST (no stamp required) REDDITCH, WORCS. B98 0BR

Telephone (0527) 43169

TWO SIDES TO YOUR SUCCESS FROM VERO

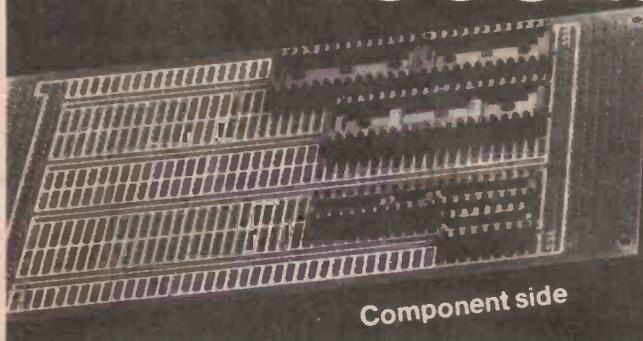

Component side

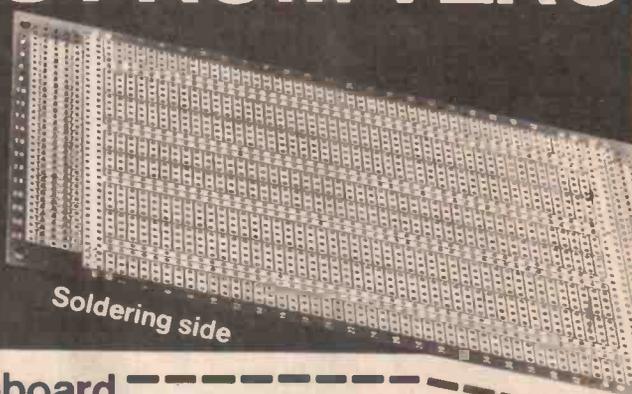

Soldering side

The Low Cost Eurocard Size Microboard

Fully Compatible with indirect connectors and Card Frames to the latest international specifications.

Accepts any Integrated circuit package - allows high packing density.

Screen Printed with 'island' pattern for ease of use - ideal for solder and wire wrap applications.



Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hampshire SO5 3ZR. Tel (04215) 62829

| PLEASE SUPPLY QTY. | ORDERCODE | DESCRIPTION | SIZE | PRICE |
|--------------------|------------|-------------|-------------|---------------------------------------|
| | 200-22271B | MICROBOARD | 160 x 100mm | £3.47 each (including VAT & carriage) |
| | 200-22270E | MICROBOARD | 160 x 233mm | £5.47 each |


ET1.11.81

Name: _____

Address: _____

Postal Code: _____

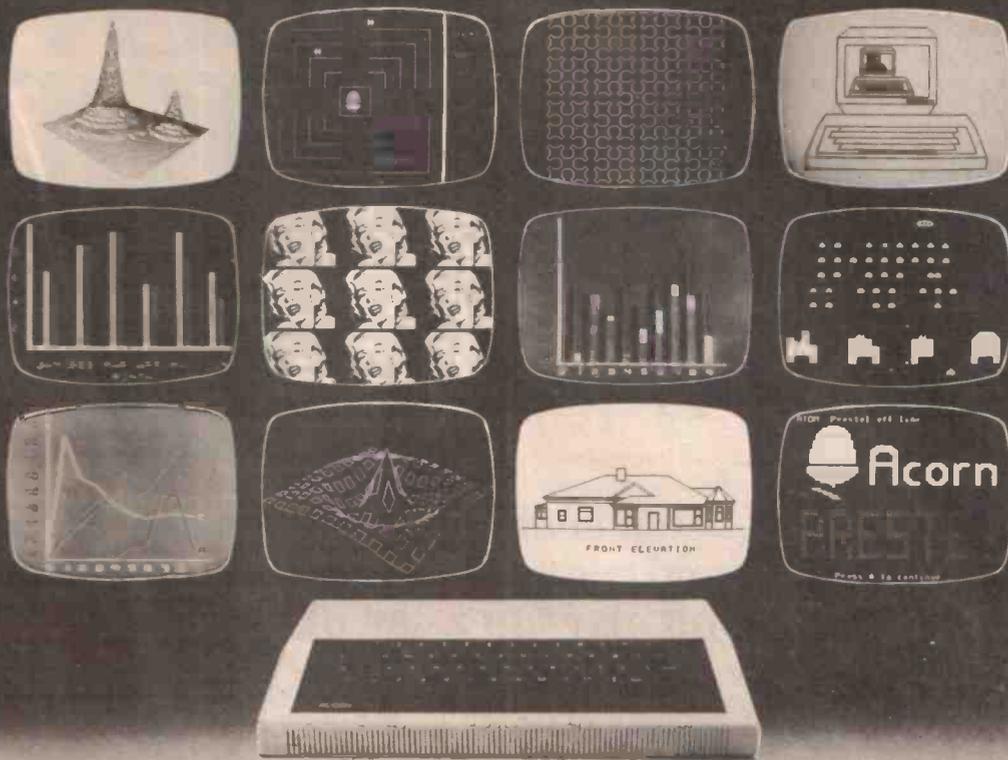My Access/Barclay No. Is: _____ Signed: _____



CHOOSE ATOM POWER

At work or play - everything you need in a personal computer

The Atom is a machine to be used. Every day, day after day. It's a full function machine - check the specification against others. It's rugged, easy to operate built to last and features a full-size typewriter keyboard.

Just look at some of the features!

- More hardware support than any other microcomputer
- Superfast BASIC - can be updated to BBC BASIC if required
- High resolution and comprehensive graphics ideal for games programmers and players*
- Integral printer connection*
- Software available for games, education, maths, graphs, business, word processing, etc.
- Other languages: Pascal, FORTH, LISP
- I/O port for control of external devices
- Built-in loudspeaker
- Cassette interface
- Full service/repair facility
- Users club

* Expanded version only

Optional Extras

- Network facility with Econet
- Disk
- PAL UHF colour encoder
- Add-on cards include 32K memory, analogue to digital, viewdata VDU, disk controller, daisywheel printer, plus many, many more!
- Power supply

FREE MANUAL

The Atom's highly acclaimed manual comes free with every Atom and leaves nothing out. In just a while you'll be completely at ease with your new machine! Within hours you'll be writing your own programs.



YOU AND YOUR CHILDREN

More and more schools are buying Atoms. More and more children will learn on an Atom. You can give them that extra familiarity with an Atom in the home.



4a Market Hill,
CAMBRIDGE CB2 3NJ

When you order your Atom we will include full details of all software packs and the optional hardware.

To: Acorn Computer Limited, 4A Market Hill, Cambridge CB2 3NJ.

I enclose a cheque/postal order for £.....

Please debit my Access/

Barclaycard No.....

Signature.....

Name (please print).....

Address.....

Telephone Number.....


Registered No. 1403810 VAT No. 215 400 220

| Quantity | Item | Item price inc. VAT + P&P | Totals |
|----------|----------------------------------|---------------------------|--------|
| | Atom Kit 8K ROM + 2K RAM | @ £140.00 | |
| | Atom Assembled 8K ROM + 2K RAM | @ £174.50 | |
| | Atom Assembled 12K ROM + 12K RAM | @ £289.50 | |
| | Power Supply | @ £ 10.20 | |
| | | TOTAL | |

Computer stores are stocking Atoms - there's a list below, but if you have any problems getting hold of one just fill in the coupon and we'll rush one to you within 28 days. If the machine isn't all you expected, or all we've told you, just return it within 14 days for a full refund.

MOM, Aberdeen 22863. Broadway Elect, Bedford 213639. Owl Computers, Bishops Stortford, 52682. Eltec Services, Bradford 491371. Gamer, Brighton 698424. Electronic Information Systems, Bristol 774564. Cambridge Comp Store, Cambridge 65334. Cardiff Micros, Cardiff 373072. Bellard Elect. Chester 380123. Emprise, Colchester 865926. Silicon Centre, Edinburgh 332 5277. Esco Computing, Glasgow 204 1811. Control Universal, Harlow 31604. Unitron Elect, Haslington. Castle Elect, Hastings 437875. Currys Micro Systems, High Wycombe. Customised Electronics, Leeds 792332. D.A. Computers Leicester 708402. Microdigital, Liverpool 236 0707. Barrie Elect, London 488 3316. Eurocalc London 729 4555. Microage London 959 7119. Sinclair Equip. Int (Export) London 235 9649. Off Records, SW12, 674 1205. Technomatic, NW10 452 1500. NSC Comp Shops, Manchester 832 2269. Customised Electronics, Middlesbrough 247727. Compshop, New Barnet 441 2922. H.C.C.S., Newcastle. 821924. Newcastle Comp Services, Newcastle 615325. Anglia Comp Centre, Norwich 29652. Leaslink Viewdata, Nottingham 396976. R.D.S. Electrical Portsmouth 812478. Computers for All, Romford 751906. Intelligent Artefacts, Royston, Arrington 689. Computer Facilities Scunthorpe. Datron Micro Centre Sheffield 585490. Superior Systems, Sheffield 77824. Q-TEC Systems, Stevenage 65385. 3D Computers, Surbiton (01) 337 4317. Abacus Micro Comp, Tonbridge, Paddock Wood 3861. Northern Comp, Warrington 601683. Compass Design Wigan Standish 426252.

ROBOTICS TODAY

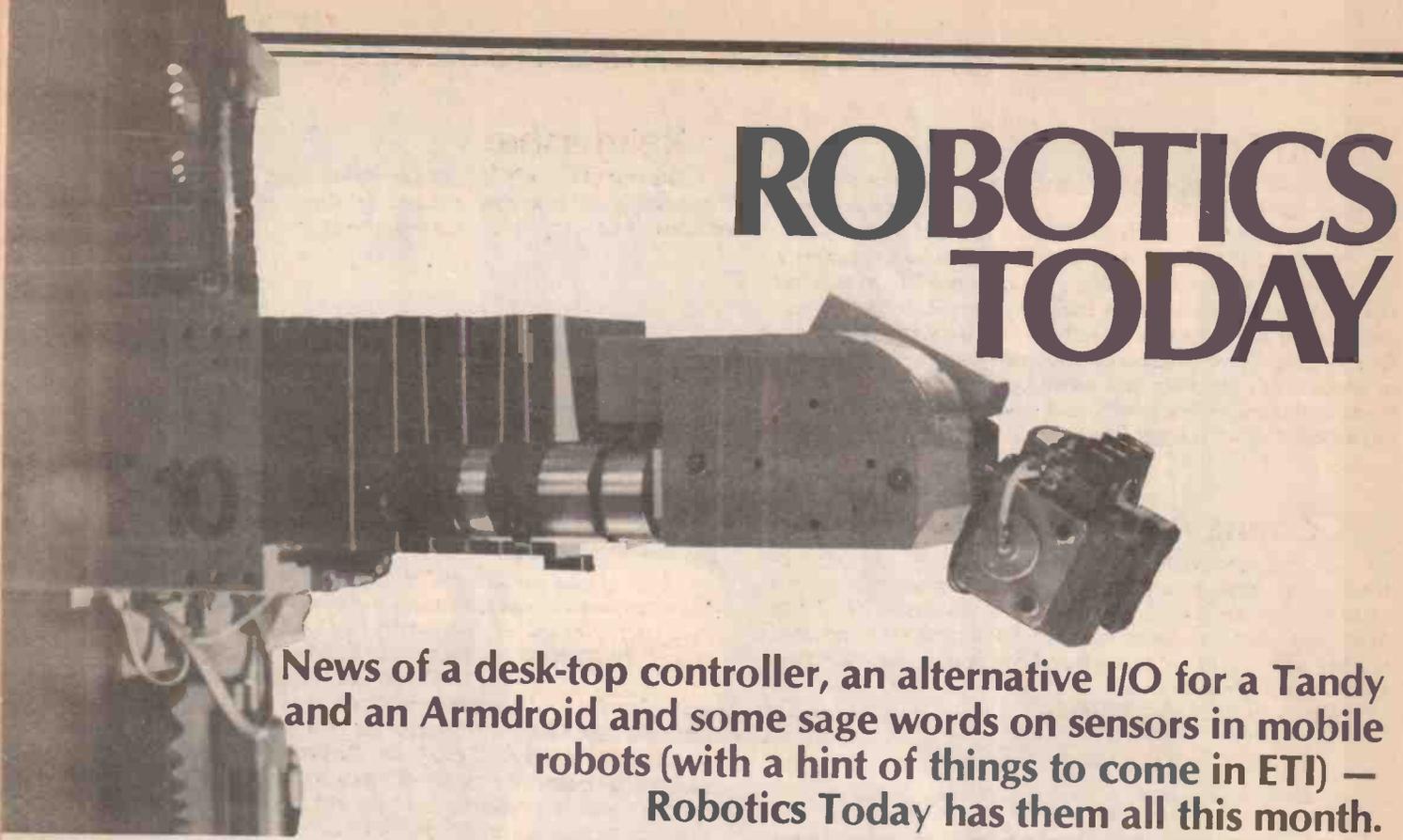

News of a desk-top controller, an alternative I/O for a Tandy and an Armdroid and some sage words on sensors in mobile robots (with a hint of things to come in ETI) — Robotics Today has them all this month.

The greatest single problem still to be solved for home roboticists is that of position sensing. It is fairly straightforward to produce an 'intelligent' mobile unit, which will have control over its own drive system and be able to operate an arm or gripper. Stored away in the memory can be routines which tell the unit how to handle common situations, such as running into a wall or chair etc, and command routines instructing it how to pick up items at the right time.

All this power is, of course, totally useless if the robot never knows where it is! The only thing home-built robots seem to have been able to do up to now is bounce off obstacles, trying different directions until they succeed in passing the barrier. Very crude and limiting on size.

After all, it is reasonable for something the size of a toy tank to bounce around the skirting boards at low velocity, but would you allow a 4 ft steel box on tracks moving at 5 mph to navigate your home in the same manner? Not unless you're round the loop you wouldn't.

Answers On A Postcard Please . . .

What is required is a reliable form of detection and avoidance initiation such that the mobile is capable of reacting to an obstacle, before it grinds it into the carpet.

There are many available techniques for this:

- Line or wire following
- Ultrasonic
- Infra-red
- Mapping
- Vision sensing or image recognition.

Line Following This involves running a white line or signal-carrying wire around the required path of the mobile. In the first case, photo-diodes can be used to ensure the machine travels the line without deviation. Humans then have to keep clear of the robot!

This technique is widely used in factory environments with low personnel counts, such that a machine doggedly trotting down the line does not disrupt too many working days.

Wire following is more sophisticated, in that different

signals can be passed through different 'paths' and the robot set to detect the changes at various points, thus giving a more flexible routing capability.

Ultrasonic And Infra-red Both involve the reception and/or transmission of signals from the robot such that the received signals can be interpreted under program control to give the machine a 'picture' of its environment.

Ultrasonics are the most suitable for home or office machines and can be employed in two ways, either as a form of 'song', pinging out pulses of sounds and translating the received 'echoes' into a map of the surrounding world, or by use of location beacons placed around the workspace which send out recognisable signals which the robot then relates to its own position.

Mapping Simply, this is just reading into the robot, by whatever means, a complete and detailed map of the area it is supposed to operate in. This works perfectly as long as no-one moves a chair, or a filing cabinet — or a palette full of car parts! Not really suitable for all but the rare occasion where things do not change over a decent period, say a day.

If used in conjunction with some other sensors — say ultrasonic — which update the map continually and allow for people wandering around from time to time, then mapping can be a powerful technique.

Image Recognition Universally accepted as the ultimate end for robot sensors. 'Eventually all robots will be made this way', etc. Having a machine which can recognise objects as something more than a block to bend the chassis around is an obvious advantage.

Much work is being done, mainly with line-scan camera techniques, but we are a long way off the 'Star Wars' approach to mechanical creatures yet. Processing power and defining the image fast enough are the problems which are presently holding things up.

This is the only method that would not require collision sensing built in as well. If it can see it — it can avoid it. All the other techniques require the failsafe facility to stop if they hit something, or someone, undetected until impact.

And So?

It would thus appear that none of the available *practical* sensing techniques solves the problem fully. The only answer is to combine them to form the necessary facility.

As far as ETI is concerned, there is little point presenting a robot project to our readership if its only use lies in running down the expensive batteries used to power it. A mobile that runs around looking pretty is pretty pointless too in our opinion. Our investigations into sensors have been from the point of view of producing a machine that could be put to use in both the home and work environments, and developed into a powerful intelligent mobile in logical steps.

Coming Attraction

We reckon we've found a way of doing it, too. Coming very soon — as soon as we arrange the metalwork side to our satisfaction — will be a ETI mobile robot, which will be a **TRUE** robot, not an animal approximation, not a program-controlled toy, but a device to put to work and develop an understanding of robotics in the real sense.

Watch these pages for details.

Readership

The first of our readers to take up last month's offer to use these pages for publicity is a Mr. D. Watts of Lincoln, who reckons he can improve upon our arm I/O.

Dear Sir,

Would you please send the Robot machine code program listing, for the Tandy Model 1.

Some comments on the article, just for interest: I am delighted to see that all the hardware mechanics have been made available as a complete kit, since mechanical parts are not nearly so universal as standard silicon chips. It would be useful if a single stepping motor and gearbox could be purchased separately for control systems other than the robot arm. Also, we are not all sufficiently well heeled to throw £200 at one go.

Having just constructed a similar type of interface for a paper tape reader, may I say that I am not too happy about having the input buffer strobed out of its tri-state by data line 1. No doubt the software program will make sure that there is no conflict with internal data on the bus, but if there is corruption, or no program at all, then I would guess there will be trouble amongst the hardware. Perhaps I have overlooked something and it is fail-safe?

The straightforward **OUT** and **IN** strobes available on the Tandy edge connector are the obvious and safe way of controlling the tri-states. I assume you have not used these so that the system is more easily adapted to other micros, which do not have the grace to supply strobe lines.

On second thoughts, your design does avoid the need for memory decoding to port number, but this can be neglected, or reduced to a single line if necessary.

Another point in the circuit design is the use of an inverting buffer for reading the microswitches. Why not use a non-inverting type, so that for all normal purposes, a 1 is a 1 and a 0 is a 0? The inversion can be provided by one line in the software, CPL, or 'complement the bits in the accumulator'. The same thing in BASIC is $X = 255 - INP(1)$.

To finish off, I have included my own input/output design on the next sheet.

Yours sincerely,
D. Watts.
Lincoln.


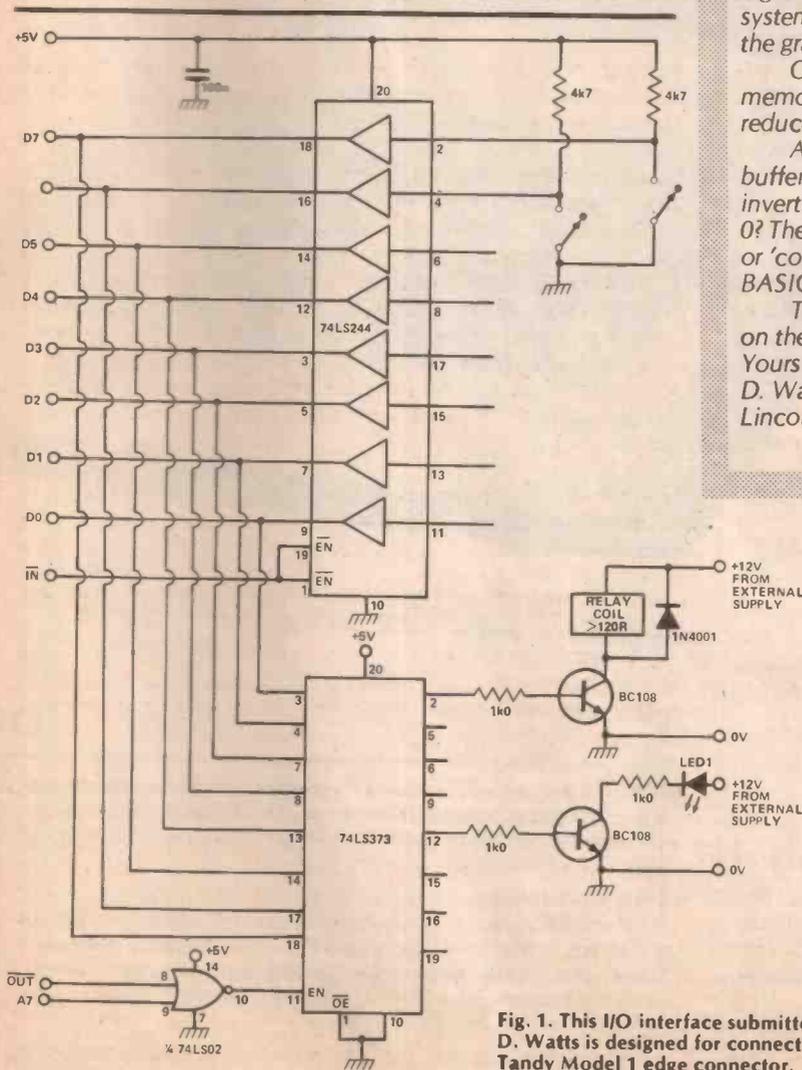


Fig. 1. This I/O interface submitted by D. Watts is designed for connection to a Tandy Model 1 edge connector.

HOW IT WORKS

The three 74LS chips may be powered from the Tandy +5 V on the edge connector. Any other devices must have a separate supply, with only the negative line in common with the Tandy negative. The BC108s act as voltage level shifters, allowing the 5 V TTL logic to switch 12 V relays, for example.

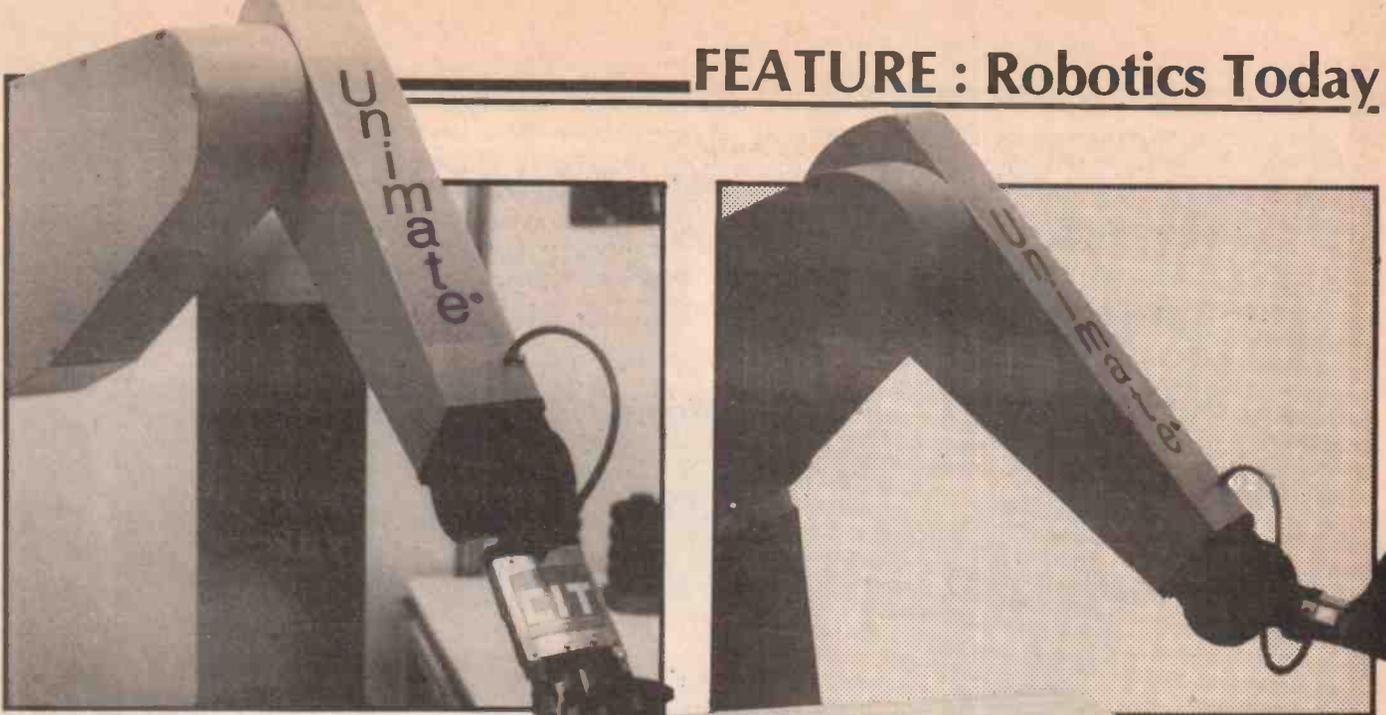The interface may be used with BASIC or machine code. One reason for the NOR gate is to avoid a spurious **OUT** strobe which occurs every time a **CLS** is operated, or a **READY >** prompt occurs. This gives the equivalent of an unwanted **OUT 255, 0** in the middle of a BASIC program. The interface will respond to any port number between 0 and 127.



The top two photographs show the Cranfield hand fitted to a Unimate Puma. Unlike most grippers, this one is designed to simulate the human hand — both Japan and the USA are trying to buy it.

A BASIC test program is as follows:

```

10 CLS
20 X = INP(1)
30 PRINT X;
40 OUT 1, 255
50 FOR Z = 1 TO 100
60 NEXT Z
70 OUT 1,0
80 FOR Z = 1 TO 100
90 NEXT Z
100 GOTO 20
    
```

It will read the switches and pulse all the outputs. To obtain the inverse of the switches use

```
20 X = 255 - INP(1)
```

and to mask off any unwanted bits, one may use the AND function, eg

```
25 X = X AND 128
```

will only respond to bit 8, with all other bits set to zero internally.

Computer Controller For Robots

Called the 'Snipe Engineer', this little desk-top machine is designed as an intelligent terminal, or controller for stand-alone applications.

It has 32K of memory on-board and can be lined to any existing computer installation. As you can see, a novel LCD display format has been adopted, presumably to bring down costs.

There exists a range of SNIPE products, including terminals and peripherals, all of which are produced by FELTEC, Queensway, New Milton, Hants (telephone 0425 617477).



This little box could solve a few big problems for anyone with a robot to control. A desk-top intelligent terminal, it's one of a range of products from FELTEC.

ETI

This new series will provide a stage upon which our readers may display their robotics achievements. It is intended to cover the practical application of robots in Britain today, be it at hobbyist level or in industry.

Readers in either category are invited to write to the editor of ETI, detailing their experiments, projects, application or usage of robotics. Any articles published will be paid for at commercial rates. It is also hoped to run an 'Ideas Forum' wherein readers can exchange views and ideas but that depends upon the response of our readers — you!

Write to: THE EDITOR, ETI MAGAZINE, 145 CHARING CROSS ROAD, LONDON WC2H 0EE and mark your envelope "Robotics Today".

404 EDGWARE RD. LONDON, W2 1ED TEL: 01-402 6822

TANGERINE • TANGERINE • TANGERINE • TANGERINE • TANGERINE

MICROTAN 65

Microtan 65 is the most advanced, powerful, expandable micro computer available - it also happens to be the most cost effective!



Electronic Today International held a mammoth survey of kits. The result: Microtan 65 WINS COMPUTER CLASS!

MICROTAN 65 CONTENTS

High quality, plated thru hole printed circuit board, solder resist and silk screened component identification. 6502 microprocessor, 1K monitor, TANBUG. Now with Y Bug, 1K RAM for user programme, stack and display memory. VDU alphanumeric display of 16 rows by 32 characters. MICROTAN 65 system file binder, 136 page, bound, users hardware/software manual with constructional details and sample programmes. Logic and discrete components to fully expand MICROTAN 65.

The MICROTAN 65 kit has won widespread acclaim for its superb presentation. We pay attention to detail!

KIT FORM **£69.00** + V A T £10.35, total £79.35.

MICROTAN 65 assembled and tested. Specification as above, but assembled and fully bench tested by ourselves **£79.00** + V A T £11.85, total £90.85.

MICROTAN 65 OPTIONS

LOWER CASE PACK

Two integrated circuits which connect into locations on MICROTAN allowing 128 displayable characters **£9.48** + V A T £1.42, total £10.90.

GRAPHICS PACK

Five integrated circuits which connect into locations on MICROTAN allowing the display of chunky graphics (64 x 64 pixels). What are chunky graphics? Well, imagine a piece of graph paper with 64 squares vertically and 64 squares horizontally, a total of 4096. Each square can be made black on white. **£6.52** + V A T 98p, total £7.50.

20 WAY KEYPAD

Inexpensive means of getting up and running. Uses 'Schoeller' key-switches, and connects to MICROTAN through a 16 pin 0.111 plug on ribbon cable. Black anodised escutcheon, with TANGERINE legends, finishes off what must be the best value for money keypad available. Available assembled and tested **£10.00** + V A T £1.50, total £11.50.

*Space Invaders game (for use with keypad only)

£15.22 + V A T £2.28, total £17.50.

POWER SUPPLIES

MPS 1 Input 120 or 240V AC Output 5 Volts at 3 Amps Regulated. MPS 1 will power both MICROTAN and TANEX fully expanded. Built on the same size printed circuit board as MICROTAN etc. Available as a fully built and tested unit.

£23.00 = V A T £3.45, total £26.45.

X MPS2 +5V 6A, +12V, -5 and -12V switch mode system PSU **£69.13** + V A T.

MINI-SYSTEM RACK

We have produced a mini-system rack which accepts MICROTAN 65, TANEX and our mini-mother board. It has an integral power supply, just plug it into the mains and away you go! Finished in TANGERINE/BLACK, it gives your system the professional finish. Front panel access for I/O cables. AVAILABLE AS AN ASSEMBLED UNIT.

£43.00 + V A T £6.45, total £49.45.

FULL SYSTEM RACK

For the man that has everything! 19 inch wide system rack which accepts MICROTAN 65, TANEX, TANRAM, SEVEN FURTHER EXPANSION BOARDS, TANDOS and THE SYSTEM POWER SUPPLY. Available in many formats, e.g. Individual front panels, full width hinged front panel, back panel with or without connectors.

£49.00 + V A T £7.35, total £56.35.

NEW PRODUCTS

NOW AVAILABLE

HIGH DEFINITION COLOUR GRAPHICS CONTROLLER CARD **£90.85** inc VAT **£120.00** - V A T

SERIAL I/O CARD (From) **£58.00** - V A T
PARALLEL I/O CARD (From) **£47.50** - V A T
ROM CARD (BUILT) LESS ROM **£47.50** - V A T
AIM, KIM INTERFACE CARD **£59.00** - V A T
SERIAL I/O KIT **£17.25** (inc) V A T

SYSTEM MOTHER BOARD WITH 4 SOCKETS FOR SYSTEM RACK **£39** - V A T
SYSTEM MOTHER BOARD WITH 12 SOCKETS FOR SYSTEM RACK **£55** - V A T
32K RAM CARD **£115** - V A T
32K ROM CARD (LESS CHIPS) **£54.65** inc V A T

MICRON COMPUTER

FULLY BUILT, TESTED, and housed in ATTRACTIVE CASES.



£395 inc V A T P&P

6502 based microcomputer VDU alpha numeric display. Powerful monitor TANBUG, 8K RAM, 32 parallel I/O lines, 2 TTL serial I/O lines. Four 16 bit counter timers, Cassette interface, Data bus buffering, Memory mapping control, 71 key ASCII Keyboard, including numeric keypad. Includes power supply. Also includes the first "10K MICROSOFT BASIC" available in the U.K. All the usual BASIC commands.

TANRAM

Available now tanram - 40K Bytes on one board. Single board of bulk memory offering 7K Static RAM (2114), and 32K Dynamic RAM (4116). Onboard refresh is totally transparent to CPU operation and is unaffected by normal DMA's. TANRAM fully expands the available address space of the 6502 microprocessor. MICROTAN, TANEX and TANRAM together provide 16K RAM, 48K RAM, and 1K I/O - that's a lot of memory and a lot of I/O! Built and tested. TANRAM ASSEMBLED.

40K RAM CARD with 16K DYNAMIC RAM £76 - V A T

CONTENTS: High quality plated thru hole printed circuit board, solder resist and silk screened component identification. Full complement of I.C. sockets for maximum expansion 64 way 0.111 edge connector 1K RAM (2114). Data bus buffering. TANRAM users manual.

EXTRA RAM: 1K STATIC (2114) £2.95 each 16K DYNAMIC (4116) £1.50 each

MEMORIES EXPAND YOUR SYSTEM WITH OUR TANGERINE DISCOUNTS 10% for 4, 15% for 8, 20% for 16 APPROVED CHIPS


2102 1K x 1 Static RAM 80p IM 6402 UART £4.50
2708 £6.50 2114 1K x 4 Static RAM £2.95
2716 £6.50 8080A £5.00
MK 4116 16K x 1 Dynamic RAM 4118 1K x 8 Static RAM £7.50
£1.50 All plus V A T

MONITORS (PROFESSIONAL)

RECONDITIONED AND NEW - FROM £35.00 to £129.95

CENTRONICS Ideal for Tangerine PRINTERS

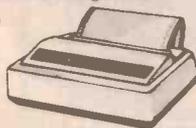CENTRONICS P.I. **£150** + V A T
SHEIKOSHIA **£199** + V A T
Model 730 **£350** + V A T
Model 737 **£395** + V A T



NEW MICROTANTEL POST OFFICE APPROVED PRESTEL - VIEWDATA

• FULL COLOUR GRAPHICS • MICROTAN OWNERS CAN COMMUNICATE WITH EACH OTHER • CAN STORE PRESTEL • CAN BE USED AS AN EDITING TERMINAL • CAN BE INTERFACED WITH PET, APPLE etc.

Just connect to the aerial socket of any colour or black and white domestic T V receiver and to your Post Office installed jack socket and you are into the exciting world of PRESTEL. Via simple push button use, you are able to view 170,000 pages of up to the minute information on many services, order goods from companies - all this without leaving your armchair!

£170 + V A T

TANEX £43.00

Minimum Config Kit

+ V A T £6.45, total £49.45

CONTENTS

High quality plated thru hole printed circuit board, solder resist and silk screened component identification. I.C. sockets for maximum expansion 64 Way 0.111 edge connector 1K RAM, cassette interface, 16 parallel I/O lines, a TTL serial I/O port, two 16 bit counter timers, data bus buffering, memory mapping, logic and discrete components for maximum expansion. TANEX users manual.

TANEX (Minimum configuration) Assembled **£53.00** + V A T £7.95, total £60.95



TANEX EXPANSION

Expanded, TANEX offers 7K RAM, locations for 4K EPROM (2716), locations for 10K extended MICROSOFT BASIC, 32 parallel I/O lines, two TTL serial I/O ports, a d serial I/O port with RS232/20mA loop, full modem control and 16 programmable baud rates, four 16 bit counter timers, cassette interface, data bus buffering, and memory mapping.



EXPANDED TANEX KIT (Excludes ROM, XBUG and BASIC)

£89.70 + V A T £13.46, total £103.16

EXPANDED TANEX ASSEMBLED

£99.70 + V A T £14.96, total £114.66

OPTIONS TO FULLY EXPANDED TANEX IN SIMPLE INEXPENSIVE STAGES.

10K Extended MICROSOFT BASIC in EPROM (with manual) £49.00 + V A T £7.35, total £56.35

Extra RAM 1K (2 x 2114) £5.20 + V A T 78p, total £5.98

SERIAL I/O KIT £10.26 + V A T £1.60, total £11.86

6522 VIA £8.00 + V A T £1.20, total £9.20

XBUG £17.35 + V A T £2.60, total £19.95


AS YOU CAN SEE THE PRICES OF OUR EXPANSION COMPONENTS ARE VERY, VERY COMPETITIVE!

TANGERINE DISC SYSTEM

Z8 CONTROLLER CARD **£150.00** - V A T

DOUBLE SIDED DOUBLE DENSITY DRIVE **£215.00** - V A T

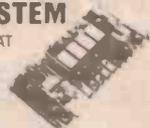CP/M DISK OPERATING SYSTEM **£80** + V A T



71 KEY ASCII KEYBOARD £56.34 + V A T

NO EXTRAS NEEDED.

Uses gold crosspoint keys. Includes numeric keypad and ribbon cable. Available as fully assembled and tested.

SUPER METAL CABINET IN TANGERINE/BLACK

£20.00 + V A T £3.00, total £23.00



PROFESSIONAL ASCII KEYBOARDS Ideal for Tangerine

£29.95 - V A T



• 52 key 7 bit ASCII coded

• Positive strobe +5V -12V

• ASCII characters

• Parallel output with strobe

• Power light on control

• Chip by General Instrument

(G1) TTL output

• Superbly made
• Size 13 x 5.5 x 1.5 ins
• Black keys with white ledgers
• Escape shift return & reset keys
• Control repeat & bell keys
• Complete with DATA

ADD-ON KEYPAD

A compact 12 button keypad suitable for use with above keyboard to extend its functions plus four extra keys. Supplied brand new with with data. A 4x4 non-encoded single mode keyboard.

LIST PRICE £22.00
OUR PRICE **£7.95** - V A T

PLUS MANY NEW EXCITING PRODUCTS IN DEVELOPMENT AUTOMATICALLY AVAILABLE FROM US WHEN RELEASED BY OUR PRINCIPALS TANGERINE LTD

All products are available from stock


FULLY GUARANTEED - BUY WITH CONFIDENCE

BRITISH DESIGN & MANUFACTURE AND ON DEMONSTRATION IN OUR COMPUTER DEPT.

SEND FOR FREE BROCHURE

TANGERINE • TANGERINE
Stockist Enquiries on headed notepaper to:
COMPUTER KIT LTD. (Principal Distributors in U.K.)
11/12 Paddington Green, London, W2, Tele 01-723 5095
Telex: 262284 Ref 1400 TRANSONICS

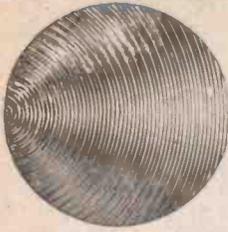All orders pre-paid and official advertised here and elsewhere in this magazine by TANGERINE to be forwarded DIRECTLY to
COMPUTER DEPT., 11/12 PADDINGTON GREEN, LONDON W2




APPROVED
thandar
STOCKIST

B.K. ELECTRONICS

A SOUND CHOICE

APPROVED
thandar
STOCKIST

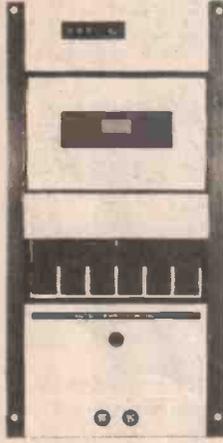★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY




6 piano type keys

STEREO CASSETTE TAPE DECK MODULE.

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2 in x 11 1/2 in. Clearance required under top panel 2 1/2 in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

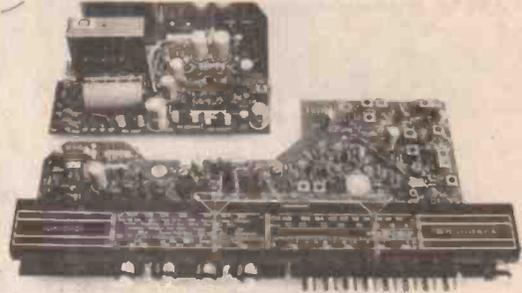Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.



GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS.

Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc., AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3dB.

Tape Sensitivity: Output – typically 150 mV. Input – 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz – 108MHz. Long wave 145kHz – 108kHz. Medium wave. 520kHz – 1620kHz. Short wave. 5.8MHz – 16MHz. **Size:** Tuner – 2 3/4 in x 15 in x 7 1/2 in approx. Power amplifier – 2 in x 7 1/2 in x 4 1/2 in approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £23.50 plus £2.50 postage and packing.**

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").

These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Price: –**


15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each. £2.50 Packing and Carriage each.**

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz. magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each. £2.50 Packing and Carriage each.**

8" 50 watt R.M.S. Impedance 8 ohm, 20 oz. magnet, 1" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone and black protective grill. **Price £8.90 each. £1.25 Packing and Carriage each.**

PIEZO ELECTRIC TWEETERS – MOTOROLA

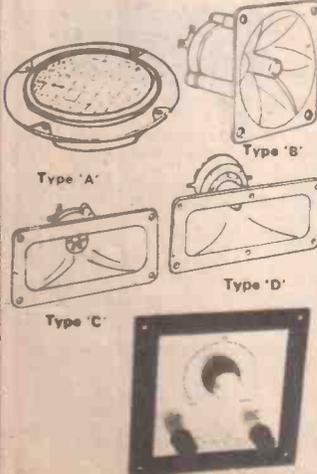Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**




Type 'A' 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.45 each.**

Type 'B' 3 1/2 in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**

Type 'C' 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**

Type 'D' 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco. **Price £6.90 each.** Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

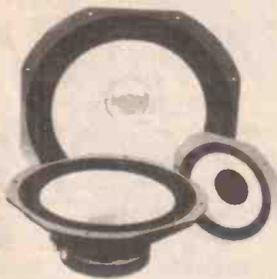Piezo Level Control/Loudspeaker Terminals. Combines two spring-loaded loudspeaker terminals, wire wound potentiometer and resistor network. All mounted on a smart brushed aluminium plate. Fits neatly through a 3" x 3" cut out on rear of speaker cabinet. **Price £2.99 + 20p postage and packing.**



JVC TURNTABLE.

JVC Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

- ★ 'S' shaped tone arm.
 - ★ Belt driven.
 - ★ Full size 12in platter.
 - ★ Precision calibrated counterbalance weight (0.3 grms.)
 - ★ Anti-skate (bias) device. Nylon thread weight.
 - ★ Damped cueing lever.
 - ★ 240V AC operation, (50Hz).
 - ★ Cut-out template supplied. Size – 12 3/4 in x 15 3/4 in (approx).
- Price £28.50 plus £2.50 postage and packing.**

Matching 3-way loudspeakers and crossover

Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover

Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring-loaded loudspeaker terminals and recessed mounting panel. **Price £19.95 per kit + £2.50 postage and packing.** Available separately, prices on request.

12" 80 watt R.M.S. loudspeaker. A superb general purpose twin cone loudspeaker. 50 oz. magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. **Attractive blue cone with aluminium centre dome.** **Price £16.49 ea + £2.50 P&P.**



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



Happy Memories

| Part type | 1 off | 50-99 | 100 up |
|-----------------------|----------------|----------------|--------|
| 4116 200ns | .95 | .85 | .75 |
| 4116 250ns | .90 | .80 | .70 |
| 2114 200ns Low power | 1.30 | 1.20 | 1.10 |
| 2114 450ns Low power | 1.25 | 1.15 | 1.05 |
| 4118 250ns | 3.50 | 3.15 | 2.95 |
| 6116 150ns CMOS | 8.75 | 8.25 | 7.95 |
| 2708 450ns | 1.95 | 1.75 | 1.65 |
| 2716 450ns 5 volt | 2.25 | 2.05 | 1.95 |
| 2716 450ns three rail | 7.40 | 7.00 | 6.75 |
| 2732 450ns Intel type | 4.50 | 4.15 | 3.95 |
| 2532 450ns Texas type | 4.95 | 4.60 | 4.40 |
| Z80A-CPU £5.25 | Z80A-P10 £4.75 | Z80A-CTC £4.75 | |

Low profile IC sockets:

Pins 8 14 16 18 20 22 24 28 40
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5 inch SSDD £17.00 5 inch DSDD £21.00

8 inch SSDD £21.00 8 inch DSDD £26.65 8 inch DSDD £31.75
74LS series TTL large stocks at low prices with DIY discounts starting at a mix of just 25 pieces.

Write or 'phone for list.

Please add 30p post & packing to orders under £15 and VAT to total

Access & Barclaycard welcome.

24hr service on (054 422) 618

Government and Educational orders welcome, £15 minimum

Trade accounts operated, 'phone or write for details

Prices are still tending to drop, 'phone for a quote before you buy

Happy Memories (ETI), Gladestry, Kington, Herefordshire HR5 3NY. Tel: (054 422) 618 or 628

Right first time.



Portable VOM

If you've never built a kit before, Heathkit have some very pleasant surprises for you. Their kits are easy to build. Simple, but detailed instructions take you through every

Rechargeable Light

stage. Everything is included. Even the solder you need is there.

Follow the steps and you'll end up with a hand-crafted, well designed piece of equipment. Much better than shop bought, mass-produced. Because you built it yourself.



Digital Clock

There's a great range of kits to start you off. From a buzzer alarm to a digital electronic clock, or a portable rechargeable fluorescent light to a portable VOM.

With all this going for you, you can count yourself very lucky you started off with Heathkit. Because all first time kit builders will get a free soldering iron and 10% discount off ten selected kits.



Buzzer Alarm

To: Heath Electronics (UK) Limited, Dept (ET11), Bristol Road, Gloucester GL2 6EE.


To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____

Address _____

You build on our experience

HEATHKIT

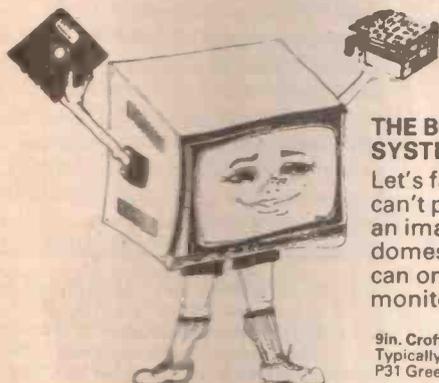

THE BODY OF ANY SYSTEM

Let's face it - you can't produce as crisp an image on a domestic TV as you can on a Crofton monitor.

| 9in. Crofton Monitors | |
|-----------------------|--------|
| Typically P4 White | £84.97 |
| P31 Green | £79.32 |

These monitor and Shugart prices are dependent upon sterling/dollar conversion rates. Phone us for up-to-date prices.

SHUGART FLOPPY DISK DRIVES

No case. No power supply.

| | |
|---------------------------|---------|
| SA 400 5 1/4 in. S.S.S.D. | £149.05 |
| SA 450 5 1/4 in. D.S.S.D. | £283.31 |
| SA 800 8 in. S.S.S.D. | £340.52 |

FLOPPY DISKS - BOXES OF TEN

| | |
|------------------------------------|--------|
| Single-sided 35/40 Track | £26.45 |
| Double-sided 35/40 Track 5 1/4 in. | £37.95 |
| Single-sided 77 Track | £41.40 |
| Double-sided 77 Track 5 1/4 in. | £47.15 |
| Single-sided 8in. | £40.25 |

IKEGAMI 12in. MONITORS

| | |
|-----------|---------|
| P4 White | £171.50 |
| P31 Green | £184.97 |

2/3in. FULLY INTERLACED C.C.T.V. CAMERAS... £149.00

ALL THE ABOVE PRICES INCLUDE V.A.T. AND CARRIAGE



ALL MAJOR CREDIT CARDS ACCEPTED: Small surcharge



CROFTON ELECTRONICS LTD.

35 Grosvenor Road, Twickenham, Middx, TW1 4AD
01-891 1923/1513

CAR ALARM

This cunning car alarm uses the battery earth strap as a sensor to detect when a courtesy light or other electrical load occurs if a thief enters the vehicle. Design and development by Phil Wait.

A significant proportion of cars are stolen at least once in their lifetime. The thieves are generally 'joyriders' who use them for a few hours and then abandon them after vandalising such items as wheels, seats, stereo/radios and so on. If you fit a good, reliable alarm you're bound to deter all but the most determined of criminals — who are usually professionals out to 'redo' the car or strip it completely for parts. There's almost nothing that will stop the latter type of thief — alarms, steering locks or any other deterrents notwithstanding.

Early car alarms were electromechanical by nature. They generally had a balanced cantilever or a pendulum with a switch contact attached. Any movement of the vehicle would close the contact and latch on a relay sounding the horn. Simple and effective — but prone to false triggering. They've all but disappeared. Others operated from a series of hood and door switches, but installation often proved a major undertaking,

Drop Detectors

Later alarms became more sophisticated — one type sensed the slight voltage-drop pulse that appears across the vehicle battery's terminals when a load is connected — such as a 'courtesy' light being operated when a door is opened. Reliability often proved a problem with these alarms as they depended on the internal resistance of the battery, which causes the voltage-drop pulse following the connection of a load (the battery terminal voltage drops momentarily and then rises again). Any variation in the terminal clamp resistance produces the same effect — giving rise to false triggering problems.

A cunning variation on this is to detect a voltage drop anywhere in the vehicle's electrical system. The battery 'earth' strap has a small, but finite, resistance. Any load on the battery will cause a current to flow through the earth strap (since the vehicle's chassis is used as the return circuit). The current causes a small voltage drop across the earth strap resistance. This is detected


and used to trip the alarm circuit that sounds the car's horn. A thief entering the vehicle will inevitably operate a 'courtesy' light or something that draws current, thus tripping the alarm. As the 'sensing' input is essentially a very low impedance input, false triggering from magnetic induction or other sources is avoided. Other voltage drop sensing schemes essentially have a medium to high input impedance, hence their susceptibility to false triggering.

Pulsed Protection


The sense and trigger circuit detects when the voltage drop across the battery earth strap rises above a predetermined amount. When triggered, this then arms the entry/exit delay. If the alarm does not remain triggered after the delay period nothing further will happen. If it does remain triggered, the delay circuit will trip the latch and start the alarm period timer. The alarm trip indicator will also light. When the alarm period timer is activated the relay driver is also activated. The relay pulser will then turn the relay on and off at one-second intervals, pulsing the horn on and off too.

The relay pulser circuit operates continuously and flashes a dashmounted LED to indicate that the alarm unit is 'armed'.

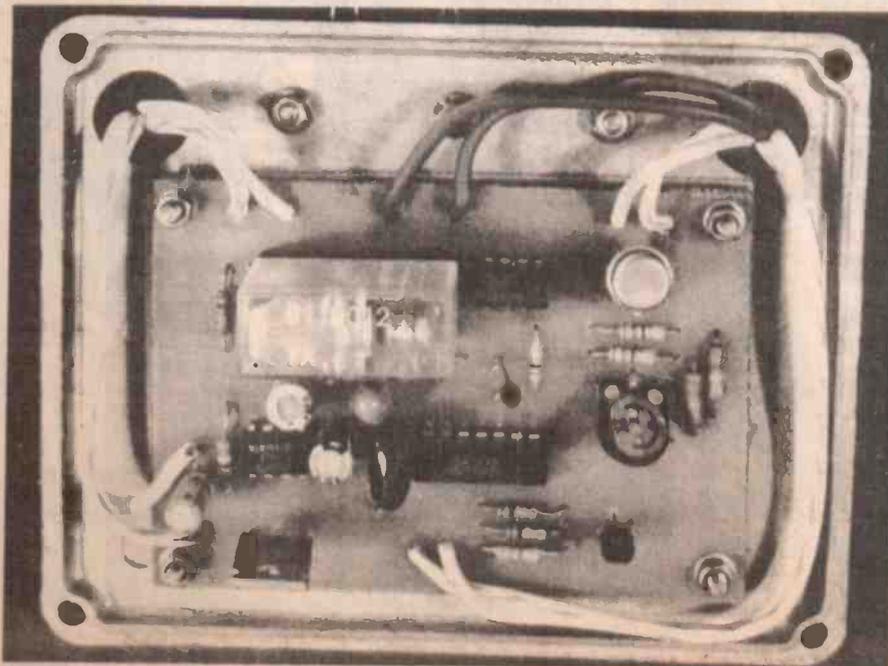After the alarm period timer completes its period, the relay driver is turned off and the horn will cease pulsing on and off. If someone attempts to steal your car, trips the alarm and then abandons the attempt, the alarm trip indicator LED will remain on, telling you that the alarm was tripped in your absence.



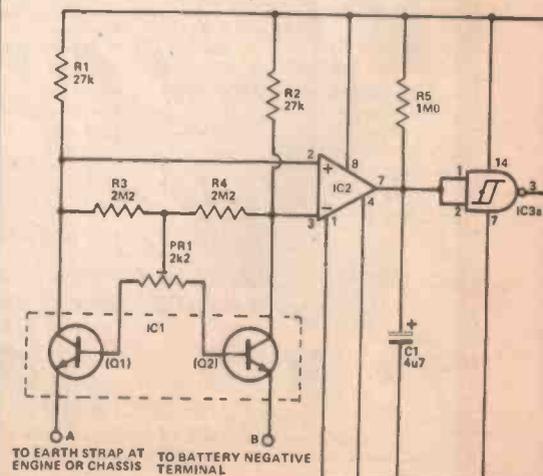(Left) The completed unit was mounted on the lid of a diecast box with a scrap of blank PCB substrate underneath as an insulating spacer. The external leads are passed through two grommetted holes to a terminal block on the outside.



TO EARTH STRAP AT ENGINE OR CHASSIS TO BATTERY NEGATIVE TERMINAL

Construction

Our prototype was constructed on a PCB; while this is not absolutely necessary — the project could be constructed on matrix board — a PCB does reduce the possibility of wiring errors which have to be sorted out when you first power up the project.

There is no particular order for assembling the components but it is usually easier to solder the resistors and capacitors in place first. Take care with the orientation of the tantalum and electrolytic capacitors. Follow with the semiconductors. Again, watch orientation of these components. The relay should be mounted last of all.

The completed board can be mounted in any convenient case — we housed ours in a diecast box measuring 120 x 40 x 95 mm. A diecast box was chosen because it can be effectively sealed against the ingress of dirt, moisture and other undesirable substances.

We mounted the PCB on the underside of the diecast box's lid and fitted a 10-way terminal block on the outside of the lid for all the external connections. Leads from the PCB to the 10-way terminal block are passed through grommetted holes.

Installation

First, mount the two LEDs on the dash in convenient positions where they can be seen from outside the vehicle. The alarm is switched on by a concealed switch which may be located under the dash or under the driver's seat. Alternatively, an externally mounted keyswitch may be used. If you install the latter, entry and exit delay may be reduced to about half a second by changing the value of C1 to 1uF.

We used a two-pole switch for SW1, one pole to switch the supply to the alarm, the other to short out the points when the alarm is switched on.

Thus, if somebody does gain entry to the car and ignores the alarm or disconnects the horn, they will not be able to start the car even if they hot-wire the ignition!

Connection to the earth strap is quite straightforward. Take a wire from

terminal A and solder it to the end of the earth strap. A wire from terminal B is soldered to the battery terminal connection. It's a good idea to keep these leads fairly short to reduce noise pick-up. Ours were about 1 m long.

The positive supply, via the alarm

HOW IT WORKS

The current in the earth strap is sensed by a pair of transistors connected in a common base configuration. These two transistors, Q1 and Q2, are encapsulated in an integrated circuit package (IC1) and are on a single chip of silicon, ensuring that they have very closely matched characteristics. The base-emitter voltages of each transistor will track within 50 uV of each other, a characteristic which is exploited here.

When no current is being drawn from the battery there will be no potential drop across the resistance of the battery earth strap (ignoring the miniscule current drawn by this alarm). Thus, the emitters of each transistor in IC1 will be at the same potential. As the base-emitter voltage of each is virtually identical the collector currents will be identical. Thus initially, the collector-emitter voltage of each transistor will be the same.

When current is drawn from the battery (when a courtesy lamp is operated, for example), a small voltage drop will appear across the battery earth strap. Thus, point A (emitter of Q1) will be raised to a higher potential than point B (emitter of Q2). That is, point A will be more positive than point B. The voltage on the collector of Q1 will thus rise (a common base amplifier is a non-inverting amplifier).

The voltage on the collector of each transistor in IC1 (Q1 and Q2) is initially set by a preset, which varies the current fed to each base. This compensates for any slight mismatch between Q1 and Q2 (the DC gain of this circuit is very high) and also acts as a 'sensitivity threshold' control by introducing an offset which must be overcome by a certain level of current through the battery earth strap before the alarm will trigger.

The voltage difference between the collectors of Q1 and Q2 is monitored by a differential input comparator (IC2). When the voltage on its non-inverting input exceeds the voltage on its inverting input the comparator's output switches high. IC2 has an open collector output requiring an external load resistor (R5). When the output of IC2 is low the timing capacitor, C1, is held discharged by IC2's output circuitry. When the alarm is tripped and the output of IC2 goes high C1 starts to charge

through R5. After a time determined by the time constant of R5 and C1 the Schmitt gate IC3a toggles over and its output, pin 3, goes low.

The Schmitt gates IC3b and IC3c form a latch circuit. On power up, the latch is automatically reset by R6 and C2 placing a momentary low on pin 8. The output of IC3c is high and the output of IC3b is low, Q3 is turned off and LED1 is not lit.

When the output of IC3a goes low the latch toggles over. The output of IC3b goes high, turning on Q3 and lighting LED1. The output of IC3c goes low at the same time. The latch remains in this state until it is reset when the power is turned off and then on again.

Before the alarm is triggered the output of IC3c is high and the input of IC3d is held high by R9. As IC3d is wired as an inverter its output is low and Q4 is turned off. When the alarm is triggered the output of IC3c goes low, and since C3 is discharged, the input of IC3d is pulled low, its output goes high and Q4 is switched on, allowing the relay to operate.

The timing capacitor, C3, slowly charges through R9 and, after a period determined by the time constant of C3/R9, IC3d switches over, turning Q4 off again and stopping the horn.

The relay RLA, and therefore the horn, is pulsed on and off about once per second during the horn timing period. IC5 is a 555 timer wired as a free-running oscillator. The frequency of oscillation is determined by the time constant of R12 and C5. As the 555 is capable of driving quite high currents it is connected directly to the relay, which is then switched by Q4. In other words, the 555 pulses the supply to the relay.

The output from the 555 is also used to pulse LED2 (mounted on the dash) as a warning to would-be car thieves and as an indication that the alarm is on.

A three-terminal regulator, IC4, drops the battery voltage down to 5 V to supply the sense and timing circuits. This protects against false triggering from battery voltage variations and also helps to remove noise from the supply.

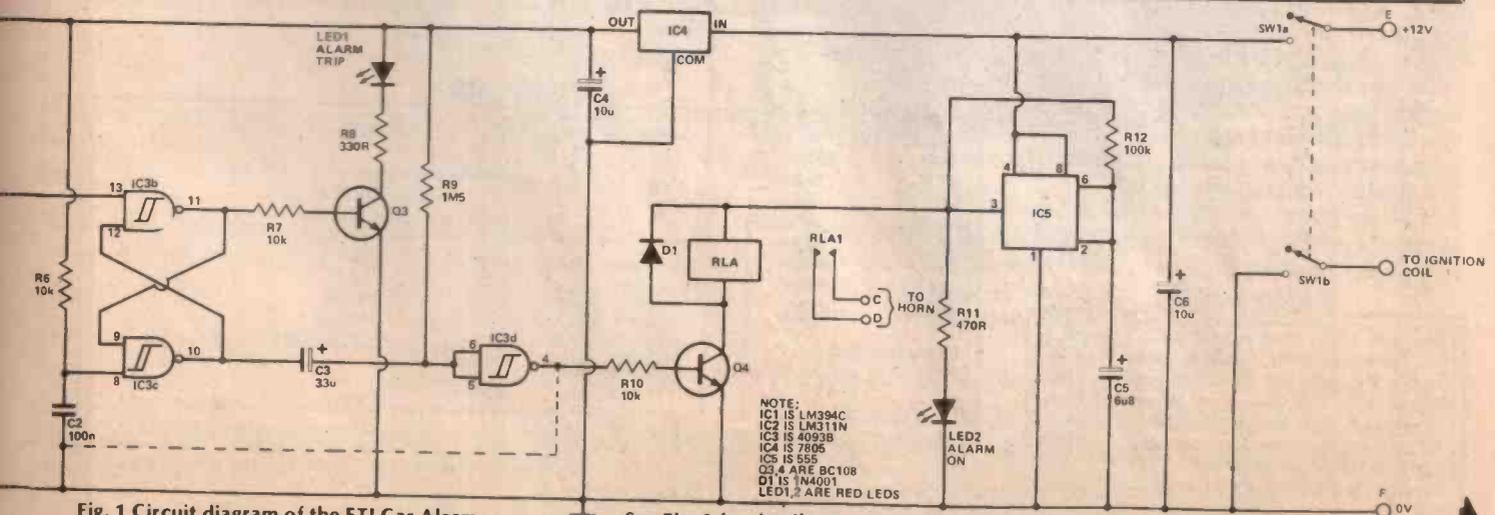


Fig. 1 Circuit diagram of the ETI Car Alarm.

See Fig. 2 for details on connecting the project to the car's electrics.

switch, should be taken through an in-line fuse holder, directly from the battery positive terminal.

The output from the alarm is a pair of switched contacts, which operate the horn by bypassing the horn switch or, on some cars, the horn relay. We have shown two common horn circuits. In the first circuit the horn switch is bypassed by the relay contacts. The second circuit is a little more complex and requires an extra pole on the alarm switch. If you want to short out the points as well you will need a three-pole double-throw switch. Make sure you break the connection from the ignition switch to the horn as shown, or when you switch the alarm on you will also switch on the ignition!

Try to make all wiring as neat as possible and try to blend it in with the car's wiring so it is not obvious to a thief what wire he has to pull out to stop the alarm.

Setting Up

When all the wiring is complete, all that remains is to set the sensitivity preset. Disable the entry and exit delay by removing C1, or alternatively connect a high impedance voltmeter across C1. With no current being drawn from the battery, adjust PR1 until the alarm just fails to trip or C1 fails to start to charge. Note the position on the preset. Turn on the interior light and the alarm should trip. If it does not, check your first adjustment; if it is correct, you probably have the leads to the earth strap and the battery negative terminal swapped.

Turn the preset until the alarm just won't trip or C1 doesn't charge when the interior light is turned on. Note this position. The correct position for PR1 is midway between these limits, for reliable operation.

Next check that the alarm doesn't trip on the car radio or the electric clock. Some mechanical clocks are rewound by a motor every few hours, or even days, and these are often a cause of false triggering. If false triggering occurs from the radio or the clock, reduce the sensitivity. In some extreme cases it may be necessary to use a higher wattage interior light, though we found operation to be extremely reliable with a 5 W light, and there was sensitivity to spare!

BUYLINES

The only tricky components are IC1 and IC2 — these are both available from Technomatic. The relay is type RL111 from Watford Electronics. The case can be any diecast aluminium box about 120 mm x 95 mm x 40 mm; suitable ones are available from West Hyde Developments (order as EDD40) and Watford (DCB8). The PCB is available from our PCB Service (see page 76).

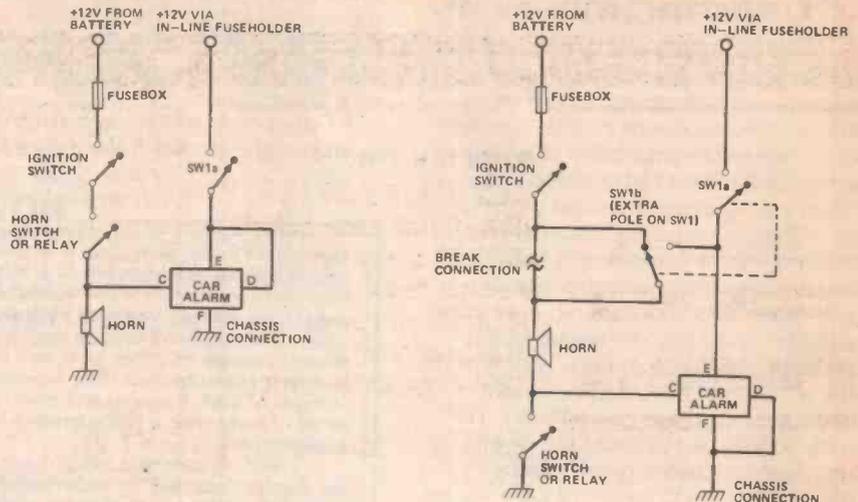


Fig. 2 Common horn circuits and how to connect the alarm to them. The circuit on the left will have only one wire from the horn. The one on the right is found in cars such as the Leyland Mini LS and is rather more complex.

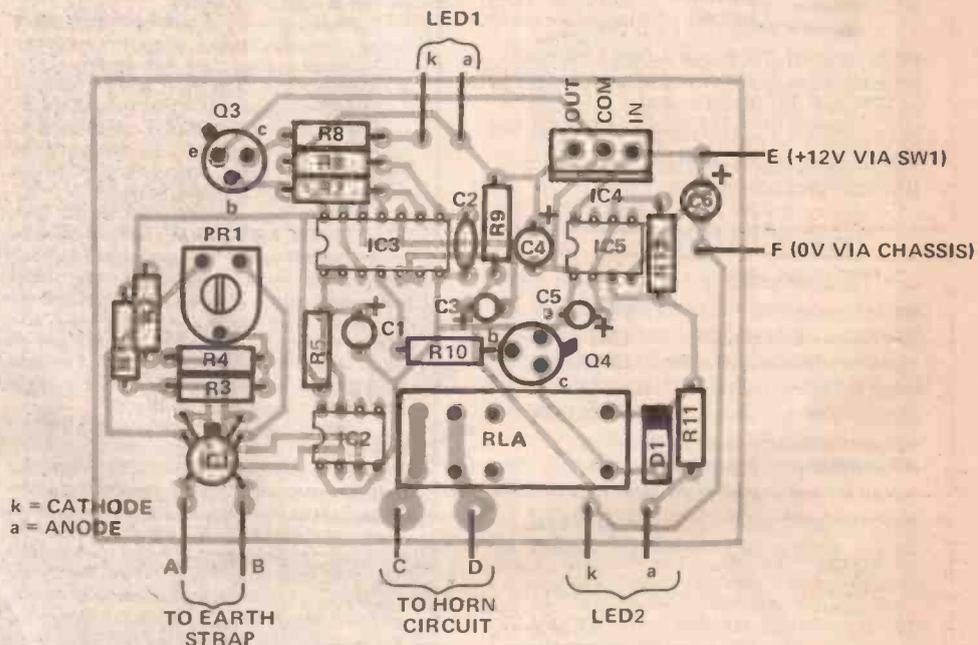


Fig. 3 Component overlay for the Car Alarm. There are a lot of polarised capacitors so make sure you get them all the right way round.

ETI

PARTS LIST

| | | | |
|---------------------------|---------------------------------|---|------------------------------|
| Resistors (all 1/4 W, 5%) | C5 | 6u8 16 V tantalum | |
| R1,2 | 27k | | |
| R3,4 | 2M2 | Semiconductors | |
| R5 | 1M0 | IC1 (=Q1,2) | LM394C |
| R6,7,10 | 10k | IC2 | LM311N |
| R8 | 330R | IC3 | 4093B |
| R9 | 1M5 | IC4 | 7805 |
| R11 | 470R | IC5 | 555 |
| R12 | 100k | Q3,4 | BC108 |
| Potentiometer | | D1 | 1N4001 |
| PR1 | 2k2 miniature horizontal preset | LED1,2 | 0.2" red LED |
| Capacitors | | Miscellaneous | |
| C1 | 4u7 16 V tantalum | RLA | 12 V DPCO PCB-mounting relay |
| C2 | 100n polyester | SW1 | DPST or 3PST toggle switch |
| C3 | 33u 16 V tantalum | PCB (see Buylines); case (see Buylines); 10-way terminal strip. | |
| C4,6 | 10u 16 V PCB electrolytic | | |

CHROMASONIC electronics

48 JUNCTION ROAD, ARCHWAY LONDON N19 5RD — 100 yards from Archway Station & 9 Bus Routes
 TELEPHONE: 01-263 9493/01-263 9495

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPUTERS

PET



- 4016 16K RAM
- 4032 32K RAM
- 4040 Dual Drive Disk
- 4022 80 column tractor feed.
- 3023 80 column friction feed.
- C2N Cassette Unit.

For the business man we stock the 8000 range inc 8032 and 8050 with daisy wheel printers coming soon.

PHONE FOR MOST COMPETITIVE PRICES WORD PROCESSING AND 32K SYSTEMS PHONE FOR DETAILS

UK101

- UK101 Kit inc 8K memory £125
- Ready Built inc 8K memory £175
- Complete in case £199
- 4K Expansion 8x2114 £14
- Memory Expansion Kit 8K £79.95
- Memory Expansion Kit 16K £106.95
- Parallel Printer Interface £29.95
- Sound generator plus PIO kit £29.95
- Cases £24.50
- NEW** Chromasonics Sound Kit £24.95
- Colour Kit £84.95

Inc. Demo Tape & Full Documentation Send for details

DOWN IN PRICE

VIC 20

VIDEO GENIE



£279 EG3003
 Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features. Simply plugs into monitor or UHF TV. With V.U. Meter.

- PARALLEL PRINTER INTERFACE INC CABLE £33.00
- CHROMASONICS PROGRAMMABLE SOUND KIT £24.95
- SOUND KIT (FITTING EXTRA) £7.00
- LOWER CASE KIT (FITTING EXTRA) £27.50
- COLOUR KIT (FITTING EXTRA) £34.95
- EXPANSION BOX WITH/WITHOUT RS232 £215/£185
- 16K/32K RAM BOARD £94/£129
- NEW GENIE II NOW AVAILABLE** £299

VIC 20

Colours

24 total. 8 for characters, 8 for border, 16 for screen mixed as you wish. Basic colours on program keys are black, white, red, blue, light blue, green, yellow and purple.

Sound

3 Tone Generator for music, "White Noise" Generator for language and sound effects. Each Generator gives 3 octaves. Reproduction is through TV speaker.

Character/Line Display

22 Characters by 23 lines, 64 ASCII characters, pet-type graphic character set.

Keyboard

DIN typewriter keyboard with 8 programmable function possibilities via 4 special function keys. Colours are directly addressable from the keyboard.

Peripherals/Accessories

VIC Datas cassette with special interface to guarantee high reliability read/write quality (PET/CBM compatible)

Price only £165.00.
Cassette recorder £34.75
with 6 Free sample programmes.



APPLE

APPLE II PLUS

- 48K Machines £595
- Disk Drive with Controller £349
- Disk Drive without Controller £299
- Graphic Tablet £425
- Colour Card £69

Accessory cards, Software
 All available — Phone for Details



PRINTERS



INTERFACES AND CABLES FOR APPLE II, PET, TRS80, RS232, UK101, SHARP SUPERBOARD ALL AVAILABLE.

EPSON MX80 £359

Dot-matrix printer with Pet graphics interface. Centronics parallel and serial. Pet and Apple compatible. True bidirectional, 80 cps.

EPSON MX80 FT/1 £399

Dual single sheet friction and tractor feed, 9 wire head, true descenders.

EPSON-MX FT/2 £449

An FT/1 with high resolution graphics.

EPSON MX100 £575

Friction and Tractor Feed, High Resolution Graphics, Wide carriage 15 1/2".

SEIKOSHA GP80A £199

Dot matrix 5 x 7, 80 columns, 30 cps graphics, double width characters.

JUST PHONE FOR FURTHER DETAILS

MONITORS

- Green Monitor £99.00
- MONI 9" (illust) B&W £82.00
- Hitachi professional monitors
- 9" Black & White £99.95
- 12" Black & White £149.00



TANTEL

PRESTEL BY TANTEL
COMMUNICATIONS AT YOUR FINGERTIPS
FOR BUSINESS & HOME. UP TO DATE INFO


180,000 pages of information on Travel, News, Investment, Holidays, Hotels Etc., Etc.

£170


TANTEL IS POST OFFICE APPROVED. SEND FOR DETAILS.
 DEMONSTRATION AVAILABLE AT OUR SHOWROOM.



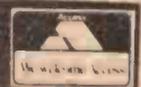Please add VAT 15% to all prices. Postage on computers, monitors, printers and cassette decks charged at cost, all other items P&P 30p. Place your order using your Access or Barclaycard (Min. tel. order £5). Export enquiries welcome. Official orders welcome.



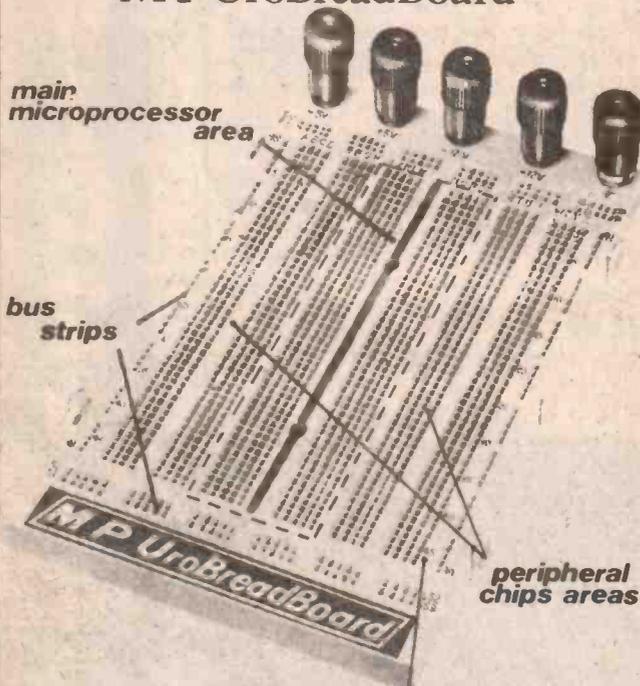If you're into
MICROPROCESSORS
then they should be into an
MP UroBreadBoard



- * MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- * Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- * Power Bus Strips on all sides
- * 5 incoming turret Power Terminals
- * Component Support Bracket included
- * Over 1400 contact points
- * Alpha-Numeric column and row indexing
- * Eurocard size (160mm x 100mm)
- * Slots onto all BIMBOARDS
- * Non-Slip rubber backing
- * Ideal for schools and colleges
- * Long life, <10m.ohms, nickel silver contacts

The PROFESSIONALS breadboard
that BEGINNERS can start on

BOSS INDUSTRIAL MOULDINGS LTD

2 Herne Hill Rd, London SE24 0AU, England
Telephone 01-737 2383 Telex 919693
Cables & Telegrams: LITZEN LONDON SE24

Please send me MPUroBreadBoard(s) at £18.00

This price includes VAT & PP, is applicable from March 1981 but please add 15% for Overseas Orders, make cheques/P.O. payable to BOSS Industrial Mouldings Ltd and allow 10 days for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £.....

Name

Company

Address

Telephone Number

ET11/11/81



TARGET ELECTRONICS

16 Cherry Lane, Bristol BS1 3NG
Telephone: 0272 421196

Panel Meters



Dims:- 110 x 82 x 35mm. Require 58mm dia. cut out
FINE QUALITY -

| | |
|------|------------|
| 043 | 0 - 30 uA |
| 045 | 0 - 50 uA |
| 0410 | 0 - 100 uA |
| 0420 | 0 - 200 uA |
| 0450 | 0 - 500 uA |

£4.75
40p p&p + VAT
10 Plus 10% Discount



Dims:- 60 x 47 x 33mm. Require 38mm dia. cut out
FINE QUALITY -

| | |
|-----|------------------|
| T21 | 0 - 50 uA |
| T22 | 0 - 100 uA |
| T23 | 0 - 500 uA |
| T24 | 0 - 1 mA |
| T25 | 0 - 5 mA |
| T26 | 0 - 10 mA |
| T27 | 0 - 50 mA |
| T28 | 0 - 100 mA |
| T29 | 0 - 500 mA |
| T30 | 0 - 1 AMP |
| T31 | 0 - 2 AMP |
| T32 | 0 - 25 Volts |
| T33 | 0 - 50v AC |
| T34 | 0 - 300v AC |
| T35 | "uV" |
| T36 | "mV" |
| T40 | 50 - 0 - 50 uA |
| T41 | 100 - 0 - 100 uA |
| T42 | 500 - 0 - 500 uA |
| T43 | 0 - 30v DC |

£3.75
40p p&p + VAT
10 plus 10% Discount

Illuminating kit for meters

15p + 15% VAT



Dims:- 52mm(H) x 58mm(W) x 43mm(D)
44mm dia. cut out.

ref. cat. I.F.S.D. Int. Resistance

| DC MICROMETERS | | |
|------------------|------|----------------------------|
| XME18 | MU45 | 0 - 50 uA 3500 ohms |
| XME19 | MU45 | 0 - 100 uA 3500 ohms |
| XME20 | MU45 | 0 - 500 uA 430 ohms |
| DC GALVANOMETERS | | |
| XME21 | MU45 | 50 - 0 - 50 uA 3500 ohms |
| XME22 | MU45 | 100 - 0 - 100 uA 1450 ohms |
| DC MILLIAMMETERS | | |
| XME23 | MU45 | 0 - 1 ma 200 ohms |
| XME24 | MU45 | 0 - 5 ma 8 ohms |
| XME25 | MU45 | 0 - 10 ma 3 ohms |
| XME26 | MU45 | 0 - 50 ma 1.5 ohms |
| XME27 | MU45 | 0 - 100 ma 0.8 ohms |
| XME28 | MU45 | 0 - 500 ma 0.2 ohms |
| DC AMMETERS | | |
| XME29 | MU45 | 0 - 1 amp 0.1 ohms |
| XME30 | MU45 | 0 - 2 amp 0.8 ohms |
| XME31 | MU45 | 0 - 5 amp 0.02 ohms |
| DC VOLTMETERS | | |
| XME32 | MU45 | 0 - 25 volts 1000 ohms |
| XME33 | MU45 | 0 - 50 volts 1000 ohms |
| VU METER | | |
| XME34 | MU45 | 1.228 VAC (OVU) |

£3.00
40p p&p + VAT
10 Plus 10% Discount

XME35



£1.05
35p p&p + 15% VAT
10 plus 10% discount

VU meter
Resistance:- 1500 ohms
Sensitivity:- 100 uA
Window dims:- 31 x 23mm
Overall dims:- 40 x 41 x 20mm

XME36



55p
35p p&p + 15% VAT
10 plus 10% Discount

Level meter. Scaled signal and power.
Window dims:- 17 x 11mm
Overall dims:- 18 x 18 x 15mm

XMT1 KRT5001 50,000 opv



£14.00
£1.25 p&p + 15% VAT

RANGE DOUBLER
AC volts:- 0 - 5 - 10 - 25 - 50 - 125
-250 - 500 - 1000
DC volts:- 0 - 0.125 - 0.250 - 1.25 -
2.5 - 5 - 10 - 25 - 50 -
125 - 250 - 500 - 1000
DC current:- 0 - 2.5 - 5 - 25 - 50 - 250
500 mA
0 - 5 - 10 amp
Resistance:- 0 - 2 K - 20 K - 200 K ohms
0 - 2 meg - 20 meg ohms
Decibels:- -20 db to + 62 db
Dims:- 170 x 124 x 50mm

Official Orders Welcomed, GVT/Educational Dept etc



We can offer you Barclaycard or
Access facility, just telephone your card number to
place an order.





NEW BAIA MUSICAL ELECTRONIC KITS



Send for your FREE CATALOG now!

We have products ranging from effect units for guitars to computer controlled Polyphonic synthesizers. Whether your interest is sound synthesizers, music creation or homerecording, we have the products for you. Find out how easy and at what low cost you can get the products that dominate the USA market. Whether you live in the U.K. or elsewhere in Europe we will send you our 4 colour catalog at no cost.

() Please rush me a free catalog

Name _____
 Address _____
 City _____ Country _____

Send to **BAIA EUROPE** Dr. Kristinas väg 31, 193 00 Sigtuna, SWEDEN
 Telephone (46) 76051475

ONE OF THE MOST USEFUL PIECES OF TEST EQUIPMENT

AUDIO SIGNAL GENERATOR

10Hz - 100KHz .02% distortion (1KHz)

MODEL A0113M



1v RMS variable output

Available as a kit of parts or ready made

- A0113 BK (plastic case) Kit £26.90, Made £33.90 (A0113PA)
- A0113 UK (MAINS) (plastic case) Kit £32.20, Made £41.40 (A0113PUA)
- A0113 M (metal case) Assembled £35.65
- A0147 PB (push-button version) Kit £26.90, Made £33.90 (A0147PA)
- A0149 BK Superior Model (not illustrated) £35.50, Made £41.50 (A0149BA)

TELERADIO ELECTRONICS (Closed Thursdays)
 325 Fore Street, Edmonton, London, N9 0PE - 01-807 3719

Other instruments, RF Sig. Gen., Freq. Meters, THD Analyser, S.W.R. Meters, S.A.E. for full lists. Function Generators.



12 TIM ONLY £65



15 WDM ONLY £80

THESE SUPERB PROFESSIONAL DISPLAYS OFFER THE MICRO ENTHUSIAST A NEVER-TO-BE-REPEATED CHANCE TO HAVE A VDU WITH A SPECIFICATION UNRIVALLED BY DISPLAYS AT THREE TIMES THE PRICE. MADE BY AN ENGLISH MANUFACTURER TO AN EXACTING SPEC. BUILT TO LAST THE KEYBOARD ALONE IS WORTH OUR PRICE.

- * GREEN SCREEN FOR REDUCED EYESTRAIN
- * 80 CHARACTERS PER LINE, 26 LINES
- * STANDARD V24 INTERFACE LEVELS
- * PRINTER DRIVE PORT
- * ASCII SUBSET 600 1200 2400 BAUD
- * ON SCREEN EDITING AND FULL CURSOR CONTROL
- * MODEM CONTROL, CAN BE MULTIPLEXED

GRAPHICS

- * CALCOMP 565 INCREMENTAL X-Y PLOTTERS
- * 10 THOU STEPS
- * EASY MICRO-COMP INTERFACING
- * SINGLE SHEET OR ROLL PAPER
- * PRECISION INSTRUMENT ONLY



SECONDHAND EQUIPMENT SUPPLIED IN WORKING ORDER BUT UNGUARANTEED

HARD COPY

- * ASCII CODED
- * SIMPLE INTERFACE
- * INDUSTRY STANDARDS
- * PLAIN PAPER
- * 110 BAUD
- * FLOOR STAND £7.50
- * SET OF 3 MANUALS FOR ONLY £7.50

- RO 390 PRINTER ONLY £65
- KSR 33 WITH KEYBOARD £95
- ASR 33 £160
- AS ABOVE PLUS PAPER TAPE PUNCH AND READER

MAWSON ASSOCIATES
 124 LENNARD ROAD
 BECKENHAM, KENT BR3 1QP
 01-778 3600

WE ALSO BUY SURPLUS COMPUTERS AND COMPUTER PERIPHERALS PLEASE RING FOR DETAILS

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D I Y world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the normal.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems, function light, and security changeover switch. Will work all rev counters.



Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case, Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. ET1/11
 2 Bath Street, Walsall WS1 3DE
 Phone: (0922) 614791

Name _____
 Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D

I enclose cheque PO's for

X5 KIT £16.95

ACCESS OR BARCLAY CARD No.

£

Cheque No.

Send SAE if brochure only required.

ELECTRONIC GAMES

COLOUR CARTRIDGE T.V. GAME



SEMI-PROGRAMMABLE T.V. GAME
• 4 Cartridges • Mains Adaptor
Normal Price £73
NOW REDUCED TO: £39.50 inc. VAT

DATABASE T.V. GAME



FULLY PROGRAMMABLE CARTRIDGE T.V. GAME
14 Cartridges available
Normal Price £87.86
NOW REDUCED TO: £59 inc. VAT

ATARI T.V. GAME



The most popular T.V. Game on the market with a range of over 40 cartridges including SPACE INVADERS with over 112 games on one cartridge.
£95.45 inc. VAT

SPACE INVADERS



Hand-held Invaders Games available £19.95
• Invaders Cartridges available to fit ATARI RADOFIN ACETRONIC PHILIPS G7000
• Cartridges also available for MATTEL TELENG/ROVTRON/DATABASE/INTERTON

CHESS COMPUTERS



MANY UNITS ARE COVERED BY THE EXCLUSIVE SILICA SHOP 2 YEAR GUARANTEE

We carry a range of over 15 different Chess computers:
Electronic Chess £29.95
Chess Traveller £39.95
Chess Challenger 7 £79.00
Sensory 8 £119.00
Sensory Voice £259.00
SPECIAL OFFERS:
VOICE CHESS CHALLENGER
Normal Price £245 NOW £135.00
SARGON 2.5/BORIS 2.5
Normal Price £273.70 NOW £199.95
All prices include V.A.T.

TELETEXT



ADD-ON ADAPTOR £199


THE RADOFIN TELETEXT ADD-ON ADAPTOR

Plug the adaptor into the aerial socket of your colour TV, and receive the CEEFAX and ORACLE television information services.

THIS NEW MODEL INCORPORATES:

- Double height character facility
- True PAL Colour
- Meets latest BBC & IBA broadcast specifications
- Push button channel change
- Unnecessary to remove the unit to watch normal TV programmes
- Gold plated circuit board for reliability
- New SUPERIMPOSE News Flash facility

SPEAK & SPELL

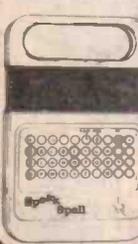

Normal Price £49.95
NOW REDUCED TO: £39.50 inc. VAT

Teach your child to spell properly with this unique learning aid. Fully automatic features and scoring. Additional word modules available to extend the range of words

ADDING MACHINE OLYMPIA HHP 1010



Normal Price £57.21
NOW REDUCED TO: £34 inc. VAT

Uses ordinary paper! No need to buy expensive thermal paper!
Fast add listing PRINTER CALCULATOR 2 lines per second, 10 digit capacity
Uses normal adding machine rolls. Battery or mains operated.
Size 9 1/2" x 4 1/2" x 2 1/4"
(Mains adaptor extra)


24 TUNE ELECTRONIC DOOR BELL



Normal Price £19.70
NOW REDUCED TO: £12.70 inc. VAT

Plays 24 different tunes with separate speed control and volume control. Select the most appropriate tune for your visitor, with appropriate tunes for different times of the year!

MATTEL T.V. GAME

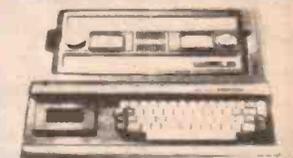

The most advanced TV game in the world 20 cartridges available. Axi on KEYBOARD coming soon to convert the MATTEL to a home computer with 16K RAM fully expandable and programmable in Microsoft Basic. Other accessories will be available later in the year.
£199.95 inc. VAT

HAND HELD GAMES EARTH INVADERS



These invaders are a breed of creature hitherto unknown to man. They cannot be killed by traditional methods. They must be buried. The battle is conducted in a maze where squads of aliens chase home troops. The only way of eliminating them is by digging holes and burying them.
£23.95 inc. VAT

THE OLYMPIA — POST OFFICE APPROVED TELEPHONE ANSWERING MACHINE WITH REMOTE CALL-IN BLEEPER

This telephone answering machine is manufactured by Olympia Business Machines, one of the largest Office Equipment manufacturers in the U.K. It is fully POST OFFICE APPROVED and will answer and record messages for 24 hours a day. With your remote call-in bleeper you can receive these messages by telephone wherever you are in the world. The remote call-in bleeper activates the Answer/Record Unit, which will at your command repeat messages, keep or erase them and is activated from anywhere in the world, or on your return to your home or office. The machine can also be used for message referral, if you have an urgent appointment, but are expecting an important call simply record the 'phone number' and location where you can be reached. With optional extra




bleepers (£13 each) this facility can be extended to colleagues and members of the family. Using a C90 standard cassette you can record as many as 45 messages. The announcement can be up to 16 seconds long and the incoming message up to 30 seconds long. The machine is easy to install and comes with full instructions. It is easily wired to your junction box with the spade connectors provided or alternatively a jack plug can be provided to plug into a jack socket. Most important, of course, is the fact that it is fully POST OFFICE APPROVED. The price of £135 (inc. VAT) includes the machine, an extra-light remote call-in Bleeper, the microphone message tape, A.C. mains adaptor. The unit is 9 1/2" x 6" x 2 1/4" and is fully guaranteed for 12 months. The telephone can be placed directly on the unit — no additional desk space is required.
£135 inc. VAT

HAND HELD GAMES GALAXY 1000



The 2nd generation Galaxy Invader. The invaders have re-grouped and have a seemingly endless supply of spacecraft whilst the player's arsenal is limited to just 250 missiles to be launched from 3 missile stations. You have to prevent the invaders landing or from destroying your home defences.
£19.95 inc. VAT

PRESTEL VIEWDATA

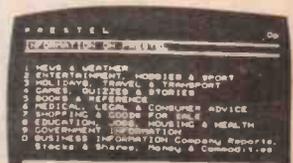

The ACE TELCOM VDX1000 Prestel Viewdata adaptor simply plugs into the aerial socket of your television and enables you to receive the Prestel Viewdata service in colour or black & white.

Features

- Simplified controls for quick, easy operation
- Special graphics feature for high resolution
- State-of-the-art microprocessor controller
- Standard remote telephone keypad with Prestel keys
- Auto dialler incorporated for easy Prestel acquisition
- True PAL colour encoder using reliable IC chroma filter and delay line incorporated for minimum picture interference maximum fidelity
- Includes convenient TV — Prestel switchbox
- Easily connected to standard home or office telephone lines
- Fully Post Office approved

SPECIAL PRICE £228.85 inc. VAT

FOR FREE BROCHURES — TEL: 01-301 1111




For free illustrated brochure and reviews on our range of electronic games, please telephone 01 301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS-BARCLAYCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48hr delivery service available.
CALLERS WELCOME. Demonstrations daily at our Sidcup shop, open from 9am to 6pm Monday-Saturday (Early Closing Thursday 1pm, Later Closing Friday 5pm).
2 YEAR GUARANTEE. All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 Year Guarantee.
AFTER SALES SERVICE. Available on all machines, out of guarantee.
COMPETITIVE PRICES. We are never knowingly under-sold.
HELPFUL ADVICE. Available on the suitability of each machine.
CREDIT FACILITIES. Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
PART EXCHANGE SCHEME. Available on second hand machines.
CREDIT CARDS WELCOME. Access, BarclayCard, Diners Club, American Express.

SILICA SHOP LIMITED ET/11/81


1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX
Telephone: 01-301 1111 or 01-309 1111




PCB FOIL PATTERNS

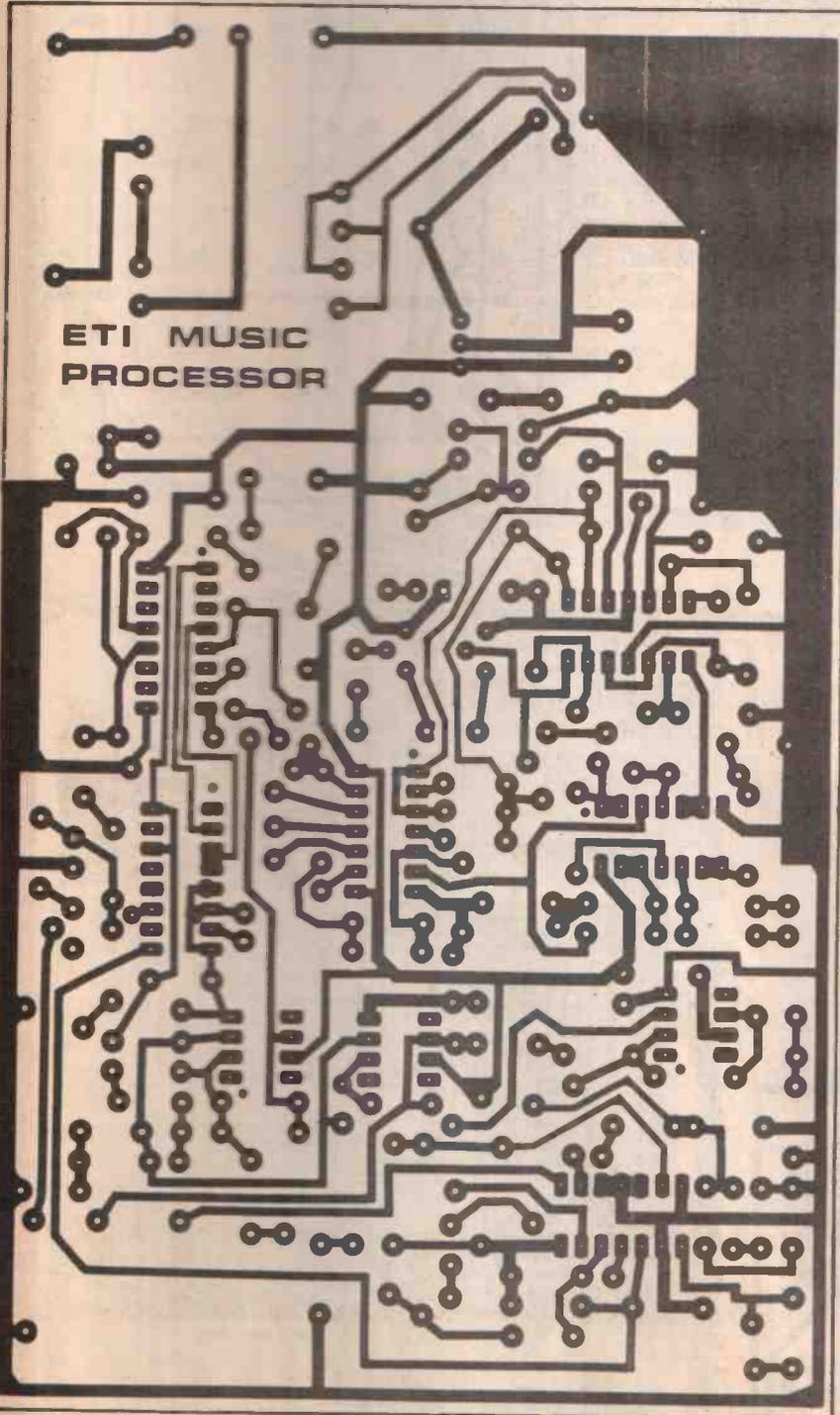


foil pattern for the Music Processor.

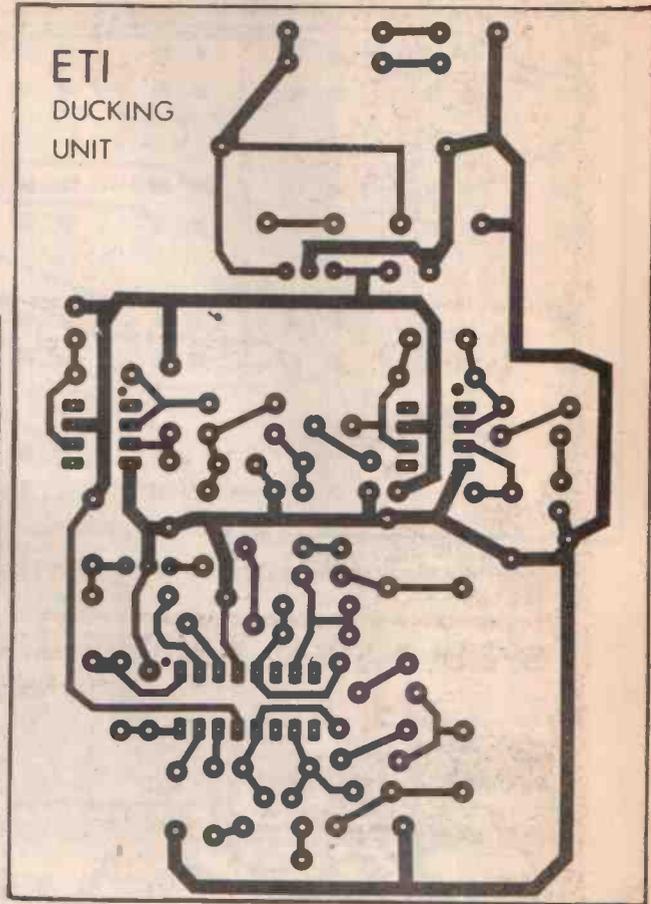

The Voice-over PCB.

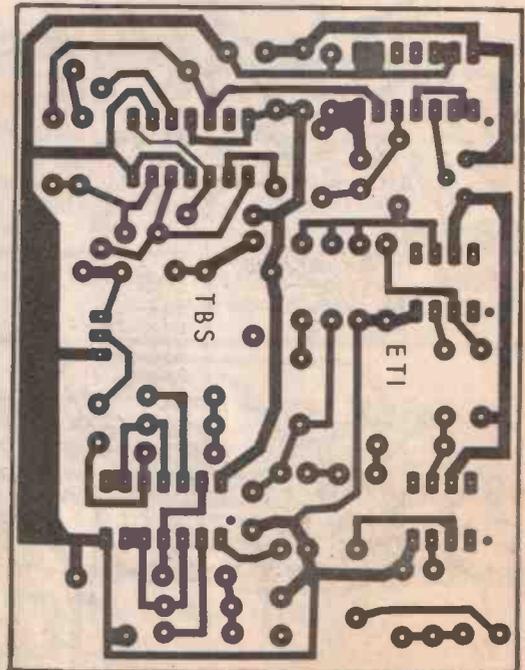


The board for the Phone Bell Shifter.

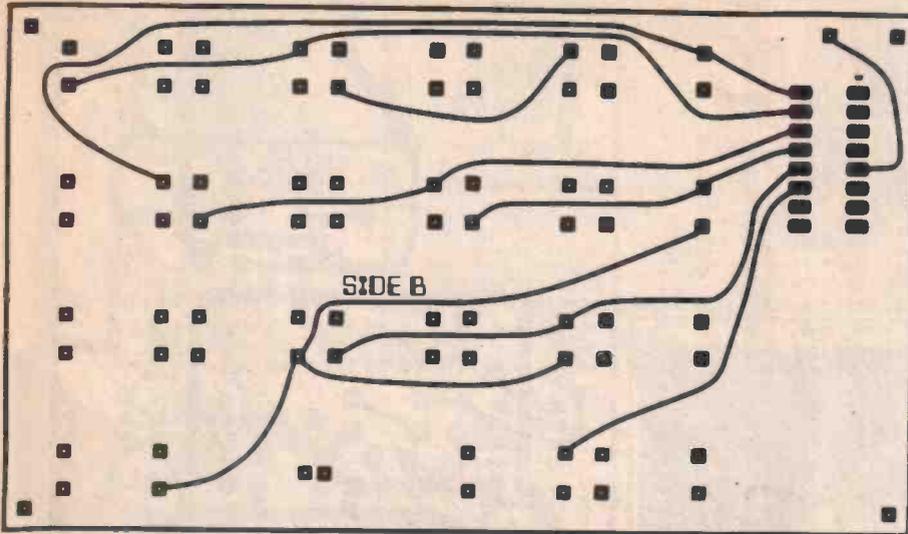


Above: The underside of the keypad PCB for last month's FM Mains Remote Control system.


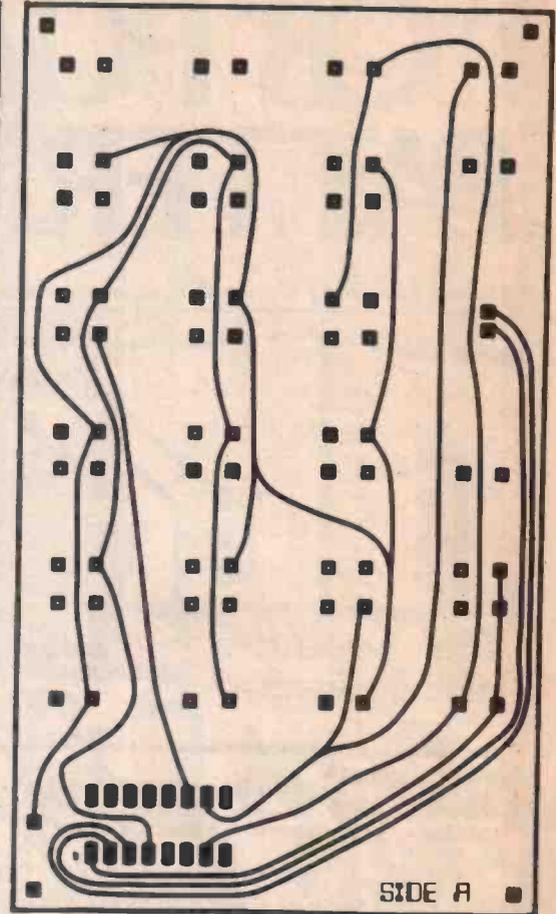
Right: The component side foil pattern of the double-sided keypad.



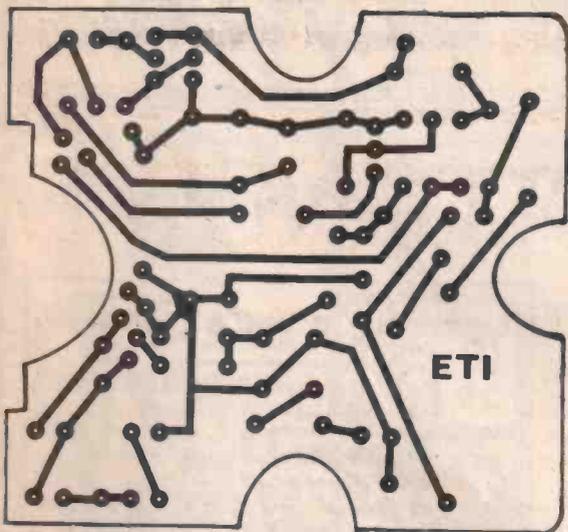Below: FM Mains Remote Control receiver board.



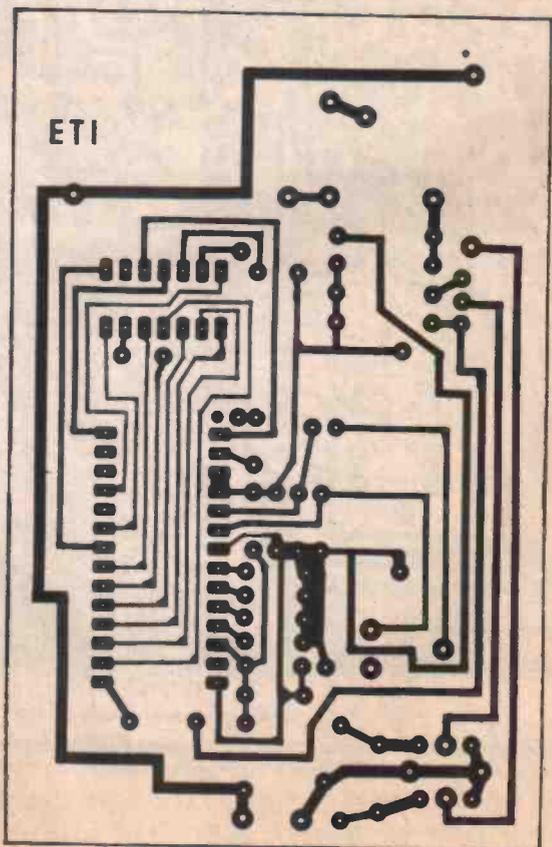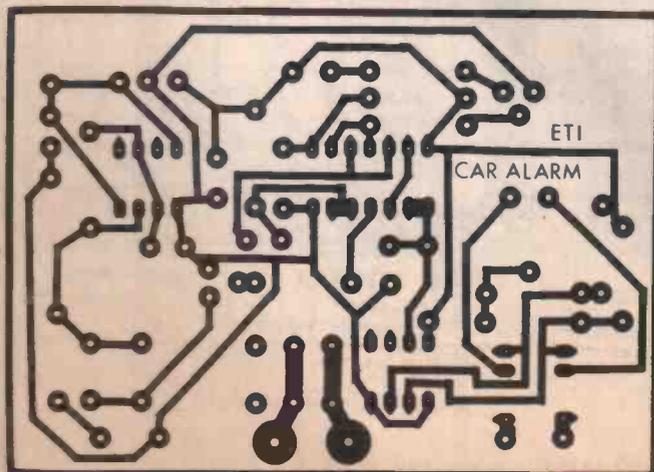Below: Foil pattern of the ETI Car Alarm.



The Remote Control Transmitter PCB.

LINEAR ICs

THE LOWEST PRICES FOR PRIME CMOS/TTL/74C IN THE UK

TRANSISTORS

| | | | | | | | | | | | | | |
|-----------------|-----------------|---------------|-------------|-----------|------------|-----------|------------|------------|-----------|------------|------------|----------|-----------|
| TBA1205 1.00 | SL1610P 1.60 | HA11223 2.15 | 4000 series | 4060 0.95 | 4566 1.59 | 7448 0.56 | 74125 0.40 | 74190 0.55 | 7405 J14 | 7496 1.20 | 74190 0.60 | 74C CMOS | BF194 18p |
| L200 1.95 | SL1611P 1.60 | HA11225 1.45 | 4000 0.13 | 4061 1.15 | 4569 2.18 | 7450 0.14 | 74126 0.40 | 74191 0.55 | 7408 0.14 | 74107 0.25 | 74191 0.60 | | BF195 99p |
| U237B 1.28 | SL1612P 1.60 | HA12002 1.45 | 4001 0.13 | 4066 0.38 | 4572 0.30 | 7451 0.14 | 74132 0.50 | 74192 0.55 | 7409 0.14 | 74109 0.25 | 74192 0.68 | | BF224 22p |
| U247B 1.28 | SL1613P 1.89 | HA12017 0.80 | 4002 0.14 | 4067 4.30 | 4569 1.95 | 7453 0.14 | 74136 0.65 | 74193 0.55 | 7410 0.13 | 74112 0.25 | 74193 0.68 | | BF241 18p |
| U257B 1.28 | SL1620P 2.17 | HA12402 1.95 | 4007 0.19 | 4068 0.18 | 4572 0.30 | 7454 0.14 | 74136 0.65 | 74194 0.55 | 7411 0.16 | 74113 0.25 | 74194 0.42 | | BF274 18p |
| U267B 1.28 | SL1621P 2.44 | HA12411 1.20 | 4008 0.70 | 4069 0.18 | 4582 0.99 | 7460 0.14 | 74141 0.85 | 74195 0.55 | 7412 0.15 | 74114 0.25 | 74195 0.42 | | BF440 21p |
| LM1301M 0.67 | SL1623P 2.44 | HA12412 1.55 | 4009 0.30 | 4070 0.25 | 4584 0.49 | 7472 0.27 | 74142 1.85 | 74196 0.55 | 7413 0.28 | 74122 0.40 | 74196 0.66 | | BF441 21p |
| LM1301N 0.30 | SL1624C 3.28 | LF13741 0.33 | 4010 0.30 | 4071 0.22 | 4585 1.00 | 7472 0.27 | 74143 2.50 | 74197 0.55 | 7414 0.49 | 74123 0.55 | 74197 0.65 | | BF442 21p |
| LM1308TC 0.65 | SL1625P 2.17 | SN76660N 0.80 | 4011 0.24 | 4072 0.22 | 4702 4.50 | 7473 0.28 | 74144 2.50 | 74198 0.55 | 7415 0.16 | 74124 1.80 | 74198 0.65 | | BF443 21p |
| LM1324 0.54 | SL1626P 2.44 | | 4011 0.15 | 4073 0.22 | 4703 4.48 | 7474 0.28 | 74146 0.75 | 74199 1.00 | 7420 0.13 | 74125 0.29 | 74202 0.25 | | BF444 21p |
| LM1339N 0.66 | SL1630P 1.62 | | 4012 0.20 | 4078 0.18 | 4704 4.24 | 7475 0.28 | 74147 1.50 | 74201 1.00 | 7421 0.15 | 74126 0.29 | 74221 0.60 | | BF445 21p |
| LM1348N 0.86 | SL1640P 1.85 | | 4013 0.35 | 4076 0.60 | 4705 4.24 | 7476 0.30 | 74148 1.09 | 74202 1.51 | 7422 0.14 | 74127 0.45 | 74240 0.99 | | BF446 21p |
| LF351N 0.49 | SL1641P 1.89 | | 4015 0.70 | 4077 0.23 | 4706 4.50 | 7480 0.26 | 74150 0.79 | 74246 1.50 | 7422 0.15 | 74128 0.29 | 74241 0.99 | | BF447 21p |
| LF353N 0.76 | TD42002 1.25 | | 4016 0.30 | 4078 0.25 | 4720 4.00 | 7481 0.20 | 74151 0.85 | 74248 1.89 | 7423 0.16 | 74133 0.40 | 74241 1.03 | | BF448 21p |
| LM1374N 0.375 | ULN2242A 3.95 | | 4017 0.55 | 4082 0.25 | 4723 0.85 | 7482 0.25 | 74153 0.85 | 74249 1.89 | 7424 0.16 | 74136 0.28 | 74242 1.65 | | BF449 21p |
| LM1380N-14 1.00 | ULN2283B 1.00 | | 4019 0.38 | 4093 0.48 | 4724 0.95 | 7483 0.60 | 74154 0.55 | 74249 1.89 | 7426 0.35 | 74138 0.40 | 74243 1.65 | | BF450 90p |
| LM1380N 1.00 | CA3090C 14.00 | | 4020 0.88 | 4099 0.99 | 4725 2.24 | 7485 0.75 | 74155 0.55 | 74251 1.08 | 7430 0.13 | 74139 0.40 | 74244 0.83 | | BF451 90p |
| NE565N 1.81 | CA3098E 1.80 | | 4021 0.75 | 4175 1.18 | 40014 0.54 | 7486 0.24 | 74156 0.55 | 74252 0.66 | 7432 0.14 | 74145 1.20 | 74245 1.50 | | BF452 90p |
| NE560N 3.50 | CA3140C 3.35 | | 4022 0.88 | 4502 0.90 | 40085 0.99 | 7490 0.30 | 74157 0.55 | 74253 2.57 | 7433 0.16 | 74147 2.10 | 74247 1.35 | | BF453 90p |
| NE562N 4.05 | CA3189E 2.20 | | 4023 0.19 | 4503 0.95 | 40098 0.54 | 7491 0.55 | 74158 0.55 | 74254 1.51 | 7437 0.17 | 74148 1.60 | 74248 1.85 | | BF454 90p |
| NE564N 4.29 | CA3240 1.27 | | 4024 0.45 | 4506 0.78 | 40106 0.54 | 7491 0.55 | 74159 1.90 | 74255 1.08 | 7438 0.16 | 74151 0.36 | 74249 1.36 | | BF455 90p |
| NE565N 1.00 | CA3300P 0.80 | | 4025 0.18 | 4507 0.48 | 40180 0.69 | 7492 0.35 | 74161 0.85 | 74256 1.30 | 7440 0.13 | 74153 0.35 | 74251 0.46 | | BF456 90p |
| NE566N 1.80 | CA3309E 0.80 | | 4026 1.05 | 4508 1.98 | 40181 0.69 | 7493 0.35 | 74162 0.85 | 74257 1.30 | 7442 0.40 | 74154 0.89 | 74252 0.46 | | BF457 90p |
| NE567N 3.85 | CA3389E 2.20 | | 4028 0.80 | 4510 0.70 | 40182 0.69 | 7494 0.70 | 74163 0.58 | 74258 3.50 | 7447 0.42 | 74158 0.50 | 74253 0.58 | | BF458 90p |
| NE568N 1.00 | CA3390C 0.80 | | 4029 0.35 | 4511 0.85 | 40163 0.69 | 7496 0.48 | 74164 0.58 | 74259 1.00 | 7448 0.86 | 74159 0.50 | 74254 0.58 | | BF459 90p |
| NE570N 3.85 | LM3909N 0.68 | | 4030 0.35 | 4512 0.70 | 40174 0.69 | 7497 1.40 | 74165 0.75 | 74260 1.00 | 7449 0.81 | 74161 0.38 | 74255 0.39 | | BF460 90p |
| SL824 3.28 | LM3914N 2.80 | | 4032 0.75 | 4514 2.20 | 40175 0.69 | 7497 1.40 | 74166 0.75 | 74261 1.00 | 7450 1.14 | 74162 0.40 | 74256 0.70 | | BF461 90p |
| TD4651 1.81 | LM3915N 2.80 | | 4033 0.85 | 4515 2.50 | 40192 0.75 | 7498 0.90 | 74167 1.25 | 74262 1.00 | 7451 1.14 | 74163 0.40 | 74257 0.70 | | BF462 90p |
| UA709HC 0.64 | LM4000 0.80 | | 4034 0.68 | 4516 0.75 | 40193 0.75 | 7499 0.90 | 74168 0.85 | 74263 1.00 | 7452 1.14 | 74164 0.40 | 74258 0.70 | | BF463 90p |
| UA709PC 0.46 | LM4001 0.60 | | 4043 0.93 | 4517 0.78 | 40194 0.68 | 7499 0.90 | 74169 0.85 | 74264 1.00 | 7453 1.14 | 74165 0.40 | 74259 0.70 | | BF464 90p |
| UA710HC 0.65 | LM4002 0.60 | | 4044 0.68 | 4520 0.80 | 40195 0.68 | 7499 0.90 | 74170 1.10 | 74265 1.00 | 7454 1.14 | 74166 0.40 | 74260 0.70 | | BF465 90p |
| UA710PC 0.59 | LM4003 0.60 | | 4047 0.89 | 4522 1.40 | | 7499 0.90 | 74171 1.10 | 74266 1.00 | 7455 1.14 | 74167 0.40 | 74261 0.70 | | BF466 90p |
| UA741CN 0.66 | LM4004 1.80 | | 4048 0.89 | 4527 0.98 | | 7499 0.90 | 74172 1.10 | 74267 1.00 | 7456 1.14 | 74168 0.40 | 74262 0.70 | | BF467 90p |
| UA741CN 0.27 | LM4005 1.09 | | 4050 0.30 | 4528 1.40 | | 7499 0.90 | 74173 1.10 | 74268 1.00 | 7457 1.14 | 74169 0.40 | 74263 0.70 | | BF468 90p |
| UA747CN 0.70 | TD44420 2.85 | | 4051 0.65 | 4539 1.10 | | 7499 0.90 | 74174 1.10 | 74269 1.00 | 7458 1.14 | 74170 0.40 | 74264 0.70 | | BF469 90p |
| UA748CN 0.36 | KB4423 2.30 | | 4052 0.55 | 4539 1.10 | | 7499 0.90 | 74175 1.10 | 74270 1.00 | 7459 1.14 | 74171 0.40 | 74265 0.70 | | BF470 90p |
| UA783 2.44 | KB4424 1.85 | | 4053 0.68 | 4549 3.50 | | 7499 0.90 | 74176 0.75 | 74271 1.00 | 7460 1.14 | 74172 0.40 | 74266 0.70 | | BF471 90p |
| UA758 2.35 | K34431 1.85 | | 4054 1.30 | 4552 1.40 | | 7499 0.90 | 74177 0.75 | 74272 1.00 | 7461 1.14 | 74173 0.40 | 74267 0.70 | | BF472 90p |
| FB4820M 0.78 | KB4432 1.85 | | 4055 1.30 | 4556 0.58 | | 7499 0.90 | 74178 0.75 | 74273 1.00 | 7462 1.14 | 74174 0.40 | 74268 0.70 | | BF473 90p |
| KA940E 1.80 | KB4433 1.85 | | 4056 1.35 | 4550 2.15 | | 7499 0.90 | 74179 0.75 | 74274 1.00 | 7463 1.14 | 74175 0.40 | 74269 0.70 | | BF474 90p |
| TD41028 2.11 | KB4436 2.53 | | 4057 0.52 | 4539 1.10 | | 7499 0.90 | 74180 0.75 | 74275 1.00 | 7464 1.14 | 74176 0.40 | 74270 0.70 | | BF475 90p |
| TD41029 2.11 | KB4437 1.75 | | 4058 0.68 | 4549 3.50 | | 7499 0.90 | 74181 1.22 | 74276 1.00 | 7465 1.14 | 74177 0.40 | 74271 0.70 | | BF476 90p |
| TD41054 1.45 | KB4438 2.22 | | 4059 0.68 | 4549 3.50 | | 7499 0.90 | 74182 0.70 | 74277 1.00 | 7466 1.14 | 74178 0.40 | 74272 0.70 | | BF477 90p |
| TD41062 1.95 | KB4441 1.35 | | 4060 0.30 | 4529 1.40 | | 7499 0.90 | 74183 1.22 | 74278 1.00 | 7467 1.14 | 74179 0.40 | 74273 0.70 | | BF478 90p |
| TD41074 5.04 | KB4445 1.29 | | 4061 0.85 | 4539 1.10 | | 7499 0.90 | 74184 1.20 | 74279 1.00 | 7468 1.14 | 74180 0.40 | 74274 0.70 | | BF479 90p |
| TD41074A 5.04 | KB4446 2.75 | | 4062 0.35 | 4549 3.50 | | 7499 0.90 | 74185 1.20 | 74280 1.00 | 7469 1.14 | 74181 0.40 | 74275 0.70 | | BF480 90p |
| TD41083 1.95 | KB4448 1.65 | | 4063 0.68 | 4549 3.50 | | 7499 0.90 | 74186 1.98 | 74281 1.00 | 7470 1.14 | 74182 0.40 | 74276 0.70 | | BF481 90p |
| TD41090 2.00 | NE5044M 2.80 | | 4064 0.85 | 4549 3.50 | | 7499 0.90 | 74187 1.22 | 74282 1.00 | 7471 1.14 | 74183 0.40 | 74277 0.70 | | BF482 90p |
| HA1137 1.20 | NE5532N 1.85 | | 4065 1.30 | 4556 0.58 | | 7499 0.90 | 74188 1.00 | 74283 1.00 | 7472 1.14 | 74184 0.40 | 74278 0.70 | | BF483 90p |
| HA1196 2.00 | SD6000 3.75 | | 4066 1.35 | 4550 2.15 | | 7499 0.90 | 74189 0.75 | 74284 1.00 | 7473 1.14 | 74185 0.40 | 74279 0.70 | | BF484 90p |
| HA1197 1.00 | SL6270 2.03 | | 4067 1.35 | 4550 2.15 | | 7499 0.90 | 74190 0.75 | 74285 1.00 | 7474 1.14 | 74186 0.40 | 74280 0.70 | | BF485 90p |
| TD41220 1.40 | SL6310 2.03 | | 4068 0.70 | 4550 2.15 | | 7499 0.90 | 74191 0.55 | 74286 1.00 | 7475 1.14 | 74187 0.40 | 74281 0.70 | | BF486 90p |
| LM1303 0.59 | SL6600 3.75 | | 4069 0.30 | 4550 2.15 | | 7499 0.90 | 74192 0.55 | 74287 1.00 | 7476 1.14 | 74188 0.40 | 74282 0.70 | | BF487 90p |
| LM1307 1.55 | SL6640 2.75 | | 4070 0.25 | 4550 2.15 | | 7499 0.90 | 74193 0.55 | 74288 1.00 | 7477 1.14 | 74189 0.40 | 74283 0.70 | | BF488 90p |
| MCI310P 1.90 | SL6640 POA 2.00 | | 4071 0.22 | 4550 2.15 | | 7499 0.90 | 74194 0.55 | 74289 1.00 | 7478 1.14 | 74190 0.40 | 74284 0.70 | | BF489 90p |
| MCI330 1.70 | SL6680 2.00 | | 4072 0.22 | 4550 2.15 | | 7499 0.90 | 74195 0.55 | 74290 1.00 | 7479 1.14 | 74191 0.40 | 74285 0.70 | | BF490 90p |
| MCI350 1.70 | SL6700 2.35 | | 4073 0.22 | 4550 2.15 | | 7499 0.90 | 74196 0.55 | 74291 1.00 | 7480 1.14 | 74192 0.40 | 74286 0.70 | | BF491 90p |
| HA1370 1.90 | ICL8038CC 4.50 | | 4074 0.25 | 4550 2.15 | | 7499 0.90 | 74197 0.55 | 74292 1.00 | 7481 1.14 | 74193 0.40 | 74287 0.70 | | BF492 90p |
| HA1388 2.75 | MSL9382 1.75 | | 4075 0.25 | 4550 2.15 | | 7499 0.90 | 74198 0.55 | 74293 1.00 | 7482 1.14 | 74194 0.40 | 74288 0.70 | | BF493 90p |
| TD41490 1.86 | MSL9383 1.75 | | 4076 0.60 | 4550 2.15 | | 7499 0.90 | 74199 0.55 | 74294 1.00 | 7483 1.14 | 74195 0.40 | 74289 0.70 | | BF494 90p |
| MCI496P 1.25 | HA11271 1.95 | | 4077 0.23 | 4550 2.15 | | 7499 0.90 | 74200 0.55 | 74295 1.00 | 7484 1.14 | 74196 0.40 | 74290 0.70 | | BF495 90p |

Team Up With TH Electronics

for top-quality components, innovative kits
FAST SERVICE AND LOW, LOW PRICES

Prices do not include V.A.T. Add 50p P. & P. + 15% V.A.T. to total. Overseas customers add £1.50 (Europe), £4 (elsewhere). Access and Barclaycard welcome. Send s.a.e. for price list and with enquiries. Shop open: 9-5 (Mon.-Fri.), 10-4 (Sat.)
11 BOSTON ROAD, LONDON, W7 3SJ
Tel: 01-579 9794/2842

THE KEY TO YOUR SECURITY



IS IN OUR LOCK

If you have problems with people tampering with your car, electrical and electronic equipment, or if you are just in a habit of forgetting your door keys, we have just the kit for you.

Our ELECTRONIC LOCK KIT includes a 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is pre-wired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7 x 6 x 3 cms. Power consumption is 40uA at 5V, to 15V, d.c.

At only £10.50 + V.A.T., it will make a smaller hole in your pocket than a bunch of keys!

LOCK I.C.s

| | |
|---|--------|
| LS7220 with SAVE memory | £2.75 |
| LS7225 with latched and momentary outputs and a tamper output | £2.90 |
| Electric lock mechanism | £12.50 |

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 1KW £4

MK2 SOLID STATE RELAY
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. £2.60

MK3 BAR/OOT DISPLAY
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

MK4 PROPORTIONAL TEMPERATURE CONTROLLER
Based on a new zero voltage switch IC, this kit may be wired to form a "burst fire" power controller, enabling the temperature of an enclosure to be maintained within 0.5°C. Thermistor failure causes output to switch off. Temperature range ambient to 90°C. 3KW. £5.55

MK5 MAINS TIMER
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. £4.50

TRIACS

| | |
|---------------------------|------|
| 400V Plastic Case (Texas) | 49p |
| 5A TIC206D | 58p |
| 8A TIC226D | 85p |
| 12A TIC236D | 95p |
| 16A TIC246D | 130p |
| 25A TIC256D | 195p |
| 6A with trigger Q406LT | 80p |
| 8A isolated tab TXAL226B | 65p |
| Diac | 18p |
| Opto-isolated Triac | |
| MOC3020 0.6A/400V | 110p |

REMOTE CONTROL COMPONENTS AND KITS

| | | | |
|---|------|--|------|
| LD2711 IR Emitting Diode | 36 | ML927 16-channel Receiver, 4 Momentary Binary Outputs | 1.40 |
| SF4205 Photodiode Detector | .90 | ML928 16-channel Receiver, 4 Latched Binary Outputs | 1.40 |
| SL480 IC Pulse Amp | 1.70 | ML929 16-channel Receiver, 4 Latched Binary Outputs | 1.40 |
| SL490 32-command Encoder/Transmitter | 2.40 | Clip-on Plastic Reflector for IR LEDs, increases range | .20 |
| ML922 10-channel Receiver + 3 Analogue Outputs | 4.20 | | |
| ML926 16-channel Receiver, 4 Momentary Binary Outputs | 1.40 | | |

LS925 A decoder designed for model/toy control, providing a 2-speed drive motor and three-position latched steering system or a vehicle with momentary action steering and a third motor, e.g. gun, turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. £2.10

KITS ★★★★★ KITS ★★★★★ KITS ★★★★★ KITS

| | |
|--|--------|
| MK6 - Simple Infra-Red TRANSMITTER. A pulsed infra-red source which comes complete with a hand-held plastic box. Requires a 9V. battery. | £4.20 |
| MK7 - Infra-Red RECEIVER. Single channel, range approximately 20ft. Mains powered with a triac output to switch loads up to 500W. at 240V. a.c. but can be modified for use with 5-15V. d.c. supplies and transistors or relay outputs. | £9.00 |
| MK8 - Coded Infra-Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8 x 2 x 1.3 cms. and requires a 9V. (PP3) battery. | £5.90 |
| MK9 - 4-way KEYBOARD. For use with MK8 Kit. | £1.90 |
| MK10 - 16-way KEYBOARD for use with MK8 kit, to generate different codes for decoding by the ML928-926 receiver (MK12 kit). | £5.40 |
| MK11 - 10 on/off channel IR RECEIVER with 3 analogue outputs (0-10V.) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC, includes its own mains supply. | £12.00 |
| MK12 - 16-channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which, with further suitable circuitry, such as relays, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. | £11.95 |
| MK13 - 11-way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and - analogue - and - CL mute, normalise analogue outputs, and on/standby. | £4.35 |

DVM/THERMOMETER KIT



Based on the ICL7126 (a low power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement - giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.
£15.50 + VAT

SPECIAL OFFER

orders must be received before 30.11.81

| | | | |
|------------------|------|---------------|------------|
| 556 | .35 | ML926 | 1.20 |
| AY-3-1270 | 7.50 | ML928 | 1.20 |
| LM377 | 1.30 | S566B | 2.05 |
| LM380 | .65 | SN76477 | 1.70 |
| LM3914 | 1.95 | TIL38 IR Leds | 5 for 1.00 |
| 20 0.2" Red LEDs | 1.60 | IR Leds | 4 for 50p |

INTEGRATED CIRCUITS

| | |
|---|------|
| 555 Timer | .21 |
| 556 Dual 555 Timer | .40 |
| 741 Op-Amp | .19p |
| 1A0590 Constant Current Temperature Sensor | 2.75 |
| AY-5-1224 Clock | 2.60 |
| AY-5-1230 Clock/Timer | 4.50 |
| AY-3-1270 Thermometer | 8.20 |
| CA3080 Transconductance Op Amp | .72 |
| CA3130 CMOS Op. Amp. | .75 |
| CA3140 CMOS Op. Amp. | .43 |
| ICL7106 DVM (LCD drive) | 7.00 |
| ICM755 CMOS 555 Timer | .79 |
| LM377 Dual 2W. Amp. | 1.40 |
| LM3795 Dual 5W. Amp. | 3.50 |
| LM380 2W. Audio Amp. | .80 |
| LM382 Dual low-noise Pre-Amp. | 1.00 |
| LM386 250mW. Low Voltage Amp. | .75 |
| LM1830 Fluid Level Detector | 1.50 |
| LM2917 F-V. Converter (14-pin) | 1.60 |
| LM3905 LED Flasher/Oscillator | .50 |
| LM3911 Thermometer | 1.20 |
| LM3914 Dot/Bar Driver (linear) | 2.10 |
| LM3915 Dot/Bar Driver (log.) | 2.20 |
| LS7220 Electronic Combination Lock with "Save" feature | 2.75 |
| LS7225 Electronic Combination Lock with tamper output | 2.60 |
| MM74C911 4-digit display controller | 6.50 |
| MM74C915 7-segment BCD Converter | .96 |
| MM74C926 Counter/7-seg. output | 4.50 |
| S566B Touchdimmer | 2.50 |
| SL440 A.C. Power Controller | 1.75 |
| SL441 Burst Fire Controller | 1.35 |
| SN76477 Complex Sound Generator | 1.75 |
| TBA806 5W. Audio Amp. | .68 |
| TBA810A5 7W. Audio Amp. | 1.00 |
| TMS1121 Clock/7-day Timer | 8.50 |
| Data for TMS1121 | 1.20 |
| TDA1024 Zero Voltage Switch | 1.80 |
| TDA2020 20W. Audio Amp. | 2.85 |
| TDA4290 D.C. Controlled, Base, Treble and Volume Pre-Amp. | 1.98 |
| TL081 J-FET Op. Amp. | .37 |
| TL082 Dual J-FET Op. Amp. | .60 |
| TL084 Quad J-FET Op. Amp. | 1.00 |
| ZN414 A.M. Radio | .98 |
| ZN1034E Timer | 1.80 |

Most ICs supplied with Data Sheet
Data Sheets only - per device .10



NOT JUST ANOTHER CLOCK

but a PROGRAMMABLE TIMER KIT which can run your central heating, burglar alarm, lighting, tape-recorder/radio and lots more. Designed to control four mains outputs independently, switching these on and off on selected days and times in a seven-day cycle.

Features include:

- ★ 0.5in. LED 12-hour display
- ★ Day of week, a.m./p.m. and output status indicators
- ★ Zero Voltage Switching Outputs
- ★ 50/60Hz mains operation
- ★ Battery back-up saves stored programmes and continues time keeping during power failures (battery not supplied)
- ★ Display blanking during power failure to conserve battery power
- ★ 18 programme time sets
- ★ Powerful "Everyday" function enabling output to switch every day but use only one time set
- ★ Useful "sleep" function - turns on output for one hour
- ★ Direct switch control enabling output to be turned on immediately or after a specified time interval
- ★ 20-function keypad for programme entry
- ★ Programme verification at the touch of a button

To control your central heating, for example (including different switching times at weekends), just connect it to your system, programme it, set it and forget it. The clock will do the rest. There has never been a clock capable of so much at this price.

CT5000K Timer Kit (includes all components, assembly and programming instructions, and an attractive black case)

£45.00

MEMORIES & MICROS

| | | | |
|-------|------|----------|------|
| 2114 | 1.35 | Z80A CPU | 5.00 |
| 2708 | 2.25 | M6802P | 5.50 |
| 2716 | 2.65 | 8035L | 8.00 |
| 2732 | 7.60 | Z80A CTC | 4.00 |
| 4116 | 1.40 | Z80AP10 | 4.00 |
| 6810 | 1.40 | 6850P | 1.85 |
| 6821P | 1.85 | 6852P | 3.00 |

YOU MUST HAVE BETTER THINGS TO DO

than getting up to switch lights on when it gets dark. Our Lamp Dimmer Kit with INFRA-RED REMOTE CONTROL will enable you to switch the lights on or off, and set the brightness, at a push of a button without leaving your armchair, water-bed, etc. Not only will you save time but it has also been estimated that the savings in shoe leather and carpet wear alone would pay for this unit in approximately 1.3697 years or more!



This unit has, of course, considerable practical uses, especially for the old, infirm and disabled. It works like a conventional dimmer, enabling you to switch the lights on or off, or to dim to whatever brightness you require, by touch or remotely using the hand-held infra-red transmitter. When assembled, it fits into a plaster depth box to



replace your conventional switch or dimmer with no rewiring and will control up to 300w of lighting. TD300K Dimmer Kit £14.30, and MK6 Transmitter Kit £4.20
We also still sell our highly-popular TD300K Touch Dimmer Kit at £7.00 and the LD300K rotary-controlled Dimmer Kit at only £3.80 (plus V.A.T. to above prices).
All kits contain all necessary components and full assembly instructions. You will need a soldering iron, cutters and a few hours.



WILMSLOW AUDIO

The firm for Speakers

Everything in stock for the speaker constructor!

BAF, Long Fibre Wool, Foam, Crossovers, Felt Panels, Components, Speaker Stands and Brackets, etc. Large selection of Grille Fabrics (send 30p in stamps for fabric samples).

HI-FI DRIVE UNITS



| | |
|-----------------------------|---------|
| AUDAX HD12 9D25 | £8.75 |
| AUDAX HD100D25 | £8.75 |
| AUDAX HD11P25EBC | £7.50 |
| AUDAX HD20825-4 | £14.95 |
| AUDAX HD13034H | £12.95 |
| AUDAX HD24S45C | £21.95 |
| AUDAX WFR15S | £23.95 |
| COLES 4001 | £7.65 |
| COLES 3000 | £7.65 |
| COLES 3100 | £7.95 |
| COLES CE2000 8in. | £14.95 |
| CELESTION HF1300 II | £13.60 |
| CELESTION HF2000 | £13.60 |
| DALESFORD D10 Isofofluid | £8.95 |
| DALESFORD D30/110 | £11.95 |
| DALESFORD D50/153 | £12.95 |
| DALESFORD D50/153 polymer | £15.25 |
| DALESFORD D50/200 | £12.95 |
| DALESFORD D50/200 polymer | £15.25 |
| DALESFORD D100/250 | £29.95 |
| DALESFORD D300 | £35.75 |
| DECCA London Horn | £89.95 |
| ISOPHON KKB/8 | £8.25 |
| ISOPHON KK10/8 | £8.75 |
| JORDAN 50mm tweeter | £31.50 |
| JORDAN Crossover, pair | £31.90 |
| JORDAN WATTS Module Mk. III | £28.50 |
| JORDAN WATTS HF 100 | £10.50 |
| KEF T27 | £9.45 |
| KEF B110 | £12.25 |
| KEF B200 | £13.50 |
| KEF B139 | £27.75 |
| KEF DN12 | £9.95 |
| KEF DN13 SP110S | £7.75 |
| KEF DN13 SP1017 | £6.95 |
| LOWTHER PM6 | £63.00 |
| LOWTHER PM6 Mk. I | £67.75 |
| LOWTHER PM7 | £99.90 |
| PEERLESS K0100T | £11.50 |
| PEERLESS DT104FC | £10.95 |
| PEERLESS K040MRF | £14.75 |
| RICHARD ALLAN CG8T | £14.25 |
| RICHARD ALLAN CG12T Super | £30.95 |
| RICHARD ALLAN HP12B | £35.75 |
| RICHARD ALLAN DT20 | £10.75 |
| RICHARD ALLAN DT30 | £11.50 |
| SEAS H107 | £8.95 |
| SEAS H211 Ferrofluid | £10.95 |
| SHACKMAN ES Units, pair | £136.00 |
| SHACKMAN ES with Cabs. pair | £170.00 |
| TANNOY DC386 | £199.00 |
| TANNOY DC316 | £159.00 |
| TANNOY DC296 | £118.00 |
| VOLT B250 | £58.00 |
| VOLT 10in. ABR | £32.00 |
| VOLT B220 | £49.00 |
| VOLT 8in. ABR | £25.00 |

PA GROUP & DISCO UNITS



| | |
|----------------------------|---------|
| CELESTION G12/50TC | £19.50 |
| CELESTION G12/80CE | £24.50 |
| CELESTION G15/100CE | £37.95 |
| CELESTION G15/100TC | £38.50 |
| CELESTION G18/200 | £64.75 |
| CELESTION G18/250 | £81.75 |
| FANE Classic 10/100 | £17.50 |
| FANE Classic 12/50 | £15.75 |
| FANE Classic 12/100 | £21.75 |
| FANE Classic 15/100 | £29.75 |
| FANE Classic 15/150 | £38.50 |
| FANE Classic 15/200 | £44.00 |
| FANE Classic 18/200 | £47.95 |
| FANE Classic 18/250 | £51.75 |
| FANE Disco 100/2 | £28.75 |
| FANE Guitar 100L | £26.75 |
| FANE Guitar 100B | £27.50 |
| FANE PA 100 | £26.75 |
| FANE Bass 100 | £39.00 |
| FANE Studio 12L, 12B | £45.50 |
| GAUSS 12in. models | £146.00 |
| GAUSS 15in. models | £162.00 |
| GAUSS 18in. models | £220.00 |
| GOODMANS PP12 | £22.50 |
| GOODMANS DI12 | £25.50 |
| GOODMANS GR12 | £24.95 |
| GOODMANS HiFax 50HX | £21.85 |
| GOODMANS HiFax 100HX | £24.50 |
| McKENZIE C12/100GP | £24.45 |
| McKENZIE C12/100TC | £24.45 |
| McKENZIE C12/100 Bass | £24.45 |
| McKENZIE C12/125GP | £39.95 |
| McKENZIE C12/125TC | £39.95 |
| McKENZIE C12/200 | £54.25 |
| McKENZIE GP15 | £35.10 |
| McKENZIE TC15 | £35.10 |
| McKENZIE C15 Bass | £59.60 |
| McKENZIE C15/200 | £63.25 |
| McKENZIE C10/100 | £22.50 |
| MOTOROLA Piezo 3 1/2in. | £4.50 |
| MOTOROLA Piezo 2in. x 6in. | £8.75 |
| RCF L12P24 | £63.50 |
| RCF L12P11C | £82.75 |
| RCF L15P03 | £68.95 |
| RCF L15P/100A | £85.50 |
| RCF L15P/06C | £87.75 |
| RCF TW101 | £39.95 |
| RCF TW25 | £21.95 |
| RCF TW105 | £18.75 |
| RCF H2010 Flare | £8.75 |
| RCF H4823 Flare | £32.50 |
| RICHARD ALLAN HDB, HDBT | £21.25 |
| RICHARD ALLAN HD10, HD10T | £22.95 |
| RICHARD ALLAN HD12P | £31.25 |
| RICHARD ALLAN HD12 Super | £41.75 |
| RICHARD ALLAN HD15 | £55.25 |
| RICHARD ALLAN Atlas 18 | £99.75 |

WILMSLOW AUDIO



KITS FOR MAGAZINE DESIGNS etc.
Kits include drive units, crossovers, BAF/long fibre wool, etc., for a pair of speakers.
Carriage £3.95 unless otherwise stated.
Prices per pair.

| | |
|---|-------------------------|
| Everyday Electronics EE70 | £144.00 |
| Everyday Electronics EE20 | £29.95 |
| Hi-Fi Answers Monitor | £148.00 |
| Hi-Fi for Pleasure Compact Monitor | £116.00 |
| Hi-Fi for Pleasure ECM inc. foam, felt panels, etc. | £77.50 |
| Hi-Fi News State of the Art | £205.00 |
| Hi-Fi News Midline | £119.75 |
| Hi-Fi News Miniline | £49.00 |
| Hi-Fi News Tabor with J4 Bass Units | £69.00 |
| Hi-Fi News Tabor with H4 Bass Units | £73.50 |
| Popular Hi-Fi Boxer | £299.00 |
| Popular Hi-Fi Boxer Cabinets, pair | £109.00 |
| Popular Hi-Fi Jordan System 1 | £120.00 |
| Popular Hi-Fi Mini Monitor | £84.00 |
| Practical Hi-Fi PRO9TL inc. felt panels and level controls | £156.75 |
| Practical Hi-Fi B5C3 | £68.00 |
| Wireless World T.L. Kef Units | £125.00 |
| Flat-pack Cabinet Kits are available for LS3 Micromonitor, BSC3, HFP Compact Monitor, EE20, EE70, Wharfedale E50, E70, E90 (also E90 in Pro disco style). | |
| Wilmslow Audio BA1 Sub Bass Amplifier/Crossover Kit | £37.95 plus £1 carriage |

All prices include V.A.T. at 15% and are correct at 1-7-81

Building speakers is easy with the new WILMSLOW AUDIO FLAT-PACK CABINET KITS!

CARRIAGE & INSURANCE

| | |
|-------------------------|-----------|
| Tweeters/Crossovers | 70p ea. |
| Speakers: | |
| 4in. to 6 1/2in. | 30p ea. |
| 8in. to 10in. | £1.10 ea. |
| 12", 13" x 8", 14" x 9" | £2 ea. |
| 15in. | £3 ea. |
| 18in. | £5 ea. |
| Speaker Kits | £3.95 pr. |
| Mag. Design Kits | £3.95 pr. |
| unless otherwise stated | |

SPEAKER KITS



Speaker Kits. Prices per pair. Carriage £3.95 unless otherwise stated.

| | |
|---|---|
| COLES Nimbus mounted-on Baffle... | £69 |
| DALESFORD D including Cabinets | |
| DALESFORD D Major inc. Cabinets | £69.95 |
| DALESFORD Rock Kit inc. Flatpack Cabinet Kit | £139.00 |
| KEF Ref. 104AB (carr. £5) | £73.50 |
| KEF Cantata | £133.00 |
| KEF Cantata | £199.00 |
| LS3 Micromonitor | £84.00 |
| LS3 Micromonitor inc. Cabinets, etc. | |
| LOWTHER PM6 Kit | £103.95 |
| LOWTHER PM6 Mk. I Kit | £132.75 |
| LOWTHER PM7 Kit | £139.95 |
| LOWTHER PM7 Kit | £199.00 |
| RICHARD ALLAN Tango Twin | £58.00 |
| RICHARD ALLAN Marimba Triple 8 | |
| RICHARD ALLAN Charisma Triple | £83.00 |
| RICHARD ALLAN RA8 | £119.50 |
| RICHARD ALLAN RA82 | £87.50 |
| RICHARD ALLAN RA82L | £106.50 |
| RICHARD ALLAN Super Sarabande II | £116.50 |
| SEAS 223 | £169.95 |
| SEAS 253 | £42.50 |
| SEAS 403 | £67.00 |
| SEAS 603 | £79.95 |
| SEAS Disco 47 | £134.95 |
| SEAS Disco 47 Cabinets, pair, assembled (carr. £15) | £167.50 |
| WHARFEDALE Denton XP2 | £167.50 |
| WHARFEDALE Shelton XP2 | £31.45 |
| WHARFEDALE Linton XP2 | £40.40 |
| WHARFEDALE L60 | £56.20 |
| WHARFEDALE L80 | £52.50 |
| WHARFEDALE L100 | £72.00 |
| WHARFEDALE E50 | £87.00 |
| WHARFEDALE E70 | £129.00 |
| WHARFEDALE E90 | £160.00 |
| WHARFEDALE E90 | £249.00 |
| WILMSLOW Audio WE50 Total Kit - Wharfedale E50 Kit plus WE50 Flat-pack Cabinet Kit including Reflex Port Trims, Acoustic Wadding Grille Fabric, Nuts, Bolts, Terminals, etc., pair | £182 Carriage £8 |
| WILMSLOW Audio WE70 Total Kit as above but with E70 | £220 pair Carriage £8 |
| WILMSLOW Audio WE90 Total Kit as above but with E90, pair | £330 Carriage £10 |
| WILMSLOW Audio WE90 Pro Total Kit - Wharfedale E90 Kit plus WE90 Flatpack Cabinet Kit including Reflex Port Trims, Acoustic Wadding Grille Fabric, Heavy-Duty Handles, Castors with Brakes, Protective Corners, Black Vynide Cabinet Covering, Input Panels, Protective Fuses, Nuts, Bolts, etc. An ideal high-quality disco speaker for amplifiers up to 150 watts (disco) or 200 watts (domestic Hi-Fi), each | £187 Carriage £8 or £369 pair; carriage £10 |

ALL PRICES INCLUDE V.A.T. AT 15% AND ARE CORRECT AT 1.7.81

SWIFT
OF WILMSLOW
The firm for Hi-Fi
5 Swan Street,
Wilmslow, Cheshire.

Send 50p for our 80-page catalogue - (or price list only free of charge) packed with pictures and specifications of speakers, kits, cabinets, crossover, mics, amps, mixers, grilles, effects, etc.
Export catalogue £1 or \$3 U.S.

Telephone 0625-529599 for speaker drive units, kits, P.A. equipment, mail order enquiries, and all export enquiries.


Telephone: 0625-526213 for Hi-Fi equipment and complete speaker enquiries.

Lightning service on telephoned credit card orders!

WILMSLOW
AUDIO
The firm for Speakers

35/39 Church Street,
Wilmslow, Cheshire.

ELECTRONIC IGNITION KIT

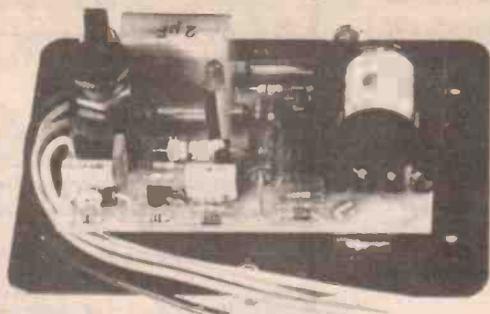

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN ELECTRONICS TODAY MAGAZINE

JUNE '81 ISSUE

Quote "the kit is very impressive"

"well written instructions and a good performance".

"Excellent value for money. Highly recommended".

FITS ALL VEHICLES, 6 or 12 volt, with or without ballast
NEGATIVE EARTH ONLY

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS

Some older current impulse types (Smiths pre '74) require an adaptor —
PRICE £2.95

STANDARD CAR KIT £14.85 PLUS £1
TWIN OUTPUT KIT £22.94 U.K. P.&P.

For MOTOR CYCLES and CARS with twin ignition systems
Prices include V.A.T.

ELECTRONIZE DESIGN

Magnus Road, Wilnecote
Tamworth, B77 5BY
Phone (0827) 281000



DIMENSIONS:
Length 12.5 cm
Width 8.9 cm
Height 4.3 cm
Lead length 100.0 cm

TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µS at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

SUPER POWER DISCHARGE CIRCUIT A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

HIGH EFFICIENCY INVERTER A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

PRECISION SPARK TIMING CIRCUIT This circuit removes all unwanted signals caused by contact volt drop, contact shuffler, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

TYPICAL SPECIFICATION

| | TOTAL ENERGY DISCHARGE | ORDINARY CAPACITIVE DISCHARGE |
|---|------------------------|-------------------------------|
| SPARK POWER (PEAK) | 140 W | 90 W |
| SPARK ENERGY (STORED ENERGY) | 36 mJ 135 mJ | 10 mJ 65 mJ |
| SPARK DURATION | 500 µS | 160 µS |
| OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS) | 38 KV | 26 KV |
| OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS) | 26 KV | 17 KV |
| VOLTAGE RISE TIME TO 20 KV (Load 50pF) | 25 µS | 30 µS |

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

INFRA RED IMAGE CONVERTER type 9606 (CV144) 1 1/2" dia Requires single low current 3KV to 6KV supply. Individually boxed. With data. £12.50 ea. 10 off £100.
 INFRA RED QUARTZ LAMPS. 230V 620 Watts Size 13 1/2 x 1/2" dia. £1.50 ea. 10 off £10.
 240V 1650 Watts Size 22 1/2 x 1/2" dia £3 ea. 10 off £25.
 AMPHENOL 17 way chassis mount edge connectors 0.1 connectors 0.1 spacing 15 ea
 I.E.C. MAINS LEAD. Moulded (3 vertical flat pins) 60p ea 10 off £5.
 FANS 115V 13 Watt Size 3 1/2 x 3 1/2 x 1 1/2". Secondhand £2.50 ea.
 CENTAUR FANS 115V 4 1/2 x 4 1/2 x 1 1/2". New £4.50 ea. Secondhand £2.50 ea.
 DELAY LINES 50 nanosecs. Gas-cooled. Size 2 x 7/16 x 5/16". New 25p ea. 10 off £2.
 PULSE TRANSFORMERS. Sub-min Size 1/2 x 5/16 x 1/4" Secondary centre tapped. New. Suitable for Thyristor triggering. 20p ea. 10 off £1.80. 100 off £15.
 MOTORS 12V DC with pulley & semiconductor speed control. New £1 ea. 10 off £8.
 LEDEX ROTARY SOLENOIDS. 115V DC No switch assembly. 15p ea. 10 off £1. 100 off £8.
 DIAMOND H CONTROLS ROTARY SWITCH Single pole 10 way. Printed circuit mount. New 10p ea 100 off £7. 1000 off £50.
 REMO TV TYPE MULTIPLIER. Two high voltage outputs & focus £1 ea. 10 off £8.
 DON'T TAKE CHANCES Use the proper EHT Cable 10p metre. £7.50 100 metres p8p £2.
 RAPID DISCHARGE CAPACITORS-6 mfd 4KV £5 each. p8p £2.
 HUNTS CAPACITOR 0.1 mfd 3KV DC Wkg. Size 1 1/2" dia x 3". £1.25 ea. 10 for £10.
 E.H.T. CAPACITOR 500 pf 8KV 20p each.
 DECOUPLING CAPS 0.05mfd 10V; 0.01mfd; 0.047 250V; 330pf. 100 off one type £1.80.
 CAPACITORS all at 5p each: 3300pf. 220nf 250V; 0.01mfd 160V; 0.1 uf 400V.
 TANTALUM BEAD CAPACITORS 2.2uf 20V 10 off £1, 100 off £7.50. 300uf 6.3V 15p ea.
 TANTALUM CAPACITORS. 22mfd 6V, 33mfd 10V; 22mfd 35V. All 10p 100 off £7.50
 GEC 4 Button UHF Tuner £1.50 ea. 10 off £12.

GEC 6 Button UHF/VHF TUNER. £2 ea. 10 off £15.
 SOLID STATE UHF TUNER 38MHz £1 ea. 10 off £8.
 RANCO 250V 18A THERMOSTATS with Control Knob calibrated 50-200°C. £2.50 ea.
 MICROPHONE/EARPIECE INSERTS. Ex Min. Brand New wrapped. 75p ea. 10 off £6.
 TRANSFORMERS — All Brand New.
 Auto 240V Input 115V 1 Amp output £1.25 ea.
 240V Input Sec 6V 1.86A. Size 2 1/2 x 2 x 2". Good quality. £1.50 ea.
 240V Input Sec 12V 100MA. Size 60 x 40 x 42 mm 50p ea.
 240V Input Sec 12-0-12V 50MA. Size 53 x 45 40 mm £1 ea.
 115V Input Sec 5V 250MA Size 1 1/2 x 1 1/2 x 1 1/2". 2 for 50p
 240V Input Sec 2 windings 12V and 24V 1 Amp. Size 2 1/2 x 2 x 2" £2 ea.
 Sub-Min 0-120-240V Input Sec 12-0-12V rated 4VA. 75p ea. 10 off £8, 100 off £45.
 TOROIDAL 0-115-230V Input. Output 13.5-0-13.5V rated 8VA. £1.70 ea. 10 off £16.
 TOROIDAL 0-120-240V Input. Output 0-12V; 0-12V 10VA per winding. Encapsulated. Identical to R.S. Components at £9.40. OUR PRICE £5 ea.
 TELEPHONES — P&P £1.50 ea. 5-10 units £6. Over by arrangements.
 706 style Black, Grey, Blue, Green £5.50 ea. 10 off £45.
 Discoloured £4 ea. 10 off £27.50
 746 style Black or Grey £7.50 ea. Older Black style £2.50 ea
 TRIMMERS Sub-min 0.25-1.25pf; 1-4.5pf; 7-45pf. All at 6p ea.
 PC MOUNT POTS. Wire wound with knob. 200ohm & 10 ohm. 10p ea. 100 off £7.
 HONEYWELL HUMIDITY CONTROLLERS 50p ea. 10 off £4.50
 THYRISTOR TIMER. Solid State. 15 secs adjustable (reset). 7 pin base 50p ea.
 4 DIGIT 7 SEGMENT DISPLAY. Good brilliance at 1.5V. 15 connections £1.95 ea.
 MONANRO SIAPLY type MAN 101A0.3" display 75p ea.
 FILAMENT DISPLAY 7 Segment DIL 16 pin 5V at 8Ma per segment. Char height 9.2mm As new. Connections supplied 50p ea.
 PUSH BUTTON CIRCUIT BREAKER. Small Compact 3 ratings 0.8; 1.8 oe 10Amp. 75p ea.

A MUST FOR THE COMPUTER OR VIDEO MAN
CONRAC 14" MONITOR. Solid state sync plus video input sockets. Not cased. Used but tested.
£35 each. Carriage £6
 Other monitors available including colour. Please enquire

CREED MODEL 75
 Printer with keyboard. Late model.
 Only £25 each
 Receive Only £18 each. Carriage £6

COSSOR VDU with KEYBOARD
 80 characters x 13 lines; 600/1200 baud;
 RS232; standard 240 volts input; screen size 9 inches. Very good condition. Tested.
£70 each. Carriage at cost.

GENERAL PURPOSE OSCILLOSCOPE TECH TYPE T0-2
 Single beam. Size approx 6 x 7 x 9 1/2 in. Weight 7lbs
 Ideal for the beginner or school user.
ONLY £49.50 each P&P £3

SINE & SQUARE WAVE AUDIO GENERATOR
 Type TE22
 20HZ-200KHZ. Portable. As new.
ONLY £55 each P&P £3

MULTIMETER
 Russian type 4324 AC/DC volts; AC/DC current; ohms, etc. Brand new, boxed,
£12.50 each P&P £2.50

RADAR AERIALS
 Rotary, complete with Waveguide Couplers. These are brand new, Ministry boxed. Very impressive. Dish diameter 27 inches
£65 each. Carriage £6

METROHM INSULATION AND CONTINUITY TESTER 500 volts
 Portable. Battery Operated. Standard PP7 (Battery not supplied).
 Complete with carrying case. As new £40 ea.
 Used but good condition £25 ea.
 As above but 250 volts. Used £17.50 ea. P&P £3

MINIMUM ORDER OF GOODS £3. MINIMUM PACKAGING & POSTAGE £1.50. VAT at 15% MUST be added to TOTAL of GOODS & PACKAGING BUT PLEASE ensure sufficient monies is sent to cover PACKAGING and Postage to avoid delays in us dispatching your order
 CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome


CHILTMEAD LTD

NORWOOD ROAD, READING TELEPHONE NO READING 669656

2nd turning left past Reading Technical College in King's Road then first right — look on right for door with "Spoked Wheel"

The Finest Amplifiers deserve the Finest Kits

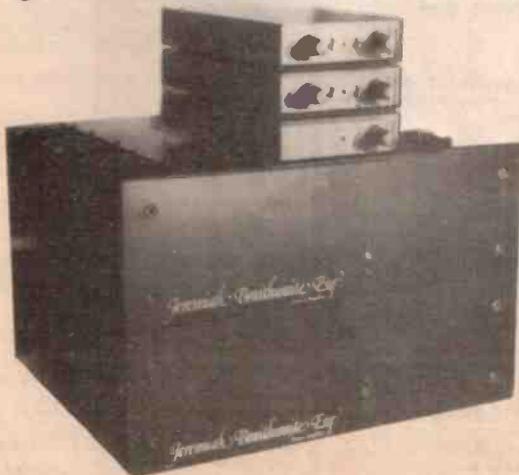The Electronics Today System A, designed by Stan Curtis comprises two monophonic Class A Power Amplifiers and a modular pre-amplifier of such superlative performance that they stand comparison with commercial products in any price range.



Braithwaite KITS

- ★ are approved by the designer
- ★ use the finest quality components
- ★ offer a unique "get you out of trouble" service and full technical support.
- ★ offer a unique post-assembly testing service

Complete Kits
 (Part Kits available)
 Pre-Amplifier £76.90
 Mono Power-Amplifier £221.95
 including VAT (carriage extra).

Details and price list from:

Braithwaite KITS

215, High Street, Offord Cluny,
 Huntingdon, Cambs. (0480) 811659



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30

RAM AND EPROM NEW LOW VAT INCLUSIVE PRICES

| | | | | |
|---------------|-------|-----------|-------------------|--------------|
| 2716 5v Rail | £6.00 | 4116 | 200 NS 16KX1 DYN. | 8 for £19.95 |
| 2716 3 Rail | £7.50 | 2114L-3 | 300 NS 1KX4 ST. | 8 for £22.50 |
| 2708 450 NS | £4.50 | 2102L-3 | 650 NS 1KX1 ST. | 8 for £ 5.50 |
| 2708 Ex Equip | £2.25 | TMS4030JL | 300 NS 4KX1 DYN | 8 for £ 9.95 |

All devices full spec. and guaranteed. Bulk enquiries welcome.

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

TELETYPE ASR33 I/O TERMINALS



From **£195** + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT
Sound proof enclosure £25.00 + VAT

ICL TERMIPRINTER 300 BAUD TERMINALS



PRICES REDUCED

ONLY **£295**

+ CAR + VAT

Made under licence from the world famous GE Co. The ICL Termiprinter is a small attractive unit with so many features it is impossible to list them in the space available! Brief spec. as follows: RS232 serial interface, switchable baud rates 110, 150, 300, (30 cps), upper and lower case correspondence type face, standard paper, almost silent running, form feed, electronic tab settings, suited for word processor applications plus many more features. Supplied in good condition and in working order. Limited quantity.

MPU EXPERIMENTORS + 5v + 12v + 12v + 24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 160mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:
+ 5v @ 2 amps DC + 12v @ 800 ma DC
- 12v @ 800 ma DC + 24v @ 350 ma DC
and if that's not enough a fully floating 5v output @ 50 ma DC which may be seriesed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 340V AC mains input. They are ex GPO and may have minor scratches on the front panels, they are sold untested but in good internal condition. **£16.50 each + £2.50 p+p** complete with circuit and component list. Transformer guaranteed. **HURRY WHILE STOCKS LAST!!**

HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd. to a "no cost spared" spec for the GPO, the Modem 12 is a synchronous Modem for use on DATEL 2412 services, or other data links. Many features include switchable V28 modulation, 2400 baud full duplex 800/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication, CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc.
£185.00 + £9.50 carriage + VAT.
*Permission may be required for connection to PD lines.


PERTEC

PERTEC TAPE DRIVES

7 track 6840 — 75-25 **£175.00** + VAT
9 track 6840 — 9-25 **£295.00** + VAT

Phone for more details

EQUIPMENT CASES

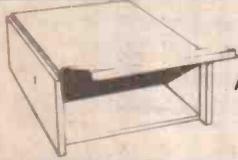

GIVE YOUR M.P.U. A HOME ONLY **£9.95** + 1.85 pp

Superb professional fully enclosed, made for the G.P.O. to the highest standard; offered at a fraction of their original cost they feature aluminium sides, hinged removable-front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand new may have minor scuff marks/scratches due to bad storage. Dimensions 16" D x 6 1/2" H x 14 3/4" W

NATIONAL MA1012 LED CLOCK MODULE

- ★ 12 HOUR
- ★ ALARM
- ★ 50/60 HZ



The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only
Suitable transformer **£1.75** **£5.25**

MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those unnerving hang ups and data glitches. fit one now and cure your problems! Suppression Devices SDS A10 5 amp **£8.95**
Corcom Inc F1900 30 amp **£13.95** + pp **£1.00**

MUFFIN FANS

Keep your equipment Cool and Reliable with our tested ex-equipment "Muffin Fans" almost silent running and easily mounted. Available in two voltages: 110 V.A.C. £5.95 + pp 90p OR 240v A.C. £8.15 + pp 90p DIMENSIONS 4 1/2" x 4 1/2" x 1 1/2"

ELECTRONIC COMPONENTS & EQUIPMENT


66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc etc surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads, for unbeatable value!! Sold by weight

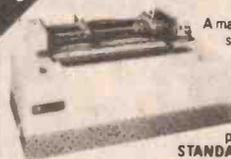2.5lbs **£ 4.75** + pp **£1.25** 5lbs **£ 6.75** + pp **£1.80**
10lbs **£11.75** + pp **£2.25** 20lbs **£19.99** + pp **£4.75**

SAVE OVER **£1400**

THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232C/V24 serial interface ★ 7xal controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eeproms easily reconfigured for custom fonts etc.

All this and more, not refurbished but BRAND NEW At Only **£525** + VAT + carriage and ins. **£18.00** + VAT
OPTIONAL EXTRAS ★ Lower case **£25.00** ★ 16K buffer **£30.00** ★ Second tractor for simultaneous dual forms **£85.00** ★ Logabax maintenance, P.O.A

MAJOR SAVINGS

HARD DISK DRIVES

Another major purchase allows us to bring you the professional technology of hard disk drives at a price you can now afford. Just imagine absolutely masses of correct data transferred or saved on your system by the time your finger leaves the carriage return key!! All drives offered are made to the highest professional standard by the DRE Co., perhaps the largest of UK OEM peripheral manufacturers. All components are batch selected to obtain the utmost reliability and after having run two series 30 and a 4000 drive continuously 24 hours a day for over a year without a single read/write error we can most certainly vouch for the quality.

DIABLO/DRE series 30. Fully refurbished this 2.5 MB drive accepts 2315 exchangeable (via removing top cover) disk cartridges. Sectoring is a feature of the disk pack and may range from 8-48. Fully DEC RK05, Nova, Texas, system compatible. Requires +8 — 15v DC Supply.
Series 30 Drive, **£475** + VAT Series 30 Front Loader **£695** + VAT

DC Power Supply for 2 series 30's £125 + VAT
DRE 4000 B Series. Model 4044. Technology at its finest, this drive currently manufactured by DRE features 10 MB's of on line storage split into two disk platters, 1.5 MB fixed and 1 top load 5 MB type 5440 exchangeable cartridge. Features, DC drive motor, built in air conditioning system, write protect, mains powered, etc. Supplied Brand New and Boxed complete with Manual and Rack Slides.
Fully Ampex, Hawk, Wango, Nova compatible.
Manufacturers current price **£3100**, our price **£1495** — VAT.

*For DEC compatibility or alternate sectoring please enquire, Xylogics DECLSI 11 controller for 4 S30 or 2 4000 drives **£850** + VAT Newton Labs S100 controller for 4 S30 or 2 4000 **£625** + VAT Controller for TRS80, PET, APPLE. Price to be announced.
NEW 2315 12 sector disk packs **£40** + VAT
NEW 5440 any sector packs **£48** + VAT

ORDER NOW!! These prices may never be repeated. Specialist carriage S30 **£15.00** + VAT 4000 **£20** + VAT.

ELECTRONICS

Dept. ETI, 64-66 Melfort Road, Thornton Heath Croydon, Surrey - Tel: 01-689 7702 or 01-689 6800

MAIL ORDER INFORMATION

Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value **£2.00** Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bona Fida account orders minimum **£20.00**. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

EX STOCK SOFTY EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMs or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. **£115** + carr. + VAT. Optional 2716, 2716 Function Card **£40** + VAT. PSU **£20** + **£1.50** carr. + VAT.
Write of phone for more details.

9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75 Ω composite input, tested but unguaranteed. **£39.99** + **£7.50** carriage + VAT. Complete with circuit.

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistor, diodes, IC's, base, diodes, bridge nics, etc. etc. All devices guaranteed brand new full spec. with manufacturers markings. Fully guaranteed 50 + bag **£2.95** 100 + bag **£5.15**
TTL 74 Series
A genuine purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer our 100+ "mixed" TTL "grab bags" at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ **£6.90** 200+ **£12.30** 300+ **£19.50**

RCA FULLY CASED ASCII CODED KEYBOARDS



IDEAL - TANGERINE, OHIO ETC.

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of case fastened keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust. TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

| | |
|---|---------------|
| VP601 7 bit fully coded output with delayed stroke, etc. | £43.95 |
| VP611 Same as VP601 with numeric pad. | £54.95 |
| VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. | £64.26 |
| VP616 Same as VP606, with numeric pad, Plug and cable for VP601, VP611 | £84.34 |
| Plug for VP606, VP616 | £2.10 |
| Post, Packing and Insurance. | £1.95 |

ORDER NOW OR SEND FOR DETAILS.


5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply. Supplied complete with circuit at only **£10.95** + **£1.75** pp. Believed working but untested, unguaranteed.

BARGAINS



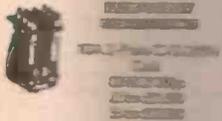L.D.R. SHIELD TO PROTECT FROM SHIELD WITH 50% OFF ONLY 30c



GEC CONTACTOR 3 NO CONTACTS 90W 250V 0.5A

TOGGLES 200V 10A 240V BIASED FEMALE GAS SOLID STATE 1/8" Pop

GLASS FIBRE 20mm QUICK BLOW 1" (FITS 1 1/8" O.D. BLOW HOLDER) BLOW SURROUND 10 40 100 CAN

ROLLER 20mm SPST 15c 10mm GLASS SOCKET BULGIN 3A 3 PIN PLUG AND SOCKET 50c USEFUL



LELELELE
LELELELE
LELELELE
LELELELE

ADD 50p P&P
ORDERS OVER
£5 post free

FOR THE ELECTRONICS MAN WITH NEARLY EVERYTHING!

22mm THERMIONIC VALVE IN A THERMIONIC PAPERWEIGHT. IDEAL PRESENT ONLY £2.10

LATCHING RELAY WITH MANUAL RESET



ONLY £1.00

LOW-COST, RUGGED TEMPERATURE CONTROL



BIG QUALITY TEMP. GAUGE 0° - 120°C Remote sensor on 38" capillary, panel mounting dial 55mm. dia. ONLY £1.85

200V 10A THERMOSTAT

200V 10A THERMOSTAT (to over boiling point) capillary. £2.30, including control knob

100°C THERMAL CUT-OUT 100°C

50 240V Sensing coil on 41in. capillary panel mounting with reset button £1.20

ORDER OF ABOVE FOR £4.85

ELECTRO SUPPLIES

| | | | | |
|------------|--------|------|---------|------|
| UNL AR ICs | SALTER | 150p | TDA1170 | 175p |
| CA3022 | SARSK | 100p | YDA1190 | 200p |
| CA3060 | SARSK | 100p | TDA2524 | 150p |
| LM324 | TALAZ | 40p | TDA2541 | 150p |
| LM741 | TALAZ | 40p | TDA2560 | 150p |
| LM1458 | TALAZ | 40p | TDA2581 | 175p |
| LM3900 | TALAZ | 40p | | |
| MC1307 | TALAZ | 40p | | |
| MC1310 | TALAZ | 40p | | |
| MC1349 | TALAZ | 40p | | |
| MC1350 | TALAZ | 40p | | |
| MC1558 | TALAZ | 40p | | |
| NE535T | TALAZ | 40p | | |
| NE555 | TALAZ | 40p | | |

SPECIAL OFFER
AY-5-3507 DVM CHIP
(with data) £2.00
(limited quantity)

SPECIAL OFFERS

| | |
|-------------------------------|--------------------------------------|
| LM1011N (DOLBY BUC) £2.50 | TALAZ05 £2.00 |
| TDA2020 (20-watt) £2.50 | MM53-100N (TV clock timer) £2.00 |
| MM57105 (PAL colour TV) £2.00 | AY-5-1013 (UART) c/w data £2.00 |
| (CW Data) £2.50 | C7102A-4 (1K static ram) 3 for £1.00 |
| | 4116-4 c/w data £1.75 |
| | Red LEDs 2" 12 for £1.00 |

MISCELLANEOUS

| | |
|---|-----------------------------------|
| 80-way DS .17 pitch edge connectors £3.00 | 14-volt 50-watt zener £1.00 |
| 16-pin DIL 4 p.c. socket £1.00 | DIL relay double pole 2 for £1.00 |
| 25-way D range socket £2.00 | 12 BC107 £1.00 |
| | 12 BC109 £1.00 |

FOR EXTRA SPECIAL OFFERS LOOK OUT FOR OUR STAND AT THE ARRA EXHIBITION AT CASTLE DONNINGTON ON 29th, 30th, 31st OCTOBER BRING THIS ADVERT FOR FREE GIFT

Prices include VAT. Please add 50p p&p S.A.E. for Lists

MAIL ORDER DEPT.
(Callers please phone first)
BOWNESS MILL
SHAWCLOUGH ROAD
WATERFOOT
ROSSENDALE, LANCS
TEL. ROSSENDALE 215556

RETAIL SHOP
(Open 6 days)
6A TODD STREET
MANCHESTER
(next to Victoria Station)
TEL. 061-834 1185

GREENWELD

443A Millbrook Road Southampton SO1 0HX
All prices include VAT @ 15% - Just add 40p post

AMAZING! COMPUTER GAMES

PCBs FOR PEANUTS!!

A bulk purchase of PCBs from several well known computer games including Space-ships, Simons, Logic 5 and Starburst enable us to offer these at incredible low prices:

| | | | | | |
|--------------|-------|--------|--------|---------|------|
| AC176 | 14p | BC547B | 5p | BSY95A | 612p |
| AD181/2 | 45p | BC548 | 5p | BU407 | 60p |
| BC107 | 7p | BC549 | 5p | BC108 | 412p |
| BC108 | 6p | BC556A | 6p | PN109 | 5p |
| BC109 | 7p | BC557A | 6p | TIP30 | 22p |
| BC109C | 6p | BC559 | 6p | TIP31A | 17p |
| BC114 | 5p | BC771 | 11p | TIP41A | 28p |
| BC115 | 5p | BCY72 | 10p | TIP42A | 29p |
| BC117 | 6p | BC131 | 6p | TIP42C | 33p |
| BC119 | 14p | BD132 | 18p | TIP2955 | 46p |
| BC125 | 6p | BD133 | 18p | TIP3055 | 45p |
| BC138 | 14p | BD137 | 20p | TIS43 | 20p |
| BC141 | 16p | BD138 | 20p | 2N1132 | 16p |
| BC143 | 15p | BD139 | 16p | 2N1711 | 18p |
| BC147 | 5p | BD140 | 20p | 2N1893 | 16p |
| BC148 | 5p | BD221 | 35p | 2N2369 | 12p |
| BC149 | 5p | BD222 | 35p | 2N2894 | 12p |
| BC159 | 5p | BD245 | 30p | 2N2904 | 16p |
| BC169 | 5p | BD278 | 28p | 2N2926 | 412p |
| BC172 | 5p | BD525 | 24p | | |
| BC182B | 412p | BD526 | 24p | 2N2926R | |
| BC183 | 412p | BD543 | 30p | | |
| BC183L | 4p | BO95A | 45p | 2N3011 | 14p |
| BC209 | 7p | BD686A | 4p | 2N3055 | 30p |
| BC212 | 412p | BF173 | 13p | 2N3638A | 7p |
| BC212B | 412p | BF181 | 15p | 2N3642 | 6p |
| BC214L (T05) | BF184 | 14p | 2N3645 | 9p | |
| BC237B | 4p | BF194 | 512p | 2N3703 | 412p |
| BC238B | 5p | BF195 | 512p | 2N3704 | 412p |
| BC239B | 5p | BF196 | 512p | 2N3705 | 412p |
| BC239B | 5p | BF197 | 512p | 2N3706 | 412p |
| BC252 | 7p | BF198 | 512p | 2N3710 | 412p |
| BC256 | 6p | BF244 | 18p | 2N4062 | 5p |
| BC207 | 6p | BF257 | 18p | 2N4124 | 7p |
| BC306B | 5p | BF258 | 20p | 2N5226 | 7p |
| BC309 | 5p | BF259 | 20p | 2N4403 | 6p |
| BC317 | 5p | BF324 | 13p | 2N4410 | 6p |
| BC318B | 5p | BF355 | 18p | 2N4418 | 6p |
| BC319B | 5p | BF394 | 512p | 2N5193 | 20p |
| BC320 | 7p | BF414 | 612p | 2N5226 | 7p |
| BC321B | 5p | BF450 | 912p | 2N5226 | 7p |
| BC326 | 7p | BF451 | 3p | 2N5401 | 17p |
| BC348 | 7p | BF757 | 27p | 2N5447 | 6p |
| BC351 | 14p | BFR40 | 17p | 2N5551 | 10p |
| BC413 | 5p | BFY17 | 19p | 2N5831 | 20p |
| BC441 | 19p | BFY54 | 15p | 2N5858 | 7p |
| BC461 | 20p | BFY51 | 13p | 2N6121 | 15p |
| BC485B | 6p | BFY52 | 13p | 2N6290 | 40p |
| BC486A | 6p | BFY64 | 15p | 40673 | 45p |
| BC546B | 6p | BSX20 | 13p | | |

COMPONENT PANELS

AS04 Stack case 50-50-70mm with oval base. PCB accepts test 20V read relay, 200V 7A SCR, 4-5A 200V rect. etc. 08p.
Z529 76 Series ICs - Gates and complete logic. 29 series ICs on pinners £1.50 ICs £4.
Z527 2x20V test relays. 6-250030 or Z5230. 6-400V rect., plus fls. Only 50p.
Z535 RAM panel - 36 2102A-4 static RAM's. also 26 other chips. etc. 7 x L575. 4 x 74368. 3 x 74188, etc. Only £5.
Z536 As above but extra 15 74LS chips etc.

LINEAR, OPTO

TIL311 Residual display with decoder, 0-9 and A-F. 1000 data £1.50.
AD5320 0-A converter. Only £3.50.
FNA3220 2 digit 1/2" 7-seg. display on PCB.
CC. With data £1.98. 7-seg. displays: FND360, 501, all 50c; S38. 847, 850, all £1.50. Regs. T03 chip: 7804 120p, 7805 100p, 7808 100p, 7912 100p, 79CS 220p. Others on B/L 13.
Op-Amps: uA413B 138p; uA776 145p; uA777 30p; uA718 24p.
Isolators: FCD31, 815, TIL118, all 60p.

CAPACITOR BARGAINS

2200uF 100V case 77 x 35mm dia. 75p; 10 - £5.99.
220uF 10V axial 5p; 100 £2.30, 1000 £16.
400 - 100uF 275V 102 x 44mm dia. 75p; 10 £5.99.
200uF 350V, 100 - 100 + 50uF 300V can. 75 x 44mm dia. 40p; 10 - £3; 100 - £20.
100uF 25V axial. £3 - 100.

4 TERMINAL REGS

uA78MG in power mini-dip case 5-30V at 1/2A £1.
uA79MG Negative version of above £1.20.
Only 4 extra components required (50p extra) to make a fully variable supply! Data supplied.

1W AMP PANELS

A011 Compact audio amp intended for record player on panel 95x65mm including vol control and switch, complete with knobs. Apart from amp circuitry built around LM380N or TBA820M, there is a speed control circuit using 5 transistors. 9V operation, connection data supplied. ONLY £1.50.

VU METERS

V006 Very attractive 55x48mm scaled 20 to .5dB. 250uA movement. Only £1.75 or £3 pr.

OP-AMP PSU KIT

A198. All parts + instructions to make a 50mA +15.0. -15V supply from mains input. Only £1.95

COPPER CLAD BOARD

K522. All pieces too small for our etching kits. Mostly double sided fibreglass. 250gm (approx. 110 sq in) for just £1.

JOB LOT OF COMPONENTS

9,500 1N4006; 10,000 .033/50; 22,000 10pF/50; 15,000 .22/12; 11,000 270pF/50; 15,000 88pF/50. 30,000 various resistors. Total 112,500 components for £350 inc VAT & carr.

12 VOLT INDICATORS

Ideal for light chasers, etc. Miniature 12V 75mA wire ended lamps in yellow, red, green, blue and clear. 10p each 20 each colour, total 10p for £5.50. 100 clear only £4.50.

EPROMS

INTEL 2716-1 £3.00
FAIRCHILD 2708 £3.00
T.I. 2516-45 £3.00

THE SPECTACULAR 1981 GREENWELD Component Catalogue

- Bigger and better than ever!!!
- ★ 60p discount vouchers
- ★ First Class reply paid envelope
- ★ Free Bargain List
- ★ Priority Order Form
- ★ VAT inclusive prices
- ★ Quantity prices for bulk buyers
- ★ Free Data Sheet

SEND 75p FOR YOUR COPY NOW!!

ODDS AND ENDS

Transformer, mains in, 1770V 10mA out £2.50.
W847 PCB mntg. relay 11 x 33 x 20mm. 37R 5-10V SP00 3A 95p.
90145 Picking DIL relay 500R, SP make. 3.7-10V, ex-equip. on PCB, 75p.
X905 140 x 10mm ferrite rod with EW and MW windings, 45p.
K520 Switch pack - 20 different, rocker, slide, rotary, toggle, push, micro, etc. Only £2.
K521 Heatshrink pack - 5 diff. sizes, each 200mm, 50p.
10M 1/2W 5% CF Resistors - pack of 200, £1.
40W amp PCB + CCT + layout. £1. All parts to make, £3.50.
1% 1/2W Rs - 111k, 333k, 500k, 900k, 950k. All 10p/25p.

TV TEST GEAR

Wobulators, Calibration Gens., Modulators, Sync. Generators Encoders, Converters, etc. All cheap. SAE List.

VDU CRTS


Approx. 250 12" and 15" 110" tubes available for callers only. All £15 each.

For your FREE Catalogue
Send 30p to cover P&P

NEW DISTRIBUTORS WANTED

Quality Two Part DIN 41612
& Min 'D' Connectors.

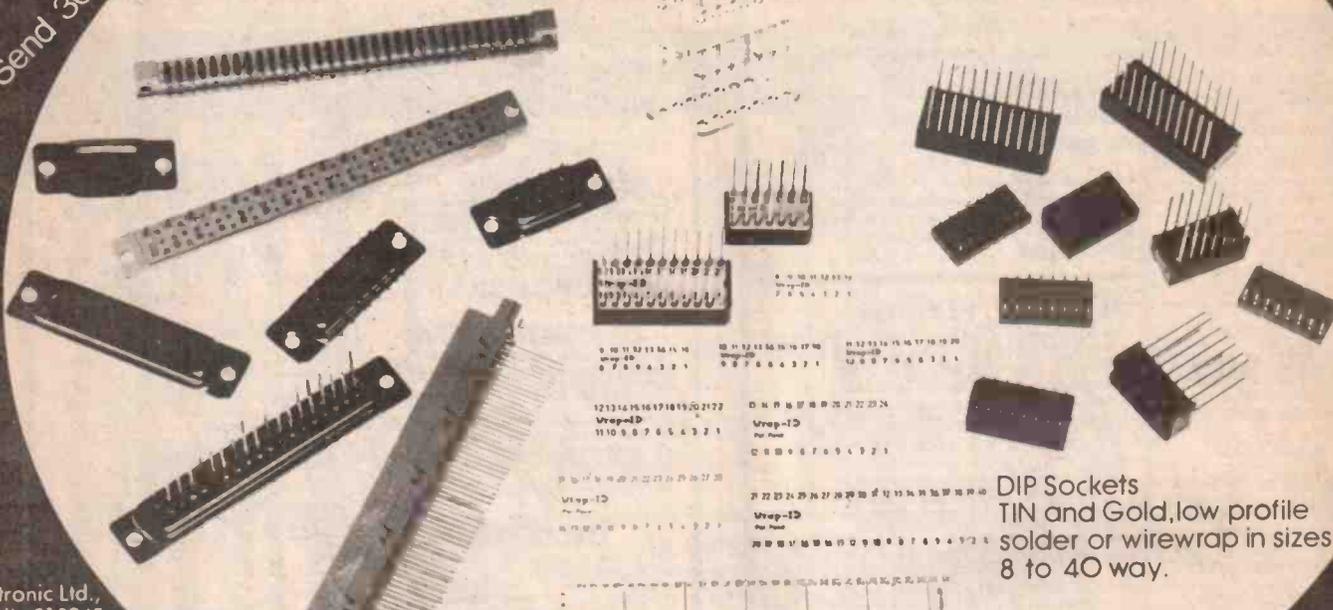Wrap ID Eliminate Errors
for instant locking-numbering
& identifying DIP Sockets



DIP Sockets
TIN and Gold, low profile
solder or wirewrap in sizes
8 to 40 way.

ELECTROWARE*

DUTTON LANE EASTLEIGH SO5 4AA TEL(0703)610944/5

AVAILABLE FROM ALL LEADING ELECTRONIC DISTRIBUTORS

Neltronic Ltd.,
Dublin 510845
Cobbles Ltd.,
London. 01-699-2282
Microdigital Ltd.,
Liverpool. 051-227-2535
Electronico CG Ltd.,
Manchester. 061-788-0656

Spectron Electronics (Manchester) Ltd.,
Salford. 061-834-4583

Jee Distribution Ltd.,
Middlesex. 01-897-3429

Watford Electronics Ltd.,
Watford. 0923-37774

Technomatic Ltd.,
London. 01-452-1500

Transam,
London. 01 405 5240
A. Morshall (London) Ltd.,
London. 01-624-0805
Interface Components Ltd.,
Amersham. 02403-22307
New Bear Computing Store Ltd.,
Newbury. 0635-30505

* A DIVISION OF OK MACHINE & TOOL UK LIMITED

ETI PROJECT KITS FROM MAGENTA ELECTRONICS LTD

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.T.I. Projects. We supply carefully selected sets of parts to enable you to construct E.T.I. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or veroboard are, of course, included as specified in the original article, we even include nuts, screws and IC sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.T.I. which includes the project you will need to order the instruction reprint as an extra 45p each.

Reprints available separately 45p each + p&p 40p

| | |
|--|--------------|
| BNLARGER TIMER Oct '81 | £26.59 |
| SOUND BENDER Oct '81 | £20.76 |
| MICROPOWER THERMAL ALARM Oct '81, less case | £9.88 |
| MICROPOWER PENDULUM Oct '81 less case | £5.54 |
| MAINS AUDIO LINK, Sept. '81 | £49.98 |
| LAB PSU, Sept. '81. Less case | £37.98 |
| WATCHDOG HOME SECURITY SYSTEM, Aug. '81 | £43.33 |
| Rechargeable battery | £20.98 extra |
| HEARTBEAT MONITOR, Aug. '81 | £26.26 |
| HANDCLAP SYNTHESIZER, Aug. '81 | £29.98 |
| FLASH SEQUENCER, Aug. '81. Less flash sockets | £35.65 |
| SMART BATTERY CHARGER, July '81 | £31.98 |
| WAH PHASE, June '81. Less pedal | £13.44 |
| LED JEWELLERY, June '81, Cross £2.47 Spiral £7.20 Star £9.41 | |
| ALIEN ATTACK, Jan. '81 | £19.76 |
| ANTENNA EXTENDER, June '81 | £21.68 |
| MINI DRILL SPEED CONTROLLER, June '81 | £25.13 |
| DIGITAL CLOCK, May '81 (round leds) | £43.97 |
| CARAVAN LIGHTS CHECKER, April '81, less glue | £10.16 |
| GUITAR NOTE EXPANDER - ETI, April '81 | £16.47 |
| DRUM MACHINE, April '81 | £65.94 |
| MUSICAL BOX, April '81 | £12.54 |
| ENGINEERS STETHOSCOPE, Mar '81 | £19.19 |
| SOUND PRESSURE LEVEL METER, Feb. '81 | £45.75 |
| PULSE GENERATOR, Feb. '81 less case | £35.33 |
| Case extra | £27.47 |
| INFRA RED ALARM, Feb. '81 | £54.98 |
| UNIVERSAL TIMER, Jan. '81 | £31.77 |
| MULTI-OPTION SIREN, Jan. '81 | £26.91 |
| LED TACHO, Jan '81. Less case | £34.77 |
| 4 INPUT MIXER, Dec. '80 | £19.77 |
| BENCH AMPLIFIER, Dec. '80 | £23.95 |

| | |
|---|--------|
| MUSICAL DOORBELL, Dec. '80 | £11.61 |
| AUDIO TEST OSCILLATOR, Nov. '80 | £18.30 |
| RIAA PRE-AMP (stereo), Nov. '80 | £6.83 |
| 2W POWER AMP, Nov. '80 | £6.09 |
| METRONOME, Nov. '80 | £5.98 |
| LIGHT SWITCH, Nov. '80 | £8.54 |
| TOUCH BUZZER, Nov. '80 | £6.11 |
| SUSTAIN/FUZZ BOX, Oct. '80 | £24.99 |
| CASSETTE INTERFACE, Oct. '80. Less case | £11.57 |
| ULTRASONIC BURGLAR ALARM, Aug. '80 | £26.82 |
| CAPACITANCE METER, Aug. '80 | £20.26 |
| CMOS LOGIC TESTER, Aug. '80 | £10.97 |
| SIGNAL TRACER, Mar. '80 | £11.98 |
| TUNING FORK, Feb. '80 | £14.82 |
| ACCENTUATED BEAT METRONOME, Jun. '79 | £17.90 |
| CLICK ELIMINATOR, April '79 less case | £46.57 |
| Case extra | £14.98 |
| GUITAR EFFECTS UNIT, April '79 | £14.78 |
| COMPLEX SOUND GENERATOR, Oct. '78. Less case | £21.97 |
| TELEPHONE BELL EXTENDER, Oct. '78. Less speaker | £16.47 |

The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

The instructor is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the instructor and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk. 2. Circuits are built on a plug in Euroboard. Kit includes Euroboard £27.85, or less Euroboard £21.65.
INSTRUCTOR COURSE NOTES AND OPERATING INSTRUCTIONS - EXTRA £2.96

MAGENTA ELECTRONICS LTD.

ET6, 135 HUNTER STREET, BURTON-ON-TRENT, STAFFS, DE14 2ST
0283-65435. 9-5 MON.-FRI. MAIL ORDER ONLY

ALL PRICES INCLUDE VAT
ADD 40p P&P TO ALL ORDERS
S.A.E. WITH ALL ENQUIRIES PLEASE

Irish Republic & B.F.P.O. Europe deduct 10% from prices shown. Payment must be in sterling.



Accepted Barclaycard (Visa) orders accepted by phone or post.

1981 ELECTRONICS CATALOGUE

KITS
ICs
TRANSISTORS
CAPACITORS

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery.
Send 70p in stamps or add 70p to your order.

TOOLS
RESISTORS
HARDWARE
CASES

TTL CMOS 74LS LEDs

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

SUPERSALE 81
All full spec. 2114 (450ns) £1.20, 8 of £9.00. P&P 35p. 2708 £1.85 p&p 35p. TEXAS INSTRUMENTS £7.16 single rail full spec. £3.80, ITT 4116 (200ns) £1.35, 8 for £1.15 each. Texas 4116 (1250ns) £1, p&p 35p.

Shugart 8" drives 5 x 115 volts 50 Hz. Model 900-4 complete with read write p.c.b., 24 volt stepper. Supplied in good serviceable condition. From £45-£75 (depending on condition). Callers only.
Switched mode PSU plus 12V, minus 12V, Plus 5V about 20 amps as new, no data £29.50 Callers only MK 1002P (dual 128 bit Shift Reg) 35p.

UA710DC 14 bit 22p, 6 for £1, p&p 30p. (All Full Spec)
2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 35p.
MM5240 AA/J Character Generator £3.50 + data, p/p 35p.
LEAR SIEGLER dot matrix print-head, 7 needle, £19.50 p/p 50p.
ZETTLER low profile PCB relay 30mm x 36mm, 4/8/6.9v d.c. 2/2.5 amps a.c. contacts. 85p p/p 35p.

D TYPE CONNECTORS
9 Way: sockets (solder) 55p.
15 Way: wirewrap plugs only 75p.

15 Way Plugs 85p.
15 Way Sockets 70p.
50 Way Plug £1.65
50 Way: skt (wirewrap) £1.65.
50 Way: skt £1.45, p&p 25p.
25 Way plug (soldercaill), 25 Way socket £1.50 each.

COVERS
37 Way: 90p (plastic), p&p 35p.
9 Way (metal) 60p, 15 Way (metal) 95p, 25 Way (open metal) 85p, 37 Way reduced from 90p to 80p. 50 Way (plastic) 90p.

DISPLAYS
HP 5082/7414 4 digit DIL display full spec £1.50 each, p&p 35p. Large quantities POA.
LED 3 Digit DIL 55p, p&p 35p.

HP5082/7650 4" cc, left and right decimal point, high brightness (unmarked), only 50p, 12 for £5, p&p 35p.

SUPERSAVER 1
Ribbon Cable Headers 16 DIL Jermyn, gold-plated, with cover 45p, o&p 25p.
Anslay Header plugs. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation piercing type) p/p 35p.

Anslay I/O Header plugs PCB Mounting 1in 26 Way 65p, 26 Way (right-angled) 85p, 40 Way £1 p/p 35p. **SUPERSAVER 2**
Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.

SUPERSAVER 3
PRICE SMASH FND500 5in. LED displays, full spec 50p each, p&p 35p, large quantities POA. **SUPERSAVER 5**
Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.

SUPERSAVER 6
EAO KEY SWITCH oblong fascia, 25mm x 18mm (approx. 18mm hole), fixing supplied, brand new with 2 keys. £2.95 p&p 35p.

SUPERSAVER 7
Thyristors Type 16 Ria 100 Vrrm 1000 Volts at 22 amps £1.65 each. Limited stock, p/p 35p.
Stud mounted rectifiers, type 40 HF 100 1250 volts, 450 amp, 4 for £2.50 p/p 35p.

SUPERSAVER 8
ITT 4cx 250b brand new full spec £7.50 each p&p 35p.
SUPERSAVER 9
5 digit 7 segment DIL LED. 11" displays 5 for £1.50 p/p 35p.

SUPERSAVER 10
Tangerine Microtram 65 PCB Brand new plus circuit diagram £4.50 p/p 50p (Limited quantity).

SUPERSAVER 11
74LS266 50p. 74LS245 £2.00. 74LS240 60p. 74S260 35p. P&P on all above 35p.

SUPERSAVER 12
2.5 power plug and 2 metres of cable. Only £1.00 for 10 p/p 25p. Trade enquiries welcome.

SUPERSAVER 14
BOX FANS 115V 50/60Hz. 120mm x 120mm. New. £4.50. P/P £1.00.

SUPERSAVER 15
5K 3/4" multitrn trimpots, PCB mounting, per box of 14 £2.50. As above 1K and 50K, p&p 35p.

SUPERSAVER 16
OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1, p&p 35p.

SUPERSAVER 17
VU METER 48mm x 50mm approx. overall size. Face size 50mm x 28mm approx. Brand new. £1.15 p&p 30p. (Sent at purchaser's risk).

SUPERSAVER 18
PCB AMP (LM380). Unused. 65mm x 95mm approx. 9-12v DC. £1.35 p&p 35p.

SUPERSAVER 19
10 DIGIT (Red). LED display. (1.22in. digit size). With built-in driver chip and built-in lens magnifier. Data sheet supplied. Brand new. £2.50 p&p 35p.

SUPERSAVER 20
4 1/2in. JUMPER LEAD. 16 DIL header to 16 DIL header. 95p p&p 30p.

SUPERSAVER 21
2 1/2in. JUMPER LEAD. 14 DIL header to 14 DIL header. 65p p&p 30p.

SUPERSAVER 22
11b reel of solder 18 SWG 64/36 alloy £6.50 p&p 90p.

A SUMMER GIVEAWAY. 280
PIO. Only £3.75 p&p 35p. MC1489 Brand new 46p each. Large quantities P.O.A. p&p 30p.

NICADS AA SIZE - 500 MAH 1-25v rechargeable 50 milliamp 12-15 hours, £1.44, P&P 35p.

TMS 4030, 4096 x 1 dynamic RAM 200 ns removed from PCBs. 65p each. 16 for £8, p&p 35p.

GPO LINE MATCHING TRANSFORMER. With 12V reed relay etc. removed from equipment. £1 + 40p p&p.

CAPACITOR SCOOP. 1.600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 + 35p p&p.

DON'T KILL YOUR EPROMS. Augat 24 Way low profile socket. Solid gold pins. A superb socket. Leave your eproms in them for programming or usage to prevent breaking off pins. Only 40p each, p&p 35p.

GIVEAWAY 18 pin low profile dill socket 13p EACH or 8 for £1

AUGAT IC SOCKETS
(The best available)

16 Dill 20p 24 Dill 40p
18 Dill 25p 40 Dill 55p
20 Dill 30p p&p 35p

WE STOCK a vast range of TTL, CMOS, some 74LS, MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

NEW LINES
GUEST (gold plated) IC test clip. 40 way, 28 way £4.50 per pair. P/P 50p.

REG PCB (less components), 5V 1amp, 12V 1amp and heatsink (60mm x 90mm). Brand new, £1.00. Heatsink only, 55p. P/P 35p.

NEC FIP4B13 4 digit glass display (green with centre colons and plus and minus sign), only £1.35. P/P 30p.

PL259 SOCKET CHASSIS MOUNT. 50p p&p 30p.

TRANSFORMERS 012, 024 1 amp £2.50, P&P 50p.
TTL SALE. 7410 9p, 7413 18p, 7416 18p, 7490 28p, 74155 45p, 74174 60p, 74181 80p, 74284 28p, 74285 £2.25. P&P 35p.

WHY PAY POUNDS? - Just arrived Amphenol 36-way plug and socket (used) to fit all your printer. Only £2.75 per pair. P/P 35p.

Terms cash with order (official orders welcomed from colleges, etc). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

STOP PRESS
MK4027 (or equivalent) 250NS £1 each, 8 for £6 p/p 35p

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.
SURPLUS STOCKS

PURCHASED FOR CASH

LB ELECTRONICS
11 HERCULES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND
All enquiries s.a.e. please

Telephone answering machine service out of business hours.
New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.

ALL PRICES INCLUSIVE OF VAT
UXBRIDGE 55399
All components full spec

NAMAL ASSOCIATES

No. 1 CLAYGATE ROAD; CAMBRIDGE CB1 + JZ
Tel. 0223 248257 TLX 817445

| | | | | | | |
|-----------------------|-------|-------------------|------|--------------------|------|-----|
| COMPUTER I.C.s | 7408 | .13 | 4526 | .72 | 92 | .35 |
| 2144-450 | .99 | 7414 | .29 | 4527 | .99 | 93 |
| 2114-200LP | .99 | 7420 | .12 | 4528 | .77 | 95 |
| 2532 | 4.90 | 7442 | .33 | 4532 | .88 | 109 |
| 2708 | 2.50 | 7448 | .38 | 4541 | 1.12 | 112 |
| 2716 | 1.95 | 7474 | .20 | 4543 | 1.12 | 113 |
| 2732 | 5.25 | 7486 | .20 | 4555 | .40 | 114 |
| 4116-450 | .95 | 7490 | .21 | 4556 | .45 | 122 |
| 4116-200 | .95 | 74107 | .20 | 4558 | 1.02 | 123 |
| 5516 2K x 8 | 11.00 | 74151 | .26 | 74LS SERIES | | |
| 6800 | 3.25 | 74159 | .58 | 00 | .10 | 125 |
| 6802 | 4.25 | 74167 | 1.15 | 01-04 | .12 | 126 |
| 6809 | 8.75 | 74172 | 2.75 | 05 | .14 | 132 |
| 6810 | 1.30 | 74178 | .43 | 08-13 | .12 | 136 |
| 6821 | 1.70 | 74179 | .43 | 14 | .42 | 138 |
| 6845 | 9.75 | 74184 | .90 | 15-22 | .12 | 145 |
| 6850 | 1.60 | 74185 | .90 | 26 | .16 | 148 |
| 8080A | 2.20 | 74198 | .55 | 27 | .12 | 151 |
| 8085A | 6.50 | 74199 | .56 | 28 | .16 | 153 |
| 8224 | 2.20 | 74273 | .80 | 30 | .12 | 155 |
| 8228 | 4.00 | 74278 | .88 | 32 | .12 | 154 |
| 8255 | 3.90 | 74284 | 1.44 | 33 | .16 | 156 |
| Z89 CPU | 3.75 | 74351 | .87 | 37 | .15 | 157 |
| Z80ACPU | 4.85 | C-MOS 4000 | | | | |
| Z80 PIO | 3.80 | 4000 | .11 | 40 | .12 | 160 |
| Z89APIO | 4.00 | 4001 | .11 | 42 | .35 | 161 |
| Z80 CTC | 4.60 | 4011 | .12 | 47 | .40 | 162 |
| Z89ACTC | 4.78 | 4013 | .32 | 48 | .65 | 133 |
| Z80ASIO | 12.00 | 4016 | .25 | 49 | .60 | 164 |
| VOLTAGE REGU: | 4020 | .64 | 51 | .12 | 166 | |
| 7805 5V + | .48 | 4024 | .36 | 54 | .14 | 173 |
| 7812 12V + | .48 | 4047 | .76 | 55 | .12 | 174 |
| 7815 15V + | .48 | 4060 | .85 | 73 | .21 | 175 |
| 7824 24V + | .50 | 4093 | .40 | 74 | .16 | 181 |
| 7905 5V + | .58 | 4099 | 1.20 | 75 | .25 | 190 |
| 7912 12V + | .58 | 4508 | 2.22 | 76 | .20 | 191 |
| 7915 15V + | .58 | 4514 | 1.50 | 78 | .20 | 192 |
| 7924 24V - | .58 | 4516 | .70 | 83 | .45 | 193 |
| Standard TTL's | 4518 | .70 | 85 | .70 | .40 | 194 |
| 7400 | .12 | 4520 | .70 | 86 | .15 | 195 |
| 7401 | .12 | 4521 | 1.60 | 90 | .30 | 196 |
| 7404 | .13 | 4522 | 1.20 | 91 | .78 | 197 |

| | | | | | | | |
|---------------------|------|-----------------|------|---------------------|------|--------|------|
| 221 | .55 | LM706 | .65 | 6,144MHz | 1.25 | BUX84 | 1.40 |
| 240 | .98 | LM723 | .45 | 6,400MHz | 1.50 | FVP1 | 4.50 |
| 241 | 1.10 | LM726 | 6.75 | 10,000MHz | 1.50 | MJE702 | .30 |
| 242 | .80 | LM733 | .70 | 18,000MHz | 1.50 | MJE703 | .30 |
| 244 | .68 | LM741 | .20 | 20,000MHz | 1.50 | MJE800 | .35 |
| 245 | 1.10 | LM747 | .40 | I.C. SOCKETS | | | |
| 247 | .37 | LM760 | 2.90 | 8 PIN | .08 | MJE801 | .35 |
| 248 | .68 | MC1314 | 3.00 | 14 PIN | .09 | TIP110 | .35 |
| 249 | .68 | MC1405 | 5.75 | 16 PIN | .10 | TIP111 | .40 |
| 257 | .52 | MC14512 | .60 | 18 PIN | .14 | TIP116 | .40 |
| 259 | 1.00 | MC14515 | 1.00 | 20 PIN | .15 | TIP29 | .28 |
| 261 | 3.00 | MC14516 | .68 | 22 PIN | .18 | VN46AF | 1.20 |
| 273 | .78 | MC14526 | .68 | 24 PIN | .20 | 2N1131 | .08 |
| 290 | .55 | MC14528 | .68 | 28 PIN | .26 | 2N1525 | .28 |
| 373 | .75 | MC14543 | .80 | 40 PIN | .30 | 2N2218 | .12 |
| 374 | .75 | MC14553 | 2.50 | TRANSISTORS | | | |
| 377 | .90 | MC14555 | .40 | BC141/10 | .18 | 2N2258 | .09 |
| 378 | .70 | MC1461G | 1.09 | BC161/10 | .18 | 2N2483 | .13 |
| 390 | .62 | MC1494L | 4.25 | BD139/10 | .18 | 2N3054 | .43 |
| 393 | .55 | MC1489P | .57 | BD140/10 | .18 | 2N3325 | .15 |
| Linear I.C's | | | | BD441 | .25 | 2N3415 | .09 |
| LM324 | .30 | 81LS95 | 1.18 | BD442 | .25 | 2N3771 | 1.20 |
| LM325 | 1.88 | 81LS96 | 1.22 | BD679 | .45 | 2N3773 | 1.70 |
| LM326 | 1.25 | 81LS97 | 1.18 | BD680 | .45 | 2N3819 | .30 |
| LM327 | 1.43 | 81LS98 | 1.25 | BD245 | .48 | 2N3829 | 1.70 |
| LM329 | 2.10 | 8T26A | 1.45 | BD249 | .80 | 2N4060 | .09 |
| LM3342 | 1.00 | 8T28A | 1.48 | BD250 | .80 | 2N4347 | .65 |
| LM3362 | 1.25 | 8T95N | 1.48 | BD346 | .55 | 2N4427 | .50 |
| LM337K | 3.40 | 8T97N | 1.48 | BD378 | .22 | 2N458A | 1.00 |
| LM337P | 1.00 | 8T98 | 1.48 | BF679 | .40 | 2N4871 | .25 |
| LM338K | 4.75 | Crystals | | | | 2N4901 | .82 |
| LM339 | .40 | 32.768kHz | .98 | BF926 | .28 | 2N4910 | .40 |
| LM341-P-1 | 8.50 | 1000MHz | 3.00 | BF979 | .60 | 2N5050 | 1.65 |
| LM342P-1 | 5.50 | 2000MHz | 2.82 | BFW92 | .28 | 2N5179 | .48 |
| LM348 | .60 | 2.562MHz | 3.25 | BSW45 | .09 | 2N5193 | .40 |
| LM350 | 3.80 | 3.276MHz | 1.00 | BSY51 | .09 | 2N5248 | .30 |
| LM3524N | 2.75 | 3.579MHz | 1.00 | BU100A | 1.00 | 2N5296 | .40 |
| LM358 | .40 | 3.932MHz | 1.00 | BU111 | .90 | 2N5378 | .12 |
| LM372 | .60 | 4,000MHz | 1.58 | BU137A | 1.75 | 2N5458 | .38 |
| LM543 | 2.60 | 4,194MHz | 1.85 | BU204 | .90 | 2N5492 | .28 |
| LM555 | .40 | 4,433MHz | .85 | BU205 | .90 | 2N5591 | 5.40 |
| LM565 | .90 | 4,000MHz | 1.85 | BU207 | .80 | 2N5648 | 1.00 |
| LM567 | .85 | 5,120MHz | 1.08 | BU208 | .80 | 2N5945 | 8.90 |
| LM703 | .30 | 6,000MHz | 1.95 | BU311 | .70 | 2N5956 | .85 |
| | | | | BUX28 | 2.40 | 2N6080 | 3.40 |

WE GUARANTEE:- Factory Prime Parts - Competitive Prices - In Depth Stocks
FREE PRICE LIST - Please send SAE (20p in U.K.)
Minimum Order £10.00. Please add P&P .50p and V.A.T.
Government and Colleges etc orders welcome

JOIN THE PROFESSIONALS...

If you are looking for amplification, take advantage of the same superb quality Crimson modules that the BBC, IBA, KEF and numerous recording studios have been using for years! Our expertise in this field of electronic design is internationally renowned, our reputation is based on quality, reliability and value for money and when it comes to technology, our modules feature possibly some of the world's most advanced audio circuitry yet devised. The Crimson range of audio amplifier modules is available to industry and public alike and is backed by full technical data, free technical advisory service, fast delivery and a full range of complimentary components available such as toroidal power supplies and heatsinks, etc.

SPECIFICATIONS

| Type | O/P 8 ohms* | O/P 4 ohms | PSU | H/sinks | Slew limit | S/N | Sensitivity | TMD (typ) | FR1 - 3dB | Size |
|--------|----------------|---------------|--------|---------------|---------------|-------|-------------|-----------|-------------|------------|
| CE 608 | 32 | — | CPS 80 | H550 | 30Vu5 | 110dB | 775mV | 0.0035% | 1.5Hz-50KHz | 80-120-25 |
| CE1004 | 44 | 70 | CPS150 | H550/100 | 30Vu5 | 110dB | 775mV | 0.0035% | 1.5Hz-50KHz | 80-120-25 |
| CE1006 | 65 | — | CPS150 | H550/100 | 30Vu5 | 110dB | 775mV | 0.0035% | 1.5Hz-50KHz | 80-120-25 |
| CE1704 | 85 | 121 | CPS250 | H5100/150/FM1 | 30Vu5 | 110dB | 775mV | 0.0035% | 1.5Hz-50KHz | 80-120-25 |
| CE1708 | 125 | — | CPS250 | H5100/150/FM1 | 30Vu5 | 110dB | 775mV | 0.0035% | 1.5Hz-50KHz | 80-120-25 |
| CE3004 | 170 | 250 | CPS250 | H5150/FM2 | 30Vu5 | 110dB | 775mV | 0.008 % | 1.5Hz-50KHz | 161-102-35 |
| CPR1X | OUTPUT | 775mW | REG1 | — | 3Vu5 | 70dB | 2.8mV | 0.008 % | 10Hz-50KHz | 138-80-35 |
| MC1X | OUTPUT | 2mW | REG1 | — | 3Vu5 | 65dB | 70/150uV | 0.008 % | 10Hz-50KHz | 80-120-35 |
| XO2/3 | OUTPUT | 775-2500mW | REG1 | — | 9Vu5 | 90dB | 775mV | 0.01 % | Preset | 150-50-20 |

*Power output is quoted at 1000Hz and is given for two modules off the same power supply. Higher powers can be obtained if using our dual power supplies or one module per PSU or if using a stabilised power supply.

Crimson modular audio amplifiers feature:
 • low values of transient and steady state distortions • envelope distortion (below 500 Hz) less than 0.03% • on board electronic protection • PCB pin and edge connector termination • full range of complimentary components available ie. PSUs, heatsinks, etc.

NEW: We now have a completely new Hi-Fi Kit package to offer:
 CK 1010 contains CPR1X, all metalwork connectors wire, etc., to make a complete pre-amp.

CK 1040 contains 2 x 608s, all metalwork dual power supply, connectors, heatsinks, wire, etc., to make a complete 40 w/channel power amp.

CS 1100 as CK 1040 but at 100 w/channel

Unlike other module manufacturers CRIMSON have a major share of the esoteric, specialist Hi-Fi market. Unlike many manufacturers we acknowledge the massive audible differences that small component/circuit changes can produce. However our amplifiers are technically outstanding have been subjectively 'tuned' to a stunning level of crisp and detailed reproduction.

PRICES

Power amp modules

| | | |
|--------|--------|--------|
| CE 608 | £21.00 | CPS80 |
| CE1004 | £24.50 | CPS150 |
| CE1006 | £27.50 | CPS150 |
| CE1704 | £35.00 | CPS150 |
| CE1708 | £35.00 | CPS250 |
| CE3004 | £49.00 | CPS250 |

Pre amp modules

| | | |
|-------|--------|-------------------|
| CPR1X | £36.00 | Active crossovers |
| MC1X | £32.00 | XO2 |
| REG1 | £ 9.30 | XO3 |
| TR6 | £ 3.30 | MU1 |

Power supply modules

| | | |
|--------|--------|-------|
| CPS80 | £26.24 | H5 50 |
| CPS150 | £31.77 | H5100 |
| CPS150 | £29.74 | H5 50 |
| CPS150 | £36.40 | FM1 |
| CPS250 | £36.83 | FM2 |
| CPS250 | £45.34 | |

Heatsinks

| | |
|-------|--------|
| H5 50 | £ 1.84 |
| H5100 | £ 2.99 |
| H5 50 | £ 4.20 |
| FM1 | £36.95 |
| FM2 | £41.52 |

All prices include VAT. Please add £1.10 for orders up to £20.00, £2.50 up to £50 and £2.65 £50 and over. To allow for post and packing (UK only).

Export—No problem. Please write for quotation or quote your Visa/Master-Charge card number.

COMPLETE KITS

| | |
|---------------------|---------|
| PRE-AMP CK1010 | £90.00 |
| POWER AMP CK1040 | £119.00 |
| POWER AMP CK1100 | £149.00 |
| (MOVING COIL ADD-ON | £25.00) |



Please send more details of all CRIMSON ELEKTRIK amplifier modules

Name _____
 Address _____
 Ref: ET/11

Crimson Elektrik

9 Claymill Road, Leicester LE4 7JU • Tel 0533 761920 • Telex 34964 Chamco G Crimlek

Lost in the Hi Fi Jungle?

Phone Wilmslow 526213

for an expert guide to the territories of:

A&R **Dual** **MISSION ELECTRONIC** **PIONEER**

AIWA **HITACHI** **OPTONICA** **Sansui**

Plus

ARISTON • AKA • B & W • CELESTION • GRADO • JR
 KEF • MONITOR AUDIO • NAGAOKA • ORTOFON
 ROGERS • THORENS • TRIO • VIDEOTONE

The Excellent New CJ-55 TURNTABLE

Sensible advice from expert staff

3 years guarantee on Hi Fi

Service Department on Premises

Very competitive prices

SWIFT
OF WILMSLOW

5 Swan Street, Wilmslow,
Cheshire Telephone 0625 526213

| TTL | 17157 | 45p | 4518 | 45p | LS161 | 45p | BF337/8 | 38p | MICROS | |
|-------|-------|--------|------|------|-------|-------|---------|----------|--------|------|
| 7400 | 10p | 74180 | 54p | 4520 | 65p | LS164 | 45p | BF80 | 2102 | 105p |
| 7402 | 10p | 74161 | 54p | 4543 | 115p | LS174 | 58p | BFX29 | 2114 | 145p |
| 7403 | 14p | 74164 | 64p | 4555 | 40p | LS175 | 58p | BFX84/5 | 4116-3 | 210p |
| 7404 | 14p | 74174 | 70p | | | LS221 | 64p | BFX87/8 | 2420 | 210p |
| 7407 | 24p | 74175 | 70p | | | LS241 | 85p | BFY50/2 | 2708 | 210p |
| 7410 | 14p | CMOS-B | | | | LS242 | 85p | BRV35 | 2716 | 375p |
| 7413 | 25p | 4001 | 12p | | | LS244 | 85p | BSX20 | 8080A | 400p |
| 7414 | 30p | 4002 | 12p | | | LS245 | 85p | BU205 | | |
| 7416 | 25p | 4011 | 14p | | | LS246 | 85p | BU208 | | |
| 7420 | 14p | 4012 | 18p | | | LS247 | 85p | TIP31/2A | DL704 | 95p |
| 7426 | 28p | 4013 | 33p | | | LS248 | 85p | TIP41/2A | DL707 | 95p |
| 7430 | 15p | 4016 | 28p | | | LS249 | 85p | 2N3055 | | |
| 7441 | 34p | 4017 | 50p | | | LS250 | 85p | 2N3055 | | |
| 7442 | 34p | 4023 | 19p | | | LS251 | 85p | 2N3055 | | |
| 7447 | 45p | 4024 | 39p | | | LS252 | 85p | 2N3055 | | |
| 7451 | 16p | 4027 | 27p | | | LS253 | 85p | 2N3055 | | |
| 7473 | 26p | 4029 | 75p | | | LS254 | 85p | 2N3055 | | |
| 7474 | 25p | 4046 | 60p | | | LS255 | 85p | 2N3055 | | |
| 7476 | 25p | 4046 | 70p | | | LS256 | 85p | 2N3055 | | |
| 7486 | 25p | 4049 | 28p | | | LS257 | 85p | 2N3055 | | |
| 7490 | 28p | 4050 | 28p | | | LS258 | 85p | 2N3055 | | |
| 7492 | 35p | 4051 | 62p | | | LS259 | 85p | 2N3055 | | |
| 7493 | 30p | 4052 | 62p | | | LS260 | 85p | 2N3055 | | |
| 74107 | 26p | 4053 | 62p | | | LS261 | 85p | 2N3055 | | |
| 74109 | 35p | 4055 | 95p | | | LS262 | 85p | 2N3055 | | |
| 74121 | 28p | 4060 | 85p | | | LS263 | 85p | 2N3055 | | |
| 74123 | 35p | 4069 | 16p | | | LS264 | 85p | 2N3055 | | |
| 74141 | 45p | 4081 | 22p | | | LS265 | 85p | 2N3055 | | |
| 74151 | 40p | 4082 | 22p | | | LS266 | 85p | 2N3055 | | |
| 74153 | 40p | 4511 | 55p | | | LS267 | 85p | 2N3055 | | |

MAIL ORDER, CWO Add 35p P&P, VAT 15% Many more items in stock. Send SAE for full price list. 10% DISCOUNT ON ORDERS OVER £20

AUDIO VIDEO SERVICES
 19 GALS WORTHY AVENUE
 ROMFORD RM6 4PX. 01-599 6680

TV SOUND TUNER ETI SEP 80 PROJECT

All parts available / send for list

ALSO

**No. 1 for Teletext Kits
 TV Spare Parts and Components**

Callers welcome at Shop Premises

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD
 TELEPHONE: 01-794 8751

Near West Hampstead Jubilee & British Rail Stations

MICRO TIMES

19 Mill St., Bideford, North Devon
EX39 2JR, England
Telephone Bideford (023 72) 79798

INTRODUCING CMOS AND TTL

see below for micro prices

| CMOS | THYRISTORS |
|------|------------|
| 4001 | 12p |
| 4002 | 12p |
| 4006 | 68p |
| 4007 | 13p |
| 4008 | 60p |
| 4010 | 36p |
| 4011 | 12p |
| 4012 | 18p |
| 4013 | 33p |
| 4014 | 80p |
| 4015 | 62p |
| 4016 | 28p |
| 4017 | 53p |
| 4018 | 58p |
| 4019 | 36p |
| 4020 | 85p |
| 4023 | 18p |
| 4024 | 38p |
| 4025 | 14p |
| 4026 | £1.28 |
| 4027 | 35p |
| 4028 | 62p |
| 4029 | 70p |
| 4030 | 48p |
| 4031 | £1.95 |
| 4040 | 66p |
| 4042 | 55p |
| 4044 | 60p |
| 4046 | 74p |
| 4047 | 78p |
| 4048 | 44p |
| 4049 | 27p |
| 4050 | 27p |
| 4051 | 60p |
| 4052 | 60p |
| 4056 | £1.50 |
| 4060 | 86p |
| 4063 | £1.18 |
| 4066 | 36p |
| 4068 | 18p |
| 4069 | 15p |
| 4070 | 22p |
| 4071 | 18p |
| 4075 | 20p |
| 4077 | 22p |
| 4078 | 20p |
| 4081 | 18p |
| 4093 | 42p |
| 4503 | 65p |
| 4510 | 68p |
| 4511 | 51p |
| 4518 | 70p |
| 4520 | 70p |
| 4560 | £2.20 |
| 4572 | 30p |

50p OFF VOUCHER

When £5 plus order of CMOS, TTL or LINEAR is placed. Return Voucher with order. ETI/VN

| | | | |
|---------|-------|----------|-------|
| 74LS157 | 35p | LM358P | 38p |
| 74LS161 | 42p | LM390 | 65p |
| 74LS163 | 42p | LM3900N | 45p |
| 74LS164 | 50p | LM3914 | £2.00 |
| 74LS173 | 75p | LM3915 | £2.00 |
| 74LS174 | 77p | LM13600 | £1.20 |
| 74LS175 | 58p | SN76477N | £1.75 |
| 74LS221 | 63p | UA709 | 28p |
| 74LS244 | 83p | LM741 | 15p |
| 74LS245 | £1.20 | UA733 | 68p |
| 74LS251 | 45p | JJA747 | 58p |
| 74LS257 | 55p | UA748 | 26p |
| 74LS261 | £3.10 | TL074CN | £1.20 |
| 74LS366 | 38p | TL081CP | 38p |
| 74LS373 | 78p | TL082CP | 60p |
| 74LS374 | 78p | TL084CN | 98p |
| 74LS393 | 80p | LM3302 | 85p |
| | | TL490 | £1.10 |
| | | 1488 | 70p |
| | | 1489 | 70p |
| | | 8T26 | £1.50 |
| | | 8T28 | £1.50 |
| | | 8T95 | £1.50 |
| | | ICM7555 | 80p |

LOW PROFILE DIL SOCKETS

| | |
|--------|-----|
| 40 pin | 30p |
| 28 pin | 26p |
| 24 pin | 24p |
| 22 pin | 22p |
| 18 pin | 16p |
| 16 pin | 14p |
| 14 pin | 12p |
| 8 pin | 9p |

ENCODER/TRANSMITTER RECEIVER/DECODER

| | |
|----------------------------|-------|
| LM 1871 | £1.90 |
| LM 1872 | £1.90 |
| Data £1 pr. Large SAE 20p. | |

TILs

| | |
|--------------|-------|
| TIL32 | 45p |
| TIL209 red | 10p |
| TIL232 green | 18p |
| TIL272 yell. | 16p |
| TIL276 red | 18p |
| TIL228 red | 20p |
| TIL220 red | 12p |
| TIL224 | 18p |
| TIL311 | £5.50 |
| TIL312/3 | £1.00 |
| TIL321/A | £1.15 |
| TIL330A | £1.15 |

SOUND EFFECTS GENERATOR

Suitable for video games, alarms, toys, etc.

Data 75p. Large SAE 20p.

LINEAR ICs

| | |
|---------|-------|
| NE555 | 17p |
| NE556 | 48p |
| RC4136 | 65p |
| LM301AN | 26p |
| LM311P | 46p |
| LM318 | £1.45 |
| LM324N | 42p |
| LM339N | 40p |
| LM348N | 75p |

NEW S-100 PROM BLASTER

PROGRAMS MOST FAMILIES OF EPROMS!

Bareboard £49
Promwriter £40
KIT* £175
Incl. all parts ckts. and Promwriter*
Del: 3 weeks

KITS

WHEEL OF FORTUNE £5
ULTRONIC FLY REPELLER £4.50

S-100 KLUGE CARD

SIMPLIFY YOUR PROJECTS WITH A PROTOTYPE BREADBOARD WITH EXTRAS!

- 4 On-Board Pwr. Supplies up to 3 of which can be +5, or ±5, ±12.
- Switch Selectable Memory or Device Address.
- On-Board Address/Device Decoding.
- Bi-Directional Data Bus Buffering.
- On-Board Wait States.
- Large Breadboard Area.
- Bare Board & Manual. £33.00.
- Complete kit £48 Delivery 2 wks

FLOPPY DISC CONTROLLERS

| | |
|-----------|--------|
| FD1771 | £21.00 |
| FD1791-2 | £21.00 |
| WD1691D | £14.50 |
| WD2143-01 | £5.00 |

★SPECIAL★ Complete Pkg. £50.
Includes FD1791-2 + WD1691D + WD2143-01
Set data available £3.00 (51p SAE please).

EPROMS

| | | |
|-----------------|--------|-------|
| 2708 450ns | £2.55 | £2.50 |
| 2716 5v 450ns | £2.65 | £2.60 |
| 2732 Intel type | £9.50 | wa. |
| Buy 5 off for | £49.00 | |

6809 SINGLE BOARD COMPUTER

Uses Motorolas powerful MC 6809 CPU!
4K/8K/16K ROM 2K RAM, ACIA, PIA, 8080 simulated I/O, RS-232 Handshake, 8 sel. Baud Rates.
BARE BOARD £48★
Uses 6809: 6850: 6821 - Buy set for £18.40.
COMPLETE KIT £175 + 15% VAT + £1 P&P.
Manual includes: 11x17in. Schematic Parts List, user notes, Software listings and more!
ADMONS (2716) £24.00
DATA AVAILABLE ON 6809, SAE please.

MEMORIES

| | | |
|-----------------------------|--------|--------|
| 2114 450ns | £1.30 | £1.25 |
| 2114 300ns | £1.45 | £1.40 |
| TC5514P | £3.66 | £3.46 |
| (4K CMOS RAM (1Kx4) 450ns.) | | |
| 4116 200ns | £1.20 | £1.18 |
| 4116 150ns | £1.70 | £1.65 |
| CMOS RAM 5101 | £3.45 | £3.40 |
| NM 6116-3 (16K 150ns) | £15.50 | £15.25 |

CPU's

| | | | |
|------|--------|-------|-------|
| 6502 | £5.45 | 8080A | £4.15 |
| 6504 | £7.25 | 8085A | £6.45 |
| 6802 | £5.70 | Z80 | £4.00 |
| 6809 | £15.00 | Z80A | £5.85 |

SUPPORT DEVICES

| | | | |
|------|--------|-----------|--------|
| 6520 | £3.10 | Z80 CTC | £4.25 |
| 6522 | £5.55 | Z80 PIO | £4.25 |
| 6532 | £7.70 | Z80ACTC | £5.40 |
| 6810 | £2.50 | Z80APIO | £5.40 |
| 6821 | £1.90 | Z80DMA | £14.95 |
| 6845 | £15.00 | Z80ADMA | £18.00 |
| 6850 | £1.90 | Z80SIO/0 | £17.90 |
| 6852 | £3.25 | Z80ASIO/0 | £22.50 |
| 8212 | £1.75 | Z80SIO/1 | £17.50 |
| 8216 | £1.75 | Z80ASIO/1 | £22.50 |
| 8228 | £3.95 | Z80SIO/2 | £17.50 |
| 8255 | £4.10 | Z80ASIO/2 | £22.50 |

Z80 COMBO CHIP

MK3886, 21/2 meg. £19.50
Data £1.00 plus 51p SAE.

AY-3-8910 GI SOUND COMPUTER CHIP

Features:

- Full software control of sound generation
- Interfaces with most 8-bit and 16-bit microprocessors
- 3 independently programmed analogue outputs
- Two 8-bit general purpose I/O ports
- Single +5 volt supply

SPECIAL PRICE £6.95
Data £1. Large SAE please

VEROBLOC SOLDERLESS BREADBOARD

360 reliable contacts. Will accommodate any size IC. Can be full interlocked one with another. £3.55 each

\$100 Prototyping Boards:

Microboard Pattern 06-2175L £16.40
Sq. Pad Universal Pattern £16.40
Prototyping Board for your APPLE I/II/20X £8.37

ANTEX SOLDERING IRONS

Model CX, 17W £4.25
Kit SK1, 15W £6.00
Incl. base/stand + solder.
Kit SK3, 17W £8.00
Kit SK4, 25W £6.00
SK3 and SK4 complete with stand.
MLX Repair Kit £4.80
Can be used where no mains elec. is available.
Spare Bits 50p

ORDERING INFORMATION

Please add 50p P&P. Plus 15% VAT to all orders.
EXPORT ORDERS ACCEPTED.
Add 15% P&P on total order. VAT not applicable.
ACCESS/BARCLAYCARD WELCOME.
Please add 15% VAT after P&P.
Schools, Univ. Official Orders welcome.
It is our policy to offer you brand new, full-spec. devices. Prices subject to change without notice.


PET, ATOM, UK101 MEMORY REVOLUTION.

Memory expansion boards 16K complete kit £50, built £58. 32K kit £74, built £82.
OHIO SCIENTIFIC COMPUTERS
Superboard 3 Pos. 4K extra ram £10.80. 16K memory expansion complete kit £50, built £58. 32K memory expansion kit £74, built £82. Power supply kit £11.95. Modulator £3.50. Guard band kit £10. Case £27.
Cegron £22.50. Wernon £19.95. Assembler/Editor tape £25. Word Processor Program £10. Display expansion kit for Superboard 2 series 1 only £14.
Centronics interface kit £10. 610 expansion board p.p.a. Minifloppy disc drive p.p.a. Cassette recorder p.p.a. Colour adaptor board built £45.

VIDEO GENIE £279



PRINTERS

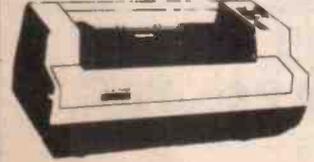

Buy any of the below and get a free Interface kit and word processor program for UK101 or Superboard - Epson MX70 £259. Epson MX80 £259. Epson MX80F/TT £395. Epson MX80F/TT £449. Epson MX100 £575. OKI Microline 80 £296. OKI Microline 82 £399. OKI Microline 83R £699. OKI Microline 82 £399. OKI Microline 83 £699. Centronics 737 £395. Seikosha GP80A £199.

TV GAMES*

AY-3-8800 + kit £12.98. AY-3-8550 + kit £9.26.

SWANLEY ELECTRONICS
Dept ET1, 32 Goldsrd Rd., Swanley
Kent BR8 8EZ
Tel Swanley (0322) 64851

SINCLAIR PRODUCTS*

Sinclair Products only are all Post free. SC110 Oscilloscope £158.95, adaptor £5.69, rechargeable batteries £8.63, x1 Probe £9.78, x10 Probe £11.50, carry case £8.86. PFM200 £57.27, adaptor £5.69, case

BATTERY ELIMINATORS*

3-way type 6/7.5/8V 300ma £3.50. 100ma radio types with Press studs 9V £4.95. 9 + %V £6.25. Car converter 12V input, output 3/4.5/6/7.5/9V 800ma £3.04.

BATTERY ELIMINATOR KITS*

100 ma radio types with Press-studs 9V £1.79. 9 + 9V £2.50. Stabilized 8-way types 3/4.5/6/7.6/9/12/15/18V 100ma £3.13. 1.30, 1.30V 1A £8.50. 1.30V 2A £15.30. TTL and computer supplies 5V stabilized 1.5A £9.3A £14.6A £23.12V car converters 6/7.5/9V 1A £1.62.

SHARP COMPUTERS

MZ80K 20K £380. 36K £394. 48K £408. PC1211 £82.



BI-PAK AUDIO MODULES*

AL30A £4.36. PA12 £9.31. PS12 £1.75. T538 £2.90. S 450 £27.90. AL60 £52. PA100 £19.24. SP180 £5.26. BMT80 £6.36. Stereo 30 £21.00. AL60 £8.56.

VIC 20 COMPUTER £165



Postage £3.50 computers, £4.50 on Printers and 45p on other orders. Lists 27p Post free. Please add VAT to all Prices except those sections marked with a * which already include it. Overseas and official credit orders welcome.

Quality support for; ATOM ZX80 ZX81

ZX80 ACTION !
2 games per cassette - for only £4!!
Flicker-free action games for your ZX80. Only 1K RAM needed, and the original (4K) ROM.
Cassette C80A: **BRKOUT** ----- **ACK-ACK** £4-
Cassette C80B: **SHELL GAME** ---- **INVADERS** £4-

The ZX80 Magic Book
** WITH 8K ROM / ZX81 SUPPLEMENT **
Games programs, computer music, converting programs written in other BASICS. Improving the picture, RAM and I/O circuits, and much more. £4.75
Getting Acquainted with your ZX81
A Tim Hartnell masterpiece. £4.95
23+23 WAY ZX80/81 EDGE CONNECTOR SOCKET £3.50

ATOM CASSETTES ; £5 each
CAAA: **BREAKOUT + CUPBALL + 3D MAZE + SIMON 2**
CAAB: **PINBALL + LETTERS + SPACEWAR + DRIVE**
Both tapes need 1K VDU + 5K text RAM

The ATOM Magic Book
A wealth of games and other programs; storing speech in your ATOM, converting programs written in other BASICS, tape recording hints, plus many other useful hardware and software tips. £5.50

16/32K ATOM RAM Boards from £9.50
Single Eurocard, can fit inside Atom's case. Built & tested. Also suitable for other 6502/6800 computers. Bare PCB only £23. S.a.e. for further details

ALL PRICES INCLUDE U.K. P&P + VAT WHERE APPLICABLE

TIMEDATA Ltd. 57 Swallowdale, Basildon, Essex

NEW POWER DIMMING MODULES

- Substitution
- Multi-channel operation during chase
- Fluorescent dimming power factor
- Control "off" and "on" times
- Control "fade" and "hold"
- Control "hold" or "off" outputs

Power Dimming Modules
A range of power dimming modules, complete with panels, and the correct connector to the supply/reference leads.

Slave power modules SPC
Controls up to 100W of power
RFI suppression
Slave power: 250W SPC
Controls up to 250W of power
from a remote slave
Master control: SPC
Will master dim from 1 standard of 22 SPC units.
Remote slave: 220W SPC
Will override the SPC at a remote location to the main master control of SPC.
Supply/reference leads
Provides the necessary supply voltages and signals to drive loads. Suitable for "CFL" and "TL" modules to any combination of modules.

| PRICES (£) | |
|-----------------|--------|
| RFI suppression | £11.90 |
| Slave power | £9.90 |
| Master control | £7.20 |
| Supply | £8.50 |
| Supply | £18.20 |

SPECIAL DISCOUNTS
Are available on power dimmers.
Total year order up and discount:
From £799 - 20%
Over £1799 - 25%
Over £3499 - 30%

3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC **£32.70**



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti-interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

STEREO DISCO MIXER/PREAMP


LBPA3
M - Magnetic
C - Ceramic



£33.70
Magnetic or ceramic deck versions - please state
All the requirements of a stereo disco preamp on one board, left and right deck mixers/tone controls/misc. mixer/tones/mic. auto. fade over decks/and P.F.L. The unit can be used with either LB 100/150/250.
Full set of pots - **£8.63**

2/4/8 CHANNEL CHASER

LB81000LC

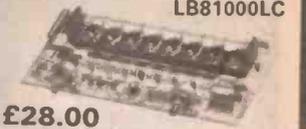

£28.00
An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

MULTI - 4

£54.90



Attractive blue panels with white letters, complete with LED monitors, knobs and mains illuminated switch.
£9.70

The Multi-4 is a comprehensive sound and chase module, offering a wide range of forward, reverse or random effects, with additional sound modulation facilities. Modes of operation are set on control pots which act as electronic switches. The unit has a wide speed range and will accept virtually any sound level input. The Multi-4 also provides monitor circuits for LED driving. The triac outputs may be used to drive up to 4000W of lighting or up to 10 metres of rope lights.

POWER AMPLIFIERS

Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to 4 ohms).

| 25W R.M.S. | 100W R.M.S. | 150W R.M.S. | 250W R.M.S. |
|--|--|--|--|
| 20Hz to 60K 0.07% THD 96DB S/N LB25 | 5Hz to 25K 0.1% THD 110DB S/N LB100 | 5Hz to 25K 0.1% THD 110DB S/N LB150 | 5Hz to 25K 0.1% THD 110DB S/N LB250 |

£11.20 £19.70 £29.20 £43.50
Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

PROGRAMMABLE - 8

£114.90

P/P INS
£1.50



Complete with blue panel/white letters
8 channel 400W each
16, 32, 64, 128 patterns
Automatic program recycle
Adjustable cycle on/off speed
Quality reduced, suppressed tones
Either common leaded or fine lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be recalled as the stored order, with control over the rate on and off time. At the end of the program the system reverts to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although retaining the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following night's requirements. The module obviously provides unlimited effects and is a must for all serious lighting shows.

L & B ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon
Surrey CR0 3EB. Tel. 01-689 4138

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.
All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.O./Registered cash/Access number. C.O.D. service £1 extra. For further information send a s.a.e. stating which model.
PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

SUPPLY UNITS

| LBPSU1 FOR PA3 AND ACD1 | LBZPS FOR 1/2 LB25 | LB100PS FOR 1/2 LB100 | LB150PS FOR 1/2 LB150 |
|-------------------------|--------------------|-----------------------|-----------------------|
| £7.20 | £11.20 | £16.20 | £19.00 |

3-WAY ACTIVE CROSSOVER

LBACO1 **£17.90**



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1. (1 or 2).

3 CHANNEL SOUND/LIGHT

LB31000SL **£22.70**



All the advantages of the SLC without chase.
Controls: bass/mid/treble/master sensitivity.

4 CHANNEL SEQUENCER

LB41000LS **£19.20**



A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

7 HUGHENDEN ROAD, HASTINGS, SUSSEX. TN34 3TG
Telephone: HASTINGS (0424) 436004

AMTRON LTD ELECTRONIC KITS

| | |
|--|--|
| KS470 SOUND OPERATED SWITCH 9-12V D.C. £11.27 inc VAT | KS143 L.E.D. VU DISPLAY, INPUT 1-100W 5-12V D.C. £9.15 inc VAT |
| KS490 NICAD BATT CHARGER 10-20-45-100-150 mA, 15V. D.C. MAX. 240V A.C. £3.86 inc VAT | UK232 AM.FM ANTENNA AMPLIFIER 12V D.C. £6.04 inc VAT |
| SK370 2 TONE SIREN, OUTPUT 18 W at 4 OHM, 6 W at 8 OHM, 1000BPM £5.14 inc VAT | KS445 COURTESY LIGHT TIMER FOR CARS, 10-15V D.C. £7.79 inc VAT |
| KS165 DUSK SWITCH 9V D.C. SWITCHES 240V 5A MAX £16.46 inc VAT | KS150 LONG PERIOD TIMER 40 SEC-90 MIN, 9-15V D.C. £9.35 inc VAT |

Post & Packing, 50p per KS kit, 75p per UK kit. Send 20p S.A.E. for catalogue of our extensive range of kits & cabinets. Trade, Educational & Export enquiries welcomed.

BARCLAYCARD VISA

Please mention
ELECTRONICS
TODAY
INTERNATIONAL
when replying
to adverts.

LONDON'S
TEST EQUIPMENT
CENTRES

AUDIO ELECTRONICS

Retail • Mail Order • Industrial • Educational • Export

OPEN SIX DAYS A WEEK • CALL IN AND SEE FOR YOURSELF

ALL MODELS
ON DISPLAY
ALL PRICES INCLUDE VAT



LCD DIGITAL MULTIMETERS

SPECIAL PURCHASE - LIMITED PERIOD ONLY

6220 Reliable 22 range hand held 3 1/2 digit LCD with volt/ohms auto range, unit and range signs, 10 amp AC/DC, battery warning, lower power ohms range. Model 6110 Also has range hold, continuity buzzer and improved accuracy. All models high quality rotary operation Resolution 0.1 milli volt: 10-Micro amp: 0.1 ohm

6220 1000v DC: 0.2/10A AC/DC 600v AC: 2mea ohm Was £55.95 **NOW £42.95**

6110 As above plus 20mA AC/DC and improved accuracy Was £85.95 **NOW £59.95**

THIS SPECIAL OFFER IS QUALITY WITH VALUE

Also in stock
6200 20/200mA version of 6220 (i.e. no 10 amp) £37.95
6100 0.2A version of 6110 (i.e. no 10 amp) £49.95
188m 16 range with Hfe checker 10 Amp DC £43.50
189m 30 range with Hfe checker 10 Amp AC/DC £69.95



HAMEG OSCILLOSCOPES


Range of top quality scopes for Amateur and Professional (UK c/p *307 £3.00, other £4.00)
307 Single trace 10 MHz: 5mV: 0.5 micro sec. Plus built in component tester. 6 x 7cm display. £158.70
(Optional carry case £18.40)

203 Dual 20 MHz: Trig to 30 MHz: 5mV: 0.5 micro sec: 8 x 10cm display (replace model 312) £253.00
412-5 Dual 20 MHz delayed sweep: trig to 40 MHz: 5mV: 0.1 micro sec. 8 x 10cm display. £402.50

512 Dual 50 MHz. Delayed sweep: Single sweep: Delay line: Trig to 70 MHz: 5mV: 0.1 micro sec. 8 x 10cm display £667.00

Options 203/412/512 Viewing hood £6.90
Component tester 203, 412, 512 £46.00
Carry case (state model) £21.85

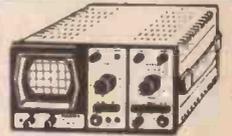Optional Probes (All models) X1 £7.95; X10 £9.45
X1-X10 £10.50; X100 £16.95



GLOBAL SPECIALISTS EQUIPMENT

Generators (UK c/p £1.00)


2001 1 HZ-100 KHZ sweepable function generator. TTL/Sine/Square/Triangle. All facilities: Mains £89.00
4001 Ultra Variable Pulse Generator: 0.5 HZ-5 MHz Every facility: Mains. £109.00

Frequency Counters (UK c/p 80p)

MAX100 100 MHz Counter. Battery operated. 8 Digit 30mv typical. Bench portable LED £89.00
MAX50 6 Digit 50 MHz Hand held LED £56.00
MAX550 2 range 6 Digit 550 MHz hand held LED £97.75
PS500 500 MHz prescaler for MAX50/100 £34.50

Circuit Powered Logic Probes Pulsers and Monitors (UK c/p 65p)

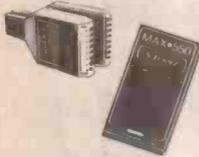LP1 DTL/TTL/CMOS: 10 MHz. 100K ohm: Pulse: Memory £35.50
LP2 DTL/TTL/CMOS: 1.5 MHz. 300K ohm: Pulse £19.95
LP3 DTL/TTL/CMOS: 50 MHz. 500K ohm: Pulse: Memory £55.95
LM1 All. 8, 10, 12, 14 & 16 Pin IC'S. Indicates Pins on/off DTL/TTL/CMOS/HTL. Logic Monitor £33.00
OP1 Digital Pulse. Single shot or 100pps. £58.50



KEITHLEY PROFESSIONAL DIGITAL MULTIMETER

Model 130. 25 range. Easy to hold and use LCD DMM. Size 7 x 3.1 x 1.5

Ranges
DC Volts 200mV-1000V 0.5% 100 micro volt
AC Volts 200mV-750V 1% 100 micro volt
DC current 2mA-10AMP 1-2% 1 micro amp
AC current 2mA-10AMP 2% 1 micro amp
Resistance 200 ohm-20 Meg 0.5% 0.1 ohm

£102.35



PROFESSIONAL TRANSISTOR CHECKERS UKC/P £1.50


All feature auto test and matching.
LTC 906A plus DC Parameters £111.55
LVT plus F.E.T. multimeter £147.20
Multi band signal injector £173.60
Also LTC 905 Semi conductor curve trace (use with scope) £95.45

SAFGAN PORTABLE OSCILLOSCOPES

Range of low cost Dual Trace Scopes mains operated. Made in UK to exacting standards. Available as 10 MHz: 15 MHz or 20 MHz. All feature 5mV sensitivity; 0.5 micro sec: 6.4 x 8cm display. (UK c/p £2.50)

DT410 Dual 10 MHz £194.35
DT415 Dual 15 MHz £201.25
DT420 Dual 20 MHz £216.20

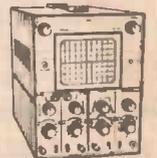Optional probes available (see Hameg above)



SABTRONICS EQUIPMENT

New reliable range of DMM's and frequency computers with those extra facilities and competitive prices. All battery operated (supplied). Except 5020A mains. Optional mains eliminators available.

8 DIGIT COUNTERS 0.1 HZ to 10 HZ Res. 10mV sensitivity to 100 MHz

(UK c/p £1.00)

8110A 20 HZ-100 MHz in 2 ranges £95.45

8610A 20 HZ-600 MHz in 3 ranges £113.85

9 DIGIT COUNTERS 30mV sensitivity to 1GHz. Resolution 0.1 HZ-10 HZ

8610B 10 HZ-600 MHz in 3 ranges £125.35

8000B 10 HZ-1GHz in 3 ranges £184.00

FUNCTION GENERATOR (UK c/p £1.00) with mains adaptor

5020A 1 HZ-200 KHZ Sine/Square/Triangle/TTC Freq sweep. Low distortion £98.90

DIGITAL MULTIMETERS Two LCD hand held - one with temperature range. Also LCD and LED Bench models

2035A 3 1/2 digit LCD hand. 2A AC/DC 20Meg ohm ETC £95.45

2037A As 2035A with -50°C to -150°C Temp. range 0.1° resolution £109.25

2015A LCD version of above. £109.25

1 c/p 2035/37A 65p. All others £1.00



VARIABLE REGULATED POWER SUPPLIES

Mains operated regulated single metre (UK c/p £1.50)
241 0/12-0/24V 1 amp £35.00
154 5-15 volt 3 amp £44.00
423 0/12-0/24V 3 amp £54.00



AMATEUR/CB

KDM6 1.5 to 250 MHz Dip meter 6 ranges £38.50
SWR9 3-150 MHz SWR + F/S £9.50

SWR50 Twin meter SWR + Power 1KW max. £13.95

310 Single meter SWR + Power 10W £8.95

110 SWR/Power/F/S-10/100W £11.95

171 As '110' Twin meter £14.50

175 SWR/F/S/AE Match (40 MHz) £13.80

176 As '175' + 0/5/50 Watt power £16.95

178 As '175' + 0/10/100W + MOD Scale £19.50

HM20 SWR meter Plus 20K/Volt 19 range Multimeter £28.95

(Note: SWR-Power ETC to 144/150 MHz)

Just a selection of a huge range in stock - send for latest lists including professional ranges.

Options Touch & hold Probe for DMM's £14.95

Battery eliminators (state model) £5.69

13.8 volt. Output regulated mains operated (c/p £1.00)


3 to 5 amp £15.50

5 to 8 amp £17.95

LASCAR BENCH MULTIMETER

3 1/2 Digit LCD Made in UK: 25 ranges with basic 0.1% accuracy: 2A AC/DC with 0.1. Microamp resolution: 1KV AC/DC 20Meg ohm ETC.
LM100 £89.00 (UK c/p £1.00)
Also model LM2001 hand held model 2Meg ohm 2A AC/DC ETC. £57.70 (UK c/p 65p)

LEADER AUDIO RF FM TV GENERATORS

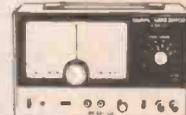

High quality mains operated equipment (UK c/p £1.50)

LSG16 RF Generator (matches LAG26)

5 ranges 100 KHZ-100 MHz (300 MHz harmonics). Int/Ext MOD: 100mV

o/p: ± 1.5% accuracy £63.25

LSG 231 FM Stereo Generator 100 + MHz. All facilities £211.60

AUDIO
LAG26 4 range 20 HZ-20 KHZ. Sine/Square: SV o/p: Distortion 0.5-1% £73.60

LAG120A 5 range 10 HZ-1 MHz. Sine/Square: 3V o/p: 0.05-0.8% Max Distortion Switched attenuator. £146.00

LAG125 Low distortion (0.02%) version of LAG120A Plus 'Burst' type signals for Speaker test £273.00

DISCOUNTS Small and large quantity Discounts available for most products for UK and Export Your Enquiries Invited.

ALSO STOCKED Range of chassis speakers and kits, microphones and public address equipment accessories etc.

ALL PRICES INCLUDE VAT

AUDIO ELECTRONICS

Cubegate Limited

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564
ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2

OPEN SIX DAYS A WEEK • CALL IN AND SEE FOR YOURSELF

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order

FREE CATALOGUE!

Send large SAE (20p UK) Schools, Companies, etc. free on request.

CLASSIFIED

ETI RATES

7-4 Insertions £9.00 per scc
 5-11 Insertions £8.00 per scc
 12+ Insertions £7.00 per scc
 30p per word (min 12 words)
 Box No. £2.00
 Closing date 1st Friday in month preceding publication.

HE RATES

1-3 Insertions £6.00 per scc
 4-11 Insertions £5.50 per scc
 12+ Insertions £5.00 per scc
 21p per word (min 15 words)
 Box No. £2.00
 Closing date 2nd Friday in month preceding publication.

Classified Advertisements must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

CENTURION ALARMS

BURGLAR ALARM EQUIPMENT AT UNBEATABLE VALUE JUST LOOK!

Order No
100 ALARM TRIGGER MODULE, 100% Solid State. Battery operation. Pos & Neg Rings. N/C for 4-wire contacts. N/O for Mats, etc. One Amp Switching Capacity. Only **£9.95**
210 Quality White Flush fitting 4-wire MAGNETIC REED CONTACT + matching magnet **£1.10**
220 Surface 4-wire MAGNETIC REED CONTACT **£1.50**
240 PRESSURE MAT, Standard size 4-wire 30" x 15" **£2.20**
250 PRESSURE MAT, Star size 4-wire 23" x 6 1/2" **£1.73**
260 VIBRATION DETECTOR, Pendulum type in Ivory Case with contacted Lid + self adhesive backing. Adjustable sensitivity **£3.50**
360 SIX INCH UNDER DOOR BELL **£9.95**
390 BEST QUALITY BELL HOUSING, PVC coated metal, not to be confused with the cheaper decoy covers. Fully sign written with our Centurion insignia **£9.50**
400 DECOY P.V.C. BELL COVER **£6.80**

Note: All equipment operates on 12 Volts DC.
 710 SCOP Offer SMOKE ALARMS. Self-contained ionisation type (1 5% obscuration) with low battery warning at the UNREPEATABLE PRICE of only **£8.75** While Stocks Last!!!
 Terms: Add 15% VAT to Prices + 40p Postage & Packing.

No Minimum Order.
 Access telephone orders welcome on 0484-35527 or send SAE for Full list to
CENTURION ALARMS & ELECTRONIC SALES, Dept. ME, 265 Wakefield Road, Huddersfield, W. Yorks HD5 9BE.



ZX81 TEMPERATURE sensors (plug-in compatible). Including UK P&P £19.50. Free leaflet, Cheshire Micro Design, 66 Close Lane, Alsager, Stoke on Trent.

TRANSCENDENT 2000 synthesiser, will demonstrate. Must sell. Only £160 o.n.o. Phone Romford 61064.

TRANSCENDENT 2000 synth £180. Evans EP100 echo machine £95. Both excellent condition. Sold together for £265. Phone 03632 3027 evenings.

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send £9 for complete kit and get into a fast-growing business. Prompt despatch.



BOLSTER INSTRUMENT CO. (ET29)
 11 Percy Avenue, Ashford, Middx. TW15 2PB

KLIFCO COMPLETE DISCO STEREO AMPLIFIER OFFER £27.95. PROFESSIONALLY FINISHED, TREBLE, BASS, HEADPHONES+TAPEING. FET. IC —60W (240v AC) — MAGNETIC PICKUPS (3MV)+ MIC (+ SPEAKERS £60 COMPLETE). KLIFCO — ILKLEY.

DO YOU TRANSMIT AUDIO SIGNALS OVER CABLE CIRCUITS?

We manufacture a full range of interface equipment for transmission of audio signals over private wire or telephone circuits, from Narrow Band STD systems (300Hz-3.4kHz) up to Wide Band Music Circuits.

PARTRIDGE ELECTRONICS

(A. C. Partridge Ltd.)
 56 Fleet Road, Benfleet, Essex
 Tel: (STD 03745) 3256
 We also manufacture audio mixers and sub-assemblies

SECURITY SYSTEM KITS . . . All components and full instructions. Send large SAE for latest catalogue of advanced projects for car, caravan and home. Computech Systems, Ind Est, N. Walsham, NR28 0AN. Tel: (0692) 405600.

SOUND/LIGHT in smart two-tone case, only 1 1/4" high! All parts, hardware 600w per channel, 13-95. Cheques JDG Electronics Ltd, 9 Clifford Manor Road, Guildford, Surrey.

BURGLAR ALARM Component Catalogue out now. Ring: C.W.A.S. 0274 682674.

TRANSCENDENT DPX. Built, working beautifully. See Powertran ads for specification. Could deliver up to 50 miles. £350. Phone Slough 70111 ext 246. Ask for Gilbert.

TRANSCENDENT 2000. Fully working, hardly used. £200 o.n.o. Tel. Steve 01 572 1239.

ACORT ATOM UTILITY ROM

Upgrade your Atom now! Our 4K ROM simply plugs into the spare socket and provides 18 new commands and utilities including: renumber, range delete, find, auto line numbers, program compression, disassembler, true keyboard scanning, memory dump, and much more. Supplied with full instruction manual. To order send cheque/PO for £35 inclusive (delivery 1 week) or SAE for further details.

WILLOW SOFTWARE
 PO Box 6, Crediton, Devon EX17 1DL

POWERTRAN DPX Polypaonic synthesizer. Virtually completed & working. £395 o.n.o. Tel. 0264 71385.

CHEAP CHIPS UA 741 ICs 10 for £1.40. NE555 ICs 10 for only £1.60. BC108 transistors 10 for 70p. Components new full spec, return of post servis p/p free. Cheques/POs payable to G. Monaghan. Post to (ELECTRONICS) 24 Tower Road, Tadworth, Surrey.

BUILD A 12 into 2 mixer for £100. Details £3.50. P.O. to Mr J. A. Lovatt, Flat 5, 36 William Ave., Margate, Kent.

ZX80 8K ROM DISPLAY. Six I.C. design gives SLOW mode operation with correct character alignment. Circuit £4. M. B. Daniels, 58 blacklock, Springfield, chelmsford, Essex.

BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

- 1 With alarm repeat. S.R.S.P. of £17.00. Offered at **£3.95**, inc. VAT, or 3 for **£9.95**, inc. VAT
- 2 With luxury lamp and repeat alarm. S.P.S.P. **£31.00** Offered at **£7.95** inc. VAT each, or 3 for **£19.95** inc. VAT

These will be sold as received from our customers with the existing fault(s) and without guarantee.

U.K. only
 Discounts available on large bulk purchase.
PRESCOTT CLOCK & WATCH CO. LTD.

PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

ZX80/ZX81 KEYBOARD

Full size 40 key keyboard. All symbols marked in two colours.

Kit £19.95 Built £22.95
Keyboard connector £1.95

IN/OUT PORT

24 lines controlled in BASIC. Drive motors, printers etc.

Kit £14.50 Built £15.95
In/Out connector £3.95
ZX8*/ZX81 connector £2.95

MOTHERBOARD

Drives RAM pack and two boards. Includes ZX80/ZX81 connector and one board connector.

Kit £13.39 Built £13.90
2nd connector £2.95

Postage on above 80p
SAE for FREE illustrated catalogue.

Redditch Electronics

21 Ferny Hill Ave,
Redditch, Worcs. B97 4RU.
Tel: 0527 61240

NE MI PROFESSIONAL ZERO
EXTRACTION FORCE IC SOCKETS, 24 &
40 pin, £3.50 & £4.20. SOLID-STATE
MINI-BUZZERS, 1.5 to 24V (specify when
ordering), £3.30. PXP 20p inc. EPROM
PROGRAMMING, £3/1K inc. PETRON
ELECTRONICS, Courtlands Rd, Newton
Abbot, Devon.

VHF/FM TRANSMITTER KIT. New IC
design — tuneable 88-108MHz. Ideal bug.
ONLY £1.95+30p P&P. (Unlicensable). M
Henry, Dept ET1, 30 Westholme Gardens,
Ruislip.

COMPONENTS GALORE Prices to shock
— Send SAE NOW for lists. T.H.D. Elec-
tronics (Bristol), 90 Longford, Yate, Bristol
BS17 4JW.

TELEPHONE ANSWERING Machine (twin
cassette) drilled p.c.b.+full instructions
£3.95. Burglar alarm p.c.b. drilled+com-
ponents full domestic installation instructions
positive/negative rings, entry/exit delays
£5.95. Unbeatable accessory catalogue.
Rapid Service North West Alarms, 5 Spinney
close, Glossop, Derbyshire, 04574 5493.

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT — never gains
or loses, SELF SETTING at switch-on, 8 digits
show Date, Hours, Minutes and Seconds, auto
GMT/BST and leap year, also parallel BCD output
for computer and audio to record and show time on
playback, receives Rugby 60KHz atomic time signals,
built-in antenna, 1000Km range. TIME RIGHT, £62.80.
60KHZ RUGBY RECEIVER, as in MSF Clock, serial
data and audio outputs, £17.90.

Each fun-to build kit includes all parts, printed circuit,
case, instructions, postage etc, money back assurance
so GET yours NOW.

CAMBRIDGE KITS

45 (TV) Old School Lane, Milton, Cambridge.

RESISTOR SETS

High Quality Carbon Film ¼W 5%, E24 Series. 60 values
10 per Value.

£5 including V.A.T., P&P

COVE COMPONENTS
58 SOUTHWOOD RD., COVE,
FARNBOROUGH, HANTS GH14 0JJ

Mail Order Only

ATTENTION SHARP PC-1211/TRS-80 POCKET COMPUTER/MEMOWRITER USERS

PFS-123 Paper feed stand with Free 3" Dia, paper roll
..... £3.95
Pack of 5 rolls 3" Dia, For above £3.00
Pocket BASIC programming worksheets — 40 sheet pad
..... £2.95

AT LAST BOOKS FOR THE PC1211/TRS-80 POCKET COMPUTERS

5 Titles available — Lots of new programs
PC1211 Software, hardware and accessories. Send for
our New catalogue.

ELKAN ELECTRONICS

28 Bury New Rd, Prestwich,
Manchester M25 8LD

Get into the 21st Century with a pocket computer

CIRCUIT DESIGN, Prototype construction,
analogue or Digital, Single Circuits or
Complete Instruments/Systems. Write A. J.
ATTWOOD, C.Eng., MIERE, Heathercote,
Heatherthorn Park, Taunton, Somerset, TA4
1ET, or Phone Bradford-on-Tone (082-346)
536.

PRE-PACKED SCREWS, Nuts, Washers,
Solder Tags, Studding. Send for price list.
A1 Sales (ETI), P.O. Box 402, London SW6
6LU.

PRINTED CIRCUITS. Make your own sim-
ply, cheaply and quickly! Golden Fotolac
light-sensitive lacquer — now greatly im-
proved and very much faster. Aerosol
cans with full instructions, £2.25. De-
veloper 35p. Ferric Chloride 55p. Clear
acetate sheet for master 14p. Copper-clad
fibreglass board, approx. 1mm thick
£1.75 sq. ft. Post/packing 75p. White
House Electronics, Castle Drive, Praa
Sands, Penzance, Cornwall.

T. & J. ELECTRONICS COMPONENTS —
Quality components, competitive prices.
Illustrated catalogue 45p. 98 Burrow
Road, Chigwell, Essex.

MAIL ORDER PROTECTION SCHEME

If you order goods from mail order advertisers in
this magazine and pay by post in advance of
delivery, this publication *Electronics Today
International* will consider you for compensation
if the advertiser should become insolvent or
bankrupt, provided:

1. You have not received the goods or had your
money returned; and
2. You write to the publisher of this publication
Electronics Today International explaining the
position not earlier than 28 days from the day
you sent your order and not later than 2
months from that day.

Please do not wait until the last moment to
inform us. When you write, we will tell you
how to make your claim and what evidence
of payment is required.

We guarantee to meet claims from readers
made in accordance with the above procedure
as soon as possible after the advertiser has
been declared bankrupt or insolvent to a limit
of £1,800 per annum for any one advertiser
so affected and up to £5,400 p.a. in respect of
all insolvent advertisers. Claims may be paid
for higher amounts, or when the above pro-
cedures has not been complied with, at the
discretion of this publication *Electronics Today
International*, but we do not guarantee to do
so in view of the need to set some limit to
this commitment and to learn quickly of
readers' difficulties.

This guarantee covers only advance payment
sent in *direct* response to an advertisement in
this magazine (not, for example, payments
made in response to catalogues, etc, received
as a result of answering such advertisements):
Classified advertisements are excluded.

KLIFCO RETURN An Ad N^o 6. Return + £3
for a 240V-AC/40V-DC smoothed power
supply. Douglas screened transformer. 1
Regent Road, Ilkley LS29 9EA.

CASIO AX-210 L.C.D. analog/digital watch.
Melody alarms, chrono, timer, calendar,
12/24 hr, dual time, £26. Microplex, 5 De
Vere Gardens, Ilford, Essex. No callers
please.

SINCLAIR ENTERPRISE Programmable
Calculator, slight used, £20 o.n.o. Phone
(0482) 781517 after 6.00pm.

ELECTRONIC CLEARANCE PACKS

HUGE SCOOP PURCHASE

Containing Transistors, capacitors, resistors, pots,
switches, radio and audio items, connectors, relays and
many electronic devices. Must be worth over £20 per
pack. Our price £5 carr. £1.75.

JUMBO PACK

Must be worth over £50. Our price £10 carr. £2.50.
Money back if not delighted.

HAVE YOU SEEN THE GREEN CAT?

1000s of components. Audio, radio, and electronic.
Almost everything electronic at unbelievably low prices.
Something for everyone. Send 35p P.O. or cheque and
receive FREE RECORD SPEED INDICATOR.

MYERS

Dept. E.T.I., 12 Harper Street,
Leeds LS2 7EA
Tel: 452045

HIGH QUALITY AM CAR RADIO

Push button. Provision for rear speakers with
independent volume control. Made in Japan to highest
specification for leading American Car Manufacturer.
Complete with installation kit but excluding Makers
name plate. £12.50 including V.A.T., Postage &
Packing.

GEEMARC LTD.

1-3 Albert Place, London N3 1QB
Tel: 01-346 9374 Telex: 261957 GMARC G

**SIRALARM
SECURITY
SYSTEMS LTD.**

136 Woodside Avenue,
Thundersley, Essex.
Sth Benfleet 4055

INTRUDER ALARM COMPONENTS

Write or phone for free list

RAMAR CONSTRUCTOR SERVICES
MASONS ROAD STRATFORD-ON-AVON WARWICKS, TD, 4879

Send 15p for catalogue.

Comprehensive range Constructors Hardware and accessories

Selected range of popular components Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices

P.C. Boards to individual designs Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Affix range of etch resist transfers and other drawing materials for p.c. boards

PRINTED CIRCUITS HARDWARE

THE SCIENTIFIC WIRE COMPANY
 PO Box 30, London E.4.

ENAMELLED COPPER WIRE

| | |
|----------|-------|
| SWG 40z | 2.02 |
| 11b | 80z |
| 11b | 1.50 |
| 30 to 34 | 1.80 |
| 35 to 39 | 2.00 |
| 40 to 43 | 2.60 |
| 44 to 47 | 3.19 |
| 48 to 49 | 5.98 |
| 48 to 49 | 15.96 |
| 48 to 49 | 9.58 |
| 48 to 49 | 3.32 |
| 48 to 49 | 8.37 |
| 48 to 49 | 4.75 |
| 48 to 49 | 2.60 |
| 30 to 34 | 3.20 |
| 35 to 39 | 3.40 |
| 40 to 43 | 4.75 |
| 44 to 47 | 5.32 |
| 48 to 49 | 9.58 |
| 48 to 49 | 15.96 |
| 48 to 49 | 3.32 |
| 48 to 49 | 8.37 |
| 48 to 49 | 4.75 |
| 48 to 49 | 2.60 |
| 30 to 34 | 3.20 |
| 35 to 39 | 3.40 |
| 40 to 43 | 4.75 |
| 44 to 47 | 5.32 |
| 48 to 49 | 9.58 |
| 48 to 49 | 15.96 |
| 48 to 49 | 3.32 |
| 48 to 49 | 8.37 |
| 48 to 49 | 4.75 |
| 48 to 49 | 2.60 |
| 30 to 34 | 3.20 |
| 35 to 39 | 3.40 |
| 40 to 43 | 4.75 |
| 44 to 47 | 5.32 |
| 48 to 49 | 9.58 |
| 48 to 49 | 15.96 |
| 48 to 49 | 3.32 |
| 48 to 49 | 8.37 |
| 48 to 49 | 4.75 |
| 48 to 49 | 2.60 |
| 30 to 34 | 3.20 |
| 35 to 39 | 3.40 |
| 40 to 43 | 4.75 |
| 44 to 47 | 5.32 |
| 48 to 49 | 9.58 |
| 48 to 49 | 15.96 |
| 48 to 49 | 3.32 |
| 48 to 49 | 8.37 |
| 48 to 49 | 4.75 |

It's easy to complain about advertisements.

Every week, millions of advertisements appear in the press, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice and are legal, decent, honest and truthful.

But if you find one that, in your opinion, is wrong in some way, please write to us at the address below.

We'd like you to help us keep advertising up to standard.

**The Advertising
Standards Authority.**



A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics – now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE
BOOK**

To ICS, Dept. N265, Intertext House,
London SW8 4UU

Name _____

Address _____

Age _____

ICS

To ICS, Dept. N265, Intertext House
London SW8 4UU
or telephone 01-622 9911 (all hours)

ADVERTISEMENT INDEX

| | | | |
|----------------------------------|--------------|------------------------------|---------|
| Acorn Computers | 87 | LEM Services | 109 |
| Akhter Instruments | 11 | Magenta Electronics | 110 |
| Ambit International | 103 | Manor Supplies | 113 |
| Amtron (UK) Ltd | 115 | Marshalls | 25 |
| Audio Electronics | 7, 16 & 116 | Mawson Associates | 99 |
| Aukdio Video Services | 113 | Memotech | 13 |
| Baydis | 44 | Micro Times | 114 |
| Bi-Pak Semiconductors | 15 | Midwich Computer Co | 8 |
| BK Electronics | 92 & 111 | Namal Associates | 112 |
| Black Star Ltd | 7 | OK Machine & Tool | 110 |
| B.N.R.S. | 24 | Parndon Electronics | 85 |
| Boss Instrustrial | 98 | T. Powell | 80 |
| Braithwaite Kits | 107 | Powertran | 2 & 123 |
| Calculator Sales & Service | 86 | Rapid Electronics | 18 |
| Cambridge Learning | 44 | J.W. Rimmer | 49 |
| C.H.J. Supplies | 111 | Riscomp | 13 |
| Chiltmead | 107 | R.T.V.C. | 77 |
| Chordgate | 44 | Safgan Electronics | 18 |
| Chromasonics | 97 | Shure Electronics Ltd | 124 |
| Chromatronics | 8 | Silica Shop | 100 |
| Clef Products | 85 | Silicon Speech Systems | 80 |
| Crimson Electric | 113 | Sinclair Research | 34 & 35 |
| Crofton Electronics | 93 | Swanley Electronics | 114 |
| Delta Tech & Co | 28 | Swift of Wilmslow | 113 |
| Display Electronics | 108 | Target Electronics | 98 |
| E.D.A. | 99 | Technomatic | 23 |
| Electro Supplies | 109 | Teleradio | 99 |
| Electronize Design | 106 | Tempus | 6 & 7 |
| Electrovalue | 16 | Texas Instruments | 80 |
| Greenbank | 36 | Timedata Ltd | 114 |
| Greenweld | 109 | TK Electronics | 104 |
| G.S.C. | 29 | Vero Electronics | 86 |
| Happy Memories | 93 | Videotone | 49 |
| Heath Electronics | 93 | Watford Electronics | 5 |
| Henrys Radio | 18, 85 & 91 | Wetab, Wallden Trading | 99 |
| ILP Electronics | 30 & 31 & 85 | Wilmslow Audio | 105 |
| LB Electronics | 115 | Yale Security Products | 13 |
| L & B Electronics | 112 | | |

When you're ready to "face" the music we have a tip for reduced distortion

The hyperelliptical stylus tip, acclaimed for its low distortion and high trackability, is now available in a whole series of Shure pickups. Whether you're seeking to reproduce the full dynamic range of today's new superdiscs, or simply to obtain maximum listening pleasure from treasured records in your collection, you'll find an HE pickup with the combination of features and performance that best meets your needs from the list below.

V15 Type IV

Perfectionist's Choice! With unprecedented trackability, ultra-flat response, Dynamic Stabilizer, low effective stylus mass.

V15 III-HE

One of the best-selling pickups ever! Performance second only to the V15 Type IV - but at a more modest price.

M97HE

Top-of-the-line features and excellent performance at an intermediate price. Features Dynamic Stabilizer and SIDE-GUARD stylus protector.

M97HE-AH The Headliner™

All the design and performance of the M97HE plus the simplicity of plug-in connection. Allows instant attachment to the tone arm of most turntables.

M95HE

Features high trackability, flat frequency response, low-loss/high output magnetic pole piece, at a modest price.

M75HE Type 2

NEW!

The first time HE stylus offered in such a low price range! High trackability, and excellent performance.

M75HE-J Type 2

NEW!

Designed to deliver the best performance from heavier tracking tone arms. Exceptionally modest price.

V15LT & M97LT (Linear Tracking Models)

NEW!

Get the most from advanced technology linear tracking turntables! Performance comparable to V15 Type IV and M97HE (respectively).

MV30HE

Sleek, integral pickup/carrier arm combination for use with SME Series III and SME Series IIIS tone arms. Performance similar to V15 Type IV.

For more information about Shure pickup cartridges please write to us at the address below

Setting the World Standard in Sound



Shure Electronics Limited

Eccleston Road


Maidstone ME15 6AU

Telephone: Maidstone (0622) 59881

The HE Family: Hyperelliptical-Equipped



V15 Type IV
¾-1¼ grams

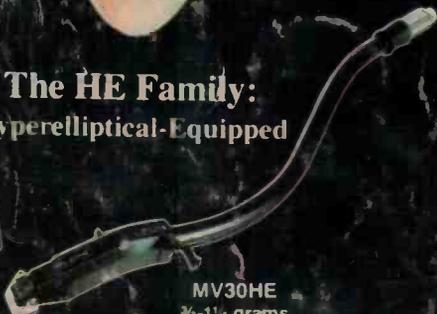

MV30HE
¾-1¼ grams



V15 LT
1¼ grams



V15 Type III-HE
¾-1¼ grams



M97HE
¾-1½ grams



M97HE-AH
(with attached headshell)
¾-1½ grams



M97 LT
1¼ grams



M95HE
¾-1½ grams



M75HE Type 2
¾-1½ grams



M75HE-J Type 2
1¼-2½ grams