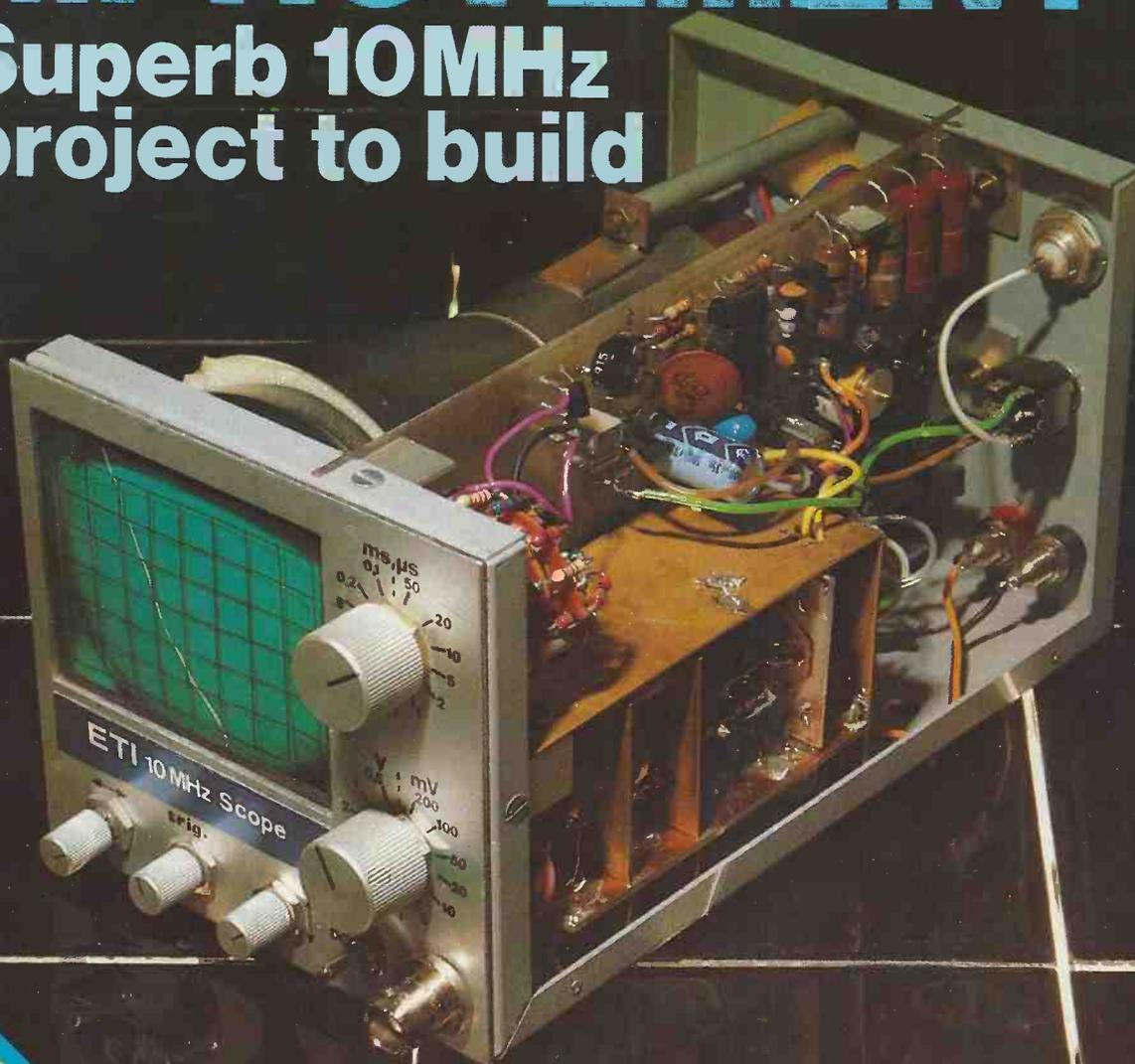


## SCOPE FOR IMPROVEMENT?

### Superb 10MHz project to build



**ENGINEERS GUIDE TO PRINTERS**  
Full technical details on hard copy peripherals

- **Insulation Tester:** Makes rewiring quick, easy and safe!
- **Slot-car controller:** Novel design techniques
- **Electro-music circuits** to try from Tim Orr

# POWER PACKED — by POWERTRAN

Powertran's black boxes are packed with punch. Not only are they superb kits to buy and build they really do the job! Imaginative and ingenious design goes hand in hand with top quality materials and outstanding performance capability. With their smart black styling the kits harmonise visually as well as musically.

Your can build each unit independantly for its set task and then gradually increase your array until you have a complete bank of formidable controllable power.

THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS — SEE INSIDE BACK COVER OF THIS ISSUE!



Complete Kit — £49.90 + VAT

**MPA 200** is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first-time builder.



Complete Kit — £49.50 + VAT

**CHROMATHEQUE 5000** — a 5-channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single-board design.



Complete Kit — £175.00 + VAT

**ETI VOCODER** — 14 channels, each with independent level control, for maximum versatility and intelligibility; Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts.



Complete Kit — £64.90 + VAT

**SP2 200** twice the power with two of the reliable, durable and economic amps from the MPA200; fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over!) the standard of high priced factory-built units.



**DJ90 Stereo Mixer** — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything...the whole works — AND — under £100 complete! (We have illustrated the DJ90 teamed in our own console with the Chromatheque and an SP2 200 and speakers.

Complete Kit — £97.50 + VAT



**Digital Delay Line** — our latest kit! With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo & vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,000! Complete kit (400 mS delay) **£130** + VAT. Parts for extra 400 mS delay £9.50p.

..... Quite simply the best way to make music

# POWERTRAN



## WORLD LEADERS IN ELECTRONIC KITS

- **Money Back Guarantee** — If you are not completely satisfied with your Powertran Kit return it in original condition within 10 days for full refund.
- **Free Soldering Practice Kit** — To assist the beginner we will supply, on request with your first kit order, a free soldering practice kit with useful tips and illustrations.
- **Component Packs** — Most-kits are available as separate packs (e.g. PCB component sets, hardware sets etc). Prices in our FREE catalogue.
- **Ordering** — Full ordering details, delivery service, and sales counter opening — outside back of this issue.


PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

ORDER BY PHONE  
(0264) 64455  
Simply telephone us with your order and quote your Access or Barclaycard number.  
FREE CATALOGUE  
FULL DETAILS OF ALL OUR KITS

# electronics today

INTERNATIONAL

MAY 1982 VOL 11 NO 5

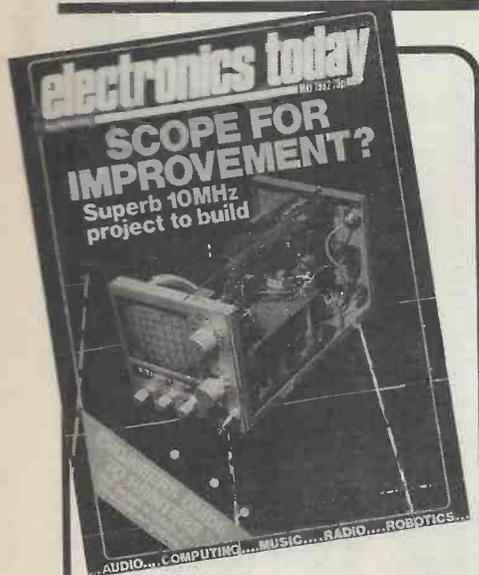

**Ron Harris B.Sc** : Editor  
**Peter Green** : Assistant Editor  
**Tina Boylan** : Editorial Assistant  
**Rory Holmes** :  
**Phil Walker** : Project Editors  
**Alan Griffiths** : Advertisement Manager  
**T.J. Connell** : Managing Director

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 145 Charing Cross Road, London WC2H 0EE.

**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)

**PRINTED BY:**  
 QB Limited, Colchester.

**COVERS PRINTED BY:**  
 Alabaster Passmore.

**OVERSEAS EDITIONS and their EDITORS**  
 AUSTRALIA — Roger Harrison  
 CANADA — Halvor Moorshead  
 GERMANY — Udo Wittig  
 HOLLAND — Anton Kriegsman



Member of the  
 Audit Bureau  
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. ©1982 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.


□ Subscription Rates. UK £11.95 including postage. Airmail and other rates upon application to ET1 Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

## EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.  
 Telex 8811896.
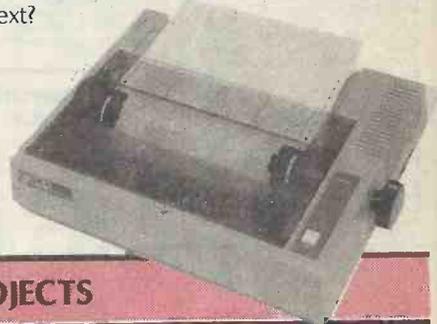
## FEATURES

- DIGEST** ..... 9  
 A light-hearted look at the latest news on the electronics scene.
- COLUMN LOUDSPEAKER DESIGN** . . . 17  
 Throw your sound into the audience and you can avoid nasty feedback. We tell you how to do it on the cheap.
- AUDIOPHILE** ..... 28  
 Our reviewer settles back in his armchair to appraise yet another piece of hi-fi hardware.
- ENGINEERS' GUIDE TO PRINTERS** . . . 40  
 Puzzled by printing peripherals? Our article will guide you in your choice of machine.
- ELECTROMUSIC TECHNIQUES PART 2** ..... 47  
 A veritable plethora of musically-oriented circuits. Turn to the second of Tim Orr's design series and be enthralled.
- TECH TIPS** ..... 60  
 More of the circuits dreamed up by our inventive readership.
- DESIGNER'S NOTEBOOK** ..... 67  
 Why get up and walk across the room to turn off your hi-fi when you can do it by remote control and quietly vegetate?
- CROSSWORD NO. 3** ..... 76  
 Reach for the dictionary and win yourself some money.
- READ/WRITE** ..... 86  
 Two whole pages of readers unburdening themselves — in public too. Whatever next?



## PROJECTS

- ECONOMICAL HEATER CONTROLLER** ..... 22  
 Fight back against the fuel bills! Time your appliances with this gadget and save yourself some money.
- ROBOT CONTROLLER PART 3** ..... 34  
 Construction for last month's PWM board.
- SOUND EFFECTS 3** ..... 63  
 Build the Phasor and Explosion board and pretend you're killing Klingons; a must for all closet Captain Kirks.
- OSCILLOSCOPE** ..... 53  
 No, your eyes don't deceive you — this month we describe a constructional project that results in a high quality piece of test gear.
- INSULATION TESTER** ..... 73  
 Make certain you don't get caught shorted by building this extremely-high-resistance meter.
- SLOT CAR CONTROLLER** ..... 79  
 This gadget has so many extras that you'll only get more realism by driving a Formula One into your living room.
- SOUND EFFECTS 4** ..... 89  
 Our final effect is just a shot in the dark; it simulates a gun being fired.
- FOIL PATTERNS** ..... 92

## INFORMATION

- NEXT MONTH'S ETI** ..... 15  
**BOOK SERVICE** ..... 27  
**PCB SERVICE** ..... 45
- ELECTRONICS DIGEST** ..... 65  
**NEXT MONTH'S HE** ..... 71



**SWITCHES**  
 TOGGLE: 2A, 250V, SPST 33p  
 DPDT 44p

**SUB-MIN TOGGLE**  
 SPST on/off 54p  
 SPDT covered 60p  
 SPDT centre off 85p  
 SPDT biased both ways 105p  
 DPDT 6 tags 75p  
 DPDT centre off 88p  
 DPDT biased both ways 145p  
 DPDT 3 positions on/off 185p  
 3-pole 2 way 205p

**SLIDE 250V**  
 DPDT 1A 14p  
 DPDT 1A c/off 15p  
 DPDT 1A 13p

**PUSHBUTTON 6A**  
 with 10mm Button  
 SPDT latching 99p  
 SPDT latching 145p  
 SPDT moment 99p  
 DPDT moment 145p

**Mini Non Locking Push to Make Push to Break** 15p

**DIL SWITCHES**  
 (SPST) 4 way 70p; 6 way 85p;  
 8 way 90p; 10 way 145p.  
 (SPDT) 1 way 190p.

**ROTARY SWITCHES:**  
 (Adjustable Stop type)  
 1 pole/2 to 12 way; 2p/2 to 6 way;  
 3 pole/2 to 4 way; 4p/2 to 3 way 45p

**ROTARY:** Mains DP 250V 4 Amp on/off 56p

**ROTARY:** (Mak-a-switch)  
 Make a multiway switch. Shafting assembly has adjustable stop. Assembles up to 6 wafers (max. 6 pole/12 way + DP switch). Mechanism only 90p

**WAFERS:** (make before break) to fit the above switch mechanism.  
 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6p/2 way  
 Mains DP 4A Switch to fit  
 Spacers 4p. Screen 6p

**ROCKER 5A/250V SPST** 28p  
**ROCKER: 10A/250V SPDT** 38p  
**ROCKER: 10A/250V DPDT c/off** 95p  
**ROCKER: 10A/250V DPST with neon** 85p

**VEROBOARD 0.1in**

1/2 x 3/4	73p	52p
2 1/2 x 5	83p	
3 3/4 x 3 3/4	83p	
3 3/4 x 5	95p	71p
3 3/4 x 17	326p	219p
4 3/4 x 17	426p	

Pkt. of 100 pins 50p  
 Spot face cutter 112p  
 Pin insertion tool 16p

**VQ Board** 150p  
**DIP Board** 130p  
**Vero Strip** 44p

**PROTO DECS** 375p  
 Veroblock 350p  
 S-Dec 520p  
 Eurobreadboard 520p  
 Binboard 1 785p  
 Superstrip SS2 1350p

**FERRIC CHLORIDE**  
 1 lb bag Anhydrous 195p  
 50p P&P

**DALO ETCH RESIST PEN** 90p  
 + Spare tip

**ULTRASONIC TRANSDUCER** 40KHz 395p pr

**COPPER CLAD BOARDS**

Fibre Single sided	Double sided	S.R.P.B
6" x 12"	90p	110p
6" x 12"	150p	95p
6" x 12"	150p	95p

**DIL SOCKETS (8X18)** Lot Prof. Wire Wrap

8pin	8p	25p
14pin	10p	35p
16pin	10p	42p
18pin	16p	52p
20pin	22p	60p
22pin	22p	60p
24pin	25p	70p
28pin	28p	80p
36pin	—	109p
40pin	30p	99p

**EDGE CONNECTORS:** (Double type)

2 x 15 way	—	140p
2 x 18 way	180p	145p
2 x 22 way	199p	200p
2 x 23 way	210p	—
2 x 25 way	225p	220p
2 x 30 way	245p	—
2 x 36 way	295p	—
2 x 40 way	315p	—
2 x 43 way	395p	—
2 x 75 way	550p	—

**D CONNECTORS (Cannon type)**

Pins	Plugs	Sockets	Covers	Soldercon
9 way	90p	110p	100p	100 pins
15 way	130p	160p	98p	70p
25 way	160p	210p	95p	500 pins
37 way	250p	350p	135p	325p

**PLUGS & SOCKETS**

**IDC HEADERS (Speed block type)**

IC Header PCB	Plug
With Free Strt. Angl	
Latch Sckt. pins	
2 x 5 way	90p 85p 60p 65p
2 x 8 way	130p 110p 70p 78p
2 x 10 way	145p 125p 80p 90p
2 x 13 way	175p 150p 95p 110p
2 x 17 way	200p 160p 110p 135p
2 x 20 way	220p 190p 125p 150p
2 x 25 way	235p 200p 150p 175p
2 x 60 way	— 230p 200p 220p

**EURO CONNECTORS**

DIN41618 31 way	180p	195p
DIN41612	—	—
2 x 32 way	295p	350p
DIN41612	3 x 32 way	388p 425p 470p

**RIBBON CABLE** Grey Color

10 way	12p	22p	14 pin	44p	99p
16 way	18p	32p	16 pin	49p	105p
20 way	25p	40p	24 pin	88p	178p
24 way	35p	50p	40 pin	250p	255p
34 way	48p	60p	—	—	—
40 way	55p	75p	—	—	—
50 way	65p	90p	—	—	—

**DIL PLUG HEADERS**

14 pin	44p	99p
16 pin	49p	105p
24 pin	88p	178p
40 pin	250p	255p

**ZERO INSERTION FORCE DIL SOCKETS** 24 way 650p  
 28 way 820p

**25 way 'D' CONNECTORS** Plug Socket  
 PCB Pins 200p 245p  
 RT. angle 210p 275p

We stock many more Plugs, Sockets and Jumper Leads.

**25 way 'D' CONNECTOR** Jumper Lead Cable Assembly  
 18" long, Single End, Male 650p  
 18" long, Single End, Female 670p  
 36" long, Double Ended, M/M 1328p  
 36" long, Double Ended, F/F 1318p  
 36" long, Double Ended, M/F 1275p

**ANTENNE SOLDERING IRON**  
 C.15W 420p; CX17W 430p;  
 CCN-15W 440p; CX25W 445p.  
 Spare tips, assorted sizes 210p  
 Iron stand with sponge 160p

**PANEL METERS**

60x46x35mm

0-50uA	120p
0-10mA	120p
0-500uA	120p
0-1mA	120p
0-5mA	120p
0-10mA	120p
0-50mA	120p
0-500mA	120p
0-10A	120p
0-2A	120p
0-25V AC	120p
0-300V AC	120p
0-500V AC	120p

495p each

**CRYSTALS**

32.768KHz	150
100KHz	270
200KHz	295
455KHz	370
1MHz	226
1.008M	290
1.28MHz	392
1.6MHz	395
1.8MHz	395
1.8432M	220
2.0MHz	240
2.4675M	220
3.278M	220
3.5794M	150
3.6864M	300
4.032MHz	230
4.19430M	200
4.43619M	120
5.0MHz	200
5.185MHz	300
5.2268M	330
6.144MHz	240
6.5636MHz	250
7.168MHz	250
7.68MHz	200
8.0MHz	200
8.85723M	240
9.00MHz	200
10.0MHz	200
10.24MHz	200
11.7	220
12.0MHz	290
14.316MHz	240
16.0MHz	250
18.0MHz	240
18.432M	240
19.968MHz	325
24.0MHz	250
26.59	250
27.848M	330
27.145M	240
38.6667M	290
48.0MHz	270
100.0MHz	375
116.0MHz	300

**CONTINENTAL Cradle Type Relays:**  
 Miniature Plug-in relays, 110V DC;  
 12 V AC, 2 A DC; 2.5 A AC  
 30V/100V;  
 2 pole c/over 185V; 6V-18V RL201;  
 2 pole c/over 13V to 35V; 7001;  
 RL202;  
 4 pole c/over 9V to 18V; 1851;  
 RL203;  
 High Power "Heavy Duty" PCB  
 Mountain, Cradle type,  
 S.P.C.O. Power Gain 1:8000 380V  
 AC/16A; 3.5k VA, 8 to 19V; 190M  
 295p

**PIEZO TRANSDUCERS**  
 Type PB-2720 75p

**BUZZERS**, miniature, solid-state  
 6V, 9V, 12V 70p

**LOUDSPEAKERS**  
 Miniature, 0.3W; 8Ω;  
 2in, 3in, 2 1/2in, 3in  
 2 1/2in 4011, 6411 or 8011 80p

**GAS & SMOKE DETECTORS**  
 For the detection of combustible and  
 toxic gases like: Propane, Butane,  
 Methane, Ammonia, Carbon Monoxide.  
 Sulphur and Organic solvents vapours  
 like Alcohol, Benzene, etc. ideal for  
 use in Boats, Caravans etc.  
 Type: TG5812 & 813 525p  
 Socket for above 40p

**ASTEC UHF MODULATORS**  
 Standard 6MHz 280p  
 Wideband 8MHz 425p

**ETI Autoringing Digital Capacitance Meter.** All parts available.

**DIL PLUGS**

14pin	44p
16pin	49p
24pin	88p
40pin	250p

**JUMPER LEADS (Ribbon Cable Assembly)**

Length	14 pin	16 pin	24 pin	40 pin
Single ended DIP Jumper	145p	165p	240p	380p
Double ended DIP Jumper	180p	205p	300p	465p
6 inches	198p	215p	315p	490p
12 inches	210p	235p	345p	540p
24 inches	230p	260	375p	595p
36 inches	—	—	—	—

**AMPHENOL PLUGS**

IEEE (24 way)	675p
Centronic panel (36 way)	550p

**TRANSFORMERS:** Prim. 240V

6-0-6V; 9-0-9V; 12-0-12V 100mA	98p
pcb mounting, Miniature, Sp. Bobbin	
3VA; 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A;	
2x15V-0.1A	200p
6VA; 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A;	
2x15V-0.2A	270p

Standard Split Bobbin type:

6VA; 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A;	
2x15V-0.25A	340p (60p p&p)
12VA; 2x4.5V-1.3A; 2x6V-1A; 2x9V-0.6A;	
2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A	350p (60p p&p)
24VA; 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A;	
2x15V-0.8A; 2x20V-0.6A	330p (60p p&p)
50VA; 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A;	
2x20V-1.2A; 2x25V-1A; 2x30V-0.8A	440p (60p p&p)
100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A;	
2x25V-2A; 2x30V-1.5A; 2x50V-1A	920p (75p p&p charge to be added over and above our normal postal charge)

**VOLTAGE REGULATORS**

1A TO220	Plastic Casing	7905	55p
5V 7805	45p	7908	70p
12V 7812	50p	7912	55p
15V 7815	50p	7915	55p
18V 7818	50p	7918	55p
24V 7824	50p	7924	70p

**100mA TO92 Plastic Casing**

5V 78L05	30p
6V 78L06	30p
8V 78L08	30p
12V 78L12	30p
15V 78L15	30p

**CA3085** 95p  
 LM300H 170p  
 LM3004H 170p  
 LM305H 140p  
 LM305B 135p  
 LM317K 35p  
 LM317KP 35p  
 LM317H 28p  
 LM317T 125p  
 LM323K 500p  
 LM323T 445p  
 LM326N 240p  
 LM723 35p  
 TAA550 50p  
 TBA625B 75p  
 TDA1412 150p  
 78H05 + 5V/5A 550p  
 78H4G + 5V to +25V 5A 599p  
 79H-2 25V to 24V 5A 785p

**WATFORD'S UNIVERSAL MICRO EXPANSION SYSTEM**

Designed by Watford Electronics, this extremely versatile and economical Expansion System as published in E.T.I., starting from December 1981 issue, offers a low cost flexible expansion system for: ZX81, UK101, SUPERBOARD, Acorn ATOM, PET, TANGERINE, TRS80, VIC 20, etc.

The Motherboard (interfaces with the Computer) has capability to accept up to five daughter Cards and can be paralleled for even more daughter cards.

All PC Boards are of Computer grade and are supplied in Kit form.

Just look at the Expansion possibilities:

**MOTHERBOARD:** Accepts up to five Daughter Cards. Full Kit: £36.50  
**SOUND CARD** - Utilising up to three AY-3-8910 sound chips. 10ne supplied with Kit). Full Kit: £24.95  
**PIO Card** - Using two 6520 PIO chips, this Board offers centronics parallel printer driver, digital to analogue converter & a host of other output facilities. Full Kit: £25.95  
**PROM Programmer** - This simple but extremely useful card can blow 2716 or 2732 single level EPROMS. Full Kit: £19.95  
**PROM Card** - P.C.B. cards for housing four 2716 or two 2732 EPROMS.  
 For 4 x 2716 Full Kit: £11.95  
 For 2 x 2732 Full Kit: £11.75  
**RAM Card** - 8K RAM card, Accepts 16 x 2114 chips. Supplied fully populated. Full Kit: £28.80  
**Coming soon:** Speech Card, Disc Interface Card; 32K Dynamic RAM Card; High Resolution colour graphics Card.  
 (N.B. P.C.B.s may be bought separately)

**WATFORD'S BUSHOP CORNER**

Texas TTL Data Book (Revised Edition) 850p  
 TTL Cook-Book 930p  
 European CMOS DataBook (Comprehensive) 795p  
 CMOS Cook-Book 895p  
 Illustrating BASIC 440p  
 A Bit of BASIC 540p  
 Advanced BASIC 840p  
 BASIC Computer Games 590p  
 More BASIC Computer Games 590p  
 Some Common BASIC Programs 1150p  
 Practical BASIC Programs 1250p  
 6502 Software Applications 910p  
 6502 Application Book 1020p  
 Programming the 6502 (C202) 1100p  
 Programming & interfacing the 6502 1120p  
 6502 Assembly Language Programming 1300p  
 6809 Assembly Language Programming 1350p  
 Practical Intro to PASCAL 550p  
 Using CP/M: A self teaching guide 950p  
 Z80 Microcomputer Handbook 840p  
 8080/280 Assembly Lang. Techniques 925p  
 Programming the Z80 (C280) 1250p  
 Z80 Assembly Language Programming Intro to TRS-80 Graphics 840p  
 TRS80 BASIC - A self teaching guide 840p  
 PET & the IEEE 488 Bus (GP1B) 1350p  
 PET Graphics 1200p  
 PET/IBM Personal Computer Guide 1200p  
 PET Revealed 1000p  
 Library of PET Subroutines 1000p  
 Apple II Users' Guide 1250p  
 Programming in PASCAL (revised) 900p  
 CRT Controller Handbook 650p  
 CP/M Handbook with MP/M 1200p  
 Microcomputer Interfacing Technique 1350p  
 S100 & Other Micro Buses 3E 750p  
 Writing Interactive Compiler 750p  
 Getting Acquainted with your ZX81 500p  
 Mastering Machine Code on your ZX81 600p  
 ZX81 Companion 800p  
 ZX81 Pocket Book 650p  
 32 BASIC Programs for the PET Computer 1350p  
 PIC Revealed 1000p

Please add 55p P&P charge on books  
 No VAT on books

**CUSTOMER:** How can WATFORD sell full spec devices so cheaply?  
**WATFORD:** It's simple. By bulk buying (direct from manufacturers where possible), low overheads and smaller margins which give us an edge over our competitors.

**CMOS**

4000	14	4073	20	4532	110
4001	14	4075	20	4534	500
4002	14	4076	60	4536	295
4005	66	4078	26	4538	113
4007	18	4078	26	4540	17
4008	62	4081	26	4541	140
4009	35	4082	21	4543	135
4010	40	4085	85	4544	150
4011	15	4086	70	4549	395
4012	18	4089	140	4553	299
4013	34	4093	43	4555	50
4014	75	4094	168	4555	50
4015	66	4095	90	4556	55
4016	32	4096	90	4557	320
4017	48	4097	320	4558	120
4018	68	4098	88	4559	395
4019	42	4099	95	4560	180
4020	61	4100	95	4561	104
4021	70	4101	95	4562	495
4022	96	4102	99	4566	175
4023	20	4103	99	4568	250
4024	45	4174	99	4569	175
4025	19	4175	106	4572	36
4026	130	4192	00	4580	460
4027	38	4194	105	4581	250
4028	58	4208	790	4582	99
4029	77	4409	99	4583	175
4030	50	4410	725	4584	48
4031	170	4411	695	4585	99
4032	125	4412	800	4597	330
4033	185	4415	480	4598	290
4034	195	4419	280	4599	595
4035	95	4422	770	4600	88
4036	275	4428	00	40098	193
4037	115	4433	770	40100	215
4038	110	4435	850	40101	130
4039	290	4440	999	45002	180
4040	59	4450	350	40103	175
4041	78	4451	350	40104	95
4042	60	4490	350	40105	115
4043	70	4500	675	40106	75
4044	65	4501	28	40107	60
4045	170	4502	99	40108	450
4046	75	4503	50	40109	100
4047	75	4504	105	40110	300
4048	55	4506	65	40114	240
4049	30	4507	40	40161	194
4050	30	4508	265	40163	90
4051	78	4510	68	40174	65

# Sinclair ZX81 Personal Comp the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

## Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



**New BASIC manual**

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC – from first principles to complex programming.

## Kit: £49.<sup>95</sup>

### Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



## Built: £69.<sup>95</sup>

### Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



uter-



## Available now- the ZX Printer for only £49.<sup>95</sup>

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha- numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

## 16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

### How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95
<input type="checkbox"/> Please tick if you require a VAT receipt				TOTAL £
*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £				
*Please charge to my Access/Barclaycard/Trustcard account no.				
*Please delete/complete as applicable				
Name: Mr/Mrs/Miss				Please print.
Address:				
FREEPOST - no stamp needed. Offer applies to UK only.				ETI 05

# sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: (0276) 66104 & 21282.

# Rapid Electronics

Tel: 0206 36412  
Hill Farm Industrial Estate  
Boxted, Colchester  
Essex CO4 5RD



## CAPACITORS

Polyester. Radial Leads. 250V 280type.  
0.01, 0.015, 0.022, 0.033, 6p, 0.047, 0.068, 0.1, 1.7p;  
0.15, 0.22, 9p; 0.33, 0.47, 13p; 0.68, 20p; 1u 23p.

Electrolytic Radial or Axial leads  
0.47/63V, 1/63V, 2/2/63V, 4.7/63V, 10/25V, 7p;  
22/25V, 47/25V, 8p; 100/25V, 9p; 220/25V, 14p;  
470/25V, 22p; 1000/25V, 30p.

Polyester. Siemens PCB  
1n, 2n2, 4n3, 4n7, 6n8, 10n, 15n, 7p; 22n, 33n, 47n, 68n, 8p;  
100n, 9p; 150n, 11p; 220n, 13p; 330n, 20p; 470n, 26p;  
680n, 29p; 1u, 33p; 2u, 50p.

Tantalum bead  
0.1, 0.2, 0.33, 0.47, 1.0 @ 35V 12p; 2.2, 4.7, 10 @  
25V, 20p; 15/16V 30p, 22/16V, 27p; 33/16V, 45p;  
47/6V, 27p; 47/16V, 70p; 68/6V, 40p; 100/10V, 90p.

Ceramic 22p-0.01u, 50V, 3p each.  
\* Mullard Miniature ceramic plate.  
1.8pF to 100pF, 6p each.  
Polystyrene 5% tolerance  
10p-100p 6p, 150p-470p 8p, 680p-0.012 10p.  
Trimmers, Mullard 808 Series.  
2-10pF 22p, 2-22pF 30p, 5.5-65pF 35p.

## COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at reduced prices.

1/4W 5% Resistor Kit. Contains 10 of each value from 4.7Ω to 1M (650 resistors) 480p.

Ceramic Capacitor Kit. Contains 5 of each value from 22p to 0.01 (135 caps) 370p.

Polyester Capacitor Kit. Contains 5 of each value from 0.01 to 1uF (65 caps) 375p each.

Presets Kit. Contains 5 of each. Value from 100Ω to 1M (total 65 presets). 425p each.

Nut and Bolt Kit. Total 300 items. 140p.

25 6BA 1/4" bolts  
25 4BA 1/4" bolts  
25 6BA 1/2" bolts  
50 6BA nuts  
50 6BA washers

## POTENTIOMETERS

Rotary. Carbon track Log or Lin 1K-2MΩ.  
Single 32p. Stereo 85p  
Slide 60mm travel single  
Log or Lin 5K-500K, 63p.  
Presets. Submin horiz.  
100M-1M 7p each

## BRIDGE RECTIFIERS

1A 50V	22	18 0M	240
1A 400V	35	18 432M	220
2A 200V	40	19 968M	300
2A 400V	45	38 6667M	320
6A 100V	80	48 0M	220
6A 400V	95	116M	300

VN18 DIL  
0.9A 200V

## OPTO

\* 3mm red 8  
\* 3mm green 12  
\* 3mm yellow 12

Clips to suit 3p each

Rectangular	TIL 32	40
* red	TIL 78	40
green	TIL 111	60
yellow	ORP12	85
TIL 38	TIL 100	90

Seven Segment Displays

Com. cathode	DL704 0.3"	95
* FND500 0.5"	TIL 412 0.1"	105
* TIL 313 0.3"	TIL 321 0.5"	115
TIL 322 0.5"		115

All seven segment displays are supplied with connection details 2N5777 45 Dual Colour LED 60

## CRYSTALS

100KHz	290
200KHz	370
1MHz	300
1.000M	370
1.8432M	300
2.0M	270
2.4576M	220
3.276M	240
3.579M	120
4.0M	150
4.194M	150
4.43M	125
5.0M	240
6.0M	200
6.144M	180
7.00M	250
8.0M	170
10.0M	180
12.0M	290
16.0M	240
18.0M	240
18.432M	240
19.968M	300
38.6667M	320
48.0M	220
116M	300

## BOXES

Dimensions in inches. Aluminium

3 x 2 x 1	70p	6 x 4 x 2	120p
4 x 1 x 1.5	85p	6 x 4 x 3	150p
4 x 3 x 2	100p	8 x 6 x 2	180p

Plastic Project Boxes  
Complete with lid and screws

1 x 2 x 1in. 55p
4 1/2 x 3 x 1 1/2in. 80p
7 x 4 x 2in. 160p

Switches

Submit Toggle  
SPST 55p DPDT 60p \* DPDT 50p

Miniature Toggle  
SPDT 80p DPDT centre off 90p  
DPDT 90p DPDT centre off 100p

Standard toggle  
SPST 35p DPDT 48p

\* Miniature DPDT Slide 12p  
\* Push to make 12p Push to break 22p

Rotary type adjustable stop  
1P12V, 2P2W, 3P4W, 4P3W all 55p each

DIL switches  
4 SPST 80p 6 SPST 80p 8 SPST 100p

## CABLES

20 metre pack single core connecting cable, ten different colours 65p

Speaker cable 10p/m

Standard screened 16p/m

Twin screened 24p/m

2 5A 1 core mains 22p/m

10 way ribbon 65p/m

21 way ribbon 120p/m

## OPTO SPECIALI

Special pack containing thirty 5mm LEDs. Ten red, ten green, ten yellow.

Our normal price is 320p.

Special Offer price just 250p!

Offer expires 30th April 82.

Please note these are top quality grade 1 devices.

## HARDWARE

PPH Battery clips 6p

Red or black crocodile clips 6p

Black pointer control knob 15p

Pair Ultrasonics 350p

\* 6V Electronic buzzer 60p

\* 12V Electronic buzzer 65p

\* PBZ20 Piezo transducer 75p

TOTM transistor socket 15p

64mm 64 ohm speaker 70p

64mm 8 ohm speaker 70p

## PCB MATERIALS

Afac PCB transfer sheets - please state type (e.g. DIL pads etc.) 45p

Dale etch resist pen 70p

Fibre glass board 3.75" x 8" 100p

Ferric Chloride 250ml bottle 100p

## DIODES

\* Verobloc 350p

Size: 0.1 matrix

2.5 x 1"	22p
2.5 x 1.75"	75p
2.5 x 5"	85p
3.75 x 5"	95p

VQ Board 160p

Verobip per 100  
Single sided 50p  
Double sided 60p  
Spot face cutter 105p

BY127 12 \* 1N4001 3  
OA47 10 1N4002 5  
OA90 8 1N4006 7  
OA91 7 1N4007 7  
OA200 8 1N5401 15  
OA202 8 1N5404 16  
1N914 4 1N5406 17  
\* 1N4148 2 40kV 50V 6p  
\* 1Z561 Series 50p  
\* 1.3W 4W 3W 15p each.

## ORDERING INFO

All prices exclude VAT. Please add to total order. Please add 50p carriage on all orders under £10 in value. Send cheque/PO or Access/Visa number with your order. Please note our new address. Callers most welcome - we are just 10 minutes from the centre of Colchester. Telephone orders welcome with Access and Visa. Official orders welcome from colleges and schools etc. Export orders no VAT but please add carriage.

## TRIACS + SCRS

SCRS	TRIACS	
TIC45 28	400V 4A 60	
C106D 30	400V 8A 70	
400V 8A 70	400V 16A 105	
400V 12A 99		

## SOLDERING IRONS

Antex CX 17W Soldering Iron 2.5mm and 4.7mm bits to suit 420p

CX 17W element 55p

Antex X25 25W Soldering Iron 3.0mm and 4.7mm bits to suit 440p

X25 25W element 190p

Solder pump/desoldering tool 480p

Spare nozzle for above 70p

10 metres 22 swg solder 100p

## REGULATORS

Positive	Negative
* 78L05 25	79L05 65
78L12 30	79L12 65
78L15 30	79L15 65
* 7805 45	* 7905 45
* 7812 45	* 7912 45
7815 60	7915 60
LM309K 130	LM723 40
LM317K 320	LM338K 475
LM337T 120	78H05 40
LM323K 350	5A 5V 550

## CONNECTORS

DIN	Plug	Sket	Jack	Plug	Sket
2 pin	9p	9p	2.5mm	10p	10p
3 pin	12p	10p	3.5mm	* 7p	* 7p
5 pin	13p	11p	Standard	20p	20p
Phono	10p	12p	Stereo	14p	35p

1mm 13p 13p 4mm 18p 17p

UHF (CB) Connectors  
PL259 Plug 40p Reducer 14p  
SO239 Square chassis socket 38p  
SO239S Round chassis socket 40p

IFC 3 pin 250V/6A  
Plug chassis mounting 38p  
Socket free hanging 60p  
Socket with 2m lead 120p

## TRANSISTORS

AC125 35	BC158 10	BC558 10	BF X84 25	TIP 10	45	* ZTX107 8	1N2N3054 55
AC126 25	BC159 8	BC570 10	BF X85 25	TIP 10A	40	* ZTX108 8	1N2N3055 50
AC127 25	BC169C 10	BC572 18	BF X86 28	TIP 30	60	ZTX109 12	2N3442 120
* AC128 20	BC169K 10	BD131 35	BF X87 25	TIP 30C	50	ZTX130 14	* 2N3702 6
AC176 25	BC170 8	BD132 35	BF Y51 23	TIP 31B	45	ZTX 102 15	* 2N3704 6
AC187 22	BC171 10	BD133 50	BF Y52 23	TIP 32A	45	ZTX 104 15	2N3705 9
AD18 120	BC172 8	BD135 50	BF Y53 32	TIP 32B	55	ZTX 105 15	2N3706 9
AD19 80	BC173 18	BD137 30	BF Y54 32	TIP 32C	60	ZTX 106 15	2N3708 10
AD161 40	BC179 18	BD138 30	BF Y56 32	TIP 33A	50	ZTX 107 15	2N3709 10
AD162 40	BC182 10	BD139 35	BK X20 20	TIP 34A	75	ZTX 108 18	2N3722 190
AF124 60	* BC182L 8	BD140 35	BK X29 35	TIP 34C	85	ZTX 109 25	* 2N3731 210
AF129 40	BC183 10	BD141 35	BK X30 35	TIP 35A	160	ZTX 101 16	2N3703 70
AF139 40	BC184 10	BD142 110	BU 205 160	TIP 35C	180	ZN706A 20	2N3704 65
AF136 70	* BC184L 7	BF 180 35	BU 210 170	TIP 36C	195	ZN708 20	2N3866 90
BC107 10	BC212 10	BF 182 35	BU 215 170	TIP 41A	60	ZN709 35	2N3903 10
* BC108 9	BC212L 10	BF 183 35	BU 220 170	TIP 42A	60	ZN710 40	* 2N3905 6
BC108B 12	BC213 10	BF 185 25	BU 225 170	TIP 42B	60	ZN218A 25	2N4007 45
BC108C 12	BC214 10	BF 194 25	BU 230 170	TIP 42C	90	ZN219A 25	2N4017 45
* BC109 9	BC215 10	BF 195 12	BU 235 170	TIP 42D	90	ZN221A 25	2N4058 10
BC112 12	BC216 10	BF 196 12	BU 240 170	TIP 42E	120	ZN222A 20	2N4060 10
BC114 22	BC217 8	BF 197 12	BU 245 170	TIP 42F	120	ZN236A 25	2N4061 10
BC115 22	BC218 14	BF 204 10	BU 250 170	TIP 42G	120	ZN237A 25	2N4062 10
BC117 22	BC219 15	BF 209 10	BU 255 170	TIP 42H	90	ZN249A 25	2N4517 36
BC119 35	BC220 14	BF 210 10	BU 260 170	TIP 42I	90	ZN250A 45	2N4518 36
BC127 14	* BF 211 18	BF 211 18	BU 265 170	TIP 42J	40	ZN251A 45	2N4519 30
BC128 14	BC221 14	BF 212 18	BU 270 170	TIP 42K	40	ZN252A 45	2N4520 36
BC129 14	BC222 14	BF 213 18	BU 275 170	TIP 42L	40	ZN253A 45	2N4521 36
BC130 14	BC223 14	BF 214 18	BU 280 170	TIP 42M	40	ZN254A 45	2N4522 36
BC131 14	BC224 14	BF 215 18	BU 285 170	TIP 42N	40	ZN255A 45	2N4523 36
BC132 14	BC225 14	BF 216 18	BU 290 170	TIP 42O	40	ZN256A 45	2N4524 36
BC133 14	BC226 14	BF 217 18	BU 295 170	TIP 42P	40	ZN257A 45	2N4525 36
BC134 14	BC227 14	BF 218 18	BU 300 170	TIP 42Q	40	ZN258A 45	2N4526 36
BC135 14	BC228 14	BF 219 18	BU 305 170	TIP 42R	40	ZN259A 45	2N4527 36
BC136 14	BC229 14	BF 220 18	BU 310 170	TIP 42S	40	ZN260A 45	2N4528 36
BC137 14	BC230 14	BF 221 18	BU 315 170	TIP 42T	40	ZN261A 45	2N4529 36
BC138 14	BC231 14	BF 222 18	BU 320 170	TIP 42U	40	ZN262A 45	2N4530 36
BC139 14	BC232 14	BF 223 18	BU 325 170	TIP 42V	40	ZN263A 45	2N4531 36
BC140 14	BC233 14	BF 224 18	BU 330 170	TIP 42W	40	ZN264A 45	2N4532 36
BC141 14	BC234 14	BF 225 18	BU 335 170	TIP 42X	40	ZN265A 45	2N4533 36
BC142 14	BC235 14	BF 226 18	BU 340 170	TIP 42Y	40	ZN266A 45	2N4534 36
BC143 14	BC236 14	BF 227 18	BU 345 170	TIP 42Z	40	ZN267A 45	2N4535 36
BC144 14	BC237 14	BF 228 18	BU 350 170	TIP 42AA	40	ZN268A 45	2N4536 36
BC145 14	BC238 14	BF 229 18	BU 355 170	TIP 42AB	40	ZN269A 45	2N4537 36
BC146 14	BC239 14	BF 230 18	BU 360 170	TIP 42AC	40	ZN270A 45	2N4538 36
BC147 14	BC240 14	BF 231 18	BU 365 170	TIP 42AD	40	ZN271A 45	2N4539 36
BC148 14	BC241 14	BF 232 18	BU 370 170	TIP 42AE	40	ZN272A 45	2N4540 36
BC149 14	BC242 14	BF 233 18	BU 375 170	TIP 42AF	40	ZN273A 45	2N4541 36
BC150 14	BC243 14	BF 234 18	BU 380 170	TIP 42AG	40	ZN274A 45	2N4542 36
BC151 14	BC244 14	BF 235 18	BU 385 170	TIP 42AH	40	ZN275A 45	2N4543 36
BC152 14	BC245 14	BF 236 18	BU 390 170	TIP 42AI	40	ZN276A 45	2N4544 36
BC153 14	BC246 14	BF 237 18	BU 395 170	TIP 42AJ	40	ZN277A 45	2N4545 36
BC154 14	BC247 14	BF 238 18	BU 400 170	TIP 42AK	40	ZN278A 45	2N4546 36
BC155 14	BC248 14	BF 239 18	BU 405 170	TIP 42AL	40	ZN279A 45	2N4547 36
BC156 14	BC249 14	BF 240 18	BU 410 170	TIP 42AM	40	ZN280A 45	2N4548 36
BC157 14	BC250 14	BF 241 18	BU 415 170	TIP 42AN	40	ZN281A 45	2N4549 36
BC158 14	BC251 14	BF 242 18	BU 420 170	TIP 42AO	40	ZN282A 45	2N4550 36
BC159 14	BC252 14	BF 243 18	BU 425 170	TIP 42AP	40	ZN283A 45	2N4551 36
BC160 14	BC253 14	BF 244 18	BU 430 170	TIP 42AQ	40	ZN284A 45	2N4552 36
BC161 14	BC254 14	BF 245 18	BU 435 170	TIP 42AR	40	ZN285A 45	2N4553 36
BC162 14	BC255 14	BF 246 18	BU 440 170	TIP 42AS	40	ZN286A 45	2N4


# DIGEST

## 'Ears A Novelty

This new calculator has been specifically designed for Arab oil producers who wish to calculate up-to-the-minute profit figures while driving between oil wells. The device may be unobtrusively powered from the car battery via the discreet power lead, and for road safety one hand can always remain on the steering wheel since the buttons are operated by ear.

Well, that's what we first thought when this photograph fell out of our mail, but a glance at the accompanying press release revealed a more mundane explanation. Philips have received a share of an order from the Kingdom of Saudi Arabia for the delivery and installation of a national automatic mobile telephone network. Covering 32 cities and several of the nation's traffic corridors, the network involves 18,000 mobile telephones and 48 base-station sites, half of which are to be supplied by Philips. The full duplex system operates in the 420-470 MHz band and provides 866 channels nationwide. The mobile telephone network can be automatically connected into the 'fixed' telephone system, allowing any number in the world to be called. Facilities include a push-button dialling, dialled-number LCD display, automatic display/keyboard illumination to suit the lighting conditions, last-number recall and malicious-call tracing (wonder what the Saudi penalty for that is?). Naturally, the whole kaboodle is built round a microprocessor, and will give Saudi Arabia one of the most modern systems in the world.

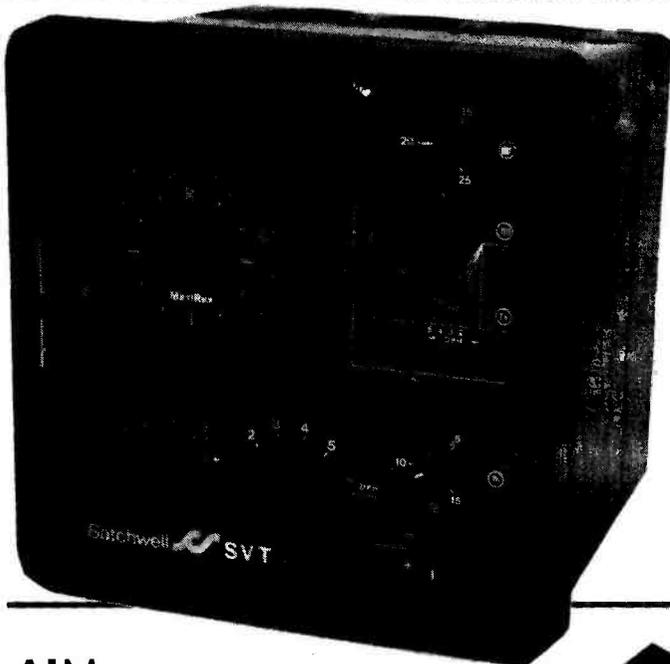Somehow our explanation seemed so much more fun...



## Satch A Good Idea


If you don't fancy a trip to London for the energy control seminar (see Save It!), for about the same money (£100) you can purchase a simple optimiser from the bottom end of the Satchwell control system range. This gadget, called the SVT, optimises the heating system in smaller commercial buildings and can allow companies whose fuel bills are only a few thousand pounds to recover the cost very quickly. Payback periods range from six months, to as little as 12 weeks in exceptional circumstances. The device is aimed at shops, small offices, clubs and so on who are presently unaware of the benefits of optimum start control. For more details contact Michael Edwards, Satchwell Control Systems Ltd, PO Box 57, Farnham Road, Slough, Berks SL1 4UH.

## Long Live Batteries

And now, the battery that goes on working, stops. Israel's Tel Aviv University has developed a unique lithium-sulphur battery which yields one of the highest energy densities available. The cell can be used for a period of up to 10 years, yet is more compact and cheaper to construct than conventional long-term batteries. Existing in prototype form only at present, projected uses include microcomputer power failure back-up, calculators and watches, inaccessible instrumentation (eg military equipment) and pace-makers, where you don't really want to stick new batteries in every couple of months.
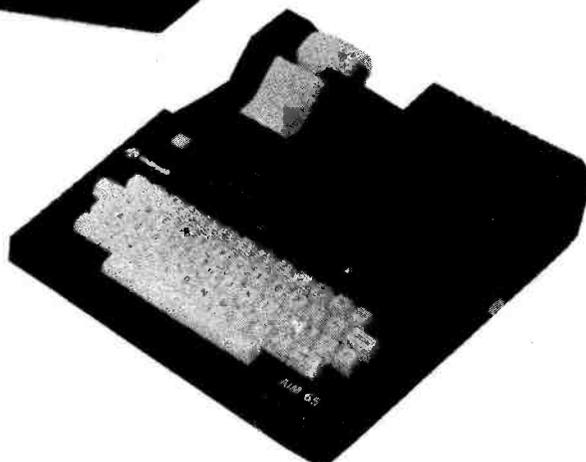
## AIM To Please

If you're a fan of the AIM 65 'bare-board' microcomputer you will doubtless be glad to know that you can now cover up its naked little body with an accessory enclosure from Rockwell. The ABS enclosure has a brown non-reflective crinkle finish, on-off and reset switches and internal AC lines. An optional power supply providing +5 V at 3 A and +24 V at 500 mA is also available with the enclosure. Available from all AIM 65 distributors as well as many computer store dealers, the enclosure has a retail price of about £90 with the PSU and £50 without.




## Save It!

Are you stuck in a mental rut as regards traditional mechanical and electrical devices? Do you worry about the energy costs of your company? Kill two birds with one stone and visit a one day seminar on microcomputers and energy conservation. The seminar, to be held on Tuesday 20th April at the CEGB in London EC1, will explore what computers can and cannot do to save energy, from controlling electricity demand to optimising combustion in boilers. The seminar fee is £100 plus VAT per delegate and further details can be obtained from Miss Mallory Barker, Scientific and Technical Studies, Norwich House, 11-13 Norwich Street, London EC4A 1AB (Tel. 01-242 2481).




# EXPRESS from MAPLIN

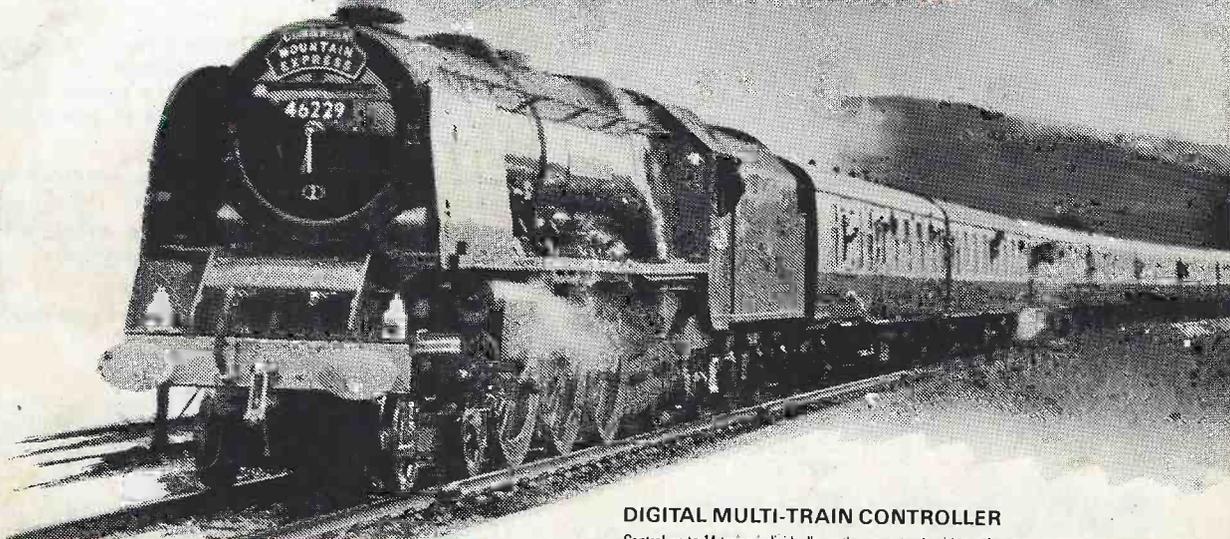
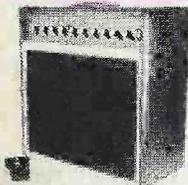
## COMBO-AMPLIFIER

Easy to build portable 120W MOSFET amp for all stage musicians. Built in flanger, five step equaliser, two inputs for guitars, keyboards or microphones, low-noise pre-amp.  
Full details in our book. Price 60p.  
Order As XA01B.



## DIGITAL MULTI-TRAIN CONTROLLER

Control up to 14 trains individually on the same track with any four simultaneously! Low cost kits available.  
Full details in our projects book. Price 60p.  
Order As XA02C.

Photo by W.A. Sharman.



## STOP-WATCH

Multi-mode 8-digit stopwatch accurate to hundredths of a second. Easy to build - complete kits available.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.




## HOME SECURITY SYSTEM

Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.
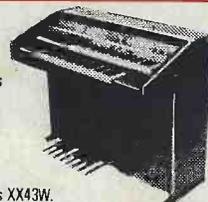
## MATINÉE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50.  
Order As XH55K.  
Complete kits available:  
Electronics - £299.95,  
Cabinet - £99.50 (carriage extra).  
Demo cassette price £1.99. Order As XX43W.



## MILES PER GALLON METER

Digital display shows you how economical your driving is as you go along.  
Complete kits available.  
Full details in our projects book.  
Price 60p.  
Order As XA02C.



\* Don't miss out - get a copy of our catalogue now!  
Over 140,000 copies sold already!

\* On sale now in all branches of WHSMITH price £1.

\* 320 big pages packed with data and pictures of over 5,500 items.



## Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&ph). If I am not completely satisfied I may return the catalogue to you and have my money refunded.  
If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name \_\_\_\_\_

Address \_\_\_\_\_

ET15/82

# MAPLIN

ELECTRONIC  
SUPPLIES LTD.


All mail to:  
P.O. Box 3, Rayleigh, Essex S56 8LR  
Tel: Sales (0702) 552911 General (0702) 554155

Shops at:  
159 King St., Hammersmith, London W6. Tel: 01-748 0926  
284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000  
Note: Shops closed Mondays
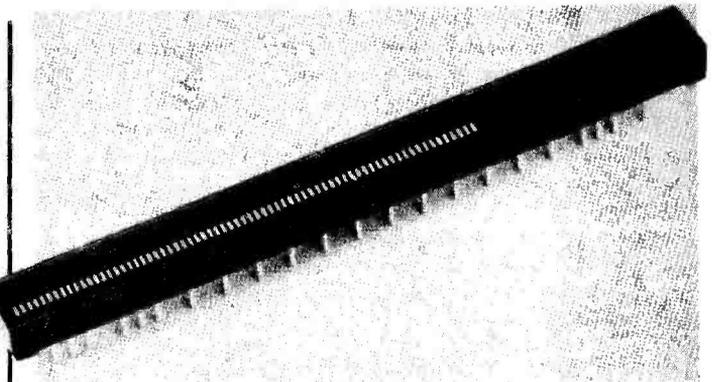
## Improving Memories

Not many people know this, but computer RAM chips have a built-in mechanism for producing errors — the casing of the IC. Trace elements of radioactive isotopes found in the device packaging materials give off alpha particle radiation, causing soft errors in both static and dynamic RAM chips. Two companies have tackled this problem using two very different approaches.

Dow Corning decided that shielding the silicon surface seemed the most logical approach, and developed a silicone rubber which is applied to the memory chips in the last step before hermetic sealing. One syringeful of the liquid silicone (30 cc) can coat 2400 static 4K RAMs and give at least one order of magnitude failure rate reduction. Hitachi, on the other hand, have improved the reliability of their new plastic-packaged 64K dynamic RAMs using a combination of design features. These include higher cell charge storage capacities and higher signal read-out levels, resulting in a two orders of magnitude improvement over non-coated devices. Hitachi expect these chips to replace conventional ceramic 64K dynamic RAMs in the majority of applications.



## Big, Big, Bar

LED bargraphs are considerably more robust and visually attractive than mechanical meters, but suffer from poor resolution due to the limited number of LEDs available. Until now, that is. This massive beast from the Hewlett-Packard stable contains 101 — count them — LED elements in a 10.58 cm long package; the wide elements (1.52 mm) and 1% resolution result in accurate and reliable meter indication. The LEDs are red and configured as a common cathode arrangement to simplify interfacing; HP say the HDSP-8820 is particularly well-suited to industrial process control systems. In one off quantities the device costs £35.10 from HP authorised distributors — for more information contact Enquiries Section, Hewlett-Packard Ltd, King Street Lane, Winnersh, Wokingham, Berks RG11 5AR.



## This Is A Recording

A telephone answering machine which uses a microprocessor to combine simplicity of operation with versatility of use has been launched by Panasonic. The KX-T1524BE (who the hell dreams up these names?) is a twin cassette system using standard cassette tapes for both incoming and outgoing messages, eliminating the need for 'endless loop' or other specialist tapes. A variety of operating modes are available to cater for most user requirements and by using an individually coded pocket bleeper, you can retrieve messages by calling your own number from anywhere in the world. Skip and repeat functions are speeded up by using a message search system; a tone is added to the beginning and end of each message which is easily identified by the search system. The unit is available from dealers of Panasonic Business Equipment. Now if only British Telecom could do something about wrong numbers...

## OOPS

A couple of boops to comment on this month. First, the Music Processor (November '81). There are two R38s on the overlay; the one connected to pin 7 of IC5 is an error, but makes little difference as pin 7 is not connected internally. The published PCB has IC6 pins 5 and 6 connected together; pin 6 should only connect to C15 so cut the extra track. Boards supplied by our PCB Service do not have this error. The lead from R51 is marked LED1 anode on the overlay; it should be LED3 anode. The point marked LED3 cathode should also go to LED1 cathode.

Second, two errors appeared in the Guitar Tuner circuit diagram (January '82). The supply pin numbering for IC3 is reversed; (+ve is pin 4, -ve is pin 11), and IC3c is drawn incorrectly. Pin 5 goes to the V/2 rail only; R12 and C10 should go to pin 6. The overlay is correct. Incidentally, it appears that some people have been buying TMS 1000 ICs from sources other than Magenta and finding that the project doesn't work. This is because the IC is a mask-programmable chip and different versions do different things (some of them are doorbell chips, for example). Only chips described as TMS 1000 — MP0121 will work in this circuit and only Magenta sells them.

This is the last time that OOPS will appear in the Digest pages. From now on amendments and improvements to our projects will appear in the READ/WRITE pages.



## Just Dropped In

New equipment approved by the Electricity Council for high voltage live-line testing of overhead power cables and switchgear busbars will incorporate taut-band meter movements from Sifam Ltd of

Torquay. One of the tests involved dropping the meters five times from a height of two metres onto a concrete floor; since Sifam won the contract we assume the photograph shows the meters being assembled prior to testing, and not repaired afterwards.



### MULLARD SPEAKER KIT

40 watt R.M.S. 8ohm DESIGNED BY MULLARD SPECIALIST TEAM IN BELGIUM comprising a Mullard 8" woofer with foam rolled surround, Mullard 3" high power dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loudspeaker terminals and recessed mounting panel. Supplied complete with assembly and cabinet details. Recommended cabinet size 240 x 216 x 445mm.

PRICE £13.90 + £1.50 P&P per kit



### LEADER LSG


**WIDE BAND SIGNAL GENERATOR**

- 100KHz to 100MHz in five ranges
- Up to 300MHz (Harmonics)
- Slow motion tuning
- Internal modulation 1KHz
- External mod. input facility
- Power supply 240V AC
- Size - 150 x 250 x 130mm
- Price - £63.25 - UK. Post Free

PRICE £63.25  
UK Post FREE
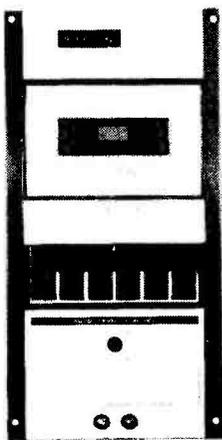
### BK ELECTRONICS

Prompt Deliveries  
VAT inclusive  
prices  
Audio Equipment  
Test Equipment  
by  
Thandar  
and  
Leader



**STEREO CASSETTE TAPE DECK MODULE.** Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2 in x 11 1/4 in. Clearance required under top panel 2 1/4 in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

**Price £26.70 + £2.50 postage and packing.** Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

6 piano type keys.

### 1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
- Compact size 4 3/4" x 1 3/4" x 2 1/2" x 1 1/4"
- Easy snap in fixing through panel/ cabinet cut out
- Insulated plastic case
- Full wave control using 8amp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads

Innumerable applications in industry, the home, and discos/ theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)



### GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems etc.


- Rolled fabric surround
- Twin cone
- 8ohm impedance
- 15 watt RMS
- 1" voice coil
- 13oz magnet
- Frequency range 50/ 15000Hz

Price: £6.90 each + 75p P&P

### BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price: £28.50 + £2.50 P&P

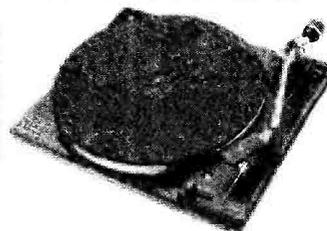


**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price:-

**15" 100 watt R.M.S.** Impedance 8ohm 59 oz magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each. £2.50 Packing and Carriage each.


**12" 100 watt R.M.S.** Impedance 8 ohm, 50 oz magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. Price £23.70 each. £2.50 Packing and Carriage each.

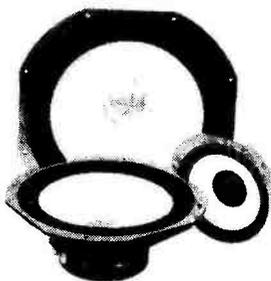**8" 50 watt R.M.S.** Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: White cone £8.90 each. Black cone/grill £9.50 each. P & P £1.25 each.


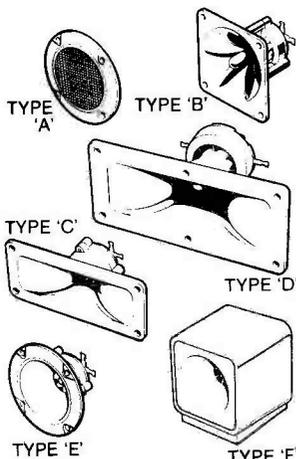
### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized hi-fi speakers. Price £3.45 each.

**TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.35 each.

**TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality hi-fi systems and quality discos etc. Price £5.45 each.


**TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality hi-fi systems and quality discos. Price £6.90 each.

**TYPE 'E' (KSN1038A)** 3 1/2" horn tweeter with attractive silver finish trim. Suitable for hi-fi monitor systems etc. Price £4.35 each.

**TYPE 'F' (KSN1057A)** Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each. U.K. post free (or SAE for Piezo leaflets).



### POWER AMPLIFIER MODULES

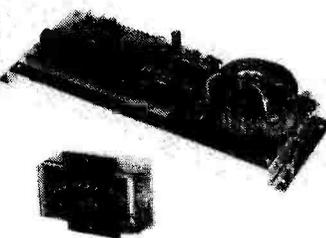

Vu Meter

### 100 WATT R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. V.u. meter, available as an optional extra.

#### SPECIFICATION:

Max. output power 100 watts R.M.S. (OMP100)  
Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response 20Hz-25KHz ± 3dB  
Sensitivity for 100 watts 500mV at 10K T.H.D. 00.1%  
Size: 360 x 115 x 80mm  
Prices: OMP 100W £29.99 £2.00 P&P  
V.u. Meter £6.50

### Matching 3-way loudspeakers and crossover


Build a quality 60watt RMS system 8ohms  
Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover

Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring-loaded loudspeaker terminals and recessed mounting panel.  
**Price £22.00 per kit + £2.50 postage and packing.** Available separately. prices on request.
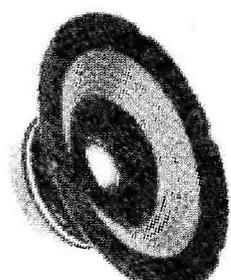
### 12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. **Attractive blue cone with aluminium centre dome**  
Price £17.99 each + £2.50 P&P.



# B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



## Mao-Tse Tongue

Chinese publishers and businesses can now handle text with the same electronic ease as their Western counterparts; Ferranti Computer Systems have just developed a unique Chinese word processing system. Text is input onto disc using Chinese phonetics, the computer's software helping the operator to select the correct character from a dictionary of over 8,000. Text can then be edited, formatted into tables or forms, coded for telex transmission or printed on paper. Incoming telex messages can also be decoded. No technical knowledge is required to run the processor, just the ability to speak and read Chinese. Bet Mao would have liked one for his little red book!



## Is VIC There?

Whenever a major company launches a peculiarly limited computer, someone somewhere will start to design improvements for it. It happened to the ZX81 and now B & B Computers of Bolton have produced an add-on unit for Commodore's VIC-20. The 'black box' will increase the 22 column display to 40 columns and expand the memory from the meagre 3K to 35K; all connecting cables and an additional PSU are included. The expansion unit costs £220 plus VAT by mail order from Beelines Ltd, Freepost, Bolton BL3 6YS; the comparable CBM system would cost £337.81 plus VAT.

## Tangerine Toolkit

Hard on the heels of their high definition Programmable Graphic Module, the Tangerine User Group are now offering a powerful Toolkit for comprehensive control of both PGM and chunky graphics on the Microtan 65. As well as fast plotting from both machine code and BASIC instructions, a number of extras such as BASIC line renumbering are offered. The PGM Toolkit is supplied in a 2716 EPROM with a comprehensive user manual and costs £26.69 for non-members.

# EXCITING OFFERS!

## DIGITAL VOLTMETER MODULE

Fully built & tested



- Positive and negative voltages with an FSD of 999mV which is easily extended.
- Requires only single supply 7 - 12V.
- High overall accuracy  $\pm 0.1\% + 1$  digit.
- Large bright 0.43" (11mm) LED displays.
- Supplied with full data and applications information.

ONLY £11.95 +VAT

Using this fully built and calibrated module as a basis now means that you can easily build a wide range of accurate equipment such as multimeters, thermometers, battery indicators, etc. etc. at a fraction of the cost of ready-made equipment. Full details are supplied with each module showing how to easily extend the voltage range and measure current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, universities, the P.O. and many companies.

## Temperature Measurement

£2.15 +VAT

An easily constructed kit using an I.C. probe providing a linear output of 10mV/°C over the temperature range from -10°C to +100°C. The unit is ideal for use in conjunction with the above DVM module providing an accurate digital thermometer suitable for a wide range of applications.

## Power Supply

£4.95 +VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V providing current levels of up to 250mA each. The unit is ideally suited for powering the DVM and the Temperature Measurement module.

## ULTRASONIC ALARM MODULE

Fully built & tested

ONLY £10.95 +VAT



Range adjustable from 5' - 25'

A really effective fully built module which contains both ultrasonic transmitter and receiver, together with the necessary circuitry for providing the appropriate delays and false alarm suppression. Using this module with a suitable 12V power supply and relay unit such as that shown, a really effective though inexpensive intruder alarm may be constructed. The module, which is supplied with a comprehensive data sheet, is easily mounted in a wide range of enclosures. A ready drilled case, together with all the necessary hardware, is available below.

## Power Supply & Relay Unit

£3.95 +VAT

Incorporating a stabilised 12V supply and a s.p.c.o. relay with 3A contacts, this unit is designed to operate in conjunction with the above ultrasonic unit. Fully built and tested, its compact size makes it ideal for constructing the smallest of units.

## Siren Module


£2.57 +VAT

Producing a very loud and penetrating wailing sound, this module operates from 9-15V. Capable of driving one or two 8 ohm speakers. Suitable horn speakers available at £4.30 each + VAT.
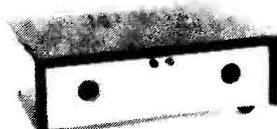
## Hardware Kit

£3.95 +VAT

A suitable ready drilled case together with the various mounting pillars, nuts and bolts, and including a mains switch and 2mm sockets designed to house the ultrasonic alarm module, together with its associated power supply. Size 153mm x 120mm x 45mm.



In addition to the above a wide range of competitively priced electronic components is stocked. Please telephone your specific requirements.

- V.A.T. must be added on all items.
- Shop hours 9 - 5.30 (Weds. 9 - 1)
- ex-stock delivery on all items.
- Units on demonstration, callers welcome.
- Post and packing charge 50p per order.
- S.A.E. with all enquiries please.

## RISCOMP LIMITED

Dept. E.T.I.7.

21 Duke Street,

Princes Risborough, Bucks.

Tel: Princes Risborough (084 44) 6326

# KITS, COMPONENTS MICROS & PARTS

## THE GARAGE DOOR AT YOUR COMMAND

At last, a kit to enable your motorised garage door to be opened without setting foot from your car, and also enable the lights in your garage and drive to be switched on or off at the touch of a button. A momentary relay output operating the door control circuits (relay closes only while a valid code is transmitted) is indicated by LED. It features two latched outputs with common reset for solid state switches (1kW maximum). A hand-held transmitter for 9V PP3 battery operation constituting 4 function keys: Open/Close, on 1, on 2, Off, giving a range of approximately 40 feet is included. As a general purpose remote control in the home for switching lights, television and other appliances. This unit is ideal for the aged or disabled.

AS FEATURED IN P.E. FEB & MARCH

£23.75

ALL PRICES  
EXCLUDE VAT

### DISCO LIGHTING KITS

**DL1000K**  
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.80



**DL21000K**  
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DLAt ..... 60p  
Allowing audio ("beat")—light response.

### XK102 3-NOTE DOOR CHIME

Based on a single integrated circuit (IC80800), this kit comes complete with loudspeaker and drilled box (size: 95 x 71 x 35mm) and requires only a PP3 battery and pushbutton to complete.

The unit produces a 3-note harmonically related tone sequence when the pushbutton is operated and may be used to replace any doorbell or switched by logic in such applications as alarms, PA systems and toys. The unit draws less than 1uA from the battery in the standby mode and produces 150mW output which may be readily amplified if a louder sound is required. The small number of components make this an ideal project for beginners.



£5.00

### DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (—50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.50



### FOR FREE SHORT FORM CATALOGUE SEND SAE TODAY

We also stock:  
Vero products  
Antex Soldering Irons  
Babani Books

### MEMORIES AND MICROS

2114	.....95
2708	.....2.25
2716	.....2.45

### PRICES SLASHED

2732	.....4.80	8035L	.....5.50
6810	.....1.25	M6802P(CPU)	.....3.85
6821P	.....1.25	Z80ACPU	.....3.30
6850P	.....1.50	Z80ACTC	.....2.90
6852P	.....2.55	Z80APIO	.....2.90

### 74 LSTTL

LS00 .12	LS14 .48	LS42 .40	LS93 .37
LS01 .12	LS15 .15	LS47 .42	LS95 .48
LS02 .13	LS20 .14	LS51 .15	LS107 .24
LS03 .13	LS21 .15	LS54 .15	LS109 .24
LS04 .14	LS22 .15	LS55 .15	LS112 .24
LS05 .15	LS26 .18	LS73 .20	LS113 .24
LS08 .15	LS27 .15	LS74 .18	LS114 .24
LS09 .15	LS30 .14	LS75 .27	LS123 .51
LS10 .14	LS32 .15	LS76 .21	LS126 .29
LS11 .15	LS37 .17	LS85 .64	LS132 .44
LS12 .15	LS38 .16	LS86 .18	LS160 .40
LS13 .27	LS40 .14	LS90 .32	LS161 .40

### CMOS

4000 .14	4026 1.05	4093 .45
4001 .14	4027 .40	4501 .24
4002 .14	4028 .50	4511 .85
4007 .14	4040 .68	4514 1.80
4011 .15	4050 .30	
4012 .17	4050 .30	
4013 .35	4060 .90	
4015 .70	4069 .18	
4016 .30	4070 .24	
4017 .65	4071 .22	
4019 .38	4077 .24	
4023 .22	4081 .22	
4025 .18		



### THE KEY TO YOUR SECURITY IS IN OUR LOCK

If the thought of car thieves, house breakers or people tampering with your electrical and electronic equipment upsets you, you have just the kit for you. Our ELECTRONIC LOCK KIT includes a 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is prewired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7x6x3 cms. Power Consumption is 40uA at 5V to 15V d.c.  
At only £10.50 + VAT, it will make a smaller hole in your pocket than a bunch of keys! Electric Lock Mechanism £12.50  
Suitable for use with existing door locks and above electronic lock kit.

### THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.




#### FEATURES INCLUDE—

- ★ 0.5" LED 12 hour display
- ★ Day of week, am/pm and output status indicators.
- ★ 4 zero voltage switched mains outputs
- ★ 50/60Hz mains operation.
- ★ Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- ★ Display blanking during power failure to conserve battery power.
- ★ 18 programme time sets.
- ★ Powerful "Everyday" function enabling output to switch every day but use only one time set.
- ★ Useful "sleep" function—turns on output for one hour.
- ★ Direct switch control enabling output to be turned on immediately or after a specified time interval.
- ★ 20 function keypad for programme entry.
- ★ Programme verification at the touch of a button


THERE HAS NEVER BEEN A CLOCK CAPABLE OF SO MUCH AT SUCH A LOW PRICE—  
ONLY £45.00  
(including components, assembly and programme instructions in an attractive case).
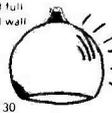
### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting.



TDR300K	Remote Control Dimmer	£14.30
MK6	Transmitter for above	£ 4.20
TD300K	Touchdimmer	£ 7.00
TDE K	Extension kit for 2 way switching for TD300K	£ 2.00
TD300K	Rotary Controlled Dimmer	£ 3.50

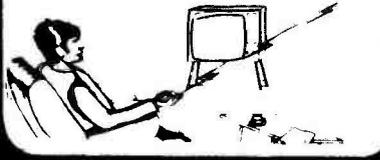

### REMOTE CONTROL COMPONENTS

If you can design your own system, we stock a wide range of remote control components at very competitive prices.

LD271 IR Emitting Diode	.....38
SF205 Photodiode Detector	.....90
SL480 IC Pulse Amp.	.....1.70
SL490 3Z Command Encoder/transmitter	.....2.40
ML922 10-channel receiver + 3 analogue outputs	.....4.20
ML924 Programmable RC receiver	.....1.85
ML925 A decoder designed for model/robot control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg gun turret, wch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights etc.	.....£2.10
ML926 16-channel receiver, 4 momentary binary outputs.	.....1.40

WE HAVE compiled a booklet on remote control, containing circuits, hints, date sheets and details of our remote control kits and components. So don't control yourself—Send us 30p and a stamped addressed envelope for your copy TODAY!

### 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



CT1000K Basic Kit	.....£14.90
CT1000K with white box (56/131 x 71mm) (Ready Built)	.....£17.40
	.....£22.50


Add 50p postage & packing + 15% VAT to total.  
Overseas Customers:  
Add £1.50 (Europe), £4.00 (elsewhere) for p&p.  
Send S.A.E. for further STOCK DETAILS.  
Goods by return subject to availability.  
OPEN 9am to 5pm (Mon to Fri)  
10am to 4pm (Sat)

## FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to—

# TK ELECTRONICS

11 Boston Road  
London W7 3SJ

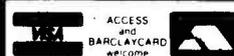


Telephone: 01 579 9794/2842



# electronics today

INTERNATIONAL

NEXT  
MONTH

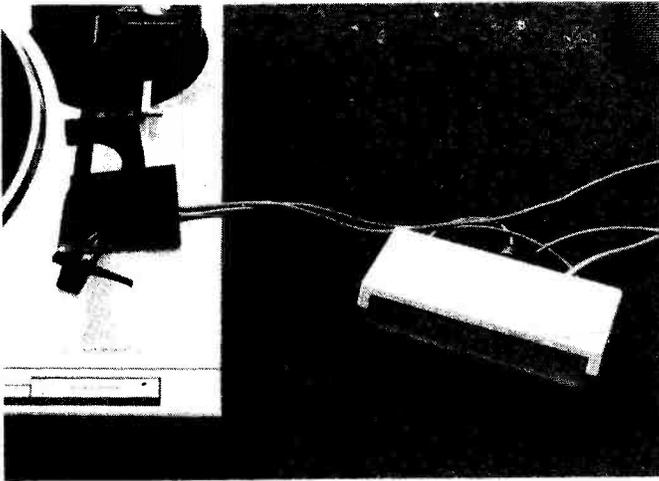

## STYLUS TIMER

Diamond is pretty tough stuff but eventually all that bumping and grinding through the dusty grooves of your records takes its toll. To prevent damage to your precious discs the stylus should be changed at the end of its recommended life but how do you know when that is? Simple — you build the ETI Stylus Timer which ticks away as long as your stylus is in use and remembers the accumulated time period even when the hi-fi is powered down. At the end of the recommended lifetime the unit indicates that it's time for a change. The sensor has been designed so that no electrical connection whatsoever is required to the hi-fi, and the whole thing is neat and compact. For audiophiles everywhere.

## ETI MOBILE

With the publication next month of the digital PWM board (held over for lack of space) and the infra-red proximity detector, our mobile robot is starting to take shape. Even if you're not a robot freak, the designs are versatile enough to be used in a whole range of other applications. Something for everyone — that's the June ETI.

## BREADBOARDING SYSTEMS


As we pointed out last month, there are many new breadboarding systems being released. Unfortunately most of them are so new that they didn't arrive in time for us to write the feature this month. Never mind, though — it's all here now and ready for our in-depth testing and review. If you're not keen on etching PCBs, wait with bated breath for the revelations that will unfold before your very eyes in next month's issue.

## NEGATIVE ION GENERATOR

One or two letters have come flooding in, demanding an ion generator design. Ever eager to please, we'll be publishing a simple experimental device next month so that you can see for yourself whether the claims are justified. Cleaner air, fewer headaches, allergies alleviated, a happy disposition even while reading your morning paper; all this can be yours at no risk of electrocution (we've been quite careful about that). Delve into bioelectronics with ETI next month.
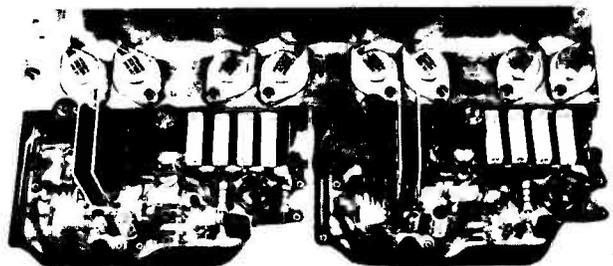
## SERIES 5000 MOSFET AMP

We broke new ground with our System A Class A power amps and now we've a superb project for people who like MOSFETs and masses of power. By 'masses' we mean 150 good old-fashioned root-mean-square watts per channel, with extremely low harmonic, transient and intermodulation distortion. The output stage employs recently released Hitachi MOSFETs and is a real 'no-compromise' design (but then you've come to expect that from ETI, haven't you?). Naturally something that sounds as good as this should look good, too, and the project will be built into a very cheap, standard 19" rack using the somewhat substantial heatsinks as a design feature. If you like it LOUD, get the June issue of ETI.



Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

LOOK OUT FOR THE  
JUNE ISSUE ON SALE  
7th MAY

# SALE ELECTRONIC GAMES



**NOW £40 OFF**

**ATARI T.V. GAME**  
THE GAME WITH 50 CARTRIDGES  
R.R.P. £129.95 (inc. VAT)  
**OUR PRICE**  
**£78.22 + VAT**

(= £89.95 inc. VAT)  
The Atari is supplied with a free mains adaptor, a pair of paddles, a pair of joysticks and a combat cartridge and is the most popular television game on the market and has a range of over 40 different cartridges. In addition to the standard Atari range we also now stock the new Activision cartridges which are currently on special offer reduced from £18.95 to **£16.95 inc. VAT**

**ATARI CARTRIDGES**  
20% OFF R.R.P.  
Atari Soccer £29.95  
**NOW £23.95**  
Activision Dragster £18.95  
**NOW £14.95**  
Activision Boxing £18.95  
**NOW £14.95**

**ATARI OWNERS CLUB** — Why not join our FREE Silica Atari Owners Club and receive our bi-monthly newsletter with special offers and details of the latest new cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.

**MATTEL INTELLIVISION**  
**NOW £50 OFF**



THE ULTIMATE T.V. GAME  
R.R.P. £229.95 (inc. VAT)  
**OUR PRICE**  
**£156.48 + VAT**

(£179.95 inc. VAT)  
6 NEW CARTRIDGES JUST RELEASED:  
ASTROSMASH \* SNAFU \* BOWLING  
SPACE ARMADA \* BOXING  
TRIPLE ACTION  
All 19 current cartridges + the six new ones above now retail at £19.95 — Silica special offer price **£17.95 inc. VAT**

The Mattel Intellivision is the most advanced T.V. game in the world with a range of over 25 different cartridges all at our special offer price of £17.95. This game uses a 16-bit microprocessor giving 16 colours and three-part harmony sound. The picture quality is incredible with 3D effects and realistic animation. An add-on keyboard will be available in the Spring 1982 to convert the Mattel into a full home computer with 16K RAM which will be fully expandable and programmable in Microsoft Basic. Other accessories will be added later in the year. The normal price of the Intellivision + free soccer cartridge is £229.95 but our special offer price is £179.95 inc. VAT saving you £50.00.

**MATTEL OWNERS CLUB** — Why not join our Mattel Owners Club and receive our regular newsletters containing details of all the latest cartridge releases. Telephone us with your name and addresses and we will add your name to our computer mailing list.  
**FREE 16 PAGE CARTRIDGE CATALOGUE** — If you are interested in owning a Mattel, we now have available a 16 page catalogue describing the latest six cartridges to be released, as well as a new Mattel colour leaflet with brief descriptions of all 25 cartridges. Telephone us for further details.

## T.V. GAME CARTRIDGES

We specialise in the whole range of T.V. games and sell cartridges for the following games: ATARI \* MATTEL \* ACETRONIC \* PHILIPS \* DATABASE \* ROWTRON \* INTERTON \* TELENG. Let us know if you own any of these games and we will let you have details of the range of cartridges available.  
Attention INTERTON & ACETRONIC owners we have over 75 assorted used cartridges in stock all with 1 year guarantee — **SPECIAL OFFER £8.95 each**

We also have a number of secondhand games and cartridges.



**ELECTRONIC CHESS**  
Liquid crystal battery chess computer with 100-200 hrs battery life and two levels of play. Comes with separate chess board and pieces.  
**NOW £5 OFF**  
R.R.P. £24.95  
**SALE PRICE**  
**£19.95** (inc. VAT)

**GRADUATE CHESS**  
A deluxe version of the electronic chess set with integral chess board. The ideal portable chess set — see illustration.  
**NOW**  
**£29.95** INC VAT

## FIDELITY MINI-SENSORY CHESS COMPUTER

The very first chess computer of its price to offer a portable computer with integral sensory board Battery (6-8 hrs) or mains operated. This is a modular game and additional plug-in modules are planned for 1982 for advanced chess, popular openings, greatest master games, draughts and reversi.

**MINI-SENSORY COMPUTER WITH STANDARD CHESS MODULE** Was £54.50 **NOW £49.95 INC VAT**

Silica Shop are one of the country's leading specialists in Chess Computers and now stock a range of more than 20 Chess Computers, including Challenger 7/10/Voice, Sensory 8 and Sensory Voice, Diplomat, System 3, Morphy, Great Game Machine, Voice Champion, and the new Scicys Mark V.


**LESS THAN 1/2 PRICE**

**COLOUR CARTRIDGE T.V. GAME**  
Semi Programmable TV game  
4 cartridges  
+ mains transformer  
**NOW £43.80 OFF**  
R.R.P. £73  
**SALE PRICE £29.50** (inc. VAT)

**SCOOP PURCHASE NOW**

**BACKGAMMON COMPUTER**  
Silica stock a wide range of Backgammon computers from £28.95 upwards. Special offers now available on Gammoneer.  
Was £99.95  
**NOW £48.95** inc VAT

## CALL JOTTER — THE AFFORDABLE ANSWER

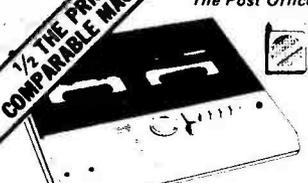


**1/2 THE PRICE OF COMPARABLE MACHINES**  
The Post Office certified telephone answering machine  
"Sorry darling, I will be late home — Love John"  
The Call Jotter 1 brings the affordable answer at the amazing price of £69 (or £99 for the Call Jotter 2 with built-in remote recall facilities). These amazing telephone answering machines are Post Office certified and guaranteed for one year. They make a thoughtful gift for home or business use.  
Call Jotter 3 illustrated **NOW £69.00** inc VAT  
TWINTAPE £139




**NOW £75 OFF**  
**ADD-ON ADAPTOR**  
Was £199 inc. VAT  
**SALE PRICE £124** inc VAT

**RADOFIN TELETEXT**  
Plus the adaptor into the aerial socket of your colour TV and receive the CEEFAX and ORACLE television information services.  
**THIS NEW MODEL INCORPORATES**  
\*Double height character facility  
\*True PAL Colour  
\*Meets latest BBC & IBA broadcast specifications  
\*Push button channel change  
\*Unnecessary to remove the unit to watch normal TV programmes  
\*Gold plated circuit board for reliability

# FOR FREE BROCHURES — TEL: 01-301 1111

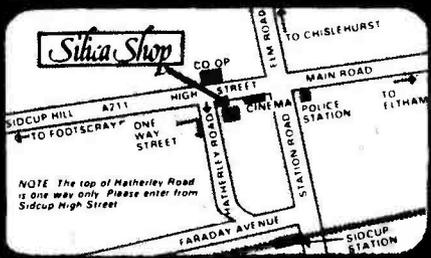

For free illustrated brochure and reviews on our range of electronic games, please telephone 01-301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/BARCLAYCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48 hour delivery service available.  
● **CALLERS WELCOME** Demonstrations daily at our Sidcup shop open from 9am-6pm Monday-Saturday (Early Closing Thursday 1pm, Late Opening Friday 8pm)  
● **2 YEAR GUARANTEE** All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee.  
● **MONEY BACK UNDERWRITING** If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.  
Available on all machines out of guarantee  
● **AFTER SALES SERVICE** We are never knowingly undersold  
● **COMPETITIVE PRICES** Available on the suitability of each machine  
● **HELPFUL ADVICE** Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.  
Available on second hand machines  
● **CREDIT FACILITIES** Access, Barclaycard, Diners Club, American Express.  
**SILICA SHOP LIMITED ET10562**  
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX  
Telephone: 01-301 1111 or 01-309 1111

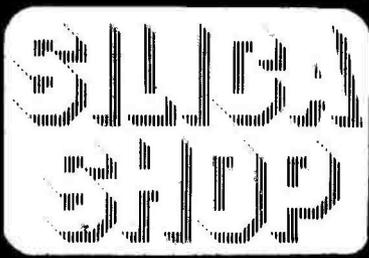

# COLUMN LOUDSPEAKER DESIGN

The column loudspeaker is an example of a directional sound source which is of special use if acoustic feedback is a problem; it is most commonly found in sound reinforcement or public address applications. David Hornsby describes a novel design that can be made at a fraction of the cost of its commercial equivalent.

A standard loudspeaker tends to radiate sound in all directions, both forwards and backwards. It is helpful to look at this sort of response on a polar diagram (Fig. 1); the circle round the sound source shows that the sound loudness is about the same in all directions. If the loudspeaker is now placed in an enclosure then sound is allowed to radiate forwards only and we have a 'unidirectional' source. The polar diagram for it in Fig. 2 shows a balloon-like shape for the sound radiation pattern, which now covers an angle of slightly less than 180°. The dotted line shows the response if the enclosure lets a little sound out backwards.

If polar diagrams are new to you, these two diagrams will probably have given you a fairly good feel for what they are all about. They are similar to the contour lines on a map, but instead of showing height they show the sound intensity or loudness. The further the line on the polar diagram is from the sound source at the centre then the louder the sound is in that direction.

## One-Way Sound

The unidirectional sound source is the one most of us use in our homes and cars but it's not very good for live performances where the microphone(s) is in the same area. Diffraction effects, echoes and reverberations all help to spread the sound back from the loudspeaker to the microphone so that as soon as the sound is turned up, positive feedback makes the system oscillate and howl.

There are one or two different solutions to this problem but the most common and probably the best is to use a highly directional sound source. This tends to concentrate the sound into the area where it is needed, the audience, but well away from the microphone.

One type is the horn loudspeaker which has good directional properties and is also very efficient electrically. Unfortunately it has to be physically large to be effective at low frequencies. The fog horn at your local lighthouse (you do have one, don't you) and the PA in a cinema have space for large horn

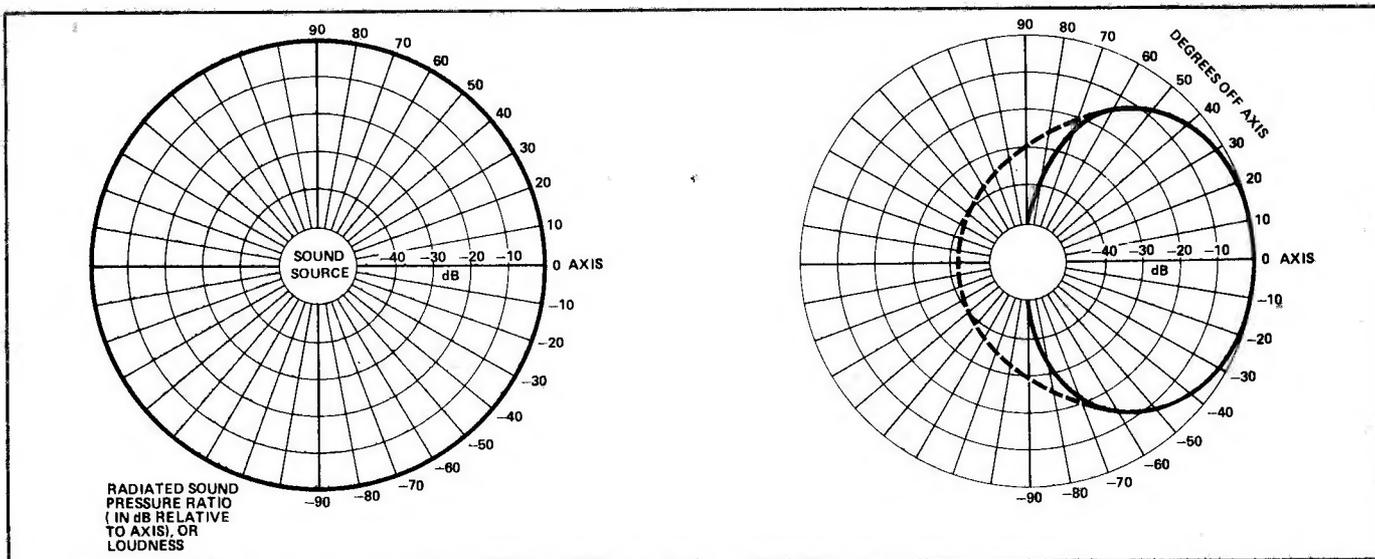


Fig. 1 Polar diagram of a sound source which radiates equally in all directions (approximated by an unmounted loudspeaker). The sound source is at the centre of the diagram.

Fig. 2 Polar diagram of a sound source which radiates mostly forwards (approximated by a loudspeaker mounted on an infinite baffle enclosure). If a little sound is allowed out backwards the dotted line applies.

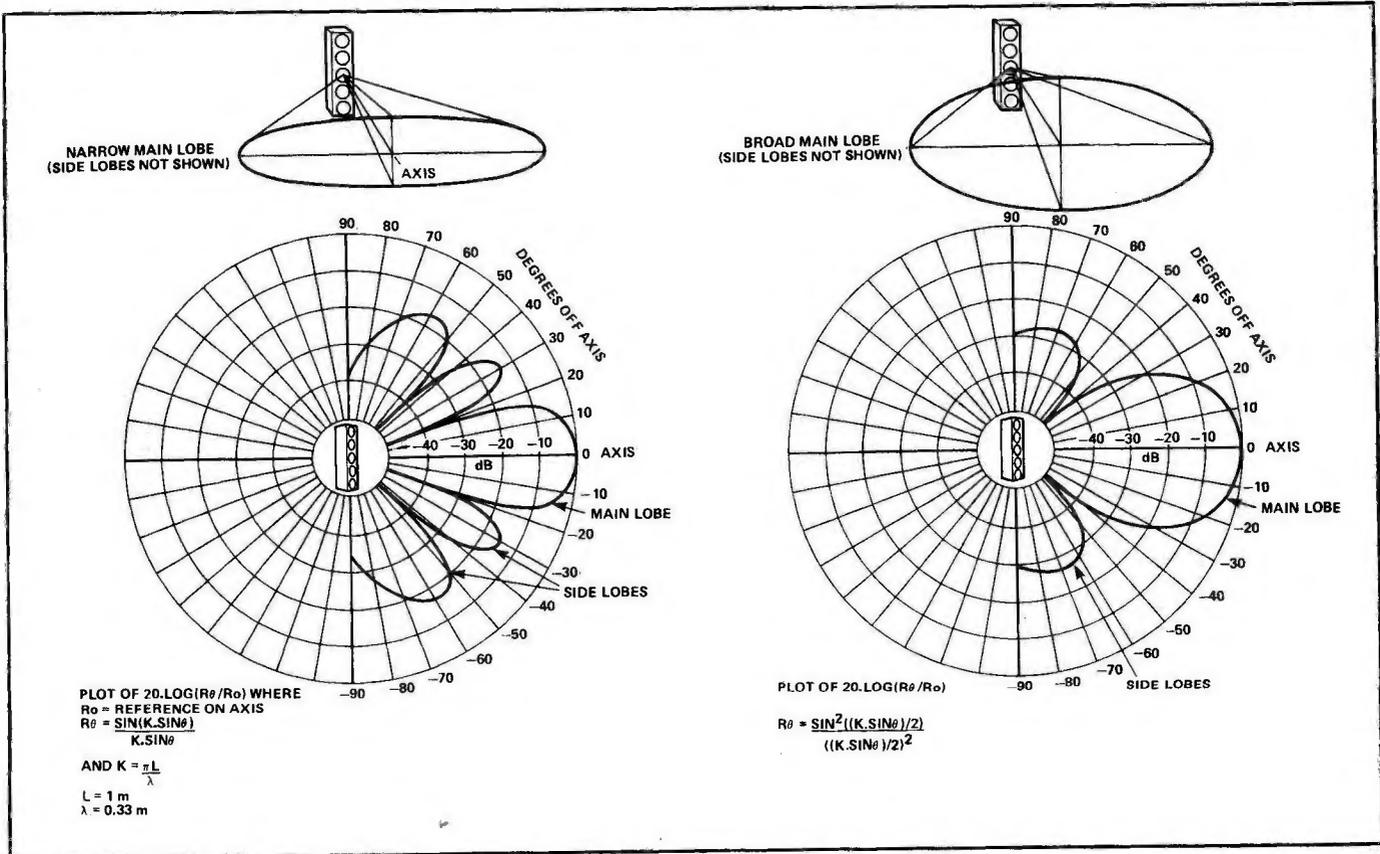


Fig. 3 Polar diagram of a column loudspeaker at 1 kHz.

Fig. 4 Polar diagram of a column loudspeaker at 1 kHz with graded aperture.

units, but in the domestic scene we either have to use a folded horn design or just use tiny horns for high frequency tweeter applications.

The other directional type of loudspeaker in common use is the 'line source' or column loudspeaker, and that's the one we're going for here. The theory tells us that all we need is a loudspeaker with a cone which is long and narrow, rather like an elliptical loudspeaker taken to the extreme. Put that in a similarly long and narrow enclosure and that should be it! We do still have the problem that unless we allow the length to be at least a few feet then we will lose the beaming effect on the low frequencies, but there's a far worse problem — how do we actually get hold of our crazy-shaped loudspeaker? Does such a beast even exist? Actually it probably could be made with an electrostatic speaker but that's not for us. Instead we can approximate a line source with several conventional round speakers stacked in a line. Commercial designs use three or more, often quite a few more, and this works well. Our design uses five speakers spaced evenly along an enclosure of one metre length.

### Directional Characteristics

It is at this stage that we must look again at a polar diagram for our design, Fig. 3, and this is where this diagram begins to give us some useful information. The first thing to note is how the shape is drastically changed from a balloon to a series of fingers of various sizes. The largest finger is the main beam or lobe of our column loudspeaker while the smaller fingers are unwanted side lobes. If you have seen interference patterns on a ripple tank then you will probably understand the reason for this sort of pattern. To improve the directional properties of the speaker system still further, we want to reduce the side lobes and enlarge the main lobe. It would probably also be useful to have a slightly broader main lobe, since it is unlikely that we can

arrange for the audience to be confined into too narrow a region.

Without going into all the maths of the solution, both these aims may be reached by a process known as 'grading' or 'tapering' the aperture. This is a little trick that is used in all sorts of situations, not just column loudspeakers. Microwave dish aerial systems often do just the same, for example. In our case, tapering the aperture simply means that we must arrange to evenly decrease the power fed to each of the individual loudspeakers as we move away from the central one on the column. The effect of this is shown in Fig. 4. Note that these diagrams both apply only at one frequency, 1000 Hz. At higher frequencies the lobes are narrower and more numerous, but they become wider and less numerous at lower frequencies until below about 500 Hz, the wavelength of sound is comparable with the length of the column and the beaming effect begins to fail. Fortunately acoustic feedback is likely to be worst at frequencies well above 500 Hz so one metre is as long as we need to make the column.


You may occasionally come across giant column loudspeakers which are also curved so that they look concave from the listener's vantage point. This produces the same effect as tapering but is not necessary except for systems much longer than one metre.

### Electrical Design

So now a way of arranging the power fed to each speaker has to be devised. If series resistors of appropriate values are wired in with the speakers, then, although things work well enough acoustically and electrically, we will have an inefficient design which wastes much of the power of the amplifier as heat in these resistors. The common commercial solution is to forget about tapering altogether, or for expensive units to use a special matching transformer with tapings for each individual


# FEATURE : Column Loudspeakers

speaker. This not only adds to the cost but also to the weight of the final product. Don't forget that no transformer has yet been designed which gives zero distortion, so that's yet another problem. While pondering this (in the bath — where else!) the author devised what seems to be a splendid engineering solution; that is, one that cheats the situation by winning several points at one go but without making any serious concessions. The key is to use identical speaker units but with different coil impedances. After many calculations with a range of different combinations, one design stood out as being almost ideal. It produces an effective impedance of 6.15 ohms, gives an even tapering and uses just 8 ohm and 15 ohm speaker units which are readily available.

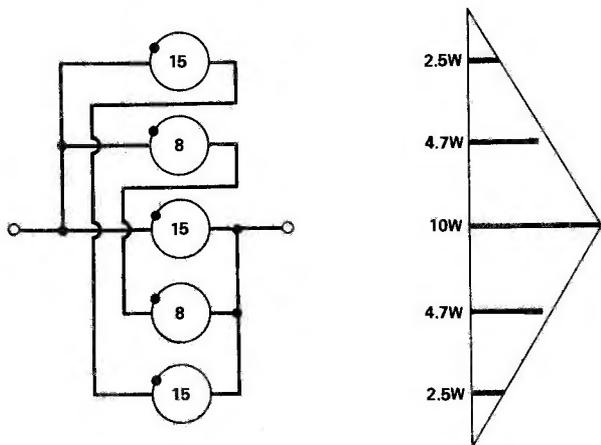

**Fig. 5** The wiring diagram for the 8 and 15 ohm speakers. Note how each speaker is wired in phase. For 10 W speaker units the power handling is about 25 W (actually 24.375 W). At right is shown the profile of the graded aperture.

The electrical set-up is given in Fig. 5 and for nominal 10 W units produces a speaker system of 25 W capability. The actual make of loudspeaker unit doesn't really matter provided you can get both 8 and 15 ohm units in the same style. The original design used R.S. Component's wide-range six-and-a-half inch loudspeakers which have given reliable service for over four years now. Some may object that five 10 W speakers ought to give a system capable of more than 25 W. It is, of course, the tapering of the system which causes this reduced power rating,

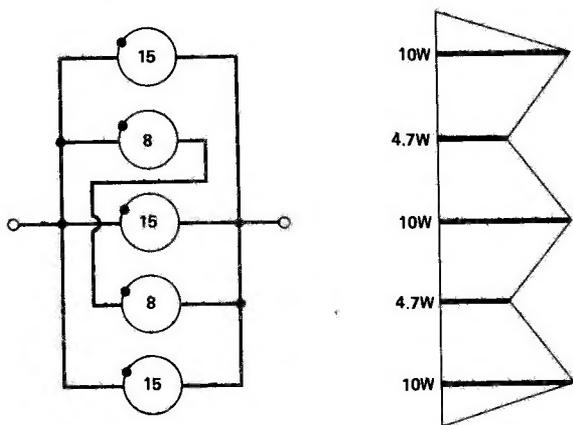


**Fig. 6** An alternative way to wire the speakers. This gives a power handling of nearly 40 W but is not recommended as the aperture is not correctly graded. The profile of the aperture is irregular, as shown.

but its electrical efficiency is fair and there is no real problem. It is in fact possible to rewire the individual units so as to increase the power rating to 40 W, as shown in Fig. 6, but the tapering goes out of the window with this arrangement and it is not recommended.

Calculations show that the series/parallel combination of speaker units in our design gives an effective impedance of 6.15 ohms. This is just about ideal and suits the 4 to 8 ohm range that most power amplifiers are designed to feed. If you happen to have one which cannot drive impedances less than 8 ohms then you will need to add a 2 ohm series resistor to get things right. However, most column loudspeakers are necessarily mounted some distance from the amplifiers and the leads' resistance may provide some or all of this extra 2 ohms if you are lucky.

## A Case In Point

The cabinet for the design may be made from chipboard. Three-quarter-inch thick is about the right grade for this job. If you are going to use the R.S. speaker units then, provided your woodworking skills are fair, it is only necessary to refer to Fig. 7 for all the details. If you have or can gain access to a circular saw (what about woodwork evening classes?) the task is that much easier. None of the dimensions are that critical, but the overall volume has been designed to match the suspension characteristics of the speakers themselves and should be kept the same. The unusual cross-sectional shape is not an essential

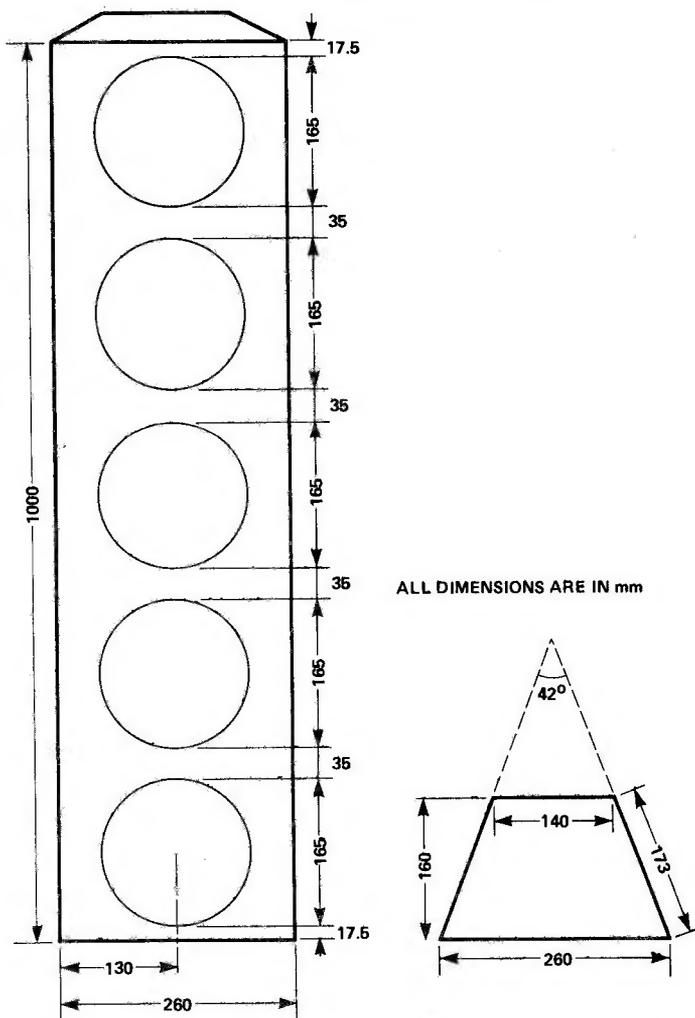

**Fig. 7** Cabinet details — all dimensions are in millimetres. The total cabinet volume is 0.324 cubic metres. A suitable material to use is 3/4" chipboard and this thickness needs to be added to the dimensions shown where appropriate.

part of the design either but was chosen so that the column could be neatly and permanently mounted on a wall and still point in the right direction. If your intended use is stage work then a square or rectangular cross-section giving the same volume would be easier to make.

Take care to close all joints with enough glue to make the unit reasonably airtight since this is a requirement of this type of speaker unit's cone suspension. The inside of the cabinet is filled with acoustic wool or similar sound-absorbing material so as to reduce internal sound reflections which otherwise give an unnatural colouration to the performance. I once knew a musician who insisted that internal lining of an enclosure reduced the high frequency response, but he had simply come to enjoy a particular type of distortion — don't leave it out! The best way to fix it is to tack it on lightly before the front is put on the enclosure. If it is not fixed it will soon fall to the bottom and lose most of its effect; if it is glued it tends to become compressed on to the glue which again cuts down on its absorption properties. Similarly, use a proprietary make of grille material for the front rather than any old material or again you will distort the sound. Most probably it will be the high frequencies that you lose this time if you are tempted to use the spare curtains because they are the right colour!

If the final unit is to be attached to a wall, a small screw recess can be provided near the top of one side for this. Most ironmongers stock screw-on brass plates that are ideal as a reinforcement for this. Don't forget to provide electrical connections on the back before the unit is assembled. Suitable types are available from the same sources as supply the acoustic wool and grille material (and the speakers themselves for that matter). The finish on the outside of the cabinet is obviously a matter of personal choice. If you wish to make a feature of it you can use a wood veneer or vinyl covering to achieve a smart appearance. The original design was made to appear unobtrusive (if that's not a contradiction in terms) by simply painting it the same colour as the wall it was to hang on, and this worked very well.

## Performance

In assessing how well the design works we must first decide what it is we are looking for. With a speaker system intended for hi-fi applications we might look at the frequency response and phase linearity, for instance, but this design is for sound reinforcement purposes. The chief needs are to reduce acoustic feedback by efficient beaming of the sound and to improve the audibility of whatever is behind the microphone. The design was originally made to meet the needs of a church of moderate size (about 50 by 30 feet) for both music and singing from the music group at the front, and for speech from the pulpit (but not both at the same time!).

Judged by these standards the final product is totally effective; the beaming effect is very noticeable. When it was tested in the living room at home before installation the sound appeared to be thrown forwards towards the listener in a way that the conventional speaker cannot achieve. With a pair of speakers now hanging on side walls each side at the front of the church, their base being six feet from the floor and the axis of each speaker pointing towards the floor at the mid point of the back wall, the comparison with the old temporary single speaker units is really quite spectacular. At the front of the church the sound is beamed high over people's heads and so is not deafeningly loud. At the back, however, the beams reach down to ear level and the sound seems every bit as loud as at the front even though you are further from the speakers. What is more, the sound, particularly speech, is strangely clearer. The effect is perhaps not unlike that in the Whispering Gallery in St. Paul's Cathedral, where you might be surrounded by background noise yet can hear a whisper with startling clarity from a spot exactly opposite. The speakers do not whisper but the sound seems to surround you in the same way.

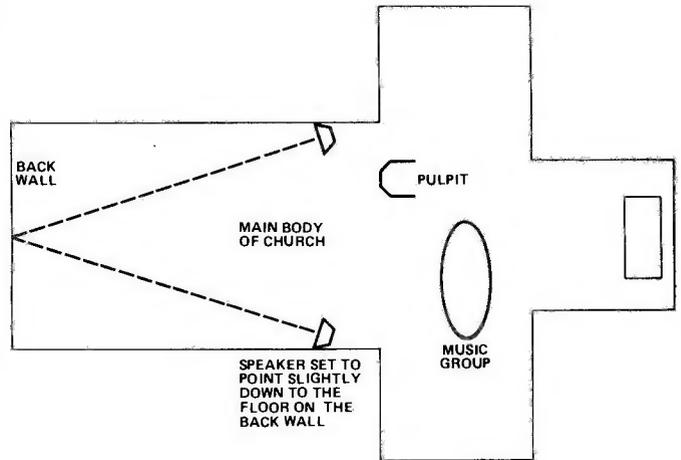


Fig. 8 The working layout of the speakers in the church.

The power handling of the column loudspeaker, 25 W, is more than adequate. The two units are driven by mere 15 W amplifiers but even these are never turned up anywhere near full volume. Acoustic feedback is no longer a critical problem, no mean achievement in a stone church building. The improvement is so pronounced that the music group now need to be provided with extra speakers to provide foldback.

The frequency response of the units is essentially that of the individual loudspeakers — about 70 to 16 kHz for the R.S. units in an enclosure of this volume. Purists will notice and object to the lack of the extreme high frequency element, but this is unimportant in this application. In fact a design of this type will have rather better characteristics than the straight theory predicts since the matching of the system to the air is improved with the larger surface area of many loudspeaker cones. At low frequencies in particular it appears the response goes down well below 70 Hz although no measuring equipment was available to make quantitative measurements. If operation above 16 kHz is important for you don't despair: add a horn tweeter and mount it on top of the cabinet.

The overall impression of the speakers is of clean effortless performance, lacking only in that extreme high frequency content. They have been used regularly for four years now with 100% reliability. Applications have included not only the live sound sources mentioned earlier but also the playing of taped music and use for film shows. Once when playing back a tape-recorded voluntary from the pipe organ, several members of the congregation admitted to me afterwards that they had to look at the organ to check that it was not live playing — quite remarkable really when you think that the organ is at the back of the church and the column speakers at the front! This is the result obtained with directional sound: it seems to come directly to you. If you want to test for yourself and are in range of North Buckinghamshire, why not pop into Holy Trinity Church, Deanshanger and make up your own mind?

One last note of caution for you: do position your column speaker the right way round, that is vertically. You will have seen from Figs. 3 and 4 how the sound beam spreads out from the system. Possibly because this spreading is the opposite of what might at first be expected or perhaps because of plain ignorance, column loudspeakers are occasionally positioned the wrong way round! In fact I know of one not many miles from my home, where, in a specially converted stable, a column speaker is attached horizontally to an old oak ceiling beam. Wild horses wouldn't drag the exact location of the stable from me (pun intended — groan); I enjoy the little theatre too much to want to upset them.

ETI

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite

BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles

## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble
- Supplied in superb presentation gift box

## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles

## TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble

## VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble. A real challenge for the electronics enthusiasts!

## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

All EDA-SPARKRITE products and designs are fully covered by one or more World Patents

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

Allow 28 days for delivery

NAME \_\_\_\_\_ ETI.5.82

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF. \_\_\_\_\_


CHEQUE NO. \_\_\_\_\_  
24 hr. Answerphone  
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD  
SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!
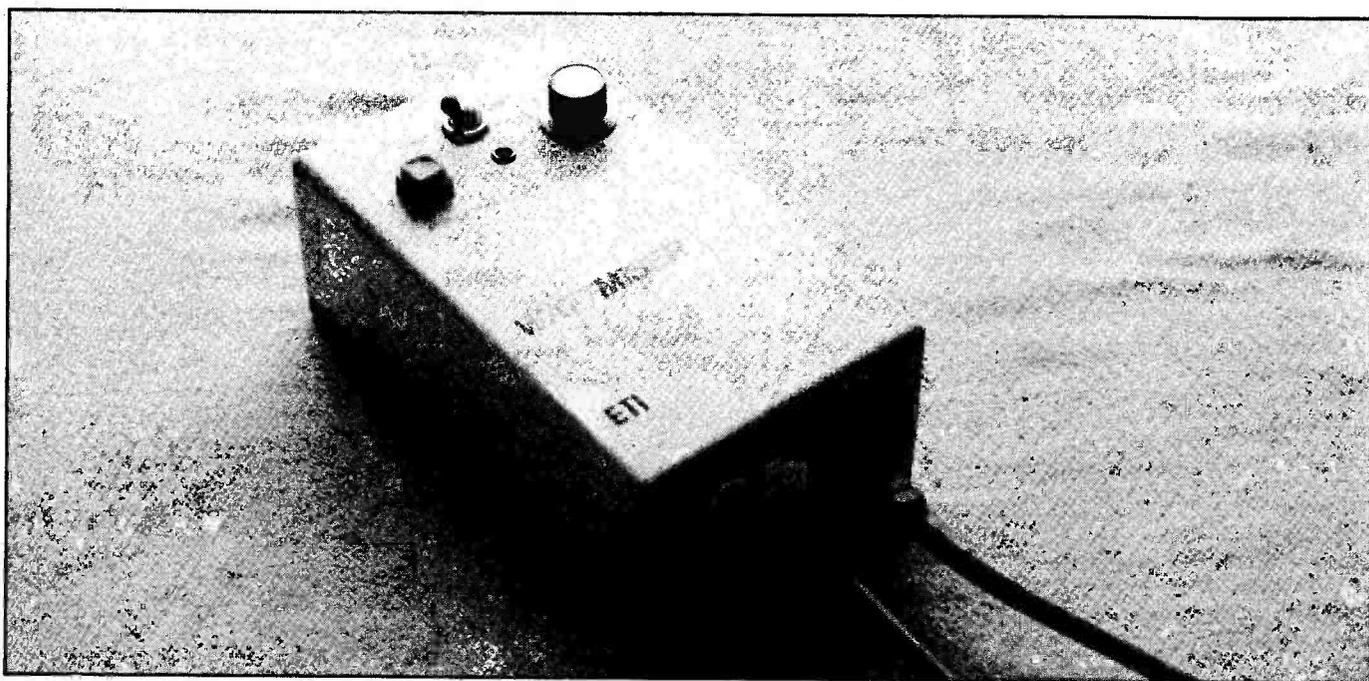
# ECONOMICAL HEATER CONTROLLER

Save energy and master the meter; control your power consumption with the ETI Wattmiser. Design and development by Phil Walker.



**A**fter this winter's snow, frost and electricity bills we are probably looking for ways to save a little money without losing comfort or convenience. This project is designed so that appliances such as electric fires or water heaters can be set to turn on a little before they are needed. This will ensure that the room or tank of water, etc is comfortable or ready for immediate use when required, but has not been consuming those precious units all the time.

The device could also be used to control other things such as tape recorders, radios and so on where the precise timing is not too critical.

## Operation

The device operates by dividing the mains frequency (50 Hz) by 180, 224 to get a signal with a period of

about 1 hour. The actual division required was 180,000 but the 180,224 was more easily achieved and the error involved was less than 1 part in 500, or about 40 seconds in the maximum period of 9 hours delay.

This 1 cycle per hour signal advances a divide-by-10 counter which has 10 separate outputs. Each output is active for 1 hour and only one is active at a time. One of the outputs is selected to drive the mains power switching triac — thus giving an 'on' period of 1 hour after a selectable off period. Also it is possible (if SW4 is on) to have the output come on permanently after its set delay (this is always the case on the 9 hour delay setting).

To use the device, set the number of hours delay with SW3, select whether '1 hour only' or 'permanently on' operation is required with SW4 and

press SW2 to start the device working.

## Installation

When using the device, the mains supply must be fed from a plug or switched fuse outlet containing a fuse rated for the appliance used. Also the wire used should be suitably rated — round flex rated at about 15 A usually sold for electric fires or similar applications could be used in most cases.

## Construction

The construction of the PCB should present no great difficulties. The first thing to do is to ensure that the mounting holes are of a suitable size and that the correct ones are being used if the specified box is utilised. Next put some M3 x 12 mm bolts

through the mains power connection pads, heads on the copper side. Run some solder around these heads to secure them and improve the contact.

Now fit the wire links and the other components with the exception of the switches, LED1 and SCR1. Make sure that D1 and D2 are the right way round. Also note that IC1 is the opposite way round to IC2, 3 and 4.

Next fit SCR1 and its heatsink to the board, using an M3 x 6 mm bolt.

Use heatsink compound under SCR1 to improve thermal conductivity. Bend the leads out from SCR1 to go through the proper holes. Note that if the lower rating triac is used, the fixing hole nearer the contact pads should be used and vice versa. SW3 should now be fitted. If the contacts are on a 22 mm diameter circle they may be connected straight to the board, otherwise short lengths of stiff wire should be used. (If all else fails you could fix the switch to

the cover of the box and connect to the board using thin flexible wire — leave enough to remove the lid when fitted).

Attach some lengths of flex (6") to the PCB at the remaining switch positions (SW2 and SW4), LED1 position and transformer connections. Fit the transformer diagonally into the corner of the box (the end with the wider spaced fixing bosses) and then the cable glands, neon, mains switch

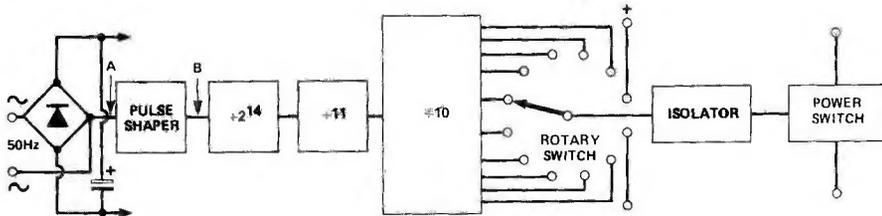


Fig. 1 Block diagram of the unit.

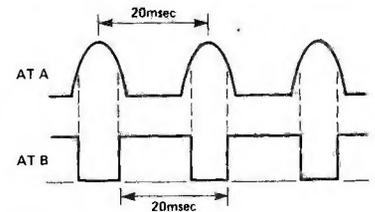


Fig. 2 Pulse shaper action.

## PARTS LIST

### Resistors (all 1/4 W, 5%)

R1	15k
R2	220k
R3,4	100k
R5	27k
R6	1k2
R7	820R
R8	56R
R9	100R

### Capacitors

C1	1000u 40 V axial electrolytic
C2	1n0 ceramic
C3	1u0 63 V axial electrolytic

### Semiconductors


IC1	4093
IC2	4060
IC3	4516
IC4	4017
IC5	MOC3020
Q1	BC477
D1,2	1N4148
BR1	W01 bridge rectifier (100 V, 1 A)
SCR1	TIC263D (400 V, 25 A) or TIC246D (400 V, 16 A)
LED1	3 mm red LED

### Miscellaneous

SW1	DPDT mains on/off rocker switch (miniature)
SW2	1 pole push-to-make switch, momentary action
SW3	1 pole 12 way rotary wafer switch, contacts on 22 mm diameter circle
SW4	SPST toggle switch
FS1	1A anti-surge fuse and panel fuse holder (20 mm)
LP1	Mains neon indicator with integral resistor (panel mounting)
T1	6 VA mains transformer (9 V secondary, 240 V primary)

PCB (see Buylines); case (see Buylines); 2 off cable glands (8-10 mm — see Buylines); 3 off 16 pin and one off 14 pin IC sockets (if used); heatsink (TO-220 style) knob; M3 nuts and bolts, spacers, etc.

Fig. 3 Component overlay.

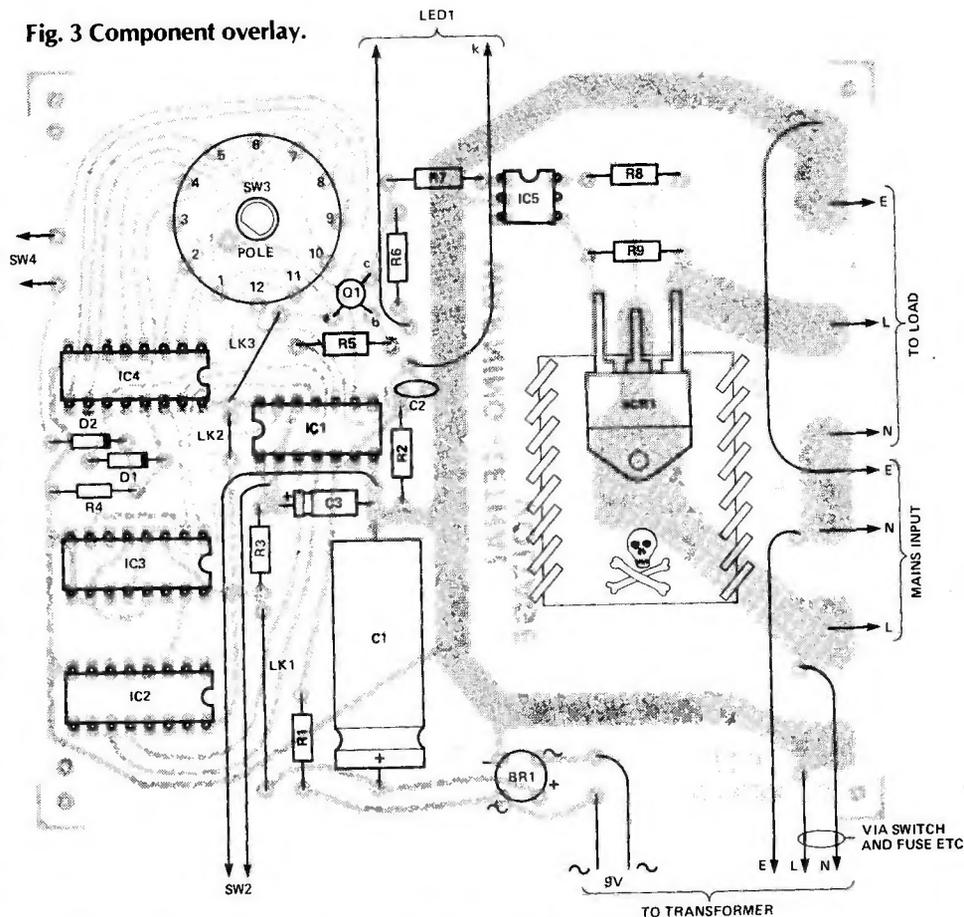

## BUYLINES

Most of the components used in this project are standard off-the-shelf items. The MOC3020, TIC263D and TIC246D may be a little harder to track down and can be obtained from TK Electronics. The case we

used was a BOC 450 from West Hyde Developments; the same company can provide the cable glands we specify. The PCB can be obtained from our PCB Service using the advert/order form on page 45.

# PROJECT : Heater Control

and fuseholder into the end-plate. Wire up as shown on the circuit diagram.

Finally fit SW2, SW4 and LED1 to the lid of the box and cut a hole through to take SW3 spindle. Wire up as per the circuit diagram. Mount the PCB on pillars using M3 bolts at such a height that the SW3 spindle protrudes far enough to take the knob when the case top is in place.

In use it is advisable to solder eyelets to the mains wires to fit on to the PCB bolts; alternatively the ends of the wires should be soldered to stiffen them.

**NOTE:** As mains voltages are present, care must be taken that no unearthed metal parts are accessible from the outside and that clearances between live and earthed parts are maintained under all circumstances.

## HOW IT WORKS

IC1a takes the raw AC 50 Hz signal applied to the bridge rectifier and converts it to a train of pulses at the same frequency. This is divided by  $2^{14}$  (16,384) by IC2. Further division is done by IC3 which is connected with IC1c to divide by 11<sup>(10)</sup>.

This is accomplished by loading 1011<sub>2</sub> into IC3 each time it counts down to 0000<sup>(2)</sup>. At the Q<sub>4</sub> output of IC3 there is a signal which has a period of  $20\text{ms} \times 16,384 \times 11 = 3,604,480\text{ms} = 3,604.48\text{seconds}$ . This signal is applied to the clock input of IC4, a divide-by-10 device with 10 decoded outputs. The output of IC4 selected will change every 3,604.48 seconds (about 1 hour) until the '9' output (pin 11) is high. At this time further clocking of IC4 is prevented by a signal at pin 13 via D1.


SW3 selects which output of IC4 drives the output power switch. This varies from permanently on (position 1), through zero

delay (position 2), up to 9 hours delay (position 11), to permanently off (position 12).

If SW4 is open then in the 0 to 8 hour delay positions the output will be on for 1 hour after the set delay only, whereas if SW4 is closed or a 9 hour delay is selected the output will stay permanently on after the delay period.

IC1c takes the output signal from SW3 and drives Q1 and thus IC5. IC5 is an optically isolated triac which enables us to have the logic circuitry safely at earth potential while switching the mains power with SCR1.

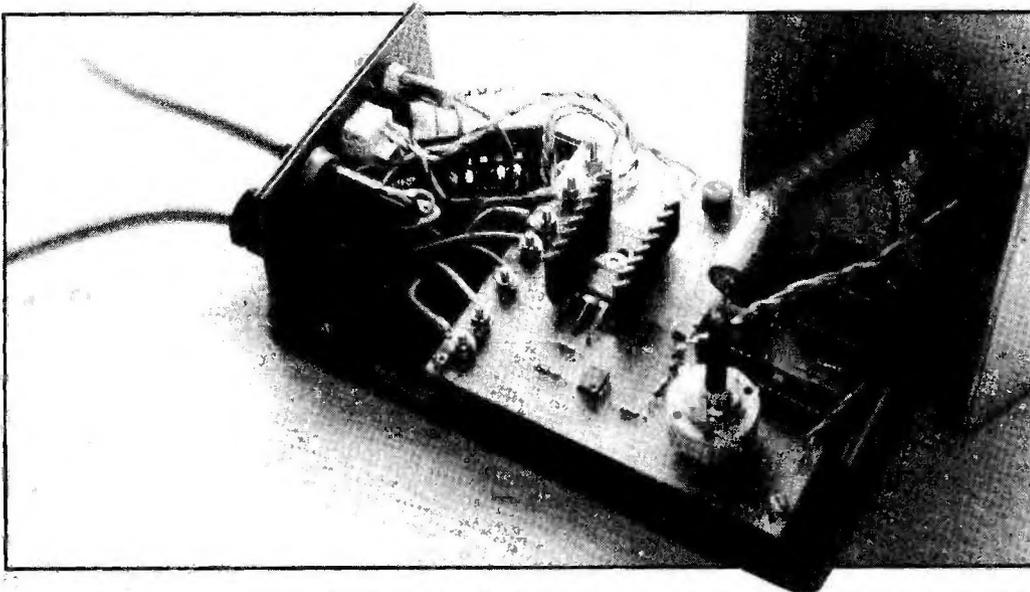The last part of the circuit is that around IC1a and IC1d. This is the reset circuitry which ensures that the time period will be consistent and start when SW2 is released. IC2 and IC4 are reset to 0 by IC1a, while IC3 is set to 1011 (decimal 11) by IC1d.



With the lid off, the general layout of the project should be clear. With the large currents involved, the mains wiring is secured to the PCB with nuts and bolts.

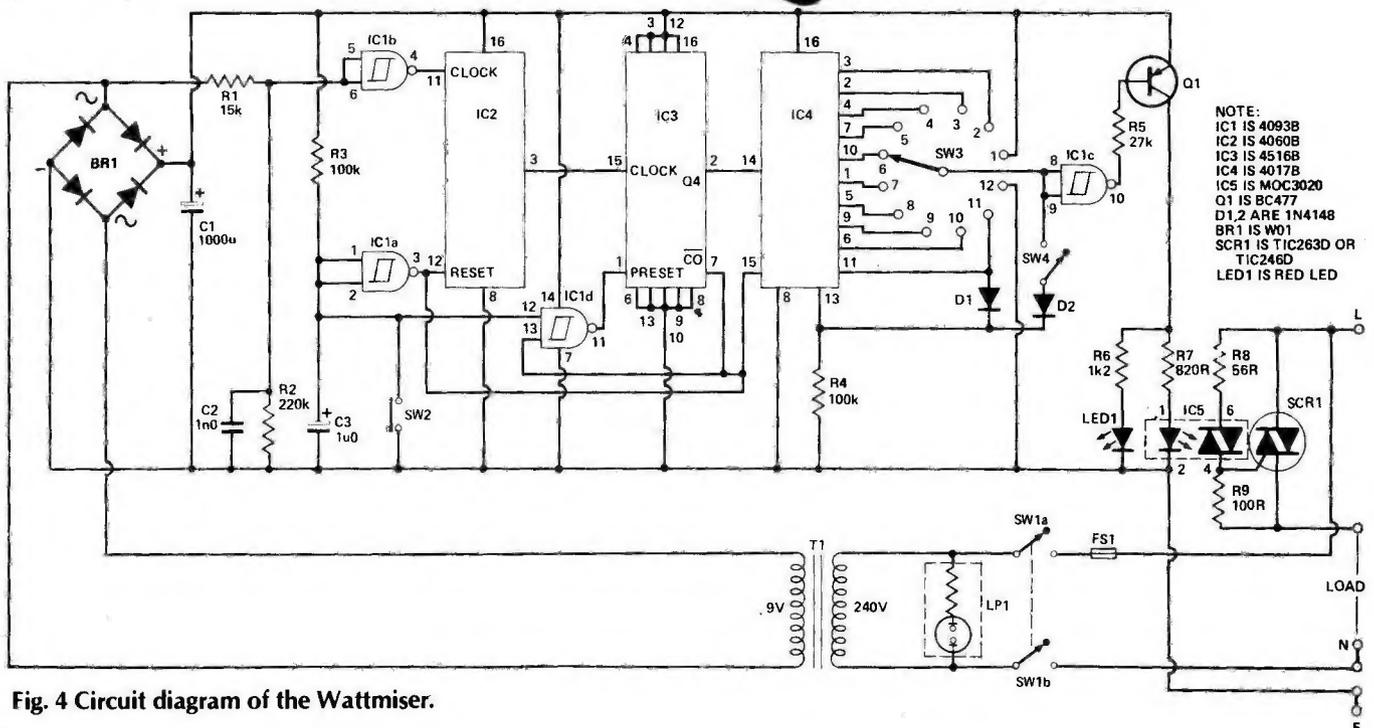


Fig. 4 Circuit diagram of the Wattmiser.

# Lack of ZX81 memory giving you headaches..?



## The Memotech 64K Memopak

The growth of interest in computer use caused by the introduction of the Sinclair ZX81 has made new and exciting demands on the ingenuity of electronic engineers. At Memotech we have focused our attention on the design of an inexpensive, reliable memory extension.

The Memopak is a 64K RAM pack which extends the memory of the ZX81 by a further 56K. Following the success of our 48K memory board the new memory extension is designed to be within the price range expected by Sinclair users. It plugs directly into the back of the ZX81 and does not inhibit the use of the printer or other add-on boards. There is no need for an additional power supply or for leads.

The Memopak together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts such basic commands as 10 DIM A(9000) 0-8K ...Sinclair ROM


8-16K...This section of memory switches in or out in 4K blocks to leave space for memory mapping, holds its contents during cassette loads, allows communication between programmes, and can be used to run assembly language routines.

16-32K...This area can be used for basic programmes and assembly language routines.

32-64K...32K of RAM memory for basic variables and large arrays.

With the Memopak extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

**DEALER ENQUIRIES WELCOME**

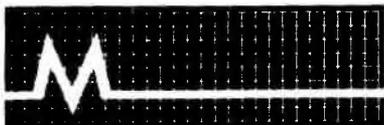

**MEMOTECH**

Memotech Ltd  
3 Collins Street  
Oxford · OX4 1XL  
Tel · 722102/3/4/5

Please debit my  
BARCLAYCARD/ACCESS\*  
account number:

\*Please delete  
whichever does not apply

Signature



Date

NAME

ADDRESS

Please rush me:

	Quantity	Price	Total
64K RAM, Assembled		£68.69	
HINTS & TIPS FOR ZX81 (BOOK BY ANDREW HEWSON)		£4.25	
Stock Control Programme		£ 25.00	
Payroll Programme		£ 25.00	

VAT @ 15%

Postage £2.00


ET12 TOTAL

To: Memotech Ltd., 3 Collins Street, Oxford, OX4 1XL Telephone (0865) 722102

# BE A SHARP BUSINESSMAN for only £278 +VAT
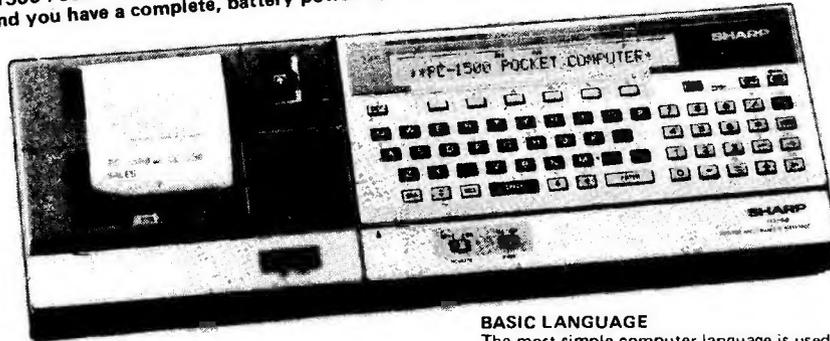
## COMPUTER AND 4-COLOUR PRINTER

The sensational new PC-1500 Pocket Computer approaches the Personal Computer in ability. Add the revolutionary CE-150 Graphic Printer and a cassette recorder and you have a complete, battery powered, Business Computer System that travels in your briefcase!




**SHARP CE-150**  
4-colour Graphic  
Printer  
**£130.39 + VAT;**  
Total £149.95

**SHARP PC-1500**  
'Basic' Pocket  
Computer  
**£147.78 + VAT;**  
Total £169.95

Price includes **SECURICOR 24 HOUR DELIVERY\***.  
Same day despatch, subject to availability.


### BUSINESS APPLICATIONS

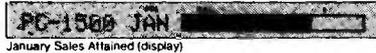


Quick and accurate data processing in daily business. Estimates, records and charts of sales, salaries, invoicing and all other data crucial to efficient business operations can be easily programmed, calculated and summoned.
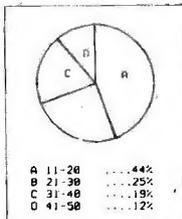
### ENGINEERING APPLICATIONS

Technical calculations in fields such as mathematics, statistics, measurements and mechanics are done superbly and easily. The calculator more than meets the requirements of engineers and scientists.




Sales Chart (printout)

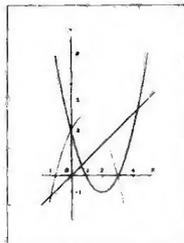

Equational Graph (printout)
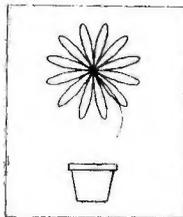
### MANAGEMENT APPLICATIONS

Balance sheets, so crucial to management analysis, and profit calculations by break-even point analysis are instantly yours with the PC-1500. By using the integral clock, calendar and alarm functions, this computer can also be used as a schedule reminder.



Computer Graphic (printout)

### HOBBY APPLICATIONS

Many popular computer games can be played, including Blackjack, utilising the random number function. Use the clock and alarm for speed games. The Computer Graphics will draw virtually any pattern.



Train (display)

### BASIC LANGUAGE

The most simple computer language is used for programming ease. Additional BASIC terms provide variables including two-dimensional arrays, variable strings and many other advanced features.

### LARGE MEMORY

16K bytes of ROM and 3.5K bytes of RAM, with 2.6K bytes in the user area. Adding the optional CE-151, 4K byte memory module, expands the RAM to 7.5K bytes. An 8K byte memory module will be available soon. The PC-1500 is battery powered and program and data memories are fully protected, even when switched off.

### MINI-GRAPHIC DISPLAY

The 7 x 156 dot matrix allows almost any display, including game symbols. Line width is 26 characters and/or numbers.

### HIGH SPEED DATA PROCESSING

The C-MOS 8-bit CPU enables swift data processing. Complicated technical or business calculations require far less time.

### QWERTY TYPEWRITER KEYBOARD

The first in a pocket computer. Lower case letters are available. With the optional CE-150 colour graphic printer, the PC-1500 can serve as a small personal typewriter. Word Processor software will be available soon.

### SIX SOFTWARE KEYS

These can serve as reservable keys, or as definable keys to define programs.

### CE-150 4-COLOUR GRAPHIC PRINTER/CASSETTE INTERFACE

Automatic program, data and calculation printing. It prints virtually any drawing in either red, black, green, or blue. Characters are printed in nine different sizes and in lines ranging from 4 to 36 digits in length. You can control the printer completely and direct the printing either up, down, left, or right. As a cassette interface it will connect up to two cassette recorders, one for data and program storage, the other for their recall. The CE-150 has a built-in rechargeable battery and is supplied with a mains adaptor, type EA-150.

### AVAILABLE SOON

\* RS-232C interface. \* Software board to serve as input keys in graphics, or pictures, previously drawn on a template. \* ROM (MASK ROM) module also applicable. \* A wide range of business software.

### DIMENSIONS

PC-1500: 195Wx25.5Hx86Dmm (7-11/16x1x3-3/8") Wt 375g (0.83lb)  
CE-150: 330Wx50Hx115Dmm (13x2x4 inches). Wt 900g (1.98lbs).

Full 12 MONTHS guarantee, with **EQUIPMENT LOAN SERVICE** during downtime.

**\*SAME DAY DESPATCH** of orders — Systems by **SECURICOR 24** hour service, (to attended premises only) or by first class registered post. **AT NO EXTRA COST\***

**SEND FOR FULL DETAILS** to **TEMPUS**, the Hand-Held Computer Specialists.

# TEMPUS

38 Burleigh Street, Cambridge CB1 1DG.  
Tel: 0223 312866

To: **Tempus**, FREEPOST, 38 Burleigh St, Cambridge CB1 1BR.

QTY	ITEM	INFO	PRICE	TOTAL
	PC-1500 Pocket Calculator		£169.95	
	CE-150 Four Colour Printer		£149.95	
	CE-151 4K Byte RAM Module		£ 49.95	
			<b>Total inc VAT</b>	

For information only tick appropriate box

I herewith enclose a cheque or Postal Orders value £ \_\_\_\_\_  
or I wish to pay by Access B'card/Visa.

My number is:

Name:

Address:

# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

## BEGINNERS

- Beginners Guide to Electronics Squires £4.50
- Beginners Guide to Transistors Reddihough £4.50
- Beginners Guide to Integrated Circuits Sinclair £4.50
- Beginners Guide to Radio King £4.50
- Beginners Guide to Audio Sinclair £4.50
- Introducing Amateur Electronics Sinclair £4.50
- Introducing Microprocessors £5.20
- Understanding Electronic Circuits Sinclair £5.30
- Understanding Electronic Components Sinclair £5.30

## APPLICATIONS COOKBOOKS

- TV Typewriters Cookbook £9.35
  - CMOS Cookbook £9.85
  - Active Filter Cookbook £11.30
  - IC Timer Cookbook £8.65
  - IC Op-Amp Cookbook £12.20
  - ITL Cookbook £9.15
  - MC 6809 Cookbook Carl D. Warren £5.30
  - PLL Synthesiser Cookbook Kinley £5.85
  - 8085A Cookbook Titus £10.75
- 
- How To Build Electronic Kits Chapel £3.45
  - 110 Electronic Alarm Projects Marston £5.25
  - 110 Semiconductor Projects for the Home Constructor Marston £5.25
  - 110 Integrated Circuit Projects for the Home Constructor Marston £5.25
  - 110 Thyristor Projectors Using SCRs Marston £5.25
  - 110 Waveform Generator Projects Marston £5.25
  - 99 Practical Electronic Projects Friedman £4.20

## COMPUTING & MICROPROCESSORS

- What is a Microprocessor? 2 cassette tapes plus a 72-page book £10.00
- Beginners Guide to Computers and Microprocessors with projects £6.05
- Basic Computer Games Ahl £6.05
- Basic for Home Computers Albrecht £6.60
- Illustrating Basic Alcock £4.25
- Troubleshooting Microprocessors and Digital Logic Goodman £6.10
- Z-80 Microcomputer Handbook £9.35
- Microprocessors in Instruments and Control Bibbero £15.30
- Basic Basic Coan £9.95
- Advanced Basic Coan £9.95
- 1001 Things to do with your Personal Computer Sawusch £8.00
- Microcomputers, Microprocessors, Hardware, Software and Applications Hilburn £17.40
- Microprocessor Systems Design Klingman £21.95
- Introduction to Microprocessors Leventhal £11.25
- Microprocessor Technology, Architecture and Applications £11.30
- Basic with Style Nagin £6.30
- Microcomputer Design Ogden £9.25
- Hands on Basic with a PET Peckham £11.95
- 6800 Software Gourmet Guide and Cookbook Scelbi £9.30
- 8080 Software Gourmet Guide and Cookbook £9.30
- The 8080A Bugbook Rony £10.05
- 8080/8085 Software Design Titus £10.05
- How to Design, Build and Program your own Working Computer System £7.10
- Your Own Computer Waite £2.25
- Microcomputer Interfacing Handbook A/D & D/A £6.35
- Crash Course in Microcomputers Frenzel £14.95
- Musical Applications of Microprocessors Chamberlain £20.95
- The Pascal Handbook Tiberghien £12.45
- 50 Basic Exercises Lamoitier £11.10
- Learning Basic with the Sinclair ZX80 £4.95
- Microprocessors for Hobbyists Coles £4.25
- Introduction to Microcomputer Programming Sanderson £5.25

- Microprocessors and Microcomputers for Engineering Students and Technicians Woolland £5.95
- Using CP/M - Self Teaching Guide Ashley Fernandez £6.95
- Digital Counter Handbook Frenzel £8.65
- 33 Challenging Computer Games for TRS80-Apple-Pet Chance £5.75
- How to Build Your Own Working Robot Pet Dalesta £5.75
- Microprocessor and Digital Computer Technology £16.00
- Guidebook to Small Computers Barden £4.20
- How to Debug Your Personal Computer Huffman £6.30
- How to Troubleshoot and Repair Microcomputers Leuk £6.30
- 6809 Microcomputer Programmes and Interfacing with Experiments Staugaard £11.45
- Wordprocessors Programmed. Training Guide with Practical Application £
- Digital Circuits and Microcomputers Johnson £9.75
- Experiments in Artificial Intelligence for Small Computers £7.25

## TEST

- The Oscilloscope in Use Sinclair NEW EDITION 1982
- How to Get More Out of Low-cost Electronic Test Equipment Tobery £5.50

## THEORY

- Digital Signal Processing. Theory and Applications Rabiner £26.40
- Electronic Communication Systems Kennedy £8.95
- Principles of Communication Systems Taub £8.40
- Introduction to Digital Filtering Bognor £13.30
- Transistor Circuit Design Texas Instruments £10.95
- Electronic Circuit Design Handbook Design of active filters, with experiments: Berlin £6.80

## REFERENCE

- Electronic Engineers Reference Book Turner £42.00
- Electronic Components Colwell £4.00
- Electronic Diagrams Colwell £4.00
- International Transistor Selector Towers New £10.70
- International FET Selector Towers £4.60
- International Op-Amp Linear IC Selector Towers £8.00
- International Microprocessor Selector Towers £16.00
- Dictionary of Audio - Radio and Video Roberts £16.00
- Dictionary of Electronics Amos £16.00
- Dictionary of Electrical Engineering Amos £16.00
- Dictionary of Telecommunications Amos £16.00
- Giant Book of Electronic Circuits Collins £12.75
- World Radio/TV Handbook Vol. 35 1981 £10.50
- How to Build Electronic Projects Malcolm £6.45
- Modern Electronic Circuit Reference Manual Marcus £33.50

Please send me the books indicated. I enclose cheque/postal order for £.....

I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4						
4	9	2	9						


Signed .....

Name .....

Address .....
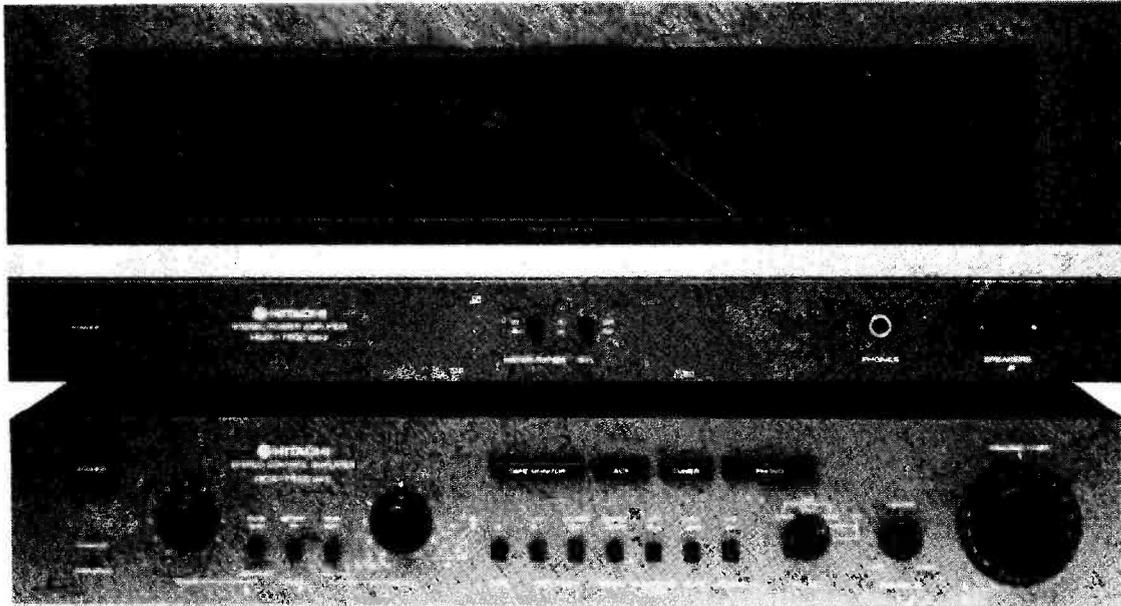
# AUDIOPHILE

It's dents-in-the-desk time, as Ron Harris listens to some hernia-inducing Hitachi hi-fi. This MOSFET combo is mighty in more ways than one.



This month an excursion into MOSFET territory, made in the sure company of Hitachi — who can be regarded as something of pioneers in the field. Actually, this review comes about, in its present form, by the strangest of circumstances. Firstly, I was assembling a 'group-test' of four or five high-quality amplifier combinations of various technical bents. I know that sounds like an orgy in an all-male laboratory, but I can assure you my motives were pure.

As with all things in life, some arrive ahead of others, and the Hitachi came weeks ahead of the rest. (The Bishop's actress would have been proud of them. . . .) In between times, there was a press launch from a major manufacturer for one of those few new models which can raise the eyebrows and clean out the ears in anticipation.

More detail than that I dare not reveal — the BOYS are leaning over my shoulder, hands on violin cases, even as I write this — death comes but once and that painfully. Embargo dates shalt thou keep, lest thy tender bits be removed and cast upon the waters. Watch next month's Audiophile. If I'm still in possession of my faculties, all questions will be answered. (I'm too young to die, I still haven't had that romantic dinner with Felicity Kendal. . . .)

Anyway, returning to the track upon which we embarked, the fact that I had to tie up large chunks of next month, allied to the somewhat tardy arrival of all the other amplifiers, left Hitachi home-free this month with their HMA-7500 II power-amp and HCA-7500 preamp combination — unusual for its employment of MOSFETs.

This is a subject upon which we have received much correspondence — mainly requests to produce a project. Well we did — two years ago. Ahead of our time again, you see. Designs age, however, and that Ambit unit is somewhat irrelevant by today's standards of quality. If we were going to retain our reputation for state-of-the-art electronics, a complete re-design was called for. Next month you will be presented with the results of our efforts. A hundred and odd watts of pure magic. MOSFET magic.

## Hitachi 7500 IIs

The 7500 IIs are actually cheaper than the Mark Is, but offer more facilities for lesser amounts of green stuff. The preamp is well-decked out with variable turnover tone controls, two tape inputs, moving-coil pre-preamp and variable input parameters on moving magnet. In addition the volume control is bedecked with little decibel numbers and there is a loudness control, a mute switch and a subsonic filter.

The power amp is bloody huge. It would be polite to call it 'large', but polite here is insufficient. Bloody huge somehow captures the spirit of the thing in a way that 'large' simply fails to do. The front panel sports huge meters, too — carefully graduated in watts RMS into four and eight ohms. In addition there is a 'BTL' facility which allows the 80 W stereo to be transformed into 150 W mono at no sacrifice in quality. Two pairs of speakers are catered for, although some care in choice is required.

All inputs and outputs on the preamp are phono — the dreaded DIN is nowhere in sight. Three cheers for Oriental partisanship. Sometimes anyway.

## HCA-7500 II Preamp

At £139 this design represents a large number of buttons per pound. There are a restricted number of separate preamps available on the shop-shelves today and most cost considerably in excess of £139. Strange as it may seem to those descendants of Ebenezer Scrooge reading this, the Hitachi can be safely regarded as a BUDGET unit.

These days I am becoming increasingly suspicious of the disc-amplifier stages in all designs, especially if they are intended to cope with the moving-coil variety of groove followers.

Accordingly all preamps get somewhat of a beating about the equalisation if they pass this way. Well, it makes a starting point and we all need one of those, do we not? In addition the continual march of digital and high-quality 'super-discs' places ever increasing demands upon these stages. They are thus increasingly under the microscope.

Regrettably the 7500 did not pass this particular line unscathed. Technically it fared well under test. You can read the results for yourselves. However, in use, the pickup stage sounded below par — especially when compared to the rest of the 7500 set-up.

The moving-magnet amp added a certain warmth to the sound, which spoke of low-frequency colouration and clouded detail right up into the mid-range. The moving-coil option added some noise but did nothing to cleanup the sound.

These are absolute judgements you realise, relative to a reference far more expensive than the 7500. Taking price into consideration alters the balance to the extent that the Hitachi is a good value performer for its cost and one which does not seem ill-mannered in all but the most exalted company.

### Pickup Downs

Apart from this, the HCA is a fine unit indeed. It is quiet and efficient and does its job with a minimum of fuss. Pulse testing the unit reveals a good handling of transients, a function of the unit's wide bandwidth and fast slewing, and conventional tests point to low-noise and flat frequency response.

Mechanically the controls operate smoothly and give the impression of having been well engineered. The volume control is a 'click-stop' type of high quality. Somehow, though, I found it awkward to use. It seemed to be wired the wrong way around! An odd observation I know, but if you tried it I think you would see what I mean. The dB graduations, which get lower in value as the volume goes up, don't help either, correct though they may be!

Cartridges tried with the HCA-7500 included the Dynavec-tor Ruby and the DV20AII, the Goldring G900IGC and the Shure MV30H reported upon last month. Tuner source was the trusty (and unsurpassed?) Pioneer TX9500.

Tape facilities allow for two decks, with monitor on either and dubbing between the two in either direction. There is an unobtrusive little push-button labelled "Source Copy" which enables the outputs to tape. Forget to push this and you can have all sorts of fun trying to find out "where has all the signal gone."

Three impedances are available for moving magnets (22k, 47k and 100k) and two input levels for moving-coil, (0.1 mV and 2.5 mV) at 100R input impedance. More useful perhaps would be capacitance switching for the MM units, to better control high frequency behaviour.

### Loudness Played Softly

I've never understood why a button which corrects for hearing losses at low levels is called loudness. Still I suppose 'softness' conjures up images of fabric conditioners and woolly sounds.

If you must have one of these ill-named tone controls, then this is about the best you'll find! Most tend to wildly overdo things in the bass with an excess of 10 dB boost at 100 Hz and below — and no top-end correction at all. Figure 1 shows the

Fletcher-Munson curves upon which all such correction is based and you can see the required top-end lift quite clearly.

Because human hearing is less sensitive to extremes in the audio range, at low listening levels your perception of bass and treble is severely limited. Loudness controls are intended to compensate by shaping the frequency response into an inverse plot of the hearing sensitivity curve you see in the diagram.

At high levels, where frequency has far less effect upon perceived level, they should be inoperative.

As I said, the Hitachi HCA 7500 II boasts a somewhat more believable compromise than most.

### Powerful Amps

The HMA-7500 II is a hefty piece of work, sporting two well-endowed power supplies and those massive meters. It is possible to switch the machine into bridged mode, doubling the power available into eight ohms. Those PSUs boded well for the burst power capability of the amp, an idea which seemed to be borne out by early listening tests — only to cause confusion in the lab!

The rated 75 W was delivered uncomplainingly from 5 Hz to 70 kHz (RMS) and at 1 kHz 90 W was available. This with less than 0.01% total distortions (THD and IM). Burst power delivery proved to be a disappointing 104 W into 8R — I would have expected greater things in view of the sheer size of the power supplies. Into 4R, delivery was, as near as dammit, the same — 100 W. Into 2R strange things began to happen, courtesy of the protection, and no readings were feasible.

Lesson? Be careful with speaker choice if you intend to push the 7500 II near its limits.

### Burst Testing

I've had some puzzled letters — and one very aggrieved epistle for which 'tirade' is a good word — enquiring as to how I


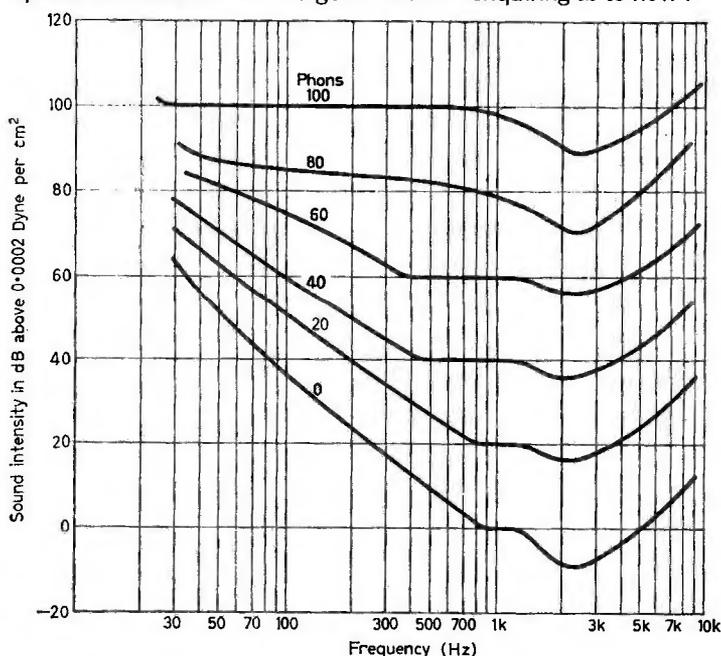


Fig. 1 Above: the Fletcher-Munson graphs of equal loudness. The curves plot the amount of energy required to produce a sound of equal intensity at the ear, for varying frequencies.

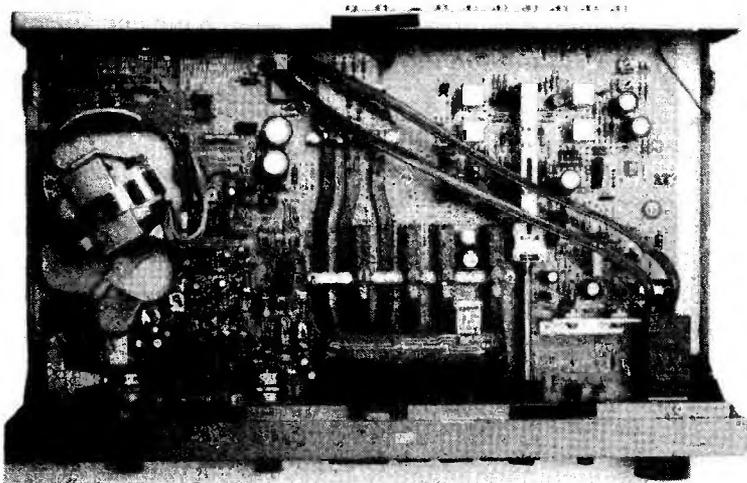

Left: the inside story on the 7500 preamp. Note the use of mechanical couplers to the input switching, which is PCB-mounted near the input sockets. Just about everything that can be done to reduce noise, has been done.

obtain my oft-quoted burst delivery power measurements.

The basic idea is to better simulate what the amp is capable of doing with music, as opposed to sine or square waves, thus correlating more closely lab test results with listening tests. As a music signal is composed of a whole spectrum of short-duration tone-bursts scattered from 20 Hz-20 kHz fairly randomly (!?), I don't think that a sine wave at 1 kHz is a close enough approximation, even in short pulses.

My own way of obtaining a number is to gate a 1 mS-10 mS burst of white noise, modulated by a sine wave, into the unit under test and read the resulting power delivery into an eight-ohm load. At present I'm working on improving the load, so that it will better approximate a speaker.

The variable length of the input pulse is required to discover when and where the protection, or limiting, operates in the amplifier circuitry. A perfect amplifier would deliver X watts into 8R, 2X watts in 4R, 4X watts into 2R and ∞ watts into a short-circuit! All without blowing fuses of course.


Allied to the good and true RMS readings, for long term delivery, I think these burst measurements paint a fairly good picture of the capabilities of a particular unit with regard to actually playing records.

I would welcome readers' comments on the method outlined so far, or any suggestions as to how it could be improved. (Physically possible suggestions only please, it's a big test-bench.)
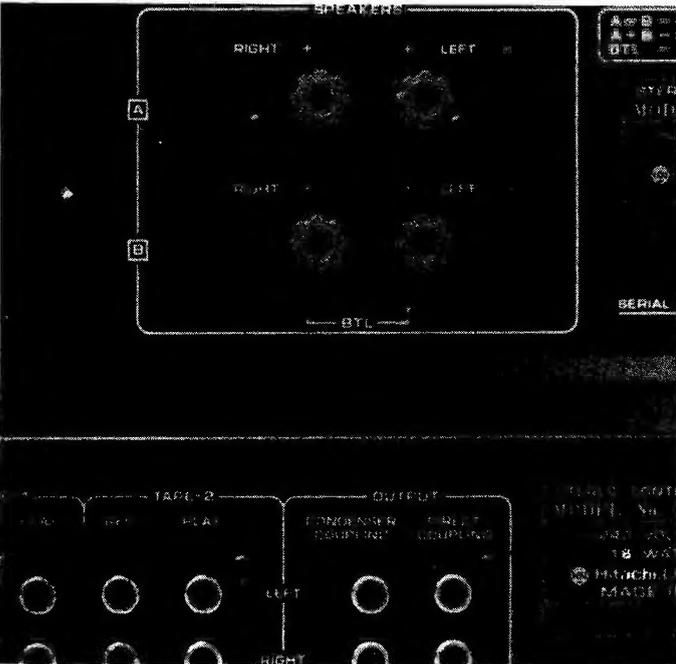
### Hitachi Hi-Power

In the bridged mode the 7500 II delivered 150 W into 8R all the way from 20 Hz-20 kHz. Burst power was a very healthy 201 W into 8R and 189 W into 4R. It is somewhat more choosy about impedance in this mode, so I did not attempt a 2R reading. Test loads are expensive and I'm running out of fuses.

Signal-to-noise was an impressive 94 dB down, unweighted and damping factor held above 50 down to 40 Hz. Provided the speaker doesn't take a downward leap in impedance, therefore, good control of the bass could be expected.



Bridging the 7500 II means connecting across the 'lives' of the two sets of speaker terminals. This is denoted by the obscure legend BTL. It actually stands for "Bridge Transformer Less"! I kid you not.

### Testing Conclusions

Overall then, the combination gave a good technical performance, with the power amp appearing to be of a higher standard than the preamp, with only a very few reservations.

In order to test both, the combination was first tried together and then independent of each other, with known preamp and

power units standing in for the missing partner where necessary. In this way a clearer idea of the sound behaviour of each unit could be obtained.

## TEST RESULTS

### HCA - 7500 II

#### Signal To Noise Ratios (to output, weighted)

Moving magnet	: 85dB
Moving coil	: 74dB
Tuner/aux	: 88dB
Tape	: 88dB

#### Frequency Response (to output)

Disc input	: 20Hz - 20kHz ± 1.5dB
Tuner/aux	: DC - 100kHz ± 1dB

#### Total Distortions (at output)

Moving magnet	:
Moving coil	: Less than 0.01% from 20Hz - 20kHz
Tuner/aux	:

#### Overload/Max output

Moving magnet	: 300mV (for 0.01% THD)
Moving coil	: 21mV (for 0.01% THD)

#### Sensitivity (for 1V output)

Moving magnet	: 3mV
Moving coil	: 0.1mV
Tuner/aux	: 180mV
Tape	: 180mV

### HMA - 7500 II

#### Power Output (into 8R/4R)

RMS (both channels)	: 94W (20Hz - 20kHz) 91W (4R)
Burst Power (see text)	: 104W (8R) 100W (4R)

#### Bandwidth

: DC - 180kHz

#### Frequency Response

: DC - 20kHz ± 0.5dB

Harmonic Distortion	: 0.01%
TIM Distortion	: zero
IM Distortion	: 0.01%

#### Signal - to - Noise (incl. hum, weighted)

: 120dB

#### Damping Factor (100Hz)

: 60 (110 at 1kHz)

Price for pre/power : approx. £400

### Making MOSFET Music

As a pair the 7500s performed well — with the previously stated reservation on pickup input — sounding clear and powerful. Mid-range rendition was good and bass transients well handled. The treble tended to be a little 'soft', if the unit is driven hard — an effect which is infinitely preferable to the biting edge some designs reveal under these conditions.


The preamp has a good performance for the price, which is low enough that, should you upgrade your cartridge beyond its capabilities, you could afford a specialist pickup amplifier to overcome the differences.

The power amp is very good indeed. It separates out the components of a complex piece very well, and portrays a convincing stereo image. The wildly dancing meters are impossible to ignore — what that means to you, be it good or bad, is a personal decision.

In bridged mode — which I have only been able to try in mono as yet — I felt the amp was even better, more open and with a more confident bass. I have contacted Hitachi and hope to be able to include a bridged pair of 7500s in the forthcoming comparison.
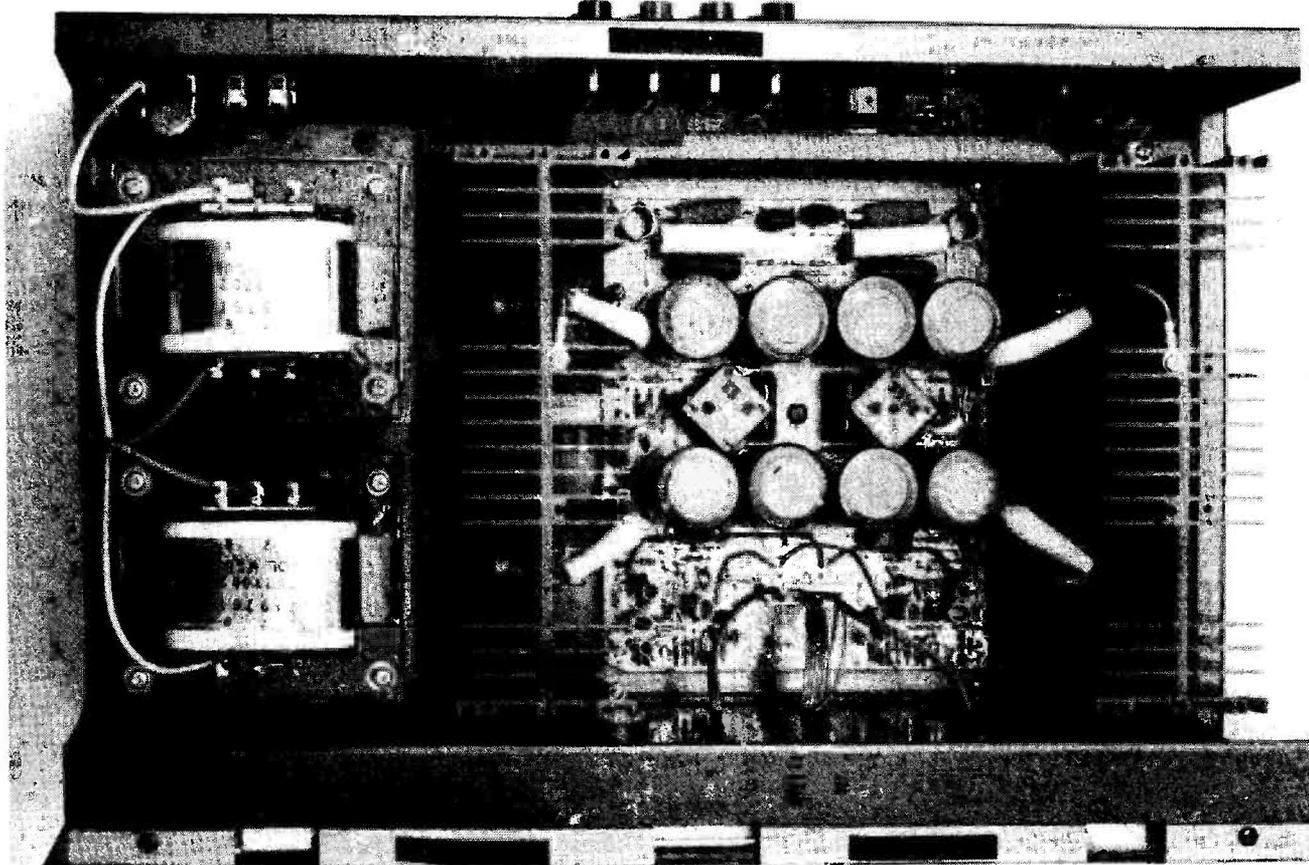
### Final Notes

Final comments? Very good power amp by any standards. The preamp is good value for money, but the pickup input lets it down slightly. Overall a worthy production and one that cannot be considered expensive at £400.



Above: the mighty internals of the 7500 II power amp. Those huge transformers endow the machine with excellent separation and good power delivery.

ETI


## The complete PCB production system

- \*INEXPENSIVE
- \*EASY TO USE\*
- \*SAFE
- \*COMPLETE KIT

Unique etching system, leakproof storage box, Neutraliser, 'dalo' etch-resist pen, abrasive cleaning block, two 6" x 4" copper clad boards, plus FREE pack of etch-resist transfer symbols

**MAKES**  
at least 12  
Euroboards  
for...

**£9.50 ONLY**  
incl. p&p and VAT!

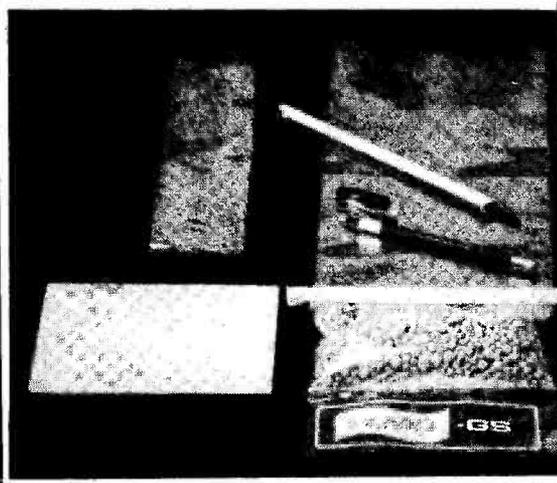

Please send me  
PO / Cheque to Decon Laboratories Ltd. Total £

Name

Address

kits at £9.50 each  
Decon Laboratories Ltd. Total £

Send to:  
FREEPOST  
Decon Laboratories Ltd.  
Conway Street,  
Hove, Sussex  
BN3 3LY

*FREE-pack of etch resist transfer symbols with every system*




Many of you have been our customers for many years. Our shop has been in CRICKLEWOOD for over a decade under a different name, which we will not mention out of respect. CRICKLEWOOD is the shop with probably the widest range of components, because of our policy of stocking to the needs of our customers. CRICKLEWOOD'S approach is different because we listen & learn from our customers. If you don't see what you wish discuss it with us - we may be able to help. All in-stock items despatched to you same day. Quantity discounts given. Govt. Depts., Schools, Exports catered for. Please enquire.

**ORDER FROM CRICKLEWOOD IS EASY!!!**  
 \* PY PHONE (QUICKEST WAY): Quote Barclaycard, Visa, American Express, Access number for immediate service. (No minimum order)  
 \* BY POST: Cheque, PO or send card no. with signature (No minimum order)  
 \* CALL IN & COLLECT: Our expert staff are there to help you. Just 1 1/2 miles from MI on main A5 (Edgware Rd.) Approx 3 1/2 miles from Marble Arch  
 Please add 15% VAT & 70p p&p to all orders - more for heavier goods.  
**CRICKLEWOOD ELECTRONICS LTD., 40 BROADWAY, LONDON NW2. TEL: 01-452 0161**

1N5700 42p	1N1152 1.75	6 amp type	VA1065 40p	LM1008 3.90	MC3340 1.45	TDA1012A 2.89	74161 82p	74ALS283 1.59	74C164 1.15	4553 2.90	Z80APIO 3.50	10 0MHz 2.75
1N5704 46p	1N1154 1.85	Square with hole	VA1055 40p	LM11CH 5.50	MC3401 = 1.45	TDA1022 2.80	74162 82p	74C165 2.00	4556 2.90	Z80D58 3.75	10 0MHz 2.75	
1N5707 46p	1N1154A 2.41		VA1056 40p	LM114 5.90	LM3401 1.45	TDA1024 1.00	74163 82p	74C173 98p	4560 2.90	Z80D68 3.75	10 0MHz 3.25	
1N5708 46p	1N1154A 2.41		VA1057 40p	LM137K 11.62	MC3402 1.45	TDA1034 3.00	74164 82p	74C174 1.22	4562 2.90	Z80D78 3.75	10 0MHz 3.25	
1N5709 46p	1N1154A 2.41		VA1058 40p	LM301A 1.00	MC3403 1.45	TDA2020 3.20	74165 82p	74C175 1.00	4564 2.90	Z80D88 3.75	10 0MHz 3.25	
1N5710 46p	1N1154A 2.41		VA1059 40p	LM301AH 2.90	MC3404 1.45	TDA2022 4.00	74166 82p	74C182 1.15	4566 2.90	Z80D98 3.75	10 0MHz 3.25	
1N5711 46p	1N1154A 2.41		VA1060 40p	LM305A 1.00	MC3405 1.45	TDA2522 4.00	74167 82p	74C193 1.13	4568 2.90	Z80D108 3.75	10 0MHz 3.25	
1N5712 46p	1N1154A 2.41		VA1061 40p	LM305AH 2.90	MC3406 1.45	TDA2524 3.00	74168 82p	74C194 1.20	4570 2.90	Z80D118 3.75	10 0MHz 3.25	
1N5713 46p	1N1154A 2.41		VA1062 40p	LM305B 1.00	MC3407 1.45	TDA2526 3.00	74169 82p	74C195 1.06	4572 2.90	Z80D128 3.75	10 0MHz 3.25	
1N5714 46p	1N1154A 2.41		VA1063 40p	LM305BH 2.90	MC3408 1.45	TDA2528 3.00	74170 82p	74C200 1.00	4574 2.90	Z80D138 3.75	10 0MHz 3.25	
1N5715 46p	1N1154A 2.41		VA1064 40p	LM305C 1.00	MC3409 1.45	TDA2530 3.00	74171 82p	74C211 1.20	4576 2.90	Z80D148 3.75	10 0MHz 3.25	
1N5716 46p	1N1154A 2.41		VA1065 40p	LM305CH 2.90	MC3410 1.45	TDA2532 3.00	74172 82p	74C221 1.20	4578 2.90	Z80D158 3.75	10 0MHz 3.25	
1N5717 46p	1N1154A 2.41		VA1066 40p	LM305D 1.00	MC3411 1.45	TDA2534 3.00	74173 82p	74C232 1.20	4580 2.90	Z80D168 3.75	10 0MHz 3.25	
1N5718 46p	1N1154A 2.41		VA1067 40p	LM305E 1.00	MC3412 1.45	TDA2536 3.00	74174 82p	74C243 1.20	4582 2.90	Z80D178 3.75	10 0MHz 3.25	
1N5719 46p	1N1154A 2.41		VA1068 40p	LM305F 1.00	MC3413 1.45	TDA2538 3.00	74175 82p	74C254 1.20	4584 2.90	Z80D188 3.75	10 0MHz 3.25	
1N5720 46p	1N1154A 2.41		VA1069 40p	LM305G 1.00	MC3414 1.45	TDA2540 3.00	74176 82p	74C265 1.20	4586 2.90	Z80D198 3.75	10 0MHz 3.25	
1N5721 46p	1N1154A 2.41		VA1070 40p	LM305H 2.90	MC3415 1.45	TDA2542 3.00	74177 82p	74C276 1.20	4588 2.90	Z80D208 3.75	10 0MHz 3.25	
1N5722 46p	1N1154A 2.41		VA1071 40p	LM305I 1.00	MC3416 1.45	TDA2544 3.00	74178 82p	74C287 1.20	4590 2.90	Z80D218 3.75	10 0MHz 3.25	
1N5723 46p	1N1154A 2.41		VA1072 40p	LM305J 1.00	MC3417 1.45	TDA2546 3.00	74179 82p	74C298 1.20	4592 2.90	Z80D228 3.75	10 0MHz 3.25	
1N5724 46p	1N1154A 2.41		VA1073 40p	LM305K 2.90	MC3418 1.45	TDA2548 3.00	74180 82p	74C309 1.20	4594 2.90	Z80D238 3.75	10 0MHz 3.25	
1N5725 46p	1N1154A 2.41		VA1074 40p	LM305L 1.00	MC3419 1.45	TDA2550 3.00	74181 82p	74C320 1.20	4596 2.90	Z80D248 3.75	10 0MHz 3.25	
1N5726 46p	1N1154A 2.41		VA1075 40p	LM305M 1.00	MC3420 1.45	TDA2552 3.00	74182 82p	74C331 1.20	4598 2.90	Z80D258 3.75	10 0MHz 3.25	
1N5727 46p	1N1154A 2.41		VA1076 40p	LM305N 2.90	MC3421 1.45	TDA2554 3.00	74183 82p	74C342 1.20	4600 2.90	Z80D268 3.75	10 0MHz 3.25	
1N5728 46p	1N1154A 2.41		VA1077 40p	LM305P 1.00	MC3422 1.45	TDA2556 3.00	74184 82p	74C353 1.20	4602 2.90	Z80D278 3.75	10 0MHz 3.25	
1N5729 46p	1N1154A 2.41		VA1078 40p	LM305Q 1.00	MC3423 1.45	TDA2558 3.00	74185 82p	74C364 1.20	4604 2.90	Z80D288 3.75	10 0MHz 3.25	
1N5730 46p	1N1154A 2.41		VA1079 40p	LM305R 2.90	MC3424 1.45	TDA2560 3.00	74186 82p	74C375 1.20	4606 2.90	Z80D298 3.75	10 0MHz 3.25	
1N5731 46p	1N1154A 2.41		VA1080 40p	LM305S 1.00	MC3425 1.45	TDA2562 3.00	74187 82p	74C386 1.20	4608 2.90	Z80D308 3.75	10 0MHz 3.25	
1N5732 46p	1N1154A 2.41		VA1081 40p	LM305T 1.00	MC3426 1.45	TDA2564 3.00	74188 82p	74C397 1.20	4610 2.90	Z80D318 3.75	10 0MHz 3.25	
1N5733 46p	1N1154A 2.41		VA1082 40p	LM305U 2.90	MC3427 1.45	TDA2566 3.00	74189 82p	74C408 1.20	4612 2.90	Z80D328 3.75	10 0MHz 3.25	
1N5734 46p	1N1154A 2.41		VA1083 40p	LM305V 1.00	MC3428 1.45	TDA2568 3.00	74190 82p	74C419 1.20	4614 2.90	Z80D338 3.75	10 0MHz 3.25	
1N5735 46p	1N1154A 2.41		VA1084 40p	LM305W 1.00	MC3429 1.45	TDA2570 3.00	74191 82p	74C430 1.20	4616 2.90	Z80D348 3.75	10 0MHz 3.25	
1N5736 46p	1N1154A 2.41		VA1085 40p	LM305X 2.90	MC3430 1.45	TDA2572 3.00	74192 82p	74C441 1.20	4618 2.90	Z80D358 3.75	10 0MHz 3.25	
1N5737 46p	1N1154A 2.41		VA1086 40p	LM305Y 1.00	MC3431 1.45	TDA2574 3.00	74193 82p	74C452 1.20	4620 2.90	Z80D368 3.75	10 0MHz 3.25	
1N5738 46p	1N1154A 2.41		VA1087 40p	LM305Z 1.00	MC3432 1.45	TDA2576 3.00	74194 82p	74C463 1.20	4622 2.90	Z80D378 3.75	10 0MHz 3.25	
1N5739 46p	1N1154A 2.41		VA1088 40p	LM305AA 2.90	MC3433 1.45	TDA2578 3.00	74195 82p	74C474 1.20	4624 2.90	Z80D388 3.75	10 0MHz 3.25	
1N5740 46p	1N1154A 2.41		VA1089 40p	LM305B 1.00	MC3434 1.45	TDA2580 3.00	74196 82p	74C485 1.20	4626 2.90	Z80D398 3.75	10 0MHz 3.25	
1N5741 46p	1N1154A 2.41		VA1090 40p	LM305C 1.00	MC3435 1.45	TDA2582 3.00	74197 82p	74C496 1.20	4628 2.90	Z80D408 3.75	10 0MHz 3.25	
1N5742 46p	1N1154A 2.41		VA1091 40p	LM305D 2.90	MC3436 1.45	TDA2584 3.00	74198 82p	74C507 1.20	4630 2.90	Z80D418 3.75	10 0MHz 3.25	
1N5743 46p	1N1154A 2.41		VA1092 40p	LM305E 1.00	MC3437 1.45	TDA2586 3.00	74199 82p	74C518 1.20	4632 2.90	Z80D428 3.75	10 0MHz 3.25	
1N5744 46p	1N1154A 2.41		VA1093 40p	LM305F 1.00	MC3438 1.45	TDA2588 3.00	74200 82p	74C529 1.20	4634 2.90	Z80D438 3.75	10 0MHz 3.25	
1N5745 46p	1N1154A 2.41		VA1094 40p	LM305G 2.90	MC3439 1.45	TDA2590 3.00	74201 82p	74C540 1.20	4636 2.90	Z80D448 3.75	10 0MHz 3.25	
1N5746 46p	1N1154A 2.41		VA1095 40p	LM305H 1.00	MC3440 1.45	TDA2592 3.00	74202 82p	74C551 1.20	4638 2.90	Z80D458 3.75	10 0MHz 3.25	
1N5747 46p	1N1154A 2.41		VA1096 40p	LM305I 1.00	MC3441 1.45	TDA2594 3.00	74203 82p	74C562 1.20	4640 2.90	Z80D468 3.75	10 0MHz 3.25	
1N5748 46p	1N1154A 2.41		VA1097 40p	LM305J 2.90	MC3442 1.45	TDA2596 3.00	74204 82p	74C573 1.20	4642 2.90	Z80D478 3.75	10 0MHz 3.25	
1N5749 46p	1N1154A 2.41		VA1098 40p	LM305K 1.00	MC3443 1.45	TDA2598 3.00	74205 82p	74C584 1.20	4644 2.90	Z80D488 3.75	10 0MHz 3.25	
1N5750 46p	1N1154A 2.41		VA1099 40p	LM305L 1.00	MC3444 1.45	TDA2600 3.00	74206 82p	74C595 1.20	4646 2.90	Z80D498 3.75	10 0MHz 3.25	
1N5751 46p	1N1154A 2.41		VA1100 40p	LM305M 2.90	MC3445 1.45	TDA2602 3.00	74207 82p	74C606 1.20	4648 2.90	Z80D508 3.75	10 0MHz 3.25	
1N5752 46p	1N1154A 2.41		VA1101 40p	LM305N 1.00	MC3446 1.45	TDA2604 3.00	74208 82p	74C617 1.20	4650 2.90	Z80D518 3.75	10 0MHz 3.25	
1N5753 46p	1N1154A 2.41		VA1102 40p	LM305P 1.00	MC3447 1.45	TDA2606 3.00	74209 82p	74C628 1.20	4652 2.90	Z80D528 3.75	10 0MHz 3.25	
1N5754 46p	1N1154A 2.41		VA1103 40p	LM305Q 2.90	MC3448 1.45	TDA2608 3.00	74210 82p	74C639 1.20	4654 2.90	Z80D538 3.75	10 0MHz 3.25	
1N5755 46p	1N1154A 2.41		VA1104 40p	LM305R 1.00	MC3449 1.45	TDA2610 3.00	74211 82p	74C650 1.20	4656 2.90	Z80D548 3.75	10 0MHz 3.25	
1N5756 46p	1N1154A 2.41		VA1105 40p	LM305S 1.00	MC3450 1.45	TDA2612 3.00	74212 82p	74C661 1.20	4658 2.90	Z80D558 3.75	10 0MHz 3.25	
1N5757 46p	1N1154A 2.41		VA1106 40p	LM305T 2.90	MC3451 1.45	TDA2614 3.00	74213 82p	74C672 1.20	4660 2.90	Z80D568 3.75	10 0MHz 3.25	
1N5758 46p	1N1154A 2.41		VA1107 40p	LM305U 1.00	MC3452 1.45	TDA2616 3.00	74214 82p	74C683 1.20	4662 2.90	Z80D578 3.75	10 0MHz 3.25	
1N5759 46p	1N1154A 2.41		VA1108 40p	LM305V 1.00	MC3453 1.45	TDA2618 3.00	74215 82p	74C694 1.20	4664 2.90	Z80D588 3.75	10 0MHz 3.25	
1N5760 46p	1N1154A 2.41		VA1109 40p	LM305W 2.90	MC3454 1.45	TDA2620 3.00	74216 82p	74C705 1.20	4666 2.90	Z80D598 3.75	10 0MHz 3.25	
1N5761 46p	1N1154A 2.41		VA1110 40p	LM305X 1.00	MC3455 1.45	TDA2622 3.00	74217 82p	74C716 1.20	4668 2.90	Z80D608 3.75	10 0MHz 3.25	
1N5762 46p	1N1154A 2.41		VA1111 40p	LM305Y 1.00	MC3456 1.45	TDA2624 3.00	74218 82p	74C727 1.20	4670 2.90	Z80D618 3.75	10 0MHz 3.25	
1N5763 46p	1N1154A 2.41		VA1112 40p	LM305Z 1.00	MC3457 1.45	TDA2626 3.00	74219 82p	74C738 1.20	4672 2.90	Z80D628 3.75	10 0MHz 3.25	
1N5764 46p	1N1154A 2.41		VA1113 40p	LM305AA 2.90	MC3458 1.45	TDA2628 3.00	74220 82p	74C749 1.20	4674 2.90	Z80D638 3.75	10 0MHz 3.25	
1N5765 46p	1N1154A 2.41		VA1114 40p	LM305B 1.00	MC3459 1.45	TDA2630 3.00	74221 82p	74C760 1.20	4676 2.90	Z80D648 3.75	10 0MHz 3.25	
1N5766 46p	1N1154A 2.41		VA1115 40p	LM305C 1.00	MC3460 1.45	TDA2632 3.00	74222 82p	74C771 1.20	4678 2.90	Z80D658 3.75	10 0MHz 3.25	
1N5767 46p	1N1154A 2.41		VA1116 40p	LM305D 2.90	MC3461 1.45	TDA2634 3.00	74223 82p	74C782 1.20	4680			
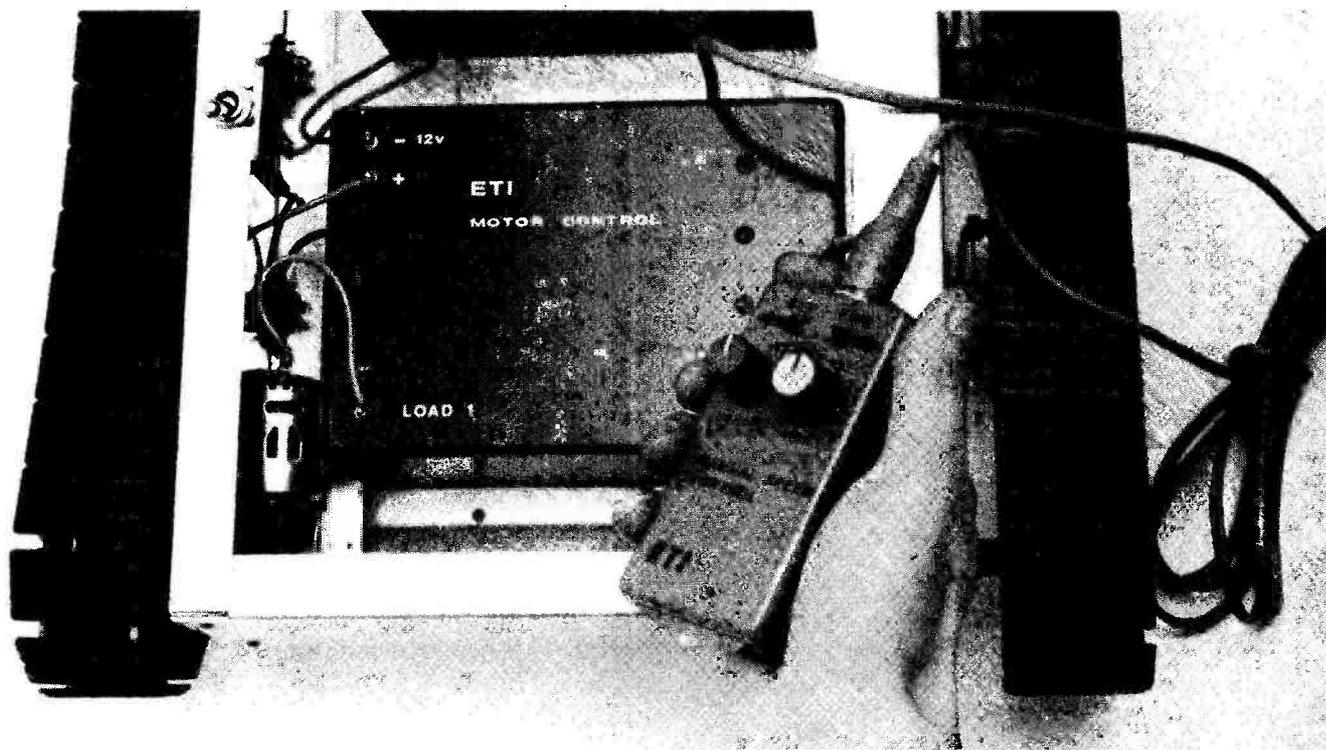
# ROBOT MOTOR CONTROL PART 3

This month we describe the construction of the analogue pulse width modulator and show how to interface it to the dual motor controller. Design and development by Rory Holmes.



The overlay diagram for the analogue pulse width modulator described last month is shown in Fig. 2. Assemble the PCB following the component orientations indicated and soldering in sockets for the ICs. If only one channel is required, the board can be cut in half along the dividing line, omitting the two links and assembling the circuit for channel 1. Overlay pictures for the transistors are correct for the specified 'L' versions and pin outs should be identified carefully if other types are used.

Veropins should be soldered in at all the points marked for terminations (18 in all). Spare positive and ground terminals have been included near the input and output points for flexibility. The resistor shown on the circuit diagram in last month's issue as the speed feedback input and marked as Rx on the overlay, should be included on the board; a value of 100k is

required. A 1M $\Omega$  shorting resistor should also be connected between the terminal pins marked for speed feedback input (GND and INPUT). This resistor prevents stray interference in the basic unit and can be easily removed for later addition of closed loop velocity control.

After mounting the two presets they should be set at about half-travel. (Ceramic base presets can crack quite easily, so take care when inserting these into the PCB.) These presets are used to apply a DC offset to the voltage summing amplifier, so shifting the control voltage range to the required level.

## Installation

Without plugging in the ICs, a 12 V power source can be connected to the board as shown. The power rails should be checked at the relevant pins on the IC sockets; also check that the 8 V

reference is present at the positive end of C13 and C6. If all is well, the power can be disconnected and the ICs plugged in. At this stage the board can now be mounted using brackets or insulating pillars directly above the power switching PCB in the diecast box. The 12 V power source is taken from the existing bridge-rectifier tags, and the two output signals, PWM and FOR/REV, should be wired to the corresponding pins on each channel of the power switching PCB. Have a look at the internal photographs with the analogue board.

The two manual control potentiometers, RV1 and 2 can now be wired up to the control voltage input. In the circuit diagram the positive ends of RV1 and 2 are shown connected to the +8 V reference; a four core cable would thus be needed for the remote attachment of these potentiometers with their limiting resistors R8 and R22.


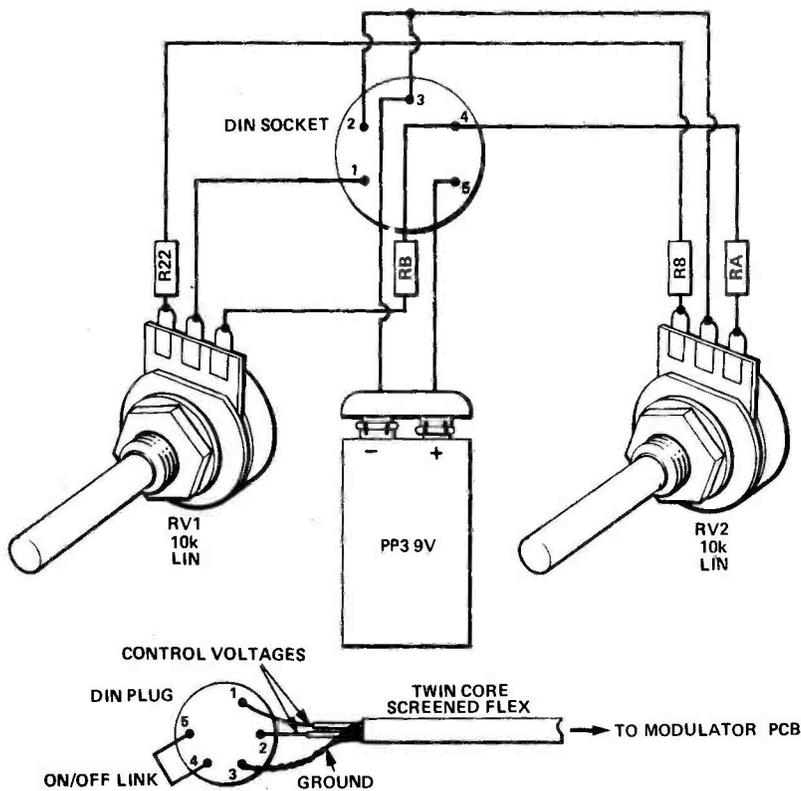


Fig. 1 Wiring diagram for the manual control unit.

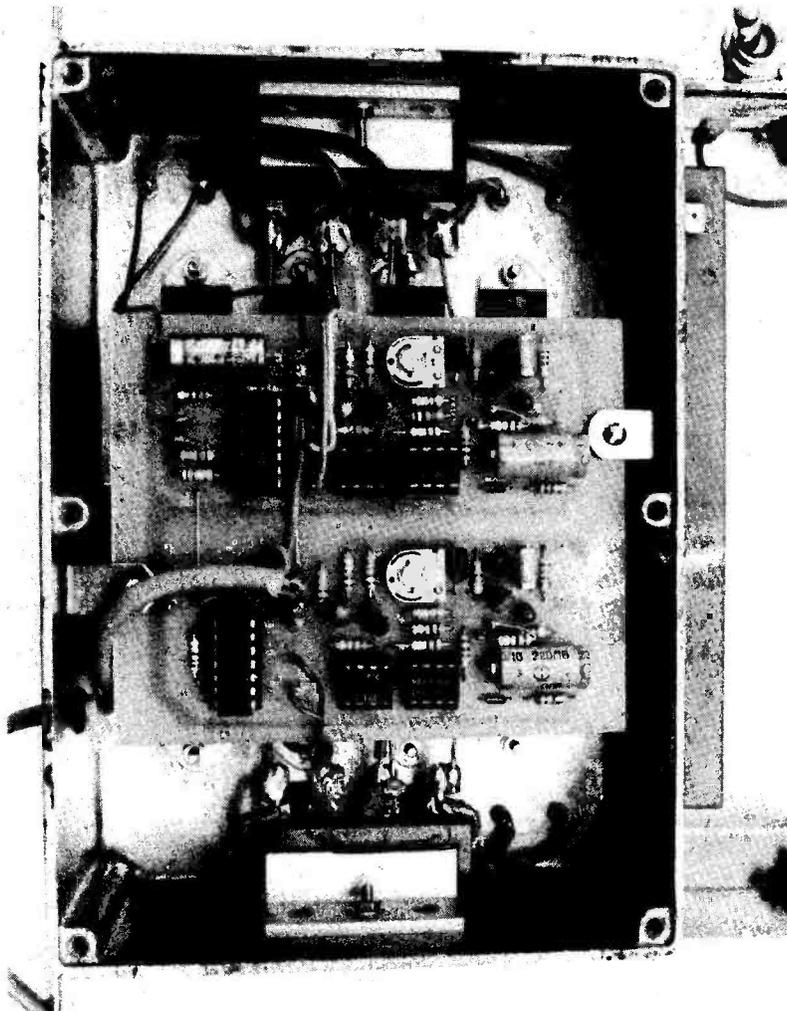

The analogue PWM board installed above the dual motor driver.

Essentially all that's required is a voltage variable from 0 to 8 V applied to the base of Q3, so to allow the use of cheaper twin core screened cable we mounted our pots in a small hand-size box with their own 9 V PP3 battery power source. A five pin DIN plug and socket mounted at one end connects the control voltages from the pot sliders, via the cable, to the modulator PCB. The cores are wired to the input terminals at the bases of Q3 and Q6, with the screen taken to the adjacent ground pin. Figure 1 illustrates the manual control wiring, the accompanying photo the internal appearance.

R8 and R22 are shown on the circuit diagram as 1k $\Omega$ ; these may be altered as required to limit the maximum reverse speed. RA and RB however are optional resistors for limiting the maximum slider voltage to 8 V; we used 1k $\Omega$  resistors to suit the 9 V battery.

If this type of manual forward/reverse control is not required the associated components can be omitted during assembly (C4, C11, Q3, Q6, IC2, IC5, R9, R23, R10, R24). Pin 6 of sockets IC2 and 5 now becomes the FWD/REV logic control, the unused collector pad of Q3 and 6 becomes the control voltage input.


The ratio of R15 to R13 determines the gain of this input, and with the specified 1M $\Omega$  values is set at unity. Thus an input variation over a 3 V range will provide 0% to 100% duty-cycle control. The input should be referenced to the 0 V ground, and PR1 and 2 can provide full offset adjustment of the control ranges. To increase the gain, the value of R13 should be decreased.

## Testing

Once the manual potentiometers have been wired up in a suitable fashion the completed controller may be set up for proper operation. Temporarily disconnect the PWM signal wires and solder them to the adjacent ground terminals; this will prevent the power stages being damaged if there are any errors.

Connect a 12 V supply to the main controller; two glowing LEDs are the first signs of success! A voltmeter or scope set for 12 V FSD should now be hooked up to the FWD/REV output; depending on the pot position a 0 V or 12 V level will be present, and should sharply change state as the pot is turned through its centre travel. A ramp waveform of 3 V peak should be observed if a scope is put on pin 6 of IC3 or IC6. The PWM output can now be measured for each channel with the meter, indicating a voltage

# PROJECT : Robot Motor Control Part 3

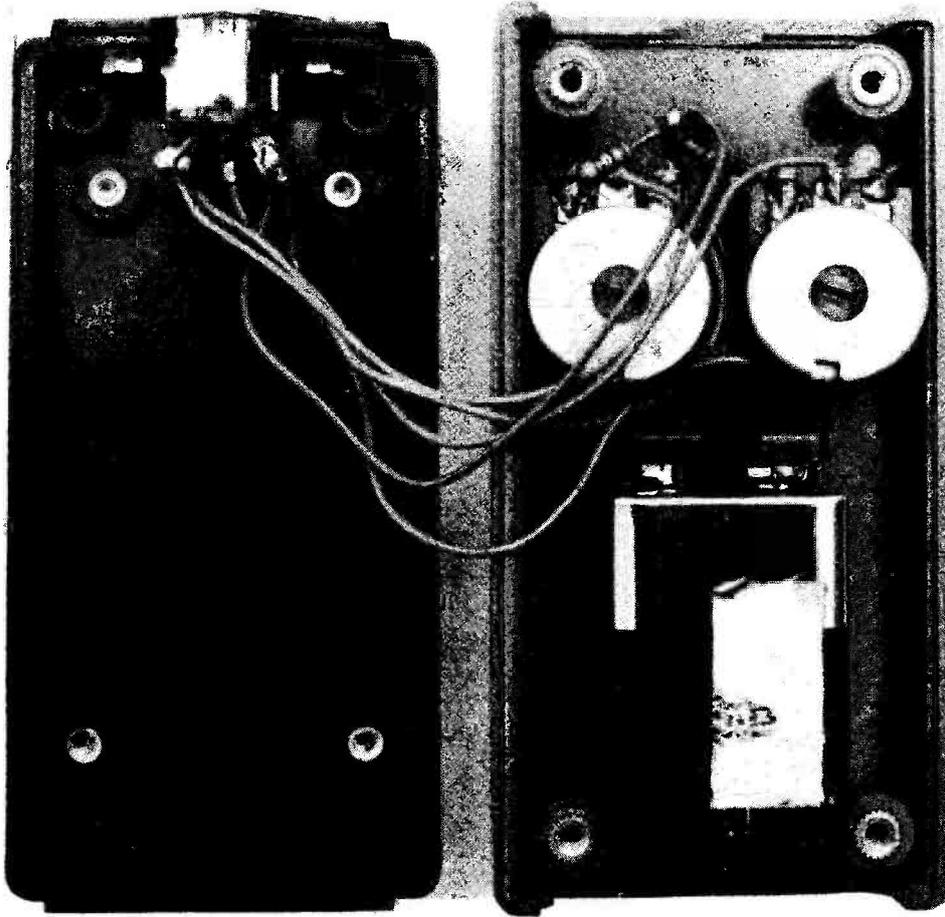

The manual control unit.

proportional to duty-cycle, or a scope to show the pulse waveform. For a given position of the control pot, clockwise adjustment of the corresponding preset will increase the duty cycle. Leaving the preset and now turning the manual pot towards centre travel will decrease the duty-cycle linearly until the pulse width vanishes, giving a dead band of 0 V. Turning the presets again, anticlockwise this time, will increase the deadband. A small proportion of the pot rotation should be left as deadband, so enabling the motor stop position to be easily located. Adjustment is more difficult with a meter than a scope, but with patience the desired setting can soon be achieved.

The PWM signal wires can now be reconnected to the outputs and the chosen motors wired across the power amplifier load terminals. A 20 A toggle switch wired in series with the positive battery supply is strongly recommended at this stage. (WARNING: If the motors used are rated at less than 6 V, the maximum obtainable duty-cycle should be limited accordingly by increasing the deadband; good motors are usually expensive.) A 12 V bulb will provide a good motor substitute for the purposes of testing. Each manual pot will now independently control the average power into any load; bidirectionally!

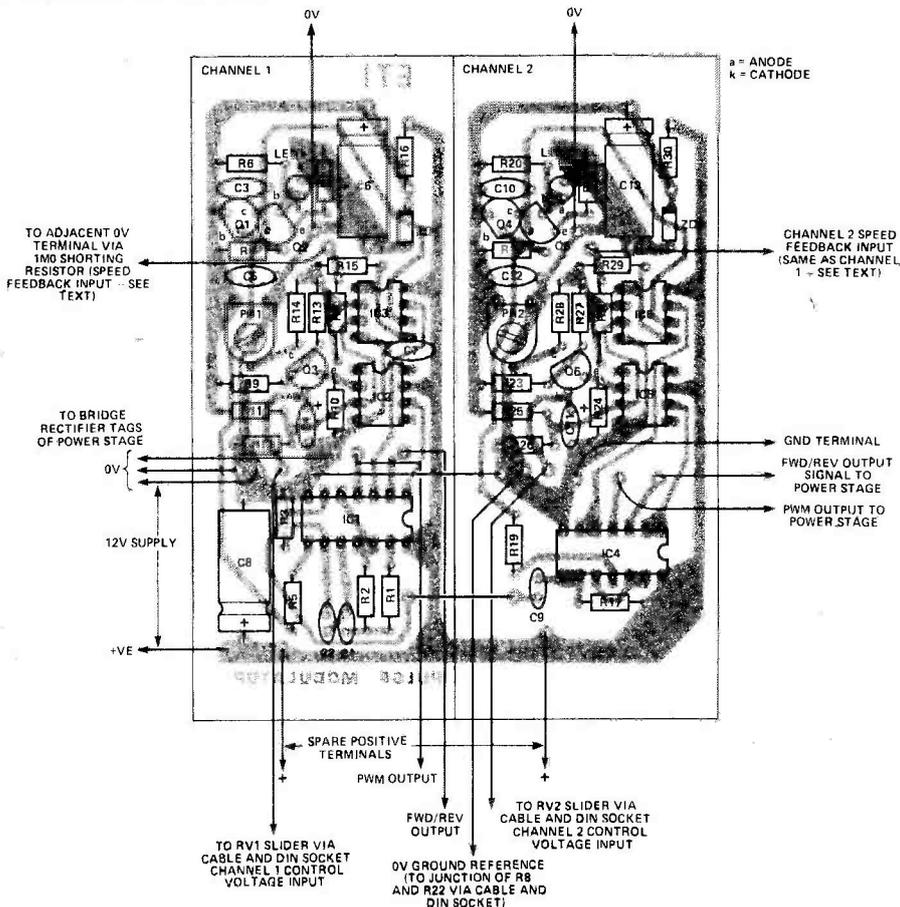


Fig. 2 Component overlay for the analogue PWM unit.

## PARTS LIST

### MANUAL CONTROL BOX

Resistors RA and RB; 1kΩ (¼ W, 5%) (see text)  
Case (see Buylines)  
5 pin DIN plug and socket  
PP3 9 V battery  
Twin core screened cable (length to suit remote operation)  
Two control knobs

## BUYLINES

You shouldn't have any supply problems with the components for this project — everything is absolutely standard. The case we used is a Vero type 65-2514F and should be available from any Vero stockist. We can supply the PCB — the order form is on page 45.

Coming next month: not only the digital PWM board for direct computer control of the motors, but an infra-red proximity detector too. We also begin to assemble the modules into a working mobile.

# LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Self assembly simulated wood cabinet. £4.50 + £1.50 p+p.

Featured in April issue Practical Electronics, reprint 50p - Free with Kit.

INTRODUCTORY OFFER - ONLY  
**£32<sup>95</sup>**  
+ £2.75 p&p.



## P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP ● TAPE COUNTER
- SWITCHABLE E.O.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

## STEREO AMPLIFIER KIT



- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/2" x 3 3/4" (approx).
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.


**£16-50**  
+ £2.90 p&p.

**SPECIFICATIONS:** Suitable for 4 to 8 ohm speakers  
40Hz - 20KHz  
P.U. 150mV. Aux. 200mV.  
Mic. 1.5mV.  
Bass ±12db @ 60Hz  
Treble ±12db @ 10KHz  
0.1% typically @ 8 watts  
220 - 250 volts 50Hz.

**8" SPEAKER KIT** Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p. when purchased with amplifier. Available separately £6.75 & £1.70 p+p.

## PRACTICAL ELECTRONICS

### CAR RADIO KIT SERIES II

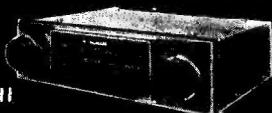

#### 2 WAVE BAND, MW - LW

• Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits. All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p&p. **£12-95** + £2.00 p&p.

### BIRDAUDIO STEREO CAR RADIO BOOSTER



To boost your car radio or radio cassette to 15W r.m.s. per channel.

**£9-95** + £1.50 p&p.

## 125W HIGH POWER AMP MODULE

KIT: **£10-50** BUILT: **£14-25**  
+ £1.15 p&p + £1.15 p&p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions. **ACCESSORIES:** Suitable mains power supply kit with transformer: £7.50 plus £3.15 p&p. Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



#### SPECIFICATIONS:

Max. output power (RMS): 125W.  
Operating voltage (DC): 50 - 80 max.  
Loads: 4 - 16 ohms.  
Frequency response measured @ 100 watts: 25Hz - 20KHz.  
Sensitivity for 100 watts: 400mV @ 47K.  
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.  
Dimensions: 205 x 90 and 190 x 36 mm.

## HI-FI SPEAKERS AT BARGAIN PRICES



#### GOODMANS TWEETERS

8 ohm soft dome radiator tweeter (3 1/4" sq.) for use in up to 40W systems; with 2 element crossover. **£3.50 each (p&p £1) or £5.95 pair (p&p £2).**

#### 35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIF11JSM. Complete with 2 element crossover. Total impedance of system 4 ohms.




**£7.95**  
PER SET + £2.70 p&p.

## P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System. **FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.


**£17-95**  
Plus £2.50 p&p.

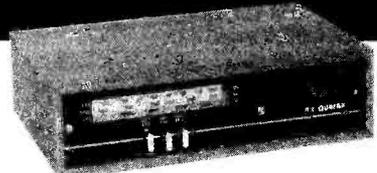Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4". **£3.50** Plus £1.50 p&p.



**SPECIAL OFFER! TUNER KIT PLUS:**  
• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider controls for bass, treble and volumes. **£21.95** + £3.80 P&P.

## TV SOUND TUNER KIT

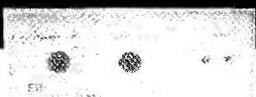

**£11-45**  
+ £1.50 p&p.

As featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. **£1.95 + 75p p&p.**

## MONO MIXER AMP



**£39-95**  
+ £3.70 p&p.

**50 WATT** Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/4" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

#### ALL MAIL TO:

21E HIGH STREET, ACTON, W3 6NG.  
Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All items subject to availability. Prices correct at 31/1/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch.

ALL PRICES INCLUDE VAT AT 15%.

ALL CALLERS TO: 323 Edgware Rd, London W2. Telephone: 01-723 8432. Open 9.30 - 5.30pm. Closed all day Thursday. RTVC Limited reserve the right to update their products without notice.



# MICRO TIMES

19 Mill St., Bideford,  
North Devon EX39 2JR, England  
Telephone: Bideford (023 72) 79798

VAT No. 321 1198 01

## CMOS

4001	13p
4002	13p
4006	65p
4007	18p
4008	60p
4011	14p
4012	18p
4013	33p
4014	60p
4015	60p
4016	24p
4017	50p
4018	58p
4019	36p
4020	60p
4022	74LS74
4024	38p
4025	16p
4026	£1.28
4027	32p
4028	60p
4029	70p
4030	48p
4031	£1.75
4040	58p
4042	55p
4044	60p
4046	70p
4047	75p
4048	44p
4049	27p
4050	28p
4051	65p
4052	88p
4056	£1.50
4060	86p
4063	£1.08
4066	36p
4068	18p
4069	17p
4070	20p
4071	22p
4075	20p
4077	28p
4078	24p
4081	18p
4093	40p
4503	65p
4510	50p
4511	50p
4518	60p
4520	70p
4560	£1.70
4572	30p

## 74LS TTL

74LS00	14p
74LS01	14p
74LS02	13p
74LS03	13p
74LS04	14p
74LS08	14p
74LS10	15p
74LS14	48p
74LS20	13p
74LS26	18p
74LS30	14p
74LS32	14p
74LS38	14p
74LS42	39p
74LS47	40p
74LS73	21p
74LS74	18p
74LS75	29p
74LS86	34p
74LS90	35p
74LS93	35p
74LS107	40p
74LS112	39p
74LS123	50p
74LS125	29p
74LS132	48p
74LS138	39p
74LS151	40p
74LS155	40p
74LS157	35p
74LS161	42p
74LS163	42p
74LS164	48p
74LS173	70p
74LS174	67p
74LS175	59p
74LS221	60p
74LS244	80p
74LS245	£1.20
74LS251	40p
74LS257	50p
74LS261	£1.90
74LS366	38p
74LS373	75p
74LS374	78p
74LS393	58p

## LINEAR IC's

NE555	16p
NE556	45p
RC4136	65p
LM301AN	25p
LM311P	60p
LM318	£1.45
LM324N	40p
LM339N	40p
LM348N	40p
LM358P	60p
LM380	65p
LM3302	85p
LM3900N	44p
LM3914	£2.00
LM3915	£2.00
LM13600	£1.20
LM1871	£1.90
LM1872	£1.90
SN76477N	£1.69
UA741	14p
UA747	58p
UA748	26p
TL074CN	£1.00
TL061CP	38p
TL082CP	35p
TL084CN	95p
TL490	£1.10
MC1488	59p
MC1489	59p
8728	£1.30
8728	£1.30
8735	£1.30

## TILs

TIL32	45p
TIL209 red	10p
TIL212 yell	16p
TIL216 red	18p
TIL220 red	12p
TIL224 yell	18p
TIL228 red	20p
TIL232 grn	18p
TIL311	£5.25
TIL312/3	£1.00
TIL321/A	£1.15
TIL330A	£1.15

## Z80 COMBO CHIP

MK3886 2 1/2 meg	£15.50
------------------	--------

## THYRISTORS

C106D	28p
-------	-----

## ELECTROWARE

We are distributors for all Electroware Products.  
Tools, Kits, Boards etc.  
Catalogue available. Please send 30p p.p.

## MEMORIES

2114 300ns.	£1.20
2114 450ns.	95p
TC5614P 450ns	£3.50
4k CMOS RAM (1k x 4)	
4116 150ns.	£1.25
4116 200ns	£1.00
HM6116 3 (2k x 8)	£7.95

## EPROMS

2708 450ns.	£2.30
2716 450ns.	£2.45
2732 Intel type	£3.85

## CPU's

6802	£4.95
6504	£6.20
6802	£5.70
6809	£15.00
8080A	£5.50
8085A	£5.50
Z80	£4.00
Z80A	£4.80

## SUPPORT DEVICES

6520	£3.10
6522	£5.00
6532	£7.70
6810	£1.35
6821	£1.70
6845	£10.50
6850	£1.70
6852	£2.45
8212	£1.50
8216	£1.50
8228	£3.80
8255	£3.80
Z80CTC	£4.00
Z80PIO	£4.00
Z80ACTC	£4.00
Z80APIO	£4.50
Z80DMA	£11.50
Z80ADMA	£14.00
Z80S10/0	£13.50
Z80S10/1	£13.50
Z80S10/2	£13.50
Z80S10/2	£14.50

## INTERISL ICL76600

Voltage Converter	£2.25
-------------------	-------

## AY-3-8910 £5.95

GI SOUND COMPUTER CHIP  
Data £1.  
(Large SAE please 15 p.p.)

## SN76477N £1.69

SOUND EFFECTS GENERATOR  
Data available 75p  
(Large SAE please 28 p.p.)

## VEROBLOC SOLDERLESS BREADBOARD

360 reliable contacts. Will accommodate any size IC. Can be fully interlocked one with another £3.85 each  
VERO  
S100 Prototyping Boards:  
Microboard Pattern 06 2175L £17.95  
Square Pad, Universal Pattern £17.95  
Prototyping Board for Apple IIT 2020 £9.15  
Other Vero Products available on request.

## SUPER STEREO DRUM KIT \*\*\*\*\*

\* 6 Rhythms, each with 3 sub-rhythm options.  
\* 5 Instruments: Snare, Hi-Hat, Tom-Tom, Cymbal, Bass Drum.  
\* Board 4" x 5" Packed with components.  
\* Kit includes rhythm selection switch and tempo control.  
Price: Kit £23.95  
Assembled & Tested (excl. case) £30.00

## LOW NOISE EQUALIZER MODULE KIT

Board size 1.3" x 1.1"  
Treble and Bass. + 15dB at 10kHz and 50Hz.  
Price: £4.95 for Kit.  
Assembled and Tested £8.00

## LOW PROFILE DIL SOCKETS

6 pin	8p
14 pin	10p
16 pin	11p
18 pin	15p
22 pin	20p
24 pin	22p
28 pin	26p
40 pin	29p

## ANTEX SOLDERING IRONS

Model CX 17W	£4.80
Kit SK1 15W	£6.50
incl. Base, stand, solder.	
Kit SK3 17W	£8.50
Kit SK4 25W	£8.50
MLX Repair Kit	£5.30
Spare Bits (each)	60p

## KITS FOR BEGINNERS

Electronic Wheel of Fortune £5.00  
Ultrasonic Fly Repeller £4.50  
Light Activated Switch £3.75

## VOLTAGE REGULATORS

7805 5V	39p
7812 12V	39p
7805 5V	55p
7812 12V	55p
100mA	
78L05 5V	29p
78L12 12V	29p
79M05 5V	60p
79M12 12V	60p
723	31p

## FLOPPY DISC CONTROLLERS

FD1771B-01	£17.95
FD1791-2	£32.00
WD1691D	£11.70
WD2143-01	£5.00
FD1791-2, WD1691D, WD2143-01	£48.00

Sold as complete package £48.00  
Data available £3.00 plus 50p P.P.P.

## 6809 SINGLE BOARD COMPUTER KIT IEEE S-100 STANDARD

Complete Kit £175  
15% VAT + £2.00 P.P.P.  
Please allow 21 days delivery  
BARE BOARD £48.00  
Uses 6809, 6850, 6821  
ADSMON (2716) £28.00  
Data available on 6809SBC  
Stamped addressed envelope please.

## S-100 KLUGE CARD

Simplify your project with a prototype Breadboard with extras!  
BARE BOARD £33.00  
with MANUAL  
Please allow 21 days delivery.

## S-100 PROM BLASTER

PROGRAMMES MOST FAMILIES OF EPROMS!  
\* Accepts 1K/2K/4K or 8K EPROMs.  
\* Extended Device Option.  
\* Phantom Slave Option.  
\* All Programming characteristics Software Controlled!  
\* Accepts Single or 3 Supply Parts.  
\* Device Address Switch Selectable.  
\* On-Board Wait States.  
Put your frequently used routines into EPROM!  
BARE BOARD £48.00  
PROMWRITER £40.00  
KIT £175.00  
incl. All Parts, Sockets & Promwriter.  
Delivery 21 days. P.P.P. £2.00 plus VAT.  
PROMWRITER provides complete software to Program most families of Eprom.  
2 Versions available.  
Promwriter 1. in 2716 runs under Adsmn with our 6809 S.B.C.  
Promwriter 2. on diskette, suitable for 8080/Z80 type system running C/P.M.  
Please specify which you require.

## ORDERING INFORMATION


Please add 50p P.P.P. plus 15% VAT to all orders.  
EXPORT ORDERS WELCOME.  
Add 15% P.P.P. VAT not applicable.  
Excellent delivery service.



ACCESS/BARCLAYCARD orders welcome.  
Schools, Univ., Official orders welcome.  
All items Brand New. Full Spec.
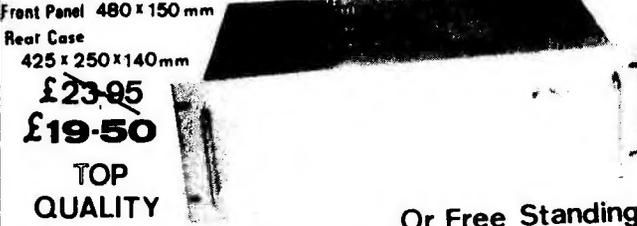
## RELAY-A-QUIP 19 RACK MOUNTING CASE

\* Top, bottom and rear cover removable for access \* Plates have heavy duty grey paint finish \* Front panel is heavy gauge - 3mm aluminium \* Strong, screwed, construction throughout - screws included \* Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from \* Front panel is of brushed aluminium finish enhanced with heavy chromed handles \*




Front Panel 480 x 150 mm  
Rear Case 425 x 250 x 140 mm  
£23.95  
£19.50  
TOP QUALITY  
Or Free Standing

a - 150(d) x 90(h) x 50(w)mm	high impact styrene
b - 198(d) x 113(h) x 60(w)mm	Z-BOX
c - 130(d) x 68(h) x 41(w)mm	natural aluminium lid
d - 83(d) x 54(h) x 28(w)mm	

A -	£1.55
B -	£2.05
C -	£1.10
D -	£0.80

FREE!  
NEW CATALOGUE

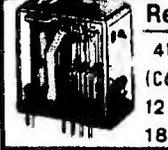ADD VAT at sfd rate %  
Order value under £5.00  
Add 50p. P and Pkg




**SPECIAL OFFER**  
Relay+Base £2.95  
Two for £5.00  
Contact details:  
5amp at 28 VDC/115 VAC

## METAL CABINETS

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife!), louvre for ventilation and finished in an attractive two tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.


A	£1.70	£2.22
B	£2.55	£3.20
C	£3.04	£3.80
D	£4.08	£5.00

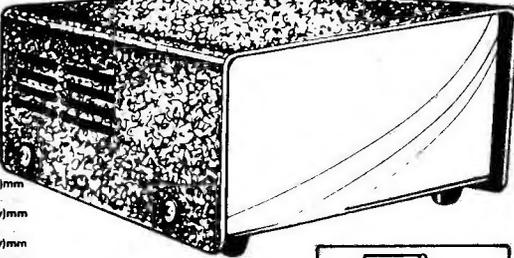

a -	102(d) x 56(h) x 83(w)mm
b -	150(d) x 61(h) x 103(w)mm
c -	150(d) x 76(h) x 134(w)mm
d -	184(d) x 70(h) x 160(w)mm

RELAY-A-QUIP

## POWERSINK

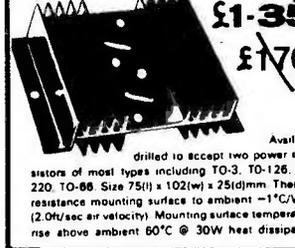

£1.35  
£1.70  
drilled to accept two power transistors of most types including TO-3, TO-18, TO-220, TO-99. Size 75(l) x 102(w) x 25(d)mm. Thermal resistance mounting surface to ambient -1°C/Watt (2.0ft/sec air velocity). Mounting surface temperature rise above ambient 60°C @ 30W heat dissipation

## Bridge Rectifier 1amp 50v WD.005 - 16-5p

1P2T	£0.10	4P4T PCB	0.45
2P2T	0.12	6P3T ALI KNOB	0.45
2P3T	0.19	1P2T Mom	0.20
4P2T PCB	0.28	ROCKER 6amp	
4P3T	0.35	250VAC	
2P2T	0.12	ON/OFF	0.24
1P4T	0.26	ON/ON	0.26
6P3T	0.42		

EXPORTS & TRADE ENQUIRIES ARE WELCOME.  
TELEX 995901 GLOTLX-G  
Quote ref R7

3amp TOGGLE mini	
250VAC ON/NONE/ON	0.85
250VAC ON/OFF/ON	0.88

## DIODES

1N4148	- 2p
1N4001	- 3p
1N4002	- 3 1/2p
1N4003	- 4 1/2p
1N4004	- 5p

## SEIKO 30w Soldering Iron £2.95

RELAY-A-QUIP PRODUCTS  
Moat Lodge, Stock Chase,  
Maldon, Essex, U.K. CM9 7AA.  
Tel 0621-57242 & 58686 (24hour)

# THE POWERFET AMPLIFIER



**PFA 80**  
(100W plus into 8Ω)

### Elegant Simplicity

Advances in high technology should make life simpler. A cluttered power amplifier board may well perform superbly but its busy elaboration is an indication that its design is pushing the limit of its component technology.

There are now many first class bipolar power amps on the market. All of them are complex and consequently expensive. Any additional improvements in the areas where they are weak (e.g. H.F. distortion) can only be obtained with yet further complexity and cost.

Only a new technology can provide the sort of quantum jump in component performance necessary to reduce the clutter on the board, reduce the cost and make the highest frequency more affordable.

### Powerfets

So far 29 semiconductor manufacturers have invested in this new technology. Clearly powerfets are something special.

Their enormous power gains eliminate conventional drive circuitry in power amps, permitting delightfully simple designs. Their freedom from secondary breakdown and their tendency to shutdown when thermally overstressed, result in inherently stable and destruction proof output stages, not needing protection circuitry. And perhaps best of all, their lack of charge storage makes them fast and responsive, producing amplifiers of wide bandwidth and low distortion even at high frequencies.



**Power Supply Components available**

**PFA 120**  
(150W plus into 8Ω)  
300W INTO 4Ω!



The PFA is perhaps the perfect realisation of the classic powerfet amp design. The superb PCB allows the use of either one or two pairs of output devices, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads).

The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

Specification	PFA80	PFA120
Bandwidth	10Hz	100KHz 1dB
Output Power	80W (Vs = ± 50V)	120W (Vs = ± 55V)
R.M.S into 8Ω		
THD (20Hz-20KHz) (KHz at rated output)	≤ 0.008	≤ 0.005
SNR	170dB	
Slew Rate	> 20V/μs	
Gain	X22	
Rin	30K	
Vs max	± 70V	

Cost	PFA80	PFA120	P. & P. 75p
(Board)	£17.45	£24.85	
(Kit)	£14.95	£21.85	

### Power Amp PAN 1397

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation, providing high powers from low supply voltages.

### Specification

Output power RMS	20W into 8Ω at ± 22V
	20W into 4Ω at ± 19V
THD	0.02% at 1KHz 1W to 12W
SNR	90dB
Input	100mV into 50K
Cost (Board)	£5.80 (P. & P. 40p)

**PAN 1397**



**PSU 101**



**PSU 101 Power Supply Board for 1 or 2 PAN 1397s. Provides ±22V at 3A AND ± 27V with 2 second run-up (for anti-thump circuit on PAN 1397). (Board) £3.95. P/P 75p**

Mains transformer for above 17 0 17v 50VA £3.95 (P. & P. £1)

### Pre-amp PAN 20

The design is unique Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain attenuator control (volume control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag. PLIs and space on the board is available for different equalisations.

### Specification

B.W	20Hz-30KHz ± 1dB
THD	0.003% typ.
at rated o.p.	
SNR	85 dB (ref. 5mV RIAA)
	105 dB (ref. 100mV flat)
Vs	± 20V
Output	1V (clips at ± 20dB)
Cost	£6.75 2 needed for stereo (P. & P. 40p)
(Board)	
(less controls)	

## THE POWERFET SPECIALISTS

# pantechnic

(incorporating J.W. Rimmer)

Mail order only to:

Dept ET1/5, 148 Quarry Street, Liverpool L25 6HQ.

Telephone: 051 428 8485

Technical enquiries:

367 Green Lanes, London N4 1DY. Tel. 01 800 6667

# CAMBRIDGE LEARNING

## SELF-INSTRUCTION COURSES

# A PRACTICAL DIGITAL ELECTRONIC KIT FOR

## ★ LESS THAN £20 ★



## SUITABLE FOR BEGINNERS

## NO SOLDERING!

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

seven LS TTL integrated circuits, breadboard, LEDs, and all the

DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19-90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits.

This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

It is supported by our theory course

**DIGITAL COMPUTER LOGIC AND ELECTRONICS** ~~£8.50~~ £6.00 for beginners, and our latest, more advanced text,

**DIGITAL DESIGN** £7.00

Please send for full details (see coupon below).

**GUARANTEE** No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

**CAMBRIDGE LEARNING LIMITED, UNIT 15 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND. TELEPHONE: ST IVES (0480) 67446. VAT No 313026022**

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK

Please send me:

.....SUPERKIT(S) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a \*cheque/PO payable to Cambridge Learning Ltd for £..... (\*delete where applicable)

Please charge my:

\*Access / American Express / Barclaycard / Diners Club Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No .....

Signature.....

Telephone orders from card holders accepted on 0480 67446 Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.




Name.....

Address.....

Cambridge Learning Limited, Unit 15 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).
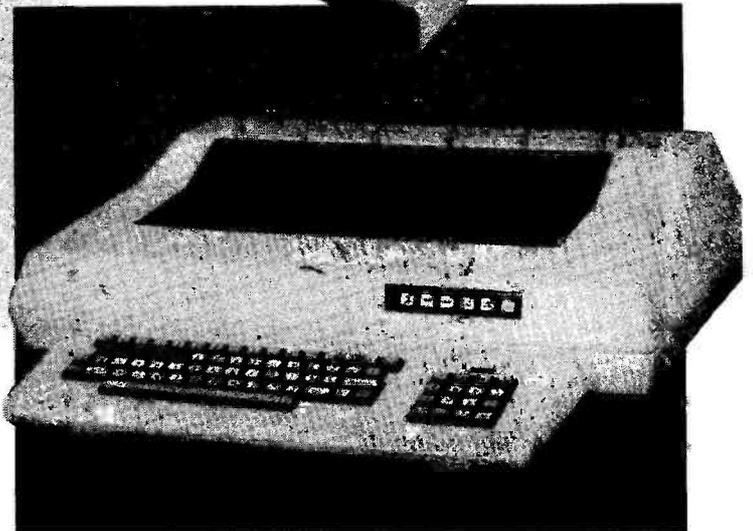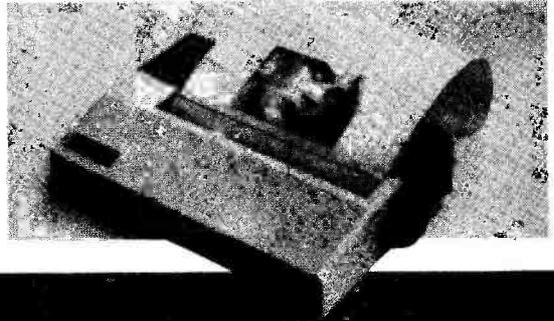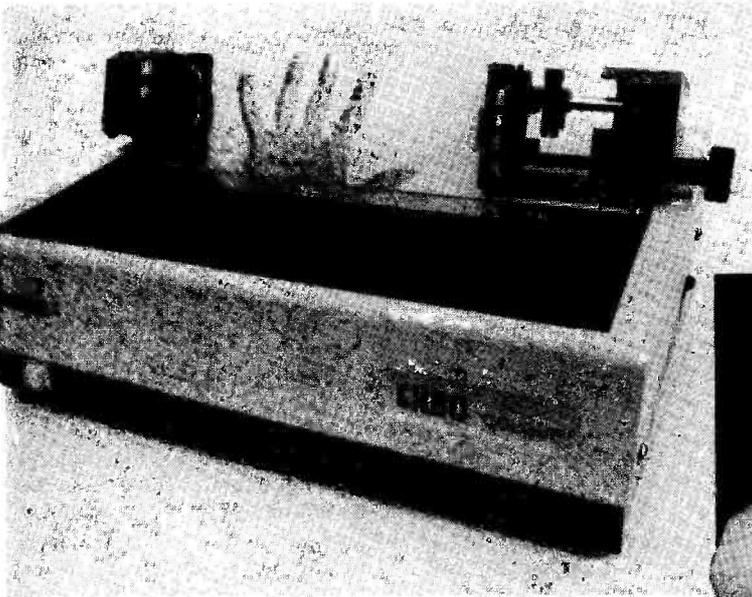
# ENGINEER'S GUIDE TO PRINTERS

Whether you type LPRINT or OPEN 1, 4, not much is going to happen unless you've got a printer hanging off the back of the computer. Robert Traub helps you decide which one is right for you.



Printers vary greatly in their functions and features. There are a great number of types to choose from and the choice can be almost impossible. Some very basic points about printers may assist in the selection of a printer for personal use.

The first point to cover is columns. What is a column? Some printers will print 132 columns, some only 40 columns and some just about everything in between and more. A column is the space occupied by a single character. Consider first printers with fixed pitch. Fixed pitch means that each character occupies the same amount of space on the page. The common fixed pitch is 10 characters per inch; this standard pitch would allow 85 columns across an 8½ inch wide paper if no room is allowed for margins.

If the page were allowed to have margins of approximately ½ inch on each side, that would leave 7.2 inches. At 10 characters per inch, that would give us 72 columns, and this is the standard print page for TTY type printers (and others). If the printer were to offer 132 columns, then the paper would have to be at least 10 characters per inch divided into 132 columns equals 13.2 inches wide. If margins were to be included it would bring the width of the paper to 15 ½ inch. Therefore a common 132 column page would be 15 ½ inches wide by 11 inches deep.

Some fixed pitch printers offer the ability to select the pitch at which the characters will be fixed. Some common values are 12 characters per inch and 13.5 characters per inch. A bit of math would soon tell us that a printer with a fixed pitch of 13.5 characters per inch could print up to 96 characters or columns on a standard page with margins, while a printer with a fixed pitch of 12 characters per inch could print 87 columns in the same space. The 13.5 character per inch printers compress the

characters much closer together and may be a bit harder to read if they don't use a good quality print head. Some dot matrix printers offer a very compressed print of 132 columns in eight inches or 16.5 characters to the inch.

Next we will look at printers that are not fixed pitch. A few printers offer the ability to allow a given amount of space on the line to each character. With this type of printer, less space would be allowed for the letter "i" than would be allowed for letters such as "m" or "w". Each letter is assigned a given amount of space on the line, as well as the distance between each letter. (With fixed pitch printers the amount of space allotted is the same for all characters.) This type of print is referred to as proportional spaced print.

With this type of print you can develop excellent quality documents and avoid the common "river of white" that is found running through the body of text done with fixed pitch printers. Proportional spaced printers are the type required for professional word processing systems; the quality of print is excellent, and the overall appearance of the documents produced on the system is outstanding. These types of printers are very expensive, and very elaborate software is required for their operation in order to exploit their full potential.

Before leaving this subject, there are a couple of terms that you may run across and not be sure of their meaning, these being *pica* and *elite*. The term *pica* refers to typewriter type providing 10 characters to the inch, while *elite* is typewriter type that provides 12 characters to the inch.


### Type Of Type

The next thing to consider is the type of print. One common type is dot matrix print. This type of printer comes in many dot matrix forms; some may be 5 by 7, some 7 by 9, some 9 by 9, and some even greater. The dot matrix is comprised of a number of small wires or pins that are struck against a ribbon and the paper leaving a dot on the paper. The number of dots that the matrix has will determine the fullness of the character that it is reproducing. A 5 x 7 dot matrix is comprised of 35 small dot positions arranged in such a manner as to have a total of five dots across (horizontal) and seven vertical rows of five dots each. This arrangement is the minimum number of dots required to produce a decent upper case letter set and numerals. The characters are not always well formed as can be seen by the "S" not being curled around at the top and bottom, and by such characters as the slash (/). The slash will have a small vertical line on both ends rather than being a single straight line.

A 7 x 9 dot matrix is arranged in such a manner as to have seven dots across (horizontal) and nine vertical rows of seven dots each for a total of 63 dots. This type of matrix will produce much better letters, and give a more natural look to the overall print. As the number of dots in the matrix increases, the ability to reproduce characters increases and some very nice natural-looking print can be found with such printers. Of course, if graphics are being considered, the greater the matrix dot count, the better the quality of graphic representation. Better quality print will be produced by matrixes with greater numbers.

The least expensive of the dot matrix printers will generally have a standard 5 by 7 matrix print head. This printer is satisfactory for general use, but is not intended for word processing as it does not have descenders. A descender is the tail of lower case characters such as 'p', 'q', 'j', 'y', etc. Note that the tail of these characters will extend below the base line on a normal typewriter quality printer. On dot matrix printers this is not always available, and never on a 5 x 7 dot matrix. As the number of dots in the matrix increases, so does the price and overall general quality of the printer. The very elaborate dot matrix printers that are now available can rival almost any type of print, but are very expensive and therefore not generally appropriate for hobby applications.

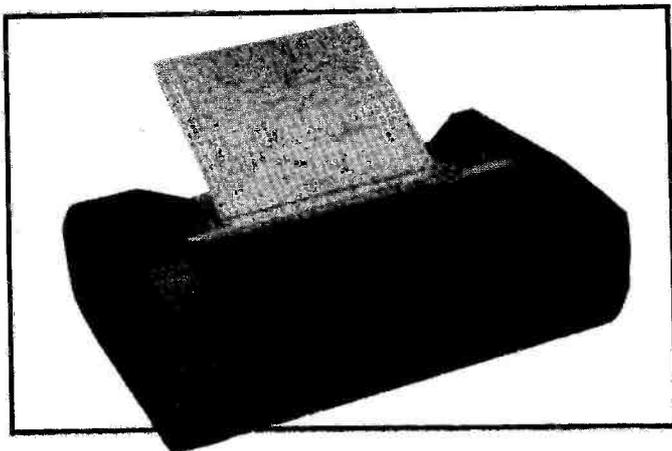Printers that offer fully-formed characters such as found on typewriters are the best quality for word processing at a more reasonable cost. Fully formed characters are the type found in typewriters and are cast in metal or plastic. Some systems have the characters formed on a ball, some have them formed on a cylinder and others use a daisy wheel, to name but a few methods.




The daisy wheel comes in different sizes with 88, 92 or 96 characters per wheel and can be cast in either plastic or metal. Some of the cheaper printers, whether dot matrix or full formed character type, do not offer lower case characters; again, this may or may not be important to the user, although lower case is a must if word processing is being considered. Each printer must be studied in order to determine if it offers lower case characters, descenders and other features (graphics) that would be of interest to the user.

### Feed For Thought

This brings us to the question of friction feed or tractor feed. In the case of friction feed, the paper is held in place by some small pinch rollers that press against the printer's platen. The paper is inserted between these pinch rollers and the platen. This is fine in most cases where each line is advanced one at a time by a carriage return-line feed combination, but if the lines were to be advanced by the inch with a sudden command, as is the case with the form feed character, the paper could 'slip' as the platen first starts its fast advance. To overcome this problem, the tractor feed type of paper advance systems can be used. With this type of printer option, paper can be advanced rapidly with assurance that the print will start at the same line on each page or form.

One other type of paper feed system is the pin feed; this system is used on TTY printers to ensure that forms such as telegraphs will always line up properly. Another feature offered by the tractor feed and pin feed systems is the assurance that the printed line is horizontal with respect to the top and bottom edge of the paper. With friction feed systems, the page can slip slightly one way or the other.

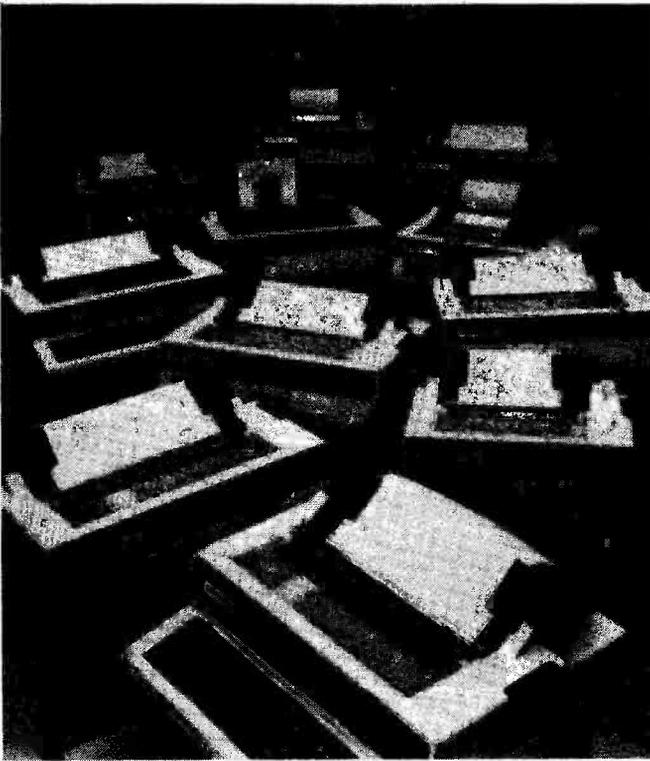As there are different systems that can be used to feed paper, the choice will depend on the type of work the printer will be required to do. If a lot of forms are going to be filled out, then of course a printer with the tractor feed option would be a good choice. If individual letters are the order of the day, then the standard friction feed type of paper advance will serve well.



### BAUDy Stories



Briefly we will take a look at the question of baud rates. The baud rate or just plain baud means number of code elements per second. If the ASCII code were taken as a 10 unit code, then a baud rate of 1200 baud would transfer data at the rate of 1200 elements per second divided by 10 units per character for 120 characters per second. If the ASCII code were to be considered as an eight unit code, then 1200 baud would represent a rate of 1200 elements per second divided by eight units per character for total of 150 characters per second. Many printers will accept data at a rather high baud rate, say 9600 baud; this is the rate at which they accept data into their buffers and not the rate at which they print. The printer may only be able to produce 150 characters per second on paper; therefore, that printer's true baud rate is 1200 baud if an eight unit ASCII code is assumed. The baud rate then is the speed at which the data or information can be printed.

There are many reasons why a faster speed is needed in some cases and not at all needed in other cases. Typical baud rates range from a slow 110 baud to a fast 9600 baud, but be sure to check if the baud rate is the rate that the printer will print characters or if it is the rate at which the host computer can send characters to its internal storage area (buffer).
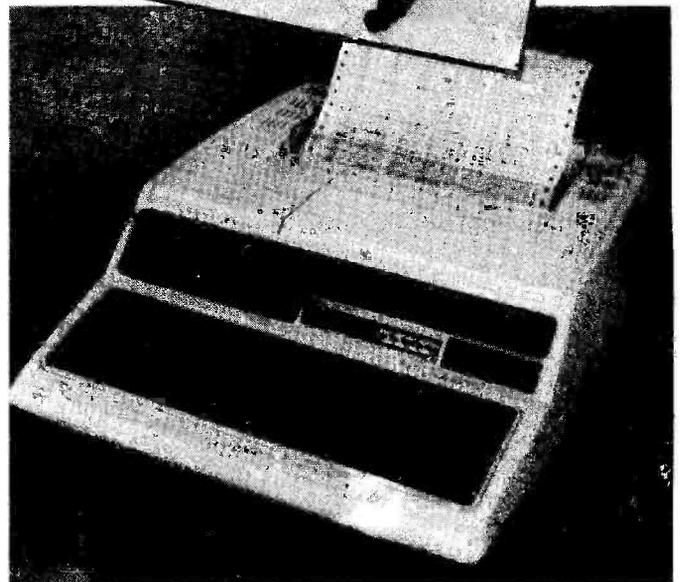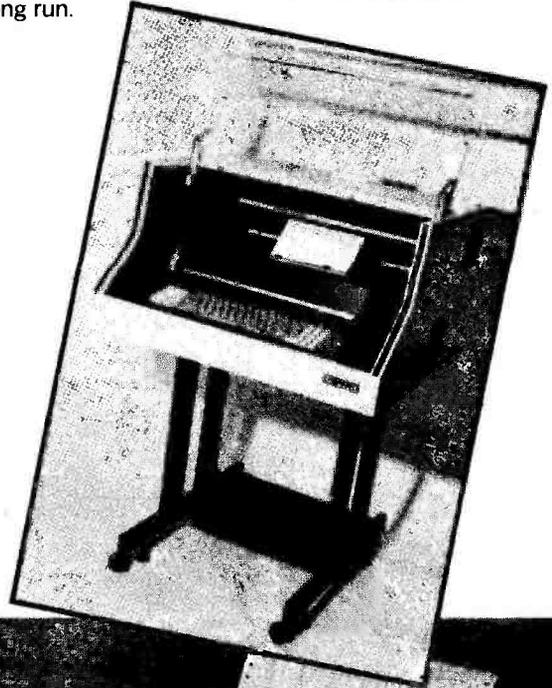
### Drop Me A Line

Some printers you hear about are called *line printers*; a line printer is a special type of printer that will not print each character as it is received, but rather will wait for the complete line and then print the entire line at once, a character at a time. The length of the line that it prints is determined by the sending of the RETURN character, as a return signifies the end of that line in text. Line printers require special handling by the host computer and provisions must be made for *handshaking*. Line printers have buffers to store the data in before it is printed and handshaking is simply the printer's method of telling the computer when to send more data to the buffer and when to stop sending data as it cannot handle any more at the moment. Printers are generally slower than the host computer, although there are some very fast printers not generally used by the hobbyist.

One other thing that you might run across is the term *bi-directional* printer. What this means is that the print head will print a line from left to right across the paper, advance the line (line feed) and then print the next line from the right side back to the left. The *bi-directional* printer requires fewer mechanical parts and movements than single direction types and this is one reason for increased printer speeds. With the conventional type of printers, a carriage return is required in order to bring the print head back to the start of the next line. This takes time and computers have to send the printer a *pad* or *fill* character in order to assure that the head has returned to the far left before it starts printing again. After many, many line feeds and carriage returns the amount of time wasted can be considerable. Therefore the *bi-directional* printer, which does not return the head every line, is capable of greater speeds (throughout). Because there are fewer mechanical parts to wear out, reliability is also increased in the long run.



### Summary

At this point there are a few things to consider. If the printer is going to be used for listing BASIC or assembly programs, the dot matrix type of printer or the teletype printer may do the job very well. If a teletype printer is used, you will have upper case only, a slower 110 baud rate and require a 20 mA loop interface. Printers of the dot matrix type vary by a great amount and will require either a parallel or RS232 serial interface.


The lower priced 5 x 7 dot matrix printers have a great deal to offer those wishing listings. They can be found in a variety of speeds ranging from 110 baud to 9600 baud, and vary greatly as to the size of paper that they can accommodate. If you require listings at 10 characters per inch on an 11 x 8.5 sheet of paper (11 inches horizontal and 8.5 inches vertical), you may find that the printer will not accommodate this size of paper and, in fact, the largest that it can handle is 9.5 inches horizontal.

If the printer cannot handle wide paper, check out the print quality of the printer at its most compressed setting, 13.5 characters per inch for instance, and use a very complex BASIC program line with as many characters and commands as possible. This will allow you to see first hand the type of printout you will be trying to work with. You may find it unsatisfactory for long listings, as the heavily compressed text makes it very hard to find semi-colons and other required BASIC syntax characters. If you will be doing a lot of amortization charts, or charts of any type, then it is recommended that you look at a printer that falls into the line printer category, as the speed will be needed. You would soon go broke trying to produce amortization charts at 110 or even 300 baud.

There are as many reasons for getting a printer as there are printers on the market; it is advised that the first thing you do when thinking about getting a printer is sit down in your computer room and try to determine exactly what service you want that printer for, and then proceed to find one that will do those limited number of things. You can never be sure that you have covered all the bases, so be sure to explain to the dealer what use you wish to put the printer to, and he will be in a position to advise you as to what you might need that you have overlooked. Try to stay away from a printer that will do everything; they require special features and will do all the different things if you buy a lot of extras, for example.


Some printers offer tractor feed as an option; this may be a valuable option to have, as trying to stop the printer at the right time to change paper for the next page is not always desirable. Check your computer program and see if you can stop the printer from the terminal keyboard at any given time, or if the software will do that automatically. If not, you will need tractor feed and continuous form paper for the job you are doing or roll paper if friction feed. If the printer is to be used for word processing, even on a small scale, it is recommended that you have lower case with descenders at the very least. Speed is not important in this type of printer and print rates of 30 to 55 characters per second are common. What is important is the quality of print and that is what you should look at first and last.

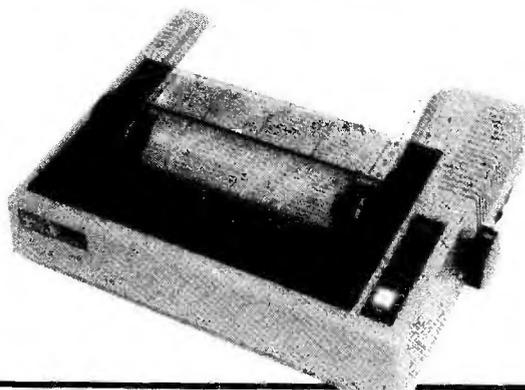There are other things to consider in purchase of a printer, such as whether a warranty or service contract is available. Second-hand equipment often does not come with service contracts. The application the printer will be used for will largely determine the quality of print required, but the cost could be the main consideration for the hobbyist.



ETI

## Guess who builds this great

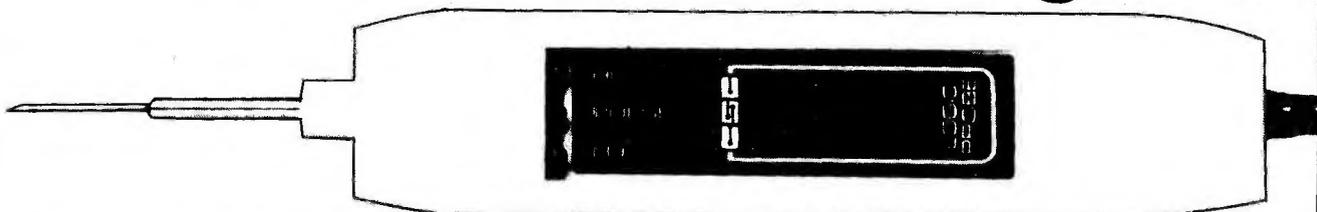

## Logic Probe...YOU! for only £12.50


With this easy-to-build Logic Probe Kit from GSC and just a few hours of easy assembly — thanks to our very descriptive step-by-step manual — you have a full performance logic probe.

With it, the logic level in a digital circuit is indicated by light from the Hi or Lo LED; pulses as narrow as 300 nanoseconds are stretched into blinks of the Pulse LED, triggered from either leading edge. You'll be able to probe deeper into logic with the LPK-1, one of the better tools from GSC.



Complete, easy-to-follow instructions help make this a one-night project.

### GLOBAL SPECIALTIES CORPORATION

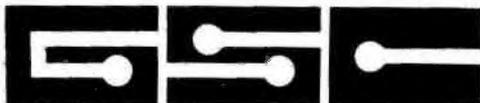

**G.S.C. (UK) Limited, Dept. 9Z**  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex. CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477.

GLOBAL SPECIALTIES CORPORATION, DEPT 9Z  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name \_\_\_\_\_

Address \_\_\_\_\_

Inc P&P and 15% VAT

**LPK-1 £15.52**

I enclose cheque

PO for £ \_\_\_\_\_

FREE Catalogue

tick box

Phone your order with Access, Barclaycard  
or American Express

Card No. \_\_\_\_\_

Expiry date \_\_\_\_\_

# NICADS: UK's LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW -

Available at your newsagent or direct, for 70p inc.

Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 £1 discount vouchers. In a recent supplier survey, we were one of only two suppliers listed in all categories!

There's a few examples of some super low prices

78XX 1A 37p

BC237/8/9 8p

3SK51 54p

10MHz XTALS

£2

8 Pole 10.7MHz XTAL

filters £14.50

2GHz coax relay

150W £10.95

All the "usual" stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micrometals toroids, Fairrite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.

CAPACITY	TYPE	1-9	10-49
500 mAh	AA	80	74
2200 mAh	C	2.35	1.99
1200 mAh	D	2.14	2.06
4000 mAh	D	3.05	2.85
110 mAh	PP3	3.70	3.50

Price on the page

CMOS		TTL		N	
4000	0.11	4514	1.25	7406N	0.22
4001	0.11	4515	1.25	7407N	0.22
4002	0.12	4516	0.60	7408N	0.15
4007	0.13	4518	0.35	7409N	0.15
4008	0.50	4520	0.60	7410N	0.12
4008AE	0.80	4521	1.30	7411N	0.18
4009	0.25	4522	0.89	7412N	0.19
4010	0.30	4527	0.80	7413N	0.27
4011AE	0.24	4528	0.85	7414N	0.51
4011	0.11	4529	0.70	7416N	0.27
4013	0.25	4531	0.85	7417N	0.27
4015	0.50	4532	0.80	7420N	0.13
4016	0.22	4534	4.00	7421N	0.28
4017	0.40	4536	2.50	7423N	0.22
4019	0.38	4538	0.85	7425N	0.22
4020	0.55	4539	0.80	7426N	0.22
4021	0.55	4543	0.80	7427N	0.22
4022	0.55	4549	3.50	7430N	0.12
4023	0.15	4553	2.70	7432N	0.23
4024	0.33	4554	1.20	7437N	0.22
4025	0.15	4555	0.35	7438N	0.22
4026	1.05	4556	0.40	7440N	0.14
4027	0.26	4557	2.30	7441N	0.54
4028	0.50	4558	0.80	7442N	0.42
4029	0.55	4559	3.50	7443N	0.62
4030	0.35	4560	2.50	7444N	0.62
4035	0.67	4561	1.00	7445N	0.62
4040	0.50	4562	2.50	7446N	0.62
4042	0.50	4566	1.20	7447N	0.62
4043	0.50	4568	1.45	7448N	0.56
4043AE	0.93	4569	1.70	7450	0.14
4044	0.60	4572	0.22	7451N	0.14
4046	0.60	4580	3.25	7453N	0.14
4047	0.68	4581	1.40	7454N	0.14
4049	0.24	4582	0.70	7460N	0.14
4050	0.24	4583	0.80	7470N	0.28
4051	0.55	4584	0.27	7472N	0.27
4052	0.55	4585	0.45	7473N	0.28
4053	0.55	4702	4.50	7474N	0.28
4054	1.30	4703	4.48	7475N	0.35
4055	1.30	4704	4.24	7476N	0.30
4056	1.30	4705	4.24	7480N	0.26
4059	5.75	4706	4.50	7481N	0.20
4060	0.75	4720	4.00	7482N	0.75
4063	1.15	4723	0.95	7485N	0.75
4066	0.30	4724	0.95	7486N	0.24
4067	4.30	4725	2.24	7489N	1.05
4068	1.16	40014	0.54	7490N	0.30
4068AE	0.14	40085	0.99	7491N	0.55
4070	0.16	40098	0.54	7492N	0.35
4071	0.16	40106	0.69	7493N	0.35
4072	0.16	40160	1.05	7494N	0.70
4073	0.16	40161	1.05	7495N	0.60
4075	0.16	40162	1.05	7496N	0.45
4076	0.55	40163	1.05	7497N	1.40
4077	0.18	40174	1.05	74100	1.10
4078	0.18	40175	1.05	74104	0.62
4081	0.12	40192	1.08	74105	0.62
4082	0.18	40193	1.08	74107	0.26
4093	0.30	40194	1.08	74109N	0.35
4099	0.80	40195	1.08	74110N	0.54
4175	0.80			74111N	0.68
4502	0.60			74112N	1.70
4503	0.50			74116N	1.98
4506	0.70	7400N	0.10	74118N	0.85
4507	0.37	7431N	0.10	74119N	1.20
4508	1.50	7402N	0.20	74120N	0.95
4510	0.55	7403N	0.11	74121N	0.34
4511	0.45	7404N	0.12	74122N	0.34
4512	0.55	7405N	0.12	74123N	0.40

70p  
3 x £1 Vouchers Inside

Prices shown EXCLUDE VAT. Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO. **POSTAGE and PACKING 50p per order**

74125N	0.40
74126N	0.40
74128N	0.65
74132N	0.50
74136N	0.65
74141N	0.45
74142N	1.85
74143N	2.50
74144N	2.50
74145N	0.75
74147N	1.50
74148N	1.09
74150N	0.79
74151N	0.55

74153N	0.55
74154N	0.55
74155N	0.55
74156N	0.55
74157N	0.55
74159N	1.90
74160N	0.55
74161N	0.55
74162N	0.55
74163N	0.55
74164N	0.55
74165N	0.55
74166N	0.75
74167N	1.25

74170N	1.25
74173N	1.10
74174N	0.75
74175N	0.75
74176N	0.75
74177N	0.75
74178N	0.90
74179N	1.35
74180N	0.75
74181N	1.22
74182N	0.70
74184N	1.20
74185N	1.20
74188N	3.00

74190N	0.55
74191N	0.55
74192N	0.55
74193N	0.55
74194N	0.55
74195N	0.55
74196N	0.55
74197N	0.55
74198N	0.85
74199N	1.00
74221N	1.00
74246N	1.50
74247N	1.51
74248N	1.89
74249N	0.11
74251N	1.05
74265N	0.66
74273N	2.67
74278N	2.49
74279N	0.89
74283N	1.30
74284N	3.50
74285N	3.50
74290N	1.00
74293N	1.05
74297N	2.36
74298N	1.85
74365N	0.85
74366N	0.85
74367N	0.85
74368N	0.85
74390N	1.85
74393N	1.85
74490N	1.85

74LSN	
74LS00N	0.10
74LS01N	0.10
74LS02N	0.11
74LS03N	0.11
74LS04N	0.14
74LS05N	0.13
74LS08N	0.12
74LS09N	0.12
74LS10N	0.12
74LS11N	0.12
74LS12N	0.12
74LS13N	0.20
74LS14N	0.30
74LS15N	0.12
74LS20N	0.12
74LS21N	0.12
74LS22N	0.12
74LS26N	0.14
74LS27N	0.12
74LS28N	0.15
74LS30N	0.12
74LS32N	0.12
74LS33N	0.15
74LS37N	0.15
74LS38N	0.14
74LS40N	0.13
74LS42N	0.30
74LS47N	0.35
74LS48N	0.45
74LS49N	0.55
74LS51N	0.13
74LS54N	0.14
74LS55N	0.14
74LS73V	0.21

74LS74N	0.16
74LS75N	0.22
74LS76N	0.20
74LS78N	0.19
74LS83N	0.40
74LS85N	0.60
74LS86N	0.14
74LS90N	0.32
74LS91N	0.28
74LS92N	0.31
74LS93N	0.31
74LS95N	0.40
74LS96N	1.20
74LS107N	0.25
74LS109N	0.20
74LS112N	0.20
74LS113N	0.20
74LS114N	0.19
74LS122N	0.35
74LS123N	0.35
74LS124N	1.60
74LS125N	0.24
74LS126N	0.24
74LS132N	0.42
74LS133N	0.24
74LS136N	0.20
74LS138N	0.30
74LS139N	0.30
74LS145N	1.20
74LS151N	0.30
74LS153N	0.27
74LS154N	0.89
74LS155N	0.35
74LS156N	0.37
74LS157N	0.30
74LS158N	0.30
74LS160N	0.37
74LS161N	0.37
74LS162N	0.37
74LS163N	0.37
74LS164N	0.40
74LS165N	0.80
74LS166N	0.80
74LS168N	0.70
74LS169N	0.85
74LS170N	0.30
74LS173N	0.80
74LS174N	0.40
74LS175N	0.40
74LS181N	1.05
74LS183N	1.75
74LS189N	1.28
74LS190N	0.45
74LS191N	0.45
74LS192N	0.45
74LS193N	0.45
74LS194N	0.35
74LS196N	0.55
74LS197N	0.60
74LS200N	3.40
74LS202N	3.45
74LS221N	0.50
74LS240N	0.80
74LS241N	0.80
74LS242N	0.80
74LS243N	0.70
74LS244N	0.60
74LS245N	0.60
74LS247N	1.35

74LS248N	1.35
74LS249N	1.35
74LS251N	0.35
74LS253N	0.35
74LS257N	0.40
74LS258N	0.37
74LS259N	0.60
74LS260N	0.50
74LS266N	0.22
74LS273N	0.70
74LS275N	3.20
74LS279N	0.35
74LS280N	2.50
74LS283N	0.42
74LS290N	0.50
74LS293N	0.40
74LS295N	1.50
74LS298N	0.76
74LS365N	0.32
74LS366N	0.34
74LS367N	0.32
74LS368N	0.35
74LS373N	0.70
74LS374N	0.70
74LS375N	0.40
74LS377N	0.85
74LS378N	0.65
74LS379N	0.60
74LS384N	2.50
74LS385N	2.05
74LS386N	0.29
74LS390N	0.68
74LS393N	0.61
74LS395N	2.10
74LS396N	1.99
74LS398N	2.75
74LS399N	2.30
74LS445N	1.40
74LS447N	1.95
74LS490N	1.10
74LS668N	1.05
74LS669N	1.05
74LS670N	1.70

RAM	
2102	1.70
2112	3.40
2114	2.49
4027	5.78
4116	2.59
4116	3.49
4864P	12.50
6116P	9.00
6116P	11.25
8254	12.50

74CXX	
74C00	0.20
74C02	0.20
74C04	0.20
74C06	0.20
74C10	0.20
74C14	0.55
74C20	0.20
74C30	0.20
74C32	0.20
74C42	0.80
74C48	1.03
74C73	0.50
74C74	0.50

||
||
||

# ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate, and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

<b>APRIL 79</b>	<input type="checkbox"/> Guitar Effects Unit	£1.98	<b>MARCH 81</b>	<input type="checkbox"/> Engineer's Stethoscope	£1.99	<b>NOVEMBER 81</b>	<input type="checkbox"/> Music Processor	£5.51
	<input type="checkbox"/> Click Eliminator	£4.98					<input type="checkbox"/> Voice-Over Unit	£2.98
<b>JUNE 79</b>	<input type="checkbox"/> Accentuated Beat Metronome	£2.70	<b>APRIL 81</b>	<input type="checkbox"/> Musical Box	£1.98		<input type="checkbox"/> Car Alarm	£2.11
				<input type="checkbox"/> Drum Machine (two boards)	£4.20		<input type="checkbox"/> Phone Bell Shifter	£2.22
<b>FEBRUARY 80</b>	<input type="checkbox"/> Tuning Fork	£1.98		<input type="checkbox"/> Guitar Note Expander	£2.40	<b>DECEMBER 81</b>	<input type="checkbox"/> Alcohometer (two boards)	£3.99
<b>MARCH 80</b>	<input type="checkbox"/> Signal Tracer	£1.70	<b>JUNE 81</b>	<input type="checkbox"/> Mini-drill Speed Controller	£2.20		<input type="checkbox"/> Bodywork Checker	£1.48
				<input type="checkbox"/> Antenna Extender	£2.40	<b>JANUARY 82</b>	<input type="checkbox"/> Component Tester	£1.12
<b>AUGUST 80</b>	<input type="checkbox"/> CMOS Logic Tester	£1.98		<input type="checkbox"/> Alien Attack	£1.98		<input type="checkbox"/> Parking Meter Timer	£1.78
	<input type="checkbox"/> Capacitance Meter	£2.20		<input type="checkbox"/> LED Jewellery: Cross	£1.10		<input type="checkbox"/> Infant Guard	£1.35
	<input type="checkbox"/> Ultrasonic Burglar Alarm	£2.15		<input type="checkbox"/> Spiral (two boards)	£1.98		<input type="checkbox"/> Guitar Tuner (two boards)	£4.48
				<input type="checkbox"/> Star (two boards)	£1.99	<b>FEBRUARY 82</b>	<input type="checkbox"/> Ripple Monitor	£1.56
<b>OCTOBER 80</b>	<input type="checkbox"/> Cassette Interface	£2.20		<input type="checkbox"/> Waa-phase	£1.15		<input type="checkbox"/> Pest Monitor	£1.39
	<input type="checkbox"/> Fuzz/Sustain Box	£2.45	<b>JULY 80</b>	<input type="checkbox"/> System A A-MM/A-MC	£1.99		<input type="checkbox"/> I Ching Computer (two boards)	£3.98
<b>NOVEMBER 80</b>	<input type="checkbox"/> Touch Buzzer	£1.45		<input type="checkbox"/> System A A-PR	£3.88		<input type="checkbox"/> Moving-magnet stage	£2.85
	<input type="checkbox"/> Light Switch	£1.45		<input type="checkbox"/> Smart Battery Charger	£1.48		<input type="checkbox"/> Moving-coil stage	£2.85
	<input type="checkbox"/> Metronome	£1.45	<b>AUGUST 81</b>	<input type="checkbox"/> System A Power Amp (A-PA)	£3.58	<b>MARCH 82</b>	<input type="checkbox"/> Infinite Improbability Detector	£2.53
	<input type="checkbox"/> 2W Power Amp	£1.45		<input type="checkbox"/> Flash Sequencer	£2.58		<input type="checkbox"/> Capacitance Meter (two boards)	£10.64
	<input type="checkbox"/> RIAA Preamplifier	£1.45		<input type="checkbox"/> Hand-clap Synthesiser	£2.98		<input type="checkbox"/> Robot Motor Controller	£2.85
	<input type="checkbox"/> Audio Test Oscillator	£2.35		<input type="checkbox"/> Heartbeat Monitor	£1.37		<input type="checkbox"/> Light Wand	£1.40
<b>DECEMBER 80</b>	<input type="checkbox"/> Musical Doorbell	£2.10		<input type="checkbox"/> Watchdog Home Security (two boards)	£3.98	<b>APRIL 82</b>	<input type="checkbox"/> Contrast Meter	£2.12
	<input type="checkbox"/> Bench Amplifier	£1.90	<b>SEPTEMBER 81</b>	<input type="checkbox"/> Mains Audio Link (three boards)	£5.51		<input type="checkbox"/> Sound Effects board	£1.80
	<input type="checkbox"/> Four Input Mixer	£1.98		<input type="checkbox"/> Laboratory PSU	£3.40		<input type="checkbox"/> High Impedance Probe	£1.48
<b>JANUARY 81</b>	<input type="checkbox"/> LED Tacho	£3.10					<input type="checkbox"/> Guitar Practice Amp	£5.68
	<input type="checkbox"/> Multi-Option Siren	£2.40	<b>OCTOBER 81</b>	<input type="checkbox"/> Enlarger Timer	£2.55	<b>MAY 82</b>	<input type="checkbox"/> Accurate Voltage Monitor	£1.54
	<input type="checkbox"/> Universal Timer	£2.48		<input type="checkbox"/> Sound Bender	£1.99		<input type="checkbox"/> DVMeg	£2.19
<b>FEBRUARY 81</b>	<input type="checkbox"/> Infra-red Alarm (four boards)	£4.98		<input type="checkbox"/> Thermal Alarm	£1.97		<input type="checkbox"/> Analogue PWM	£2.53
	<input type="checkbox"/> Pulse Generator	£2.68		<input type="checkbox"/> Micropower Pendulum	£1.66		<input type="checkbox"/> Oscilloscope (four boards)	£9.89
							<input type="checkbox"/> Slot Car Controller	£3.72
							<input type="checkbox"/> Wattmeter	£3.40
							<input type="checkbox"/> Sound Effects Board	£1.80

**How to order:** indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices may be subject to change without notice.

Total for boards    £ . . . . .  
 Add 40p p&p            0.40  
 Total enclosed        £ . . . . .

I wish to pay by Access/Barclaycard. Please debit my account

BARCLAYCARD

VISA

5	2	2	4																
4	9	2	9																

Signed .....


Name .....

Address .....


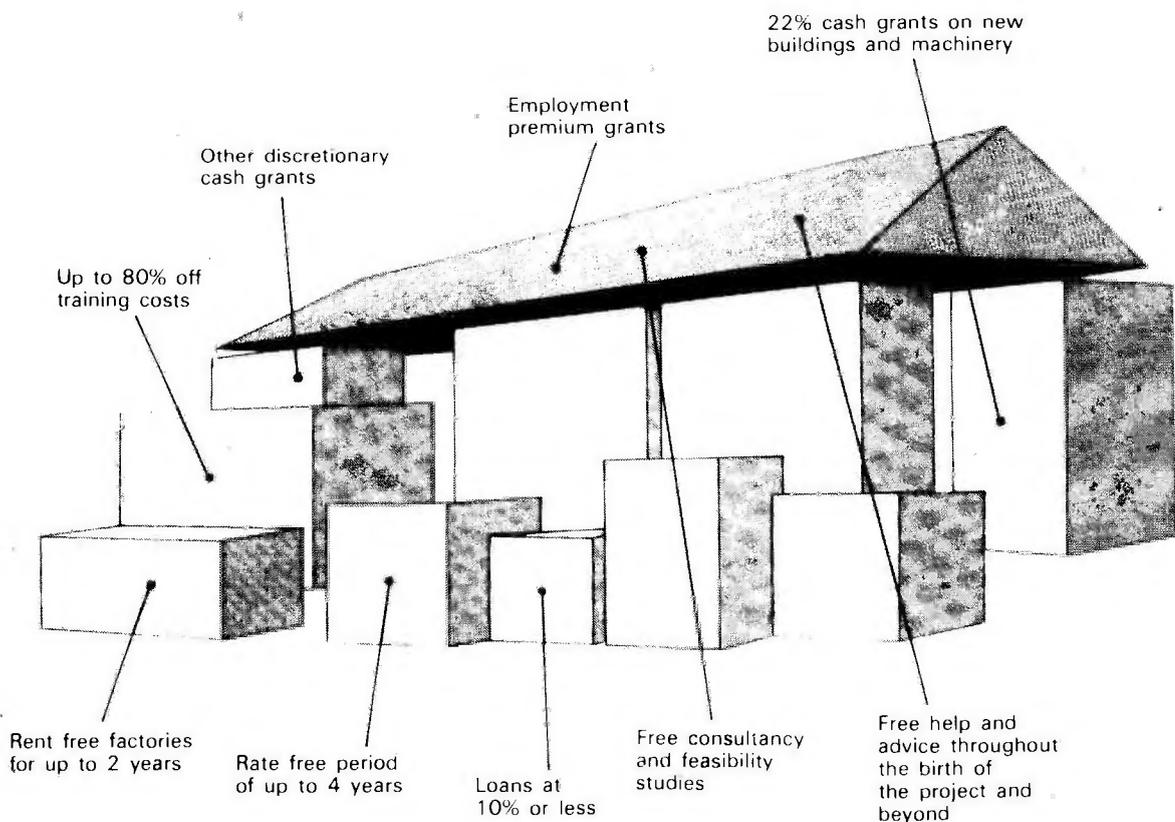
# Derwentside

...probably the best financial package in the country



Starting a new business or relocating an existing one couldn't be easier than in Derwentside. The move is working for others. Make it work for you. Contact one of the resident team of helpful experts at, in the strictest of confidence of course,

**DERWENTSIDE INDUSTRIAL DEVELOPMENT CENTRE**  
Berry Edge Road, Consett, Derwentside DH8 5PT. Tel: Consett 509124/5

24-Hour Answering Service

# ELECTROMUSIC TECHNIQUES

The second in this design series by leading-expert-in-the-field Tim Orr features voltage controlled filters, voltage controlled amplifiers and ring modulators.

The first group of circuits we consider this month are voltage-controlled filters. Figure 1 shows the circuit for a state variable filter with four frequency responses; lowpass, highpass, bandpass and notch. All four responses can be controlled by varying the gain of the two integrators. The Q factor of the filter can also be voltage controlled. If the Q is set to maximum, by turning off the feedback CA3080, then the circuit will become a sine wave oscillator (because the damping has been reduced to zero). Prior to this, very high Q factors can be obtained, of the order of 400. The frequency responses are shown in Fig. 2. Most synthesisers use a -24 dB/octave lowpass VCF, but the more responses that are available, the wider is the choice of sound that can be produced.

VCFs are usually swept with a control voltage from an ADSR. Every time a note is played on the keyboard the VCF is swept, the shape of the ADSR signal and its polarity determining the type of sound that is heard. Figure 3 is a circuit for sweeping a VCF. Both positive and negative sweeps are obtained on one control pot. Curtis make a VCF chip, the CEM3320 (Fig. 4). The configuration shown is a four pole (-24 dB/octave) lowpass filter with a +1 V/octave sensitivity and voltage control of the Q factor.

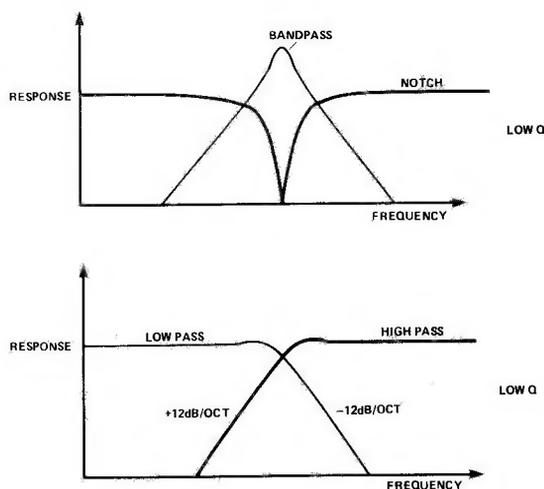


Fig. 2 State variable filter responses.

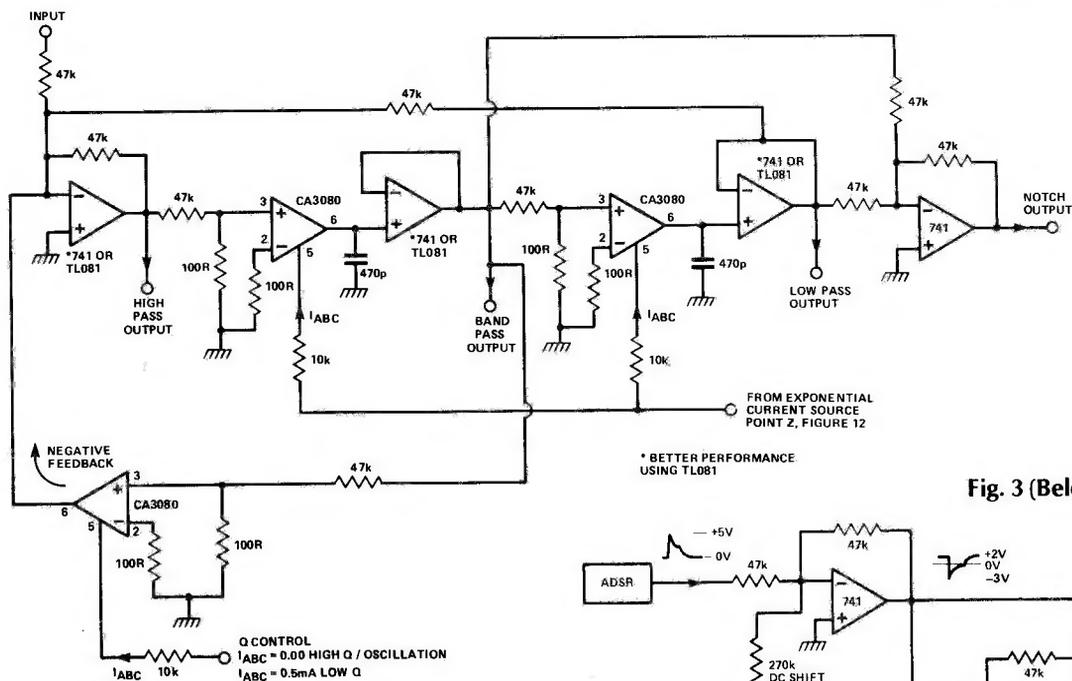


Fig. 3 (Below) VCF sweep control unit.

Fig. 1 State variable VCF.



out by adding a small DC voltage to the non-inverting terminal, which should eliminate most of the control breakthrough. Any residual breakthrough is due to current mirror mismatches in the CA3080 and is unavoidable. Distortion may also be rather high, perhaps in the region of 0.5%, but this is not generally considered to be a problem in synthesiser circuits. Lowering the input signal level will reduce the distortion at the expense of an increase in the noise level.

A better VCA is shown in Fig. 9, the CEM3330 made by Curtis. This is a dual device with both log and linear control inputs, low noise and low distortion plus very low control feedthrough. A third VCA is shown in Fig. 10, this one being constructed from a CA3046 transistor array. It uses two of the transistors as a predistortion circuit so that a higher operating signal level can


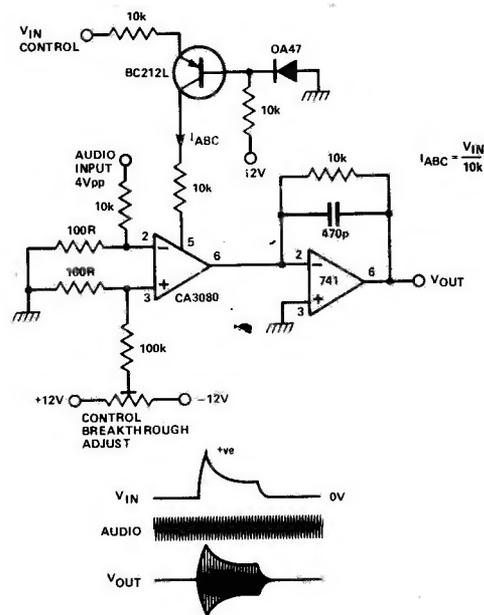


Fig. 8 (Above) Simple VCA.

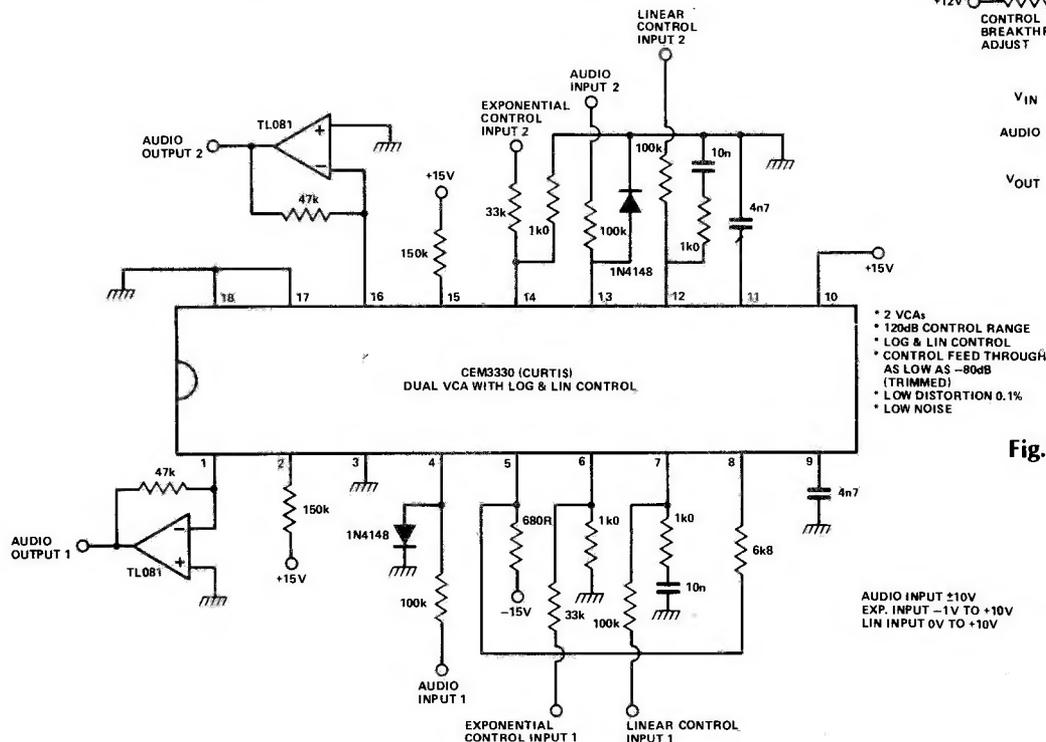

- 2 VCAs
- 120dB CONTROL RANGE
- LOG & LIN CONTROL
- CONTROL FEED THROUGH AS LOW AS -80dB (TRIMMED)
- LOW DISTORTION 0.1%
- LOW NOISE

AUDIO INPUT  $\pm 10V$   
EXP. INPUT  $-1V$  TO  $+10V$   
LIN INPUT  $0V$  TO  $+10V$

Fig. 9 (Left) Monolithic VCA circuit.

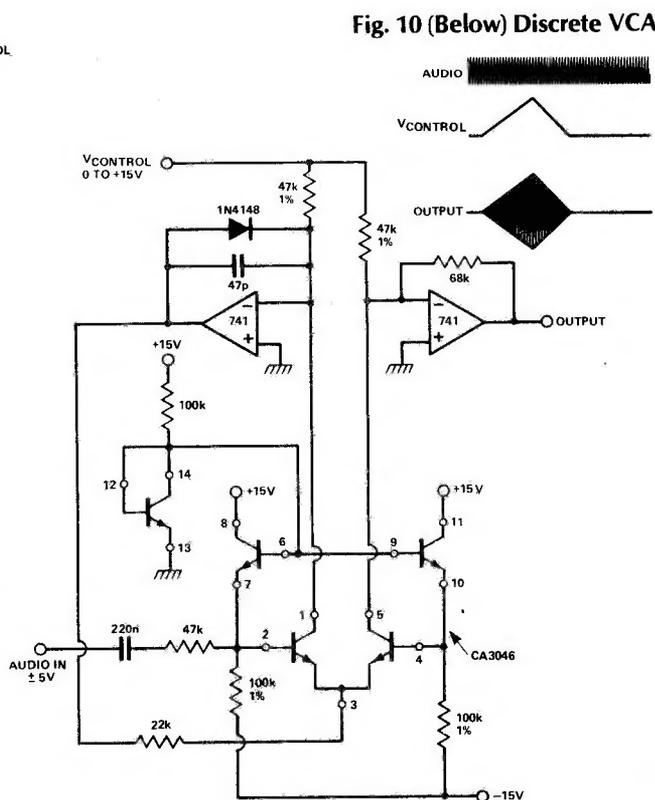


Fig. 10 (Below) Discrete VCA.

be used for the same level of distortion. In fact, the predistortion principle is used in several multiplier chips, including the LM13600 which is used in the next circuit, (Fig. 11). The two LM13600 circuits are used a low distortion VCAs. A predistortion diode bias current is inserted into the IC at pins 2 and 15. The gain of each VCA is controlled by the  $I_{ABC}$  current (pins 1 and 16), this current being derived from a pair of complementary control voltages. As the gain of the channel increases the other decreases. Some interesting effects can be obtained with this circuit; for example a note can pan from left to right every time it is played.

The VCAs mentioned so far have all been two quadrant multipliers. The operation of a four quadrant multiplier (sometimes called a balanced modulator or ring modulator) is very different (Fig. 12). When two sine waves are multiplied together the result is a signal composed of sum and difference tones. For example, if the two input sine waves have frequencies of 100 Hz and 1 kHz, then the output will be composed of two tones, one at 1100 Hz (sum) and one at 900 Hz (difference). If the same sine wave is applied to both inputs, then the sum tone is twice the original frequency, and the difference tone is a DC voltage. Ring modulators are used to produce discordant sounds and special effects such as the BBC Dalek voice.

Figure 13 is a simple ring modulator circuit. The performance suffers a bit from poor X and Y feedthrough, which can be minimized by adjustment of the two presets. A better modulator is shown in Fig. 14; this circuit employs a balanced modulator chip made by National Semiconductor and others.





# COMPUTER WAREHOUSE

NOW OPEN  
MONDAY SATURDAY  
9 30 5 30

**BULK BUY SPECIALS**

### RAM SCOOP

4116 200 NS 8 for £12.95  
4184 200 NS £8.50 each  
2102-650 NS 8 for £5.50  
INC VAT

### 25 WAY "D" CONNECTORS

	50+	100+
25p	1.70	1.10
25s	1.90	1.20

ALL + VAT

### WIRE WRAP SKTS.


24 Pin Vers 28p  
14 Pin Gold 22p  
18 Pin Gold 24p  
100 PCS Min Ord.

**C10 DATA CASSETTES**  
10 for £5.75  
Inc. VAT

### RF CONNECTORS

50Ω BNC PLG 50p  
75Ω BNC PLG 50p  
PL259 PLG 40p  
S0238 SKT 35p  
100 PCS MIN ORD.

## TELETYPE ASR33 I/O TERMINALS

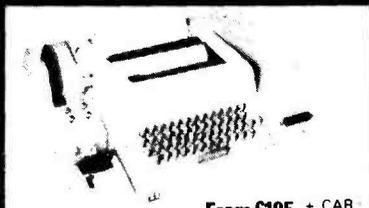

From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT

KSR33 With 20ma loop interface £125.00 + VAT.  
Sound proof enclosure £25.00 + VAT

## "OLIVETTI TE300" PRINTER/TERMINALS



A complete I/O terminal with integral 8 hole paper tape punch and reader, full ASCII keyboard, 120 column printer, and control unit. The printer is capable of 150 baud with a serial TTL or balanced input-output sold in good overall condition but untested. Complete with circuit unguaranteed. Connect direct to your micro at ONLY £99.00 + £11.50 carr + vat.

## MPU EXPERIMENTORS +5v, 12v, 12v, 24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 160mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:

+5v @ 2 amps DC +12v @ 800 ma DC  
-12v @ 800 ma DC +24v @ 350 ma DC  
and if that's not enough a fully floating 5v output @ 50 ma DC which may be seriesed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v mains input. They are ex GPO and may have minor scratches on the front panels, they are sold unrestored but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!

## HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd to a "no cost spared" spec for the GPO, the Modern 12 is a synchronous Modem for use on OATEL 2412 services, or other data links. Many features include switchable V28 modulation, 2400 baud full duplex 600/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc. £185.00 + £9.50 carriage + VAT.  
\*Permission may be required for connection to PD lines

## DISTEL ©

"Dial our Database!"  
Get information on 1000's of stock items and order via your computer. 300 baud on 01-689 6800  
18.30 to 0900 6 days a week and all day Sundays. IT'S FREE!

## DIABLO S30 DISK DRIVES

Another shipment allows us to offer you even greater savings on this superb 2.5 MB (formatted) hard disk drive. Two types are available both fully refurbished and electronically identical, the only difference is the convenience of changing the disk packs.

S30 front loader, pack change via front door £550 + vat  
S30 fixed, pack change via removal of top cover £295 + vat  
+ & - 15v PSU for 2 drives £125 + vat

Carriage & insurance on drives £15.00 + vat fully DEC RK05, NOVA, TEXAS compatible further info on controllers etc on request.

## MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those unerving hang ups and data glitches, fit one now and cure your problems! Suppression Devices SD5 A10 5 amp £6.95  
Corcom Inc F1900 30 amp £13.95 + pp £1.00

## DC SYSTEM SUPPLY

Professional fully cased fan cooled system supply. Standard 240V ac input with the following DC outputs 5V @ 11 amps + 15-17v @ amps, -15-17v @ 8 amps and +24v @ 4 amps. All outputs are fully crowbar protected and the 5 volt output is fully regulated. Sold tested and in a new or little used condition complete with circuit £55.00 + carr £8.50 + vat DIM 15.5" x 9" x 6"

## NATIONAL MA1012 LED CLOCK MODULE

★ 12 HOUR  
★ ALARM  
★ 50/60 HZ



The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 11" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only Suitable transformer £1.75. £5.25


ELECTRONIC COMPONENTS & EQUIPMENT

**66%**  
DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kds £ 4.75 + pp £1.25    5kds £ 6.75 + pp £1.80  
10kds £11.75 + pp £2.25    20kds £19.99 + pp £4.75
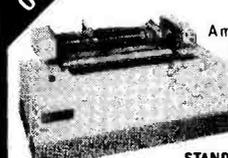
## THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232/V24 serial interface - 7x24 controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eeproms easily reconfigured for custom fonts etc.

All this and more, not refurbished but BRAND NEW At Only £525 + VAT

OPTIONAL EXTRAS \* lower case option £25.00 \* 16k buffer £30.00 \* Second tractor for simultaneous dual forms £85.00 \* Floor stand £45.00 \* specialist carriage £19.00 All items plus VAT data sheet on request.

## 8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you a 100% bus compatibility with most drives available today, the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring, IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc. compatible. Supplied BRAND NEW with user manual and 90 day warranty.



7100 single sided ..... £225.00 + 9.50 carr + vat  
7200 double sided ..... £295.00 + 9.50 carr + vat  
full technical manual £20.00 alone £9.00 with drive, refund of difference on purchase of drive. Data sheet on request.  
SPECIAL new, KODE PSU, drives 2 DRE drives £39.99 + carr + vat  
8" single sided, single or double density diskettes £1.80 each £15.00 for 10 inc. lib case + vat.

## COOLING FAN SPECIAL

Keep your equipment cool and reliable with our range of professional fans.  
ETRI 99XU01 Miniature equipment fan 240 vac working DIM 92 x 92 x 25 mm BRAND NEW complete with finger guard. Maker's price £16 our price £10.25  
BUHLER 89.11 22 micro miniature 8-16 vDC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor, almost silent running ideal portable equipment, life in excess of 10,000 hours. BRAND NEW manufacturers price £2.00 our price £13.95  
MUFFIN/CENTAUR cooling fans, tested ex equipment 240V £8.60, 115v £6.50 + p&p £1.90  
KOOL TRONICS Powerful snail type blower gives massive air movement with centrifugal rotor DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50 Hz ac working ONLY £9.95 + £1.90 p&p.

## SOFTY 1 & 2 EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.  
Softy 2 for 2719/2732 £169 + VAT  
Write of phone for more details.

## 9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75Ω composite input, tested but unguaranteed. £39.99 + £7.50 carriage + VAT. Complete with circuit.

## SEMICONDUCTOR GRAB BAGS

Unicized Semis amazing value contents include transistors, diodes, linear, I.C.'s, triacs, diodes, bridge rect., etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed. 50-bag £2.95 100-bag £3.15 TTL 74 Series

A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three times in the bag would normally cost to buy. Fully guaranteed at I.C.'s full spec. 100+ £8.99 200+ £12.99 300+ £18.99

## RCA FULLY CASED ASCII CODED KEYBOARDS



IDEAL - TANGERINE, OHIO ETC.

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. £43.95  
VP601 Same as VP601 with numeric pad. £54.95  
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. £84.26  
VP616 Same as VP606, with numeric pad, Plug and cable for VP601, VP611 £2.25  
Plug for VP606, VP616 £2.10  
Post, Packing and Insurance. £1.95  
ORDER NOW OR SEND FOR DETAILS.

## 5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.; 240 or 110v A.C. input. Outputs of 5v @ 3.4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply. Supplied complete with circuit at only £10.95 + £1.75pp. Believed working but untested, unguaranteed.

# ELECTRONICS

Dept. E.T.I., 64-66 Melfort Rd., Thornton Heath, MAIL ORDER  
Croydon, Surrey. Tel: 01-689 7702 or 01-689 8800 INFORMATION  
Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00 Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bond Fida account orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

# Greenbank

Greenbank Electronics  
 (Dept T4E), 92 Chester Road, New Ferry  
 Wirral, Merseyside L62 5AG  
 (Tel. 051 645 3391)



**TERMS. VAT. C.W.O. Cheques etc payable to Greenbank Electronics and crossed.**  
 Add VAT to all prices at 15% except where stated otherwise. Post etc: UK 40p  
 (+6p VAT = 46p) per order. Export: NO VAT but add 40p (Eire), £1 (Europe) and  
 £3.50 elsewhere. Access. Barclaycard, Visa, telephoned orders accepted.  
 (Polys. universities, gov't depts. etc can telephone their orders for immediate  
 despatch on account.)



## QUARTZ

32.768KHz (watch)	£2.50
60 KHz	£9.95
100 KHz	£2.90
200 KHz	£2.90
204.8 KHz	£3.50
282.14 KHz	£3.92
307.2 KHz	£3.92
312.5 KHz	£3.92
455.2 KHz	£3.92
512.0 KHz	£3.92
1.000 MHz	£2.95
1.008 MHz	£3.50
1.280 MHz	£3.92
1.6 MHz	£4.26
1.8 MHz	£4.26
1.8432 MHz	£2.99
2.048 MHz	£2.99
2.097152 MHz	£3.23
2.4576 MHz	£2.99
2.560 MHz	£3.92
3.000 MHz	£3.62
3.2768 MHz	£2.70
3.579545 MHz	£1.75
3.9312 MHz	£3.92
4.000 MHz	£1.99
4.032 MHz	£1.99
4.096 MHz	£1.99
4.19048 MHz	£1.99
4.43319 MHz	£1.99
4.608 MHz	£3.23
4.800 MHz	£1.99
4.9152 MHz	£3.92
5.000 MHz	£1.99
5.120 MHz	£3.23
5.185 MHz	£3.23
5.6288 MHz	£4.25
5.760 MHz	£2.70
5.8144 MHz	£1.99
6.400 MHz	£3.23
6.55360 MHz	£1.99
7.000 MHz	£2.99
7.168 MHz	£1.99
7.680 MHz	£1.99
7.86432 MHz	£3.23
8.000 MHz	£1.99
8.08333 MHz	£3.62
8.38868 MHz	£3.92
8.66727 MHz	£1.99
9.375 MHz	£2.99
10.745 MHz	£3.23
10.700 MHz	£3.23
10.92 MHz	£3.92
11.200 MHz	£3.92
12.000 MHz	£3.92
14.0 MHz	£3.92
14.31818 MHz	£2.99
16.000 MHz	£2.99
16.432 MHz	£2.99
19.968 MHz	£3.00
20.000 MHz	£3.00
20.1134 MHz	£3.23
24.0 MHz	£3.92
26.890 MHz	£2.99
27.0 MHz	£3.92
27.145 MHz	£3.00
27.648 MHz	£3.23
38.666 MHz	£3.92
48.000 MHz	£2.99
48.000 MHz	£2.99
116.000 MHz	£3.00

## VEROBORD

0.1" Pitch with copper strips	£1.01
2 1/2" x 1 1/2" (100) 50	£3.50
2 1/2" x 5"	£3.50
2 1/2" x 17"	£3.50
3 1/2" x 3 1/2"	85p
3 1/2" x 5"	95p
3 1/2" x 7"	1.25
4 7/8" x 17 1/2"	£4.26
0.1" Plainboard (no strips)	£2.95
3 1/2" x 2"	52p
3 1/2" x 5"	79p
3 1/2" x 17"	£2.11
Terminal pins 1.50	50p
V.O.P. board	£1.58
DIP breadboard	£3.98
Split face cutter	£1.18
Pin insertion tool	£1.82

## CMOS

These cut prices for Amateur Users and Export  
 Note: industrial users' quantity prices available  
 Mostly Motorola, RCA

4000	14p	4042	60p	4093	43p	4409	£7.90	4531	£1.30
4001	14p	4043	75p	4094	£1.60	4410	£7.20	4532	£1.10
4002	14p	4044	80p	4095	90p	4411	£6.95	4534	£1.00
4006	66p	4045	£1.70	4096	90p	4412VP	£8.00	4536	£2.95
4007	18p	4046	75p	4097	£3.20	4415V	£4.80	4537L	£26.10
4008	82p	4047	75p	4098	88p	4422	£5.88	4538	£1.15
4009	35p	4048	55p	4099	88p	4423	£7.70	4539	£1.15
4010	40p	4049	40p	4100	£1.92	4435V	£5.40	4541	£1.10
4011	15p	4050	30p	4101	£1.30	4450	£3.50	4543	£1.35
4012	18p	4051	78p	4102	£1.80	4461	£3.93	4549	£3.95
4013	34p	4052	78p	4103	£1.75	4462	£4.41	4552	£1.85
4014	66p	4053	78p	4104	96p	4490PP	£3.50	4553	£2.99
4016	32p	4054	£1.25	4105	£1.15	4490VP	£3.14	4559	£1.98
4018	32p	4055	32p	4106	75p	4501	29p	4555	50p
4017	48p	4056	£1.20	4107	60p	4502	£1.20	4556	55p
4018	88p	4059	£4.80	4108	£4.50	4503	70p	4557	£3.20
4019	42p	4060	90p	4109	£1.00	4505	£5.71	4560	£1.20
4020	81p	4062T	£9.95	4110	£3.00	4506	90p	4559	£3.95
4021	70p	4063	90p	4111	£2.77	4507	40p	4560	48p
4022	66p	4064	20p	4160	£1.54	4508	£2.65	4561	81p
4023	20p	4067	£3.99	4161	£1.54	4510	68p	4562	£4.95
4024	45p	4068	22p	4162	£1.54	4511	68p	4566	£1.59
4025	18p	4069	20p	4163	£1.54	4512	75p	4568	£2.38
4026	£1.30	4070	26p	4174	£1.54	4513	£1.99	4569	£1.75
4027	38p	4071	26p	4208	£7.54	4514	£1.95	4571	36p
4028	58p	4072	20p	4182	£1.90	4515	£1.95	4580	£4.60
4029	77p	4073	20p	4192	£2.41	4517	£4.15	4581	£2.50
4030	60p	4075	20p	4193	£2.41	4517	£4.15	4582	98p
4031	£1.70	4076	60p	4194	£1.05	4518	42p	4583	90p
4032	£1.25	4077	26p	4195	£1.05	4519	29p	4584	48p
4033	£1.68	4078	26p	4209	£7.54	4521	79p	4589	£2.44
4034	£1.95	4081	28p	4160	95p	4522	£2.00	4598	£2.90
4035	95p	4082	28p	4161	95p	4522	£1.11	4599	£5.95
4037	£1.18	4085	65p	4162	95p	4526	95p	4700	£1.75
4038	£1.10	4086	65p	4163	95p	4527	£1.15	ICM7038A	£4.25
4039	£2.9	4086	70p	4174	95p	4528	£1.15		
4040	59p	4089	£1.40	4175	£1.05	4529	£1.30		
4041	78p			4194	£1.05	4530	70p		

## 74C

74C00	28p	74C76	57p	74C163	£1.15	74C304	57p	74C926	£6.99
74C02	28p	74C83	£1.34	74C164	£1.00	74C305	£7.53	74C927	£5.99
74C04	28p	74C86	£1.34	74C165	£1.00	74C307	57p	74C928	£5.99
74C06	28p	74C89	£4.62	74C174	93p	74C308	£1.00	74C929	£7.90
74C08	28p	74C90	89p	74C175	93p	74C309	£1.69	74C930	£7.90
74C10	28p	74C93	90p	74C182	£1.15	74C310	£1.69		
74C12	28p	74C96	£1.06	74C183	£1.15	74C311	£7.39	80C95	85p
74C14	30p	74C98	£1.06	74C184	£1.15	74C312	£7.39	80C96	92p
74C20	28p	74C150	£3.81	74C221	£1.41	74C315	£1.15	80C97	85p
74C30	28p	74C151	£2.55	74C373	£1.79	74C316	£1.15	80C98	92p
74C32	28p	74C154	£3.81	74C374	£1.79	74C317	£1.15	80C99	£6.20
74C42	96p	74C157	£2.29	74C375	£1.79	74C318	£1.15	80C30	£2.90
74C48	15p	74C161	£1.40	74C391	57p	74C319	£1.15		
74C73	57p	74C162	£1.15	74C392	79p	74C322	£3.78		
74C74	50p	74C162	£1.15	74C393	57p	74C323	£5.49		
						74C325	£5.99		

## 74LS

74LS00	12p	74LS55	50p	74LS151	39p	74LS243	85p	74LS387	37p
74LS01	13p	74LS53	25p	74LS153	39p	74LS244	80p	74LS388	66p
74LS02	14p	74LS74	25p	74LS154	70p	74LS245	£1.18	74LS389	66p
74LS03	14p	74LS75	25p	74LS155	39p	74LS247	40p	74LS374	75p
74LS04	14p	74LS76	25p	74LS156	39p	74LS248	65p	74LS375	48p
74LS05	15p	74LS77	24p	74LS157	39p	74LS249	68p	74LS377	90p
74LS06	15p	74LS78	24p	74LS158	39p	74LS251	40p	74LS378	69p
74LS08	15p	74LS79	24p	74LS159	39p	74LS252	40p	74LS379	65p
74LS10	15p	74LS80	38p	74LS160	41p	74LS257	40p	74LS384	86p
74LS11	15p	74LS81	38p	74LS162	41p	74LS258	40p	74LS386	86p
74LS12	15p	74LS82	35p	74LS163	41p	74LS259	85p	74LS390	62p
74LS13	30p	74LS83	95p	74LS164	40p	74LS260	21p	74LS393	60p
74LS14	48p	74LS84	95p	74LS165	79p	74LS261	£1.96	74LS395	£1.99
74LS15	15p	74LS85	95p	74LS166	85p	74LS262	25p	74LS396	£1.90
74LS16	15p	74LS86	95p	74LS167	85p	74LS263	25p	74LS398	£2.75
74LS17	15p	74LS87	95p	74LS168	85p	74LS264	25p	74LS399	£2.80
74LS18	15p	74LS88	95p	74LS169	85p	74LS265	25p	74LS400	£2.80
74LS19	15p	74LS89	95p	74LS170	72p	74LS266	25p	74LS401	£2.80
74LS20	15p	74LS90	35p	74LS171	72p	74LS267	25p	74LS402	£2.80
74LS21	15p	74LS91	80p	74LS172	72p	74LS268	25p	74LS403	£2.80
74LS22	15p	74LS92	35p	74LS173	72p	74LS269	25p	74LS404	£2.80
74LS23	15p	74LS93	95p	74LS174	72p	74LS270	25p	74LS405	£2.80
74LS24	15p	74LS94	45p	74LS175	58p	74LS271	25p	74LS406	£2.80
74LS25	15p	74LS95	45p	74LS176	58p	74LS272	25p	74LS407	£2.80
74LS26	15p	74LS96	£1.16	74LS177	58p	74LS273	25p	74LS408	£2.80
74LS27	15p	74LS97	43p	74LS178	58p	74LS274	25p	74LS409	£2.80
74LS28	20p	74LS98	43p	74LS179	58p	74LS275	25p	74LS410	£2.80
74LS29	20p	74LS99	43p	74LS180	58p	74LS276	25p	74LS411	£2.80
74LS30	18p	74LS100	43p	74LS181	58p	74LS277	25p	74LS412	£2.80
74LS31	18p	74LS101	43p	74LS182	58p	74LS278	25p	74LS413	£2.80
74LS32	18p	74LS102	43p	74LS183	58p	74LS279	25p	74LS414	£2.80
74LS33	16p	74LS103	30p	74LS184	58p	74LS280	25p	74LS415	£2.80
74LS34	16p	74LS104	30p	74LS185	58p	74LS281	25p	74LS416	£2.80
74LS35	16p	74LS105	30p	74LS186	58p	74LS282	25p	74LS417	£2.80
74LS36	16p	74LS106	30p	74LS187	58p	74LS283	25p	74LS418	£2.80
74LS37	16p	74LS107	30p	74LS188	58p	74LS284	25p	74LS419	£2.80
74LS38	16p	74LS108	30p	74LS189	58p	74LS285	25p	74LS420	£2.80
74LS39	16p	74LS109	30p	74LS190	58p	74LS286	25p	74LS421	£2.80
74LS40	16p	74LS110	30p	74LS191	58p	74LS287	25p	74LS422	£2.80
74LS41	16p	74LS111	30p	74LS192	58p	74LS288	25p	74LS423	£2.80
74LS42	16p	74LS112	30p	74LS193	58p				

# 10 MHz OSCILLOSCOPE


Fed up with those awkward moments when you want to measure a sine wave and your oscilloscope's at home? This instrument is everything you could wish for — small, handy, efficient and independent of the mains. Design by K.W. Dugge.

Compared with conventional instruments this oscilloscope is smaller, lighter and better value for money. It is barely larger than a house brick and about as heavy as a good multimeter; thus it is ideally suited to mobile usage on building sites, in installation work, in motor vehicles and so on. The instrument can be powered either from the mains, using a separate 240 V to 12 V transformer, or direct from a 12 V battery. The specifications are given in the table.

The individual circuit blocks are connected by ribbon cable. The 12 V DC or AC supply enters via two connectors on the rear of the instrument, passing through a two-pole switch (linked to the X-position potentiometer) to the power supply card. After stabilisation to 10 V, the various working voltages are generated here using a 25 kHz switching circuit. Stabilisation of the input has the advantage that all the output voltages are thereby simultaneously stabilised, ie they are independent of supply variations. Because a switching regulator represents a voltage source having a low internal resistance and the current output to the individual circuit blocks is largely constant, further secondary stabilisation measures are unnecessary.

Also on the power supply card are the individual trimmers (focus, astigmatism, brightness) and the voltage multiplier for the tube supply, so that the tube (up to the deflection plates) can be connected directly from here by means of a six-way ribbon cable. The connections for the tube are made direct to the base. No socket is used, because the additional capacitance would considerably reduce the bandwidth.

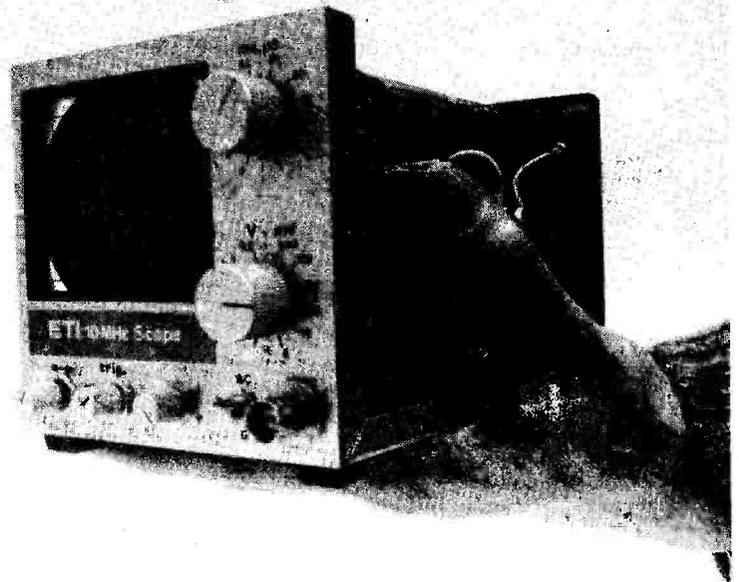A seven-way ribbon cable connects the main circuit board with the various supply voltages, and the



Now this is what we call small . . . .

(flyback) blanking pulse goes from the main board to the grid G1 of the tube. The main board contains the trigger switching, the sawtooth generator and the X- and Y-deflection amplifiers.

The three potentiometers mounted on the front panel (X- and Y-shift, trigger level) are connected by a five-way ribbon cable to the main or preamplifier boards, as appropriate. Similarly the time-base selector on the

front panel is connected by three single wires to the main board.

The input voltage divider forms a complete screened assembly, comprising switch SW1 and the voltage divider and preamplifier boards — thus no additional external wiring is required. The complementary output of the Y-amplifier passes to the Y-deflection amplifier on the main board.

## SPECIFICATION


**Bandwidth:** 0-7.5 MHz (−3 dB) for six divisions (one div = 7 mm)  
0-10 MHz (−3 dB) for four divisions.

**Input:** BNC connector, switchable AC/DC/ground.

**Sensitivity:** 5 mV/div to 20 V/div in 12 calibrated 1/2/5 steps.

**Case Size:** approximately 175 x 105 x 100 mm.

**Weight:** approximately 1 kg.

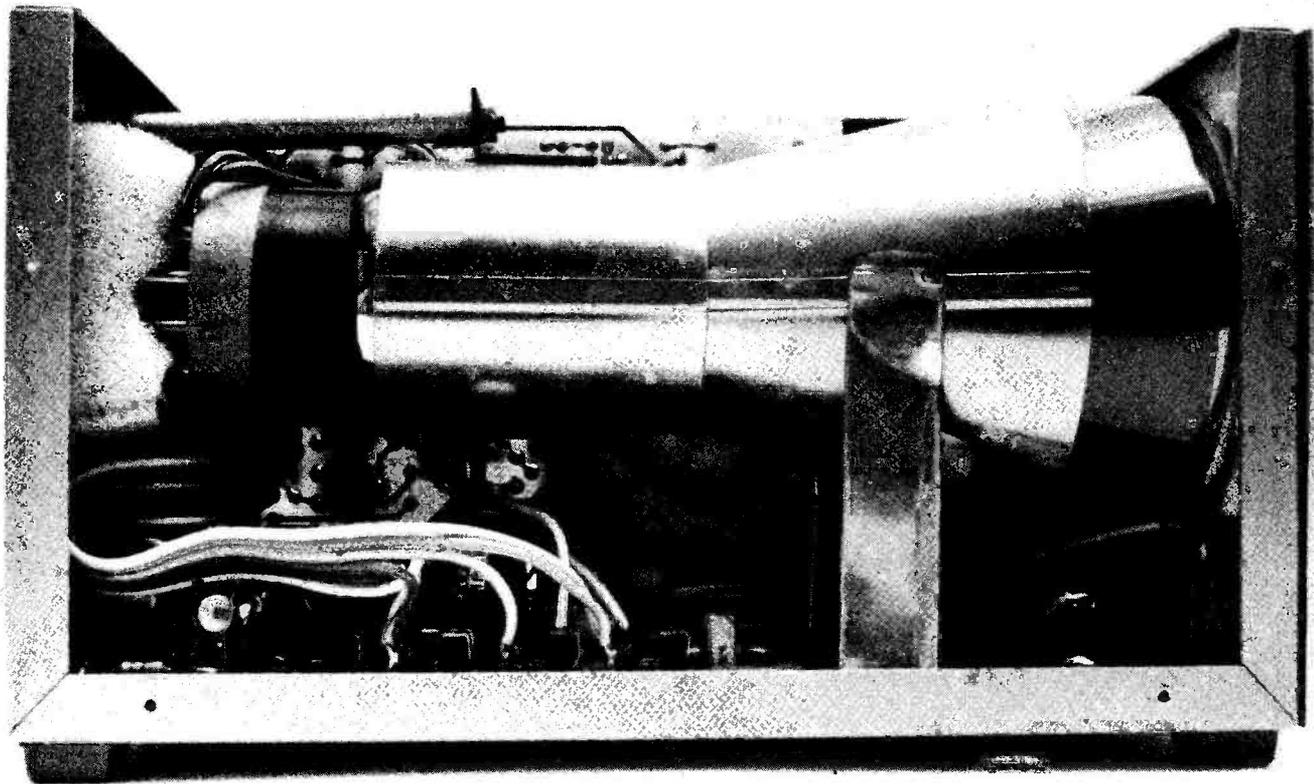

The tube is supported by its metal screen and cushioned by foam draught excluder. The power supply is mounted beneath it.

## HOW IT WORKS

### VOLTAGE DIVIDER AND PREAMPLIFIER

The input signal reaches the input voltage divider from the BNC connector and the mode selector SW2. After passing through the voltage dividers, the signal goes via R3 (over-voltage protection for Q1) to the gate of the dual FET Q1. The second gate of this transistor is connected to the Y-shift potentiometer RV1 and permits vertical shifting of the 0 V line on the screen. Any mismatch between the two halves of Q1 can be trimmed out by means of trimmer PR1. Q1, which is connected in the source-follower mode, serves merely to buffer the high impedance of the instrument input and the voltage divider from the low input impedance of the preamplifier IC1. The gain is fixed and determined by R12. Complementary output signals appear at Q and Q' and pass along single wires from here to the Y-deflection amplifier on the main board.

### MAIN BOARD

The two transistors Q2 and Q3 on the left of the diagram take care of the final amplification of the Q and Q' signals provided by the preamplifier. The amplified signal is connected to the Y and Y' deflection plates using short, single wires (lowest possible capacitance!) going directly to the base pins. The working point of the stage is adjusted by PR3, the gain by PR2. C10 and CV10 serve to linearise the frequency response.

The trigger signal is taken from Q1 via C8. Q4 and Q5 form a preamplifier whose working point is adjusted by the trigger level potentiometer, RV2. Q5 feeds the Schmitt trigger IC2a which con-

verts the input signal into rectangular pulses. These rectangular pulses are differentiated into 'spikes' by C17 and R43, and are fed to the 'set' input of the gating flip-flop (pin 4 of IC26). The gating flip-flop enables the sawtooth generator for one beam-sweep (in a horizontal direction on the tube).

In order that a 0 V line will be traced in the absence of an input signal (and therefore in the absence of the 'spikes') — for example, for direct voltage measurement, or for reference purposes with the input switch on 'G' — transistor Q6 is switched into conduction and thus gives a continuous 'set' condition. As long as rectangular pulses are present at the output pin 3 of the Schmitt trigger, they will be rectified by D1 and D2, generating a negative gate voltage for Q6, so that this stays non-conducting. Thus the 'Free-run/Automatic' Q6 only works when there are no trigger pulses available.

The output (pin 8) of the gating flip-flop switches on Q7. This provides base current — through R50 and PR4 — to transistor Q8, which is connected as a constant current source. The magnitude of the constant current which Q8 provides is determined by emitter resistors R44 to R49 (selected by the time base switch SW3). As soon as Q8 is switched on (by Q7) one of the two capacitors C19 or C20 will be charged (according to the position of the time base selector). Since this charging takes place from a constant current source, the voltage on the capacitor increases linearly with respect to time. This linear (sawtooth) voltage in-

crease is fed to the X-deflection transistors Q12/Q13 by Q9 and Q10, so that the X and X' deflection plates receive a linear beam sweep (from left to right on the screen). A part of this voltage is fed via R54/R55 to the input pin 12 of the reset trigger (IC2d). As soon as the sawtooth voltage attains such a level that the beam reaches the right hand side of the screen, pin 11 of IC2b switches low (approximately 0 V). This switches Q11 on, and also supplies G1 of the tube (via C24) with a negative-going, 40 V pulse, which blanks the beam. At the same time, the timing capacitor (C19 or C20) is discharged, which returns the beam (blanked during the flyback) to the left-hand side of the screen. Pin 11 of the reset trigger also drives the 'reset' input (pin 10) of the gating flip-flop. This switches off Q7 and Q8. As a result there will be no new beam sweep for the moment, while the current source Q8, which charges the timing capacitors, is switched off. A new sweep will only be initiated by a trigger pulse on the 'set' input pin 4, and this will occur at exactly the same point on the waveform of the input signal as for the preceding sweep. This ensures that successive traces in a continuous sequence are written on the screen in a uniform manner, provided that the input signal is not altered. Trimmer PR4 provides for calibration of the timing circuit (charging current adjustment), PR6 is the working point adjustment, and PR5 is the gain (picture width) control for the X-deflection amplifiers. The trace can be shifted from right to left on the screen, from the front panel, by RV3.


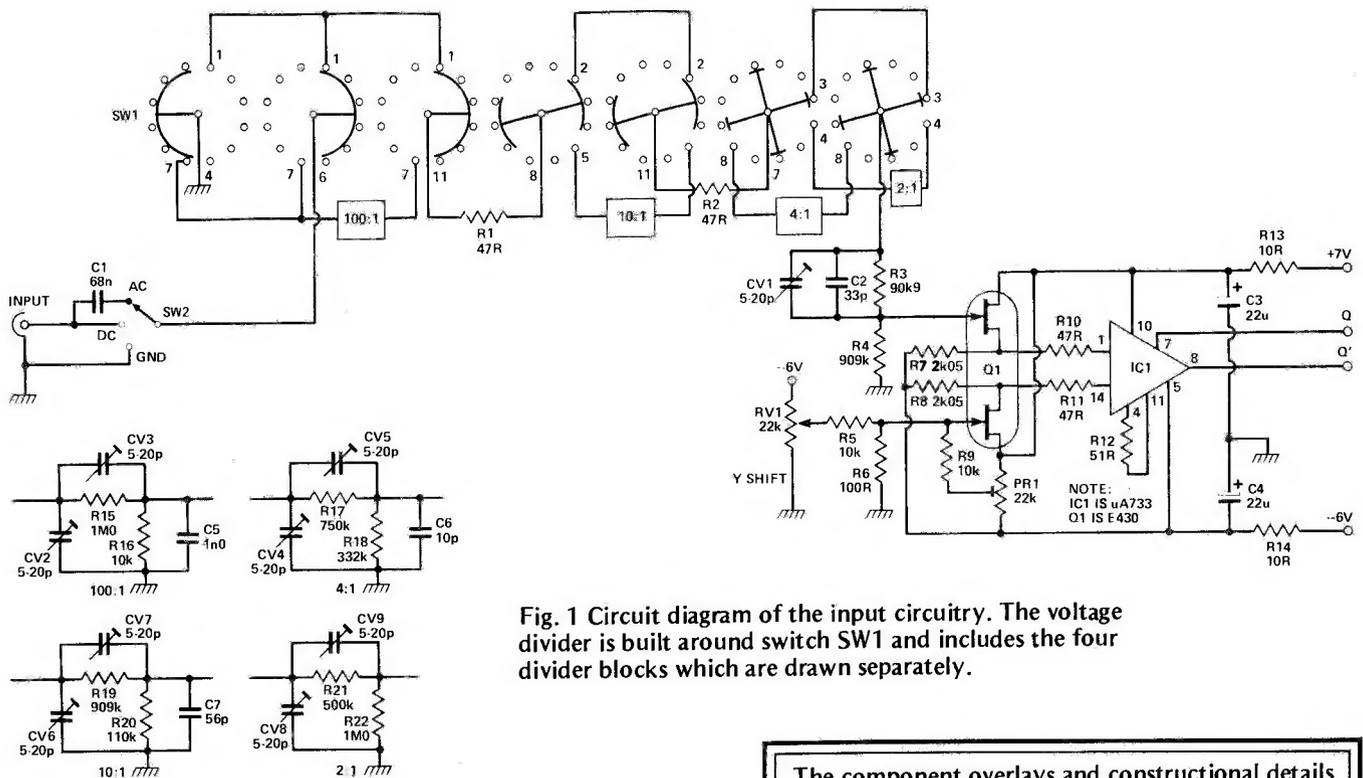


Fig. 1 Circuit diagram of the input circuitry. The voltage divider is built around switch SW1 and includes the four divider blocks which are drawn separately.

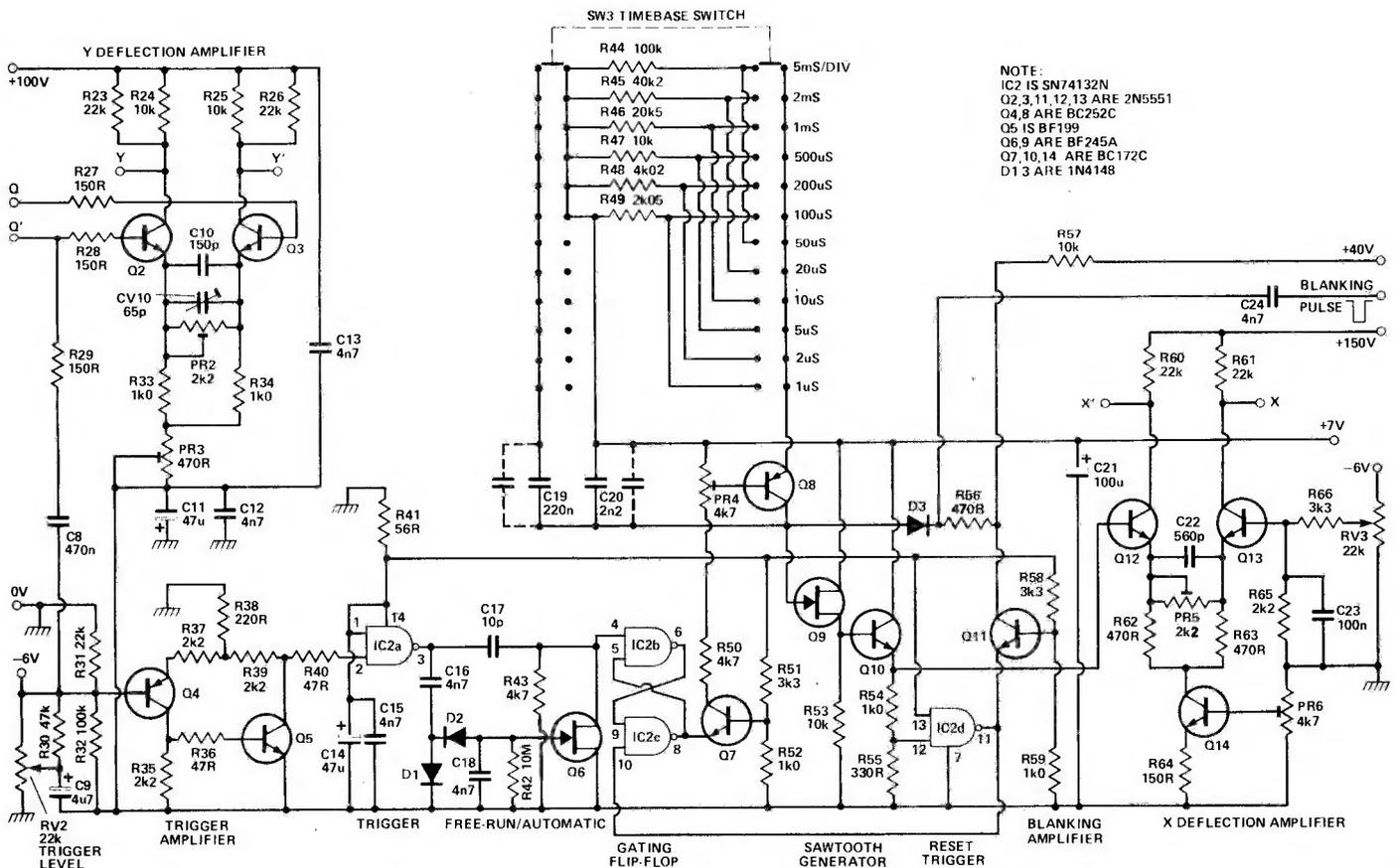The component overlays and constructional details for the oscilloscope will be given next month.



NOTE:  
 IC2 IS SN74132N  
 O2,3,11,12,13 ARE 2N5551  
 O4,8 ARE BC252C  
 O5 IS BF199  
 O6,9 ARE BF245A  
 O7,10,14 ARE BC172C  
 D1,3 ARE 1N4148

Fig. 2 Circuit diagram of the main board. The two dotted capacitors in parallel with C19 and C20 may be required for trimming purposes — this is covered next month.

Fig. 3 Circuit diagram of the power supply.

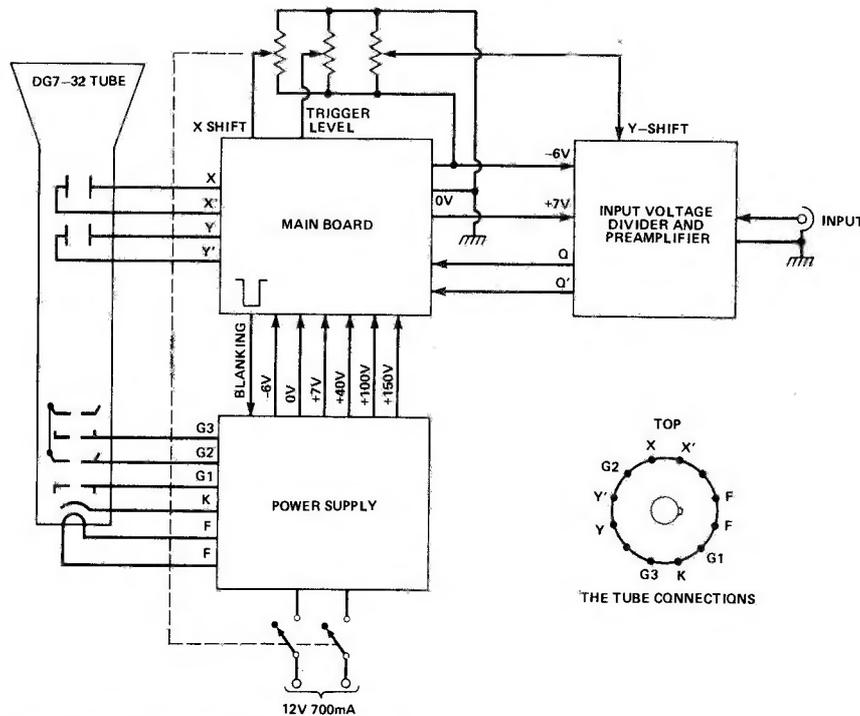
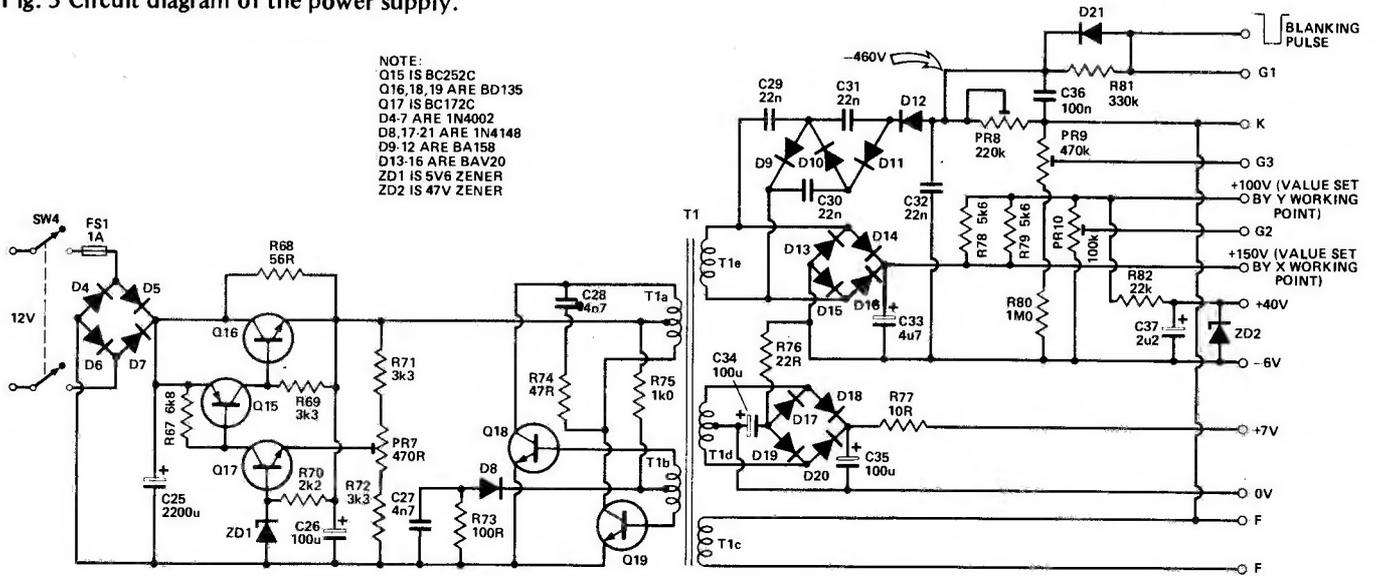


Fig. 4 Block diagram of the oscilloscope.

## HOW IT WORKS

### THE POWER SUPPLY

The incoming supply voltage from SW4 (coupled to the X-position potentiometer) and fuse FS1 is rectified by D4 - 7. These also ensure correct polarity of the input voltage in the case of a DC source. The supply voltage is stabilised to 10 V by Q15, Q16 and Q17. The constant and almost ripple-free voltage then passes to the transformer T1 and the 25 kHz oscillator formed by Q18 and Q19.



R73 limits the base current to Q18 and Q19. R74/C28 suppress switching voltage spikes. R75 in conjunction with D8 acts as a starting circuit (for the oscillation).

The tube heater voltage is generated by the transformer secondary winding T1c. Winding T1d delivers a 156 V square wave, which is rectified by diodes D13 - 16 and passed to the deflection amplifiers. Diodes D13-16 must be BAV20 and D9-12 must be BA158, as specified in the Parts List; on no account can ordinary bridge rectifiers or rectifier diodes (eg 1N400X) be used, as these are an order of magnitude too slow to rectify a 25 kHz signal.



The 156 V is reduced to 100 V (for the Y-deflection amplifier) by R78/R79. From this is derived, through PR10, the tube G2 voltage (astigmatism adjustment) and also the 40 V DC for the flyback switching, via R82 and ZD2. All the voltage values given in the circuit diagram are measured with respect to ground.

T1d also feeds the voltage multiplier (D9 - 12, C29 - 32) for the generation of the tube EHT supply of -460 V. This voltage is fed to a potential divider (PR8 - brightness, PR9 - focus, R80) on which the individual electrode potentials for the tube are available.


The +7 V and -6 V supplies are generated by T1e. The asymmetry of these voltages is a result of the different values of resistors R76 and R77. This is necessary for the supply to the preamplifier IC1, whose inputs, pins 1 and 14, sit at about +1 V. The supply (source voltage of Q1) is therefore sufficiently compensated that the positive voltage (on pin 10) is somewhat greater than the negative voltage on pin 5.

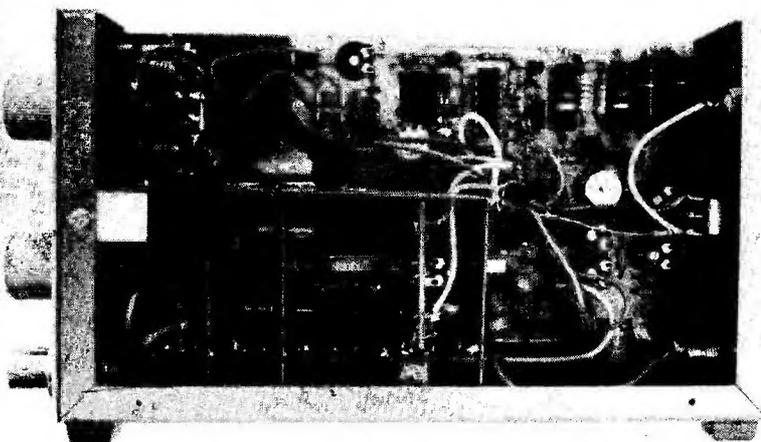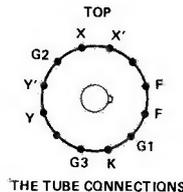


# THE CASE FOR

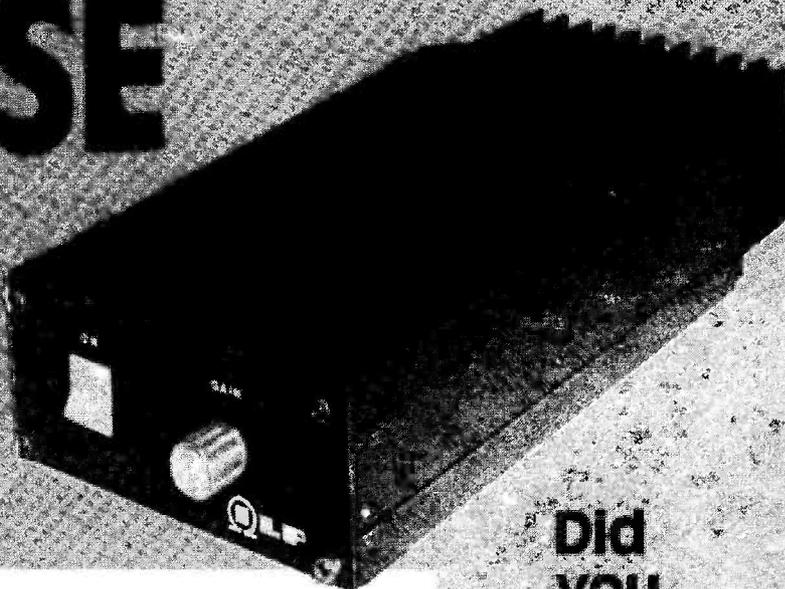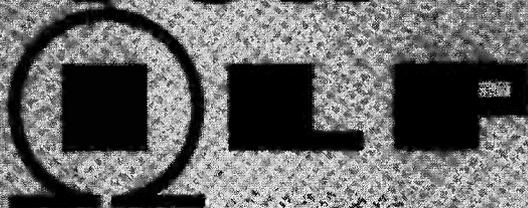
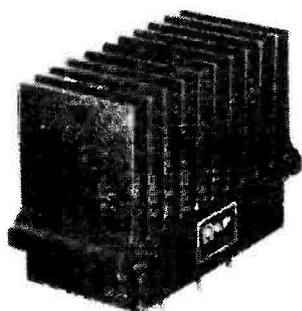
## It's the chance every constructor wants



**POWER AMPS**

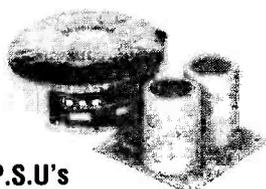

**P.S.U.'s**



**PRE-AMP MODULES**

It's something you have always wanted... something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

### WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN. It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



**FREEPOST 4**  
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP  
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

**FREEPOST**  
Mark your envelope clearly FREEPOST 4 and post it WITHOUT a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

### Did you know

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are TWENTY power amplifiers from 15 to 240 watts RMS including the very latest super-quality Modules to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?

**SEND COUPON**  
(NO STAMP NECESSARY)  
**FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE**

To: I.L.P. ELECTRONICS LTD.  
PLEASE SEND ME I.L.P. CATALOGUE,  
POST PAID BY RETURN

I HAVE/HAVE NOT PREVIOUSLY  
BUILT WITH I.L.P. MODULES

Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

*I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.*

TTL CMOS 74LS LEDs

# LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

**SUPERSALE '81**  
All full spec. brand new devices.  
2114 (450ns) £1.00, 4116 (200ns) £1.15, 2708 £1.85, 2516 (single rail) £3.00, NEC 2732 £5.50, 2532 £6.00, 2114 (200ns) £1.40. P/P 35p on above devices.  
Brand new and boxed, Lie Detector. Made for the Open University. size: 150mm (length) x 100mm (width) x 90mm (height). Complete with 100 microamp motor movement 90mm x 75mm. Supplied complete with leads and pads, less batteries (2 x 4.5v) £7.50 + £2 p/p.

**SELF-CONTAINED** battery powered digital recorders. Complete with data entry keyboard with 10 digit LED display plus modern interface and charger. Some data £25 per system. Sorry, callers only.

**ZETTLER** low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.5 amps a.c. contacts. 85p p/p 35p.

**D TYPE CONNECTORS**  
9 Way Socket (solder) 75p  
15 Way wirewrap plug £1.00  
37 Way Plug (solder) £1.80  
37 Way Socket (solder) £1.80  
25 Way Plug (solder) £1.85  
25 Way Socket (solder) £1.85  
25 Way Plug (insulation piercing) £2.85  
25 Way Socket (Insulation piercing) £2.85  
50 Way Plug (solder) £2.00  
P/P on above 35p

**COVERS**  
37 Way (Plastic) £1.00, 50 Way (Plastic) £1.20, 25 Way (Plastic) 95p, 25 Way (Metal) £1.25, 25 Way (Metal) ITT open £1.00, 15 Way (Plastic) 60p, 15 Way (Metal) 95p  
P/P on above 35p

**DISPLAYS**  
HP 5082/7414 digit DIL display full spec £1.50 each, p&p 35p. Large quantities POA.

HP5082/7650. 4"CA left and right decimal point, high brightness, only 65p, 12 for £6.60, p&p 35p

**SUPERSAVER 1**  
DIL header Plugs (No covers) 14 way 18p, 16 way 25p, 24 way 95p (all gold plated) p/p 35p.  
Anselv Header plugs. 14 Way 75p, 16 Way 95p, 24 Way £1.50. (Insulation piercing type) p/p 35p.  
Anselv I/O Header plugs PCB Mounting. 1in 26 Way straight 65p. 40 Way r/a £1 p/p 35p.

**SUPERSAVER 2**  
Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.

**SUPERSAVER 3**  
**PRICE SMASH** FND500 .5in. LED displays, full spec 65p each, p&p 35p. large quantities POA.

**SUPERSAVER 5**  
3M 34 way (17 x 17) .1" insulating piercing edge connectors for disc drives etc. £3.50 each, p/p 35p.

**SUPERSAVER 6**  
**VIDEO LEAD**  
1 1/2 metres with PL259 plug £1.00 p/p 35p

**SUPERSAVER 7**  
Thyristors Type 16 Ria 100 Vrrm 1000 Volts at 22 amps £1.65 each. Limited stock, p/p 35p  
Stud mounted rectifiers, type 40 HF 100 1250 volts, 40 amp, 4 for £2.60 p/p 35p

**SUPERSAVER 8**  
**ONE ONLY - TEXAS SILENT**  
700 TERMINAL RS232 110 baud. As new - £236. Carriage at cost.

**SUPERSAVER 9**  
**VELLEMAN EPROM** Programmer kit £200. Built £300 + VAT. S.A.E. for full descriptive leaflet.

**SUPERSAVER 10**  
Tangerine Microtan 65 Blank PCB. Brand new plus circuit diagram £4.50, p/p 50p (6502 based, 1K on board).

**SUPERSAVER II**  
**PAPST MINI-FAN** 3 3/4" x 3 3/4" x 1.5" deep. 220v 50Hz. Brand new and boxed. £9.50 p/p £1.00.

**SUPERSAVER 12**  
12.5mm power plug and 2 metres of cable. Suitable for Acorn Atom, ZX81 etc. Only £1.00 per 10 p/p 25p. Trade enquiries welcome.

**SUPERSAVER 14**  
**BOX FANS** 115V 50/60Hz. 120mm x 120mm. New. £4.50. 250V £6.50, P&P £1.00.

**SUPERSAVER 15**  
5K 3/4" multiton trimpots, PCB mounting, per box of 14 £2.50. As above 1K and 50K, p&p 35p.

**SUPERSAVER 16**  
**OPTRON OPTO SLOTTED SWITCH** (Type OPB-814) £1, p&p 35p.

**SUPERSAVER 17**  
**VU METER** 48mm x 50mm approx. overall size. Face size 50mm x 28mm approx. Brand new. £1.15 p&p 30p. (Sent at purchaser's risk).

**SUPERSAVER 18 SALE**  
**PCB AMP** (LM380). Unused. 65mm x 95mm approx. 9-12v DC. 85p p&p 35p.

**SUPERSAVER 19**  
10 DIGIT (Red). LED display. (.122in. digit size). With built-in driver chip and built-in lens magnifier. Data sheet supplied. Brand new. £1.50 p&p 35p.

**SUPERSAVER 20**  
4 1/2in. JUMPER LEAD. 16 DIL header to 16 DIL header. 95p p&p 30p.

**SUPERSAVER 21**  
2 1/2in. JUMPER LEAD. 14 DIL header to 14 DIL header. 65p p&p 30p.

**SUPERSAVER 22**  
11b reel of solder 18 SWG 64/36 alloy £5.60 p&p 90p.

**A TERRIFIC GIVEAWAY. MC 1489 RS232 RECEIVER.** Brand new 48p each. 10 for £3.50. Large quantities p.o.a. p&p 30p.

**SUPERSAVER 23**  
16K EPROM PCB 275mm x 18mm takes 8 x 4K eeproms + address decoder logic ranged as 16K x 16. Sorry no data. £3.50 p/p 30p.  
**JUST ARRIVED** large quantity of assorted Microwave Wave Guides, various bands + noise sources from £5. Callers only.

**MICRO REVOLUTION**  
The New Z8 Processor. Complete PCB and parts to produce this new CBU, built in tiny Basic and 4K Ram. RS232C output plus User Ports. Only 4.5" x 4.5" £85 + VAT. Further details SAE P/P £2.00. Motherboard plus Eprom Programmer to follow shortly.

**AUGAT IC SOCKETS**  
(The best available)  
16 DIL 20p 24 DIL 50p  
18 DIL 25p 40 DIL 55p

**WE STOCK** a vast range of TTL, CMOS, some 74LS. MINIATURE TOGGLES, etc.  
**PSUs.** We have a large stock of power supplies at very realistic prices (callers).

**NEW LINES**  
**UECL** Edge connector. 1" 75 Way gold plated (wire wrap) £1.65 each p/p 35p.

**REG PCB** (less components), 5V 1 amp, 12V 1 amp and heatsink (60mm x 90mm). Brand new, £1.00. Heatsink only, 55p. P/P 35p.

**NEC FIP4B13** 4 digit glass display (green with centre colons and plus and minus sign), only £1.35. P/P 30p.

**PL259 SOCKET CHASSIS MOUNT.** 50p p&p 30p.  
**TRANSFORMERS** 012, 024 1 amp £2.50, P&P 50p.  
**TTL SALE** 7410 9p, 7413 18p, 7416 18p, 7490 28p, 74155 45p, 74174 60p, 74181 74285 £2.25. P&P 35p.



**WHY PAY POUNDS? - Just arrived** Amphenol 36-way plug and socket (used) to fit all your printer. Only £2.75 per pair. P/P 35p.  
Terms cash with order (official orders welcomed from colleges, etc.). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

**STOP PRESS**  
2716 Single rail Eprom (used). Fully erased, replacement guaranteed. £1.95. 10 for £17.  
**P/P FREE**

**PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.**  
**SURPLUS STOCKS PURCHASED FOR CASH**

**LB ELECTRONICS**  
11 HERCIES ROAD  
HILLINGDON, MIDDLESEX  
UB10 9LS, ENGLAND  
All enquiries s.a.e. please  
Telephone answering machine service out of business hours.  
New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.  
ALL PRICES INCLUSIVE OF VAT  
**UXBRIDGE 55399**  
All components full spec

# New Products

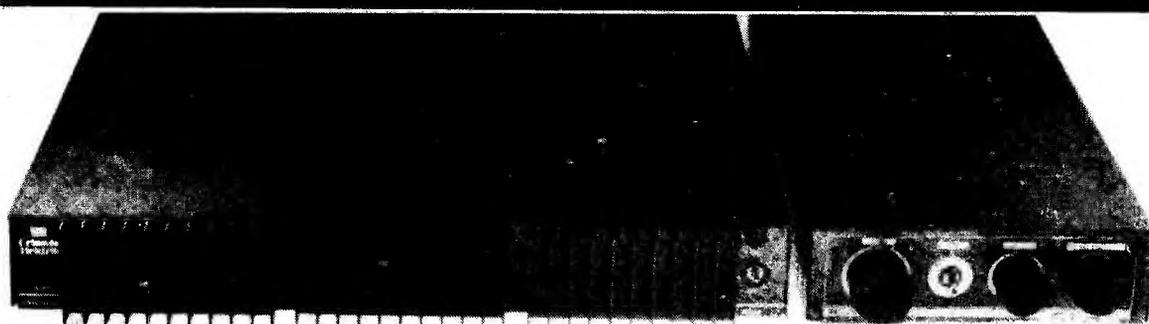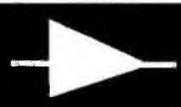

## HIFI STEREO AMPLIFIER KITS

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty.  
These new kits offer the choice of moving magnet or moving coil inputs, 40 to 100 watts per channel, in fact, everything that made the previous models so popular is included but with added style, easier construction and a full two year warranty.

The new range consists of The CK 1010 Stereo Pre Amplifier, The CK 1040 WPC Power Amplifier, The CK 1100 WPC Power Amplifier.

### CK 1010

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled and tested therefore construction is simply a matter of point to point wiring and mechanical assembly of the connections and controls to the pre punched chassis.  
The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

### CK 1040

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsinks, wire and connectors are included and protection is provided from short circuit outputs.

### CK 1100

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard.  
When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kit-build field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few - such as the KA-1000 (£500+) - are of comparable standard. . . . I can say no more than that for £250 it (CK 1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

**PRICES** CK 1010 - RRP £90.00; CK 1040 - RRP £119.00; CK 1100 - RRP £149.00; MC2K - RRP £25.000; PSK - RRP £20.00

Barclaycard or Access accepted, otherwise send C.W.O. C.O.D. £1.00 extra. All prices include P&P to anywhere in the U.K. Export: Write for pro-forma



# Crimson Elektrik

**FREEPOST, 9 CLAYMILL ROAD  
LEICESTER LE4 5ZD. ENGLAND  
TEL. 0533 761920, TLX 34694**

# MICROCOMPUTER COMPONENTS

## LOWEST PRICES - FASTEST DELIVERY

Device	Price	Device	Price	Device	Price	Device	Price
<b>MEMORIES</b>		<b>REGULATORS</b>					
2114L-200ms	1+0.93	7805	0.30	4012	0.15	74LS11	0.12
25+0.89		7812	0.30	4013	0.29	74LS12	0.12
2114L-300ms	1.95	7815	0.30	4014	0.58	74LS13	0.22
(FOR ACORN ATOM)		7818	0.29	4015	0.58	74LS14	0.39
2708 450ms	1+2.25	78L05	0.29	4017	0.25	74LS15	0.12
25+1.99		78L12	0.29	4018	0.45	74LS20	0.12
2716 450ms	1+2.49	78L15	0.25	4019	0.58	74LS21	0.12
(single +5V)		7905	0.58	4020	0.29	74LS22	0.12
25+2.29		7912	0.55	4021	0.58	74LS26	0.15
2716 350ms	0.95	7915	0.55	4022	0.60	74LS27	0.12
25+4.25				4023	0.62	74LS28	0.15
2732 450ms	1+3.99	79L05	0.50	4024	0.17	74LS30	0.12
25+3.80		79L15	0.50	4025	0.35	74LS32	0.12
2732 350ms	7.50	LM309K	0.99	4026	0.18	74LS33	0.16
4116 200ms	+0.74	LM317K	3.20	4027	0.99	74LS37	0.15
100+0.87		LM323K	4.95	4028	0.30	74LS38	0.15
		LM338K	4.75	4029	0.55	74LS40	0.12
				4031	1.85	74LS42	0.34
				4033	1.60	74LS47	0.39
				4034	1.55	74LS48	0.60
				4035	0.72	74LS49	0.59
				4036	0.54	74LS51	0.14
				4041	0.69	74LS54	0.15
				4042	0.54	74LS55	0.15
				4043	0.59	74LS73	0.19
				4044	0.64	74LS74	0.16
				4045	1.85	74LS75	0.24
				4046	0.68	74LS76	0.20
				4047	0.68	74LS78	0.19
				4048	0.54	74LS83	0.44
				4049	0.26	74LS85	0.65
				4050	0.28	74LS86	0.15
				4051	0.59	74LS90	0.30
				4052	0.66	74LS91	0.75
				4053	0.59	74LS99	0.34
				4054	1.20	74LS93	0.34
				4055	1.20	74LS95	0.43
				4060	0.79	74LS109	0.21
				4063	0.95	74LS112	0.21
				4066	0.34	74LS113	0.23
				4068	0.17	74LS114	0.19
				4069	0.17	74LS122	0.39

# FREE OFFER

With each order with a value in excess of £20

- \* 20 page Component Catalogue
- \* Reply Paid Envelope
- \* Voucher Value £1 (redeemable against future orders over £20)


Device	Price	Device	Price	Device	Price	Device	Price
<b>DATA CONVERTERS</b>		<b>8080 FAMILY</b>		<b>74LS SERIES</b>			
ZM425E-8	3.45	8080C	11.80	74LS00	0.10	74LS243	0.79
ZM426E-8	3.00	8080J	9.99	74LS01	0.11	74LS244	0.85
ZM427E-8	5.99	8080L	10.99	74LS02	0.12	74LS245	0.99
ZM428E-8	4.75	8080M	12.50	74LS03	0.12	74LS247	0.83
ZM429E-8	2.10	8080N	11.99	74LS04	0.12	74LS248	0.83
ZM432CJ-10	28.99	8080P	11.99	74LS05	0.13	74LS249	0.83
ZM433CJ-10	2.59	8080Q	10.99	74LS06	0.12	74LS251	0.40
*M440	58.83	8080R	10.99	74LS07	0.12	74LS252	0.40
ZM432E-10	14.75	8080S	5.50	74LS08	0.12		
ZM447	9.14	8080T	1.70	74LS09	0.85		
ZM448	6.85	8080U	1.70	74LS10	0.99		
ZM449	3.20	8080V	1.70	74LS11	0.99		
		8080W	1.70	74LS12	0.99		
		8080X	1.70	74LS13	0.99		
		8080Y	1.70	74LS14	0.99		
		8080Z	1.70	74LS15	0.99		
		8080AA	1.70	74LS16	0.99		
		8080AB	1.70	74LS17	0.99		
		8080AC	1.70	74LS18	0.99		
		8080AD	1.70	74LS19	0.99		
		8080AE	1.70	74LS20	0.99		
		8080AF	1.70	74LS21	0.99		
		8080AG	1.70	74LS22	0.99		
		8080AH	1.70	74LS23	0.99		
		8080AJ	1.70	74LS24	0.99		
		8080AK	1.70	74LS25	0.99		
		8080AL	1.70				
		8080AM	1.70				
		8080AN	1.70				
		8080AO	1.70				
		8080AP	1.70				
		8080AQ	1.70				
		8080AR	1.70				
		8080AS	1.70				
		8080AT	1.70				
		8080AU	1.70				
		8080AV	1.70				
		8080AW	1.70				
		8080AX	1.70				
		8080AY	1.70				
		8080AZ	1.70				
		8080BA	1.70				
		8080BB	1.70				
		8080BC	1.70				
		8080BD	1.70				
		8080BE	1.70				
		8080BF	1.70				
		8080BG	1.70				
		8080BH	1.70				
		8080BI	1.70				
		8080BJ	1.70				
		8080BK	1.70				
		8080BL	1.70				
		8080BM	1.70				
		8080BN	1.70				
		8080BO	1.70				
		8080BP	1.70				
		8080BQ	1.70				
		8080BR	1.70				
		8080BS	1.70				
		8080BT	1.70				
		8080BU	1.70				
		8080BV	1.70				
		8080BW	1.70				
		8080BX	1.70				
		8080BY	1.70				
		8080BZ	1.70				
		8080CA	1.70				
		8080CB	1.70				
		8080CC	1.70				
		8080CD	1.70				
		8080CE	1.70				
		8080CF	1.70				
		8080CG	1.70				
		8080CH	1.70				
		8080CI	1.70				
		8080CJ	1.70				
		8080CK	1.70				
		8080CL	1.70				
		8080CM	1.70				
		8080CN	1.70				
		8080CO	1.70				
		8080CP	1.70				
		8080CQ	1.70				
		8080CR	1.70				
		8080CS	1.70				
		8080CT	1.70				
		8080CU	1.70				
		8080CV	1.70				
		8080CW	1.70				
		8080CX	1.70				
		8080CY	1.70				
		8080CZ	1.70				
		8080DA	1.70				
		8080DB	1.70				
		8080DC	1.70				
		8080DD	1.70				
		8080DE	1.70				
		8080DF	1.70				
		8080DG	1.70				
		8080DH	1.70				
		8080DI	1.70				
		8080DJ	1.70				
		8080DK	1.70				
		8080DL	1.70				
		8080DM	1.70				
		8080DN	1.70				
		8080DO	1.70				
		8080DP	1.70				
		8080DQ	1.70				
		8080DR	1.70				
		8080DS	1.70				
		8080DT	1.70				
		8080DU	1.70				
		8080DV	1.70				
		8080DW	1.70				
		8080DX	1.70				
		8080DY	1.70				
		8080DZ	1.70				
		8080EA	1.70				
		8080EB	1.70				
		8080EC	1.70				
		8080ED	1.70				
		8080EE	1.70				
		8080EF	1.70				
		8080EG	1.70				
		8080EH	1.70				
		8080EI	1.70				
		8080EJ	1.70				
		8080EK	1.70				
		8080EL	1.70				
		8080EM	1.70				
		8080EN	1.70				
		8080EO	1.70				
		8080EP	1.70				
		8080EQ	1.70				
		8080ER	1.70				
		8080ES	1.70				
		8080ET	1.70				

# TECH TIPS
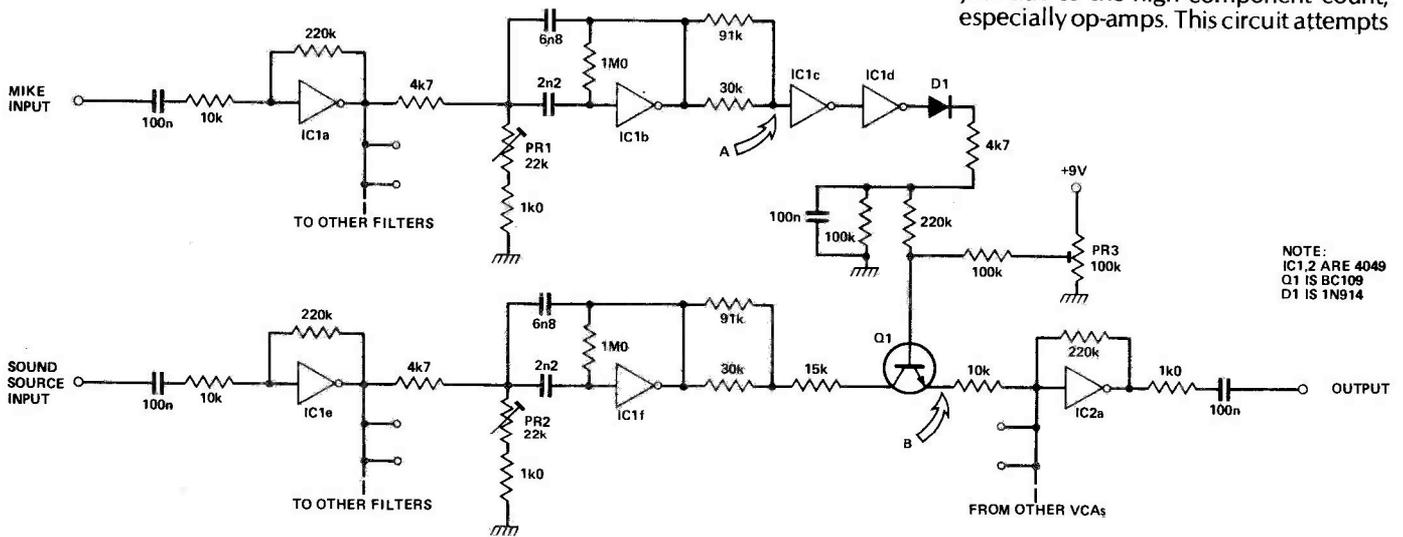
## Economy CMOS Vocoder

S.P. Giles, Edmonton


The principle of the vocoder has been well covered in ETI in the past but it is very expensive to construct such a project due to the high component count, especially op-amps. This circuit attempts



NOTE:  
IC1,2 ARE 4049  
Q1 IS BC109  
D1 IS 1N914

Fig. 1 Circuit of one channel of the CMOS vocoder.

Fig. 2 Several channels are connected in parallel to form the complete vocoder.

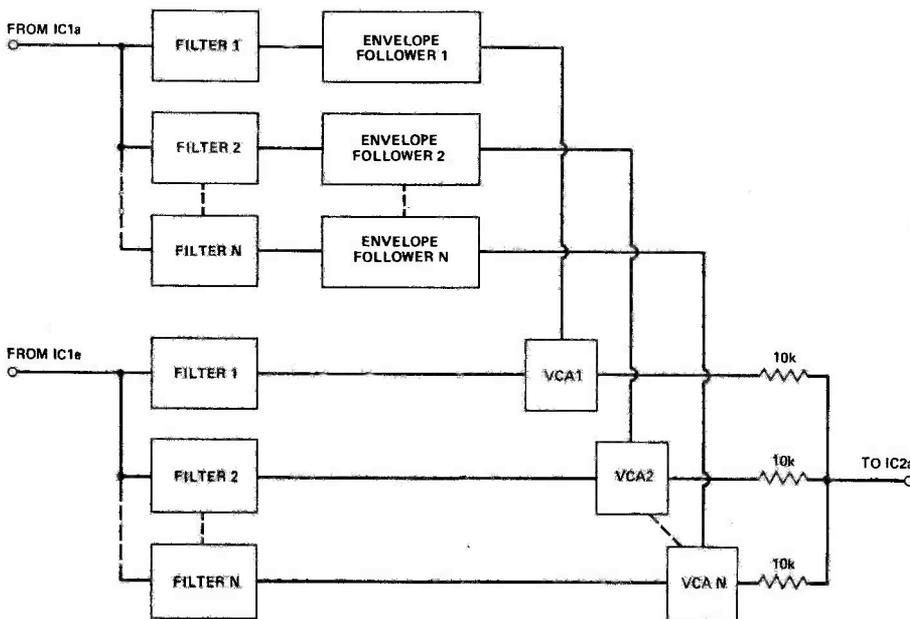

to bring the vocoder nearer the pockets of those who would not normally have sufficient funds. CMOS inverters are used instead of op-amps for cheapness.

The signal to be analysed, normally the human voice, is fed into the mike input and amplified by inverter IC1a. IC1b, a bandpass filter, allows a very narrow band of the input through. The centre frequency of this band is determined by PR1. The amount of energy present in this narrow band is measured by an envelope follower consisting of inverters IC1c, d and D1.

If a sound source is connected to the other input it is necessary to transfer on to it the energy present at point A. This is done by Q1, a voltage-controlled amplifier with the level set by the envelope follower voltage. PR3 should be adjusted for zero output at point B with no input. Inverter IC2a is a simple mixer for all the VCA outputs.

The second diagram shows how the filter bank is built up. It is suggested that a minimum of 20 channels be used to get the best results. In this case PR1 and PR2 should be set to approximately 1k2 intervals from one channel to the next. The greater the number of channels the better the results.

Tech-Tips is an advice column and is not aimed at the beginner. We regret we cannot give comments on these items. ETI is prepared to consider requests for technical information, but all correspondence should be paid for at a convenient rate. Diagrams should be clearly drawn and the text should be legible. All correspondence should be sent to the Editor, ETI, 1000 Birchmount Road, Toronto, Ontario, Canada M1G 1A2. Circuits may not be reproduced without the permission of the Editor.



# BI-PAK BARGAINS

## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All type" Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm-2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.

\*Quantities approximate, count by weight.

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1p-56p	£1
SX19	100	Mixed Ceramics 60p-0.5m1	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000mf	£1
SX24	20	Tantalum Beads, mixed	£1

\*Quantities approximate, count by weight.

## AUDIO PLUGS, SOCKETS AND ACCESSORIES

**25** pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240°. In-line 3-6 Pin. Speakers, Phono, Jack, Stereo and Mono, etc. etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

SX26	3 Pks of 6 pin 240° DIN Plugs and Chassis Sockets	50p
SX27	1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket.	30p
SX28	4 Phono plugs and 2 dual phono connectors	30p
SX29	1 x 2.5mm Plug to 3.5mm Socket adaptor	20p
SX30	1 x 3.5mm Plug to 2.5mm Socket adaptor	20p
SX31	1 x 3.5mm Plug to Phono Socket adaptor	20p

## BARGAINS

SX42	20 small .125 Red LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded. New	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm	50p
SX49	20 Assorted Slider Knobs Black/Chrome, etc.	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

## TRIACS — PLASTIC

4 AMP — 400v — T0202 — TAG 136G		
1 OFF	10 OFF	50 OFF
40p	£3.75	£17.50
8 AMP 400v — T0220 — TAG 425		
60p	£5.75	£27.50
		£50.00

**2N3055** The best known Power Transistors in the World — 2N3055 NPN 115w. Our BI-PAK Special Offer Price:

10 off	50 off	100 off
£3.50	£16.00	£30.00

**80312** COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055.

Equivalent M12955 — 80312 — T03

SPECIAL PRICE £0.70 each

10 off £6.50

## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish! all identifiable and valued in current catalogues as well over £25.00. Our Fight Against Inflation

— Beat the Budget  
— Down with Depression

Price —  
**JUST £6.50.**

Or no SX85

## £1 FREE PAK

Get a £1 FREE PAK. Orders over £10 excluding VAT. Choose £1 Pack free (or 2 x 50p) add it to your order and save even more money.

This offer only applies to this advertisement

*Guarantee*  
Satisfaction or your money back has always been BI-PAK's GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received.

## MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours.	£1.
SX58	25 Assorted TTL Gates 7400 Series. 7401-7460	£1
SX59	10 Assorted Flip Flops and MSI TTL	£1.
SX60	20 Assorted Slider Potentiometers	£1
SX61	25 Assorted Potentiometers. Rotary, Dual, etc.	£1
SX62	40 Assorted Pre-Sets Hor/Vert etc.	£1
SX79	10 Reed Switches — glass type 3 Micro Switches — with lever	£1

## STILL MORE!

### SLIDER POTENTIOMETERS

SX63	5 x 470 ohms Lin	SX67	5 x 47k Lin
SX64	5 x 1k Lin	SX68	5 x 47k Log
SX65	5 x 22k Lin	SX69	5 x 100k Lin
SX66	5 x 22k Log	SX70	5 x 1 meg Lin

All at 50p per pack.

SX71 50 BC108 "Fallouts". Manufacturers out of spec on volts or gain. You test. £1

SX72 A mixed bundle of Copper clad Board. Fibre glass and paper. Single and double sided. A fantastic bargain. £1

SX78 Genuine MULLARD OC71 Germanium PNP Transistors. Brand New 10 for £1

## 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncoded — you select for VLTS ALL perfect devices — NO Duds Min 50v 50 for £1.00 — worth double ORDER NO. SX76

Silicon General Purpose NPN Transistors TO-18 Case Lock fit leads — coded CV7644 Similar to BC147 — BC107 — Z89 ALL NEW! VCE 70v IC500mA Hfe 75-250 50 off 100 off 500 off 1000 off

PRICE: £2.00 £3.80 £17.50 £30.00

Silicon General Purpose PNP Transistors TO-18 Case Lock fit leads coded CV9507 similar 2N2905A to BF330 VCE 60 IC 600mA Min Hfe 50 ALL NEW! 50 off 100 off 500 off 1000 off

PRICE: £2.50 £4.00 £19.00 £35.00

## BI-PAK'S OPTO BARGAIN OF THE YEAR!

Valued at over £10—Normal Retail—we offer you a pack of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow and Clear. 7 Segment Displays both Common Cathode and Common Anode PLUS bubble type displays—like DL-33 Photo Transistors—similar to OCP71 Photo Detectors—like MEL11-12 This whole pack of 25 devices will cost you just

**£4.00**

AND we guarantee your money back if you are not completely satisfied. FULL data etc included  
**Order No. SX57.**

## The Third and Fourth Hand...

... you always need but have never got until now! This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2 diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 £5.50 Without magnifier ORDER NO. T400 £4.75

## MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points

Charges —	Power
PP3 (9V)	220-240V AC
U12 (1.5V penlite)	Dims —
U11 (1.5V C)	210 x 100 x 50mm
U2 (1.5V D)	

**POWER SUPPLY OUR PRICE £3.25**

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug. Input — 240V AC ~0Hz Output 3.4 5 7.5 9 & 12V DC. Rating — 300 ma MW88

## 5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification  
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz — 3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price

**£2.25**

You could not build one for this price.

## BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p

# BI-PAK

Send your orders to Dept ET1.5 BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST, WARE HERTS  
TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRD 388 7005  
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order. Total Postage add 75p per total order.

# SOUND EFFECTS 3

The SN76488 is pretty versatile. So is our sound effects PCB. Hence their return this month with two new noises to astound and amaze, the first being a phasor and explosion. Design by Phil Wait.

This combines a 'phasor' effect and the explosion effect employed in the Bomb Drop and Explosion unit last month. One could liken the sound produced to what you would expect after shooting down a 'flying saucer' or something! This project uses about as many components as the Bomb Drop and Explosion board.

The SLF sweeps the VCO up and down in pitch at quite a rapid rate — the push-button is held down to start the effect, which takes several seconds to complete. The explosion is heard following a period of the phasor sound. As with the other units, if you wish to vary any of the parameters of the effect it is best to vary the resistor values.

Take care with the orientation of the electrolytic and tantalum capacitors during construction. Note that, as with the Bomb Drop and Explosion unit, there are two links on the board; make sure you don't miss the small link at the 'notch' end of the IC.

## PARTS LIST

Resistors (all 1/4W, 5%)

R1,5 470k  
R2 100k  
R3 150k  
R4 220k

Capacitors

C1,2,5 4u7 16 V PCB electrolytic  
C3 4n7 polycarbonate  
C4 470p ceramic  
C6 100u 16 V PCB electrolytic

Semiconductors

IC1 SN76488

Miscellaneous

PB1 SPST push-button switch  
PCB (see Buylines); 50 mm diameter 8 ohm speaker; PP3 battery and clip.

## BUYLINES

The SN76488 is available from Technomatic at a price of £3.50, while the PCB (identical to last month's one) will cost £1.80 from our PCB Service (see page 45) if you don't want to etch it yourself. Everything else is pretty run-of-the-mill.

## HOW IT WORKS

This unit is closely related to the Bomb Drop and Explosion. In fact, if you compare the two circuits you will find very little difference! In this unit the SLF is programmed to oscillate at several Hertz and the triangle wave output employed to control the VCO frequency. Thus the VCO is swept up and down in frequency several times per second. This creates the phasor sound. The explosion is triggered after the phasor sound runs for a few seconds, the whole sequence being controlled by the System Inhibit block in much the same way as done in the Bomb Drop and Explosion unit.

When PB1 is pressed, a high (+5 V) is applied to the input of the System Inhibit block, pin 9. This triggers the One Shot timing period, starting the SLF oscillating. This sweeps the VCO up and down as explained above and the signal passes to the speaker through the Mixer, Envelope Generator (which is inoperative at this time) and amplifier stages. When the One Shot completes its timing period the Envelope Select Logic becomes operative, the SLF is disabled and the Envelope Generator commences to do its thing. The Mixer now selects the Noise Generator/Filter output and the sound is heard to decay away, simulating an explosion.

The oscillation frequency of the SLF is determined by R2 and C2, while that of the VCO is determined by R3 and C3. The One Shot timing period is determined by R1 and C1, while the noise characteristic is determined by R4 and C4 on the Noise Filter programming pins (pins 5 and 6).

Audio output is coupled to the speaker via the obligatory 100uF electrolytic capacitor, C6.

Fig. 1 Circuit for the Phasor and Explosion effect.


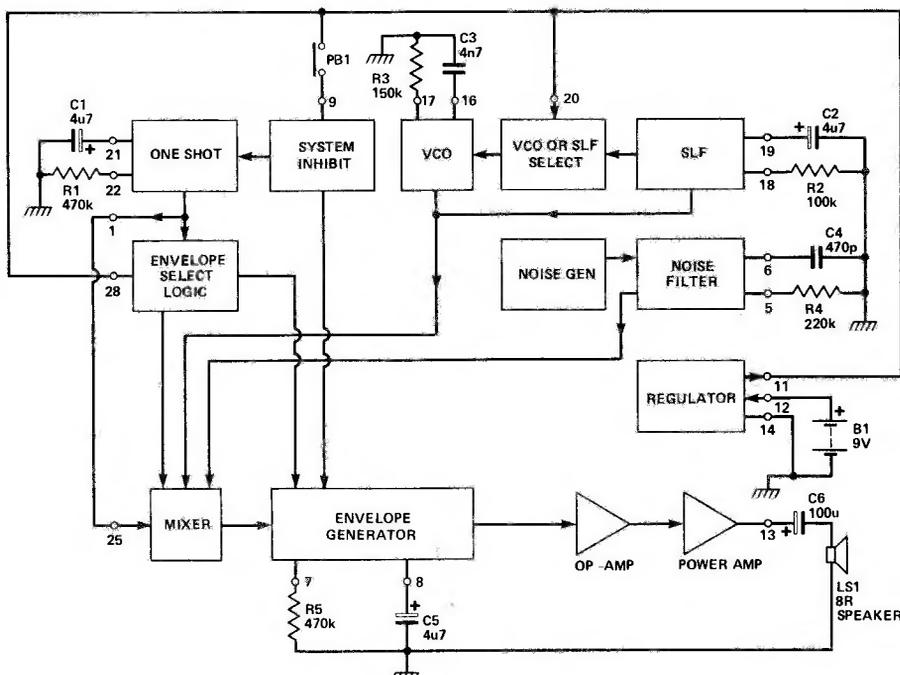


Fig. 2 Component overlay for this project.

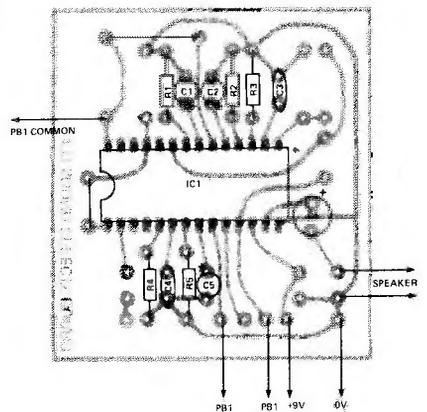

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL

LONDON'S TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY



**CROTECH 3035 10 MHz Scope Plus Component Tester**

5" - 130mm Flat Face Tube DC - 10 MHz  
5mV/DIV 220/240V AC Trig. to 20 MHz

SAVE £21 PLUS

As advertised by us at £189.75 inc VAT  
**NOW £168.50** inc.VAT  
(UK c/p £3.50) Exclusive to Audio Electronics

**PROFESSIONAL 100 K OHM/VOLT MULTIMETER**


30 ranges 15A AC/DC  
1.5 KV, 200 meg ohms.

Features mirror scale, polarity reverse, electronic overload protection, taut band suspension.

As advertised by us at £67.50 + case i.e. £84.00

**NOW £49** Inc. VAT  
(UK c/p £1.50) with leather case Exclusive to Audio Electronics

SAVE £35

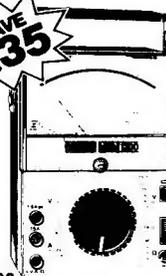

**LCD LOW COST MULTIMETERS**


D0801 3 1/2 digit LCD 26 range push button 2A AC/DC 20 meg ohm basic 0.5% £36.50  
HCT80 8 1/2 digit version of above £54  
D10011A/180m 3 1/2 digit LCD 15 range push button plus Hfe Tester 10A DC (No AC A) £43.50  
180m 3 1/2 digit LCD 30 range Rotary switch plus Hfe Tester 10A AC/DC £68.95

Callers will always find a range of low cost test equipment accessories, tools, irons and boards in stock, also special offers for certain equipment which will vary from time to time

Price correct at time of preparation E&OE  
All prices include VAT

CHOOSE FROM UK'S LARGEST RANGE

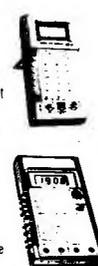**STOP PRESS** Few only 6110 23 range 10A AC/DC range hold continuity buzzer plus much more Rotary switch £59.95



**SABTRONICS EQUIPMENT NEW LOW PRICES!!**

New reliable range of DMM's and frequency computers with those extra facilities and competitive prices. All battery operated (supplied). Except 5020A mains. Optional mains eliminators available.

**8 DIGIT COUNTERS** 0.1 Hz to 10 Hz Res 10mV sensitivity to 100 MHz (UK c/p £1.00)

8110A 20 Hz-100 MHz in 2 ranges £77.00  
8610A 20 Hz-600 MHz in 3 ranges £94.00

**9 DIGIT COUNTERS** 30mV sensitivity to 1GHz. Resolution 0.1 Hz-10 Hz

8610B 10 Hz-600 MHz in 3 ranges £113.85  
8000B 10 Hz-1GHz in 3 ranges £178.00

**FUNCTION GENERATOR** (UK c/p £1.00) with mains adaptor

5020A 1 Hz-200 KHz Sine/Square/Triangle/TTT Freq. sweep. Low distortion £90.00

**DIGITAL MULTIMETERS** Two LCD hand held - one with temperature range. Also LCD and LED Bench models. 0.1% basic accuracy.

2035A 3 1/2 digit LCD hand 2A AC/DC 20Meg ohm ETC £71.00  
2037A As 2035A with -50°C to +150°C Temp. range 0.1°C resolution £77.00  
2010A 3 1/2 Digit LED Auto decimal & minus. 10A AC/DC. 20Meg ohm etc. £81.50  
2015A LCD version of above £95.00

C/P 2935/37A 65p  
All others £1.00

THP20 Touch and Hold Optional probe for DMM's £14.95



**HAMEG OSCILLOSCOPES**


Range of top quality scopes for Amateur and Professional (UK c/p 307 £3.00 other £4.00)

307 Single trace 10 MHz. 5mV. 0.5 micro sec. Plus built in component tester 6 x 7cm display £158.70  
(Optional carry case £18.40)

203 Dual 20 MHz. Trig to 30 MHz 5mV. 0.5 micro secs 8 x 10cm display (replace model 312) £253.00  
412-5 Dual 20 MHz delayed sweep: trig to 40 MHz. 5mV 0.1 micro sec 8 x 10cm display £402.50  
705 Dual 70MHz Delayed sweep: Single sweep: Delay line: Trig to 70MHz: 2mV: 0.1 micro sec. 8 x 10cm display £667.00

Options: 203/412/705 Viewing hood £6.90  
Component tester 203, 412, 1206 £46.00  
Carry case (state model) £21.85

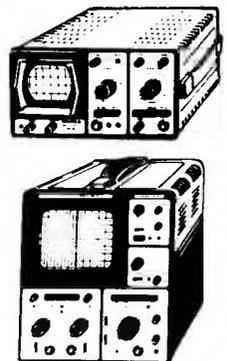Optional Probes (All models) X1 £7.95: X10 £9.45  
X1-X10 £10.50: X100 £16.95  
HZ65 Add on component tester - Any Scope £29.95




**RF AND AUDIO SIGNAL GENERATORS** Mains operated (UK c/p £1.00)

Audio 20 Hz-200 KHz 4 band. Sine/Square o/p

TE220 Distortion max 1% £69.95  
LAG26 Distortion 0.5-1% leader £73.70  
LAG120A 5 range 10 Hz-1 MHz. Size/sq. 0.05-0.8% DIS £146.00  
LAG125 Low distortion version of LAG120A 0.02% £273.00  
AG202A Distortion 0.5-1% Trio £78.20  
AG203 10Hz-1 MHz 5 band max distortion 0.1% Trio £126.50

RF All feature Int/Ext. MOD. Variable output

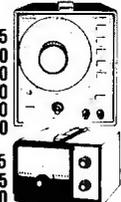TE20D 100 KHz-100 MHz 6 band (300 MHz harmonics) £59.95  
LS616 100 KHz-100 MHz 6 band (300 MHz harmonics) Leader £63.25  
SG402 100 KHz-30 MHz 6 band professional trio £68.00



**VARIABLE AND FIXED POWER SUPPLIES** (UK c/p £1.00 any model).

SPECIAL PURCHASE 1206 13.8v 6 to 8 amp £13.95

\*PP241 0/12-12-24V 0/1 amp £35.00  
\*PP243 0/12-12/24V 0/3 amp £59.95  
\*RP154 5-15V 0/3 amp £49.95  
\*meter display



**THURLBY DIGITAL MULTIMETER MODEL 1503**

4 1/2 Digit. 0.05% 7 Function LCD  
30 ranges: 1200V DC, 750V AC, 10A AC/DC, 32 Meg ohm. Also includes frequency measurement to 4MHz and 4KHz output. Made to exacting standards in the U.K.

Price is with batteries, test leads and mains adaptor.  
(optional carry case £20.45)

**£171.00**  
UK c/p £1.00



**AMATEUR/CB TESTING** - Full lists send SAE

KDM6 1.5 to 250 MHz 6 range DIP meter £47.95  
HM20 20K/VOLT multirange multimeter. Plus SWR/Power meter. 150 MHz £28.95  
RC1000 0/10/100/1000 watts SWR etc. 150 MHz max. £52.50  
MJ666A 10 ch. Pocket 2 metre scanner £69.00  
MJ666M Marine band version £69.00

UH74 SWR 0/10w Power. 0/50/144/430 MHz tester. £21.00  
FC100M 12V 100 MHz Freq. Counter £69.95

**SPECIAL CB ACCESSORY PURCHASES** (Post 55p)

CB20 SWR/Power twin meter to 30 MHz 1Kw £11.95  
175 SWR/Field strength/aerial matcher single m. £11.95  
171 Twin meter SWR/Field strength 0/10/100w £11.95  
Power 144 MHz £11.95  
1206 13.8v 6 to 8 amp regulated power supply (post £1.00) £13.95

Just a selection of a huge range in stock - send for latest lists including professional ranges.




**PROFESSIONAL MULTIMETERS** (UK c/p £1.50)

All featuring AC/DC Volts/Current & Ohms ranges.

M1500 43 range 20K/Volt: AC/DC 10A £67.50  
M1200 30 range 100K/Volt: AC/DC 15A 200 Meg ohm £49.00

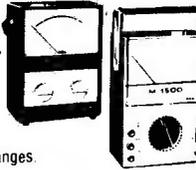K1400 26 range large scale 20K/Volt: 10A AC/DC: 20 Meg ohm: 5kV AC/DC £95.00  
K200 39 range 10 Meg ohm input. 25 Hz-1 MHz £105.00  
OPTIONS Cases: M 1500 & 1200 £16.50: K 1400 £19.00  
Temperature Probe for K1400 £16.00



**DIRECT READ HV PROBE** (UK c/p 65p)

0/140KV. 20K Volt £18.40




**SAFGAN PORTABLE OSCILLOSCOPES**

Range of low cost Dual Trace Scopes mains operated. Made in UK to exacting standards. Available as 10 MHz, 15 MHz or 20 MHz. All feature 5mV sensitivity. 0.5 micro sec. 6.4 x 8cm display (UK c/p £2.50)

DT410 Dual 10 MHz £205.95  
DT415 Dual 15 MHz £217.95  
DT420 Dual 20 MHz £228.95


OPTIONAL SCOPE PROBES - SEE HAMEG ABOVE

**MADE IN UK**

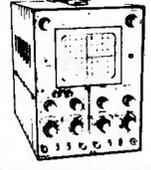

**LOGIC PROBES/MONITORS/PULSERS circuit powered** (UK c/p 60p)

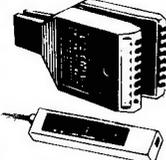LP1 DTL/TTL/CMOS 10 MHz: Pulse: Memory £35.50  
LP2 DTL/TTL/CMOS 1.5 MHz: Pulse: £19.95  
LP3 DTL/TTL/CMOS 50 MHz: Pulse: Memory £55.95  
LM1 Logic monitor for 8 to 16 pin IC's £33.00  
DP1 Digital pulser. Single or 100pps £58.50  
LDP076 50 MHz: 10Meg ohm: Logic Probe. with case £56.90



ALL PRICES INCLUDE VAT

**AUDIO ELECTRONICS** CUBEGATE LIMITED

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564  
ALSO AT HENRY'S RADIO, 404/406 EDGWARE ROAD, LONDON W2

WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order  
Allow up to 10 days for delivery

**FREE CATALOGUE**

Send large SAE (20p UK) Schools, Companies, etc. free on request.






# ELECTRONICS DIGEST

£1.60

Vol.2 No.4

## Gateway to Electronics Complete Constructor's Course

# 20

Projects to Build  
Including:

Mini Synth, Radio Time, Digital Speedo, Electronic Music, and more.

From the Publisher

**OUT NOW!**



# DESIGNER'S NOTEBOOK

Remote control is this month's topic, as Don Keighley looks at ways to do things at arm's length — or further.

If you've followed ETI over the years you'll have seen how the trends in remote control have taken place — from simple, single-channel on/off ultrasonic systems through to super-duper luxury systems which allow you to adjust contrast or brilliance on your colour TV without even twitching your leg. The electronics industry being what it is, I don't suppose you will have been surprised by the rapid increases in complexity which were required to produce all the facilities of the later systems. What you may find surprising, however, is that the more complex the systems seem to be, the fewer components are actually inside them! For example, one of the most recent hand-controllers — which offers no less than 32 facilities — uses less than a dozen components (not including key-switches).

This great decrease in the number of components (and hence a new-found ease of system manufacture) is due to medium-scale and large-scale integration. With such integration one IC can do the work of literally hundreds of discrete components, making possible highly complex systems at low prices.

## Distant Data

Quite a number of manufacturers of all nationalities have been jumping onto the remote-control bandwagon — each producing its own varieties. Plessey's 490/922 range provides for remote-control over ultrasonic, infra-red or simple cable links. Pulse position modulation (PPM) is used for data transmission and this gives good noise immunity — even with control distances of about 10 m. A block diagram of the remote-control encoder (SL490) is shown in Fig. 1.

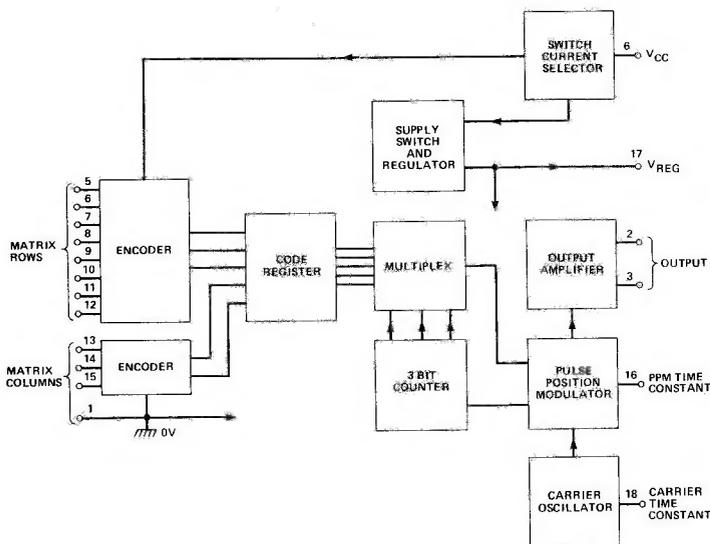


Fig. 1 Block diagram of the SL490 remote control encoder.

The circuit of a basic ultrasonic hand-held transmitter is shown in Fig. 2. A bank of 21 single-pole push-buttons is used in a key-matrix. As each push-button is operated the encoder IC detects closure at a matrix crosspoint and emits a modulated code word of six bits (five data bits and a synchronising bit). The code word is repeated at regular intervals until the push-button is released. A five bit data word allows a range of  $2^5 = 32$  different code words — but the matching receiver/decoder IC (SL922) can only decode 21 code words: hence the 21 key matrix.

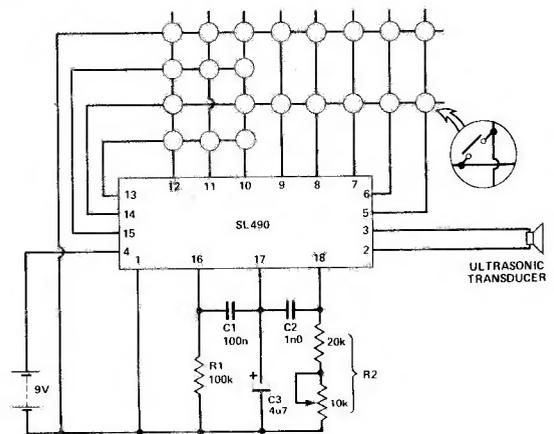


Fig. 2 Circuit of a 21-facility remote control transmitter using the SL490 encoder with an ultrasonic transducer.

The ratios of each part of a code word are shown in Fig. 3. Starting with a fixed pulse-length, L, the total length of the code word is dependent on the binary word to be transmitted. The example shown of the binary word 01011 (followed by a synchronising bit of length 18L) takes 54L to transmit.

The basic pulse length, L, is defined by the values of resistor R1 and capacitor C1 according to the equation


$$L = 0.14 C1.R1 \text{ seconds,}$$

so for the values shown, the pulse length is approximately 10 mS and so the code word given in the example would take 540 mS to transmit.

Capacitor C2 and resistor R2 set the carrier to a frequency given by the equation

$$f = \frac{1}{C2.R2}$$

The values shown give a carrier frequency range of 30-50 kHz. Most ultrasonic transducers are resonant at frequencies around 38-40 kHz so the component values shown in Fig. 3 are satisfactory.

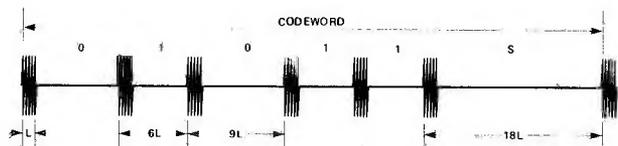

**Fig. 3** Typical output code word of the SL490 encoder. Each part of the code word is defined as a multiple of the basic pulse length L. A pulse is formed by a burst of carrier frequency.


The outputs (pins 2 and 3) from the encoder are in antiphase and can interface directly with the transducer. The range of this circuit would be up to five or six metres. Adding transistors Q1 and Q2 to the circuit (Fig. 4) increases the range to approximately 10 m. A current drain of only 6 uA in standby and 8 mA in transmitting mode means that a standard PP3-sized battery will last for months with normal usage.

If the IC is to be used in an infra-red transmitter, no carrier is strictly required, so components C2 and R2 can be replaced by a single resistor (say 10k) from pin 18 to ground.

### Are You Receiving Me?

The SL922 receiver is shown in block form in Fig. 5. From this you can see that the chip provides:

- a four-bit binary output to control system inputs: such an in-

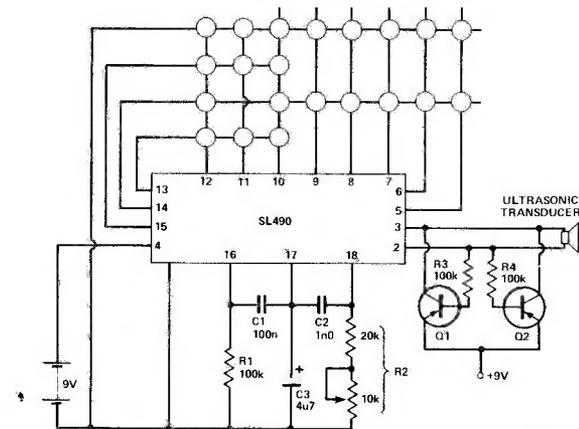


**Fig. 4** The addition of transistors Q1 and Q2 increase the range of the transmitter to about 10 m.

put could be a TV channel, audio signal, motor control and so on. With extra decoding circuitry one of a range of up to 16 inputs at a time can be selected

- three analogue outputs (for DC control of volume, tone, colour, brightness etc)
- a low-going pulse output (whenever an input change is selected)
- a toggle output (for muting etc)
- an on/standby output

A typical SL922 receiver circuit is shown in Fig. 6 and from the diagram you'll appreciate how simple it is to use this versatile device. Some form of receiver/preamplifier is necessary to provide positive-going PPM pulses of sufficient amplitude from the received infra-red or ultrasonic signals. Ultrasonic signals must also be demodulated in some way to remove the carrier. Such a receiver/preamplifier could be constructed using op-amp circuitry or a purpose-built IC.

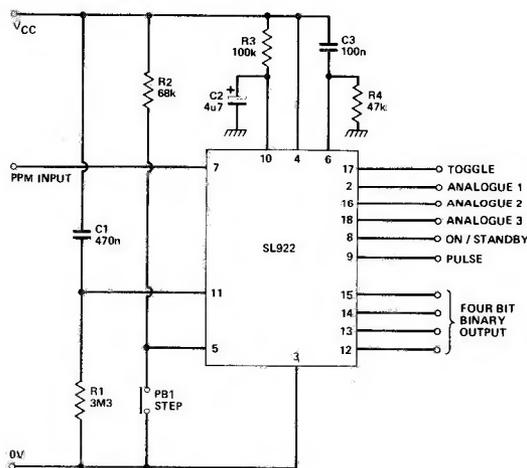


**Fig. 6** Circuit diagram of a remote control receiver using the SL922. A preamplifier is required at its input.


### Looking East

Japanese manufacturers didn't take long to get on the scene, of course, and a number of companies produce their own varieties. Nippon Electric Company (NEC) — although more famous for complete equipment such as video cassette recorders and computers — has produced its own range of remote control ICs which is ideal for the electronics designer.


NEC's uPD1986C is a similar device to the SL490, capable of transmitting up to 27 commands. Its block diagram is shown in Fig. 7 and you can see the IC is much simpler than the 490 and

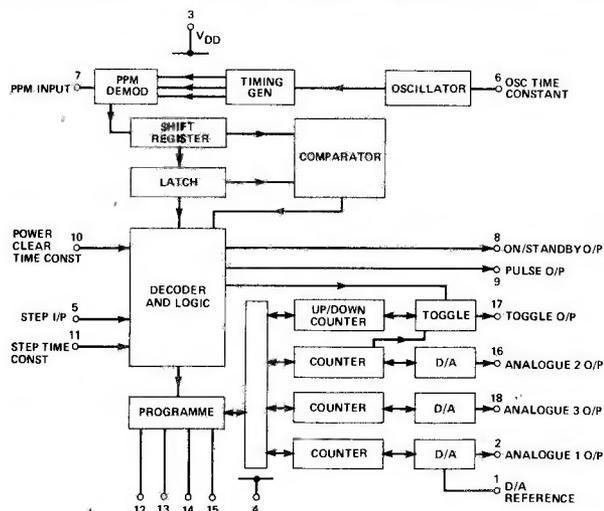

**Fig. 5** Block diagram of the SL922 remote control receiver.

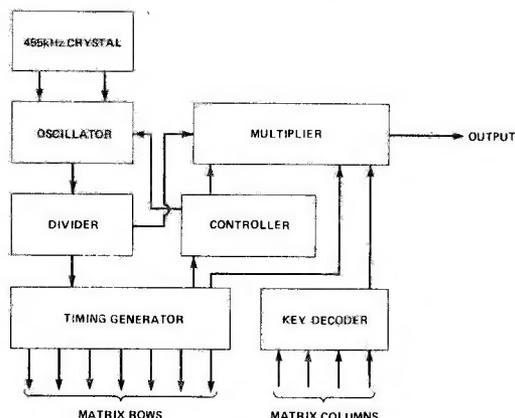

**Fig. 7** Block diagram of NEC's remote control encoder — the uPD1986C.

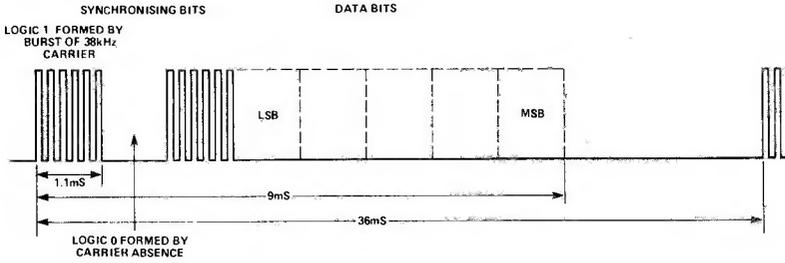


**Fig. 8** The code word of the uPD1986C encoder, consisting of three synchronising bits and five data bits.

so is inherently easier to use with respect to circuit design. Standby current is low (less than 1 uA) so long battery life is obtained too.

A uPD1986C code word consists of eight bits as Fig. 8 shows. The first three bits transmitted (101) are synchronising bits to enable the receiver to detect whether a code word has arrived. A logic 1 bit is represented by a 1.1 mS burst of 38 kHz carrier with a 50% duty cycle. Logic 0 is represented by carrier absence. Thus, the IC should be usable with either ultrasonic or infra-red transducers without modification.

The remaining five bits of the code word are the data bits of the transmitted remote-control message — corresponding to the key pressed. The code word is repeated every 36 mS until the key is released.


Figure 9 shows the circuit of an 18-function infra-red transmitter circuit using the uPD1986C. Oscillator frequency is controlled by a 455 kHz crystal to give carrier and code word timing accuracy — a factor which obviously aids long-distance remote-control transmission.

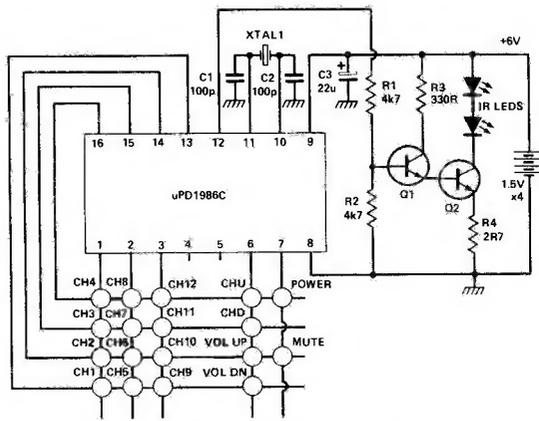


**Fig. 9** Circuit of an 18-facility remote control transmitter using NEC's uPD1986C.

Reception and decoding of the transmitted code word is undertaken by the uPD1937C remote-control receiver IC. A block diagram of the IC is shown in Fig. 10, and a typical circuit using it is in Fig. 11. As with the 490/922 chip set, a preamplifier is required to detect and amplify the received low-level signal.


Input selection can be either sequential (ie stepping up or down at a fixed rate) or direct (ie straight to the required input). The output waveform for sequential input-select is shown in Fig. 12a. A sequence step-time of about 0.72 S means that it takes over 12 S to step through from input 1 to input 18. The output waveform for direct input selection is shown in Fig. 12b. The number of pulses in the shift pulse code is one less than the required input number.

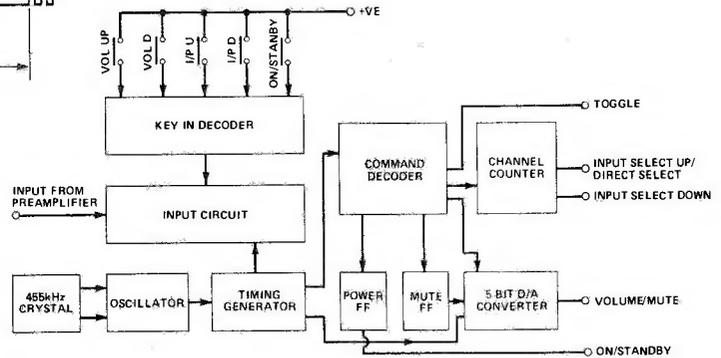


**Fig. 10** Block diagram of the uPD1937C remote control receiver.

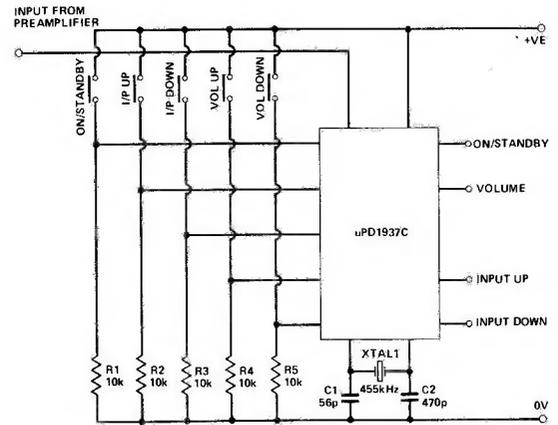

**Fig. 11** A typical circuit for a remote control receiver using the uPD1937C. A preamplifier is needed at the input.

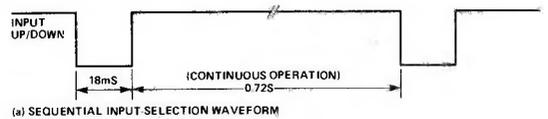

(a) SEQUENTIAL INPUT SELECTION WAVEFORM

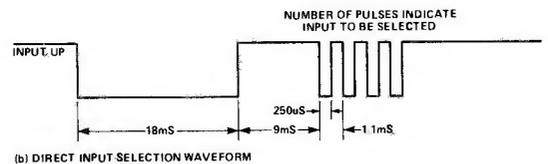


(b) DIRECT INPUT SELECTION WAVEFORM

**Fig. 12** (a) Sequential input select waveform, and (b) direct input select waveform of the uPD1937C remote control receiver.

These waveforms need to be interpreted by decoding circuitry so that the chosen input is switched through. A decoding interface could be easily made with a 4017 or similar counter — alternatively NEC manufacture input selectors specifically for the job.

ETI
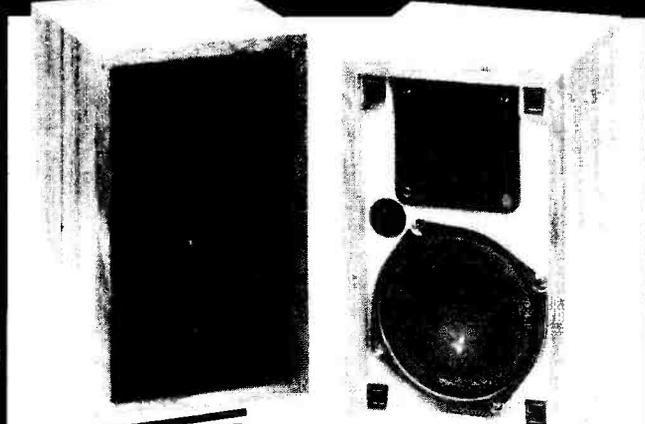
# Has seven years of success gone to our heads?



**NEW IMPROVED**

## MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

### POPULAR HI-FI

"Switching to the Minimax' from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." *Comparative test* OCTOBER 1975.

### HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" *JANUARY 1975.*

### PRACTICAL HI-FI & Audio

"The depth, clarity and openness of sound produced is quite astonishing". *JUNE '75*

### WHAT HI-FI

"... the ability of the Mini-

max to take a lot of power and still sound good could be decisive" — *Comparative test; APRIL 1977.*

### PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". *JANUARY 1981.*

### Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms.  
 Frequency Response: 80Hz — 20KHz ±5dB.  
 Finish: natural teak, veneer with black frets.  
 Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.  
 Weight: 4.1 Kgs (9 lbs) each.  
**ONLY £69.95 A PAIR**

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

**VIDEOTONE** 98 CROFTON PARK ROAD LONDON SE4.

Send for our free brochure and details of outlets in the U.K.


Post to: Videotone, Crofton Park Road, London SE4. ET5

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

# CALCULATORS

## CASIO

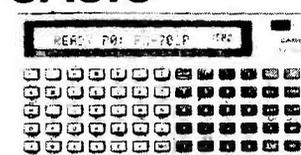

FX702P PROGRAM IN BASIC LANGUAGE 1680 STEPS/226 MEMORIES (MAX) 56 FUNCTIONS  
**£115.95**



FX802P 10+2 DIGIT ALPHA NUMERIC DOT MATRIX DISPLAY UP TO 512 STEPS/88 MEMORIES 50 FUNCTIONS  
 FX802P **£71.95**  
 FX801P **£51.95**

FA2 CASSETTE INTERFACE FOR FX501/502/601/602/702P WITH REMOTE TAPE START  
 FP10 PRINTER UNIT FOR FX501/502/601/602/702P **£18.95**  
**£41.95**



FX3000P 38 STEPS 2 PROGRAMS, 61 FUNCTIONS, LITHIUM BATTERY  
**£21.95**



FX8100 8+2 DIGIT 46 FUNCTIONS WITH CLOCK, TIMER, ALARM AND 11000 STOPWATCH ETC  
**£23.95**



FX550 10 DIGIT 50 FUNCTIONS STANDARD DEVIATION ETC  
**£18.95**



AX210 VERSATILE MULTI DISPLAY, MULTI FUNCTION ALARM CHRONOGRAPH, 12/24 HOUR DISPLAY CHOICE OF ALARM TONES OR TUNES  
**£27.95**



W250 WATER RESISTANT TO 10 ATMOSPHERES STOPWATCH, ALARM, DAY, DATE ETC STAINLESS STEEL CASE AND STRAP  
**£18.95**

CASIO NEW BOXING GAME CLOCK/CALCULATOR BG15 **£15.95**  
 CASIO SL801 SOLAR POWERED **£11.95** CASIO FT7 FORTUNE TELLER **£15.95**  
 CASIO MG885 MISSILE GAME CALCULATOR **£10.95**

## TEXAS INSTRUMENTS



TI 51-111 32 KEY STROKES ..... **£29.95**  
 TI 57 150 KEY STROKES ..... **£26.95**  
 TI 58 480 STEPS/80 MEMORIES (MAX) 172 FUNCTIONS ..... **£57.95**  
 TI 58C AS TI 58 BUT CONSTANT MEMORY ..... **£36.95**  
 58C CONSTANT MEMORY ..... **£38.95**  
 TI 59 MAG CARD 980 STEPS/100 MEMORIES (MAX) ..... **£121.95**  
 PC 100C PRINTER FOR 58/59 ..... **£148.95**  
 58/59 SOFTWARE, MATHS/UTILITIES, APPLIED STATS, ELECTRICAL ENGINEERING, BUSINESS DECISIONS, LEISURE, SURVEYING ALL AT ..... **£35.95**  
 PC100C ROLLS PACK OF TEN ..... **£29.95**




TI59

Full range and accessories in stock

TI58

## SHARP

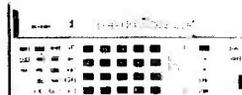

EL 5100 24 DIGIT  
 EL 5103 SCIENTIFIC PROGRAMME  
 CE 121 CASSETTE INTERFACE **£27.95**  
**£15.95**

EL 5101 16 DIGIT **£41.95**  
 PC 1211 POCKET COMPUTER **£31.95**  
 CE 122 PRINTER/INTERFACE **£71.95**

## HEWLETT PACKARD



HP41C/41CV

NEW HP11C UP TO 203 PROGRAM LINES, 21 DATA STORAGE REGISTERS. SPECIAL PRICE **£99.95**

HP41C COMPREHENSIVE SYSTEM. LCD DISPLAY, 319 REGISTERS, 2240 PROGRAM LINES, 10 PROGRAM LABELS, 64 USER DEFINABLE KEY FUNCTIONS, 58 FLAGS, 6 SUB ROUTINES, ACCESSORIES INCLUDE PRINTER, BAR CODE LIGHT PEN, MAGNETIC CARD READER, MEMORY MODULES, PROGRAM MODULES.

HP41C ..... **£182.95**  
 HP41CV AS 41C BUT FIVE TIMES MEMORY CAPACITY ..... **£237.95**

ALL PRICES INCLUDE VAT, POST, AND PACKING. ALL GOODS NEW AND FULLY GUARANTEED. LARGE S.A.E. WITH ENQUIRIES PLEASE

**CALCULATOR SALES & SERVICE**  
 PO BOX 13 REDDITCH, WORCS B98 8NS  
 Telephone (0527) 43169

# C.S.S.

# ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range, decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types.



Order using the FREEPOST coupon below.  
Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. GUARANTEED 5 YEARS.

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE inc. VAT	PRICE ex VAT
30 VA 70 x 35mm 0.45 Kg Regulation 18%	1X010	6+6	2.50	£5.28	£4.48
	1X011	9+9	1.66	+0.87p	+0.87p
	1X012	12+12	1.25		
	1X013	15+15	1.00		
	1X014	18+18	0.83		
	1X015	22+22	0.68		
	1X017	30+30	0.50		
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2X010	6+6	4.16	£5.83	£4.93
	2X011	9+9	2.77	+£1.10	+£1.10
	2X012	12+12	2.08		
	2X013	15+15	1.66		
	2X014	18+18	1.38		
	2X015	22+22	1.13		
	2X016	27+27	0.90		
80 VA 90 x 30mm 1 Kg Regulation 12%	3X010	6+6	6.64	£6.51	£5.47
	3X011	9+9	4.44	+£1.43	+£1.43
	3X012	12+12	3.33		
	3X013	15+15	2.66		
	3X014	18+18	2.22		
	3X015	22+22	1.81		
	3X016	27+27	1.50		
120 VA 90 x 40mm 1.2 Kg Regulation 11%	4X010	6+6	10.00	£7.55	£6.38
	4X011	9+9	6.66	+£1.43	+£1.43
	4X012	12+12	5.00		
	4X013	15+15	4.00		
	4X014	18+18	3.33		
	4X015	22+22	2.77		
	4X016	27+27	2.40		
160 VA 110 x 40mm 1.6 Kg Regulation 8%	5X010	6+6	13.33	£9.92	£8.44
	5X011	9+9	8.89	+£1.43	+£1.43
	5X012	12+12	6.66		
	5X013	15+15	5.33		
	5X014	18+18	4.44		
	5X015	22+22	3.63		
	5X016	27+27	3.20		

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE inc. VAT	PRICE ex VAT
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6X012	12+12	9.38	£11.83	£10.06
	6X013	15+15	7.50	+£1.73	+£1.73
	6X014	18+18	6.25		
	6X015	22+22	5.11		
	6X016	27+27	4.50		
	6X017	30+30	3.75		
	6X018	35+35	3.21		
	6X019	40+40	2.81		
	6X020	45+45	2.50		
	6X021	50+50	2.25		
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7X013	15+15	10.00	£13.67	£11.66
	7X014	18+18	8.33	+£1.73	+£1.73
	7X015	22+22	6.82		
	7X016	27+27	6.00		
	7X017	30+30	5.00		
	7X018	35+35	4.28		
	7X019	40+40	3.75		
	7X020	45+45	3.33		
	7X021	50+50	3.00		
	7X022	110	2.77		
500 VA 140 x 60mm 4 Kg Regulation 4%	8X016	25+25	10.00	£18.17	£15.53
	8X017	30+30	8.33	+£2.05	+£2.05
	8X018	35+35	7.14		
	8X019	40+40	6.25		
	8X020	45+45	5.55		
	8X021	50+50	5.00		
	8X022	55+55	4.54		
	8X023	110	4.54		
	8X024	220	2.27		
	8X025	240	2.08		
625 VA 140 x 75mm 5 Kg Regulation 4%	9X017	30+30	10.41	£25.10	£21.54
	9X026	40+40	8.92	+£2.20	+£2.20
	9X025	45+45	7.81		
	9X033	50+50	6.25		
	9X042	55+55	5.68		
	9X028	110	5.68		

**IMPORTANT: Regulation** — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

### The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

### How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders. Also available at Electrovalve, Maplin, Marshalls, Technomatic and Watford Electronics.

Please send me the following ILP modules

Total purchase price

I enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No.

Name

Address

Signature

ET 6/5

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone (0227) 54778. Technical (0227) 64723. Telex 965780



**ILP TRANSFORMERS**  
(a division of ILP Electronics Ltd)

## STAY AHEAD. STAY WITH US

# CLEF ELECTRONIC MUSIC

## ELECTRONIC PIANOS

SPECIALISTS SINCE 1972



Clef Pianos adopt the most advanced form of Touch Sensitive action which simulates piano Key action using a patented electronic technique.

Two Domestic Models are available including the 88-note full size version, four intermediate Voice Controls may be used to obtain a wide variation of Piano Tone, including Harpichord.

Both Soft and Sustain Pedals are incorporated in the Design and optional Effects are provided in the form of Tremolo, Horry, Chorus, and Phase/Flanger.

A power amplifier integrates into the Piano Top which may be removed from the Base for easy Manipulation.

Component Kits include Keyboard, Key-switch hardware, and all electronic components and may be purchased in four stages at no extra cost.

Complete Kits further contain Cabinets, wiring harness, Pedals and in the case of Domestic Models both Power Amplifier and Speaker.

Send for Full Lists, inc. manufactured prices

## COMPONENT KITS

SIX OCTAVE £217

7 1/2 OCTAVE £244



COMPLETE KIT £349

## "THE COMPUTER BAND-BOX"

(As Published in conjunction with "Practical Electronics")



PRICES INCLUDE MASTER RHYTHM

MANFD. £399

A revolution in the field of Computer Music Generation!

MUSICIANS - SOLOISTS - SINGERS - RECORDING

INSTRUMENT FOR PRACTICE - LIVE PERFORMANCE - COMPOSITION

The BAND-Box provides an Electronic Backing Trio consisting of Drums, Bass and a Chord Instrument (one of 16 Waveform Envelopes combinatorial), with the capacity to store over 3,000 User Programmable Chord Changes on more than 120 different Chords. Using advanced Microprocessor technology. Playback of 50-100 Scores can be executed in any Key and at chosen Tempo. Complete Music Pad is electronically indexed and stored on secondary battery back-up. Facility exists for composition of Intro, Repeat Chorus and Coda sections including Multiple Score Sequences. Sockets are provided for Volume Pedal and footswitch plus separate and mixed instrument Outputs. Total base "9" x "11" x "4 1/2" incorporating Master Rhythm.

OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE

Please send a p.p. for complete list of our products. VISA, ACCESS service. Very competitive EXPORT rates. In America please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept 11)  
44A BRAMHALL LANE SOUTH, BRAMHALL  
STOCKPORT, CHESHIRE SK7 1AH  
TEL 061 439 3297

# JUMP TO IT!

Climb aboard the breadboarding breadwagon with GSC's new WK-1 wire jumper kit — just what you've always wanted to make breadboarding easier and quicker than ever before. Here, in one neatly compartmented box, are all those different lengths of insulated hook-up wire you need — 25 pieces of each, in 14 lengths ranging from 0.1 inch to 4 inches. What's more, the GSC kit makes your job even easier by colour-coding all the different lengths and providing a quarter-inch length at each end with the insulation stripped off and bent through 90°. So GSC jumper wires come ready to plug straight into your quick-test sockets, bus strips or breadboard system. No more fiddling around with wire cutters, strippers or pliers — everything you need in one box. Take the plunge right now by filling in the GSC coupon.

GSC (UK) Ltd., Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: (0799) 21682. Telex: 817477.

WK-1 Jumper Kit £5.50 Nett Unit price inc. P&P 15% VAT £7.47 (Qty Reqd)

Please deduct £1 postage from each additional order.

I enclose cheque/PO for £ . . . . .

or debit my Barclaycard, Access, American Express card

No . . . . . Exp. date . . . . .

or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME . . . . .

ADDRESS . . . . .

GLOBAL SPECIALTIES CORPORATION



FREE catalogue tick box

Global Specialties Corporation (UK) Limited, Dept. 9RR

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

## TOMORROW'S TOOLS TODAY

APRIL OFFER SEE BELOW FOR DETAILS									
<b>POWER SUPPLY:</b> For micros and TTL Stabilised 1A5/5V. Built tested uncased. . . . . 600p	CA3130E 80p	1N4005 4p	LS11/12 15p	7446 72p	74194/5 54p	BC212 9p	BFX84 23p	2N1613 21p	DIL SKTS 40 pin 10 for 200p
<b>AS ABOVE</b> less transformer 240p	CA3140 46p	1N5400 11p	LS13 24p	7447A 7453 6p	74197 44p	BC212L 9p	BFX86 18p	2N2217 18p	
<b>PCB</b> for above or 12V or 15V 100p	CA3160E 80p	1N5401 12p	LS14 36p	7448 35p	74198 99p	BC213 9p	BFX87 23p	2N2222A 15p	
<b>CERAMIC CAPACITORS (50V)</b>	ICL7106 70p	1N5402 12p	LS20 14p	7450 11p	74199 60p	BC213L 9p	BFX88 22p	2N2369 14p	
33pF to 50,000pF . . . . . 3p	LF351N 45p	1N5404 14p	LS21/27 15p	7451 6p		BC214 9p	BFY50 20p	2N2484 18p	
<b>POLYSTYRENE CAPACITORS (50V)</b>	LF356N 90p	1N5404 14p	LS30 14p	7452 13p	<b>TRANSISTORS</b>	BC214L 9p	BFY51 15p	2N2484 40p	
10pF to 1000pF . . . . . 3.5p	LM10C 400p	<b>GREEN LED</b>	LS32 17p	7453 6p	BC237 7p	BC238 5p	BFY52 18p	2N2904 17p	
<b>POLYESTER CAPACITORS (100V)</b>	LM301AN 25p	<b>YELLOW LED</b>	LS42 35p	7454 7p	AC127 25p	BC261B 7p	BRV39 30p	2N2926G 10p	
1nF to 680nF 6p 1uF 1u5 2u2 4u7 8p	LM308N 30p	<b>CMOS</b>	LS47 48p	7470 14p	AC128 22p	BC301 25p	BU20 10p	2N3055 25p	
<b>ELECTROLYTIC CAPACITORS</b>	LM311 82p	4000 13p	LS48 45p	7471 16p	AC128/176 mt. pair 23p	BC328 7p	BU205 105p	2N3055 44p	
(uF/V)	LM318H 80p	1000 14p	LS49 45p	7472 16p	AC141/2 15p	BC338 18p	BU208 115p	2N3702 to 2N3711 8p	
1/25 to 150/25 6p 160/25 640/16 3p	LM318N 100p	4001 13p	LS73 20p	7473 23p	AC153 20p	BC347 18p	MJ2955 90p	2N3773 150p	
220/25 470/25 10p 470/40 mini 12p	LM339N 46p	4002 13p	LS74 18p	7475 20p	AC176 12p	BC547/8 7p	MJE340 33p	2N3819 21p	
1000/10 2200/6 12p 1500/40 33p	LM380N 65p	4006B 45p	LS75 25p	7476 20p	AC187 13p	BC549 9p	MPF104 40p	2N3820 35p	
2000/18 33p 10/50 unpolarised 3p	LM381N 100p	4007 11p	LS76 25p	7477 16p	AC188 20p	BC557/8 7p	MPF105 40p	2N3823 52p	
<b>TRANSFORMER</b> 0-9V 2 Amp . . . 360p	LM339N 46p	4008 56p	LS78 22p	7478 20p	AD149 37p	BCY30 40p	OC2B/35 40p	2N3866 40p	
<b>HEAT SINK</b> TO-220 10" C/W . . . 40p	LM380N 65p	4009 28p	LS86 21p	7479 20p	AF124/5 40p	BCY34 30p	TIP29 25p	2N4037 35p	
<b>VERO BOARD</b> (0.1" copper clad) 2.5 x 5" 60p	LM381N 100p	4010B 33p	LS90 40p	7480 22p	AF126 25p	BCY70 13p	TIP30 25p	2N4058 to 2N4061 8p	
<b>SWITCHES</b>	LM339N 46p	4011B 14p	LS93 28p	7481 20p	AF139 35p	BCY71 14p	TIP30B 28p	2N5458 40p	
DIL 3 way SPST . . . . . 20p	LM1830 170p	78M12 + 20p 4012 17p	LS93 28p	7482 20p	AF139 35p	BCY72 14p	TIP31 20p	2N5459 35p	
DIL 3 way SPDT . . . . . 30p	LM1830 170p	79M105 - 20p 4013 28p	LS95 50p	7483 25p	AF186 40p	BCY72 14p	TIP31A 22p	2N6027 18p	
DIL 7 way SPST . . . . . 30p	LM2917 220p	79M12 - 20p 4014 58p	LS109 30p	7484 40p	ASV54/5 18p	BCY72 14p	TIP31A 22p	3N128 20p (star buy)	
<b>ROTARY 2A/250V DPST</b> 9mm bush . 18p	LM2917 220p	79M24 - 20p 4015B 60p	LS122 35p	7485 35p	BC107 10p	BC113 6p	BD121 46p		
<b>SLIDE 1A/250V SPDT</b> . . . . . 18p	LM3500N 40p	7805 55p	LS123 40p	7486 20p	BC108/9 10p	BC113/12 35p	BD131/2 5p		
<b>SLIDE 1A/250V DPDT</b> . . . . . 7p	LM3500N 40p	7805/12 55p	LS154 40p	7487 16p	BC113 6p	BC117/9 10p	BD135/6 25p		
<b>SLIDE 3A/50V DPST</b> 3 way or 1A/250V with 1 throw panel cutout . . . 10p	LM3500N 40p	7815 58p	LS154 40p	7488 20p	BC117 6p	BC119 10p	BD137/8 25p		
<b>RESISTORS</b> (1/4W 5% carbon film)	LM3500N 40p	7818 52p	LS157 36p	7489 22p	BC119 10p	BC123 50p	BD139 35p		
10ohms to 10Mohms E12 . . . . . 2p	LM3500N 40p	7905 58p	LS157 36p	7490 22p	BC123 50p	BC123 50p	BD140 35p		
<b>PRESETS</b> (miniature horizontal)	LM3500N 40p	7912 60p	LS157 36p	7491 38p	BC123 50p	BC123 50p	BD115 27p		
100ohms to 1Mohms . . . . . 6p	LM3500N 40p	7915 62p	LS157 36p	7492 38p	BC123 50p	BC123 50p	BD115 27p		
<b>CERMET:</b> (1 Watt)	LM3500N 40p	7918 52p	LS157 36p	7493 38p	BC123 50p	BC123 50p	BD115 27p		
100K Linear precision 40 turn . . . 30p	LM3500N 40p	7925 58p	LS157 36p	7494 40p	BC123 50p	BC123 50p	BD115 27p		
<b>POTENTIOMETERS</b> (1/4W): Linear and Log Scale 4K7 to 2M2 . . . 28p	LM3500N 40p	7925 58p	LS157 36p	7495 35p	BC123 50p	BC123 50p	BD115 27p		
<b>ZENER DIODES</b> (400mW)	LM3500N 40p	7915 62p	LS157 36p	7496 38p	BC123 50p	BC123 50p	BD115 27p		
2V7 to 30V . . . . . 6p	LM3500N 40p	7918 52p	LS157 36p	7497 16p	BC123 50p	BC123 50p	BD115 27p		
<b>TRIACS:</b> C206D 400V: 3A . . . 55p	LM3500N 40p	7925 58p	LS157 36p	7498 20p	BC123 50p	BC123 50p	BD115 27p		
600V: 10A 50p 15A 55p 30A 65p	LM3500N 40p	7925 58p	LS157 36p	7499 22p	BC123 50p	BC123 50p	BD115 27p		
High performance glass passivated for high voltage isolation. By THYROTEK CORP of Texas in 3 pin pressfit plastic case with superior spec to plastic ones. Full data supplied. ONCE SOLD THIS CAN NEVER BE REPEATED.	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
<b>DIAC</b>	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
ST2 20p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
<b>THYRISTORS</b>	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
300V: 4A 18p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
(MOTOROLA)	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
400V: 5A 35p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
(C104RD)	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
100V: 12A 20p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
(TEXAS INT)	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
400V: 8A 34p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
(MOTOROLA)	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
<b>DIODES</b>	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
OAS91 7p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
OA200/2 5p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS101 12p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS04 13p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS05/8 14p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS10 14p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
<b>TTL "LS"</b>	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS00/1 12p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS02/3 12p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS04 13p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS05/8 14p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
LS10 14p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
<b>TTL "N"</b>	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7400/1 11p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7402 11p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7403 10p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7404 9p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7405 11p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7406 15p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7407 24p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7408 16p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7409 13p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7410 11p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7411 17p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7412 15p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7413 19p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7414 44p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7416 18p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7417 16p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7418 70p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7419 38p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7420 18p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7421 35p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7422 35p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7423 13p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7424 35p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7425 13p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7426 35p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7427 37p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		
7428 46p	LM3500N 40p	7925 58p	LS157 36p	7500 22p	BC123 50p	BC123 50p	BD115 27p		

# INSULATION TESTER

Some time ago we published a design for a very low resistance meter. Now we've built the DVMeg, for resistances up the other end of the scale. Design and development by Phil Walker.

The ohms range on most multimeters is fine for most electronics work but if you start dealing with hundreds rather than tens of volts then there is the possibility that damp, contaminated, or merely inadequate insulation could cause equipment failure or personal danger. In these circumstances the 1V5 or sometimes 15 V used by most multimeters is not sufficient to show up the dangers. To avoid the false sense of security which may be given by low voltage tests, a voltage somewhat higher than the normal working voltage of the circuit under test must be used. In the case of mains wiring this is often 500 V and this is about the level generated by our project. D is the Roman numeral for 500 and the instrument measures in the megohm range — hence the name, DVMeg.


## HOW IT WORKS

When the device is turned on, Q2 will start to conduct due to current flowing via L1a and R1 into its base. This causes the supply voltage to appear across L1b, which by transformer action increases the voltage (and current) available in Q2's base circuit. This ensures that Q2 will be held on during this part of the cycle.

As L1 is an inductance and the voltage across it is by now fairly constant, the current flowing through it will rise linearly. However, the current also flows through R3, causing a voltage to appear across it which is proportional to the instantaneous value of this current. When the voltage across R3 becomes large enough, Q1 is turned on and robs Q2 of its base current. Q2 promptly turns off and its collector voltage rises sharply. This rise is coupled back to Q1 base via C2 to keep Q1 on during this period. At the same time, the voltage across L1c will be in a direction such that D3 conducts and charges C3. A short time later Q1 will turn off as it has no base drive once C2 is charged, and Q2 will turn on to start another cycle. D2 provides a discharge path for C2 at the start of a cycle as Q2 turns on.

If when C3 is being charged its voltage exceeds about 500 V, the voltage across L1a will be greater than the supply (due to transformer action with L1c) and D1 will conduct, diverting the excess energy back into C1 and the battery. The 500 V on C3 is applied via R5 to the circuit under test. The resulting current then passes through D5 in parallel with M1 and PR1. D4 provides protection if the probes are accidentally connected to a live circuit, while D5 protects the meter from excess current and also modifies its response.

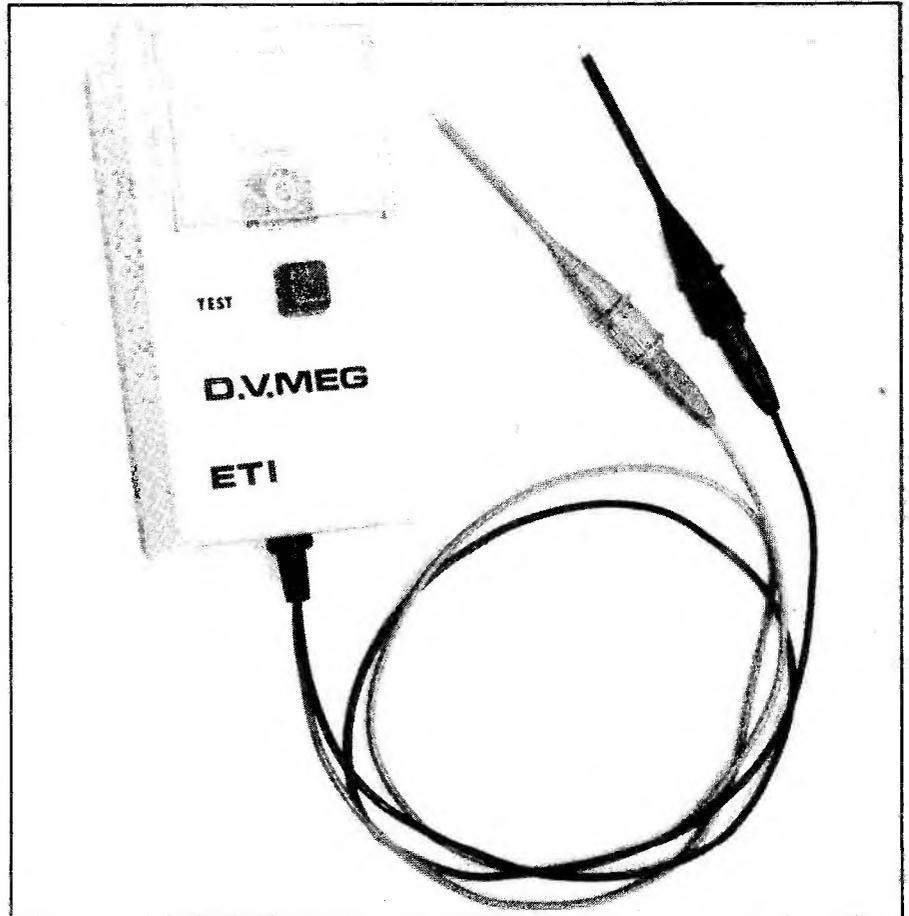R4 in the high voltage section ensures that the output voltage dissipates quickly when the instrument is turned off.



## The Instrument

The project is designed to use a standard PP6 9 V battery and contains a low power DC-DC converter to produce an output of about 500 V. This output is limited so that it does not rise too much even when off-load. The output current is also limited; about 500 uA maximum, even when short-circuited. Even so IT BITES! — so be careful!

In use the test leads are connected to the circuit under test and when the

button is pressed, the circuit generates a high DC voltage which is applied to the test leads via a 1M0 resistor. The resulting current through the insulation is monitored by the meter and displayed as a resistance. When the button is released, the internal capacitor and the circuit under test are discharged fairly rapidly to avoid the risk of shock.

## Construction

The coil is constructed using a

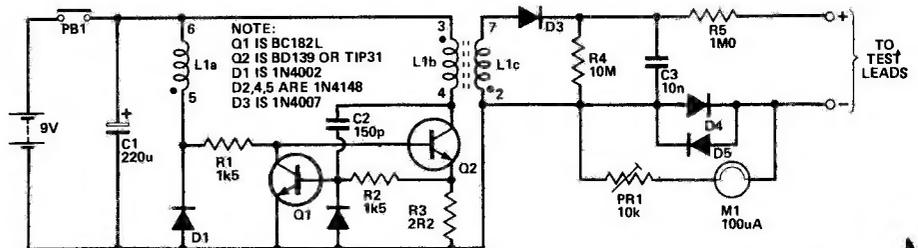


Fig. 1 Circuit diagram of the DVMeg insulation tester.

Neosid potcore. Wind 220 turns of 40 SWG enamelled copper wire on to the former in four layers; start at pin 2 and finish at pin 7. Each layer should be about 55 turns and as this is less than the width of the former, the space each side should be filled with a single layer of insulating tape 2-3 mm wide. A layer of tape the width of the former should be laid on top of each winding. Next wind on 22 turns of 32 SWG enamelled copper wire starting at pin 3 and finishing on pin 4. Insulate this as before and then wind another four

turns of the same wire starting at pin 5 and finishing at pin 6.

Construction of the circuit board should pose no problems so long as component polarities are observed. The wires to the test probes should be flexible and well insulated.

The two types of transistor specified for Q2 have different connections, so the TIP31 must be mounted 'upside-down' if used (see diagram).


Installation into the box is also fairly simple. The meter is fitted at one

end of the box lid and the push-button just below it, but a little to one side to allow the battery to fit inside the case. The circuit board is stuck or bolted to the inside of the case lid and the battery leads connected via the switch. The meter leads are also connected, after which the battery may be connected and fixed into place with sticky pads or wedged with foam.

## PS

It also tests neons!

Fig. 2 Component overlay and component pinouts for the DVMeg.

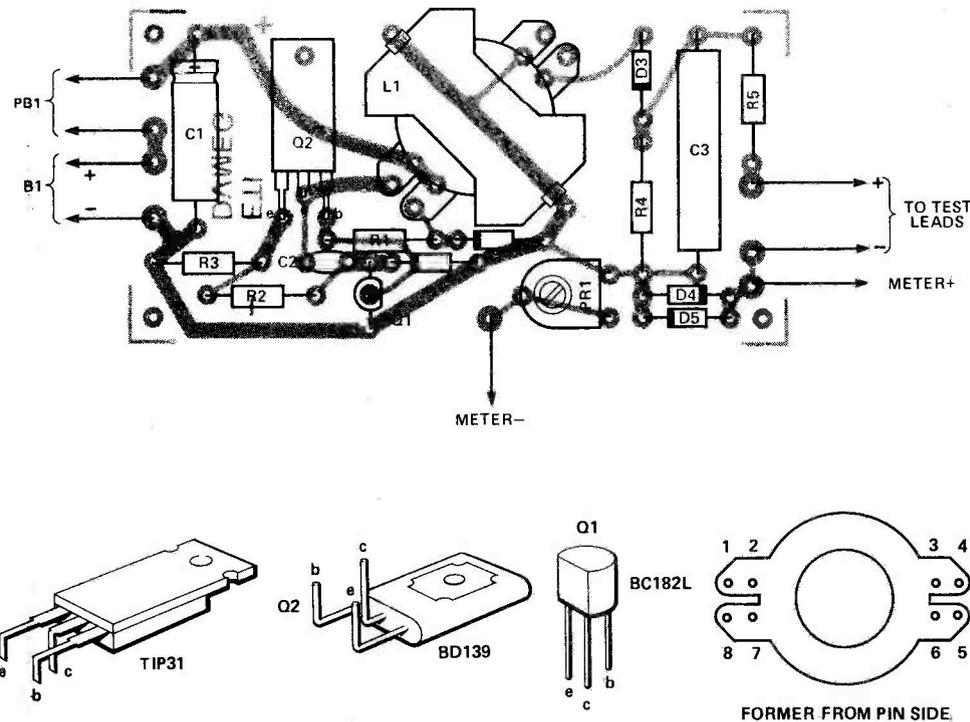

## PARTS LIST

### Resistors (1/4W 5% except where stated)

- R1,2 1k5
- R3 2R2
- R4 10M 1/2W
- R5 1M0 1/2W

### Potentiometer

- PR1 10k miniature horizontal preset

### Capacitors

- C1 220u 16 V axial electrolytic
- C2 150p 160 V ceramic
- C3 10n 1000 V mixed dielectric

### Semiconductors

- Q1 BC182L
- Q2 BD139 or TIP31
- D1 1N4002
- D2,4,5 1N4148
- D3 1N4007

### Miscellaneous

- L1 RM10 pot-core, former, clips (A, about 400)
- PB1 push-to-make non-latching
- M1 100 uA meter
- PCB (see Buylines); case (West Hyde ref. BOC440); grommet; flexible wire; test prods; PP6 battery and connectors.


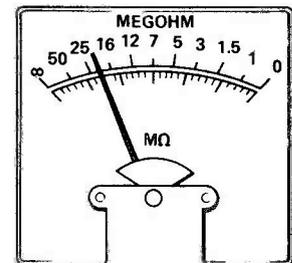
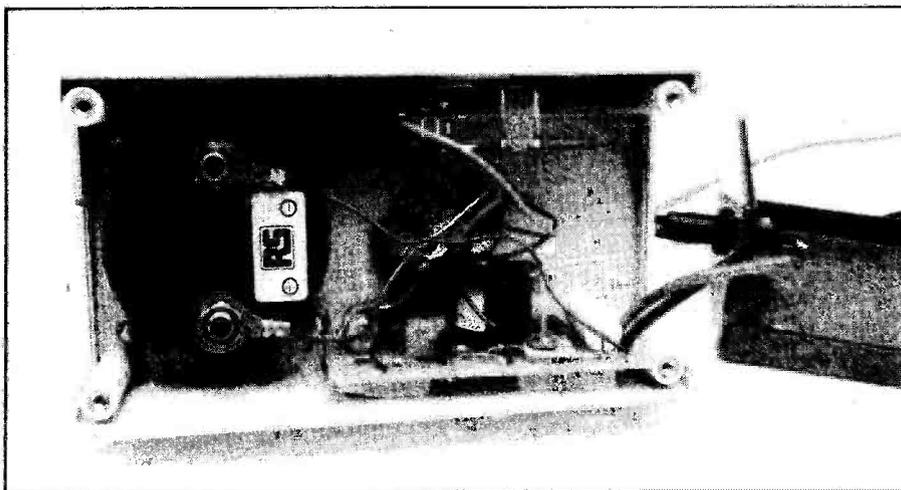


Fig. 3 A suitable meter scale.

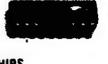


## BUYLINES

The pot core used to wind the inductor for this project is available from Neosid Small Orders, PO Box 86, Welwyn Garden City, Herts AL7 1AS; quote ref. 29-835-41 when ordering. West Hyde supply the case we used; for people who want to use substitutes the size is 150 x 80 x 55 mm. The PCB can be obtained using the order form on page 45.

<b>D.I.L. MINIATURE ON-OFF SWITCHES</b> Gold-plated contacts. Sealed base. Ideal for programming. 6-position at less than half manufacturer's price. <b>ONLY 75p</b> Will fit into 14-pin di socket. Ten at 65p ea., per 100 55p ea.	<b>HONEYWELL PROXIMITY DETECTOR</b> integral amplifier, 8v. D.C. £3.50 en <b>PHOTO CONDUCTIVE CELL</b> , £1.25. High-power CdS cell, 600mW, for control circuits. Resistance 800 ohm to 4K. Max. volts 240. Size 1/2" x 1/2". <b>RIBBON MICROPHONE</b> with pre-amp on chassis. £1.75.	<b>MULLARD MODULES</b> LP1171 IF Strip AM, FM front end. Pair £5.75. Complete with Data LP1157 varicap. Med & Long Tuner £2.50 <b>CRYSTALS COLOUR TV</b>	<b>ULTRA SONIC TRANSDUCERS</b> 40Kc/s. Complete on 18in. Screened cable. £1.75 each, pairs £2.95. <b>ULTRA SONIC TRANSMITTER</b> Complete unit (uncased requires 15v). £3.25. <b>FOSTER DYNAMIC MICROPHONES</b> 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
<b>U.M.F. MODULATORS</b> Latest type, adjustable, ideal for computers with data circuit. Size 2" x 7/8" x 1 inch. Only £3.50. In screened case.	<b>LM380 Amplifier</b> . . . . 85p <b>LM318N Hi-Slew Op. Amp.</b> £1.50 <b>LM323K</b> , 5v. 3-amp. reg. £3.80 <b>LM310N Volt. Follower Amp.</b> £1.20 <b>LM311H High Perf. Volt. Comparator</b> £1.00 <b>LM384N</b> , 5-watt Amp. £1.20 <b>LM353N</b> , Dual Com. . . . 60p <b>7905 Reg.</b> . . . . 75p	<b>QUALITY FANS</b> "Whisper Model" by Roton. Low power consumption (less than 10 watts). Silent running 115v (two in series for 230v 50/60Hz). Size 4" x 4" x 1". <b>Only £6.50 inc. VAT</b> <b>BRAND NEW</b> 50% less than manufacturers price.	 <b>CHIPS</b> 2102 450 n/s. £1.00 2114 300 n/s. £1.75 4116 200 n/s. £1.50 2732 450 n/s. £7.50
<b>MINIATURE EDGE INDICATOR</b> meter with illuminated dial. Scale 0-10. F.S.D. 100 microamp. Size 1 1/2" x 1 1/2" x 1/2" deep. Only £1.65.	<b>STEREO CASSETTE TAPE HEADS</b> . Quality replacement for most recorders with mounting plate Record/Replay £2.80 <b>MARRIOTT TAPE HEADS</b> Quarter track. Type XPS18 Record/Replay (each). £2.00 XRP336 Record/Replay (each). £2.00 XES11 Erase (each). £1.00	<b>HEWLETT-PACKARD DISPLAYS</b> <b>5082-7650</b> HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each. Set of 6 for £5. Half-inch red common cathode will replace DL707. 14-pin Di.	<b>EX-MOTOROLA 5+5-WATT CAR STEREO AMPLIFIERS</b> Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in.) with circuit and data. Only £5 pair. Includes pre-amp.
<b>MONSANTO</b> Half-inch + 1 Display. High Intensity. £1 each. set of 4 £3.50. Common anode. 14 Pin Di Package.	<b>RECHARGEABLE BATTERIES</b> VARTA 3.6 volts DEAC. M/AM 225. £1.50 DRYFIT 6-volt. 4.5 amp. £7.50 XTAL. FILTER 10.7mc/s. 12.5dB separation. 1/2x1/4x1 inch £7.00 100KC/S + 1 meg. 3-pin £2.00	<b>"CHERRY" ADD-ON KEYPAD</b> LIST PRICE £22.00 <b>OUR PRICE ONLY £7.50 INC. VAT</b> A compact 12-button keypad suitable for use with Cherry Keyboard to extend its functions plus four extra keys. Supplied brand new with data. A 3 x 4 non-encoded single mode keyboard.	
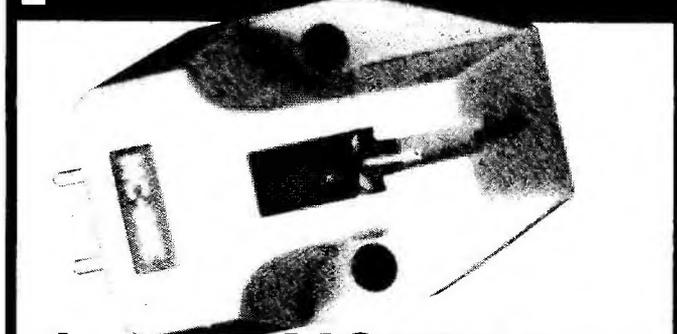
# A moving coil cartridge that breaks the price barrier!



## the new MC88E from CORAL

The new MC88E represents a breakthrough in high output moving coil cartridges. No step-up device or amp is required and it is available at a sensational price of only £29.95. yet generating high magnetic flux density; compliance of 17 cu's. The result is a cartridge with flat frequency response over the super wide range of 20Hz - 40KHz, removing the distortion caused by certain frequencies, which can be found in many conventional cartridges. Coral's considerable experience in moving coil cartridges has enabled them to offer the ultimate in quality and performance at this incredibly low price.

The high output voltage of 2.5mV does away with the need for a head amplifier or step-up transformer, which add to the expense of using most previous moving coil cartridges. We can't emphasise enough, just how advanced the technology that has produced this breakthrough is - a miniaturised and specially shaped armature; unique coil winding technique; a magnet that is so compact,

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32
- All products are only available direct or from selected authorised dealers throughout the U.K.

**VIDEOTONE** 98 CROFTON PARK ROAD LONDON SE4.  
 Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. ET5

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

## QUALITY DOES NOT HAVE TO COST VERY MUCH!

**AUDAX HI-FI - SPECIAL PURCHASES**

HD20B25H4C 8" Bass mid range Bextrene cone. 40/60 watt systems	£9.95
HD24S452C 10" high performance bass. Foam suspension. 60/80 watt systems	£12.95
HD13B25H4C 5 1/2" bass mid range Bextrene cone. 40/60 watt systems. Heavy magnet.	£6.95
HD13B25J Smaller magnet version	£5.95
HIF20JSMC 8" bass mid range foam surround. "square" silver front. 30/50 watt system	£8.95
HIF20ESM 8" bass mid range. For 30/50 watt systems roll surround. treated cone. 4 ohm £6.95 8 ohm £7.95	
HIF87BSM0 4" closed back mid range for 30/50 watt systems	£5.50
HD100D25HR 1" dome tweeter. 4" frame for 60/80 watt systems	£5.95

All models for 8 ohms unless stated. (UK Post etc. Speakers 70p, tweeters and mid range 50p).

**TV SOUND FROM YOUR HI-FI (Mk III)**

High quality TV sound converter, plugs into aerial socket of your FM tuner. 9 volt battery operated (battery not supplied). Nothing to look at... but just listen! Covers all U.K. UHF Channels.

\*Fitted slow-motion drive (Mk III) £11.50  
 Four button push-button version £14.50 c/p 65p. (UK Post etc. 65p)  
 On Demonstration for callers to 301 Edgware Road.

**PIEZO TWEETERS**

Clear sound. Very low distortion tweeters. No crossover required. Suitable up to 100 watts - more in series.

1 Mid-range horn for disc/pa groups	£7.95	Two For £16.50
2 Tweeter horn for hi-fidelity groups	£5.95	£11.40
3 Popular hi-fi and disco	£4.95	£9.70
4 Flat type hi-fi	£3.95	£7.60
5 Round version of No 3	£4.95	£9.70
6 Boxed free standing hi-fi piezo	£9.95	£17.50

UK Post Free. On Demonstration to callers.

**ORDER BY POST (OR PHONE) OR CALL IN** ALL PRICES INCLUDE VAT

Cubegate Limited

**AUDIO ELECTRONICS** FREE Catalogue send large 20p SAE

301 Edgware Rd. London W2 1BN  
 Tel: 01-724 3564  
 Also at Henrys Radio 404 Edgware Rd. W2

# PRIZE CROSSWORD


**FIRST PRIZE £50: SECOND £10: THIRD £5**

Time once again for our every-alternate-month stretching of your brains — the ETI Prize Crossword. Many of you obviously found Crossword No. 2 more difficult than the first one, since few readers were able to complete it correctly; but of those that did, the following three were picked out as our prizewinners:

**FIRST PRIZE:** H.R.W. Thurlow, Gravesend  
**SECOND PRIZE:** A.M. Tucker, Dorchester  
**THIRD PRIZE:** Nicholas Brasier, Frimley Green

Congratulations to them, and good luck to everyone who enters for Crossword No. 3; hopefully we've made it less obscure!

LAST MONTH'S SOLUTION

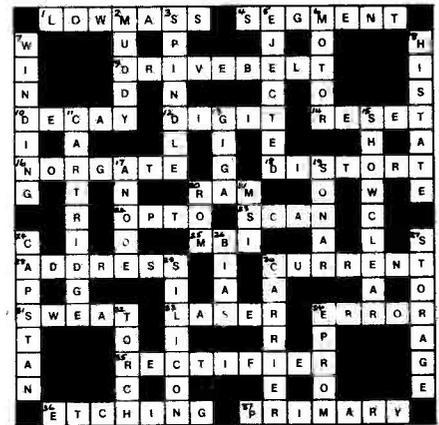


ACROSS

1. Switching device from RX to TX. (8)
4. Rotating member in the motor. (8)
9. 'Son of Crystal'. (7)
11. Roman numeral shapes up for a trip. (7)
13. Short magazine has centre spread between I and E to get picture. (5)
14. The initial effect on transistor by farmer's land. (3)
15. The right place for electronic discharge. (3)
16. Backwards or forwards it indicates the same. (5)
17. Something more than an ordinary BC182. (1,4)
19. Signal selector. (5)
20. West, central in twisted rope. (5)
21. Fix the result — Good Buddy! (3)
22. Timely happening. (5)
27. Re-organise magnetic formation. (5)
28. Airborne beacon electronic test set — may help initially. (5)
29. Unit of luminous flux. (5)
30. Broken cart — ideal vision. (3)
32. Perhaps an about turn would change a short sagging economy ready for inflation. (3)
33. A symbol no good ohm should be without! (5)
34. Reagan changes tune about radioactive weapon. (7)
36. Used by Ken Dodd to trigger laughter? (7)
38. Port side, one of a disc jockey's pair. (4,4)
39. Rest period for computers. (4,4)

DOWN

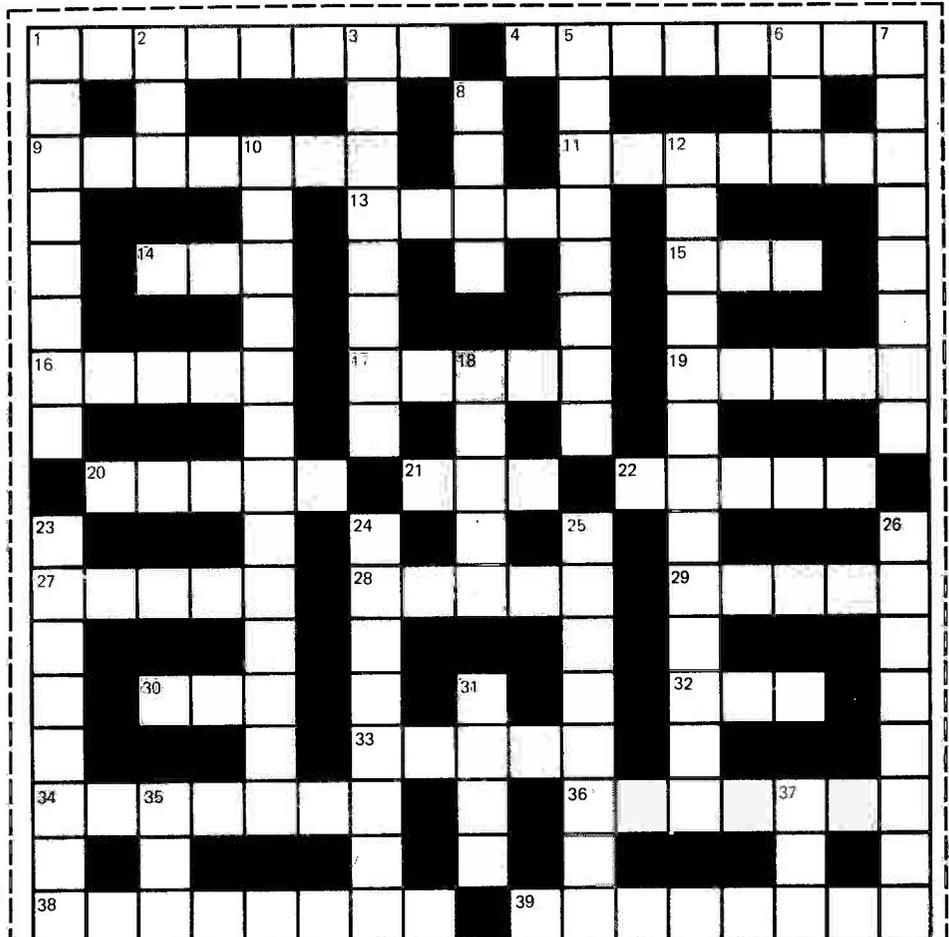1. 10-1 your ears may ring at these excessive levels. (8)
2. Precisely the right approach for golfers when using radar. (3)
3. Go east, go north, then round and round. (8)
5. Found in radio cabin and Laker Airlines! (8)
6. The French are crazy about celestial visitors. (3)
7. Computer's credit card — not this side of the channel. (8)
8. Twice as good as stereo. (4)
10. Fortune finder? (5,8)
12. Backward thinking? (8,5)
18. Vertical reference. (1,4)
23. Trim Lane roundabout for meeting point. (8)
24. Hurt coin produces second wave attack. (8)
25. Floating input may be lonely. (8)
26. Mixed hen cargo — great top-up! (2,6)
31. Highest point of AC cycle. (4)
35. TV or not TV, that is the answer. (3)
37. Large Scale Integration. (3)




NAME .....

ADDRESS .....

BLOCK LETTERS PLEASE  
 ETI PRIZE CROSSWORD NO. 3  
 MAY 1982 ISSUE  
 CLOSING DATE: 5th MAY

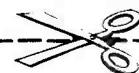The coupon provided in the magazine must be used. Photocopies are NOT acceptable. Employees of ASP and their relatives are not eligible for entry. The judges' decision is to be considered final and no correspondence will be entered into concerning the competition.



# ONE STOP SHOPPING

No need to waste your time and money searching for components. No need for unfinished projects because you are unable to obtain that last component. We stock complete sets of parts for ETI projects — leaving you to concentrate on the electronics and construction.

## 3 WAYS TO BUY:

**FULL KITS** — include printed circuit board, all components, hardware, IC sockets, case etc. (Not batteries).

**LESS CASE** — as above but less the case.

**PCB + PCB MOUNTED COMPONENTS** — PCB plus all the parts which are mounted on the board — plus leds, potentiometers + off board semi-conductors.

FULL LESS PCB  
KIT CASE PLUS

<b>AUTORANGING CAPACITANCE METER</b>			
<b>AUTORANGING CAPACITANCE METER</b> Mar/Apr 82	£71.99		
<b>ACCURATE VOLTAGE MONITOR</b> Apr 82	£13.63		
<b>AUTOMATIC CONTRAST METER</b> Apr 82, less extrusion	£26.77		
<b>SOUND EFFECTS 1 BOMB DROP</b> Apr 82	£12.47		
<b>SOUND EFFECTS 2. STEAM TRAIN</b> Apr 82	£11.87		
<b>INFINITE IMP. DET.</b> Mar 82	15.98	9.50	—
<b>ROBOT MOTOR CONTROL (DUAL)</b> Mar 82	38.67	33.72	—
<b>1 CHING COMPUTER</b> Feb 82, less book	£32.83	£24.20	—
<b>HIGH QUALITY PHONO AMPLIFIERS</b> Feb 82			
<b>MOVING COIL STAGE</b>	17.98	—	—
<b>MOVING MAGNET STAGE</b>	17.68	—	—
<b>PEST CONTROL</b> Feb 82	6.77	—	—
<b>INFANT GUARD</b> Jan 82	6.39	—	—
<b>PARKING METER TIMER</b> Jan 82	8.99	—	—
<b>GUITAR TUNER</b> Jan 82	28.98	26.27	18.98
<b>ALCOPHOMETER</b> Dec 81	£26.49	£22.99	—
<b>COMPONENT TESTER</b> Dec 81	£7.98	£6.17	—
<b>BODYWORK CHECKER</b> Dec 81	£6.88	£4.59	—
<b>MUSIC PROCESSOR</b> Nov 81	49.98	36.98	31.84
<b>PHONE BELL SHIFTER</b> Nov 81	19.35	13.61	8.32
<b>VOICE OVER UNIT</b> Nov 81	27.62	21.22	15.32
<b>CAR ALARM</b> Nov 81	17.98	14.45	12.80
<b>ENLARGER TIMER</b> Oct 81	26.59	21.85	9.98
<b>SOUND BENDER</b> Oct 81	20.76	15.76	11.77
<b>MICROPOWER PENDULUM</b> Oct 81	—	5.50	—
<b>LAB PSU</b> Sept 81	—	37.98	22.40
<b>WATCHDOG SECURITY ALARM</b> Aug 81	43.33	35.83	19.98
<b>RECHARGEABLE BATTERY</b>	19.98	—	—
<b>HEARTBEAT MONITOR</b> Aug 81	26.26	21.65	13.80

<b>HANDCLAP SYNTHESIZER</b> Aug 81	29.98	23.58	18.44
<b>SMART BATTERY CHARGER</b> July 81	31.98	25.98	9.84
<b>WAH PHASE</b> June 81. Less pedal	—	13.44	9.14
<b>LED JEWELLERY</b> June 81	—	2.47	—
Star	9.41	—	7.20
Spiral	—	—	—
<b>ALIEN ATTACK</b> Jan 81	19.76	16.47	12.83
<b>GUITAR NOTE EXPANDER—ETI</b> April 81	16.47	11.25	6.44
<b>DRUM MACHINE</b> April 81	59.98	46.94	35.38
<b>MUSICAL BOX</b> April 81	12.54	—	—
<b>ENGINEERS STETHOSCOPE</b> Mar 81	19.19	14.92	11.10
<b>SOUND PRESSURE LEVEL METER</b> Feb 81	39.98	32.98	—
<b>INFRA RED ALARM</b> Feb 81	54.98	46.12	35.38
<b>MULTI-OPTION SIREN</b> Jan 81	26.91	21.63	15.25
<b>4 INPUT MIXER</b> Dec 80	19.77	15.71	11.98
<b>MUSICAL DOORBEL</b> Dec 80	11.61	10.61	9.39
<b>AUDIO TEST OSCILLATOR</b> Nov 80	18.30	—	—
<b>METRONOME</b> Nov 80	5.98	—	—
<b>SUSTAIN/FUZZ BOX</b> Oct 80	24.99	21.49	18.72
<b>CASSETTE INTERFACE</b> Oct 80	—	11.57	—
<b>ULTRASONIC BURGLAR ALARM</b> Aug 80	26.82	22.98	17.62
<b>CAPACITANCE METER</b> Aug 80	20.26	16.46	8.21
<b>CMOS LOGIC TESTER</b> Aug 80	10.97	—	—
<b>CLICK ELIMINATOR</b> April 79	61.55	46.57	—
<b>GUITAR EFFECTS UNIT</b> April 79	14.78	10.97	6.41
<b>COMPLEX SOUND GENERATOR</b> Oct 78	—	21.97	—

OM335 I.c. £8.98  
LM394CH £2.48

If you do not have the issue of E.T.I. which includes the project you will need to order the instruction reprint as an extra — 45p each. Reprints available separately 45p each + p&p 40p.  
REPRINTS EXTRA

### GUITAR TUNER

Full kit as described in Jan 82. Includes case, pcb and meter etc £28.98  
All parts available separately

## MAGENTA ELECTRONICS LTD.

EW12, 135 HUNTER STREET, BURTON-ON-TRENT, STAFFS, DE14 2ST  
0283-65435. 9-5 MON-FRI. MAIL ORDER ONLY

ALL PRICES INCLUDE VAT  
ADD 45p P&P TO ALL ORDERS  
S.A.E. WITH ALL ENQUIRIES PLEASE



Irish Republic & B.F.P.O. Europe deduct 10% from prices shown. Payment must be in sterling.

Access and Barclaycard (Visa) orders accepted by phone or post.

### MARCO TRADING

Over 10 million registers in stock!!

1/4W 5% Carbon Film — 5 1/2 million 1/4W 5% Carbon Film — 5 million  
Full range of values.  
1/4W — £3 per 1,000 1/2W — £3.50 per 1,000

**DEVELOPMENT PACKS:** These famous resistor packs are now available in two sizes: Carbon film 5% resistors, every value individually packed in a clearly labelled bag. 10 of every value in the E24 range between the values stated:  
1/2 Watt Pack: 10 ohm to 1 Meg (610 resistors) £5.00 per pack + VAT  
1 Watt Pack: 10 ohm to 2M2 (650 resistors) £6.00 per pack + VAT

**MULTIMETER SPECIAL** Russian type U4324 (Advertised elsewhere in this magazine for over £15.00 each recently)  
d.c. Voltage: 0.6, 1.2, 3, 12, 30, 60, 120, 600, 1200.  
a.c. Voltage: 3.6, 15, 60, 150, 300, 600, 900.  
d.c. intensity m/a: 0.06, 0.6, 6, 60, 600, 3000  
a.c. intensity m/a: 0.3, 3, 30, 300, 3000.  
d.c. resistance: 0.2, 5, 50, 500, 5000, kOhm.  
g.e. level dB: 10 to 12.



**FANTASTIC SPECIAL PRICE** £12.00 including P.P and VAT

#### TRANSFORMERS

British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v:	4.5-0-4.5v	400m/a	50p	45p	35p
240v:	6-0-6v	100m/a	58p	52p	43p
240v:	6-0-6v	500m/a	85p	60p	48p
240v:	9-0-9v	200m/a	75p	70p	58p



#### EUROPEAN ADAPTORS



Manufacturers note: We can supply FROM STOCK, 1000+ quantities of the above transformers and adaptors below.

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit the UK shaver socket.


REF.	D.C. Voltage	Current	1+	10+	100+
E08	4.5V	200m/a	50p	45p	32p
EM3	6V	200m/a	£1.00	80p	55p
E09	6V	400m/a	£1.50	£1.25	85p
ET4	9V	150m/a	£1.50	£1.25	85p

Please note that there is no extra P/P charge on the above transformers & adaptors.  
Export please add Sea/Air mail at cost.  
Callers welcome Mon-Fri 9-5.

This advert is only a fraction of our range, send 25p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to:

Dept. ETI, MARCO TRADING,  
The Old School, Edstaston, WEM, Shropshire SY4 5RJ.

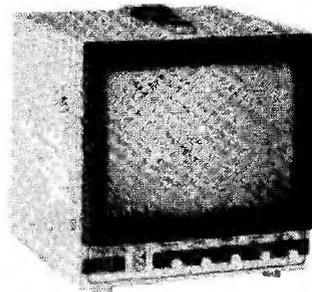Special Offer Test Equipment Catalogue available upon request. Send S.A.E. or Telephone.  
All orders despatched by return of mail. Tel: (094872) 464/465.




Metal cased 9" PM101

## CROFTON MONITOR

10 MHz Bandwidth  
P4 Standard  
Also available with P31. Price on application.

## NEW PRINCE MONITOR

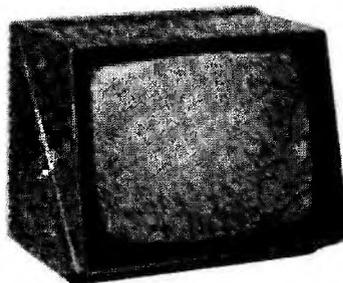

High resolution  
24 MHz Bandwidth  
P31 (green) and P4  
high resolution  
standard. Price on application.

Dealer and OEM enquiries welcome

CROFTON ELECTRONICS LTD  
35 Grosvenor Road, Twickenham, Middx TW1 4AD  
01-891 1923/1513

INFRA RED IMAGE CONVERTOR type 9606 (CV144) 1 1/4" dia. Requires single low current 3KV to 6KV supply. Individually boxed. With data. £12.50 ea. 10 off £100.

INFRA RED QUARTZ LAMPS. 230V 620 Watts Size 1 3/4 x 1/4" dia. £1.50 ea. 10 off £10. 240V 1650 Watts Size 2 1/4 x 1/4" dia. £3 ea. 10 off £25.

FANS 115V 13 Watt Size 3 1/4 x 1/4 x 1/4". Secondhand £2.50 ea. CENTAUR FANS 115V Size 4 1/4 x 1/4 x 1/4". New £4.50 ea. Secondhand £2.50 ea.

DELAY LINES 50 nanosecs. Ground-in-out. Size 2 x 7/16 x 5/16". New 25p ea. 10 off £2.

PULSE TRANSFORMERS. Sub min Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New. Suitable for Thyristor triggering. 20p ea. 10 off £1.80. 100 off £15.

MOTORS 12V DC with pulley & semiconductor speed control. New £1 ea. 10 off £8.

DIAMOND H CONTROLS ROTARY SWITCH Single pole 10 way. Printed circuit mount. New 10p ea. 100 off £7. 1600 off £50.

STEPPING MOTORS - 200 Steps 20 oz/in torque. 12/24V Input 5 wire. £12 ea.

STEPPING MOTORS - 200 Steps 20 oz/in torque 120V input 3 wire. £4 ea.

STEPPING MOTORS 5 Volt 3.3 Amp operation 2 Wire. PPS 0-220. RMP 0-250. Used £16 ea.

STEPPING MOTORS - 6/12 position can be used as a tach. 12/24V will work on 5V £1.50 ea. 5 for £5.

SINGLE PLY TELEPRINTER PAPER. Size 8 1/2" x 3 7/8". 1.25 each or 12 rolls for £12 P&P £3.50.

BLACK RIBBONS FOR TELEPRINTERS 75p each or 6 for £4.

MIN KEYBOARD Push contacts, marked 0-9 & A-F & 3 optional. £1.75 ea. 10 for £15.

KEYBOARD PAD Size 3 x 2 1/2 x 2" high with 12 Alma Reed Switches. Blue keys marked in green. 0.9 & a star with one blank. £4 ea. 5 off £15. P&P £2.50.

DON'T TAKE CHANCES Use the proper EHT Cable 10p metre. £7.50 100 metres P&P £2.

RAPID DISCHARGE CAPACITORS 8 mfd 4kV £5 each. P&P £2.

HUNTS CAPACITOR 0.1 mfd 3kV DC Wkg. Size 1 1/2" dia x 3". £1.25 ea. 10 for £10.

E.H.T. CAPACITOR 500 pf 8kV 20p each.

DECOUPLING CAPS 0.05mfd 10V, 0.01mfd; 0.047 250V; 330pf. 100 off one type £1.50.

CAPACITORS all as sp each. 3300pf; 220nf 250V. 0.01mfd 160V; 0.1 of 400V.

REMO TV Type MULTIPLIER. Two high voltage outputs & focus £1 each. 10 for £8.

RANCO 250V 18A THERMOSTATS with Control Knob calibrated 50 200°C £2.50 each.

MICROPHONE/EARPIECE INSERTS Ex Min. Brand New wrapped. 75p ea. 10 off £6.

TRANSFORMERS - All Brand New.

Auto 240V Input 115V 1 Amp output £1.25 ea.

240V Input Sec 6V 1.8A. Size 2 1/2 x 2 x 2". Good quality £1.50 ea.

240V Input Sec 12V 100MA. Size 60 x 40 x 42mm 50p ea.

240V Input Sec 12-0-12V 50MA. Size 53 x 45 x 40mm £1 ea.

115V Input Sec 5V 250MA Size 1 1/2 x 1 1/2 x 1 1/2". 2 for 50p.

240V Input Sec 2 windings 12V and 24V 1 Amp. Size 2 1/2 x 2 x 2". £2 ea.

Sub-Min 0.120-240V Input Sec 12-0-12V rated 4VA. 75p ea. 10 off £6.

100 off £45.

TOROIDAL 0-115-230V input. Output 13.5-0-13.5V rated 8VA. £1.70 ea. 10 off £15.

TOROIDAL 0-120-240V input. Output 0-12V. 10VA per winding. Encapsulated identical to R.S. Components at £9.40. OUR PRICE £5 ea.

TELEPHONES - P&P £1.50 ea. 5-10 units P&P £6. Over by arrangements. 706 style Black, Grey, Blue, Green £5.50 ea. 10 off £45. Discoloured £4 ea. 10 off £27.50.

746 style Black or Grey £7.50 ea. Older Black style £2.50 ea.

SOME EHT TRANSFORMERS & CAPACITORS always available - please enquire.

VARIACS - 2 Amp. Ex-equipment. Good condition. £12 ea. P&P £3.

TRANSISTOR INVERTOR. 115V AC 1.7 Amp input Switching at 20KHz. Output windings from Pot Core. Can be rewound or broken for components. Circuit Supplied. £1.25 ea. P&P £2. 10 off £10 Carriage £6.

Convert this unit to a SUPER BATTERY CHARGER. Attractive green ministry quality case - removable top/bottom plates - heavy duty power switches - high power resistors to control current - centre mounted amp meter - wing nut terminals on front panel for connecting leads. £3.50 ea. P&P £5 FOUR UNITS £12 Carriage £6.

Miniature VARIAC 0.6 amp in Blue Case size 10 1/2 x 6 1/4 x 6 1/2" with 20 coloured screw style 4mm sockets giving multiple voltage & current outputs. As new £12 P/P £4.

AMPLIFIER BOARD complete with Heat Sink & two output Transistors type 2N5293 Circuit supplied £1.50 ea.

CABLE TIES Black 13cm long or White 9cm. 50 for 50p.

TOGGLE SWITCH. Centre off. 20p each 10 for £1.80.

4 CORE CURLY WIRE extending to 2 metres. 20p ea. 10 off £1.80; 100 off £15 Min Potentiometres. - Erie. 1K Lin; 3.3K Lin; 4.7K Lin. All 15p each. 100 off £12.

WIRE WOUND RESISTORS 4 WATTS all at 10p ea; 10 off 85p; 100 off £7 Values - 100; 2R2; 2R4; 750R; 22K 1R5; 82R; 100R; 150R; 820R; 9K1; 15K. MULTICORE CABLE. 18 Way. Multicolour. 75p per metre. 100 metre drum £55. Carr £6.

GEC 4 Button UHF TUNER £1.50 ea. 10 off £12.

GEC 6 Button UHF/VHF TUNER. £2 ea. 10 off £15.

SOLID STATE UHF TUNER 38MHz £1 ea. 10 off £8.

PHOTOMULTIPLIERS - All with information - P&P all tubes £1.50 ea. British 2" window £2 ea; American 2" £3 ea; RCA type 2020 £4 ea. Special American by RCA £6 ea; MULLARD 150AVP Useful dia 32mm £4 ea.

HONEYWELL STRIP CHART PAPER 1221 rolls. Ref no 378528-0100 EVEN 12/89; 50p per roll; 10 rolls £4 P&P £3.50.

BLUE THERMAL PAPER 430ft roll 8 1/2" wide £1.50 per roll P&P £2. 6 rolls £6. Carr £6.

FOR FULL COMPONENT & TEST EQUIPMENT LIST WRITE OR PHONE

WAYNE KERR BRIDGE B221 ..... £70 ea.

WAYNE KERR UNIVERSAL BRIDGE B521 (CT375) ..... £50 ea.

MARCONI SIGNAL GENERATOR TF801D/IS 10-485 MHZ ..... £65 ea.

AVO VALVE TESTER CT160. .... 20 ea.

ADVANCE AUDIO SIGNAL GENERATOR J1A ..... £30 ea.

**TELETYPE PRINTERS**

ASR33 ASCII keyboard with 8 bit paper tape punch and reader ..... £75

KSR33 (No punch and reader) ..... £50

PDP8 in 6ft RACK CABINET ..... £100

**AVO SIGNAL GENERATOR**

No. 2 AM/FM AM 0.05-225MHz FM 26-100MHz £75 each

**ISOLATING TRANSFORMER**

240V Input 240V Output 1300 Watts £15 each Carr. £6

**TEKTRONIX PLUG-INS**

TYPE D Single Trace High Gain DC Differential ..... £20

TYPE E Single Trace Low Level AC Differential ..... £20

TYPE G Single Trace Wide Band DC Differential ..... £25

TYPE L Single Trace 30MHz High Gain ..... £25

TYPE M 4 Trace DC 20MHz ..... £125

TYPE O Operational Amplifier ..... £96

TYPE Q Transducer & Strain Gauge ..... £75

TYPE R Transistor Rise Time ..... £75

TYPE TU-2 Testing ..... £25

TYPE W Differential Comparator ..... £125

TYPE Z Differential Comparator ..... £75

TYPE 1A5 DC-50 MHz Differential ..... £75

TYPE 1S1 Sampling ..... £175

**MULTIMETER**

Russian type 4324 AC/DC volts; AC/DC current; ohms etc. Brand new, boxed £12.50 each P&P £2.50

**SINE & SQUARE WAVE AUDIO GENERATOR**

240V Input 240V Output 1300 Watts £15 each Carr. £6

**SCOPE STYLE CASE** size 7 1/2 x 7 1/8 x 13 1/2" deep with attractive blue covers & strap handle. As is a TACHISTOSCOPE but ideal for the home constructor for parts. £4.50 each P&P £2.50

**KEGAMI 20" BLACK & WHITE MONITORS**

Solid State. Video in. Int & Ext Sync. £75 each.

**TV TEST EQUIPMENT**

KORTING COLOUR BAR GENERATOR DUAL STANDARD £150 each

LARGE BAR COLOUR BAR GENERATOR Type T22 £90 each

RANK EHT METER 0-30kV £35 each

VIDEO CIRCUITS TUBE TESTER type V33 Carriage all units £6 £45 each

MINIMUM ORDER OF GOODS £3. MINIMUM PACKAGING & POSTAGE £1.50. VAT at 15% MUST be added to TOTAL of GOODS & PACKAGING, BUT PLEASE ensure sufficient monies is sent to cover PACKAGING and Postage to avoid delays in us dispatching your order. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

# CHILTMead LTD


NORWOOD ROAD, READING

TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

Please mention **E.T.I.** when replying to all adverts

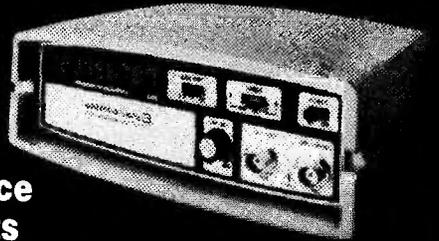An entire range of low-cost high-performance instruments



**sabtronics**

'Making Performance Affordable'

- |        |   |        |   |
|--------|---|--------|---|
| *2010A | 3 1/2-Digit L.E.D. Bench DMM                              | 5020A  | 1Hz-200KHz Function Generator           |
| *2015A | 3 1/2-Digit L.C.D. Bench DMM                              | *8110A | 100MHz 8-Digit Frequency Meter          |
| 2020   | 3 1/2-Digit L.E.D. Bench DMM with Microcomputer Interface | *8610A | 600MHz 8-Digit Frequency Meter          |
| 2033   | 3 1/2-Digit L.C.D. Hand DMM                               | *8610B | 600MHz 9-Digit Frequency Meter          |
| *2035A | 3 1/2-Digit L.C.D. Hand DMM                               | 8000B  | 1GHz 9-Digit Frequency Meter            |
| *2037A | 3 1/2-Digit L.C.D. Hand DMM with Temp.                    | 8700   | 10MHz Universal Frequency Counter/Timer |
| LP-10  | 10MHz Logic Probe   | PSC-65 | 600MHz Prescaler                        |
|        |   | 9005   | 5MHz Single Trace Oscilloscope          |
- \* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from: **BLACK STAR LTD., 9a Crown Street, St. Ives, Cambs. PE17 4EB**  
Tel: (0480) 62440. Telex 32339



AUDIO VIDEO SERVICES				MEMORIES			
19 Galsworth Avenue, Romford RM6 4PX				LS174	68p	2102	105p
Mail Order: CWO Please add 40p P&P				LS175	58p	2114-3	105p
VAT 15%. Send sae for price list				LS221	70p	2114L-3	145p
TTL	74109	35p	4025	16p	LS242	95p	
7400	10p	74121	32p	4027	27p	LS244	85p
7402	10p	74123	35p	4029	75p	LS245	110p
7403	14p	74141	45p	4040	60p		
7404	14p	74151	40p	4046	70p	TRANSISTORS	
7407	25p	74153	40p	4049	28p	BC107/8	11p
7409	17p	74157	60p	4050	28p	BC109	12p
7410	14p	74160	55p	4051	62p	BC147/8	9p
7413	25p	74161	55p	4052	62p	BC182/4	9p
7414	34p	74162	54p	4053	62p	BC157/8	10p
7416	25p	74164	55p	4055	60p	BC212/4	9p
7420	14p	74174	70p	4060	85p	BCY71/2	22p
7426	28p	74175	70p	4066	35p	BD131/2	40p
7430	15p			4069	17p	BF194/7	10p
7438	26p			4081	22p	BF259	32p
7441	55p	CMOS-B		4082	22p	BFY51	30p
7442	40p	4001	12p	4083	22p	BU208	150p
7447	45p	4002	12p	4084	22p	2N3055	44p
7451	16p	4009	12p	4511	55p		
7454	16p	4011	14p	4518	85p	DIL SOCKETS	
7473	26p	4012	18p	4520	65p	Low Profile	
7474	25p	4013	33p	4543	115p	8 pin	8p
7486	25p	4016	28p	4555	40p	14 pin	9p
7490	25p	4017	50p			16 pin	10p
7492	35p	4020	60p	74LS		18 pin	16p
7493	30p	4023	19p	LS00	12p	24 pin	20p
74107	32p	4024	39p	LS02	15p	28 pin	24p
				LS03	15p	32 pin	32p
				LS04	15p		

# SLOT CAR CONTROLLER

Some spare cash and an idle Saturday afternoon led into the labyrinthine world of slot cars. The basic slot car set is so basic that we decided to improve it, and this project is the result. Design and development by Jonathan Scott.

Well, let's not beat about the bush. Slot cars are fun. The genesis of this project was the purchase of a cheap set and the realisation that there was much room for improvement in the whole thing, especially the 'electronics'. Since then, we have built several controllers, purchased an alarming length of track, bought and modified many controllers and cars, and generally had a load of fun!

In the course of this research, use has been made of calculators, programmable calculators, desktop computers, plotters, engineering degrees, physics degrees, computer science degrees, a mound of components, a lot of paper and a hell of a lot of electricity — so be warned that one can get pretty involved. Closet racers, prepare for exposure!

## The Ultimate Controller

If you're after something really exciting, then this is it — but it's not a project for beginners. The controller gives independent supplies for each lane and can operate in voltage and current modes; it can handle a wide range of maximum torques on sets of 4V5 to 12 V rating.

For superior performance, the controller has several 'extras'. First, there is *fuel tank simulation*; this means that the control box has a meter which represents fuel in the car. A button 'refuels' the car, provided it is stationary. When it has petrol, you can go again. As the petrol is used up the car gets more acceleration, corresponding to the 'reduction in weight'. The degree of the effect is presettable by a resistor (R7 — or R107 for the second car). It is rather exaggerated with the value given, but this is more fun. Of course, if you run out of fuel, the car slows down and finally coughs to a stop.

Next, the project offers *controlled*

*overshoot*. If the output momentarily exceeds the level that your hand controller commands, the car responds more 'snappily'. This accelerates it a bit harder at first, corresponding to 'dropping the clutch', and brakes hard when it is slowing down corresponding to hard braking. You can even lock up, if you are too hasty!

The controller also informs you if it is folding, such as when the track is short-circuited. In the current mode, it warns of open circuit as well. It does not load the hand controller rheostats, as they do not carry the car current. (In some sets the controller handsets get very warm.) The controller is, of course, short-circuit protected.


The two modes, current and voltage, each offer their own advantages. Current mode gives torque proportional to control depression, as torque is proportional to current. It has slower take-off and generally sloppier (though perhaps more realistic) operation. It is also more immune to bad contact in the track and brushes, if you are having trouble in that direction. Voltage mode, which we prefer, gives a very tight control with a snappy response from the car; perhaps less realistic, but more fun. It seems to demand more from the drivers, though performance is considerably superior.

## Construction

Construction of this unit is fairly flexible and will depend somewhat upon how you plan to house the unit. It is advisable to use a fairly spacious housing as this demands less careful layout and allows easy access for adjustment or debugging. The only requirement for the case is that if you are using our PCB the meters must be spaced horizontally by the required amount, as the board mounts on the meter terminals.

First step in the construction is to drill the case and panel. Note that the power supply transformer and rectifier-filter components are not included on the PCB and are mounted on the case in a convenient position. You will have to position these components so that they do not foul any other components, and drill the case to suit. The power supply components are mounted off-board for a number of reasons. First, they are bulky and would add seriously to the PCB size and the space needed for it, and second, it means that a set of higher current capacity diodes and a higher VA-rating transformer may be used for powering more than two lanes. A 40 VA transformer will power two lanes, a 60 VA will power up to four lanes.

We found it convenient to mount

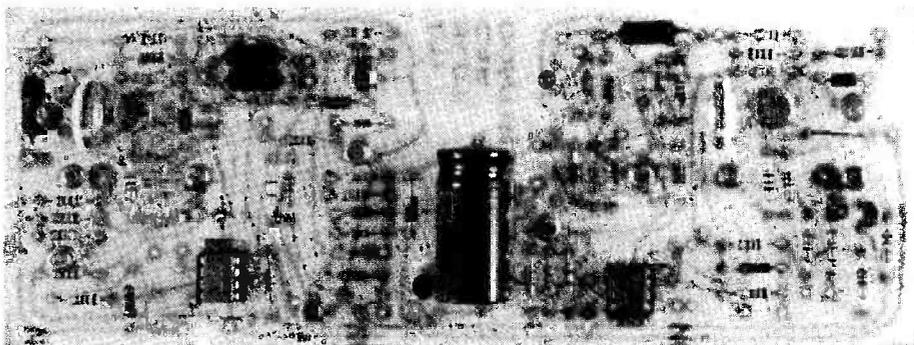

The slot car controller board before interwiring.

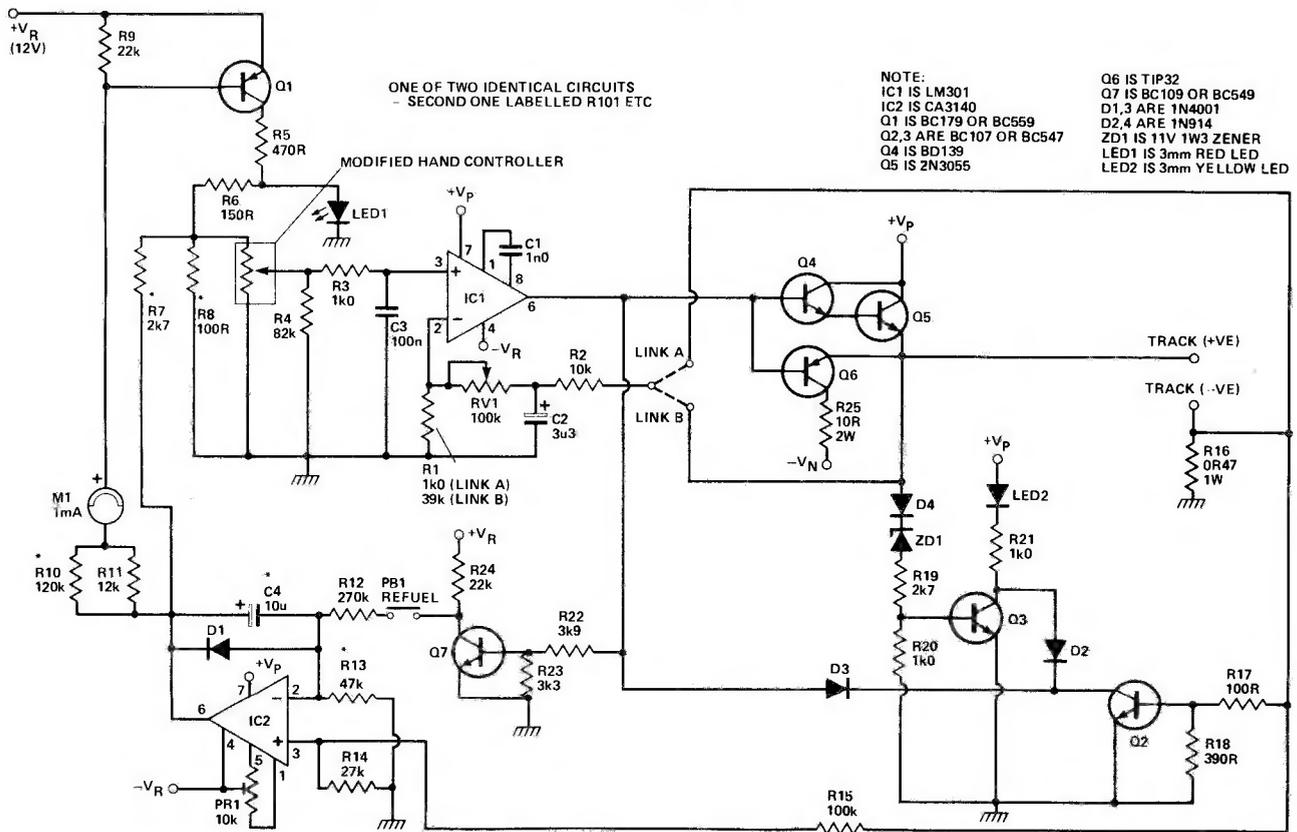


Fig. 1 Circuit diagram of one channel of the controller.

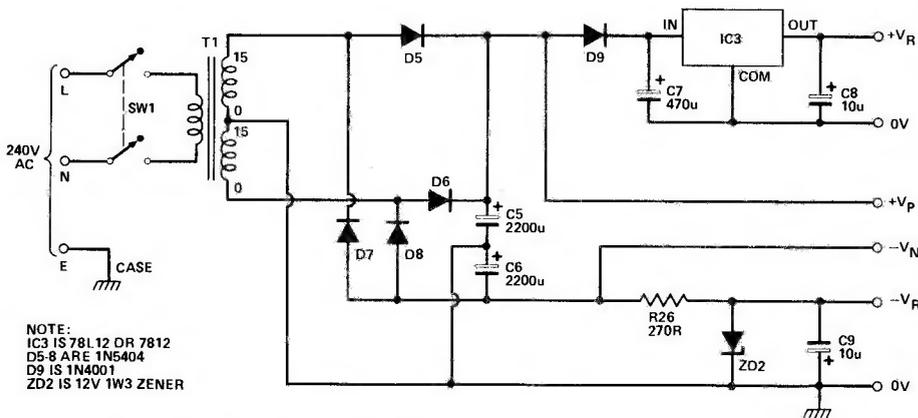


Fig. 2 Circuit diagram of the power supply.

the mains supply terminating block, cable clamp (or clamp-grommet), output terminals and presettable pots (RV1, RV101) on the rear panel of our box. We used ordinary potentiometers for RV1 and RV101, rather than preset types, cut the shafts short and cut a slot in the end of the shafts. To avoid fouling other components, mount the pots so that they are below the height of the transformer.

Next, prepare the front panel. Drill it first, locating the meter holes carefully as the PCB determines their spacing. For panel marking we used rub-down lettering (such as Letraset, etc) put directly on the panel after cleaning it

Apply a spray-on lacquer to protect the panel markings. With this job finished, fit the meters, LEDs, and so on. Finally, drill the mounting holes for the power transistors, which are mounted off the board. These dissipate little heat so they merely need mechanical support.

The next step is to assemble the components to the PCB. As there are quite a few flying leads, it may pay to use pins for the termination of these to the board. Pay attention to all the usual details — orientation of tantalum and electrolytic capacitors, orientation of semiconductors, etc. Choose the components in Table 1 to suit your requirements, according to the

instructions given with the Table. When all the components are soldered in place, fit the flying leads to the LEDs and push-buttons which are mounted on the front panel, along with the meters. These can be secured and the PCB bolted to the meter terminals before the leads to the main case are fitted. Be sure that all flying leads are long enough to allow the box to be fitted together and dismantled without straining the connections. Long leads can be kept neatly 'loomed' with plastic sleeving slipped over a bunch before one group of ends is terminated.

Assemble the transformer, power supply components and potentiometers in the case next and wire them up. Take particular care with the mains wiring. The rectifier components are supported on a tagstrip and we'll leave the wiring details to you for this one.

The final step before testing is to modify the hand-held controllers from rheostats to true potentiometers. Open up the case of a controller and you will find that it consists of a short coil of resistance wire wound on some sort of former, with a wiper contact which moves along the coil according to how far the thumb or finger control is depressed. When fully released, the wiper rests in a position where it does not touch the coil. There will be two wires coming from the hand controller — one leading to the wiper and one from an end of the resistance wire. It is

## HOW IT WORKS

The unit comprises a power supply, a control section (involving IC1), a driver circuit (involving Q4, 5 and 6) and associated components, an overload protection and warning circuit (Q2, 3 etc), an 'electronic fuel tank' (Q1 plus IC2 and associated components) and a 'refuel' circuit (Q7 etc).

The circuit has two modes of operation — voltage and current. The mode to be employed is selected by means of a link on the PCB. In the voltage mode, the hand controller sets the voltage delivered to the track (and thus the slot car's motor). In the current mode the hand controller sets the current delivered to the car's motor via the track. In either mode, a potentiometer (RV1) sets the maximum value of the voltage or the current.

### POWER SUPPLY

Transformer T1 has two 15 V (RMS) secondaries, connected in series. There are two rectifier circuits — one to provide a positive supply rail, the other to provide a negative supply rail. The joining of the two secondaries provides a 0 V connection.

Diodes D5-D6 and capacitor C5 provide a nominal +21 V supply rail (+V<sub>p</sub>) while D7-D8 and C6 provide a nominal -21 V supply rail (V<sub>N</sub>). From these two rails +12 V and -12 V regulated rails are derived. The +12 V rail is achieved by IC3, a three-terminal positive supply regulator (a 7812 or 78L12). This rail is used as a reference for the hand controller and metering circuit. Capacitor C8 ensures high frequency stability for the three-terminal regulator and acts as a supply rail bypass. The -12 V rail is derived by a simple zener circuit involving R26 and ZD2. C9 is a supply rail bypass. The negative rail is limited to 12 V so that the maximum supply voltage limitation of the op-amps, which is about 36 V, is not exceeded.

### CONTROL SECTION

This centres on IC1. A certain current (which we will discuss in detail a little later) is passed through the hand controller resistance. This develops about 200 mV drop across it. Thus, when the hand controller is operated, a voltage ranging between 0 and 200 mV is applied to pin 3 of IC1, the precise voltage depending on how far the 'driver' has depressed the controller lever. C3 smoothes out any variations — many hand controllers have momentary loss of contact between the wiper and the resistance as the wiper traverses the resistance element. You may need to vary the value of C3 according to how coarse the resistance variation happens to be in your controller. For the inexpensive controllers — which are really quite adequate despite the coarse variation they provide — a value of 470nF to 1uF is suitable.

Now, IC1 attempts to drive its output (pin 6) in such a fashion as to induce the same voltage on its inverting input (pin 2) as is on its non-inverting input (pin 3).

In the voltage mode, pin 2 of IC1 is connected via RV1, C2 and associated components to the positive track terminal so that the position of the wiper on the hand control resistance sets the output voltage. In the current mode, pin 2 of IC1 is connected to the end

of the 'current sense' resistor (R16) so that current is defined by the position of the wiper on the hand controller resistance.

In either mode, RV1 — which is in series with the negative feedback path — in conjunction with R1 sets the maximum voltage or current delivered to the car's motor via the track. C2 induces some 'overshoot' in the feedback which enhances acceleration and braking according to controller movement.

### DRIVER

The driver circuit comprises Q4, Q5 and Q6 plus R25. Its function is merely to amplify the current delivered from the output of IC1.

Transistors Q4 and Q5 are connected as a Darlington pair which provides considerable current gain (the beta of Q5 is multiplied by the beta of Q4). The output of IC1 (pin 6) swings positive during acceleration (depressing the hand controller lever) and Q4-5 amplify the current, the emitter of Q5 being connected to the track positive terminal. Q6 is reverse biased during this time. During braking, pin 6 of IC1 can go negative (particularly if you 'drop' the hand controller lever). This reverses the voltage delivered to the track or reverses the current flow (depending on which mode you're employing). When this occurs, Q4 and Q5 are reverse biased and Q6 is forward biased — and it amplifies the negative excursions from pin 6 of IC1.

The function of R25 is to protect Q6 against momentary current overload.

### PROTECTION

The protection circuit involves Q2, Q3 and associated components. If the voltage output to the track exceeds about 13 V, ZD1 and D4 conduct, forward biasing the base of Q3. When Q3 turns on, it draws collector current via LED2 and R21. LED2 lights, providing warning of a fault. If the output current exceeds about 1A5 the current through R16 (which is in series to the supply to the track) induces a voltage drop across it of about 0V7 or so and this forward biases the base of Q2 via R17 and R18. Q2 thus turns on and it draws collector current via D2, R21 and LED2. However, the collector voltage of Q2 will be around a few hundred millivolts and the output of IC1 will be shunted to the 0 V rail via D3 and the collector-emitter junction of Q2.

Thus, you receive a warning of supply overload and the supply, track etc., is protected against overcurrent damage.

### FUEL TANK

The 'fuel tank' is simulated by IC2 and associated components. This op-amp is connected as an integrator. A 'full' tank corresponds to 0 V on the output of IC2, an 'empty' tank to about 12 V. As current flows through the load (car motor), and hence via R16, a voltage is dropped across R16. This voltage is integrated by IC2 which has an RC network (R13-C4) in the feedback loop. As more load current is drawn, pin 6 of IC2 rises towards 12 V.

The meter, M1, indicates the output voltage of IC2 and is marked like a fuel gauge. While the fuel tank is full or partially full, the current through M1 flows via the base of Q1,

forward biasing it. Thus, Q1 is held on while this current flows. The collector current of Q1 flows via LED1 (the hand controller and associated resistors). LED1 lights, indicating you have fuel in the tank. When the fuel 'runs out', pin 6 of IC2 is at 12 V and no current flows through M1; thus the base of Q1 receives no bias and it turns off. LED1 extinguishes at this stage and no voltage is delivered to the hand controller. IC1 interprets this as if you have the controller set to the rest or off position and no power is supplied to the track. Your car stops.

The 'capacity' of the fuel tank is defined by the values of C4 and R13. The values shown give a 'full tank' of about 60 amp-seconds — which corresponds to about 30 rapid laps of a 2½ metre long track in 1/64th scale. The values of C4 and R13 may be varied to suit your taste, as indicated in the table on page 33.

While there is fuel, LED1 is on and its terminal voltage is about 1V7. This voltage permits about 10 mA to flow through the resistance of the hand controller via R5. (Recall we have yet to see what its current is.) In addition, R7 permits some current to flow into the controller — generally between 0 and 5 mA — from pin 6 of IC2. This current increases as fuel is 'used up', corresponding to the car getting lighter, and you get more acceleration at any particular hand controller setting as you 'use up' fuel. R7 defines how much more acceleration is obtained when the car is 'lighter'.

When the fuel runs out and Q1 turns off, the current delivered through R5 to the hand controller plummets and only the 5 mA flowing via R7 is available. This gives a 'soft' end, allowing you to limp to the pits — if you aren't too far away on the track.

The parallel combination of R8 and the hand controller should be around 15 ohms. If your controller has a high resistance, or you want to substitute a 1k0 wirewound pot, for example, R8 should be derived from the following formula:

$$R8 = \frac{R_{\text{CONTROLLER}} \times 15}{R_{\text{CONTROLLER}} - 15}$$

### REFUEL CIRCUIT

'Refuelling' is effected by PB1 and Q7. When the car motor is not drawing power, the output of IC1 is low (less than one volt) and thus Q7, which derives its base bias from pin 6 of IC1, is off. Pressing PB1 connects R12 to the +12 V rail via R24 and IC2 will discharge C4. The output of IC2 will drop to 0 V (which is the 'tank full' condition). Q1 will turn on again and current will be supplied to the hand controller circuit. When you power the car again, the voltage on pin 6 of IC1 will rise, the base of Q7 will be biased on and its collector will draw current via R24. Thus, if you try to 'top up' while the car is in motion, R12 will be virtually connected to the 0 V rail via the collector-emitter junction of Q7 and you won't be able to drive the output of IC2 low. In addition if you attempt to drive the car while refuelling, the refuelling action will be stopped by the same means.

necessary to have a third contact, connected to the other end of the coil (the end without a connection).

Remove the existing wires (some of these have considerable resistance themselves) and fit the two new wires, then the third. These run to the controller unit. Make sure you have plenty of length to play with. Now re-

assemble the hand controller, being careful to tie off the wires in the same way the original two were secured.

You should now be ready for a test run.

### Test Run

Make up a simple circle of track. On powering up, the car should work

to some degree. If not, stop and recheck. Once it works it is necessary to adjust the presets and so forth. PR1/101 should be adjusted to minimise 'fuel tank' circuit drift in the absence of power being delivered. (These are the integrator offset adjustments.) At this stage it is probably worth assembling the unit

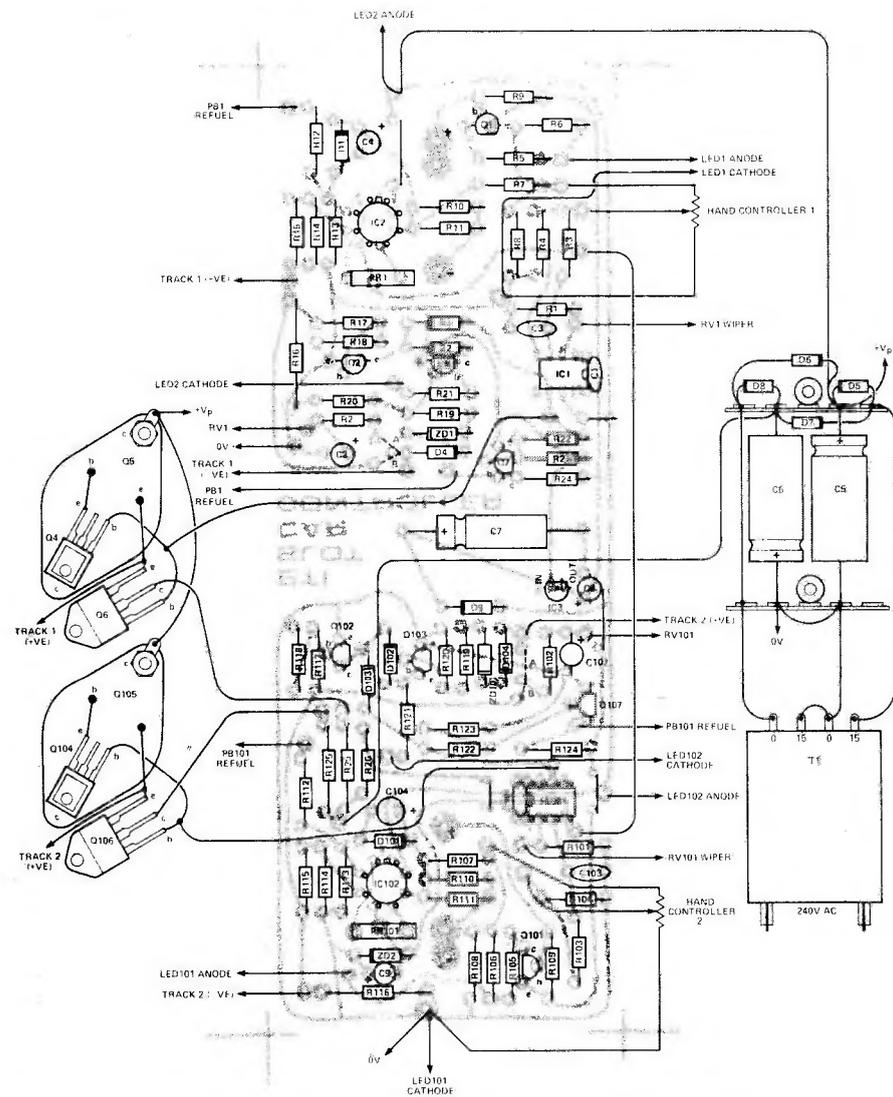


Fig. 3 Component overlay and interwiring diagram for the ETI Slot Car Controller. Note that we mounted three of the transistors for each channel on the case itself, and that some of the power supply components are mounted separately on a piece of tagstrip. The board itself is fastened to the front panel by means of the meters, which are bolted directly to the PCB (you can see the bolt heads in the photo on page 79). A choice of mounting pads is provided to allow for different meter dimensions — most 2" panel meters should fit, but check before buying.

TABLE 1

COMPONENT	NOMINAL VALUE	FUNCTION	HOW TO VARY IT
C4 (C104)	10u	Sets fuel tank capacity.	Increase its value to increase fuel tank capacity. Range: 10 to 47u.
R13 (R113)	47k	Sets fuel tank capacity, along with C4.	Increase its value to increase fuel tank capacity. Range: 10k to 100k.
R10,11 (R110, 111)	120k in parallel with 12k	Calibrates M1 for full scale deflection at 'full tank' status; allows other meter FSD values to be used.	Reduce R10 to increase reading. Choose R10/R11 to give value according to $11.4/I_{FSD}$ . This should not need much adjustment if a 1 mA meter is used.
R7 (R107)	2k7	Sets the variation of engine power with remaining fraction of fuel.	Reducing R7 gives a greater gain in power as the fuel runs out. Range: 2k2 to 22k.
R8 (R108)	100R	Sets the effective controller resistance to about 15 ohms.	Choose R108 so that R8 in parallel with the controller resistance gives a combined resistance of 15 ohms.

PARTS LIST

Resistors (all 1/4 W, 5% except where stated)

- R1 1k0 (link A), 39k (link B)
- R2 10k
- R3,20,21 1k0
- R4 82k
- R5 470R
- R6 150R
- R7 2k7\*
- R8 100R\*
- R9,24 22k
- R10 120k\*
- R11 12k
- R12 270k
- R13 47k\*
- R14 27k
- R15 100k
- R16 0R47, 1 W
- R17 100R
- R18 390R
- R19 2k7
- R22 3k9
- R23 3k3
- R25 10R, 2 W
- R26 270R

Potentiometers

- RV1 100k linear
- PR1 10k miniature vertical preset

Capacitors

- C1 Tn0 ceramic
- C2 3u3 10 V tantalum
- C3 100n polyester
- C4 10u 16 V tantalum
- C5,6 2200u 25 V axial electrolytic
- C7 470u 25 V axial electrolytic
- C8,9 10u 16 V tantalum

Semiconductors

- IC1 LM301
- IC2 CA3140
- IC3 78L12 or 7812
- Q1 BC179 or BC559
- Q2,3 BC107 or BC547
- Q4 BD139
- Q5 2N3055
- Q6 TIP32
- Q7 BC109 or BC549
- D1,3,9 1N4001
- D2,4 1N914
- D5-8 1N5404
- ZD1 11 V, 1W3 zener
- ZD2 12 V, 1W3 zener
- LED1 3 mm red LED
- LED2 3 mm yellow LED

Miscellaneous


- T1 0-15-0-15 40 VA transformer (or 60 VA)
- SW1 DPDT mains-rated toggle switch
- PB1 momentary action push-button
- M1 1 mA FSD meter
- PCB (see Buylines); case to suit (see Buylines); tagstrip; terminal block; mains cord and plug; clamp grommet; mounting hardware etc.

NOTE

The controller circuit is duplicated for the second track, so you will require two of each component with the exception of R26, C5-9, IC3, D5-9, ZD1, SW1 and T1. Components for the second controller are designated R101, C101, D101 etc.

\*Components marked with an asterisk may need alteration to suit your particular requirement (see text).

Our hand controller after modification.

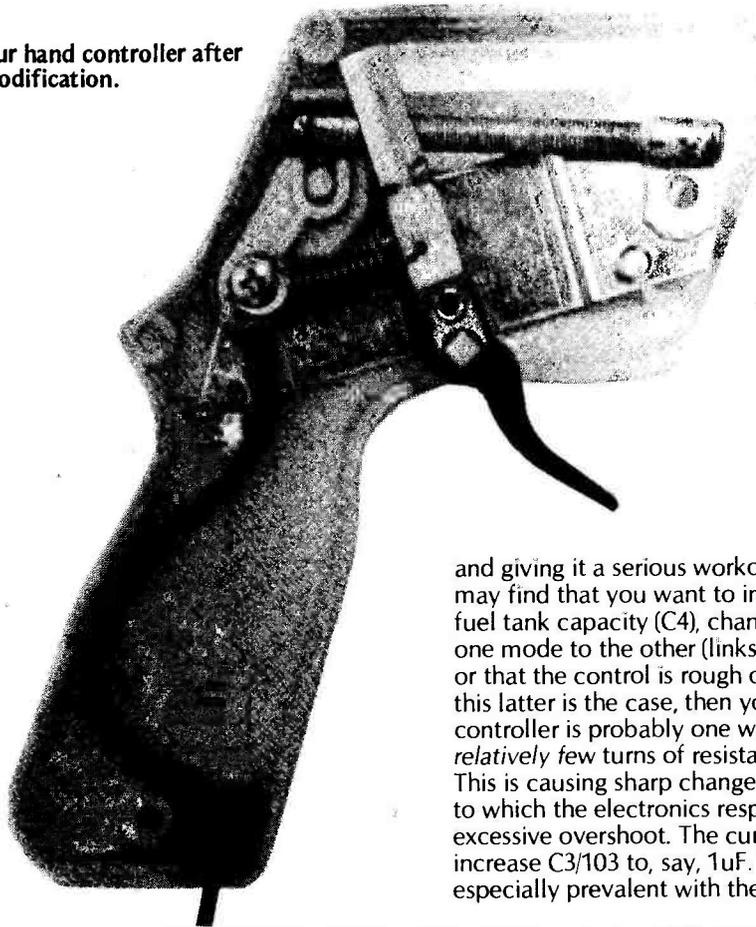

## BUYLINES

There should be no problems obtaining any of the components used in this project. Note, however, that the PCB is laid out to accept TO5-packaged CA3140s — not the D11 type — so make sure you buy the correct ones. The case we used is one from the Vero range, order no. 65-2523E, but any similar-sized one will do (about 220 x 156 mm). The PCB can be obtained from us at a cost of £3.72 by filling in the order form on page 45.

and giving it a serious workout. You may find that you want to increase the fuel tank capacity (C4), change from one mode to the other (links A and B) or that the control is rough or jittery. If this latter is the case, then your controller is probably one with *relatively few* turns of resistance wire. This is causing sharp changes in level, to which the electronics respond with excessive overshoot. The cure is to increase C3/103 to, say, 1uF. This is especially prevalent with the cheap,

6 V operated sets. After you have had a while in the seat, remove the front panel and alter the appropriate components (marked with an asterisk) in order to produce the effects desired. To find out what these are, consult Table 1.

A note should be included on the correct adjustment of the maximum torque presets, RV1/101. This is much a matter of preference. They should be adjusted so that the car does not get ridiculous amounts of power just prior to running out of fuel, but so that the car can just be crashed on full power with a full tank. It is probably also a good idea to set the two channels alike with a multimeter to ensure fairness. (Be sure to have equal amounts of fuel when doing this adjustment!)

ETI

### 8" FLOPPY DISC DRIVES

1.6 Megabyte Double Sided Double Density BRAND NEW DRE7200 Floppy disc drives at a remarkably low price.

- \*\*\* 1.6 megabyte capacity.
- \*\*\* Double Sided.
- \*\*\* Double Density.
- \*\*\* 154 // tracks.
- \*\*\* 240v AC, 24v D - 5v
- \*\*\* Well also read write single sided single density.
- \*\*\* Internal strapping allow easy to most systems.
- \*\*\* User Handbook included.
- \*\*\* ONLY £260.00 - £5 carr

### HARD COPY

These Data Dynamics R0390 printers feature silenced cases and come with a BRAND NEW print head. Most have seen little use and all may be configured for RS232 or 20 mA current loop, making them the ideal choice for most home MICRO systems.

- \*\*\* ASCII Character Set
- \*\*\* Plain paper
- \*\*\* Friction Sprocket feed
- \*\*\* 1100 Baud
- \*\*\* ONLY £65.00 - £15 carr

Cannot be repeated at this price when stocks exhausted.

Honeywell Bull D120 Hard disk - Brand new boxed ONLY £450.00  
DRE4000A (258-3901) Hard disk - Brand new boxed ONLY £500.00  
Plessey Standby Inverters - 375VA, Mains O/P from car batteries ONLY £110.00  
LOGABAX LX180 Printer upper/lower case ONLY £350.00  
Amplex TM7 1/2" Tape deck 7/9 track ONLY £100.00  
Precision Irs 1217 1/2" tape deck ONLY £100.00  
SHUGART 801 B" floppy drives ex. new equipment ONLY £200.00

CARRIAGE AND PACKING AT COST  
CALLERS WELCOME BY APPOINTMENT

**MAWSON ASSOCIATES**  
124 LENNARD ROAD,  
BECKENHAM, KENT BR3 1QP  
**01-778 3600**

WE ALSO BUY SURPLUS COMPUTERS AND COMPUTER PERIPHERALS. PLEASE RING FOR DETAILS.

Please mention **E.T.I.** when replying to all adverts

# ELECTROVALUE

INVITE YOU TO

## Read all about it!

A selection of much-demanded books from the very large stocks we carry. (More in our Catalogue 82 with over 6,000 items for constructors from a washer to a computer - 70p post free, with 70p refund voucher for use on orders £10 and over.

### TI SEMICONDUCTOR BOOKS

(All prices in TI section are Nett)

MOS Memory	£3.95	Op-Amp Selector	£6.95
Bipolar Memories	£1.00	Microprocessor Selector	£14.95
Optoelectronics	£4.00	Elektr Digibook	£5.45
Opto Theory and Practice	£6.00		
Linear Control	£4.00		
Voltage Regulators	£4.50		
Bipolar Microcomputer	£4.50		
Components	£7.00		
Interface Circuits	£7.00		
TTL Data Book	£8.50		

### BARBANI BOOKS

Selection	
BP42 50 LED Circuits	95p
BP43 Walkie Talkies	£1.50
bp44 IC 555 Projects	£1.95
BP52 TV DX	£1.95
BP57 Building a solid state oscilloscope	£1.50
BP55 Radio Stations Guide	£1.75
BP70 Radio Fault Finding	70p
BP75 Remote Control Projects	£1.95
BP85 International Transistor Equivalents	£2.95
BP211 Diode Data	£1.25
BP222 Six Receivers	£1.25
BP224 Fifty CMOS Projects	£1.35

### "Understanding Series"

Solid State Electronics	£3.95
Digital Electronics	£3.95
Microprocessors	£3.95
Calculator Mathematics	£3.95
Communication Systems	£3.95
Computer Science	£3.95

### Pocket Guides

Volume One - TTL	£3.50
Volume Two - Linear and Interface	£2.50

### COMPUTER BOOKS

All prices in this section are Nett

Programming the 280 (Zaks)	£11.50
CP/M Handbook	£9.45
Basic Computer Games	£5.95
More Basic Computer Games	£6.25
Using CP/M	£5.95
CP/M Users Guide	£10.10
Z. 80 Programming Manual	£9.50

### TOWERS INTERNATIONAL SERIES

Transistor Selector	£9.50
FET Selector	£3.50

VAT is *not* charged on books. Discounts (on book orders) - 5% on orders over £20, 10% on orders over £50 - not applicable on items marked N (nett) or where stated for sections above. Postage - Add 40p for orders for books totalling less than £5.00

**ELECTROVALUE LTD** 28E St Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB. Phone: Egham (STD 0784: London 87) 33603. Telex 264475.  
**NORTHERN BRANCH.** 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone 061-432 4945.

# GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT at 15% — just add 50p post

## ULTRASONIC ALARM — £14.95

Originally made to retail at over £50, these neat units housed in a 120 x 100 x 45mm case are brand new and boxed. They work by transmission of a 40kHz beam which responds to movement by detecting the Doppler freq. shift. Mains operated with internal buzzer and provided with data, these units are excellent value at only £14.95

## 1000 RESISTORS £2.50

We've just purchased another 5 million preferred resistors, and can make a similar offer to that made two years ago, at the same price!!! K523 — 1000 mixed 1/4 and 1/2W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values. 1000 for £2.50; 5000 £10.20k £35

## 200 ELECTROLYTICS £4.00

K524 Large variety of values/voltages, mostly cropped leads for PCB mntg. 1—1000uF, 10—63V. All new full spec components, not chuck-outs!! 200 £4. 1000 £17.50

## CHEAP CHIPS

76477 Sound IC £1.25  
2102A RAM 8 for £3  
MK4027 shift reg. 8 for £6  
uA78MG + volt reg £1.00  
uA79MG — volt reg £1.20  
74LS112 Dual Flip Flop 8 for £1  
TIL311 Hexadecim display with decode 0—9 and A—F. With data £3.50.

## CAPACITOR BARGAINS

2200uF 100V cans 80 x 40mm dia 75p; 10/£5.50;  
220uF 10V axial 5p; 100 £2.30; 1000 £16; 400 +  
1000uF 275V 102 x 44mm dia. 75p; 10 £5.50;  
2000uF 350V, 100 + 100 + 50uF 300V can 75 x  
44mm dia. 40p; 10/£3; 100/£20; 100uF 25V Axial  
£3/100;  
0.33uF 50V rad. £1.50/100, £12/1000  
0.47uF 50V rad. £1.50/100, £12/1000 elec  
22uF 50V rad £3/100, £24/1000  
Electrolytics: 10u40V PC mntg 25/£1.25 100/£3;  
4.7u/63V PC mntg same price  
1250u/25V can 10/£1.60 100/£10  
1500u/40V can 10/£2.20 100/£15  
800u/250V can 10/£5.50 100/£44  
400u/400V can 10/£8 100/£58  
100u/350V, 100 + 100 + 50/300V (all in one can)  
10/£5.00 100/£36.00

## LIE DETECTOR



Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 4 1/2 V batts. Overall size 195 x 100 x 100mm. Only £7.95 — worth that for the case and meter alone!

## SOLENOIDS AND RELAYS

W921 Solenoid rated 48V at 25% duty cycle, but work well on 24V 1700gm pull, 10mm travel) push or pull 27 x 18 x 15mm 55p  
W822 Mains 240V ac solenoid, 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50  
W895 9V DC relay 500R SPCO 28 x 24 x 19. 50p  
W733 11 pin plug in relay, 240V ac, 3PCO 5A contacts £2.50. Base £36p  
W838 700R 24V 4PCO "continental" relay 35 x 30 x 18, only 84p; 10/£7.00  
W847 37R 5—10V relay. SP 3A contact, PCB mntg 11 x 33 x 20. 95p; 10/£7.50  
W893 Omron LY4 mains relay, 4PCO 5A contacts. £2.50  
W896 24V ac coil, but works well on 6V DC. 2 x 10A c/o contacts. Ex-equip, only 60p

## MIXED LED PACK

All new full spec by Micro, Fairchild, etc. Red, Yellow, Green, Amber, Clear, 3mm & 5mm. Pack of 50 asst £3.95; 250 £15

## 5V 3A REGULATED PSU KIT

A197 All components + heat sink to build this simple yet useful power supply. A regulated output of 5V at up to 3A for just £2.50. Suitable transformer (9V 3A) £4.85.

## 741 OP-AMP — 12 for £1

A recent purchase of Raytheon IC's included a large quantity of 14 DIL 741 op-amps, so take advantage while stocks last! 12 741's £1.00.

## 1982/3 CATALOGUE

Bigger! Better!! Buy one!!  
Only 75p inc. post — Look what you get!!  
● Vouchers worth 72p  
● 1st class reply paid envelope  
● Wholesale list for bulk buyers  
● Bargain List with hundreds of surplus lines  
● Huge range of components  
● Low, low prices  
Sent free to schools, colleges etc.

## AMAZING! COMPUTER GAMES PCB'S FOR PEANUTS!!

A bulk purchase of PCB's from several well known computer games including Battleships, Simon, Logic 5 and Starbird enable us to offer these at incredibly low prices:

### 'STARBIRD'

Gives realistic engine sounds and flashing laser blasts — accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt. clip (needs PP3). PCB size 130 x 60mm. Only £2.95

### 'SIMON'

The object of this game is to repeat correctly a longer and longer sequence of signals in 3 different games. (Instructions included). PCB contains chips, switches, lampholders and lamps, and is tested working, complete with speaker. Needs PP3 and 2 x HP11. PCB size 130 x 130mm. Only £3.95

### 'COMPUTER BATTLESHIPS'

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and set the board for its component value: SN76477 sound IC; TMS1000 u-processor; bat clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra

### 'MICROVISION' Cartridges


These are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag is we don't have any consoles!! However, they can be used as an oscillator with 4 different freq. outputs simply by connecting a battery and speaker. Tested and working (as an osc) with pin out data. PCB size 72 x 60mm.

ONLY 25p each!!

## LOGIC 5 PANEL

Tested Logic 5 now sold out — but we have some PCB's with 10 LED's and chip on, but no keyboard. Not tested. 50p

## ELECTRO-DIAL

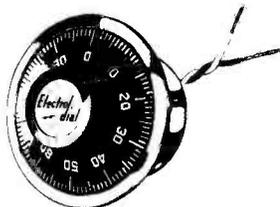

Electrical combination lock — for maximum security — pick proof. 1 million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid. Overall dia. 65mm x 60mm deep. Only £9.95  
Also available without combination — Only £3.95

## 1W AMP PANELS

A011 Compact audio amp intended for record player on panel 95 x 65mm including vol control and switch, complete with knobs. Apart from amp circuitry built around LM380N or TBA820M, there is a speed control circuit using 5 transistors. 9V operation, connexion data supplied. ONLY £1.50.

## RELAY/TRIAC PANEL MKII

Z537A PCB 100 x 75mm containing a wealth of components: 2 x 12V DPCO min relays; SC146E 10A 400V triac; 555 timer; 10 x 1N4001 diodes; 2N5061 SCR. 2 x 3mm LED's 3 x 2N3704; R's & C's — Amazing value — if bought separately, parts would cost around £8!! Our price for the panel, just £1.50.

7 HUGHENDEN ROAD, HASTINGS, SUSSEX. TN34 3TG  
Telephone: HASTINGS (0424) 438004



LTD  
ELECTRONIC KITS



KS100 MINI VHF SUPER-REGENERATIVE RECEIVER 88-108MHz 9V D.C. £5.34 inc VAT



KS272 6 CHAN HIGH POWER VU DISPLAY, 300W PER CHAN, 240V A.C. £21.29 inc VAT



KS200 MINI F.M. TRANSMITTER 88-108 MHz 9V D.C. (NOT LICENCEABLE IN UK) £7.39 inc VAT



KS238 3 CHANNEL MICROPHONE OPERATED SOUND TO LIGHT, 300W PER CHAN 240V A.C. £14.43 inc VAT



KS240 3 CHAN SOUND TO LIGHT, OUTPUT 3 X 1KW 240V £13.70 inc VAT



UK504 LOGIC PROBE, SUITABLE FOR TTL-DTL-SMOS CIRCUITS, 5V D.C. £9.86 inc VAT



KS260 3 CHAN CHASE LIGHT, 1KW PER CHAN, 240V A.C. £11.27 inc VAT



UK993 CROSS HATCH GENERATOR R.F. OUTPUT, U.H.F. INTERNAL 9V D.C. SUPPLY £22.94 inc VAT



Post & Packing, 50p per KS kit, 75p per UK kit. Send 20p S.A.E. for catalogue of our extensive range of kits & cabinets. Trade, Educational & Export enquiries welcomed.



# WILMSLOW AUDIO

The firm for Speakers

Just 50p will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits . . .

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS.  
GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS — PLUS MICROPHONES — AMPLIFIERS — MIXERS — COMBOS — EFFECTS — SPEAKER STANDS AND BRACKETS — IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our listening lounge. (Customer operated demonstration facilities)
- ★ Ample parking ★
- ★ Access Visa American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Lightning service on telephoned credit card orders!



## POWER DIMMING MODULES

- ★ Fully isolated
- ★ Multi channel common wiring lines
- ★ Master dimming over banks
- ★ Remote override
- ★ Dead "kill" and "all on"
- ★ Low voltage feed lines
- ★ Common neutral or live outputs

**Power Dimming Modules**  
A range of isolated digitally controlled dimming modules, complete with panels. Each type requires connection to the supply/reference board.

**Slave power controllers (SPC)**  
Controls up to 1000W via the slider.  
**RFI suppressed/fused**  
**Slave power unit (SPU)**  
Controls up to 1000W via a logic signal from a remote slave.  
**Master controllers (MC)**  
Will master dim from 1 to a bank of 20 SPC units.  
**Remote slaves (RS) - (Preset)**  
Will override an SPC at a remote location to the main system or control an SPU.  
**Supply/reference board**  
Provides the necessary supply voltages and signals to all units. Facilities for "Kill" and "all on." Supplies up to any combination of 50 modules.

**PRICES (1 of)**  
SPC ..... £13.90  
SPU ..... £9.90  
MC ..... £7.20  
RS ..... £8.50  
Supply ..... £18.20

Post/Pack £1.50  
Total order

**SPECIAL DISCOUNTS**  
Are available on power dimmers.  
Total your order up and deduct:  
£100 to £199 ..... 20%  
£200 to £299 ..... 25%  
£300 to £399 ..... 30%

## 3 CHANNEL SOUND/LIGHT

CHASER £35.70  
LB31000SLC


(FASCIA)  
£3.70



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti-interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

## STEREO DISCO MIXER/PREAMP

LBPA3  
M - Magnetic  
C - Ceramic

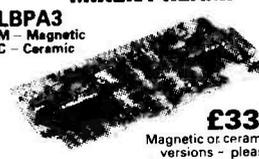

£33.70

Magnetic or ceramic deck versions - please state on one board: left and right deck mixers/controls/misc. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with either LB 100/150/250.  
PSU1 (+, - 15v for PA3) £7.20

## NEW NEW NEW

### 4 CHANNEL SOUND LIGHT AUTO-CHASER

- ★ Bass/mid/presence/treble
- ★ Automatic level filter control
- ★ Automatic input gain control
- ★ L.E.D. monitor drivers
- ★ 10Hz to 30KHz response
- ★ Super sensitive
- ★ Zero reference triggering
- ★ Fascia/LED, etc. available

★ £49.90 (panels, etc. £9.20)

Phone or write for immediate details of the LB41000SLC

## NEW NEW NEW

### 2/4/8 CHANNEL CHASER



£28.00

An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

### 4 CHANNEL SEQUENCER



£19.20

A 4 channel sequence generator for banks of lamps up to 1,000 watts each. Facilities include controls, cross effect to provide settings between seconds and rapid burst.

## PROGRAMMABLE - 8

£114.90

P/P INS  
£1.50



Complete with blue panel/white letters

- ★ 8 channel 400W each
- ★ 16, 32, 64, 128 patterns
- ★ Automatic program recycle
- ★ Adjustable cycle on/off speed
- ★ Optically isolated, suppressed
- ★ Either common Neutral or live lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be replayed in the stored order, with control over the cycle on and off time. At the end of the program the system re-cycles to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although removing the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following night's performance. The module obviously provides unlimited effects and is a must for all serious lighting shows.

## 3 CHANNEL SOUND/LIGHT

LB31000SL



(FASCIA)  
£7.70

£22.70

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

## 4 CHANNEL SOUND CHASER



A forward running Chaser with sound input speed modulation. Ideal for rope lights, etc.  
LB41000LC-S  
£24.20

Each module is manufactured from the highest quality components, fully tested, supplied with a connection diagram and guaranteed for twelve months. All prices shown are VAT inclusive. Please include 75p post/packing except where individually stated. To mail order send cheque/P.O./Registered cash/Access number. C.O.D. service £1 extra. For further information send a s.a.e. stating which model. PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

**L & B ELECTRONIC MODULES**  
PROFESSIONAL ENGINEERING BY PROFESSIONALS  
45 Wortley Road, West Croydon  
Surrey CR0 3EB. Tel. 01-689 4138  
WE ARE OPEN MON TO FRI 9 TO 5

## NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ahr	SUB 'C' 1.2Ahr	'C' (HP11) 1.65Ahr	'C' (HP11) 2.0Ahr	'D' (HP2) 4.0Ahr	PP3 0.1Ahr
1-24	£0.85	£1.38	£1.89	£2.25	£2.97	£3.79
25-49	£0.75	£1.28	£1.68	£2.10	£2.77	
50-99	£0.65	£1.15	£1.52	£2.02	£2.67	
100 up	£0.59	£1.05	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

**CHARGERS** - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04  
DUAL O/P CHARGER £5.72

**TRANSFORMERS** - as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Data and charging circuits free with orders over £10 otherwise 30p post. P&P 10% if order less than £10. 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order.

Cheques, P.O.'s Mail Order to:-  
**SOLID STATE SECURITY,**  
Dept. (ETI) Bradshaw Lane,  
Parbold, Wigan, Lancs.  
Telephone 02576-3018.

## PARNDON ELECTRONICS LTD.

Dept. No.23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.  
£1.00 per hundred mixed (Min 10 per value)  
£8.50 per thousand mixed (Min 50 per value)

Special stock pack 60 values 10 off each £5.50

**DIODES:** IN4148 3p each. Min order quantity 15 items.  
£1.60 per hundred

**DIL SWITCHES:** Gold plated contact in fully sealed base - solve those programming problems  
4 Way 86p each 6 Way £1.00 each 8 Way £1.20 each

**DIL SOCKETS:** High quality, low profile sockets  
8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.  
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

# ALARMS

## DIY KITS 'N' BITS

PROFESSIONAL EQUIPMENT AT DISCOUNT PRICES!

- KITS £32, £50, £75, £85 including full instructions
- CONTROL PANELS £18, £23, £29, £37
- BELL BOXES £6.25, £7.50
- PRESSURE PADS £1.06, £1.45, £1.95
- 4 CORE CABLE (100m) £8
- SIRENS £7.50
- CONTACTS 72p, 74p, 76p
- ULTRASONIC £34.50
- DOOR PHONES £49.42

BUY A KIT OR DESIGN YOUR OWN SYSTEM

SEND SAE OR PHONE NOW FOR FREE FULLY ILLUSTRATED CATALOGUE. IT TELLS YOU ALL YOU NEED TO KNOW!

Carriage Included. VAT Extra 10%

A.D. Electronics, 217 Warbeck Moor, Aintree, Liverpool L9 0HV 051 523 8440

Trade Enquiries Welcome

## VERY LOW DISTORTION AUDIO SIGNAL GENERATORS. (.002%) (Battery operated)


Model A0 149a  
£41.50 (p.p. £2.25)

Other models.		
146B	Kit version	£35.65
150A	(with Freq. meter)	£576.50 (illus)
113A	.02% distortion	£33.25
113K	Kit version	£26.45

Mains versions available.

S.A.E. for full lists of above plus Function Generators Milli-voltmeters, R.F. Sig. Gen. Distortion Analyser, Frequency Meters, Multi Meters etc.

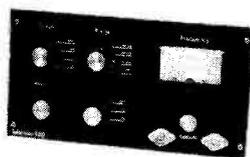**TELERADIO ELECTRONICS,**  
325, Fore St., London N9 0PE.  
01-807 3719. Closed Thursdays.



# READ/WRITE

Letters for this page should be addressed to Read/Write at our Charing Cross Road address.


Dear Sir,

I am afraid Vivian Capel, in his *User's Guide to Microphones* in the Feb. 82 issue, is not quite correct in his otherwise excellent article when he states that the resonance of a ribbon microphone is "high, near or beyond the normal range." In fact, the resonance in most ribbon mikes is in the region of 35 to 45 Hz and is usually damped by the use of resistive screens placed close to the ribbon.

One of the reasons why the ribbon type exhibits a warm, natural tone is that the resonance is low down and not at, or above, the high frequency range as is the case with capacitor types, some of which display a very hard tone especially with stringed instruments. The upper end of the ribbon's frequency response trails away gradually and this gives the warm tone when compared with the capacitor.

For further information I would refer Mr. Capel to the excellent BBC Engineering Monograph No. 4 of 1955, which gives a lot of detail on the design of ribbon microphones.

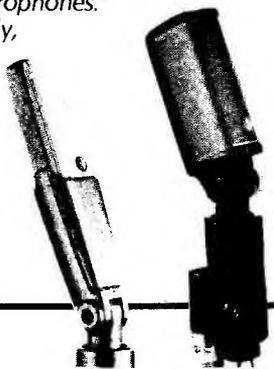Yours faithfully,  
Cyril Gott,  
Southall.



Dear Sir,

Did you know ETI has improved a lot lately. This is the first time I've ever written to a mag, I hope you will print this in your next ETI and answer my following questions:-

- 1) The Pest Control Feb 82 — can it give out more power, because I tried it near a cat and it didn't do anything.
- 2) The Computer Expansion System — can it be used on the VIC 20 and what is the difference between RAM and ROM.

Yours faithfully,  
Sukkin Pang,  
Harlow.

PS. Keep up the good work.  
PPS. Happy birthday.

1) Stepping up the supply voltage would give more power but isn't recommended because the components would complain! It

shouldn't really be necessary to get more power — we had a phone call from a large shopping centre whose automatic doors were letting in all the local cats and dogs until they fitted one with an Allez-Cat, whereupon the animals fled. They now intend using Allez-Cats on all the doors; are you sure the cat in question isn't deaf?

2) The computer expansion will work with the VIC 20; we'll provide details of how to do this in a later issue. RAM is random access memory which is easy to alter but forgets everything when the power supply is disconnected. ROM is Read-Only Memory which retains information even when the computer is turned off, but in the form the hobbyist normally uses (EPROM) data can only be changed by erasing the chip under ultraviolet light and then reprogramming it using a special series of pulses.

Dear Sir,

I recently purchased an amplifier kit from Hart Electronic Kits Ltd, Oswestry. When built, it worked the first time. The quality of parts was excellent and the packing was very good. Even the finish was first-class. However, there was one small omission — no base for the relay.

Upon phoning them (a lady was very helpful) the missing part arrived by return of post. So I am very pleased and will use this firm again because they obviously wish to provide a good service and should be encouraged. If you publish these facts in your *Audiophile* article perhaps other readers may benefit.

Oh yes, I almost forgot, I enjoy your magazine; especially the way things are explained, because it's hard to teach old dogs like me new tricks. Please keep *Audiophile* going — it's a great little article. I have purchased the Coral MC88F from your suggestion and, again, am very pleased with it — anyone should be at that price.

Cheerio now and watch that blood pressure!

Yours faithfully,  
L.T. Bowler,  
Cardigan.

My thanks for your medical meditation. My blood pressure is firmly under control at most times in life (the

exceptions are those things worth living for. . .). It is a welcome change to hear tales of wonder rather than of woe. Any other readers who can recount the good and chivalrous deeds of companies — let's hear about it! We could all do with good news these days.

Dear Sir,

With reference to your article *Pickup Amp Design*, Jan. 82.

I have a problem in determining the correct values of C and R to accommodate the pre-1955 standards for 78 rpm records where the bass turnover frequency can be between 300 Hz to 450 Hz depending on the manufacturer. Also the 50  $\mu$ s time constant gives a 3 dB point at a different frequency from post-RIAA.

I would be grateful if your next article in the series could contain a figure to indicate the values of C and R for the time constants 3180  $\mu$ s, 450  $\mu$ s and 50  $\mu$ s. Is it also desirable for the reasons mentioned in the article to attenuate the bass as per new RIAA?

The text and Fig. 2 of the article both indicate the old RIAA bass time constant to be 3150  $\mu$ s, should this be 3180  $\mu$ s?

Can you please pass this letter to Mr. Tilbrook.  
With thanks,  
Yours faithfully,  
R.F. Butson,  
Cardiff.

Your comments will be passed on to Dave Tilbrook; unfortunately he writes for our Australian edition, so it may be a while before we get a reply!

Dear Sir,

Re: Computer Controlled Live Music, Feb 82.

In recent months I have begun to see many cases of micro for micro's sake but I believe that some of the ideas in this article have blown the subject up out of all proportion to its usefulness and have gone about using it in the wrong way.

I am speaking from the point of view of someone who is working towards the use of computer (don't forget common-or-garden digital) control for both live music and studio recording and I have talked with several professional and semi-professional engineers and musicians about the subject.

Some of the points that have arisen are these:

- 1) Any small band (such as those at which this article was aimed) not using a

PA and/or mixer system, does so because they can't afford such things, or they want to keep their set-up simple for the benefit of the music. No one in this situation is going to want to buy a £500 micro and display to control their two or three amps.

2) I have never seen a band without a mixer, who are content to leave their amp and effect controls alone throughout a set, because they 'couldn't hear themselves' or they 'thought it could be that little bit better'. The point that arises here is that either the black box takes over from the amp controls completely, which no self-respecting musician would allow, or the controls work in parallel to the computer. In this case any itchy fingers on the controls would render any future changes by the computer totally wrong.

3) Any computer control system for live music must be continuously monitored and updated. No two live performances are exactly the same, especially since any mix in an empty hall is generally wrong once you've got an audience. Such continuous control can only come from an engineer sitting at some sort of mixing console. For instance, what would happen if half way through your ZX81-controlled set, someone knocked the 16K RAM pack? The best place for any computer in a PA chain is therefore within the arm span of some single completely trustworthy person.

A live music system with computer control can therefore be reduced to a computerised, or even just digital, mixing desk. EQ changes during a performance are usually few and far between and stereo panning at high sound levels is too subtle for constant use and so can be left to the human side of the band (if there is one left). Your hyper-expensive-computerised-personal-amplifier system is thus reduced to a bank of voltage controlled amplifiers linked up to a small memory. You don't even have to spend a thousand quid on a Roland Computamix to do it either. Such a system comes into its own if it is part of the mixing desk in the first place.

No band or individual musician should be given the idea that if you don't tag along with computers you'll get left behind. It is the exception rather than the rule that any home brewed micro-systems will ever improve your music or even save time. If you want to use a computer for live music, first check your motives and reasons and if you're still certain, then start with it cheap, simple and easy to operate. It saves wasted time and money and the loss won't be so great as to put you off computers for good.

Yours,  
Dave Pallant,  
London.



Dear Audiophile,

Two years ago I built ETI's Audiophile 4000 system, the power amp is, I think, a very good design and the sound quality, for which I can vouch, is of the best quality.

I have used this power amp with many preamps including the one designed for the 4000, although in the case of the 4000 preamp I did a mod by deleting the filters.

Last year when System A was published I built the preamp with MM input because I thought it offered improvements over the 4000 preamp and also there are no tone controls.

I didn't really expect such marked improvement as I have got from this combination of '4000 power amp and System A preamp'. The improvement in sound detail, separation, clarity and bass response is really satisfying.

I wonder if any other readers have tried this combination.

I am about to change my tuner, it is an old Sony STR-6040 tuner amp from the early seventies but I only use the tuner section, it has been the most reliable piece of equipment I've ever owned. I am interested in a Sony ST-J75 tuner which I have seen mentioned in two of your Audiophile articles. I wonder if you would comment on its pros and cons.

My present system consists of:  
System 'A' preamp with MM input  
Audiophile 4000 power amp  
Thorens TD160S SME Mk III with  
Technic EPC 205 Mk III  
Technics RS615 Cassette Deck  
Rogers Studio 1 Speakers

I have noticed that you never published a MOSFET Power Amp, I wonder why?

In conclusion I am a very satisfied reader of your very good magazine.

I remain,  
Yours faithfully,  
I.R. Worrell,  
Wood Green.

**The ST-J75 is a good tuner. A full review appeared in ETI June '81. It is capable of very clean reproduction indeed and should serve you well. (Listen to the Revox too if you get the chance.) Against the Sony is the fact that it could handle large scale works a little better than it does, having a tendency to sound confused. A minor blemish though.**

**What do you mean, we haven't published a MOSFET amp? Of course we have. As punishment for not knowing instantly which issue it was in I'm not going to tell you! Look to your indexes, sir.**

Dear Mr Harris,

Your excellent magazine's latest article on 'Buying Mail Order' has prompted me to contact you.

I am currently trying to start my own business and most of the suppliers I am using at the moment are companies I have used in the past through my hobby.

The different ways in which companies treat their customers is almost unbelievable, and I think that if a magazine could run a 'league table' of particularly good and terribly bad suppliers it would be a useful guide to prospective customers and would also encourage suppliers to keep on their toes.

Example 1: I am in the process of buying a VDU for my home computer which I am adapting for business use. I wrote to two of your regular advertisers that claim to have VDUs for sale. In both cases I have asked for technical data, warranty conditions if any and delivery time and price.

Neither company has bothered to reply to my enquiry! — but they are both still advertising VDUs. I wonder why, if they will not sell them?

Example 2: I was recently stuck for some resistors. I had purchased some instrument kits and two kits were short of odd components. I telephoned to see if they could help out. They quoted me a fairly good price and said that they would despatch ASAP.

I couldn't believe it when the Postman handed me a 'Jiffy Bag' the following morning with all my resistors. Quite something when I tell you I hadn't rung until 4 pm the previous day and my mail arrived at 7.15 am!

One final point.

Some components that are used in vast quantities are rarely ever advertised, eg insulating materials, hardware such as screws, nuts and washers, grommets, etc and, most of all, wires and cables.

It doesn't matter how complex your PCB might be, it has to connect to the outside world sometime. But if nobody advertises wire, how do we do it?

Yours faithfully,  
C.R. Tattersall M.Inst.E.,  
Haslingden.

**If we did as you suggest and started publishing blacklists, the libel suits would start flying around faster than insults in the House of Commons!**

Dear ETI,

Thank you for at last introducing the READ/WRITE forum.

Yours faithfully,  
D.P. Allen,  
Wembley.

ETI

# NAMAL ASSOCIATES

No. 1 CLAYGATE ROAD, CAMBRIDGE CB1 4JZ

Tel. 0223 248257 TLX 817445

## COMPUTERS

We stock computers and accept Sinclair ZX 81 in part exchange. Minimum of £20.00 is offered for your ZX81 in part exchange for a VIC 20 or Arcom colour Computers.

## NEW

**Domestic cassette INTERFACE for VIC 20 ONLY £17.00**

Simply connects your VIC 20 to any Cassette player. A bargain at half the usual price.

## NEW

**VIC 20 Memory expansion Packs**

3K RAM ..... **£21.00**  
8K RAM ..... **£58.70**

(Expandable to 16K)

16K RAM ..... **£83.48**

Simply plug into the existing expansion port of VIC 20.

Battery Ram backup available. Price on application.

### Computer I.C.s

2144-200	.99	27	.12	132	.44
2144-200LP	.99	28	.15	138	.33
2532	4.10	30	.12	145	.74
2716	1.95	32	.12	148	.95
2732	4.10	33	.16	151	.30
4116-150	.75	37	.15	153	.28
4116-200	.65	38	.15	154	.80
6116	4.75	40	.12	155	.38
5516	7.50	42	.33	156	.36
6800	2.75	47	.38	157	.30
6802	3.60	48	.59	161	.37
6809	8.75	49	.59	162	.40
6810	1.15	51	.59	163	.38
6821	1.15	54	.14	164	.46
6850	1.40	55	.12	165	.90
8085A	5.25	73	.21	173	.69
8224	1.85	74	.16	174	.46
8228	3.75	75	.24	175	.46
8255	3.30	76	.20	193	.45
Z80 CPU	3.25	78	.19	196	.57
Z & ACPU	3.60	83	.44	197	.60
Z80 P10	3.60	85	.60	240	.87
Z80 AP10	3.60	86	.15	241	.87
Z80 CTC	2.75	90	.30	242	.78
Z80 ACTC	3.25	91	.74	244	.60
		92	.33	245	.88
		93	.33	247	.60
		95	.42	248	.60
		109	.21	257	.43
		112	.21	259	.78
		113	.21	266	.22
		123	.43	273	.70
		124	.90	290	.55
		125	.24	373	.70
		126	.25	374	.72
				393	.60

### Voltage Regu:

7805 5V +	.35
7812 12V +	.35
7812 15V +	.35
7905 5V +	.35
7912 12V	.35
7915 15V	.35
7924 24V	.35
LM323K	3.00

### Crystals

100Hz	2.75
2.00MHz	2.65
3.276MHz	1.00
3.579MHz	1.00
3.932MHz	1.00
4.000MHz	1.58
4.194MHz	1.35
6.000MHz	1.00
6.144MHz	1.25
6.400MHz	1.50
10.000MHz	1.50

### IC Sockets

8 PIN	.06
14 PIN	.09
16 PIN	.09
18 PIN	.13
20 PIN	.14
22 PIN	.17
24 PIN	.18
28 PIN	.25
40 PIN	.25

### 74LS Series

00	.10	109	.21
0104	.12	112	.21
05	.14	113	.21
08-13	.12	123	.43
14	.38	124	.90
15-22	.12	125	.24
26	.16	126	.25

### WE GUARANTEE FACTORY PRIME PARTS

In depth stocks. Competitive prices. Government and colleges orders welcome. Please inquire for special prices for quantity orders. Please add P&P £1 & VAT. Minimum Order £10. Access orders welcome.

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

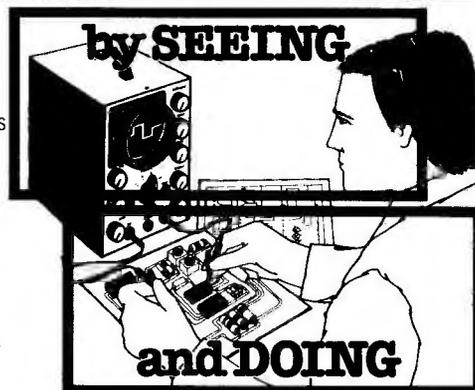

## New Job? New Career? New Hobby? Get into Electronics Now!

**FREE!**  
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

ETI/5/821

NAME \_\_\_\_\_

COURSE IN ELECTRONICS as described above

RADIO AMATEUR LICENCE

MICROPROCESSORS

OTHER SUBJECTS \_\_\_\_\_

LOGIC COURSE \_\_\_\_\_

ADDRESS \_\_\_\_\_

BLOCK CAPS PLEASE

POST NOW TO

**British National Radio & Electronics School Reading, Berks. RG1 7BR**

# SOUND EFFECTS 4

Our fourth and final sound effect using the SN76488 should come in handy for any amateur drama group contemplating Agatha Christie — it's a gunshot. Design by Phil Wait.

This unit is quite straightforward. The Noise Generator blocks in the IC are employed to produce a suitable sound, which is heard for about a fifth of a second, dying away rapidly. The effect is triggered (pardon the pun) by the push-button. Only half a dozen components are required apart from the IC! With care, patience and a little juggling, the unit could be fitted inside a toy plastic gun by simply soldering the components between the IC pins. You would have to obtain a tiny loudspeaker, headphone unit or rocking armature insert for a speaker — whatever will fit in the gun assembly.

## Supply Bypassing

A short word on this subject may prevent difficulties in some cases. In general, we found that the power supply rail doesn't really need bypassing. However, provision has been made on the PCB for the inclusion of a bypass capacitor. This is located near the battery positive lead input on the board, which connects to pin 12 of the IC. Have a look at the component overlay for the Bomb Drop and Explosion unit, in last month's ETI. Locate C6, a 10nF polyester. This is the

supply bypass. A capacitor having any value between 10nF and 10uF, and which will fit on the board, will do the job.

That's it! Have fun with your Sound Effects. We're sure that, with a

little ingenuity and experimentation, you'll be able to devise a few effects of your own. (If you do, we'd like to hear from you and will pay for any items published.)

## HOW IT WORKS

A gunshot is simulated by producing a burst of noise that decays very quickly. This unit employs the Noise Generator, Noise Filter, One Shot, Mixer and Envelope Generator to generate the required sound.

The Mixer select pin (25) and the Envelope select pin (28) are both held high (+5 V), selecting the One Shot output function from the Mixer. When the push-button, PB1, is pressed it puts a high on pin 9 and the Systems Inhibit block triggers the One Shot and activates the Envelope Generator. For the duration of the One Shot period, the modified noise from the Noise Generator/Filter is passed through the Mixer and Envelope Generator and then to the audio output stages.

The One Shot period, determined by R1 and C1, is quite short (about 1/5 second) and the decay period of the Envelope Generator a little longer. Audio output is coupled to the speaker via the 100uF DC blocking capacitor, C4.

## PARTS LIST

Resistors (all 1/4W, 5%)

R1,3 470k  
R2 6k8

Capacitors

C1,3 470n 35 V tantalum or PCB electrolytic  
C2 470p ceramic  
C4 100u 16 V PCB electrolytic

Semiconductors

IC1 SN76488

Miscellaneous

PB1 SPST push-button switch  
PCB (see Buylines); 50 mm diameter 8 ohm speaker; PP3 battery and clip.

## BUYLINES

As with the other projects in this series, no problems at all with supply — PCBs from us (page 45), IC1 from Technomatic, and everything else from anyone at all!

Fig. 1 Circuit diagram for the gunshot effect.

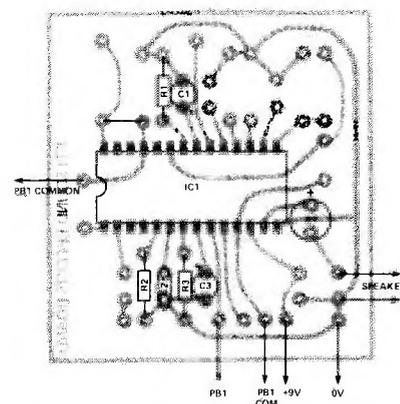
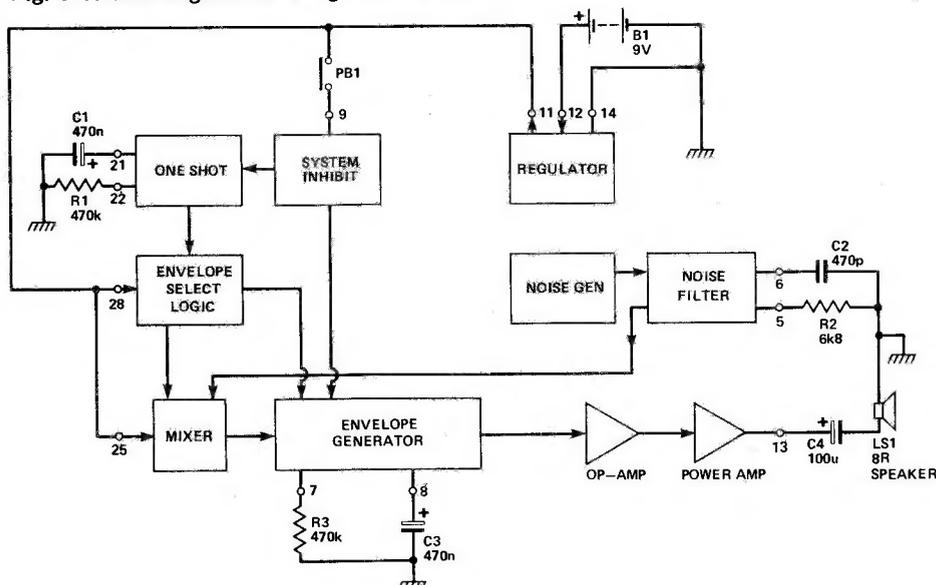


Fig. 2 Component overlay for the gunshot, using the same PCB as all the other sound effect projects. Don't forget to insert the link on the board.

# WHAT'S ON NEXT?

## Audio Frequency Signal Generator

It's so simple it's almost laughable — but it provides an output of up to 1 volt RMS at any frequency from 20 Hz to 30 kHz, in three decade ranges. A most useful addition to any workshop.

## Digital Thermometer

Based on display circuitry similar to that used in our Digital Capacitance Meter, last month this attractively finished project will find many uses around the house — or it would make perfect gift.

## HE Reverb

Part of our **Project Music** series, this flexible device is mainly intended to add depth to flat recordings or to put a bit of life in vocal performances — but the creative musician will find many other uses for it, as well.

## The Electronic Revolution

The first part of a new series, tracing the history and development of electricity and electronics, from the beginning. Once upon a time in a country far away . . . .

## Sines of the Times

We all know what sine waves are, don't we? If you think you know it all, this feature will give you a surprise — or two.

## Scaling the Hi-Fi Heights

The final part of our popular series for first-time hi-fi buyers looks at adding a tuner or cassette deck to your brand new sound system.

**May issue on sale 9th April.**

### PLACE YOUR ORDER NOW!

Simply fill out and cut the coupon, then hand it to your newsagent. Your personal copy of the May issue of HE will be reserved for you.

Please reserve . . . . . copies of the May issue of  
**Hobby Electronics**  
for  
Name . . . . .  
Address . . . . .  
. . . . .  
. . . . .

Although these articles are being prepared for the next issue, circumstances may alter the final content.

## USED EQUIPMENT

Ex-P.O. Multimeters in leather case. AC/DC Volts, DC current, ohms. Absolute Bargain £5

### 500V MEGGER

Transistorised Insulation Tester and four decade resistance bridge with four ranges. Invaluable piece of test gear. In case with carrying handle. Uses one PP9 batt. £15.00 + £2 P&P

Recent Style P.O. Telephones £4.75 + £1.80 P&P  
2 for £9 + £2.50. 5 for £20 + £5

5 Digit Counters 48V coil. Non resettable 75p

**AUTOMATIC DIAL UNIT.** (mains powered). These units were made to connect into a telephone and dial a number when a punch-card is inserted. Card & instructions supplied. Cards readily available. Many uses. Only £8 + £1 p&p

**UNISELECTORS.** 50v, 4 Bank + Homing Bank, 25 way £3.50

**D CONNECTOR SOCKETS** with cover. 50 way £2

**60V 8A TRANSFORMER.** Ideal for big power supply unit or amplifier £12 inc. p&p. BEAT THAT!

FREE on request - Leaflet 'D.I.Y. Telephone Systems and Automatic Exchange Design'.

## LOW-COST, RUGGED TEMPERATURE CONTROL




**HIGH QUALITY TEMP. GAUGE 0° - 120°C**  
Remote sensor on 38" capillary, panel mounting dial 55mm. dia.

**ONLY £1.85**

**16A 240V RANCO THERMOSTAT**  
Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. £2.30, including control knob

**RANCO THERMAL CUT-OUT 100°C**  
15A 240V. Sensing coil on 41in. capillary panel mounting with reset button £1.20

**BUY ONE EACH OF ABOVE FOR £4.85**

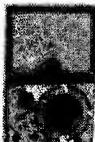

### AVOMETER

Similar to Model 71 which currently retails for over £45. These units are, as with all of our used equipment, Tested and Guaranteed to be in good working order. Price includes Leather case.

20K Ohms per Volt (D.C.) 1K Ohms per Volt (A.C.)  
D.C. Volts - 1, 2.5, 10, 25, 100, 250, 1,000  
A.C. Volts - 10, 25, 100, 250, 1,000  
D.C. mA - .05, 1, 10, 100, 1,000  
OHMS - x 1, x 100, x 10K  
**LIMITED STOCK AT £14.50 + £1 p&p**

### PROFESSIONAL QUALITY P.A. MODULES

All to near broadcast spec. 7" x 2" rack mounting. Require 40 to 50 volt stabilised supply. Line Distribution Amp 30K in, 4 x 600 out. Gain control gives up to 20dB. Mixer - 10 stereo or 20 mono channels (no controls) gain up to 10dB. £12 each + £1.50 p&p.  
**MIC AMP** - Switchable gain + fine gain control + L.F. Cut. £14.50 + £1.50 p&p.



**L.E.M. SERVICES**  
230 RUGBY ROAD  
LEAMINGTON SPA CV32 6DY  
WARWICKSHIRE



**ADD 50p P&P**  
**ORDERS OVER**  
**£7.50 POST FREE**  
unless stated otherwise

TEL: 0926 30622 FOR QUANTITY DISCOUNTS ETC.  
ALL ITEMS - MONEY BACK IF NOT DELIGHTED.

## NEED ENCLOSING?

Now, GSC are really in the hardware business, with a series of plastic cases ideally suited to applications ranging from hand-held probes to hi-fi equipment. GSC cases are moulded in robust plastic and come with all the necessary screws, covers and, where appropriate, battery compartments, connectors and transparent panels for displays. And GSC can provide customer-specified variations for large-quantity orders. Fill in the coupon for more details.

GSC (UK) Ltd., Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.  
Telephone: (0799) 21682. Telex: 817477.

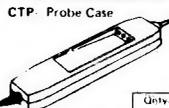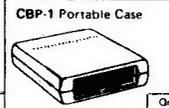 CTP - Probe Case (£3.50 Nett) <b>£4.88</b>	 DMC-2 Design-Mate Case (£4.00 Nett) <b>£5.46</b>	 CBP-1 Portable Case (£6.30 Nett) <b>£8.39</b>
 CTH-1 Handheld Case (£3.90 Nett) <b>£5.35</b>	 DMC-1 Design-Mate Case (£4.50 Nett) <b>£6.03</b>	 CTB-1 Bench Topper Case (£7.75 Nett) <b>£10.06</b>

Bold prices include P & P and 15% VAT. Please deduct £1 postage from each additional order.  
I enclose cheque/PO for £ \_\_\_\_\_  
or debit my Barclaycard, Access, American Express card  
No \_\_\_\_\_ Exp. date \_\_\_\_\_  
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

**GLOBAL SPECIALTIES CORPORATION**  
**GSC** FREE catalogue tick box   
Global Specialties Corporation (UK) Limited, Dept 9MM  
Unit 1, Shire Hill Estate, Saffron Walden, Essex CB11 3AQ

**TOMORROW'S TOOLS TODAY**

## ELECTRONIC IGNITION

Makes a good car better



As a KIT or READY BUILT

**TOTAL ENERGY DISCHARGE** electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** - higher output voltage under all conditions.

**IMPROVED ECONOMY** - no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** - prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** - immune to contact bounce and similar effects which can cause loss of power and roughness.

### PLUS

**SUPER POWER SPARK** - 3/4 times the energy of ordinary capacitive systems - 3/4 times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems - essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** - full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components - plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

### IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided - all you need is a small soldering iron and a few basic tools.

**AS REVIEWED IN**  
ELECTRONICS TODAY INTERNATIONAL June '81 Issue  
and EVERYDAY ELECTRONICS December '81 Issue

**FITS ALL NEGATIVE EARTH VEHICLES,**  
6 or 12 volt, with or without ballast

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS**  
Some older current impulse types (Smiths pre '74) require an adaptor -  
PRICE £2.95

**STANDARD CAR KIT £14.85**  
**Assembled and Tested £24.95**

**TWIN OUTPUT KIT £22.95**  
For MOTOR CYCLES and CARS with twin ignition systems  
**Assembled and Tested £34.70**

PLUS  
£1.00  
U.K.  
P. & P.  
Prices  
Include  
VAT.

### ELECTRONIZE DESIGN







Dept. D., Magnus Road, Wilnecote  
Tamworth, B77 5BY



Phone: (0827) 281000
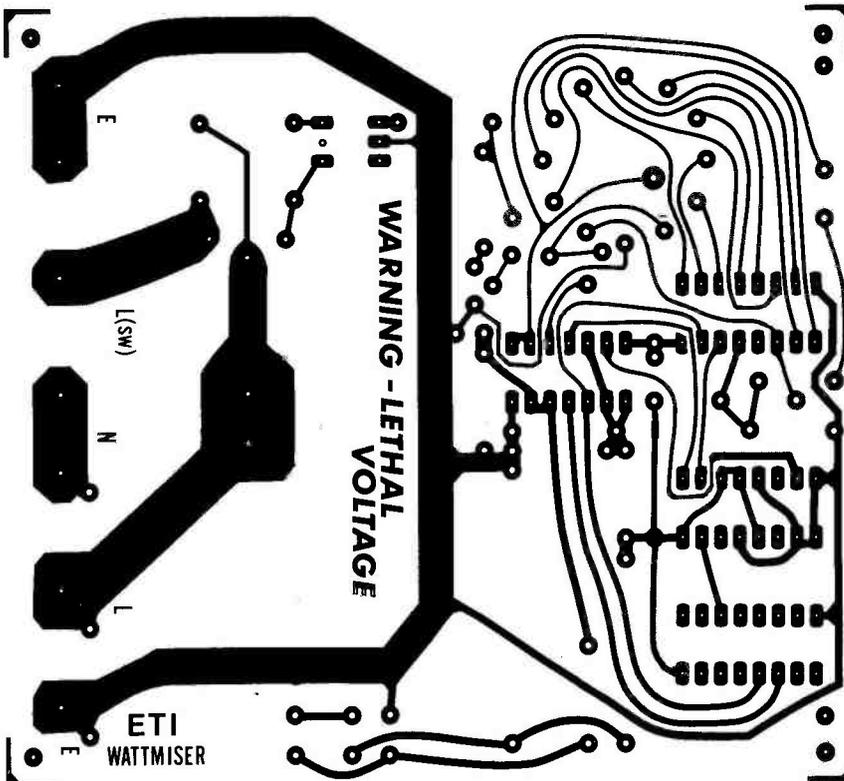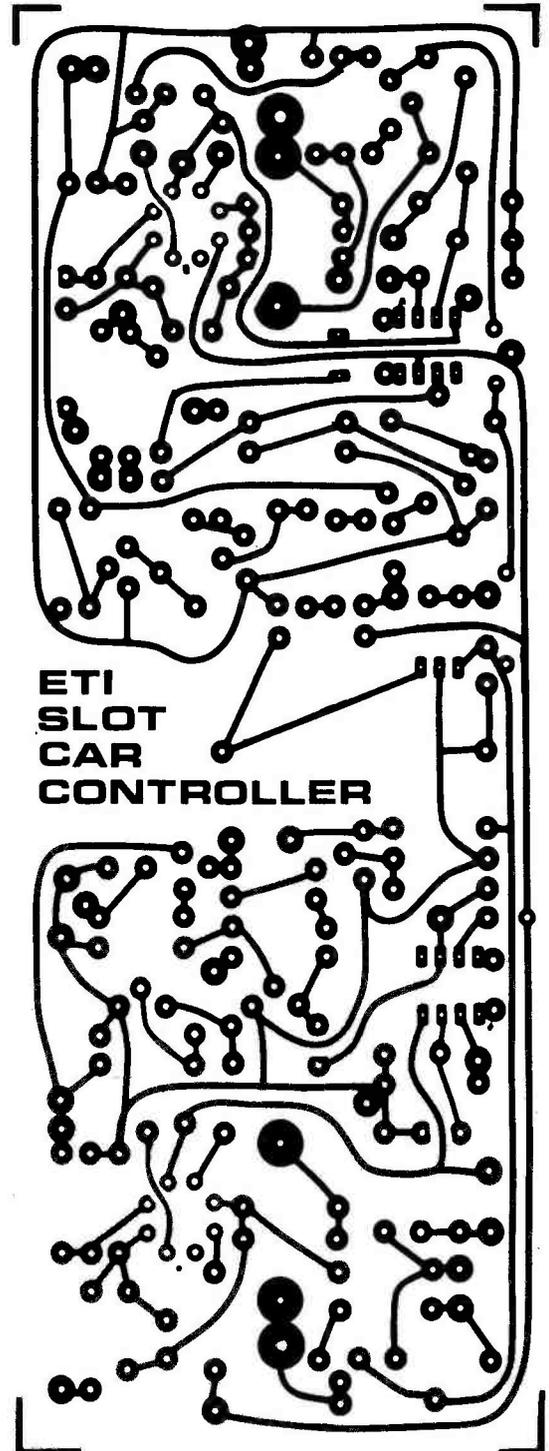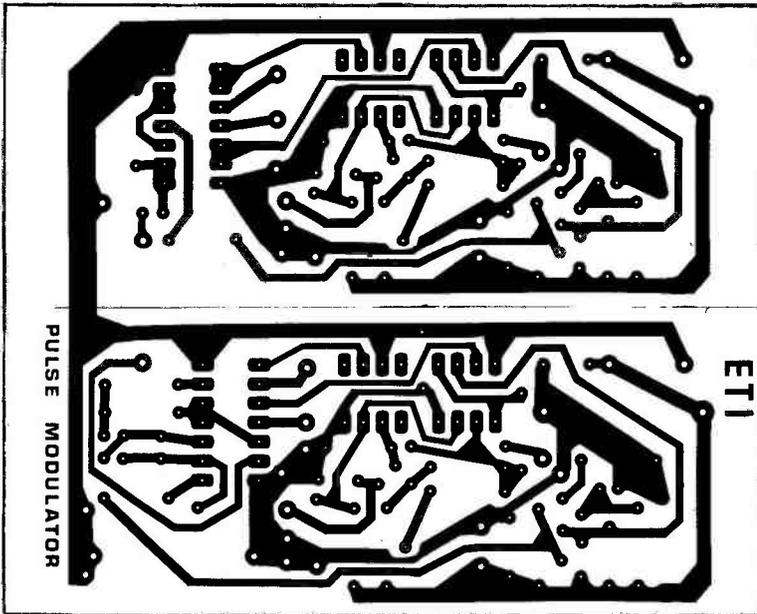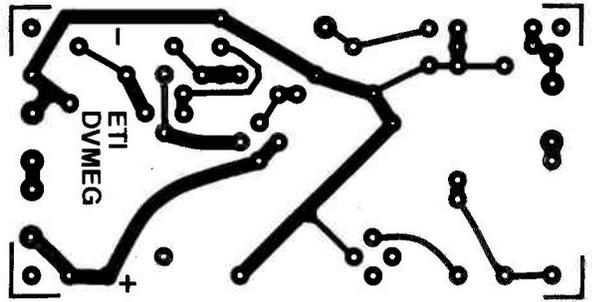
# PCB FOIL PATTERNS

The foil pattern for the Sound Effects board appeared in last month's ETI. Lack of space has prevented us reproducing it a second time. The foil patterns for the oscilloscope will be published next month.





# ELECTROMART

**MONTHLY IN  
ELECTRONICS TODAY —  
YOUR OWN 'WHERE TO  
BUY IT' GUIDE**

## BEDFORDSHIRE

### BROADWAY ELECTRONICS

1 The Broadway, Bedford,  
Tel: 0234 213639

Open: 6 days 9.5.30 - ½ day Thur.  
lunch 1.30-2.30.  
Specialists in electronic components and  
Acorn computers.

## DORSET

**D.J. ELECTRONICS**  
64 Ensbury Park Road,  
Bournemouth.

Tel: (0202) 515073.

Open: Mon-Sat 9am-6pm.

## HAMPSHIRE

### GAINS ELECTRONICS

3, West Street, Fareham.  
Tel: (0329) 234891

Open: 6 days 9am-5.30pm.  
RS component stockist. Wide range of components for  
the enthusiast.

## HERTFORDSHIRE

**GODDARDS COMPONENTS**  
110 London Road, St. Albans.  
Tel: St. Albans 64162

Open: Mon-Sat 9.30am-5.30pm  
(½ day Thur)

**FOR SERVICE AND  
CONVENIENCE — USE  
YOUR LOCAL DEALER!**

**LOOKING FOR  
COMPONENTS! HARDWARE!  
CASES! TRY YOUR LOCAL  
LISTED STOCKIST**

## S. IRELAND

### peats the world of electronics

25 Parnell St, Dublin 1.  
Tel: Dublin 740662

Open: 6 days 9am-5.30pm  
Components. Computers. Video games.

## LANCASHIRE

### ETESON ELECTRONICS

15B Lower Green,  
Poulton-le-Fylde, Blackpool  
Tel: (0253) 885107

Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.  
Electronic Component Specialists.

## LONDON

### SAMSONS ELECTRONICS LTD

9/10 Chapel St. 21/23 Bell St. NW1.  
Tel: 01-262-5125, 01-723-7851.

Open: 10am-6pm. (Sat 11am-5pm).  
Vast selection of components at ridiculous  
prices.

## W. MIDLANDS

### PATH ELECTRONIC SERVICES

369 Alum Rock Road, B'ham.  
Tel: 021 327 2339.

Open: 10am-6pm weekdays.  
Sat 9.30am-5pm. Contact Peter A.  
Thomas. Wholesale and retail supplies.

## NOTTINGHAMSHIRE

### DAMON electronics

99 Carrington St. Nottingham.  
Tel: 53880 (mail order available)

Open: 6 days 9.30am-5.30pm.  
Specialists in T.V. F.M. aeriads.

**FOR YOUR BUSINESS TO  
BE INCLUDED, CALL  
ELECTROMART ON  
01-437-1002.**

## TYNE AND WEAR

### AITKEN BROS & CO

35 High Bridge  
Newcastle Upon Tyne.  
Tel: 326729

Open: 9am-5.30pm (Sat 5pm) closed Wed.  
Retail and Wholesale supplied.

## S. WALES

### CARDIGAN ELECTRONICS

Chancery Lane, Cardigan,  
Tel: Cardigan (0239) 614483

Open: Mon-Sat 10am-5pm. Closed Wed.  
Electronic components &  
Acorn computer stockist.

## WILTSHIRE

### camlab electronics

27 Faringdon Rd. Swindon  
Tel: (0793) 34917

Open: 6 days 9am-5.30pm  
Specialists in loud speakers. Wide selection: 1¼"-18"

## YORKSHIRE

### ACE MAILTRONIX LTD.

3A Commercial Street,  
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)  
Retail and wholesale.

**PLEASE MENTION  
ELECTRONICS TODAY  
WHEN USING THESE  
SHOPS!**

Please include my business details in the next available issue of Electronics Today International:

Business Name: .....

Address: .....

Tel. No.: .....

Open Hrs: .....

Contact (Office Use Only): .....

Post To: Electromart Computing Today, 145 Charing Cross Rd., London WC2H 0EE.



**CLASSIFIED**  
 THE PATH TO  
 SUCCESSFUL SALES!  
 01-437 1002

## ADVERTISEMENT RATES

Semi-Display (min 2 cms)

1-3 insertions **£10.00** per cm  
 4-11 insertions **£ 9.00** per cm  
 12+ insertions **£ 8.00** per cm  
 Lineage 35p per word (min 15 words)  
 Box Nos. **£2.50**

**Closing date 1st Friday of the month preceding publication date.**

All advertisements in this section must be prepaid. Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

Send your requirements to:

**E.T.I. CLASSIFIED ADVERTISING,**  
 145, CHARING CROSS RD, LONDON WC2H0EE.

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

### L.E.D. ALARM CLOCK BARGAINS

Fig. 1

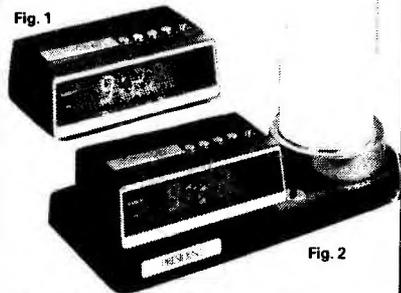


Fig. 2

Returned to our Service Department within guarantee period.

- (1) Offered at **£2.95** each or **£7.95** for three plus £1 p&p (Available new for **£18.00** each).
- (2) Offered at **£5.95** each or **£14.95** for three plus £1.00 for p&p (Available new for **£32.00** each).

These will be sold as received from our customers with the existing fault(s) and without guarantee. U.K. only. Further discounts available on bulk purchases.

Send cheques or Postal Orders to:

**PRESCOTT CLOCK & WATCH CO. LTD.**

Prescott House, Humber Road, London NW2 6ER  
 Telephone: 01-452 9871

**ZX-D.I.Y.!** 128 user definable graphics characters from under £1! Send **£3.00** for full circuit/construction details ('80 or '81). J. Buchanan, (36D.C.), R.M.C.S., Shrivenham, Swindon, Wilts.

**DIPLOMA IN ELECTRONICS** Full time courses in Electronic Engineering. Also courses leading to **CITY AND GUILDS Examinations.** Tel: **LONDON SCHOOL OF ELECTRONICS: 01-263 5938.**

**STOCK CLEARANCE** Mixed resistor Packs: 1/4W/ 1/2W, Pre-formed, unused. 1 lb Pack (2500 plus) **£2.50**; 2 lb Pack **£4.60**; Exceeding 2 lbs **£2.00** per lb. All inclusive VAT, P&P. **LINWAY ELECTRONICS, 843 Uxbridge Road, Hayes End, Middx. UB4 8HZ. Tel: 01-573 3677.**

**WANTED: ELECTRONIC COMPONENTS** and Test Equipment. Factories cleared. Good prices given. Q Services, 29 Lawford Crescent, Yateley, Camberley, Surrey. 0252 871048.

**PROM PROGRAMMING** All prices include Prom. Up to 8K **£5**, 16K **£8**, copies **£3.50**, wash 80p. Send typed or handwritten Hex code. C.W.O. Oakstech Engineering Ltd, 9 Millfields, Stanstead, Essex.

**STEREO CASSETTE BOARD** Ready built. Untested but assumed O.K. with data, **£3.00.** Details: (0582) 54315 between 5.30pm-7.30pm.

**PROXIMITY SENSORS** infra-red range 6 inch single 5-7V supply ideal for mobile robots **£21.95** leaflet. Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent, Staffs.

**TRANSCENDENT 2000** Ex condition Plus Data **£120** ono. 061-250 7478 Manchester.

**CLOSE ENCOUNTERS GROUP** Personal introductions and social events. Meet interesting, attractive people. Local, 051-931 2844 (24 hours).

### TIME WRONG?

**MSF CLOCK** is ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and leap year, also parallel BCD output for COMPUTER or alarm and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET yours NOW.

### CAMBRIDGE KITS

45 (TE) OLD SCHOOL LANE, MILTON, CAMBRIDGE

**GRUNDIG CASED PSU 0/25V 2A.** Excellent working condition. Voltage current metered overload protection. **£20 + £5.** S.H.E. 5, St. Joseph's Park, Ballycruttell, Downpatrick BT30 7EN.

**CENTURION BURGLAR ALARM EQUIPMENT** Send SAE for free list or a cheque/PO for **£5.95** for our special offer of a full sized decoy bell cover. To Centurion Dept ETI265, Wakefield Rd., Huddersfield W. Yorkshire. **Access & Barclaycard** Telephone orders on 0484-35527.

### CABINET FITTINGS

Cabinet & Flightcase Fittings, fretcloths, coverings, handles, castors etc. Jacks & sockets. Cannon. Bulgins reverb trays. Emular compression drivers. AKG mics. Celestion speakers. ASS glassfibre horns. Send 30p postal order for illustrated catalogues to

**ADAM HALL (ET SUPPLIES)**  
 Unit B, Charlton Court, Grainger Road,  
 Southend-on-Sea, Essex SS2 5BZ

## RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture  
 Tested & fully guaranteed  
 Ex-stock delivery

**£6-95** inc VAT  
 Post & Pack 60p

Ideal for the experimenter  
**COMPLETE WITH DATA**

**HENRY'S**

404 EDGWARE ROAD, LONDON W2 1ED

### BROADCAST QUALITY FOR YOUR NEXT MIXER PROJECT

●Over 100 Audio Sub-Units ●Kit or Ready Built

Our new Mic & Mag Disc Pre-amps incorporate the super low noise Mullard/Signetic NE5534 IC

All items listed are identical to those used in our own professional consoles

**PARTRIDGE ELECTRONICS**  
 THE MIXER PEOPLE

56 Fleet Road, Benfleet,  
 Essex SS7 5JN, England

(LARGE SAE PLEASE)

**PROJECT 80 Synthesizer.** 11 modules. Suitable for expansion £170. 49 note keyboard and contacts. Unused £30. Tel: 021-373 5448.

**ONE PCB** by Cemeche gives you ALL the following facilities for your ZX81: fully buffered 8K memory; 8 output — 13 input lines; 8-bit D/A + A/D conversion; wire-wrap area for your own circuits.

Quality fully documented pre-drilled silk-screened fibreglass board. PCB, circuit diagram and example software — **£12.95** from

**CEMECHE LTD**  
136 Cromwell Road, London SW7  
ACCESS ACCEPTED

**NEW 1982 ACE COMPONENT CATALOGUE** Let your problems be our business. Be certain; have your components delivered quickly and efficiently and get that project working. **Send 30p now** for the easy to use 1982 Catalogue to: Ace Mailtronix, Dept E.T.I. 3A, Commercial Street, Batley, W. Yorks WF17 5HJ.

### 600 RESISTORS

High quality Carbon Film ¼W 5% E12 series  
60 values 10 per value

£5 INCLUDING VAT P&P

#### COVE COMPONENTS

58 Southwood Rd., Cove,  
Farnborough, Hants GU14 0JJ  
Mail Order only

**PARAPHYSICS JOURNAL** (Russian translations); Psychotronic Generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9". Paralab, Downton, Wilts.

**T. & J. ELECTRONICS COMPONENTS** — Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

**BURGLAR ALARM** trigger module. Can control complete system. Send £6.45 Home Security Services, 17 Southfield Close, Hurworth, Darlington, Co. Durham.

**CIRCUIT DESIGN**, Prototype construction, analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET, or Phone Bradford-on-Tone (082-346) 536.

### COMPUTER SALE

2114's (450ns low power)  
£0.60 each or £17.50 for 32

1771 disk controllers ..... £8.00 each  
8253 triple timers ..... £5.00 each  
8251's ..... £4.00 each

All above brand new — full spec.

2147's (70ns) 4K x 1  
low power static RAM's as used in many mainframes  
B quality (cosmetic rejects, but electronically sound:  
guaranteed) with data sheet  
£0.60 each or 32 for £12.50

PLEASE ADD 50p CARR/INS TO ALL ORDERS

Payment with orders to

**J. WRIGHT**  
27 Broomhill Drive,  
Glasgow G11 7AB

**SPARE PARTS** For all digital watches. Batteries, crystals, displays etc. Send SAE for full list. Profords, Copnersdrive, Holmergreen, Bucks HP15 6SG.

### MOS-FET AUDIO MODULES

Hitachi devices, Hitachi spec., glass boards, extruded heatsinks, tested, guaranteed 24 months.

120 watts/8 ohms; 120v/2A supply; £13.95  
240 watts/4 ohms; 120v/4A supply; £19.95  
400 watts/2 ohms; 120v/7A supply; £29.95

Power supplies/pre-amps available. Post/packing 80p. Stamp for details. Quantity discount.

Audio-Tech., 8 Parsons Close, Church Crookham, Aldershot, Hants GU13 0HL.  
Tel: 02514 22303.

### HAVEN HARDWARE ZX KITS:

Programmable Graphics £23.95 (UK101/S2 £39.95), Keyboard £18.95, Repeating Keymodule £2.95, Inverse-video, Colour, I/O Port P.O.A. S.A.E. for details/built prices. 4 Asby Road, Asby, Workington, Cumbria.

**VHF/FM TRANSMITTER KIT.** New IC design — Smaller than all imitations. Takes 5 minutes to build this miniature FM bug. Receive on domestic radio (VHF 88-108MHz). Instruction etc. all included. **ONLY £3.00 inc. p&p.** (Unlicensable). Cheques/POs/Cash to: M. Henry, Dept ETG., 30 Westholme Gardens, Ruislip. (Money Back Guarantee).

**GOULD ADVANCE OS245A** 10MHz Dual trace scope, 8 x 10 DIV Bright line, variable trigger 5MV/DIV display. £175 carriage paid. Brand new unused.

### GUITAR/P.A. MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50; 60 watt £44; 200 watt £68; 100 watt twin channel, sep. treble/bass per channel £65; 60 watt £52; 200 watt £78; 100 watt four channel, sep. treble/bass per channel, £75; 200 watt £98; slaves 100 watt £37; 200 watt £60; 250 watt £70; 500 watt £140; fuzz boxes, fuzz sound £12; bass fuzz £12.90; overdrive fuzz with treble and bass boosters £28; 100 watt combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £100; twin channel £115; bass combo £118; speakers 15in. 100 watt £36; 12in. 100 watt £24; 60 watt £18; microphone Shure Unidyn B £28.

Send cheque/P.O. to:  
**WILLIAMSON AMPLIFICATION**  
62 Thorncliffe Avenue, Dukinfield,  
Cheshire. Tel: 061-308 2064.

**SLIDER FADERS** — The pro-fader (pat. pend). A great looking fader with full 100mm. Action and smooth operation. Discard those noisy, sticky slider pots and give your mixer the professional touch for only **£3.75** each (+ 50p p&p). Send, stating requirements to: Western Products, 57 Maybole Road, Ayr.

**ELECTRONICS COMPONENT SHOP** IN MAIDSTONE, KENT! Thyronics control systems. 8 Sandling road, Maidstone, Kent. Maidstone 675354.

**BUILT TRANSMITTERS £2.90.** Receive on FM. Range 150 yds. Refund Guarantee. (Unlicensable). P. Faherty, 37 College Dr., Ruislip.

## IONISER KIT (Mains Operated)

This negative ion generator gives you the power to saturate your home or office with millions of refreshine ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions ..... **£12.50**  
A suitable case including front panel, neon switch, etc. .... **£10.50**

Price includes post & VAT. Barclaycard/Access welcome

**T. POWELL**

Advance Works, 44 Wallace Road, London N1 Tel: 01-226 1489  
Hours: Mon-Fri 9-5 pm Sat 9-4.30 pm

## D2114L2 Intersil, ceramic

200ns Static RAM

Limited	1	8	24
Stock	£1.20	£1.10	£1.05

P&P 40p for RAM under £20

Micro Computer CASSETTE in library box,  
GUARANTEED

<b>C-12</b>	10	25	100
	40p	35p	30p

P&P 40p per 5 cassettes

Please add VAT at 15% to TOTAL!

**INTELLIGENT COMPUTING ELECTRONICS**  
6 Dryden Court, London SE11 4NU  
Tel: 01-752 4432

**AMAZING ELECTRONICS PLANS.** Lasers, Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue 95p — From Plancentre, 16 Mill Grove, Bilbrook, Codsall, Wolverhampton.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**COPPER CLAD BOARD** double sided fibre glass. **10 sheets** 12" x 8" £6.00. **5 sheets** 12" x 8" £4.00. Including P&P. Complete PCB service. Davron, 1 Bankside, off New Street, Chelmsford.

**SECURITY ALARMS** Kits from £37. Full range of accessories. MFP Ltd, Harrison Road, Erdington, Birmingham B24 9AB. 021-373 0450.

**AERIAL AMPLIFIERS** Improve weak television reception. Price £6.70, S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

### UNREPEATABLE OFFER

Digital thermometer .5" LED Display, calibrated in degrees C range -50° to +99.9°C with Platinum Resistance Probe. 12v operation. B.C.D. Outputs available housed in A.B.S. DIN styled case, W96 x H48 x D150mm

Give away at **£49.95** inc. VAT. (valued at £135.50)

Mains Adaptor for above unit **£5.75** inc. VAT

P&P **£2.50**

Circuit Date supplied

Cheques or P.O. with Order to:—

**MICRO ELECTRONIC SYSTEMS**  
Martin Buildings, Stonehouse St.,  
Middlesbrough, Cleveland  
Telephone No. 0642 829238



# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, T.V. Electronics Technicians  
Radio Amateurs  
Electrical Installation Work

## Diploma Courses

Colour T.V. Servicing  
CCTV Engineering  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

To ICS, Dept. 265U, Intertext House,  
London SW8 4UU

Name

Address

Age

**ICS**

To ICS, Dept. 265U, Intertext House,  
London SW8 4UU  
or telephone 01-622 9911 (all hours)

## ADVERTISEMENT INDEX

A.D. Electronics	64, 85
Ambit International	44
Amtron	84
Audio Electronics	75
Audio Video	78
Bicc Vero	93
Bi-Pak	62
BK Electronics	12, 59
Black Star	78
Braithwaite Kits	72
B.N.R.S.	88
C.C.S.	70
Cambridge Learning	39
Chiltmead	78
Clef Products	71
Cricklewood Electronics	32, 33
Crimson Electric	58
Crofton Electronics	77
Decon Laboratories	31
Delta Tech	72
Derwent District Council	46
Display Electronics	51
EDA Sparkrite	21
Electronize Design	91
Electro Supplies	66
Electrovalue	83
Greenbank	52
Greenweld	84
G.S.C.	43, 71, 91
Happy Memories	66
Henry's Radio	75
ILP	58
LB Electronics	58
L & B Electronics	85
LEM Services	91
Magenta Electronics	77
Maplin	100
Marco Trading	77
Mawson Associates	83
Memotech	25
Microtimes	38
Midwich Electric	59
Namal Associates	88
Pantechnic	39
Parndon Electronics	2 & 99
Rapid Electronics	8
Relay-A-Quip	38
Riscomp	13
R.T.V.C.	37
Silica Shop	16
Sinclair Research	6 & 7
Solid State Security	85
Swanley Electronics	59
Technomatic	10
Teleradio	85
Tempus	26
TK Electronics	14
Videotone	70, 75
Watford Electronics	4 & 5
Wilmslow Audio	84

# PRECISION - by POWERTRAN

THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS

For more than eleven years Powertran have been designing and manufacturing the finest quality electronic kits. All of our now considerable range have featured in the electronics press and literally thousands have been bought and built by contractors in the UK and World-wide.

Our philosophy is always the same — we offer ingenuity and originality in the construction phase by using only top class designers. We offer machines with power, versatility and performance — capability fully equal to their factory built rivals. We offer only the highest quality materials and components throughout to ensure years of useful and reliable service, we offer clear comprehensive and easy to follow construction manuals to place our kits within the scope of the careful first time builder as well as the dedicated enthusiast.

Our hallmark of success lies in the number of our clients who have built our whole range — many assembling several units for others to use often on the professional music scene.

We believe in taking every care throughout — months spent checking and testing the design and development. Vigorous checking of every component, constant pre-despatch quality control, careful packaging... even door to door delivery by Securicor!

We are naturally very proud of our Transcendent range of synthesizers designed by Tim Orr and regularly featured in ETI. They represent the best in constructional interest and in musical performance.

**TRANSCENDENT POLYSYNTH** — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.  
Complete kit **£275.00** plus VAT (single voice)  
Extra voice (up to three more) **42.00** plus VAT.

**EXPANDER** — A new matching 4 voice expander to team up with your polysynth for even a greater range and capability.  
Complete kit **£249.00** plus VAT.

**TRANSCENDENT DPX** — Offers a five octave keyboard with power to match. Two audio outputs (can be used simultaneously) to give harpsichord and piano/honkytonk or reed with strings/brass and both are fully polyphonic. Other features include switchable touch sensitivity and a chorus ensemble unit with strong/mild effect switching. An advanced design made simple with our clearly laid out instruction manual.  
Complete kit **£295.00** plus VAT.

**TRANSCENDENT 2000** — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it... play it! You will know you have made the right choice.  
Complete kit **£165.00** plus VAT.

**1024 COMPOSER** — Come right up to the minute with this new design. It will control your synthesiser with a sequence of up to 1024 notes — or an equal selection of shorter sequences. The Composer is mains powered with automatically charged battery to preserve your programme after switch-off.  
Complete kit **£85.00** plus VAT.

**DEMONSTRATION TAPE** — Demonstration tape now available of all three kits (30 minutes).  
**£2.00**



... Quite simply the best way to make music



## WORLD LEADERS IN ELECTRONIC KITS.

**PRICE STABILITY:** Order with confidence irrespective of any price changes we will honour all prices in this advertisement until the end of the month following the month of publication of this issue. (Errors and VAT rate changes excluded.)  
**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1 handling and documentation.  
**U.K. ORDERS:** Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed. Cheques, Access, Barclaycard accepted.  
**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.  
**SALES COUNTER:** If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m.-12 noon, 1-4.30p.m. Monday-Thursday.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM (0264) 64455.

Order by phone **VISA**  
**(0264) 64455**  
Simply telephone us with your order and quote your Access or Barclaycard number.  
40 page catalogue free — contains full details of all our kits.