

electronics today

ISSN 0142-7229

INTERNATIONAL JUNE 1982 75p

MOSFETS MAKE THE GRADE!

Brilliant new design for peak performance

Clean up the air -
build our ion
generator!

Novel design
techniques to secure
your home or car



Exclusive
review of brand-new
breadboarding system

POWER PACKED — by POWERTRAN

THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS — SEE INSIDE BACK COVER OF THIS ISSUE!

Powertran's black boxes are packed with punch. Not only are they superb kits to buy and build they really do the job! Imaginative and ingenious design goes hand in hand with top quality materials and outstanding performance capability. With their smart black styling the kits harmonise visually as well as musically. Your can build each unit independantly for its set task and then gradually increase your array until you have a complete bank of formidable controllable power.



Complete Kit — £49.90 + VAT

MPA 200 is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first-time builder.



Complete Kit — £49.50 + VAT

CHROMATHEQUE 5000 — a 5-channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single-board design.



Complete Kit — £175.00 + VAT

ETI VOCODER — 14 channels, each with independent level control, for maximum versatility and intelligibility; Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts.




Complete Kit — £64.90 + VAT

SP2 200 twice the power with two of the reliable, durable and economic amps from the MPA200; fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over!) the standard of high priced factory-built units.




DJ90 Stereo Mixer — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! (We have illustrated the DJ90 teamed in our own console with the Chromatheque and an SP2 200 and speakers.

Complete Kit — £97.50 + VAT

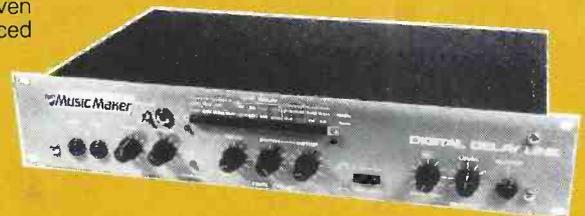

Digital Delay Line — our latest kit! With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo & vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,000! Complete kit (400 mS delay) **£130** + VAT. Parts for extra 400 mS delay £9.50p.

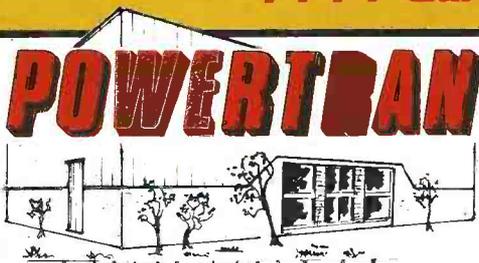..... Quite simply the best way to make music



WORLD LEADERS IN ELECTRONIC KITS

- **Money Back Guarantee** — If you are not completely satisfied with your Powertran Kit return it in original condition within 10 days for full refund.
- **Free Soldering Practice Kit** — To assist the beginner we will supply, on request with your first kit order, a free soldering practice kit with useful tips and illustrations.
- **Component Packs** — Most kits are available as separate packs (e.g. PCB component sets, hardware sets etc). Prices in our FREE catalogue.
- **Ordering** — Full ordering details, delivery service, and sales counter opening — outside back of this issue.


PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

ORDER BY PHONE
(0264) 64455
Simply telephone us with your order and your Access or Barclaycard number & CATALOGUE FREE. CONTAIN FULL DETAILS OF ALL OUR KITS

electronics today

INTERNATIONAL JUNE 1982 VOL 11 NO 6

electronics today

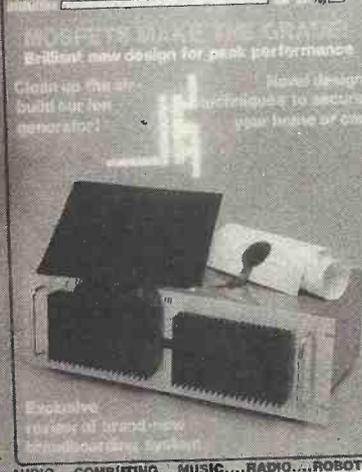

AUDIO... COMPUTING... MUSIC... RADIO... ROBOTICS...

Ron Harris B.Sc : Editor
Peter Green : Assistant Editor
Tina Boylan : Editorial Assistant
Kathryn McFarland : Editorial Secretary
Rory Holmes : Project Editors
Phil Walker :
Alan Griffiths : Ad Manager
T.J. Connell : Managing Director

PUBLISHED BY:
 Argus Specialist Publications Ltd.,
 145 Charing Cross Road, London WC2H 0EE.
DESIGN AND ORIGINATION BY:
 MM Design & Print Ltd,
 145 Charing Cross Road,
 London WC2H 0EE.
DISTRIBUTED BY:
 Argus Press Sales & Distribution Ltd.,
 12-18 Paul Street, London EC2A 4JS
 (British Isles)
PRINTED BY:
 QB Limited, Colchester.
COVERS PRINTED BY:
 Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS
 AUSTRALIA — Roger Harrison
 CANADA — Halvor Moorshead
 GERMANY — Udo Wittig
 HOLLAND — Anton Kriegsman



Member of the
 Audit Bureau
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. ©1982 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.


□ Subscription Rates. UK £11.95 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.


FEATURES

- DIGEST** 10
 Be informed, be entertained, be amused, be amazed — it's all in the news this month.
- TECH TIPS** 26
 When they're not writing letters, our readers are designing circuits. Here's a few more that have been submitted.
- DESIGNER'S NOTEBOOK** 36
 Some merry MOSFET marvels, with a discussion of the advantages of VMOS and a few circuits for you to play with.
- READ/WRITE** 56
 More missives from our readers about sound, speakers, System A, life, the Universe and everything..
- ELECTROMUSIC TECHNIQUES PART 3** 59
 Tim Orr winds up this designer's delight with a few well-chosen building blocks.
- BREADBOARDING SYSTEMS** 74
 Put away the plywood, the solder and the 6" nails, there are better ways of prototyping circuits nowadays.

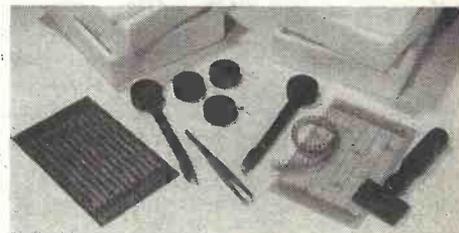

PROJECTS

- NEGATIVE ION GENERATOR** 19
 Spray some negative ions into the atmosphere and feel positive. You can build this project the way we did or experiment with the emitter design yourself.
- OSCILLOSCOPE PART 2** 30
 This month we feature the constructional details for this amazing little gadget. A small piece of test gear with a big performance.
- STYLUSTIMER** 41
 Don't destroy your precious discs by neglecting your needle; build this gadget and you'll be certain when to change your stylus.
- 150W MOSFET AMPLIFIER** 48
 Here's the amplifier you've always promised yourself. Modern technology and brilliant design give a truly state-of-the-art performance.
- ROBOT MODULES: DIGITAL PWM** 66
 Two for the price of one this month; first, an interface board for computer control of DC motors ...
- OPTICAL SENSOR** 69
 ... and second, a cunning infra-red device that'll detect walls and a whole bunch of other stuff.
- LOGIC LOCK** 79
 Complicated enough to thwart Dr. Who's Adric, it'll certainly baffle your friendly neighbourhood burglar; yet it's very simple to build.
- FOIL PATTERNS** 86

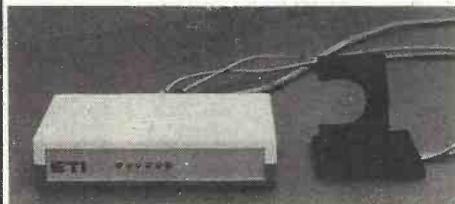

INFORMATION

- NEXT MONTH'S ETI** 17
BINDERS 23
ZX COMPUTING 45
BOOK SERVICE 64
PCB SERVICE 82
SUBSCRIPTIONS 84

WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME
Tel. Watford (0923) 40588. Telex: 8956095

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 50p TO ALL ORDERS. OVERSEAS ORDERS POSTAGE AT COST. AIR SURFACE. ACCESS ORDERS WELCOME.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including p&p.
We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street.
Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car Parking space available.

ELECTROLYTIC CAPACITORS: (Values in uF) 500V: 10uF 52p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 8p; 10 10p; 15 15p; 22 22p; 33 33p; 47 47p; 68 68p; 100 100p; 220 220p; 330 330p; 470 470p; 680 680p; 1000 1000p; 2200 2200p; 3300 3300p; 4700 4700p; 6800 6800p; 10000 10000p; 22000 22000p; 33000 33000p; 47000 47000p; 68000 68000p; 100000 100000p; 220000 220000p; 330000 330000p; 470000 470000p; 680000 680000p; 1000000 1000000p; 2200000 2200000p; 3300000 3300000p; 4700000 4700000p; 6800000 6800000p; 10000000 10000000p; 22000000 22000000p; 33000000 33000000p; 47000000 47000000p; 68000000 68000000p; 100000000 100000000p; 220000000 220000000p; 330000000 330000000p; 470000000 470000000p; 680000000 680000000p; 1000000000 1000000000p; 2200000000 2200000000p; 3300000000 3300000000p; 4700000000 4700000000p; 6800000000 6800000000p; 10000000000 10000000000p; 22000000000 22000000000p; 33000000000 33000000000p; 47000000000 47000000000p; 68000000000 68000000000p; 100000000000 100000000000p; 220000000000 220000000000p; 330000000000 330000000000p; 470000000000 470000000000p; 680000000000 680000000000p; 1000000000000 1000000000000p; 2200000000000 2200000000000p; 3300000000000 3300000000000p; 4700000000000 4700000000000p; 6800000000000 6800000000000p; 10000000000000 10000000000000p; 22000000000000 22000000000000p; 33000000000000 33000000000000p; 47000000000000 47000000000000p; 68000000000000 68000000000000p; 100000000000000 100000000000000p; 220000000000000 220000000000000p; 330000000000000 330000000000000p; 470000000000000 470000000000000p; 680000000000000 680000000000000p; 1000000000000000 1000000000000000p; 2200000000000000 2200000000000000p; 3300000000000000 3300000000000000p; 4700000000000000 4700000000000000p; 6800000000000000 6800000000000000p; 10000000000000000 10000000000000000p; 22000000000000000 22000000000000000p; 33000000000000000 33000000000000000p; 47000000000000000 47000000000000000p; 68000000000000000 68000000000000000p; 100000000000000000 100000000000000000p; 220000000000000000 220000000000000000p; 330000000000000000 330000000000000000p; 470000000000000000 470000000000000000p; 680000000000000000 680000000000000000p; 1000000000000000000 1000000000000000000p; 2200000000000000000 2200000000000000000p; 3300000000000000000 3300000000000000000p; 4700000000000000000 4700000000000000000p; 6800000000000000000 6800000000000000000p; 10000000000000000000 10000000000000000000p; 22000000000000000000 22000000000000000000p; 33000000000000000000 33000000000000000000p; 47000000000000000000 47000000000000000000p; 68000000000000000000 68000000000000000000p; 100000000000000000000 100000000000000000000p; 220000000000000000000 220000000000000000000p; 330000000000000000000 330000000000000000000p; 470000000000000000000 470000000000000000000p; 680000000000000000000 680000000000000000000p; 1000000000000000000000 1000000000000000000000p; 2200000000000000000000 2200000000000000000000p; 3300000000000000000000 3300000000000000000000p; 4700000000000000000000 4700000000000000000000p; 6800000000000000000000 6800000000000000000000p; 10000000000000000000000 10000000000000000000000p; 22000000000000000000000 22000000000000000000000p; 33000000000000000000000 33000000000000000000000p; 47000000000000000000000 47000000000000000000000p; 68000000000000000000000 68000000000000000000000p; 100000000000000000000000 100000000000000000000000p; 220000000000000000000000 220000000000000000000000p; 330000000000000000000000 330000000000000000000000p; 470000000000000000000000 470000000000000000000000p; 680000000000000000000000 680000000000000000000000p; 1000000000000000000000000 1000000000000000000000000p; 2200000000000000000000000 2200000000000000000000000p; 3300000000000000000000000 3300000000000000000000000p; 4700000000000000000000000 4700000000000000000000000p; 6800000000000000000000000 6800000000000000000000000p; 10000000000000000000000000 10000000000000000000000000p; 22000000000000000000000000 22000000000000000000000000p; 33000000000000000000000000 33000000000000000000000000p; 47000000000000000000000000 47000000000000000000000000p; 68000000000000000000000000 68000000000000000000000000p; 100000000000000000000000000 100000000000000000000000000p; 220000000000000000000000000 220000000000000000000000000p; 330000000000000000000000000 330000000000000000000000000p; 470000000000000000000000000 470000000000000000000000000p; 680000000000000000000000000 680000000000000000000000000p; 1000000000000000000000000000 1000000000000000000000000000p; 2200000000000000000000000000 2200000000000000000000000000p; 3300000000000000000000000000 3300000000000000000000000000p; 4700000000000000000000000000 4700000000000000000000000000p; 6800000000000000000000000000 6800000000000000000000000000p; 10000000000000000000000000000 10000000000000000000000000000p; 22000000000000000000000000000 22000000000000000000000000000p; 33000000000000000000000000000 33000000000000000000000000000p; 47000000000000000000000000000 47000000000000000000000000000p; 68000000000000000000000000000 68000000000000000000000000000p; 100000000000000000000000000000 100000000000000000000000000000p; 220000000000000000000000000000 220000000000000000000000000000p; 330000000000000000000000000000 330000000000000000000000000000p; 470000000000000000000000000000 470000000000000000000000000000p; 680000000000000000000000000000 680000000000000000000000000000p; 1000000000000000000000000000000 1000000000000000000000000000000p; 2200000000000000000000000000000 2200000000000000000000000000000p; 3300000000000000000000000000000 3300000000000000000000000000000p; 4700000000000000000000000000000 4700000000000000000000000000000p; 6800000000000000000000000000000 6800000000000000000000000000000p; 10000000000000000000000000000000 10000000000000000000000000000000p; 22000000000000000000000000000000 22000000000000000000000000000000p; 33000000000000000000000000000000 33000000000000000000000000000000p; 47000000000000000000000000000000 47000000000000000000000000000000p; 68000000000000000000000000000000 68000000000000000000000000000000p; 100000000000000000000000000000000 100000000000000000000000000000000p; 220000000000000000000000000000000 220000000000000000000000000000000p; 330000000000000000000000000000000 330000000000000000000000000000000p; 470000000000000000000000000000000 470000000000000000000000000000000p; 680000000000000000000000000000000 680000000000000000000000000000000p; 1000000000000000000000000000000000 1000000000000000000000000000000000p; 2200000000000000000000000000000000 2200000000000000000000000000000000p; 3300000000000000000000000000000000 3300000000000000000000000000000000p; 4700000000000000000000000000000000 4700000000000000000000000000000000p; 6800000000000000000000000000000000 6800000000000000000000000000000000p; 10000000000000000000000000000000000 10000000000000000000000000000000000p; 22000000000000000000000000000000000 22000000000000000000000000000000000p; 33000000000000000000000000000000000 33000000000000000000000000000000000p; 47000000000000000000000000000000000 47000000000000000000000000000000000p; 68000000000000000000000000000000000 68000000000000000000000000000000000p; 100000000000000000000000000000000000 100000000000000000000000000000000000p; 220000000000000000000000000000000000 220000000000000000000000000000000000p; 330000000000000000000000000000000000 330000000000000000000000000000000000p; 470000000000000000000000000000000000 470000000000000000000000000000000000p; 680000000000000000000000000000000000 680000000000000000000000000000000000p; 1000000000000000000000000000000000000 1000000000000000000000000000000000000p; 2200000000000000000000000000000000000 2200000000000000000000000000000000000p; 3300000000000000000000000000000000000 3300000000000000000000000000000000000p; 4700000000000000000000000000000000000 4700000000000000000000000000000000000p; 6800000000000000000000000000000000000 6800000000000000000000000000000000000p; 10000000000000000000000000000000000000 10000000000000000000000000000000000000p; 22000000000000000000000000000000000000 22000000000000000000000000000000000000p; 33000000000000000000000000000000000000 33000000000000000000000000000000000000p; 47000000000000000000000000000000000000 47000000000000000000000000000000000000p; 68000000000000000000000000000000000000 68000000000000000000000000000000000000p; 100000000000000000000000000000000000000 100000000000000000000000000000000000000p; 220000000000000000000000000000000000000 220000000000000000000000000000000000000p; 330000000000000000000000000000000000000 330000000000000000000000000000000000000p; 470000000000000000000000000000000000000 470000000000000000000000000000000000000p; 680000000000000000000000000000000000000 680000000000000000000000000000000000000p; 1000000000000000000000000000000000000000 1000000000000000000000000000000000000000p; 2200000000000000000000000000000000000000 2200000000000000000000000000000000000000p; 3300000000000000000000000000000000000000 3300000000000000000000000000000000000000p; 4700000000000000000000000000000000000000 4700000000000000000000000000000000000000p; 6800000000000000000000000000000000000000 6800000000000000000000000000000000000000p; 100 100p; 22000000000000000000000000000000000000000 22000000000000000000000000000000000000000p; 33000000000000000000000000000000000000000 33000000000000000000000000000000000000000p; 47000000000000000000000000000000000000000 47000000000000000000000000000000000000000p; 68000000000000000000000000000000000000000 68000000000000000000000000000000000000000p; 1000 1000p; 2200 2200p; 3300 3300p; 4700 4700p; 6800 6800p; 100 100p; 22000 22000p; 33000 33000p; 47000 47000p; 68000 68000p; 1000 1000p; 2200 2200p; 3300 3300p; 4700 4700p; 6800 6800p; 100 100p; 22000 22000p; 33000 33000p; 47000 47000p; 68000 68000p; 1000 1000p; 2200 2200p; 3300 3300p; 4700 4700p; 6800 6800p; 100 100p; 22000 220

SWITCHES
TOGGLE: 2A, 250V, SPST 33p
DPDT 44p

DIL SWITCHES
(SPST) 4 way 70p; 6 way 85p;
8 way 90p; 10 way 145p.
(SPDT) 4 way 190p.

ROTARY SWITCHES:
(Adjustable Stop Type):
1 pole/2 to 12 way; 2p/2 to 6 way;
3 pole/2 to 4 way; 4p/2 to 3 way 45p

ROTARY: Mains DP 250V 4 Amp on/off 56p

ROTARY (Mak-a-switch)
Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch).
90p

WAFERS: (make before break) to fit the above switch mechanism.
1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6p/2 way 56p
Mains DP 4A Switch to fit Spacers 4p. Screen 6p

ROCKER: 5A/250V SPST 28p
ROCKER: 10A/250V SPDT 38p
ROCKER: 10A/250V DPST c/o/off 45p
ROCKER: 10A/250V DPST with neon 85p

SLIDE 250V:
DPDT 1A 14p
DPDT 1A c/o/off 15p
DPDT 2A 13p

PUSHBUTTON BA
with 10mm Button
SPDT latching 99p
SPDT moment 99p
DPDT moment 146p

Mini Non Locking Push to Make 25p
Push to Break 19p

ETI PROJECTS
We stock most of the parts

JUMPER LEADS (Ribbon Cable Assembly)
Length 14 pin 18 pin 24 pin 40 pin
24 inches Single ended DIP Jumper 145p 165p 240p 380p
Double ended DIP Jumper 185p 205p 300p 465p
6 inches 185p 205p 300p 465p
12 inches 198p 215p 315p 490p
24 inches 210p 235p 345p 540p
36 inches 230p 250p 375p 595p

AMPHENOL PLUGS IEEE (24 way) 67p
Centronic parallel (36 way) 66p

VEROBOARD 0.1in
7/32" clad plain 175
DIP Board 388
Vero Strip 144
3/4" x 3/4" 83p
3/4" x 5" 83p
3/4" x 5" 95p 79p
3/4" x 17" 425p 211p
4 3/4" x 17" 425p 211p
Pkt. of 100 pins 51p
Spot face cutter 118p
Pin Insertion tool 162p

PROTO DECS
Veroblock 375p
S Dec 350p
Eurobreadboard 520p
Bimboard 1 575p
Superstrip SS2 1360p

VERO WIRING
PEN + Spool 310p
Spare Spool 75p
Combs 6p

DALO ETCH RESIST PEN
+ Spare tip 90p

FERRIC CHLORIDE
1 lb bag Anhydrous 195p
+ 50p P&P

ULTRASONIC TRANSDUCER
40KHz 395p pr

COPPER CLAD BOARDS
Fibre Single Double S.R.B.P.
glass sided sided 9.5" x 8.5"
6" x 6" 90p 110p 95p
6" x 12" 150p 195p

DIL SOCKETS (TEXAS) Low Wire Prof. Wrap
8pin 8p 25p
14pin 10p 35p
16pin 10p 45p
18pin 10p 52p
20pin 22p 60p
22pin 25p 70p
24pin 25p 70p
28pin 28p 80p
40pin 30p 95p

EDGE CONNECTORS (Double type)
2 x 15 way + 140p
2 x 18 way 180p 145p
2 x 22 way 195p 200p
2 x 23 way 210p 200p
2 x 25 way 225p 220p
2 x 30 way 245p
2 x 36 way 295p
2 x 40 way 315p
2 x 43 way 355p
2 x 75 way 690p

D CONNECTORS (Cannon type)
Pins Plugs Sockets Covers
9 way 50p 110p 100p
15 way 130p 160p 95p
25 way 180p 210p 105p
37 way 250p 350p 135p

Solderless Pins
100 pins
500 pins
325p

PLUGS & SOCKETS
IDC HEADERS (Speed-block type)
IDC Header PCB-Plugs
with Free Strt. Angl
Latch Sckt. pins
2 x 5 way 90p 65p
2 x 8 way 130p 110p
2 x 10 way 145p 125p
2 x 13 way 175p 150p
2 x 17 way 205p 180p
2 x 20 way 225p 190p
2 x 25 way 250p 200p
2 x 30 way 280p 220p

EURO CONNECTORS
DIN Socket Plug Plug
4618-31 way 180p Strt Angle
41612 A + B 290p 220p 235p
41612 A + C 310p 225p 240p
41612 A + B + C 380p 245p 280p

RIBBON CABLE
Grey Color price/ft
10 way 12p 22p
16 way 18p 32p
20 way 22p 40p
24 way 26p 50p
34 way 36p 60p
50 way 55p 75p

PANEL METERS
F89 60x46x35mm
0-50uA
0-100uA
0-500uA
0-1mA
0-5mA
0-10V
0-50mA
0-100mA
0-500mA
0-1A
0-2A
0-25V
0-50V AC
0-300V AC
"S"
"VU"
496p each

RELAYS
REED, Encapsulated, Single Pole, 5W Normally Open, 200mA, 50V DC
RL12 70011 6V to 9V 120p
RL13 1K1 9V to 12V 120p
RL14 1K71 12V to 18V 120p
RL15 3K1 18V to 30V 135p
Single Pole, Change Over
RL16 1K1 4V to 10V 295p
RL17 1K1 9V to 12V 295p
Double Pole, Normally Open
RL18 35011 9V to 12V 200p
Miniature, enclosed; PCB mount. Our RL6 series.
RL6-91 17011 coil, 7V5 to 12V DC; 380V/6A AC; 1300VA/50W D.P.C.O.
431 coil, 4V2-7V DC; 250V AC; 5A; 1100VA/150W 218p
RL6-111 17011 coil, 8V-14V; 250V AC 220p
RL6-114 74011 coil, 17V5-28V 250V 5A AC 222p

CRYSTALS
32.768KHz 170
100KHz 250
200KHz 290
455KHz 375
1MHz 290
1.008MHz 282
1.29MHz 320
1.8MHz 335
3.3MHz 335
1.8432M 220
2.0MHz 240
2.4576M 220
3.278M 98
3.5794M 98
3.8954M 300
5.1954M 150
4.032MHz 200
4.80MHz 200
4.194304M 200
4.43619M 120
5.0MHz 160
5.1954M 150
5.24288M 300
6.144MHz 140
6.5536MHz 225
7.188MHz 220
7.68MHz 150
8.0MHz 260
8.832M 200
9.00MHz 175
10.0MHz 175
10.24MHz 170
10.7 275
12.0MHz 200
14.31814M 150
15.0MHz 200
16.0MHz 170
18.42M 250
19.968MHz 160
20.0MHz 150
24.0MHz 170
27.84M 170
27.145M 160
38.66667M 330
48.0MHz 190
100.0MHz 295
116.0MHz 175

PIEZO TRANSUCERS
Type PB-2720 76p

BUZZERS, miniature, solid-state 6V, 9V & 12V 70p

LOUDSPEAKERS
Miniature, 0.3W; 8Ω
2in, 3in, 2 1/2in, 3in 80p
2 1/2in 4011, 6411 or 8011 80p

GAS & SMOKE DETECTORS
For the detection of combustible and Toxic Gases like: Propane, Butane, Methane, Ammonia, Carbon Monoxide, Sulphur and Organic solvents vapours like Alcohol, Benzene, etc. Ideal for use in Boats, Caravans etc.
Type: TGS81 & 813 525p
Socket for above 40p

ASTEC UHF MODULATORS
Standard 6MHz 280p
Wideband 8MHz 425p

ETI Autoringing Digital Capacitance Meter. All parts available.

CMOS

4000	10	4073	15	4536	286
4001	12	4076	15	4538	110
4002	12	4078	15	4539	110
4006	50	4077	18	4541	140
4007	15	4078	18	4543	100
4008	40	4081	16	4544	150
4009	24	4082	16	4549	375
4010	24	4085	60	4553	275
4011	11	4086	60	4554	190
4012	16	4089	125	4556	35
4013	25	4083	30	4556	35
4014	50	4084	120	4557	320
4015	60	4095	75	4558	120
4016	20	4096	75	4560	175
4017	22	4217	75	4566	175
4018	45	4098	75		
4019	25	4089	110		
4020	50	4160	95		
4021	60	4161	99		
4022	50	4162	99		
4023	15	4163	99		
4024	33	4164	99		
4025	16	4175	105		
4026	80	4194	105		
4027	24	4408	790		
4028	50	4409	790		
4029	60	4411	725		
4030	30	4411	675		
4031	125	4412	775		
4032	85	4415	480		
4033	125	4419	280		
4034	140	4422	770		
4035	85	4433	770		
4036	85	4435	850		
4037	115	4440	999		
4038	110	4450	350		
4039	290	4451	350		
4040	50	4490	350		
4041	60	4500	675		
4042	45	4501	28		
4043	50	4502	60		
4044	50	4503	40		
4045	105	4504	75		
4046	60	4505	35		
4047	60	4507	35		
4048	40	4508	150		
4049	25	45106			
4040	25	4511	50		
4051	45	4512	50		
4052	60	4513	199		
4053	50	4514	125		
4054	95	4515	125		
4055	95	4516	65		
4056	95	4517	275		
4057	1915	4518	40		
4058	60	4519	30		
4060	65	4520	30		
4061	2295	4521	130		
4062	995	4522	125		
4063	85	4526	70		
4064	30	4527	85		
4067	2965	4528	110		
4068	16	4529	110		
4069	18	4530	90		
4070	15	4531	130		
4071	15	4532	80		
4072	15	4534	485		

OPTO ELECTRONICS
LEDs with Clips
TIL209 Red 13
TIL211 Grn. 17
TIL212 Yel. 18
TIL220.2" Red 14
2" Green, Yellow or Amber 18
0.2" Bi colour 18
Red/Green 55p
Green/Yellow 78p
0.2" Tri colour 85p
Red/Green/Yellow 85p
Square LEDs, Red, Green, Yellow, 30p
Triangular LEDs, Red, Green or yellow 22p
LD271 Infra Red 46p
SPH205 Detector 91p
TIL32 Infra Red 58p
TIL78 Detector 90p
TIL38 45p
TIL100 80p
BARGRAPH, Red 10 segments 225p

ISOLATORS
IL74 55p
IL074 99p
IL074 185p
TIL111/2/4 90p
TIL117 125p
4N33 Photo Darlington 135p

7 Segment Displays
TIL307 675p
TIL312 3" CA 105p
TIL313 3" CC 105p
TIL321 5" CA 115p
TIL322 5" CC 115p
TIL704 3" CC 99p
DL707 3" CA 99p
DL747 6" CA 180p
8" Orange CA 250p
FND357 Red 120p
FND357 Green 120p
3" Green CA 150p
6" Green CA 215p
3" x 1 Red CA 150p
3" x 1 Green CA 150p
DVM178 1885p
LCD 3 1/2 Digits 595p
LCD 4 Digits 850p
LCD 8 Digits 750p

NEON with resistor, push fit. 2.50V mains. Round.
Red or Amber 30p
LCD 3 1/2 Digits 595p
giving Red, Amber, Green 30p
2N5777 45p
TIL139 170p
Reflective Optical Switch 290p

COMPUTER CORNER

- VIC 20 Micro Computer. Connects directly to a colour TV. Still only £185
- VIC Cassette Deck including a free 6 programme Cassette £185
- EPSON MX80T 90" Tractor Feed, 9 x 9 matrix, 80 column, Speed 80 CPS, Bi-directional, Centronics interface, Baud rate 110-9600 (RS232). £315
- EPSON MX80TF Has Friction feed & Tractor feed plus all the MX89's facilities. £345
- VIDEO MONITOR 9", B&W, Attractively cased, Fully guaranteed. Value for money at. £75
- SOFTY-2 As reviewed in PE Sept. '81 by Dr A.A. Berk. The complete microprocessor development system for Engineers and beginners alike. New powerful instructions. Accepts any 24 pin 5V single rail EPROM. Supplied fully built, tested. Enclosed in a black ABS case. Plug-in power supply included. £169
- TEX EPROM ERASER Erases up to 32 ICs in 15-30 minutes. £33
- SPARE 'UV' Lamp bulb £9
- 5V/5A Power Supply Ready-built & tested £25
- ABS CASE Attractive, Beige/Brown for Superboard, UK101 NASCOM, or Home brew £26
- Stack-Pak Drawers including 10 x C12 Cassettes. £50p
- C12 CASSETTES in library cases. 40p
- WEMON Watford's own 4K Ultimate Monitor IC specially designed to produce the best from your Superboard, UK101 & Enhanced UK 101 Superboard. As reviewed by Dr A.A. Berk in Practical Electronics June 1981. £15

(p&p on most of the above items is extra)

WATFORD'S UNIVERSAL MICRO EXPANSION SYSTEM
Designed by Watford Electronics, this extremely versatile and economical Expansion System as published in E.T.I., starting from December 1981 issue, offers a low cost flexible expansion system for: ZX81, UK101, SUPERBOARD, Acorn ATOM, PET, TANGERINE, TRS80, VIC 20, etc.
The Motherboard interfaces with the Computer has capability to accept up to five daughter Cards and can be paralleled for even more daughter cards. All PC Boards are of Computer grade and are supplied in Kit form.
Just Look at the Expansion possibilities:
MOTHERBOARD: Accepts up to five Daughter Cards. Full Kit: £36.50
SOUND CARD - Utilising up to three AY-3-8910 sound chips. (One supplied with Kit, Full Kit: £24.95
PIO Card - Using two 8250 PIA chips, this Board offers centronics parallel printer driver, digital to analogue converter & a host of other output facilities. Full Kit: £18.95
ROM Programmer - This simple but extremely useful card can blow 2716 or 2732 single rail EPROMs. Full Kit: £26.95
EPROM Card - P.C.B. cards for housing four 2716 or two 2732 EPROMS. For 4 x 2716 Full Kit: £11.95
For 2 x 2732 Full Kit: £11.75
RAM Card - 8K RAM card. Accepts 16 x 2114 chips. Supplied fully populated. Full Kit: £28.50
Coming soon: Speech Card, Disc Interface Card; 32K Dynamic RAM Card; High Resolution colour graphics Card.
(N.B. PCBs may be bought separately)

WATFORD'S BOOKSHOP CORNER

Texas TTL Data Book (Revised Edition) 850p
TTL Cook-Book 930p
European CMOS DataBook (Comprehensive) 755p
CMOS Cook-Book 695p
Illustrating BASIC 440p
A Bit of BASIC 640p
Advanced BASIC 840p
BASIC Computer Games 690p
More BASIC Computer Games 590p
Some Common BASIC Programs 1150p
Practical BASIC Programs 1250p
6502 Software Design 810p
6502 Application Book 1000p
Programming the 6502 (C202) 1100p
Programming & Interfacing the 6502 1120p
6502 Assembly Language Programming 1300p
6809 Assembly Language Programming 1350p
Practical Intro to PASCAL 560p
Using CP/M: A self teaching guide 950p
Z80 Microcomputer Handbook 840p
8080/Z80 Assembly Lang. Techniques 925p
Programming the Z80 (C280) 1250p
Z80 Assembly Language Programming Intro to TRS-80 Graphics 1300p
TRS80 BASIC - A self teaching guide 840p
PET & the IEEE 488 Bus (GP1B) 1350p
PET Graphics 1200p
PET/CBM Personal Computer Guide 1200p
PET Revealed 1000p
Library of PET Subroutines 1000p
Apple II Users' Guide 1250p
Programming in PASCAL (revised) 900p
CRT Controller Handbook 550p
CP/M Handbook with MP/M 1200p
Microprocessor Interfacing Techniques 1350p
S100 & Other Micro Buses 3E 750p
Writing Interactive Compiler 750p
Getting Acquainted with your ZX81 500p
Mastering Machine Code on your ZX81 800p
ZX81 Companion 800p
ZX81 Pocket Book 650p
32 BASIC Programs for the PET Computer 1350p
VIC Revealed 1000p

Please add 55p P&P charge on books
No VAT on books

CUSTOMER: How can WATFORD sell full spec devices so cheaply?
WATFORD: It's simple. By bulk buying (direct from manufacturers where possible), low overheads and smaller margins which give us an edge over our competitors.

Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!


Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

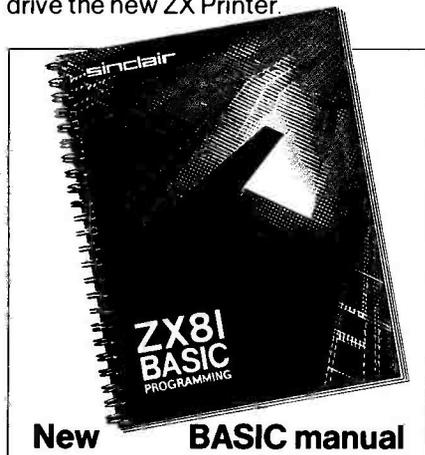And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

Kit: £49.⁹⁵

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 700 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



uter-



Available now - the ZX Printer for only £59.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha- numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call

01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.

Qty	Item	Code	Item price £	Order Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (700 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	29.95	
	Sinclair ZX Printer.	27	59.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing			2.95

Please tick if you require a VAT receipt

TOTAL £ _____

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____

*Please delete/complete as applicable. _____

Please print.

Name: Mr/Mrs/Miss _____

Address: _____

FREEPOST - no stamp needed. Offer applies to UK only.

ET106

sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB21SN.
Tel: (0276) 66104 & 21282.

AS THINGS GET TOUGH

**WHAT DO YOU DESIRE?
UNFORTUNATELY, THIS PROGRAMME CAN ONLY
OFFER TOTAL WINNING KNOWLEDGE, THE BASIC
ELEMENT SO ABSOLUTELY NECESSARY FOR
POSITIVE HUMAN DEVELOPMENT**

As a man thinketh, so he will be
This is a major breakthrough programme in human development disciplines which is destined to effect the lives of thousands of thinking men and women. It engages a remarkable new concept —

**A MULTI-DIMENSIONAL
APPROACH TO HUMAN
SUCCESS AND TOTAL
ACHIEVEMENT**

**A must for the Listening Library of
every thoughtful man and woman
GROWTH and RENEWAL**

Develop The Action Qualities And Success Attitudes Of The Winner

POSITIVE SELF-EXPERIMENTANCY
POSITIVE SELF-MOTIVATION

POSITIVE SELF-IMAGE
POSITIVE SELF-CONTROL
POSITIVE SELF-DIRECTION
POSITIVE SELF-AWARENESS
Even the first instructional tape will return to you many times over in the form of valuable self-redirection and attitude reinforcement, your investment

POSITIVE SELF-PROJECTION
POSITIVE SELF-DIMENSION

POSITIVE SELF-DISCIPLINE POSITIVE SELF-ESTEEM



SELF-REALIZATION

A lesson in winning — Broadside 1

is not a psychological gimmick but a profound professional in-depth study into the attitudes and the qualities that go into the formation of the total winner. It is a programme based upon years of exhaustive research, using clinically controlled feedback studies, into the every present human desire for success and achievement as the basic motivating winning force that brings men and women alike to the forefront of our society. It is a unique and masterful attempt to define and to formulate into a controlled audio pack, the exact guide lines for creating the winner.

The motivated need

**Have you ever given thought as to why some people are more successful than others?
The secret of the successful lies in direct relation to their positive attitudes and their defined purpose control.**

ACTION

**Each unit of human life is composed greatly from dreams derived from the unconscious. He who has the ability and know-how to translate them into positive reality, will truly be placed amongst the great. Ana is Nin
BROADSIDE 1 — THE INSTRUMENT OF HUMAN DEVELOPMENT**

**To: Broadside Associates
2 The Spinney,
North Gray,
Kent.**

GUARANTEE

I understand that if I am not fully satisfied, I can, within 15 days after despatch, return the complete programme and obtain a full refund.

Please send me the full Broadside 1 programme for which I enclose a cheque/postal order (crossed) for the sum of £25 (incl. VAT and Postage) made payable to BROADSIDE (allow a maximum 28 days for delivery)

PLEASE PRINT

Name

Address

Postcode County

Memotech's New Memory System for the ZX81

It grows as you progress



Memopak 16K Memory Extension


- £39.95 incl.VAT

It is a fact that the ZX81 has revolutionised home computing, and coupled with the new Memopak 16K it gives you a massive 16K of Directly Addressable RAM, which is neither switched nor paged. With the addition of the Memopak 16K your ZX81's enlarged memory capacity will enable it to execute longer and more sophisticated programs, and to hold an extended database.

The 16K and 64K Memopaks come in attractive, custom-designed and engineered cases which fit snugly on to the back of the ZX81, giving firm, wobble-free connections. See below for ordering information.

Coming Soon...

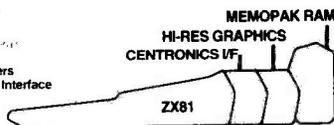Memotech Hi-Res Graphics
Centronics Interface and Software Drivers
Memotech Digitising Tablet RS232 Interface



All these products are designed to fit 'piggy-back' fashion on to each other, and use the Sinclair power supply. WATCH THIS SPACE for further details. We regret we are as yet unable to accept orders or enquires concerning these products – but we'll let you know as soon as they become available.

How to order your Memopak.

- By Post:** Fill in the coupon below and enclose your cheque/P.O./Access or Barclaycard number.
- By Phone:** Access/Barclaycard holders please ring Oxford (0865) 722102 (24-hour answering service).

Please make cheques payable to Memotech Limited
Please debit my Access/Barclaycard* account number

*Please delete whichever does not apply

SIGNATURE _____ DATE _____

NAME _____ ADDRESS _____



Memopak 64K Memory Extension

- £79.00 incl.VAT

The 64K Memopak is a pack which extends the memory of the ZX81 by a further 56K, and together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts basic commands such as 10 DIM A(9000).

BREAKDOWN OF MEMORY AREAS

0-8K ... Sinclair ROM

8-16K ... This section of memory switches in or out in 4K blocks to leave space for memory mapping, holds its contents during cassette loads, allows communication between programmes, and can be used to run assembly language routines.

16-32K ... This area can be used for basic programmes and assembly language routines.

32-64K ... 32K of RAM memory for basic variables and large arrays.

With the Memopak 64K extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

Unique 3 month trade-in offer!

When your programming needs have outgrown the capacity provided by 16K RAM, and you find it necessary to further extend your ZX81's capacity, we will take back your 16K Memopak and allow a discount of £15.00 against your purchase of our 64K model.*

*We reserve the right to reject, for discounting purposes, units which have been either opened or damaged in any way.

Please send me:

	Quantity	Price	Total
16K RAM, Assembled		£39.95	
64K RAM, Assembled		£79.00	
		Postage	£2.00
Total Enclosed			

ET13

We want to be sure you are satisfied with your Memopak – so we offer a 14-day money back Guarantee on all our products.
Memotech Limited, 3 Collins Street, Oxford OX4 1XL, England Telephone: Oxford (0865) 722102/3/4/5


DIGEST

Ace Catalogue

Whoops — we forgot to mention Ace Mailtronix in the 'Buying Mail Order' article. This is a shame because they've got a good little catalogue with a wide range of components at reasonable prices — what's more the prices are VAT-inclusive (I hate pricing an order and then finding I've got to add on 15%). Ace offer all the services in the survey except surplus components and books, and can be found at 3A Commercial Street, Batley, West Yorks, WF17 5HJ.


Power Tower

That's what Binatone are calling this hi-fi stack system, and what you have to do is guess the price of it. Nope, you're wrong — the whole lot costs £150. Honest. From the top down we've got a belt-drive record deck, three-waveband stereo tuner, stereo cassette deck with soft eject, LED meter and metal tape facility, 40 W total peak music power (hmmm...) stereo amp and matching two-way stereo speakers. The cabinet also has storage space for singles, albums and cassettes and at the price, Binatone are feeling quite pleased with themselves.

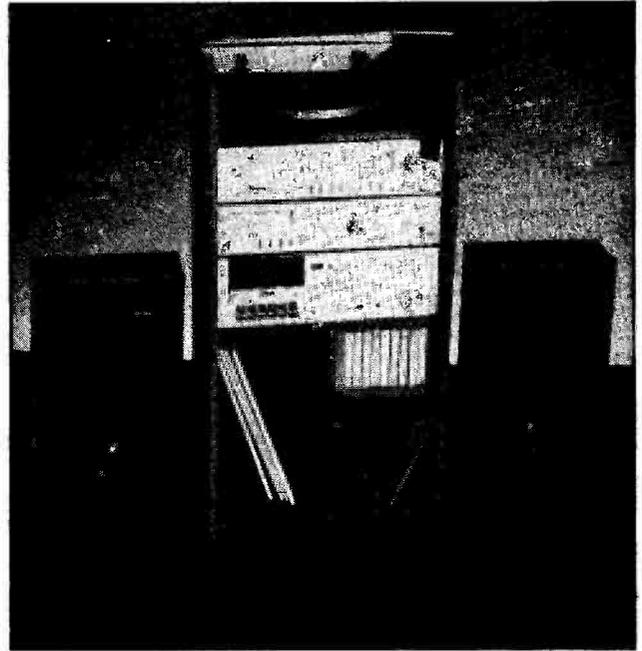

Eye Of The Needle

It's definitely electronics-as-art month; here's a sample of the work of Manchester photographer Ad Sternberg. Mr Sternberg has developed a unique method of photographing microchips, many of which are only slightly larger than a typewriter dot. Most of his work is done in full colour and is on display in companies such as Plessey, National Semiconductor and Ferranti. It took a great deal of time to develop the custom-built equipment for such an exacting branch of photomicrography, but the results are certainly worth it.

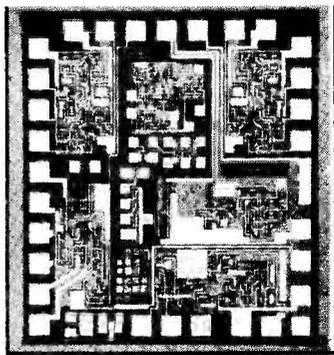

Robot Revival

We're not ones to boast, but since we published our report on Industrial Robots in September '81 things appear to be picking up a bit. The British robot population is now growing at more than 35% a year and has moved up to fifth in the world league table. Last year's total was approximately 700. Even more encouraging is the attitude of the unions, which is surprisingly lacking in hostility. In fact Terry Duffy, AUEW president, has this to say of robots on the factory floor: "Failure to accept the challenge of new technology would, in my opinion, be to sabotage our national future. Robots are here to stay." How very refreshing to hear such sensible sentiments.

Another promising trend is the entry into the market of the major computer manufacturers who, until now, hadn't bothered to compete with the specialist firms. GEC, for example, is expected to augment its own in-house robotics facility through co-operation deals with Japanese companies (Japan still dominates the world robotics scene). With this sort of investment by big companies there seems to be no reason why Britain shouldn't become a major supplier of industrial robots within the next two or three years.

Master Minds

What have the following five in common: Jack Kilby, Henry Ford, Ottmar Mergenthaler, Ernest O. Lawrence and Max Tishler? Well, no, none of them have appeared on the Muppet Show, but we had something else in mind. They've all just been appointed to the US National Inventors' Hall of Fame, and the one we're really interested in is Jack Kilby. He's the Texas Instruments engineer who, back in 1958, invented the integrated circuit and hence fathered all the goodies we've got today. Kilby holds more than 50 patents and is still going strong as a consultant to TI. Wonder what it feels like to be responsible for the state of the world's technology....

Dial-A-Muzak

It's bad enough being assaulted by non-stop muzak in shops and hotels but now you won't be able to escape even when making phone calls. The Hong Kong Trade Development Council have sent us details of the Music Phone; as well as the usual modern features like auto-redial and jack plug connection, this gadget has a 'music switch'. If someone wants to place you on hold without you hearing their discussion with a third party, this control plays soft music to you while you're waiting. The manufacturers, Yee King Enterprises Company, are producing 12,000 phones a month and exporting most of them to the USA and Europe; further evidence that it's all a fiendish oriental plot to subvert the West. Arrgggh!



Stamp On It

No real reason for using this photograph in Digest except that it intrigued us. Apparently it's

some kind of tiny inductor thingy and since none of you have got soldering irons that small you won't want to know anything else about it, will you?

Make it with MAPLIN



KEYBOARD WITH ELECTRONICS FOR ZX81

- * A full size, full travel 43-key keyboard that's simple to add to your ZX81 (no soldering in ZX81).
- * Complete with the electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections making entry far easier.
- * Powered from ZX81's own standard power supply - with special adaptor supplied.
- * Two-colour print for key caps.
- * Amazing low price.

Full details in our projects book. Price 60p. Order As XA03D

Complete kit for only £19.95 incl. VAT and carriage. Order As LW72P

25W STEREO MOSFET AMPLIFIER



A superb new amplifier at a remarkably low price.

- * Over 26W per channel into 8Ω at 1kHz both channels driven.
- * Frequency response 20Hz to 40kHz ± 1dB.
- * Low distortion, low noise and high reliability power MOSFET output stage.
- * Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
- * Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in our projects book. Price 60p. Order As XA03D

Complete kit for only £49.95 incl. VAT and carriage. Order As LW71N


MATINÉE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50. Order As XH55K.

Complete kits available: Electronics - £299.95,

Cabinet - £99.50 (carriage extra).

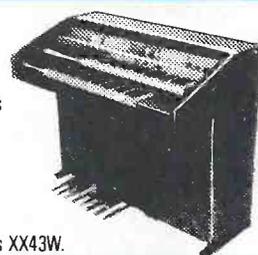Demo cassette price £1.99. Order As XX43W.



HOME SECURITY SYSTEM



Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability. Full details in our projects book. Price 60p. Order As XA02C.

MILES PER GALLON METER

Digital display shows you how economical your driving is as you go along.

Complete kits available.

Full details in our projects book.


Price 60p.

Order As XA02C.



DIGITAL MULTI-TRAIN CONTROLLER

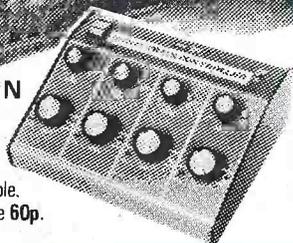Control up to 14 trains individually on the same track with any four simultaneously! Low cost kits available. Full details in our projects book. Price 60p. Order As XA02C.



Don't miss out - get a copy of our catalogue now! Over 140,000 copies sold already!

On sale now in all branches of WHSMITH price £1.

320 big pages packed with data and pictures of over 5,500 items.



Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded.

If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____

ETI682

MAPLIN

ELECTRONIC SUPPLIES LTD.

All mail to:

P.O. Box 3, Rayleigh, Essex SS6 8LR

Tel: Sales (0702) 552911 General (0702) 554155

Shops at:

159 King St., Hammersmith, London W6. Tel: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000

Note: Shops closed Mondays

Rapid Electronics

Tel: 0206 36412
Hill Farm Industrial Estate
Boxted, Colchester
Essex CO4 5RD



LINEAR			
*555 CMOS 80	ICL7106	790	LM382
555CMOS 150	ICL7621	180	LM384
*741 14	ICL8038	320	LM393
748 35	ICM7555	80	LM709
9400CJ 350	ICM7556	150	LM710
AY-3-1270 840	LF351	45	LM711
AY-3-891060	LF353	40	LM725
*AY-3-8912	LF356	90	LM731
625	LM10	395	*LM747
CA3046 60	LM301A	25	LM748
CA3080 65	LM3111	70	*NE555
CA3090 215	LM318	120	LM355
CA3130E 90	*LM324	40	LM391
CA3140E 45	LM330	50	LM395
CA3160E 100	LM348	65	LM3911
CA3160E 100	LM358	50	LM3912
CA3160 140	LM377	150	LM3915
CA3189 290	*LM380	65	LM13600
CA3240 110	LM381	120	MC1310

TRANSISTORS			
BC157 10	BC558 10	BF814 25	*TIP30
BC158 10	BCY70 18	BF815 25	*TIP30A
AC125 35	*BC159 8	BF816 25	TIP30B50
AC126 25	BCY72 18	BF817 25	*TIP30C
AC127 25	BC168C 10	BF818 25	*TIP30E
*AC128 20	BC169C 10	BD131 35	BFY50
AC176 25	BC170 8	BD132 35	BFY51
AC187 22	BC171 10	BD133 50	BFY52
AC188 22	BC172 10	BD135 50	BFY53
AD142 120	BC177 10	BD136 30	BFY55
AD149 10	BC179 18	BD138 30	BFY56
AD161 40	BC179 18	BD138 30	BRV19
AD162 40	BC182 10	BD139 35	BSX20
AF124 60	*BC182L 8	BD140 35	BSX29
AF126 50	BC183 10	BD204 110	BSY95A
AF139 40	BC183L 10	BD205 110	BW205
AF186 70	BC187 10	BF191 12	BF521
AF239 75	*BC184L 7	BF192 35	BU208
BC102 10	BC212 10	BF192 35	BU208
*BC107B 9	BC213 10	BF192 35	BU208
*BC108 9	BC213L 10	BF192 35	BU208
BC108C 12	BC214 10	BF191 12	BU208
*BC109 9	*BC214L 8	BF191 12	BU208
BC109C 12	BC237 8	BF192 35	BU208
BC114 22	BC238 14	BF198 10	MPS405
BC115 22	BC238 14	BF198 10	MPS405
BC117 22	BC238 14	BF198 10	MPS405
BC119 35	BC238 14	BF198 10	MPS405
BC137 40	BC337 14	BF245 25	MPS456
BC139 40	BC338 14	BF256B 45	MPS456
BC140 30	BC477 30	BF257 32	MPSU06
BC141 30	BC478 30	BF258 32	MPSU06
BC142 25	BC479 30	BF259 35	MPSU06
BC143 25	BC517 40	BF337 40	TIP29
BC147 8	*BC547 7	BF440 23	TIP29A
BC148 8	BC548 10	BF480 25	TIP29B
BC149 9	BC549 10	BF482 25	TIP29C

CMOS			
*4017 43	4018 43	4036 285	4055 115
*4001 14	4019 35	4040 55	4063 85
4002 14	4021 65	4042 55	*4066 35
4006 65	4022 70	4043 60	4067 395
4007 17	4023 18	4044 60	4068 15
4008 58	4024 40	4046 70	4069 18
4009 30	4025 18	4047 70	4070 18
4010 35	*4026 96	4048 55	4071 18
*4011 13	4027 30	*4049 28	4072 18
*4012 17	4028 55	4050 28	4073 20
*4013 26	4029 75	4051 28	4074 20
4014 60	4030 35	4052 70	4075 20
4015 60	4031 170	4053 60	4077 25
*4016 26	4034 170	4054 110	4081 18

TTL			
7400 11	7413 24	7442 40	7480 45
7401 11	7414 35	7444 40	7481 45
7402 12	7415 25	7446 60	7482 70
7403 14	7416 25	7448 45	7483 75
7404 14	7417 25	7450 16	7484 180
7405 17	7418 20	7451 16	7485 28
7406 26	7420 20	7452 16	7486 45
7407 26	7421 20	7453 16	7487 45
7408 15	7422 20	7454 16	7488 120
7409 16	7423 28	7455 16	7489 120
7410 16	7424 28	7456 16	7490 120
7411 20	7425 28	7457 16	7491 30
7412 20	7426 30	7458 16	7492 30
	7427 30	7459 16	7493 30
	7428 30	7460 16	7494 35
	7429 30	7461 16	7495 50
	7430 30	7462 16	7496 60
	7431 30	7463 16	7497 120
	7432 30	7464 16	7498 120
	7433 30	7465 16	7499 120
	7434 30	7466 16	7500 120

LS TTL			
LS00 13	LS21 15	LS76 20	LS125 30
LS01 14	LS22 16	LS78 24	LS126 30
LS02 14	LS23 16	LS81 30	LS132 45
LS03 14	LS24 16	LS82 35	LS133 45
LS04 15	LS25 16	LS83 35	LS134 45
LS05 15	LS26 16	LS84 35	LS135 45
LS06 16	LS27 16	LS85 35	LS136 45
LS07 16	LS28 16	LS86 35	LS137 45
LS08 16	LS29 16	LS87 35	LS138 45
LS09 16	LS30 16	LS88 35	LS139 45
LS10 16	LS31 16	LS89 35	LS140 45
LS11 16	LS32 16	LS90 35	LS141 45
LS12 15	LS33 16	LS91 35	LS142 45
LS13 25	LS34 16	LS92 35	LS143 45
LS14 48	LS35 16	LS93 35	LS144 45
LS15 15	LS36 16	LS94 35	LS145 45
LS20 15	LS37 16	LS95 35	LS146 45

REGULATORS		DIODES		HARDWARE	
Positive	Negative	BY127 12	*1N4001 3	PP3 battery clips	6p
78L05 30	79L05 65	OA47 10	1N4002 3	Red or Black crocodile clips	15p
78L12 30	79L12 65	OA90 8	1N4003 5	Black pointer control knob	60p
78L15 30	79L15 65	OA91 8	1N4004 5	Pr Ultrasonic transducers	350p
7805 45	79L15 65	OA200 8	1N5400 17	*6V Electronic buzzer	65p
7812 45	79L15 65	OA202 8	1N5404 16	*12V Electronic buzzer	65p
7815 50	79L15 65	IN914 4	*1N5406 17	*PB2270 Piezo transducer	75p
LM309K 130	LM723 40	*1N4148 2	400mV Zen 6p	*64mm 4 ohm speaker	70p
LM317K 320	LM338K 475	*BZ6X1 Series zeners		64mm 8 ohm speaker	70p
LM317T 120	78H05 150	*1.3W 4V7-39V 15p each		20mm panel fuseholder	25p
LM323K 350	5A 5V 550				

OPTO			
*3mm red 8	*5mm red 8	*3mm green 12	*5mm green 12
*3mm yellow 12	*5mm yellow 12		
Clips to suit 3p each			
Rectangular	TIL32 40	TIL78 40	TIL111 60
*red 12	TIL78 40	ORP12 85	TIL100 90
green 17	TIL111 60	TIL100 90	Dual color 60
yellow 17	ORP12 85	TIL100 90	
TIL38 40	TIL100 90		
2N5777 45	Dual color 60		
Seven Segment Displays			
Com cathode	Com anode		
DL704 0.3" 95	FD707 0.3" 95		
*FND500 0.5" 80	FND507 0.5" 80		
TIL313 0.3" 105	TIL312 0.3" 105		
TIL322 0.5" 115	TIL321 0.5" 115		

TRANSFORMERS	
Miniature mains	Please add carriage charge to suit normal post charges
60W, 90W, 120V all @ 100mA	100p each
High quality, Split bobbin construction	
6VA 0.6, 0.6 @ 0.5A, 0.9, 0.9V @ 0.4A	0.12 0.12 @ 0.1A 220p each.
12VA 0.6, 0.6 @ 1A, 0.9, 0.9V @ 1.2A	0.12 0.12 @ 0.5A, 0.15V @ 0.4A
25p each (plus 40p carriage)	
25VA 0.6, 0.6 @ 1.5A, 0.9, 0.9V @ 1.2A	0.12 0.12 @ 1A, 0.15, 0.15V @ 0.8A
330p each (plus 60p carriage)	
50VA 0.12 0.12V @ 2A, 0.15, 0.15V @ 1.5A	400p each (plus 75p carriage)

PANEL METERS	POTENTIOMETERS
Size: 60 x 46 x 35mm	Rotary, Carbon track Log or Lin 1K-2M2
0-500uA 0-500mA	Single 32p. Stereo 85p
0-100uA 0-1A	Slide 60mm travel single
0-500uA 0-50V AC	Log or Lin 5K-500K, 63p.
0-1mA VU	Preset. Submin horiz.
0-100mA 0-300V AC	100M-1M, 7p each.
0-100mA 0-25V	Cermet precision multirun.
495p each	0.75W 1/4in 10ohms to 100K. 80p each

REGULATOR MADNESS!			
Special prices on popular regulators.			
Prices valid to 30th June 82.			
78L105 T092	5	100mA	25p
78L12 T092	12	100mA	25p
7805 Plastic	5	1	38p
7815 Plastic	12	1	38p
7905 Plastic	5	1	45p

SOCKETS			
*8 pin 7p	22 pin 20p	24 pin 20p	26 pin 20p
*14 pin 10p	30 pin 32p	36 pin 32p	40 pin 32p
*16 pin 10p	Soldercon pins		
18 pin 15p	60p	100	
20 pin 18p			



CRYSTALS			
100KHZ 290	6.0M 300	6.144M 180	7.375 60
200KHZ 370	7.00M 250	7.375 60	7.412 43
1MHz 300	8.0M 170	7.412 43	7.418 60
1.000MHz 370	10.0M 180	7.412 43	7.418 75
1.6432M 300	10.0M 180	7.412 43	7.419 70
2.000 270	10.0M 180	7.412 43	7.419 70
2.4576M 220	10.0M 180	7.412 43	7.419 70
3.276M 240	10.0M 180	7.412 43	7.419 70
3.579M 120	18.432M 220	7.412 43	7.419 70
4.1M 150	19.968M 300	7.412 43	7.419 70
4.194M 150	18.6667M 320	7.412 43	7.419 70
4.433M 125	48.0M 220	7.412 43	7.419 70
5.0M 1240	116M 300	7.412 43	7.419 70

CAPACITORS			
Polyester Radial Leads 250V 280type			
0.01, 0.015, 0.022, 0.033, 6p; 0.047, 0.068, 0.1, 7p;	0.15, 0.22, 9p; 0.33, 0.47, 13p; 0.68, 20p; 1u 23p.		
Electrolytic Radial or Axial Leads			
0.47, 63V, 1.63V, 2.2, 2.63V, 4.7, 6.3V, 10, 25V, 7p;	22, 25V, 47, 25V, 8p; 100, 25V, 9p; 220, 25V, 14p;		
470, 25V, 22p; 1000, 25V, 30p; 2200, 25V, 50p			
Polyester Miniature Siemens PCB			
1n, 2n, 5n, 10n, 20n, 30n, 47n, 100n, 220n, 330n, 470n, 680n, 80p;	100n, 9p; 150n, 11p; 220n, 13p; 330n, 20p; 470n, 26p;		
680n, 29p; 1u, 33p; 220, 50p			
Tantalum bead			
1.0, 0.22, 0.33, 0.47, 1.0 @ 35V 12p; 2.2, 4.7, 10 @ 25V, 20p; 15/16V 30p; 22/16V, 27p; 33/16V, 45p;	47/6V, 27p; 47/16V, 70p; 68/6V, 40p; 100/10V, 90p.		

BOXES			
Dimensions in inches Aluminium			
3 x 2 x 1	70p	6 x 4 x 2	120p
4 x 3 x 1 1/2	85p	6 x 4 x 3	150p
4 x 3 x 2	100p	8 x 2 x 1	180p
Plastic with lid and screws.			
3 x 2 x 1in	55p		
4 1/2 x 3 x 1 1/2in	88p		
7 x 4 x 2in	160p		

PCB MATERIALS			
Alfac PCB transfer sheets - please state type (e.g. DIL pads etc.)			
Dalco etch resist pen	100p		
Fibre glass board 3.75" x 8"	75p		
Ferric Chloride 250ml bottle	100p		

SOLDERING IRONS			

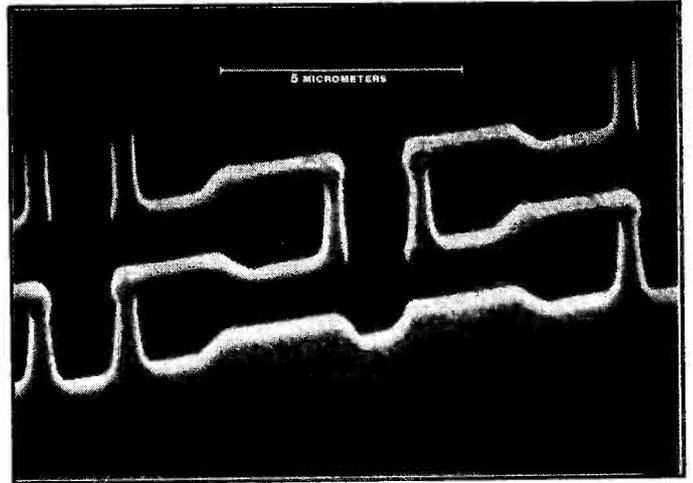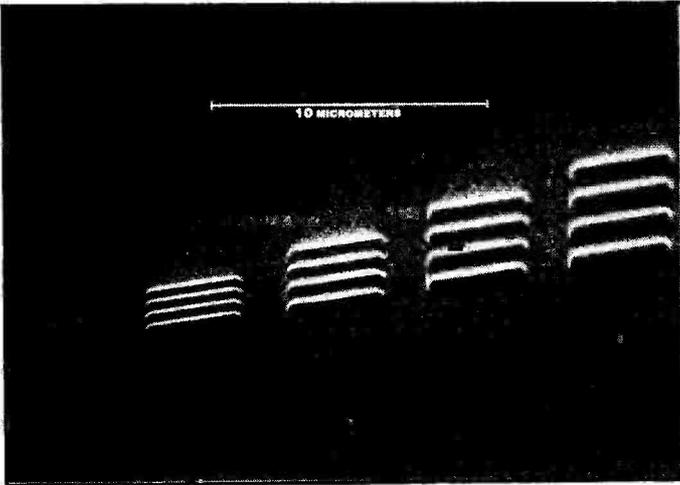


Submicron Sculpture

These remarkably neat and tiny patterns were produced using the new Direct-Write Lithography System (VLS-1000) developed by Varian Associates of California. The system will produce high-density, submicron circuits at a throughput of 10-15 four inch wafer levels per hour. The first picture is a resolution test pattern while the second is a gate array pattern — somewhat beautiful, is it not?

New UD

Maxell have brought out a new MUD cassette with a considerably better performance than the previous one. High frequency saturation level, bias noise level and housing stability are said to be particularly good. Apparently it's due to the wonder ingredient, New PX Gamma Ferric Oxide, which has fewer voids and more uniform particle size. The magnetic particle layer is also extremely uniform, causing modulation noise and DC noise to be minimised. The New UD cassettes will be on sale from early April. By the way, lads, just love the new TV ad.

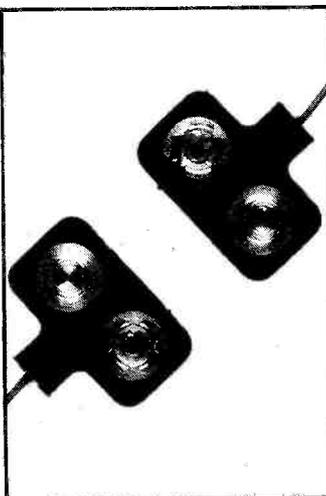


Making Connections

A new range of low cost moulded battery clips have been announced by Dau. The moulded connector (a PP3 type is shown) offers long term reliability by overcoming corrosion problems. For further information contact Dau (UK) Ltd, 70-74 Barnham Road, Barnham, Bognor Regis, West Sussex PO22 0ES.

Shorts

- Good news for kit builders — the new Spring/Summer 82 catalogue from Heathkit is out, with several additions to their already extensive range and a Spring Sale on many items.
- A word processing package is now available for the TRS-80 Model I and II that offers a professional range of facilities for a reasonable price. You'll need 48K, one disc drive, and £79.00 plus VAT and postage. "Newsprint" is available from E.A. International, 8 High St., Meldreth, Royston, Herts SG8 6JV.
- Hewlett-Packard are getting a bit carried away with VLSI technology — they've just developed a chip set for mainframe-like performance which includes a 32-bit processor running off an 18 MHz clock, a 16K x 8 RAM and a 16K x 40 ROM chip. Jeez....
- Made in Wales... the TC-2011 20" colour TV from Panasonic. The set features auto-search tuning, channel memory, a teak cabinet and 3 W audio output, and is available now from authorised dealers.
- Celdis of Reading can now supply the new Mostek MK4802 16K static RAM direct from stock. Organised as 2K x 8 for ease of use, the chip is compatible with all the other members of Mostek's Bytewyde memory family.
- The latest BAEC newsletter has reached us; amongst other things it contains a catalogue survey, projects, book reviews and a nice write-up on the Breadboard exhibition. Thank you, gentlemen — we're glad you enjoyed it too.
- Rapid Electronics are on the move — by the time you read this they'll be at Hill Farm Industrial Estate, Boxted, Colchester, Essex. This is just off the A12 and Rapid say callers will be most welcome.
- Winner of the recent "Office of 2000 AD" design competition was an attache case containing a data processor/transmitter/receiver; if you press a button the case describes itself and how it works through a built-in loudspeaker. The day my briefcase starts talking to me is the day I give up the Beaujolais....

- Still and moving pictures from one shop; the Fotovalue photographic franchise are to introduce Telefunken VHS video into their camera shops. Products for sale are a video recorder, four televisions, accessories (including a Teletext adaptor) and a colour camera.
- Good old Goonhilly (you remember, Telstar and all that) is to get a facelift. British Telecom are replacing the antenna ready for use with the Intelsat system from the end of 1984. Cost is estimated at £3 million.
- Semiconductor Specialists are now stocking two of Raytheon's high-performance dual low-noise op-amps, the RC5532 and the RC5532A. Suitable for applications in high quality audio equipment and instrumentation circuits, these chips are an all-round improvement over standard items such as the 1458.
- Why send us a press release about Britain exporting Tigers to Africa, we wondered? Because Tigers are telephone management and accounting systems manufactured by Minster Automation, that's why. Nice to see some foreign cash flowing this way for a change.
- IMF Electronics have launched a couple of professional monitor loudspeakers and a studio monitor. They feature such esoteric delights as a "ferro-fluid damped tweeter" and are apparently rather good.
- KGB Micros Ltd are now selling an IEEE 488 interface bus for Superbrain for £200. With a name like that, how can you dare refuse to buyone?
- Build a better photodiode and the world will beat a path to your door. The BPW41D from Ferranti has a very high rejection of wavelengths below 700 nm and is ideal for infra-red remote control and data transmission systems.
- Mitsubishi — bless you — have recently succeeded in manufacturing an amorphous solar cell, with the world's highest energy conversion efficiency (8.5%). My dictionary says amorphous means 'shapeless'; must be great fun trying to build them into equipment.

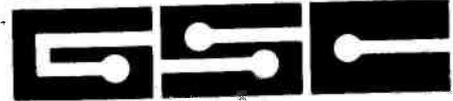

At last the message has come through, all you old solderers can throw away the soldering irons and the perforated circuit boards. NOW you can use PROTO-BOARDS from GSC. Despite daily break-throughs in components and packaging, designing and testing new circuit concepts is often a lot more manual work than creative work. No wonder if you are using old fashioned perforated boards and time-consuming soldering. With PROTO-BOARDS any component can be plugged in, tested, removed, and used again. Circuits can often be designed from component pinouts and the circuit diagram does not need to be drawn until after the circuit is working properly. PROTO-BOARD designing is very much like careful single-sided printed circuit design in terms of the effects of parasitics and in terms of operation at high frequency or low levels. Well planned grounds and judicious use of shielded cable can permit operation through VHF frequencies. So, you old solderers, stop soldering on! Send off for our FREE 40 page catalogue; we have a PROTO-BOARD to fit any size budget.

PROTO BOARDS

Models PB-203, PB-203A and PB-203AK offer a large breadboarding area and a built in regulated power supply housed in a rugged metal cabinet. Models PB6 to PB105 offer various breadboarding areas screw mounted onto sturdy back plates with non slip, non scratch vinyl feet. Red and black binding posts are included, the red being electrically insulated from the back plate, the black being electrically connected for ground.

PB 203

Includes 5VDC, 1 amp power supply, available at binding posts, two binding posts (V1, V2) remain uncommitted. The perfect board for TTL and other 5 volt logic designs.

PB 203A

Every development engineer should have one of these, includes 5VDC 1 amp power supply. Also includes separate + 5.5 to 18 VDC and + 5 to 18 VDC power supplies, each capable of supplying 500 mA at 15 VDC. Power supplies are factory preset to + 15 VDC but can be independently adjusted.

PB 203AK

Identical to PB 203A but in kit form.

PB 6

A kit form breadboard with 4 binding posts, 630 contact points and includes non slip rubber feet.

PB 100

Another kit form breadboard with 760 contact points.

PB 101

A robust laboratory breadboard accepts up to 10 IC'S, 940 contact points.

PB 102

A fully assembled breadboard with 1240 contact points.

PB 103

With 2250 contact points this board is perfect for prototyping and custom circuit applications.

PB 104

A total IC capacity of 32 with 3060 contact points makes this the ultimate electronics development engineers breadboard.

PB 105

The newest Protoboard, 4560 contact points, 48 IC capacity!

24 HOUR SERVICE FROM GSC

Call (0799) 21682 with your Access, American Express, Barclaycard number and your order will be put in the post immediately.

MODEL NO	NO OF SOLDERLESS TIE POINTS	IC CAPACITY (34 pin DIP's)	UNIT PRICE	PRICE INC P&P 15% VAT	QTY REQUIRED
PB6	630	6	9.75	12.30	
PB100	760	10	12.50	15.52	
PB101	940	10	17.90	22.31	
PB102	1240	12	24.95	30.41	
PB103	2250	24	39.00	46.57	
PB104	3060	32	49.00	56.07	
PB105	4560	48	71.00	83.95	
PB203	2250	24	61.00	72.95	
PB203AK	2250	24	89.00	104.65	
				83.95	

NAME

ADDRESS

I ENCLOSE CHEQUE / P.O. FOR £

DEBIT MY CREDIT CARD NO

EXPIRY DATE

PLEASE SEND FREE CATALOGUE TICK

GLOBAL SPECIALTIES CORPORATION Global Specialties Corporation (UK) Ltd,
 Dept 90
 Unit 1
 Shire Hill Industrial Estate
 SAFFRON WALDEN
 Essex
 CB11 3AQ

West Hyde Wonders

We've just received the latest West Hyde catalogue; curiously they're always out of step with the seasons (this one's dated Winter 81-82) but who cares, there are lots of goodies inside. With boxes and racks to suit any application you can think of, and then some, this is definitely the first place to look if you're after an enclosure.





Solar Sums

Provided you don't want to do any calculations in the dark, Hanimex's new light-activated calculators dispense with the need for batteries. Even dim light is sufficient now that a new generation of very efficient light-sensitive cells have been developed, and Hanimex expect these calculators will become the leading solar calculators of the year. The SC852 has a list price of £13.95 while the 853 is £10.95.

Who's Kidding Who?

Now this is very silly. In fact we thought it was a joke, except that the press release is dated March 1st, not April 1st. Anyway, BL Systems and ITR have announced the TARDIS — Time and Attendance Direct Input System — which is claimed to be much more efficient than traditional shop floor clocking-on methods. It says here that the key feature of TARDIS is the use of TIMELORD clocks — honest! — and that the computer-controlled system cuts the work involved in payroll/attendance calculations by up to 75%. Watch out, Doctor; the Time-and-motion Men are out to get you!

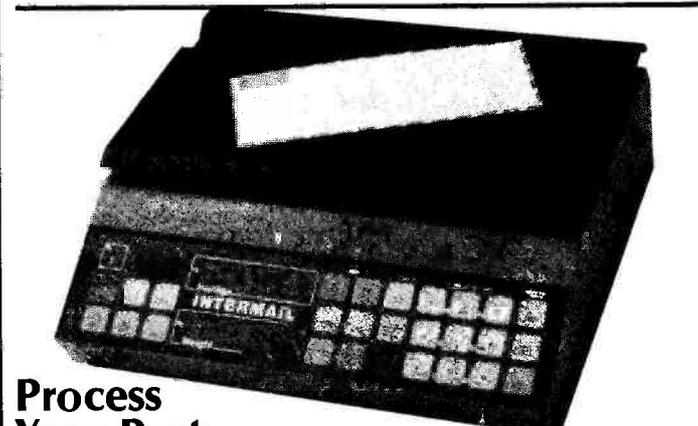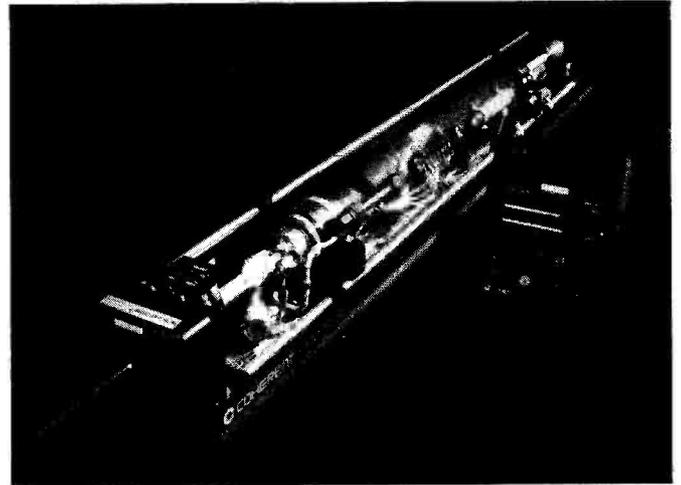

Process Your Post

Hands up all those with ordinary weighing machines in their postrooms? Bit of a drag, isn't it, peeling the sticky labels off the scale and fixing new ones every time the PO puts its rates up? This microprocessor-controlled scale can be easily updated by the customer to keep track of inflation, and it offers a lot more


besides. The scale is "user-friendly", letting you know what you've done wrong, and can be helpful in other ways (weighs?) too. For example, it can tell you the cheapest way to send a packet overseas. For more details on the Intermail XK 10/25 contact Paul Numan of C. Stevens and Son (Weighing Machines) Ltd, 287/289 Goswell Road, London EC1V 7LD.

In Coherent

Innova 90 lasers, developed by Coherent (UK) Ltd and to be exhibited at Electro-optics/Laser International 82, are an entirely new concept in ion laser design. The "Cool Disc" bore technology gives higher guaranteed power capability with longer life expectancy, while other design features mean a hands-off, trouble-free laser for both research and industry. Maybe we can get our hands on one and have a real game of Space Invaders...

A Fine Pear

Apparently the microcomputer industry has some sort of pre-occupation with fruit. We already have the Apple and Tangerine systems and shortly we'll have the PEAR II. This PAL-colour microcomputer is based on the ubiquitous 6502 microprocessor and is intended for the more advanced user who wants to choose from various programming languages. Typical options are BASIC, Pascal, FORTRAN or COBOL. The standard system has 32K of RAM, on-board expandable to 96K using bank-select. Further expansion to suit your requirements is accomplished using plug-in cards. The PEAR II will be available around September/October of this year for £975 plus VAT, and further information can be obtained from Pearcom Ltd, 17 Nobel Square, Basildon, Essex SS13 1LP. Anyone for pomegranite?

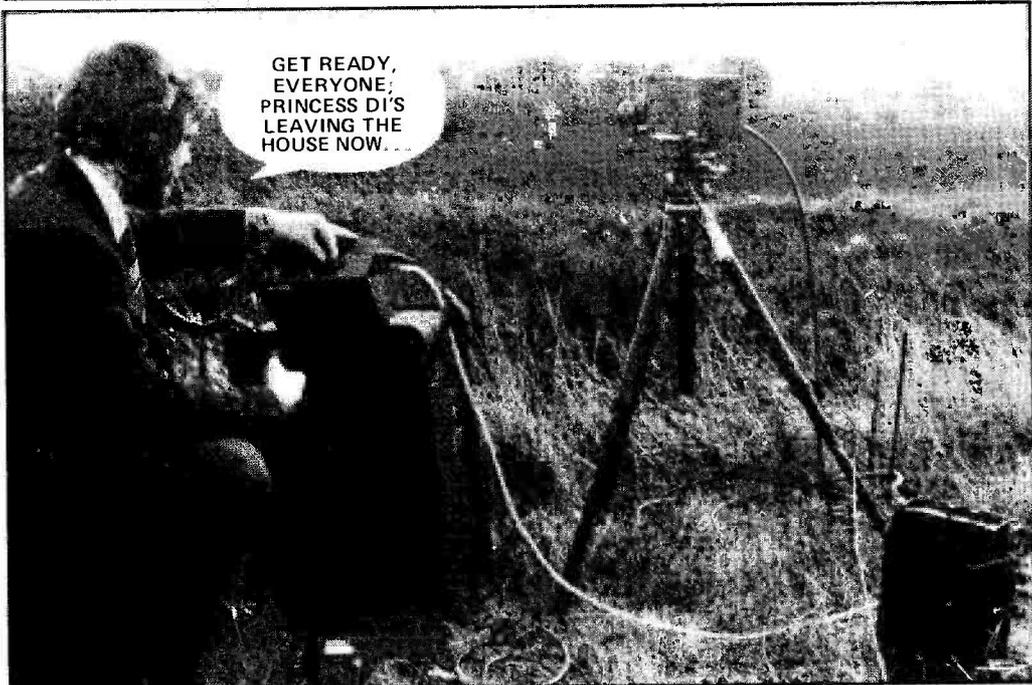

Dai-Electric

Hospitals at Wrexham and Swansea are to have reliable fire and alarm monitoring systems fitted by the Welsh Health Technical Services Organisation. The Statican System is based on a single three-core cable and uses time-division multiplexing to transmit hundreds of signals from the monitoring points to the central consoles. (Of course, you all know about TDM because we featured it in Notebook in April.) The system is produced by Static Systems Group of Wolverhampton and will no doubt be of great use when the home rule nuts run out of English holiday cottages to burn. •

ENFIELD ELECTRONICS

For up to the minute prices please ring:-
01-366-1873.
Please add 15% VAT
+ £1.00 p & p per item ordered.



A superb stereo headphone

Specifications:

- 1) sensitivity 110DB at 1,000Hz with 1mw
- 2) Frequency response: 20-19,000Hz
- 3) UNIT impedance 8 ohms
- 4) matching impedance 4-16 ohms
- 5) Maximum input 0.5 watts per channel
- 6) Individual slide volume control (stereo/mono switch)
- 7) 10 foot coiled cord with stereo phone plug
- 8) Leathery-soft ear pads and head cushion

price £5.95.
Order No. LE-76VS



IDEX

stereo headphone
Sensitivity 98dB at 1kHz with 1mw.
Frequency response 20-25,000 Hz. Impedance 35 ohms.
Maximum input 0.4 watts. 7ft cord with 3.5 stereo phone plug.


Price £7.50
Order No. MHD-3



Altai Multitester & Transistor Tester

DC volts 0-1v-5v-2.5v-10v-50v-250v-1000v ± 3%
AC volts 0-10v-50v-250v-1000v ± 3%
DC current 0-50uA-2.5mA-25mA-0.25A ± 3%

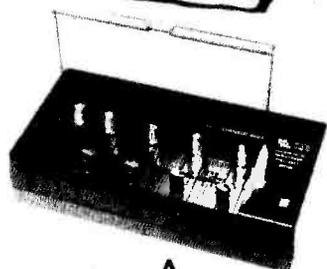Resistance:
Minimum 0-2.2-200-200k ohms
Midscale 20-200-20k-200k ohms
Maximum 2k-20k-2m-20m ohms } ± 3%
As a transistor tester
Leakage current 0-150uA at X1k range
0-15mA at X10 range
0-150mA at X1 range } ± 5%
Price £14.95
Order No YN 360TR



Regulated power supply with short circuit protection. On/off Power LED. Protection by primary fuse.
Input: 240V AC. 50 Hz
Output:- 12V nominal DC (13.8V DC)
Rating:- 3 amps (5 amp surge)
Dims:- 155 x 115 x 60mm

Price £11.95
Order No. PP 1203 GS

Universal NI-CAD, battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges:- PP3 (9V), U12 (1.5V penlite), U11 (1.5V "C"), U2 (1.5V "D"). Power:- 220-240V AC. Dims:- 210 x 100 x 50mm.
Super Special Offer at only £7.50.

Order No. MW 398



This 3 1/2 inch super horn (Flush Flange) piezo ceramic tweeter converts electrical energy into acoustic energy at an efficiency in excess of 50%, a level not possible with any other type of loudspeaker. Economy is added to high efficiency by the elimination of crossover networks, because the unit rejects low frequency power. It has a high impedance of over 1,000 ohms at 1 kHz and 20 ohms at 40 kHz and it presents no added load to the amplifier.



A Super Special Offer of £4.65
Order No LOS2

NOISE FILTER SYSTEM

A sophisticated combination of filters designed to eliminate interfering noises from all vehicular sources including ignition spark, alternator/generator, other accessories, metal to metal contact etc.

Contents:- Generator noise filter, alternator noise filter, Dual line noise filter and ignition noise filter.

Price £8.50
Order No. NFS-1000

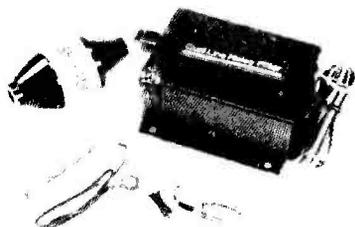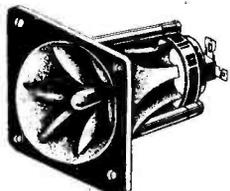

Please allow 21 days for delivery.

Adaptors	Cable Cont. wrapping stripper	Desolder braid	Frequency counter	LED displays	Pre-amps	Sockets	Tinned copper wire
Adhesives	Chokes	Desolder pump	Gas sensor	Mains adaptor	Photo electric relays	Sleeving	Transducers
Aerials	Capacitors	Diacs	Grommets	Matrix board	Rectifiers	Solder	Toroids
Alarms	air spaced	Diodes	Group panels	Memory I.C.s	Resistors	Soldering irons	Terminals
Aluminium boxes	trimmer	light emitting photo rectifier	Gronso	Meters	carbon film	Sirens	Tuning cells
A.B.S. boxes	suppression lead through ceramic	signal zener germanium infra-red	Headphones	Microphones	metal film	Speakers	Tuning condenser
Amplifiers	electrolytic polyester	Displays	Heat sinks	inserts	metal oxide	Switches	Ultrasonic
Audio leads	silver mica tantalum	Drills	Inspection glasses	stands	wirewound	mercury tilt micro reed	transmitter
Audible warning devices	Enamelled copper wire	Earpieces	I.C.s	Microprocessors	Ring cores	rockers	Ultrasonic receiver
Batteries	Coilformers	Earphones	I.C. sockets	Morse key	Regulators	rotary	Vero products
chargers	Connectors	Enamelled copper wire	Infra-red source	Multistors	Relays	toggle	
connectors	Coils	Etch resist products	Infra-red sensor	Neon bulbs	Resistance chart	water slide	
holders	Continuity testers	Filters	Indicators	Ni-Cad batteries	Signal injector	push-button	
Bezels	Convertors	Ferric chloride	Insulating tape	Ni-Cad chargers	Service aids		
Books	Crimp tools	Ferrite cores	Jack connectors	Opto electronic	silver paint		
Boxes	Crocodile clips	Ferrite rods	Jewellers screwdrivers	Oscilloscopes	switch lubricant		
Bridge rectifiers	Crystals	Fixing feet	Knobs	Panels	solder mop		
Bulbs	Demagnetisers	Fuses	Keynector	Pick-up coils	silicone grease		
holders		Fuse holders	Knobs	Pliers	anti-static spray		
Busbars		Fluorescent displays	Lamps	Pre-sets	freelitz		
Buzzers		Field strength motors	Lamp holders	Potentiometers	plastic seal		
Cable			Leads	P.C.B.s	Aero klene		
clips			Liquid crystal displays	P.C.B. transfers	heat-sink compound		
ties			LED displays	Probes	Aero duster		
markers			LED arrays	Plugs	Spacers		
sleeving				Pressure mats	SWR meters		

We are open from
9am-6pm
Monday
to
Saturday

208 Baker Street, Enfield, Middlesex.
01-366 1873.

BI-PAK BARGAINS



5T21 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET
5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm **£1.75**

5T41 TOOL SET
5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers - H 0 and H 1 Hex key wrenches - 1.5, 2 and 2.5mm **£1.75**

5T51 WRENCH SET
5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm **£1.75**
BUY ALL FOUR SETS 5T21, 5T31 and get HEX KEY SET FREE
HEX KEY SET ON RING
Sizes 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm
Made of hardened steel
HX/1 **£1.25**



BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
*3 1/2 digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single handed, pushbutton operation *Over range indication *12.5mm (1/2 inch) large LCD readout *Diode check *Fast circuit protection *Test leads, battery and instructions included

Max indication 1999 or - 1999
Polarity indication Negative only
Positive readings appear without + sign
Input impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range -5°C to 50°C
Power Supply 1 x PP3 or equivalent 9V battery
Consumption 20mW
Size 155 x 88 x 31mm

RANGES
DC Voltage 0-200mV
0-2-20-200-1000V Acc. 0.8%
AC Voltage 0-200-1000V
Acc. 1.2% DC Current 0-200uA
0-2-20-200mA 0-10 A. Acc. 1.2%
Resistance 0-2-20-200k ohms
0-2 Megohms Acc. 1%
BI-PAK VERY LOWEST POSSIBLE PRICE
£35.00 each



"IRRESISTABLE" RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm-2M2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 Meg. Save pounds on these resistor paks and have a full range to cover your projects
*Quantities approximate, count by weight.

"CAPABLE" CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pf-56pf	£1
SX19	100	Mixed Ceramics 68pf-0.5mf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000µf	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180° 240°, Inline 3-6 Pin, Speakers, Phono, Jack, Stereo and Mono, etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

SX26	3 Pcs. of 6 pin 240° DIN Plugs and Chassis Sockets	50p
SX27	1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket.	30p
SX28	4 Phono plugs and 2 dual phono connectors	30p
SX29	1 x 2.5mm Plug to 3.5mm Socket adaptor	20p
SX30	1 x 3.5mm Plug to 2.5mm Socket adaptor	20p
SX31	1 x 3.5mm Plug to Phono Socket adaptor.	20p

BARGAINS


SX91	20 x Large .2" RED LED	£1
SX42	20 small 125 Red LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded New.	£1
SX47	4 Black Instrument Knobs-winged with pointer 1/4" Standard screw. Fil size 29 x 20mm.	50p
SX49	20 Assorted Slider Knobs. Black/Chrome, etc.	£1
SX80	12 Neons and Fluorescent Lamps. Low voltage and mains - various types and colours - some panel mounting	£1

MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm
Bi-Pak's Mini Vice at a Mini Price only

£2.50

ORDER NO. SX82

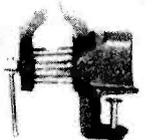

The Third and Fourth Hand...

... you always need but have never got "until now" This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
Without magnifier ORDER NO. T400 **£4.75**



MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer. MM100G suitable for guitar pre-amp mixer.
The MM100 and MM100G mono pre-amplifiers are compatible with the AL60, AL80, AL120 and AL250 power amplifiers and their associated power supplies.
MM100 Supply voltage 40-65v inputs. Tape Mag P.U. Microphone Max output 500mv **£12.45**
MM100G Supply voltage 40-65v inputs 2 Guitars, Microphones Max output 500mv **£10**



SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. Ins.	Price
FB1	4	9 x 2 1/2"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD


FB4	2	14 x 4"	110	£2.00
-----	---	---------	-----	-------

SILICON POWER TRANSISTORS - 703

NPN like 2N3055 - but not full spec
100 watts 50V min.
10 for £1.50 - Very Good Value
100s of uses - no dud's
Order No. SX90

BI-PAK SOLDER - DESOLDER KIT

Kit comprises ORDER NO. SX80
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit
1 Quality Desoldering pump - High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle
1.5 metres of De-soldering braid on plastic dispenser
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt tool Tweezer Type
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£8.95**

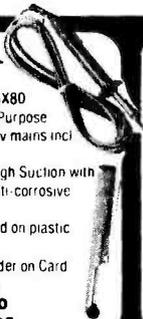

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12V DC incl 3 collets & 1 x 1mm Twist bit
1 Sheet PCB Transfers. 210mm x 150mm
1 Etch Resist Pen.
1 1/2 pack FERRIC CHLORIDE crystals
3 sheets copper clad board.
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.75**
ORDER NO. SX81



MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with built up lid. Charge/Test switch. LED indicators at each of the five charging points
Charges - Power -
PP3(9V) - 220-240V AC
U12 (1.5V penlite) - Dims -
U11 (1.5V C) - 210 x 100 x 50mm
U2 (1.5V D) - **£8.95**

POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket
Fused for safety. Polarity reversing socket.
Voltage switch. Lead with multi plug
Input 240V AC 50HZ Output -3 -4 -5 -6 -7 -5 -9 & 12V DC Rating - 300 ma MW88

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification
● Power Output 5 watts RMS ● Load impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz -3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%
BI-PAK'S give away price




£2.25

You could not build one for this price.

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers - rotary and slider, presets - horizontal and vertical. Resistors of mixed values 22ohms to 2M2 - 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish! all identifiable and valued in current catalogues as well over £25.00. Our Fight Against Inflation Price -

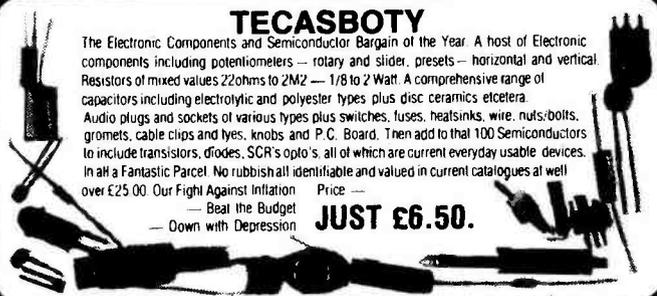— Beat the Budget
— Down with Depression
JUST £6.50.



BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember: Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time - it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p



BI-PAK

Send your orders to Dept ET16 BI-PAK PO BOX 6 WARE HERS
SHOP AT 3 BALDOCK ST WARE HERTS
TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS
BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182, GIRD 388 7006
ADD 15% VAT and 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order.
Total Postage add 75p per total order.

electronics today

NEXT
MONTH

INTERNATIONAL

TV BARGRAPH

Surely your television can be put to better use than as an aid for insomnia? The video game manufacturers pointed the way and we've published a couple of designs ourselves — but how about using the television as a research tool? Next month we do just that with our TV Bargraph project; a device that displays analogue voltages as a histogram (columns) on any domestic 625-line set. The horizontal axis may be at the bottom of the screen (for positive-only inputs) or half-way up for AC signal displays, and the number of channels is user-selectable. The basic unit has eight, while additional channel cards will give 16, 32 (how about 1/3 octave spectrum analysis over the audio band?), 64 and even 128 channels on a good TV. We could have used a video controller chip for this project, but you wouldn't have learnt much from it; the circuit uses standard logic ICs so you can see how the TV sync signals are generated. Don't wait for ITV2; get a new channel on your telly with the July ETI.

MOSFET BRIDGING MODULE

Now you'd think most ordinary people would be more than happy with the power output of the MOSFET amplifier published this month. But we know better. Time and again it's been proved that ETI readers like to provoke their neighbours, weaken their foundations and generally make their presence felt with LOUD music; and who are we to argue? To forestall the inevitable requests for more power, next month we show you how a cheap, simple add-on circuit will enable you to bridge two ETI-5000 modules, giving a 300 W output and shattered windows in the living room.

**LOOK OUT
FOR THE JULY ISSUE
ON SALE JUNE 5th**

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

VIDEO SYSTEMS

Next month we fearlessly take the lid off video recording — literally. Taking time off from hi-fi, Stan Curtis has been unbolting all kinds of video recorders and finding out exactly what's inside and what it does. You never knew there was so much in it. Don't miss the July issue for the story even the video magazines couldn't bring you.

AUDIOPHILE

We've been waiting to get our hands on one of these for a long time. Look at the sleek lines, the compact build, the elegant black enclosure, the hint of mysteries within to enthrall you long into the night. (And if you haven't figured out that next month's article features the power amp rather than the admittedly lovely lady, then one of us has the wrong magazine). The long months of flattery, threats, bribery and begging have finally resulted in a Magnetic Field Power Amplifier — the Carver Cube — being delivered into the hot, eager hands of your editor (now stop that!). As Stan Curtis pointed out a year ago, this extraordinary amp is only 7" on a side and can punch out an incredible 200 W per channel. In that article the technical merits of the design were examined; now Ron Harris can reveal all concerning the sound quality. It's in Audiophile next month — be there!



The MICRO PROFESSOR solves the 'mystery' of micro-processors.

Micro-Professor is a low-cost Z80A based microcomputer which provides you with an interesting and inexpensive way to understand the world of microprocessors.

Micro-Professor is a microprocessor learning tool for students, hobbyists and engineers. It is also an ideal educational tool for teaching in schools and universities.

The main object of **Micro-Professor** is for the user to understand the software and hardware of a microcomputer easily and conveniently. Besides the complete hardware/software system you have the users experimental manual. It includes self-learning text with 20 experiments which range from simple, software

programming to designing a complex electronic game. Completed programmes can be stored and re-read via the cassette interface. 2K bytes of monitor source program with documentation is also provided in the manual.

Micro-Professor provides a wide range of other applications: Low cost prototyping tool • Low

cost development tool • Process controller • Electronic music box • Timer • Noise generator • Home appliance control • Burglar alarm • System control simulation Tester

... and much more!

New Add on products
Speech synthesiser board
EPROM programmer board

TECHNICAL SPECIFICATION

CPU Z80A CPU high performance microprocessor with 158 instructions.

SOFTWARE COMPATIBILITY Capable of executing Z80/8080/8085 machine language program.

RAM 2K bytes expandable to 4K bytes.

ROM 2K bytes of sophisticated monitor expandable to 8K bytes.

INPUT/OUTPUT 24 system I/O lines.

DISPLAY 6 digit 0.5" red LED display.

AUDIO CASSETTE INTERFACE 165 bit per second average rate for data transfer between memory and cassette tape.

EXTENSION CONNECTORS Provides all buses of CPU, channel signals of CTC and I/O port bus of PIO for user's expansion.

COUNTER TIMER CIRCUITS Socket is provided. Z80-CTC IC extra.

PARALLEL I/O CIRCUITS Socket is provided. Z80-PIO IC extra.

SPEAKER AND SPEAKER DRIVER CIRCUITS A 2.25" diameter speaker is provided for user's applications.

USER'S AND EXPERIMENT MANUAL Complete self-learning text with experiments and applications.

OPTIONS (Prices on application) Z80-CTC. EPROM programmer board. Prototyping Board. Z80-PIO. Speech synthesiser board. Audio Cassette. 2K Ram.


KEYBOARD 36 keys including 19 function keys, 16 hex-digit keys and 1 user defined key.



Use the unique Micro-Computer to truly understand the inside workings of microprocessors, or simply use as a Z80A evaluation system.

A 9V, 0.5A adaptor and 350 page manual is provided. Formal orders requiring Acc & 30 days credit. Please ask for price list.

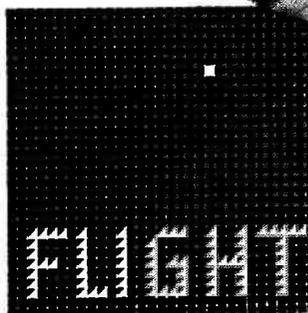New "BASIC" EPROM & Keyboard Overlay £9.95



£69.95 * + p & p


Flight Electronics Ltd. * Mail Order only

MICRO-PROFESSOR is a trade mark of Multitech Industrial Corporation. Z80 is a trade mark of Zilog Inc.

To receive your MICRO-PROFESSOR Complete the coupon today!
Please send me MICRO-PROFESSOR(S) (+ £2.95 p & p)
I enclose cheque/P.O. for £
Name _____
Address _____
Please allow 28 days for delivery
Flight Electronics Ltd. Flight House
Quayside Road, Southampton
Tel: 0703 34003/27721
Telex: 477783
ETI

NEGATIVE ION GENERATOR

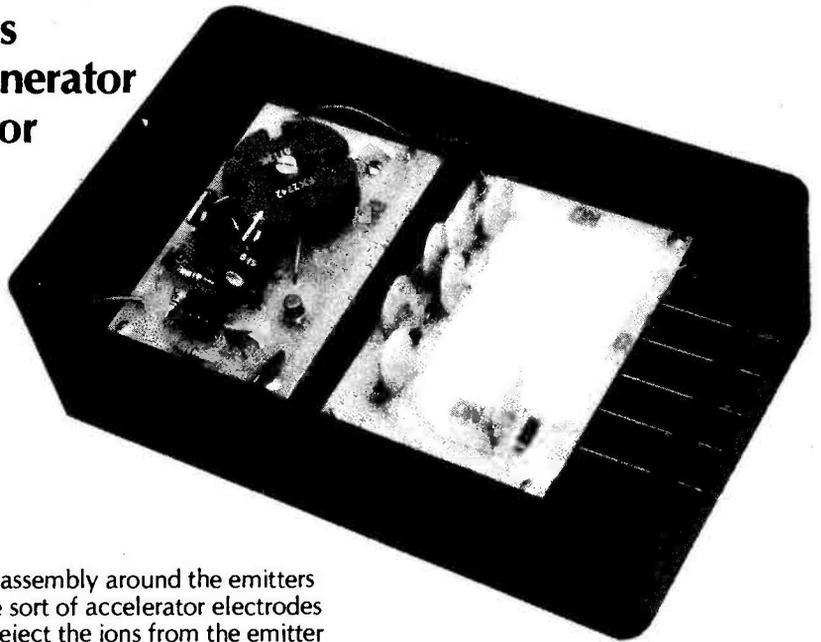For readers who just have to find out for themselves what this subject is all about, this negative ion generator should provide a good basis for experiment. Design by Jonathan Scott. Development by Graeme Teesdale.



The rise in popularity of negative ion generators, the claims made for them, and the attention they have received in newspapers and magazines recently has undoubtedly intrigued many readers with a technical background or interest. As the electronics associated with a negative ion generator is relatively simple, generally employing readily available components, this article describes how to build a unit that can be used as the basis for experiment.

Design Of The Emitter Head

The object of the emitter head is to take in the HT, in our case about 3 kV, and produce a stream of negative ions flowing forwards into the room in which the generator is placed. The ions are produced by a very intense field gradient, which is induced by the high voltage and the geometry of the head assembly. This ion flow is a corona wind.

It is a basic principle of electrostatic physics that the field gradient is stronger in the immediate vicinity of a point projection, the gradient being greater when the point is sharper so most ion generators employ some combination of sharp projections and high voltage.

Pointing The Way

If the points are spaced well away from other parts of the unit the ions will naturally repel themselves away from the region of emission. However, if the point or points are partially enclosed in the case of the device there may need to be either a chimney-

shaped assembly around the emitters or some sort of accelerator electrodes to help eject the ions from the emitter head. We didn't require an accelerator as the points protrude beyond the slot in the case.

Wherever there is ion production there will be ozone production. Ozone is corrosive as well as a strong antibacterial agent, and is poisonous in sufficient concentration. In order to keep it to a minimum, as low a voltage as possible should be used. Our project has been designed to give the lowest voltage compatible with adequate ion production. The design should be such as not to allow any arcing or serious breakdown; this is really only likely if you try using an "accelerator", as there will be no metal in close proximity to the emitter otherwise.

The best metal for the points which is easily obtainable is steel, preferably stainless. This is hard enough to hold an edge and will resist the effects of cathode stripping. The latter is undesirable both because the fine point will be eroded away, and also because the heavy metal ions which are ejected are undesirable agents in the air we breathe (stick to getting your minerals from cornflakes).

There is no shock hazard as the unit is not mains powered and there is a very large series resistance between the points and the multiplier output. At

most, there results something between a nip and a tickle if you touch the emitter points.

Construction

First stage of construction is to assemble the components on the PCBs; commence with the inverter board. Insert the resistors, capacitors, IC and transistors before assembling the transformer to it. As usual, take care with the orientation of the diode, IC1 and the transistors. Next, wind the transformer — details are given in the box. The transformer employs a potcore and this can be held on to the PCB with a nylon bolt — do not use a metal bolt. Cut the transformer coil wires to length, scrape off the insulation and solder them in place. The TIP31C transistors, Q1 and Q2, do not actually require any heatsink, though they do get warm in operation.

The high voltage board may be assembled next. Take care with the orientation of the diodes. Stand the capacitors erect on the board so that they do not touch each other or you may have arc-over problems between these components.

Mount the appropriate components on the 'blinker' board


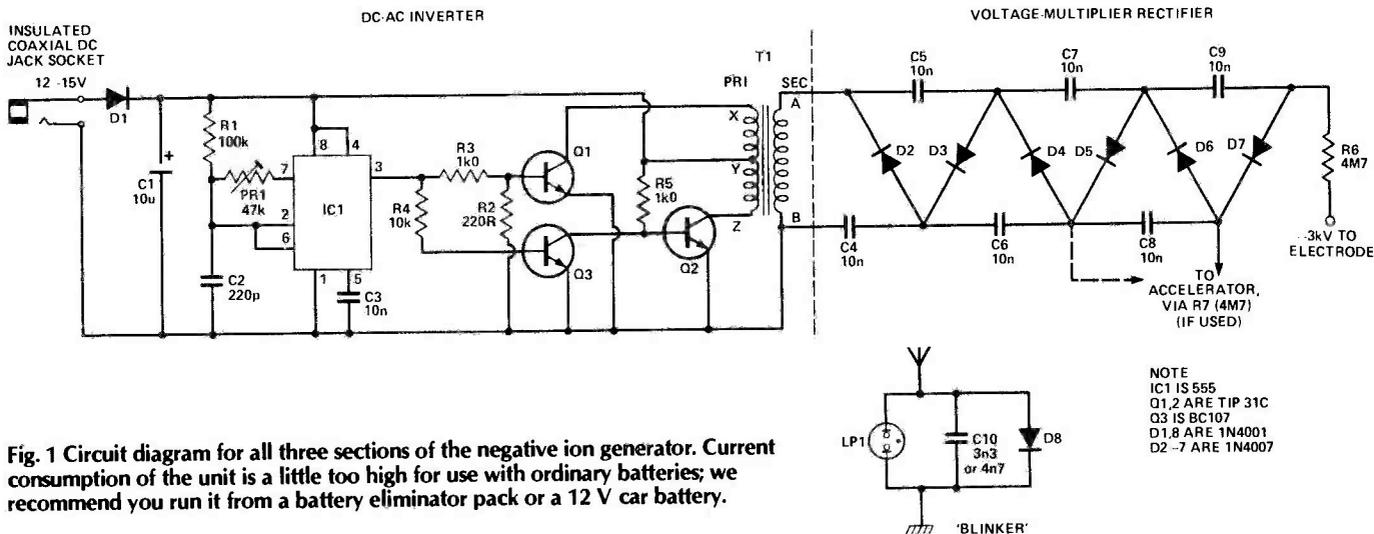


Fig. 1 Circuit diagram for all three sections of the negative ion generator. Current consumption of the unit is a little too high for use with ordinary batteries; we recommend you run it from a battery eliminator pack or a 12 V car battery.

NOTE
 IC1 IS 555
 Q1,2 ARE TIP 31C
 Q3 IS BC107
 D1,8 ARE 1N4001
 D2-7 ARE 1N4007

PARTS LIST

- Resistors (all 1/4 W, 5%)**
- R1 100k
- R2 220R
- R3,5 1k0
- R4 10k
- R6,7 4M7
- Potentiometer**
- PR1 47k miniature vertical preset
- Capacitors**
- C1 10u 16 V tantalum
- C2 220p ceramic
- C3 10n polycarbonate
- C4-9 10n 1 kV ceramic
- C10 3n3 or 4n7 polystyrene or ceramic
- Semiconductors**
- IC1 555
- Q1,2 TIP31C
- Q3 BC107 or BC547
- D1,8 1N4001
- D2-7 1N4007 or similar (1 kV PIV)
- Miscellaneous**
- LP1 wire-ended neon bulb (no series resistor)
- PCBs (see Buylines); potcore and former (FX2242 — see Buylines); coaxial DC jack socket; case (180 x 110 x 55 mm, Vero ref. 75-2861D); five needles.

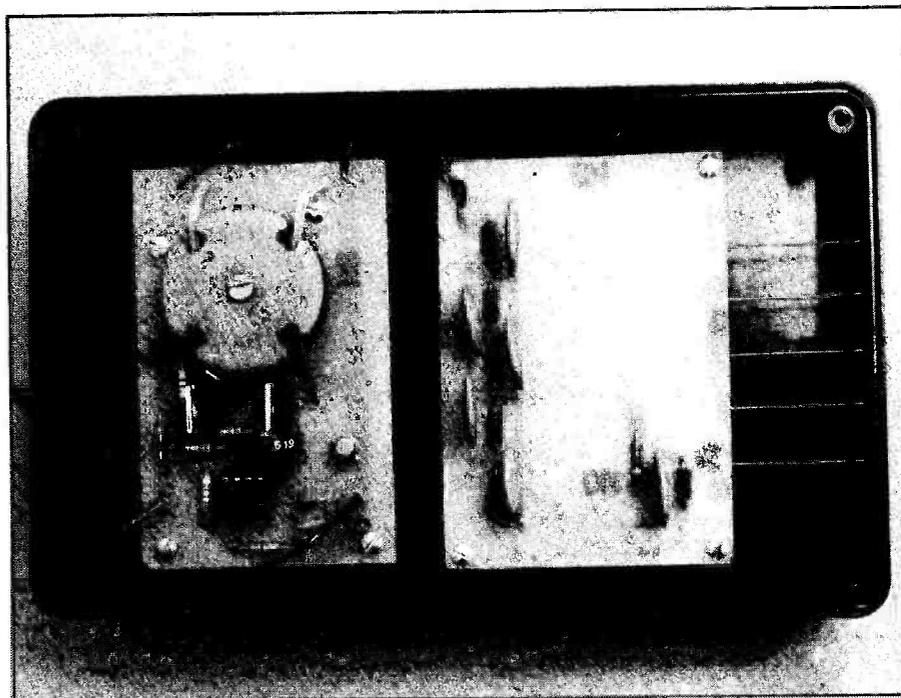

The inverter and high voltage boards mounted side by side in the case, with the emitter needles protruding through the slot in the side of the case.

next, as you'll need this for a testing aid. It is important to watch the diode polarity here. The cathode of the diode goes to the pad marked with the 'ground' symbol. Note that the components are mounted on the copper side.

The emitter points are steel needles soldered directly to the PCB. The easiest method is to tape the needles, parallel and the correct distance apart, so they overhang the end of a wooden block etc. Support the board underneath, and touching, the overhanging needles and solder them in place before removing the tape. Since ions will be ejected from any sharp point we recommend you

cut all the component leads on the high voltage board and then resolder them, using enough extra solder to give rounded solder blobs. (Make sure the same is true of the needle connections). This will prevent unwanted ion leakage.

The DC input socket we mounted on one side of the box. Exactly how the DC coaxial jack socket is wired will depend on how your plug pack output plug is wired. Some have the outer connector connected to positive, while others have it connected to the negative.

Getting It Going

You will need a multimeter and a supply of between 9 V DC and 14 V

DC. Switch the meter to the current range to read 300 mA full scale or more, and connect it in series with the DC supply input. Switch the supply on and, assuming all is well, adjust PR1 on the inverter board for *minimum* current. This could be between about 220-280 mA.

Run the unit for a few minutes, then switch off, discharge the rectifier capacitors and feel Q1 and Q2. One should not be markedly hotter than the other, otherwise you have adjusted PR1 incorrectly or you have a fault — most likely a transistor inserted incorrectly or a dry joint between the output of IC1 (pin 3) and the bases of Q1, Q2, or Q3. Having confirmed everything

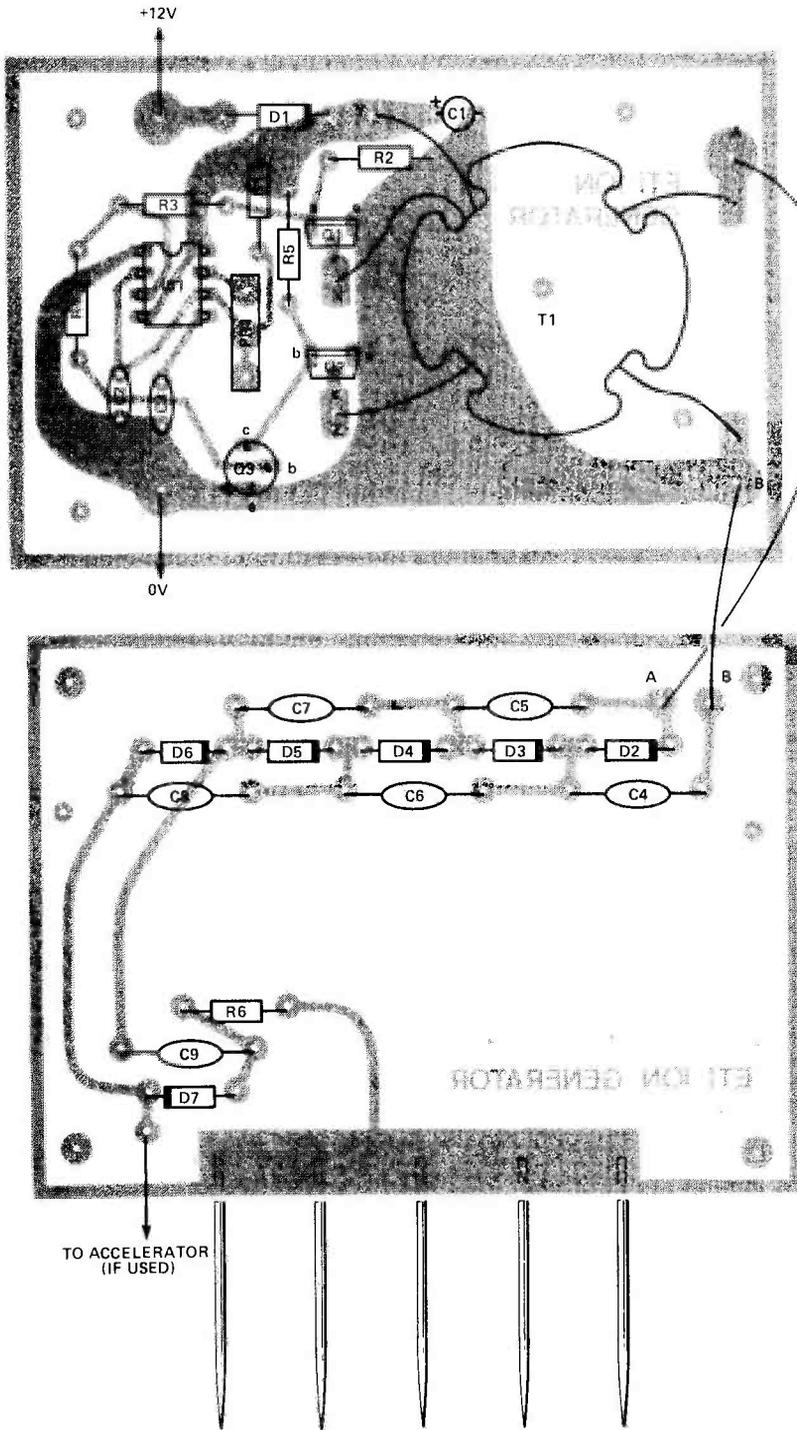


Fig. 2 Component overlay and wiring for the ion generator. The two-board design will allow for different physical layouts and connection pads are provided for experimentation with accelerators and off-board emitters.

works as it should, and having adjusted PR1, assemble it all into the case and you can check its operation with the blinker.

Turn the ioniser on and grasp the blinker so that your thumb is in good contact with the pad marked by the 'ground' symbol. Hold the blinker such that the 'antenna' pad is about 10 mm

in front of the emitter. You should be able to count around one blink per second if all is well and this is a good 'benchmark' for successful operation when you experiment with different head designs and geometries.

Notes On Experimentation

This project shows but one way to

HOW IT WORKS

The DC-to-AC inverter consists of a 555 astable multivibrator, the output of which is used to drive two transistors operated in push-pull. The collectors of Q1 and Q2 switch current through each side of the transformer (T1) primary in turn. Diode D1 prevents any damage from a supply connected with reverse polarity. Capacitor C1 is a bypass. IC1 oscillates at around 25 kHz, determined by R1 and C2. The exact frequency is unimportant. The mark-to-space ratio of the output of IC1 (at pin 3) may be adjusted by PR1, which is connected in series with pin 7 of IC1.

The output of IC1 drives the base of Q1 directly, via R3 and R2. Q1 turns on when the output of IC1 goes high. Resistor R3 is there principally to limit the base current supplied to Q1, while R2 serves to discharge the base emitter junction capacitance so that Q1 turns off quickly when the output of IC1 goes low.

When pin 3 of IC1 goes high, Q3 also turns on, preventing Q2 from turning on. When pin 3 of IC1 goes low, Q1 and Q3 turn off and Q2 will turn on as base bias will be supplied via R5. Thus current is alternatively switched through each side of the primary T1. The secondary provides a voltage step-up of 25:1. If the supply voltage is 12 V DC, then the peak-to-peak output from the secondary of T1 will be 600 V.

The voltage-multiplier rectifier employs the well-known Cockcroft-Walton circuit, where the output of successive half-wave rectifiers is connected in series with the previous one. This circuit provides a multiplication of six times. Thus, with a 12 V DC supply, the output will be about -3.6 kV. With a 10 V DC supply (as can be obtained from a 9 V DC battery eliminator), about -3 kV is obtained. An output for an 'accelerator' is provided.

The high voltage output to the emitter head is taken via a 4M7 resistor to ensure that only low short-circuit current occurs if the emitter head is accidentally contacted or excessively humid air causes 'flashover' from the emitter.

The blinker is simply a crude relaxation oscillator. When a charge builds up on the 'antenna' pad, it will charge C10. When the voltage on C10 reaches the breakdown voltage of LP1 (about 70 V), the neon will conduct. This will discharge the capacitor, the voltage across it falling until it reaches the extinguishing voltage of the neon (about 30-40 V), which will then cease conduction. While the neon conducts, it will emit light, but as it discharges C10 fairly rapidly, all you will see is a brief flash from the neon. Diode D8 ensures only negative charges operate the blinker.


When the neon ceases conduction, the charge on C10 will build up again and the whole process will be repeated.

construct a negative ion generator and the electronics can readily serve as the basis for experimenting with different designs. Higher voltages are unnecessary — and are not usual in commercial designs — and can lead to problems with ozone generation, breakdown, etc. A connection is available on the high voltage board for

supplying an 'accelerator' on an emitter head. It should be connected via a 4M7, ¼ W resistor. The accelerator voltage could be tapped off lower down the rectifier chain if desired — we suggest at the junction of C6 and C8.

The exact value of capacitors C4 to C9 on the high voltage board is not important and may be any value between about 1nF and 22nF or so, but should not be lower than 1nF. The voltage rating of these capacitors should not be less than 1000 V.

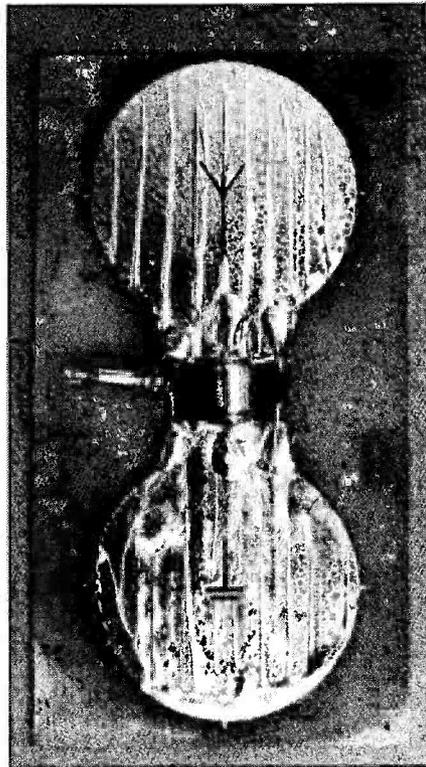The DC supply should not be greater than 15 V or more turns be wound on the secondary of T1, else you may experience insulation breakdown within the transformer.



The assembled blinker, which we tinned with solder to avoid sweaty finger marks and oxidation. The cathode of D8 is at the bottom.

TRANSFORMER WINDING DETAILS

Potcore: FX2242

Secondary: 125 turns of 0.2 mm diameter enamelled copper wire.

Primary: 10 turns, centre-tapped, of 1.0 mm diameter enamelled copper wire.

The secondary is wound on the potcore bobbin first. Wind it in five or six neat layers. Slip thin plastic sleeving over the start and finish leads so that the sleeving is held well inside the bobbin. As you finish winding each layer, insulate it with 1 mm mylar sticky tape (if you can obtain it) or electrical insulation tape (a bit heavy, but it will do the job). Wind the next layer on the insulation of the previous layer, and so on until you finish winding. Wind several layers of insulation over the completed secondary. Leave the start and finish wires protruding from the different sides of the bobbin so that they exit via different slots of the assembled potcore.

Wind the primary over the secondary; it can be wound bifilar (two wires together, five turns, connect finish of one to start of other to provide centre tap) or in one winding — but don't forget the centre tap. Wind the primary so that its wires exit the potcore opposite the secondary wires.

In operation, if you have breakdown problems (arcing sounds inside the potcore) it means you have not wound or insulated your secondary carefully enough and you'll have to rewind the transformer.

BUYLINES

None of the electronic components for this project should cause any supply problems. The FX2242 is stocked by C.T. Electronics (Acton) Ltd. of 267/270 Acton Lane, London W4 5DG. Suitable steel needles can be obtained from your family sewing drawer! Failing that, any sewing accessories supplier can help you. The boards can be obtained from our PCB Service at the prices given on page 82.

ETI

RELAY-A-GUIP 19 RACK MOUNTING CASE

★ Top, bottom and rear cover removable for access ★ Plates have heavy duty grey paint finish ★ Front panel is heavy gauge — 3mm aluminium ★ Strong, screwed, construction throughout — screws included ★ Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from ★ Front panels of brushed aluminium finish enhanced with heavily chromed handles ★

Front Panel 480 x 150 mm
Rear Case 425 x 250 x 140 mm

£23.95
£19.50

TOP QUALITY

Or Free Standing

This is a professional rack mounting cabinet that will allow you to get your equipment off the bench. Rack mounting provides security for your equipment and easy access for maintenance. This Precision rack mounting cabinet has all the features you would expect from a professional unit.

a - 160(d) x 90(h) x 50(w)mm	high impact styrene
b - 196(d) x 113(h) x 60(w)mm	Z-BOX
c - 130(d) x 68(h) x 41(w)mm	natural aluminium lid
d - 83(d) x 54(h) x 28(w)mm	

A - £1.55
B - £2.05
C - £1.10
D - £0.80

FREE!
NEW CATALOGUE

ADD VAT at std rate %
Order value under £5 00
Add 50 p. Pand Pkg

METAL CABINETS

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife!), louvers for ventilation and finished in an attractive two tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.

A	£1.70	£2.12
B	£2.55	£3.20
C	£3.04	£3.80
D	£4.08	£5.00

a - 102(d) x 58(h) x 83(w)mm
b - 150(d) x 61(h) x 103(w)mm
c - 150(d) x 78(h) x 134(w)mm
d - 184(d) x 70(h) x 160(w)mm

RELAY-A-GUIP

POWERSINK

£1.35
£1.70

Available drilled to accept two power transistors of most types including TO-3 TO-126 TO-220 TO-66 Size 75(1) x 102(w) x 25(d)mm Thermal resistance mounting surface to ambient -1°C/Watt (2 Ohm/sec air velocity) Mounting surface temperature rise above ambient 60°C @ 30W heat dissipation

Bridge Rectifier

1amp 50V
W0.005 — 16-5p

SLIDE SWITCHES	
1P2T	0.10
2P2T	0.12
2P3T	0.19
4P2T PCB	0.28
4P3T	0.35
2P2T	0.12
1P4T	0.26
6P3T	0.42

ROCKER 6amp 250VAC	
4P4T PCB	0.45
6P3T ALL KNOB	0.45
1P2T Mom	0.20
ON/OFF	0.24
ON/ON	0.26

EXPORTS & TRADE ENQUIRIES ARE WELCOME.

TELEX 995901 GLOTX-G
Quote ref R7

3amp TOGGLE mini	
250VAC ON/NONE/ON	0.85
250VAC ON/OFF/ON	0.88

SPECIAL OFFER

Relay + Base £2.95
Two for £5.00

Contact details:
185 OHM 5amp at 28 VDC/115 VAC

DIODES

1N4148	— 2p
1N4001	— 3p
1N4002	— 3½p
1N4003	— 4½p
1N4004	— 5p

SEIKO 30w Soldering Iron £2.95

RELAY-A-GUIP PRODUCTS
Moat Lodge, Stock Chase,
Maldon, Essex, U.K. CM9 7AA.
Tel 0621-57242 & 58686 (24hour)

CAMBRIDGE LEARNING SELF-INSTRUCTION COURSES

A PRACTICAL DIGITAL ELECTRONIC KIT FOR ★ LESS THAN £20 ★



**SUITABLE FOR
BEGINNERS**

NO SOLDERING!

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

seven LS TTL integrated circuits, breadboard, LEDs, and all the DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19.90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits. This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

It is supported by our theory course

DIGITAL COMPUTER LOGIC AND ELECTRONICS £8.50 £6.00
for beginners, and our latest, more advanced text,

DIGITAL DESIGN £7.00

Please send for full details (see coupon below).

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 16 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND. TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK

Please send me:

.....SUPERKIT(5) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club Eurocard / Visa / Mastercard / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446 Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, Unit 16 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).

ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range, decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types.

Order using the FREEPOST coupon below.

Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. GUARANTEED 5 YEARS.

TYPE	SERIES No	SECONDARY VOLS	RMS Current	PRICE inc VAT	PRICE ex VAT
30 VA 70 x 30mm 0.45 Kg Regulation 18%	1X010	6 + 6	2.50	£5.28	£4.48
	1X011	9 + 9	1.66	+ 0.870	+ 0.870
	1X012	12 + 12	1.20		
	1X013	15 + 15	0.90		
	1X014	18 + 18	0.83		
	1X015	22 + 22	0.68		
	1X016	25 + 25	0.60		
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2X010	6 + 6	4.16	£5.83	£4.93
	2X011	9 + 9	2.77	+ £1.10	+ £1.10
	2X012	12 + 12	2.08		
	2X013	15 + 15	1.66		
	2X014	18 + 18	1.38		
	2X015	22 + 22	1.13		
	2X016	25 + 25	1.00		
80 VA 90 x 30mm 1 Kg Regulation 12%	3X010	6 + 6	6.64	£6.51	£5.47
	3X011	9 + 9	4.44	+ £1.43	+ £1.43
	3X012	12 + 12	3.28		
	3X013	15 + 15	2.66		
	3X014	18 + 18	2.22		
	3X015	22 + 22	1.81		
	3X016	25 + 25	1.60		
120 VA 90 x 40mm 1.2 Kg Regulation 11%	4X010	6 + 6	10.00	£7.55	£6.38
	4X011	9 + 9	6.66	+ £1.43	+ £1.43
	4X012	12 + 12	5.00		
	4X013	15 + 15	4.00		
	4X014	18 + 18	3.33		
	4X015	22 + 22	2.77		
	4X016	25 + 25	2.40		
160 VA 110 x 40mm 1.8 Kg Regulation 8%	5X011	9 + 9	8.89	£9.92	£8.44
	5X012	12 + 12	6.66	+ £1.43	+ £1.43
	5X013	15 + 15	5.33		
	5X014	18 + 18	4.44		
	5X015	22 + 22	3.63		
	5X016	25 + 25	3.20		
	5X017	30 + 30	2.66		
240 VA 140 x 60mm 4 Kg Regulation 4%	6X016	25 + 25	10.00	£11.41	£9.52
	6X017	30 + 30	8.33	+ £2.05	+ £2.05
	6X018	35 + 35	7.14		
	6X019	40 + 40	6.25		
	6X020	45 + 45	5.56		
	6X021	50 + 50	5.00		
	6X022	55 + 55	4.55		
525 VA 140 x 75mm Regulation 4%	8X016	25 + 25	10.00	£18.17	£15.53
	8X017	30 + 30	8.33	+ £2.05	+ £2.05
	8X018	35 + 35	7.14		
	8X019	40 + 40	6.25		
	8X020	45 + 45	5.56		
	8X021	50 + 50	5.00		
	8X022	55 + 55	4.54		
525 VA 140 x 75mm Regulation 4%	9X017	30 + 30	10.41	£25.10	£21.54
	9X018	35 + 35	8.92	+ £2.20	+ £2.20
	9X019	40 + 40	7.81		
	9X020	45 + 45	6.94		
	9X021	50 + 50	6.25		
	9X022	55 + 55	5.68		
	9X023	110	5.88		
9X029	220	2.84			
9X030	240	2.60			

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain full load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovaive, Maplin, Marshalls, Technomatic and Watford Electronics

Please send me the following
ILP modules

Total purchase price

I enclose Cheque

Postal Orders

Int. Money Order

Please debit my Access/Barclaycard No.


Name

Address

Signature

ET 6/6

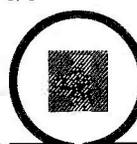
Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778; Technical (0227) 64723 Telex 965780.




ILP
TRANSFORMERS
(a division of
ILP Electronics Ltd)

STAY AHEAD. STAY WITH US


THE CASE FOR

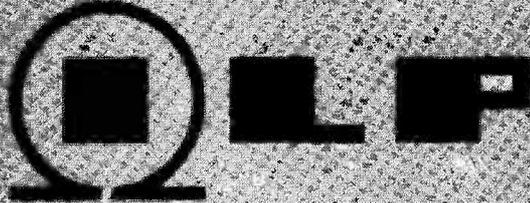

It's the chance every constructor wants

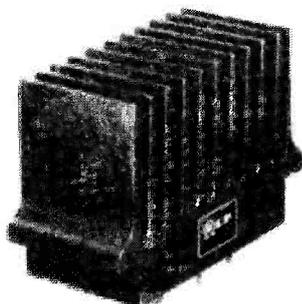

POWER AMPS

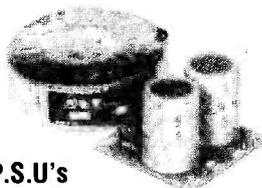

P.S.U.'s



PRE-AMP MODULES

It's something you have always wanted....something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. **ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN.** It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



FREEPOST 4
 GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
 Telephone Sales (0227) 54778 **Technical Only** (0227) 64723 Telex 965780
FREEPOST
 Mark your envelope clearly **FREEPOST 4** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

Did you know

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are **TWENTY** power amplifiers from 15 to 240 watts RMS including the very latest super-quality models to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.C., I.B.A., N.A.S.A., British Aerospace, General, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?

SEND COUPON
 (NO STAMP NECESSARY)
FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE

To: I.L.P. ELECTRONICS LTD.
 PLEASE SEND ME I.L.P. CATALOGUE,
 POST PAID BY RETURN

Name: _____
 Address: _____

I HAVE/HAVE NOT PREVIOUSLY BUILT WITH I.L.P. MODULES

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

TECH TIPS


Surgeless 555 Clock

H.B. Broughton, Bishop's Stortford

The CMOS version of the 555 has two major advantages over the bipolar type: a) it is a micropower device; b) it is largely free of the supply current surges generated by an ordinary 555 every time its output changes state. This is important because the surge can upset other circuits powered from the same supply, but the problem can be avoided by using the rather unusual configuration shown, saving 60p an oscillator over the CMOS answer to this difficulty!

Experiment has shown that the supply surge (typically 300 mA by 100 ns) is roughly halved by using pin 3 (OUTPUT) of the 555 to charge/discharge the capacitor rather than pin 7 (DISCHARGE) and a resistor to V+. It is reduced to less than 25% of its typical size by using pin 3 and wiring the capacitor to V+, and is then small enough to be removed by a 100nF capacitor between the supply rails.

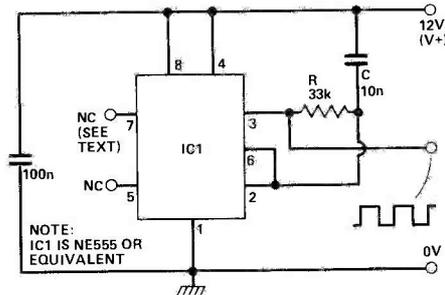This gives the circuit shown, a 'surgeless' clock with frequency $f = 6RC$



(R in ohms, C in microfarads), mark/space ratio of typically 3:2, and voltage swing of 1 to 11 V. These figures were found using a load impedance of 330k; the frequency is affected if load impedance is less than about $10 \times R$, but if low impedances are to be driven, pin 7 can be used and the load wired from pin 7 to power: alternatively, a 1k5 resistor can be taken from pin 7 to power and the load put between pin 7 and ground, though this reduces the available voltage swing at pin 7.


With the component values shown, this clock runs at 2 kHz and produces a nice clean square wave with low rise times.

Stylophone With Memory


J.R. Walker, Norwich

This single-octave 'stylophone' can store and play back over a minute of music (two in 'slow' mode). The keyboard was constructed by pushing drawing pins into a plastic box on to which a C to C keyboard was drawn. The drawing pins are numbered one to twelve; this is just the order in which they are scanned and it doesn't matter what notes they actually are, since they are manually tuned by the presets PR1-12. LED1 indicates that no more memory is left, while SW2 allows you to stop in the middle of playback/record without affecting the tune. The unit is automatically reset when switching from play to record, and by leaving it on reset you can play tunes without affecting the one in memory. Like magnetic tape, recording completely wipes out what was previously recorded. To obtain the best results, record in 'slow' and play back in 'fast', since one finger playing is not a speedy operation!

In 'fast' mode IC6 oscillates at about

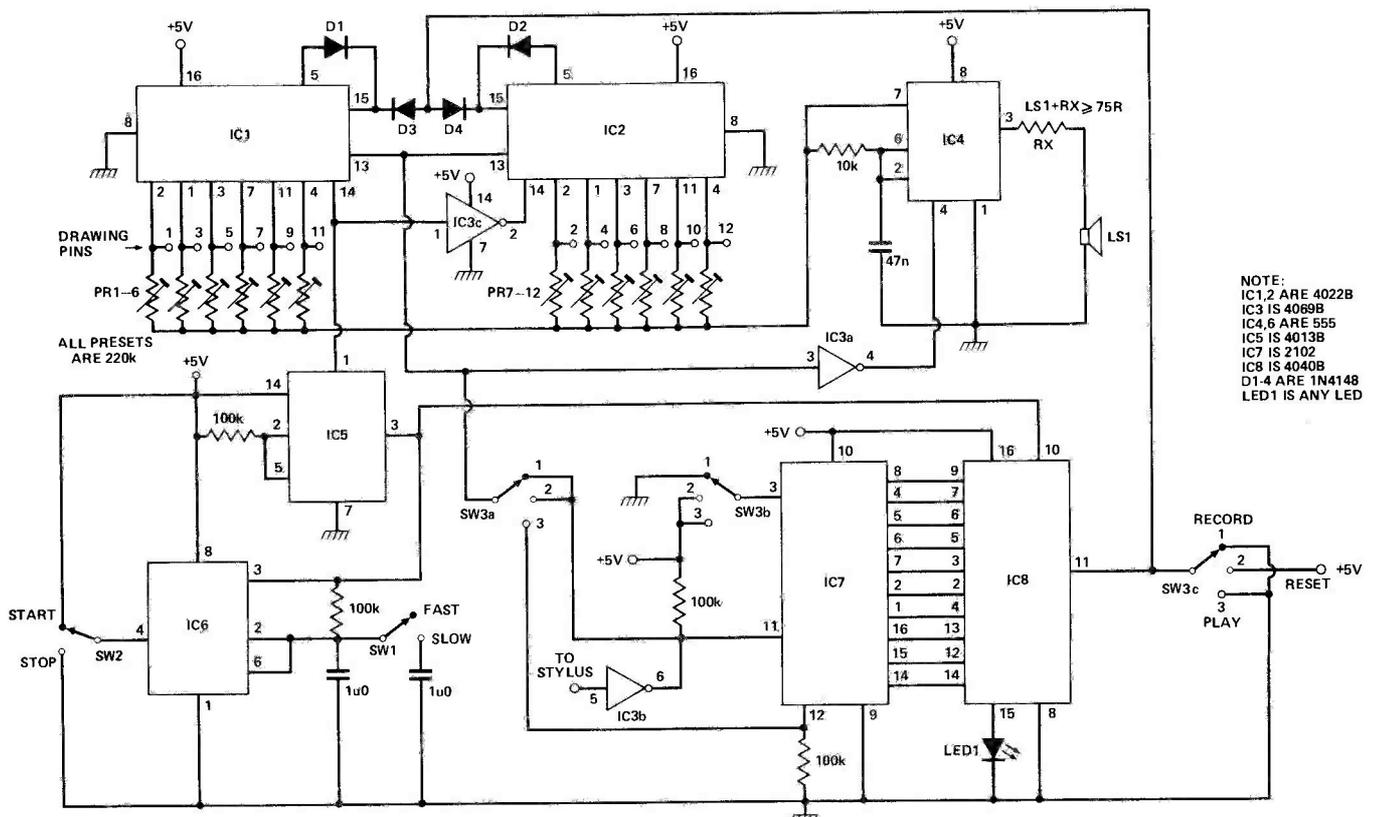

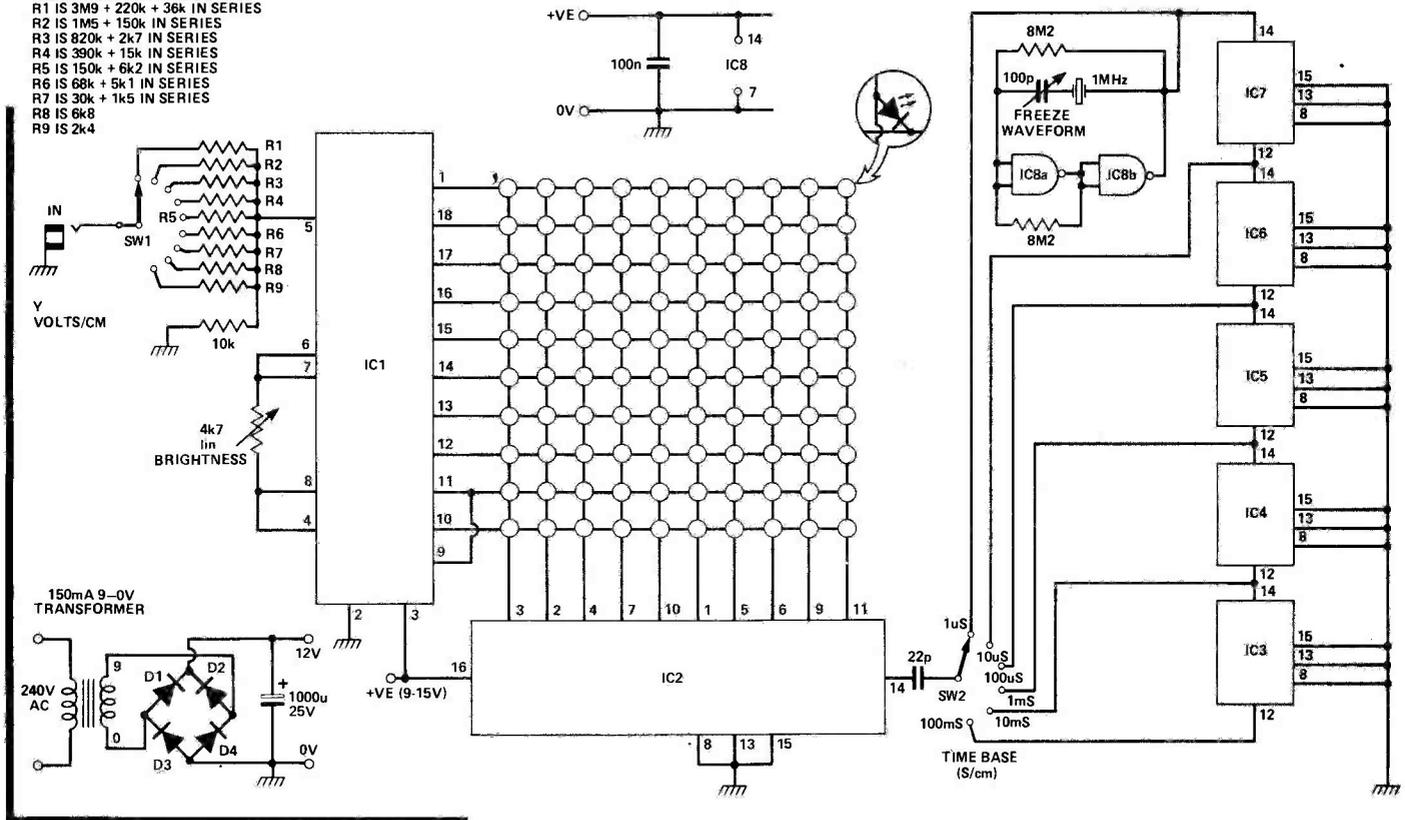NOTE:
 IC1 IS LM3914
 IC2-7 ARE 4017B
 IC8 IS 4011B
 D1-4 ARE 1N4001
 LEDs ARE STANDARD 0.2" RED
 R1 IS 3M9 + 220k + 36k IN SERIES
 R2 IS 1M5 + 150k IN SERIES
 R3 IS 820k + 2k7 IN SERIES
 R4 IS 390k + 15k IN SERIES
 R5 IS 150k + 6k2 IN SERIES
 R6 IS 68k + 5k1 IN SERIES
 R7 IS 30k + 1k5 IN SERIES
 R8 IS 6k8
 R9 IS 2k4



10 Hz, causing IC1 and IC2 to scan the keyboard (each one clocks on by one alternately). IC4 is held off by IC3a. If the stylus is placed on one of the drawing pins, nothing will happen until the counters get to that pin. At this point they stop and IC4 turns on, producing a note. The pitch of the note depends on which preset is driving pin 7 of IC4. The note stays on until the probe is removed from the pin, whereupon everything carries on as before.

With each pulse of IC6, IC7 clocks on once, counting from 1 to 1024 in the memory. IC8 remembers if a note was played at that point. On playback all counters are reset and IC8 plays back the tune, taking 1024/10 or over 100 seconds to do so. Slow mode takes roughly twice as long.

The power rail (5 V at 200 mA) should be well smoothed (say 1000uF-3300uF) to preserve the memory if the supply flickers (memory is lost on power-down). Although the circuit doesn't draw anything like 200 mA the capacity to deliver this current is important as IC4 and IC6 can draw heavily on the power rails.

Solid State Scope Using LEDs

G. Durant, Selby

This 'scope' is completely solid state, with the absence of the cathode ray tube. The tube is replaced by a 10 by 10 matrix of LEDs which provide a smaller, more robust substitute. The Y input is connected via a series resistor to IC1, an LM3914 which is an LED bargraph driver. The IC is used in the dot mode and therefore, if a waveform is applied to the Y input, a single 'dot' will appear to move up and down with the voltage from the wave. Input sensitivity is adjusted via SW1, which brings different series resistors into circuit. The resistors are odd values and are made up by placing two or three in series. If 1% resistors are used, an accuracy of about 0.25% can be achieved.

The LEDs must be spaced 1 cm apart, both on the X and Y axis. The use of an LED matrix screen means that the scope can be very thin — in fact pocket-size. Also, an LED screen does not need

very high voltages to work it, so batteries could be used. The only problem is that at high frequencies the resolution is not as good as it could be, although the scope can be used nevertheless at frequencies up to 1 MHz.

The time base uses a crystal-controlled CMOS clock running at 1 MHz. This is broken down into lower frequencies by a string of divide-by-10 chips, in this case 4017s. These frequencies go to a six-way selector switch which selects the timebase frequency. The time base is variable from 100 ms right down to 1 uS in steps of 10. A 100pF variable capacitor, marked 'freeze waveform' is used to fine-tune the main oscillator, so the waveform can be frozen.

A suitable power supply is also shown, but any supply may be used with an output voltage of about 12 V (not more than 15 V). Even a 9 V battery could be used (eg PP9) as, in theory, only one LED is on at a time.

The scope can be expanded to use more LEDs, or to have a trigger device. For the beginner, however, the scope shown would be sophisticated enough to be of great service.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot accept liability for any damage caused by the use of the circuits or ideas submitted by readers for this page. All items sent should be clearly marked 'Tech-Tips'. Drawings should be as clear as possible and the text should be typed. Text and drawings must be original and should be clearly marked 'Tech-Tips'. Circuits must not be subject to copyright. Items for consideration should be sent to ETI Tech-Tips, 145 Charing Cross Road, London WC2R 3EL.

QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

AUDAX HI-FI - SPECIAL PURCHASES


- HD20B25H4C 8" Bass mid range Bextrene cone. 40/60 watt systems £9.95
- HD24S452C 10" high performance bass. Foam suspension. 60/80 watt systems £12.95
- HO13B25H4C 5 1/4" bass mid range Bextrene cone. 40/60 watt systems Heavy magnet. £6.95
- HO13B25J Smaller magnet version. £5.95
- HIF2QJSMC 8" bass mid range foam surround. "square" silver front 30/50 watt system. £8.95
- HIF2QESM 8" bass mid range. For 30/50 watt systems roll surround treated cone. 4 ohm £6.95 8 ohm £7.95
- HIF87BSMQ 4" closed back mid range for 30/50 watt systems £5.50
- HO100D25HR 1" dome tweeter. 4" frame for 60/80 watt systems £5.95



All models for 8 ohms unless stated. (UK Post etc. Speakers 70p tweeters and mid range 50p)

TV SOUND FROM YOUR HI-FI (Mk III)

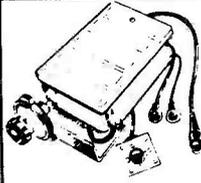High quality TV sound converter, plugs into aerial socket of your FM tuner 9 volt battery operated (battery not supplied). Nothing to look at... but just listen! Covers all U.K. UHF Channels.



*Fitted slow-motion drive (Mk III) £11.50
Four button push-button version £14.50 c/p 65p. (UK Post etc. 65p)
On Demonstration for callers to 301 Edgware Road.

PIEZO TWEETERS

Clean sound. Very low distortion tweeters. No crossover required.

Suitable up to 100 watts - more in series

1 Mid-range horn for disc/plays

2 Tweeter horn for hi-fi/discs/plays

3 Popular hi-fi and disco

4 Flat type hi-fi

5 Round version of No 3

6 Boazd free standing hi-fi piezo

UK Post Free

- 1025A £6.90
- 1018A £5.45
- 1005A £4.35
- 1038A £3.45
- 1038A £4.35
- 1057A £8.95

On Demonstration to callers

ORDER BY POST (OR PHONE) OR CALL IN

ALL PRICES INCLUDE VAT



Cubegate Limited

AUDIO ELECTRONICS

301 Edgware Rd. London W2 1BN

Tel: 01-724 3564

Also at Henrys Radio 404 Edgware Rd. W2

FREE Catalogue send large 20p SAE

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p EACH
POSTAGE 15p PER PACK

BUY SIX PACKS AND GET A SEVENTH PACK FREE!

- MN2. 200 1/4 & 1/2-watt Resistors
- MN3. 100 1 & 2-watt Resistors
- MN4. 50 Wirewound Resistors
- MN5. 100 metal oxide Resistors 1%, 2% and 5%
- MN6. 12 asstd potentiometers
- MN7. 25 asstd. skeleton pre-set Resistors
- MN8. 50 asstd Electrolytic Capacitors.
- MN9. 100 asstd Ceramic Capacitors. Ptte, disc, tub and monolithic etc.
- MN10. 100 mixed capacitors Polyester, Polystyrene, Metallised, Radial and Axial types.
- MN11. 20 asstd Silver Mica Capacitors.
- MN12. 8 Tantalum Bead Capacitors (useful values)
- MN13. 20 asstd Transistors BC, 2N Series + Power etc.
- MN14. 40 IN4148 Diodes
- MN16. 20 min. wire-ended Neons
- MN17. 2 12-volt Relays Ex nearly new equip.
- MN18. 3 Encapsulated Reed Relays. 9-12v. coil, d-pole and t-pole
- MN19. 2 24-volt Relays Ex nearly new equip
- MN20. 1 240-110 to 12-volt. 100ma Transformer
- MN21. 1 240-110 to 24-volt 100ma Transformer
- MN22. 8 2" Led s with clips. 4 red. 2 yellow. 2 green
- MN23. 300 asstd screws, nuts, washers, self-tappers etc.
- MN24. 100 asstd small springs
- MN27. 200 items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.

- MN29. 75mts equipment wire, asstd colours and sizes
- MN31. 12 asstd trimmer capacitors. compression film. Air spaced etc.
- MN32. 15 30pF Beehive trimmers
- MN33. 20 coil formers, ceramic, plastic, reed relay etc.
- MN34. 25 min. glass reed switch
- MN35. 10 asstd switches, toggle, slide, micro etc.
- MN37. 10 asstd audio connectors Din phone etc.
- MN38. 1 PCB with triac control IC data etc.
- MN39. 1 oscillator PCB loads of components (no data)
- MN40. 50 Polystyrene capacitors.
- MN41. 12 BC549C (Plastic BC109C) Transistors
- MN42. 10 BC107 Transistors.
- MN43. 10 BC108 Transistors.
- MN44. 10 Screwfix S.P.C.O min. slide switches.
- MN51. 10 x 0.2" Red LEDs.
- MN52. 20 x 0.1 MFD 25V Ceramic disc capacitors
- MN54. 20 x 0.01 MFD 25V Ceramic disc capacitors
- MN56. 10 14 pin low profile IC skt. DIL
- MN57. 10 16 pin low profile IC skt. DIL
- MN58. 2xCA723 Voltage Regulator
- MN59. 3 places of Verdo board. Useful sizes. Min total 35 sq inch
- MN62. 10 x 0.125" Red LEDs.
- MN63. 50 mixed polyester caps. C280 Siemens etc.
- MN64. 5 Press to make min. switches.
- MN69. 4 min push to break switch

CHORDGATE LTD. Dept. A

75 FARINGDON ROAD, SWINDON, WILTS
TEL: SWINDON (0793) 33877

RETAIL SHOP AT ABOVE ADDRESS! SCHOOLS, COLLEGES, OFFICIAL ORDERS WELCOME

PLEASE QUOTE NO. OF PACKS WHEN ORDERING

SPECIAL OFFER

2114L-450	1-24	25-99
2114L-200	90p	95p
2716 (+5V)	225p	210p
2532	459p	
2732	450p	400p
4116-200	450p	400p
6116-150	90p	85p
	550p	500p

CONNECTOR SYSTEMS

I.D. CONNECTORS		D-CONNECTORS		DIL HEADER PLUGS		RIBBON CABLE (Grey)	
No. of wires	Plug	Header Recept. tabs	Edge Conn.	9 way	15 way	25 way	37 way
10	90p	30p	200p	MALE		10 way	60p
20	165p	165p	240p	Solder	95p	14 way	80p
26	200p	200p	300p	Angled	180p	16 way	90p
34	240p	240p	380p	FEMALE		20 way	105p
40	270p	270p	550p	Solder	125p	28 way	140p
50	310p	310p	600p	Angled	175p	34 way	170p
				Hood	190p	40 way	285p
				37 way Centronix Type Plug	190p	50 way	330p
					£6.50	64 way	370p

JUMPER LEADS

24" Ribbon Cable with headers	
1 end	145p
2 ends	210p
24" Ribbon Cable with sockets	
20 pin	26 pin
34 pin	40 pin
1 end	180p
2 ends	280p
24" Ribbon Cable with D Conn.	
25 way Male 550p	Female 550p

EDGE CONNECTORS

0.1" 0.156"	
2 x 16 way	150p
2 x 22 way	310p
2 x 23 way	170p
2 x 25 way	350p
1 - 43 way	290p
2 - 43 way	450p
2 - 50 way	400p
1 x 77 way	700p
S100 Conn.	800p

EURO CONNECTORS

(Indirect Edge Conn.)	
DIN STD	Plug
41617 21 way	180p
41617 31 way	200p
41617 2 x 32 way	300p
41617 3 x 32 way	350p
41617 3 x 32 way	370p
41617 3 x 32 way	450p
2 x 32 way IDC A + C	475p
(for 2 x 32 way specify a + b or a + d)	

BOOKS (NO VAT) (p & p 50p/book)

Prog. the 6502	£10.75	Motorola Micro Comp HB	£7.00	Sinclair Prog./Reel App.	£6.95
6502 Applications	£15.50	8080 Micro HB	£5.90	50 Rip Roving Games	£4.95
Prog. 5 Interfacing 6502	£18.50	Getting Acquainted ZX81	£4.95	ZX81 Pocket Book	£5.95
6502 Assy, Lang, Prog.	£12.10	Hints & Tips ZX81	£4.25	Atom Business	£7.95
Prog. the Z80	£11.95	Mastering M/C Code ZX81	£5.95	Atom Magic Book	£5.95
Z80 Master Data Book	£6.50	M/C Lang. Made Simple ZX81	£8.95	Getting Acquainted ATOM	£7.95
				Prog on BBC Micro	£5.95

ACORN ATOM

Basic Built 8K + 2K £135 Expanded 12K + 12K £180
(p&p £3 per unit) (expanded unit includes F.P.From)
ATOM PSU £7.00 (£1.20 p&p) 3A5V Regulated PSU £22 (p&p £2)
F.P.ROM £20 1K RAM (2 x 2114L) £2 Tool Box ROM £25
New colour card £32

ATOM SOUND BOARD: Kit comprises of a PSG, VIA and a 2K ROM with demo program and connectors. The board can be plugged into the ATOM Bus to provide parallel and serial output ports and audio output to mini speaker or hi-fi amplifier
Complete Kit £35

ATOM VISION: See April/May PE for project details. Interesting experiments with computer measurements and tracking. Complete kit £46 Software Cassette/demonstration £46

Full range of software available ex stock
Send for our detailed ATOM LIST

SPECIAL OFFER: ACORN INTRODUCTORY PACKAGE £10 (including interactive teaching, financial planning, household and games pack)

PRINTERS

SEIKOSHA GP100A dot matrix printer, full graphics, double width characters up to 10" paper width, self testing.
£199 + Carriage

EPSON MX80 F/T 9x9 Matrix Printer. 80 CPS bidirectional with logic seeking condensed, emphasised and enlarged characters or full graphics

MX 80 F/T1 £350
MX80F/T2 £350 + Carr
BMC 12" Green Screen, 18 MHz bandwidth £149

SOFTY II

The complete microcompressor development system for both Engineers and Hobbyists. You can develop programs, debug, verify and commit them to EPROMs. Will accept most +5V EPROMs. Can also be used as a ROMULATOR. Full review in September '81 P.E. Built unit complete with PSU and TV lead £169.

16K DRAM CARD

Low CBT Memory expansion system for 6502, 280 and 8085 based microcomputers. Kit complete with PCB, all ICs and sockets (Excluding Rs and Cs) £26.00

BBC MICRO MEMORIES CONNECTORS NOW AVAILABLE

74 SERIES	74285	200p	74LS374	70	4076	60p	LM394CH	30p	SP8515	750p	
7400	11p	74286	100p	74LS375	50p	4077	26p	LM709	30p	TA7210	160p
7401	12p	74287	100p	74LS376	70p	4078	20p	LM710	50p	TA7204	200p
7402	12p	74288	100p	74LS377	60p	4079	16p	LM711	70p	TA7205	90p
7403	12p	74365	40p	74LS390	55p	4082	16p	LM733	70p	TA7222	160p
7404	12p	74366	40p	74LS393	50p	4086	72p	LM747	18p	TA7310	160p
7405	18p	74367	40p	74LS395	190p	4089	150p	LM748	35p	TA7431	160p
7406	25p	74368	60p	74LS400	200p	4093	200p	LM748	35p	TBA611AX	275p
7407	25p	74369	100p	74LS444	110p	4094	150p	LM1871	450p	TBA641BX1	275p
7408	14p	74393	100p	74LS540	135p	4095	95p	LM1872	450p	TBA651	300p
7409	15p	74490	120p	74LS541	135p	4096	95p	LM1886	700p	TBA651	300p
7410	15p	74LS SERIES		74LS540	200p	4097	340p	LM1889	350p	TBA800	90p
7411	20p	74LS00	11p	74LS541	200p	4098	90p	LM193	200p	TBA810	100p
7412	20p	74LS01	12p	74LS542	200p	4099	90p	LM302	90p	TBA820	90p
7413	22p	74LS02	12p	74LS543	200p	4099	20p	LM3900	50p	TBA920	200p
7414	22p	74LS03	12p	74LS544	250p	4099	20p	LM3909	95p	TBA950	225p
7415	25p	74LS04	12p	74LS545	250p	4503	50p	LM3911	130p	TC9109	900p
7416	25p	74LS05	12p	74LS546	200p			LM3914	210p	TC9120	350p
7417	25p	74LS08	45p	74LS562	170p	4504	75p	LM3915	225p	TC9A20	350p
7420	16p	74LS09	45p	74LS562	400p	4506	35p	LM3916	225p	TC9A40	175p
7421	20p	74LS10	15p	74LS564	400p	4507	40p	LM3918	110p	TD1004A	300p
7422	20p	74LS11	15p	74LS564	400p	4507	40p	LM1360	110p	TD1008	320p
7423	22p	74LS12	15p	74LS568	400p	4510	85p	M51513L	300p	TD1010	225p
7424	22p	74LS13	15p			4510	85p	M51516L	300p	TD1010	225p
7426	20p	74LS14	25p	74S SERIES		4511	50p	MB3712	150p	TD1022	520p
7427	26p	74LS14	25p	74S00	60p	4512	65p	MC1310P	200p	TD1024	120p
7428	28p	74LS15	30p	74S02	60p	4514	150p	MC1488	40p	TD1034B	250p
7429	18p	74LS20	15p	74S04	60p	4515	150p	MC1495L	350p	TD1110	200p
7430	25p	74LS21	15p	74S05	75p	4516	75p	MC1496	70p	TD1200/235p	
7431	27p	74LS22	15p	74S08	75p	4518	50p	MC3340P	120p	TD2020	320p
7432	27p	74LS23	15p	74S10	60p	4520	70p	MC3401	90p	TL071/81	25p
7433	27p	74LS24	15p	74S12	60p	4521	150p	MC3403	70p	TL072/82	45p
7434	27p	74LS25	15p	74S13	60p	4526	75p	MC3407	60p	TL074	100p
7435	27p	74LS26	15p	74S14	60p	4527	90p	MC3430	90p	TL084	90p
7436	27p	74LS27	15p	74S15	60p	4528	200p	MC5038	75p	TL094	200p
7437	27p	74LS28	15p	74S16	60p	4532	90p	ML920	50p	TL170	50p
7438	27p	74LS29	15p	74S17	60p	4532	90p	MM57160	620p	TL170	50p
7439	27p	74LS30	15p	74S18	60p	4534	500p	MM6221A	600p	TL430C	70p
7440	27p	74LS31	15p	74S19	60p	4534	500p	NE531	150p	UA2240	300p
7441	27p	74LS32	15p	74S20	60p	4538	120p	NE555	150p	UA2240	300p
7442	27p	74LS33	15p	74S21	60p	4539	120p	NE556	150p	UA2240	300p
7443	27p	74LS34	15p	74S22	60p	4543	100p	NE557	150p	UA2240	300p
7444	27p	74LS35	15p	74S23	60p	4543	100p	NE558	150p	UA2240	300p
7445	27p	74LS36	15p	74S24	60p	4543	100p	NE559	150p	UA2240	300p
7446A	60p	74LS37	15p	74S25	60p	4543	100p	NE560	150p	UA2240	300p
7447A	45p	74LS38	15p	74S26	60p	4543	100p	NE561	150p	UA2240	300p
7448	45p	74LS39	15p	74S27	60p	4543	100p	NE562	150p	UA2240	300p
7449	45p	74LS40	15p	74S28	60p	4543	100p	NE563	150p	UA2240	300p
7450	17p	74LS41	75p	74S29	60p	4543	100p	NE564	150p	UA2240	300p
7451	17p	74LS42	75p	74S30	60p	4543	100p	NE565	150p	UA2240	300p
7452	17p	74LS43	75p	74S31	60p	4543	100p	NE566	150p	UA2240	300p
7453	17p	74LS44	75p	74S32	180p	4543	100p	NE567	150p	UA2240	300p
7454	17p	74LS45	75p	74S33	180p	4543	100p	NE568	150p	UA2240	300p
7455	17p	74LS46	75p	74S34	180p	4543	100p	NE569	150p	UA2240	300p
7456	17p	74LS47	75p	74S35	180p	4543	100p	NE570	150p	UA2240	300p
7457	17p	74LS48	75p	74S36	180p	4543	100p	NE571	150p	UA2240	300p
7458	17p	74LS49	75p	74S37	180p	4543	100p	NE572	150p	UA2240	300p
7459	210p	74LS50	30p	74S38	225p	4543	100p	NE573	150p	UA2240	300p
7460	210p	74LS51	30p	74S39	225p	4543	100p	NE574	150p	UA2240	300p
7461	210p	74LS52	30p	74S40	225p	4543	100p	NE575	150p	UA2240	300p
7462	210p	74LS53	30p	74S41	225p	4543	100p	NE576	150p	UA2240	300p
7463	210p	74LS54	30p	74S42	225p	4543	100p	NE577	150p	UA2240	300p
7464	210p	74LS55	30p	74S43	225p	4543	100p	NE578	150p	UA2240	300p
7465	210p	74LS56	30p	74S44	225p	4543	100p	NE579	150p	UA2240	300p
7466	210p	74LS57	30p	74S45	225p	4543	100p	NE580	150p	UA2240	300p
7467	210p	74LS58	30p	74S46	225p	4543	100p	NE581	150p	UA2240	300p
7468	210p	74LS59	30p	74S47	225p	4543	100p	NE582	150p	UA2240	300p
7469	210p	74LS60	30p	74S48	225p	4543	100p	NE583	150p	UA2240	300p
7470	210p	74LS61	30p	74S49	225p	4543	100p	NE584	150p	UA2240	300p
7471	210p	74LS62	30p	74S50	225p	4543	100p	NE585	150p	UA2240	300p
7472	210p	74LS63	30p	74S51	225p	4543	100p	NE586	150p	UA2240	300p
7473	210p	74LS64	30p	74S52	225p	4543	100p	NE587	150p	UA2240	300p
7474	210p	74LS65	30p	74S53	225p	4543	100p	NE588	150p	UA2240	300p
7475	210p	74LS66	30p	74S54	225p	4543	100p	NE589	150p	UA2240	300p
7476	210p	74LS67	30p	74S55	225p	4543	100p	NE590	150p	UA2240	300p
7477	210p	74LS68	30p	74S56	225p	4543	100p	NE591	150p	UA2240	300p
7478	210p	74LS69	30p	74S57	225p	4543	100p	NE592	150p	UA2240	300p
7479	210p	74LS70	30p	74S58	225p	4543	100p	NE593	150p	UA2240	300p
7480	210p	74LS71	30p	74S59	225p	4543	100p	NE594	150p	UA2240	300p
7481	210p	74LS72	30p	74S60	225p	4543	100p	NE595	150p	UA2240	300p
7482	210p	74LS73	30p	74S61	225p	4543	100p	NE596	150p	UA2240	300p
7483	210p	74LS74	30p	74S62	225p	4543	100p	NE597	150p	UA2240	300p
7484	210p	74LS75	30p	74S63	225p	4543	100p	NE598	150p	UA2240	300p
7485	210p	74LS76	30p	74S64	225p	4543	100p	NE599	150p	UA2240	300p
7486	210p	74LS77	30p	74S65	225p	4543	100p	NE600	150p	UA2240	300p
7487	210p	74LS78	30p	74S66	225p	4543	100p	NE601	150p	UA2240	300p
7488	210p	74LS79	30p	74S67	225p	4543	100p	NE602	150p	UA2240	300p
7489	210p	74LS80	30p	74S68	225p	4543	100p	NE603	150p	UA2240	300p
7490A	210p	74LS81	30p	74S69	225p	4543	100p	NE604	150p	UA2240	300p
7491	210p	74LS82	30p	74S70	225p	4543	100p	NE605	150p	UA2240	300p
7492A	30p	74LS83	30p	74S71	225p	4543	100p	NE606	150p	UA2240	300p
7493A	30p	74LS84	30p	74S72	225p	4543	100p	NE607	150p	UA2240	300p
7494	30p	74LS85	30p	74S73	225p	4543	100p	NE608	150p	UA2240	300p
7495A	40p	74LS86	30p	74S74	225p	4543	100p	NE609	150p	UA2240	300p
7496	40p	74LS87	30p	74S75	225p	4543	100p	NE610	150p	UA2240	300p
7497	40p	74LS88	30p	74S76	225p	4543	100p	NE611	150p	UA2240	300p
7498	40p	74LS89	30p	74S77	225p	4543	100p	NE612			

OSCILLOSCOPE PART 2

Be the first on your block with a hand-held scope. We continue this superb project with the full constructional details and setting-up instructions. Designs by K.W. Dugge.

The mechanical construction of voltage divider and preamp is shown in Fig. 1. The major component (and main constructional member) is the switch SW1 (a Makaswitch type). Between wafers 1 and 2 is fitted screening plate 2 (measurements as in Fig. 3) and between wafers 2 and 3, screening plate 3 (dimensions in Fig. 4). The screening plates support the voltage divider board and are soldered to it (on the copper track). The preamplifier board forms the end of the switch assembly. The entire section is surrounded by screening plate 1 (dimensions in Fig. 1) which is screwed to the bottom of the case and to the front structure.

In order to achieve a good earth connection for the switch rotor a safety pin, mounted on screening plate 3 before assembly (Fig. 5) is used as an earth contact.

The component layouts for the voltage divider and preamplifier boards are shown in Figs. 6 and 7. Resistors R1, R2, R15, R17, R19 and R21 are soldered directly to the switch contacts. Resistor R15 passes through screening plate 2 (drill diameter 4 mm). The two 3 mm holes are used for the (insulated!) passage of the connecting wires for switch contact 1 as well as for the connection to R15/R16. The same is true for R19 and screening plate 3.

The equipment is housed in an aluminium case; Fig. 6 shows the necessary drillings and cut-outs in the front panel. The screen cut-out (64 x 55 mm) must be fitted with a 'light tube', to prevent the entry of unwanted light. In the prototype instrument a plastic box was used from a pack of screws, having the appropriate outside dimensions. Behind this cut-out, a green film is fitted (from stationers) on which the measurement scale (6 x 8 squares of 7 mm side) has been drawn with Indian ink. The screen is fixed to the inside of the front panel using strips of foam draught excluder.

Figure 6 illustrates how the main board and screening plate 1 are fixed to the front section, using a bracket for each (M3 countersunk screw through the front section and the fixing bracket).

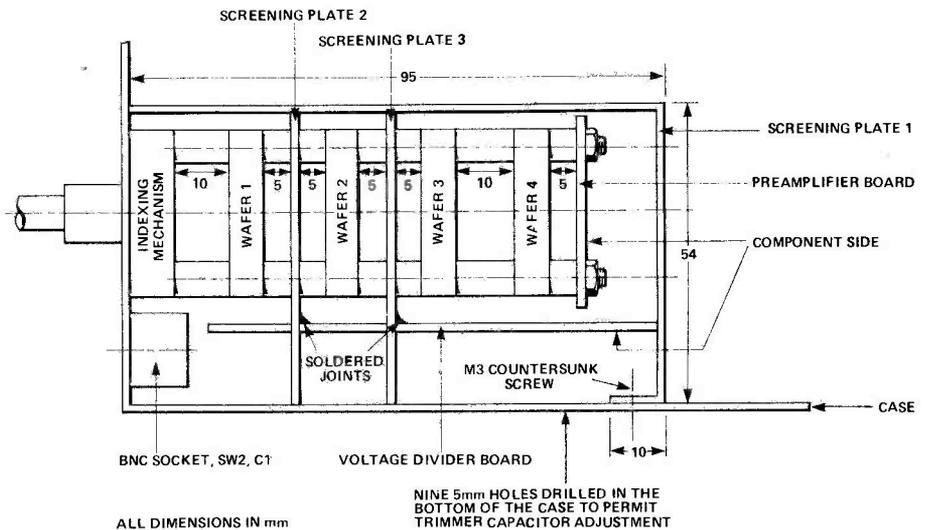


Fig. 1 Assembly of the voltage divider and preamp unit.

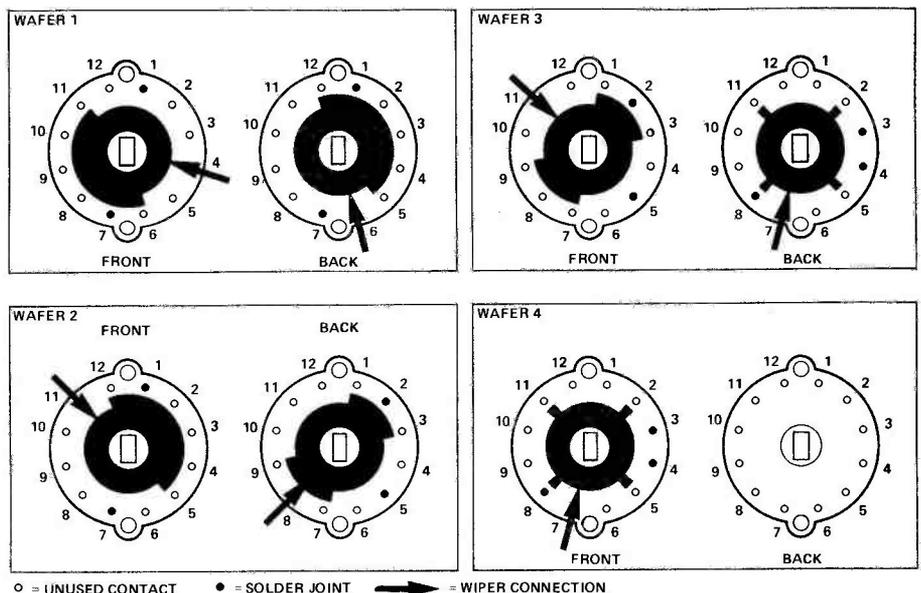


Fig. 2 SW1 contact wafer arrangement. Use in conjunction with the circuit diagram published last month.

The main board provides lengthwise stiffening of the case, since it is screwed at one end to the front section and at the other to the back panel (aluminium angle 10 x 10 x 1 x 70 mm long). The front half of the main board also provides lateral screening of the input voltage divider.

There are nine 5 mm diameter

holes in the bottom of the case (mark and drill from the circuit board, after the components have been fitted) for the adjustment of trimmer capacitors CV1-9. There is also a countersunk hole to take the M3 screw used for fixing screening plate 1 (as in Fig. 1) and three other M4 countersunk holes for securing the power supply board

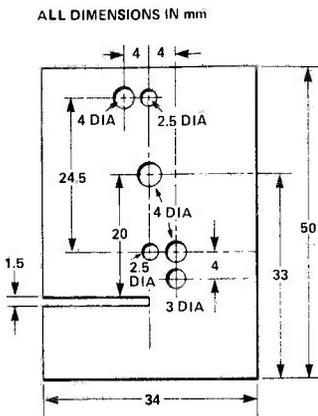


Fig. 3 Screening plate 2.

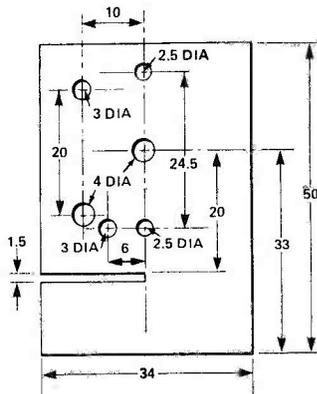


Fig. 4. Screening plate 3.

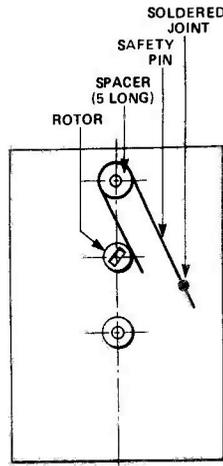


Fig. 5 Another view of screening plate 3.

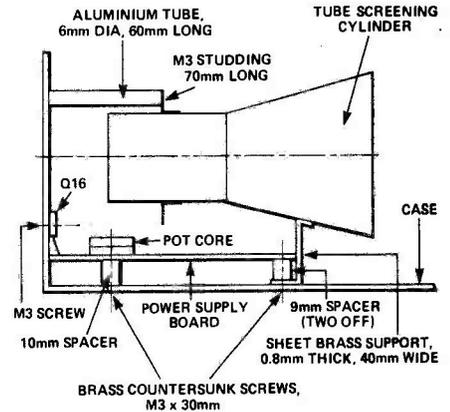


Fig. 7 The internal construction of the oscilloscope

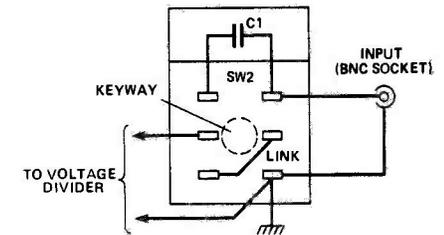
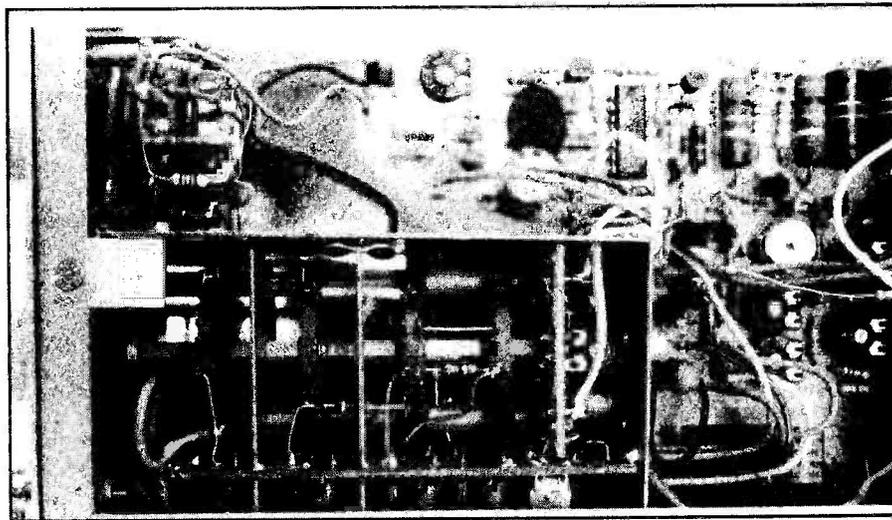


Fig. 8 The wiring details for SW2.

(marked out from the board). Note that the screw which passes through the transformer core should be made of brass or plastic.

The cathode ray tube is passed through — and only held by — the draught-excluder-coated screening cylinder. The fixing of this cylinder is as shown in the photograph. The sheet brass supports are formed to the shape of the screening cylinder and soft-soldered or glued with Araldite. Q16 is screwed to, and insulated from, the back panel of the case (use a mica washer, and test the insulation after fixing!).

The back panel has six holes as follows; two x 8 mm for the insulated phono sockets (for the source voltage), four x 3.2 mm for the main circuit board fixing bracket, the M3 studding (tube fixture) and transistor Q16.

Switching On And Setting Up

An ammeter must be connected in the supply line for the initial operation. At switch-on, a current of about 850 mA (DC) should flow for a short time; this should fall within a few seconds to about 700 mA as the tube heater warms up and increases in resistance. The following checks and adjustments should be made in the order in which they are given.

Set the stabilised supply voltage (on C26) to 10 V, using PR7.

Check the V_{CE} voltage on Q18 or

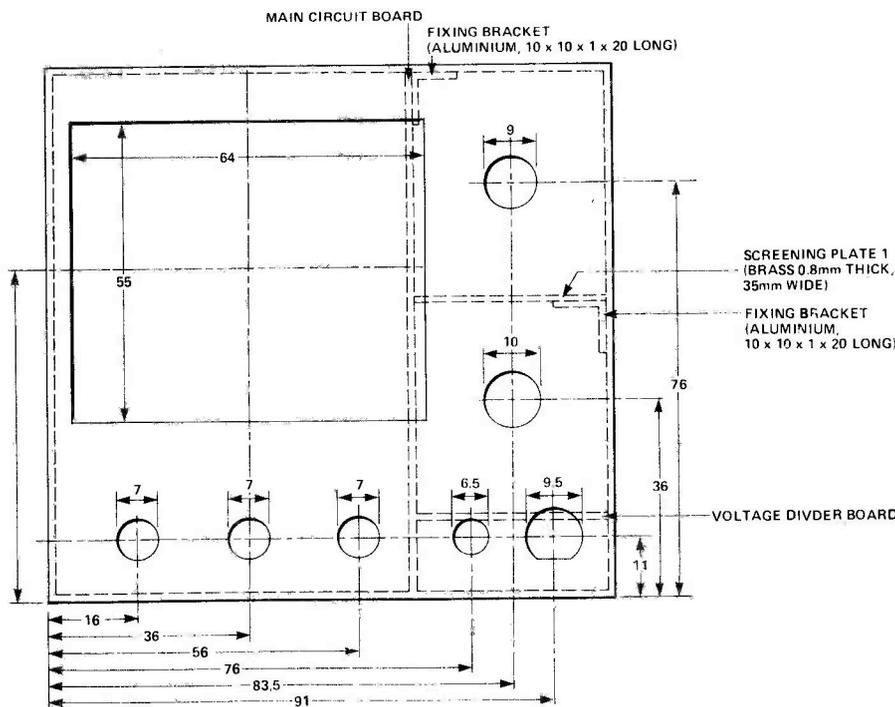


Fig. 6 The front panel drilling details.

PROJECT : Oscilloscope Part 2

Q19. This should be a 25 kHz square wave with an amplitude of 20 V peak-to-peak and an overshoot of less than 10 V. Due to tolerances in the pot core, the frequency may vary from 25 kHz.

Check the tube heater voltage: a 12-13 V peak-to-peak square wave. The heater voltage cannot be measured with a simple multimeter! The relatively high frequency of 25 kHz will

cause false readings. Check the +7 V, -6 V, +150 V and -460 V (on C36) supplies. Set the working point of the X-output stage, with PR6, to give 6 mA in the 150 V line. Set the working point of the Y-output stage, with PR3, to give +100 V 'after' R78/79. Set the beam to sufficient brightness with PR8 (not too bright, or the trace will be blurred). Adjust the trace for optimum sharpness

in the middle of the screen with PR9 and PR10. Set the picture width with PR5. Rotate the tube so that the X-axis is exactly parallel to the drawn scale. Fix the tube in this position using adhesive tape. Turn the Y-position potentiometer to its mid-position, and adjust the trace to the middle of the screen using PR1 (on the preamplifier board).

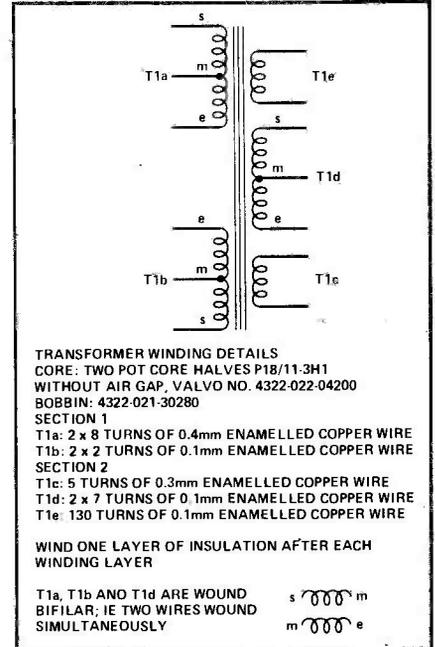
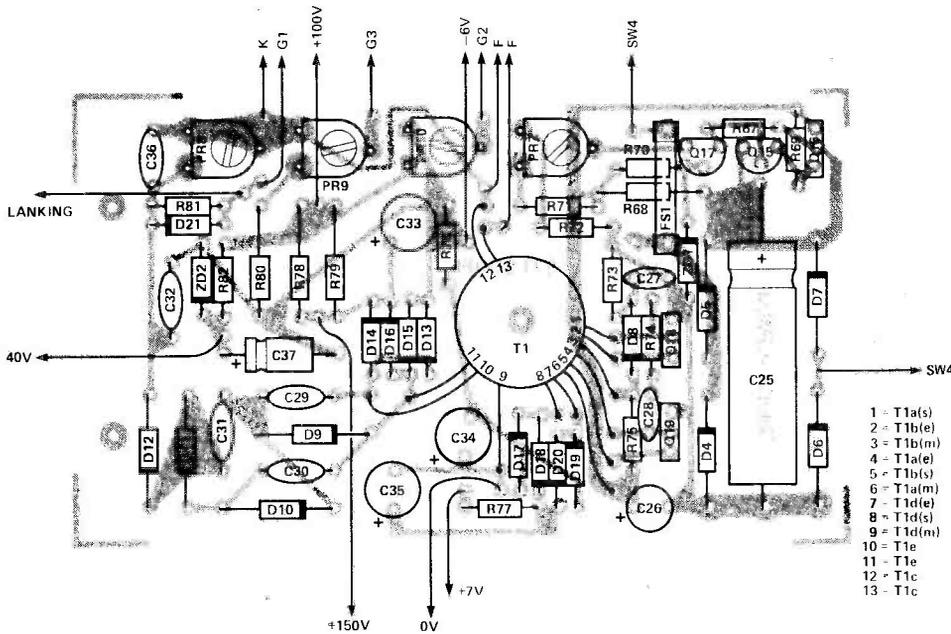


Fig. 11 Component overlay for the power supply board.

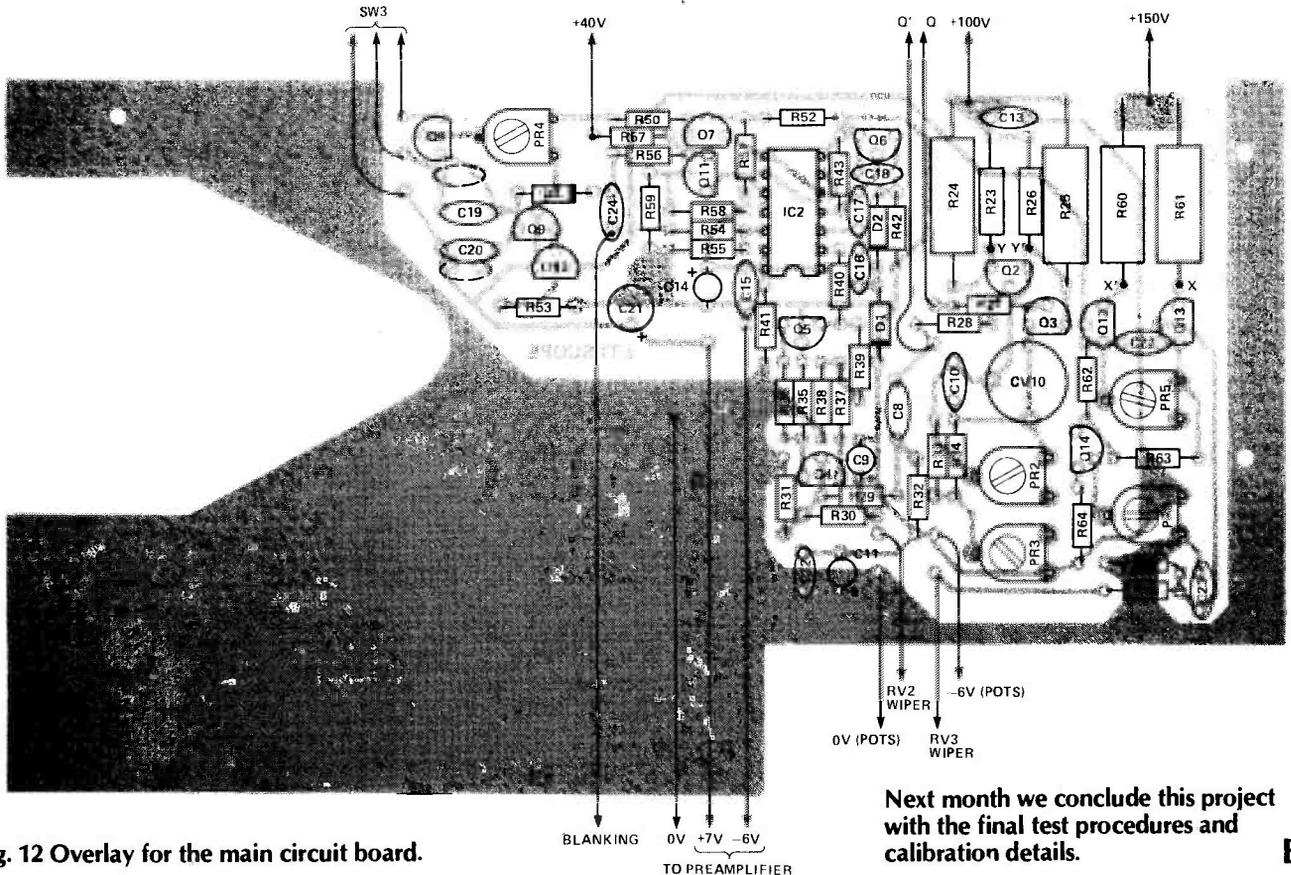


Fig. 12 Overlay for the main circuit board.

Next month we conclude this project with the final test procedures and calibration details.



COMPUTER WAREHOUSE

NOW OPEN
MONDAY-SATURDAY
9.30-5.30

BULK BUY SPECIALS



RAM SCOOP

4116 200 NS 8 for £12.95
4184 200 NS £9.50 each
2102-650 NS 8 for £5.50
INC VAT

25 WAY "D" CONNECTORS

	50+	100+
25p	1.70	1.10
25c	1.80	1.20

ALL + VAT

WIRE WRAP SKTS.


24 Pin Vers 28p
14 Pin Gold 22p
16 Pin Gold 24p
100 PCS Min Ord.

C10
DATA CASSETTES
10 for £5.75
Inc. VAT

RF CONNECTORS

50Ω BNC PLG 99p
75Ω BNC PLG 60p
PL258 PLG 40p
S0236 SKT 35p
100 PCS MIN ORD.

TELETYPE ASR33 I/O TERMINALS

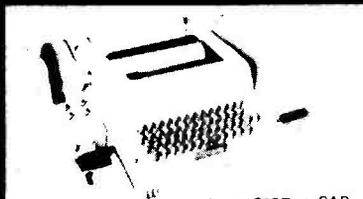


From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT

KSR33 With 20ma loop interface £125.00 + VAT.
Sound proof enclosure £25.00 + VAT

"OLIVETTI TE300" PRINTER/TERMINALS

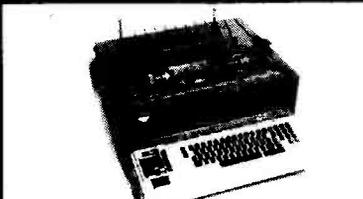

A complete I/O terminal with integral 8 hole paper tape punch and reader, full ASCII keyboard, 120 column printer, and control unit. The printer is capable of 150 baud with a serial TTL or balanced input-output sold in good overall condition but untested. Complete with circuit unguaranteed. Connect direct to your micro at ONLY £99.00 + £11.50 carr + vat.

MPU EXPERIMENTORS +5v, 12v, 12v, 24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 180mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:
+5v @ 2 amps DC
+12v @ 800 ma DC
-12v @ 800 ma DC
+24v @ 350 ma DC
and if that's not enough a fully floating 5v output @ 50 ma DC which may be seriesed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v mains input. They are ex GPD and may have minor scratches on the front panels, they are sold untested but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!

HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd. is a "no cost spare" spec for the GPD, the Modem 12 is a synchronous Modem for use on DATEL 2412 services, or other data links. Many features include switchable V26 modulation, 2400 baud full duplex, 800/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication, CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc.
£185.00 + £9.50 carriage + VAT.
*Permission may be required for connection to PD lines.

DISTEL

"Dial our Database!"
Get information on 1000's of stock items and order via your computer. 300 baud on 01-889 8800
18.30 to 0900 6 days a week and all day Sundays. IT'S FREE!

DIABLO S30 DISK DRIVES

Another shipment allows us to offer you even greater savings on this superb 2.5 MB (formatted) hard disk drive. Two types are available both fully refurbished and electronically identical, the only difference is the convenience of changing the disk packs.

S30 front loader, pack change via front door £550 + vat
S30 fixed, pack change via removal of top cover £285 + vat
+ & - 15v PSU for 2 drives £125 + vat
Carriage & insurance on drives £15.00 + vat fully DEC RK05, NOVA, TEXAS compatible further info on controllers etc on request.

MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those unerving hang ups and data glitches, fit one now and cure your problems! Suppression Devices SD5 A10 5 amp £8.95
Corcom Inc F1900 30 amp £13.95 + pp £1.00

DC SYSTEM SUPPLY

Professional fully cased fan cooled system supply. Standard 240V ac input with the following DC outputs 5V @ 11 amps +15-17v @ amps. -15-17v @ 8 amps and +24v @ 4 amps. All outputs are fully crowbar protected and the 5 volt output is fully regulated. Sold tested and in a new or little used condition complete with circuit £55.00 + carr £8.50 + vat DIM 15.5" x 9" x 6"

NATIONAL MA1012 LED CLOCK MODULE

★ 12 HOUR
★ ALARM
★ 50/60 HZ



The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am/pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only Suitable transformer £1.75. £5.25

ELECTRONIC COMPONENTS & EQUIPMENT


66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's., P.C.B.'s., Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

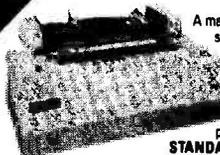2.5kds £ 4.75 + pp £1.25
5kds £ 6.75 + pp £1.80
10kds £11.75 + pp £2.25
20kds £19.99 + pp £4.75

SAVE OVER £1400

THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS * Full ASCII character set * Standard ink ribbon * RS232C/V24 serial interface - 7 xtal controlled baud rates up to 9600 * 194 characters per line * Parallel interface * Handshakes on serial and parallel ports * 4 Type fonts, italic script, double width, italic large, standard * Internal buffer * Internal self test * 170 CPS * Variable paper tractor up to 17.5" wide * Solid steel construction * All software in 2708 eeproms easily reconfigured for custom fonts etc.

All this and more, not refurbished but BRAND NEW At Only £525 + VAT
OPTIONAL EXTRAS * lower case option £25.00 * 16k buffer £30.00 * Second tractor for simultaneous dual forms sheet on request.

8" FLOPPY DISK DRIVES


Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today, the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring, IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.



7100 single sided £225.00 + 9.50 carr + vat
7200 double sided £295.00 + 9.50 carr + vat
full technical manual £20.00 alone £9.00 with drive, refund of difference on purchase of drive. Data sheet on request.
SPECIAL new, KODE PSU, drives 2 DRE drives £39.99 + carr + vat
8" single sided, single or double density diskettes £1.80 each £15.00 for 10 inc. lib case + vat.

COOLING FAN SPECIAL

Keep your equipment cool and reliable with our range of professional fans.
ETRI 99XU01 Miniature equipment fan 240v ac working DIM 92 x 92 x 25 mm BRAND NEW complete with finger guard. Markets price £18 our price £10.25
BUHLER 69.11.22 micro miniature 8-16 v DC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor, almost silent running ideal portable equipment, life in excess of 10,000 hours. BRAND NEW manufacturers price £32.00 our price £13.95
MUFFIN/CENTRAUR cooling fans, tested ex equipment 240v £8.50, 115v £5.50 + p&p £1.50
KOOL TRONICS Powerful snail type blower gives massive air movement with centrifugal rotor DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50Hz ac working ONLY £9.95 + £1.90 p&p.

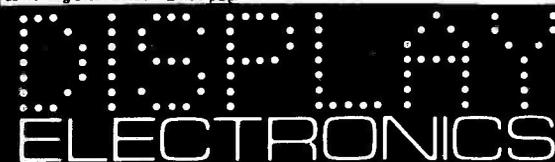

ELECTRONICS

Dept. E.T.1., 64-66 Melfort Rd., Thornton Heath, Croydon, Surrey. Tel: 01-889 7702 or 01-889 8800
MAIL ORDER INFORMATION
Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00 Prices and Postage quoted for UK only. Where post and packing not indicated please add 80p per order. Bone Fide account orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

SOFTY 1 & 2

EPROM BLOWER
Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMs or emulates EPROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.
Softy 2 for 2716/2732 £189 + VAT
Write of phone for more details.

9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75Ω composite input, tested but unguaranteed. £39.99 + £7.50 carriage + VAT. Complete with circuit.

SEMICONDUCTOR 'GRAB BAGS'

Without Semis amazing value contents include transistors, diodes, linear, I.C.'s, triacs, diodes, bridge rect., etc. etc. All devices guaranteed brand new full spec with manufacturer's markings, fully guaranteed. 50+ bag £2.95 100+ bag £2.18 TTL 74 Series

A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "moochy TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed at I.C.'s full spec. 100+ £8.99 200+ £12.30 300+ £19.80

RCA FULLY CASED ASCII CODED KEYBOARDS



IDEAL - TANGERINE, OHIO ETC.
Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. £43.95
VP611 Same as VP601 with numeric pad. £54.95
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. £64.28
VP616 Same as VP606, with numeric pad, Plug and cable for VP601, VP611 £2.25
Plug for VP606, VP616 £2.10
Post, Packing and Insurance. £1.95
ORDER NOW OR SEND FOR DETAILS.

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply. Supplied complete with circuit at only £10.95 + £1.75 pp. Believed working but untested, unguaranteed.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM



SX1000 Electronic Ignition

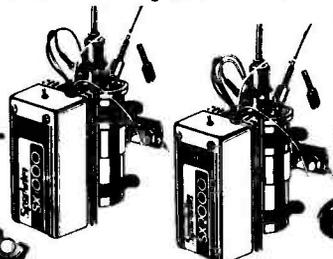- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles






SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



MAGIDICE Electronic Dice

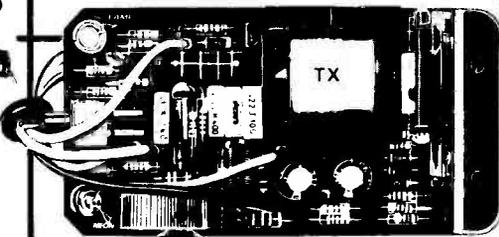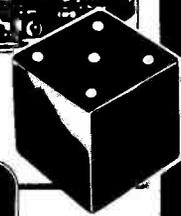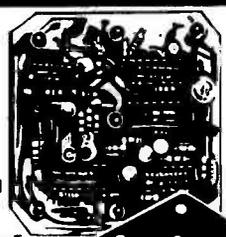- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble
- Supplied in superb presentation gift box



TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble

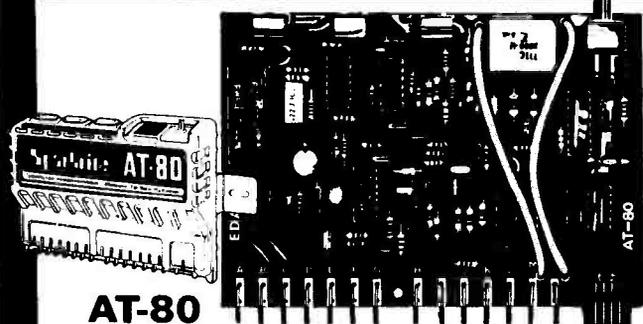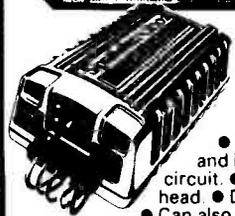


AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble. A real challenge for the electronics enthusiast!

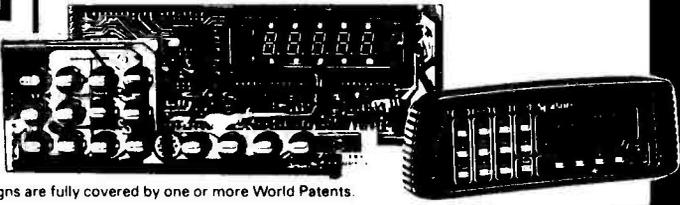

All EDA-SPARKRITE products and designs are fully covered by one or more World Patents.

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

NAME _____ ETI 6.82
 ADDRESS _____

 I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR
 £ _____ KIT REF. _____
 CHEQUE NO. _____
 24 hr. Answerphone
 PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
 SEND ONLY SAE IF BROCHURE IS REQUIRED

Allow 28 days for delivery

BRANDEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

DESIGNER'S NOTEBOOK

It's definitely a MOSFET month; we've shown you how to design big with our 150 W amp, and now Don Keighley provides a counter-balance with lots of smaller applications.

Field effect transistors (FETs) are peculiar brutes. If you've used them you'll know what I mean — negative bias voltages, depletion layers, pinch-off voltages and so on, ad infinitum. If you haven't used a FET before, the theory is simple enough: a FET is essentially a doped-silicon resistor (Fig. 1), much like a normal carbon resistor. The doped-silicon, however, exhibits a change of resistance if an electric field through the resistor varies. The electric field depends on the voltage present at the gate of the FET (Fig. 2), so a change of gate voltage changes the current through (and hence the resistance across) the device. Essentially a FET forms a voltage controlled resistance. In the example shown in Fig. 2 (a P-channel FET) a gate voltage of 0 V will produce a resistance of approximately 100R and a gate voltage of 5 V will produce a 1M0 resistance. For an N-channel FET the opposite is true; a gate voltage of 0V will give a resistance of 100R, -5V gives 1M0. For low drain-source voltages and low drain-source currents, the resistance change is linearly related to the gate voltage.

FETs have two enormous advantages over bipolar transistors. First, the gate input resistance is very high, meaning that virtually no current needs to be drawn from preceding circuitry. Second, FETs can exhibit very fast switching speeds — they can be used quite easily up to frequencies of many megahertz.

Problems, Problems

So, everything is fine — as long as you follow the rules. In low-power applications there is no reason why FETs can't be used anywhere a bipolar transistor can (they are, in fact, more versatile than bipolars — in low-power applications). But, therein lies the rub — *power*. It is very difficult (and expensive) to make a FET which can pass large currents: the main reason being the horizontal make-up of ordinary FETs. Bipolar transistors have vertical current flow and can pass larger currents

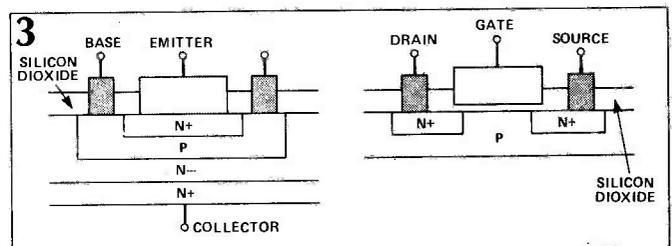


Fig. 3 Cross-sections through a) a bipolar transistor; b) a field effect transistor.

because of it. Figure 3a shows the theoretical cross-section of a bipolar transistor and a similar cross-section of a FET is shown in Fig. 3b. Current flow in the bipolar is vertically upwards from collector to emitter and the large area through which the current passes allows large currents. FET current flow is from left to right (drain to source) and the small area of current flow means smaller currents than in a similar-sized bipolar transistor.

Recently, VMOS FETs have been manufactured which overcome the power problems normally associated with FETs. A typical VMOS FET cross-section is shown in Fig. 4. Current flow is now vertically upwards, from drain to source, in much the same way as in bipolar transistors. The larger chip area means large current. Hence we have transistors exhibiting all the advantages of FETs without the usual power limits. VMOS FETs also have some other very interesting advantages:

- low ON resistance — good for audio switching purposes.
- power amplification — as high as 10^6 .
- positive temperature coefficient on the ON resistance — as the temperature goes up the transistor passes less current, therefore remaining thermally stable.
- easily operated in parallel to increase overall current flow — due to the inherent thermal stability no 'current hogging' by one device occurs.

We'll see applications using these advantages shortly.

The equivalent circuits of a VMOS FET (such as the VN67AF) in its OFF and ON states, are shown in Fig. 5. The zener diode protects the transistor from over-voltage on the transistor gate — it is a feature on many VMOS FETs but *not all!* If a VMOS transistor does not have such a gate-protection zener diode, it must be handled as a CMOS IC. You must take care to avoid static build-up between connections.

In the VMOS FET's OFF state (gate is low), diode D1 is reverse-biased and no current can flow from drain to source. In the ON state the diode is effectively shorted by a $2R_0$ resistor, allowing current flow from drain to source. With gate-voltages between 0 V and + V the resistor value is within the range $2R_0$ to ∞ .

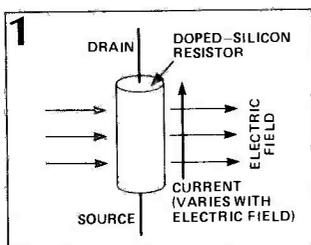


Fig. 1 A field effect transistor (FET) is a doped-silicon resistor, the resistance of which can be varied by changing the electric field through it.

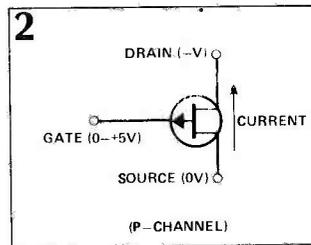


Fig. 2 The symbol for a FET. Current through the FET and hence the resistance across it is controlled by the voltage at the gate.

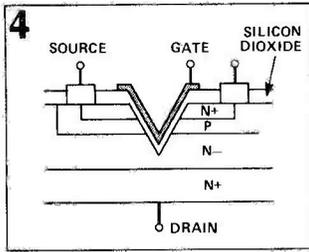


Fig. 4 Cross-section through a VMOS FET. Current flow is vertical, as in a bipolar transistor.

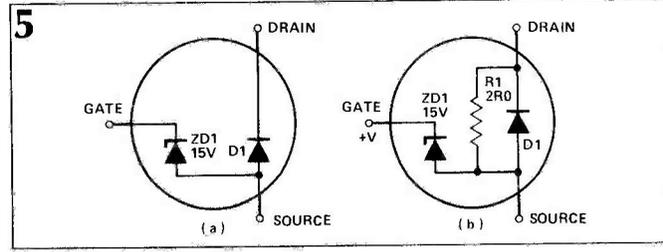


Fig. 5 Equivalent diagrams of a VMOS FET a) in the OFF state; b) in the ON state.

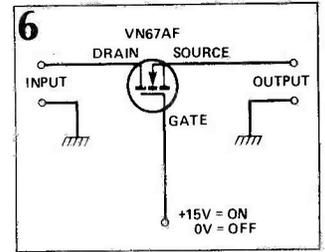


Fig. 6 A simple unidirectional audio switch formed by a single VMOS FET.

Applications

Low ON resistances and high OFF resistances make VMOS FETs ideal for use in audio switching networks. Figure 6 shows a simple on/off audio switch controlled by the voltage on the transistor gate: +15 V turns the switch on and 0 V turns it off. Audio signals can only pass in one direction, from drain to source, but any audio voltage of about $-\frac{1}{2}$ V to +5 V can be switched.

The extremely high gate-input resistance of VMOS FETs means that they can be switched by virtually any control method, such as CMOS, TTL, op-amps and so on. A four-channel audio multiplexer is shown in Fig. 7, which uses a bank of four VMOS FETs as input switches with the transistors being clocked

in turn by a 4017 decade counter. The fourth output of the 4017 is connected to the reset pin, giving a 1-2-3-4 count to control the VMOS FETs. As each FET is enabled by the 4017 counter the audio input at its drain is connected, via the source and a 10k resistor, to the op amp.

If TTL logic is used to control VMOS FETs, a gate pull-up resistor must be inserted (Fig. 8) to ensure that the gate voltage is pulled up to +5 V when on — sufficient to give about 500 mA of current through the transistor. Figure 8 also shows the principle of VMOS current control through a load, in this case an indicator lamp. The load can, however, be virtually anything requiring current, eg relays, LEDs or loudspeakers.

Figure 9 shows the circuit of a simple siren using an astable (formed by CMOS gates), a VMOS FET and a loudspeaker. When the transistor is on, its drain to source resistance is about $3R_0$ so about 1 A (ie $V/R = 11/11$) passes through the loudspeaker. The average current (assuming a 50% duty cycle from the astable) is therefore about 500 mA. Audio output power is thus about 2 W.

Paralleling two or more VMOS FETs in an output stage easily increases current-handling capacity. The siren circuit of Fig. 9 is redrawn in Fig. 10 with four paralleled output transistors. This more powerful siren will produce an output power in the region of 6 W. You can see that no ballasting resistors are needed (as you would require with a similar circuit using bipolar transistors) because of the positive temperature coefficient of the drain-to-source 'on' voltage. The explanation of parallel operation is very simple: if any one of the VMOS transistors begins to conduct a larger than average current it will tend to get warmer and so current flow will reduce.

Linear Applications

So far we've only considered switching applications using VMOS FETs (ie on or off), but they can just as easily be operated in a linear mode (to act as voltage controlled resistors) in the same way as ordinary FETs.

Linear regulators in power supplies are easily constructed:

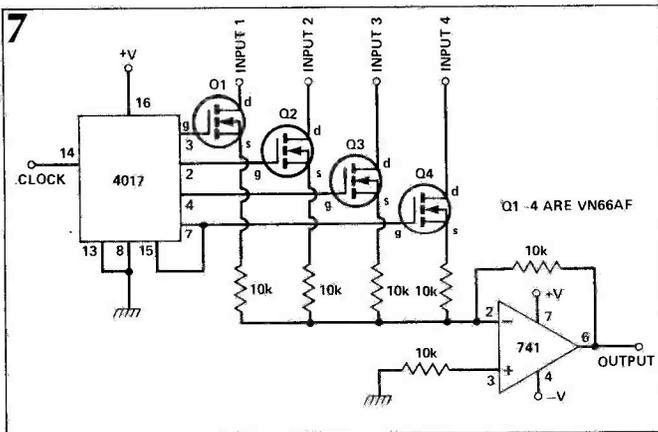


Fig. 7 Four VMOS FETs used in a four-channel audio multiplexer giving a time division multiplexed output signal.

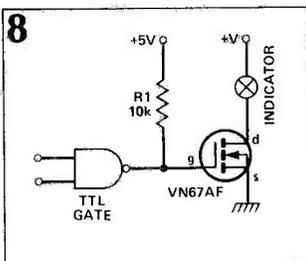


Fig. 8 TTL gate logic can be used to control VMOS FETs but a gate pull-up resistor must be used to ensure that the FET gate reaches a high enough voltage to allow sufficient current flow through the FET.

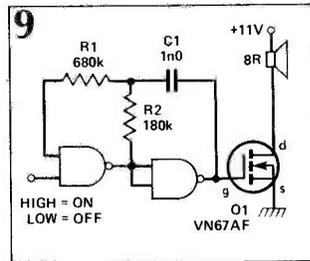


Fig. 9 Simple audio siren. An astable oscillator provides drive to switch the VMOS FET on and off at an audible rate.

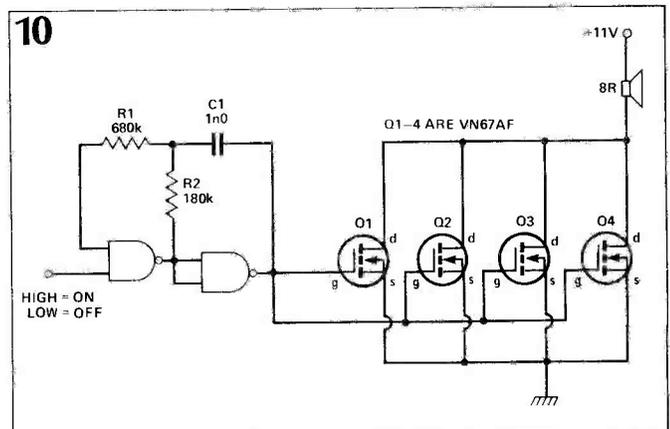


Fig. 10 Paralleling output VMOS FETs can be done simply because they are inherently thermally stable.

such a circuit is shown in Fig. 11. An op-amp compares the output voltage with a reference voltage derived from a zener diode and parallel variable resistance. The reference voltage is thus variable from 0V to about 11V. If the output voltage is less than the reference voltage, the op-amp increases the drive voltage to the VMOS FET, and vice versa, in a negative-feedback controlled loop.

Constant-current sources suitable for charging Nicad cells can be made easily using VMOS FETs, and a simple unregulated circuit is shown in Fig. 12. The current output is defined primarily by the gate voltage of the transistor by altering the ratio of the two resistors R1 and R2. By varying the gate voltage between 0V and 5V, a range of currents of approximately 0 - 250 mA will be obtained. Although the high output impedance of the transistor (relative to that of a bipolar) provides a level of current regula-

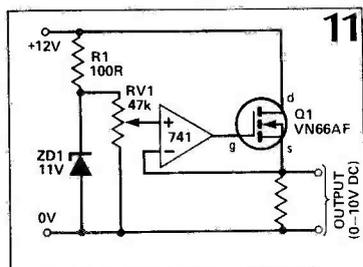


Fig. 11 A VMOS FET used in a linear voltage regulator. An op-amp is used in a negative feedback loop to provide the controlling gate voltage for the VMOS FET.

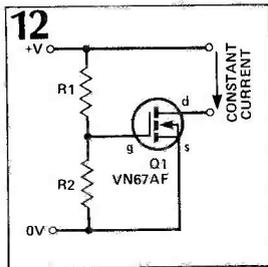


Fig. 12 Unregulated constant current source formed around a VMOS FET.

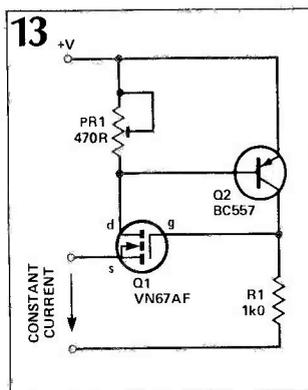


Fig. 13 Transistor Q2 holds the gate-to-source potential of the VMOS FET constant for any load. The current is therefore constant.

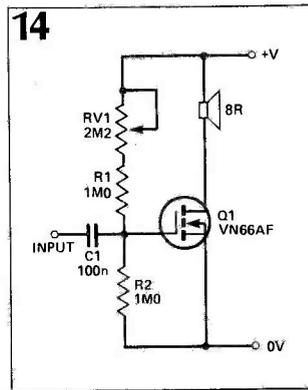


Fig. 14 A simple class A power amplifier.

tion, differing loads will produce differences in current flow.

The circuit of Fig. 13 overcomes this problem with a negative feedback loop formed by Q2. This transistor holds the gate-to-source potential of the VMOS FET constant for any load. Thus the current flow is constant whatever the load.

A Class A power amplifier can be constructed with a VMOS transistor and because of the inherent thermal stability of the FET, very few precautions need be taken with the circuit (Fig. 14). The high transistor input resistance allows very high value biasing resistors. Although obviously an audio power amplifier (the transistor load is a loudspeaker!) the circuit itself will operate up to the megahertz regions. **ETI**

POWER DIMMING MODULES

- ★ Fully isolated
- ★ Multi channel common wiring lines
- ★ Master dimming over banks
- ★ Remote override
- ★ Dead "kill" and "all on"
- ★ Low voltage feed lines
- ★ Common neutral or live outputs

Power Dimming Modules
A range of isolated digitally controlled dimming modules, complete with panels. Each type requires connection to the supply/reference board

PRICES (1 of)
 SPC £13.90
 SPU (1K) £9.90
 SPU (2K) £23.90
 MC £7.20
 RS £8.50
 Supply £18.20
 Post/Pack £1.50
 Total order

SPECIAL DISCOUNTS
 Are available on power dimmers.
 Total your order up and deduct:
 £100 to £199 20%
 £200 to £299 25%
 £300 to £399 30%

3 CHANNEL SOUND/LIGHT CHASER £35.70

LB31000SLC

A high performance sound to light providing bass, mid and treble separation, employing active filters. Automatic switching to chase in the absence of a music signal 1000W/Chan

STEREO DISCO MIXER/PREAMP

Magnetic or Ceramic

Main supply £7.20
PFL supply £1.00

£33.70
Magnetic or ceramic deck versions please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/controls/misc mixer/tones/mic auto fade over decks and P.F.L. The unit can be used with virtually any power amp

NEW NEW NEW

4 CHANNEL SOUND/LIGHT AUTO CHASER

£49.90

A high performance sound to light providing bass, mid, presence and treble, employing auto level filters. Automatic switching to chase in the absence of a music signal 750W/Chan.

PROGRAMMABLE — 8

£114.90

P/P INS £1.50

Complete with blue panel/white letters

- ★ 8 channel 400W each
- ★ 16, 32, 64, 128 patterns
- ★ Automatic program recycle
- ★ Adjustable cue on/off speed
- ★ Optically isolated, suppressed
- ★ Either common Neutral or live lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be replayed in the stored order, with control over the cycle on and off time. At the end of the program the system re-cycles to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although removing the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following night's performance. The module obviously provides unlimited effects and is a must for all serious lighting shows.

MULTI-4 £48.90

The Multi-4 is a comprehensive sound and chase module, offering a wide range of forward, reverse or random effects with additional sound modulation facilities. Modes of operation are set on control pots which act as electronic switches. The unit has a wide speed range and will accept virtually any sound level input. The Multi 4 also provides monitor circuits for LED driving. The triac outputs may be used to drive up to 4000W of lighting or up to 10 metres of rope lights

NOW AVAILABLE!

BLUE FASCIA PANELS (White Lettering)

Type	Knobs	Units	Sw	Price
Multi	5	4	1	£9.70
41000SLC	2	4	1	£9.20
31000SLC	5	1		£8.70
31000SL	4	1	1	£7.70

NEW NEW NEW

2/4/8 CHANNEL CHASER

LB81000LC

£28.00

An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re cycle delay

3 CHANNEL SOUND/LIGHT LB31000SL

£22.70
All the advantages of the SLC without chase
Controls: bass/mid/treble/master sensitivity

4 CHANNEL SOUND CHASER

A forward running Chaser with sound input speed modulation. Ideal for rope lights, etc.

LB41000LC-S
£24.20

4 CHANNEL SEQUENCER LB41000LS

£19.20
A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst

L & B

ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon
Surrey CR0 3EB. Tel. 01-689 4138
Goods by return (stocks allowing)
We are open Mon to Fri 9 to 5

Each module is manufactured from the highest quality components, fully tested, supplied with a connection diagram and guaranteed for twelve months.
All prices shown are VAT inclusive. Please include 75p post/packing except where individually stated. To mail order send cheque/P.O. Registered cash Access number. C.O.D. service £1 extra. For further information send a self-addressing high model.
PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

introducing

The WERSI Comet



CLOSE UP OF COMET KEYBOARD

Aura Sounds have pleasure announcing the Comet, the "Band in One" organ, is now available through our branches. Once again the Comet achieves the optimum performance in its class.

It offers:—

- Numerous realistic and interesting tonal colours with guitar voices, synthesiser and other modern sounds together with the more traditional drawbar and orchestral sounds
- Playing aids include chord memory, WRS, Keyboard Selector, Wersimatic rhythm and automatic accompaniment section plus much, much more



THE COMET TRANSPORTABLE W10 T

- Comet can accept up to four external keyboards (in addition to the 2 keyboards on the organ — a five man band can play on one instrument.
- Wersi have simplified self assembly even more, with plug in circuits etc.
- Ergonomic playing table eases operation.

The Comet is available in the elegant lines of the spinet (W10 S) and with chromed steel legs (W10 T) for transportability.

The Comet, the Organ to see us through the eighties — available now.

For more details of this superb organ, ring us now on 01-668 9733 or write to Aura Sounds Ltd. at the Purley Branch.

AURA SOUNDS LTD.

are the first company to successfully market WERSI organs and kits in the U.K. We have modern show-rooms where we pride ourselves you will receive a friendly welcome Why not pop in and see the WERSI range for yourself — we can always arrange a free demonstration. We also offer a free technical telephone support service which is second to none.

Alternatively, fill in the coupon below for free details. For immediate action telephone 01-668 9733 24 hour answering service.



THE COMET SPINET W10 S

AURA SOUNDS LTD.

14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.
Tel: 01-668 9733
17 Upper Charter Arcade, Barnsley, Yorkshire.
Tel: (0226) 5248
1729 Coventry Road, Sheldon, Birmingham.
Tel: 021-707 8244
Micro Centre, Albany Road, Newquay, Cornwall.
Tel: Newquay 5953

WERSI and AURA — The Winning Combination

Please send me FREE, all the details of The Comet and Wersi Range

NAME _____
ADDRESS _____

ETI/6

Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.



PORTABLE POWER?

After years of writing books on computers and awarding his famous 'White Elephants' to the industry, Adam Osborne finally took the ultimate step and produced the Osborne I. Despite the fact it is portable, well... almost, and fairly reasonably priced as hardware goes, the main attraction seems to be the fact that you get several hundred pounds' worth of software thrown in for free.

Having humped the system up hill and down dale and generally put it through its paces, our reviewer will hopefully have recovered sufficiently to put pen to paper and report on his findings.

SIMULATING FORTH

The interest sparked off by our recent series on FORTH has been so great that even we were taken by surprise. As a result, next month we'll be publishing a rather novel BASIC simulator for FORTH operations so those of you who would like to try out the language — without actually having to buy a version of it for your system — can have a go. It certainly won't break any speed records, in fact it is extremely slow, but it does allow you to get to grips with Reverse Polish Notation.

PROGRAMMERS' TWO-STEP

OK, so you've learnt to program in BASIC. Now, perhaps, you'd like to have a go at assembly but you're put off by the fact that you can't alter your programs with the same ease as you can in BASIC. Well, what you need is our two-pass assembler which lets you write and modify the assembly code first and then turn it into machine code **without** destroying your original.

So, if you'd like a professional software tool to help you with your assembly language programming, don't miss out on our next issue!

ARE YOU SECURE?

Or, to be more precise, are your programs? In our next issue we'll be taking a look at a rather clever method of program protection which actually allows your programs to be copied but then won't let them run on any other system... frustrating in the extreme! We will also be publishing an extremely ingenious Voting Loader which guarantees perfect loading from cassettes at almost any speed. So, for your own peace of mind and the security of your programs and data, make sure you secure a copy of our June issue.

Articles described here are in an advanced state of preparation but circumstances may dictate changes to the final contents.


NAME
ADDRESS
Please reserve me a regular copy of Computing Today
GIVE THIS TO YOUR NEWSAGENT

JUNE ISSUE ON SALE
FRIDAY 14th MAY



STYLUS TIMER

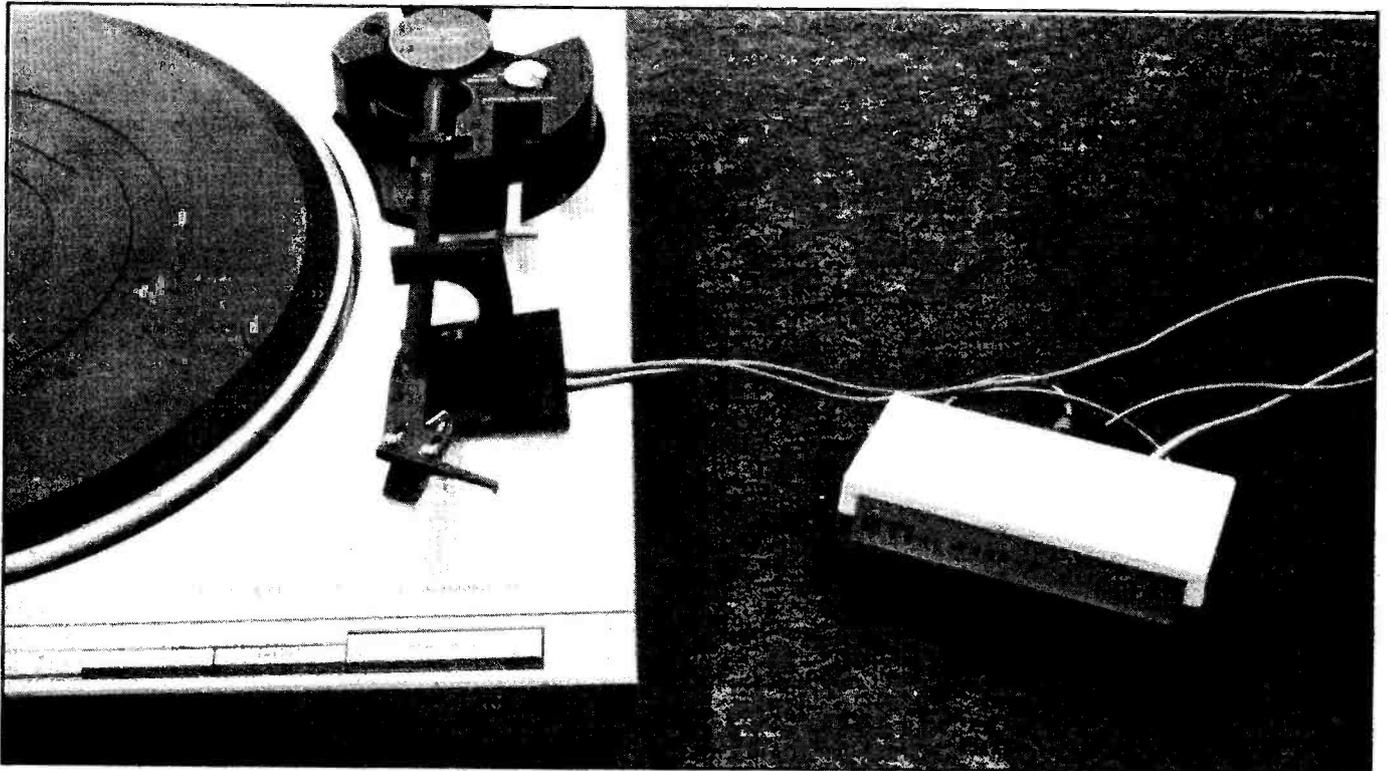Do you play your records with a smoothly-contoured, precision-engineered, highly-polished stylus — or a worn-out nail? Check your playing hours with the ETI Stylus Timer. Design and development by Phil Walker.



For modern styli and cartridge combinations the life of the stylus may run to many hundreds or even thousands of hours before replacement is necessary. The trouble is that even at five hours each and every day (which is quite a lot) it will take over six months to accumulate 1000 hours playing time. If you are like us you could easily forget whether you changed the old nail last week or last year, quite apart from knowing how long it has been used since then.

Don't worry, help is at hand — this device is designed to measure the total number of hours your stylus has been in use since you last changed it and give some indication of that measurement.

The device has six LEDs which, in the basic configuration, change every 200 hours. This could be used to indicate that a check on stylus condition should be carried out either at home or by your local dealer. When the last one comes on it will stay on until the device is reset (assuming the power is on).

As mentioned above, the basic

design allows for 200 hours per step, the last one occurring after 1000 hours. This can be modified to 400, 500, 1000 or even 2000 hours per step giving replacement times of up to 10,000 hours for the very lightest equipment (or Scrooges), or 100 hours per step if your equipment is a little heavier than some or you want to keep your stylus in tip-top condition all the while.

In order to eliminate dependence on mains supplies when the equipment is not in use, the device contains a rechargeable battery which provides the microamp or so needed to keep the CMOS devices active. Also the LED display is turned off when not required to conserve battery power. To prevent accidents the reset facility is disabled when the device is on standby.


Designs Discussed

The circuit uses standard CMOS integrated circuits for most functions in order to keep the standby power as small as possible. This enables us to use a PP3-sized rechargeable Ni-cad battery, ensuring that with intermittent use the device should operate almost

indefinitely. (In fact a normal dry-cell PP3 battery will give a very long life but may not like the charging current flowing into it via R7).

The power for the LED display and the timing signal for the logic are taken from the AC input. This is any 50 Hz voltage source giving between 12 and 20 V at about 50 mA. For preference this supply should be switched with the turntable or equipment mains supply.

There was much discussion in the office about the actual method of detecting stylus use. The first method we considered involved detecting the presence of a music signal from the pickup, in a similar manner to the Watchdog auto-switch-off project we published in October '77. However, if the signal was tapped off after the RIAA preamp we realised the project couldn't be built by readers who lacked the confidence to muck about inside their expensive commercial hi-fi. On the other hand, putting the project between the deck and the preamp would lead to the knotty design problem of not degrading the pickup performance. Thus we opted for a

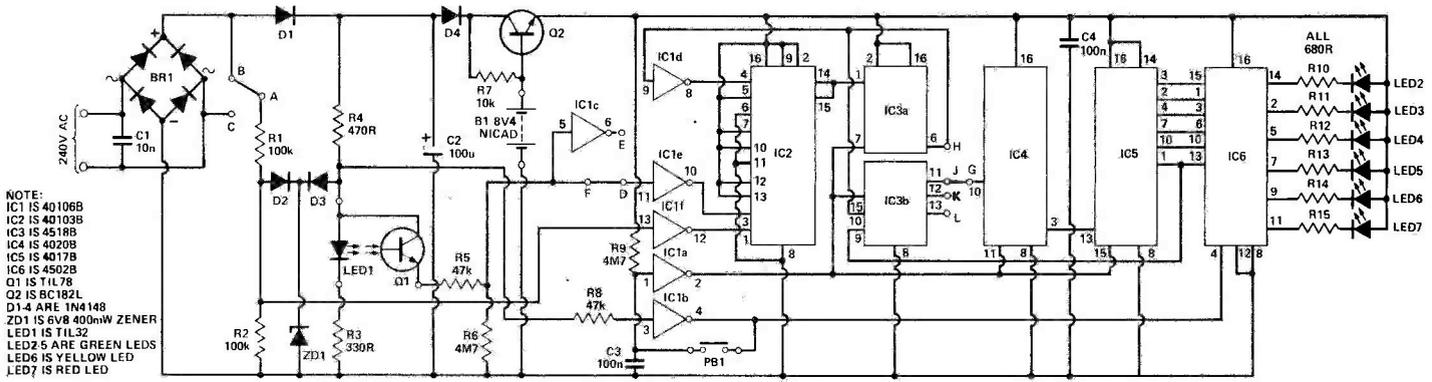

NOTE:
 IC1 IS 40106B
 IC2 IS 40103B
 IC3 IS 4518B
 IC4 IS 40208
 IC5 IS 4017B
 IC6 IS 4502B
 Q1 IS T1L78
 Q2 IS BC182L
 D1-4 ARE 1N4148
 ZD1 IS 6V9 400mW ZENER
 LED1 IS T1L32
 LED2-5 ARE GREEN LEDES
 LED6 IS YELLOW LED
 LED7 IS RED LED

Fig. 1 Circuit diagram of the ETI Stylus Timer. The various lettered links are used to select the timing period (see text).

HOW IT WORKS

The 50 Hz power input is rectified by BR1 and charges C2 via D1. Q2 and R7 form a simple voltage regulator using the battery B1 as a reference. If there is no AC input then D6 isolates the rectifier circuitry from Q2 and B1 supplies the very small bias current needed to keep the CMOS devices active via the base-emitter junction of Q2.

R4, D3 and ZD1 form a moderately stable voltage for the optical sensor and an input to the power detection circuitry IC1b. The output from the optical sensor (LED1 and Q1) is taken via R5 and R6 to IC1e either directly or via IC1c. This allows the circuit to operate with either an open or blocked light path as required.

Depending on the position of link A-B or A-C a 50 or 100 Hz signal will be applied to IC1f. The voltage of this signal is limited by R1, R2, D2 and ZD1 to prevent damage to IC1.

IC2 is connected such that it divides by 220 or 219 as determined by the input from IC1d. This is accomplished by the device loading its internal eight bit counter with the binary number on its inputs each time it reaches a count of zero. In this case the most significant seven bits are wired to 1101101X = 218₁₀ while the least significant bit (X) is switched between 0 and 1. The output from this stage drives IC3, a dual decade divider. The Q₄ output from IC3a controls the division ratio of IC2 as

outlined above. As the Q₄ output is only high for two clock periods out of 10 the effective division ratio of IC2 is:—

$$8/10 \times 220 + 2/10 \times 219 = 219.8$$

IC3b is used to divide by 2 in the standard circuit and then drives IC4 which does the rest of the division required (a factor of 2¹⁴ or 16384) to give a one cycle in 200 hours signal.

IC5 is a decade counter with 10 decoded outputs. Each output is high for one clock period of the 200 hour input signal (or longer if counting is suspended). Only the first six outputs are used to drive IC6 and the sixth output also inhibits IC3b to prevent further counting. IC6 is a hex buffer with three-state outputs which have a fairly high current sink capability and can be forced to a high impedance state by a signal on pin 4. This facility is used to prevent the LED display taking current while the AC supply is off.

The reset switch PB1 is connected in an unusual place so that it can only pull the input to IC1a low when the power sense circuit indicates that the AC supply is present. When operated, the reset circuit applies a high logic level to the reset inputs of ICs 3, 4 and 5 for about a second. IC2 is not reset and will cause an error of two or four seconds in the timing but in a hundred hours or so this is not significant.

mechanical solution, but adventurous readers may care to adapt this project and the Watchdog circuit for their own needs. Note that we CANNOT give any technical advice if you do try it.

The circuit operates by detecting when the tone arm is away from its rest position and then allowing the rest of the circuit to count at 50 or 100 Hz. The 50 or 100 Hz is divided by about 72 million in order to drive the final counter at one pulse every 200 hours. The already decoded outputs of this device (IC5) are used by the output driver (IC6) to power the display. The division ratio actually used is 72, 024, 064, this being:-

$$2^{14} \times 20 \times (1/5 \times 219 + 4/5 \times 220) \\
 (IC4) (IC3) \quad (IC2)$$

The error between this figure and the theoretical 72,000,000 is 0.033% or 20

minutes in 1000 hours.

The final counter (IC5) has 10 decoded outputs of which only the first six are used. These control IC6 and thus the display. When the sixth output of IC5 goes high it disables the counter chain causing the sixth LED to remain on indefinitely.

IC6 contains six inverting buffers which have three-state outputs. This facility is used to switch off the LEDs and conserve power.

A transistor (Q2) was used in the standby battery circuit so that when operating from the AC input, the supply voltage to the ICs was little different to that when operating from battery alone. Also the LED voltage can be stabilised at the correct value. The configuration allows the battery to be trickle-charged from the same supply.


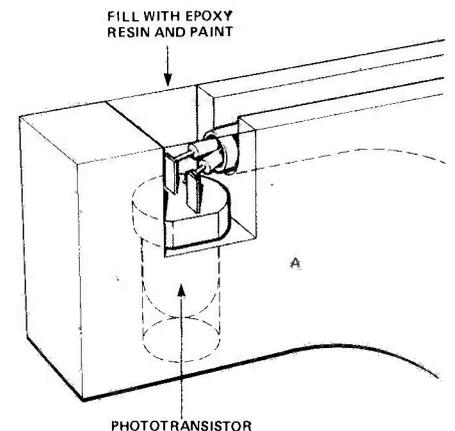
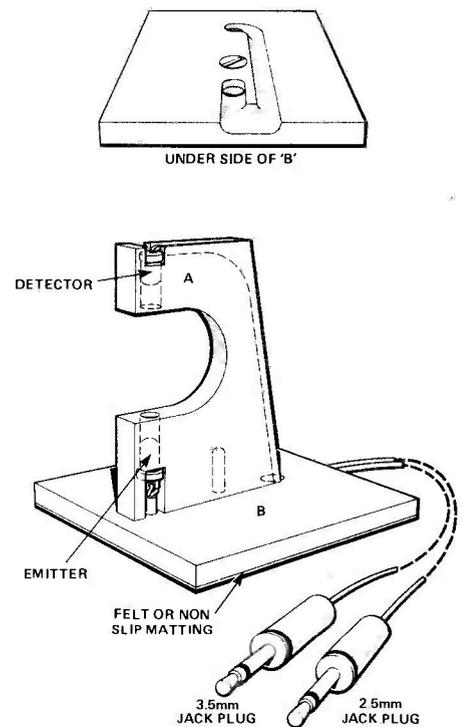


Fig. 2 Constructional details of our sensor. Using different sized jack plugs will prevent incorrect connection.

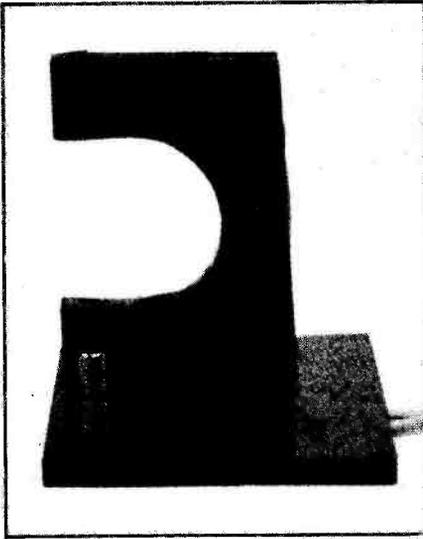

Construction

The construction of the main unit is straightforward, if a little fiddly on account of its small size. Assemble the components onto the PCB including the three links but excluding LED 2-7. Place the assembled PCB in the bottom of the box and align it over the wider spaced fixing holes with C2 next to the space for the battery. Mark the positions for the LEDs on the front panel and the jack sockets and PB1 on the back panel. Also mark a position for the power cable grommet. Drill all these holes in sizes to fit your components.

Wire up the switch and sockets. The common connection from R4 on the board should go to the sleeve connections on the jack sockets to

prevent accidental short circuits via the panel. The LEDs should now have their leads bent so that they will go into the board while the LED body protrudes through the panel. Finally connect the battery connector and the AC power lead. The latter should be a twin core screened cable terminated in a three pin DIN plug or similar to pick up the supply.

The Sensor

The purpose of the sensor housing is to hold the emitter and receiver in line and exclude some of the ambient light. Our sensor was constructed from an offcut of black Perspex about 90 x 55 x 6 mm. This was cut into two pieces (36 x 55 and 52 x 55 mm). A U-shaped slot was cut out of the longer side of the smaller piece; then a hole was drilled in the thickness of the material in both legs of the U to take the optical devices and hold them in line. The back edge of the U was slotted to take the screened wire from the phototransistor.

Three holes were drilled along the centre line of the other piece of Perspex; two to take wires and one to take a fixing screw. The underside of the base piece was channelled out using a rasp attachment in a hobbyist drill to conceal the wires.

The sensor device is mounted in the top hole to reduce the amount of ambient light reaching it. The screened wire from the phototransistor is run along the slot in the plastic and down the hole in the base. The slot can be filled with resin and painted when finished.

If a small three-way connector can be obtained this could be used in place of the two jacks and a single length of screened cable would suffice to connect the sensor.

Power supply

The AC power supply is very simple and consists of a small mains transformer, fuse, neon indicator and three pin DIN socket mounted in a small box. Construction is very straightforward and, if the specified box is used, most small 6 VA transformers will fit onto the moulded pillars in the box, obviating the need for external screws.

Use and Modifications

To use the stylus timer, the sensor should be positioned so that the tone arm interrupts the light beam when it is in the rest position. Make sure that it does not foul the arm at any time if you have any sort of automatic control.

If possible the AC power supply for the device should be obtained from your system. Anything from 12 to 15 V AC may be used without modification.

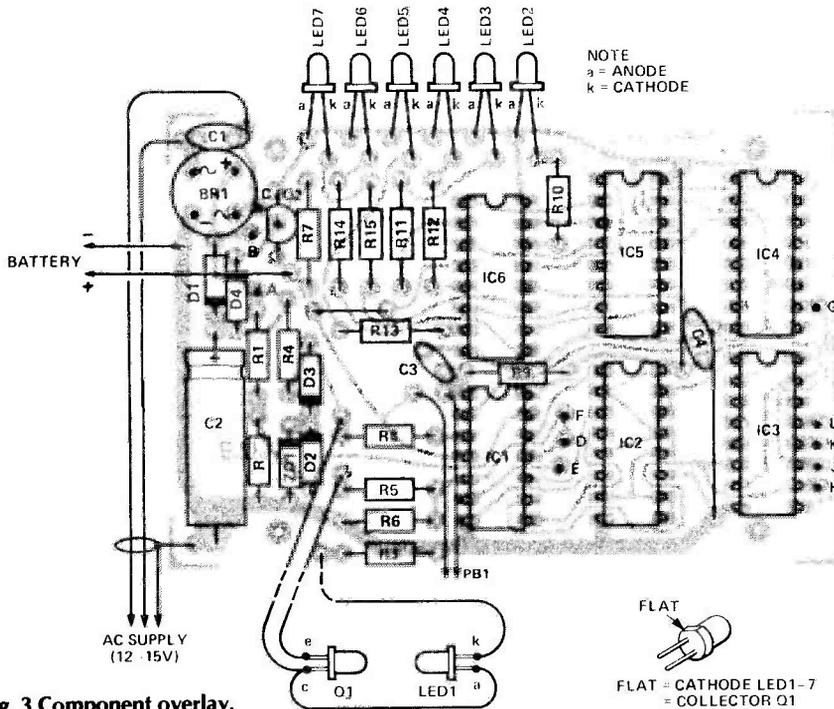


Fig. 3 Component overlay.

PARTS LIST

Resistors (all 1/4 W, 5%)

R1,2	100k
R3	330R
R4	470R
R5,8	47k
R6,9	4M7
R7	10k
R10-15	680R

Capacitors

C1	10n ceramic
C2	100u 40 V axial electrolytic
C3,4	100n ceramic

Semiconductors

IC1	40106B
IC2	40103B
IC3	4518B
IC4	4020B
IC5	4017B
IC6	4502B
Q1	TIL78 IR receiver
Q2	BC182L
D1-4	1N4148
ZD1	6V8 400 mW zener

BR1	50 V, 1 A bridge rectifier
LED1	TIL32 IR transmitter
LED2-5	2 mm green LED
LED6	2 mm yellow LED
LED7	2 mm red LED

Miscellaneous

PB1	subminiature push-button
B1	8V4 PP3-size Ni-cad (or PP3 — see text)

PCB (see Buylines); PP3-size battery clips; case 125 x 65 x 30 mm (Vero ref. 75-2682A); 3.5 and 2.5 mm jack plugs and sockets; three pin DIN plug (if required to connect to power unit); thin screened twin cable; small grommet; 100 x 55 x 6 mm acrylic sheet.


AC POWER UNIT (IF REQUIRED)

12 V, 6 VA mains transformer; 100 mA fuse and fuseholder; mains neon; case 125 x 65 x 50 mm (Vero ref. 75-2684B); three pin DIN socket; three-core mains cable; grommet; solder tags.

Up to 25 V may be used but R4 and R7 should then be 1k0 1 W and 27k respectively. If the supply is greater than 25 V, one side of any available supply is earthed or if you prefer not to tamper with your system then use the simple mains power supply described.

With the sensor in position and a suitable AC supply connected, press the reset button on the unit. The first green LED should light and stay alight for 200 hours of playing time, followed by the next LED until the red LED lights to indicate replacement overdue. If the power supply is switched off at any time the accumulated time is stored until the power is restored.

Other time intervals can be used in the device by changing the link positions. Changing A-B to A-C doubles the time period. Changing G-J to G-K or G-L increases the interval by 2½ or 5 respectively while changing it to G-H halves it, although it will not stop on the last count as before. The link adjustments therefore give a range of 100 to 2000 hours per LED on the display — further reductions could be made by using pin 2 or 1 of IC4 as output instead of pin 3, giving ½ or ¼ of the period. In some of these other positions the intervals between the lighting of each LED may not be as

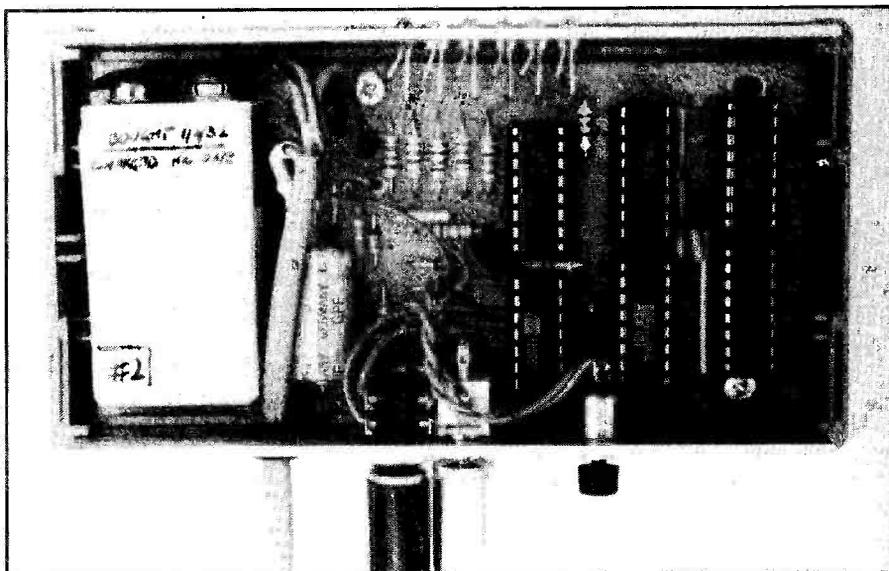

Inside the Stylus Timer. Take care during construction as things are a little cramped.

regular as before (especially G-K). If it is desired to have counting enabled when the light path is obstructed then link D-F should be changed to D-E.

We would like to thank Sonic Sound Audio, who live under our offices and kindly dismantled a rack hi-fi system so we could take our lead photograph.

BUYLINES

None of the electronic bits and pieces should present any problems; try any of the component companies advertising in this issue. The PCB can be obtained from our PCB Service using the order form on page 82; for the Perspex you can try plastics suppliers, arts and crafts shops or DIY emporia.

ETI

MASTER ELECTRONICS NOW!

The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

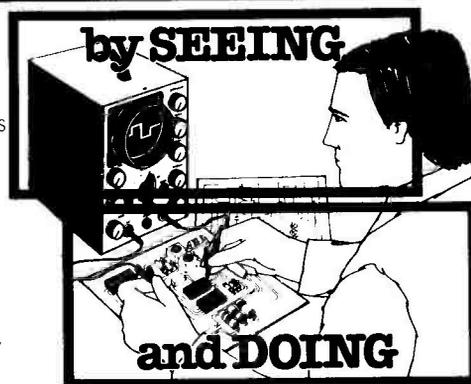

New Job? New Career? New Hobby? Get into Electronics Now!

FREE!
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

ETI/6/821

NAME _____

COURSE IN ELECTRONICS as described above

ADDRESS _____

RADIO AMATEUR LICENCE

OTHER SUBJECTS _____

MICROPROCESSORS

LOGIC COURSE



POST NOW TO

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 7BR

ZX COMPUTING

Britain's Biggest Magazine For The Sinclair User

Over 100 pages of information and programs for the ZX81 and ZX80 user including a 1K Chess routine!

ZX Computing is a quarterly magazine with over 100 pages of programs, articles, hints and tips for the ZX81 and ZX80. We've put the magazine together with just one aim in mind — to make sure you get the most use and enjoyment out of your Sinclair computer.

In the first issue, as well as a host of 1K and 16K programs (the majority dumped directly onto the printer), we've got two articles to help dispel the mysteries of machine code, a chess routine which takes up just 1K, an explanation of PEEK and POKE, an entire section on business uses of the ZX81 (complete with a program to handle the accounts of up to 100 customers) and a construction article which will show you — even if you've never used a soldering iron before — how to cheaply double the memory on your ZX81.

If you're serious about exploring the full potential of your Sinclair computer, and you want an easy-to-understand series of articles to improve and develop your programming skills, then ZX Computing is for you. Issue one is on sale now.

- **Software Reviews** — which programs are the best buy?
- **Business Routines** — put your ZX to work!
- **Expansion Systems** — how good and how much?
- **Machine Code for ZX81** — secrets revealed at last!
- **DIY Memory Upgrade** — cheap way of adding bytes

**POST FREE
SUBSCRIPTION**

SUBSCRIPTION ORDER FORM

Cut out and SEND TO :



**513, LONDON ROAD,
THORNTON HEATH,
SURREY,
CR4 6AR.**

Please use **BLOCK CAPITALS** and include post codes.

Name (Mr/Mrs/Miss)
delete accordingly
Address

Signature

Date

ETI JUNE 82

Please commence my subscription to ZX Computing with the issue.


SUBSCRIPTION RATES (tick as appropriate)

£7.00 for 4 issues
U.K.


£1.75 for a single
copy of the issue

*I am enclosing my (delete as necessary)
Cheque/Postal Order/International Money
Order for £.....
(made payable to ASP Ltd)
OR
Debit my Access/Barclaycard*
(*delete as necessary)*

SC110 FULLY PORTABLE OSCILLOSCOPE

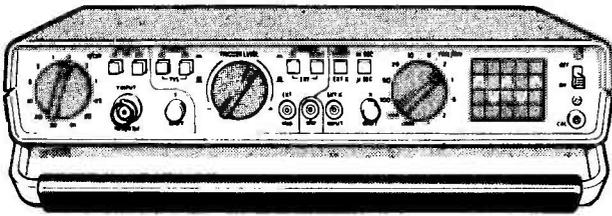

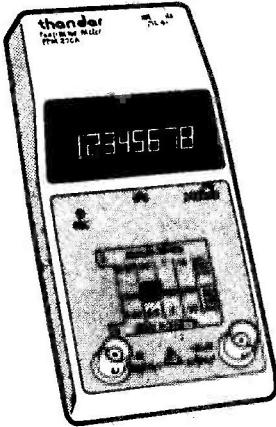The new THANDAR SC110 represents a break through in Oscilloscope development. The SC110 is less than 2" thick and weighs under 21lbs, yet it retains the standard features of a bench oscilloscope.



FULL-SIZED PERFORMANCE

- 10MHz band width
 - 10mV per div. sensitivity
 - Full trigger facilities are provided including bright line and auto, with T.V. line and frame filtering
 - RUNS ON ORDINARY HP11 (four) batteries or rechargeables
 - Basic price - £159 UK Post free
- Optional extras -*
 AC Adaptor £5.69; Rechargeable batteries £8.63; X1 Probe £8.05; X10 Probe £9.20; X1/X10 Switched Probe £10.90; Carry Case £8.86.

PFM200A FREQUENCY METER

- Pocket size ● 8-Digit LED display ● Frequency range 20Hz-200MHz ● Resolution 0.1Hz ● Sensitivity typically 10mV rms
 - Timebase accuracy 2ppm ● Battery life 10 hours ● Frequency: 2 ranges, 4 gate times
 - Price £67.50 UK Post free
- Optional extras -* AC Adaptor £5.69

LARGE SAE FOR COMPLETE LIST

All prices include VAT. Official orders welcome. Mail order only, or callers by prior appointment. Barclaycard/Access welcome. Cash/cheque, etc., with order. Large SAE for complete Thandar list. Government and Educational Establishments official orders welcome.


B.K. ELECTRONICS

37 Whitestone Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY



Tel: Southend 627572

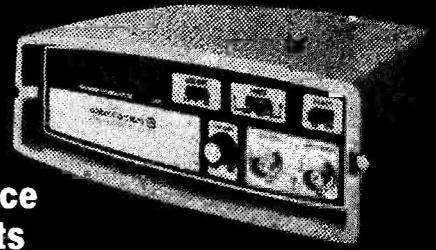An entire range of low-cost high-performance instruments



sabtronics

'Making Performance Affordable'

*2010A	3½-Digit L.E.D. Bench DMM	5020A	1Hz-200KHz Function Generator
*2015A	3½-Digit L.C.D. Bench DMM	*8110A	100MHz 8-Digit Frequency Meter
2020	3½-Digit L.E.D. Bench DMM with Microcomputer Interface	*8610A	600MHz 8-Digit Frequency Meter
2033	3½-Digit L.C.D. Hand DMM	*8610B	600MHz 9-Digit Frequency Meter
*2035A	3½-Digit L.C.D. Hand DMM with Temp.	8000B	1GHz 9-Digit Frequency Meter
*2037A	3½-Digit L.C.D. Hand DMM with Temp.	8700	10MHz Universal Frequency Counter/Timer
LP-10	10MHz Logic Probe	PSC-65	600MHz Prescaler
		9005	5MHz Single Trace Oscilloscope

* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from:
BLACK STAR LTD.,
 9a Crown Street, St. Ives,
 Cambs. PE17 4EB
 Tel: (0480) 62440. Telex 32339



Now our name means more, than ever before.

If the name BICC-Vero sounds only half familiar, that's not the only difference you're going to notice.

Because not only have we added to our name we've also added to our technology. Building upon our well established industrial product range and incorporating the very latest ideas and techniques to ensure that you too are working at a state-of-the-art standard.

But you will of course still recognise the old favourites. Products like Veroboard, which pioneered in so many ways, today's thriving pastime of electronics.


Bigger means better in other respects. Being part of the giant BICC-Vero Electronics Group ensures that we're a major force in electronics technology. Our R and D scope is enlarged, and our supply and distribution facilities improved.

And because we're professionals we appreciate the very real professionalism of the hobbyist market - and service it accordingly.

Yes, we're sure you'll notice the difference. As well as that pleasantly familiar personal touch.

BICC-VERO ELECTRONICS LTD.

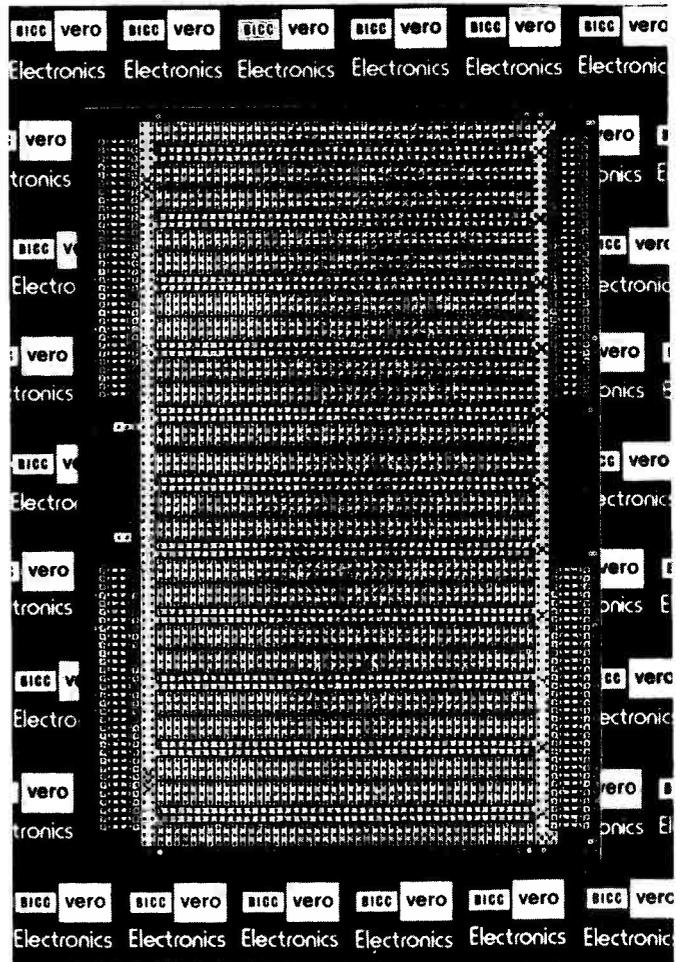Industrial Estate, Chandlers Ford,
 Eastleigh, Hampshire SO5 3ZR.
 Tel: Chandlers Ford (04215) 62829.



SALE ELECTRONIC GAMES

NOW £40 OFF



ATARI T.V. GAME

THE GAME WITH 50 CARTRIDGES
R.R.P. £129.95 (inc. VAT)
OUR PRICE
£78.22 + VAT
(= £89.95 inc. VAT)

The Atari is supplied with a free mains adaptor, a pair of paddles, a pair of joysticks and a combat cartridge and is the most popular television game on the market and has a range of over 40 different cartridges. In addition to the standard Atari range we also now stock the new Activision cartridges which are currently on special offer reduced from £18.95 to **£16.95 inc. VAT**

ATARI CARTRIDGES

20% OFF R.R.P.
Atari Soccer £29.95
NOW £23.95
Activision Dragster £18.95
NOW £14.95
Activision Boxing £18.95
NOW £14.95

ATARI OWNERS CLUB — Why not join our **FREE** Silica Atari Owners Club and receive our bi-monthly newsletter with special offers and details of the latest new cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.

MATTEL INTELLIVISION



NOW £50 OFF

THE ULTIMATE T.V. GAME
R.R.P. £229.95 (inc. VAT)

OUR PRICE
£156.48 + VAT
(£179.95 inc. VAT)

6 NEW CARTRIDGES JUST RELEASED
**ASTROSMASH * SNAFU * BOWLING
SPACE ARMADA * BOXING
TRIPLE ACTION**

All 19 current cartridges + the six new ones above now retail at £19.95 — Silica special offer price **£17.95 inc VAT**

The Mattel Intellivision is the most advanced T.V. game in the world with a range of over 25 different cartridges all at our special offer price of £17.95. This game uses a 16-bit microprocessor giving 16 colours and three-part harmony sound. The picture quality is incredible with 3D effects and realistic animation. An add-on keyboard will be available in the Spring 1982 to convert the Mattel into a full home computer with 16K RAM which will be fully expandable and programmable in Microsoft Basic. Other accessories will be added later in the year. The normal price of the Intellivision + free soccer cartridge is £229.95 but our special offer price is £179.95 inc. VAT saving you £50.00.

MATTEL OWNERS CLUB — Why not join our Mattel Owners Club and receive our regular newsletters containing details of all the latest cartridge releases. Telephone us with your name and addresses and we will add your name to our computer mailing list.


FREE 16 PAGE CARTRIDGE CATALOGUE — If you are interested in owning a Mattel, we now have available a 16 page catalogue describing the latest six cartridges to be released, as well as a new Mattel colour leaflet with brief descriptions of all 25 cartridges. Telephone us for further details.

T.V. GAME CARTRIDGES

We specialise in the whole range of T.V. games and sell cartridges for the following games: **ATARI * MATTEL * ACETRONIC * PHILIPS * DATABASE * ROWTRON * INTERTON * TELENG**. Let us know if you own any of these games and we will let you have details of the range of cartridges available.

Attention INTERTON & ACETRONIC owners we have over 75 assorted used cartridges in stock all with 1 year guarantee — **SPECIAL OFFER £8.95 each**

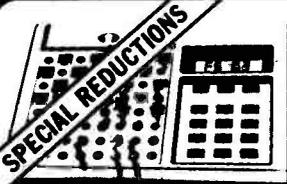We also have a number of secondhand games and cartridges.



SPECIAL REDUCTIONS

ELECTRONIC CHESS

Liquid crystal battery chess computer with 100 200 hrs battery life and two levels of play. Comes with separate chess board and pieces.
R.R.P. £24.95
SALE PRICE
£19.95
(inc. VAT)

GRADUATE CHESS

A de luxe version of the electronic chess set with integral chess board. The ideal portable chess set — see illustration.
R.R.P. £29.95
NOW
£29.95
INC VAT

FIDELITY MINI-SENSORY CHESS COMPUTER

The very first chess computer of its price to offer a portable computer with integral sensory board. Battery (6-8 hrs) or mains operated. This is a modular game and additional plug-in modules are planned for 1982 for advanced chess, popular openings, greatest master games, draughts and reversi.

MINI-SENSORY COMPUTER WITH STANDARD CHESS MODULE WAS £54.50 **NOW £49.95 INC VAT**

Silica Shop are one of the country's leading specialists in Chess Computers and now stock a range of more than 20 Chess Computers, including Challenger 7/10/Voice, Sensory 8 and Sensory Voice, Diplomat, System 3, Morphy, Great Game Machine, Voice Champion, and the new Silicos Mark V.

HAND-HELD GAMES EARTH INVADERS

These invaders are a breed of creature hitherto unknown to man. They cannot be killed by traditional methods — they must be buried. The battle is conducted in a maze where squads of aliens chase home troops. The only way of eliminating them is by digging holes and burying them.
R.R.P. £26.95 **NOW £18.95 inc. VAT**



NOW £8 OFF
NOW £10 OFF

PAC MAN 2

Pac Man 2 is based on the latest pub game. It is a two-colour game of strategy, tactical pursuit and destruction pitting Pac Man against the large Ghosts. The object of the game is for Pac Man to attain as high a score as possible by capturing and destroying Ghosts, Bugs and Energy dots without being himself destroyed by the Ghosts. Pac Man 2 incorporates the most modern and complex status displays ever produced and is now on release for the first in the UK offering an ideal present.

R.R.P. £34.95 **NOW £24.95 inc. VAT**

SPACE INVADERS

Based on one of the most popular arcade games, Space Invader™ packs in lots of action with multi-shaped, brilliant LED vessels, including attack ships, bombs, defenders, missile rockets and a beam force cannon, plus exciting electronic sound effects. The attack ships attempt to bomb the ground defenders as they are moving. You manoeuvre the missile rockets — avoiding alien bombs — and destroy the invader force as quickly as you can. Progressive degree of difficulty includes automatic digital scoring. For ages 6 to adult.

R.R.P. £24.95 **NOW £16.95 inc. VAT**

LESS THAN 1/2 PRICE
COLOUR CARTRIDGE T.V. GAME
Semi Programmable TV game
4 cartridges
mains transformer
R.R.P. £73
SALE PRICE £29.50 inc. VAT

SEMP PURCHASE PRICE NOW
BACKGAMMON COMPUTER
Silica stock a wide range of Backgammon computers from £28.95 upwards. Special offers now available on Gammomaster.
NOW £48.95 inc. VAT

CALL JOTTER — THE AFFORDABLE ANSWER

The Post Office certified telephone answering machine



1/2 THE PRICE OF COMPARABLE MACHINES

"Sorry darling, I will be late home — Love John"
The Call Jotter 1 brings the affordable answer at the amazing price of £69 for £99 for the Call Jotter 2 with built-in remote recall facilities. These amazing telephone answering machines are Post Office certified and guaranteed for one year. They make a thoughtful gift for home or business use.


Call Jotter 3 illustrated TWINTAPE £138 **NOW £69.00 inc. VAT**

RADOFIN TELETEXT

Plug the adaptor into the aerial socket of your colour TV and receive the CELEK and ORACLE television information services.

THIS NEW MODEL INCORPORATES
*Double height character facility *True PAL Colour
*Meets latest BBC & IBA broadcast specifications
*Push button channel change *Unnecessary to remove the unit to watch normal TV programmes
*Gold plated circuit board for reliability
ADD-ON ADAPTOR
WAS £199 inc. VAT
SALE PRICE £124 inc. VAT


FOR FREE BROCHURES — TEL: 01-301 1111

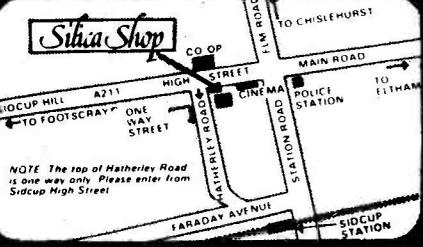

For free illustrated brochure and reviews on our range of electronic games, please telephone 01-301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/BARCAYCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48 hour delivery service available.

- CALLERS WELCOME Demonstrations daily at our Sidcup shop open from 9am-6pm (Monday-Saturday (Early Closing Thursday 1pm. Late Opening Friday 8pm).
- 2 YEAR GUARANTEE All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year guarantee.
- COMPETITIVE PRICES We are never knowingly undersold.
- HELPFUL ADVICE Available on the suitability of each machine.
- CREDIT FACILITIES Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
- PART EXCHANGE SCHEME Available on second hand machines.
- CREDIT CARDS WELCOME Access, Barclaycard, Diners Club, American Express.

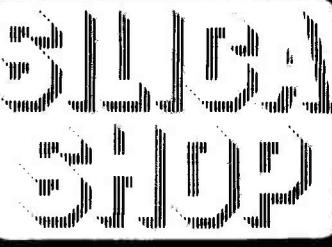SILICA SHOP LIMITED ET10682
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX
Telephone: 01-301 1111 or 01-309 1111




150 W MOSFET AMPLIFIER

Employing MOSFETs, this power amplifier features a 'no compromise' design from Dave Tilbrook and is rated to deliver 150 W RMS maximum; it features extremely low harmonic, transient and intermodulation distortion. This is achieved by overcoming the many basic problems encountered in the use of MOSFETs for audio amplification.

The objective of this project is to provide a power amplifier module of the highest possible performance. Ideally the power amp should produce an amplified version of its input signal and contribute no sound of its own. In order to design a practical amplifier that will come as close as possible to this ideal, it is necessary to 'define' limits on the input signal characteristic and then ensure that the power amp exceeds these limits.

The problem of amplitude overload cannot be eliminated, since no practical power amplifier has access to infinite supply voltage. In order to overcome this problem, the ETI-5000 module has been designed to exceed in excess of ± 50 V rails, giving it a conservative power rating of 100 W RMS into 8 ohms. The output stage has been designed so that the MOSFETs will not operate outside their safe operating area on any load in which the effective series resistance does not drop excessively below 8 ohms. Increasing the supply rails will increase the audio power output (up to 150 W RMS max.) but for normal use, we recommend sticking to ± 55 V.

Similarly, since no power amp has an infinite slew rate or infinite frequency response, the input signal has been limited by a passive input filter. It can be easily demonstrated by experiment that the introduction of a passive filter that does not excessively affect the frequency response within the audio passband will not affect the sound of the input signal. This filter will define a maximum possible input slope. It is therefore only necessary to design the amplifier with a slew rate that exceeds this by a sufficient margin to ensure freedom from slew-induced distortion. Since the amplifier is operated below its slew rate limit, the

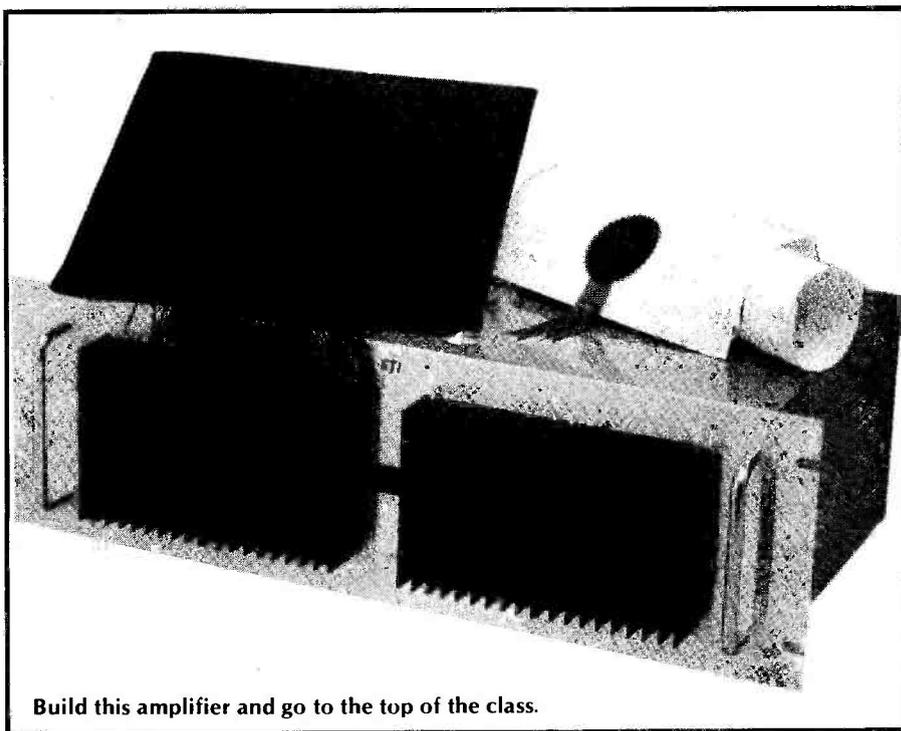

Build this amplifier and go to the top of the class.


application of negative feedback will decrease distortion produced as a result of the signal slope approaching the slew rate (TIM).

Pair Difference

Differential pairs have been used throughout the design to form not only the input stage but also the voltage gain stage. This ensures that the distortion characteristics of the input and voltage gain stages are low enough so that the open loop characteristics of the amplifier will be determined by the output stage. The improved frequency and phase linearity of the differential pair make it considerably easier to ensure that the amplifier meets the

Nyquist stability criterion. Another advantage of the differential pair is its relatively high supply rejection, a parameter which is often not given sufficient attention in power amp design.

Careful control of the feedback loop and the use of a passive filter/load on the output of the module, coupled with the design points mentioned above, have yielded an amplifier with particularly low dynamic distortion characteristics. An amplifier that has been designed with these objectives in mind will automatically have low THD and TID figures. The ETI-5000 is no exception, with a THD at 1 kHz and 10 W RMS of less than 0.001%, rising

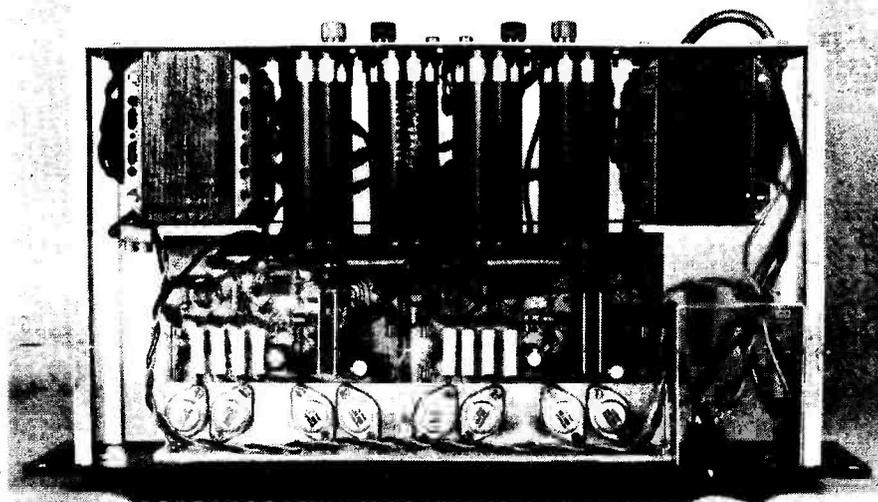

A general view showing the internal layout of the amplifier. Toroidal transformers can be used instead.

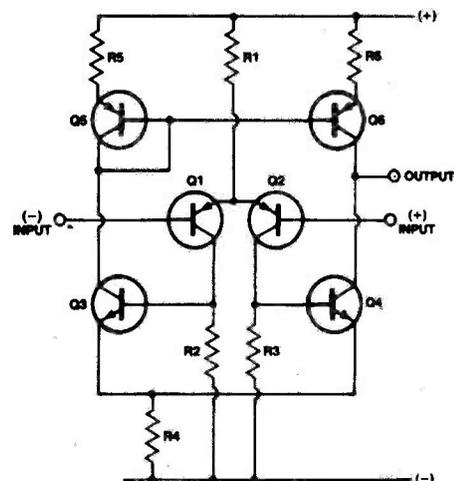


Fig. 1 The basic voltage gain stage of the ETI-5000 MOSFET amplifier.

impression of being 'over smooth', ie the amplifier on first listening sounds clean and unobtrusive. Further listening test reveals, however, that these amplifiers lack detail, and complex sounds like a symphony orchestra tend to become a single mass of sound rather than being rendered as single instruments. The ETI-5000 does not suffer from this problem!

Carefully Does It

Particular care has been taken to minimise slew-rate limiting and harmonic distortions. An inspection of the 'How It Works' section will reveal the techniques employed.

Follow the suggested constructional method and no problems will be encountered.

Construction — Module

The construction of the power amp module is not difficult since all the components are mounted on a single board. Since the design employs a fairly large amount of negative feedback, the board pattern is a critical factor in attaining the maximum theoretical performance. It would be virtually impossible to achieve the same performance if the board pattern were altered, without recourse to a distortion analyser with a sensitivity of at least 0.005% and a very good spectrum analyser. The board pattern shown ensures freedom from earth path interaction and therefore does not degrade the distortion performance of the design.

Commence construction by soldering all the resistors onto the circuit board. The 0R22 (0.22 ohm), 5 W source resistors in the output stage get warm if the amplifier is operated for extended periods at high power.

SPECIFICATIONS

Power output

100 W,RMS into 8 ohms
(± 55 V supply)
(up to 150 W with suitable PSU)

Frequency response

8 Hz to 20 kHz, +0 -0.4 dB
2.8 Hz to 65 kHz, +0 -3 dB
NOTE: These figures are determined solely by passive filters.

Input sensitivity

1 V RMS for 100 W output

Hum

-100 dB below full output (flat)

Noise

-116 dB below full output
(full, 20 kHz bandwidth)

2nd harmonic distortion

<0.001% at 1 kHz
(0.0007% on prototypes)
at 100 W output using a
± 56 V supply rated at 4 A
continuous
<0.003% at 10 kHz and 100 W

3rd harmonic distortion

<0.0003% for all frequencies less
than 10 kHz and all powers below
clipping.

Total harmonic distortion

Determined by 2nd harmonic
distortion (see above).

Intermodulation distortion

<0.003% at 100 W
(50 Hz and 7 kHz mixed 4:1)

Stability

Unconditional

slightly to around 0.003% at 10 kHz (top end distortion figures are a function of bias current). It should be remembered, however, that obtaining low THD figures should not be the prime objective of a good power amplifier design, but results from the reduction of dynamic distortion mechanisms.

Tested And Trying?

The module has been tested exhaustively and all prototypes have performed with negligible differences.

When attempting to measure distortion figures as low as these, great care must be taken with the earthing arrangement to the test equipment. The

amplifier module will give its lowest distortion figures only when measured with respect to the correct earth. It may be necessary to remove the connection between mains earth and signal earth inside some distortion analysers. This problem will not arise when the amplifier is connected to a loudspeaker. This condition is not unique to the 5000 module, but will occur whenever an alternative earth path is provided to the output signal earth.

The sound is clean with no sign of the aggressive high frequency performance common to many transistor amplifiers. There are some amplifiers that give the subjective

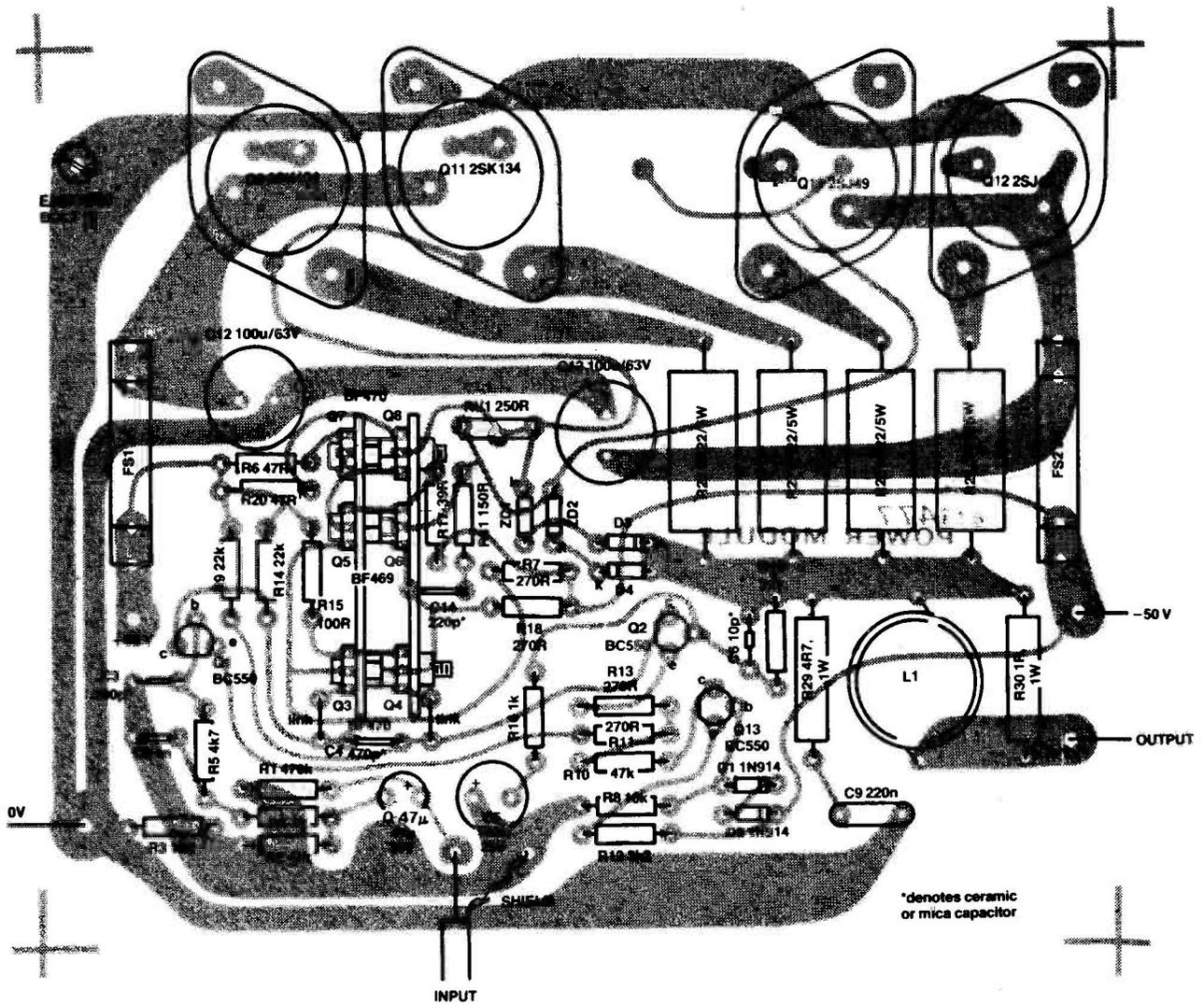


Fig. 2 Component overlay of the MOSFET amp module.

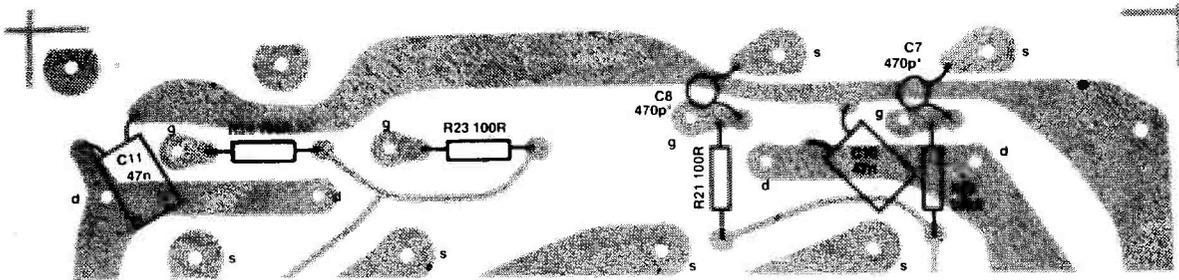


Fig. 3. This overlay shows the components which are mounted directly on the copper side of the PCB.

They should never get hot enough to burn the circuit board, since any fault capable of causing this much power dissipation should blow the supply fuses first. Nevertheless, it is good construction practice to space these resistors a few millimeters off the surface of the board. The 4.7 ohm, 1 W resistor R29 should *definitely* be spaced off the board since it will overheat if a fault condition should cause oscillation of the amplifier at high frequencies. Do not mount the four 100 ohm resistors R21, R22, R23, R24 at this stage. These are mounted on the rear of the circuit

board and are best left until after the MOSFETs are mounted.

Solder the four fuse clips into the board next. Now mount all of the capacitors, with the exception of C7, 8, 10, and 11. Once again, these mount on the rear of the board. Make sure the electrolytic capacitors C1, C5, C12 and C13 are inserted with the correct orientation as these are polarised components. Mount the 1N914s and zener diodes, taking care to orient them correctly. Solder the trimpot RV1 into place and then the small-signal transistors, Q1, Q2 and Q13.

Next step is to mount the six voltage amp transistors, Q3 through Q8. These are situated on the board in two parallel rows, each row with three transistors. In the prototype modules, the heatsinks were constructed from two pieces of aluminium, as can be seen from the photographs. The transistors are mounted using 6BA bolts, each passing through a pair of transistors. This forms a very strong assembly which can then be soldered onto the board. Insulating mica or plastic washers should be used between the metal side of the

transistors and the heatsink strip, using a small quantity of heatsink compound between each mating surface. When this transistor-heatsink assembly is completed, but before soldering it into the circuit board, check that each transistor is effectively insulated from

the heatsink. Using a multimeter on the resistance range, check for shorts between the centre lead (collector) of each transistor and the heatsink strip. Note that the bolts through the six transistors are automatically insulated from the metal rear of the transistor by the plastic body of the device so no additional insulation of the bolts should be necessary.

Before mounting the MOSFET output devices it is necessary to make the heatsink bracket. This is cut from a suitable aluminium extrusion. The board has been designed to suit extrusions with one of the sides at least 40 mm wide. The transistor mounting holes have been placed so that the heatsink brackets used in the ETI 300 W modules (April '80) are compatible, although there will be some unused holes.

The output assembly should now be checked for shorts. Remove the earthing bolt first (see overlay). The resistance between the case of each MOSFET and the bracket should be checked with a multimeter. If any device shows a short to the bracket it should be disassembled and the short found. Usually it is necessary to replace the TO-3 insulating washer as most faults of this type are the result of small metal burrs cutting through the washer when mounting the device.

Once the MOSFETs are mounted, the last passive components — resistors R21, R22, R23 and R24 plus capacitors C7, C8, C10 and C11 can be mounted on the rear of the circuit board. These are positioned on the rear of the board so that lead length is kept as short as possible. Cut the leads just short enough to mount the components in place.

Set-up Procedure

The recommended supply voltage for the modules is around ± 55 V. With this voltage and reasonable supply regulation, the module will deliver around 100 W RMS into a nominal 8 ohm load.

First, re-check that the output devices are not shorted to the heatsink bracket. This is best done with the earthing bolt removed as mentioned earlier. If no shorts are found, replace the earthing bolt.

Do the same check for shorts between the six voltage amp transistor collectors and their heatsinks.

Check the polarity of all polarised components. It is often difficult to tell one end from the other on diodes since the markings are easily rubbed off. If in doubt, check these with a multimeter. Wind the wiper of the trimpot RV1 fully *counterclockwise* (least resistance). This ensures no bias is applied to the output stage. Now, remove the fuses from the board if they have been fitted and replace them with 10 ohm, $\frac{1}{2}$ W resistors.

The module can now be connected to a power supply.

Make sure that the power supply connections are sound, with good solder joints. If you have access to a current limited bench supply it is best to connect the module to this for the set-up and initial test. If you can do this, set the current limit to around 200 mA. *Do not* connect a load to the output of the module at this stage.

If the power is now turned on, the current through the two 10 ohm resistors replacing the fuses should be low. If these resistors start to smoke, this indicates a fault condition — turn the power off immediately.

PARTS LIST

Resistors (all $\frac{1}{2}$ W, 5%)	
R1	470k
R2,11	47k
R3	10R
R4,16	1k0
R5	4k7
R6,20	47R
R7,10,13,18	270R
R8	10k
R9,14,19	22k
R12	3k3
R15,21-24	100R
R17	39R
R25-28	0R22, 5 W
R29	4R7, 1 W
R30	1R0, 1 W
R31	150R

Potentiometer	
RV1	250R vertical trimpot

Capacitors	
C1	470n, 25 V PCB electrolytic
C2	1n0 polyester
C3	330p ceramic or mica
C4,7,8	470p ceramic or mica
C5	100u 25 V PCB electrolytic
C6	10p ceramic or mica
C9	220n polyester
C10,11	47n polyester
C12,13	100u 63 V PCB electrolytic
C14	220p ceramic or mica

Semiconductors	
Q1,2,13	BC550
Q3,4,7,8	BF470
Q5,6	BF469
Q9,10	2SK134
Q11,12	2SJ49
D1,2,3,4	1N914 or similar
ZD1,ZD2	12 V, 400 mW zener

Miscellaneous
PCB; four fuse clips; two 3 A fuses; one plastic bobbin or similar former, 15 mm diameter; one metre of 0.8 mm dia. enamelled copper wire; two strips of 20g aluminium, each 15 mm wide by 47 mm long (for voltage amp heatsink); heatsinks, case to suit.

Semiconductors	
BR1	200 V, 35 A bridge rectifier

Capacitors	
C1,2,3,4	10,000 uF, 80 V can electrolytics
C5,6,7,8	100n polyester
C9	470n polyester

Transformers	
T1,T2	two x 35 V secondaries

Miscellaneous
SW1... illuminated rocker switch, 240 V AC rated; 1 off 2A fuse and fuseholder, 1 off 3-pin DIN socket; 2 off 2-way plastic terminal blocks; 2 off phono sockets; 2 off red and 2 off black heavy duty screw terminals; clamp grommet and sundry rubber grommets; hookup wire; nuts, bolts etc; heatsink/front panel, metalwork etc.

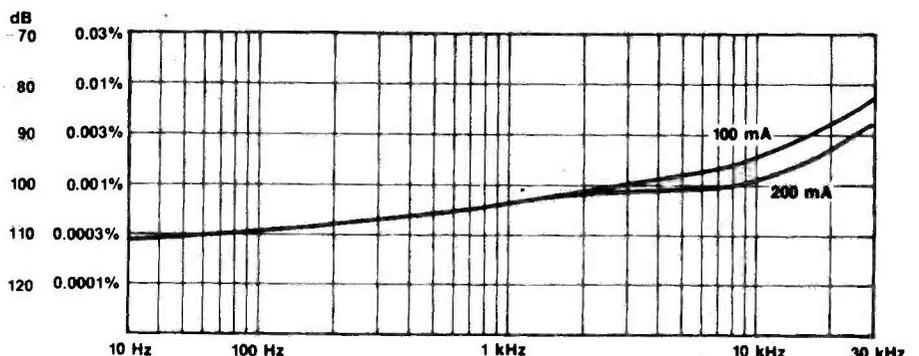


Fig. 4 This graph shows the measured distortion versus frequency for two values of quiescent current in the output stage.

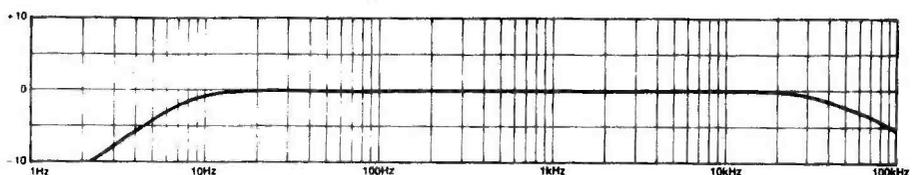


Fig. 5 The measured frequency response of the amplifier (single module). Roll-off points are defined by the input filter (low end) and output amplifier compensation network (high end).

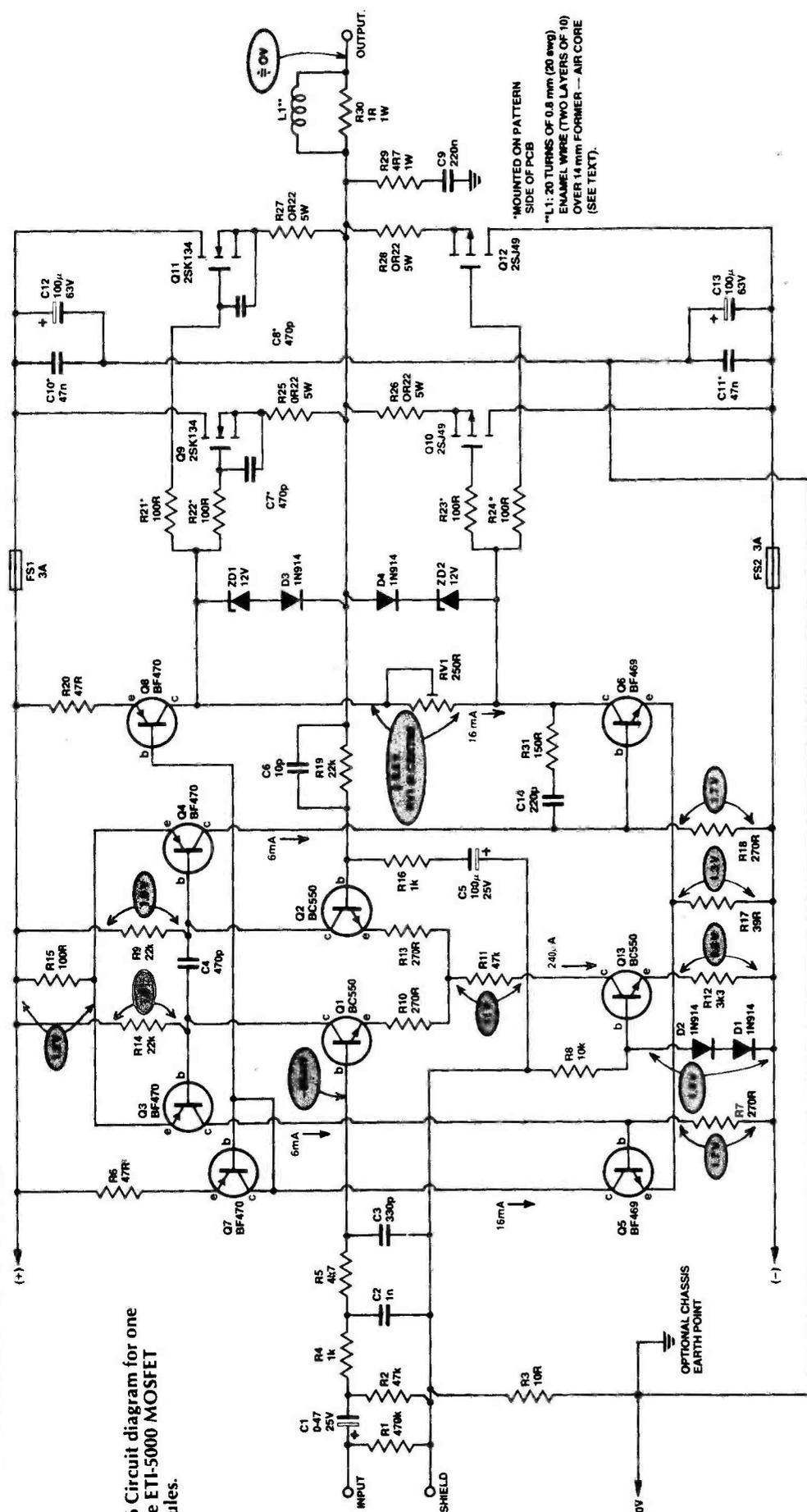


Fig. 6 Circuit diagram for one of the ETI-5000 MOSFET modules.

BUYLINES

The MOSFETs and other transistors used in this amplifier can be obtained from Pantechnic who advertise in ETI. If necessary, the 2SK (35/2S)50 complementary MOSFET pair could be substituted (these have a higher breakdown voltage). Pantechnic will also supply the can electrolytics for the power supply (at a cost of £4.75 each including VAT, p&p 40p extra). Various companies supply suitable transformers — browse through the ads in this issue to find them. Our PCB Service will be selling the boards for this project as usual; the 19" rack that we used for a case is available at a reasonable price from Relay-A-Quip Products, Moat Lodge, Stock Chase, Malden, Essex CM9 7AA.

The 0V6 drop of Q3 and Q4, will cause a voltage drop of 1V2 across resistor R15, causing a current of 12 mA to flow in this resistor. This current is shared by Q3 and Q4 and causes a 1V7 drop across resistors R7 and R18. Once again, the effective input impedance of Q5 and Q6 is in parallel with the resistors, but in this case the value of R7, and R18 is very much lower than the base impedances of Q5 and Q6, so this effect can be ignored in a DC analysis like this. The voltage across R7 and R18 minus the 0V6 drop of Q5 and Q6 will cause 1V3 to be dropped across 32 mA through the resistor. Again Q5 and Q6 form a differential pair, and this current is shared equally by the two transistors. The load for these devices is formed by a current mirror, Q7-Q8, that ensures the current through Q5 and Q6 will remain the same. Transistors Q4 and Q5 therefore form the main voltage gain section of the amplifier and have a typical emitter-collector current of 16 mA. The preset RV1 will drop nominally 1V across it when the output stage quiescent current has been set.

Diodes D3, D4 and zeners ZD1, ZD2 protect the MOSFET output devices from being overdriven, as described in the text. The RC-RL network on the output ensures that the amplifier has a correct load at all frequencies thereby eliminating the problem of oscillation that could otherwise result.

This very brief DC analysis of the circuit is intended to help the constructor rationalise the voltages quoted on the circuit diagram. The voltages are the result of averaging voltage measurements on a number of prototypes, and slight deviations from these should be expected.

The input signal is fed to three RC filter sections formed by C1/R2, R4/C2 and R5/C3. The C1/R2 filter defines the low end 3 dB point of the amplifier at around 7 Hz, with an attenuation rate below this frequency of 6 dB/octave. The two sections R4/C2 and R5/C3 both have 3 dB points of around 30 kHz defining the top end response of the amplifier. This filter limits the maximum signal slope to less than the slowest stage in the amplifier. It also provides protection against RF interference.

Transistor Q13 and the associated components R8, R12 and D1, D2 form a constant current source (or sink), maintaining a final DC current through the differential pair Q1, Q2 of around 240 mA. Under no-signal conditions this current is shared equally between Q1 and Q2. The resistances of R9 and R14 are in parallel with the equivalent input resistances of the transistors Q3, Q4, decreasing the effective load resistances of the differential pair to around 15k. The voltage drop across R9 and R14, should therefore be 1V8 approximately. This voltage, minus

When designing amplifiers intended, as this project is, for extremely low distortion, it is essential that all stages in the amplifier be designed for as low a distortion as possible. When the negative feedback is applied, truly excellent performance can be expected.

In any practical power amplifier design the bulk of the open loop gain is provided by the main voltage gain stage. The difference amplifier will generally provide some voltage gain but its main objective is to provide a linear difference signal with respect to its two inputs. In some power amps the output stage is a common drain or source follower MOSFET design and consequently has a voltage gain slightly less than unity.

An analysis of the distortion characteristics of the differential pair reveals that it is significantly better than a single transistor operated in common emitter configuration. If we assume that the distortion in a bipolar transistor is due exclusively to the exponential relationship between collector current and base-emitter voltage, the distortion generated by a differential pair and a single transistor can be calculated by techniques of Fourier analysis.

As well as having low distortion itself, a differential voltage amplifier will enable both outputs of the input differential pair to be used, thus giving a balanced output. This overcomes the problem of asymmetrical loading of the input pair by the input impedance of a single-ended voltage amplifier, a problem that would otherwise lead to increased distortion in the first stage.

Figure 1 is a circuit diagram of the voltage gain stage developed for this project. The stage is really a double differential pair with 'current mirror' load. Transistors Q1 and Q2 form the first differential pair with R1 as the common emitter resistor. The output of the Q1, Q2 pair provides a differential drive to Q3 and Q4. The latter pair, however, must be converted into a single-ended stage suitable for driving the output stage. This is the job of the current mirror formed by Q5, Q6, R5 and R6. Transistor Q5 has its base-collector junction shorted and therefore acts like a diode, but with the same characteristics as the base-emitter junction of Q6. The bases of Q5 and Q6 are connected together and therefore the voltage on the bases is identical. Since Q5 forms a 'mirror image' of the base-emitter junction of Q6, the voltage drop across the two transistors will be almost identical, depending on how well the two transistors are matched. Since the voltage on the bases and the voltage drop across the base-emitter junctions is almost identical,

the voltage on the bottoms of R5 and R6 will be almost identical. If these two resistors are made the same value, the current through each resistor, and therefore the current in the collectors of Q3 and Q4 will be identical. This ensures the Q3, Q4 pair will operate symmetrically, even when a single-ended load is attached to the pair.

Furthermore, since the collector of Q3 is connected directly to the base of Q6, the transistors Q6 and Q4 combine to form a push-pull pair with very high gain.

In order to achieve good transient performance when driving the slightly capacitive load of the output stage it is necessary to run a fairly large amount of current through this stage, especially the final differential pair and the associated current mirror. In the 5000 there is approximately 16 mA through these transistors, and the average power dissipation is therefore around 0.8W.

These transistors will run fairly hot, approximately 60°C on the small heatsink shown, but the transistors are well inside their maximum ratings. The result is a voltage amplifier stage of exceptional linearity and very high gain. Coupled with a well-designed input differential amplifier and a good output stage, the phase linearity produced by this voltage stage is excellent, and makes it an easy matter to ensure total stability of the amplifier.

Since the output of the voltage gain stage has been designed to have sufficiently low output impedance to drive the gates of two MOSFETs in parallel, the output stage consists simply of the MOSFETs themselves. If a preset pot is inserted between the collectors of Q6 and Q4 in the voltage amplifier stage of Fig. 1 the voltage across this preset can be used as the bias voltage for the output stage. This is shown in the circuit diagram.

The gates of the output devices are connected to either side of the preset via resistors R21, R22, R23 and R24. As mentioned earlier, these resistors increase the time constant associated with the MOSFET gate capacitance, reducing the frequency response of the output stage slightly but ensuring stability.

Both N-channel and P-channel MOSFETs are used in this project. The important difference is the value of gate-source capacitance for the two devices. If this is not equalised the presence of asymmetrical reactance in the output stage makes it almost impossible to ensure stable operation. The only cure is to decrease the open-loop gain of the whole amplifier, so that the negative feedback is reduced, and accept the consequent increase in distortion.

The most common method employed to achieve this is to increase the value of the emitter resistors in the input stage. This reduces the voltage gain of the input stage, at the same time increasing its small-signal bandwidth. Consequently, in a power amplifier employing MOSFETs in the output stage, the relatively small amount of negative feedback available will not be able to linearise the transfer characteristics of the output devices, and the result is an amplifier with only mediocre performance.

The problem of the asymmetry of the gate-source capacitance is cured by the addition of the capacitors C7 and C8 shown in the circuit diagram. With these capacitors in the circuit and with the 100R resistors R21, R22, R23 and R24, the only other component required to ensure total stability of the output stage is the power RLC combination formed by R29, C9, R30, L1 and the supply bypass capacitors C10, T1, T2 and T3.

When a square wave, for example, is fed into a purely capacitive load, the output stage will virtually see a short circuit since the high frequency (> 100 kHz) Fourier components of the sine wave will see very little impedance in the capacitive load.

The inductor L1 ensures that this does not happen by inserting a reactance that increases at high frequencies. The resistor R30 is placed in parallel with the inductor so the top end frequency response of the amplifier is not unduly affected.

The other two components of this network, R29 and C9, ensure that the amplifier always has a load at high frequencies. Without this 4R7 load the gain of the output stage is slightly greater than unity, due to the presence of positive feedback caused by the effective capacitance around the output devices, and this causes oscillation.

The 220nF capacitor is necessary since the resistor must be removed from the circuit for frequencies inside the audio passband or the high power dissipation in the resistor would destroy it instantly.

Resistors R25, R26, R27 and R28 provide slight emitter degeneration to the output devices. This helps to linearise the output transfer characteristic of the amplifier and thereby assists in ensuring stability of the output stage.

The final components needed to ensure stability of the output stage are the supply bypass capacitors C10, C11, C12 and C13. Capacitors C12 and C13 are 100uF electrolytics that provide general supply bypassing to frequencies inside the audio passband, but have little effect at 1 MHz, where the MOSFET would tend to oscillate.

For this reason capacitors C10 and C11 have been included also. These capacitors must be positioned very near the output

devices, since the resistance of only several centimetres of track will greatly decrease their effectiveness.

In the 5000 these capacitors are mounted on the rear of the circuit board with one lead soldered directly to the drains of the output devices.

The gate resistors R21, R22, R23 and R24 and the gate power capacitors C7 and C8 are also mounted on the rear of the circuit board, again soldered directly to the MOSFETs.

The remaining components in the output stage are the zener diodes ZD1 and ZD2 and their associated diodes D3 and D4, and the bias preset RV1. The maximum gate to source voltage of these MOSFETs is 14 V; if this voltage is exceeded the MOSFET can be destroyed, so the zeners and diodes are placed between the gate and the output of the power amp to prevent the drive voltage ever becoming more than 12V6 above or below the output voltage.

This condition would mainly occur when the output is driving a short circuit or a capacitance load big enough to look like a short circuit. Under these conditions the output voltage cannot deviate much from 0 V since it is shorted to 0 V, and the negative feedback loop will drive the output of the voltage gain stage into clipping in an attempt to compensate for the error.

The gate to source voltage is now around ± 50 V, well above the absolute maximum voltage for the output devices. The diodes D3 and D4 are necessary to prevent the zeners from shorting out the gate drive under normal operating conditions.

The current flowing through the preset RV1 will give rise to a voltage drop across the preset that can be varied by adjusting RV1; this acts as the bias voltage for the output devices. If the diodes D3 and D4 are not present, the gates of Q10 and Q12 for example can never go more than 0V6 above the output voltage, due to the 0V6 forward voltage drop of ZD2. Since the voltage drop across RV1 is around 1 V, the drive voltage to the gates of Q9 and Q11 can never go higher than the sum of these two voltages, ie above the output voltage, and this limits drive to the MOSFET. The same occurs to negative-going signals due to the 0V6 forward turn-on voltage of ZD1.

The combination of all these techniques yields an output stage that is totally free of instability and with a bandwidth of a round 5 MHz! Furthermore, the transfer characteristics and phase response of the output stage are predictable, making it relatively easy to ensure stability of the overall feedback loop.

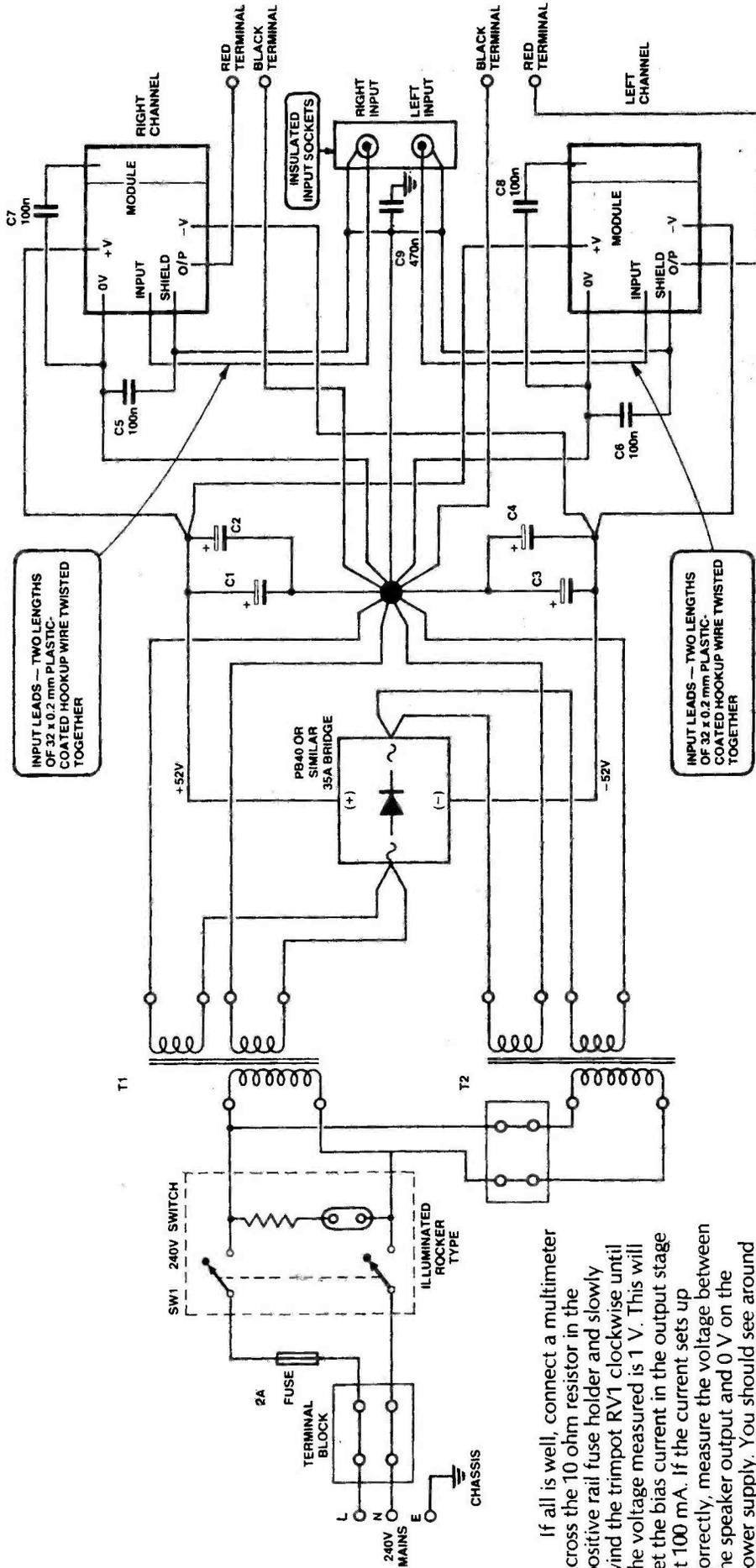


Fig. 7 Interwiring diagram for the complete (stereo) amplifier.

insignificant (ie around the noise level), so independent supplies offer no real advantage. On the other hand the use of two power transformers in a single power supply yields a supply capable of more than 100 V at over 7 A

continuous. The transformer we used has two independent 35 V windings. These are connected in parallel to produce a single 35 V RMS winding capable of supplying 5 A RMS. It is unimportant whether these are toroidal or ordinary types — use whatever you

can get.

If the same type of transformer cannot be obtained locally, then any type which can supply 35 V at 5 A is compatible.

One terminal of each transformer is connected to the bridge rectifier, a 35 A type. The filtering for the power supply is done with two 8000uF capacitors to form a total of 16 000uF across each half of the DC supply rails. The resulting supply voltage should be approximately ± 52 V, unloaded. At


full power this will drop to around ± 50 V. With a 10 V drop across the output devices the peak signal voltage before clipping is around 40 V, which gives 100 W into a eight ohm load. In reality, the voltage drop across the MOSFETs is not as high as this since the module uses two devices in parallel. The maximum output power of the prototype unit using the power supply shown was 112 W single channel and 105 W both channels driven (RMS).

If all is well, connect a multimeter across the 10 ohm resistor in the positive rail fuse holder and slowly wind the trimpot RV1 clockwise until the voltage measured is 1 V. This will set the bias current in the output stage at 100 mA. If the current sets up correctly, measure the voltage between the speaker output and 0 V on the power supply. You should see around ± 25 V. If you only have an analogue multimeter, this voltage may be too low to measure; in this case it is sufficient to show that the output is at 0 V.

If the module passes all these tests, it is safe to replace the fuses and connect the load.

Construction — PSU

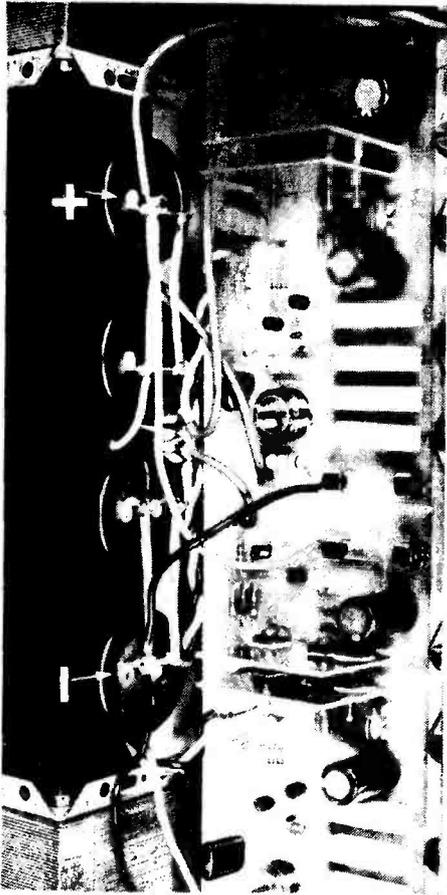The advantage normally associated with independent power supplies is the reduction of crosstalk between channels. In the case of the ET1 module however, the high supply rejection of the design reduces crosstalk to a level that is completely



Wiring of the four filter capacitors. Note the common 0 V point between the two inner capacitors.

Interwiring

By far the biggest problem in the design and construction of any amplifier is that of earthing. If maximum performance is to be obtained from the ETI-5000 modules great care must be taken to ensure complete isolation of high current earths from low current ones such as the input signal earth. If this is not done the large currents flowing in the speaker return earths, for example, will interact with the input and distortion results. Similarly, if the earth current from the electrolytic capacitors is allowed to interact with any low current signal earth amplifier will have degraded hum figures and may even be unstable. The board layout has been designed to overcome these problems through the use of a *single-point* earthing arrangement. Earth lines from the output devices and power earth capacitors are kept separate until they reach the 0 V point on the circuit board.

The main input signal earth is the most critical. To overcome any problem the input earth is isolated from the 0 V track on the circuit board by the 10 ohm resistor R3, shown on the circuit diagram. The input wiring to the module is done with a twisted pair

input signal earth line. The best way to do this is to break the connection between the chassis of the power amp and the 0 V point on the power supply. In this way the power amp still has a valid earth reference at its input but the possibility of a hum loop is eliminated.

The disadvantage of this technique is that the chassis can no longer act as an effective shield to external electrical noise sources, but this problem can be overcome by capacitively coupling the chassis to the 0 V track at selected places in the power amplifier. The relatively high impedance of these capacitors at 50 Hz still maintains an effective open circuit to prevent the hum loop problem.

The earthing procedure outlined above has consistently given good results both in the prototype and in numerous other power amps, and provides the power amplifier with good earthing that is not affected excessively by the earthing configuration in the preamp.

Lead Astray

The input wires to each module should be attached at this stage. We used a twisted pair of 32 x 0.2 mm plastic-coated hookup wire. This is superior to standard shielded cable for this application. The input wiring must be kept away from the 240 V wiring at the rear of the power switch.

The input 'earth' on each board has to be AC-coupled to the 0 V line on each board for the reasons discussed earlier. This is done by soldering a 100nF capacitor on the rear of each board, immediately beneath R3. The 'earthing bolt', which makes connection to the heatsink bracket, is assembled with a transistor mounting insulator on the underside of the board so that the bolt is insulated from the 0 V line on the board. A solder lug is placed under the bolt. A 100nF capacitor is then soldered between this lug and the 0 V track adjacent.

Follow the interwiring diagram carefully and recheck at each stage.

Do the bridge rectifier and transformer wiring first. Then do the capacitors. The lower terminals of all four capacitors are connected together using heavy braid stripped from a piece of RF type coax cable. The centre of this bus becomes the central 0 V return point (refer to the photograph). The two right hand capacitors also have their terminals bridged by a length of braid, as do the two negative terminals of the left hand capacitors. The positive output terminal from the bridge rectifier then connects to the positive terminal of the innermost right hand capacitor. The negative terminal of the bridge rectifier connects to the negative terminal of the innermost left hand capacitor. Two wires from each transformer secondary are wired directly to the central 0 V point (see wiring diagram).

Next wire in the amp modules, the speaker terminals and the 240 V circuitry.

Check everything carefully once you have finished.

Getting It Going

Having satisfied yourself that all is well, remove the fuses on each board, arm yourself with a multimeter, hold your breath ... and switch on. Assuming no disasters occur, measure the supply rail voltages. They should be around 52 V. If you have previously set up your modules then you can replace the four fuses and proceed with listening tests. Before replacing the fuses allow sufficient time for the electrolytic capacitors to discharge. This will take several minutes.

Once you have completed the set-up procedure, your amplifier is ready for listening tests.

The top and bottom covers can be screwed in place once you've confirmed all is well. We recommend you use aluminium for these items as steel plates will react with the field of the transformers and produce quite a loud hum.

READ/WRITE

Letters for this page should be addressed to Read/Write at our Charing Cross Road address.

Dear Sir,

I am writing to you about two separate matters. First, a friend of mine recently purchased a kit for the ETI System A preamp from Jelgate, as recommended in Buylines. The screened cable supplied for the internal wiring was the kind which has a semiconducting layer between the screen and the inner conductor insulation. My friend did not know of such cable and, as a result, his preamp had several strange 'faults.' This could, of course, be blamed on my friend's inexperience, but I think that the same mistake could be made by other constructors. I leave the matter to your judgement, but respectfully suggest that you contact Jelgate with the suggestion that they include a note in future kits making the special nature of the cable quite clear.

Second, I refer to the articles on Pickup Amplifier Design (ETI Jan. and Feb. 1982). Mr Tilbrook makes reference in the first article to a resonance which is "a function of both the mass and the compliance of the cantilever and suspension system," which occurs around 10 Hz. As far as I am aware, there is a resonance which occurs around 10 Hz, and it is a function of the cartridge compliance. However, the mass involved in this particular resonance is the mass of the whole cartridge plus the effective mass of the pickup arm (as 'seen' by the stylus tip). This mass is of the order of 5-10 grams. The effective mass of the cartridge cantilever and suspension system will be (at a guess!) 5-100 milligrams. This would lead to a resonance around 100 Hz according to Mr. Tilbrook's equation ($F = (2\pi \sqrt{mC})$, where m is the mass of the cantilever and suspension system and C is its compliance).

I was also under the impression that the RIAA roll-off point around 50 Hz was defined by a time-constant of 3180 μ S, and not 3150 μ S, as published. Perhaps this was changed by RIAA at the same time as the 20 Hz roll-off was added?

Signetics data shows the input current of the NE5534 to be less than 2 μ A, typically 0.5 μ A. My own experiments have led me to believe that the operation of a moving-magnet cartridge is not affected by a current of this order flowing through it. However, in a preamp which must suit all cartridges, a DC blocking capacitor

must be a good idea.

To sum up then, thanks for an article which treats the cartridge preamp very well indeed, despite some small confusion over resonances.

Yours faithfully,
S J Merrick,
Lancashire

David Tilbrook has been contacted about these points and we hope to be running a reply from him very soon.

Dear Mr Harris,

I advertised in ETI for 18 months but have never received any editorial comment.

We are THE UK specialists in pocket computers. This is a very exciting field which has not been taken seriously. We started by selling the PC-1211 and recently the CASIO FX-702P and at last the new SHARP PC-1500. This really is a fantastic machine. We really look after our customers with hardware software and consumables. Our mailing list has grown and we are selling all over the world.

We have the only range of books on pocket computing in the UK. Our new book "POCKET COMPUTING MADE EASY" has sections on the PC-1211 — FX-720P and the new PC-1500. This is the most comprehensive book available on pocket computing. We are giving it FREE on all orders for the PC-1500. Our 1982 catalogue is being printed and we will send free copies to your readers.

CAN YOU IGNORE ALL THIS EFFORT?

Give a small dedicated company a break. Mrs Thatcher will be grateful.

Yours faithfully,
Barry Elkan,
Elkan Electronics,
28 Bury New Road,
Prestwich,
Manchester M25 8LD

O.K. You've had a mention. So stop moaning!

Dear Sirs,

May I ask you to consider the following as the basis for a future article.

It is widely known that high sound levels can cause temporary, even

permanent hearing damage. However, although this fact is widely known it is not properly understood by the public. have not seen any 'in-depth' articles on the subject in the magazines that I take.

This seems to be a glaring omission when magazines such as yourselves devote pages and pages to the production of sound in ever-increasing variety and power. I am not immediately involved in this subject at the moment, but my colleagues are, and frequently bemoan the lack of understanding they encounter.

Would you consider publishing an article to clearly explain the hearing process and subsequently explain the effects of abnormal sound levels. This could be supported by details of audiometrics, possibly even a circuit (or project) of an audiometer.

When you consider that many of your readers are interested in the beauty of sound, from Bach to The Police, would it not be a great benefit to help them to continue to enjoy their pleasures for as long as possible, by not having those pleasures diluted by unnecessary hearing loss?

I hope you feel that this idea has sufficient merit to result in the printed word being published.

Yours faithfully,
G.M. Francis,
Ipswich

We have published a project for a SPL meter recently, but the point on high levels is well taken and we'll look at the idea for an article in more detail.

Dear Mr. Harris,

I am writing to say how delighted we are with Peter Freebrey's article on building the Wharfedale E70 speakers using our flatpack cabinet kit!

Just a point, though, — the article refers several times to "chipboard". Our cabinet kits are made from MDF board which is much finer grained, smoother and more consistent in texture and density than the highest density chipboard. Being ideal for speaker enclosures, this material is now being used by a number of up-market manufacturers (in spite of being more expensive than chipboard).

We found the April 82 issue of ETI interesting and enjoyable.

Yours sincerely,
R.F.C. Stephens,
Managing Director,
Wilmslow Audio Ltd.

To be honest no-one here had ever heard of MDF before and even now we can't find out what 'MDF' stands for!

Never was any good at woodwork anyhow.

ETI


LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook up wire.

Self assembly simulated wood cabinet. £4.50 + £1.50 p+p.

INTRODUCTORY OFFER - ONLY
£32⁹⁵
+ £2.75 p&p.

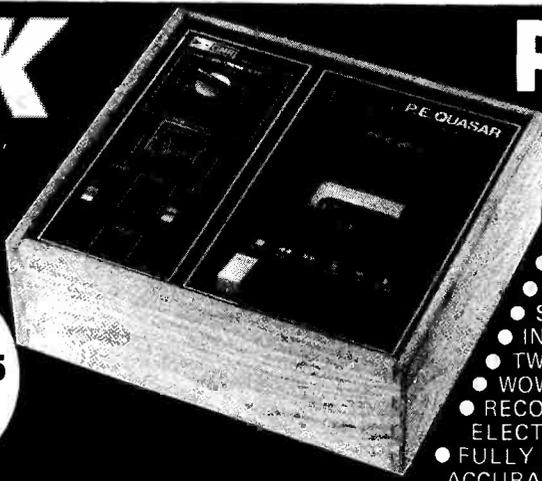
Featured in April issue Practical Electronics, reprint 50p - Free with Kit.



P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.Q.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

STEREO AMPLIFIER KIT

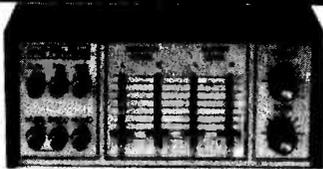

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/4" x 3 3/4" (approx).
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.

£16-50
+ £2.90 p&p.

Suitable for 4 to 8 ohm speakers
40Hz - 20KHz
P.U. 150mV. Aux. 200mV.
Mic. 1.5mV.
Bass ± 12 db @ 60Hz
Treble ± 12 db @ 10KHz
0.1% typically @ 8 watts
220 - 250 volts 50Hz.

8" SPEAKER KIT Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately £6.75 & £1.70 p+p.

125W HIGH POWER AMP MODULE

KIT: **£10-50** BUILT: **£14-25**
+ £1.15 p&p + £1.15 p&p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Suitable mains power supply kit with transformer: £7.50 plus £3.15 p&p.
Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



SPECIFICATIONS:

Max. output power (RMS): 125W.
Operating voltage (DC): 50 - 80 max.
Loads: 4 - 16 ohms.
Frequency response measured @ 100 watts: 25Hz - 20KHz.
Sensitivity for 100 watts: 400mV @ 47K.
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.
Dimensions: 205 x 90 and 190 x 36 mm.

HI-FI SPEAKERS AT BARGAIN PRICES

GOODMANS TWEETERS

8 ohm soft dome radiator tweeter (3 1/2" sq.) for use in up to 40W systems; with 2 element crossover.

£3.50 each (p&p £1) or £5.95 pair (p&p £2).



35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIFI1JSM. Complete with 2 element crossover. Total impedance of system 4 ohms.



£7.95
PER SET + £2.70 p&p.


P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

£17-95
Plus £2.50 p&p.

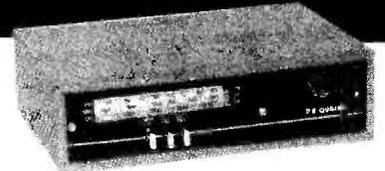Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4".
£3.50 Plus £1.50 p&p.



SPECIAL OFFER! TUNER KIT PLUS:
• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider £21.95 controls for bass, treble and volumes. + £3.80 P&P.

PRACTICAL ELECTRONICS

CAR RADIO KIT SERIES II



2 WAVE BAND, MW - LW

• Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.


Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p&p.

£12-95
+ £2.00 p&p.

BIRD AUDIO STEREO CAR RADIO BOOSTER

To boost your car radio or radio cassette to 15W r.m.s. per channel.

£9-95 + £1.50 p&p.

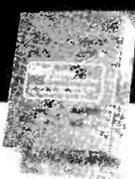

TV SOUND TUNER KIT

£11-45
+ £1.50 p&p.

As featured in E.T.I., December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. £1.95 + 75p p&p.

MONO MIXER AMP

£39-95
+ £3.70 p&p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/4" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.



ALL MAIL TO:

21E HIGH STREET, ACTON, W3 6NG.
Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All items subject to availability. Prices correct at 31/1/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch.

ALL PRICES INCLUDE VAT AT 15%.

ALL CALLERS TO: 323 Edgware Rd, London W2. Telephone: 01-723 8432.
Open 9.30 - 5.30pm. Closed all day Thursday.
RTVC Limited reserve the right to update their products without notice.



NICADS: UK's LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW


Available at your newsagent or direct, for 70p inc.

Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 £1 discount vouchers. In a recent supplier survey, we were one of only two suppliers listed in all categories!

There's a few examples of some super low prices.

78XX 1A	37p
BC237/8/9	8p
3SK51	54p
10MHz xtals	£2
8 Pole 10.7MHz xtal filters	£14.50
2GHz coax relay 150W	£10.95

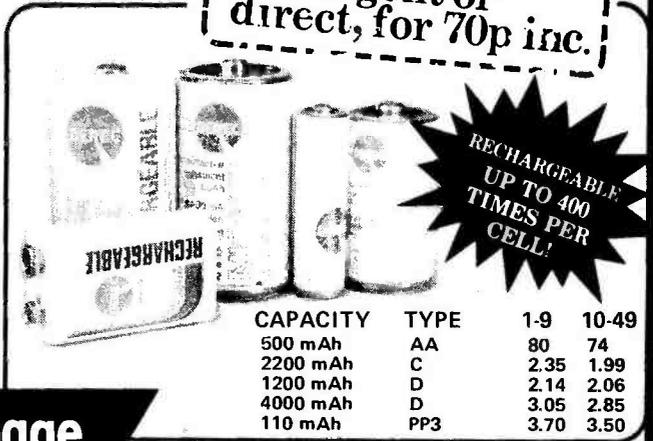All the "usual" stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micro-metals toroids, Fairrite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.




RECHARGEABLE UP TO 400 TIMES PER CELL!

CAPACITY	TYPE	1-9	10-49
500 mAh	AA	80	74
2200 mAh	C	2.35	1.99
1200 mAh	D	2.14	2.06
4000 mAh	D	3.05	2.85
110 mAh	PP3	3.70	3.50

Price on the page

CMOS	4000 0.11	4514 1.25	7406N 0.22
	4001 0.11	4515 1.25	7407N 0.22
	4002 0.12	4516 0.60	7408N 0.15
	4007 0.13	4518 0.35	7409N 0.15
	4008 0.50	4520 0.60	7410N 0.12
4008AE	0.80	4521 1.30	7411N 0.18
4009	0.25	4522 0.89	7412N 0.19
4010	0.30	4527 0.89	7413N 0.27
4011AE	0.24	4528 0.65	7414N 0.51
4011	0.11	4529 0.70	7416N 0.27
4013	0.25	4531 0.85	7417N 0.27
4015	0.50	4532 0.80	7420N 0.13
4016	0.22	4534 4.00	7421N 0.28
4017	0.40	4536 2.50	7423N 0.22
4019	0.38	4538 0.85	7425N 0.22
4020	0.55	4539 0.80	7426N 0.22
4021	0.55	4543 0.80	7427N 0.22
4022	0.55	4549 3.50	7430N 0.13
4023	0.15	4553 2.70	7432N 0.23
4024	0.33	4554 1.20	7437N 0.22
4025	0.15	4555 0.35	7438N 0.22
4026	1.05	4556 0.40	7440N 0.14
4027	0.26	4557 2.30	7441N 0.54
4028	0.50	4558 0.80	7442N 0.42
4029	0.55	4559 3.50	7443N 0.62
4030	0.35	4560 2.50	7444N 0.62
4035	0.67	4561 1.00	7445N 0.62
4040	0.50	4562 2.50	7446N 0.62
4042	0.50	4566 1.20	7447N 0.62
4043	0.50	4568 1.45	7448N 0.56
4043AE	0.93	4569 1.70	7450 0.14
4044	0.60	4572 0.22	7451N 0.14
4046	0.60	4580 3.25	7453N 0.14
4047	0.68	4581 1.40	7454N 0.14
4049	0.24	4582 0.70	7460N 0.14
4050	0.24	4583 0.80	7470N 0.28
4051	0.55	4584 0.27	7472N 0.28
4052	0.55	4585 0.45	7473N 0.28
4053	0.55	4702 4.50	7474N 0.28
4054	1.30	4703 4.48	7475N 0.35
4055	1.30	4704 4.24	7476N 0.30
4056	1.30	4705 4.24	7480N 0.26
4059	5.75	4706 4.50	7481N 0.20
4060	0.75	4720 4.00	7482N 0.75
4063	1.15	4723 0.95	7485N 0.35
4066	0.30	4724 0.95	7486N 0.24
4067	4.30	4725 2.24	7489N 1.05
4068	0.16	40014 0.54	7490N 0.30
4069AE	0.14	40085 0.99	7491N 0.55
4070	0.16	40098 0.54	7492N 0.35
4071	0.16	40106 0.69	7493N 0.35
4072	0.16	40160 1.05	7494N 0.70
4073	0.16	40161 1.05	7495N 0.60
4075	0.16	40162 1.05	7496N 0.45
4076	0.55	40163 1.05	7497N 1.40
4077	0.18	40174 1.05	74100 1.10
4078	0.18	40175 1.05	74104 0.62
4081	0.12	40192 1.08	74105 0.62
4082	0.18	40193 1.08	74107 0.26
4093	0.30	40194 1.08	74109N 0.35
4099	0.80	40195 1.08	74110N 0.54
4175	0.80		74111N 0.68
4502	0.60		74112N 1.70
4503	0.50		74116N 1.95
4506	0.70	7400N 0.10	74118N 0.95
4507	0.37	7401N 0.10	74119N 1.20
4508	1.50	7402N 0.20	74120N 0.95
4510	0.55	7403N 0.11	74121N 0.34
4511	0.45	7404N 0.12	74122N 0.34
4512	0.55	7405N 0.12	74123N 0.40

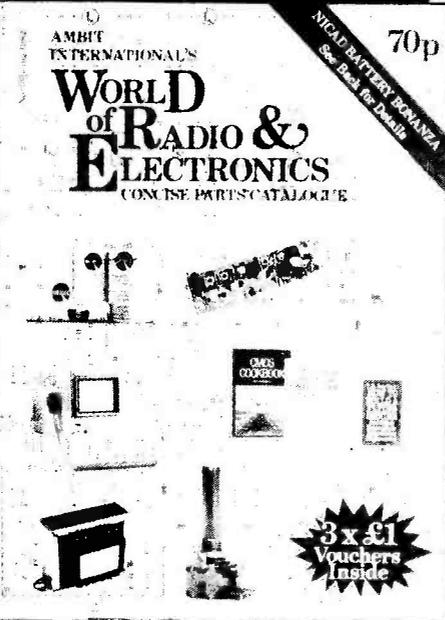

AMBIT INTERNATIONAL'S
WORLD of RADIO & ELECTRONICS
CONCISE PARTS CATALOGUE

70p
NICAD BATTERY BONUS!
See Back for Details

3x£1 Vouchers Inside

Prices shown EXCLUDE VAT. Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO.

POSTAGE and PACKING
50p per order

74125N 0.40	74153N 0.55	74170N 1.25
74126N 0.40	74154N 0.55	74173N 1.10
74128N 0.65	74155N 0.55	74174N 0.75
74132N 0.50	74156N 0.55	74175N 0.75
74136N 0.65	74157N 0.55	74176N 0.75
74141N 0.45	74159N 1.90	74177N 0.75
74142N 1.85	74160N 0.55	74178N 0.90
74143N 2.50	74161N 0.55	74179N 1.35
74144N 2.50	74162N 0.55	74180N 0.75
74145N 0.75	74163N 0.55	74181N 1.22
74147N 1.50	74164N 0.55	74182N 0.70
74148N 1.09	74165N 0.55	74184N 1.20
74150N 0.79	74166N 0.70	74185N 1.20
74151N 0.55	74167N 1.25	74188N 3.00

74190N 0.56	74LS74N 0.16	74LS248N 1.35	74C74 0.75
74191N 0.55	74LS75N 0.22	74LS249N 1.35	74C76 1.05
74192N 0.55	74LS76N 0.20	74LS251N 0.35	74C83 1.05
74193N 0.55	74LS78N 0.19	74LS253N 0.35	74C85 1.25
74194N 0.55	74LS83N 0.40	74LS257N 0.40	74C86 0.60
74195N 0.55	74LS85N 0.60	74LS258N 0.37	74C89 2.10
74196N 0.55	74LS86N 0.14	74LS259N 0.60	74C90 1.05
74197N 0.55	74LS90N 0.32	74LS260N 0.50	74C93 1.05
74198N 0.85	74LS91N 0.28	74LS266N 0.72	74C95 1.25
74199N 1.00	74LS92N 0.31	74LS273N 0.70	74C107 0.60
74221N 1.00	74LS93N 0.31	74LS275N 3.20	74C151 2.10
74246N 1.50	74LS95N 0.40	74LS279N 0.35	74C154 3.05
74247N 1.51	74LS96N 1.20	74LS280N 2.50	74C157 2.10
74248N 1.89		74LS283N 0.42	74C160 1.05
74249N 0.11	74LS107N 0.25	74LS290N 0.50	74C161 1.05
74251N 1.05	74LS109N 0.20	74LS293N 0.40	74C162 1.05
74265N 0.66	74LS112N 0.20	74LS295N 1.50	74C163 1.05
74273N 2.67	74LS113N 0.20	74LS298N 0.76	74C164 1.05
74278N 2.49	74LS114N 0.19	74LS365N 0.32	74C165 1.10
74279N 0.89	74LS122N 0.35	74LS366N 0.34	74C173 1.05
74283N 1.30	74LS123N 0.35	74LS367N 0.32	74C174 1.05
74284N 3.50	74LS124N 0.80	74LS368N 0.35	74C175 1.05
74285N 3.50	74LS125N 1.24	74LS373N 0.70	74C192 1.08
74290N 1.00	74LS132N 0.42	74LS374N 0.70	74C193 1.08
74293N 1.05	74LS133N 0.24	74LS375N 0.40	74C195 1.08
74297N 2.36	74LS136N 0.20	74LS377N 0.85	74C200 6.50
74298N 1.85	74LS138N 0.30	74LS378N 0.65	74C221 1.55
74365N 0.85	74LS139N 0.30	74LS379N 0.60	74C901 0.55
74366N 0.85	74LS145N 1.20	74LS384X 2.50	74C903 0.55
74367N 0.85	74LS151N 0.30	74LS385N 2.05	74C904 0.55
74368N 0.85	74LS153N 0.27	74LS386N 0.29	74C905 6.50
74390N 1.85	74LS154N 0.99	74LS390N 0.68	74C906 0.55
74393N 1.85	74LS155N 0.35	74LS393N 0.61	74C907 0.55
74490N 1.85	74LS156N 0.37	74LS395N 2.10	74C908 1.10
	74LS157N 0.30	74LS396N 1.99	74C909 2.10
	74LS158N 0.30	74LS398N 2.75	74C910 1.00
	74LS160N 0.37	74LS399N 2.30	74C914 1.10
	74LS161N 0.37	74LS445N 1.40	74C918 1.30
	74LS162N 0.37	74LS447N 1.95	74C925 6.00
	74LS163N 0.37	74LS490N 1.10	74C926 6.00
	74LS164N 0.40	74LS668N 1.05	74C927 6.00
	74LS165N 0.60	74LS669N 1.05	
	74LS166N 0.80	74LS670N 1.70	
	74LS168N 0.70		
	74LS169N 0.85		
	74LS170N 0.90		
	74LS173N 0.60		
	74LS174N 0.40		
	74LS175N 0.40		
	74LS181N 1.05		
	74LS183N 1.75		
	74LS189N 1.28		
	74LS190N 0.45		
	74LS191N 0.45		
	74LS192N 0.45		
	74LS193N 0.42		
	74LS194N 0.35		
	74LS196N 0.55		
	74LS197N 0.60		
	74LS200N 3.40		
	74LS202N 3.45		
	74LS221N 0.50		
	74LS241N 0.80		
	74LS242N 0.70		
	74LS243N 0.70		
	74LS244N 0.60		
	74LS245N 0.80		
	74LS247N 1.35		

Processors	
8080 Series	
8080AFC/2	7.30
8212	2.30
8214	3.50
8216	1.95
8224	3.50
8251	6.21
8255	5.40
Z80 Series	
Z80A	3.75
Z80ADRT	7.50
Z80APIO	3.50
Z80ASIO/1	11.00
Z80ASIO/2	9.95
Z80ASIO/9	11.00
Z80CTC	4.00
Z80ACTC	4.50
Z8001	65.00
PROM	
2708	2.00
2716	3.00
2532	0A
2732	4.00

AMBIT international TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
200 North Service Road, Brentwood, Essex
West London Retail Shop at 102, CHURCHFIELD ROAD, ACTON, W3 6DH Tel: 01-992 7748

ELECTROMUSIC TECHNIQUES PART 3

In the final part of this electronic extravaganza, Tim Orr tidies up the loose ends with details of ADSR and signal input circuits, plus controllers and sequencers.

The ADSR unit has become industry standard for generating envelope contours and for filter sweeps. Curtis produce an entirely voltage controlled device, the CEM3310 (Fig. 1). The A, D and R inputs have an exponential sensitivity; these time constants will vary an octave for a 18 mV voltage change (or 60 mV per decade) at the input pins of the IC. The control voltages are externally attenuated by a resistor pair (30k and 470R). The time constants are controllable over four decades, that is from 2 milliseconds to 20 seconds. The sustain level is variable from 0% to 100%, again using voltage control (0 V to + 10 V, linear law). The CEM3310 is ideally suited to polyphonic systems where one set of ADSR pots will control 5 or 10 independent ADSR units, by use of voltage control. An ADSR unit that employs a separate pot for each parameter is shown in Fig. 2. Time constants from three milliseconds to two seconds are available. This unit can be used in monophonic synthesiser systems.


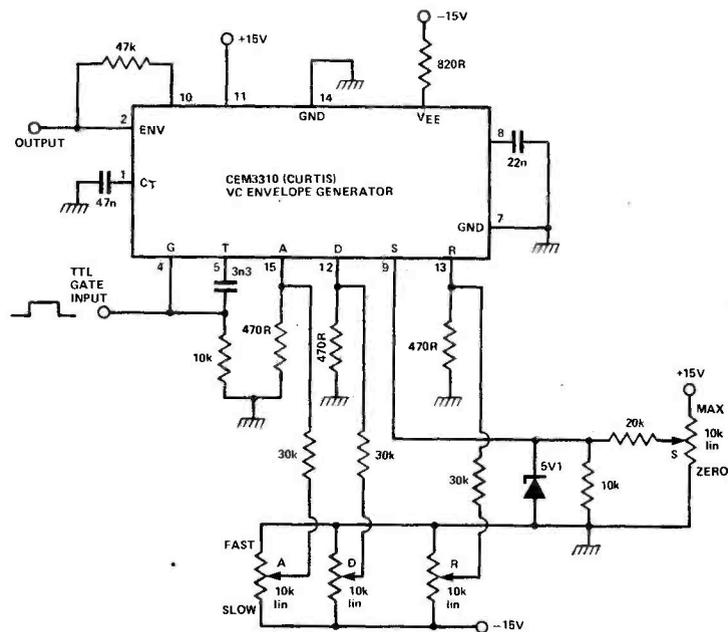


Fig. 1 (Right) A monolithic ADSR circuit using the Curtis chip. The A, D and R time constants are variable from 2 milliseconds to 20 seconds.

Fig. 2 (Below) An ADSR unit using discrete components (courtesy of Powertran Electronics).

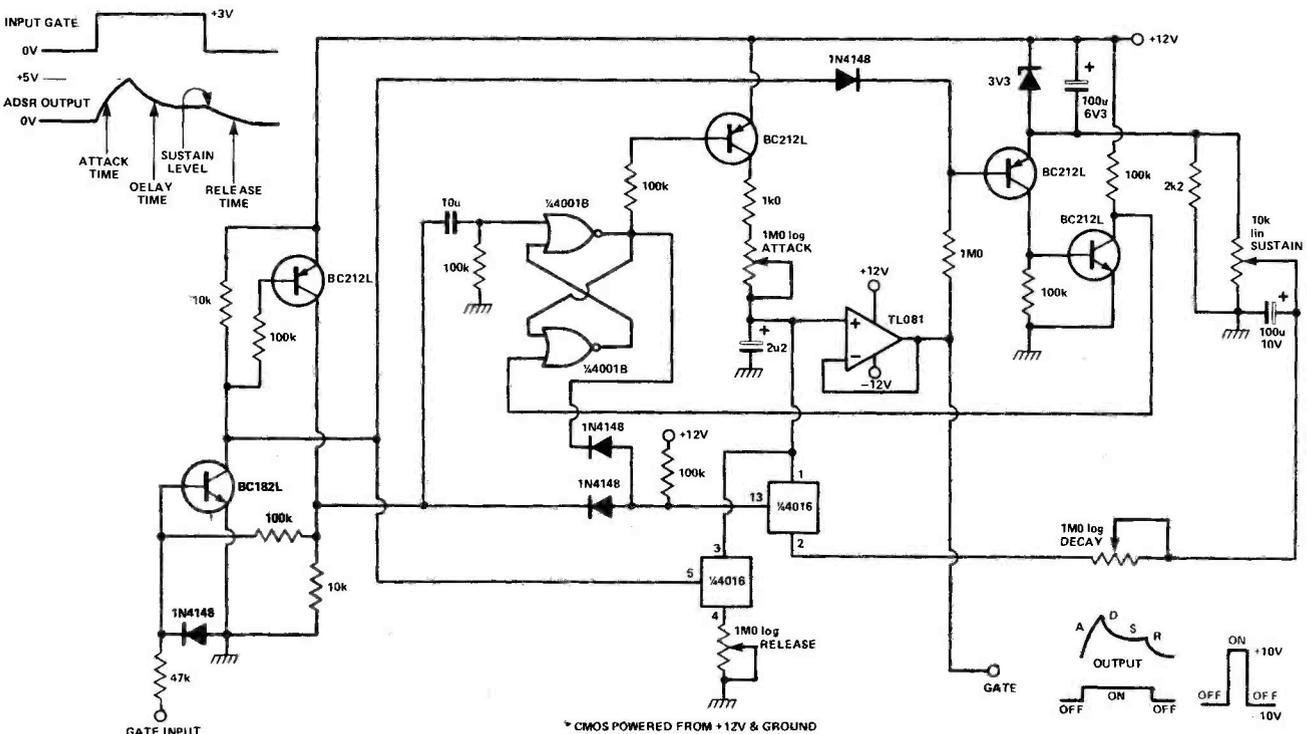

* CMOS POWERED FROM +12V & GROUND

HI INPUT
GAIN = +20dB TO -30dB
 $Z_{IN} = 100k$
SUITABLE FOR HIGH IMPEDANCE
MICROPHONE OR GUITAR

LOW INPUT
GAIN = +49.5dB TO -0.5dB
 $Z_{IN} = 1k2$
SUITABLE FOR LOW IMPEDANCE MIC

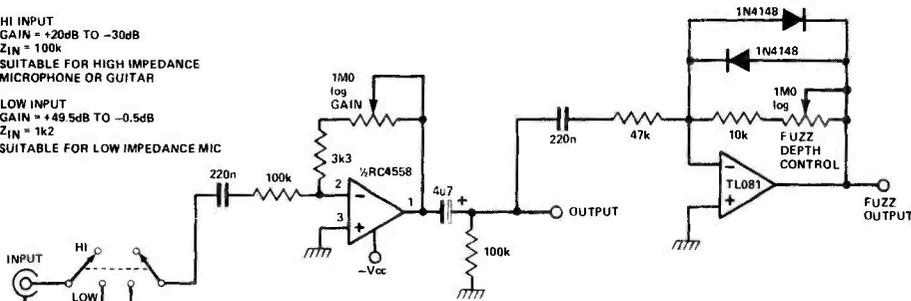


Fig. 3 (Left) An input amplifier suitable for a synthesiser, with both high and low level inputs.

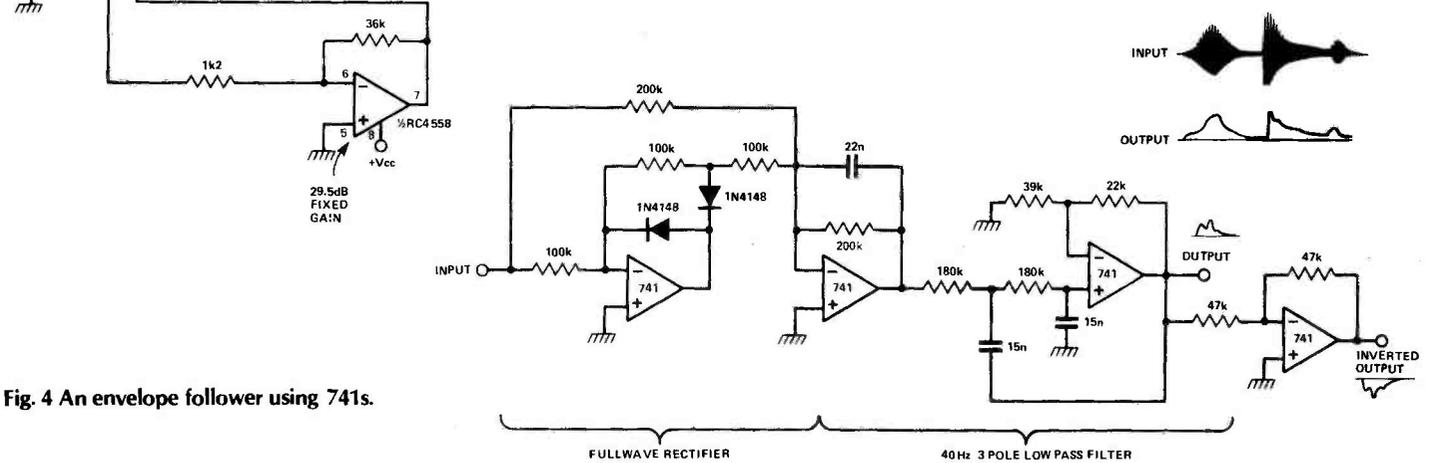


Fig. 4 An envelope follower using 741s.

Signal Input Circuits

Synthesisers are often used as signal processors, and so a variable gain input amplifier is needed (Fig. 3). This circuit has a high level high impedance input, which makes it suitable for guitars, plus a low level impedance input suitable for a low impedance microphone. A fuzz circuit has also been included so that severe harmonic distortion can be introduced to the signal. Another useful device is the envelope follower (Fig. 4). This is a fullwave rectifier followed by a lowpass filter. The envelope is often used to sweep a VCF or a VCO, to produce dramatic effects.

Controllers

Most synthesisers are controlled from a musical keyboard. The keyboard has to generate and remember a pitch voltage (+ 1 V/octave) plus a gate signal to indicate that a note is being pressed (Fig. 5). The pitch circuit is a stable current source that drives a resistor chain. A potential of 83.3 mV is set up across each 15 ohm resistor. When one note is pressed, the potential of that note is stored in a sample-and-hold unit. When the note is released the potential is retained. If more than one note is pressed, then the lower note is selected.

A sample-and-hold unit cannot retain its information for ever; it droops. A no-droop solution to pitch generation is to use a digital system, as in Fig. 6. The 74C922 is a keyboard encoder; it scans a keyboard and generates a digital code representing the last note pressed. Unfortunately it can only define 16 notes (the 74C923 can define 20) and so must be limited to rather small keyboards. The digital code is converted into a pitch voltage with an eight bit DAC, only using the most significant top four bits. Some keyboards have a dynamic feature, so that the faster you play the note the louder it sounds. This is done by timing the key transition, but it is very difficult to get a natural feel to the keyboard. Some keyboards are pressure sensitive; the harder you press down, the more pitch bend or vibrato you add to the VCO pitch. Other manual controllers such as pitch bend/vibrato wheels and joysticks are also employed (Fig. 7). The wheels are always mounted on the left hand side of the keyboard so that the musician can operate them with his left hand and play the music with his right. The pitch voltage from a

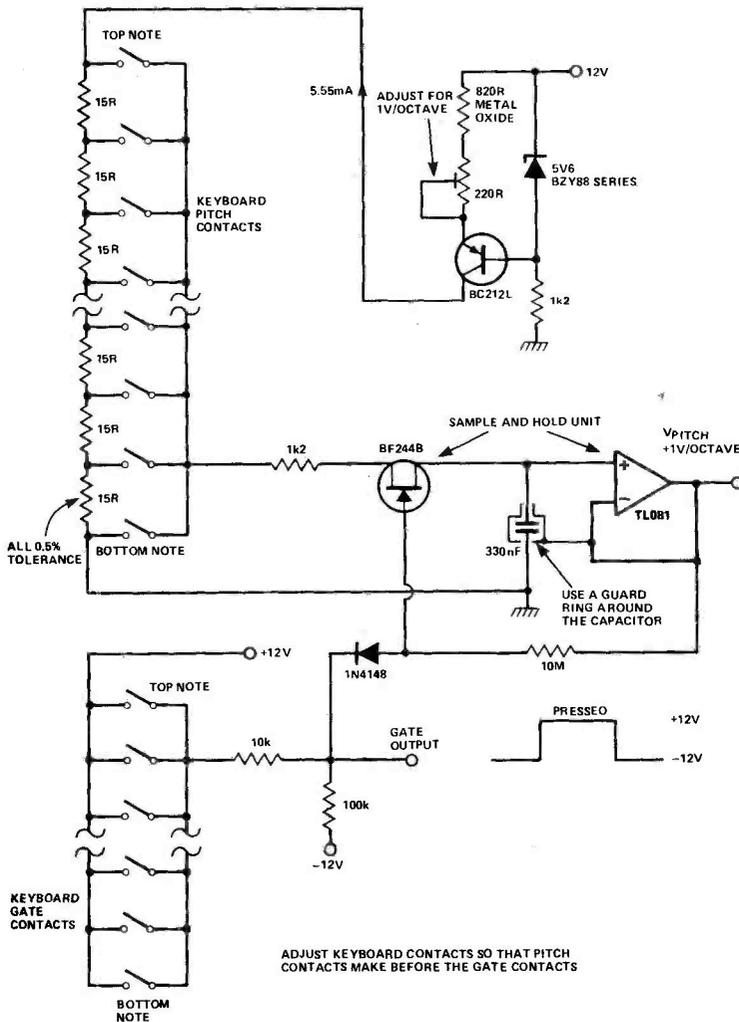


Fig. 5 Typical monophonic synthesiser keyboard unit.

FEATURE : Electronic Music Part 3

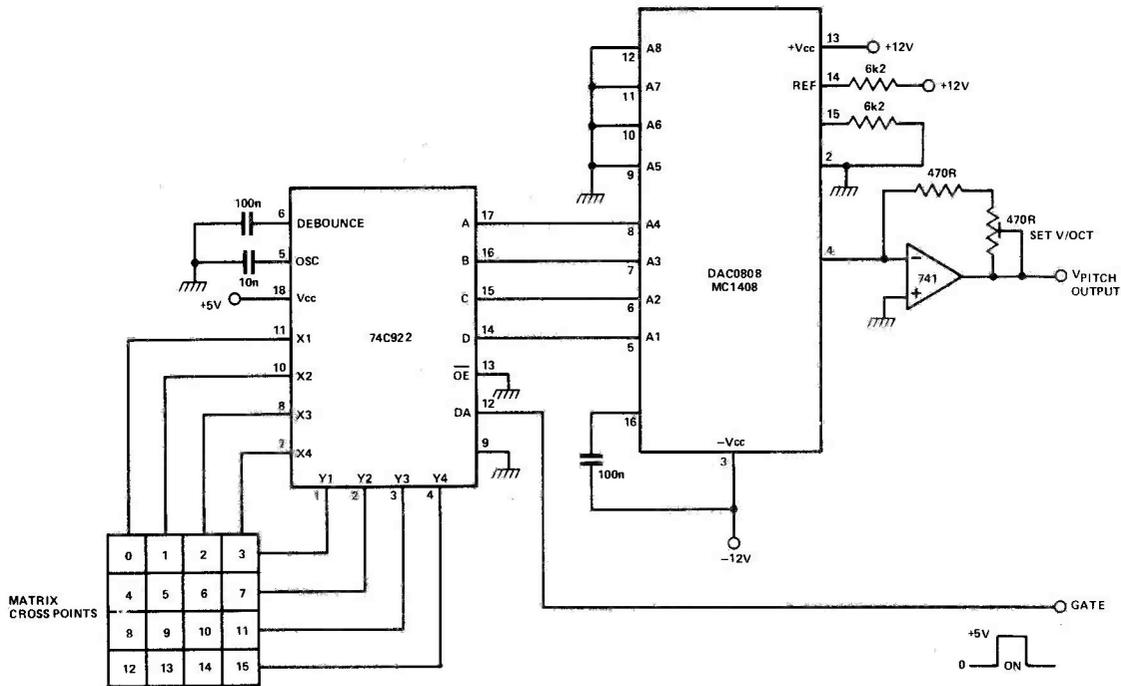


Fig. 6 A digital keyboard, in this case for a 16-note range.

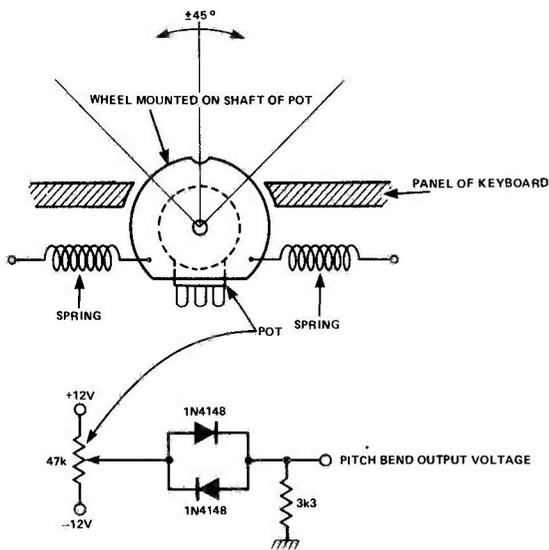


Fig. 7 Two methods of manually controlling the pitch of a VCO; a pitch bend wheel (above) and a joystick controller (right).

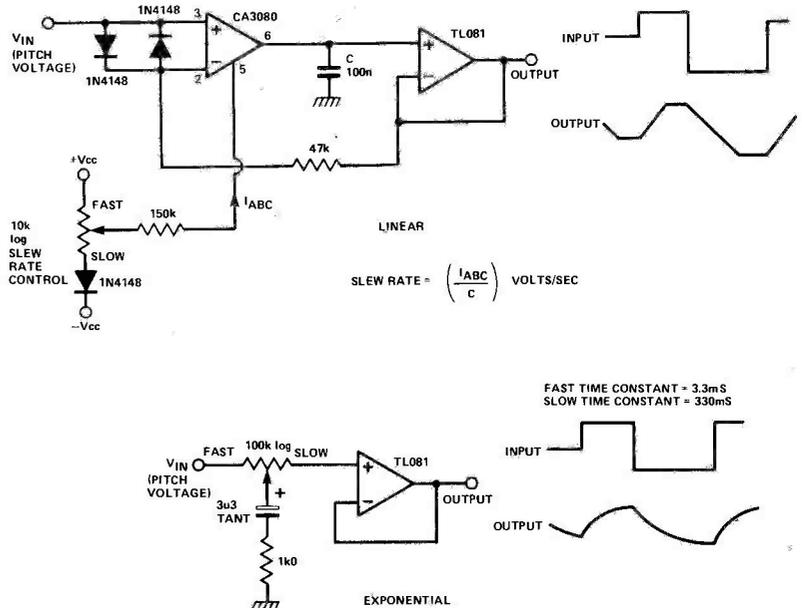
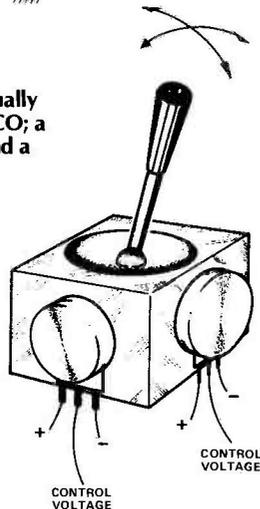


Fig. 8 Two portamento circuits; one linear (top), the other exponential (bottom).

keyboard is often processed by a portamento unit (Fig. 8). The pitch then glides from its last note to the next. Some people prefer exponential glides, others linear.

Sequencers

Electronic music often has a background rhythm, which is generated by some sort of sequencer (Fig. 9). A sequencer generates a string of pitch voltages which change on the beat. These are used to control a VCO which is perhaps passed through an ADSR and VCA unit. The result is a rhythmic string of notes. In the circuit, the clock is externally generated, although

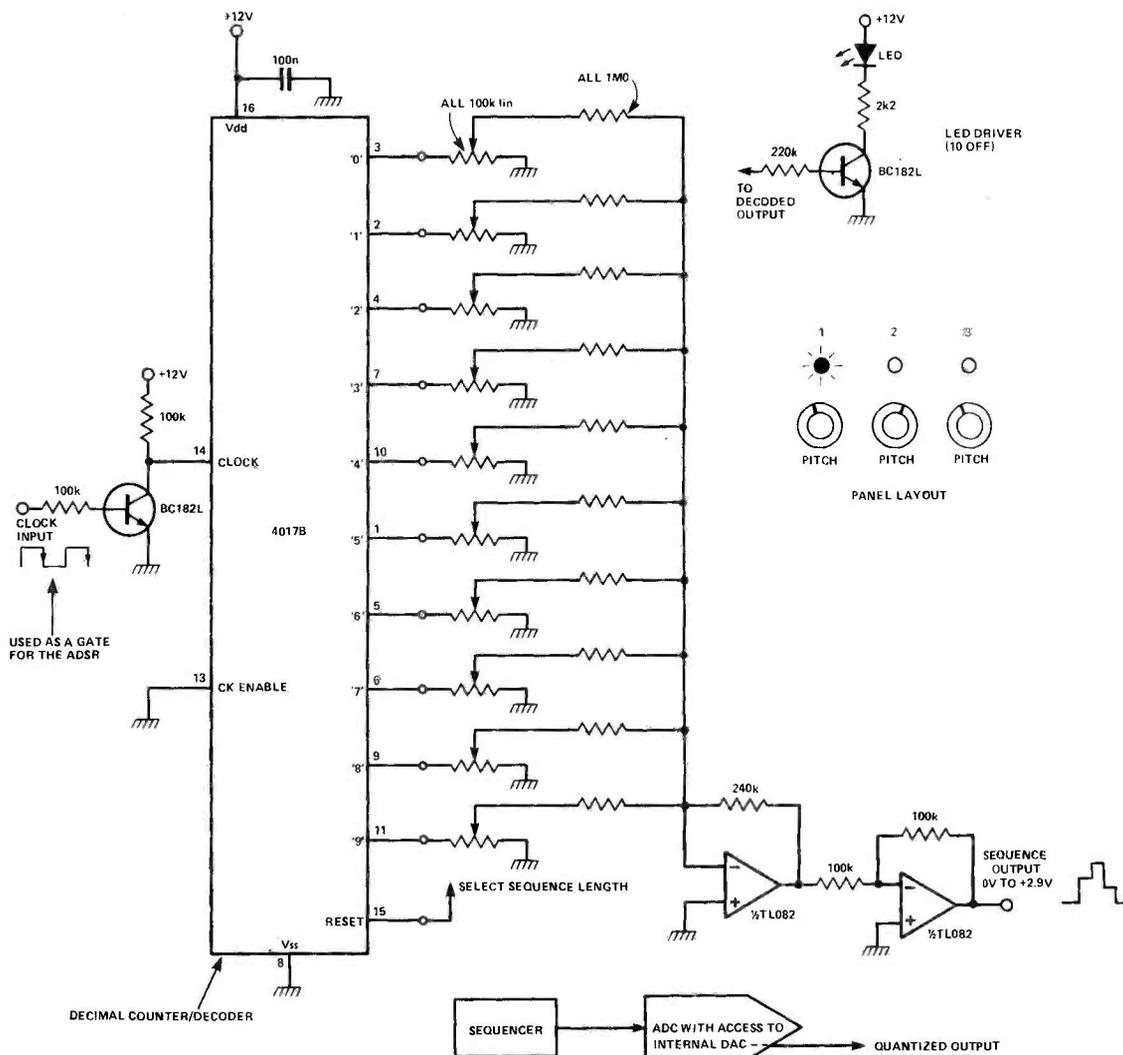


Fig. 9 A simple sequencer.

there is no reason why the sequencer should not have its own dedicated oscillator. The sequence length can be modified by connecting the reset line to any output; if you connect it to the '8' output the sequence length will be 8. An LED indicates which decoded output is active. The pitch pots have been given a three octave range, which might make tuning rather difficult; 0.1% of the pot rotation equals 3.6 cents of pitch (100 cents = 1 semitone). Either a smaller pitch range could be used or multiturn pots could be employed, but these are rather expensive. Some sequencers quantise the pitch into semitone steps so that 2.7% of the pot rotation would equal one semitone. During this 2.7% rotation, the output pitch remains fixed. This can be done by inserting the pitch voltage into an ADC, using the beat signal to start the conversion and taking the DAC output as the quantised pitch output voltage.

Final Points

A modular synthesiser should have one or two simple audio mixer circuits (Fig.10). These can be used to mix the final output signal or to send the signal to external treatments such as reverberation units, phasers or chorus units, and electronic or tape echoes.

A synthesiser relies heavily on stable and clean power supply rails. A good rule is never to dump large currents down the ground rail, as this is used as a voltage reference throughout the system. If you are going to turn lamps on and off, run them between the positive and negative rails. Ordinary 78XX and 79XX voltage regulators can be used, but if they get hot then their output voltage will drift and will give the system a long warm-up

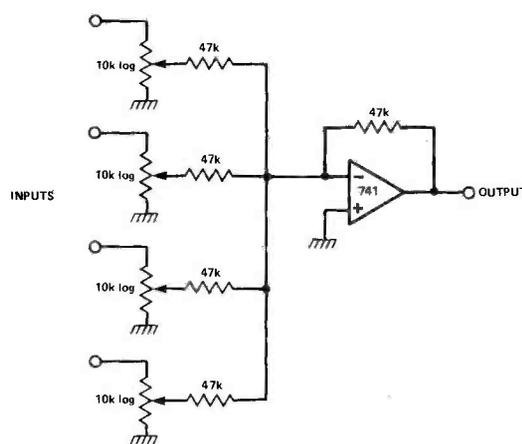


Fig. 10 A simple audio mixer with four inputs.

time. A 723 regulator plus a power bypass transistor will give better temperature stability performance. Any hum on the supply rails will frequency modulate all the VCOs.

Good Books

- Musical Applications of Microprocessors — Hayden Book Company.
- Active Filter Cookbook — Howard Sams.
- Musical Engineers Handbook — Electronotes.

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS

- Beginners Guide to Electronics** Squires £4.50
- Beginners Guide to Transistors** Reddihough £4.50
- Beginners Guide to Integrated Circuits** Sinclair £4.50
- Beginners Guide to Radio** King £4.50
- Beginners Guide to Audio** Sinclair £4.50
- Introducing Amateur Electronics** Sinclair £4.50
- Introducing Microprocessors** £5.20
- Understanding Electronic Circuits** Sinclair £5.30
- Understanding Electronic Components** Sinclair £5.30

APPLICATIONS COOKBOOKS

- TV Typewriters Cookbook** £9.35
 - CMOS Cookbook** £9.85
 - Active Filter Cookbook** £11.30
 - IC Timer Cookbook** £8.65
 - IC Op-Amp Cookbook** £12.20
 - ITL Cookbook** £9.15
 - MC 6809 Cookbook** Carl D. Warren £5.30
 - PLL Synthesiser Cookbook** Kinley £5.85
 - 8085A Cookbook** Titus £10.75
-
- How To Build Electronic Kits** Chapel £3.45
 - 110 Electronic Alarm Projects** Marston £5.25
 - 110 Semiconductor Projects for the Home Constructor** Marston £5.25
 - 110 Integrated Circuit Projects for the Home Constructor** Marston £5.25
 - 110 Thyristor Projects Using SCRs** Marston £5.25
 - 110 Waveform Generator Projects** Marston £5.25
 - 99 Practical Electronic Projects** Friedman £4.20

COMPUTING & MICROPROCESSORS

- What is a Microprocessor?** 2 cassette tapes plus a 72-page book £10.00
- Beginners Guide to Computers and Microprocessors** with projects £6.05
- Basic Computer Games** Ahl £6.05
- Basic for Home Computers** Albrecht £6.60
- Illustrating Basic** Alcock £4.25
- Troubleshooting Microprocessors and Digital Logic** Goodman £6.10
- Z-80 Microcomputer Handbook** £9.35
- Microprocessors in Instruments and Control** Bibbero £15.30
- Basic Basic** Coan £9.95
- Advanced Basic** Coan £9.95
- 1001 Things to do with your Personal Computer** Sawusch £6.00
- Microcomputers, Microprocessors, Hardware, Software and Applications** Hilburn £17.40
- Microprocessor Systems Design** Klingman £21.95
- Introduction to Microprocessors** Leventhal £11.25
- Microprocessor Technology, Architecture and Applications** £11.30
- Basic with Style** Nagin £6.30
- Microcomputer Design** Ogdin £9.25
- Hands on Basic with a PET** Peckham £11.95
- 6800 Software Gourmet Guide and Cookbook** Scelbi £9.30
- 8080 Software Gourmet Guide and Cookbook** £9.30
- The 8080A Bugbook** Rony £10.05
- 8080/8085 Software Design** Titus £10.05
- How to Design, Build and Program your own Working Computer System** £7.10
- Your Own Computer** Waite £2.25
- Microcomputer Interfacing Handbook A/D & D/A** £6.35
- Crash Course in Microcomputers** Frenzel £14.95
- Musical Applications of Microprocessors** Chamberlain £20.95
- The Pascal Handbook** Tiberghien £12.45
- 50 Basic Exercises** Lamoitier £11.10
- Learning Basic with the Sinclair ZX80** £4.95
- Microprocessors for Hobbyists** Coles £4.25
- Introduction to Microcomputer Programming** Sanderson £5.25

- Microprocessors and Microcomputers for Engineering Students and Technicians** Wooland £5.95
- Using CP/M – Self Teaching Guide** Ashley Fernandez £6.95
- Digital Counter Handbook** Frenzel £8.65
- 33 Challenging Computer Games for TRS80-Apple-Pet** Chance £5.75
- How to Build Your Own Working Robot Pet** Dalesta £5.75
- Microprocessor and Digital Computer Technology** £16.00
- Guidebook to Small Computers** Barden £4.20
- How to Debug Your Personal Computer** Huffman £6.30
- How to Troubleshoot and Repair Microcomputers** Leuk £6.30
- 6809 Microcomputer Programmes and Interfacing with Experiments** Staugaard £11.45
- Wordprocessors Programmed. Training Guide with Practical Application** £
- Digital Circuits and Microcomputers** Johnson £9.75
- Experiments in Artificial Intelligence for Small Computers** £7.25

TEST

- The Oscilloscope in Use** Sinclair **NEW EDITION 1982**
- How to Get More Out of Low-cost Electronic Test Equipment** Tobery £5.50

THEORY

- Digital Signal Processing. Theory and Applications** Rabiner £26.40
- Electronic Communication Systems** Kennedy £8.95
- Principles of Communication Systems** Taub £8.40
- Introduction to Digital Filtering** Bognor £13.30
- Transistor Circuit Design** Texas Instruments £10.95
- Electronic Circuit Design Handbook** Design of active filters, with experiments: Berlin £6.80

REFERENCE

- Electronic Engineers Reference Book** Turner £42.00
- Electronic Components** Colwell £4.00
- Electronic Diagrams** Colwell £4.00
- International Transistor Selector** Towers New £10.70
- International FET Selector** Towers £4.60
- International Op-Amp Linear IC Selector** Towers £8.00
- International Microprocessor Selector** Towers £16.00
- Dictionary of Audio – Radio and Video** Roberts £16.00
- Dictionary of Electronics** Amos £16.00
- Dictionary of Electrical Engineering** Amos £16.00
- Dictionary of Telecommunications** Amos £16.00
- Giant Book of Electronic Circuits** Collins £12.75
- World Radio/TV Handbook Vol. 35 1981** £10.50
- How to Build Electronic Projects** Malcolm £6.45
- Modern Electronic Circuit Reference Manual** Marcus £33.50

Please send me the books indicated. I enclose cheque/postal order for £.....

I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4																	
4	9	2	9																	

Signed

Name

Address

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL

LONDON'S TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY



CROTECH 3035 10 MHz Scope Plus Component Tester

5" - 130mm Flat Face Tube DC - 10 MHz 5mV/DIV 220/240V AC Trig. to 20 MHz

SAVE £21 PLUS

As advertised by us at £189.75 inc. VAT
NOW £168.50 inc. VAT
 (UK c/p £3.50) Exclusive to Audio Electronics


PROFESSIONAL 100 K OHM/VOLT MULTIMETER

30 ranges 15A AC/DC 1.5 KV, 200 meg ohms. Features mirror scale, polarity reverse, electronic overload protection, taut band suspension.

As advertised by us at £67.50 + case i.e. £84.00

NOW £49 inc. VAT
 (UK c/p £1.50) with leather case Exclusive to Audio Electronics

SAVE £35

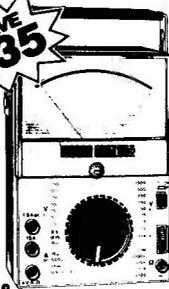


LCD LOW COST MULTIMETERS

- 00001 3% digit LCD 25 range push button 2A AC/DC 20 meg ohm Basic 0.5% £36.50
- HC703 0.1% version of above £54.00
- SABTRONICS version of above £39.95
- 000011A/100m 3% digit LCD 15 range push button plus Hfe Tester 10A DC (No AC A) 100m 3% digit LCD range Rotary switch plus Hfe Tester 10A AC/DC £69.95

Callers will always find a range of low cost test equipment accessories tools, irons and boards in stock, also special offers for certain equipment which will vary from time to time. Price correct at time of preparation E&OE. All prices include VAT.

CHOOSE FROM UK'S LARGEST RANGE

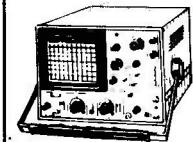STOP PRESS Few only 6110 23 range 10A AC/DC range hold, continuity buzzer plus much more. Rotary switch. £59.95




TRIO OSCILLOSCOPES

Range of mains operated Scopes with 5" displays, triggered sweep (UK c/p £3.50)

- DUAL TRACE
- CS1582A 10 MHz, 10 MV, 1 micro sec. £267.95
- CS1580A 11 15 MHz, 10mV, 0.5 micro sec. £341.55
- CS1566A 20 MHz, 5mV, 0.5 micro sec. £363.40
- CS1577A 35 MHz, 2mV, 0.1 micro sec. £523.25
- CS1820 20 MHz, 2-5mV 1 micro delay sweep £483.00
- CS1830 Mk II 300 MHz, 2mV, 0.2 micro sec (fitted delay line) New low price £453.00
- CS1575 5 MHz, 1mV, 0.5 micro sec. Multi display Audio scope. £312.80

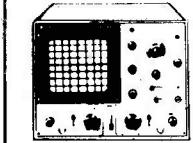SINGLE TRACE
 C013030 5 MHz, 10mV, low sweep for observation below 1 Hz and up to 450 MHz, 75mm display (UK c/p £2.00) £124.20





CROTECH OSCILLOSCOPES

Range of Portable Scopes mains and battery operated. Plus special features (UK c/p £3.00)

- 3030 Single trace 15 MHz, 5mV, 0.5 micro secs. Plus built in component tester, 95mm tube £172.50
- 3131 Dual trace 15 MHz, trg to 35 MHz, 5mV, 0.5 micro sec 130mm tube, plus component tester £276.00
- 3034 Battery-mains dual trace 15 MHz, trig to 20 MHz built in Nicads, 5mV, 0.5 micro secs (Eliminator charger optional £28.75) £356.50

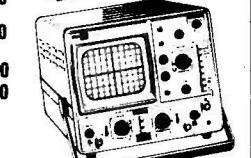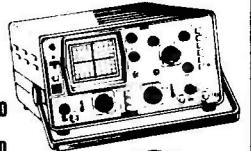Also Available 3033, single trace 3034 3337, dual MHz, 130mm £322.00 £454.00



DIRECT READ HV PROBE (UK c/p 65p)


0/40KV, 20K Volt £18.40



OSCILLOSCOPE PROBE KITS

(UK c/p 50p per 1 to 3) Available BNC plug or Banana X1 £7.95 X10 £9.45 X1-X10 £10.50 Also X100 (BNC only) £16.95

MULTIMETERS

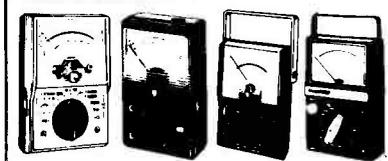

- (UK c/p 65p or £1.00 for two)
 CHOOSE FROM UK'S LARGEST RANGE
- KRT101 10 range pocket 1K/Volt £4.95
 - KRT102 12 range pocket 1K/Volt £5.50
 - T10L 12 range 1K/Volt + overload £5.75
 - MH55 10 range pocket 2K/Volt £6.50
 - ST5 11 range pocket 4K/Volt £7.50
 - AT1 12 range pocket Deluxe 2K/Volt £8.95
 - MH56R 22 range pocket 20K/Volt £11.95
 - YN300TR 19 range plus Hfe test 20K/Volt £14.95
 - KRT501 16 range 10 amp DC range double 50K/Volt £17.95
 - ST303TR 21 range plus Hfe Test 20K/Volt £18.95
 - AT1020 19 range Deluxe plus Hfe Test 20K/Volt £18.95
 - ECT5000 As KRT5001 plus colour scales 50K/Volt £18.95
 - 7081 18 range double 10A DC 50K/Volt £23.75
 - TMK500 23 range plus 12A DC plus cont. buzzer 30K/Volt £24.50
 - 168m 36 range large scale 10A AC/DC 50K/Volt £28.50
 - AT2050 17 range Deluxe plus Hfe tester 50K/Volt £29.95
 - AT210 23 range Deluxe 12A AC/DC 100K/Volt £32.50
 - 360TR 23 range large scale 10A AC/DC Hfe test 50 meg ohm 1KV AC/DC 100K/Volt £39.95

CLAMP-ON-METERS INSULATION TESTERS




- Multi-range clamps all with resistance range, carry case & leads. Also digital and DC clamp in stock (UK c/p 75p)
- ST300 300A 600V 9 ranges £28.50
 - ST310 300A 600V 9 ranges £32.95
 - K2802 150A, 600V, AC 7 ranges £35.95
 - *K2806 300A, 600V, AC 8 ranges £49.50
 - K2803 300A, 600V, AC 9 ranges £59.95
 - K2903 900A, 750V, AC 9 ranges £77.50
 - K2103 1000A, 750V, AC 9 ranges £95.00
 - *Optional temperature probe £13.80
- ELECTRONIC INSULATION TESTERS
 Battery operated complete with carry case (UK c/p £1.00)
 YF500L 500V/100Meg. Plus 0-100 ohm £65.00
 K3103 600V/100Meg. Plus 0-2.6K ohm £109.00
 K3106 500V & 1000V, 1000 & 2000Meg. £119.00
 K4101 Earth resistance tester £149.00
 M500 Hand cranked insulation tester 500V/100Meg. £79.50

THANDAR - SINCLAIR

Reliable low cost portable instruments, bench models all 25.5 x 15 x 15cm. Generators mains operated rest battery (supplied). UK c/p Hand models 65p bench £1.15

- DIGITAL MULTIMETERS (3% digit LCD)
- TM354 Hand held, DC 2A, 2m ohm, 1mV - 1000V DC, 500V AC £45.94
 - TM352 Hand held, DC 10A, Hfe test, Continuity test £57.44
 - TM353 Bench 2A AC/DC 1000V AC/DC 20M ohm. Typical 0.25% NEW LOW PRICE £86.25
 - TM351 Bench, 10A AC/DC, 1000V AC/DC, 20M ohm £113.85
- FREQUENCY COUNTERS (8 Digit)
- PFM200A Hand held LED 200 MHz 10mV (600 MHz with TP600) £67.50
 - New Model fitted BNC sockets. £126.50
 - TF040 Bench LCD, 40 MHz, 40mV (400 MHz with TP600) £166.75
 - TF200 Bench LCD, 200 MHz, 10-30mV (600 MHz with TP600) £166.75
- TP600 600MHz + 10 Prescaler 10 mV £43.13
- GENERATORS (All bench models) mains operated,
- TG100 Function 1Hz-100 KHz. Sine/SQ/Triangle/TTL £90.85
 - TG102 Function 0.2 Hz-2 MHz Sine/SQ/Triangle/TTL £186.75
 - TG105 Pulse, 5 MHz-5Hz (200ns-200ms) various outputs £97.75
- OSCILLOSCOPE (Bench model low power portable)
 10 MHz 2" trace, 10mV, 0.1 micro sec. All facilities. £159.85
 Model SC 110
 Rechargeable battery pack £8.63, AC adaptor/charger £5.69
- OPTIONAL ITEMS
 Carry case (bench only) £6.84 AC Adaptors (state model) £5.69
- TH301 DIGITAL thermometer handheld - 50° to 750°C £68.43

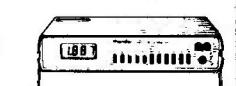

KEITHLEY PROFESSIONAL DIGITAL MULTIMETER UK c/p 75p

Model 130, 25 range. Easy to hold and use LCD DMM. Size 7 x 3.1 x 1.5

Ranges

- DC Volts 200mV-1000V 0.5% 100 micro volt
- AC Volts 200mV-750V 1% 100 micro volt
- DC current 2mA-10AMP 1-2% 1 micro amp
- AC current 2mA-10AMP 2% 1 micro amp
- Resistance 200 ohm-20 Meg 0.5% 0.1 ohm

Model 129 as above £79.35 £102.35



TV COLOUR GENERATORS

- PAL UHF and VHF Models
 - LC6393 VHF 6 pattern £143.75
 - LC6392u UHF 15 pattern £228.85
 - LC6392v VHF 15 pattern £231.15
 - LC6399 VHF/UHF 13 pattern £572.70
 - MC101 UHF pocket colour £162.50
- Fitted NICADS

LOGIC PROBE (UK c/p 45p)

Leader LDP76 50 MHz, 10MEG ohm, 10n Sec. with carry case Model 125 as above £78.25 CP10 10MHz Probe £20.50



SCOPE ADD ON UNITS

SUITABLE FOR ALL SCOPES

- LTC905 Semiconductor Curve tracer £95.45 (post 85p)
- HZ65 Component Tester £29.95 (Post 55p)

AUDIO ELECTRONICS CUBEGATE LIMITED
 301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564
 ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2
 WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order
 Allow up to 10 days for delivery

FREE CATALOGUE
 Send large SAE (20p UK) Schools, Companies, etc. free on request.

ALL PRICES INCLUDE VAT

ROBOT MODULES

A brace of projects for our mobile this month; a digital PWM interface board for the motor controller so your computer can take your robot for a walk, and an optical sensor so it won't run over your cat/budgie/kids. Here's the first one. Design and development by Rory Holmes.


The digital pulse width modulator is constructed entirely from CMOS logic ICs to provide pulse control of two independent channels. Pulse width modulation can be used to control a variety of analogue functions; this design is offered to allow computer control of ETI's Dual Motor Switching Amplifier, featured in part 1.

Binary counters are used to count both the ON and the OFF periods of the mark-space cycle; thus the duty cycle is independent of the timing circuitry, being an exact ratio of two numbers.

The duty cycle data for either channel is loaded through an eight bit port common to both, and is addressed to a particular channel by the use of two strobe lines. When a strobe line is taken low the input data is latched into the associated control channel, which generates a pulse width corresponding to the input value. The pulse width will remain at this value after the data has changed and until its strobe line is activated again. The minimum strobe pulse required is 50 μ s; thus both motor speeds can be changed in about 100 μ s.

To suit the standard eight bit data bus of most microprocessors we have allowed seven bits for controlling the pulse width, with a further bit for setting the forward/reverse motor direction. Pulse widths can thus be obtained with a resolution of one part in 128. With the modulation frequency set at 20 kHz (just above audibility), the pulse width can be increased from zero in 390 ns increments up the maximum of 50 μ s; this represents 100% duty cycle modulation (50 μ s = one cycle at 20 kHz).

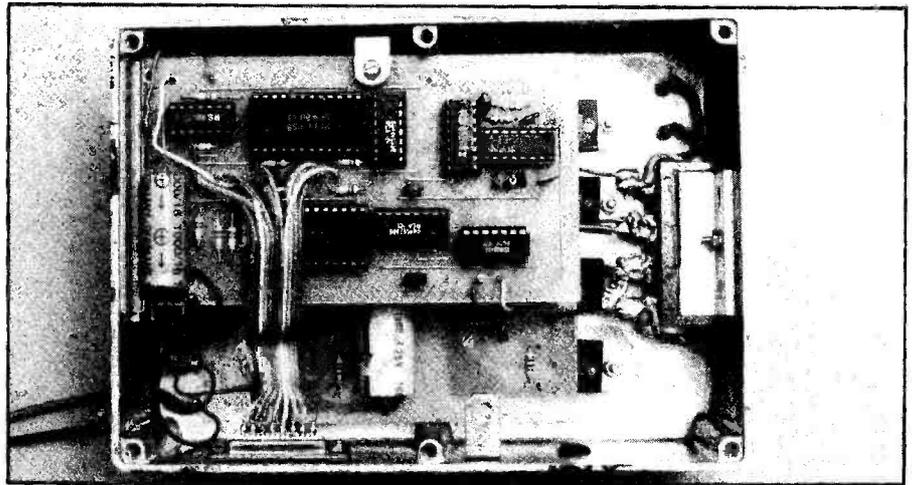Timing signals for pulse generation can, of course, be implemented directly with software from the controlling microprocessor; however, this creates large overheads on processor time. Furthermore, any application software must be designed around these timing routines which can soon become a nightmare of interactive real-time programming.



This photo shows the digital PWM board mounted above the motor driver board from Part 1 of the series.

Our design strategy has been to dedicate external hardware circuitry to the mundane and repetitive tasks, thus freeing the controlling processor for running the more sophisticated command programs.

Figure 2 shows the circuit diagrams of both channels with the accompanying description. The unit is assembled on a PCB which fits inside the existing motor driver amplifier case and runs off the same 12 V power source. A 15-way D-type cannon socket mounted on the side of the diecast box provides input for the programming data.

Construction

The PCB should be assembled as illustrated in the overlay diagram. We recommend soldering in the 14 links first, followed by the resistors and IC sockets. Veropins should be inserted at all the input and output terminals, 17 in all, and finally the capacitors can be soldered in. Before plugging in the ICs, connect a 12 V power source at the supply points shown and check the ground and positive rail voltages at all the IC sockets. If all is well, a short length of 11-way ribbon cable can be wired up to the eight input bits, ground, and the two strobe lines.

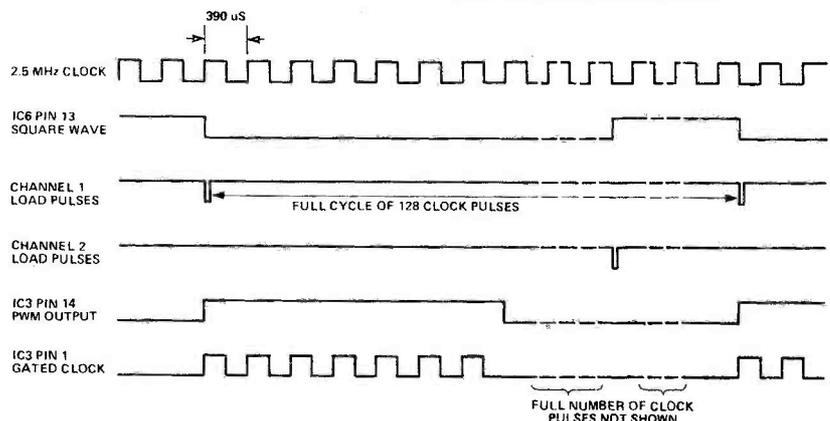


Fig. 1 Timing diagram for the digital pulse width modulator.

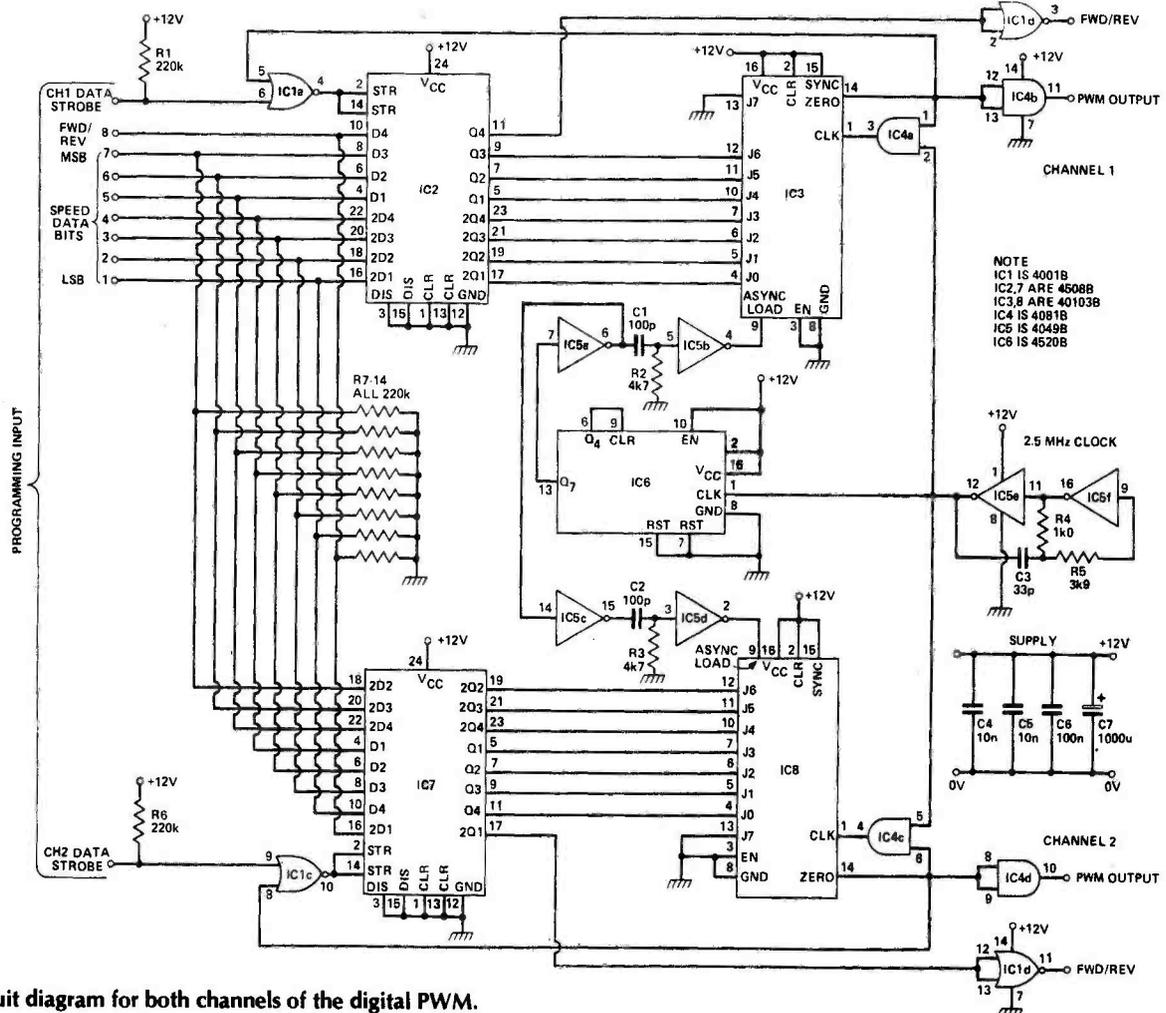


Fig. 2 Circuit diagram for both channels of the digital PWM.

HOW IT WORKS

Each of the two control channels operates in an identical fashion with some circuitry common for both. We shall describe the basic circuit action referring to the upper half of the circuit diagram in Figure 2. IC3 is the heart of this circuit, being an eight bit binary down counter with presettable data inputs; it is used to generate the variable pulse widths. The eight data bits presented at the preset inputs J0 to J7 are loaded into the counter when the synchronous load input on pin 9 is pulsed to logic low. If a clock is now fed to pin 7 the counter will start counting down to zero from this preset value. When zero is reached the previously high zero detect output on pin 14 goes low. In our configuration this zero output is used to gate the clock input via AND gate IC4a. Thus, as soon as zero is reached the clock is disabled, leaving pin 1 low and so allowing the zero output on pin 14 to remain low also. The counter IC3 can only be restarted by another load pulse to pin 9, which presets the count start value and returns the zero output to logic high, thus enabling the clock for the down count. A look at the timing diagram of Fig. 1 should clarify this sequence.

The 'zero detect' output on pin 14 directly provides the required PWM signal and is buffered by AND gate IC4b before driving the power switching stage. The load pulses are produced by the edge detector implemented using inverter gates IC5a and b. These negative-going pulses are very narrow, with a width set by differentiator C1/R2 of about 200 nS; they are derived

from the negative-going edges of a square wave produced by the counter IC6. The load pulses for the other channel are generated in a similar fashion, but from the positive-going square wave edges. This ensures the 180° relative phase offset of the two PWM signals, necessary for reducing the peak supply current.

This square wave determines the full period of each pulse width cycle and thus sets the constant frequency of the PWM output. The counter IC6 is a dual four-bit binary counter; the stages are wired in cascade for ripple counting, and the square wave is taken from the seventh output bit. A 2.5 MHz astable clock built around IC5e and f drives both IC6 and the down counter IC3. IC6 will thus divide the master clock by 128, providing load pulses at a repetition frequency of 20 kHz which is the required modulation frequency. For a maximum duty cycle modulation of 100% the down counter must have a maximum start count of 128, giving a resolution of one part in 128. This is achieved by using only the first seven input bits of IC3 and taking the eighth to logic low. The pulse width is thus variable from 0 to 50 μS in 400 nS increments. The eighth bit of the input port is used to set the forward/reverse direction of the motor.

The pulse width data for the preset inputs of counter IC3 must be continuously available, since it is loaded afresh for each cycle on the negative-going edge of the asynchronous load pulse. The eight bit data port from the 'outside world' is thus latched

by IC2, a dual four bit hold-follow latch (the CMOS 4508). When the 'store' inputs on pins 2 and 14 are logic high the data appearing at the Q outputs will follow the data on the inputs; when 'store' is taken low the current data is held internally and remains on the Q outputs to control the down counter.

The corresponding data input bits of each control channel on IC2 and 7 are wired together to form a common input port; data is thus altered for a particular motor channel by taking its associated store input to logic high. Strobing in new speed data is achieved using IC1a, a NOR gate. One input, the strobe line, is held normally high by R1, and the other input is taken from the PWM output.

When the strobe line is now taken low the store input will only go high as the PWM output signal goes low. This arrangement ensures that any new data will be stable when it is loaded into the down counter; it also prevents the forward/reverse control from changing state while the motor driver transistors are turned on. Once the required data has been set up on the inputs, the data strobe line must be taken low for a minimum period of 50 μS to ensure the data has been latched. NOR gate IC1b is used to buffer the forward/reverse control line before it leaves the PCB. The 12 V power requirement is taken from the motor driver stage described in Part 1, with C7 providing smoothing and C4, 5, and 6 decoupling the fast switching pulses.

PARTS LIST

DIGITAL PWM

Resistors (all 1/4 W, 5%)

R1,6-14	220k
R2,3	4k7
R4	1k0
R5	3k9

Capacitors

C1,2	100p ceramic
C3	33p ceramic
C4,5	10n ceramic
C6	100n ceramic
C7	1000u 16 V axial electrolytic

Semiconductors

IC1	4001B
IC2,7	4508B
IC3,8	40103B
IC4	4081B
IC5	4049B
IC6	4520B

Miscellaneous

PCB (see Buylines); Veropins.

BUYLINES

No problems at all here; most mail order companies advertising in this issue should be able to supply the components. See page 82 for the price of the PCB.

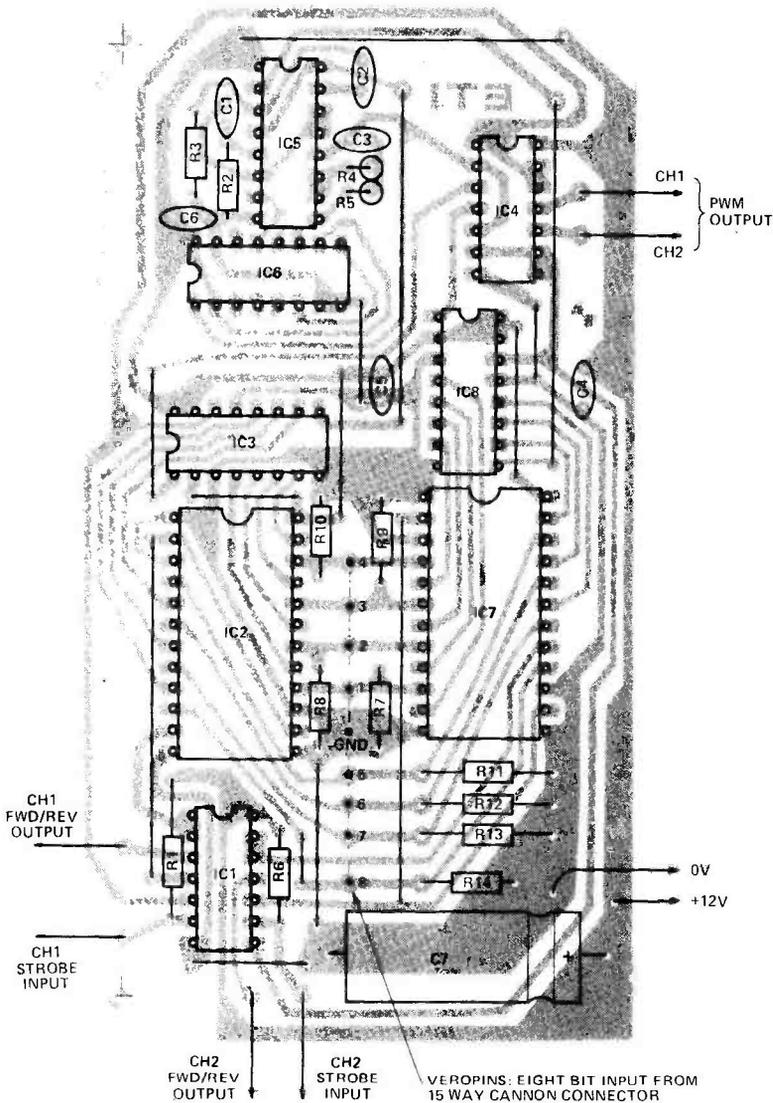


Fig. 3 Component overlay for the PWM board.

Testing Times

With nothing connected to the ribbon cable inputs, the two pulse width modulation outputs should be continuously low and the two FWD/REV outputs should be high (you may need to briefly touch the strobe input wires to a ground terminal). These outputs may be observed with either a 12 V FSD meter or a scope. If a scope is used, the 2.5 MHz clock can also be checked; a square wave should be observed on pins 2 and 5 of IC4.

Pulse width control for each channel may now be verified. Wire bit seven of the ribbon cable to the positive terminal. When either strobe is now taken briefly to ground, the corresponding PWM output line will change to a square wave. The duty cycle is now 50%, this ratio being 64 (bit 7) divided by 128 (full cycle), and

the meter will read 6 V. If a scope is being used the square wave pulse trains from each channel can be observed; they should be 180° out of phase with each other (in the case of square waves this looks like inversion).

This process can be repeated, taking only bit 1 positive, to give the minimum pulse width of 1/128th of the full 50 uS cycle (about 390 nS). This very small pulse cannot be detected by the meter but can be seen on an oscilloscope. Further bit combinations can be strobed in, to provide varying pulse widths in increments of 390 nS.

Modifications

The eighth bit of the data input port is used to set the forward/reverse signal line. For applications that do not require a separate direction signal, ie a computer-controlled pulse generator,

this bit may be utilised for higher resolution pulse width control; the full eight bits give a resolution of one part in 256. To implement the modification the following changes can be made.

The tracks to pins 1 and 2 and pins 12 and 13 of IC1 should be cut; this provides two unused NOR gates, whose input pins should be connected to the nearest ground track via insulated links. The tracks to pins 13 of both IC3 and IC8 should be cut; pin 13 of IC3 is now linked to pin 11 of IC2 and pin 13 of IC8 to pin 17 of IC7. Pin 7 of IC5 should be cut from its track and linked to pin 14 of IC6. The forward/reverse input line, bit 8, now becomes the most significant bit of the pulse width control.


The pulse width modulator now works in exactly the same way as before but with an output frequency of 10 kHz, exactly half the original value.

Once the board has been tested it can be mounted using brackets or adhesive PCB slots directly above the motor driver board in the diecast box. The two supply pins are wired to the existing 12 V input terminals, while the FWD/REV and PWM outputs are connected to the corresponding inputs of each motor driver channel. We used a 15-way D-type Cannon socket bolted onto the case side for the eight bit data input. The two strobe lines and ground wire should also be wired to this connector.

ETI

PROXIMITY DETECTOR

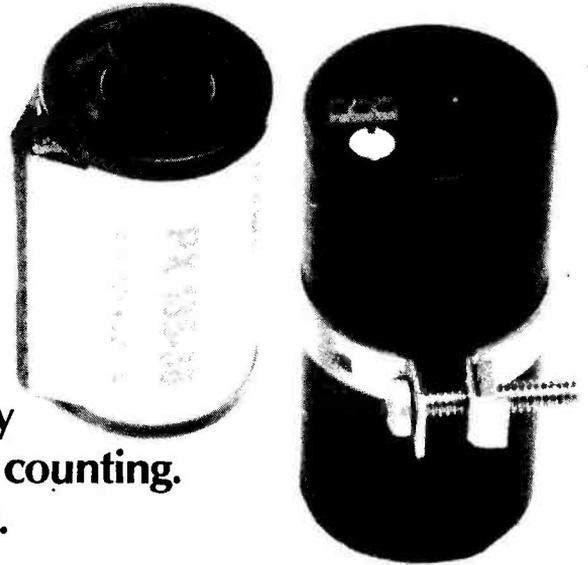This project will endow your man of steel with infra-red vision; and it's not much bigger than a human eyeball. Alternatively you can use in applications such as batch counting. Design and development by Rory Holmes.



This project provides a very useful means of detecting the presence of *anything* by the reflection of infra-red light, and provides a direct digital output of object detection.

The transmitter and receiver of the infra-red beam are both mounted on the same miniaturised PCB, which is housed in a short length of aluminium tube for screening and protection. By the use of modulation and high power bursts of infra-red at a very low duty cycle, a detection range of over a foot is achieved. The receiving photo-amplifier is tuned to the same modulating frequency of 1 kHz, and thus provides good rejection of stray infra-red interference. Bright lights will not affect the operation of the module.

The module features a wide supply voltage range, with an LED to indicate correct operation. A preset adjustment pot at the rear of the sensor allows the detection range to be preset at any distance between 1 and 35 cm.

Construction

Although the PCB layout (Fig. 2) is quite dense, with several vertical mounting resistors, the assembly should be straightforward. The only component of note is PR1, a ¼" 20 turn rectangular cermet preset. These are readily available, though, and should fit the board exactly. The power transistor Q3 is mounted flat, with the metal side face down; likewise, observe the orientation of the other transistors. Photodiode D1 has a chamfered edge on one side; this is mounted to face the infra-red emitter LED2, so allowing the sensitive surface to face outwards. The infra-red LED should be mounted with the flat side facing away from the photodiode (the flat identifies the cathode). After assembly of the board it is important to mount a small guard between the infra-red emitter and detector, to prevent infra-red light

passing directly to the detector before it has been reflected. The guard should be a 7 mm square, cut from un-etched PCB or a piece of aluminium. It can be stuck between the two diodes and directly in front of C4 with a blob of superglue.

The board is mounted in a 55 mm length of aluminium tube, of internal diameter 27 mm or greater.


The diagram of Fig. 3 illustrates how a 6BA nut is soldered sideways onto the PCB track directly beneath the 3-way connector socket. Holes are drilled in one end of the tube to mate up with the indicator and preset adjustment screw. A rectangular hole also needs to be cut, allowing access to the connector socket. A 6BA bolt can now be used to tighten the board against the tube end. The sensing end of the tube may be covered with anything that is transparent to infra-red (red filter plastic polarising sheet, or just clear plastic). If openings are cut for the emitter and detector then an aluminium disc could also be used. The disc should be cut to fit the tube and mounted flush against the small guard plate with epoxy. The sensor tube may be mounted with a circular clamp that tightens round the tube; this can be seen on the photographs of our prototype.

C2, the smoothing capacitor, is shown on the circuit diagram as a

100uF 10 V tantalum electrolytic. This value was chosen to fit on the PCB and consequently limits the supply to 9 V maximum, although the circuitry is capable of operating up to 35 V. To allow higher supply voltages, change C2 to 22uF 35 V tantalum. An additional electrolytic of 100uF 40 V should be mounted underneath the board and soldered to the same pads as C2.

The sensor is now ready for testing, and the three way connector plug should be wired to a suitable power source capable of providing 100 mA (this is for the benefit of the bulb, if used; the circuit itself only takes 20 mA). A PP9 9 V battery is adequate. One of the test circuits illustrated in Fig. 4 should be adopted; if the LED arrangement is used, for example, the LED will be on when the sensor points into free space. Start with the preset fully anticlockwise; this gives minimum sensitivity and the sensors should not trigger at all.

Keeping the sensor pointed at free-space, the preset should be turned clockwise to increase the sensitivity until the LED just goes out. The preset should now be backed off until the LED just comes on again, thus setting the maximum range. Placing a hand about 12" in front of the sensor will now turn off the test LED, while striking a match next to the sensor should make no difference!

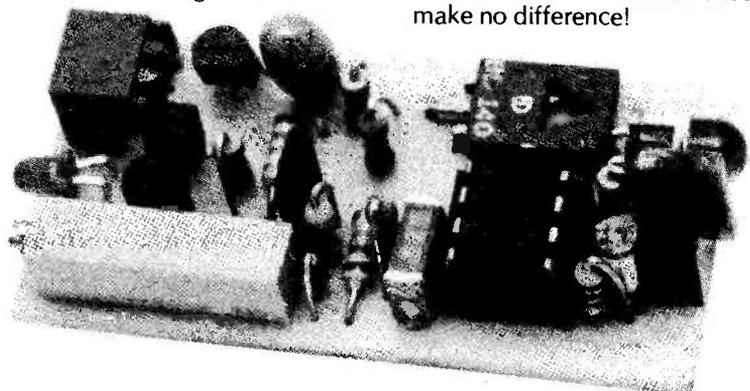

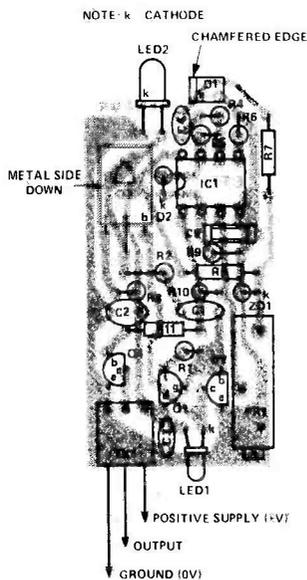


Fig. 1 Component overlay for the optical sensor. The photos overlay show how small the unit is.

HOW IT WORKS

The proximity sensor works on the principle of transmitting a beam of modulated infra-red light from the emitter diode LED2, and receiving reflections from objects passing in front of the beam with a photodiode detector D1. The circuit can be split into three distinct stages; the infra-red transmitter, the photodiode amplifier, and a variable threshold comparator.

The transmitter provides 1 A peak current pulses for 10 μ s through the infra-red emitter diode, at a repetition rate of 1 kHz. Q1 is arranged as a constant current source to supply the base of Q2, and to charge up C1. As C1 charges up, the base voltage of Q2 rises until it reaches about 0V6 relative to ground. Q2 then turns on, so turning on another constant current source formed by Q3 and LED1. This current source sets a temperature compensated voltage of about 1V5 across R3, thus defining a current of 1 A through the infra-red emitter LED2. After Q3 turns on, a negative pulse through C1 turns off Q2 again, thus re-starting the oscillation cycle. The current pulse, determined by C1 and R2 is set at 10 μ s. A 10 μ s pulse every 1 ms is equivalent to a duty factor of 1:100, so that although 1 A peak pulses are generated, the average current required is only 10 mA. Capacitors C3 and C2 are there to provide power supply smoothing to decouple the fast current pulses.

The detector is built around IC1, a CA3240 dual op-amp. IC1a is configured as an inverting amplifier with a gain of -2. It amplifies the infra-red signal picked up by photo-diode D1. C4, which couples the diode signal to IC1a, acts as a high-pass filter in combination with the input impedance of the amplifier. Positive-going pulses of 10 μ s duration are fed from the output, via rectifier D2, to a smoothing filter C5 and R9. This provides the signal voltage reference for the inverting input of comparator IC1b. A 2V7 reference, formed by R8 and ZD1, provides the biasing voltage for the photodiode through R7. It also provides the reference voltage for the non-inverting comparator input, set by potential divider PR1. R10 creates positive feedback round the comparator, to improve the switching, and introduce a small amount of hysteresis. Thus, if a reflected light signal received due to the presence of an object rises above the threshold set by PR1, the comparator output will go into negative saturation. The comparator output is used to turn Q4 on or off, thus providing an open collector output for digital interfacing to logic circuits.

NOTE:
IC1 IS CA3240
Q1 IS 2N3819
Q2,4 ARE BC184L
Q3 IS BD140
D1 IS PHOTODIODE
D2 IS 1N4148
ZD1 IS 2V7 400mW ZENER
LED1 IS 3mm RED LED
LED2 IS INFRA-RED LED

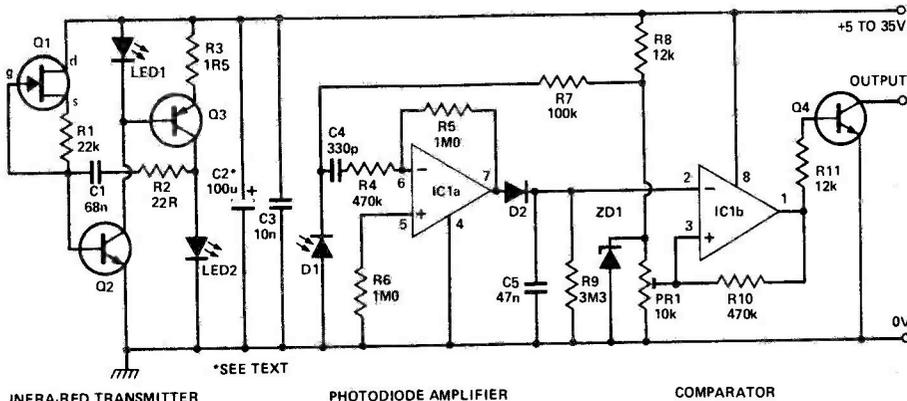


Fig. 2 Circuit diagram for the sensor.

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)

R1	22k
R2	22R
R3	1R5
R4,10	470k
R5,6	1M0
R7	100k
R8,11	12k
R9	3M3

Potentiometers

PR1	10k $\frac{3}{4}$ " 20 turn cermet trimmer
-----	--

Capacitors

C1	68n ceramic
C2	100u 10 V tantalum
C3	10 n ceramic
C4	330p ceramic
C5	47n polycarbonate

Semiconductors

IC1	CA3240
Q1	2N3819
Q2,4	BC184L
Q3	BD140
D1	Photo-diode (TIL100 or similar)
D2	1N4148
LED1	3 mm red LED
LED2	infra-red LED (TIL38 or similar)

Miscellaneous

PCB (see Buylines); three-way PCB plug and socket (see Buylines); aluminium tube (27 mm diameter, 55 mm long).

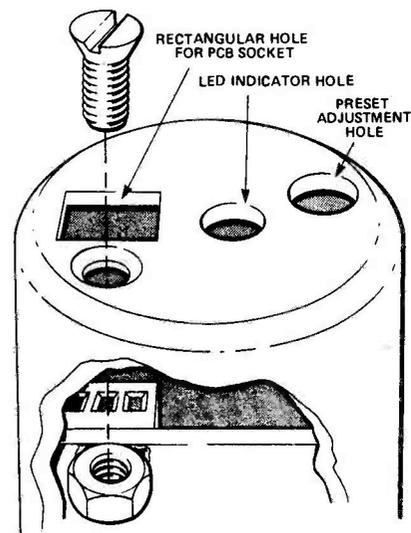


Fig. 3 This is how we mounted the PCB in the aluminium tube. The nut is soldered to the ground track under SK1.

BUYLINES

The only out-of-the-ordinary thing used in this project is the inter-PCB plug and socket (also known as the KK system). This, of course, is not essential, but if you want to use it for neatness it can be obtained from Watford, or via your local supplier from RS Components. We are selling the PCB; the order form is on page 82.

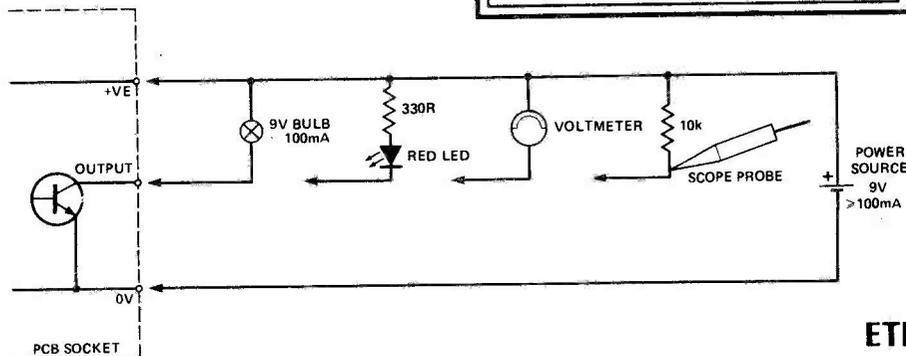


Fig. 4 Any of these test circuits may be used to check out the sensor.

HAPPY MEMORIES

Part type	1 off	25-99	100 up
4116 200ns	0.95	0.85	0.70
4116 250ns	0.90	0.80	0.60
4816 100ns For BBC comp	3.30	2.95	2.70
4164 200ns	6.15	5.25	4.65
2114 200ns Low power	1.25	1.15	0.95
2114 450ns Low power	1.20	1.10	0.90
4118 250ns	3.45	3.15	2.65
6116 150ns CMOS	4.95	4.45	3.65
2708 450ns	1.95	1.90	1.80
2716 450ns 5 volt	2.25	2.15	1.95
2716 450ns three rail	6.40	6.00	4.95
2732 450ns Intel type	4.25	3.95	3.35
2532 450ns Texas type	4.25	3.95	3.35

Z80A-CPU £4.75; Z80A-P10 £4.95; Z80A-CTC £4.25
 Low profile IC sockets:
 Pins 8 14 16 18 20 22 24 28 40
 Pence 9 10 11 14 15 18 19 25 33
 Soft-sectored floppy discs per 10 in plastic library case: 5 inch SSSD £17.00; 5 inch SSDD £19.25; 5 inch DSDD £21.00; 8 inch SSSD £19.25; 8 inch SSDD £23.65; 8 inch DSDD £25.50
 74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces.

Write or phone for list.

Please add 30p post & packing to orders under £15 and VAT to total. Access & Barclaycard welcome. 24 hour service on (054 422) 618. Government & Educational orders welcome, £15 minimum. Trade accounts operated, phone or write for details.

HAPPY MEMORIES (ETI)

Gladestry, Kinston, Herefordshire HR5 3NY
 Telephone: (054 422) 618 or 628

SINCLAIR COMPUTERS

We are the leading world-wide Sinclair expert specialist including Norway, Sweden, Finland and Denmark. Write for our surprisingly low prices.

PRINTERS

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard.
 Seikosha GP100A £205. Centronics 737 £335. Centronics 739 £419. OKI Microline 80 £275. OKI Microline 82A £399. Epson MX701 £259. Epson MX801 £339. Epson MX80F/T1 £375. Epson MX80F/T2 £375. Epson MX100 £495.

VIC 20 COMPUTER

Two special offers: If it is bought with the Vic 20 we can supply the cassette recorder for £30.43. Alternatively, we will supply a free kit with each Vic 20 to allow the use of an ordinary cassette recorder. Vic 20 £165. Ordinary cassette conversion kit £6. Vic 20 cassette recorder £36.50. Vic printer £189. Floppy disc drive £309. Ram cartridges: 3K £24, 8K £35, 16K £57. Game cartridges: Superlander, Alien or Avenger £15 each. Joystick £6.52. Intro to Basic Part 1 £12. New low cost memory board, no need for a mother-board, comes with 3K ram on board + socket for a ram + sockets for another 24K of low current Nimos ram (Just plug in chips to expand memory) £49. Extra memory chips £7.80 per 2K.



UK101 AND SUPERBOARD

UK101 32 x 48 display expansion kit £9. The below accessories suit both the UK101 and Superboard: Extra ram £2.10 per K. 16K memory expansion complete kit £50, built in 58. 32K memory expansion kit £74, built in £82. Ceyman £22.50. Wemom £14.95. Word processor program £10. Centronics Interface kit £10. 610 expansion board £179. Cased minifloppy disc drive with DOS £275. The below suit only Superboard: Guard band kit £10. Series 1 only 30 x 50 display expansion kit £14.

SWANLEY ELECTRONICS

Dept ET1, 32 Goldsel Rd., Swanley
 Kent BR8 8EZ
 Tel Swanley (0322) 64851

NEW GENIE 1 £299

EG3014 Expansion box with 16K/32K ram £199/£213. We are Cumana disc drive specialists for the Genie. Single sided disc drives: 40 track £205, dual 40 track £345, 80 track £269, dual 80 track £469. Double sided disc drives: 80 track £399, dual 80 track £699. Double density converter £72. Parallel printer interface £36.

5V POWER KITS

Fully stabilised 5V computer and TTL power kits. Short circuit and over voltage protection. 1.5A £7.83, 3A £12.17, 6A £20.

BATTERY ELIMINATORS*

3 way type 6/7.5/9V 300ma £3.50. Stabilised model 3/6/7.5/9V 400ma £7.95. 100ma radio types with press studs 9V £4.95, 9V + 9V £6.25. Car converter 12V input, output 3/4.5/6/7.5/9V 800ma £3.04.

BATTERY ELIMINATOR KITS*

100ma radio types with press-studs 9V £1.79, 9 x 9V £2.50. Stabilised 8-way types 3/4.5/6/7.5/12/15/18V 100ma £3.12, 1A £8.50. Stabilised power kits 2-18V 100ma £3.12, 1-30V 1A £8.50, 1-30V 2A £15.30. TTL and computer supplies 5V stabilised: 1.5A £9, 3A £14, 6A £23. 12V car converters 1A £1.62.

TV GAMES*

AY 3-8550 + kit £9.26.

BI-PAK AUDIO MODULES*


AL30A £4.35. PA12 £9.31. PS12 £1.75. T538 £2.90. AL60 £5.62. SPM80 £5.26. BM180 £6.36. Stereo 30 £19. AL80 £8.56.

COMPONENTS*

1N418 1.5p. 1N4002 3.7p. NE555 8 di 20p. 741 8 di 14p. 2114 low current 300ns £1.05. Resistors 5% 1/4 watt E12 10R to 10M 1p, 0.8p for 50 + of one value. Polystyrene capacitors £12.63V 10 to 1000pF 4p; 1n2 to 10n 5p. Ceramic capacitors 50V E6 22pF to 47n 2.5p. Electrolytic capacitors 50V 5, 1, 2mf 6p; 25V 5, 10nF 6p; 16V 22.33mf 6p; 47mf 4p; 100mf 6p; Preset pots subminiature 0.1W horiz or vert 100 to 2MΩ 8P. IC sockets 8 di 8.7p, 14 di 10.1p, 16 di 12p.

Postage £3.50 computers, £4.50 on Printers and 4p on other orders. Lists 27p Post free. Please add VAT to all Prices except those sections marked with a * which already include it. Overseas and official credit orders welcome.

THE BIGGEST NAME IN BRITISH BREADBOARDS

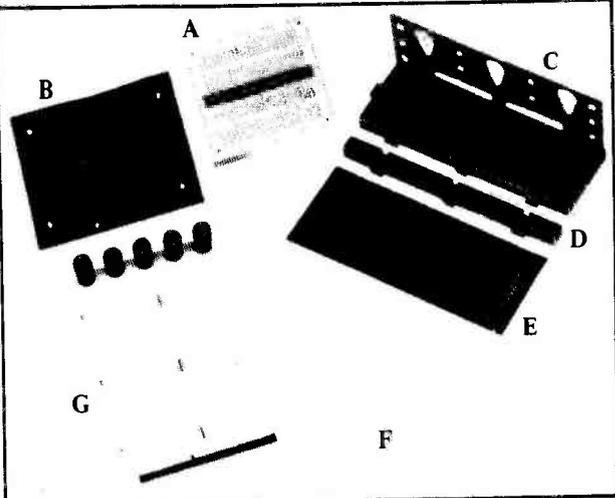

All BOSS Breadboards directly accept .3", .4", .5" & .6" pitch DIL IC's and have numbered and lettered rows and columns allowing exact location indexing.

- A. EuroBreadBoard. 500 contacts, ideal for schools and training establishments.
 - B. EuroSolderBoard. Exact printed circuit board copy of 'A' enabling progression to permanent and rugged assembly.
 - C. BIMBOARD 1. 550 contacts plus component support bracket. BIMBOARD's 2, 3 and 4 also available providing 1100, 1650 and 2200 contacts respectively.
 - D. BIMBUSTRIP. 2 additional power lines, slot onto any 'C', 'G' or BIMBOARD DESIGNER.
 - E. PC BIMBOARD. Exact printed circuit board copy of 'C' plus 'D' enabling permanent pcb circuits to be generated.
 - F. Layout Pad. Exact paper copy of 'E' for planning or recording layouts.
 - G. MPUroBreadBoards. 1422 contacts including power bus strips on all sides. Specifically for MPU circuits it is standard 160 x 100mm Eurocard size.
- Adventures with Microelectronics. A beginners book based on BIMBOARD 1. Covers simple circuits, built step by step and includes component lists and sources.

Note: All BIMBOARD's 1, 2, 3 and 4, BIMBUSTRIP and MPUroBreadBoards slot onto each other thereby providing larger circuit development working areas.

JUST RELEASED BIMBOARD DESIGNERS.

Incorporate 2 BIMBOARDS (4 to special order) plus integral fixed 5V and adjustable ±5V to ±15V power supplies.

BOSS INDUSTRIAL MOULDINGS LIMITED

James Carter Rd, Mildenhall, Suffolk, IP28 7DE
 Tel: Mildenhall (0638) 716101 Telex 818758

KITS, COMPONENTS MICROS & PARTS

**FORGET
YOUR PEN
RING 5 to 10
IT'S COMPONENT
MAIL ORDER MADE EASY**

**OUR NEW SALES NO.
567-8910**
FIVE • SIX • SEVEN • EIGHT • NINE • TEN
(01 OUTSIDE LONDON)
THE NUMBER YOU CAN'T FORGET

**ALL PRICES
EXCLUDE VAT**

DISCO LIGHTING KITS

DL1000K
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.80



DL2100K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum.

Only £8.00
Optional opto input DLA1 £0p
Allowing audio ("beat")-light response.

XK102 3-NOTE DOOR CHIME

Based on a single integrated circuit (SA80600), this kit comes complete with loudspeaker and drilled box (size: 95 x 71 x 35mm) and requires only a PP3 battery and pushbutton to complete.

**ELECTRONIC DOOR
CHIME**



The unit produces a 3-note harmonically related tone sequence when the push-button is operated and may be used to replace any doorbell or switched by logic in such applications as alarms, PA systems and toys. The unit draws less than 1uA from the battery in the standby mode and produces 150mW output which may be readily amplified if a louder sound is required. The small number of components make this an ideal project for beginners.

£5.00

DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.



Price £15.50

NEW 1982 FREE SHORT FORM CATALOGUE SEND SAE TODAY (6" x 9")

We also stock:
Vero products
Antex Soldering Irons
Babani Books

MEMORIES AND MICROS

211495
27082.25
27162.45

PRICES SLASHED

27324.80	8035L5.50
68101.25	M6802(PCPU)3.05
6821P1.25	Z80ACPU3.30
8850P1.50	Z80ACTC2.90
6852P2.55	Z80API02.90

74 LSTTL

LS00 .12	LS14 .48	LS42 .40	LS93 .37
LS01 .12	LS15 .15	LS47 .42	LS95 .48
LS02 .13	LS20 .14	LS51 .15	LS107 .24
LS03 .13	LS21 .15	LS54 .15	LS109 .24
LS04 .14	LS22 .15	LS55 .15	LS112 .24
LS05 .15	LS26 .18	LS73 .20	LS113 .24
LS06 .16	LS27 .15	LS74 .18	LS114 .24
LS09 .15	LS30 .14	LS75 .27	LS123 .51
LS10 .14	LS32 .15	LS76 .21	LS126 .29
LS11 .15	LS37 .17	LS85 .84	LS132 .44
LS12 .15	LS38 .18	LS86 .18	LS160 .40
LS13 .27	LS40 .14	LS90 .32	LS161 .40

CMOS

4000 .14	4025 .18	4081 .22
4001 .14	4026 1.06	4093 .46
4002 .14	4027 .40	4501 .24
4007 .14	4028 .50	4511 .85
4011 .15	4040 .88	4514 1.80
4012 .17	4049 .30	
4013 .36	4050 .30	
4015 .70	4080 .80	
4016 .30	4089 .18	
4017 .86	4070 .24	
4019 .38	4071 .22	
4023 .22	4077 .24	

THE KEY TO YOUR SECURITY IS IN OUR LOCK

If the thought of car thieves, house breakers or people tampering with your electrical and electronic equipment upsets you, we have just the kit for you.

Our **ELECTRONIC LOCK KIT** includes a 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is pre-wired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7x6x3 cms. Power Consumption is 40uA at 5V to 15V d.c.

At only £10.50 + VAT, it will make a smaller hole in your pocket than a bunch of keys!
Electric Lock Mechanism £12.50
Suitable for use with existing door locks and above electronic lock kit.

THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

**ONLY £45 WITH
SO MANY EXTRA
FEATURES.**

FEATURES INCLUDE:-

- 0.5" LED 12 hour display.
- Day of week, am/pm and output status indicators.
- 4 zero voltage switched mains outputs.
- 50/60Hz mains operation.
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets.
- Powerful "Everyday" function enabling output to switch every day but use only one time set.
- Useful "sleep" function—turns on output for one hour.
- Direct switch control enabling output to be turned on immediately or after a specified time interval.
- 20 function keypad for programme entry.
- Programme verification at the touch of a button.

THERE HAS NEVER BEEN A CLOCK CAPABLE OF SO MUCH AT SUCH A LOW PRICE—

(Kit includes all components, assembly and programme instructions & an attractive case).



HOME LIGHTING KITS


These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TDR300K	Remote Control Dimmer	£14.30
MK6	Transmitter for above	£ 4.20
TD300K	Touchdimmer	£ 7.00
TDE/K	Extension kit for 2-way switching fro TD300K	£ 2.00
LD300K	Rotary Controlled Dimmer	£ 3.50



REMOTE CONTROL COMPONENTS

LD271 IR Emitting Diode34
SD4205 Photoconductive Detector36
SL480 IC Pulse Amp1.70
SL480 32 Command Encoder/transmitter2.40
ML922 10-channel receiver + 3 analogue outputs4.20
ML924 Programmable RC Receiver1.90
ML925 A decoder designed for model/hobby control, providing a 2-speed driver motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg gun turret, winch, etc.2.10
Outputs also available for other facilities such as horn, turn indicators, headlights etc.2.10
ML926 16-channel receiver, 4 momentary binary outputs1.40
ML927 16-channel receiver, 4 momentary binary outputs1.60
ML928 16-channel receiver, 4 latched binary outputs1.40
We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself - Send us 30p and a stamped addressed envelope for your copy TODAY!

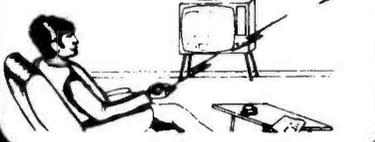

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.

CT1000K Basic Kit£14.90
CT1000K with white box (56/131 x 71mm)£17.40
(Ready Built)£22.50

Add 50p postage & packing + 15% VAT to total.

Overseas Customers;

Add £1.50 (Europe), £4.00 (elsewhere) for p&p.

Send S.A.E. for further STOCK DETAILS.

Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri)

10am to 4pm (Sat)



FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to -

THE ELECTRONICS

11 Boston Road
London W7 3SJ



CLOCK TOWER

UXBRIDGE ROAD

CAR PARK

10 AM AND
RESERVATION
REQUIREMENTS

BOSTON RD

EALING & NORTH
CIRCULAR RD

HANWELL
LT GARAGE

TEL: 01-567 8910 ORDERS
01-579 2842 TECHNICAL (AFTER 3PM)

ENQUIRIES
01-579 9794

BREADBOARDS

In the beginning there was the bird's nest; and engineers saw that it was bad. Since then a great many systems for prototyping and small scale production of electronic circuits have been developed, and Peter Green has been getting his hands on some of the latest ones.

Breadboards have come a long way since the days when a prototype circuit was an impenetrable jungle of wires soldered to nails banged into a piece of wood. (Honest, it really was like that once!) When the plug-in type of breadboard arrived on the scene it was a great advance; components could be unplugged and swapped around with great ease if the circuit didn't work, and if you needed to build larger circuits you simply linked more boards together. However, connections still had to be made with loops of wire all over the place, and the boards were no use for small scale production; this had to be done by track cutting on Veroboard, which can get a bit tedious, or by designing a PCB, which can get expensive.


The new generation of breadboarding systems have been designed to overcome these disadvantages. They fall into two general categories; a 'wrap-and-solder' type where enamelled wire is wrapped around the component pins and then soldered to make the connection, and the IDC types. Insulation displacement connection involves forcing plastic-coated wire between tines of some sort which pierce the insulation and make an electrical connection to the conducting core without breaking the wire. Both types have the same attractive features — that is, the boards are low-profile with neat wiring and no unsightly loops to be pulled off accidentally. Furthermore, all three systems that we looked at come in standard board sizes and are capable of being plugged into a card frame, etc, and used in the same way as a normal PCB.

Quick/Connect

Quick/Connect is an IDC system sold by Dage Eurosem, and many readers will have seen it on their stand at the Breadboard Exhibition last November. A handheld wiring pen is used to push 30 awg solid copper wire into two-pronged tines on the wiring side of the board. The tines pierce the insulation to make a gas-tight joint without soldering; up to two wires will fit into a single tine, giving the equivalent of four levels of wire-wrapping. Components are then inserted into the sockets which form the other end of the tined pins.



The Quick/Connect wiring pen and bobbin.

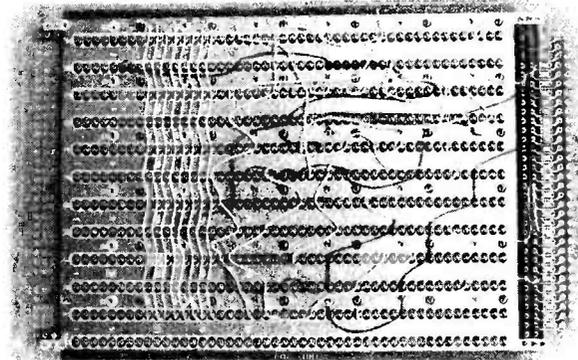

This photo shows the underside of a Quick/Connect Eurocard. Interwiring of the components is done between the tines and a data bus, for example, is easily wired (left of board). At the top of the page you can see the component side of this board; ICs are especially suited to the system.

The Quick/Connect pen is metal and plastic and consists of a tube which terminates in a guide channel/insertion head. Wire is fed down the tube from a bobbin held between offset metal prongs at the top of the pen. This bobbin is also made of metal and is quite large (4 cm in diameter); consequently the pen feels somewhat unbalanced and awkward and doesn't handle easily. At first the prongs held the bobbin so tightly that wiring up was heavy going, but flexing them outwards to give a looser fit cured the problem and made the pen almost effortless to use. The wire itself is available in a wide range of colours so that colour-coding may be employed on complicated boards.

Boards are available either fully populated with sockets or blank for the user to insert sockets as and where he requires. We were provided with a fully populated single Eurocard for this review, so we cannot comment on the ease or otherwise of socket insertion; but it would appear from the catalogue that only industrial users would be interested. A variety of expensive tools, including a press are required (unless you fancy your chances with a mallet), and the hobbyist wouldn't want that sort of outlay; however, in industry people might well prefer this capital outlay to paying for full boards with lots of pins they'll never use. A large range of standard boards either exist or are planned, including various Eurocard sizes and boards compatible with Apple, S-100, Dec Unibus and other microcomputer buses.

Apart from the balance aspect, once the tension in the bobbin is correct the tool is very easy to use; very little pressure is required to force the wire between the tines. However, you need good light and lots of concentration because misalignment of the insertion head over the tines means you sever the wire instead of connecting it (as I found to my dismay on several occasions). When you want to cut the wire, at the end of a wiring run, you'll have to use side-cutters — no built-in cutting device is provided.

Component insertion depends on what you're actually trying to plug in, and is easiest for ICs — after all, this system is primarily designed for digital applications. The IC simply plugs

into the sockets on the component side of the board, where it is firmly held. The manufacturer recommends the use of a special tool but we found insertion fairly easy without one. The problems start when you want to use other types of component. Tantalum, ceramic and polycarbonate capacitors fitted OK, as did 3 mm LEDs and small signal transistors. We found that some ¼ W resistors fitted while others had leads just a little too thick; 1N4148s are OK but not the 1N400X series; while 5 mm LEDs, electrolytics, polyesters and anything in a T0220 package were much too big. The catalogue suggests that such components be soldered to the sockets (bye bye reuseability) or soldered to DIL 'component carriers' (ie header sockets) which are then plugged into place. However, we found a simpler solution; all you have to do is plug in ordinary DIL IC socket into the board sockets and then plug your large components into the IC socket. The photograph shows an example. This would be useful if you wanted to put a 7805 voltage regulator on a computer card, for example.

Quick/Connect is a system which will obviously have a lot of appeal to industrial users, as it offers easy, reliable wiring in development work and a low profile finished board which can be stacked in a card frame on a ½" pitch. However, it's unfortunate that the pen has the odd 'feel' to it (at least it did to me), and of course the price will not be any help to it as regards sales to the hobbyist market.

Distributed by: Dage Eurosem Ltd, Rabans Lane, Aylesbury, Bucks HP19 3RG.

Prices: Fully populated Eurocard £59.00 + VAT. Wiring pen £10.00 + VAT. Reel of wire (50ft) £3.36 + VAT.


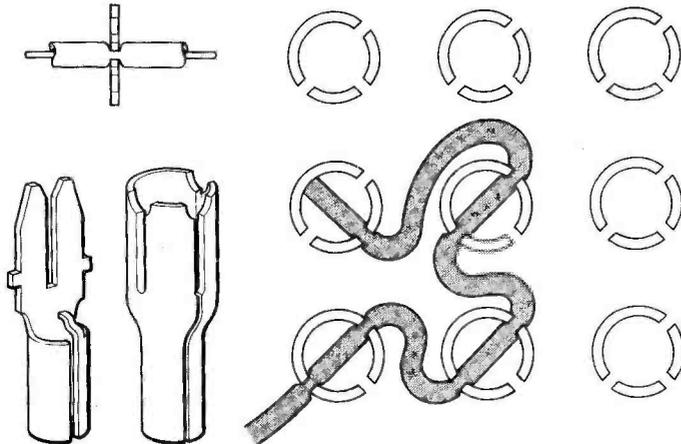


Fig. 1 Working anticlockwise from the top left, we have the IDC principle, the Quick/Connect and Speedwire pins, and a diagram showing the Speedwire termination technique.

Speedwire

This is so new that the sample we played with is one of only five pre-production sets in the country, and jealously guarded it was too! However, we were informed that the launch was to be at the All-Electronics Show here in London; this should have been a few days ago as you read this, so if you went you may have seen the system on the BICC-Vero stand.

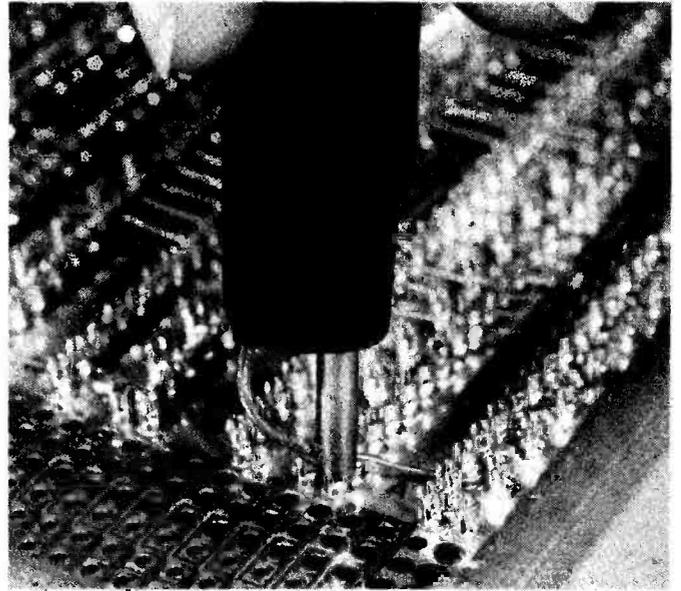Speedwire is a similar system to Quick/Connect but some features show the benefits of industrial hindsight. The pen and



Close-up of the Speedwire pen.

bobbin are plastic with a central metal guide tube, and consequently very light, while the bobbin itself is pivoted on the pen axis rather than off-centre, so that balance and handling are better.

The wiring tines are quite innovative, being a castellated tube — rather like the top of a castle turret, with slots cut on three sides but not the fourth (see the diagram). The pins are arranged in the board so that their slots are all orientated in the same direction. To daisy-chain terminals together, the tool is held so that you insert the wires through the pair of opposing slots, which make the IDC connection as usual. You work across the board in this manner, holding the tool at the same angle to the board, until you reach the endpoint of the signal chain. The tool is then rotated 90° so that the wire is forced through the single slot on the final insertion; this makes the last IDC connection while the unslotted pin face opposite automatically severs the wire. Damn clever, these British...

The Speedwire sockets suffer from the same problem as Quick/Connect, namely that large component leads won't fit; but the same solutions apply and in any case, the Speedwire sockets are slightly larger (all the ¼ W resistors fitted).


When Speedwire becomes available it will be sold both with fully populated boards (again, we saw a single Eurocard), and as drilled boards with fit-them-yourself pins. However, the process is easier than for Quick/Connect as only one tool is required, looking rather like a safety razor. You open it up and insert the pins (which are supplied on a strip like Soldercon sockets), then push them home into the required holes and snap off the carrier strip. The tool ensures that the pins are inserted to the correct depth, and we found it quite easy to use. This is obviously much more economical for the small-scale user, or the large-scale user with only a small amount of components per board.


Initially there will be two kits available. The first contains a plain unpopulated Eurocard, contacts and insertion tool, wiring pen and spare wire, while the second has fully populated Eurocard, a wiring pen and spool of wire, spare wire spools and a pair of Speedwire cutters.

Although we didn't have our hands on it for more than two hours before it was whisked away again, we were impressed by the quality of this system. Indeed, once the kits are available we'd like to have another go with it (that's a hint, Mike!).

Distributed by: BICC—Vero Electronics (Retail Dept), Industrial Estate, Chandler's Ford, Eastleigh, Hants SO5 3ZR.

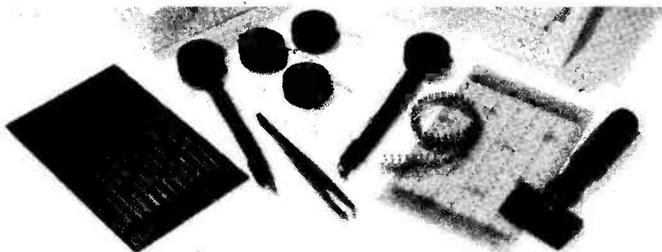Prices: Not yet known. Apply to BICC-Vero for further information.



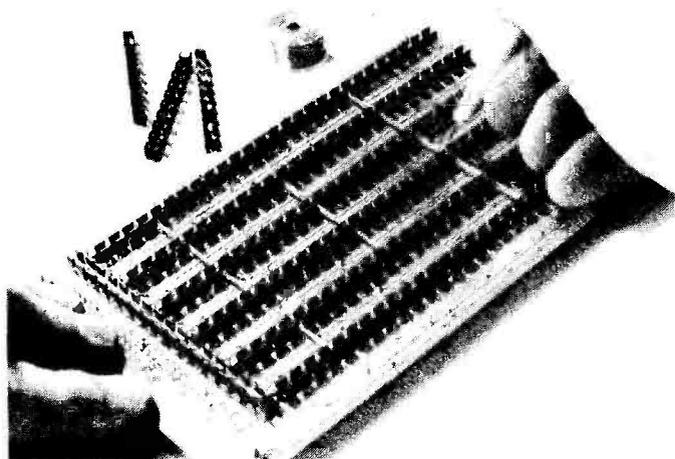


Roadrunner

This is the sole 'wrap-and solder' system of the three mentioned in this article. The system is based around two components; a distribution pen for feeding out the wire, and plastic distribution strips which act as guide channels. In use, this method is quite different from the others under consideration; it is also well established, and was on show at Breadboard 81. The wire used is 36 swg quick soldering enamel (or QSE); the bobbins are only 2 cm in diameter and so the pen is smaller and lighter than the other types.

Before using the pen, the distribution strips must be secured to the wiring side of the board. The manufacturers supply two specially designed "Roadrunner" boards, a single height Eurocard and a double height Eurocard; however, the beauty of the system is that any type of board is suitable since connections are made directly to the component pins rather than to special sockets. For example, Veroboard, bare matrix board (no copper) or even a bit of scrap paxolin you've drilled a few holes in, can all be used if circumstances demand. The plastic strips are of two types; 2" press-fix for use on boards with 1.02 mm diameter holes on a 2.54 mm pitch matrix, and 6" lengths which must be glued in place with a contact adhesive. The photos show the castellated nature of the strips, which can hold a large number of wires while allowing easy routing to the component pins and maintaining a low profile.

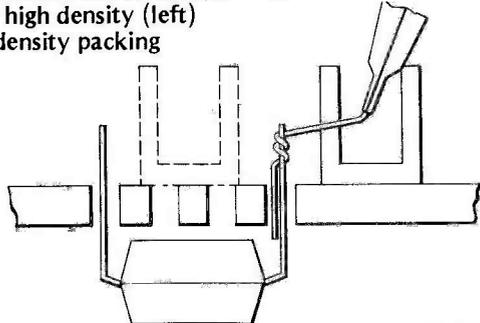How to position the Roadrunner distribution strips for high density (left) and low density packing (right).



A word of warning on the location of the strips is in order here. The pins on the press-fix type automatically locate the strips correctly relative to the matrix, but more care is needed with the other sort. The first time I used Roadrunner I glued down the strip centred on a row of holes, then discovered it was unusable. The strip should cover two rows of holes, so that the strip is equidistant from the rows on either side, otherwise half the IC legs are too close for the tool to wrap. (The diagrams explain all). If you're bothered by this, don't worry — just fit the strips after the ICs are in place and you can see exactly what you're doing.

Naturally Roadrunner is not restricted to ICs or components with thin leads, as are the other systems. Wrapping the wire round the component lead means you can use anything

that will fit through the holes in the board, just like ordinary PCB construction. To use the system most effectively, a wiring schedule should be prepared; this will not only act as a point-to-point wiring guide but also encourages thought about the optimum arrangement of the components. Wire runs should be kept to a minimum for efficient operation.

With all the strips and components in place, wiring can begin. The protruding wire end (about 4 mm) is bent over slightly to prevent it being pushed back up the guide tube, then inserted into the first hole and wrapped several times around the pin. The wire is routed into the strip through one of the cutouts, then along and out to the next connecting point where another wrap is made. When the first run is complete, press down on the wire against the board with the metal guide tube; this severs the wire. Feed out another 4 mm of wire, bend it over and wire the second run. Continue working through the schedule until all the connections have been made.


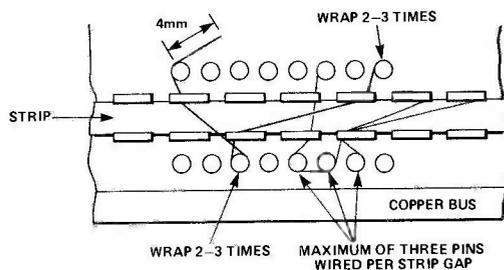


Fig. 3 Plan view of Roadrunner wiring. No more than three pins should be wired from each break in the strip.

To complete the construction, all the connections are soldered using a high temperature iron and resin cored solder. The solder removes the insulating lacquer on the wire and makes good the joint. Note that a high temperature is very important here, otherwise the enamel will not burn off properly resulting in poor or non-existent electrical contact. The bit temperature should be approximately 420°C, and certainly higher than 400°C. My iron wasn't really up to it, but Roadrunner will supply suitable types.

Although the fact that soldering is involved makes mistakes a little harder to correct than with IDC, it is possible. Incorrect wires should be cut at the component and left in place — pulling them out of a tightly packed loom could strip the enamel from adjacent wires and cause short circuits. If you haven't used IC sockets, a faulty IC can be cut away on the component side and a replacement soldered to the original leads.

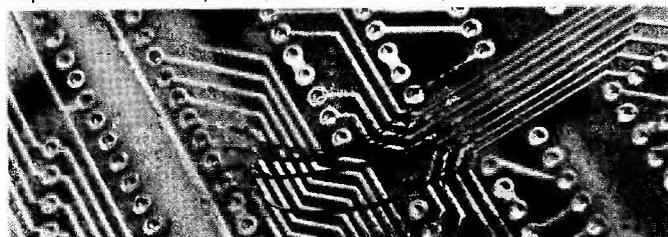To sum up, Roadrunner has many advantages. Any type of component or board can be utilised, and in digital circuits a very high packing density can be achieved. The complete boards have a very low profile and may be mounted in card frames on a 0.6" pitch. Furthermore, existing PCBs may be modified or repaired with the system, unlike the IDC systems.



Modifying a PCB using the Roadrunner system.

Distributed by: Roadrunner Electronic Products, 116 Blackdown Rural Industries, Haste Hill, Haslemere, Surrey GU27 3AY.


Prices: Euro Introkit £15.99 + VAT. Single Eurocard £4.50 + VAT. Wiring Pencil and bobbin £2.99 + VAT. QSE wire (pack of four) £2.12 + VAT. High temperature soldering iron £5.99 + VAT.



MULLARD SPEAKER KIT

40 watt R.M.S. 8ohm DESIGNED BY MULLARD SPECIALIST TEAM IN BELGIUM comprising a Mullard 8" woofer with foam rolled surround, Mullard 3" high power dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loudspeaker terminals and recessed mounting panel. Supplied complete with assembly and cabinet details. Recommended cabinet size 240 x 216 x 445mm.

PRICE £13.90 + £1.50 P&P per kit

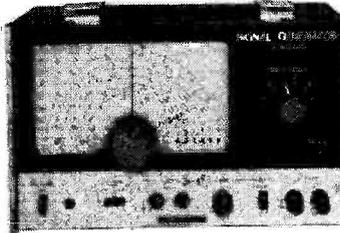

LEADER LSG/16


WIDE BAND SIGNAL GENERATOR

- 100KHz to 100MHz in five ranges
- Up to 300MHz (Harmonics)
- Slow motion tuning
- Internal modulation 1KHz
- External mod. input facility
- Power supply 240V AC
- Size - 150x250x130mm
- Price - £63.25 - UK. Post Free

PRICE £63.25
UK Post FREE

BK ELECTRONICS

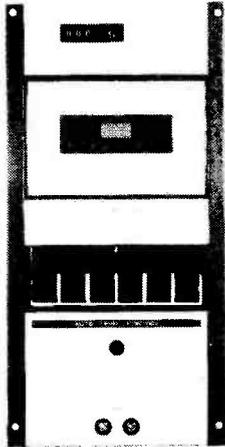Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader



6 piano type keys

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
- Compact size
- 4 3/4" x 13" x 2 1/2" 16
- Easy snap in fixing through panel/cabinet cut out
- Insulated plastic case
- Full wave control using 8amp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads


Innumerable applications in industry, the home, and discos/theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)

BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price: £28.50 + £2.50 P&P

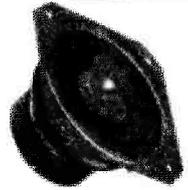


GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems etc.

- Rolled fabric surround
- Twin cone
- 8ohm impedance
- 15 watt RMS
- 1" voice coil
- 13oz magnet
- Frequency range 50/15000Hz

Price: £6.90 each + 75p P&P

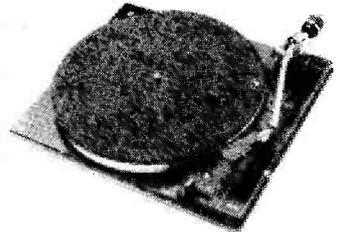


NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price:-


15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each. £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz Sensitivity 95dB. Price £23.70 each. £2.50 Packing and Carriage each.

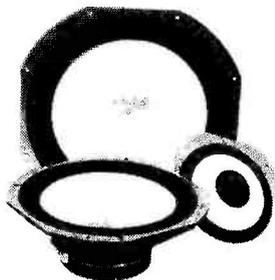8" 50 watt R.M.S. Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz, Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: White cone £8.90 each. Black cone/grill £9.50 each. P & P £1.25 each.



POWER AMPLIFIER MODULES

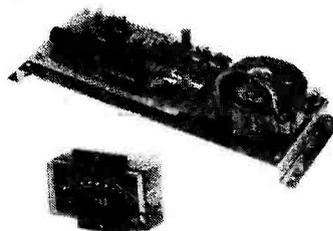

Vu Meter

100 WATT R.M.S.


Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. V.u. meter, available as an optional extra.

SPECIFICATION:

Max. output power 100 watts R.M.S. (OMP100)
Loads: (Open and short circuit proof) 4-16 ohms
Frequency Response 20Hz-25KHz ± 3dB
Sensitivity for 100 watts 500mV at 10K
T.H.D. 00.1%
Size: 360 x 115 x 80mm
Prices: OMP 100W £29.99 £2.00 P&P
V.u. Meter £6.50

PIEZO ELECTRIC TWEETERS MOTOROLA

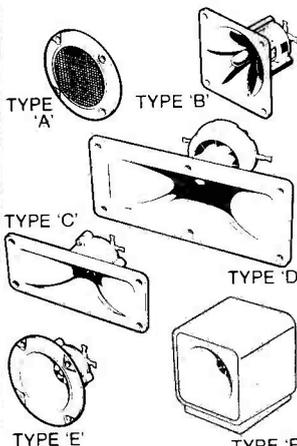Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £3.45 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.35 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.45 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £6.90 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.35 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each. U.K. post free (for SAE for Piezo leaflets).

Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms
Build a quality 60 watt R.M.S. system.



- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover

Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.

Price £22.00 per kit + £2.50 postage and packing. Available separately, prices on request.

12" 80 watt R.M.S. loudspeaker.

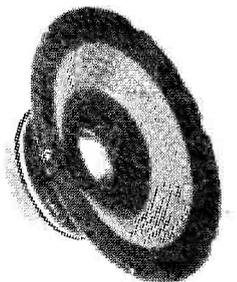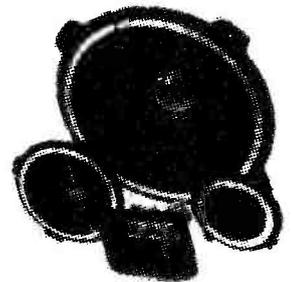A superb general purpose twin cone loudspeaker. 50 oz. magnet 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome. Price £17.99 each + £2.50 P&P.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY


★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



Here's the case... now what's the project?

If you're about to start on a new project, you're no doubt looking for the right enclosure. With around 1,000 different cases and 250,000 case parts currently in stock, we must be your number one choice. Why not send for our catalogue, price £1 including P&P.

Month	Project	Case
June 1981	Antenna Extender	BOA 115
July 1981	Super Dice	BOC 450G
September 1981	LAB PSU	SWF 222X
November 1981	Music Processor	CL2 ADJ
	Voice-over Unit	ACE 150K
December 1981	TV Sound Tuner	CL2 AEL
	Component Tester	MIN 030
		+ MIN 030V
February 1982	I Ching Computer	BOC 708
May 1982	Insulation Tester	BOC 440
	Water Heater Controller	BOC 450

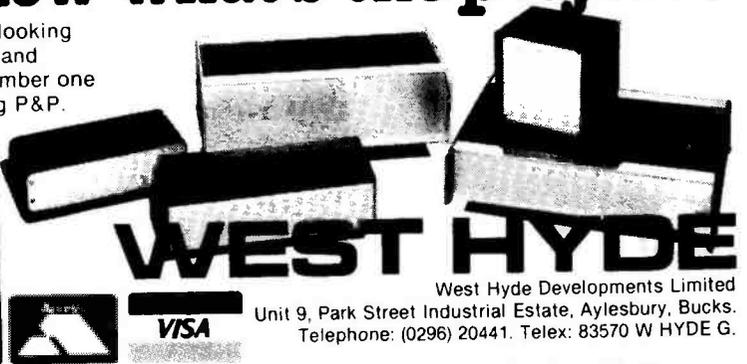


West Hyde Developments Limited
Unit 9, Park Street Industrial Estate, Aylesbury, Bucks.
Telephone: (0296) 20441. Telex: 83570 W HYDE G.

Written or telephone orders accepted from Access and Barclaycard holders.

8" FLOPPY DISC DRIVES

1.6 Megabyte Double Sided Double Density
BRAND NEW DRE7200 Floppy disc drives at a ridiculously low price

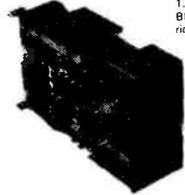- 1.6 megabyte capacity.
- Double Sided.
- Double Density.
- 154/77 Tracks
- 240V AC + 24u to 5v
- Will also read/write single sided single density
- Internal stepping allow coupling to most systems
- User Handbook included
- ONLY £200.00 + £5 carr



Honeywell Bull D120 10 megabyte Hard disc.
BRAND NEW ONLY £450.00 carr. £10.00
DRE 4000A 6258-99011 hard exchangeable disk
BRAND NEW ONLY £600.00
Plessey standby invertors 375va mains from car batteries
ONLY £110.00
Ampex TM7 1/2" Tape deck 7/9 track ONLY £100.00
Precision Ins 1217 1/2" Tape deck ONLY £100.00
Shugart 801 8" floppy drive ONLY £200.00

POWER SUPPLIES

Modern multirail unit giving 5v at 4A, 12v twice at 2.5A and 350mA. Toroidal transformer and overcurrent shut-down make this ideal for your micro
ONLY £17.50 plus £1.80 carr.
5 volt 5 amp regulator. This modern module forms the perfect basis for your supply. £2.50 carr 50p
5 volt 60 amp switch mode compact supply only 5" x 6.5" x 11"
£25.00 plus £2.35 carr.
12 volt 8 amp switch mode supply 3.5" x 4" x 6.5" £17.50 plus £1.30 carr
24 volt 8 amp switch mode supply 3.5" x 6.5" x 7" £20.00 plus £1.50 carr

PRINTERS

IBM Selectric 735 Golfball printer/keyboard for superb letters
ONLY £199.00 plus £10.00 carr
Dolphin 8D80 80 column, 112 char/sec matrix printer, 900 char buffer, RS232 at 150 to 9600 baud or parallel.
ONLY £199.00 plus £10.00 carr
Dolphine 8D80P similar to 8D80 but 125 char/sec 50 to 19200 baud or IEEE or parallel interface
ONLY £249.00 plus £10.00 carr
WE ALSO BUY SURPLUS COMPUTERS AND COMPUTER PERIPHERALS. PLEASE RING FOR DETAILS.

CARRIAGE AND PACKING AT COST
CALLERS WELCOME BY APPOINTMENT

MAWSON ASSOCIATES
124 LENNARD ROAD,
BECKENHAM, KENT BR3 1QP
01-778 3600

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, can expand to Years, Months, Weekdays and Milliseconds, also STOPCLOCK and parallel BCD output for computer or alarm, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, GET the RIGHT TIME, only £62.80.

LOSING DX? Antenna fault? Poor reports? Check FAST with an Antenna Noise Bridge, MEASURE resonance 1-150MHz and radiation resistance 2-1000 ohms, MORE DX, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, instructions, money back guarantee so GET yours NOW.

CAMBRIDGE KITS

45 (TF) Old School Lane, Milton, Cambridge

CLEF ELECTRONIC MUSIC

ELECTRONIC PIANOS

SPECIALISTS SINCE 1972



KITS COMPLETE
SIX £363.90
7% £399.90

Get Piano with the most advanced form of Touch Sensitive action which creates more Key motion using a patented electronic technique.
Even Dancers Music can be used in hitting the 88 note full size instrument. Easy to maintain. Most electronic pianos tend to exhibit a dark or uneven Piano Tone, including Keyboard.
In our Solid and Synthetic Plastic are incorporated in the On-board support Effects are provided in the form of 'Sustains', 'Voices', 'Chorus', and 'Pulse' Effects.
A power amplifier integrates into the Piano Top which may be removed from the base for easy transportation.
Equipment fits in into Keyboard. Key cover in hardware, and all electronic components housed in a case based on front shelves of the instrument.
Complete Kits further contain: Cabinet, wiring harness, Pedals and all the usual Electronic Music Unit Power Amplifier and Speaker. Small but full size, and, outstanding features.

COMPONENT KITS

SIX OCTAVE £217
7% OCTAVE £244



COMPLETE KIT £349

"THE COMPUTER BAND-BOX"

(As Published in conjunction with 'Practical Electronics')

COMPLETE KIT £289



PRICES INCLUDE MASTER RHYTHM

A revolution in the field of Computer Music Generation!
A MUSICIANS FOR SOLIDISTS SINGERS RECORDING INSTRUMENT FOR PRACTICE LIVE PERFORMANCE COMPOSITION

The BAND BOX provides an Electronic Backing Trap consisting of Drums, Bass and a Chord instrument. One of 16 Waveform Envelope instruments with the capability to store over 3,000 User Programmable Chord Changes no more than 120 different Chords. Using advanced Microprocessor technology. Playlists of 50, 100 Scores can be created in any key and at chosen Tempo. Computer Music can be electronically isolated and stored on secondary battery back up. Facility exists for comparison of Intro, Repeat Chorus and Coda sections including Multiple Stereo Sequences. Scores are provided for Volume Pedal and Footswitch plus separate and insert instrument Outputs. Total size 19" x 11" x 4 1/2" incorporating Master Rhythm.

OUR PRICES INCLUDE V.A.T., CARRIAGE AND INSURANCE
Please send a £1.00 cheque for our catalogue V&A. (£1.00 worth).
New catalogue FREE! any order includes one copy. (We do not supply ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. E11)
44A BRAMHALL LANE SOUTH BRAMHALL,
STOCKPORT, CHESHIRE SK7 1AH
TEL: 061 439 3297

STRING ENSEMBLE

Electronic String Synthesiser with split keyboard facility and programme memory
COMPLETE KIT £179.00


KEYBOARDS

Square Front with ten hole interface ready to go
49 NOTE £28.75 61 NOTE £38
73 NOTE £47 88 NOTE £57

THE Programmable DRUM MACHINE

EIGHT TRACK PROGRAMMING TWENTY FOUR PATTERNS TWELVE INSTRUMENTS SEQUENCE OF OPERATION
COMPLETE KIT £79.00
MANFO £399

The Clef Master Rhythm is capable of storing 24 sets of 16 patterns. The patterns, drum patterns, instrument tracks, and stored by the Operator and Eight Instrumental tracks. A three pattern drum translation control expands the number of instruments available to twelve, grouped into sections typical of playing with Drums, Hi-Hats, or Low Drum, Snare and Cymbal. Sequence operation allows two rhythm sections to be stacked with the second (B) section appearing at four eighth or sixteen bar repetition. All drums can be adjusted for level and resistance on an internal control to suit individual taste, thus producing good musical results on a battery driven unit 8 1/2" x 11" x 4 1/2".

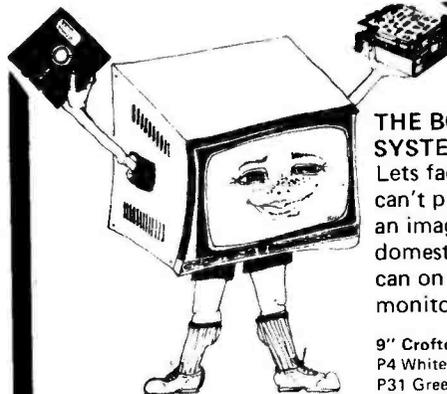

THE BODY OF ANY SYSTEM
Lets face it — you can't produce as crisp an image on a domestic T.V. as you can on a Crofton monitor.

9" Crofton Monitors
P4 White
P31 Green

SHUGART FLOPPY DISK DRIVES

No case, No Power Supply
SA 400 5 1/4" S.S.S.D.
SA 450 5 1/4" D.S.S.D.
SA 800 8" S.S.S.D.

FLOPPY DISKS — BOXES OF TEN

Single sided 35/40 Track
Double sided 35/40 Track 5 1/4"
Single sided 77 Track
Double sided 77 Track 5 1/4"
Single sided 8"

PRINCE 12" MONITORS

P 4 White
P31 Green

2/3" FULLY INTERLACED C.C.T.V. CAMERAS

PLEASE PHONE FOR CURRENT PRICES

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW1 4AD
Telephone 01 891 1923/01 891 1513 Telex 295093 CROFTN G

COMBINATION LOCK

A dazzling digital device, deftly designed to defend your domicile from dangerous desperadoes. Design and development by Rory Holmes.

For almost every lock made there's a thief to match it, and for every set of keys there's always someone to lose them. Such problems of security can now be overcome thanks to ETI's new Logic Lock, where the only moving part is the door latch! The complete device including the keypad and control-box can be built for about £10 and incorporates some very useful features in the design, resulting in total simplicity of operation.

The keypad, pictured above, can be built by anyone using completely standard components. It provides a waterproof and very rugged touch-sensitive input, which will last much longer than mechanical contact switches since there's virtually nothing to go wrong with it.

Programmed Protection

A single switch on the control-box puts the lock into either 'program' or normal 'operation' mode. In 'program' mode new combination sequences of any length from one to 14 digits can be entered directly through the keypad. Any number of repeated digits may be used, and the complete sequence will be stored in CMOS memory. A change of combination can thus be effected in seconds. After programming, the lock is left in 'operate' mode where the 5101 CMOS memory consumes only 10 uA of standby current, allowing long operating life from a 6 V battery.

As soon as the first number is



entered the memory receives full power for a 25 second period, allowing the combination sequence to be entered. The front panel LED illuminates for each number received to provide operator feedback, and also gives low battery indication by remaining off when replacement is due. The keypad input has been fully debounced to eliminate false entry errors. When the last digit is tapped in, the solenoid door bolt will activate for a preset time of around six seconds allowing the door to be opened. The LED also comes on during this period to confirm entry of the correct code.

The Logic Lock has well over four million *million* combinations, and an alarm was therefore considered unnecessary. Your local illegal entry operative can tamper with this lock until the cows come home; it won't open. Even a PDP-11 hooked into the keypad cable would take nigh on 6000 years of computing power to crack the code!

An optically coupled solid state relay is used to switch power to the solenoid, again being cheaper and more reliable than its mechanical counterpart. The PCB will accommodate several optional output configurations, for switching either mains or DC solenoid door latches.

Installation

Since the solenoid bolt mechanism is remote from the keypad and control-box, the logic lock may be placed anywhere in the vicinity and is not restricted to door mounting, although this would be more conventional. Obviously, the important factor is mounting the keypad on the outside and the control-box on the inside — the keypad could be mounted next to the bell push, allowing the ribbon cable to take the same route into the house as the bell wires. The control-box is screwed or stuck to the inside of the door and the keypad can be fixed to the outside using a strong epoxy. Alternatively the inside of the keypad can be filled with resin or Araldite and a long fixing bolt allowed to set in the resin. The keypad can then be bolted directly through the door. A hole drilled behind the keypad lets the ribbon cable pass through the door to the control-box. The wires for connecting up the solenoid latch, which are normally tacked across the door and pass across the hinges, should be connected up to the control box as shown in the wiring diagram.

The inclusion of an earth terminal for mains switching applications provides an extra degree of protection in the unlikely event of an opto-isolator fault.

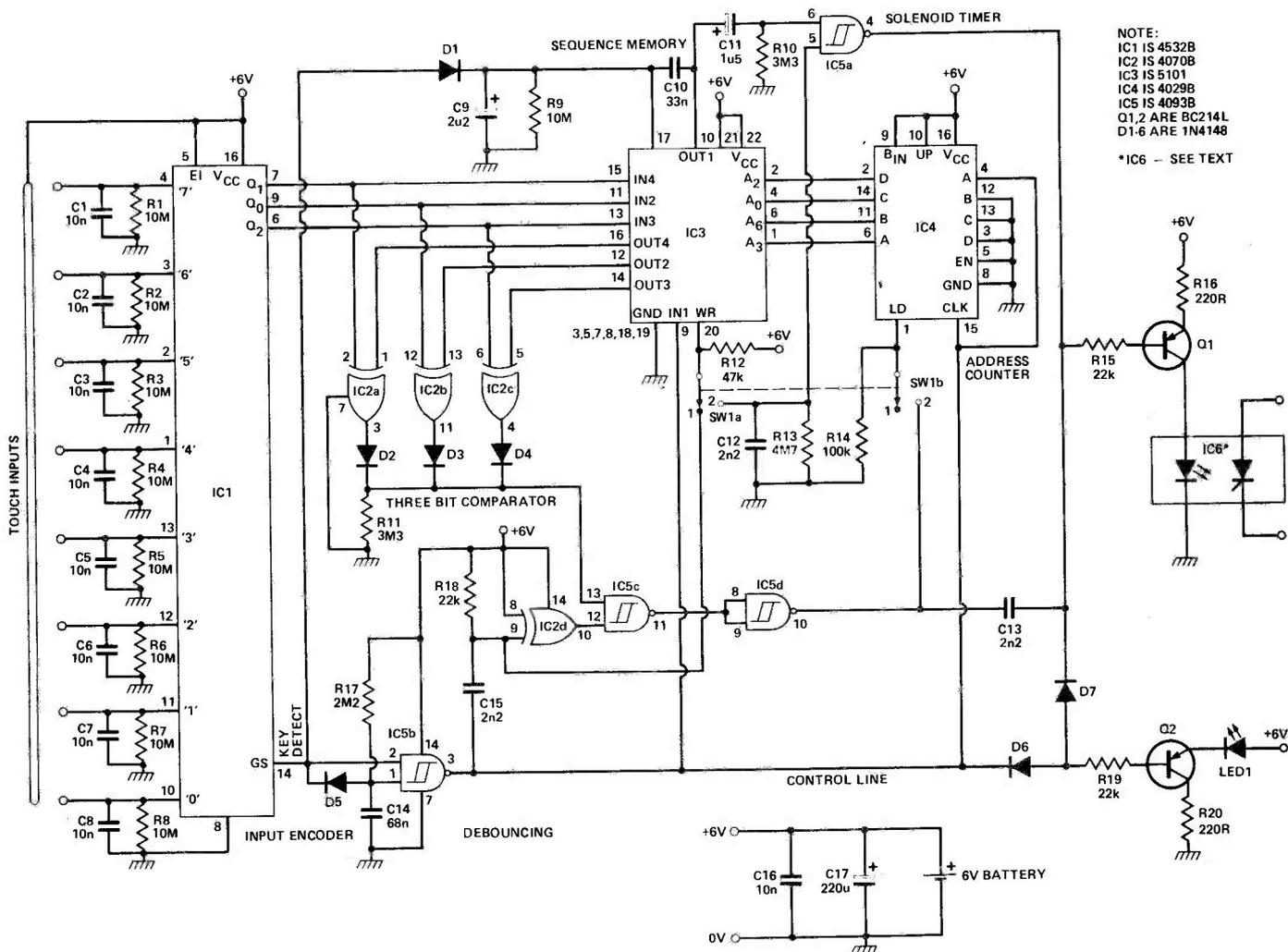


Fig. 1 The complete circuit diagram for the ETI Logic Lock. A general-purpose output is provided; next month several application circuits are given to suit mains or DC solenoids.

HOW IT WORKS

Numerical input to the lock is achieved using IC1, an eight input priority encoder. When one of its input lines is taken high, the corresponding number allocated to this line appears in binary form on its output lines, pins 6, 7, and 9. An input key detect signal, GS, is also available on pin 14; this line goes high if any input line is activated.

The eight input lines are activated using a touch keypad. Resistors R1-8 keep the inputs normally low, and they are taken high when the skin resistance of a finger bridges the input pins to the central +6 V rail. Capacitors C1 to 8 debounce this switching action to provide a measure of stability and the key detect output is further debounced to give completely reliable operation of the sequencing logic.

The rest of the circuitry consists of a four-bit counter IC4, which addresses part of a 256 x 4 bit CMOS memory (IC3). The data output of the memory is compared with the three bit keyboard word using EXOR gates IC2a, b and c, to provide an equal (logic low) or unequal (logical high) signal for controlling the subsequent action.

All of this circuitry has two modes of operation. With the switch in position 1, the 'write' mode is selected for programming a new combination sequence; position 2 is

the 'operate' mode where the circuit waits for a valid combination sequence to activate the lock.

To explain the 'write' mode we shall assume that the counter IC4 is on count 1 (ie only output A is at logic 1), and there are zeroes in all memory locations.

IC5b, a NAND Schmitt trigger, provides a debounced control signal from the GS line. GS is normally low, thus pin 2 of IC5b is low; also C14 is discharged via D5, so holding pin 1 low. Thus the output on pin 3 is normally logic high. When any input number is touched the GS line goes logic high, taking pin 2 of IC5b high and allowing C14 to charge up through R17 with a 150 ms time constant.

Now, as long as the GS line is still high when the pin 1 voltage reaches the trigger threshold, the gate output will switch low. When the touch input is released, GS goes low, C14 discharges through D5, and the Schmitt trigger output returns high again.

The control output from pin 3 is taken to five different circuit points. The negative-going edge is differentiated by C15 and R18 to produce a brief negative pulse as an input number is activated. During the 'write' mode this pulse is routed via SW1 to the write-line of the memory, IC3 pin 20. As this pin is taken low the current

data on pins 11, 13 and 15 (corresponding to the input number) is recorded at the present address. The IN1 memory input on pin 9 is also taken directly from the control line and will thus always be zero when the 'write' pulse occurs. This data bit is used to indicate the end of a correct combination sequence during the 'operate' mode (a necessary marker, since any length of sequence is permissible). The control line is taken directly to the clock input on pin 15 of IC4 and also to the preset input A at pin 4. As the control line returns to logic high when the touch input is released, the address counter IC4 is clocked on by one count on the positive-going edge.

The cathode of D6 is also taken low by the control line, thus turning on Q2 via R19 to illuminate the front panel indicator LED1. This shows that an input has been received to give a measure of operator feedback. As the timing diagram of Fig. 2 indicates, the above recording process repeats for each number that is selected on the touch pad, with the corresponding binary values being stored sequentially in consecutive memory addresses.

After entering the required digits, the sequence is terminated by moving SW1 to position 2, the 'operate' mode. As the switch closes, one last write pulse is

PROJECT : Combination Lock

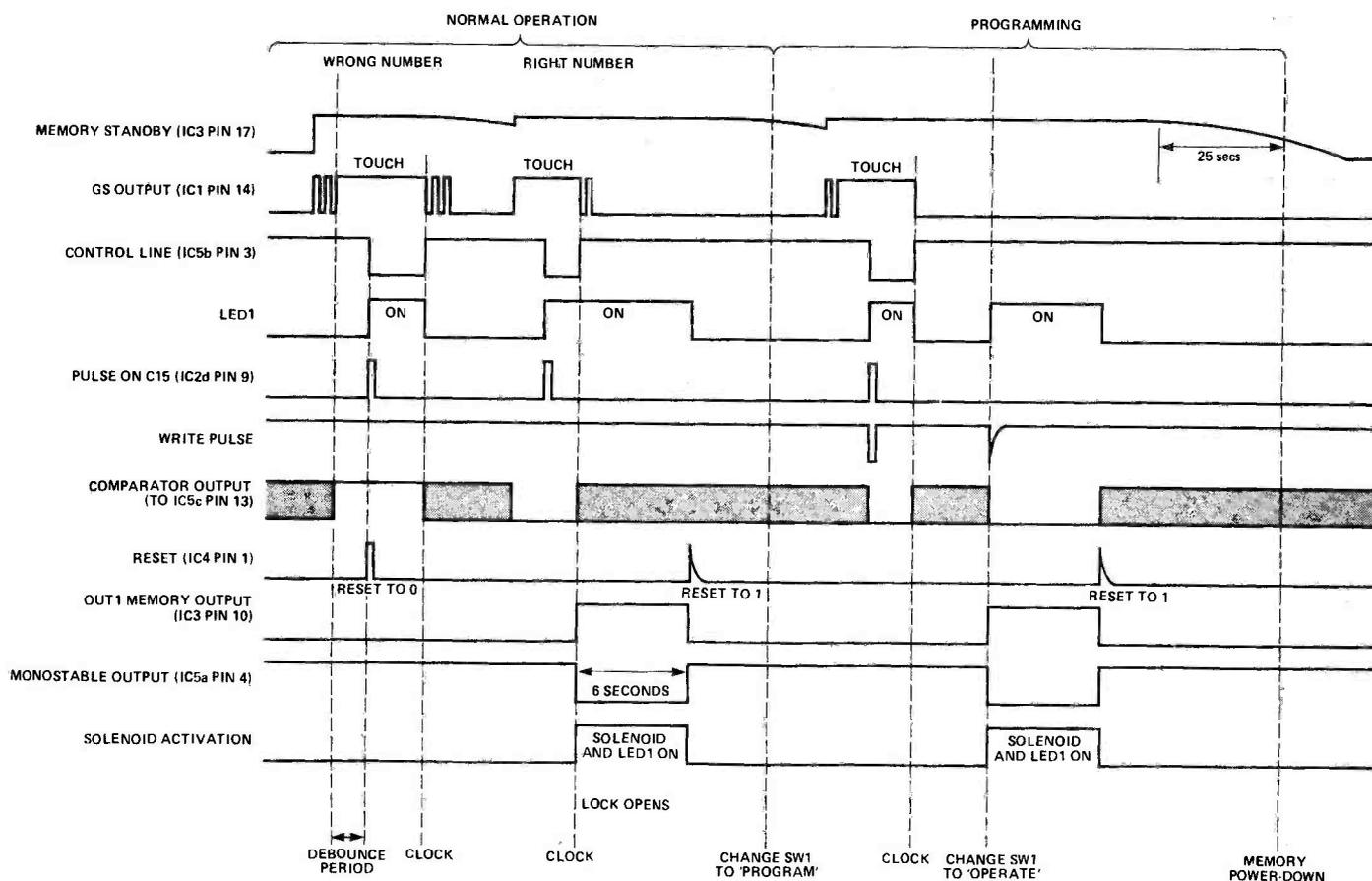


Fig. 2 Timing diagram for the Logic Lock logic! It will repay careful study in conjunction with the circuit diagram and How It Works section.

Next month we conclude this project with the component overlay and application circuits.

generated as C12 charges up through R12 (C12 was previously discharged via R13). No touch inputs are activated so the IN1 memory input is held at logic 1 by the control line. When the logic 1 is written to memory the associated OUT1 output also goes high, activating the solenoid timer monostable built around IC5a. (The solenoid is energised by this monostable for both normal lock operation and at the end of a write sequence. Although the door must already be open during reprogramming, the solenoid provides a useful indication of successful reprogramming.)

The pin 5 input of IC5a is normally held low by R13, thus disabling this gate. However, after the brief write pulse caused by changing SW1, pin 5 is taken high via R12. Pin 6 was also held low by R10, but as the OUT4 data output goes from low to high, the previously discharged capacitor C11 takes pin 6 high. The gate output on pin 4 will thus go low for a period set by the R10-C11 time constant. This time period is about five seconds and is used to turn on both the front panel indicator (via D7), and the solenoid lock mechanism, thus allowing plenty of time to open the door.

The monostable signal turns on

transistor Q1, which applies current to the LED in an opto-isolator and allows isolated external power to be switched to the solenoid. (Transistor or thyristor opto-isolators may be used).

When the monostable finishes its time period, the output returns high again. C13 differentiates this positive-going edge to provide a load pulse to the counter IC4. The preset A input is held at logic 1 by the control line, so the counter will return to its first state, switching the OUT1 memory output back to logic low.

The lock has now been programmed with the desired sequence and remains in its resting state of count position 1. When a number is now entered, the negative-going pulse produced through C15 appears on pin 9 of the EXOR gate IC2d.

This gate is wired as an inverter and the positive-going output pulse is fed to the pin 12 input of NAND gate IC5c. The other input to the NAND gate comes from the three bit comparator at the junction of D2,3 and 4. These diodes (with R11) form a three input AND gate; thus, if the data from the input encoder wired to one side of the digital comparator has the same binary value as the data currently on the OUT memory outputs feeding the other side,

then the pin 13 input of IC5c will remain low via R11. However, if the two values are not equal, there will be a logic high output from at least one of the exclusive OR gates IC2a, b or c, taking the input of IC5c high via the corresponding diode. Thus if a wrong number is entered, the short positive pulse from IC2d will appear in inverted form on the pin 11 output of IC5c. IC5d further inverts this pulse before feeding it to the load input on pin 7 of counter IC4. Since the preset A input of the counter is held low by the control line when this load pulse is received, the counter resets to zero. At the end of the wrong number input the control line goes high to clock the counter on to its count 1 resting state. Every wrong number entered will always return the counter back to the beginning of the sequence, regardless of where it occurs. As long as the correct numbers are entered in sequence, no reset pulses occur and the counter will be clocked on to the next number at the end of each entry.

After the last number in the sequence is entered, the counter will address the terminating location. The previously low OUT1 output goes high, triggering the solenoid timer monostable as described earlier and the door will now open.

ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you *could* make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be *sure* it's accurate, and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

APRIL 79		APRIL 81		DECEMBER 81	
<input type="checkbox"/> Guitar Effects Unit	£2.64	<input type="checkbox"/> Musical Box	£2.64	<input type="checkbox"/> Alcohometer (two boards)	£5.32
<input type="checkbox"/> Click Eliminator	£6.64	<input type="checkbox"/> Drum Machine (two boards)	£5.60	<input type="checkbox"/> Bodywork Checker	£1.97
JUNE 79		<input type="checkbox"/> Guitar Note Expander	£3.20	<input type="checkbox"/> Component Tester	£1.49
<input type="checkbox"/> Accentuated Beat Metronome	£3.60	JUNE 81		JANUARY 82	
FEBRUARY 80		<input type="checkbox"/> Mini-drill Speed Controller	£2.93	<input type="checkbox"/> Parking Meter Timer	£2.37
<input type="checkbox"/> Tuning Fork	£2.64	<input type="checkbox"/> Antenna Extender	£3.20	<input type="checkbox"/> Infant Guard	£1.80
MARCH 80		<input type="checkbox"/> Alien Attack	£2.64	<input type="checkbox"/> Guitar Tuner (two boards)	£5.97
<input type="checkbox"/> Signal Tracer	£2.27	<input type="checkbox"/> LED Jewellery: Cross	£1.47	FEBRUARY 82	
AUGUST 80		<input type="checkbox"/> Spiral (two boards)	£2.64	<input type="checkbox"/> Ripple Monitor	£2.08
<input type="checkbox"/> CMOS Logic Tester	£2.64	<input type="checkbox"/> Star (two boards)	£2.65	<input type="checkbox"/> Pest Monitor	£1.85
<input type="checkbox"/> Capacitance Meter	£2.93	<input type="checkbox"/> Waa-phase	£1.53	<input type="checkbox"/> I Ching Computer (two boards)	£5.31
<input type="checkbox"/> Ultrasonic Burglar Alarm	£2.87	JULY 80		<input type="checkbox"/> Moving-magnet stage	£3.80
OCTOBER 80		<input type="checkbox"/> System A A-MM/A-MC	£2.65	<input type="checkbox"/> Moving-coil stage	£3.80
<input type="checkbox"/> Cassette Interface	£2.93	<input type="checkbox"/> System A A-PR	£5.17	MARCH 82	
<input type="checkbox"/> Fuzz/Sustain Box	£3.27	<input type="checkbox"/> Smart Battery Charger	£1.97	<input type="checkbox"/> Infinite Improbability Detector	£3.37
NOVEMBER 80		AUGUST 81		<input type="checkbox"/> Capacitance Meter (two boards)	£14.19
<input type="checkbox"/> Touch Buzzer	£1.93	<input type="checkbox"/> System A Power Amp (A-PA)	£4.77	<input type="checkbox"/> Robot Motor Controller	£3.80
<input type="checkbox"/> Light Switch	£1.93	<input type="checkbox"/> Flash Sequencer	£3.44	<input type="checkbox"/> Light Wand	£1.87
<input type="checkbox"/> Metronome	£1.93	<input type="checkbox"/> Hand-clap Synthesiser	£3.97	APRIL 82	
<input type="checkbox"/> 2W Power Amp	£1.93	<input type="checkbox"/> Heartbeat Monitor	£1.83	<input type="checkbox"/> Contrast Meter	£2.83
<input type="checkbox"/> RIAA Preamplifier	£1.93	<input type="checkbox"/> Watchdog Home Security (two boards)	£5.31	<input type="checkbox"/> Sound Effects board	£2.40
<input type="checkbox"/> Audio Test Oscillator	£3.13	SEPTEMBER 81		<input type="checkbox"/> High Impedance Probe	£1.97
DECEMBER 80		<input type="checkbox"/> Mains Audio Link (three boards)	£7.35	<input type="checkbox"/> Guitar Practice Amp	£7.57
<input type="checkbox"/> Musical Doorbell	£2.80	<input type="checkbox"/> Laboratory PSU	£4.53	<input type="checkbox"/> Accurate Voltage Monitor	£2.05
<input type="checkbox"/> Bench Amplifier	£2.53	OCTOBER 81		MAY 82	
<input type="checkbox"/> Four Input Mixer	£2.64	<input type="checkbox"/> Enlarger Timer	£3.40	<input type="checkbox"/> DV Meg	£2.92
JANUARY 81		<input type="checkbox"/> Sound Bender	£2.65	<input type="checkbox"/> Analogue PWM	£3.37
<input type="checkbox"/> LED Tacho	£4.13	<input type="checkbox"/> Thermal Alarm	£2.63	<input type="checkbox"/> Slot Car Controller	£4.96
<input type="checkbox"/> Multi-Option Siren	£3.20	<input type="checkbox"/> Micropower Pendulum	£2.21	<input type="checkbox"/> Wattmeter	£4.53
<input type="checkbox"/> Universal Timer	£3.31	NOVEMBER 81		<input type="checkbox"/> Sound Effects Board	£2.40
FEBRUARY 81		<input type="checkbox"/> Music Processor	£7.35	JUNE 82	
<input type="checkbox"/> Infra-red Alarm (four boards)	£6.64	<input type="checkbox"/> Voice-Over Unit	£3.97	<input type="checkbox"/> Ion Generator (two boards)	£6.22
<input type="checkbox"/> Pulse Generator	£3.57	<input type="checkbox"/> Car Alarm	£2.81	<input type="checkbox"/> Ion 'Blinker'	£2.60
MARCH 81		<input type="checkbox"/> Phone Bell Shifter	£2.96	<input type="checkbox"/> MOSFET Amp Module	£6.99
<input type="checkbox"/> Engineer's Stethoscope	£2.65			<input type="checkbox"/> Logic Lock	£3.41

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. Prices may be subject to change without notice.

Total for boards £.....
 Add 45p p&p 0.45
 Total enclosed £.....

I wish to pay by Access/Barclaycard. Please debit my account

BARCLAYCARD

VISA


5	2	2	4																
4	9	2	9																

Signed 
 Name
 Address

Road Runner

WIRING SYSTEM

SPECIAL INTRODUCTORY OFFER!

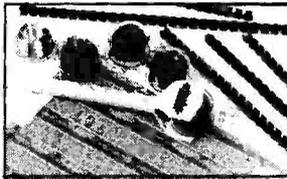

PROJECT KIT - ONLY £5.40
MORE THAN 25% OFF
 Normal Price £7.26

Consists - High density hobby board, wiring pencil, 5 x 6" Glue Strips, 4 coloured enamelled wire bobbins, 1 tinned copper wire bobbin.

ROADRUNNER IRON
 - ONLY £5.00

MORE THAN 15% OFF
 Normal Price £5.99

Spec - 240V 17W High Temp Iron suitable for soldering enamelled wire.



ROADRUNNER PRODUCTS IDEAL FOR

- WIRING SIMPLE LOGIC CIRCUITS
- WIRING MICROS & MEMORIES
- WIRING DISCRETE CIRCUITRY
- REPAIRING & MODIFYING PCB's
- USE AS A TRAINING AID

WIRING SYSTEM	£
EURO INTROKIT	15.99
PROJECT KIT	7.26
MINI KIT A	6.68
MINI KIT B	6.21
PCB REPAIR KIT	5.41
TRAINING KIT	8.95
GEN. GLUE STRIPS 20/PKT	3.10
H/D GLUE STRIPS 20/PKT	3.39
PRESS STRIPS 20/PKT	2.71
QSE PENCIL	2.99
TOW PENCIL	2.94
BLUE BOBBINS 4/PKT	2.12
COPPER COLOUR	2.12
GREEN COLOUR	2.12
PINK COLOUR	2.12
MIXED PACK OF 4	8.98
TOW BOBBINS 2/PKT	1.75
HOBBY BOARD 5 SIDED	3.80
PROJECT EUROCARD S SIDED	4.50
SINGLE EUROCARD D SIDED	8.60
DOUBLE EUROCARD D SIDED	1.95
HOBBY BOARD CONNECTOR 28 WAY MODULAR TYPE	1.95
WW PINS	1.95
SOLDERTAGS	1.95

LOW PROFILE IC SOCKETS	TINNED CONTACTS
8 WAY 9p	14 WAY 12p
16 WAY 18p	20 WAY 18p
22 WAY 23p	24 WAY 22p
28 WAY 25p	40 WAY 35p
GOLD CONTACTS	
8 WAY 17p	14 WAY 18p
16 WAY 20p	18 WAY 24p
20 WAY 27p	22 WAY 28p
24 WAY 31p	28 WAY 40p
40 WAY 50p	
DIN 41612 CONNECTORS	
32 way B type Plug	0.93
32 way Socket WW Pins	1.42
32 way Socket Solder tag	2.32
64 way C type Plug	1.46
64 way Socket WW Pins	2.21
64 way Socket Solder tag	3.08
96 way also available	
EUROCARD SUBRACKS	
Kits of 2 end plates, 2 front & rear rails, fixing screws and integral fixing for DIN 41612 Connectors	
3U/84HP 19" wide frame	19.86
3U/40HP 10" wide frame	17.90
3U/20HP 6" wide frame	15.94
6U/84HP 19" wide frame	29.99

ONE-PIECE GUIDE BLOCKS	2.8" CARD FITCH
3U & 6U 84HP	2 per pack 2.68
3U 40HP	1.43
3U 20HP	0.78
INDIVIDUAL RAILS	0.16
DIN 41612 Conn. fixing screws	0.36/20
*Other accessories available	
ROADRUNNER IRONS	
High temp. Iron	5.99
General Purp. Iron	5.48
Iron stand	4.82
Spare Iron bits ea	0.67
Weller Iron bits ea	1.55
Desolder braid ea	0.95
Microshears	3.47
Knife	0.45
Tweezers	1.49
Spotface cutter	1.49
Pin inserter	1.91
Solder Pins 100	0.50
22 SWG Xersin 2 kg	8.50
Glue strip adhesive	0.44

USE ROADRUNNER PRODUCTS FOR VERSATILITY, ECONOMY AND PROFESSIONAL RESULTS

TAKE ADVANTAGE OF THIS INTRODUCTORY OFFER TO THE ROADRUNNER WIRING SYSTEM & ORDER NOW

WHEN ORDERING ASK FOR THE NEW ROADRUNNER CATALOGUE FREE!

GOOD VALUE FROM ROADRUNNER

19" Eurocard Subrack complete

ONLY £19.86

Full range of accessories available.

ADD 5% TO NET ORDER VALUE TO COVER CARRIAGE AND PACKAGING. THEN ADD 15% VAT. Please supply requested items.

I enclose cheque/P.O. for £
 or debit my Barclay Card/Access No.

Signature

Name (Please print)

Address

Orders to ROADRUNNER ELEC. PRODS, 116 BLACKDOWN RURAL INDUSTRIES, HASTE HILL, HASLEMERE, SURREY GU27 3AY (0428 53850)



Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our listening lounge. (Customer operated demonstration facilities)
- ★ Ample parking ★
- ★ Access Visa American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!

ZX81 HARDWARE

40 KEY KEYBOARD Kit £20.95 Built £25.75 (RE77)

- * Proper typewriter style keys.
- * All legends and graphics in two colours.
- * No soldering required to ZX81. Plugs in. (RAM/Printer not affected)
- * Complete with all parts, connectors, feet and comprehensive instructions.

24 LINE IN/OUT PORT Kit £16.95 Built £18.95 (RE98)

- * Each line either in or out.
- * Controlled by BASIC.
- * Allows printer, RAM to be used without a motherboard. (Motherboard version kit £13.50 Built £14.50)

3 CHANNEL SOUND/TIMER BOARD

Kit £16.95 Built £18.95 (RE161)

- * 3 independent channels.
- * Controlled by BASIC.
- * Full range of notes.
- * Complete instructions with examples provided.
- * Can be used as a sophisticated timer/counter.

MOTHERBOARD Kit £15.75 Built £18.50 (RE82)

- * Two connectors on board.
- * Six connector board. TBA.

CONNECTORS & PLUGS

- * 23 Way female connector for ZX80/1. (RE80) £2.95
- * 23 Way male connector. (RE87) £1.30
- * 23 Way male connector to fit two female connectors together. (RE90) £1.60
- * 30 Way ribbon cable. £1.40 metre
- * RAM pack connector. Allows RAM pack to be remote from ZX80/1. (RE170) £6.95 built
- * In/out connector and sound board connector. (RE78B) £2.95

BOOKS & TAPES

- Getting acquainted with ZX81 £4.95
- Mastering machine code £5.95
- Programming for real applications £6.95
- Tape for real applications book £11.44



Send SAE 5" x 7" for free illustrated catalogue.
 All products available ex stock (allow 7 days extra for built products).
 Payment: Cash with order. Or ACCESS/BARCLAYCARD.
 Official order welcome. Dealers write for rates.

All prices include P & P and VAT. Overseas add £1.80

REDDITCH ELECTRONICS

DEPT ET1
 21 FERNEY HILL AVE.,
 REDDITCH,
 WORCS. B97 4RU
 TEL: (0527) 61240

New Products

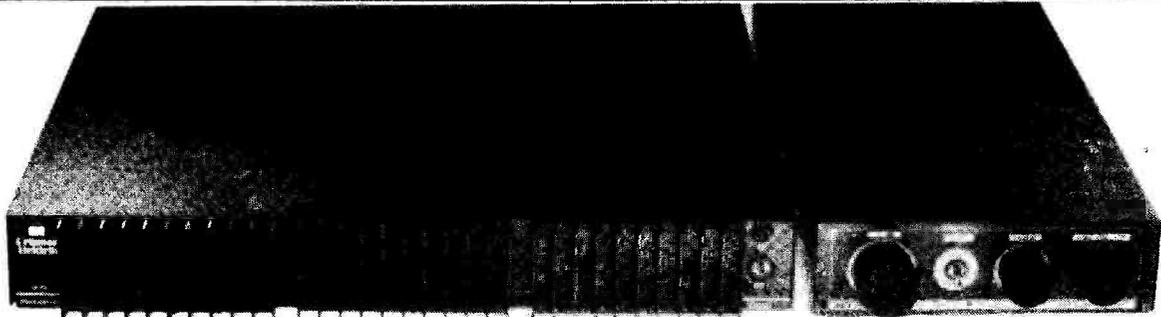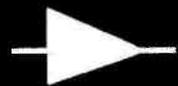

HIFI STEREO AMPLIFIER KITS

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty.

These new kits offer the choice of moving magnet or moving coil inputs, 40 to 100 watts per channel, in fact, everything that made the previous models so popular is included but with added style, easier construction and a full two year warranty.

The new range consists of The CK 1010 Stereo Pre Amplifier, The CK 1040 WPC Power Amplifier, The CK 1100 WPC Power Amplifier.

CK 1010

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled and tested therefore construction is simply a matter of point to point wiring and mechanical assembly of the connections and controls to the pre punched chassis.

The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

CK 1040

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsinks, wire and connectors are included and protection is provided from short circuit outputs.

CK 1100

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard. When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kit-build field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few — such as the KA-1000 (£500+) — are of comparable standard. . . . I can say no more than that for £250 it (CK 1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

PRICES CK 1010 — RRP £90.00; CK 1040 — RRP £119.00; CK 1100 — RRP £149.00; MC2K — RRP £25.000; PSK — RRP £20.00

Barclaycard or Access accepted, otherwise send C.W.O. C.O.D. £1.00 extra. All prices include P&P to anywhere in the U.K. Export: Write for pro-forma

SEND FOR FULL DETAILS ON OUR HIFI KIT PRODUCTS BY WRITING TO FREEPOST ADDRESS BELOW

FREEPOST, 9 CLAYMILL ROAD

LEICESTER LE4 5ZD. ENGLAND

TEL. 0533 761920, TLX 34694



Crimson Elektrik

MAY OFFER

SEE BELOW FOR DETAILS

<p>POWER SUPPLY: For micros and TTL Stabilised 1A5/5V. Built tested uncased. 650p</p> <p>AS ABOVE less transformer 300p</p> <p>PCB for above or 12V or 15V 100p</p> <p>CERAMIC CAPACITORS (50V)</p> <p>33pF to 50,000pF 3p</p> <p>POLYSTYRENE CAPACITORS (50V)</p> <p>10pF to 1000pF 3.5p</p> <p>POLYESTER CAPACITORS (100V)</p> <p>1nF to 680nF 6p 1uF 1u5 4u7 8p</p> <p>ELECTROLYTIC CAPACITORS (uF/V)</p> <p>1/25 to 150/25 6p 160/25 6A0/16 3p</p> <p>220/25 470/25 10p 470/40 mini 12p</p> <p>1000/10 2200/6 12p 1500/40 22p</p> <p>2000/18 22p</p> <p>TRANSFORMER 230V/2 Amp 360p</p> <p>HEAT SINK to 220°C/W 45p</p> <p>VERO BOARD (0.1" copper clad)</p> <p>2.5 x 5" 60p</p> <p>SWITCHES</p> <p>DIL 3 way SPST 20p</p> <p>DIL 3 way SPDT 30p</p> <p>DIL 7 way SPST 30p</p> <p>ROTARY 2A/250V DPST 9mm bush 18p</p> <p>SLIDE 3A/50V DP 3 way or 1A/250V</p> <p>with 1 throw panel cutout 7p</p> <p>RESISTORS (1/4W 5% carbon film)</p> <p>10 ohms to 10Mohms E12 2p</p> <p>PRESETS (miniature horizontal)</p> <p>100 ohms to 1Mohms 6p</p> <p>POTENTIOMETERS (1/4W) Linear</p> <p>and Log Scale 4K7 to 2M2 28p</p> <p>ZENER DIODES (400mW)</p> <p>3V3 to 30V 6p</p> <p>600V: C2060 400V 3A 55p</p> <p>600V: 10A 50p 15A 55p</p> <p>High performance glass passivated for high voltage isolation. By THYROTEK CORP of Texas in 3 pin presilt metal case with superior spec to plastic ones. Full data supplied. ONCE SOLD THIS CAN NEVER BE REPEATED.</p> <p>LINEAR CIRCUITS</p> <p>709-B 20p</p> <p>710-14 20p</p> <p>741-B 20p</p> <p>747-14 40p</p> <p>748-B 25p</p> <p>AY-1-1313 600p</p> <p>AY-1-5050 90p</p> <p>AY-3-1270 800p</p> <p>AY-3-8912 650p</p> <p>AY-5-1224A 200p</p> <p>AY-5-4007/450p</p> <p>CA3018H 50p</p> <p>CA3019 80p</p> <p>CA3028AH 50p</p> <p>CA3048N 30p</p> <p>CA3048 245p</p> <p>CA3054 40p</p> <p>CA3080 65p</p> <p>CA3080 65p</p> <p>CA3090AQ 70p</p> <p>(star buy)</p>	<p>CA3130E 90p</p> <p>CA3140 45p</p> <p>CA3160 80p</p> <p>ICL7106 700p</p> <p>LF351N 45p</p> <p>LF352N 90p</p> <p>LM10C 400p</p> <p>LM301A-14 20p</p> <p>LM308N 30p</p> <p>LM311 80p</p> <p>LM318H 82p</p> <p>LM318N 100p</p> <p>LM339N 65p</p> <p>LM380N 65p</p> <p>LM381N 100p</p> <p>LM382N 90p</p> <p>LM733 80p</p> <p>LM1458N 35p</p> <p>LM1830 170p</p> <p>LM2917 220p</p> <p>LM3900N 40p</p> <p>LM3914 200p</p> <p>LM3915 240p</p> <p>LM1360N 140p</p> <p>MC1310N 75p</p> <p>MC1495L 350p</p> <p>MC1496P 70p</p> <p>MK50398 600p</p> <p>ML322 35p</p> <p>ML323 155p</p> <p>NE555 22p</p> <p>NE562 400p</p> <p>NE566 160p</p> <p>NE567 160p</p> <p>SN76115AN 50p</p> <p>TAA521 280p</p> <p>TBA641B 125p</p> <p>TBA651 80p</p> <p>TBA800 65p</p> <p>TBA820 80p</p> <p>TD1004 350p</p> <p>TD1008 355p</p> <p>TL074 140p</p> <p>UAA170 190p</p> <p>ZN424E 150p</p> <p>RED LED 10p</p> <p>GREEN LED 11p</p> <p>YELLOW LED 11p</p> <p>RECT GREEN 13p</p> <p>VOLTAGE REGULATORS</p> <p>4011B 34p</p> <p>4012 17p</p> <p>4013B 28p</p> <p>4014 58p</p> <p>4015B 60p</p> <p>4016 20p</p> <p>4017 35p</p> <p>4019 33p</p> <p>4020B 65p</p> <p>4021 56p</p> <p>4022 37p</p> <p>4023 15p</p> <p>4025 14p</p> <p>4027 30p</p> <p>4028 40p</p> <p>4029 65p</p> <p>4030 18p</p> <p>4035 92p</p> <p>4041 75p</p> <p>4042 55p</p> <p>4043 70p</p> <p>1A/50V 18p</p> <p>1A/200V 18p</p> <p>1A/400V 20p</p> <p>1A/600V 20p</p> <p>2A/100V 20p</p> <p>3A/600V 33p</p> <p>BRIDGE RECTIFIERS</p> <p>W02M 16p</p> <p>W06M 17p</p> <p>1A/50V 18p</p> <p>1A/200V 18p</p> <p>1A/400V 20p</p> <p>1A/600V 20p</p> <p>2A/100V 20p</p> <p>3A/600V 33p</p> <p>DIL SOCKETS</p> <p>8 pin 6p</p> <p>14 pin 10p</p> <p>16 pin 11p</p> <p>18 pin 18p</p> <p>22 pin 16p</p> <p>24 pin 18p</p> <p>28 pin 24p</p> <p>40 pin 24p</p> <p>LS11/12 15p</p> <p>LS13 24p</p> <p>LS14 36p</p> <p>LS20 14p</p> <p>LS21/27 15p</p> <p>LS30 14p</p> <p>LS32 17p</p> <p>LS42 35p</p> <p>LS42 35p</p> <p>LS05/8 14p</p> <p>LS10 14p</p> <p>LN4005 4p</p> <p>LN5400 11p</p> <p>LN5401 12p</p> <p>LN5402 13p</p> <p>LN5404 14p</p> <p>LS47 48p</p> <p>LS48 45p</p> <p>LS73 20p</p> <p>LS74 18p</p> <p>LS75 25p</p> <p>LS76 26p</p> <p>LS78 22p</p> <p>LS86 21p</p> <p>LS90 40p</p> <p>LS93 28p</p> <p>LS95 50p</p> <p>LS109 30p</p> <p>LS122 35p</p> <p>LS123 40p</p> <p>LS154 40p</p> <p>LS157 35p</p> <p>LS163 42p</p> <p>LS221 52p</p> <p>LS251 50p</p> <p>LS253 50p</p> <p>LS279 30p</p> <p>TTL "N"</p> <p>7400/11 11p</p> <p>7402 11p</p> <p>7403 10p</p> <p>7404 9p</p> <p>7405 11p</p> <p>7406 15p</p> <p>7407 14p</p> <p>7408 16p</p> <p>7409 13p</p> <p>7410 11p</p> <p>7411 17p</p> <p>7412 15p</p> <p>7413 15p</p> <p>7414 15p</p> <p>7415 48p</p> <p>7416 38p</p> <p>7417 23p</p> <p>7418 21p</p> <p>7419 60p</p> <p>7420 35p</p> <p>7421 45p</p> <p>7422 37p</p> <p>7423 30p</p> <p>7424 30p</p> <p>7425 30p</p> <p>7426 30p</p> <p>7427 16p</p> <p>7428 35p</p> <p>7429 13p</p> <p>7430 13p</p> <p>7431 19p</p> <p>7432 15p</p> <p>7433 15p</p> <p>7434 14p</p> <p>7435 12p</p> <p>7436 11p</p> <p>7437 11p</p> <p>7438 12p</p> <p>7439 11p</p> <p>7440 11p</p> <p>7441 11p</p> <p>7442 58p</p> <p>7443 35p</p> <p>7444 72p</p> <p>7445 38p</p> <p>7446 72p</p> <p>7447A 35p</p> <p>7448 35p</p> <p>7449 11p</p> <p>7450 50p</p> <p>7451 8p</p> <p>7452 13p</p> <p>7453 7p</p> <p>7454 22p</p> <p>7455 23p</p> <p>7472 25p</p> <p>7473 14p</p> <p>7474 18p</p> <p>7475 23p</p> <p>7476 18p</p> <p>7477 25p</p> <p>7478 25p</p> <p>7479 48p</p> <p>7480 25p</p> <p>7481 45p</p> <p>7482 50p</p> <p>7483 45p</p> <p>7484 11p</p> <p>7485 30p</p> <p>7486 30p</p> <p>7487 30p</p> <p>7488 30p</p> <p>7489 30p</p> <p>7490 22p</p> <p>7491 30p</p> <p>7492/3 30p</p> <p>7493 30p</p> <p>7494 40p</p> <p>7495 35p</p> <p>7496 35p</p> <p>7497 166p</p> <p>7498 16p</p> <p>7499 19p</p> <p>7500 52p</p> <p>7501 90p</p> <p>7502 21p</p> <p>7503 7p</p> <p>7504 21p</p> <p>7505 46p</p> <p>7506 46p</p> <p>7507 10p</p> <p>7508 10p</p> <p>7509 10p</p> <p>7510 23p</p> <p>7511 23p</p> <p>7512 23p</p> <p>7513 6p</p> <p>7514 10p</p> <p>7515 10p</p> <p>7516 10p</p> <p>7517 10p</p> <p>7945 </p>
---	---

WE WILL BEAT BY 5% ANY LOWER PRICE ADVERTISED BY COMPETITORS*



100 METRE WATER RESISTANT



W-100
Resin
case/strap
£19.95

W-150C
S/S case,
resin strap
£21.95

W-150
All
S/S
£24.95

Time and auto calendar. Alarm and hourly chimes. Countdown alarm timer with repeat memory function. Professional 1/100 second stopwatch. Time is always on display, regardless of display mode. Amazing 5 year lithium battery life. Superior to the W-250

50 METRE WATER RESISTANT



W-20
REsin
case/strap
£12.95

W-21
Resin
S/S trim
£14.95

W-30
All
S/S
£19.95

12/24 hour time and auto calendar. Alarm and hourly chimes. Professional 1/100 second stopwatch to 12 hrs. Compact and slim cases, approx. 8mm thick. 5 year lithium battery.

OTHER MODELS

AX-210. The world's most versatile watch?

Analog Display
LC Display of hours and minutes
Digital Display
● Local time, 12 or 24 hour
● Full calendar display
● Dual time, 12 or 24 hour
● Countdown alarm timer with memory function
● Professional 1/100 second stopwatch
Hourly time signal. Daily alarm electronic buzzer or 3 selectable melodies. Rapid forward/back setting. 9.4 x 35.4 x 36mm
Usual price: £29.95
Lowest price elsewhere
● **£27.95**



****NEW****
CA95. Calculator, 4 alarms, hourly time signal, stopwatch Black resin case/strap **£19.95.**
CA951 Metal case/bracelet version of CA95 **£29.95.**
Other models. CA85 **£19.95;** CA851 **£29.95;** J100 **£19.95;** GM10 **£19.95;** SA50 **£14.95;** SA50G **£19.95.**

LOOK, NO BATTERIES



FX-950 SOLAR CELL SCIENTIFIC
Powered by almost any light. 50 scientific functions, with nesting of up to 15 parentheses at 5 levels. Hyperbolics, Standard Deviations, etc. 10 digit display. 5.4 x 73 x 129mm
Supplied with wallet.
£22.50

FX-900 8-digit version with less functions **£19.95**

* Providing the advertiser has stocks and we do not sell at a loss

Sharp Portable Colour Computer for only £278 + VAT

The Revolutionary New PC-1500 and CE-150



PC-1500 Computer
£169.95
CE-150 4-colour Printer
£149.95
CE-151 4K Byte RAM
£49.95
CE-155 8K Byte RAM
£79.95

We are convinced that this is the world's most advanced PC-1500 software.


MICROL 1500 SOFTWARE SERIES

The Portable Computer Comes of Age with advanced ready-to-run software to meet the needs of management, science, engineering and the professions. Major features include: (1) 100% reliable performance for total dependability. (2) "User-friendly" commands and prompts. (3) Comprehensive "plain English" operating manuals. (4) No computer experience required. (5) Designed for easy personalisation. (6) Future-compatible, with full hardware and software add-on capability. Plus: Full colour print commands with Auto-Colour, Audit-Trail and Archive options, sophisticated user-error recovery systems and Database Integrity Protection option.

MICROL 1500 Software Series from £200 to under £20.
Brochure on request
Worldwide dealer network now being established
Dealer enquires welcome.

The PC-1500 approaches the Personal Computer in ability. 16K bytes of ROM and up to 11.5K bytes of RAM memory, with battery protection. Multiple program storage capacity. "BASIC" program language with two dimensional arrays and variable strings. QWERTY keyboard with upper and lower case. (Word-processor software available soon.) Mini-graphic 7 x 156 dot matrix display. Line width 26 characters. The CE-150 4-colour Graphic Printer/Two Cassette Interface (for saving/loading) prints virtually any drawing, with complete control of up, down, left and right printing. Variable line length from 4 to 36 characters. With rechargeable battery and mains adaptor.
Dimensions: PC-1500 195 x 25.5 x 86mm. Wt 375g. CE-150 330 x 50 x 115mm. Wt 900g.
Available soon: RS-232C Interface. Software board to serve as input keys in graphics, or pictures, previously drawn on a template.
Brochure on request.

The Scientific Portable Computer

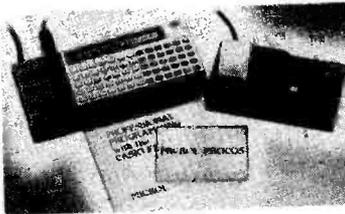

CASIO FX-702P Only £99.95

Plus FREE MICROL Professional Programming Pack (RRP £9.95) or we will beat any lower price by 5%.

The widest range of math, science and statistics, (55 in all, including Regression and Correlation). BASIC. Up to 1,680 program memory steps, up to 226 data memories. Subroutines, 10 levels; FOR:NEXT looping, 8 levels. Edit, debug and trace modes. 240hrs battery life. 17 x 165 x 82mm. Wt 176g.

MICROL 702 PROCOS Professional Computing Solutions on tape. Save up to 90% of programming time with this electronic equivalent of pen and paper. 'Visicalc-type' systems answers 'what if' questions and analyses trends. £24.95.

Peripherals for FX-702P, 602P, 601P and 502/501P
FA-2 Remote control Cassette Interface £19.95
FP-10 Permanent hard copy printer. AC/DC £44.95


702 PACKAGE DEALS

Pack A: FX-702P + MICROL PPP £99.95
Pack B: 702 + FA-2 + PROCOS £139.95
Pack C: 702 + PPP + FP-10 + PROCOS £179.95

World's Fastest Programmable?

CASIO FX-602P Only £74.95

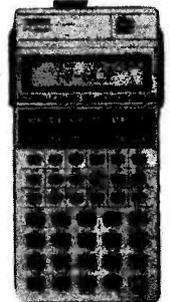With FREE MICROL Professional Programming Pack (RRP £9.95) or we will beat any lower price by 5%. 50 scientific functions. Up to 512 program steps, up to 88 memories, all protected when switched off. Programs; P0 to P9. G0T0 up to 10 pairs. Up to 9 subroutines nestable to 9 levels. 33 brackets at 11 levels.
FA-2 £19.95
FP-10 £24.95



CASIO FX-601P Now only £39.95

Similar to the FX-602P but with 128 program steps, 11 memories; 18 brackets, up to 6 levels; up to 9 subroutines, nestable up to 4 levels.

Other Scientifics

FX-3600P 38 program steps £22.95* Others £21.95*
FX-8100 With Clock, Alarms, Stopwatch £19.95
FX-950 £22.95; FX-900 £19.95; FX-550 £19.95; FX-100 £16.95; FX-82 £12.95; FX-7 £10.95; FX-5 £8.95.

Calculating Alarm Clocks

FT-7 Fortune Teller £16.95; BG-15 Boxing £16.95; ML-75 Card. 12 melody alarms £14.95; ML120 wallet version £14.95; UC360 Card, UC365 Wallet £19.95.
BASIC. LC950 Metric Conversions on two displays £16.95; MG777 3 games/clock £14.95; MG880 £10.95.

CASIOTONE CT-701 COMPUTERISED PROGRAMMABLE KEYBOARD/ORGAN

Fully Programmable, 5 octave, Polyphonic Keyboard



CT-701

(RRP £555) ONLY £495

Other Casiotones:
VL-10 £26.95; VL-1 £35.95; MT-31 £69; MT-40 £99; CT-101 £195; CT-202 £275; CT-403 £275.

Program the 345 melody steps and the 201 chord steps (max) with music specially scored in bar code and read by a light pen, or enter your own chords and melody via the keyboard, with full editing and repeat facilities.

3-way replay: Automatic. One key play, Melody Guide (lights above the keyboard indicate the next note to play). Split keyboard, 20 superb instrument voices, 16 rhythm accompaniments, fingered or auto chords with walking bass and arpeggio, fill-in and effect buttons. 37 1/2 x 137 1/2 x 5". Weight: 12.5kg (27.6lbs).

CT601. As 701 but without programming functions £395


Price includes VAT and P&P. Send cheques, PO. or phone your ACCESS, VISA or B'CARD number to:

TEMPUS


LEADING CASIO SPECIALISTS
Dept ET1
38 Burtleigh Street, Cambridge CB1 1DG
Telephone: 0223 312866

DELIVERY
NORMALLY
BY RETURN

PCB FOIL PATTERNS

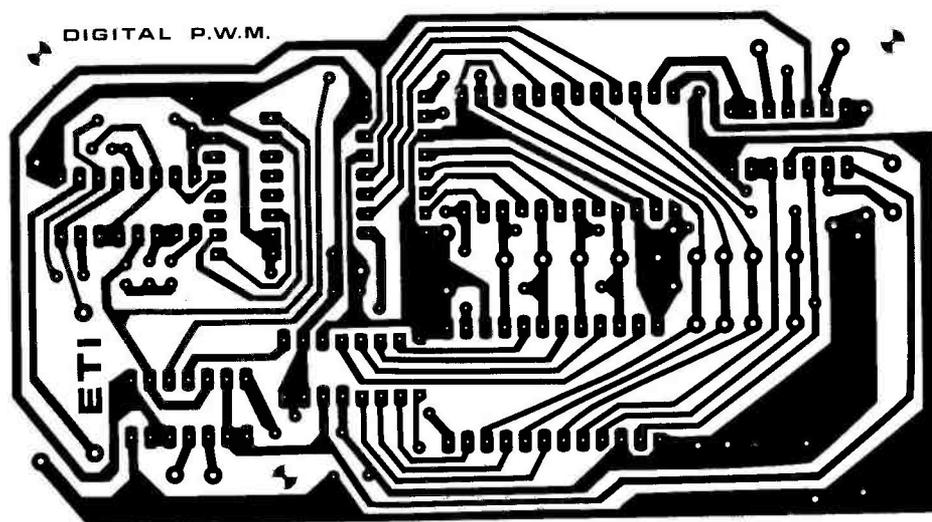






Above: The Digital PWM foil pattern.

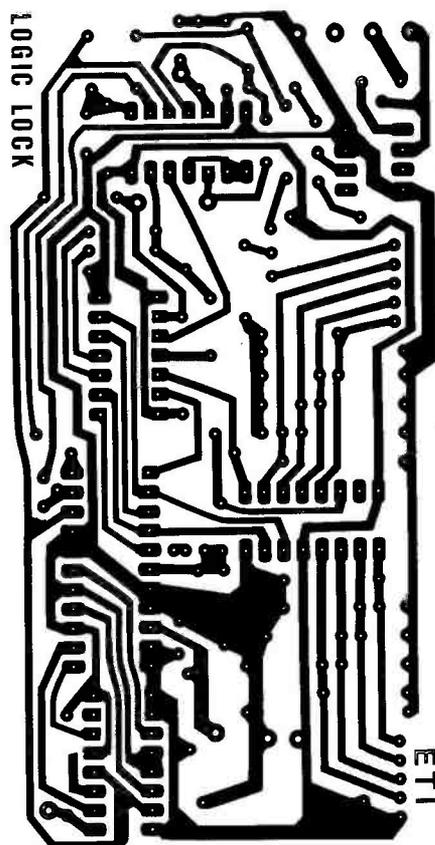

Above: The Logic Lock PCB.

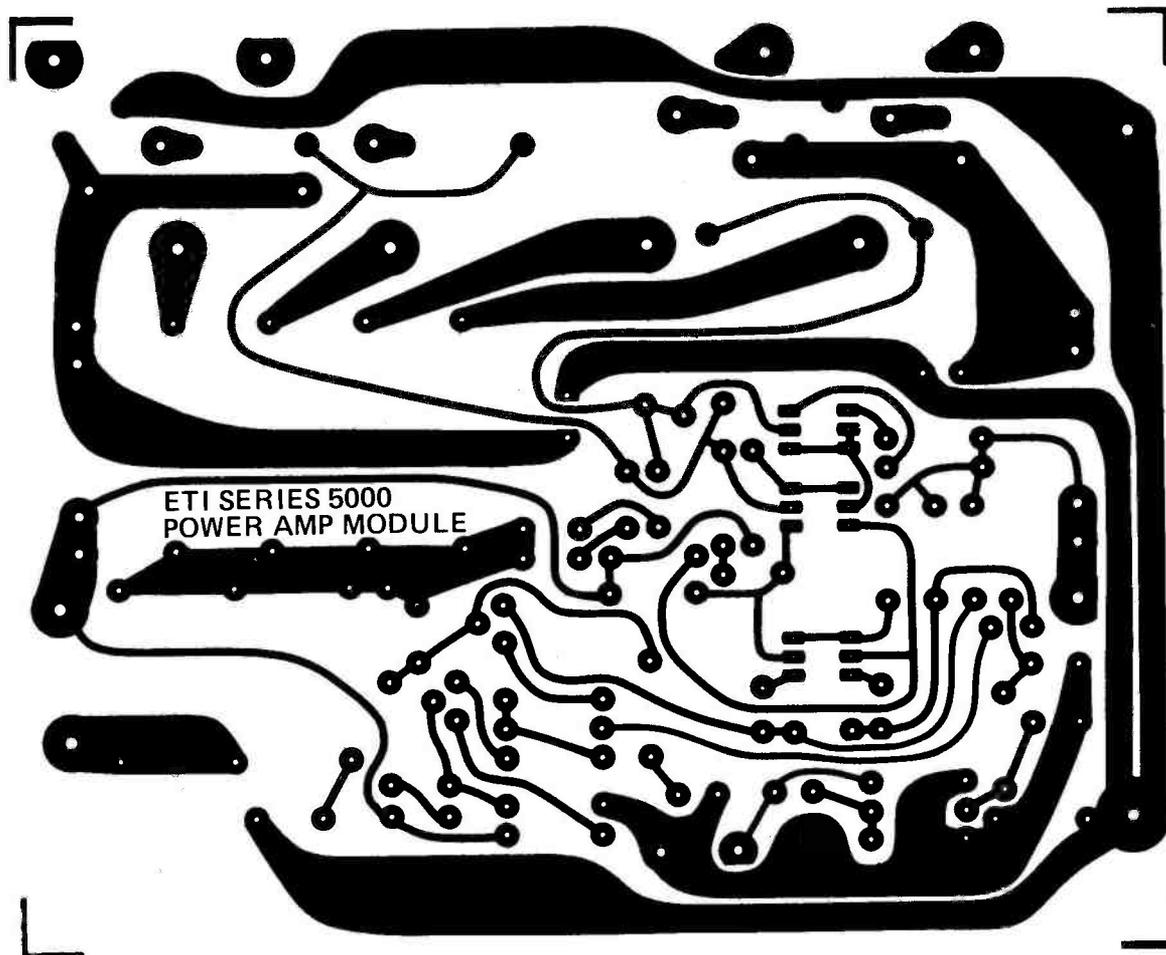Below: The board for the MOSFET power amp module.




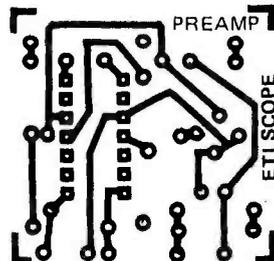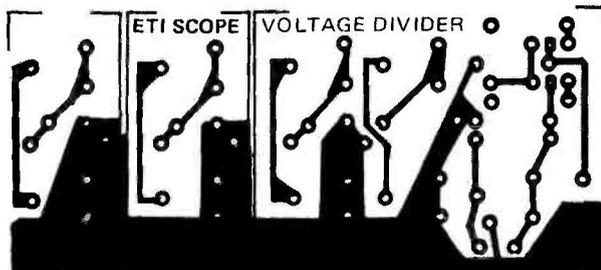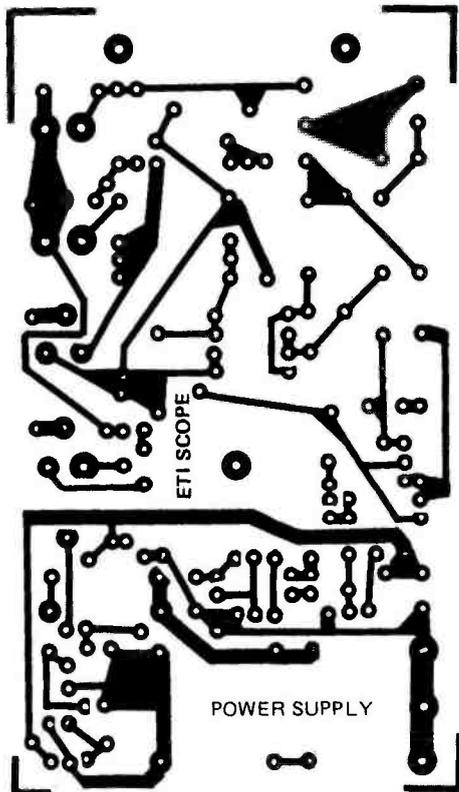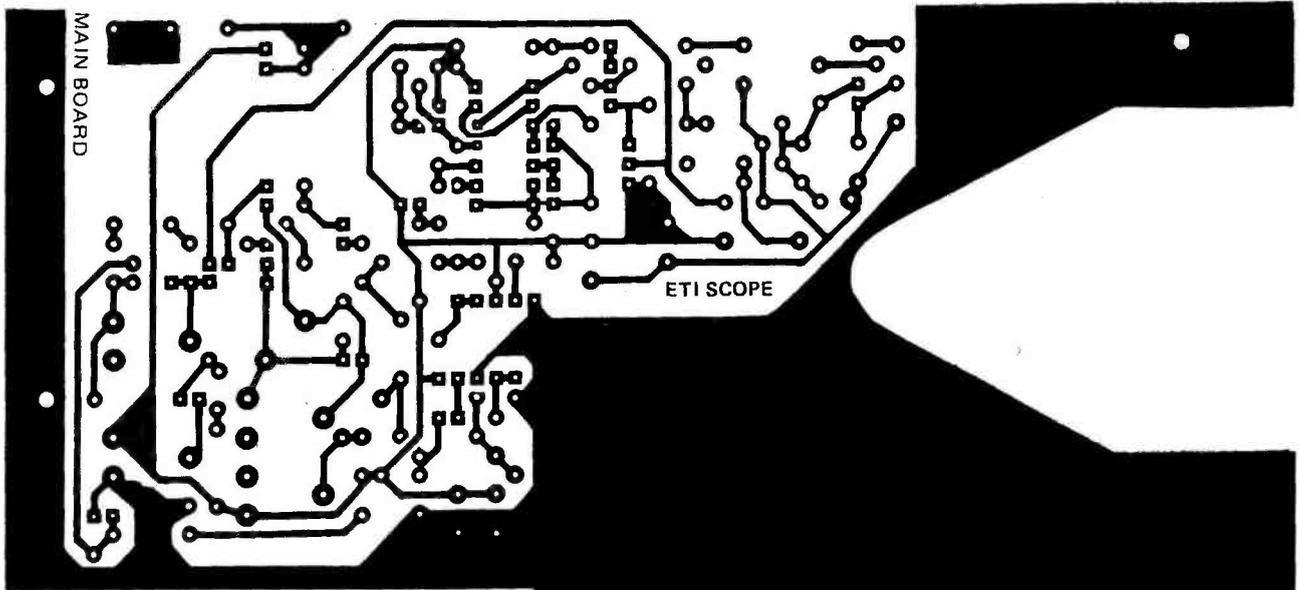

Above and left: The four boards for the Oscilloscope.



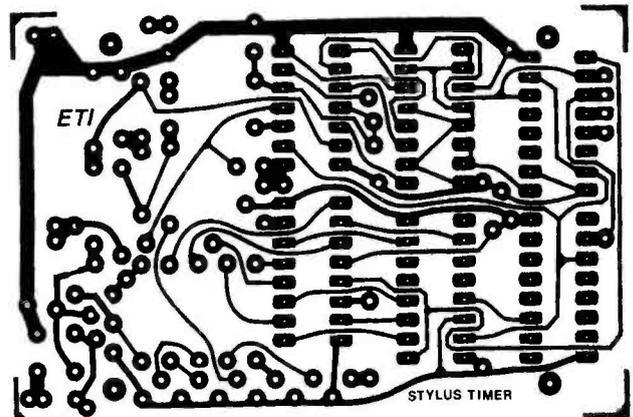Left: The Proximity Detector PCB.
Right: Foil pattern for the ETI Stylus Timer.



ELECTROVALUE

**A SPECIAL
SUMMER
PROMOTION**



**FREE VOUCHERS
TO SAVE YOU UP TO**

£2.10

THREE 70p REFUND VOUCHERS FREE for spending singly at any time on any one C.W.O. (U.K.) order minimum list value £10. This can quickly save you up to £2.10 in addition to the other benefits you enjoy by buying from Electrovalue. Send 70p for Catalogue 82 + 3 free vouchers by return now

+ USUAL DISCOUNTS + FREE POSTAGE

DISCOUNTS

5% on orders over £23 (inc. V.A.T.)
10% on orders over £57.50 (inc. V.A.T.)
on most catalogue items, but not on payments by credit cards.

POSTAGE

Not charged on U.K. orders over £5.75 inc. V.A.T. If under, add 40p handling charge.

- SEMI-CONDUCTORS/ICs/OPTOs
 - COMPUTERS/SOFTWARE etc.
 - CAPACITORS/RESISTORS
 - CONNECTORS/SWITCHES/KNOBS
 - POTS/FERRITES/METERS
 - BOOKS/SOLDER TOOLS
- AND MORE AND MORE AND MORE**

ELECTROVALUE LTD. DEPT. 280 St. James Road, Englefield Green, Egham, Surrey TW20 0HB
Phone: Egham 33603 (STD 0784; London 87). Telex: 264475
Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1MA. Phone: (061) 42 4945

USED EQUIPMENT

Ex-P.O. Multimeters in leather case. AC/DC Volts, DC current, ohms. Absolute Bargain
£8 + £1.50 p&p

500V MEGGER

Transistorised Insulation Tester and four decade resistance bridge with four ranges. Invaluable piece of test gear. In case with carrying handle. Uses one PP9 batt. £15.00 + £2 P&P

Recent Style P.O. Telephones
£4.75 + £1.80 P&P
2 for £9 + £2.50. 5 for £20 + £5

5 Digit Counters 48V coil. Non resetable
75p

AUTOMATIC DIAL UNIT. (mains powered). These units were made to connect into a telephone and dial a number when a punch-card is inserted. Card & instructions supplied. Cards readily available. Many uses. Only £8 + £1 p&p


UNISELECTORS. 50v, 4 Bank + Homing Bank, 25 way £3.50

D CONNECTOR SOCKETS with cover. 50 way £2

60V 8A TRANSFORMER. Ideal for big power supply unit or amplifier £12 inc. p&p. BEAT THAT!

FREE on request - Leaflet 'D.I.Y. Telephone Systems and Automatic Exchange Design'.

LOW-COST, RUGGED TEMPERATURE CONTROL

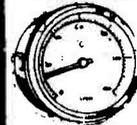

HIGH QUALITY

TEMP. GAUGE 0° - 120°C

Remote sensor on 38" capillary, panel mounting dial 55mm. dia.

ONLY £1.85

16A 240V RANCO THERMOSTAT

Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. £2.30, including control knob

RANCO THERMAL CUT-OUT 100°C

15A 240V. Sensing coil on 41in. capillary panel mounting with reset button £1.20

BUY ONE EACH OF ABOVE FOR £4.85



AVOMETER

Similar to Model 71 which currently retails for over £45. These units are, as with all of our used equipment, Tested and Guaranteed to be in good working order. Price includes Leather case.

20K Ohms per Volt (D.C.) 1K Ohms per Volt (A.C.)
D.C. Volts - 1, 2.5, 10, 25, 100, 250, 1,000
A.C. Volts - 10, 25, 100, 250, 1,000
D.C. mA - .05, 1, 10, 100, 1,000
OHMS - x 1, x 100, x 10K

LIMITED STOCK AT £14.50 + £1 p&p

PROFESSIONAL QUALITY P.A. MODULES

All to near broadcast spec. 7" x 2" rack mounting. Require 40 to 50 volt stabilised supply. Line Distribution Amp 30K in, 4 x 600 out. Gain control gives up to 20dB. Mixer - 10 stereo or 20 mono channels (no controls) gain up to 10dB. £12 each + £1.50 p&p.
MIC AMP - Switchable gain + fine gain control + L.F. Cut. £14.50 + £1.50 p&p.



L.E.M. SERVICES
238 RUGBY ROAD
LEAMINGTON SPA CV32 6DY
WARWICKSHIRE

**ADD 50p P&P
ORDERS OVER
£7.50 POST FREE**
unless stated otherwise

TEL: 0926 30622 FOR QUANTITY DISCOUNTS ETC.
ALL ITEMS - MONEY BACK IF NOT DELIGHTED.

MAGENTA ELECTRONICS LTD.

E.T.I. KITS - full kits include printed circuit boards, components, hardware, I.C. sockets, case etc. unless stated. (Not batteries). If you do not have the issue of E.T.I. which includes the project - you will need to order the instruction reprint as an extra 45p each. Reprints available separately 45p each + p&p 45p.

INSULATION TESTER May 82.....	£16.98	RECHARGEABLE BATTERY extra.....	£43.33
SOUND EFFECTS 3. PHASOR/EXPLOSION May 82.....	£11.29	HEARTBEAT MONITOR Aug 81.....	£26.26
SOUND EFFECTS 4. GUNSHOT May 82.....	£10.98	HANDCLAP SYNTHESISER Aug 81.....	£29.98
AUTORANGING CAPACITANCE METER Mar /April 82.....	£71.99	WAH PHASE June 81, Less pedal.....	£19.19
ACCURATE VOLTAGE MONITOR Apr 82.....	£13.63	LED JEWELLERY June 81, Cross Star £9.41, Spiral £7.20.....	£2.47
AUTOMATIC CONTRAST METER Apr 82, less extrusion.....	£26.77	ALIEN ATTACK Jan 81.....	£19.76
SOUND EFFECTS 1 BOMB DROP Apr 82.....	£12.47	GUITAR NOTE EXPANDER April 81.....	£16.47
SOUND EFFECTS 2. STEAM TRAIN April 82.....	£11.87	DRUM MACHINE April 81.....	£59.98
HIGH QUALITY PHONO AMPLIFIERS Feb 82, less case.....	£17.98	ENGINEERS STETHOSCOPE Mar 81.....	£19.19
MOVING COIL STAGE.....	£17.98	SOUND PRESSURE LEVEL METER Feb 81.....	£39.98
MOVING MAGNET STAGE.....	£17.68	INFRA RED ALARM Feb 81.....	£54.98
PEST CONTROL Feb 82.....	£6.77	4 INPUT MIXER Dec 80.....	£19.77
GUITAR TUNER Jan 82.....	£28.98	MUSICAL DOORBELL Dec 80.....	£11.61
COMPONENT TESTER Dec 81.....	£7.98	METRONOME Nov 80.....	£5.98
MUSIC PROCESSOR Nov 81.....	£49.98	CASSETTE INTERFACE Oct 80.....	£26.82
CAR ALARM Nov 81.....	£17.98	ULTRASONIC BURGLAR ALARM Aug 80.....	£20.26
ENLARGER TIMER Oct.....	£26.59	CAPACITANCE METER Aug 80.....	£10.97
SOUND BENDER Oct 81.....	£20.76	CMOS LOGIC TESTER Aug 80.....	£11.56
WATCHDOG SECURITY ALARM Aug 81.....	£16.98	CLICK ELIMINATOR April 79.....	£61.56

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST
Price list included with orders or send sae (9 x 4)
CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery

Send 80p in stamps or add 80p to order.


MORE KITS FROM H.E., E.E. and E.T.I. PROJECTS IN THE PRICE LIST

SOLDERING/TOOLS

ANTEX XS SOLDERING IRON 25W £5.48
SOLDERING IRON STAND £2.40
SPARE BITS Small, standard, large. For XS and X25 irons 65p each
SOLDER Handy size 99p
SOLDER CARTON £1.84
DESOLDER BRAID 69p
DESOLDER PUMP £6.48
HEAT SINK TWEEZERS 29p
HOW TO SOLDER LEAFLET 12p
LOW COST CUTTERS £1.69
LOW COST LONG NOSE PLIERS £1.88
WIRE STRIPPERS + CUTTERS £2.69

HELPING HANDS JIG £6.30

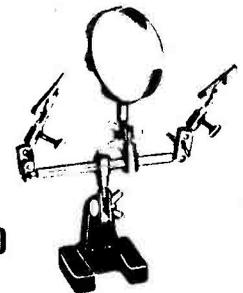VERO SPOT FACE CUTTER £1.49
PIN INSERTION TOOL £1.98
VEROPINS (pk of 1001 0.1" 52p)
MULTIMETER TYPE 1 (1,000 opv) £6.66
MULTIMETER TYPE 2 (20,000 opv) with transistor tester. Very good £14.75
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips..... 98p
RESISTOR COLOUR CODE CALCULATOR..... 21p
CONNECTING WIRE PACK TYPE ED, 11 colours..... 49p



ILLUMINATED MAGNIFIERS
Small 2" dia. (5x mag.)..... £1.14
Large 3" dia. (4x mag.)..... £2.40
CAST IRON VICE..... £2.98
SCREWDRIVER SET..... £1.98
POCKET TOOL SET..... £3.98
EUROBREADBOARD..... £6.20
S DECO BREADBOARD..... £3.98
BIMBOARD 1 BREADBOARD..... £6.98
VEROBLOC BREADBOARD..... £4.20

SEMICONDUCTOR DATA BOOK. Newnes Revised..... £5.90
3mm RED LEDs with clips 10 for..... 99p
GLASS MERCURY TILT SWITCHES 5 for..... 99p

MIN SPST pcb mounting Slide Switches 10 for..... 50p
TIL38 I.R. emitter 3 for..... 99p
BPW41 I.R. detector 3 for..... £1.40
OM355 I.C..... £8.98
LM394CH..... £2.48

Please mention Electronics Today when replying to this advert

MAGENTA ELECTRONICS LTD

EX13, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS
DE14 2ST. 0283 65435. MON.-FRI. 9-5. MAIL ORDER ONLY
ADD 45p P & P TO ALL ORDERS

ALL PRICES INCLUDE 15% V.A.T. P & P 45p



OFFICIAL ORDERS WELCOME.
IRISH REPUBLIC & B.F.P.O. EUROPE.
Deduct 10% from prices shown Payment must be in Sterling.
ACCESS and BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST.
SAE ALL ENQUIRES.

GREENWELD

443A Millbrook Road Southampton SO1 0HX

All prices include VAT at 15% — just add 50p post

1982/3 CATALOGUE

Bigger! Better! Buy one!!

- Only 76p inc. post — Look what you get!!
 - Vouchers worth 60p
 - 1st class reply paid envelope
 - Wholesale list for bulk buyers
 - Bargain List with hundreds of surplus lines
 - Huge range of components
 - Low, low prices
- Sent free to schools, colleges etc.

1000 RESISTORS £2.50

We've just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same price!! K523 — 1000 mixed ¼ and ½W 5% carbon film resistors, preformed for PCB mntg. Enormous range of preferred values. 1000 for £2.50: 5000 £10: 20k £36

200 ELECTROLYTICS £4.00


K524 Large variety of values/voltages, mostly cropped leads for PCB mntg. 1—1000uF, 10—63V. All new full spec components, not chuck-outs!! 200 £4: 1000 £17.50

LIE DETECTOR



This beautifully made precision instrument is not a toy or gimmick, it was originally used on an Open University course to measure changes in emotional balance by detecting small changes in skin resistance. Full details of how to use it are provided, together with a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 x 4½V batteries. Overall size 155 x 100 x 100mm. The 100-0-100uA 4" panel meter is worth more than we're asking for the whole unit!! £7.95

STABILIZED PSU PANEL

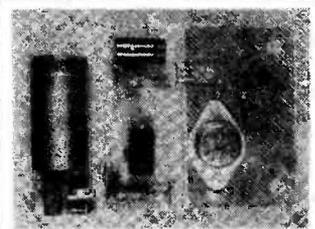

A199 A versatile stabilized power supply with both voltage (0-30V) and current (20mA-2A) fully variable. Many uses inc bench PSU, Nicad charger, gen. purpose testing. Panel ready built, tested and calibrated. £7.75. Suitable transformer and pots £6.00. Full data supplied.

PACKS PACKS PACKS

K517 Transistor Pack. 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114, 117, 172, 182, 183, 198, 239, 251, 214, 255, 320, BF198, 255, 394, 2N3904 etc etc. Retail cost £7+. Special low price 275p

K520 Switch Pack. 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p

K521 Heatshrink pack, 5 different diameters each 200mm long. What a bargain 50p

K522 Copper clad board. All pieces too small for our etching kits. Mostly double sided fibreglass. 250g (approx 110 sq ins) for 100p


K541 It's back!! Our most popular pack ever — Vero offcuts. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq ins of vero copper clad offcuts, average size 4 x 3". Offered at around ½ the price of a new board 320p

'MICROVISION' Cartridges

These are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag is we don't have any consoles!! However, they can be used as an oscillator with 4 different freq. outputs simply by connecting a battery and speaker. Tested and working (as an oscil with pin out data. PCB size 72 x 60mm.

ONLY 25p each!!

ELECTRO-DIAL

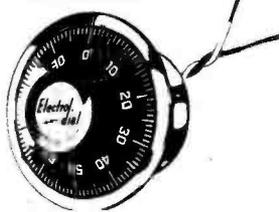

Electrical combination lock for maximum security, absolutely pick-proof!! One million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid etc. Overall dia 65mm x 60mm deep. Finished in bright chrome. With combination the price is £9.95. Also available without combination, but instructions are provided on how to find it. Takes about 20mins £2.95

COMPONENTS

2200uF 100V cans 77 x 35mm 75p each; 10 for £5.50
MK4027 shift register 8 for £6
2102B RAM 8 for £3
2708 EPROM £1.50
MIR50 infra red 5mm LED 30p
DM160 tuning indicator 50p
RC4136 op-amp similar to 741. 14DIL package 10 for £1
AY-5-4007D 24DIL chip counter/display. 4 decade up/down 7 seg o/p 0-6MHz. — 12, — 5V supply £1
FND501 + — 1 0.5in red display comm. cathode £25p
MAN6710 Dual digit Red 0.56in 7 seg display. Supplied with pin-out and data £1.00
Murata ceramic filter 5.5MHz 40p
10M ½W resistors 5% carbon film. Pack of 200 for £1

MIXED LED PACK

All new full spec by Micro, Fairchild, etc. Red, Yellow, Green, Amber, Clear, 3mm & 5mm. Pack of 50 assid £3.95; 250 £15

SOLENOIDS AND RELAYS

W921 Solenoid rated 48V at 25% duty cycle, but work well on 24V 1700gm pull, 10mm travel) push or pull 27 x 18 x 15mm 55p

W922 Mains 240V ac solenoid, 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50

W895 9V DC relay 500R SPCO 28 x 24 x 19. 50p
W733 11 pin plug in relay, 240V ac, 3PCO 5A contacts £2.50. Base £36p

W838 700R 24V 4PCO "continental" relay 35 x 30 x 18, only 84p; 10/£7.00

W847 37R 5—10V relay, SP 3A contact, PCB mntg 11 x 33 x 20. 95p; 10/£7.50

W893 Omron LY4 mains relay, 4PCO 5A contacts. £2.50

W896 24V ac coil, but works well on 6V DC. 2 x 10A c/o contacts. Ex-equip, only 60p

5V 3A REGULATED PSU KIT

A197 All components + heat sink to build this simple yet useful power supply. A regulated output of 5V at up to 3A for just £2.50. Suitable transformer (9V 3A) £4.85.

AMAZING! COMPUTER GAMES PCB's for PEANUTS!!

A bulk purchase of PCB's from several well known computer games including Battleships, Simon, Logic 5 and Starbird enable us to offer these at incredibly low prices:

'STARBIRD'

Gives realistic engine sounds and flashing laser blasts — accelerating engine noise when pointed up, decelerating engine noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt. clip (needs PP3). PCB size 130 x 60mm. Only £2.95

'SIMON'

The object of this game is to repeat correctly a longer and longer sequence of signals in 3 different games. (Instructions included). PCB contains chips, switches, lampholders and lamps, and is tested working, complete with speaker. Needs PP3 and 2 x HP11. PCB size 130 x 130mm. Only £3.95

'COMPUTER BATTLESHIPS'

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value only (PCB may be chipped or cracked): SN76477 sound IC; TMS1000 u-processor; batt clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

SECOND GENERATION POWERFET AMPLIFIERS

NEW DESIGNS


With the introduction of two new boards PANTECHNIC have pushed forward the performance and reliability of their powerfet amplifiers. Four key improvements have been incorporated in these second generation modules —

- 1.) The use of H-PAK powerfets, resulting in improved thermal efficiency and consequently enhanced power output capabilities.
- 2.) Low C_{OB} drivers now in power transistor packages, maintaining the superb HF performance and improving driver reliability.
- 3.) Separate driver and input supply rails allowing a 10% increase in available output power by increasing output stage efficiency.
- 4.) Bridge mode input pin allowing instant bridging between any two amplifiers without the need for extra circuitry.

PFA100 Specification

Bandwidth 10Hz-100KHz + 1dB
Output Power into 8M 100W (V_s = + 55V)
THD (20Hz-20KHz) 0.006%
THD (1KHz at 100W) 0.004%
SNR 120dB
Slew rate 20 V/μs
Gain x 23
Rin 30K
V_s max + 70V

Price £18.45

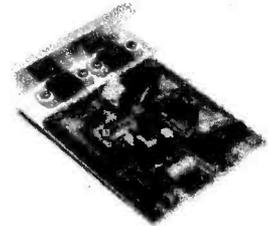


PFA100 120W into 8M

PFA200 Specification

Bandwidth 10Hz-100KHz + 1dB
Output power into 8M 150W (V_s = + 60V)
THD (20Hz-20KHz) 0.005%
THD (1KHz at 150W) 0.002%
SNR 120dB
Slew rate 20V/μs
Gain x 23
Rin 30K
V_s max + 70V

Price £25.95

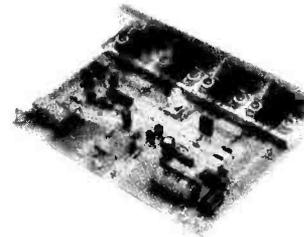

PFA200 180W into 8M
300W into 4M

POWER SUPPLY COMPONENTS

Toroidal Mains Transformers

Voltage	160	225	300	500	625
40-0-40	11-51	13-75	15-59	—	—
45-0-45	—	13-75	15-59	20-45	—
50-0-50	—	—	—	20-45	27-53

Special low flux windings. Carriage + VAT included

25A 400PIV Bridge rectifier £2.50
100,000uF 80V Electrolytics £4.75

Phone or write for advice on selecting the right components for your particular application.

All prices VAT inc. Carriage 75p. Trade lists available.

Ask about our preamps, protection boards and lower and higher power amp modules.

THE POWERFET SPECIALISTS

pantechnic

(incorporating J.W. Rimmer)

Dept ET1/5, 148 Quarry Street, Liverpool L25 6HQ.

Telephone: 051 428 8485

Technical enquiries:

367 Green Lanes, London N4 1DY. Tel. 01 800 6667

TTL CMOS 74LS LEDs

LB ELECTRONICS

LINEAR RAMS EPROMS SURPLUS

TELEPHONE: UXBRIDGE 55399

SUPERSALE '81

All full spec. brand new devices. 2114 (450ns) £1.00, 4116 (200ns) £1.15, 2708 £1.85, 2516 (single rail) £3.00, NEC 2732 £5.50, 2532 £6.00, 2114 (200ns) £1.40. P/P 35p on above devices.
Brand new and boxed, Lie Detector. Made for the Open University. size: 150mm (length) x 100mm (width) x 90mm (height). Complete with 100 microamp motor movement 90mm x 75mm. Supplied complete with leads and pads, less batteries (2 x 4.5v) £7.50 + £2 p/p.

SELF-CONTAINED battery powered digital recorders. Complete with data entry keyboard with 10 digit LED display plus modern interface and charger. Some data £25 per system. Sorry, callers only.

ZETTLER low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.5 amps a.c. contacts. 85p p/p 35p.

D TYPE CONNECTORS

9 Way Socket (solder) 75p
15 Way wirewrap plug £1.00
37 Way Plug (solder) £1.80
37 Way Socket (solder) £1.80
25 Way Plug (solder) £1.85
25 Way Socket (solder) £1.85
25 Way Plug (insulation piercing) £2.65
25 Way Socket (insulation piercing) £2.65
50 Way Plug (solder) £2.00
P/P on above 35p

COVERS

37 Way (Plastic) £1.00, 50 Way (Plastic) £1.20, 25 Way (Plastic) 95p, 25 Way (Metal) £1.25, 25 Way (Metal) ITT open £1.00, 15 Way (Plastic) 60p, 15 Way (Metal) 95p
P/P on above 35p

DISPLAYS

HP 5082/7414 4 digit DIL display full spec £1.50 each, p&p 35p. Large quantities POA.

HP5082/7650 4" CA left and right decimal point, high brightness, only 65p, 12 for £6.50, p&p 35p.

SUPERSAVER 1

DIL header Plugs (No covers) 14 way 18p, 16 way 25p, 24 way 95p (all gold plated) p/p 35p.
Ansley Header plugs. 14 Way 75p, 16 Way 95p, 24 Way £1.50. (Insulation piercing type) p/p 35p.
Ansley I/O Header plugs PCB Mounting .1in 26 Way straight 65p, 40 Way r/a £1 p/p 35p.

SUPERSAVER 2

Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.

SUPERSAVER 3

PRICE SMASH FND500 5in. LED displays, full spec 65p each, p&p 35p, large quantities POA.

SUPERSAVER 5

3M 26 way insulation piercing sockets £1.40 p/p 25p.

SUPERSAVER 6

VIDEO LEAD
1 1/2 metres with PL259 plug £1.00 p/p 35p

SUPERSAVER 7

Thyristors Type 16 Ria 100 Vrrm 1000 Volts at 22 amps £1.65 each. Limited stock, p/p 35p
Stud mounted rectifiers, type 40 HF 100 1250 volts, 40 amp, 4 for £2.50 p/p 35p

SUPERSAVER 8

ONE ONLY - TEXAS SILENT 700 TERMINAL. RS232 110 baud. As new - £235. Carriage at cost.

SUPERSAVER 9

VELLEMAN EPROM Programmer kit £200. Built £300 + VAT. S.A.E. for full descriptive leaflet.

SUPERSAVER 10

Tangerine Microtran 65 Blank PCB. Brand new plus circuit diagram £4.50, p/p 50p (6502 based, 1K on board).

SUPERSAVER II

PAPST MINI-FAN 3 1/4" x 3 1/4" x 1.5" deep. 220v 50Hz. Brand new and boxed. £9.50 p/p £1.00.

SUPERSAVER 12

2.5mm power plug and 2 metres of cable. Suitable for Acorn Atom, ZX81 etc. Only £1.00 per 10 p/p 25p. Trade enquiries welcome.

SUPERSAVER 14

BOX FANS 115V 50/60Hz. 120mm x 120mm. New. £4.50. 250V £6.50. P&P £1.00.

SUPERSAVER 15

5K 3/4" multiturn trim pots, PCB mounting, per box of 14 £2.50. As above 1K and 50K, p&p 35p.

SUPERSAVER 16

OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1, p&p 35p.

SUPERSAVER 17

VU METER 48mm x 50mm approx. overall size. Face size 50mm x 28mm approx. Brand new. £1.15 p&p 30p. (Sent at purchaser's risk).

SUPERSAVER 18 SALE

PCB AMP (LM380). Unused. 65mm x 95mm approx. 9.12v DC. 85p p&p 35p.

SUPERSAVER 19

10 DIGIT (Red), LED display. (1.22in. digit size). With built-in driver chip and built-in lens magnifier. Data sheet supplied. Brand new. £1.50 p&p 35p.

SUPERSAVER 20

4 1/2in. JUMPER LEAD. 16 DIL header to 16 DIL header. 95p p&p 30p.

SUPERSAVER 21

8251 £3.00 ea, 8253 £6.00 ea, 8224 £2.00 ea, AY/5/1013 £2.25 p/p 35p.

SUPERSAVER 22

11b reel of solder 1R SWG 64/36 alloy £5.50 p&p 90p.

A TERRIFIC GIVEAWAY. MC

1489 RS232 RECEIVER. Brand new 46p each, 10 for £3.50. Large quantities p.o.a. p&p 30p.

SUPERSAVER 23

64 Way DIN 41612 edge connectors to fit Microtran etc. plug or socket £3.45 ea. p/p 35p ea.

JUST ARRIVED large quantity of assorted Microwave Wave Guides, various bands + noise sources from £5. Callers only.

MICRO REVOLUTION

The New Z8 Processor, Complete PCB and parts to produce this new CBU, built in tiny Basic and 4K Ram. RS232C output plus User Ports. Only 4.5" x 4.5" £85 + VAT. Further details SAE P/P £2.00. Motherboard plus Eprom Programmer to follow shortly.

AUGATIC SOCKETS

(The best available)

16 DIL 20p 24 DIL 50p
18 DIL 25p 40 DIL 55p

WE STOCK a vast range of TTL, CMOS, some 74LS, MINIATURE TOGGLES, etc.

PSUs. We have a large stock of power supplies at very realistic prices (callers).

NEW LINES

UECL Edge connector .1" 75 Way gold plated (wire wrap) £1.65 each p/p 35p.

REG PCB (less components), 5V 1 amp, 12V 1 amp and heatsink (60mm x 90mm). Brand new, £1.00. Heatsink only, 55p. P/P 35p.

NEC FIP4B13 4 digit glass display (green with centre colons and plus and minus sign), only £1.35. P/P 30p.

PL259 SOCKET CHASSIS MOUNT. 50p p&p 30p.

TRANSFORMERS 012, 024 1 amp £2.50, P&P 50p.

TTL SALE 7410 9p, 7413 18p, 7416 18p, 7490 28p, 74155 45p, 74174 60p, 74181 74285 £2.25. P&P 35p.

WHY PAY POUNDS? - Just arrived Amphenol 36-way plug and socket (used) to fit all your printer. Only £2.75 per pair. P/P 35p.

Terms cash with order (official orders welcomed from colleges, etc.). All enquiries s.a.e. please. All prices inclusive of VAT, unless otherwise stated. Postage as shown per item.

MICRO REVOLUTION

The new Z8 processor complete PCB and parts to produce this new RS232 CPU. Built in tiny basic and 4K RAM only 4.5" x 4.5" £85.00 + VAT p/p £2.00. Leaflet SAE.

PLEASE DO NOT ORDER GOODS FROM OLD ADVERTS. PHONE BEFORE ORDERING.

SURPLUS STOCKS
PURCHASED FOR CASH

LB ELECTRONICS
11 HERCIES ROAD
HILLINGDON, MIDDLESEX
UB10 9LS, ENGLAND

All enquiries s.a.e. please
Telephone answering machine service out of business hours.

New retail premises, now open Mon, Tues, Thurs, Fri, and Sat, 9.30-6.00 Lunch 1-2.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer.

ALL PRICES INCLUSIVE OF VAT
UXBRIDGE 55399
All components full spec.

NAMAL ASSOCIATES

No. 1 CLAYGATE ROAD, CAMBRIDGE CB1 4JZ
Tel. 0223 248257 TLX 817445

Computer I.C.s

2144-200	.99	27	.12	132	.44
2144-200LP	.99	28	.15	138	.33
2532	4.10	30	.12	145	.74
2716	1.95	32	.12	148	.95
2732	4.10	33	.16	151	.30
4116-150	.75	37	.15	153	.28
4116-200	.65	38	.15	154	.80
6116	4.75	40	.12	155	.38
5516	7.50	42	.33	156	.36
6800	2.75	47	.38	157	.30
6802	3.60	48	.59	161	.37
6809	8.75	49	.59	162	.40
6810	1.15	51	.14	163	.38
6821	1.15	54	.14	164	.46
6850	1.40	55	.12	165	.90
8085A	5.25	73	.21	173	.69
8224	1.85	74	.16	174	.46
8228	3.75	75	.24	175	.46
8255	3.30	76	.20	193	.45
Z80 CPU	3.25	78	.19	196	.57
Z & A CPU	3.60	83	.44	197	.60
Z80 P10	3.60	85	.60	240	.87
Z80 AP10	3.60	86	.15	241	.87
Z80 CTC	2.75	90	.30	242	.78
Z80 ACTC	3.25	91	.74	244	.60
		92	.33	245	.88
		93	.33	247	.60
		95	.42	248	.60
		100	.21	257	.43
		109	.21	259	.78
		112	.21	266	.22
		113	.21	273	.70
		123	.43	290	.55
		124	.90	373	.70
		125	.24	374	.72
		126	.25	393	.60

74LS Series

00	.10	109
0104	.12	112
05	.14	113
08-13	.12	123
14	.38	124
15-22	.12	125
26	.16	126

Voltage Regu:

7805 5V +	.35
7812 12V +	.35
7815 15V +	.35
7905 5V +	.35
7912 12V	.35
7915 15V	.35
7924 24V	.35
LM323K	3.00

Crystals

100Hz	2.75
2.00MHz	2.65
3.276MHz	1.00
3.579MHz	1.00
3.932MHz	1.00
4.000MHz	1.58
4.194MHz	1.35
6.000MHz	1.00
6.144MHz	1.25
6.400MHz	1.50
10,000MHz	1.50

IC Sockets

8 PIN	.06
14 PIN	.09
16 PIN	.09
18 PIN	.13
20 PIN	.14
22 PIN	.17
24 PIN	.18
28 PIN	.25
40 PIN	.25

COMPUTERS

We stock computers and accept Sinclair ZX 81 in part exchange. Minimum of £20.00 is offered for your ZX81 in part exchange for a VIC 20 or Arcom colour Computers.

NEW

Domestic cassette INTERFACE for VIC 20 ONLY £17.00

Simply connects your VIC 20 to any Cassette player. A bargain at half the usual price.

NEW

VIC 20 Memory expansion Packs

3K RAM £21.00

8K RAM £58.70

(Expandable to 16K)

16K RAM £83.48

Simply plug into the existing expansion port of VIC 20.

Battery Ram backup available. Price on application.

WE GUARANTEE FACTORY PRIME PARTS

In depth stocks. Competitive prices. Government and colleges orders welcome. Please inquire for special prices for quantity orders. Please add P&P £1 & VAT. Minimum Order £10. Access orders welcome.

D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts Sealed base ideal for programming 6 position at less than half manufacturer's price ONLY 75p  Will fit into 14-pin dit socket. Ten at 65p ea., per 100 55p ea.	HONEYWELL PROXIMITY DETECTOR integral amplifier. By D.C. £3.50 ea. PHOTO CONDUCTIVE CELL £1.25. High-power CdS cell, 600mW, for control circuits. Resistance 800 ohm to 4K. Max. volts 240. Size 1/2" x 1/2". RIBBON MICROPHONE with pre-amp on chassis. £1.75	MULLARD MODULES LP1171 LP1179 IF Strip AM, FM Front end Pair £5.75 Complete with Data LP1106 LP1157 varicap Med & Long Tuner £2.50 CRYSTALS COLOUR TV 4,63819 mcs £1.25 Miniature type coded	ULTRA SONIC TRANSDUCERS 40KCS. Complete on 18in. Screened cable £1.75 each pairs £2.95. ULTRA SONIC TRANSMITTER Complete unit (uncased requires 15V). £3.25 FOSTER DYNAMIC MICROPHONES 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair
U.N.P. MODULATORS Latest type adjustable ideal for computers with data circuit. Size 3.2" x 1.1" inch. Only £2.50 in screened case	LM380 Amplifier 85p LM318N Hi-Slew Op Amp £1.50 LM323K 5v, 3 amp reg. £2.80 LM310N Volt. Follower £1.20 LM311H High Perf. Volt. Comparator £1.00 LM384N 5-watt Amp £1.20 LM383N Dual Com. 80p 7805 Reg 5v 75p	QUALITY FANS "Whisper Model" by Roton. Low power consumption (less than 10 watts). Silent running 115v (two in series for 230v 50/60Hz). Size 4 1/2" x 4 1/2" x 1 1/2". Only £8.50 inc. VAT BRAND NEW 50% less than manufacturer's price	STEREO CASSETTE Mechanisms 8 or 12 volt. Complete with Heads-Erase & Selenoid. £5.50 each. Grand new. TV Convergence Pots (Lini) 50 ohm 100 ohm 200 ohm 5K ohm all 50p each
MINIATURE EDGE indicator with illuminated dial. Scale 0 to 1.5 D. 100 messages. See 1 1/2" x 1 1/2" deep. Only £1.85	STEREO CASSETTE TAPE HEADS Quality replacement for most recorders with mounting plate Record/Replay £2.00 MARRIOTT TAPE HEADS Quarter track. Type KRPS18 Record/Replay (each) £2.00 KRPS36 Record/Replay (each) £3.00 XES11 Erase (each) £1.00	HEWLETT-PACKARD DISPLAYS 5082-7650 HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each.  Set of 6 for £5 Half-inch red common anode will replace DL707, 14-pin Di.	EX-MOTOROLA 5+5-WATT CAR STEREO AMPLIFIERS Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in) with circuit and data. Only £5 pair. Includes pre-amp.
MONSANTO Half-inch x 1 Display High Intensity. £1 each. set of 4 £3.50. Common anode. 14 Pin Dit Package.	RECHARGEABLE BATTERIES VARTA 3.6 volts DEAC. M-AN 225 £1.50 DRYFIT 6-volt, 4.5 amp £7.50 XTAL FILTER 10.7mcs, 12.5DB separation, 1/2" x 1/4" x 1/4" inch £3.00 100KCS + 1 meg 3.00 £2.00	"CHERRY" ADD-ON KEYPAD  A compact 12-button keypad suitable for use with Cherry Keyboard to extend its functions plus four extra keys. Supplied brand new with data. A 3 x 4 non-encoded single mode keyboard.	QUANTITY DISCOUNTS ON ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW unless otherwise stated. DELIVERY from stock - add post 35p per order. incl. VAT.

Henry's 01-723 1008/9
 Callers to: 404 EDGWARE ROAD, LONDON W2 1ED
 All mail orders/export enquiries, 11/12 Paddington Green, London W2

AUDIO VIDEO SERVICES
 19 Galsworth Avenue, Romford RM8 4PX
 01 599 6680
 Mall Order: CWO Please add 40p P&P
 VAT 15%. Send see for price list

TTL	74109 35p	4025 18p	LS10 18p
7400 10p	74121 32p	4027 27p	LS12 17p
7402 10p	74123 35p	4029 75p	LS13 32p
7403 14p	74141 45p	4040 60p	LS16 48p
7404 14p	74151 40p	4046 70p	LS20 16p
7407 25p	74153 40p	4049 25p	LS26 19p
7409 17p	74157 60p	4050 28p	LS30 18p
7410 14p	74160 55p	4051 62p	LS42 36p
7413 25p	74161 55p	4052 62p	LS51 17p
7414 34p	74162 54p	4053 62p	LS54 18p
7416 25p	74164 55p	4055 80p	LS73 30p
7420 14p	74174 70p	4060 85p	LS74 25p
7426 28p	74175 70p	4068 36p	LS80 33p
7430 15p		4069 17p	LS92 42p
7438 28p		4081 22p	LS93 39p
7441 55p	CMOS-B	4081 22p	LS107 35p
7442 40p	4001 12p	4082 22p	LS108 30p
7447 45p	4002 12p	4511 55p	LS123 60p
7451 16p	4009 12p	4518 45p	LS125 54p
7454 18p	4011 14p	4520 85p	LS126 49p
7473 25p	4012 18p	4543 115p	LS133 32p
7474 25p	4013 33p	4555 40p	LS138 60p
7486 25p	4016 28p	7415 74LS	LS139 40p
7480 25p	4017 50p		LS157 57p
7492 35p	4020 80p		LS160 54p
7493 30p	4023 19p		LS161 54p
74107 32p	4024 39p		LS164 49p

MEMORIES
 2102 105p
 2114-3 105p
 2114L-3 145p
 4116-3 95p
 2708 210p
 2716 375p

TRANSISTORS
 BC107/8 11p
 BC109 12p
 BC147/8 9p
 BC157/8 10p
 BC182/4 9p
 BC212/4 9p
 BCY71/2 22p
 BD131/2 40p
 BF194/7 10p
 BF259 32p
 BFY51 30p
 BU208 150p
 2N3055 44p

OPTO
 DL704 95p
 DL707 95p

LEDs
 Green, Red
 Small 12p
 Large 15p

REGS. TO-220
 7805 55p
 7812/5 60p
 7905/12/5 60p

DIL SOCKETS
 Low Profile
 8 pin 9p
 14 pin 9p
 16 pin 10p
 18 pin 18p
 24 pin 20p
 28 pin 24p
 40 pin 32p

VEROBOARDS
 Coprocessed 0.1" (A)
 Low Profile
 2.5" x 3.75" 73p
 2.5" x 5" 83p
 3.75" x 3.75" 83p
 5" x 3.75" 95p
 3.75" x 17" 326p
 4.7" x 17" 426p

ALARMS MADE

DIY KITS 'N' BITS

PROFESSIONAL EQUIPMENT AT DISCOUNT PRICES!

- KITS £32, £50, £75, £85 including full instructions ● CONTROL PANELS £18, £23, £29, £37 ● BELL BOXES £6.25, £7.50 ●
- PRESSURE PADS £1.06, £1.45, £2.45 ● 4 CORE CABLE (100m) £8 ● SIRENS £7.50 ● CONTACTS 72p, 74p, 76p ●
- ULTRASONIC £34.50 ● DOOR PHONES £49.42 ●

BUY A KIT OR DESIGN YOUR OWN SYSTEM
 SEND SAE OR PHONE NOW FOR FREE FULLY ILLUSTRATED CATALOGUE. IT TELLS YOU ALL YOU NEED TO KNOW!
 Carriage Included. VAT Extra 15%

A.D. Electronics, Dept ET6, 217 Warbrick Moor, Aintree, Liverpool L9 0HV 051 523 8440
 Trade Enquiries Welcome

ELECTRONIC IGNITION

Makes a good car better



As a KIT or READY BUILT

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3 1/2 times the energy of ordinary capacitive systems — 3 1/2 times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN
 ELECTRONICS TODAY INTERNATIONAL June '81 Issue
 AND EVERYDAY ELECTRONICS December '81 Issue

FITS ALL NEGATIVE EARTH VEHICLES,
 6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS
 Some older current impulse types (Smiths pre '74) require an adaptor — PRICE £2.95

STANDARD CAR KIT £14.85
Assembled and Tested £24.95

TWIN OUTPUT KIT £22.95
Assembled and Tested £34.70

PLUS £1.00 U.K. P. & P. Prices include VAT.

ELECTRONIZE DESIGN
 Dept. D., Magnus Road, Wilnecote Tamworth, B77 5BY
 Phone: (0827) 281000

VISA

Please
mention
E.T.I.
when replying
to all
adverts

LIGHTNING

DO YOU NEED: Electronic components, Tools, Test Equipment, Cases, Cabinets and Hardware Etc. **IN A HURRY??**
THEN YOU NEED:
LIGHTNING Electronic Components
WHY??????

Because **LIGHTNING** Strikes out where others fail:
Express Despatch
All Low Prices
In Depth Stock
All New Guaranteed Goods from Leading Manufacturers
With all that going for us, going to you, can you really afford to be without a copy of our brand new exciting CATALOGUE

Many Prices Reduced - Many More Stock Lines
Send for YOUR Copy Now ONLY 70p Post Paid

LIGHTNING ELECTRONIC COMPONENTS
84 Birchmoor Road, Birchmoor, Tamworth, Staffs B78 1AB
(NOTE New Address)

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.6AHr	SUB 'C' 1.2AHr	'C' (HP11) 1.65AHr	'C' (HP11) 2.0AHr	'D' (HP2) 4.0AHr	PP3 0.1AHr
1-24	£0.85	£1.38	£1.69	£2.25	£2.97	£3.79
25-49	£0.75	£1.28	£1.58	£2.10	£2.77	
50-99	£0.65	£1.15	£1.42	£2.02	£2.67	
100 up	£0.59	£1.05	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

CHARGERS - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with living leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04
DUAL O/P CHARGER £5.72

TRANSFORMERS - as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Data and charging circuits free with orders over £10 otherwise 30p post. P&P 10% if order less than £10. 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order.

Cheques, P.O.'s Mail Order to:-
SOLID STATE SECURITY,
Dept. (ETI) Bradshaw Lane,
Parbold, Wigan, Lancs.
Telephone 02576-3018.

CALCULATORS

SHARP



ONLY
£158.95

7 156 dot matrix display, 65 keys, 16K ROM, 3.5K RAM program in basic language


CE150 4 COLOUR PRINTER/INTERFACE £139.95
CE151 4K PLUG IN RAM PACK £47.95



EL5100
61 functions, 24 digits, 10 memories, 80 steps **£49.95**

EL5103 dot matrix display, 63 functions, 6 memories, 80 steps £28.95

CASIO

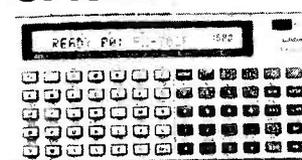

FX702P program in basic language, up to 1680 steps/226 memories, 55 functions

£97.95



FX602P
10 + 2 digit dot matrix display 50 functions, up to 512 steps/88 memories
£71.95

FA2 Cassette Interface £19.95

FP10 Printer Unit for 602/702 ... £43.95



AX210

versatile multi display, multi function alarm chronograph
£27.95



W250

water resistant to 10 atmospheres, day date, alarm, etc. stainless steel
£19.95



FX3600P
38 steps, 2 programs, 61 functions, lithium powered
£21.95



FX550
most sophisticated non programmable 50 functions, 10 digits
£18.95

TEXAS INSTRUMENTS

T158C
172 functions up to 480 steps/60 memories
£65.95

T159
magnetic card, up to 960 steps/100 memories
£119.95
Printer PC100C
£151.95
Programmer LCD new
£44.95



NEW T155-II
122 functions, 2 variable stats, linear regression up to 56 steps/8 memories, 10 digit LCDE
£32.95

hp HEWLETT PACKARD

HP41C
professional machine with full range of peripherals. 319 registers, 2240 program lines etc.

£182.95

HP11C
see ETI review
203 program lines, 21 addressable memories

£99.95

Export welcome - all payments in £ sterling
ALL PRICES INCLUDE VAT, POST & PACKING UK
All goods new, boxed and fully guaranteed. Large SA/E with enquiries please.

C.S.S. CALCULATOR SALES & SERVICE
PO Box 13, Reddith, Worcs B98 8NS
Telephone (0527) 43169



TECHNICAL STAFF

Would you like an opportunity to live in Australia and pursue a career in Telecommunications?

The Overseas Telecommunications Commission (Australia) which links Australia with the rest of the world by communications satellites, submarine cables and radio has vacancies for Technicians and Technical Officers.

The successful applicants will be involved in one of the following areas in the operation and maintenance of the Commission's:

- processor controlled switching and transmission equipment in the Sydney Metropolitan area
- international satellite communication facilities at Carnarvon - Western Australia, Ceduna - South Australia and Moree - New South Wales.
- submarine cable and HF radio facilities at Commission stations situated on the Australian Coast and Guam.

REMUNERATION:

Technician
Technical Officer Grade 1
Technical Officer Grade 2
Senior Technical Officer Grade 1

\$A14805-16080 p.a.
\$A14805-17759 p.a.
\$A18180-19086 p.a.
\$A19597-20517 p.a.

QUALIFICATIONS:

Successful completion of Part 3 - full Technological Certificate of the Telecommunications Technician's Course conducted by the City & Guilds of London Institute.

The Higher National Certificate in electrical or Electronic Engineering and registration as a Technician Engineer with the U.K. Engineer Registration Board. Or a recognised equivalent of the above.

For Technicians: 4 years of experience including time in training.

For Technical Officer: 6 years of experience including time in training.

General:

OTC offers excellent working conditions. At most locations staff work rostered shifts with a 9-day fortnight and attractive shift penalties are applicable.

Good opportunities exist for advancement to higher positions. Successful applicants must be prepared to serve at any of the Commission's stations within Australia if and when required. The Commission will reimburse removal expenses between stations.

Applications should set out details of position/s applied for, present position, qualifications and experience. Applications should be addressed to:

**The Director, Personnel and Administration Branch,
 Overseas Telecommunications Commission (Australia),
 G.P.O. Box 7000, SYDNEY, N.S.W. 2001.**

Applicants will be supplied with an information leaflet giving full details of the positions and conditions of employment. OTC Representatives will be conducting interviews in the United Kingdom.

C727D

PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7ER. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
 Special stock pack 60 values 10 off each **£5.50**

DIODES: **1N4148** 3p each. Min order quantity - 15 items.
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
 4 Way **86p** each 6 Way **£1.00** each 8 Way **£1.20** each

DIL SOCKETS: High quality, low profile sockets.
 8 pin - **16p**. 14 pin - **11p**. 16 pin - **12p**. 18 pin - **19p**. 20 pin - **21p**.
 22 pin - **23p**. 24 pin - **25p**. 28 pin - **27p**. 40 pin - **42p**.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
 MIN ORDER - U.K. £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

AMARAL Limited

26 HIGHFIELDS, EARLEY, READING RG6 2RZ, ENGLAND

Tel: National 0734 864745; International +44 734 864745

Access or Barclaycard Add VAT 15% 50p p&p, Mail Orders / Tel orders only
Send SAE for complete list

CMOS - 4001 15p; 4002 15p; 4006 52p; 4011 15p; 4012 15p; 4013 25p; 4016 26p; 4017 45p; 4020 53p; 4022 47p; 4023 15p; 4024 40p; 4025 15p; 4027 29p; 4028 50p; 4029 80p; 4040 50p; 4046 47p; 4046 67p; 4049 26p; 4050 26p; 4051 52p; 4052 52p; 4053 47p; 4060 78p; 4066 31p; 4068 15p; 4069 15p; 4070 15p; 4076 56p; 4081 15p; 4082 15p; 4085 39p; 4086 39p; 4511 57p; 4518 59p; 4520 57p; 4543 87p; 4555 43p; 40106 17p.

74LS - 00 12p; 02 13p; 04 14p; 08 14p; 10 13p; 11 14p; 14 47p; 20 13p; 21 15p; 27 15p; 28 18p; 30 13p; 32 13p; 40 13p; 42 40p; 73 24p; 74 22p; 76 24p; 85 71p; 86 17p; 90 39p; 93 44p; 112 23p; 123 60p; 126 31p; 132 40p; 138 38p; 139 38p; 153 47p; 155 47p; 157 37p; 164 55p; 166 116p; 173 53p; 174 37p; 175 37p; 193 63p; 221 60p; 240 83p; 241 83p; 244 73p; 245 90p; 251 46p; 253 51p; 257 44p; 279 39p; 283 46p; 366 38p; 367 38p; 373 81p; 374 79p; 393 80p.

MICROS ETC - Z80CPU 345p; Z80ACPU 395p; Z80CTC 295p; Z80ACTC 295p; Z80AP10 370p; Z80AP10 370p; 8085 375p; 8085A 525p; MC1488 58p; MC1489 58p.

CRYSTALS - 3.6864 125p; 4.0000 125p; 6.144 125p.

SPECIAL OFFER - Buy a Micro from us and get a crystal for 75p.

IC SOCKETS - 14 pin 8p; 16 pin 8p; 18 pin 12p; 24 pin 18p; 28 pin 24p; 40 pin 28p.


REGULATORS - T.O. 220 1 type - 7805 38p; 7812 38p; 7815 38p.

HENRY'S COMPUTER KIT DIVISION

404 EDGWARE RD, LONDON W2 1ED TEL: 01-402 6822
• TANGERINE • TANGERINE • TANGERINE

MICROTAN 65

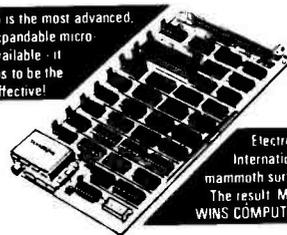Microtan 65 is the most advanced, powerful, expandable micro computer available - it also happens to be the most cost effective!



Electronic Today International held a mammoth survey of kits. The result: Microtan 65 WINS COMPUTER CLASS!

MICROTAN 65 CONTENTS

High quality plated thru hole printed circuit board, solder resist and silk screened component identification 8502 microprocessor 1K memory TANGUG Now with Y Bug 1K RAM for user programme, stack and display memory, VDU alphanumeric display of 16 rows by 32 characters, MICROTAN 65 system file binder 136 page, bound, users hardware/software manual with constructional details and sample programmes. Logic and discrete components to fully expand MICROTAN 65.

The MICROTAN 65 kit has won widespread acclaim for its superb presentation. We pay attention to detail - Kit Form **£69.00** + £10.35 VAT, total £79.35

MICROTAN 65 assembled and tested.

Specification as above, but assembled and fully bench tested by ourselves **£79.00** + £11.85 VAT, total £90.85

YOU MAY DEDUCT
£10

FROM MICROTAN 65 KITS AND ASSEMBLED UNITS LISTED HERE ONLY FROM US DELIVERY EX-STOCK POST PAID

Limited Quantity Available

ELECTROMART

**MONTHLY IN
ELECTRONICS TODAY —
YOUR OWN 'WHERE TO
BUY IT' GUIDE**

BEDFORDSHIRE

BROADWAY ELECTRONICS

1 The Broadway, Bedford,
Tel: 0234 213639

Open: 6 days 9.5.30. ½ day Thur.
lunch 1.30-2.30.
Specialists in electronic components and
Acorn computers.

DORSET

D.J. ELECTRONICS
64 Ensbury Park Road,
Bournemouth.
Tel: (0202) 515073.

Open: Mon-Sat 9am-6pm.

HAMPSHIRE

GAINS ELECTRONICS

3, West Street, Fareham.
Tel: (0329) 234891

Open: 6 days 9am-5.30pm.
RS component stockist. Wide range of components for
the enthusiast.

HERTFORDSHIRE

GODDARDS COMPONENTS
110 London Road, St. Albans.
Tel: St. Albans 64162

Open: Mon-Sat 9.30am-5.30pm
(½ day Thur)

**FOR SERVICE AND
CONVENIENCE — USE
YOUR LOCAL DEALER!**

**LOOKING FOR
COMPONENTS! HARDWARE!
CASES! TRY YOUR LOCAL
LISTED STOCKIST**

S. IRELAND

peals the world of electronics

25 Parnell St, Dublin 1.
Tel: Dublin 740662

Open: 6 days 9am-5.30pm
Components. Computers. Video games.

LANCASHIRE

ETESON ELECTRONICS

E.E. 15B Lower Green,
Poulton-le-Fylde, Blackpool
Tel: (0253) 885107

Open: 9.30am-12.30. 1.30-5.30. Closed Wed & Sun.
Electronic Component Specialists.

LONDON

SAMSONS ELECTRONICS LTD
9/10 Chapel St. 21/23 Bell St. NW1.
Tel: 01-262-5125, 01-723-7851.

Open: 10am-6pm. (Sat 11am-5pm).
Vast selection of components at ridiculous
prices.

W. MIDLANDS

PATH ELECTRONIC SERVICES
369 Alum Rock Road, B'ham.
Tel: 021 327 2339.

Open: 10am-6pm weekdays.
Sat 9.30am-5pm. Contact Peter A.
Thomas. Wholesale and retail supplies.

NOTTINGHAMSHIRE

DAMON electronics
99 Carrington St. Nottingham.
Tel: 53880 (mail order available)

Open: 6 days 9.30am-5.30pm.
Specialists in T.V. F.M. aerials.

**FOR YOUR BUSINESS TO
BE INCLUDED, CALL
ELECTROMART ON
01-437-1002.**

TYNE AND WEAR

AITKEN BROS & CO

35 High Bridge
Newcastle Upon Tyne.
Tel: 326729

Open: 9am-5.30pm (Sat 5pm) closed Wed.
Retail and Wholesale supplied.

S. WALES

CARDIGAN ELECTRONICS

Chancery Lane, Cardigan,
Tel: Cardigan (0239) 614483

Open: Mon-Sat 10am-5pm. Closed Wed.
Electronic components &
Acorn computer stockist.

WILTSHIRE

camlab electronics
27 Faringdon Rd. Swindon
Tel: (0793) 34917

Open: 6 days 9am-5.30pm
Specialists in loud speakers. Wide selection: 1¼"-18"

YORKSHIRE

ACE MAILTRONIX LTD.
3A Commercial Street,
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)
Retail and wholesale.

**PLEASE MENTION
ELECTRONICS TODAY
WHEN USING THESE
SHOPS!**

Please include my business details in the next available issue of Electronics Today International:

Business Name:

Address:

Tel. No.:

Open Hrs:

Contact (Office Use Only):

Post To: Electromart Computing Today, 145 Charing Cross Rd., London WC2H 0EE.



CLASSIFIEDS

ETI RATES

1-5 Insertions £10.00 per scc
6-11 Insertions £9.00 per scc
12+ Insertions £8.00 per scc
35p per word (min 15 words)
Box No. £2.50
Closing date 1st Friday in month preceding publication.

HE RATES

1-3 Insertions £6.00 per scc
4-11 Insertions £5.50 per scc
12+ Insertions £5.00 per scc
21p per word (min 15 words)
Box No. £2.00
Closing date 2nd Friday in month preceding publication.

Classified Advertisements must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO:- ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

RECHARGEABLE BATTERIES

PRIVATE OR TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. S.A.E. FOR LISTS. £1.45 for Booklet. "Nickel Cadmium Power" plus Catalogue. "New range of sealed lead now available". Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021-354 9764.

STOCK CLEARANCE Mixed resistor Packs: ¼W/¼W, Pre-formed, unused. 1 lb Pack (2500 plus) £2.50; 2 lb Pack £4.60; Exceeding 2 lbs £2.00 per lb. All inclusive VAT, P&P. LINWAY ELECTRONICS, 843 Uxbridge Road, Hayes End, Middx. UB4 8HZ. Tel: 01-573 3677.

PARAPHYSICS JOURNAL (Russian translations); Psychotronic Generators, Kirlianography, gravity lasers, telekinesis. Details: SAE 4 x 9". Paralab, Downton, Wilts.

CLOSE ENCOUNTERS GROUP Personal introductions and social events. Meet interesting, attractive people. Local, 051-931 2844 (24 hours).

BUILT TRANSMITTERS £2.90. Receive on FM. Range 150 yds. Refund Guarantee. (Unlicensable). P. Faherty, 37 College Dr., Ruislip.

BURGLAR alarm equipment. Ring Bradford (0274) 308920 for our catalogue, or call at our large showrooms opposite Odsal Stadium. C.W.A.S. Ltd.

MOS-FET AUDIO MODULES

Hitachi devices, Hitachi spec., glass boards, extruded heatsinks, tested, guaranteed 24 months.

120 watts/8 ohms; 120v/2A supply; £13.95.
240 watts/4 ohms; 120v/4A supply; £19.95.
400 watts/2 ohms; 120v/7A supply; £29.95.

Power supplies/pre-amps available. Post/packing 80p. Stamp for details. Quantity discount.

Audio-Tech., 8 Parsons Close, Church Crookham, Aldershot, Hants GU13 0HL. Tel: 02514 22303.

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

IONISER KIT (Mains Operated)

This negative ion generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions £12.50
A suitable case including front panel, neon switch, etc. £10.50

Price includes post & VAT. Barclaycard/Access welcome

T. POWELL

Advance Works, 44 Wallace Road, London N1 Tel: 01-226 1489
Hours: Mon-Fri 9-5 pm Sat 9-4.30 pm

GUITAR/P.A. MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50; 60 watt £44; 200 watt £68; 100 watt twin channel, sep. treble/bass per channel £65; 60 watt £52; 200 watt £78; 100 watt four channel, sep. treble/bass per channel, £75; 200 watt £98; slaves 100 watt £37; 200 watt £60; 250 watt £70; 500 watt £140; fuzz boxes, great sound £12; bass fuzz £12.90; overdrive fuzz with treble and bass boosters £28; 100 watt combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £100; twin channel £115; bass combo £118; speakers 15in. 100 watt £36; 12in. 100 watt £24; 60 watt £18; microphone Shure Unidyn B £28.

Send cheque/P.O. to:
WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield,
Cheshire. Tel: 061-308 2064.

DIPLOMA IN ELECTRONICS Full time courses in Electronic Engineering. Also courses leading to **CITY AND GUILDS** Examinations. Tel: **LONDON SCHOOL OF ELECTRONICS: 01-263 5938.**

WANTED: ELECTRONIC COMPONENTS and Test Equipment. Factories cleared. Good prices given. Q Services, 29 Lawford Crescent, Yateley, Camberley, Surrey. 0252 871048.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

T. & J. ELECTRONIC COMPONENTS - Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

600 RESISTORS

High quality Carbon Film 1/4W 5% E12 series
60 values 10 per value

£5 INCLUDING VAT P&P

COVE COMPONENTS

58 Southwood Rd., Cove,
Famborough, Hants GU14 0JJ
Mail Order only

CENTURION BURGLAR ALARM EQUIPMENT Send SAE for free list or a cheque/PO for **£5.95** for our special offer of a full sized decoy bell cover. To Centurion Dept ET1265, Wakefield Rd., Huddersfield W. Yorkshire. Access & Barclaycard Telephone orders on 0484-35527.

CIRCUIT DESIGN, Prototype construction, analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET, or Phone Bradford-on-Tone (082-346) 536.

COPPER CLAD BOARD double sided fibre glass. **10 sheets 12" x 8" £6.00. 5 sheets 12" x 8" £4.00.** Including P&P. Complete PCB service. Davron, 1 Bankside, off New Street, Chelmsford.

ANY SINGLE SERVICE SHEET £1/L.S.A.E. Largest stockists Service/Repair manuals. Named T.V. Repair data £6.50 (with circuits £8.50). S.A.E. pricelists, free publications, quotations. Auseti, 76 Churches Larkhall, Lanarkshire.

HAVEN HARDWARE (WINNER OF THE DAILY EXPRESS/PHILISHAVE BUSINESS AWARD). ZX KITS (S.A.E. for Built prices/details). PROGRAMMABLE GRAPHICS £19.95 (First ever for ZX80/81). Works with printer - no hidden bugs - edge connector not used. Repeating Keypad £3.45. Keyboard £17.50 (P&P £1.00). Edge connector £2.20. Inverse Video/I.O Port/Memory/Colour (Extended sheet available) P.O.A. 4 Asby Road, Asby, Workington, Cumbria.

TELETEXT, (Ceefax/Oracle) or Viewdata (Prestel) add-on adaptors for your existing television or microcomputer. Discount prices. Mail order. Bristol (0272) 502008 anytime.

SPARE PARTS For all digital watches. Batteries, crystals, displays etc. Send SAE for full list. Profords, Copnersdrive, Holmergreen, Bucks HP15 6SGD.

KEYBOARDS / CONSOLES / POWER SUPPLIES New fully encoded ASCII keyboards made by world's largest keyboard manufacturer. Slimline stabilised power supply 240V/120V input, 5 volt 1 amp output, 350-400 m.A. Keyboards from £47 to £55. Consoles £19. Power Supplies £12.50. GIVE AWAY PRICES FOR EXISTING STOCKISTS. Keytronic International 01-428 0111.

ROBOTS Specially developed robot interfaces for the robot hobbyist. Easily connected to your micro. Write for full details: Gleaves Robodynamics, 20 Hartington Road, off Smithdown Road, Liverpool 8, L8 0SG.

CABINET FITTINGS

Cabinet & Flightcase Fittings, fretcloths, covers, handles, castors, etc. Jacks & sockets. Cannons. Bulgins reverb trays. Emular compression drivers. AKG mics. Celestion speakers. ASS glassfibre horns. Send 30p postal order for illustrated catalogues to

ADAM HALL (ET SUPPLIES)
Unit B, Charlton Court, Granger Road,
Southend-on-Sea, Essex SS2 5BZ

GRUNDIG CASED PSU 0/25V 2A. Excellent working condition. Voltage current metered overload protection. £20 + £5. S.H.E. 5, St. Joseph's Park, Ballycruttell, Downpatrick BT30 7EN.

AMAZING ELECTRONICS PLANS. Lasers, Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue 95p - From Plancentre, 16 Mill Grove, Bilbrook, Codsall, Wolverhampton.

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS

■ THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS

■ UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET

■ PRECISION INSTRUMENT METAL CASED WEIGHT 20Z

■ MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture
Tested & fully guaranteed
Ex-stock delivery

£6.95 inc VAT
Post & Pack 60p

Ideal for the experimenter
COMPLETE WITH DATA

HENRY'S

404 EDGWARE ROAD, LONDON W2 1ED

CONSTRUCTING AN AUDIO MIXER?

To achieve a high quality finish you need commercially produced printed panels — sub-frames — main frames etc designed and manufactured specifically for this purpose.

PARTRIDGE ELECTRONICS

THE MIXER PEOPLE

56 Fleet Road, Benfleet,
Essex SS7 5JN, England
(Large SAE please)



A really compact high performance CCTV camera for only £130.00 plus VAT plus P/P, Total £152.95. Size 3"x3"x9". 240v operation. 1v p-p output. Lens extra.

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM,
MIDDLESEX TW1 4AD
Telephone 01-891 1923/01-891 1513
Telex 295093 CROFTN G

COMPUTER CONTROLLED SOUND IS HERE!

This unique device receives serial data from any computer, baud rate up to 4800, responds only to its own address code (preset by on-board d.i.l. switch) and is capable of attenuating any audio signal in 1.5db steps from 0db to infinity. Once the device has been enabled, all other devices will ignore the commands until a new address has been transmitted. These devices can be built into amplifiers, mixers etc, or anywhere computer control of audio signals is required. The kit comes complete with all parts, sockets etc, and is supplied with instructions for use. A 5V power supply is required. Up to 127 devices can be individually addressed on one loop. Order ref: MED01.

Price £69.50 + VAT P&P £1.50

Cheques, postal orders crossed and payable to:

MEDIATRONICS

3 Alnwick Drive, Hollins, Bury, Lancs
061-796 6410

L.C.D. DIGITAL METER MODULE

A versatile module which will enable you to construct an accurate digital multimeter, digital thermometer, and many other useful projects.

- * 0.5" high, 3 1/2 digit L.C.D.
- * F.S.D. + 199.9 mV, but may be expanded by external attenuators.
- * Decimal point link selectable or externally programmable
- * Metal film resistors and 20T cermet potentiometer for high stability
- * Accuracy $\pm 0.1\% \pm 1$ count
- * Input resistance — 100 M Ω (protected to 100v)
- * Supplied assembled and calibrated, with full technical information. (Not a kit.)

Send £17 to include P&P etc to:

CHANNEL ELECTRONICS

111 Harptree Drive,
Walderslade, Chatham, Kent

SMALL REED switches 10p. Reed relays 6v-12v DC 40p. Postage 25p. Grimsby Electronic Components, Lambert Road, Grimsby, South Humberside. Hundreds bargains at shop. SAE list.

PROXIMITY SENSORS infra red. 6 inch range 5 to 15v supply. Miniature design 6.5 x 5 x 2cm. Only £16.50. Leaflet. Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent, Staffs.

ADVERTISEMENT INDEX

A. D. Electronics	91	Happy Memories	72
Ambit Int.	58	Henry's Radio	91, 93
Amral Ltd.	93	ILP	24, 25
Audio Electronics	28, 65	L & B Electronics	38
Audio Video Services	91	Hy-Tek	40
Aura Sounds	39	L.E.M. Services	89
BICC Vero	46	Lightning Elec. Comp	92
Bi-Pak	16	Mawson Assoc	78
BK Electronics	46, 77	Maplin	100
Black Star	46	Magenta Electronics	88
BNRS	44	Memotech	9
Boss Industrial Mouldings	72	Midwich Computers	23
T. J. Brine	83	Namal Assoc.	90
Broadside Assoc.	8	OTC Australia	93
C.S.S.	92	Parndon Electronics	93
Chiltmead	71	Powertran	2, 99
Chordgate Ltd	28	Rapid Electronics	11
Clef Products	78	Pantechnic	89
Cambridge Kits	78	R.T.V.C.	57
Crimson Elektric	84	Relay a Quip	22
Crofton Electronics	78	Redditch Electronics	83
Delta-Tech.	84	Silica Shop	47
Display Electronics	34	Sinclair Research	6, 7
E.D.A. Sparkrite	35	Solidstate Security	92
Electronize Design	91	Swanley Electrical	72
Electrovalue	88	Technomatic	28, 29
Enfield Electronics	15	Tempus	85
Greenbank Electronics	63	TK Electronics	73
Greenweld	89	Watford Elec.	4, 5
Global Spec. Corp	13	West Hyde Develop.	78
Flight Electronics	18	Wilmslow Audio	83

PRECISION - by POWERTRAN

THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS

For more than eleven years Powertran have been designing and manufacturing the finest quality electronic kits. All of our now considerable range have featured in the electronics press and literally thousands have been bought and built by contractors in the UK and World-wide.

Our philosophy is always the same — we offer ingenuity and originality in the construction phase by using only top class designers. We offer machines with power, versatility and performance — capability fully equal to their factory built rivals. We offer only the highest quality materials and components throughout to ensure years of useful and reliable service, we offer clear comprehensive and easy to follow construction manuals to place our kits within the scope of the careful first time builder as well as the dedicated enthusiast.

Our hallmark of success lies in the number of our clients who have built our whole range — many assembling several units for others to use often on the professional music scene.

We believe in taking every care throughout — months spent checking and testing the design and development. Vigorous checking of every component, constant pre-despatch quality control, careful packaging... even door to door delivery by Securicor!

We are naturally very proud of our Transcendent range of synthesizers designed by Tim Orr and regularly featured in ETI. They represent the best in constructional interest and in musical performance.

TRANSCENDENT POLYSYNTH — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.
Complete kit **£275.00** plus VAT (single voice).
Extra voice (up to three more) **42.00** plus VAT.

TRANSCENDENT 2000 — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it... play it! You will know you have made the right choice.
Complete kit **£165.00** plus VAT.

EXPANDER — A new matching 4 voice expander to team up with your polysynth for even a greater range and capability.
Complete kit **£249.00** plus VAT.

1024 COMPOSER — Come right up to the minute with this new design. It will control your synthesiser with a sequence of up to 1024 notes — or an equal selection of shorter sequences. The Composer is mains powered with automatically charged battery to preserve your programme after switch-off.
Complete kit **£85.00** plus VAT.

TRANSCENDENT DPX — Offers a five octave keyboard with power to match. Two audio outputs (can be used simultaneously) to give harpsichord and piano/honkytonk or reed with strings/brass and both are fully polyphonic. Other features include switchable touch sensitivity and a chorus ensemble unit with strong/mild effect switching. An advanced design made simple with our clearly laid out instruction manual.
Complete kit **£295.00** plus VAT.

DEMONSTRATION TAPE — Demonstration tape now available of all three kits (30 minutes). **£2.00**



... Quite simply the best way to make music



WORLD LEADERS IN ELECTRONIC KITS.

PRICE STABILITY: Order with confidence irrespective of any price changes we will honour all prices in this advertisement until the end of the month following the month of publication of this issue. (Errors and VAT rate changes excluded).
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed. Cheques, Access, Barclaycard accepted.
SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.
SALES COUNTER: if you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m.-12 noon, 1-4.30p.m. Monday-Thursday.

T20 + 20 — Originally designed by Texas Engineers. This is a 20 watt amplifier with true Hi Fi performance at a minimal cost. New features include true Toroidal transformer, new wiring, single circuit board and improved presentation. An ideal beginners project. Complete kit **£29.50** plus VAT. Also T30 + 30 - 30 watt version complete kit **£34.50** plus VAT.

LINSLEY HOOD 75 DE LUXE — A 75 watt amplifier originally published in Hi-Fi News. Superb performance characteristics with less than .01% distortion. Modular construction with 14 interconnecting boards — virtually no wiring so assembly is easy as is subsequent checking and maintenance. Complete kit **£75.00** plus VAT.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM (0264) 64455.

Order by phone **(0264) 64455** 
Simply telephone us with your order and quote your Access or Barclaycard number.
40 page catalogue free — complete full details of all our kits.