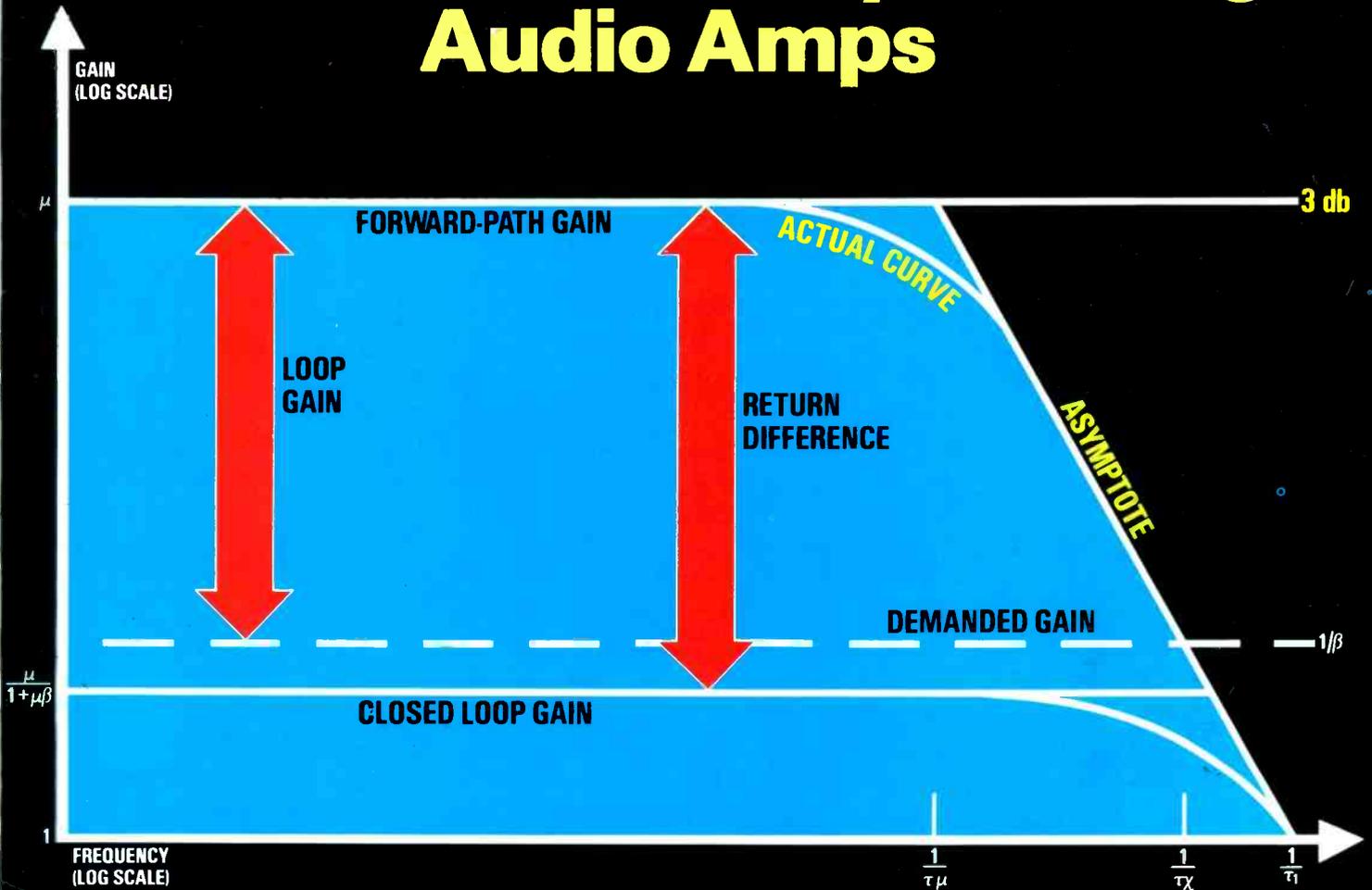


electronics today

INTERNATIONAL

APRIL 1983 85p

NDFL – A New Way To Design Audio Amps




PLUS

ZX81 music board

Teach your micro to tell the time

How to use voltage multipliers

Switched Mode PSUs

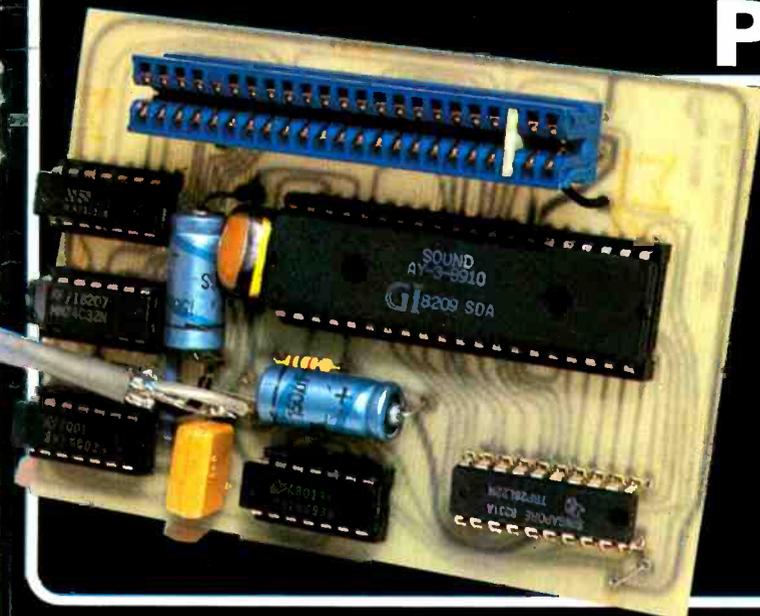

Star sounds ** Star quality **

Star features **

Free SECURICOR DELIVERY on all orders over £100 (UK mainland only) Add just £2.50 on lower price orders

BIG NEWS ABOUT OUR LATEST ADVANCES IN ROBOTICS SEE INSIDE BACK COVER

DJ90 Stereo Mixer — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! Complete kit **£97.50 + VAT**



TRANSCENDENT 2000 — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it — play it! You will know you have made the right choice.

Complete kit **£165.00 + VAT**



SALES COUNTER Collect your order from the factory. Open 9-2/1-4.30 Mon-Thurs. Easy parking, no waiting

Digital Delay Line — With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo &



vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB.

Compare with units costing over £1,000! Complete kit (400 mS delay)

£130 + VAT

Parts for extra 400 mS delay

£9.50 + VAT

KIT PRICES

Input channel	£ 9.90	Ease joint and wooden front	£27.50
Output channel	£ 3.50	Fair of mahogany end cheeks	£12.50
Auxiliary channel	£22.50	Power Supply and cabinet	£19.50
Blank Panel	£4.00		

All prices are VAT exclusive

TRANSCENDENT POLYSYNTH — A four octave polyphonic synthesizer with outstanding design characteristics and versatility and performance to match.

Complete kit **£275.00** plus VAT (single voice)
Extra voice (up to three more) **£42.00** plus VAT




Free Soldering Practise Kit with your first kit — useful tips, well illustrated.

Component packs for most kits are available. See our great free catalogue, full details of all our range

MPA 200 — a low price, high power 100W amplifier, its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first time builder. Complete kit **£45.90 + VAT**. Chrometone 5000 — a 5 channel lighting system complete enough for professional discos yet compact size for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single board design. Complete kit **£43.50 + VAT**

ET1 VOCODER — 11 channels each with independent level control, for maximum versatility and intelligibility. Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts. Complete kit **£175.00 + VAT**

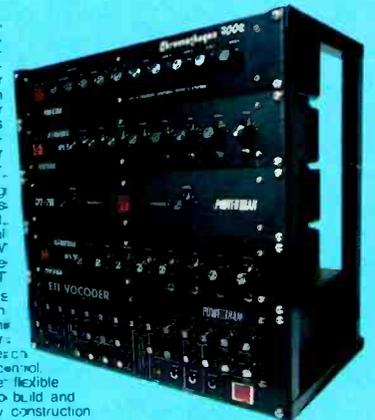SP2 200 twice the power with two of the reliable, durable and economic amps from the MPA 200, fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over) the standard of high price factory-built units! Complete kit **£64.90 + VAT**



WORLD LEADERS IN ELECTRONIC KIT DESIGN AND SUPPLY

PORTWAY INDUSTRIAL ESTATE

ANDOVER, HANTS SA10 3NM.

ORDER BY PHONE (0264) 64455

Simply request your chosen kit and quote your Access or Barclaycard Number.



electronics today

INTERNATIONAL

EDITORIAL AND ADVERTISEMENT OFFICE


145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.
Telex 8811896.

FEATURES

- DIGEST** 11
All that's new in electronics, at least for the last month or so.
- DESIGNER'S NOTEBOOK I** 23
You'll be surprised to learn what you can get out of a humble 1N4148 or two. Here we show how to generate 430 V from a mere 18 V.
- DESIGNER'S NOTEBOOK II** 63
Switched mode power supplies have for too long been a no-go area for non-experts. Here's an article to help change all that.
- CONFIGURATIONS** 78
If switched mode turns you off, Ian Sinclair is here to explain some of the basic facts of life of conventional PSUs.


FEVAs 37
Semiconductors are obsolete! Field Effect Voltage Amplifiers are sweeping them aside and buildings in Silicon Valley are raining executives.

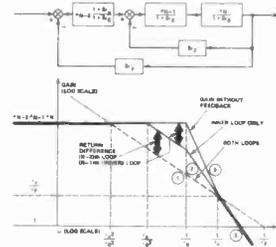NDFL 46
A new method of designing audio amplifiers that results in extremely low distortion from everyday components. Here's how it's done.




PROJECTS

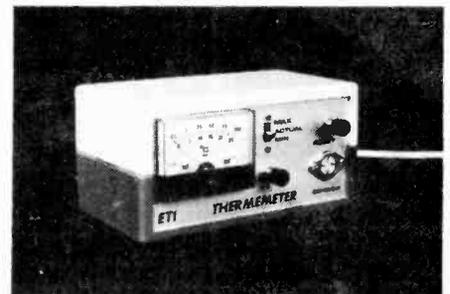- ZX81 MUSIC BOARD** 16
From the Beatles to Bach, all with your very own Sinclair.
- REAL TIME CLOCK** 31
For a long time here at ETI, we have been educating our readers about micros; now it's your turn to teach your micro to tell the time.
- ORGAN PART 3** 56
Design details of the rhythm unit for this world-beating music project.




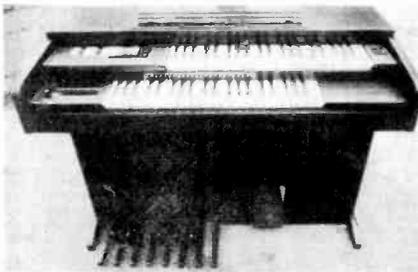- ETI THERMETER** 70
A thermometer that remembers the maximum and minimum readings.
- STAGE LIGHTING UNIT** 42
Overlay diagrams of the main memory and display boards.
- FOIL PATTERNS** 84



INFORMATION

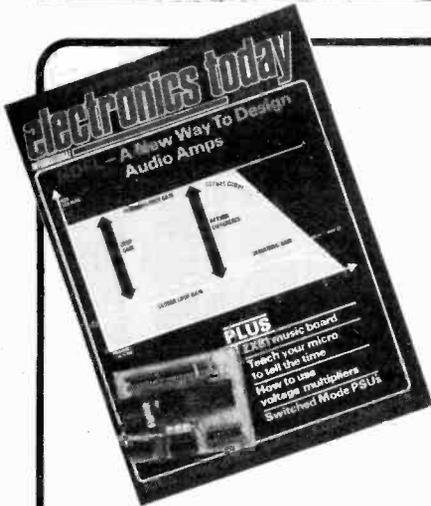- NEXT MONTH'S ETI** 7
- COMPUTER EXHIBITIONS** 21
- BOOK SERVICE** 53
- PCB SERVICE** 87



Dave Bradshaw: Editor
Peter Green: Deputy Editor
Phil Walker: Project Editor
Jerry Fowler: Technical Illustrator
Gary Price: Divisional Advertisement Manager
Ron Harris B.Sc: Managing Editor
T.J. Connell: Managing Director

PUBLISHED BY:
Argus Specialist Publications Ltd.,
145 Charing Cross Road, London WC2H 0EE.

DISTRIBUTED BY:
Argus Press Sales & Distribution Ltd.,
12-18 Paul Street, London EC2A 4JS
(British Isles)

PRINTED BY:
QB Limited, Colchester.

COVERS PRINTED BY:
Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS

AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsmann



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1983 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates UK £13.15 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

WATFORD ELECTRONICS

33/34 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
 MAIL ORDER, CALLERS WELCOME
 Tel. Watford (0923) 40588. Telex. 8956095

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER OR ACCESS. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT ENQUIRY WELCOME. P&P ADD 50p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. CUSTOMERS ONLY.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car Parking space available.

ELECTROLYTIC CAPACITORS: (Values in μF) 500V: 10uF 52p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7 8p; 10 12p; 15 22p; 22 33p; 33 15p; 47 12p; 68 20p; 100 20p; 220 20p; 50V: 68 20p; 100 17p; 220 15p; 40V: 6.8 15p; 22 33p; 33 12p; 33G: 47 32p; 100 45p; 220 50p; 25V: 1.5, 4.7, 10, 22, 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 1500 42p; 2200 50p; 3300 78p; 4700 82p; 16V: 47, 68, 100 8p; 125 12p; 330 16p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 4700 75p.

TAG-END CAPACITORS: 64V: 2200 130p; 3300 180p; 4700 205p; 50V: 2200 110p; 3300 154p; 40V: 4700 160p; 25V: 2200 80p; 3300 80p; 4000, 4700 100p; 1000 320p; 1500, 2000 350p.

POLYESTER CAPACITORS: Axial Lead Type
 400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 15p; 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 1uF 68p; 2u2 82p; 2u2 82p.
 100V: 10nF, 12n, 39n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 38p; 1uF 42p; 1u5 48p; 2u2 48p; 4u7 68p.
 1000V: 10nF, 10nF 30p; 15n 40p; 22n 33p; 33n 42p; 47n, 100n 42p.

POLYESTER RADIAL LEAD CAPACITORS: 250V
 10n, 15n, 22n, 27n 8p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 15p; 1u 23p; 1u5 40p; 2u2 46p.

TANTALUM BEAD CAPACITORS
 35V: 0.1uF, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 25p; 15V: 2.2, 3.3 12p; 4.7, 6.8, 10 15p; 39p, 22 33p; 33 47 40p; 10 75p; 10V: 1.5, 2.2, 28p; 33, 47 30p; 100 65p; 8V: 100 42p.

MYLAR FILM CAPACITORS
 100V: 1nF, 2, 4, 4nF, 10 8p; 15nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 8p; 50V: 470nF 12p.

CERAMIC CAPACITORS 50V:
 Range: 0.5pF to 10nF 4p, 15nF, 22nF, 33nF, 47nF 5p, 100nF/30V 7p, 200nF/6V 8p.

POLYSTYRENE CAPACITORS:
 10pF to 1nF 6p; 1.5nF to 12nF 10p.

SILVER MICA (Values in pF)
 2, 3, 4, 7, 6.8, 8, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180pF 16p each
 200, 220, 250, 270, 300, 330, 360, 390, 470, 800, 800, 820 21p each
 1000, 1200, 1800, 2200 30p each
 3300, 4700pF 40p each

MINIATURE TRIMMERS CAPACITORS
 2-8pF, 2-10pF 22p; 2-25pF, 5-60pF 30p; 10-80pF 35p.

RESISTORS Carbon Film Hi-Stab. 5%, miniature

RANGE	Val	1-99	100+
1W 202-4M7	E24	2p	1p
1W 202-4M7	E12	2p	1p
1W 202-4M7	E12	6p	4p
2% Metal Film	E24	6p	4p
1% Metal Film	E24	8p	4p

 100 + price applies to Resistors of each type not mixed.

REBISTORS Network S.I.L.
 7 Commoned: (8 pins) 1000, 6800, 1K 2k, 4K7, 10k, 47k 100k
 8 Commoned: (9 pins) 1500, 1800, 2700, 3300, 1K, 2k, 4k, 7k, 10k, 22k, 47k & 100k

DIODES
 AA119 15
 AA129 20
 AA130 15
 BA100 15
 BA101 15
 BA102 15
 BA929 15

SWITCHES

TOGGLE: 2A, 250V. SPST 34p DPDT 43p... SUB-MIN TOGGLE SPST on/off 50p...

DIL SWITCHES

(SPST) 4 way 70p; 6 way 85p; 8 way 90p; 10 way 145p. (SPDT) 4 way 180p...

VEROBOARD

0.1in clad plain 2 1/2 x 3 1/4 80p... 3 1/4 x 3 1/4 100p...

VO Board

180 350 374 Dip Strip

PROTO DECS

Veroblock 405p S-Dec 350p Eurobreadboard 520p...

IDC CONNECTORS

PCB Plug with latch 16 way 100p 150p 20 way 165p...

EURO CONNECTORS

DIN41617 31 way 170p DIN41612 2x32 A+B 275p...

PANEL METERS

FSD 80 x 46 x 35mm 0-50A 100p...

RELAYS

Miniature, enclosed, PCB mount. SINGLE POLE Changeover...

AMPHENOL PLUGS

IEE 24 Way Centronics Parallel 36 Way solder 530...

PUSHBUTTON 6A

with 10mm Button SPDT latching 99p DPDT latching 145p...

ROCKER

5A/250V SPST 28p 10A/250V SPDT 38p...

FERRIC CHLORIDE

1 lb bag Anhydrous 195p 50p P&P

COPPER CLAD BOARDS

Fibre Single Double S.R.B.P. class sided 9.5 x 8.5"

DIL SOCKETS

Low Wire Prof Wrap 8pin 8p 14pin 10p...

EDGE CONNECTORS

2 x 15 way 1.156 2 x 18 way 180p...

DIL PLUG (Header)

14pin 40p 99p 16pin 48p 106p...

RIBBON CABLE

price per foot 10 way 150 28p 16 way 250 40p...

CRYSTALS

32.768KHz 100 100KHz 235 200KHz 288 455KHz 370...

BUZZERS

miniature, solid-state 6V, 9V & 12V 70p

ETI PROJECTS

We stock most of the parts 24 inches 18p 36 inches 230p...

JUMPER LEADS

(Ribbon Cable Assembly) 14 pin 16 pin 24 pin 40 pin...

ANTEX SOLDERING IRON

C-15W 465p CX17W 475p CCN-15W 485p CX25W 510p...

SIL SOCKETS

0.1" pitch 20 way 85p

'D' CONNECTORS

miniature 9 way 15 way 25 way 37 way

ZIF DIL SOCKETS

28 pin 675p 40 pin 820p

TRANSFORMERS

3-0-3V; 6-0-6V; 9-0-9V; 12-0-12V; 15-0-15V @ 100mA...

VOLTAGE REGULATORS

1A TO220 Plastic Casing 5V 7805 40p 7905 45p...

SOLDERCON PINS

Ideal for making SIL or DIL Sockets 100 pins 75p 500 pins 350p

ALUM BOXES

3 x 2 1/2 x 1 1/2 85p 4 x 2 1/2 x 2 1/2 103p...

'SPECIAL OFFER'

25 way 'D' CONNECTOR (RS232) 495p

COMPUTER CORNER

MX80FT/3 EPSON PRINTER 10" & Friction feed, 9x9 matrix...

NEC PC8023BE-C PRINTER

Europe's most popular Printer 100CPS bi-directional, Logic seeking, 80 column...

MONITORS

MICROVITEC 1431. 14" Colour Monitor. RGB input (as used in BBC prog.) £250

WEROM FOR ACORN ATOM

A highly sophisticated Acorn Utility ROM. Plugs straight into floating point Atom's Utility Socket.

ULTIMUM

WATFORD'S own most versatile MICRO EXPANSION SYSTEM. Ideal for interfacing with APPLE, ATOM, DRAGON, PET, RESEARCH MACHINE, SPECTRUM, SUPERBOARD, VIDEO GENIE, ZX81, etc.

Table with columns for CMOS, 4075, 4076, 4077, 4999, 5000

OPTO ELECTRONICS

LEDs with Clips 10 TL1209 Red 14 TL1211 Gm 10 TL1212 Yel. 14 TL1220 2" Red 12 2" Green, Yellow or Amber 14 0.2" Bi colour 18 Red/Green 65 Green/Yellow 78 0.2" Tri colour 104 Red/Green/Yellow 86 Hi-Brightness Red 59 Flashing red 4099 0.2" red 56 Square LEDs, Red, Green, Yellow 30 Rectangular Stackable LEDs 450 Red, Green or Yell 18 Triangular LEDs 18 Green or yellow 22 LD271 Infra Red 46 SLD205 Detector 118 TL132 Infra Red 58 TL178 Detector 58 TL138 46 TL1100 80 BARGRAPH. Red 10 segments 225

ISOLATORS

IL74 55 ILD74 99 IL074 186 TL1111/2/4 90 TL1117 125 4N33 Photo Darlington 135 7 Segment Displays TL1312 3" CA 105 TL1313 3" CC 105 TL1321 5" CA 115 TL1322 5" CC 115 DL704 3" CC 99 DL707 3" CA 99 FND357 Red 120 FND500 115 3" Green CA 150 5" Green CA 215 3" x 1 Red CA 160 3" x 1 Red CA 160 DVM175 22 LCD31 Digits 495 LCD4 Digits 530 LCD6 Digits 625

NEONS

Rectangular, not fixing RS400C 255 Red, Amber, Green 30p REFLECTIVE Optical Switch type TIL139 170p SLOTTED Optical Switch similar to RS 180p

OPTO

LSA007 255 CP71 200 ORP12 86 ORP61 86 2N5777 46 BPX25 186 BPW21 295 BPX85 270

COMPUTER CORNER

MX80FT/3 EPSON PRINTER 10" & Friction feed, 9x9 matrix 80 column, Speed 80CPS, Bidirectional, Centronics Interface standard, Baud-rate 110-9600 (BBS232, Hi-Res, Bit Image graphics, Subscript & Superscript, Underlining facility plus 500 sheets of paper FREE £324 + £7 carr

NEC PC8023BE-C PRINTER

Europe's most popular Printer 100CPS bi-directional, Logic seeking, 80 column, 7x9 Dot matrix head, true descenders on lower case, Superscript & Subscript & Underlining facility. Proportional spacing, Forward & reverse line feed, Tractor or friction feed, Hi-res & block graphics. Auto underlining. Plus FREE 500 sheets of Paper. Price: Only £320 + £7 carr.

MONITORS

MICROVITEC 1431. 14" Colour Monitor. RGB input (as used in BBC prog.) £250 BMC BM1401 14" Colour Monitor, RGB input £165

WEROM FOR ACORN ATOM

A highly sophisticated Acorn Utility ROM. Plugs straight into floating point Atom's Utility Socket. Gives many unique BASIC Extensions: Hi-speed Tape Interface, 2 Key rollover Keyboard, Full disassembler, Memory dump modify, Machine code breakpoints: Basic error trapping; READ, DATA & RESTORE; Full BASIC Keyboard scanner (BBC like); Find line & delete; Auto line numbering; Plus: Chain, Cursor movement, Loopaborting; Easily extended further. Manual supplied. INTRODUCTORY OFFER ONLY £9.95

ULTIMUM

WATFORD'S own most versatile MICRO EXPANSION SYSTEM. Ideal for interfacing with APPLE, ATOM, DRAGON, PET, RESEARCH MACHINE, SPECTRUM, SUPERBOARD, VIDEO GENIE, ZX81, etc. Low Cost, High Spec. As published in Practical Electronics starting from November 1982. Send SAE for details.

BRADLEY MARSHALL LTD.

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

1983 CATALOGUE NOW AVAILABLE

SEND LARGE SAE + 75p TO ADDRESS BELOW

CRIMSON ELEKTRIK



PROFESSIONAL AMPLIFIER MODULES
NOW AVAILABLE OVER THE COUNTER!

NEW TELETEXT KIT NOW AVAILABLE
WITH PRESTEL ADAPTER (OPTIONAL EXTRA)
BASIC KIT £120

PRODUCTS ABOVE AS FEATURED IN RECENT
ELECTRONIC EXHIBITIONS

VELLEMAN KITS

HIGH PRECISION STOPWATCH	K615	£43.13
DIGITAL THERMOMETER	K2557	£26.57
INFRA RED DETECTION SYSTEM	K2549	£10.63
ELECTRIC DRILL SPEED CONTROL	K2577	£7.59

PLUS MANY MORE KITS IN STOCK - PLEASE CALL AT ADDRESS BELOW TO SEE DISPLAYS
(Prices incl. of VAT)

COMPUTER CHIPS NOW AVAILABLE

Z80A CPU	£3.20	2732 300NS	£7.50
Z80A CTC	£3.20	2764 300NS	£11.00
Z80A P10	£3.20		

PRICES EXCLUSIVE OF VAT

OFFICIAL TEXAS INSTRUMENT SUPPLIER

Sole Distribution **BRADLEY MARSHALL LTD.** 325 EDWARE ROAD. LONDON W21 BN. TEL: 01-723 4242

COMTECH ELECTRONICS

TRANSISTORS		LINEAR ICs		L.E.D.s		IC SOCKETS		THIS MONTH'S SPECIAL OFFER WITH ALL ORDERS OVER £8 - A FREE, YES FREE!	
8C107B	12p	BCY70	17p	555*	15p	3mm RED	7p	8 pin	7p
8C108C	12p	BCY71	18p	556*	43p	5mm RED	7p	14 pin	9p
8C109C	13p	BD115	50p	741	14p	3mm GREEN	10p	18 pin	12p
8C113/4	17p	BD131	47p	747CN*	58p	5mm GREEN	10p	20 pin	14p
8C115/6	19p	BD132	47p	748C	35p	3mm YELLOW	11p	22 pin*	16p
8C119*	32p	BD135	32p	CA3089	180p	5mm YELLOW	11p	24 pin*	18p
8C139*	30p	BD136	32p	CA3090AQ	330p	Rectangular	17p	28 pin*	22p
8C140	28p	BD137	30p	CA3189	280p	Red	13p	40 pin*	25p
8C141	28p	BD138	35p	ICM7556	150p	Green	17p		
8C142/3	27p	BD139*	35p	LF351*	45p	Yellow	17p		
8C160*	32p	BD140*	35p	LF353*	80p				
8C161	32p	BD204	90p	LF355*	85p				
8C169C*	9p	BD206*	75p	LF358*	85p				
8C171B	9p	BD222	60p	LM301A	110p				
8C172C	9p	BFX29	27p	LM311	24p				
8C173C	9p	BFX84	27p	LM324	40p				
8C177B	16p	BFX877	26p	LM339	47p				
8C178C	16p	BFX88*	23p	LM348	65p				
8C179C*	17p	BFY50	24p	LM358	50p				
8C182B	9p	BFY51	24p	LM380	68p				
8C183B/C	9p	BFY52	23p	LM382	115p				
8C184B/C	9p	BFY53	23p	LM386	125p				
8C212B	9p	BSY95A	23p	LM393	72p				
8C213B/C	9p	BU205	150p	LM711*	54p				
8C214B/C	9p	BU206*	170p	LM747	14p				
8C237B	9p	BU208	160p	LM748	35p				
8C238B/C	10p	MJE340	48p	LM1458	36p				
8C239B/C	10p	MJE520	65p	MC1455*	16p				
8C251	12p	MJE521	70p	MC1458*	33p				
8C257/B	16p	MJE2955	99p	MC1748	35p				
8C259	16p	MJE3055	68p	MC3302*	72p				
8C300/1	45p	MPSA05	20p	RC4558	44p				
8C302/3	45p	MPSA06	20p	SN76115	125p				
8C307A/B	10p	MPSA12	24p	SN76660	110p				
8C308B/C	10p	MPSA13	24p	TDA1024	130p				
8C309A/B	10p	MPSA55	24p	TDA2002*	95p				
8C327*	12p	MPSA56	25p	TDA2030	200p				
8C328	12p	TIP29A	29p						
8C337*	12p	TIP29C	34p						
8C338	12p	TIP30A	30p						
8C384	15p	TIP30C	36p						
8C413C	10p	TIP31A	33p						
8C414C	10p	TIP32A	33p						
8C415C	10p	TIP41A	42p						
8C416C	10p	TIP42A	45p						
8C477	25p	TIP3055	59p						
8C478*	25p	TIS43	40p						
8C479	25p	TIS44	45p						
8C546	10p	TIS90	24p						
8C547B	9p	TIS91	25p						
8C548B	9p	TIS92*	24p						
8C549C	9p	2N1613	30p						
8C556	10p	2N2218A	25p						
8C557B	9p	2N2219A	27p						
8C558B	9p	2N2221A	24p						
8C559C*	9p	2N2222*	18p						

Comtech Electronics

MAIL ORDERS

205 STURDEE ROAD,
LEICESTER LE2 9FY
Telephone: (0533) 779578

SUPER LOW PRICES!


electronics today

INTERNATIONAL

NEXT
MONTH

AUDIO BUYING GUIDE

The special audio buying guide will tell you which system to buy to suit your pocket. There will be good, sensible advice on all aspects of system choice and upgrading, but none of the 'buy a Lynotrio Cystemdek for £10,000 and listen to it through Granny's hearing aid until you've paid off the mortgage' variety. Incidentally, we've inserted the CENSORED stickers for your own good, to prevent you from going out and buying any gear until you've read the guide (and bought next month's ETI, of course).

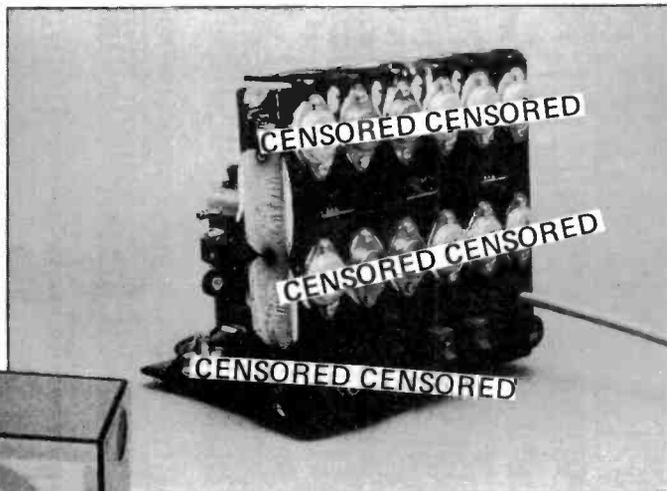

PROJECTS GALORE!

In case there are a few die-hard out there who still want to build their own gear (Heaven forbid!), we'll be including the odd project or two.....

- An entirely new type of power amp using NDFL techniques
- A Balanced Input Preamplifier to overcome noise problems on long signal cable runs
- A Noise Reduction Unit with an excellent specification — this must be amongst the most requested of all projects
- A Power Supply that can be used as a stand-alone unit, or to upgrade a good amplifier to the dizzy heights of super-fi
- The PseudoROM, a bit (well, 65536 of 'em to be precise) that looks like ROM until you move the switch..... very useful for operating system development, which is exactly why we built one.

ALL IN NEXT MONTH'S ETI
ON SALE ON APRIL 1st (HONEST!)

DON'T MISS OUT -- ORDER YOUR COPY NOW

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

CRICKLEWOOD — STOCKING PARTS OTHER STORES CANNOT REACH!

Items not fully covered on this list include: OPTO 7 seg LEDs, LCDs bezelled LEDs, Lamps, Lampholders, FUSES: 20mm 1 1/2 inch, slow or quick blow. Fuseholders. CONNECTORS: DIL DIN Phono, 1mm, 2mm, 4mm. BULGIN USA. I.E.C. KNOBES: Plastic, Aluminium, Anodised, Collet, Point. SWITCHES: Toggle, Biased, Rocker, Rotary, Slide, Dil, Push. METERS: LCD, Analogue. Test and Panel. TOOLS: Pliers, Cutters, Strippers, Trimmers, Cable Cutters. And much, much more. All in stock items (that's 95%) posted same day. OFFICIAL ORDERS FROM SCHOOLS, GOVT DEPTS ETC WELCOME. OVERSEAS ORDERS WELCOME (CWO + ADEQUATE POSTAGE).

★ THE LAZY WAY Phone your order through on Access, Barclaycard, Visa or American Express for immediate service, no extra charge, no minimum order.
★ THE TRADITIONAL WAY Send cheque, PO or credit card number. Cash not encouraged but accepted (no coins please). All in stock items shipped same day.
★ THE IDEAL WAY Call in and collect. We are on the main Edgware Rd (A5) just 1 1/2 miles from Staples Corner and approx 3 miles from Marble Arch.
VAT please add VAT at the current rate to all orders except books. VAT not chargeable abroad.
POST, PACKING & INSURANCE Standard small order charge is 70p (more for heavier goods). Export orders minimum £1.50.

CRICKLEWOOD ELECTRONICS LTD., 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET.
TEL: 01-462 0161, Telex 914977

TIS62	44p	1N1192	1.75	6 amp type
TIS64	67p	1N1194	1.65	LM100A-6 AMP
TIS67	80p	1N1194A	1.80	State value in
TIS68A	82p	1N1198A	2.41	amps and we will
TIS69	23p	1N1198B	2.86	supply nearest
TIS91	30p	1N1201A	97p	to above
TIS92	30p	1N1204A	1.00	20mm slow 17p
TIS93	54p	1N1206	1.20	20mm quick 10p
TIS94	54p	1N1207	1.20	1.25" slow 17p
1N1010M	85p	1N3065	45p	1.25" quick 10p
VN46AF	85p	1N3066	78p	
VN46F	85p	1N3067	78p	
ZTX107	10p	1N3492	1.88	
ZTX108	10p	1N3493	2.20	
ZTX109	10p	1N3620	3.30	
ZTX300	13p	1N3604	45p	
ZTX301	15p	1N3786	3.00	
ZTX302	15p	1N3787	3.00	
ZTX303	23p	1N3788R	4.50	
ZTX304	15p	1N4001	4.00	
ZTX310	15p	1N4002	4.1p	
ZTX311	15p	1N4003	1.80	
ZTX312	15p	1N4004	5.1p	
ZTX313	35p	1N4005	6.1p	
ZTX314	24p	1N4006	6.1p	
ZTX320	25p	1N4007	7.5p	
ZTX330	25p	1N4008	20p	
ZTX341	24p	1N4148	18p	
ZTX500	14p	1N4150	18p	
ZTX501	14p	1N4151	18p	
ZTX502	14p	1N4152	22p	
ZTX503	17p	1N5172	30p	
ZTX504	24p	1N5176	34p	
ZTX505	24p	1N5177	34p	
ZTX520	25p	1N5401	13p	
ZTX531	25p	1N5402	14p	
ZTX850	26p	1N5403	16p	
ZTX850	26p	1N5404	16p	
ZTX850	26p	1N5405	17p	
ZTX850	26p	1N5406	18p	
ZTX850	26p	1N5488	100p	

LM100C	4.25	MC3340	1.45	TD100A	2.87	74159	75p	74LS280	95p	74C164	1.16	4553	2.35	Z80ALMA	10 1/2	10 00MHz	1.75
LM111C	4.00	NE531N	1.36	TD100S	3.94	74160	40p	74LS283	40p	74C165	2.00	4554	2.00	Z80AHO	2.80	10 00MHz	1.98
LM114	6.75	NE543N	2.50	TD101A	2.25	74161	40p	74LS289	4.70	74C173	40p	4556	3.00	ZM425E8	3.30	20 00MHz	1.88
LM137K	11.52	NE540	4.95	TD102A	4.25	74162	40p	74LS290	4.00	74C174	40p	4557	3.00	ZM42E8B	3.30	27 848MHz	2.20
LM301A	25p	NE544N	1.80	TD102A	2.19	74163	40p	74LS293	4.00	74C190	2.00	4558	1.48	ZM427E	5.80	48 000MHz	1.70
LM305A	2.90	NE555	1.60	TD103A	2.90	74164	40p	74LS295	7.5p	74C192	70p	4559	1.80	ZM428E	4.05	100 00MHz	5.50
LM305H	95p	NE558	1.89	TD2030	2.85	74165	40p	74LS298	7.5p	74C193	70p	4560	1.80				
LM307H	1.00	NE559	3.25	TD2522	4.20	74170	12p	74LS299	1.55	74C194	70p	4561	1.80				
LM308A	3.15	NE565	1.18	TD2523	3.30	74171	2.50	74LS324	1.45	74C200	10 00	4562	1.80				
LM308AH	2.18	NE566	1.49	TD2540	4.10	74173	48p	74LS325	2.95	74C221	1.20	1860A	7.00				
LM308B	2.15	NE567	1.37	TD2560	4.10	74175	54p	74LS326	2.80	74C221	1.20	2602A	11.00				
LM309	2.80	NE571	3.75	TD2581	3.75	74176	39p	74LS327	2.00	74C222	1.20	8502	3.24				
LM310H	1.95	NE575	1.25	TD2590	5.20	74178	80p	74LS332	1.55	74C223	1.20	8503	3.00				
LM311H	1.00	EM533A	7.20	TD2591	4.73	74181	1.15	74LS333	1.55	74C224	1.20	8504	3.00				
LM311H	70p	EM533A	7.20	TD2591	4.73	74181	1.15	74LS334	1.55	74C225	1.20	8505	3.00				
LM317K	2.80	SL450	12.75	TD2611A	3.50	74184	90p	74LS336	2.7p	74C226	1.20	8506	3.00				
LM317K	2.80	SL450	12.75	TD2611A	3.50	74184	90p	74LS337	2.7p	74C227	1.20	8507	3.00				
LM317H	1.50	RC4194	3.95	TD2640	3.84	74185	48p	74LS338	2.7p	74C228	1.20	8508	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS339	2.7p	74C229	1.20	8509	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS340	2.7p	74C230	1.20	8510	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS341	2.7p	74C231	1.20	8511	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS342	2.7p	74C232	1.20	8512	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS343	2.7p	74C233	1.20	8513	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS344	2.7p	74C234	1.20	8514	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS345	2.7p	74C235	1.20	8515	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS346	2.7p	74C236	1.20	8516	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS347	2.7p	74C237	1.20	8517	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS348	2.7p	74C238	1.20	8518	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS349	2.7p	74C239	1.20	8519	3.00				
LM318H	2.40	RC4195	2.95	TD2640	3.84	74186	48p	74LS350	2.7p								

DIGEST

£1000 Reward

Well, that's got your attention — now here's the problem. It would seem that some light-fingered gentlemen have been at work in deepest Surrey. Aura Sounds Ltd, sole importer of Wersi organs, pianos and accessories in the UK, suffered a burglary three days ago (that's Saturday 5th February as I write this) and several expensive items were stolen. Amongst the lost instruments was a computer-controlled rhythm unit, known in the trade as a Wersimatic CX 1. The director of Aura, Mr. Arthur Griffiths says "The thief couldn't have stolen a more easily traceable item! This CX 1 is the only model of its type in the UK at the moment. Indeed, it is virtually a prototype and there are only 10 in existence world-wide. It is absolutely essential that we retrieve this instrument, and we are offering a reward for its recovery. Information leading to the return of the CX 1 and apprehension of the thief (thieves) concerned will carry with it a £1000 reward". Anyone who thinks they have in-




A Safe Bet

Here's another attention-getter for this page—can you stand the excitement? Nike Clark (for it is she) is unique, with a lot to offer, says the British Safety Council, and that's why they've chosen her to help promote their Action Days. These will be staged to assist industry avoid the disruption of accidents and unnecessary losses by bringing all the latest relevant information, products, expertise and techniques within easy, cost-effective reach of companies all over the country.

The dates are Leeds (13/14 April), Cardiff (22/23 June), Plymouth (14/15 September), Middlesbrough (12/13 October) and London (20 May). Anyone wishing some Action should contact Faye Rothwell, British Safety Council, 62/64 Chancellor's Road, London W6 9RS (telephone 01-741 1231 ext. 293).

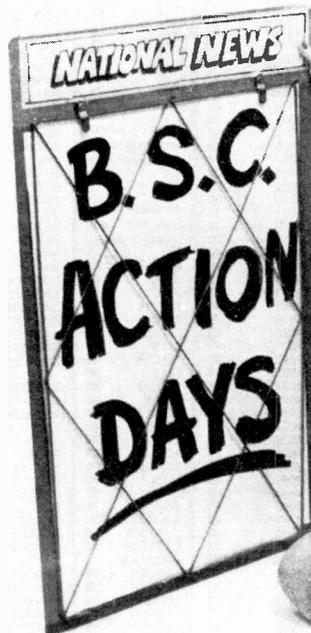Information should contact Mr. Griffiths at Aura Sounds Ltd, Royal Oak Centre, Brighton Road, Purley, Surrey (telephone 01-668 9733).



MegaMania Mania

Having reviewed a fair number of games for the January ETI, your intrepid Star Warrior/Deputy Editor had come to the conclusion that high-resolution machines like the Intellivision and Atari 400 rather left the Atari VCS out in the cold. A new game from ActiVision has changed all that, however, because it's so good it's almost worth buying a VCS just for this one cartridge. ActiVision have proved that it's the game design that counts, not the screen resolution. Using only the simplest of shapes they've produced a challenging and absorbing 'space shootout', one which led to the extraordinary sight of eight ASP employees crowded into the ETI workshop one night queuing to play. This is unprecedented, because said employees would normally be quaffing draughts of ale in the local tavern after work.

What does MegaMania involve? Each attack cycle consists of eight waves of Invader-type aliens with loony shapes — these are hamburgers, cookies, bugs, radial tyres, diamonds, steam irons, bow ties (!) and dice (personally I think they look more like lumps of cheese). There are no bases to hide under, which is tricky because some of the baddies move from left to right, others move down the screen, and some do both. The screen wraps round from top to bottom and left to right so if you miss any they come back for another shot, but it's very easy to get trapped unless you can figure out the patterns and the best tactics for each

wave. The patterns of movement are, naturally, different for every cycle. Chris 'Fingers' Palmer of Personal Computing Today holds the office record at present with 216, 530 on option 1, difficulty b, a pretty stiff target to beat. MegaMania costs £29.95 and, even though it's only February, gets our vote as game of the year. Go out and buy one. Now.

Microtutor

We have received a letter from Tangerine Computer Systems Ltd, designers of the Microtutor project that was featured in the August, September and October issues of ETI last year. In it they state that they have had many problems with it, paramount being their inability to obtain the necessary components. As a result of this they have taken the decision to withdraw the project from the market. Both we and Tangerine would like to offer our apologies to any readers who may have been inconvenienced by the situation.

Cross Words

Oops! we forgot to give the winners of Crossword No. 5. They were John R. Baldwin of Dorset, A. R. Moss of Hampshire and Stuart McWilliam of West Yorks. Answers:

ACROSS: 1 Chassis. 4 All Pass. 10 Ambient. 11 Dry Cell. 12 PNP. 16 Mid Range. 17 Nanovolt. 18 SME. 19 Monitors. 21 Low Power. 23 Function. 26 Anodised. 29 Owl. 30 Resonant. 32 Betatron. 34 Hum. 36 As-able. 38 Voltaic. 39 P C Board. 40 Housing. DOWN: 2 Hybrid. 3 ITT. 5 LCD. 6 Stereo. 7 Maximum. 8 Pan. 9 Flutter. 12 Press. 13 Panel. 14 Watt. 15 Loop. 20 NPN. 22 WPS. 23 Faraday. 24 Tone. 25 Notch. 26 Album. 27 Dial. 28 DIN Jack. 31 Static. 33 RF Gain. 35 USB. 37 EOR. 38 VCO.

Disc-continued

We continue the mini-floppy disc saga; Sony announced today (January 20th) that 13 leading floppy industry companies, composed of the following disc drive and media manufacturers, have agreed to support a mutually compatible 3.5" floppy disc format: Atari, Athana, BASF Systems Corporation, Fuji Photo Film Co. Ltd, Memorex Corporation, Media System Technology, Inc, Shugart Associates, Sony Corporation, TDK, 3M, Verbatim Corporation, Wabash Datatech, Inc and Xidex. "The major technological issues relating to compatibility have been settled," Sony said. "The compatibility will strengthen the

position of the 3.5" disk with a hard covering as the leading format for a microfloppy industry, as well as reduce costs and expand the potential market through greater second sourcing opportunities." The media itself holds up to 1 megabyte in a double-sided, 135 track per inch version. The media's hard covering protects the user's data, while the precise centring and proven 135 tracks per inch technology contribute to greater reliability by reducing the potential for positioning errors. Once the remaining specifications have been settled, Sony will grant non-exclusive manufacturing licenses to any qualified media manufacturer in order to promote widespread adoption of the standard by manufacturers.

ELECTROVALUE

- 24 HOUR NORMAL DESPATCH TIME
- ESTABLISHED 1965
- ALL GOODS GUARANTEED BRAND NEW AND TO SPECIFICATION
- APPOINTED SIEMENS DISTRIBUTORS

CAPACITORS

Polyethylene, Siemens
5% Tolerance 160V
5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p;
47, 56, 68, 82, 100, 120, 150, 180, 220,
270, 330, 390, 470, 560, 680, 820pF, 1n,
1n2, 1n5, 1n8, 2n2, 2n7, 3n3, 3n9, 4n7,
10p; 5n6, 6n8, 8n2, 10, 13p
Ceramic Very small 1.8, 2.2, 2.7 etc, up to
1n 5p each. 1n5, 2n2, 3n3, 4n7, 6n8, 8p;
10n, 22n, 33n, 47p, 7p, 100n, 6p
Polyester, Siemens Layer Type 7.5mm
lead spacing 100V
1n, 1n5, 2n2, 3n3 8p; 4n7, 6n8, 8n2, 10n
12n, 15n, 18n, 22n, 33n, 47n, 7p 56n, 68n,
7p, 82n, 100n, 9p 120n, 150n, 15p; 180n,
220n, 12p; 270n, 330n, 330n, 390n, 470n,
15p; 560n, 680n, 24p; 10mm spacing 1uF
25p; 15mm spacing 2u2 35p; 22.5mm
spacing 1uF 400V 50p; 3.3uF 100V 69p; in
depth stocks.

DIGITAL & ANALOGUE I.C. SECTION

COMPUTER		74LS	
74LS00	11	74LS161	36
74LS02	11	74LS163	36
74LS04	12	74LS164	30
74LS05	12	74LS165	60
74LS08	12	74LS166	60
74LS10	12	74LS167	55
74LS11	12	74LS174	45
74LS12	12	74LS175	40
74LS13	12	74LS191	36
74LS14	12	74LS193	40
74LS15	12	74LS195	39
74LS16	26	74LS196	48
74LS20	13	74LS197	60
74LS30	12	74LS221	48
74LS32	13	74LS240	55
74LS33	13	74LS241	55
74LS37	14	74LS242	55
74LS38	14	74LS243	55
74LS42	28	74LS244	55
74LS47	36	74LS245	70
74LS51	14	74LS251	30
74LS53	18	74LS253	30
74LS54	16	74LS259	55
74LS56	15	74LS262	70
74LS57	15	74LS273	55
74LS58	40	74LS279	30
74LS59	22	74LS299	150
74LS60	30	74LS367	30
74LS63	30	74LS368	28
74LS67	20	74LS370	80
74LS72	34	74LS373	80
74LS74	24	74LS374	80
74LS75	25	74LS375	45
74LS76	25	74LS376	45
74LS77	25	74LS377	45
74LS78	25	74LS378	45
74LS79	25	74LS379	45
74LS80	25	74LS380	45
74LS81	25	74LS381	45
74LS82	25	74LS382	45
74LS83	25	74LS383	45
74LS84	25	74LS384	45
74LS85	25	74LS385	45
74LS86	25	74LS386	45
74LS87	25	74LS387	45
74LS88	25	74LS388	45
74LS89	25	74LS389	45
74LS90	25	74LS390	45
74LS91	25	74LS391	45
74LS92	25	74LS392	45
74LS93	25	74LS393	45
74LS94	25	74LS394	45
74LS95	25	74LS395	45
74LS96	25	74LS396	45
74LS97	25	74LS397	45
74LS98	25	74LS398	45
74LS99	25	74LS399	45

ANALOGUE	
74157	30
74158	30
74159	30
74160	30
74161	30
74162	30
74163	30
74164	30
74165	30
74166	30
74167	30
74168	30
74169	30
74170	30
74171	30
74172	30
74173	30
74174	30
74175	30
74176	30
74177	30
74178	30
74179	30
74180	30
74181	30
74182	30
74183	30
74184	30
74185	30
74186	30
74187	30
74188	30
74189	30
74190	30
74191	30
74192	30
74193	30
74194	30
74195	30
74196	30
74197	30
74198	30
74199	30
74200	30

CRYSTALS

(in MHz)	4.433	128
0.032768	4.915	157
0.100000	5.000	157
1.000	5.026	128
1.8432	6.000	157
2.000	6.144	157
2.4576	6.5536	128
3.2768	8.000	188
3.579	8.867	128
4.000	10.000	167
4.194	10.432	188

ZENNER DIODES

400mV/2.7-3.5V 7p; 1.3W/303-100V
15p; 20W/7.5-75V £1.88

REGULATORS

7805, 7806, 7808, 7812, 7815, 7818,
7824 each 40p; 78L05, 78L12, 78L15,
78L24 each 32p; 7905, 7906, 7908,
7912, 7915, 7918, 7924, 79L05,
79L12, 79L15, 79L24 each 50p.

CONNECTORS

DIN AUDIO	PARALLEL TYPE
Pin 2	16 way 1.30
Pin 3	8p 8p 1.30
Pin 4	16 way 1.25 1.45
Pin 5	17p 14p 1.50 1.70
Pin 6	17p 11p 3.4 way 1.85 1.95
Pin 7	18p 8p 4.0 way 1.85 2.10
Pin 8	20p 20p 2.00 2.00
Pin 9	20p 30p 2.00 2.00

BOXES

High quality Black ABS plastic or die-cast plain or stove grey.

L	W	D	Abs	Plain	Stove Gr
50	50	25	5001F	90p	123p
100	60	25	2002	86p	5002 154p
113	63	31	2003	109p	5003 143p
121	66	40	2004	115p	5004 210p
152	82	50	2005	134p	5005 288p
192	113	61	2006	236p	5006 314p

VERO RANGE plastic boxes

L	W	D	54p	Case	70p	84p	108p	£7.68	
72	47	25	21024	54p	134	90	44	21089	£7.68
120	50	35	21390	87p	224	140	64	21090	£11.62
180	110	55	21391	100p	302	170	84	21091	£15.78

VEROBX CASES

to give a completely professional finish to a much valued project.

L	W	H	TYPE	PRICE
205	140	40	21034	£4.82
205	140	75	21035	£5.22
205	140	210	21036	£8.54
180	120	39	21037	£4.11
180	120	65	21038	£4.40
180	120	90	21039	£4.69
155	85	39	21040	£3.31
155	85	60	21041	£3.30
155	85	80	21042	£4.30
125	65	30	21047	£2.48
125	65	39	21048	£3.16
125	65	50	21049	£3.58

SEMICONDUCTORS

1N914	03	2N3819	22	AA118	9
1N914B	10	2N3820	40	AA119	32
1N916	02n	3823	05	AC126	25
1N4007	06	2N3904	15	AC127	25
1N4148	03	2N3906	16	AC128	25
1N5402	14	2N4036	46	AC151R	56
1N5407	18	2N4058-62	09	AC153K	20
2N697	23	2N4124	28	AC176	25
2N706	18	2N4126	25	AC177	37
2N930	20	2N4284	30	AC178	120
2N1132	23	2N4286	18	AC179	99
2N1302	110	2N4289	23	AC220	90
2N1303	62	2N4291	24	AC221	96
2N1305	62	2N4292	21	AC229	327n
2N1306	62	2N4591	62	AC241	10
2N1307	67	2N5192	110	AD136	150
2N1308	147	2N5195	106	AD149	88
2N1309	99	2N5457	32	AD181	35
2N1599	100	2N5459	36	AD182	35
2N1711	25	2N6050	380	AF114	37
2N1893	32	2N6057	375	AF116	54
2N2218A	31	6F40	162	AF117	64
2N2219A	26	16F40	166	AF124 AF125 37	37
2N2222A	25	40F40	225	AF126 37	37
2N2389A	21	40361DIS	21	AF127 37	37
2N2484	46	40362	66	AF200	10
2N2904	26	40406	71	AF239	114
2N2904A	26	40408	96	AF279	30
2N2905A	26	40412	108	AFY12	20M
2N3053	23	40430	100	AFY18	327n
2N3054	58	40595	123	AFY18B	310n
2N3055	48	40636	147	AFY42	481n
2N3405	64	40673	146	AU106	240
2N3663	16	A9903	18	AU111	1use
2N3702-11	06	AA113	13	AU116	1use
2N3717	180	AA116	9	AU122	10.95
2N3794	21	AA117	13	BO140	25n

METERS

Large range of types in stock; also probes, leads, accessories, etc.

PANEL MOUNTING in 50, 100, 500mA; 1, 5, 10, 50, 100, 500mA; 1A either model.

MULTIMETERS

NH56A 20kΩ/V AC/DC/RES/DB in 23 ranges: 130 x 85 x 37mm £11.20N

YN360TR 20kΩ/V AC/DC/RES/DB/Transistor test: in 21 ranges: 145 x 95 x 45mm £16.45N

BC214	08	BFR39-41	23	E1210	76
BC214L	08	BFR79-81	23	E2506	154
BC238C	09	BF765	119	ES383	23
BC239C	09	BF766	182	MJ2955	90
BC2588B	08	BFX29	24	MJE340	55
BC267B	16	BFX84	24	MJE2955	95
BC300	32	BFX85	24	MJE3055	70
BC301	24	BFX87	28	MPE102	40
BC303	30	BFX88	26	MPS631	40
BC327	15	BFY50	24	MPS6534	42
BC328	11	BFY51	24	MPSA12	36
BC337	14	BFY52	24	MPSA63	38
BC338	11	BFY90	143	NSA20655	81
BC413	09	BR34	70	OA47	12
BC414	09	BR41	110	OA90	10
BC415	24	BRV39	46	OA91	10
BC456	10	BSX20	22	OA95	DIS
BC457	38	BSX26	22	OA202	14
BC458	09	BSX63	789n	OC28	75
BC459	09	BT106	147	OC29	75
BC460	09	BT108	100	OC35	75
BC461	09	BT109	170	OC36	90
BC462	09	BU124	86	OC84	25
BC463	09	BU208	180	PMTA2	373
BC464	09	BUX26	360N	PN70	10
BC465	09	BUX28	546	PN72	05
BC466	09	BUX81	744	QA06L1	104
BC467	09	BUX85	249	QA010L7	115
BC468	09	BUZ10A	478	QA025H	450
BC469	157	BUZ15	12.27	TZ700D	189
BC470	18	BUZ20	623	TZ800D	104
BC471	18	BUZ23	787	TAC3-400	100
BC472	18	BUZ24	12.60	TAC209-400	95
BC473	10	BUZ32	825	TAC209-600	95
BC474	10	BUZ33	844		
BC475	45n	BUZ41A	637	TIC106B	48
BC476	26	BUZ44A	8.67	TIC108M	55
BC477	27	BUZ45	9.67	TIC126D	64
BC478	30	BUZ46	16.94	TIC208D	64
BC479	30	BUZ47	16.94	TIC226D	64
BC480	09	BUZ50A	763	TIC236D	64
BC481	09	BUZ54A	21.43	TIC246D	105
BC482	09	BUZ58	739	TIP31A	36
BC483	09	BUZ60	84	TIP32A	36
BC484	09	BUZ63	11.29	TIP35A	55
BC485	09	BUZ64	11.96	TIP36A	55
BC486	09	BUZ68A	12.75	TIP37A	55
BC487	09	BUZ71	15.4	TIP42C	60
BC488	09	BUZ72	15.4	TIP42D	60
BC489	09	BUZ73	15.4	TIP42E	60

Quartz Into Pint Pot?

The world's first analogue quartz chronograph wrist-watch has been introduced by Seiko. The biggest and most experienced watch house worldwide, Seiko is renowned for its innovative achievements having many world firsts to its credit, including the recent introduction of the first television watch (see ETI Digest, September 82). Until now quartz chronographs with digital readouts have been commonplace but the introduction of the Seiko Analogue Quartz Chronograph is the result of many years of research and development. It is an achievement which is thought to be far in advance of any other watch house. Four independent micro-step motors have been successfully miniaturized into a small wrist-watch module and it is this fact that has made possible the development of this new analogue quartz chronograph. Micro technology has also played an important factor in terms of design; the watch itself is much thinner than conventional chronographs with mechanical movements.

Other impressive technical features of this new Seiko model include a chronograph with a 5/100th second capability, a split time measurement facility, the ability to record two consecutive finishes, a tachymeter, and a remaining time indicator as well as a tally counter. All three chronograph hands go round once for demonstration purposes, by simply depressing the buttons. Four different models, one of which is a Sports 100 watch (water resistant to 100 metres), will be available in the shops in May. Each model has a stainless steel case and bracelet and the range of watches offers a choice of different colour dials and prices vary between £110.00 and £140.00 each retail.



Shorts

● Anyone who fancies going back to school this summer is invited to attend the 1983 Electronic Systems Summer School at the University of Essex. Two courses are offered, 'Feedback and Communication Systems' and 'Digital and Computer Systems'. The school will run from Sunday evening, 10th July to Friday afternoon, 15th July, and teachers wishing to obtain further details of the courses should contact Mrs J. Mead, Dept. of Electrical Engineering Science, University of Essex, Colchester (telephone 0206 862286 ext. 2358).

● Or perhaps you want to find out more about computer based training, in which case you should contact Sue Punch of Mills and Allen Communications Ltd, 1-4 Langley Court, Long Acre, London WC2E 9JY (telephone 01-240 1307). They're holding a one-day course on CBT techniques and uses, followed by a two-day workshop on CBT and practical design. Dates are 23rd, 24th and 25th of March and the venue is in Central London.

● Can't imagine what's come

over Motorola's PR people: their new development system based on the MC6809 processor, XDOS operating system and BASIC-M compiler has been named the EXORset 100. Nought out of 10 for good taste, gentlemen...

● As usual, we've received word of a number of catalogues this month: first off is one from Wavetek Electronics, the test and measurement equipment manufacturers. New products include a VHF frequency synthesiser, a 3.7-7.6 GHz microwave signal generator, and a cross channel spectrum analyser. Free copies of the 210-page catalogue are available from Wavetek's new sales and service office at Tag Lane, Hare Hatch, Reading, Berks. RG10 9LT (telephone 073522 2124).

● OK Industries UK Ltd have produced the second one; it's a new 16-page full colour brochure describing the range of Elrack terminal enclosures, lab racks and computer desks. Lots of the stuff is 19" rack-sized and, although constructed to industrial standards, most products in the range are suitable for the electronics amateur. OK Industries are at Dutton Lane, Eastleigh, Hants SO5 4AA (telephone 0703 610944).

● Finally the F.C. Lane Group have their 1982/83 catalogue out which contains pots, fuses, resistors, ferrites, and a wide range of connectors and accessories, plus flat cable. Contact F.C. Lane Electronics Ltd, Slinfold Lodge, Horsham, West Sussex, RH13 7RN (telephone 0403 790661).

● The Blacksbury Group, Inc want to encourage as many radio amateurs and shortwave listeners as possible to use the newly-assigned 10 MHz (30 metre) band. Their Slinky Dipole (good grief!) can do the job but requires new tuning information, which Blacksbury are giving away free to any Slinky Dipole owner. Simply send your name, address, and two International Reply Coupons for your Tuning Chart. The address is PO Box 242, Blacksbury,

Virginia 24060, USA.


● Got nothing booked for May 16-17th this year? Logical Solutions, Inc and Network Conferences are holding a seminar on the design for testability (what an awful word) of LSI/VLSI circuits, including components, subassemblies and systems. Full details from Network Conferences Ltd, Printers Mews, Market Hill, Buckingham, MK18 1JX (telephone 02802 5226).

● Had any wizard wheezes lately? A new book called "The Practical Guide for People with a New Idea" will help you through the jungle that comprises the modern patent process. It also contains information about marketing your idea effectively, choosing trademarks etc etc. The book is available for £5.95 post paid from Laurence Shaw, George House, George Road, Edgbaston, Birmingham B15 1PG.

● Dragon 32 and Tandy TRS-80 colour computer owners will be pleased to hear that a new monthly magazine of USA origins and dealing exclusively with these computers is now available. A sample copy of "Rainbow" can be obtained by sending £1.95 plus a large 56p SAE to Elkan Electronics, Freeport, 11 Bury New Road, Prestwich, Manchester M25 6LZ (or ring 061-798 7613 — 24 hour service).

● A new company with an 80% British shareholding reckons that more than £400 million will be spent on constructing new cable TV networks in Britain by next year. Cable TV Construction Ltd will act as consultants and expects to create jobs for several hundred people.

● If you fancy interfacing your Commodore 64 or VIC 20 to a Centronics printer, Wego Computers of 22a High Street, Caterham, Surrey can sell you the necessary interface for your serial port. The device is completely compatible with the other port devices such as disc drives and draws its power from the printer. The cost is £79 plus VAT and the phone number is 0883 49235 if you want more information.

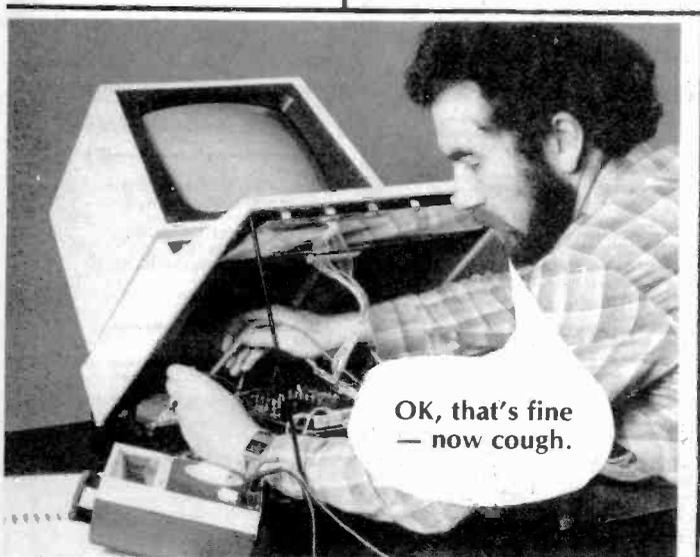

BI-PAK BARGAINS



5T21 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case. Sizes — 0.8, 1.4, 2.2, 4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET
5 precision nut drivers in hinged plastic case. With turning rod. Sizes — 3, 3.5, 4, 4.5 and 5mm **£1.75**

5T41 TOOL SET
5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers — H 0 and H 1 Hex key wrenches — 1.5, 2 and 2.5mm **£1.75**

5T51 WRENCH SET
5 precision wrenches in hinged plastic case. Sizes — 4, 4.5, 5, 5.5 and 6mm **£1.75**
BUY ALL FOUR SETS 5T21-5T51 and get HEX KEY SET FREE
HEX KEY SET ON RING
Sizes 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm
Made of hardened steel
HX/1 **£1.25**



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.
*Quantities approximate, count by weight.

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240° Inline 3-6 Pin, Speakers, Phono, Jack Stereo and Mono etc Valued at well over £3 normal Order No. SX25.
Our Price **1.50** per pak.
Guaranteed to save you money.
SX26 3 Pcs of 6 pin 240° DIN Plugs and Chassis Sockets 50p
SX27A 60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD £1.00
SX28A 50 Assorted Silver Mica Caps. 5.6pF-150pF £1.00
SX29A 50 Assorted Silver Mica Caps. 180pF-4700pF £1.00
SX30A 50 High Voltage Disc Ceramics 750v min up to 8KV Assorted useful values £1.00
SX31A 50 Wirewound 9 watt (avg) Resistors Assorted values 10hm-12K £1.00

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pf-56pf	£1
SX19	100	Mixed Ceramics 68pf-0.5mf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50 1000mf	£1
SX24	20	Tantalum Beads, mixed	£1


*Quantities approximate, count by weight.

BARGAINS

SX91	20 x Large 2" RED LED	£1
SX42	20 small 125 Red LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX44	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded. New	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm.	50p
SX49	20 Assorted Slider Knobs. Black/Chrome, etc	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
*3 1/2 digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single-handed, pushbutton operation *Over range indication *12.5mm (1/2-inch) large LCD readout *Diode check *Fast circuit protection *Test leads, battery and instructions included
Max indication 1999 or — 1999
Polarity indication Negative only
Positive readings appear without + sign
Input impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range — 5°C to 50°C
Power Supply 1 x PP3 or equivalent 9v battery
Consumption 20mW
Size 155 x 88 x 31mm
RANGES
DC Voltage 0-200mV
0-2-20-200-1000V Acc 0.8%
AC Voltage 0-200-1000V
Acc 1.2% DC Current 0-200uA
0-2-20-200mA 0-10 A Acc 1.2%
Resistance 0-2-20-200K ohms
0-2 Megohms Acc. 1%
BI-PAK VERY LOWEST POSS PRICE
£35.00 each

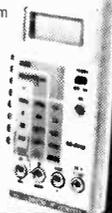

LEATHER CASE FOR RE188m £2.50 each

SIREN ALARM MODULE
American Police type sreamer powered from any 12-volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. BP124 5 watt 12v max — Siren Alarm Module
£3.85
Order No BP124

The Third and Fourth Hand...
... you always need but have never got "until now
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2 diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
Without magnifier ORDER NO. T400 **£4.75**




SX52 6 Black Heatsink will fit TO-3 and TO-220 Ready drilled. Half price value **£1**
SX53 1 Power finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design. pre drilled TO-3 Size 45mm square x 20mm high 40p
SX54 10-66 size 35mm x 30mm x 12mm 35p
SX55 1 Heat Efficiency Power Finned Heatsink 90mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices **£1.50** each

SINGLE SIDED FIBREGLASS BOARD
Order No. Pieces Size Sq. Ins. Price
FB1 4 9 x 2 1/2" 100 £1.50
FB2 3 11 x 3" 100 £1.50
FB3 4 13 x 3" 156 £2.00
DOUBLE SIDED FIBREGLASS BOARD
FB4 2 14 x 4" 110 £2.00
SILICON POWER TRANSISTORS — T03
NPN like 2N3055 — but not full spec 100 watts 50V min. 10 for **£1.50** — Very Good Value 100s of uses — no dud's Order No. SX90

BI-PAK SOLDER — DESOLDER KIT
Kit complete ORDER NO. SX80
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit
1 Quality Desoldering pump. High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle
1.5 metres of De-soldering braid on plastic dispenser.
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt Tool Tweezer Type
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£8.95**

BI-PAK PCB ETCHANT AND DRILL KIT
Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit
1 Sheet PCB Transfers 210mm x 150mm
1 Etch Resist Pen
1 1/2 lb pack FERRIC CHLORIDE crystals
3 sheets copper clad board
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards.
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.75**
ORDER NO. SX81

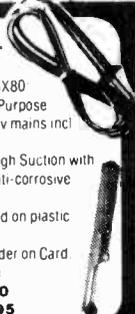

PROGRAMMABLE UNIUNCTION TRANSISTOR
"PUT" case T0106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon
Price: 1-9 10-49 50-99 100+ Normal Retail Price £0.35 each
Each: 20p 18p 15p 13p
SX33A 6 small (min) SDST/SPDT Toggle Switches 240v 5amp **£1.00**
SX35A 6 Rocker Switches 250V 2A **£1.00**
SX32A 12 Assorted Jack & Phono plugs, sockets and adaptors, 2.5m, 3.5mm and standard sizes **£1.00**
SX71 50 BC108 "Fallouts" Manufacturers out of spec on volts or gain You test. **£1.00**
SX72 A mixed bundle of Copper clad Board Fibre glass and paper. Single and double sided. A fantastic bargain **£1.00**

REGULATED VARIABLE STABILISED POWER SUPPLY
Variable from 2.30 volts and 0.2 Amps Kit includes —
1 — VPS30 Module, 1 — 25 volt 2 amp transformer, 1 — 0-50v 2" Panel Meter, 1 — 0-2 amp 2" Panel Meter, 1 — 1470 ohm wirewound potentiometer, 1 — 4K7 ohm wirewound potentiometer Wiring Diagram included VPS30 KIT **£20.**



TECASBOTY
The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices in all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation — Beat the Budget Down with Depression
JUST £6.50.
O/No. SX85

SX38 100 Silicon NPN Transistors—all perfect Coded mixed types with data and eqvt sheet. No rejects. Real value. **£3.00**
SX39 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt. sheet. No rejects. Fantastic value. **£3.00**
2N3055 The best known Power Transistors in the World — 2N3055 NPN 115w. Our BI-PAK Special Offer Price:
10 off 50 off 100 off
£3.50 £16.00 £30.00
BD312 COMPLIMENTARY PNP POWER TRANSISTORS: 10 2N3055 Equivalent MJ2955 — BD312 — T03 SPECIAL PRICE **£0.70** each
10 off **£6.50**

MORE BARGAINS!
SX51 60 metres PVC covered Hook-up wire single and stranded. Mixed colours **£1**
SX58 25 Assorted TTL Gates 7400 Series 7401-7460 **£1**
SX59 10 Assorted Flip Flops and MSI TTL **£1**
SX60 20 Assorted Slider Potentiometers **£1**
SX62 40 Assorted Pre-Sets Hor/Vert etc. **£1**
SX79 10 Reed Switches — glass type 3 Micro Switches — with lever **£1**

BI-PAK
Send your orders to Dept. ET14 BI-PAK PO BOX 6, WARE, HERTS. SHOP AT 3 BALDOCK ST., WARE, HERTS.
TERMS. CASH WITH ORDER. SAME DAY DESPATCH. ACCESS BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRD 388 7006
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Waite 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order. Total Postage add 75p per Total order.

BI-PAK BARGAINS

TRIACS — PLASTIC

4 AMP — 400v — T0202 — TAG 136D	1 OFF	10 OFF	50 OFF	100 OFF
	40p	£3.75	£17.50	£30.00
8 AMP 400v — T0220 — TAG 425	60p	£5.75	£27.50	£50.00

SLIDER POTENTIOMETERS

Plastic 40mm Travel Mono

SX63 5 x 470 ohm Ltr	SX676 5 x 47k Lin
SX64 5 x 1k Lin	SX685 5 x 47k Log
SX65 5 x 22k Lin	SX686 5 x 100k Lin
SX66 5 x 22k Log	SX706 1 meg Lin

ALL AT 50p PER PAK

SX40	250 Silicon Diodes—Switching like IN4148 DO-35 All good—uncoded Worth double our price 45v 75mA	£1.25
SX41	250 Silicon Diodes—General Purpose like OA200/202 BAX13/16 Uncoded 30-100v 200mA DO-7	£1.25

OPTO 7-Segment Displays Brand New 1st Quality LITRONIX DL 707R 14-pin

Red 0.3" Common Anode Display 0-9 with right hand decimal point TTL compatible 5v DC Supply. Data supplied.

5 pieces £3 (60p each)
10 pieces £5 (50p each)
50 pieces £20 (40p each)
100 pieces £35 (35p each)
1,000 pieces £300 (30p each)

THE MORE YOU BUY — THE LESS YOU PAY!

MINIATURE TOOLS FOR HOBBYISTS

MINIATURE ROUND NOSE SIDE CUTTERS
insulated handles 4 1/2 inch length Order No YD43

MINIATURE LONG NOSE PLIERS insulated handles 5 1/2 inch length Order No YD44

MINIATURE BEND NOSE PLIERS insulated handles 5 1/2 inch length Order No YD45

MINIATURE END NIPPERS insulated handles 4 1/2 inch length Order No YD46

MINIATURE SNIP NOSE PLIERS with side cutter and serrated jaws — insulated handles 5 inch length Order No YD42

ALL AT 1.25 each

FLEXKEY DRIVER
A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch Order No FS-1 Flat blade 4mm FS-2 Cross point no 1 £1.75 each

GRIP-DRIVER
binch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places Order No SD-1 Flat blade 4mm SD-2 Cross point no 0 95p each

INEXPENSIVE TOOLS OF IMMENSE VALUE
Combined wire stripper, cutter, crumper incl 25 ass't terminals for crimping Order No WS2 Our low price £1.20 each

BA NUT DRIVER SET
Set of 5 BA spanner shafts plus universal handle in roll-up wallet. Sizes 0 BA 2-4-6-8 BA. Order No T182

NEON SCREWDRIVER
7 1/2 inch blade no NS1 0.65p each
5 1/2 inch blade no NS2 0.55p each

Guarantee
Satisfaction or your money back has always been BI-PAK's GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received

EXPERIMENTAL BOXES — ALUMINIUM — PLASTIC ALUMINIUM BOXES

Made with Bright Aluminium folded construction with deep lid and screws

SIZE" L	W	H	Order No.	Price
5 1/4	2 1/4	1 1/2	159	83p
4	2 1/4	1 1/2	161	83p
4	2 1/2	2	163	83p
3	2	1	164	57p
8	6	3	166	£1.08
6	4	2	167	£1.12

All measurements for boxes are shown in inches. L = Length W = Width H = Height

Plastic Boxes

Coloured Black Close fitting Flanged Lid, fixing screws into brass bushes.

SIZE" L	W	H	Order No.	Price
4	2	1	141	£1.00
4 1/4	2 1/2	1 1/2	143	£1.30
6	3 1/4	2	144	£1.50

Plastic as above but with aluminium top panel

SIZE" L	W	H	Order No.	Price
4	2 1/4	1	146	£1.40

Plastic sloping front

SIZE" L	W	H	Order No.	Price
5 1/2	4 1/4	2 1/4	slope to 148	£2.14

IC SOCKETS The lowest price ever.

The more you buy the cheaper they come!

Pin	10 off	50 off	100 off
8 pin	95p	£3.50	£8.00
14 pin	90p	£3.75	£8.50
16 pin	95p	£4.00	£7.00
28 pin	£2.50	£11.00	£20.00

VOLTAGE REGULATORS T0220

	Positive +	Negative -
7805	— 50p	7905 — 55p
7812	— 50p	7912 — 55p
7815	— 50p	7915 — 55p
824	— 50p	7924 — 55p

BI-PAK'S OPTO 83 SPECIAL

A selection of Large & Small size LED's in Red Green, Yellow and Clear, plus shaped devices of different types. 7 Segment displays, photo transistors, emitters and detectors. Types like MEL11, FPT100 etc. Plus Cadmium Cell DRP12 and germ. photo transistor OCP71. TOTAL OF 25 PIECES

O/N/O SX57A
Valued - Normal Retail £12.00
Our Price **£5.00**

SEMICONDUCTORS FROM AROUND THE WORLD

100 A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices

Guaranteed Value over £10 at Normal Retail Price

Yours for only **£4.00** Data etc. in every pak. Order No SX56

MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch LED indicators at each of the five charging points

Charges — Power —
PP3 (9V) — 220-240V AC
U12 (1.5V penlite) Dims —
U11 (1.5V C) — 210 x 100 x 50mm
U2 (1.5V D) — £6.95

POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket Fused for safety Polarity reversing socket Voltage switch Lead with multi plug Input — 240V AC 50HZ Output — 3 4 5 6 7 5.9 & 12V DC Rating — 300ma MW88

1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncoo.J — you select for VLT5 ALL perfect devices — NO duds Min 50v 50 for £1.00 — worth double ORDER NO SX76

Silicon General Purpose NPN Transistors TO-18 Case Lock fit leads — coded CV7644 Similar to BC147	50 off	100 off	500 off	1000 off
— BC107 — 2T89 ALL NEW VCE 70v IC500mA				
He 75-250 50 off 100 off 500 off 1000 off	PRICE £2.00	£3.80	£17.50	£30.00

Silicon General Purpose PNP Transistors TO-5 Case Lock fit leads coded CV9507 similar 2N2905A to BFX30 VC 60 IC 600mA Min He 50 ALL NEW!	50 off	100 off	500 off	1000 off
PRICE	£2.50	£4.00	£19.00	£35.00

Silicon NPN'L Type Transistors

TO-92 Plastic centre collector Like BC182L — 183L — 184L VCBO 45 VCEO 30 IC200mA Hfe 100-400

ALL perfect devices — uncoded ORDER AS SX183L	50 off	100 off	500 off	1000 off
PRICE	£1.50	£2.50	£10.00	£17.00

PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line VCED 40 VCBO 35 Ic 300mA Hfe 50-400	Brand New — Uncoded — Perfect Devices	50 off	100 off	500 off	1000 off
PRICE		£2.00	£3.50	£15.00	£25.00

DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit 0-2V± instructions provided to extend voltage 6 current ranges Operating voltage 9-12V Typ Power Consumption 50mA O/N/O SX99 Once only price **£9.95**

ELECTRONIC SIREN 12v DC

Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch — 100 cycles per minute Dims — 30mm [o.a.] 60mm [depth] Power — 12v DC Our Price:— **£5.50!**

SILICON BRIDGE RECTIFIERS

Comprising 4 x 1 1/2 amp rectifiers mounted on PCB

VRM — 150vIts IFM — 1.5Amps Size: 1 inch square

10 off	£1.00
50 off	£4.50
100 off	£7.50

Order No. As: 4RI BRect.

MULTITESTERS

1,000 opv Including test leads & Battery. AC volts— 0-15-150-500-1,000. DC volts— 0-15-150-500-1,000. DC currents— 0-1ma-150ma. Resistance— 0-2.5 K ohms 100 K ohms Dims— 90 x 61 x 30mm

30,000 opv. Including test leads and case. AC volts— 0.25-10-25-100-250-500-1,000. DC volts— 0-0.25-1-2.5-10-25-100-250-1,000. DC current— 0-50ua 0-5ma-50ma 0-12amps. Resistance— 0-6K ohms-70K ohms-6meg ohms-60meg ohms

Oecbels: — -20db to plus 56db Short test: — Internal buzzer. Dims — 160 x 110 x 50mm.

O/N/O.1322.OUR PRICE **£6.50 ONLY**

DOME TWEETER

Dome Tweeter for systems up to 50W. Impedance 8 ohms, Frequency Response 2000-20000Hz. Dims 98mm dia x 31mm deep. OUR PRICE **£2.85** O/N/O. DMT200

O/N/O. 1315. OUR PRICE **ONLY £24.75**

INTRUSION ALARM

The DOOR BIRD OB 2000 alerts you before your door is opened. Just hang on the inside door knob — alarm is activated as soon as the outside door knob is touched. ONLY **£3.95**

EDGE CONNECTORS for SINCLAIR

23-way as used for ZX81 **£1.95 each**
28-way as used for Spectrum **£2.25 each**

RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 and 7mm size, 2-cross point, sizes 4 and 6. 1 Ratchet handle. 5-in-1 Kit **£1.45 each** O/N/O. 329B. 40 amp Silicon Rects. 300PIV, T048 STUD. 65p each. 5 for **£1.**

BI-PAK

Send your orders to Dept. HE3, BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST., WARE HERTS. TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS BARCLAYCARD ALSO ACCEPTED. TEL. 1062013182. GIRO 388 7006 Add 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember: you must add VAT at 15% to your order. Total Postage add 50p per Total order.

ZX81 MUSIC BOARD

There have been a great many commercial and hobbyist designs for ZX81 peripherals, but we feel this one is something special. Full software listings will be given to help you use the board and the price is low. Design and development by M. P. Moore.

Give your space invaders program real 'zapp' — this add-on board enables you to hear those little green monsters being blasted away. Plug in the board, load the software cassette, and with two instructions you have a wide range of on-board sounds for your computer games; or you can copy music for your ZX81 to play, or devise your own sound effects for use in your own programs. You can also mix your own sound effects with the on-board sounds if you wish.

The unit is a sound generator with a fusible-link memory programmed with sounds varying from gunshots to spaceships, and with a basic octave of notes from which a range of seven or more octaves of music is obtained. When

used with the software supplied it will bring ZX81 games to life with startling realism. The board will produce sounds with the basic 1K ZX81 but its full potential is realised with a 16K expansion, when the music program can provide a completely new use for those who are wondering what to do with their ZX81 now they have it.

A complete kit of parts is available (see Buylines), which also includes a comprehensive user's manual and software cassette. A demonstration cassette containing on-board sounds and music generated by the add-on sound board is available at an all-inclusive price of 95p. Petron Electronics have been good enough to grant us permission to publish both their PCB design and the complete

software listings, including the PROM hex dump, to satisfy those diehard readers who insist on doing everything themselves. However, given the low price of Petron's kit, which contains all the hardware required plus documentation, we think that this is the best way to go for cost-effectiveness, ease of construction and convenience.

Construction

All components in the circuit are mounted on a single-sided PCB (see overlay): IC sockets are supplied for all ICs. Two screened leads provide the connection from the PCB to your amplifier; all other connections to the board are made via an edge connector which plugs straight into the back of the ZX81



The ZX81 music and sound effects board, like most other ZX peripherals, plugs directly into the computer.

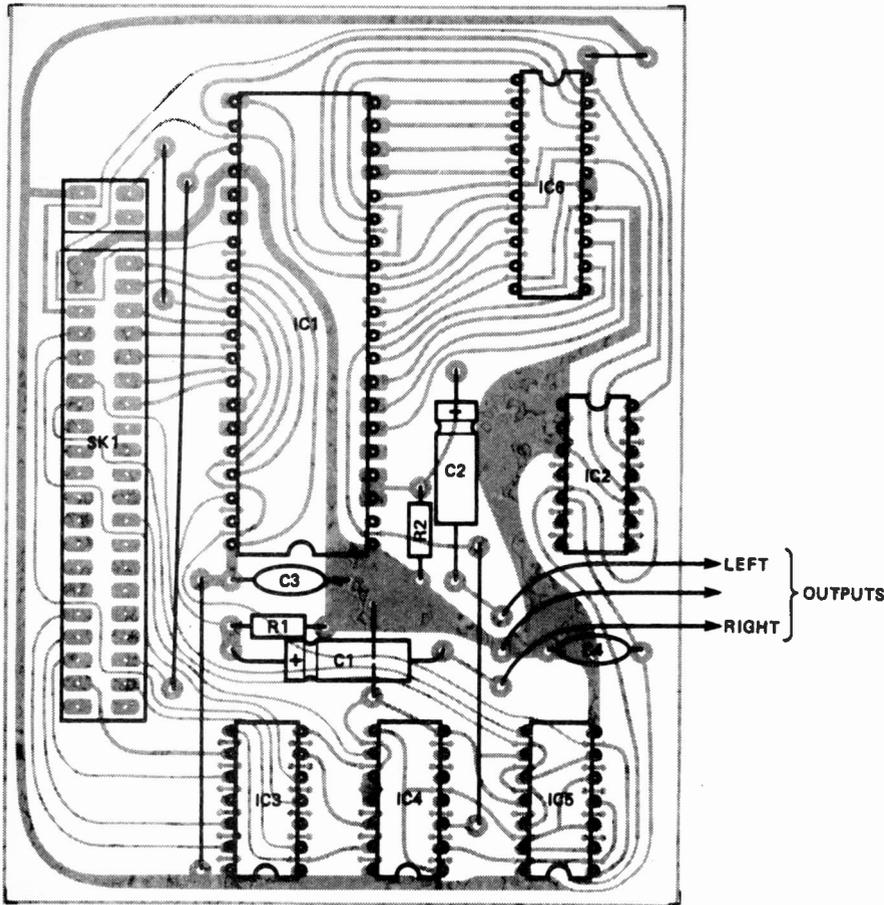


Fig. 1 Component overlay for the ZX81 sound board.

(or 16K RAM pack if used).

First of all solder the six IC sockets and then the six links: some of these are close to each other or to other components and the use of insulated wire is recommended. Now solder resistors R1 and R2 — these resistors can be of any value between 1k0 and 1k8. Solder the electrolytic capacitors C1 and C2, taking care to mount them the right way round (see overlay), and then capacitors C3 and C4. Finally, carefully insert and solder the edge connector leaving a gap of approximately 7 mm between the connector and the PCB. The pin corresponding to 9 V on the connector is not required and, for safety purposes, has been cut. Now carefully check all your soldered joints, preferably with a magnifying glass, and make sure that there are no bridges across any of the tracks.

If the board is to be used with a stereo amplifier, cut the length of screened cable supplied in half and solder the inner cores to one end to the left and right outputs, and connect the outer cores (screen) to the point marked GND. Take care to insulate these wires so that they will

not short across other component leads. If you wish to use the board with a mono amplifier, connect a wire link between the two outputs and to this link connect the inner core of one of end of the screened cable, taking the screen to 0 V and insulating the cable as before. Connect the phono plugs (or one of them if you are using a mono amplifier) to the other end of the screened cable.

Now, carefully checking the orientation of the ICs, insert them into the IC sockets. Note that IC2 and IC6 are mounted in the opposite direction to the other ICs. With your ZX81 switched off, carefully plug the board into the back of the ZX81. If you have a 16K RAM pack, plug this on first: the sound board will plug onto the back of your RAM pack. Switch on your ZX81 and wait for the inverse K prompt to appear on your screen.

On-Board Sound Program

This program enables you to include the on-board sounds listed in Table 2 in your own programs. To use these sounds all you have to do is to load the first short program

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)
R1, 2 1k2

Capacitors
C1, 2 100u 16 V axial electrolytic
C3, 4 100n polyester

Semiconductors
IC1 AY-3-8910
IC2 74LS93
IC3 74C20
IC4 74C32
IC5 74C02
IC6 TBP28L22N

Miscellaneous
PCB; edge connector; IC sockets; two off phono plugs; 2 m of screened cable.

BUYLINES

Petron Electronics supply a full kit of parts for the project. The kit includes the PCB and all components, and comes complete with a comprehensive user's manual and software cassette. The kit price is £24.05 all inclusive. The board is also available ready-built, together with manual and cassette, for £29.95. A demonstration cassette is available for 95p all inclusive. The manual may be purchased separately for £1.25, refunded upon subsequent purchase of a kit. Petron Electronics may be found at 1 Courtlands Road, Newton Abbot, Devon.

from the software cassette and connect up your amplifier, keeping the volume fairly low. The following program will allow you to review the range of principal on-board sounds available before incorporating them in your own programs.

```

10 PRINT "SOUND NO.?"
20 INPUT S
30 POKE 16531,S
40 RAND USR 16514
50 CLS
60 GOTO 10
    
```

In order to run this program type GOTO 10. ➔

The computer will now ask you the number of the sound you wish to hear: SOUND NO. ? As an example, type 153 NEWLINE. The computer will repeat this question after each sound. A continuous sound (eg helicopter) must be silenced by typing 0 or another sound number.

In order to use these sounds in your own programs, enter your program without altering line 1 of program "S". At each point in your program where you require a sound to be generated, you simply include the following program lines: ➔

HOW IT WORKS

IC6 is a fusible-link read-only memory (PROM) programmed with the data for all the on-board sounds and a basic octave of notes for music. This memory is accessed through the ports on IC1.

IC1 is a programmable sound generator (PSG), an AY-3-8910 which can be programmed to generate a wide range of sounds. Once data is written to this chip it produces and maintains the sound without continuous CPU maintenance, thus making it ideal for use with computer programs.

The PSG has three analogue outputs: outputs A and B are connected directly together and, via C1, connect to one channel of your amplifier; output C is connected via C2 to the other amplifier channel. The board will, therefore, give a dual image effect when used with a stereo amplifier. If you wish to use a mono amplifier, the analogue output C is connected directly to A and B.

IC3 and IC4a are used as an address decoder: the output of IC4a will be logic 0 when address lines A0, A1 and A4 - A7 are 1; M1 must also be logic 1. IC4b is used to provide a chip select signal for the PSG only when the Input/Output request (IORQ) is at logic 0. Thus the output of IC4b will be 0 only when a read or write operation on the PSG is to be performed. Whenever the output of IC4b is logic 1, the outputs of IC5c and IC5d will be 0, BC1 and BDIR will both be 0, and the PSG will be in the inactive state: see Table 2. (Since whenever it is deselected the 'inact' signal is sent, it is not necessary for the ZX81 program to send 'inact' to the PSG.)


IC5a and IC5b are used, together with IC5c and IC5d, to provide the necessary combinations of 0 and 1 for BC1 and BDIR. The output of IC4c drives the fusible-link PROM chip select input: this is to minimise the possibility of data bus contention between the PSG and the PROM should PSG port D accidentally be programmed as an output port, since IC4c output will only be 0 during a PSG read cycle.

The maximum clock frequency to the PSG is 2 MHz. IC2 is a low power Schottky version of the 7493 counter and is used here to divide the ZX81 clock frequency by 2.

Next month we will conclude this project by giving full listings and explanations of software to play up to 833 chords of music; to devise your own sound effects; and to mix your effects with the on-board sounds.

TABLE 2

Sound N	Description	Continuous?	Sound N	Description	Continuous?
0	Silence	—	92	Mid blip	No
8	Cannon fire	No	106	High blip	No
9	Pistol shot	No	204	Musical blip	No
50	Rifle shot	No	57	Steam engine	Yes
64	Missile	No	145	Steam engine with whistle	Yes
18	Sonar	Yes	167	Train horn lower note	Yes
153	Explosion	No	178	Train horn upper note	No
190	Helicopter	Yes	32	Propellor aeroplane	Yes
28	Fog horn	Yes	39	Jet plane on the ground	Yes
29	Fog horn	Yes	134	Jet plane flying	Yes
21	Compressor	Yes	52	Mechanical hammer	Yes
99	Waterfall	Yes	49	UFO	Yes
101	Waterfall	Yes	131	UFO	Yes
121	Low bong	No	213	UFO	Yes
33	Mid bong	No	214	UFO	No
45	High bong	No	231	UFO	Yes
78	Low blip	No			

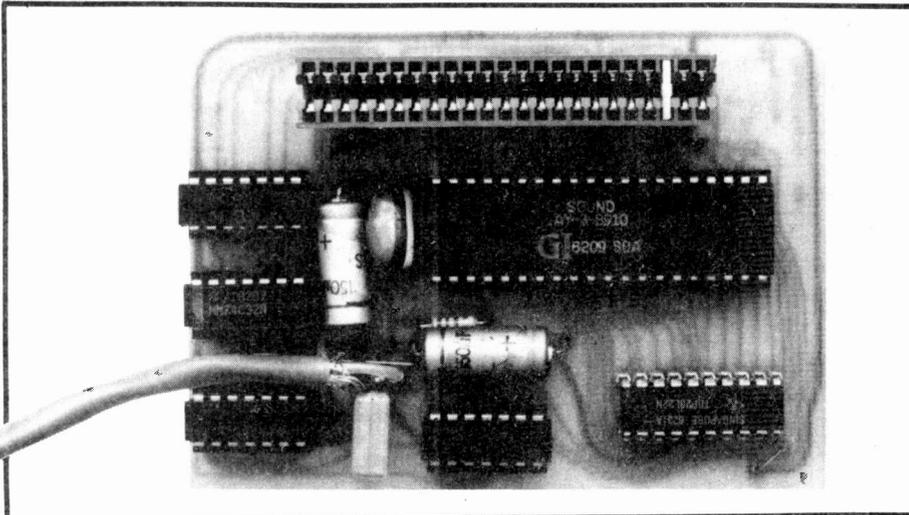

Close-up of the prototype board.

TABLE 1

BC1	BDIR	FUNCTION
0	0	INACTIVE
0	1	WRITE TO PSG
1	0	READ FROM PSG
1	1	LATCH ADDRESS

POKE 16531, x
RAND USR 16514

where x is the number of the sound required from table 2.

The sound POKEd to 16531 remains the same until changed. Therefore, if you wish to repeat the same sound, there is no need to repeat **POKE 16531,x** — all you need to do is repeat the line **RAND USR 16514**.

Fast repetition of single sounds can be used to give a different effect. For example, the following program uses the rifle shot (sound 50) to generate a machine gun sound:

```

70 POKE 16531,50
75 FOR D=1 TO 40
80 RAND USR 16514
85 PAUSE 1
90 NEXT D
    
```

Now type **GOTO 70** and the computer will generate a burst of machine gun fire.

Table 2 gives the principal sounds that may be obtained, but there are many other interesting sounds which you can find by experimenting with other numbers not listed in this table.

EPROM DATA

00	00	00	00	00	00	00	00
00	00	00	00	00	00	1F	07
10	10	10	FF	28	09	69	00
00	3B	00	00	10	FF	32	08
96	02	C8	02	64	02	0F	00
10	10	10	3C	00	08	00	32
03	0F	00	10	10	10	3C	00
08	07	10	10	10	FF	05	09
07	08	10	10	96	03	08	07
10	00	10	FF	0C	0F	BE	00
BE	00	BE	00	00	38	10	10
10	00	01	09	5F	00	5F	00
5F	00	00	38	10	10	10	00
01	09	2F	00	2F	00	2F	00
00	38	10	10	10	00	01	09
17	00	17	00	17	00	00	00
10	10	10	00	03	09	19	00
32	00	41	00	1E	00	0A	0A
0A	6E	00	6E	00	00	00	09
10	0C	0F	10	96	03	08	1F
07	10	10	10	FF	64	09	5A
01	5A	01	5A	01	00	38	0F
0F	0F	05	01	05	01	05	01
00	38	10	10	10	00	19	09
FA	03	00	00	03	05	10	0A
10	FF	01	0C	A0	01	64	01
96	00	0F	30	10	10	10	32
02	09	FF	3F	10	10	10	FF
32	08	5C	0F	70	0E	A0	0D
DC	0C	28	0C	28	0C	68	0B
D2	0A	46	0A	9A	09	22	09
22	09	A0	08	28	08	AE	07


PROGRAM 'S'

1 REM (Our machine code).

Machine code at line 1:

3E	07	D3	FF	3E	78	D3	F7
21	B4	40	E5	01	FB	0E	C5
16	xx	3E	0E	D3	FF	7A	D3
F7	14	3E	0F	D3	FF	ED	A2
20	F0	C1	E1	16	00	7A	D3
FF	5E	7B	D3	F7	14	10	F5
C9	xx						
xx							

PROJECT: ZX81 Music Board

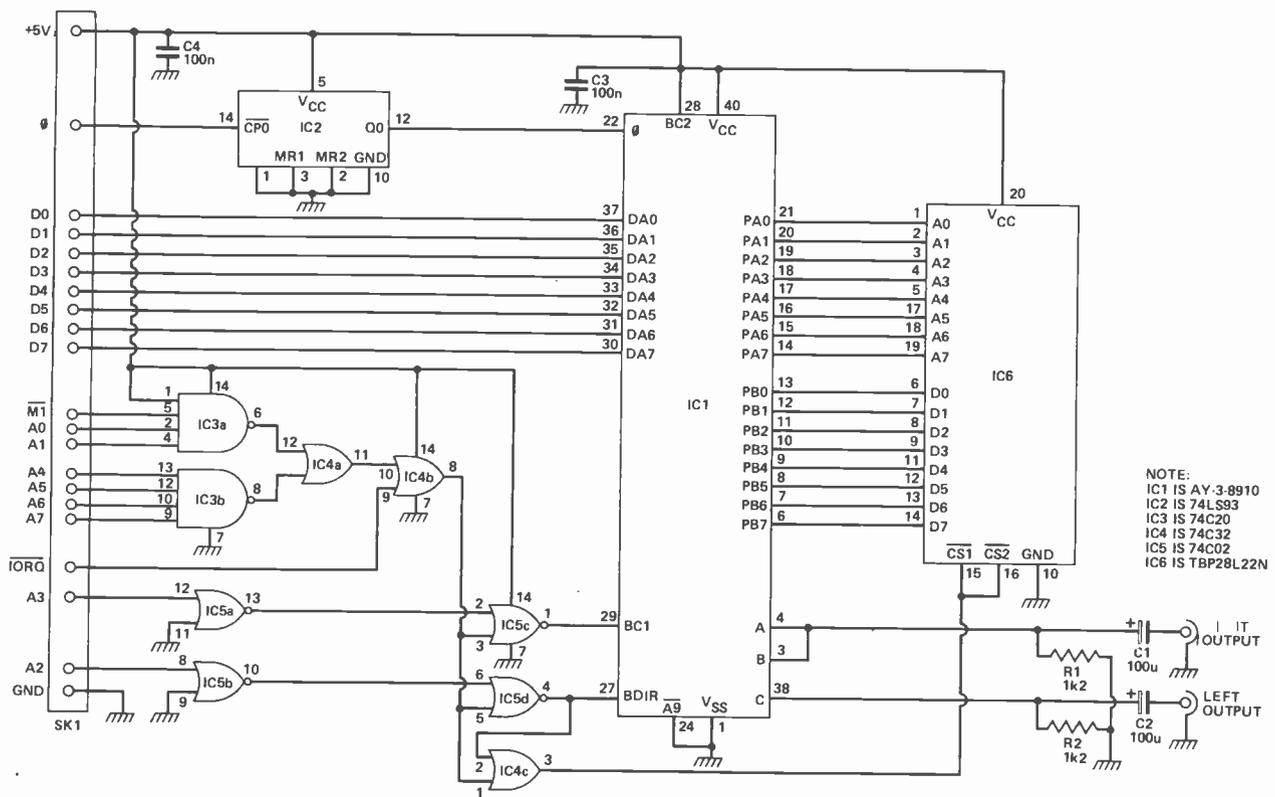

NOTE:
 IC1 IS AY-3-8910
 IC2 IS 74LS93
 IC3 IS 74C20
 IC4 IS 74C02
 IC5 IS 74C02
 IC6 IS TBP28L22N

Fig. 2 Complete circuit diagram for the ZX81 sound board.

ETI

The 2001 sweeps the board at only £110*



Get all the waveforms you need - 1 Hz to .1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and low-level main outputs.

An applied DC Voltage at the Sweep input can shift the 2001's frequency; or sweep up to 100: 1 with an AC signal. A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

For value for money the 2001 sweeps the rest off the board.

For immediate action — The G.S.C. 24 hour, 5 day a week service
 Tel: (0799) 21682 and give us your Access, American Express, Barclaycard
 number and your order will be in the post immediately or just clip out the coupon.
 Goods despatched within 48 hours.

*price excluding P&P and 15% VAT

GLOBAL SPECIALTIES CORPORATION



G.S.C. (U.K.) Limited, Dept. 9999
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex CB11 3AQ
 Tel: Saffron Walden (0799) 21682 Telex: 817477

Global Specialties Corporation (UK) Limited Dept. 9999
 Unit 1, Shire Hall Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 2001 Sweepable Function Generator	£129.95 (inc. P&P and 15% VAT)	Qty Reqd.	For FREE catalogue tick box
--	-----------------------------------	--------------	--------------------------------

Name Address


I enclose PO/Cheque for £..... or debit my
 Barclaycard/Access/American Express No exp date



MULLARD SPEAKER KITS


Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm
Price £14.90 each + £2.00 P & P.
 5" 30W system — recommended cabinet size 160 x 175 x 295mm
Price £13.90 each + £1.50 P & P.

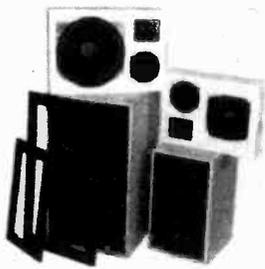Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc.
 8" system cabinet kit **£8.00 each + £2.50 P & P.**
 5" system cabinet kit **£7.00 each + £2.00 P & P.**




STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.
Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V D.C. at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.
Price £28.70 + £2.50 postage and packing.
 Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) **£3.50.**

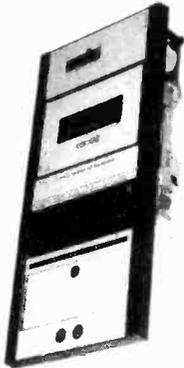


LOUDSPEAKERS

15" 100 watt R.M.S. (HI-FI, P.A., DISCO, BASS GUITAR) Die cast chassis, 2" aluminium voice coil, white cone with aluminium centre dome. 8 ohm imp., Res. Freq. 20Hz., Freq. Resp. to 2.5KHz., Sens. 97dB (As photograph). **Price: £32.00 + £3 carriage.**
12" 100 watt R.M.S. (HI-FI) Die cast chassis. 2" aluminium voice coil. Black cone. 8 ohm imp., Res. Freq. 20Hz., Freq. Resp. to 4.5KHz. Sens. 95dB. (As photograph). **Price: £23.50 + £3 carriage.**
8" 50 watt R.M.S. (HI-FI, P.A.) 1 1/2" aluminium voice coil. White cone. 8 ohm imp. Res. Freq. 40Hz., Freq. Resp. to 6KHz. Sens. 92dB. Also available with black cone fitted with black metal protective grille. (As photograph). **Price: White Cone £8.90, Black cone/grille £9.50 P&P £1.25.**
12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. **Price: £22.00 + £3 carriage.**
12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. **Price £22 + £3 carriage.**
15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. **Price: £47 + £4 carriage.**

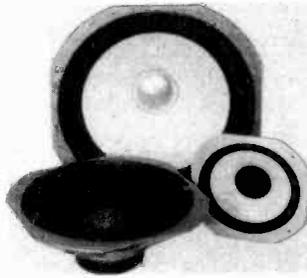

PIEZO ELECTRIC TWEETERS MOTOROLA

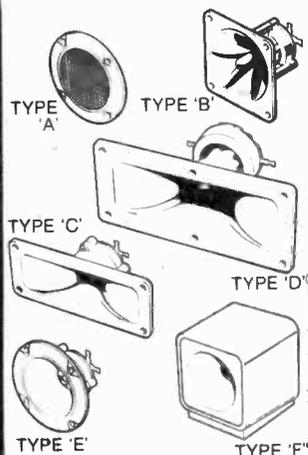Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. **Price £3.45 each.**
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £4.35 each.**
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. **Price £5.45 each.**
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. **Price £6.90 each.**
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. **Price £4.35 each.**
TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. **Price £10.75 each.**
P&P 20p ea. (or SAE for Piezo leaflets).



OMP 80 LOUDSPEAKER

The very best in quality and value. Ported tuned cabinet in hardware black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms, 45Hz-20KHz. Size: 20in x 15in x 12in; Weight: 30 pounds.
Price: £48.00 each. £90 per pair
Carriage: £5 each. £7 per pair

1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
 - Compact size
4 1/4" x 13" x 2 1/2"
 - Easy snap in fixing through panel/cabinet cut out
 - Insulated plastic case
 - Full wave control using 8amp triac
 - Conforms to BS800
 - Suitable for both resistance and inductive loads
- Innumerable applications in industry, the home, and discos/theatres etc.


Price: £11.70 each + 50p P&P (Any quantity)

BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Antiskate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.
Price: £28.50 + £2.50 P&P



POWER AMPLIFIER MODULES

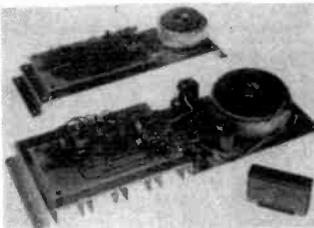

KEYBOARDS



MEMBRANE KEYBOARDS manufactured from a tough poly-carbonate film mounted on 1mm glass fibre printed circuit board assembly incorporating silver plated contacts.

16 way numeric keyboard Standard keyboard providing 0-9 and A-F functions.
 Size: 100mm x 100mm x 2mm. **Price: £5.95 + 35p P&P**
 Alpha Numeric Keyboard Full size 55 key non encoded keyboard with the commonly required functions in a Qwerty array. Matrix output via a 16 pin DIL socket.
 Size: 350mm x 100mm x 2mm. **Price: £13.99 + 50p P&P**



100 WATT R.M.S. AND 300 WATT R.M.S. MODULES


Power Amplifier Modules with integral toroidal transformer power supply, and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. An LED Vu meter is available as an optional extra.

SPECIFICATION:
Max Output Power: 110 watts R.M.S. (OMP 100) 310 watts R.M.S. (OMP 300)
Loads: Open and short circuit proof. 4-16 ohms.
Frequency Response: 20Hz — 25KHz ±3dB.
Sensitivity for Max. Output: 500mV at 10K (OMP 100) 1V at 10K (OMP 300)
T.H.D.: Less than 0.1%
Supply: 240V 50Hz
Sizes: OMP 100 360 x 115 x 72mm
 OMP 300 460 x 153 x 65mm
Prices: OMP 100 £31.50 each + £2.00 P&P
 OMP 300 £89.00 each + £3.00 P&P
 Vu Meter £6.50 each + 50p P&P

Matching 3-way loudspeakers and crossover


Build a quality 60watt RMS system 8ohms
 Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer 35Hz-4.5KHz
 - ★ 3" Tweeter 2.5KHz-19KHz
 - ★ 5" Mid Range 600Hz-8KHz
 - ★ 3-way crossover 6dB/oct 1.3 and 6KHz
- Recommended Cab-size/26" x 13" x 13"**
 Fitted with attractive cast aluminium fixing es-cutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.
Price £22.00 per kit + £2.50 postage and packing. Available separately, prices on request.

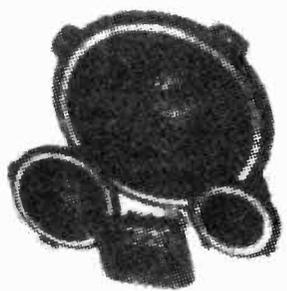

12" 80 watt R.M.S. loudspeaker.

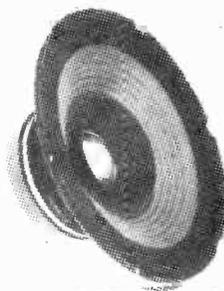A superb general purpose twin cone loudspeaker. 50 oz. magnet. 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.
Price £17.99 each + £3.00 P&P.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



Manchester Home Computer Show

MIDLAND HOTEL

April 21/22/23

Your diary dates are:

Brighton May
Birmingham June
Nottingham September
Newcastle October
Cardiff December

Sponsored jointly by:
Personal Computing Today
ZX Computing
Computing Today
Home Computing Weekly
Personal Software

At the Home Computer Shows will be a complete cross section of the hardware and software available to the home user. The emphasis is on the lower end of the price bracket with computers from £50-£400.

If you are interested in computers and what they can do for you then come along to our **COMPUTER ADVICE CENTRE**: experts will be on hand to give you impartial advice on equipment available.

Try out the machines in our own demonstration area and see programs running covering educational, games and small business applications.

There is a **COMPETITION** at every show to:

WIN TWO COMPUTERS.

Win a computer for yourself as well as one for the school of your choice: free entry form with advance tickets. Also available at the show with the show catalogue.

**ADMISSION £2.00 (CHILDREN UNDER 8 & O.A.P's FREE)
AND IF YOU'RE A PARTY OF 20 OR MORE, THERE'S A 25%
DISCOUNT**

Thursday 21 April '83 (12am-7pm)

Friday 22 April '83 (10am-6pm)

Saturday 23 April '83 (10am-6pm)

**The Manchester Home Computer Show
Midland Hotel. (Opposite Town Hall).**

For advance tickets send cheque/postal order to:
ASP Exhibitions
Argus Specialist Publications
145 Charing Cross Rd,
London WC2H OEE
Tel: 01-437-1002

ADVANCE TICKET OFFER
MANCHESTER HOME COMPUTER SHOW
SAVE £1.00

Name Mr/Mrs/Miss
Address

ETI APRIL 83

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting.

- TDR300K Remote Control Dimmer £14.30
- MK6 Transmitter for above £4.20
- TD300K Touchdimmer £7.00
- TDE/K Extension kit for 2-way switching for TD300K £2.00
- LD300K Rotary Controlled Dimmer £3.50



HOME CONTROL CENTRE

This New Remote Control Kit enables you to control up to 16 different appliances anywhere in the house from the comfort of your armchair. The transmitter injects coded pulses into the mains wiring which are received by receiver modules connected to the same mains supply and used to switch on the appliance addressed. Receivers are addressed by means of a 16-way keyboard, followed by an on or off command. Since pushing buttons can become rather boring, the transmitter also includes a computer interface so you can programme your favourite micro to switch lights, heating, electric blanket, make your coffee in the morning, etc., without rewiring your house. JUST THINK OF THE POSSIBILITIES. The KIT includes all PCBs and components for one transmitter and two receivers, plus a drilled box for the transmitter. **Order as XK112. £42.00**

Additional Receivers XK111 £10.00

ELECTRONIC LOCK KIT XK101

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15 V d.c. at 40mA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £10.50**

Electric lock mechanism for use with latch locks and above kit **£13.50**

THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

FEATURES INCLUDE:

- 0.5" LED 12 hour display.
- Day of week, am/pm and output status indicators.
- 4 zero voltage switched mains outputs.
- 50/60Hz mains operation.
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets.
- Powerful "Everyday" function enabling output to switch every day but use only one time set.
- Useful "sleep" function—turns on output for one hour.
- Direct switch control enabling output to be turned on immediately or after a specified time interval.
- 20 function keypad for programme entry.
- Programme verification at the touch of a button.

(Kit includes all components, PCB, assembly and programming instructions). **ORDER AS CT5000**



NOW ONLY £39 WITH SO MANY EXTRA FEATURES. OPTIONAL BLACK PLASTIC CASE. READY DRILLED. £2.50

Have you got our **FREE ORANGE CATALOGUE** yet? NO?! Send S.A.E. 6" x 9" TODAY!!

It's packed with details of all our **KITS** plus large range of **SEMICONDUCTORS** including CMOS, LS TTL, linear, microprocessors and memories; full range of LEDs, capacitors, resistors, hardware, relays, switches etc. We also stock VERO and Antex products as well as books from Texas Instruments, Babani and Elektor.

ALL AT VERY COMPETITIVE PRICES. ORDERING IS EVEN EASIER — JUST RING THE NUMBER YOU CAN'T FORGET FOR PRICES YOU CAN'T RESIST.

5-6-7 8-9-10

and give us your Access or Barclaycard No. or write enclosing cheque or postal order. Official orders accepted from schools, etc. **Answering service evngs & weekends**

MINI KITS

- MK1 TEMPERATURE CONTROLLER/THERMOSTAT** Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. 1KW **£4.00**
- MK2 Solid State Relay** Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. **£2.60**
- MK3 BAR/DOT DISPLAY** Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.50**
- MK4 PROPORTIONAL TEMPERATURE CONTROLLER** Based on the SL441 zero voltage switch, this kit may be wired to form a "burst fire" power controller, matching the temperature of an enclosure to be maintained to within 0.5°C. Max. load 3KW **£5.55**
- MK5 MAINS TIMER** Based on the ZN1034E Timer-IC this kit will switch a mains load on (or off) for a preset time from 20 mins. to 35 hrs. Longer or shorter periods may be realised by minor component changes. Max. load 1KW. **£5.00**

3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3-9V battery and push-switch to complete. **AN IDEAL PROJECT FOR BEGINNERS** Order as XK102 **£5.00**

XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. **IDEAL FOR BEGINNERS** **£5.00**

COMPONENT PACKS

- PACK 1** 650 Resistors 47 ohm to 10 Mohm — 10 per value **£4.00**
- PACK 2** 40 x 16V Electrolytic Capacitors 10µF to 1000µF — 5 per value **£3.25**
- PACK 3** 60 Polyester Capacitors 0.01 to 1µF/250V — 5 per value **£5.55**
- PACK 4** 45 Sub-miniature Presets 100 ohm to 1 Mohm — 5 per value **£2.90**
- PACK 5** 30 Low Profile IC Sockets 8, 14 and 16 — pin — 10 of each **£2.40**
- PACK 6** 25 Red LEDs (5mm dia.) **£1.25**

DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. **Price £15.50**



DISCO LIGHTING KITS

- DL1000K** This value-for-money kit features a bidirectional sequence speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **£14.60**
- DL2100K** A lower cost version of the above, featuring unidirectional channel selection with speed variable by means of a pre set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Optional opto input DLA1. Allowing audio ("beat") light response. **60p**
- DL3000K** This 3 channel sound to light kit features zero voltage switching, automatic level control and built in mic. No connections to speaker or amp required. No knobs to adjust simply connect to mains supply and lamps. (1KW channel) **Only £11.95**

"OPEN-SESAME"

The XK103 is a general purpose infra-red transmitter/receiver with one momentary (normally open) relay contact and two latched transistor output. Designed primarily for controlling motorised garage doors and two auxiliary outputs for drive/garage lights at a range of up to 40 ft. The unit also has numerous applications in the home for switching lights, TV, closing curtains, etc. Ideal for aged or disabled persons. The Kit comprises a mains powered receiver, a four button transmitter, complete with pre-drilled box, requiring a 9V battery and one opto-isolated solid state switch kit for interfacing the receiver to mains appliances. As with all our kits, full instructions are supplied. **ONLY £23.75**

THE JUPITER ACE MICROCOMPUTER

uses FORTH which executes about 10 times faster and requires less program memory than a comparable program using basic. Features 8K ROM, 3K RAM, built in speaker, 40 key keyboard and a 32 x 24 line-flicker free display on TV. Comes supplied complete with leads, mains adaptor, a comprehensive easy-to-follow manual on Forth programming + FREE cassette containing 5 sample programs.

ONLY £75.00 (+ £2.00 carriage + VAT)

WHY NOT COME IN AND SEE IT FOR YOURSELF!

LCD 3 1/2 DIGIT MULTIMETER

16 ranges including DC voltage (200 mv-1000v) and AC voltage, DC current (200 mA-10A) and resistance (0.2 M) + NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155 x 88 x 31mm. Requires PP3 9V battery. **£29.00** Test leads included.

REMOTE CONTROL KITS

- MK6 SIMPLE INFRA RED TRANSMITTER** Pulsed infra red source complete with hand-held plastic box. Requires a 9V battery. **£4.20**
- MK7 INFRA RED RECEIVER** Single channel, range approx. 20ft. Mains powered with a triac output to switch loads up to 500W at 240V ac. **£3.00** (RS500K—Special Price for MK6 and MK7 together. **£12.50**)
- MK8 CODED INFRA RED TRANSMITTER** Based on the SL490, the kit includes all components to make a coded transmitter and only requires a 9V (PP3) battery and keyboard. 8 x 2 x 1.3cms **£5.90**
- MK10 16-WAY KEYBOARD** For use with MK8 and MK18 to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. **£5.40**
- MK11 10-Channel + 3 Analogue o/p IR Receiver** Based on LM922 decoder IC. Functions include on/standby output, toggle, control of volume, tone and lamp brightness. Includes its own mains supply. **£12.00**
- MK12 16-CHANNEL IR RECEIVER** For use with MK8 kit with 16 on/off outputs, which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Latched or momentary outputs—please specify when ordering. Includes its own mains supply. **£11.95**
- MK13 11-WAY KEYBOARD** For use with MK8, MK18 and MK11 kits. **£4.35**
- MK18 Mains Powered IR Transmitter** Mains powered for continuous operation—single channel, for applications such as burglar alarms, automatic door openers, etc. Range approx. 6ft. **£2.50**
- MK17 12V d.c. IR RECEIVER** For use with MK6 or MK16. Relay output with DP 3 Amp change-over contacts, may be used as latched, momentary or "break beam" receiver. Operates from 6-13V d.c. **£9.50**
- MK18 HIGH POWER IR TRANSMITTER** Similar to MK8 but with range of approx. 60ft. **£6.20**
- Ancillary Kits:** **MK2 Solid State Relay** Opto-isolated with zero voltage switching. No. triac supplied. **£2.60**
- MK15 DUAL LATCHED SOLID STATE RELAY** Comprises 2 x solid state relays and latch for use with momentary version of the MK12. 2 output triacs required (not supplied). **£4.50**

24 HOUR CLOCK/APPLIANCE TIMER KIT

- Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.
- CT1000K Basic Kit **£14.90**
- CT1000K with white box (56-131 x 71mm) **£17.40**
- (Ready Built) **£22.50**



Add 55p postage & packing +15% VAT to total. Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability. **OPEN** 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

For a detailed booklet on remote control — send us 30p and S.A.E. (6" x 9") today.


ALL PRICES EXCLUDE VAT

FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to —

ELECTRONICS ETI

11 Boston Road London W7 3SJ

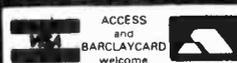

TEL: 01-567 8910 ORDERS 01-579 9794 ENQUIRIES 01-579 2842 TECHNICAL AFTER 3PM

DESIGNER'S NOTEBOOK

Who needs to bother winding miles of wire onto a bobbin when high voltages can be generated with some inverters and a handful of diodes and capacitors? Rory Holmes shows how it's done.

In this month's first Designer's Notebook we shall be looking at a variety of interesting voltage multiplier circuits that can be built using ordinary CMOS gates and common-or-garden 1N4148 signal diodes. DC-to-DC converters for a number of applications became possible by simply driving voltage multiplier chains with an AC clock signal, again implemented with CMOS gates. The initial supply voltage can be multiplied both positively and negatively, to give for example a split rail op-amp supply from a standard 5 V TTI supply. Negative and positive voltage references used in analogue-to-digital conversion and other signal conditioning circuits can also be generated, as can general purpose high voltage bias rails.

By using a novel 'chain' of inverter gates to independently drive each node of a diode-capacitor ladder, some rather unique circuits result.

Chain Reaction

First, let's look at the usual multiplier circuits shown in Fig. 1a. These are normally used with rectifier-type diodes, low frequency AC inputs (sine waves) from transformers, and electrolytic smoothing capacitors. At first glance there seems to be no common pattern between them, and little similarity to the multiplier chains used in TVs and other EHT power supplies.

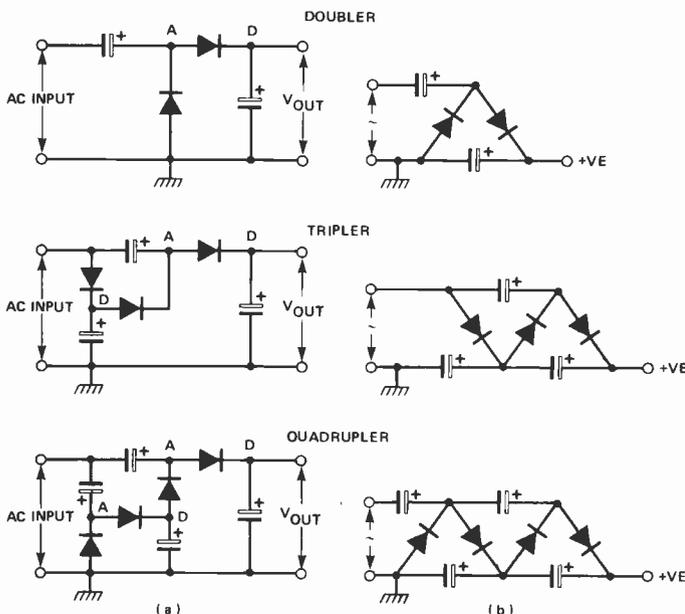


Fig. 1 Standard voltage multiplier circuits.

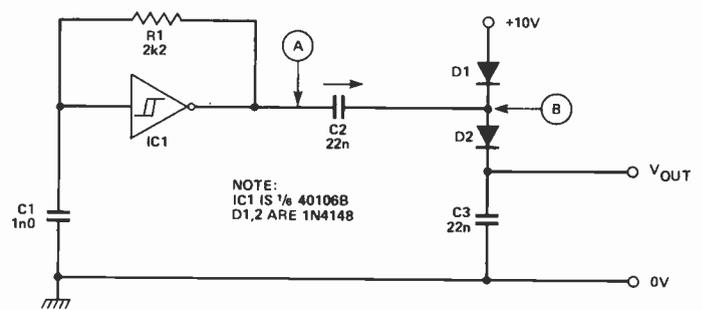


Fig. 2 A CMOS doubler circuit.

However, in all cases the AC input waveform is fed via capacitors to appear at those circuit junctions marked 'A' in Fig. 1a, while those junctions marked 'D' will maintain a steady DC potential relative to the earth point. We can thus redraw the circuits by connecting up the capacitors in two series chains (assuming their values are altered accordingly) and still preserve the same circuit action. One chain carries the AC signal, while the other accumulates the DC voltage shifts. Figure 1b shows these redrawn circuits, which now appear as extensions of the standard ladder network. The doubler, of course, remains in its original form since it only has one set of capacitors.

Starting with the doubler, we can build a very simple DC-to-DC converter using one CMOS gate as shown in Fig. 2. The Schmitt inverter gate is configured as a square wave oscillator running at about 100 kHz — the multiplier capacitors C2 and C3 will therefore have a low impedance at this frequency, which is also within the switching speed capability of the 1N4148s. For this reason, rectifier diodes such as the 1N4001, which have much slower switching speeds, cannot be used in these circuits.

The oscillator output at point 'A' will therefore be switching between the 0 V and 10 V supply levels. When the output is at logic low, capacitor C2 will charge up positively (in the direction of the arrow) via D1. D2 is reverse biased and so effectively out of circuit. When point 'A' goes high to +10 V the positive end of C2 at 'B' will be raised to +20 V. This reverse biases D1 and allows C3 to charge up through D2. The voltage on C3 is thus maintained at about +20 V less two diode drops (ie at 18V6) as the cycle repeats itself. This is known as a diode charge pump.

Building An Extension

This principle can be extended using exactly the same chainlike structure as illustrated in the positive and negative multipliers of Fig. 3. In both cases the inverter gates are cascaded and driven from a square wave

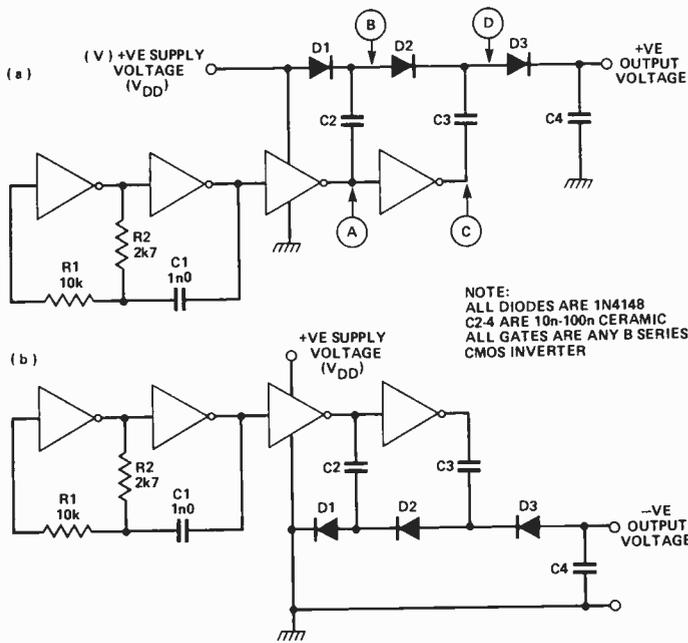


Fig. 3a A two-stage positive voltage multiplier (multiplies by +3). b. A two-stage negative voltage multiplier (multiplies by -2).

oscillator at around 100 kHz. Each inverter gate contributes its own output current (a maximum of around 2 mA) via the capacitors into the multiplier chain: because of this, the available output current will always be the same no matter how many times the voltage is multiplied (two times in this case).

The positive multiplier output of Fig. 3a includes the initial positive supply potential, and so generates three times this voltage less the three diode drops of 0V7 each. The negative multiplier of Fig. 3b, on the other hand, is referenced to the ground rail, giving -2 times the voltage (again less the diode drops).

As mentioned before, all the diodes are 1N4148s: the multiplier capacitors C2-4 are all non-critical and may be anything from 10nF to 100nF. C4 may be a polarised tantalum capacitor of a few microfarads to provide further smoothing. Any type of CMOS gate which can be connected as an inverter could be used, as well as all the standard inverters, though the 4049B hex inverter offers slightly more output current. It's also possible to use the 74C series types such as the 74C04 or 74C14. Pin-outs for these chips are given in Fig. 4 and not on any of the circuit diagrams, since they differ from type to type.

The oscillator implementation and its frequency are also non-critical; you could experiment with anything

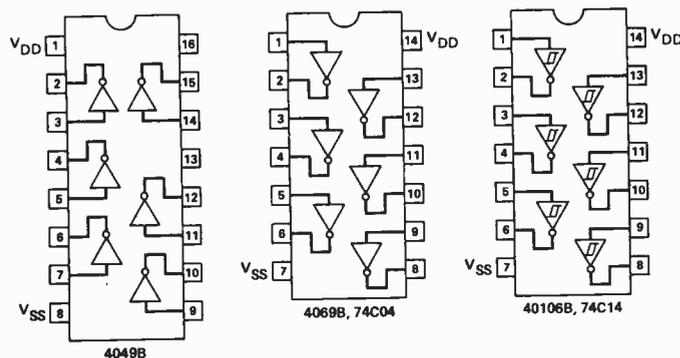


Fig. 4 Pin-outs for the standard hex inverter packages which may be used in the circuits given in this article.

from several kilohertz to several hundred kilohertz. Remember, though, that as the frequency decreases, the impedance for a given capacitor value will increase, so increasing the impedance of the multiplier output.

Table 1 lists out the different voltages you can expect from different chain lengths and supply voltages, based on the circuits of Fig. 3. The number of stages refers to the number of capacitors that are actively driven from inverter outputs. Using this table it becomes very easy to design a generator for any voltage requirement; the output voltage could be clamped to the exact level required using an ordinary zener diode regulator. But remember there isn't much current available, and as the output is loaded the voltage will decrease due to the supply impedance. The higher supply voltages will generally provide more output current.

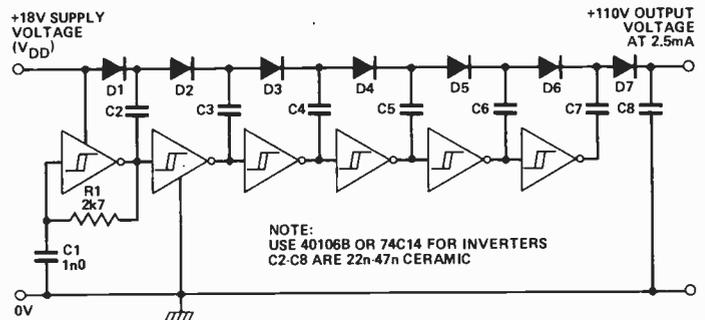


Fig. 5 A 110 V supply using one hex inverter IC.

As an example, Fig. 5 shows a longer multiplier designed to give 110 V and built using only one hex inverter IC, of the Schmitt trigger type (40106B). Using ceramic capacitors, this circuit could be built to a very small size.

Operating Principles

How do these multipliers actually work — the doubler circuit of Fig. 2 is straightforward, but what about the longer types? Voltage multiplier explanations are usually notoriously difficult to follow, let alone understand, and

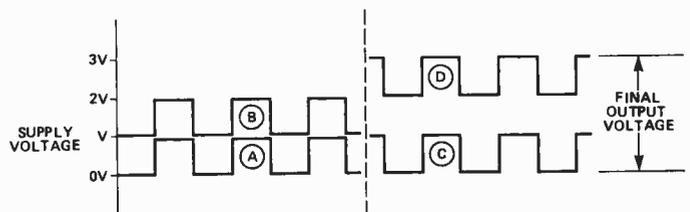


Fig. 6 Waveforms for a two-stage positive multiplier (idealised for clarity with diode drops ignored).

we shall therefore adopt a more graphic approach. If we measure the voltages at the lettered points in Fig. 3a and plot them against time, we get the waveforms shown in Fig. 6. These waveforms have been idealised for clarity — no account has been taken of the voltage drops due to the diodes in the circuit. From these it can be seen that the voltage across C2 (the difference between the waveforms A and B) is a constant 1V, where V is the supply voltage, while that across capacitor C3 (between points C and D) is 2V. We also know that the final output voltage across C4 is 3V. Moving down the chain towards the final output, then, we find that each capacitor maintains a DC charge which increases in integer multiples of the supply voltage. How so?

Consider capacitor C2 in Fig. 3a. At power-on it is discharged but when point A switches low, it charges up

		CMOS SUPPLY VOLTAGE					
		5V		10V		18V	
OUTPUT POLARITY	NO. OF STAGES	+	-	+	-	+	-
	1	8.6	3.6	18.6	8.6	34.6	16.6
	2	12.9	7.9	27.9	17.9	51.9	33.9
	3	17.2	12.2	37.2	27.2	69.2	51.2
	4	21.5	16.5	46.5	36.5	86.5	68.5
	5	25.8	20.8	55.8	45.8	103.8	85.8
	6	30.1	25.1	65.1	55.1	121.1	103.1
	7	34.4	29.4	74.4	64.4	138.4	120.4

Table relating supply voltage and number of stages to the (unloaded) output voltage, for positive and negative output multipliers based on the circuits of Figs. 3a and 3b and allowing 0V7 for each diode drop.

to the supply voltage via D1 (neglecting diode drops). Point B is therefore at supply voltage. When point A switches high, then, point B is raised to twice the supply voltage. Point C must be at zero volts since it is the inverse of point A, so current flows via D2 (which is now forward biased) from point B into C3 until C3 is charged up to the voltage at B (ie twice supply). The next clock pulse takes point A low, so point B is at supply less the voltage that has leaked into C3, and C2 is topped up via D1 again. Meanwhile point C has switched to supply voltage, so point D is now at three times supply and D2 is reverse biased, preventing C3 from discharging back into C2. C3 can discharge into C4 via D3, however, so the voltage across C4 is maintained at three times supply.

It should now be clear that no matter what the length of the multiplier, each capacitor in the chain maintains a steady DC charge which equals that on the previous one plus the supply voltage, and each capacitor tops up the next one in the chain on each alternate half-cycle. Figure

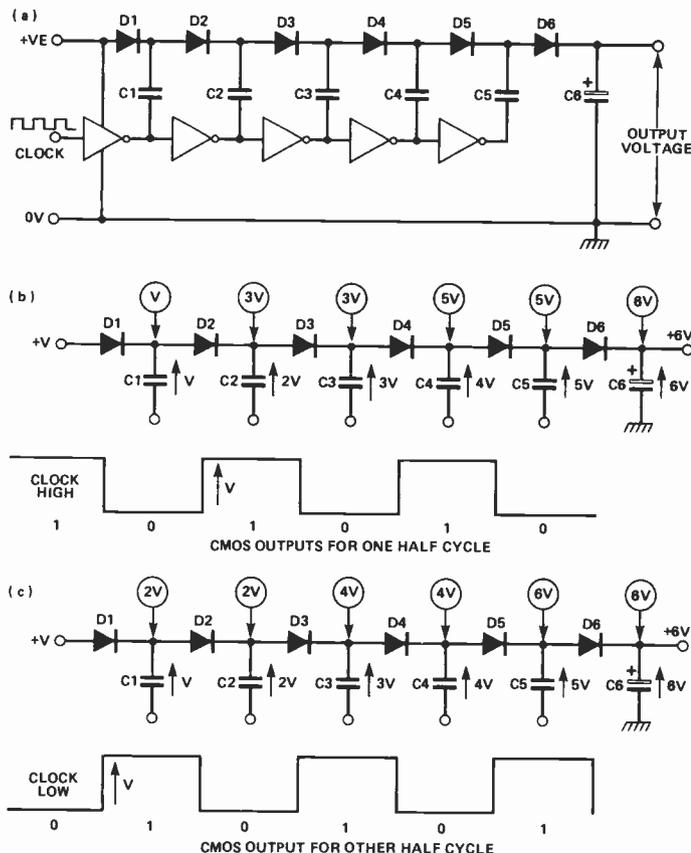


Fig. 7 How multiplier voltages accumulate down the chain.

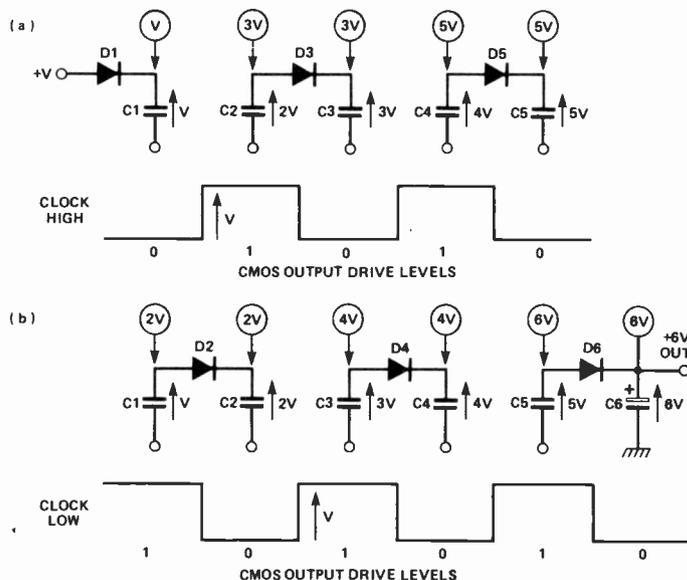


Fig. 8 Charging paths for an extended multiplier chain. The diagrams only show those diodes which are forward biased (conducting) during alternate half cycles of the drive waveform.

7a, for example, shows five stages of a multiplier chain driven by a square wave signal, while Figs. 7b and 7c use a waveform to represent the voltage levels at each capacitor node for each half of the cycle. The direction and voltage of the DC charges on each capacitor is also shown — remember these are constant as shown by the graph of Fig. 6.

Looking at C1 and C2 in Fig. 7b we can see that the positive (top) end of C1 will be at V volts (V is the supply voltage) while the positive end of C2 is at 3V volts (2V of its own, raised up a further V volts at the CMOS output). Diode D2 will therefore be reverse biased and effectively out of circuit. For similar reasons C3 will be at 3V volts (less that which has leaked away) and can therefore be charged up via D3 from C2. On the other half cycle in Fig. 7c, however, C3 will be raised up to 4V volts by the CMOS output, while C2 returns to 2V. So this time D3 is reverse biased and will not conduct. C1 is now raised to 2V and can thus charge C2 via D2. The conducting and non-conducting parts of the circuit for each half cycle are shown in Fig. 8, which gives a much clearer illustration of the diode charge pump action.

The Appliance Of Science

Figure 9 shows the circuit of a split-rail power supply that generates ± 10 V from a 5 V supply input. It could be

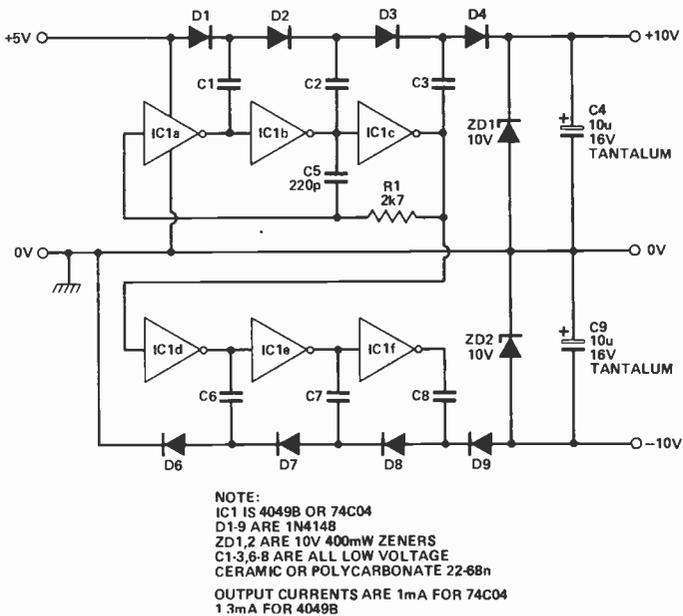


Fig. 9 A split-rail supply using one hex inverter package.

used to power low current op-amp circuitry and other CMOS circuits from a standard TTL power supply. Again, only one hex inverter pack is required and we recommend that the 4049B is used with its slightly higher output current capability. The circuit takes advantage of the three cascaded inverters that drive the positive multiplier chain, by also using them to form a 'ring-of-three' oscillator. The multiplier chain is therefore self-oscillating!

The positive side in turn drives the negative chain of IC1d, e and f. From Table 1 we would expect the available output voltages to be $+17V_2$ and $-12V_2$, which are then clamped to the $\pm 10V$ levels by zeners ZD1 and ZD2. Series limiting resistors for the zener diodes are unnecessary due to the current-limited output of the multiplier.

Figure 10 shows a variation on the previous circuit's positive multiplier section, using all six inverters to provide more output current at $\pm 10V$. To achieve higher output currents, simply parallel the CMOS gates that drive the capacitor chain: the available currents will add together due to the nature of the CMOS output FETs. This technique is useful for CMOS operating at low supply voltages.

Figure 11 gives the circuit for a 24-stage positive multiplier to generate a high-voltage, low-current supply. This could be used for a solid state 'megger' (high resistance meter and insulation tester). The 24 stages can be achieved using only four hex inverter packs, and will provide 433 V from an 18 V supply. This circuit illustrates the fact that the inverters may be wired up in any fashion so long as alternate capacitors receive opposite phases of the square wave.

The circuit will deliver at least 2 mA at 430 V! — not lethal but pretty painful, so be careful. We suggest the addition of a 1M Ω series resistor in the positive supply lead to limit the available current to about 400 μ A. A 100 μ A meter would provide suitable megohm readings.

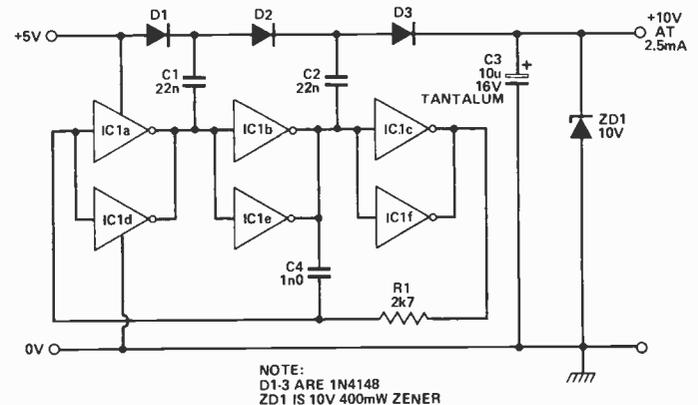


Fig. 10 Paralleling inverter stages to give a higher current supply.



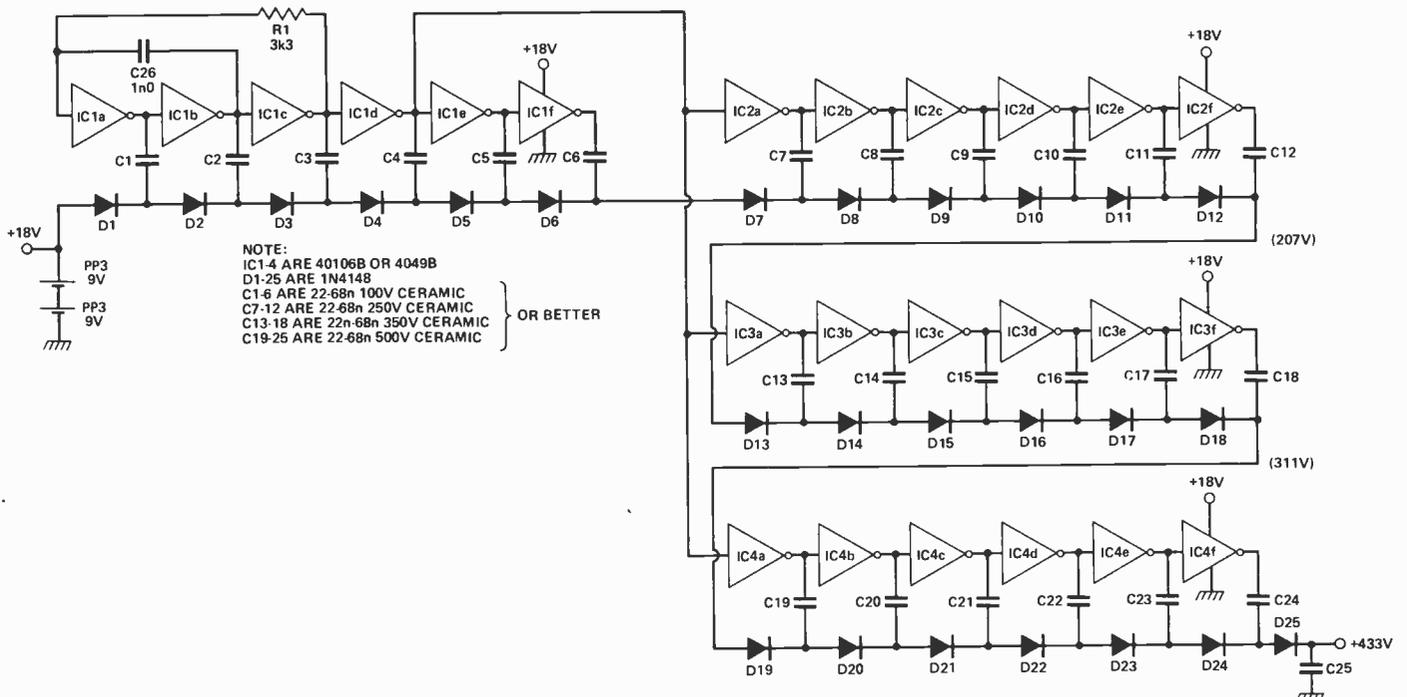


Fig. 11 A 433 V generator using a 24-stage positive multiplier and an 18 V supply.

SC110A FULLY PORTABLE OSCILLOSCOPE

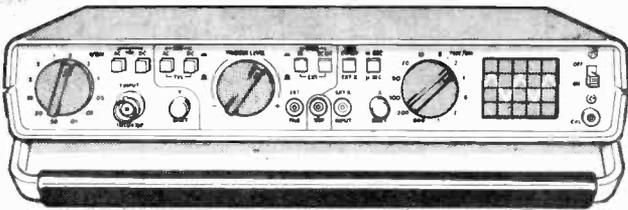

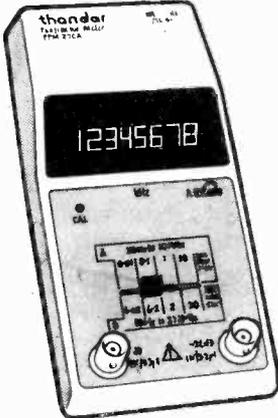The new THANDAR SC110A represents a break through in Oscilloscope development. The SC110A is only 2" thick and weighs under 2 lbs yet it retains the standard features of a bench oscilloscope.



FULL-SIZED PERFORMANCE

- 10MHz band width
 - 10mV per div. sensitivity
 - Full trigger facilities are provided including bright line and auto, with T.V. line and frame filtering
 - RUNS ON ORDINARY HP11 (four) batteries or rechargeables
 - Basic price — £170 UK Post free
- Optional extras*
AC Adaptor £5.69; Rechargeable batteries £8.63; X1 Probe £8.05; X10 Probe £9.20; X1/X10 Switched Probe £10.90; Carry Case £8.86.

PFM200A FREQUENCY METER

- Pocket size ● 8-Digit LED display ● Frequency range 20Hz-200MHz ● Resolution 0.1Hz ● Sensitivity typically 10mV rms
 - Timebase accuracy 2ppm ● Battery life 10 hours ● Frequency: 2 ranges, 4 gate times ● Price £77.50 UK Post free
- Optional extras* — AC Adaptor £5.69

LARGE S.A.E. Brings details of: Oscilloscope, Frequency Meters, Signal Generators, Function Generators, Pulse Generators, Analogue and Digital Multimeters, Digital Thermometer, C.R.T. Tester, Logic Analyser etc.

All prices include VAT. Official orders welcome. Mail order only, or callers by prior appointment. Barclaycard/Access welcome. Cash/cheque, etc., with order. Government and Educational Establishments official orders welcome.

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY
Tel: Southend 527672



RECONDITIONED TELEPHONES

Push Button Trilphones £15 + £1.80 P&P. 2 for £28 + £2.50
Push Button 746 £13.50 + £1.80. 2 for £25 + £2.50
Recent Style Dial Phones £4.75 + £1.80. 2 for £9 + £2.50. 5 for £20 + £5
Seconds (in good working order)
Class A (not too bad) £3.50 + £1.80. 5 for £15 + £5
Class B (grotty) £2.25 + £1.80. 5 for £9 + £5

Desk-top Ten Way Manual Exchange (key & lamp unit) £8 + £1.80 P&P

Older style black telephones, £3.00 as above. Our leaflet explains how to use G.P.O. phones in home intercom systems.

5 Digit Counters 48V coil. Non resetable 75p

UNISELECTORS. 50v, 4 Bank + Homing Bank, 25 way £3.50


P.O. TYPE 4 pole jack plug with moulded lead and panel socket. ONLY £1

Various stabilised power supplies available — Excellent prices send for details.

FREE on request — Leaflet 'D.I.Y. Telephone Systems and Automatic Exchange Design'.

LOW-COST, RUGGED TEMPERATURE CONTROL

HIGH QUALITY

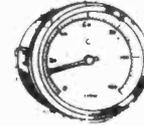

TEMP. GAUGE 0° — 120°C
Remote sensor on 38" capillary, panel mounting dial 55mm. dia.

ONLY £2.50

16A 240V RANCO THERMOSTAT

Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. £2.30, including control knob

RANCO THERMAL CUT-OUT 100°C

15A 240V. Sensing coil on 41in. capillary panel mounting with reset button £1.20

BUY ONE EACH OF ABOVE FOR £5.50

LIGHT DEPENDENT RESISTORS in plastic housing with window, heavy-duty lead. Similar to ORP 61. You normally pay well over double for resistor alone. Only 30p or £2.35 for 10.

GEARED Synchronous motor, 8 r.p.m., 240V A.C. 3 Watt £2.

SOLENOID GAS VALVE. 240V A.C. 5 P.S.I. suitable for non-corrosive fluids. £2.20

BULGIN 3 pin free plug & panel socket, 2A 240V 50p

DIAL-OUT WITH YOUR COMPUTER. P.C.B. with custom chip, drive circuits and high-speed relays enables your computer to dial-out (with suitable interface). Ex-equipment. Tested. £12 with explanatory notes.




L.E.M. SERVICES
22 Emscote Road,
Warwick,
Warwickshire

ADD 50p P&P
ORDERS OVER
£7.50 POST FREE
unless stated otherwise

ALL ITEMS — MONEY BACK IF NOT DELIGHTED.

MODULES FOR SECURITY & MEASUREMENT

INTRUDER ALARM CONTROL UNIT CA 1250

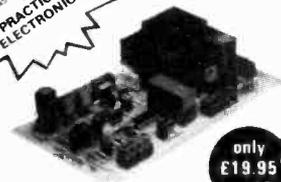

only
£19.95
+ VAT

This exciting new module offers all the possible features likely to be required when building an intruder alarm system. Whether used with only 1 or 2 magnetic switches or in conjunction with several ultrasonic alarm modules or infra-red units, a really effective system can be constructed at a fraction of the cost of comparable ready-made units. Supplied with a fully explanatory Data Sheet that makes installation straight forward, the module is fully tested and guaranteed.

*available in kit form £16.95 + VAT

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage for external units
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for switching external loads
- Test loop facility

DIGITAL VOLTMETER MODULE DVM 314

Fully built & tested



only
£11.95
+ VAT

- Positive & negative voltage with an \pm SD of 999mV which is easily extended
- Requires only single supply 7-12V
- High overall accuracy 0.1% + 1 digit
- Large bright 0.43" LED displays
- Supplied with full applications data

With this fully built and calibrated module a wide range of accurate equipment such as multimeters, thermometers, battery indicators etc. can be constructed at a fraction of the cost of ready-made units. Full details are supplied for extending the voltage range, measuring current, resistance and temperature. Fully guaranteed. The unit has been supplied to electricity authorities, Government departments, etc.

Temperature Measurement Kit DT.10

£2.25 + VAT

Using the I.C. probe supplied, this kit provides a linear output of 10mV/°C over the temperature range from 10°C to +100°C. The unit is ideal for use in conjunction with the DVM module providing an accurate digital thermometer.

Power Supply PS.209


£4.95 + VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V, 250mA each. The unit is ideally suited for operating the DVM at Temperature Measurement module.

ULTRASONIC ALARM MODULE US 4012

Fully built & tested

only
£10.95
+ VAT

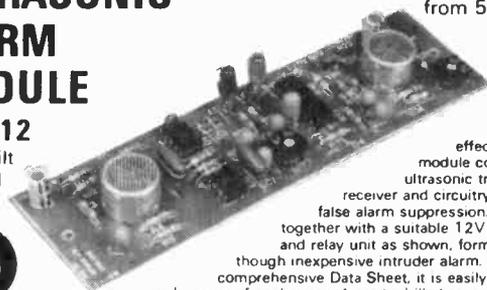

Adjustable range from 5ft. to 25ft.

A really effective fully built module containing both ultrasonic transmitter and receiver and circuitry for providing false alarm suppression. This module, together with a suitable 12V power supply and relay unit as shown, forms an effective though inexpensive intruder alarm. Supplied with comprehensive Data Sheet, it is easily mounted in a wide range of enclosures. A ready-drilled case and necessary hardware is available below.

Power Supply & Relay Units PS 4012

£4.25 + VAT

Provides a stabilised 12V output and relay with 3A contacts. The unit is designed to operate one or two of the above ultrasonic units. Fully built and tested.

Hardware Kit HW 4012

£4.25 + VAT

A suitable ready-drilled case with the various mounting pillars, mains switch socket and nuts and bolts. Designed to house the ultrasonic alarm module together with its power supply. Size: 153mm x 120mm x 45mm.

Siren Module SL 157

£2.95 + VAT

Produces a loud and penetrating sliding tone operating from 9-15V. Capable of driving 2 off 8 ohm speakers to SPL of 110db at 2M. Contains an inhibit facility for use with shop lifting loops etc. or other break to activate circuits.

* ACCESSORIES *

- 3-position Key Switch for use with CA 1250 supplied with 2 keys £3.43
- Magnetic switch (with magnet) £1.17
- 5" Horn speaker for use with CA1250 and SL157 £4.95

Add VAT & 50p post and packing to all orders.

Shop hours 9.00 - 5.30 p.m.

(Wed. 9.00 - 1.00 p.m.)

Units on demonstration - callers

welcome, S.A.E. with all enquiries.

RISCOMP LIMITED

Dept: ET115

21 Duke Street,

Princes Risborough, Bucks.

Princes Risborough 1084 441 6326

BBC Micro Computer

Please phone for availability



BBC Model A **£299**
 BBC Model B **£399**
 including VAT plus £8 carr.
 Model A to Model B
 Fitting charge **£15**
 Individual upgrades
 also available

WORD PROCESSOR 'VIEW'
 16K ROM **£52**
TELETEXT ADAPTOR
£195.00

PRESTEL ADAPTOR
£90.00
2nd PROCESSOR 6502 £170
2nd PROCESSOR Z80 £290

FLOPPY DISC INTERFACE
 Incl. 1.0 operating system
£95 + £20 installation

Phone or send for our BBC leaflet

BBC FLOPPY DISC DRIVES
 Single drive 5 1/4" 100K **£235 + £6 carr.**
 Dual drive 5 1/4" 800K **£799 + £8 carr.**

BBC COMPATIBLE DRIVES
 These are drives with TEAC FD50 mechanism
 and are complete with power supply
SINGLE: 100K £190; 200K £260; 400K £340
DUAL: 200K £360; 400K £490; 800K £610

OFFICIAL BBC DEALER

ACORN SOFT/BBC SOFT/GAMES PADDLES IN STOCK

CASSETTE RECORDER

Ferguson 3T07 **£26.50 & £1.50 carr**
 Cassette Leads **£3.50**
 Computer Grade Cassettes
£0.50 each £4.50 for 10 & £1 carr

MONITORS


MICROVITEC 1431 14" Colour Monitor **£249 + £8 carr.**
 MICROVITEC 2031 20" Colour Monitor **£319 + £8 carr.**
 SANYO 14" Colour Monitor RGB **£255 + £8 carr.**
 Lead for SANYO RGB **£10**
 SANYO 12" Hi Res Green Monitor **£99 + £6 carr.**

ACORN ATOM

Basic Built **£135** Expanded **£175**
 (carr £3 per unit)
 Atom Disc Pack **£299 + £6 carr**
 3A 5V Regulated PSU **£26 + £2 carr.**
 Phone or send for our BBC Atom list.

NEC PC 8023 BE-C

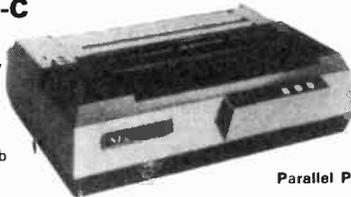Features include:
 80 cols 100CPS,
 Bi-Directional, Logic seeking,
 Proportional Spacing,
 Forward & Reverse Line
 Feed, Hi-Res and Block
 Graphics, International
 and Greek characters,
 Auto-Underline, Super & Sub
 Scripts, Friction & Tractor,
 2K Buffer, Cartridge Ribbon.



£320 + £8 carr.

PRINTERS

SEIKOSHA GP 100A


80 Cols 30 CPS
 Full ASCII e GRAPHICS
 10" Wide paper

Now only **£190 + £6 carr.**
 Ask for details on GP 250A

Parallel Printer lead for BBC/Atom to most printers **£13.50**
 Variety of interfaces, ribbons in stock
 2,000 fan fold sheets 9 1/2" x 11" **£13.50 + £3 p & p**

EPSON MX 80 and 100F/T3

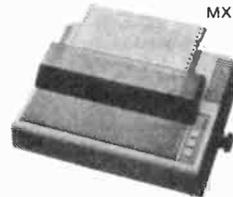MX 80 80CPS 80 cols
 MX 100 100CPS 136 cols
 Logic Seeking, Bi-
 directional, Bit Image
 Printing, 9 x 9 Matrix
 Logic Seeking, Bi-directional,
 Bit Image Printing, 9 x 9
 Matrix, Auto Underline,
 Tractor and Friction Feed,
 Centronics & Bit Parallel
 Interface as standard.



MX 80 F/T3 **£325**
 MX 100 F/T3 **£430**
 (£8 Carr/Printer)

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calender receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided. See July/August ETI for details. Complete Kit **£120 + £2.00 p&p**


MICROTIMER

6502 Based Programmeable clock timer with
 * 224 switching times/week cycle
 * 24 hour 7 day timer
 * 4 independent switch outputs directly interfacing to thyristor/triacs
 * 6 digit 7 seg. displays to indicate real time, ON/OFF and Reset times
 * Output to drive day of week switch and status LEDs.
 Full details on request. Price for kit **£57.00**

I.D. CONNECTORS		CONNECTOR SYSTEMS		RIBBON CABLE (Grey)	
(Speedblock Type)		JUMP LEADS		AMPHENOL CONNECTORS	
No of Header	Recep- Edge	4in Ribbon Cable with headers	14 pin 16 pin 24 pin 40 pin	36 way Solder Type Plug (centronix type)	550p
ways Plug	Conn	1 end 145p 165p 240p 380p	2 ends 210p 230p 345p 54Cp	36 way Solder Socket (centronix type)	550p
10	90p 90p 200p	24in Ribbon Cable with sockets	20 pin 28 pin 34 pin 40 pin	36 way IDC Plug (centronix type)	500p
20	145p 125p 240p	1 end 160p 210p 270p 300p	2 ends 290p 385p 490p 540p	24 way Solder Plug (IEEE type)	500p
26	175p 150p 300p	24in Ribbon Cable with D. Conn	25 way Male 500p Female 550p	24 way Solder Socket	500p
34	200p 160p 380p			24 way IDC Plug	485p
49	220p 190p 550p				
50	235p 200p 600p				
D-CONNECTORS		EURO CONNECTORS		EDGE CONNECTORS	
9 way 15 way 25 way 37 way	MALE	RS232 CONNS (25 way D)	(Indirect Edge Conn)	0.1in 0.156in	
Solder	90p 130p 160p 250p	24" Single end Male £5.50	DIN STD Plug Skt	2x18 way	140p
Angled	160p 230p 265p 425p	24" Single end Female £6.00	41617 21 way 170p 170p	2x22 way	200p 170p
	FEMALE	24" Female, Female £11.00	41617 31 way 180p 180p	2x25 way	210p
Solder	110p 160p 210p 350p	24" Male-Male £10.00	41612 2 x 32 way 250p 320p	2x25 way	225p 220p
Angled	175p 240p 310p 500p	24" Male-Female £11.50	41612 2 x 32 way 325p 375p	2x43 way	260p
Hood	95p 95p 95p 125p		41612 3x32 way 275p 380p	2x43 way	395p
			41612 3x32 way 400p	2x50 way	—
			2x32 way zidc a + c 525p	1x77 way	700p
			(for 2x32 way specify a + b or a + c)	S100 Conn	800p

MICRODOCTOR

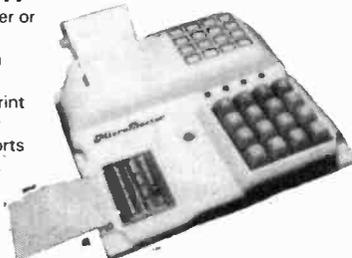This is not a logic analyser or an oscilloscope. It tests a microsystem and gives a printed reprint on RAM, ROM and I/O — it will print memory map, search for code, check dataline shorts and operates peripherals. Microdoctor complete with PSU, Printer, probe cable and two configuration boards. **£295.**



SOFTY II INTELLIGENT PROGRAMMER

The complete micro processor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most +5v Eproms. Softy II complete with PSU, TV Lead and Romulator lead **£169**

SPECIAL OFFER

2114L 80p
 2716 (+5v) 250p
 2532 350p
 4116-2 80p
 4164-2 450p
 6116P-3 350p

BOOKS (No VAT p&p £1)

CMOS Cook Book **£7.75**
 CRT Controller H/Book **£7.95**
 Programming the Z80 **£11.50**
 Z80 Microcomp. handbook **£6.95**
 Programming the 6502 **£10.25**
 6502 Assy. Lang. **£12.10**
 6502 Applications **£10.20**
 6502 Software Design **£9.05**
 6502 Games **£10.52**
 Large selection of databooks, inter-
 facing books, books on BBC, etc in
 stock. As for our list.

UV ERASERS

UVI8 up to 6 Eproms **£47.50**
 UVIT with Timer **£60.00**
 UV140 up to 14 Eproms **£61.50**
 UV141 with Timer **£78.00**
 (Carr £2/eraser)
 All erasers are fitted with
 mains switches and safety
 interlocks

TRAINER KITS

6502 Junior Computer **£85.00**
 6802 Nancomp I **£80.00**
 6809 Nancomp II **£80.00**
 1802 Micro Trainer **£64**
 E80 Manta **£115**
 Z80 Menta **£115**
 (fully built and documented)
 Full details on request

PLEASE SEND SAE FOR PRICE LIST

74 SERIES

Table listing 74 series components including part numbers, descriptions, and prices.

74LS SERIES

Table listing 74LS series components including part numbers, descriptions, and prices.

74S SERIES

Table listing 74S series components including part numbers, descriptions, and prices.

4000 CMOS

Table listing 4000 CMOS components including part numbers, descriptions, and prices.

COUNTERS

Table listing counter components including part numbers, descriptions, and prices.

LINEAR ICs

Table listing linear IC components including part numbers, descriptions, and prices.

VOLTAGE REGULATORS

Table listing voltage regulator components including part numbers, descriptions, and prices.

OTHER REGULATORS

Table listing other regulator components including part numbers, descriptions, and prices.

OPTO ELECTRONICS

Table listing opto electronics components including part numbers, descriptions, and prices.

OPTO ISOLATORS

Table listing opto isolator components including part numbers, descriptions, and prices.

LEDS

Table listing LED components including part numbers, descriptions, and prices.

DISPLAYS

Table listing display components including part numbers, descriptions, and prices.

DRIVERS

Table listing driver components including part numbers, descriptions, and prices.

COMPUTER COMPONENTS

Table listing computer components including part numbers, descriptions, and prices.

CPUs

Table listing CPU components including part numbers, descriptions, and prices.

RAMs

Table listing RAM components including part numbers, descriptions, and prices.

SUPPORT DEVICES

Table listing support device components including part numbers, descriptions, and prices.

ROMs/PROMs

Table listing ROM/PROM components including part numbers, descriptions, and prices.

EPROMs

Table listing EPROM components including part numbers, descriptions, and prices.

LOW PROFILE SOCKETS BY TI

Table listing low profile sockets by TI including part numbers, descriptions, and prices.

WIRE WRAP SOCKETS BY TI

Table listing wire wrap sockets by TI including part numbers, descriptions, and prices.

MODULATORS

Table listing modulator components including part numbers, descriptions, and prices.

CRYSTALS

Table listing crystal components including part numbers, descriptions, and prices.

INTERFACE ICs

Table listing interface IC components including part numbers, descriptions, and prices.

CHARACTER GENERATORS

Table listing character generator components including part numbers, descriptions, and prices.

KEYBOARD ENCODERS

Table listing keyboard encoder components including part numbers, descriptions, and prices.

BAUD RATE GENERATORS

Table listing baud rate generator components including part numbers, descriptions, and prices.

ZIF SKTs

Table listing ZIF socket components including part numbers, descriptions, and prices.

REAL TIME CLOCK

Table listing real time clock components including part numbers, descriptions, and prices.

TRIACS PLASTIC

Table listing triac plastic components including part numbers, descriptions, and prices.

DIODES

Table listing diode components including part numbers, descriptions, and prices.

THYRISTORS

Table listing thyristor components including part numbers, descriptions, and prices.

BRIDGE RECTIFIERS

Table listing bridge rectifier components including part numbers, descriptions, and prices.

PCB MOUNTING RELAYS

Table listing PCB mounting relay components including part numbers, descriptions, and prices.

TECHNOMATIC LTD. PLEASE ADD 40p p&p & 15% VAT (Export: no VAT, p&p at Cost)

MAIL ORDERS TO: 17 BURNLEY ROAD, LONDON NW10 1ED. Orders from Government Dept. & Colleges etc. welcome.

SHOPS AT: 17 BURNLEY ROAD, LONDON NW10. Detailed Price List on request.

(Tel: 01-452 1500, 01-450 6597, Telex: 922800). Stock items are normally by return of post.

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RKO5, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 news- letter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £8.95
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. **OUR PRICE ONLY £12.95 complete with data.**
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!
7 days per week 84 hrs. per day
01-683 1133

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available LESS PSU with internal dim. 19" w, 16" d, 10.5" h, £19.95". Carriage & insurance £9.50.

8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality!! The 7100 single sided and 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB (7100) 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMANS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. Carriage and insurance £9.75.

7100 Single sided £225.00 + Carr. 7200 Double sided £295.00 + Carr.
Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

VIDEO MONITORS

MOTOROLA 9" open chassis monitor. Standard 240 v AC with composite 75 ohm video input, bandwidth in excess of 18 mhz. Monitors are ex equipment and although unguaranteed they are all tested prior to despatch, and have no visible burns on the screens. Dim approx 9" x 9" x 9". Supplied complete with mains and input lead. Ideal ZX81 etc. or giving the tele back to the family!! Black and white phosphor. **£35.00 + £9.00 Carr.**


12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync. and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". **ONLY £199.00 PLUS £9.50 CARR.**

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499 + VAT

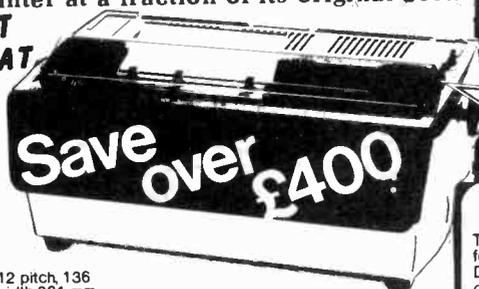

Made to the very highest spec. the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro processor electronics offer full DIABLO/QUIME compatibility plus Bi directional printing, 10 or 12 pitch, 136 or 163 chars per line, full width 381 mm friction or single sheet paper, - order now or call sales office for more information and print sample. Please specify RS232 or CENTRONICS interface. Supplied complete with FREE dust cover and daisy wheel. Optional extras: RS232 data cable £10.00 - Tech. manual £7.50. Carriage & Ins. (UK) £12.50. - Tractor feed option £120.00

TELETYPE ASR33 I/O TERMINALS

Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT. KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator. Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah. will deliver over 300 amps on short circuit!! Brand new at only **£2.95**
SAFT VR2C size 'C' 1.2v 2 ah. nickel cadmium **£1.50** each 10 for **£11.50**

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only **£75.00**
MODEM 28/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. **£85.00**
MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link. 75 baud transmit - 1200 baud receive. Auto answer. **£130.00**
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. **£130.00**
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. **£130.00**
Carriage. 13A £4.50. 28/C & 20 £9.50.
For more details contact sales office.

D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO unit all silicon electronics. Outputs give +5v @ 2 amps, +12v @ 800 ma. -12v @ 800 ma. +24v @ 350 ma. 5v @ 50 ma. floating. Dim 160 x 120 x 350 mm. All outputs fully regulated and short circuit proof. Removed from working equipment, but untested. Complete with circuit. Transformer guaranteed. Only **£14.50** + £2.50 pp.
CUSTOM POWER CO55 5v @ 3 amp. Very compact unit dim. approx 60 x 90 x 190 mm. Semi open chassis, full crowbar overvoltage protection. Tested Ex Equipment. **£11.95** + pp £1.25
MINI SYSTEM PSU Ex equipment unit ideal for the small micro. Outputs give 5v @ 3 amps. +12v @ 1 amp and -12v @ 300 ma. Crowbar overvoltage protection and current limit. Fully tested. Dim 70 x 165 x 320 mm. Complete with Circuit only **£12.95** + £2.00 pp.
PERIPHERAL SYSTEM SUPPLY. Fully cased unit supplied in a Brand new or little used condition. Outputs give 5v @ 11 amps, "+" 15-17v @ 8 amps, "-" 15-17v @ 8 amps and "+" 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested, with circuit. **£55.00** + £8.50 carr.
MAIN FRAME SUPPLY. A real beefy unit designed for MINI or MAINFRAME use outputs give 5 volts @ 50 amps. +12v @ 5 amps. -12v @ 10 amps. All output are fully regulated with crowbar overvoltage protection on the 5v output. Supplied with circuit and tested. Ex-Equip. 110v AC input. Only **£49.95** + carr. £10.50.

66% DISCOUNT ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you play plus we always include something from our ads. For unbeatable value!! Sold by weight.

2.5kls **£4.25** + pp **£1.25** 5kls **£5.90** + pp **£1.80**
10kls **£10.25** + pp **£2.25** 20kls **£17.50** + pp **£4.75**

ALL PRICES PLUS VAT

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed. **50+ £2.95 100+ £5.15**
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. **100+ £6.90 200+ £12.30 200+ £19.50**

OLIVETTI TE300

REDUCED TO CLEAR
Complete input output terminal with integral 8 hole paper tape punch and reader. Unit operates at 150 baud in standard ASCII. Ideal as a cheap printer for a MICRO etc. 120 columns. Serial data i/o. Supplied complete with data, untested, unguaranteed **£65.00** + £11.50 carr.

DISPLAY ELECTRONICS

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government depts, Schools, Universities and established companies **£20.00** Where post and packing not indicated please ADD **80p** + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
01-689 7702 - 01-689 6800 Telex 27924



REAL TIME CLOCK/CALENDAR

It seems strange that many microcomputers cannot tell the time of day or the date when such a facility can be so useful to the programmer. Never fear, ETI is here, with a simple peripheral for 6502-based machines. Design by M.D. Bedford

Programmers who are familiar with mainframe or minicomputers will probably be aware that it is generally possible to access the actual time and date from within a program. Such a facility is known as a real time clock and is often not available on the more modest microcomputers. It is not difficult to see that a real time clock would enhance any system — applications range from control programs, to the determination of the elapsed time between occurrences, to giving listings that professional touch by using the time and date in the header.

Two approaches are possible for the implementation of a real time clock — software or hardware. Traditionally, a software solution has been used in which a hardware interrupt is generated at regular intervals, probably every 20 milliseconds, these being counted by the interrupt handling routine which then calculates the time and date. Such a system obviously requires initialising and would prompt the user for the time and

date each time the computer was switched on (*our own word processor uses this system — Ed*). Quite apart from the possible inconvenience, this method is probably unsuitable for most microcomputer users as it would require modification of the monitor program in ROM to prompt for the time and date. On the other hand, it is possible to devise a hardware alternative with battery back-up which is transparent to the system when not being accessed and doesn't lose the time and date on power-down of the main system.

For these reasons a hardware approach is presented here. The design is primarily intended for the Tangerine Microtan system, the PCB given here being of such a size that it will plug directly into the system rack. From an electronic point of view, however, there is no reason why the board may not be used with any 6502-based computer.

Functional Description


The real time clock, which may be configured to occupy any 16-byte block within the Tangerine

I/O area, has 16 registers as specified in Table 1. It will be noticed that 12 of the registers are used to store the time and date, two registers being used to store (in BCD format) any number which may take a value greater than nine. For example, the value of the minutes is calculated as $(10 \times \text{REGISTER 5}) + \text{REGISTER 4}$. Of these 12 registers, registers 1-3 are read-only, these 'seconds' registers being automatically set to zero on starting the clock.

Each time the clock is updated, ie every tenth of a second, a flip-flop is set, writing a value of 15 to all the readable registers to indicate that an update has taken place since the last read. Reading a register under these conditions resets the flip-flop so that a further read will produce a valid result.

This board may also be used to generate interrupts at regular intervals, this function being controlled by register 15 as described in Table 2. Switch SW2 may be used to disable interrupts, a facility which is especially useful in view of the fact that this board does not reset at switch-on.

The remaining registers are write-only and have various control functions. Register 0 should have a value of 0 written to it to select non-test mode for normal operation. A value of 1, 2, 4 or 8 should be written into register 13 to indicate leap year, leap year + 1, leap year + 2, or leap year + 3 respectively. A value of 1 written to register 14 will start the clock, whereas a value of 0 will stop it. Switch SW1 gives the board write-protection, hence obviating the accidental overwriting of the time and date once initialised. This facility does not affect register 15 so that interrupts may still be selected when the

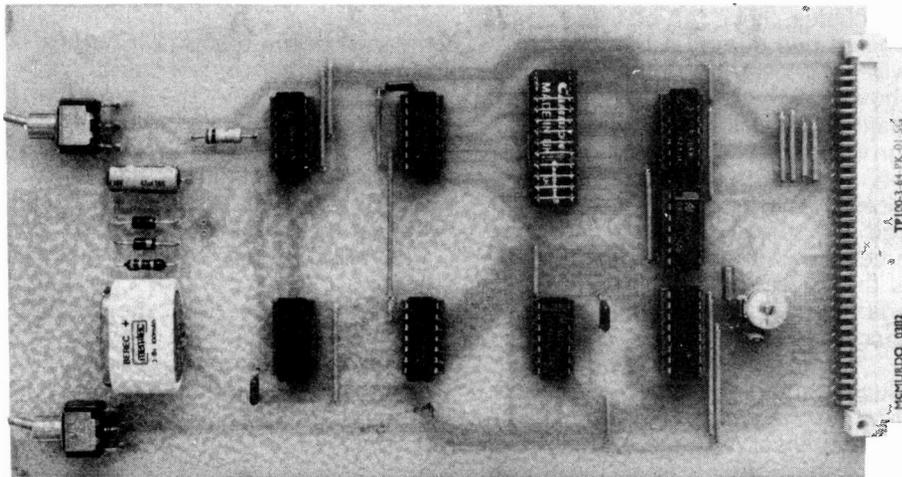

A bird's eye view of the completed project.

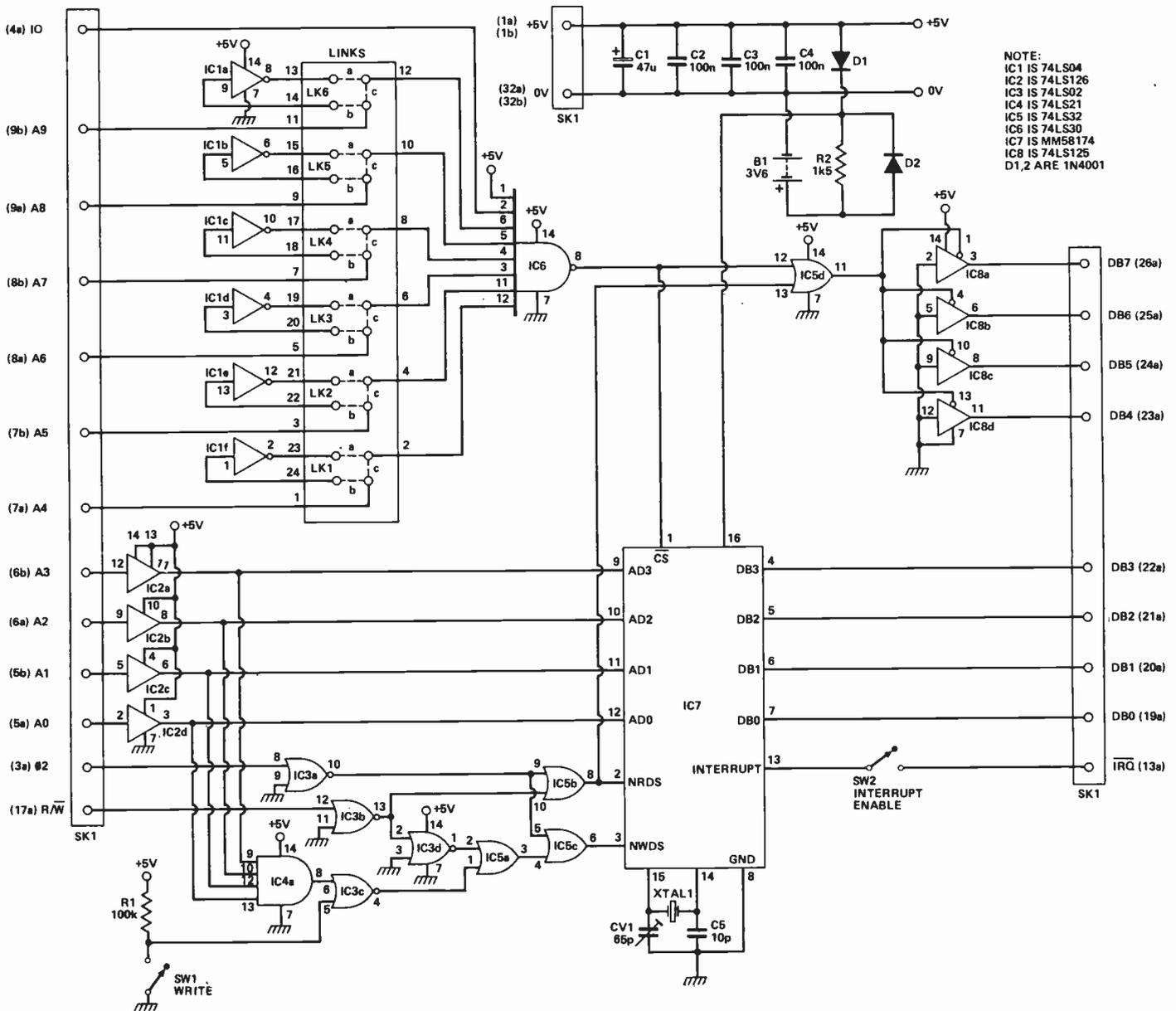


Fig. 1-Circuit diagram of the real time clock/calendar. Non-Microtan owners will find a circuit to generate the IO signal in last month's ETI.

board is write-protected. Both switches are mounted so that 'down' selects the enabling of the appropriate function.

The battery back-up facility allows data to be retained when the computer is not switched on, hence avoiding the need to initialise the clock at power-on. The time and date will be retained for about three months with a fully charged battery and a minimum of one hours use every nine days will ensure that the battery remains in a state of full charge.

Construction

If the printed circuit board layout presented here is adhered to,

construction should present no difficulties. Since the board is of a single-sided design, a number of wire links need to be fitted as shown on the component layout diagram. Sockets should be used throughout for the integrated circuits. It should be noted that the MM58174 IC is fabricated in CMOS and accordingly the usual precautions of not touching the pins of the IC and not soldering the board while the IC is in its socket should be adhered to.

We suggest that DIL headers plugged into DIL sockets should be used for the wiring of the selectable address links. A 16-pin and an 8-pin socket should be used to make up the 24-pin by 0.3" socket used for

these links. The required start address should be set up as follows: the start of the board is 16* (the binary number represented by links 1-6) from the start of the Tangerine I/O area, where link 1 is the least significant bit. Making links a and b gives a 0, making link c gives a 1. So, for example, the following links will set up the board to start at 48 bytes from the start of the I/O area: link 6 ab, link 5 ab, link 4 ab, link 3 ab, link 2 c, link 1 c. If the board is to be constructed to a different layout to suit non-Tangerine systems, the only points to be borne in mind are that C2, C3 and C4 should be well distributed around the board and that XTAL1, CV1 and C5 should be mounted close to IC7.

PROJECT: Real Time Clock

HOW IT WORKS

The heart of the circuit, IC7, is the MM58174 real time clock which reads and writes four bits of data onto DB0-DB3. Although not absolutely necessary (since the top four bits could be masked out by programming), a neat hardware solution is provided by the use of IC8 to zero DB4-DB7 during read operations. The circuitry comprising IC1, IC6 and the DIL links gives a chip select for IC7 and IC8 when an address in the range selected by the links is accessed.

Since the MM58174 is specifically intended to interface with microprocessors such as the 8080 or Z80, the circuitry comprising IC3 and most of IC5 is required to generate the NRDS and NWDS signals from the 6502 R/W and $\phi 2$. Hence write protection

may be provided by blocking NWDS when SW1 is in the closed position. IC4 is used to detect when register 15 is being addressed (A0-A3 all high) and under these circumstances overrides the write protection.

IC2 is to buffer A0-A3 — in fact, the whole circuit is designed to present no more than one TTL load to any bussed signal.

D1 is used to pass the +5 V supply to IC7 when it is present, the battery being trickle-charged through R2 under these conditions. When the +5 V supply is not present, D1 prevents the battery from discharging through the power supply and IC7 is supplied with sufficient voltage to operate in standby mode via D2.

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)	
R1	100k
R2	1k5
Capacitors	
C1	47u 16 V axial electrolytic
C2-4	100n disc ceramic
C5	10p ceramic plate
CV1	5-65p trimmer
Semiconductors	
IC1	74LS04
IC2	74LS126
IC3	74LS02
IC4	74LS21
IC5	74LS32
IC6	74LS30
IC7	MM58174 (see Buylines)
IC8	74LS125
D1,2	1N4001
Miscellaneous	
SW1,2	SPCO PCB-mounting toggle switches (see Buylines)
B1	3V6 PCB-mounting Nicad battery (see Buylines)
SK1	2 x 32 way A + B DIN Euro connector (male, angled pins) — see Buylines
PCB (see Buylines); DIL sockets to suit.	

TABLE 1

List of Real Time Clock Registers

Reg No	Function	Access Mode
0	test	write
1	tenths of seconds	read
2	units of seconds	read
3	tens of seconds	read
4	units of minutes	read/write
5	tens of minutes	read/write
6	units of hours	read/write
7	tens of hours	read/write
8	units of days	read/write
9	tens of days	read/write
10	day of week	read/write
11	units of months	read/write
12	tens of months	read/write
13	year status	write
14	start/stop	write
15	interrupt	read/write

TABLE 2

DESCRIPTION OF INTERRUPT MODES

Function	Value in Register 15
no interrupts	0 or 8
single interrupt after 60 seconds	4
repeated interrupts at 60 second intervals	12
single interrupt after 5 seconds	2
repeated interrupts at 5 second intervals	10
single interrupt after 0.5 seconds	1
repeated interrupts at 0.5 second intervals	9


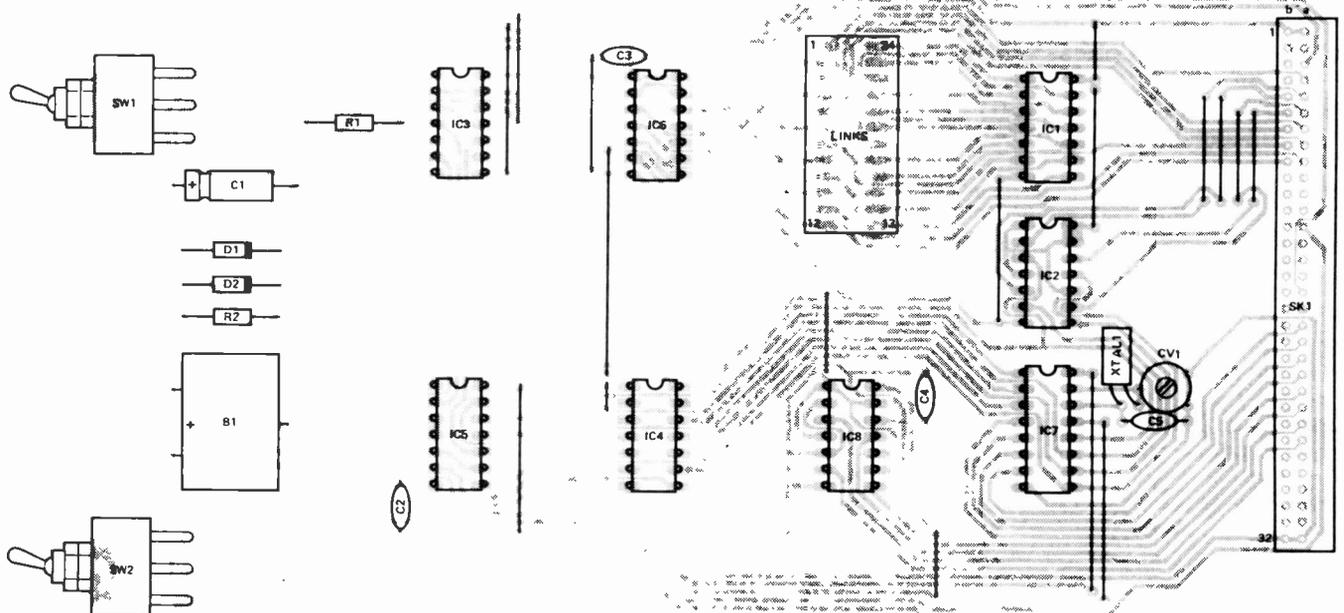


Fig. 2 Component overlay for the real time clock.

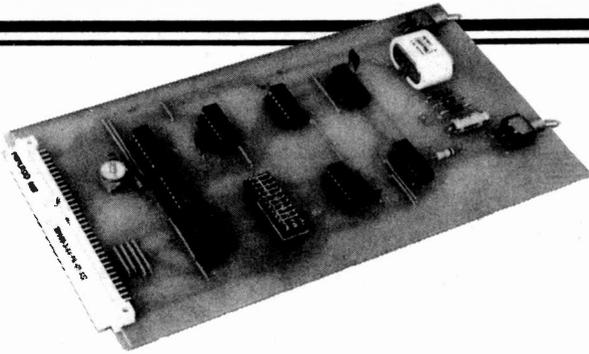

Programming

The following BASIC program is used for initialising the real time clock/calendar. The board should be write-enabled before running the program — however, if this is not done the user will be instructed to do so by the program. The program will fully validate the information given before writing it to the clock, to reduce the likelihood of human errors. We suggest that a time and date a few minutes ahead of the actual time is entered, the RETURN following the day of the week request being pressed exactly as this time arrives.

```

10 REM . . .MM58174 REAL TIME
  CLOCK INITIALISATION
  PROGRAM
20 DEF FNC(I) = VAL(MID$(TD$,
  I, 1))
30 DEF FNN(I) = 10 * FNC(I) +
  FNC(I+1)
40 DIM DM(12)
50 DATA 31, 28, 31, 30, 31, 30,
  31, 31, 30, 31, 30, 31
60 FOR I=1 TO 12: READ
  DM(I):NEXT I
70 PRINT "MM58174
  INITIALISATION"
80 INPUT "ENTER START
  ADDRESS OF BOARD"; AD
90 POKE AD, 0:REM . . . NON
  TEST MODE
100 POKE AD+15, 0:REM . . .
  DISABLE INTERRUPTS
110 POKE AD+14, 0:REM . . .
  STOP CLOCK
120 I=PEEK(AD+4):J=PEEK(AD+4)
130 J=15 AND (I+1):POKE AD+4,
  J
140 I=PEEK(AD+4)
150 IF I=J THEN 180
160 PRINT "WRITE ENABLE REAL
  TIME CLOCK — RETURN
  WHEN DONE"; :GET A$
170 GOTO 120
180 INPUT "ENTER TIME AND
  DATE IN THE FORM HH MM
  DD/MM/YY"; TD$
190 HH = FNN(1)
200 IF HH < 0 OR HH > 23 THEN
  180
210 POKE AD+7, FNC(1): REM . . .
  HOURS * 10
220 POKE AD+6, FNC(2): REM
  . . .HOURS
230 MM = FNN(4)
240 IF MM < 0 OR MM > 59 THEN
  180

```

```

250 POKE AD+5, FNC(4):REM . . .
  MINUTES * 10
260 POKE AD+4, FNC(5):REM
  . . .MINUTES
270 YY = FNN(13)
280 IF YY < 0 OR YY > 99 THEN 180
290 YR =
  2 ↑ (3 - (YY - 4 * INT(YY/4)))
300 IF YR=8 THEN
  DM(2)=29:GOTO 320
310 DM(2)=28
320 POKE AD+13, YR:REM . . .
  YEAR STATUS
330 MM = FNN(10)
340 IF MM < 1 OR MM > 12 THEN
  180
350 POKE AD+12, FNC(10):REM
  . . . MONTH * 10
360 POKE AD+11, FNC(11):REM
  . . . MONTH
370 DD = FNN(7)
380 IF DD < 1 OR DD > DM(MM)
  THEN 180
390 POKE AD+9, FNC(7):REM . . .
  DAY * 10
400 POKE AD+8, FNC(8):REM . . .
  DAY
410 INPUT "ENTER DAY OF WEEK
  (1-7, 1=MONDAY)"; DW
420 IF DW < 1 OR DW > 7 THEN
  410
430 POKE AD+10, DW:REM . . .
  DAY OF WEEK
440 POKE AD+14, 15:REM . . .
  START CLOCK
450 PRINT "WRITE DISABLE REAL
  TIME CLOCK"
460 STOP
470 END

```

To access the time and date from within a program, the following BASIC subroutine may be used: a few words of explanation are probably appropriate. Line 1040 clears the update flip-flop by reading the clock once. The following two lines then loop until a value of 15 is read, indicating that an update has just taken place and that a tenth of a second is available to read the registers before the next update. It is the requirement to read 11 registers in this 100 milliseconds time slot (in order to avoid the possibility of an update occurring between the reading of two registers) which accounts for the strange appearance of much of the rest of the subroutine. The inherent slowness of BASIC on an eight-bit microcomputer dictated the

avoidance of FOR-NEXT loops, subscripted variables and numerical constants in the time-critical portion. The routine returns with numeric values of seconds, minutes . . . months in R2-R7 respectively, an ASCII representation of the time in TM\$ and an ASCII version of the date in DT\$.

```

1000 REM . . .MM58174 READING
  ROUTINE
1010 R2=AD+2:R3=AD+3:R4=
  AD+4:R5=AD+5
1020 R6=AD+6:R7=AD+7:R8=
  AD+8:R9=AD+9
1030 RA=AD+10:RB=AD+11:
  RC=AD+12
1040 Z = PEEK(AD+2)
1050 Z = PEEK(AD+2)
1060 IF Z < > 15 THEN 1050
1070 R2=PEEK(R2):R3=PEEK(R3):
  R4=PEEK(R4)
1080 R5=PEEK(R5):R6=PEEK(R6):
  R7=PEEK(R7)
1090 R8=PEEK(R8):R9=PEEK(R9):
  RA=PEEK(RA)
1100 RB=PEEK(RB):RC=PEEK(RC)
1110 TM$=CHR$(48+R7)+CHR$(
  48+R6)+":"'+CHR$(48+R5)
  +CHR$(48+R4)
1120 TM$=TM$+"'"'+CHR$(48+
  R3)+CHR$(48+R2)
1130 DT$=CHR$(48+R9)+CHR$(
  48+R8)+"/"'+MM$(RB+
  10*RC)
1140 R2 = R2 + 10*R3
1150 R3 = R4 + 10*R5
1160 R4 = R6 + 10*R7
1170 R5 = R8 + 10*R9
1180 R6 = RA
1190 R7 = RB + 10*RC
1200 RETURN

```

Prior to calling the above subroutine, the following portion of program should be executed to store the names of the months in the array MM\$:

```

10 DIM MM$(12)
20 DATA "JANUARY",
  "FEBRUARY", "MARCH",
  "APRIL", "MAY", "JUNE"
30 DATA "JULY", "AUGUST",
  "SEPTEMBER", "OCTOBER",
  "NOVEMBER", "DECEMBER"
40 FOR N=1 TO 12: READ
  MM$(N):NEXT N

```

BUYLINES


The MM58174 real time clock/calendar IC is available from Cricklewood Electronics, Technomatic or Watford Electronics. The PCB-mounting switches and Nicad battery might be a bit tricky to find unless you have industrial contacts, but non-PCB types could be used and wires taken to the PCB pads; there's enough room on the PCB, which is available from our PCB Service as usual. See page 87. The Euro connector is stocked by Watford Electronics.

ETI

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.


Sparkrite

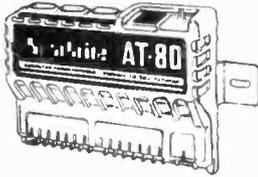BRANDLEADING ELECTRONICS
NOW AVAILABLE IN KIT FORM




AT-80 Electronic Car Security System

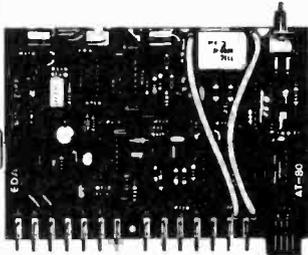- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble




VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms, warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories, 2,000 miles, 180 gallons, 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!

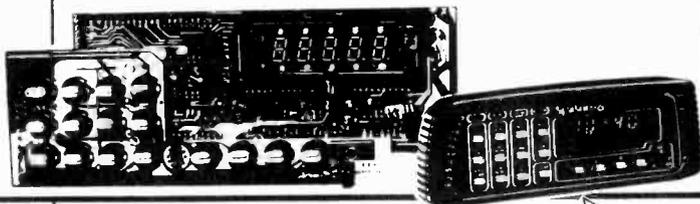

SX1000 Electronic Ignition

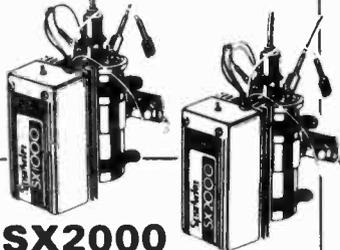- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles

TX1002 Electronic Ignition

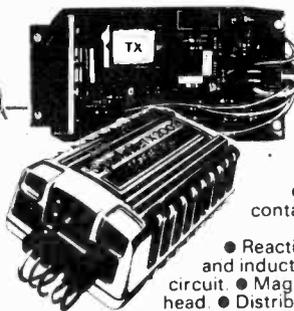- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble.




TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge, Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents.

SPECIAL OFFER

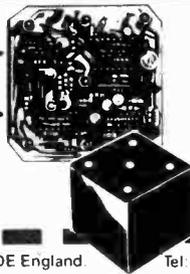"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw, 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE | 82 Bath Street, Walsall, West Midlands, WS1 3DE England

Tel: (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC. VAT, POSTAGE & PACKING

NAME _____ ETI/4/83

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____

CHEQUE NO. _____



BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

FEVAS

Could the end be in sight for semiconductors? Once again ETI gets a world exclusive, as Owen Bishop describes the revolutionary technology which is poised to take us through to the 21st Century.

It seems an age since the Gemini spaceflights of the middle nineteen-sixties, yet then was born an entirely new concept in electronics which has only just been brought to production stage. Almost weekly we hear of spin-offs from space-age technology, but this is one which threatens to render obsolete almost all of today's circuit designs. Opto-technology, surface acoustic wave devices and bubble memories are out of the running before they have hardly begun to crawl.

FEVAs, Field Effect Voltage Amplifiers, were born in the sixties, grew up in the seventies and, in the eighties, are ready to take over all the functions that are performed by semiconductor and related devices today. Their full designation is SCFEVAs, which gives a clue to their origin, for this is an abbreviation of Space-Channel Field Effect Voltage Amplifiers. The space channel will soon replace all the N-channel and P-channel devices we take for granted nowadays.

Serendipity

No, this is not the acronym for yet another complex electronic wonder but a word which means 'making unexpected discoveries by accident'. FEVAs began this way during one of the early space-walks of the Gemini missions. The immense potential of the discovery was realized immediately by astronaut Lee Old, but it is only today that the news is beginning to surface.

It happened like this. During their second space-walk, the astronauts were engaged in a capsule-service practise routine. Their task was to insert a plug of expanded polystyrene into a recess in the rear of the capsule in order to enhance its aerodynamic qualities in readiness for re-entry into Earth's atmosphere. You may think that expanded polystyrene is an unlikely material for this purpose but it has several features in its favour. Its strength-to-mass ratio is one of the highest, a factor of immense importance in space travel. As any handyman knows, another advantage of expanded polystyrene is that it is easily cut, and as any handyman also knows, the best way of cutting it is to use a hot wire. The extremely high thermal insulating properties of expanded polystyrene mean that a hot-wire cutter functions perfectly, even in the sub-zero temperatures of outer space. So it was to be a neat and well-thought-out manoeuvre, but then the unexpected happened.

Blowing In The Wind

Whenever Lee switched on his hot-wire cutter, his colleague 'Gig' Potter was alarmed by intense activity on the Solar Wind Detector. This was an on-board experiment devised by the Department of Applied Physics of the University of Minniwauke, the purpose of which was to monitor the streams of electrons being repelled from the Sun's chromosphere. When the wire was hot, the effect was like a solar gale! Lee immediately realized that there must be some kind of interaction between his hot wire and

the Solar Wind Detector. Electromagnetic interference was immediately ruled out, for the wire was not coiled and, in any event, was powered by direct current.

It must be that electrons from the atoms of the wire were being energised by the heating, were escaping from the confines of the wire and passing to the Solar Wind Detector. Maybe there was an electric field caused by the friction between Lee's space-gloves and the expanded polystyrene which was accelerating the electrons toward the detector.

Back To Earth

We hear a lot about taking Earth-bound manufacturing technologies to space to gain the advantages of the conditions there, but this is a case of bringing the conditions of space down to Earth. Lee's penetrating insight told him that the key to implementing his discovery was to create space conditions on Earth, and the solution to this problem was blindingly simple. Take a suitable container and suck the air out of it! The space channel is, in fact, known in everyday parlance as a *vacuum*. Lee resigned his commission in order to devote himself full-time to promoting the commercial aspects of his discovery. But Lee was back on Earth in more senses than one! He soon came up against the incredulity and stultifying caution of the financial world, at whose door must be laid the blame for the excessive delay in bringing to the human race the far-reaching benefits of this new technology.

The FEVA Diode

Curiously enough, one of the key devices in this new range does not in fact amplify voltages. It mirrors the original space-walk conditions: enclosed in a sealed glass capsule (Fig. 1) is a hot wire and a metal plate. When the wire is heated by passing a current through it, and a potential difference is applied between the wire and the plate, electrons flow from the wire to the plate across the space channel. We have an *electric current*. As in the original scenario, the plate (corresponding to the solar wind detector) is *unheated*, so electrons do not flow from the plate to the wire. Current flows *in only one direction*, just as at a PN junction in semiconductors. These devices have taken their name from their semiconductor equivalent device and are known as FEVA *diodes*. But whereas we have to use highly purified silicon and rare metals such as antimony to manufacture a semiconductor device, the FEVA needs nothing but sweet nothingness to provide its conducting channel. Apart from the low-cost metals used for making the wire and plate, the FEVA is constructed entirely of re-cycled glass and plastic.

The story of the terminal pin design is an amusing one. Lee was looking for something to hold his prototype FEVA diode when he came across a handy four-pin socket which had resided for years unused in his junkbox (Fig. 2). He had never known the original purpose of this socket, for it had been in the box when it was donated to him by

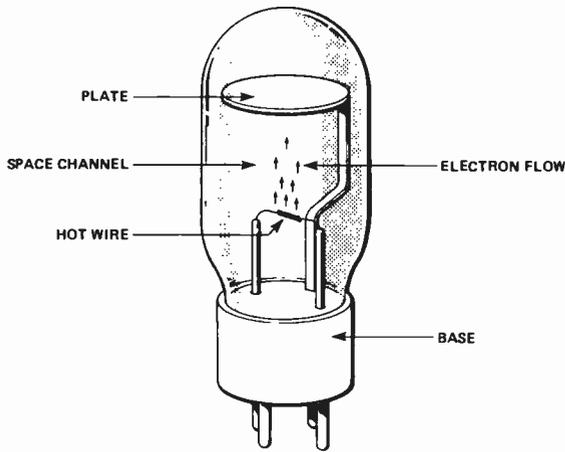


Fig. 1 The prototype FEVA diode. The base is of formaldehyde-phenol plastic (known as Bakelite) and is not to be confused with the base of a transistor.

his grandfather. It suited the present purpose well and, such is the way of things once they have been found to suit, there was no real incentive to re-design the socket for later devices. The novel 'kite' configuration of the pins offers many advantages over the old-fashioned DIL array. As many electronics hobbyists known to their cost, it is so easy to insert the IC the wrong way round, but this is quite impossible with a FEVA.

Field Effect Devices

If the FEVA diode is the counterpart of the semiconductor diode, the basic FEVA device typified by the PM2DX (Fig. 3) is the equivalent of the field effect transistor. The so-called 'grid' is a sheet of wire gauze cunningly introduced by Lee between the wire and plate to modulate the electric field and so regulate the flow of electrons in the space channel. A very small change in the potential of this plate has a significant effect on the current flowing through the device, simulating the effect of gate potential in a conventional FET, though the mechanism is somewhat different and at present less well understood. A resistor placed in series with the plate (or *anode* as it is now called, referring of course to the corresponding anode terminal of the semiconductor diode) develops a useful change of potential running to several tens of volts. Incidentally, these devices work at high voltages, levels that would reduce the ordinary FET to a bead of charred silicon!

Integration

No sooner had the initial designs been proven in extensive laboratory and field trials than the logical follow-up was to put more than one device in the same capsule. An early example is the ECH21 frequency converter (Fig. 4), but already the OEMs, eager for the rapid and profitable returns that this new technology will generate for many decades to come, are pressing ahead with mind-boggling developments.

The first commercial product incorporating the new range of miniaturized FEVAs is to be launched in April 1983. This is a digital time-piece of elegant and sizable proportions. No need for the short-sighted to put on their specs to read this one! It comes with a durable PVC backpack for the battery power supplies, with a choice of embroidered shoulder straps for the ladies. Those of you who have a half-acre building-plot to spare and have planning permission for a five-storey block, will be pleased to know that the first 1-kilobyte FEVA-technology personal com-

puter is due to be launched in April 1984. The installation expenses may readily be recouped, for it incorporates heat-exchangers which may be connected as a thermal source for your local district-heating scheme.

In the meantime, hobbyists can throw away their magnifying glasses and turn to the man-sized technology of the future. Mauldin Electronics Ltd and Armpit International are both marketing a hobbyist familiarization conversion kit which includes an assortment of FEVAs, 3kg of FEVA sockets, four square metres of 14 swg aluminium sheet for mounting the FEVA sockets ('chassis' is the newly coined term), a 50 W soldering iron with 8 mm bit, an oven-glove for use in handling hot FEVAs and a colourful but comprehensive wall-chart on first aid for electrocuted persons. Our own sister magazine, Spam Radio Today, is hoping to publish details of a transceiver project using these devices.

Coming Of Age

The heady days of the development era of the FEVA are over. The name itself, harking back to the sixties, is nowadays thought to be too flippant for a technology which is to bring Britain back to world domination in the

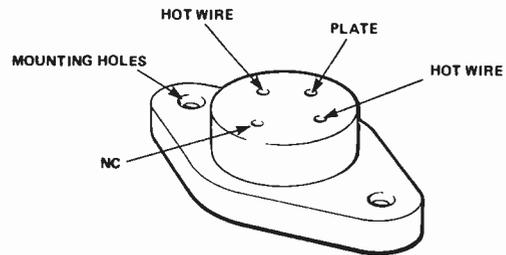


Fig. 2 Yet another type of socket to add to the massive range we already have. Known as the UX4, it is the new standard socket for FEVA diodes, and is available in a range of attractive colours: black, brown, grey or buff.

electronics of the twenty-first century (and beyond?). There is a strong move afoot to rename FEVAs even before their first name becomes a byword to the man in the street. For one thing, with the advent of the Shuttle, space technology is becoming commonplace and no longer excites the imagination as it once did. The new name for this technology firmly faces facts, replacing 'space channel' by 'vacuum'. So if you never hear anything more about FEVAs, the wonder of our age, keep a sharp look-out for their new designation — Vacuum Linked Voltage Expanders. The new name is sticking well and already the back-room boys have affectionately shortened this to 'VALVE'.

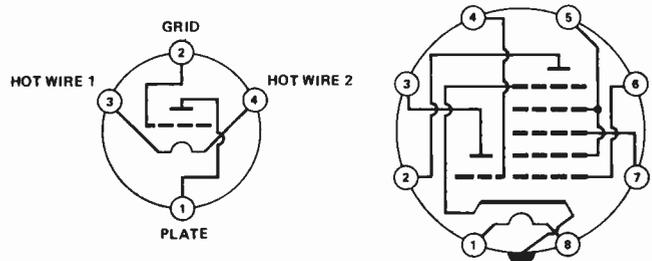


Fig. 3 (Left) Pin-out schematic of the PM2DX, the basic FEVA amplifier.

Fig. 4 (Right) Pin-out schematic of the ECH21, the FEVA technology frequency counter. Is this the first step towards a computer in a capsule?

ETI

Who but the people who made the micro possible
could help you understand it?

The Texas Instruments Electronic Library.

An in-depth series in understanding today's world of electronics.

The Understanding Electronics Series was specially developed and written to give you an in-depth knowledge of this world.

Each book is comprehensive, yet easy to understand. As informative for the electronics buff as for someone who's simply interested in what's going on today.

Together the library will give you the most complete range of titles available. Take advantage of our introductory offer and choose the book, or books you want from the titles below. You'll find whole new worlds of advanced technology unfolding before you.

Everything you've always wanted to know about:

1. Understanding Electronic Control of Energy Systems.

1st edition. Ref. LCB 6642. Covers motor, generator, power distribution, heating, air conditioning, internal combustion engine, solar and nuclear systems. *Softbound 272 pages. £3.95.*

2. Understanding Electronic Security Systems.

1st edition. Ref. LCB 7201. A complete guide covering the basics of hard wired, photosensitive, infrared, ultrasonic and microwave systems and their use in different applications. *Softbound 128 pages. £1.95.*

3. Understanding Solid State Electronics.

3rd edition. Ref. LCC 3361. The principles of solid state theory. It explains electrical movement, with intermediate tuition on the applications of solid state devices. *Softbound 282 pages. £3.95.*

4. Understanding Digital Electronics.

1st edition. Ref. LCB 3311. Describes digital electronics in easy-to-follow stages. It covers the main families of digital integrated circuits and data processing systems. *Softbound 260 pages. £3.95.*

5. Understanding Microprocessors.

1st edition. Ref. LCB 4023. An in-depth look at the magic of the solid state chip. What they are, what they do. Applications of 8-bit and 16-bit microprocessors; and design from idea to hardware. *Softbound 288 pages. £3.95.*

6. Understanding Computer Science.

1st edition. Ref. LCB 5471. This book tells you in everyday English how today's computer has been developed, what goes on inside it, and how you tell it what to do. *Softbound 278 pages. £3.95.*

7. Understanding Communications Systems.

1st edition. Ref. LCB 4521. An overview of all types of electronic communications systems. *Softbound 282 pages. £3.95.*

8. Understanding Calculator Maths.

1st edition. Ref. LCB 3321. Brings together the basic information - formulae, facts, and mathematical tools - you need to "unlock" the real power of the hand-held calculator. *Softbound 230 pages. £3.95.*

9. Understanding Optronics.

1st edition. Ref. LCB 5472. Optronics is the application of light and electronics to perform a wide range of useful tasks. From car headlights to missile guidance systems. *Softbound 270 pages. £3.95.*

10. Understanding Automotive Electronics.

1st edition. Ref. LCB 5771. Learn how electronics is being applied to automobiles. How the basic mechanical, electrical and electronic functions and the new microprocessors and microcomputers are being applied in innovative ways for vehicle drive train control, motion control and instrumentation. *Softbound 288 pages. £3.95.*

How to order

Fill in the coupon below or if someone else has already used it, simply:

1. List reference numbers and quantities required.
2. Calculate total order value. Add £1.50 for postage and packing.
3. Send the list, plus your cheque payable to Texas Instruments Ltd, PO Box 50, Market Harborough, Leicestershire. Allow 30 days for delivery.

**TEXAS
INSTRUMENTS**



ENERGY CONVERSION 2



WATER RESERVOIR
(POTENTIAL ENERGY)

DAM

WATERFALL

ELECTRIC
GENERATOR

OUTLET WATER FLOW
(WASTE KINETIC ENERGY)

TURBINE
PROPELLER
BLADES

MECHANICAL ROTATION
(KINETIC ENERGY)

Potential Energy of Elevated Water into
Electric Energy

2 ENERGY CONVERSION

To: Texas Instruments Limited, PO Box 50, Market Harborough, Leics.
Please send me the following publications:

REFERENCE NO.	QTY	REFERENCE NO.	QTY
1.		7.	
2.		8.	
3.		9.	
4.		10.	
5.			
6.			

Free title choice: Understanding _____

I enclose a cheque for £ _____

Name _____

Company (if any) _____

Address _____

Registered office: Texas Instruments Ltd, Manton Lane, Bedford MK41 7PA.
Registered number: 574102 England.

FOSSIL FUEL
(COAL GAS OIL)

LOW TEMPERATURE

INTRODUCTORY OFFER
Order three books and get
any one of the
"Understanding" series
FREE.

Sinclair ZX Spectrum

**16K or 48K RAM...
full-size moving-
key keyboard...
colour and sound...
high-resolution
graphics...**

**From only
£125!**

First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

Professional power— personal computer price!

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASIC ROM dramatically increases your computing power.

You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can update later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.



Ready to use today, easy to expand tomorrow

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.

There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232/network interface board.



Key features of the Sinclair ZX Spectrum

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard—all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

STAGE LIGHTING

PART 3

Design by David Colven and Ian Cleverley.

Setting Up

Set SW5, the manual/auto switch, to manual for the channel designated '0'. Check that the master blackout switch is off, and that RV1 for that channel is set to minimum (the manual slide pot). Set the speed-up switch SW4 to off, and turn PR8 to minimum. Now switch on the mains and set PR9 to mid-position. Slide RV1 to maximum and adjust PR7 for maximum light output. Then slide RV1 to minimum and set PR8 to give minimum light output (the bulb should just glow). Repeat these adjustments until the light glows at the minimum setting of RV1 and is full on at the maximum setting.

To set up the auto-fade units, first set SW5 for the channel to automatic, with RV1 at minimum. Set PR6 on the channel to be calibrated to minimum and set the scene select switches to '00'. Now, using the keyboard, program the channel, '00', the lighting level, '0', and the time duration, '37'. Press the enter button; the display should now read '00 0 37'. Enter the following:

SCENE	DATA
01	00137
02	00237
03	00337
04	00437
05	00537
06	00637
07	00737

Remember to press the enter button after each entry of five digits. Now set the scene selector switches to '07' and press SW1. Set PR5 one-third of a

rotation clockwise from minimum, set PR13 to maximum, and adjust PR6 to give the maximum light output. Now set the scene selector switch to '00' and press SW1 again. Adjust PR1 for minimum light output (the light should just glow). Now by using the scene select switches and the scene change switch to step through the data sequence just programmed in, the remaining presets PR2,3,4,10,11 and 12 may be adjusted as appropriate to give the eight lighting levels.

To adjust for an even ramp rate, reset the scene select switch and press the scene change switch so as to compare the time between the light

rising to the preset level and falling to zero. If there is any difference, adjust PR5 until the time rise and fall times of the light level are about the same. Alternatively, if you have a scope you can inject a signal at pin 2 of IC29 and look at the output (pin 6). Adjust PR5 to give a square wave with equal mark-space ratio.

This completes the setting-up for the first channel. Repeat for the other channels, but remember when programming to change the channel number as appropriate for the first two key presses ('01' for the next channel and so on).

PARTS LIST

Resistors (all 1/4W, 5%)

R1	270R
R2-4	10k
R5	100R
R6	390R
R7-36	180R
R37,38	560R
R39	22k
R40,42-50	1k0
R41	1k5
R88,89	470R
Capacitors	
C1,3,4,26	100n polycarbonate or polyester
C2	33u 16 V tantalum
C5	1u0 35 V tantalum


Semiconductors


IC1	74LS123
IC2	4017
IC3,4	74LS08

IC5	74LS04
IC6-9	74LS75
IC10-13	74LS47
IC14	74LS163
IC15-18	74LS02
IC19	74LS154
IC20	74LS109
IC21	74LS00
IC22	6116
IC23,24	81LS97
Q1,2	BC108
D21,22	1N4148
ZD1	2V7 400 mW zener
DISP1-5	0.5" common-anode seven segment displays

Miscellaneous

SW1	SPCO push-button or toggle
PCBs (see PCB Service ad on page 87).	

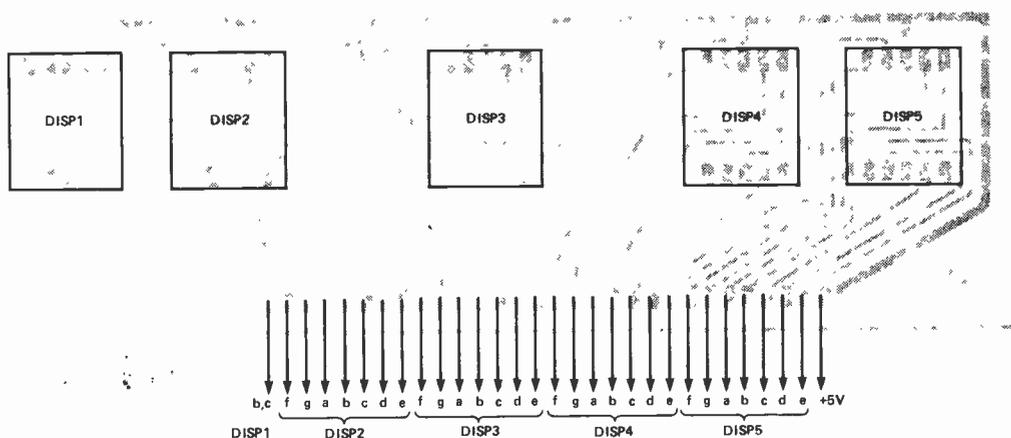

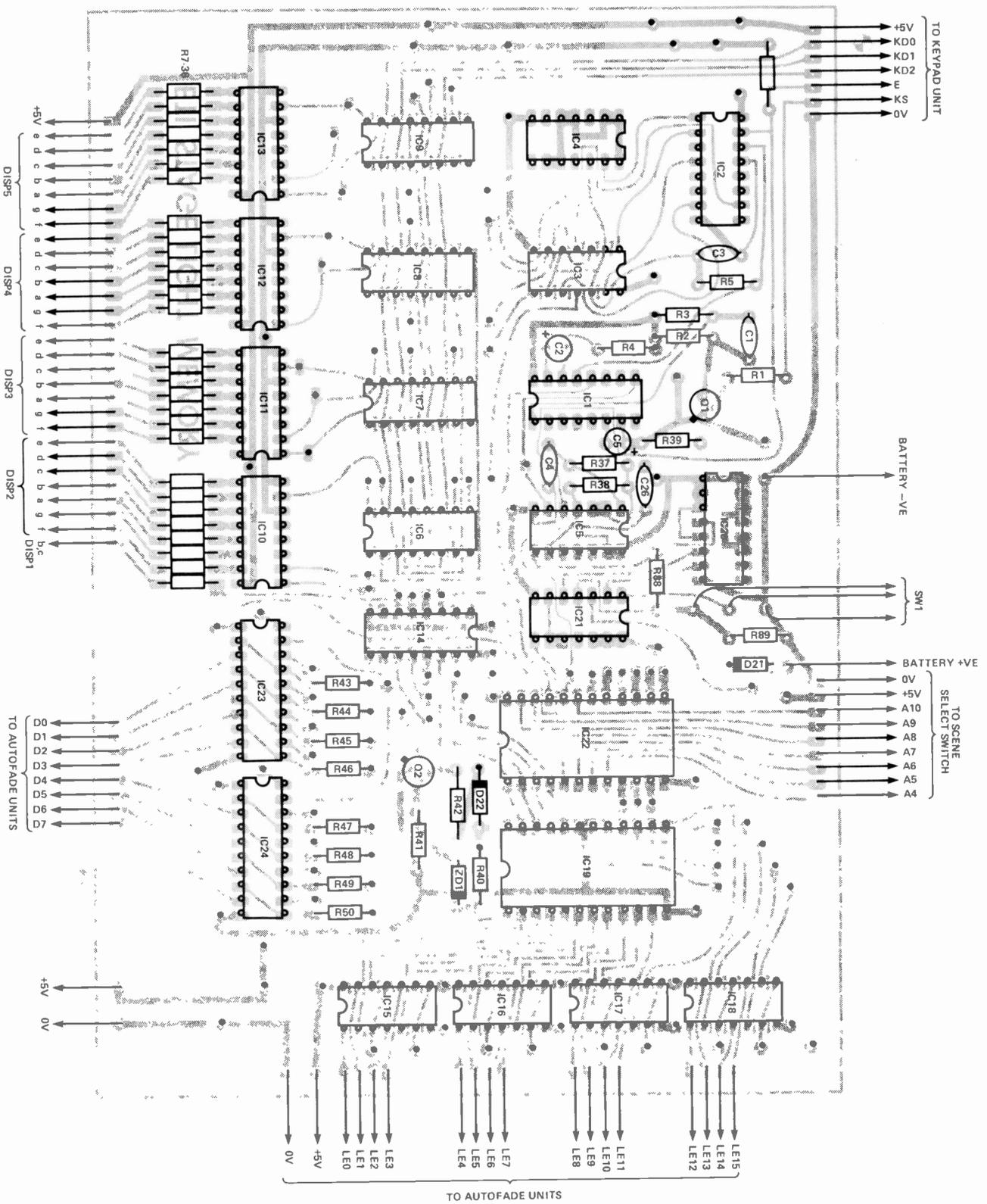

ROBOTICS FANS!!! LOOK!!



ONLY
£4.95

"BIG TRAK" MOTORIZED GEARBOX

These units are as used in the "Big Trak" computerized vehicle, and offer the experimenter in robotics the opportunity to purchase the electro-mechanical parts required in building remote controlled vehicles. The unit comprises:

- a) 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle;
- b) A gearbox contained within the black ABS housing reducing the final drive speed to approx 50rpm.

Data is supplied with the unit showing various options on driving the motors, as well as a direction controller circuit, enabling the unit to turn, right, left or go straight ahead.

2N3055

SCOOP!!

Made by Texas — full spec devices, 60p each; 10 for £4; 25 for £9; 100 for £34; 250 for £75; 1000 for £295.

AA NI-CADS 10 for £9.95

Brand new nickel cadmium batteries by GE, standard 1.2V at 450mA/H. Professional quality with solder tags both ends. Special price, £11.40 ea; 10 for £9.95; Box of 80 £85.

Nicad Charger: Charges up to 4AA, C or D cells + PP3. Only £7.95.

COMPUTER SOFTWARE


We now sell a range of tapes and books for DRAGON 32, SPECTRUM, ZX81, BBC and VIC20. Send s.a.e. for list stating for which computer required, or call in our shop.

SIMON GAME

Simon is back again. Another supply of ready built PCB's for this flashing light/pulsating tone computerised game is now with us. Supplied tested and working with speaker and instructions. £4.95.

COMPUTER BATTLESHIPS

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value only (PCB may be chipped or cracked), SN76477 sound IC; TMS1000 u-processor; batt clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

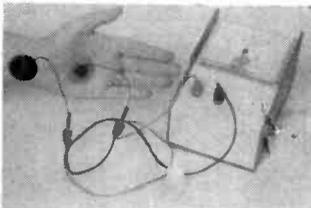

LIE DETECTOR

Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 4.5V batts. Overall size 155x100x100mm. Only £9.95 — worth that for the case and meter alone!

GREENWELD

443A MILLBROOK ROAD, SOUTHAMPTON SO1 0HX
All prices include VAT — just add 50p post. Tel (0703) 772501



NOW
REDUCED
TO £3.95

ELECTRO DIAL

Electrical combination lock-for maximum security-pick proof. One million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid. Overall dia 65mm x 60mm deep. Only £3.95.

FERRIC CHLORIDE

New supplies just arrived — 250mg bags of granules, easily dissolved in 500ml of water, Only £1.15. Also abrasive polishing block 95p.

STABILIZED PSU PANEL

A199 A versatile stabilised power supply with both voltage (0-30V) and current (20mA-2A) fully variable. Many uses inc bench PSU, Ni-cad charger, gen, purpose testing. Panel ready built, tested and calibrated £7.75. Suitable transformer and pots £8.00. Full data supplied.

REED RELAYS

Manufacturers rejects — DIL and other PCB mounting types. SP, DP and 4P — make, break and c/o contacts. Not tested, so may be only partially working or o/c etc, so very low price — pack of 10 assorted £1; 25 £2.00; 100 £7.00.

TELESCOPIC AERIALS

As used in Sinclair microvision, 9 section 100-610mm. Only 95p.

IN4148 — BEST PRICE EVER

Supplied in packs of 100, by Toshiba £2 per pack; 3 packs £6.50; 10 packs £15; 25 packs £32; 100 packs £115.

COMING SOON . . .
MORE COMPUTER GAMES PCB's
— MICROVISIONS, ALPHIE,
AVENGER, INTRUDER, AND
STARBIIRD

POWERFET AMPLIFIERS

NEW DESIGNS

With the introduction of four new boards PANTECHNIC have pushed forward the performance and reliability of their powerfet amplifiers. Four key improvements have been incorporated in these second generation modules —

- 1.) The use of H-PAK powerfets, resulting in improved thermal efficiency and consequently enhanced power output capabilities.
- 2.) Low C_{OB} drivers now in power transistor packages, maintaining the superb HF performance and improving driver reliability.
- 3.) Separate driver and input supply rails allowing a 10% increase in available output power by increasing output stage efficiency.
- 4.) Bridge mode input pin allowing instant bridging between any two amplifiers without the need for extra circuitry.

PFA100 Specification

Bandwidth	10Hz-100KHz ± 1dB
Output Power into 8Ω	100W (V _s = ± 55V)
THD (20Hz-20KHz)	<0.008%
THD (1KHz at 100W)	0.004% typ.
SNR	120dB
Slew rate	> 30 V/μs
Gain	x 23
Rin	30K
V _s max	± 70V

Price

£17.35 (Built & Tested)

£15.17 (Kit)



PFA100 120W into 8Ω (V_s = ± 60V)

PFA200 Specification

Bandwidth	10Hz-100KHz ± 1dB
Output power into 8Ω	150W (V _s = ± 60V)
THD (20Hz-20KHz)	<0.005%
THD (1KHz at 150W)	0.002% typ
SNR	120dB
Slew rate	> 30 V/μs
Gain	x 23
Rin	30K
V _s max	± 70V

Price

£23.87 (Built & Tested)

£21.70 (Kit)



PFA200 180W into 8Ω
300W into 4Ω (V_s = ± 67V)

And for those with a taste for power . . .

- PFA500 Delivers 475W into 4 ohms and 600W into 2 ohms. These highly current capable units can deliver 25 amps continuous into a load, whilst maintaining the exemplary performance figures of the smaller units. £42.00 (built & tested)
- PFA/HV A very special module aimed at digital audio and wide dynamic range programme material. Delivers 300W into 4 ohms and 8 ohms on a continuous basis, it will peak for musically significant periods of time at up to 5dBs above this. The PFA/HV is the widest dynamic range power amplifier currently available. £34.30 (built & tested)
- THE HEAT EXCHANGER. Other people sell heatsinks. Pantechnic design, manufacture and sell heatexchangers. Re-examination of the heat transfer process has resulted in a radically new design possessing greatly improved efficiency. The unit 7" x 4" x 2" handles PFAs up to 300W or 1.2KW when blown. £7.50

POWER SUPPLY COMPONENTS

Toroidal Mains Transformers

Voltage	160VA	225 VA	300 VA	500 VA	625 VA
40-0-40	9.71	11.36	12.32	—	—
45-0-45	—	11.36	12.32	16.05	—
50-0-50	—	—	—	16.05	18.80

Special low flux windings. Carriage included

25A 400PIV Bridge rectifier	£2.17	For the PFA/HV 500VA	70-0-70
10,000uF 90V Electrolytics	£4.13		£16.05
30,000uF 75V Electrolytics	£10.00	10,000uF 100V Electrolytics	£5.70

Phone or write for advice on selecting the right components for your particular application.

All prices excl. VAT. Carriage 75p. Trade supplied

Ask about our preamps, protection boards and active crossovers

THE POWERFET SPECIALISTS

pantechnic

(incorporating J.W. Rimmer)

Mail order only to:

Dept ET1/3, 148 Quarry Street, Liverpool L25 6HQ.

Telephone: 051 428 8485

Technical enquiries

Phil Rimmer 01-800 6667

electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

ELECTRONIC IGNITION



IS YOUR CAR AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines max. (even with 8 cylinders).
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best. Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.

★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the 'near misfires' whilst an electronic filter smooths out the effects of contact bounce etc.

Most **NEW CARS** already have **ELECTRONIC IGNITION**. Update **YOUR CAR** with the most powerful system on the market - 3 1/2 times more spark power than inductive systems - 3 1/2 times the spark energy of ordinary capacitive systems, 3 times the spark duration.

Total Energy Discharge also features: **EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, LED STATIC TIMING LIGHT, LOW RADIO INTERFERENCE, CORRECT SPARK POLARITY** and **DESIGNED IN RELIABILITY**.

★ **IN KIT FORM** it provides a top performance system at less than half the price of competing ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

FITS ALL NEGATIVE EARTH VEHICLES
6 or 12 volt, with or without ballast.

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS:
(Older current impulse types need an adaptor).


STANDARD CAR KIT £15-90
Assembled and Tested £26-70

PLUS
P. & P.
£1 (U.K.)

TWIN OUTPUT KIT £24-55
For Motor Cycles and Cars with twin ignition systems
Assembled and Tested £36-45

Prices
include
VAT

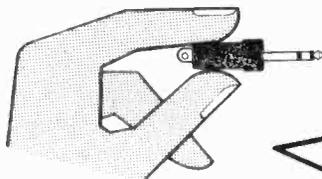PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



Don't Wait Until
Its too Late ~
Fit one **NOW!**

- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
- ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
- ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
- ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
- ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.

★ **DISABLES IGNITION SYSTEM** when alarm is armed.

★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.

FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.
SUPPLIED COMPLETE WITH ALL NECESSARY LEADS AND CONNECTORS PLUS TWO KEY PLUGS

CAR ALARM KIT £24-95

ASSEMBLED AND TESTED £37-95

PLUS
P. & P.
£1 (U.K.)
Prices
include
VAT



Access and Visa
Welcome. Write or
Phone Quoting Number

ELECTRONIZE DESIGN

Dept. D · Magnus Rd · Wilnecote
Tamworth · B77 5BY
tel: 0827 281000

DESIGNING NDFL AMPS

The use of nested differentiating feedback loops (NDFLs) is a new technique for reducing audible-frequency distortion in an amplifier to a vanishingly low level. As the name implies, NDFLs rely on negative feedback, but they use it in a new way. Edward M. Cherry, Associate Professor of the Department of Electrical Engineering, Monash University, explains the theory involved.

In order to understand just how far the new NDFL technique can improve an amplifier, we first need to know the fundamental limits to the reduction of distortion that can be achieved with conventional techniques. To begin with, we survey familiar negative-feedback theory.

Figure 1 is a block diagram of an amplifier with negative feedback. In this diagram, the forward path corresponds to the amplifier before feedback is applied, and its gain is traditionally designated by the Greek letter μ . The feedback network returns a fraction β of the output to the input circuit, where it is in some way subtracted from the true input to provide the actual input to the forward path.

In many practical amplifiers, the subtraction is accomplished by applying the input and feedback signals to the two inputs of a balanced differential first stage of the forward path. Figure 2 is an outline practical circuit. In this circuit the feedback factor β is the attenuation of the network comprising R_{F1} and R_{F2}

$$\beta = \frac{R_{F1}}{R_{F1} + R_{F2}} \quad (1)$$

A typical value for an audio power amplifier might be 1/20. The forward-path gain μ in Fig. 2 corresponds to gain from input to output when the feedback network is removed. A typical value for a simple audio power amplifier might be 1000.

For Fig. 1, the overall closed-loop gain A is given precisely by

$$A = \frac{\text{Output}}{\text{Input}} = \frac{\mu}{1 + \mu\beta} \quad (2)$$

The quantity $\mu\beta$ is called the loop gain. Physically, loop gain is the gain that would be observed if the feedback 'loop' in Fig. 1 was cut at some point, a signal was injected into one side of the cut, and the resulting signal at the other side of the cut was measured.

If the values of μ and β are such that loop gain is small compared with unity, the closed-loop gain is very nearly equal to the forward-path gain (that is, the gain without feedback)

$$A \rightarrow \mu \quad (3)$$

$$\mu\beta \ll 1$$

However, if loop gain is large compared with unity, the closed-loop gain approaches the reciprocal of the feed-

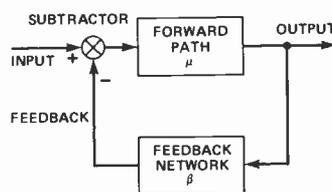


Fig. 1 Block diagram of a feedback amplifier.

back factor and becomes almost independent of the forward-path gain

$$A \rightarrow 1/\beta \quad (4)$$

$$\mu\beta \gg 1$$

The quantity $1/\beta$ is often called the demanded gain, as it is the value the overall closed-loop gain would take in ideal circumstances.

As a numerical example, if we substitute the above values $\mu = 1000$ and $\beta = 1/20$ into Equation 2, the gain of our 'typical' audio power amplifier works out as $A = 19.6$. The approximate Equation 4 predicts $A \rightarrow 20$, within 2% of the correct answer.

The quantity $1 + \mu\beta$ occurs often in feedback theory. It is called the return difference F .

$$F = 1 + \mu\beta \quad (5)$$

Physically, return difference has the significance

$$F = \frac{\text{forward-path gain}}{\text{closed-loop gain}} \quad (6)$$

For values of loop gain greater than about 10, loop gain and return difference are almost equal — in our 'typical' example the value are 50 and 51 respectively.

Simplified treatments of feedback theory show that, if the distortion generated in the forward path (that is, the amplifier without feedback) at a particular output signal amplitude is D_μ , then the resulting closed-loop distortion D_A at the same output signal amplitude is

$$D_A = D_\mu/F \quad (7)$$

Distortion is improved when feedback is applied to an amplifier by a factor equal to the return difference. In our 'typical' amplifier, $F = 51$; if the distortion without feedback happened to be 10%, then feedback should reduce the distortion to 0.196%.

More rigorous treatments of feedback theory show that Equation 7 is no more than a poor approximation to the truth. In the first place, real amplifiers are far more complicated than Fig. 1 suggests, because several different feedback paths (not all intentional!) can be identified. For example, the collector-base capacitances of transistors inevitably provide some unintended feedback at high frequencies. There is a very real problem in interpreting just

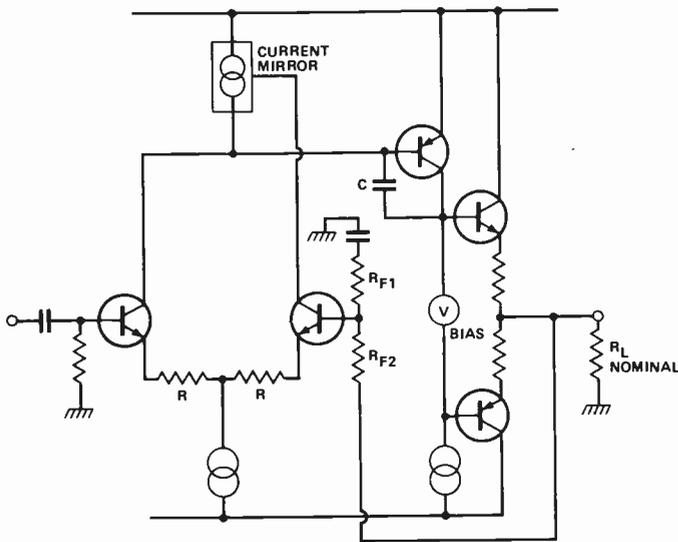


Fig. 2 Outline circuit of an audio power amplifier.

what loop gain and return difference mean when there is more than one feedback loop. Once the correct interpretation is established, return difference invariably turns out to be a function of frequency, and the reduction of distortion corresponding to Equation 7 depends on the value of return difference at the frequency of the distortion, not the frequency of the input. Feedback therefore, does not reduce all distortion components equally.

Finally, it is found that the closed-loop distortion of an amplifier can contain new components that were not present in the distortion that existed in the forward path before feedback was applied. These new distortion components initially increase as loop gain is increased, but they fall away again towards zero as loop gain is made large.

Despite all these complications, the fact remains that adequate negative feedback, properly applied, does reduce distortion. Why, then, do amplifier designers not simply apply some arbitrarily large amount of feedback and reduce amplifier distortion to the vanishing point?

TIM, IIM, PIM, . . .

In the last 10 years or so, readers of audio magazines have been made aware of a conjecture that goes something like this:

"Harmonic distortion and the usual intermodulation distortion decrease with increasing feedback. Transient intermodulation distortion (TIM) increases with increasing feedback, and is approximately directly proportional to the feedback. Therefore, there is an optimum value for the feedback at which the subjective distortion sensation is least. This optimum feedback is unlikely to exceed about 20 dB."

More recently, there has been conjecture that heavy overall feedback should be applied with caution if interface intermodulation distortion (IIM) is to be avoided. An amplifier should provide a low open-loop output impedance so that the need for feedback-generated loudspeaker damping is minimised.

There has also been conjecture that negative feedback, which reduces the usual intermodulation distortion, may increase phase intermodulation distortion (PIM) by converting amplitude nonlinearities into phase nonlinearities.

Unequivocally, none of these conjectures has any basis in the new NDFL amplifiers. As an aside, there is a

substantial body of opinion that none of these conjectures has any basis, full stop; interested readers should refer to References 1-9.

Instability And Oscillation

A fundamental limit to the amount of feedback that can be applied to an amplifier is set by the onset of instability and oscillation.

If the magnitudes of the forward-path gain and demanded gain of the idealised Fig. 1 are plotted versus angular frequency ω (in radian/second) on logarithmic scales, the resulting graph looks something like Fig. 3. The 3 dB bandwidth of the amplifier without feedback is $1/\tau_\mu$, and the gain-bandwidth product (at which gain drops to unity) is $1/\tau_x$.

Because the graph is on logarithmic scales, the separation between the curves of forward-path gain and demanded gain is the loop gain (remember that, to divide two numbers, you subtract their logarithms; if you divide μ by $1/\beta$, you get $\mu\beta$). The magnitude of loop gain falls to unity at the frequency $1/\tau_x$ where the curves intersect and their separation is zero (remember that the logarithm of unity is zero).

By a similar argument, return difference is the separation between the curves of forward-path gain and closed-loop gain, as indicated in Fig. 3.

We could make a similar graph to Fig. 3, showing the phases of μ and $1/\beta$. Again, the phase of loop gain would turn out to be the separation between the two curves. However, there is a remarkable piece of mathematics due to Bode, who used a transformation evolved by Hilbert (1862-1943), which shows that there is a relation between the magnitude and phase of the response of any linear system. Subject to some qualifications, our proposed graph of the phases is completely predictable from Fig. 3 and contains no new information. Interested readers may refer to Chapter 14 of Bode's book (Reference 10) but are warned that it is anything but easy going!

As an example, many readers will know that, if the forward-path in Figs. 1 and 2 has a high-frequency cut-off rate variously described as single pole, 20 dB/decade, or 6 dB/octave, then its phase shift is 45° at the 3 dB cut-off frequency $1/\tau_\mu$, and is asymptotic to 90° at very high frequencies.

In 1932, Nyquist applied a theorem which dates back to Cauchy (1789-1857) to derive the condition for a feedback amplifier to be stable and free from oscillation. If a polar plot is made of the magnitude and phase of return difference as frequency is varied, a vaguely 'snail-shaped' curve results. Such a polar plot is called a Nyquist diagram. Subject again to some qualifications, the stability criterion for a feedback amplifier is that its polar plot of return difference should not enclose the origin. Figure 4

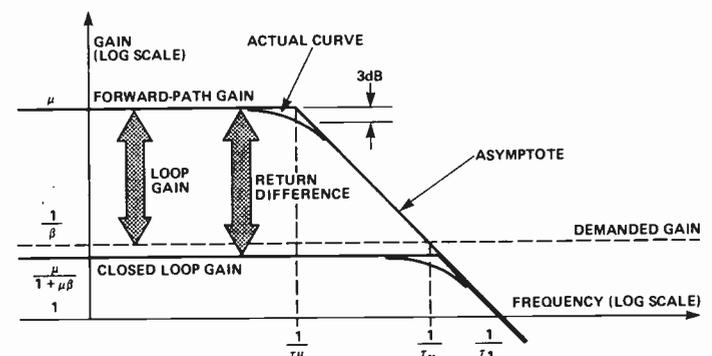


Fig. 3 Logarithmic plots of gain versus frequency for Fig. 1.

shows one example each of a stable situation and an unstable situation.

Because the phase of return difference can be predicted from Fig. 3 via Bode's result a Nyquist diagram can also be constructed from Fig. 3 and the onset of instability can be predicted. In 1945 Bode showed that Nyquist's criterion could in fact be expressed in terms of the gradients of the curves in Fig. 3, thereby eliminating the work of finding the phase explicitly and plotting the Nyquist diagram. Bode's exact rule is complicated, but a useful paraphrase is

"If in graphs such as Fig. 3 the separation between the forward-path gain and demanded gain decreases toward zero at a rate not exceeding 30 dB/decade, the amplifier is unlikely to oscillate."

This paraphrase makes no allowance for the tolerances on components. It assumes, in effect, that everything about the forward path is well known and constant. In the audio context, the paraphrase takes no cognizance of the fact that the capacitance of the leads that connect an amplifier and loudspeaker is anything but well known. A more conservative rule, applicable to the audio context, is therefore

"In graphs such as Fig. 3, the separation between the forward-path gain and demanded gain should not decrease towards zero at a rate exceeding 20 dB/decade."

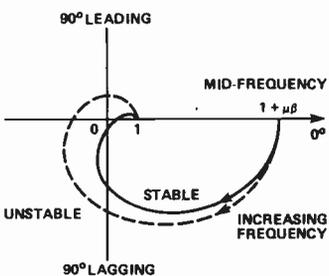


Fig. 4 Nyquist's stability criterion. The curves are polar plots of return difference for changing frequency.

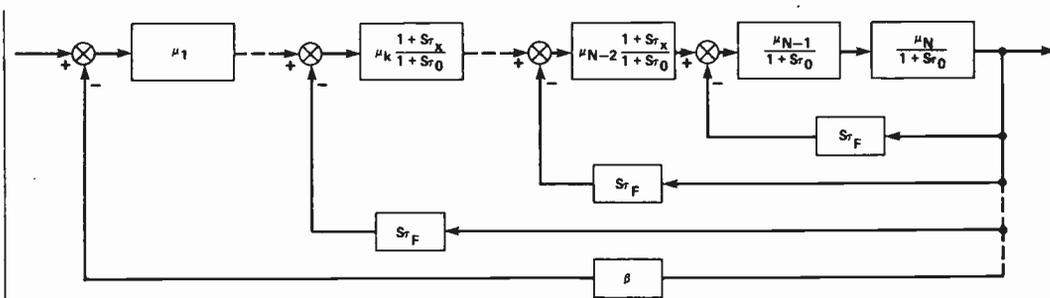


Fig. 5 Block diagram of an NDFL amplifier.

The practical consequence is that the forward path of an audio amplifier with conventional resistive feedback should have a single dominant pole which sets the fall-off of gain at frequencies above $1/\tau_x$. The second and subsequent poles should lie at frequencies substantially above $1/\tau_x$ (the frequency where the separation reaches zero), because each pole contributes a 20 dB/decade downwards slope to the graph of forward-gain path.

Maximum Available Feedback

In Fig. 2, the first stage is a long tailed pair with a current mirror at its output; the input and feedback signals are applied to the two bases to perform the subtraction process of Fig. 1. The second stage provides a large voltage gain, and the lag compensating capacitor C provides the dominant pole of the forward path corresponding to $1/\tau_x$ in Fig. 3. The third stage is a complementary class-B emitter follower whose function is to transfer the output voltage from the second stage to the loudspeaker load. In practice, the transistors in the second and third stages are often Darlington's, and the input transistors are often replaced by FETs.

In any similar amplifier, there is at least one pole associated with the finite transit time of electrons through each transistor. The transit time for typical small-signal

transistors is a fraction of a nanosecond, but for power transistors of the ubiquitous 2N3055 class the transit time may be as long as a few tenths of a microsecond. Thus, the output stage of Fig. 2 may have a pole in the vicinity of 1 MHz.

As we saw in the previous section, the unity-loop-gain frequency $1/\tau_x$ in Fig. 3 must be substantially less than the frequency of all poles except the dominant pole $1/\tau_x$ if an amplifier is to be stable. If the power transistors are of the 3055 class then, no matter how fast the other transistors may be, there is going to be one pole at about 1 MHz. Therefore $1/\tau_x$ must be chosen to correspond to something like 200 kHz. Even with more modern power transistors, $1/\tau_x$ is restricted to about 1 MHz. The art of designing a stable power amplifier involves choosing the lag compensating capacitor C such that $1/\tau_x$ is appropriate to the transistors actually used.

The geometry of Fig. 3 is such that, no matter how μ , β and τ_x are separately chosen, the return difference $F(\omega)$ at any angular frequency ω cannot exceed

$$F(\omega) \leq 1/\omega\tau_x \quad (8)$$

Thus, if $1/\tau_x$ is designed to correspond to 200 kHz, return difference at 20 kHz cannot exceed 10 (= 20 dB), and cannot exceed 200 (= 46 dB) at 1 kHz. An amplifier that boasts 80 dB of feedback ($F = 10,000$ at low frequencies) must have $1/\tau_x$ corresponding to about 20 Hz; return difference must begin falling above 20 Hz, and the former

values at 1 kHz and 20 kHz (46 dB and 20 dB) still apply.

Returning now to Equation 7, the effectiveness of feedback in reducing distortion is set by the frequency of the distortion, not the frequency of the input. The audible frequency range is generally reckoned to extend to about 20 kHz and, with the foregoing constraints, return difference at this frequency cannot exceed 10. Remembering that 20 kHz is the third harmonic of 6.667 kHz, we see that feedback cannot reduce offensive odd-harmonic distortion of mid-treble input signals by more than a factor of 10. Remembering too that 20 kHz is the seventh harmonic of 2.857 kHz, we see that feedback cannot reduce crossover distortion of mid-range input signals by more than a factor of 10.

Until recently there has been no way around this problem except to increase the unity-loop-gain frequency $1/\tau_x$, and this demands that the frequencies of the transistor poles must be increased if stability is to be preserved. Fragile, expensive power transistors, with narrow bases to achieve short transit times, become mandatory.

The NDFL Approach

There is, however, another solution to the stability problem. If the forward-path gain has two dominant poles, so that its gain falls at 40 dB/decade, the rate of closure

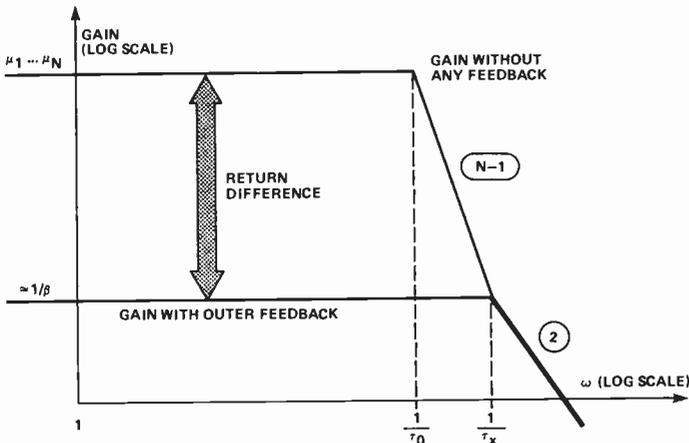


Fig. 6 Logarithmic plots of gain versus frequency for Fig. 5.

between the graphs of forward-path gain and demanded gain would still be 20 dB/decade provided the demanded gain itself were to fall at 20 dB/decade. In essentials, this requires that the usual frequency-independent resistive feedback factor β should be replaced by something having a frequency dependence of the form $\omega\tau_f$ (remember that the demanded gain is the reciprocal of the feedback factor). Mathematicians tell us that a linearly rising frequency response corresponds to differentiation with respect to time and, in hardware terms, a capacitive feedback network will perform just this action.

Figure 5 shows the outline of an amplifier incorporating nested differentiating feedback loops. Notice first that the forward path has been separated into a number of stages, whose mid-frequency gains are μ_1 to μ_N respectively. The variable s is what mathematicians call complex frequency; for sinusoidal signals its magnitude is equal to the angular frequency ω of the sinusoid. Factors of the form $(1 + s\tau_x)$ represent a frequency response that rises proportional to frequency above the frequency $1/\tau_x$ — that is, they represent a zero. Similarly, factors of the form $1/(1 + s\tau_0)$ represent a frequency response that falls inversely proportional to frequency above the frequency $1/\tau_0$ — that is they represent a pole. Thus, the stages in Fig.

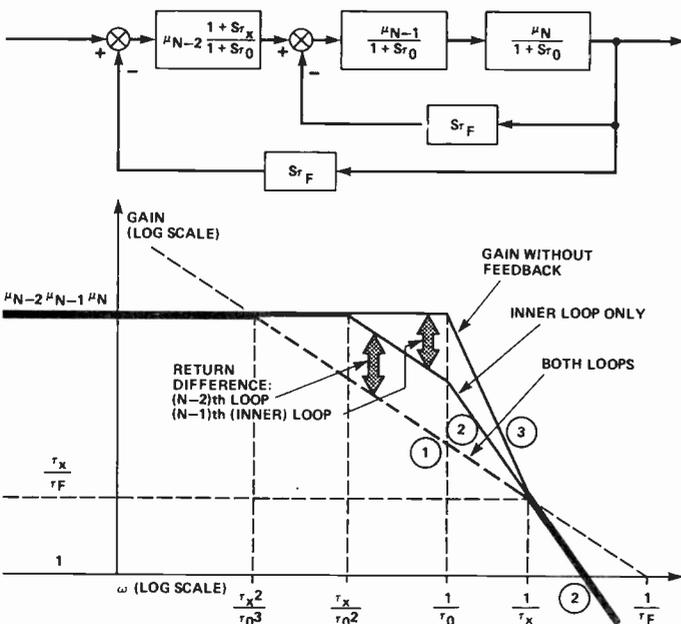


Fig. 8 The (N-2)th loop of Fig. 5.

5 have special frequency responses: all stages except the first have a pole at $1/\tau_0$, and all except the first and last two have a zero at $1/\tau_x$.

Notice also that there are differentiating feedback networks, each denoted by $s\tau_f$, linking the output back to various points in the forward path. The resulting feedback loops are arranged one inside another, like a nest of Chinese boxes — hence the name nested differentiating feedback loops.

The amplifier is completed by an overall resistive feedback network β .

If we removed all the feedback from Fig. 5, the forward-path gain would be shown in Fig. 6: constant up to the frequency $1/\tau_0$, then falling at an $(N-1)$ -pole rate $(20(N-1)$ dB/decade) up to $1/\tau_x$, and finally levelling off somewhat to a two-pole rate (40 dB/decade).

If we now applied just the overall resistive feedback β , the return difference would be as shown in Fig. 6. Distortion would be reduced by a constant large amount, approximately $\mu_1 \mu_2 \dots \mu_N \beta$, at all frequencies up to $1/\tau_0$. Choosing $1/\tau_0$ to correspond to 20 kHz would virtually

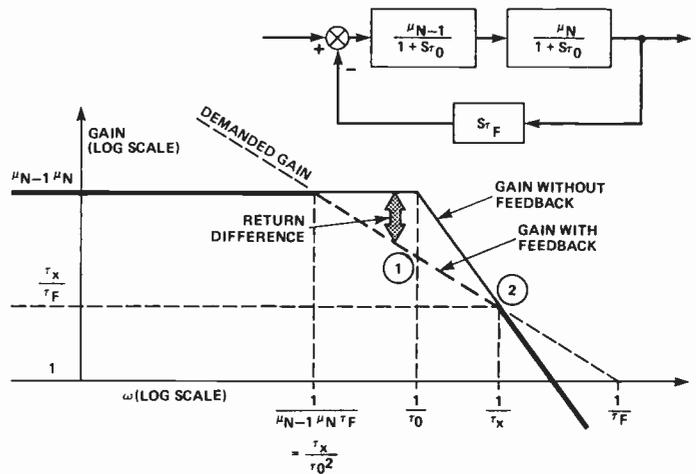


Fig. 7 The inner loop of Fig. 5.

eliminate audible-frequency distortion. *But the amplifier would be unusable because of oscillation.*

The rate of closure of the forward-path gain and demanded gain curves breaks the rule of 20 dB/decade. Let us see how inclusion of the nested differentiating feedback loops solves the problem.

Figure 7 shows just the last two stages and the inner differentiating feedback factor. This 'clump' is a feedback amplifier in its own right, and Fig. 7 shows its forward-path gain (that is, the gain of the last two stages without any feedback), the demanded gain, and the resulting closed-loop gain. Although the forward-path gain falls at a two-pole rate (40 dB/decade), the demanded gain falls at a one-pole rate (20 dB/decade), and their rate of closure is 20 dB/decade. By itself, this 'clump' is stable.

Figure 8 shows what happens when we add the antepenultimate stage and another differentiating feedback factor. Again this 'clump' can be considered as a feedback amplifier in its own right. Provided we choose.

$$\mu_{N-2} = \tau_0/\tau_x$$

the various gains line up as shown. The forward-path gain is the combined gain of stage $(N-2)$ and stages $(N-1)$ and N with their local feedback, and this is the middle solid curve in Fig. 8. The demanded gain is the dashed curve passing through $1/\tau_x$. Once again the forward-path gain and demanded gain close at 20 dB/decade, so the stability criterion is satisfied for this larger 'clump'.

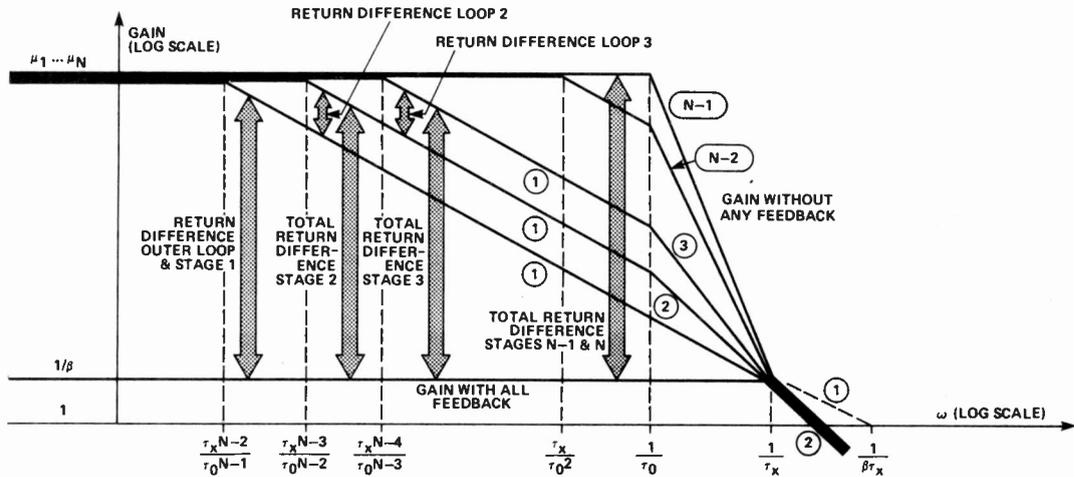


Fig. 9 Complete plots of gain versus frequency for Fig. 5.

And so it goes on. We can add more stages and differentiating feedback factors, and each time the curves line up as required for stability provided we choose

$$\mu_1 \mu_{N-1} \mu_N B = (\tau_0/\tau_x)^2, \quad (9)$$

$$\tau_f = \mu_1 \beta \tau_x, \quad (10)$$

$$\mu_k = \tau_0/\tau_x \text{ for } 2 \leq k \leq N-2. \quad (11)$$

Figure 9 shows the gain curves for the complete amplifier.

In designing an NDFL amplifier, the starting point is to choose the frequency $1/\tau_x$ so that the various transistor poles are sure to lie at substantially higher frequencies. Next choose the frequency $1/\tau_0$ up to which the return difference should remain constant; 20 kHz is a suitable value for audio amplifiers. After this, the circuit more or less designs itself via Equations 9-11. above.

Outline Practical Circuit

Figure 10 shows how an amplifier of the basic topology of Fig. 2 can be modified to include two NDFLs. Interested readers should refer to references 11, 12 for more details.

Notice first that the lag compensating capacitor, C, in the penultimate stage of Fig. 2 has been removed in Fig. 10. In its place are two capacitors (C) linking the output back to various points in the forward path. These capacitors are the feedback networks of the nested differentiating feedback loops.

The output stage has been changed to include a modified form of Thiele's load-stabilising network. Some form of LRC filter is required to locate one of the poles correctly, and with the circuit shown we get double value from the components.

The input stage itself is unchanged, but an inexpensive small capacitor in the overall feedback network β can be used to correct the group delay and improve the reproduction of transient waveforms.

Another essential addition is an amplifying stage between the two nested differentiating feedback factors. This rather peculiar circuit (which dates back to Rush in 1964) seems largely to have been forgotten. It uses one NPN transistor and one

PNP to provide a well-defined gain (13).

As already suggested, once the demanded gain $1/\beta$ and the critical frequency $1/\tau_x$ are chosen, the circuit almost designs itself. The equations are:

$$\frac{R_{F1}}{R_{F1} + R_{F2}} = \beta, \quad (12)$$

$$RC = \beta \tau_x, \quad (13)$$

$$R_V C_V = \tau_x, \quad (14)$$

$$\tau_L = (\sqrt{3} - 1)\tau_x. \quad (15)$$

All stage gains and poles and zeros automatically look after themselves.

Figure 11(a) shows the 5 kHz square-wave response of Fig. 10 as built from 5%-tolerance resistors, 20%-tolerance capacitors, and unselected production transistors. Evidently the circuit is 'designable'; Equations 12-15 really do predict component values for good transient response.

A nice feature of the modified Thiele circuit in Fig. 10 is that, when the load is made capacitive (a well-known source of high-frequency oscillation in amplifiers), the voltage waveform at the FEEDBACK POINT is the waveform the amplifier would have delivered into its nominal resistance load. Figures 11(b) and (c) illustrate this; the violent ringing in Fig. 11(b) is simply an LC resonance between the filter inductor and the load capacitance, and is in no way indicative of approaching instability.

Figure 12 shows details of the 1 kHz sinusoidal response under overdrive conditions. Note the quick,



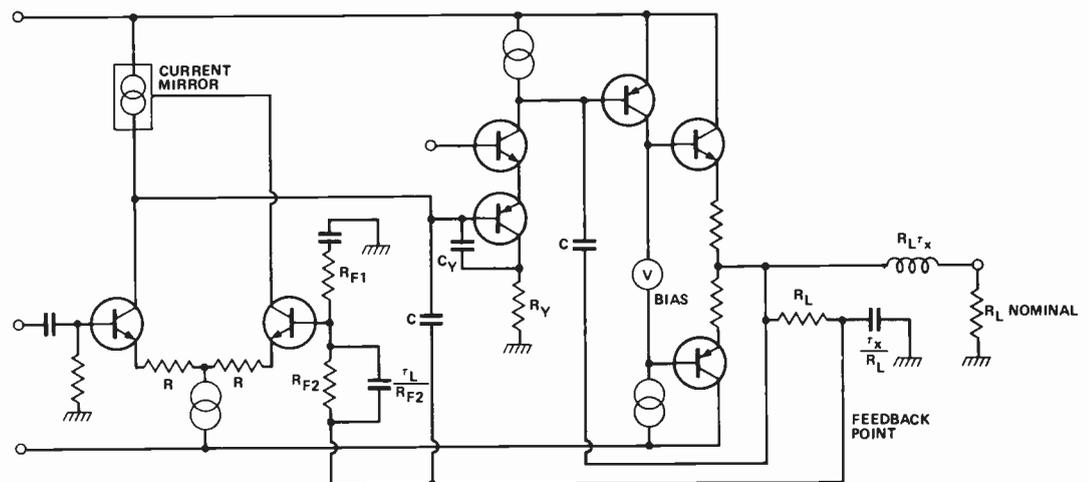


Fig. 10 Outline circuit for an NDFL amplifier.


Fig. 11 5 kHz square wave response of Fig. 10.

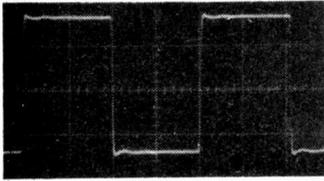

(a) 8 ohm resistance load.

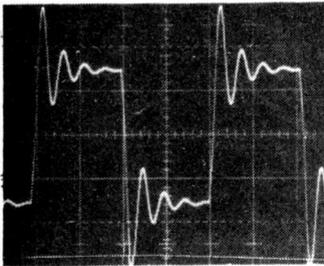

(b) 8 ohm and 2uF parallel load.

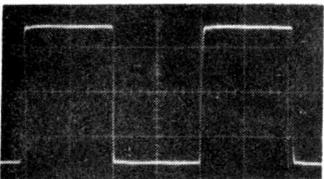

(c) waveform at feedback point for (b).



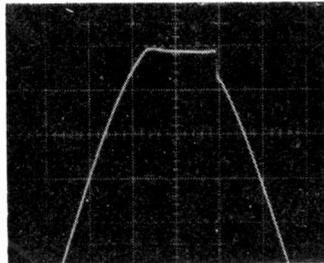


Fig. 12 Detail of output waveform from Fig. 10 under overdrive.

Fig. 14 2 kHz crossover distortion when bias is set wrongly.

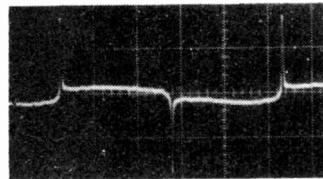

(a) Fig. 2 (conventional amplifier).

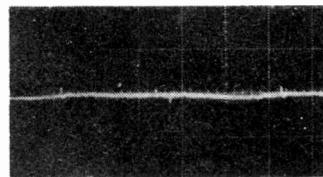

(b) Fig. 10 (NDFL amplifier).

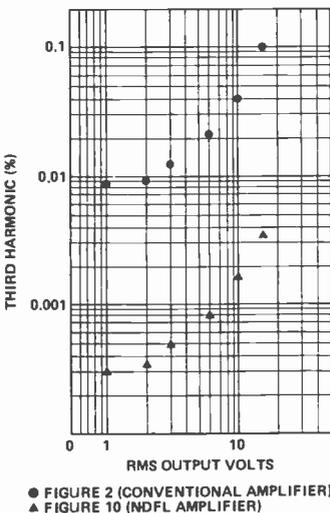


Fig. 13 1 kHz harmonic distortion.

clean recovery.

An amplifier has been built in which the circuit can be switched from Fig. 2 to Fig. 10, to illustrate the improvement in performance of adding two NDFLs. Figure 13 compares the measured third-harmonic distortions of 1 kHz. Notice how the distortion of Fig. 10 drops away to below three parts per million at small signal amplitudes. Such behaviour is more typical of class-A amplifiers than class-B amplifiers, and may account for the clean sound of NDFL amplifiers.

Crossover distortion associated with incorrect bias of the output stage is one of the most audibly annoying forms of distortion. Audio amplifiers based on Fig. 2 sometimes have a type of crossover distortion that does not show up

in normal measurements. Correct biasing of the output stage relies on close tracking of the thermally-compensated biasing device and the power transistors. At best the biasing device can be thermally bonded to the power transistor case. More usually it is bonded to the heatsink, but there is no way it can simultaneously sense the actual junction temperatures of all the power transistors. Under rapidly-fluctuating dynamic signal conditions, the junction temperatures may be wildly different from each other and from the case or heatsink temperatures, and therefore the biasing may be wrong.

Figure 14 compares the static cross-over distortion of Figs. 2 and 10 when the bias is deliberately set OV5 too low. Dynamic mistracking of the biasing circuit should not introduce audible crossover distortion in an NDFL amplifier.

One final point. The NDFL technique maximises the return difference (and hence minimises distortion components) at frequencies up to $1/\tau_0$. Above this frequency the return difference falls away rapidly, and distortion rises. Choosing $1/\tau_0$ to correspond to 20 kHz minimises audible-frequency distortion, but does not minimise ultrasonic distortion.

For example, a common specification for audio power amplifiers is their THD at 20 kHz. The harmonics of 20 kHz lie at 40 kHz, 60 kHz, 80 kHz, and so on. All are ultrasonic (and hence inaudible) and the NDFL technique does not minimise them. A measurement of THD at 20 kHz may therefore give a quite misleading indication of an NDFL amplifier's audible performance. Valid objective tests include the SMPTE and CCIF tests for two-tone intermodulation distortion, the proposed IEC test for TIM (14), Cordell's proposed three-tone test for TIM (15) and the proposed test for input-output intermodulation distortion IOD (6). The distinguishing feature of all these tests is that they measure the distortion at audible frequencies.

References

- W. G. Jung, M. L. Stephens and C. C. Todd, *An overview of SID and TIM*, Audio, vol 63; part 1, pp 59-72, June 1979; part 2, pp 38-47, July 1979; part 3, pp 42-59, August 1979.
- R. R. Cordell, *Open-loop output impedance and interface intermodulation distortion in audio power amplifiers*, 64th Audio Eng Soc Convention, preprint no. 1537, Dec 1979.
- R. R. Cordell, *Another view of TIM*, Audio, vol 64; part 1, pp 38-49, Feb 1980; part 2, pp 42-59, March 1980.
- E. M. Cherry, *Transient intermodulation distortion: Part 1 - hard nonlinearity*, IEEE Trans, vol ASSP-29, pp 137-146, April 1981.
- R. R. Cordell, *Phase intermodulation distortion - instrumentation and measurement results*, 70th Audio Eng Soc Convention, preprint 1842, Nov 1981.
- E. M. Cherry and G. K. Cambrell, *Output resistance and intermodulation distortion of feedback amplifiers*, J. Audio Eng Soc, vol 30, pp 178-191, April 1982.
- E. M. Cherry, *Feedback, sensitivity, and stability of audio power amplifiers*, J. Audio Eng Soc, vol 30, pp 282-294, May 1982.
- E. M. Cherry and K. P. Dabke, *Transient intermodulation distortion: Part 2 - soft nonlinearity*, IEEE Trans, to be published*.
- E. M. Cherry, *Amplitude and phase of intermodulation distortion*, J. Audio Eng Soc, to be published*.
- H. W. Bode, *Network analysis and feedback amplifier design*, van Nostrand (Princeton NJ) 1945.
- E. M. Cherry, *Nested differentiating feedback loops in simple audio power amplifiers*, J. Audio Eng Soc, vol 30, pp 295-305, May 1982.
- E. M. Cherry, *A new result in negative-feedback theory, and its application to audio power amplifiers*, Int J. Circuit Th, vol 6, pp 265-288, July 1978.
- C. J. Rush, *New techniques for designing fast-rise transistor pulse amplifiers*, Rev Sci Instr, vol 35, pp 149-156, Feb 1964.
- IEC Publication 269.3, *Part III - Amplifiers: Clause 22.6 "High-frequency intermodulation distortion"*. (Proposal dated June 1981).
- R. R. Cordell, *A fully in-band multitone test for transient intermodulation distortion*, J. Audio Eng Soc, vol 25, pp 578-586, Sept 1981.

*Manuscript copies available from the author.

MIDWICH COMPUTER COMPANY LIMITED

FAST EX-STOCK DELIVERY OF MICROCOMPUTER COMPONENTS AT UNBEATABLE PRICES

Official **BBC** Dealer

BBC COMPUTERS

Model B 346.95
Model B + Disc Interface 441.95
(carriage 6.50 by Securicon)

BBC MICRO DISC DRIVES

BBC 31 Single 100K Drive Expandable to 2x100K 229.00
BBC 32 Dual 100K Drives 340.00
BBC 33 100K Upgrade for BBC 31 122.00
BBC 34 Dual 400K Drives 649.00

All Disk Drives (except BBC 33) are complete with Manual, Utilities Disc, and Connecting Cables

BBC MICRO UPGRADE KITS

BBCA2B Complete A to B Upgrade 44.75
BBC 1 16K Memory 18.00
BBC 2 Printer/User I/O Kit 7.50
BBC 3 Disc Interface Kit 95.00
BBC 4 Analogue Input Kit 6.70
BBC 5 Serial I/O & RGB Kit 7.30
BBC 6 BUS Expansion Kit 8.45

All Kits are supplied with full fitting instructions.

BBC CONNECTORS

BBC 21 Printer Cable and Amphenol Plug (not assembled) 13.00
BBC 22 User Port Connector and Cable 36" 2.46
BBC 23 Cassette Lead 3.50
BBC 24 7 Pin DIN Plug 0.80
BBC 25 6 Pin DIN Plug 0.80
BBC 26 5 Pin DIN Plug 0.80
BBC 35 Disc I/O Cable 34W IDC to 2x34 way card edge 12.00
BBC 36 Disc Power Cable 6.00
BBC 44 Analogue Input Plug and Cover 2.25
BBC 66 IM Bus Connector + 36" Cable 3.50

BBC ACCESSORIES

BBC 45 Joysticks (per pair) 11.30
BBC 67 EPROM Programmer (assembled) 57.95
BBC 71 Teletext Receiver 225.00
BBC 72 Second Processor (6502) 170.00
BBC 73 Second Processor (Z80) 170.00

ACORN SOFTWARE FOR THE BBC

SBE03 Business Games 8.65
SBE04 Tree of Knowledge 8.65
SBE02 Peeko Computer Inc. Manual 8.65
SBE01 Algebraic Manipulation Pk 8.65
SBX01 Creative Graphics Cassette 8.65
SBX02 Graphics and Charts Cassette 8.65
SBB01 Desk Diary inc Manual 8.65
SBL02 LSP Cassette 14.85
SBL01 FORTH Cassette 14.85
SBG01 Philosophers' Quest 8.65
SBG07 Sphinx Adventure 8.65
SBG03 Monsters 8.65
SBG04 Snapper 8.65
SBG15 Planetoid 8.65
SBG06 Arcade Action 10.35
SBG05 Rocket Raid 8.65
SGB13 Meteors 8.65
SGB14 Arcadians 8.65
SGB10 Chess 8.65

ACORN SOFTWARE BOOKS FOR THE BBC MICRO

SBD01 Creative Graphics 7.50
SBD02 Graphs and Charts 7.50
SBD04 LSP 7.50
SBD03 FDRTH 7.50

Please ring for current delivery on Acornsoft Products before ordering.

BBC MICRO COMPONENTS

4516 100ns 2.25
6522 3.19
74LS244 0.59
74LS245 0.89
74LS163 0.34
DS3691N 4.50
DS88LS120N 4.50
UPD7002 4.50

BBC SOFTWARE IN EPROM

Wordprocessor 'View' 52.00
1.2 MOS 10.00

SPECIAL OFFER

Spectrum 32K Upgrade Kit **24.95**

DATA SHEETS are available on items marked D. Prices are as follows:

D1 0.75
D2 1.00
D3 1.25
D4 2.00
D5 2.50
D6 3.00
D7 4.00

MEMORIES

2114L-200ns D1 0.80
2708 450ns D2 2.95
2716 450ns D1 2.45
2716 350ns D1 4.95
2716 3 rail D1 7.25
2532 450ns D2 3.45
2732 450ns D1 3.45
2732 350ns D1 5.45
2764 300ns D1 5.99
4116 150ns D2 0.85
4116 200ns D2 0.80
4118 150ns D1 3.25
5516 200ns D2 9.45
6116 150ns D1 3.30
6116 Low Power 150ns D2 4.95
4164 150ns TI D3 4.45
4164 200ns TI D3 3.95
4164 150ns Mostek D3 4.45
4516/4816 100ns D2 2.25
4532 200ns D2 2.95

8800 FAMILY

6800 D7 2.25
6802 D5 2.50
6809 D6 6.30
6810 D1 1.15
6821 D3 1.00
6840 D4 3.75
6845 D5 6.50
6850 D2 1.10
68488 D2 7.30
68800 D7 5.25
68809 D6 12.00
68B10 D1 2.26
68B21 D3 2.20
68B40 D4 6.00
68B50 D2 2.20

Z80 FAMILY

Z80ACPU D2 2.99
Z80BCPU D2 9.00
Z80ACTC D1 2.80
Z80BCTC D1 9.00
Z80ADART D1 5.50
Z80ADMA D2 6.95
Z80BP10 D1 2.75
Z80BP10 D1 9.00
Z80AS10 D4 9.00

8080 FAMILY

8085A D4 3.50
8212 1.10
8216 1.00
8224 2.10
8228 3.27
8251A D5 2.50
8253 4.00
8255A D5 2.25

6500 FAMILY

6502 D3 3.25
6502A D3 5.00
6520 D1 2.50
6520A D1 3.18
6522 D5 3.19
6522A D5 5.50
6532 D2 5.50

FLOPPY DISC CONTROLLERS

8271 36.00
FD1771 D5 15.00
FD1791 D6 22.00
FD1793 D6 23.00
FD1795 D6 28.00
FD1797 D6 28.00
WD1691 D2 12.00
WD2143-01 D2 6.99

INTERFACE DEVICES

6402 3.80
75107 0.47
75110 0.56
75150 0.84
75154 0.77
75160 2.56
75161 2.80
75162 3.95
75172 1.95
75173 1.44
75174 1.95
75175 1.44
75182 0.50
75183 0.50
75188 0.37
75189 0.37

75451 0.22
75452 0.22
75453 0.22
75454 0.22
75468 0.88
75491 0.31
75492 0.42
AY31015 D2 3.00
AY31270 6.47
AY38910 D6 4.40
AY53600 D2 6.70
DP8304 D1 2.50
MC1488 D1 0.37
MC1489 D1 0.37
MC3242A 6.30
MC3446 D1 2.50
MC3448A D1 3.75
MC3480 D5 7.30
MC3487 D1 2.00
MC14411 D1 7.65
MC14412 9.45
R032513L D1 6.50
R032513U D1 6.50

UMF MODULATORS

UM1111 6MHz D1 2.60
UM1233 8MHz D1 3.90

BUFFERS

81LS95 0.80
81LS96 0.80
81LS97 0.80
81LS98 0.80
81T26A 0.90
81T28A 0.90
81T95 0.90
81T97A 0.90
81T98 0.90

LINEARS

L201 0.65
LF398N 4.75
LM301AN 0.24
LM308N 0.48
LM311P 0.50
LM319N 1.99
LM324AN 0.30
LM348N 0.60
NE555P 0.16
NE556CP 0.45
TL010 0.39
TL011 0.32
TL012 0.34
TL014 0.36
TL021 0.34
TL061 0.29
TL062 0.49
TL064 0.98
TL066 0.29
TL068 0.32
TL071 0.29
TL072 0.47
TL074 1.00
TL081 0.28
TL082 0.46
TL084 1.58
TL091 0.40
TL092 0.58
TL094 1.34
TL487 0.82
TL489 0.82
TL494 1.63
TL496 0.60
TL507 1.33
725 1.80
741 0.14
747 0.48
748 0.27

REGULATORS

78L05 0.30
78L12 0.30
78L15 0.30
7805 0.40
7812 0.40
7815 0.40
7905 0.45
7912 0.45
7915 0.45
LM309K 1.20
LM317K 2.40
LM323K 4.50
LM338K 6.25

DATA CONVERTERS

UPD7002 D1 4.28
ZN425 D1 3.45
ZN426 D1 3.00
ZN427 D1 5.99
ZN428 D1 4.75

ZN429 D1 2.10
ZN432 D1 13.00
ZN449 D1 2.55

CRYSTALS

1M 2.75
1008M 2.75
1032M 1.92
24576M 2.00
36864M 1.88
4M 0.64
6M 0.86
8M 0.86
98304 1.68
196608 2.48

OIL SOCKETS (TEXAS)

PINS TIN GOLD WW
8 7 16 25
14 10 28 35
16 10 29 40
18 13 33 50
20 15 37 60
22 17 38 65
24 21 46 70
28 24 55 80
40 30 76 99

ZIF SOCKETS (TEXT00L)

24 pin 5.75
28 pin 8.20
40 pin 9.75

CMOS 4000

4000 0.10
4001 0.10
4002 0.12
4006 0.42
4007 0.14
4008 0.32
4009 0.24
4010 0.24
4011 0.10
4012 0.16
4013 0.20
4014 0.40
4015 0.36
4016 0.20
4017 0.32
4018 0.36
4019 0.38
4020 0.36
4021 0.40
4022 0.40
4023 0.13
4024 0.32
4025 0.13
4026 0.74
4027 0.20
4028 0.32
4031 0.84
4033 0.86
4034 0.94
4035 0.38
4040 0.36
4041 0.36
4042 0.34
4043 0.36
4044 0.36
4045 1.35
4046 0.42
4047 0.70
4048 0.38
4049 0.34
4050 0.23
4051 0.38
4052 0.44
4053 0.44
4054 0.85
4055 0.85
4060 0.39
4063 0.85
4066 0.24
4068 0.14
4069 0.14
4070 0.13
4071 0.13
4072 0.13
4073 0.14
4075 0.13
4076 0.43
4077 0.13
4078 0.15
4081 0.13
4082 0.13
4085 0.50
4086 0.44
4093 0.20
4502 0.46
4507 0.32
4508 0.86

4510 0.40
4511 0.41
4512 0.40
4514 0.98
4515 0.98
4516 0.98
4518 0.40
4519 0.27
4520 0.40
4521 0.90
4522 0.52
4526 0.52
4527 0.52
4528 0.41
4532 0.72
4541 0.50
4543 0.50
4553 1.57
4555 2.59
4556 0.35
4585 0.75

74LS SERIES

00 0.11
01 0.11
02 0.11
03 0.12
04 0.12
05 0.12
08 0.12
10 0.12
11 0.12
12 0.12
13 0.12
14 0.25
15 0.12
20 0.12
21 0.12
22 0.12
26 0.12
27 0.12
28 0.12
29 0.12
30 0.12
32 0.12
33 0.12
34 0.12
37 0.12
40 0.12
42 0.28
47 0.35
48 0.45
49 0.45
51 0.12
54 0.12
55 0.12
73 0.18
74 0.16
75 0.18
76A 0.17
78A 0.18
83A 0.36
85 0.42
86 0.16
90 0.22
91 0.60
92 0.32
93 0.22
95B 0.40
109A 0.27
112A 0.20
113A 0.20
114A 0.22
122 0.28
123 0.34
125A 0.24
126A 0.25
132 0.34
136 0.25
139 0.27
145 0.57
148 0.70
151 0.40
153 0.40
155 0.30
157 0.25
158 0.30
160A 0.32
161A 0.35
162A 0.35
163A 0.35
164 0.40
165A 0.50
166A 0.80
173A 0.55
174 0.40
175 0.36
181 0.90
190 0.35
191 0.35
192 0.35

193 0.35
194A 0.35
195A 0.35
196 0.45
197 0.45
221 0.46
240 0.55
241 0.55
242 0.55
243 0.55
244 0.55
245 0.70
248 0.55
249 0.55
251 0.30
253 0.35
257 0.30
258A 0.35
259 0.55
261 1.00
266 0.20
273 0.54
279 0.30
283 0.40
290 0.39
291 0.30
293 0.12
365 0.27
366 0.12
367 0.27
368 0.27
373 0.82
374 0.82
375 0.35
377 0.60
378 0.60
379 0.90
386 0.35
390 0.45
393 0.45

OIL JUMPERS

Shie Ended 24" 5' 12" 18"
14 PIN 1.45
16 PIN 1.85
24 PIN 2.40
40 PIN 3.80

Double Ended

14 PIN 1.85 1.99 2.42
16 PIN 2.05 2.15 2.68
24 PIN 3.00 3.15 3.96
40 PIN 4.65 4.90 6.18

25 WAY D-TYPE CONNECTORS

Male-Male 12.00
Male-Female 12.00
Male single ended 18" cable 4.95
Female single ended 18" cable 3.95

IOC CONNECTORS

Shrouded Headers (with ejectors) (Right Angle PCB Mtg) 0.86
10 PIN 1.22
16 PIN 1.34
20 PIN 1.46
26 PIN 1.76
34 PIN 2.06
40 PIN 2.32
50 PIN 2.35
60 PIN 3.20

IOC SOCKETS

Fitted with 36" cable
10 PIN 1.40
14 PIN 1.82
16 PIN 2.10
20 PIN 2.46
26 PIN 3.24
34 PIN 3.80
40 PIN 4.90
50 PIN 5.48
60 PIN 6.38

DATA BOOKS by Texas Instruments

Linear Control Circuits 4.00
Voltage Regulators 4.50
MOS Memory 3.95
Interface Circuits 7.00
TTL 5th Edition 8.50
Bipolar Micro 4.50
TTL Pocket Guide 3.50
Linear Pocket Guide 2.50

CARRIAGE Orders up to £199 sent by 1st class post and £200+ by Securicon.

CHARGES 0-£100 = £0.50, £100-199 = £1.25, £200+ = £5.00.
PRICES All prices and carriage charges quoted are exclusive of VAT and are subject to change without notice.

QUANTITY DISCOUNTS Available on most products. Please telephone for details.

OFFICIAL ORDERS are welcome from Educational Establishments, Government Bodies and Public Companies



BARCLAYCARD
VISA

CREDIT ACCOUNTS Are available subject to status. Payment strictly nett 30 days.

CREDIT CARDS Payment by credit cards is accepted on most products with no surcharge.

OUT OF STOCK Items out of stock will follow with £0.45 Carriage charge at our discretion, or a refund will be issued if requested.

DELIVERY All stock orders received up to 3.30pm are despatched the same day.

MIDWICH COMPUTER COMPANY LIMITED

DEPT ET1, RICKINGHALL HOUSE, RICKINGHALL, SUFFOLK IP22 1HH
TELEPHONE (0379) DISS 898751

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC20 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. Prices include postage and packing. Prices may be subject to change without notice.

BEGINNERS GUIDES

- Beginner's Guide to Basic Programming Stephenson £4.95
- Beginner's Guide to Digital Electronics £4.95
- Beginner's Guide to Electronics £4.95
- Beginner's Guide to Integrated Circuits £4.95
- Beginner's Guide to Computers £4.95
- Beginner's Guide to Microprocessors £4.95

COOKBOOKS

- Master IC Cookbook Hallmark £8.65
- Microprocessor Cookbook M. Hordeski £6.60
- IC Op Amp Cookbook Jung £13.15
- PLL Synthesiser Cookbook H. Kinley £6.60
- Active Filter Cookbook Lancaster £12.00
- TV Typewriter Cookbook Lancaster £9.95
- CMOS Cookbook Lancaster £10.85
- TTL Cookbook Lancaster £10.00
- Micro Cookbook Vol. 1 Lancaster £14.00
- BASIC Cookbook K. Tracton £5.20
- MC6809 Cookbook C. Warren £5.95

ELECTRONICS

- Principles of Transistor Circuits Amos £8.50
- Design of Active Filters with experiments Berlin £10.40
- 49 Easy to Build Electronic Projects Brown £5.20
- Electronic Devices & Circuit Theory Boylestad £11.95
- How to build Electronic Kits Capel £3.55
- How to Design and build electronic instrumentation Carr £7.95
- Introduction to Microcomputers Daglecs £7.20
- Electronic Components and Systems Dennis £15.00
- Principles of Electronic Instrumentation De Sa £11.40
- Giant Handbook of Computer Software £11.00
- Giant Handbook of Electronic Circuits £14.75
- Giant Handbook of Electronic Projects £9.95
- Electronic Logic Circuits Gibson £5.55
- Analysis and Design of Analogue Integrated Circuits Gray £26.95
- Basic Electronics Grob £10.50
- Lasers — The Light Fantastic Hallmark £6.60
- Introduction to Digital Electronics & Logic Joynson £5.25
- Electronic Testing and Fault Diagnosis Loveday £6.60
- Electronic Fault Diagnosis Loveday £5.75
- Essential Electronics A-Z Guide Loveday £7.20
- Microelectronics Digital & Analogue circuits and systems Millman £11.80
- 103 Projects for Electronics Experimenters Minis £7.25
- VLSI System Design Muroga £30.00
- Power FETs and their application Oxner £23.00
- Practical Solid State Circuit Design Olesky £8.40
- Master Handbook of IC Circuits Powers £10.95
- Electronic Drafting and Design Raskhodoff £21.85
- VOM — VTVM Handbook Risse £7.25
- Video and Digital Electronic Displays Sherr £25.40
- Understanding Electronic Components Sinclair £7.50
- Electronic Fault Diagnosis Sinclair £4.50
- Physics of Semiconductor Devices Sze £14.50
- Digital Circuits and Microprocessors Taub £32.00
- Active Filter Handbook £6.50
- Designing with TTL Integrated Circuits Texas £14.00
- Transistor Circuit Design Texas £14.00
- Digital Systems: Principles and Applications Tocci £11.85
- Master Handbook of Telephones Traister £8.65
- How to build Metal/Treasure Locators Traister £5.20
- 99 Fun to Make Electronic Projects Tymony £7.25
- 33 Electronic Music Projects you can build Winston £5.95

COMPUTERS & MICROCOMPUTERS

- BASIC Computer Games Ahl £6.35
- From BASIC to PASCAL Anderson £7.95
- Mastering Machine Code on your ZX81 T. Baker £6.95
- UNIX — The Book Banaham £7.80
- Z80 Microcomputer Handbook Barden £10.00
- Microcomputer Maths Barden £10.75
- Digital Computer Fundamentals Barter £9.20
- Visicalc Book. APPLE Edition Bell £14.50
- Visicalc Book. ATARI Edition Bell £14.50
- Introduction to Microprocessors Brunner £22.00
- Programming your APPLE II Computer Bryan £7.95
- Microprocessor Interfacing Carr £6.60
- Microcomputer Interfacing Handbook A/D & D/A Carr £8.10
- Musical Applications of Microprocessors Chamberlain £25.50
- 30 Computer Programs for the Home Owner in BASIC D. Chance £7.95
- Microcomputers Dirkson £7.95
- APPLE Personal Computer for Beginners Dunn £8.50
- Microcomputers/Microcomputers — An Intro Gioone £10.90
- Troubleshooting Microprocessors and Digital Logic Goodman £7.95

- Getting Acquainted with your VIC 20 Hartnell £8.50
- Getting Acquainted with your ZX81 Hartnell £5.95
- Let your BBC Micro Teach you to program Hartnell £7.90
- Programming your ZX Spectrum Hartnell £8.50
- The ZX Spectrum Explored HArtnell £6.95
- How to Design, Build and Program your own working Computer System Haviland £7.95
- BASIC Principles and Practice of Microprocessors Heffer £7.15
- Hints and Tips for the ZX81 Hewson £5.25
- What to do when you get your hand on a Microcomputer Holtzman £8.65
- 34 More Tested Ready to Run Game Programs in BASIC Horn £6.60
- Microcomputer Builders' Bible Johnson £10.75
- Digital Circuits and Microcomputers Johnson £13.00
- PASCAL for STudents Kemp £7.20
- The C — Programming Language KERNIGHAN £17.20
- COBOL Jackson £7.95
- The ZX81 Companion Maunder £9.50
- Guide to good Programming Practice Meek £5.70
- Principles of Interactive Computer Graphics Newman £12.95
- Theory and Practice of Microprocessors Nichols £11.35
- Exploring the World of the Personal Computer Nilles £11.35
- Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll £8.90
- Beginner's Guide to Microprocessors Parr £5.10
- Microcomputer Based Design Peatman £10.50
- Digital Hardware Design Peatman £9.10
- BBC Micro Revealed Ruston £9.45
- Handbook of Advanced Robotics Safford £12.15
- 1001 Things to do with your own personal computer Sawusch £7.50
- Easy Programming for the ZX Spectrum Stewart £7.15
- Microprocessor Applications Handbook Stout £34.40
- Handbook of Microprocessor Design and Applications Stout £37.60
- Programming the PET/CBM West £17.80
- An Introduction to Microcomputer Technology Williamson £6.20
- Computer Peripherals that you can build Wolfe £10.50
- Microprocessors and Microcomputers for Engineering Students and Technicians Wooland £6.60

REFERENCE BOOKS

- Electronic Engineers' Handbook Fink £56.45
- Electronic Designers' Handbook Giacometto £59.55
- Illustrated Dictionary of Microcomputer Technology Hordeski £7.25
- Handbook for Electronic Engineering Technicians Kauffman £27.50
- Handbook of Electronic Calculators Kauffman £34.40
- Modern Electronic Circuit Reference Manual Marcus £40.70
- International Transistor Selector Towers £10.70
- International Microprocessor Selector Towers £16.00
- International Digital IC Selector Towers £10.95
- International Op Amp Linear IC Selector Towers £8.50
- Illustrated Dictionary of Electronics Turner £12.95

VIDEO

- Servicing Home Video Cassette Recorders Hobbs £11.80
- Complete Handbook of Videocassette Recorders Kybett £7.95
- Theory and Servicing of Videocassette Recorders McGinty £11.95
- Beginner's Guide to Video Matthewson £5.20
- Video Recording: Theory and Practice Robinson £14.40
- Video Handbook Van Wezel £21.90
- Video Techniques White £12.95

Please send me the books indicated. I enclose cheque/postal order for £
Prices include postage and packing.
I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4				
4	9	2	9				


Signed

Name

Address


.....
.....
.....

GET BIG POWER

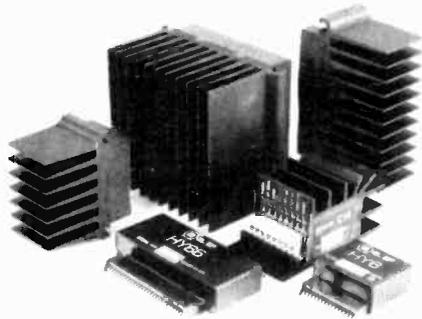

Modular Amplifiers the third generation

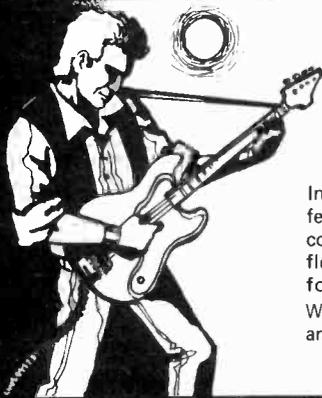Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ μ s. Risettime: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

WITH A LOT OF HELP FROM



PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

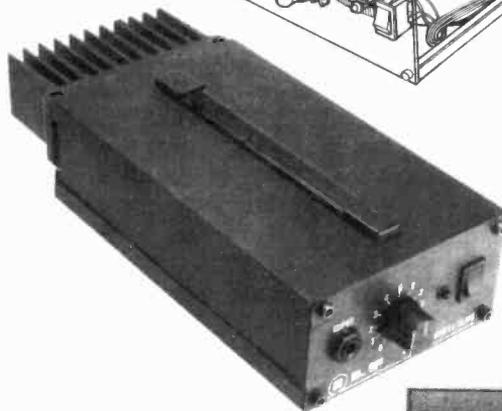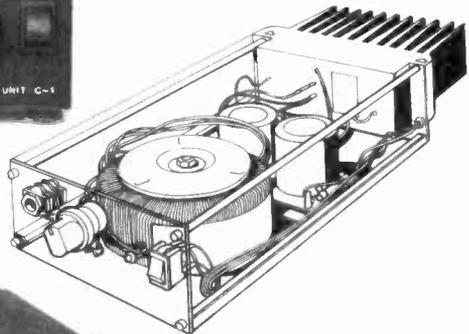Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED

UNICASES

HiFi Separates						Price inc. VAT
UC1	Preamp					£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi		£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi		£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi		£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi		£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi		£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi		£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi		£84.95
Power Slaves						
US1X	60W/4 Ω	Bipolar	Power	Slave		£59.95
US2X	120W/4 Ω	Bipolar	Power	Slave		£79.95
US3X	60W/4-8Ω	MOS	Power	Slave		£69.96
US4X	120W/4-8Ω	MOS	Power	Slave		£89.95

Please note X in part number denotes mains voltage. Please insert 'O' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.



Post to: ILP Electronics Ltd., Freepost 4, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone: (0227) 54778. Technical: (0227) 64723. Telex: 965780.

Please send me the following _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

ORGAN PART 3

Design by Richard Watts.

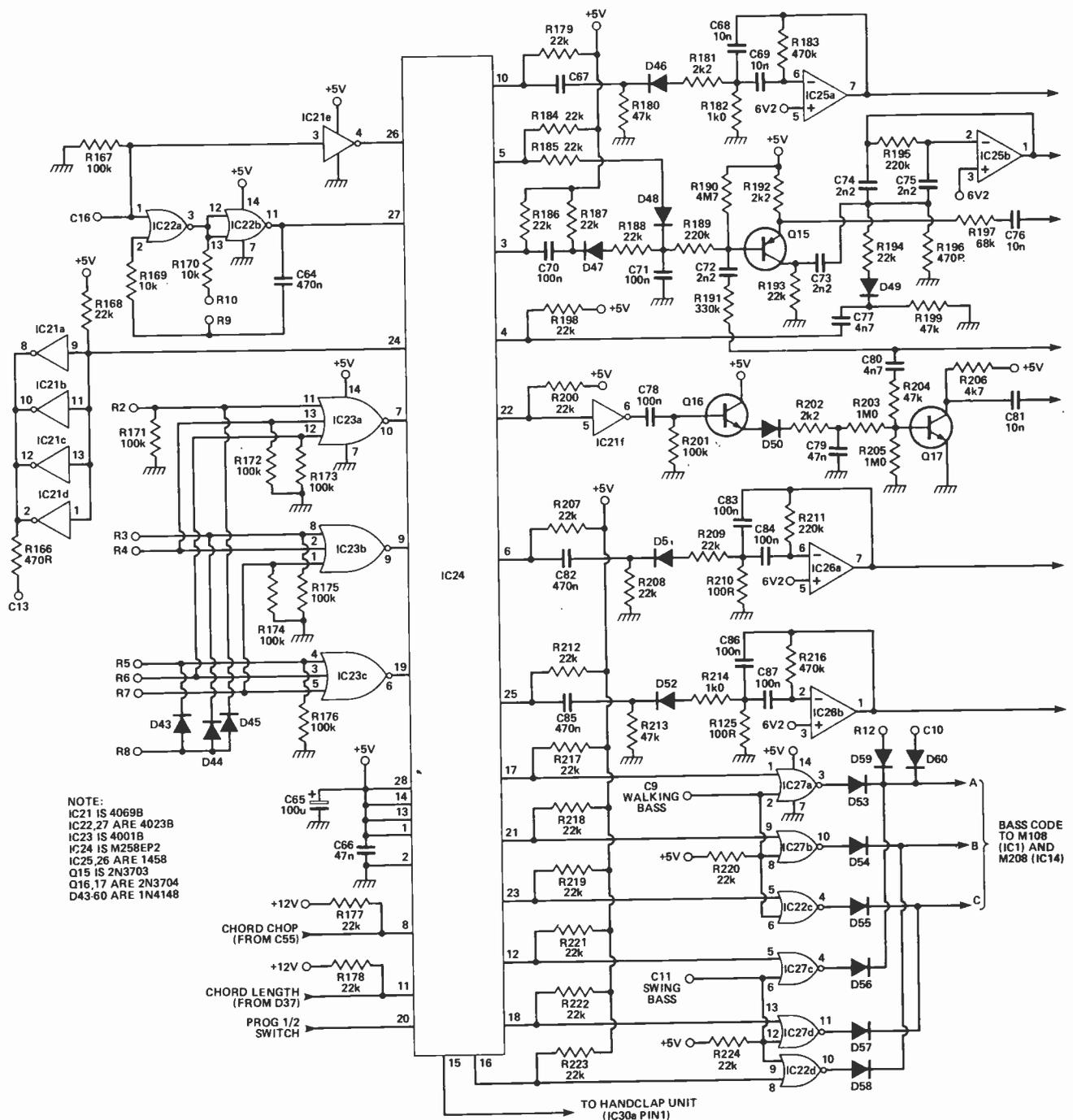


Fig. 1 Circuit diagram of the rhythm section of the Victory organ, including the handclap generator.

This month we conclude the description of the organ circuitry ready for the constructional notes next month. Before doing so, some minor notational changes are required due to continuing development work on the prototype and the consequent re-allocation of certain switches. In Fig. 1 of the February article, the terminal marked R15 (by D6) is now C17, and the terminal marked C15 in Fig. 4 of last month's article should be connected to +12 V, not +5 V. Mark these changes, spread out the two previous issues for reference, and away we go with the rhythm unit.

I Got Rhythm

The heart of the rhythm unit is the M258 ROM (IC24). This has a maximum capacity of 8K, organised as 16 rhythms of 32 counts with 16 outputs. In fact this is not all used, as some rhythms have only a 24 count requirement. All inputs to and outputs from the IC are active low.


When the rhythm on/off switch is on, connector C13 is taken low. This low is applied to inverter IC21e, which causes a high to be input to pin 26 of the ROM. Although this is a bi-directional connection capable of outputting sync pulses, it is used in this

case as the reset input. The low on terminal C16 is also taken to pin 1 of IC22a. This NOR gate, together with IC22b, R169, R170, C64 and the tempo potentiometer (which is connected across terminals R9, R10) form the rhythm clock generator. The clock input is supplied to pin 27 of the M258. Selection of a rhythm is achieved by switching four input lines (pins 7, 19, 9 and 20) which the IC then decodes using an internal four-to-16 line decoder.

The 16 rhythms are available from nine switches such that each of the first eight is used for two rhythms, called up by the ninth switch (called program 1/2). The eight rhythm switches are mechanically latched and self-cancelling on a new selection. The switches connect +5 V to each of the terminals R2 to R8 which connect to triple three-input NOR gate IC25, used here as an eight-to-three line encoder. Notice that the leftmost rhythm switch does not connect to any points, but due to the mechanical cancelling action of the switches removes +5 V from any of the NOR gate inputs, thus giving the eighth state of all outputs high. The program selector switch provides the fourth bit of information to pin 20 of IC24. The final input requirements are that pins 28, 14, 3 and 1 be at +5 V and pin 2 at ground. This covers the input requirements for the M258: now to the outputs.

Timing within the M258 is arranged such that each count of a rhythm lasts for two cycles of the clock input. The 16 active-low outputs normally remain active for one clock cycle only, but eight of them have the option that they may remain active for the whole count (two clock cycles). This gives the facility of selecting whether the output is pulsed per clock cycle or can be either high or low. In the first state the output must always return to high; in the second it may not, depending on programming. In this ETI organ application pins 5 and 11 are programmed in the second manner: their full purpose in life will be described later.

Output pins 17, 21, 23, 12, 18 and 16 are all used to control the automatic bass patterns when the walking bass 1 and 2 features are selected. If walking bass 1 is selected, point C9 is taken low and enables the NOR gates on the outputs from pins 17, 21 and 23. These gates act as inverters and supply positive pulses through diodes D53-55 to pins 8-10 of both the M108 and M208 ICs. ▶

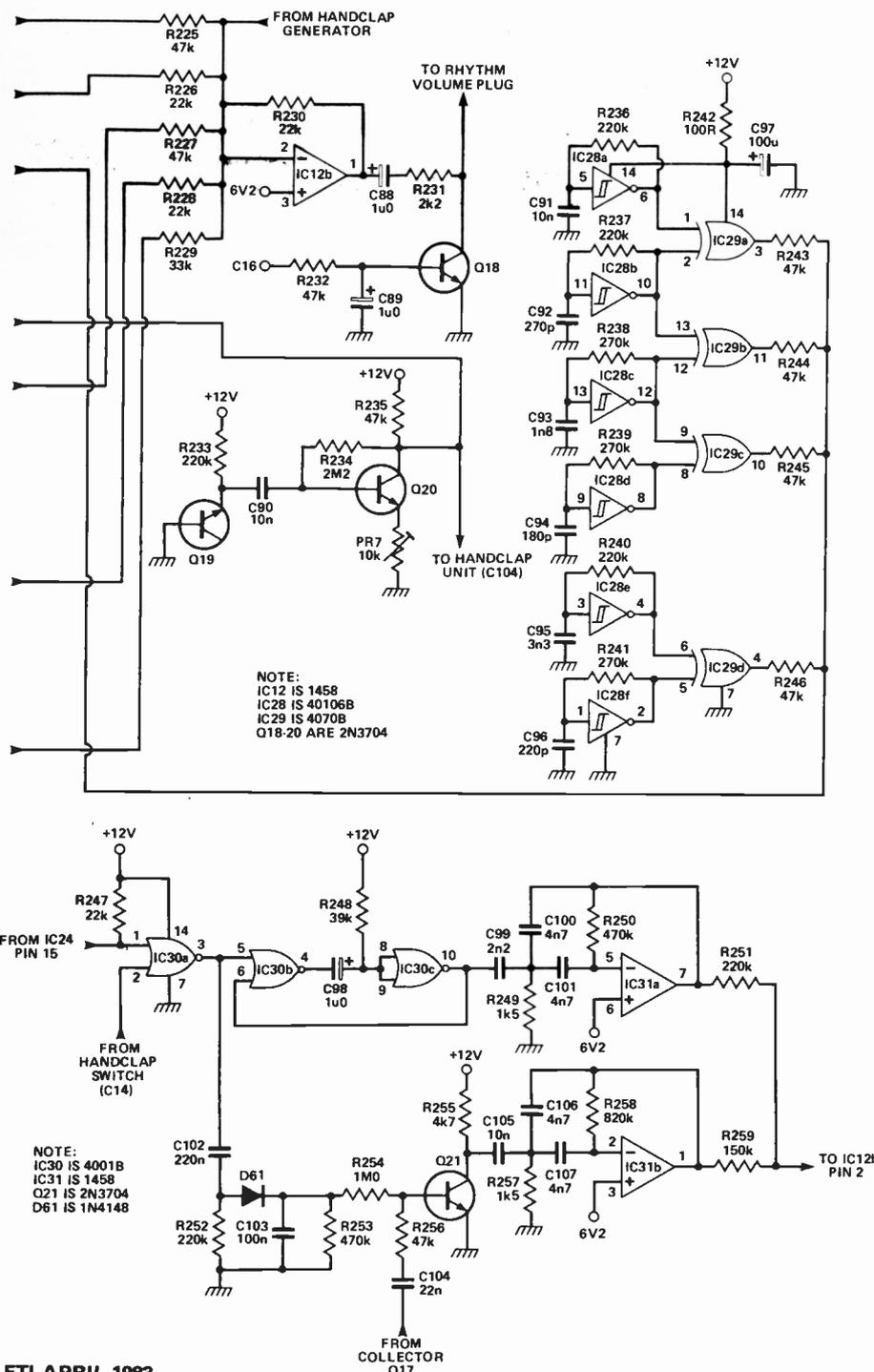

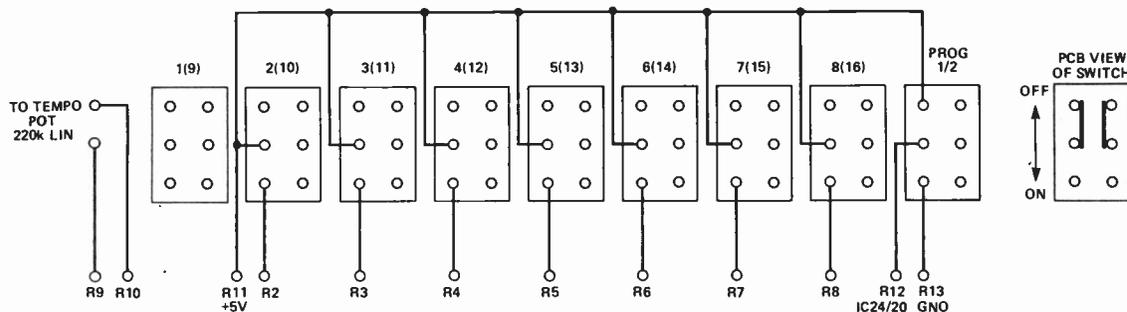


Fig. 2 Connection details for the rhythm switch.

The effect of this is to cause any bass note being played (from either the lower keyboard or the pedals) to be varied in accordance with the codes appearing on pins 8-10. When walking bass 2 is selected, point C9 is pulled high through R220 to +5 V since the grounding by the walking bass switch is cancelled; point C11 is also taken low. This now enables the outputs from the other set of M258 pins (12, 16 and 18) to control the bass note.

Triggering for the bass envelope is developed in either of these modes from pin 12 of the M108/208 which provides an active-low pulse named TDB (trigger decay bass) every time the bass code changes. This pulse is inverted by either IC5b or IC5d, which are enabled since the selection of either walking bass 1 or 2 removes the high (+12 V) from point C10. This turns off IC7a, thus letting the input of IC6a go high and hence its output low. This low enables the NOR gates as inverters and allows them to pass trigger pulses to the bass output gating circuits. If both walking bass 1 and 2 are switched off while the rhythm is still running, the outputs from the M258 are prevented from passing through the NOR gates (IC27a-d and IC22c,d) and their outputs will be low. Point C10 going high also enables other triggering arrangements for the bass since the TDB signal will no longer be present. If either walking bass 1 or 2 is selected and the rhythm switched off then all the outputs from the M258 will be disabled (high) and therefore all the outputs from the NOR gates will be low. Pin 8 of the M108/208 is now taken high by point C16 from the rhythm on/off switch via D59.

Bass trigger changeover is made by point C17 going low (through the rhythm on/off switch) and pulling the input to inverter IC6a low via D6. Point C17 going low also causes IC2a to turn off momentarily due to the coupling by C8. This briefly removes F5 from B6, which connection normally gives the

latched output at pin 7 of the M208. This is necessary to ensure that, when the rhythm is stopped, the pedals do not continue of their own accord. This momentary disable circuitry is also used on the input side of the M108 to cancel any memorised chord if the rhythm is switched off. It is worth pointing out here that the M258 and the NOR gates supplying the bass codes run from +5 V while the M108/208 run from +12 V. This does not cause a problem since the bass code inputs of the M108/208 will accept anything from +4 V to +18 V as a high level input on these pins when running from +12 V itself.

The M258 output pin 24 is a down-beat indicator and goes low on the first count of any selected rhythm. This signal is connected to four parallel inverters from IC21 to provide current drive to the LED downbeat indicator. Output pin 8 was discussed last month with the lower manual rhythm guitar voice and is used to trigger this voice. The length of decay for the rhythm guitar is determined by the state of output pin 11: this output is one which has the steady state output programmed. If this pin is high the discharge time of C54 is long, thus giving a long chord from the guitar. If the pin is low the discharge time is shortened by putting R145 across C54 and thus giving the short guitar chord. This feature is very important in providing a good, musically interesting backing, and emulates the 'real' guitarist's performance more correctly.

Rhythm Voices

Eight different 'instruments' can be triggered by the M258 outputs. These are cymbal long, cymbal short, cymbal strike tone, handclap, tom-tom, clave, snare drum and bass drum. The bass drum, clave and tom-tom all use similar damped oscillator circuits but with different resonant frequencies. As an example of their operation, the clave voice is triggered by pin 10 of IC24. The

oscillator comprises IC25a, R182, 183, C68 and C69, the resistors and capacitors determining the frequency of oscillation. Normally the circuit does not oscillate but when a low appears on pin 10 of the M258 a pulse is generated by C67, D46 and R181 which causes the circuit to oscillate momentarily. This damped oscillation synthesizes the sound of the clave and is fed via R225 to IC12b, which is the rhythm mixer/preamp. After decoupling by C88 and the output impedance raised by the series resistance R231, the rhythm sounds pass to the rhythm volume control and then to the final mixer/preamp. Q18 is connected to the rhythm on/off switch so that with the switch-off, Q18 is turned on and shorts out any residual rhythm noise.

The cymbal voice is more complex than any other because of its importance in rhythms. It is developed by triggering a mixture of two noise sources and, optionally, a cymbal strike tone generator which also doubles as cymbal voicer. The first noise source develops white noise and comprises the reverse-biased base-emitter junction of Q19 connected to Q20, which is the amplifier. The output level of this circuit is adjusted by PR7 and is coupled through R191 and C72 to the base of Q15.

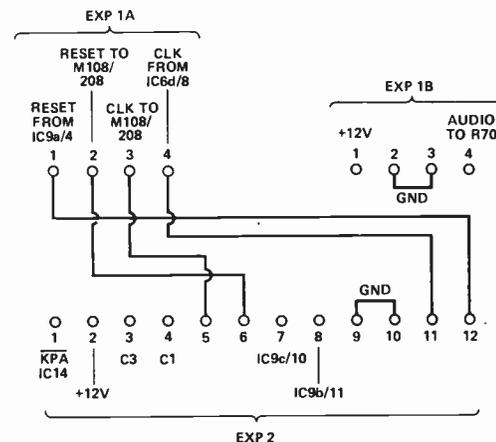


Fig. 3 The wiring of the expansion socket.

The other noise source is responsible for the metallic 'ring' content of the cymbal sound and comprises hex Schmitt inverter IC28 and quad EXOR gate IC29. IC28 is used to form six oscillators, which are EXORed in various combinations and finally mixed together and coupled via C76 and R197 to the emitter of Q15.

The cymbal trigger pulse from pin 3 of the M258 passes via C70 and causes Q15, normally biased off by R190, to conduct and output a mixture of the two noise sources to its collector, where it is filtered by IC25b. The duration of the cymbal sound is largely determined by how long C71 in the base circuit of Q15 remains discharged. If the M258 output on pin 5 is not active, ie is high, C71 will be charged fairly quickly via R185 (22k) and D48 in parallel with R190. If, however, pin 5 is low, C71 will take much longer to charge through R190 (4M7) alone. These two time constants give the long and short cymbal sounds. Output pin 5 is the other output referred to which does not always return to its high state with each clock cycle. The cymbal strike tone is derived from output pin 4 and makes use of the cymbal filter as a damped oscillator. By careful programming of the ROM, excellent hi-hat effects can be produced in conjunction with the short cymbal sound.

The snare noise trigger is from pin 22 of the M258 and is inverted by IC21f. This positive-going pulse is then coupled via C78 to the emitter follower Q16: D50, R202, C79 and R203 provide shaping for the pulse which is fed to the base of Q17. This transistor is also fed with white noise from Q19, 20 and is normally off: hence no snare noise. When the trigger pulse arrives, Q17 is switched on and amplifies the white noise, which then appears on its collector. Thus the snare drum noise is developed from a passive strike tone, resultant from the fast rise time of the trigger, together with the white noise. The drum part of the snare is produced by the tom-tom generator IC26a.

The last voice on the rhythm unit is the handclap generator, which is gradually appearing on commercial units and will become an industry standard during the year. The generator is enabled by taking pin 2 of IC30a (a NOR) low. Note that IC30 is connected to a +12 V supply, which is necessary for one of the gates to be used elsewhere on the organ. (This highlights one other useful feature of the M258 — all

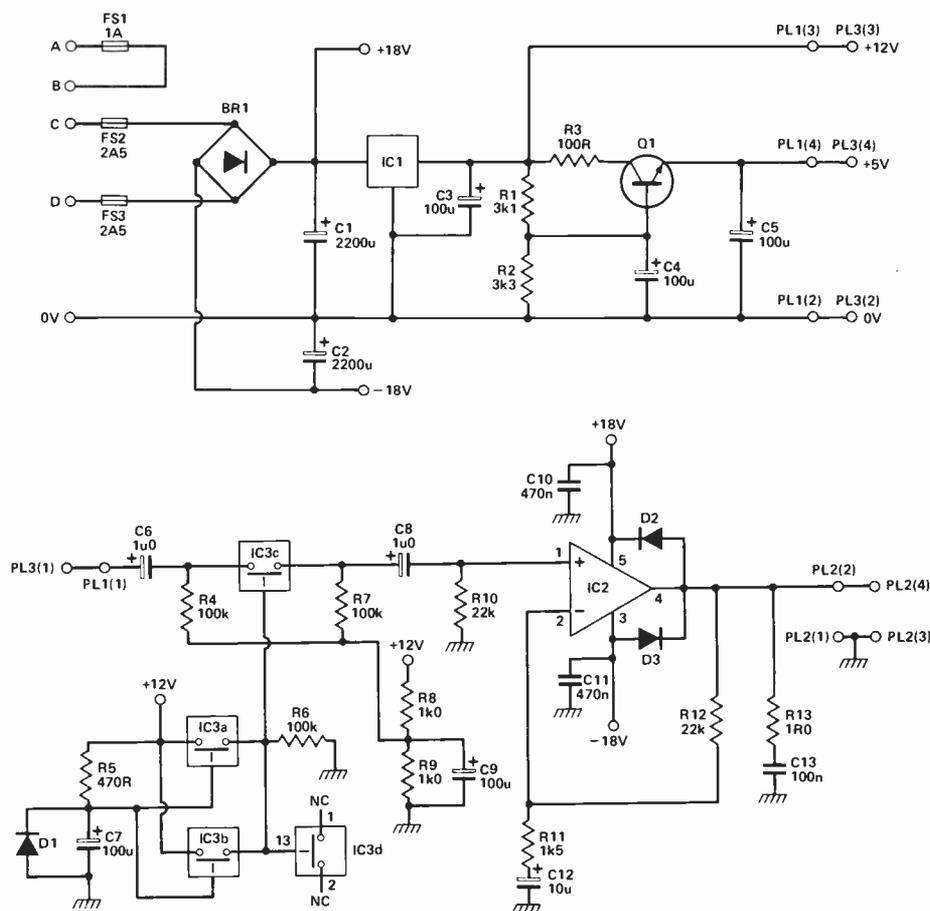


Fig. 4 Circuit diagram of the PSU and amplifier (component numbers restart from 1).

outputs are open-drain and can therefore be pulled up to whatever voltage is required. A quick look at the schematic will show this feature used to effect.) The positive-going output from IC30a pin 3 is fed to Q21, which gates white noise from Q19, 20, and also IC30b,c which are connected as a monostable. The rising and falling edges of this monostable will trigger the damped oscillator of IC31a, producing two beats of the handclap. This is overlaid with white noise from Q21 and filtered by IC31b. Both sound components are summed in the rhythm mixer IC12b.

Amplifier/Power Supply

The power supply is of a standard configuration, the ± 18 V supplies being used for the amplifier IC. The 12 V supply is obtained from a 7812 regulator IC fed from the +18 V rail and the +5 V (used only in the rhythm section) is derived from the +12 V by Q1.

The power amplifier is an integrated circuit type TDA2030L. Its output is fed to a four ohm loudspeaker via a headphone socket which breaks the connection to the speaker when

used. Signal reduction for headphone use is made by a 100R resistor attached to the headphone socket.

The input to the power amplifier is made via IC3c (part of a 4016) which is used to keep the audio line disconnected for a short period immediately after switch-on. This eliminates spurious outputs from both the generator ICs and the rhythm unit caused by switching transients. The audio line both into and out of IC3c is biased at +6 V by R4 and R7, fed from the junction of R8, 9 and C9. This is necessary since IC3 is running from a single supply.

At switch-on, IC3c is off because pin 5 is tied to ground through R6. C7 is allowed to charge through R5 until the voltage on C7 is sufficient to turn on IC3a and IC3b, which are connected in parallel. This then applies the +12 V to pin 5 of IC3c, turning it on and connecting the audio line to the power amplifier.

BUYLINES

Prices for kits of organ parts are available on application to Leighton Electronic Services, 17 Bridge Street, Leighton Buzzard, Beds LU7 7AH (tel. 0525 382504). A demo cassette is available for £1.95.

hobbyboard

mail order products for electronic projects

SPECIAL INTRODUCTORY KIT OFFERS

To enable the price conscious enthusiast to be a **PROFESSIONAL**

Hobbyboard Systems are derivatives from well proven, high quality PCB manufacturing techniques - they produce quality products for technical projects - why settle for less?

PRINTED CIRCUIT TRANSFER & ETCH (KIT HB/1)

A complete kit which includes simple Foil Pattern transfer system, rub down transfers, copper clad PCB and all processing materials and requirements including explicit instructions. (Up to 10 circuits/kit)

Normal Price £15.00

SPECIAL OFFER PRICE £12.00 INCL. VAT

PRINTED CIRCUIT PHOTO RESIST PRINT & ETCH (KIT HB/2)

A complete kit which enables you to make top quality PCB's the professional way. Includes full set of artwork aids, photo resist PCB and all process materials and requirements. (Up to 10 circuits/kit)

Normal Price £24.00

SPECIAL OFFER PRICE £16.00 INCL. VAT

DAYLIGHT PHOTOGRAPHIC SYSTEM (KIT HB/3)

Now you can make your own Photopositives and Negatives to professional standards - NO DARKROOM - complete kit with Pos. & Neg. film and all process aids.

Normal Price £19.50

SPECIAL OFFER PRICE £13.00 INCL. VAT

PHOTO LABEL & PANEL SYSTEM (KIT HB/4)

Now make professional labels & panels for your project cases - finish the job properly - complete kit includes artwork transfers and materials to print fully laminated Plastic Panels in 5 colours. (Up to 20 labels/kit)

Normal Price £22.50

SPECIAL OFFER PRICE £15.00 INCL. VAT

BUILD YOUR OWN UV UNIT (HB/UV1)

UV Lamp, Holder & Shade supplied with full assembly instructions to build a unit which will give superb results normally only obtained from very high cost systems - FAST EXPOSURE - FINE LINE REPRODUCTION

Normal Price £27.00

SPECIAL OFFER PRICE £18.00 INCL. VAT

Hobbyboard UV ARTBOX (HB/UV2)

A fully built, self-contained artwork table and UV exposure unit - TWO for the price of ONE - EXPOSURE AREA 9" x 6" - EXCELLENT VALUE

Normal Price £65.00

SPECIAL OFFER PRICE £49.00 INCL. VAT

Even greater savings if you order kits HB2, HB/3 and HB/4 with your new exposure unit.

KIT HB/5 FULL PHOTO KIT - £60.00 INCL. VAT
KIT HB/6 FULL PHOTO KIT - £90.00 INCL. VAT

ORDER FORM

(Cheques or Postal Orders only please for Special Offers.)

Please send me the following as quickly as possible

QTY	DESCRIPTION	Price Cat.	TOTAL
<input type="checkbox"/>	KIT HB/1 - PCB TRANSFER & ETCH KIT -	£12.00 -	£ :
<input type="checkbox"/>	KIT HB/2 - PCB PHOTO RESIST KIT -	£16.00 -	£ :
<input type="checkbox"/>	KIT HB/3 - DAYLIGHT PHOTOKIT -	£13.00 -	£ :
<input type="checkbox"/>	KIT HB/4 - PHOTOLABEL/PANEL KIT -	£15.00 -	£ :
<input type="checkbox"/>	KIT HB/5 - FULL UV/1 PHOTOKIT -	£60.00 -	£ :
<input type="checkbox"/>	KIT HB/6 - FULL UV/2 PHOTOKIT -	£90.00 -	£ :
<input type="checkbox"/>	HB/UV1 - DIY UV EXPOSURE UNIT -	£18.00 -	£ :
<input type="checkbox"/>	HB/UV2 - Hobbyboard UV ARTBOX -	£49.00 -	£ :
	TOTAL	£ :	£ :

Name P & P £ 0.60
Address Cheque/POE :

Please Send further details



KELAN (Hobbyboard)
North Works, Hookstone Park,
Harrogate, North Yorkshire.
☎ 0423-883672

A division of Kelan Engineering Ltd.

ET/483

CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS


ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES

ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)

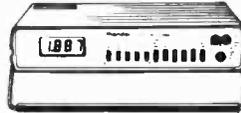

HAND HELD		
K025C* 13 range 0.2A DC 2 meg ohm	£24.95	
K030C* 26 range 1A AC/DC 20 meg ohm	£34.95	
K055C* 28 range 10A AC/DC 20 meg ohm	£39.95	
6010+ 22 range 10A AC/DC 20 meg ohm	£34.40	
7030+ As 8010 but 0.1% basic.	£41.30	
188M 16 range 10A DC. 2 meg plus Hfe tester	£39.95	
189M 30 range 10A AC/DC. 20 meg plus Hfe tester	£69.95	

HAND HELD AUTO RANGE

DM2350* 21 range 10A AC/DC 20 meg ohm (Miniature)	£49.95
HD30 16 range 0.2A AC/DC 2 meg ohm	£41.95
HD30/B As above plus cont. buzzer	£44.50
HD31 22 range 10A AC/DC 2 meg ohms plus cont. buzzer	£58.95



BENCH MODELS (3 1/2 digit unless stated)

TM353* 27 range LCD 2A AC/DC	£86.25
TM355* 29 range LCD 10A AC/DC	£86.25
TM351* 29 range LCD 10A AC/DC	£113.85
2001 28 range LCD 10A AC/DC plus 5 range Cap. Meter with case	£108.00
TM451 4 1/2 digit LCD every facility (0.02%)	£171.00
1503a 4 1/2 digit LCD every facility (0.05%)	£171.00
1503b 0.03% basic version of above	£189.00
+Optional carry case £2.95	*With free carry case
-Optional carry case £6.84	

EDUCATIONAL DISCOUNTS AVAILABLE FOR ALL STOCKS - PLEASE ENQUIRE

FREQUENCY COUNTERS



PFM200A 200 MHz hand held pocket 8 digit LED	£67.50
8110A 8 digit LED bench 2 ranges 100 MHz	£77.00
8610B 9 digit LED bench 2 ranges 800 MHz	£113.85
8000B 9 digit LED 3 ranges 1 GHz	£178.00
TF040* 8 digit LCD 40 MHz	£126.50
TF200* 8 digit LCD 200 MHz	£166.75
* Optional carry case £6.84	
Prescalers - Extended range of most counters	
TP600 600 MHz	£43.00
TP1000 1 GHz	£74.00

SIGNAL GENERATORS (220/240v AC)



FUNCTION : All sine/square/triangle/TTL, etc	
TG100 1 Hz - 100 KHz	£90.00
TG102 0.2 Hz - 2 MHz	£166.75
PULSE	
TG105 Various facilities 5 Hz - 5 MHz	£97.75
AU010 : Multiband Sine/Square	
LAG27 10 Hz to 1 MHz	£86.00
AG202A 20 Hz to 200 KHz	£78.00
RF	
SG402 100 KHz to 30 MHz	£59.95
LSG17 100 KHz to 150 MHz	£71.00

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case £83.00

MULTIMETERS (UK C/P 65p)

Y7206 20K/V	
19 range pocket meter	
SPECIAL PRICE	£7.95
C7081 50K/V 21 ranges	
Range doubler 10A DC	
SPECIAL PRICE	£15.95
ETC5000/5001 21 ranges. 50K/V. Range doubler. 10A DC.	£16.50
TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer.	£23.95
NH56R 20K/V. 22 range pocket	£10.95
EU102 14 range 2K/V pocket	£5.95
830A 26 range 30K/V. 10A AC/DC overload protection, etc.	£23.95
360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe	£36.95
AT1020 18 range 20K/V. Deluxe plus Hfe tester	£17.50
ST303TR 21 range 20K/V plus Hfe tester	£16.95

VARIABLE POWER SUPPLIES

PP241 0/12/24V. 0/1A.	£35.00
PP243 3 amp version	£59.95
(UK C/P £1.00)	

DIGITAL THERMOMETER

TH301 LCD -50°C to +750°C with thermocouple £68.43

AC CLAMP METER

ST300 0/300A: 0/600 VAC. 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

LOGIC PROBES

LP10 10 MHz £28.50
LDP076 50 MHz £56.90

OSCILLOSCOPES



Full specification on any model on request. SAE by post.

'HM' Series HAMEG; 'SC' THANDAR; 'CS' Series TRIO; '3' Series CROTECH

SINGLE TRACE	
3030 15 MHz 5mV. 95mm tube plus component tester C/P £3.00	£172.50
SC110A* Miniature 10 MHz battery portable Post free	£171.00
HM103 15 MHz 2mV. 6 x 7 display plus component tester C/P £3.00	£177.00
* Optional carry case £6.84 AC adaptor £6.69 Nicad's £12.50	
DUAL TRACE (UK C/P £4.00)	
HM203/4 Dual 20 MHz plus component tester	£276.00
CS1566A Dual 20 MHz. All facilities	£299.00
HM204 Dual 20 MHz plus component tester sweep delay.	£419.75
OPTIONAL PROBE KITS	
X1 £7.95 X10 £9.45	
X1 - X10 £10.50 X100 £16.95	

STOCKISTS FOR TRIO: HAMEG; CROTECH; SAFGAN SCOPES. MOST MODELS IN STOCK.

HIGH VOLTAGE METER

Direct reading 0/40 KV. 20K/Volt. (UK C/P 65p) £18.40

DIGITAL CAPACITANCE

0.1 pF to 2000 mfd LCD 8 ranges DM6013 £57.95 [Carry case £2.95]

TRANSISTOR TESTER

Direct reading PNP: NPN, etc. TC1 (UK C/P 65p) £21.95

AUDIO ELECTRONICS

Cubegate Limited

301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724.3564

ALSO AT HENRY'S RADII.

404/406 EDGWARE ROAD, LONDON W2


FREE CATALOGUES SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT

Order by Post with CHEQUE/ACCESS/ VISA or you can telephone your orders. All orders despatched within 5 days unless advised.

TWO NEW HANDHELD DIGITAL MULTIMETERS 200µA – 10 AMP AC-DC

28 Ranges each will full overload protection
AMAZING VALUE SPECIFICATION

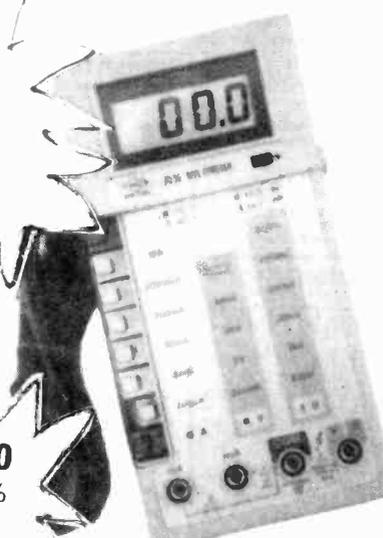

MODEL 6010
DC accuracy 0.5%
£29.95
plus VAT
= £34.44

MODEL 7030
DC accuracy 0.1%
£35.95
plus VAT
= £41.34

MODE SELECT: Push button
AC DC CURRENT: 200µA to 10A – 6 Ranges
AC VOLTAGE: 200mV to 750V – 5 ranges
DC VOLTAGE: 200mV to 1000V – 5 Ranges
RESISTANCE: 200Ω to 20MΩ – 6 Ranges
INPUT IMPEDANCE: 10MΩ
DISPLAY: 3½ Digit 13mm LCD
O/LOAD PROTECTION: All ranges
BATTERY: Single PP9 type (included)
BATTERY LIFE: 200 hours
DIMENSIONS: 170 x 89 x 38mm
WEIGHT: 400g inc battery

OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads, spare fuse and operators manual included.
Optional carrying case

Cheques/PO please to

AFDEC ELECTRONICS LTD

Kempshott Lane, Basingstoke, Hants RG22 5LT

PLEASE SUPPLY (All prices include VAT & P&P)

.....Model 6010 — £34.44
.....Model 7030 — £41.34
.....Carrying Case — £2.00
Total

PLEASE PRINT CLEARLY

NAME

ADDRESS

The portable professional



A frequency counter that fits in the palm of your hand. That's the MAX-550 from G.S.C. An accurate, easy-to-use instrument with a guaranteed measuring range from 1kHz to 550MHz, the MAX-550 measures only 2x6x1.5 inches and weighs less than half a pound. Yet its bright 6-digit LED display and its internal crystal-controlled timebase combine to give readings with an accuracy of 3 parts per million on signals down to 250mV.

Simple to operate? It has to be, with no need for switching or adjustment of polarity, slope, trigger or input level, and with built-in automatic lead-zero blanking. It runs from internal rechargeable batteries or an external d.c. supply, comes with a whole range of accessories, and costs – believe it or not – only £85 (plus V.A.T. and P.&P.)

To find out more, fill in the coupon right away.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept 9B

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Telephone: Saffron Walden (0799) 21682. Telex: 817477.

G.S.C. (UK) Limited, Dept. 9B, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

MODEL MAX-550	FREQ. COUNTER	Unit price inc. P.&P. 15% VAT £100.05	Qty Reqd

Name _____

Address _____

I enclose cheque/P.O. for £ _____

American Express card no. _____

or debit my Barclaycard/Access/

exp. date _____

FOR IMMEDIATE ACTION – The G.S.C. 24-hour, 5 day a week service

Telephone (0799) 21682 and give us your Barclaycard/Access/American Express number and your order will be in the post immediately.

For FREE catalogue tick box

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/150/250/500/1KΩ 1.5kΩ

£3.10, + 50p P&P (£3.91 inc. VAT).

50 WATT 250Ω £5.50 + 50p P&P (£6.90 inc. VAT).

100 WATT 1/5/10/25/50/100/250/300/500/1KΩ/1.5kΩ/2.5kΩ/3.5kΩ

£7.25 + 75p P&P (£8.20 inc. VAT).

Black Silver Skirted Knob calibrated in Nos. 1-9, 1 1/2 in dia. brass bush.

Ideal for above Rheostats 30p ea. + VAT.

SOLID STATE E.H.T. UNIT

Input 230V A.C. Fully isolated. Approx. 15KV. Built-in 10 sec. Timer. Easily

modified for 20 sec. 30 sec. to continuous operation. Size

155x95x50mm. Price £5 + 75p P&P. (Total inc. VAT £6.61).

240V A.C. SOLENOID VALVE

Designed for Air/Gas at 0-7. Water 0.5 psi. Inlet/outlet 3/8". Forged brass

body. Manuf. Dewra Switch Asco.

Price: £5.50 + 75p P&P (£7.10 inc. VAT). N.M.S.

METERS (New) - 90mm DIAMETER

AC Amp. Type 62T2: 0, 1A, 0-5A, 0-10A.

AC Volt: 0-150V, 0-300V.

DC Amp. Type 65C5 0-5A, 0-10A, 0-50A, 0-100A. DC Volt 30V. All types

£3.50 ea. + P&P 75p (£5.00 inc. VAT) except 0-50A DC, 0-100A DC. Price

£5.00 + 75p P&P (£6.61 inc. VAT).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £8.70 inc. VAT £10.00 (callers only).

2ft 20 watts £8.20. Post £1.25 (£9.57 inc. VAT & P).

(For use in standard bi-pin fittings).

12in 8 watt £3.00, + 45p (£3.97 inc. VAT P&P).

9in 8 watt £2.50, + 45p (£3.39 inc. VAT P&P).

6in 4 watt £2.50, + 45p (£3.39 inc. VAT P&P).

Complete ballast unit for either 6V, 9V or 12V tube 230V AC op. £5.50

Post 55p (£6.96 inc. VAT P&P). Also available for 12V DC £5.50 Post 55p

(£6.96 inc. VAT P&P).

BLACK LIGHT BULBS

Self-ballasted Mercury U.V. 175W Bulbs. Available for either B.C. or E.S.

fitting. Price incl. p&P & VAT £11.50.

400W UV LAMP AND BALLAST complete £38.00 Post £3.50 (£47.73 inc.

VAT & P). 400W UV LAMP only £14.00. Post £2.00 (£16.40 inc. VAT & P).

SOLENOIDS

230V A.C. approx 20lb pull, heavy duty £7.50 + £1.50 p&P (£10.36 inc.

VAT).

240V A.C. approx 10lb pull. £1.93 + 50p p&P (£2.79 inc. VAT)

12V D.C. approx 1 1/2lb pull. £1.85 + 40p p&P (£2.36 inc. VAT)

CONTACTOR

AMF 230V AC 2 c/o 25A. £5.50 + 75p p&P (£7.19 inc. VAT)

AEG, Arrow-Hart, etc. from stock. Phone your enquiries

Stockists for

Finnigam Hammerite paint and Waxoyl products

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-280V

2000V 1 amp inc. a.c. voltage	£15.00
0.5 KVA (2 1/2 amp MAX)	£19.00
1 KVA (5 amp MAX)	£25.00
2 KVA (10 amp MAX)	£41.00
3 KVA (15 amp MAX)	£49.00
5 KVA (25 amp MAX)	£79.00
10 KVA (50 amp MAX)	£174.00
15 KVA (75 amp MAX)	£270.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual input 200-240V or 380-415V. Star connected	£113.40
3 KVA 5 amp per phase max	£170.10
6 KVA 10 amp per phase max	£345.45
10 KVA 16 amp per phase max	£345.45

All plus
carriage
and VAT

Comprehensive range of L.T., AUTO (110-240V),
ISOLATION TRANSFORMERS available for im-
mediate delivery. Leaflet on request.

EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case, to include 12" 8 watt 2537 Angat Tube. Ballast unit, pair of bi-pin leads. Neon indicator, safety microswitch, on/off switch and circuit. LESS CASE. Price: £13.60 + 75p P&P. (Total incl. VAT £16.50). Warning: Tube used in this circuit is highly dangerous to the eyes. Unit MUST be fitted in suitable case.

FROM STOCK AT PRICES THAT DEFY COMPETITION!

AC GEARED MOTORS
DC MOTORS
MICROSWITCHES
RELAYS
REED SWITCHES
SOLENOIDS
PROGRAMME TIMERS

C.F. BLOWERS
AC CAPACITORS
STROBE KITS
FLASHTUBES
CONTACTORS
SYNCHRONOUS
MOTORS

Phone in your enquiries

GEARED MOTORS

5rpm 240V A.C. Mf. by Carter. £6.06 £1 p&P (£8.11 inc. VAT)

7 1/2rpm Motor approx 30lb in. 110V A.C. complete with Transformer for 240V A.C. £10.20 + £1.50 p&P (total inc. VAT £13.45)

71rpm WYNSCALE motor approx. 10lb in.

A.C. supplied with auto transformer 240V.

A.C. operation. £9.75 p&P £1.50 (£12.94 inc. VAT).

N.M.S.

42 rpm. 110 A.C. 50Hz. 100lb in. reversible, will operate on 230 A.C. Speed remains at 42 rpm but torque reduces by 50%. Price £18.15 p&P

£2.50 (£23.75 inc. VAT). N.M.S.

TRANSFORMER 240V A.C. operations £15.07

38.3 rpm GEARED MOTOR. Torque 35lb.in. reversible 115V AC inc. start

capacitor. Price: £11.55 + £2 P&P (total incl. VAT £15.38).

Suitable Transformer 230V A.C. operation. Price: £7.15 + 50p P&P (total

incl. VAT £8.60).

N.E.C. GEARED MOTOR. 152 rpm. 200lb.in. 230V A.C. 50Hz. Ratio 9.2 to 1. Non reverse. Incl. capacitors. Fraction of maker's price. £41.25 + Carr + VAT. N.M.S.

INDUSTRIAL STROBE KIT

Ideal for Industrial and Educational purposes. Produces high intensity flash variable from approx. 1 to 70 f.p.s. Price less case: £27 + £2 P&P (total incl. VAT £33.36). Suitable Case and Reflector £12.50 + £2 P&P (total incl. VAT £16.68).

HY-LYGT Mk V Designed for Disco, Theatrical uses, etc.

Approx. 4 joules. Adjustable speed. Price £27 + £2 P&P. (Total inc. VAT

£33.36). Case and reflector price £12.50 + £2 P&P. (total incl. VAT

£16.68). Foolsap SAE for further details including Super Hy-Lyght.

COMPRESSOR

Thomas single diaphragm. Max. 20 psi. 1 1/4" cfm., approx. 110V A.C.

£16 + £2 P&P (total incl. VAT £20.70). OR, to include Transformer for

230/240V A.C. £26.45 incl. VAT.

BLOWER/VACUUM PUMP

3 phase A.C. motor 220/250V or 380/440V. 1,425 rpm, 1/8 h.p. cont. Direct

coupled to William Allday Alcosa carbon vane blower/vacuum pump.

0.9 cfm 8hg. £22 + £4 P&P (total incl. VAT £29.90).

INSULATION TESTERS NEW

500 VOLTS 500 megohms £49.00 P&P £2.00

(£58.65 inc. VAT & P) 1000 VOLTS 1000Ω £55.00

P&P £2.00 (£66.55 inc. VAT & P). SAE for leaflet

SANGAMO WESTON TIME SWITCH

Type S251 200/250 AC 2 on/2 off every 24 hours. 20 amps contacts

with override switch. Diameter 4" x 3". price £9.50 P&P £1.00

(£12.00 inc. VAT & P). Also available with solar dia. R&T.

Also available Sangamo Weston 60 amp and AEG 80 amp. Phone

for details.

Type S288 1 on, or 1 timed c/o every 24 hours, day omitting device.

Price £11 + £1 P&P. (£13.80 incl. VAT). N.M.S.

Type S388. As above, plus 36 hours spring reserve. Less perspex

cover. Price: £13 + £1 P&P (£16.10 incl. VAT). N.M.S.

N.M.S. - New Manufacturers' Surplus.
R&T - Reconditioned and Tested.

SERVICE TRADING CO

Ample parking space
Showroom open
Monday-Friday



57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB, 01-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only. Open Saturdays
9 Little Newport Street
London WC2H 7JJ
Tel: 01-437 0576

THANDAR PORTABLE TEST BENCH

A wide range of high performance instruments, at prices that are hard to beat, puts professional test capability on your bench.

COUNTERS - TF200 10Hz to 200MHz; TF040 10Hz to 40MHz; PFM200A 20Hz to 200MHz (hand-held model); TP600 prescales to 600MHz; TP1000 Prescales to 1GHz.

MULTIMETERS - TM351 0.1% 3 1/2 digit LCD; TM353 0.25% 3 1/2 digit LCD; TM355 0.25% 3 1/2 digit LED; TM354 0.75% 3 1/2 digit LCD (hand-held model); TM451 0.03% 4 1/2 digit with autoranging and sample hold.

OSCILLOSCOPE - SC110A 10MHz, 10mV sensitivity, 40mm CRT with 6mm graticule divisions.

THERMOMETERS - TH301 - 50°C to +750°C, 1° resolution; TH302 - 40°C to +1100°C and -40°F to +2000°F, 0.1° and 1° resolution. Both accept any type K thermocouple.

GENERATORS - TG100 1Hz to 100kHz Function, Sine, Square, Triangle Wave; TG102 0.2Hz to 2MHz Function, Sine, Square, Triangle Wave; TG105 5Hz to 5MHz Pulse, Free Run, Gated or Triggered Modes.

LOGIC ANALYSERS - TA2080 8 channel 20MHz; TA2160 16 channel 20MHz.

ACCESSORIES - Bench rack, test leads, carrying cases, mains adaptors, probes, thermocouples etc.

Send for our latest catalogue and price list.
Thandar Electronics Ltd,
London Road, St. Ives,
Huntingdon, Cambridgeshire PE17 4HJ.
Telephone (0480) 64646. Telex 32250.



TH12



thandar
ELECTRONICS LIMITED

PUTTING THE BEST WITHIN YOUR GRASP

DESIGNER'S NOTEBOOK 2

Our second Notebook topic is that much-misunderstood beast, the switched mode power supply. P.S. Wilson of International Rectifier gives a step-by-step explanation of the various types and design examples.

The term 'switching mode power supply' is used to describe DC-to-DC converters and AC-to-DC converters which operate on a switching principle. Using switching techniques, voltage step-up and voltage inversion can be achieved, as well as the more common voltage step-down function. The advantages of using switching techniques over a linear solution are the reduction in the size of components (such as power transformers and output filter capacitors) by operating at high frequency, and dramatic improvements in efficiency, since the power elements are either fully turned 'on' or 'off' and do not operate in the linear mode. The disadvantages of switching mode solutions are increased noise and radio frequency interference (RFI) which is generated during the switching transitions. Circuit complexity is increased, as in addition to the control circuit, a power switch, rectifier, high frequency transformer or inductor and drive circuitry is required.

Switching mode solutions are, however, cost-competitive with linear power supplies in off-line applications at and above the 100 W level. Switch mode power supplies are also used at lower power levels in DC-to-DC converters where there is a special requirement such as high efficiency, for example in solar energy conversion, or small size for mobile communications equipment.

Basic Principles

The circuit and waveforms in Fig. 1 illustrate the basic principle of the switching mode supply by comparison with a linear regulator. The circuit configuration shown is for a voltage step-down conversion. When switch SW1 is closed the input supply voltage is applied to the inductor L1, and current flow in the inductor will rise with a ramp waveform, charging capacitor C1 and also supplying the load connected at the output of the supply. When SW1 is opened (equivalent to turning off a semiconductor device) the inductor current diverts into the rectifier, D1. The voltage at circuit node 'P' falls instantaneously to a rectifier forward voltage drop below the 0 V line, and the current flow in the inductor follows a negative ramp waveform. The power supply load is now supplied both from the inductor and from the output capacitor, C1. When SW1 again closes, D1 becomes reverse biased and the inductor is again connected to the input supply. In the steady state condition, the positive volt-second product applied to the inductor must balance the negative volt-second product applied when the rectifier conducts. The voltage at the output of the supply is regulated by controlling the 'on'/'off' ratio, or duty cycle of the switch SW1. Because the switching element is either 'on' or 'off' the power loss is small and the efficiency of the supply approaches 100%.

Comparison with the linear regulator (Fig. 1b) shows an efficiency of approximately V_o/V_{in} .

Figure 2 illustrates how, by rearranging the circuit elements SW1, L1 and D1, voltage step-up and voltage inversion can be achieved. Provided that the current flowing in L1 does not fall to zero between the conduction phases of SW1, the circuit configuration in Fig. 2a can be said to provide a 'non-pulsating' output current. This feature allows low output ripple voltage to be achieved. The configuration shown in Fig. 2b, however, will exhibit a 'pulsating' output current as the inductor current is diverted from the output when SW1 closes. The input current flow, however, can be arranged to be non-pulsating, so reducing the ripple voltage on the input supply. The voltage inverting circuit, Fig. 2c has pulsating current waveforms at both input and output terminals.

To overcome this apparent restriction on operating mode, transformer-coupled circuits can be used. The voltage conversion achieved is then defined by the transformer turns ratio and the polarity of the output rectifiers. Figure 3 illustrates the most common circuit configurations in use today. In addition to increasing flexibility, the transformer-coupled solution offers the option of an isolated output supply.

Figure 3a shows a transformer-coupled circuit configuration analogous to the voltage step-up circuit in Fig. 2b. The dots against the transformer windings indicate

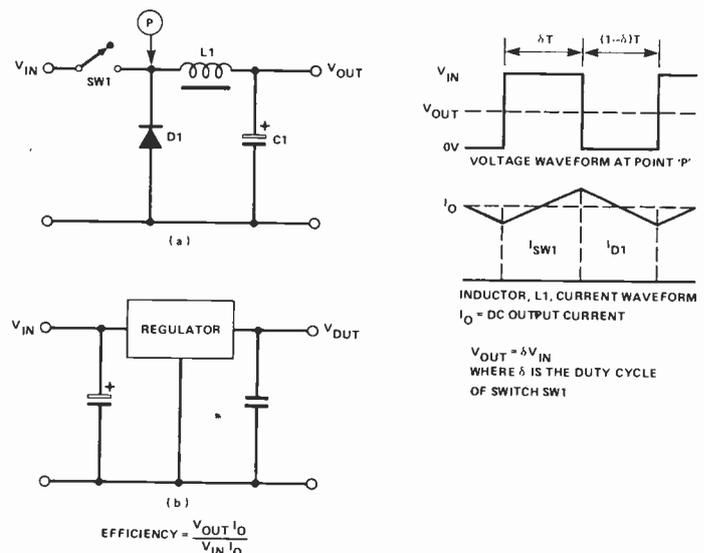


Fig. 1 Basic principles. (a) The forward converter (buck converter). (b) The basic linear regulator.

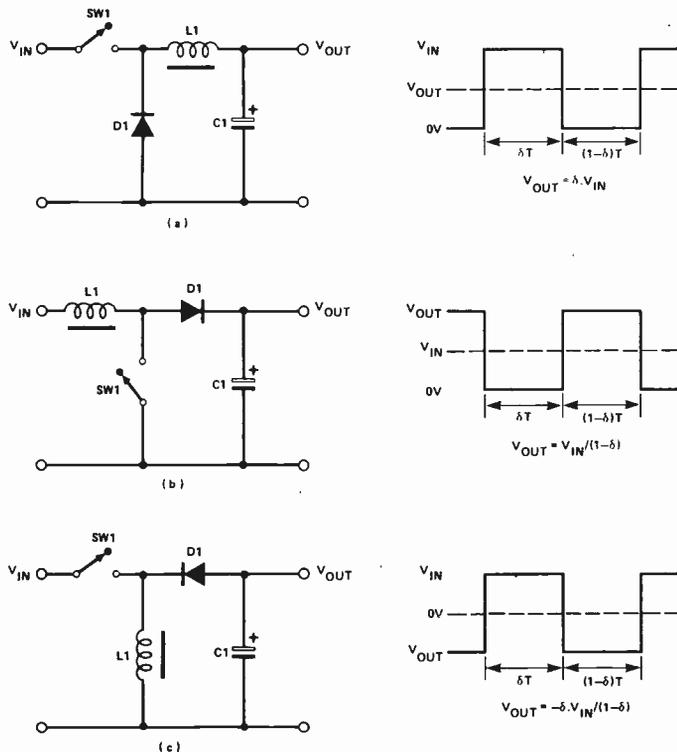


Fig. 2 Circuit configurations to achieve different V_{IN}/V_{OUT} . (a) Voltage step-down. (b) Voltage step-up. (c) Voltage inversion.

their polarity. SW1 and D1 conduct during opposite phases of the drive signal, that is, they conduct non-simultaneously.

Figure 3b is analogous to the voltage step-down circuit in Fig. 2a. SW1 and D1 conduct simultaneously. During the switch 'off' time, current flow in L1 is diverted through a second rectifier, D2. The purpose of the third winding on the transformer is to reset the magnetic core of the transformer during the switch 'off' time. If this was not done, the magnetic core would become DC-biased and may saturate, resulting in poor performance (low efficiency and high pulse currents in the primary winding and SW1).

Figure 3c, the push-pull converter, is again analogous to the circuit in Fig. 2a. The difference between this circuit configuration and the forward converter shown in Fig. 3b is that the transformer is biased bidirectionally by switches SW1 and SW2 which conduct alternately. Consequently the 'reset' winding shown in Fig. 3b is not required. The output filter components L1, C1 operate at twice the switching frequency, allowing some size reduction. Each switching device (SW1, SW2) passes only one half of the output current divided by the transformer turns ratio, n . Consequently this solution may be preferred to the solution shown in Fig. 3b at higher power levels (greater than 100 W).

Figure 3d illustrates a type of push-pull converter commonly used in off-line applications. Its main advantage, apart from the automatic resetting of the transformer core, is that the maximum voltage seen by either switch does not substantially exceed the input supply line voltage. Consequently, 400 V switches can be used when working directly from the rectified 240 V mains supply. Capacitor C2 prevents DC biasing of the transformer core which may otherwise arise through asymmetry in the switching waveforms of SW1 and SW2. Capacitors C3, C4 effectively divide the supply to the transformer by two.

Finally, Fig. 3e represents a further modification to the

basic forward converter in Fig. 2a. The capacitors C3, C4 in the previous figure are replaced by two more switches; SW3, SW4. DC magnetisation of the transformer core is prevented by capacitor C2. The full supply voltage is now applied across the transformer primary as switches SW1 and SW4 and then SW2 and SW3 close simultaneously. The maximum voltage applied to any of the switches will not exceed the supply voltage significantly. This 'full bridge' configuration is used in high power switching power supplies where the size and cost of capacitors C3, C4 to replace the switches would be prohibitive. The same circuit configuration is used to drive reversible DC motors.

Switching power supplies can use capacitive elements as the energy transfer medium, rather than magnetic components which have been considered so far. Generally, capacitive circuits are limited to use at high frequency (greater than 10 kHz) and relatively low power levels. Figure 4 shows a capacitive voltage multiplier and a voltage inverting circuit. An example of such a circuit, which is available in integrated form, is the ICL7660 from Intersil Inc.

Operation of the circuit in Fig. 4a is as follows. Initially, SW2 is closed and SW1 'off'. Capacitor C1 is charged to V_{IN} through rectifier D2 and SW2. SW2 then opens and SW1 is closed. This causes the voltage seen at the anode of rectifier D1 to rise from V_{IN} to a value determined by the relative sizes of capacitors C1, C2. When $C1 = C2$, the voltage at the output of the supply will rise toward $2V_{IN}$. SW1 is then opened and SW2 closed to repeat the cycle.

The circuit in Fig. 4b operates on the same principle. SW1 charges capacitor C1 to V_{IN} . SW2 is then closed, taking the cathode of rectifier D1 negative to a value determined by C1, C2. Capacitor C1 is then recharged through SW1 and D2.

What Semiconductor?

As is inferred by the name 'switching mode' the semiconductor devices required for this application are primarily switching devices. The requirements for the switches are:

- Low conduction losses.
 - Fast switching times.
 - Voltage rating to match the circuit configuration and input supply voltage.
 - Ability to withstand an overload.
 - Good safe operating area (SOA) when used in an inductive load switching circuit.
- These requirements can be met, largely, by a wide variety of bipolar transistors, thyristors and SCRs. More recently, power MOSFETS have been introduced with voltage and current ratings suitable for use in switching power supplies (current ratings to 40 A and voltage ratings to 500 V). These devices offer substantial advantages over bipolar transistors in the following areas:
- Low gate drive power — simplifying the driver stage.
 - Fast switching times which are largely temperature insensitive — allowing operation at frequencies greater than 50 kHz.
 - Good overload capability — the device is not limited by gain or second breakdown. Power dissipation is the limiting factor.
 - The positive temperature coefficient of 'on' resistance assists current sharing when devices are parallel-connected to achieve higher current ratings.
- Rectifiers for switching power supplies have similar requirements to the switching devices. The type of rectifier used is governed by the circuit application as indicated in Table 1.

Monolithic switching regulator circuits of limited output power capability are available (Fairchild uA78S40,

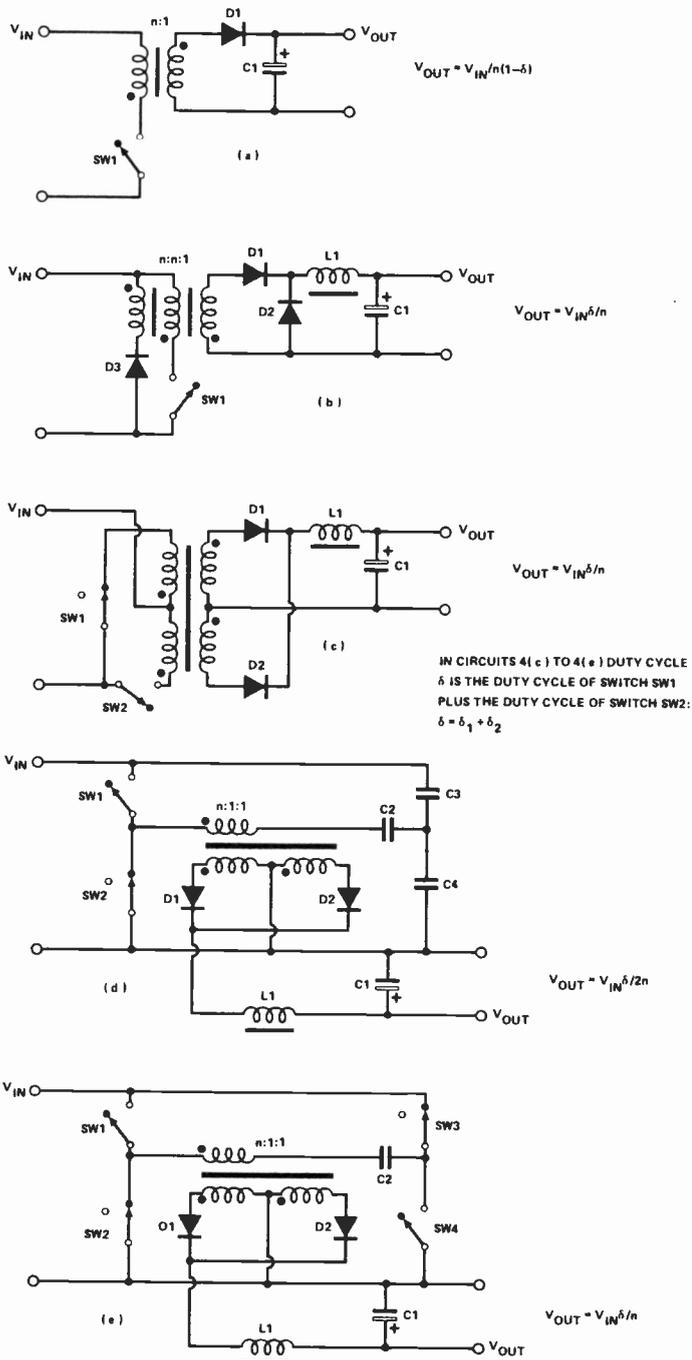


Fig. 3 Transformer-coupled switching mode circuits. (a) Flyback converter. (b) Single-ended forward converter. (c) Push-pull converter. (d) Half bridge circuit. (e) Full bridge circuit.

Texas TL497A), and the trend toward integrated power functions can be expected to accelerate. There are a number of integrated control circuits for switching mode power supplies available, allowing the control circuit board complexity to be reduced. The functions available in these circuits include: an oscillator, a voltage reference, a regulator, a current limit function and a driver stage. Some of the more common devices are: Philips TDA1060 which is pin-for-pin compatible with the Signetics NE5560, the Silicon General SG3524 which is multi-sourced, the Texas Instruments TL494 which is also available from Motorola, Fairchild and Fujitsu (as MB3759) and the Motorola MC3420.

TABLE 1

Application	Rectifier type
High Frequency Switching	Schottky Epitaxial Fast recovery, diffused
High Current, Low Voltage Switching	Schottky Epitaxial Germanium
High Voltage Switching	Silicon diffused Rectifier stack

Magnetic Component Design

Magnetic components are used in the majority of switching mode power supplies. It is, generally, only at low power and high frequency that capacitive circuits can be used. Magnetic components are used not only as high frequency transformers and DC inductors, but also as drive transformers, providing isolation between the control circuit and the power switching elements, and as current sensing elements.

Some of the criteria for the selection of a magnetic component as a high frequency transformer core are:

- Operating frequency range.
 - Maximum magnetic flux density.
 - Loss coefficient at the operating frequency.
 - Available winding area.
 - Primary to secondary coupling factor, and isolation.
- Ferrite cores in a variety of shapes and materials are available. Metal powder cores, laminated and tape wound cores are also available for specialist applications.

Transformer Design

As an example, consider the design of a switching mode transformer to operate at 50 kHz in a half bridge circuit (refer to Fig. 3d). The input voltage is 310 V + 5%, - 10% and the output required is 5 V at 40 A.

Step 1. Select a core material suitable for operation at 50 kHz and a core size commensurate with the power loading. Example: Mullard FX3740 core, A16 material; Philips EC52/24/14 core, 3C8 material.

Step 2. Calculate the number of primary turns required to avoid saturation of the transformer core under worst case loading. Check that the worst case core losses do not cause excessive core operating temperature. Check that the winding area is adequate. Check that the magnetising current is less than 10% of the load current for efficient

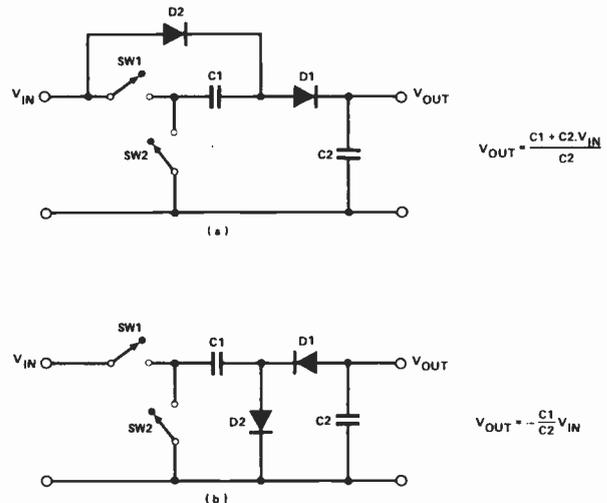


Fig. 4 Capacitive converter circuits. (a) Capacitive voltage multiplier. (b) Capacitive voltage inverter.

operation. Example: Worst case loading will occur with maximum input supply voltage and maximum duty cycle for the switches.

$$V_{IN\max} \frac{\delta \max}{f_o} = \widehat{B} \cdot Ae \cdot n$$

where $V_{IN\max}$ is the maximum voltage applied to the transformer = $\frac{310 + 5\% V}{2}$

f_o is the operating frequency = 50 kHz

\widehat{B} is the peak working flux density of the core, at elevated temperature = 200 mT

Ae is the magnetic cross sectional area of the core = 180 mm²

n is the minimum required number of turns

Hence $n_{min} = 40.7$ turns

Working at a peak flux of 200 mT, at 50 kHz, core losses are approximately 1W8. This corresponds to a rise in core temperature above ambient of approximately 20°C. Assuming a conversion efficiency of 70%, the input power requirement is 286 W. The lowest input voltage, applied across the transformer primary is $(310 - 10\%)/2 V = 139 V$. This gives a primary winding current, assuming 0.9 duty cycle, of approximately 2A3.

Assuming a current density in the transformer winding of 4 A/mm², the cross-sectional area of wire used for the primary winding should be 0.57 mm², corresponding to a wire of diameter 0.85 mm. Assuming a packing factor of two (because a circular cross-section conductor is used) the winding area consumed by the primary winding will be $2n \times 0.57 \text{ mm}^2 = 46.7 \text{ mm}^2$. The available winding area on the core, after making an allowance for isolation is 304 mm². The primary winding will take only 1/6 of the available area.

The magnetising inductance of the winding is determined by:

$$L_m = \frac{\mu_o \mu_a n^2 Ae}{l_e}$$

where L_m is the magnetising inductance in Henries

μ_o is the permeability of free space = $4 \times 10^{-7} \text{ H/m}$

μ_a is the amplitude permeability of the core = 10^3

l_e is the magnetic path length in the core = 105 mm

$$L_m = 3.62 \text{ mH}$$

The peak magnetising current is given by the equation:

$$\frac{V_{in\min}}{2} = \frac{2 \cdot L_m \cdot I_m \cdot f_o}{\delta \max}$$

$$\text{So } I_m = \frac{V_{in\min} \cdot \delta \max}{4 \cdot L_m \cdot f_o} = 86 \text{ mA}$$

The peak magnetising current represents 4% of the load current, which is acceptable.

Step 3. Establish the transformer turns ratio. Example: The voltage required at the secondary winding of the transformer is a function of the power supply output voltage (5 V), the duty cycle of the switches SW1, SW2, and the voltage dropped across the rectifiers and resistance of the output inductor L1. Disregarding the circuit losses initially, the transformer output voltage can be found by balancing the volt-second products for the output inductor in the minimum input supply condition, when the duty cycle is 0.9.

$$(V_x - V_o) = (V_o + V_f) (1 - \delta)$$

where V_x is the transformer output voltage.

V_o is the supply output voltage = 5 V

δ is the duty cycle = 0.9

V_f is the rectifier forward drop = 1 V

$$V_x = 5V7$$

To this figure must be added the circuit losses, $V_f + I_o \cdot R_L$,

where I_o is the rated output current, and R_L is the series resistance of L1 and the circuit wiring.

A minimum output voltage of 7 V can be used. The minimum input voltage is 139 V, so the transformer turns ratio is 20:1. Assuming a primary winding of 40 turns (marginally below the minimum, resulting in a slightly higher peak flux density, \widehat{B} , which can be tolerated in this example), each secondary winding comprises two turns.

Step 4. Transformer winding design. The correct design of the transformer windings will result in a reproducible and efficient transformer design. The conductor size and placement can have a significant effect on winding losses in a high frequency design. Example: The primary winding consists of 40 turns of 0.85 mm diameter wire, which can be wound in two layers each comprising 20 turns. The available winding breadth on the transformer core is approximately 20 mm after an allowance of 4 mm at either end for isolation. The secondary consists of two windings, each of two turns. The conductor for these windings is in strip form, being 8 mm in width and 0.625 mm thick. The windings are wound side by side on the former. Electrostatic screens and isolation are wound between primary and secondary windings. Worst case windings losses arise at maximum loading. Primary winding loss is 3W4 maximum, and the secondary winding loss 1W25 watts maximum. When added to the transformer core losses of 1W8 the worst case transformer loss is 6W45 at a core temperature of 100°C. The transformer is capable of operating in ambient temperatures up to 35°C without additional heatsinking. (Core data and ratings are drawn from the manufacturers' literature).

Inductor Design

The operating conditions of the magnetic core in the inductor are significantly different from those of the switching mode transformer. The core must withstand a DC magnetising field, without saturation. For this reason, an air gap is commonly introduced into a magnetic circuit. This can be either in the form of a single gap introduced, say, in the centre pole of an 'E' core, or can be a distributed gap throughout the core material. The distributed gap solution presents a lower radiated magnetic field. When a gapped core is used, the magnetic flux is sorted mainly in the gap. There are small flux excursions as the load current ramps up and down. As an example, consider the design of an output filter inductor to be used with the 50 kHz transformer previously designed. The operating frequency will be 100 kHz. The maximum output current is 40 A and the minimum output current for continuous current flow in the inductor is 4 A.

Step 1. Calculate inductance value required, and the energy storage capability required. Example: The minimum voltage applied to the inductor by the transformer secondary winding is 5V7 with a 0.9 duty cycle. The current in the inductor can be allowed to rise by 8 A maximum during this time if the current flow is to remain continuous when the output loading is minimum, ie 4 A.

$$(V_{in\min} - V_o) = L \min \cdot \frac{I_L \cdot f_o}{\delta \max}$$

where $V_{in\min}$ is the voltage applied to the inductor = 5V7

V_o is the output supply voltage = 5V

$L \min$ is the minimum inductance value

I_L is the peak to peak inductor current = 8 A

f_o is the operating frequency = 100 kHz

$\delta \max$ is the switch duty cycle = 0.9

$$L \min = 1.6 \text{ microhenries}$$

The energy storage capability is $L \cdot I_m^2$ where I_m is the peak current flowing in the inductor = 44 A, so $L \cdot I_m^2 = 3.1 \text{ mJ}$.

FEATURE: Designer's Notebook

Step 2. Select a suitable inductor core and determine the air gap required (if it is not a distributed gap material). The majority of magnetic core manufacturers provide selection charts/guides for this purpose. Example: Philips core EC35/17/10 with a 0.9 mm air gap will meet the energy storage requirement (equivalent to the Mullard FX3720).

Step 3. Calculate the number of turns required and determine the inductor losses. The core data gives an effective permeability or an A_L value (inductance per turn of the coil) for gapped cores, which enables the number of turns to be calculated and rounded up to the nearest half turn. The inductor losses are primarily in the winding and these can be determined using a similar method to that used to calculate the transformer winding losses. Example: For the Philips EC35/17/10 core with a minimum air gap of 0.9 mm, 4 turns are required to give an inductance of 1.6 microhenries. The winding losses can be written as $I_{eff}^2 \cdot F_R \cdot R_{DC}$ where I_{eff} is the RMS current flowing in the inductor winding F_R is a resistance multiplier to account for high frequency operation R_{DC} is the DC resistance of the winding.

The high frequency impedance of the winding is a minimum for a conductor of thickness 0.57 mm. Making the winding with copper strip of thickness 0.5 mm and width 20 mm gives a 100°C AC winding resistance of 0.58 mR. The winding loss is 0W93, resulting in an inductor temperature rise above ambient of 18°C when fully loaded.

Drive Transformer Design

Various approaches to the design can be made, though the choice is frequently restricted by the operating conditions and the drive requirements of the semiconductor switch. Thyristors and power MOSFETS can be driven by pulse transformers. The length of the trigger pulse and the circuit impedance are designed to comprehend the drive requirements of the worst case drive. Bipolar transistors require a continuous base current supply which often results in a larger transformer core being needed. The need for a wide variation in switch duty cycle often results in the drive supplied to the switching device being compromised: the forward base current supplied during long duty-cycle operation may be the bare minimum to maintain the transistor in saturation. At short duty-cycles the base current supplied can be far in excess of the device requirements, compromising its switching performance. This effect is less severe when power MOSFETS are used as the switches, since they do not exhibit storage time effects.

As an example, consider the design of drive transformers for power MOSFETS when used as the switches in the 50 kHz switching mode power supply. A single transformer with two primary and two isolated secondary windings could be used. A disadvantage of this approach, however, is the absence of negative gate bias to turn off the MOSFETs at any duty cycle other than the maximum of 0.5, which would give poor noise immunity in normal operation. Instead, separate transformers are used and the magnetising energy stored in the transformer core during the conduction phase is used to assist turn-off. The transformer design is similar to that required for a single-ended forward converter, Fig. 3b.

Step 1. Select a suitable magnetic material and core size. Example: The operating frequency is 50 kHz and the average current flow in the windings will be low. A core material with a high permeability is desirable to maintain a low level of magnetising current. Winding area is a significant factor in determining the core size and will depend on the isolation voltage rating desired. For this application consider the Philips core P1418 in 3B7 material, with an A_L

value of 2,200 nH/1000 turns and a total winding area of 9.4 mm².

Step 2. Calculate the number of turns required for the primary winding and the magnetising inductance and current. Example: To avoid core saturation when operating at maximum duty cycle, with a supply voltage of 15 V, the minimum number of turns required in the primary winding is given by:

$$V_{in} \cdot \delta \max^c = \widehat{B} \cdot A_e \cdot n_{min} \cdot f_o$$

where V_{IN} is the supply voltage = 15 V
 $\delta \max$ is the maximum duty cycle = 0.45
 f_o is the operating frequency = 50 kHz
 \widehat{B} is the peak magnetic flux density in the core = 180 mT
 A_e is the magnetic cross sectional area of the core = 25.1 mm²
 n_{min} is the minimum number of primary turns
Hence $n_{min} = 30$ turns
The magnetising inductance, with n , the number of turns equal to n_{min} is given by:

$$n_{min} = 10^3 \sqrt{\frac{L_M}{A_L}}$$

where:

L_M is the magnetising inductance in millihenries
 A_L is the inductance factor in nanohenries/1000 turns = 2,200

Hence $L_M = 2.0$ mH

The magnetising current at maximum duty cycle is

$$I_M = \frac{V_{IN} \cdot \delta \max}{L_M \cdot f_o} = 67.5 \text{ mA}$$

Step 3. Check that the winding area on the ferrite core is adequate. Example: To calculate the winding area required for the primary winding, we must first estimate the average current flow. The current required to drive the power MOSFET IRF720, which would be used in this application, at 50 kHz, is low compared to the magnetising current (1.7 mA averaged over a switching cycle). So, the average magnetising current level can be assumed. A suitable wire gauge is 0.1 mm diameter. Because of handling difficulties, a 0.2 mm wire may be preferred. The winding area consumed is approximately 20% of the total winding area of the transformer. Assuming that the drive transformer has a 1:1 turns ratio, giving a ± 15 V gate drive to the power MOSFET, the winding area is adequate, after an allowance for isolation spacing has been made.

Step 4. Calculate the minimum permitted drive pulse for safe turn-off. Example: Because this design relies on the transformer magnetising energy to switch off the power MOSFET, a minimum drive pulse must be defined where by the magnetising energy equals the worst case turn-off energy for the MOSFET. Turn-off energy requirements for the MOSFET = $Q_G \cdot \Delta V$ where Q_G is the maximum gate charge figure.

ΔV is the gate voltage swing = 30 V
Magnetising energy in the transformer = $(V_{IN} \cdot t_{on \min})^2 / L_M$

where $t_{on \min}$ is the duration of the minimum drive pulse. Equating these figures, assuming $Q_G = 17$ nC for the IRF720 device, gives a minimum drive pulse of $t_{on \min} = 2.15$ microseconds, which represents a minimum duty cycle, at 50 kHz, of 0.22.

In the June ETI we will be publishing a switching mode power supply similar to the half bridge design used for the examples here: the project will look more closely at the functions of the actual controller IC.

ETI

TOROIDALS



The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within **7 DAYS** together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
30 VA 70 x 30mm 0.45Kg Regulation 18%	1x010	6+6	2.50	£5.12 +p/d £1.04 +VAT £0.92 TOTAL £7.08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2x010	6+6	4.16	£5.70 +p/d £1.30 +VAT £1.05 TOTAL £8.05
	2x011	9+9	2.77	
	2x012	12+12	2.08	
	2x013	15+15	1.66	
	2x015	22+22	1.13	
	2x016	25+25	1.00	
80 VA 90 x 30mm 1 Kg Regulation 12%	3x010	6+6	6.54	£6.08 +p/d £1.67 +VAT £1.16 TOTAL £8.91
	3x011	9+9	4.44	
	3x012	12+12	3.33	
	3x013	15+15	2.66	
	3x014	18+18	2.22	
	3x015	22+22	1.81	
120 VA 90 x 40mm 1.2 Kg Regulation 11%	4x010	6+6	10.90	£6.90 +p/d £1.97 +VAT £1.79 TOTAL £9.86
	4x011	9+9	6.86	
	4x012	12+12	5.00	
	4x013	15+15	4.00	
	4x014	18+18	3.33	
	4x015	22+22	2.72	
160 VA 110 x 40mm 1.8 Kg Regulation 8%	5x011	9+9	8.89	£7.91 +p/d £2.67 +VAT £1.44 TOTAL £11.02
	5x012	12+12	6.66	
	5x013	15+15	5.33	
	5x014	18+18	4.44	
	5x015	22+22	3.63	
	5x016	25+25	3.20	

- ★ 234 TYPES TO CHOOSE FROM!
- ★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
- ★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6x012	12+12	9.38	£9.20 +p/d £2.00 +VAT £1.64 TOTAL £12.88
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7x013	15+15	10.00	£10.17 +p/d £2.00 +VAT £1.83 TOTAL £14.00
	7x014	18+18	8.33	
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
500 VA 140 x 60mm 4 Kg Regulation 4%	8x016	25+25	10.00	£13.53 +p/d £2.35 +VAT £2.38 TOTAL £18.26
	8x017	30+30	8.33	
	8x018	35+35	7.14	
	8x026	40+40	6.25	
	8x025	45+45	5.55	
	8x033	50+50	5.00	
625 VA 140 x 75mm 5 Kg Regulation 4%	9x017	30+30	10.41	£16.13 +p/d £2.70 +VAT £2.47 TOTAL £21.47
	9x018	35+35	8.92	
	9x026	40+40	7.81	
	9x025	45+45	6.94	
	9x042	55+55	5.68	
	9x028	110	5.68	

IMPORTANT: Regulation - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain full load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

- For 110V primary insert "0" in place of "X" in type number.
- For 220V primary (Europe) insert "1" in place of "X" in type number.
- For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalve, Maplin and Technomagic.

Please send _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd, Freepost 4 Graham Bell House, Roper Close,
Canterbury CT2 7EP, Kent, England.
Telephone Sales (0227) 54778; Technical (0227) 64723; Telex 965780.



NEW! T.V. SOUND TUNER

BUILT AND TESTED

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction.



£22.95 + £2.00 p&p.
This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 1/4" x 8 3/4" x 3 3/4". E.T.I. kit version of above without chassis, case and hardware. £12.95 plus £1.50 p&p.

PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT

COMPLETE WITH CASE

ONLY £31.00 plus £2.75 p&p.



- NOISE REDUCTION SYSTEM - AUTO STOP.
- TAPE COUNTER - SWITCHABLE E.O.
- INDEPENDENT LEVEL CONTROLS.
- TWIN V.U. METER.
- WOW & FLUTTER 0.1%.
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING.
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.

PERSONAL LS AMPLIFIER KIT


Amplifier for your personal stereo cassette player - as featured in January issue of Everyday Electronics. Turn your personal stereo into a mains powered home unit.



Parts:
Stereo power amp PCB with all components, £3.50 + 75p p&p.
Power supply unit £1.95 + £1.50 p&p. Pair of elliptical speakers, £1.50 the pair + £1 p&p. Input & output sockets and plugs, £1.50. Recommended case (for the power supply and amp only), £2.95 + 80p p&p. P&P inclusive price of £1.75 for any two or more.

125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is performed and ready to use. Supplied with all parts, circuit diagrams and instructions.

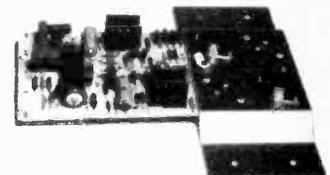

SPECIFICATIONS:
Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

ACCESSORIES: Suitable mains power supply kit with transformer: £8.50 + £2.00 p&p. Suitable LS coupling electrolytic. £1 + 25p p&p.

KIT £10.50 +£1.15 p&p
BUILT £14.25 +£1.15 p&p

BSR RECORD DECK SPEAKER BARGAINS

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45rpm spindle adaptor ideally suited for home or disco.



£12.95 + £1.75 p&p. 13" x 11" app.
SPECIAL OFFER! Replacement Stereo cassette tape heads - £1.80 each. Mono: £1.50 each. Erase: £0.70 each. Add 50p p&p to order.

2 WAY 10 WATT SPEAKER KIT
8" bass/mid range and 3 1/2" tweeter. Complete with screws, wire, crossover components and cabinet. All wood pre-cut - no cutting required. Finish - chipboard covered wood simulate. size 14 1/2" x 8 3/4" x 4". **PAIR FOR ONLY £12.50 plus £1.75 p&p.**



All mail to: **21E HIGH STREET, ACTON, W3 6NG.**
Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/10/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

ALL CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT.



CLEF ELECTRONIC MUSIC



ELECTRONIC PIANOS

SPECIALISTS SINCE 1972
Clef Pianos adopt the most advanced form of Touch Sensitive action which simulates piano Key inertia using a patented electronic technique.

7½ OCTAVE DOMESTIC MODEL COMPONENT KIT £266 COMPLETE KIT £442 MANUFACTURED £695

Two Domestic Models are available including the 88 note full size version.

Four intermixable Voice Controls may be used to obtain a wide variation of Piano tone, including Harpsichord. Both Soft and Sustain pedals are incorporated in the Design and internal Effects are provided in the form of Tremolo, Honky Chorus, and Phase Flanger.

A power amplifier integrates into the Piano top which may be removed from the Base for easy transportation.

SIX OCTAVE DOMESTIC MODEL COMPONENT KIT £234 COMPLETE KIT £398 MAN £620

Component Kits include Keyboard, Key switch hardware, and all electronic components and may be purchased in four stages at no extra cost.

Complete Kits further contain Cabinets, wiring harness, Pedals and in the case of Domestic Models both Power Amplifier and Speaker.

The Six Octave Stage Piano has the same range of Voices and Effects and is designed for use with an External Amplifier and Speaker.

SIX OCTAVE STAGE MODEL COMPONENT KIT £234 MANUFACTURED £580

AMDEK Kits

- Distortion £32
- Compressor £36
- Phaser £40
- Tuning Amp £36
- Metronome £63
- Flanger £54
- Chorus £54
- St. Mixer £90
- Graphic £72
- Delay £130
- Percussion £54
- Rhythm £90

by ROLAND



MICROSYNTH THE COMPACT MUSIC SYNTHESIZER



COMPLETE KIT £129.00

- SWITCH ROUTING
- THUMBWHEEL

- 2½ OCTAVES
- 2 OSCILLATORS
- 2 SUB-OCTAVES

STRING ENSEMBLE

A very popular Keyboard Synthesizer Kit for Group or Home use. Four Octave polyphonic instrument with split Keyboard facility. Cabinet requires control panel (not supplied) to be fitted to side of keyboard.

COMPONENT KIT £197.50
CABINET £41.40

ROTOR-CHORUS

Comprehensive two speed organ rotor simulator plus a three phase chorus generator.

COMPONENT KIT £88.00

KEYBOARDS

Our Square Front Keyboards
88 NOTE (A-C) £62.67
73 NOTE (F-F) £51.75
FIVE OCTAVE £41.97
FOUR OCTAVE £31.62

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published in technical magazines. With musical quality of paramount importance, new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability. Back up TELEPHONE advice is available to all our customers. All instruments are on show.

PRICES INCLUDE VAT, UK CARRIAGE & INSURANCE (CARRIAGE EXTRA ON MPD PIANOS). Please send S.A.E. for our complete list, or use our telephone VISA/ACCESS Service. Competitive quotations can be given for EXPORT orders - in Australia please contact JAYCAR in Sydney. Visit our showroom.


CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. ET1), 44A Bramhall Lane South, Bramhall, Stockport, Cheshire SK7 1AH 061-439 3297

"THE COMPUTER BAND-BOX"

COMPLETE KIT £235

£320 MANFD.

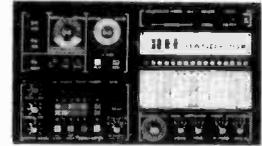

(MASTER RHYTHM ALSO REQUIRED)

A revolution in the field of Computer Music Generation!

A musicians instrument for vocal & instrumental soloists practice - live performance - recording

The BAND BOX provides an Electronic Backing Trio consisting of Drums, Bass, and a Chord Instrument (one of 16 Waveform/Envelope combinations), with the capacity to store over 3,000 User Programmable Chord Changes on more than 120 different Chords. Using advanced Microprocessor technology, Playback of 50-100 Scores can be executed in any Key and at chosen Tempo. Complete Music Pad is electronically indexed and stored on secondary battery back-up. Facility exists for composition of Intro, Repeat Chorus, and Coda sections including Multiple Score Sequences. Sockets are provided for Volum Pedal and Footswitch plus separate and mixed instrument Outputs. Total size 19" x 11" x 4" incorporating Master Rhythm.

THE Programmable DRUM MACHINE

EIGHT TRACK PROGRAMMING/
TWENTY-FOUR PATTERNS/
TWELVE INSTRUMENTS/
SEQUENCE OPERATION.
COMPLETE KIT £79

MANFD. - £119



The Clef Master Rhythm is capable of storing 24 selectable rhythmic drum patterns, invented, modified, and entered by the Operator on to Eight Instrumentation tracks. A three position Instrumentation control expands the number of instruments available to twelve, grouped into sounds typical of playing with Drumsticks, Brushes, or Latin American Bongos and Claves. Sequence operation allows two rhythm sections to be coupled with the second (B) section appearing at four, eight or sixteen Bar repetition. All drums can be adjusted for level and resonance on internal controls to suit individual taste, thus producing good musical sounds on a battery driven unit 8½" x 5" x 2½".

Accurate Digital Multimeters at Exceptional Prices

NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION MODELS 6010 & 7030

- 10 amp AC/DC
- Battery: Single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm.
- Weight: 400g inc. battery.
- Mode Select: Push Button.
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 2MΩ
- Input Impedance: 10MΩ
- Display: 3½ Digit 13mm LCD
- O/Load Protection: All ranges

OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010
-5% Accuracy
£29.95

7030
-1% Accuracy
£35.95

NEW HM102 BZ
£13.00

NEW HM 102 BZ SPECIFICATION

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500µA, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.

HM 101 POCKET SIZE MULTIMETER SPECIFICATION

- DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts
- Decibels: -10 to +22dB
- DC Current: 0-100mA
- Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- Price £5.50

Add 15% to your order for VAT. P&P is free of charge. Quantity discount for trade on application.

ARMON ELECTRONICS LTD.


Cottrell House, 53-63 Wembley Hill Road, Wembley Middlesex HA9 8BH, England

Telephone 01-902 4321 (3 lines)

TELEX No 923985



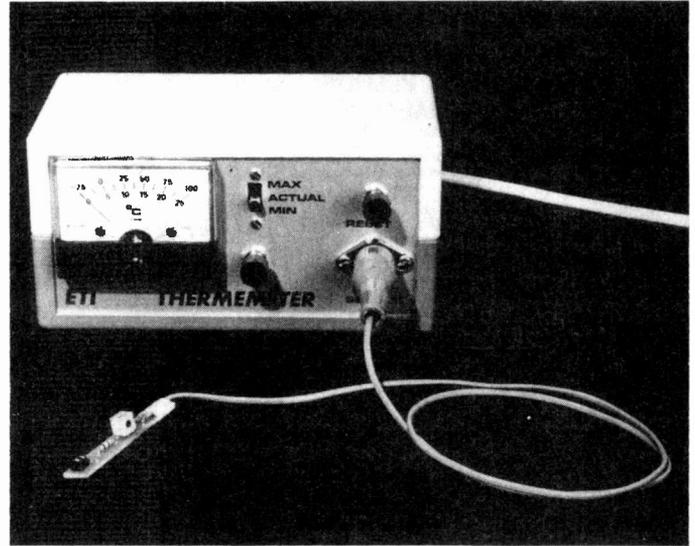Time was when a maximum-minimum thermometer had alcohol and mercury and little magnetic things in the glass tube. The ETI version is less fragile, more versatile, and can interface to control equipment. Design by Phil Walker.



MAX/MIN THERMOMETER

This project can monitor the temperature of its surroundings while storing the maximum and minimum temperatures reached in digital form. While the normal readout is by analogue meter, the data on the maximum and minimum temperature can be read out as two eight-bit numbers, possibly into a micro system or other type of data or control system. The unit will store its information until the mains supply is switched off or the reset button is activated. Switching the readout mode will not change the date.

Units such as this are useful for checking the central heating, making sure that the greenhouse is not getting too hot or cold, weather forecasting, or even checking the freezer. With a few simple mods it would be possible to convert the unit to an under or over temperature alarm and program it digitally. (This is left as an exercise for the reader — please don't write to us!)

The Circuit

This can be considered as several main blocks. First we have the clock generator which produces a series of narrow pulses at a fairly low frequency. These pulses are deliberately made narrow to avoid the possibility of spurious clock pulses being generated by the comparator circuits when the analogue output voltage from the D-to-A converters changes. These clock pulses are applied to gating circuits which will allow them to go

on to the D-to-A converters only when conditions are correct.

The D-to-A converters used in this project are of a type which contain an internal eight-bit counter. This allows us to make an A-to-D converter with few external components. Moreover we can stop and start the conversion process whenever required.

The method used for A-to-D conversion is to reset the counters to all zeros at which time the analogue output voltage will fall to 0 V, and then supply clock pulses to the counter until the analogue

output rises sufficiently to cause a comparator to change output states and cut off the clock pulses. The analogue output voltage from the D-to-A converter will now match the voltage at the other input to the comparator and will stay at this level until the other input voltage changes in such a way that the comparator changes state again and re-enables the clock pulses to the counter.

The two configurations used in this project both work in this way, except that one D-to-A output is used direct for the 'MAX' detector

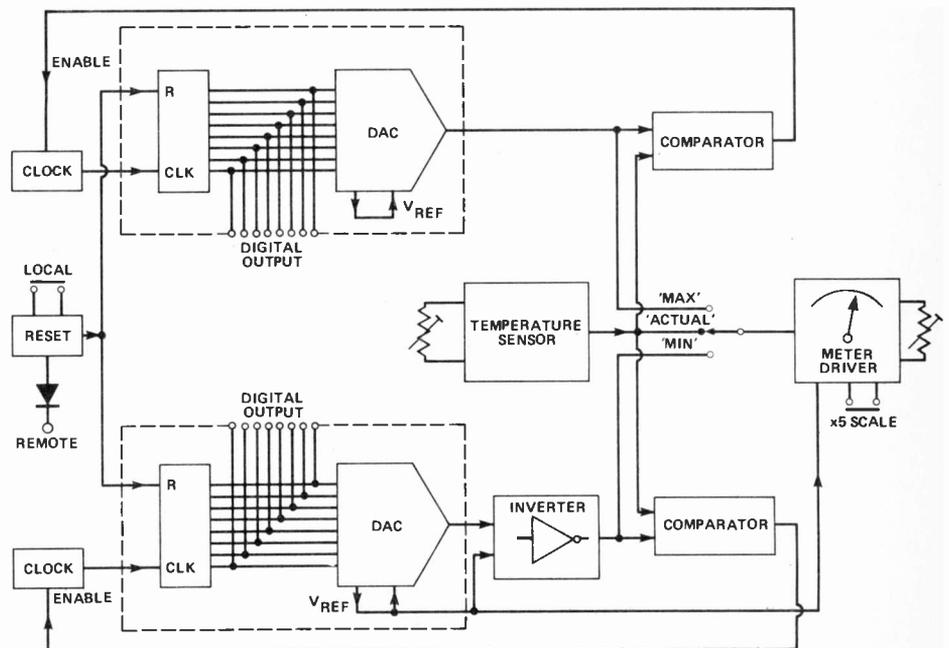


Fig. 1 Block diagram of the max/min thermemeter ('cos it remembers — geddit?).

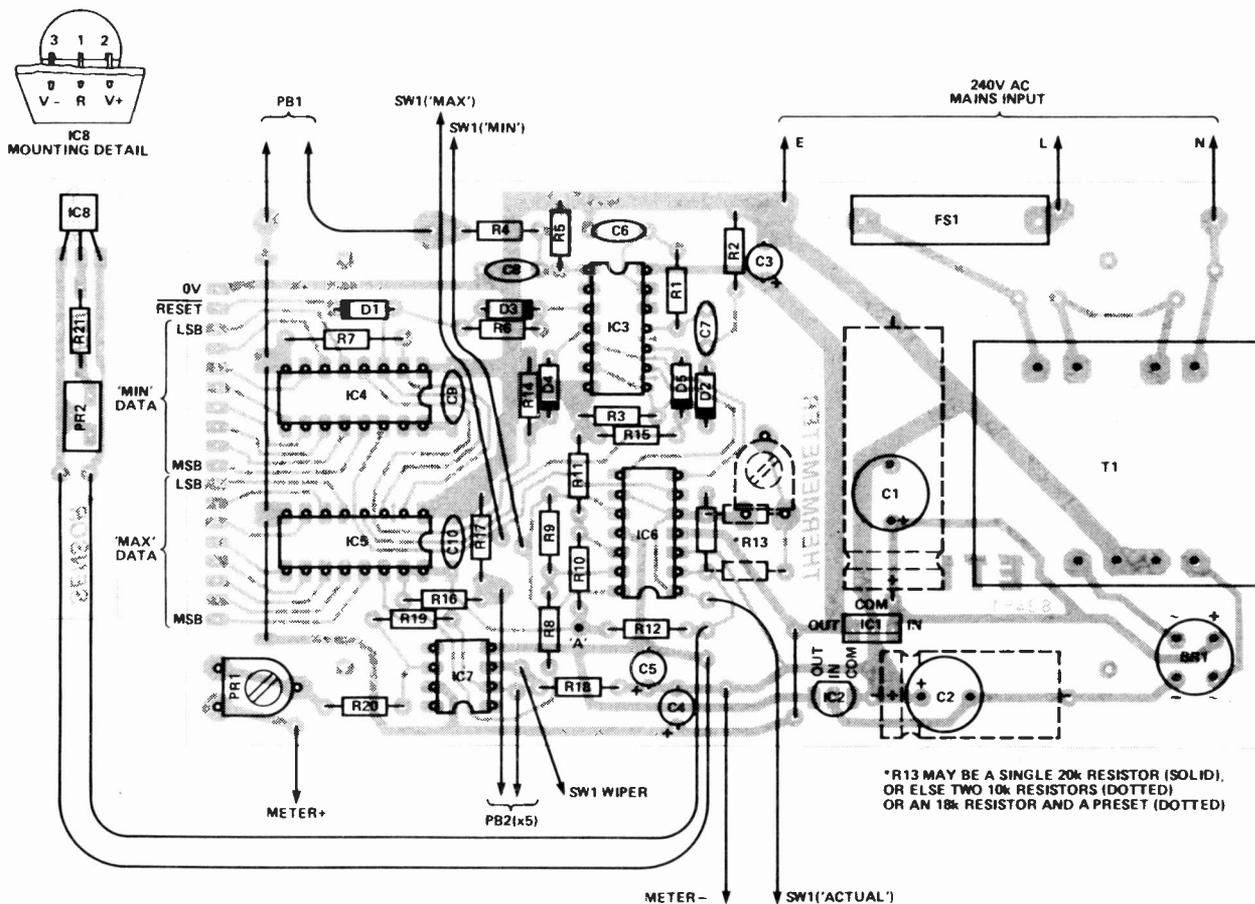


Fig. 2 Component overlay for both boards.

while the other is inverted, such that it starts at maximum volts and falls towards 0 V as the counter increments. This is used to drive the 'MIN' detector circuit. The result of the circuitry is that one D-to-A

output follows and stores the maximum voltage while the other follows and stores the minimum.

The other input to the comparators mentioned above is a voltage proportional to temperature.

In the first instance this is generated as a current by a LM334Z IC. The current through this device is directly proportional to *absolute* temperature. This current is fed into the summing input of an operational amplifier together with a constant offset current derived from the reference voltage source of the D-to-A converter. The resultant current generates a voltage at the output of the op-amp suitable for driving the comparator inputs.

The final part of the circuit is the readout. This is provided by a moving coil meter driven by a high impedance buffer. This can be switched to read 'MAX', 'MIN' or 'ACTUAL' temperatures over the ranges -25 to +100°C or 0 to +25°C.

Construction

Construction of the PCB for this project should cause no problems. The main things to be careful with are remembering to insert the four wire links, the orientation of the ICs, diodes, capacitors etc and BR1. R13 can be either a single 20k 1% resistor as shown, two 10k 1% resistors or even an 18k 5% and a 4k7 preset. Pads are available on

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5% except where stated)

R1, 3, 5, 14-16, 19	100k
R2	10k
R4, 6, 7	1k Ω
R8-11	100k 1%
R12	10k 1%
R13	20k 1% (see text)
R18	1M Ω
R20	3k Ω
R21	180R

Potentiometers

PR1	2k Ω miniature horizontal preset
PR2	100R miniature vertical cermet preset

Capacitors

C1	470 μ 25V electrolytic (radial or axial)
C2	100 μ 25V electrolytic (radial or axial)
C3-5	10 μ 10 V electrolytic (PCB-mounting)
C6, 9, 10	220n polycarbonate
C7	470p ceramic
C8	100n polycarbonate


Semiconductors

IC1	7805
IC2	79L05
IC3	4093B
IC4, 5	ZN425E
IC6	TL084
IC7	TL081
IC8	LM334Z
D1-5	1N4148
BR1	Wo1 (100 V, 1 A potted bridge rectifier)

Miscellaneous

PB1, 2	Miniature push-to-make push-button
SW1	3-way slide switch, one pole only used
T1	9-0-9 V 3 VA miniature PCB-mounting mains transformer
FS1	500 mA, 20 mm fuse and PCB-mounting fuseholder
M1	500 μ A moving coil meter (60 x 47 mm)
PCBs	(see Buylines); Verocase, 155 x 85 x 80 mm; three-pin DIN plug and socket; cable, cable clamp, hardware etc.

Fig. 3 Complete circuit diagram.

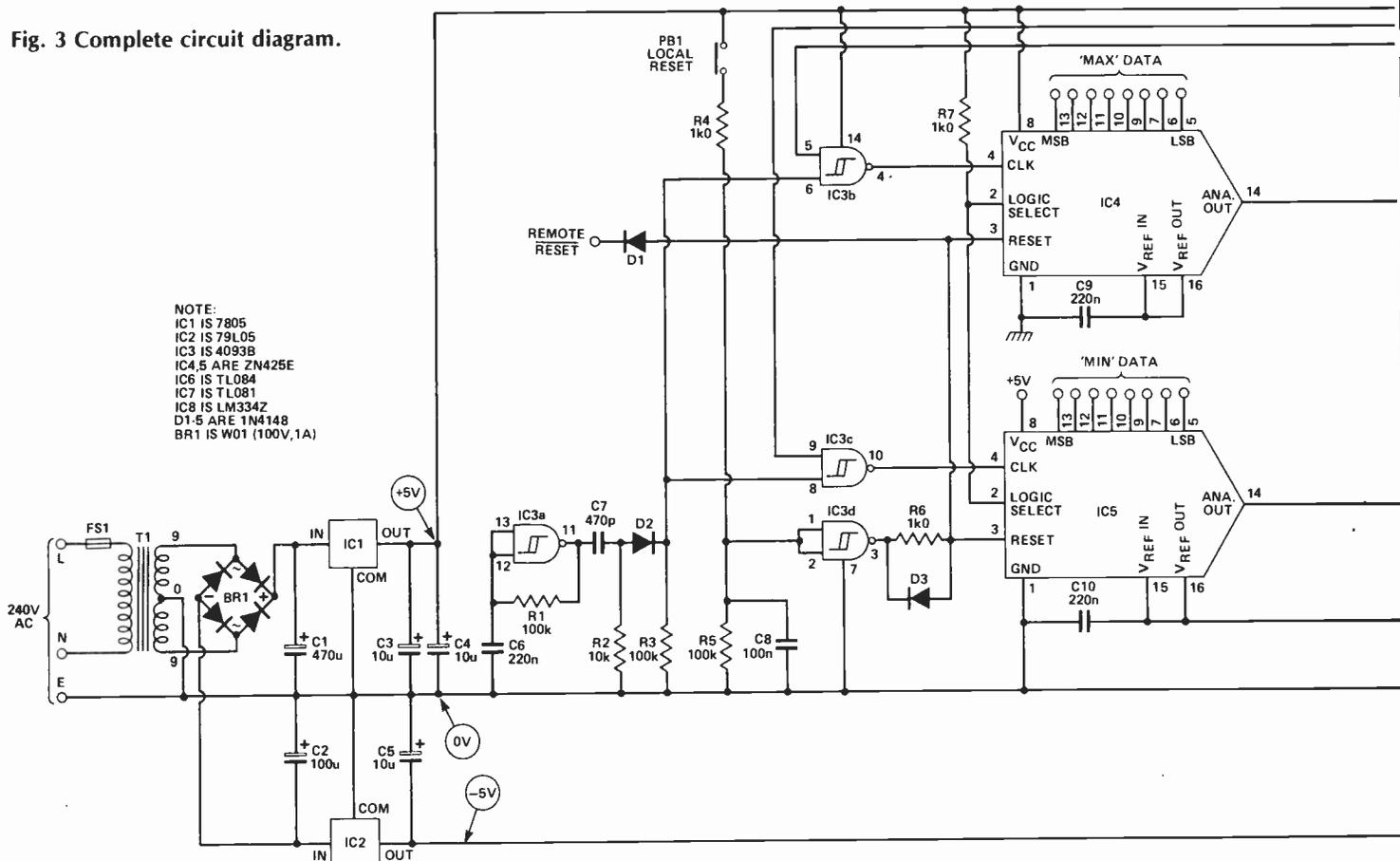

NOTE:
 IC1 IS 7805
 IC2 IS 79L05
 IC3 IS 4093B
 IC4,5 ARE ZN425E
 IC6 IS TL084
 IC7 IS TL081
 IC8 IS LM334Z
 D1-5 ARE 1N4148
 BR1 IS W01 (100V,1A)

HOW IT WORKS

IC3a, R1 and C6 form the master clock circuit, which generates a square wave of around 50 Hz or so. This is differentiated by C7 and R2 and the positive spikes only are passed via D2 on to IC3b and IC3c. Only when the other inputs to these gates are high will the spikes be inverted and passed on to the D-to-A converters, IC4 and IC5, as clock pulses. IC3d, R4, R5 and C8 take the input from PB1 and produce a suitable reset signal for the two DACs. This can, however, be overridden by a direct input via D1 (take terminal low to reset), allowing remote control by a computer, for example.

The D-to-A converters, IC4 and IC5, contain an internal counter which can be used when pin 2 of the device is high. This condition is maintained by R7. The counter is reset by a low on pin 3 and will respond to clock pulses on pin 4. After reset the output from the device is at 0 V: at each clock pulse the output voltage rises by 10 mV to a maximum of 2V55 (another clock pulse at this point will take it back to 0 V). The output from IC4 is compared with the output from the temperature sensor circuit by comparator IC6c and while it is lower, IC6c output will be high, so IC3b pin 5 will be high and enable the clock signal to IC4. While this condition persists the output from IC4 will rise steadily until it equals

and exceeds the output from the sensor circuit. Now the output from IC6c will go low, IC3b input will be low and no more clock pulses will reach IC4. The output from IC4 will stay at the same level until either the temperature sensor voltage exceeds it again or the reset function is used. The output from IC4 is thus a measure of the maximum temperature reached, since it can only increase unless reset.

The circuit around IC5 works in a very similar way except that its output is inverted by IC6a such that the voltage presented to the comparator IC6d starts at 2V55 and falls to 0 V as the counter in IC5 is incremented. In this case the output from IC6d is high while the output from IC6d is higher than the output from the temperature sensor circuit. This means that the voltage from IC6d will start from 2V55 at reset and fall until it matches the output from the temperature sensor. It will stay at that level until the temperature sensor output falls to a lower level or the reset is operated. This means that the output from IC6d is a measure of the minimum temperature, since it can only decrease unless reset.

The temperature sensor device is an LM334Z. This IC is designed as a constant current device but has a linear

temperature coefficient. In effect the current is proportional to the absolute temperature ($0^{\circ}\text{C} = 273^{\circ}\text{K}$ or Absolute). In this circuit R12 supplies a constant 255 μA from the voltage reference terminal of IC5 to the virtual earth (inverting) input of IC6b. The temperature sensor IC8 is set up so that it takes this amount of current at -25°C : this means that the output voltage of IC6b will be 0 V at this temperature. As the temperature rises the current drawn by IC8 will increase and the output voltage from IC6b must rise so that the extra can be sent through R13. The voltage across R13 will be directly proportional to the temperature rise. Setting of the sensor current is accomplished by PR2 and R21.

The normal method of indication for this project is by means of a moving coil meter, with SW1 selecting the display of the maximum, minimum or actual temperature. IC7 is normally used as a high impedance buffer but by means of PB2 its gain can be increased to x5 for greater ease of reading in the range of 0 to 25°C . The sensitivity of the meter is set by PR1.

The power supplies for this project are quite simple but a mains-derived type was felt to be desirable as the drain on the +5 V rail is in the region of 70 mA.

the PCB for all these options.

C1 and C2 may be vertical or horizontally mounted as desired, although we had to make C2 an axial type so as not to foul any of

the components mounted on the front panel of our tight-fit case. Take care to ensure that the mains input to the board cannot touch the rear panel (use insulating tape if

necessary). Use a cable clamp to secure the wire. Wiring to the front panel components is straightforward: the sensor PCB is connected to the main board via a

PROJECT: Thermometer

length of cable and a three-pin DIN connected on the front panel. The length of the wire is not critical so long as its insulation is good; however, care must be taken to keep the polarity correct.

For those people using the same meter as us (see Buylines), we've reproduced the artwork we drew for our prototype meter scale at the back of the magazine with the foil patterns (page XX). If you wish you can cut it out (get Mummy to help you with this) and use it to replace the existing scale.

Setting Up


The Meter Circuit. Zero the meter mechanically with the power off. Connect the input of IC7 (pin 3) to point 'A' (marked on the overlay diagram at the junction of R10 and R12) instead of to the wiper of SW1, apply the power and set the meter to full scale deflection using PR1. Remove the power and restore the connection from IC7 input to SW1 wiper.

The Sensor Circuit. Ensure that the total value of R13 is twice that of R12. If desired, R13 can be two 10k 1% resistors in series, or an 18k 5% resistor and a 4k7 trimmer if a 20k 1% device is not available. Pads have been provided on the PCB for one or two resistors or a resistor and a preset — the alternative positions are shown dotted on the overlay. The theoretical value for R13 is actually $2.016 \times R12$ but this sort of value is not easily available.


Connect the sensor, switch on the power and with the sensor immersed in a melting ice and water mixture, adjust PR2 until a reading of 0°C is obtained (one-fifth of full scale deflection). The unit should now be ready for use: coverage will be -25°C to $+100^\circ\text{C}$ in increments of 0.5°C approximately (256 steps) for the maximum and minimum functions, while the actual temperature is continuous.

BUYLINES



All the tricky bits for this project can be obtained from Rapid Electronics Ltd, Unit 1, Hill Farm Industrial Estate, Boxted, Colchester, Essex CO4 5RD. They stock the 1% resistors, the meter, the Verocase, the PCB-mounting transformer and the ZN425E. Everything else we've used is either readily available or not too critical. Our PCB Service order form is on page 87 if you aren't able to etch your own board.

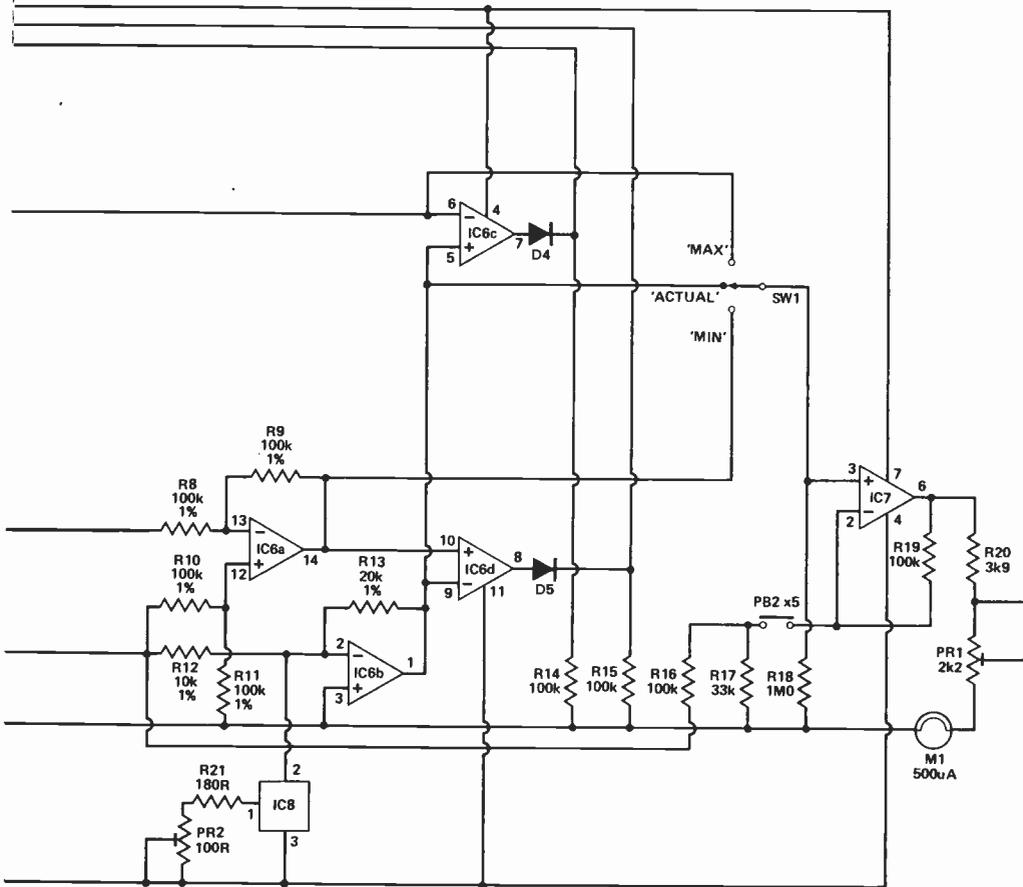

OPERATION OF VOLTAGE INVERTER

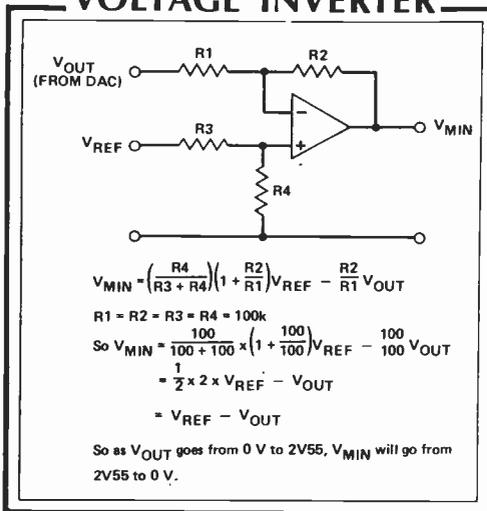

OPERATION OF REFERENCE

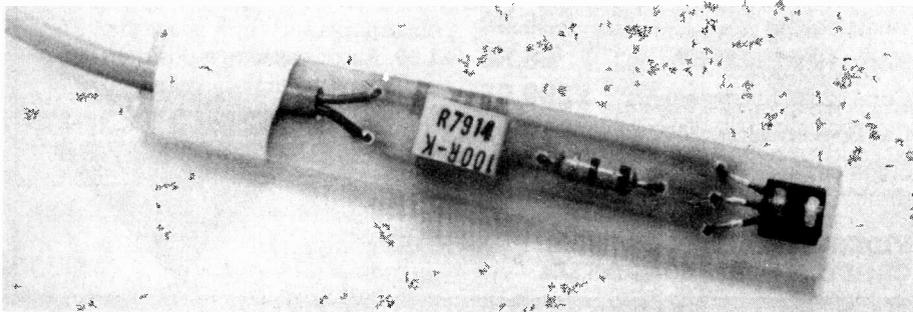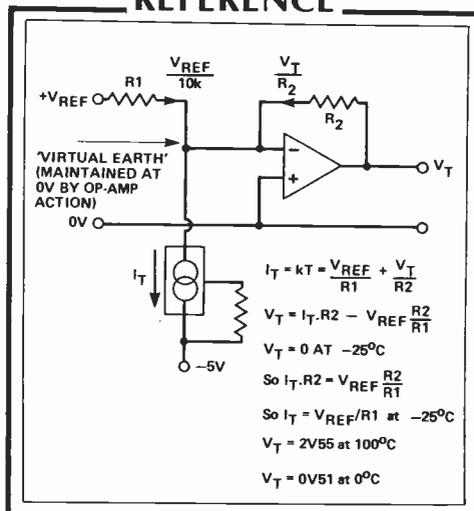

A close-up of the sensor probe; we used a cermet preset for stability.

PROJECT: Thermometer

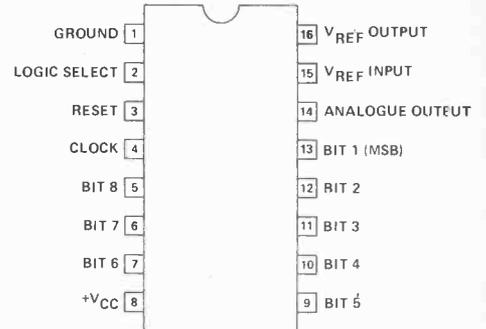
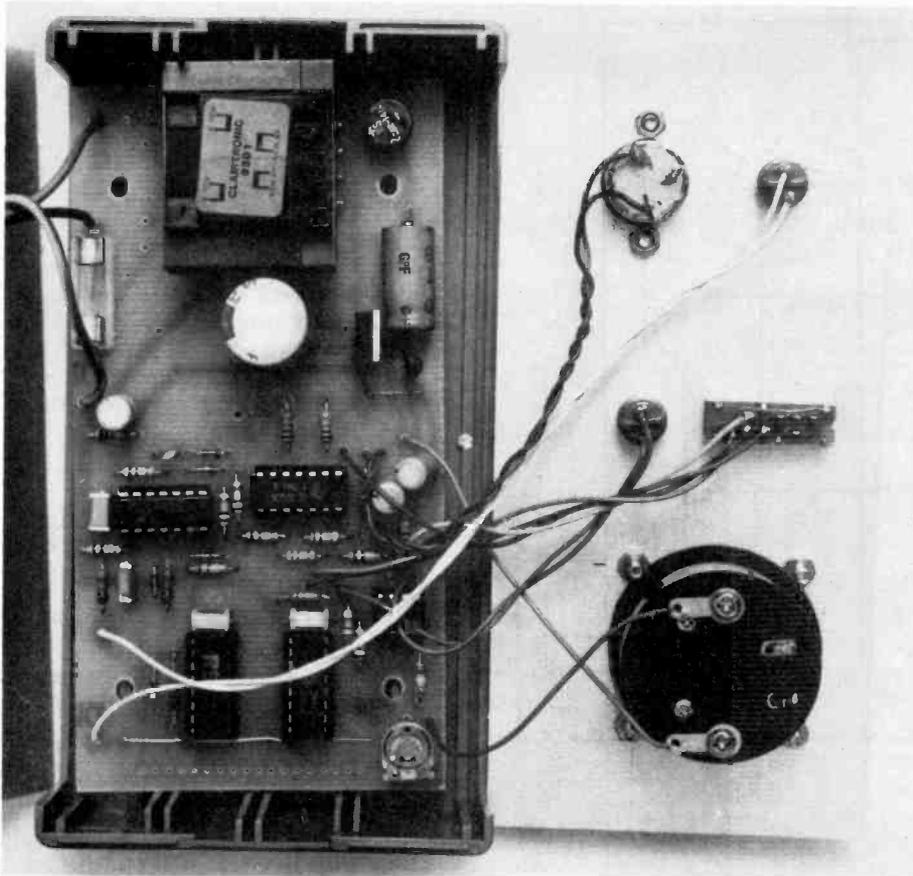


Fig. 4 (Above) The pin-out for the ZN425E digital-to-analogue converter.

(Right) Inside the box, you can see how cramped things are, and inexperienced constructors may wish to use a bigger box than the one we specify in Buylines. This is especially the case if you intend to fit some kind of interface socket for a digital readout of the data, to a control unit, for example. We didn't bother on the prototype.

ETI

'83 HOBBYISTS' BONANZA

* FIRST COME
* FIRST SERVED

For the first time in ten years, Videotone is to make available directly to the hobbyist, a selection from its vast amount of experimental and prototype stock.

We have large quantities of first-class components, semi-finished and finished goods, including those listed below:-

Telephone or write with stamped, addressed envelope for full list of sale items. Technical enquiries on a personal basis only.


- | | | | |
|---|----------|--|---------------------------------------|
| 20 Watt Amplifiers | £29.95 | Cassette Mechanisms | £3.99 |
| 50 Watt Amplifiers | £34.95 | Complete Record Players | £24.95 |
| 40 Watt Loudspeakers | £29.95 | Fluorescent Clock Displays | £3.95 |
| 25W Encyclopaedia
loudspeakers | £26.00 | Various speaker cabinets, speaker
components, and Hi-Fi components from | £1.00. Audio cassette tapes from 45p. |
| Stereo Headphones (from) | £6.50 | Reductions on all stock items. | |
| Coral 120W Loudspeakers ... | £299.95 | | |
| Car Door speakers 20W | £10.95 | | |
| Speaker Drive Units
(from) (5W - 100W) | £2 - 100 | | |

**OPEN
FOR THE
WEEKEND OF
8th, 9th, 10th APRIL
FOLLOWING
FRIDAY 15th
& SAT 16th**



**VIDEOTONE LTD, 98 CROFTON PARK ROAD,
CROFTON PARK, LONDON SE4**

MONITORS

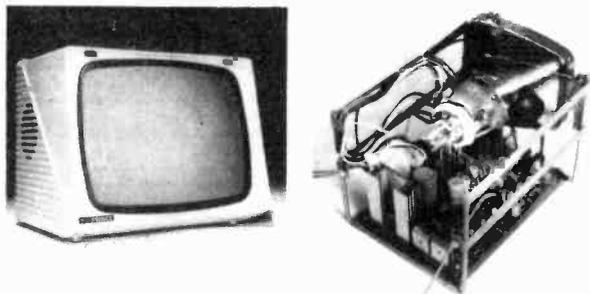

HIGH RESOLUTION - AND LOW COST!

Either cased or open frames to OEM's. The specification is right, the price is even better.

Phone or write to our Sales Manager, Richard Cox, for immediate action.

CROFTON ELECTRONICS LTD

35, Grosvenor Road, Twickenham, Middx, TW1 4AD.
Telephone: 01-891 1923/1513 Telex: 295093 CROFTN G

SPEAKER BUILDERS!



The 128/20 by **IMF ELECTRONICS** is the advanced bass driver used in that company's ruthlessly accurate professional and domestic monitors. A massively constructed styrene and fibreglass coned woofer, the 128/20 enables outstanding bass performance (free air resonance is typically only 20Hz) and is now available to the home constructor from sole distributor **Badger**.

128/20 is only one of a series of new IMF Electronics drivers featured, with data, enclosure suggestions and even active conversions (our 204011 active system was the main project in ETI September 1982) in our 1983 catalogue. Please send 4 x 15½p (overseas 3 dollars).

Stockists of **CRIMSON ELEKTRIK** components and kits


BADGER SOUND SERVICES LTD

46 WOOD STREET,
LYTHAM ST. ANNES,
LANCS. FY8 4QG

Telephone: 0253 729247
(closed Mondays)



New Products

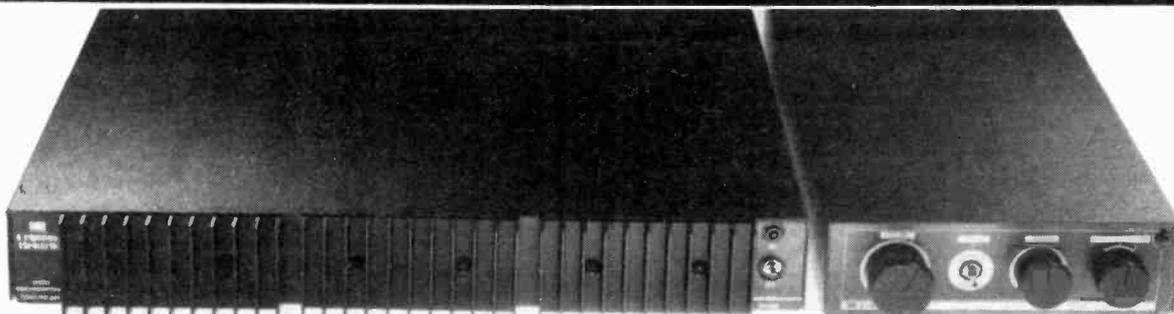

HIFI STEREO AMPLIFIER KITS

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty.

These new kits offer the choice of moving magnet or moving coil inputs, 40 to 100 watts per channel, in fact, everything that made the previous models so popular is included but with added style, easier construction and a full two year warranty.

The new range consists of The CK 1010 Stereo Pre Amplifier, The CK 1040 WPC Power Amplifier, The CK 1100 WPC Power Amplifier.

CK 1010

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled and tested therefore construction is simply a matter of point to point wiring and mechanical assembly of the connections and controls to the pre punched chassis.

The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

CK 1040

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsinks, wire and connectors are included and protection is provided from short circuit outputs.

CK 1100

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard. When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kit-build field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few — such as the KA-1000 (£500+) — are of comparable standard. . . . I can say no more than that for £250 it (CK 1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

PRICES CK 1010 — RRP £92.00; CK 1040 — RRP £121.00; CK 1100 — RRP £151.00; MC2K — RRP £25.00; PSK — RRP £20.00

Barclaycard or Access accepted, otherwise send C.W.O. C.O.D. £1.00 extra. All prices include P&P to anywhere in the U.K. Export: Write for pro-forma

SEND FOR FULL DETAILS ON OUR HIFI KIT PRODUCTS BY WRITING TO FREEPOST ADDRESS BELOW



Crimson Elektrik (Stoke)

LONDON DISTRIBUTOR: BRADLEY MARSHALL LTD, 325 EDGWARE ROAD, LONDON W21 8BN

PHOENIX WORK
500 KINGS STREET
STOKE-ON-TRENT
TEL: 0782 330520

HAPPY MEMORIES

Part type	1 off	25-99	100 up
4116 200ns	0.90	0.81	0.78
4116 250ns	0.70	0.63	0.60
4816 100ns For BBC comp	2.25	2.01	1.95
4164 200ns	3.99	3.56	3.42
2114 200ns Low power	1.15	1.00	0.90
2114 450ns Low power	0.95	0.85	0.80
4118 250ns	3.35	3.00	2.85
6116 150ns CMOS	3.55	3.20	2.95
2708 450ns	2.35	2.10	2.02
2716 450ns 5 volt	2.60	2.25	2.10
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.50	3.15	3.00
2532 450ns Texas type	3.70	3.30	3.00
Z80A-CPU £3.95	Z80A-Pi0 2.99	Z80A-CTC £2.99	
6522 PIA 3.70	7002 A-D £4.60	3691 2.75	
88LS120 £2.20	7805 reg 0.50	7812 reg 0.50	

Low profile IC sockets:

Pins	8	14	16	20	22	24	28	40
Pence	9	10	11	14	15	18	19	25

Soft-sectored floppy discs per 10 in plastic library case: 5 inch SSSD £17.00; 5 inch SSDD £19.25; 5 inch DSDD £21.00; 5 inch DSQD £26.35; 8 inch SSSD £19.25; 8 inch SSDD £23.65; 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or phone for list.

Please add 50p post & packing to orders under £15 and VAT to total. Access & Barclaycard welcome. 24 hour service on (054 422) 618. Government & Educational orders welcome, £15 minimum. Trade accounts operated, phone or write for details.

HAPPY MEMORIES (ETI)

Gladestry, Kinston, Herefordshire HR5 3NY Tel: (054 422) 618 or 628

POWER DIMMER MODULES

A range of electronic modular dimmers designed to suit your custom channel and facility requirement


- Considerable saving over commercial equipment
- All the commercial facilities and more
- Compatible special effects
- Preset/remote/master
- Easily installed and wired

SPC - Simple but effective 1000W controller	£15.70
SPU - Used in conjunction with RS units for Remote desks in 1000 and 2000W versions	£11.90
MC - Master dimmer for SPC/RS units	£7.90
RS - Remote controller for SPU/SPC Units	£9.40
SUP/REF - Supply/signals for up to 50 modules	£20.00

Discounts on above only (order £100 to £199 25% £200 to £299 £300 + 35%)	
EFFECTS ACCESSORIES	
MXSL - Four channel sound to light	£33.20
MXLS - Four Channel Sequencer	£21.40
MXLC-S Four Channel sound chaser	£24.00
MXECF - Dip/Dipless Electronic Crossfade	£28.70

3 CHANNEL SOUND/LIGHT CHASER £35.70


LB31000SLC

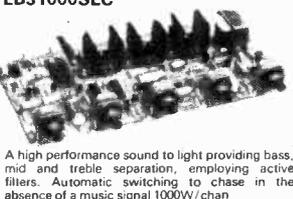

A high performance sound to light providing bass, mid and treble separation, employing active filters. Automatic switching to chase in the absence of a music signal 1000W/chan

STEREO DISCO MIXER/PREAMP

LBPA3
M - Magnetic
C - Ceramic

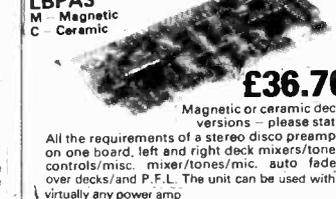

£36.70

Magnetic or ceramic deck versions - please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/controls/misc. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with virtually any power amp

3 CHANNEL SOUND/LIGHT £22.70

LB31000SL



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

AND MORE!

- * 4 CHAN S/L AUTO CHASER
- * 4 CHAN MULTI SOUND CHASER
- * 4 CHAN SEDUCER
- * 4 CHAN SOUND CHASER
- * FASCIA PANELS

Active Crossovers £17.90 (supply £7.20) (3-way 300Hz/3kHz)

Don't hesitate to write or phone for immediate information. All prices include VAT. Please include 75p post except power dimmer (£2.75). Cheques/PO/COD/Access all welcome. Tel: 01-640 6063 (Mon to Fri 9 to 4.30) L & B ELECTRONIC 34 Oakwood Ave, Mitcham, Surrey CR2 1AQ

E.T.I. KITS

ALL KITS INCLUDE PCBs

Full kits include printed circuit boards, components, hardware, I.C. sockets, cases etc. unless stated (not batteries). If you do not have the issue of E.T.I. which

includes the project - you will need to order the instruction reprint at an extra 45p each. PCBs included. Reprints available separately 45p each + p&p 45p.

ZX ADC Jan 83	£34.98	WATCHDOG SECURITY ALARM Aug 81	£47.86
SPECTRACOLUMN Dec 82. Less case and lights	£34.85	RECHARGEABLE BATTERY extra	£19.96
PLAYMATE Aug/Sept 82, less optional foot pedal + mains unit	£39.98	HANDCLAP SYNTHESIZER Aug 81	£32.98
Case extra	£28.42	WAH PHASE June 81. Less pedal	£14.78
DUAL LOGIC PROBE Sept 82	£14.98	LED JEWELLERY June 81. Cross	£2.98
AUTO VOLUME CONTROL Sept 82 £4.28 less case	£17.57	Star £9.91 Spiral £7.98	
INSULATION TESTER May 82	£17.57	GUITAR NOTE EXPANDER April 81	£17.98
AUTORANGING CAPACITANCE METER Mar/April 82	£71.99	DRUM MACHINE April 81	£85.97
HIGH QUALITY PHONO AMPLIFIERS Feb 82. Less case	£19.76	ENGINEERS STETHOSCOPE Mar 81	£20.98
MOVING COIL STAGE	£19.80	SOUND PRESSURE LEVEL METER Feb 81	£43.98
MOVING MAGNET STAGE	£19.80	INFRA RED ALARM Feb 81	£59.98
PEST CONTROL Feb 82	£7.46	4 INPUT MIXER Dec 80	£21.74
GUITAR TUNER Jan 82	£31.87	MUSICAL DOORBELL Dec 80	£12.77
COMPONENT TESTER Dec 81	£8.78	METRONOME Nov 80	£8.58
CAR ALARM Nov 81	£19.77	ULTRASONIC BURGLAR ALARM Aug 80	£29.50
ENLARGER TIMER	£28.25	CAPACITANCE METER Aug 80	£22.28
SOUND BENDER Oct 81	£22.84	CMOS LOGIC TESTER Aug 80	£11.98
		CLICK ELIMINATOR April 79 £87.70 Or less case	£49.98

MORE KITS - SIMILAR STYLE TO ETI

Instructions included (separately 45p each) Please quote ref. no. when ordering

Q1 SEAT BELT REMINDER	£4.18	Q12 METRONOME	£12.98
Q2 ZX TAPE CONTROL	£8.93	Q13 ZX INTERFACE BOARD	£11.78
Q3 3 CHANNEL SOUND TO LIGHT	£21.44	Q14 DRUM SYNTHESIZER	£21.82
Q4 WEIRD SOUND EFFECTS GENERATOR	£5.98	Q15 TELEPHONE BELL REPEATER	£3.98
Q5 IN SITU TRANSISTOR TESTER	£8.98	Q16 ECHO REVERB	£24.43
Q6 ELECTRONIC DICE	£5.71	CASE extra	£2.76
Q7 DIGITAL CAPACITANCE METER	£21.82	Q17 MEMORY BANK - MINI SYNTH	£30.43
Q8 CABLE TRACKER	£10.43	Q18 MASTHEAD AMPLIFIER	£14.98
Q9 SIGNAL TRACER	£4.31	Q19 GUITAR PRE AMP	£8.98
Q10 CONTINUITY CHECKER	£5.98	CASE extra	£2.29
Q11 FUZZBOX	£11.43	Q20 ULTRASONIC BURGLAR ALARM	£20.43

MAGENTA ELECTRONICS LTD

EB26, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS DE14 2ST 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY

ADD 45p P&P TO ALL ORDERS

ACCESS AND BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST. SAE ALL ENQUIRIES

Prices inc. VAT OFFICIAL ORDERS WELCOME OVERSEAS Payment must be in sterling. IRISH REPUBLIC and BFPO - UK PRICES. EUROPE - UK PRICES + 10%. ELSEWHERE - Write for Quote

Rocar Electronics

53 Edgeworth, Heron Garden, Yate, Avon. MAIL ORDER ONLY

CHEAPEST COMPONENTS PRICES!

Please add 50p P&P and 15% VAT

4000 10p	4027 18p	4048 35p	4081 12p
4001 10p	4028 35p	4049 20p	4082 12p
4002 10p	4029 40p	4050 20p	
4006 40p	4030 14p	4051 40p	
4007 12p	4035 50p	4052 45p	
4008 10p	4037 £1.00	4060 40p	
4009 22p	4040 35p	4066 20p	
4010 22p	4041 35p	4068 12p	
4011 10p	4042 35p	4069 12p	
4012 10p	4043 40p	4070 12p	
4013 18p	4044 40p	4071 12p	
4014 40p	4045 85p	4072 12p	
4015 35p	4046 40p	4073 12p	
4016 18p	4047 35p	4075 12p	
4017 30p		4076 40p	
4018 40p		4077 12p	
4019 22p		4078 12p	
4020 40p			
4021 35p			
4022 35p			
4023 12p			
4024 30p			
4025 12p			

SCRS C106D	40p
C116D	60p
C126D	85p

Trics TIC 206D	50p
TIC 225D	60p
TIC 226D	80p
TIC 236D	90p
TIC 246D	£1.50

Voltage Regulators

7805 5V 1 amp	T0220	30p
7812 12V 1 amp	T0220	30p
7815 15V 1 amp	T0220	30p

I.C. Sockets

8 pin - 6p	18 pin - 10p	24 pin - 15p
14 pin - 7p	20 pin - 12p	28 pin - 20p
16 pin - 7p	40 pin - 20p	

L.E.D.s

3mm	5mm
Red	8p 8p
Yellow	8p 8p
Green	8p 8p

All devices full spec Brand new and guaranteed

ALARMS

FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT

AT UNBEATABLE PRICES!

SEND S.A.E. OR PHONE NOW FOR YOUR COPY

THIEFCHECK BURGLAR ALARM D-I-Y SYSTEM

A.D. ELECTRONICS DEPT. HE3 217 WARBRECK MOOR AINTREE LIVERPOOL L9 0HU/051 523 8440

MARCO TRADING



Primary	Secondary	Current	1+	10+	100+
240V	4.5-0-4.5V	400m/a	50p	45p	35p
240V	6-0-6	100m/a	58p	52p	43p
240V	6-0-6	500m/a	65p	60p	48p

Manufacturers note: We can supply OFF THE SHELF 1000+ quantities of the above transformers.

ADAPTORS



These high quality British made European Adaptors are ideal for driving radio's, cassette recorders, TV games, calculators etc etc.

These adaptors fit the UK shaver socket.

		Current	1+	10+	100+
E08	4.5V DC	200m/a	50p	45p	32p
EM3	6V DC	200m/a	£1.00	80p	55p
E09	6V DC	400m/a	£1.50	£1.25	85p

UK POWER SUPPLY/CHARGER. Input 240V. Output 9V 200mA. Fully Regulated and Stabilised. Complete with Reversible 4 Way Plug.
Price £2.95 + 75p p&p + VAT

MULTIMETER SPECIAL

Russian type U4324 20,000 O.P.V.
DC Voltage: 0.6, 1.2, 3, 12, 30, 60, 120, 600, 1200.
AC Voltage: 3, 6, 15, 60, 150, 300, 600, 900.
DC Intensity M/A: 0.06, 0.6, 6, 60, 600, 3000
AC Intensity M/A: 0.3, 3, 30, 300, 3000.
DC Resistance: 0.2, 5, 50, 500, 5000K.
ge level dB: 10 to + 12.

Special Price £15.00 inc p/p and VAT

Brand new 3 channel chart recorders from £89 including charts etc.

Send 35p Now for our latest Catalogue. Fantastic Value it includes capacitors, diodes, resistors, transistors, LEDs, boxes, cable, prepaid envelopes and much, much more.

Please add 35p postage and packing and 15% VAT to all orders.

Send orders to:

MARCO TRADING (Dept ET3)

The Maltings, High Street,
Wem, Shropshire SY4 5EN
Telephone: WEM (0939) 32763

Every order receives our latest special offer lists. Or send SAE.

All orders despatched by return of mail.

SPECTRUM

24 LINE INPUT/OUTPUT PORT.....	£18.95
(motherboard not required)	
MOTHERBOARD - SIX SLOTS.....	£26.50
MOTHERBOARD PCB ONLY.....	£6.50
SPECTRUM 28 WAY CONNECTOR.....	£3.25
MALE CONNECTOR.....	£1.80
34 WAY RIBBON CABLE per metre.....	£1.80

ZX81

40 KEY KEYBOARD.....	£20.00
SPARE KEYS each.....	£0.25
MOTHERBOARD - 2 SLOTS.....	£15.00
24 LINE INPUT/OUTPUT PORT.....	£18.95
16K RAM PACK.....	£25.00
MUSIC BOARD.....	£18.95
23 WAY FEMALE CONNECTOR.....	£2.50
MALE CONNECTOR.....	£1.60
24 WAY RIBBON CABLE per metre.....	£1.40
GETTING ACQUAINTED WITH YOUR ZX81.....	£4.95
PROGRAMMING FOR REAL APPLICATIONS.....	£6.95
REAL APPLICATIONS TAPE.....	£11.44
MASTERING MACHINE CODE.....	£7.50

Prices are for built items. Postage 40p under £4.00. Export postage (surface) £1.80. Access accepted. Send sae for full catalogue.

REDDITCH ELECTRONICS

21 FERNEY HILL AVENUE, REDDITCH
WORCS B97 4RU




When you need to update yourself with all that is available in the "Do-it-yourself" market, then you need the Hobby Herald.

Packed with product information essential to the electronics enthusiast, this new electronics catalogue lists over 60 exciting products ranging from All Purpose Cutters to Verobloc, the solderless breadboard. All products are available throughout the U.K. from over 200 stockists.

HOBBY HERALD

Alternatively ordering products through the Herald is simplicity itself, and you can pay by either cheque, Barclaycard or Access. So make sure you get your copy of Hobby Herald by ringing

(04215) 62829.

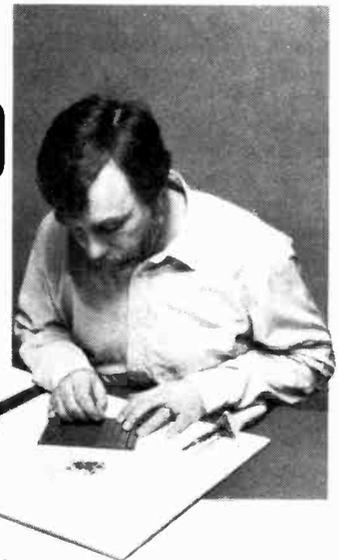

BICC-Vero Electronics Ltd.,
Industrial Estate,
Chandlers Ford, Hampshire,
SO5 3ZR.

BICC

vero

CONFIGURATIONS

Power corrupts, and absolute power corrupts absolutely. At least, it can burn out the odd diode or two. This month Ian Sinclair examines the area of power supplies and some of the facts you aren't often told.

Power packs, you might think, are among the simpler of electronic circuits to design, and yet there is probably more cut-and-try used in the power supply section of a circuit than in all the rest of the circuitry that you construct. The reason seems to be a lack of coherent explanations of the action of the reservoir capacitor — only too often you are simply told that it "provides an earth route for AC ripple", and no more. We have to start this month, then, by putting that sort of misconception to rights.

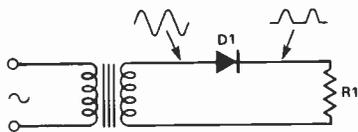


Fig. 1 Simple half-wave rectifier circuit with no reservoir capacitor. The waveform is unidirectional, but certainly not what we would call DC.

Consider for the sake of simplicity, a half-wave rectifier circuit and a load (Fig. 1). The waveform across the load will consist of about half of the input waveform, the positive half in this example because of the way we have chosen to connect the diode — reverse the diode and you will select the negative half of the wave. This type of output is called a *unidirectional* wave — the peaks are in one direction (positive) only, with no negative peaks — but it isn't exactly anyone's idea of DC. A DC voltmeter connected to the load of this circuit reads what DC voltmeters always read, the average voltage, which is around E_o/π ; approximately $0.32 E_o$, assuming that the diode is 'perfect' in the sense of having no forward voltage drop across it. We can allow for the forward drop, which can't be neglected if the output voltage is low, by subtracting its value from E_o , the peak AC input. This is only an approximation, but it is good enough for practical purposes.

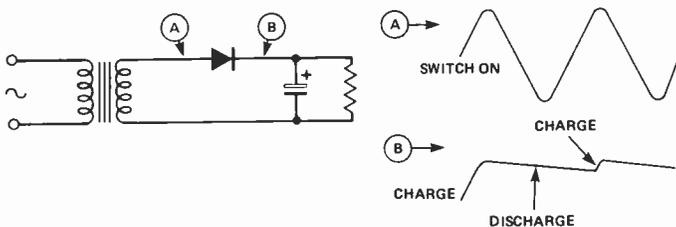


Fig. 2 A half-wave circuit with a reservoir capacitor added. The capacitor charges to the peak voltage of the input wave, and the charged capacitor supplies the load while the diode is reverse-biased.

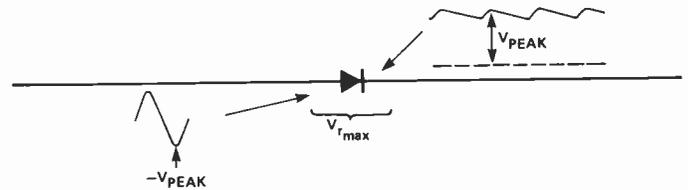


Fig. 3 This shows why the peak reverse voltage on the diode is doubled when a reservoir capacitor is used.

Bring On The Reserves

Now when a reservoir capacitor is connected to the circuit (Fig. 2), things change considerably. To start with, imagine that the load resistance is very high, so that only a small amount of current is being taken. Instead of the rectifier conducting for the whole positive cycle of the AC wave, it now conducts only for a tiny fraction of the time of the wave, right at the peak. The reason is that the first

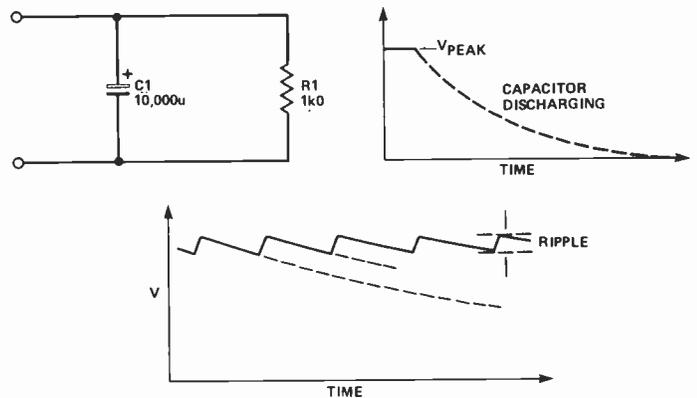


Fig. 4 The waveform of ripple, caused by the time constant of the reservoir capacitor and load resistance.

half-cycle, when the supply is switched on, will charge the reservoir capacitor to the peak positive value of the AC wave, less the forward diode drop, and when the AC input at the anode of the diode drops below this value, the diode will cut off. From this moment until the next positive peak of the wave comes along, all the current that is supplied to the load is supplied from the reservoir capacitor, which is why it's called a reservoir! Far from just being a bypass for AC, the reservoir is the main store and supplier of DC to the load.

All the current that dribbles out from the capacitor results in the voltage across the capacitor dropping as its charge is drained, so that the diode has to supply this

charge again next time it conducts. You don't get something for nothing — the diode passes large currents for short time intervals instead of conducting steadily over a half-cycle as it did when no reservoir was used. The overall result is that the diode has to be able to pass peak currents that are many times greater than the average current, it spends most of its time cut off, the maximum reverse voltage across the diode is twice the AC peak voltage (see Fig. 3), and there is a 'ripple' on the output wave which is caused by the drop in voltage as the reservoir capacitor discharges (Fig. 4). The waveform of this ripple is a sawtooth, rich in harmonics, not simply a piece of left-over sine wave as some explanations would hint at, so that it is a potent source of hum interference in the rest of the circuit.

The approximate amplitude (peak to peak) of the ripple is given by $I t / C$, where I is the average current drawn by the load, C is the size of reservoir capacitor, and t is the time between positive wavepeaks. Using units of milliamps for I , microfarads for C and milliseconds for t , we get units of volts for the amplitude of ripple. For example, if you draw 100 mA from a 1000uF capacitor with a half-wave rectifier for which t is about 20 mS, then the

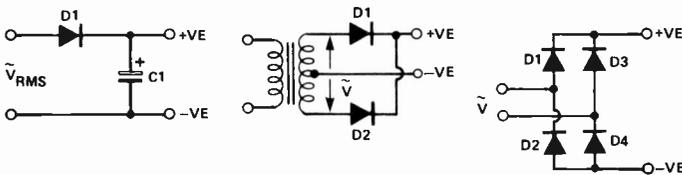


Fig. 5 A summary of the conditions for common power supply configurations.

ripple amplitude is $(100 \times 20) / 1000$, or 2 V, which isn't exactly negligible. Using a full-wave rectifier, which recharges the capacitor at 10 mS intervals, you get a 1 V ripple. This formula *isn't* foolproof — it applies only when you have the situation in hand, and will give silly answers if the reservoir capacitor is much too small or if the amplitude of the AC input is very small, but it's a good guide to realistic values for power supplies generally.

The voltage output of the circuit with no load current is equal to the AC peak voltage, but as the load current increases, the ripple also increases and the average DC output drops until it can become almost as low as the value you would get with no reservoir, $0.32 E_o$ for half-wave, and twice as much as for full-wave (bridge or split-secondary type of circuit). Figure 5 summarises the operating conditions for different rectifier configurations. Ripple, and the drop of output voltage when output load

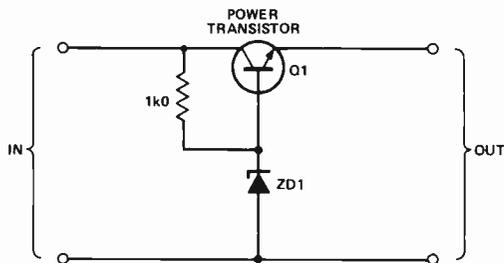


Fig. 6 An elementary stabiliser — the power transistor in this example would be a medium-power type with a high value of h_{fe} .

current is taken, can be minimised by increasing the size of the reservoir capacitor. Obviously, it is also an advantage to have a short time between recharging the reservoir, so that high-frequency supplies need less in the way of reservoir capacitance — one of the many reasons for the popularity of switch-mode power supplies these days.

A Stable Situation

Another defensive measure is stabilisation. Stabilisation does not mean that some circuit is used which will miraculously bump up the voltage output from the reservoir capacitor, it simply means making the best of what you have. Suppose you have a nominal 8 V supply, and that at the full planned output current of 150 mA it can have a 2 V peak-to-peak ripple. This value implies that the voltage will drop momentarily as low as 6 V twice on each AC cycle, assuming that full-wave rectification is used, so that if we use only 5 V of this supply, these changes caused by ripple will not affect the 5 V output at all. This is the action of a stabiliser — it's a circuit which is a voltage-dropper, but arranged so that the drop is variable, keeping the output voltage constant while the input voltage varies.

A stabiliser has to operate so as to fulfil two requirements. First it must keep its output voltage constant as the input voltage varies, and second, it must keep the output voltage constant as the load current varies. The two may sound identical at first glance, but they are not — the first calls for the output to be constant while the voltage across the stabiliser is varying, the second calls for the combination of the stabiliser and the rest of the power pack to have almost zero internal resistance.

Figure 6 shows a very basic form of stabiliser. The voltage at the output is set by the value of the zener diode, and because of the voltage across the base-emitter of a transistor, the output voltage will be around 0V6 less than the zener diode voltage. This should ensure that the voltage of the output is stabilised against changes at the input resistances of the order of a few milliohms can be ob-

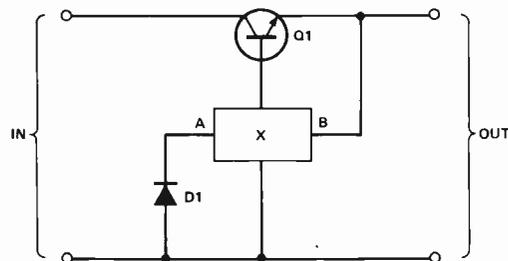


Fig. 7 A block diagram of the comparator type of power supply stabiliser. This type is rarely built nowadays because of the ready availability of IC equivalents.

tained using circuits of this type. crease to some extent as the load current increases. Nevertheless the stabilisation is better than it would be in the absence of the circuit (something wrong if it were not!), and can be improved by amplifying the signal to the base of the regulator transistor — a variation on the circuit is shown in Fig. 7. The output voltage is compared with the zener voltage, and the output of the comparator is used to control the base of the regulator transistor. Very low output resistances of the order of a few milliohms can be obtained using circuits of this type.

I've drawn the circuit as a block diagram because it isn't very often nowadays that we have to build stabilisers with separate components. The reason, of course, is the ready availability of IC regulators, particularly the 78

series. These take advantage of being ICs (so that circuit complications are not a problem for production, only for design) to incorporate features such as current foldback, meaning that the current will be regulated if there is any risk of over-dissipation. This ought to prevent overload and give these regulators a very long life — I say ought, because in my experience these regulators quite frequently fail, and I suspect that the fold-back arrangements are not always completely effective.

The 78 series covers most of the 'popular' supply voltages, but if we should want an odd value then a modification to the circuitry, as shown in Fig. 8, can do the

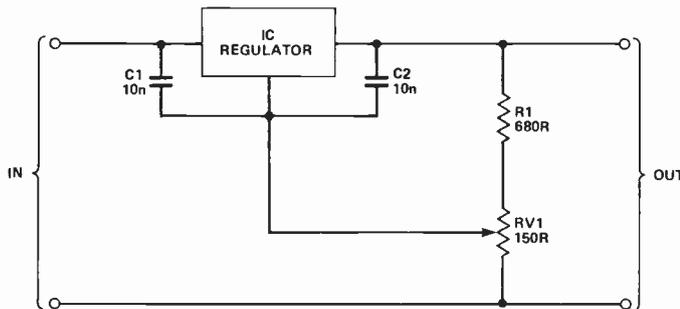


Fig. 8 Varying the output voltage of an IC stabiliser. A variable resistor is illustrated, but a fixed value resistor could be used once the correct value has been established.

needful, at the expense of a slight loss in stabilisation. Similarly, if we want a lot more current from the output than the normal 78 series can supply, then we can use the IC to control an external transistor, as shown in Fig. 9. Circuits like these can cope with about 99 per cent of our needs.

Switching The Subject

Having mentioned switch mode power supplies, however, I feel I should explain further because, unless you follow the development of TV circuitry, you may not have come across details of them (though a switch mode supply was used in the venerable Apple 2 computer, and a switch mode supply is now used in the BBC computer after early users complained that the old version burned the varnish off their tables). Basically the principle is to

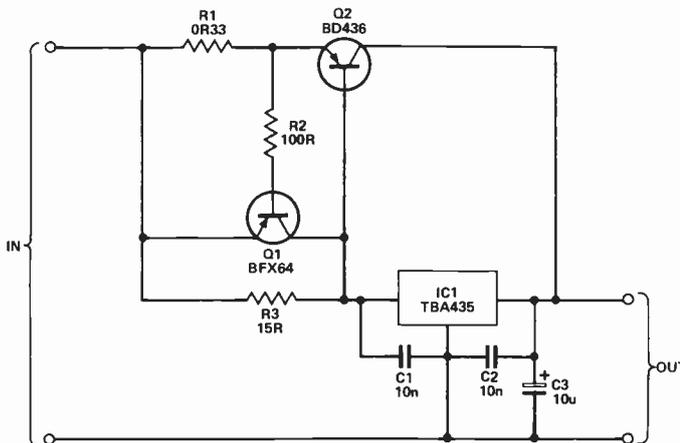


Fig. 9 Increasing the current-handling capability of an IC stabiliser. The stabiliser handles the rated current, and any amount beyond this value is handled by the auxiliary transistor circuit, preserving voltage stability.

dispense with a mains transformer, and rectify the mains voltage so as to produce a high voltage DC. By dispensing with the resistance of a mains transformer, and by using a reservoir capacitor of surprisingly modest capacitance (but rated for 500 V!), this supply voltage can be quite stable. It is then applied to a switching circuit which charges a capacitor several thousand times per second and discharges it just as frequently into the primary of a transformer which, because it operates with high-frequency signals, can be small and well-insulated. The outputs of this transformer are rectified, and need only small reservoir capacitances because of the high frequency that is used. There is no need for a stabiliser of the old-fashioned wasteful type either, because the output voltage can be sampled by a comparator, and the output of the comparator used to alter the switching times. The idea is that if the output voltage drops, the switch can spend more time passing current into the primary of the transformer; if the output voltage is too high, the switching circuits cut off earlier. There is no waste involved — what is not used is held in the reservoir capacitor ready for the next switching operation.

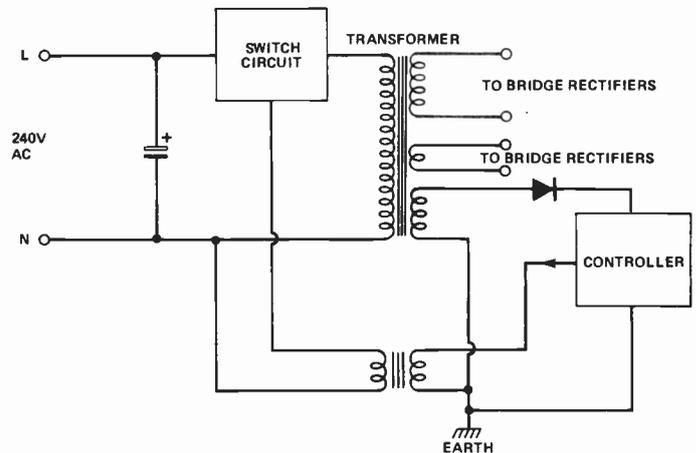


Fig. 10 An outline of a switched mode power supply. No values are shown, because the transformer is a critical component and the other circuitry can be obtained in IC form.

The main advantage is that the supply runs astonishingly cool, with no huge heatsinks needed for the regulator. The advantages for TVs and computers are obvious — I remember one computer which left scorch marks and which could have served as a sandwich toaster. Another advantage is that no AC voltage adjuster is needed — whatever the mains voltage happens to be will be compensated for by the switching process, and there are ICs which will take care of the whole operation. For a more detailed description of the operation of switched mode power supplies, see Designer's Notebook on page 63.

One point of caution concerns servicing. If you are working on a switch mode power supply, remember that it uses high voltages, and that part of the circuit is always live to the mains when it is operating. On many TV receivers, in accordance with the belief that a designer worth his salt will make the inside of a TV as dangerous as possible in order to kill off amateur mechanics, the whole chassis is live or at least not isolated from the mains. The growing trend to make TVs in monitor form so that they can be connected directly to video recorders instead of by the ridiculous method of re-modulating the signal may at last bring us electrically into line with the rest of the world in this respect.

Interak 1

HOME COMPUTERS DO NOT WORK!

You've already got a "home" computer — am I right? You may be anyone — a Hospital Electronics Workshop, a University Computer Dept., an Electronics Research Establishment, or you may be just plain Joe Soap.

Either way round — you're fed up with the boss, or your wife (may be the same thing), always asking you — "Very nice, but what does it do?" I know you can make it do things, so you must be pretty clever, but what a mess. What's that heap of junk plugged in the back — talk about spaghetti!

They look lovely, home computers, don't they — until you bolt on all the things round the back that the designer couldn't (or wouldn't) include.

I think we both know what is needed: A "rack and card" build it yourself system (Interak 1). Something like Acorn's and Tangerine's original plug in systems, before they went on to more profitable things, but you don't want it 6502-based — Interak 1 uses the Z80A. (Doesn't everybody who has any sense?).

If you use Interak 1, the Z80A CPU is on one card, the VDU Interface is on another, Dynamic RAM on another, and so on. Very tidy, and very modular because "any card fits in any slot". And that ugly expansion adaptor, and the special box of bits you've got sticking out of the back, can be neatly re-packaged and slid into the spare slots in Interak 1.

I've got no space to say more (this advert's cost a few hundred pounds already!), so send me a stamp (20p) and/or SAE, or neither, or phone if you prefer, and I'll send you the 38-page low-down.

David Parkins

P.S. Although this advert may sound a bit corny (we have to get your attention somehow) Interak 1 really is a serious, sensible system with thousands of cards sold, and in daily use. Cards, Manuals, all available separately inc. circuit diagrams.

Greenbank

Greenbank Electronics (Dept. T3E), 92 New Chester Road, New Ferry, Wirral, merseyside L62 5AG
Telephone: 051-645 3391

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

NEW MICROPROCESSORS & Microelectronics £6.50

Now you can learn all about microprocessors — their construction, design, and operation — using our programmed learning technique. Suitable for all ages, all levels of interest, this course has been designed for ease of understanding. It assumes no prior knowledge other than arithmetic; and at the end you will know what that piece of "black plastic" in your computer is actually doing.

Contents include: algorithm design, programmable logic, microcomputer architecture, a microprocessor family, semiconductor technology, number systems, arithmetic — integer and floating point, data representation and scaling, programming, microprocessor development system.

GSC SUPERKIT £19.90



Learn the wonders of digital electronics — without the problems of soldering.

This practical beginners' kit comes complete with instruction manual, components, and EXP300 bread-board to teach you all the basics of digital electronics. The only extra you need to buy is a 4½V battery.

This self-instruction course teaches gating, boolean logic, R-S and J-K flipflops, shift registers, ripple counters, and half-adders.

DIGITAL COMPUTER DESIGN £8.50

This up-to-date theory course covers the design of digital computers, both from their individual logic elements and from integrated circuits. You are first shown the way in which simple logic circuits operate and then, through a series of exercises, arrive at a design for a working machine.

Please send for our free booklet for further information on these and our other courses.

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 15 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND.
TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra — please ask for prepayment invoice). Giro A/c No 2789159. Please allow 28 days for delivery in UK.

- SUPERKIT(S) @ £19.90
- DIGITAL COMPUTER DESIGN(S) @ £8.50
- MICROPROCESSORS & MICROELECTRONICS @ £6.50

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club
Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446
Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....
Address.....

Cambridge Learning Limited, Unit 15 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs. PE17 4BR, England. (Registered in England No 1328762).

9" MONITOR in attractive case. With info £25 each. Carr £7. Matching Keyboard with Numeric Keypad. ASCII coded, £25 each. P&P £5. The Pair £40, Carr £7.
12" MONITOR cased, with info, £20 each, Carr £7. Together with matching Keyboard, £36. Carr £7.
POWER UNIT 240V Input. Outputs +5V/15A; +24V/1.5A; -24V/3A, £12 each. Carr £7.
INSTRUMENT CASE, standard 19" width x 16" depth x 10" high, £5 each, Carr, £7.

FOR MORE INFORMATION CONTACT DWAYNE STEWART

GEARED MOTOR 117/234 Volt Input 50HZ. 4" dia x 5 1/2" deep, 1" shaft. New £5 each P&P £4.
MOTOR 12V DC Input. 3" dia x 4 1/2" deep, 1" shaft. New £3.50 each P&P £3.
DC MOTOR 6-12 Volts. Mechanical Constant Speed Control 1 1/2" dia. £1 each.
MOTOR 12V DC with pulley & semi-conductor speed control. £1 each.
SYNCHRONOUS MOTOR 2 Phase 9 volt AC. 375 RPM. Good torque (needs 30-40 mfd capacitor. Suitable for Robotics/Plotters etc. £1 each.

OTHER SYNCHRONOUS/STEPPING MOTORS AVAILABLE. PLEASE ENQUIRE

GEARED MOTOR 12V 50HZ. 4 Watt 1 rpm, 2" dia x 1 1/2" deep. £1.50 each.
CENTAUR FANS 4 1/2". Brand new, 100V 20W, 2 speed. £2 each P&P £2.
CENTAUR FANS 4 1/2". 115V New, £4.50 each.
MUFFIN 115V 4 1/2", unused, £3 each P&P £2.
TRANSFORMERS — All brand new, all 240 volts input.
Sec 25.5V 2.5A. Size 3 1/2" x 2 1/2" x 2 1/2". £2.50 each.
Sec 115V 1A (auto) £1.25 each. Sec 6V 1.56A £1.50 each.
Sec 12V 100MA 50p each.
TRANSFORMER 127/220 Volt Input. Sec 12V 1A RMS £1.50 each
TRANSFORMER 120 Volt Input. Sec 10-0-10V 1A 75p each
Sub Min TRANSFORMER 0-120-240V Input. Sec 12-0-12V 4VA 75p each 10 off £6
TOROIDAL TRANSFORMER 0-115-230V Input. Sec 13.5-0-13.5V 8VA. £1.50 each 10 off £12.
TOROIDAL TRANSFORMER 0-120-240V Input. Sec 0-12V-0-12V 10VA per winding. Encapsulated. £4 each. 10 off £25.
Sub Min PULSE TRANSFORMER. Sec centre tapped. Suitable for Thyristor triggering 20p each. 10 off £1.80.
RAPID DISCHARGE CAPACITOR 8 mfd 4KV £5 each P&P £2.
HUNTS CAPACITOR 0.1 mfd 3KV DC. £1.25 each 10 off £10.
E.M.T. CAPACITOR 500pf 8KV. 20p each 10 off £1.80.

TELEPHONES. 706 style black, blue, green, grey, £5 each. 10 off £45.
Discoured £4 each. 10 off £30. 746 style black or grey £7.50 each. P&P £2 each. 4-10 units £7. Over 10 by arrangement.
TOKIN NOISE FILTER VG215FU. 250VAC 15A 50/60HZ. With fixing bracket. New £2 each.
VU METER. Scaled 0-5, size 1 1/2" x 7/8". 50p each 10 off £4.
I.T.T. LOUD SPEAKER. 3 1/2" dia. 50 ohm 0.2 Watt. New. 75p each. 10 off £6.50.
E.M.T. CABLE. Overall dia 5mm, 10p per metre. 100 metre drum £7.50 P&P £4.
Multi Colour RIBBON CABLE 10 way, 50p per metre, 10 metres £4, 14 way 75p per metre, 10 metres £5, 100 metres £40.
ILLUMINATED ROCKER SWITCH. 2 pole 250V 8 Amp, orange, 50p each. 10 off £4.
JOYSTICK SWITCH 4 directions, £3 each. P&P £2.
CATHODE RAY TUBES. Brand new, D14-121GM & D14-12GH £40 each, SE5/2A/P31 £25 each. Many others available, please enquire.
PCB KEYBOARD PAD. 19 push contacts. 0-9; A-F plus 3 optional, £1.50 each. 10 off £12.
KEYBOARD PAD. 19 Push Contacts. Switches, push to make. £1.50 each. Blank, size 3 x 2 1/2". 2" high, £4 each. 10 off £15. P&P £3.
EPROM 2716 Single rail. £1.50 each, 2564 £4 each.

SPECTRAL BALANCE TEN TURN POT. 100 ohm 1/2W. Brand new. 75p each 10 off £8.
SLIDER POTENTIOMETER. Twin Gang, 200K or 2M, 35p each. 10 off £3.
PANEL MOUNTING FUSE HOLDER for 1 1/2" fuse, 20p each. 10 off £1.50.
BELLING LEE CHASSIS MOUNTING FUSE HOLDER for 1 1/2" fuse, 15p each. 10 off £1.
I.E.C. MAINS LEAD. 2 metre length, heavy duty, 80p each. 10 off £5.
4 CORE CURLY WIRE extending to 2 metres, 20p each. 10 off £1.80.
MICROPHONE/EARPIECE INSERTS. Brand new, 75p each. 10 off £8.
PP9 BATTERY CONNECTOR STRIP, solder tag, 10p each. 10 off 80p.
CINCH CONNECTOR STRIP 12 way, 48A Screw connection on both sides, 35p each. 10 off £3.
INFRA RED QUARTZ LAMP 230V 620 Watts, size 131 x 1" dia. £1.50 each. 10 off £10.
FERRANTI PHOTOCELL type MS15, 50p each. 10 off £4.

Minimum Order of Goods £3. Minimum P&P £1.50. VAT at 15% MUST be added to TOTAL OF GOODS & PACKAGING.
Many more components and test equipment available. S.A.E. or telephone for lists.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
Tel: (0734 68041)

Callers welcome 9 am-5.30 pm Monday to Saturday inclusive

LB ELECTRONICS

DISC DRIVE BONANZA

PERTEC FD650 DSDD 8"£199 + VAT
 PERTEC FD200 5 1/4" SSDD ..£100 + VAT

The above drives are suitable for the BBC Micro, we can supply full documentation if requested with purchase of the drives only. Also available is a word processing package with is a tape to disc program (i.e. will not run without discdrives).

Offered with Full documentation at **£9.80 p&p 50p.**

BRAND NEW AND BOXED PLUS DATA P&P AT COST

Apple controller card for two drives£40.00 + VAT p&p 50p
 ASC11 coded qwerty Keyboard manufactured by Alphamenc (Woking UK). Model 60K brand new plus data£19.95 p&p £1.50
 SELLOUT used (Guaranteed replacement by us) 2716 (5v) 1.50 each p&p 30p. 12 for £15 p&p 75p.

25 WAY 'D' Types, plugs £1.85, sockets £1.85 (solder tail) p&p 30p.
 Telephone for bulk prices.
 CASE model 430 Data modem, no information£30 each p&p £3.50

(Manuals available £5.00 each)

INTERSCAN ACOUSTIC COUPLER
 10" x 4" x 5" WITH ELECTRONICS, SOUND
 TIGHT UNIT, FOR STANDARD GPO HAND SET.
 NO DATA — £10.00 (INC VAT) P&P £1.75

LB ELECTRONICS

11 HERCIES ROAD,
 HILLINGDON,
 MIDDLESEX UB10 9LS,
 ENGLAND

TEL: UXBRIDGE 55399




FOR HI-FI & ELECTRONIC ENTHUSIASTS!

We are the specialists of electronic kits. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverbification amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control (electronic touch switch, sound activated switch, light activated switch, infra-red remote control), music generators, battery fluorescent light and high quality black anodised amplifier cases . . . etc. with illustrative pictures now available at the cost of 60p including P + P, together with a 10% discount voucher for your first order.

EQUALIZER & REVERBERATION AMPLIFIER

Built £79.50 Kit £73.50

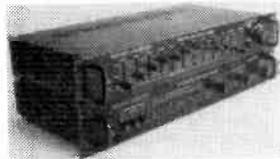


All prices include VAT

HI-FI AMPLIFIER MODULES



TA-323A 30W + 30W stereo amplifier £18.95 Kit £23.95 Ass.
 TA-280 60W + 60W stereo amplifier £27.50 Kit £32.50 Ass.
 TA-920 70W + 70W stereo amplifier £36.50 Kit £41.50 Ass.

CONTROL MODULES

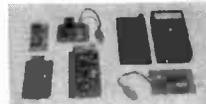

TY-7 Electronic touch switch £2.90 Kit £3.70 Ass.
 TY-11 Light activated switch £2.20 Kit £2.70 Ass.
 TY-18 Sound activated switch (Clap switch) £4.50 Kit £5.20 Ass.
 TY-38 Sound activated switch (voice switch) £5.50 Kit £6.50 Ass.
 TY-41 Infra-red remote control (Receiver and transmitter) £17.20 Kit £18.90 Ass.

PROFESSIONAL RACK MOUNTING CABINET



• Made wholly of black anodised aluminium sheets • Suitable for high quality amplifiers and many other purposes • Top, bottom and rear cover removable for access • Different sizes available • Compatible price • Front panel is of brushed aluminium finish

To: Concept Electronics Ltd., 51 Tollington Road, London N7 6PB

Mail orders only

Please send me the electronic kits catalogue & the 10% discount voucher for my first order. I enclose 60p in stamps/cheque/postal order. Make cheques payable to Concept Electronics Ltd.

Name

Address

.....Block caps please

VARIABLE VOLTAGE POWER SUPPLIES

1 - 30v 1.5A£38.75 0 - 30v 1.5A£39.99
 1 - 30v 3A£42.99 0 - 30v 3A£44.50
 1 - 30v 5A£45.75 0 - 30v 5A£47.80
 1 - 30v 10A£55.99 0 - 30v 10A£58.99

CONSTANT VOLTAGE/CONSTANT CURRENT SUPPLY

1 - 32V/100mA - 5A £55.90

HIGH EFFICIENCY SWITCHING POWER SUPPLY

2 - 32V 4A Max £52.99

ALL THE ABOVE SUPPLIES ARE FITTED WITH QUICK-FIT METERS. IF MORE ACCURATE METERING IS REQUIRED PLEASE ADD £3.00. FOR DIGITAL METERING ADD £15.

NICAD CONSTANT CURRENT CHARGER FOR ALL DOMESTIC BATTERIES £18.99

MULTIRAIL POWER SUPPLIES FOR

MICROS ETC.
 5v 5A, - 5v 1A, 12v 1A, - 12 1A, 24v 1A £34.50
 (5v HAS CROWBAR OVERVOLTAGE PROTECTION)

OTHER SUPPLIES FOR MICROS

5v 3A £25.99 5v 5A £28.99 5v 10A £35.99
 12v 1A £12.45 12v 3A £27.95

(ALL THE ABOVE HAVE CROWBAR OVER VOLTAGE PROTECTION)

1 - 15v 3A£27.99 1 - 15v 5A£34.99
 2 - 15v 3A£29.99 2 - 15v 5A£35.99
 SWITCHMODE P.S.U. 5v 5A£35.75

C.B. RADIO E.T.C. POWER SUPPLIES

12v/13.8v 3A £19.99 12v/13.8v 5A £25.99
 12v/13.8v 10A £34.99

(ALL WITH CROWBAR OVERVOLTAGE PROTECTION)

S.A.E. FOR LISTS

ALL POWER SUPPLIES ARE FULLY STABILISED AND OVERLOAD PROTECTED. ALL PRICES ARE INCLUSIVE AND INCLUDE CARRIAGE

EDWARDS ELECTRIC

UNIT 3, MILL LANE, CHURCH STREET, BRIDGWATER, SOMERSET TA6 5AT

MULTIMETERS

(UK C/P 65p)

RANGE DOUBLER 10A DC1

Special price.....£15.95

ETC 5000/5001 121 Ranges

50K/V Range Doubler 10A DC

.....£16.50

TMK 500 23 Ranges 30K/V 12A

DC Plus cont. buzzer.....£23.95

NH56R 20K/V 22 Range Pocket

.....£10.95

360TR 23 Range 100K/V. Large

scale 10A AC/DC plus Hfe.....£36.95

ATI 020 18 Range 20K/V. DeLux

plus Hfe Tester.....£17.50

ST303TR 21 Range 20K/V plus Hfe

Tester.....£16.95

SPEAKERS

(Hi-Fi, P.A., Disco, Bass Guitar)

12" 50W£14.95

12" 100W£19.95

15" 100W£29.95

18" 100W£39.95

Postage and Packaging £3

RETAIL • MAIL ORDER

EXPORT • INDUSTRIAL

EDUCATIONAL

FREE CATALOGUE

SEND LARGE

SAE

(UK 20p)

Order by Post with cheques, Access/Visa or you can telephone your orders.

ALL PRICES INCLUDE VAT

INCLUDE VAT

ORDER SEND LARGE SAE (UK 20p)

MUSICRAFT 303 EDGWARE RD, LONDON W.2. TEL: 01-402 9729/2898


LOW COST PROFESSIONAL TEST INSTRUMENTS



Belemic

Hand Held Analogue and Digital Multimeters

16 Models from £18.75

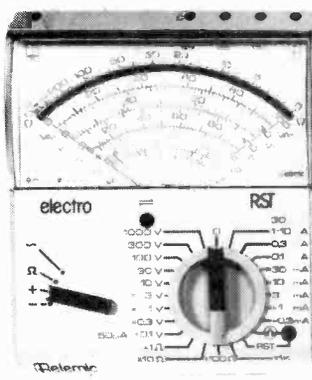

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

Black Star Ltd.
 9A, Crown Street
 St. Ives, Huntingdon
 Cambs. PE17 4EB
 Tel: (0480) 62440 Telex 32339



★★ SATURDAY BARGAINS ★★

EMOS SATURDAY SALES

Starting February 12th we will be open from 10am to 4pm every Saturday to sell our vast range of components at bargain prices. You will easily find us in Daventry on the A45, opposite the John O'Gaunt Hotel.

LARGE ELECTROLYTICS:		VOLTAGE REGULATORS	
Computer Grade.		+5V	1A TO220 40p
Made by Sanyo or General Electric		+5V	1.5A TO3 140p
Ideal for power supplies		5V	1A TO330 40p
Following values available:		5V	1.5A TO3 190p
185,000 @ 15V		+6V	0.5A TO220 35p
300,000 @ 7V		+12V	0.5A TO220 35p
120,000 @ 15V		+12V	1.5A TO3 140p
100,000 @ 30V		12V	1A TO220 40p
71,000 @ 40V	Postage and packing	12V	1.5A TO3 190p
80,000 @ 40V	1 or 2 capacitors - £1.00	+15V	1A TO220 40p
5,000 @ 50V	3 or more - £1.50	15V	1A TO220 40p
		24V	1A TO220 70p
Prices fantastic value at only £2.50 each.			

P.S.U. COMPONENTS	2N4347 (120V)	150p	723	30p
	2N6258 (250W)	180p	2N3055	35p
	400mW Zeners	5p		

Special Offer

TMS2516JL 8 x 2K EPROM	£14.90	BENCH POWER SUPPLY	
TMS4030JL 4K RAM	£3.00		
8255 P.I.A.	£1.90	See constructional article in February '82	
2N3055	£0.35	"Practical Electronics"	
Panel mounting 20mm fuseholders	20p	Available in kit form or built up	
Continental relays 2p c/o 24V or 48V	50p	Prices (inc VAT p + p):	
Heavy duty relays - 5A - 2p c/o 24V	85p	Kit	Built
Microswitch - V type - push on terminals	25p	£44.00	£72.00

CMOS - 74 - 74 LS TTL

See our adverts in last months magazines for complete lists

Very competitive prices Many devices only 9p

Dept 4D, High March, Daventry, Northants NN11 4HQ
Tel: 03272 5523 Telex: 311245 GRENEL G

Please add 50p per order postage and packing (except where higher is indicated) plus 15% VAT on total. No VAT on overseas orders, postage at cost. Cheques and postal orders made payable to Emos Limited. Send Large S.A.E. for comprehensive catalogue.

EMOS

CAMBRIDGESHIRE COLLEGE OF ARTS AND TECHNOLOGY

ARE YOU MAKING THE MOST OF YOURSELF?

HAVE YOU CONSIDERED FURTHERING YOUR TRAINING IN ELECTRONICS?

We offer:
CNA A BSc in Electronic Engineering
A four year part-time degree for mature students, includes study of Digital, Telecommunications and Control systems.
Entry qualifications: HNC or equivalent in Electrical and Electronic Engineering or Applied Physics. This degree is considered by the Council of Engineering Institutions as meeting their C.Eng. academic requirements.

HND in Electrical and Electronic Engineering
A 2½ year sandwich course, including study of Electrical, Electronic and Communication Engineering, combined with control Engineering and Digital Techniques. Entry qualifications: 1 'A' level in Mathematics or Physics.

For further details and application forms, contact The Department of Engineering, Cambridgeshire College of Arts and Technology, Cambridge CB1 2AJ. Telephone (0223) 63271.

MASTER ELECTRONICS NOW!

The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

ETI/4/821

NAME _____

COURSE IN ELECTRONICS as described above

ADDRESS _____

RADIO AMATEUR LICENCE

OTHER SUBJECTS _____

MICROPROCESSORS




LOGIC COURSE


POST NOW TO:

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 1BR

PCB FOIL PATTERNS

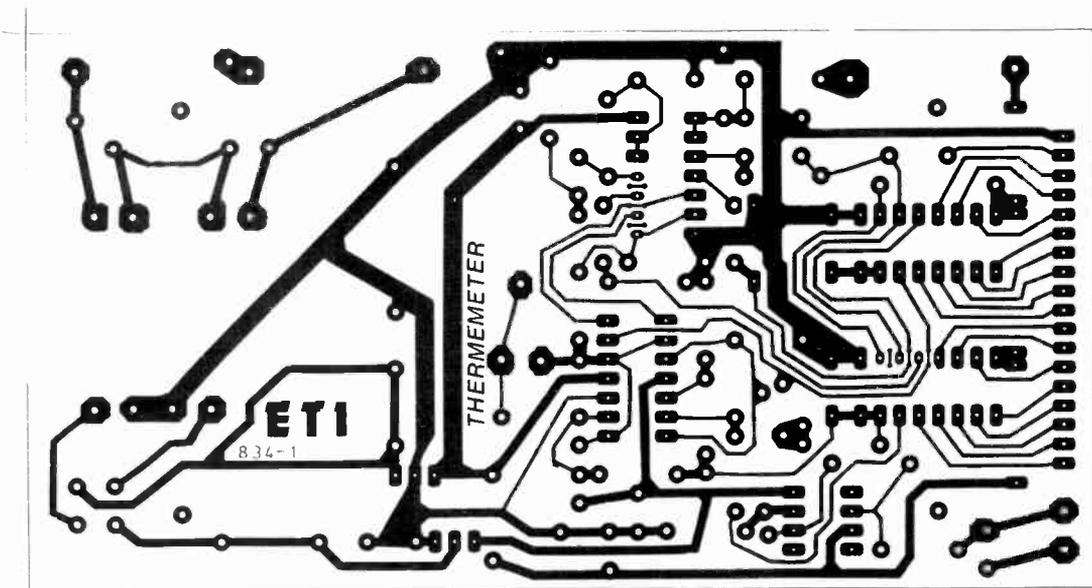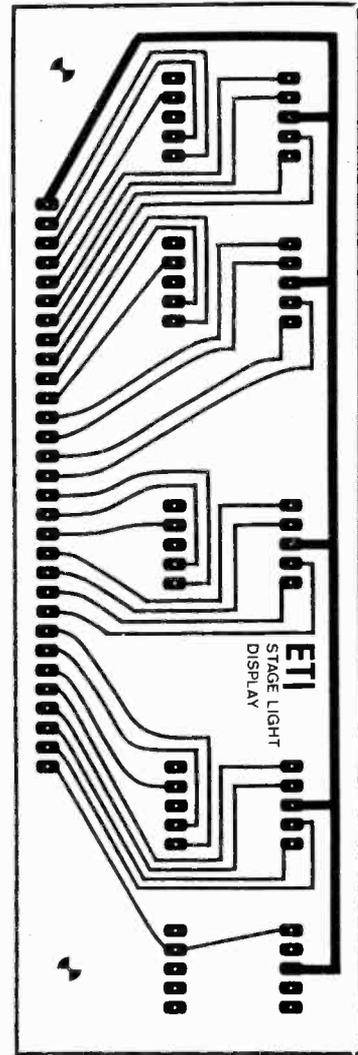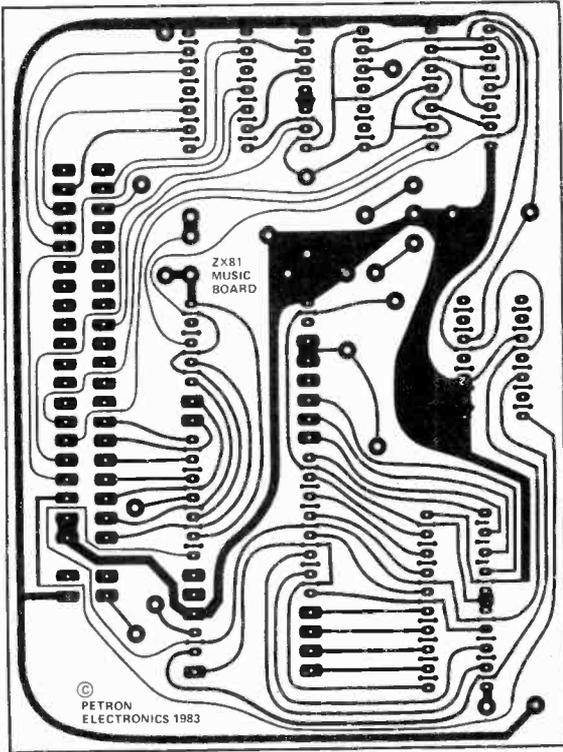

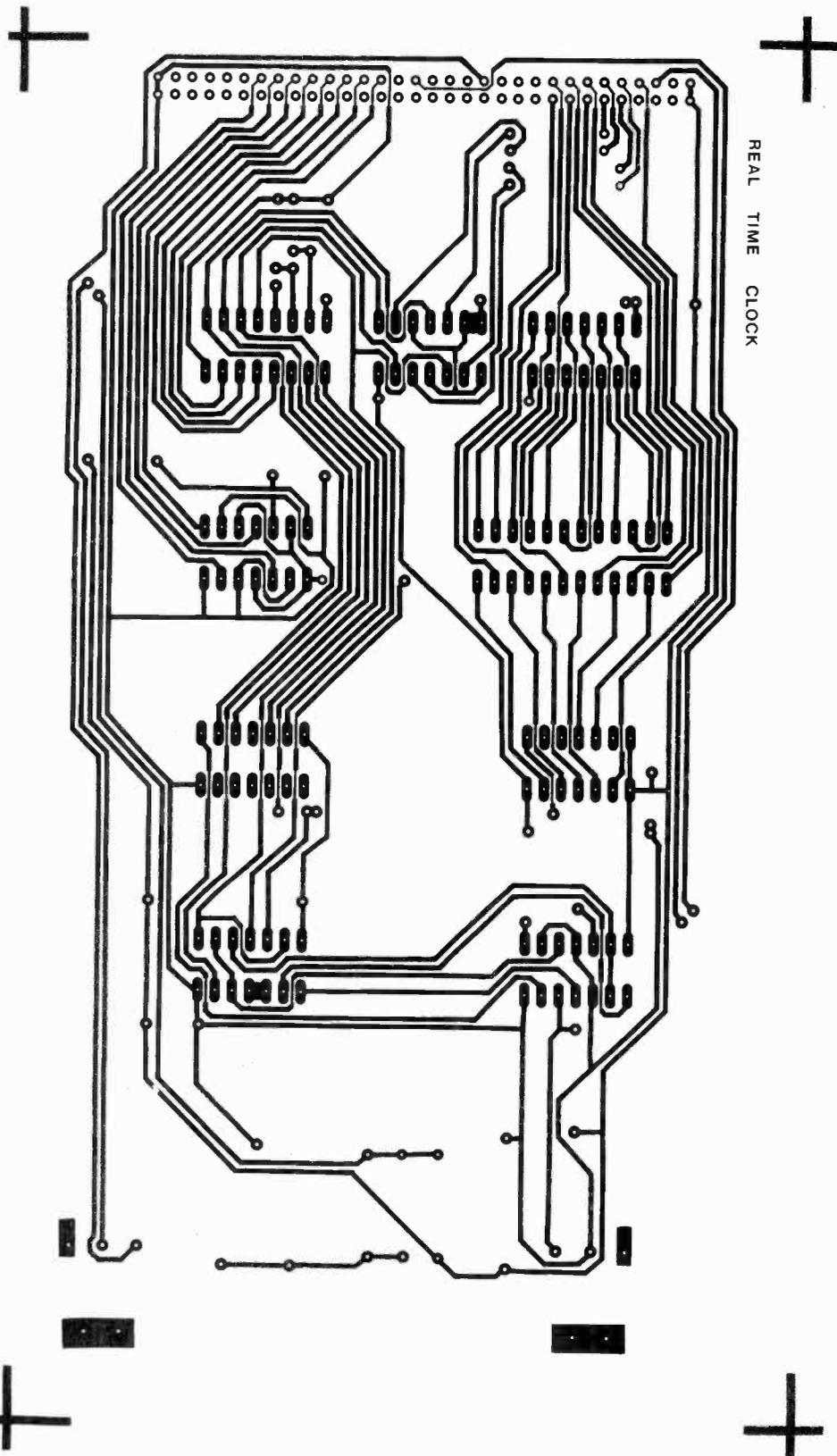

The foil patterns for the Stage Lighting memory board are too large to be printed: an SAE to us will secure a copy.

TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO IN YOUR OWN HOME - AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates

**Radio Amateurs
Basic Electronic Engineering (Joint C&G/ICS)**

Certificate Courses

**TV and Audio Servicing
Radio & Amplifier Construction
Electronic Engineering* and Maintenance
Computer Engineering* and Programming
Microprocessor Engineering*
TV, Radio and Audio Engineering
Electrical Engineering,* Installation
and Contracting** *Quality for IET Associate Membership



Approved by CACC



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest _____

Name _____

Address _____



Post to: Dept F265
ICS School of Electronics
160 Stewarts Road,
London SW8 4UJ



01-622 9911
(All Hours)

PARNDON ELECTRONICS LTD.

Dept. No.23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700


RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Bandiered and colour coded.
£1.00 per hundred mixed (Min 10 per value)
£8.50 per thousand mixed (Min 50 per value)
Special stock pack 60 values 10 off each **£5.50**

DIODES: IN4148 3p each Min order quantity - 15 items
£1.60 per hundred

**CAPACITORS, REGULATORS, SWITCHES, I.C.
TRANSISTORS, DIODES, etc., etc.**
FULL LIST AVAILABLE - SEND S.A.E.

DIL SOCKETS: High quality low profile sockets
8 pin - **10p.** 14 pin - **11p.** 16 pin - **12p.** 18 pin - **19p.** 20 pin - **21p.**
22 pin - **23p.** 24 pin - **25p.** 28 pin - **27p.** 40 pin - **42p.**

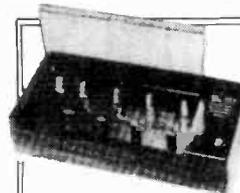ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE



Universal NI-CAD, battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.
Charges:- PP3 (9V), U12 (1.5V penlite), U11 (1.5V "C"), U2 (1.5V "D"), Power:- 220-240V AC. Dims:- 210 x 100 x 50mm. Knock down price only while stocks last.

Only **£6.00**
Order No. MW 398

Multitester & Transistor Tester

DC volts 0-1v-5v-2.5v-10v-50v-250v-1000v $\pm 3\%$
AC volts 0-10v-50v-250v-1000v $\pm 3\%$
DC current 0-50uA-2.5mA-25mA-0.25A $\pm 3\%$
Resistance:
Minimum 0-2-2-200-200k ohms
Midscale 20-200-20k-200k ohms
Maximum 2k-20k-2m-20m ohms
As a transistor tester
Leakage current 0-150uA at Z1k range
0-15mA at X10 range
0-150mA at X1 range

Only **£11.95**
Order No. HT 320



PLEASE ADD 15% VAT & £1 P&P



**ENFIELD
ELECTRONICS**

208 BAKER ST., ENFIELD,
MIDD. Tel: 01-366 1873



Visual Display Units
Burrhoughs MT686 VDUs
These versatile micro controlled programmable terminals have 3 RCA 1802 CPUs and 64K of memory. 12" Green screen (80 x 25) RS232. 106 key detached keyboard. Can also be used as quality video monitor. **£149 + £15 carr. WHILE STOCKS LAST.**

CENTRONICS 306 LINE PRINTERS



professional fast compact line-printer. 80 columns, 120 char/sec. Parallel i/f. Quality at a silly price. Vertical format unit. To inc. operations manual. **ONLY £149.00.** Carriage (England) **£17.50.** Tech manual (230 pages) **£10.00.**



FLOPPY DISC DRIVES

Fantastic MEMOREX 550 B" discs mounted in attractive case with power supply and fan. Shugart standard 50 way interface. Space for second drive. **£199 (carr. £9.50).**

MAWSON ASSOCIATES

124 Lennard Rd, Beckenham, Kent BR3 1QP

WE ALSO BUY COMPUTERS
AND COMPUTER PERIPHERALS

01-778 3600

Callers welcome by appointment
s/h items sold working but not g/ tested

TALK TO THE WHOLE WORLD

... and discover a new one for yourself. If you're experienced or even a beginner our skilled preparation will enable you to obtain a G.P.O. Licence.



British National Radio & Electronics School, Reading, Berks. RG1 1BR

FREE brochure without obligation from:-

British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name

Address

ET1/4/817

BLOCK CAPS PLEASE

NEW SURPLUS RELEASE

VERSATILE BENCH POWER SUPPLY UNITS Contains high quality transformer to exacting specifications giving one 20v output and two 30v outputs. All outputs 3 amps D.C. Input 110/250V 50c/s. Bridge rectification. Contained on metal chassis with robust compact case size 7" x 5 1/2" x 4 1/2" easily modified to give 50v and 80v outputs. Makes an ideal variable power supply. Normally cost around £60. **OUR PRICE AS NEW WITH CIRCUIT £8.50.** Carr. £3.00. 2 units for £20 carr. free.

FOOT SWITCH (Mains operation). Contains two micro switches and lead metal case. Good condition. **£3.50** each. Postage 50p. 2 for **£7.50** Post Free.

LIGHTWEIGHT HEADSETS (Govt. release). Brand new 600 ohms impedance. A Bargain at **£3.50** pp £1. Two for **£7.**

SCOOP PURCHASE PYE POCKET PHONE RECEIVERS Type PF1 normal freq. 450mHz. Supplied in used condition less battery. **£4.50** each. Carr. **£1.2** for **£9** post free. 4 for **£16** post free.

New release of MODERN DYNAMIC MOVING COIL MICROPHONES. 200 ohms impedance. Switch incorporated. Mostly with lead and DIN plug. Used but nice condition. Three designs of case housing. Price one mike our choice **£2** plus 50p pp. Bargain offer all three mikes **£4.50** pp £1.

HAVE YOU SEEN THE GREAT CAT? 1000's of new components, radio, electronic, audio at unbelievably low prices. Send 50p and receive catalogue and **FREE RECORD SPEED INDICATOR.**

Try a **JUMBO PACK.** Contains transistors, resistors, caps, pots, switches, radio and electronic devices. Over £50 worth for **£11** Carriage and packing **£2.50.** **MINI JUMBO PACK** (£20 worth) for **£5** pp **£1.50.**

PLEASE ADD 15% on all orders including carriage and pp.

Myers Electronic Devices

Dept. ET1, 12/14 Harper Street, Leeds LS2 7EA. Tel: 452045


New retail premises at above address (opposite Corals). Callers welcome 9 to 5 Mon to Sat. (Sunday 10 till by appointment). Govt. Surplus items always in stock.

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Brook House, Torrington Place, London WC1E 7HN

ETI PCB SERVICE

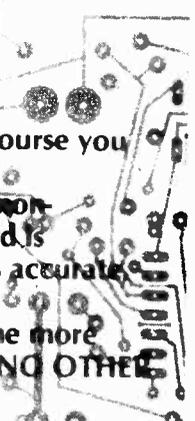

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

APRIL 79		JULY 80		<input type="checkbox"/> Ion 'Blinker' £2.47	
<input type="checkbox"/> Guitar Effects Unit	£2.64	<input type="checkbox"/> System A A-MMA-MC	£2.65	<input type="checkbox"/> MOSFET Amp Module	£6.78
<input type="checkbox"/> Click Eliminator	£6.64	<input type="checkbox"/> System A A-PR	£5.17	<input type="checkbox"/> Logic Lock	£3.06
JUNE 79		<input type="checkbox"/> Smart Battery Charger	£1.97	<input type="checkbox"/> Digital PWM	£3.34
<input type="checkbox"/> Accentuated Beat Metronome	£3.60	AUGUST 81		<input type="checkbox"/> Optical Sensor	£1.74
FEBRUARY 80		<input type="checkbox"/> System A Power Amp(A-PA)	£4.77	<input type="checkbox"/> Stylus Timer	£2.59
<input type="checkbox"/> Tuning Fork	£2.64	<input type="checkbox"/> Flash Sequencer	£3.44	<input type="checkbox"/> Oscilloscope (four boards)	£11.60
MARCH 80		<input type="checkbox"/> Hand-clap Synthesiser	£3.97	JULY 82	
<input type="checkbox"/> Signal Tracer	£2.27	<input type="checkbox"/> Heartbeat Monitor	£1.83	<input type="checkbox"/> Mike Switching Unit	£1.87
AUGUST 80		<input type="checkbox"/> Watchdog Home Security (two boards)	£5.31	<input type="checkbox"/> TV Bargraph (main board)	£4.56
<input type="checkbox"/> CMOS Logic Tester	£2.64	SEPTEMBER 81		<input type="checkbox"/> TV Bargraph (channel card)	£2.28
<input type="checkbox"/> Capacitance Meter	£2.93	<input type="checkbox"/> Mains Audio Link (three boards)	£7.35	<input type="checkbox"/> Hotwire	£2.63
<input type="checkbox"/> Ultrasonic Burglar Alarm	£2.87	<input type="checkbox"/> Laboratory PSU	£4.53	<input type="checkbox"/> Bridging Adaptor	£2.38
OCTOBER 80		OCTOBER 81		AUGUST 82	
<input type="checkbox"/> Cassette Interface	£2.93	<input type="checkbox"/> Enlarger Timer	£3.40	<input type="checkbox"/> Playmate (three boards)	£7.20
<input type="checkbox"/> Fuzz/Sustain Box	£3.27	<input type="checkbox"/> Sound Bender	£2.65	<input type="checkbox"/> Kitchen Scales	£1.84
NOVEMBER 80		<input type="checkbox"/> Thermal Alarm	£2.63	<input type="checkbox"/> Sound Track	£4.25
<input type="checkbox"/> Touch Buzzer	£1.93	<input type="checkbox"/> Micropower Pendulum	£2.21	SEPTEMBER 82	
<input type="checkbox"/> Light Switch	£1.93	NOVEMBER 81		<input type="checkbox"/> Auto Volume Control	£1.84
<input type="checkbox"/> Metronome	£1.93	<input type="checkbox"/> Voice-Over Unit	£3.97	<input type="checkbox"/> Dual Logic Probe	£1.93
<input type="checkbox"/> 2W Power Amp	£1.93	<input type="checkbox"/> Car Alarm	£2.81	OCTOBER 82	
<input type="checkbox"/> RIAA Preamplifier	£1.93	<input type="checkbox"/> Phone Bell Shifter	£2.96	<input type="checkbox"/> Message Panel (one card)	£8.79
<input type="checkbox"/> Audio Test Oscillator	£3.13	DECEMBER 81		NOVEMBER 82	
DECEMBER 80		<input type="checkbox"/> Alcometer (two boards)	£5.21	<input type="checkbox"/> Spectrum Analyst (3 boards)	£14.33
<input type="checkbox"/> Musical Doorbell	£2.80	<input type="checkbox"/> Bodywork Checker	£1.75	<input type="checkbox"/> Pulse generator	£5.29
<input type="checkbox"/> Bench Amplifier	£2.53	<input type="checkbox"/> Component Tester	£1.40	<input type="checkbox"/> Message panel interface	£1.91
<input type="checkbox"/> Four Input Mixer	£2.64	JANUARY 82		DECEMBER 82	
JANUARY 81		<input type="checkbox"/> Parking Meter Timer	£2.20	<input type="checkbox"/> ELCB	£2.41
<input type="checkbox"/> LED Tacho	£4.13	<input type="checkbox"/> Infant Guard	£1.56	<input type="checkbox"/> Servo Interface (two boards)	£5.87
<input type="checkbox"/> Multi-Option Siren	£3.20	<input type="checkbox"/> Guitar Tuner (two boards)	£5.55	<input type="checkbox"/> Spectracolumn	£4.82
<input type="checkbox"/> Universal Timer	£3.31	FEBRUARY 82		<input type="checkbox"/> Signal Line Tester	£1.25
FEBRUARY 81		<input type="checkbox"/> Ripple Monitor	£1.92	JANUARY 83	
<input type="checkbox"/> Infra-red Alarm (four boards)	£6.64	<input type="checkbox"/> Pest Monitor	£1.68	<input type="checkbox"/> ETI/831/1 Fuel Gauge	£3.00
<input type="checkbox"/> Pulse Generator	£3.57	<input type="checkbox"/> I Ching Computer (two boards)	£5.15	<input type="checkbox"/> ETI/831/2 ZX ADC	£2.25
MARCH 81		<input type="checkbox"/> Moving-magnet stage	£3.49	<input type="checkbox"/> ETI/831/3 Programmable PSU	£3.00
<input type="checkbox"/> Engineer's Stethoscope	£2.65	<input type="checkbox"/> Moving-coil stage	£3.49	MARCH 83	
APRIL 81		<input type="checkbox"/> DV Meg	£2.72	<input type="checkbox"/> ETI/833/1 6502 Sound/DAC	£11.16
<input type="checkbox"/> Musical Box	£2.64	<input type="checkbox"/> Analogue PWM	£3.06	<input type="checkbox"/> ETI/833/2 Alarm Module	£3.15
<input type="checkbox"/> Drum Machine (two boards)	£5.60	<input type="checkbox"/> Slot Car Controller	£4.51	<input type="checkbox"/> ETI/833/3 ZX81 Graphics	£0.93
<input type="checkbox"/> Guitar Note Expander	£3.20	<input type="checkbox"/> Wattmiser	£4.17	<input type="checkbox"/> ETI/833/4 Logic Probe	£2.17
JUNE 81		<input type="checkbox"/> Sound Effects Board	£2.25	APRIL 83	
<input type="checkbox"/> Mini-drill Speed Controller	£2.93	June 82		<input type="checkbox"/> Thermemeter (main board)	£3.99
<input type="checkbox"/> Antenna Extender	£3.20	<input type="checkbox"/> Ion Generator (two boards)	£5.53	<input type="checkbox"/> Thermemeter (sensor)	£0.72
<input type="checkbox"/> LED Jewellery: Cross	£1.47			<input type="checkbox"/> Stage Lighting (memory)	£11.97
<input type="checkbox"/> Spiral (two boards)	£2.64			<input type="checkbox"/> Stage Lighting (display board)	£2.96
<input type="checkbox"/> Star (two boards)	£2.65				
<input type="checkbox"/> Waa-phase	£1.53				

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards	£	PLEASE ALLOW 28 DAYS FOR DELIVERY
Add 45p p & p	0.45	
Total enclosed	£	

Signed

Name

Address

ELECTROMART

LOOKING FOR
COMPONENTS! HARDWARE!
CASES! TRY YOUR LOCAL
LISTED STOCKIST

AVON

ANNLEY ELECTRO

190 Bedminster Down Road
Bedminster Down, Bristol
Tel: 0272 632622
Open: Mon-Sat 9am-6.30 pm Wed 9am-2pm

BEDFORDSHIRE

BROADWAY ELECTRONICS

1 The Broadway, Bedford,
Tel: 0234 213639
Open: 6 days 9-5.30 ½ day Thur.
lunch 1.30-2.30
Specialists in electronic components and
Acorn computers.

DORSET

D.J. ELECTRONICS
64 Ensbury Park Road,
Bournemouth.
Tel: (0202) 515073.
Open: Mon-Sat 9am-6pm.

LANCASHIRE

ETESON ELECTRONICS
15B Lower Green,
E.E. Poulton-le-Fyde, Blackpool
Tel: (0253) 885107
Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.
Electronic Component Specialists.

MERSEYSIDE

MYCA ELECTRONICS

2 VICTORIA PL, SEACOMBE FERRY,
WALLASEY, L44 6NR.
Tel: 051 638 8847
Open Mon-Sat 10am-5.30pm
Mail Order price list 50p refundable

PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982
47 Whitechapel, Tel 051 236 5489
Liverpool 2
THE ELECTRONICS SPECIALISTS
Open: Tues-Sat 9.30-5.30

W. MIDLANDS

WAVEBANDS

103 Coventry St., Kidderminster
Components, computers, car radios,
C.B.'s, amateur radio
and all electronic hobby equipment
Open: Mon-Sat 9-6, Sun 10-2
TEL: 0562 2179

H. G. ELECTRONICS CO

1350 Stratford Rd., Hall Green
Birmingham. Tel: 021-777 2369
Open: Mon-Sat 9-5.30 (Closed Weds)
Electrical accessories, plugs, skts, leads,
Electronic components, computers, audio,
video, tape, disco, hi-fi . . .

NORTHAMPTONSHIRE

* A new company selling electronic components.
* Mail order and walk-round supermarket.
* Vast stocks and very competitive prices.
EMOS High March, Daventry. NN11 4NQ.
Telephone 03272 5523. Telex 311245.
(Off A45 opposite John O'Garra.)

FOR YOUR BUSINESS TO
BE INCLUDED, CALL
ELECTROMART ON
01-437-1002.

STAFFORDSHIRE

TP ELECTRONIC SUPPLIES 105 High St.,
Wolstanton, Newcastle
Tel: 0782 636904
Open: Mon-Wed 9-6, Thurs 9-12 & 5-7,
Fri & Sat 9-9, Sun 11-2

S. WALES

**STEVE'S ELECTRONIC
SUPPLY CO. LTD.**
45 Castle Arcade, Cardiff
TEL: 0222 41905
Open: Mon-Sat 9-5.30
For components to computers

WARWICKSHIRE

**HORIZON
ELECTRONICS**
Charlotte St, Rugby. Tel: Rugby 78138
Open 5 Days 10-6 (closed Wed)
Wide range of components and R.S. stockists
1983 Mail Order Catalogue 75p

YORKSHIRE

ACE MAILTRONIX LTD.
3A Commercial Street,
Batley. Tel: (0924) 441129
Open: Mon-Fri 9am-5.30pm. (Sat 1pm)
Retail and wholesale.

Please include my business details in the next available issue of **ELECTRONICS TODAY**
INTERNATIONAL:

BUSINESS NAME:

ADDRESS:

TEL. NO.:

OPENING HOURS:

RETAIL WHOLESALE MAIL ORDER (Please tick)

CONTACT: (FOR OFFICE USE ONLY)



BARCLAYCARD
VISA

CLASSIFIED

THE PATH TO
SUCCESSFUL SALES!

01-437 1002
Ext 213

ADVERTISEMENT RATES

Semi-Display (min 2 cms)

1-3 insertions £10.00 per cm

4-11 insertions £9.00 per cm

12+ insertions £8.00 per cm

Lineage 35p per word (min 15 words)

Box Nos. £2.50

Closing date 1st Friday in the month
preceding publication date.

All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and
conditions printed on the advertisement rate card (available
on request)

Send your requirements and cheque / P.O. to:

E.T.I. CLASSIFIED ADVERTISING,
145 CHARING CROSS RD, LONDON
WC2H 0EE

DIGITAL WATCH REPLACEMENT parts
batteries, displays, backlights etc. Also
reports publications, charts. S.a.e. for full list
Profords Conersdrive, Holmergreen, Bucks,
HP15 6SGD

BURGLAR Alarm Equipment. Please
visit our 2,000 sq.ft showrooms or write
or phone for your free catalogue.
C.W.A.S. Ltd, 100 Rooley Avenue, Brad-
ford BD6 1DB. Telephone 0274 308920.

A1

051-228 3483
INTRUDER ALARMS LTD
WHOLESALE SUPPLIES
MAIL ORDER DEPT

Bell Boxes.....	£8.00	CONTROL PANELS	
Dummy Boxes.....	£4.50	Battery T/E/E.....	£20.00
Bell 6".....	£7.50	F.S.N. 20/40.....	£36.00
SIRENS		CONTACTS	
Minimite.....	£4.50	Aluminium.....	£1.85
Electronic.....	£7.50	Surface.....	£0.75
Cable (4 core).....	£7.00	Flush.....	£0.65
PRESSURE MATS		Quickfits.....	£0.75
Stair.....	£8.95	BEAMS	
Standard.....	£1.50	Infra Red.....	£31.50
		Ultrasonic comp.....	£36.00
		Rec Battery.....	£8.95

Discount on quantity — Please add 16%
VAT

FOR ORDERS LESS THAN £30 P&P £2.00
OVER £30 P&P FREE

A1 ALARMS LTD

86 Derby Lane, Old Swan, Liverpool 13

AERIAL AMPLIFIERS Improve weak
television reception. Price £6.70, S.A.E.
for leaflets. Electronic Mailorder,
Ramsbottom, Lancashire BL0 9AGH.

PRINTED CIRCUITS. Make your own sim-
ply, cheaply and quickly! Golden Fotolac
light-sensitive lacquer — now greatly im-
proved and very much faster. Aerosol
cans with full instructions, £2.25. De-
veloper 35p. Ferric Chloride 55p. Clear
acetate sheet for master 14p. Copper-clad
fibreglass board, approx. 1mm thick
£1.75 sq. ft. Post/packing 75p. White
House Electronics, Castle Drive, Praa
Sands, Penzance, Cornwall.

BUMPER BOX OF BITS

WOW!!! We've got so many components in stock, we can't
possibly list them all! — So buy a box, in it you'll find resistors,
capacitors, displays, switches, panels with transistors, diodes, IC's
etc, coils, pots... and so on. All modern parts — guaranteed at
least 1000 items, minimum weight 10lbs. ONLY £8.50 inc.


ELECTRONICS WORLD

1e Dews Road, Salisbury, Wilts SP2 7SN

CONVERT ANY TV into Large Screen
Oscilloscope (by external unit). Costs
approx. £12 to build. Circuit and plans £3 or
SAE details. J. Bobker, 29 Chadderton
Drive, Unsworth, Bury, Lancs.

COPPER CLAD Double Sided Fibreglass,
12" x 8". 10 sheets £6. 5 sheets £4. Davron,
Box No. E.T.I.202, Asp Ltd., 145 Charing
Cross Road, London WC2.

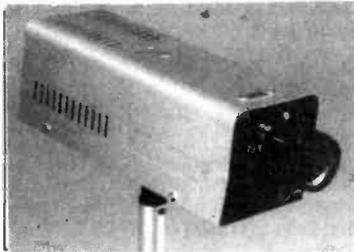HIGH POWER MERCURY ION LASER.
emits green/red light. Easily built by the
amateur constructor. Ideal school project,
etc. Comprehensive kit of plans, including
source of all materials, £5.25 + 25p P&P.
Lastertech, 31 Milll Brow, Chadderton,
Lancs.



A really compact high
performance CCTV camera
for only £130.00 plus VAT
plus P/P, Total £152.95.
Size 3"x3"x9" 240v operation.
1v p-p output. Lens extra.

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM,
MIDDLESEX TW1 4AO
Telephone 01 891 1923/01 891 1513
Telex 295093 CROFTN G

CENTURION ALARMS

We manufacture, you save £££'s
Send s.a.e. or phone for our Free list of
professional D.I.Y. Burglar Alarm Equip-
ment and accessories.
Discount up to 20% off list prices,
e.g. Control Equipment from £15.98,
Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME
0484-21000
or 0484 35527 (24 hr. ans.)
CENTURION ALARMS(ETI)
1265 Wakefield Road, Huddersfield
HD5 9BE, W. Yorkshire
Access & Visa
Orders Welcomed

GOVERNMENT SURPLUS components
and equipment, send s.a.e. for list: AFR Elec-
tronics, School Lane, Moulton,
Northampton.

WANTED: ELECTRONIC COMPONENTS
and Test Equipment. Factories cleared. Good
prices given. Q Services, 29 Lawford
Crescent, Yateley, Camberley, Surrey. 0252
871048.

SPECTRUM GAMES SALE. Venture (7
games in 1), was £6. 3 compulsive games,
was £5. The lot on one cassette for just £6.
Bobker, 29 Chadderton Drive, Unsworth,
Bury, Lancs.

SLIDE TAPE SYNCHRONISER

Synchronise slides with music and/or commentary with our PLL
slide tape synchroniser kit. Any cassette/tape recorder or deck can
be used together with any projector with remote control or
synchroniser socket.

Units can be ganged together for multi-projector use and could be
used in any project that requires tone generation/detection
remote control devices, tape based programmable controller/
sequencer etc. etc.) — full details supplied.

Basic kit £12.95 (includes PCB, relay, electronic components and
detailed instructions).
Complete kit £19.95 (as basic kit plus case and all switches, leads,
plugs and connectors required). All prices include p&p.

UNITECH (Midlands)

Dept ET3 FREEPOST, Sutton Coldfield, West Midlands B74 2BR
(no stamp required)

CIRCUIT DESIGN, Prototype construction,
analogue or Digital, Single Circuits or
Complete Instruments/Systems. Write A. J.
ATTWOOD, C.Eng., MIERE, Heathercote,
Heatherton Park, Taunton, Somerset, TA4
1ET, or Phone Bradford-on-Tone (082-346)
536.

£6.50 Post 65p MINI-MULTI TESTER
Deluxe pocket size precision moving coil instrument. Impedance + Capacity = 4000 ohms. Battery included. 11 instant ranges measure: DC volts 5, 25, 250, 500, AC volts 10, 50, 500, 1000, DC amps 0.25µA; 0.250mA. Continuity and resistance 0 to 600K ohms.

De-Luxe Range Doubler Model, 50,000
o.p.v. £18.50. 7 x 5 x 2in. Post £1.

NEW PANEL METERS £4.50
50µA, 100µA, 500µA, 1mA, 5mA, 50mA, 100mA, 25 volt, VU Meter, 500mA, 1 amp, 2 amp. Facia 2 1/2 x 2 x 1 1/2in. Post 65p.

FAMOUS LOUDSPEAKERS Post £2 each

Make	Model	Size	Watts	Ohms	Price
Seas	Tweeter	4in	50	8	£9.50
Audax	Tweeter	4in	30	8	£6.50
Audax	Mid-Range	4in	50	8	£7.50
Seas	Mid-Range	4 1/2in	100	8	£12.50
Seas	Mid-Range	5in	80	8	£12.00
Goodmans	Woofers	8in	25	4 or 8	£6.50
Audax	Woofers	8in	40	8	£14.00
Audax	Woofers	10in	50	8	£16.00
Goodmans	8HB	8in	60	8	£12.50
Rigonda	Full-Range	10in	15	8	£5.00
Baker Hi-Fi	Deluxe	12in	15	8	£14.00
Baker Hi-Fi	Major	12in	30	4/8/16	£14.00
Baker Hi-Fi	Super	12in	30	8/16	£24.00
Baker P.A.	Group 45	12in	45	4/8/16	£14.00
Baker Hi-Fi	Auditorium	12in	45	8/16	£22.00
Baker Hi-Fi	Auditorium	15in	60	8/16	£34.00
Baker P.A.	Group 75	12in	75	4/8/16	£18.00
Goodmans	GR Group	12in	90	8/16	£27.50
Baker P.A.	Group 100	12in	100	8/16	£24.00
Baker P.A.	Disco 100	12in	100	8/16	£24.00
Baker P.A.	Group 100	15in	100	8/16	£32.00
Baker P.A.	Disco 100	15in	100	8/16	£32.00
Goodmans	HPD Disco	12in	120	8	£29.50
EMI	450	13 x 8in	10	3/8	£8.00
Goodmans	HP Bass	18in	230	8	£30.00

R.C.S. LOUDSPEAKER BARGAINS
3 ohm, 5 x 3in, 7 x 4in, £2.50; 8 x 5in, 6 1/2in, £3; 8in, £4.50; 10in, £5; 8ohm, 2in, 2 1/2in, £2.00; 3in, 5in, 5 x 3in, 6 x 4in, 7 x 4in, £2.50; 6 1/2in; 8in x 5in £3; 8in; £3; 10in; £3; £3; 12in, £8.
10 ohm, 3in, 5 x 3 1/2in, 6 x 4in, 5in, £2.50; 6 1/2, 8 x 5in, £3; 25 ohm, 3in, 5 x 3in, 7 x 4in, £2.50; 120 ohm, 3 x in, dia, £1.50.

BATTERY ELIMINATOR MAINS TO 9 VOLT DC
Stabilised output, 9 volt 400 mA. UK made with terminals. Overload cut out, 5 x 3 1/2 x 2 1/2in. Transformer Rectifier Unit. Suitable Radios. Cassettes. £4.50. Post 50p.

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p;
1000mF 12V 50p; 25V 35p; 50V 50p; 1200mF 7.5V 90p.
2200mF 6V 25p; 25V 42p; 40V 60p; 2000mF 100V £1.20.
2500mF 50V 70p; 3000mF 25V 50p; 50V 65p.
3300mF 63V £1.20; 4700mF 63V £1.20; 2700mF 7.5V £1.
4700mF 40V 85p; 1000mF 100V £1.

HIGH VOLTAGE ELECTROLYTICS

8/450V	45p	8 + 8/450V	75p	50 + 50/300V	50p
16/350V	45p	8 + 16/450V	75p	32 + 32 + 32/325V	75p
32/350V	75p	20 + 20/450V	75p	100 + 100/275V	95p
50/350V	80p	32 + 32/350V	85p	150 + 200/275V	70p
50/450V	95p	32 + 32/500V	£1.80	220/450V	95p

TRIMMERS 30pF, 50pF 10p, 100pF, 150pF 15p, 500pF 30p.
CONDENSERS VARIOUS, 1pF to 0.01mF 350V 5p.
400V-0.001 to 0.05 5p; 0.1 15p; 0.25 25p; 0.47 35p.
1000V 0.1mF 25p; 0.22mF 30p; 0.47mF 60p; 1750V 0.22mF 50p.
WAFER SWITCHES, 1 pole 12W, 2 pole 6W, 3 pole 4W, 4 pole 3W, 2 pole 2W, 4 pole 2W 60p ea.
TWIN GANGS 120pF £1; 500 + 200pF £1.
SINGLE SOLID DIELECTRIC 100pF, 500pF £1.50.
GEARED TWIN GANGS 25pF 95p; 365 + 365 + 25 + 25pF £1.
SLOW MOTION DRIVE 6:1 90p. **REVERSE VERNIER** 60p.
VERNIER DIALS 36mm £2.25, 50mm £2.75.
SPINDLE EXTENDERS 85p. **COUPLERS** 85p.
NEON PANEL INDICATORS 250V. Red 1 1/2 x 1 1/2 45p. Round at 40p.
RESISTORS, 100 to 10M, 1/2W, 1W, 20% 2p, 2W 10p.
HIGH STABILITY, 1/2W 2%, 10 ohms to 1 meg, 10p.
Ditto 5%. Preferred values: 10 ohms to 10 meg, 3p.
WIRED-WOUND 10 ohm to 10K 5 watt 20p.
BLANK ALUMINIUM CHASSIS, 6 x 4 - £1.45; 8 x 6 - £1.80
10 x 7 - £2.30; 12 x 8 - £2.60; 14 x 9 - £3.00; 16 x 6 - £2.90
16 x 10 - £3.20. All 2 1/2in. 18 swg. **ANGLE ALI**, 6 x 2 1/2 x 2 1/2in, 25p.
ALUMINIUM PANELS - 18 swg, 6 x 4 - 45p; 8 x 6 - 75p;
14 x 3 - 75p; 10 x 7 - 95p; 12 x 8 - £1.10; 12 x 5 - 75p;
16 x 6 - £1.10; 14 x 9 - £1.45; 12 x 12 - £1.50; 16 x 10 - £1.75.
PLASTIC box with aluminium facia 6 1/2 x 3 1/2 x 2in, £1.50.

ALUMINIUM BOXES WITH LIDS
3 x 2 x 1 £1; 4 x 2 1/2 x 2 1/2 £1.4 x 4 x 2 1/2 £1.35
6 x 4 x 2 £1.60, 7 x 5 x 3 £2.40, 8 x 6 x 3 £2.50,
10 x 7 x 3 £3.12, 12 x 5 x 3 £2.75, 12 x 8 x 3 £3.60.
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p, 2 amp £1.00.
4 amp £1.50, 8 amp £2.50. **DIODES** 1a, 10p; 3a, 30p.
TOGGLE SWITCHES SP 40p, DPST 50p, DPDT 60p.
MINIATURE TOGGLES SP 40p, DPDT 60p.

THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes and all sizes of tape reels, A.C. mains 200/240V. £9.50 Post 95p
Ideal all Recorders.
Tapes, Discs, Cassettes, Computers.
HEAD DEMAGNETISER PROBE £5.00

MAINS TRANSFORMERS

5-8-10-16V, 1A	£2.50	24V 2 1/2A Twice	£8.00
6V 1A	£2.00	20V 1A	£3.00
6-0-6V, 1 1/2A	£3.50	20-0-20V 1A	£3.50
9V 250ma	£1.50	20/40/60V 1A	£4.00
9V 3A	£3.50	25-0-25V 2A	£4.50
9-0-9V 50ma	£1.50	28V 1A Twice	£5.00
10-0-10V 2A	£3.00	30V 1 1/2A	£3.50
10-30-40V	£3.50	30V 5A and	£3.50
12V 100ma	£2.00	17-0-17V 2A	£4.50
12V 3A	£3.50	35V 2A	£4.00
12-0-12V, 2A	£3.50	34-29-0-29-34V 6A	£12.00
16-0-16V 2A	£3.75	0-12-27V 2A	£3.50

RADIO COMPONENT SPECIALISTS
DEPT. 6, 337 WHITEHORSE ROAD, CROYDON, SURREY, U.K. TEL: 01-684 1665
Post 50p Minimum. Callers Welcome. Closed Wed. Same day despatch. Access-Barclay-Vlaa. Lists 31p.

TEST, SERVICE, REPAIRS

- Computers (Business and Personal)
- Floppy Disc Drives (all makes)
- VDU's • Monitors • S100 Boards

EPROM SERVICE

- Erase • Program • Copy • Modify
- For 1K, 2K, 4K EPROMs

MICRO UP-GRADES, HARDWARE

- Printers • Monitors • Disc Drives
- Nascom Disc Interface • Z8/Basic Computer • Euro Card Micro Expansion System • Power Supplies • Cables

A. N. Electronic & Computer Services Ltd
211 Park Barn Drive Guildford, Surrey
Tel: (0483) 504897

NEW AUDIO/RADIO/TV valves, sockets, etc. S.a.e. lists: LEC, 25 Ridge Road, Letchworth, Herts SG6 1PW.

48K SPECTRUM CASSETTE, loop filter design program for Motorola MC145152 series synthesisers (and similar), plus five other RF design programs, £4.99. El Syd, 20 Wingrove Hill, River, Dover, Kent.

Save money on drawer sets with the BITSABOX

12 drawer white cardboard bench set for your bits and pieces

Drawer size 140 x 50 x 37mm

ONLY £2.20 + 90p P&P

Cheques/PO to: DMW Boxes, 81 Somers Road London E17 Prop. R.E. Davidson
PERSONAL CALLERS & TRADE ENQUIRIES WELCOME

MATINEE ELECTRONIC ORGAN, professionally built. As new, buyer collects, no offers, £399. Tel Uckfield (0825) 4001.

AMAZING ELECTRONIC PLANS. Lasers, super-powered cutting rifle, pistol, light show, ultrasonic force fields, pocket defence weaponry, giant tesla, satellite tv pyrotechnics, 150 more projects. Catalogue £1 (refundable) form Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

BLEEPER ELECTRONIC SEAT BELT REMINDER, flashers, full kit of parts, easy fitting, £6.95 plus 55p P&P. C.w.o. Micro-Tech Industries, Brighouse, HD6 1RD.

UNBEATABLE PRICES FOR OUR ELECTRONIC COMPONENTS, CMOS, TTL Linear etc (eg NE555 12p; NE555 28p; Texas Sound Chip SN76477N £1.75). Send sae for full list -

BROADCAST QUALITY FOR YOUR NEXT MIXER PROJECT

- Over 100 Audio Sub-Units • Kit or Ready Built

Our new Mic & Mag Disc Pre-amps incorporate the super low noise Mullard/Signetic NE5534 IC.

All items listed are identical to those used in our professional consoles

PARTRIDGE ELECTRONICS
56 Fleet Road, Benfleet, Essex SS7 5JN, England (LARGE S.A.E. PLEASE)
THE MIXER PEOPLE

CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers

ADAM HALL SUPPLIES LTD.

Send 30p cheque/PO for illustrated catalogue: Adam Hall (ET Supplies), Unit B, Carlton Court, Grainger Road, Southend-on-Sea.

COMPONENTS: Chassis mounting fuse holders, 11p; 20mm fuseholder screwdriver release 6.3A, 93p; 20mm fuses, mains, from 14p, anti-surge from 17p; Aerial splitter/combiner, from £3.33; Diodes, from 4p; Capacitors from 10p; Light emitting diodes 5mm round lens: red 9p, yellow 12p, green 11p, red/green/yellow 32p. Resistors from 2p; Transistors from 13p. Postage and packing 50p. Send sae for details to: R&B Electronic, 3 Shute End, Wokingham, Berks, RG11 1BH. Mail order only.

ALL NEM COMPONENTS

CMOS
4012 - 8p, 4017 - 25p; 4019 - 14p; 4022 - 32p; 4023 - 12p; 4024 - 20p; 4025 - 12p, 4049 - 18p; 4071 - 12p; 4076 - 28p; 4081 - 10p; 4518 - 28p; 4520 - 26p; 4528 - 34p; 4557 - 140p; ME567 - 38p; SPX6 - 20p; 314A223 - 4p.

TTL
7400 - 6p; 7404 - 8p; 7412 - 8p; 7419 - 14p; 7414 - 20p; 7416FJ - 12p; 7495 - 24p; 74LS92 - 24p.

30p P + P order under £6. No VAT

V. BANSAL, 14 DAVIDDDR ROAD, HOVE, SUSSEX
UK BK13 1DD
TEL: (0273) 732419

PUSH BUTTON TELEPHONE, 40 number memory, build your own for around £16 using standard components. Full circuit, plans, and construction details, £3 (not BT approved). Ms M. J. Ellis, 1 Wells Drive, Heaton, Mersey, Stockport, Cheshire.

STEREOPOWER 120 WATT £10.85 ... Case + Controls + Sockets + Instructions ... Fibreglass PCB + Protected Outputs ... KIA, 8 Cunliffe Road, Ilkley.

TANGERINE OWNERS 40K CMOS RAM Card, new options, including kit form and prices. For details T H Microelectronics, phone 0602 392965 evenings.

WHATEVER YOU'RE SELLING DO IT QUICKLY & CHEAPLY
Phone ASP Classified
01-437 1003

Get moving with these new developments in UK Robotics

— advanced electrohydraulic designs for education, industry and now available to the home constructor.

Hebot II is a turtle-type robot which takes programming out of the two dimensional world of the VDU into the real three dimensional world. Given a DC supply of 9-15V it can perform a bewildering number of moves under computer control — forwards, backwards left and right — with each where independently controlled. It has blinking eyes, bleeps with a choice of two tones and has a solenoid operated pen to chart its progress. Touch sensor coupled to its shell return data about its environment, to the computer for it to calculate evasive or exploratory action. Hebot II connects directly to an I/O port or alternatively with the universal interface board to the expansion bus of a ZX81 or other computer.

Robotic experience is becoming as essential a subject as computing. MICROGRASP provides the lowest cost means of acquiring that experience but despite its ultra low price the robot has considerable versatility. There are 5 axes each using a servo motor and there is feedback from each of the arm movements. Control is by any computer with an expansion bus — the ZX81 being particularly suitable. Servicing is achieved with hardware on the interface board to keep programming simple and the robot is operated under BASIC commands with no computer specific software required. The interface board is memory mapped using only 64 bytes at any of 1024 switch selectable locations.

MICROGRASP robot kit with power supply £145.00
 Universal computer interface board kit £48.50
 23 way edge connector £2.50
 ZX81 peripheral/RAM Pack splitter board £3.00



MICROGRASP, INTERFACE BOARD AND ZX81



HEBOTT II

Up to the nano-second hard, firm and software developments embodied in a complete system. 2 Mega Hertz 16 bit CPU; 64K upwardly compatible DRAM; separate 16K video DRAM and 24K TI Power Basic with overwrite. Supports up to four Disc drives of mixed type with 16 serial I/O ports. Programmable Baud rate and comprehensive E Bus interface designed to support real world applications.

Very high resolution graphics gives 3D simulation in 16 colours on 36 prioritised planes of user definable characters. Software FORTH coming includes this trendy language along with NOS C/PM.

Hardware components available separately with details in Nov, Dec, and Jan issues of ETI. Software features include: Real time clock, full renumber command, buffered I/O to free machine whilst



printing, call to machine code routines, hexadecimal support and user-friendly textual error trapping messages.

If computers interest you then the Cortex will expand your understanding infinitely more than off the shelf machines. Use it in business, education, research or just play with the incredible graphics capability. At Powertran we are using these machines in conventional roles, in product control and R & D. We shall coordinate the Cortex user group and distribute software for the TMS 9995 CPU. Complete 16 bit 64K computer kit £295.00 + VAT. Complete 16 bit 64K computer ready built £395.00 + VAT.



Top of the range is the Genesis P102 which has dual speed control, continuous servo operation and double acting cylinders for increased torque on the wrist and arm rotat on joints. The microprocessor based control system has additional memory, position interrogation via the RS232C interface increasing the versatility of computer control and inputs are provided for machine tool interlacing.

6 axis system READY BUILT £1950.00
 Powertran CORTEX 16 bit 64K computer Kit £295.00 READY BUILT £395.00
 (Electronics Today International: December issue on CORTEX)

Example prices and specifications

Genesis S101
 Base: 19.5" x 11" x 7.5"
 Lifting capacity: 1500gm
 Arm lift: 6.6"
 Weight: 29Kg
 4 axis model in kit form £425
 5 axis model in kit form £475


Genesis P101
 Base: 19.5" x 11" x 7.5"
 Lifting capacity: 2000gm
 Arm lengths between axes: 14.0"
 Weight: 34Kg
 4 axis model in kit form £675
 6 axis model in kit form £595

Complete Systems as shown in Photograph above


Genesis S101
 4 axis system in kit form £681.50
 5 axis system in kit form £737.50
 5 axis system Ready Built £1450
Genesis P101
 6 axis system in kit form £945.00
 6 axis system Ready Built £1650

All prices exclusive of VAT

With prices starting below £1,000 the Genesis range of general purpose robots provide a first rate introduction to robotics for both education and industry. Each has a self-contained hydraulic power source, which enables loads of several pounds to be smoothly handled. The system operated from a single phase 240 or 120V AC supply or a 12V DC supply. The machine can be supplied with up to 6 axes each of which is fully independent but capable of simultaneous operation. Position control is achieved by means of a closed-loop feedback system based around a dedicated microprocessor. Movement sequences can be entered, stored and replayed by use of a hand held controller, alternatively the systems can also be interlaced to an external computer via a standard RS 232C link.

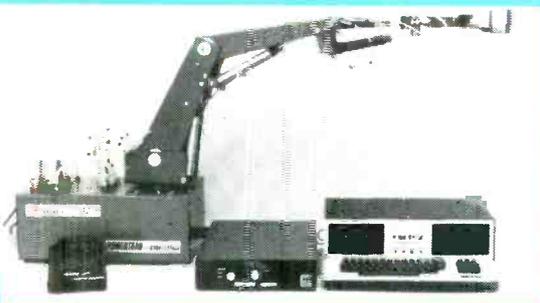

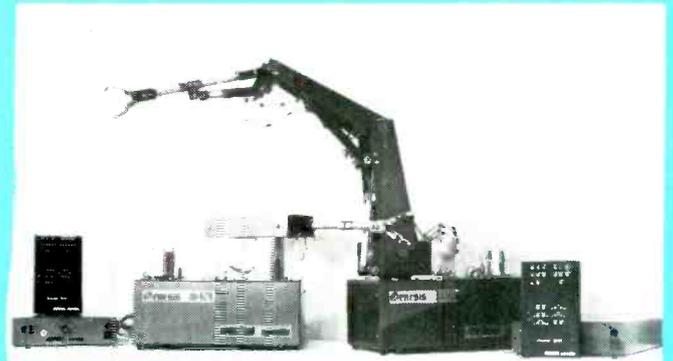GENESIS P102 PROCESSOR BOX, HAND HELD CONTROLLER AND CORTEX COMPUTER



GENESIS S101 AND GENESIS P101 WITH PROCESSOR BOXES AND HAND-HELD CONTROLLERS

**WORLD LEADERS
 IN
 ELECTRONIC
 KIT DESIGN
 AND SUPPLY**

**(CYBERNETIC DIVISION)
 PORTWAY INDUSTRIAL ESTATE
 ANDOVER HANTS SP10 3NM
 Phone Enquiries (0264) 64455**

SPEECH SYNTHESISER FOR ZX81 and VIC20

THE MAPLIN TALK-BACK

Now your computer can talk!

- ★ Allophone (extended phoneme) system gives unlimited vocabulary.
- ★ Can be used with unexpanded VIC20 or ZX81 — does not require large areas of memory.
- ★ In VIC20 version, speech output is direct to TV speaker with no additional amplification needed.
- ★ Allows speech to be easily included in programs.


Complete kit only £24.95.

Order As LK00A (VIC20 Talk-Back).
LK01B (ZX81 Talk-Back).

Full construction details in Maplin Projects Book 6.
Price 70p. Order As XA06G (Maplin Mag Vol. 2 No. 6).



KEYBOARD WITH ELECTRONICS FOR ZX81

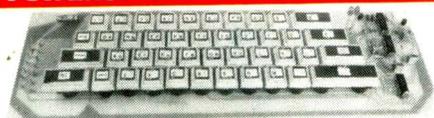

- ★ Full size, full travel keyboard that's simple to add to your ZX81 (no soldering in ZX81).
- ★ Complete with electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections.
- ★ Powered (with adaptor supplied) from ZX81's own standard power supply.

Full details in Project Book 3 (XA03D) Price 60p
Complete kit (excl. case) £19.95. Order As LW72P.
Case £4.95. Order As XG17T.
Ready built-in case £29.95. Order As XG22Y.

OTHER KITS FOR ZX81

3-Channel Sounds Generator (Details in Book 5).
Order As LW96E. Price £10.95.

ZX81 Sound On Your TV Set (Details in Book 6).
Order As LK02C. Price £19.95.

ZX81 I/O Port gives two bi-directional 8-bit ports
(Details in Book 4).
Order As LW76H. Price £9.25.

ZX81 Extendiboard will accept 16K RAM and 3 other
plug-in modules.

PCB Order As GB08J. Price £2.32.
Edge Connectors (4 needed).
Order As RK35Q. Price £2.39.

HOME SECURITY SYSTEM

Six independent channels - 2
or 4 wire operation. External
horn. High degree of protection
and long term reliability.
Full details in Projects Book 2.
(XA02C) Price 60p



MATINEE ORGAN

Easy-to-build, superb
specification. Compar-
able with organs selling
for up to £1000. Full
construction details in our
book (XH55K). Price £2.50
Complete kits available.
Electronics (XY91Y) £299.95*
Cabinet (XY93B) £99.50*
Demo cassette (XX43W) £1.99.



* Carriage extra


25W STEREO MOSFET AMPLIFIER



- ★ Over 26W/channel into 8Ω at 1kHz both channels driven
 - ★ Frequency response 20Hz to 40kHz ± 1dB.
 - ★ Low distortion, low noise and high reliability power MOSFET output stage.
 - ★ Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
 - ★ Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.
- Full details in Projects Book 3. Price 60p (XA03D).
Complete kit only £49.95 incl. VAT and carriage (LW71N).

BUY IT WITH MAPCARD

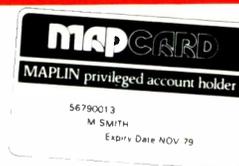Send now for an
application form — then
buy it with MAPCARD.
MAPCARD gives you
real spending power —
up to 24 times your
monthly payments,
instantly.



All prices include VAT & carriage. Please add 50p handling charge to orders under £5 total value.

MAPLIN'S FANTASTIC PROJECTS

Full details in our project books. Issues 1 to 5: 60p each.
Issue 6: 70p

In Book 1 (XA01B) 120W rms MOSFET Combo-
Amplifier ● Universal Timer with 18 program times and
4 outputs ● Temperature Gauge ● Six Vero Projects.

In Book 2 (XA02C) Home Security System ● Train
Controller for 14 trains on one circuit ● Stopwatch with
multiple modes ● Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics ●
Stereo 25W MOSFET Amplifier ● Doppler Radar Intruder
Detector ● Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 exten-
sions ● Frequency Counter 10Hz to 600MHz ● Ultrasonic
Intruder Detector ● I/O Port for ZX81 ● Car Burglar
Alarm ● Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard ●
100W 240V AC Inverter ● Sounds Generator for ZX81
● Central Heating Controller ● Panic Button for Home
Security System ● Model Train Projects ● Timer for
External Sounder.

In Book 6 (XA06G)* Speech Synthesiser for ZX81 &
VIC20 ● Module to Bridge two of our MOSFET Amps to
make a 350W Amp ● ZX81 Sound on your TV ● ZX81
Interface for Modem ● Scratch Filter ● Doorbell for Deaf
● Simple FM Tuner* ● Damp Meter*

*Projects for Book 6 were in an advanced state at the time
of writing, but contents may change prior to publication
(due 11th February 1983).

MAPLIN'S NEW 1983 CATALOGUE

Over 390 pages packed
with data and pictures
and all completely
revised and including
over 1000 new items.
On sale in all branches
of WHSMITH
Price £1.25.



Post this coupon now!

Please send me a copy of your 1983 catalogue. I enclose £1.50 (inc p&p).
If I am not completely satisfied I may return the catalogue to you and have
my money refunded. If you live outside the U.K. send £1.90 or 10 International
Reply Coupons.

Name

Address

ETI

MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD.

P.O. Box 3, Rayleigh, Essex SS6 8LR

Telephone: Sales (0702) 552911 General (0702) 554155

Shops at: Note: Shops closed Mondays

159 King St., Hammersmith, London W6. Telephone: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Telephone: (0702) 554000

Lynton Square, Perry Barr, Birmingham. Telephone: (021) 356 7292