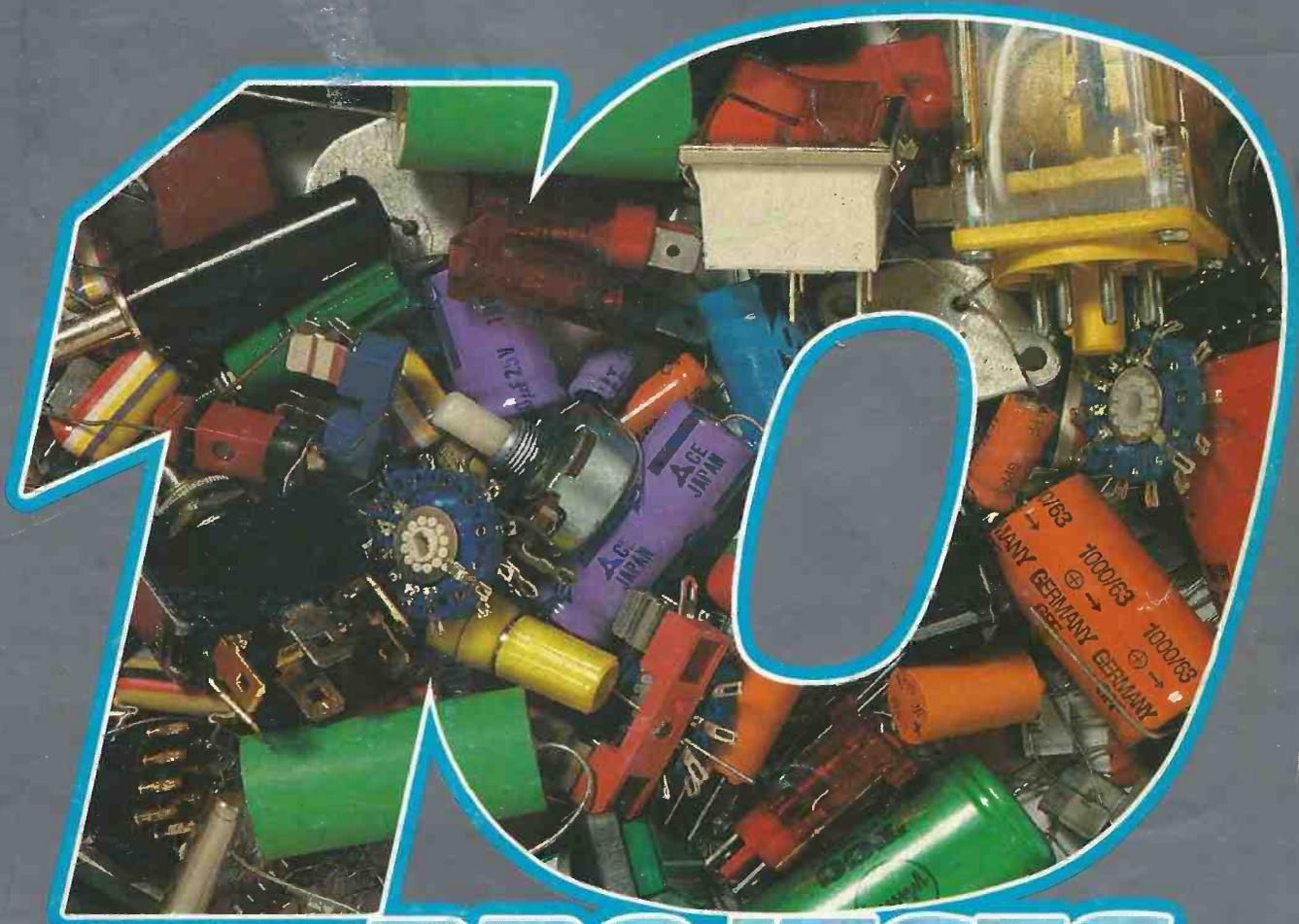


electronics today

INTERNATIONAL

NOVEMBER 1983 85p



PROJECTS

including:

- Logic probe — monitor up to 16 points all at once
- Active loudspeaker — novel, economic design
- Drum synthesiser — modular for flexibility
- Filter/amplifier for DAC/ADC — clean up your interfacing
- Multiple output port — expandable up to 40 on/off outputs

OVER 100 PAGES
Best value for money
in electronics!

..AUDIO.... COMPUTING.... MUSIC.... RADIO.... ROBOTICS..

Star sounds **

Star quality **

Star features **

**BIG NEWS
ABOUT OUR
LATEST
ADVANCES IN
ROBOTICS
SEE INSIDE
BACK COVER**

**Free
SECURICOR
DELIVERY**
on all orders over
**£100 (UK mainland
only) Add just £2.50
on lower price
orders**



DJ90 Stereo Mixer — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! Complete kit **£97.50 + VAT**

TRANSCENDENT 2000 — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it — play it! You will know you have made the right choice.

Complete kit **£165.00 + VAT**



**SALES
COUNTER**
Collect your order
from the factory.
Open 9-12/1-4.30
Mon- Fri. Easy
parking, no
waiting

Digital Delay Line — With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo &



vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,000!

Complete kit (400 mS delay) **£130 + VAT**
Parts for extra 400 mS delay **£9.50 + VAT**



This versatile modular mixer, featured as a constructional article in Practical Electronics can be built up to a maximum of 24 inputs, 4 outputs and an auxiliary channel. Each input channel has Mic and Line inputs, variable gain, bass and treble controls and a parametric middle frequency equalizer. There are send and return jacks, auxiliary, pan and fader controls and output and group switching. The output channels have PPM displays and record and studio outputs. The auxiliary channel also has a PPM display and there is a headphone monitor jack and a built-in talk-back microphone. The mixer modules plug into base units each of which takes up to 6 channels. To eliminate hum, the power supply is in a separate cabinet.

KIT PRICES

Input channel	£19.90	Base unit and wooden front	£27.50
Output channel	£18.50	Pair of mahogany end cheeks	£12.50
Auxiliary channel	£22.50	Power Supply and cabinet	£19.50
Blank Panel	£3.00		

All prices are VAT exclusive

**Free Soldering
Practise Kit on
request with your
first kit — useful
tips, well
illustrated.**

MPA 200 — is a low price, high power 100W amplifier, its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for

the first time builder. Complete kit **£49.90 + VAT**.

Chromatque 5000 — a 5 channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single board design. Complete kit **£49.50 + VAT**

ET1 VOCODER — 14 channels, each with independent level control for maximum versatility and intelligibility; Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual is within the capability of most enthusiasts. Complete kit **£175.00 + VAT**

SP2 200 twice the power with two of the reliable, durable and economic amps from the MPA 200, fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over) the standard of high prices factory-built units! Complete kit **£64.90 + VAT**



**Component
packs for most
kits are available
See our great free
catalogue, full
details of all
our range**

TRANSCENDENT POLYSYNTH — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.

Complete kit **£230.00** plus VAT (single voice)
Extra voice (up to three more) **£35.60** plus VAT



POWERTRON

**WORLD
LEADERS
IN
ELECTRONIC
KIT DESIGN
AND SUPPLY**

PORTWAY INDUSTRIAL ESTATE

ANDOVER, HANTS SA10 3NM.

ORDER BY PHONE (0264) 64455

Simply request your chosen kit and quote your Access or Barclaycard Number.



electronics today

INTERNATIONAL NOVEMBER 1983 VOL 12 NO 11

EDITORIAL AND ADVERTISEMENT OFFICE


145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.
Telex 8811896.

FEATURES

- DIGEST** 11
The best, newest, the unusual, or the just plain silly — ETI keeps you in touch with it all.
- AUDIO DESIGN**.....26
Having discussed the problems, John Linsley Hood now suggests some solutions and takes us through a practical example.
- IC UPDATE**.....63
Op-amps and the generation gap.
- FIBRE OPTICS**..... 74
This important new technology has not found much application among hobbyists, until now that is.

- MACHINE CODE PROGRAMMING**.....43
The second part of Bob Bennet's series on how to talk to a micro in it's native tongue.

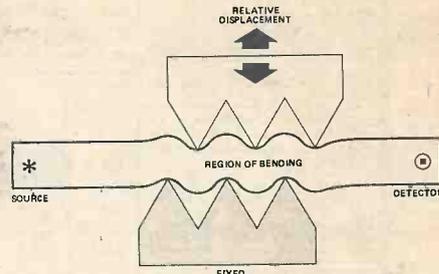- TECH TIPS**.....56
Now it's your turn!
- READ/WRITE**.....86
You tell us!



PROJECTS

- ACE INTERFACE**.....20
Are you and your Ace out of touch? Interface a proper keyboard or a joystick with this design and enjoy a closer relationship.
- MC HEAD AMP**.....31
Sneaked into the middle of Audio Design, a neat little project from John Linsley Hood.
- MINI DRUM SYNTH**.....36
If complex drum synthesisers leave you beat, build ETIs simple but flexible module.
- ALARM EXTENDER**.....39
Protection without too much racket is the aim of this useful little device.
- MULTISWITCH**.....47
Multi-way light switching without multi-cabling and multi-headaches.
- MULTIPLE OUTPUT PORT**.....52
Extend your micro's reach with up to forty switched outputs.
- DAC/ADC FILTER/AMPLIFIER**.....59
For everyone who has ever experimented with analogue interfacing and ended up wishing they hadn't.
- ACTIVE LOUDSPEAKER**.....68
This unusual design offers you all the advantages of an active system but costs less to build than you'd expect and runs from your existing amplifier.
- FAST LIGHT PEN**.....81
ETIs high speed, low cost design leaves the commercial competition at the starting post.
- LOGIC CLIP**.....91
This unique unit displays sixteen logic levels simultaneously on its dazzling three-colour display, putting single point logic probes firmly in the shade.

INFORMATION

- NEXT MONTH'S ETI** 7
BREADBOARD EXHIBITION . . . 8
ETI BOOKS SERVICE 34
- ETI PCB SERVICE** 89
READERS' SERVICES 96
ADVERTISERS' INDEX 106



Dave Bradshaw: Editor
Phil Walker: Project Editor
Ian Pitt: Editorial Assistant
Jerry Fowler: Technical Illustrator
David Kitchener: Ad. Manager
Joanne James: Assistant Ad. Manager
Lynn Collis: Copy Control
Ron Harris B.Sc: Managing Editor
T.J. Connell: Chief Executive

PUBLISHED BY:
Argus Specialist Publications Ltd.,
145 Charing Cross Road, London WC2H 0EE.

DISTRIBUTED BY:
Argus Press Sales & Distribution Ltd.,
12-18 Paul Street, London EC2A 4JS
(British Isles)

PRINTED BY:
The Garden City Press Ltd.
COVERS PRINTED BY:
Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS

AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsman



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1983 Argus Specialist Publications Ltd. □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates. UK £13.15 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

SWITCHES
TOGGLE: 2A, 250V
SPST 33p
DPDT 44p

SUB-MIN TOGGLE
SPST on/off 54p
SPST c/over 60p
SPDT centre off 50p
SPDT centre off
SPDT 6 ways 105p
DPDT 6 ways 75p
DPDT centre off 88p
DPDT 12 way 145p
DPDT 3 positions on/on/off 185p
3-pole 2 way 205p

SLIDE 250V:
DPDT 1A 14p
DPDT 1A c/off 15p
DPDT 1/2A 13p

PUSHBUTTON SA
with 10mm Button
SPDT latching 99p
DPDT latching 145p
SPDT moment 99p
DPDT moment 145p

Mint Non Locking
Push to Make 15p
Push to Break 25p

ELEKTOR PROJECTS
We stock most of the parts

JUMPER LEADS (Ribbon Cable Assembly)
Length 14 pin 16 pin 24 pin 40 pin
Single ended DIP (Header Plug) Jumper 14p 16p 24p 30p
Double ended DIP (Header Plug) Jumper 18p 20p 28p 30p
IDC Female Header Jumper Leads 14 pin 20 pin 26 pin 34 pin 40 pin
Single ended 18p 20p 28p 30p p
Double ended 29p 37p 48p 52p

TRANSFORMERS:
3.0-3V; 6.0-6V; 9.0-9V; 12.0-12V; 15.0-15V @100mA 36p

pcb mounting, Miniature, Split Bobbin
3VA: 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A
8VA: 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A; 2x15V-0.2A
Standard Split Bobbin type
8VA: 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A; 2x15V-0.25A
12VA: 2x4.5V-1.3A; 2x3V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A
24VA: 2x6V-1.2A; 2x9V-2.1A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A
50VA: 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A
Specially wound for Multirail Computer PSUs
50VA: Outputs +5V/5A; +12V; +25V; -5V; -12V at 1A
100VA: 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1.0A (75p p/p charge to be added over and above our normal postal charge).

CMOS	4075	13	4541	140	
4000	10	4076	50	4543	70
4001	10	4077	15	4544	105
4002	12	4078	15	4548	40
4006	50	4081	13	4549	375
4007	14	4082	13	4553	246
4008	32	4085	50	4554	190
4009	24	4086	30	4555	36
4010	24	4089	125	4557	32
4011	10	4093	20	4557	320
4012	18	4094	70	4558	120
4013	20	4095	95	4559	396
4014	48	4096	160	4560	160
4015	40	4097	280	4561	104
4016	20	4098	75	4562	95
4017	32	4099	110	4566	165
4018	45	4100	95	4568	250
4019	25	4102	95	4569	175
4020	42	4103	95	4572	36
4021	40	4104	95	4580	460
4022	40	4174	95	4581	260
4023	13	4175	105	4582	99
4024	13	4176	105	4583	99
4025	13	4408	790	4584	40
4026	80	4409	790	4585	60
4027	20	4410	725	4587	330
4028	30	4411	675	4589	290
4029	45	4412	775	4596	90
4030	15	4415	480	40097	45
4031	125	4419	280	40098	42
4032	80	4422	770	40100	215
4033	125	4435	850	40101	130
4034	140	4440	998	40102	140
4035	45	4450	350	40103	175
4036	275	4451	305	40104	95
4037	115	4490	350	40105	105
4038	110	4500	675	40107	80
4039	250	4501	28	40108	198
4040	40	4502	80	40109	80
4041	40	4503	40	40110	240
4042	40	4504	75	40112	125
4043	40	4505	185	40114	240
4044	40	4506	36	40116	194
4045	105	4507	36	40174	45
4046	48	4508	105	40175	50
4047	40	4510	46	40181	220
4048	40	4511	46	40182	90
4049	25	4512	50	40192	75
4050	25	4513	199	40193	70
4051	45	4514	115	40194	50
4052	60	4515	115	40195	70
4053	50	4516	56	40244	196
4054	85	4517	275	40245	196
4055	85	4518	40	40257	196
4056	85	4519	40	40373	160
4057	1915	4520	50	40374	160
4058	435	4521	90	45106	596
4060	45	4522	125		
4061	1185	4526	70		
4062	395	4527	90		
4063	85	4528	10		
4064	24	4529	150		
4067	245	4530	90	LSA400C	255
4068	14	4531	130	OC71	120
4069	16	4532	70	ORP12	80
4070	13	4533	400	ORP61	85
4071	13	4536	275	2N5777	45
4072	13	4538	80	BPX25	195
4073	15	4539	80	BPW21	295

DIL SWITCHES
(SPST) 4 way 65p 6 way 80p
8 way 85p 10 way 100p
(SPDT) 4 way 190p.

ROTARY SWITCHES:
(Adjustable Stop type)
1 pole/2 to 12 way; 2p/2 to 6 way;
3 pole/2 to 4 way; 4p/2 to 3 way 45p

ROTARY: Mains DP 250V 4 Amp on/off 68p

ROTARY: (Mak-a-switch)
Make a multi-way switch. Shifting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch) Mechanism only 90p

WAFERS: (make before break) to fit the above switch mechanism.
1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6/2 way; 6/2 way
Mains DP 4A Switch to fit Spacers 4p. Screen 6p 45p

ROCKER: 5A/250V SPST 28p
ROCKER: 10A/250V DP/OT 38p
ROCKER: 10A/250V DPST c/off 95p
ROCKER: 10A/250V DPST with neon 85p

THUMBWEHEEL Mini front mounting
Decade Switch Module 220p
B.C.D. Switch Module 275p
Mounting Chucks (per pair) 75p

VEROBOARD 0.1in
clad plain
2 1/2 x 3 1/2 85p
2 1/2 x 5" 100p
3 1/2 x 3 1/2 100p
3 1/2 x 5" 115p
1 1/2 x 7" 390p 198p
4 1/4 x 1 7/8" 495p 275p
Pkt. of 100 pins 55p
Spot face cutter 150p
Pin insertion tool 185p

VERO WIRING
PEN + spool 340p
Spare spool 75p
Combe 6p

FERRIC CHLORIDE
1 lb bag Anhydrous 195p + 50p P&P

COPPER CLAD BOARDS
Fibre Single- Double- S.R.B.P.
glass sided 125p 9.5" x 8.5"
6" x 6" 100p 125p 110p
6" x 12" 175p 225p

DIL SOCKETS
Low Wire Prof Wires
8pin 8p 25p
14pin 10p 35p
16pin 10p 42p
18pin 10p 50p
20pin 20p 80p
22pin 22p 65p
24pin 25p 70p
28pin 28p 80p
40pin 30p 95p

EDGE CONNECTORS
2 x 18 way 180p
2 x 22 way 199p
2 x 23 way 175p
2 x 25 way 225p
2 x 28 way 190p
2 x 30 way 245p
2 x 36 way 235p
2 x 40 way 315p
2 x 43 way 395p
2 x 75 way 550p

ANTEX SOLDERING IRON
C-15W 495p CS17W 495p
G-18W 520p XS25W 525p
Spare tips, assorted sizes 225p
Spare Elements 175p
Iron stand with sponge 65p

SIL SOCKET
0.1" pitch 20 way
0.2" pitch 20 way

PROTO DECS
Veroblock 405p
S-Dec 350p
Euroboardboard 525p
8-pinboard 575p
Superstrip SS2 1350p

DALO ETOCH RESIST PEN
Plus spare tip 100p

ULTRASONIC TRANSDUCER
40KHz 325 pr

PCB PLUGS
10 way 80p
16 way 130p
20 way 145p
28 way 175p
34 way 205p
40 way 220p
50 way 235p
60 way 250p

FEMALE
10 way 80p
16 way 130p
20 way 145p
28 way 175p
34 way 205p
40 way 220p
50 way 235p
60 way 250p

Female Card Edge Connect
120p

EURO CONNECTORS
Female Socket Strt. Angle Strt. Angle
DIN41617 170p - - 175p
DIN41612 2x32 A+B 275p 320p 220p 285p
DIN41612 2x32 A+C 295p 340p 240p 300p
DIN41612 3x32 A+B+C 360p 385p 260p 395p

DIL PLUG (Header)
14pin 40p 99p
16pin 40p 105p
24pin 80p 178p
40pin 250p 255p

RIBBON CABLE
price per foot
Grey Color
10 way 15p 28p
16 way 25p 40p
20 way 30p 50p
24 way 40p 65p
34 way 60p 85p
40 way 70p 90p
50 way 85p 110p
64 way 100p 135p

MALE 'D' CONNECTORS miniature
9 15 25 37
Solder lugs 80p 105p 160p 250p
Angle pins 150p 210p 250p 365p
PCB pins 120p 130p 195p 295p
FEMALE
Solder lugs 105p 160p 200p 335p
Angle pins 165p 215p 290p 440p
PCB pins 150p 180p 240p 350p
COVERS 85p 80p 80p 105p
IDC 25way 'D' Plug Socket 385p 450p

ALUM BOXES
3 x 2 x 1" 85p
4 x 2 x 2" 105p
4 x 3 x 2" 105p
4 x 4 x 2" 120p
5 x 4 x 2" 99p
5 x 4 x 3" 120p
5 x 2 1/2 x 1" 80p
5 x 2 1/2 x 2" 130p
6 x 4 x 2" 120p
6 x 4 x 3" 150p
7 x 5 x 3" 150p
8 x 5 x 3" 200p
10 x 4 x 3" 240p
10 x 7 x 3" 275p
12 x 5 x 3" 280p
12 x 8 x 3" 295p

PANEL METERS
FSD
80 x 45 x 35mm
0-100A
0-500A
0-1mA
0-5mA
0-10mA
0-50mA
0-100mA
0-50mA
0-300V AC
0-100V AC
0-25V
0-50V AC
0-300V AC

RELAYS
Miniature, enclosed, PCB mount.
SINGLE POLE Changeover
RL6-91 205Ω Coil, 12V DC (10V5 to 19.5V), 10A at 30V DC 185p
DOUBLE POLE Changeover, 6 A
30 V DC or 250 V AC
RL6-100 53 Ω Coil, 6 V DC (5V4 to 9V9) 190p
RL6-111 205 Ω Coil, 12 V DC (10V7 to 19V5) 175p
RL6-114 740 Ω Coil, 24 V DC (22 V to 37 V) 200p

AMPHENOL PLUG
IDC Solder
24way IEEE 475p 450p
35way Centronics 525p 485p

ASTEC UHF MODULATORS
6 MHz Standard 325p
8 MHz Wideband 450p

BUZZERS, miniature, solid-state
5V 9V & 12V 70p

PIEZO TRANSDUCERS
PB2720 55p

LOUDSPEAKERS
Miniature, 0.3W: 80
2in, 3in, 2in, 3in 80p
2in 400, 640 or 800 80p

CRYSTALS
32.768KHz 100
100KHz 236
200KHz 268
455KHz 370
1MHz 275
1.008M 275
1.28MHz 382
1.5MHz 386
1.8MHz 336
1.8432M 226
2.0MHz 226
2.4576M 200
3.2768M 350
3.58MHz 96
3.6864M 300
4.0MHz 150
4.032MHz 290
4.80MHz 200
4.194304M 200
4.433619M 100
5.0MHz 180
5.185MHz 300
5.24288M 300
6.0MHz 140
6.144MHz 226
6.5536MHz 226
7.0MHz 150
7.368MHz 250
8.0MHz 150
8.08333M 385
8.98723M 175
9.00MHz 175
10.0MHz 175
10.24MHz 200
10.7 150
12.0MHz 175
12.528M 300
14.31814M 170
16.0MHz 200
18.0MHz 180
18.432M 150
20.0MHz 200
27.145M 190
24.0MHz 376
24.930MHz 320
26.59M 150
27.948M 170
27.145M 190
38.56677M 175
48.0MHz 170
100.0MHz 295
116.0MHz 250

MONITORS
ZENITH - 12" Green, Hi-Resolution Popular £ 75
MICROVITEC 1431, 14" Colour RGB input. Connecting cable incl. £ 250

NEW NEW NEW
BROTHER 8300 DAISY WHEEL PRINTER/TYPewriter
Provides very high quality type in any of six interchangeable styles including Italics, Script and 4 conventional typefaces. It is therefore ideal for business use. It connects directly to a BBC Micro via standard centronics interface or can be used as a stand alone typewriter. As typewriter, it has a built in timing function to measure the operator's speed making it ideal for teaching or invoicing jobs corrected. Friction feed; 11 CPS; 12" max width; 5 different colour ribbons. Portable. Supplied complete with hard cover carrying case.
Only: £399

COMPUTER CORNER
• RX80 100 CPS, 9 x 9 matrix, dot addressable graphics, condensed & double width printing, Normal, Italics & Elite Char., Tractor Feed, Bidirectional, Logic seeking £285
• FX80 10" Tractor & Friction feed, 160 CPS, bidirectional Logic seeking, 9 x 11 matrix, hi-res bit image, Normal, Italic & Elite Char. Super & Subscript. Proportional spacing. FREE 500 sheets £385
• SEIKHOSA GP100A. 10" Tractor feed, 80 column, 30 CPS, Normal & Double width Char. Dot Res Graphics. FREE 500 Sheets. £175
• SEIKHOSA GP250X: 10", 50 CPS, Normal and Double width and height Char. RS232 and Centronics Infr. standard £235 (£7 carr).
• Printer Cable for our printers and BBC MICRO £12
• SOFTY-2: The complete Microprocessor development system. Accepts any 2pin 5 V EPROM. £169
• TEX EPROM ERASER Erases up to 32 ICs in 15-30 minutes £ 33
• TEX EPROM ERASER with a safety switch £ 35
• TEX EPROM ERASER plus our Solid State ELECTRONIC TIMER £44
• ELECTRONIC TIMER, Solid State, 15-30 min. Connects directly to above Erasers. Protects your expensive Chips from overcooking. Our timer pays for itself in no time £15
• SPARE 'UV' Lamp bulb £9
• POWER SUPPLY. Regulated with Overload protection. Variable Output, 5V to 15V at 4 A. Professionally finished £38
• C12 COMPUTER GRADE CASSETTES in library case 40p
• 8 1/2" & 9 1/2" Fan Fold Paper (1000 Sheets) £7 (carr 150p)

FLOPPY DISC DRIVES TEAC (BBC Compatible)
• CS50A - Single Cased with PSU, 40 track, 5 1/4" S/S 100K £170
• CD50A - Twin Cased with PSU, 40 track, 5 1/4" S/S 200K £330
• CS50E - Single Cased with PSU, 80 track, 5 1/4" S/S 200K £245
• CD50E - Twin Cased with PSU, 80 track, 5 1/4" S/S 400K £475
• 10 Verbatim Diskette 5 1/4" S.S.D. (5 yrs warranty) £20
• 10 Verbatim Diskettes 5 1/4" S.D.S.D. (5 yrs warranty) £35
• 10 Verbatim Diskettes 8" S.S.D.D. (5 years warranty) £28
• 10 Wabash Diskettes, 5 1/4", S/S £15
• 10 Wabash Diskettes, 5 1/4", S/S £25
• MITSUBISHI DISC DRIVES: Uncased, Double, Density, Double track, 5 1/4" Slim line. ONE MEGA BYTES. Track Density 96TPI. Track to track access time 3 msec. only: £225
• MITSUBISHI Single Slimline, 5 1/4" Cased with PSU, D.S.D.D. 1 Megabyte. (400 K with BBC) £275
• MITSUBISHI Twin Slimline, 5 1/4" Cased with PSU, D.S.D.D. 2 Megabyte. (800 K with BBC) £535

NEONS
Rectangular, nut fixing
Red; Amber; Green 30p
REFLECTIVE Optical
Switch type TIL139170p
SLOTTED Optical
Switch similar to
Comp's 186p

NEC PC8023BE-C PRINTER
Europe's most popular Printer
100CPS bi-directional, Logic seeking, 80 column, 7 x 9 Dot matrix head, true descenders on lower case, Superscript & Subscript & Underlining facility. Proportional spacing, Forward & reverse line feed, Tractor or friction feed, Hi-res & block graphics. Auto underlining. Plus FREE 500 sheets paper.
Price: Only £320 + £7 carr.

SPECTRUM FORTH - I/O Unit
12 K of fig - FORTH in ROM, Full RS232 and 24 Bits of I/O for Centronics and Control use. Can be used on BASIC or FORTH. Will work on 16 K or 48 K Spectrum. Many other features.
only: £59
(Send SAE for full details)

BBC MICROCOMPUTER & ACCESSORIES
Model A £299 Model B £399 (incl VAT)
We stock the full range of BBC Micro peripherals, Hardware & Software like, Disc Drivers (Top quality Cumana & Mitsubishi), Diskettes, Printers, printer Paper, Interface Cable, Dust Cans, Cassette Recorder & Cassettes, Monitors, Connectors (Ready made Cables, Plugs & Sockets), Plotter (Graphic Tablet) EPROM Programmer, Lightpen Kit, Joysticks, Sideways ROM Board, EPROM Eraser, Machinecode ROM. The highly sophisticated Watford's 16K BEEB DFS, WORDWISE, BEEB-CALC, Software (Educational Application & Games), BOOKS, etc., etc. Please send SAE for our descriptive leaflet.

COMTECH ELECTRONICS

TRANSISTORS				THYRISTORS				CMOS				CPU IC's				VOLTAGE REGULATORS			
BC 107B 12p	BC 546 10p	BF 195 12p	MPSA 55 20p	2N2907A 25p	C 108D 14p	40162 52p	6800 395p					Positive							
BC 108C 10p	BC 546B 10p	BF 196 12p	MPSA 56 20p	2N3053 23p	C 116D 70p	40163 52p	6802 550p					100mA							
BC 109C 12p	BC 547B 9p	BF 197 12p	MPSA 63 22p	2N3054 56p	C 126D 90p	40164 52p	6808 520p					78L05 30p							
BC 113/4 16p	BC 548B 9p	BF 198 10p	MPSA 64 22p	2N3055 50p	MCR 101 30p	40165 52p	6810 250p					78L12 30p							
BC 115/6 17p	BC 548C 9p	BF 199 12p	MPSA 92 24p	2N3055H 75p	MCR 102 34p	40166 52p	6820 250p					78L15 30p							
BC 119 28p	BC 549C 9p	BF 200 40p	MPSA 93 24p	2N3440 58p	T 2800D 110p	40167 52p	6821 190p					78L18 45p							
BC 139 32p	BC 550C 10p	BF 224 15p	TIP 29A 30p	2N3441 120p	T 2800M 165p	40168 52p	6840 595p					78L24 45p							
BC 140 28p	BC 556 10p	BF 244C 22p	TIP 29B 33p	2N3442 120p	2N4443 120p	40169 52p	6850 180p					1 A TO220							
BC 141 29p	BC 556B 10p	BF 245 25p	TIP 29C 33p		2N4444 130p	40170 52p	6852 360p					7805 36p							
BC 142 27p	BC 557B 9p	BF 256C 32p	TIP 30A 30p	2N3702 10p	2N5060 23p	40171 52p	6880 140p					7808 55p							
BC 143 27p	BC 557C 9p	BF 256LC 35p	TIP 30B 33p	2N3703 10p	2N5061 24p	40172 52p	6885 130p					7812 36p							
BC 160 30p	BC 558B 9p	BF 257 32p	TIP 30C 36p	2N3704 10p	2N5062 29p	40173 52p	6889 140p					7815 36p							
BC 161 32p	BC 558C 9p	BF 258 32p	TIP 31A 33p	2N3705 10p	2N5064 32p	40174 52p	6800 POA					1 A TO220							
BC 169C 8p	BC 559C 9p	BF 259 35p	TIP 31B 35p	2N3706 10p		40175 52p	8T26A 140p					7805 36p							
BC 171B 9p	BC 560C 10p	BF 336 36p	TIP 31C 37p	2N3707 10p		40176 52p	8T28 120p					7824 40p							
BC 172C 9p	BC 637 20p	BF 337 39p	TIP 32A 33p	2N3708 10p		40177 52p	8T95 140p					5 A TO3							
BC 173C 9p	BC 638 20p	BF 338 40p	TIP 32B 35p	2N3771 150p		40178 52p	8T97 140p					78H05 540p							
BC 177B 15p	BC 639 22p	BF 457 32p	TIP 32C 37p	2N3772 170p		40179 52p	8T98 140p					Negative							
BC 178C 15p	BC 640 24p	BF 458 32p	TIP 33A 55p	2N3773 190p		40180 52p	8T99 140p					100 mA							
BC 179 15p	BCY 70 18p	BF 459 37p	TIP 34A 60p	2N3819 20p		40181 52p	8080A 400p					79L05 50p							
BC 182 9p	BCY 71 18p	BF 494 12p	TIP 41A 46p	2N3823 50p		40182 52p	8085A 500p					79L12 50p							
BC 182B 9p	BCY 72 17p	BF 595 16p	TIP 41C 60p	2N3866 95p		40183 52p	8156C 600p					79L15 50p							
BC 183B 9p	BD 115 50p	BF 596 20p	TIP 42A 66p	2N3903 10p		40184 52p	8212C 198p					1 A TO220							
BC 183C 9p	BD 131 45p	BFX 29 28p	TIP 42C 60p	2N3904 10p		40185 52p	8224C 220p					7905 45p							
BC 184B 9p	BD 132 48p	BFX 30 28p	TIP 110 45p	2N3905 10p		40186 52p	8228C 450p					7906 65p							
BC 184C 9p	BD 133 70p	BFX 84 28p	TIP 115 45p	2N3906 10p		40187 52p	8251AC 495p					7908 65p							
BC 212 9p	BD 135 30p	BFX 85 28p	TIP 120 70p	2N4030 30p		40188 52p	8253AC 850p					7912 55p							
BC 212B 9p	BD 136 30p	BFX 87 27p	TIP 121 70p	2N4033 30p		40189 52p	8257C 750p					7915 55p							
BC 213B 9p	BD 137 30p	BFX 88 23p	TIP 122 70p	2N4037 40p		40190 52p	8259C 900p					7924 65p							
BC 213C 9p	BD 138 35p	BFY 50 23p	TIP 126 70p	2N4058 40p		40191 52p	8288 £16					-Variable-							
BC 214B 9p	BD 139 35p	BFY 51 22p	TIP 127 70p	2N4059 10p		40192 52p	TMS9980A£22					LM 309K 120p							
BC 214C 9p	BD 140 35p	BFY 52 22p	TIP 2955 70p	2N4060 10p		40193 52p	TMS9981N£25					LM 317K 250p							
BC 237 7p	BD 203 70p	BSY 95A 23p	TIP 3055 70p	2N4061 10p		40194 52p	TMS9901N590p					LM 317T 98p							
BC 238 9p	BD 204 70p	BU205 140p	TIS 44 20p	2N4062 10p		40195 52p	TMS9902N550p					LM 337T 180p							
BC 239 9p	BD 205 70p	BU206 150p	TIS 90 24p	2N4063 10p		40196 52p	Z80A 4M 580p					LM 350T 395p							
BC 251 9p	BD 206 70p	BU208 140p	TIS 92 20p	2N4400 15p		40197 52p	Z80A P10500p					LM 723CN 35p							
BC 300 36p	BD 239A 40p	MJ 2500 230p	2N1613 30p	2N4401 15p		40198 52p	Z80A DMA £16					78H05 540p							
BC 301 32p	BD 239C 50p	MJ 2501 245p	2N1711 30p	2N4402 15p		40199 52p	2101-4A 350p					OPTO							
BC 302 32p	BD 240A 42p	MJ 2955 90p	2N1893 30p	2N4403 15p		40200 52p	2114-4 120p					TIL 32 55p							
BC 303 32p	BD 240C 50p	MJ 3000 210p	2N2218 25p	2N4404 15p		40201 52p	2147-70nS 600p					TIL 38 40p							
BC 304 32p	BD 241A 42p	MJ 3001 225p	2N2218A 25p	2N4405 15p		40202 52p	2147-45nS 700p					TIL 78 50p							
BC 307 10p	BD 241C 42p	MJE 340 48p	2N2219 25p	2N4406 15p		40203 52p	2176 400p					TIL 100 100p							
BC 308 10p	BD 242A 42p	MJE 350 70p	2N2219A 25p	2N4407 15p		40204 52p	4164-150nS £10					TIL 111 85p							
BC 309 10p	BD 242C 54p	MJE 370 80p	2N2221A 20p	2N4408 15p		40205 52p	4016-200nS £7					2N5777 50p							
BC 327 12p	BD 243A 55p	MJE 371 84p	2N2222 18p	2N4409 15p		40206 52p	5101LC 340p					4N25 80p							
BC 328 12p	BD 243C 68p	MJE 520 60p	2N2222A 20p	2N4410 15p		40207 52p	5101LC-1395p					4N33 128p							
BC 337 12p	BD 244A 64p	MJE 521 68p	2N2368 23p	2N4411 15p		40208 52p						4N35 150p							
BC 338 12p	BD 244C 78p	MJE 2955 80p	2N2369A 25p	2N4412 15p		40209 52p						4N37 100p							
BC 413C 10p	BF 180 30p	MJE 3055 68p	2N2484 24p	2N4413 15p		40210 52p						BPX 38 390p							
BC 414C 10p	BF 181 30p	MPSA 05 20p	2N2646 48p	2N4414 15p		40211 52p						BPX 43 340p							
BC 415C 10p	BF 182 30p	MPSA 06 20p	2N2904 22p	2N4415 15p		40212 52p						TIL 221 200p							
BC 416C 10p	BF 183 30p	MPSA 12 22p	2N2904A 23p	2N4416 15p		40213 52p						(high output clear red)							
BC 477 25p	BF 184 30p	MPSA 13 22p	2N2905 23p	2N4417 15p		40214 52p													
BC 478 23p	BF 185 30p	MPSA 42 23p	2N2906A 22p	2N4418 15p		40215 52p													
BC 479 24p	BF 194 12p	MPSA 43 23p	2N2907 23p	2N4419 15p		40216 52p													

LINEAR IC'S				CAPACITORS				DIODES				RESISTORS				HARDWARE																												
CA 3046 72p	LM 565 100p	SAA5041 £25	Electrolytic radial/axial.	Tantalum bead.	AA 119 9p	1/2 Watt Carbon film 5% E 24 series 4.7 R. 2M2 1p each.	4xTO3 mounting kits 20p	64R 78p each.	300mW rating.	5 x TO126 bushes/washers 14p	PP3 battery snaps 6p each.	10xTO220 bushes/washers 22p	4xHP7 battery holder 22p	5 x TO3P bushes/washers 14p	6xHP7 battery holder 32p	20mm panel fuseholder 32p	20mm chassis fuseholder 7p	4mm plugs 12p.	4mm sockets 20p.	4mm insulated terminals 30p.	3.5mm jack socket 15p.	3.5mm jack plug 15p.	Phono sockets 15p.	Switches: miniature toggle, SPST 60p, SPDT 68p, DPDT 78p each.	Miniature push buttons: 1A/250V push to make 16p.	push to break 23p.	Midget rotary switches, pcb terminals 2P6W, 4P3W, 3P4W 39p each.	Slide switch 1A/250V DPDT (22 x 12 x 8 mm) 16p.																
CA 3065 190p	LM 567 150p	SAA5050 £10	Value/ V price	Value/ V price	BAX 13 5p	1/4 Watt Carbon film 5% E 24 series 4.7 R. 2M2 1p each.	CP100 60 IC sockets 8, 14, and 16 pin 20 of each	440p	CP101 20 BC182/BC212 transistors, 10 of each	130p	CP102 20 BC183/BC213 transistors, 10 of each	100p	CP103 20 BC184/BC214 transistors, 10 of each	130p	CP104 20 BC549C/BC559C transistors, 10 of each	130p	CP105 20 BC500C/BC560C transistors, 10 of each	160p	CP106 100 1N914 switching diodes, 75-100V/75mA 240p	CP107 100 1N914 switching diodes, 75-100V/75mA 280p	CP108 100 1N4148 switching diodes, 75-100V/75mA 160p	CP109 500 1N4148 switching diodes, 75-100V/75mA 800p	CP110 30 1N4002 1A/400V rectifiers	680p	CP111 10 MC1458 Dual op amps (741 type)	320p	CP112 100 400mW Zeners, 4 of each 2V7 to 33V	450p	CP113 100 1.3W zeners, 4 of each 4V7 to 51V	850p	CP114 4 LF351 JFET op amps, Low noise	170p	CP115 4 LF353 JFET op amps, dual low noise	300p	CP117 50 mixed LED's 3mm/5mm/rect/ red/green/yellow	400p	CP119 100 1N4002 1A/100V rectifiers	270p	CP120 10 C106D 400V/4A thyristors	250p	CP121 10 NE555 dual timer IC's	400p	CP124 100 mixed electrolytic capacitors 10-63V/1-1000µF	£6
CA 3086 56p	LM 710 70p	SL490 300p	1µF 63¢	0.22 35¢	OA 47 7p	1/2 Watt Metal film 1% E 24 series 10R-1M 4p each.	CP125 5 LM317T 1A/TO220 variable regulators	440p	CP126 400V 4A Thyristor 28p each.	10 for 250p.	25 for 475p.	100 for £20.	300 for £54.	500 for £85.	1000 off POA.	LM317T 1A/Adj. Regulator 98p each.	10 for 880p.	25 for £21.	100 for £68.	300 for £115.	500 for £150.	1000 off POA.	1N4148 switching diodes 3p each.	100 for 160p.	500 for £6.80.	1000 for £11.50.	Larger quantities please enquire.	1N914 switching diodes 3p each.	100 for 240p.	500 for £11.00.	1000 for £17.	Larger quantities please enquire.	Generous quantity discounts available on most lines.											
CA 3089 170p	LM 711 60p	SN76690 90p	2.2 16¢	0.33 35¢	OA 90 7p	1/4 Watt Carbon film 5% E 12 series 1R-10M 2p each.	CP127 10 NE555 dual timer IC's	400p	CP128 400V 4A Thyristor 28p each.	10 for 250p.	25 for 475p.	100 for £20.	300 for £54.	500 for £85.	1000 off POA.	LM317T 1A/Adj. Regulator 98p each.	10 for 880p.	25 for £21.	100 for £68.	300 for £115.	500 for £150.	1000 off POA.	1N4148 switching diodes 3p each.	100 for 160p.	500 for £6.80.	1000 for £11.50.	Larger quantities please enquire.	1N914 switching diodes 3p each.	100 for 240p.	500 for £11.00.	1000 for £17.	Larger quantities please enquire.	Generous quantity discounts available on most lines.											
CA 3090A Q	LM 733 75p	SN76690 90p	4.7 25¢	0.68 35¢	OA 95 7p	1/4 Watt Metal film 1% E 24 series 10R-1M 4p each.	CP129 10 NE555 dual timer IC's	400p	CP129 10 NE555 dual timer IC's	400p	CP130 10 NE555 dual timer IC's	400p	CP131 10 NE555 dual timer IC's	400p	CP132 10 NE555 dual timer IC's	400p	CP133 10 NE555 dual timer IC's	400p	CP134 10 NE555 dual timer IC's	400p	CP135 10 NE555 dual timer IC's	400p	CP136 10 NE555 dual timer IC's	400p	CP137 10 NE555 dual timer IC's	400p	CP138 10 NE555 dual timer IC's	400p	CP139 10 NE555 dual timer IC's	400p	CP140 10 NE555 dual timer IC's	400p	CP141 10 NE555 dual timer IC's	400p	CP142 10 NE555 dual timer IC's	400p								
CA 3130E 95p	LM 741 14p	TBA120S 70p	10µF 10¢	10µF 15¢	OA 99 7p	1/4 Watt Metal film 1% E 24 series 10R-1M 4p each.	CP143 10 NE555 dual timer IC's	400p	CP144 10 NE555 dual timer IC's	400p	CP145 10 NE555 dual timer IC's	400p	CP146 10 NE555 dual timer IC's	400p	CP147 10 NE555 dual timer IC's	400p	CP148 10 NE555 dual timer IC's	400p	CP149 10 NE555 dual timer IC's	400p	CP150 10 NE555 dual timer IC's	400p	CP151 10 NE555 dual timer IC's	400p	CP152 10 NE555 dual timer IC's	400p	CP153 10 NE555 dual timer IC's	400p	CP154 10 NE555 dual timer IC's	400p	CP155 10 NE555 dual timer IC's	400p	CP156 10 NE555 dual timer IC's	400p	CP157 10 NE555 dual timer IC's	400p								
CA 3140E 45p	LM 747 50p	TBA120S 70p	22µF 16¢	22µF 25¢	OA 200 7p	1/4 Watt Metal film 1% E 24 series 10R-1M 4p each.	CP158 10 NE555 dual timer IC's	400p	CP159 10 NE555 dual timer IC's	400p	CP160 10 NE555 dual timer IC's	400p	CP161 10 NE555 dual timer IC's	400p	CP162 10 NE555 dual timer IC's	400p	CP163 10 NE555 dual timer IC's	400p	CP164 10 NE555 dual timer IC's	400p	CP165 10 NE555 dual timer IC's	400p	CP1																					

electronics today

INTERNATIONAL

NEXT
MONTH

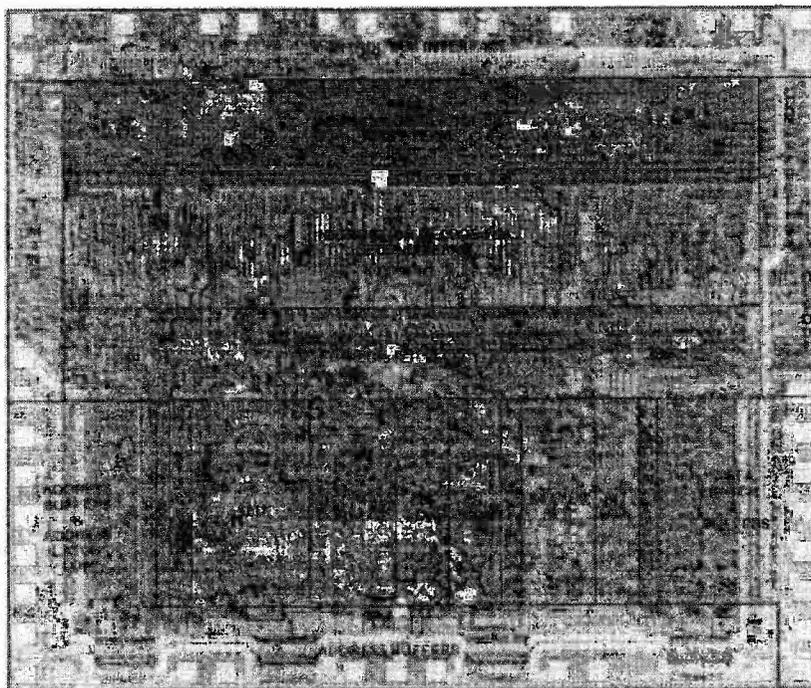


Photo of the CMOS 6502 processor courtesy of Rockwell International.

16 Channel A-to-D Board

Following on in our series of projects aimed at but not exclusively for the Mircotan, here is an A-to-D board to help you connect your computer to the outside world. If you built the D-to-A board of some months ago or would like to use your computer for control or monitoring, here is the project for you, as it will be suitable for 6502 and Z80 systems.

ZX Controlled Burglar Alarm

The idea of using a home computer to control a burglar alarm would have seemed crazy a few years ago. Laterly, however, the ZX81 seems to have become so common that many are languishing on shelves gathering dust. Well here's a job for them — controlling a buglar alarm system. The system can also be used with the Spectrum.

Modular Preamplifier

Just so that the computer freaks don't get it all their own way, here's a top-quality preamplifier that is modular in construction. The author himself describes the design as an Audio Leggo Kit, and that's just what it is. The basic unit is a motherboard into which you slot the modules that you want — so if you don't want tone controls, you don't have to have them. But unlike other preamps, you can change your mind at a later date.

Lightsaver

Problem: when light-bult filaments are cold, their resistances are very low, so when you turn on the light a very heavy current will flow momentarily: this problem is exacerbated if you just happen to turn on when the mains cycle is near its maximum voltage. Solution: buy next month's ETI and find out!

**ALL THIS AND MORE IN THE DECEMBER ETI!
RESERVE YOUR COPY NOW OR RISK MISSING OUT!**

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

If you missed
out on Breadboard
'79, '80, '81 and '82.....
Now's the time to catch up with



THE PREMIER SHOW FOR THE ELECTRONICS ENTHUSIAST!

Cunard International Exhibition Centre, Cunard Hotel,
Hammersmith, London W6

Improved Venue

We have transferred BREADBOARD to the Cunard Hotel, offering improved facilities to the visitor, including car parking and ease of access by rail, tube and car, all in a modern attractive setting. See below for our arranged reduced hotel/rail fare package to attract enthusiasts from all parts of the country.

Planned Features include

- Lectures: covering aspects of electronics and computing.
- Electronics/Computing Advice Centre.
- Demonstration: electronic organs/synthesisers.
- Holography presentation.
- Practical demonstration: 'How to produce printed circuit boards'.
- Computer Corner - 'Try before you buy'.
- Amateur Radio Action Centre.
- Computer controlled model railway competition.
- Pick of the projects - Demonstration of the best from ELECTRONICS TODAY INTERNATIONAL, HOBBY ELECTRONICS and ELECTRONICS DIGEST.
- Giant TV screen video games.
- Robotic display.

FRIDAY November 25th

10am - 6pm

SATURDAY November 26th

10am - 6pm

SUNDAY November 27th

10am - 4pm


Why not make your visit to Breadboard '83 the most enjoyable yet. At these * prices, why not bring a partner, do your Christmas shopping, have an evening on the town, see the lights, **and** have a weekend in London!

* see next page

BUILD YOUR OWN

Cortex

16 bit, 64 RAM colour computer

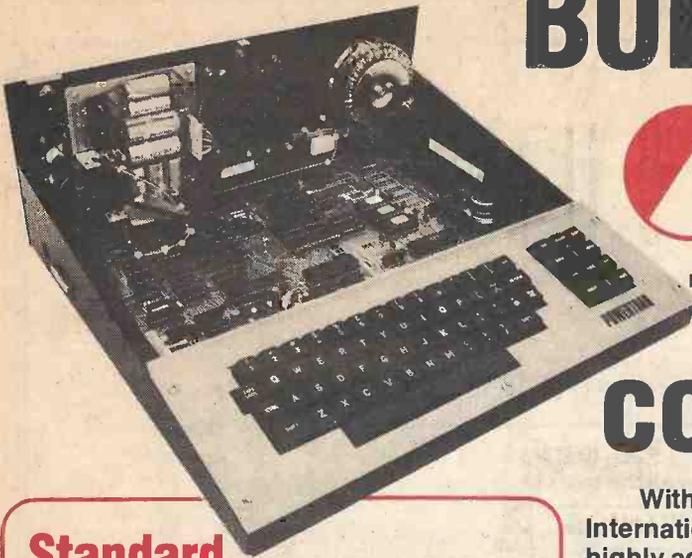

With this powerful machine (featured in Electronics Today International as a constructional project) you have access to highly advanced systems and software developed specially by MPE Ltd for the CORTEX. For business, education, R & D – or simply increasing your knowledge and understanding of computers – it beats comparably priced off-the-shelf machines hands down!

Standard features –

- High speed 24K byte extended basic interpreter
- Powerful TMS9995 16 bit microprocessor
- 48 bit floating point gives 11 digit accuracy
- High resolution (256 x 192) colour graphics
- Screen memory does not use up user memory space
- 16 colours available on the screen together in graphic mode
- Fast line drawing and point plotting basic commands
- High speed colour shape manipulation from basic
- Full textual error messages
- String and Array size limited only by memory size
- Real time clock included in basic
- Interval timing with 10mS resolution via TIC function
- Named load and save of basic or machine code programs
- Auto-run available for any program
- Powerful machine code monitor
- Assembler and Disassembler included as standard
- Auto line numbering facility
- Full renumber command
- Simple but powerful line editor
- Buffered i/o allows you to continue executing the program while still printing
- Flexible CALL statement allows linkage to machine code routines with up to 12 parameters
- Basic programs may contain spaces between key words to make programs readable without using more memory
- Over 34K bytes available for basic programs
- Extended basic includes IF-THEN-ELSE
- Supports up to 16 output devices: Screen and cassette interfaces included as standard
- Supports bit manipulation of variables from basic
- Error trapping to a basic routine included
- Basic supports Hexadecimal numbers
- Separate 16K video RAM for graphics

STATEMENTS	PRINT	TIME	RENUM	MAG	MWD	()	INT	POS	=
IF	?	WAIT	BOOT	TOF	BASE	@	LOG	COL	=
ELSE		SAVE	GRAPH	TON	COMMAN	U	SQR	MOD	=
ON		LOAD	TEXT	DIM	SIZE	#	SYS	RND	>
GOTO	1 UNIT	MOTOR	PLOT	LET	CON	FUNCTIONS	TIC	KEY	>
GOSUB	BAUD	ESCAPE	UNPLOT	DEF	CONT	ABS	SGN	OPERATORS	<
POP	CALL	NOESC	COLOUR	NEW	MON	FNA-FNZ	BIT	OR	<
REM	DATA	RANDOM	CHAR	END	BIT	ASC	CRB	LOR	<
FOR	READ	ENTER	SPRITE	CRB	TO	ATN	CRF	AND	<
NEXT	RESTOR	LIST	SHAPE	CRF	TAB	SIN	MEM	LAND	<
ERROR	RETURN	PURGE	SPUT	CRF	STEP	COS	MWD	NOT	<
INPUT	STOP	NUMBER	SGET	MEM	THEN	EXP	LEN	LNOT	<
						&	MCH	LXOR	<

Self assembly kit

£295

Ready built £395

All prices + VAT
Carriage paid



Optional extras

RS232C interface kit	£9.20	Ready built	
Floppy disc interface	£65.50	CORTEX B – Basic machine + RS232C	£410.00
Pair of 5 1/2" disc drives and hardware kit	£365.00	CORTEX C – as above + disc drives	£895.00

Full assembly instructions and 216 page user's manual.

POWERTRAN cybernetics

Portway Industrial Estate, Andover SP10 3NM. Tel: 0264 64455

To POWERTRAN CYBERNETICS, Portway Industrial Estate, Andover, Hants SP10 3NM.

Please send me _____

I enclose cheque for _____ or charge to:


Access/Barclaycard A/C No.

Name _____


Address _____


Tel. _____

PCB FOIL PATTERNS

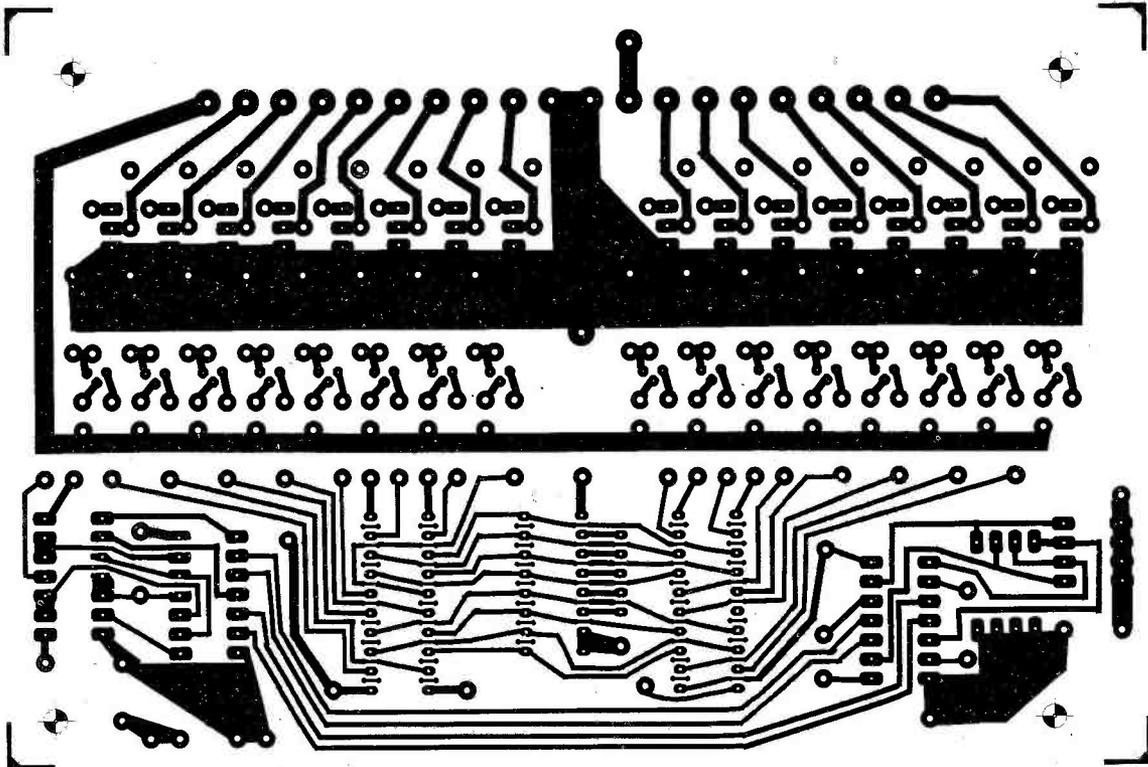


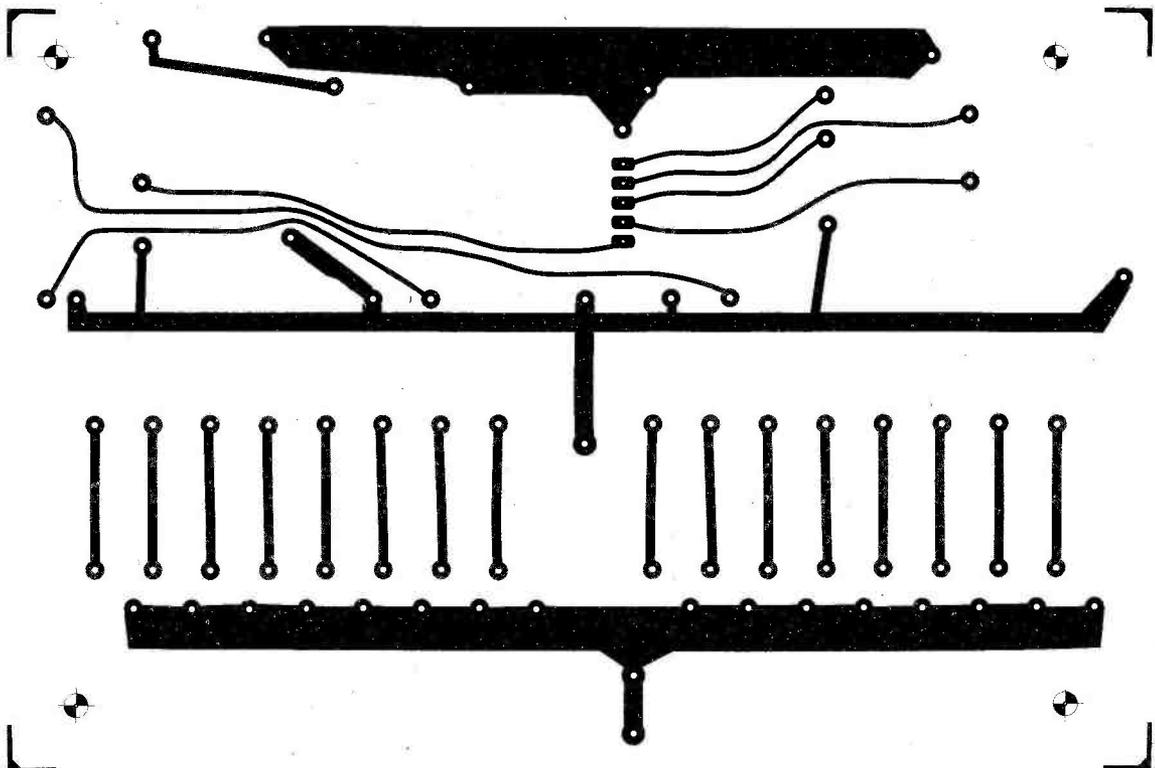Sorry! These two are foil patterns for the Output Driver, published way back in July (we've only just had space for them now).




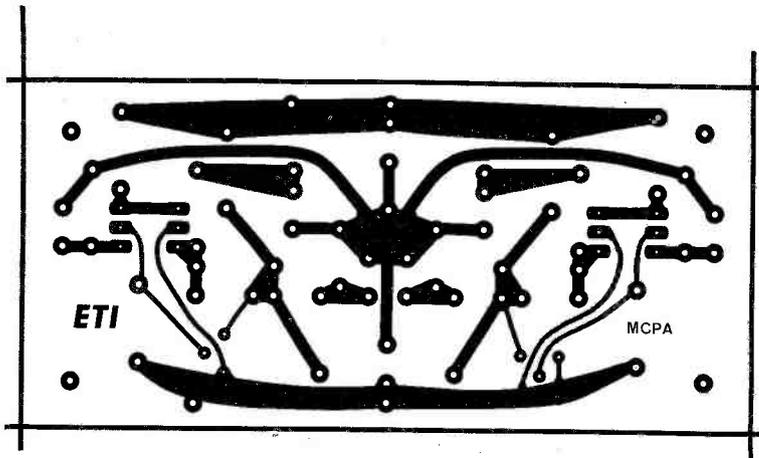



The Moving Coil Head Amplifier.

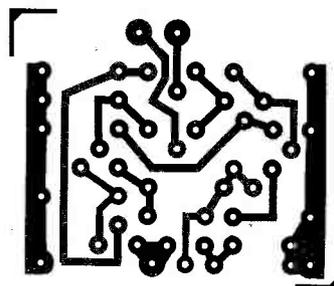

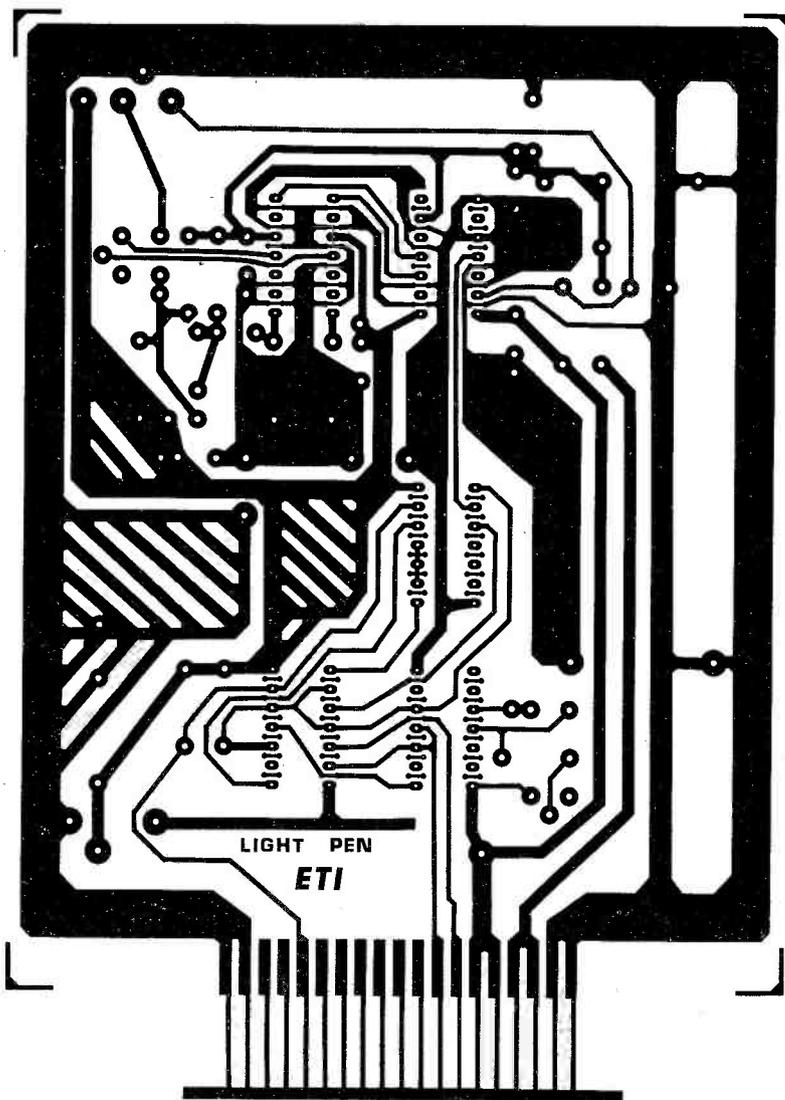
The Gain Block from Audio Design; note that this will not be available through the PCB service.




The Fast Light Pen.

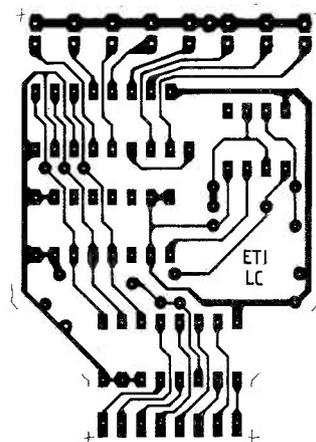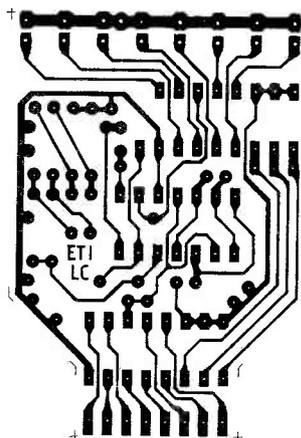


The Logic Clip.

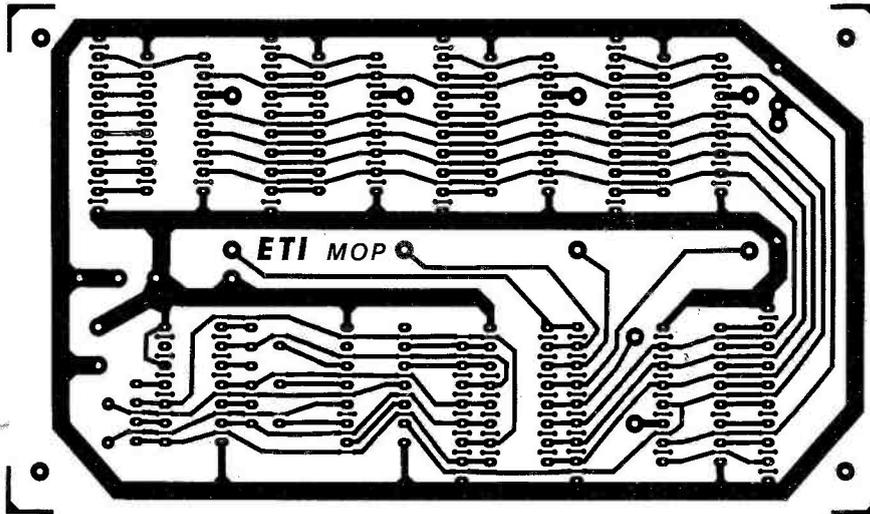


The Multiple Output Port.

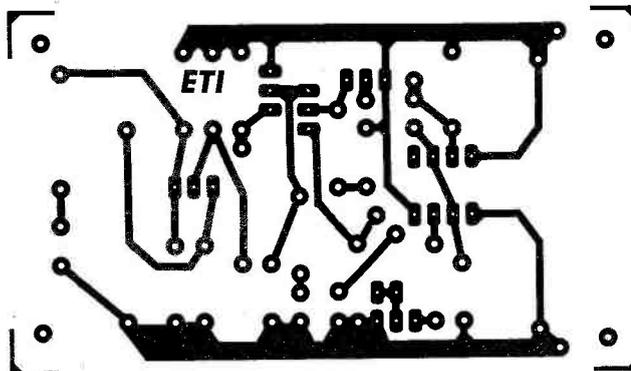


The Mini Drum Synth Module.

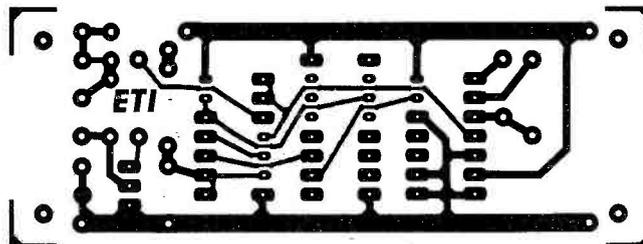


The Alarm Extender.

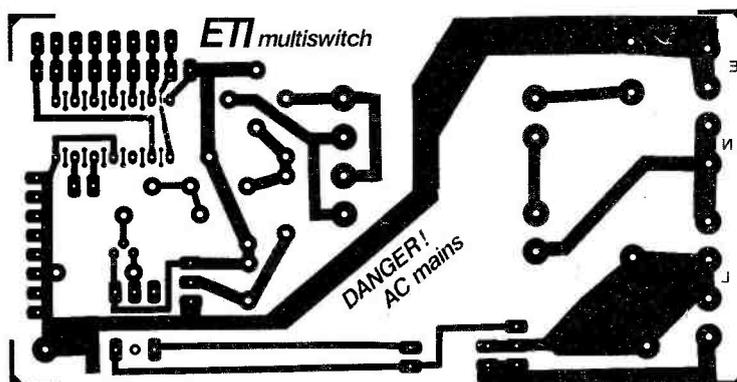


The Multiswitch.

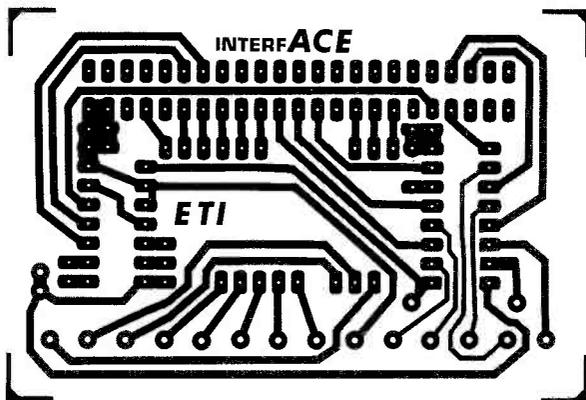

The Ace Interface.

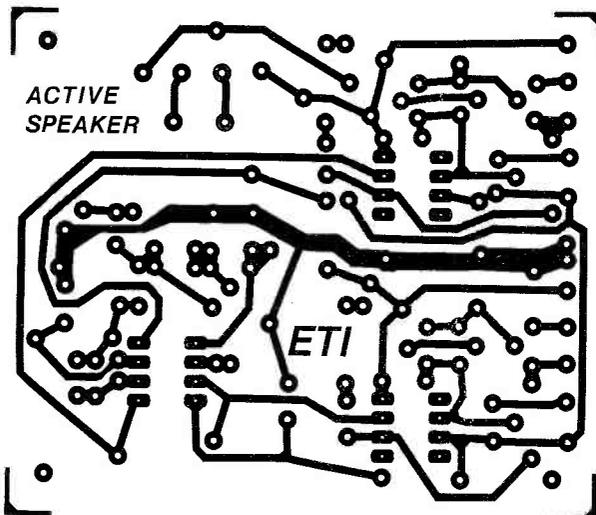

The Active Loudspeaker.

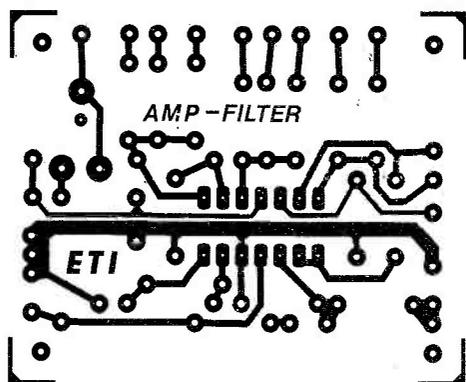

The DAC/ADC Filter Amplifier.

MAIL ORDER PROTECTION SCHEME

If you order goods from Mail Order Advertisers in this magazine and pay by post in advance of delivery, this publication will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for any one advertiser, so affected, and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures have not been complied with, at the discretion of this publication, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of reader's difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc. received as a result of answering such advertisements).

CLASSIFIED ADVERTISEMENTS ARE EXCLUDED

**It's easy
to complain
about
advertisements.**

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.
ASA Ltd, Brook House, Torrington Place, London WC1E 7HN.

Please
mention
E.T.I.
when replying
to all
adverts

Lineage:

35p per word (minimum 15 words)
Semi Display: (minimum 2 cms)
 £10.00 per single column centimetre
 Ring for information on series bookings/discounts
 All advertisements in this section must be prepaid.
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 1002
 EXT 282

Send your requirements to:
 Julie Bates,
 ASP Ltd.,
 145 Charing Cross Road,
 London WC2H 0EF

ALARMS

ALARMS

FREE BOOKLET
 on
BURGLAR ALARMS
 with
LOWEST U.K. DIY PUBLISHED PRICES
 PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
 217 WARBRECK MOOR
 AINTREE, LIVERPOOL L9 0HU

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C.TEC SECURITY, Dept E 1,
 60 Market St, Wigan WN1 1HX
 Telephone (0942) 42444

Trade Enquiries Welcome

BURGLAR ALARM EQUIPMENT: As used in the trade. JN Security Centre, 176 Sydenham Road, London SE26 5JZ. 01-778-1111. Showrooms open six days.

KITS

TIME WRONG?

MSF CLOCK IS ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD (including Weekday) output for alarm, computer etc, receives Rugby 60KHz atomic time signals, built-in antenna, 1000KHz range, £72-70.

AUDIO OSCILLATOR, 10Hz-200KHz, TTL and 0-1V sine/square outputs, £21-60. Each fun-to-build kit includes all parts, printed circuit, case, instructions, by-return postage etc, money back assurance. GET yours NOW.

CAMBRIDGE KITS
 45 (T) Old School Lane, Milton, Cambs.

WATTS NEW AT R.H.F.? V.M.O.S. F.E.T. Class A Power Amplifier Kit. Includes P.C.B., component and heatsinks. 30W R.M.S. 2 required for stereo. J-F.E.T. Preamplifier Kit, includes P.C.B., components, potentiometers and switches $\pm 15v$ power can be tapped from power amplifier. Combining F.E.T. technology and class A biasing has resulting in an amplifier of exceptional performance. For further details send S.A.E. Power Amp: £20.00. Preamplifier: £20.00. Power Supply: £18.00 (single), £30.00 (dual). ILEX Ltd, Reform Road, Maidenhead, Berks.

DIGITAL WATCH REPLACEMENT parts, batteries, displays, backlights etc. Also reports publications, charts. S.a.e. for full list Profords Conersdrive, Holmergreen Bucks. HP15 6SGD

PRINTED CIRCUITS Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

WIRES 'N CABLES

THE SCIENTIFIC WIRE COMPANY

811 Forest Road, London E17
 01-531 1568

ENAMELLED COPPER WIRE	1lb	8oz	4oz	2oz
SWG	3.63	2.09	1.10	88p
8-34	3.82	2.30	1.26	93p
42-43	5.20	2.91	2.25	1.60
44-47	8.56	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER-PLATED COPPER WIRE	14-30	9.09	5.20	1.97
TINNED COPPER WIRE	14-30	3.97	2.41	1.39
				0.94

Prices include P&P and VAT. Orders under £2 add 20p. Dealer inquiries welcome.

EQUIPMENT

ROB'S

Printed Circuit Boards to your specification from artwork through to finished board.


QUICK DELIVERY - COMPETITIVE PRICES

ERDFORD ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex
 TEL. 01-891 1923/1513 Telex. 295093

BOOKS & PUBLICATIONS

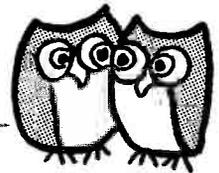PARAPHYSICS JOURNAL (Russian translation); psychotronics, kirlianography, heliophonic music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.



The Owl Series ELECTRONIC TECHNICAL DATA BOOKS

TVT(A-2) Transistor equivalent book with short form technical data covering transistors with prefix A-Z. Over 300 pages. £5.20

TVT(2N) Transistor equivalent book with short form technical data covering transistors with prefixes 2N, 2SA, 2SE, 2SD, 2SK, 3N etc. Over 400 pages. 50p

THT Thyristor data and equivalent book covering thyristors, tetrodes, trigger diodes, triacs, UJTs and PUTs. 496 pages. 520 scale drawings. £9.90

DDV/1 Part 1, European diode data and equivalent books. 500 pages. £8.00

DDV/2 Part 2 American/Japanese Diode data equivalent book £8.50

DAT 1 Part one of transistor compendium covering transistors A - BUY giving comprehensive technical data and drawings. Over 700 pages. £8.80

DAT 2 Part two of above covering transistors C-Z. Over 1100 pages. £11.00

DAT 3 Part three of above covering transistors 2N21 - 2N6735. 750 pages. £8.60

DAT 4 Part four of above covering transistors 2SA, 2SB, 2SC, 2SD, 2SJ, 2SK, 3N, 3SJ, 3SK, 4000. Over 1200 pages.

LIN 1 Linear operational amplifiers, data and comparison tables for integrated op amps and comparators. Over 400 pages. £7.00

LIN 2 Linear voltage stabilizers, data and comparison tables for integrated adjustable and non-adjustable voltage regulators. Over 350 pages. £7.00

TTL TTL digital data and equivalent book including 340 connection drawings. Over 500 pages. £8.00

All prices include postage. Please allow 14 days for reply or delivery.

TECHNICAL BOOK SERVICES LTD
 PO Box 79, Maidenhead, Berks SL6 2EG

COMPUTERS

6802 MICRO COMPUTER

This micro is designed for control applications both in industry and the home. Two models are available, PIA or VIA. Both are crystal controlled and have a 5V reg, 128 bytes of Ram, 18 in/out lines + 2 input lines. The Via also has two 16 bit timers and a shift register. The programs are held in EPROM (not included). Types 2716, 2516 and 2732 are accepted. 6862 pia kit £19.95. 6802 via kit £21.95. Assembled add £3.00. Please add 15% VAT. Discount available on 5+ qty. Orders to - Xanar, 20 Baldwin Road, King's Lynn, Norfolk PE30 4AN.

01-437 1002
 ETI CLASSIFIED

SERVICES

MENDASCOPE LTD

Repair & recalibrate
 Oscilloscopes

All makes — all models

Otter House, Weston Underwood
 Olney, Bucks MK46 5JS
 Bedford (0234) 712445
 For the complete service


REPAIRS, electrical, electronic measuring equipment. A complete service at a highly competitive price. Postage, estimates free. 14 day Turns Round. British Tele-Comm approved. Ledon Instruments Ltd, Gladstone Road, Folkstone, Kent. (0303) 57555.

YOU WANT POWER? — We got it! You specify the details of the powers supply you need — we will do the rest. R. Oliver, 2 Harkness Close, Leeming Bar, Northallerton, North Yorks. Tel: 0677 22063.

OFFERING A SERVICE?
 PHONE ASP LTD
 01-437 1002

BURGLAR Alarm Equipment. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 308920.

WHAT USE A MICRO WITHOUT A PRINTER?

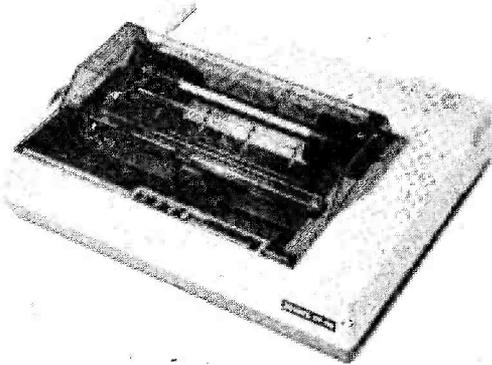

NEW A.D.M. 80 COL. DOT MATRIX WITH TRACTOR FEED. BACKED BY ONE OF BRITAIN'S LARGEST MANUFACTURERS, IT IS NOW STOCKED BY US.

INTRODUCTORY OFFER
£225 (While stocks last).

CROFTON ELECTRONICS LTD.

35 GROSVENOR ROAD, TWICKENHAM, MIDDX 01-891 1923/1513 Telex 295093

LB ELECTRONICS

FRUSTRATED EXPORT ORDER BRAND NEW & BOXED. EPSON FX80 PRINTERS £350.00 + VAT (carriage £12 tnt)

SPECIAL OFFERS (while stocks last)
Mullard 2" Red L.E.D.'s 0.06p, 7805 **38p**, 7805KC 5 Volt 1.5A **75p**, 78H05 5V 3 AMP **£3.50p**, 5K 3/4" multiturn trim pots 14 for **£2.50p**

DISC DRIVE BONANZA

PERTEC FD650 DSDD **£199 + VAT**

TEAC FD-55F 1/2 Height DSD 80 track/

40 track selectable at our new low price **£199 + VAT**

PAPST 3" Box Fan 220 volts 50hz require

1uf capacitor **£7.95 p/p £1.00**

As above but 12" 22mhz band width **£88.70 + VAT**

ASC11 coded qwerty Keyboard, manufactured by Alphanumeric (Woking UK). Model 60K brand new plus data. **£19.95p p&p £1.50**

25 WAY 'D' Types, plugs **£1.85**, sockets **£1.85** (solder tail) p&p 30p. Telephone for bulk prices.

Brand New Vero Card racks 3u 24 slot **£12.00** (callers only).

Twin 5" Cabinets with power supply **£40.00 + VAT** (providing a disc drive is purchased from us, if drives purchased elsewhere **£50.00 + VAT**).

9" Green Phosphor Monitors Brand New and Cased Composite Video Input 18mhz band width **£80 + VAT** each (carriage cost)

Textool 24 dil Zif Skt (used) **£3.95p p&p 30p**

Brand New 13" Colour monitor fully cased. Full warranty 540 x 236 pixel. RGB TTL Input plus apple Input **£220 + VAT** (carriage at cost).

BNC Lead Bonanza coax lead with BNC plug at one end, 2 metres plus **£1.00 p&p 30p** and 10 metres plus **£2.50 p&p 75p**

LB ELECTRONICS

11 HERCIES ROAD, HILLINGDON,
MIDDLESEX UB10 9 LS, ENGLAND
TEL: UXBRIDGE 55399



E.T.I. — SEPTEMBER 83 ADVERTISERS INDEX


Aitken Bros.	24
Ambit International	42
Audio Electronics	58
B K Electronics	16
Black Star	67
B.N.R&E.S	67,88
Bradley Marshall45	
Branime Marketing	67
Comtech	6
Concept Electronics	67
Cricklewood Electronics	54,55
Crimson Elektrik	38
Crofton Electronics	106
Display Electronics	90
Electronize Design.	25
Electrovalue	80
Europa Electronics	58
Frel Ltd.	46
Greenbank Electronics	85
Greenweld.	62
G.S.C.	41
Happy Memories	46
Horizon Electronics.	67
House of Instruments	62
ICS	80
ILP	38,79
Kelan Engineering.	61
L B Electronics	61
Magenta Electronics	85
Maplin.	OBC
Marco Trading.	46
Mawson Assocs	46
Microtanic.	32
Midwich Computers	51
MJL Systems.	80
Musicraft.	85
Pantehnic.	50
Parnden Electronics.	85
Phonosonics	80
Positronics.	106
Powertran	IFC,10,IBC
Qauntum Jump	85
Rapid Electronics	12
Riscomp	50
R.T.V.C.	51
Sparkrite	33
Stuarts of Reading.	61
Tape Soft	85
Technomatic	18,19
T K Electronics	14
Watford Electronics.	4,5

Low-price robots from POWERTRAN


— hydraulically powered
— microprocessor controlled

The UK-designed and manufactured range of Genesis general purpose robots provides a first-rate introduction to robotics for both education and industry. With prices from as low as £425, even the home enthusiast can aspire to his or her own robot.

Each robot in the Genesis range has a self-contained hydraulic power source operated from single phase 240 or 120v AC or from a 12v DC supply. Up to 6 independent axes are capable of simultaneous operation with positional control being provided by means of a closed-loop feedback system based on a dedicated microprocessor. Movement sequences can be programmed by means of a hand-held controller or the systems can be interfaced with an external computer via a standard RS232C link.

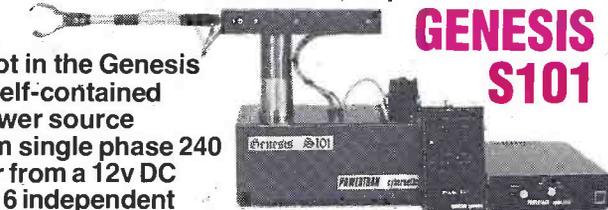


GENESIS S101

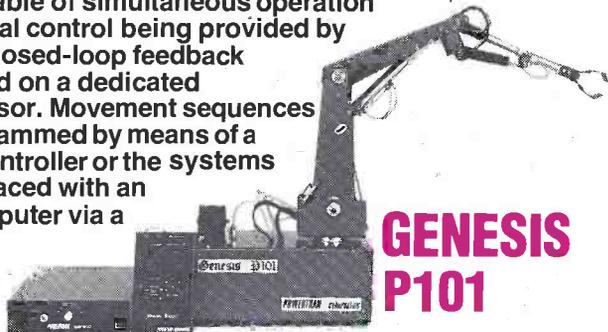


GENESIS P101

The top-of-the-range P102 has dual speed control, enhanced memory and double acting cylinders for increased torque on the wrist and arm joints. There is position interrogation via the RS232C interface, increasing the versatility of computer control and inputs are provided for machine tool interfacing.

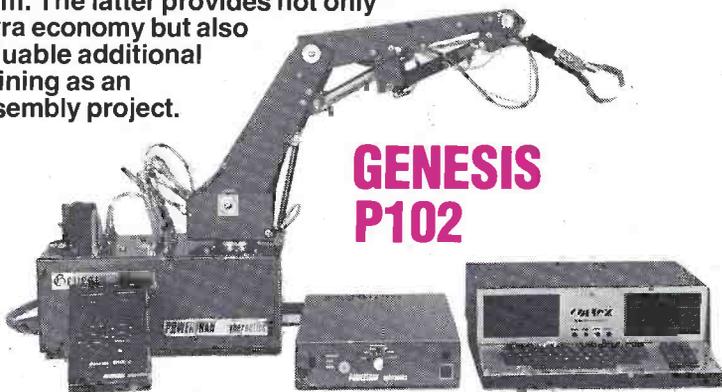All Genesis robots are available either ready-built or in kit form. The latter provides not only extra economy but also valuable additional training as an assembly project.



GENESIS P102

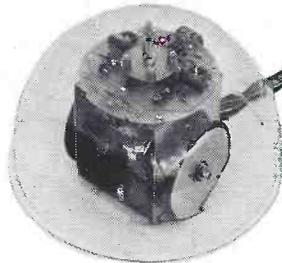

HEBOT II Turtle-type robot


For under £100, Hebot II takes programming off the VDU and into the real world. Each wheel is independently controlled by a computer, enabling the robot to perform an almost infinite number of moves. It has blinking eyes, a two-tone bleep and a solenoid-operated pen to chart its moves. Touch sensors coupled to its shell return data about its environment to the computer enabling evasive or exploratory action to be calculated.

The robot connects directly to an I/O port or, via the interface board, to the expansion bus of a ZX81 or other microcomputer.

HEBOT II

Weight 1.8kg
complete kit with assembly instructions **£85**
Interface board kit **£10**

MICROGRASP

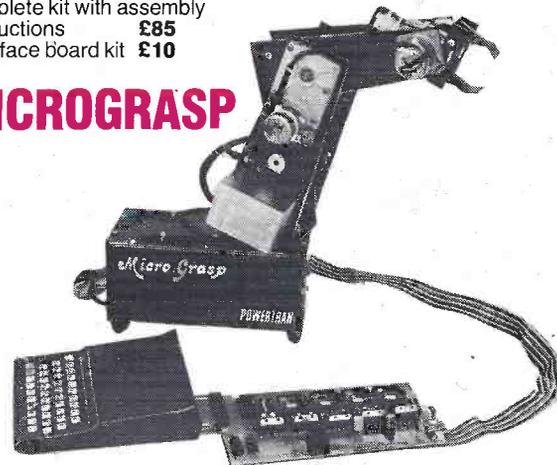

A real, programmable robot for under £200! Micrograsp has an articulated arm jointed at shoulder, elbow and wrist positions. The entire arm rotates about its base and there is a motor driven gripper. All five axes are motor driven and servo controlled, giving positive positioning. The robot can be controlled by any microcomputer with an expansion bus – the Sinclair ZX81 being particularly suitable.

MICROGRASP

Weight 8.7kg, lifting capacity 100g
Robot kit with power supply **£145.00**

Universal computer interface board kit **£48.50**
23 way edge connector **£2.50**
AX81 peripheral/RAM pack splitter board **£3.00**

GENESIS S101

Weight 29kg, lifting capacity 1.5kg
4-axis model (kit form) **£425**


5-axis model (kit form) **£475**
5-axis complete system (kit form) **£737**
5-axis complete system (ready built) **£1,450**

GENESIS P101

Weight 34kg, lifting capacity 1.8kg
6-axis model (kit form) **£675**
6-axis complete system (kit form) **£945**
6-axis complete system (ready built) **£1,650**

GENESIS P102

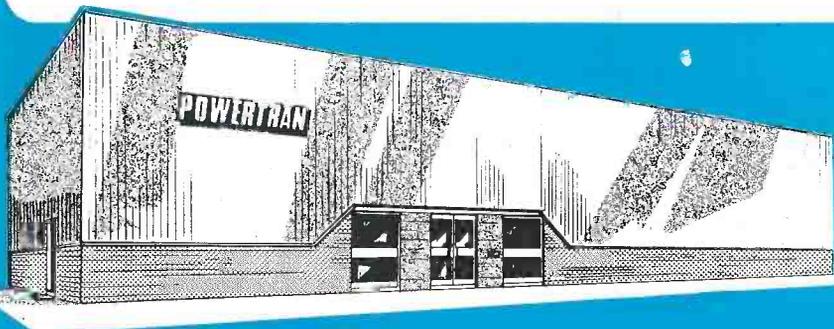Weight 36kg, lifting capacity 2kg
6-axis system (kit form) **£1175.00**
6-axis system (ready built) **£1950.00**
Powertran Cortex microcomputer self-assembly kit **£295.00**
ready-built **£395.00**



POWERTRAN cybernetics

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3ET. TEL (0264) 64455 Telex 477407

ALL PRICES ARE EXCLUSIVE OF VAT

THE NEW MAPLIN CATALOGUE FOR 84!

NOW WITH PRICES ON THE PAGE


More data, more circuits, more pictures, in the brand new 480 page Maplin catalogue. Take a look at the completely revised Semiconductor section or the new Heathkit section with descriptions and pictures of dozens of kits and educational products from digital clocks to 16-bit business computers. The much expanded computer section itself, gives details of hundreds of pieces of software for Atari, BBC, Commodore 64, Dragon, Spectrum and VIC20. In addition to all this you'll find hundreds of fascinating new items spread through the rest of the catalogue.

As always, the Maplin catalogue is tremendous value for money and now has prices on the page!

Pick up a copy at any branch of W.H. Smith or in one of our shops for just £1.35 or send £1.65 including postage to our Rayleigh address. On sale from 1st Nov 1983.

PROJECTS FOR THE HOME CONSTRUCTOR

Choose from our huge range of value-for-money projects. Projects like our Modem, Mosfet Stereo Amplifier, Home Security System, Frequency Counter and Home Computer add-on kits. Full construction details in our Project Books and brief specifications in our new catalogue. Dozens of fascinating new projects coming soon including a Keyboard for the ZX Spectrum with electronics to make all shifts, single-key operations. Full details in Project Book 9 on sale 11th November 1983. Order As XA09K. Price 70p.

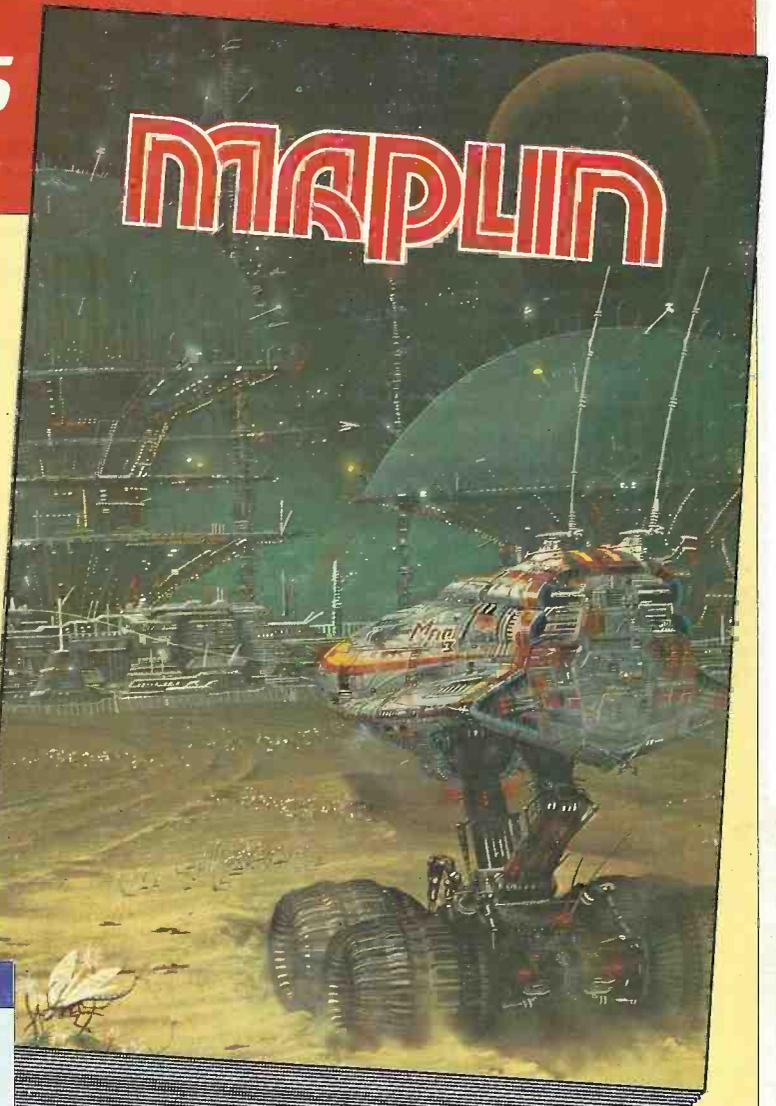

NEW MAPLIN STORE IN SOUTHAMPTON

Opening on 1st November 1983, our new south coast store is at 46-48 Bevois Valley Road, Southampton (Tel: 0703 25831). You will find our full range of components, projects and computers on sale. We are within easy reach of the city centre with good parking close by. Call in and see us soon.



Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packing. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65.

Name

Address

ET11 83

MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 ● Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926 ● 8 Oxford Road, Manchester. Tel: 061-236-0281 ● Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292 ● 282-284 London Road, Westcliff-on-Sea Essex. Tel: 0702 554000 ● *46-48 Bevois Valley Road, Southampton. Tel: 0703 25831.

*Opens 1st November 1983.

All shops closed Mondays.

All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

DIGEST

Holophony — The Continuing Saga

We received a great deal of interested enquiries over our item on Holophony back in July. At the same time, elsewhere in the press a certain amount of cynicism was expressed over the system. Well now you can judge for yourself because a record of holophonic sound effects is available.

Out on CBS (CBS recording number TA3278), the record is a 12" 45 RPM and seems to be titled Zuccarelli Holophonic by Zuccarelli Labs Ltd, and your very own intrepid editor has been giving it a listen! He writes: "I must say I was somewhat disappointed at the quality of the effects, they were nothing like as good as when played through Hugo Zuccarelli's own equipment. Also the sleeve notes are far from complete — they fail to mention that you should use single-driver speakers or small-cone headphones".


Readers will also be interested to note that the Sennheiser dummy head recordings mentioned in September's READ/WRITE are available from Hayden Laboratories Ltd, Hayden House, Chiltern Hill, Chalfont St Peter, Gerrards Cross, Bucks SL9 9UG, tel 0753 888447, at £1.15 each plus 57p postage and packing. There are just two recordings, both on 7" 45s; one is just a straight demonstration of the dummy head in a room with a commentator walking around and talking to you; the other has various sound effects, such as a jet aircraft passing overhead and a choir surrounding the dummy head.

IEEE Interface For The BBC

Cambridge Systems Technology, a new specialist computer company, has produced the first, fully operational IEEE interface for the BBC microcomputer. The CST Procyon allows users to communicate with the wide range of instruments operating to the IEEE-488 international standard, and is particularly valuable in educational or scientific establishments. It enables a BBC micro to be interfaced with high quality plotters and printers, frequency counters, voltmeters or disc drives, but may also be used to connect the "Beeb" to CBM equipment via a specially written Commodore filing system. It responds to any high level language including LISP, FORTRAN, FORTH, BASIC or APL.

The PROCYON is supplied with an 8k EPROM which fits a vacant sideways ROM socket in the BBC micro and supplies an IEEE filing system which can cope with up to 16 connected devices, accepting standard operating system file commands as well as special instructions or user-defined options. Data is transferred at up to 70k bytes of information per second, and the system is helpful and virtually fool-proof with extensive user advice facilities, error checking and visual indications of operating status.

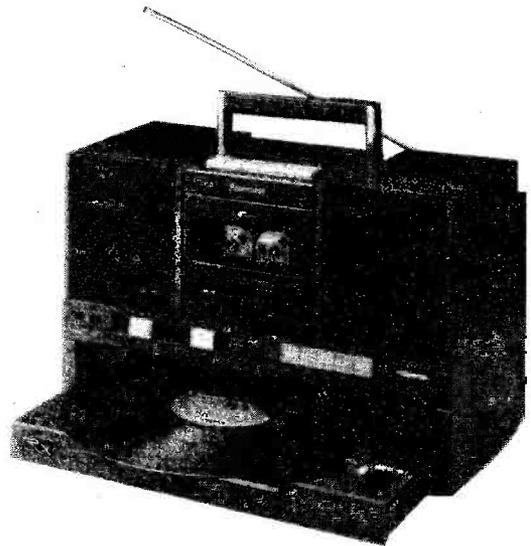A straightforward but comprehensive manual is supplied with the system, containing tutorials for beginners and advice on maximising the PROCYON's effectiveness. Cambridge Systems Technology, 30 Regent Street, Cambridge CB2 1DB, Tel (0223) 323302.



Slipped Disc?

A couple of months ago we featured two so-called portable audio units in Digest and wondered, in view of their ever increasing complexity and weight, just how long it would be before someone fitted wheels to one. Panasonic's SG-J500 does indeed have a revolving addition, but instead of being there to ease the load it just adds to it, for this truly monstrous beastie comes complete with a push-button, slide out turntable.

Part of a new range of portable audio units called 'RX Sound', the SG-J500 features an auto stop cassette deck and a three band tuner as well as the turntable and delivers four watts (whether RMS or peak is not specified) through its 'full range' speaker system. Weight is not specified, Panasonic being content to describe it as 'lightweight', and price is £133.50.

The RX-F32L from the same range does not have a turntable, presumably because they didn't have room for one after including the four, full range speakers, sur-

round effect ambience stereo, Dolby noise reduction, loudness switch, and automatic tape search system. However, for those who simply must have everything, Panasonic have produced an add-on turntable unit, the SL-N15. This is described as 'jacket sized' (we think they mean record jacket sized) but is in reality rather thicker and features linear tracking.

Last, but presumably not least since it is the most expensive item in the range, the RX-C45L. This features a five-band graphic equaliser, ten watts per channel output, Dolby noise reduction, metal tape compatibility, full auto stop, and again it can be used in conjunction with the SL-N15 turntable. There is also something in the press release about 'soft touch', but apparently this refers to the machine rather than to potential purchasers.

The RX-F32L costs £144.50 and the RX-C45L costs £177.50. Price of the SL-N15 is not given. All items should be available through Panasonic's authorised dealers nationwide.

Electronic Typewriters with RS232

National Panasonic recently launched a new range of electronic typewriters in the USA and now plan to market them in the UK from about the middle of next year. The two new machines, designated KX-E701 and KX-E708, are both available with an optional RS232C interface, thus enabling them to be used as letter quality printers.

The KX-E701 is described as an economically priced, standard electronic typewriter, while the KX-E708 is a full-feature model with a forty character display. Just what is meant by economical is not clear since no prices have been announced; indeed, when we telephoned panasonic UK to quiz them about it, they seemed unaware that the machines were due here at all! So perhaps you'll just have to make our typewriter interface after all . . .

Panasonic Business Equipment (UK) Ltd, 107-109 Whitby Road, Slough, Berkshire SL1 3DR, tel Slough 75841.

Rapid Electronics

MAIL ORDERS:
Unit 1, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
TELEPHONE ORDERS:
Colchester (0206) 36412.

ACCESS AND BARCLAYCARD WELCOME

LINEAR			
555CMOS 80	ICL7106 790	LM339 45	LM3911 120
555CMOS 150	ICL7611 95	LM348 60	LM3914 175
709 25	ICL7621 180	LM358 50	LM3915 195
748 35	ICL8038 295	LM377 170	LM13600 105
9400CJ 350	ICM721A 200	LM382 120	MC1496 68
AY-3-1270 720	ICM722A 785	LM387 120	MC1498 68
AY-3-8910 370	ICM7555 80	LM393 100	ML925 210
AY-3-8912 540	LF351 45	LM709 25	ML926 140
CA3046 60	LF353 85	LM725 35	ML927 140
CA3080 65	LF356 90	LM733 35	ML928 140
CA3089 190	LM10 360	LM733 35	ML929 140
CA3090A0 375	LM301A 25	LM747 60	MMS387A 465
CA3130E 85	LM311 70	LM747 60	NE529 225
CA3140E 36	LM318 120	LM747 60	NE531 150
CA3161E 100	LM324 40	LM747 60	NE544 205
CA319 290	LM342 100	LM747 60	NE555 160
CA3240E 110	LM335Z 125	LM3909 45	NE556 110
		LM3909 45	NE565 110

TRANSISTORS			
AC125 35	BC149 9	BC547 40	BF337-40 MPSU56 60
AC126 25	BC157 8	BC548 10	BF440 23
AC127 25	BC158 8	BC549 10	BF440 23
AC176 25	BC160 45	BC549 10	BF440 23
AC187 22	BC168C 10	BC549 10	BF440 23
AC188 22	BC169C 10	BC549 10	BF440 23
AD142 120	BC170 8	BC549 10	BF440 23
AD149 80	BC171 10	BC549 10	BF440 23
AD161 40	BC172 10	BC549 10	BF440 23
AD162 40	BC177 18	BC549 10	BF440 23
AF124 60	BC178 18	BC549 10	BF440 23
AF126 60	BC179 18	BC549 10	BF440 23
AF130 40	BC182 10	BC549 10	BF440 23
AF186 70	BC182L 8	BC549 10	BF440 23
AF239 75	BC183 10	BC549 10	BF440 23
BC109 12	BC183L 10	BC549 10	BF440 23
BC108 10	BC184 7	BC549 10	BF440 23
BC108 12	BC212 10	BC549 10	BF440 23
BC108 12	BC212L 10	BC549 10	BF440 23
BC109 12	BC213 10	BC549 10	BF440 23
BC109 12	BC213L 10	BC549 10	BF440 23
BC114 18	BC214 10	BC549 10	BF440 23
BC115 22	BC214L 8	BC549 10	BF440 23
BC117 18	BC237 8	BC549 10	BF440 23
BC119 35	BC238 14	BC549 10	BF440 23
BC137 40	BC239 12	BC549 10	BF440 23
BC139 40	BC277 14	BC549 10	BF440 23
BC140 28	BC288 14	BC549 10	BF440 23
BC141 30	BC337 14	BC549 10	BF440 23
BC142 25	BC338 14	BC549 10	BF440 23
BC143 25	BC477 30	BC549 10	BF440 23
BC147 8	BC478 30	BC549 10	BF440 23
BC148 8	BC479 30	BC549 10	BF440 23

CABLES		HARDWARE	
20 metre pack single core connecting cable ten different colours 65p		PP3 battery clips	6
Speaker cable 10p/m		Red or black crocodile clips	6
Standard screened 16p/m		Black pointer control knob	15
Twin screened 24p/m		Pr Ultrasonic transducers	350
2.5A 3 core mains 23p/m		▶12V Electronic buzzer	65
15 way rainbow ribbon 85p/m		▶12V220 Piezo transducer	75
20 way rainbow ribbon 120p/m		▶64mm 64 ohm speaker	70
10 way grey ribbon 38p/m		▶64mm 8 ohm speaker	25
20 way grey ribbon 80p/m		20mm panel fuseholder	20

REGULATORS		POTENTIOMETERS	
78L05 30	79L05 65	Rotary, Carbon track Log or Lin	
78L12 30	79L12 65	1K - 2M2, Single 32p, Stereo 500K	
78L15 30	79L15 65	Single switched 80p, Slide 60mm	
78L25 35	79L25 40	Travel single Log or Lin 5K - 50K	
78L35 35	79L35 40	63p each.	
7812 35	7912 40	Preset submin. hor. 10m ohms - 1M	
7815 35	7915 40	7p each.	
LM309K 130	LM723 35		
LM317K 270	SPECIAL OFFER!		
LM317T 120	78POS 10A +5V		
LM323K 350	only 390p each.		

DIODES		TRIACS	
BY127 12	▶1N4001 3	400V 8A	65
OA47 10	▶1N4002 5	400V 16A	95
OA90 8	▶1N4006 7	400V 4A	50
OA91 7	▶1N4007 7		
OA200 8	▶1N5401 12		
OA202 8	▶1N5404 16		
1N914 4	▶1N5408 17		
▶1N4148 3	400mWzen 6		

OPTO	
▶3mm red 7	▶5mm red 7
▶3mm green 10	▶5mm green 10
▶3mm yellow 10	▶5mm yellow 10
Clips to suit - 3p each.	
Rectangular TIL32	40
▶red 12	TIL78 40
green 17	▶TIL111 60
yellow 17	ORP12 85
▶TIL38 40	TIL100 90
2N6777 45	Dual colour 60
Seven segment displays:	
Com cathode	Com anode
DL704 0.3" 95	DL707 0.3" 95
FND500	FND507 100
0.5" 100	0.5" 100
TL3220.5" 115	TIL3210.5" 115
TL3220.5" 115	TIL3210.5" 115
LCD: 3 1/2 digit 580p.	4 digit 820p.

COMPUTER CONNECTORS		RIBBON CABLE	
ZX81 2 x 23 way edge connector		Grey Ribbon cable. Price per metre	
Wire wrap suitable for ZX81		10 way 38 34 way 150	
add-ons	150	16 way 55 40 way 170	
SPECTRUM 2 x 28 way edge connector		20 way 60 50 way 198	
add-ons	200	24 way 110 60 way 280	


RESTISORS		PCB MATERIALS	
1/4W 5% Carbon film E12 series 4.7		Alfac transfer sheets - please state type (e.g. DIL pads etc.)	45
ohm - 10M 1p each		Dalo etch resistment pen	100
1/4W 5% Carbon film E12 series 4.7		Fibre glass board 3.75 x 8"	200
ohm to 4M7 2p each		Fibre glass board 8 x 12"	800
1/4W 1% metal film E24 series 10		Ferric Chloride crystals	100
ohm - 1M 6p each.			

MIN. D CONNECTORS		SOLDERING IRONS	
9 way 15 way 25 way 37 way		Antex CS 17W Soldering iron	495
Plugs solder lugs 60p 85p 125p 170p		2.3 and 4.7mm bits to suit 85	
Right angle 120p 180p 240p 350p		CS 17Wor XS 25W element 210	
Sockets lugs 90p 130p 195p 290p		Antex XS 25W 525	
Right angle 160p 210p 290p 440p		3.3 and 4.7mm bits to suit 85	
Covers 100p 90p 100p 110p		Solder pump desoldering tool. 480	
		Spare nozzle for above 70	
		10 metres 22swg solder 100	

CMOS		VERO	
4000 10	4010 25	VEROBLOC 4	350
4001 10	4020 42	Size 0.1 matrix:	
4002 10	4030 42	2.5 x 1 22	
4006 10	4042 45	2.5 x 3.75 75	
4007 14	4022 45	2.5 x 5 85	
4008 14	4022 45	3.75 x 5 95	
4008 36	4024 33	VQ boards	160
4009 24	4025 12	Veropins per 100:	
4010 24	4026 75	Single sided 50	
4011 10	4027 20	Double sided 60	
4012 15	4028 40	Spot face cutter 105	
4013 20	4029 45	Pin insertion tool 162	
4014 45	4030 14	Wiring pen and spool 310	
4015 40	4031 125	Spare spool 75p	6

LS TTL		MICRO	
LS00 11	LS26 14	8118PS 320	8952 240
LS01 11	LS27 12	8800CPU 325	8228 220
LS02 12	LS30 15	8800CPU 250	8251 250
LS03 12	LS32 18	6522 VIA 295	6880 100
LS04 14	LS37 14	6532 570	81LS95 85
LS05 12	LS38 15	6551 ACIA 650	81LS96 85
LS08 14	LS40 13	81LS96 85	8259 390
LS09 12	LS42 28	81LS96 85	8259 390
LS10 14	LS47 35	81LS96 85	8259 390
LS11 12	LS48 45	81LS96 85	8259 390
LS12 12	LS51 14	81LS96 85	8259 390
LS13 19	LS55 14	81LS96 85	8259 390
LS14 30	LS73 20	81LS96 85	8259 390
LS15 12	LS74 20	81LS96 85	8259 390

SOCKETS		COMPONENT KITS	
8 pin	6p	214L2 99	8800 CPU 220
14 pin	35p	2716 225	8800 CPU 250
16 pin	42p	2832 290	8800 CPU 620
18 pin	12p	2732 290	8800 CPU 620
20 pin	13p	2764 425	6821 PIA 115
22 pin	16p	4116P20 85	6840 360
24 pin	18p	5101L-1 220	6850 110
28 pin	25p		
40 pin	28p		
Soldercon pins 60P/100			

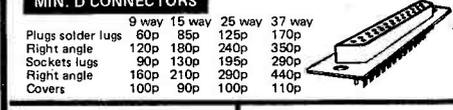

CONNECTORS
DIN Plug Skt Jack Plug Skt
2 pin 9p 9p 2.5mm 10p 10p
3 pin 12p 10p 3.5mm 9p 9p
5 pin 13p 11p Standard 16p 20p
Phono 10p 12p Stereo 24p 25p
1mm 12p 13p 4mm 18p 17p
UHF (CB) Connectors
PL259 Plug 40p. Reducer 14p.
SO239 square chassis skt 38p.
SO239S round chassis skt 40p.
IEC 3 pin 250V/6A.
Plug chassis mounting 38p
Socket free hanging 60p
Socket with 2m lead 120p

SWITCHES
Submit toggle:
SPST 55p, SPDT 60p, DPDT 65p.
Miniature toggle:
SPDT 80p, SPDT centre off 90p,
DPDT 90p, DPDT centre off 100p.
Standard toggle:
SPST 35p, DPDT 48p
Miniature DPDT slide 12p.
Push to make 14p.
Push to break 22p.
Rotary type adjustable stop.
1F12W, 2P2W, 3P4W all 55p each.
DIL switches:
4SPST 80p 6 SPST 80p, 8SPST 100p.

SCRs
▶C106D 30
400V 8A 70
400V 12A 95

VOICE SYNTHESISER!
Now your computer can talk.
The GI SP0256 speech processor is able through stored program to synthesize speech. Allophone (extended phoneme) system gives unlimited vocabulary.
Easily interfaced with any digital system; TTL compatible signals are used to select the allophone.
SP0256 925p. Data: 80p.


MICRO
8118PS 320 8952 240 8228 220
8800CPU 325 8251 250
6522 VIA 295 6880 100 8253 390
6532 570 81LS95 85 8255 225
6551 ACIA 650 81LS96 85 8259 390
214L2 99 8800 CPU 220 81LS97 85 MC1488 55
2716 225 8800 CPU 250 8080A 250 MC1488 55
2832 290 8800 CPU 620 8085AC 340 Z80A CPU 290
2732 290 8800 CPU 620 8156 350 Z80A CPU 260
2764 425 6821 PIA 115 8212 110 Z80ACTC 260
4116P20 85 6840 360 8216 100 Z80ASIO 900
5101L-1 220 6850 110 8224 120 Z80ADMA 1150

SOCKETS
Low profile Wire-wrap
8 pin 6p 25p
14 pin 35p 35p
16 pin 42p 42p
18 pin 12p 52p
20 pin 13p 60p
22 pin 16p 70p
24 pin 18p 70p
28 pin 25p 80p
40 pin 28p 88p
Soldercon pins 60P/100

COMPONENT KITS
An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. 1/4W 5% Resistor kit. Contains 10 of each value from 4.7 ohms to 1M (total of 650 resistors) 530
Ceramic Cap. kit. 5 of each value - 22p to 0.01u (135 caps) 370
Polyester Cap. kit. 5 of each value from 0.01 to 1uF (65 caps) 575
Preset kit. Contains 5 of each value from 100 ohms to 1M (total of 65 presets) 425
Nut and Bolt kit (total 300 items): 180p
25 6BA 1/4" bolts 50 6BA washers 50 6BA nuts
25 6BA 1/4" bolts 25 4BA 1/4" bolts 50 6BA washers
50 6BA nuts

The Rapid Guarantee
★ Same day despatch ★ Competitive prices
★ Top quality components ★ In-depth stocks

ORDERING INFO. All components brand new and full specification. All prices exclude VAT. Please add to total order. Please add 50p carriage to all orders under £15 in value. Send cheque/P.O. or Access/Visa number with order. Our detailed catalogue costs 45p (free with orders over £10). Callers most welcome. Telephone orders welcome with Access or Visa. Official orders accepted from Colleges, Schools, etc. . . . Callers most welcome, we are open Monday to Friday.

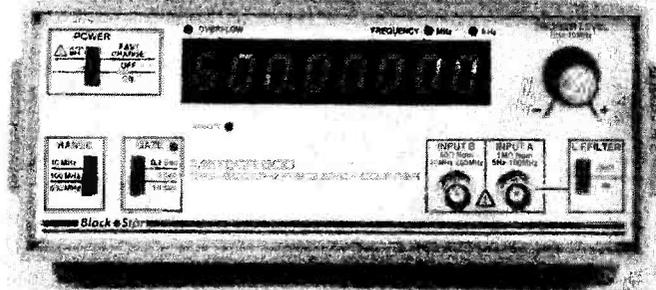

Low Cost DFM

The Meteor 600 is the first in a series of digital frequency counters announced by Black Star Ltd. It has a frequency measurement range of 2 Hz-700 MHz, sensitivity of 25mV at 600 MHz and resolution down to 0.1 Hz, and also features 8 x 1/2" bright LED displays, 3 gate times, 2 inputs, a trigger level control and an integral low pass filter. The counter is housed in an attractive,

sturdy, custom-moulded A.B.S. case with tilt stand. It can be operated from rechargeable batteries or mains and is supplied complete with a mains adaptor/charger and a comprehensive instruction manual. A wide range of optional accessories is also available.

The Meteor 600 costs £115 plus VAT and is available from Black Star Ltd, 9A Crown Street, St. Ives, Huntingdon, Cambs. PE17 4EB, tel. 0480-62440.

Hello, Computer Speaking . . .

If your micro is feeling lonely, why not introduce it to a wider circle of friends with the new UDS V.21 LP modem from Codex (UK) Ltd? This 300 baud stand alone machine comes in either manual or automatic answering versions and is approved for connection to the Public Switched Telephone Network, from which it draws its power. It stands only one inch high and is designed to fit neatly underneath the telephone. With a selling price of around £200 for the manual version and £250 for the automatic model, Codex anticipate a lot of interest from the small business and hobbyist markets, and are currently seeking distributors for the product to whom they are prepared to offer generous quantity discounts. Codex (UK) Ltd, 114/116 Thornton Road, Surrey CR4 6XB, tel. 01-689 2101.

Sculptured Circuits

Dowty Circuits Ltd have signed an agreement with Advanced Circuit Technology of America giving them exclusive rights to manufacture what they call sculptured circuits in this country. This patented technology permits the physical carving of copper into various shapes by a chemical milling process, allowing the thickness of a piece of copper to be varied along its length. In this way, connector systems can be fabricated in which each conductor has both its terminal pins and flexible lead made from a single continuous piece of copper, thereby increasing reliability, reducing series resistance, and reducing assembly costs, time, etc. Dowty anticipate the production of a wide range of standard and custom designs with various conductor diameters, pin densities, finishes and terminations. Dowty Circuits Ltd, Industrial Estate, Terminus Road, Chichester, West Sussex PO19 2UA, Tel 0234 784516.

Shorts


- ITT Cannon have introduced the AXR audio connector range, a successor to their industry standard XLR range, which features easier assembly, greater RFI protection, improved cable clamping, and lower cost. The AXR has from three to seven contacts plus a mains version, comes in sixteen shell styles, and is available from PSP Electronics Ltd, Unit 2, 2 Bilton Road, Perivale, Greenford, Middlesex UB6 7DX.
- 3M have introduced a new Scotchlok connector which may be attached to an existing cable in one action using a pair of pliers and which provides a fully insulated tapping point for a standard 1/4" blade connector. Also new is an inline fuseholder which assembles onto wire ends without prior stripping, again with only one action. Electro-Products Group, 3M United Kingdom PLC, 3M House, PO Box 1, Bracknell, Berkshire RG12 1JU, tel 0344 58755.
- Data I/O has published a thirty-two page booklet entitled 'Programmable Logic — A Basic Guide for the Designer'. It covers all aspects of design, programming and testing including a worked example, and is available free-of-charge from Microsystem Services, PO Box 37, Lincoln Road, Cressex Industrial Estate, High Wycombe, Bucks HP12 3XJ, tel 0494 41661.
- Och Aye, hoots mon, and the rest! Scottish ETI readers should note that the first Scottish Home Computer and Electronics Show is coming and will feature micros, software, CB, ham, hi-fi and video equipment. Venue is the Anderston Centre in Glasgow and the whole caledonian caboodle runs from the 11th to the 13th November. Details from Ann Lowe, Trade Exhibitions Scotland, 53/55 Commissioner Street, Crieff, Perthshire PH7 4DA, tel 0764 - 4204.
- CHO-JAC is a bonded foil and polymer sheath designed to protect ribbon cables against electromagnetic and radio frequency interference. Available in sizes to fit 16, 26, 34, 40, 50, and 60 way cables, it is claimed to give a shielding effectiveness of up to 65 db and is supplied in 100 ft rolls. Chomerics Europe, Chomerics House, 14-18 Church Street, Slough, Berkshire SL1 1PZ, tel. (0753) 822242.
- The EX 110 is a new, plunger type, electrically heated desoldering tool which weighs four ounces and is designed to be operated for extended periods without tiring the operator. It features a cassette system which eases removal of the accumulated solder, operates from the mains, has a bit temperature of 420°C, and costs about £18 plus VAT. Nietronix Ltd, West End Trading Estate, Blackfriars Road, Nailsea, Bristol BS19 2DJ, tel 0272 856697.
- We are often asked by readers to recommend someone who will repair and re-calibrate test meters, etc, and usually have to admit defeat. PIL will not, as far as we know, repair meters but they will re-calibrate them and what's more they'll do it to Defence Standard 05-24. Ring 01-639 0155 for details.
- Cambridge Microelectronics have introduced a 2516, 2532, 2716 and 2732 EPROM programmer for the ZX81. ROM-81 provides all the standard programming functions, requires four PP3 batteries, is housed in a neat ABS case which plugs into the back of the ZX81 and has a further expansion adaptor, and comes complete with a taped control program and user notes. Price is £19.95 plus VAT from Cambridge Microelectronics Ltd, 1 Milton Road, Cambridge CB4 1UY, tel 0223 - 314814.
- They may not be giving computers away with breakfast cereals yet but they are giving them with courses. Prophet Systems Ltd are running one and two day training courses in computer assisted business modelling at their Jacobean manor at Polebrook, Peterborough, and are giving away a Prophet II microcomputer to each participant. Polebrook Management Systems Ltd, Polebrook Hall, Peterborough PE8 5LN; tel 0832 72052.
- The TG-3 is a hand-held, battery operated television test generator with a direct UHF output to suit a standard 625 line set. It provides 2 MHz lines for focus check, grating pattern, dot pattern, and plain white raster, and costs £46 inclusive from Video Techniques, 101 Derby Street, Bolton, Lancashire BL3 6HH, tel 0204 - 26916.
- OK Industries new FG-201 function generator provides highly accurate sine, square and triangle waveforms from 1 Hz to 1 MHz into 50 ohms and offers both AM and FM modulation. There is also a 5 ohm output for sine and triangle while square wave may be used simultaneously with either as a trigger. The FG201 costs £230 plus VAT and is manufactured by OK Industries UK Ltd, Dutton Lane, Eastleigh, Hampshire, tel 0703-610944.
- Industrialists and Researchers are invited to the First International Conference on Lasers in Manufacturing to be held at the Brighton Metropole from 1st-3rd November. Hewlett-Packard, Rolls-Royce, and BL will be among those contributing to the conference, which aims both to highlight recent experience and to consider the future of the laser in industry. Details from The Conference Director, LIM-1, IFS (Conferences) Ltd, 35-39 High Street, Kempston, Bedford MK42 7BT, tel 0234 853605.

Plug-Together Amplifier System

If building a hi-fi amplifier from scratch sounds a bit too much like hard work, why not cheat and buy a new Boothroyd Stuart Meridian Component Amplifier? With this system you can buy just those modules you want and simply plug them together to produce an amplifier system tailored precisely to your requirements.

The Meridian Component Amplifier System consists of a number of modules of matching appearance which plug together to form a neat, slimline unit. Two coin-slot headed screws further secure the units to ensure a good connection and to prevent bits falling off when you move it around! The basic unit is a stereo power amplifier with a switch-mode power supply operating at 40 kHz. The amplifiers are conservatively rated at thirty-five watts RMS each and the power supply ensures that high power transients are accommodated without straining. Although built and sold as a single unit, this block is visually divided into four adjacent modules so as to match the appearance of the rest of the system. A slim module, half the width of the apparent power modules, contains the stereo preamplifier and volume control, and this plugs onto the right hand end of the basic block. Up to twenty (yes, twenty) input modules can be added between the power and preamp modules catering for magnetic and moving coil pickups, tape, etc, and just in case this leaves you with a monster several feet long there is also a splitter module which allows you to stack one row of modules on top of another. Other modules either already available or soon to be introduced include tone controls, an FM stereo tuner, and a power supply for the preamp alone which allows you to dispense with the main power block when driving active loudspeakers or a separate power amplifier.

Although no specifications were included in the press release, Boothroyd Stuart assure us that performance in all areas is to a very high standard and that distortion in particular is so low as to be almost immeasurable. The basic unit with preamplifier and one (disc) input should sell for about £375 including VAT. Boothroyd Stuart Ltd, 13 Clifton Road, Huntingdon, Cambridge PE18 7EJ, tel 0480 57339.

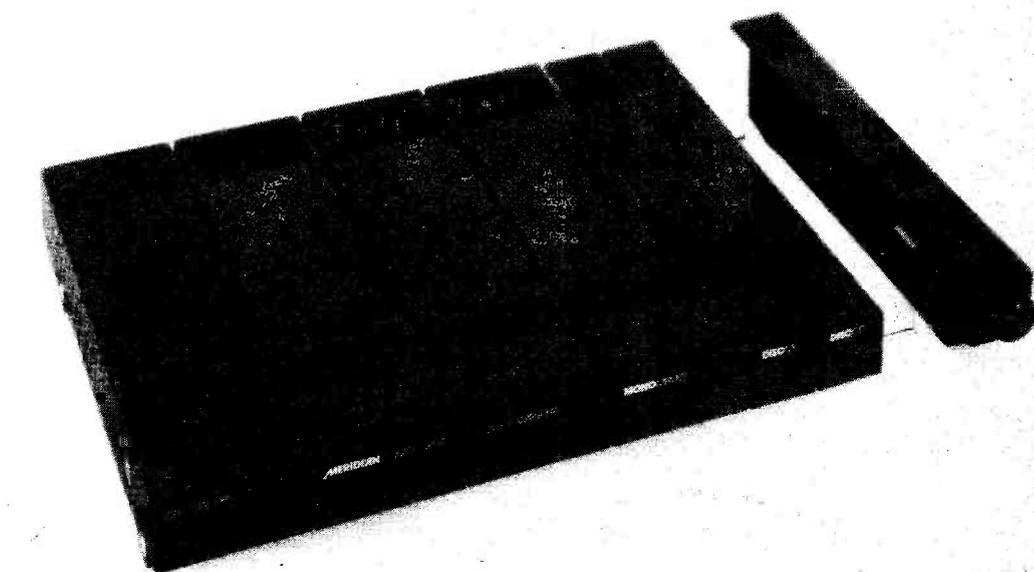

Cool, Calm and Connected

Pye Electro Devices (PED) Ltd have introduced a series of fans which use a piezoelectric system rather than the conventional magnetic system. The Series 13 module A and B cooling fans have almost no moving parts and are intended for use as spot cooling devices in solid state systems.

Piezoelectric materials can be made to change shape when a voltage is applied to them. In the new fans, two flexible piezo ceramic elements are laminated to a flexible metal strip such that, when a voltage is applied, one side expands and the other contracts, causing the metal strip to bend. Two such fan blades, matched and fed with alternating voltages such that they move in phase quadrature, produce a highly focussed stream of air. PED claim that such a system offers near infinite life since there are so few moving parts. Other advantages include very low noise output, a complete absence of electro-magnetic and radio-frequency interference, no starting surge, and very low power consumption. Versions are available for use on 115 V AC 60 Hz, 220/240 V AC 50 Hz, and DC supplies from 5 to 12 V and maximum dimensions are 71 mm x 55 mm x 17mm. Pye Electro Devices Ltd, Relay and Solenoid Division, Exning Road, Newmarket, Suffolk CB8 0AX. Tel (0638) 665161.

Microtan And Microtutor Are Alive And Well . . .

And living in Dulwich. A Microtanic, formerly purely a software house, have bought all rights to the Microtan and to the Microtutor. Not only that but they've launched a magazine for Microtan owners, Microtan World (Why are we advertising competitors? — Ed).


To do this, Microtanic have had to overcome enormous problems and they seem to be coping admirably despite it all. To ETI, it comes as a relief to see this excellent computer being kept alive, as it is truly an experimenter's system, as a casual perusal of some of the recent issues of ETI will testify.

Readers should direct their enquiries to Microtanic Computer Systems Ltd, 16 Upland Road, Dulwich, London SE22, tel 01-693 1137.

Hi-Fi VHS Announced

Ten Japanese companies have collaborated to produce a common standard for a hi-fi VHS video cassette recorder. Akai, Canon, Clarion, Hitachi, JVC, Matsushita, Mitsubishi, Orion, Sharp, and Tokyo Sanyo will produce machines to the new standard and a number of companies are expected to produce compatible videotapes with hi-fi stereo sound.

In the existing VHS video system, video signals are recorded and played back by rotary heads while fixed heads are used for audio signals. In the new system, two additional rotary heads are provided exclusively for the audio signals. It is claimed that this, plus the use of frequency modulated 1.3 and 1.7 MHz carriers, produces a marked improvement in dynamic range, distortion level, and wow and flutter. Other features include a newly-developed noise reduction system and the ability to use existing software on the new machines and vice-versa, although no details are given on how this is achieved.

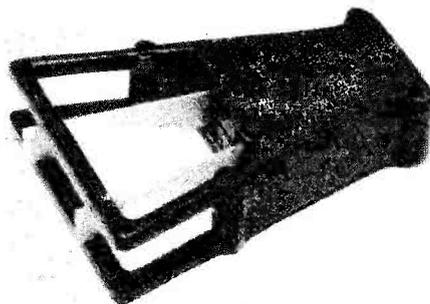




MULLARD SPEAKER KITS

Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm
Price £14.90 each + £2.00 P & P.
5" 30W system — recommended cabinet size 160 x 175 x 295mm
Price £13.90 each + £1.50 P & P.

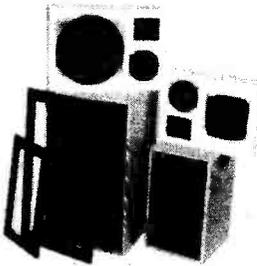
Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc.
8" system cabinet kit £8.00 each + £2.50 P & P.
5" system cabinet kit £7.00 each + £2.00 P & P.



STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.


Features: Three digit tape counter. Autostop. Six piano type keys: record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 1 1/4". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.
Price £26.70 + £2.50 postage and packing.
Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

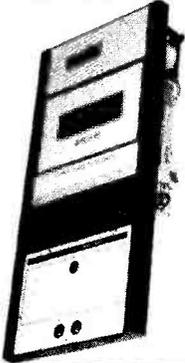

LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See 'Photo'). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Prices.**

15" 100 watt R.M.S. Impedance 8 ohms. 50 oz magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P
12" 100 watt R.M.S. Impedance 8 ohms. 50 oz magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille Price: £9.99 each. P&P £1.50.

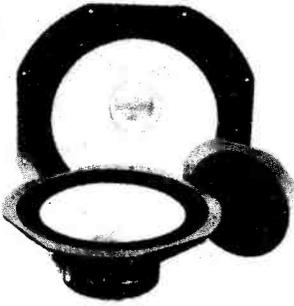


12" 85 watt R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price: £23.00 + £3 carriage.

12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £23 + £3 carriage.
15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.

PIEZO ELECTRIC TWEETERS - MOTOROLA

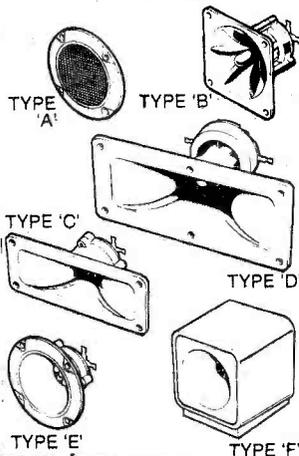Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.29 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.99 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each
P&P 20p ea. (or SAE for Piezo leaflets).



OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each

£90 per pair

Carriage: £5 each £7 per pair

BK ELECTRONICS

Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader

PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt)
Price: £7.99p

DIGITAL THERMOMETER -9.9°C to +99.9°C. LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled. professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm (9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.




3 watt FM Transmitter


BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each. £2.50 P&P

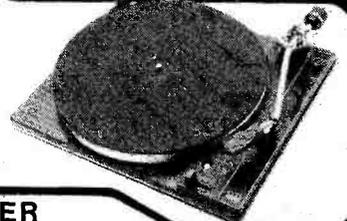

OMP POWER AMPLIFIER MODULE

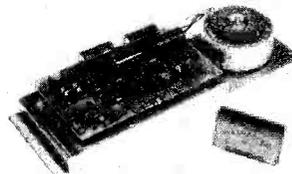

New model.
Improved-specification

MOSFET versions available up to 300W. R.M.S.

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.
SPECIFICATION
Output Power:— 110 watts R.M.S.
Loads:— Open and short circuit proof 4/16 ohms.
Frequency Response:— 15Hz - 30KHz -3dB. T.H.D.:— 0.01%.
S.N.R. (Unweighted):— -118dB ±3.5dB.
Sensitivity for Max Output:— 500mV @ 10K. Size:— 360 x 115 x 72 mm Price:— £31.99 + £2.00 P&P. Vu Meter Price:— £7.00 + 50p P&P.

HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.
Indoor alarm — Electronic swept freq. siren. 104dB output.

Outdoor Alarm — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £128 Usual price £228.85
BKE's PRICE £99.p&p£4

S.A.E. for colour brochure.




MIXERS Disco

OMP PRO MIX MONO

OMP PROMIX MONO DISCO MIXER (As illustrated), 4 Inputs, -2 Mag. Disc. 1 Aux. plus Mic. with override. Active bass and treble tone conts. Individual level controls plus master volume. Monitor output (head- phone) for all inputs. Output: 775mV Supply 240Vac. Size: 19" x 5 1/2" x 2 1/2". Price: £49.99 + £2.00 P&P

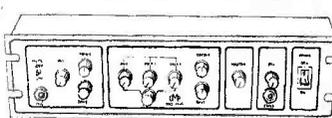ALSO STEREO DISCO MIXER with 7 band graphic. Vu display. All facilities. £99.99 + £2.00 P&P




B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR



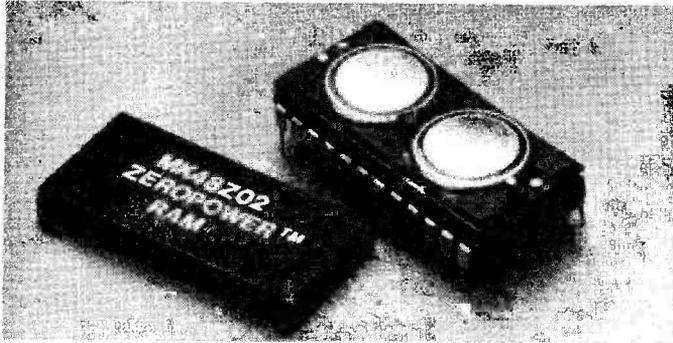★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★ All items packed where applicable in special energy absorbing PU foam. ★ Please phone 0702 527572 ★




Non-Volatile Static RAM

It seems such an obvious idea that we are amazed no one has tried it before! In order to give their new 16K static RAM the retention characteristics of a ROM, Mostek Corporation have included a lithium energy source within the IC package itself.

Designated the MK48Z02 Zeropower RAM, the new device uses HCMOS technology to ensure low current drain, resulting in a minimum operating life of five years (at 25°C) on its internal lithium cell. It is organised as 8 x 2K, comes in a standard 24-pin DIP package, and has the same pin-out as, for example, the

2716 EPROM, allowing it to directly replace 16K static RAMs in many applications. No additional circuitry is required for interfacing to microprocessors since access time, read cycle, and write cycle are all below 250 nS and require only a single +5V supply. Features include an automatic write protection circuit which comes into operation whenever Vcc drops below 4.5 volts, thus preventing inadvertent loss of data on power up and power down, and, as with other static RAMs, there is no limit on the number of write cycles that can be performed.

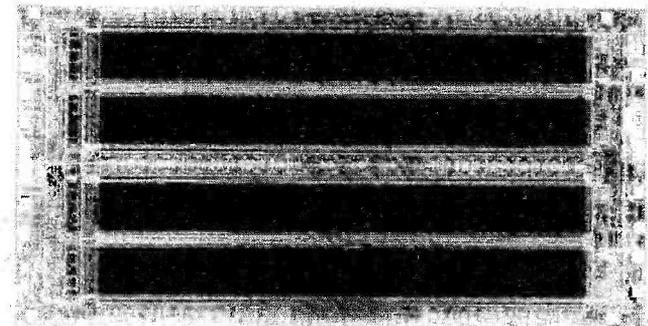The MK48Z02 Zeropower RAM is available in 200 nS and 250 nS access time versions, and one-off prices are around £43 and £39 respectively. Mostek UK Ltd, 1 Valley Drive, Kingsbury Road, London NW9, tel. 01-204 9322.



Third-Generation 64K RAM

United Technologies' Mostek Corporation claim to have produced a third-generation 64K dynamic RAM which provides access times of 80 ns to 120 ns. The MK45H64 uses the latest Mostek scaled NMOS process technology known as the LD3 process, featuring silicon gate, double-level poly interconnect, 1.5µ channel lengths and 200 Å capacitor oxide for maximum critical charge. It can be used in virtually any on-line storage memory system, including mainframe computers, minicomputers, microcomputers, and with microprocessors, and in applications such as video and

graphics memory, buffer memory and terminal memory.

Multiplexed address inputs allow the MK45H64 64K dynamic RAM to be packaged in a standard 16-pin DIP with only 15 pins required for basic functionality. It is designed to be compatible with the JEDEC standards for 64K x 1 dynamic RAMs, and features very fast page mode cycle times (equal to RAS access) and has TRAS (max) specified at 40 µS, allowing an entire page of 256 bits to be accessed within a single RAS cycle. The device also features a hidden refresh cycle which enables the component's output to be held valid for up to 40µS by holding CAS active low, allowing refresh cycles to be performed while holding data valid from a previous cycle.

Mostek U.K. Ltd, 1 Valley Drive, Kingsbury Road, London NW9, tel 01-204 9322.

Stepper Motor Control/Drive IC

New from RIFA is a monolithic IC designed for controlling and driving bipolar stepper motors, or the direct control of d.c. motors, solenoids or relays.

The PBL 3717 is a 16-pin monolithic bipolar IC that includes LS-TTL-microprocessor compatible logic inputs, three addressable current comparators, and a full H-bridge output stage with built-in protection diodes. Configured with one winding of a bipolar stepper motor, the PBL 3717 requires very few external components to form a complete control and drive stage within LS-TTL or microprocessor-based stepper motor systems. It is

capable of either half- or full-step modes, and offers a range of current control from 5mA to 500mA continuous without a heat sink, up to 800mA with a heat sink, and 1.0 A peak. Current levels may be either selected in steps or continuously varied, and supply voltage range is from 10V to 45V with a 15V reference input. It will accept analogue or digital logic inputs of 6V at 10mA, for which the ideal rise and fall times are stated as 2.0µs.

Though designed principally for stepper motor applications, the PBL 3717 may alternatively be used to drive conventional d.c. motors by the appropriate adjustment of its input signals.

The operational temperature range of the PBL 3717 is 0 to +70°C, and it is produced in the industry standard 16-pin plastic DIL package. RIFA AB, Market Chambers, Shelton Square, Coventry, Tel (0203 27259

IGT Is Here

The General Electric Company of the USA has announced the commercial availability of a new type of power semiconductor device called the Insulated Gate Transistor or IGT. It is a gate turn on-turn off device in which, it is claimed, the advantages of power MOSFETs and bipolar transistors are combined. The result is a device which has a high input impedance like a MOSFET but a low on-state conduction loss like bipolar transistors.

The cell design and MOS gate structure of the IGT are similar to that of power MOSFETs. The major difference is that the resistance of the epitaxial drain region is modulated to a low value when the gate is turned on, resulting in very low on-state voltage drops and a forward con-

duction characteristic similar to a PIN rectifier. This allows devices rated at 500 V to operate at current densities twenty times greater than power MOSFETs and five times greater than bipolar transistors, giving a significant reduction in both chip size and cost.

IGTs either already available or soon to be introduced include a 10 A, 500 V device in a TO-220 package and a 25 A, 500 V device in a TO-218 package. They are available with a range of gate turn off times from about four micro seconds down to less than 1 microsecond. General Electric say that IGTs will cost much less than equivalent power MOSFETs and will compare favourably with bipolar transistors and darlington transistors. International General Electric Company of New York, Demesne, Dundalk, Ireland, tel 010-35342 32371.

High-Performance Sample-and-Hold Amplifier

Zeltex have introduced a new sample-and-hold amplifier known as the ZMP-241 which, when used in front of 16-bit converters, has demonstrated an error contribution so small as to be impossible to discern at the output of the ADC.

The amplifier has been optimised for use with 16-bit A-Ds where it allows sampled data


rates of over 58 kHz to be achieved. Data sheet figures include a settling time of 10µsec for a 20V step, a slew rate of 5V per µsec and a small signal bandwidth of 700 kHz. Peak-to-peak noise over the 10 Hz to 100 kHz frequency range is only 75µV, and the droop rate, a measure of how long a sample-and-hold amplifier maintains its accuracy after a sample has been taken, is 5mV per second.

100-off price of the ZMP-241 is £64 and it comes in a 50 x 50 x 10 mm metal case which provides a very high level of radio frequency interference screening. Data Beta Limited, 23A Buckingham Avenue, Slough, Berkshire, SL1 4QA. Tel: (0753) 75933/4.

BBC Micro Computer System

OFFICIAL DEALER

Please phone for availability

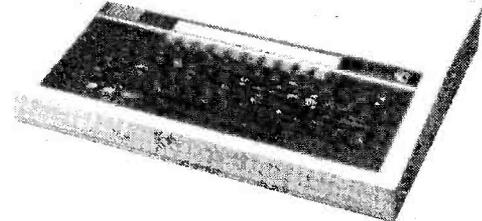

BBC Model B £399
(incl. VAT)
Carr £8/unit
Model A to Model B
upgrade kit **£50**
Fitting charge **£15**
Individual upgrades also
available
TELETEXT ADAPTOR £195
WORDWISE 8K ROM £39
TORCH Z80 DISC PACK £825

WORD PROCESSOR 'VIEW'
16K ROM **£52**

BUSINESS, EDUCATION AND FUN SOFTWARE IN STOCK

FLOPPY DISC INTERFACE incl. 1.2 Operating System £95 & £20 installation

BBC FLOPPY DISC DRIVES

Single Drive 5 1/4" 100K **£230** + £6 carr.
Double Drive 5 1/4" 800K **£699** + £8 carr.

BBC COMPATIBLE 5 1/4" DISC DRIVES

These drives are supplied in BBC matching colour cases and with necessary cables.

SINGLE DRIVES: 100K **£150**; 200K **£215** 400K **£265**

SINGLE DRIVES: with PSU 100K **£185**; 200K **£260***; 400K **£330**

DUAL DRIVES: with PSU 2 x 100K **£355**; 2 x 200K **£475***; 2 x 400K **£595**

*These drives are provided with a switch to change between 40 and 80 tracks.

DRIVE CABLES: SINGLE **£8**, DUAL **£12**.

DISC MANUAL & FORMATTING DISKETTE **£12.50**

Phone or send for our BBC leaflet

CASSETTE RECORDER

SANYO Data Recorder DR101

A superior quality data recorder with dedicated computer output and monitoring facility on both record and play

£39.50 + £1.50 carr.
SLIMLINE Cassette Recorder complete with counter and remote control

£24.50 + £1.50 carr.
Computer Grade Cassettes
£0.50 each. £4.50 for 10 + £1 carr
Cassette lead **£3.50**.

MONITORS

MICROVITEC 1431 14in Colour Monitor **£230+£8 carr**

MICROVITEC 2031 20in Colour Monitor **£319+£8 carr**

KAGA 12in RGB Monitor **£255+£8 carr**

Lead for KAGA/SANYO RGB **£10**

SANYO HI RES GREEN MONITOR **£99+£6 carr**

SANYO HI RES RGB MONITOR **£445+£8 carr.**

BBC BOOKS (no VAT; p&p £1)

Basic on BBC **£5.95**

30 House Basic **£5.95**

Programming the BBC Micro **£6.50**

BBC Micro An Expert Guide **£6.95**

Assy Lang Prog. for BBC **£8.95**

6502 Machine Codes for Beginners **£6.95**

NEC PC 8023 BE - N

120 CPS, 80 cols
Logic Seeking, Bi-directional
Forward and Reverse Line Feed.
Proportional Spacing, Auto Underline, Hi-Res and Block Graphics, Greek Char. Set.
Only **£320 + £8 carr.**



PRINTERS

SEIKOSHA

GP 100A **£175.00**

GP 250X **£235.00**

GP 700A **£425.00**

Silver Reed EX44 Daisy

Wheel with Serial Interface

£365, with Parallel Interface **£385**

Carriage/Printer **£8.00**

Parallel Printer lead for BBC/Atom to most printers **£13.50**
Variety of interfaces, ribbons in stock.
2,000 fan fold sheets 9 1/2" x 11" **£13.50 + £3 p&p**

EPSON RX80 and FX80

RX 80 100CPS 80 col
Tractor Feed **£270**

FX80 160CPS 80 col
F & T Feed **£380**

MX100 F/T3 **£425**
(Carr./printer **£8**)

NEW RX 80 FT **£319**
Carriage/Printer **£8**

SIDWAYS ROM EXPANSION BOARD

This board provides 8 high quality 28 pin sockets for expanding the computer's sideways ROM capacity by a further 128K. (As 8K Eproms consume about 40mA on standby and 16K much higher, in our opinion addition of 8 extra ROMs will not overload the computer psu nor cause internal overheating). All ROM sockets are of turned pin type gold contacts to ensure that numerous insertions and extractions will not wear out or deform them. The board is fully buffered and also dimensioned to ensure non interference with other on board components. Full fitting instructions supplied. **£25 + £2 p&p.**

TORCH Z-80 PACK

For little more than the cost of an 800K disc drive, you can now considerably extend your BBC's capabilities. The twin drives, together with the Z80 card, gives you 64K of memory and includes a database, word processor etc. Comes complete with manuals, CP/N Operating System, Demonstration and Utility programs etc. The system is fully compatible with CP/M* thus allowing the use of professional business software. **£825 + £8 p&p.**
Special offer from Torch: free software worth £1,000, for a limited period only and subject to availability.
*CP/M is a trademark of Digital Research.

CONNECTOR SYSTEMS

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header Plug	Receptacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

No. of ways			
9 15 25 37			
MALE			
Solder	80p	105p	160p
Angled	150p	210p	250p
FEMALE			
Solder	105p	160p	200p
Angled	165p	215p	290p
Hoods	90p	85p	90p
IDC 25-way plug 385p , Socket 450p			

TEXTTOOL ZIF

SOCKETS 28-pin **£8.00** 24-pin **£5.75** 40-pin **£9.75**

DIL SWITCHES

4-way 70p 8-way 90p 6-way 85p 10-way 140p

JUMPER LEADS

24" Ribbon Cable with Headers
1 end 14-pin 16-pin 24-pin 40-pin
2 ends 145p 165p 240p 350p
210p 230p 345p 540p

24" Ribbon Cable with Sockets
1 end 20-pin 26-pin 34-pin 40-pin
2 ends 160p 200p 280p 300p
290p 370p 480p 525p

Ribbon Cable with D. Conn.
25-way Male **500p** Female **500p**

RS 232 JUMPERS

(25-way D)
24" Single end Male **£5.00**
24" Single end Female **£5.25**
24" Female-Female **£10.00**
24" Male-Male **£9.50**
24" Male-Female **£9.50**

DIL HEADERS

Solder Type IDC Type
14pin 40p 100p
16pin 50p 110p
24pin 100p 150p
40pin 200p 225p

AMPHENOL CONNECTORS

36-way plug Centronics Parallel Solder **£5.25** IDC **£4.95**
36-way socket Centronics Parallel Solder **£5.50** IDC **£5.20**
24-way plug IEEE Solder **£5** IDC **£4.75**
24-way socket IEEE Solder **£5**

RIBBON CABLE

(Grey/meter)
10-way **40p**
16-way **60p**
20-way **85p**
26-way **120p**
34-way **160p**
40-way **180p**
50-way **200p**
64-way **280p**

EURO CONNECTORS

DIN 41617	Plug	Skt.
21-way	160p	165p
31-way	170p	170p
DIN 4161Z		
2x32-way St. Pin	220p	275p
2x32-way Ang. Pin	275p	320p
3x32-way St. Pin	280p	300p
3x32-way Ang. Pin	375p	350p

EDGE CONNECTORS

	0.1"	0.156"
2x18-way	190p	140p
2x22-way	190p	240p
2x23-way	175p	—
2x25-way	225p	220p
2x28-way	190p	—
1x43-way	260p	—
2x43-way	365p	—
1x77-way	600p	—
5100 Conn	—	600p

TEST CLIPS

14-pin 275p 40-pin £6 16-pin £3

DISC DRIVES FOR THE FORTH COMPUTER

5 1/4" Teac FD55 Slim Line Mechanisms.
FD55A 40 track SSDD 250kbytes unformatted
Bare: **£135**; Cased: **£155**
2 x FD55A 40 track SSDD 500kbytes unformatted
Cased x psu **£350**
FD55E 80 track SSDD 500kbytes unformatted
Bare: **£180**; Cased: **£205**
2 x FD55E 80 track SSDD 1 Mbyte unformatted
Cased + psu **£475**
5 1/4" Mitsubishi M4853 Slim Line mechanism 80 track
SSDD 1 Mbyte unformatted Bare: **£225**; Cased: **£245**
2 x M4853 2 Mbytes Cased + psu **£590**
Single drive cable **£8**; Dual Drive cable **£12**
Other parts for FORTH COMPUTER available send SAE for details.

PRODUCTION EPROM PROGRAMMER Type P800

It will blank check, copy and verify up to 8 Eproms at a time. Eprom types 2716 to 27128 can be selected by a single rotary switch.
£695 + £6 carriage.

SPECIAL OFFER

2532	350p
2732	350p
2764-25	450p
27128-25	£25
4164-2	450p
6116P-150NS	350p

UV ERASERS

UV18 up to 6 Eproms **£47.50**
UV17 with Timer **£60**
UV140 up to 14 Eproms **£61.50**
UV141 with Timer **£78**
(Carr £2/eraser)
All erasers are fitted with mains switches and safety interlocks.

'WIRELESS WORLD' PROJECTS

Semiconductors inc. I.C.s., Transistors, Displays, Connectors and Sockets for most projects are stocked by us

BOOKS

(No VAT p&p £1)
CRT Controller H/Book..... **£8.50**
Programming the Z80..... **£11.50**
Z80 Microcomp Handbook..... **£6.95**
Programming the 6502..... **£10.25**
6502 Assy. Lang..... **£12.10**
6502 Applications..... **£10.20**
6502 Software Design..... **£9.05**
6502 Games..... **£10.25**
Large selection of databooks, interfacing books, books on BBC, etc in stock. Ask for our list. **WW-12**

NEW COMPREHENSIVE CATALOGUE AVAILABLE
PLEASE SEND FOR PRICE LIST

74 SERIES 74259 100p 74LS275 175p 74C08 20p 4093 24p 4534 400p 40193 75p
 7400 18p 74265 55p 74LS280 35p 74C10 20p 4094 90p 4536 270p 40244 160p
 7401 18p 74273 120p 74LS290 180p 74C14 30p 4096 75p 4538 90p 40245 180p
 7402 18p 74278 100p 74LS292 100p 74C22 25p 4097 290p 4539 70p 40257 160p
 7403 18p 74279 55p 74LS290 100p 74C22 25p 4098 90p 4540 100p 40258 160p
 7404 22p 74283 50p 74LS293 50p 74C48 120p 4099 100p 4555 35p 44411 700p
 7405 22p 74285 160p 74LS295 70p 74C73 50p 4500 575p 4556 35p 44412 800p
 7406 90p 74286 160p 74LS297 900p 74C74 45p 4502 60p 4557 300p 44416 380p
 7408 18p 74293 90p 74LS298 50p 74C75 150p 4503 45p 4560 120p 44419 280p
 7409 18p 74298 120p 74LS300 200p 74C83 120p 4504 75p 4566 160p 44430 116p
 7410 18p 74351 150p 74LS321 240p 74C85 120p 4505 400p 4568 250p 44495 300p
 7411 18p 74354 48p 74LS323 200p 74C86 30p 4506 35p 4569 170p 44500 700p
 7412 18p 74365A 48p 74LS324/ 74C90 70p 4507 35p 4572 30p 44599 290p
 7413 27p 74366A 140p 74C93 70p 4508 130p 4573 90p 60835 350p
 7414 42p 74368A 48p 74LS348 140p 74C95 20p 4509 45p 4584 40p 80809A 570p
 7415 38p 74376 100p 74LS352 70p 74C107 100p 4511 45p 4585 75p 80354 300p
 7420 18p 74390 90p 74LS358 175p 74C150 300p 4512 48p 40014 40p 74C926 E5 8085A 570p
 7421 18p 74393 150p 74LS363 180p 74C151 100p 4514 120p 40085 90p 74C928 E6 8086 E22
 7422 22p 74490 120p 74LS364 180p 74C157 150p 4516 55p 40102 140p 72168 E22 8088 E18
 7423 22p 74LS365 180p 74LS365A 35p 74C160 90p 4518 40p 40103 170p 74C929 E11 8089A 570p
 7424 25p 74LS366 35p 74C161 90p 4520 50p 40105 110p 74C929 E12 8089A 570p
 7425 25p 74LS367 35p 74C162 90p 4521 90p 40106 40p 74C929 E12 8089A 570p
 7426 22p 74LS368 35p 74C163 90p 4522 120p 40109 100p 74C929 E12 8089A 570p
 7427 22p 74LS369 75p 74C173 48p 4526 60p 40110 275p Z80 824 E24
 7430 18p 74LS374 20p 74LS375 75p 74C174 48p 4527 60p 40163 60p 8-way 120p
 7432 22p 74LS375 20p 74LS376 85p 74C175 90p 4528 74p 10-way £100p
 7433 22p 74LS377 20p 74LS377 92p 74C192 100p 4532 70p 40175 75p
 7434 22p 74LS378 20p 74LS379 92p 74C193 115p 74C194 120p
 7436 60p 74LS380 20p 74LS380 80p 74C195 120p
 7439 36p 74LS11 20p 74LS383 90p 74C221 150p
 7440 22p 74LS12 20p 74LS395A 70p 74C246 180p
 7441 55p 74LS13 25p 74LS399 100p 74C245 160p
 7442A 40p 74LS14 36p 74LS399 120p 74C373 160p
 7443 24p 74LS15 30p 74LS344 100p 74C374 160p
 7444 75p 74LS20 20p 74LS466 120p 74C374 160p
 7446A 50p 74LS21 20p 74LS467 120p 74C902 70p
 7447A 68p 74LS22 20p 74LS468 120p 74C911 750p
 7448 65p 74LS26 20p 74LS469 120p 74C922 370p
 7449 65p 74LS27 20p 74LS470 120p 74C923 450p
 7450 38p 74LS28 20p 74LS471 120p 74C925 500p
 7451 45p 74LS29 20p 74LS472 120p 74C925 500p
 7452 20p 74LS30 20p 74LS473 120p 74C925 500p
 7453 20p 74LS32 25p 74LS508 700p 74C925 500p
 7460 30p 74LS33 20p 74LS612 E19 74LS621 500p
 7470 30p 74LS37 20p 74LS624 150p
 7472 27p 74LS38 20p 74LS626 150p
 7473 27p 74LS40 20p 74LS628 150p
 7474 25p 74LS42 86p 74LS629 150p
 7475 32p 74LS47 60p 74LS640 100p
 7476 25p 74LS48 60p 74LS640 100p
 7480 42p 74LS51 20p 74LS641 250p
 7481 18p 74LS54 20p 74LS642-1 200p
 7482 90p 74LS55 20p 74LS642-2 250p
 7483A 48p 74LS73A 20p 74LS643-1 250p
 7484A 90p 74LS74A 30p 74LS643-2 250p
 7485 90p 74LS75 30p 74LS643-3 250p
 7486 30p 74LS76A 27p 74LS644 200p
 7489 170p 74LS93A 48p 74LS645 200p
 7490A 42p 74LS95 48p 74LS646 200p
 7491 38p 74LS96 25p 74LS647 250p
 7492A 38p 74LS90 32p 74LS648 250p
 7493A 32p 74LS91 60p 74LS667 60p
 7494 75p 74LS92 40p 74LS668 70p
 7495A 75p 74LS93 32p 74LS670 120p
 7496 50p 74LS94 32p 74LS674 550p
 7497 120p 74LS95B 60p 74LS675 550p
 7498 120p 74LS96 90p 74LS676 550p
 74100 120p 74LS107 33p 74LS684 400p
 74104 50p 74LS109 33p 74LS687 450p
 74105 50p 74LS112 33p 74LS687 450p
 74106 50p 74LS113 33p 74S00 30p
 74107 27p 74LS114 33p 74S02 30p
 74109 27p 74LS115 33p 74S03 30p
 74110 45p 74LS122 60p 74S04 30p
 74111 55p 74LS123 60p 74S05 60p
 74112 170p 74LS124/ 74S06 60p
 74115 60p 74S07 60p
 74116 90p 74S08 60p
 74118 90p 74S09 60p
 74119 75p 74S11 36p
 74120 75p 74S12 36p
 74121 32p 74S13 42p
 74122 36p 74S14 42p
 74123 36p 74S15 42p
 74125 34p 74S16 42p
 74126 36p 74S17 42p
 74128 45p 74S18 42p
 74132 43p 74S19 42p
 74136 38p 74S20 42p
 74141 55p 74S21 42p
 74142 175p 74S22 42p
 74143 200p 74S23 42p
 74144 200p 74S24 42p
 74145 75p 74S25 42p
 74147 90p 74S26 42p
 74148 90p 74S27 42p
 74150 120p 74S28 42p
 74151A 40p 74S29 42p
 74153 40p 74S30 42p
 74154 120p 74S31 42p
 74155 45p 74S32 42p
 74156 48p 74S33 42p
 74157 45p 74S34 42p
 74159 150p 74S35 42p
 74160 55p 74S36 42p
 74161 55p 74S37 42p
 74162 55p 74S38 42p
 74163 55p 74S39 42p
 74164 60p 74S40 42p
 74165 75p 74S41 42p
 74166 90p 74S42 42p
 74167 200p 74S43 42p
 74168 150p 74S44 42p
 74172 250p 74S45 42p
 74173 65p 74S46 42p
 74174 55p 74S47 42p
 74175 50p 74S48 42p
 74176 50p 74S49 42p
 74177 50p 74S50 42p
 74178 90p 74S51 42p
 74179 90p 74S52 42p
 74180 55p 74S53 42p
 74181 140p 74S54 42p
 74182 50p 74S55 42p
 74183 120p 74S56 42p
 74185A 120p 74S57 42p
 74190 60p 74S58 42p
 74191 60p 74S59 42p
 74192 60p 74S60 42p
 74193 60p 74S61 42p
 74194 60p 74S62 42p
 74195 50p 74S63 42p
 74196 48p 74S64 42p
 74197 48p 74S65 42p
 74198 120p 74S66 42p
 74199 120p 74S67 42p
 74221 60p 74S68 42p
 74251 60p 74S69 42p

74LS275 175p	74LS280 35p	74LS290 180p	74LS292 100p	74LS293 50p	74LS295 70p	74LS297 900p	74LS298 50p	74LS300 200p	74LS321 240p	74LS323 200p	74LS324/ 74C90 70p	74LS348 140p	74LS352 70p	74LS358 175p	74LS363 180p	74LS364 180p	74LS365A 35p	74LS366 35p	74LS367 35p	74LS368 35p	74LS374 20p	74LS375 75p	74LS376 85p	74LS377 92p	74LS380 80p	74LS383 90p	74LS395A 70p	74LS399 100p	74LS344 100p	74LS466 120p	74LS467 120p	74LS468 120p	74LS469 120p	74LS470 120p	74LS471 120p	74LS472 120p	74LS473 120p	74LS474 550p	74LS475 550p	74LS476 550p	74LS799 550p	74LS800 550p
--------------	-------------	--------------	--------------	-------------	-------------	--------------	-------------	--------------	--------------	--------------	--------------------	--------------	-------------	--------------	--------------	--------------	--------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	--------------	--------------	--------------	--------------	--------------

COMPUTER COMPONENTS

CPU'S	8279 440p	CRT	8T97/98 90p
1802CE 650p	8284 350p	8T1LS95/96 120p	8T1LS97/98 120p
2650A E12 8755 E16	8288 E11	88LS120 350p	88LS120 350p
6502 350p	8290 E10	9637AP 160p	9637AP 160p
6502A 500p	8292 E13	9637B 160p	9637B 160p
6800 225p	8293 E13	9637C 160p	9637C 160p
6801 225p	8294 E13	9637D 160p	9637D 160p
6802 225p	8295 E13	9637E 160p	

ACE INTERFACE

Game playing and typing in should be fast and furious on the Jupiter Ace because of the use of FORTH. But with a membrane keyboard? Doug Bollen shows how to get round the rubber.

It is strange that something as simple as a set of keys and a joystick should pose such a problem for both makers and users of low cost computers. Beneath that intractable rubber keyboard, in an unassuming plastic box, lies many a good computer, spoiled by the lack of a real human interface. Of course, the reason for this is a price differential of at least twenty-five quid.

A typewriter-style keyboard can reduce frustration, and more than double program and test entering speed if the key-scan plus display routine in the computer ROM is fast enough to cope with fleeting fingers. Old mini and mainframe keyboards can be picked up now

and then quite cheaply, and some of them have excellent magnetic switches. Alternatively, a good low-cost keyboard may be built with readily available switches mounted on a piece of Veroboard.

Video games are great fun, but can you imagine piloting an airliner or spacecraft with four keypresses? There is no standard for games software direction keys so a programmable joystick is an absolute necessity for the dedicated games-player.

Once you've acquired a keyboard and a joystick, you need an interface to connect them to the computer. At this rate of expenditure you could have bought a 'Flash MK IIB' computer, but

never mind, it is all part of the learning process, and those plug-in-add-ons can be very versatile.

The Jupiter Ace has a fast key-scan routine which is capable of electric typewriter performance. The space key is a trifle slower than normal, but all other keys respond well, particularly when aided by a software or hardware key beep. If the relatively large user memory (51K expanded) of this compact language machine is taken into account along with its other features, an Ace with full-travel keyboard is capable of serious work in areas of text and data handling, as well as super-speed gaming.

This project allows a full-travel keyboard and a joystick, acting on

HOW IT WORKS — INTERFACE —

The Ace rubber keyboard uses an input port which occupies eight addresses, but all even addresses (A0 low) are reserved for internal use. Data lines D0-D4, and address lines A8-A15 are used for key-scan, while D5 is reserved for tape load. The remaining three data bits may be ignored here. Because the five Ace data lines are up with no keypress, and the Ace TTL keyboard buffers have a relatively high output impedance for logic 1, it is possible to pull down the data lines externally during keyscan, and this saves on hardware and software.

Ace keys are positioned in a matrix of 5 data lines by 8 address lines. In normal inputting key-scan mode, no keypress and multiple keypresses (other than shifts) return a zero; this is also the case with INKEY. If the keyboard is read by 'address IN' (refer to Fig. 3), a combination of any five keys on each matrix line Y0-Y7 will give a multiple keypress code. For example, F7FE IN (keys 1-5) is binary 111111 with no keypress, five keys at once 100000, key '1' on X0 111110, and key '5' on X4 101111. The MSB is the tape port which toggles between 1 and 0 only when you input a tape signal.

There is nothing very mysterious about the interface circuit of Fig. 1, it is merely a six-bit input port running in tandem with the Ace's own keyboard port, and addressed by A0 low. Two three input NORs (IC1) are configured to give an active low enable to buffer/driver IC2 during an input request. Diodes D1-D8 serve to isolate each address line. Spare input T is the alternative LOAD port. X0-X4 and Y0-Y7 form the interface input lines.

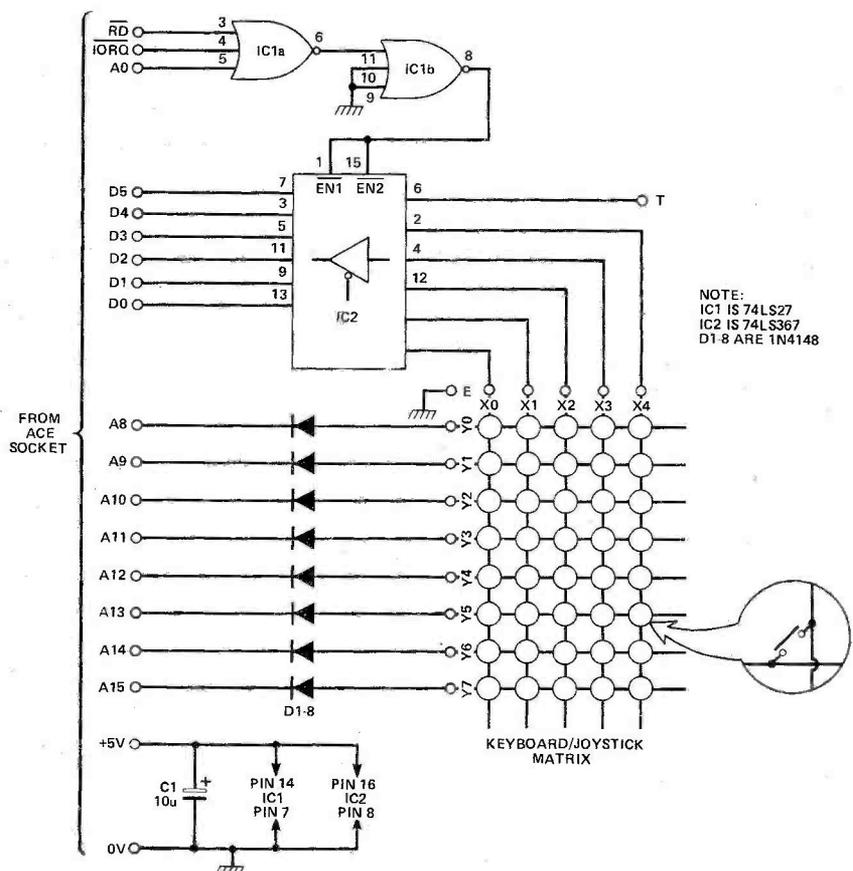


Fig. 1 Circuit diagram of the interface.

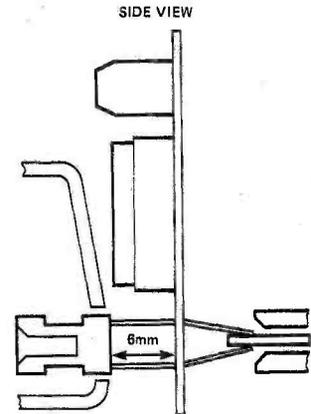
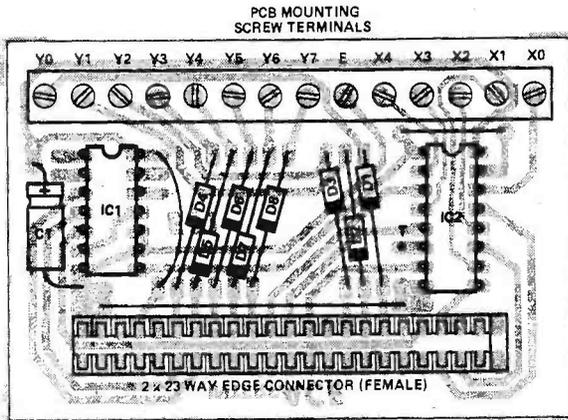


Fig. 2 (a) Overlay diagram of the PCB.

(b) detail of assembly of edge connector.

any pre-selected group of five keys, to be plugged into the back of the Ace, which will not invalidate the manufacturer's guarantee or require additional software. The interface circuit mimics the Ace's internal hardware so that dual keyboards and joystick effectively operate in parallel and simultaneously. An additional input provides DC access to the internal tape-load port of the Ace for experimental purposes.

The ability to simulate key-press with a switch (without a mess of wires soldered to the computer mainboard) can provide a range of useful facilities. Allowing for shift functions and unprintable codes, there are 106 individual codes which may be obtained using INKEY during program execution, and each represents a discrete input channel. Multiple key-presses of up to forty keys are also possible with the IN word, or a compact machine code routine, and this will yield 255 key combinations or channels.

A three-octave monophonic music keyboard, fitted with suitable contacts, can make use of the ready-made and debounced key-scan routine in Ace ROM, and leave 70 additional channels free for other functions. Multi-key-press offers three octave polyphonic operation.

A small panel of insulated material, with forty 3.5mm jack sockets, will serve as a general purpose patch-panel for switch interfacing, and is handy for quick, softwareless joystick programming. With the switch combinations available, and an equal number of possible computer responses, many other applications should spring to mind.

Construction

Ace edge connectors are not widely available, but you can use a cut-down ZX Spectrum connector, a

modified ZX81 connector, or one cut from a long block. Make sure that the edge connector wire length is at least 14mm. Some, but not all, ZX81 connectors can be modified by carefully pushing out two contacts at the end of each block with a small pair of pliers and reinserting them in the ZX blanking key position, then fitting the blanking key at the end of the row to suit the Ace.

Insert the edge connector half-way into the plain side of the PCB with the blanking key to the right.

PARTS LIST

CAPACITOR	
C1	10uF 10V tubular electrolytic
SEMICONDUCTORS	
IC1	74LS27
IC2	74LS367
D1-D8	1N4148

MISCELLANEOUS
 Double sided 23-way edge connector (see text); 14-way PCB mounting screw terminals (see text); 14-pin IC socket; 16-pin IC socket; PCB (see Buylines); keyboard; joystick (see text).

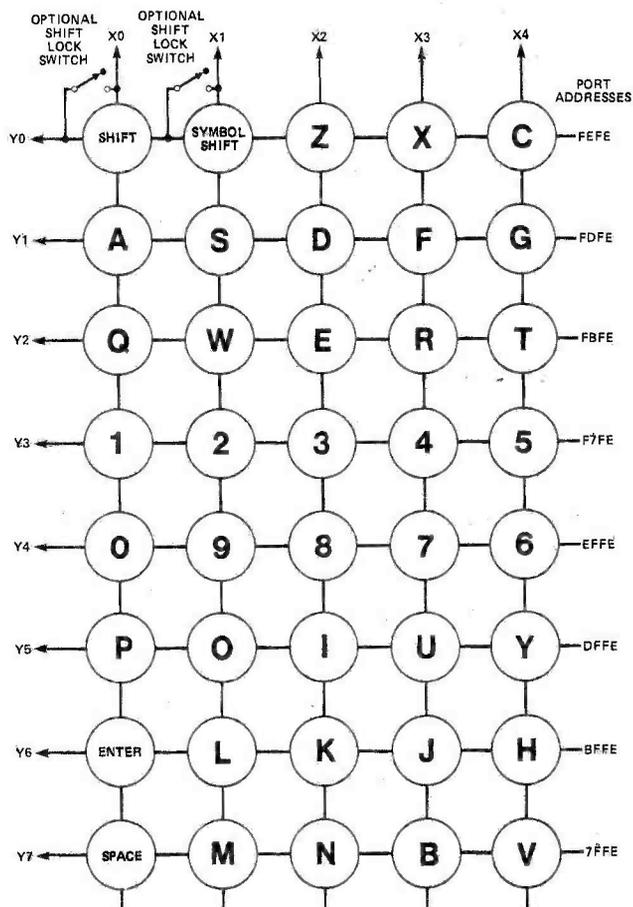


Fig. 3 The coding of the keyboard matrix.

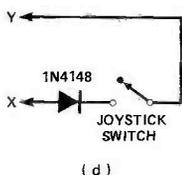
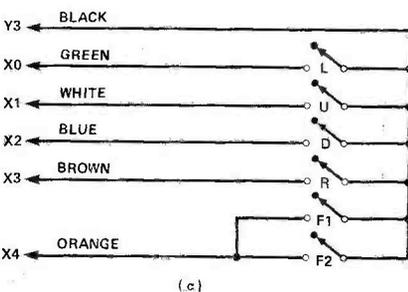
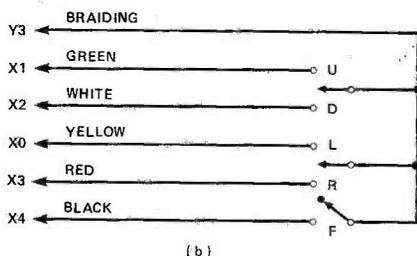
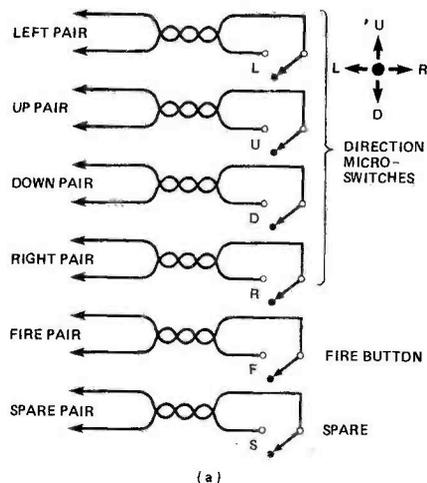


Fig. 4 Different Joystick configurations:
a. a microswitch joystick rewire for the Ace and multipress on any six keys;
b. pot switch joystick (Voltmace) shown for multi-press on keys 1 to 5;
c. diaphragm switch joystick (Spectrovideo Quickshot) shown for multipress on keys 1 to 5;
d. use of isolating diodes to avoid ghosting.

Lay a pencil along the top row of wires, on the foil side of the PCB, and apply pressure to the pencil to bend the wires inwards (see Fig. 2). Now bend the remaining row of wires inwards and adjust until the a suitable male edge connector strip into position between the wires, making sure that there is plenty of contact area free for the Rampack, and solder the wires to the strip. Position the edge connector parallel

to the PCB in all planes, 6mm away from the board, and solder to the PCB.

Now check all solder joints with a magnifying glass (even if you do have good eyesight!) and look for whiskers or blobs of solder which may cause a short between adjacent strips. Clean minute blobs of flux from the extender strip with a brass wire brush. Plug the interface into the Ace and remove it, with power supplies OFF, several times, to remove oxidation from the computer board. If you have a Rampack, push it on and off the interface rear extender strip too. Now switch on and check that the Ace behaves normally. With clean contacts, it should be possible to rock the Rampack slightly without crashing. Look for dry joints or dirty contacts if there is malfunctioning.

Insert the remaining components and link wires on the PCB, but leave out the longest link for the time being. Observe capacitor and diode polarities and DIL socket orientation. The screw terminal block can be made up of 8 + 4 + 2, 8 + 3 + 3, or 4 + 4 + 4 + 2 assemblies. It may be necessary to sandpaper the end of the blocks for a good fit on the PCB. You can insert and solder the long link wire after the diodes have been soldered.

Before inserting the ICs, check that the Ace works normally with the interface in position. Switch off, insert ICs the correct way up, and test again. The interface should have no effect on the Ace. Just to make sure, try a LOAD from a trusty tape and check all key-presses on the rubber keyboard.

Wire up the underside of your add-on keyboard according to the keyboard layout in Fig. 3, and fit optional shift lock switches if required. Try to keep switch interconnecting wiring as short as possible, to minimise circuit strays.

Your keyboard can be wired straight to the PCB terminal block, with about 1/2 metre of ribbon cable, and all key-presses then tested. If some keys work erratically, or are slow on repeat, try earthing the computer via the negative side of the power supply jack plug. A joystick can also be wired to the PCB terminal block, but cannot be reconfigured without switching the computer off because of edge connector wobble. It is a good idea to run a flexible length of ribbon cable from the PCB to two 2 A terminal blocks for the joystick, which can then be reconfigured while the computer is running.

Joysticks

There are many weird and wonderful joysticks now on the market. Analogue joysticks with pots are not suitable for this

```

: LEFT
  ." left"
;

: UP
  ." up"
;

: DOWN
  ." down"
;

: RIGHT
  ." right"
;

: FIRE
  ." fire"
;

: MULTIPRESS
  0 IN 31 AND [ get keypress and
mask off unwanted bits]
  DUP 1 AND 0=
  IF
    ( is D0 low?)
    LEFT
  THEN
  DUP 2 AND 0=
  IF
    ( is D1 low?)
    UP
  THEN
  DUP 4 AND 0=
  IF
    ( is D2 low?)
    DOWN
  THEN
  DUP 8 AND 0=
  IF
    ( is D3 low?)
    RIGHT
  THEN
  DUP 16 AND 0=
  IF
    ( is D4 low?)
    FIRE
  THEN
  DROP [ discard keypress]
;

: TEST
  BEGIN
  CLS MULTIPRESS 500 0
  DO
    [ slow routine down for displ
ay]
  LOOP
  0
  UNTIL
;

```

Fig. 5 Five-key FORTH multi-press routine.

HOW IT WORKS — MULTIPLE KEY ROUTINE

READ is a table containing a 5 × 8 byte array of ASCII codes relating directly to the logical layout of the Ace keyboard. At the end of this table is an 8 byte array, which is a table of keyboard port addresses (high byte only).

The word KEY picks up from the stack the start address of the READ table and the ASCII key value to be tested. It searches the table until it finds a match to the key value. If there is no match the routine is aborted with ERROR 0 as an invalid key code has been used.

By the time a valid match is found, the Z80's B and D registers contain an indirect pointer to the relevant port address for the key which is to be tested (B register), and the key's position within that port as a data bit (D register). If the bit is reset (=0), then the key is being pressed and a 1 is placed on the stack, otherwise a 0 is stacked, thus giving a true or false flag for testing with IF... THEN.

interface. There are 'floppy-stick' joysticks which do not 'click' but use switches which look like pots. Then there are diaphragm switch joysticks, and microswitch joysticks which 'click'. Leaving aside personal styling preferences and magnetic switch joysticks, the microswitch type is preferred for this interface, but diaphragm switch joysticks (Atari, Quickshot) will work over a limited range of keys and can be rewired (with some difficulty) for all keys.

If you can find or make a microswitch joystick it should be wired as in Fig. 4a. The pot type switch (Fig. 4b) cannot be rewired for all key positions, but will multipress a five key row. The diaphragm switch joystick, Fig. 4c, can be rewired for all keys by cutting the tracks on the switch PCB and rewiring as in Fig. 4a, but make sure there are no solder joints under the switch actuator plastic ring. Unmodified, the diaphragm switch type will multipress five keys as in Fig. 4b.

If you rewire the joystick according to Fig. 4a, use pairs of twisted insulated wire about ½ metre long. If you are also making a patch panel (which has a socket for each key), the joystick pairs can be terminated with 3.5mm insulated jack plugs. To configure the joystick for a program, merely insert the appropriate plug in the socket position corresponding to the keypress, or clamp the wire pairs in the terminal blocks by following the key/matrix diagram of Fig. 3.

Certain key combinations of diagonal plus fire button could

conceivably produce unwanted responses with a few examples of commercial software. To avoid keypress 'ghosting', place an isolating diode in each joystick 'x' wire, as in Fig 4d.

Programming For The Interface

Good games software must be responsive and easy to control, not to be confused with difficult to play. There is nothing worse than a

sluggish 'thing' which hesitantly jerks in four directions and freezes (together with the whole scenario) during a zap. It takes all the fun out of what might otherwise be an excellent game.

Multipress action is not difficult to achieve on the Ace, if INKEY is discarded in favour of IN. Up to five simultaneous keys (those in the vertical groups X0-X4 in Fig. 3 combined with other vertical groups) will give a total of 31 keypress combinations. Apart from the eight directions plus zap, pressing right plus left (or up plus down) could produce a tenth and eleventh response, but this is not possible on a joystick alone.

In the five key multipress routine Fig. 5, you supply the direction and zap definitions, in place of the demo definitions inside the dot quotes. All five-key groups are operative because MULTIPRESS uses 0 IN. If you want to employ only one group of keys, change number base to HEX, edit MULTIPRESS, and replace 0 with an address from Fig. 3, then redefine

```
CREATE READ 48 ALLOT
```

```
IN
16 BASE C? 48 0
DO
  RETYPE NUMBER DROP OVER I
  + C?
LOOP
DECIMAL
;
```

```
; HEX
16 BASE C?
;
```

```
READ IN
```

```
43 53 7A 78 63 61 73 64
66 67 71 77 65 72 74 31
32 33 34 35 30 39 38 37
36 70 6F 69 75 79 0 6C
6B 6A 68 20 6D 6E 62 76
FE FD FB F7 EF DF BF 7F
```

```
DEFINER MC
VIS CR ." BYTES:"
RETYPE NUMBER DROP CR BASE
C@ HEX SWAP ." ENTER"
0
DO
  RETYPE NUMBER DROP C,
LOOP
CR BASE C?
DOES>
CALL
;
```

```
REDEFINE IN
```

```
MC KEY (NOTE: on bytes prompt
enter 52)
```

```
DF 05 DF E1 E5 6 8 E
5 16 1 7E BB 28 B CB
22 D 23 20 F6 10 F0 E1
E7 0 3E 8 90 E1 1 28
0 9 85 6F 46 E FE ED
78 2F A2 11 0 0 28 1
13 07 FD E9
```

```
DEFINER MC
DOES>
CALL
```

```
REDEFINE MC
```

3FAE DF	RST 18
3FAF 05	PUSH DE
3FB0 DF	RST 18
3FB1 E1	POP HL
3FB2 E5	PUSH HL
3FB3 06 08	LD B,08
3FB5 0E 05	LD C,05
3FB7 16 01	LD D,01
3FB9 7E	LD A,(HL)
3FBA BB	CP E
3FBB 28 0B	JR Z,3FC8
3FBD CB 22	SLA D
3FBF 0D	DEC C
3FC0 23	INC HL
3FC1 20 F6	JR NZ,3FB9
3FC3 10 F0	DJNZ 3FB5
3FC5 E1	POP HL
3FC6 E7 00	RST 20,00
3FC8 3E 08	LD A,08
3FCA 90	SUB B
3FCB E1	POP HL
3FCC 01 28 00	LD BC,0028
3FCF 09	ADD HL,BC
3FD0 85	ADD L
3FD1 6F	LD L,A
3FD2 46	LD B,(HL)
3FD3 0E FE	LD C,FE
3FD5 ED 78	IN A,(C)
3FD7 2F	CPL
3FD8 A2	AND D
3FD9 11 00 00	LD DE,0000
3FDC 28 01	JR Z,3FDF
3FDE 13	INC DE
3FDF D7	RST 10
3FE0 FD E9	JP (IY)

Fig. 6a. All-keys multiple-key read program listing; b. assembler listing for the program (relative addressing).

PROJECT : Ace Interface

the MULTIPRESS and return to decimal. The word TEST places MULTIPRESS inside a BEGIN UNTIL loop and slows it down to allow time for a screen display. MULTIPRESS would normally be inside your program loop.

All Keys Multiple Key Read Routine

Gary Knight has kindly consented to the publication of his own forty key machine code routine.

To use the multiple key read routine you need to place on the stack the ASCII code of the lower-case letter or the number which appears on that key. So, to execute the word LEFT if the 'l' key is being pressed you would use: ASCII l READ KEY IF LEFT THEN You can test for the ENTER, SPACE, CAPS SHIFT and SYMBOL SHIFT keys by placing on the stack decimal 13, decimal 32, ASCII C or ASCII S (note the last two are in upper-case). See the 'How It Works' section for this routine.

Type in everything in the listing (Fig. 6a) exactly as it stands. There are two tables of numbers (after READ IN and after MC KEY). Type

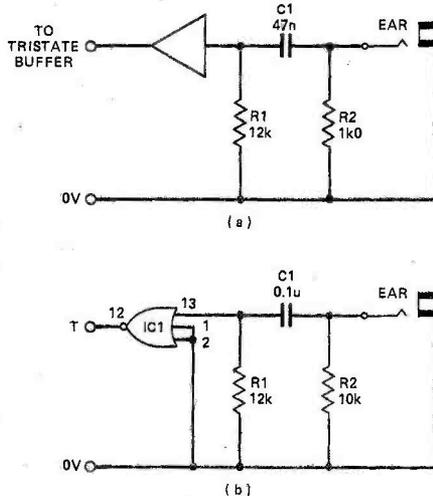


Fig. 7a. Standard Ace tape input port circuit; b. alternative tape port using spare gate on interface.

each hex number and press ENTER after each.

Tape Port and Keybeep

The standard Ace tape port input circuit is shown in Fig. 7a. R1 biases the gate input to about 2V, and R2 acts as a tape recorder output load resistor. If the gate is omitted, it is possible to feed straight into the interface T

connection from the circuit of Fig. 7a, but gate buffering is desirable.

A suggested circuit for an alternative tape port is given in Fig. 7b. The spare three input NOR in IC1 is pressed into service (the inverted signal works) and C1 is increased in value to improve sensitivity. A higher value for R2 makes it possible to feed from DIN plugs on some tape recorders. With DC access to the tape port, you can experiment with input filtering, etc.

BUYLINES

The following are available from I.T.M.
 KJ Interface PCBs £4.45 per set.
 KJ Interface Kits with PCBs £11.50 each (including full documentation).
 Assembled and tested KJ Interfaces (uncased) with applications documentation £14.50 each.
 All prices inclusive of VAT and postage. SAE for further details of KJ interfaces, patchboards etc.
 I.T.M. 119a Culverley Road, Catford, London SE6. (01-698 5351).
 Long wire ZX81 or Spectrum edge connectors are available from Technomatic (see text). PCB mounting screw terminals (0.2" pitch) and keyboard switches from Maplin or Ambient International (see text). Other components are not difficult to obtain.

ETI

AITKEN BROS.

ELECTRONIC COMPONENTS AND TEST EQUIPMENT

35, HIGH BRIDGE, NEWCASTLE UPON TYNE NE1 1EW TEL: 0632 326729

MULTIMETERS

THANDAR TM351

● Bench/portable ● 3½-digit 0.5" LCD ● 0.1% basic accuracy ● 29 ranges ● Battery life typically 2000 hrs ● Complete with batteries & test leads. £113.85.
 Accessories. Carrying case £6.84. Universal test lead set £12.65. Service Manual £3.00.

THANDAR TM353

● Bench/portable ● 3½-digit 0.5" LCD ● 0.25% basic accuracy ● 26 ranges ● Battery life typically 3000 hrs ● Complete with batteries & test leads £86.25. Accessories as TM351.

THANDAR TM354

● Pocket size. ● 3½-digit 0.5" LCD. ● 0.75% basic accuracy. ● 14 ranges ● Battery life 200 hrs. £45.94. Carrying case £3.45. Universal test lead set £12.65. Service Manual £3.00.

THANDAR TM451

● Bench/portable ● 4½-digit 0.4" LCD ● 0.03% basic accuracy ● Full auto-ranging or manual ● Sample hold ● Audible continuity test ● Complete with battery and leads £171.35.
 AC Adaptor £7.99. Universal test leads £12.65. Service Manual £3.00.

OSCILLOSCOPE

THANDAR SC110A

● Bench/portable ● Low power ● 10 MHz bandwidth ● 10mV sensitivity £171.35. Carrying case £6.34. AC Adaptor £7.99. Rechargeable battery pack £12.65. X1 probe £8.05. X10 probe £8.20. X1 X10 Switched probe £10.93. Sprung hook trimmer pack £2.88. Manual £3.00.

GENERATORS

THANDAR TG100 Function 1 Hz to 100 KHZ

£90.85
 TG102 Function 0.2 Hz to 2 MHz £186.75
 TG105 Pulse 5 Hz to 5 MHz £97.75

FREQUENCY COUNTERS

THANDAR TF200 10Hz to 200 MHz

● Bench/portable ● 8-digit Liquid Crystal Display. ● Frequency range 10 Hz - 200 MHz ● Resolution better than 1 ppm ● Sensitivity typically 10mVrms ● Time base accuracy 0.3 ppm. ● Battery life 200 hours ● Frequency, time average period, totalize & reset; 2 ranges, 5 gate times; external clock facility ● Complete with batteries. £166.75.

THANDAR TF040 10 Hz to 40 MHz

● Bench/portable ● 8-digit Liquid Crystal Display. ● Frequency range 10 Hz - 40 MHz ● Resolution 1 Hz. ● Sensitivity 40 mV rms. ● Timebase accuracy 0.5 ppm ● Battery life 80 hours. ● Frequency, totalize & reset; 2 gate times ● Complete with batteries. £126.50.

ACCESSORIES FOR TF200 & TF040 AC

adaptor £7.99, Carrying case £6.48, X1 Probe £8.05, X10 Probe £9.20, Service manual £3.00. TP600 prescaler £51.75. TP1000 prescaler £74.75.

THANDAR PFM200A 20 Hz to 200 MHz

● Pocket size ● 8-digit LED display ● Frequency range 20 Hz - 200 MHz. ● Resolution 0.1 Hz. Sensitivity typically 10 mV rms. Timebase accuracy 2 ppm ● Battery life 10 hours. ● Frequency; 2 ranges, 4 gate times ● BNC input sockets £77.62. Accessories. Carrying case £3.45, AC adaptor £7.99, X1 probe £8.05, X10 probe £9.20, Service Manual £3.00.

Full spec available on all instruments, just phone or write:

Schools, colleges, universities supplied on official orders. Prices include VAT. Please add £1.00 postage to orders under £20.00.



AUDIO DESIGN

Enough of this theoretical agonising over distortion and noise! John Linsley Hood shows us what is to be actually done about these problems — following up with a practical example, a project for a moving coil PU head-amp.

In the preceding parts of this series I have taken a, necessarily brief, look at the basic techniques of small-signal audio circuit design, and mentioned some of the problems. However, I haven't so far talked much about distortion, or looked at how these design techniques would be employed to produce a technically advanced piece of circuitry, such as is now expected in up-market hi-fi gear. I will now remedy this deficiency.

Distortion

In its most general context, this refers to the way in which the output signal from some part of the signal handling chain differs from that present at its input, excepting that due solely to uniform and frequency independent amplification or attenuation. In normal use, this term is taken to refer to the waveform distortion of a continuous uniform (*steady state*) sinusoidal waveform, either as a result of regularly occurring kinks or bends in this waveform (**harmonic distortion** — so called because the distortion products occur at frequencies which are harmonically related to the fundamental frequency) or as a result of the inadvertent interaction, due to imperfections in the signal handling channel, of two — or more — frequencies simultaneously present (**intermodulation distortion**).

Harmonic distortion can be measured by a simple test instrument of the kind shown in Fig. 1, known as a **total harmonic distortion** or **THD** meter, in which the incoming signal is measured by an AC millivoltmeter, either directly, or through a sharply tuned 'notch' filter. If the meter is set to read full scale with the filter shorted out, and then this reading is compared with the smaller reading obtained after the notch filter is used to remove the fundamental, what will be left, as a fraction of the original, is the total harmonic distortion, plus, alas, the noise and hum accompanying the original signal.

A better, but more complicated, way of measuring harmonic distortion is to use a **harmonic analyser** — shown in Fig. 2. In this the AC millivoltmeter is fed by a sharply-tuned variable-frequency filter having a narrow passband. This allows the magnitude of signals present at

any frequency to be compared with the magnitude of the signal at the fundamental frequency, and allows the user to avoid spurious results due to hum and noise. The magnitude of individual harmonics can then be identified, which gives a more significant assessment of what has happened to the signal on its passage through the unit under test. In the particular case of intermodulation distortion, this relates to the way in which two signals may combine within the signal handling stage to produce the so-called 'sum and difference' frequencies of the two components.

Although there were different standards employed, a fairly typical intermodulation distortion test would have used, for example, two frequencies at 70 Hz and 3 kHz, in a 10:1 ratio, and the Harmonic Analyser would then have been used to measure the amount of 2930 Hz and 3070 Hz present as a result of the non-linearity of the unit under test. More modern tests, of a similar kind, would use two identical magnitude signals at, say 19 kHz and 20 kHz and a simple low-pass filter could then be used to isolate for measurement the spurious 1 kHz (difference) frequency.

It has been claimed that this particular test gives results which correlate very significantly with the way in which an audio amplifier sounds. I am sceptical about this, if only because I know I could design an amplifier which would do well in this test and yet would sound awful.

The snag, of course, in all these tests is that they relate only to 'steady state' continuous sinewave tones, which really have very little to do with the sort of signals which audio equipment has to handle — with the occasional exception of the lovers of very slow-moving organ or flute music. Most of the sounds which inform or delight the listener are random, transitory and irregular in waveform. There is a relationship between the way in which an amplifier, say, will handle a steady state signal and the way in which it will sound on real life signals such as speech or music, but this is neither a simple nor a complete one; distortion measurements, though they relate to an important aspect of the behaviour of the system are not, of themselves, as meaningful as the advertisers of hi-fi goodies would have us believe. They need to be inter-

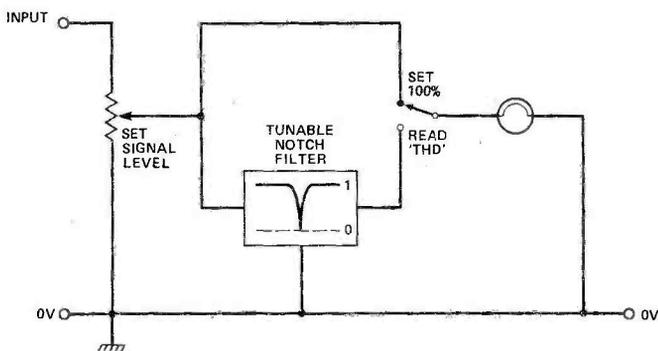


Fig. 1 Total harmonic distortion measuring instrument.

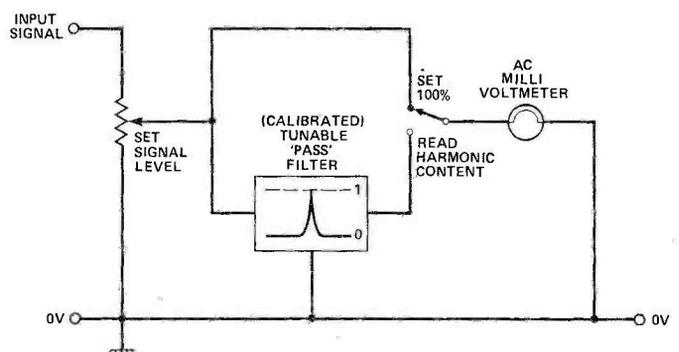


Fig. 2 Harmonic analyser arrangement.

puted, and weighted, in the light of experience and with an eye to their applicability.

So, in addition to knowing how to design for low distortion, we also need to have some understanding about the relative importance of the various types, so that if there is some need for compromise, the right decisions can be made. Happily, this isn't too difficult.

Harmonic Distortion

If a sinewave is asymmetrically distorted, as shown in Fig 3a this will give rise to even harmonics (2nd, 4th, 6th etc.). If the distortion is fairly smooth, as would be the case in most simple low-level signal stages without negative feedback, the main harmonic produced would be the 2nd. This is simply the same note, but one octave higher, and is therefore consonant, as would be the 4th, 8th and 16th harmonics, which would give the same note two, three and four octaves higher. Small amounts of such low-order harmonics — up to, say, 0.5-1.0% are musically quite tolerable, and may give an apparent richness to the sound quality — much liked by the devotees of old valve amps.

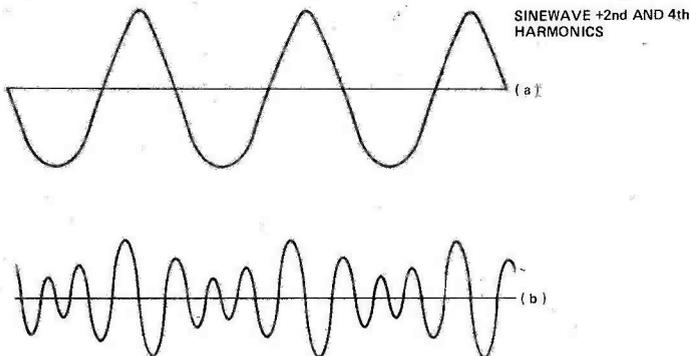


Fig. 3 Harmonic (a) and intermodulation (b) distortion.

The reason why one doesn't want even musically innocuous harmonics is shown in Fig. 3b. If a smaller signal at a different frequency were present, along with this bigger sinewave, its amplitude would vary with the excursion of output voltage — simply because the waveform distortion implies a variation in stage gain as a function of output voltage. This is what is known as **intermodulation distortion**.

Higher order even harmonics, such as the 6th, 10th, 12th, 14th, are dissonant (if 256 Hz is middle C, its third harmonic would be 768 Hz which is somewhere near G in the octave above, and the 6th harmonic would be near the G in the octave above that), as are all the 'odd' harmonics, to an extent which increases rapidly as their 'order' increases.

The odd harmonics are due to symmetrical bending of the waveform, as shown in Figs. 4a and 4b, the latter case being that due to crossover defects in push-pull systems. As an invariable rule, the smaller the proportion of the waveform which is bent the higher the harmonic, and probably the worse it will sound. In the particular case of crossover distortion in push-pull stages, in addition to making nasty sounds, it also removes low magnitude signals from the output, which makes the system have a 'thin' sound. The same sort of kinks at the tips of the waveform, as in Fig. 4c, due to symmetrical clipping, would just make the sound rather hard and 'edgy' — yet both of these could be the same harmonics, present in a numerically identical quantity, but merely shifted in phase. As a kind of working rule, 0.1% of third harmonic would not be musically objectionable (though the equipment would sound 'cleaner' without it). 5th, 7th and above should not be present above some 0.02% for a plea-

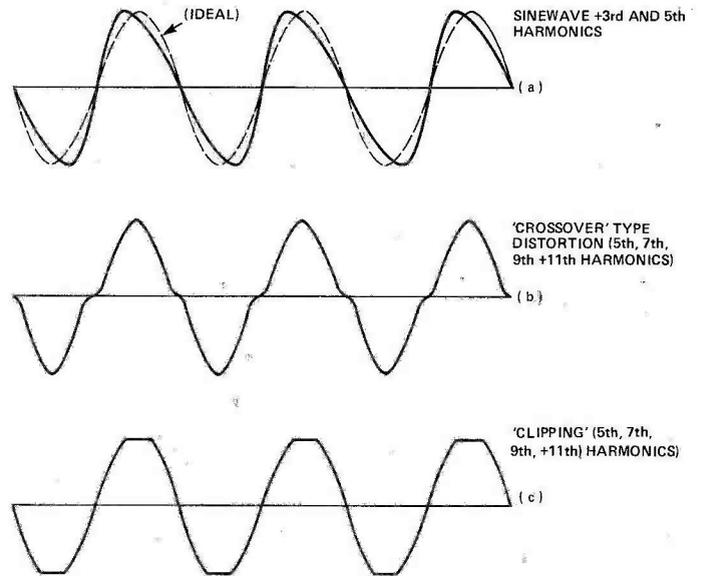


Fig. 4 Waveforms containing odd harmonic distortion.

sant sounding result.

Since these are the kinds of harmonic produced by class AB (low quiescent current) push-pull transistor output stages, it is easy to see why very low orders of THD are demanded nowadays from such amplifiers, while the old valve jobs could get away with ten times as much as this, and still be applauded.

Intermodulation Distortions (IMD)

If an incoming sinewave signal is 'bent', this implies that, for that amount of signal swing, the gain of the system varies as a function of the output voltage. It follows from this that any other signals present at the same time will be modulated in amplitude, as I've already shown in Fig. 3b. This has the effect of muddling up the sound, and making it more difficult to separate the individual components.

If an amplifier limits, either because it has been driven into clipping through too big an input signal, or because it has been made to try to follow a transient which is too fast for it, it is obvious that other signals present while it has been driven into a limit condition will be lost. This second condition is known as **slew rate limiting** or, more fancifully, as **transient intermodulation distortion (TID)**. Both of these problems are shown in Fig. 5 (over page).

Although a lot of technical capital has been made from TID, both in relation to its description and in relation to its cure, it is, in reality, rather less pervasive than normal IM distortion, if only because it only happens on transients, and it is rather more simple for the user to avoid — just drive it a little less hard!

Reducing Distortion

Harmonic distortions usually arise from one or other of three causes: non-linearity of device voltage/current transfer characteristics; intrusion of unwanted signals (which could be distorted versions of the wanted ones) from supply lines, or by capacitive coupling from later stages (which will tend to exaggerate the higher frequency components); and by coupling of unwanted components into the signal line by poorly arranged earth line return paths.

The first of these, and part of the second, is a question of circuit design, the rest is a matter of care in layout. Being aware, for example, of the need to prevent capacitive coupling of output signals back to earlier stages

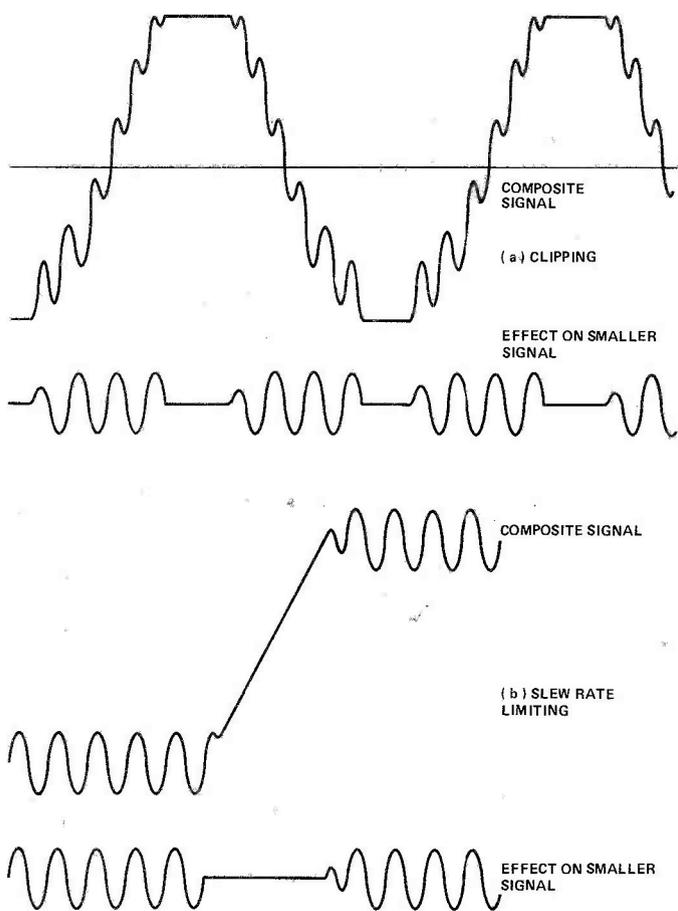


Fig. 5 Intermodulation distortion types due to (a) clipping and (b) slew rate limiting.

leads quite naturally to the thought that these parts of the circuit should be kept as far apart physically as practicable (or necessary). Being conscious of the undesirability of output circuit currents flowing in input signal paths can, without much mental stress, lead one to more elegant wiring layouts — so this isn't difficult to do adequately. It is the knowing (and remembering) which is the hard bit.

The Use Of Negative Feedback

Designing for low distortion is more demanding of thought. The major implement in this task is the use of **negative feedback (NFB)**, in which a proportion of the output signal is — effectively — subtracted from the input signal. If the output signal contains components which are not present in the input, these components will be amplified in an inverted phase, as shown in Fig. 6, and will tend to cancel the distortion components present in the output.

This technique does work, and works well, but there are snags! The first of these is that the distortion components will themselves be distorted, so that an amplifier, without feedback, having 2nd and 3rd harmonics, will, with feedback, also contain 4th, 6th and 9th — and could well sound less pleasant. Also, the use of NFB is likely to make the amplifier much less stable at HF, with the possibility of continuous or incipient oscillation. This also is ruinous for sound quality, and gave rise, some years ago, to a vogue among the less inspired circuit designers for circuits without any NFB at all. The real answer to these problems is to have enough gain in the amplifier for a decent amount of NFB to be used, and to design it with an adequate stability margin, which means mainly not having too many stages within the NFB loop.

Because the final distortion figure of any feedback

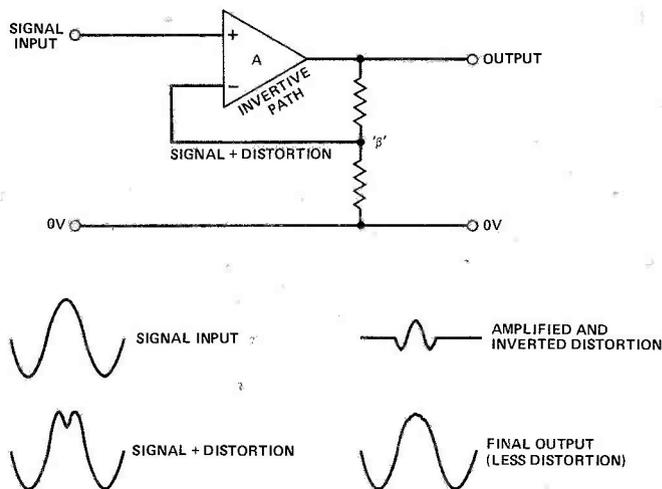


Fig. 6 Negative feedback arrangement and results.

amplifier (by this we normally mean an amplifier with *negative* feedback) depends on the initial distortion, then we need to make the amplifier as linear as possible in its open-loop condition. The formulae for calculating the effect of feedback (negative or positive) are:

$$A' = \frac{A}{(1 - \beta A)}$$

$$D_f = \frac{D}{(1 - \beta A)}$$

where A is the gain without feedback (negative for an inverting amplifier) A' is the gain after feedback is applied (if A is large enough, then we can use the approximation $A' = -1/\beta$), β is the proportion of the signal fed back, D is the distortion without feedback and D_f the distortion with feedback.

The expression $(1 - \beta A)$ is known as the **feedback factor**, and it reduces the gain and distortion equally in simple systems. It is normally expressed in decibels, for example 20dB of feedback which implies that the gain has been reduced by a factor of 10. If A and β are both positive, then the feedback factor will be less than one and both the gain and distortion will be increased, up to the point where $\beta A = 1$, where the gain becomes infinite and the amplifier will oscillate.

A High Quality, Low-Distortion Gain Block

So, how does one design, say, a low-distortion small-signal amplifier. The distortion arises because of bending in the input characteristics of the device, as shown in Fig. 7. Here I have illustrated the input voltage/output current characteristics of a small-signal silicon junction transistor and a junction FET. The bipolar transistor is obviously much more bent, and will therefore give a more distorted output, but because the upward slope of the graph is much steeper it will also give much more gain. An important point to remember, though, is that the smaller the signal which is applied to the input, the less the distortion — simply because any curve becomes a straight line if a small enough part of it is used. This means that if, by some means, we can get a high enough gain from the stage, the waveform distortion due to the input characteristic curvature will be made very small. So, one must design to get the best stage gain.

Another useful point is that push-pull circuits, because they are symmetrical, cause asymmetrical distortions to cancel out, largely. The bending of a transistor V_{base} vs. I_c

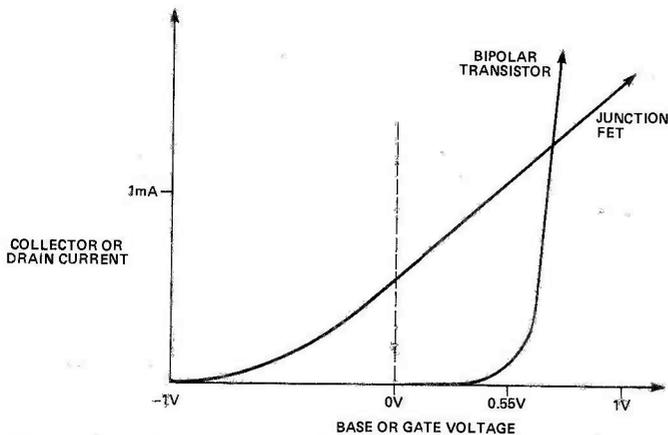


Fig. 7 Input characteristics of bipolar and field-effect transistors.

characteristic is asymmetrical, therefore a push-pull input system, such as a long-tailed pair discussed in part 1 of this series, would have less distortion — by a factor of perhaps 10 — than the equivalent single-ended input stage.

To simplify the problems of stability when negative feedback is applied, it is preferable to limit the loop, around which the feedback is applied, to two gain stages. Probably the best of the possible circuit configurations is the one in which an input long-tailed pair is followed by another push-pull amplifier stage, which is, in turn, loaded by a **current mirror** of the kind shown in Fig. 8a. A working stage of this kind is shown in Fig. 8b. I have shown this in a standard op-amp form, with a + and - DC supply, two inputs (one inverting, one non-inverting) and an output, so we can use this exactly as if it were an IC op-amp in any appropriate circuit. However, it has the advantage that it will, with suitable transistors, be usable up to DC supply voltages of 50 V or so, allowing an output voltage swing of some 96 V P-P, or an RMS output of some 34 V, which would give good headroom.

In this circuit Q3, Q4 and R1 and R4 act as a constant-current source, in which, if the current through R1 produces a voltage greater than 0.55 V, Q4 will turn on and steal the base current from Q3, to prevent Q3's emitter current from increasing any further. With the values shown this holds the current through Q1 and Q2 to 100 μ A each, which gives a satisfactorily high input impedance to this stage. For example, if Q1 and Q2 have current gains of 200, the base currents required will only be 0.5 μ A.

The best input noise figure in this stage will be given if the input transistors (Q1, Q2) are PNP types — because they have N-type base regions — and for the sort of DC supply voltages which I envisage in this application (± 15 V, so that we can also use ICs) BC214Cs are ideal. In order to get a good output drive capability from this gain-block, I have chosen to make Q5 and Q8 pass 5 mA each, which is 10 mA through R6. If this is 100R, the potential drop across it will be 1 V. So, to provide 0.55 V across the base-emitter junctions of Q5 and Q8, the voltage drop across R2 and R3 must be 1.55 V. Since Q1 and Q2 each pass 100 μ A, then R2 and R3 must each be 15.5k — the preferred value of 15k is near enough, in practice. This defines the component values, with the exception of R4, which isn't really critical in value, and R5C1 which is a phase correcting circuit.

The gain/bandwidth, noise and THD figures for this circuit block are quite excellent (see Table 1), and allow it to be used in a very high quality audio preamp to obtain a standard of performance which would not be bettered by an commercial unit on the market, though some of the more astronomically priced ones might equal it. If one restricts the \pm DC supplies to 15 V, one could substitute

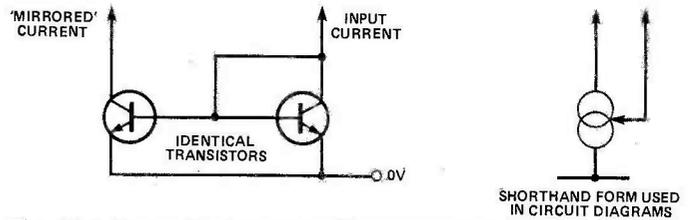


Fig. 8(a) Current mirror circuit arrangement.

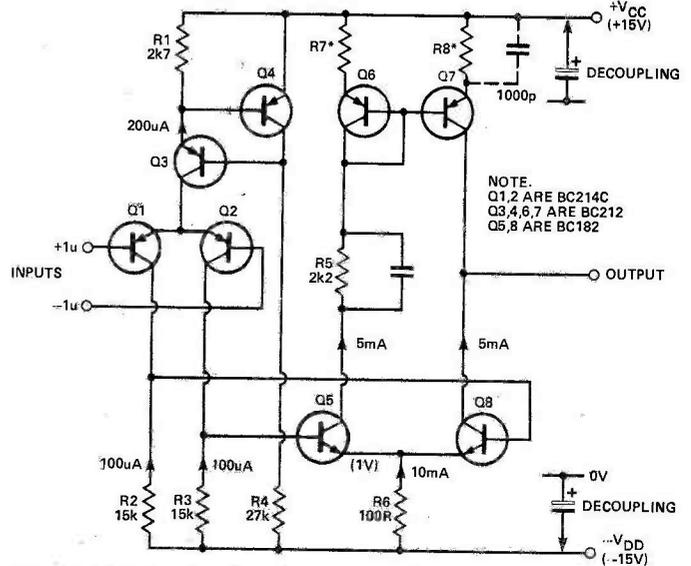


Fig. 8(b) High gain, low distortion gain block. R7 and R8 (marked with *) are optional 100R resistors which lessen the need to match the characteristics of Q6 and Q7 — they could be replaced with links.

any commercial unit on the market, though some of the the LF351 or the TL071, for this gain block with only a small lowering of audio performance, though, as mentioned above, the gain block is not so restricted in DC supply potentials.

The Passive Components

There are a few further points which are worthy of comment, at this stage, concerning components. Quite a lot of thought has been given to the sound quality changes imparted to audio circuitry by the components used. So far here, we have only considered the way in which the circuit will work, and what values of components we should employ. However, when we actually get down to the detailed design of audio stages, we can no longer simply say a resistor is a resistor is a resistor...! There are two main problems with real resistors, excess noise due to random variations in the path current will actually take through the resistance track and voltage dependence of resistance (even at power levels too low to warn it up significantly).

The consensus of opinion here is that metal film types are the best, with metal oxide types comparable in performance, followed by carbon film, and with carbon

Gain. (without NFB) 30,000x
Bandwidth. 300KHz
Distortion: Less than 0.003% at 1KHz at x100 gain
Square wave performance. No overshoot.
IMD. Not measurable.
Input noise resistance. 1k5
Note. The circuit is stable, as it stands, for gains (set by NFB) down to 5. For unity gain use, an output Zobel network of 1000pF and 180 ohms should be added.

Table 1 Performance of the gain block.

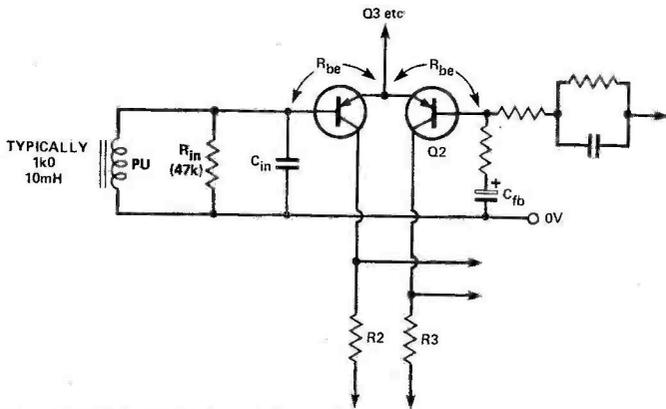


Fig. 9 RIAA stage input impedances.

composition, a long way down the list. For low values of resistance, wirewound types are excellent, but for higher values the inductive effects are troublesome. In the case of capacitors, non-polar types are always better, with polypropylene, polystyrene, polycarbonate and polyester film types shown in descending order of preference. (This is largely a function of dielectric loss and hysteresis.) In the polar types (electrolytics), low equivalent series resistance (low ESR) capacitors are preferable, but in the absence of these, supply line bypass capacitors should always be bypassed with a smaller non-polar film type. If you are really fussy you can bypass this again by a smaller monolithic ceramic type. For low signal levels, if large capacitance values are necessary, in the audio path, use one of the new low-leakage miniature aluminium types. Tantalum bead types, in addition to being very dear, are now thought to spoil the clarity of the signal.

Returning to our gain block of Fig. 8b, for the best sound quality, the DC supply lines should always be stabilised — in addition to being bypassed to the 0 volt line by an adequately large low ESR capacitor. Up to ± 24 V we can use IC voltage regulators for this purpose, which is the most economical solution.

RIAA Equalisation Stage

At the conclusion of this series, I propose to describe a high quality audio amplifier and preamp as a 'proof of the pudding'. The gain block just described will make an excellent RIAA input stage for this, though there are a few other considerations in the way it is used. In the last part of this series, I referred to resistor noise, a thing which is present in all low level circuitry as a measurable background. In the case of Fig. 8b, the important part, in relation to resistor noise, is the input circuit, shown in Fig. 9 in the way it would be connected for an RIAA equalisation stage.

Here we have two input transistors, each with their

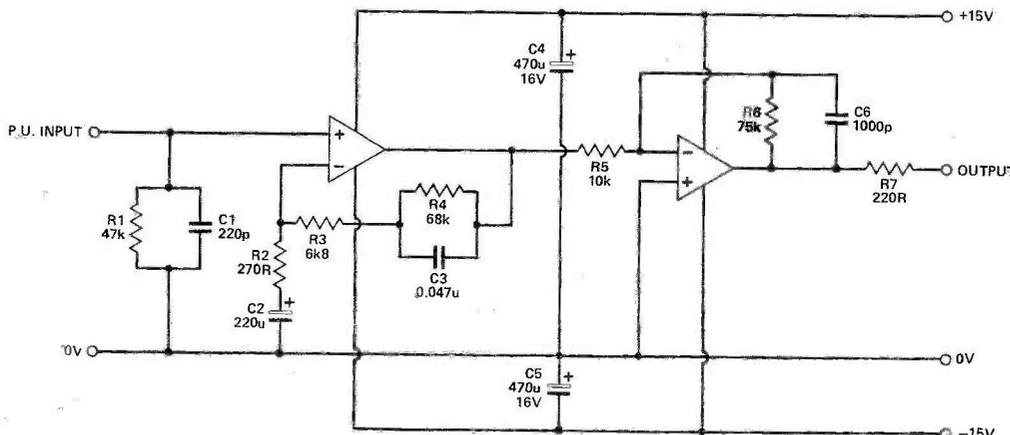


Fig. 10 (left) High quality RIAA equalisation stage, based on the gain block of Fig. 8(b) or a high-quality op-amp.


Fig. 11: (above) Component overlay for gain block of Fig. 8(b).

own internal input resistance (R_{be}), and with external impedances between their bases and the 0 V line, which are effectively in series with R_{be} so far as the noise resistance is concerned. Since the noise components due to these add as the root of the squares, and this gives the same result as if all the resistors were added together as a lump noise resistance, the task, for minimum noise, is to try to make the total — R_{in} (in parallel with the pick-up impedance) + $R_{be}(Q1) + R_{be}(Q2) + R_{be}$ (in series with C_{fb}) — as small as practicable. Here is a snag. For any sensible value of collector current for Q1 and Q2 this will be larger than likely values for R_{fb} and Z_{pu} , and limits the lower value of noise resistance to some 1k5, at low frequencies. (At higher frequencies the inductive impedance of the 10 mH or so of the PU coil will be the dominant factor anyway).

This compares with noise resistance of 4 to 5k for the better third generation audio op-amps now available. From the noise figure graph shown in the last part of this series, 1k5 will give a noise output of $0.7 \mu V$ at room temperature and 20 kHz bandwidth. This would give a signal to noise ratio of some 73dB, with reference to a typical 3 mV/5cm/sec output signal from a low output PU. However, in practice, the shape of the RIAA correction curve, which slopes down with increasing frequency, limits the effective bandwidth to about 2 kHz, and allows a practical S/N ratio of about 83dB from this sort of input noise resistance. (The TL071/LF353 would give an S/N figure, under the same conditions, of around 79 dB, which is still good).

It should be remembered, however, in order not to get lost in the wild and woolly world of specifications, that the average LP disc, when new and played on a good turntable, can manage only about 65dB S/N. Moreover, when one has had it for a little while and played it a few times, this S/N ratio is likely only to be about 55-60dB, due to surface noise.

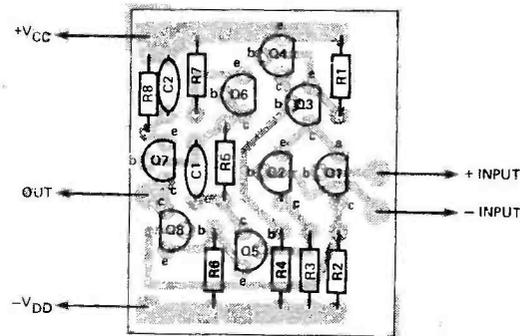In the last part of this series, when talking about op-amp ICs, I described a good quality, simple, two stage RIAA equalisation module, using a passive RC second



stage to cope with the 1 kHz-21 kHz part of the response curve. One can get a bigger output signal before overload (ie, more 'headroom') if one uses an active RC stage for the second part. A complete circuit for one channel is shown in Fig. 10.

For any readers who would like to experiment with the gain block, a suitable PCB layout for a single unit is shown in Fig. 11. However, I would like to postpone further discussion of the use of the gain block (and the design of the PCB) until I describe the complete preamp later in this series.

Moving Coil Head Amps

To the great sorrow of those companies who had been making a good living from the manufacture of precision, light-weight PU arms, aimed at the increasingly light and free tracking moving magnet or variable reluctance PU cartridges, the more massive low-output moving coil units (which are more ideally mounted on the end of a short length of crowbar) have swept the ultimate-fi scene. This is mainly, I think, because of their more vivid and dramatic stereo presentation — though the MM brigade are fighting back on this score and are narrowing the audio gap.

For the moment, MC cartridges are the choice of the critical users, and these mainly have a very low output

which is typically in the range 50-500 μ V for a 1 cm/sec recorded velocity. This level of output is too low for it to be used directly with a normal RIAA input stage, so a head amplifier is needed. This has to work with an input load impedance of typically 50 ohms, and must be designed for the lowest possible transistor and input circuit noise if it is to compete satisfactorily with the rather more mundane step-up transformer.

When head amps of this type were first employed, the low effective input noise resistance was achieved by putting a lot of small signal transistor stages in parallel, so as to reduce the overall input resistance. This was a bit inelegant as an approach, and now it is more common to choose an input transistor which has an adequately low base-emitter effective resistance on its own (these are often to be found among the plastic encapsulated small power transistors, in the 3-4 A I_c , 30-40V V_{ce} range). The actual device type must be chosen with some care, from a manufacturer of known quality. I prefer Motorola, ITT or National Semiconductors, though this is not an exhaustive list. The device should also be tested before use, under the actual operating conditions.

The circuit should then be chosen to make the gain of the first stage sufficiently high that the noise contributed by later stage transistors can be neglected in comparison

Moving Coil PU Head Amp

The theoretical background for this circuit has been discussed in the main section of Audio Design, so all that remains to be done here is to give the practical details necessary to construct the project.

There are only two points that need to be made: firstly, the electrolytic capacitors used should be low ESR types; if you don't find these easy to obtain, then you could get away with using ordinary or tantalum types (whatever your convictions are) suitably bypassed

with unpolarised capacitors.


The second point concerns the earthing. We've shown an earthing point near the input. However, there are bound to be cartridges and/or systems for which use of this particular earthing point will cause massive hum loop problems, so we recommend that you tread very carefully on your choice of earthing. Remember that you are dealing with a very small signal!

The unit should be small enough to mount in the base of

most record decks. However, the magnetic field of the motor may just manage to cause problems too . . . In any case, be very careful not to obstruct the suspension of the turntable and arm.

One final point is that you will need an on-off switch: to save the bind of having to switch the head amp, you could use a relay driven from the PSU of the pre- or power amplifier. Using a relay means that you isolate the head amp from the earth system on the main amp.

Overlay diagram for circuit of Fig. 12.

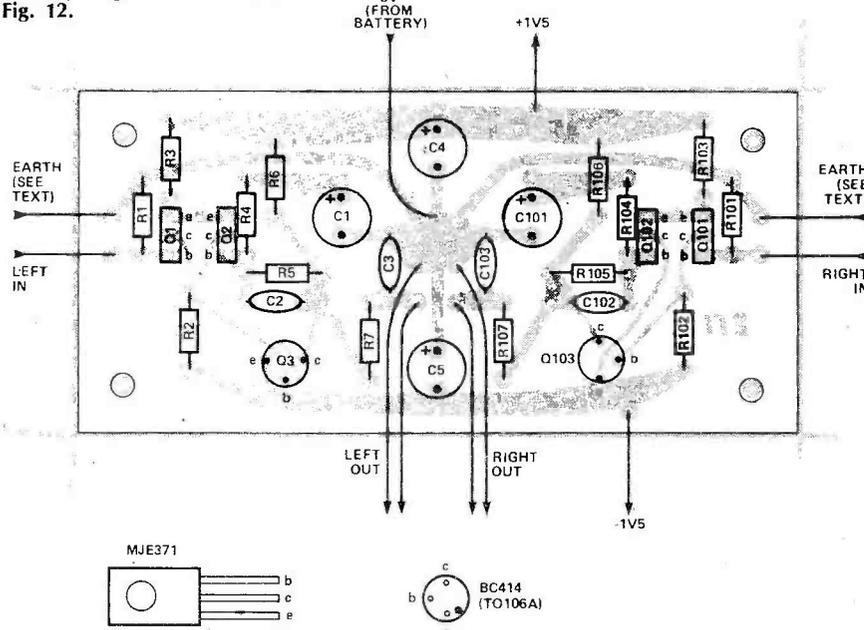

PARTS LIST

RESISTORS (all metal film, 5% or better)

R1, 101	47R
R2, 102	2k2
R3, 103	1k8
R4, 104	15R
R5, 105	680R
R6, 106	470R
R7, 107	330R

CAPACITORS

C1, C101	470 μ , 4V7 min, low ESR electrolytic
C2, 3, 102, 103	1n0 polypropylene or polystyrene
C4, 5, 104, 105	470 μ low ESR electrolytic

SEMICONDUCTORS

Q1, 2, 101, 102	MJE371
Q3, 103	BC414

MISCELLANEOUS

PCB, case to suit, battery holders, switch.

with the amplified signal. Additionally, the values of the resistors used in the circuitry should be kept as low as the circuit design can allow, and the transistors, especially the input one(s), should be operated at collector currents which will minimise R_{be} and 'shot' noise.

On the other hand, because the signal levels are so low, the harmonic distortion from such a stage can usually be ignored. This situation does not apply, however, to transient performance, so the stability margin of the negative feedback loop, if one is used, should be high. Also, perversely, the tonal characteristics of the components used, especially the capacitors in the signal line, seem to grow more important as the signal levels are reduced. So, the moral is to use the best quality components one can afford at this stage.

Having laid down these general guide-lines, the actual design of a good quality low-noise MC head amplifier is not too difficult, and I have shown a suitable circuit in Fig. 12, with a PCB layout for this in Fig. 13. Because of the very low signal levels involved, hum pick up is likely to be a problem in an 'integrated' system, so it makes life a lot simpler if one can design it so that the whole unit can be housed in a small screened box, separate from the main preamp, and isolated apart from the input and output signal connections. 'Single-point' earthing of the head amp circuitry is also very desirable.

The actual circuit in Fig. 12 is a very straightforward two stage voltage amplifier, using an input long-tailed pair of suitable PNP input transistors, biased to operate a 250uA, which is near the optimum value for the devices chosen. The second stage amplifier transistor (Q3) is a very low noise small-signal type operated at 3mA collector current (determined by R6). The overall gain is controlled to

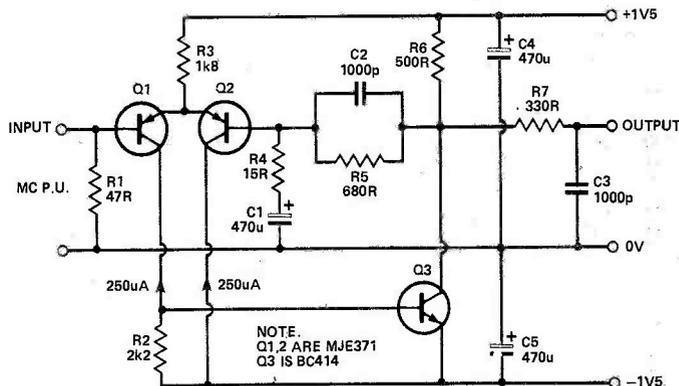


Fig. 12 Moving coil cartridge head amplifier.

45 by the feedback resistors R5 and R4. The -3dB point is set to 20 Hz (a very suitable value for record replay use) by C1. In order to avoid the possibly deleterious characteristics of capacitors in the signal path, the head amp uses a direct-coupled circuit, where the DC NFB also holds the output DC value to 0V, plus or minus a few millivolts.

Metal film resistors, and appropriately chosen capacitors (low ESR types for C1, C3 and C4, and polystyrene foil types for C2 and C5) should be employed. Because the supply voltages for which the unit has been designed are $\pm 1.5\text{ V}$, it is possible to run the unit from a pair of alkaline manganese cells, or ordinary 1.5 V 'HP' series batteries, of AA, C or D sizes (the bigger sizes will make for more economical running) which allows the unit to be separately powered and eases the task of getting a hum-free system.

ETI



IF YOU WANT FLEXIBILITY AND EXPANDABILITY THEN YOU WANT THE **MICROTAN 65**

MICROTANIC
COMPUTER SYSTEMS LTD.



Start by building your own computer
FOR LESS THAN £60



EXPANDABLE — from 1K to 256K

FLEXIBLE 6502 system with the following options:

Parallel I/O Board	Colour Graphics
Serial I/O Board	Sound Board
Disc Controller	32K Romboard
Real Time Clock	32K Ramboard
Eprom Programmer Card	ASCII Keyboard

Building into a Disc-based system with a stylish System Rack to take whatever brands suit your needs.

FULL RANGE OF SOFTWARE AVAILABLE
ALL BOARDS AVAILABLE IN KIT FORM OR FULLY BUILT

SHOWROOM: 16 Upland Road, Dulwich, London SE22
MAIL ORDER: 235 Friern Road, Dulwich, London SE22
TELEPHONE: 01-693-1137



LANGUAGES AVAILABLE: MACHINE CODE · ASSEMBLY · BASIC · FORTH
DEALER ENQUIRIES WELCOME



Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite

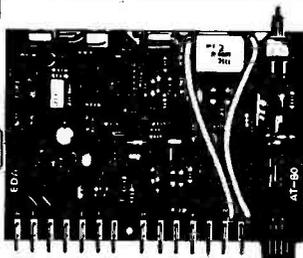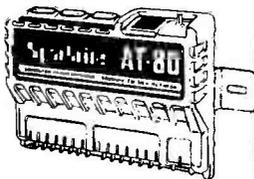BRANDLEADING ELECTRONICS
NOW AVAILABLE IN KIT FORM



AT-80

Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble


VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time.
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on.
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity.
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%.
- Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours.
- Full Imperial and Metric calibrations.
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!




SX1000 Electronic Ignition

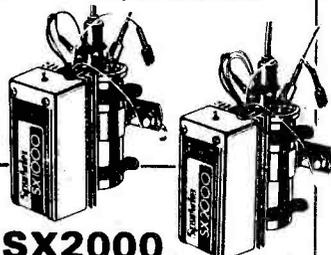- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




TX1002 Electronic Ignition

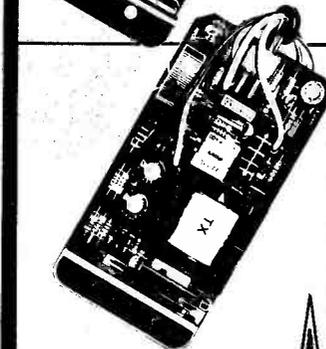- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble.



SX2000 Electronic Ignition

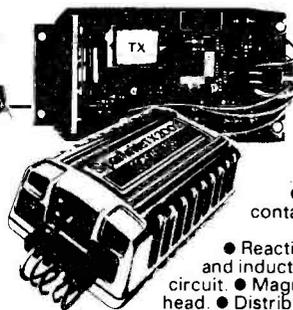- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless.
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge. Combined capacitive and inductive.
- Extended coil energy storage circuit.
- Magnetic contactless distributor triggerhead.
- Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast weatherproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents

SPECIAL OFFER

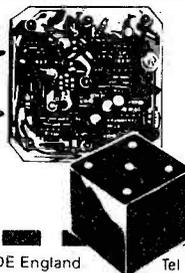"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Sleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England

Tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC. VAT, POSTAGE & PACKING

NAME _____ ET11

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____

CHEQUE NO _____



BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS GUIDE

<input type="checkbox"/>	Beginner's Guide to Basic Programming Stephenson	£5.35
<input type="checkbox"/>	Beginner's Guide to Digital Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Integrated Circuits	£5.35
<input type="checkbox"/>	Beginner's Guide to Computers	£5.35
<input type="checkbox"/>	Beginner's Guide to Microprocessors	£5.35

COOKBOOKS

<input type="checkbox"/>	Master IC Cookbook Hallmark	£10.15
<input type="checkbox"/>	Microprocessor Cookbook M. Hordeski	£7.70
<input type="checkbox"/>	IC Op Amp Cookbook Jung	£14.25
<input type="checkbox"/>	PLL Synthesiser Cookbook H. Kinley	£7.70
<input type="checkbox"/>	Active Filter Cookbook Lancaster	£13.40
<input type="checkbox"/>	TV Typewriter Cookbook Lancaster	£11.15
<input type="checkbox"/>	CMOS Cookbook Lancaster	£11.85
<input type="checkbox"/>	TTL Cookbook Lancaster	£10.95
<input type="checkbox"/>	Micro Cookbook Vol. 1 Lancaster	£15.30
<input type="checkbox"/>	BASIC Cookbook K. Tracton	£5.00
<input type="checkbox"/>	MC6809 Cookbook C. Warren	£7.25

ELECTRONICS

<input type="checkbox"/>	Principles of Transistor Circuits Amos	£8.50
<input type="checkbox"/>	Design of Active Filters with experiments Berlin	£7.70
<input type="checkbox"/>	49 Easy to Build Electronic Projects Brown	£6.00
<input type="checkbox"/>	Electronic Devices & Circuit Theory Boylestad	£13.20
<input type="checkbox"/>	How to build Electronic Kits Capel	£3.55
<input type="checkbox"/>	How to Design and build electronic instrumentation Carr	£9.35
<input type="checkbox"/>	Introduction to Microcomputers Daglecs	£7.20
<input type="checkbox"/>	Electronic Components and Systems Dennis	£15.00
<input type="checkbox"/>	Principles of Electronic Instrumentation De Sa	£11.40
<input type="checkbox"/>	Giant Handbook of Computer Software	£12.95
<input type="checkbox"/>	Giant Handbook of Electronic Circuits	£17.35
<input type="checkbox"/>	Giant Handbook of Electronic Projects	£11.75
<input type="checkbox"/>	Electronic Logic Circuits Gibson	£5.55
<input type="checkbox"/>	Analysis and Design of Analogue Integrated Circuits Gray	£30.25
<input type="checkbox"/>	Basic Electronics Grob	£11.30
<input type="checkbox"/>	Lasers - The Light Fantastic Hallmark	£7.70
<input type="checkbox"/>	Introduction to Digital Electronics & Logic Joynson	£5.25
<input type="checkbox"/>	Electronic Testing and Fault Diagnosis Loveday	£7.85
<input type="checkbox"/>	Electronic Fault Diagnosis Loveday	£6.25
<input type="checkbox"/>	Essential Electronics A-Z Guide Loveday	£7.50
<input type="checkbox"/>	Microelectronics Digital & Analogue circuits and systems Millman	£12.70
<input type="checkbox"/>	103 Projects for Electronics Experimenters Minis	£8.30
<input type="checkbox"/>	VLSI System Design Muroga	£34.10
<input type="checkbox"/>	Power FETs and their application Oxner	£9.40
<input type="checkbox"/>	Practical Solid State Circuit Design Olesky	£25.00
<input type="checkbox"/>	Master Handbook of IC Circuits Powers	£12.85
<input type="checkbox"/>	Electronic Drafting and Design Raskhodoff	£22.15
<input type="checkbox"/>	VOM - VTVM Handbook Risse	£8.50
<input type="checkbox"/>	Video and Digital Electronic Displays Sherr	£28.85
<input type="checkbox"/>	Understanding Electronic Components Sinclair	£7.50
<input type="checkbox"/>	Electronic Fault Diagnosis Sinclair	£4.50
<input type="checkbox"/>	Physics of Semiconductor Devices Sze	£17.35
<input type="checkbox"/>	Digital Circuits and Microprocessors Taub	£32.00
<input type="checkbox"/>	Active Filter Handbook	£7.60
<input type="checkbox"/>	Designing with TTL Integrated Circuits Texas	£15.20
<input type="checkbox"/>	Transistor Circuit Design Texas	£15.20
<input type="checkbox"/>	Digital Systems: Principles and Applications Tocci	£12.95
<input type="checkbox"/>	Master Handbook of Telephones Traister	£10.00
<input type="checkbox"/>	How to build Metal/Treasure Locators Traister	£6.00
<input type="checkbox"/>	99 Fun to Make Electronic Projects Tymony	£8.50
<input type="checkbox"/>	33 Electronic Music Projects you can build Winston	£6.95

COMPUTERS & MICROCOMPUTERS

<input type="checkbox"/>	BASIC Computer Games Ahl	£6.35
<input type="checkbox"/>	From BASIC to PASCAL Anderson	£9.95
<input type="checkbox"/>	Mastering Machine Code on your ZX81 T. Baker	£7.25
<input type="checkbox"/>	UNIX - The Book Banaham	£8.75
<input type="checkbox"/>	Z80 Microcomputer Handbook Barden	£10.95
<input type="checkbox"/>	Microcomputer Maths Barden	£11.90
<input type="checkbox"/>	Digital Computer Fundamentals Barter	£9.90
<input type="checkbox"/>	Visicalc Book. APPLE Edition Bell	£15.55
<input type="checkbox"/>	Visicalc Book. ATARI Edition Bell	£15.55
<input type="checkbox"/>	Introduction to Microprocessors Brunner	£23.00
<input type="checkbox"/>	Programming your APPLE II Computer Bryan	£9.25
<input type="checkbox"/>	Microprocessor Interfacing Carr	£7.70
<input type="checkbox"/>	Microcomputer Interfacing Handbook A/O & D/A Carr	£9.50
<input type="checkbox"/>	Musical Applications of Microprocessors Chamberlain	£28.85
<input type="checkbox"/>	30 Computer Programs for the Home Owner in BASIC D. Chance	£9.25
<input type="checkbox"/>	Microcomputers Dirkson	£9.30
<input type="checkbox"/>	APPLE Personal Computer for Beginners Dunn	£9.50
<input type="checkbox"/>	Microcomputers/Microcomputers - An Intro Gioone	£11.80

<input type="checkbox"/>	Troubleshooting Microprocessors and Digital Logic Goodman	£9.25
<input type="checkbox"/>	Getting Acquainted with your VIC 20 Hartnell	£8.50
<input type="checkbox"/>	Getting Acquainted with your ZX81 Hartnell	£5.95
<input type="checkbox"/>	Let your BBC Micro Teach you to program Hartnell	£7.90
<input type="checkbox"/>	Programming your ZX Spectrum Hartnell	£8.50
<input type="checkbox"/>	The ZX Spectrum Explored Hartnell	£6.95
<input type="checkbox"/>	How to Design, Build and Program your own working Computer System Haviland	£9.30
<input type="checkbox"/>	BASIC Principles and Practice of Microprocessors Heffer	£7.15
<input type="checkbox"/>	Hints and Tips for the ZX81 Hewson	£5.25
<input type="checkbox"/>	What to do when you get your hand on a Microcomputer Holtzman	£9.95
<input type="checkbox"/>	34 More Tested Ready to Run Game Programs in BASIC Horn	£7.70
<input type="checkbox"/>	Microcomputer Builders' Bible Johnson	£12.40
<input type="checkbox"/>	Digital Circuits and Microcomputers Johnson	£14.55
<input type="checkbox"/>	PASCAL for Students Kemp	£7.20
<input type="checkbox"/>	The C - Programming Language Kernighan	£18.20
<input type="checkbox"/>	COBOL Jackson	£9.25
<input type="checkbox"/>	The ZX81 Companion Maunder	£9.50
<input type="checkbox"/>	Guide to Good Programming Practice Meek	£6.40
<input type="checkbox"/>	Principles of Interactive Computer Graphics Newman	£13.95
<input type="checkbox"/>	Theory and Practice of Microprocessors Nicholas	£11.35
<input type="checkbox"/>	Exploring the World of the Personal Computer Nilles	£12.95
<input type="checkbox"/>	Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll	£9.80
<input type="checkbox"/>	Beginner's Guide to Microprocessors Parr	£5.35
<input type="checkbox"/>	Microcomputer Based Design Peatman	£11.30
<input type="checkbox"/>	Digital Hardware Design Peatman	£9.80
<input type="checkbox"/>	BBC Micro Revealed Ruston	£9.45
<input type="checkbox"/>	Handbook of Advanced Robotics Safford	£14.45
<input type="checkbox"/>	1001 Things to do with your own personal computer Sawusch	£8.50
<input type="checkbox"/>	Easy Programming for the ZX Spectrum Stewart	£7.15
<input type="checkbox"/>	Microprocessor Applications Handbook Stout	£34.40
<input type="checkbox"/>	Handbook of Microprocessor Design and Applications Stout	£37.60
<input type="checkbox"/>	Programming the PET/CBM West	£17.80
<input type="checkbox"/>	An Introduction to Microcomputer Technology Williamson	£8.20
<input type="checkbox"/>	Computer Peripherals that you can build Wolfe	£12.40
<input type="checkbox"/>	Microprocessors and Microcomputers for Engineering Students and Technicians Wooland	£7.10

REFERENCE BOOKS

<input type="checkbox"/>	Electronic Engineers' Handbook Fink	£56.45
<input type="checkbox"/>	Electronic Designers' Handbook Giacometto	£59.55
<input type="checkbox"/>	Illustrated Dictionary of Microcomputer Technology Hordeski	£8.45
<input type="checkbox"/>	Handbook for Electronic Engineering Technicians Kauffman	£27.50
<input type="checkbox"/>	Handbook of Electronic Calculators Kauffman	£35.00
<input type="checkbox"/>	Modern Electronic Circuit Reference Manual Marcus	£44.00
<input type="checkbox"/>	International Transistor Selector Towers	£10.70
<input type="checkbox"/>	International Microprocessor Selector Towers	£16.00
<input type="checkbox"/>	International Digital IC Selector Towers	£10.95
<input type="checkbox"/>	International Op Amp Linear IC Selector Towers	£8.50
<input type="checkbox"/>	Illustrated Dictionary of Electronics Turner	£12.95

VIDEO

<input type="checkbox"/>	Servicing Home Video Cassette Recorders Hobbs	£12.95
<input type="checkbox"/>	Complete Handbook of Videocassette Recorders Kybett	£9.25
<input type="checkbox"/>	Theory and Servicing of Videocassette Recorders McGinty	£12.95
<input type="checkbox"/>	Beginner's Guide to Video Matthewson	£5.35
<input type="checkbox"/>	Video Recording: Theory and Practice Robinson	£14.40
<input type="checkbox"/>	Video Handbook Van Wezel	£21.90
<input type="checkbox"/>	Video Techniques White	£12.95

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing. I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed.....

Name.....

Address.....

Digital & Micro ELECTRONICS

No 1 WINTER 1983

An Argus Specialist Publication

£2.25

Photographic Colour-
Process Monitor: use your
Spectrum for accurate
darkroom control

State Scope kit
A low-cost high
performance Solid

Build a
low-cost joystick
for the Video Genie

The BBC Finds Its Voice.
Speech synthesis system
for the BBC Computer
reviewed



NEW! OUT SOON

MINI DRUM SYNTH

Why beat about the bush when you could be beating upon our latest up-beat offering? Design by A.G. Atkins; development by Phil Walker.

Since commercial drum machines first appeared in the late '70s there have been numerous designs published for the home constructor. Some of them were very good, some were not too bad, and some appeared in magazines other than ETI, but almost without exception they were comparatively complex and cost quite a lot to build. Whilst the little unit described here cannot claim as many facilities as some of its illustrious forbears, it does offer good performance at a very low price, and it is very easy to build.

The circuit is that of a manually operated, single channel drum synthesiser. The input sensor consists of a small loudspeaker operating as a microphone, the circuit being arranged so that a light tap on the loudspeaker will cause the synthesiser to produce a drum beat. The circuit includes controls for the adjustment of pitch, decay

time and output level and features two basic pitch modulation envelopes. With SW1 open, the pitch remains constant throughout the drum beat, while with SW1 closed, the pitch falls sharply as the beat decays. With short decay times this latter effect produces a very natural sound, while with longer decay times the sound becomes less drum-like but if anything more interesting, opening up lots of possibilities for off-beat effects.

Construction

Construction is pretty straightforward since everything except the potentiometers, the switch, the input sensor, the battery, and the output connector is mounted on the PCB. The IC can, if desired, be fitted into a socket, but however you do it make sure it's the right way round. The same goes for the electrolytic capacitors (C1, 2, 3, and 6) the two diodes, and of

HOW IT WORKS

The input sensor can be almost any small loudspeaker. Its output is fed to the amplifier formed by Q1 and its associated components. The amplified signal is converted into pulses by Q2 which then charge up C4. This charge leaks away via R6 and RV1, the latter setting the decay time. Q3 acts as a buffer, passing the voltage on C4 to Q5 via R9. IC1, the 555 timer is connected to form a free-running oscillator whose frequency is controlled by RV3. The oscillator output is fed via R10 to the base of Q5. Q5 acts as a crude modulator, the output from its collector taking the form of a series of pulses whose amplitude is determined by the voltage on C4. These pulses are then fed to the output via D2 and RV2.

If SW1 is closed, current flows from the collector of Q4 into the oscillator circuit. The magnitude of this current is roughly proportional to the voltage on C4, and causes the oscillator frequency to increase as C4's voltage increases and to decrease when it falls. Thus, as the charge on C4 leaks away after each trigger pulse, the oscillator frequency will drop from its initial value.


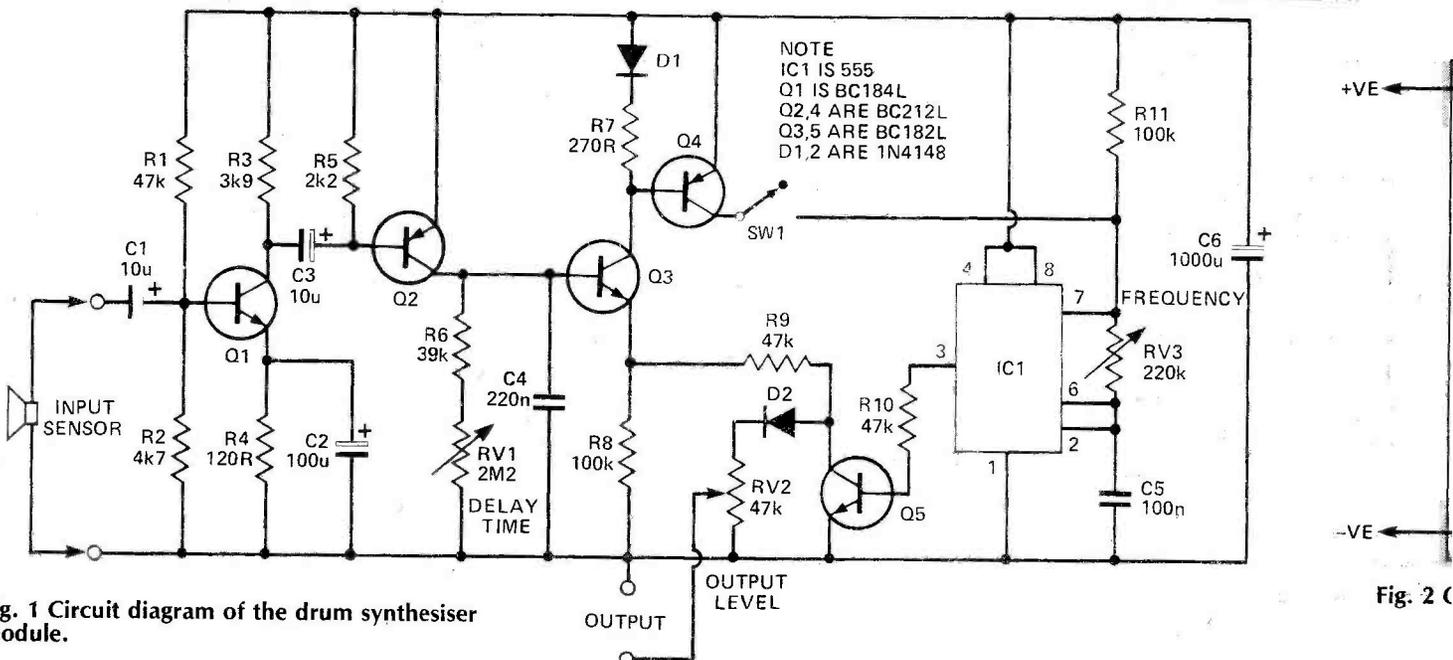


Fig. 1 Circuit diagram of the drum synthesiser module.

Fig. 2 C

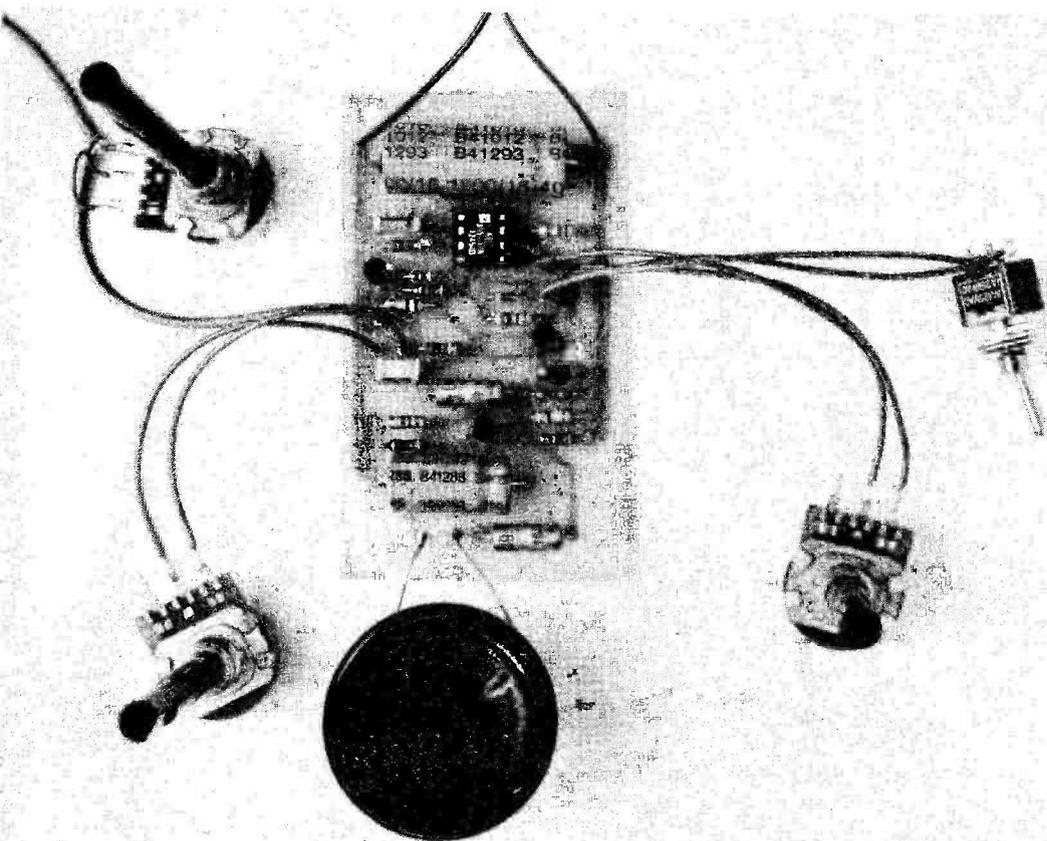

Going Modular


For the ambitious constructor, this simple circuit offers plenty of scope for development. Several units could be built and set to produce different sounds, allowing a comprehensive mini drum kit to be built up. Taking the idea a stage further, some of our more experienced readers might feel able and inclined to produce a multi-channel drum synthesiser to their own requirements. By dispensing with the input sensor and modifying the input amplifier, the circuit could be adapted to trigger from logic pulses, whereupon any number of units might be controlled from a fairly simple digital timing circuit. From there on, the sky's the limit.

course all the transistors. No case has been described since there are no real layout problems and almost anything you can come up with should be suitable. One possibility, however, is to mount all the bits in a drum-shaped container with the sensor held against the underside of the upper surface. The instrument can then be 'played' by tapping on this surface with a pencil, or your fingers, or even a drum-stick! If

preferred, the electronics can be mounted in a more conventional case and the sensor connected via a suitable length of lead. Ordinary twisted flex should be fine; since the sensor has a very low impedance there should be no problems with noise pick-up. SW1 can be any single pole switch, and if the battery is to be permanently installed in the case you may wish to include an on-off switch.

PARTS LIST ETI

RESISTORS (all 1/4W, 5%)	
R1, 9, 10	47k
R2	4k7
R3	3k9
R4	120R
R5	2k2
R6	39k
R7	270R
R8, 11	100k
RV1	2M2 linear
RV2	47k log
RV3	220k linear
CAPACITORS (10V working min)	
C1, 3	10u electrolytic
C2	100u electrolytic
C4	220n polyester
C5	100n polyester
C6	1000u electrolytic
SEMICONDUCTORS	
IC1	555
Q1	BC184L
Q2, 4	BC212L
Q3, 5	BC182L
D1, 2	1N4148
MISCELLANEOUS	
SW1	single pole switch
PCB (see Buylines); 9V battery (any size); small loudspeaker of between 8 and 80 ohms; battery connector; output connector; case; on-off switch, IC socket, knobs, etc. as desired.	

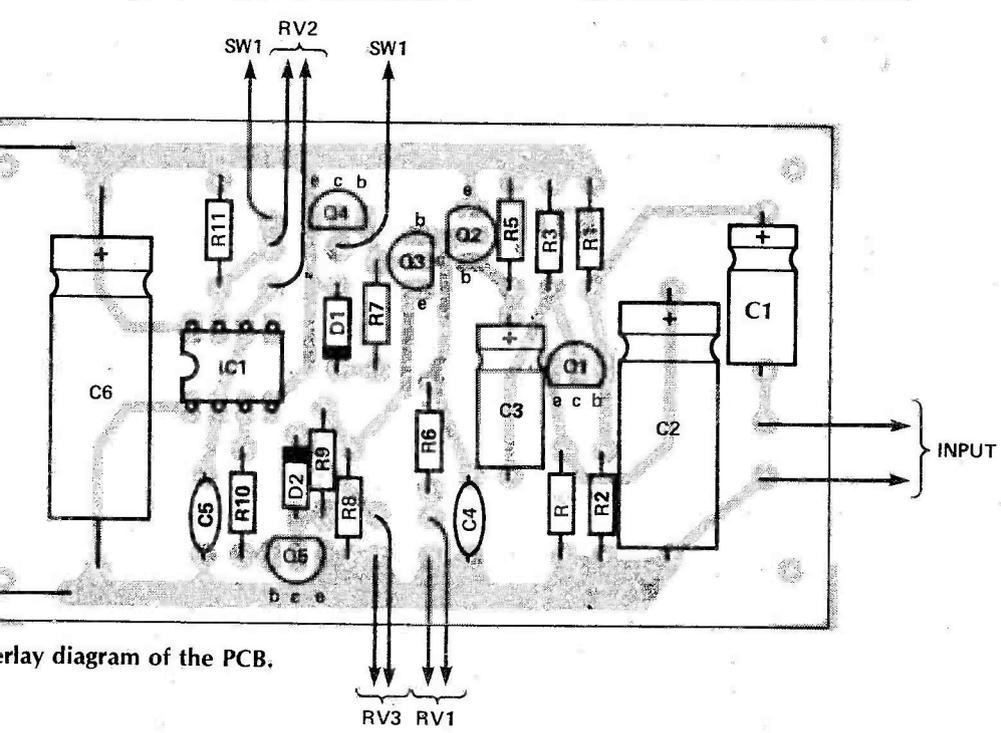

overlay diagram of the PCB.


BUYLINES

Absolutely no problems at all with this one. All of the components, semiconductors included, are available from any number of regular advertisers, and the PCB is, as always, available through our PCB service (see page 89).

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

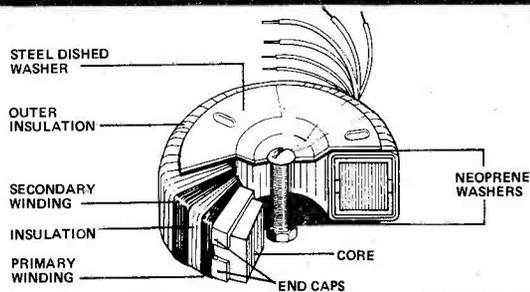Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm 0.35Kg Regulation 19%			50 VA 80 x 35mm 0.9Kg Regulation 13%			120 VA 90 x 40mm 1.2Kg Regulation 11%			225 VA 110 x 45mm 2.2Kg Regulation 7%			500 VA 140 x 60mm 4Kg Regulation 4%		
SERIES SECONDARY RMS			80 VA			160 VA			300 VA			625 VA		
No	Volts	Current	90 x 30mm 1Kg Regulation 12%	110 x 40mm 1.8Kg Regulation 8%	110 x 50mm 2.6Kg Regulation 6%	140 x 75mm 5Kg Regulation 4%								
0x010	6+6	1.25	3x010 6+6 4.16	5x011 9+9 8.89	7x013 15+15 10.00	9x017 30+30 10.41								
0x011	9+9	0.83	3x011 9+9 4.44	5x012 12+12 6.66	7x014 18+18 8.33	9x018 35+35 8.92								
0x012	12+12	0.63	3x012 12+12 3.33	5x013 15+15 5.33	7x015 22+22 6.82	9x026 40+40 7.81								
0x013	15+15	0.50	3x013 15+15 2.66	5x014 18+18 4.44	7x016 25+25 6.00	9x025 45+45 6.94								
0x014	18+18	0.42	3x014 18+18 2.22	5x015 22+22 3.33	7x017 30+30 5.00	9x033 50+50 6.25								
0x015	22+22	0.34	3x015 22+22 1.81	5x016 25+25 3.20	7x018 35+35 4.28	9x042 55+55 5.68								
0x016	25+25	0.30	3x016 25+25 1.60	5x017 30+30 2.66	7x019 40+40 3.75	9x028 110 5.68								
0x017	30+30	0.25	3x017 30+30 1.33	5x018 35+35 2.28	7x026 40+40 3.75	9x029 220 2.84								
(encased in ABS plastic)			3x028 110 0.72	5x026 40+40 2.00	7x025 45+45 3.33	9x030 240 2.60								
			3x029 220 0.36	5x028 110 1.45	7x033 50+50 3.00									
			3x030 240 0.33	5x029 220 0.72	7x028 110 2.72									
				5x030 240 0.66	7x029 220 1.36									
					7x030 240 1.25									

Why a Toroid?

- * Smaller size & weight to meet modern 'slimline' requirements.
- * Low electrically induced noise demanded by compact equipment.
- * High efficiency enabling conservative rating whilst maintaining size advantages.
- * Lower operating temperature.

Why ILP?

- * Ex-stock delivery for small quantities.
- * Gold service available. 21 days manufacture for urgent deliveries.
- * 5 year no quibble guarantee.
- * Realistic delivery for volume orders.
- * No price penalty for call off orders.

Prices including P&P and VAT

VA	Size	£	VA	Size	£
15	01	6.79	160	5	11.67
30	1	7.58	225	6	13.64
50	2	8.60	300	7	14.87
80	3	9.64	500	8	19.30
120	4	10.51	625	9	22.62

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade - We will open your credit account immediately upon receipt of your first order.


Post to: ILP Electronics Ltd., Dept. 2
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780

For 110V primary insert "O" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.
IMPORTANT: Regulation - All voltages quoted are FULL LOAD.
Please add regulation figure to secondary voltage to obtain off load voltage.



ELECTRONICS LTD.

BUILD A BETTER AMPLIFIER!

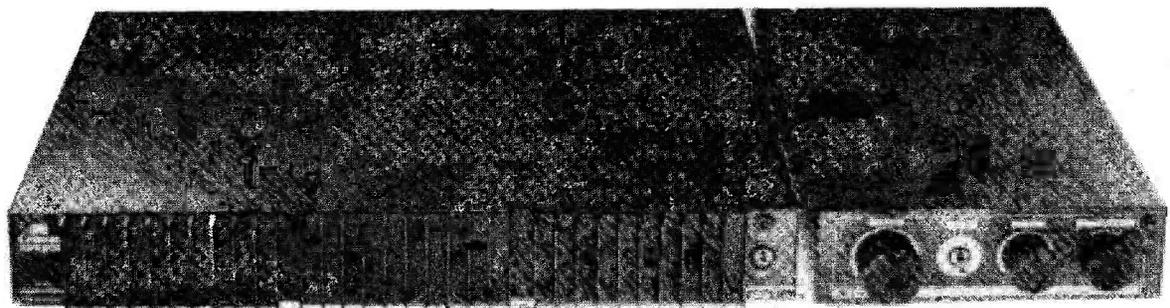

How can you own a top class HIFI amplifier, of comparable standard to Naims, Meridians, Quads etc., for an outlay of less than £250? — Simple! Build it yourself — with a Crimson kit.

It is not necessary to spend a small fortune to obtain true Hifi performance. Crimson Kits offer all the features and sound quality of the most esoteric amplifiers available and their ease of assembly ensures that they work first time and continue to do so. Not only do Crimson Kits offer outstanding value, but they also have the flexibility to adapt to any users needs. All the P.C.B.'s are ready assembled and tested (they are not "pot-ted" as we believe disposable modules are rather extravagant!) therefore constructing a kit is pleasurable in itself and, once built, will give years of untroubled service. So, whether you use a simple record player or a compact disc, you can be sure to get the most from your system. E.T.I. said, in their review of the CK1010/1100: "I can say no more than that for £250 it is a bargain and one that will become the reference point for kit amplifiers from now on." Need we say more?

PRICES

CK1010 — STEREO PRE-AMPLIFIER (moving magnet, tape, tuner input) takes power from any CK power amp or separate p.s.u. type P.S.K.	£92.00
CK1040 — STEREO POWER-AMPLIFIER 40 watts R.M.S./Chanel	£121.00
CK1080 — STEREO POWER-AMPLIFIER 80 watts R.M.S./Chanel	£134.00
CK1100 — STEREO POWER-AMPLIFIER 100 watts R.M.S./Chanel	£151.00
MC2K — Moving coil add on kit for CK1010	£25.00
P.S.K. — power supply for CK1010 (if not used with a CK power amp)	£20.00

CRIMSON also supply power amp, pre amp and electronic crossover modules, power supplies and hardware — too much to list here — but on receipt of an S.A.E. we will be happy to supply full details.

TO ORDER Send C.W.O. or quote your access card no (phone orders accepted) Crimson Products are also available from Bradley Marshall Ltd, 325 Edgeware Road, London.



CRIMSON ELEKTRIK STOKE

MANUFACTURERS OF PROFESSIONAL, DOMESTIC & INDUSTRIAL AMPLIFICATION
PHOENIX WORKS, 500 KING STREET, LONGTON, STOKE-ON-TRENT, STAFFORDSHIRE. ST2 1EZ ☎ 0782 330520

ALARM EXTENDER

Is your alarm system the talk of the neighbourhood? Fit ETIs simple add-on unit and protect your social conscience. Design by S.W. Terry.

Many of the alarm systems currently in use, whether commercial designs or home-made units, have an output that remains on continuously once triggered, stopping only when reset. There is obviously a danger with such alarms that they will be triggered when you are absent for a long period, initially drawing attention as desired but going on to cause considerable annoyance to the neighbours. At its worst, this could result in your facing a little legal unpleasantness. One way of overcoming the problem is to have an alarm which sounds only for a pre-determined time, long enough to attract attention but not so long that it becomes a nuisance to those nearby.

The ETI Alarm Extender provides this facility and is designed so that it may be easily fitted to

existing alarm installations. It will work from any supply voltage between five and fifteen volts, enabling it, in most cases, to be connected directly to the existing supply and making it ideal for use with car alarm systems. With the values of R1 and C1 given the alarm will sound for about twenty minutes, but this may readily be adjusted to suit the requirements of the user.

Construction

Everything except the relay is mounted on the PCB. The three ICs are CMOS types and are best mounted in sockets rather than soldered direct. Make sure that they are inserted the right way round, and similarly take care with Q1, C3, and D1. Note that C3 is quite close to the mounting holes at that end of the PCB, and that if a physically

HOW IT WORKS

IC1 is a 4047, a CMOS multivibrator which can operate as a monostable, but which is here used as a bistable, its frequency being set by R1, C1. IC2, a 4020, is a 14-stage ripple binary counter which counts the pulses generated by IC1. When the ALM input is low, IC3b pulls pin 4 of IC1 high which prevents it oscillating, while IC3d holds pin 11 of IC2 high, thus holding its output low.

When ALM goes high, the relay is turned on via IC3b, IC3a, and Q1. IC1 and IC2 are enabled and IC1 starts supplying pulses at the rate of about 12 Hz (assuming the values of R1, C1 given) to IC2. After 16,384 pulses have been received, the Q14 output (pin 3) of IC2 goes high, turning off the relay and preventing further input pulses from reaching IC2.

The period can be adjusted by altering the values of C1 and R1, and is equal to

$$36,045 R1 C1 \text{ seconds.}$$

The output time can also be halved by using Q13 (pin 2) instead of Q14 on IC2.

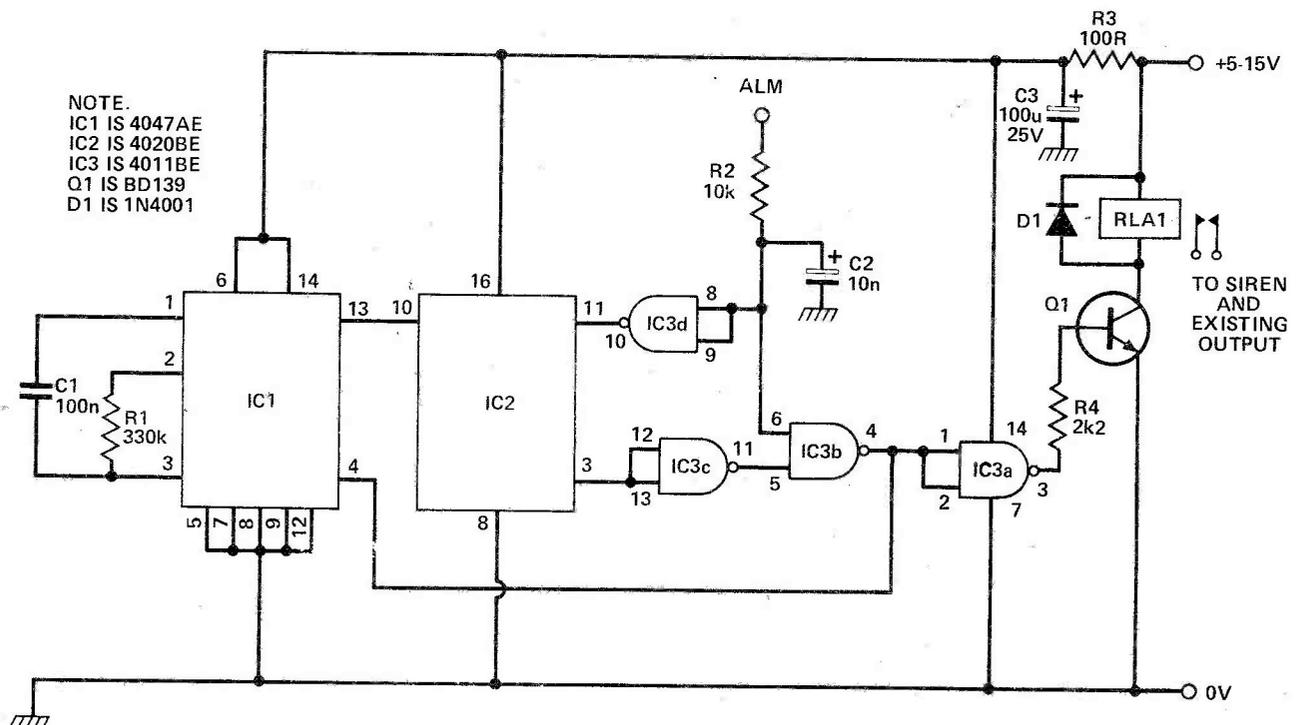


Fig. 1 Circuit diagram of the alarm extender

PROJECT : Alarm Extender

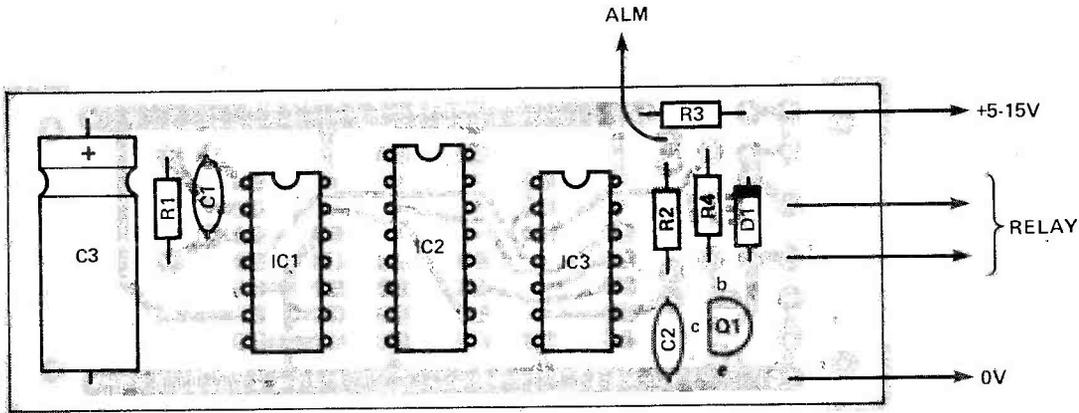


Fig. 2 Component overlay for the PCB

large capacitor is used here you may need to pass the mounting bolts or whatever through the holes before fitting it.

No case has been shown since it is assumed that the unit will be fitted inside an existing alarm, but if this proves impractical almost any small case would be suitable. Note that, if the alarm is fitted outdoors, the case and inter-unit wiring should be made as weathertight as possible. The relay can be mounted on a simple bracket, or even set in Araldite if you prefer.

Having built and installed the PCB and relay, the final step is the modification of the existing alarm wiring. If the alarm circuitry operates on a voltage higher than fifteen volts (you did check the alarm voltage before commencing construction, didn't you?) you will have to arrange a suitable dropper circuit. This should not present too many problems because the Alarm Extender is fairly tolerant of supply voltage variations. Aim for a supply voltage of rather less than fifteen (eg, twelve volts) so as to allow some room for manouevre. If the alarm voltage falls within the range

five to fifteen volts and is stabilised there are no problems and you can connect the Alarm Extender directly.

Moving on to the input and relay connections, you will have to locate within the existing alarm wiring the output lead. Depending on the type of alarm you have, this may be the + ve feed to the relay which activates the output transducer (bell, siren, etc.), or it may be the direct connection between a semiconductor switching device and the output transducer. Again, you should check this before commencing construction since we cannot guarantee that the alarm extender will work with ALL alarm systems. Having located this lead (and only after switching the alarm off!), break it and take the two ends to the two normally open contacts on the relay of the alarm extender. Identify which of these leads comes from the alarm trigger circuitry and run a further lead from it to the ALM input on the alarm extender. Note that, if the alarm runs from a

high voltage and you have had to drop the supply rail before connecting the alarm extender, you may also need to insert a further resistance in series with the ALM input (or to increase R2 in value). The unit is now ready for testing.

PARTS LIST

RESISTORS (all $\frac{1}{4}$ W, 5%)
 R1 330k (see text)
 R2 10k (see text)
 R3 100R
 R4 2k2

CAPACITORS
 C1 100n (see text)
 C2 10n
 C3 100u tubular electrolytic 16 V (min) working


SEMICONDUCTORS
 IC1 4047
 IC2 4020
 IC3 4011
 Q1 BD139
 D1 1N4001

MISCELLANEOUS
 185R, 12V relay (Varley VP2 or similar);
 PCB; two 14 pin and one 16 pin DIL sockets; mounting bolts, spacers, etc.

BUYLINES


A suitable relay is available from Maplin and everything else is just too available for words. For the PCB see page 89.

ETI

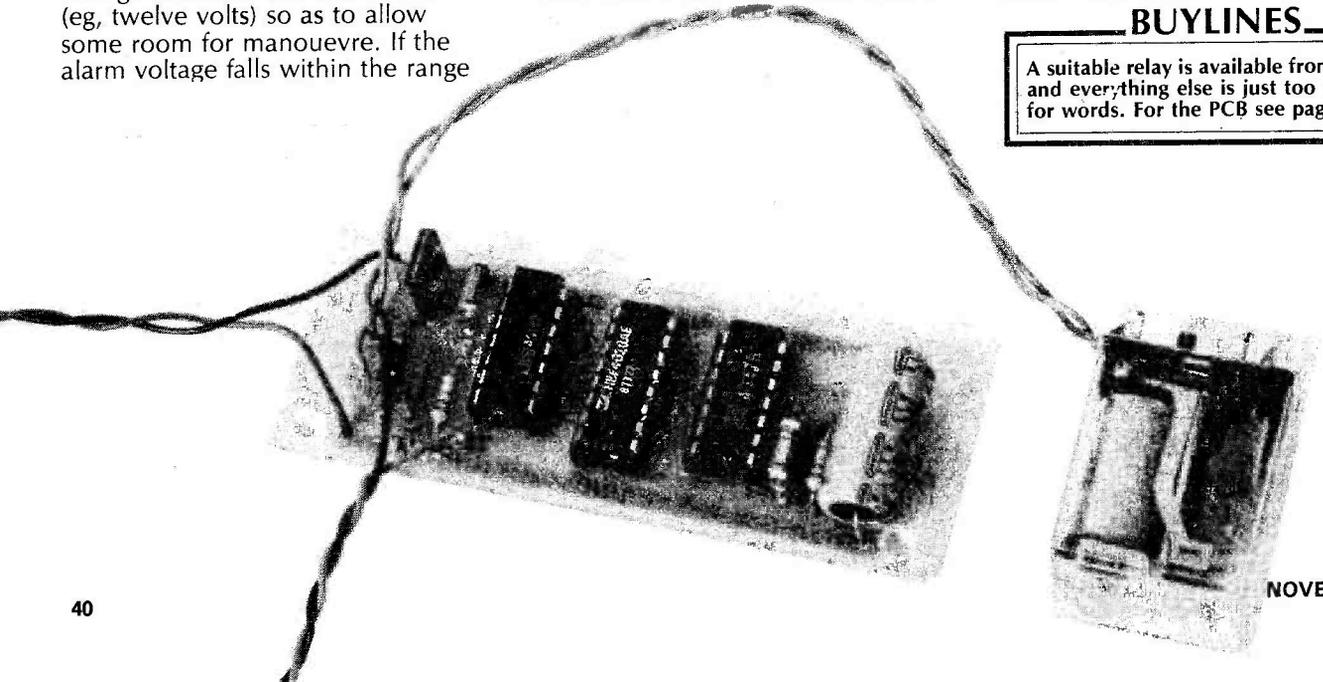

You win every time!

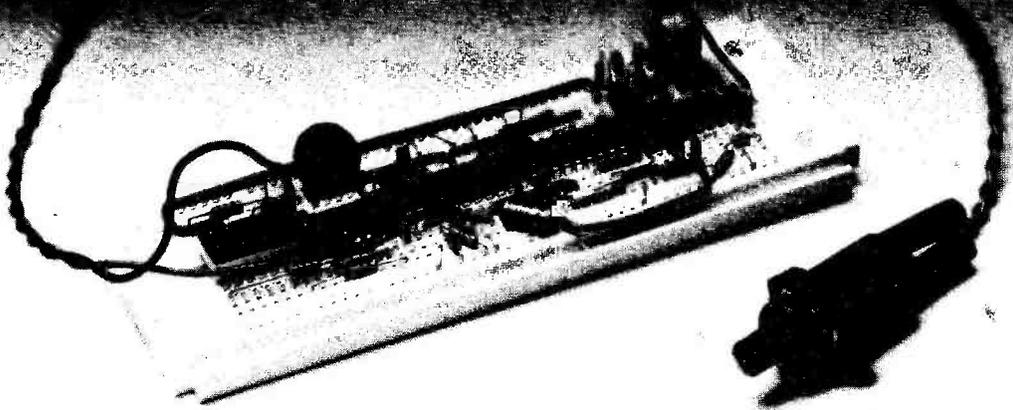
When you get this NEW & FREE project from GSC



NEW: an exciting range of projects to build on the **EXP300** breadboards.
NOW anybody can build electronics projects; it's as easy as **A.B.C.** with **G.S.C.!**

EXPERIMENTOR BREADBOARDS

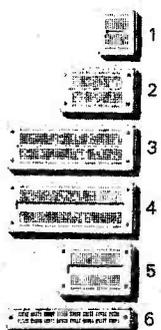The largest range of breadboards from GSC. Each hole is identified by a letter/number system. EACH NICKEL SILVER CONTACT CARRIES A LIFE TIME GUARANTEE. Any Experimentor breadboard can be 'snap-locked' with others to build a breadboard of any size.



1. **EXP 325 £2.00** The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.
2. **EXP 350 £3.45** Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.
3. **EXP 300 £6.00** The most widely bought breadboard in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.
4. **EXP 600 £7.25** Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.
5. **EXP 650 £4.25** Has 6" centre spacing so is perfect for MICROPROCESSOR applications.
6. **EXP 4B £2.50** Four more bus-bars in "snap-on" unit.

PROTO-BOARDS

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.

7. **PROTO-BOARD 6 KIT £11.00** 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

8. **PROTO-BOARD 100 KIT** Complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with kit economy. **£14.25**



FREE project:


AUTO-DICE

Live up your board games with this sophisticated electronic dice circuit! When the 'throw' switch is pressed, a numerical display flashes up rapidly changing numbers. After a few seconds, the 'rolling' stops, and the final result is displayed; any number, randomly selected, from 1 to 6. A few seconds later the display turns off to conserve your battery, letting the games go on uninterrupted for weeks!

HOW DO YOU MAKE IT?

Our **FREE** project sheet gives you a large, clear diagram of the components layed out on an **EXP 300** breadboard. Each component is labelled, and the values are given in a component listing. Even the 'row and column' lettering of our **EXP 300** is shown to make the location of the correct holes, in which to push the components, easy to find. There's no soldering involved; it **couldn't be easier!** As an extra bonus, there's a full circuit description, and the details of a regulated power supply on the other side of the sheet.

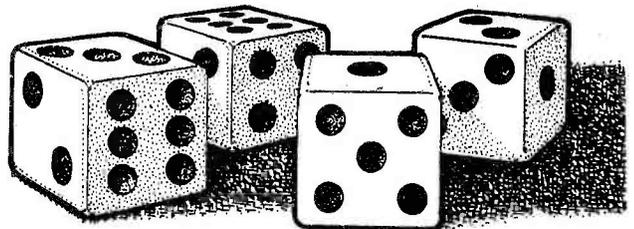"Clip the coupon" and get your **FREE** project sheet with each **EXP 300** bought. **AND** a free catalogue! Just ask about our other free projects too.



For further details of our **FULL PROTO-BOARD RANGE**, please send for our free catalogue.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Ltd. Dept. 9B,
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex CB11 3AQ
 Telephone: Saffron Walden (0799) 21682

G.S.C. (UK) Limited Dept 9B, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ
 Prices include P & P and 15% VAT

1	QTY.	2	QTY.	3	QTY.	4	QTY.	5	QTY.	6	QTY.	7	QTY.	8	QTY.
	£3.16		£4.83		£8.05		£9.40		£5.75		£3.73		£13.80		£17.53

Name _____ Address _____


I enclose Cheque/P.O. for £ _____ or debit my Barclaycard/Access/
 American Express card no. _____ expiry date _____

FOR IMMEDIATE ACTION - The G.S.C. 24 hour, 5 day a week service
 Telephone (0799) 21682 and give us your Barclaycard, Access, American
 Express number and your order will be in the post immediately

For **FREE**
 catalogue
 tick box

New cats for old !

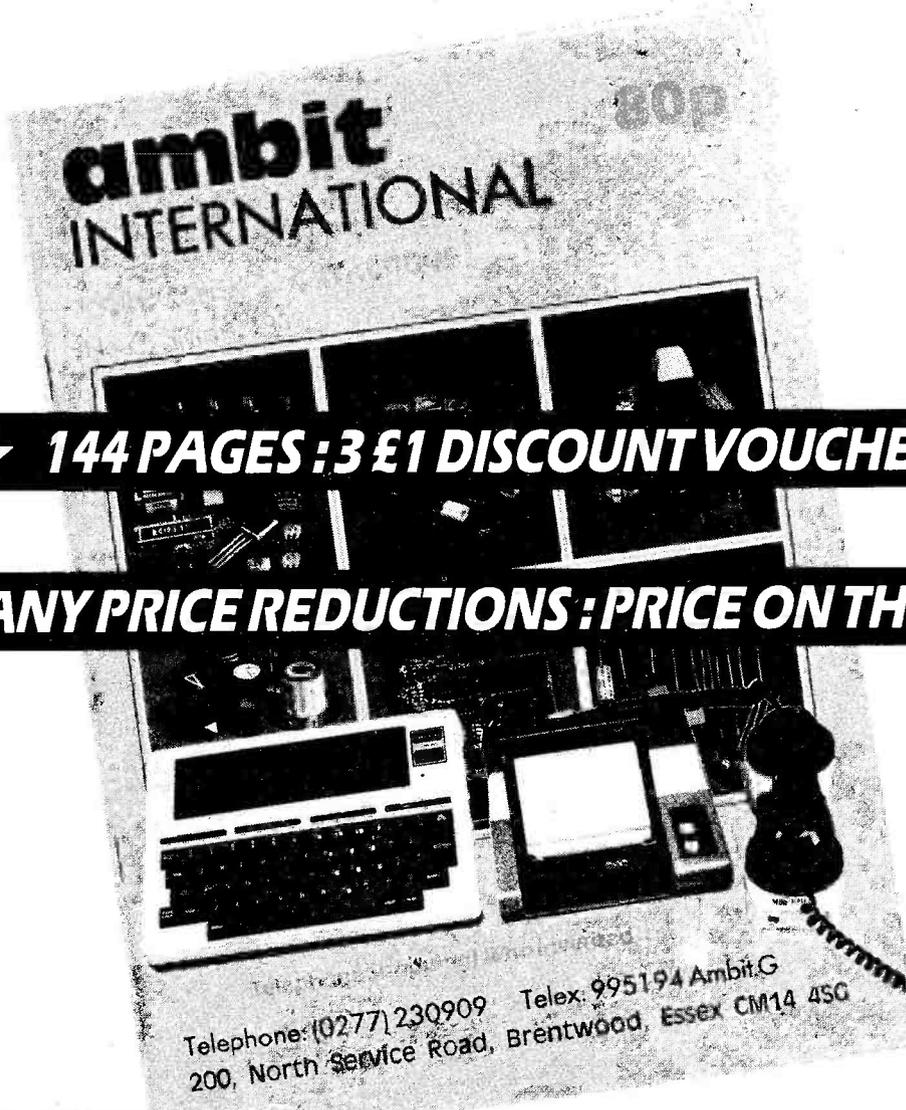SEND US THE COVER FROM ANOTHER COMPONENT SUPPLIERS CURRENT CATALOGUE, PLUS A 40p STAMP, AND WE'LL SEND YOU A FREE COPY OF THE LATEST (SUMMER) AMBIT CONCISE COMPONENT CATALOGUE. ALTERNATIVELY YOU CAN SEND 80p TO THE ADDRESS BELOW.....



★ 144 PAGES : 3 £1 DISCOUNT VOUCHERS

★ MANY PRICE REDUCTIONS : PRICE ON THE PAGE

★ DIRECT FROM.....


ambit INTERNATIONAL

200 North Service Road
Brentwood
Essex
CM14 4SG

Telephone 0277-230909
Telex 995194 AMBIT G
Data 0277-232628 REWTEL))
300 BAUD DUPLEX

MACHINE CODE PROGRAMMING

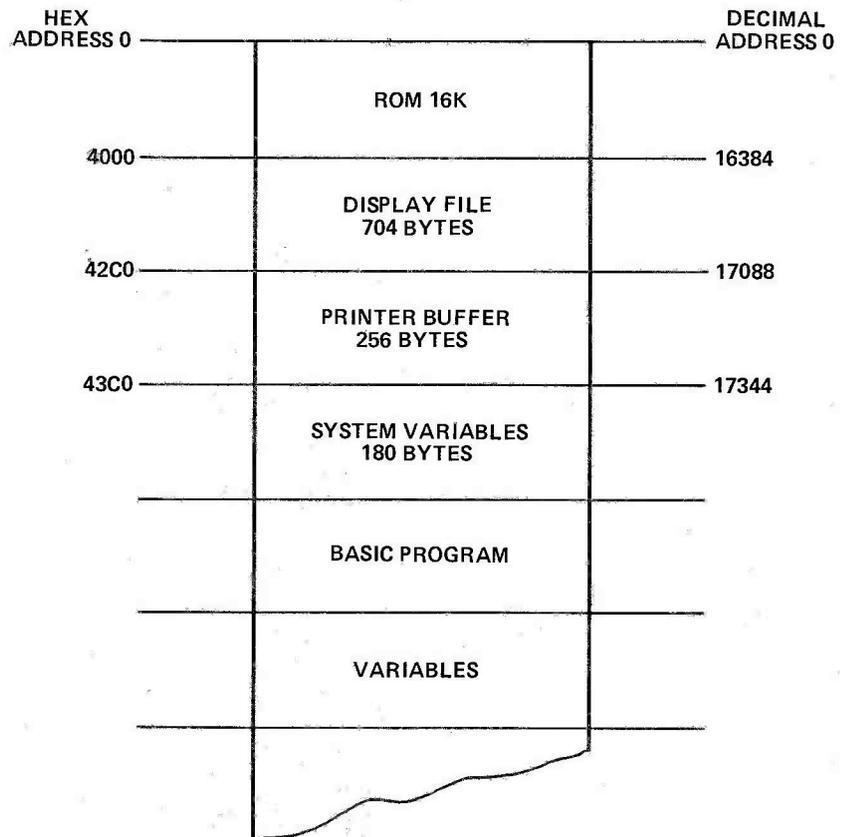In this second part of this series, Bob Bennett looks for implied and immediate addresses on the computer's memory map.



Whereabouts in RAM your machine code program will go depends on the memory structure of your computer. A look at the computer's memory map will show the areas in RAM reserved by the computer for 'housekeeping' duties. These duties consist of keeping tabs on everything that happens whilst the computer is switched on. Figure 5 shows a portion of a memory map for no computer in particular; how it works is fairly simple, but does require a lengthy explanation.

The **display file** is shown as occupying 704 addresses, each of one byte: these 704 bytes store information relating to the picture on the screen. The working area of the screen in our example consists of 32 columns by 22 rows, and 32 times 22 equals 704. The reason I referred to working area is that there are usually two rows at the bottom of the screen reserved for the input data. As a rule the top left hand corner of the screen is position 0,0, and this is the first address in the display file. Suppose that you printed the letter A in position 0,0: the code for letter A would be stored in address 16384.

The **print buffer** is merely a temporary store for data going out to a printer, but this area can often be used by the programmer.

Any good computer handbook has a section devoted

to the **system variables**, which are a series of reserved addresses usually given short names. These addresses contain information, dealing with which comprises the major portion of the housekeeping I mentioned before. Each system variable consists of one, two, or very rarely, three or more bytes. If there is only one byte then the address will usually contain a number, the value of which may determine the action to be taken by the computer. The Spectrum, for example, has a single byte system variable called PIP that contains a number which determines the length of the keyboard click.

If there are two bytes, then the two consecutive addresses of the system variable themselves hold an address. This is usually the starting address of an area in RAM where a particular variable is stored. For example, when you assign letters or strings as variables, the information relating to those variables is held in an area of memory. If you had a system variable called VARS, this would consist of two bytes, and would hold the starting address of that area.

The area of RAM, from the system variables onwards, is the part that is of primary interest to machine code programmers. As your list of variables is added to, or subtracted from, then the area it occupies can fluctuate. This

is true of the area taken up by your BASIC program, as you add or delete lines. Areas in RAM can be reserved for machine code programs, and there is usually plenty of information around telling you how to do it for your particular computer.

How . . .

Once you have found out where to put your program, the next task is to get it there! There is really only one way it can get there, but there are several methods of doing it (that's a bit like saying 'there is only one road to Rome, but there are many means of transportation'). The program is POKEd into addresses, byte by byte. Starting with the first address, and the first byte, the addresses are incremented after each POKE.

If you have never met POKE before it's how you get information into RAM. Consider this example of a direct command, POKE 32000,119 decimal: this means place the decimal number 119 into address 32000. If your computer allows you to use hex direct then the command could be POKE 32000,77 hex. The complementary command to POKE is PEEK, so, after entering the above example, the instruction PEEK 32000 would cause the number 119 decimal to be printed to the screen. Of course, you can only POKE information into RAM, but you can PEEK at either RAM or ROM.

Probably the most widely used method of entering machine code programs into home micros is via a hex loader. If your micro doesn't support hex direct then the hex code has to be entered as a string, sliced and then converted to decimal before POKEing into the addresses. Otherwise, the decimal conversion can be left out. Another method might use the READ/DATA statements if your computer has them.

Assemblers and compilers can also be used to get your program into memory. Taking the assembler first, this is a program that could either be resident in ROM or loaded in via tape, etc. This will take your assembler language statements and convert them into machine code. Before the program can run, however, the statements are checked for validity, and an opportunity is given to edit the program. A compiler is a program, usually loaded into the computer, which converts a higher level language, such as BASIC, into machine language. If the last two methods have to be loaded in then they do use up memory, which is usually a precious commodity. So how the program gets into the computer is a combination of personal preference and what your computer will support.

What . . .

The instruction set, mentioned last month, is where you will find all the instructions you will use in machine code programming. Ideally they will be in tabular form, giving both decimal and hexadecimal notation, and sometimes you might find the binary form given as well. Also they should include the assembler mnemonics, and the number of bytes per instruction. Those of you with Sinclair micros have everything that you need, apart from the byte count, in the handbook. Because the instruction set for the Z80 is very comprehensive I will be using that for the examples I give. Don't worry if your computer doesn't have a Z80 CPU, the same principles will apply.

Don't Forget The Post Code!

Before very long 16-bit micros will be as common in the home as the eight-bit ones are now, but until then I will be dealing only with the eight-bit variety. Addressing modes are simply a way of getting round the fact that ad-

resses require 16 bits, but our data word is only eight bits long. The first addressing mode I'll explain is the implied because it is the simplest, and only one byte long.

Sometimes known as the register direct, the **implied mode** is so named because the data source and destination are implied in the instruction. For example, to load the B register with the contents of the C register requires the instruction 41 hex in the Z80 set. Here the source is the C register and the destination the B register, this could be shown as C→B. Incrementing and decrementing registers, and No OPERATION and RETURN instructions use the implied mode.

NOP, or no operation, is self explanatory, nothing happens (nothing, that is, except a fractional waste of time). This is a very useful instruction that could be used in a timing loop, or to occupy addresses that you intend to overwrite with data later on in the program. Or perhaps you haven't quite decided what to do in one patch of the program. An approximate number of NOPs will reserve the space for you until you have made up your mind. As for the RETURN, this is perhaps the most important instruction you will use. Without it, in some computers, you could be stuck in an infinite loop. In its simplest form, it can be regarded as an instruction to return to the place from whence you were sent — more will be explained later.

All simple register to register transfers use the implied mode, but as an exercise see how many of these instructions you can find in your set. The golden rule is that there is only byte in the whole instruction.

For Your Immediate Attention

The immediate mode is the next easiest addressing mode that you can use. As with the implied, the immediate mode does not involve any addresses, but there are now two bytes per instruction. The instruction 3E hex in the Z80 set means load register A with the number that follows; in the 6502 set the same instruction would be A9 hex. This might have the mnemonic Ld A,n, or M→A, or even MVI A,D8; note well that the names are not CPU instructions; they are just humanised memory aids. That last mnemonic sums everything up nicely because it means, move immediate(ly) into A a data byte of eight bits. Other instructions of this type include add n to a particular register or subtract n from a particular register. Again as an exercise, pick out all the immediate mode instructions out of your set.

Now that we have reached two byte instructions, I'd like to clear up a point that seems to confuse newcomers to machine code programming. The idea that the same byte can represent two different things might seem at first glance to be perplexing, but stop and think. Let me take as an example the instruction above, load A with n. This could be written in a Z80 program as 3E, 3E (or for the 6502,A9,A9). What happens is that when the computer gets to the first 3E it regards it as an instruction, an instruction to load the byte that follows (which also happens to be 3E) into register A. What the second number stands for is up to you, as the programmer, to decide. It may be just a number you want to manipulate, or it could be the code of a character you want to print to the screen. Whatever, the computer recognised the first 3E (or A9), as an instruction requiring two bytes. After carrying out that instruction the computer would carry on with the rest of the program from the instruction which came after the second byte. Every instruction belongs to a class that requires one, two, or more bytes for proper execution. It is the programmers responsibility to ensure that the computer starts off in the right place!

ETI

BRADLEY MARSHALL LTD

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

325 EDGWARE ROAD, LONDON W2 1BN Tel: 01-723-4242 Tlx: 295441

CRIMSON ELEKTRIK

JOIN THE PROFESSIONALS

No	Modules	Price
2580	CE 608 40W Mono	18.26
2581	CE1004 100W 4 Mono	21.30
2582	CE1008 100W 8 Mono	23.90
2583	CE1704 170W 4 Mono	30.43
2584	CE1708 170W 8 Mono	30.43
2585	CE3004 300W 4 Mono	42.60
2585a	FE 908 90W FET Mono	25.65
2585b	FE1704 170W FET Mono	33.48
2585c	BD1 Bridge Unit for Modules	7.13
2608	CPR 1X Pre-Amp Module	41.70

WE ALSO STOCK ALL THE POWER SUPPLIES TO DRIVE THESE MODULES PS. THESE KITS AND MODULES ARE EXCLUSIVE OF VAT

No	Complete Pre-Amp Kit	CK1010	Price
2616	Complete 40W Stereo Amp Kit	CK1040	£80.00
2616a	Complete 80W Stereo Amp Kit	CK1080	£105.00
2617	Complete 100W Stereo Amp Kit	CK1100	£131.00
2618	Add on Moving Coil Kit	MC12K	£21.74
2619	Pre-Amp Power Supply Kit	PSK	£17.39
	TS70 70° Thermal Switch		£2.02
	HS50 50mm Heatsink		£2.44
	HS100 100mm Heatsink		£3.87
	HS150 150mm Heatsink		£5.61

PLEASE NOTE ALL CRIMSON MODULES ARE GUARANTEED FOR 2 YEARS.

VELLEMAN KITS

Some are easy some are hard

No	Description	Price
K610	Mono UU using LEDs.	10.05
K1798	Stereo UU using LEDs	18.77
K1874	Running Light Kit	14.95
K2571	Light Computer with EPROM	36.23
K2569	Three Tone Chime	8.57
K2575	Microprocessor Doorbell 25 tunes	15.53
K2544	Complex Sound Generator	10.26
K2032	Digital Panel Meter	16.61
K2557	Digital Thermometer	26.57
K2545	50Hz Crystal Time Base	12.00
K615	High Precision Stopwatch	50.29

WE STOCK A WIDE RANGE OF BOXES TO HOUSE THESE KITS IN. FROM VERY SMALL TO VERY LARGE 19" MAXIMUM PS. ALL KITS INCLUDE VAT

No	Transistor Ignition	11.16
K2543	Digital Freq Counter for Receivers	45.40
K2555	3 Channel Coloured Light Organ	19.19
K2572	Universal Stereo Pre-Amplifier	6.56
K2574	Universal 4 Digit U/D counter with memory	44.72
K2577	Electric Motor Speed Control	11.17
K2579	Universal Start/Stop Timer	7.45
K2583	Heating Controller	81.45
K1682	Microprocessor Universal Timer (no case)	61.72
K2580	Electronic Power Switch Dimmer	12.37
K2551	Central Alarm Unit	15.48

CALL IN AT OUR SHOP AND SEE DISPLAYS

TELETEXT KIT

This unit will make your TV fully remote control (infra-red) and bring you closer to the amazing world of teletext. The kit can also be updated to incorporate full Prestel, and with a keyboard this can give you full message facilities for ordering foods or sending and receiving messages (E.G) Booking your Holidays!

With a microcomputer as an alternative keyboard the world is even greater adding bulk updating to viewdata computers and receiving telesoftware for implementation to any personal computer.

Even without the Prestel option, Telesoftware from the Teletext pages free!

The full features of Teletext, including subtitles are all included in the basic kit.
An attractive stylish case is available to complement the finished kit.

Basic Teletext Kit (no box) £130 + VAT P/P £2.50
with box £144.95 + VAT P/P £3.00
box by itself £14.95 + VAT P/P 75p

SEE US AT



83

THE PREMIER SHOW

FOR THE TRUE ELECTRONICS ENTHUSIAST
Cunard International Exhibition Centre
November 25, 26th, 27th

ANTEX

Soldering Irons

XS25	25W	5.46+
CX	17W	5.30+
C "iron"	15W	5.20+
CCN "ceramic"	15W	5.00+

Wide range of bits and elements in stock now.
Soldering iron stand 2.40
We stock multicore solder for normal use or fine.

Iso-tip Cordless Iron	31-90+
Miniature low voltage soldering station	13.95+
Oryx50 50W temp controlled	15.50
Oryx super 30	5.90+

All irons are 240V mains. Earth Leakage current is less than 3 ua.
The temperature controlled iron can be controlled within ± 2% temperature range from 200°C to 400°C.

ORYX

COMPONENTS

EDGE CONNECTORS

Device	Price	ZX81 E.C.	2.98
Z80A	3.20	Spectrum E.C.	3.78
Z80A PIO	3.20	VIC 20 E.C.	3.78
Z80A CTC	3.20	50 Way E.C.	3.30
6800	6.50	18 Way E.C.	2.80
6810	3.00	64 Way E.C. Plug	2.50
6821	4.25	64 Way E.C. Socket	4.80
6502CPU	7.50	31 Way E. C. Plug	2.00
2114(200ns)	1.80	31 Way E. C. Socket	2.10
2708	3.00		
2716	3.20		
2732	7.50		
2532	3.50		
2764 (200ns)	11.00		
ADC0816 (8 bit)	14.90		

We also stock 74 series 74LS, C mos, transistors, capacitors, resistors, LED's, zeners, diodes, jack plugs, mains plugs XLR plugs, cannon plugs, arrow switches BNC connectors, reducers, photolaki, developer, PC board, sensitive & normal, boxes, wire cutters, strippers, Edge connectors, pots, batteries, digital pulsers, logic probes, proto-boards, vero board.

This is just a small sample of what we stock, if you like to see more send £1.00 to us for our NEW 1983 CATALOGUE.

We stock a very wide range of opto-devices, from Infra-Red to LED's to Opto-Couplers.
Check us out for competitive prices and helpful service.

BOOKS


*New Books

Please Note. Books are VAT exempt but add £1.00 to cover P/P

A-Z Transistor Equivalent book (2 Volumes)	9.50
The 9900 Family Data Book	10.00
The Opto-Electronics Data Book	4.00
The Bipolar Microcomputer Databook	4.50
The Interface Circuits Data Book	7.00
The TTL Data Book	8.50
MDS Memory Data Book	3.95
The Linear Control Circuits Data Book	4.00
The Voltage Regulator Data Book	4.50
The Power-semiconductor Data Book	9.00
*TTI Data Book Volume I	9.00
*TTI Data Book Volume II	8.00
301 Circuits	5.00
Towers Transistor Equivalent	9.50
Towers Digital Selector	9.95
Towers Linear 10 Selector	7.50
FE Towers Equivalent book	7.50

Why not try our mail order service, it's fast and efficient. We take Barclay, Access, Am Exp, Diners or Cheque. Cheques made payable to Bradley Marshall Ltd.

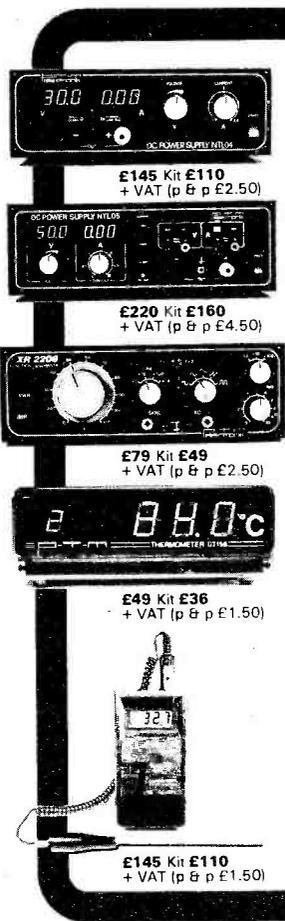PLEASE REMEMBER TO ADD VAT AT 15% + 70p P&P



NTL04 POWER SUPPLY

0-30V, 0-2.5A ● voltage setting with 10T pot. giving 0.1V resolution ● fully protected floating output ● selection of current limiting or current foldback mode ● 3 digit displays for voltage & current with 0.1% FSD accuracy ● automatic dissipation control ● line stability 0.01% for ±10% mains voltage change ● load regulation 0.02% for 100% load change ● ripple 2mV typ. ● transient response <50us

£145 Kit £110 + VAT (p & p £2.50)

NTL05 POWER SUPPLY

0-50V, 0-3A ● voltage setting with 10T pot. giving 0.1V resolution ● fully protected floating output ● automatic changeover from constant voltage to constant current mode ● 3 digit displays for voltage & current can be used for external measurement: range -9.9V to 99.9V, 0.1V resolution; 0 to 5A 0.01A resolution; meter accuracy 0.01% FSD ● automatic dissipation control ● line stability 0.01% for ±10% mains voltage change ● load regulation 0.01% for 100% load change ● ripple 1mV typ. ● current stability with current control 0.1% +1mA typ. ● transient response <50us ● LED function indicators

£220 Kit £160 + VAT (p & p £4.50)

XR2206 FUNCTION GENERATOR

frequency range 10Hz to 220Hz ● linear setting over 8 ranges ● waveforms: sine, triangle, square ● sawtooth & negative pulse at approx. twice the set frequency available ● distortion of the sine wave <1% at 1KHz ● output AC for all waveforms adjustable: 0-10mV, 0-100mV, 0-1V, impedance approx. 5 ohms ● output SYNC square or negative pulse TTL compatible

£79 Kit £49 + VAT (p & p £2.50)

DT155 DIGITAL THERMOMETER

alternate reading of 2 measuring points ● temperature range -55°C to +100°C ● resolution 0.1°C ● 3 digit 16mm red LED display ● automatic changeover of the probes at 10 sec interval with LED indication ● sensor probes can be located at a distance of up to 100m from the instrument ● mains supply for permanent operation ● brushed anodised alum. enclosure 136 x 47 x 115mm (W x H x D) ● choice of 3 sensor probes:

£49 Kit £36 + VAT (p & p £1.50)

LM 135 -55°C to +100°C £10 Kit £8

LM 235 -40°C to +100°C £8 Kit £6

LM 335 -10°C to +100°C £6 Kit £4

DT600 DIGITAL THERMOMETER

precision thermometer with one Pt100 platinum film probe to BS1904 grade 11 covering -70°C to +600°C in 2 ranges: -70°C to +199.9°C, resolution 0.1°C; -70°C to +600°C, resolution 1°C ● lineariser circuit, guarantees accuracy of 0.2% ±1 digit over entire range ● measuring rate 3/sec ● response time 10sec to 99% in moving water ● memory switch ● 3 wire probe connection allows measurement over extension cable up to 25m ● probe with handgrip, 1.5m spiral cable & Spole DIN socket ● battery 9V PP3 for approx. 30hr operation ● low battery indicator

£145 Kit £110 + VAT (p & p £1.50)

Our kits contain all the material required for the assembly including pcb, enclosure, annotated front plate & all electronic parts. A comprehensive assembly manual is provided with step by step instructions & circuit description.

Elektronik



NEW


WOG2206 SWEEP GENERATOR

- makes easy work of establishing and displaying on the oscilloscope frequency responses of equalisers, active filters, crossover networks, audio amplifiers, etc.
- excellent function generator: frequency range 0.2Hz to 200KHz
- professional appearance at low cost
- save pounds and enjoy assembling kit version

function generator: 0.2Hz to 200KHz with linear setting over 6 ranges ● waveforms: sine, square, triangle ● sine wave distortion <1% at 1KHz ● sine & triangle continuously adjustable from 1.5mV to 15Vpp; square wave in 4 steps from 12mV to 12V ● DC offset adjustable for sine & triangle waves sweep generator: sweep rate of 0.5sec to 10 sec ● internal sweep linear 100:1 logarithmic 500:1 (1000:1 typ) ● trigger output 5V TTL

£115 Kit £70 + VAT (p & p £2.50)

Prices are subject to 15% VAT

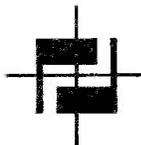

FREL LTD.

ELECTRONIC DESIGN & MARKETING
P.O. BOX 10 LUDLOW
SHROPSHIRE SY8 1DB
TELEPHONE: 0584 5620

Happy Memories

Part type	1 off	25-29	100 up		
4116 200ns	1.25	1.15	1.10		
4816 100ns For BBC comp	1.95	1.85	1.75		
4164 200ns	4.20	3.95	3.85		
2114 200ns Low power	1.15	1.00	.90		
2114 450ns Low power	.95	.85	.80		
6116 150ns	3.35	3.00	2.85		
6116 150ns Low power	4.90	4.40	4.20		
2708 450ns	3.25	2.95	2.80		
2716 450ns 5 volt	2.35	2.10	2.02		
2716 450ns three rail	5.75	5.00	4.65		
2732 450ns Intel type	3.35	3.00	2.85		
2532 450ns Texas type	3.35	3.00	3.00		
2764 250ns	4.20	3.75	3.60		
27128 250ns	16.00	14.30	13.75		
Z80A-CPU	£2.99	Z80A-PIO	£2.99	Z80A-CTC	£2.99
6522 PIA	£3.70	7805 reg	.50	7812 reg	.50

Low profile IC sockets:

Pins	8	14	16	18	20	22	24	28	40
Pence	12	13	14	16	18	22	24	27	38

Wabash soft-sectored floppy discs per 10 in plastic library case:
5 inch SSSD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00
5 inch DSQD £26.35
8 inch SSSD £19.25 8 inch SSDD £23.65 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 50p post & packing to orders under £15 and VAT to total. Access & Visa welcome. 24 hr service on (054 422) 618. Government & Educational orders welcome, £15 minimum. Trade accounts operated, 'phone or write for details.

Happy Memories (ETI), Gladestry, Kington, Herefordshire. HR5 3NY. Tel: (054 422) 618 or 628

BUY NOW WHILE STOCKS LAST!

MULTIMETER SPECIAL Russian type U4324
d.c. Voltage: 0.6, 1.2, 3, 12, 30, 60, 120, 600, 1200
a.c. Voltage: 3, 6, 15, 60, 150, 300, 600, 900
d.c. intensity m/a: 0.06, 0.6, 6, 60, 600, 3000
a.c. intensity m/a: 0.3, 3, 30, 300, 3000
d.c. resistance: 0.2, 5, 50, 500, 500kOhm.
a.e. level dB: 10 to +12, 20,000 DPV.

FANTASTIC SPECIAL PRICE: £12.00 including P/P and VAT

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit in the UK shaver socket.

REF	D.C. Voltage	Current	1+	10+	100+
EOB	4.5V	200mA	50p	45p	32p
EM3	6V	200mA	£1.00	80p	55p
EO9	6V	400mA	£1.50	£1.25	85p

(Postage & Packing: 45p per adaptor or £1.60 per 10, £4.50 per 100).

Please add 15% VAT to the above prices.

MARCO TRADING, DEPT. ET1
THE MALTINGS, HIGH STREET, WEM, SHROPSHIRE, SY4 9EN.
All orders despatched by return of mail. Tel: (0939) 32763



SPECIAL RESISTOR PACKS
1/4W 5 ea. value 10R - 1M
305 off for £3.00
1/4W 10 ea. value 10R - 1M
610 off for £5.00
1/4W 5 ea. value 2R2 - 2M2
365 off for £3.50
1/4W 10 ea. value 2R2 - 2M2
730 off for £6.00



EUROPEAN ADAPATORS

CENTRONICS 306 LINE PRINTERS

Calcomp 563 drum plotter XY plots up to 31" by 120ft!
Immaculate condition
£350 + carriage.
5 Volt 5 Amp Reg Module.
The perfect basis for your custom power supply. **ONLY £2.50p** plus 50p p&p.
12" display scope. Neat Unit but no data hence only **£49.00p** plus £9.50 p&p.
DRE 4000A 5Mbyte hard disc drives brand new boxed **£599.**



professional fast compact line-printer. 80 columns, 120 char/sec. Parallel i/f. Quality at a silly price. Vertical format unit. To inc. operations manual. **ONLY £129.00.**
Carriage (England) **£17.50.** Tech manual (230 pages) **£10.00.**



FLOPPY DISC DRIVES

Fantastic **MEMOREX 550 8"** discs mounted in attractive case with power supply and fan. Shugart standard 50 way interface. Space for second drive. **£149.00** (carr. £9.50).

MAWSON ASSOCIATES
124 Lennard Rd, Beckenham, Kent BR3 1QP

WE ALSO BUY COMPUTERS AND COMPUTER PERIPHERALS

01-778 3600

Callers welcome by appointment s/h items sold working but not g'teed

MULTISWITCH

Light seeks switches; in fact, lots of switches: object, turning on (and off). Bright idea by D J Rayner; development by Dave Bradshaw.

Have you ever wished you could have extra light switches controlling the same light, yet baulked at the idea of ripping out your plastering to install those four-way mains cables that this necessitates? Figure 1a shows what would be involved in wiring up such a system in the conventional way.

Never fear, help is at hand, in the form of the ETI Multiswitch. The equivalent circuit diagram is shown in Fig. 1b. In fact this diagram

doesn't show all the unit's advantages; here are a few more:

- all wiring is at earth (or +5 V relative to earth) so there's no need to use mains cable. You can use the thinnest cable you can get hold of, so it can be concealed fairly easily without the need to chase it into the wall;
- similarly, the switches do not have to be mains-rated, although you can leave your existing switches in place and use them;
- you can have up to eight

switches all controlling the same light, and you can add or remove switches without having to alter any of the rest of system;

- finally, as the light can be switched on and off from lots of different positions, it's likely to be switched on and off quite a lot! Zero voltage switching can improve bulb life dramatically under these circumstances, and so the unit has been designed to allow the light to come on only when the line voltage is close to zero.

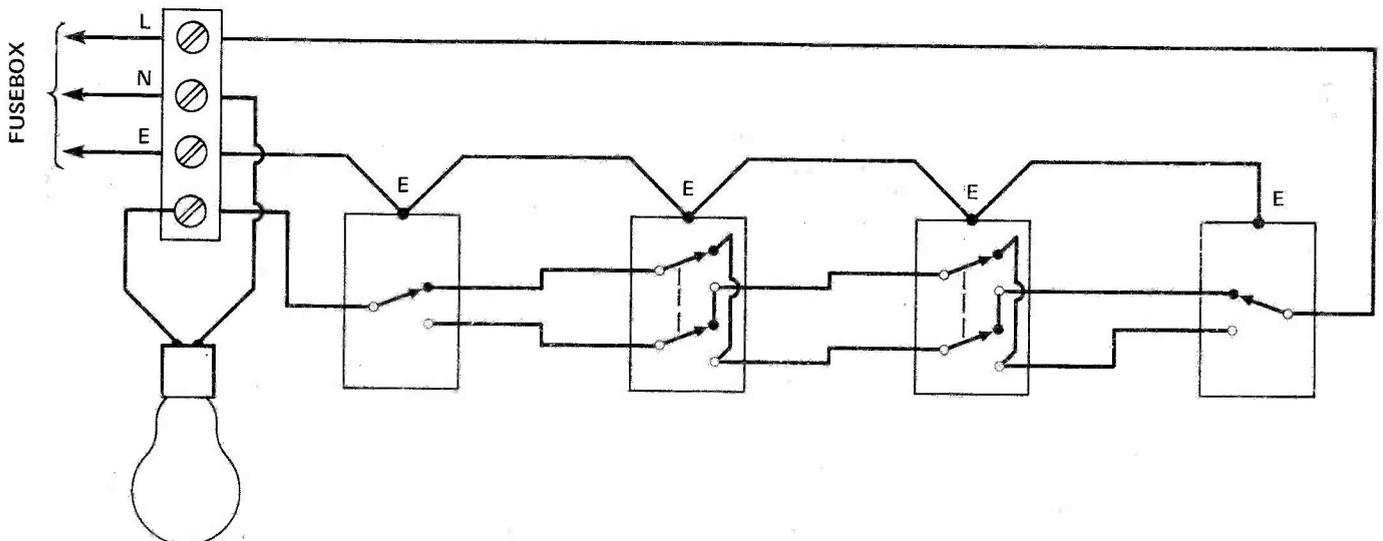


Fig. 1a Ah, in the good old days this was the circuit you'd have to use to switch a light from more than a couple of switches; it was a good circuit — it kept many a plasterer in gainful employment, not to mention the copper mills . . .


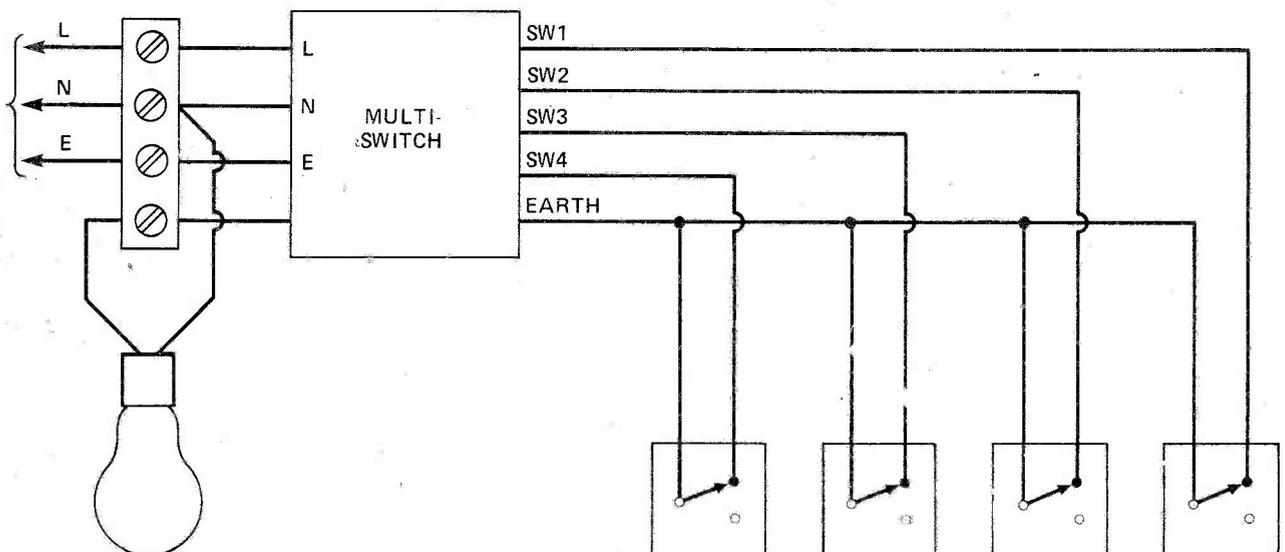


Fig 1b . . . then those young heathens from ETI came along and designed a thingummy that didn't require big thick wires to be buried in the wall — such is progress.

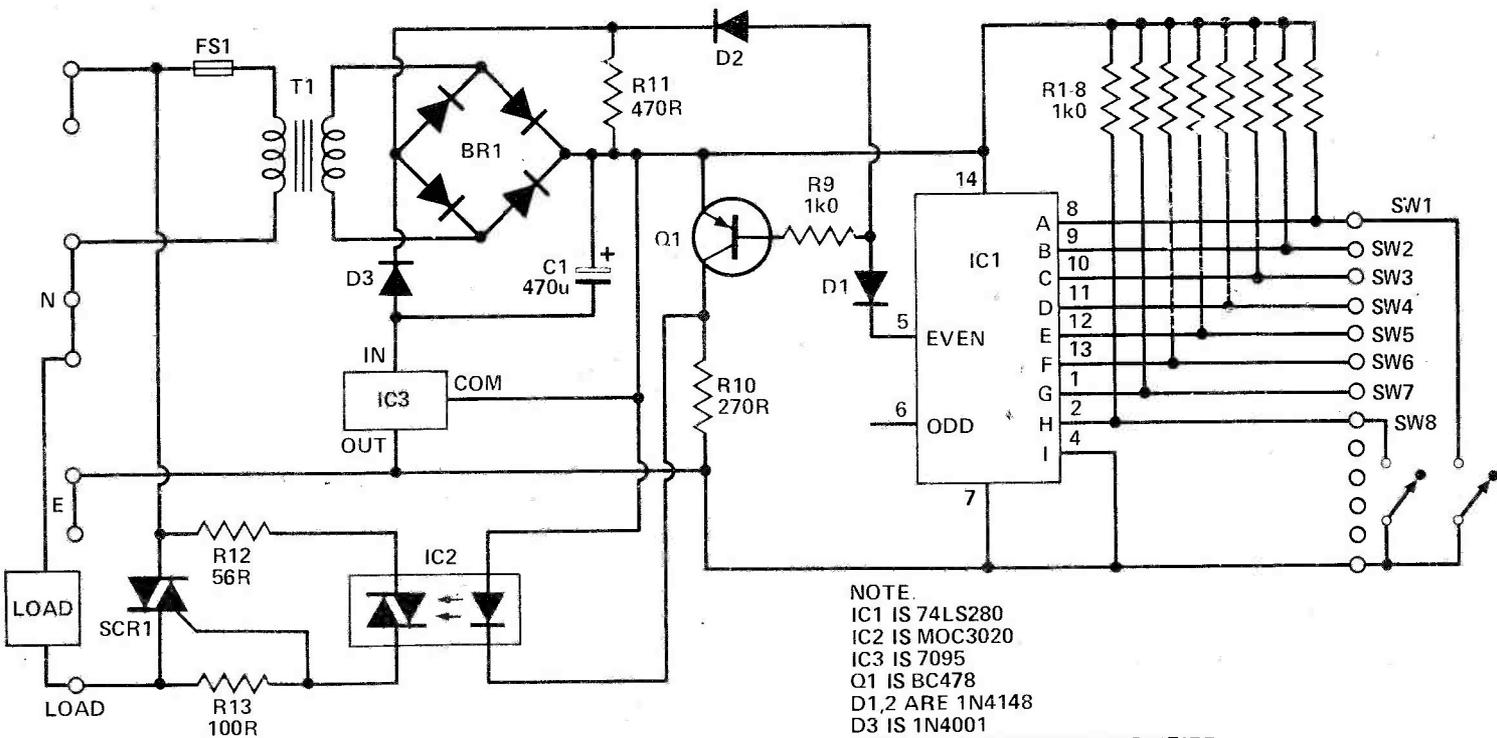

NOTE.
 IC1 IS 74LS280
 IC2 IS MOC3020
 IC3 IS 7905
 Q1 IS BC478
 D1,2 ARE 1N4148
 D3 IS 1N4001
 BR1 IS 1A 50V BRIDGE RECTIFIER
 SCR1 IS 400V 4A TRIAC TIC246D

Fig. 2 Circuit diagram of the thingummy.

The idea for this unit germinated when it was noticed that the Karnaugh map required for such a unit was exactly the same as that for a parity checker, ie the output should change state when one and only one of several inputs changes state (ie, a switch goes from open to closed or vice-versa).

Unfortunately, there is no readily available CMOS parity checker (at least, not that we could find), and therefore the circuit had to be implemented using TTL. However, once it was decided that a PSU had to be designed, it was noticed that for very little extra in the way of components, the unit could also be made to perform zero voltage switching, as mentioned already.

Construction

Not very much needs to be said about the construction of the PCB itself, though it should be pointed out that mains is present on about half of the board, and it should be accorded with suitable respect. You can finish it off by installing it in a suitable plastic or metal case — note that if you use a metal case it must be earthed. Make holes at opposite ends for the mains cables and the switch wiring.

Installation

The unit is intended to be installed well out of the way of tiny,

IC1 is the parity checker. All inputs are pulled high by R1 to 8, unless any of the switches SW1 to 8 are closed. Fewer switches may be used, and unused inputs left unconnected. We have left you the option of using either even or odd parity outputs, so that you can arrange for the lights to be either on or off with all the inputs high.

If the parity is odd, then the even output from IC1 will be low, the base of Q1 will be pulled low via D1 turning it on, and the LED in IC2 will be extinguished, so that SCR1 will also be off.

The extra circuitry to detect zero voltage crossing consists of D2, D3 and R11. When no current is flowing from BR1, D3 frees the negative output of BR1 from remaining at the voltage at the negative end of C1. Thus the negative output voltage from BR1 will rise to the positive supply voltage, pulled up by R11. Q1 can only turn off when this voltage is close to the positive supply voltage (and when the even output of IC1 is high). When Q1 turns off, the load will be energised via IC2 and SCR1.

If you need to drive only a very small lamp, you could drive it directly using just IC2, and omitting SCR1. However, this risks blowing IC2 should the bulb blow (it's not uncommon for light bulbs to go momentarily S/C when blowing).

RESISTORS (all $\frac{1}{4}$ W 5% unless stated)
 R1-8 SIL resistor pack, 8 by 1kO
 R9 1kO
 R10 270R
 R11 470R, $\frac{1}{2}$ W
 R12 56R
 R13 100R

CAPACITOR
 C1 470 μ 16V PCB type

SEMICONDUCTORS
 IC1 74LS280
 IC2 MOC3020 opto-triac
 IC3 7905 regulator (-5V)
 Q1 BC478 or similar
 D1, 2 1N4148 or similar
 D3 1N4001 or similar
 BR1 1A 50V bridge rectifier
 SCR1 400V 4A(min) triac, TIC246D or similar

MISCELLANEOUS
 Transformer (mains to 9V + 9V, 3VA total, PCB mounting, see Buylines); 20mm fuse (0A5 max) plus PCB mounting holder; PCB-mounting screw terminals, vertical (2 off); PCB; case; veropins for switch connections; switch to choice (see text).



BUYLINES

The transformer that the PCB is designed for is available from Rapid Electronics, and they sell it as their standard 3VA PCB mounting type. The PCB is, as ever, available through our PCB service.

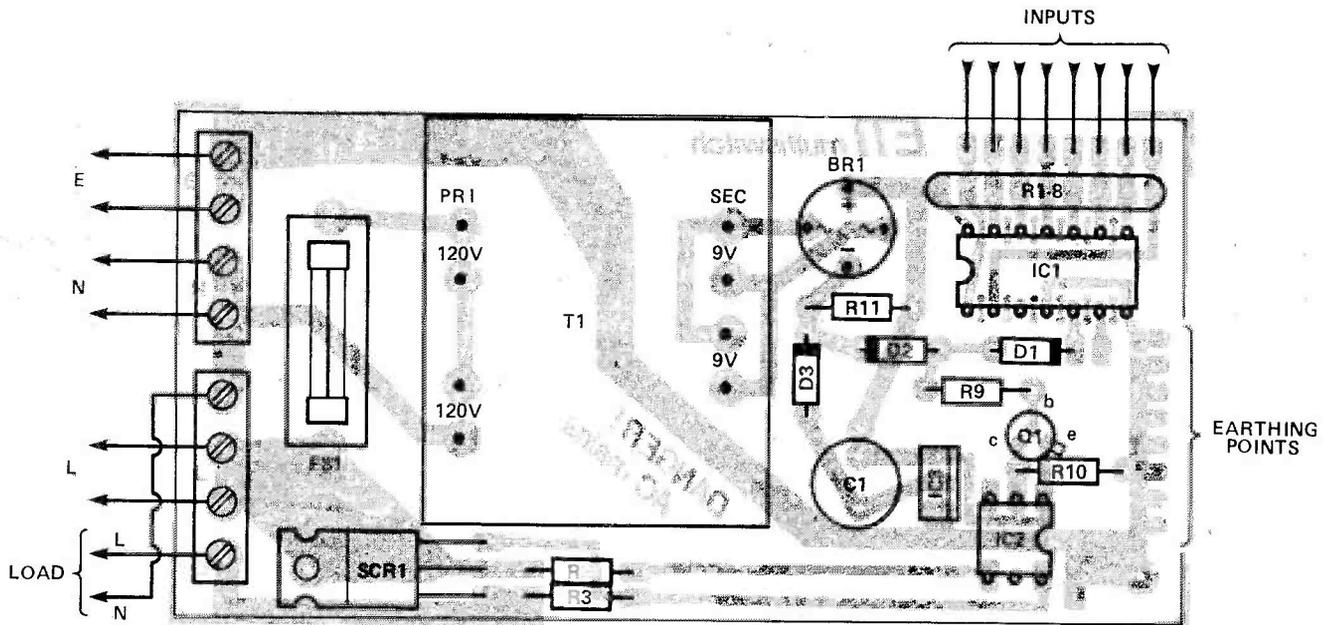


Fig. 3 Overlay diagram of the thingummy. Note that R11 gets a little warm and should be mounted standing slightly proud of the board.

inquisitive fingers, and it is **not** suitable to be treated as anything but a piece of electrical wiring hardware. The screw terminals are **not** intended to support either the weight of the unit, or of a light fitting, etc. If you do use the unit

with flex, rather than fixed cable wiring, then you must anchor the cable in some way, by using suitable cable glands for instance.


Fig. 1b shows the wiring diagram if you're using the unit in a new system; alternatively, you can

wire up an existing two-position circuit (provided it's in good condition) as just one switch, by earthing one end and connecting the other as an input to the Multiswitch.

ETI

THE VICTORY ORGAN

- * Exciting range of authentic voices
- * Preset sounds—Piano, Harpsichord, Hawaiian Guitar (with glide), Banjo (with repeat), Accordion
- * 16 modern rhythms with superb sounds including handclap
- * Full range of 'Easi-Play' features * Custom Programmed ROM
- * Walking Bass on Lower Manual and Pedals
- * Real wood veneer cabinet with American walnut finish
- * The only organ with update facilities for synthesizer and "add-a-chord" unit
- * Starter kit from £98.80 + VAT
- * Full kit £280.54 + VAT Carriage extra on kits

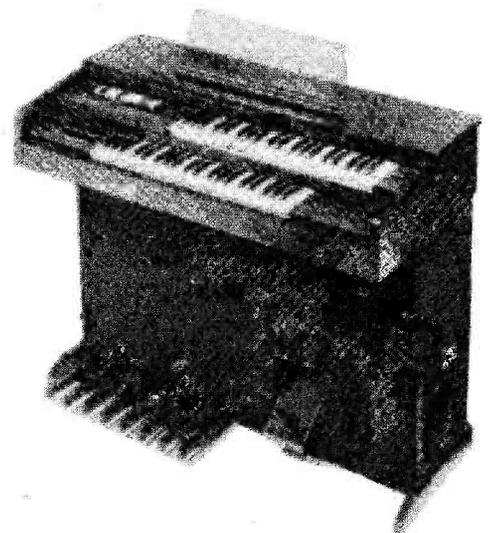

Send for a demonstration tape today only £1.95 inclusive. Hear the difference yourself.

Full details & specification on request

LEIGHTON ELECTRONIC SERVICES

17 BRIDGE STREET, LEIGHTON BUZZARD, BEDFORDSHIRE LU7 7AH

TELEPHONE (0525) 382504

pantechnic

THE POWERFET SPECIALISTS

OEM USERS

Pantechnic present the most adaptable high powered amplifier ever.

FET SYSTEM AMP

Features:

- HIGH POWER. 1.2KW (single ended).
 - LOW VOLUME. 1/15 Cubic foot inc. Heat Sink.
 - VERSATILE. Delivers more than 1KW into 1/2 to 8 ohms.
- OR 2 x 600W into 2 to 8Ω
OR 4 x 300W into 2 to 4 Ω (200W into 8Ω)
OR { 1 x 600W into 2 to 8Ω
1 x 300W into 2 to 4 Ω
1 x 150W into 4 to 8 Ω

Etc. Etc.

Having been closely involved in a wide variety of OEM applications of their amp boards, Pantechnic became aware of numerous implementation problems often left untackled by other amp board manufacturers. These problems specifically of size and thermal efficiency became particularly aggravated at high powers and considerably lengthened OEM product development time.

By including thermal design in the totality of board design it has been possible to reduce the size of the electronics, and increase the efficiency of the transistor to heatsink thermal circuit. The combined effect of this has been to dramatically increase the volumetric efficiency of the amplifier/heatsink assembly. The **SYSTEM** Amp offers 1.2KW of power in a space of 180mm x 102mm x 77mm, excluding PSU and Fan.

The basis of this considerable advance is the PANTECH 74 Heat Exchanger, newly designed and manufactured by us. By eliminating the laminar air flow found in conventional, extruded heat sinks, heat transfer to the environment is greatly enhanced.

The flexibility of the 1.2KW amp stems from its division into 4 potentially separate amplifiers of 300W each (downrateable with cost savings to 150W.) These can be paralleled, increasing current capability or seriesed (bridged in pairs) doubling voltage capability. In consequence a large variety of amplifier/load strategies can be implemented.

Pantechnic offer a full range of customising options including DC coupling, ultra high slew etc. Contact Phil Rimmer on 01-800 6667 with your particular application problem.

OTHER POWERFET AMPLIFIER MODULES

Model	Price	Range (RMS)	Dyn-load	Notes
*PFA100	21.96	50-150W	4, 8, 16	Physically small (32 x 78 x 108mm)
*PFA200	29.52	100-300W	4, 8, 16	High watts/£ ratio
PFA/HV	36.04	200-300W	4, 8, 16	5dB dynamic headroom Drives 70V line direct.
*PFA500	45.22 55.33	250-600W	2, 4, 8, 16	25A cont. output current. mounted on type 74 Heat Exchanger (see below).

*The power output of these amplifiers can be increased by approx 15% with no diminution in quality by adding PSU102 (£7.61) to your existing power supply.

Some Other Products & Components

Type 74 Heat Exchanger. Dissipates 300W (1.2KW blown) £7.50.
25A 400PIV Bridge Rect. £2.17

100,000uF 100V cptn. grade with clip £9.75

PAN20 Pre-amplifier module. Very low noise and distortion £8.48

PAX2/24 2 Way active crossover (specify frequency) £10.10

PAX3/24 3 Way active crossover (-do-) £19.50

PSU103 Powers 2 x PAN20 + 2 Xovers £6.91

PAN1397 20W power amp. (LOW THD) £5.04

PSU101 Powers 2 x PAN1397 £3.43

Transformer for 101 £4.30 (inc. postage)

TOROIDAL TRANSFORMERS

with special low flux windings

Nom. VAC	160VA	225VA	300VA	500VA	625VA	750VA
40-0-40	10.43	12.00	13.04	—	—	—
45-0-45	—	12.00	13.04	16.96	—	—
50-0-50	—	—	—	16.96	19.84	22.00
70-0-70	—	—	—	16.96	—	—

(for PFA/HV)

Transformer prices include postage. Ask for leaflet "Choosing a Transformer."

Carriage £1, Add VAT at 15% to all prices.

THE POWERFET SPECIALISTS

pantechnic

Mail order only to

Dept ET1/11 148 Quarry Street, Liverpool L25 6HQ

Telephone: 051-428 8485

Technical enquiries

Phil Rimmer 01-800 6667

SECURITY

Build your own system and SAVE POUNDS!

DIGITAL ULTRASONIC DETECTOR US 5063



NEW

- 3 levels of discrimination against false alarms
 - Crystal control for greater stability
 - Adjustable range up to 25ft.
 - Built-in delays
 - 12V operation
- This advanced new module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions. The module has a built-in exit delay and timed alarm period, together with a selectable entrance delay, plus many more outstanding features. This advanced new module is available at

only £13.95 + V.A.T.


ULTRASONIC MODULE US 4012



- Adjustable range from 5-25ft.
- This popular low cost ultrasonic detector is already used in a wide range of applications from intruder detectors to automatic light switches and door opening equipment, featuring 2 LED indicators for ease of setting up, the unit represents outstanding value at

£10.95 + V.A.T.

INFRA-RED SYSTEM IR 1470

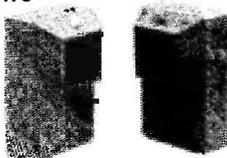

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft, operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications, the system is available at

only £25.61 + V.A.T. Size 80 by 50 by 35mm.

POWER SUPPLY & RELAY UNIT PS 4012

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470. Price £4.25 + V.A.T.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110db at 2 metres. Operating from 9-15V, the module contains an inhibit facility for use in 'break to activate' circuits. Price £2.95 + V.A.T.

5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110db at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £4.95 + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-pos. key switch intended for use with the CA 1250. Price £3.43 + V.A.T.

All modules are supplied with comprehensive instructions.

Units on demonstration.
Shop hours 9.00-5.30 p.m.
Wed. 9.00-1.00 p.m.
SAE with all enquiries.

Add 15% VAT to all prices.

Add 50p post & packing to all orders.

Order by telephone or post using your credit card.



ALARM CONTROL UNIT CA 1250



The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation, or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for switching external loads
- Test loop facility

Price £19.95 + V.A.T.

SIREN & POWER SUPPLY MODULE PSL 1865



NEW

A complete siren and power supply module which is capable of providing sound levels of 110db at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 or US 4012 to form a complete alarm.

Price £9.95 + V.A.T.

HARDWARE KIT HW 1250



only £9.50 + V.A.T.

NEW

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

HARDWARE KIT HW 5063




only £9.95 + V.A.T.

NEW

This hardware kit provides the necessary enclosure for a complete self-contained alarm system which comprises the US 5063, PS 1865, loud speaker type 305 and key switch 3200. Attractively styled, the unit when completed, provides an effective warning system without installation problems.

ULTRASONIC MODULE ENCLOSURE

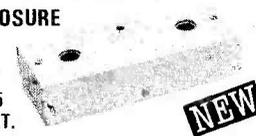

only £2.95 + V.A.T.

NEW

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

RISCOMP LIMITED

Dept. ET16
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326

Midwich

EAST ANGLIA'S LEADING SUPPLIER OF MICROCOMPUTERS AND COMPONENTS TO EDUCATIONAL ESTABLISHMENTS.

BBC Microcomputers

Model B 346.95
Model B + Disc Int 431.95
NB Credit cards are not accepted in payment for BBC Microcomputers.

BBC Micro Econet

Full range of products available. Installation service available

BBC Compatible Disc Drives

Cased drives, finished to match the BBC Micro are supplied complete with connecting cables, manual and utilities disc.
All single cased drives may be expanded to dual configuration by the addition of the appropriate uncased mechanism.

Disc capacity	Single	Dual	Uncased
100K	195.00	335.00	142.00
200K	235.00	449.00	216.00
400K	290.00	545.00	260.00

Trade/quantity discounts are available.

BBC Micro Upgrade Kits

BBC A2B Complete A TO B 44.75
BBC3 Disc Interface 84.95
Fitting service available.

BBC Micro Connectors

BBC21 Printer Cable 7.50
BBC22 User Port Connector & Cable 2.45
BBC23 Cassette Lead 3.50
BBC24 7 Pin Din Plug 0.60
BBC25 6 Pin Din Plug 0.60
BBC26 5 Pin Din Plug 0.60

BBC Micro Accessories

BBC45 Joysticks 11.30

BBC Micro Software

View Wordprocessor 52.00
1.2MOS 10.00

BBC Micro Software

Full range available. Please telephone for stock position.

Memories

2114L 200NS D1 0.80
2706 450NS D2 2.85
2716 450NS D1 2.45
2716 350NS D1 4.85
2716 3 Real D1 7.25
2532 450NS D2 3.45
2732 450NS D1 3.45
2732 350NS D1 5.45
2734 300NS D1 7.55
4116 150NS D1 0.85
4116 200NS D2 0.80
4118 150NS D1 3.25
5516 200NS D2 9.45
6116 150NS D1 3.00
6116 Low Power 150NS D2 4.85
4164 200NS TI D3 3.95
4164 200NS NEC D3 3.95
4516/4816 100NS D2 2.25
4532 200NS D2 2.95

8080 Family

8085A D4 3.50
8212 D1 1.10
8216 D1 2.45
8224 D2 2.10
8228 D3 3.27
8251A D5 2.50
8253 D4 4.00
8255A D5 2.25

6500 Family

6502 D3 3.25
6502A D3 5.00
6520 D1 2.50
6520A D1 3.16
6522 D5 3.00
6522A D5 5.50
6532 D2 5.50

Floppy Disc Controllers

8271 48.00
FD1771 D5 15.00
FD1791 D6 22.00
FD1783 D6 23.00
FD1795 D6 28.00
FD1797 D6 28.00
WD1691 D2 12.00
WD2143-01 D2 6.99

6800 Family

6800 D7 2.25
6802 D5 2.50
6809 D6 6.30
6810 D1 1.15
6821 D3 1.00
6840 D4 3.75
6845 D5 6.50
6850 D2 1.10
68468 D2 7.30
68B00 D7 5.25
68B09 D6 12.00
68B10 D1 2.26
68B21 D3 2.20
68B40 D4 6.00
68B50 D2 2.20

Z80 Family

Z80 ACPU D2 2.99
Z80 BCPU D2 9.00
Z80 ACTC D1 2.60
Z80 BCTC D1 9.00
Z80 ADART D1 5.60
Z80 ADMA D2 6.95
Z80 AP10 D1 2.75
Z80 BP10 D1 9.00
Z80 AS10 D4 9.00

Interface Devices

6402 3.80
75107 0.47
75110 0.56
75150 0.64
75154 0.77
75160 2.56
75161 2.80
75162 3.95
75172 1.95
75173 1.44
75174 1.95
75175 1.44
75182 0.50
75183 0.50
75188 0.37
75189 0.37
75451 0.22
75452 0.22
75453 0.22
75454 0.22
75458 0.88
75491 0.31
75492 0.42
75493 0.42
AY31015 D2 3.00
AY31270 D1 6.47
AY38510 D6 4.40
AY53600 D2 6.70
DP8304 D1 2.50
MC1488 D1 0.37
MC1489 D1 0.37
NC3242A. D1 6.30
MC3446 D1 2.50
MC3448A D1 3.75
MC3460 D5 7.30
MC3487 D1 2.00
MC14111 D1 7.65
MC14112 9.45
RO32513L D1 6.50
RO32513U D1 6.50

Regulators

78L05 0.30
78L12 0.30
78L15 0.30
7805 0.40
7812 0.40
7815 0.40
7905 0.45
7912 0.45
7915 0.45
LM309K 1.20
LM317R 2.40
LM323K 4.50
LM338K 6.25

Data Convertors

UPD7002 D1 4.26
ZN425 D1 3.45
ZN426 D1 3.00
ZN427 D1 5.99
ZN428 D1 4.75
ZN429 D1 2.10
ZN432 D1 13.00
ZN449 D1 2.55

Crystals

1MHz 2.75
1.8432MHz 1.92
4MHz 0.64
8MHz 0.86

DIL Sockets

Pins	Tin	Gold	W/W
8	7	16	25
14	10	26	35
16	16	29	40
18	13	33	50
20	15	37	60
22	17	38	65
24	21	46	70
28	24	55	80
40	30	76	99

ZIF Sockets

24 Pin 5.75
28 Pin 8.20
40 Pin 9.75

Data sheets are available on items marked D.

Prices are as follows:
D1 0.75 D5 2.00
D2 1.00 D6 3.00
D3 1.25 D7 4.00
D4 2.00 D8 5.00

A full range of the following products is carried in our FREE catalogue

- ★ 74LS Series TTL
- ★ 4000 Series CMOS
- ★ TL Bipolar Memories
- ★ 9300 Series Micros
- ★ Crystals
- ★ IDC, Card Edge & D-Type Connectors
- ★ Dip Jumpers
- ★ Monochrome & Colour Monitors (NEC & KAGA)
- ★ Custom Cable Assemblies
- ★ Eeprom Programmers & Erasers
- ★ Custom Cable Assemblies

SPECIAL OFFER! SPECTRUM 32K UPGRADE KIT £24.95

Carriage. Orders up to £199 are sent by 1st class post and £200+ by Securitor.
£100.50 (£100 + £19.25 £200+5.00 by Securitor.
Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice.
Quantity Discounts are available on many products, please ring for details.
Official Orders are welcome from Education Establishments, Government Bodies and Public Companies.
Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month.
Credit Cards are accepted (Access and Visa) for telephone and post orders and NO SURCHARGE is made.
Out of stock items will follow automatically, at our discretion, or a refund will be given if requested.

T.V. SOUND TUNER

BUILT AND TESTED

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 3/4" x 8 1/2" x 3 1/4" E.T.I. kit version of above without chassis, case and hardware. £12.95 plus £1.50 p&p.



COMPLETE WITH CASE

£24.95 + £2.00p&p.


Practical Electronics Stereo Cassette Recorder Kit COMPLETE WITH CASE

SPECIAL OFFER!

ONLY £31.00 plus £2.75 p&p.

- NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

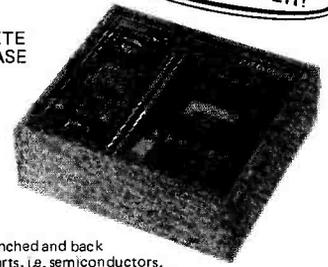Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.



STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July '81). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM-ferrite rod, FM-75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

SPECIAL OFFER!
£13.95 + £2.50 p&p.

STEREO CASSETTE DECK

Stereo cassette tape deck transport with electronics. Manufacturer's surplus - brand new and operational - sold without warranty.

£11.95 plus £2.50 p&p.

Just requires mains transformer and input/output sockets and a volume control to complete. Supplied with full connection details.



125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PCB board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Stereo/mono mains power supply kit with transformer: £10.50 plus £2.00 p&p.

SPECIFICATIONS.
Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £10.50 BUILT £14.25
+£1.15p&p +£1.15 p&p.

AUDAX 8" HIGH QUALITY 40 WATTS RMS BASS/MIDRANGE

Ideal for either Hi-Fi or Disco use this speaker features an aluminium voice coil a heavy 70mm diameter magnet. Frequency res: 20Hz to 7KHz. Impedance: 8 ohms. £5.95 +£2.20 P&P.

AUDAX 40W Ferro-Fluid Hi-Fi Tweeter
X/over on 5kHz - 22kHz. 60mm square. 8 ohm. £5.50 +60p p&p.

All mail to: 21E HIGH STREET, ACTON, W3 6NG.

Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/5/83 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

SPEAKER BARGAINS

2 WAY 10 WATT SPEAKER KIT

8" bass/mid range and 3 1/4" tweeter. Complete with screws, wire, crossover components and cabinet. All wood pre-cut - no cutting required. Finish - chipboard covered wood simulate. size 14 1/2" x 8 3/4" x 4". PAIR for ONLY £12.50 plus £1.75 p&p.

ALL CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT.



MULTIPLE OUTPUT PORT

Is your computer a megalomaniac at heart? Here's a circuit that will allow it to have up to 40 slaves, by Stephen Huckstepp.

This project is intended for use with virtually any computer, the only prerequisite being access to the data and address buses and to the control signals IORQ and WR or their equivalents.

There can be up to 40 on/off outputs from the port, all of which can be used to drive external circuitry. The port is expanded in groups of eight, with eight being the minimum (well, you could have a port with no outputs if you really wanted . . .). As the board makes provision for the maximum number of outputs, subsequent expansion up to the maximum is no problem.

However, the main draw-back is that this circuit will be fairly slow and software-intensive to operate. This is because each write operation outputs to only one bit in any group of eight outputs, but to each group simultaneously. So, for instance, while writing to bit 3 in group 2, you will be writing to bit 3 in all the other groups (though not the same information). Most of the software you will need will involve setting up

the data in the correct format to go to the port.


Provision has not been made to drive equipment that requires a handshake control. However, an alternative use for a spare output data line from the computer might be as a 'data valid' signal, rather than as a clear as suggested in the 'How It Works' section.

Construction

There is very little to say about the construction of this project except to recommend that the usual CMOS precautions should be followed. Although all the devices used are relatively inexpensive, it is probably still a good idea to use IC sockets, as failed device could be a !!!! to remove.

When connecting up to the computer, note that the lines for D5 and D7 have been transposed on the PCB. Check your computers memory map to set up a suitable address for the port, and use the links to make the port occupy this address.

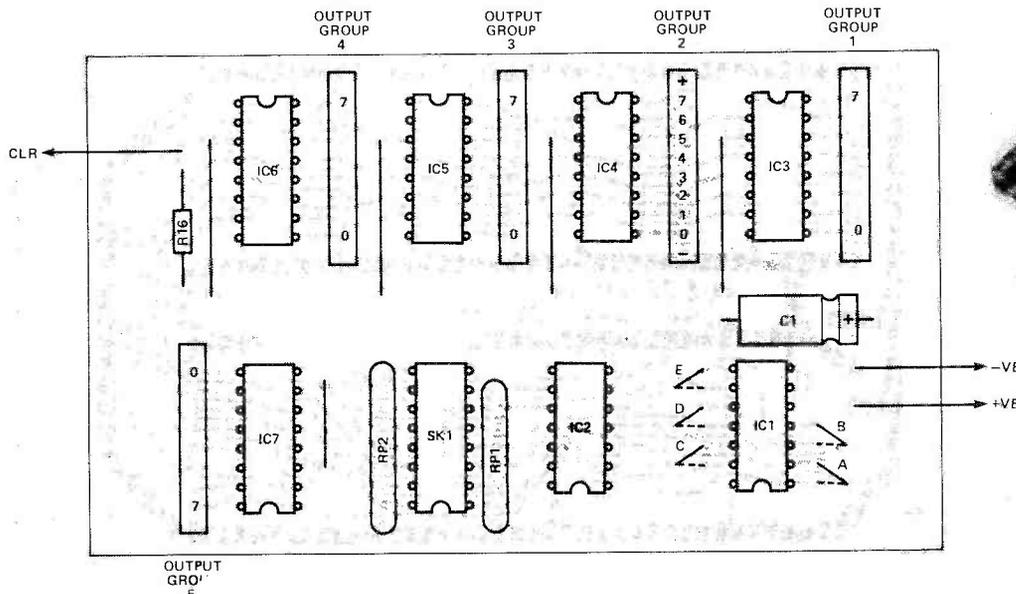Overlay diagram of the multiple output port; note that the pin-out for SK1 is given on the circuit diagram.



BUYLINES

Nothing in this project should cause any difficulties. The SIL connectors are available from Maplin and others, the ICs are widely available, and the PCB is available through our very own PCB service.

PARTS LIST

RESISTORS

- R1-7 SIL resistor pack, 7 by 10k
- R8-15 SIL resistor pack, 8 by 10k
- R16 10k 1/4W 5%

CAPACITOR


- C1 100µ 6V (min) tubular electrolytic


SEMICONDUCTORS

- IC1 4069
- IC2 4072
- IC3-7 4099

MISCELLANEOUS

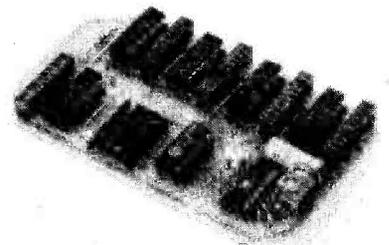- SK1 16-pin DII socket and header plug
- SK2-5 10-way SIL connectors, 0.1" pitch
- PCB; case to choice; wire, etc.



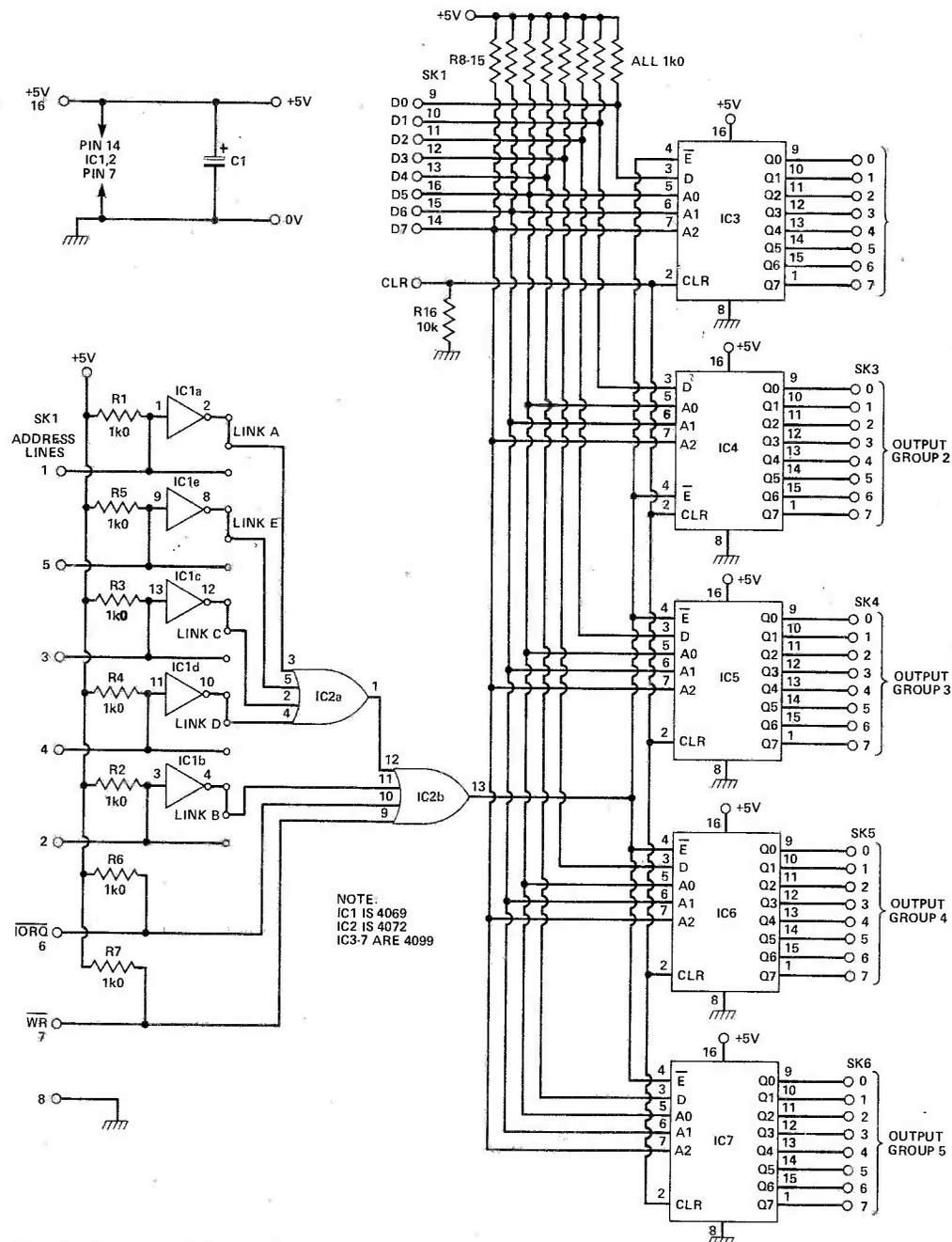

Circuit diagram of the multiple output port.

HOW IT WORKS

This circuit is based on the 4099 eight-bit latch, used for IC3 to 7, which is one of the cheaper low-power latches that are readily available. The circuit shown is relatively slow to operate, but is very cheap to build!

Five address lines are used to select the port; the inverters, IC1a to e can be selected in or out using the links, so as to set up an address that is convenient.

IC2 decodes both the address and the port request lines, IORQ and WR. The output from IC2b enables all the chip select lines on all the latches. Thus

when a write operation occurs, the same bit on all the latches is written to at once.

Of the data bits, D5 to D7 are used to address the bit to be written to. The remaining data bits are the data that is to be written, D0 being the data for the selected bit in the first latch (IC3), D1 for the second latch (IC4), etc.

Because of the mode of addressing selected, if you want to leave a particular bit in one latch unchanged, while altering the same bit in the other latches, you must re-write the same data as

before.

There is no need to install all the latch ICs if you do not need them, the system will still work with just one latch in position (though you'll only get eight outputs, of course). If you don't use the full capability, you may find it useful to connect the clear (CLR) input to one of the unused data bits.

Note that the data inputs D5 to D7 feed inputs on all five latches; this may make it necessary to buffer these lines at the computer, depending on what other peripherals are connected to the data bus.

CRICKLEWOOD ELECTRONICS LTD

40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET.
TELEPHONE 01-452 0161 TELEX 914977

ALL PRODUCT FIRST GRADE FRANCHISED SOURCE

All advertised items are guaranteed to conform with, or surpass manufacturer's current data sheets. This list represents a fraction of our stock. New items are constantly being brought into stock. Cricklewood Electronics keep up with the times. Please phone about all your electronic needs.

HOW TO ORDER? Mail order with cheque, P.O., Bank Draft, Registered Cash, or write Credit Card* number on order with signature. Please add 60p post, packing and insurance, more for heavy goods.

Stocking parts other stores cannot reach!

Securicard available. Phone your order quoting Credit Card* number. Call in. You will be more than welcome. Official orders accepted from Govt. Depts., Schools, Colleges, Armed Service Establishments, P.L.C.s and approved accounts. Overseas orders by Bank Draft in Sterling and £2.00 minimum post and packing. DHL plus £65.00 no V.A.T. V.A.T. applicable to U.K. only. Please add 15% after adding P&P to order. No V.A.T. on books and datasheets.

DELIVERY all in stock items despatched same day (95% of all advertised items are in stock), items out of stock in a few days - any problems and you will be informed immediately.



BF197	12p	ME6102	28p	TS143	40p
BF198	15p	ME8001	47p	TS145	48p
BF199	15p	ME8002	50p	TS146	48p
BF200	75p	ME8003	50p	TS147	48p
BF240	32p	ME9001	56p	TS148	50p
BF241	35p	ME9002	56p	TS149	50p
BF242	38p	ME9003	56p	TS150	50p
BF243	38p	ME9004	56p	TS151	50p
BF244	38p	ME9005	56p	TS152	50p
BF400	38p	ME9161	56p	TS308	50p

BRIDGE	
1 amp type	W100 20p
2 amp type	W200 20p
4 amp type	W400 20p
8 amp type	W800 20p
15 amp type	W1500 20p
25 amp type	W2500 20p
50 amp type	W5000 20p
100 amp type	W10000 20p
200 amp type	W20000 20p
400 amp type	W40000 20p
800 amp type	W80000 20p
1600 amp type	W160000 20p
3200 amp type	W320000 20p
6400 amp type	W640000 20p
12800 amp type	W1280000 20p
25600 amp type	W2560000 20p
51200 amp type	W5120000 20p
102400 amp type	W10240000 20p
204800 amp type	W20480000 20p
409600 amp type	W40960000 20p
819200 amp type	W81920000 20p
1638400 amp type	W163840000 20p
3276800 amp type	W327680000 20p
6553600 amp type	W655360000 20p
13107200 amp type	W1310720000 20p
26214400 amp type	W2621440000 20p
52428800 amp type	W5242880000 20p
104857600 amp type	W10485760000 20p
209715200 amp type	W20971520000 20p
419430400 amp type	W41943040000 20p
838860800 amp type	W83886080000 20p
1677721600 amp type	W167772160000 20p
3355443200 amp type	W335544320000 20p
6710886400 amp type	W671088640000 20p
13421772800 amp type	W1342177280000 20p
26843545600 amp type	W2684354560000 20p
53687091200 amp type	W5368709120000 20p
107374182400 amp type	W10737418240000 20p
214748364800 amp type	W21474836480000 20p
429496729600 amp type	W42949672960000 20p
858993459200 amp type	W85899345920000 20p
1717986918400 amp type	W171798691840000 20p
3435973836800 amp type	W343597383680000 20p
6871947673600 amp type	W687194767360000 20p
13743895347200 amp type	W1374389534720000 20p
27487790694400 amp type	W2748779069440000 20p
54975581388800 amp type	W5497558138880000 20p
109951162777600 amp type	W10995116277760000 20p
219902325555200 amp type	W21990232555520000 20p
439804651110400 amp type	W43980465111040000 20p
879609302220800 amp type	W87960930222080000 20p
1759218644441600 amp type	W175921864444160000 20p
3518437288883200 amp type	W351843728888320000 20p
7036874577766400 amp type	W703687457776640000 20p
1407374	

TECH TIPS

Cassette Logic Driver

Mike Hobbs,
Basingstoke

This circuit allows microcomputers with cassette motor relays to control a logic controlled cassette deck with a remote control socket. It was originally designed for the BBC Microcomputer but will be suitable for many others. The circuit was designed to drive a TEAC C-3X cassette deck but is suitable for any machine where the control inputs are grounded to operate the control circuitry.

When you LOAD a program the cassette relay closes and this is used to trigger IC2b to give the cassette deck a PLAY pulse. When the cassette relay opens it triggers IC2a to give a STOP pulse. When you need

to SAVE a program you press the RECORD SET button before pressing RETURN on the computer. IC3 holds the record mode until the STOP pulse clears it when the operation is complete. This is done to prevent inadvertently recording when intending to read into the computer.


Additionally the circuitry around IC4 provides control from the computer user port so you can have direct control from the software. Obviously it is a simple matter to extend the capabilities of this interface to provide control of the rewind and fast forward functions also. In fact there is a spare gate in IC4, IC5 and IC6 which can be used for, say, the rewind function without any additional ICs being required. The computer user port has direct control over the cassette control signals and therefore the software must provide the correct pulse duration to activate the deck solenoids. The user port signal lines

must be driven low to activate the cassette deck because on the BBC Microcomputer the port is set up as an input port on power-up which means that the inputs to IC4 will float high and not try to activate all cassette solenoids at once!

Isolation is provided by the optoisolator so that there is no risk of damaging components in either the interface or the cassette deck due to different earth potentials or accidental shorting.

IC1 is a schmitt trigger inverter IC to eliminate contact bounce which is quite considerable on some microcomputer cassette relays.

The whole interface will fit onto a module 100 x 120 mm which will fit neatly inside the BBC Microcomputer and with careful mounting and suitable connectors the connector can be accessed from the gap at the rear of the BBC machine. The RECORD SET button can be mounted neatly next to the row of LEDs on the front panel. The power can, of course, be taken direct from the power supply's external output and the cables routed back into the machine via the gap above the port access recess underneath.

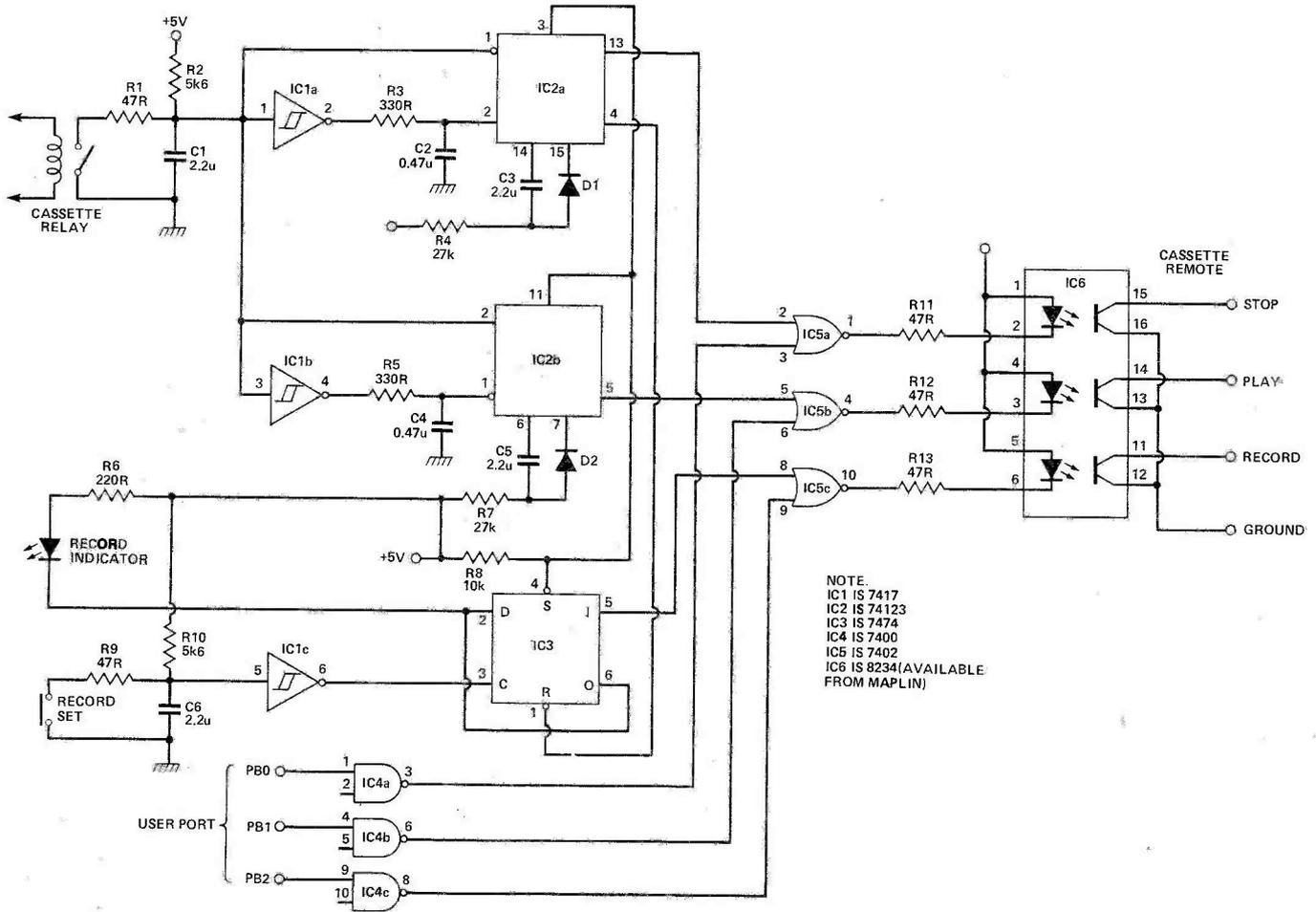

NOTE.
IC1 IS 7417
IC2 IS 74123
IC3 IS 7474
IC4 IS 7400
IC5 IS 7402
IC6 IS 8234(AVAILABLE
FROM MAPLIN)


Capacitor Tester

Andy D'Rozario,
Manchester.

During circuit development, situations often arise which call for a capacitor to be checked to ascertain

whether or not it is functioning. The circuit shown here gives a quick audio and visual indication of the state of the capacitor by using its most basic property — that of DC blocking.

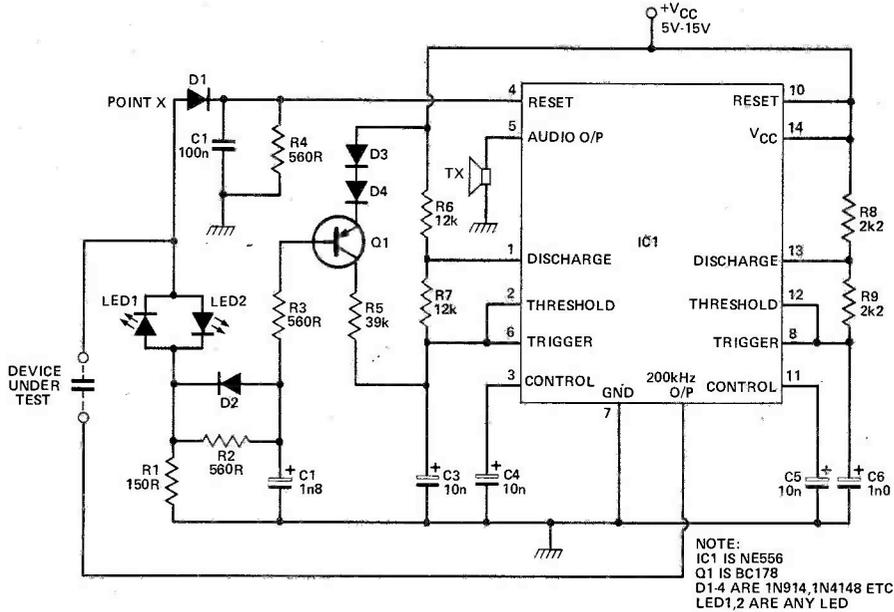Half of the NE556 oscillates at approximately 200 kHz and is used to



provide a train of positive pulses. These pulses are passed through the device under test to the two LEDs and an audio oscillator formed by the other half of the NE556.

The resultant pulses appearing at point X will vary with the device under test as follows:


Capacitor OK — positive and negative pulse train at point X, both LEDs illuminated; Q1 conducts and an audio tone is produced.

Capacitor S/C — only a positive pulse train at point X, only one LED illuminated, C1 charges up and a lower tone produced.

Capacitor O/C — no pulse train, neither LED illuminated, C2 discharges and the audio oscillator is reset.

A PB2720 piezoelectric transducer was used at the output of the audio oscillator, but a high impedance speaker or earpiece should do just as well.

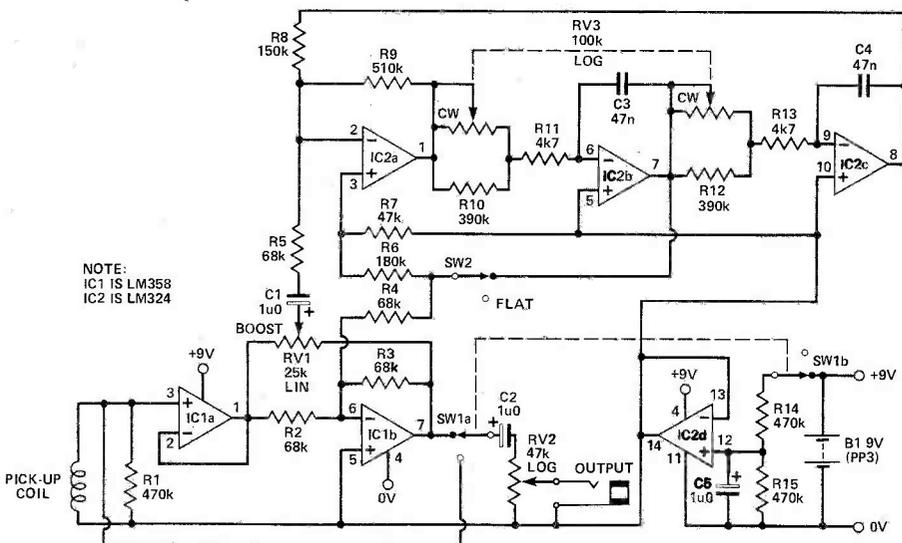The tester needs the capacitor under test to be greater than 30nF to produce an audio output reliably, however the LEDs will indicate the correct condition down to 100pF at 5 V supply voltage, and 50pF at 12 V.



Active Bass Tone Control

Ian Willats, Worcester

The circuit was designed to improve the tonal variation of a bass guitar, being physically small enough to replace the passive tone controls in the guitar body. Low power consumption is achieved by the use of LM324 type op-amps (the LM358 is 'half an LM324'), allowing battery operation from a PP3. Current drain is about 1 mA.

Operation of the tone control is

as follows: the pickup signal is buffered by IC1a and fed via R2 to mixer IC1b. The boost/cut control RV1 allows a combination of signals to enter the state-variable filter formed by IC2a,b,c, whose centre frequency can be varied by means of RV3 between 40 and 700 Hz (with the given components). The output of the filter is then fed back into the mixer via R4.

In this manner, the selected frequency can be boosted or cut by up to ± 10 dB. If SW2 is opened, however, R4 is grounded via R6 and R7 so that a flat frequency response results. This allows a preset effect to

be easily applied to the guitar.

The Q of the filter is set at about 1.4 by R6 and R7. This rather broad peak was found to be musically more useful than a very 'peaky' filter response. Note that the frequency control RV3 is wired so that low frequency effects are obtained when it is turned fully clockwise, giving a subjectively linear control.

IC2d simply provides a low impedance signal ground at half the supply voltage. Switch SW1 is provided to simultaneously switch off the active circuitry and bypass it, for operation in the event of battery failure. In the passive mode only the volume control RV2 is used.

None of the component values given are critical, and some experimentation is useful to match the circuit to a particular guitar. There is no reason why the circuit should not be used in a lead guitar if C3 and C4 are changed to, say, 22nF, to suit the higher frequency range.

Finally, a note about construction — as space is generally very limited inside a guitar body, the circuit can be built directly onto the undersides of the IC sockets and the pots, allowing for easy mounting. The smallest available components should be used. SW2 can be incorporated as a push-pull switch on pot RV1, which makes pre-setting effects very easy to accomplish.

ETI

HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT

THERMAL MATRIX & LINE PRINTER

SAVE £57

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER
 £113.00 + VAT. (UK POST etc £1.05) (List approx £187)
 150 to 180 LPM • Full 96 CH ASC II • 40 CPL • 280 Dots P/L
 Auto-underline • 50 Graphic Symbols • Back Space • Self Test • VU/HDR TABS • 7 x 10 Matrix • 4.4" Wide Paper
 Bidirectional • 220/240 V AC • Size Approx. 9.8 x 2.8 x 7.2"
 SUITABLE FOR: TANDY • BBS • DRIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc.
 (Your enquiries invited).
 Interface unit with leads £15 - state model).

DIGITAL MULTIMETERS

■ With case (rotary switches)
 + Side button - case £2.95
 KD25C ■ 13 range 0.2A DC.
 2 meg ohm £23.50
 KD305 ■ 16 range 10A DC.
 2 meg ohm £26.95
 KD30C ■ 26 range 1A
 AC/DC 20 meg ohm £33.50

COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER
 £113.00 + VAT. (UK POST etc £1.05) (List approx £187)
 150 to 180 LPM • Full 96 CH ASC II • 40 CPL • 280 Dots P/L
 Auto-underline • 50 Graphic Symbols • Back Space • Self Test • VU/HDR TABS • 7 x 10 Matrix • 4.4" Wide Paper
 Bidirectional • 220/240 V AC • Size Approx. 9.8 x 2.8 x 7.2"
 SUITABLE FOR: TANDY • BBS • DRIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc.
 (Your enquiries invited).
 Interface unit with leads £15 - state model).

KD55C ■ 28 range 10A AC/DC 20 meg ohm
 Metex 3000 ■ 30 range 10A AC/DC.
 20 meg ohm £33.24
 6010 • 28 range 10A AC/DC 20 meg ohm £34.40
 7030 • 40 AS6010 high acc. 0.1% basic £41.30
 KD615 ■ 16 range 10A DC 2 meg plus Hfe tester £39.95
 SIFAM 2200 B 21 range 2A AC/DC 20 meg Bench Models £29.95
 TM355 29 range LEO 10A AC/DC 20 meg. Thandar £86.25
 TM356 26 range LEO 10A AC/DC 20 meg. Thandar (Replaces TM353) £97.75
 TM351 29 range LEO 10A AC/DC 20 meg. Thandar £120.75
 SIFAM 2500 24 range LEO 2A AC/DC 20 meg. ALSO IN STOCK Thurlby, Metrix and Beckman. Professional series incl. True Rms. etc.

'CHERRY' ADD-ON KEYPAD

A compact 16 button keypad suitable for use with cherry keyboard to extend its functions. Supplied brand new with data. A 4 x 4 non-encoded single mode keyboard.
£5.95 (inc. V.A.T.)
 UK C/P Free

MULTIMETERS (UK C/P 65p)

CT081 50 K/Volt range doubler. 10A DC. Total 36 ranges. Special Offer £12.50
 HM102B 220K/V 10A DC 22 range & cont. buzzer £13.50
 TMK500 23 ranges 30K/V. 12A DC plus cont. buzzer £23.95
 NH56R 20K/V. 22 range pocket £30A 26 range 30K/V. 10A AC/DC overload protection. etc. £23.95
 360TR 23 range 100K/V. Large scale 10A AC/DC plus Hfe £39.95
 AT120 31 range 100K/V deluxe. 12A AC/DC £33.50
 AT102 18 range 20K/V. Deluxe plus Hfe tester £18.95
 YN360TR 19 range 20K/V plus Hfe tester £15.95

SANYO DM21 12 HIGH RESOLUTION MONITOR

12" green display:
 Composite video:
 1280 characters.
 Over 15 MHz R/W:
 240V AC 34 w.
 16" x 11 1/2" x 12 1/2"
 Alphanumeric and
 Graphic display. Usually £89.95 - £99.95
 inc VAT
£69.95 (UK C/P & ins £2.05)

SIGNAL GENERATORS (220/240V AC)

FUNCTION: All sine/square/triangle/TTL etc.
 TG100 1HZ-100 KHZ £90.00
 TG101 1HZ-200 KHZ £113.85
 TG102 0.2HZ-2 MHZ £166.75
 PULSE
 TG105 Various facilities 5 Hz-5 MHz £97.75
 AUDIO: Multiband Sine/Square
 LAG27 10 HZ to 1 MHZ £90.85
 AG20A 20 HZ to 200 KHz (list £94.50) £83.50
 LAG 120A 10 HZ-1 MHz Low Distortion £159.85
 RF
 SG402 100 KHZ to 30 MHz (list £79.50) £69.50
 LSG17 100 KHZ to 150 MHz £79.35

I.T.T. 2020 CABINET

Complete PROFESSIONAL SIGNAL Case beautifully constructed with cut out for one 'CHERRY' keyboard, plus ample room to house a COMPLETE SYSTEM and power supply. Complete with fittings (Case top detachable). Unit is silver grey in colour. Robust construction. Sloping front with side ventilation. Ideal for NASCOM. ACORN. TANGERINE or your own system. Size 18" x 15 1/2" x 4 1/2" (front slopes).
£27.50 inc. VAT (UK C/P £2.50)

OSCILLOSCOPES

Full specification any model on request. SAE by post.
 'HM' Series HAMEG: 'SC' THANDAR: 'CS' TRIO: '3' CROTECH 'Y' HITACHI
 SINGLE TRACE UK C/P £3.00
 3030 15 MHz 5mV, 95mm tube plus component tester C/P £3.00 £177.10
 SC110A = Miniature 10 MHz battery portable Post free £171.00
 HM103 15 MHz 2mV, 6 x 7 display plus component tester C/P £3.00 £181.70
 ■ Optional carry case £6.84 AC adaptor £6.69
 Nicads £12.50
 DUAL TRACE (UK C/P £4.00)
 HM203/4 Dual 20 MHz plus component tester £303.60
 CS1562A Dual 10 MHz (List £321.00) £269.50
 3131 Dual 15 MHz + component tester £276.00
 CS1566A Dual 20 MHz All facilities (List £401.35) £349.50
 HM204 Dual 20 MHz plus component tester sweep delay £419.75
 HM705 Dual 70 MHz sweep delay £676.00
 V212 Dual 20 MHz £399.25
 V222 Dual 20 MHz plus extra facilities £391.00
 V422 Dual 40 MHz portable £586.50
 V203F Dual Trace 20MHz sweep delay £408.25
 V134 Dual Trace 10 MHz storage £1092.50
 All HITACHI, CROTECH & TRIO MODELS AVAILABLE

LOGIC PROBES

LP10 10 MHz £28.50
 DLPS0 50 MHz with carry case and accessories £49.95

VARIABLE POWER SUPPLIES

(UK C/P £1.00)
 PP241 0/12/24V 0/1A £35.00
 PP243 3 amp version £59.95
 PS1307S 8/15V 7 amp 1/4in meter £24.95

HIGH VOLTAGE METER

Direct reading 0/40 KV.
 20K/Volt. £23.00 (UK C/P 65p)

TRANSISTOR TESTER

Direct reading PNP: NPN, etc.
 TC1 (UK C/P 65p) £21.95

DIGITAL CAPACITANCE METER

0.1 pF to 2000 mfd LCD 8 ranges
 DM6013 £52.75

FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket 8 digit LED £77.60
 MET1008 8 digit LED bench 2 ranges 100 MHz £102.35
 MET6008 8 digit LED bench 3 ranges 600 MHz £132.25
 MET1000 8 digit LED 3 ranges 1 GHz £182.85
 TF040 8 digit LCD 40 MHz Thandar £126.50
 TF200 3 digit LCD 200 MHz Thandar £166.75

TRANSISTOR TESTER

Direct reading PNP: NPN, etc.
 TC1 (UK C/P 65p) £21.95

DUAL TRACE (UK C/P £4.00)

HM203/4 Dual 20 MHz plus component tester £303.60
 CS1562A Dual 10 MHz (List £321.00) £269.50
 3131 Dual 15 MHz + component tester £276.00
 CS1566A Dual 20 MHz All facilities (List £401.35) £349.50
 HM204 Dual 20 MHz plus component tester sweep delay £419.75
 HM705 Dual 70 MHz sweep delay £676.00
 V212 Dual 20 MHz £399.25
 V222 Dual 20 MHz plus extra facilities £391.00
 V422 Dual 40 MHz portable £586.50
 V203F Dual Trace 20MHz sweep delay £408.25
 V134 Dual Trace 10 MHz storage £1092.50
 All HITACHI, CROTECH & TRIO MODELS AVAILABLE

VARIABLE POWER SUPPLIES

(UK C/P £1.00)
 PP241 0/12/24V 0/1A £35.00
 PP243 3 amp version £59.95
 PS1307S 8/15V 7 amp 1/4in meter £24.95

OPTIONAL PROBE KITS

X1 £7.95 X10 £9.45 X1 - X10 £10.50

FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket 8 digit LED £77.60
 MET1008 8 digit LED bench 2 ranges 100 MHz £102.35
 MET6008 8 digit LED bench 3 ranges 600 MHz £132.25
 MET1000 8 digit LED 3 ranges 1 GHz £182.85
 TF040 8 digit LCD 40 MHz Thandar £126.50
 TF200 3 digit LCD 200 MHz Thandar £166.75

OPTIONAL PROBE KITS

X1 £7.95 X10 £9.45 X1 - X10 £10.50

FREQUENCY COUNTERS

PFM200A 200 MHz hand held pocket 8 digit LED £77.60
 MET1008 8 digit LED bench 2 ranges 100 MHz £102.35
 MET6008 8 digit LED bench 3 ranges 600 MHz £132.25
 MET1000 8 digit LED 3 ranges 1 GHz £182.85
 TF040 8 digit LCD 40 MHz Thandar £126.50
 TF200 3 digit LCD 200 MHz Thandar £166.75

OPTIONAL PROBE KITS

X1 £7.95 X10 £9.45 X1 - X10 £10.50

HENRY'S AUDIO ELECTRONICS

301 Edgware Road, London, W2 1BN
 01-724 3564 (All mail to this address)

404-406 Edgware Road, London, W2 1ED
 Computer: 01-402 6822. Components: 01-723 1008
 Test Equipment & Communications: 01-724 0323

CUBEGATE LIMITED
 Huge stocks of semiconductors, components, tools, etc.
 Large range of CB equipment and telephones in stock.
 CALL IN AND SEE FOR YOURSELF.
 ORDER BY POST OR PHONE.

301 Edgware Road, London, W2 1BN
 01-724 3564 (All mail to this address)

EUROPA ELECTRONICS

Mail Order to 160 High Road, Willesden, London NW10 2PB
 TEL: 01-907 1659

SEND FOR A FREE LIST OF OUR LARGE RANGE OF ITEMS
 ALL DEVICES ARE NEW, FULL SPEC AND GUARANTEED

Post & Packing: Add 30p to all orders under £5.
 VAT: All UK orders add 15% to total cost including p&p.

VALS SERIES		TRANSISTORS		COMPUTER CHIPS		LINEAR IC'S		4000 CMOS	
74LS00	20p	AD161	42p	280A	320p	741	14p	4001	10p
74LS01	20p	BC107	12p	280AC	250p	CA3010	80p	4002	12p
74LS02	20p	BC108	12p	280ADARY	700p	CA3046	70p	4006	50p
74LS03	20p	BC109	10p	280DPIO	290p	CA3048	220p	4007	14p
74LS04	20p	BC109C	12p	280S10	910p	CA3059	285p	4008	38p
74LS05	20p	BC177	12p	6802	225p	CA3059	255p	4009	24p
74LS06	20p	BC178	16p	6803	100p	CA3090	72p	4010	24p
74LS07	20p	BC179	20p	6840	375p	CA3096	48p	4011	11p
74LS08	20p	BC182L	10p	6850	110p	CA3130E	90p	4012	19p
74LS09	20p	BC183L	10p	6852	250p	CA3130T	110p	4013	20p
74LS11	20p	BC184L	10p	6875	500p	CA3140C	90p	4014	40p
74LS12	20p	BC212L	10p	8085	450p	CA3140E	90p	4015	40p
74LS13	20p	BC213L	10p	8154	950p	CA3160E	100p	4016	20p
74LS14	20p	BC214L	12p	8156	350p	CA3161E	110p	4017	25p
74LS15	20p	BC547	12p	8212	100p	CA3162E	450p	4018	45p
74LS16	20p	BC548	12p	8218	100p	CA3190E	300p	4019	25p
74LS17	20p	BC549C	14p	8238	270p	CA3240E	110p	4020	45p
74LS18	20p	BC556	15p	8250	850p	CA3250G	200p	4021	40p
74LS19	20p	BC557	15p	8253	390p	LF347	150p	4022	45p
74LS20	20p	BC558	15p	8255	255p	LF351	48p	4023	13p
74LS21	20p	BC559	15p	8258	400p	LF353	48p	4024	35p
74LS22	20p	BFY50	23p			LF355	85p	4025	15p
74LS23	20p	BFY52	23p			LF356	85p	4026	80p
74LS24	20p	BFY53	23p			LM307	110p	4027	20p
74LS25	20p	BFY54	23p			LM307A	25p	4028	40p
74LS26	20p	BFY55	23p			LM310	120p	4029	45p
74LS27	20p	BFY56	23p			LM311	70p	4030	15p
74LS28	20p	BFY57	23p			LM312	110p	4031	11p
74LS29	20p	BFY58	23p			LM313	210p	4038	110p
74LS30	20p	BFY59	23p			LM324	30p	4040	40p
74LS31	20p	BFY60	23p			LM324Z	90p	4041	40p
74LS32	20p	BFY61	23p			LM335Z	140p	4042	40p
74LS33	20p	BFY62	23p			LM339	50p	4043	40p
74LS34	20p	BFY63	23p			LM348	85p	4044	40p
74LS35	20p	BFY64	23p			LM350	100p	4045	100p
74LS36	20p	BFY65	23p			LM391N	115p	4046	50p
74LS37	20p	BFY66	23p			LM392	160p	4048	50p
74LS38	20p	BFY67	23p			LM393	100p	4049	24p
74LS39	20p	BFY68	23p			LM398	95p	4051	45p
74LS40	20p	BFY69	23p			LM399	100p	4052	50p
74LS41	20p	BFY70	23p			LM3990	50p	4058	14p
74LS42	20p	BFY71	23p			LM3990N	85p	4059	14p
74LS43	20p	BFY72	23p			LM3991	125p	4070	14p
74LS44	20p	BFY73	23p			LM3994	25p	4071	14p
74LS45	20p	BFY74	23p			LM3995	25p	4072	14p
74LS46	20p	BFY75	23p			LM3996	25p	4073	14p
74LS47	20p	BFY76	23p			LM3997	25p	4074	14p
74LS48	20p	BFY77	23p			LM3998	25p	4075	14p
74LS49	20p	BFY78	23p			LM3999	25p	4076	14p
74LS50	20p	BFY79	23p			LM3999A	25p	4077	14p
74LS51	20p	BFY80	23p			LM3999B	25p	4078	14p
74LS52	20p	BFY81	23p			LM3999C	25p	4079	14p
74LS53	20p	BFY82	23p			LM3999D	25p	4080	14p
74LS54	20p	BFY83	23p			LM3999E	25p	4081	14p
74LS55	20p	BFY84	23p			LM3999F	25p	4082	14p
74LS56	20p	BFY85	23p			LM3999G	25p	4083	14p
74LS57	20p	BFY86	23p			LM3999H	25p	4084	14p
74LS58	20p	BFY87	23p			LM3999I	25p	4085	14p
74LS59	20p	BFY88	23p			LM3999J	25p	4086	14p
74LS60	20p	BFY89	23p			LM3999K	25p	4087	14p
74LS61	20p	BFY90	23p			LM3999L	25p	4088	14p
74LS62	20p	BFY91	23p			LM3999M	25p	4089	14p
74LS63	20p	BFY92	23p			LM3999N	25p	4090	14p
74LS64	20p	BFY93	23p			LM3999O	25p	4091	14p
74LS65	20p	BFY94	23p			LM3999P	25p	4092	14p
74LS66	20p	BFY95	23p			LM3999Q	25p	4093	14p
74LS67	20p	BFY96	23p			LM3999R	25p	4094	14p
74LS68	20p	BFY97	23p			LM3999S	25p	4095	14p
74LS69	20p	BFY98	23p			LM3999T	25p	4096	14p
74LS70	20p	BFY99	23p			LM3999U	25p	4097	14p
74LS71	20p	BFY00	23p			LM3999V	25p	4098	14p
74LS72	20p	BFY01	23p			LM3999W	25p	4099	14p
74LS73	20p	BFY02	23p			LM3999X	25p	4100	14p
74LS74	20								

DAC/ADC FILTER/AMPLIFIER

ETI supplies the missing link for all your analogue to computer interface circuits. Design by C. D. Oddy.

Anyone who has ever seriously experimented with analogue interfaces to home computers must be all too aware of the problems involved — if you're not too careful you wind up with op-amps everywhere in a variety of hastily concocted amplifier, buffer, and filter circuits. And some of them won't even be hastily concocted; some of them will have taken up a considerable amount of your precious time in the designing. What you need is a handy little unit that will perform any or all of the functions of amplifier, buffer, and filter at the mere twiddle of a control or two. What you need is the ETI filter-amplifier.

The filter-amplifier consists of two active blocks together with

input and output buffers and switchable AC or DC coupling. The two active blocks are an amplifier with a variable gain of 0 to 100 and a plus or minus five volt variable offset followed by a low pass filter whose cutoff frequency may be varied over the range 16 Hz to 30 kHz and which may be switched out of circuit when not required. It can be used as an amplifier to match low level signals to the input of an ADC, as a buffer to correct mismatching of signal sources, as a filter to smooth the stepped output of a DAC, and for a multitude of other similar purposes.

Construction

Assembly is simplified by the use of a single quad op-amp for the

PARTS LIST

RESISTORS (all $\frac{1}{4}$ W, 5%)

R1	1M0
R2	1k0
R3	33k
R4	47k
R5, 6	560R
R7	39k
R8	10k
R9, 11	120k
R10	150k
RV1	20k horizontal skeleton preset
RV2	50k linear with centre click-stop
RV3	100k linear
RV4	100k dual gang log

CAPACITORS

C1, 4, 5, 7	100n polyester
C2, 3	10u 35V tantalum
C6, 8	10n polyester

SEMICONDUCTOR

IC1	TL074
-----	-------

MISCELLANEOUS

SW1	SPST
SW2	DPDT
SW3	SPDT
PCB; case, input and output sockets, knobs, etc as desired.	


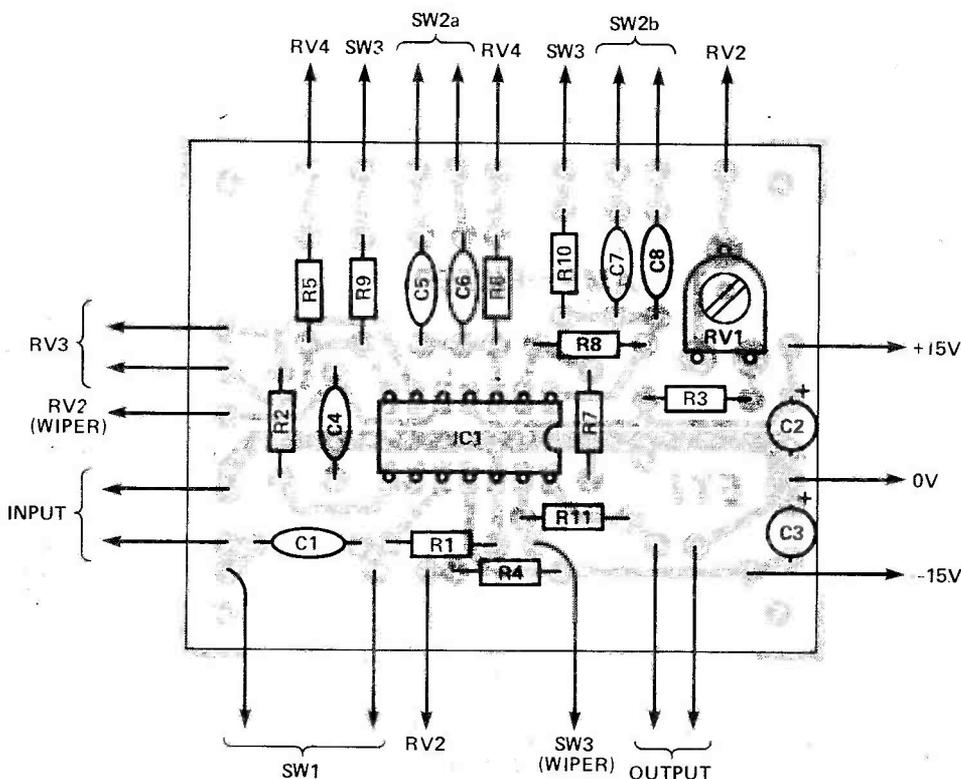


Fig. 1 (left) Component overlay for the PCB

Fig. 2 (below) Connections to RV4

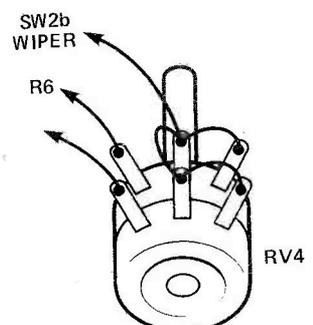

The only unusual item here is the centre click-stop potentiometer and that is available from Ambit. PCB from our PCB service (where else?) for which see page 89.

BUYLINES

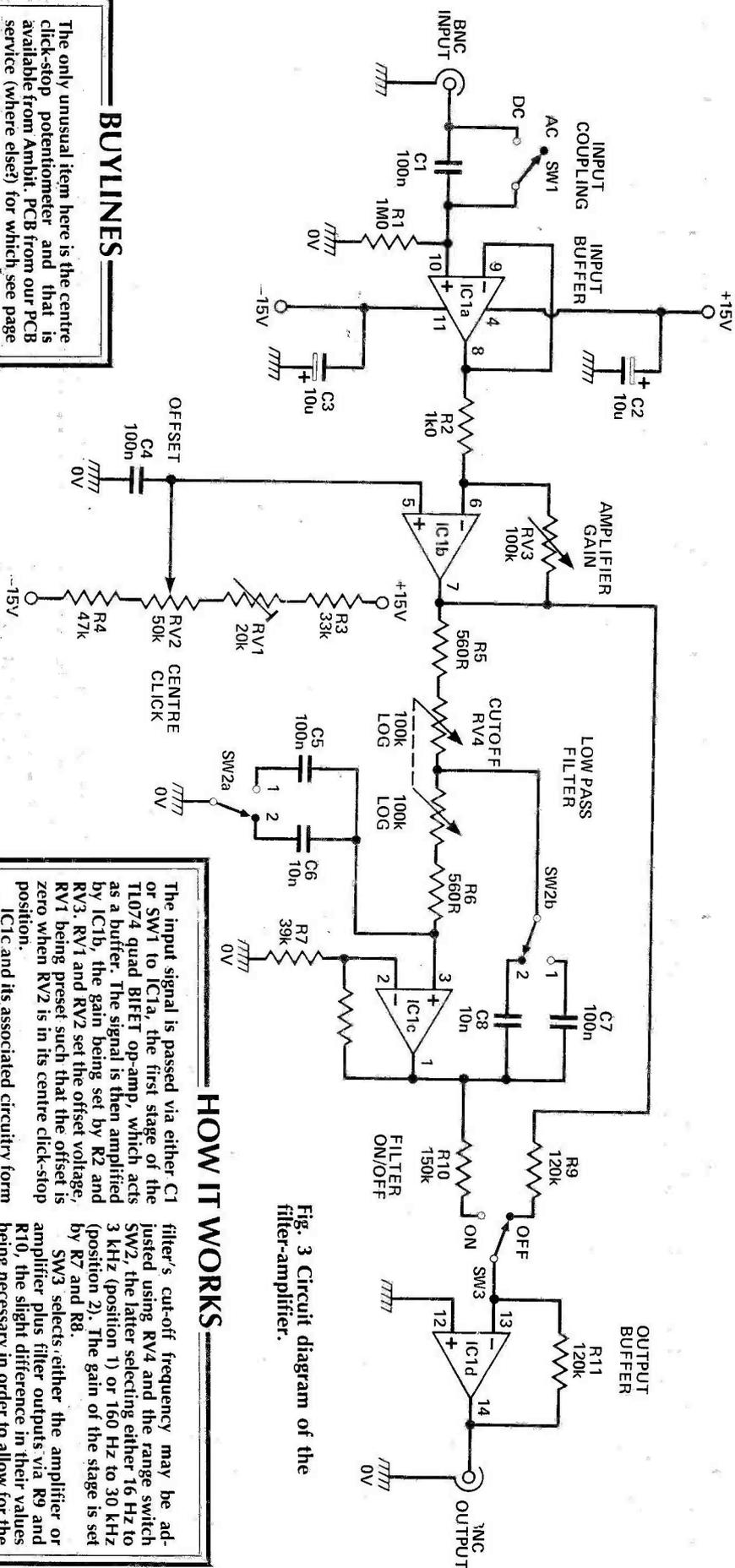
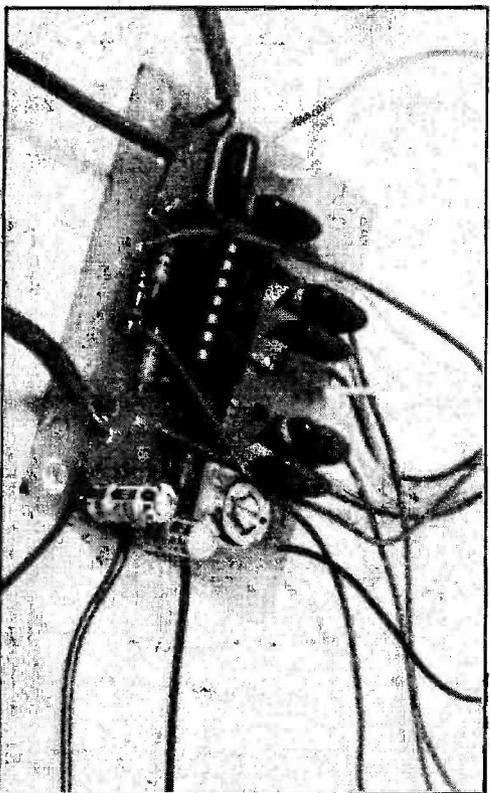


Fig. 3 Circuit diagram of the filter-amplifier.

HOW IT WORKS

The input signal is passed via either C1 or SW1 to IC1a, the first stage of the TL074 quad BIFET op-amp, which acts as a buffer. The signal is then amplified by IC1b, the gain being set by R2 and RV3. RV1 and RV2 set the offset voltage, RV1 being preset such that the offset is zero when RV2 is in its centre click-stop position.

IC1c and its associated circuitry form a low pass filter of the second order Bessel type which is well suited to the smoothing of stepped signals, such as those obtained from DAC outputs. The filter's cut-off frequency may be adjusted using RV4 and the range switch SW2, the latter selecting either 16 Hz to 3 kHz (position 1) or 160 Hz to 30 kHz (position 2). The gain of the stage is set by R7 and R8.

SW3 selects either the amplifier or amplifier plus filter outputs via R9 and R10, the slight difference in their values being necessary in order to allow for the gain (approx. 2.3 db) of the filter. The signal then passes through IC1d, the final buffer stage, to the output.


four stages, and the only point to check on the PCB itself is that this IC and the two electrolytic capacitors (C2, C3) are inserted the right way around. Take care with the wiring of the potentiometers and switches, especially SW2 which has two separate elements whose wiring must be in agreement if the filter is to work correctly. Note also the wiring around RV4 and the connection between this potentiometer and SW2, as shown in Fig. 2.

We have not shown either a

case or a power supply for this project because it is intended more as a building block than as a complete, self-contained unit. For the really serious experimenter there is obviously a lot to be gained from having several of these filter-amplifiers built into a single unit and equipped with a common power supply, whereas for others, one would probably be sufficient and could be powered from whatever you're using to supply the ICs you're experimenting with.

POSITRONICS

FOR PROFESSIONAL POWER SUPPLY UNITS

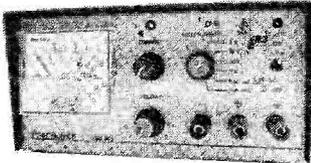

Positronics leads the field in providing an inexpensive range of professional specification power supply units, to industry and the enthusiast. Their features and performance being worthy of instruments twice their price, such as visual LED indication of mode, either constant current or constant voltage, ripple less than 1mv, voltage regulation better than 0.01%, load regulation better than 0.01% plus overload protected.

Also available in kit, they come complete with a step by step guide to problem free construction, placing them well within the pocket and competence of even the novice.

PSU 301

- * 0 - 30 volt output
- * 0 - 1 amp output continuous
- * Integral 6 range meter giving, 0 - 3v 0 - 100 mA 0 - 110v 0 - 300 mA 0 - 30v 0 - 1 A
- * In Kit **£37.90**
- Built & Tested **£49.90**

PSU 301.5

- * 0 - 30 volt output
- * 0 - 1.5 amp output continuous
- * Integral 6 range meter giving, 0 - 3v 0 - 100 mA 0 - 10v 0 - 500 mA 0 - 30v 0 - 1.5 A
- * In Kit **£46.90**
- Built & Tested **£59.90**

PSU 303 (DVS)

- * 0 - 30 volt output
- * 0 - 3 amp output continuous
- * Integral 6 range meter giving, 0 - 3v 0 - 100 mA 0 - 10v 0 - 500 mA 0 - 30v 0 - 3 A
- * Performance light weight toroidal transformer.
- * DVS Dual Voltage Switched Designed by Positronics this allows the unit to deliver twice the current of conventional variable power supply units.
- * In Kit **£58.90**
- Built & Tested **£74.80**

From kit or built and tested you will have a highly controllable power source of exacting design, engineering and quality.

All prices inclusive of VAT. P&P £2.90. Please allow 21 days delivery.

POSITRONICS

Unit 4, New Enterprise III, Montgomery Street
Starbrook, Birmingham B11 1DS
Tel: 021-350 2267

9" MONITOR in attractive case. Non Standard Input. With Info **£25** each. Carr **£7**. Matching ACSII coded Querty Keyboard with Numeric Keypad and 27 Function Keys **£25** each P&P **£5**. The Pair **£40**. Carr **£7**.

12" MONITOR. Cased. Non Standard Input. With Info **£20** each. Carr **£7**. With Matching ACSII coded Querty Keyboard with Numeric Pad and 24 Function Keys **£25** the Pair. Carr **£7**.

AZTEC 20" black & white monitor. Video in **£50**. TV style 20" Monitors **£30**

INSTRUMENT CASE standard 19" width x 16" depth x 10" high. **£5** each. Carr **£7**

FLOPPY DISK DRIVE B by MEMOREX. Connection details **£75** each P&P **£5**

CREEED 75 TELEPRINTER. Very good condition. **£25** each. Carriage **£7**.

ELECTROLYTIC CAPACITOR 15,000 mfd 25V. 20p ea. 10 off **£1.80**.

SLOTTED OPTO SWITCH with data 50p. 10 off **£4**.

INFRA RED QUARTZ LAMP 230V 620 Watts. Size 1 3/4" x 1/4" dia **£1.50** ea. 10 off **£10**.

FERRANTI PHOTOCELL type MS15 - 50p ea. 10 off **£4**

AMPLIFIER BOARD complete with heat sink & 2 output transistors type 2N5293. 12/24V Input. At least 5 Watt output. Circuit supplied **£1.50**.

VARIAC 2 amp. Ex-sea. Good condition **£12** ea. P&P **£4**

LED type TIL209 Red with holder - 8p ea. 10 off **70p**

I.C. SOCKET 16 pin - 8p ea. 100 off **£8**.

GEARED MOTOR 117/234 Volt Input 50HZ. 4" dia x 5 1/2" deep. 1" shaft. New **£5** each P&P **£4**

MOTOR 12V DC Input. 2" dia x 4 1/2" deep. 1/2" shaft. New **£3.50** each P&P **£3**.

DC MOTOR 6-12 Volts. Mechanical Constant Speed Control 1 1/2" dia. **£1** each.

MOTOR 12V DC with pulley & semi-conductor speed control. **£1** each.

SYNCHRONOUS MOTOR 2 Phase 9 volt AC. 375 RPM. Good torque (needs 30-40 mfd capacitor. Suitable for Robotics/Plotters etc. **£1** each.

OTHER SYNCHRONOUS/STEPPING MOTORS AVAILABLE. PLEASE ENQUIRE

GEARED MOTOR 120V 50HZ. 4 Watt 1 rpm. 2" dia x 1 1/2" deep. **£1.50** each.

CENTAUR FANS 41". 115V New. **£4.50** each.

MUFFIN 115V 41". unused. **£3** each P&P **£2**.

TRANSFORMERS - All brand new, all 240 volts input.

Sec 25.5V 2.5A. Size 3 1/2" x 2 1/2". **£2.50** each.

Sec 115V 1A (auto) **£1.25** each. Sec 6V 1.66A **£1.50**

Sec 12V 100MA **50p** each.

TRANSFORMER 120 Volt Input. Sec 10-0-10V 1A **70p** each

Sub Min TRANSFORMER 0-120-240V Input. Sec 12-0-12V 4VA **75p** each 10 off **£5**

TOROIDAL TRANSFORMER 0-115-230V Input. Sec 13.5-0-13.5V 5VA. **£1.80** each 10 off **£12**.

TOROIDAL TRANSFORMER 0-120-240V Input. Sec 0-12V. 0-12V 10VA per winding. Encapsulated. **£4** each. 10 off **£35**.

Sub Min PULSE TRANSFORMER. Sec centre tapped. Suitable for Thyristor triggering 20p each. 10 off **£1.80**

RAPID DISCHARGE CAPACITOR 8 mfd 4KV **£5** each P&P **£2**.

TELEPHONES. 706 style black, blue, green, grey. **£5.50** each. 10 off **£45**.

Discoloured **£4** each. 10 off **£30**. 746 style black or grey **£7.80** each. P&P **£2** each. 4-10 units **£7**. Over 10 by arrangement.

TOKIN NOISE FILTER V6215FU. 250VAC 15A 50/60HZ. With fixing bracket. New **£2** each.

VU METER. Scaled 0-5, size 1 1/2" x 7/8". **50p** each 10 off **£4**

I.T.T. LOUD SPEAKER. 3 1/2" dia. 50 ohm 0.2 Watt. New. **75p** each. 10 off **£8.50**.

E.H.T. CABLE. Overall dia 5mm. 10p per metre. 100 metre drum **£7.80** P&P **£4**.

Multi Colour RIBBON CABLE 10 way. **50p** per metre. 10 metres **£4**. 14 way **75p** per metre. 10 metres **£5**. 100 metres **£40**.

ILLUMINATED ROCKER SWITCH. 2 pole 250V 8 Amp. orange. **50p** each. 10 off **£4**.

JOYSTICK SWITCH 4 directions. **£3** each. P&P **£2**

PCB KEYBOARD PAD. 19 push contacts. 0-9; A-F plus 3 optional. **£1.50** each. 10 off **£12**.

KEYBOARD PAD. 12 Alps Reed Switches, push to make. 0-9; *; # Blank, size 3 x 2 1/2" high. **£4** each. 10 off **£18**. P&P **£3**.

EPROM 2716 Single row. **£1.50** each. 2564 **£3**

SPECTRAL RELIANCE TEN TURN POT. 100 ohm ± 1%. Brand new. **75p** each 10 off **£8**

SLIDER POTENTIOMETER. Twin Gang. 200K or 2M. **35p** each 10 off **£3**.

PANEL MOUNTING FUSE HOLDER for 1 1/2" fuse. **20p** each. 10 off **£1.50**.

BELLING LEE CHASSIS MOUNTING FUSE HOLDER for 1 1/2" fuse. **15p** each. 10 off **£1**.

I.E.C. MAINS LEAD. 2 metre length, heavy duty. **50p** each. 10 off **£5**.

4 CORE CURLY WIRE extending to 2 metres. 20p each. 10 off **£1.80**

MICROPHONE/EARPIECE INSERTS. Brand new. **70p** each. 10 off **£5**.

TORIN SNAIL type BLOWER 230Volts 22 Watts. Overall size 5" x 1 1/2". **£4** each P&P **£2**.

TURNABLE STYLE 240V AC MOTOR. Size 82 x 75 x 73mm. Shaft 43 x 4mm dia. **£1.50** ea P&P **£2**

TRANSFORMER Input 0-220-240V Sec 0-12. 0-24V 1 Amp. **£2** each.

EXECUTIVE TELEPHONE-PUSH BUTTON. Functions include 10 number memory; repeat dialing; internal Microphone & Speaker and separate handset etc. Will connect direct to British Telecom System. **BRAND NEW. ONLY £25** ea. P&P **£4**.

Minimum Order of Goods **£3**. Minimum P&P **£1.50**. VAT at 15% MUST be added to TOTAL of GOODS & PACKAGING.

Many more components and test equipment available. S.A.E. or telephone for lists.

EASY ADD-ONS
for ZX81-
SPECTRUM-ACE

NEW



17 exciting electronic projects to build and run on your own micro.

- **LIGHT PEN**
- **PICTURE DIGITISER**
- **KEY PAD**
- **MODEL CONTROLLER**
- **WEATHER STATION**
- **+ OTHER EXCITING & INTERESTING PROJECTS**

REALISE THE REAL WORLD POTENTIAL OF YOUR MICRO.

A newly released book written by well known author Owen Bishop and published by Bernard Babani gives fully descriptive details on how to build all 17 projects - all are fairly simple and inexpensive to construct - The most complex component (the DECODER) is supplied in kit form ready to assemble with all components and plated through PCB. - Components for the projects are readily available locally or found in your workshop drawers.

Once assembled and connected to your micro the decoder is able to run any or all of the projects simultaneously.

Simple Programmes are included to get you started but of course the more experienced programmer can have hours of fun writing complex programmes to take full advantage of these easy but exciting projects.

Please send by return. Specify which computer

QTY	REF	DESCRIPTION	PRICE	TOTAL
	HB/2000	"EASY ADD-ONS" + DECODER KIT & BOOK	£24.00	
	HB/2001	"EASY ADD-ONS" BOOK ONLY	£3.00	
	HB/2002	DECODER KIT ONLY	£22.00	
	HB/2003	DECODER PCB ONLY	£8.00	
			TOTAL	

Price inclusive of VAT & carriage. Please allow 21 days for delivery. Cheques, PO's or signed Access orders welcomed.

Please Send Full Hobbyboard Mail Order Catalogue with full range of PCB materials & Hardware

Name

Address

hobbyboard a division of **KELAN ENGINEERING Ltd**
Hookstone Park
Harrogate, N. Yorks

complete P.C.B. workshop **ETI/11/83**

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL


Tel: 0734 68041

Callers welcome 9 am-5.30 pm Monday to Saturday inclusive



THE 1984 GREENWELD CATALOGUE

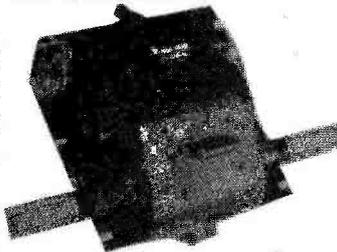Now in the course of production, the 1984 GREENWELD catalogue will be published in November. It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00! Order now for early delivery!



MOTORIZED GEARBOX

These units are as used in computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable wheels also available.

Motorized gearbox price £5.95

3" Dia plastic with black tyre, drilled to push-fit on spindle. 2 for £1.30 (limited qty).

3" dia aluminium disc 3mm thick, drilled to push-fit on spindle. 2 for 68p.

10W AMP PANEL

Neat board 115 x 62 mm with Class B output. Uses 2 x 2N5293, 2 x BFY50, BFX29. Supply can be either 36V or 18-0-18V Input sensitivity 1V for 10W output. Small H/S on board: £2.95. Suitable transformer, bridge rect, smoothing and o/p capacitor: £5.50. Supplied with circuit/connection data.

NICAD CHARGER

Versatile unit for charging AA, C, D and PP3 batteries. Charge/test switch, LED indicators at each of the 5 charging points. Mains powered. 210 x 100 x 50 mm £7.95

STABILIZED PSU PANEL

A199 A versatile stabilized power supply with both voltage (0-30V) and current (20mA-2A) fully variable. Many uses inc bench PSU, Nicad charger, gen: purpose testing. Panel ready built, tested and calibrated. £7.75. Suitable transformer and pots £6.00. Full data supplied.

TTL PANELS

Panels with assorted TTL inc LS types. Big variety. 20 chips £1.00; 100 chips £4.00; 1000 chips £30.00

RIBBON CABLE

Special purchase of multi-coloured 14 way ribbon cable —40p/metre; 50m £18; 100m £32.00; 250m £65.00

ALL PRICES INCLUDE VAT: JUST ADD 60p P&P

GREENWELD

443A Millbrook Road Southampton S01 0HX

RELAYS

Reed relays like RS 348-970 etc.

W950 12V SP make 500R 60p

W953 12V SPCO 500R 90p

W954 24V SP make 750R 60p

W955 24V DP make 750R 90p

W922 Mains 240V ac solenoid, 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50

W733 1 pin plug in relay, 240V ac, 3PCO 5A contacts £2.50. Base 36p

W848 700R 24V 4PCO "continental" relay 35 x 30 x 18mm, only 84p, 10/£7.00

W847 37R5-10V relay, SP 3A contact, PCB mntg 11X30X20. 95p 10/£7.50

W893 Omron LY4 mains relay, 4PCO 5A contacts. £2.50

W925 5V DIL reed relay. SP make 75p

W924 6V reed relay, 500R coil, DP break contacts. 60p

W926 24V Omron relay type G2L 113P, PCB vert mntg. 28 x 25 x 10mm 75p


MICROPROCESSOR PANELS

Z903 Panel 240 x 165 with 6802uP, 6821 PIA, 6850 ACIA, 4040, 4512 x 2, LS00, LS367 x 2, 555 x 2 all in sockets, plus R's, C's, plugs, sockets etc, also 12V sub-min relay. £4.95

Z904 Panel 240 x 165 mm with 6 x 4099, 723 all in sockets, 14 x 8A 200V triacs, 45 small signal transistors, 14 R/C networks, 30 x 1N4001, sub-min relay, R's, C's, etc. £4.95

HEATSINK

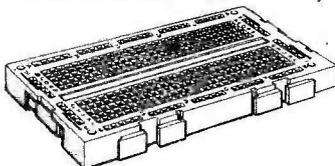Z905 Finned black ally heatsink 125 x 198 x 23 mm with 4 x 2N3055 and 4 x OR25 5W R's. Only £2.50



VEROBLOC £1 off

Our biggest selling breadboard on offer at a special price of £4.10.


NUTS SCREWS WASHERS & BOLTS

Over 2 million in stock, metric, BA, self-tappers etc. SAE for list.

COMPUTER GAMES

Z901 Can you follow the flashing light/pulsating tone sequence of this famous game? Supplied as a fully working PCB with speaker (no case) plus full instructions. Only £4.95

Z902 Probably the most popular electronic game on the market — based on the old fashioned pencil and paper battleship game, this computerized version has brought it bang up to date! We supply a ready built PCB containing 76477 sound effect chip, TMS1000 micro-processor chip, R's, C's etc. Offered for its component value only (board may be cracked or chipped), it's only £1.95. Instructions and circuit, 30p.

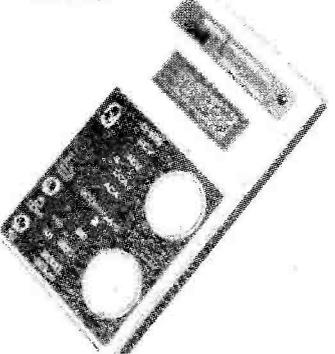

TREAT YOURSELF TO A NICE NEW DIGITAL MULTIMETER!!

KD55C A DVM for the professional — this 3 1/2 digit multimeter has overload protection, low battery and over range indication. Full auto-polarity operation. AC Volts: 0.2-700 DC Volts: 0.2-1000 AC Current: 200uA-10A DC Current: 200uA-10A Resistance: 200R-200M Total 28 ranges for just £44.95

hi! performance hi! competitive hi!

MORE people are buying TRIO

*** FOR ***

MORE DISPLAY


nearly 50% more with the NEW LARGE 6 inch rectangular CRT with illuminated inner face graticule, 6KV accelerator voltage for a brighter, higher resolution display with guaranteed accuracy.

MORE SENSITIVITY

1 milli Volt per cm in the vertical axis, valuable for observing complex low level waveforms especially with 20 nano sec per cm Sweep Speed.

MORE FACILITIES

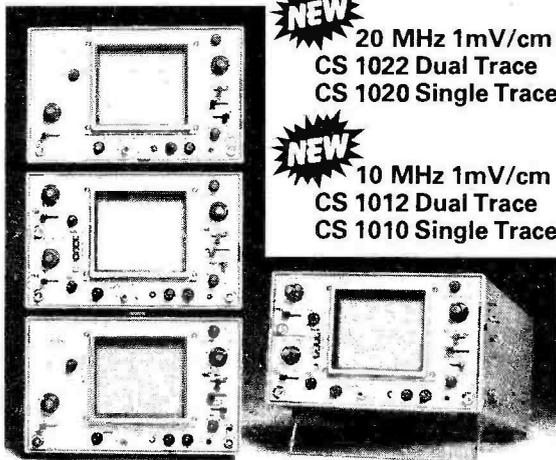like push-button MODES inc. Add, Sub, Alt and Chop - V mode trigger SOURCE - NEW super video sync - Front panel control of Astig, Trace rotation, Scale illum and X-Y - Chan I O/P, Int. Mod etc, etc.



NEW 20 MHz 1mV/cm
CS 1022 Dual Trace
CS 1020 Single Trace

NEW 10 MHz 1mV/cm
CS 1012 Dual Trace
CS 1010 Single Trace

AT REAL VALUE FOR MONEY PRICES

Fully Guaranteed for 2 years inc.
Free 'pick up' and 'return'



In a hurry? Then ring (0799) 24922

House of Instruments,
Clifton Chambers, 62 High Street,
Saffron Walden, Essex CB10 1EE
Telephone: (0799) 24922 Telex: 818750.

Ask for FREE DATA

TRIO

hi! competitive hi!

hi!

House of Instruments Ltd.

ETI November 1983



IC UPDATE

The world of op-amps never stands still, as a glance at the specifications of these devices will testify. No sooner have we got used to the third (or fourth, depending on which manufacturer's literature you've been reading) than the next one comes along.

OP-27, OP-37 Very Low Noise Op-Amps

Features

- Very low noise; spectral noise density: $3\text{nV}/\sqrt{\text{Hz}}$
1/f noise corner frequency 2.7Hz
- Very low Vos drift: $0.2\mu\text{V}/\text{month}$
 $0.2\mu\text{V}/^\circ\text{C}$
- High gain: $1.8 \times 10^6\text{V/V}$
- High output drive capability: $\pm 12\text{V}$ into 600Ω load
- High slew rate: $2.8\text{V}/\mu\text{S}$ ($17\text{V}/\mu\text{S}$, OP37)
- Wide gain bandwidth product: 8MHz (63MHz , OP37)
- Good common mode rejection ratio: 126dB
- Low input offset voltage: $10\mu\text{V}$
- Minimum low frequency noise: $0.08\mu\text{V}_{\text{p-p}}$ 0.1Hz to 10Hz
- Low input bias and offset currents: 10nA

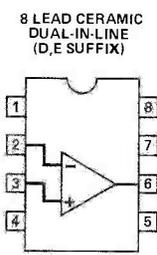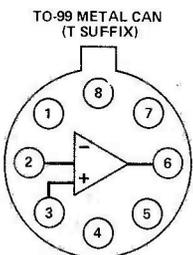




PIN	FUNCTION
1	V _{OS} TRIM
2	INVERTING INPUT
3	NON-INVERTING INPUT
4	V ₋
6	OUTPUT
7	V ₊
8	V _{OS} TRIM

Absolute Maximum Ratings

Supply Voltage.....	+22V
Input Voltage ¹	$\pm 22\text{V}$
Differential Input Voltage.....	$\pm 0.7\text{V}$
Internal Power Dissipation.....	500mW
Output Short Circuit Duration.....	Indefinite
Storage	
Temperature Range.....	-65°C to $+150^\circ\text{C}$
Operating Temperature Range	
OP-37A/B/C.....	-55°C to $+125^\circ\text{C}$
OP-37E/F/G.....	-25°C to $+85^\circ\text{C}$

Description

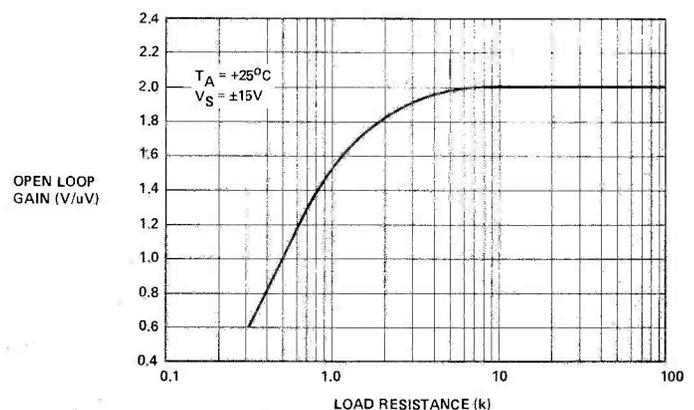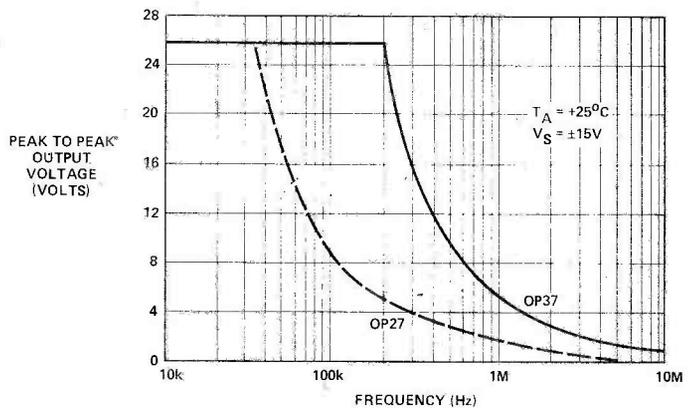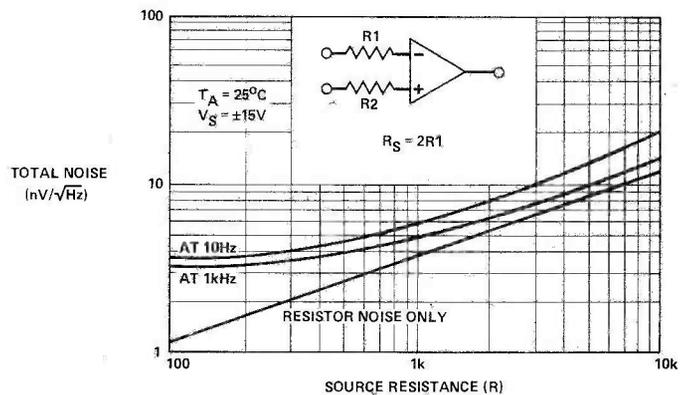The OP27 and OP37 are designed for use where low noise (both spectral density and burst), wide bandwidth, and high slew rate are required along with low input offset voltage, low input offset temperature coefficient, and low input bias currents in gains greater than or equal to ten. Digital nulling techniques performed at wafer sort make it



Electrical Characteristics

($V_s = \pm 15V$ and $T_A = 25^\circ C$ unless otherwise stated)

Parameters	Test Conditions	OP-27A/E OP-37A/E			OP-27B/F OP-37B/F			OP-27C/G OP-37C/G			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Input Offset Voltage ⁵			10	25		20	60		30	100	μV
Input Offset Current			7.0	35		9.0	50		12	75	nA
Input Bias Current			± 10	± 40		± 12	± 55		± 15	± 80	nA
Input Noise Voltage ²	0.1Hz to 10Hz		0.08	0.18		0.08	0.18		0.09	0.25	μV_{p-p}
Input Noise Voltage Density ²	$f_o = 10Hz$		3.5	5.5		3.5	5.5		3.8	8.0	$\frac{nV}{\sqrt{Hz}}$
	$f_o = 30Hz$		3.1	4.5		3.1	4.5		3.3	5.6	$\frac{nV}{\sqrt{Hz}}$
	$f_o = 1000Hz$		3.0	3.8		3.0	3.8		3.2	4.5	$\frac{nV}{\sqrt{Hz}}$
Input Noise Current Density ²	$f_o = 10Hz$		1.7	4.0		1.7	4.0		1.7		$\frac{pA}{\sqrt{Hz}}$
	$f_o = 30Hz$		1.0	2.3		1.0	2.3		1.0		$\frac{pA}{\sqrt{Hz}}$
	$f_o = 1000Hz$		0.4	0.6		0.4	0.6		0.4	0.6	$\frac{pA}{\sqrt{Hz}}$
Input Resistance (Diff. Mode) ⁴		1.5	6.0		1.2	5.0		0.8	4.0		M Ω
Input Resistance (Com. Mode)			3.0			2.5			2.0		G Ω
Input Voltage Range ³		± 11	± 12.3		± 11	± 12.3		± 11	± 12.3		V
Slew Rate ⁴ (OP27)	$R_L \geq 2k\Omega$	1.7	2.8		1.7	2.8		1.7	2.8		V/ μS
Slew Rate ⁴ (OP37)	$R_L \geq 2k\Omega$	11	17		11	17		11	17		V/ μS
Gain Bandwidth Prod. ⁴ (OP27)		5.0	8.0		5.0	8.0		5.0	8.0		MHz
Gain Bandwidth Prod. ⁴ (OP37)	$f_o = 10kHz$	45	63		45	63		45	63		MHz
Open Loop Output Resistance	$V_o = 0, I_o = 0$		70			70			70		Ω
Power Consumption			90	140		90	140		100	170	mW
Offset Adjustment Range	$R_p = 10k\Omega$		± 4.0			± 4.0			± 4.0		mV



Notes: 1. For supply voltages less than $\pm 22V$, the absolute maximum input voltage is equal to the supply voltage.

2. This parameter is tested on a sample basis only, and guaranteed to an LTPD of 10.

3. Caution the common mode input range is a function of supply voltage, see typical performance curves. Also, the input protection diodes do not allow the device to be removed or inserted into the circuit without first removing power.

4. Parameter is guaranteed by design.

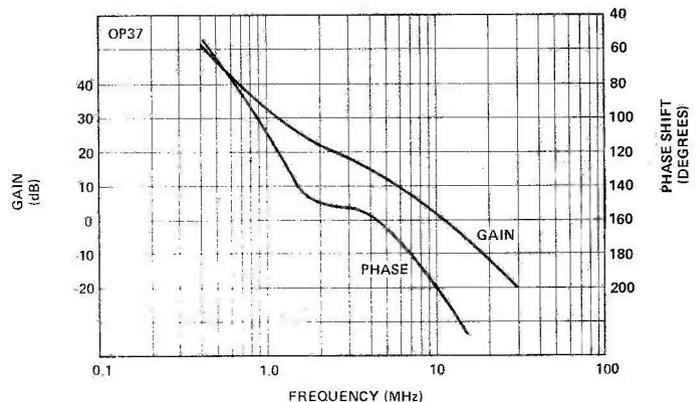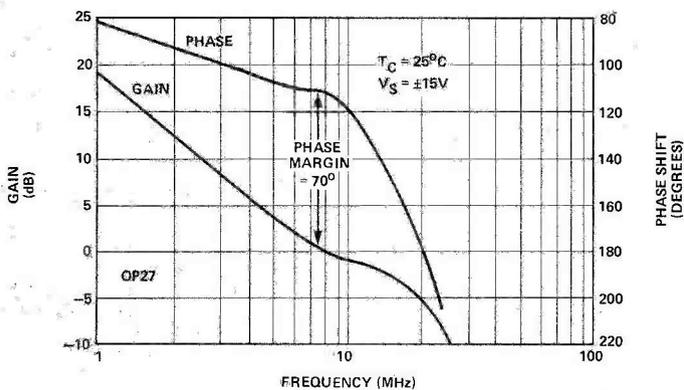5. Input offset voltage measurements are performed by automated test equipment approximately 0.5 seconds after application of power.



feasible to guarantee temperature stable input offset voltages as low as $25 \mu V$. Input bias current cancellation techniques are used to obtain 10 nA input bias currents.

These op-amps are especially useful for instrumentation and professional quality audio systems. Applying the slew rate — power bandwidth equation ($f_p = SR/2\pi V_p$) the OP27 will have an undistorted output up to its power bandwidth frequency of 34 kHz, and an undistorted output of $8V_{p-p}$ at 100 kHz. The same equation applied to the OP37 gives a power bandwidth frequency of 208 kHz, with an undistorted output of $8 V_{p-p}$ at 338 kHz. This performance is adequate for the most demanding high fidelity

applications.

In addition to providing superior performance for the professional audio market the design of these op-amps uniquely addresses the needs of the instrumentation designer. Power supply rejection and common mode rejection are both typically 120dB. Input offset voltage can be externally trimmed without affecting input offset voltage drift with temperature or time.

The OP27 has a phase margin of 70° at unity gain, which guards against peaking (and ringing) in low gain feedback circuits. Stable operation can be obtained with capacitive loads up to 2000pF. By decoupling the load


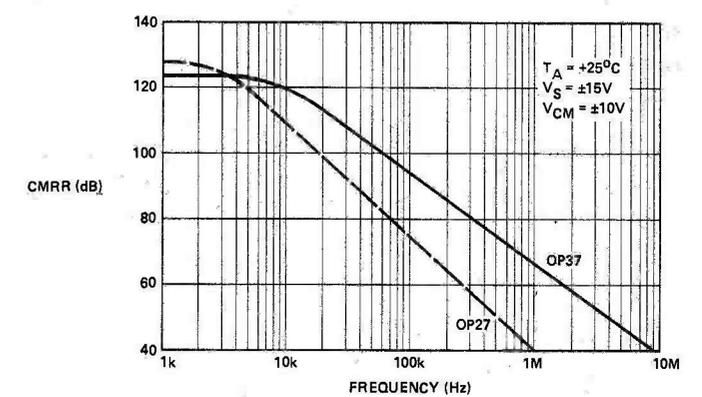
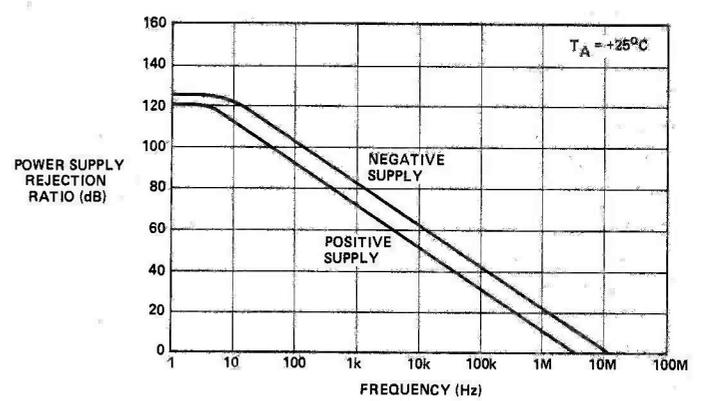
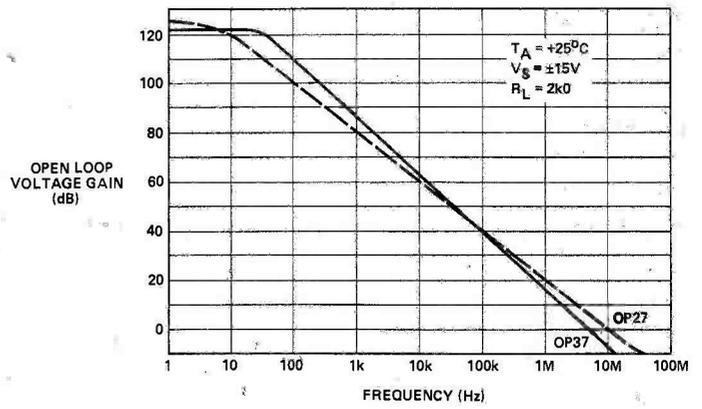
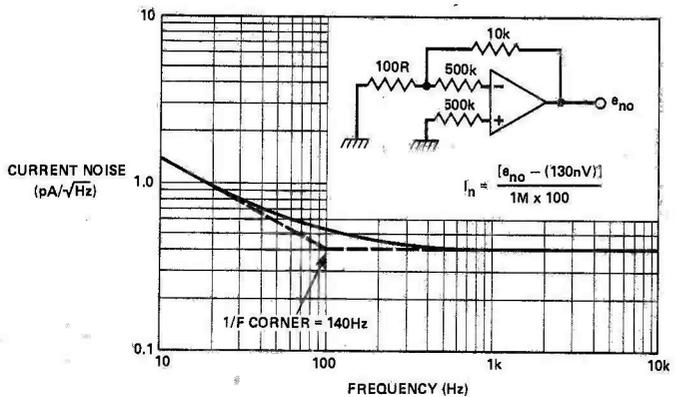
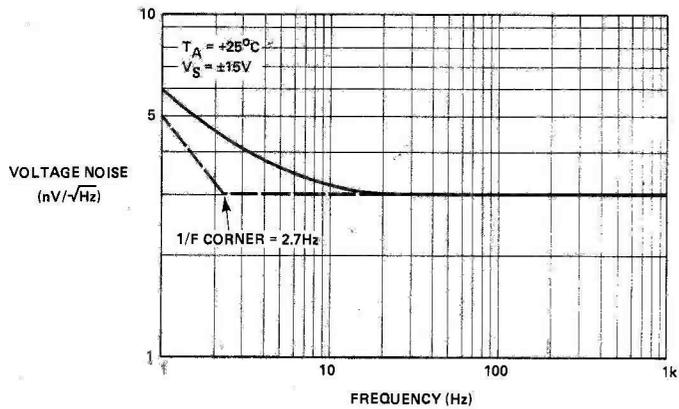
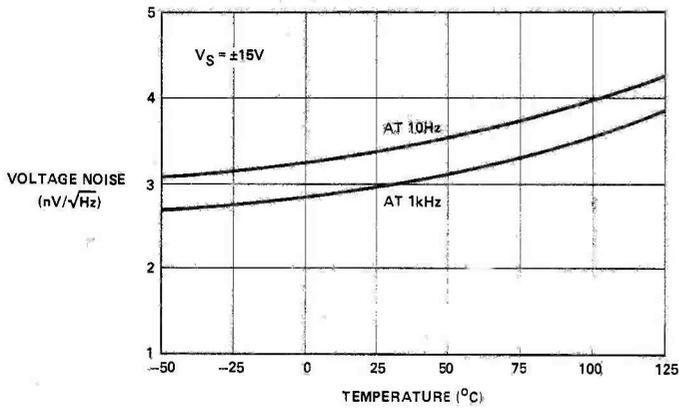


Fig. 1 (left) Offset nulling
Fig. 2 (right) Large signal transient response of OP37

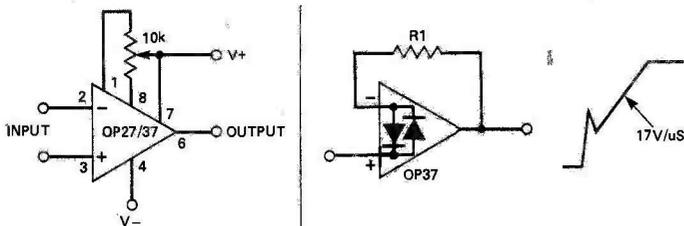


capacitance with a series resistor of 50R or more load capacitances larger than 2000pF can be accommodated. Input offset voltage can be externally trimmed without affecting input offset voltage drift with temperature or time.

Low Impedance Microphone Preamp

In this preamp the transformer converts the low microphone impedance up to a value that is close to the optimum source impedance required by the OP37 for best noise performance. The optimum source impedance can be calculated as the ratio of e_n/i_n which for the OP37 is ap-

Fig. 3 Low-Z microphone preamp.

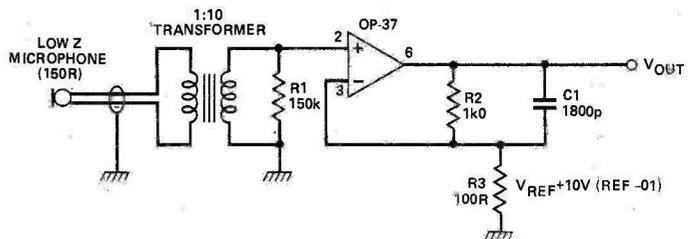

proximately 7000R. Fortunately the noise performance does not degrade appreciably until the source impedance is four or five times this optimum value. The source impedance at the output of this transformer of 15k still provides near optimum noise performance. C1 rolls off the high frequency response at 90 kHz giving a noise power bandwidth of 140 kHz.

Instrumentation

The OP27 and OP37 are particularly adaptable to instrumentation applications. When wired into a single op-amp difference amplifier configuration, they exhibit

outstanding common mode rejection ratio. The spot voltage noise is so low that it is dominated almost entirely by the resistor Johnson noise.

The three op amp instrumentation amplifier of Figure 8 avoids the low input impedance characteristics of difference amplifiers at the expense of two more operational amplifiers and a slight degradation in noise performance. The noise increases because two amplifiers are contributing to the input voltage spectral noise instead of one. Thus the noise contribution, exclusive of resistor Johnson noise, increases by slightly more than the $\sqrt{2}$. The spectral noise voltage increases from approximately 3 nV/ $\sqrt{\text{Hz}}$ to approximately 4.9 nV/ $\sqrt{\text{Hz}}$, with the third amplifier contributing about 10% of the noise.

The gain of the input amplifier is set at 25 and the second stage at 40 for an overall gain of 1000. R7 is trimmed to optimize the common mode rejection (CMRR) with frequency. With balanced source resistors a CMRR of 100dB is achieved. With a 1k source impedance imbalance CMRR is degraded to 80dB at 5 kHz due to the finite (3G Ω) input impedance.

RIAA Phono Preamp

The new moving coil magnetic phono cartridges have sensitivities that are an order of magnitude lower than the sensitivity of a typical moving magnet cartridge (0.1 mV per cm/S versus 1.0 mV per cm/S). This places a greater burden on the preamplifier to achieve more gain and less noise. The OP27 is ideally suited for this task. The object in designing an RIAA phono preamp is to achieve the RIAA gain-frequency response curve while contributing as little noise as possible to avoid masking the very small signal generated by the cartridge. The circuit shown is adjusted to match a 40dB RIAA curve. Note that by convention the RIAA gain is specified at 1 kHz. With the "break points" of the curve specified at 50, 500 and 2.1 kHz respectively the entire curve is fixed by the specified gain at 1 kHz.

The circuit is designed to operate with a 3/4000 step up transformer to present the optimum source impedance to the amplifier for best noise figure. The optimum source impedance is obtained as the ratio of the spectral noise voltage e_n to the spectral noise current i_n (when e_n has dimensions of nV/ $\sqrt{\text{Hz}}$ and i_n has dimensions of pA/ $\sqrt{\text{Hz}}$ and the ratio has dimensions of k Ω). The circuit is designed to be tested and adjusted independent of the transformer; for this purpose introduce a very low level signal around 1mV at test point TP-1. The first stage is a wideband stage which provides a small amount of gain (1 + R4/R5) approximately equal to 10dB. Low value feedback resistors must be used to prevent additional noise due to the spectral current noise or excessive Johnson noise. The gain of the first stage reduces the noise contribution of the second stage. The RIAA transfer curve poles and zeros are due entirely to the feedback network of the second stage.

The poles and zeros of the RIAA feedback network are

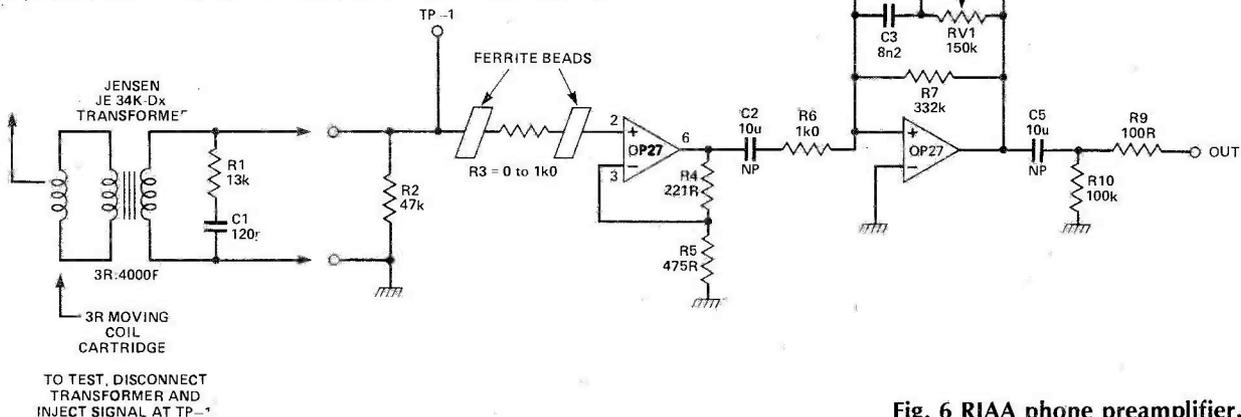


Fig. 6 RIAA phono preamplifier. ETI


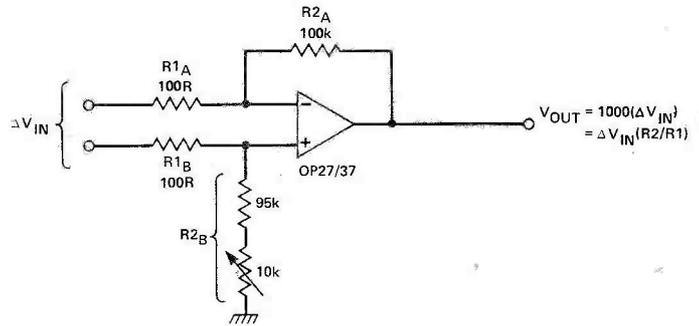


Fig. 4 Single op-amp difference circuit.
Fig. 5 Three op-amp difference amplifier.

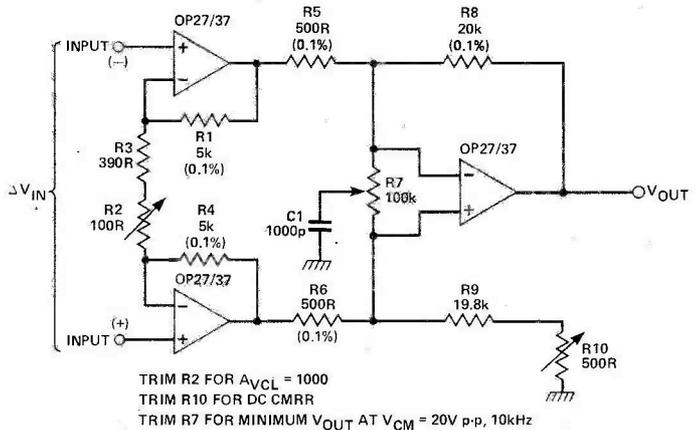

sufficiently separated in frequency that they may be estimated with the following equations:

$$f_1(50\text{Hz}) \approx \frac{1}{2\pi R7C3} \quad f_2(500\text{Hz}) \approx \frac{1}{2\pi R8C3}$$

$$f_6(2100\text{Hz}) \approx \frac{1}{2\pi R8C2}$$

These equations are only approximations. Final tuning is performed with the adjustable capacitors and potentiometers; by successfully injecting 100 Hz, 1000Hz and 21 kHz at TP1 and adjusting CV1, RV1 and CV2 for -6dB, -20dB, and -40dB (relative to LF response).

HORIZON ELECTRONICS
(Midlands)
Dept. H/H Charlotte St. Rugby Tel: 78138
Prime quality. TERRIFIC PRICES. Mail order only

REGULATORS (5/12/15V)	COMPACITORS	AXIAL	LINEAR IC's
100mA 7.5V 28p	200µA (60V)	1.0 MFD 7p	741 50c
1 amp 7.5V 33p	1.0 MFD 7p	2.2 MFD 4.7p	748 7555 70p
7.5V 25p	2.2 MFD 8p	4.7 MFD 10p	ICM 7556 130p
ZENERS (3.3 to 30V)	4.7 MFD 10p	10 MFD 12p	LM 301A 40p
3.00mV 5p	10 MFD 12p	22 MFD 14p	LF 353 70p
1.3 watt 12p	22 MFD 14p	47 MFD 21p	LM 324 27p
DIODES	47 MFD 21p	100 MFD 25p	LM 390 80p
IN 4001 3p	100 MFD 25p	220 MFD 47p	NE 567 85p
4002 3p	TRANSISTORS	470 55p	ICM 2320 285p
4004/6 8p	BC107B 8p	1000 70p	TDA 2002 185p
IN 2401 12p	BC108B 9p		
5408 13p	BC109B 10p		
5408 14p	BC140 25p		
DIODES	BC142 22p		
1 amp 50v 2 Red 7p	BC160 35p		
2 amp 100v 2 Green 8p	BC170 15p		
2 amp 200v 2 Yellow 8p	BC182 7p		
LED's	BC212 7p		
2 Red 7p	BC237 8p		
2 Green 8p	BD300 52p		
2 Yellow 8p	BC301 52p		
TRIACS (plastic)	BC302 35p		
4 amp 400v 4 amp 400v 80p	BC303 35p		
8 amp 400v 8 amp 400v 80p	BC304 40p		
25 amp 400v 165p	BD138 33p		
	BD138 35p		

ABOVE: Just a few examples. Send S.A.E./List
ADD: 65p p&p to all orders under £5.00
VAT: add 15% VAT to total order value

FOR HI-FI & ELECTRONICS ENTHUSIASTS
CONCEPT ELECTRONICS LTD
51 Tollington Road, London N7 6PB
Mail order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverbation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

Professional rack mounting cabinet

Panel Size	Rear Box	Price
WH (inch)	WHD	AL STEEL
19 x 5	17 x 4.5 x 10	27.54 23.54
19 x 4	17 x 3.5 x 10	25.24 21.24
19 x 3.5	17 x 3 x 10	24.09 20.09
19 x 3	17 x 2.5 x 10	24.09 —
19 x 2.5	17 x 2 x 10	22.94 18.94
19 x 6	17 x 5.5 x 12	28.69 24.69
19 x 5	17 x 4.5 x 12	27.54 23.54
19 x 4	17 x 3.5 x 12	25.24 21.24
19 x 3.5	17 x 3 x 12	24.09 20.09
17 x 3.5	15.5 x 3 x 9	21.79 17.79
17 x 2.5	15.5 x 2 x 9	20.64 16.64
17 x 4	15.5 x 3.5 x 12	25.24 21.24
17 x 3	15.5 x 2.5 x 12	24.09 20.09

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover removable for access
★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.

The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

CONTROL MODULES

TY-7 Electronic touch switch **£2.90 Kit £4.50 Ass.**
TY-11 Light activated switch **£2.20 Kit £3.50 Ass.**
TY-18 Sound activated switch (Clap switch) **£4.50 Kit £5.95 Ass.**
TY-38 Sound activated switch (voice-switch) **£5.50 Kit £7.50 Ass.**
TY-41 Infra-red remote control (Receiver and transmitter) **£17.20 Kit £21.95 Ass.**

HI-FI AMPLIFIER MODULES

TA-323A 30W + 30W stereo amplifier **£18.95 Kit £23.95 Ass.**
TA-820 60W + 60W stereo amplifier **£27.50 Kit £33.50 Ass.**
TA-920 70W + 70W stereo amplifier **£35.50 Kit £42.50 Ass.**

BECOME A RADIO AMATEUR

Train now for the Radio Amateur Licence examination. No previous knowledge needed, only a few hours per week of home study for 3 to 6 months. Post coupon now for details or tel. 0734 51515 (24 hr service)

British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE brochure without obligation from:—
British National Radio & Electronics School
READING, BERKS. RG1 1BR

ACCREDITED BY
COUNCIL FOR THE ACCREDITATION
OF CORRESPONDENCE COLLEGES
CACC

Name

Address

ETI/11/846 BLOCK CAPS PLEASE

Branime
TEACHING KITS
BUY YOUR KNOWLEDGE

TYPE 161B
DUAL POWER SUPPLY KIT

INCORPORATES A POSITIVE & A NEGATIVE REGULATED SUPPLY

BOTH ARE ISOLATED & ADJUSTABLE 1.3V TO 16V D.C.
Interconnect to give 2.6V to 32V or
-1.3V/0/+1.3V to -16V/0/+16V
Output current 1A at 16V to 0.35A at 1.3V
Ripple is less than 1mV

£25.99
inc. P & P and VAT

Built & Tested
£37.95 inc. P&P and VAT

Comprehensive design details with calculations are included so that the kit is an exercise in power supply design. The kit, which uses quality components, is complete with instructions. Case punched and stove enamelled in attractive blue and grey with a printed front panel to give a professional finish. Excellent for the beginner, the experienced amateur and as a tutorial for schools and colleges.

SEND CHEQUE OR P.O. ALLOW 21 DAYS FOR DELIVERY

BRANIME MARKETING LTD DEPT. ETI/11
BALTHANE IND. EST., BALLASALLA, ISLE OF MAN

FREQUENCY COUNTERS

The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

★ Measuring typically 2Hz - 1.2GHz	★ Low Pass Filter
★ Sensitivity <50mV at 1GHz	★ Battery or Mains
★ Setability 0.5ppm	★ Factory Calibrated
★ High Accuracy	★ 1-Year Guarantee
★ 3 Gate Times	★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100 (100MHz)	£104.07	Illustrated colour brochure with technical specification and prices available on request.
METEOR 600 (600MHz)	£133.97	
METEOR 1000 (1GHz)	£184.57	

BLACK STAR LTD, 9A Crown Street, St.Ives, Huntingdon, Cambs. PE17 4EB, England.
Tel: (0480) 62440 Telex: 32339

Designed and manufactured in Britain. **Black★Sta**



ACTIVE LOUDSPEAKER

In the halycon days of the hi-fi boom, DIY loudspeakers were published at a rate of several a month. However, it's now been over a year since we last published a design in ETI. Jeff Macaulay takes a fresh look!

There is confusion reigning in the hi-fi world at the moment, and reading some hi-fi magazines you might well be convinced that the only approach is to spend all your money on just the record deck and make do with whatever amp and speakers you can afford on the little change you have left from your life's savings.

The alternative is to make do with the latest chrome-plated wonder with built-in obsolescence (though, thankfully, hi-fi rack systems seem to have gone out of fashion). To read the advertising blurb that accompanies these units, one could be forgiven for thinking that products launched as recently as the previous week were junk

Fig. 1 (below and page facing) Circuit diagram of the active loudspeaker.

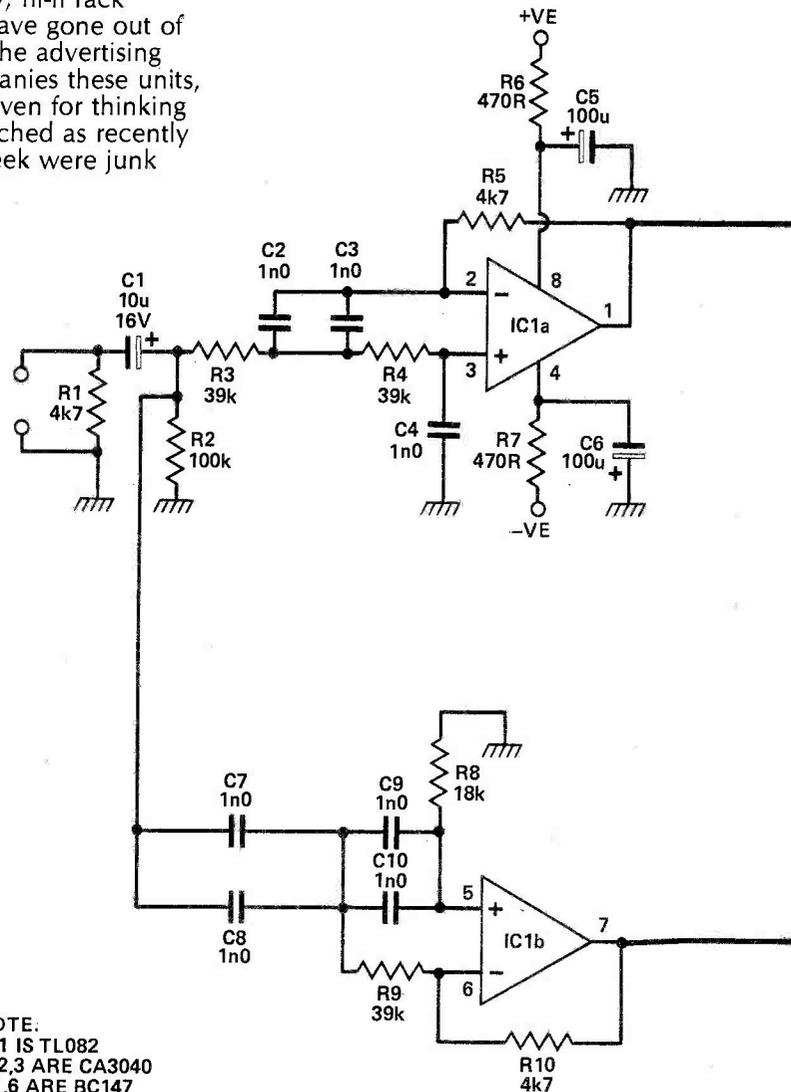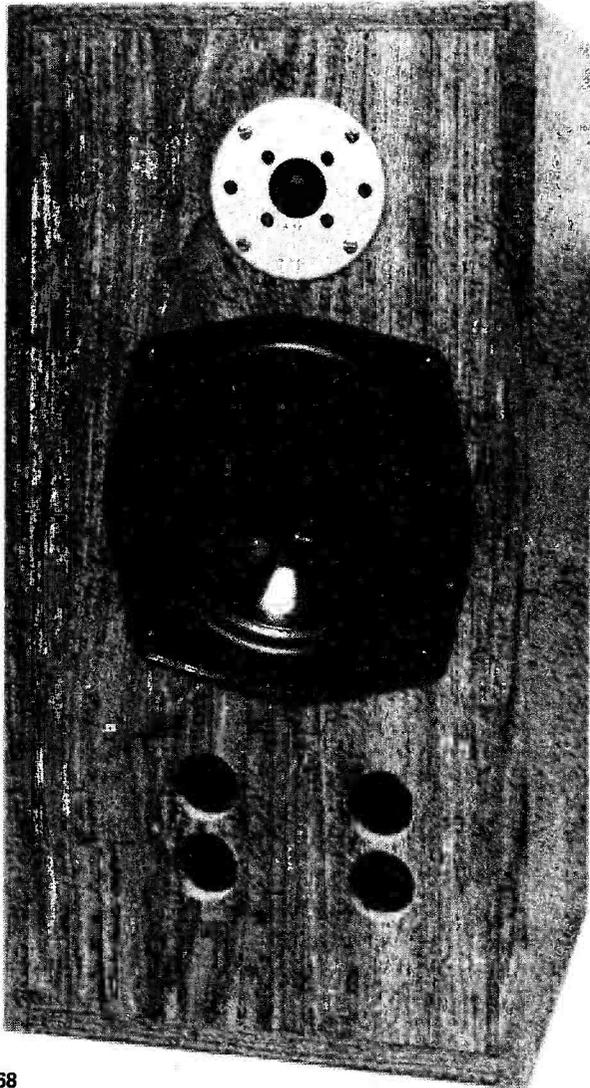

NOTE:
 IC1 IS TL082
 IC2,3 ARE CA3040
 Q1,6 ARE BC147
 Q2,7 ARE BC142
 Q3,5,8,9 ARE 2N3055
 Q4,9 ARE BC143
 LS1 IS B200 8R
 LS1 IS HD100/25 8R

*Q3,5,8,10 ARE MOUNTED ON A HEATSINK

HOW IT WORKS

compared to the current 'flavour of the month'.

This situation has been compounded by the introduction of compact disc — is it worth spending money on analogue systems when digital is just around the corner? One can already hear the cries of anguish from certain highland-dwelling turntable manufacturers.

While we'll admit that it is a truism that if you degrade the sound at the start of its journey through your hi-fi, there is absolutely nothing you can do to improve it, there is still a case for having a good speaker system to do the final conversion of electrical energy into sound energy.

Unfortunately no currently available drive unit can be made to cover the whole audio spectrum properly. For good bass response a heavy large diameter cone is required. The actual amount of bass that can be radiated by the speaker is directly proportional to both the

For the purposes of analysis, the circuit can be split up into four sections: the low-pass filter around IC1a, the high-pass filter around IC1b and the two power amplifiers around IC2 and IC3.

The two filters are based on the well-known Sallen and Key configurations, and both have component values such as to give a Butterworth type response with a Q of 0.7. All that this means is that the values are chosen so as to give a minimum of response ripples in the pass-band whilst giving a maximum roll-off outside the pass-band that a two-pole filter can deliver.

It is usual to include some compensation for the unevenness of the responses of the drive units at this stage. However, as we've already explained, both the drive units selected have very good flat responses, and this was judged to make compensation superfluous.

Both the power amplifiers are the same (with the minor difference of the connection C13 and C14), and are based on the 'brains and brawn' principle. In this, the op-amps IC2 and IC3 provide the open-loop gain for the system, while the transistors simply provide a current sourcing capability well beyond that of


the op-amps.

Taking a close look at the bass amplifier circuit, IC2 is a CMOS type op-amp which offers very low noise and a very good slew rate. The output from this is fed to the quasi-complementary output stage built around Q1 to 5.

To avoid serious distortion at the crossover between the lower and upper sets of driver transistors, a bias voltage is provided between the 'bases' of the compound output transistors (Q2/3 and Q4/5) by Q1 which is, with PR1, wired as a V_{be} multiplier.

Because of the high input signal, very low gain is needed from the power stage, so the feedback level can be very high. R12 and RV1 in one arm and R11 in the other set the level of feedback, so RV1 can be used to adjust the level of the bass output — in fact, it's wired as a balance control, so it simultaneously adjusts the treble output.

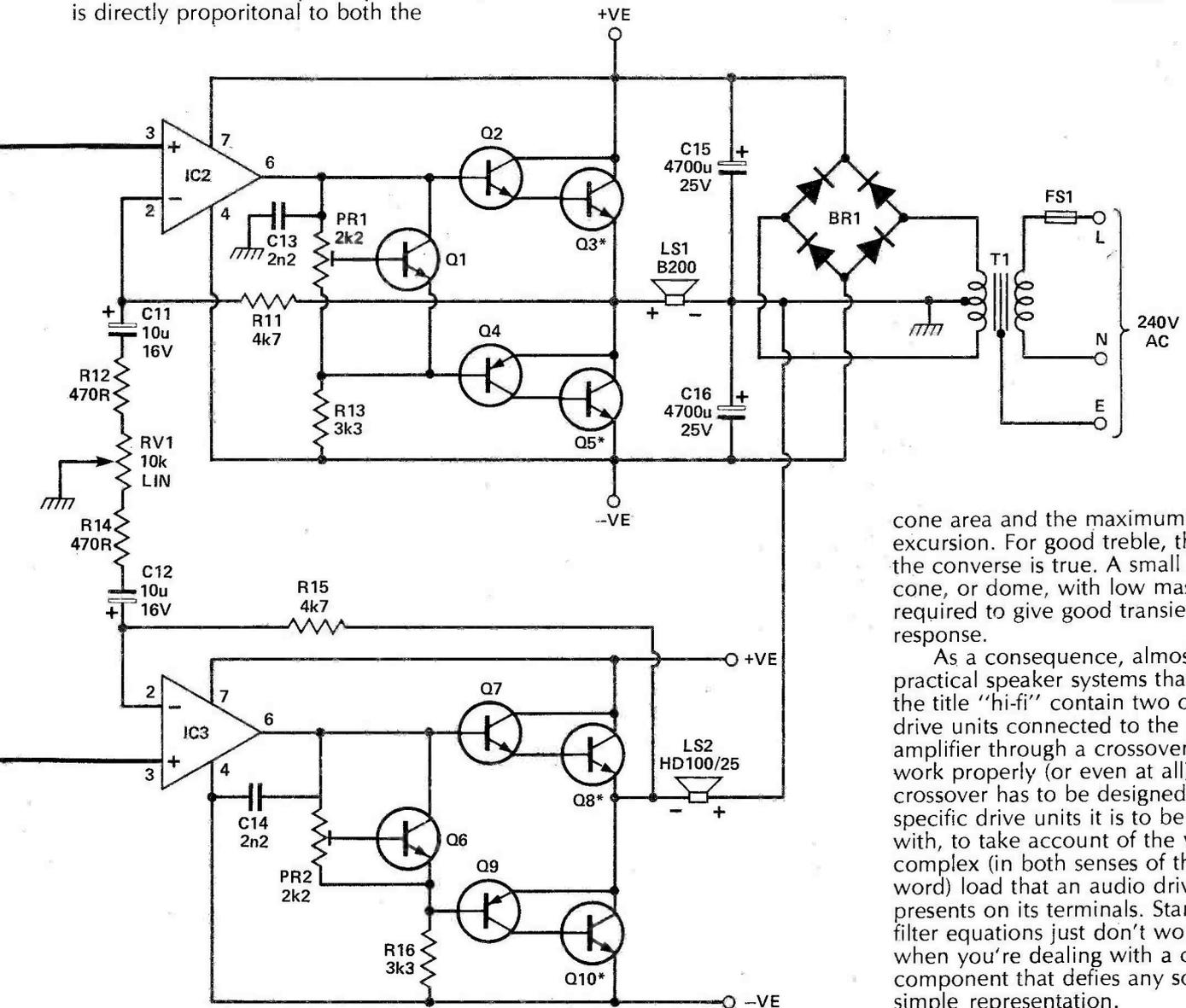Finally, note that the treble and bass units are connected in the opposite phases. This is to keep the response level at crossover; without this the two units would be in antiphase at the crossover point (this is due to the inevitable phase alteration caused by the filters).



cone area and the maximum cone excursion. For good treble, though, the converse is true. A small light cone, or dome, with low mass is required to give good transient response.

As a consequence, almost all practical speaker systems that merit the title "hi-fi" contain two or more drive units connected to the power amplifier through a crossover. To work properly (or even at all) the crossover has to be designed for the specific drive units it is to be used with, to take account of the very complex (in both senses of the word) load that an audio drive unit presents on its terminals. Standard filter equations just don't work when you're dealing with a circuit component that defies any sort of simple representation.

Another problem is that crossovers, being passive components, absorb power intended for the audio drive units. As a result, a 100W amplifier may be needed to drive a speaker system whose drive units would require only a few watts without the crossover in the way.

Using active (or passive if you prefer) filters before the power amplifier has the potential to solve all these problems. For a start, the filters are built using standard components and will produce near-perfect text-book responses; the impedance variations of the drive units will have no effect at all.

A hidden benefit is that if the bass unit is driven into clipping, the ill effects are not transmitted to the high frequency unit, in a conventional cross-over system, the high-frequency harmonics caused by clipping are directly coupled to the tweeter and this can have destructive consequences.

Amongst the many other benefits from this approach is that the speakers will be much better damped, because they see the low impedance of the amplifier, and this leads to a much lower Q figure for any resonances.

Unfortunately, all commercially made active speakers are very expensive — doubly so because you will have to change the amplifier to use them. We've already published one active design, ourselves, back in September 1982, which, although very much cheaper than commercial units, was still rather expensive and large. We felt that there was room for an active design towards the bottom end of the market, so here it is!

To make a simple but effective design, it was decided to restrict the drive unit count to two, and to use two fairly well known units — the KEF B200 and the Audax HD100/25.

The first of these units must be just about the best known bass drive unit of all time! It features an exceptionally flat response up to

about 3 kHz and gives an excellent neutral sound. Driven directly, 12 W RMS will produce 96 dB of sound pressure. The B200 also has quite a nice low bass resonance.

The HD100/25 is a soft dome unit, which delivers a response within ± 3 dB of flat within the range 1.5 kHz to 20 kHz. Soft domes have the advantage over hard domes of not having a resonance within their working range.

Having selected the drive units, the next task is to decide the cross-over characteristics, namely the cross-over frequency, and the roll-off rates.

The choice of these parameters is rather more limited than you might at first think. The B200 has a mechanical roll-off at 3 kHz, and this sets the absolute maximum frequency that you can use this unit to. The HD100 has a fundamental resonance at 800 Hz, so the cross-over point has to be somewhere between these limits. After quite a lot of experimentation and listening tests, 2.5 kHz was found to produce the best results.

Choosing the rate of roll-off was the next task. In theory, higher

order filters with steep cut-offs are attractive, as they will limit the range of frequencies over which both the drive units are operating. In practice, such filters give problems with transient response and in the end, second-order filters were chosen.


Here comes the clever bit: to make the loudspeakers directly compatible with existing equipment (we assumed that potential constructors would have a power amplifier already), the gain of the driver amplifiers was set at close to unity. The consequence of this is that they operate in very low distortion and negligible noise regimes, even with a comparatively simple circuit. The measured distortion from the power amps was found to be well below 0.1% at all output levels short of overload.


This approach has the additional advantage that the active speaker can be hooked directly up to the back of your existing power amplifier.

Boxing It Up

The last part of the design to be considered is the enclosure. The response of any speaker system is critically dependent upon the enclosure. Despite over 50 years of research and development the choice of enclosure type is still rather limited. At present the two most common are the infinite baffle and the reflex.

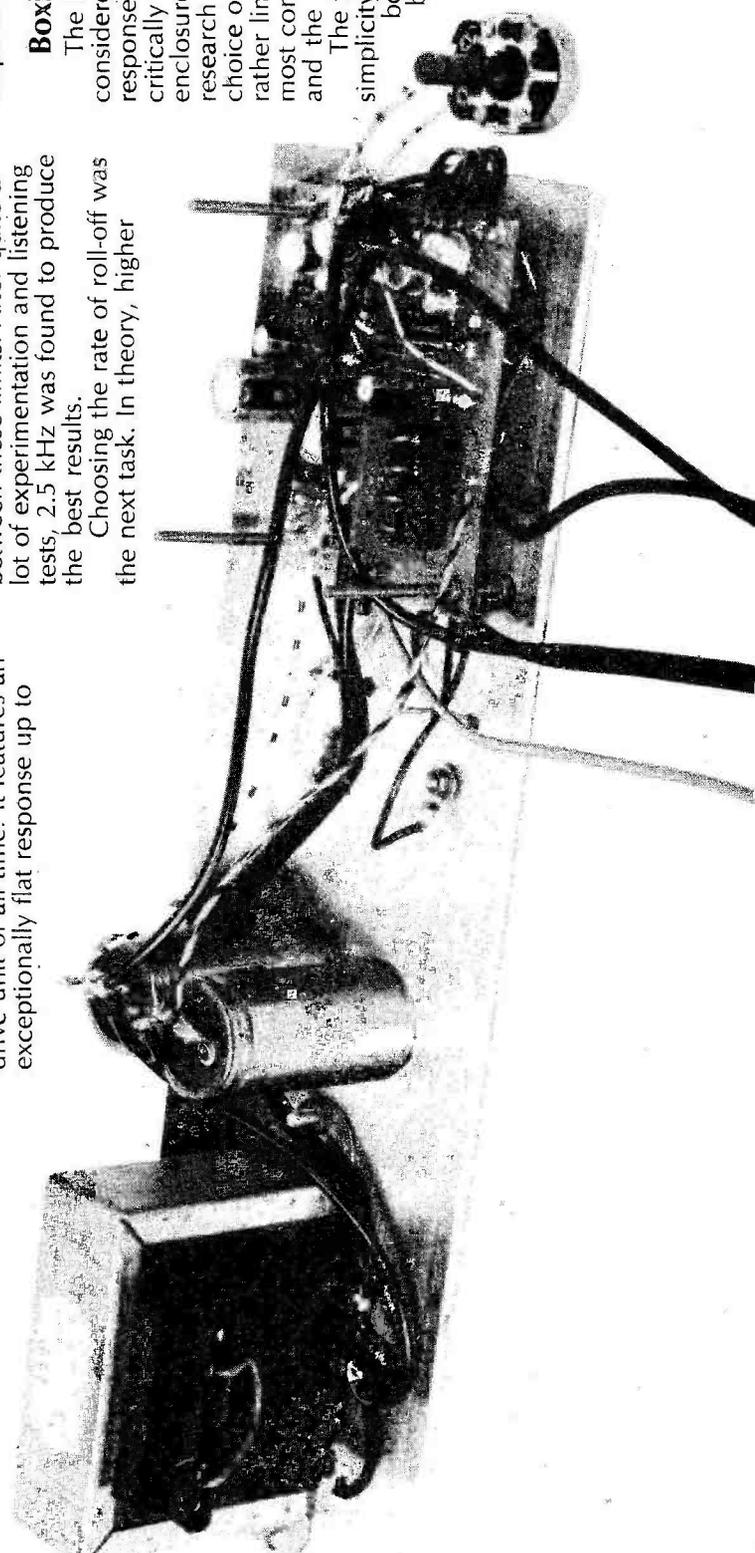The former has the advantage of simplicity since it is merely a closed box. The reflex is also a box but with a tuning port incorporated. The



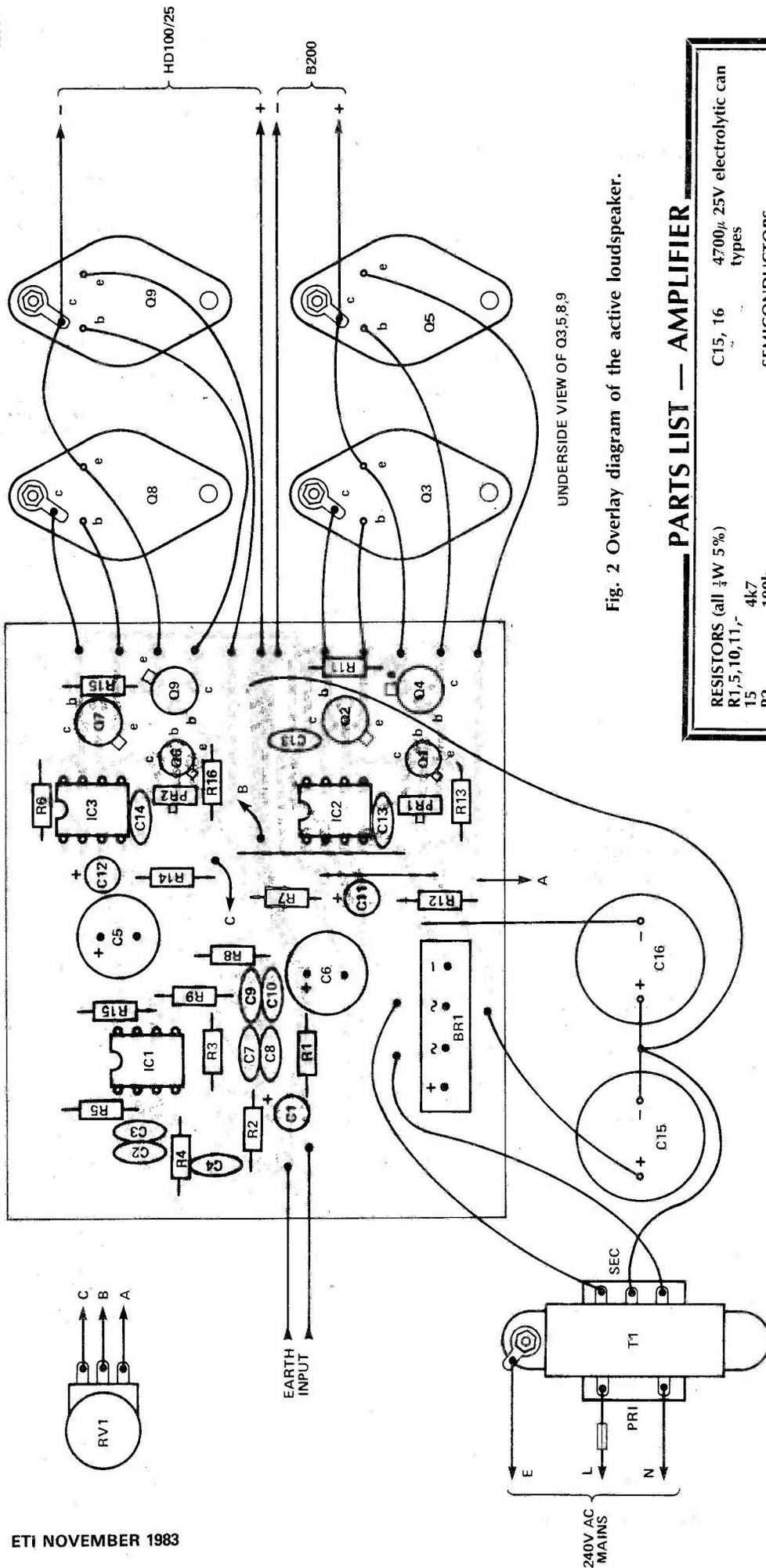

UNDERSIDE VIEW OF Q3,5,8,9

Fig. 2 Overlay diagram of the active loudspeaker.

PARTS LIST — AMPLIFIER

RESISTORS (all $\frac{1}{4}$ W 5%)	C15, 16	4700 μ 25V electrolytic can types
R1, 5, 10, 11, 15	4k7	
R2	100k	
R3, 4, 9	39k	
R6, 7, 12, 14	470R	
R13, 16	3k3	
R8	18k	
RV1	10k linear pot	
PK1, 2	2k2 linear present pots	
CAPACITORS		
C1, 11, 12	10 μ 16V electrolytic, PCB type	
C2, 3, 4, 7, 8, 9, 10	1n0 ceramic or polyester, 5% or better	
C5, 6	100 μ 63V electrolytic, PCB type	
C13, 14	2n2 ceramic or polyester	
SEMICONDUCTORS		
IC1	TL082	
IC2, 3	CA3040	
Q1, 6	BC147	
Q2, 7	BC142	
Q3, 5, 8, 10	2N3055	
Q4, 9	BC143	
BR1	100 PIV 2A bridge rectifier	
MISCELLANEOUS		
T1	Mains transformer, 24V 1.5A	
	mounting kits for 2N3055s (4 off); heatsink (1.1 $^{\circ}$ C/W total or better); PCB; clips for C15, C16; PCB; audio input socket; mains input socket; 1A fuse and holder; wire; nuts and bolts; etc.	

BUYLINES

A full designer-approved kit is available from Bewbush Audio, 26 Hastings Road, Pound Hill, Crawley, Sussex RH10 4AT. The price is £30 per enclosure all-inclusive, for the electronic components, the PCB and heatsink. This does not include the chipboard or the drive units. Please order as kit ET152.

PCBs are available separately for £10 inclusive per pair, and, for the lazy but affluent, ready-built speakers are available at £200 per pair. Please allow 28 days for delivery, as usual. Drive Units are available from Willslow Audio Ltd, 35/39 Church Street, Wilmslow, Cheshire SK9 1AS.


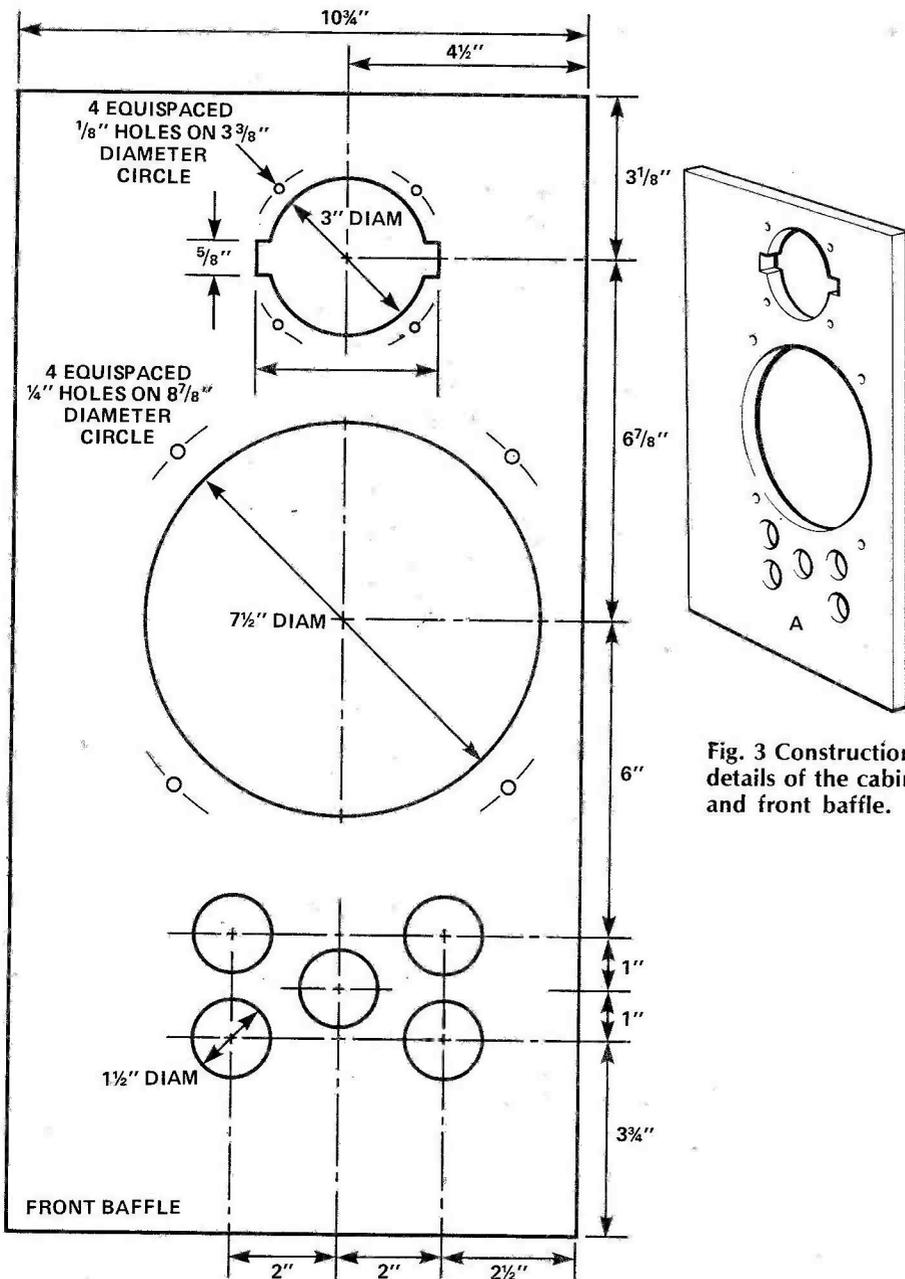


Fig. 3 Construction details of the cabinet and front baffle.

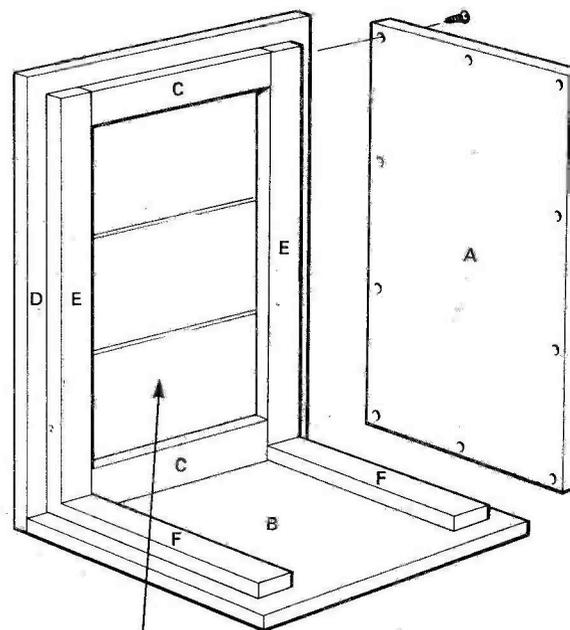

TILES FITTED BETWEEN BATTENS AS SHOWN

PARTS LIST LOUDSPEAKER

These are the parts required for one speaker.

DRIVE UNITS	
Tweeter	Audax HD100/25
Bass Unit	KEFB200
PANELS (all cut from 3/8"/15mm melamine faced chipboard)	
A (2 off)*	21 3/4" by 10 3/4"
B (2 off)	12" by 10 3/4"
C (4 off)	6 1/2" by 2 1/4"
D (2 off)	23" by 12"
E (4 off)	21 3/4" by 2 1/8"
F (4 off)	9" by 2 1/8"
MISCELLANEOUS	
Ceramic tiles, 00" by 00", 00 off; BAF acoustic wadding 00" thick, 00" by 00"; wood glue and chipboard screws.	
*One of these to form the front baffle, see Fig. 3 for details.	

tuning extends the LF response by making the enclosure into a mechanical tuned circuit. However, to operate effectively the enclosure and drive unit have to be matched and adequately damped. This can be difficult for the constructor.

For this design, a resistive port enclosure has been used. This form of loading is similar to the reflex but in this instance the port is fabricated from a series of small holes in the front baffle. This form of loading has one major advantage over both reflex and infinite baffle types. The Q of the speaker resonance is greatly reduced. This renders the enclosure essentially aperiodic at low frequencies. At the same time, deep bass output is augmented by the port whilst the transient response is better than both reflex or sealed box.

Construction

The construction of this project can be neatly divided into two parts, electronic and mechanical. The electronics can be tackled first. As you can see from Fig. 2 most of the components are mounted on the PCB. Very little comment is required about this except to ensure that all the semiconductors and electrolytics are correctly orientated.

The board is mounted on the heatsink along with the power transistors. Before mounting the board, though, be sure to solder the veropins in! To avoid the underside of the board shorting out on the heatsink spacers are used. Alternatively the board can be supported by means of nuts on the retaining bolts.

The power transistors and transformer should now be

mounted onto the heatsink. The latter is mounted with self tapping screws into 1/8" pilot holes drilled as shown. The output stage power transistors are mounted on their insulating kits and a check for short circuits between the cases and the heatsink should be made. Last to be mounted are the smoothing capacitors C15 and C16.

Now the interwiring should be attended to. The leads to the drive units, to the collector and emitters of the power transistors, and those between the PCB and the smoothing capacitors should all be in fairly heavy duty wire.

To set the quiescent current, the following procedure should be followed. First, adjust the two potentiometers PR1 and PR2 so that their sliders are shorted to the outputs of IC2 and IC3 respectively. Check that

this is the case using a multimeter.

Remove the two wire links (or, if you're very clever, don't fit them in the first place!) and connect up two 100R resistors instead. When you switch on, you should find a 2 V voltage drop across both of these. If you don't find this, there must be a fault somewhere — this will be particularly noticeable if either of the resistors should decide to burn out! Also check that the amplifier outputs are at zero volts.

Next adjust PR1 until the voltage across the 100R resistor near to C11 has risen by a further 1.0 volts. Adjust PR2 for a further 1.0 volts increase across this resistor.

Switch off, replace the wire links; the amplifier module is now ready for use. Repeat this procedure for the other channel's module.

Cabinet Making


The mechanical work consists of making the cabinet. Fig. 3 shows the plans for this item. It is absolutely vital to ensure that the chipboard is cut accurately to size, or a little over as you can trim it down to the exact size with a Surform or similar.

It's usual to use either high density or mixed density chipboard for loudspeaker construction. We've taken the slightly unusual step of using melamine-veneered type because the high density chipboard tends to have resonances with higher Qs. The mixed density chip could be used instead, but it's not easy to obtain. Before assembly begins, carefully check the sizes of all the panels. Also check the squareness.

Assembly is achieved as follows: first fix the battens in place using chipboard screws and a suitable glue. Assemble the enclosure except for the front panel, using screws and glue again.

Next fit the amplifier module as shown in the rear of the case; drill holes to accommodate RV1's spindle and the wiring to the mains transformer and for the input connections. You can use either a piece of wire (dodgy) or suitable connectors for these, but do be sure not to leave any air gaps.

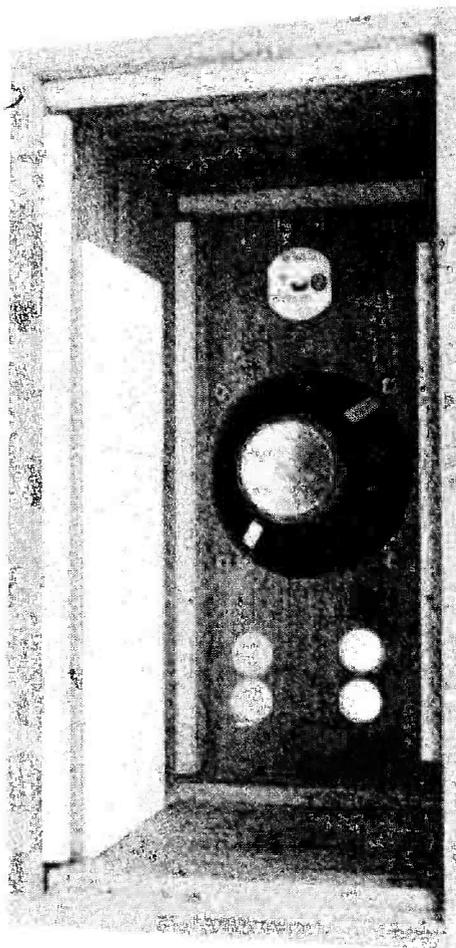Damping of the cabinet walls — by adding mass to them in the form of ceramic tiles — will help to prevent radiation from the rear of the drive unit reaching the outside world through the walls. The tiles will reflect the sound back into the wadding (which you'll be putting into the cabinet at a later stage) where it can be absorbed.



One position where it isn't appropriate to use tiles is on the rear panel behind the bass unit: sound would be reflected back to the cone, which would then re-radiate it, resulting in a smeared sound. However, adequate mass loading is achieved by the heatsink, which, because of its shape, doesn't generate the same problems with reflection.

The ceramic tiles should be glued in as shown; they will fit neatly between the battens with a clearance of about $\frac{1}{4}$ ". Many adhesives are suitable for this job, but we've found that Araldite Rapid, applied as a blob on each corner, gives reliable results.

All that now remains is the front baffle (see Fig. 3 for cutting details). Note that the front baffles are made in mirror image pairs, and that the drive units are slightly offset from the centre line to avoid possible diffraction problems.

The B200 is mounted using the template provided with the speaker unit. Note that the 7.5 mm recess is not cut here. Initial experiments with the recess cut showed no discernible audio advantage so the unnecessary complication has been avoided. Note, though, that the

foam gasket supplied has been used. Also supplied with the B200 are the mounting screws and T nuts.

The tweeter is fitted with four self-tapping screws; $\frac{3}{4}$ " No. 6 size is suitable. Note the recesses needed for the tweeter's terminals: these should be cut out with a rasp or similar. Connect the wires to the tweeter before fitting as it can be difficult to manoeuvre the soldering iron in the confines of the recess.

The last part of the assembly consists of fitting the BAF wadding. This is done in two stages. First cut a section out of the sheet about 12" square. This is stretched across the rear of the B200 and fixed into place with a few panel pins.

The remainder is now rolled up and placed in the cabinet. Finally screw the front baffle into place with chipboard screws. Now the speaker is ready for use!

We haven't included a mains switch in the speaker; if your amp has one, wire the speakers to a suitable switched outlet socket on the existing amplifier. Connect the input to the loudspeaker to the output of the power amplifier, using screened cable if you wish (though this is probably not necessary), and switch on.

USING FIBRE OPTICS

Does copper wire leave you stranded? Is your data missing the bus? L. N. Owen focusses our (tunnel?) vision on a radical alternative.

It is common knowledge that British Telecom and similar organisations now use optical fibres as a transmission medium instead of conventional wiring. This comparatively new technology has been refined to provide a highly efficient system for long-distance telecommunications, but as yet has not been used widely by the experimenter and hobbyist. This is almost certainly because of the high cost and the scale of typical applications (do you really want to build a 10 km transmission line?), but like most new technologies it has produced a number of spin-offs, and some of these do fall within the scope of the humble experimenter.

The main cause of the high cost of transmission systems is the need to use coherent light, that is, light of a specific phase and wavelength. To achieve this, and because of the need for a concentration of high energy to overcome long distance transmission losses, lasers are used. Obviously, if we can do without the laser, things become much cheaper. If we use a much lower energy source, and one which produces incoherent (random) light, we lose the ability to transmit over distances greater than 50m and to use certain phase dependent techniques, but we open up a very broad field of applications indeed.

In all the sample circuits given here, the incoherent light source is a narrow-beam, high-intensity, red LED. These can be bought ready mounted into fibre optic hardware, or, for the painstakingly adventurous, bought loosely and then mounted and polished for the specific application. The former method is strongly recommended for the inexperienced.

When using fibres, signals are transmitted using light. Light is electromagnetic radiation, and thus since it has no electrical charge, it cannot be affected by electric fields. In other words, by using fibre optics, the system is free from electrical noise such as mains or radio interference.

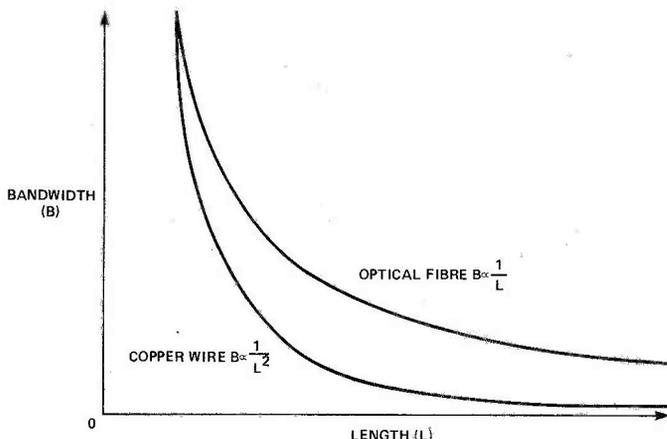


Fig. 1 Comparison of bandwidth over distance for copper wire and optical fibre.

Similarly, magnetic fields have no effect on the signal, and two fibres cannot interfere with each other since the light travels longitudinally, any stray photons being absorbed by the fibre jacket material. Thus crosstalk is non-existent, reducing the need for heavy screening and filtering equipment. Furthermore, as light is the carrier, any safety hazards that may arise with warm wires or electrical sparks are eliminated, a considerable advantage in, for example, the petro-chemical industry, where fibre-optic sensors are rapidly replacing all other systems. In addition, most optical fibres are chemically inert, small in size, light in weight, and are sufficiently flexible to be run just about anywhere. And yet, in spite of all these advantages, the single most important factor in the choice of fibre-optics as a transmission system is the range of frequencies it will handle (see Fig. 1).

For optical fibres

$$\text{Bandwidth} \sim 1/\text{length}$$

whereas for electrical cables

$$\text{Bandwidth} \sim 1/(\text{length})^2$$

Fibre Physics

Before using fibre a few principles must be understood, the most fundamental being that of the critical angle, or total internal reflection (TIR). Referring to Fig. 2, when light passes from one medium to another of a different density, some light will be reflected and the remainder will be refracted. The angle of emergence of the refracted ray, θ , is found from Snell's Law:

$$n_1 \sin \theta = n_2 \sin \phi$$

where n_1 , n_2 are the respective refractive indices and θ is the angle of incidence.

If θ is increased, there will be a specific point where the angle of emergence, θ , is 90° . At this angle there is no partial reflection, and this is known as the critical angle, θ_c . The critical angle can be determined from:

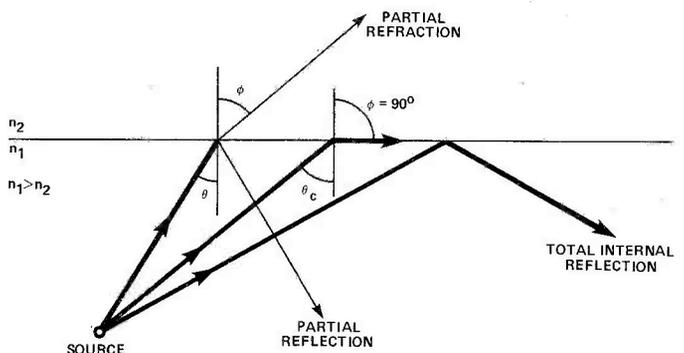


Fig. 2 Illustration of Total Internal Reflection.

$$n_1 \sin \theta_c = n_2 \sin \theta$$

$$\theta = 90^\circ \text{ at the critical angle}$$

$$\sin 90^\circ = 1$$

$$\theta_c = \sin^{-1} (n_2/n_1)$$

If the angle of incidence is further increased, then all the light rays are internally reflected, and this is known as total internal reflection (TIR). Light is transmitted through a fibre by TIR; all other spurious partially reflected, or sub-critical rays dissipate very rapidly.

From this it can be seen that there is a discrete range of angles of valid input. This range is illustrated in Fig. 3 for an air/fibre interface, and is called the acceptance angle, θ_a . Applying Snell's Law again we have:

$$n_0 \sin \theta_a = n_1 \sin (90 - \theta_c)$$

$$= n_1 \cos \theta_c$$

$$= n_1 \sqrt{1 - \sin^2 \theta_c}$$

but $\sin \theta_c = n_1/n_2$

$$\sin \theta_a = \frac{n_1 \sqrt{1 - (n_2/n_1)^2}}{n_1 - n_2}$$

$$= 0.45 \text{ typically}$$

For the most typical case $n_0 = 1$ (air)

$$\sin \theta_a = \frac{n_1 \sqrt{1 - (n_2/n_1)^2}}{\sqrt{n_1^2 - n_2^2}}$$

$$= 0.45 \text{ typically}$$

$\sin \theta_a$ is known as the numerical aperture, and it is a basic parameter for fibre selection.

Fibre is a three-dimensional media, and as such it supports several modes of propagation, the fundamental two being meridional and skew. Skew rays follow light paths which never intersect the fibre axis; a special case of the skew mode of travel is that of a ray which travels parallel to the fibre axis, never being reflected throughout the fibre length. Fundamental fibre theory is concerned only with meridional rays. These, as implied, travel through the fibre axis after each rebound from the fibre/cladding interface.

The final piece of mathematics waiting to be tackled is in calculating transmission losses. There losses come from three major sources:

- i) curvature loss
- ii) core/cladding interface
- iii) fibre material

The curvature loss is a long-distance phenomena and can be ignored for our purposes. Core/cladding interface losses are due to slight non-uniformities causing a localised change in c (the speed of light in the fibre body) and subsequent transmission loss. The attenuations in the fibre material are due to two processes. Firstly, impurities in the fibre can cause light to be scattered in a similar manner to the core/cladding interface. Secondly, impurities within the fibre can absorb certain wavelengths. There are two ways around this latter problem: buy an expensive, highly purified cable, or choose a suitable emitter whose peak

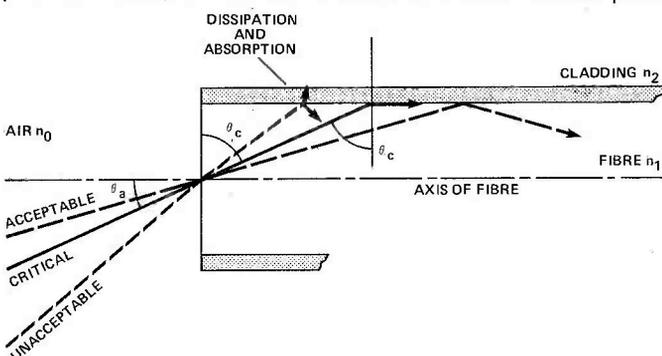


Fig. 3 Acceptable Angle needed to achieve TIR.

wavelength coincides with the maximum transmission spectra of the fibre.

Additional transmission losses come from couplings. The coupling loss is generally given in the respective data sheet (usually in dB/connection). For fibres it is given as dB/km. Thus, for a 1m length of polymer cable with a LED emitter and two bulkhead connectors, the representative calculations are:

Overall

$$\text{attenuation} = (\text{emitter coupling loss}) + 2 * (\text{bulkhead loss}) + (\text{fibre attenuation}) + (\text{detector coupling loss})$$

$$= 2 + 5 + 1 + 2$$

$$= 10 \text{ dB}$$

but the overall

$$\text{attenuation} = 10 \log(\text{emitter flux}/\text{detector flux})$$

$$= 10 \log(\Phi_i/\Phi_r)$$

$$\log \Phi_r = \log \Phi_i - 1 \text{ dB}$$

We usually know the maximum transmissible power, Φ_i = 20 μ W say

$$\log \Phi_r = \log 20 - 1$$

$$\Phi_r = 2 \mu \text{ W}$$

It is also usual to know the optical sensitivity of the detector,

$$S = 0.44 \text{ A/W, say.}$$

Hence

$$\text{current} = 0.44 \text{ or}$$

$$= 0.88 \mu \text{ A maximum}$$

This example shows the importance of keeping connections to a minimum, especially when using high attenuation fibres, which the cheaper variety tend to be.

Techniques

Optical fibres can be used in one of three ways: illumination, data transmission and sensing.

Taking the simplest case first, fibres can be used very effectively as illuminators, the principle being that of providing a light source channelling it where you will. Any form of optical fibre can be used for this purpose, in fact several types of heavy-gauge fishing line have sufficed for short distances. many cables can use the same source and thus provide a very effective and efficient means of illumination. Typical examples are instrument panels, microscopes, meters, switches, logos, etc.

Transmission of data is, as mentioned earlier, not generally practicable for the hobbyist, but there are exceptions, and a few possibilities are discussed in the section on circuits. Both analogue and digital data may be transmitted, although digital data will have to be handled serially.

Sensing covers an enormous range of fibre-optic applications. Optical sensors must be able to convert an input (pressure, temperature, flow, etc.) into variations of either light intensity, phase spectrum, or polarisation, but within the limitations we have set ourselves only amplitude modulation can be used. This not as great a restriction as it might seem because the majority of sensors use amplitude modulation anyway.

Amplitude can be modulated by absorption, emission, and by changes in refractive index. By juggling with these three parameters, fibre optics can be used for measuring strain, pressure, vibration, liquid and solid levels, gas presence, shaft position, temperature, and much more depending upon the type of end transducer used.

One of the simplest applications of fibres as sensory devices is in position detection (Fig. 4a). A similar system using reflected light could be equally well employed (Fig. 4b). The same system can be extended easily to counting

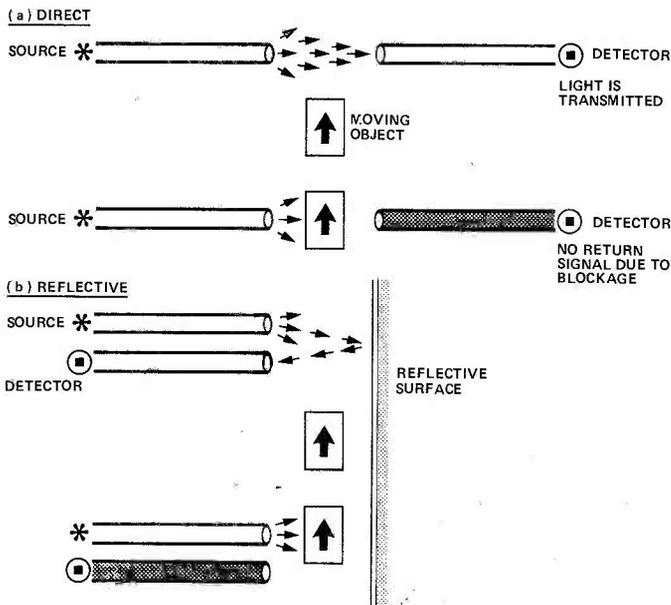


Fig. 4 Position detection using optical fibres.

applications, using pulse counting circuitry, and some forms of quality control. In the reflective mode there is a threshold of surface finish order for the light to be reflected at sufficient intensity, and in the direct mode there are intensity thresholds depending upon the colour density or opacity of the moving object (eg. testing paper quality).

Taking the principle a stage further why not apply it to a shaft encoder — too late, several systems are already in use, operating both in the reflective and direct modes (Fig. 5). Encoders are also being mechanically coupled to measure pressure. With the same ingenuity, attach fins to

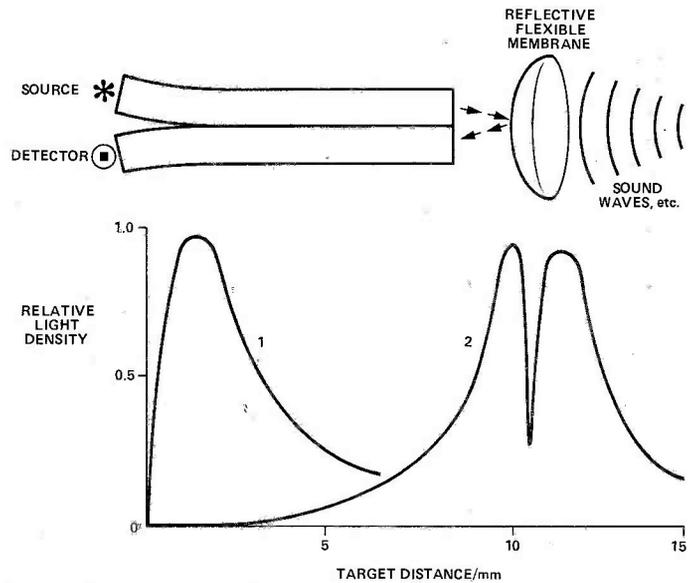


Fig. 6 Measurement of pressure.

another encoded disc (Fig. 5c) and you have a successful form of flow measurement. This particular type operates by counting the number of pulses per unit time and thus calculates the flow rate.

If the reflection method is reconsidered and the polished surface is replaced by a reflective flexible membrane then a form of pressure transducer is realised. Physical arrangement and typical response are shown in Fig. 6. Response 1 is for a single fibre pair whereas trace 2

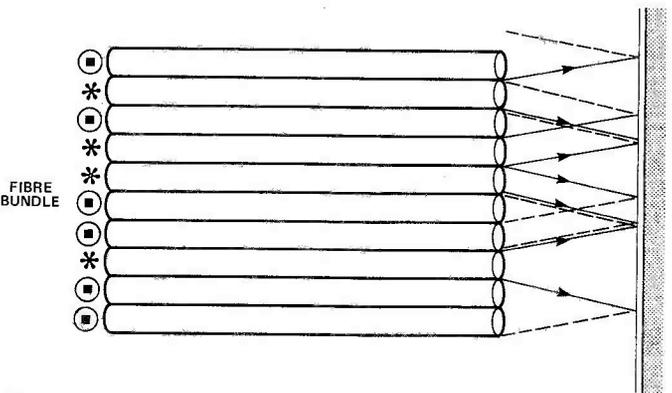


Fig. 7 Principle of the optical level.

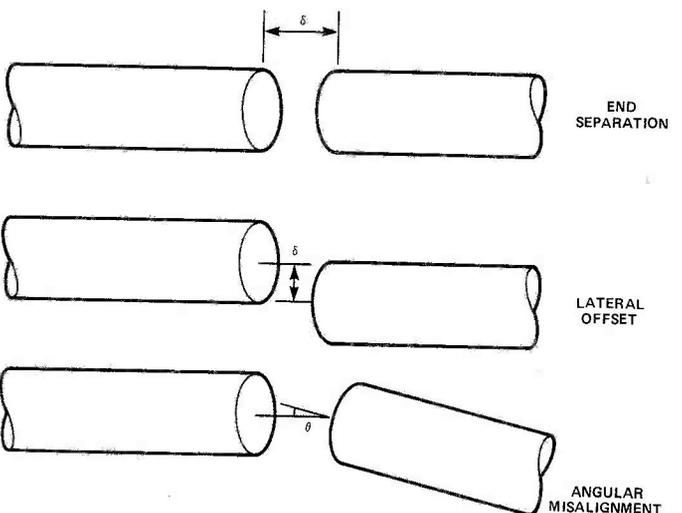


Fig. 8 Transmission loss sensors.

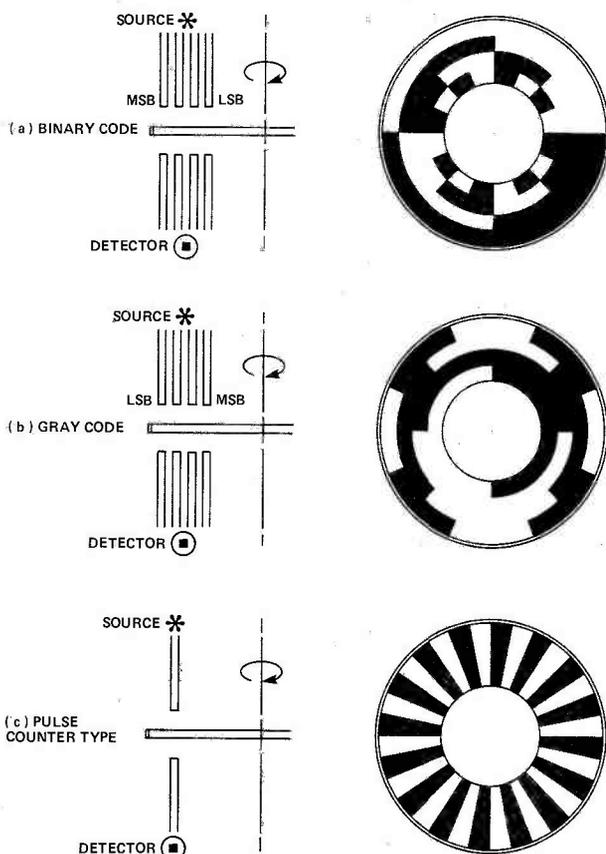


Fig. 5 Shaft encoders and flow meters.

is for a semicircular fibre bundle. This vividly shows that transmission and reception need not be limited to a single fibre, in fact, most cases employ bundles of fibre in various configurations. One of the most popular is a random bunch of emitter and receiver fibres in a larger circular or semicircular cable. The reasoning behind this is that light leaves the fibre generating a cone of light rays. Reflecting this cone will disperse the rays even more, thus covering a greater reception area (Fig. 7). This technique is known as an optical lever.

A very sensitive optical sensor can be produced using the principle illustrated in Fig. 8. Two fibres can be made to lose transmission energy in three different ways, according to the distance between the ends, the lateral displacement, and the angular displacement. Using this technique, researchers have managed to measure displacement of as little as 0.005 angstroms. A graph showing typical characteristics for the three methods is given in Fig. 9.

All of the sensors described above work by interfering with the transmission of light between two terminated fibres. This is by no means the only way in which amplitude modulation can be used in sensor applications,

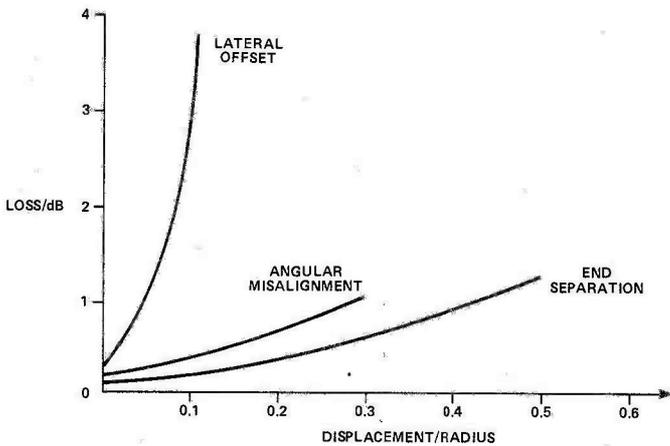


Fig. 9 Characteristics of transmission loss sensors.

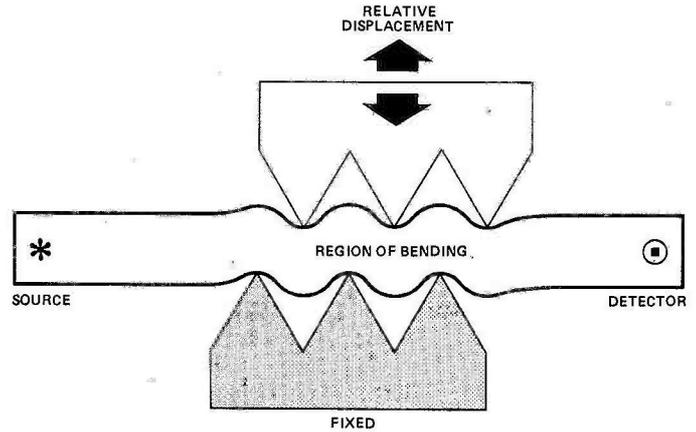


Fig. 10 Fixed/floating microbending transducer.

and a possible alternative is shown in Fig. 10. As mentioned earlier, where the angle of incidence exceeds the critical angle, light is transmitted through the cladding, thus reducing the overall intensity at the detection end. If the critical angle is artificially exceeded by some external excitation, then not only have we another form of displacement sensor, we also have one which modulates an unbroken beam of light. Such microbending transducers can be adapted to measure many different variables, but they are obviously ideally suited to the measurement of pressure. They have been used in microphones, since acoustic signals produce pressure changes, in flow meters (measuring turbulence) and in various other vibrational measuring devices.

Circuits!

The purpose of this section is simply to present a few tested emitter/detector circuits as a guide to further experimentation. Design usually revolves around input sensitivity and speed of serial transmission; however, various other factors such as analogue linearity, fitting, etc., do creep in.

The first circuit, Fig. 11, is one of the most useful since

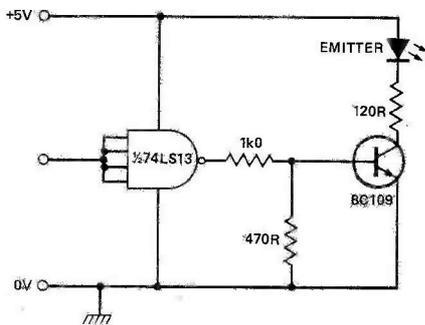


Fig. 11 (above) TTL compatible link.


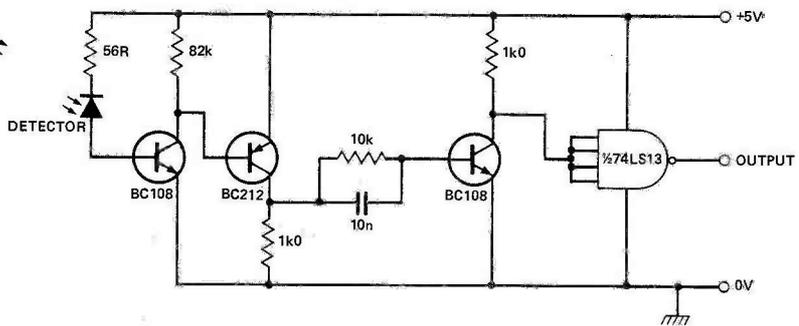


Fig. 12 (below) RS232 replacement link.

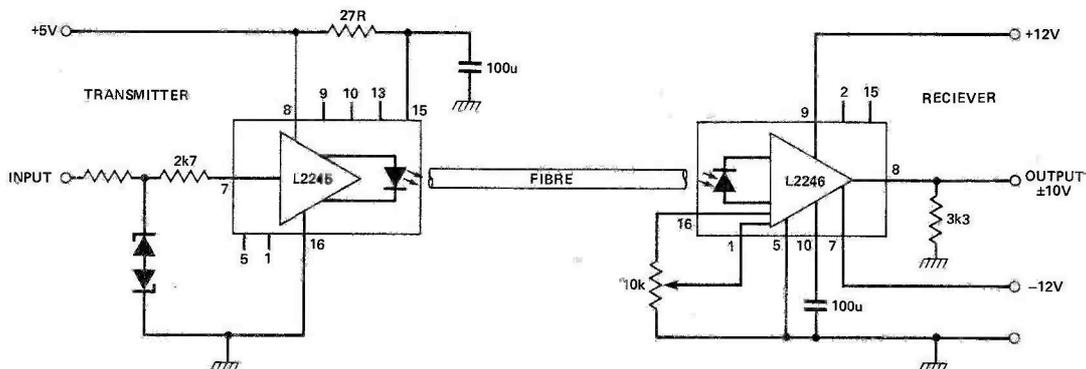

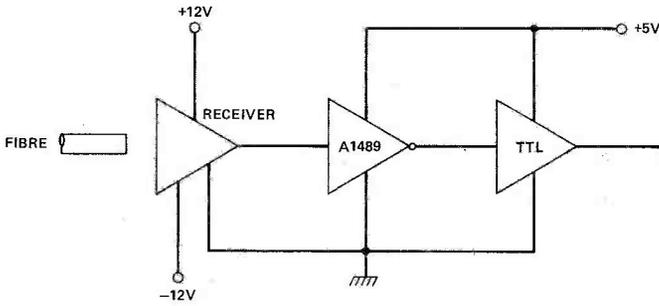


Fig. 13 TTL receiver

it provides a medium-distance TTL-compatible link. Using standard polymer cable this circuit can transmit up to 200K bit/s over a distance of 10m.

Figure 12 is a standard transmission line, the RS232. Belling-Lee produce a pair of transmitter/receiver modules designed to directly replace RS232 links. The use of fibres then eliminates all the noise problems, twisted pairs and emitting loops. The modules are made for PCB mounting with screw-on connectors. Primarily they are intended for glass fibres but any type can be used. They provide viable computer/VDU links up to 200m.

The circuit of Fig. 12 can be modified to become a TTL or CMOS transmission system simply by shorting the 2k7 input resistor of the transmitter and modifying the receiver as shown in Fig. 13. The A1489 linear receiver acts as a current buffer and thus provides the RS232 to TTL interface.

Figure 14 is an audio frequency fibre optic transmitter. It is simply an inverting amplifier with a gain of about -60 which drives the emitter via an NPN transistor. The preset, RV1, should be set to give 0V at the collector of Q1.

If power consumption is a problem with transmitters then a series-driven emitter circuit is required (Fig. 15a). This configuration is TTL compatible, gives easy digital control, and high brightness. The driving current in the LED is given by

$$I_f = (V_{cc} - V_f - V_{ol})/R1$$

where V_{cc} = supply voltage

V_f = ON voltage of LED

V_{ol} = low voltage of the open-collector output

If the current step is so high that supply line modulation is occurring, a shunt driven emitter can be used (Fig. 15b). The power consumption is greater than a series circuit but the current step is reduced. The drive current is given by

$$I_f = (V_{cc} - V_f)/R1$$

Receiver design depends on which parameter you want to measure, and whether it is digital or analogue. However, the final signal processing is up to you.

Figure 16 is an audio frequency receiver compatible with the transmitter of Fig. 14. In its base form it is a simple one transistor amplifier driven by a photodiode. Obviously there are many variations on this simple theme: DC/AC amplifiers, A/D convertors, logarithmic or linear, etc.

Finally, for the keen and wealthy, there are several optical communication receiver hybrid circuits available. These provide most of the reception functions on chip, the user being able to control the sensitivity and operating speed. One such chip is the LH0082. This requires only a photodiode and a stable power supply for its basic preparation (Fig. 17a). Add a few minor components and the device can function over a range of 3 nW input sensitivity (@ 100 Kbit/s) to 300 nW input sensitivity (@ 15 Mbit/s). Additionally it can operate in an analogue mode (Fig. 17b).

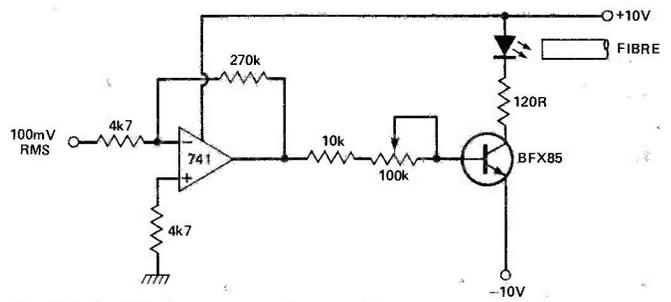


Fig. 14 Audio frequency transmitter.

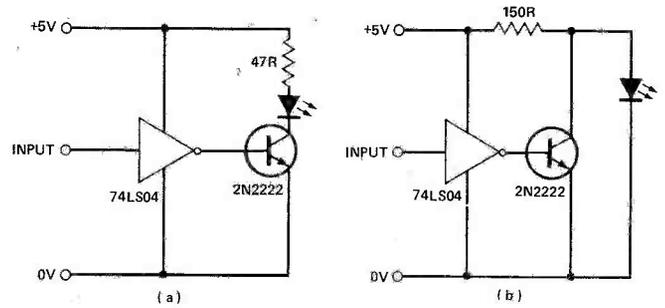


Fig. 15 Series and shunt driven transmitters.



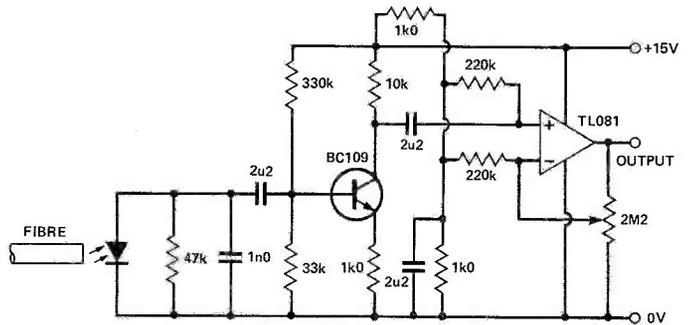


Fig. 16 Audio frequency receiver.

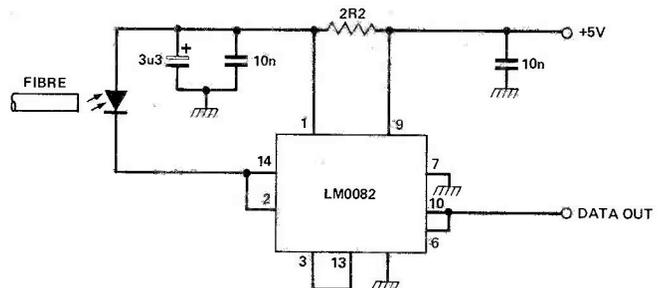

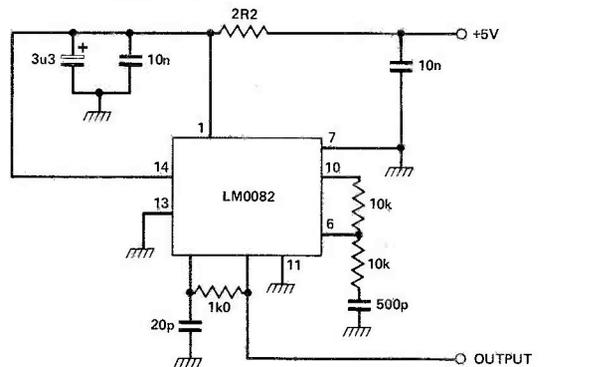(a) BASIC CONFIGURATION, 30nW, 650 kbit/s





(b) ANALOGUE CONFIGURATION, 50mV/uW

Fig. 17 Optical communication receiver.


Hopefully these circuits will provide a useful springboard for many projects, as well as making a relatively new technology accessible to the masses! **ETI**

GET BIG POWER

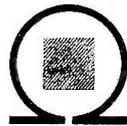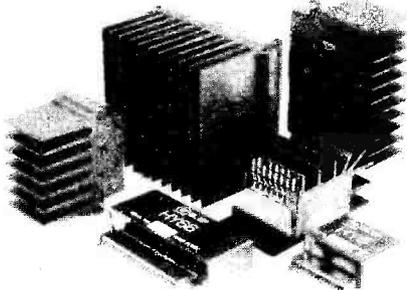

Modular Amplifiers the third generation

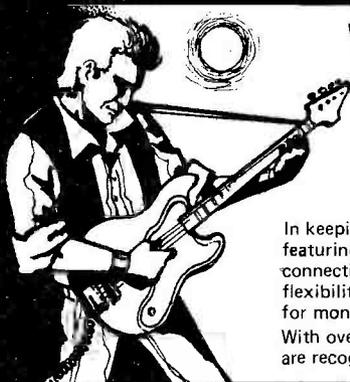Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ μ s. Risettime: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY124	£17.07
PSU 53X	2 x MOS128	£17.86
PSU 54X	1 x HY248	£17.86
PSU 55X	1 x MOS248	£19.52
PSU 71X	2 x HY244	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms

Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

ILP Electronics Ltd., Dept 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone: (0227) 54778 Technical (0227) 64723. Telex: 965780.

THEATRE & BAND LIGHTING

12 x 1K LESS THAN £200!

The days of hiring your electronics are over. You know we manufacture a range of power packs, desks, lanterns, stands, etc. NOW WE ARE PLEASED TO INTRODUCE THE APD SERIES OF MODULAR DIMMERS. Incorporating technology that allows the control of Inductive as well as resistive loads, you build a system exact to your requirements, and save a fortune in process. So where is the sense in hiring????

Contact our sales for free info:

The Sales Manager
MJL SYSTEMS LTD
 45 Wortley Road
 W. Croydon CR0 3EB
 Surrey, U.K.

Tel: 01-689 4138
 (Mon-Fri 9-5pm)

SUPERKITS! FOR BETTER MUSIC & EFFECTS

SETS INCL PCB'S, ELECTRONIC PARTS, INSTRUCTIONS, BOXES, WIRE, SOLDER. BATTERIES NOT INCL, BUT MOST WILL RUN FROM 9V TO 15V DC SUPPLIES. FULLER DETAILS IN LIST

CHORUS UNIT: A solo voice of instrument sounds like more	KIT162	£28.60
COMPRESSOR: Limits & levels maximum signal strength	KIT133	£12.38
ECHO UNIT: With double tracking	KIT168	£38.10
FREQUENCY DOUBLER: Raises guitar frequency by 1 octave	KIT98	£9.34
FREQUENCY CHANGER & WAVEFORM MODIFIER: Tunable unit	KIT172	£29.66
FLANGER: Fascinating effects plus phasing	KIT153	£18.73
FUZZ: Smooth distortion whilst keeping natural attack & decay	KIT91	£9.28
GUITAR EFFECTS: Multiple variation of level & filter modulation	KIT42	£13.54
GUITAR OVERDRIVE: Fuzz plus variable filter quality	KIT56	£17.53
GUITAR SUSTAIN: Extends effective note duration	KIT75	£9.36
JABBROVOX: Voice disguiser with reverb & tremolo	KIT150	£19.68
MAD-ROJ: Variable sirens, incl police, galaxy, machine guns	KIT146	£8.23
METRONOME: With audible & visual beat & down-beat marking	KIT143	£11.28
MICROPHONE PRE-AMP: with bass & treble switching	KIT144	£7.06
NOISE LIMITER: reduces tape & system hiss	KIT145	£8.33
PHASER: with automatic & manual depth & rate controls	KIT164	£17.56
REVERB: with variable delay & depth controls	KIT122	£16.86
RHYTHM GENERATOR: 15 switchable rhythms	KIT170	£32.40
RING MODULATOR: with integral oscillator control	KIT179	£13.83
ROBOVOX: versatile robot type voice modifier	KIT165	£18.16
ROGER 2-GONG: 2 gongs sounded at end of transmission	KIT126	£10.04
SCRAMBLER: Codes & decodes transmissions authorised chans	KIT117	£18.09
SPEECH PROCESSOR: for clearer transmission	KIT110	£9.65
STORM EFFECTS: Automatic & manual, wind, rain, surf	KIT154	£13.66
TREMOLO: deep tremolo with depth & rate control	KIT136	£8.44
VOCODAVOX: modular vocoder	KIT152	£59.09
VODALEK: Robot type voice modulator	KIT155	£10.21
VOICE-OP-SWITCH: with variable sensitivity & delay	KIT123	£13.80
WAH-WAH: with auto-trigger, manual & oscillator control	KIT140	£14.18

MANY OTHER GREAT KITS IN CATALOGUE such as Autowah, bass boost, call sign comparator, frequency generator, Funky-wobulol, harmonica, hum-cut, mixers, sequencers, synthesiser interface, treble boost, tone control, vibrato, voice filter, voice operated fader, Wheeby-jeebly, wobble-wah. Plus digital synthesiser, junior synthesiser, envelope shapes, D-A converter, multiwaveform VCO, Keyboards, contacts, etc. Send S.A.E. for comprehensive catalogue (overseas send £1).

Add £1 P&P & 15% VAT to all orders. (Overseas post details stated in ct). Payment CWO, Chq. P.O. Access. Barclay, or pre-arranged collection. Despatch usually 10-14 days. Details correct at press, E&OE.

PHONOSONICS MAIL ORDER

Dept ET3N, 8 Finucane Drive, Orpington, Kent BR5 4ED
 Tel: Orpington (STD 0689) 37821. Mon-Fri 10.5.

Callers by appointment

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

FAST LIGHT PEN

If you want to use your computer for some real work instead of all these silly games, a light pen can be a useful tool. Design by Martin Postranecky.

This circuit will enable you to build a light pen for use with most home computers, but at a fraction of the price of any commercial unit with comparable performance. Apart from cost, the circuit's main advantages are the very high response speed and the compatibility with a large range of TV or monitor brightness and contrast settings.

Going Soft

In order to construct a light-pen system, both software and hardware are needed. This article covers the hardware in some detail, but, apart from giving some hints, leaves the construction of the software largely up to the reader. However, we do hope to be able to give software details in a future issue (no promises, though, so there's no excuse for laziness on your part).

Generally, computers have a dedicated area of RAM that contains the information for the TV display. Words of data are read sequentially, each word being enough information to determine the brightness and colour of an area of screen known as a pixel. The size of the pixel — the number of lines it extends across and how far it extends along them — depends on the computer, but the pixel will be refreshed at a standard rate, every 40 mS in the UK system of two fields of $312\frac{1}{2}$ lines in 20 mS.


When the electron beam "hits" the pixel at which the light pen is pointing the sudden change in phosphor brightness will trigger the light pen circuit. The resultant TTL output pulse can then be used to generate an interrupt which will identify the display file pointer position for that pixel. Your software should then either vary the content of that particular display element or

generate an offset vector to move the element to follow (TRACK) the light pen.

Light Hardware

Obviously the response of the light pen must be very fast to enable you to capture the required element. With the photodiode used in this design, the TTL pulse is generated in under 300 nS; if an even faster response is required try a silicon PIN photodiode, eg BPX-65.

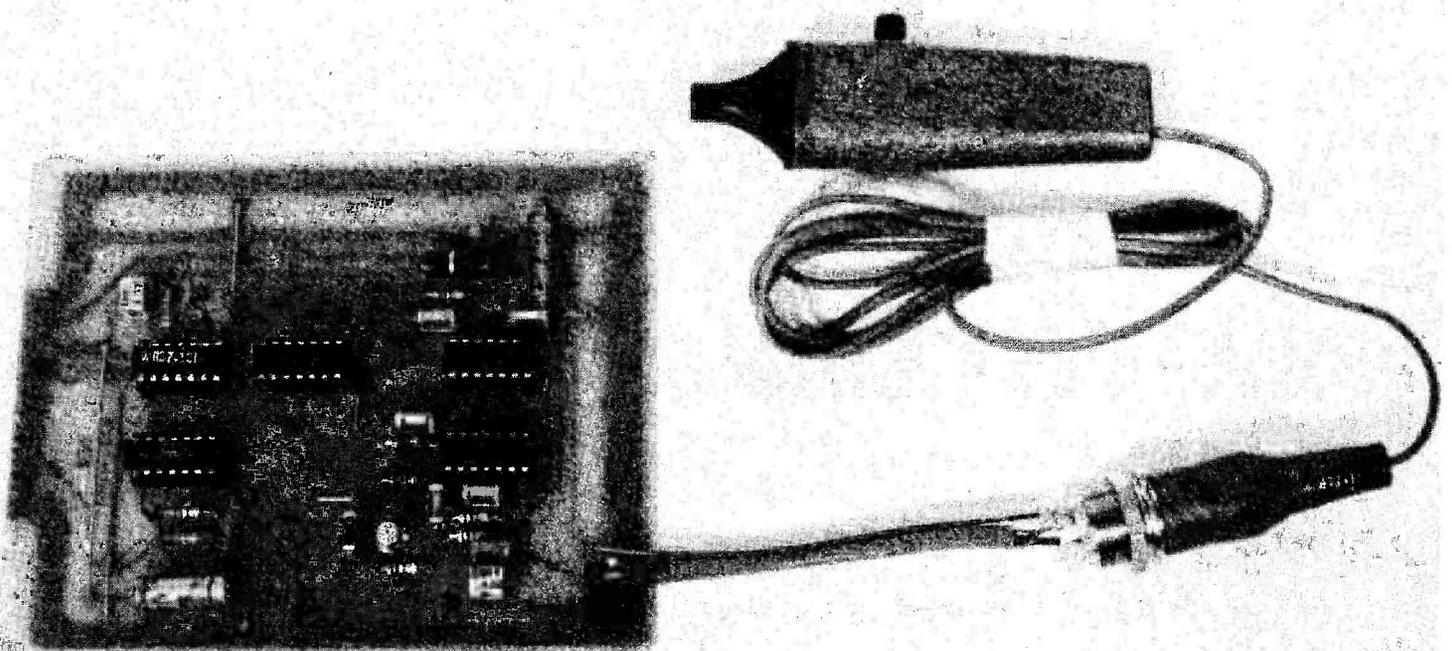The circuit is very easy to build using the PCB layout provided. The only difficult part is the negative supply line, -7.0 V at about 30mA (the Video Amplifier will probably catch fire above ± 8 V and the comparator will not work with less than -6 V!). But as most computers provide -7 V, -12 V or -15 V line, the simple BZY88 (6V8) Zener regulator should be satisfactory provided the correct



The ETI version of the light pen — unlike the author, we used the body of a highlight pen so that we could fit in the optional switch.

value for the series resistor, R11, is used, as given by Table 1.

The MIXED SYNC line is normally available at the TTL level in any computer somewhere on the video mixer board — most likely as an output of a ZNA134J or an equivalent IC. If all else fails try the cheap and simple circuit shown in Fig. 3 using the VIDEO OUTPUT line of your computer.

Body Building

To form the lightpen body, I used the barrel of a cheap ball-point pen with the photodiode push-fitted in the "sharp" end behind the 1mm 'hole'. But any ball-point / fountain / felt-tip pen / cigar tube / etc would be just as effective — use your imagination! Two points to remember — it is much easier to use a pen barrel

where the tip separates or unscrews from the body so that you don't have to work in a 4" long tube. And make sure that the photosensitive element "sees" only a single TV line width. This depends on the size and resolution of the CRT but the aperture in front of the photodiode should not exceed 1 mm diameter. If you like weight-lifting you could even use one of those large 12-colour ball-point pens and build the whole circuit into the body of the pen (though you'll have to re-design the PCB!)

Two suggestions you might like to use are:

- you could mount the main PCB inside your computer case, and connect the pen to the circuit board using a three-pin DIN plug and socket;

HOW IT WORKS

Light falling on the reverse-biased photodiode PD1 increases the leakage current through the diode and R1. The resultant voltage change is AC coupled to the emitter follower Q1 and appears across its emitter load R4. Signal amplification is further provided by the variable-gain Video Amplifier IC1. The SET GAIN potentiometer PR1 is connected between the high gain select pins 4 and 11 and allows the voltage gain to be set between about 50 and 200.

Any small change in the amplifier output (about 10 mV) is detected by the analog voltage comparator, IC2 and appears as a negative-going TTL pulse at the output pin 11. This pulse is inverted by IC3a and clocks out the two complementary output lines LPOUT (Q1, pin 5) and LPOUT (Q1, pin 6) of the dual flip-flop, IC4 with its DATA 1 (pin 2) tied high via R8.

The low-going edge of LPOUT also triggers the monostable IC5. After the preset time period — variable by the SET PULSE LENGTH potentiometer PR2 — the high-going edge of the IC5 output Q

(pin 1) clocks-out the low-going output Q2 (pin 8) of the flip-flop IC4 (DATA 2, pin 12, is again tied high via R7). After passing through gate IC3b and inverter IC3c, this pulse sets the CLEAR 1 (pin 1) of IC4 low and thus clears the flip-flop IC4 outputs, LPOUT and LPOUT. The CLEAR 1 will remain low (and so prevent any further triggering of IC4) until the CLEAR 2 (pin 13) is brought low by the next Line Sync pulse of the MIXED SYNC line. This system ensures that only one pulse in any TV scan line is passed to the computer and prevents any spurious triggering caused by the CRT flyback or sync pulses.

The STROBE (pin 13) of IC2 is normally held high by R2. If the optional switch SW1 is used in the LIGHT PEN body the STROBE will normally be low, inhibiting the IC2 output. The operation of the push-to-break switch SW1 allows the STROBE line to swing high enabling the IC2 output. Capacitor C4 removes the worst of the switch bounce from the STROBE line.

BUYLINES

No problems with the components here — NE529A and NE592A are offered by a number of suppliers advertising in this magazine, and the photodiode PD1 (RS Components Stock No. 305-462 used in the prototype) can be any fast response/visible light silicon diode in TO18 can. The PCB is available through our PCB service.

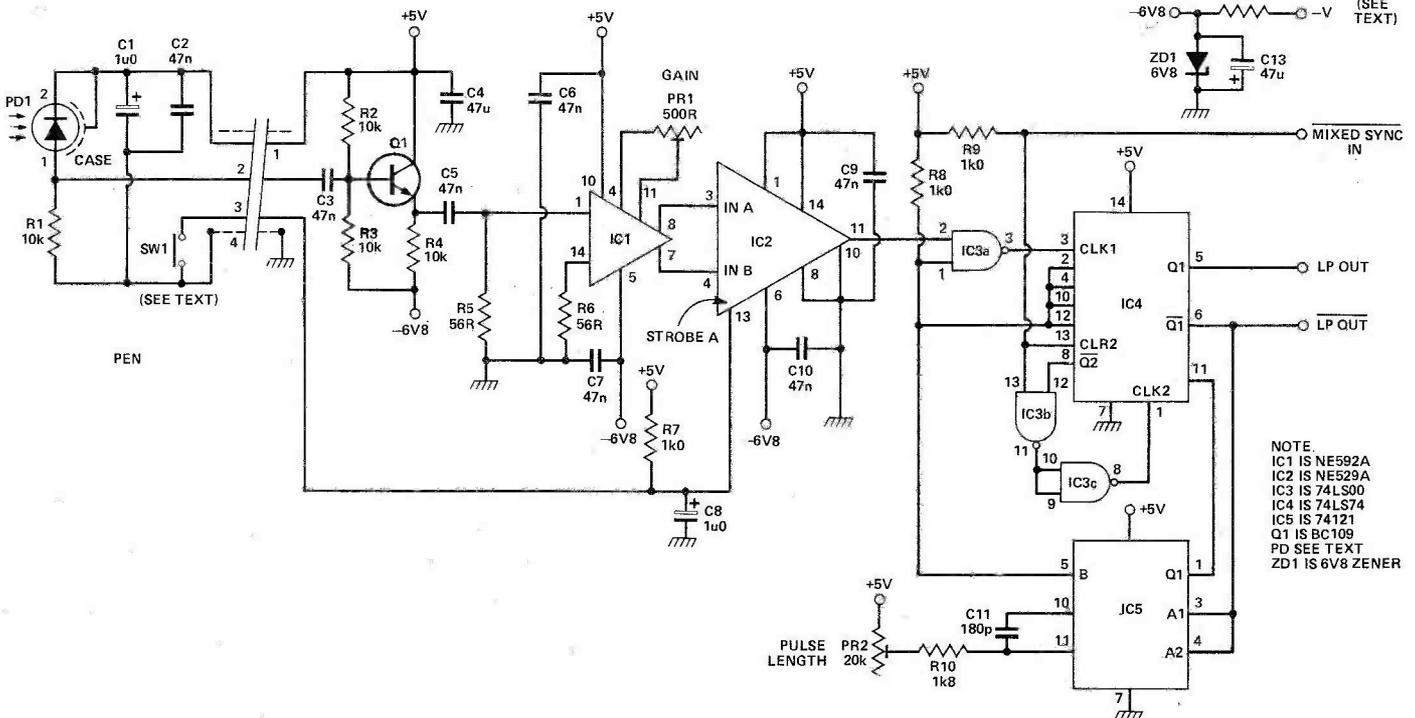


Fig. 1 Circuit diagram of the light pen.

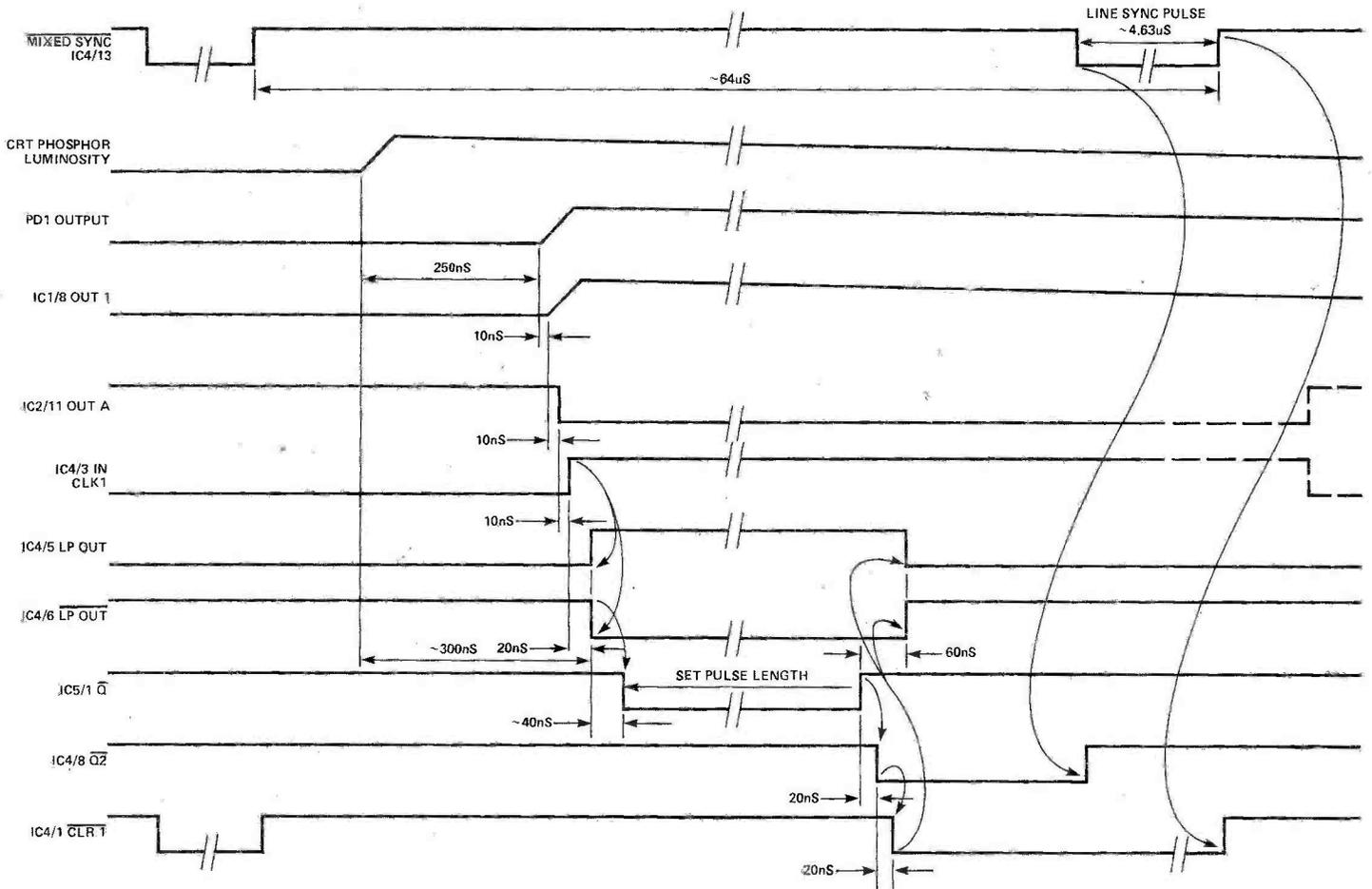


Fig. 2 Timing diagram of the light pen.

● if the size of the light pen body permits, you might find it useful to mount a small push-to-make switch on it (SW1) connected between the ground (shield) and the third wire. You can use SW1 as a push-to-write switch.

Setting Up

Construction of the main PCB should pose no problems. Please make sure that all the ICs are the right way round — they don't all fit the same way! Don't forget to insert all

five links as shown on the PCB overlay and re-check the polarity of the zener ZD1 and the electrolytic capacitors. (If you think all this is superfluous, you don't know your Murphy's law).

Use an oscilloscope or a logic probe to look at the output of IC4 pin 5. Point the light pen at the TV screen with the brightness and contrast setting fully down (ie, dark) and adjust the GAIN present potentiometer PR1 so that the line stays low.

Then set both brightness and contrast back to the usual level and

point the light pen at some white display element. Slowly increase PR1 until a single pulse appears on the TTL output line. Because the light pen could cover two or more scan lines depending on the CRT size, you may get two or three pulses repeated at $64 \mu\text{S}$ interval. You should be able to reduce the gain with PR1 and/or TV brightness control sufficiently to obtain just a single pulse.

Finally set the required pulse duration by the PULSE LENGTH potentiometer, PR2 (adjustable between about 200 nS and $2 \mu\text{S}$).

All that remains now is to sit down and write your software to actually use the light pen. What about a (computer) game of battleships . . . ?


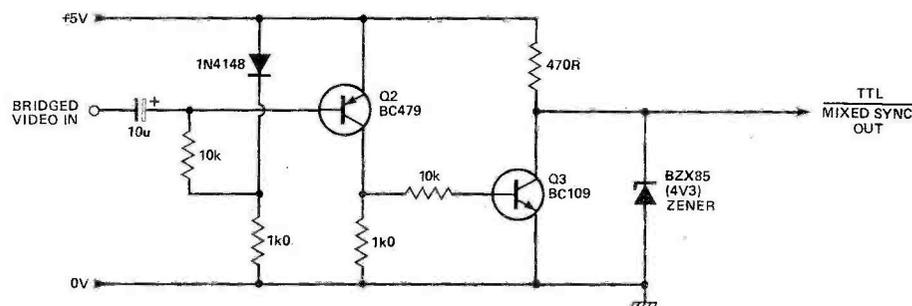


Fig. 3 Circuit to recover the MIXED SYNC pulse from the composite video.

SUPPLY VOLTS	R11 VALUE
-7	10R/1W
-12	120R/1W
-15	220R/1W

Table 1 Values of R11 for various negative host computer supply voltages.

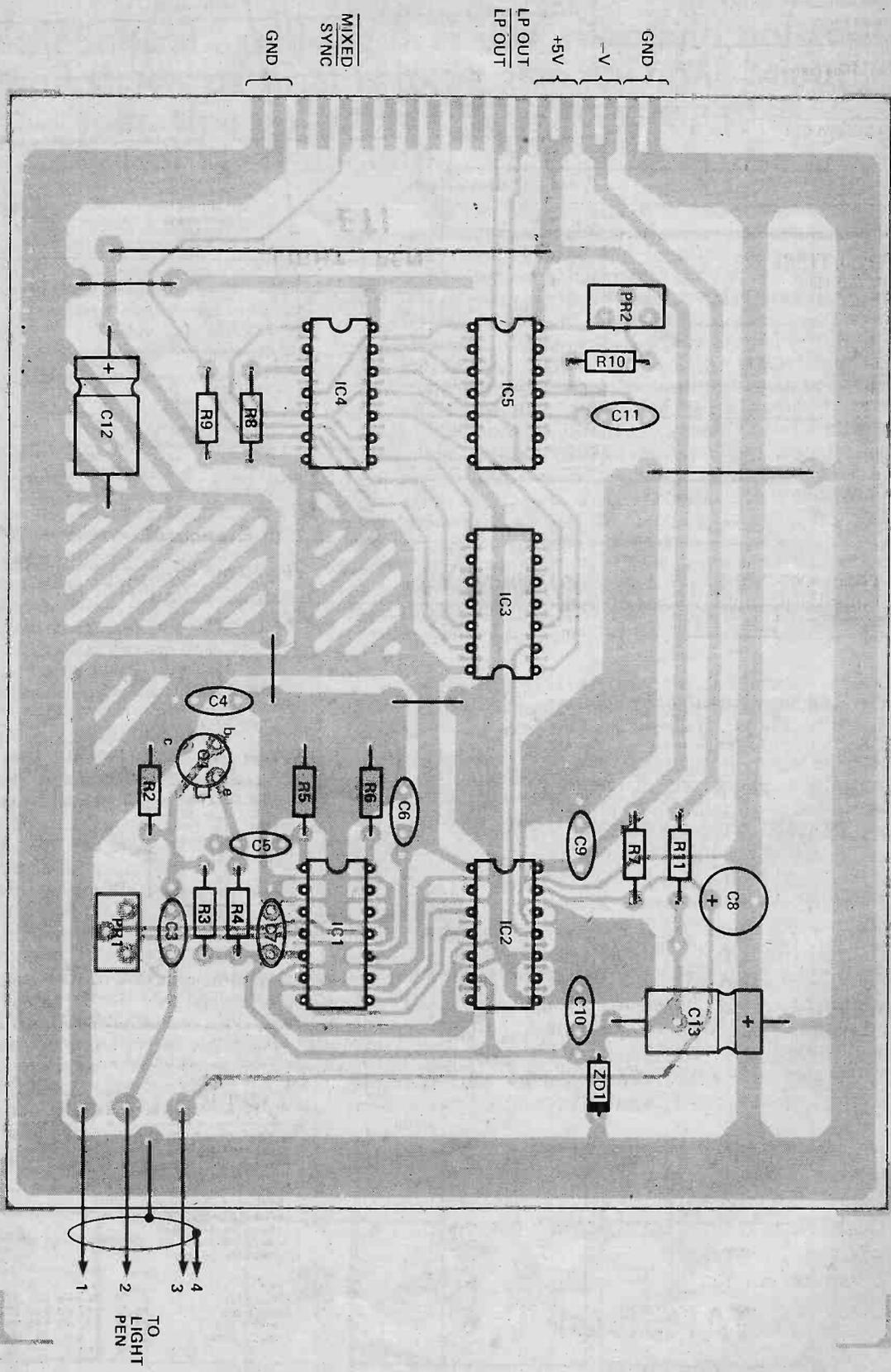

PARTS LIST

RESISTORS (all 1/4W 5% unless stated)

R1, 2, 3	10k
R4, 7, 8, 9	1k0
R5, 6	56R
R10	1k8
R11	See Table 1
PR1	500R lin preset
PR2	20k lin preset

CAPACITORS

C1, 8	1u0 10V tant
C2-7, 9, 10	47n polyester
C11	180p ceramic
C12, 13	47u 10V tubular electrolytic

SEMICONDUCTORS

IC1	NE592A	PD1
IC2	NE529A	
IC3	74LS00	
IC4	74LS74	
IC5	74121	ZD1
Q1	BC109	

MISCELLANEOUS

High-speed visible light photodiode in TO18 can — see text
 BZX85 (6V8) 1W zener diode

MISCELLANEOUS

PCB: three-core plus shield cable (or two core without SW1); light pen body — see text; SW1; miniature push-to-make switch (optional); three-pin DIN plug and socket (optional).

E.T.I. KITS

Full Kits inc. PCBs, hardware, electronics, cases (unless stated), Less batteries.
Project reprints 45p extra. Separately 45p + p&p

BALANCED INPUT PREAMP May 83 no case	£10.99
COMPRESSOR/LIMITER May 83 no case	£19.43
MAX/MIN THERMOMETER Apr 83	£43.78
DUAL LOGIC PROBE Sept 83	£14.99
ALARM MODULE Mar 83	£24.87
DUAL LOGIC PROBE Sept 82	£14.99
AUTO VOLUME CONTROL Sept 82 £4.28 less case	
INSULATION TESTER May 82	£17.87
HIGH QUALITY PHONE AMPLIFIER Feb 82	£19.75
MOVING COIL STAGE less case	£19.99
PEST CONTROL Feb 82	£7.45

MAGENTA ELECTRONICS LTD
ET7, 135 Hunter St, Burton-on-Trent
Staffs., DE14 2ST. Mail Order Only
(0283) 65435
Add 50p p&p to all orders. Prices include VAT. Access & Vias phone/post

GUITAR TUNER Jan 82	£31.87
COMPONENT TESTER Dec 81	£8.78
CAR ALARM Nov 81	£19.77
SOUND BENDER Oct 81	£22.84
WATCHDOG SECURITY ALARM Aug 81	£47.98
RECHARGEABLE BATTERY extra	£21.37
HANDCLAP SYNTHESIZER Aug 81	£32.98
WAH PHASE June 81. Less pedal	£14.78
LED JEWELLERY June 81. Cross	£2.98
Star £9.01 Spiral £7.98	
GUITAR NOTE EXPANDER April 81	£17.98
DRUM MACHINE April 81	£85.37
ENGINEERS STETHOSCOPE Mar 81	£20.98
SOUND PRESSURE LEVEL METER Feb 81	£43.98
INFRARED ALARM Feb 81	£59.98
4 INPUT MIXER Dec 80	£21.74
MUSICAL DOORBELL Dec 80	£12.77
METRONOME Nov 80	£8.58
ULTRASONIC BURGLAR ALARM Aug 80	£29.80
CAPACITANCE METER Aug 80	£22.28
CROSS LOGIC TESTER Aug 80	£11.98
CLICK ELIMINATOR April 79 £87.70 Or less case	£49.98

Official school orders welcome.
OVERSEAS: Payment must be in sterling.
IRISH REPUBLIC + BFPO — UK PRICES.
EUROPE: UK PRICES + 10%
ELSEWHERE: WRITE FOR QUOTE.

MULTIMETERS

(UK C/P 65p)	
RANGE DOUBLER 10A DC1	
Special price.....	£15.95
ETC 5000/5001 121 Ranges	
50K/V Range Doubler 10A DC	
.....	£16.50
TMK 500 23 Ranges 30K/V 12A	
DC Plus cont. buzzer.....	£23.95
NH56R 20K/V 22 Range Pocket	
.....	£10.95
360TR 23 Range 100K/V. Large	
scale 10A AC/DC plus Hfe.....	£36.95
ATI 020 18 Range 20K/V. DeLuxe	
plus Hfe Tester.....	£17.50
ST303TR 21 Range 20K/V plus Hfe	
Tester.....	£16.95

SPEAKERS

(Hi-Fi, P.A., Disco, Bass Guitar)

8" 60W...	£11.95
10" 50W...	£12.95
12" 100W...	£26.95
18" 100W...	£39.95

MOTOROLA PIEZO TWEETERS IN STOCK
RETAIL • MAIL ORDER
EXPORT • INDUSTRIAL
EDUCATIONAL

Order by Post with cheques, Access/Visa or you can telephone your orders.

ALL PRICES INCLUDE VAT	FREE CATALOGUE SEND LARGE SAE (UK 20p)
------------------------	--

MUSICRAFT 303 EDGWARE RD, LONDON W.2. TEL: 01-402 9729/2898

SILVER-REED

PRINTER/TYPEWRITER

AS FEATURED ON LAST MONTH'S FRONT COVER

R.R.P. £339.25
EX42 SPECIAL PRICE £245.00

JUST LOOK WHAT YOU GET!

1. Latest technology daisywheel printer
2. High quality keyboard
3. Interface option to most micros
4. Automatic correction (16 characters)
5. Post, packing & insurance free
6. Other quality features

We also supply other Silver Reed models.
Phone for details of our interface.
Cash refund if returned undamaged within 14 days.
Cheques/POs to

TAPESOFT

01-892-1909
55 Morley Road, Twickenham, TW1 2HG.

Interak 1

BUILD YOUR OWN COMPUTER

Where have all the constructors gone? All the people who some years ago would have been building their own low distortion amplifiers, their own synthesizers, speaker cabinets, digital alarm clocks and so on?

From our experience they're still here — what they're building now is the "Interak" computer. The trouble is, a supplier like us of the necessary materials is in dreadful competition in the "consumer" home computer market — flooded with companies backed by millions of pounds of venture capital, and all seemingly hell-bent on boom or bust, so we have to make do with "low profile" adverts like this to spread the word.

The excitement of computers now goes on in the board-room wranglings and wheelings and dealings, and mostly there's no excitement or sense of participation left for the poor old user, who is simply used as a pawn in the power game. Several years ago things were different: the only computers in ordinary hands were ones which were painstakingly built by the individual constructor — often with chips costing fifty pounds a time, which had to be ordered specially from the USA. When you had built a computer like that, you had something you could be proud of! There was more pleasure in building your own computer than buying any number of today's "plastic" computers. And as a bonus you had the benefit of gaining riches beyond price — the know-how — the ability to understand what really goes on inside, almost to be able to see the electrons flowing down the wires and through the chips!

Those days are not quite gone: you can still build your own rack and card computer — Interak!
Example prices (excluding VAT): 4 MHz Z80A CPU card £10.95, Manual £1.50, Main Parts £13.41 (everything is available separately, and full after sales service in case you make a mistake).
40 type-written pages of description, specification, price lists etc. are yours for the asking (a 20p stamp and/or SAE is a help, but not essential, or telephone if you prefer).

Greenbank

Greenbank Electronics (Dept. T11E), 92 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391

PARNDON ELECTRONICS LTD.

Dept. 23, 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance
Bandoliered and colour coded. Full Range 1R0-10M.
£1.00 per hundred mixed (Min 10 per value) £8.50 per thousand mixed (Min 50 per value)
Special stock pack 60 values, 10 of each £5.50

RECTIFIERS 1 Amp 3 Amp 50V 3p 14p 100V 4p 14p 200V 5p 14p 400V 6p 19p 600V 8p 29p 1000V 9p 25p	3½ Digit LCD Display: 1 colon, 3 decimal points plus/minus sign and lo bat indicator. Complete with low power 7106 A/D converter display driver. Driver set £8.95 Display £3.50 Driver £6.50
DIODES: IN4148 £1.60 per hundred	

DIL SOCKETS 8 pin — 10p. 14 pin — 11p. 16 pin — 12p. 18 pin — 19p. 20 pin — 21p. 22 pin — 23p. 24 pin — 25p. 28 pin — 27p. 40 pin — 42p.

Full List Available — SEND SAE
ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE
Same Day Despatch

OPTICAL FIBRES

FOR COMMUNICATIONS AND LIGHTING

- ★ Silica fibre PTFE coated, 25 dB/km 0.05mm² active area. Xmits near UV
- ★ Glass fibre urethane coat, 60dB/km 0.03mm² active area. Xmits near IR
- ★ Acrylic fibre, 0.75mm² active area 800dB/km. Xmits visible light only
- ★ Glass Bundle, PVC sheath, 400dB/km 1.0mm² active area, 440 fibres
- ★ Acrylic Bundle, sheathed, 800dB/km 0.78mm² active area, 16 fibres

Type	Length in Metres	
Silica Fibre	10 25 50	£6.26 £14.88 £27.57
Glass Fibre		£5.20 £12.40 £23.23
Acrylic Fibre		£3.03 £6.90 £13.55
Glass Bundle		£3.80 £8.75 £17.09
Acrylic Bundle		£8.10 £19.33 £37.07

SAMPLE PACK: contains six metres of Acrylic fibre plus one metre samples of the other fibres. In the Pack is a booklet that contains circuit diagrams, drawings, and practical tips. Its forty pages give details of fibre theory, manufacture, properties, and many uses. Send £5.45 + 50p P&P.

MARE'S TAIL: A ferruled bundle of 5000 glass fibres that spread out into a 22" diameter dome shape. For use in a fibre optics lamp. Send £11.50 inclusive.

QUANTUM JUMP LIMITED
Dept ET1, 98 Queens Drive, Liverpool L18 1JN.

Add 50p postage on orders under £10. Don't add VAT. Mail order only.

READ/WRITE

Component Supplies

Dear ETI,

Your IC Update feature is most interesting, not least for your introductory remark about neither IC being actually available to the hobbyist.

It encapsulates something I've long been feeling — that the home constructor/hobbyist/amateur etc is often regarded as a convenient disposal route for the obsolete, substandard and just plain trashy.

Maybe I'm in a minority, my electronics interests being focused on audio with aspirations to the building of equipment with the sonic qualities of Mark Levinson, Threshold, etc. It's a continual pain to deal with suppliers who can't even deliver what they advertise (and what they advertise often lags far behind industrially-available components).

I'd have thought that there was scope for someone, somewhere to get on a platform as a purveyor of genuine quality up-to-date goods as an alternative to the present system of 'bargain packs' and 'just as good only cheaper' (it's never as good and always costs you more to put right in the long run). Not that I condemn the cheapos entirely, many of us started there — but to what extent are we stuck there for the want of an alternative and for the want of a bit of imaginative energy?

Yours
Dick Bowman
London E17

We're very glad that at least one reader concurs with our remarks. We have, ourselves, access to 'professional' sources for components, and frequently we are unable to specify components that we'd like to because they are not available on the hobby market. So what do we do — do we leave out the devices in question, as we've done so far, or do we use them and hope that we can persuade someone, somewhere to sell them to readers?

To a great extent, what actually makes its way on to the hobby market depends on manufacturers' pricing policies — if the 100 (or even 1000) off prices are punitive,

none of the advertisers in our magazine will stock bits because no one will buy them. And can you blame them?

We've spent quite a lot of effort trying to get manufacturers to recognise that the hobbyist market is important. It is very frustrating indeed to speak to an engineer who started out as a hobbyist (admittedly, probably before going on to do a formal qualification in electronics) who still doesn't recognise that we're important. It's also surprising how little it is recognised that ETI and (to be generous to the opposition for once!) other hobbyist magazines are widely read by professional engineers.

ZX81 Tape Mod

Dear Sir,

On page 61 of the February issue you publish an article by Mr Ian Ridout concerning modifications to facilitate recording programs from the ZX81 on to cassette. Talk about a sledgehammer to crack a nut!

A year or so ago I did modify my son's ZX81 — and then quite a few of his friends' got done — to increase the write signal to cassette. Inspection of the Sinclair circuitry had revealed, as Mr Ridout states, that only about 1 millivolt RMS of signal emerged from the '81' at the cassette port, after the double 47 μ S filter. Changing Sinclair components R29/C12 to 330K and 150pF worked with some 20 different machines, from metered hi-fi decks to auto-levelled portables. This, of course, tripled the signal to the cassette. 220K/220 PF combinations were also acceptable, giving a fivefold increase approx.

To use an FET as a buffer is a substantial overkill — needless when even a loading of, say, 10k/4n7 would be acceptable to the machine and give over 100 mV of signal, RMS. It is far more likely to create difficulties with the circuit published in your magazine owing to the very high signal level, than the easy and modest change of 1 resistor and 1 capacitor.

Yours sincerely,
P. A. Duvall
Theydon Bois

We don't accept that using one transistor is comparable to using a sledgehammer! Certainly, if we'd managed to fit in a couple of ICs, perhaps a dedicated micro to handle the tape signals . . . then that criticism really would be in order. As to difficulties with high signal levels, we've had none reported as yet — and, in any case, it's always far easier to get rid of excessive levels than it is to boost inadequate ones.

Fuel Economy

Dear Sir,

Your comments on the Hyonomiser suggested that readers might be interested in the possible advantages of electronic mpg devices. Mine is a Mobelex Maximiser, giving an instantaneous readout in mpg, and a record of fuel used, to tenths of a gallon. My car is a 1972 Datsun Bluebird (1600cc) which, until a replacement carburettor was fitted a few years ago gave exceptionally economical consumption. I had always suspected that I had been lucky, and when the consumption on a run increased from the early 40s to the late 30s I fitted the meter to check up on the situation.

I had hoped that the meter might indicate places on the performance curve where the carburettor was delivering an economical mixture, and this proved to be the case. Observing the meter readings at steady speeds showed that just above 50mph gave a noticeably low reading. This was a rather lower cruising speed than the one I had found by trial and error to be economical with the previous carburettor, but checks on mileage and fuel put in (which agreed very closely indeed with the meter readings) showed that I could now get an overall consumption very close to 50 mpg, though traffic hold-ups and so on seemed perpetually to conspire to limit me to forty-nine point something and deny the triumphant fifty-plus. Nevertheless, I found the improvement of over ten miles per gallon very satisfying on those unavoidable long runs.

Of course, it is not all joy, and meter watching needs a certain frame of mind, where driving satisfaction comes from saving, rather than the wind in the hair. The meter shows what we all know but prefer not to believe. Hard acceleration can show as little as six or seven mpg, while one

enthusiastic overtaking up hill can more than counteract ten miles of careful driving on the level. Most of the economical methods I already knew, but didn't practise regularly until the meter kept reminding me of my wastefulness. One new — to me — tip is not to let the speed increase as the car breaths a hill. Easing off to keep the speed constant can show startling improvements, which of course follows logically if one considers that if acceleration is costly, acceleration up hill is far worse.

One doesn't need to watch the meter all the time — in fact, once one has explored the performance envelope with it, if you drive by your findings you don't need to use it at all, yet I personally wouldn't be without one in future. On the other hand the ideal meter would differ in some respects from the one I have fitted. When one is using small quantities of petrol the fuel flow transducer appears to give a signal every second or two, and the combination of this data with the more frequent speed signals gives a display that flickers over some 5-10 mpg. It would be easy to be dismissive about the meaningfulness of the display, but in fact the trend of the figures is quite easily followed — indeed, after some degree of use one can begin to read subtleties into the way the display is operating. Nevertheless, some kind of integrating device that would operate over a second or two would make the device easier to interpret, particularly by the impatient or non-technical. Again, reading the tenths against the mileage enables a quick check on mpg attained over the last five miles or fifty miles, or since the beginning of the journey, but it would be pleasant to do this automatically rather than by mental arithmetic.

Incidentally, the best mpg I have ever attained over a distance was coming eastward on the M4 from the service area on the summit level. A strong tail wind enabled me to display (and check on the mileage/consumption figures) over 80 mpg for some thirty miles. Needless to say, awful rush-hour jams at the London exit reduced my overall figure to about fifty . . .

Unfortunately I lack both the time and the expertise to design my own ideal meter, but I feel that I would now be able to offer quite a lot of useful advice to anybody thinking of obtaining or designing one.

I am sure that a device like the Hyconomiser could improve the consumption of any car that, like mine on its new carburettor, was operating slightly rich. However I don't understand the emphasis on the so-called optimum mixture, where the oxygen and hydrocarbons are present in the exact quantities needed for the theoretical reaction. In real life, some of the petrol and some of the oxygen just can't get together, and both petrol and oxygen are wasted. For some forty or fifty years two mixtures have been aimed at:

1. A rich mixture for maximum power with excess fuel, where all the oxygen is burned, but some petrol is wasted.
2. A weak mixture for cruising, with excess air, where all the fuel is burned, but some oxygen passes off unburned (don't forget that four fifths of the gas in the cylinder is nitrogen, that passes out hot but unchanged, so a little excess oxygen is unimportant). Modern carburettors try to operate in these two regimes, and avoid the 'optimum' mixture like the plague. The problem, leaving aside gross failures to atomize, is that no improvement in mixing arrangements can improve the mixing beyond a certain point determined by the mathematics of probability.

This effect was first noticed, to my knowledge, in connection with the Lumiere 'Autochrome' colour photographic plates circa 1910. The system depended on an intimate mixture of red, green and blue fine transparent powders to produce a mosaic screen with many million elements to the square inch. However aggregations of many grains all of the same colour produced objectionable spots on the plates, and it became apparent that more thorough mixing did nothing to alleviate the problem. In the 1920s E. J. Wall showed that the number and size of these clumps of grains was very close to that predicted by probability theory. Even larger clumps of grains should have been present, but plates with these were presumably rejected by visual inspection.

Anyone who hopes to create an ideal mixture without 'lumps' merely by mixing or agitation is, I am afraid, attempting to evade one of the laws of nature.

Yours sincerely
Michael C. Jones
Harrow

We have considered doing a project for a fuel consumption monitoring system, as the electronics involved would be relatively simple and easy to design. However, the problems come in trying to design the fuel volume and the distance travelled transducers.

Tropical Programming

Dear Editor,

I'm having infinite trouble with my Atari Cassette Programmer and wrote to HE wondering if their EPROM project earlier this year (the magazine takes some time to reach me out here!) would be of use. They say not, but suggested contacting you.

I need some way of storing programs and loading them; my 410 program recorder seems to store them but won't load. There are two of us in Fiji with Ataris and both of us have exactly the same problem. My friend got a disc drive, but that's packed up too, so we are driven to lying on the beach, drinking from a coconut and dreaming of programming. Any suggestions welcome.
Rob Patterson
Lelan Memorial School
Fiji

This must be the cruellest letter we've received in a long time — how is it possible for anyone to worry about programming when there's important business like lying on the beach to get on with? There's nowt so queer as folk (well known north of England saying No. 42).

So far as we are aware, the 410 programmer is a reliable piece of equipment and should work. However, it's probably the excess heat that's giving the trouble, by causing the timing components in either the recorder or the interface to change value just enough for the two not to be compatible. Have you tried using the computer and recorder in an air conditioned room? Alternatively, we suggest contacting Atari themselves.

ETI welcomes all its readers (publishable) opinions on the contents of the magazine, and issues related to electronics. Send your letters to The Editor, ETI, 145 Charing Cross Road, London WC2H 0EE.

ETI

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.


Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.

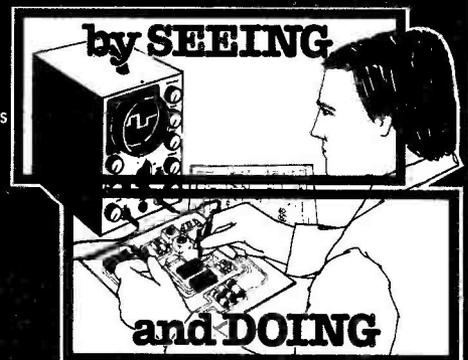

British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

ETI/11/841

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)



British National Radio & Electronics School Reading, Berks. RG1 1BR

ETI PCB SERVICE

The best way to get a really professional finish to your project is to use a professionally made PCB — look no further, here they are!

In order to ensure that you get the correct board, you must quote the reference number when ordering — if you don't, you may get sent the wrong board. The code can also be used to identify the year and month that a particular project was outlined in: the first two numbers are the year, the third is the month and the number after the hyphen indicates the particular project.

Note that these are all the boards that are available — if it isn't listed, we don't have it.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until we receive payment.

- | | | |
|--|---|--|
| <p>1979</p> <p><input type="checkbox"/> E/794-1 Guitar Effects Unit2.64</p> <p><input type="checkbox"/> E/794-2 Click Eliminator6.64</p> <p><input type="checkbox"/> E/796-1 Accented Beat Metronome 3.60</p> <p>1980</p> <p><input type="checkbox"/> E/803-1 Signal Tracer2.27</p> <p><input type="checkbox"/> E/808-1 CMOS Logic Tester2.64</p> <p><input type="checkbox"/> E/808-3 Ultrasound Burglar Alarm</p> <p><input type="checkbox"/>2.87</p> <p><input type="checkbox"/> E/8010-1 Cassette Interface2.93</p> <p><input type="checkbox"/> E/8010-2 Fuzz/Sustain Box3.27</p> <p><input type="checkbox"/> E/8011-5 RIAA Preamp1.93</p> <p><input type="checkbox"/> E/8011-6 Audio Test Oscillator3.13</p> <p><input type="checkbox"/> E/8012-1 Musical Doorbell2.80</p> <p><input type="checkbox"/> E/8012-3 Four Input Mixer2.64</p> <p>1981</p> <p><input type="checkbox"/> E/811-1 LED Tacho4.13</p> <p><input type="checkbox"/> E/811-2 Multi-Option Siren3.20</p> <p><input type="checkbox"/> E/812-1 Universal Timer3.31</p> <p><input type="checkbox"/> E/812-2 IR Alarm (4 boards)6.64</p> <p><input type="checkbox"/> E/812-5 Pulse Generator3.57</p> <p><input type="checkbox"/> E/813-1 Engineer's Stethoscope2.65</p> <p><input type="checkbox"/> E/814-2 Drum Machine (2 boards)</p> <p><input type="checkbox"/>5.60</p> <p><input type="checkbox"/> E/814-4 Guitar Note Expander3.20</p> <p><input type="checkbox"/> E/816-8 Waa-Phase1.53</p> <p><input type="checkbox"/> E/816-9 Alien Attack3.48</p> <p><input type="checkbox"/> E/817-1 System A-Input</p> <p><input type="checkbox"/> (MM or MC)2.65</p> <p><input type="checkbox"/> E/817-2 System A — Preamp5.17</p> <p><input type="checkbox"/> E/817-3 Smart Battery Charger1.97</p> <p><input type="checkbox"/> E/818-3 Hand Clap Synth3.97</p> <p><input type="checkbox"/> E/818-5 Watchdog Home</p> <p><input type="checkbox"/> Security (2 boards)5.31</p> <p><input type="checkbox"/> E/819-1 Mains Audio Link</p> <p><input type="checkbox"/> (3 boards)7.35</p> <p><input type="checkbox"/> E/819-4 Laboratory PSU4.53</p> <p><input type="checkbox"/> E/8110-1 Enlarger Timer3.40</p> <p><input type="checkbox"/> E/8110-2 Sound Bender2.65</p> <p><input type="checkbox"/> E/8111-1 Voice Over Unit3.97</p> <p><input type="checkbox"/> E/8111-2 Car Alarm2.81</p> <p><input type="checkbox"/> E/8111-3 Phone Bell Shifter2.96</p> | <p><input type="checkbox"/> E/8112-1 Alcoholmeter (2 boards) 5.21</p> <p><input type="checkbox"/> E/8112-3 Bodywork Checker1.75</p> <p><input type="checkbox"/> E/8112-4 Component Tester1.49</p> <p>1982</p> <p><input type="checkbox"/> E/821-1 Parking Timer2.20</p> <p><input type="checkbox"/> E/821-3 Guitar Tuner (2 boards) ..5.55</p> <p><input type="checkbox"/> E/822-1 Ripple Monitor1.92</p> <p><input type="checkbox"/> E/822-2 Allez Cat Pest Repeller1.68</p> <p><input type="checkbox"/> E/822-5 Moving Magnet Stage3.49</p> <p><input type="checkbox"/> E/822-6 Moving Coil Stage3.49</p> <p><input type="checkbox"/> E/823-4 Capacitance Meter</p> <p><input type="checkbox"/> (2 boards)10.14</p> <p><input type="checkbox"/> E/824-5 Voltage Monitor1.86</p> <p><input type="checkbox"/> E/825-1 DV Meg2.72</p> <p><input type="checkbox"/> E/825-2 Analogue PWM3.06</p> <p><input type="checkbox"/> E/825-3 Slot Car Controller4.51</p> <p><input type="checkbox"/> E/826-1 Ion Generator</p> <p><input type="checkbox"/> (3 boards)8.00</p> <p><input type="checkbox"/> E/826-4 MOSFET Amp Module6.78</p> <p><input type="checkbox"/> E/826-5 Logic Lock3.06</p> <p><input type="checkbox"/> E/826-6 Digital PWM3.34</p> <p><input type="checkbox"/> E/826-7 Optical Sensor1.74</p> <p><input type="checkbox"/> E/826-9 Oscilloscope</p> <p><input type="checkbox"/> (4 boards)11.60</p> <p><input type="checkbox"/> E/827-7 TV Bargraph Main4.56</p> <p><input type="checkbox"/> E/827-3 TV Bargraph Channel2.28</p> <p><input type="checkbox"/> E/827-4 Hotwire2.63</p> <p><input type="checkbox"/> E/827-5 Bridging Adapter2.38</p> <p><input type="checkbox"/> E/828-1 Playmate (3 boards)7.20</p> <p><input type="checkbox"/> E/828-4 Kitchen Scales1.84</p> <p><input type="checkbox"/> E/828-5 Sound Track4.25</p> <p><input type="checkbox"/> E/829-1 Auto Volume Control1.84</p> <p><input type="checkbox"/> E/829-2 Dual Logic Probe1.93</p> <p><input type="checkbox"/> E/8210-1 Message Panel</p> <p><input type="checkbox"/> (2 boards)10.70</p> <p><input type="checkbox"/> E/8211-4 Pulse Generator5.29</p> <p><input type="checkbox"/> E/8212-1 ELCB2.41</p> <p><input type="checkbox"/> E/8212-2 Servo Interface</p> <p><input type="checkbox"/> (2 boards)5.87</p> <p><input type="checkbox"/> E/8212-4 Spectracolumn4.82</p> <p>1983</p> <p><input type="checkbox"/> E/831-1 Fuel Gauge3.00</p> | <p><input type="checkbox"/> E/831-2 ZX ADC2.25</p> <p><input type="checkbox"/> E/831-3 Programmable PSU3.00</p> <p><input type="checkbox"/> E/833-1 SoundBoard11.16</p> <p><input type="checkbox"/> E/833-2 Alarm Module3.15</p> <p><input type="checkbox"/> E/833-3 ZX81 User Graphics0.93</p> <p><input type="checkbox"/> E/833-4 Logic Probe2.17</p> <p><input type="checkbox"/> E/834-1 Real Time Clock7.60</p> <p><input type="checkbox"/> E/834-2 Thermometer</p> <p><input type="checkbox"/> (2 boards)8.47</p> <p><input type="checkbox"/> E/834-4 Stage Lighting — Main ..11.94</p> <p><input type="checkbox"/> E/834-5 Stage Lighting — Display 3.00</p> <p><input type="checkbox"/> E/835-1 Compressor/Limiter5.38</p> <p><input type="checkbox"/> E/835-2 Single PSU2.75</p> <p><input type="checkbox"/> E/835-3 Dual PSU3.49</p> <p><input type="checkbox"/> E/835-4.2 NDFL Amp6.85</p> <p><input type="checkbox"/> E/835-5 Balance Input Preamp2.81</p> <p><input type="checkbox"/> E/835-6 Stage Lighting</p> <p><input type="checkbox"/> Autofade5.38</p> <p><input type="checkbox"/> E/835-7 Stage Lighting —</p> <p><input type="checkbox"/> Triac Board4.12</p> <p><input type="checkbox"/> E/836-1 to 3 PseudoROM</p> <p><input type="checkbox"/> (3 boards)3.15</p> <p><input type="checkbox"/> E/836-4 Immersible Heater2.00</p> <p><input type="checkbox"/> E/836-5 Atom Keypad4.50</p> <p><input type="checkbox"/> E/837-1 Flash Sequencer2.32</p> <p><input type="checkbox"/> E/837-2 Trigger Unit Main Board ..2.32</p> <p><input type="checkbox"/> E/837-3 Trigger Unit Transmitter ..1.44</p> <p><input type="checkbox"/> E/837-4 Switched Mode PSU14.00</p> <p><input type="checkbox"/> E/838-1 Graphic Equaliser7.91</p> <p><input type="checkbox"/> E/838-2 Servo Fail-Safe</p> <p><input type="checkbox"/> (four-off)2.55</p> <p><input type="checkbox"/> E/838-3 Universal EPROM prog8.38</p> <p><input type="checkbox"/> E/839-1 NiCad Charger/Regen3.28</p> <p><input type="checkbox"/> E/839-2 Digger2.96</p> <p><input type="checkbox"/> E/839-3 64K DRAM12.24</p> <p><input type="checkbox"/> E/8310-1 Supply Protector.....1.90</p> <p><input type="checkbox"/> E/8310-2 Car Alarm.....3.46</p> <p><input type="checkbox"/> E/8310-3 Typewriter Interface.....3.63</p> <p><input type="checkbox"/> E/8311-1 Mini Drum Synth 2.67</p> <p><input type="checkbox"/> E/8311-2 Alarm Extender 2.79</p> <p><input type="checkbox"/> E/8311-3 Multiswitch 3.12</p> <p><input type="checkbox"/> E/8311-4 Multiple Port. 3.77</p> <p><input type="checkbox"/> E/8311-5 DAC/ADC Filter 2.80</p> <p><input type="checkbox"/> E/8311-6 Light Pen. 4.00</p> <p><input type="checkbox"/> E/8311-7 Logic Clip 2.18</p> <p><input type="checkbox"/> E/8311-8 MC Head (JLLH) 2.76</p> |
|--|---|--|

Prices quoted are valid until December 1983

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £.....

Add 45p p&p 0.45

Total enclosed £.....

**PLEASE ALLOW
28 DAYS FOR
DELIVERY**

Signed

Name

Address

.....

.....

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 news-letter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. **£9.95.**
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £6.95**
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost **£32.00. OUR PRICE ONLY £12.95 complete with data.**
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

**DON'T MISS THOSE BARGAINS
CALL NOW, IT'S FREE!**

01-679 1888

8 BIT WORD - NO PARITY

7 days per
week 24 hrs.
per day

COMPUTER 'CAB'



All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" x 10.5" x 11.5". Also available LESS PSU, with FANS etc. Internal dim. 19" w. 16" d. 10.5" h. **£19.95.** Carriage & insurance £9.50.

8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality!! The 7100 single sided drive accepts hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB of storage. Absolutely SHUGART, BASF, SIEMENS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. **7100 Single sided £225.00 + Carriage and insurance £10.00.**

Optional accessories: Full technical manual £20.00 alone. £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

RECHARGEABLE NICADS

SAFT VR2C 1.2v 'C' size nicads. 18 cells in ex equipment pack. Good condition - easily split to single cells. **£9.50 + £1.90 post and packing.**

VIDEO MONITORS

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 MHz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit, 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**

24" CASED. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition. **ONLY £55.00 PLUS £9.50 CARR. & INS.**

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL RGB with separate sync. and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col. definition. Brand new and guaranteed. Complete with full data & circuit. 240 v AC working. Dim. 14" x 13" x 13". **ONLY £199.00 PLUS £9.50 CARR.**

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed. **50+ £2.95 100+ £5.15.**

TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. **100+ £6.90 200+ £12.30 300+ £19.50**

CALLING DEC USERS

Brand new and boxed

RSX 11M 3.2 Documentation kits, fill 3 feet of your bookshelf! Under half price only **£120.00** carr. £6.50 v at on manuals. DEC MSV11-DD 32k x 16 bit RAM **£195.00** We are always keen to buy all types of used or surplus DEC equipment.


SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter

Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499+ VAT

Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUIME command compatibility and full control via CPM Wordstar etc. Many other features include bi directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable £10.00. Tech manual £7.50. Tractor feed £140.00. Spare daisy wheel £3.00. Carriage & Ins. (UK Mainland) £10.00.

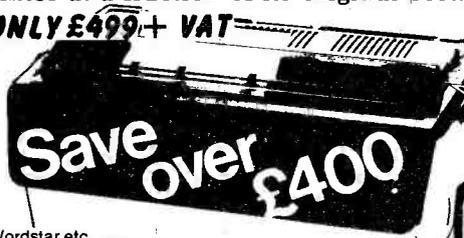

TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order

Options: Floor stand **£12.50 + VAT**
KSR33 with 20ma loop interface **£125.00 +**
Sound proof enclosure **£25.00 + VAT**

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only **£75.00**
MODEM 2B/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. **£85.00**
MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link. 75 baud transmit - 1200 baud receive. Auto answer. **£130.00**
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. **£130.00**
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. **£130.00** Carriage. 13A £4.50. 2B/C £20 £9.50.
DATA PUMP MODEM compact unit upto 1200 baud full duplex over 4 wires or half duplex over 2 wires. BELL specification with data i/o via RS232 25 way D socket, remote test etc. 240 v operation. Supplied complete with data **£85.00** carr. £4.50.

For more information or details of other types of ex stock modems contact sales office.

SPECIAL MODEM OFFER

EX TELECOM. Direct connect, 2 wire, European standard, 75/1200 baud data modems. Normally priced at £140.00, we have a limited quantity of guaranteed working, but cosmetically defective (ie scratches and scuffs on panels etc.) units at a super low price of only **£49.95.** Modems are made to the highest standard and conform to the CCITT tone spec. Ideal for MICRONET, PRESTEL or DISTEL's forthcoming high speed ports. Standard RS232 data i/o via 25 way D skt. With data.
MODEM 2A Early version of modem 2B/C 300 baud full duplex, send-receive, auto answer. RS232 i/o. With data but untested. End of line clearance. Only **£35.00.** Supplied complete with data. Carriage & Ins. £9.50

8" WINCHESTER price SLASH

\$100 Bus 19 Mb. Subsystem. A cancelled order and change of policy by a major British disk drive manufacturer enables us to offer you 'last year's model' at a plug in and ready to go SUPER LOW PRICE. Our own custom controller pugs direct into the S100 bus and will control 2 disk drives, offering a total storage of OVER 36 Mbs! and at data transfer rates in excess of 7 Mb/sec seeing is believing!! Supplied complete with user configurable BIOS etc. Save a fortune. Limited quantity only.

3100 19 Mb. Disk drive **£499.00** PSU unit **£165.00**
CD1100 controller & BIOS **£345.00** PSU extension cable **£9.95**
Full tech Manual **£20.00**

Special SUBSYSTEM prices. 1 x 3100 disk + PSU + Controller **£799.00**
or 2 x 3100 disks + 2 PSU + Controller **£1295.00**
All prices + VAT and carriage. 90 day guarantee. Data on request.

ALL PRICES PLUS VAT

DISPLAY
-ELECTRONICS-

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00.** Minimum Credit Card order **£10.00.** Minimum BONA FIDE account orders from Government depts, Schools, Universities and established companies **£20.00** Where post and packing not indicated please ADD **60p + VAT** Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

32 Biggin Way, Upper Norwood, London
Tel: 01-679 4414 Telex. 27924



LOGIC CLIP

Ever been frustrated trying to test a digital circuit with only one single-point logic probe? Never fear, ETI comes to the rescue with this 16-point, 4-state CMOS/TTL logic probe.

This logic clip is a very useful addition to a digital test-set, speeding up the tedious testing of MSI devices, such as flip-flops and counters. Such clocked logic requires both stimulus and effect to be observed, and this is difficult to do with a conventional logic probe. The usual solutions of a multi-trace oscilloscope and a logic analyser will be just a bit beyond the means of the average ETI reader. The ETI logic clip provides equivalent facilities at a much more approachable cost.

When built, the logic clip simply clips on top of the IC to be tested (using an IC test clip), showing the logic state (high, low, undefined or pulsing) of all 16 pins of the IC. The probe caters for both TTL and CMOS ICs — the high and low logic levels are selected by a single switch.

Goodbye Tedious Testing

The logic clip is the ideal partner for the ETI Dicrobe logic pulser (September 1982), which can provide suitable stimuli for the IC under test. For example, let us suppose that we wish to test for the proper operation of a binary counter. If we use a normal probe, each counter output must be checked before the next clock pulse can be applied, to make sure that the clock pulse is producing the desired response — a binary count. Contrast this with using the logic clip, which simply fits on top of the counter chip, leaving your hands free. You sit back, push the pulser button and watch the count progress.

Dazzling Dual Colour

The circuit basically consists of two identical logic probes, which compare the input with selectable logic levels for low and high, and drive the display LEDs accordingly. The small size of the clip is

achieved by scanning eight pins on either side of the test IC, and feeding the selected test voltage to these two logic probes. Of course, there would be little point in doing this if all the data was displayed on one LED — the result would be a meaningless blur, so the display is made up of two rows of eight multiplexed dual colour LEDs, one row for each logic probe.

These dual colour LEDs are connected between the outputs of the high and low comparators, and give the following indications:

High: green

Low: red

Undefined: off

Oscillating: yellow

With experience, the mark/space ratio of an oscillating mode can be estimated from the degree of red or green in the yellow indication. To make the device easier to read, the LEDs are laid out in the pattern of the IC pins (see Fig. 2a), each LED

corresponding to the test pin below it.

The scanning is done by 4051 CMOS one-of-eight analogue selectors for both input and display. These have an on resistance of about 160R, and so will limit the current through the LEDs. The scan address lines are provided by the binary counter IC2, fed by oscillator IC1, which runs at a frequency high enough to maintain persistence of the display (ie, no flicker). The rather odd order in which the pins are scanned is due simply to the constraints of the PCB design.

Construction

The probe consists of two circuit boards attached to an IC test clip, each board displaying the state of the eight pins on it's side of the IC. Start the construction by soldering the wire links above R6 on board 2, then insert the resistors

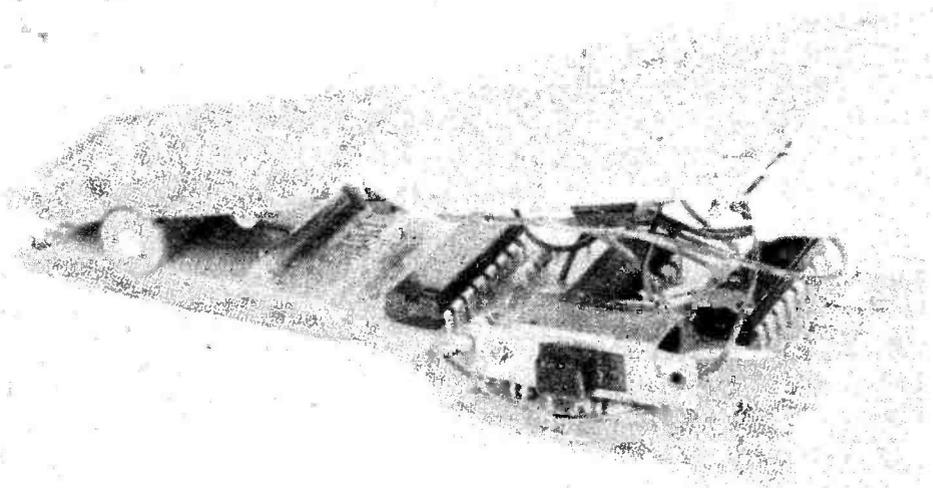


Fig. 1 Construction of the logic clip is on two boards which are then glued onto an IC clip.

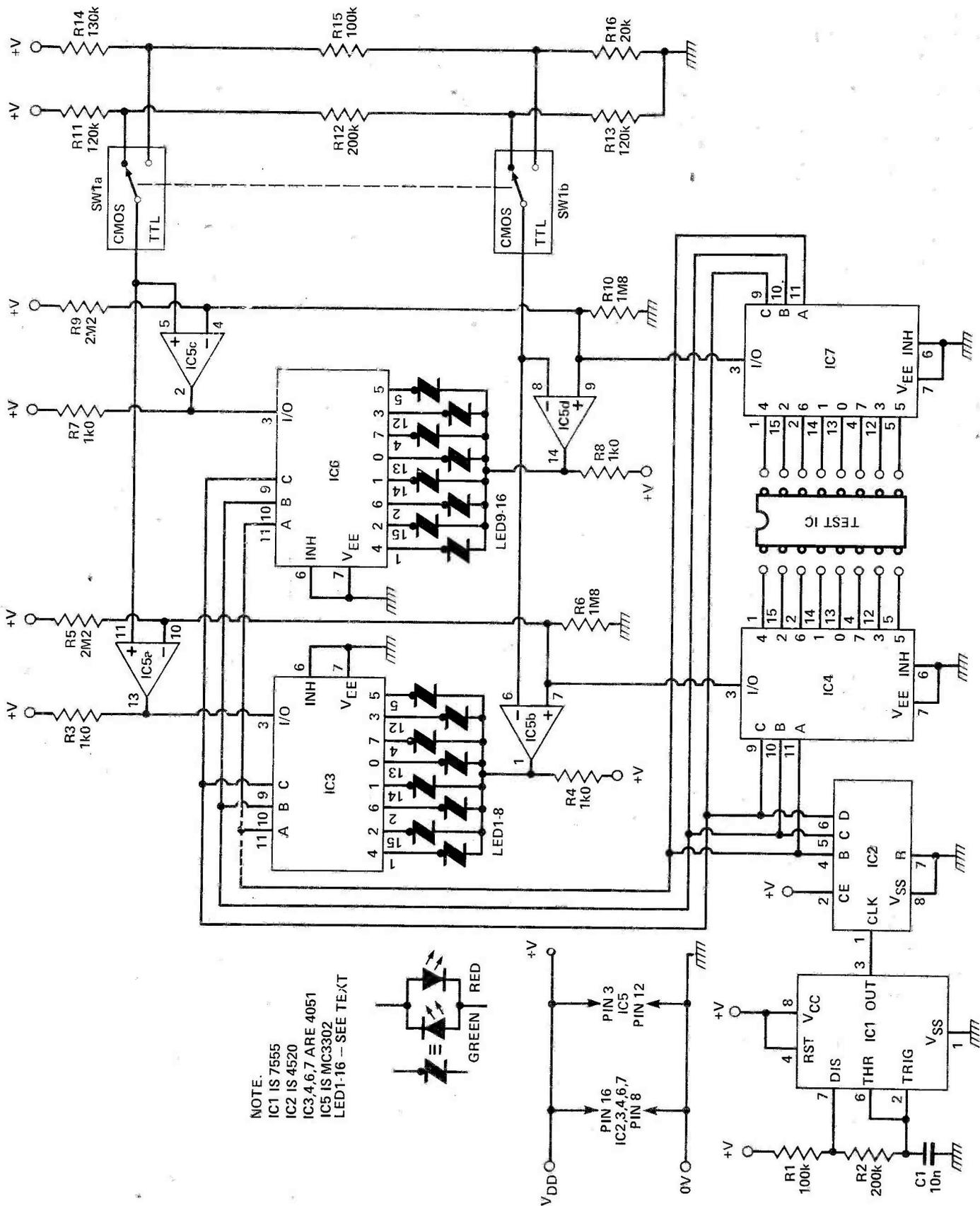


Fig. 2 Circuit diagram of the Logic Clip.

HOW IT WORKS

The logic clip relies on the multiplexing/demultiplexing action of the 4051 analogue selectors. The scan address is provided by the dual binary counter, IC2. Only one of the counters is used, and the count outputs B, C and D are taken to the 4051s for ease of PCB design. The counter is fed by the 7555 oscillator, IC1. The components used set the oscillation frequency at around 500 Hz, so each of the test IC pins is scanned approximately 30 times a second.

As each of the pins is scanned in turn, the voltage at that pin is fed to the high and low comparators of IC5 (two comparators for each side of the chip). The upper and lower threshold voltages are provided by R11-R16, and are selected by SW1. The outputs of the comparators vary with input as shown in Table 1.

The comparators have uncommitted collector outputs, so can sink current, but are passive high, i.e. they just sit there and do nothing when high. Thus, the LEDs have to be driven by resistors R3, 4, 7 and 8. When an output is low, the open collector sinks current to ground, preventing the LED from lighting. When the output is high, the current can flow through the LED. The outputs of the low comparators, IC5b and IC5d, are connected to the commoned green anodes, and the high comparators, IC5a and IC5c, are connected to the demultiplexers, IC3 and IC6. These are fed by the same address lines as the multiplexers, and have a similar PCB layout, so each LED corresponds to the test pin directly below it. The net result of all this is a four-state display of what is happening on the sixteen pins of the IC under the clip.

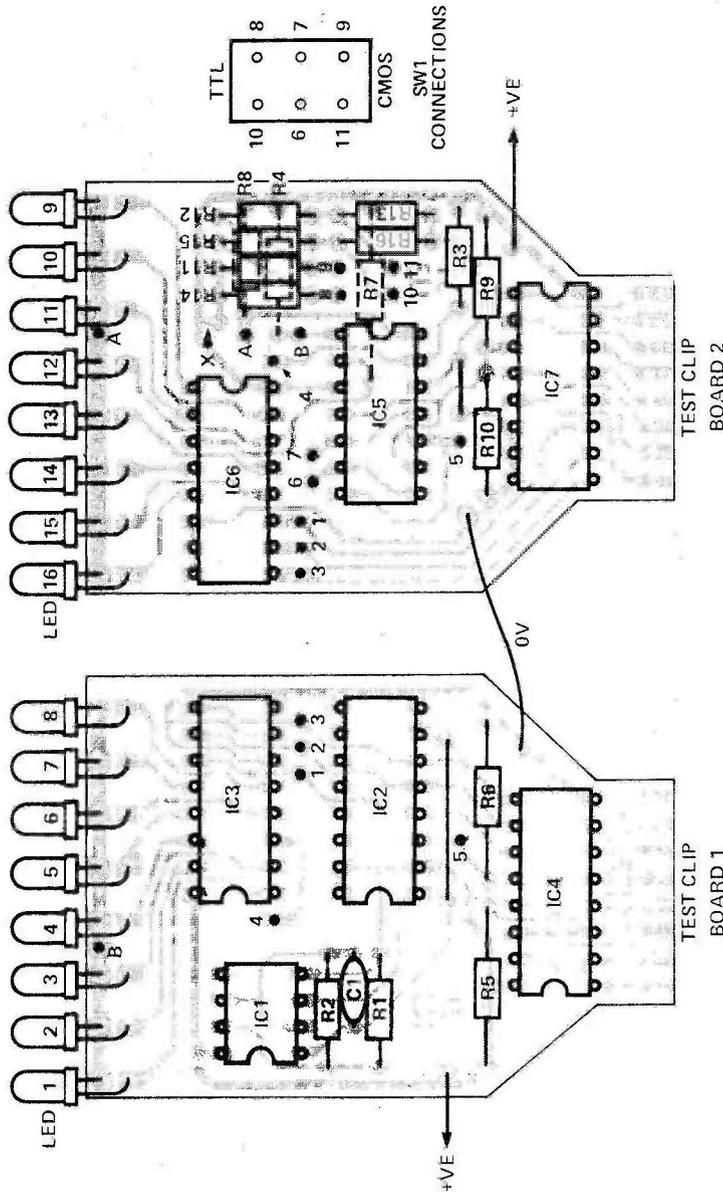


Fig. 3 Overlay diagram of the logic clip. Note that all the numbered points and the points with letters A and B should be joined up (ie, join 1 to 1, 2 to 2, A to A, etc. The point marked 'X' is where the foil may be cut if you want to power the clip from an external source (see Expanda-clip section of text). Note also that resistors R4, R7 and R8 are mounted on the foil side of the PCB, and should be very carefully soldered onto the pads provided to avoid lifting the track.

BUYLINES

Problems here are the LEDs and the test clip. Make sure that the LEDs are 2-lead devices, NOT the 3-lead common cathode type sometimes called 'dual colour'. Suitable LEDs are available from Watford Electronics.

Our test clip was obtained from Basic Electronics, but Maplin, GSC and RS stock equally suitable clips (order codes FY74R, 08-0016 and 423-627 respectively).

PARTS LIST

RESISTORS (all 1/4W 5%)			
R1, R15	100k		
R2, R12	200k		
R3, R4, R7, R8	1k0		
R5, R9	2M2		
R6, R10	1M8		
R11, R13	120k		
R14	130k		
R16	20k		
CAPACITOR			
C1	10n (837448)	LED 1-16	0.2' two-lead red/green dual colour
SEMICONDUCTORS			
IC1	7555		MISCELLANEOUS
IC2	4520		PCBs, DPDT switch (as small as possible), IC test clip, 2.5mm jack plug and socket, two core lead, red and black croc. clips.
IC3, 4, 6, 7	4051		
IC5	MC3302		

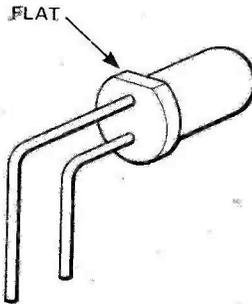
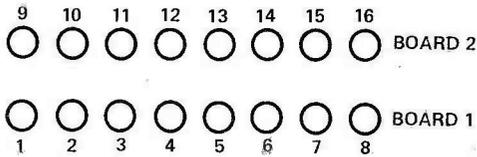


Fig. 4(a) The layout of the indicator LEDs. (b) Mounting details of the two-colour LEDs.

and C1. Next, fit the LEDs: these are dual colour devices, with a flat on the package that indicates the red anode/green cathode lead. Form the LED leads as shown in figure 4b.

Connect SW1 to points 6 to 11, following the layout shown in the overlay diagram. Now solder the ICs in place, noting their orientation and taking care not to make any solder bridges across the many fine tracks. Next, carefully solder the resistors R3, 4, 7 and 8 on the foil side of board 2, keeping the resistors as close to the board as possible. Finally, solder the power jack socket in place, taking both power rails to each board from the socket.

Once the boards have been assembled, it would be advisable to test them before attempting final construction. Temporarily wire the boards together using lengths of insulated wire to join points 1-5. Plug in the power jack and apply suitable test voltages to each of the sixteen inputs (e.g. try V+, 0V and V+/2). Check that the LEDs light correctly for both CMOS and TTL threshold levels. If they do not, check that the LEDs are connected the right way round, and that all the components are inserted correctly.

Tricky . . .

Now for the tricky bit of mounting the boards onto the test clip. Details will depend on the type of clip used, but the method we used for our hinged clip will apply to most types.

First, shape the test contacts so they fit through the holes in the PCB. Bend these pins to make the edge of the board flush with the plastic of the clip. Then solder the boards to the clip with the components facing inwards. This joint may be strengthened by filling between the board and the clip with epoxy resin, such as Araldite. Finally, make the inter board

connections 1 to 5 with lengths of fine, flexible insulated wire. These wires will be flexed as the clip is used, so it would be wise to reduce the strain on them. This can be done by making a loop in the wire like that shown in figure 5, and ensuring that the wire is at right angles to the board.

. . . But You Can Do It

The probe is a rather odd shape, so we recommend building a case around the boards, using 60 thou plastic sheet ('Plasticard'), available from most good model shops. This should be cut to size and glued together with polystyrene cement.

If you have never worked with plasticard before, we had better explain how easy it is to use. To cut it, you just score a line with a sharp knife, such as a scalpel (fairly heavily for 60 thou), and snap along the score line. As the clip hinges, there are two halves to the case, which simply shroud the boards, covering the soldering. The logic select switch is glued into a hole in one of the sides, and the power jack socket into the other.

If you feel unable to build the case, then find a suitably sized box to hold both boards, wire the boards firmly together, and connect

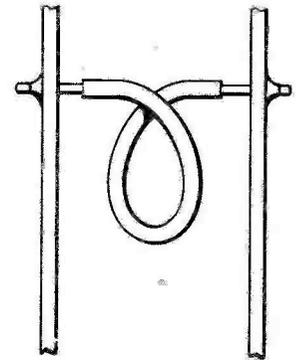


Fig. 5 How we suggest looping the connecting wires between the two boards.


the test clip to the probe unit via a length of ribbon cable.

Expanda-clip

There are other possible uses of the clip, for instance, a number of similar units could be built on one board (with a different PCB layout), for use on 40-pin devices. Alternatively, the logic clip could be used to monitor bus lines, etc.

Also, it is worth noting that there is facility on the board for the clip to be powered by a supply other than that of the circuit under test, allowing low voltage devices to be tested, whilst keeping the LEDs brightly lit. This can be done by breaking the foil at the point marked 'X' (the connection between the +ve supply and the resistor divider chain) and connecting a voltage sense line to the spare PCB pad just below point X. This line is then connected to the +ve supply rail of the unit under test, with the clip powered by another source. This may be necessary even for TTL circuits, due to the variation in 'on' resistance of the 4051 selectors.

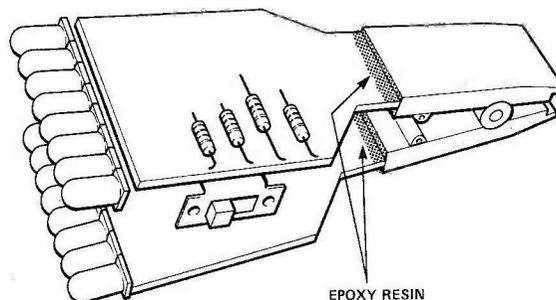Having struggled through a rather involved construction, you should be left with a very useful and time saving tool. Happy probing!



SAVE HUNDREDS ON YOUR HI-FI-NOW!

HI-FI NOW! – the new magazine with a new way of giving you the buying information you need – NOW!

HI-FI NOW! – will tell you the £99 speaker that sounds like £200 – NOW!

HI-FI NOW! – will help you spend £15 to make your personal stereo like a million dollars – NOW!

HI-FI NOW! will even make sure you spend £2,000 wisely – NOW!

HI-FI NOW! – answers the questions you are asking about hi-fi – NOW!



Wharfedale, KEF, Rotel, Sansui, Marantz, Koss, Sony, Pioneer, Hitachi. Just some of the names in the first issue of HI-FI NOW!

HI-FI NOW! AT YOUR NEWSAGENT NOW! ONLY 85p!

IT LIVES AGAIN!

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.

Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics – It's Easy**. Originally a long-running series in Electronics Today International, **Electronics – It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenomenally successful publication is available again, in its third reprint. **Electronics – It's Easy** is a comprehensive and simply-written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics – It's Easy** by mail order using the coupon below. Make cheques or postal orders payable to ASP Ltd; alternatively you may pay by Access or Barclaycard.

Send to: Sales Office (Specials),
513 London Road, Thornton Heath
Surrey CR4 6AR

Please send me copies of Electronics –
It's Easy. I have enclosed £ (£4.95 each
including p&p).

NAME

ADDRESS

Please debit my account
My Access/ Barclaycard No. is

Signature



SERVICE SHEET

Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;
- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);
- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;
- We will not reply to queries that are not accompanied by an SAE (or international reply coupon). We are not able to answer enquiries over the telephone. We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.
- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

Subscriptions

The prices of ETI subscriptions are as follows:
UK: £13.15
Overseas: £16.95 Surface Mail
£36.95 Air Mail

Send your order and money to: ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

Backnumbers

Below we list the backnumbers that are available from our backnumbers department. Please note that this list will be out of date if you use an old copy of the magazine. Backnumbers cost £1.50 (UK or overseas by surface mail) and are available from: ETI Backnumbers Department, 513 London Road, Thornton Heath, Surrey CR4 6AR (cheques should be made payable to ASP Ltd).

Even if the copy of ETI you need is not listed, all may not be lost, because we run a photocopying service. For £1.50 (UK and overseas) we will photocopy an entire article (note that parts of a series of articles count as separate articles). Your request should clearly state what article you require and the month and year in which it appeared (the index for 1980 and 1981 was published in January 1982, and the index for

1982 appeared in December 1982). Send your request to ETI Photocopies, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE (cheques should be made out to ASP Ltd).

November 78
November 79
April 80
September 80
October 80
November 80
December 80
January 81
February 81
March 81
April 81
May 81

June 81
November 81
December 81
March 82
May 82
June 82
July 82
August 82
September 82
October 82
December 82
February 83

Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details. (Don't forget to give us your telephone number).

We don't bother with the bureaucracy for Tech Tips — all you do is to send in your idea, stating clearly if you want an acknowledgment of receipt. If possible, please type your explanation of why the circuit is different, what it does and how it works, on a separate sheet from the circuit diagram; both sheets should carry your name, address and the circuit title. We'll let you know (within a month or so) if we want to use your Tech Tip.

Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

OOPS!

We have in the past published small corrections to projects on the letters page, and major corrections separately. From now on corrections will appear on this page, and will be repeated for several months (just to increase our embarrassment). If a correction is too large to fit on here, we will publish it just once, but will note the fact that a correction does exist, and that copies of it can be obtained from us provided you send in an SAE. But please — request copies only if you really do need them; if this service is abused, we may be forced to withdraw it.

Programmable Power Supply (January 1983)

Lascar Electronics have now moved to Module House, White Parish, Salisbury, Wiltshire SP5 2SJ.

Flash Sequencer (July '83)

Q1 should be BC184L; Q2-5 should be BC182L.

Telescope (August 1983)

We had a shower of annotation falling off our diagrams! On Fig. 1, C19 (below IC14) was not labelled nor was Q2 (above R1), and there were two C23s — one should be IC22 and it doesn't matter which. In Fig. 5, IC12 was not labelled. Unfortunately, there was a mistake in the correction (blush!): C14 is the 22µ tant on the -5 V line.

Graphic Equaliser (August 1983)

D2 and D3 are shown the wrong way round in the power supply circuit diagram on page 20.

Universal EPROM Programmer (August 1983)

Quite a few sillies here! On the circuit diagram (page 46), C6 is 100u and C9 is 100n, not the other way round as given. Some bars were omitted from note three of Table 1 on page 48: it should have read "CE/PGM (27 series) is equivalent to PD/PGM (not PD/PGM) (25 series)." The penultimate sentence of the first paragraph on page 50 should read "... adjust RV1 for a potential of +25 V at IC10 output." On the overlay, IC7 is between SK2 and SK1, IC6 is between SK1 and C10, IC11 is between R7 and R10, R3 is between R2 and Q2, and Q7 is between Q6 and Q8. A link is missing between IC7 and SK1, and the unidentified pins at the right hand end of SK3 are the +5V line. Finally, C10 appears twice in the parts list but only the first entry is correct, and the second DIL socket should, of course, be 8, not 80, way.

Z80 Controller Computer (August 1983)

On the overlay, SW1 is the rectangle beside ICs 5 and 6, C6 should be shown between ICs 3 and 7, and a link through has been missed — to the right of pin 18, IC11.

Typewriter Interface (October 1983)

There are two errors in Table 1 on page 24: location 3C should contain E7 and location 3F should contain 5F.

Car Alarm (October 1983)

In the semiconductors section of the parts list, Q1, 2, 5, and 7 should be BC212L, Q3 should be BC182L, and Q4, 6 should be TIP31 or BD131. There was also another (inconsequential) silly but we bet you've already spotted that one!

Tech Tips (October 1983)

Ramped Pulse Generator For Stepper Motors — pin 1 of IC2 should be grounded, the Ramp Up and Ramp Down inputs accept negative, not positive, going pulses, and IC7 should be a 4011 rather than a 4001.

SAVE £4.25 by receiving a FREE magazine binder when you subscribe to

electronics today

INTERNATIONAL

Cut out and SEND TO :

electronics today

513, LONDON ROAD,
THORNTON HEATH,
SURREY, CR4 6AR
ENGLAND.

Please send my free binder and commence my personal subscription to with the Issue

SUBSCRIPTION RATES
(tick as appropriate)

£13.15 for 12 Issues UK
£16.95 for 12 Issues overseas surface
£36.95 for 12 Issues Air Mail

All you have to do to receive your FREE binder is book a new subscription or renew an existing subscription to Electronics Today International. What could be simpler?

SPECIAL OFFER

I am enclosing my (delete as necessary) Cheque/Postal Order/International Money Order for £

(made payable to ASP Ltd)

OR

Debit my Access/Barclaycard* (*delete as necessary)

Insert card no.

Please use BLOCK CAPITALS and include post codes

Name (Mr/ Mrs/ Miss)

Address

Signature

Date

TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO

IN YOUR OWN HOME - AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates

Radio Amateurs
Basic Electronic Engineering (Joint C&G/ICS)

Certificate Courses

TV and Audio Servicing
Radio & Amplifier Construction
Electronic Engineering* and Maintenance
Computer Engineering* and Programming
TV, Radio and Audio Engineering
Electrical Engineering,* Installation and Contracting

*Qualify for IET Associate Membership



Approved by CACC



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest

Name

Address



Post to: Dept N 265
ICS School of Electronics
160 Stewarts Road
London SW8 4UJ



01-622 9911
(All Hours)

ELECTROVALUE



THE E.T.I. ENTHUSIAST'S

A-Z

BUYING GUIDE

It's amazing what you'll find in the pages of our current Autumn price list, be you beginner expert or professional. The list below gives some idea of the enormous stocks we carry and our service is just everything you look for and is backed by nearly 20 years of specialised experience. Write, Phone or call for our Autumn price list now!

It's FREE!

Good Bargains

Good choice

Prompt mail order service

Please mention this journal when applying

Access facilities	Connectors	Lamps	Switches
Aerosols	Discounts	Meters	Solder tools
Batteries	Electrolytics	Opto-electronics	Tools
Boxes	Ferrites	Quantity prices	Transformers
Breadboards	Grommets	Quartz crystals	Vero products
Computers & equipmnt.	Hardware	Resistors	Visa facilities
Capacitors	I.C.s.	Relays	Zeners
	Knobs	Semi-conductors	

ELECTROVALUE LTD. 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB. Phone - Egham 33603 (STD 0784; London 87) Telex: 264475; Northern Shop 680 Burnage Lane, Manchester (Callers Only) EV (061-432 4945) Computing shop 700 Burnage Lane M/c. (061-431 4866).

ELECTROMART

AVON

ANNLEY ELECTRO

190 Bedminster Down Road
Bedminster Down, Bristol
Tel: 0272 632622
Open: Mon-Sat 9am-6.30 pm Wed 9am-2pm.

CHESHIRE



41 Winwick St., Warrington
Tel. 54174
Open: Mon-Fri 9.30-6
(closed Tues) Sat 9.30-5
Components, aerials & burglar alarm
specialists

IRELAND

IRELAND
Call **A&A ELECTRONICS**
For wide range of kits.
17 Cuala Road
Bray, Co. Wicklow
Tel: 01 862422

LANCASHIRE

ETESON ELECTRONICS

15B Lower Green,
E.E. Poulton-le-Fyde, Blackpool
Tel: (0253) 885107
Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.
Electronic Component Specialists.

MONTHLY IN ELECTRONICS TODAY — YOUR OWN 'WHERE TO BUY IT' GUIDE

MERSEYSIDE

MYCA ELECTRONICS

2 VICTORIA PL, SEACOMBE FERRY,
WALLASEY, L44 6NR.
Tel: 051 638 8647
Open Mon-Sat 10am-5.30pm
Mail Order price list 50p refundable

PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982
47 Whitechapel, Tel 051 236 5489
Liverpool 2
'THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30



WYMCA Building, College St.,
St. Helens Tel. 50707
Open: Mon-Fri 9.30-5.30
(closed Thurs) Sat 9.30-5
Components, aerials & burglar alarm
specialists

NORTHAMPTONSHIRE

- * A new company selling electronic components.
- * Mail order and walk-round supermarket.
- * Vast stocks and very competitive prices.

EMOS High March, Daventry, NN11 4HQ.
Telephone 03272 5523. Telex 311245.
(Off A45 opposite John O' Gaunt.)

TYNE & WEAR

**NOW OPEN IN NEWCASTLE
FOR THE BEST IN ELECTRONIC COMPONENTS
TEST EQUIPMENT AND ACCESSORIES**

Marlborough Electronic Components
15 Waterloo Street, Newcastle NE1 4DE1
Tel: 818377

Open 9am-6pm Mon-Sat Easy Parking
STOCKISTS OF
TRANSISTORS, RESISTORS, CAPACITORS,
I.C. DIODES, ELECTRONIC BOOKS Etc.
REPAIRS UNDERTAKEN

S. WALES

**STEVE'S ELECTRONIC
SUPPLY CO. LTD.**
45 Castle Arcade, Cardiff
TEL: 0222 41905
Open: Mon-Sat 9-5.30
For components to computers

WORCS/W. MIDLANDS

WAVEBANDS

103 Coventry St., Kidderminster
Components, computers, car radios,
C.B.'s, amateur radio
Spares & Repairs
Open: Mon-Sat 9-6,
TEL: 0562 2179



YORKSHIRE



ACE MAILTRONIX LTD.
3A Commercial Street,
Batley. Tel: (0924) 441129
Open: Mon-Fri 9am-5.30pm. (Sat 1pm)
Retail and wholesale.

Please include my business details in the next available issue of **ELECTRONICS TODAY INTERNATIONAL**:

BUSINESS NAME:

ADDRESS:

TEL. NO.:

OPENING HOURS:

RETAIL WHOLESALE MAIL ORDER (Please tick)

CONTACT: (FOR OFFICE USE ONLY)

