


electronics today

INTERNATIONAL

NOV 1984 99p

CASH 5
1.10

BUMPER PROJECTS ISSUE

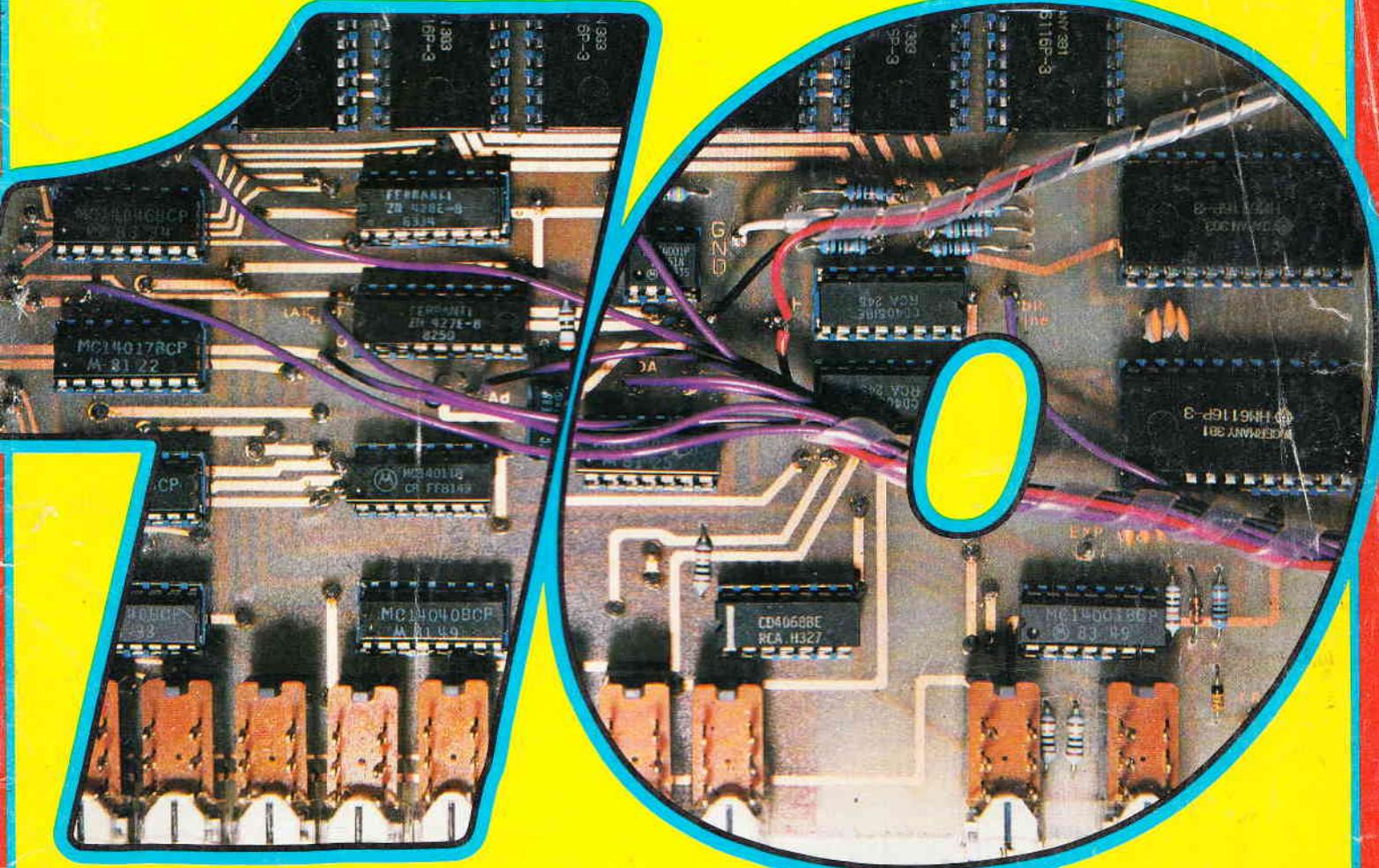

PROJECTS
to while away your
evenings. **Including:**

**AM/FM Portable Radio –
Switch On and Tune In!**

**Video Vandal –
Special Effects On-Screen
In Your Own Home**

**Electron Speech Board –
Turn Your Acorn Into
A Chatterbox**

**Capacitance Meter –
Simple, Direct-Reading
Design**

As seen in the national press

WIN a
**DREAM
HOLIDAY**

in our
**GREAT
COMPETITION**

MUSIC.... RADIO.... ROBOTICS...

neptune

for low-cost training in real-life robotics



The advanced design of the Neptune 2 makes it the lowest cost real-life industrial robot.

It is electro-hydraulically powered, using a revolutionary water based system (no messy hydraulic oil!)

It performs 7 servo-controlled axis movements (6 on Neptune 1) – more than any other robot under £10,000.

Its program length is limited only by the memory of your computer. Think what that can do for your BASIC programming skills!

And it's British designed, British made.

Other features include:

Leakproof, frictionless rolling diaphragm seals.

Buffered and latched versatile interface for BBC VIC 20 and Spectrum computers.

12 bit control system (8 on Neptune 1).

Special circuitry for initial compensation.


Rack and pinion cylinder couplings for wide angular movements.

Automatic triple speed control on Neptune 2 for accurate 'homing in'.

Easy access for servicing and viewing of working parts.

Powerful – lifts 2.5 kg. with ease.

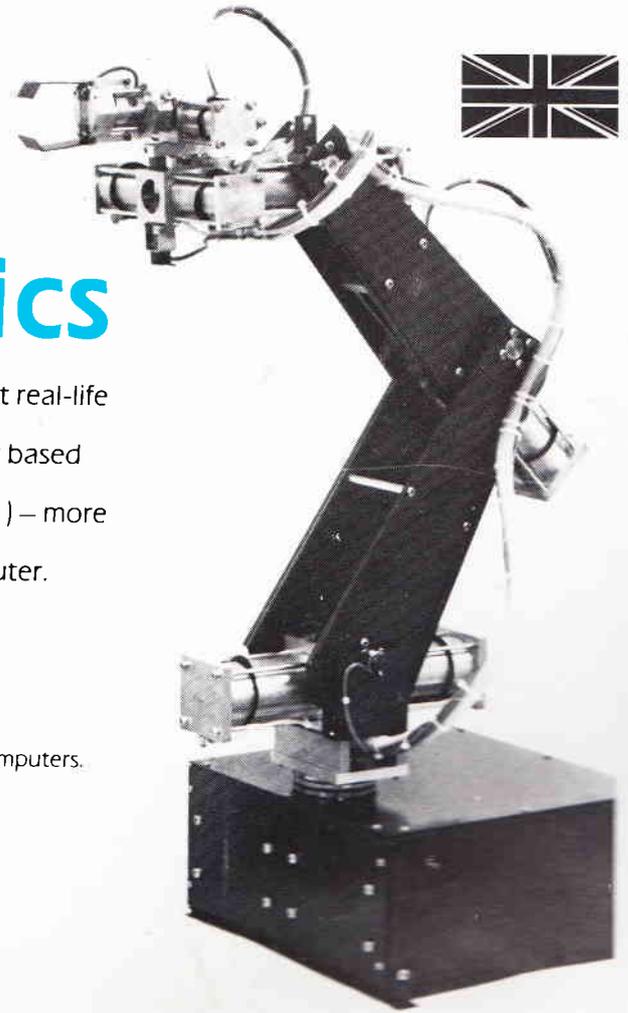Hand held simulator for processing (requires ADC option).



Neptune robots are sold in kit form as follows:

Neptune 1 robot kit (inc. power supply)	£1250.00	ADC option (components fit to main control board)	£95.00
Neptune 1 control electronics (ready built)	£295.00	Hydraulic power pack (ready assembled)	£435.00
Neptune 1 simulator	£45.00	Gripper sensor	£37.50
		Optional extra three fingered gripper	£75.00
Neptune 2 robot kit (inc. power supply)	£1725.00	BBC connector lead	£12.50
Neptune 2 control electronics (ready built)	£475.00	Commodore VIC 20 connector lead and plug-in board	£14.50
Neptune 2 simulator	£52.00	Sinclair ZX Spectrum connector lead	£15.00

All prices exclusive of VAT and valid until the end of 1984.

mentor desk-top robot

This compact, electrically powered training robot has 6 axes of movement, simultaneously servo-controlled. It gives smooth operation, and its rugged construction makes it ideal for use in educational establishments. Other features include long-life bronze and nylon bearings, integral control electronics and power supply, special circuitry for inertial compensation, optional on-board ADC, and hand-held simulator as the teaching pendant. Like Neptune, Mentor's program length is limited only by your computer's memory. Programming is in BASIC.

Mentor is all-British in design and manufacture and comes in kit form at an astonishingly low price.

Mentor robot kit (inc. power supply)	£345.00
Mentor Control electronics (ready built)	£135.00
Mentor Simulator (requires ADC option)	£42.00
ADC option (Components fit to control electronics board)	£19.50
BBC connector lead	£12.50
Commodore VIC 20 connector lead and plug-in board	£14.50
Sinclair ZX Spectrum connector lead	£15.00

All prices exclusive of VAT and valid until the end of 1984.



Cybernetic Applications

CYBERNETIC APPLICATIONS LIMITED

PORTWAY TRADING ESTATE, ANDOVER, HANTS SP10 3ET
TEL: (0264) 50093 Telex: 477019

electronics today

INTERNATIONAL NOVEMBER 1984 VOL 13 NO 11



Dave Bradshaw: Editor
 Phil Walker: Project Editor
 Ian Pitt: Assistant Editor
 Jerry Fowler: Technical Illustrator
 Paul Stanyer: Ad. Manager
 Kerry Fowler: Copy Control
 Jim Connell: Chairman

PUBLISHED BY:
 Argus Specialist Publications Ltd,
 1 Golden Square, London W1R 3AB.
 DISTRIBUTED BY:
 Argus Press Sales & Distribution Ltd,
 12-18 Paul Street, London EC2A 4J5
 (British Isles)
 PRINTED BY:
 The Garden City Press Ltd.
 COVERS PRINTED BY:
 Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS
 AUSTRALIA — Roger Harrison
 CANADA — Halvor Moorshead
 GERMANY — Udo Wittig
 HOLLAND — Anton Kriegsman



Member of the Audit Bureau of Circulation


Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1984 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.
 □ Subscription Rates. UK £14.35 including postage. For further details and Airmail rates etc, see the Readers' Services page.

EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.
 Telex 8811896.

FEATURES

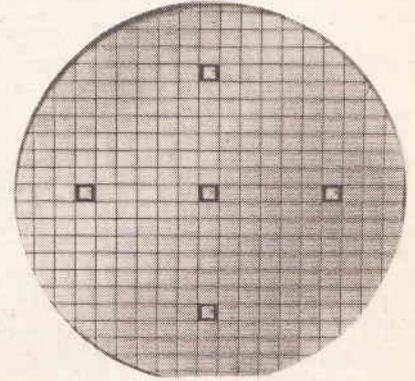- EDITORIAL** 7
 Following the collapse of their trusty soap box, the ETI team have been forced to seek another outlet for their effusions.
- DIGEST**..... 9
 Neglected press releases seek sympathetic readers.
- CUSTOMISED ICs**..... 44
 Precisely tailored to our readers' requirements — an examination of this important new technique.



PROJECTS

- LOUDSPEAKER SQUEAKER** ... 17
 Be it a woofer or a tweeter, Phil Walker's handy little gadget will make it squeak up for itself.
- AM/FM RADIO** 21
 A radio project at last — who says ETI isn't tuned in to its readers' wishes?
- DIGITAL CONTROL PORT**..... 29
 The final part of Mike Wynne Jones' design for Spectrum computers.
- ACTIVE LOUDSPEAKER** 36
 Enough of this theorising! With Black and Decker in hand and tongue in cheek, Barry Porter describes the construction of the Active-8 system.
- DIRECT-READING CAPACITANCE METER** 41
 For the low Cs and the high Cs.
- VIDEO VANDAL** 50
 The constructive way to pull a TV programme to bits.
- ELECTRON SPEECH BOARD**... 57
 John Wike describes a speech synthesiser board for the Electron computer.
- TEMPERATURE CONTROLLER**... 63
 This versatile circuit is clearly a few degrees above the average design.
- MAINS FAILURE ALARM**..... 66
 Make a fuss about power cuts with the ETI Vogonoff.
- KNIFE LIGHT** 69
 The latest novelty from the ETI armoury — no kit car should be without it!
- SPECTRUM STAGE LIGHTING INTERFACE**..... 72
 Right on cue — a design to make our stage lighting unit easier to control.
- PERPETUAL PENDULUM**... 77
 Damon Hart-Davis describes a more attractive desk-top toy.

INFORMATION

- ETI BOOK SERVICE**..... 68
ETI PCB SERVICE 86
PCB FOIL PATTERNS..... 80
- NEXT MONTH'S ETI** 62
ADVERTISER'S INDEX 90

WATFORD ELECTRONICS

33/34 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

MAIL ORDER, CALLERS WELCOME

Tel. Watford (0923) 40588. Telex. 8956095

ALL DEVICES FULLY GUARANTEED. SEND CHEQUE, P.O.s, CASH, BANK DRAFT WITH ORDERS. TELEPHONE ORDERS BY ACCESS/MASTER CHARGE ACCEPTED. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS OFFICIAL ORDERS WELCOME. P&P ADD 75p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car parking space available.

ELECTROLYTIC CAPACITORS: (Values in uF) 500V: 10uF 52; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6p 10p 15, 22, 12p; 33 15p; 47 12p; 68 20p; 100 19p; 220 26p; 1000 70p; 2200 99p; 50V: 66 10p; 100 17p; 220 24p; 40V: 22 9p; 33 12p; 330 47 32p; 1000 48p; 2200 90p; 25V: 1.5, 4.7, 10, 22, 47 6p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 1500 42p; 2200 50p; 3300 76p; 4700 92p; 16V: 47, 68, 100 9p; 125 12p; 330 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 26p; 4700 72p.

TAG-END CAPACITORS: 64V: 2200 139p; 3300 198p; 4700 245p; 50V: 2200 110p; 3300 184p; 40V: 4700 180p; 25V: 2200 90p; 3300 96p; 4000, 4700 99p; 10000 320p; 15000 345p; 16V: 22000 350p.

POLYESTER CAPACITORS: Axial Lead Type
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 150n 20p; 220n 30p; 330n 42; 470n 52p; 680n 1uF 68p; 2u2 82p. 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 100n 42p.

POLYESTER RADIAL LEAD CAPACITORS: 250V
10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 8p; 150n 20p; 220p 30p; 330n, 470n 15p; 680n 19p; 1u5 40p; 2u2 48p.

TANTALUM BEAD CAPACITORS
35V: 0.1uF, 0.22, 0.33 15p; 0.47, 0.66, 1.0, 1.5 18p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10, 20, 22, 25, 2.2, 3.3, 15p; 3.3, 6.8, 10 19p; 15, 36p; 22, 45p; 33, 47 50p; 100 95p; 10V: 2.2 26p; 3.3, 4.7 50p; 100 80p; 6V: 100 55p.

MYLAR FILM CAPACITORS
100V: 1nF, 2, 4, 4nF, 10 6p; 15nF, 22n, 33n, 40n, 47n 7p; 56n, 100n, 200n 9p; 50V: 470nF 12p.

CERAMIC CAPACITORS 50V:
Range: 0.5pF to 10nF 4p, 15nF, 22nF 33nF, 47nF 5p, 100nF/300V 7p, 200nF/6V 8p.

POLYSTYRENE CAPACITORS:
10pF to 1nF 6p, 15nF to 12nF 10p.

SILVER MICA (Values in pF)	COMPUTER ICs
2.2, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18	8205
22, 33, 39, 47, 50, 56, 58, 75, 82	8212
65, 100, 120, 150, 180pF	8214
200, 220, 250, 2.2, 3.3, 15p, 30p	2102L
300, 470, 800, 500, 820	2114
100, 120, 1500, 2200	2147
3300, 4700pF	2516
	395
	8236
	2532
	400
	8245
	2532
	400
	8251A
	850
	8251B
	850
	8255
	850
	8255
	850
	8256AC
	850
	8257
	850
	8259
	850
	8271
	850
	8272
	850
	8273
	850
	8499
	850
	8500

MINIATURE TRIMMERS Capacitors
2-6pF 2-10pF 22p; 2-25pF; 5-65pF 30p; 10-88pF 36p.

RESISTORS Carbon Film, miniature, Hi-Stab, 5%. RANGE Val 1-99 100+
0.25W 202 - 10M E24 3p 1p
0.5W 202 - 4M7 E12 3p 1p
1W 202 - 1M E24 6p 4p
2% Metal Film 510 - 1M E24 6p 4p
1% Metal Film 510 - 1M E24 8p 6p
100+ price applies to Resistors of each type not mixed.

RESISTORS NETWORK S.I.L.
7 Commended: (8 pins) 100n, 680n, 1K 2K, 4K7, 10K, 47K, 100K 25p
8 Commended: (9 pins) 150n, 180n, 270n, 330n, 1K, 2K, 4K, 68K, 10K, 22K, 47K, 100K, 25p.

DIODES	BRIDGE RECTIFIERS	75 SERIES
AA118	1A/50V	75107/76
AA120	1A/50V	75110/76
AA130	1A/100V	75114/15
BA100	1A/400V	75121/2 130
BAX	2A/800V	75150
BY100	2A/50V	75158 125
DY125	2A/200V	75158 150
CY127	3A/400V	75159 195
CRO23	2A/800V	75160 420
CA9	6A/100V	75162 650
CA47	6A/400V	75162 98
CA70	10A/200V	75166 98
CA75	10A/600V	75166 140
CA81	20A/200V	75162 360
CA85	25A/800V	75162 390
CA90	5A/16V	75162 150
CA91	6A/16V DIL	75162 150
CA95		75162 150
CA200		75162 150
CA202		75162 150
IN14		

Rapid Electronics

MAIL ORDERS:
Unit 1, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
Tel. Orders: Colchester (0206) 36412.
Telex: 987756.

ACCESS AND BARCLAYCARD WELCOME

MIN. D. CONNECTORS

9 way	15 way	25 way	37 way
Plugs solder lugs	55p	86p	150p
Right angle	90p	135p	350p
Sockets solder lugs	80p	100p	250p
Right angle	120p	180p	420p
Covers	100p	90p	110p

SOLDERING IRONS

Antex CS 17W Soldering iron	430
2.3 and 4.7mm bits to suit	85
Antex XS 25W soldering iron	580
3.3 and 4.7mm bits to suit	85
Solder pump/desoldering tool	600
Spare nozzle for above	100
10 metres 22 swg solder	700
0.5kg 22 swg solder	750

CONNECTORS

DIN Plug Skt Jack Plug Skt	
2 pin 9p 9p 2.5mm 10p 10p	
3 pin 12p 10p 3.5mm 9p 9p	
5 pin 13p 11p Standard 16p 20p	
Phono 10p 12p Stereo 24p 25p	
1mm 12p 13p 4mm 18p 17p	
UHF (CB) Connectors:	
PL259 Plug 40p Reducer 14p.	
SO239 square chassis skt 38p.	
SO238S round chassis skt 40p.	
IEC 3 pin 250V 5A.	
Socket free hanging	38p
Socket free mounting	60p
Socket with 2m lead	120p

VERO

Verobloc	395
Veroboard Size 0.1 in matrix	
2.5 x 1	26
2.5 x 3.75	95
3.75 x 5	120
3.75 x 17	350
4.75 x 17	450
V.O. board	195
Verobooks per 100:	
Single sided	55
Double sided	65
Spot face cutter	145
Pin insertion tool	185
Wiring pen	375
Spare spool 75p	6

SWITCHES

Submin toggle:	
SPST 60p DPDT 60p DPDT 65p.	
Miniature toggle:	
SPDT 60p SPDT centre off 90p	
DPDT 90p DPDT centre off 100p.	
Standard toggle:	
SPST 35p DPDT 48p	
Miniature DPDT slide 14p.	
Push to make 15p.	
Push to break 22p.	
Rotary type adjustable stop.	
1P12W, 2P6W, 3P4W all 55p each.	
DIL switches:	
4SPST 80p 6SPST 80p 8SPST 100p.	
Min. DPDT slide 14p. Push-make 15p.	

MICRO

27128-250	1225	6800	200	8522	330
6116P3	520	6802	280	8512	520
6264P15	2980	6806	600	8551	540
4116P4	70	6810	140	8085A	320
4164-15	480	6821	140	8156	380
4126-15	2850	6840	360	8251	350
270A CPU	290	6850	165	8253	370
270A P10	320	6852	240	8255	320
270A CTC	320	6857	500	8259	400
2764-250	595	6860	100	MC1488	70
2764 88C	595	6882	370	MC1489	70
2780A DMA	880	6950			

SOCKETS

8 pin	7p	28p
14 pin	11p	45p
16 pin	11p	55p
18 pin	12p	60p
20 pin	13p	68p
22 pin	15p	75p
24 pin	17p	82p
28 pin	19p	98p
40 pin	28p	135p
Professional ZIF sockets:		
24 pin 430p	28 pin 480p	
40 pin 585p		

COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. **WAV 5% Resistor kit.** Contains 10 of each value from 4.7 ohms to 1M (total of 650 resistors). **Ceramic Cap. kit.** 5 of each value - 22p to 0.01uF (135 caps) - 530 **Polyester Cap. kit.** 5 of each value from 0.01 to 1uF (85 caps) - 575 **65 presets.** 65 of each value from 100 ohms to 1M (total) - 425 **Nut and Bolt kit (total 300 items):** 180p
50 6BA washers 50 6BA nuts
25 6BA 1/2" bolts 25 6BA 1/4" bolts
50 6BA nuts 50 6BA washers

TRANSISTORS

AC125	35	BC168	11	BC558	10	BFR40	23	2N1613	30	2N3906	10	ZN459	285
AC126	30	BC169	10	BC559	10	BFR81	23	2N2219A	25	2N4057	45	ZN1034C	200
AC127	30	BC169	10	BC560	10	BFR82	30	2N2221A	25	2N4060	10	TIP36C	125
AC128	30	BC169	10	BC561	10	BFR83	30	2N2222A	25	2N4061	10	TIP36C	130
AC176	25	BC168C	10	BC562	10	BFR84	30	2N2368	25	2N4062	10	TIP36C	130
AC187	25	BC169C	10	BC563	10	BFR85	30	2N2369	18	4036	40	TIP41A	45
AC188	25	BC170	10	BC564	10	BFR86	30	2N2484	27	4036	50	TIP42A	45
AD142	120	BC171	10	BC565	10	BFR87	30	2N2646	60	4036	50	TIP120	60
AD161	42	BC172	8	BC566	10	BFR88	30	2N2904	28	40408	50	TIP121	60
AD162	42	BC177	16	BC567	10	BFR89	30	2N2904A	28	2N4547	30	TIP122	60
AF124	60	BC178	16	BC568	10	BFR90	30	2N2905	28	2N4548	30	TIP141	110
AF126	50	BC179	18	BC569	10	BFR91	30	2N2905A	28	2N4549	30	TIP142	120
AF139	40	BC182	10	BC570	10	BFR92	30	2N2906	28	2N4585	35	TIP147	120
AF186	70	BC182L	10	BC571	10	BFR93	30	2N2906A	28	2N4597	45	TIP2955	70
AF239	55	BC183	10	BC572	10	BFR94	30	2N2907A	28	2N4698	40	TIP3055	60
BC107	10	BC183L	10	BC573	10	BFR95	30	2N2926	28	2N4704	20	TIS43	40
BC107B	12	BC184	10	BC574	10	BFR96	30	2N3054	28	2N4705	25	TIS44	45
BC108	10	BC184L	10	BC575	10	BFR97	30	2N3055	55	2N4706	35	TIS45	45
BC108A	12	BC212	10	BC576	10	BFR98	30	2N3055A	55	2N4707	35	TIS46	45
BC108C	12	BC212L	10	BC577	10	BFR99	30	2N3056	55	2N4708	35	TIS47	45
BC109	10	BC213	10	BC578	10	BFR100	30	2N3056A	55	2N4709	35	TIS48	45
BC114	22	BC214	10	BC579	10	BFR101	30	2N3057	55	2N4710	35	TIS49	45
BC115	22	BC214L	10	BC580	10	BFR102	30	2N3058	55	2N4711	35	TIS50	45
BC117	22	BC237	10	BC581	10	BFR103	30	2N3059	55	2N4712	35	TIS51	45
BC119	35	BC238	10	BC582	10	BFR104	30	2N3060	55	2N4713	35	TIS52	45
BC137	40	BC308	10	BC583	10	BFR105	30	2N3061	55	2N4714	35	TIS53	45
BC139	38	BC327	12	BC584	10	BFR106	30	2N3062	55	2N4715	35	TIS54	45
BC140	29	BC328	12	BC585	10	BFR107	30	2N3063	55	2N4716	35	TIS55	45
BC141	30	BC337	12	BC586	10	BFR108	30	2N3064	55	2N4717	35	TIS56	45
BC142	28	BC338	12	BC587	10	BFR109	30	2N3065	55	2N4718	35	TIS57	45
BC143	30	BC477	22	BC588	10	BFR110	30	2N3066	55	2N4719	35	TIS58	45
BC147	10	BC478	22	BC589	10	BFR111	30	2N3067	55	2N4720	35	TIS59	45
BC148	10	BC479	22	BC590	10	BFR112	30	2N3068	55	2N4721	35	TIS60	45
BC149	10	BC517	30	BC591	10	BFR113	30	2N3069	55	2N4722	35	TIS61	45
BC157	11	BC547	10	BFR114	30	BFR114	30	2N3070	55	2N4723	35	TIS62	45

RESISTORS

Carbon film	1p	25+
1/2W 5% 4.7ohm - 10M	2p	1p
1/2W 5% 4.7ohm - 4M7	3p	2p
Metal film		
1/2W 1% 10ohm - 1M	4p	3p
25% price applied to 25+ per value not mixed.		

TTL

7401	25	7440	25	7476	40	74107	40	74157	80	74180	85
7402	36	7442	74	7480	50	74109	60	74160	90	74181	230
7403	25	7444	105	7483	65	74121	50	74161	90	74182	85
7404	25	7416	43	7446	130	7485	110	74122	50	74183	120
7405	25	7417	43	7447	98	7486	110	74123	50	74184	120
7406	25	7420	48	7448	99	7487	110	74124	50	74185	120
7407	25	7421	30	7450	25	7490	55	74125	50	74186	110
7408	25	7422	30	7451	25	7491	80	74126	50	74187	110
7409	25	7423	30	7452	25	7492	55	74127	50	74188	110
7410	25	7424	30	7453	25	7493	55	74128	50	74189	120
7411	25	7425	30	7454	25	7494	55	74129	50	74190	120
7412	25	7426	30	7455	25	7495	55	74130	50	74191	120
7413	25	7427	30	7456	25	7496	55	74131	50	74192	120
7414	25	7428	30	7457	25	7497	55	74132	50	74193	110
7415	25	7429	30	7458	25	7498	55	74133	50	74194	80
7416	25	7430	30	7459	25	7499	55	74134	50	74195	120
7417	25	7431	30	7460	25	7500	55	74135	50	74196	120
7418	25	7432	30	7461	25	7501	55	74136	50	74197	120
7419	25	7433	30	7462	25	7502	55	74137	50	74198	120
7420	25	7434	30	7463	25	7503	55	74138	50	74199	120
7421	25	7435	30	7464	25	7504	55	74139	50	74200	120

CMOS

4001	18	4019	35	4040	46	4050	70	4085	60	4503	45	4532	60
4002	18	4020	48	4041	46	4051	70	4086	60	4504	45	4533	60
4003	18	4021	55	4042	45	4052	70	4087	60	4505	45	4534	60
4004	18	4022	60	4043	45	40							

EDITORIAL

In this issue, we have two projects that are the direct result of examinations in electronics. On page 50, Giles Read's 'Video Vandal' was made as the practical component for an 'A'-level electronics course; and on page 77, Damon Hart-Davies' 'Perpetual Pendulum' was the result of the requirements of an 'AO' syllabus.

These two projects are quite different, in complexity and in purpose. Yet there is one factor in common: both authors have used a lot of skill and resourcefulness to get the electronics to do what they want. Both authors spent a long time developing their own circuitry finding that at first it didn't work as intended, then modifying and trying again until the darned project did what it was meant to do.

This is the fundamental process of electronics: design a circuit to do the job, build it, try it out, and when it doesn't work (how many circuits *do*, first time?) find out why and modify. Without learning how to diagnose faults and design around them, we don't see how anyone can fully understand electronics.


Because of this, we are deeply worried by a growing tide of technical enquiries from people who are building ETI projects as part of their 'O', 'AO' or 'A'-level or 'Tech' course. We fail to see what anyone can gain from following someone else's footsteps so closely, even if they *do* understand the circuit they are building. However, the person who comes to us for advice frequently does not understand the circuit sufficiently to do the debugging and to pick up the odd error that has slipped past the ETI editorial team. Even more worrying, it's quite often painfully apparent that the person teaching them doesn't understand the circuit either.

The introduction of electronics into schools and colleges is something that should have happened many years ago; better late than never, but better even later than not properly. We are most concerned at the toleration — even encouragement — of some examining boards of non-original course work. The whole objective of electronics is the designing and building of circuits and we cannot see how anyone should be allowed to pass an examination in electronics if they haven't partaken, even in the smallest way, in this central activity.

Finally, a word to our older readers: don't worry, the 'editorial' spot will not be a permanent feature of the magazine. We'll only be using it when we have something we think worth saying.

ETI

DIGEST

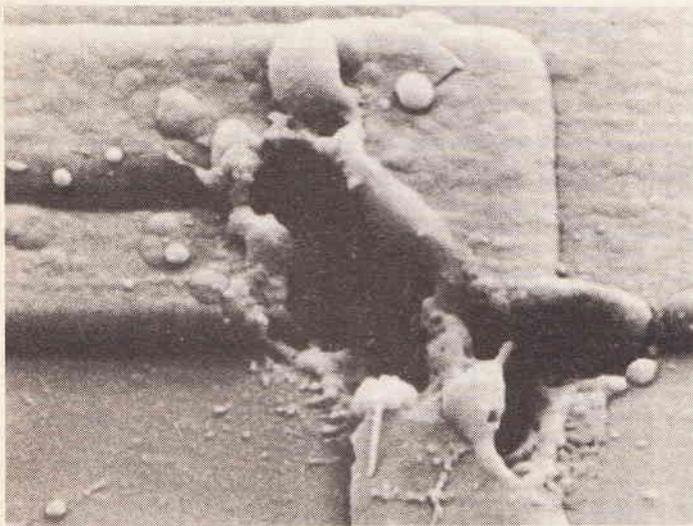

Zap Your Silicon!

The above electron micrograph is of a portion of an 8085 IC's surface after it has been zapped with a simulated static discharge. It shows just what damage static can do to ICs.

The picture was supplied by Hartley Measurements Ltd, who are marketing a new computer-controlled unit which will test for devices' sensitivities to controlled static discharges. The unit can administer varying pulses, up to a maximum of 4kV with a rise-time of 15ns, and then, using a built-in curve plotter, display an analysis of the characteristics of every pin before, during and after the test.

The unit in question is called the Autozap 200RD, and Hartley say that it makes the measurement of static sensitivity faster and more accurate than ever before. Hartley Measurements Ltd, Unit 4, Bear Court, Daneshill East, Basingstoke, Hampshire RG24 0QT, tel 0256 56695.

What's This Ear?

Cirkit have branched out into computing with the collaborative launch of a low-cost and potentially world-beating acoustic modem; their partners in the enterprise are Protek Computing Limited, the home computer product marketing and development specialists.

When they claim low cost, these chaps really mean it — the final price in the shops will be £59.95 for the modem, which will need a standard RS232 interface to drive it. However, do not despair if your micro doesn't have RS232; Cirkit and Protek will be marketing a range of adaptors, and Spectrum, BBC B and Commodore 64 versions will be available with appropriate software from the launch date. Prices are £24.95 for the Spectrum version and £14.95 for the other two.

The modems will be made by Cirkit and marketed by Protek. Although the unit was designed by Cirkit in what must be record time — six months from initial design to full-scale production and marketing — the idea was hatched by both companies together, apparently due to them by chance occupying adjacent stands at a trade fair.

The modem is seen as one in a series of collaborative projects between the two companies, although they were keeping tight-lipped about what any of the future projects might have been. However, they do seem to have perceived a need in the home computer market for products that make it possible for home computers to be used for more serious applications than games playing.

The modem will enable computer users to use the telephone network to access data bases such as Micronet, Prestel and BT Gold, to exchange software and messages with other users, to send telexes and to use electronic mail services. It can be used to transmit signals to the 1200/75 baud international standard. It can also operate on 1200/1200, software selected.

Cirkit say that their position as a major supplier of specialist items to trade and amateur markets put them in a very strong position for the development of this device. They were able to obtain and incorporate the very latest in ICs, well ahead of their rivals. This combined with the speed of the designing and marketing mean that if the Cirkit/Protek partnership can continue to deliver, they should become a formidable combination. Uncle Clive look out!

FPLAs Come To Town

Texas Instruments have announced two field-programmable logic arrays (FPLAs) providing the highest performance available — propagation delays of 20 nanoseconds maximum/10 ns typical — and supplied in compact, 24-pin, 300-mil packages. By comparison, other 20- and 28-pin FPLAs offer propagation delays of 30ns maximum/20ns typical and 50ns maximum/35ns typical, respectively, and only the 20-pin device is supplied in a space-saving package. The TIFPLA839 (three-gate outputs) and TIFPLA840 (open-collector outputs) have 14 inputs, 32 product terms and six outputs. Output polarity is programmable.

These sorts of devices are used as high-speed, datapath logic replacements. In most applications, designers use field-programmable logic to fill the gap between SSI/MSI catalogue (eg TTL) logic devices and large-scale integration (LSI) and gate arrays. Like programmable array logic devices, FPLAs are used primarily as random logic replacements to "glue" together system building blocks. They are used in applications including minicomputers and superminicomputers, peripherals, professional computers and automated office equipment.

The basic FPLA logic structure is a programmable-AND array which feeds a programmable-OR

array. This configuration provides greater programming flexibility than widely used PAL devices. The FPLAs use a titanium-tungsten (TiW) fuse technology developed at TI in 1970 to improve programming reliability. Proven TiW construction essentially eliminates the tendency of a blown fuse to grow back by insulating it with a layer of titanium oxide.


The TIFPLA830 and TIFPLA840 are fabricated in an oxide-isolated Advanced Schottky technology to provide 20ns maximum performance. Each device consumes 180 milliamps maximum.

The TIFPLA839 and TIFPLA840 operate from a single 5V (+/-5%) supply. The devices will be available from TI and authorised distributors towards the end of this year. Military-temperature range versions, designated with an "M" suffix, will be available later. Texas Instruments Limited, Manton Lane, Bedford, MK41 7PA, tel 0234 63211.

Digital Cassette Deck

Our resident gnome still managed yet another boohoo, this time leaving off the supplier for the deck of the digital cassette deck. The supplier is, in fact, Cirkit (formally Ambit), the order code is 72-03600, and the price is £38.00 plus VAT plus P&P. Unfortunately, Cirkit inform us that they are out of stock but they will have plenty in a month or so! Cirkit Holdings PLC, Park Lane, Broxbourne, Hertfordshire, tel 0992 444111.

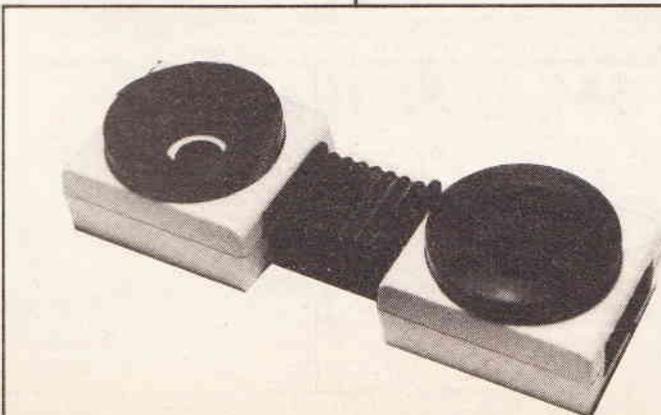● Hah! The cheek of it! Marshall's of 85 West Regent Street, Glasgow G2 2AW (tel 041 332 4133) have used an illustration from *Elektron* on the front cover of their new catalogue. And they dare to charge 75p for it! Well, we shan't give them a mention, shall we?



COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished **DIABLO/DRE** series 30 2.5 Mb disk drives. **DEC RK05, NOVA, TEXAS** compatible.
Front load. Free stand or rack mount £559.00
Exchangeable type (via lid removal) £795.00
me3029 PSU unit for 2 drives £173.00
DIABLO/DRE 44-4000A/B 5+5 ex stock from £995.00
1000's of spares for S30, 4000, 3200, HAWK ex stock.
Plus in house repair, refurbishing service
Call for details or quotation.

EX STOCK INTEGRATED CIRCUITS

OVER 100,000 ITEMS INCLUDING:
Intel D8085AH-2 £25.00 D8271 £65.00
D8202 D8257-5 8255 D3002
2732 EPROM SPECIAL fully guaranteed
450ns £3.75, 350ns £4.00, 300ns £4.50

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 69XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.
GOULD JB-SAR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £6.95** £12.95 complete with data.
BUHLER 69.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. **OUR PRICE ONLY £12.95** complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

DUAL 5" DISK DRIVES

Current, quality, professional product of a major computer company, comprising 2 x 40 track MPI or Shugart FULLY BBC COMPATIBLE single sided drives in a compact, attractively styled, grey ABS structured case with internal switched mode PSU. The PSU was intended to drive both drives and an intelligent 280 controller with over 70 i.c's. The controller has been removed leaving ample space and current on the +, -5, +12 and -12 supply for all your future expansion requirements. Supplied tested with 90 day guarantee in BRAND NEW condition with cable for BBC micro. Ex Stock at only **£259.00** + £10.00 carr. Limited Quantity Only

GE TERMIPRINTER

A massive purchase of these desk top printer terminals enables us to offer you these quality 30 cps printers at a SUPER LOW PRICE against their original cost of over £1000. Unit comprises of full QWERTY electronic keyboard and printer mech with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case, standard RS232 serial interface, internal vertical and horizontal tab settings, standard ribbon adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working **£130.00** or untested **£85.00**, optional floor stand £12.50 Carr & Ins £10.00.

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 20-1 Compact unit for use with MICRONET, PRESTEL or TELECOM GOLD etc. 2 wire direct connect. 75 baud transmit 1200 baud receive. Data i/o via RS232 'D' socket. Guaranteed working with data **£99.95**
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit **£130.00**
TRANSDATA 307A 300 baud acoustic coupler RS232 i/o **£95.00** brand new. **£4.50**
NEW DSI L2123 Multi Standard modem selectable V21 300-300 bps, V23 75-1200, V23 1200-75 full duplex. Or 1200-1200 half duplex modes. Full auto answer via modem or CPU. LED status indicators. CALL or ANSWER modes Switchable CCITT or BELL 103 & 202. Housed in ABS case size only 2.5" x 8.5" x 9". **£286.00** + VAT
For further data or details on other EX STOCK modems contact sales office.
Carriage on all modems £10.00 + VAT.

HOT LINE DATA BASE

DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base. 1000's of stock items and one off bargains. ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity. **01-679 1888**

STILL IN STOCK

FP1500 Heavy Duty 25 cps daisy wheel RS232 interface, bi directional printers, Brand New at **£499.00**
CALL FOR MORE DETAILS

SAVE £250

SUPER PRINTER SCOOP

BRAND NEW CENTRONICS 739-2



ONLY £199

The "Do Everything Printer" at a price that will NEVER be repeated. Standard CENTRONICS parallel interface for direct connection to BBC, ORIC, DRAGON etc. Superb print quality with full pin addressable graphics and 4 type fonts plus HIGH DEFINITION internal PROPORTIONAL SPACED MODE for WORD PROCESSOR applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available ONLY from DISPLAY ELECTRONICS at the ridiculous price of **ONLY £199.00** + VAT. Complete with full manual etc. Limited quantity - Hurry while stocks last.
Options: Interface cable (specify) for BBC, ORIC, DRAGON or CENTRONICS 36 way plg £12.50. Spare ribbon £3.50 each BBC graphics screen dump utility program £8.60. Carriage and Ins. £10.00 + VAT

SPECIAL 300 BAUD MODEM OFFER

Another GIGANTIC purchase of these EX BRITISH TELECOM, BRAND NEW or little used 2B data modems allows us to make the FINAL REDUCTION, and for YOU to join the exciting world of data communications at an UNHEARD OF PRICE OF **ONLY £29.95**. Made to the highest POST OFFICE APPROVED spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!

- 300 baud full duplex
- Full remote control
- CCITT tone standards
- Supplied with full data
- Modular construction
- Direct isolated connection
- CALL, ANSWER and AUTO modes
- Standard RS232 serial interface
- Built in test switching
- 240v Mains operation
- 1 year full guarantee
- Just 2 wires to comms. line

NOW ONLY £29.95

Order now - while stocks last. Carriage and Ins. £10.00

8" 19MB WINCHESTER DISK DRIVE

Made in the UK by a subsidiary of the World's largest disk drive manufacturer. This BRAND NEW "end of line" unit offers an outstanding opportunity to add a MASSIVE 19 mb of storage to your computer system. Superbly constructed on a heavy die cast chassis the DRE 3100 utilises 3 x 8" platters in a dust free cavity. All drive functions are controlled by microprocessor electronics using an INTEL 8035 cpu and TTL support logic. Data to the outside world is via two comprehensive 8 bit TTL level bi directional data buses with full status reporting for ease of interfacing. Many features such as Av. seek time 35 ms, 512 bytes per sector, +24, -24 and +5 v DC supply, plug in card system, and compact size of approx. 19cm H x 21cm W and 42cm D etc, etc, make this item a real snip.

Units are BRAND NEW and BOXED and sold at a FRACTION of original cost - hence unguaranteed. Complete with 150 page manual, circuits and applications guide.

ONLY £225.00 Carriage £10.00

Suitable power supply unit - sold ONLY with drive £39.95.

PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great QWERTY, full travel, chassis keyboard offer at fractions of their original costs.
ALPHAMERIC 7204/80 full ASCII 60 key, upper, lower + control key, parallel TTL output plus strobe. Dim 12" x 6" +5 & -12 DC. **£39.50**
DEC LA34 Uncoded keyboard with 67 quality, GOLD, normally open switches on standard X, Y matrix. Complete with 3 LED indicators & i/o cable - ideal micro conversions etc. pcb DIM 15" x 4.5" **£24.95** Carriage on keyboards £3.00.

66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Caps, PCB's, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the 'BARGAIN PARCEL OF A LIFETIME'. Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.
2.5kls **£4.25** + pp **£1.25** 5kls **£5.90** + **£1.80**
10kls **£10.25** + pp **£2.25** 20 kls **£17.50** + **£4.75**

ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies **£20.00**. Where post and packing not indicated please add **£1.00**. + VAT. Warehouse open Mon-Fri 9.30 - 5.30, Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only **£49.95** + Carr. Dim 19" high 16" deep 10.5" high. Useable area 18" w 10.5" h 11.5" d. Also available LESS PSU, with FANS etc. Internal dim. 19" w 16" d 10.5" h. **£19.95** Carriage & insurance **£9.50**.

BUDGET RANGE

VIDEO MONITORS

At a price YOU can afford, our range of EX EQUIPMENT video monitors defy competition!! All are for 240v working with standard composite video input. Units are pre tested and set for up to 80 col use on BBC micro. Even where MINOR screen burns MAY exist - normal data displays are unaffected.

1000's SOLD TO DATE

- 9" HITACHI Very compact fully cased, dim. 21cm H x 21cm W x 22cm D. Black and white screen **£44.95**
- 12" KGM 320-321, high bandwidth input, will display up to 132 columns x 25 lines. Housed in attractive fully enclosed brushed alloy case. B/W only **£32.95** GREEN screen **£39.95**
- 24" KGM large screen black & white monitor fully enclosed in light alloy case. Ideal schools, shops, clubs etc. **ONLY £55.00**

14" BRAND NEW Novex COLOUR type NC1414-CL. Many exacting features such as RGB TTL and composite video input, GREEN TEXT key, internal speaker and audio amp. Even finished in BBC micro matching colours. Fully guaranteed. **ONLY £199.00**

Carriage and ins on ALL videos **£10.00**

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s, triacs, diodes, bridge recs, etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed, 50+ **£2.95** 100+ **£3.15**.
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ **£4.90** 200+ **£12.30** 300+ **£19.50**

EX STOCK DEC CORNER


- BA11-MB 3.5" Box, PSU, LTC **£385.00**
- DH11-AD 16 x RS232 DMA interface **£210.00**
- DLV11-J 4 x EIA interface **£310.00**
- DUP11 Sych. Serial data i/o **£650.00**
- DZ11-B 8 line RS232 mux board **£650.00**
- LA36 Decwriter EIA or 20 ma loop **£270.00**
- LAXX-NW LA180 RS232 serial interface and buffer option **£130.00**
- LAX3-AL LA34 tractor feed **£85.00**
- MS11-JP Unibus 32 kb Ram **£80.00**
- MS11-LB Unibus 128 kb Ram **£450.00**
- MS11-LD Unibus 256 kb Ram **£850.00**
- MSC4804 Qbus (Equip MSV11-L) 256 kb **£499.00**
- PDP11/05 Cpu, Ram, i/o, etc. **£450.00**
- PDP11/40 Cpu, 124k MMU **£1850.00**
- RT11 ver. 3 Bp documentation kit **£70.00**
- RK05-J 2.5 Mb disk drives **£650.00**
- KLBJA PDP 8 async i/o **£175.00**
- MISE PDP 8 Bootstrap option **£75.00**
- VTDU VDU and Keyboard - current loop **£175.00**

1000's of EX STOCK spares for DEC PDP8, PDP8A, PDP11 systems & peripherals. Call for details. All types of Computer equipment and spares wanted for PROMPT CASH PAYMENT.

DISPLAY ELECTRONICS

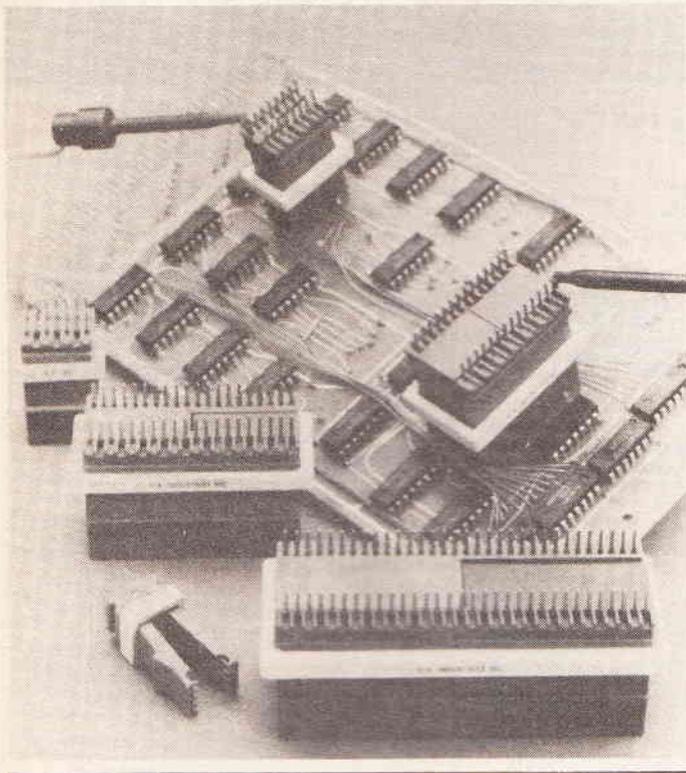32 Biggin Way, Upper Norwood, London SE19 3XF
Telephone 01-679 4414 Telex 27924





Stressless IC Clip

OK Industries' new 'Chip-Clip' IC test clip attaches by means of a snap action locking ring which simply slides down and snaps gently into the closed position for reliable positive contact.

OK say that the result is no stress to the IC because the clip spring is loaded in an outward, rather than inward, direction. Spacing in the open position is just enough to allow it to slide over the IC.

Clip contacts are gold plated and bodies are high dielectric nylon. The units are available in 8, 14, 16, 24-28, 36-40 and 64 pin sizes or in a kit form with the most commonly used sizes in a handy carrying case. OK Industries UK Ltd, Dutton Lane, Eastleigh, Hants SO5 4AA tel: 0703 619841.

Gauge Your CRT

EMCO Electronics, Britain's largest supplier of data CRTs has recently introduced a simple defects control gauge to allow engineers to measure faults on cathode ray tubes.

EMCO Electronics will be pleased to send one of these, free of charge, to engineers on request.

EMCO say that they distribute Britain's widest range of CRTs, from Fivre and VTM, as well as data display kits and monitors from Indesit. EMCO Electronics, Unit 1, 129/131 Coldharbour Lane, Camberwell, London SE5 9NY, Tel: 01-737 3333.

● Brunel Computer Club will be at the Home Tech '84 Exhibition, October 26-29, Bristol Exhibition Centre, and they will be displaying several Cortex computers (ETI, Nov 1982 et seq), and will be holding a Cortex surgery — all advice and help free of charge.

Ceramics Get Smaller

Breaking the size barrier are two new series of multilayer ceramic capacitors from G. English Electronics. Constructed using newly-developed techniques, these highly compact multilayer types are claimed to be ideally suited to applications in which film capacitors are conventionally used.

The X5T and Y5V series of multilayer ceramic capacitors, manufactured by NEC, are produced using a new, low-temperature fired technology and high dielectric-constant material. The ceramic formulation and processing techniques employed have enabled the introduction of these compact multilayer ceramic capacitors to meet application requirements normally satisfied by the more bulky film capacitor type.

Series X5T is available in preferred values from 0.001 to 1.5uF, $\pm 10\%$ or $\pm 20\%$, at voltage ratings of 25, 50 and 100V DC. The series has good frequency characteristics, offers high reliability and high volumetric efficiency. The Y5V series may be supplied in preferred values from 1000pF to 4.7uF, at voltage ratings of 25V DC or 5V DC. The Y5V features an extremely high capacitance-to-volume ratio and low impedance at high frequencies, and is intended principally for bypass applications.

Both series of capacitor may be supplied taped, for automatic assembly, or individually, and both can withstand flow soldering. G. English Electronics Ltd, 34 Bowater Road, Woolwich, London SE18 5ST, tel: 01-855 0991.

Amateur Licence Changes

When they come to re-new their licences, the 55,000-odd radio amateurs (many of whom read ETI, and one of whom edits ETI) will notice some changes.

In fact the main change is cosmetic: the schedule, or table of frequencies available for use, is being tidied up to make it easier to see what frequencies are available for what sort of transmission, and whether amateurs have primary or secondary status on the band concerned.


However, there are a couple of non-cosmetic changes tucked away in the small print. The first is the transfer of functions of the Radio Interference Service from British Telecom to the Department of Trade and Industry; this is simply a reflection of an adminis-

trative change that has already taken place, presumably as part of the preparations for the sale of British Telecom.

The second change removes the restriction on the codes that can be used for radio teleprinter (RTTY) — up until now, amateurs have only been allowed to use International Telegraph Code No 2 with transmission speeds of 45.5 or 50 baud.

The second issue of the Anglia consumer wallchart is now available free of charge and features many new items. These include a new range of teletext ICs, an extended audio IC range and also a competitively priced universal tripler. Anglia consumer say that they ensure that all orders received before 4.00 p.m. are despatched the same day with Access/Visa credit cards readily accepted. For your free copy, contact Anglia Consumer, Burdett Road, Wisbech, Cambs., PE13 2PS, tel: 0945 63281.

A Case For Fingers

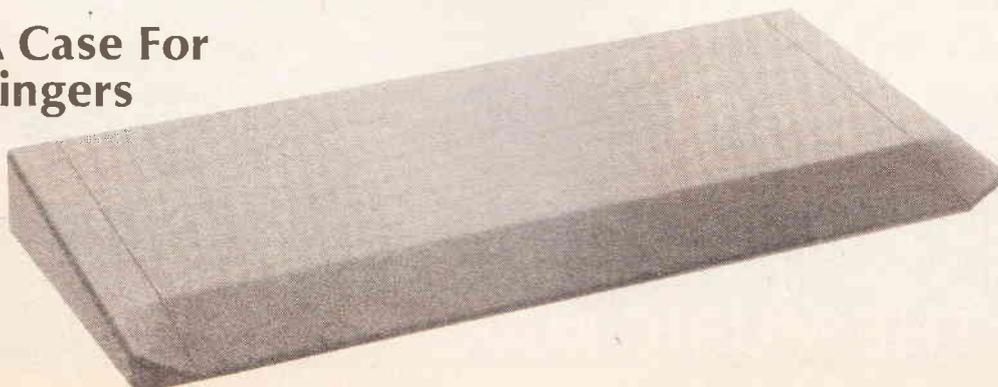

A slim, modern design characterises the new 'Manta' keyboard case available from West Hyde.

It is moulded in beige ABS and incorporates a shallow ledge at the front to provide a hand rest for the keyboard operator. The case has moulded bosses to support a PCB and cable clamps for both circular and ribbon cables. The base plate is zinc steel which aids rigidity and provides extra weight to prevent unintentional movement.

The Manta keyboard case is available in three widths from West Hyde and is supplied complete with a cable grommet, feet and screws. West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET, tel 0296 20441.

HI-FI
TV
VIDEO

HY-TEK ELECTRONICS

DISCO
IN-CAR
CB

Discomixer Phonic 6050

- ★ 2 mag deck i/p
- ★ 2 line i/p
- ★ 1 mic i/p
- ★ 7 band graphic
- ★ twin vu meter
- ★ headphone monitor
- ★ mic over ride
- ★ mains operated



£124.98

pb p 2.50

Discomixer Phonic MX7700

- ★ 2 mag deck i/p
- ★ 2 switchable mic/line inputs
- ★ 5 band graphic
- ★ led vu meters
- ★ cross-fade
- ★ separate record output
- ★ mains operated



£109.98

pb p 2.50

Discomixer Phonic SM 501

- ★ Full headphone monitor
- ★ 2 x line i/p
- ★ 2 x mag deck i/p
- ★ 1 x mic i/p
- ★ twin vu meters
- ★ mains operated




£44.98

pb p 2.00

Howland & West MX950 Microphone Mixer

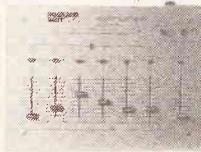- ★ six mic i/p's
- ★ stereo line i/p
- ★ headphone monitor
- ★ stereo/mono sw
- ★ master fader
- ★ mains operated




£65.98

pb p 2.00

Howland & West MX850 Stereo Graphic Equaliser

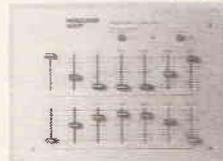- ★ 7 bands/channel
- ★ 12db boost or cut
- ★ tape monitor button
- ★ mains operated



£65.98

pb p 2.00

Phonic EQ1005 Stereo Graphic Equaliser

- ★ 5+5 equaliser bands
- ★ led vu meters
- ★ tape monitor
- ★ meter level controls
- ★ connections by phono plugs



£44.98

pb p 2.00

DEI Analog Echo Machine

- ★ BBD echo system
- ★ mic i/p
- ★ line i/p
- ★ foot switch skt
- ★ output attenuator
- ★ peak led
- ★ mains operated



£79.98

pb p 2.50

MC350 E Tape Echo

- ★ using endless loop tape cassette
- ★ high & low i/p
- ★ high & low o/p
- ★ echo balance control
- ★ 300ms delay
- ★ foot switch skt



£69.98

pb p 2.00

Echo Microphone

- ★ echo volume control
- ★ echo on/off
- ★ battery operated
- ★ 10ft cable
- ★ vinyl carrying case




£34.98

pb p 2.00

Digital Sound Effects Unit

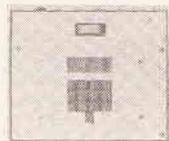- ★ over 30 effects including ★ gunshot ★ bomb drop ★ organ ★ piano ★ machine gun ★ plus many others ★ mains operated




£99.98

pb p 2.50

Cassette Recorder for VIC20/64

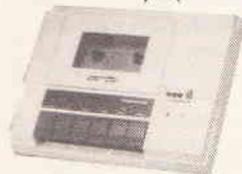- ★ pre set levels
- ★ save led
- ★ simple operation
- ★ plugs direct into VIC20/64
- ★ tape counter



£29.98

pb p 2.00

Electronic Reverb

- ★ BBD delay system
- ★ mic i/p
- ★ line i/p
- ★ battery operated
- ★ slide control
- ★ 95ms delay



£29.98

pb p 2.00

250W Power Amp

- ★ 125w per channel into 4ohms ★ 20-20kHz frequency response ★ open & Short circuit proof ★ cannon i/p & o/p ★ level control for each channel x twin vu metres ★ 19" rack mount



£169.98

pb p 5.00

400W MOS-FET Power Amp

- ★ 2 x 200W ★ 5Hz to 30KHz + 1 db frequency response
- ★ latest mosfet technology ★ twin o/p meters ★ fully short circuit proof x 19" rack mount



£234.98

pb p 5.00

700W Power Amp

- 2 x 350W/channel into 4 ohms ★ 20Hz to 20KHz frequency response ★ cooling fan ★ cannon i/p + o/p connectors ★ twin vu meters.



£324.98

pb p 5.00



48 Dalston Lane,
London, E8
Tel 01-249 4814
Open 10am to 6pm Mon-Fri
9.30am to 5.30pm Sat

FOR MAIL ORDER

ALL OFFERS ARE SUBJECT TO AVAILABILITY

For mail order just add postage and packing (all prices include VAT) and send PO. Cheque made payable to Hy Tek Electronics or phone stating Access Barclaycard Number (Dalston address)

TRADE ENQUIRIES WELCOME

THE MUSIC MAKERS

TAKE ADVANTAGE
OF THE HY-TEK
PRICE POLICY

Superkit II — Not The Movie


Superkit II is the second in the practical digital electronics Superkit series from Cambridge Learning. It consists of a dual instruction manual, written for use with both the Eurobreadboard and the GSC EXP300 breadboard, and a set of components in a plastic wallet. The components and breadboard from the first Superkit are also required to complete all the circuits.

The components in the kit include resistors, capacitors, a seven-segment LED display, integrated circuits, and wire.

Superkit II explains how to design and use: adders; subtractors; counters (ripple, up/down, synchronous, decade, and Gray code); registers; pattern recognisers; and seven-segment displays.

Cambridge Learning say that the practical kit is backed up by their theory course, Digital Computer Design.

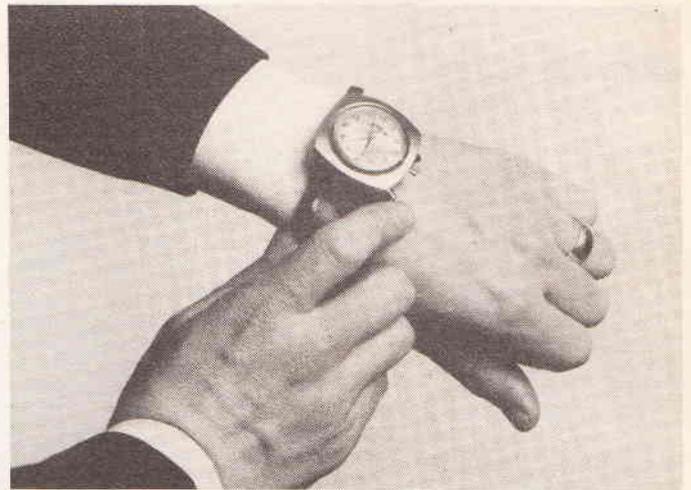Superkit II costs £16.00 Superkit costs £22.00 or both kits together are £35.00, (all prices inc. VAT and p&p) and can be ordered direct from: Cambridge Learning Ltd, FREEPOST, Unit NR, Rivermill Site, St Ives, Huntingdon, Cambridgeshire PE17 4BR. Telephone orders from credit card holders can be accepted on 0480 67446.



Life-Saving Timepiece

The watch on this man's wrist is much more than a timepiece. It could save his life.

In an emergency, a tiny circuit inside the wrist-watch can trigger a miniature radio device which either transmits a warning signal to a matching receiver in a neighbour's house, or automatically dials up the number of a 24-

hr monitoring service. The unit can also be housed in a decorative pendant to be worn round the neck.

This valuable security device for elderly or housebound people is manufactured by Emerald Electronics Ltd of Alnwick. The printed circuit board, no more than an inch square, is made by BT-approved contractors GSPK (Circuits) Ltd, Manse Lane, Knaresborough, N. Yorks HG5 8LF, tel: 0423 865641.

VDU Look- Alike LCD Controller

Norbain Displays Limited, the UK's leading specialist distributor of visible components, has launched a single chip graphics LCD controller designed to make graphic LCDs compatible with standard VDU applications in terms of the facilities available. "What a good idea", you might say, as we did here at ETI/



Manufactured by Epson in Japan and designated the E1330, the device is capable of receiving and interpreting all control commands and data from the 8080 and 68000 family microprocessors. The E1330 controller chip has been designed specifically to enable graphics LCD panels to directly replace VDUs in most typical applications.

The E1330 uses scrolling and layered functions to reproduce data stored in the display memory

as diverse graphics on an LCD. As a complete LCD control circuit, it frees the main processing unit from all display tasks while providing features like standard text, using a built-in character generator, graphic text, inverse, underline, graphics, simple animation and flexible scrolling.

The device features a character display mode with 80 characters per line and 16 lines per screen, flexible scrolling by page or partial page, a two-screen layered function with reverse characters and underline and an internal and external character generation capability as well as a graphic display mode of 640 x 256 dots with a layered function of up to three screens.

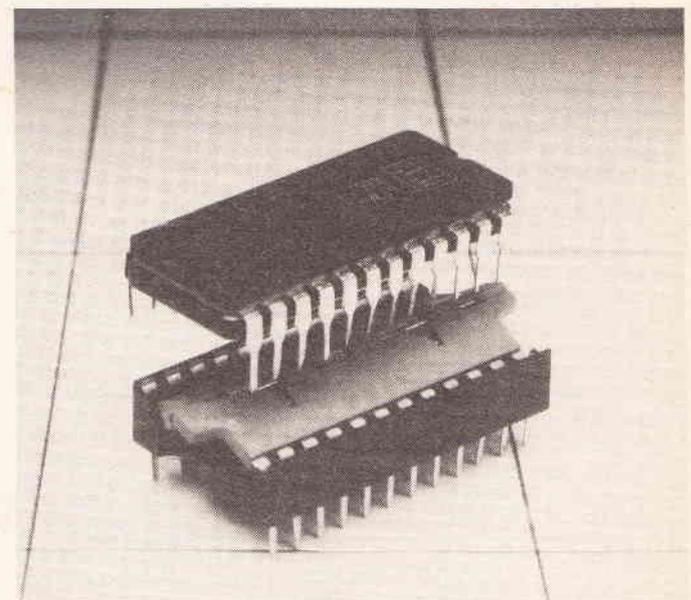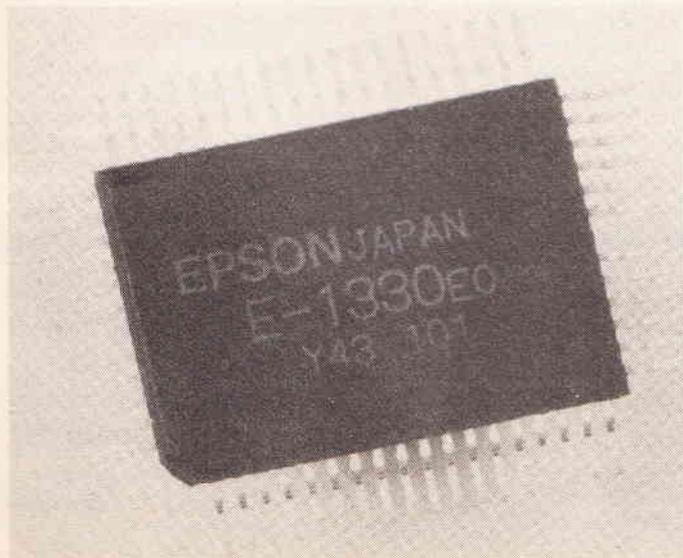Other features include a 64K display memory, an 8 bit parallel interface, high speed CMOS LSI and a clock rate of 6MHz all operating on a single 5V power supply. Norbain Displays Ltd, Norbain House, Boulton Road, Reading, Berkshire RG2 0LT, tel 0734 864411.



New Style ZIF Sockets

No force is required to insert or remove ICs from Dage's new ZIF series IC socket range. The sockets have a hinged base with fingers that protrude by approximately 1.5 mm at either end. After the IC is inserted, a little pressure on these fingers cause the hinge to click over, locking the IC's legs in place.

Four versions are available, for

ICs with 24-, 28-, 40- or 48-pins. All are low-profile style with a height of 5 mm. The contacts are made of copper-beryllium with either tin-lead or selective gold plating according to order.

The sockets are stackable, side-to-side, for high density PCB layouts. A lead-in entry point ensures easy IC insertion, with the point of contact located 0.8 mm from the top of the socket. Dage Eurosem, Rabans Lane, Aylesbury, Bucks HP19 3RG, tel 0295 33200. Telex: 83518.

OMP POWER AMPLIFIER MODULES

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.



OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV a 10K, Size 360 x 115 x 72mm. PRICE £32.99 + £2.50 P&P.



OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £2.50 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. PRICE £79.99 + £4.50 P&P.

Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 LED diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order — Standard or P.A.



19" RACK CASED MOS-FET STEREO AMPLIFIERS with twin power supplies and LED Vu meters plus XLR connectors. Prices on application.

LOUDSPEAKERS

5 to 15 INCH Up to 300 WATTS R.M.S. All speakers 8 ohm Impedance.



POWER RANGE
8" 50 WATT R.M.S. Hi-Fi/Disco.
 20 oz. magnet. 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £9.90 Available with black grille £10.90. P&P £1.50 ea.
12" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £26.00 - £3.00 P&P ea.
15" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 20Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. PRICE £34.00 - £3.00 P&P ea.

McKENZIE
12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco.
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £24.99 + £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £24.99 - £3.00 P&P ea.
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £49.99 - £4.00 P&P ea.

WEM
5" 70 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £20.00 - £1.50 P&P ea.
8" 150 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £27.00 - £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £30.00 - £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £38.00 - £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)
5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £8.99 + £1.00 P&P ea.
6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £9.99 + £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £11.99 + £1.50 P&P ea.

BURGLAR ALARM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit — Houses microwave radar unit, range up to 15 metres, adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.
Indoor alarm — Electronic swept freq. siren 104dB output.
Outdoor Alarm — Electronic swept freq. siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/250 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £148.00 Usual Price £228.85

BKE's PRICE £79.99 + £4.00 P&P
 ? Why buy a collection of self assembly boards!


IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.




OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinylite with protective corners, grille and carry handle. All models 8 ohms. Full Range 45Hz - 20KHz.
OMP 12 100 watts 20" x 15" x 12" £125.00 per pair
OMP 10 200 watts 18" x 15" x 11" £145.00 per pair
OMP 12 300 watts 20" x 15" x 11" £169.00 per pair

Delivery Securicor £8.00 per pair

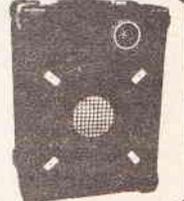

STEREO CASSETTE DECK

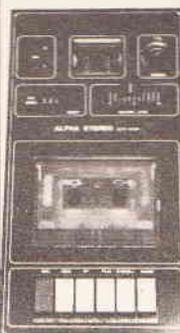

STEREO CASSETTE DECK
 Ideal for installing into Disco and Hi-Fi cabinet/Consoles. Surface mounting (Horizontal). Supplied as one unit with all electronics including mains power supply.
 * Metal top panel Black finish
 * Piano type keys including pause
 * Normal/Chrome tape switch
 * Twin Vu Meters
 * 3 Digit counter
 * Slider Record Level control
 Size 171 x 317 mm Depth 110 mm
PRICE £35.99 + £3.00 P&P

1 K-WATT SLIDE DIMMER

* Control loads up to 1Kw
 * Compact Size 4 1/2" x 1" x 2 1/2"
 * Easy snap in fixing through panel/cabinet cut out
 * Insulated plastic case
 * Full wave control using 8 amp triac
 * Conforms to BS800

* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.
PRICE £12.99 + 75p P&P (Any quantity)


BSR P256 TURNTABLE

P256 turntable chassis. S shaped tone arm. Belt driven. Aluminium platter. Precision calibrated counter balance. Anti-skate (bias) device. Damped cueing lever. 240 volt AC operation (Hz). Cut-out template supplied. Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.
Price £32.35 each. £2.50 P&P



PIEZO ELECTRIC TWEETERS MOTOROLA

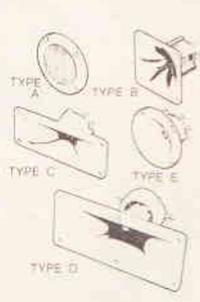Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 Watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**




TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each - 40p P&P
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.49 each - 40p P&P
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.49 each - 40p P&P
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £8.99 each - 40p P&P
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.49 each - 40p P&P
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P

STEREO DISCO MIXER

STEREO DISCO MIXER with 7 band graphic equaliser and 10 segment L.E.D. Vu Meters. Many outstanding features.
 5 Inputs with individual fader controls:—
 2 Mag. turntable, 2 Aux. plus Mic. with talk-over switch. Headphone monitor. Master output control with Hi-Low outputs. Compatible with our OMP Power Amplifiers.
 Size: 360 x 200 x 120 mm. Supply 240V/50Hz AC.

PRICE £119.99 + £3.00 P&P

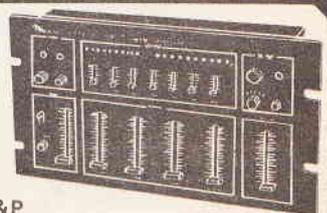

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90 - 105MHz with very sensitive microphone. Range: 100-300 metres. 57 x 46 x 14mm (9 volt). Price: £7.99 + 75p P&P
3 WATT FM TRANSMITTER 3 WATT 85 - 115MHz varicap controlled, professional performance. Range up to 3 miles. 35 x 84 x 12mm (12 volt). Price: £12.49 + 75p P&P
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp. 240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9 12 volt). Price: £16.49. Transmitter 80 x 50 x 15mm (9 12 volt). Price: £10.29 P&P + 75p each. S.A.E. for complete list.




3 watt FM Transmitter

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.



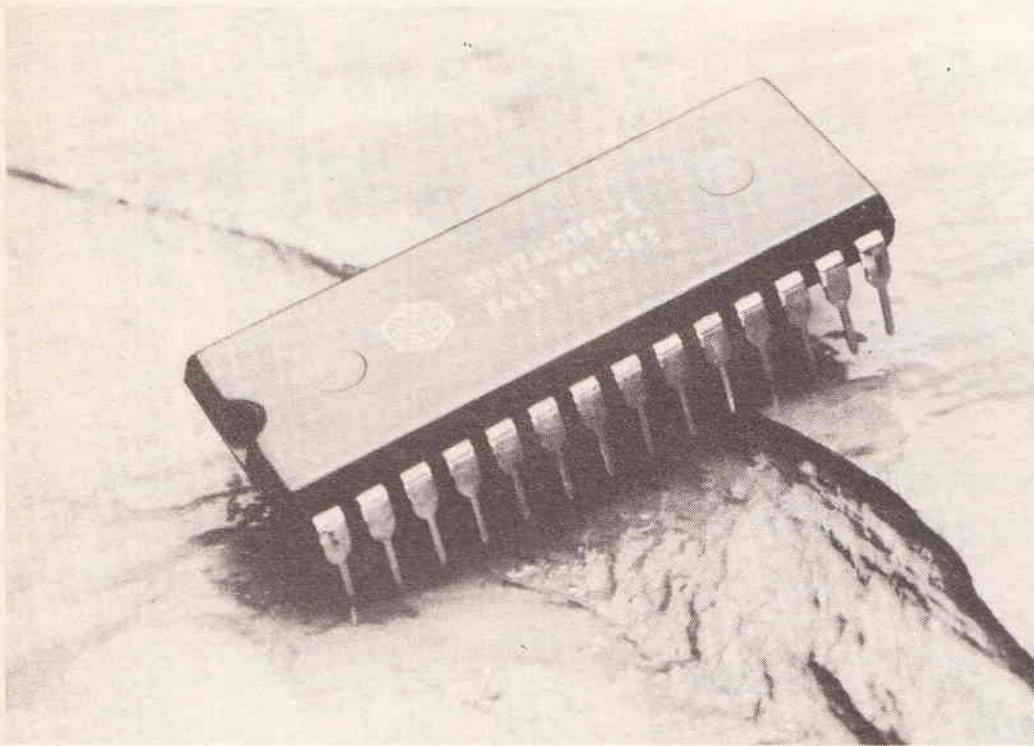B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



World's Fastest ROMs, Episode 192

A new line of high density 256K CMOS ROMs with access times as fast as 75 nanoseconds is now available from Solid State Scientific, Inc., Willow Grove, PA, USA. These new devices, announced recently, are claimed to be the fastest 256K CMOS ROMs in the world. No doubt, it will not take long for someone to come along and dispute that claim.

The ROMs have been under development for approximately one year and are now being produced on a 2 micron HCMOS II process. Price in production volumes is below \$20 each. On request, prototypes can be made available in as little as three weeks; and production volumes in seven weeks.

The new ROMs feature worst-case access times of 100 and 120 ns over the commercial temperature range (0 to +70°C). Industrial (-40 to +85°C) and military (-55 to +125°C) temperature range devices are available with 150 ns worst case access times. Under typical operating conditions, all versions operate with access times as fast as 75 ns. They also feature, under worst case conditions, operating current of 25 mA maximum, standby current of 100 uA maximum, and LSTTL-compatible inputs and outputs. In addition, they are asynchronous and fully static; no clocks or strobes are required.

They are pin compatible with NMOS EPROMs, so the EPROMs can be used for prototyping, providing due allowance is made for the EPROMs slower speed. More complete details on these 23C256 256K CMOS ROMs are available upon request from Solid State Scientific, Inc., 3900 Welsh Road, Willow Grove, PA 19090, USA, tel (USA) 215 657-8400.

Hurry now to re-new your subscription to the British Amateur Electronics Club, as their subscription rates rise as of 1st January 1985 from £5.50 to £7.00 (UK and Eire; otherwise from £7.00 to £8.50 surface mail or £8.50 to £12.50 airmail). BAEC may be contacted at "Dickens", 26 Forrest Road, Penarth, South Glamorgan.

One of the problems of DIY loudspeaker building is that you can't tell what the results will be like. However, Wilmslow audio have solved this problem by opening a hi-fi studio at Church Street, Wilmslow, where you can hear ready-made and kit loudspeakers and amplifiers. Wilmslow Audio Ltd, 35/39 Church Street, Cheshire SK9 1AS.

Philips Test and Measuring is offering a useful, full-colour A2-size poster giving essential facts about their very latest instrumentation. The poster, free on application, would grace any laboratory or test room wall and can be obtained from Philips Test and Measuring, Pye Unicam Ltd, York Street, Cambridge CB1 2PX, tel 0223-358866, telex 817331.

Buff Up Your Computer

Developed specifically for the home computer enthusiast and the semi-professional user by Memorex's Media Retail Division, the Computer Care Kit will be available from major retailers and independent stores. However, this is one clean-up kit that won't stop you playing those smutty computer games, reported in certain Sunday papers.

The comprehensive range of products consists of: VDU and TV Screen cleaning kit, comprising twenty foil sealed sachets of cleaning tissues and two anti-static cloths and priced at £4.95; case and keyboard cleaning kit also priced at £4.95 and comprising aerosol spray foam, cleaning cloth and cotton buds; disc drive and head cleaning kit with ten disposable head cleaners and aerosol spray cleaner for wet and dry action, costing £9.95; and a storage case for 5.25" floppy discs, costing £2.25. Each kit comes complete with a set of instructions.


Approved Irons

The British Electrotechnical Approvals Board for Household Equipment have given their seal of approval to Cooper Tools for the company's Weller S115, S125, and S140 soldering irons, plus the WH1 and WH2 hobby kits. These are the only soldering-related products currently on the market which are entitled to display the BEAB mark.


The BEAB mark indicates that an electric appliance meets the requirement of the British Standard BS 3456 and enables consumers to identify products which are of sound manufacture and are deemed safe to use. This is a particularly important form of assurance since the use of inferior

electrical goods can result in serious or sometimes fatal accidents.

Cooper Tools' emphasis on product quality and safety was further highlighted by the presentation of a National Safety Award from the British Safety Council. Only a small percentage of Britain's workplace qualify for this award each year which is won by achieving a lower accident incident rate than the national average. Cooper Tools Limited, Sedling Road, Wear, Washington, Tyne & Wear, NE38 9BZ, tel: 091 416 6062.

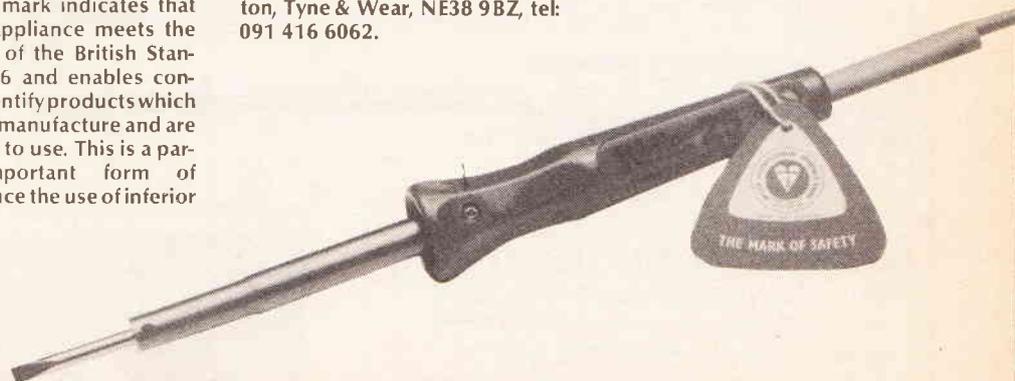

SPEAKER SQUEAKER

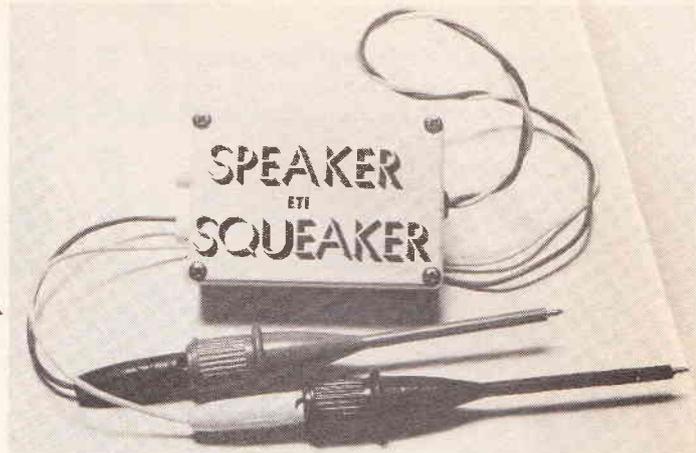

For roadies who have better things to do with their vocal chords than shout 'testing' all the time, Phil Walker has designed a self-contained loudspeaker tester.

If you ever find yourself setting up loudspeaker systems for discos, groups or public address etc, sooner or later you will need to check various parts of the equipment. This tiny piece of test gear should make life a lot easier.

One way to test continuity is to use a multimeter on the ohms range but this has at least two disadvantages in that you have to look at the scale (often in poor light) to see what is happening and it does not prove that a loudspeaker is working even if the resistance reads correctly. This project has the advantage that it gives an audible indication of continuity from its built in sounders and will also drive a loudspeaker connected to its terminals.

The Circuit

The heart of the project is the LM3909 IC. This was originally designed as a low power LED flasher but will function quite well as an audio oscillator under the right conditions. A notable feature of the device is that it will operate from a single 1.5 volt dry cell. This enables us to build a very simple and compact unit.

Most of the circuit is completely standard except that we have used two low impedance earpieces instead of a loudspeaker. This was done so that the complete project would fit into a small plastic box. If you can find a small loudspeaker with a coil impedance of 16 ohms or more this would do instead or alternately an eight ohm speaker in series with a coil (50 turns of 22 swg enamelled wire wound on a 2BA steel bolt) may be worth a try.

In operation the battery supply


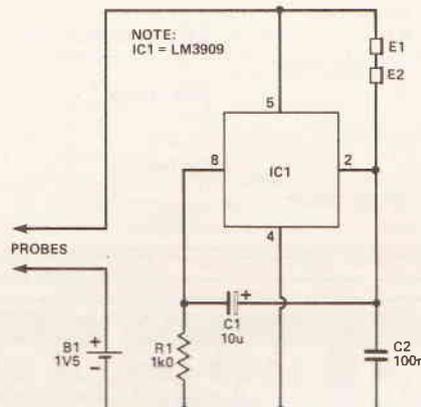


Fig. 1 Circuit diagram of the Speaker Squeaker.

HOW IT WORKS

All the active components in this project are contained in the LM3909 IC. This can be considered as a Schmitt trigger switch and a few resistors. In this case there is no polarity change between input and output. C1 provides feedback between input and output while the rest of the components help to determine the frequency of oscillation.

Fig. 2 Internal circuitry of the IC used.

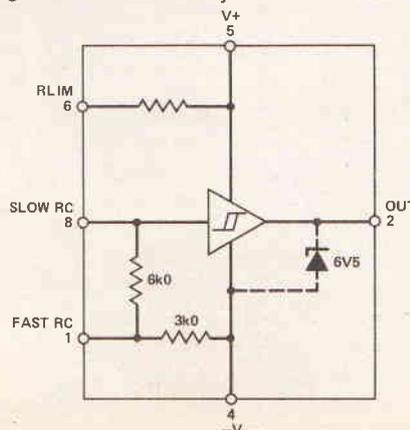

is completed via the test probes and the external circuit. If the resistance of the external circuit is low enough the LM3909 will oscillate and produce a tone from the two earpieces. The frequency and loudness of this tone will depend on the resistance and reactance of the external circuit and the characteristics of E1 and E2. Our prototype was just audible at 100 ohms resistance between the probes.

Construction

This project is a little unusual in that we have not designed a PCB to go with it. Instead we used a small piece of 0.1" matrix Veroboard 13 by 9 holes. This accommodates the four components quite easily, and the only point to watch is that four of the tracks need to be broken as shown in the diagram. Make sure the tracks run parallel to the long edge of the board.

IC1 and IC2 must be inserted the right way round and the battery connection must also be correct. The wires to the battery were soldered in place but a holder could be used if you wish and have room.

The earpieces E1 and E2 usually come with a length of wire and a miniature jack plug already fitted. These should be cut off leaving about 2 inches of wire on the earpiece. One wire from each earpiece should then be soldered together and insulated with tape or sleeving. The remaining wires can be connected to the circuit board.

In our model the probe wires were knotted inside the case and went out through a small grommet.

PROJECT : Speaker Squeaker

This prevents the wires from being pulled out. The earpieces were pushed through holes in the side of the case and secured with a little glue. The battery was held in a self adhesive cable clip and the circuit board was fastened down with a double sided sticky pad.

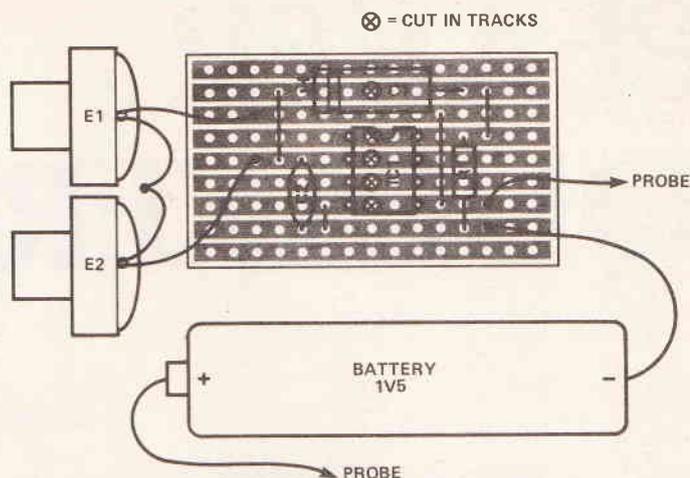
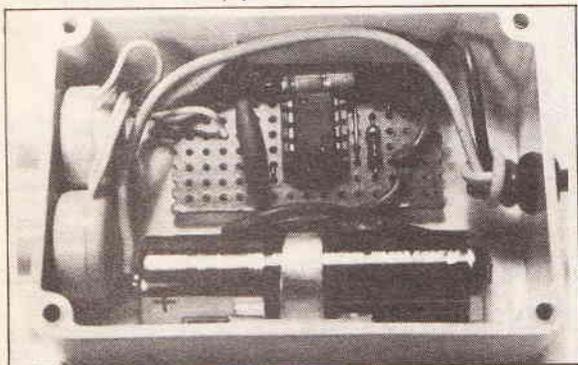


Fig. 3 Veroboard layout for the project.

BUYLINES

No problems here at all. There's no PCB to worry about and the case, earpieces and IC are all available from a number of suppliers including Maplin, TK Electronics and Cricklewood.

PARTS LIST

ETI

RESISTOR

R1

1k0 ¼W carbon film

CAPACITORS

C1

100n ceramic disc

C2

10µ16V electrolytic

SEMICONDUCTOR

IC1

LM3909

MISCELLANEOUS

E1,2


miniature 8 ohm earpieces

B1

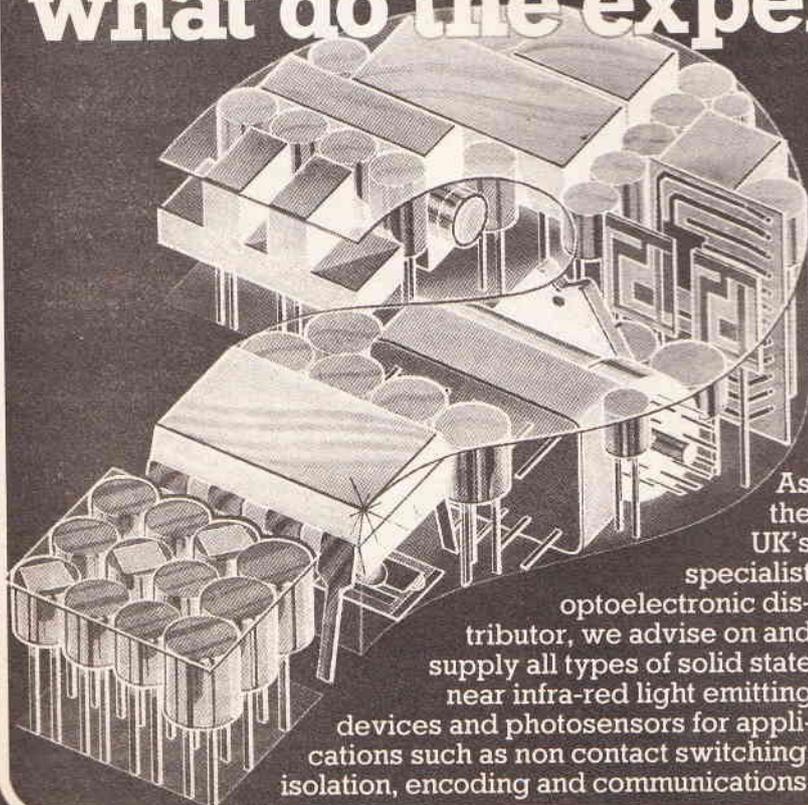1.5 volt dry cell (preferably alkaline)

Verobox type 202-21025 2.9 x 2.0 x 1.0 inch; test probes; piece of Veroboard, 9 by 13 holes; grommet or strain clips relief bush; battery holder or clip.

With so much choice what do the experts choose?



As the UK's specialist optoelectronic distributor, we advise on and supply all types of solid state near infra-red light emitting devices and photosensors for applications such as non contact switching, isolation, encoding and communications.

TRW - PHOTOLOGIC (TM) ASSEMBLIES


Available in a wide variety of package styles, these photologic (TM) assemblies from TRW feature on-board amplification and Schmitt Trigger.



NORBAIN ELECTRO-OPTICS LIMITED

Norbain House,
Boulton Road, Reading,
Berkshire RG2 0LT


Telephone: (0734) 864411 Telex: 847203

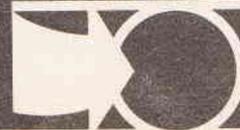

Circle this number on Reply Card for further information

Cirkit. Making it bigger and better.

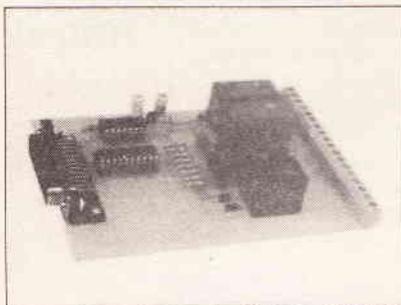Cirkit stock all the components, accessories and tools and the kits you're looking for. Designed and selected to offer the best possible standards at the best possible price.



Centronics Interface

Cirkit Kits

CIRKIT ELECTRONICS TOOL KIT

Contains: 15W Soldering Iron 2 spare bits, heat shunt, solder, pliers, cutter, screwdriver 40-00007 15.56

AUDIO FUNCTION GENERATOR

Versatile waveform generator with sine, triangular and square wave outputs. On board mains PSU 41-01302 27.00

STEREO 40W AMPLIFIER

Single board 40W per channel stereo amplifier 41-01301 38.00

STEREO VU METER

5 LED per channel stereo VU meter for use with stereo amplifiers 41-01401 11.50

5W AUDIO AMP

A very compact audio output stage for use in a wide range of equipment 41-01406 4.60

UNIVERSAL AMP

A universal audio pre-amp with a gain of 10 41-01604 6.45

MONO REVERBERATION UNIT

Single channel, spring line reverb unit to add echo effects to tape recording etc. 41-01602 10.00

TONE GENERATOR AND DETECTOR

Very low distortion tone generator and signal detector for circuit fault finding 41-01603 10.45

10MHz DFM

8 Digit LED digital frequency meter and period measurement 41-01500 54.10

50MHz PRESCALER

Extend the range of the 10MHz DFM to 50MHz 41-01501 8.55

1-5MHz PRE AMP

Low frequency pre-amp and waveform shaper for the 10MHz DFM 41-01502 5.13

70cm PRE AMP

Low noise, miniature pre-amp for the 70cm amateur band 41-01506 4.78

70cm CONVERTER

70cm to 144MHz low noise converter featuring pre-aligned helical filter, schottky diode mixer and low noise transistors 41-01405 21.50

1-30V 1mA-2A PSU

Adjustable 1-30V Power supply with pre-settable current limit from 1mA-2A 41-01600 37.46

5-12V 1A PSU

Adjustable PSU from 5-12V with current protection, 1 amp max output 41-01504 6.45

1-30V 1.5A PSU

1-30 volt adjustable PSU with protected output up to 1.5 Amps 41-01402 10.45

3 DIGIT LED DVM

DVM to read up to 99.9 volts or configured as an ammeter to read up to 9.99 amps 41-01403 17.00

INFRA RED LINK

Single channel IR Link with relay output 41-01300 9.60

TEMPERATURE SENSOR

Thermistor based temperature sensor with relay output 41-01303 6.20

LOCOMOTIVE SOUND GENERATOR

Realistic steam sound and whistle for model railways 41-01304 9.20

LAMP DIMMER

Control lamps and drill speed 41-01305 5.70

WATER LEVEL ALARM

Alarm to indicate high water level or flooding 41-01601 2.70

3 NOTE CHIME

Doorbell chime with adjustable tones 41-01503 7.00

2M PRE AMP


Miniature low-noise MOSFET pre-amp for the 2m amateur band 41-01307 3.91

2M CONVERTER

Low noise 144MHz-28MHz amateur band converter 41-01306 17.35

2M POWER AMP

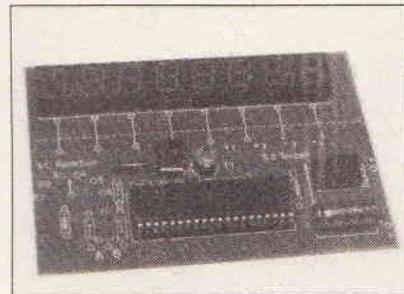20W - 10dB gain - power amplifier for the 2m band. Automatic TX switch over, RX pre-amp, robust construction 41-01404 32.87



10MHz DFM

CRYSTAL CALIBRATOR

Crystal reference calibrator for alignment of receivers, outputs at 4, 2, 1MHz, 100, 50 AND 10KHz 41-00801 4.32

CB NOISE SQUELCH

Improves to mute performance of the majority of CB rigs 41-01605 5.40

CENTRONICS INTERFACE

Connect your personal computer to the outside world via the Centronics printer output 41-01406 22.50

70cm PA

10W Power amp to boost the output of handheld and portable 70cm transceivers 41-01505 33.82

Selected Lines

BBC to Centronics		
Connect Cable	03-10019	7.25
Dragon to Centronics		
Connect Cable	03-10017	7.25
C12 Computer Cassette	21-00012	0.55
Interface 84 multiplexed		
Ram Card	40-84000	59.95
Z80A industrial controller	40-82000	54.95
EPROM Eraser 84T	40-82001	59.95
6502 Micro Controller	40-65020	54.95
6802 Micro Controller	40-68020	54.95
PB2720	80dB Piezo Buzzer	43-27201 0.55
10M15A	10.7 Center Freq.	20-10152 2.10
10M08AA	10.695 Center Freq.	20-11152 3.49
FC177	LCD (Freq.)	39-17700 20.00
CM161	LCD Clock	40-80161 8.25
8 x 0.3"	IC socket	28-00800 0.12
14 x 0.3"	IC socket	28-14000 0.13
16 x 0.3"	IC socket	28-16000 0.13
6V	KUIT-A Relay	46-80000 0.48
9V	KUIT-A Relay	46-80001 0.48
12V	KUIT-A Relay	46-80002 0.48
CX120P	COAX Relay	46-90120 11.96
CX520D	COAX Relay	46-90520 26.98
CX540D	COAX Relay (BNC)	46-90540 26.98



HT-320

Multimeter (20kΩ-V) 56-83201 14.00

Please add 15% VAT to all advertised prices and 60p post and packing. Minimum order value £5 please. We reserve the right to vary prices in accordance with market fluctuation. Just send for our catalogue or visit one of our three outlets at:

200 North Service Road, Brentwood, Essex. CM14 4SG;
53 Burrfields Road, Portsmouth, Hampshire. PO3 5EB;
Park Lane, Broxbourne, Hertfordshire. EN10 7NQ.

To: Cirkit Holdings PLC, Park Lane, Broxbourne, Hertfordshire. EN10 7NQ. I enclose 85p. Please send me your latest catalogue and 3 x £1 discount vouchers! If you have any enquiries please telephone us on Hoddesdon (0992) 444111.

Name _____

Address _____

Telephone _____

Area of Special Interest _____

ET111

Cirkit

Bigger Stock. Better Service.


NEW WINTER
CATALOGUE
OUT NOW!

ANTEX a world of soldering

Tomorrows Soldering Technology Today.

ANTEX has a worldwide reputation for quality & service & for many years has been one of the best known & most popular names in soldering. Always at the forefront of technology, ANTEX is continually researching new and better ways of achieving more accurate, reliable, and cost effective soldering. On ANTEX Soldering Irons, the advanced design of the interface between the element & the bit allows more efficient heat transfer to the bit and improved stability of the temperature at the point of contact with the work. Indeed, experiments have shown that an XS25 watt iron can be used for tasks where a 40 watt iron would normally have been required.

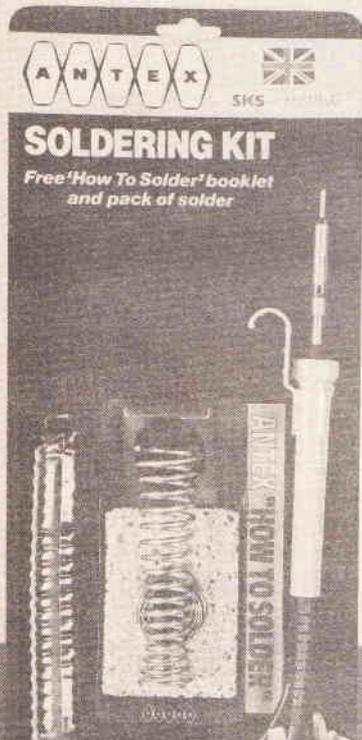ANTEX Soldering Irons exhibit exceptionally low leakage currents & hence are suitable for use on Static Sensitive Devices. Sophisticated temperature controlled soldering units have recently been added to the ANTEX range.



SK5 Soldering Kit

Model XS

Model CS

Model C

ST4 Stand

TCSU1 Soldering Unit

TCSU-D Temperature-Controlled Soldering Unit

Model C
- 15 Watts Available for 250, 220, 115, 100, 50 or 24 volts

Model XS
- 25 Watts Available for 240, 220, 115, 100, 50, 24 or 12 volts

Model XS-BP
- 25 Watts 240 volts, fitted with British Plug

ST4 Stand
- To suit all irons

SK5 Soldering Kit. Contains model CS 240v Iron, an ST4 Stand and solder.

SK6 Soldering Kit. Contains model XS240v Iron, an ST4 Stand and solder.

SK5-BP and SK6-BP Soldering Kits as above with British Plug

Model CS
- 17 Watts Available for 240, 220, 115, 100, 50, 24 or 12 volts

Model CS-BP
- 17 Watts 240 volts, fitted with British Plug

TCSU1
- Very robust temperature controlled Soldering Unit, with a choice of 30 Watt (CSTC) or 40 Watt (XSTC) miniature irons Range 65°C to 420°C Accuracy 2%

TCSU-D
Elegant Temperature Controlled Soldering Unit with 50 W Iron (XSD) and built around FERRANTI custom-made ULA. Range Ambient to 450°C Accuracy $\pm 5^\circ\text{C}$ Zero crossing switching Detachable sponge tray.


ANTEX Made in England Telex: 45296

ANTEX (Electronics) Ltd. Tel: 0752 867377

Mayflower House, Plymouth, Devon. Please send literature, price list and my nearest stockist to:

Name _____ Address _____ Telephone _____

AM/FM PORTABLE RADIO

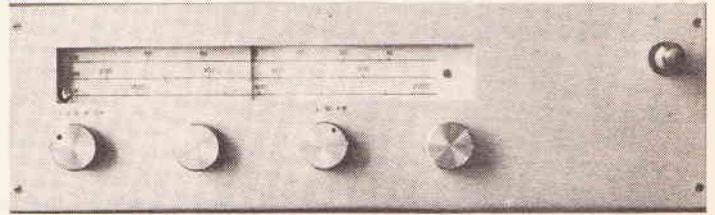

It's quite a long time since ETI last featured a radio project, as a glance at last month's index will show. L. Boullart makes good the omission.

As everyone knows, it is not really possible to compete with the majority of commercial portable radios. However there still exists something of a gap between the very cheap, flimsy, gadgets and the expensive, sophisticated sound machines.

Apart from the fun of DIY, it is worth the effort to build a reliable receiver with good sensitivity and acceptable sound quality at a reasonable price.

The present design is not spectacularly innovative as it uses well-tried techniques, but it is absolutely reliable. Practically all alignment problems have been eliminated so anyone who can hold a soldering iron should be able to achieve optimum results.

The block diagram of figure 1 shows the different sections of the receiver. These consist of an AM-FM tunerhead, separate IF amplifiers for AM and FM, an audio IC and the power supply.

Tunerhead FF 317

Although this is not the latest word on tunerheads, it contains a well-made FM amplifier with MOSFET VHF amplifier and a separate transistor for the oscillator circuit. Apart from the three-section FM tuning capacitor it also contains a two-section AM-gang, used as CV2. A 3:1 reduction drive is also provided, which will allow a simple dial assembly. The positive supply voltage must be connected via a 150 ohms resistor.

AM Section

The heart of the AM amplifier and detector (Fig.2) consists of an HA1197 IC by Hitachi. It contains

an HF-IF section and a detector. To improve signal-to-noise ratio, the low impedance input is preceded by an FET source-follower, Q2. The gate of the FET has a very high input impedance, so the usual practice of using taps on the MW and LW coils on the ferrite rod can be dispensed with. The

total signal strength from the antenna coils (which is not great anyway!) can therefore be put across the gate input with no significant loss. At MW mid-band (1 MHz) we get

$$\begin{aligned} Z &= 2 \pi f L O \\ &= 10^6 \times 6.28 \times 234 \times 100 \\ &= 146 \text{ k} \end{aligned}$$


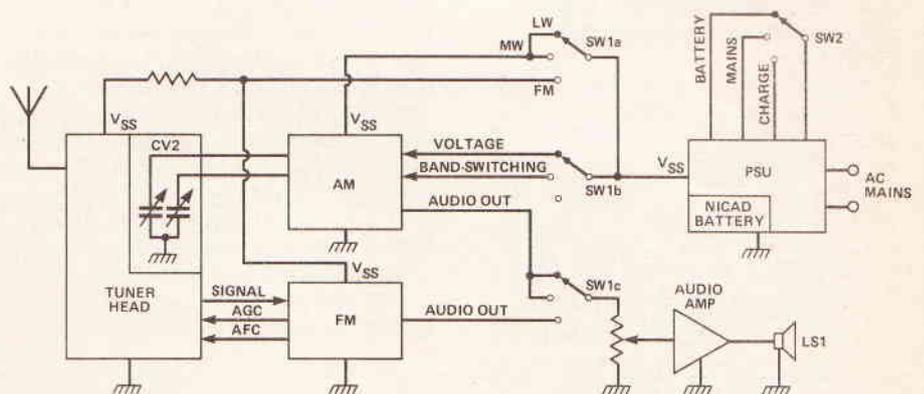


Fig. 1 Block diagram of the complete AM-FM tuner

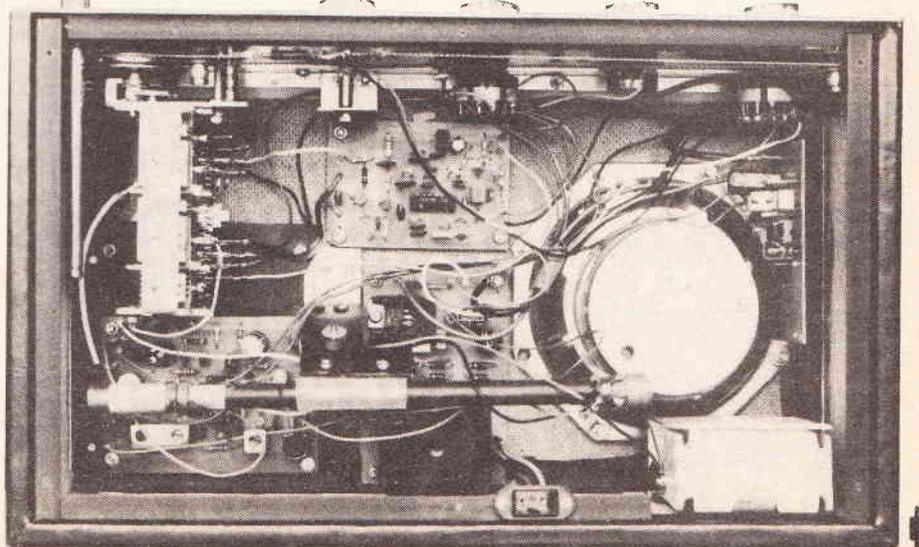

To avoid losses and unwanted atmospheric on the connecting wires, band switching is effected directly on the printed circuit board by means of transistors Q1 and Q3. The arrangement is somewhat unusual: the antenna coils are connected in series for long wave reception and on medium wave the LW coil is short-circuited, by applying the positive supply voltage to the base of Q1. For the oscillator section, additional capacitors (C6 and CV3) are switched into the circuit by means of Q3. Note that the LW coil is damped by a 120 — 150k resistor, R3, to avoid instability and improve frequency response: a long wave coil with a Q factor of 100 will result in a bandwidth of $200 \text{ kHz}/100 = 2 \text{ kHz}$, which means a very poor audio response!

The tap on the oscillator coil, L4, is shunted with a 68R resistor, R7, and the connection to the tuning capacitor has a 3μH choke, L3, in series. This can be made up of a 1M0 0.33 W resistor with 50 turns of 0.15 to 0.25 mm wire wound at random. As a result, the oscillator voltages across the tap will be reasonably constant over the entire tuning range (approximately 150 mV).

AM selectivity is mainly determined by the CFU bandfilter, L5, in the IF section. The secondary should be damped by a 5k6 resistor, R8.

At the detector output is an 8—10 kHz whistle filter comprising L7 and C22. The coupling capacitor C23 has been chosen for a time-constant of 100 μS to compensate

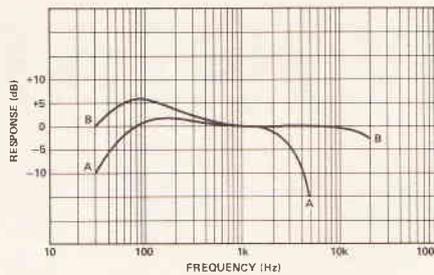


Fig. 3 Audio-response curve for AM (A) and FM (B)

for a moderate amount of bass-lift in the audio amplifier (of which more later on). Too much bass lift on AM would result in "boomy" sound! The AF frequency response is shown in Fig. 3, curve A.

FM Section

The IF amplifier of Fig 4 is built around the time-honoured CA 3089 IC. It should be noted however that the phase-detector coil arrangement has been replaced by a ceramic filter type CDA 10.7 MA. Two more ceramic filters precede the CA3089, together with Q4, which compensates for the losses of the filters and offers some gain into the bargain. With the use of ceramic filters throughout the IF amplifier, no alignment procedure is required and yet the results are quite satisfactory: harmonic distortion is below 0.35% with a frequency deviation of $\pm 50 \text{ kHz}$.

In conjunction with the FF317 tunerhead, the useful sensitivity at the antenna input should lie in the neighbourhood of 1 μV, which is rather exceptional for a portable

receiver. With this kind of sensitivity, the AGC connection on the FF317 becomes a very useful feature, because without it overload on strong stations could hardly be avoided.

The AFC output of the CA 3089 is of the wrong polarity for the FF317, so a polarity-reversing stage has been added with Q5. For simplicity's sake, the AFC is not switchable. This could easily be arranged, making use of pin 10 of the IC with a 4k7 resistor in series, but in the authors opinion it is quite unnecessary. Although the amount of AFC in the present design is adequate to compensate for the oscillator drift, under normal circumstances even the weakest signals should not be pulled away by strong neighbours. R37 (3k3) may need some adjustment in order to keep the potential at the collector of Q5 below 7 volts with a supply voltage of 12 volts. If so, just solder the appropriate parallel resistor on the copper side of the PC board.

Audio Amplifier

Once again an IC, TBA 820M has been chosen for simplicity and reliability (see Fig. 5). It requires a minimum of external components and delivers a clean 1.2 Watts audio power into an 8 ohm load with a 12 V supply. Distortion is 0.25%, quite acceptable for a portable radio. Besides, it offers the possibility of adding an external bass-boost circuit. The components have been carefully chosen to achieve optimum results with the specified loudspeaker and

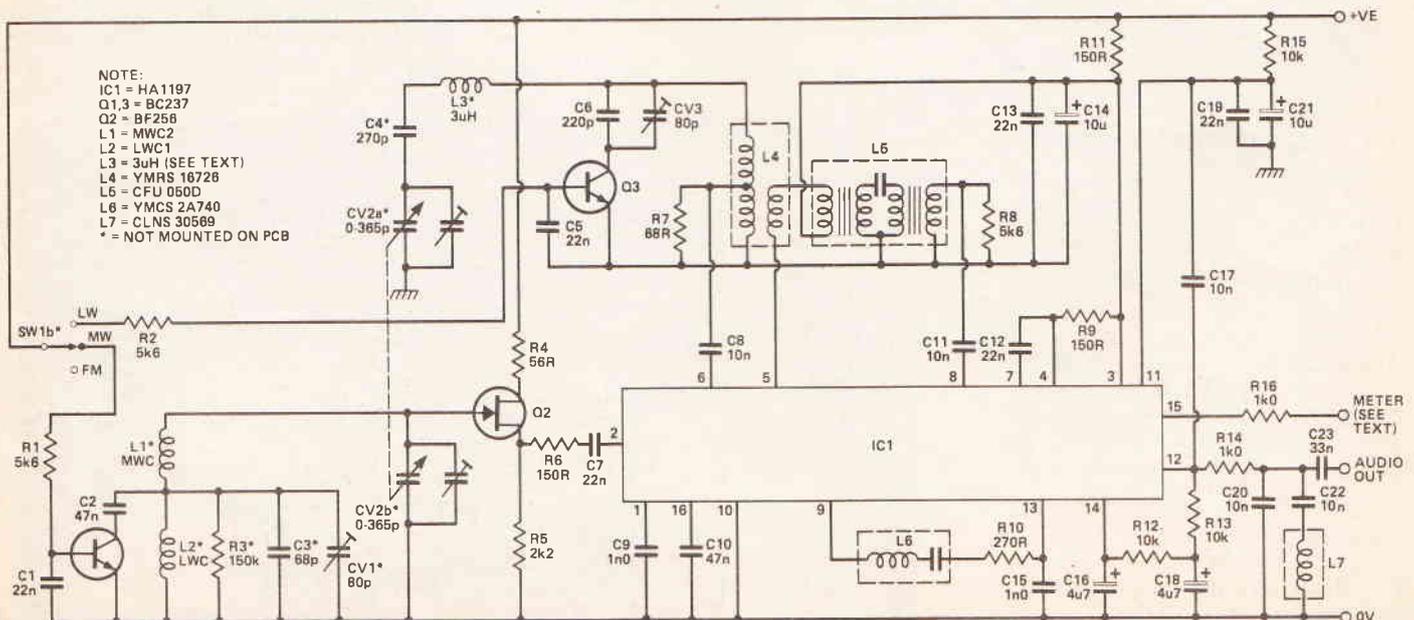


Fig. 2 AM IF-amplifier circuit

PROJECT: AM/FM Radio

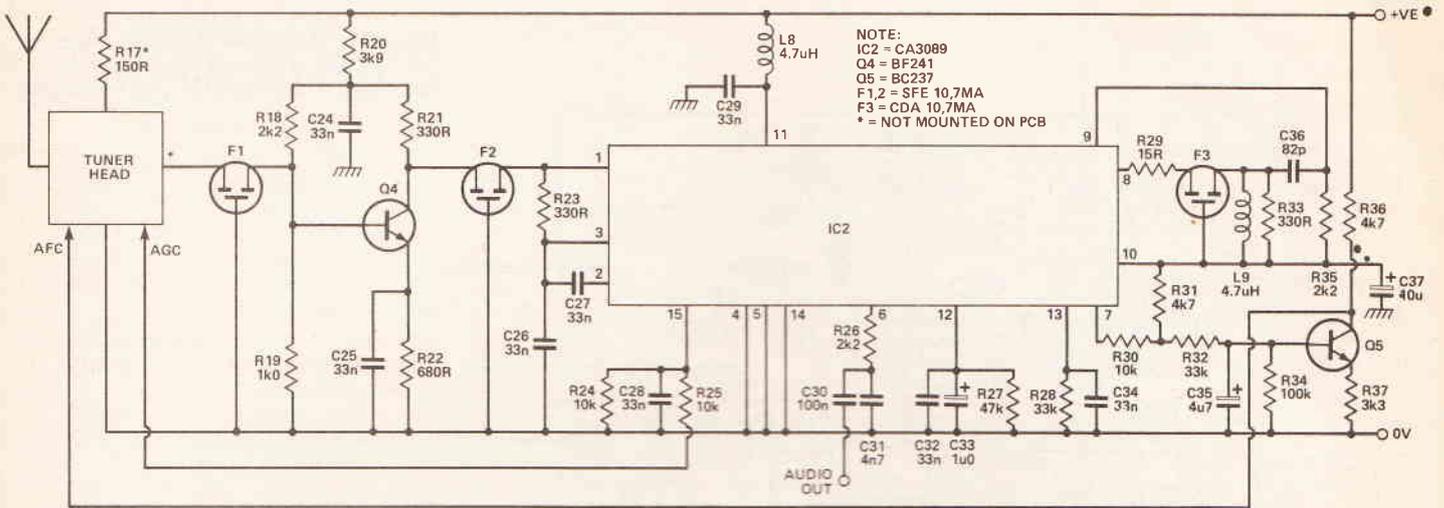


Fig. 4 FM IF-amplifier circuit

enclosure. Since the response of the loudspeaker-enclosure assembly begins to fall off in the region of 200 Hz, bass-boost reaches a maximum of 5.5 dB at 90 Hz and then drops steeply to 0 dB at 30 Hz, controlled by the time-constants of R39, C38 and C43, pin 1 at the TBA 820M output. The overall frequency response on FM can be seen in Fig. 3, curve B.

Several combinations of small woofers and tweeters were tried out, but in the end the Phillips AD 5061 M8 full-range loudspeaker was considered the best choice for this particular application.

Although modestly priced, it gives a very good account of itself in a small enclosure: good attack, smooth and clear treble without shrillness. Of course one can't expect a full-fledged reproduction of the bass-drum (or the hammer in Mahler's 6th Symphony!) from an enclosure of barely 5 litres...

Power Supply

It stands to reason that a portable radio has to be battery-powered; yet we must bear in mind that the apparatus will often be used in a place where a mains outlet is available. For this reason, a mains supply should be included. On the other hand, the price of the usual carbon-zinc batteries has gone up steadily. With a current drain of 24 mA on AM and 38 mA on FM and with another 10 mA added at quite a modest sound volume, the prospect becomes very gloomy...

The modern solution lies in the use of NiCad batteries. They must be about the only item on the market that has become cheaper! Another advantage is that their potential voltage remains fairly constant over the entire discharge

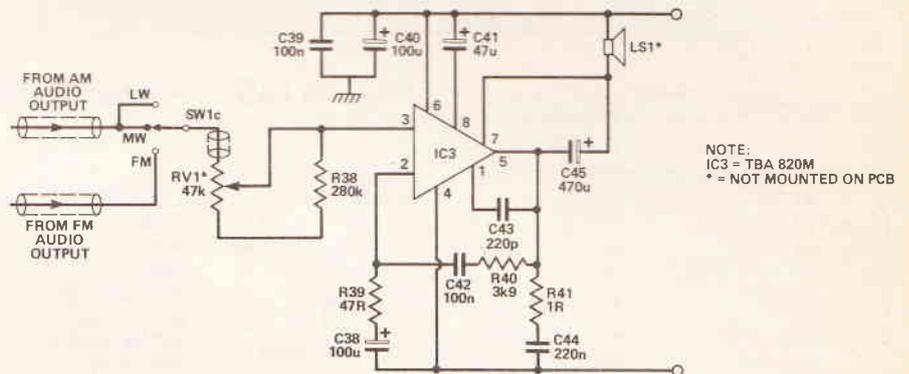


Fig. 5 Audio amplifier circuit

period and they can be recharged by the built-in power supply (Fig. 6). This arrangement also makes it possible to play the set normally while the batteries are being charged. The capacity of the NiCad cells is from 10 hours on FM to 14 hours on AM, when the receiver is playing at a moderate volume. This is not a very cheap solution, of course, but we should consider that, when compared with only six replacements of the carbon-zinc batteries, the NiCads

are already less expensive.

The power supply circuit is quite straightforward, but the 7812 regulator should be mounted on a small heatsink.

On position 4 of the switch SW2, the NiCad batteries are charged through a constant current source Q6. Full charge takes 16 hours at a current of 45 mA. Adjust RV1 for a voltage drop of 0.45 V over R3, which brings the charging current to 45 mA: $0.045 \times 10 = 0.45$ V.


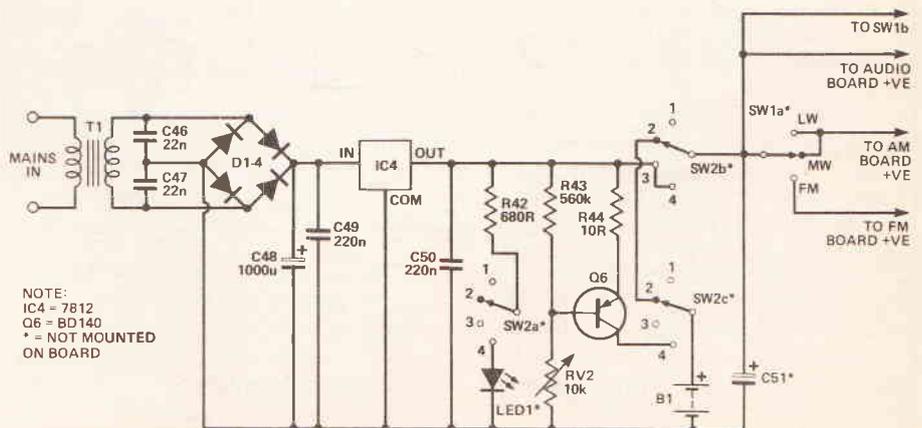


Fig. 6 Power supply circuit

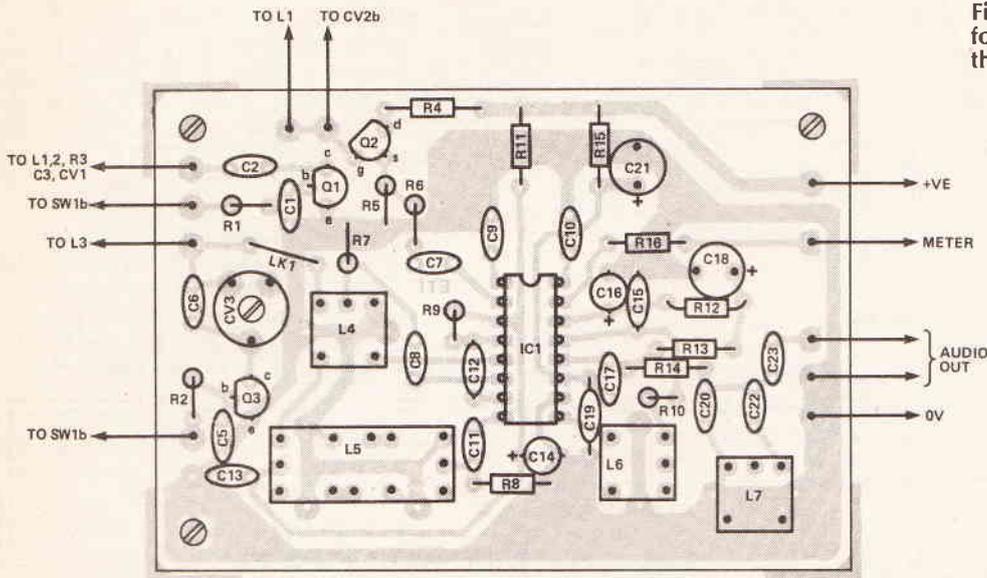Figs. 7, 8, 9 and 10 Overlay diagrams for the AM IF Board, The FM IF Board, the audio board and the power supply.



PARTS LIST — AM BOARD

RESISTORS (all 1/4 W 5%)

- R1,2,8 5k6
- R3 150k
- R4 56R
- R5 2k2
- R6,9,11 150R
- R7 68R
- R10 270R
- R12,13 10k
- R14,16 1k
- R15 10R

CAPACITORS (all ceramic or silver mica unless otherwise stated)

- C1,5,7,12,13,19 22n
- C2,10, 47n

- C3 68p
- C4 270p
- C6 220p
- C8 11,17,20,22 10n
- C9,15 1n0
- C14,21 10u 16V radial electrolytic
- C16,18 4u7 16Vradial electrolytic
- C23 33n
- CV1,3 80p trimmer
- CV2 365p (contained within tuner head)

- SEMICONDUCTORS**
- IC1 HA1197 (Hitachi)

- Q1,3 BC237
- Q2 BF256
- MISCELLANEOUS**
- L1,2 MWC2 and LWC1 coils mounted on ferrite rod aerial
- L3 3uH (see text)
- L4 YMRS 16726
- L5 CFU 050D
- L6 YMCS 2A740
- L7 CLNS 30569
- SW1b 3 (or 4) pole, 3 way rotary switch (see audio and PSU boards)
- PCB; mounting bracket for ferrite rod.

PARTS LIST — FM BOARD

RESISTORS (all 1/4 W, 5%)

- R17 150R
- R18,26,35 2k2
- R19 1k0
- R20 3k9
- R21,23,33 330R
- R22 680R
- R24,25,30 10k
- R27 47k
- R28,32 33k
- R29 15R
- R31,36 4k7
- R34 100k
- R37 3k3


CAPACITORS (all ceramic or silver mica unless otherwise stated)

- C24-29,32,34 33n
- C30 100n
- C31 4n7
- C33 1u0 16V radial electrolytic

- C35 4u7 16V radial electrolytic
- C36 82p
- C37 10u 16V radial electrolytic

- SEMICONDUCTORS**
- IC2 CA3089
 - Q4 BF241

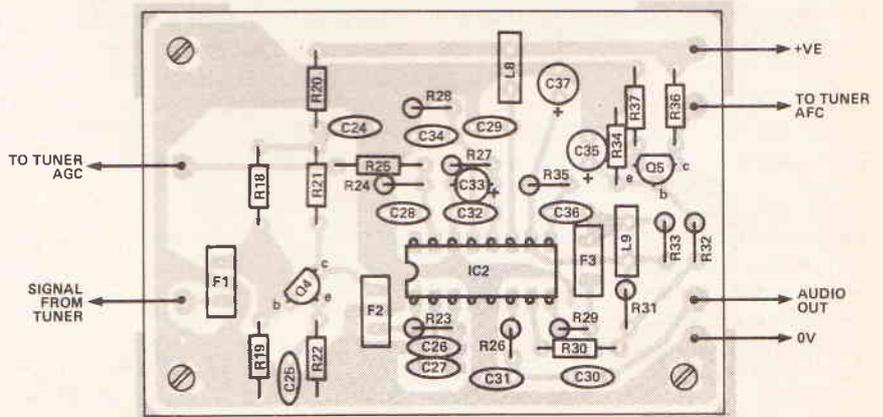- Q5 BC237
- MISCELLANEOUS**
- F1,2 SFE 10, 7MA
- F3 CDA 10, 7MA
- L8, 9 4.7 uH RF choke
- PCB; tuner head, type FF317; rod antenna and/or socket for external antenna.



PROJECT: AM/FM Radio

PARTS LIST — AUDIO BOARD

RESISTORS (all 1/4 W 5%)

R38	820k
R39	47R
R40	3k9
R41	1R0
RV1	47k log. potentiometer

CAPACITORS

C38,40	100µ 16V radial electrolytic
C39,42	100n
C41	47µ 16V radial electrolytic
C43	220p
C44	220n
C45	470µ 16V radial electrolytic

SEMICONDUCTOR

IC1 TBA 820M


MISCELLANEOUS

LS1 8R Phillips AD 5061M8 or similar

SW1c

3 (or 4) pole, 3 way rotary switch (see PSU and AM boards)

PCB.

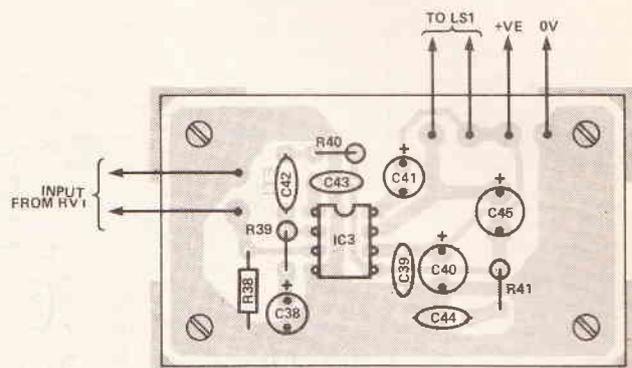

PARTS LIST — PSU

RESISTORS

R42	680R
R43	560R
R44	10R
RV2	10k horizontal skeleton preset

CAPACITORS


C46,47	22n Ceramic
C48	1000µ 25V radial electrolytic
C49,50	220n Ceramic
C51	1000µ 16V axial electrolytic

SEMICONDUCTORS

IC4	7812
Q6	BD140
D1 — 4	IN 4007
LED1	Red LED, panel mounting

MISCELLANEOUS

B1	12V NiCad pack eg. 8 off AA NiCad cells in series
----	---

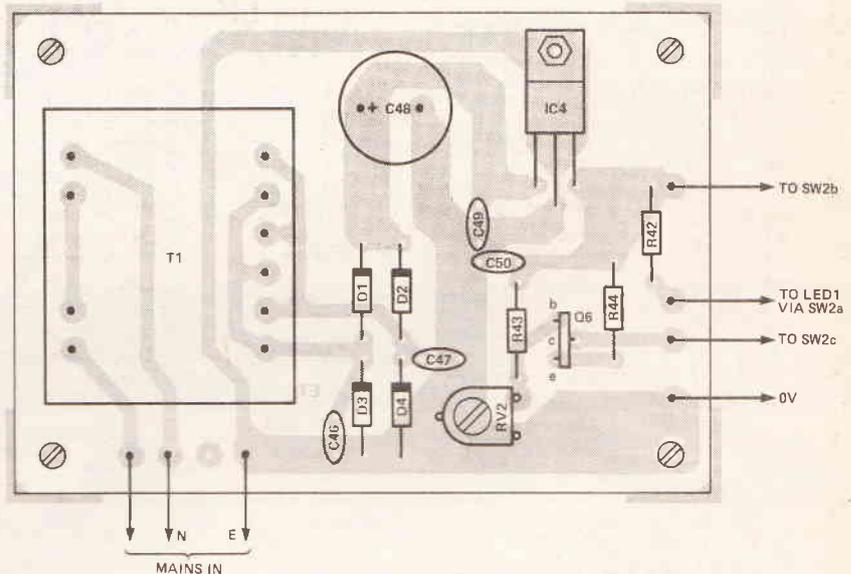

SW1a

3 (or 4) pole, 3 way rotary switch (see audio and AM boards)

T1

15V 6VA PCB mounting transformer (eg. Drake P0615)

SW2

3 pole, 4 way rotary switch

PCB; small heatsink; nut and bolt to mount IC4; mains input socket or mains cable and strain relief bush.

Construction

Four PC boards are needed; Figs. 7 to 10 show the lay-out. They can easily be hand-made at home by means of transfers and a bottle of ferric chloride (I did!). Of course, you can buy them from the ETI PCB service.

You could buy a proprietary brand of case to house the radio (plastic, of course, not metal), but our experience suggests that with

radios, the best results are obtained by making your own, provided you are reasonably handy with a saw and glue. What follows is a description of how to make the prototype's case.

The sides of the case were made from four pieces of 8 mm plywood and the top of the case was made up with 5 mm hardboard, but 8 mm ply might be more suitable. Counter-sunk screws were used to mount the speaker, PCBs and to bolt on the

control sub-panel. Obviously, a cut-out for the loudspeaker cone is also needed as well.

There are a total of three control panels! First, there's the sub-panel onto which the control pots and switches are mounted, along with the aerial and the tuning scale and pulley for the tuning drive cord; next is the plywood panel and finally, the neat control panel itself. With plywood back and front, it should be possible to dispense with the plywood panel, as

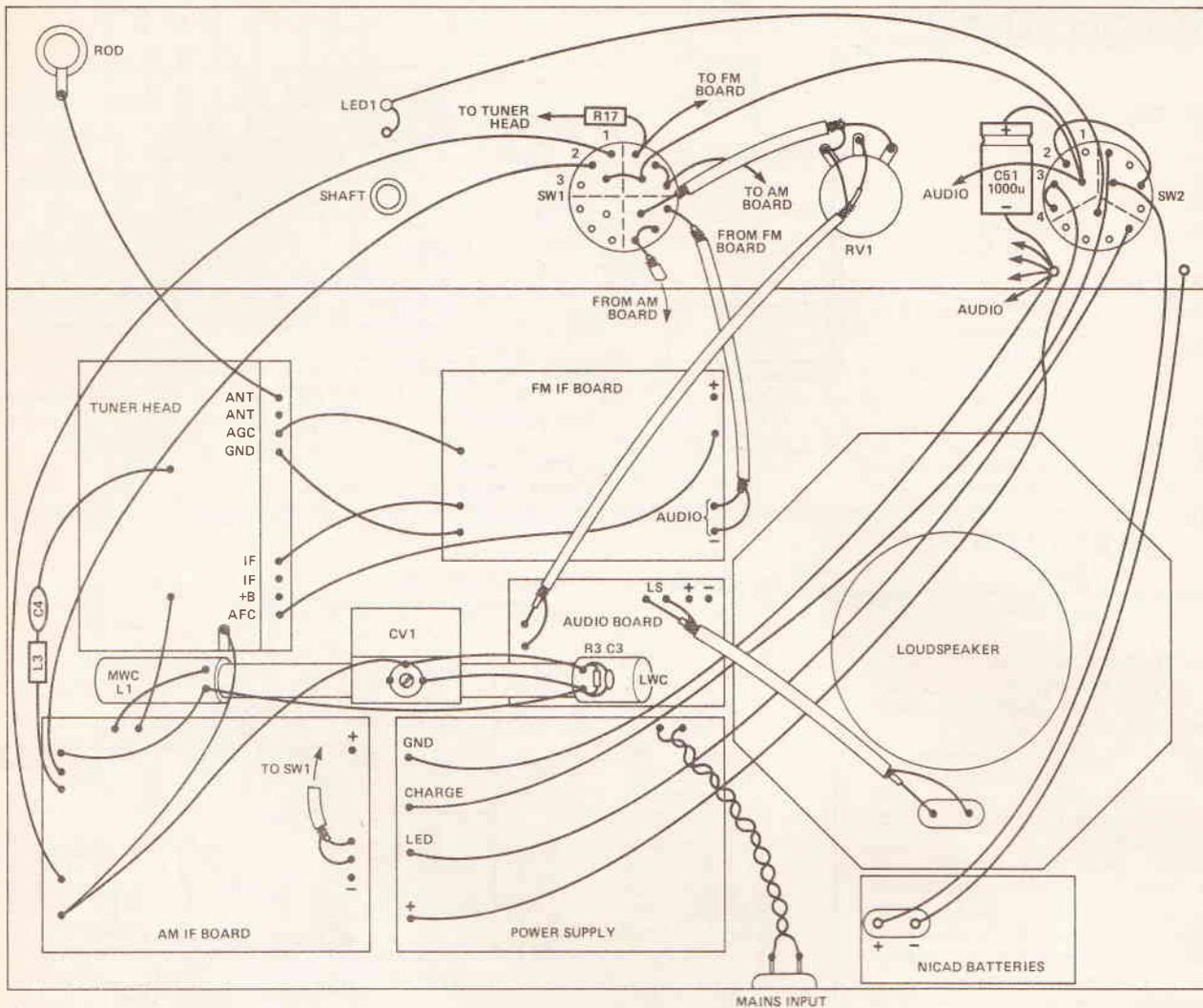


Fig. 11 Wiring diagram for the complete set

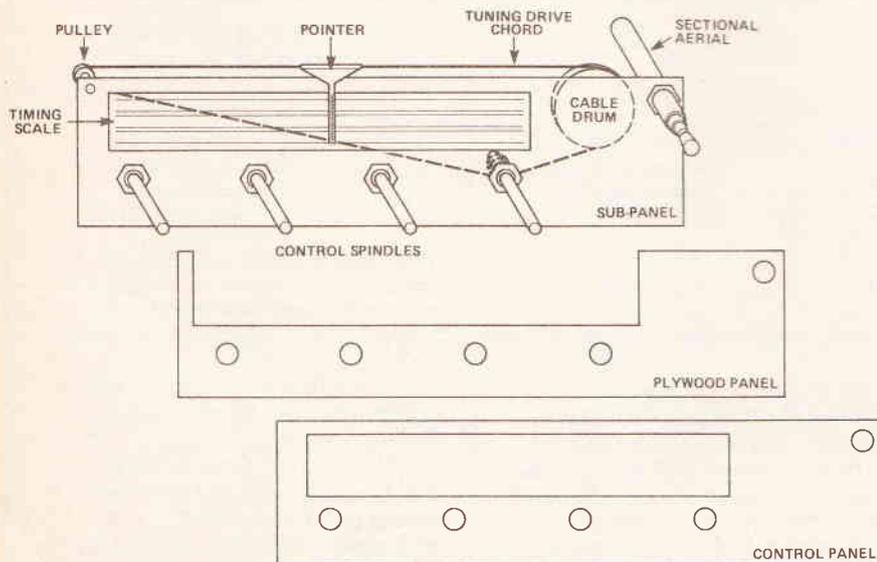


Fig. 12 Construction of the receiver front panel!

the case should be strong enough without it.
With a 3:1 reduction drive on the variable capacitor, a cable

drum of 35 to 40mm will give a scale length of 168 to 192mm, which is ample for most purposes. If no scale drum is available, a

knob of suitable dimensions will do the trick.

Fig. 11 shows details of the inter-wiring in the case, and Fig. 12 shows details of the control panel. However, these are as a suggestion only, you'll have to work out your own exact details depending on what you have available, the size of the cable drum, etc.

Alignment

FM: Theoretically, no adjustments have to be carried out. If you do want the last decibel or so, connect a sensitive voltmeter to pin 13 of the CA3089 (across R23) and try carefully to increase the signal level on a weak station by adjusting the trimmers on the 2HF sections of the variable capacitor.

AM: A little more work has to be done on the medium and long wave bands.

1. Switch to MW. The band has to cover from 525 to 1580 kHz
2. Connect a high impedance

PROJECT: AM/FM Radio

meter with a 0.5V scale to pin 15 of the HA 1197 (a connection is provided on the PC board).

3. If you have an RF generator, turn it to 525 kHz and tune the rejection coil L7 for maximum signal level.

4. Adjust the oscillator coil, L4, at the lower end of the scale. Move the MW, L1, coil on the fourth ferrite rod for maximum signal level.

5. Now turn the RF generator to 1580 kHz and adjust the oscillator trimmer on the variable capacitor at the other end of the scale. Adjust the HF trimmer for maximum signal level.

6. Repeat operations 4 and 5.

7. Next, go to 650 kHz and move the MW coil to reach a maximum.

8. Finally, adjust the HF trimmer on the variable capacitor at a frequency of 1300 kHz.

Points 7 and 8 are carried out for a regretably simple reason: the difference between the incoming and the oscillator frequency should always be 470 kHz (the IF). Unfortunately, this cannot be the case over the complete band, because neither the coils nor the

capacitance variations are identical. In practice the tracking error will show an S-curve (see Fig. 13). It is then merely a question of choosing the most appropriate spot for F1 and F2.

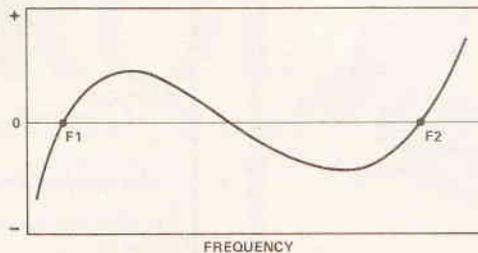


Fig. 13 General curve of the tracking error on MW.

If no RF generator is available, the above procedure may be carried out using the signal of the broadcasting stations at or close to the indicated frequencies. If you want to make a nice job of it, you can plot the points on a piece of graph paper and draw a curve, which will show what small corrections to apply.

9. The long wave band covers from 150 to 266 kHz. The same

alignment procedure is followed. The LW trimmer is mounted on the bracket for the ferrite antenna. Final adjustment is carried out at 166 and 250 kHz.

10. The rejection coil L7 is once more adjusted for maximum signal strength.

Conclusion

Your portable AM-FM receiver may not be the cheapest on the market (far from it!), but the sensitivity and the pleasing sound quality will come as an agreeable surprise. Lastly, if the instructions and the lay-out diagrams are followed carefully, it is virtually impossible to go wrong.

BUYLINES

The tuner-head, the ferrite rod assembly and the coils and filters are all available from Cirkit (formerly Ambit) who advertise in our pages. None of the other parts should cause any problems and the PCBs are available from us. Note that only the electronic components are given in the parts lists.

ETI

SECURITY

Assemble and install your own system and save pounds

SECURITY

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.



contains:
Control Unit CA 1250
Enclosure & mechanical fixings HW 1250
Key Switch & 2 keys KS 3901
L.E.D.'s LED 1
5 1/2" Horn Speaker HS 588
4 high quality surface mounting Magnetic Switches MS 1025

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straight forward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today
Order code: CS 1370.

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 + its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided. Order Code: CS 1480.

SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063 only £37.00 + V.A.T.



Requires no installation. Easily assembled using our professionally built and tested modules.
•Adjustable range up to 25 ft.
•Built-in entrance and exit delay
•Built-in timed alarm
•Key operated switch - Off, Test and Operate
•Provision for an extension speaker.
•Fully self-contained
•Uses US 5063, PSL 1865 Key Switch 3901, 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90db of sound, or even 110db with an additional speaker. All parts included and supplied with full instructions for ease of assembly.
Size 200 x 180 x 70mm Order as CK 5063

ALARM CONTROL UNIT CA 1250



Price £19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.
•Built-in electronic siren drives 2 loud speakers
•Provides exit and entrance delays together with fixed alarm time
•Battery back-up with trickle charge facility
•Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
•Anti-tamper and panic facility
•Stabilised output voltage
•2 operating modes full alarm/anti tamper and panic facility
•Screw connections for ease of installation
•Separate relay contacts for external loads
•Test loop facility

HARDWARE KIT HW 1250

only £9.50 + V.A.T.



This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

Add 15% V.A.T. to all prices
Add 70p post and packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday
Saturday 9.00 to 1.00 p.m.
SAE with all enquiries
Order by telephone or post using your credit card

SIREN & POWER SUPPLY MODULE PSL 1865

only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110db at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

POWER SUPPLY & RELAY UNIT PS 4012 Price £4.95 + V.A.T.

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470.

SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces extremely high sound pressure levels (110db at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £2.95 + V.A.T.

5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110db at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £4.95 + V.A.T.

3-POS. KEY SWITCH 3901

Single pole, 3-key switch intended for use with the CA 1250. Price £3.43 + V.A.T.

MAGNETIC SWITCH MS 1025

Surface mounting superior quality. Price £1.17 + V.A.T.

US 4012 ULTRASONIC MODULE

Basic low cost ultrasonic detector suitable for wide range of movement detection applications featuring 2 LED indicators and having adjustable range 5-25 ft. Price £1.95 + V.A.T.

DIGITAL ULTRASONIC DETECTOR US 5063



only £13.95 + V.A.T.

•3 levels of discrimination against false alarms
•Crystal control for greater stability
•Adjustable range up to 25ft.
•Built-in delays
•12V operation
This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063, for US 4012 order SC 4012.

INFRA-RED SYSTEM

IR 1470 only £25.61 + V.A.T.




Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft. operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 by 50 by 35mm.

RISCOMP LIMITED

Dept ETI/22
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326

Sweet sixteen

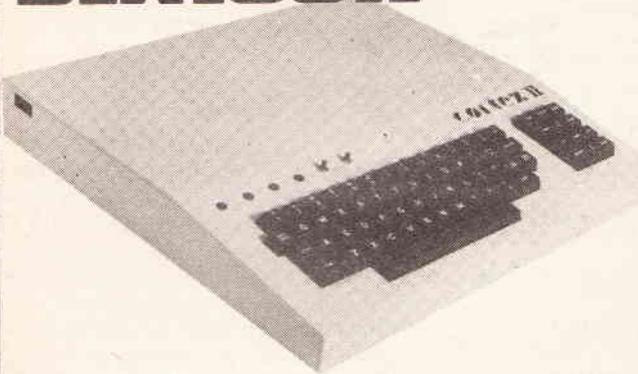

The Cortex II offers serious users speed (12 MHz CPU) and power (16-bit) at an easily affordable price.

Cortex II offers over 34K byte memory for basic programmes. High speed 24k byte basic interpreter. Auto-line numbering facilities and full renumbering command. Full textural error messages. Arrays and strings limited only by memory. Extended Basic (IF-THEN-ELSE). Assembler/Disassembler. Machine code monitor. Real time clock.

Cortex II has excellent colour graphic capability. High resolution graphics (256 x 192). 16 colours. Separate 16k video ram for graphics, does not use Basic RAM. Sprite graphics. Fast line and point plotting.

All these features as standard, with various upgrades available.

Supplied either as a self-assembly kit or fully built and tested, the Cortex II is designed to grow with the needs of the operator.

Cortex II is the successor to the popular Cortex, which first appeared in November 1982. The new model incorporates a number of modifications to the original and is supplied with a 216 page users manual.

Cortex II standard kit (Includes RS232C, TV & Cassette Interfaces)	£299.00
RGB interface kit	£28.50
Floppy disc interface kit (electronics)	£86.50
Floppy disc interface kit (hardware & connectors)	£24.50
Disc Drive 5 1/4" SSSD	£150.00
Disc Drive 5 1/4" DSDD	£295.00
Housing for Twin disc drives	£29.95
Centronics printer interface kit (requires E-Bus)	£35.00
E-Bus Kit (basic components)	£17.50

Cortex II Built and Tested
— Standard Model **£399.00**

Contact Sales Office for other options.

All prices are VAT exclusive and are correct at time of going to press.

Cortex II is available by mail order from:

Powertran Cybernetics Limited
Portway Industrial Estate
Andover
Hants
SP10 3ET



Access/Visa card holders can order
by phone on (0264) 64455

cortex II

THE GROWN-UP MICROCOMPUTER

ELECTROVALUE

Your SPECIALIST SUPPLIERS for SOLDER TOOLS



From a simple 15 watt model to a precision temperature controlled iron, we stock solder irons to suit all manual requirements together with supporting stocks of bits, de-solder tools, materials etc.

ANTEX

C.240 - 15W/240V
CS - 17W/240V
XS - 25W/240V

Replacement bits from 3/32" to 1/4"

De-solder heads, stands, elements and handles.

ERSA

'Sprint' high speed iron: 80/150W, 240V. Heats in 10 seconds!

ORYX

Temperature controlled solder iron TC.82 45W/240 with scale.

Oryx 50 - 50 watt temp. controlled.

Standard types

Oryx 30 - 30W/240V

Viking - 27W/240V

Oryx M.3 - 17 watts, 12 volts.

A wide range of replacement tips available for all models, also tips from 0.8 to 6.4mm dia. and flat tips.

Oryx safety stand

Oryx de-solder tool

MINIATURE SOLDER STATION

SOLDER and DE-SOLDER BRAID

Solder in various grades.

Please mention this journal when sending for latest free A-Z list.

BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 40 PAGE A-Z LIST
ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

ELECTROVALUE LTD

(0784) 33603; Telex 264475.
North - 680 Burnage Lane, Manchester. 061-432 4945.
EV Computing Shop -
700 Burnage Lane, Manchester. 061-431 4866.

28 St. Jude's Rd.,
Englefield Green,
Egham, Surrey
TW20 0HB.

ACCESS AND
BARCLAYCARD
Phoned Orders
Welcome

Interak 1

A METAL Z80A COMPUTER

Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips — not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from **£10.95** to **£17.75** + VAT; manuals **£1 - £5**.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletters etc. No fears about this one going obsolete — now in its fifth successful year! Send us your name and address with a 21p stamp and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work: Interak, Interak, Interak!

Greenbank

Greenbank Electronics (Dept T11E), 92 Chester Road,
New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391

SPECTRUM CONTROL PORT

In the second and concluding part of this project, Mike Wynne Jones finishes the description of the construction and goes on to describe the software needed.

Begin constructing the I/O boards by inserting all the through links (soldered top and bottom), resistors and the diode into the board, followed by the capacitors and IC sockets. Then insert a low profile wire wrap socket in SK1 and solder it flush with the PCB. If you cannot get low profile wire-wrap sockets, an alternative approach is shown in Fig. 8.

Take another low-profile wire-wrap socket and break all the pins

off at the shoulder before they enter the plastic socket body. If yours has no shoulder then try bending the leads outwards to about 90°; if this is not successful you should try the alternative method. Otherwise solder the remaining strips to the copper side of a small piece of 6 x 4 hole veroboard (Fig. 9). If you tin the board first it helps considerably. Next solder the legs you broke off the socket into the holes at the edge of the veroboard so that you

end up with an 8 pin socket with legs on a 0.5" spacing instead of the usual 0.3". This contraption should now fit comfortably over the SK1 you have already fitted and leave no unwanted connections. Make sure that it sits down level and in line with the existing socket and solder it into position. Clip off the leads of this part short and those of the original socket to about 2.3 mm but leave the leads of the original socket for the time being.

PARTS LIST — I/O BOARDS

RESISTORS

R1-5 1k0 ¼ W 5%

CAPACITORS

C1 100µ 16V electrolytic
C2,3 100 n ceramic
C4 47n ceramic or 100n miniature ceramic

SEMICONDUCTORS

IC1 74LS266
IC2 74LS02
IC3 74LS00
IC4 74LS283
IC5 74LS373
IC6 74LS374
D1 IN4148

MISCELLANEOUS

SK1 2 off 8 pin DIL low profile wire-wrap DIL sockets and 1 off 8 pin standard DIL socket (or half of a 16 way DIL header — see text)
SK2-4 8 pin standard or low profile DIL wire wrap socket and 8 pin standard DIL socket (or half of a 16 way DIL header — see text)
SK5,6 15 way right-angle 'D' plug (see text)
PCB; 2 x 14 pin, 2 x 16 pin and 2 x 20 pin DIL sockets.

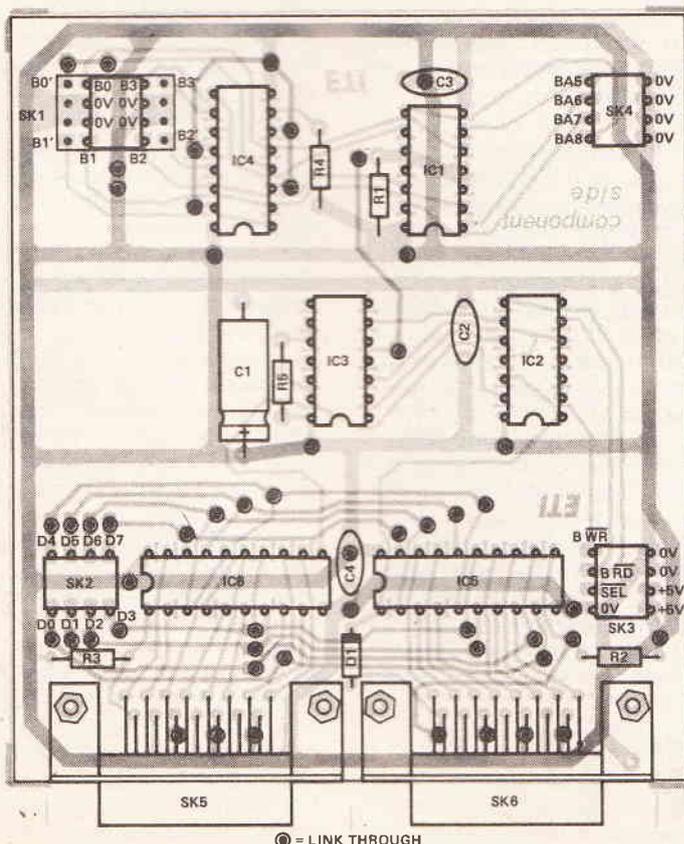


Fig. 7 I/O board PCB overlay.

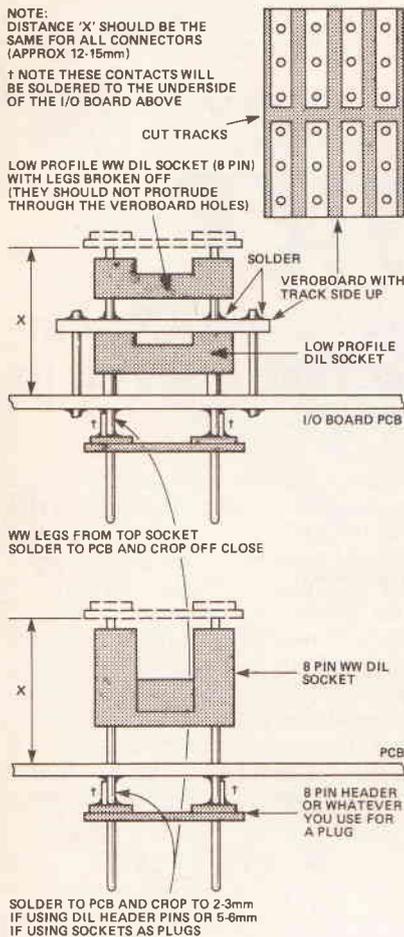


Fig. 8 Construction of SK1.

Insert but do not solder the other three 8 pin DIL sockets. Support the PCB such that it is level and parallel to a smooth flat surface and allow all the sockets to rest so that they are the same height above the PCB (with the DIL header parts plugged in). After making sure that they are also perpendicular to the PCB, solder them into position.

Now clip off the leads on the solder side to 2-3 mm (5-6 mm if you use DIL sockets instead of headers as the B plug parts). Insert the 8 pin (half of a 16 pin) DIL header plugs into the control board sockets and carefully position the I/O boards over them so that they are in the correct place. Now carefully solder them into position (this is the tricky bit!) — one or two pins only at this stage and then carefully remove the I/O board (now complete with plugs) from the control board and complete the soldering operation.

If you make more than one I/O card you can adjust the sockets to make sure that they all plug into each other. There should be enough lead length to allow this on all except SK1 so use this as a reference.

The reason for the elaborate construction is that the signals on SK1, the B signals, need to be processed on the I/O board before being passed onto the board above through a socket precisely above the socket through which they arrive. This construction technique is the reason for the double-height.

If you cannot get right-angled D connectors, take two ordinary D-type 15 way sockets and solder thicker than standard bare, single strand wires onto them. Bend these at 90° so that they fit into the holes on the board and let the sockets protrude a little over the edge of the board.

As many boards as are required may be made and stacked up on top of one another by means of the connectors described above, resulting in a sturdy tower. It is also a good idea to make a base for the system. Cut a piece of perspex, paxolin, SRBP or other plastic to the shape of the control board. Cut a smaller piece on the component side — dropping something conductive onto these strips could be fatal to the computer. The size of this piece is shown on the overlay diagram. Put the pieces of perspex in place and clamp them (not too tightly). Use a scribe to mark on the perspex the centre of the holes to be drilled in the PCB. Having done this, drill through the sandwich using a drill the size of the hole in the PCB — 2.5 mm or 0.1 inch if M2 or 8 BA bolts are to be used. Four bolts of each of two lengths will be needed — one set have the PCB and one layer of perspex to go through, the others have the PCB and two layers of perspex. It is advisable to make small spacers to go between the perspex and the board out of narrow bore plastic tube, to allow for the gap needed for the soldered connections. If no spacers are used, tightening the screws will cause unnecessary stresses in both the board and the perspex, leading to unsightly warping and possible damage to the board. Finally, glue four rubber feet onto the bottom of the lower perspex plate.

Testing

The first thing to do is to check your work until you are certain that it is perfect. Connect the control board up to the computer without the external power supply on and it should power up in the

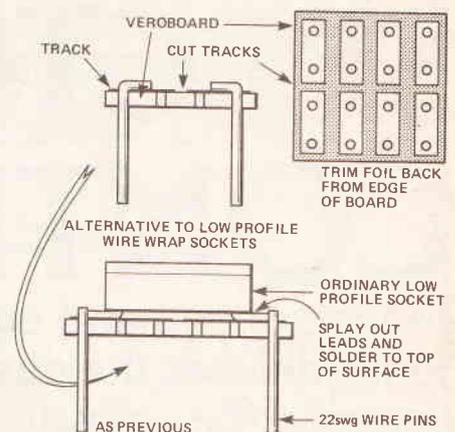


Fig. 9 Alternative for SK1 when low-profile wire-wrap sockets are not available.


usual way. If it does not, switch off IMMEDIATELY, and check the board until a fault is found. If this works, check that there is +5V across pins 7 and 14 or 8 and 16 as appropriate of all IC sockets, and across the +V and 0V connections of SK1.

Switch off the computer and disconnect the board from it. Connect up the external power supply and +5V should appear on pin 3 of IC1, but there should be no voltage detectable in any IC socket, nor on the connector back to the computer. If there is a voltage where there should not be, STOP NOW and check — it was at this point that the author blew every chip in his computer due to a faulty IC101.

If all is well, apply a voltage of 6V from batteries across 0V and +V on the edge connector and check that: —

- If only the battery supply is connected, the relay remains in its original position and 6V appears across the IC sockets.
 - If only the external power supply is connected, the relay stays in its original position and no voltage appears across any IC sockets.
 - If both supplies are in place, the relay clicks over, and 5V appears across the socket.
- Even if all these tests work, look for shorts all over the board with a magnifying glass, concentrating particularly on the power supply section.

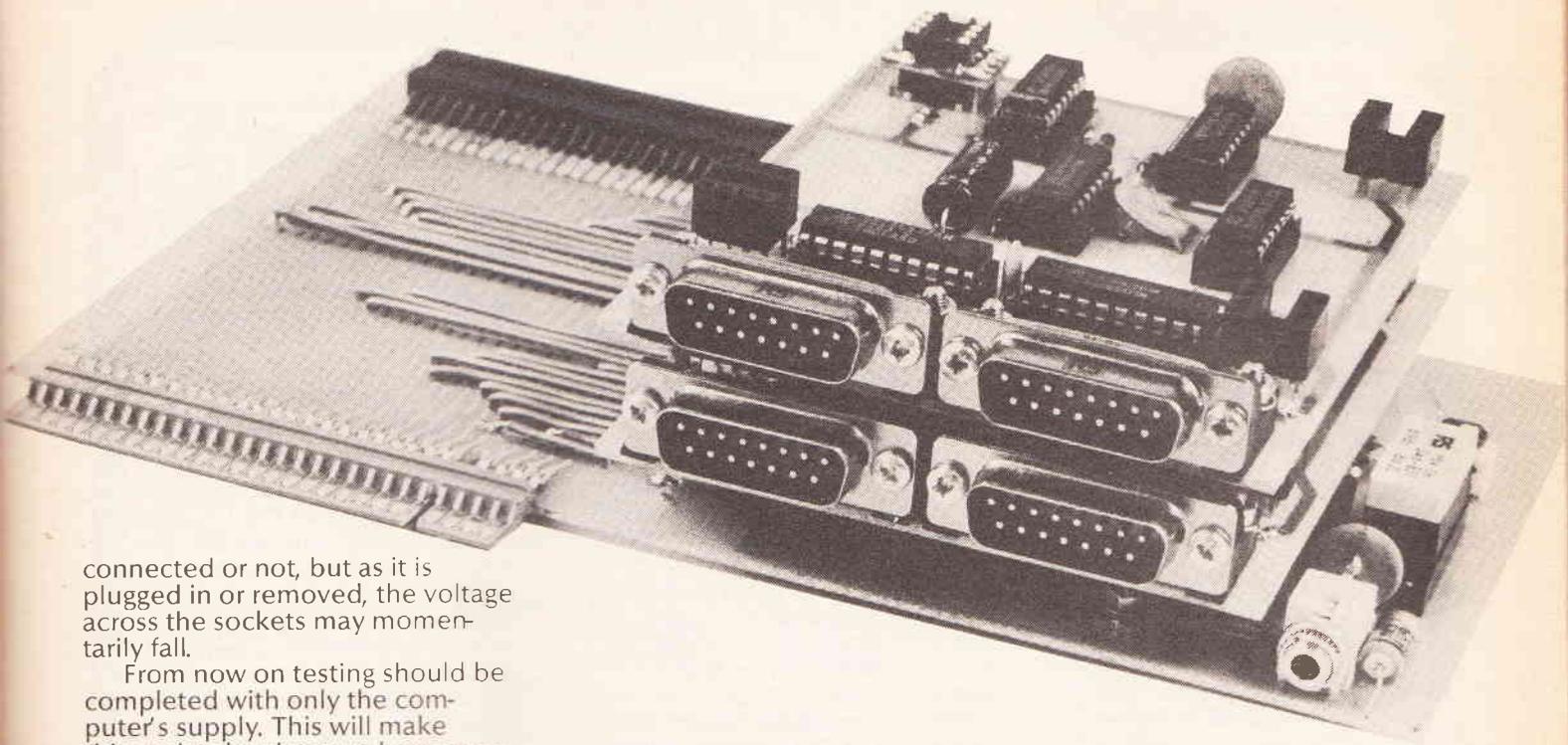If everything has gone smoothly, remove all power, plug in the computer and switch on. Now plug in the external supply, but be ready to remove it immediately at the smallest sign of anything going wrong. As it is plugged in, the relay should click. 5V should now be present across all IC sockets whether the external supply is



connected or not, but as it is plugged in or removed, the voltage across the sockets may momentarily fall.

From now on testing should be completed with only the computer's supply. This will make things simpler since we know now that the power supply section works perfectly. Switch off and insert IC102,103 and 104 in that order, making sure that power-up proceeds in the usual way between each one, and if anything fails, switch off the and check until a fault is found. Power should always be removed for the insertion or removal of any integrated circuit.

Now switch off and plug in an I/O board without ICs, then go through plugging in ICs 1,3,2,4,5 and 6 in that order, testing power up each time as before. When all is complete, it is time for the acid test: will it actually work? Wire two D-type plugs to connect the 8 inputs of the board to the corresponding output bits. Type in this program and run it, with SW101 on the control board set to "LO".

```
10 FOR A=0 TO 255
20 OUT 31,A
30 PRINT A, IN 31
40 NEXT A
```

On any line of the screen, both numbers should be the same. If the numbers are all incorrect switch off and look for a fault. If only some are incorrect, the faulty bit can be determined by comparing the binary equivalents of the printed numbers.

Now change the 31s in lines 20 and 30 to 16415, move SW101 to "HI", and check that the program runs as before. Also check that on SK1 the following signals are correct: B0=1, B1=0, B2=0.

BUYLINES

There should not be too many problems with parts for this project. All the ICs are available from Technomatic and Rapid. The right-angle D-type plugs used were purchased from Electrovalue; other types are available, but we would suggest checking that they will fit the PCB (D-types come in curious lead spacings). The PCBs will be available through our PCB service.

Check each subsequent board by replacing the first one with it and carry out the same tests. Finally, plug them all in and check that each responds to the address (0 or 16384)+31+32 X(the number of boards plugged in below the one in question).

Software And Use

If we wish to read from or write to the nth board in the stack in BASIC, then the address is:

$$31+(n-1)\times 32.$$

In machine code the instruction to use is IN A, nn or OUT nn, A provided SW101 is at "LO" and the board is the eighth in the stack or lower. If these conditions are not fulfilled, then we must resort to the instructions IN reg (C) and OUT (C), reg. Of course, these instructions will not fail to work in the first page, but those previously described will in most circumstances be more convenient. When the second type of instruction is used, register pair BC should contain this pattern:

Bit Number	Contents
0-4	all one
5-8	number of the board in the stack, zero for the lowest
9-13	all zero
14	state of SW101
15	zero

As an example, if we wish to continuously read numbers from the fourth board in the stack displaying the results on the screen, and output the one's complement of the number (all bits inverted) to the third board, this can be done as shown below (assuming SW101 is set to "LO").

```
From BASIC:
10 LET A = IN 127
20 PRINT A
30 POKE 23692, 100: REM
ENDLESS SCROLL
40 LET A = 255 - A
50 OUT 95, A
60 GOTO 10
```

```
or from machine code:
START IN A, 127
CALL PRINT
CPL
OUT 95, A
JR START
```

or by using the more general addressing method:

PROJECT: I/O Port

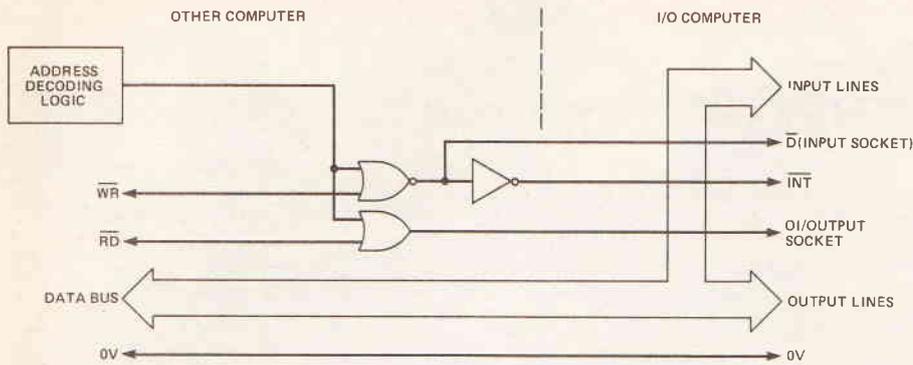


Fig. 10 Arrangements for exchanging data with another computer.

```

START LD BC, 127 d
      IN A, (C)
      CALL PRINT
      CDL
      LD BC, 95 d
      OUT (C), A
      JR START
    
```

Note that the machine code versions are both endless loops — they serve merely as examples.

Looking now at the user side of the hardware, there are several points to guard against:

1. Make sure that successive boards are plugged firmly into each other, and check that pins

have not become bent between uses. Bad connections will have unpredictable results, but are unlikely to cause permanent damage.

2. Never overload the Spectrum power supply — always use the external source when this is possible.

3. Be careful not to take so much current from the output IC that it heats up — this is one of the more costly integrated circuits.

4. It is unwise to connect both the + and the - connections on the input and output sockets to power rails of external hardware. If its

voltage is not quite the same as that of the Spectrum or I/O boards, damage could occur.

5. Remember to treat all hardware outside the computer with care. A second's carelessness in computer interfacing could cause havoc, even though every effort has been made to make the system virtually bomb-proof.

Data Exchange With Another Computer

Figure 10 shows the basic requirements of hardware used to pass data between the I/O computer (the one plugged into the control board) and another computer. With this hardware, it is the other computer which dictates when data transfer takes place. It reads when it wishes and sends the I/O computer an interrupt when it has placed some data to be read. The software side of utilizing Spectrum interrupts has been detailed several times recently in a variety of publications and is not of direct relevance to the I/O control system, so it is not considered here.

ETI

MICRORANGE ELECTRONICS

UNIT 258, STRATFORD WORKSHOPS, BURFORD ROAD (near Stratford Centre) LONDON E15 2SP. TEL: 01-536 1415

Recently opened component shop in the heart of Stratford, we have lots of special offers. (You will find us on the 2nd Floor.)

We specialize in the manufacture of:

Printed Circuit Boards. No quantity is too small.

We also supply: Photo Board and associated chemicals at very keen prices. See below:

6x4" Single sided 1.80
8x5" Single sided 2.10
6x4" Double sided 2.00
8x5" Double sided 2.40

Other sizes available
ALL PRICES INCLUDE VAT
Please add 50p for P&P

SOME SPECIAL OFFERS

(Many others in stock)

NE5534	1 off 1.15 10 off 1.05
NE5532	1 off 1.45 10 off 1.15
TL071	1 off 45p 10 off 42p
TL072	1 off 55p 10 off 50p
TL074	1 off 85p 10 off 78p
78P05 5V 10A Reg	5.50 each
7812 12V 1A Reg	30p each
VN67AF Power Fet	65p each
60W Spot Bulbs various colours	70p each
100W Spot Bulbs various colours	1.25 each
2 metre x 1 metre SPK Cloth	2.95
10x12" Fibreglass PC Board	2.25 each
150W Power amp module	12.50
3 Way 700W Sound to Lite unit	17.50
Telephone recording unit	15.00

Please come and see our range

ATTENTION TANGERINE OWNERS

*** 6809 ***

CPU BOARD

Runs with 80/82 or Colour Video Board

CONFIGURED FLEX

EPROM TO RAM CARD

SAE or Phone

RALPH ALLEN ENGINEERING CO.

Dept ETI

Fornsett End

Norwich

Tel: 095389 420

A BRITISH MADE OSCILLOSCOPE AT AN AFFORDABLE PRICE

The new Bridage single and dual trace oscilloscopes.


Single beam £195 Dual trace £225

★ Send for details today ★

Agents and distributors required worldwide.

Bridge Scientific Instruments
63-65 High Street, Skipton, North Yorkshire BD23 1EF.
Tel: (0756) 69511 (10 lines)

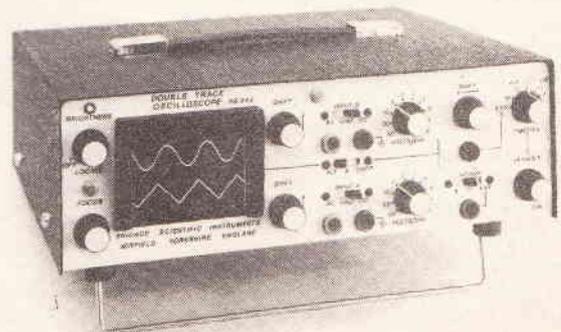Manufactured in association with Scopex Electronics Limited



hobbyboard

PROJECT DEVELOPMENT MATERIALS

ARTWORK MATERIALS TRACK TAPES

Precision slit black crepe tapes (1 roll/pack).



HB209	TAPE .020"	£1.05
HB210	TAPE .025"	£1.05
HB211	TAPE .031"	£1.05
HB212	TAPE .040"	£1.05
HB213	TAPE .050"	£1.05
HB214	TAPE .062"	£1.05
HB215	TAPE .080"	£1.20
HB216	TAPE .100"	£1.20

PADS

Pre-printed dense black on .0012 acetate film (500/roll)



	O/D	I/D	
HB222	PAD .062/.025		£3.05
HB223	PAD .075/.025		£3.05
HB224	PAD .100/.031		£3.05
HB225	PAD .125/.031		£3.05
HB226	PAD .150/.031		£3.05
HB227	PAD .180/.040		£3.05
HB228	PAD .200/.040		£3.05
HB229	PAD .220/.040		£3.05
HB230	PAD .250/.040		£3.05

IC PACK (Dual-in-line) Symbols

Pre-printed dense black on .0012 acetate film (125 symbols/pack)

●●●●●●	HB280/B	16 Pin DIL 1:1	£3.20
●●●●●●	HB281/B	16 Pin DIL 2:1	£3.45
○●○●○●○●	HB284/C	16 Pin DIL 1:1	£3.45
○●○●○●○●	HB285/C	16 Pin DIL 2:1	£4.00
●●●●●●	HB286/D	16 Pin DIL 1:1	£3.20
●●●●●●	HB287/D	16 Pin DIL 2:1	£3.45

CONNECTORS

Polyester Film-Strips 420mm Long

●●●●●●	HB/324	Conn/D 1:1 (20)	£7.10
●●●●●●	HB/325	Conn/D 2:1 (10)	£7.10
	HB/326	Conn/L 1:1 (10)	£7.10
	HB/327	Conn/M 2:1 (10)	£7.10

ARTWORK FILM & ACCESSORIES

Double Matt High Stability Polyester

HB202	Artwork Film A4 (5)	£1.78
HB/CKGA3	Precision Grid A3 (1)	£7.00
HB/352	Artwork Knife (1)	£1.44
HB/353	Blade 	(5) £0.40
HB/354	Blade 	(5) £0.50

ELECTRONIC PROJECT KITS

A special selection of popular electronic projects from Argus Publications is now available. A wide choice of interest is covered including ★Computing★Music★Hi-fi★Security★Novelty. All kits include PCB, components, case & panels and instructions, and are offered at prices to suit all pockets. SEND TODAY FOR OUR "ELECTRONIC KITS" BROCHURE.

PRINTED CIRCUIT MATERIALS

A small selection from our catalogue -

PLAIN COPPER CLAD PCB Top Quality FR4 Fibreglass

HB019	S/Sided 3"x4" (3)	£1.26
HB020	S/Sided 6"x4" (2)	£1.68
HB021	S/Sided 6"x9" (1)	£1.89
HB026	D/Sided 6"x4" (2)	£1.92
HB027	D/Sided 6"x9" (1)	£2.16

VEROBOARD

Pre-Pierced Stripboard



HB137 V/	Board 63x 95mm (1)	£1.10
HB138 V/	Board 63x127mm (1)	£1.27
HB140 V/	Board 95x431mm (1)	£5.00

PHOTO-RESIST PCB MATERIALS

Top Quality, Positive Photo-Resist PCB

HB031	Pos S/Sided 3"x4" (3)	£2.29
HB032	Pos S/Sided 6"x4" (2)	£2.73
HB050	Pos S/Sided 6"x9" (1)	£2.79
HB039	Pos D/Sided 3"x4" (3)	£2.86
HB040	Pos D/Sided 6"x4" (2)	£3.43
HB058	Pos D/Sided 9"x6" (1)	£3.49
HB062	Positive Developer (1 lit)	£2.06
HB012	Ferric Etchant (1 lit)	£1.78
HB014	Process Tray (1)	£2.54
HB017	Copper Cleaning Block (1)	£1.49

FULL PHOTO RESIST KIT

HB/2 Complete Photo Resist Kit £29.00

PHOTO-TOOL MATERIALS

PCB photo masters made to highly professional standards. UV Exposure. High intensity Image Positives or negatives for simplicity of multi-imaging.

HB3	Fototool Kit Complete	£27.00
HB101	Foto pos film 15x20cm (6)	£5.07
HB102	Foto pos film 20x30cm (6)	£8.77
HB105	Foto neg film 15x20cm (6)	£4.10
HB106	Foto neg film 20x30cm (6)	£6.49
HB109	Fototool Developer (1 lit)	£2.90
HB111	Fototool Fixer (1 lit)	£1.89

LABEL & PANEL MATERIALS

Convert Fototool masters into highly professional labels and panels. Simple process - durable finish. Packs include lamination film and Double sided adhesive.

HB114/YELL.	Yellow Fotolam 20x30 (3)	£2.76
HB114/BLUE.	Blue Fotolam 20x30 (3)	£2.76

COMPUTER LEADS & CABLES

A comprehensive range of Ribbon connectors, cables and connectors is available for most popular computing applications. SEND TODAY FOR OUR "COMPUTER LEADS & CABLES" BROCHURE.

PRINTED CIRCUIT EQUIPMENT


LOW COST D.I.Y. EXPOSURE UNIT

Photo-resist and FOTOTOOL materials require exposure to UV light - the type of light used determines the quality of reproduction - this simple-to-make D.I.Y. kit comes complete with UV lamp, holder, shade etc. and full working instructions to build your own glass contact frame - KIT HB/UV1 D.I.Y. EXP. UNIT £27.00



PRINTED CIRCUIT DRILLING MACHINE

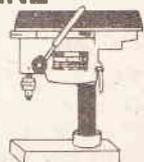COMPACT 2- SPEED PCB DRILLING M/C MAINS POWERED. PRECISION MACHINE FOR PRECISION DRILLING.



HB 187 PCB DRILL £152.00

PCB DRILLS (CARBIDE)

LONG LIFE SOLID CARBIDE FOR PRECISION



HB189	CARBIDE DRILL	0.9mm (1)	£2.02
HB190	CARBIDE DRILL	1.0mm (1)	£2.02
HB191	CARBIDE DRILL	1.1mm (1)	£2.02
HB192	CARBIDE DRILL	1.3mm (1)	£2.02
HB193	CARBIDE DRILL	1.6mm (1)	£3.05
HB194	CARBIDE DRILL	2.0mm (1)	£4.09
HB195	CARBIDE DRILL	3.0mm (1)	£5.22

COMPUTER ADD-ONS

A comprehensive range of add-on Kits (or ready-built units) is offered for ★ROBOTICS★ ★MUSIC★ ★SPEECH★ ★Scientific Development★ SEND TODAY FOR OUR "COMPLETE ADD-ONS" BROCHURE, which describes all kits. Available for most popular computers.

FULL HOBBYBOARD CATALOGUE AVAILABLE

ORDER FORM ETI/11/4

QTY REF DESCRIPTION PRICE TOTAL

Please send me full Hobbyboard

Catalogue Computer Add-ons
Electronics Kits Computer Cable

Name

Address

Cheque / PO enclosed for £

ACCESS



KELAN ENGINEERING LTD.
Circuit Products & Components Division,
27-29 Leedhall Lane - Harrogate,
North Yorkshire HG2 9NJ.

A FARNELL ELECTRONICS COMPANY Tel: (01423) 870838.

BBC Micro Computer System OFFICIAL DEALER

ACORN COMPUTER SYSTEMS

BBC Model B Special offer	£320 (a)
BBC Model B+Econet	£389 (a)
BBC Model B+DFS	£400 (a)
BBC Model B+DFS +Econet	£450 (a)

UPGRADE KITS

A to B Upgrade Kit	£75 (c)
DFS Kit	£95 (c)
Econet Kit	£45 (c)
Speech Kit	£47 (c)

ACORN ADD-ON PRODUCTS

Z80 2nd Processor	£352 (a)
6502 2nd Processor	£175 (b)
Teltext Adaptor	£190 (b)
IEEE Interface £282	282 (b)
Prestel Adaptor	£99 (b)
RH Light pen	£39.50 (c)

TORCH UNICON products including the IBM Compatible GRADUATE in stock
For detailed specification on any of the BBC Firmware/Peripherals listed here or information on our complete range please write to us.

BBC FIRMWARE

1.2 Operating System	£7.50 (d)
Basic II ROM	£22.50 (d)
View Word Processor ROM	£48.00 (c)
Wordwise Word Processor ROM	£34.00 (d)
BCPL ROM/Disc	£86.00 (b)
Disc Doctor/Gremlin Debug ROM	£28 (d)
EXMON/TOOL KIT ROM	£28 ea (d)
Printmaster (FX80)/Graphics ROM	£28 ea (d)
ULTRACALC spreadsheet ROM	£69 ea (c)
COMMUNICATION ROM	
Termi Emulator	£28 (d)
Communicator	£59 (d)
Commstar	£29 (d)

DISC DRIVES

These drives, fitted with high quality slim line Japanese mechanisms are supplied in attractive cases with BBC matching colour and come complete with data and power leads, manual and formatting disc. The 40/80T switching is supplied as standard on TEAC 80T drives. Single drives are supplied with or without power supply. All dual drives are supplied with integral switch mode power supply. TEAC & MITSUBISHI drives are compatible for both single and double density operation. These drives can also be used with any other micro with a Shuggart A400 interface.

1 x 100K TS55A (40T) TEAC	£100 (a)	CS55A TEC with PSU	£135 (a)
1 x 200K TS55E (40/80T) TEAC	£155 (a)	CS55E TEC with PSU	£165 (a)
1 x 400K TS55F (40/80T) TEAC	£185 (a)	CS55F MIT. with PSU	£195 (a)
2 x 100K TD55A (40T) TEAC with PSU	£300 (a)	40/80T Switch Module	£30 (c)
2 x 200K TD55E (40/80T) TEAC with PSU	£375 (b)	3" Hitachi 100K Drive	£115 (b)
2 x 400K TD55F (40/80T) TEAC with PSU	£420 (a)	TD55M (80TG) Mitsubishi	£400 (a)

SCOTCH 3M DISCS

This month we are offering these high performance 5.25" discs at a bumper bargain price for a limited period. The prices will be valid for orders received before 15th October. These industry standard discs have been manufactured with advanced techniques are of such high quality that their error-free performance is guaranteed for life. If ever their is a disc failure, the disc is replaced without question.

40 Track SSDD	£12.50	40 Track DSDD	£17 (c)
80 Track SSDD	21 (c)	80 Track DSDD	£22 (c)

PRINTERS

Our wide range of printers offer a choice of printer for every requirement at competitive prices. We have the full EPSON range which sets the industry standards for reliability, flexibility and versatility. The new KAGA TAXAN range provides the NLQ printing fonts and other new exciting features. For those wanting the correspondence quality printing we have the BROTHER and JUKI printers. To support our range of printers we also carry a wide range of printer interfaces, accessories and consumables.

EPSON: RX80FT £225 (a); FX80 £318 (a); FX100 £460 (a);
KAGA TAXAN: KP 810 £249 (A); KP910 £369 (a);
BROTHER: HR15 £350 (a); EP44 £199 (a);
JUKI: 6100 £359 (a).

ACCESSORIES

EPSON Serial Interface: 8143 £35 (b); 8148 with 2K buffer £50 (b).
EPSON Paper Roll Holder £17 (b); FX80 Tractor Attach £37 (b); RX/FX80 Dust Cover £4.50 (d).
EPSON Ribbons: MX/RX/FX80 £6.50; MX/RX/FX100 £12.50 (d).
JUKI: Serial Interface £60 (a); Tractor Attach. £99 (a); Sheet Feeder £199 (a); Ribbon £2.50 (a).
BROTHER HR15: Sheet Feed £199 (a); Ribbons - Carbon or Nylon £3; Multistrike £5.50 (d); 200 Sheets Fanfold with extra fine perf. 9.5" - £13.50; 115" £17.50 (b).
BBC Parallel Lead £8; Serial Lead £7 (d).

DRIVE ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives	£14.50 (c)
Single Disc Cable	£6 (d)
10 Disc Library Case	£195 (c)
30/40 Disc Lockable Box	£14 (c)
Dual Disc Cable	£8.50 (d)
30 Disc Storage Box	£6 (c)
70/80 Disc Lockable Box	£19 (b)

MONITORS

A choice of high quality RGB Monochrome monitors is available. The British made MICROVITEC Std/Med/Hi Res RGB monitors which offer a consistent reliable performance are also available in RGB/PAL/AUDIO versions. The KAGA RGB range provides a similar performance in 12" screen format. Japanese made SANYO and KAGA Hi Res green screen monitors provide an ideal solution for high clarity 80 column text display. All monitors are supplied with a lead suitable for BBC computer at no extra charge.

MICROVITEC 14" RGB

1431 Std Res £195 (a); 1431AP std Res PAL/Audio £215 (a);
1451 Med Res £295 (a); 1441 Hi Res £399 (a);
2031 20" Std Res £360 (a); Plinth for 14" Monitors £8.50.
Microvitec Monitors with TTL/Linear Inputs also available.

KAGA VISION III

Hi Res 12" RGB £358 (a);
Green Screens: KAGA 12G £106 (a); SANYO DM8112CX £99 (a);
Swivel Stand for Kaga Green £22.50 (b);
BBC Leads: KAGA RGB £5 Microvitec £3.50; Monochrome £3.50 (d).

MODEMS

Our range of modems include: TELEM0D-2, a BT approved V23 1200/75 and 1200/1200 modem, ideal for PRESTEL use £65 (b). BBC cable £3.50. BUZZBOX, a very compact BT approved V21 300/300 Baud, battery operated modem ideal for inter-computer communication, bulletin boards etc. £65 (c). BBC lead £3.50. External PSU £8. MINOR MIRACLES WS-2000 - the ultimate multi-standard modem, covering all common BELL and CCITT standards up to 1200 baud. The optional 'auto-answer' and 'auto-dial' boards gives this modem the greatest potential of all £129. Please phone for details of accessories and our comprehensive range of communication software.

EPROM II PROGRAMMER

Our current version of the highly popular Eprom programmer is now available enhanced to provide more and better facilities for easy programming by the user. The software will maintain its superiority over all currently available similar programmers. The range of eproms handled has been widened, to include the eproms with lower programming voltage and eproms which can be programmed using fast algorithms. Control of all operations has been moved to the keyboard. The screen display has been improved to give more information. The screen editing facilities have also been modified to simplify the data entry.
* The new Eprom Programmer will now program 2516, 2532, 2564, 2716, 2732, 2764, 27128 and 27128 + 5v eproms, and all but the 27256 in a single pass.
* The programmer will be supplied with integral power supply, and interfaces with the BBC via the 1MHz bus. It is fully buffered and complies with Acorn protocols. There is no power drain from the computer.
Please telephone for further details.

SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV - has a serial and parallel I/O routines. Can be used as an emulator, cassette interface.
Softy II £169.00 (b)
Adaptor for 2764/2564 £25.00 (c)

ATTENTION

All prices in this double page advertisement are subject to change without notice.
ALL PRICES EXCLUDE VAT
Please add carriage 50p unless indicated as follows:
(a) £8 (b) £2.50 (c) £1.50 (d) £1.00

SPECIAL OFFER

2764-25	£4.90
27128-25	£1
27128-30	£17
6264-15	£28
6262LP-15	£31
6264-12	£35

CONNECTOR SYSTEMS

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header Plug	Receptacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	180p	340p
50	235p	200p	380p

D CONNECTORS

No. of ways				
MALE	9	15	25	37
Solder	80p	105p	160p	250p
Angled	150p	210p	250p	365p
FEMALE				
Solder	105p	160p	200p	335p
Angled	165p	215p	290p	440p
Hoods	90p	85p	90p	100p
IDC 25-way plug	385p	Socket 450p.		

TEXTTOOL ZIF

SOCKETS	24-pin	£5.75
	28-pin	£8.00
	40-pin	£9.75

DIL SWITCHES

4-way	90p	6-way	105p
8-way	120p	10-way	150p

EDGE CONNECTORS

2" x 6-way (commodore)	0.1"	0.156"
2 x 10-way	150p	300p
2 x 12-way (vic 20)	—	350p
2 x 18-way	—	140p
2 x 23-way (ZX81)	175p	220p
2 x 25-way	225p	220p
2 x 28-way (Spectrum)	200p	—
2 x 36-way	250p	—
1 x 43-way	260p	—
2 x 22-way	190p	—
2 x 43-way	395p	—
1 x 77-way	400p	500p
2 x 50-way (\$100conn)	600p	—

EURO CONNECTORS

DIN 41612		
2 x 32 way St Pin	230p	275p
2 x 32 way Ang Pin	275p	320p
3 x 32 way St Pin	260p	300p
3 x 32 way Ang Pin	375p	400p
IDC Skt A + B	275p	
IDC Skt A + C	350p	

For 2 x 32 way please specify spacing (A + B, A + C).

AMPHENOL CONNECTORS

36-way plug Centronics Parallel	IDC £5.25
Solder £5.25	
36-way socket Centronics Parallel	IDC £5.50
Solder £5.50	
24-way plug IEEE Solder £5	IDC £4.75
24-way socket IEEE Solder £5	IDC £4.75
PCB Mtg Skt	
Any Pin 24 way Solder 600p	
36 way ZOC 650p	

RIBBON CABLE

(grey/metre)	
10-way	
16-way	
20-way	
26-way	
34-way	
40-way	
50-way	
64-way	

RS 232 JUMPERS

(25 way D)		
24" Single end Male	£5.00	
24" Single end Female	£5.25	
24" Female Female	£10.00	
24" Male Male	£9.50	
24" Male Female	£9.50	

DIL HEADERS

Solder	
14 pin	40p
16 pin	50p
24 pin	100p
28 pin	200p
40 pin	200p

TEST CLIPS

14-pin	375p	16-pin	400p
		40-pin	£10.30

ACTIVE-8 LOUDSPEAKER

Having discussed the design process at some length in the first two articles in this series, Barry Porter now turns his attention to the construction.

The time has now arrived to do your Chippendale impression, having first checked that your home insurance policy covers such unlikely events as drilling holes in the dining table and spreading the latest high technology glue over the G-Plan.

Figure 1 shows the cabinet construction in sufficient detail to enable the average DIY duffer to build a pair without too many tears. The exact method of assembly is not too important, providing the final result is rigid and all joints are airtight.

Do not attempt to cut the veneered panels with a hand-saw — find a supplier who is willing to cut them for you using a high speed circular saw. This will ensure that the edges are square, which is essential if you want the final result to have a professional appearance. The bare edges

should be covered with matching strip veneer. Avoid the type that is ironed on — plain veneer is much better, and when attached with contact adhesive is less likely to drop off.

The most difficult part of the cabinet construction is preparing the front baffle. The drive units should be recessed using the templates provided to mark out the panel before commencing. If you do not have the correct tool to route out the rebated areas, it can be done by cutting through the veneer with a sharp knife, and forming the rebate with a chisel.

Recess an area around the tuning vent to a depth of 3.5 mm using the T33 template. This is for the interchangeable escutcheon which is replaced with a similar sized blanking plate for closed box operation. These plates should be made from 10SWG alloy with a

75 mm diameter hole in the escutcheon. They should have four fixing holes in the same positions as the T33.

The escutcheon and both drive units should be attached by M4.5 x 20 machine screws with Tee nuts fixed to the inside of the baffle. Do not be tempted to fix the units with woodscrews, even though you will find some enclosed with the T33; use these for hanging your holiday snaps on a wall instead.

Before fitting the drive units, half fill the cabinet with BAF wadding or medium density polyurethane foam blocks, taking care not to pack the area behind the vent too tightly and leaving a six inch clearance around the base unit.

A suitably sized hole for the lead-out wires should be drilled through the cabinet bottom and made airtight by a liberal application of glue from the inside. The cable should be firmly attached to the inside of the enclosure with 'P' clips so that, if it is accidentally pulled, the connecting tags on the drive units will not be damaged.

If you know that the amplifier you will be using has a common output earth terminal a 3-core connecting lead is sufficient, but if the speakers are ever likely to be used with unknown amplifiers, separate connections to each drive unit should be made available. Four core mains cable is quite suitable for this purpose, as only short lengths are used.

The prototype cabinets were fitted with 50 mm dual wheel Kenrick castors, which certainly eased the job of moving them around during construction. If you are a believer in the theory that loudspeakers should be mounted on reinforced concrete pillars that

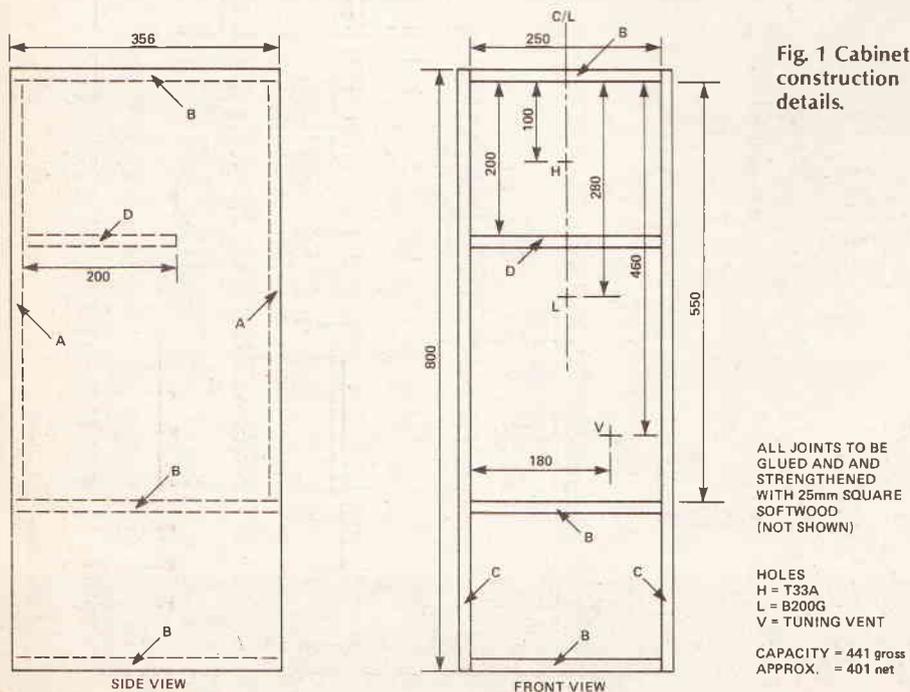


Fig. 1 Cabinet construction details.

ALL JOINTS TO BE GLUED AND AND STRENGTHENED WITH 25mm SQUARE SOFTWOOD (NOT SHOWN)

HOLES
H = T33A
L = B200G
V = TUNING VENT

CAPACITY = 441 gross
APPROX. = 401 net

descend half a mile into the bedrock (when surely seismic disturbances will influence the sound quality?) the castors can be replaced with carpet piercing spikes. In practice, no advantage has been found by doing this, which pro-

PARTS LIST — MOTHER BOARD & PSU

RESISTORS (all ¼ W 1% metal film unless otherwise stated)

R1,2	1k8
R3,4	8k2
R5,6	10k
R7	47k (see text)
R8,9	22R
R71	4k7
R72	2k2
R73	56R ½W
R74,75	1k5

CAPACITORS

C1,2	1n0 polystyrene
C3	22p polystyrene
C4	100n polycarbonate
C5,62	22µ 16v non-polarised electrolytic
C6,7,64,65	100µ 25V radial electrolytic
C8,9,66-69	100n polyester
C61	10µ 25V radial electrolytic
C63	1000µ 25V radial electrolytic
C70,71	4,700µ 40V electrolytic (see text)

SEMICONDUCTORS

IC1	NE5534
IC9	7815
IC10	7915
Q6	BC143 or any PNP 1A T05 transistor
BR1	50V 2A bridge rectifier
BR2	209V 5A bridge rectifier
D2-5	1N4148
LED1	any panel-mounting LED

MISCELLANEOUS

FS1	200mA anti-surge fuse and PC-mounting holder
FS2	1A anti-surge fuse and panel-mounting holder
RL1	DPCO relay, 12V coil
RL2	DPCO relay, 12V coil, mains contacts
SW1	SPCO PC mounting
SW2	SPDT slide, toggle, etc.
T1	6-0-6V 3VA PC-mounting transformer
T2	12-0-12V, 500mA transformer

PCB; 5 off 10 way PCB plugs; relay holders as desired; mains outlet; audio connectors; cable, cable clips, etc.

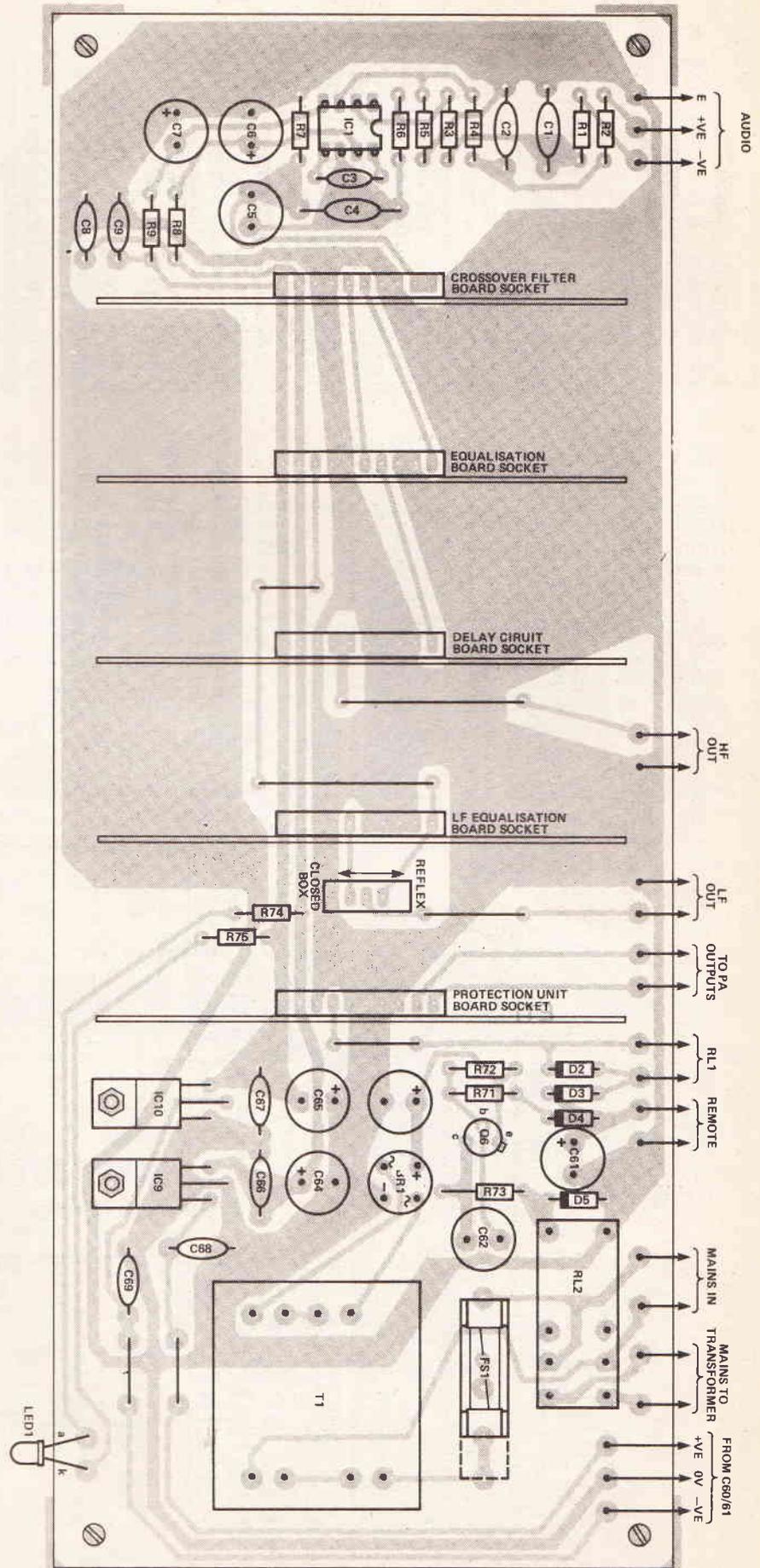


Fig. 2 Overlay of the mother board.

bably says something about the author's hearing or the quality of his living room carpet.

Should the final appearance require the drive units to be hidden from small sticky fingers or an inquisitive budgerigar, suitable grilles can be made from 12.5mm plywood covered with open weave material. Cut away the centre of the plywood to the point where the remaining frame is well clear of the units, while retaining sufficient strength to stay flat — about 50mm should cause no problems. Give the frame a coat of matt black paint before glueing or stapling the covering material into place. Attachment to the speaker

PARTS LIST — LF EQUALISATION CIRCUIT

RESISTORS (all 1/4 W metal film)

R48,49	4k7
R50,53	110k
R51,52	15k4
R54,55	200k
R56	47k
R57,58	22R

CAPACITORS

C46	1 μ 0 polycarbonate
C47,50	47n polycarbonate
C48	68n polycarbonate
C49	6n8 polystyrene
C51	100n polycarbonate
C52	22 μ 16V non-polarised electrolytic
C53,54	100 μ 25V radial electrolytic
C55,56	100n polyester

SEMICONDUCTOR

IC8	NE5532
-----	--------

MISCELLANEOUS

PCB; 10-way PCB socket.

Construction

To make the filter unit as flexible as possible (not in the bendy sense), the mother board method of construction is employed. Although this is more costly in terms of the number of individual circuit boards, it does mean that changes can be introduced quite easily, and fault correction usually means replacing a plug-in board with a spare one.

The suggested mother board layout is shown in Fig. 2, and its overall size allows considerable freedom of choice when selecting a suitable enclosure.

Some circuitry has been placed on the mother board, namely the

PARTS LIST — PROTECTION UNIT

RESISTORS (all 1/4 W metal film unless otherwise stated)

R59,60	39k
R61	220k
R62	100R
R63	100k
R64,69	10k
R65,66	56k
R67	22k
R68	330R
R70	27R 2.5W

CAPACITORS

C57	100 μ 25v non-polarised electrolytic
C58	100 μ 25v radial electrolytic
C59,60	100n polyester

SEMICONDUCTORS

Q1,3,4	BC184
Q2	BC214
Q5	BC143 or any 1A PNP T05 transistor
D1	1N4148
ZD1	6V2 300mW Zener

MISCELLANEOUS

PCB; 10-way PCB socket.

Components not mounted on the circuit boards include the connectors, power supply transformer, rectifier bridge and smoothing capacitors. Ideally a toroidal mains transformer should be used, but as the circuitry is fairly tolerant of radiated hum fields a suitably specified frame type should not cause problems. The main smoothing capacitors should be at 4700 μ f 40V, but if space is not at a premium 10,000 μ f components can be used to advantage. These should be firmly clamped to the cabinet, and the rectifier bridge mounted directly to the supply rail terminals.

The type of signal connector used will probably be decided by the constructors financial status, but the input signals should be connected via multi way sockets with at least four pins. Good quality DIN connectors are acceptable, but professional XLR connectors are preferable. The accepted standard is that signal inputs use chassis mounted sockets, the type required for the 'Active-8' inputs being terms XLR-4-31. These should be wired to the following convention:

unbalanced, using an insulated phone socket. If you want to stick with professional connectors, the outputs should employ XLR-3-32 chassis mounting plus with signal on Pin 2 and Pins 1 and 3 joined to earth.

Whether used balanced or unbalanced, the input amplifier is DC coupled to the signal source, working on the assumption that pre-amplifier output stages are normally AC coupled. If you use one that isn't, it is quite permissible to place 10 or 22 μ f non polarized capacitors between the input socket and circuit board (not forgetting to place a 0.1 μ f polycarbonate in parallel).

The internal wiring is shown in Fig. 4, and should present no problems. (On reflection, if you have progressed this far without being removed by men in white coats, you will probably build the filter unit blindfolded!)

Next month we will conclude the construction details with the delay section overlay, and give Buylines (so don't phone us!). We'll also give some suggestions for extensions.

ETI

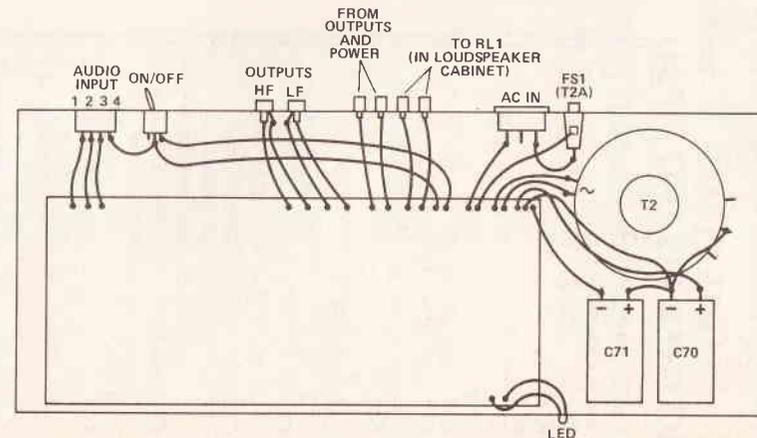


Fig. 4 Internal wiring diagram (note — BR2 not shown).

can be by the usual plastic socket fixings or, less attractively, strips of adhesive backed Velcro. If you intend packing your amplifier and filter unit in the open area at the bottom of the cabinet, the grille should be made long enough to hide the inevitable jumble of connecting cables from sight.

Once the cabinets are built and drive units installed, they may be set aside while work proceeds with the active crossover filters.


input amplifier, power supply stabilisers and remote mains switching unit, but the filter and equalisation stages are mounted on the plug-in cards shown in Fig. 3 (except for the delay unit, which will be given next month due to lack of space). Note that two locations are shown for R7; it should normally be placed at the output of the buffer, but if, for any reason, the buffer is not to be used, it should be placed at the input of the crossover filters instead.

- Pin 1 — Signal earth
- Pin 2 — Signal +
- Pin 3 — Signal —
- Pin 4 — Remote switching

If you use an unbalanced feed from your pre-amplifier, this should be taken to Pin 2, with Pins 1 and 3 joined together in the XLR cable plug.

The filter unit output is at low impedance, and the connection to the power amplifier should be

Fig. 3 Overlay of the protection, LF equalisation, crossover filters and equaliser sections.

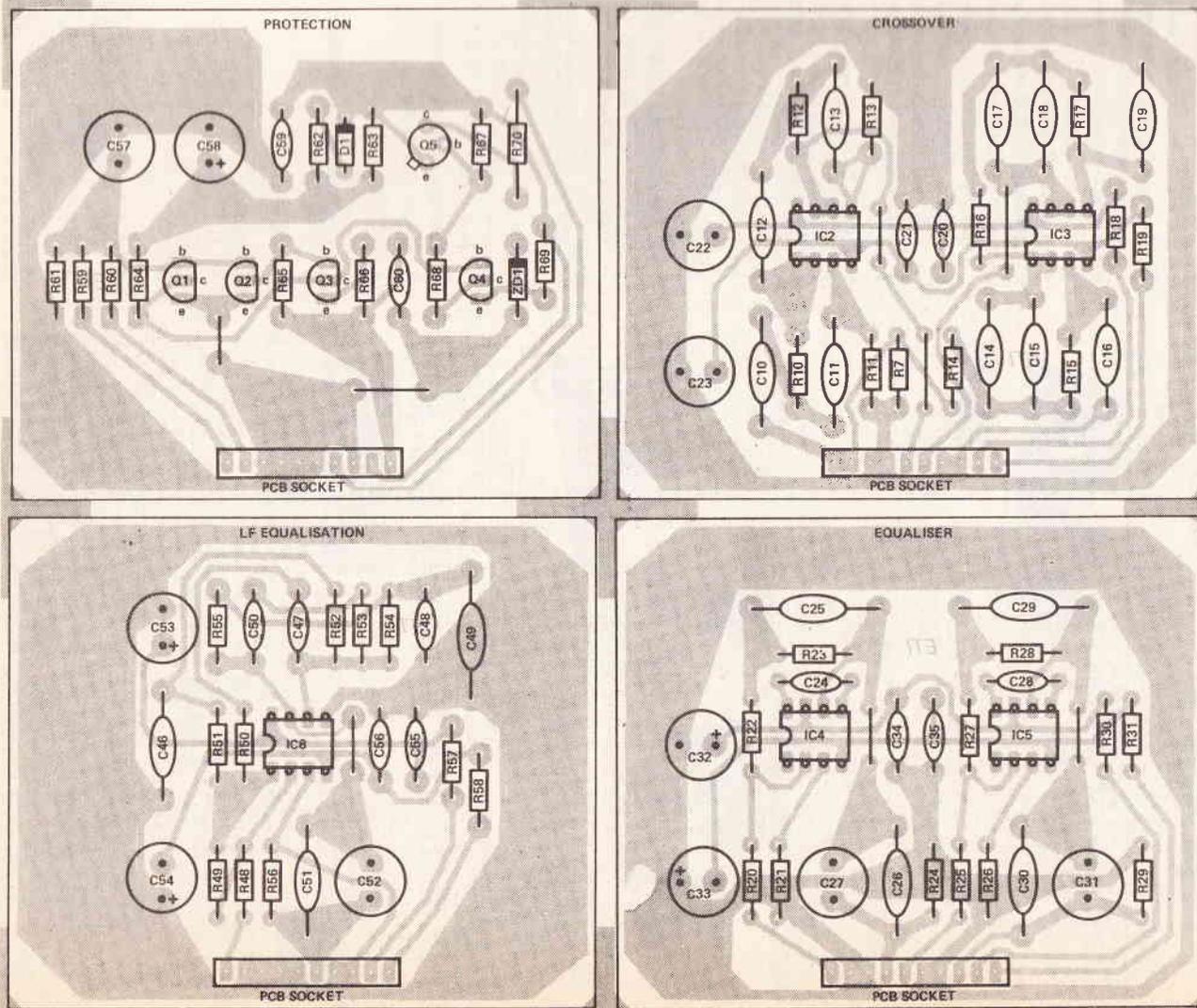

PARTS LIST — CROSSOVER FILTERS

RESISTORS (all ¼ W 1% metal film)	
R7	47k (see text)
R10,12,14,15,16,17	11k
R11,13	22R
R18,19	22R

CAPACITORS	
C10-19	3n3 polystyrene 2.5%
C20,21	100n polyester
C22,23	100µ 25V radial electrolytic

SEMICONDUCTORS	
IC2,3	NE5532

MISCELLANEOUS
PCB; 10-way PCB socket.

PARTS LIST — EQUALISER

RESISTORS (all ¼ W 1% metal film)	
R20,27,28	10k
R21,26	100R
R22	6k8
R23	3k9
R24,29	47k
R25	20k
R30,31	22R

CAPACITORS	
C24,28	22p polystyrene 2.5%
C25	10n polystyrene 2.5%
C26,30	100n polycarbonate 2.5%
C27,31	22µ 16V non-polarised electrolytic
C29	33n polystyrene 2.5%
C32,33	100µ 25V radial electrolytic
C34,35	100n polyester

SEMICONDUCTORS	
IC4,5	NE5534

MISCELLANEOUS
PCB; 10-way PCB socket.

T.V. SOUND TUNER

SERIES II BUILT AND TESTED Complete with case. **£26.50 + £2.00 p&p.**

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/2". E.T.I. kit version of above without chassis, case and hardware. **£16.20 plus £1.50 p&p.**



Also available with built-in headphone amp. **ONLY £32.50 + £2.00 p&p.**

HI-FI SPEAKER BARGAINS



TOKUDEN - 8", 8 ohm full range 7 1/2 W twin cone speaker. **£3.50 + £1.10 p&p.**


GOODMANS
12", 65W, impedance 4 ohms. Freq. res.: 35 - 6,500 Hz. Magnet: 3/4" x 4 1/4" dia. Foam surround vinyl laminated cone. For use in Hi-Fi systems up to 65 watts. Bass/Mid. **£15.95 - £2.20 p&p.**
7" 60W Bass/Mid. speaker. 8 ohm impedance. Freq. res.: 40 - 6,000 Hz. 4 1/2" x 3 1/4" magnet. **£14.95 - £1.75 p&p.**
4 1/2" 25W Bass/Mid. speaker. 4 ohm impedance. With rolled surround. **£4.95 - £1.50 p&p.**
Tweeters - 8 ohm soft dome radiator type. (3 3/4" sq.) For use in systems up to 40 watts. **£3.95 ea. + £1 p&p. or £6.95 pr. + £1.50 p&p.**

EAGLE
Full range 8" 20W, 8 ohm. Twin cone with rolled surround. **£6.95 + £2.20 p&p.**
Full range 6 1/2" 15W, 8 ohm. Twin cone with rolled surround. **£5.95 + £2.20 p&p.**
Full range 4" 8W, 8 ohm. With rolled surround. **£4.95 + £1.50 p&p.**

125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

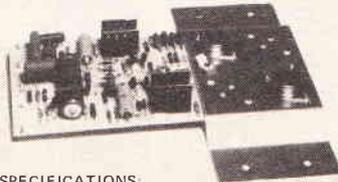Accessories: Stereo mains power supply kit with trans **£10.50 + £2 p&p.** Mono: **£7.50 + £2 p&p.**



SPECIFICATIONS:
Max. output power (RMS): 125 W. Operating voltage (DC) 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £12.00 + £1.15 p&p **BUILT £17.50 + £1.15 p&p**

NICAD CHARGERS/BATTERIES



SAFT/MAZDA BATTERIES:
RX6 (HP7/AA size) £1.10 ea. or 4 for £3.50.
RX14 (HP11/C size) £2.45 ea. or £4.10 a pair.
RX22 (PP3 size) 9 volt. £4.95 ea., £9.00 a pair.
50p p&p per order on batteries.
SAFT/MAZDA RX22 Charger (takes 2 PP3's) £2.75 + 80p p&p.
UNIVERSAL CHARGER, takes 4x AA's, or 4 C's or D's + 1 PP3. **£5.50 + £1.40 p&p.**

PAIR 10W SPEAKERS

Incorporates 4 1/2" 10 watt speaker. Finished in teak veneer simulate. Built, ready to use. Ideal extension spkrs. 12 1/2 x 7 1/2 x 4 1/4 ins. **£14.95 + £1.75 p&p.**

STEREO TUNER KIT

SPECIAL OFFER!

£13.95 + £2.50 p&p.

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with PE (July 81) For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. Front scale size 10 1/2" x 2 1/2" approx. With diagram and instructions.


MONO MIXER AMP

Ideal for halls and clubs. **£45.00 + £2 p&p.**

50 Watt, six individually mixed inputs for 2 pickups (Cer. or mag), 2 moving coil microphones and 2 auxiliary for tape tuner, organs etc. Eight slider controls - 6 for level and 2 for master bass and treble, 4 extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 W RMS (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

BSR RECORD DECKS

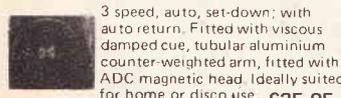Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge. **£12.95 plus £1.75 p&p.**



3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ADC magnetic head. Ideally suited for home or disco use. **£25.95**
Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. **£14.95 plus £1.75 p&p.**

All mail to: **21E HIGH ST, ACTON W3 6NG.** Callers: Mon - Sat 9.30 - 5.30, Half day Wed. Access phone orders on 01-992 8430. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/9/84 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.


CALLERS TO: **323 EDGWARE ROAD, LONDON W2.** Telephone: **01-723 8432.** (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.



FIND YOUR WAY THROUGH THE DIGITAL ELECTRONICS MAZE

First there was **SUPERKIT**

and now... **NEW SUPERKIT II**

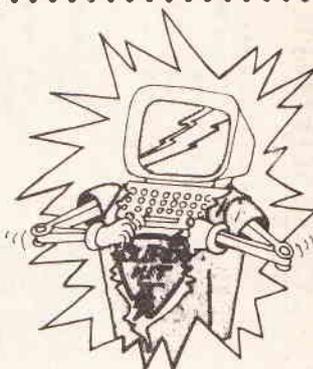

This practical self-instruction kit has been developed to extend the original beginners' **SUPERKIT**. **SUPERKIT II** includes an instruction manual and many more components, enabling you to design and use adders, subtractors, counters (ripple, up/down, synchronous, decade and Gray code), registers, pattern recognisers and 7-segment displays. You need the board and components from **SUPERKIT** to enable you to build the circuits in **SUPERKIT II**. Together the two kits provide an excellent introduction to digital electronics - what really goes on inside a computer.

SUPERKIT (SUP) £22.00 **SUPERKIT II (SUP II) £16.00**
Special price £35.00 for both (SUP + II) (inc. VAT and p & p)

The **SUPERKIT** series is backed by our theory courses, **DIGITAL COMPUTER LOGIC** (beginners' course), which covers the design of logical circuits, and **DIGITAL COMPUTER DESIGN** (more advanced), which covers the design of digital computers. **MICROPROCESSORS AND MICROELECTRONICS** teaches you what a microprocessor is and what it can do.

DIGITAL COMPUTER LOGIC (DCL) £7.00
DIGITAL COMPUTER DESIGN (DCD) £9.50
MICROPROCESSORS AND MICROELECTRONICS (MIC) £6.50

Please send for full information on these and our other courses. **GUARANTEE** If you are not completely satisfied, return the item to us within 28 days for a full refund. All prices include worldwide surface postage (ask for prepayment invoice for airmail). Allow 28 days for delivery in UK. Overseas payment by international credit card or by bank draft drawn on a London bank.

CAMBRIDGE LEARNING LTD, Unit 14, Rivermill Site, FREEPOST, St Ives, Cambs PE17 4BR, England.
Tel: 0480-67446

VAT No 313026022 Transcash No 2789159 Reg No 1328762

Please send me (initial letters used):

..... **SUP** @ £22.00 **DCL** @ £7.00
..... **SUPII** @ £16.00 **DCD** @ £9.50
..... **SUP + II** @ £35.00 **MIC** @ £6.50

I enclose a cheque/PO payable to Cambridge Learning Ltd for £.....

Please charge my credit card,

No Expiry date

Telephone orders from credit card holders accepted on 0480 67446 (24 hrs)

Name

Address

..... Signature



CAMBRIDGE LEARNING

Unit 14, Rivermill Site, FREEPOST, St Ives, Cambs PE17 4BR, England.



DIRECT-READING CAPACITANCE METER

Returning almost immediately to our pages after his recent Audio Design series, John Linsley Hood presents a simple, low-cost capacitance meter design.

Most electronics enthusiasts will have some means of measuring voltages and resistance values at their disposal. Indeed, the humble bench multi-meter will do an adequate job in this respect, at a modest cost. However, knowing if the capacitor one has fished out of the junk box, or even out of the parcel of new components freshly delivered from Bloggs Electronics, is indeed what it's markings say it is will be a different matter.

A small gadget to measure capacitance values therefore makes a useful addition to the test bench, and can be invaluable if one is building an audio filter stage, a sine-wave oscillator, or anything else which requires accurate, or at least well matched values of capacitance.

One of the simplest ways of measuring capacitance is to connect the component under test to a suitable (low voltage) source of AC, and then measure the current which flows through it. For small values of capacitance, this is obviously not going to be very big, so some kind of electronic amplifier will be needed.

A suitable arrangement is shown in outline form in Fig. 1. The only

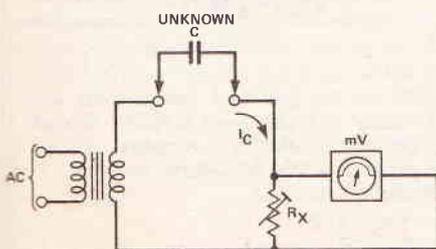


Fig. 1 A simple method of measuring capacitance.

specific requirement is that R_x must be very small in value in comparison with the impedance of the capacitor under test.

The Circuit

The actual circuit used in the instrument is shown in Fig. 2, and is simply a high input impedance milli-voltmeter having a FSD input sensitivity of about 27mV and built around a TL071 op-amp.

The range switch is chosen to give full scale capacitance value indications of 10pF to 100uF. The capacitance ranges increment in steps of 1:10:100, etc., using the given values for R1-R9, but there is no reason why the constructor should not adopt a 1:3:10:30 series by making the resistor bank have values in the 3M3, 1M0, 330K, 100K ... sequence.

For testing electrolytics, it is desirable that there is a small

polarising voltage on the capacitor under test. This is done by switching the lower end of the resistor bank of SW1 to the -5V line. This effectively puts the DC supply smoothing capacitor of this line in series with the capacitor under test, so it is advisable to make these large with respect to the 100uF maximum instrument range.

Construction

Virtually all of the low-voltage circuitry is mounted on the PCB, including the meter and the range-setting switch with its associated resistors. However, neither the transformer nor the mains fuse are mounted on the board because of the risk of AC pick-up from them.

Assembling the PCB should present no problems provided the overlay is followed carefully. Begin by soldering SW1 into place and then move on to the resistors and


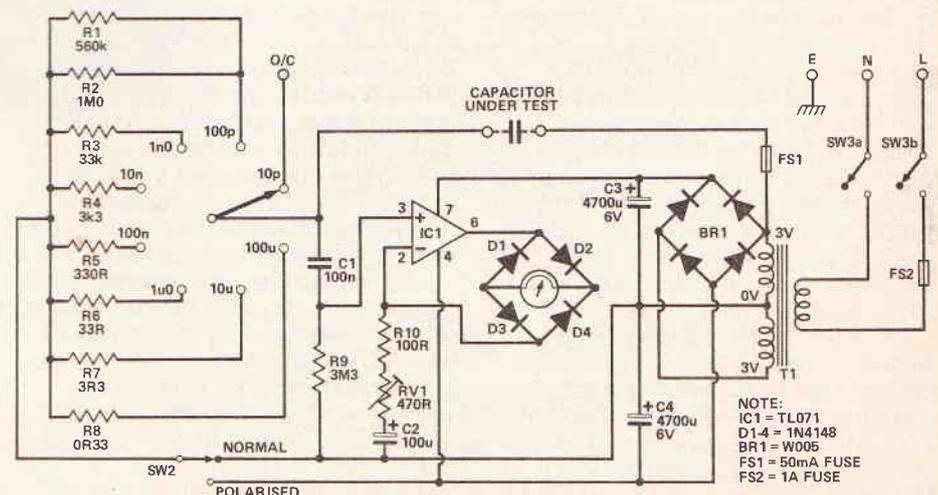


Fig. 2 Circuit diagram of the direct-reading capacitance meter.

PROJECT : Capacitance Meter

Fig. 3
Component
overlay of the
PCB.

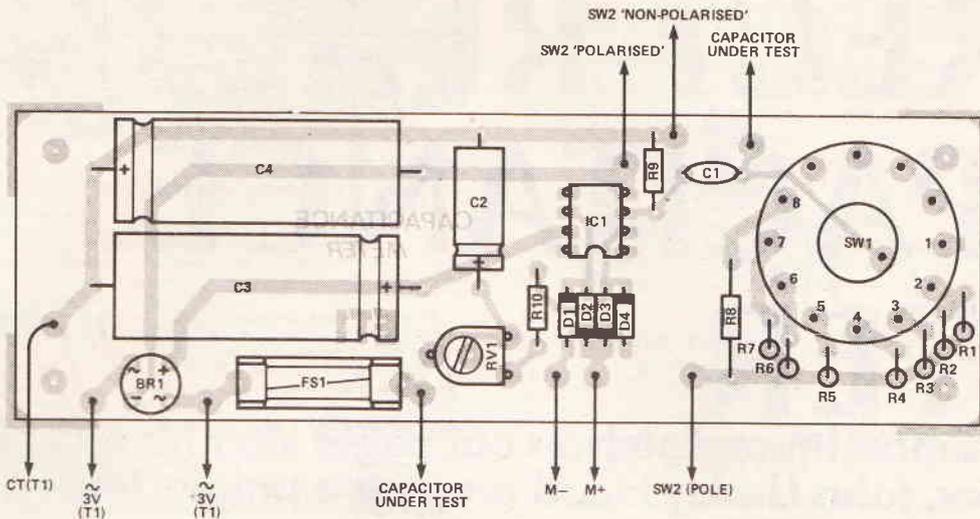

PARTS LIST

RESISTORS

R1	560k
R2	1M0
R3	33k
R4	3k3
R5	330R
R6	33R
R7	3R3
R8	R33
R9	3M3
R10	100R
RV1	470R

CAPACITORS

C1	100n
C2	100u 16V electrolytic
C3,4	4700u 6V electrolytic

SEMICONDUCTORS

IC1	TL071
D1-4	1N4148
BR1	W005

MISCELLANEOUS

M1	100uA moving coil meter
SW1	1 pole 8 way rotary switch
SW2	SPDT toggle switch
SW3	DPDT mains toggle switch

T1	3-0-3V 3VA chassis mounting transformer
F1	50mA 20mm fuse and chassis mount- ing holder
F2	loudspeaker-type twin spring terminals

PCB; diecast box; mains cable and strain relief bush; knob for SW1; spacers, nuts and bolts for mounting PCB and T1; screening material.

capacitors, taking care with C2, 3 and 4 which are electrolytic and must be inserted the right way around. Finally install the diodes and the op-amp, again taking note of polarity. The op-amp is a bi-FET device and requires no special handling precautions; some constructors may prefer to use a socket for it but this is not essential.

Because of the susceptibility of the high impedance input to AC pick-up, it is recommended that the instrument be housed in a diecast box. No particular type is specified, but you should choose one which is large enough to accommodate the PCB plus the off-board controls and which has sufficient depth to allow the transformer to be placed well away from sensitive parts of the circuit.

The test terminals should be positioned close to the appropriate pads on the PCB and then connected up using very short lengths of wire. These two leads should not, of course, be twisted together since this would introduce a certain amount of capacitance and thus affect the accuracy of the unit. SW2

presents no such problems and can be wired up in the normal way.

The transformer and the mains switch and fuse should all be positioned well away from the op-amp and the test terminals, particularly the terminal which connects to the wiper of SW1 since this point is at high impedance and therefore very sensitive to AC pick-up. The leads from the secondary of the transformer to the PCB should be tightly twisted together since this will reduce the magnetic field around them and hence the risk of pick-up. It may also be necessary to screen the op-amp and the high impedance terminal completely if the meter is to operate correctly on its two most sensitive ranges.

Setting up the instrument, on completion, requires the availability of a few good quality capacitors of which the capacitance is known to an adequate degree of accuracy. The value of RV1 can then be adjusted to give the best fit over several ranges.

It is possible to attach a pair of leads to the test terminals and use them to test capacitors in situ, but

AC pick-up on the high impedance lead will introduce errors and this method can therefore only be used with large values of capacitance. In all other circumstances it is advisable to place the capacitor under test directly across the test terminals. If the size or construction of a capacitor prevents its being connected in this way, attach a flying lead to the low impedance test terminal (the one from the secondary of the transformer) and use this to connect to one side of the capacitor while the other side is inserted directly into the high impedance terminal.

BUYLINES

All of the specified components are readily available and suitable diecast boxes are sold by a number of suppliers. The PCB is available from us.

ETI

ETI NOVEMBER 1984

LB ELECTRONICS

SPEACH SYNTHESISER kit as in March/April Electronics & Computing. Kit £24.95 p/p £1.50. Ready Built £34.95 p/p £1.50. Details S.A.E.

LOGITEC FT50001 dot matrix printer 100cps, friction/tractor £289 + VAT. Carriage £10. S.A.E. leaflet plus print-out.

PRESTEL monitors 6" green phosphor screen 12 digit keyboard printer port, cassette port, keyboard port (for full qwerty keyboard) Brand new and boxed £175 + VAT. Leaflet S.A.E.

DISC DRIVE BONANZA

TEAC FD-55F 1/2 Height DSD 80 track/40 track, selectable at our new low price £199 + VAT. £8 carriage. Shinon 1/2 height 5 1/4" drive, 40 track, brand new, single sided, double density £140 + VAT. Carriage £8. **COMPETITION.** We thank all our customers for purchasing our Teac drive and as a bonus we are now offering every 50th disc drive to be sold will be sent totally FREE. The 1st winner is: Mr A.P. White, Hertford, Huntingdon, Cambs. This offer is excluded from trade or bulk buyers.

EDGE CONNECTORS 1" 56x56 wire wrap keyway at 30 £1.80 p/p 25p, 30x30 156 Gold 80p p/p 25p 1" 80x80 1 £2.85 p/p 25p.

Twin 5" Cabinets with power supply £40.00 + VAT (providing a disc drive is purchased from us, if drives purchased elsewhere £50.00 + VAT).

LS IC's in Stock. Phone for prices.

Monitors 12 inch Green Phosphor (Motorola chasis) fully cased 240 volts ac separate vertical horizontal sync. circuits supplied for composite video (5 transistors) £35.00 (used) ideal for BBC, Micro etc. Sorry callers only.

KEY BOARD BONANZA. Brand new ASCII coded single 5 volt rail. Some with numeric key pad, some without £29.95p p/p £1.50p. Leaflets S.A.E.

Our business is now expanded and we have computer showrooms at MICRO HOUSE, 416 DERBY ROAD, GREENFORD, MIDDLESEX. Tel: 01-575 2860. Many computer peripheral bargains on show. We now stock the new **Sanyo MBC550** £749 + VAT (single drive) **MBC555** £999 + VAT. (Twin drive) 128K standard expandable to 256K, with 555 model £1200 worth of software with this system (i.e. WordStar, SpellStar, Mailmerge, ReportStar, etc...). Full demonstrations available phone for S.A.E. New monitors, printers, disc drives, diskettes, paper, ribbons, etc, etc... Supplied at realistic prices. Please note our retail component shop is still in operation at Hercies Road.




LB ELECTRONICS

11 HERCIES ROAD, HILLINGDON,
MIDDLESEX UB10 9 LS, ENGLAND
TEL: UXBRIDGE 55399

American
Express



THEATRE & BAND LIGHTING!

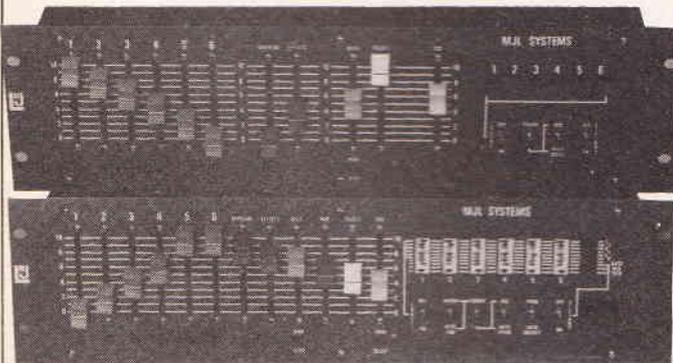

MJL are one of the UK's leading suppliers of stage lighting equipment, with a range of products to suit theatre, band, disco and club installation. And our prices are the most competitive you will find. So whether its just 3000 Watts or a 300,000 Watt rig you need, our advice comes free by contacting the following:

The Sales Manager
MJL SYSTEMS LTD
45 Wortley Road
W. Croydon
Surrey CR0 3WEB
Tel: 01-689 4138 Mon-Fri 9-5

IF YOU WANT TO
SEE THE LATEST
IN LEISURE
ELECTRONICS.....

AT LEISURETRONICS
Horticultural Hall,
Victoria.
November 8-11
ON STANDS
G1 & H1

YOU NEED TO SEE
A SPECIALIST!

See the latest equipment for your kind of electronics. Logic probes, breadboards, including our new low cost prototyping board. Special offers for the period of the Show - and much more!

It's worth a trip to LEISURETRONICS just to meet the specialists!



GLOBAL SPECIALTIES

An Interplex Electronics Company

Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Telephone: (0799) 21682 Telex: 817477 GSC LTD.

CUSTOMISED ICs

Customised ICs are catching on as fast as customised number plates. S.M. Smith explains how PLAs and ULAs have brought down the price.

In the past ten years or so the complexity and density of circuits integrated onto one chip has increased dramatically. This trend is continuing for the following reasons:

Size: usually, one chip is smaller than twenty. Smaller circuits fit into smaller boxes, which are cheaper to manufacture and transport than large heavy ones. If several PCBs can become one, inter-PCB connections are saved.

Power consumption: in general a single device consumes less power than several. The consequent drop in heat dissipation may allow natural instead of fan-assisted cooling, or reduction of heatsink sizes, or both. Also a less bulky power supply is needed. The whole equipment may then reduce in size and weight by far more than the initial amount caused directly by integration.


Speed: devices on large scale ICs tend to be smaller than those in medium or small-scale ICs. The switching speed of small devices is usually faster than that of large devices, so the single chip is faster than several.

Reliability: one chip is more reliable than several. Reducing the chip count in equipment reduces the number of interconnections and hence the probability of a faulty connection. More reliable equipment means cheaper equipment, as less money has to be allocated for fixing faults arising during and after production.

Security: a board full of TTL ICs is easily copied by unscrupulous competitors. An anonymous black plastic block can only be copied with a lot of effort.

There are several ways of putting a logic system on a chip, ranging from the full custom IC down to the familiar PROM. A fully custom integrated circuit is a complicated device that takes months to design and develop, and requires massive investment in plant to manufacture. To recoup the cost of this requires sales of either a huge number of devices at reasonable prices, or a few sales at ridiculous prices, the latter being luxury indulged in only by the aerospace and defence industries. To understand

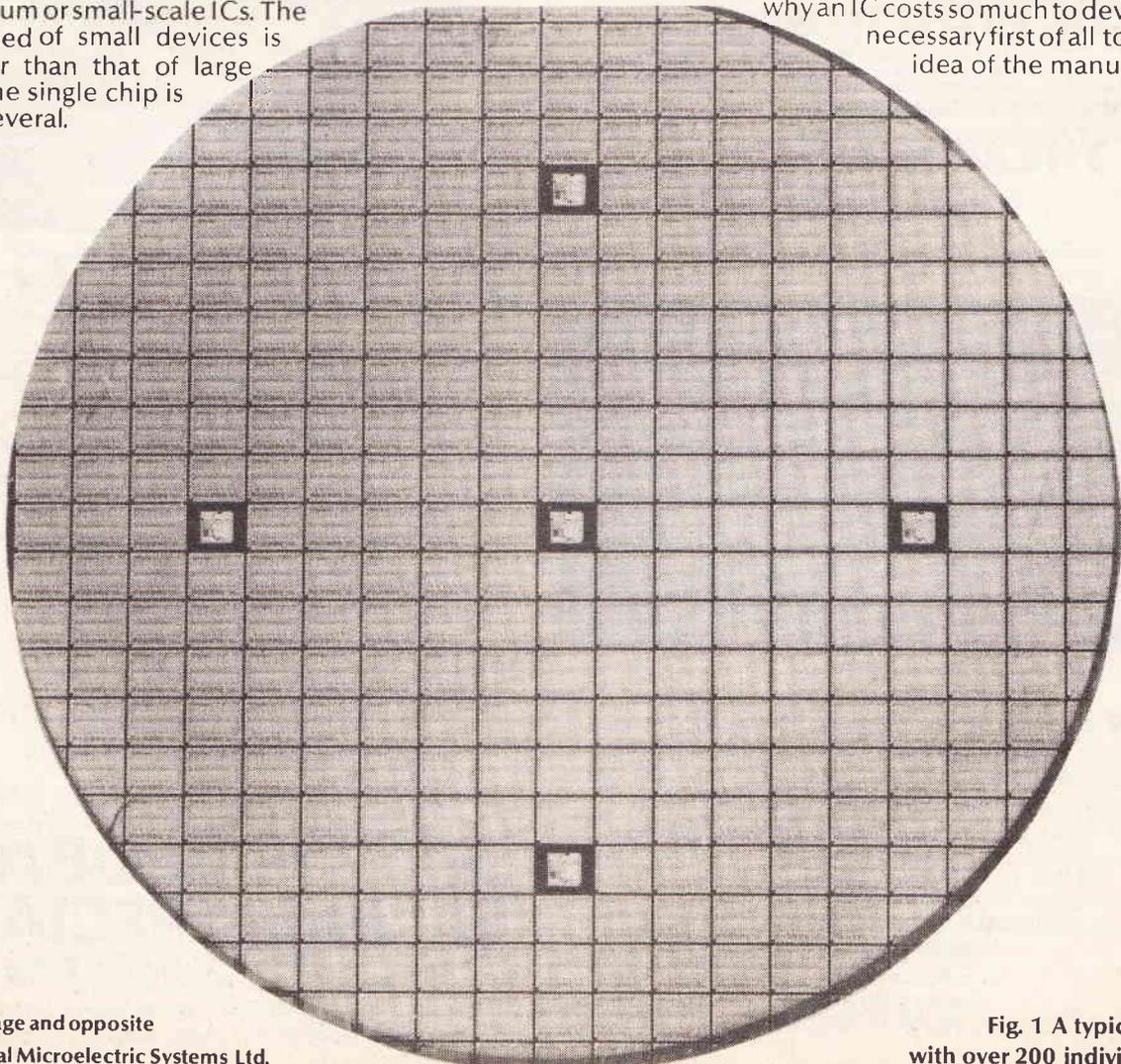why an IC costs so much to develop, it is necessary first of all to have an idea of the manufacturing process.



Photos on this page and opposite are courtesy Racal Microelectric Systems Ltd.

Fig. 1 A typical wafer, with over 200 individual ICs.

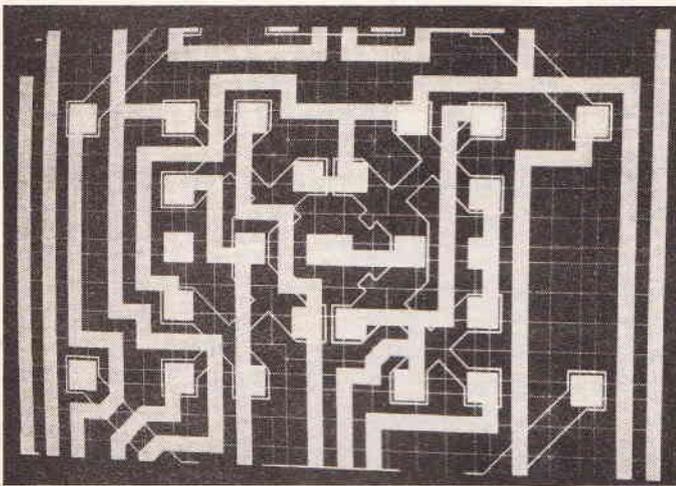


Fig. 2 Metal tracks laid out on a ULA, as seen on a VDU during design. The filled-in white area are metal tracks, the thin white lines outline transistors and diffused cross-unders, while the faint grey lines mark allowed track placements.

Integrated circuits are fabricated on thin sheets of silicon, 2" to 5" in diameter, called wafers. The silicon used for IC fabrication has to be extremely pure — 99.99999% pure. It must also be mono-crystalline, with the atoms laid out in a regular three-dimensional pattern and no defects. Since the wafer is polycrystalline silicon, a near-perfect layer of single-crystal silicon must be grown on the wafer surface, using a process called epitaxy.

Making Transistors

Transistors and resistors are made by *doping* the silicon with minute quantities of other elements, such as boron, gold, phosphor and indium. Obviously, a single transistor 3" in diameter is of little use, so the doping is introduced only to selected areas of the silicon surface. Areas to be doped are defined by holes in a layer of silicon dioxide on the wafer; the oxide prevents dopant reaching the silicon.

The shape and location of the holes in the oxide layer are ultimately determined by a pattern held in a computer. This pattern is converted into a 400 X full size master print which is photographically reduced in two or three stages onto a chrome-coated glass plate, the 'mask'. Several hundred patterns are repeated across the mask in a precise regular array, so one wafer will yield several hundred chips (see Fig. 1).

The wafer is coated with a photo-resistive polymer, which reacts to ultra-violet light (a similar process is used in PCB production). The mask is then placed over the wafer, in precise alignment with previous processing steps, and then the wafer is exposed to UV. The mask is removed and the unexposed resist is rinsed off with a solvent — the exposed resist, hardened under the ultra-violet, does not rinse away. Now the un-covered section of the oxide can be etched away with acid, leaving silicon exposed for doping.

The final mask defines the metallisation layer, which is a thin network of aluminium tracks interconnecting devices on the chip. There may be several metal layers, separated by insulating oxide layers.

There are around seven processing stages for each mask, and an IC design may require 5 to 12 masks. This makes the process long, expensive and error-prone.

The Expertise Gap

There are few engineers capable of designing an

integrated circuit at this level of complexity, with control over doping levels, transistor sizes and so on. Fortunately, many applications do not require minute control over the electrical characteristics of the devices on the chip. Semi-custom logic design allows an ordinary logic designer to design an integrated circuit.

The most complex semi-custom approach is the standard cell. Here the designer has access to a computer database containing mask layouts for often-used devices and functions up to the complexity of, perhaps, a full adder. The designer extracts from the database the devices and functions needed; he or she may have some control over electrical performance if layouts are held for different versions of the same device.

This is still an expensive method; although design data has been previously calculated for each function required, new masks have to be made for each IC. To be cost effective, large returns on sales must be certain. The advantage over full custom is the lower expertise required of the designer and faster design time, with only a small loss in performance.

Uncommitted Logic

The next level down in terms of cost/time is the gate array, or uncommitted logic array (ULA), to which the bulk of this article is devoted. In the ULA the devices and some inbuilt interconnection are ready-fabricated. The devices are laid out in a regular array with channels between groups of devices for interconnection routing (Fig. 2). The designer's job is to complete the interconnection by specifying a metallisation mask layout.

Although the designer has no control over electrical performance of the devices, and some waste of silicon area is inevitable due to the fixed form of the array, the ULA is attractive because of its fast design time (5 to 12 weeks) and lower production costs (only one or possibly three new masks have to be produced). It is therefore suitable for projects expecting relatively low sales volume.

Fuse Programming

Next comes the fuse-programmable logic array (FPLA; some versions are called PAL or PLA). These come in a number of different versions, but basically consist of a set of AND gates feeding a set of OR gates. Fusible links control which of the chip inputs go to which AND input, and which AND output to which OR input. Some FPLA's incorporate D-types, registers and optional feedback loops to allow sequential circuits to be burnt in.

FPLAs have the advantage of very fast design time (a few minutes from specification of the logic function to production of the program for blowing the array). They tend to lack versatility compared with a ULA and make inefficient use of silicon. They have the advantage of in-house programming (no need to send them away to the manufacturer, with the attendant delays) and can be very cost-effective in some applications.

And PROMs Too!

The final option is to use the PROM (Programmable Read Only Memory). This has the advantage again of on-the-spot programming and may implement more complex logic functions than the FPLA. The required truth-table is programmed into the PROM; the address lines are used as the logical inputs, and the data lines are the required outputs. However, the PROM is a comparatively slow device, and its use may often be a waste of silicon; as an extreme example, an octal inverter (16 transistors in CMOS) implemented on a PROM requires 256 words by 8 bits — a 2K memory!

Because of the reasons above, the ULA is the most important of the routes to a semi-custom logic IC at present. It is likely to become more so in the future as the pace of technology quickens, demanding new designs in shorter timescales, and as the software tools for ULA design improve, allowing more fully automated design and design of larger chips.

CMOS is the fastest-growing gate array technology at the moment, due to its combination of speed, power consumption, packing density and ease of design.

Designing A ULA

It would be almost impossible to design a ULA without the help of a computer. People are slow, they find checking boring and they make mistakes. Fortunately, computers are not yet intelligent enough to get bored.

The design starts, usually, with a 'breadboard' model of the circuit, in TTL or CMOS or whatever is most suitable. This stage is used to check if the ideas are correct; it may be considered unnecessary if a well-known design is being implemented. The design is then translated into a form suitable for putting on a ULA. There will be some differences between the breadboard and ULA versions of the circuit because in CMOS arrays some logic structure are more easily implemented than in bipolar technology or 4000-series CMOS.

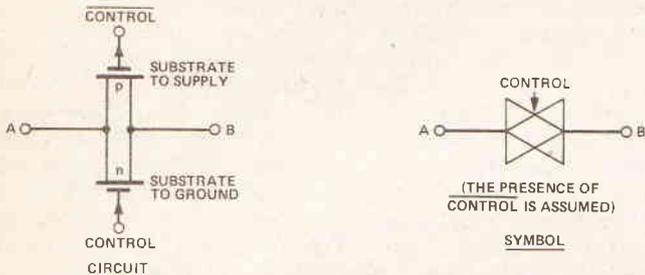


Fig. 3 The transmission gate.

One basic unit, fundamental to CMOS gate array design, is the transmission gate, a pair of P and N channel transistors with their sources and drains tied together, with complementary gate signals, Fig. 3. When CONTROL is high the N-channel transistor is turned on, and since CONTROL is low, the P-channel transistor is turned on too. Thus a signal can pass from A to B.

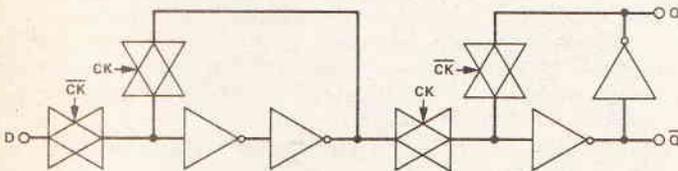


Fig. 4 D-type flip-flop (positive edge triggered) using 16 transistors (two per transmission gate, two per inverter — circuit not shown for inverter, but assumed very simple).

Using this construct, a D-type flip-flop, for instance, can be made with just 16 transistors, Fig. 4. An even more economical D-type can be implemented using only eight transistors, Fig. 5. This relies on the charge stored at

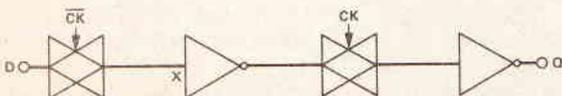


Fig. 5 Faster, more economical D-type using the gate capacitance at point X as a storage element.

X during CK lows. When CK goes high the signal propagates to Q. Of course, the gate capacitance at X will leak, so a minimum clock frequency of a few kHz must be guaranteed.

Because transistors in the ULA are individually accessible, composite gates can be built up using less silicon area than if a gate array really were an array of gates, rather than transistors, Fig. 6.

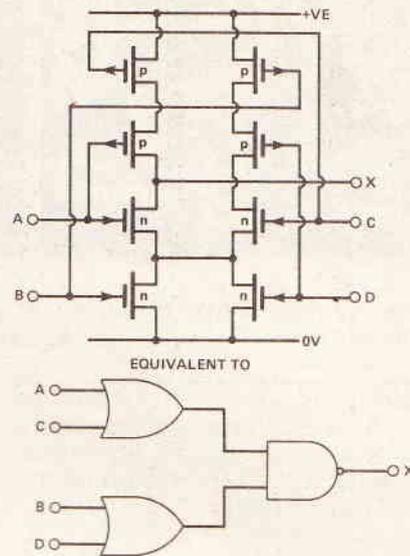


Fig. 6 Composite gate, where the gate function has been implemented directly rather than been broken down into individual elements.

Once initial design is completed, some verification of the design will be required. At around £10,000 per fabrication run, the 'suck-it-and-see' approach is not popular. This is where CAD (Computer Aided Design) is used.

Verification Procedure

Initially electrical characteristics, usually just propagation delay in logic design, are checked. Most common elements, inverters, AND gates, adders and so on will already have been simulated by the manufacturer, but a few special functions may require investigation.

To simulate a circuit at this level (device level) requires a program with device models incorporated, and a knowledge of the model parameters to use, things like channel length, oxide thickness and doping levels for very thorough simulations, or turn-on voltage and channel dimensions for more approximate simulations. The program takes its information from a file containing the circuit description, and a set of instructions on what to do to the circuit.

For propagation delay analysis, the circuit is stimulated with a known input waveform, and the program instructed to give the input and output voltages at, say, 1 ns intervals. The output can be plotted by another part of the program and delays read off, Fig. 7.

To simulate a whole circuit at device level is possible, but rather pointless; the detail is unnecessary and the program execution time too large. Other, circuit level, simulators are employed, for which the parameters used are simply gate delays. The output from this simulation is used to detect hazards and glitches which may not have been present in the breadboard model due to its different layout, logic family or size.

A hazard exists when different delay paths in a circuit cause the output to change state when it is not expected

FEATURE: Customised ICs

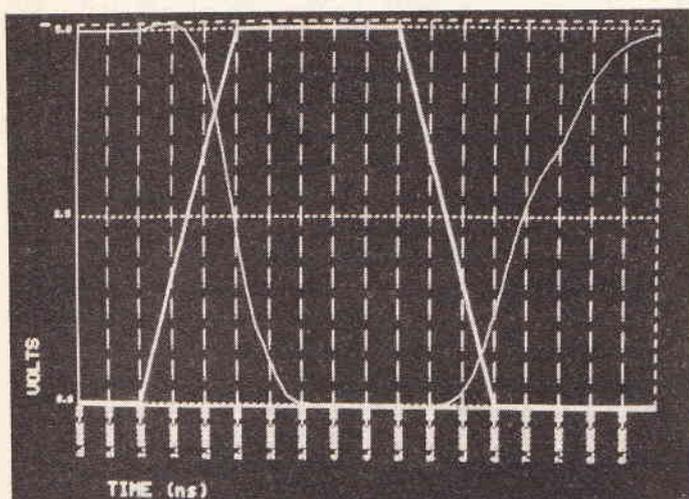


Fig. 7 Output from propagation delay analysis program.

to. The output of Fig 8 should be low only when $ABC=011$. A transition of ABC from 001 to 111 should therefore have no effect on X — it will remain high. However it can be seen from the timing diagram that if the AND and NAND gates have different propagation delays (as they often do in practice) there is an output change.

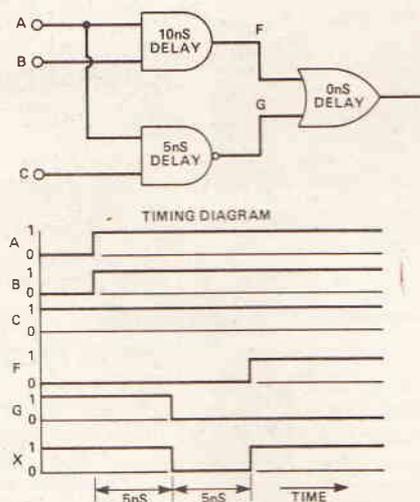


Fig. 8 An example of a timing hazard.

The presence of problems like this may mean the difference between success and failure of a design. Hazards can be eliminated by careful design, or made irrelevant by using fully synchronous (clocked) logic, essentially allowing the circuit plenty of time to settle between input changes.

Another important factor a designer must consider is testability. An IC may contain the equivalent of 2000 gates and yet have only 40 pins. It is not possible to put test probes inside an IC, as it is too small. Every test node must somehow be brought out to a pin, or at least a bonding pad.

Getting Stuck

The two most usual fault conditions in an IC are a gate input stuck at '1', and a gate input stuck at '0'. Consider the circuit of Fig 9. If this circuit operated correctly, then input $ABC=0$ would produce the output $X=0$. However, if B is stuck at 1 the output will be 1. The pattern $ABC=100$ is a test for the fault B S-A-1 (B stuck at 1).

The problem in an integrated circuit is that the circuit of Fig 9 may be 'buried' deep in the IC, and it is difficult to

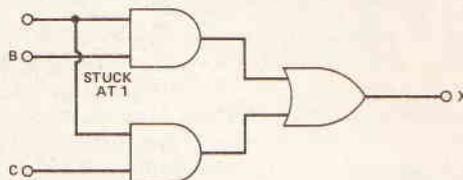


Fig. 9 Fault testing: suppose the input B is stuck at 1.

get the required test patterns to it — perhaps other circuits have to go through several states before the values on ABC reach 100. One rather elegant solution to this problem is called *scan design*.

Most logic circuits have flip-flops and registers on them. By designing a few more and adding some extra steering gates, the on-chip registers can be connected as a long shift register, and the latches used to hold test patterns.

Three extra pins are needed: 'TEST', 'TEST DATA IN' and 'TEST DATA OUT'. When TEST is high, the circuit is in test mode, and test data is serially fed in to the flip-flop chain. After a number of clock pulses the required test pattern is in the circuit under test. TEST is taken low and the circuit operated normally. Test outputs are sent to the registers. Then TEST goes high again and the output values are clocked out along the shift register to TEST DATA OUT.

There are algorithms for finding test patterns for the possible faults in a circuit. Given the logic diagram, correct software and some time, the computer can generate test patterns for most faults. It can also detail those faults which are undetectable with the circuit as it stands; such faults often indicate some redundancy in the circuit.

The gate level simulator can be used to simulate a faulty circuit. This may seem unnecessary, but it is useful to test the efficiency of test patterns.

The Layout

The next stage is the circuit layout. The designer will probably start with a paper sketch showing roughly where each functional block will go, and proceed from there. He or she will try to interconnect the blocks along certain allowed lines (there will be a set of design rules, governed by the accuracy of the manufacturing process, which determine track minimum widths and spacings, etc). There are automatic connection routing programs, but they are usually for two or more metallisation layers, while most ULA's have only one. People produce more compact layouts than computers, especially when constricted to fixed channels allowing only a certain amount of interconnection tracks.

Finally, automatically, semi-automatically, or manually, a layout is produced. The likelihood of an error, especially with a manual layout, is high.

A piece of software called a *design rule checker* will look for tracks too close together, incomplete tracks and so on, reporting back to the designer, who can edit mistakes at an interactive graphics terminal. There is also the question of whether the circuit drawn actually performs the intended function, even if it complies with the rules for physical layout. A *circuit extractor* program can work out the function of the layout, simulate it, and compare the results against those expected from the circuit. This is a difficult and time-consuming task, even for a powerful computer. The need for this stage can be reduced by careful design, or eliminated completely by the use of automatic layout and interconnection.

Finally the data describing the complete, checked

layout are fed to another program which generates instructions for a machine which produces the metallisation masks. Masks traditionally are made by photographic reduction of a 400 X full size master, cut by a computer-controlled knife. Nowadays electron-beam lithography is common; an electron beam scans the actual size mask, exposing electron-sensitive resist. This latter method is more accurate than the first, allowing higher circuit densities, and, because each chip pattern is individually written, it costs little extra to change the program halfway and write two, three or four different metallisation layouts onto one mask. This allows smaller than usual quantities to be economically committed.

The Future

What of future developments? Most predictions are based on company forecasts, and they obviously predict a rosier future for whatever semi-custom method or technology they are marketing that their competitors do not have. However it is possible to say some things with reasonable certainty.

Silicon-gate CMOS arrays are likely to dominate the market in most applications, due to their combination of speed, density and low power. Low power density is important with high levels of integration — chips which dissipate more than a watt or so require special packaging to keep them cool and the package may cost more than the chip it houses.

Software is still chasing hardware in sophistication — 20 000 gate arrays are announced but no CAD system can adequately handle them yet. 30 000 gate arrays have been predicted for 1985. Array manufacturers are becoming aware of these difficulties, and are employing software writers to produce product-specific CAD tools at the same time as hardware designers work on the physical design of the array.

Most ULA sales are in the 300-1000 gate range, the very large arrays tending to be purchased by the computer industry. A recent FPLA chip (the AmPAL22V10 from Advanced Micro Devices) claims to offer the versatility of a 500 to 1000 gate array be celver design and the provision of over 5800 fuses. Perhaps we shall see FPLAs making headway into markets previously the domain of the gate array.

By the end of this decade CAD software may have advanced to the level where the standard cell will exceed the gate array in popularity. This is because most systems are not composed only of logic circuits — they contain RAM, ROM, EPROM and linear devices like op-amps, analogue to digital converters and voltage references. There are arrays which have linear functions and memory areas on them (an ordinary array wired as a RAM is very wasteful of silicon) but the problem is always how much space to allocate to each function. If too many choices are offered none will sell in large numbers and the advantages of mass production are lost. With a standard cell IC there are no such problems — as much ROM, etc, as is needed is fabricated.



Increasing levels of integration bring problems of pinout too — 64 pins is the usual maximum in a DIL package. However a semi-custom IC may be replacing a whole PCB with over 80 connections. We are likely to see more and more exotic packages such as flatpacks and pin-grid arrays (which look like a bed of nails from the pin side).

In conclusion, then, it seems likely that more and more products will employ semi-custom ICs of one sort or another. These ICs will be designed by ordinary circuit designers, using powerful software tools running on mini-computers or special-purpose micro-computers.

ETI

HENRY'S

AUDIO ELECTRONICS

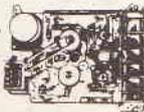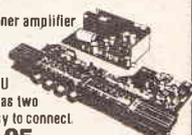UK'S NO.1 FOR ELECTRONICS		ALL PRICES INCLUDE VAT	
STEREO RADIO TUNER Ready built Mw-Lw Stereo FM By well known Hi-Fi manufacturer Approx. 6½ x 3½ x 1½" With Data £4.95 post 65p		HEXADECIMAL KEYPAD 16 button encoded (requires IC's) £7.50 post per 1 or 2 50p	
CASSETTE MECHANISMS Fitted counter. Motor. Stereo record and erase heads. Solenoid, etc. Brand new available 6V DC or 12V DC (state which) £5.95 (UK C/P 65p)		CHERRY ADD-ON KEYPAD 16 button pad non-encoded £5.95 (UK post 50p per 1 to 2)	
THERMAL PRINTER COMPLETE WITH FULL HANDBOOK, 3 ROLLS PAPER £49.95 (UK C/P £1.05) SUITABLE FOR TANDY BBC ORIC NASCOM GEMINI ACORN DRAGON ETC. ETC. (interface unit with leads £15 - state model) (your enquiries invited).		ITT 2020 CABINET Professional computer case with keyboard cutout. 18" x 15.5" x 4.5" (front slopes). Ideal for single board computers like the Nascom or Gemini Multiboard (3 cards, etc). Very heavy gauge (25") plastic with metal base. Attractive silver grey finish. £22.95 (UK post £2.05)	
NICADS/DEACS Rechargeable packs EVERREADY 8.4 Volt HEAVY DUTY NICAD approx 3" Diam x 3" with magnetic switch £5.95 post 55p Two for £11.00 post 65p; Four for £20.00 post 85p DEACS (UK post 50p) 24 Volt 225 mA £3.95 6 Volt 90 mA £1.25 3.6 Volt 225 mA £1.50		ASC11 KEYBOARD 69SD5 Compact. 64 key - 5 function keys. Hall effect keyboard with reprogrammable (2716) ASCII output decoder EPROM. Steel key frame for good rigidity. Negative going strobe. Requires +5 volt +12 volt supplies. £24.95	
COMPUTER POWER SUPPLIES Large range in stock - many at very low prices.		COMPACT 58 KEY ASCII KEYBOARD Contactless capacitive high reliability keys. Full 128 ASCII codes. Steel key frame for positive rigidity. 1ms strobe, single -5 volt supply. Repeat key, control and caps. lock. £32.50 (UK C/P £1.00 either model)	
RECHARGEABLE BATTERIES & CHARGER Charger takes any 4 'AA', 'C' or 'D' cells plus PP3 type. With free mains plug £5.50 (UK C/P & Ins 65p) 4 x 'AA' (HP7 size) rechargeable cells £2.95 (UK C/P 30p) Other sizes in stock		TV AMPS/DISTRIBUTION UHF SET BACK Ku700 7dB £6.95 Ku8G £10.95 Ku650 7dB for 2 x TV's £8.50 UHF MAST TMB 30dB (MKII) £18.95 DISTRIBUTION - VHF/UHF 40 to 860MHz 4 way £28.95 6 way £37.95 8 way £42.95	
COMPUTER FANS (UK C/P 60p each. £1.00 per pair)		POCKET RADIATION DETECTORS Dosimeter for Gamma and X-Rays. 0-5r (UK Post 55p) £6.95	
MARRIOTT TAPE HEADS (UK post 50p per 1 to 4) ½ TRACK KRPS36 Low imp. £3.50 KRPS18 Med imp. £2.50 XES11 Erase for above £1.25 ½ TRACK BX RP63 R/P £2.25 Erase for above £1.25		STEREO TUNER/AMPLIFIER 1000's sold 4 wave-band stereo tuner amplifier by GEC MW/LW/SW stereo FM radio 10 + 10 watt stereo amplifier. Inputs for PU tape in/out. Supplied as two assembled units - easy to connect as illustrated £21.95 (UK C/P £1.50)	
CASSETTE HEADS Stereo £2.95 Mono £1.95 Stereo erase £1.00		MODEM CARDS/COUPLER Brand new. Tested, answer and originate 300 BAUD unceasing acoustic modem card by famous manufacturer. RS232 input/output, power supply +/- 12V at 180mA. Requires 2 magnetic earpieces, 2 switches, 2 LEDs and connectors to complete. Data supplied. Card only £29.95 Card and remainder of small components £33.45 Telephone Direct Line coupler type LTU 11 MKII. Suitable for direct coupling PRESTEL adaptors and the above acoustic modems. Integral Line select and autodial relays requiring TTL inputs data supply. £14.95 1200 BAUD receive 75 BAUD send direct coupled modem for PRESTEL. Requires +5V supply with TTL inputs for data. Line select and autodial. LTU 11 direct coupler required. See above. Data supplied. PRESTEL modem card £14.95	
TOROIDAL TRANSFORMER 100 watts isolation 230/240 V AC plus 8.0-8V 4A 15.0-15V 8.645A 30V 0.16A size approx. 4½" dia. x 1 ¾" (UK C/P 75p) £7.95		UHF MODULATORS (UKC/P 40p) Video input RF outputs cased for computers etc. Astec UM 1233 £3.50 ITT version £3.50	
CB/HAM RADIO Large range in stock - ask for leaflets			

ALL PRICES INCLUDE VAT

ORDER BY POST OR TELEPHONE

CALL IN AND SEE FOR YOURSELF

OPEN 6 DAYS A WEEK



VISIT OR PHONE

OPEN 6 DAYS
A WEEK
ALL STOCKS
ON DISPLAY

HENRY'S

AUDIO ELECTRONICS




EQUIPMENT • COMMUNICATIONS • COMPUTERS • COMPONENTS

ALL PRICES
INCLUDE
VAT


SCOPES

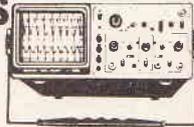(UK C/P £6.00 or £18.00 Securicor)
HITACHI
2 year warranty
ALL MODELS
WITH 2 PROBES
V212 Dual 20 MHz 6" CRT with delay line **£343.85**
V222 As 212 plus DC offset, etc. **£431.25**
V203F Dual 20MHz Sweep delay 5 1/2" CRT **£431.25**
All other models available.



HAMEG

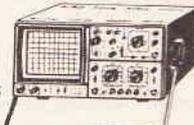2 years warranty
Optional probes see below
HM103 Single trace 10MHz 6 x 7cm display component tester **£192.05**
HM203/5 Dual 20MHz 8 x 10cm display component tester, etc. etc. **£303.60**
HM204-2 Dual 20MHz, sweep delay, 1mV component tester, etc. **£419.75**
Also **HM605** Dual 60MHz **£592.25**



CROTECH

Optional probes see below
3030 Single trace 15MHz component tester 9 1/2cm display **£194.35**
3035 Single trace 15MHz 13cm (5") display component tester **£217.35**
3132 Dual 20MHz Trig to 40MHz, 2mV/div 130mm (5") display, algebraical add/sub Reg DC O/P's - 5V AD - 12V. Built-in component comparator **£325.45**



LOW COST

10MHz 5mV single trace 75mm CRT general purpose **£169.00**



THANDAR

2 year warranty
SC110A 10MHz battery portable 32 x 26mm display with batteries **£189.75** (UK post, etc. £1.50)
OPTIONS Carry case: **£6.84**
AC adaptor/charger **£7.99** Nicad pack **£12.65**



HIGH VOLTAGE METER

Direct meter reading
LHM80A 0/40KV **£32.20** (UK C/P £1.00)



AC CLAMPMETER

0/300A 0/600V AC 0/1K ohm
Total 9 ranges with carry case and lead
ST300 **£29.95** (UK C/P 65p)



COMPONENTS ■ TOOLS ACCESSORIES

LARGE RANGE IN STOCK
Tel: 01-723 1008 for small or large quantities.

TRANSISTOR TESTER

Direct PNP/NPN and diodes
Hfe, leakage, etc. General purpose TC1 (UK C/P 65p) **£26.95**



DIGITAL MULTIMETERS

Controls
s=Slide, R=Rotary
PB=Push button
All feature AC/DC volts, DC amps (many with AC amps) others, etc.
(UK C/P 65p) * WITH CARRY CASE
* **KD25C** 12 range 0.2A DC 2 Meg ohm(s) **£23.43**
* **KD30C** 14 range 10A DC 2 Meg ohm(s) **£27.95**
* **KD30C** 26 range 1A AC/DC 20 Meg ohm (R) **£33.50**
* **METEX 3500** 30 range 10A AC/DC 20 Meg ohm (R) **£39.68**
* **METEX 3510** 30 range 10A AC/DC 20 meg ohm plus Hfe tester plus cont. tester (R) **£43.70**
6010 28 range 10A AC/DC 20 Meg ohm (PB) **£34.95**
* **KD55C** 26 range 10A AC/DC 20 Meg ohm (R) **£39.95**
* **KD615** 18 range 10A DC 2 Meg ohm plus Hfe tester (R) **£39.95**
7030 As 6010 but 0.1% basic (PB) **£44.50**
HC 5010 31 range 10A AC/DC Cont. buzzer 20M ohm (R) **£48.95**
* **DM3350** Autorange plus cont. tester 18 range 10A AC/DC 2 Meg ohm (R) **£49.95**
* **DM2350** Mini autorange plus cont. tester 19 range 10A AC/DC (20A Max) 2 Meg ohm (PB) **£62.95**
* **3100** Pen type auto ranging AC/DC V 20 Meg ohm buzzer **£44.85**
SDAR MES40 Manual/Autoranging plus cont buzzer, 19 range 10A AC/DC 20 Meg ohm (R) **£44.85**




ANALOGUE MULTIMETERS

(*mirror scale) (UK C/P 65p)
HC6015 15 range pocket 10K/Volt 1 Meg ohm **£8.50**
M200 30 range 20K/Volt 20KHZ **£7.95**
SPECIAL PURCHASE **£7.95**
HM102BZ 22 range 20K/Volt 10A DC plus cont. buzzer 10 Meg ohm **£13.50**
TMK500 23 range 20K/Volt 12A DC plus cont. buzzer 20 Meg ohm **£23.95**
MH56R 22 range 10K/Volt 6 Meg ohm **£11.95**
830A 26 range 30K/Volt 10AC/DC 10 Meg ohm **£23.95**
360TR 23 range bench, 100K/Volt large scale 10A AC/DC plus Hfe tester 10 Meg ohm **£39.95**
AT2100 31 range de luxe 100K/Volt 10A AC/DC 100 Meg ohm **£33.50**
AT1020 18 range de luxe 20K/Volt plus Hfe tester 5 Meg ohm **£21.00**
YM 360TR 19 range 20K/Volt plus Hfe tester 1 Meg ohm **£13.95**
KRT5001 Range doubler 35 range total 50K/Volt 10A DC 20 Meg ohm **£19.95**
ST363TR 22 range 20K/Volt plus Hfe tester 12A DC 1 Meg ohm **£17.95**



LCD COUNTERS

(UK C/P & INS 65p) 
THANDAR battery portable 8 digit LCD counters, Size 255 x 150 x 50mm. Complete with batteries. Optional: Carry case **£6.84** AC adaptor **£7.99**
TF400 10HZ to 40MHZ 1HZ Res. 49mV sensitivity **£138.00**
TF200 10HZ to 200MHZ, 1ppm res. 10mV sensitivity, many features. A&B inputs, etc. **£189.75**
TP600 600MHZ prescaler (Powered by computer) **£51.75**
TP1000 1000MHZ (1GHZ) Prescaler with power supply **£74.75**
PFM200A Pocket 20HZ to 200MHZ LED counter 0.1HZ res. 10mV sensitivity **£79.73**
NEW TF600 LED 600 MHZ counter. **P.O.A.**

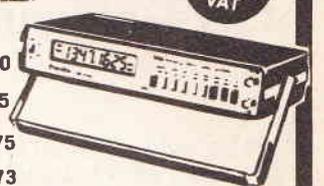


GENERATORS

Function and Pulse (UK C/P 65p) 
THANDAR bench mains portable. Size 255 x 150 x 50mm
Options: Carry case **£6.84**
TG101 0.02HZ to 200KHZ function, sine, square, triangle. Variable DC offset, TTL O/P. Ext. sweep mode. Variable 600 ohm 10V PP **£120.75**
TG102 0.2HZ to 2MHZ function. Sine, square, triangle. Variable DC offset, TTL O/P. Ext. sweep mode variable 600 ohm O/P. 10V PP **£178.25**
TG105 5HZ to 5MHZ pulse, TTL and Sync O/P. Variable 50 ohm O/P. Free run, gated or trig. modes. **£120.75**




LCD & LED MULTIMETERS

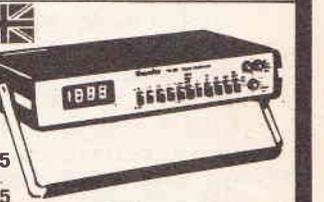(UK C/P 65p) 
THANDAR BENCH PORTABLES Size 255 x 150 x 50mm
Option: Carry case **£6.84**
TM355 3 1/2 digit LED, 29 ranges, 0.25% basic, 100mV res. 10A AC/DC, 20M ohm (AC adaptor option £6.95) **£97.75**
TM356 3 1/2 digit LCD, 29 ranges as TM355, 3000 hour battery life (supplied) **£109.25**
TM351 3 1/2 digit LCD, 29 ranges, 0.1% basic. Ranges as above, 2000 hour battery life. **£132.25**




LED COUNTERS

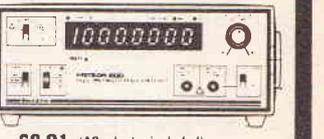(UK C/P 65p) 
METEOR mains or battery portable 8 digit LED counters, Size 219 x 240 x 98mm. 5mV sensitivity 0.1HZ resolution
100 5HZ to 100MHZ **£109.25**
600 5HZ to 600MHZ A&B inputs **£139.15**
1000 5HZ to 1000MHZ (1GHZ) A&B inputs **£189.75**
Options:
6 NICAOS **£12.19** RF pickup Aerial **£8.91** (AC adaptor included)



FUNCTION GENERATOR

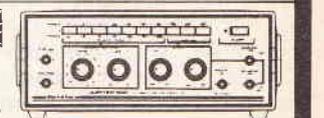(UK C/P 65p) 
JUPITER 500 Function generator 0.1HZ to 500KHZ or better. Sine, square, triangle O/P to ±30 volts. TTL O/P. DC offset ±15V variable, Ext AM and sweep facilities 220/240V AC operated. **£126.50**



DIGITAL CAPACITANCE METER

(UK C/P 65p)
0.1 pF to 2000 mfd LCD 8 ranges
DM6013 **£59.95**



PROBE KITS

In wallets with adaptors, etc. BNC fittings for scopes/counters/generators, etc.
X1 **£7.95** **X10** **£9.50**
X100 **£18.40** **X1/X10** Switchable **£11.50**
Demodulator **£18.50**
(UK C/P free with other items or 65p per 1 to 3 kits)

DIGITAL THERMOMETER

Pocket size LCD thermometers complete with battery. Accept any type K probe
(UK C/P 65p)
TH301 LCD -50° to +750°C 1°C resolution with thermocouple **£68.43**



LEAFLETS available for most items send SAE (Large 22p for latest catalogue)

GENERATORS

220/240V AC (UK C/P, etc. £1.20)
AUDIO
LEADER LAG27 5 band sine/square O/P 0/5V RMS Dist 0.05% 10HZ to 1MHZ **£106.95**
TE220 4 range sine/square O/P 5V RMS 0.5% Dist 20HZ to 200KHZ **£78.00**
TRIO A6202A 4 band 20HZ to 200KHZ, 10V RMS O/P 0.5% dist CR DCS **£102.35**



RF
TRIO SG402 6 range 100KHZ to 30MHZ RF 0.1V RMS Int/ex mod **£82.80**
LEADER LSG17 6 band 100KHZ to 150MHZ (96 to 450 MHZ on Harmonics) RF 0.1V RMS Int/ex Mod. AF 1 KHZ volt (1 MHZ Xtal optional £3.50) **£132.25**
TE20D 6 range low cost version of above up to 110MHZ (300MHZ Harmonics) **£69.95**

TR DIP METER 1.5 to 200MHZ 6 band (UK C/P 65p) **£49.95**



SUPPLIERS OF ELECTRONICS FOR EVERY PURPOSE

Official orders welcome. (Subject to confirmation)

ALL PRICES INCLUDE VAT

ORDER BY POST OR PHONE



Up to £1000 instant credit
Available through Lombard Tricity Finance

301 Edgware Road, London, W2
Test Equipment, Audio, Communications 01-724 3564
404 Edgware Road, London, W2
Computers 01-402 6822 • Equipment 01-724 0323 • Components 01-723 1008

CALL IN AND SEE FOR YOURSELF All mail to Cubegate Ltd, 1st Floor, 406 Edgware Road, London W2 1ED



VIDEO VANDAL

Does Wogan leave you feeling green, or the news make you blue? Get your own back with ETI's video effects unit.

The Video Vandal is a colour video effects generator which can change a normal video image in many different ways. The effects available include:

- (1) Posterisation, where the picture is resolved into a variable number of brightness levels in a way similar to, but more controllable than, photographic solarisation, as used in many pop videos;
- (2) pseudo-Mosaic, where the picture is cut into vertical 'ribbons', an effect similar to that used in certain cigarette adverts in magazines;
- (3) use with a computer as a frame grabber or for image analysis, and
- (4) 'false colour', in conjunction with a suitable monitor or PAL encoder, where colours are used to represent different brightnesses in a manner similar to that of the well-known electronic Infra Red imaging systems.

This last effect is extremely eerie — it is very like the effect used in the title sequence of the BBC's *Day Of The Triffids*.

The circuit is shown in block diagram form in Fig. 1. The video signal is switched either 'straight through' or processed. If processing is selected, the signal is amplified, has the sync pulses stripped from it and has its maximum level limited, while a portion of the colour information is filtered off by a capacitor acting as a high pass filter. The syncless signal is presented to the analogue to digital converter chip whose clock is locked to the sync pulses. The digitised signal is next put through six 'bit switches' before being fed into a buffer and the digital to analogue converter and thence to the output section. Here, the sync and luminance are re-combined into a composite video signal which finally feeds, with the colour signal added, the output socket and, if selected, a UHF modulator.

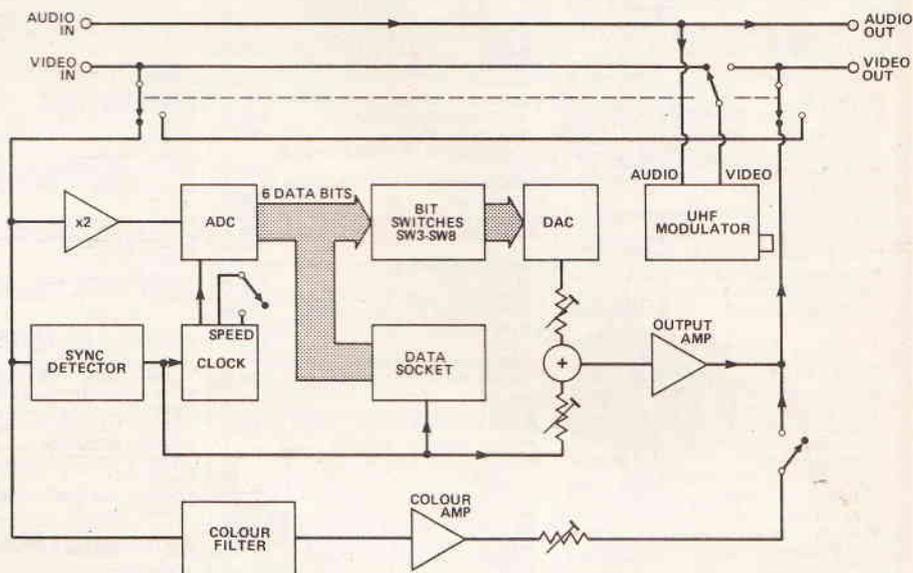


Fig. 1 Block diagram of the Video Vandal.

CONSTRUCTION

There is nothing particularly critical about the construction of the Vandal, provided the high frequencies are taken into account.

The boards should be assembled in the usual sequence of links, IC sockets, passive components, semiconductors. Do not insert the ICs (except the regulators) until you start set up. Be very careful when you handle the ADC chip, as it is static sensitive, and on a chip of that price all precautions such as an earthed metal working surface should be used — a stainless steel draining board is ideal (but don't drop anything down the plughole!). Once in situ, however, the ADC chip is fairly robust, as its input is protected by R19.

There are a lot of large-ish screened cables to connect, so care is recommended while working. The wiring diagram is intended to guide you as far as what goes where, and the use of cable ties when wiring is complete is a must. Audio quality screened cable may be used where screened cable is specified, providing the core is at least 7/0.2.

The bit switches should be connected to the DIL header plug via a length of ribbon cable, which is also used to connect the DATA socket. If there is interference on the video signal, then wrapping the ribbon cable with aluminium foil (and earthing it) is beneficial.

The connections to SW9 should preferably be made with

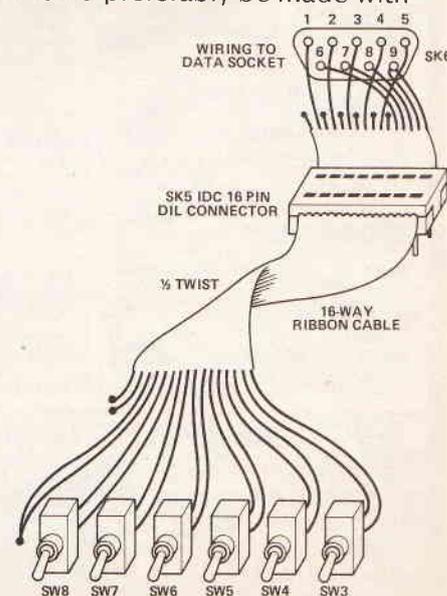


Fig. 2 Connecting up SK5, SK6 and the bit switches.

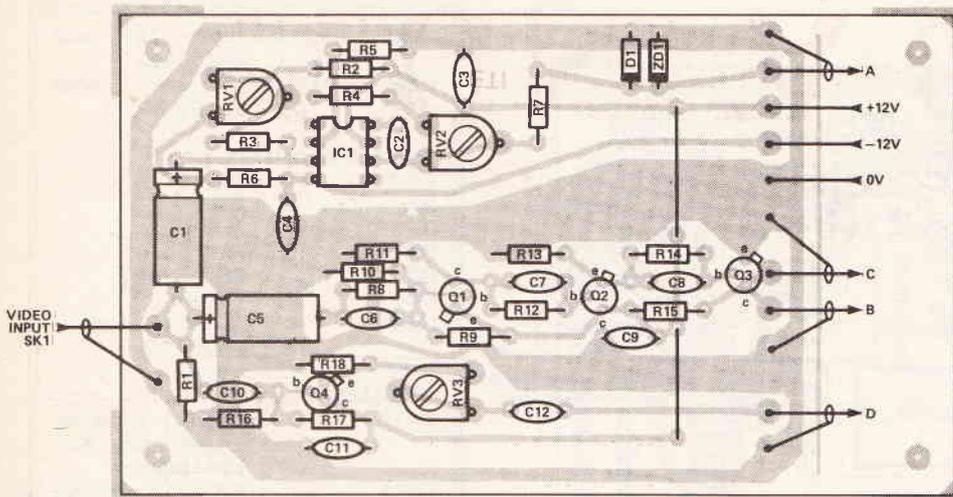


Fig. 3 Component overlay for the input board.

PARTS LIST — INPUT BOARD

RESISTORS (all 1/4 W 5%)

R1	68R
R2,3,6,9	10k
R4,5,13,14	1k0
R7	100R
R8,12	270R
R10	120k

R11	1k5
R15	560R
R16	220k
R17	100k
R18	1k2
RV1	10k horizontal preset

RV2	10k horizontal preset or lin. pot. — see wiring diagram.
RV3	220R horizontal preset

CAPACITORS

C1,5	10u 16V radial electrolytic
C2	18p
C3,4,9,11	100n
C6,7,8	22n
C10	4n7
C12	1n0

SEMICONDUCTORS

IC1	NE531
Q1	BC178
Q2-4	BC108
D1	OA91
ZD1	BZY88C 4V7

MISCELLANEOUS

SK1	BNC socket
SW1a	DPDT miniature toggle (see also PSU board)
SW2	SPDT miniature toggle
PCB.	

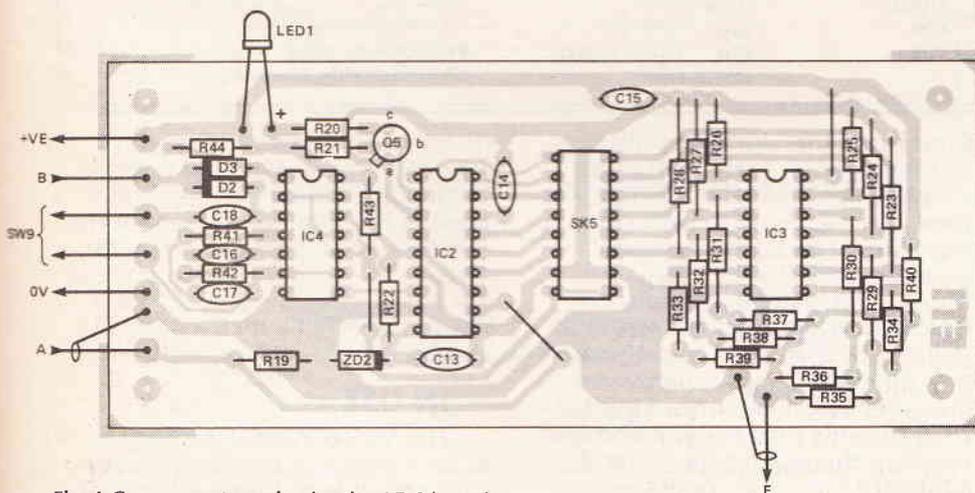


Fig. 4 Component overlay for the ADC board.

PARTS LIST — ADC BOARD

RESISTORS (all 1/4 W 5% unless otherwise stated)

R19	1M0
R20	220R
R21-28,43,44	1k0

R29,34,35,38,40	1k0 2% or better
R30	3k9 2% or better
R31	6k8 2% or better
R32	15k 2% or better
R33	22k 2% or better

R36	100R 2% or better
R37	1k2 2% or better
R39	10k 2% or better
R41,42	5k6

CAPACITORS

C13,14,15	100n
C16	82p
C17	3p3
C18	120p

SEMICONDUCTORS

IC2	RS 3300 ADC
IC3	7417
IC4	7404
Q5	BC108
D2,3	OA91
LED1	panel-mounting red LED
ZD2	BZY88C 3V9

MISCELLANEOUS

SK5	16 pin DIL socket and 16 pin header to suit
SW3-9	SPDT miniature toggles
PCB;	16-way ribbon cable.

low-capacitance wire, or simply use self-supporting solid wire. In the prototype, two torn off lines of ribbon cable were used. Remember to sleeve all the mains connections for safety.

SETTING UP

These instructions assume that a dual-trace oscilloscope with TV

line triggering, a multimeter, a colour video source and a TV or colour monitor are available.

Assemble the Vandal, leaving all the ICs except the voltage regulators out. Set all presets to mid-travel. Switch on the mains and check that the supply voltages coming from the PSU are correct. If so, switch off and install IC1,

BUYLINES

Most of the components are available from any number of our advertisers, the UHF modulators are available for Cirkit and the PCBs from us. The ADC is an RS part (order code 302-069) and can be ordered through Crewe-Allan & Co, 51 Scrutton Street, London EC2.

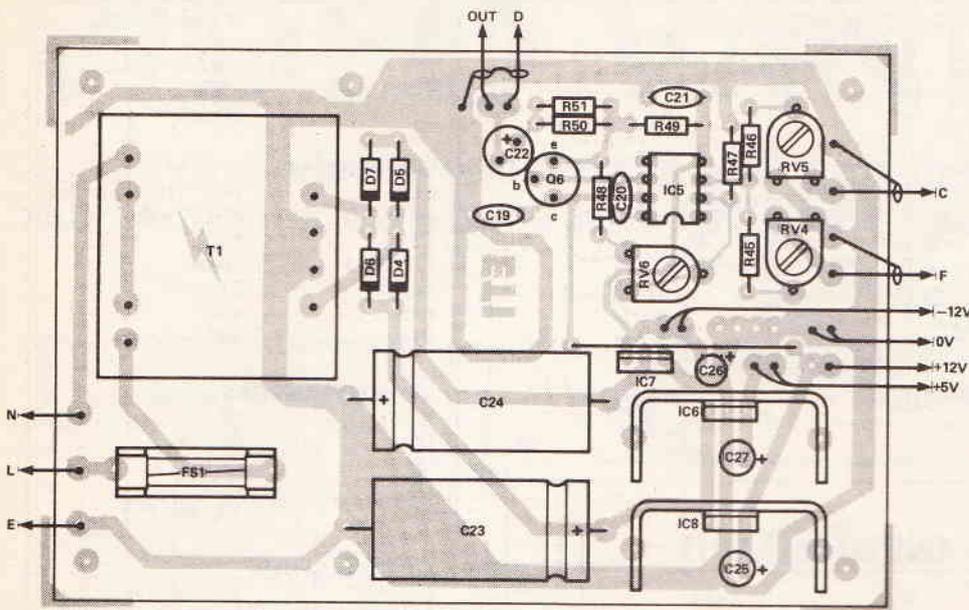


Fig. 5 Component overlay for the PSU board.

PARTS LIST — PSU & CASE

RESISTORS

R45,46	100k	
R47,52	1k0	
R48	100R	
R49	220k	
R50,51	150R	
RV4,5	47k	horizontal preset

RV6	10k	horizontal preset
-----	-----	----------------------

CAPACITORS

C19,21	100n	
C20	18p	
C22	47u	16v radial electrolytic

C23,24	1000u	25V axial electrolytic
C25-27	4u7	16V radial electrolytic

SEMICONDUCTORS

IC5	NE531
IC6	7805
IC7	7912
IC8	7812
Q6	BFY51
D4-7	1N4001
LED2	panel-mounting green LED

MISCELLANEOUS

SW1b	DPDT miniature toggle (see also input board)
SW10	SPDT miniature toggle
SW11	SPDT mains toggle
FS1	100mA fuse and PC- mounting holder
T1	12-0-12V 12VA PCB-mounting
MOD1	UM1286 (sound) or UM1233 (no sound) UHF modulator
SK2	BNC socket
SK3,4	phono sockets
SK6	9 pin 'D' socket
SK7	mains input socket

PCB; case; heatsinks for IC6 & IC8; knob; screened cable, mounting bolts, etc.

connect a colour video source (such as a video recorder) to the input, switch the Through/Process switch to Process and power up again. Connect channel 1 of the scope to the input, and adjust it until a steady display of one line (NOT a field) like Fig. 7a is obtained, with the timebase at about 100us. All further instructions concerning the scope will refer to channel 2. Next, connect the scope to the point marked A on the circuit diagram (the video output from the Input Board to the ADC/DAC) and adjust RV1 until the observed signal looks like that of Fig. 7b. Next, check that points B and C (the sync outputs) on the input board both have sync pulses which look like Fig. 7c present. Now connect the scope to point D (the colour detector output) with SW2 open. Check that there is a colour burst and some noise present, as shown in Fig. 7d. This completes the basic adjustment of the input board.

There are no adjustments to make to the ADC-DAC board.

Turn off the power again, wait at least a minute for the capacitors to discharge and insert the remaining ICs carefully. Turn on again.


Check that the clock is oscillating by testing pin 7 of the ADC. This should show several megahertz (as shown in Fig. 7e) with SW9 open, less with it closed, but in both cases keying off with every sync pulse. Switch all the bit switches (SW3-8) on, connect the scope to point F (DAC output) and check that the signal looks roughly like that of Fig. 7b. Connect a 68 R (or 75 R) dummy load resistor and the scope to the output socket, and adjust RV4 and RV5 until the signal is as shown in Fig. 7a, ie with the ratio of luminance to sync at about 70:30. Adjust RV6 until the output is about 1-1.5V peak-to-peak. Connect the monitor and with a colour video source adjust RV3 until the colours are at about the correct saturation level. The colour will go unstable and then

disappear when RV3 is set too low: this is caused by the colour burst going below the detection level of the monitor. Note that the simple colour filter arrangement distorts the colour slightly and that the colour burst on the output is not to the CCIR specification, but in most cases it will be sufficient.

IN USE

The Video Vandal is designed to be strung into line between two video recorders during editing, or between a camera and monitor or recorder. It is possible to switch it in or out of circuit (except the modulator) so that it doesn't affect the signal if not required.

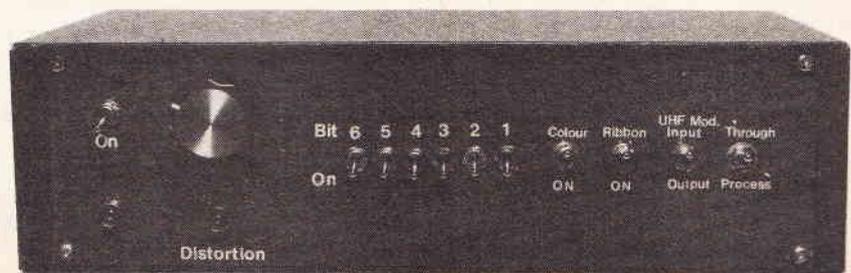To set up the Vandal for use, switch the Through/Process switch to Process to put it in line and apply a video signal. Adjust the



PROJECT: Video Vandal

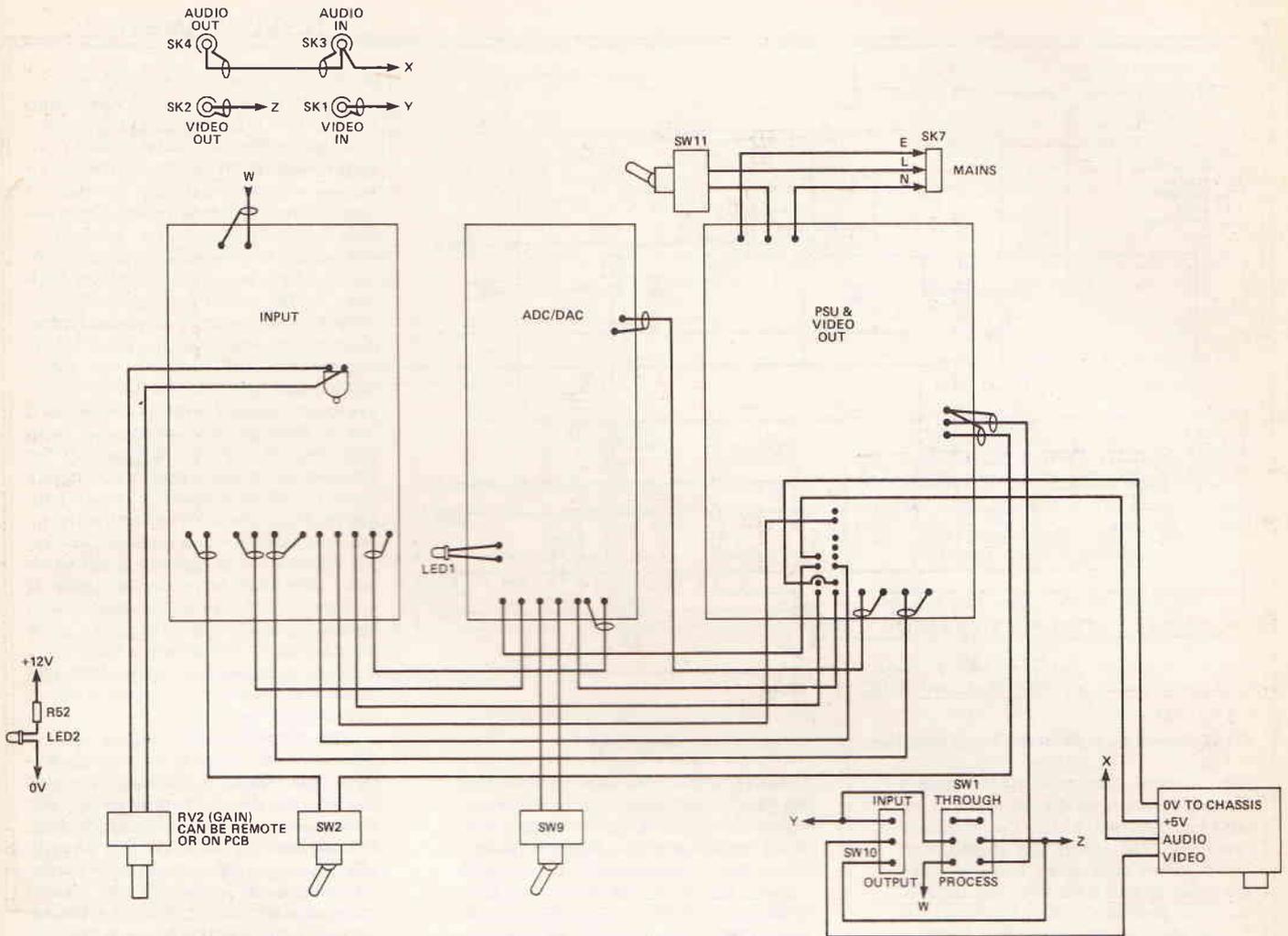


Fig. 6 Wiring diagram. Note that the connections to SK5, SK6 and the bit switches have been omitted for clarity.

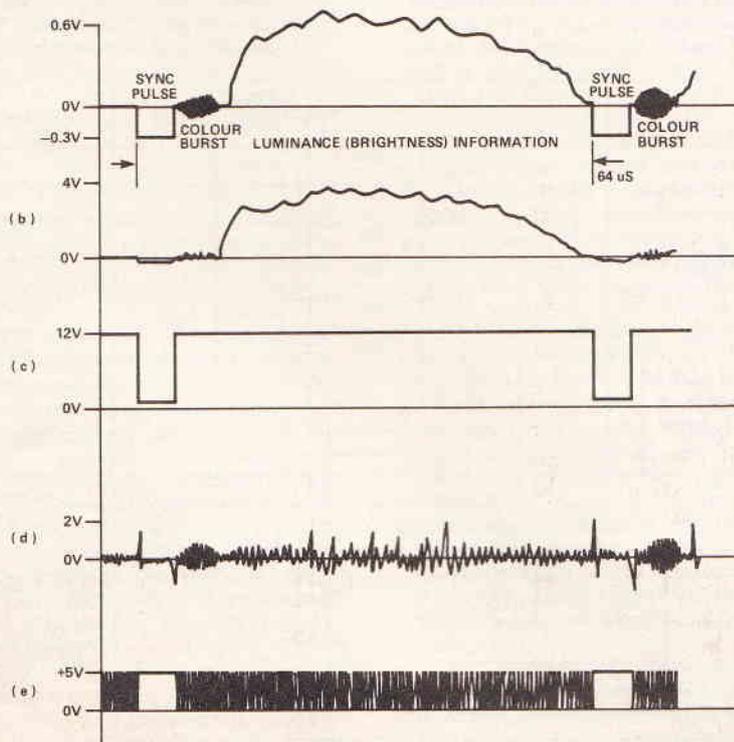


Fig. 7 Waveforms to be expected at various points in the circuit.

Gain control until the Distortion LED just doesn't light. Should you be working in monochrome, the colour switch SW2 should be switched to Off. If monitoring of the effects is required, then a TV (or whatever) should be connected to the UHF output. Now, taking the effects listed in the introduction in order:

1. Posterisation is achieved by switching the Bit Switches on and off. For example, eight levels of brightness (the setting most used by the Author) are achieved by switching on only bits 1, 2 and 3, the most significant bits. Another variation on this theme is to make any people on the screen look as though they have some kind of plague, by switching all bits except 1 on, and adjusting the gain control until their faces appear to have black patches on them.
2. The Ribbon (pseudo-Mosaic) effect is created by slowing the clock down with SW9. (Incidentally, if a 470K pot is connected in series with SW9 and C18 is increased to 220p, the stripe width becomes variable.)

HOW IT WORKS

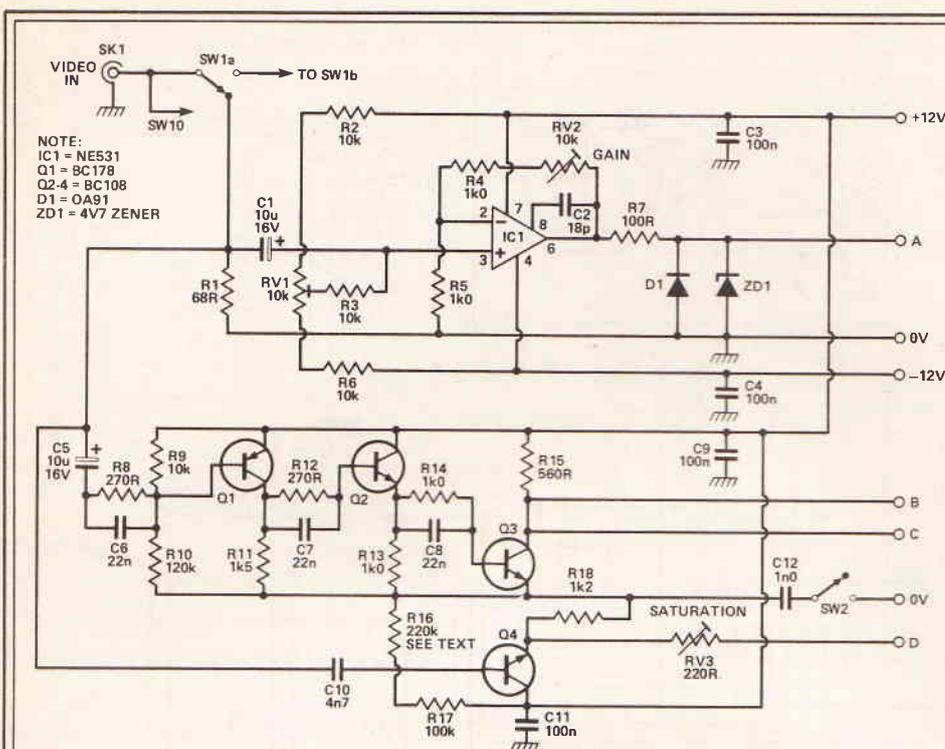


Fig. 8 Circuit diagram of the input amplifier, sync detector and colour filter.

The incoming composite video signal is first terminated by R1 to make it an approximate match for the standard (nominal 75R) video line impedance. The coupling capacitor C1 next isolates the input so that a DC bias (for DC restoration) provided by RV1 can be added before the signal is amplified by IC1, whose gain is adjusted by RV2 between about 1 and 10 to allow for variations in input levels and special 'white out' type effects. The ADC chip cannot tolerate negative voltages on its input, so diode D1 performs the dual function of limiting the maximum negative voltage to some $-0.2V$ and removing the negative going sync pulses — see Fig. 7b. The y (luminance) signal is not affected much by this providing that the bias from RV1 is adjusted so the black level is rough $0V$ or so as explained under the Setting Up section. D2 is included so that any spikes above $5V$ cannot get into the ADC. R7 limits the current which can flow into the diodes, protecting both them and the op-amp.

Sync detection is performed by the circuitry around Q1-Q2-Q3. Q1 is biased so that it is normally turned hard off. When a sync pulse comes along, it drags the base low via the differentiator C5 so that the transistor conducts during the pulse. This signal has not got very sharp edges, however, so R12/C7/Q2 and C8/R14/Q3 perform pulse shaping to improve the square wave edges. Q3 is the sync output device which drives the output circuit and synchronises the ADC's clock.

The chroma signal and some of the high frequency luminance is passed through C10 acting as a high-pass filter. This chroma signal is highly attenuated

however, so it is amplified by Q4. Matching the colour output level to the rest of the video signal is fairly important to avoid under- or over-saturation of hues on the final display and to ensure reliable colour burst detection. The colour level is adjusted by RV3, AC coupled to the output by C12 and may be switched on and off by SW2. There is no reason why the saturation level shouldn't be made variable from the front panel with a pot, but note that the leads to such a pot would have to be screened, as do the

leads to the colour killer switch SW2.

The ADC chip is the heart of the Video Vandal, so it is worth taking time over a description. The chip is of the 'Flash Converter' type which can manage some 19 million conversions per second. A slightly simplified description of how the chip works follows. The reference voltage on pin 9 is divided into 63 identical segments by a resistor ladder. Each 'rung' of the ladder is connected internally to one input of a window comparator (op-amp), with the other inputs commoned and brought out via a sample-and-hold (S&H) on pin 11. When a voltage is applied to pin 11 and the S&H lets it through, one of the 63 comparators will find its two inputs at the same potential and its output will change state. The 63 outputs are fed into a 1-of-63 to 6-bit converter — probably an array of diodes — and then into an output latch which is clocked at the same rate as the S&H. An extra comparator is included as an over-range indicator, with its input brought out on pin 2. To allow high accuracy, the resistors have to be laser trimmed during manufacture, and this is one reason why the chips are so expensive.

The amplified video signal coming from the input board is fed directly into the input of the ADC, but note R19 which protects the chip from damage by static discharge during assembly and testing. The high value is chosen so that it has no effect upon the input voltage. Pin 9 is the reference input, held at $3.9V$ by D3 and decoupled by C13. Q5 drives the 'Distortion' LED; although D2 protects the ADC against overvoltage, if the quantising range is exceeded, distortion in the form of bright whites 'peaking out' will occur. This effect is sometimes useful, though, so the ability to do it by setting the Gain

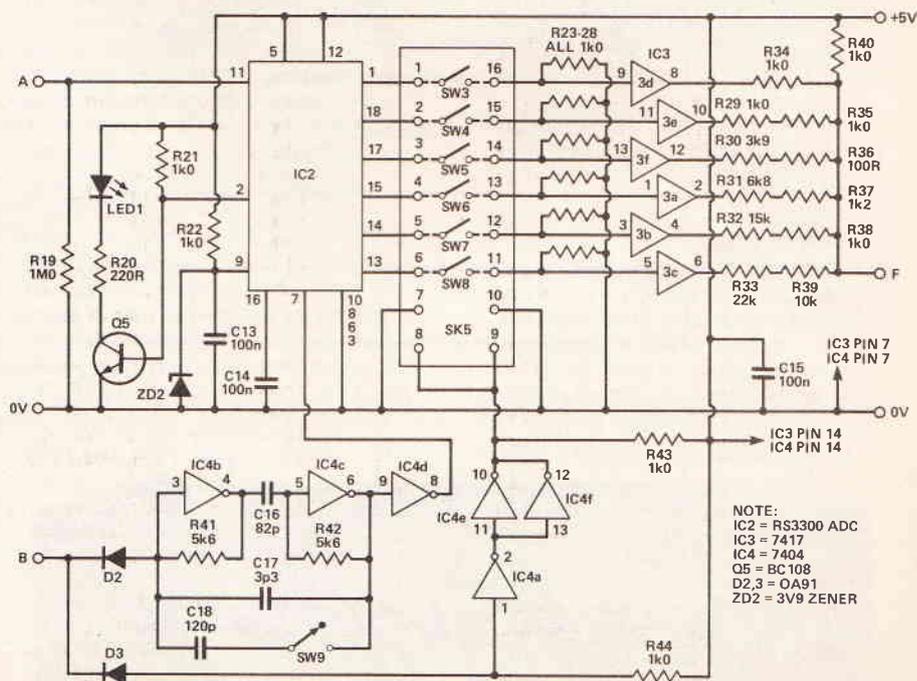


Fig. 9 Circuit diagram of the clock, ADC and DAC board.

PROJECT: Video Vandal

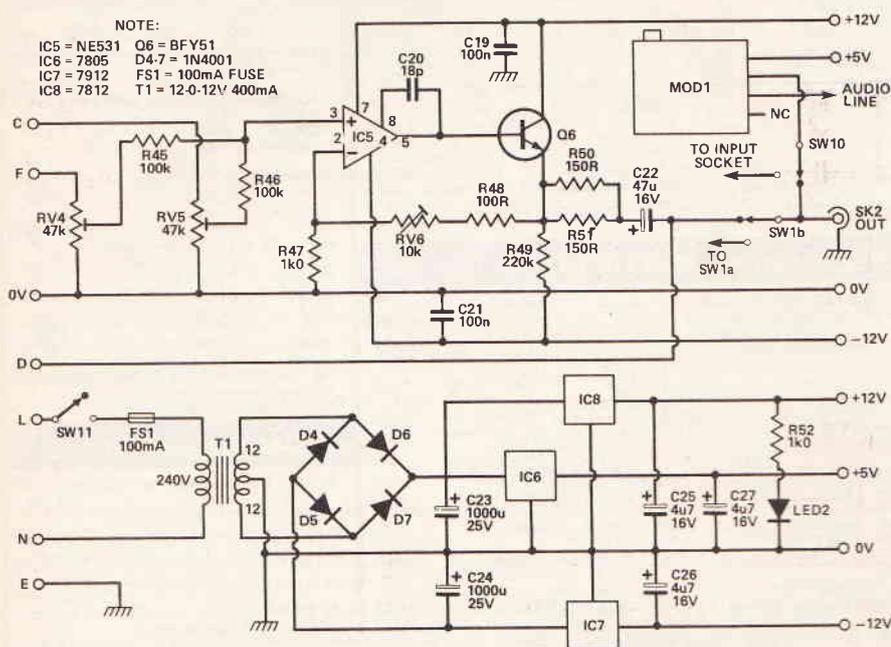


Fig. 10 Circuit diagram of the output amplifier and PSU.

control too high has been left.

The ADC chip is clocked at some 4-8 MHz by the oscillator built around two gates of IC4. It does not run at anything like the highest speed that IC2 can work at because of the need to adjust the frequency of clocking to provide the 'Ribbon' effect (which is nothing more or less than a digital S&H). If this effect is not required then C16 could be reduced to about 10pf, and C17 could be replaced by a crystal to reduce in-band quantisation noise (16 MHz was used in the MK.1 prototype) and C18/SW9 left in situ: this would make most sense as the ADC would work at the highest possible frequency unless specifically required to go slowly. The advantage of using a capacitor rather than a crystal is that it is much cheaper.

If the oscillator was allowed to run free, the 'Ribbon' effect would be completely unstable, so during sync pulses the clock is interrupted by D4 grounding an input. The otherwise unused gates in IC4 are used to provide a TTL sync output to the DATA socket.

'Bit Switches' SW3-8 switch on and off the output bits from IC2 to the Digital to Analogue Converter (DAC), R34-40. The switches provide the variable resolution feature of the Vandal. If all six switches are closed the output is practically the same as the input; with just S1 (most significant bit or MSB) set, the output is literally black and white with no grey between the extremes. If compared with photographic film, this is the electronic equivalent of 'lith' film. Putting different switches on and off creates different effects.

The DAC is of the simplest parallel type known to man — the R-2R ladder. This works by having resistances proportional to the significance of a bit switched in and out, pulling a line up or

down proportionally. For example, the MSB is connected via the lowest value of resistor (1K), the next most significant bit via twice that (remember we're working in binary) and the third four times etc. The overall effect is that the output voltage at point F is proportional to the binary number presented to the buffer gate array's inputs. Note that much of the linearity of the circuit is dependent on the DAC; for best results 2% or preferably 0.5% tolerance metal film resistors should be used.

The pull-down resistors R23-28 are included because a floating TTL input — apart from being a bad thing — considers itself to be 'high' (logic 1), and hence is in the wrong state as far as the DAC is concerned where a bit which is 'off' is considered to be grounded.

The output board's function is to recombine the y and sync signals into a composite signal, current amplify them, change from high impedance to 75 ohms, and finally pipe the colour back in again. The y and sync signals are simply added together in a passive mixer (RV4,5) and fed into an op-amp. Q6, which boosts the output current capability, is included in the op-amp's negative feedback loop so that the circuit will theoretically remain linear under all circumstances. R50 and R51 match the output to 75R impedance, with C22 AC coupling the circuit. The colour signal is the last thing which is added to the output because its frequency is higher than can be put through the op-amps without risk of instability. The NFB loop of R48 and RV6 sets the output level.

The power supply which shares the same board is quite straightforward: 12-0-12 VAC from the secondary of T1 is bridge rectified by D6-9 and regulated to +5V and $\pm 12V$ by ICs 6, 7 and 8.

3. This function requires the use of a computer with suitable software driving it — which is way beyond the scope of this article — but the connections between the computer's port and the DATA socket are of the 6 data bits and the sync pulse.

4. False colour (which should not be confused with the ordinary colour) is created by connecting an RGB monitor (the sort used with Oric, Electron and BBC computers is suitable) to the DATA socket, with the RGB inputs connected to bits 2, 1 and 3 respectively. This creates colours representing brightness, which may be filmed or displayed 'live'. Alternatively, the bits may be connected to a PAL encoder and then recorded or displayed.

THE DATA SOCKET AND BEYOND


The DATA socket is a very important part of the Video Vandal concept. Through this, it is possible to expand the system, as it carries the important 6 data lines along with the sync line, all at TTL levels. Through this socket it is possible to connect computers (for frame grabbing) or with an encoder or RGB monitor it is easy to produce 'false colour' pictures, where the RGB inputs of a monitor (or RGB to PAL encoder) are connected to the three most significant bit outputs so that differing colours represent the brightnesses. For example, green footballers playing on magenta grass with a red ball is a typical output. If there is sufficient interest, an RGB to PAL encoder card will be designed. Other than this, the Vandal could be used as a fast analogue to digital converter for other purposes, which is one reason why it is built on separate boards — if just the ADC/DAC board is built then a stand-alone high speed analogue to digital converter is at your fingertips.

The cheap n' cheerful Video Vandal should cost around £100-£130 to build: the nearest professional (studio quality) device that the Author has yet found — albeit also a Time Base Corrector — doesn't leave much change out of £17,000!

The author wishes to thank G8BVI for help with various prototype colour pass filters, and Mr. M. Boote of Beaminster School for help and the loan of test gear.

MICROPROCESSOR TIMER KIT

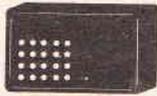Designed to control 4 outputs independently switching on and off at preset times over a 7-day cycle. LED display of time and day, easily programmed via 20-way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back-up circuit. Includes box, 18 time settings.



CT6000K £39.00
XK114 Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £3.90
701115 Additional Relays £1.65

BT STYLE PHONE CONNECTORS



Line Jack Units— Master Unit (first line unit) has bell capacitor and surge arrester.

Flush or surface mounting. Screw connectors.
Master (flush) (960 110) £3.00
Master (surface) (960 112) £3.00
Master (mini surface) (960 113) £3.00
Secondary (flush) (960 114) £2.65
Secondary (surface) (960 116) £2.65
Secondary (mini surf) (960 117) £3.00
Dual outlet adaptor (960 118) £4.20
4-way line cord — with plug to spade terminals (960 120) £2.00
4-way line cord (960 130) £0.20 per m

SECURITY PRODUCTS

Protect your home and property and save by building your own burglar alarm system.



Stair Mat 23 x 7 in (950 120) £1.70
Floor Mat 29 x 16 in (950 125) £2.60
Tamper-proof connecting block (950 110) £0.30
Door/Window Contacts, Flush mounting, 4 wire, Magnet/switch Per Pair. (950 140) £0.95
Window Tape 0.5" wide 50m. (950 145) £2.50
Window Tape Terminations Per pair. (950 150) £0.36
Key-operated Switch, 1 5A/250V

SPST Heavy chrome metal, (350 120) £4.50
Passive Infra-Red Detector
 Detects intruder's body heat. Range 10 metres. 12V DC, n/o & n/c contact. Size: 4 x 2 x 2 ins. (950 135) £45.00
Alarm Control Unit, 4 input-circuits, 2-instant and 2-delayed. Adjustable entry, exit and alarm times. Built and tested. Full instructions supplied. Size: 180 x 130 x 30mm. Supply: 12V DC. (950 160) £26.00
Smoke Detector, Easily installed. No adjustment. 1 year operation from PP3 alkaline battery. Consumption 25uA. Size: 175mm dia. x 45mm. White plastic case. (950 165) £8.50
8W Horn Speaker, 5.5 ins. 8 ohm. Ideal for sirens, etc. 2.5m lead and 3.5mm jack plug. (403 148) £6.15

OTHER KITS

CT1000K Clock/Timer £14.90
CT1000KB* Clock/Timer + Box £17.40
XK101 Electronic Lock £11.50
XK102* 3-Note Door Chime £5.50
XK113 MW Radio £5.50
XK126 DVM/Thermometer £15.50
DL1000K 4-Channel Light Chaser with Dimmer £15.95
DL3000K 4-Channel Chaser 3-Channel Sound-to-Light £8.95
TD300K + 300W Touchdimmer £12.95
TS300K + 300W Touchswitch £7.75
LD300K + 300W Lightdimmer £3.95
TDR300K + IR Remote Controlled Lightdimmer £14.95
MK6* IR Transmitter for TDR300K £4.50
TDE/K + Touchdimmer extension £2.50
TSA300K + Time Delay Touch Switch (300W) £5.00
MK1 Thermostat £4.60
MK2 Solid State Relay £2.60
MK4 Proportional Temperature Controller £6.50
MK5 Mains Timer (1KW) £4.50
 * includes box. + includes front panel
All kits include PCBs, components and assembly instructions.
 For further details send S.A.E.

LCD DIGITAL MULTIMETERS

LOW COST! 10M ohm. 3 1/2 digit 0.4 in display. Auto zero and polarity, low batt. indication, overload protection. Includes test leads, battery, spare fuse, manual, carrying case.
AC Volts: 0-200-500.
DC Volts: 0-2-20-200-1000.
DC Current: 0-20m-200mA.
Resistance: 0-2k-20k-200k-2M.
Size: 138 x 86 x 36mm. (405 202) £23.95
Professional — 10M, 0.5 in, 3 1/2 digit. Overrange and low battery indication. Overload protection. Includes leads, spare fuse, battery, manual and case. Transistor Checker. Size: 175 x 93 x 42mm.
AC Volts: 0-200-750.
DC Volts: 0-200m-2-20-200-1000.
DC Current: 0-20u-2m-20m-200mA-0-10A.
Ohms: 0-200-2k-20k-200k-2M-0-20M (405 204) £32.00



Auto Ranging, 3 1/2 digit 10mm display. Continuity buzzer, low battery, overload and range indication. 10A internal shunt for AC/DC current measurement. Carrying case supplied.
AC Volts: 0-2-20-200-600.
DC Volts: 0-0.2-2-20-200-1000.
AC Current: 0-200mA-0-10A.
DC Current: 0-200mA-0-10A.
Resistance: 0-200-2k-20k-200k-0-2M.
Size: 160 x 85 x 29mm. (405 206) £44.85
High Sensitivity Temperature Probe. For use with a multimeter to measure temperatures from -50°C to +250°C. Accuracy: 1.5°C@25°C, 2°C@100°C. Response time (in water), 5 seconds. Includes case, calibrated scale and instructions. (405 220) £7.95

COMPONENT PACKS

PACK 1 650 Resistors 47R-10M 10 per value £4.00
PACK 2 40 x 16V Electrolytics 10-1000uF, 5 per value £3.25
PACK 3 60 x Polyester Capacitors, 0.01-1uF/250V, 5 values £5.55
PACK 4 45 Presets 100R-1M £2.90
PACK 5 30 x Low Profile IC Sockets, 8, 14 & 16 pin £2.40
PACK 6 25 Red LEDs (5mm) £1.50

ELECTRONICS

11-13 Boston Road

London W7 3SJ

ORDERS

01-567 8910

ENQUIRIES

01-579 9794

01-579 2842 TECHNICAL AFTER 3pm



CLOCK TOWER




EALING & NORTH CIRCULAR RD

UXBRIDGE ROAD



CAR PARK

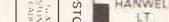

GARAGE

TOP QUALITY... TOP SERVICE BOTTOM PRICES!

For FREE CATALOGUE send 9 x 5 SAE contains full list of stock range at our competitive prices. Cash with order (except account customers). Access or Barclaycard telephone orders welcome. Add 8% p&p + 15% VAT to all UK orders. Overseas customers add £2.50 p&p. Europe, 1.60 elsewhere. GPO No. 529314002. Goods by return subject to availability. Shop open 9am - 5pm (Mon-Fri), 10am - 4pm Sat. ALL PRICES EXCLUDE VAT.

COMPUTER SHOWROOM
 TOP HARDWARE, LATEST
 SOFTWARE, PERIPHERALS,
 ACCESSORIES AND MUCH
 MUCH MORE!
 Export Enquiries welcome.

Anglia Industrial Auctions

Specialist Auctioneers to the Radio and Electronic Industry

NEXT SALE OF OVER 700 LOTS WILL BE HELD ON OCT. 17th 1984

THE LOTS BELOW WILL BE OFFERED FOR SALE UNLESS PREVIOUSLY SOLD

Lot No.	Description	Qty	Lot No.	Description	Qty	Lot No.	Description	Qty
1	H.P. SHF Signal Generators Type 620A/6203/620A	3	51	Telegon Oscilloscope Type D43R	2	101	Co-ax Cable Type Unradio M112	300M
2	Schomand Wave meters Type FD1 with converters	2	52	Radiometer Generator Type M27g	2	102	Tektronix Oscilloscope Type 551 C/W Plug-ins & Trolley	1
3	EH Research Labs Pulse Generator Type 139MB	3	53	Coulant Power Unit 7v 15a. 12v 1a. 4v 3a. 24v 7a	1	103	Rhode & Schwartz Microwave Power Meter Type BN4212	1
4	H.P. Rx Meter Type 250B	1	54	Marconi Sine Square Pulse & Bar Generator 625	1	104	Marconi Microwave Sweep Oscillator Type 6600A	1
5	Airmec Millivoltmeter Type 301A	3	55	H.P. DC Power Supply 0-43v 3amp	1	105	Marconi Signal Generator Type TF 995A	1
6	Airmec Millivoltmeter Type 301	3	56	H.P. VTVM Model 400D	2	106	Schomand Modulator MAF Type BN 41962	1
7	Data Dynamics Terminal	1	57	Jerrild Field Strength Meter Model T7048	1	107	Schomand Decade Signal Generator 300Hz-100MHz Type ND 100M	1
8	Marconi Timebase Delay Generator Type TF 1415	1	58	Marconi Universal Bridge Type TF 868A	2	108	Rhode & Schwartz Decade Signal Generator Type BN 41104	1
9	Marconi FM/AM Modulation Meter Type TF 2300	1	59	Marconi Standard Signal Generator Type TF 867	3	109	Telegon Oscilloscope Type S32A	4
10	AIM Electronics Variable Function Generator	1	60	Airmec Sweep Signal Generator Type 352	1	110	Marconi AM Signal Generator Type TF 801D/8S	1
11	Pye VHF Signal Generator Type SG2V	1	61	Solartron Digital Voltmeter Type LM 1420 2	1	111	Marconi VHF Signal Generator Type TF 1064B/EM	1
12	Pye HF Transceiver 6 channel Type SSB 130	1	62	Marconi Programmable FM/AM Modulation Meter Type TF 230A	1	112	Marconi Universal Bridge Type TF 868B	2
13	Pye Signal Generator Type SSSU	1	63	Marconi Programmable UHF Attenuator Type TF 216B	1	113	Marconi Tx & Rx Output Test Set Type TF 1065	2
14	Pye Battery Chargers Type FC0 9 volt.	96	64	Wavetek Programmable VCG Model 155	1	114	H.P. SHF Signal Generator Model 618B	1
15	Pye Modulation Meter Type MM1	3	65	Cave True RMS Valve Meter Type 612A	3	115	Marconi Noise Generator Type TF 106/2	2
16	H.P. Wave Analyser Model 302A	1	66	Racal VHF Callistors Type 850	10	116	Marconi Signal Generator Type TF 995A/5	2
17	Tektronix Oscilloscope Type 545A Less Plug-ins	2	67	Eddystone Communications Receiver Type 680X	1	117	Marconi Signal Generator Type TF 995B/5	2
18	KSM Electronics Pulse Generator Type T1B/D	2	68	Sanders Microwave Oscillator Type CLC 2-4	1	118	Marconi VHF Alignment Oscilloscope Type TF 1104/1	1
19	EMI Electronics Oscilloscope Plug-ins Type TF 76	2	69	General Radio Standard Signal Generator Type 1925	1	119	Marconi Signal Generator Type TF 1066B/6S	1
20	EMI Electronics Oscilloscope Plug-ins Type T7/1	6	70	Telegon Oscilloscope Type D43	1	120	Tektronix Oscilloscope Type RM17	1
21	Pye Motophone Portables Mid Band	1	71	Marconi Frequency Selector Unit Type TK7047	1	121	Telegon Oscilloscope Type S31R	1
22	Dynacore Oscilloscope Type D7100	1	72	Marconi RF Power Meter Type TK 7056	1	122	Telegon Oscilloscope Type D52	1
23	Wayne Kerr Universal Bridge Type CT375	2	73	Marconi Programmable Voltmeter Type TK 2607	1	123	Marconi Audio Tester Type TF 894A	1
24	Decwriter Terminal	1	74	Electro International UHF Pre Amp Type Ap501R	1	124	Telegon Oscilloscope Type S43	2
25	Ferro-Mag 3ph 240v 5.4kva Transformer	1	75	Honeywell Power Line Test Set Type PLT-1	1	125	Marconi FM Signal Generator Type TF 2006 10-220 FHz	1
26	Tektronix Oscilloscope Plug-ins Type G	4	76	Telex Digital Voltmeter Type TE313 03	1	126	Pye W30 Westminster Low Band 24 volt.	14
27	Marconi RF Power Meter Type TF 1020A	1	77	BPL Super Megohmmeter Type RM 170	1	127	Racal Communications Receiver Type RA 17	1
28	Marconi 100 Watt 7db Attenuator Type TM 5280	1	78	Chart Recorders Various	3	128	Advance Oscilloscope Type OS 25A	3
29	Advance Oscilloscope Type OS 2000R	1	79	Marconi AF Power Meter Type TF 2500	1	129	Marconi UHF Signal Generator Type TF 1060/2	2
30	Marconi VHF Signal Generator Type TF 1064B	2	80	Rhode & Schwartz Signal Generator Type BN 41409	1	130	LAN-Elec Ltd. Scabios P.U. Type LP 401T	1
31	Rhode & Schwartz Power Signal Generator BN 41001	1	81	Trendala Test Set No. 5	1	131	SE Labs Oscilloscope Type SM 111	1
32	Ferranti Computer Terminal Type WDM 2000	1	82	General Radio VHF Oscillator Type 1363	1	132	Advance Oscilloscope Type OS210	2
33	Pye IF Signal Generator	4	83	Tektronix Oscilloscope Type 545B less Plug-ins	1	133	Rhode & Schwartz UHF Test Receiver Type BN 1521	1
34	Marconi Oscilloscope Type TF 1331A	1	84	Nargard Oscilloscope Type 311 C/W 3 Plug-ins	1	134	Tektronix Oscilloscope Type S47 less Plug-ins	1
35	Bruel & Kjaer Microphone Amplifier Type T 2604	1	85	Marconi Deviation Test Set Type 5076B	4	135	Telegon Oscilloscope Type V91 30475	4
36	Tektronix Oscilloscope Type 531A C/W Type H Plug-in	1	86	Scalamp Galvanometers	10	136	Airmec Modulation Meter Type 409	2
37	Tektronix Oscilloscope Type S47 C/W Type I A2 Plug-in	1	87	Electrolytic Capacitors 2200mfd. 25 volt.	1500	137	Marconi RC Oscillator Type TF 1101	2
38	Advance Signal Generator Type C2	1	88	Electrochrome 9in Video Monitors	4	138	Marconi Sensitive Valve Voltmeter Type TF 1100	2
39	Marconi 25 MHz Pulse Generator Type 2025	1	89	Equipment & Multi Core Cables	16	139	Foster Old Field Varac 0-270vair 40amp.	1
40	Rhode & Schwartz Power Test Adaptor Type BN 413115	1	90	Telegon Oscilloscope Type S 51B	2	140	Hewlett Packard Sweep Oscillator Type 692D	1
41	Marconi Frequency Coverter Type TF 2400/TM7164	1	91	Sony Emby Video Tape Reels Type RH7V	33	141	Xenon Time Mark Generator Type RM 181	1
42	Solartron Recorder Drive Unit Type A295	1	92	Electronics Instruments Ltd. Chronotron Type 25E	1	142	Tektronix Time Mark Generator Type 180A	1
43	Marconi UHF FM Signal Generator Type TF 2012	1	93	Beltex Power Supply Unit Type TSS 76	1	143	Telegon Oscilloscope Type S54AR	1
44	Wandel & Gollermann Filter Unit Type LDEF-2	1	94	Advance Millivoltmeter Type 77A	5	144	Telegon Oscilloscope Type S31R	1
45	Rhode & Schwartz Wave meter Type BN 15221	1	95	Roband Double P.S.U. Type T104	1	145	Sony Video Tape Type V-30H	108
46	Pye UHF Signal Generator	3	96	Marconi Output Power Meter Type TF 893	3	146	Equipment Oscilloscope Calibrator Type C1	1
47	H.P. Signal generator Model 606A	1	97	H.P. Storage Oscilloscope Type 181 Complete with Manuals	1	147	Marconi 20 FHz Sweep Generator Type TF 1099	1
48	Avo Signal Generator	1	98	Marconi AF Power Meter Type TF 893A	3	148	Transistor Type 2N1740	750
49	Rhode & Schwartz Polyskop Type oA 2090B	1	99	Marconi Valve Volt meter Type TF 1041	3	149	Venner Digital Counter Type TSA 663A/2	2
			100	Telegon Oscilloscope Type S54A	3			

5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE. Phone ELY (0353) 860185

ELECTRON SPEAKER

Turn your Electron into a chatterbox with this project from John Wike.

As the title suggests this is a project to add a speech unit to the Acorn Electron. It plugs into the rear edge connector, is easy to use and does not interfere with any other devices that are connected.

The system is based on the ubiquitous General Instruments speech processor, type SPO256-AL2. This chip contains all the components necessary to produce 64 speech sounds (or allophones).

Associated with it are six other chips for interfacing and audio output.

The board is driven by a short Basic PROCEDURE and 73 bytes of machine code; the latter is easily assembled using the built-in assembler on the Electron. The speech codes are stored in a queue and once the process has

started a non maskable interrupt (NMI) routine is used to get data from the queue. This means that the computer can carry on with the rest of the program while the circuit is speaking.

The Hardware

The circuit consists of the speech processor, oscillator, address latch, decoding, and NMI generator. The oscillator circuit is

HOW IT WORKS — HARDWARE

Gates IC1a, IC1b and IC2a decode the address and control lines so that a write operation in the range &C000 to &DFFF will cause the eight least significant bits of the address bus to be latched in IC3. Also address line A12 will be latched in IC6a and a clear pulse will be applied to latch IC6b.

When the circuit is reset the standby (SBY) output of the speech processor (IC5) goes high and latch IC6a, pin 8 goes low, disabling gates IC2b and IC1c. When the computer writes to latch IC3 at address &C001, line A12 will be low so

IC6a,8 will go high and IC2b,6 will apply a low level to the address load (ALD) input of IC5. Less than a microsecond later SBY will go low again and IC2b,6 will go high, clocking latch IC6b.

As the outputs of both IC6a and IC6b will now be high, IC1c,3 will go low causing a non maskable interrupt (NMI). In response to this the computer will write to IC3 at address &C0xx and latch IC6b will be cleared, cancelling the NMI via IC1c. Some tens of milliseconds later, SBY will go high again, causing IC2b,6 and ALD to go low. IC5 will load data

from IC3, SBY will go low, there will be an NMI and the computer will write to IC3 at a new address &C0yy. When there is no more speech data the computer prevents further interrupts by writing to address &D000. This sets IC6a,8 low and disables IC1c.

Note that because new data is loaded into IC3 as soon as the old data has been loaded into IC5, the speech inflection bits are one step ahead of the actual speech data.

The inflection circuit is based around a voltage controlled oscillator chip, IC4. The control voltage for this is derived via a crude analog to digital converter formed by R3, R4, RV1, RV2 from the latch outputs IC3,9 and IC3,12. The output of IC5 is a pulse width modulated square wave which is passed through filter R5, R6, C4, C5 and volume control RV3 to the audio amplifier IC7.

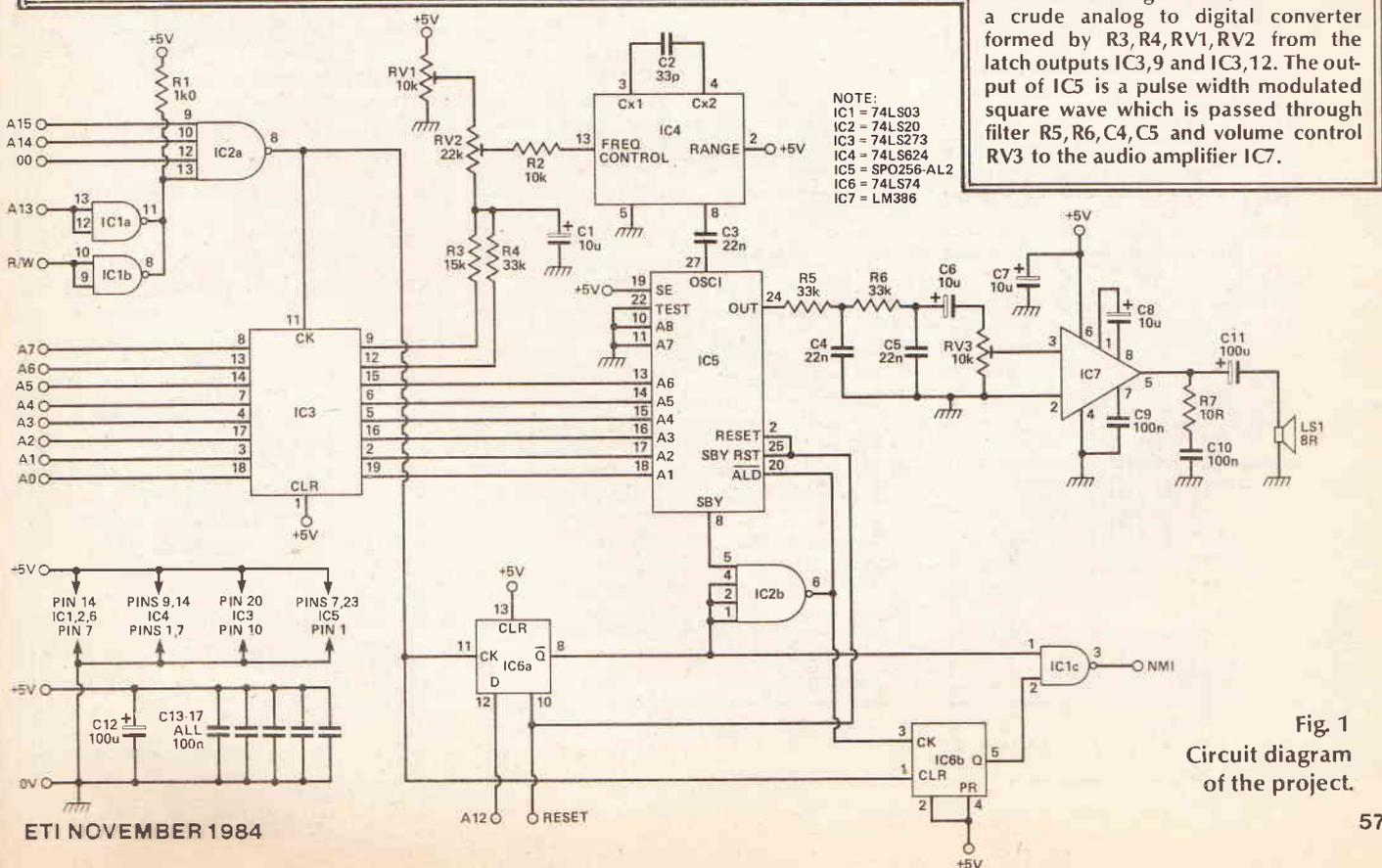


Fig. 1
Circuit diagram
of the project.

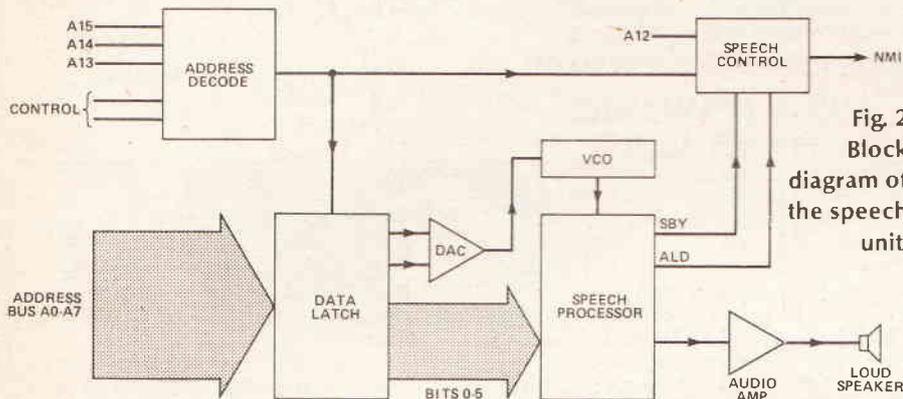
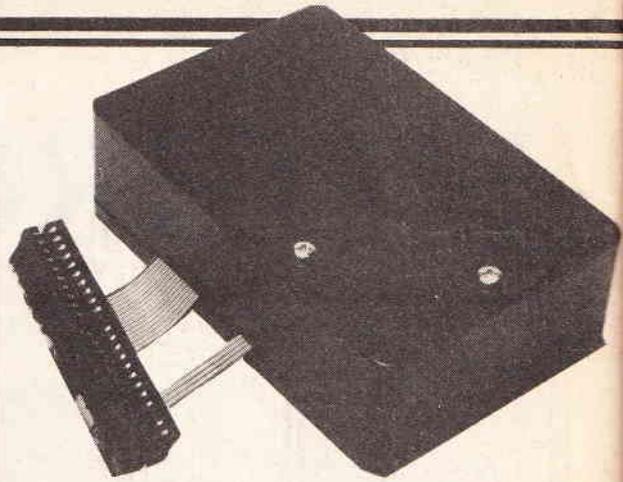
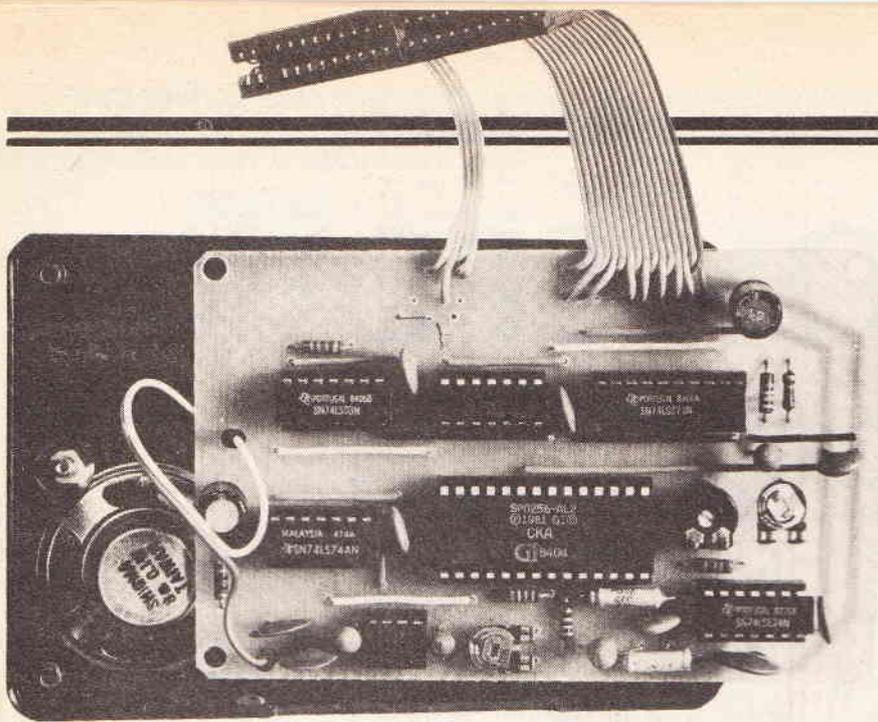


Fig 2 Block diagram of the speech unit.

in fact voltage controlled. The control voltage is produced by a rough digital to analog converter from the two most significant bits of the speech data. This allows a certain amount of inflection in the output voice. To allow the speech processor to load fresh data as quickly as possible it is necessary to latch each allophone while the previous one is being spoken. This means that the inflection bits will affect the preceding allophone.

BUYLINES

There should be no problems here. The SPO256-AL2 and the box are available from Rapid Electronics, and the PCB is available from the author at 9, Lon-y-Garwa, Caerphilly, Mid-Glamorgan for £6 inc. p&p.


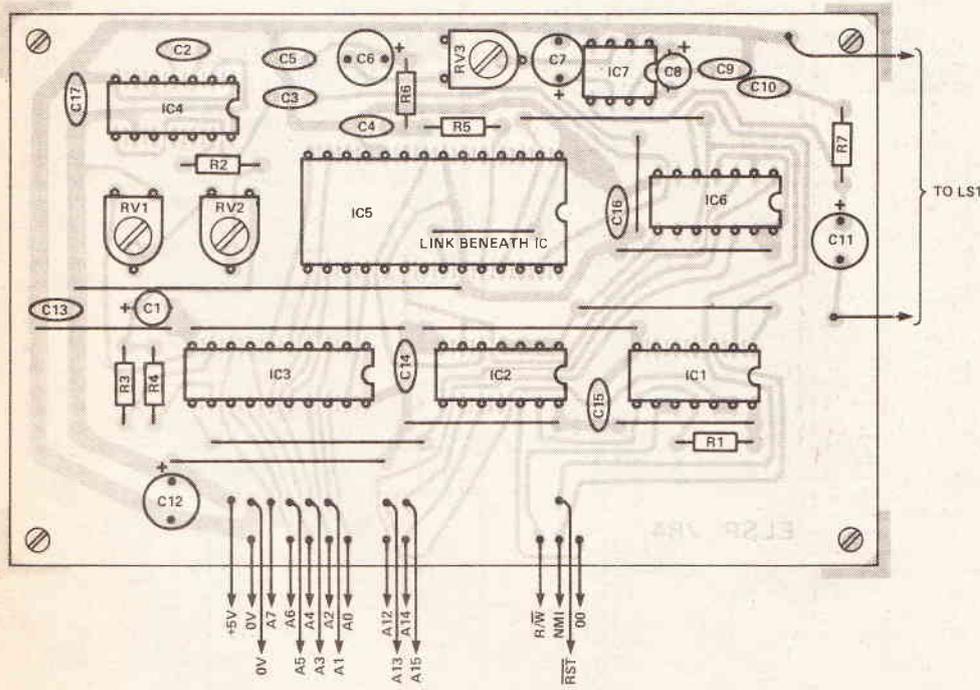


Fig 3 (above) Overlay diagram.

Fig 4 (left) Connector details.

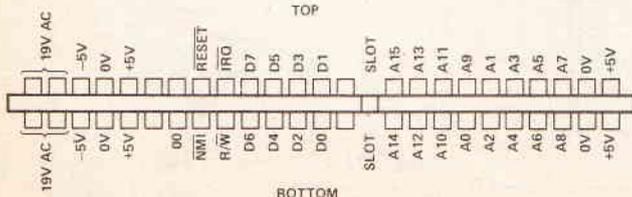

PARTS LIST

RESISTORS (all 0.25 watt 5%)

R1	1k
R2	10k
R3	15k
R4,5,6	33k
R7	10 R
RV1,3	10k
RV2	22k

CAPACITORS

C1,6,7,8	10uF Tantalum
C2	33pF
C3,4,5	22nF
C9,10,13-17	100nF
C11,12	100uF electrolytic

SEMICONDUCTORS

IC1	74LS03
IC2	74LS20
IC3	74LS237
IC4	74LS624
IC5	SPO256-AL2
IC6	74LS74
IC7	LM386

MISCELLANEOUS

Double sided 25 way edge connector; ribbon cable; IC sockets; printed circuit board; 8 ohm 0.1 watt loudspeaker; BICC/VERO plastic box 3" x 4.5" x 1.5".

PROJECT: Electron Speaker

```
LIST
10 PROCINIT:ONERRORGOTO40
20 DIM Q1% (100),Q2% (100)
30 CLS:PRINT:PRINT:PRINT
40 PROC SPEAK(796)
50 REPEAT:PROC SPEAK(799)
60 PRINT"PLEASE ENTER A NUMBER ";
70 INPUT I%
80 PROC SPEAK(I%+800)
90 UNTIL FALSE
95 :
```

```
796 DATA 4,155,135,173,15,117,132,4,216,70,131,26,154,80,67,18,143,79
797 DATA 67,19,196,13,19,132,24,134,67,7,45,7,105,77,167,152,139,131,55,183
798 DATA 137,147,136,116,67,0
799 DATA 9,45,19,43,3,7,11,2,13,51,3,20,3,11,15,16,1,28,51,0
```

```
800 DATA 43,60,53,0
801 DATA 46,15,15,11,0
802 DATA 13,31,0
803 DATA 29,14,19,0
804 DATA 40,40,58,0
805 DATA 40,40,6,35,0
806 DATA 55,55,12,12,2,41,55,0
807 DATA 55,55,7,7,35,12,11,0
808 DATA 20,2,13,0
809 DATA 11,24,6,11,0
810 DATA 13,7,7,11,0
811 DATA 12,45,7,7,35,12,11,0
812 DATA 13,48,7,7,45,35,0
813 DATA 29,51,1,2,13,19,11,0
820 DATA 13,48,7,7,11,1,2,13,19,0
900 DATA 57,15,15,11,1,2,33,39,12,12,1,21,0
950 :
```

```
1000 DEF PROC SPEAK(X%)
1010 RESTORE X%:A%=0
1020 IF Q1%=Q2% Q%=Q1% ELSE Q%=Q2%
1030 REPEAT:READ B%:(Q%+A%)=B%
1040 A%=A%+1:UNTIL B%=0
1050 CALL start,Q%:END PROC
1055 :
```

The address decoding was designed with two factors in mind. The first factor was that the circuit should not interfere with any additions that might use the official extension addressing area (&FC00 to &FCFF). The second factor was a desire to keep the chip count down. It was decided to make the circuit write-only and to address it in parallel with the operating system ROM. The addresses chosen (&C000 to &DFFF) mean that only 3 address lines need decoding and as the computer normally only reads from this area there will be no faulty triggering. The one snag with this is that Acorn have not disabled the ROM during write operations, so any data output by the speech routines would conflict with data from the ROM. This problem was overcome by using indexed addressing to output the data on the address bus. A read followed by a write will latch the lower eight bits of the address bus whilst ensuring that the data bus does not conflict with the contents of the ROM.

When the speech processor is ready to receive more data, an NMI is generated, to be cleared when the new data is latched.

Fig 5 The software needed to use the unit.

```
2000 DEF PROC INIT
2010 point=&8D:lasto=&8F:block=&601
2020 spon=&C000:spoff=&D000
2030 O%=&D00
2040 FOR I=0 TO 2 STEP 2
2050 P%=0%
2060 { OPT I
2065 :
2070 .inter PHA
2080 LDAlasto
2090 BNEinter2
2100 LDAspoff
2110 STAspoff
2120 PLA
2130 RTI
2135 :
2140 .inter2 TYA
2150 PHA
2160 LDY#0
2170 LDA(point),Y
2180 JSRstart2
2185 :
2190 INCpoint
2200 BNEinter4
2210 INCpoint+1
2215 :
2220 .inter4 PLA
2230 TAY
2240 PLA
2250 RTI
2255 :
2260 .init LDA#0
2270 BEQstart2
2275 :
2280 .start LDAlasto
2290 BNEstart
2295 :
2300 LDAblock
2310 STApont
2320 LDAblock+1
2330 STApont+1
2335 :
2340 LDY#0
2350 LDA(point),Y
2360 TAX
2370 INY
2380 LDA(point),Y
2390 STApont+1
2400 STXpoint
2405 :
2410 TYA
2415 :
2420 .start2 STAlasto
2430 TAY
2440 LDAspon,Y
2450 STAspon,Y
2460 RTS
2465 :
2470 } :NEXT
2480 CALLint:ENDPROC
>
```

HOW IT WORKS — SOFTWARE

The machine code interface, assembled in PROCINIT (lines 2000 to 2470), uses three zero-page memory locations. The two labelled "point" form a 16 bit pointer into the speech queue, and the one labelled "lasto" stores the last byte output. If "lasto" contains zero then the speech processor is inactive.

There are three entry points into the machine code. Entry at ".init" (line 2260) initialises the system by clearing location "lasto" and the speech data latch.

Entry at ".start" (line 2280) causes the program to halt until the previous speech queue is finished (lines 2280 to 2290). It then examines the parameter block at &601 and loads "point" with the start of the next queue (lines 2300 to 2400). Then a non-zero pause value, ie. 1, is stored in "lasto" and interrupts are enabled by writing to &C001 (lines 2410 to 2460).

Entry at ".inter" occurs only in response to a non maskable interrupt. If "lasto" contains zero then further interrupts are disabled by writing to &D000 (lines 2070 to 2130). Otherwise a byte from the queue is written to the speech latch and "lasto", and the pointer is up-dated (lines 2140 to 2250).

The BASIC section of the test program contains the speech data strings (lines 796 to 900). The main loop (lines 10 to 90) dimensions two queues, Q1% and Q2%, and prompts for a number to be entered. The procedure PROC SPEAK (lines 1000 to 1050) restores a pointer to the correct data string and loads the string into alternate queues. It then calls the machine code with the start of the queue as a parameter.

In order to produce your own speech strings you must first choose each allophone from the table. Then decide on the inflection value (0, 64, 128, or 192) required for each allophone and add this to the following allophone, forming them into a DATA statement ending in zero. To produce your sounds use procedure PROC SPEAK (line number of your data).

Writing to addresses in the range &C000 to &CFFF enables interrupts, and the range &D000 to &DFFF disables them.

The audio output is amplified by an IC power amplifier and applied to a small 100mW loudspeaker. The board has been designed to fit with the loudspeaker inside a BICC/VERO 3" x 4.5" x 1.5" plastic box using the box lid screws for mounting.

The Software

The program listed here to test the circuit contains Basic routines, machine code, and sample data strings. Two sound queues are provided so that one can be loaded

PROJECT: Electron Speaker

while the other is being output. These queues obviously have to be long enough to accommodate the longest data string used. When the data has been loaded into a queue a machine code routine is called to set up a pointer into the queue for use by the interrupt routine and to start the speech processor by writing to address &COO1.

In Electron Basic, a call to a machine code routine can be followed by several parameters. The locations where the values of these parameters are stored are

put into a block of memory starting at &600, and the location of the first parameter is in &601- &602. This facility is used here: the start address of the queue is held in a variable which is given as a parameter to the machine code call. The contents of &601-2 are then used to find the value of the variable which is stored as a pointer.

Each data string must end with a zero, which is used as an end marker. If this would affect the inflection of the last spoken data a pause with the correct inflection

bits can be inserted. As each byte is written to the speech board it is also stored in a memory location. When the interrupt routine detects a zero in that location it disables further interrupts by writing to address &D00.

As the NMI routine in the Electron must start at &D00 that is where the machine code is assembled. The assembly is included in the initialisation PROCEDURE because pressing BREAK resets the byte at &D00 to a return from interrupt instruction.

Construction

Construction of this project should present no difficulty. The board is single sided and there are only thirteen links to fit. The use of IC sockets is recommended — do not forget the link underneath IC5. Once all the components have been soldered in, the edge connector can be attached via approximately three inches of 19-way ribbon cable and the loudspeaker can be connected with about four inches of wire. If the board is going to be mounted in a box, a slot must now be made in the side of the box at the point where the ribbon cable will come out.

Setting Up

Having checked very carefully for shorted tracks etc, insert all the ICs and connect the board to the Electron. Type in ?&&C013=?&&C013 and you should hear a repetitive noise. It is actually an 'ee' sound but do not worry if it is not immediately recognisable. Adjust RV3 to give a suitable volume level out of the speaker. Now type ?&&C000=?&&C000 and the noise should stop.

If you have access to an oscilloscope, program function key 1 to do ?&&C000=?&&C000 and function key 2 to do ?&&C0C0=?&&C0C0, using the *KEY commands. Monitor the waveform on pin 8 of IC4 and you should see the frequency changing when you press the two function keys. Adjust RV1 and RV2 so that the frequency produced by key 1 is as close as possible to 2.5 MHz and that from key 2 is as close as possible to 3.5 MHz.

If you cannot get to an oscilloscope, program the keys to ?&&C013=?&&C013 and ?&&C0D3=?&&C0D3 and adjust RV1 and RV2 to give the best sounding voice and variation. Now try the test program and make any final adjustments.

ETI

Sound Type	Symbol	Code	Duration	Example	Notes	
Silences	/PA1/	00 0	10ms			
	/PA2/	01 1	30ms			
	/PA3/	02 2	50ms			
	/PA4/	03 3	100ms			
	/PA5/	04 4	200ms			
Short vowels	/IH/	0C 12	70ms	sIt	These vowel sounds can be doubled to lengthen them.	
	/EH/	07 7	70ms	End		
	/AE/	1A 26	120ms	hAt		
	/UH/	1E 30	100ms	bOOk		
	/AO/	17 23	100ms	AUght		
	/AX/	0F 15	70ms	sUcceed		
	/AA/	18 24	100ms	hOt		
	Long Vowels	/IY/	13 19	250ms		sEE
/EY/		14 20	280ms	trAy		
/AY/		06 6	250ms	klIt		
/OY/		05 5	420ms	vOlce		
/UW1/		16 22	100ms	tO		
/UW2/		1F 31	260ms	fOOd		
/OW/		35 53	240ms	zONe		
/AW/		20 32	370ms	dOWn		
R-coloured vowels	/ER1/	33 51	160ms	lettER		
	/ER2/	34 52	300ms	fERn		
	/OR/	3A 58	330ms	fORtune		
	/AR/	3B 59	290ms	aARm		
	/YR/	3C 60	350ms	hEAR		
	/XR/	2F 47	360ms	stARe		
Resonants	/WW/	2E 46	180ms	We	(See also /WH/)	
	/RR1/	03 14	170ms	Read		
	/RR2/	27 39	130ms	cRane		
	/LL/	2D 45	110ms	Like		
	/EL/	3E 62	190ms	angLE,	squirrEl	
	/YY1/	31 49	130ms	cUte,	compUter (Y-sound)	
Voiced Fricatives	/VV/	23 35	190ms	Vest		
	/DH1/	12 18	290ms	THis		
	/DH2/	36 54	240ms	baTHe		
	/ZZ/	2B 43	210ms	Zoo		
Voiceless Fricatives	/ZH/	26 38	190ms	pleaSure,	aZure	
	/FF/	28 40	150ms	Food	These allophones may be used doubly for initial or singly for final positions.	
	/TH/	10 29	180ms	THin		
	/SS/	37 55	90ms	veST		
/SH/	25 37	160ms	SHip			
Voiced stops	/HH1/	18 27	130ms	He	(see also /WW/)	
	/HH2/	39 57	180ms	Hoe		
	/WH/	30 48	200ms	WHig		
	/BB1/	1C 28	80ms	riB		Usually need 10-30ms silence preceding these.
	/BB2/	3F 63	50ms	Beast		
	/DD1/	15 21	70ms	enD		
	/DD2/	21 33	160ms	Down		
	/GG1/	24 36	80ms	Guest		
/GG2/	3D 61	40ms	Got			
/GG3/	22 34	140ms	peG			
Voiceless Stops	/PP/	09 9	210ms	Pow	Usually need 50-80 ms silence preceding these.	
	/TT1/	11 17	100ms	parTs		
	/TT2/	0D 13	140ms	To		
	/KK1/	2A 42	160ms	Can't		
	/KK2/	29 41	190ms	speak		
	/KK3/	08 8	120ms	Crane		
Affricatives	/CH/	32 50	190ms	CHurCH		
	/JH/	0A 10	140ms	JudGe		
Nasal	/MM/	10 16	180ms	Milk		
	/NN1/	0B 11	140ms	thiN		
	/NN2/	38 56	190ms	No		
	/NG/	2C 44	220ms	aNGer		

Table 1 The allophones that the unit can generate.

**KITS FROM £7
...TO £60**


Sparkrite

Buy Sparkrite Brand Leading Auto Electronics in self-assembly kit form – And save pounds!!

- Electronic Ignition systems – contact triggered and contactless
- Electronic Car Security Systems – including a new ultrasonic unit
- Car Drive Computer – with 12 functions

SEND FOR FREE LITERATURE PACK – TODAY!

8 SOPHISTICATED
KITS TO CHOOSE
FROM.

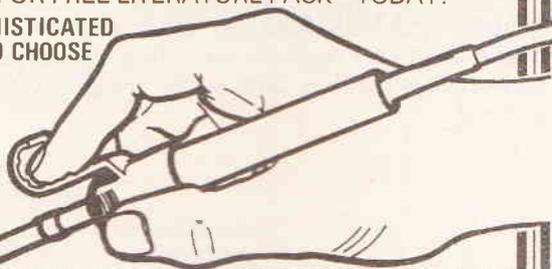

To: SPARKRITE (A Division of Stadium Ltd), Queensway, Enfield, EN3 4SD.
Telephone: 01-804 4343

NAME

ADDRESS

ETI

**GW ELECTRONIC
TEST INSTRUMENTS
OSCILLOSCOPE G05-3310**



Triggering Oscilloscope

- Sensitivity: 5mV to 5V/div
- Bandwidth: DC or 2Hz to 10MHz
- Sweep Rate: 10ms to 0.1us/div



GATEWAY LTD

PO Box 11 Bishop's Stortford
Herts CM23 2XA Tel 0799 21489

Master Electronics – Microprocessors – Now! The Practical Way!

- Electronics – Microprocessors – Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio – T.V. – hi-fi and all types of electronic/computer/industrial equipment.



New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

Please send your brochure without any obligation to: –

I am interested in:

NAME

ADDRESS

ETI/11

BLOCK CAPS PLEASE

- ELECTRONICS
 MICROPROCESSORS
 RADIO AMATEUR LICENCE
 CITY & GUILDS EXAMS

Other Subjects

OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)

British National Radio & Electronics School Reading, Berks. RG1 1BR



**NEXT
MONTH**

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

TV FRAMESTORE

Would you like to be able to capture a TV picture, then manipulate it with your home computer? We're going to tell you how it's done. This project for experimenters will use a flash-converter ADC with state-of-the-art circuitry to make it possible to use relatively slow DRAMs for the actual storage.

VARIO UPDATE

Following on the success of the original article, Lindsay Ruddock has had a look at some of the points we've been asked about by readers, including improved temperature compensation and some suggestions for 'total energy'.

DIGITAL DELAY LINE

Of course, the other sort of analogue signal you might be interested in storing in a digital form is music. So that's just what we're going to show you how to do in the description of this project. Developed with value for money in mind, this is a high-quality unit with some novel circuitry. It offers percussion and freeze, and a maximum delay time of 1.3 seconds (with 5 kHz bandwidth). The unit can be used to generate a large number of effects, including chorus, flanging, vibrato, pseudo-reverb, slap-back (What? - Ed.), long echoes, single and multiple echoes, etc, etc.

EXPERIMENTER'S DRAM CARD

Phil Walker's been looking for some extra memory of late, and here's the result, a 64K DRAM card. We originally designed the card because of difficulties with reliability and supply of the DRAM controller IC in our original design, but we found that we could do the same job more cheaply than the original anyway!

DISTORTION METER


A project here for audio designers and the ilk, here is a relatively simple distortion meter from John Linsley Hood. Using a simple Wein network with a soupcon of feedback to increase the notching, this design works by filtering out the original signal and leaving the distortion behind. The unit also includes a wide-range audio millivoltmeter.

PLUS — SPECIAL SUPPLEMENT: EIGHT PAGES OF TECH TIPS!

Here's our answer to all those readers who have been contacting us to find out what's happened to the Tech Tip they sent in five years ago. Seriously, we will be presenting eight pages of readers' up-to-the-moment ideas, in an extra eight pages of the magazine. All the more reason for buying the one and only ETI!

**ALL THIS AND MORE IN THE NEXT ISSUE,
ON SALE NOVEMBER 9th.
BE NICE TO YOUR NEWSAGENT AND HE'LL
KEEP YOUR COPY FOR YOU.**

TEMPERATURE CONTROLLER

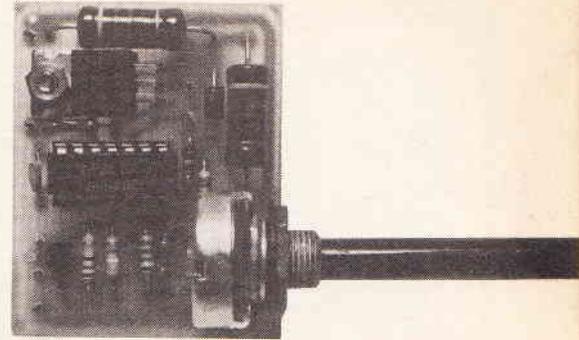


The ever popular Phil Walker no longer has any problems keeping his fans under control — not now that he's built himself an ETI Secon.

This project is intended to be a simple but effective temperature controller. It brings together two readily available devices to make a unit which can act either in a linear mode or as an on/off switching controller. A single small PCB accommodates the complete circuit including a temperature-setting potentiometer, the temperature sensor and and, for applications where only small amounts of heat are required, two large resistors which act as heating elements. It is also possible to mount the sensor away from the PCB and to use the output to drive a fan, an external heating element or any other device which draws a current of a few amps or less from a 10-30V supply.

The Circuit

The temperature sensing element in this project is the LM334Z current source IC. This is programmed by means of a resistor to pass a current of about 1 mA. Due to the nature of the device the current is not greatly affected by the voltage across it but is affected by the temperature. In fact the current increases linearly as the temperature rises and this is used to generate a voltage proportional to the absolute temperature. In order to make use of this effect we have employed a well-known voltage regulator IC, the 723. This gives us several functions in one device which would otherwise have to be provided separately. First it contains a temperature stable voltage reference which is used to supply the temperature sensor and the reference adjusting potentiometer. Second it contains an operational amplifier with a moderately high gain and lastly it has an output transistor capable of passing up to 150 mA.

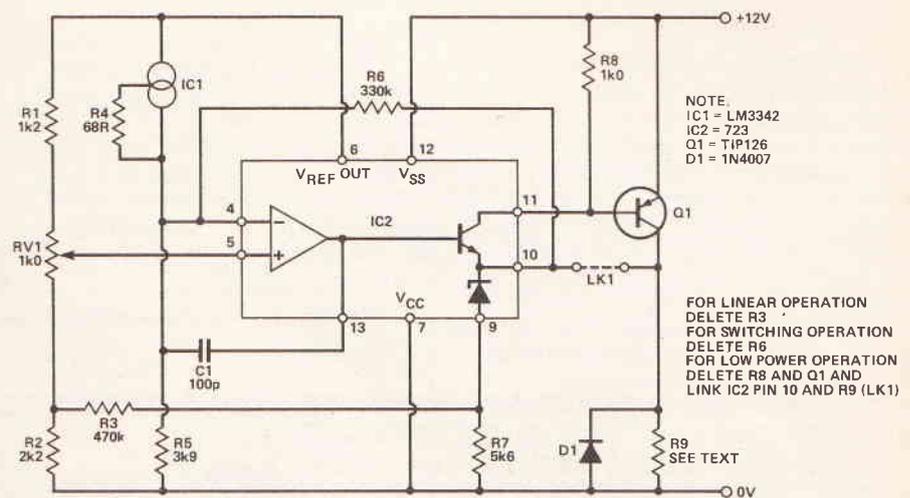

HOW IT WORKS

IC1 is an LM334Z adjustable current source. It has a voltage sensitivity of about 0.02%/volt and a temperature coefficient of about 0.33%/°C. The effects of voltage sensitivity are largely eliminated by using a regulated reference to feed it and the temperature setting potentiometer. This reference voltage is obtained from the 723 voltage regulator IC.

The LM334Z is set to pass about 1mA through R5 which thus develops a voltage of about 3.9V with respect to 0V. This is applied to the inverting input of the op-amp inside the 723, IC2. Connected to the reference supply from IC2 pin 6 there is a potential divider network consisting of R1, R2 and RV1. The values in this network are chosen such that the bottom end of RV1 is at about 3.0V while the top end is at 4.5V. These are equivalent to a temperature range of about $\pm 50^\circ\text{C}$. With suitable changes to R1 and R2 this can be modified at will. The output from RV1 slider is applied to the non-inverting input of the op-amp where it is compared with the output of the sensor circuit. If the temperature of the sensor is too high the voltage at the inverting input of the op-amp will be higher than that set by RV1 and the output of the op-amp will go low tending to turn off the output transistor. This in its turn will turn off Q1 and reduce the power in the load (R9).

To make the regulating effect operate over a defined range, R6 feeds back some of the output voltage into the sensor circuit to give an amplifier gain of about


80. The result is that the output at pin 10 of IC2 should change at a rate of about 1V/°C. This will give a regulating range of 6°C when using a 12V supply. (A 1k resistor across the Link A may be needed.) For use as an on/off switching controller R6 should be used instead. A value of 470k should give $\pm 1^\circ\text{C}$ switching window.

The output from the op-amp in the 723 is connected directly to a power transistor capable of handling up to 150mA. For some applications this may be enough and R8 and link A can be shorted. For higher power applications Q1 is used to boost the power handling of the circuit. This device could be as power transistor such as TIP32 with R8 470R and R7 1k5 or, as we have specified, a TIP126 power darlington. These can handle currents up to 5A, but it is not a good idea to run them too close to this limit because of the effects of switch-on surges and the like. It should also be borne in mind that no heatsinking has been provided on the PCB and this will further limit the maximum safe current the device can handle.

R9 is the actual heating element if mounted on the PCB (two positions for this are provided — either or both can be used) or the load can be remote. If the load is not resistive, D1 should be fitted to absorb switching transients. If the load is remote it may be desirable to mount the sensor near it and pads on the PCB are provided for this. If long leads are used R4 should be mounted close to IC1 and not on the PCB.

PROJECT: Temp Controller

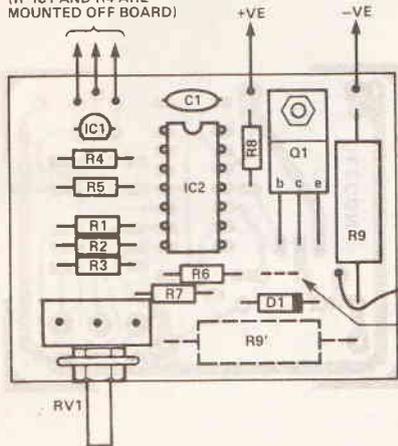REMOTE CONNECTIONS
(IF IC1 AND R4 ARE
MOUNTED OFF BOARD)



INSERT EITHER R3
(FOR SWITCHING OPERATION)
OR R6 (FOR LINEAR OPERATION)
DO NOT USE BOTH

OUTPUT
(IF R9 NOT USED)

LK1—DO NOT INSERT LINK
IF R8 AND Q1 ARE USED

PARTS LIST

RESISTORS (1/4 W 5% unless otherwise stated)

R1	1k2
R2	2k2
R3	470k (see text)
R4	68R
R5	3k9
R6	330k (see text)
R7	5k6
R8	1k (see text)
R9	see text
RV1	1k0 linear potentiometer

CAPACITOR

C1 100p

SEMICONDUCTORS

IC1 LM334Z

IC2 723

Q1 TIP126 (see text)

D1 IN4007

MISCELLANEOUS

PCB; short length of 16 SWG solid wire;
14-pin DIL socket; nut and bolt to secure Q1.

The circuit is configured such that increasing temperature tends to reduce the power in the load. To use this in a linear mode feedback can be provided from the output to the inverting input to the op-amp section. The resistor value chosen for this gives about 1 volt per degree Centigrade. For switching mode operation the necessary feedback is provided to the non-inverting input of the op-amp which gives a sharp on-off action. The rate of switching will depend on external factors such as thermal inertia and sensor position, etc.

For low power operation it may be possible to omit the output transistor from the circuit and use the 723 output device only. This is made possible by shorting IC2 pin 10 to R9 using LK1 and replacing R8 with another link.

For wide range operation you may find it necessary to put a resistor of 1k or so across link LK1. The diode D1 is only necessary when inductive loads such as relays or fans are used instead of resistors.

Construction

This is quite simple so long as the components are correctly placed. RV1 should be a PCB mounting type and can be secured with a loop of 16 SWG wire soldered into the holes provided. The remaining threaded boss on the potentiometer spindle can be used to secure the whole unit to a panel with an extra nut.


If the unit is to be used for low power then R9 can be mounted on the PCB. Note that R3 or R6 may be fitted but not both. Also, link A may be fitted if Q1 is not used and a 1k resistor used for linear operation or an open circuit for switch mode operation. R8 should be linked across if Q1 is omitted.

If IC1 is to be mounted remotely then R4 should be mounted with it and two wires only connected back to the PCB.

ETI

BUYLINES

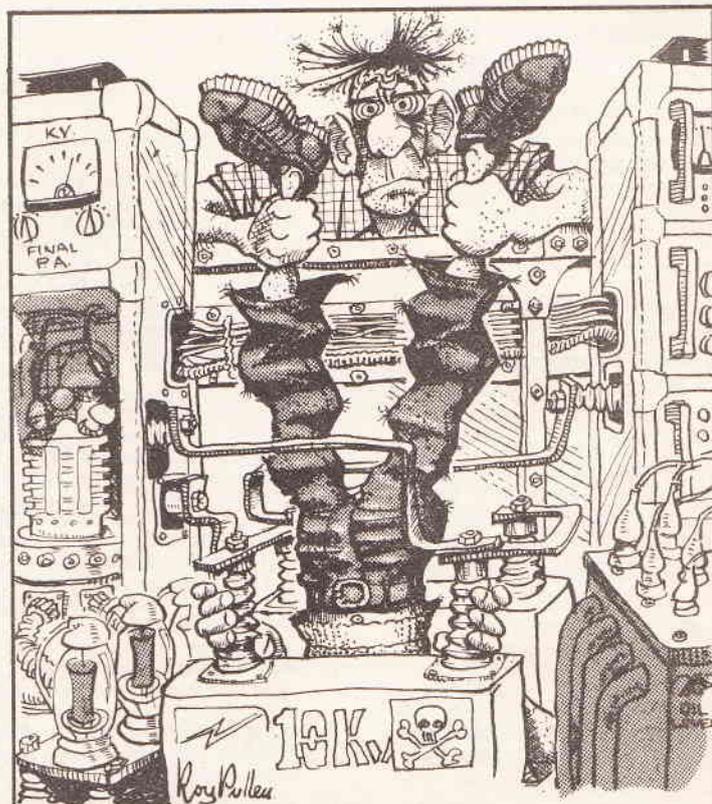Nothing here to cause any problems — all the devices here are quite widely available. The PCB is, as ever, available through our PCB service.



STEADY - OK - I CAN READ IT NOW,
IT SAYS: "DANGER LETHAL VOLTAGES,
EVEN WHEN POWER IS DISCONNECTED."

NEW from



Peerless

This exciting new range of designs covers all domestic HiFi applications. There are 20, 30 and 40 litre designs using the famous Peerless Polypropylene bass units (newly released to the DIY market), a 7 litre mini speaker and two designs specifically intended for use with digital systems. The Wilmslow Audio Total kits include all cabinet components, accurately machined from MDF board, drive units, crossover kits, wadding, grille fabric, terminals, nuts, bolts, etc. Full details are in the Peerless Manual for Loudspeaker Constructors which is available F.O.C. (send 12" x 9" SAE)



Total kit Prices per pair inc. VAT

Design 50/2R (7 litre, reflex)	£92.50 plus carr./ins	£6.00
Design 65/2R (20 litre, reflex, Polypr.)	£111.00 plus carr./ins	£6.50
Design 825/2R (30 litre, reflex, Polypr.)	£115.00 plus carr./ins	£10.00
Design 100/3 (40 litre, IB, Polypr.)	£172.00 plus carr./ins	£10.00
Design CD825/2R (25 litre, reflex) for digital	£128.50 plus carr./ins	£10.00
Design CD825/3R (30 litre, reflex) for digital	£185.00 plus carr./ins	£10.00

Basic kits (drive units and crossovers only) per pair

Design 50/2R	£67.50 plus carr./ins	£4.50
Design 65/2R	£77.00 plus carr./ins	£4.50
Design 825/2R	£77.00 plus carr./ins	£4.50
Design 100/3	£128.50 plus carr./ins	£5.50
Design CD825/2R	£88.95 plus carr./ins	£5.00
Design CD825/3R	£144.00 plus carr./ins	£5.50

Active versions of the three 825 designs are available

VERY COMPETITIVE PRICES on speaker drive units:
AUDAX • CELESTION
DECCA • ELAC • FANE
GAUSS • GOODMAN'S
KEF • MCKENZIE
PEERLESS • SCANSPEAK
SEAS • TANNOY • VOLT
WHARFEDALE etc.
COMPREHENSIVE CATALOGUE!
Pages & pages of drive units, kits, crossovers, designs for PA cabinets crossover calculations etc.
£1.50 Post Free (Export £3.50 or \$6)


Visit our new **HIFI STUDIO** for a great deal on **Ariston, A&R, B&W, Dual, Kef, M-Short, Mission, Monitor, Nad, Rotel, Trio, Walker etc.**



Constructor Series Speakers

IT'S SO EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit. No electronic or woodworking knowledge necessary and the end result is a proven top quality design that you'll be proud of. Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc. The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl. Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.

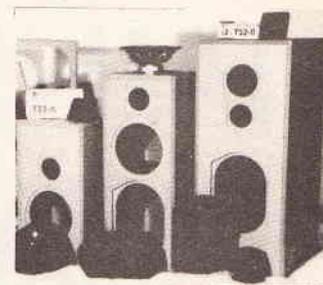

Prices per pair

CS1 (as 101)	£111 pr. inc. VAT, plus carr./ins	£6.00
CS1A (simplified LS3/5A)	£108 pr. inc. VAT, plus carr./ins	£6.00
CS3 (as 103.2)	£131 pr. inc. VAT, plus carr./ins	£10.00
CS5 (as Carlton II)	£196 pr. inc. VAT, plus carr./ins	£15.00
CS7 (as Cantata I)	£263 pr. inc. VAT, plus carr./ins	£18.00


Kef Constructor Series basic kits (drive units and crossovers only)

CS1	£88.50 carr./ins	£5.00
CS1A	£84.00 carr./ins	£5.00
CS3	£100.50 carr./ins	£5.00
CS5	£139.95 carr./ins	£5.50
CS7	£193.05 carr./ins	£5.50



Dept ET1
35-39 Church St, Wilmslow, Cheshire SK9 1AS
Tel: 0625 529599

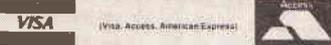Wilmslow Audio Catalogue post free **£1.50**
 Celestion Cabinet Handbook post free **£1.00**
 Fane loudspeaker enclosure design post free **£2.95**
 Peerless Manual for Loudspeaker Constructors FOC
ALL the above £5 post free



CRIMSON ELECTRIK amplifier kits, modules, active crossovers. **YAMAHA Professional and Producer series products.** 3rd Generation mixers, amplifiers. **McGregor PA amplifiers, combos etc.**
All at very competitive prices!

Lightning service on telephoned credit card orders
EFFICIENT EXPORT SERVICE

10 SOLARTRON CD1740 Dual Trace 50MHz Dual Trace Scope	£1100
13 TERA4 Dual Trace 50MHz Dual Trace Scope	£950
15 CROSCOP COUPLER 20MHz	£100
17 SE LABS SIM 11 Dual Trace 20MHz	£100
20 SOLARTRON CD1740 Dual Trace 50MHz	£1100
23 TERA4 Dual Trace 50MHz Dual Trace Scope	£950
27 TERA4 Dual Trace 50MHz Dual Trace Scope	£950
28 MARCONI UNIVERSAL BRIDGE TESTER 100Hz-10MHz	£110
29 MARCONI UNIVERSAL BRIDGE TESTER 100Hz-10MHz	£110
30 MARCONI UNIVERSAL BRIDGE TESTER 100Hz-10MHz	£110
100 MARCONI UNIVERSAL BRIDGE TESTER 100Hz-10MHz	£110

FREE CAREER BOOKLET
Train for success, for a better job, better pay

Enjoy all the advantages of an **ICS Diploma Course**, training you ready for a new, higher paid, more exciting career. Learn in your own home, in your own time, at your own pace, through **ICS home study**, used by over 8 million already! Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an **ICS Diploma Course** there for you to use. Send for your **FREE CAREER BOOKLET** today—at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY


<input type="checkbox"/> ELECTRONICS ENGINEERING	<input type="checkbox"/> TV & AUDIO SERVICING
<input type="checkbox"/> ELECTRICAL ENGINEERING	<input type="checkbox"/> RUNNING YOUR OWN BUSINESS

Name _____
 Address _____

ICS Dept I BSB4
 ICS School of Electronics
 180 Stevens Road
 London SW8 4UJ
 01 622 9911
 (all hours)

MAINS FAILURE ALARM

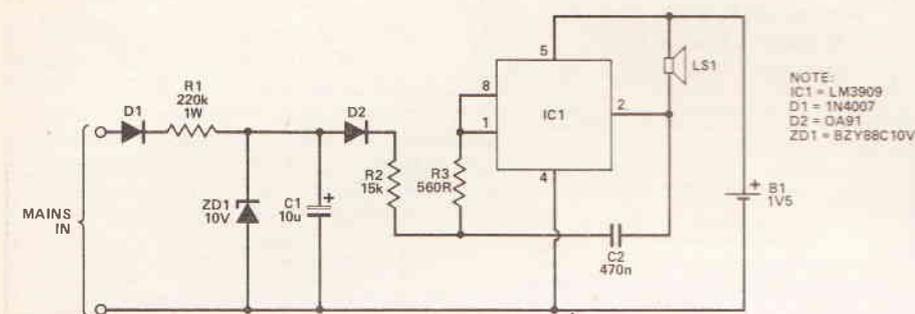Help! Help! I'm powerless! There are some items around the house or lab that you'd like to say that to you when necessary. The ETI Vagonoff gives them a voice. Design and development by Phil Walker.



This very simple project will continuously monitor the mains supply to any pieces of equipment and let you know if someone pulls the plug or the power goes off for any other reason.

The circuit is very simple and consists mainly of a LM3909 connected up as an oscillator and driving a small loudspeaker. In normal operation it is prevented from oscillating by a small current into C2 from the rectified mains. If this current fails due to the absence of mains input the LM3909 will oscillate and cause a sound to be emitted from the loudspeaker. The power to drive the speaker is obtained from the 1½ volt dry cell which under the normally very low




HOW IT WORKS

The mains supply to be monitored is rectified by D1 and regulated by R1 and ZD1 such that about 10V appears on C1. This produces a current via D2 and R2 into C2 and the input to IC1 such that the input of IC1 is held above its upper switching threshold. Under these circumstances, the output of IC1 is also high so no current flows through LS1.

If the mains input fails, the charge on C1 will leak away until the voltage at the input to IC1 reaches its lower threshold. IC1's output will then switch and go low drawing current through LS1. Due to the internal circuit operation of IC1 and the characteristics of LS1 and C2, the output of IC1 will switch back to the high state after a short time and start continuous oscillation which is heard as a tone from the loudspeaker.

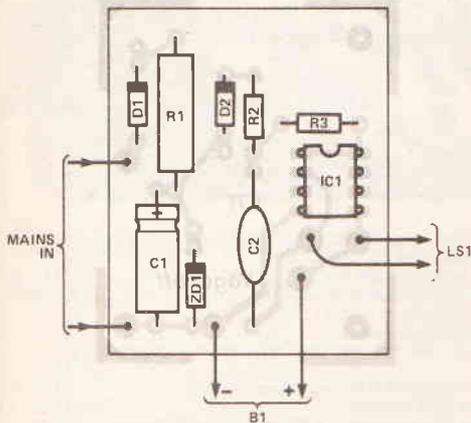Since the non-operational state of the project draws very little current from the cell it should last a long time before needing replacement



power drain when the circuit is not oscillating will last a very long time.

Possible applications for this device may include monitoring mains supplies to darkroom or other laboratory equipment, tape recorders and record players where prolonged stationary contact would cause flats to develop on pinch rollers, etc, and even as an anti-theft device (although the noise it makes is not very loud).

PARTS LIST

RESISTORS	
R1	220k 1W
R2	15k 0.25W
R3	560R 0.25W
CAPACITORS	
C1	10 μ F 25V electrolytic
C2	470nF 100V polyester
SEMICONDUCTORS	
IC1	LM3909
D1	1N4007
D2	0A91
ZD1	BZY88C10V
MISCELLANEOUS	
LS1	2.5 in. 64R loudspeaker
B1	1.5 V dry cell prefer alkaline type
PCB: see buylines; box: plastic box 4½ x 3 x 1½ inches approx; wire; grommets or glands; (nylon) nuts and bolts; 8 pin DIL socket if required.	

nylon bolts to secure the circuit board, loudspeaker and battery. Wiring to the outside world should be made with well insulated mains cable through a grommet or cable gland and the cable should be well secured inside the case.

The construction of the PCB should pose no problems so long as the IC and polarised diodes and capacitor are correctly positioned. The dry cell can be permanently wired in place as it should last a very long time. Use an adhesive cable clip to hold it in place.


The loudspeaker could well be glued to the inside of the box with a few **small** holes to let the sound out. We recommend that these holes be covered by some additional insulation if the finished unit is accessible.

Construction

The main thing to bear in mind when making this product is that all the circuitry is at mains potential and this must not be accessible from outside of the case. To this end we recommend that you use

BUYLINES

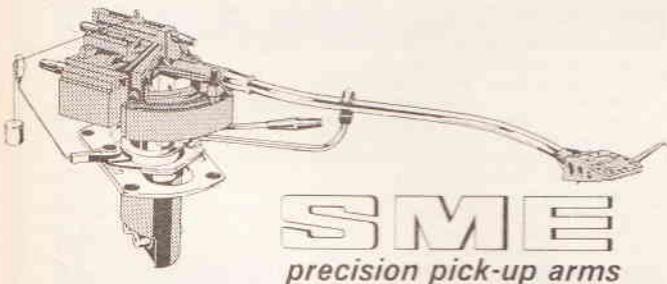
Nothing that we can see in this project should cause any problems here. The PCB is available from your usual friendly source — our own PCB service.



Please call or write:
SME Limited, Steyning, Sussex, BN4 3GY
Telephone: 0903 814321 Telex: 877808 G

CENTURION[®] ALARMS

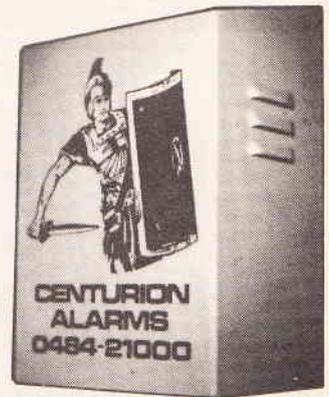Manufacturers of Professional Alarm Equipment, for **DIY** & the **TRADE**. Send now for our New 16-page Brochure, Full of **Information** & the **Lowest prices**.



Just Look !

Ord. No.	Description	Price
210	Flush Contact	0.65
240	Pressure Mat Large	1.50
140	Single Zone Panel	39.50
320	Racal Passive 772	29.90
355	Eclipse Ext/PIR.	74.00
370	Two-Tone Siren 12v	7.00
390	Quality Bell Box	6.95
545	Rech. Battery 12v	6.95
725	Questions & Ans Bk	3.50



Tel: (0484)
21000
or 35527 24 hr.

and **lots more** in our **FREE** list, all prices plus 15% VAT, P&P £2

CENTURION Dept E
93 Wakefield Road
Huddersfield
HD5 9AB
W. Yorks.

© "CENTURION" is a Registered Trademark of Centurion Alarms

VIDEO TERMINAL BOARD

★ 80 characters X 24 lines ★

Requires ASCII encoded keyboard and monitors to make fully configurable intelligent terminal. Uses 6802 micro and 6845 controller. Program and character generator (7 X 9 matrix with descenders) in two 2716 EPROMs. Full scrolling at 9600 baud with 8 switch selectable rates. RS232 interface.

Bare boards with 2 EPROMs and program listing — £48 plus VAT. Assembled and tested — £118
Send for details or CWO to:



A M Electronics
Wood Farm, Leiston, Suffolk IP16 4HT
Tel: 0728 831131

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 1, Golden Square, London W1R 3AB. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS GUIDE

<input type="checkbox"/> Beginner's Guide to Basic Programming Stephenson	£5.35
<input type="checkbox"/> Beginner's Guide to Digital Electronics	£5.35
<input type="checkbox"/> Beginner's Guide to Electronics	£5.35
<input type="checkbox"/> Beginner's Guide to Integrated Circuits	£5.35
<input type="checkbox"/> Beginner's Guide to Computers	£5.35
<input type="checkbox"/> Beginner's Guide to Microprocessors	£5.35

COOKBOOKS

<input type="checkbox"/> Master IC Cookbook Hallmark	£10.15
<input type="checkbox"/> Microprocessor Cookbook M. Hordeski	£7.70
<input type="checkbox"/> IC Op Amp Cookbook Jung	£14.25
<input type="checkbox"/> PLL Synthesiser Cookbook H. Kinley	£7.70
<input type="checkbox"/> Active Filter Cookbook Lancaster	£13.40
<input type="checkbox"/> TV Typewriter Cookbook Lancaster	£11.15
<input type="checkbox"/> CMOS Cookbook Lancaster	£11.85
<input type="checkbox"/> TTL Cookbook Lancaster	£10.95
<input type="checkbox"/> Micro Cookbook Vol. 1 Lancaster	£15.30
<input type="checkbox"/> BASIC Cookbook K. Tracton	£6.00
<input type="checkbox"/> MC6809 Cookbook C. Warren	£7.25

ELECTRONICS

<input type="checkbox"/> Principles of Transistor Circuits Amos	£8.50
<input type="checkbox"/> Design of Active Filters with experiments Berlin	£11.30
<input type="checkbox"/> 49 Easy to Build Electronic Projects Brown	£6.00
<input type="checkbox"/> Electronic Devices & Circuit Theory Boylestad	£13.20
<input type="checkbox"/> How to build Electronic Kits Capel	£3.55
<input type="checkbox"/> How to Design and build electronic instrumentation Carr	£9.35
<input type="checkbox"/> Introduction to Microcomputers Daglecs	£7.20
<input type="checkbox"/> Electronic Components and Systems Dennis	£15.00
<input type="checkbox"/> Principles of Electronic Instrumentation De Sa	£11.40
<input type="checkbox"/> Giant Handbook of Computer Software	£12.95
<input type="checkbox"/> Giant Handbook of Electronic Circuits	£17.35
<input type="checkbox"/> Giant Handbook of Electronic Projects	£11.75
<input type="checkbox"/> Electronic Logic Circuits Gibson	£5.55
<input type="checkbox"/> Analysis and Design of Analogue Integrated Circuits Gray	£30.25
<input type="checkbox"/> Basic Electronics Grob	£11.30
<input type="checkbox"/> Lasers - The Light Fantastic Hallmark	£7.70
<input type="checkbox"/> Introduction to Digital Electronics & Logic Joynson	£5.25
<input type="checkbox"/> Electronic Testing and Fault Diagnosis Loveday	£7.85
<input type="checkbox"/> Electronic Fault Diagnosis Loveday	£6.25
<input type="checkbox"/> Essential Electronics A-Z Guide Loveday	£7.50
<input type="checkbox"/> Microelectronics Digital & Analogue circuits and systems Millman	£12.70
<input type="checkbox"/> 103 Projects for Electronics Experimenters Minis	£8.30
<input type="checkbox"/> VLSI System Design Muroga	£34.10
<input type="checkbox"/> Power FETs and their application Oxner	£9.40
<input type="checkbox"/> Practical Solid State Circuit Design Olesky	£25.00
<input type="checkbox"/> Master Handbook of IC Circuits Powers	£12.85
<input type="checkbox"/> Electronic Drafting and Design Raskhodoff	£22.15
<input type="checkbox"/> VOM - VTVM Handbook Risse	£8.50
<input type="checkbox"/> Video and Digital Electronic Displays Sherr	£28.85
<input type="checkbox"/> Understanding Electronic Components Sinclair	£7.50
<input type="checkbox"/> Electronic Fault Diagnosis Sinclair	£4.50
<input type="checkbox"/> Physics of Semiconductor Devices Sze	£17.35
<input type="checkbox"/> Digital Circuits and Microprocessors Taub	£32.00
<input type="checkbox"/> Active Filter Handbook	£7.60
<input type="checkbox"/> Designing with TTL Integrated Circuits Texas	£15.20
<input type="checkbox"/> Transistor Circuit Design Texas	£15.20
<input type="checkbox"/> Digital Systems: Principles and Applications Tocci	£12.95
<input type="checkbox"/> Master Handbook of Telephones Traister	£10.00
<input type="checkbox"/> How to build Metal/Treasure Locators Traister	£6.00
<input type="checkbox"/> 99 Fun to Make Electronic Projects Tymony	£8.50
<input type="checkbox"/> 33 Electronic Music Projects you can build Winston	£6.95

COMPUTERS & MICROCOMPUTERS

<input type="checkbox"/> BASIC Computer Games Ahl	£6.35
<input type="checkbox"/> From BASIC to PASCAL Anderson	£9.95
<input type="checkbox"/> Mastering Machine Code on your ZX81 T. Baker	£7.25
<input type="checkbox"/> UNIX - The Book Banaham	£8.75
<input type="checkbox"/> Z80 Microcomputer Handbook Barden	£10.95
<input type="checkbox"/> Microcomputer Maths Barden	£11.90
<input type="checkbox"/> Digital Computer Fundamentals Barter	£9.90
<input type="checkbox"/> Visualc Book. APPLE Edition Bell	£15.55
<input type="checkbox"/> Visualc Book. ATARI Edition Bell	£15.55
<input type="checkbox"/> Introduction to Microprocessors Brunner	£23.00
<input type="checkbox"/> Programming your APPLE II Computer Bryan	£9.25
<input type="checkbox"/> Microprocessor Interfacing Carr	£7.70
<input type="checkbox"/> Microcomputer Interfacing Handbook A/D & D/A Carr	£9.50
<input type="checkbox"/> Musical Applications of Microprocessors Chamberlain	£28.85
<input type="checkbox"/> 30 Computer Programs for the Home Owner in BASIC D. Chance	£9.25
<input type="checkbox"/> Microcomputers Dirkson	£9.30
<input type="checkbox"/> APPLE Personal Computer for Beginners Dunn	£9.50
<input type="checkbox"/> Microcomputers/Microcomputers - An Intro Gioone	£11.80

<input type="checkbox"/> Troubleshooting Microprocessors and Digital Logic Goodman	£9.25
<input type="checkbox"/> Getting Acquainted with your VIC 20 Hartnell	£8.50
<input type="checkbox"/> Getting Acquainted with your ZX81 Hartnell	£5.95
<input type="checkbox"/> Let your BBC Micro Teach you to program Hartnell	£7.90
<input type="checkbox"/> Programming your ZX Spectrum Hartnell	£8.50
<input type="checkbox"/> The ZX Spectrum Explored Hartnell	£6.95
<input type="checkbox"/> How to Design, Build and Program your own working Computer System Haviland	£9.30
<input type="checkbox"/> BASIC Principles and Practice of Microprocessors Heffer	£7.15
<input type="checkbox"/> Hints and Tips for the ZX81 Hewson	£5.25
<input type="checkbox"/> What to do when you get your hand on a Microcomputer Holtzman	£9.95
<input type="checkbox"/> 34 More Tested Ready to Run Game Programs in BASIC Horn	£7.70
<input type="checkbox"/> Microcomputer Builders' Bible Johnson	£12.40
<input type="checkbox"/> Digital Circuits and Microcomputers Johnson	£14.55
<input type="checkbox"/> PASCAL for Students Kemp	£7.20
<input type="checkbox"/> The C - Programming Language Kernighan	£18.20
<input type="checkbox"/> COBOL Jackson	£9.25
<input type="checkbox"/> The ZX81 Companion Maunder	£9.50
<input type="checkbox"/> Guide to Good Programming Practice Meek	£6.40
<input type="checkbox"/> Principles of Interactive Computer Graphics Newman	£13.95
<input type="checkbox"/> Theory and Practice of Microprocessors Nicholas	£11.35
<input type="checkbox"/> Exploring the World of the Personal Computer Nilles	£12.95
<input type="checkbox"/> Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll	£9.80
<input type="checkbox"/> Beginner's Guide to Microprocessors Parr	£5.35
<input type="checkbox"/> Microcomputer Based Design Peatman	£11.30
<input type="checkbox"/> Digital Hardware Design Peatman	£9.80
<input type="checkbox"/> BBC Micro Revealed Ruston	£9.45
<input type="checkbox"/> Handbook of Advanced Robotics Safford	£14.45
<input type="checkbox"/> 1001 Things to do with your own personal computer Sawusch	£8.50
<input type="checkbox"/> Easy Programming for the ZX Spectrum Stewart	£7.15
<input type="checkbox"/> Microprocessor Applications Handbook Stout	£34.40
<input type="checkbox"/> Handbook of Microprocessor Design and Applications Stout	£37.60
<input type="checkbox"/> Programming the PET/CBM West	£17.80
<input type="checkbox"/> An Introduction to Microcomputer Technology Williamson	£8.20
<input type="checkbox"/> Computer Peripherals that you can build Wolfe	£12.40
<input type="checkbox"/> Microprocessors and Microcomputers for Engineering Students and Technicians Wooland	£7.10

REFERENCE BOOKS

<input type="checkbox"/> Electronic Engineers' Handbook Fink	£56.45
<input type="checkbox"/> Electronic Designers' Handbook Giacoletto	£59.55
<input type="checkbox"/> Illustrated Dictionary of Microcomputer Technology Hordeski	£8.45
<input type="checkbox"/> Handbook for Electronic Engineering Technicians Kauffman	£27.50
<input type="checkbox"/> Handbook of Electronic Calculators Kauffman	£35.00
<input type="checkbox"/> Modern Electronic Circuit Reference Manual Marcus	£44.00
<input type="checkbox"/> International Transistor Selector Towers	£10.70
<input type="checkbox"/> International Microprocessor Selector Towers	£16.00
<input type="checkbox"/> International Digital IC Selector Towers	£10.95
<input type="checkbox"/> International Op Amp Linear IC Selector Towers	£8.50
<input type="checkbox"/> Illustrated Dictionary of Electronics Turner	£12.95

VIDEO

<input type="checkbox"/> Servicing Home Video Cassette Recorders Hobbs	£12.95
<input type="checkbox"/> Complete Handbook of Videocassette Recorders Kybatt	£9.25
<input type="checkbox"/> Theory and Servicing of Videocassette Recorders McGinty	£12.95
<input type="checkbox"/> Beginner's Guide to Video Matthewson	£5.35
<input type="checkbox"/> Video Recording: Theory and Practice Robinson	£14.40
<input type="checkbox"/> Video Handbook Van Wezel	£21.90
<input type="checkbox"/> Video Techniques White	£12.95

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed.....

Name.....

Address.....

ETI KNITE-LITE

A figment of flippant foollery for functional fantasy fans, fully fabricated by Phil Walker.

For some reason there seems to be a requirement for computer-controlled cars and alien robots to be endowed with roving red eyes. Well, this offering from the cybernetic cavern of the ETI workshop will enable all and sundry to share in the excitement. Now you too can upgrade your latest creation with the roving red-eye look from the ETI stable.


The Circuit

In principle this is very simple. The display consists of ten red LEDs driven by an LM3914 linear bar-graph IC. This IC also contains a voltage reference source and all the necessary comparators to control the display.

In order to produce the smooth to-and-fro sweep two sections of a quad operational amplifier have been configured as a triangle wave generator. The output from this is applied to the lower end of the voltage reference and comparator chain while the other end of the comparator chain is connected to the upper end of the voltage reference.

This means that the reference voltage is sitting on top of the triangle wave generator and is being swept up and down past a reference applied to what is normally the signal input pin. This produces the basic back and forth sweep on the display.

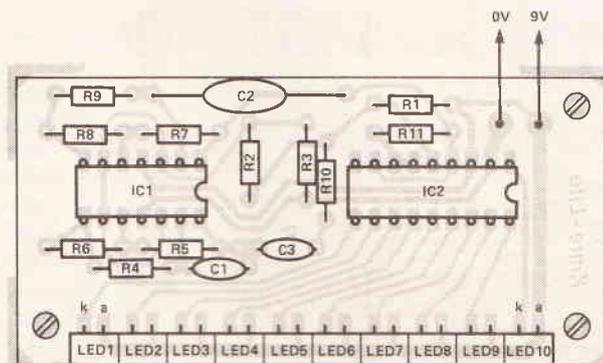As it stands so far the display would be jerky so some method



PARTS LIST

RESISTORS

R1	82k
R2,4,10	15k
R3,6,8	100k
R5,11	1k Ω
R7	18k
R9	3M Ω

CAPACITORS (ceramic or polycarbonate)

C1	1n Ω
C2	1 $\mu\Omega$
C3	68n

SEMICONDUCTORS


IC1	TL084
IC2	LM3914
LED1-10	Rectangular red LED

MISCELLANEOUS

PCB (see buylines); battery: PP3 size 9V; battery clips; SPST switch if required; box: optional 4½ x 3 x 1½ or larger if to contain battery as well.

BUYLINES

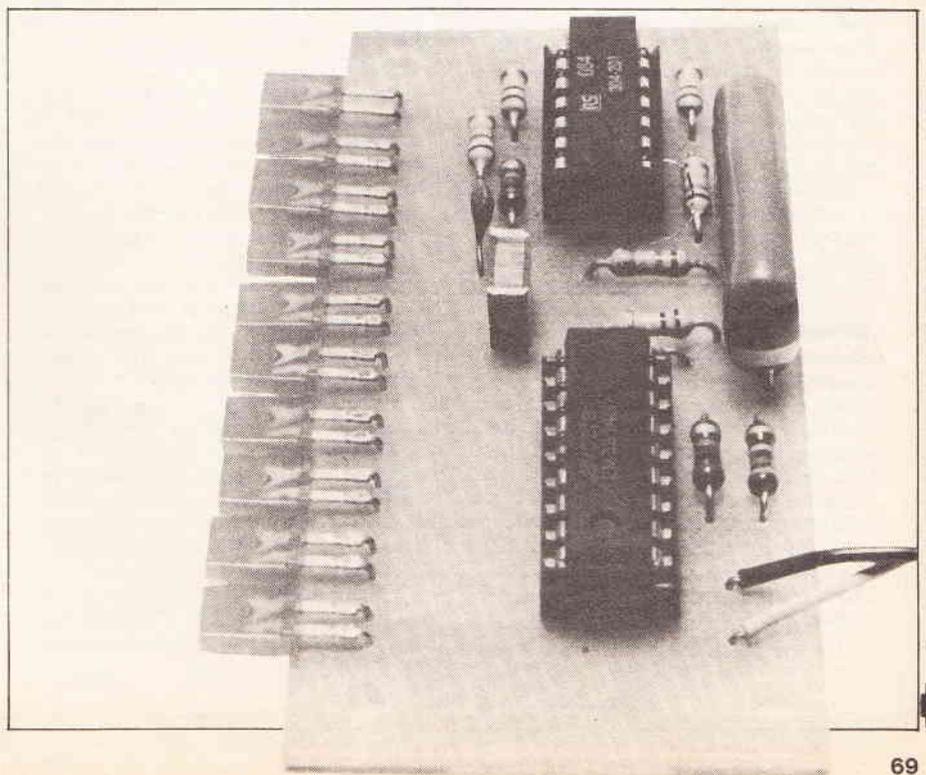Nothing here to cause any problems; the square LEDs used in the prototype were obtained from Rapid Electronics, but lots of other suppliers sell them. The two ICs are quite widely available, too, and the PCB is available from our PCB service.



PROJECT: Knite-Lite

of smoothing out the transition between adjacent LEDs is necessary. This is done by connecting up the remaining two sections of the quad op-amp to form another triangle wave generator operating at a much higher frequency. The output from this is mixed with the reference voltage

to smear the display over two or three LEDs at a time. This makes the display much smoother and more realistic.

Construction


The construction of this project is quite simple as all the com-

ponents are mounted on the PCB. Make sure, however, that you get both the ICs the right way round and do not confuse anode and cathode connections on the LEDs. If you want to mount them off the board it should make no difference to the circuit operation.

The type of box used for the project is entirely up to you, but we suggest one large enough to hold a PP6 or PP9 size battery to power the circuit for a day or so (continuous operation). Although the circuit does not draw a large current (about 20mA) it is a good idea to fit a switch in the battery lead.

The circuit should operate with supply voltages from 6 volts to 20 volts but some adjustments will have to be made to several resistor values if you want to vary the supply voltage from the intended 9V. This is caused by the fact that the amplitude and frequency of the two oscillator circuits is dependent on the supply voltage. Frequency effects can be countered by changing the capacitor values but amplitude changes especially in the sweep oscillator are much more difficult to remove.

ETI

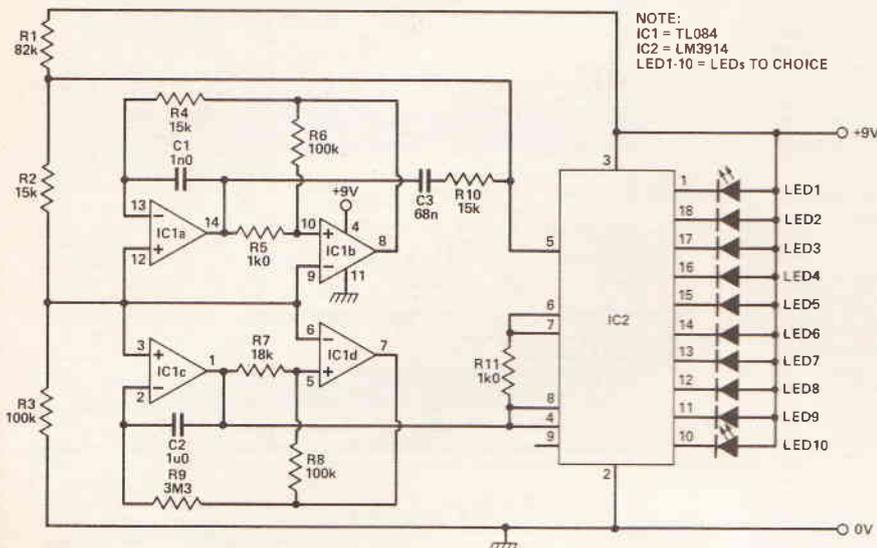

HOW IT WORKS

The principles of operation governing this project are quite straightforward but unfortunately the practice is a little more obscure.

The main work in the project is done by the LM3914 IC. This is a bar-graph display driver which contains a voltage reference, graded comparator string and current-limited output drivers. There is also some internal logic which enables the user to have either a dot or bar mode display. In this application we use only the dot mode so pin 9 which selects the mode is left open circuit.

The on-chip voltage reference source is not referenced to 0V and can be floated within the supply rail boundaries (with some restrictions). We must note however that the current drawn from the reference supply also determines the LED driver output current. In this circuit R11 sets the LED current to about 12 or 13mA.

The circuit is configured such that the 1.25V reference of the LM3914 sits on top of the sweep ramp generated by IC1c and IC1d. The resistor ratios and capacitor value used in this circuit are selected to provide a triangular wave sweep of about 2 seconds with a peak-to-peak value of about 1.2 volts. The amplitude is set by R7/R8 while the frequency is determined by R9 and C2.

The configuration of IC1c and IC1d

is that of the integrator and Schmitt trigger. IC1c and C2 form the integrator. If the output of IC1d is high then current will flow through R9 into C2 (the input current to IC1c can be ignored). As this happens, the input side of C2 is kept at the reference voltage supplied by the R1,2,3 divider chain by the action of IC1c. This causes the output of IC1c to go linearly in a negative direction.

At some stage the output voltage from IC1c via R7 will pull the input of IC1d slightly negative overcoming the effect of the positive output of IC1d via R8. This will cause the output of IC1d to go to the negative rail very rapidly. Now current will be drawn out of C2 via R9 and the output of IC1c will ramp in the positive direction. This will continue until the output of IC1c can pull the input of IC1d positive and switch its output positive also. The whole cycle will repeat indefinitely.

As the output of IC1c ramps up and down the lower end of the voltage comparator chain in the LM3914 to which it is connected is also driven. In addition the upper end of the chain also goes up and down but 1.25 volts more positive. This is set by the floating voltage reference.

As the whole comparator chain is ramped up and down, it passes the fixed voltage from R1,2,3 divider chain.

This causes the dot display to sweep to and fro along the LEDs. This is equivalent to holding the bottom end of the comparator chain fixed and sweeping the input terminal instead, but it overcomes the need for a low impedance R1,2,3 divider chain. The signal input needs less than 50nA bias current while the comparator input impedance is only about 10k and would take 120µA; some other means of setting the LED current would be necessary.

The voltage actually present at pin 5 of the LM3914 is about 0.6 volts more than the reference to the oscillators. This means that the input seen by the LM3914 is always in the comparator range and gives the correct display.

The display given by the circuitry described so far is not as smooth as it might be as the transition between one LED and the next is quite abrupt. To overcome this another oscillator similar to the first is configured around IC1a and b. This operates in exactly the same way as the other but at a much higher frequency. Its output "wobbles" the reference voltage seen by the LM3914 via R10/C3 such that the dot mode display is "smeared" across two or three LEDs and the transitions are much smoother. There is some interaction between the two oscillators but this is not visually obvious.

SPECTRUM STAGE LIGHTING INTERFACE

Would you like to computerize your scene changes, or light your living room? Richard Neep could have the project for you.

The stage lighting unit, published in January, February, April and May of 1983 is still giving cause for interest, if readers' letters are anything to go by (perhaps it's just that we forgot to tell you the specs of some of the transformers at the time . . .). The design presented here will interface a Sinclair Spectrum home-computer to the unit.

This project replaces the keyboard and memory of the original project and is directly compatible with the autofade units. Using the computer has several advantages over the original control system. The data can be stored on tape instead of relying on battery backed-up RAM, the lighting changes can be more sophisticated; and the whole system can be made more user friendly. This last point is perhaps the most important; data can be entered in plain, ordinary decimal and displayed on the TV monitor rather than in octal on the LED display on the original.

First, we shall look at the hardware, then we shall give some notes on the necessary software; finally, we shall look at other uses.

Ins And Outs

The Spectrum has a very large capacity for control applications, there being potentially 65,535 input or output locations. Some of these are reserved by the machine for the keyboard, tape interface, printer, etc. There are further limitations in that the Spectrum is happier if only one of the lower five address lines goes low at any one time, which, as we've seen before (Spectrum Control Port, p44, ETI October) means that projects are best designed to use output addresses which are one less than multiples of 32.

If these numbers are written out in binary, it can be seen that

the lower five address bits are all high. The next four address bits, A5 to A8, are used to decode the 16 outputs of the interface. Extrapolating, this method can provide up to 2048 such outputs.

The actual circuit of the decoder is quite straightforward. When an OUT command is processed by the Spectrum, the $\overline{\text{IORQ}}$ and $\overline{\text{WR}}$ lines are taken low. The circuit is designed so that when the lowest five address lines go low, the next four address lines (A5 to A8) will be used to point to one of the autofade units. This autofade unit will then latch in the buffered and slightly rearranged data on the Spectrum's data bus.

The re-arrangement of the data was found to be less hassle than writing software to do the re-arranging. The autofade units use bits D0 to D2 to determine the final light-level from the controlled lamp, while bits D3 to D7 are used to determine the fade speed (how quickly the light changes from the old level to the new one). The authors of the original had decided to reverse the significance of the bits, ie D3 is the most significant of the speed bits, whereas D2 is the most significant of the final level bits.

Software Options

The software to accompany this project is largely a matter of personal taste and is best tailored to individual requirements. On the Spectrum, the format of the OUT command is: OUT (address), (value), where the value is a number between 0 and 255, ie a single byte written in decimal.

In the stage lighting unit, the eight bits of the byte are split into two sections; as already mentioned, the top five bits (D7 to D3) are used to control the fade speed, but with D7 as the LSB and D3 the

MSB. However, the connections to these bits are reversed on the interface PCB, making D7 the MSB and D3 the LSB so far as the software is concerned. The lower three bits, D0 to D2, control the final brightness, with D2 the MSB.

The light level and fade speeds would obviously be most conveniently entered into the computer as decimal numbers, and stored in an array. Therefore a routine is needed to combine the two decimal numbers and produce a single number between 0 and 255.

The use of the five bits for the fade speed means that there are a total of 2^5 or 32 different fade speeds, from 0 to 31 decimal. Three bits for the final light level means 2^3 different level settings, from 0 to 7. If required, it would be a simple enough matter to write a routine which allows these to be entered as percentages and then scales the percentages to the nearest equivalent whole number in the range 0 to 31 or 0 to 7, as appropriate.

The next step is to combine the two numbers into one; this can be achieved by multiplying the fade speed by 8 and adding the light level. A worked example would perhaps make this clearer.

Suppose we wish to fade to a light level of 45% at a speed of 85%. First, convert to the scaled 3-bit (level) and 5-bit (speed) components:


speed: $85\% \times 31/100 = 26.35$; truncated to 26; binary 11010

level: $45\% \times 7/100 = 3.15$; truncated to 3; binary 011

Next multiply speed by 8:
speed: $26 \times 8 = 208$; binary 1101000

(Note: it is vital that the truncation is carried out before the multiplication, otherwise the fractional

HOW IT WORKS

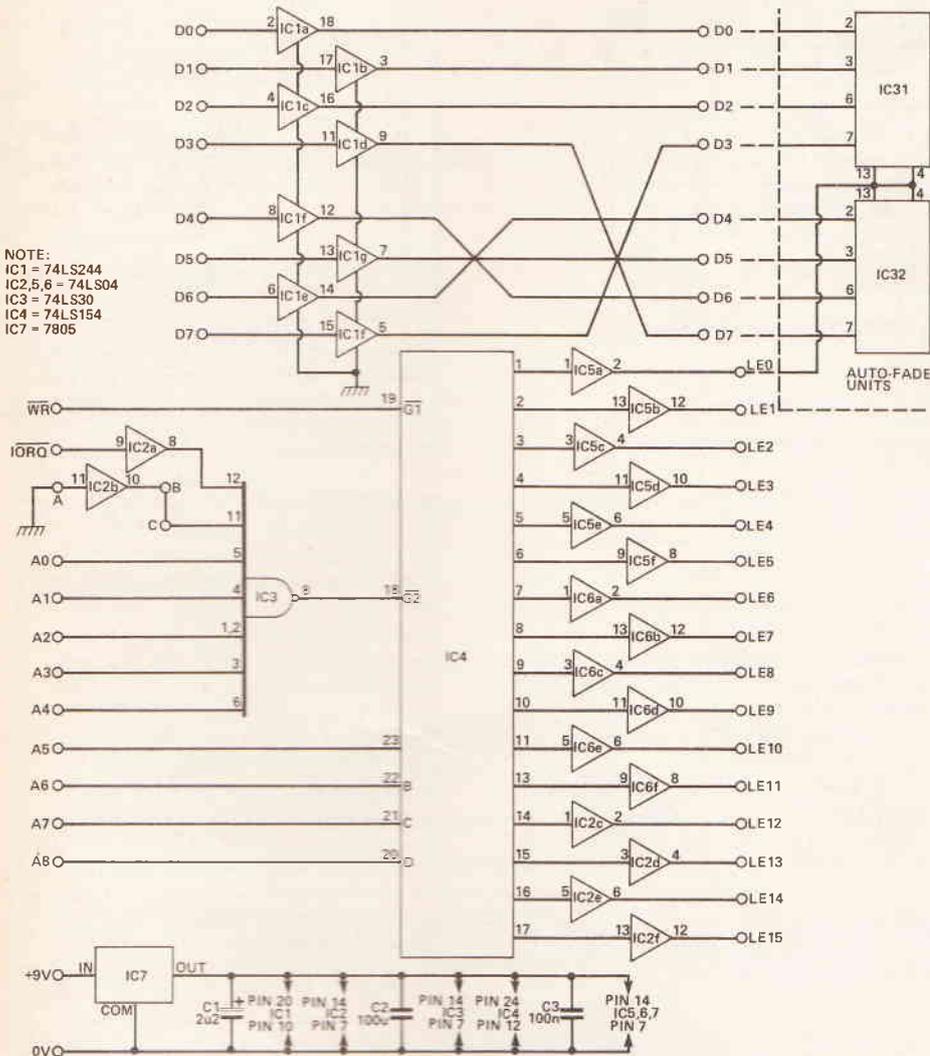

NOTE:
IC1 = 74LS244
IC2,5,6 = 74LS04
IC3 = 74LS30
IC4 = 74LS154
IC7 = 7805

The data lines are buffered by IC1a-h, then crossed to change the order. This is made necessary by the auto-fade units in the original stage-lighting units have the data for the fade speed (D3 to D7) back-to-front, ie D3 is the most significant bit and D7 the least. It is, of course, generally easier to cross a few tracks than it is to write complicated software. The buffered data is then fed to all the autofade units in the main stage lighting unit; D0 to D2 control the final brightness of the controlled light.

IC4 is a 4-to-16 line decoder; when the two gate inputs G1 and G2 are low, the output line pointed to by address inputs A, B, C, D will go low (all outputs are normally high). This is used to select which of the auto-fade units is to latch in the data on the data lines.

Gating of the decoder is performed by IC2a and IC3; the WR line is taken directly to one gate input of IC4, as this is the narrowest of the signals from the Z80. IORQ is inverted then NANDed with the address lines A0 to A4; this is then used to provide the input to the other gate input on IC4.

The power for the circuit is derived from the unregulated 9V supply available on the Spectrum edge connector; a 7805 regulates the 9V to the required 5V.

Fig. 1 Circuit diagram; note that IC30 and 31 are on the fader boards of the main unit.

part of the speed will throw up non-zero digits in the lower three bits after multiplication.

Next, add the two numbers:

speed: 208 binary: 11010000
level: +3 binary: 011

combined: 211 binary: 11010011

This is the final result; looking at the first five bits, 11010, this is 26 decimal or 84% of 31. (31 is the maximum speed). The final three bits are 011 which is 3 decimal or 43% of 7 (7 is the maximum brightness).

The rest of the software depends on the individual preferences of the user and the speed of operation required. Two programs have been written by the author, one of which is fast but gives limited information suitable for rock band or disco applications; the other program is slower for traditional theatre use, and gives

pretty coloured bar-graphs of the light levels for each scene.

Other Uses

Dare we say it, but this port could fairly simply be converted to an output-only control port. All that would be necessary would be to have a number of pairs of four-bit latches, like ICs 31 and 32 in Fig. 1, all wired in parallel to the data lines, but with their individual latch lines going to different latch enable outputs from the interface.

Individual bits on the data bus can be controlled quite easily. The general rule is that if you wish to control the nth bit on the data bus, you multiply 0 or 1 (as appropriate) by 2^n . The numbers generated in this way can just be added together to take the number to be OUTPUT. So, to put 1 on the bit 0, 1 on bit 2 and 1 on bit 3, the sum is

$$1 \times 2^0 + 1 \times 2^1 + 0 \times 2^2 + 1 \times 2^3 \\ = 1 \times 1 + 1 \times 2 + 0 \times 4 + 1 \times 8 \\ = 1 + 2 + 0 + 8 \\ = 11$$

11 in binary is 1011, which is what is required.

Up to sixteen latch pairs can be driven this way, giving a grand total of 128 on/off switches!

Construction

Construction of this project should be quite straightforward. We have designed the PCB so that the Spectrum edge connector can sit directly on the PCB.

We suggest commencing construction of the PCB by inserting and soldering all the IC sockets. It will then be fairly easy to locate all the wire links, of which there are 20, all in the supply lines. After soldering the wire links, insert and solder the capacitors and SK1.

PROJECT: Lighting Interface

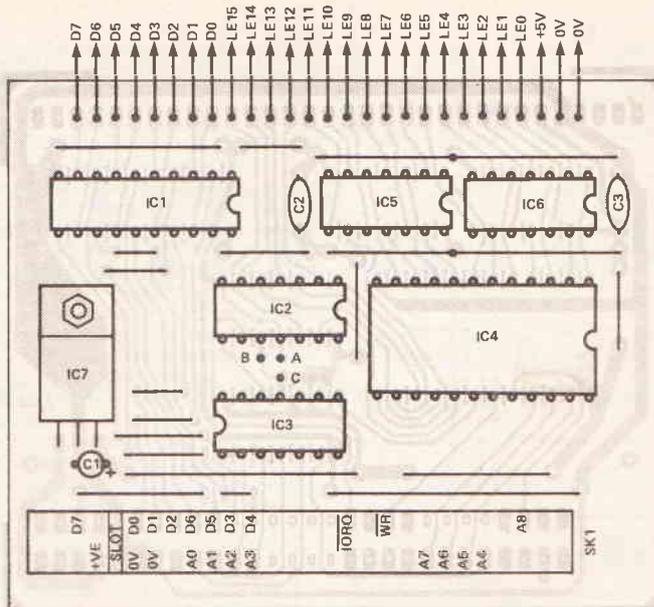


Fig. 2 Overlay diagram of the PCB.

We suggest the next stage as a check against shorts on the PCB. Plug in the board and check that your Spectrum works correctly with the board in position; if it does not, switch off immediately and look for the fault. If it does, insert and solder IC7, and repeat, this time checking for 5V across all the supply line decoupling capaci-

tors and the appropriate IC socket pins.

Finally, insert the remaining ICs and test again; try outputting data in the relevant address range, to check that this does not cause any faults.

When linking up to the stage lighting unit, you can use ribbon cable and just parallel all the data

PARTS LIST

CAPACITORS

C1 2μ2 16V tantalum bead
C2,3 100n ceramic

SEMICONDUCTORS

IC1 74LS244
IC2,5,6 74LS04
IC3 74LS30
IC4 74LS154
IC7 7805

MISCELLANEOUS

PCB; Spectrum edge connector; ribbon cable, wire, solder, etc.

BUYLINES

Nothing here should cause any problems; the PCB will be available through our PCB service.

and latch enable lines, if you used the PCBs as printed with the original articles, as all the latch selection was done with links on the PCB. Alternatively, you could use ribbon cable for just the data bus, and single wires to the relevant latch enables.

Before using the light unit in anger, we would suggest performing OUTs to the latches and checking that the correct data arrives at them (don't forget that the data bus is twisted).

ETI

Price Inc. Post n VAT

4 FARNELL N100 ±5V, ±12V, ±24V, 100W	75.00
1 FARNELL F237/D7/10SC 0-7V, 10A	50.00
1 FARNELL N 300 ±5V, ±12V, 200W	95.00
1 FARNELL G12/10S, 8V-12.6V, 10A	130.00
3 FARNELL 7/10RC (EX EQUIP) +5V, 10A	50.00
2 FARNELL 7/10RC (EX EQUIP) 2 X 12V, 10A	50.00
9 HEWLETT PACKARD G2605M 5V, 100A	60.00
1 GOULD DC 360 5V, 20A	60.00
9 GOULD PMA 51/24 0-30V, 5A	120.00
1 GOULD PMA 47 (MARKED) 0-15V, 3A	50.00
1 GOULD MG5-20B 5V, 20A	75.00
1 ADVANCE PMA 51 0-30V, 5A	100.00
1 ADVANCE MG5/40 5V, 40A (EX EQUIP BUT AS NEW)	100.00
4 ITT MP20BS 0-30V, 20A (WEIGHT 18KG)	65.00
10 ITT 484LFE7560 27.5V, 10A (WEIGHT 15KG)	50.00
QTY 19" RACK KITS DIE PANELS 8 3/4" X 16" WITH GUIDES N STRIP	20.50
QTY LYNX KEYBOARDS 58 KEYS IN 8X BY 10Y ELECTRICAL MATRIX	20.50
18 CENTRONICS PRINTER MOD 792 (SERIAL) SPECIAL PURCHASE OF DISCONTINUED MODEL. SPARES STILL AVAILABLE. NEW N BOXED	195.00
QTY RODIME 5MEG HARD DISK DRIVES SERIES RO200 A LOW COST WAY TO IMPROVE YOUR SYSTEM TECH SPEC AND INTERFACE DATA SUPPLIED	250.00

REMEMBER, ALL PRICES INCLUDE VAT AND CARRIAGE. TRADE ENQUIRES WELCOME QUANTITY ITEMS.

DIONICS


UNIT 50, WHITEMOOR ROAD, KENILWORTH, WARWICKS CV8 2BP

TEL: 0926 59658

TELEX: 312440 PBSSPA G

ELECTRONIC SECURITY

ALM22 ALARM CONTROL UNIT

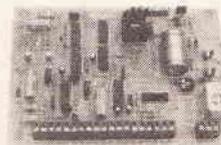

This high performance module is used in AUTROL professional alarm equipment. It will enable you to assemble a sophisticated alarm system at a very low price. It will support all types of detection devices such as magnetic contacts, pressure mats, ultrasonic or passive infra red movement detectors. Screw terminals are fitted for easy installation.

Just look at the advanced features! * Immediate alarm circuit * Separate delayed access circuit * Independently adjustable entry and exit delays * Anti-false alarm circuitry * 24 hour tamper protection * Tamper protected wiring * Walk test facility * On board courtesy buzzer * Bell shutdown timer * Auto reset option * Soak test facility * On board 1 Amp fused power supply * Automatic standby battery charger * Extensive interference filtering. The unit requires 15-0-15 V. transformer, keyswitch, and LEDS (3).

READY BUILT AND TESTED £25.95 + VAT

SBM10 SELF ACTIVATING BELL MODULE



Used in conjunction with the ALM22, this module goes inside the external bell unit and monitors its feed wiring. Any tampering with the unit or its wiring will cause the bells to sound. READY BUILT AND TESTED £5.95 + VAT

KS2. 2 position keyswitch for use with ALM22 £3.38 + VAT

KS4. 4 position keyswitch for use with ALM22. Allows upstairs to be switched off at night. £5.70 + VAT

MT1. 15-0-15 1 A. transformer for use with ALM22. £3.45 + VAT

WB. External bell box, red or white plastic coated. £8.00 + VAT

CH1. Control unit housing, 18 SWG hinged front door, size: 12"x9"x3" undrilled. £8.00 + VAT

B3. Rechargeable standby battery 12 V. 1.9 AH. £9.45 + VAT

COMPREHENSIVE LITERATURE IS AVAILABLE ON ALL ITEMS

We supply a complete range of accessories and equipment from magnetic switches to complete ready built systems. Send for full information. Add 70p carriage to all orders. Add 15% VAT to order total. (inc. carriage). Please allow 14 days for delivery.

AUTROL LTD (Dept C)

Ten Acres, Foundry Lane, Loosley Row, Princes Risborough, Bucks. HP17 0NY
Tel. Factory: 084 44 7805 Literature: 0494 33171 (Mailing Agency!)

Cortex

HARDWARE
SOFTWARE

MDEX disc O/S + BASIC £95
MDEX Professional Dev. Sys. £275
CORTEX POWER-BASIC disc extensions £45

MDEX Languages

ASM FORTH PASCAL SPL QBASIC META
Software to make the CORTEX go!

Disc Drives

80 track double-sided double-density £190
40 track single-sided double-density £120

E-BUS Floppy/Winchester Controller

E-BUS 64/128 K/bytes DRAM card

E-BUS 9995 Processor card

80*24 Character video card

CORTEX tape


Space Bugs, Pontoon, Small Breakout, Micropede,
Pengo each £6

User Group!!! 'Brainstem' out NOW.

Please add VAT to all prices.



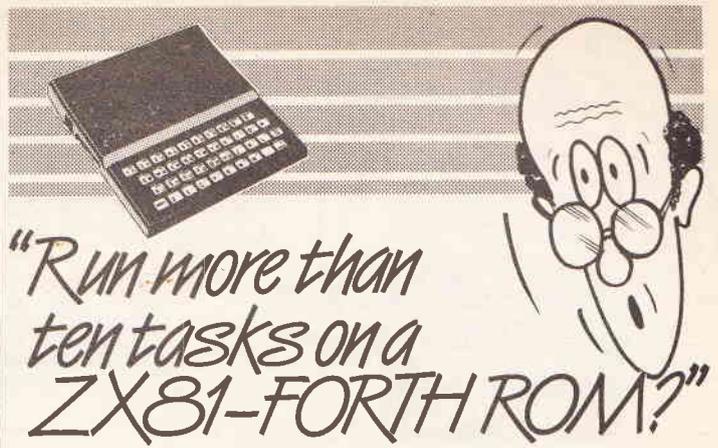MICRO PROCESSOR ENG LTD
21 HANLEY ROAD SHIRLEY
SOUTHAMPTON
SO1 5AP
TEL: 0703 780084



"Run more than ten tasks on a ZX81-FORTH ROM?"

Sure! More than 10 tasks simultaneously and, in some cases, up to 300 times faster! That's what replacing the basic ROM with the new FORTH does for the ZX81 - and more!

The brains behind the breakthrough belong to David Husband, and he's building Skywave Software on the strength of it. Already orders are flooding in and it's easy to see why.

The ZX81-FORTH ROM gives you a totally new system. In addition to multi-tasking and split screen window capability, you can also edit a program while three or four others are executing, schedule tasks to run from 50 times a second to once a year, and with a further modification switch between FORTH and BASIC whenever you like.

The ZX81-FORTH ROM gives you a normal keyboard with a 64 character buffer and repeat, it supports the 16k, 32k, 64k RAM packs, it is fig-FORTH compatible and it supports the ZX printer.

The price, too, is almost unbelievable. As a "fit it yourself Eprom", complete with manual, it's just £25 + VAT. Add £2 p&p UK (£5 Europe, £10 outside Europe) and send your order to the address below.



SOFTWARE


David Husband
73 Curzon Road, Bournemouth,
BH1 4PW, ENGLAND.
Tel: (0202) 302385.
International +44 202 302385.

ETI/22

Heathkit - IT'S A PLEASURE TO BUILD

Bring the enjoyment back into your hobby with a kit from Heathkit. The beautifully illustrated documentation and step-by-step instructions make building a Heathkit a relaxing, absorbing pleasure! Choose from their huge range of fascinating kits and self-instruction electronics and computing courses.

The Heathkit range includes the ultimate in amateur radio kits, computerised weather stations, a highly sophisticated robot, a 16-bit computer kit and a range of home (or classroom) learning courses. These state-of-the-art courses have easy-to-understand texts and illustrations, divided into sections so that you can progress at your own pace, whilst the hands-on experiments ensure long-term retention of the material covered.

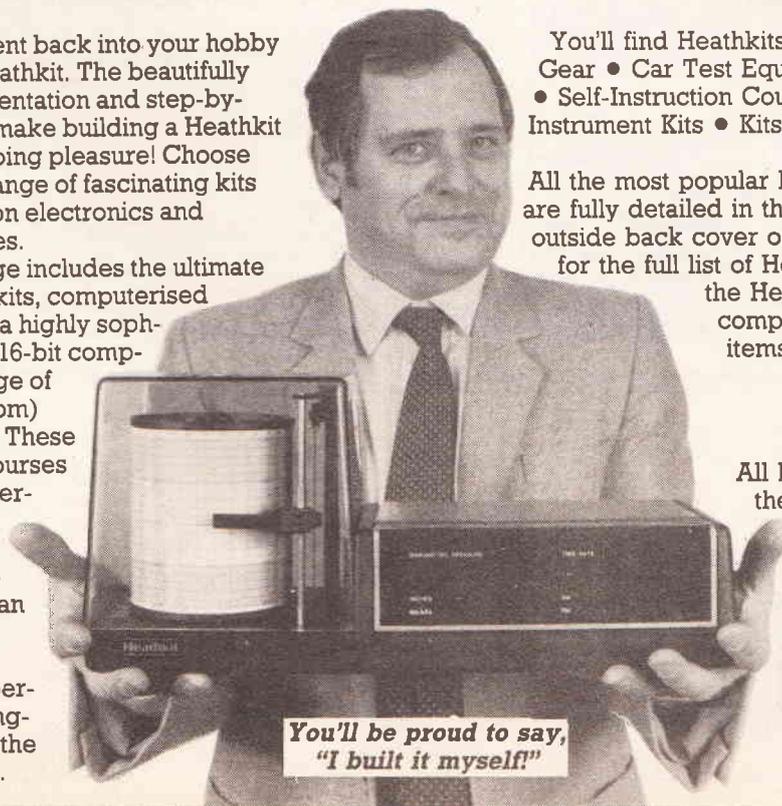

*You'll be proud to say,
"I built it myself!"*

You'll find Heathkits available for Amateur Radio Gear • Car Test Equipment • Kits For The Home • Self-Instruction Courses • Computer Kits • Test Instrument Kits • Kits For Weather Measurements.

All the most popular kits and educational products are fully detailed in the 1984 Maplin catalogue (see outside back cover of this magazine for details) or for the full list of Heathkit products send 50p for the Heathkit International Catalogue complete with a UK price list of all items.

All Heathkit products available in the UK from:

Maplin Electronic Supplies Ltd.

P.O. Box 3, Rayleigh,
Essex, SS6 8LR.

Tel: (0702) 552911.

(For shop addresses see back cover.)

As seen in the national press




The Prizes:

You could win **£2,500** to be spent on a dream holiday of your choice for you and your family!

Second prize — a complete Canon portable video outfit worth £1,300.

Third prize — a BBC Model B micro computer plus software worth £450.

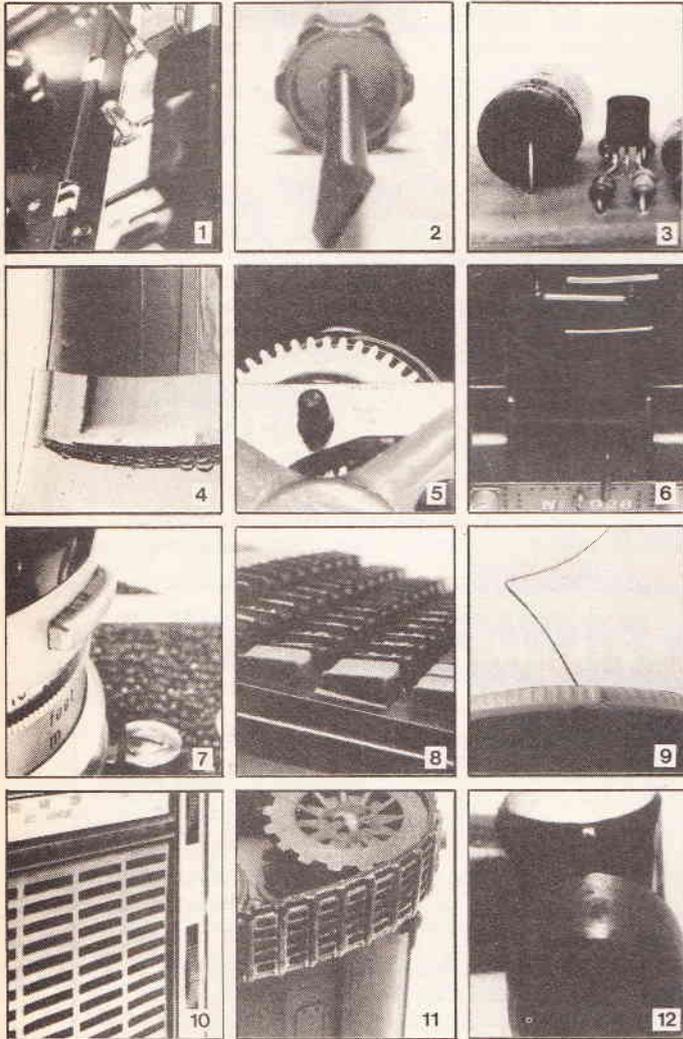Fourth prize — Minolta X700 camera with a 50mm lens and flashgun, worth £280.



How to enter:

Just identify the twelve objects pictured opposite....

HINT — the Argus Specialist Magazines listed below might give you a clue:

Electronics Today International
Personal Computing Today
Movie Maker
Your Model Railway
Clocks
Home Computing Weekly
Beatbox
Ham Radio Today
Electronics
35mm Photography
Model Cars
Woodworker

Games Computing
Photoplay Movies and Video
ZX Computing
Military Modelling
Hi-Fi Now!
Winemaker
Citizens' Band
Model Boats
Video Today
Popular Crafts
Which Video?
Your Commodore

and write your (one-word) answers in the spaces provided on the coupon. For instance, if you think that number 9 is a record, write 'record' in the space next to 9 on the coupon and so on. Then tell us in up to 20 words why **MAGAZINES MAKE IDEAL HOLIDAY READING**. Complete the coupon in BLOCK LETTERS, and send it to: **DREAM HOLIDAY COMPETITION, Argus Specialist Publications Ltd., No 1 Golden Square, London W1R 3AB**, to reach us no later than 31st December 1984.

Competition rules

- 1 The competition is open to all UK and Eire readers except employees of Argus Specialist Publications Ltd., their printers and distributors
- 2 As long as an original coupon from the magazine(s) of your choice is used for each entry there is no limit to the number of entries per person. Photocopied coupons will not be accepted
- 3 All entries must be postmarked before 31st December 1984
- 4 The prizes will be awarded to the first four entrants who identify the twelve objects correctly and whose completed sentence is judged the most apt and original.
- 5 No correspondence will be entered into about the competition results; the judges' decision is final
- 6 Winners will be notified by post and the results will be published in a future issue of this magazine



The 12 objects are

- | | | |
|----------|----------|----------|
| 1. | 2. | 3. |
| 4. | 5. | 6. |
| 7. | 8. | 9. |
| 10. | 11. | 12. |

Magazines make ideal holiday reading because (up to 20 words)

NAME (BLOCK LETTERS) _____ AGE (if under 18) _____

ADDRESS _____

Send to **DREAM HOLIDAY COMPETITION, Argus Specialist Publications, No 1 Golden Square, London W1R 3AB.**

PERPETUAL PENDULUM



More attractive than magnetic sculptures, more swinging than a Newton's cradle, Damon Hart-Davis describes the latest thing in executive toys.

There is no such thing as perpetual motion. However, this project attempts to mimic it with the help of a little electronics and a magnet or two. It was constructed as the 'project' element of an A/O examination in electronics, and it was hoped that the swinging motion might hypnotise the examiners into giving the designer a high mark.

The basic principle behind the project is quite simple; a magnet swings on the end of a piece of cord. At the centre of the swing is a coil with some electronics. The magnet causes a small voltage to appear across the coil, and this is detected by the electronics. The electronics then causes a pulse of current to flow through another coil on the same bobbin, which administers a 'kick' to the pendulum and keeps it going.

To make the motion of the pendulum more interesting, other permanent magnets can be placed around the PCB containing the electronics and coil; this will deflect the pendulum swing from being regular, making it random, and to some minds, more interesting.

The Circuit

The circuit is quite straightforward; IC1 forms the input detector, and Q1 switches on with a sufficiently large output from IC1. IC2a and b form a monostable, IC2c inverts the output from the monostable and Q2 drives the 'kick' coil.

The main problem with this circuit will be its tendency to oscillate. The two coils on the same core constitute a transformer, and although the coupling between the coils isn't very good

HOW IT WORKS

When the pendulum moves away from the coil, a voltage is induced in L1 such that the R1 end goes negative with respect to OV. The amplitude of the induced voltage varies according to the speed of swing of the pendulum and the distance between it and the iron core of the coil, but will be of the order of 10mV.

Because the output coil L2 is wound on the same core as the sensor coil there is a risk of the higher amplitude output pulses being coupled back into the input and causing oscillation. To reduce this risk, the circuit has been arranged so that such induced voltages will be positive with respect to OV. Diode D1 will then conduct and prevent the voltage rising above its forward conduction value. R1 is included to limit the current which flows under these conditions; without it, L1 and L2 would appear as a transformer with a shorted output, and this would cause the transistor driving L2 to get very hot.

R2, R3, C1 and IC1 form an inverting amplifier with a gain of 100. C1 limits the bandwidth of the amplifier and therefore helps to prevent instability and oscillation. The output of the stage is fed to the circuit formed by R4, R5 and Q1, a switch

whose action is largely independent of the supply voltage. This converts the analogue output of the op-amp, which varies in level according to the stimulus, into a logic signal switching quickly and cleanly between logic high and low states.

The output of Q1 is then fed to a monostable multivibrator formed by IC2a, IC2c, C2 and R6. The monostable is triggered when Q1 collector goes low, whereupon the output will go low for 0.2 seconds and then return to the high state. This delay further reduces the risk of the circuit as a whole oscillating and also ensures that the output pulse is of long enough duration to drive the pendulum well away from the coil. Without it, the pendulum might well move around the coil in a small circle rather than swinging across it.

IC2b is used to invert the output of the monostable before feeding it to the coil driver transistor, Q2. R8 is included to limit the current flowing through the coil and the collector circuit of Q2 should the coil have a resistance of less than about 400R. D2 protects the transistor against high back-EMFs generated when the current through the coil is removed.

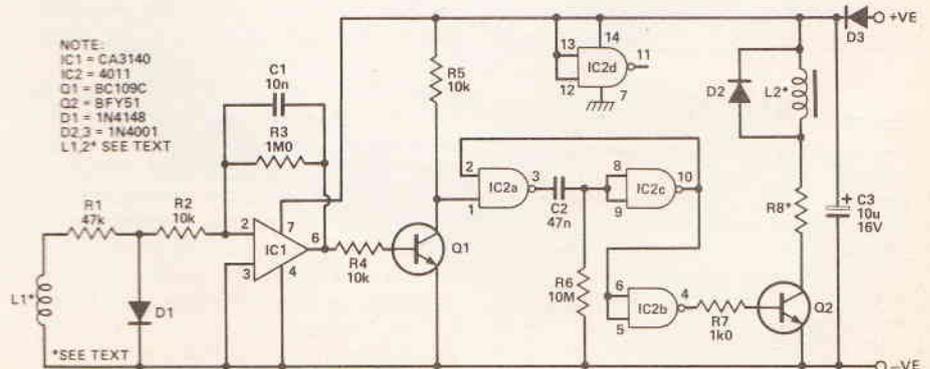


Fig. 1 Circuit diagram of the perpetual pendulum.

PROJECT: Pendulum

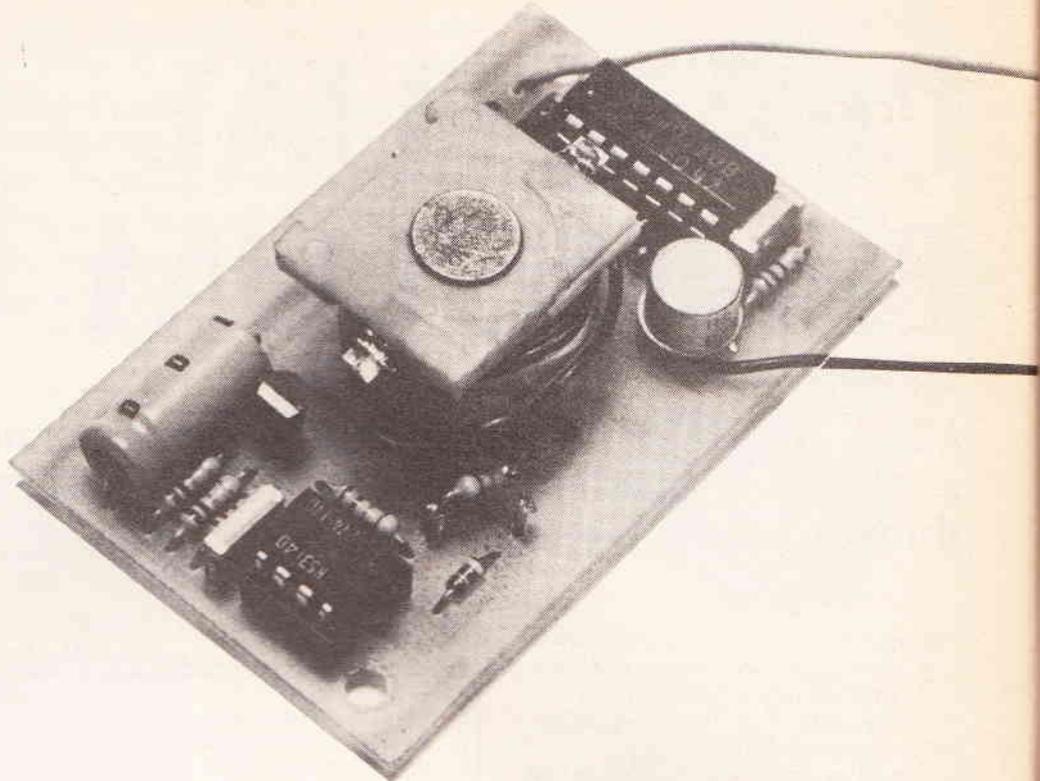
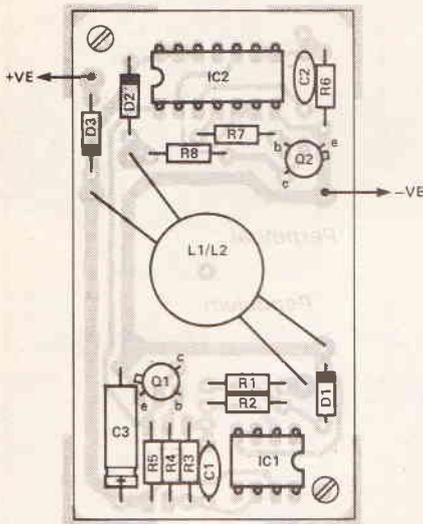


Fig. 2 Component overlay diagram for the PCB.

PARTS LIST

RESISTORS (all 1/4 W, 5%)

R1	47k (see text)
R2,4,5	10k
R3	1M
R6	10M
R7	1k
R8	as required to bring coil resistance up to approximately 400R

CAPACITORS

C1	10n ceramic
C2	47n ceramic
C3	10u, 16V axial electrolytic

SEMICONDUCTORS

IC1	CA3140
IC2	4011
Q1	BC109C or BC182L
Q2	BFY51 or 2N3053
D1	1N4148
D2,3	1N4001

MISCELLANEOUS

L1,2	see text
------	----------

PCB; sockets for ICs if desired; permanent magnet; case, battery or PSU, etc.

(it isn't meant to be) it will probably be enough to cause problems. The gain of the detector is 100, which is tapered off at higher frequencies by C1. The remainder of the circuit is nominally digital, but digital circuits have a nasty habit of behaving like analogue ones just when you don't want them to.

Construction

Assembling the PCB should present no problems and the only points to watch here are the usual ones, such as getting the ICs and the transistors the right way around and not inserting these components until after the resistors and capacitors have been soldered.

The coil used in the prototype for L1 consisted of an 'open' type relay rated at 48V, 10k. The relay was stripped of its contacts and swinging arm to leave just the coil, plastic bobbin and iron core. Two hundred turns of 36 SWG enamelled copper wire were then wound on top of the existing coil to form L2. The rating of the relay coil is not too critical and it is probable that most coils with a large number of turns and a resistance of a few k ohm or more would do. Room has been left on the PCB for resistors in series with both L1 and L2, and it may be necessary to experiment with different values of resistance to get the circuit to work correctly.

As explained in the How It Works section, it is important for correct operation that the two coils are wired in the correct sense relative to one another. The voltage induced in L1 must be positive with respect to OV when L2 is pulsed and negative with respect to OV when the pendulum is moved away from it. It should be possible to find the correct arrangement by experiment, and no damage can be done by getting it wrong at a first attempt. If you have access to an oscilloscope or a reasonably high impedance millivoltmeter, you can determine the correct arrangement by connecting up L2 and determining the polarity of the voltage across L1 when Q1 collector is temporarily shorted to ground.

Choice of case for the project is left very much up to the constructor. The prototype was installed in a clear plastic box with the supply leads taken out to an external PSU, but it could just as easily be built as a self-contained unit with its own 9V battery. The current consumption varies with the supply voltage but is of the order of a few milliamps with peaks of 10-16 mA when a pulse is delivered to L2. This is a little high for sustained operation from a PP3 and if you intend to leave the device on continuously you should use either a PP9 or a mains power supply offering between 5 and 15V.

BUYLINES

The only item here which might present any problems is the relay used for L1/L2. Ours was rescued from a fruit machine and had a 48V, 10k ohm coil, but we have not been able to locate a supplier for these. Most constructors should be able to find something in the junk box which would work reasonably well, but if you really are stuck then try one of the 24V open relays available from Maplin and other suppliers.

ETI

Ex Stock Integrated Circuits

74LS00	70p	2732	495p
74LS04	82p	2764-250	640p
74LS08	60p	611P3	675p
74LS20	45p	TC5516	750p
74LS27	40p	4164	500p
74LS32	70p	7400	30p
74LS157	70p	7404	40p
74LS244	225p	7416	45p
74LS373	210p	7407	225p

Variety of TTL & 74LS items in stock—please 'phone your enquiry.

*Please add 50p for p&p + 15% VAT to all orders.
Export—No VAT. p&p at cost.

Government & Educational Establishments' Official Orders
Welcomed

**NEW CATALOGUE AVAILABLE:
PLEASE SEND S.A.E.**

Cambridge Microcomputer Centre


The Peripheral Centre of East Anglia

153-4 East Road, Cambridge CB1 1DD
Telephone (0223) 355404 Telex 817445

Prices subject to change without notice.



Bonsai 盆景

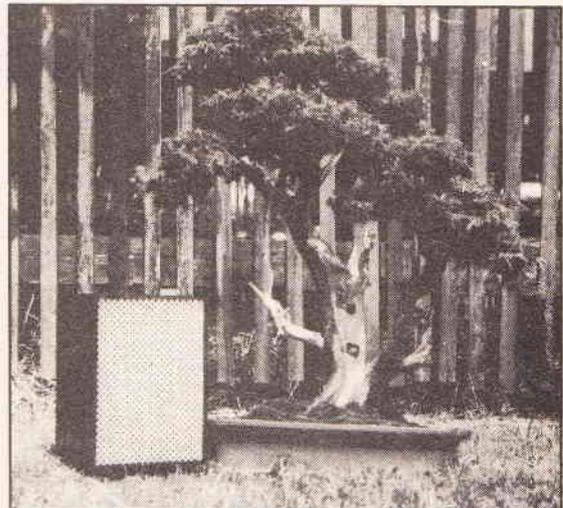

Bonsai is a Japanese technique for miniaturising trees whilst preserving all their natural characteristics. This is exactly what we have done with our new British invented and manufactured loudspeaker.

Based on a newly developed single full range driver the diminutive "Musician Bonsai" has all the qualities of the best, large multi way systems without some of their vices.

For details please contact:

Merseyside Acoustic Developments Ltd.,
Merseyside Innovation Centre,
131, Mount Pleasant, Liverpool, L3 5TF.
Tel. 051-709-0427

Two Hundred Year Old Bonsai Tree By Courtesy Of: TOKONOMA NURSERY.

Component

MINI FILE

For
Electronic and other small parts. A large variety of components can easily be kept well organized. 60 storage pockets per unit.

Unit size:
L400 W125 H77mm.

Material: Injection-moulded in impact resistant polystyrene. 4 and 6 Drawer Steel cabinets available.

The 6 Drawer cabinet, practical for field service, has lock and carrying handle.

Recommended prices (excluding V.A.T.):



6 drawer cabinet with lock and handle	£92.00
4 drawer cabinet with lock and handle	£59.00
Single drawer.	£11.00

Typical Minifile applications:


R & D Departments Prototype Kits
Production Test & Rework Service Departments
Field Service Engineers The Electronic Hobbyist
Repair kits for computers CNC-machines.

Stocked by:

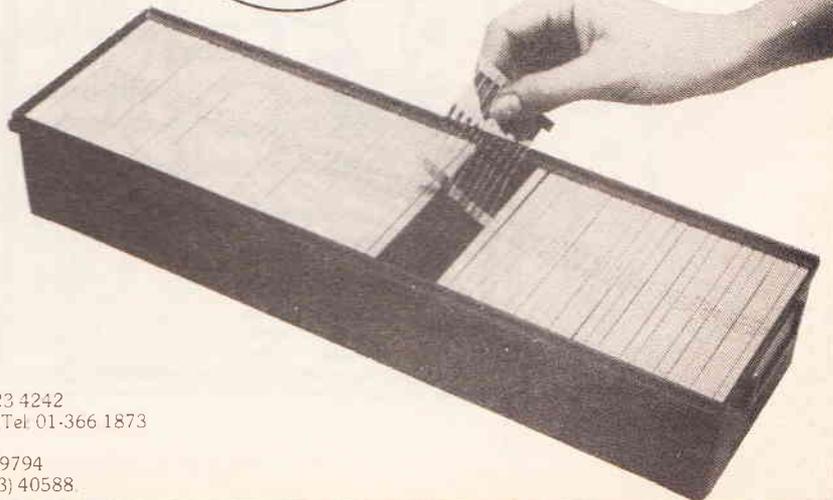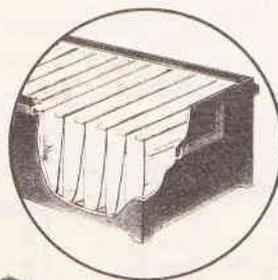
Bradley Marshall, 325 Edgware Road, London W2 1BN. Tel: 01-723 4242
Enfield Electronics, 208 Baker Street, Enfield, Middlesex EN1 3JY. Tel: 01-366 1873
Henry's, 404-406 Edgware Road, London W2. Tel: 01-724 0323
TK Electronics, 11-13 Boston Road, London W7 3SJ. Tel: 01-579 9794
Watford Electronics, 33/34 Cardiff Road, Watford, Herts. Tel: (0923) 40588.





FOIL PATTERNS



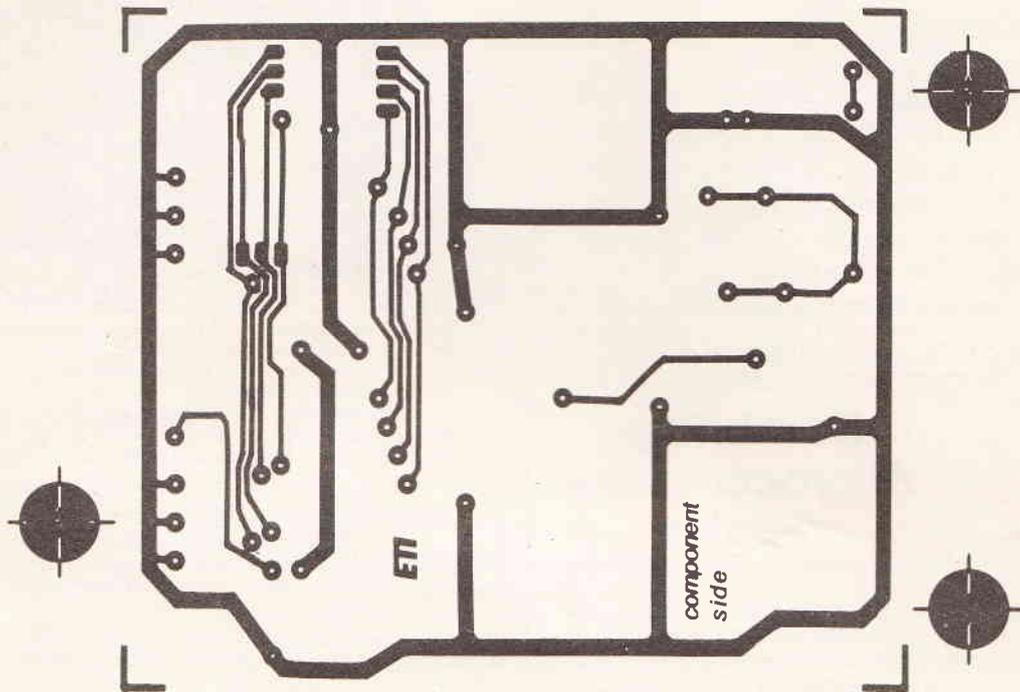


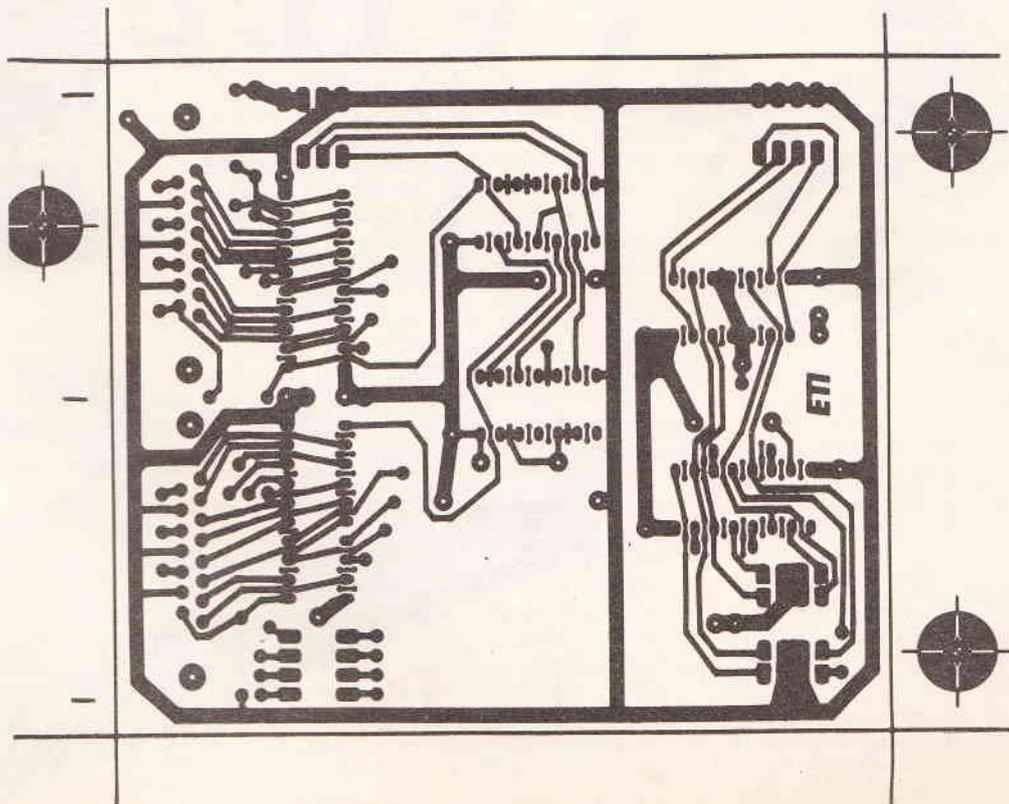The top and bottom foils of the control port I/O board.




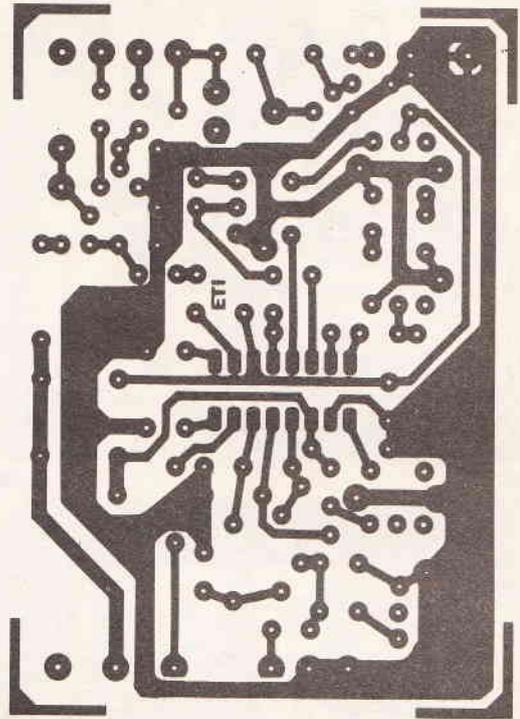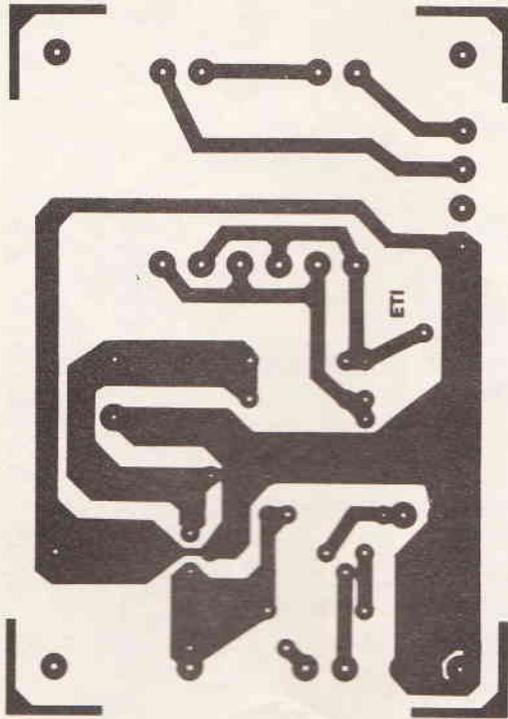

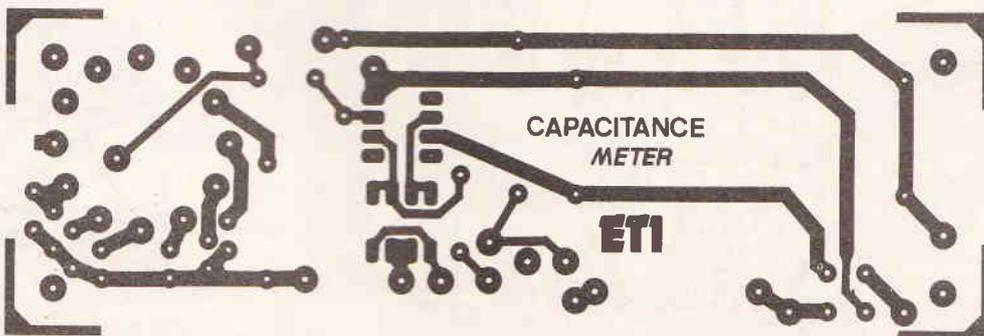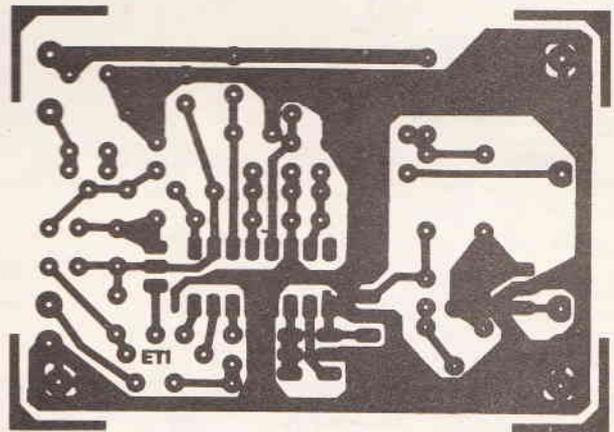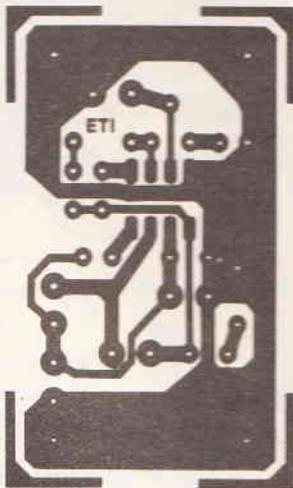These four boards are for the AM/FM radio.





The capacitance meter board.


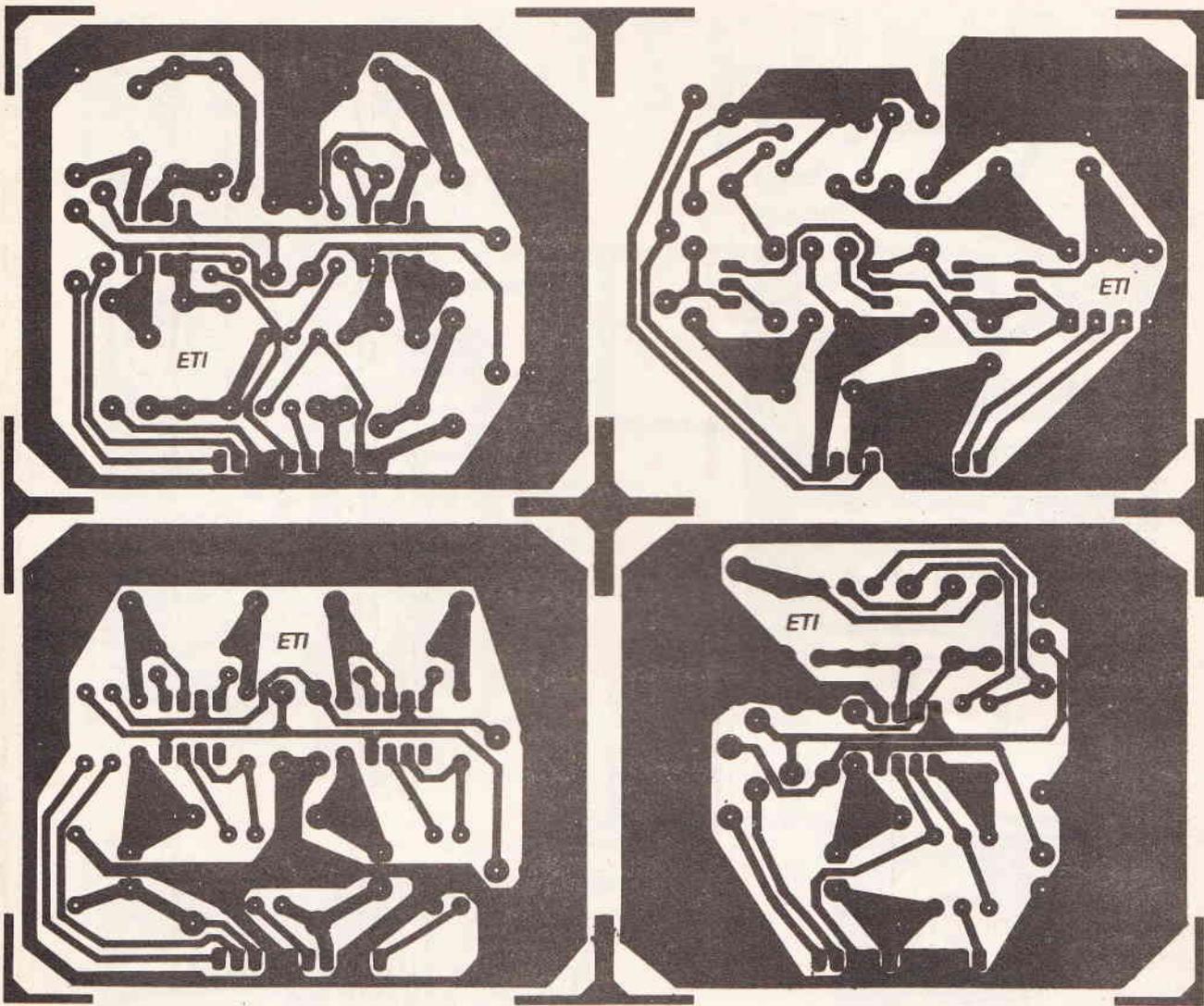


The mother board and four of the plug-in module boards for the active loudspeaker. ▶

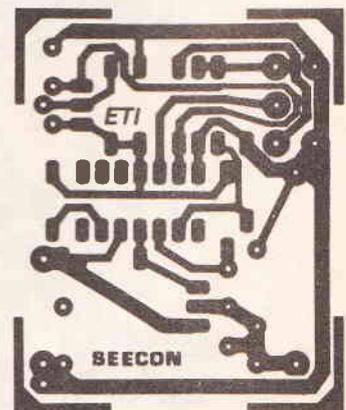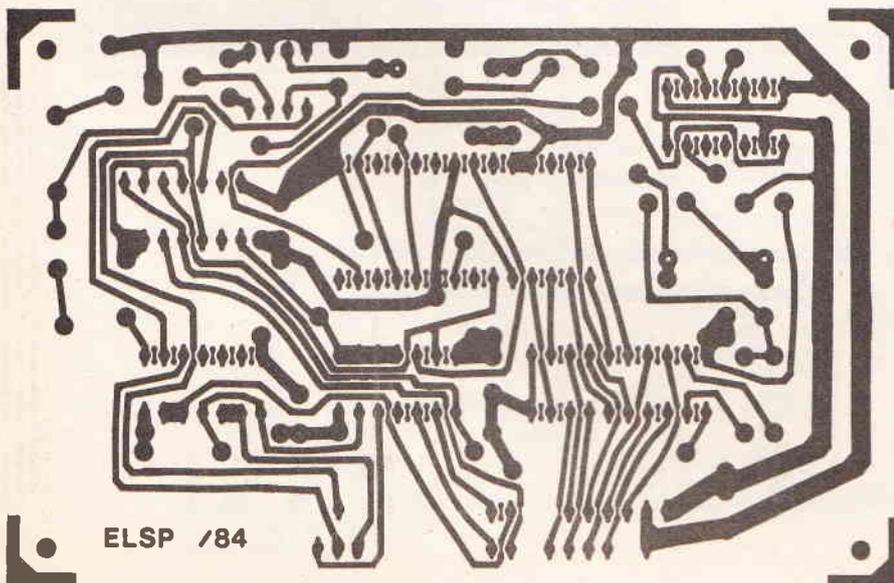
The foil pattern for the Electron speech board.




The temperature controller foil pattern.

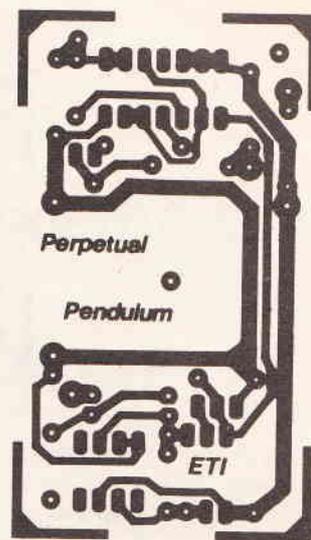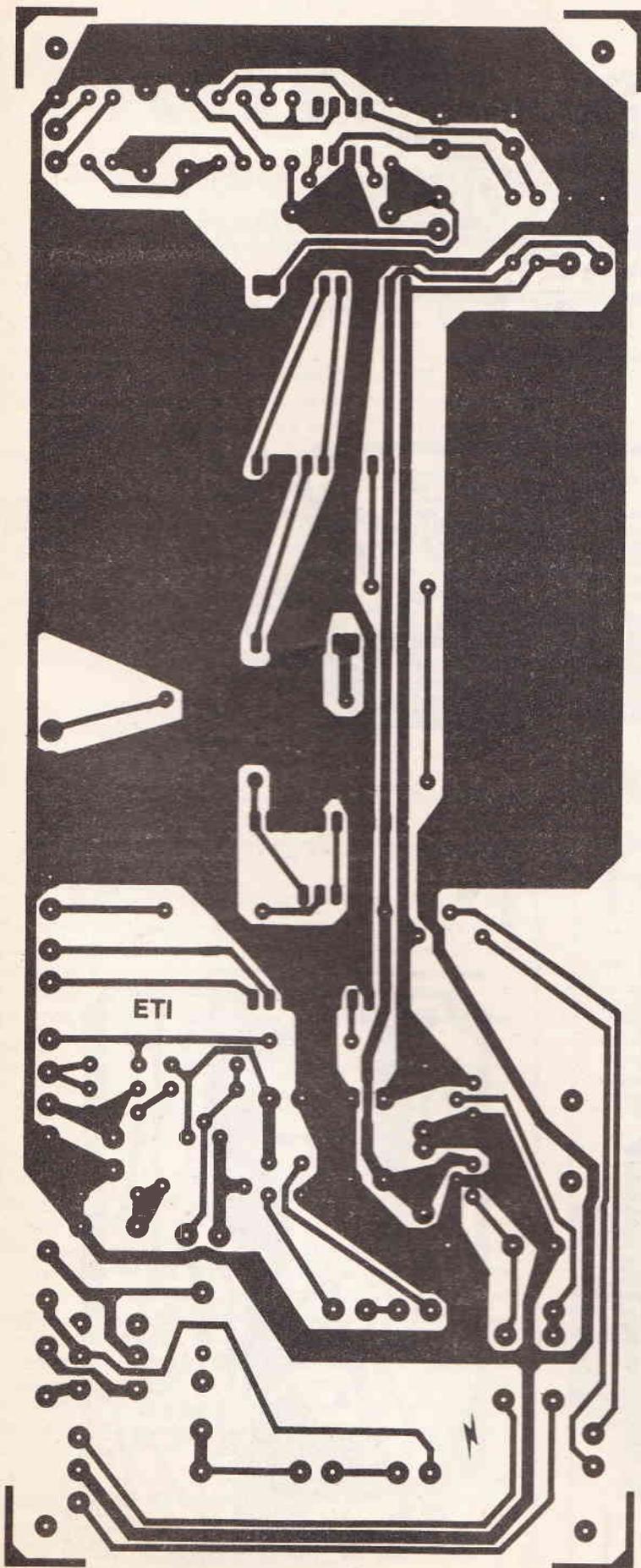


The Perpetual Pendulum foil pattern.

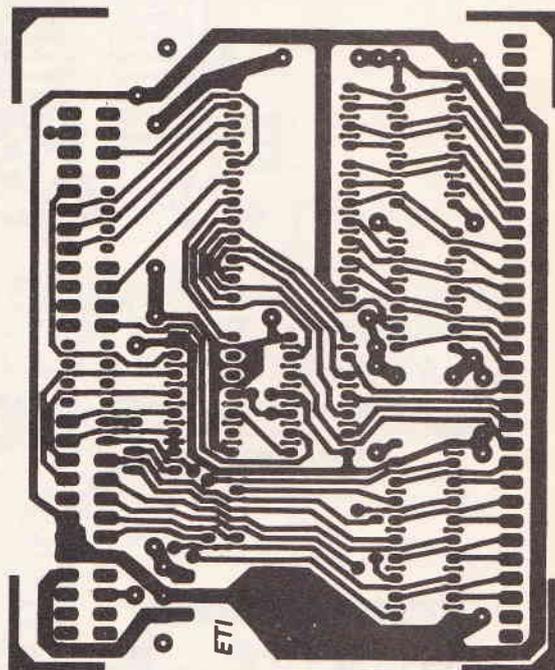

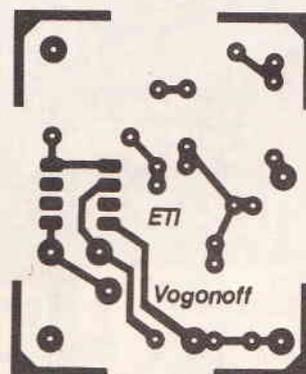
The foil pattern for the Stage Lighting Interface.





The pattern for the mains failure alarm.

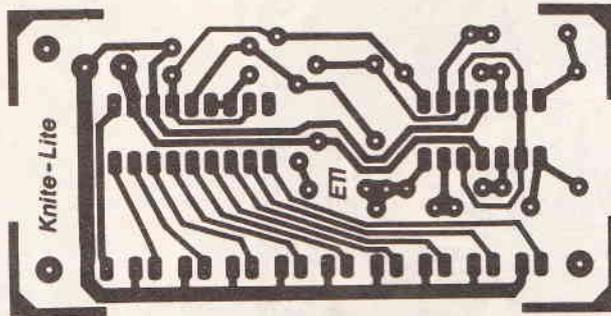

The Knite Light foil pattern.

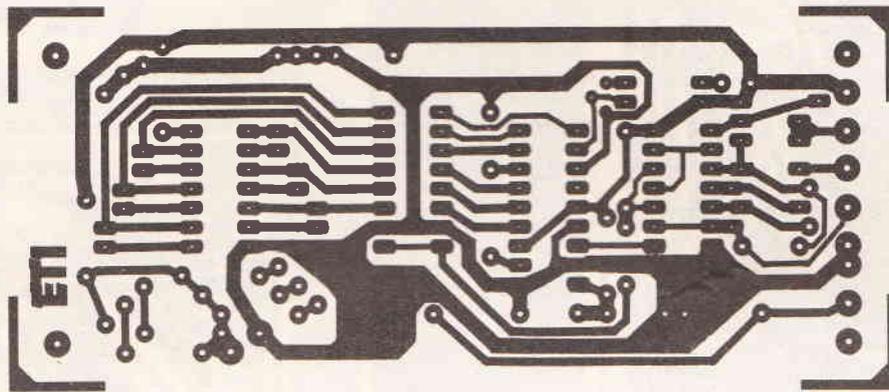

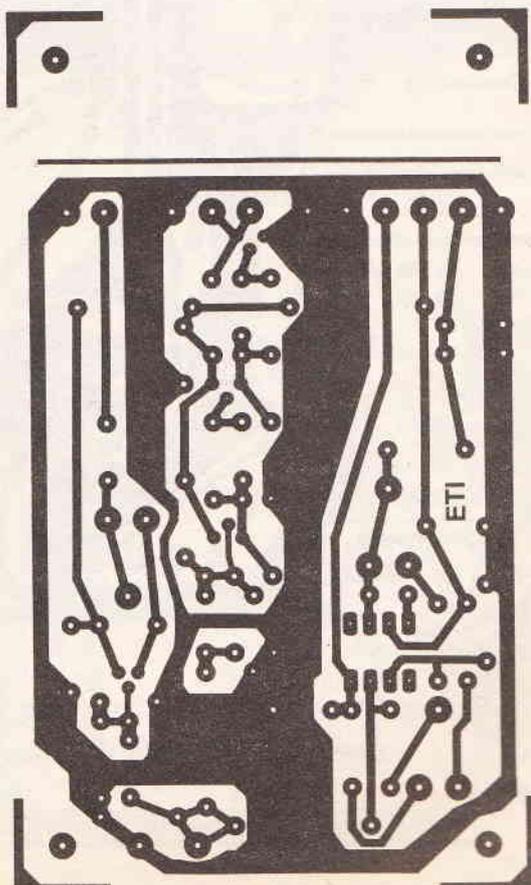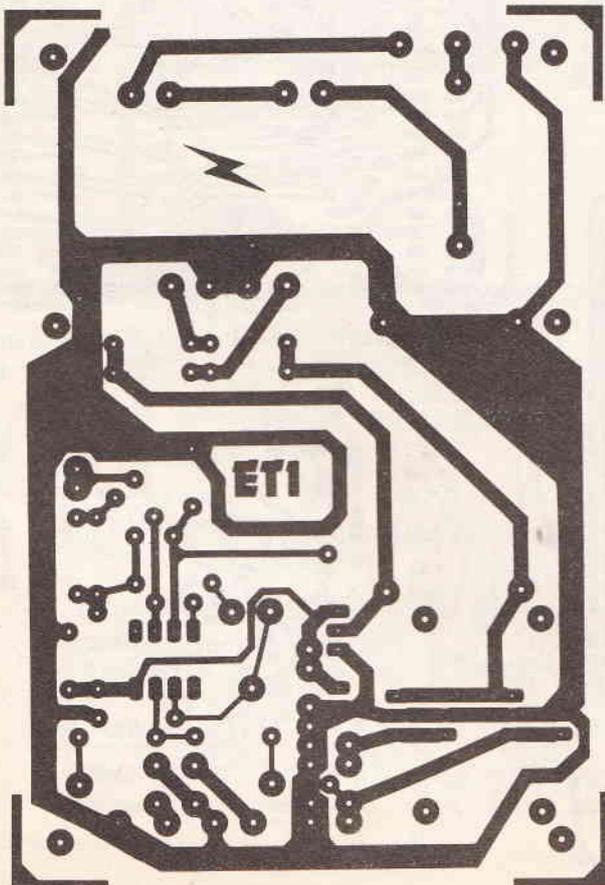These three boards are for the Video Vandal.



ATTENTION ALL WRITERS . . .

. . . or just those of you who sometimes think "I could do better than that!"

We want to hear from you!

The magazine you hold in your hand is part of ASP's electronics group of titles. These include *ETI*, *Ham Radio Today*, *Digital and Micro Electronics*, and our new magazine, *Electronics*. All these magazines are looking for new authors, so if you've designed something for yourself that you think may be of interest to others, or if you've a subject you'd like to write a feature article on, then drop us a line with an outline of what you have in mind.

We particularly need:

- Projects for the Commodore Vic 20 and 64, the Amstrad, the BBC A and B, and the Electron computers;
- Simple projects that do something useful, perhaps in a novel or instructive way;
- Radio projects (not necessarily for radio amateurs);
- Features on amateur satellite radio.

If you're interested in writing for us, send an outline of your proposed article to: Dave Bradshaw, Group Editor (Electronics), Argus Specialist Publications, 1 Golden Square, London W1R 3AB.

Please note that while we take ever care, we cannot be held responsible for the loss of unsolicited manuscripts. We advise all authors to keep a photocopy or carbon copy of any article they send us.

MAIL ORDER PROTECTION SCHEME

If you order goods from Mail Order Advertisers in this magazine and pay by post in advance of delivery, this publication will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for one advertiser, so affected, and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures have not been complied with, at the discretion of this publication, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of reader's difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not for example, payments made in response to catalogues, etc. received as a result of answering such advertisements)

CLASSIFIED ADVERTISEMENTS ARE EXCLUDED.

TELEPHONES AND ACCESSORIES LATEST B. T. TELEPHONES AVAILABLE FOR EXTENSION USE

SLIMTEL — New one piece pushbutton phone from Telecom, includes last number redial and silence feature (In Ivory colour only) £26.04, wall mounting kit for above £3.43.

We have many other types of accessories available, including: Dials, Switches and Buttons, Jack Plugs and Sockets, Jack Adaptors, Cables, Block Terminals, Telephone Cord, Mic. inserts, and Bells.

For details of Telephones, Cordless Phones Speaker Phones, Auto Dialers, Answering Machines and Novelty Phones available as well as the full range of accessories please send a large S.A.E.

NOTE: It is illegal for the consumer to install his own sockets or to alter existing B.T. installations in any way.

All prices exclude V.A.T. Please add V.A.T. at 15% to your order total. Add £2.17 p&p per telephone. Send cheques or postal orders only to:

CAPRIOL SYSTEMS

Units 19-26 Sanders Lodge Ind. Est., Rushden, Northants.

Allows 21 days for delivery.

If an advertisement
is wrong we're here
to put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

The Advertising Standards Authority. ✓

ASA Ltd, Dept 3 Brook House, Torrington Place, London WC1E 7HN

ETI PCB SERVICE

In order to ensure that you get the correct board, you must quote the reference code when ordering. The code can also be used to identify the year and month in which a particular project appeared: the first two numbers are the year, the third is the month and the number after the hyphen indicates the particular project.

Note that these are all the boards that are available — if it isn't listed, we don't have it.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until we receive payment.

1981

- E/811-1 LED Tacho 4.75
- E/811-2 Multi-Option Siren..... 3.68
- E/814-2 Drum Machine (2 boards) 6.44
- E/814-4 Guitar Note Expander 3.68
- E/816-8 Waa-Phase 1.76
- E/816-9 Alien Attack 4.00
- E/817-1 System A-Input
(MM or MC)..... 3.05
- E/817-2 System A — Preamp..... 5.95
- E/817-3 Smart Battery Charger..... 2.27
- E/818-3 Hand Clap Synth..... 4.57
- E/818-5 Watchdog Home
Security (2 boards) 6.11
- E/819-1 Mains Audio Link
(3 boards) 8.45
- E/819-4 Laboratory PSU..... 5.21
- E/8110-1 Enlarger Timer..... 3.91
- E/8110-2 Sound Bender 3.05
- E/8111-1 Voice Over Unit..... 4.57
- E/8111-2 Car Alarm..... 3.23
- E/8111-3 Phone Bell Shifter..... 3.40
- E/8112-4 Component Tester..... 1.71

1982

- E/821-3 Guitar Tuner (2 boards) ... 6.38
- E/822-1 Ripple Monitor 2.21
- E/822-2 Allez Cat Pest Repeller 1.93
- E/822-5 Moving Magnet Stage 4.01
- E/822-6 Moving Coil Stage 4.01
- E/823-4 Capacitance Meter
(2 boards) 11.66
- E/825-1 DV Meg..... 3.13
- E/826-1 Ion Generator
(3 boards) 9.20
- E/826-4 MOSFET Amp Module..... 7.80
- E/826-5 Logic Lock 3.52
- E/826-6 Digital PWM 3.84
- E/826-7 Optical Sensor 2.00
- E/826-9 Oscilloscope
(4 boards) 13.34
- E/827-4 Hotwire..... 3.02
- E/827-5 Bridging Adapter 2.74
- E/828-1 Playmate (3 boards)..... 8.28
- E/828-4 Kitchen Scales..... 2.12
- E/829-1 Auto Volume Control..... 2.12
- E/829-2 Dual Logic Probe 2.22
- E/8211-4 Pulse Generator 6.08
- E/8212-1 ELCB 2.77
- E/8212-2 Servo Interface
(2 boards) 6.75
- E/8212-4 Spectracolumn 5.54

1983

- E/831-1 Fuel Gauge..... 3.45
- E/831-2 ZX ADC..... 2.59
- E/831-3 Programmable PSU..... 3.45
- E/833-1 SoundBoard..... 12.83
- E/833-2 Alarm Module 3.62
- E/833-3 ZX81 User Graphics 1.07
- E/833-4 Logic Probe 2.50
- E/834-1 Real Time Clock 8.74
- E/834-2 Thermometer
(2 boards) 9.74
- E/834-4 Stage Lighting — Main ... 13.73
- E/834-5 Stage Lighting — Display 3.45
- E/835-1 Compressor/Limiter 6.19
- E/835-2 Single PSU 3.16
- E/835-3 Dual PSU 4.01
- E/835-4.2 NDFL Amp 7.88
- E/835-5 Balance Input Preamp..... 3.23
- E/835-6 Stage Lighting
Autofade..... 6.19
- E/835-7 Stage Lighting —
Triac Board 4.74
- E/836-1 to 3 PseudoROM
(3 boards) 3.62
- E/836-5 Atom Keypad..... 5.18
- E/837-1 Flash Sequencer 2.67
- E/837-2 Trigger Unit Main Board... 2.67
- E/837-3 Trigger Unit Transmitter... 1.66
- E/837-4 Switched Mode PSU 16.10
- E/838-1 Graphic Equaliser 9.10
- E/838-2 Servo Fail-Safe
(four-off)..... 2.93
- E/838-3 Universal EPROM prog.... 9.64
- E/837-1 NiCad Charger/Regen.... 3.77
- E/839-2 Digger 3.40
- E/839-3 64K DRAM..... 14.08
- E/8310-1 Supply Protector 2.19
- E/8310-2 Car Alarm..... 3.98
- E/8310-3 Typewriter Interface 4.17
- E/8311-1 Mini Drum Synth 3.07
- E/8311-2 Alarm Extender..... 3.21
- E/8311-3 Multiswitch 3.59
- E/8311-4 Multiple Port..... 4.34
- E/8311-5 DAC/ADC Filter 3.22
- E/8311-6 Light Pen 4.60
- E/8311-7 Logic Clip..... 2.51
- E/8311-8 MC Head (JLLH)..... 3.17
- E/8312-1 Lightsaver..... 1.85
- E/8312-2 A-to-D Board..... 12.83
- E/8312-3 Light Chaser (2 bds) 7.54
- E/8312-4 ZX Alarm 6.04

1984

- E/841-1 Vector Graphics 8.27
- E/842-1 Speech Board
(Mini-Mynah) 10.97
- MODULAR PREAMP:**
- E/842-2 Disc input (mono) 3.73
- E/842-3 Output stage (stereo) 3.73
- E/842-4 Relay/PSU 3.73
- E/842-5 Tone, main (mono)..... 3.73
- E/842-6 Tone, filter (stereo) 3.73
- E/842-7 Balanced output (st) 3.73
- E/842-8 Headphone amp (st) 3.73
- E/842-9 Mother board 9.01
- E/843-1 Power Meter 5.81
- E/843-2 Z80 DRAM..... 9.79
- E/843-3 Obedient Die..... 3.76
- E/844-1 School Timer 4.07
- E/844-2 Mains Borne RC (Rcvr) 3.70
- E/845-1 Auto Light Switch 4.01
- E/845-2 ZX81 EPROM Prog. 10.53
- E/845-2 Mains Born RC (Trans)..... 5.07
- E/845-2 Centronics Interface 4.09
- E/845-5 Vario 6.62
- E/845-6 Midi Drum Synth 3.59
- E/846-1 Oric EPROM Bd 19.58
- E/846-2 Spectrum Joystick..... 3.30
- E/847-1 Warlock Alarm 8.19
- E/848-1 Joystick Interface..... 3.07
- E/848-2 EPROM Emulator 9.11
- E/848-3 Infrared Transmitter 3.70
- E/848-4 Infrared Receiver..... 3.98
- E/848-5 CMOS Tester 4.60
- E/849-1 EX42 Kybd. Interface 3.82
- E/849-2 Banshee Siren 3.19
- E/849-3 Dry Cell Charger 2.80
- E/8410-1 Echo Unit 3.92
- E/8410-2 Digital Cassette..... 9.80
- E/8410-3 Disco/Party Strobe 4.80
- E/8411-1 AM/FM Radio (4 bds) 13.02
- E/8411-2 Control Port-control bd ... 12.15
- E/8411-3 Control Port-I/O bd..... 6.33
- E/8411-4 Capacitance Meter..... 3.55
- E/8411-5 Video Vandal (3 bds)..... 12.10
- E/8411-6 Temperature Controller ... 2.88
- E/8411-7 Mains Failure Alarm..... 2.54
- E/8411-8 Knite Light 3.25
- E/8411-8 Stage Lighting Interface... 3.73
- E/8411-10 Perpetual Pendulum 3.14

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £.....
 Add 45p p&p 0.45
 Total enclosed £.....

**PLEASE ALLOW
28 DAYS FOR
DELIVERY**

Signed

Name

Address

.....

ELECTRONICS TODAY INTERNATIONAL CLASSIFIED

Lineage:

40p per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£11.00 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699

Send your requirements to:
Will Fox
ASP Ltd.,
1 Golden Square,
London W1.

ALARMS

FOR SALE

ALARMS

FREE BOOKLET

on
BURGLAR ALARMS
with

LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY

051-523 8440

AD ELECTRONICS

217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



ALARM EQUIPMENT

Complete door entry phone kit £39.50
2 Zone B.S. panel! from £36.50
Single zone B.S. panel! £33.50
Complete CCTV kit £235.00

(Prices + VAT & Carriage)

Send for full list of fire and security equipment.

VICTOR SECURITY CENTRES LTD

Hambledonian Yard, West Row
Stockton-on-Tees, Cleveland TS16 1BB
Tel: 0642 608500

BURGLAR Alarm Equipment.
Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 731532.

KNIGHT ALARM SUPPLIES

Wholesalers of intruder and fire alarms, C.C.T.V., door entry, emergency lighting, nursing call equipment.

• External PIR/controllers
..... from £60.00 + VAT

• Digital key pads
..... from £19.00 + VAT

CATALOGUE AVAILABLE

349 Kirkstall Road, Leeds LS4 2HD
Tel: (0532) 795-079

EPROMS — Texas TMS 2716 JL/45 Triple Rail 100 new, offers. Telephone: Basingstoke 68465.

KITS

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD for computer, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, £79.70, get the TIME RIGHT.

Fun-to-build kit (ready made to order) includes ALL parts, printed circuit, case etc, by-return postage, list of other kits.

CAMBRIDGE KITS

45 (TL) Old School Lane, Milton, Cambs.

A1 INTRUDER ALARMS

Wholesale Alarm Suppliers

Latest D.I.Y. & Wholesale Published Catalogue.

Write off for your copy

86 Derby Lane, Old Swan, Liverpool 13

Tel: 051 228 3483 or 051-220 0590

SOFTWARE APPLICATIONS

CORTEX SOFTWARE

For the Powertran Cortex computer.
FORTH — Supplied in two 256k eproms. Totally standalone supports cassette, 5.25" & 8" discs. Price £35.00 inclusive.

DISCS — Forth utilities, use with above eproms, contains editor, assembler, and utilities. Price £30.00 inclusive.

AUTO-BOOT DISCS
FORTH — Use the Basic 'BOOT' command to download the Forth system, the Forth eproms are not required. Price £35.00 inclusive.

CDOS — Adds file support to Cortex Basic, named program and data files. Includes format and configure utilities. Price £50.00 inclusive. Disc orders, please state 5.25" or 8" s.a.e. with all enquiries to:-

LOMBARD SYSTEMS
18 Lombard Street, Lidlington
Bedford MK43 0RP

USE ETI
CLASSIFIED
SECTION
TO SELL YOUR
PRODUCT/SERVICE

Either fill in the
coupon or phone

01-437 0699

HOME GUARD SYSTEMS

If you want professional alarm/C.C.T.V./Door entry/security lighting equipment or DIY kits at genuine trade prices don't delay phone today for our free illustrated catalogue.

Tel: 01-651 2449
Freeport, South Croydon
Surrey CR2 9PU
(no stamp required)

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept E 1,
60 Market St, Wigan WN1 1HX.
Telephone: (0942) 42444



FOR SALE

100W AMPLIFIER — £9.95 built or use the same board for 50W, 150W, 200W into 4 or 8 ohms etc., by using alternative output transistors & P.S.U. S.A.E. for full details to ESS Amplification, Unit 11, Argyle St., Hull.

BARGAIN PACKS our speciality. Send S.A.E. for details plus free samples. Projek Electronics, 44 Mathie Crescent, Gourock PA19 1YX.

ELECTRONIC ORGAN KEY-BOARDS and other parts being cleared out as special offer. Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. 01-986 8455.

POWERTRAN CORTEX Computer. Basic unit. Most IC bases fitted for optional extras (RS232, discs). £220 o.n.o. Bedford (0234) 766111 evenings weekends except Friday.

POWER AMPLIFIERS 200 watts £12.95 ... case plus controls and sockets ... tested. Glass/PCB ... 4 x MJ3001/TO3 output. 100+ 100W ... (MRP £38.40 plus data ... KIA-8 Cunliffe Road, Ilkley LS29 9DZ.

MICRO BUG

140mm x 370mm. Extremely sensitive, powerful. Operates from 1.5V battery ready built tested only **£9.95** (in kit form **£7.50**).

Also available Automatic Telephone Recorder built tested **£11.95** (in kit form **£8.50**).

All fully guaranteed. Send cash, cheque or P.O. to:

SHAH ELECTRONICS
11 Livingstone Road
Southall, Middlesex
UB1 1TH

METRONOME KIT. Easy to assemble complete with box. You need only a soldering iron and wire cutters. £6.50 including p&p and VAT. Hunt Electronics, PO Box 57, Derby DE6 6SN.

ECOLIGHT (ETI July 84) full kit as per article. £21.05. P.C.B. only £4.50. GP Electronics, 87 Willow Tree Ave., Durham DH1 1DZ.

LINSLEY HOOD DESIGNS LOW DISTORTION AUDIO SIGNAL GENERATORS

A0 113 Kit £25 (p.p. £1)
A0 149 Kit £32 (p.p. £2)

Super Hi-Fi Amplifier (ETI)
P.C. Boards from £4

Send S.A.E. for further details:

TELERADIO ELECTRONICS
325 Fore Street, London N9 0PE
Tel: 01-807 3719

PRINTED CIRCUITS

Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

MINIATURE FM TRANSMITTERS. Frequency 60-145 MHz, range ½ mile S.G.F.-P.C.B. All components. Full instructions. 9-12V operation, broadcast reception. Super sensitive microphone. Pick-up on FM radio. £6.95 inc; or ready built £8.95: Same day despatch — Zednith Electronics, 21 Station Road Industrial Estate, Hailsham, E. Sussex BN27 2EW.

WANT RESULTS? THEN USE ETI CLASSIFIED SITUATIONS VACANT

AUDIO ENGINEER REQUIRED. Experienced in servicing all types of hi-fi, radio cassettes and in-car entertainment. Phone Ian on 01-249 4814.

COMPONENTS

UNAVAILABLE COMPONENTS? If we can't get them nobody can. Quote without obligation or charge. Quote or order period approx 2 weeks. No order is too small. Rickman Components, South Ronaldsay, Orkney KW17 2TW. Phone 085683-430.

PHONE OR WRITE for VAT inclusive price list. eg 7805 voltage regulator 38p. HUNT ELECTRONICS, PO Box 57, Derby DE6 6SN (0283) 703071.

IRISH READERS
MAIL ORDER COMPONENTS
 Top quality components
 Great prices
 Return-of-post service
 Write or phone for free price list
WAVEFORM ELECTRONICS
 12 Effra Road, Rathmines, Dublin 6.
 Phone (01) 0001 if England 987507
 Mail order only please

AERIAL AMPLIFIERS improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire, BLO 9AGH.

COMPONENTS

BUMPER BOX OF BITS

WOW! We've got so many components in stock, we can't possibly list them all — So buy a box. In it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's etc., coils, pots, and so on. All modern parts — guaranteed at least 1000 items, minimum weight 10lbs. ONLY £8.50 inc. 48 page catalogue 50p.

ELECTRONICS WORLD
 1e Dews Road, Salisbury, Wilts SP2 7SN

Betatron Electronics Supplies

Toroidal transformers primary 250V secondaries 0-40, 0-40V, 0-50, 0-50V, 0.55, 0-55V, 0-70, 0-70V at 300VA £17.55, 500VA £24.70, 625VA £30.50. Can Electolitics 63V, 6800uF SA £24.35. 10,000uF 7A £5.45. 100V 6800uF 8A £6.23, 4700uF 8A £5.50. 3300uF 7A £4.20. 2200uF 15A £3.00. Computer Grade 10,000uF 15A £14.69. MOS-FETs 2SJ50/2SK 135 £8.50. 2SJ83/2SK 227 £8.20 price per pair. 35A 200V bridge rectifiers £3.25. VAT inclusive £1.00 p&p under £7.00. Full spec. many more. Resistors, capacitors, transistors, heat sinks, amplifiers, speakers, transformers, etc. Send 4 x 9 self addressed envelope for large list.

Laver St., Cavendish, Suffolk CO10 8AP.
 Tel: 0787 280639.

2764's! (350ns) Thousands must go only £7.50 each (+V.A.T.). Ideal for BBC etc. Also bulk eeprom copying service (any type/quantity considered). DG Sharp (Computer Services), 49 Main St., Bothwell, Glasgow, G71 8ER.

TRANSISTOR/I.C. SALE

2716 EPROM £1.25
 2116 16K RAM £2.00
 MJE 3055 10 for £1.75
 TIP 29/30/31/32A
 10 ANY MIX £1.80
 BD 135/137/139 20p
 100 mixed, coded transistors. All types SS/Tower £2.
 SAE for List. 50p carriage all orders.
 J. WRIGHT
 27 Broomhill Drive
 Glasgow G11 7AB

DIODES IN4001 2½p. IN4005 3p. IN5400 7p. IN5404 9p. IN5408 12p. IN4148 1½p. BZY68C Zeners 4½p.
RESISTORS ¼ watt ½p.
 Minimum 100 off and 50p carriage.
 Webb Electronics
 41 Winwick Street, Warrington WAS 2AS
 Tel: 54174

PLANS 'N DESIGN

AMAZING ELECTRONIC plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

REPAIRS

MICRO-COMPUTER repairs. ZX Spectrum, VIC 20, C64 Pets, Commodore computers, printers and floppy disk. Phone Slough (0753) 48785. Monday to Saturday.

WANTED

Electronic test equipment, large computers, large quantities of Printed Circuit Boards, anything considered, good prices paid: "C" House, Stanhope Rd., York Town Ind. Est., Camberley, Surrey. 0276-28208.

SERVICES

JBA ELECTRONICS

Manufactures to design or specifications. One offs, small batch prototypes. Analogue digital electronic equipment. Complete electronic service — no job too small.
 1st Floor, 4a Lion Yard
 Brecon, Powys, South Wales
 Tel: (0874) 611177

PRINTED CIRCUIT BOARDS

manufactured to your specification. Quality, Quick service. Competitive Prices. COPPER-CLAD fibreglass boards cut to size. 1mm thick £1.80 sq. ft. 1.6mm £2.20 sq. ft. Postage 75p. Mondo Circuits Ltd, 35 Grosvenor Road, Twickenham, Middx. Tel: 01-891 5412.
P.C.B. DESIGN & LAYOUT, manually taped artwork professionally produced at competitive prices. James Gledhill. Tel: 01-674-8511.

FREE PROTOTYPE of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: halstead (0787) 477408.

WIRES 'N CABLES

THE SCIENTIFIC WIRE COMPANY
 811 Forest Road, London E17
 01-531.1568
ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8-34	3.63	2.09	1.10	88p
35-39	3.82	2.30	1.26	93p
42-43	5.20	2.91	2.25	1.60
44-47	8.56	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69

SILVER-PLATED COPPER WIRE
 14-30 9.09 5.20 2.93 1.97
TINNED COPPER WIRE
 14-30 3.97 2.41 1.39 0.94
 Prices include P&P and VAT. Orders under £2 add 20p. Dealer inquiries welcome.

EQUIPMENT

EPROM COPIER — STAND ALONE
 2716-27128 £175.00
 TELEPHONE CONVERSATION RECORDER £75.00
 2 LINES INTO 1 ANSWERING MACHINE
 Switching Unit £30.00
 From L.K.F. Systems Ltd
 St. Albans. Tel: 55084

BOOKS

PARAPHYSICS JOURNAL (Russian translation); psychotronics, kirlianography, heli-phonics music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

WANTED

TURN YOUR SURPLUS transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

SCOPES

Repaired & recalibrated, all makes, all models.
 Scopex Safgan, Older TEK, TQ
MENDASCOPE LTD
 Otter House
 Western Underwood, Olney
 Bucks MK46 5JS
 Tel: Bedford (0234) 712445

BOOKS EXCHANGE SERVICE

BOOKS WANTED FOR CASH
 Have you got technical books you no longer need? OR Do you need to read up on a new topic? Then EXCHANGE BOOK CLUB can help YOU!
 We buy and sell previously read books on electronics and computing. For list of currently available titles and details of our guaranteed buy back plan SAE please to:-
JAMES ELECTRONICS, P.O. Box 2
 Rothwell, Leeds LS26 0UY

MISCELLANEOUS

AGENTS

Wanted to Sell Computer Software for most computers. We now have the Dialog Electronics Part I in stock, Pools Winner & Course Winner. We can supply business software, games and computer ad ons. Phone (0288) 4179 up to 9pm most nights for your free list and details about our agents.

WANT TO BUY SELL SWOP? JUST FILL IN THE COUPON OVERLEAF OR PHONE 01-437-0699

ADVERTISERS INDEX

Ralph Allen Engineering	32
AM Electronics	67
Antex	20
Audio Electronics Ltd.	90
Autrol	74
B. Bamber	56
B.N.R. & E.S.	61
BK Electronics	14
Bridge Scientific Instruments	32
Cambridge Learning	40
Cambridge Micro Computer Centre	79
Capriol Systems	85
Centurion Alarms	67
Cirkit	19
Cricklewood Electronics	8
Cybernetic Applications	IFC
Dionics	74
Display Electronics	10
Electrovalue	28
Estatech	61
Global Specialties Corp.	43
Greenbank	28
Henry's Audio Electronics	48/49
Hi-Tek Electronics	12
ICS	65
ILP	71

Kelan Engineering	33
Kemplant	90
LB Electronics	43
Maplin	75/OBC
Marco Trading	16
Merseyside Acoustic Developments	79
Micro Processor Engineering	75
Micro Range Electronics	32
MJL	43
Newrad Instrument Cases	71
Norbain	18
Powertran	28/IBC
Rapid Electronics	6
RTVC	40
RVM Audiotronics	71
Riscomp	27
Ship Co	79
Skywave Software	75
SME	67
Sparkrite	61
Stewart of Reading	65
Systems Electronique	90
Technomatic	34 & 35
TK	56
Watford Electronics	4 & 5
Wilmslow Audio	65

LOUDSPEAKERS by
Audio Electronics Ltd.




Precision Bass mid range units for many applications manufactured in our own workshop.

Audio Electronics Ltd.
Elm Place, Station Road, Rustington, West Sussex, UK
Telephone: Rustington (09062) 6483

'GRIPMATE'

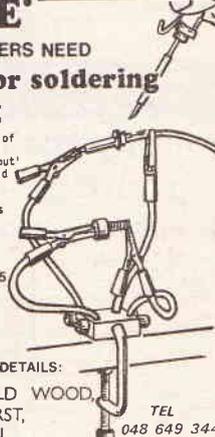ELECTRONIC ENGINEERS NEED
'Extra hands' for soldering and assembling



The basic "GRIPMATE" kit consists of a base block secured with the simple but firm clamp. Two 'stayput' wires, with croc-clip ends are held into the block with thumb screws rapidly and positively adjusted to an infinite number of positions to hold and grip small parts and components

BASIC KIT (BLOCK - CLAMP - 2 FLEXI-ARMS) £3.85
2 EXTRA FLEXI-ARMS £1.00
MAGNET ARM £1.50
MAGNIFIER ARM £2.50
ALL INCL VAT POST & PKG
SEND NOW CHO/PO OR SAE DETAILS:

KEMPLANT LTD DURFOLD WOOD,
PLAISTOW, BILLINGSHURST,
WEST SUSSEX, RH14 0PN

TEL
048 649 344

LOOK - IT'S HIS FIRST WINTER SPECIAL



BEARPARTS

We are the main stockists for 'BEARPARTS', the new name in electrical, electronic and audio components.

Interested?

Send S.A.E. and

receive your


FREE

'BEARPARTS' sample pack.

PROFESSIONAL LEVEL INDICATOR KIT ONLY £39.30p

- 240 AC Operation
- British Standards DIN Case
- Complete with P.M. Level Probe
- LED Display
- Quality P.C.B. & Components

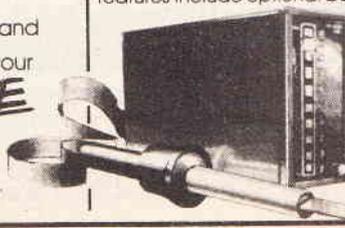When probe is immersed in a liquid its depth is indicated on the units LED display. Additional circuit features include optional battery operation & octo-isolator switching for use with alarm or logic circuits.



Ready Built with 12 months guarantee - **£44.95p**

Please add £1.45 P & P + 15% VAT.

Other kits available. Please send for details.

Call in and see our new counter now open

9.00 - 5.00 Mon-Fri

9.00 - 12.00 Sat

Too far to call? Don't worry, export / mail order is our speciality. Why not write and find out more.

**SYSTEMS
ELECTRONIQUE**

(U.K.) LTD.

26 Engineer Park, Sandycroft,
Deeside, Clwyd CH5 2QD.

Tel: (0244) 536700.

TOP QUALITY KITS AT LOW-BUDGET PRICES

We now have an arrangement with Music Maker Publications and will provide kits of projects that appear in Electronics & Music Maker and its sister publications, Home Studio Recording and Guitarist. Watch out for ads in all three mags.

MPA 200

100w Mixer/amplifier

A rugged mixer amp designed for adaptability, stability and easy assembly. The MPA 200 has four inputs (sensitivities can be easily changed), 3 separate tone controls and a master volume control. Steel cabinet to suit 19" rack systems. Complete Kit

£79.50 + VAT

SP2 200

2-channel 100watt Amplifier

An ingeniously designed power amp. The SP2 200 can deliver over 100w rms into 8 ohms on each channel. Separate volume control and a sensitivity of 0.775 mV (0dBm) make this unit suitable for virtually all pre amps or mixers. Construction is very simple, with minimal wiring and the steel cabinet is suitable for 19" rack mounting. Complete Kit

£99.50 + VAT

Chromatque 5000

5 Channel Lighting Effects System

Versatility is the key aspect of the Chromatque. Musical input can perform switching or modulation of the light output. 5 banks of lamps of up to 500w each can be controlled in either analogue or digital mode. Variable light level controls provide scope for "mood" lighting. The kit's single-board concept makes for straightforward assembly. Complete Kit

£79.50 + VAT

TRANSCENDENT 2000

Transcendent 2000

This professional quality, single board 3-octave synth is transposable 2 octaves up or down giving an effective 7-octave range. There is portamento, pitch bending, VCO with shape and pitch modulation, VCF with high and low pass outputs and separate dynamic sweep control, noise generator and an ADSR envelope generator. Complete Kit

£150.00 + VAT

Hebot II

At a price that makes even a TV look expensive, Hebot provides an exciting introduction to computer control. Independent drive of the two wheels, flashing "eyes", two-tone horn and a retractable pen are directed by your micro-computer while four collision detectors relay information about the robot's environment. Complete Kit

£95.00 + VAT

Universal computer interface board kit

£11.00 + VAT

Robot Turtle

Digital Delay Line

Digital quality at an Analogue price! With this unit you can have Phasing, Flanging, ADT, Chorus, Echo and Vibrato at the touch of a button. In a steel cabinet suitable for 19" rack mounting.

Complete kit (400ms delay)

£179.00 + VAT

Parts for Extra 400ms delay (up to 3 can be added)

£19.50 + VAT

Genesis P101

With its own dedicated microprocessor or under the control of an external computer, the Genesis P101 simulates the operation of industrial robots at a mere fraction of their cost. With this robot, practical robotics experience is available without tying up valuable capital. *6-axis robot system kit

£1050.00 + VAT
£750.000 + VAT

Hydraulic robot arm

MicroGrasp

A real programmable robot arm at an affordable price. Five motors — four with servo control — are mounted directly on the axes they drive (no fiddly strings and pulleys!). The robot can be controlled by any microcomputer with an expansion bus. Robot kit with power supply

£215.00 + VAT

Universal computer interface board kit

£57.00 + VAT

Electric robot arm

Genesis P102

A sophisticated robot system with micro-processor control, two speed, double acting hydraulic operation and the option of external computer control. The P102 offers "hands-on" experience for robotics training, at a fraction of the cost of an industrial robot.

*6-axis robot system kit

£1476.00 + VAT

*system includes Robot, Processor Box and Teach Pendant.

NEW PROJECT

DOPPLER RADAR INTRUDER ALARM

See this months Practical Electronics

All kits are complete down to the last nut and bolt and are supplied with an easy-to-follow assembly handbook.

Write or phone for further details, stating which product(s) interest you.

Access/Visa cardholders may order by telephone to avoid delays.

Prices apply to UK only. Overseas customers - please contact our Export Department for the name and address of your local dealer. Allow 21 days for delivery. Offers subject to availability.

POWERTRAN

cybernetics Ltd.



Portway Industrial Estate,
Andover, Hants, SP10 3ET



Tel: 0264 64455

HUNDREDS OF NEW LINES



The amazing Maplin Catalogue is here again! The new edition is packed with hundreds and hundreds of new electronic components to bring you right up to date with all the latest developments. As all home constructors agree (and a good many professionals too) the Maplin Catalogue is the one essential piece of equipment they really need. And now with all our **prices on the page** the Maplin Catalogue is better value than ever.

On Sale From 10th November 1984.

Pick up a copy as soon as it's published at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).



Post this coupon now for your copy of the 1985 catalogue.
 Price £1.35 + 40p post and packing. If you live outside the U.K.
 send £2.40 or 11 International Reply Coupons.
 I enclose £1.75.

Name

Address

.....

.....

ET111/84

MAPLIN
 ELECTRONIC SUPPLIES LTD

Maplin Electronic Supplies Ltd. Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Tel: Southend (0702) 552911. • Shops at: 159-161 King Street, Hammersmith,
 London W6, Tel: 01-748 0926. • 8 Oxford Road, Manchester. Tel: 061-236 0281.
 • Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292.
 • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702-554000.
 • 46-48 Bevois Valley Road, Southampton. Tel: 0703-25831. All shops closed all day Monday.