

electronics today

INTERNATIONAL

JUNE 1985


£1.10



TIME






DOMAIN

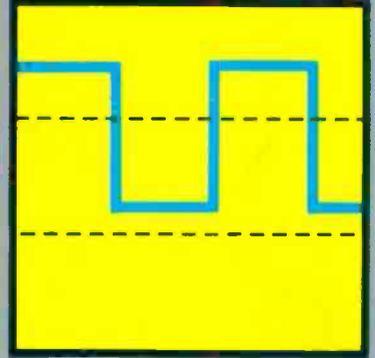

ANALYSIS —

Circuit Design On Your Home Micro

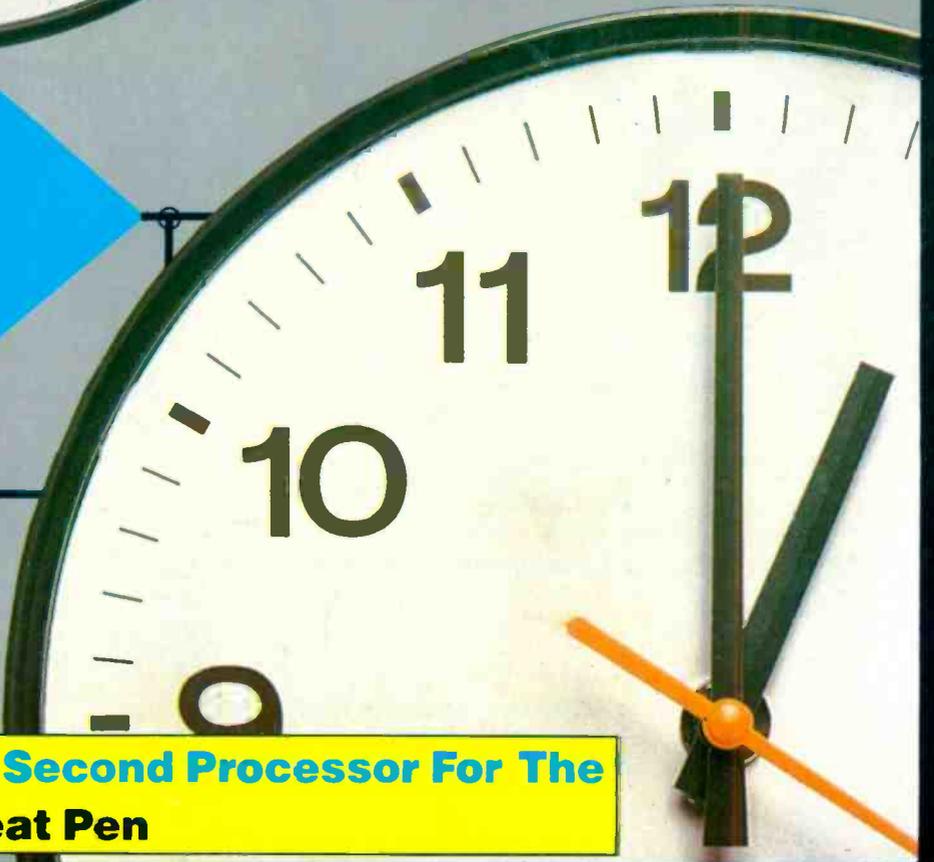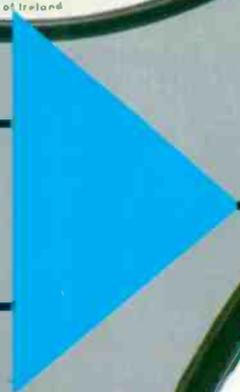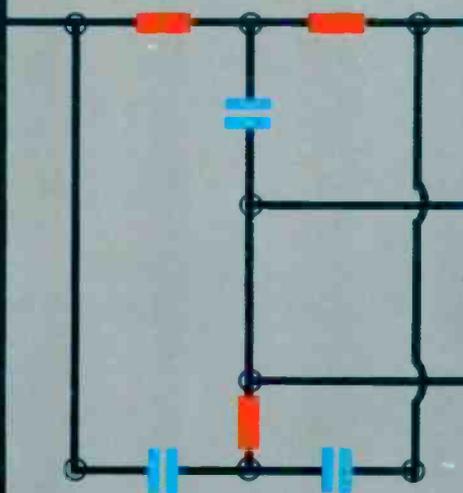

Plus:

Low Cost Audio Mixer Second Processor For The Acorn Electron The Heat Pen

LEARNING TOOLS


P101Mk2

The P101 Mk 2 Hydraulic Robot Arm offers unrivalled value for money in the field of educational robots. Either as a self-contained system or linked to an external micro, the P101 Mk 2 gives a realistic simulation of industrial robots. The P101 Mk 2's robust construction makes it an excellent basis for experimentation and general robotics research. Six-axis Robot System kit £1320 + VAT

P102Mk2

The two-speed Hydraulic Robot Arm is designed to provide "hands-on" experience in practical robotics courses. The Genesis P102 Mk 2 has most of the features of large industrial robots costing from 10 times the price. The P102 Mk 2 is supplied with its own micro-processor control system and remote control box. Alternatively an external microcomputer can be used to control the robot via its RS232C interface or parallel port. Complete Six-axis Robot System kit £1785 + VAT

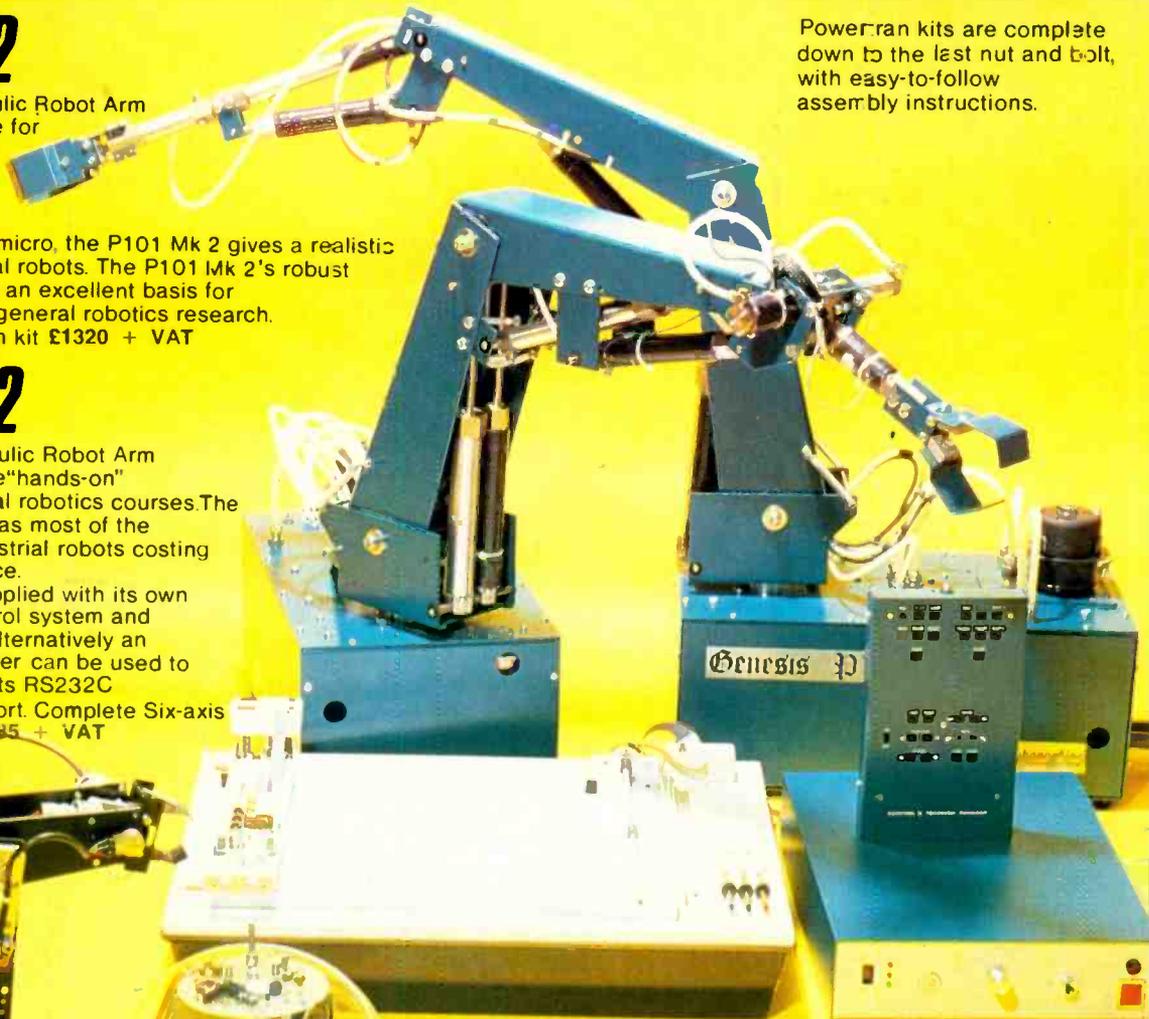Powertran kits are complete down to the last nut and bolt, with easy-to-follow assembly instructions.



Designed & produced by Mike Caring Advertising
Farnham 200211

POWERTRAN PLOTTER

Three-colour precision plotting on an A3 plane. This plotter is one of the most versatile peripherals that can be bought. Exchange the pen carriage for a router or a scriber for computer-controlled etching or machining. Available for BBC "B" or RML 380Z. £270 + VAT

MICROGRASP

A real programmable robot for the price of a printer! MicroGrasp has four servo-controlled axes and an independent gripper. The robot can be connected to most popular computers via special Powertran adaptors. Robot kit with power supply £215 + VAT
Universal interface board kit £60 + VAT

HEBOT II

With independent control of its two wheels, two-tone hooter, flashing "eyes", retractable pen and four-way collision detectors, Hebot provides an ideal introduction to computer control. Connects to most popular micros. Complete kit £85 + VAT
Universal computer interface board kit £11 + VAT

Access/Visa cardholders - save time - order by phone: 0264 64455.

POWERTRAN

CYBERNETICS LIMITED

Please send me the following kits _____

I enclose Cheque/Postal Order, value £ _____
(Don't forget to add V.A.T.)

Name _____

Address _____

To Powertran Cybernetics Limited, Portway Industrial Estate, Andover, Hampshire SP10 3ET

Please allow 21 days for delivery. Offers subject to availability. Prices apply to UK only, are exclusive of V.A.T. and correct at time of going to press. Overseas customers - please contact our Export Department.



electronics today

INTERNATIONAL JUNE 1985 VOL 14 NO 6

EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.
Telex 8811896.

FEATURES

- DIGEST**..... 7
Something old (the jokes), something new (the odd product or two), something borrowed (the rest of the jokes) and something blue (our sizzling expose of the goings-on at the Reader Survey competition draw). It's all in Digest this month.
- TIME DOMAIN ANALYSIS** 20
Andrew Armstrong describes a method of making performance calculations on circuit simulations which avoids the problems associated with frequency domain analysis and other approaches. Included
- are some practical examples in simple BASIC which can be tried on any home micro.
- THE REAL COMPONENTS** 25
John Linsley Hood continues his series on the ins and outs of electronic components with a look at some more semiconductor devices, proving that transistor design calculations really are as easy as EBC.
- TECH TIPS**..... 52
Not so much a tip, more a dead cert. ETI readers describe a few more winning ideas.

PROJECTS


- SECOND PROCESSOR FOR THE ACORN ELECTRON** 32
With John Wike's powerful add-on, the Electron can match the BBC 'B' for speed and beat it for memory. Build this second processor and let your Electron come first!
- LOW COST AUDIO MIXER** 38
John Linsley is best known for his ultra-high fidelity audio designs. There are times, however, when economy is more important than exotic performance, and this design, offers high quality at a surprisingly modest cost.
- UNIVERSAL EPROM PROGRAMMER MKII**..... 43
Following on from last month's article which described the theory and an upgrade for owners of the original design, Mike Bedford and Gordon Bennett present the complete MkII board.
- HEAT PEN** 48
Things to do with a battered Biro, or how a broken ball-pen can get you into hot water. Geoff Phillips describes a temperature measuring attachment for DVMs.

ETC

- REVIEWS**..... 59
Our resident bookworm has designs on two new titles this month.
- TRAINS OF THOUGHT** 60
Our new express service to bring you up to date with what's happening in the world of model electronics.
- OPEN CHANNEL**..... 61
Keith Brindley explains why the humble telephone will soon be taken to new heights.
- SCRATCH PAD**..... 65
Our regular diarist indulges in a little more back-biting.

INFORMATION

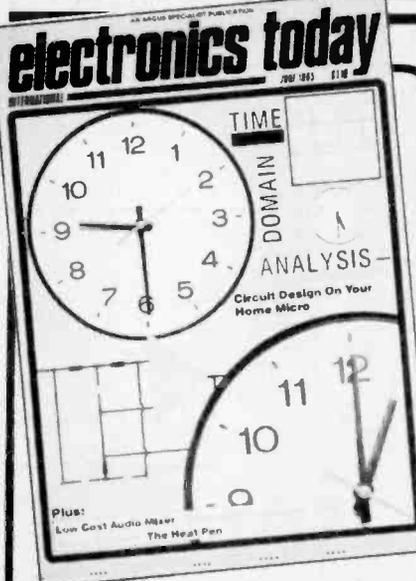- COUPONS** 24
NEXT MONTH'S ETI 30
READERS' SERVICES 51
- FOIL PATTERNS**..... 54
PCB SERVICE 58
ADVERTISERS' INDEX..... 66



Gary Herman: Editor
Ian Pitt: Assistant Editor
Jerry Fowler: Technical Illustrator
Paul Stanyer: Ad. Manager
Caroline Faulkner:
Classified Sales Executive
Kerry Fowler: Copy Control
Dave Bradshaw: Group Editor
— Electronics

Peter Welham: Publishing Director
Jim Connell: Chairman

PUBLISHED BY:
Argus Specialist Publications Ltd.,
1 Golden Square, London W1R 3AB.

DISTRIBUTED BY:
Argus Press Sales & Distribution Ltd.,
12-18 Paul Street, London EC2A 4JS
(British Isles)

TYPESET BY:
Design International

PRINTED BY:
The Garden City Press Ltd.

COVERS DESIGNED BY:
MM Design & Print.

COVERS PRINTED BY:
Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS

AUSTRALIA — Roger Harrison
CANADA — Halvor Moorshead
GERMANY — Udo Wittig
HOLLAND — Anton Kriegsman



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1985 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

■ Subscription Rates. UK £16.30 including postage. For further details and Airmail rates etc, see the Readers' Services page.

WATFORD ELECTRONICS

250 HIGH STREET, WATFORD, HERTS, ENGLAND, WD1 2AN

MAIL ORDER, CALLERS WELCOME

Tel. Watford (0923) 37774/40588 Telex. 8956095

ALL DEVICES FULLY GUARANTEED. SEND CHEQUE, P.O.S. CASH, BANK DRAFT WITH ORDERS. TELEPHONE ORDERS BY ACCESS/MASTER CHARGE ACCEPTED. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS OFFICIAL ORDERS WELCOME P&P added 75p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. **Ample Free Car parking space available.**

ELECTROLYTIC CAPACITORS: (Values in µF) 500V: 10µF 52¢, 77¢, 63V 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 8p 10 10p, 15 20 22p, 33 15p 47 12p, 68 20p, 100 19p, 220 20p, 1000 70p, 2000 99p, 50V: 60 20p, 100 17p, 220 24p, 40V: 22 9p, 33 12p, 47 13p, 100 16p, 220 20p, 1000 48p, 2200 9p, 25V: 1.5, 4.7, 10, 22, 47 8p, 100 11p, 150 12p, 220 15p, 330 22p, 470 25p, 680 100p, 1000 34p, 1500 42p, 2200 50p, 3300 76p, 4700 92p, 16V: 47, 68, 100 9p, 125 12p, 330 16p, 470 20p, 680 34p, 1000 27p, 1500 31p, 2200 26p, 4700 72p.

TAG-END CAPACITORS: 64V: 2200 120p, 3300 145p, 4700 245p, 50V: 2200 95p, 3300 155p, 40V: 4700 165p, 25V: 2200 70p, 3300 85p, 4000, 4700 75p, 10000 250p, 15000 270p, 16V: 22000 200p.

POLYESTER CAPACITORS: Axial Lead Type

400V: 1nF, 1.5nF, 2nF, 3nF, 4nF, 6nF 11p, 10n, 15n, 18n, 22n 12p, 33n, 47n, 68n 16p, 150n 20p, 220n 30p, 330n 42p, 470n 52p, 680n 1uF 68p, 2uF 82p, 1000V: 1nF 17p, 10nF 30p, 15n 40p, 22n 36p, 33n 42p, 47n, 100n 42p.

POLYESTER RADIAL LEAD CAPACITORS: 250V

10n, 15n, 22n, 27n 6p, 33n, 47n, 68n, 100n 8p, 150n, 220n 10p, 330n, 470n 15p, 680n 19p, 1uF 40p, 2uF 48p.

TANTALUM BEAD CAPACITORS

35V: 0.1µF, 0.22, 0.33 15p 0.47, 6.8, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180pF 15p each
10 20p; 16V: 2.2, 3.3 16p, 4.7, 6.8, 10, 12p; 15, 36p; 22 45p; 33, 47 50p; 100 95p; 10V: 1.5, 2.2, 26p; 33, 47 50p; 100 80p; 6V: 100 55p.

MYLAR FILM CAPACITORS

100V: 1nF, 2.4, 4nF, 10 8p; 15nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 9p; 50V: 470nF 12p.

CERAMIC CAPACITORS 50V:

Range 0.5pF to 10nF 4p, 15nF, 22nF, 33nF, 47nF, 5p, 100nF/300V 7p, 200nF/6V 8p.

POLYSTYRENE CAPACITORS:

10pF to 1nF 8p; 1.5nF to 12nF 10p.

SILVER MIC (Values in pF)

2.2, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180pF 15p each
20 20p, 25 20p, 27 20p, 30 20p, 33 20p, 39 20p, 47 20p, 50 20p, 56 20p, 68 20p, 75 20p, 82 20p, 85 20p, 100 20p, 120 20p, 150 20p, 180 20p, 200 20p, 220 20p, 250 20p, 270 20p, 300 20p, 330 20p, 360 20p, 390 20p, 400 20p, 450 20p, 500 20p, 560 20p, 600 20p, 630 20p, 680 20p, 720 20p, 750 20p, 800 20p, 850 20p, 900 20p, 950 20p, 1000 20p, 1100 20p, 1200 20p, 1300 20p, 1400 20p, 1500 20p, 1600 20p, 1700 20p, 1800 20p, 1900 20p, 2000 20p, 2100 20p, 2200 20p, 2300 20p, 2400 20p, 2500 20p, 2600 20p, 2700 20p, 2800 20p, 2900 20p, 3000 20p, 3100 20p, 3200 20p, 3300 20p, 3400 20p, 3500 20p, 3600 20p, 3700 20p, 3800 20p, 3900 20p, 4000 20p, 4100 20p, 4200 20p, 4300 20p, 4400 20p, 4500 20p, 4600 20p, 4700 20p, 4800 20p, 4900 20p, 5000 20p, 5100 20p, 5200 20p, 5300 20p, 5400 20p, 5500 20p, 5600 20p, 5700 20p, 5800 20p, 5900 20p, 6000 20p, 6100 20p, 6200 20p, 6300 20p, 6400 20p, 6500 20p, 6600 20p, 6700 20p, 6800 20p, 6900 20p, 7000 20p, 7100 20p, 7200 20p, 7300 20p, 7400 20p, 7500 20p, 7600 20p, 7700 20p, 7800 20p, 7900 20p, 8000 20p, 8100 20p, 8200 20p, 8300 20p, 8400 20p, 8500 20p, 8600 20p, 8700 20p, 8800 20p, 8900 20p, 9000 20p, 9100 20p, 9200 20p, 9300 20p, 9400 20p, 9500 20p, 9600 20p, 9700 20p, 9800 20p, 9900 20p, 10000 20p.

MINIATURE TRIMMERS CAPACITORS

2-60F 2-100pF 22p; 2-250F 5-65pF 30p; 10-88pF 36p.

RESISTORS Carbon Film, miniature, HI-Stab, 5%

RANGE Val 1-99 10p + 0.25W 202-10M E24 3p 1p 0.5W 202-4M E12 3p 1p 1W 202-10M E12 6p 4p 1/2 Metal Film 51Ω-1M E24 6p 4p 1% Metal Film 51Ω-1M E24 5p 4p 100+ type applies to Resistors of each type not mixed

RESISTORS NETWORK S.I.L.

7 Commoned (8 pins) 100Ω, 680Ω, 1K 2k, 4K, 10K 47K, 100K 25p
8 Commoned (8 pins) 150Ω, 180Ω, 270Ω, 330Ω, 1K, 2K, 4K, 7K, 10K, 22K, 47K, 100K 25p.

DIODES BRIDGE RECTIFIERS 75 SERIES

AA119	8		75107R	90
AA129	10	1A/50V	75110	90
AA130	10	1A/100V	75111	100
AA140	10	1A/400V	75121/2	130
BY100	15	1A/600V	75150	125
BY126	12	2A/50V	75154	125
BY127	10	2A/200V	75158	150
CR033	198	2A/400V	75159	195
DA1	10	2A/500V	75160	60
CAC47	19	6A/100V	75162	650
OA70	9	6A/400V	75182/4	90
OA79	10	10A/200V	75188/9	100
OA81	10	10A/600V	75322	140
OA85	10	25A/200V	75324	380
OA90	8	25A/600V	75325	20
OA91	8	BY164	75361/3	150
OA95	8		75365	90
OA200	8		75450	86
OA202	8		75451/2	52
IN914	4		75454	70
IN916	5		75491/2	65
IN4001/2	5			
IN4003	6			
IN4004/5	7			
IN4006/7	7			
IN4148	4			
IN5401	12	33V 1.3W		
IN5404	18			
IN5406	17	15p each		
IN5408	19			
IN544	9			
IN592	9			
6A/100V	40			
6A/400V	50			
6A/800V	60			

VARICAPS

BA102	50	16A800V	220
BB105B	40	25V500V	220
BB106	40	25A800V	290
BB109B	45	12800	125

SIEMENS pcb Type Miniature poly Capacitors

250V 1nF, 1n5, 2nF, 3n3, 4n7, 6n8, 10n, 15n, 22n, 27n 7p 33n, 39n, 47n 8p 56n, 150n 12p 82n, 100n 12p

100V 10n, 120n 10p 150n, 180n 12p 220n, 270n 15p 330n, 390n 20p 470n, 560n 26p 680n 30p 1uF 34p 2uF 50p

POTENTIOMETERS: Carbon Track, Rotary 0.25W Log & LIN Values.

470R, 1K & 2K (Linear only) Single Gang 35p 5K-2M Single Gang Log & Lin 35p 5K-2M Single Gang DP Switch 95p 5K-2M Double Gang 99p

SLIDER POTENTIOMETERS

0.25W log and linear values 60mm 5K-500K single gang 80p Graduated Bezels for above 45p

PRESET POTENTIOMETERS

0.1W Miniature Vertical or Horizontal, 100R to 4M3 8p 0.25W Larger 100R to 4M3 Horiz 12p 0.25W Larger 200R to 4M7 Vertical 12p

ACCESS

Just phone your orders through. We do the rest. Tel: 0923 50234

COMPUTER ICs

81LS95	175	RD-32513U	850
81LS96	175	8AAS050	875
81LS97	175	SFF9364	800
81LS98	175	SP0256	850
8202	225	SP0256A2	475
2102L	160	TC13101J	113
2114	275	MS2716-3V	725
2147	300	MS4047	100
2148	425	MS4164	395
2516	350	MS4162	395
2532	400	MS4166	250
2533	400	MS4500	512
2534	400	MS4532-3	300
2535	400	MS4532	600
2536	400	MS4533	600
2537	400	MS4534	600
2538	400	MS4535	600
2539	400	MS4536	600
2540	400	MS4537	600
2541	400	MS4538	600
2542	400	MS4539	600
2543	400	MS4540	600
2544	400	MS4541	600
2545	400	MS4542	600
2546	400	MS4543	600
2547	400	MS4544	600
2548	400	MS4545	600
2549	400	MS4546	600
2550	400	MS4547	600
2551	400	MS4548	600
2552	400	MS4549	600
2553	400	MS4550	600
2554	400	MS4551	600
2555	400	MS4552	600
2556	400	MS4553	600
2557	400	MS4554	600
2558	400	MS4555	600
2559	400	MS4556	600
2560	400	MS4557	600
2561	400	MS4558	600
2562	400	MS4559	600
2563	400	MS4560	600
2564	400	MS4561	600
2565	400	MS4562	600
2566	400	MS4563	600
2567	400	MS4564	600
2568	400	MS4565	600
2569	400	MS4566	600
2570	400	MS4567	600
2571	400	MS4568	600
2572	400	MS4569	600
2573	400	MS4570	600
2574	400	MS4571	600
2575	400	MS4572	600
2576	400	MS4573	600
2577	400	MS4574	600
2578	400	MS4575	600
2579	400	MS4576	600
2580	400	MS4577	600
2581	400	MS4578	600
2582	400	MS4579	600
2583	400	MS4580	600
2584	400	MS4581	600
2585	400	MS4582	600
2586	400	MS4583	600
2587	400	MS4584	600
2588	400	MS4585	600
2589	400	MS4586	600
2590	400	MS4587	600
2591	400	MS4588	600
2592	400	MS4589	600
2593	400	MS4590	600
2594	400	MS4591	600
2595	400	MS4592	600
2596	400	MS4593	600
2597	400	MS4594	600
2598	400	MS4595	600
2599	400	MS4596	600
2600	400	MS4597	600

LINEAR ICs

555Cmos	95				
702	75				
709C 8 pin	35				
71	48				
714 8 pin	18				
747C 14 pin	70				
748C 8 pin	130				
749C 8 pin	185				
800	158				
9400CJ	375				
ADC0808	1000				
FD1771	615	AY-1-1320	225		
FD1791	622	AY-1-5050	99		
FD1795	628	AY-1-5051	160		
FD2650	715	AY-1-6720	210		
68021	220	HD63A03PE14	AY-3-1270	730	
68030	375	HM6845SP	750	AY-3-1350	350
68040	375	HM6402	800	AY-3-8910	150
68050	375	MSB0800	1250	Booklet for	
68060	375	MC1488	100	AY-3-8910	150
68070	375	MC1489	100	AY-3-8912	500
68080	375	MC1490	100	AY-3-8913	600
68090	375	MC1491	100	AY-5-137A	600
68100	375	MC1492	100	AY-5-1350	366
68110	375	MC1493	100	CA3011	130
68120	375	MC1494	100	CA3012	175
68130	375	MC1495	100	CA3013	185
68140	375	MC1496	100	CA3014	275
68150	375	MC1497	100	CA3015	285
68160	375	MC1498	100	CA3016	300
68170	375	MC1499	100	CA3017	315
68180	375	MC1500	100	CA3018	330
68190	375	MC1501	100	CA3019	345
68200	375	MC1502	100	CA3020	

SWITCHES TOGGLE 2A 250V SPST 35DPP48p SUB-MINI TOGGLE SPST on/off 58p SPDT on/off 85p SPDT centre off 85p SPDT biased both ways 105p DPDT 6 tags 80p DPDT centre off 86p DPDT biased both ways 145p DPDT 3 positions on/off/on 185p 4-pole 2 way 220p SLIDE 250V: DPDT 1A 14p DPDT 1A c/off 15p DPDT 1A 13p PUSHBUTTON 6A with 10mm Button SPDT latching 150p DPDT latching 200p SPDT moment 150p DPDT moment 200p Mini Non Locking Push to Make 15p Push to Break 25p DIGITAL Switch Assorted Colours 75p each  GAS/SMOKE DETECTORS TGS812 or TGS813 £6 each	DIP SWITCHES (SPST) 4 way 85p; 6 way 80p; 8 way 85p; 10 way 125p (SPDT) 4 way 100p ROTARY SWITCHES (Adjustable Stop type) 1 pole/2 to 12 way; 2 pole/2 to 6 way; 3 pole/2 to 4 way; 4 pole/2 to 3 way 48p ROTARY: Mains DP 250V 4 Amp on/off 66p ROTARY: (Make+Switch) Make a multiway switch. Shifting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way + DP switch). Mechanism only 90p WAFERS: (make before break) to fit the above switch mechanism. 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6p/2 way 65p Mains DP 4A Switch to fit Spacers 4p. Screen 6p.	VEROBOARD 0.1in 2 1/2 x 3 1/2 85p SP105 5 1/2 x 5 110p 3 x 5 110p 3 1/2 x 5 125p 3 1/2 x 17 420p 4 1/2 x 17 590p Pkt of 100 pins 55p Spot face cutter 150p Pin insertion tool 185p VERO WIRING PEN + spool 380p Spare spool 75p Combs 8p FERRIC CHLORIDE 1 lb bag Anhydrous 195p + 50p p&p ULTRASONIC TRANSDUCER 40KHz 475 pr	VO Board 185p DIP Board 395p Vero Strip 95p PROTO DECS Veroblock 480p Euroboard 395p Euroboardboard 590p Bimboard 1 575p Superstrip S82 1350p DALO ETCH RESIST PEN Plus spare tip 100p	IDC CONNECTORS PCB with Pins Sirt Plugs latch Angle Female Pins Plug Female Card Edge 10 way 90p 99p 85p 120p 16 way 130p 150p 110p — 20 way 145p 166p 125p 195p 26 way 175p 200p 130p 240p 34 way 205p 236p 140p 320p 40 way 220p 250p 180p 340p 50 way 235p 270p 200p 395p 60 way — — 230p 495p	PANEL METERS FSD 60 x 46 x 35mm 0-50V 0-100A 0-500mA 0-1mA 0-5mA 0-10mA 0-50mA 0-100mA 0-500mA 0.2A 0.2A 0.25V 0.50V AC 0.300V AC 50V 490p each CRYSTALS 32.768KHz 100 100KHz 545 200KHz 370 455 455 1MHz 265 1.008M 275 1.28MHz 450 1.8MHz 200 1.8MHz 200 1.8432M 230 2.0MHz 225 2.4576M 200 3.12MHz 240 3.278M 150 3.5794M 98 3.6864M 300 4.0MHz 150 4.032MHz 290 4.1943M 100 4.433619M 100 4.608MHz 200 4.80MHz 200 5.0MHz 160 5.185MHz 300 5.2428M 390 6.0MHz 140 6.144MHz 140 6.355MHz 225 7.368MHz 200 7.7328MHz 250 7.68MHz 200 8.0MHz 150 8.089333M 395 9.86723M 220 9.00MHz 175 10.0MHz 200 10.24MHz 200 10.5MHz 250 10.7MHz 150 12.0MHz 150 12.528M 300 14.31814M 170 15.0MHz 170 16.0MHz 200 16.0MHz 180 18.432M 150 19.968MHz 150 20.0MHz 200 24.0MHz 170 24.930MHz 250 26.69M 150 27.648M 170 27.145M 180 38.6667M 240 48.0MHz 240 100.0MHz 295 116.0MHz 300	RELAYS Miniature, enclosed, PCB mount. SINGLE POLE Changeover RL-91 205R Coil, 12V DC, (10V to 19.5V), 10A at 30V DC of 250V AC 195p DOUBLE POLE Changeover, 6A 30V DC or 250V AC RL-100 53R Coil, 8V DC (5V to 9V) 190p RL-111 205R Coil, 12V DC (10V to 19.5V) 195p RL-114 740R Coil, 24V DC (22V to 37V) 200p ASTEC UHF MODULATORS Standard 8MHz 375p Wideband 8MHz 550p BUZZERS miniature, solid state, 6V, 9V & 12V 70p PIEZOE TRANSDUCERS PB2720 70p LOUDSPEAKERS Miniature, 0.3W-8 2in, 3 1/2in, 2 1/2in, 3in 80p 2 1/2in 400 64tor 800 80p 7" x 5" 8" 200p 8" x 5" 8" 250p			
ROCKER SWITCHES ROCKER 5A/250V SPST 28p ROCKER 10A/250V SPDT 38p ROCKER 10A/250V DPDT c/off 95p ROCKER 10A/250V DPST with neon 85p THUMBWHEEL Mini front mounting switches Decade Switch Module 275p B.C.D. Switch Module 295p Mounting Cheeks (per pair) 75p JUMPER LEADS (Ribbon Cable Assembly) Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 6 inches 185p 205p 300p 485p 12 inches 198p 215p 315p 480p 24 inches 210p 3235p 345p 540p 36 inches 290p 370p 480p 525p IDC Female Header Socket Jumper Leads 36 20pin 26 pin 34 pin 40 pin Single ended 180p 200p 280p 300p Double ended 290p 370p 480p 525p	EDGE CONNECTORS Low Wire 24 way — 110p Prot Wasp 2x12 way — 160p 8 pin 8p 25p 2x15 way — 165p 14 pin 10p 35p 2x18 way — 178p 16 pin 10p 42p 2x22 way 218p 250p 18 pin 16p 52p 2x23 way 175p — 20 pin 22p 65p 2x25 way 285p 275p 22 pin 22p 65p 2x28 way 190p — 24 pin 25p 70p 2x30 way 310p — 28 pin 28p 80p 2x36 way 360p — 40 pin 30p 90p 2x40 way 380p — SIL SOCKET 0.1" Pitch 20 way 65p ANTEX SOLDERING IRONS C15W 525p; CS17W 545p C18W 550p; XS25W 870p Spare Bits 85p; Elements 230p Iron Stand 175p; Heat Shunt 30p	EURO CONNECTORS Gold Plashed Contact DIN41617 170p — — 175p DIN41612 275p — 220p 285p DIN41612 295p — 240p 300p DIN41612 3 x 32 360p 385p 280p 385p DIL PLUG (Header) Solder IDC 14 pin 40p 90p 16 pin 48p 105p 24 pin 88p 178p 28 pin 290p 295p 40 pin 250p 255p RIBBON CABLE price per foot Grey Colour 10 way 15p 28p 40 way 40p 100p 20 way 30p 50p 24 way 40p 85p 28 way 55p 80p 34 way 60p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p DIL SOCKET 24 pin 575p 40 pin 695p	'D' CONNECTORS Male Solder lugs 55p 80p 120p 150p Angle pins 110p 175p 225p 300p PCB pins 100p 100p 160p 250p Female Solder lugs 90p 125p 180p 275p Angle pins 150p 200p 260p 390p PCB pins 100p 125p 185p 355p Covers 75p 70p 70p 85p IDC 25 way 'D' Plug 385p, Socket 450p 25 way 'D' CONNECTOR (RS232) Jumper Lead Cable Assembly 18" long, Single end, Male 475p 18" long, Single end, Female 510p 36" long, Double Ended, M/M 995p 36" long, Double Ended, F/F £10 36" long, Double Ended, M/F 995p	AMPHENOL PLUGS 24 way IEEE IDC Solder 485p 460p 36 way Centronics 450p 475p 36 way Female 460p 450p	TRANSFORMERS 3-0-3V; 6-0-6V; 9-0-9V; 12-0-12V; 15-0-15V @ 100mA 130p pcb mounting Miniature, Split Bobbin 3VA: 2x6V-0.25A, 2x9V-0.15A, 2x12V-0.12A, 2x15V-0.1A 235p 6VA: 2x6V-0.5A, 2x9V-0.3A, 2x12V-0.25A, 2x15V-0.2A 280p Standard Split Bobbin type: 6VA: 2x6V-0.5A, 2x9V-0.4A, 2x12V-0.3A, 2x15V-0.25A 260p 12VA: 2x4.5V-1.3A, 2x5V-1A, 2x9V-0.6A, 2x15V-0.4A, 2x20V-0.3A 345p (35p p&p) 24VA: 2x6V-1.5A, 2x9V-1.2A, 2x12V-1A, 2x15V-0.8A, 2x20V-0.6A 385p (60p p&p) 50VA: 2x6V-4A, 2x9V-2.5A, 2x12V-2A, 2x15V-1.8A, 2x20V-1.2A, 2x25V-1A, 2x30V-0.8A 680p (80p p&p) Specially wound for Multirail computer PSUs 50VA: Outputs +5V/5A, +12V, +25V, -5V, -12V at 1A 620p (60p p&p) 100VA: 2x12V-4A, 2x15V-3A, 2x20V-2.5A, 2x25V-2A, 2x30V-1.5A, 2x50V-1A 985p (175p) P&P charge to be added over and above our normal postal charge	VOLTAGE REGULATORS 1A TO220 Plastic casing +ve -ve 5V 7805 50p 7905 50p 12V 7812 50p 7908 60p 15V 7815 45p 7912 50p 18V 7818 45p 7915 50p 24V 7824 50p 7918 50p 30V 7830 50p 7924 50p 100mA TO92 Plastic package 5V 78L05 30p 79L05 50p 6V 78L06 30p — — 8V 78L08 30p — — 12V 78L12 30p 79L12 50p 15V 78L15 30p 79L15 60p ICL7660 248p RC4194 375p RC4195 160p LM309K 135p LM317K 250p LM323K 450p LM337 175p LM723 Var 30p 78S40 225p	SOLDERCON PINS Ideal for making SIL or DIL Sockets 100 pins 45p 500 pins 195p ALUM BOXES 3 x 2 x 1" 85p 4 x 2 1/2 x 1" 100p 4 x 2 1/2 x 2 1/2" 105p 4 x 4 x 2" 105p 4 x 4 x 2 1/2" 120p 5 x 4 x 1 1/2" 120p 5 x 4 x 2 1/2" 120p 5 x 2 1/2 x 1 1/2" 90p 5 x 2 1/2 x 2 1/2" 130p 6 x 4 x 2" 120p 6 x 4 x 3" 150p 7 x 5 x 3" 180p 8 x 6 x 3" 210p 10 x 4 x 3" 240p 10 x 7 x 3" 275p 12 x 5 x 3" 280p 12 x 8 x 3" 295p	ASTEC UHF MODULATORS Standard 8MHz 375p Wideband 8MHz 550p BUZZERS miniature, solid state, 6V, 9V & 12V 70p PIEZOE TRANSDUCERS PB2720 70p LOUDSPEAKERS Miniature, 0.3W-8 2in, 3 1/2in, 2 1/2in, 3in 80p 2 1/2in 400 64tor 800 80p 7" x 5" 8" 200p 8" x 5" 8" 250p	MONITORS ● ZENITH — 12" Green, Hi-Resolution Popular £66 ● MICROVITEC 1431, 14" Colour RGB Input, Connecting cable incl. £165 ● MICROVITEC 1451, 14" Medium resolution £237 ● KAGA 12", Med-res. RGB Colour, Has flicker-free characters. Ideal for BBC, Apple, VIC, etc. £225 (car £7) ● KAGA 12", As above but Hi-Resolution £310 (car £7) ● Connecting Lead for KAGA £5 Carriage £7 Securcor

CMOS	4072	25	4536	275
	4073	26	4538	80
4000	20	4075	25	4539
4001	25	4076	68	4541
4002	25	4077	25	4543
4006	70	4078	25	4548
4007	28	4081	25	4549
4008	60	4082	25	4553
4009	45	4085	80	4554
4010	45	4086	60	4555
4011	25	4093	37	4557
4012	35	4094	70	4558
4013	60	4095	95	4559
4014	60	4096	100	4560
4015	60	4097	275	4561
4016	40	4098	80	4562
4017	60	4098	80	4562
4018	60	4099	110	4566
4019	58	4160	95	4568
4020	80	4161	95	4569
4021	58	4162	98	4572
4022	67	4174	98	4580
4023	30	4175	105	4582
4024	50	4194	105	4583
4025	22	4408	850	4584
4026	90	4409	850	4585
4027	40	4410	725	4597
4028	50	4412	750	4599
4029	75	4415	590	40097
4030	35	4419	280	40098
4032	70	4422	770	40100
4033	130	4435	850	40101
4034	146	4440	900	40102
4035	70	4450	360	40103
4036	275	4451	350	40104
4037	115	4490	450	40105
4038	75	4500	385	40106
4039	280	4501	38	40107
4040	60	4502	60	40108
4041	57	4503	40	40109
4042	50	4504	99	40110
4043	42	4505	385	40114
4044	50	4506	100	40161
4045	110	4507	45	40163
4046	60	4508	130	40174
4047	60	4510	55	40175
4048	55	4511	55	40181
4049	38	4512	55	40182
4050	35	4513	150	40192
4051	70	4514	115	40193
4052	60	4515	115	40194
4053	60	4516	95	40195
4054	85	4517	275	40244
4055	85	4518	48	40245
4056	85	4519	32	40257
4057	1000	4520	53	40373
4059	435	4521	115	40374
4060	88	4522	125	45106
4061	500	4526	60	
4062	986	4527	65	
4063	85	4528	68	
4066	45	4529	150	
4067	245	4530	90	
4068	25	4531	130	
4069	25	4532	65	
4070	25	4534	400	
4071	25			

OPTO ELECTRONICS	LEDs with clips	10
	TIL209	14
	TIL211 GRN	14
	TIL212 Yel	14
	TIL230 2" Red	12
	2" Green, Yellow or Amber	14
	0.2" Bi colour	100p
	Red/Green	115p
	Green/Yellow	115p
	0.2" Tri colour	85
	Red/Green/Yellow	85
	Hi-Brightness Red	58
	High-Bi Green or Yel	68
	Flashing red	68
	0.2" red	55
	Square LEDs, Red, Green, Yellow	30
	Rectangular Stackable LEDs	80
	Red, Green or Yellow 18	18
	Triangular LEDs	18
	Red	18
	Green or yellow	22
	LD271 Infra Red	48
	SF205 Detector	118
	TIL32 Infra Red	52
	TIL78 Detector	55
	TIL38	50
	TIL100	75
	BARGRAPH, Red 10 segments	278
ISOLATORS	IL74	145
	ILD74	145
	IL074	275
	TIL11/2/4	70
	IL076 Darlington	135
	TIL117	125
	4N33 Photo Darlington	138
7 Segment Displays	TIL312 3" CA	120
	TIL313 3" CC	120
	TIL321 5" CA	140
	TIL322 5" CC	140
	TIL739/73	140
	DL704 3" CC	125
	DL707 3" CA	125
	FND357 Red	120
	FND507	130
	3" Green CA	150
	6" Green CA	215
	3" x 1 Red CA	150
	3" x 1 Green CA	150
	LCD 3 1/2 Digits	496
	LCD 4 Digits	530
	LCD 6 Digits	625
	Reflective Switch	225
	SLOTTED Optical Switch similar to RS Comp 1	295

COMPUTER CORNER

- EPSON RX80 Printer £209
- EPSON RX80 F/T Printer £219
- EPSON FX80 Printer £316
- EPSON FX100 Printer £429
- KAGA/TAXAN KP810 Printer £252
- KAGA/TAXAN KP910 Printer £339
- BROTHER HR15 Daisywheel £329

Cable for above printers to interface with BBC Micro £7

- TEX EPROM ERASER — Erases up to 25 Eproms. Has a built-in safety switch. £30
- SPARE UV Lamp Bulb

OMP POWER AMPLIFIER MODULES

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof


Supplied ready built and tested.



OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms. Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 360 x 115 x 72mm. PRICE £32.99 + £2.50 P&P



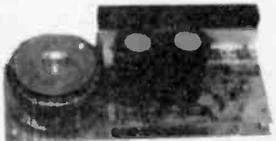OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £2.50 P&P



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. PRICE £62.99 + £3.50 P&P



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. PRICE £79.99 + £4.50 P&P

Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 LED diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P

NOTE Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order - Standard or P.A.



19" RACK CASED MOS-FET STEREO AMPLIFIERS with twin power supplies and LED Vu meters plus XLR connectors.

Three models (Ratings RMS into 4 ohms)
MF200 (100 - 100W) £169.00
MF400 (200 - 200W) £228.85
MF600 (300 - 300W) £274.85

Securicor Delivery £10.00

LOUDSPEAKERS

5 to 15 INCH Up to 300 WATTS R.M.S. All speakers 8 ohm Impedence.



POWER RANGE

8" 50 WATT R.M.S. Hi-Fi/Disco.
20 oz magnet, 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq 40Hz. Freq Resp. to 6KHz. Sens. 92dB. PRICE £10.99 available with black grille £11.99 P&P £1.50 ea.
12" 100 WATT R.M.S. Hi-Fi/Disco
50 oz magnet, 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq 25Hz. Freq Resp. to 4KHz. Sens. 95dB. PRICE £28.60 - £3.00 P&P ea.
15" 100 WATT R.M.S. Hi-Fi/Disco
50 oz magnet, 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq 20Hz. Freq Resp. to 2.5KHz. Sens. 97dB. PRICE £37.49 - £3.00 P&P ea.

McKENZIE

12" 85 WATT R.M.S. C1285GP Lead guitar/keyboards/Disco.
2" ally voice coil. Ally centre dome. Res. Freq 45Hz. Freq Resp. to 6.5KHz. Sens. 98dB. PRICE £24.99 - £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
Res. Freq 45Hz. Freq Resp. to 14KHz. PRICE £24.99 - £3.00 P&P ea.
15" 100 WATT R.M.S. C15 Bass Guitar/Disco.
3" ally voice coil. Die-cast chassis. Res. Freq 40Hz. Freq Resp. to 4KHz. PRICE £49.99 - £4.00 P&P ea.

WEM

5" 70 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq 52Hz. Freq Resp. to 5KHz. Sens. 89dB. PRICE £20.00 - £1.50 P&P ea.
8" 150 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq 48Hz. Freq Resp. to 5KHz. Sens. 92dB. PRICE £27.00 - £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1 1/2" voice coil. Res. Freq 35Hz. Freq Resp. to 4KHz. Sens. 92dB. PRICE £30.00 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1 1/2" voice coil. Res. Freq 35Hz. Freq Resp. to 4KHz. Sens. 94dB. PRICE £38.00 - £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)

5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 63Hz. Freq Resp. to 20KHz. Sens. 86dB. PRICE £9.99 - £1.00 P&P ea.
6" 150 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1 1/2" voice coil. Res. Freq 38Hz. Freq Resp. to 20KHz. Sens. 89dB. PRICE £12.99 - £1.50 P&P ea.

PANTEC HOBBY KITS.

Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £13.74 + 75p P&P
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82. Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.27 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position key operated fascia switch - off - test - armed 30 second exit and entry delay.

Indoor Alarm - Electronic swept freq siren. 104dB output.

Outdoor Alarm - Electronic swept freq siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £148.00 Usual Price £228.85

BKE's PRICE £79.99 + £4.00 P&P

? Why buy a collection of self assembly boards!

IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full Range 45Hz - 20KHz.
OMP 12/100 watts 20" x 15" x 12" £125.00 per pair
OMP 10/200 watts 18" x 15" x 11" £145.00 per pair
OMP 12/300 watts 20" x 15" x 11" £169.00 per pair

Delivery: Securicor £8.00 per pair



STEREO CASSETTE DECK



STEREO CASSETTE DECK
Ideal for installing into Disco and Hi-Fi cabinet/Consoles. Surface mounting (Horizontal). Supplied as one unit with all electronics including mains power supply.
* Metal top panel Black finish
* Piano type keys including pause
* Normal/Chrome tape switch
* Twin Vu Meters
* 3 Digit counter
* Slider Record Level control
Size 171 x 317 mm Depth 110 mm
PRICE £35.99 + £3.00 P&P


1 K-WATT SLIDE DIMMER

* Control Loads up to 1Kw
* Compact Size 4 3/4" x 1" x 2 1/2"
* Easy snap in fitting through panel/cabinet cut out
* Insulated plastic case
* Full wave control using 8 amp triac
* Conforms to BS800

* Suitable for both resistive and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.
PRICE £12.99 - 75p P&P (Any quantity)

BSR P295 ELECTRONIC TURNTABLE

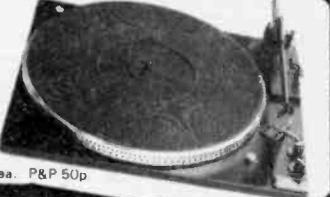
* Electronic speed control 45 & 33 1/3 r.p.m. * Plus/Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14V D.C. 65mA
Price £36.99 - £3.00 P&P



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p

PIEZO ELECTRIC TWEETERS MOTOROLA

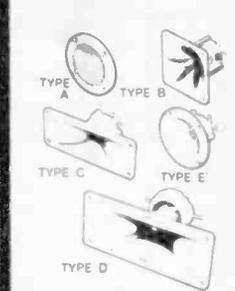
Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £5.39 each + 40p P&P
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm Price £3.99 + 40p P&P

STEREO DISCO MIXER

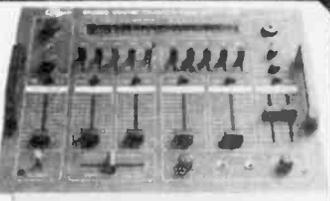STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment LED Vu Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following:
3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot L & R. Master Output controls. Output 775mV. Size 360 x 280 x 90mm.
Price £134.99 - £3.00 P&P



B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR TEL: 0702-527572

DIGEST

New Single-Chip Micro-computers


Hitachi have developed two 8-bit, CMOS, single-chip micro-computers. They are intended for use in low-end control applications and one includes integral EPROM to facilitate product development and low-volume production.

The HD6305V and HD63705V are available in 1.0, 1.5 and 2.0 MHz versions and have identical functions except that the HD63705V incorporates 4K of on-chip EPROM. They feature 4K of ROM, 192 bytes of RAM, 31 input/output ports and are com-

patible with the HD6305 family. Other features include an 8-bit timer with a 7-bit pre-scaler, a 15-bit timer which can also be used as a clock divider for serial communications interfacing and a synchronous serial communications interface. Typical power consumptions are 25mW in operation, 10mW in WAIT mode and 10uW in STOP And STANDBY modes. They are available in JEDEC-standard 40-pin DIL packages or in 54-pin flat packages.

The HD63705V has a window for ultra-violet erasing and uses 12.5V for programming. Hitachi expect it to find applications in development and initial production, allowing early samples of equipment to be produced without waiting for the permanent ROM to be prepared.

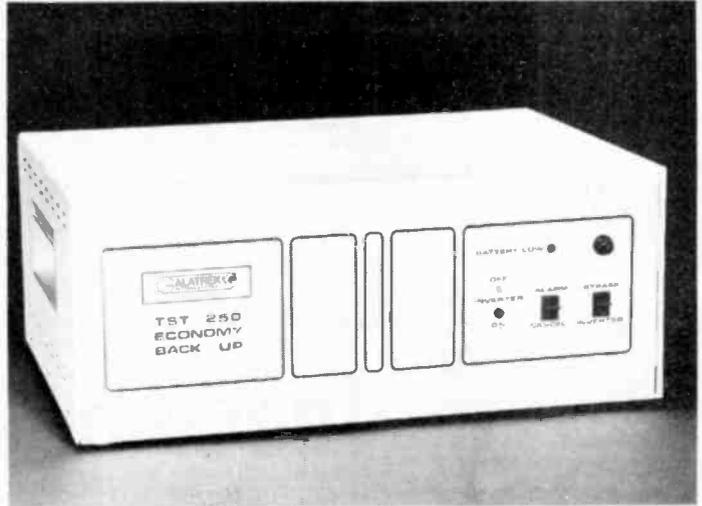The HD6305V is available now and the HD63705V should be available from May.



Uninterruptible Power Supply For Microcomputers

Galatrek have introduced a range of low cost Uninterruptible Power Supply (UPS) units which have been specially designed for the smaller and multiple micro-computer user at a price in proportion to the hardware. Three versions are available for 120, 250 and 500 VA outputs, and the prices start at £531.00.

The TST Range of UPS units can handle input voltage swings of +/- 15% and still maintain a stabilised, transient free output voltage, held within +/-5% on combined line and load variations. The wave form distortion is less than 5% and back-up power from the integral maintenance-free, lead acid batteries is normally a 20 minute cycle. However, simply by adding extra battery packs, the cycle can be extended to 24 hours and more if

required.

The series offers complete user flexibility which includes extending the frequency of the standard models from 50 HZ to 60 HZ or changing the 220/230 and 240 voltage of the standard range to 110 volts. A further special version is available which has an input voltage window variation in the range +15% to -30%.

The controls include a cancel switch for mains failure alarm and a manual by-pass switch for coping with high start-up loads. The battery discharge condition is indicated by an audible alarm and visual display which operates two minutes prior to discharge condition and shutdown.

Galatrek International Ltd, Scotland Street, Llanrwst, Gwynedd, North Wales LL26 OAL, tel: 0492-640311.



Just When You Thought It Was Safe To Open The Magazine Again . . .

ETI presents another in its series of cut-out-and-throw-away horror pics for the serious collector. Pictured above after yet another attempt to tidy his desk is former ETI editor Dave Bradshaw. Thankfully, Dave is still with us having been promoted to Group Editor. And the desk? Well, that's still around too and looking a lot tidier these days.

● Weald Electronics produce a range of specialist connectors which includes the BA, D2, SM, SMA, SMC and SREC series, along with the necessary assembly tools. The range is described in a sixteen page A4 illustrated catalogue which is available from their UK distributors, F.C. Lane (Components) Ltd, Slinfold Lodge, Horsham, West Sussex RH13 7RN, tel 0403-790200.

○ As from May of this year, the Health and Safety Executive will be making their database available to computer users in hour-long links via the services of Pergamon Infoline. The database contains information on industrial noise regulations, handling

of hazardous substances and over 6,000 other factors relating to work-place health and safety and the link-up is free. For details contact Pergamon Infoline Ltd, 12 Vandy Street, London EC2A 2DE, tel 01-377 4050.

● Canford Audio supply a wide range of mail order audio equipment, from tape recorders, mixers and amplifiers down to audio connectors, audio modules, rack-mounting and other cases, audio transformers, linear faders and cables. Their 72 page catalogue is available from the head office, Canford Audio Ltd, Stargate Works, Ryton, Tyne & Wear NE40 3EX, tel 091-413 7171.

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

RECHARGEABLE BATTERIES

Dry Fit Maintenance FREE by Sonnenschein.
A300 07191315 12v 3 AH same as RS 591-770 NEW £13.95 A300 07191202 6-0-6 1.8 AH same as RS 591-382 EX EQUIP £4.99 Miniature PCB mount 3.6v 100 Mah as RS 591-477 NEW £1.00 SAFT VR2C 1.2v "C" size NICADS in 18 cell ex equipment pack. Good condition - easily split to single cells £10.50 + pp £1.90

EX-STOCK INTEGRATED CIRCUITS

2732 ex equip £3.25, 27128 - 250Ns NEW £12.00.
6116-200 £4.50, 6116-250 £3.95,
6264LP-150 £22.00, 4164-200 £3.50, 4864-150 £4.00,
4116-300, £1.20, 2114 £1.75, 6800 £2.50, 6821 £1.00,
68A09 £8.00, 68B09 £10.00, 68B09E £14.50,
DB085AH-2 £12.00, DB086 £20.00, Z80A £2.99.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 9XU01 Dim 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.
GOULD JB-3AR Dim 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95
BUNLER 60.11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

BUDGET RANGE VIDEO MONITORS

At a price YOU can afford, our range of EX EQUIPMENT video monitors defy competition! All are for 240v working with standard composite video input. Units are pre tested and set for up to 80 col use on BBC micro. Even where MINOR screen burns MAY exist - normal data displays are unaffected.

1000's SOLD TO DATE

12" KGM 320-321, high bandwidth input, will display up to 132 columns x 25 lines. Housed in attractive fully enclosed brushed alloy case. B/W only £32.95
24" KGM large screen black & white monitor fully enclosed in light alloy case. Ideal schools, shops, clubs etc. ONLY £55.00 Carriage £10.00

DATA MODEMS

Join the communications revolution with our super range of DATA MODEMS with prices and types to suit all applications and budgets!

Most modems are EX BRITISH TELECOM and are made to the highest standard for continuous use and reliability. RS232 interfaces are standard to all our modems, so will connect to ANY micro etc. with an RS232 serial interface.

DATEL 2B see SPECIAL OFFER centre of this ad.

MODEM 13A, 300 baud. Compact unit only 2" high and same size as telephone base. Standard CCITT tones. CALL mode only. Tested with data. ONLY £45.00 + PP £4.50.

MODEM 20-1, 75-1200 baud. Compact unit for use as subscriber end to PRESTEL, MICRONET or TELECOM GOLD. Tested with data. £39.95 + PP £6.50.

MODEM 20-2, same as 20-1 but 1200-75 baud £99.00.

TRANSDATA 307A, 300 baud acoustic coupler. Brand new with RS232 interface. ONLY £49.95

OACOM DSL2123 Multi Standard Modem, switchable CCITT or USA BELL 103 standard. V21 300-300, V23 75-1200, V23 1200-75 or 1200-1200 half duplex.

Auto answer via MODEM or CPU. CALL or ANSWER modes plus LED status indication. Dim 2.5" x 8.5" x 9". BRAND NEW fully guaranteed ONLY £36.00 + PP £4.50.

DATEL 2412 Made by SE LABS for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol. Many features include Auto answer, 2 or 4 wire working etc. etc. COST OVER £800. OUR PRICE £185.00.

DATEL 4800, RACAL MPS4800 high speed good condition £285.00 CARR £10.00

HOT LINE DATA BASE

DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base 1000's of stock items and one off bargains. ON LINE NOW - 300 baud, full duplex CCITT tones. 8 bit word, no parity

01-679 1888

MAINS FILTERS

Cure those unnering hang ups and data glitches caused by mains interference.
SD5A As recommended by ZX81 news letter, matchbox size up to 1000 watt load £5.95
L2127 compact completely cased unit with 3 pin fitted socket Up to 750 watts £9.99



Anderson Jacobson

AJ810 VIDEO DISPLAY TERMINAL

Made by one of the USA's largest peripheral manufacturers the AJ510 Professional VDU terminal has too many features to include in space available - just a few are: internal Z80 cpu control, very readable 15" non glare green screen, 24 lines by 80 characters, 128 ASCII character set with lower case and graphics, standard RS232 interface, Cursor addressing, numeric key pad etc. Supplied in good TESTED second hand condition with full manual £225.00 + carr £10.00. Data sheet on request.

A Major company's over production problems, and a special BULK PURCHASE enable TWO outstanding offers.

COLOUR MONITOR SPECIALS

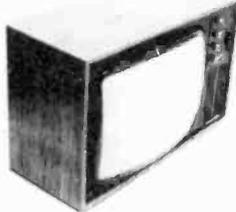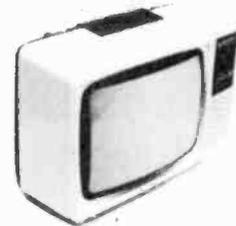

'SYSTEM ALPHA' 14" Multi Input Monitor.

Made in the UK by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future monitor requirements. Two types of video input, RGB and PAL Composite Video, allow direct connection to most makes of micro computers and VCR's. An internal speaker and audio amplifier may be connected to your system's output or direct to a VCR machine, giving superior colour and sound quality. Many other features include PIL tube, Matching BBC case colour, Major controls on front panel, Separate Contrast and Brightness - even in RGB mode, Two types of audio input Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc. etc.

This must be ONE OF THE YEAR'S BEST BUYS!!!

Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. SUPPLIED BELOW ACTUAL COST - ONLY £149.00 + Carr.

DECCA RGB 80-100 Monitor.

Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, combine with the tried and tested DECCA 80/100 series chassis to give 80 column definition and picture quality found only on monitors costing 3 TIMES OUR PRICE. In fact, WE GUARANTEE you will be delighted with this product, the quality for the price has to be seen to be believed. Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features include internal audio amp and speaker, Modular construction, auto degaussing 34 H x 24 D, 90 day guarantee. Supplied in EXCELLENT condition, ONLY £99.00 + Carr. Also available UN-MODIFIED but complete with MOD DATA. Only £75.00. Carriage and Insurance on monitors £10.00

SPECIAL 300 BAUD MODEM OFFER

Another GIGANTIC purchase of these EX BRITISH TELECOM, BRAND NEW or little used 2B data modems allows US to make the FINAL REDUCTION, and for YOU to join the exciting world of data communications at an UNHEARD OF PRICE OF ONLY £29.95. Made to the highest POST OFFICE APPROVED spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!

- 300 baud full duplex
- Full remote control
- CCITT tone standards
- Supplied with full data
- Modular construction
- Direct isolated connection
- CALL, ANSWER and AUTO modes
- Standard RS232 serial interface
- Built in test switching
- 240v Mains operation
- 1 year full guarantee
- Just 2 wires to comms line

NOW ONLY £29.95

Order now - while stocks last. Carriage and Ins. £10.00

SAVE £250 SUPER PRINTER SCOOP BRAND NEW CENTRONICS 739-2



ONLY £199

The "Do Everything Printer" at a price that will NEVER be repeated. Standard CENTRONICS parallel interface for direct connection to BBC, ORIC, ORAGON etc. Superb print quality with full pin addressable graphics and 4 type fonts plus HIGH DEFINITION internal PROPORTIONAL SPACED MODE for WORD PROCESSOR applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available ONLY from DISPLAY ELECTRONICS at the ridiculous price of ~~£499.99~~ £199.99 + VAT. Complete with full manual etc. Limited quantity - Hurry while stocks last. Options: interface cable (specify) for BBC, ORIC, DRAGON or CENTRONICS 36 way plg £12.50. Spare ribbon £3.50 each BBC graphics screen dump utility program £8.60. Carriage and Ins. £10.00 + VAT

HUNDREDS OF PRINTERS EX STOCK FROM £49.00. Call Sales Office for Details.

1 only large CALCOMP 1036 AO 3 pen drum plotter and offline 915 magtape controller. Good working order. ADD VAT TO ALL PRICES £2500.00.

EX STOCK

DEC CORNER

PDP 1140 System comprising of CPU, 124K memory + MMU 16 line RS232 interface, RP02 40 MB hard disk drive, TU10 9 track 800 BPI Mag tape drive, dual rack system, V752 VDU etc. etc. Tested and running £3750.00

BA11-MB 3.5" Box, PSU, LTC £385.00

DH11-AD 16 x RS232 DMA interface £2100.00

DLV11-J 4 x EIA interface £310.00

DLVII-E Serial Modem support £200.00

DUP11 Sych Serial data i/o £650.00

DQ200 Dialog - multi RK controller £495.00

D211-B 8 line RS232 mux board £650.00

KDF11-B MB189 PDP 1123+ £1100.00

LA36 Decwriter EIA or 20 ma loop £270.00

LAX34-AL LA34 tractor feed £85.00

MS11-JP Unibus 32 kb Ram £80.00

MS11-LB Unibus 128 kb Ram £450.00

MS11-LD Unibus 256 kb Ram £850.00

MSC4804 Obus (Equip MSV11-L) 256 kb £499.00

PDP11/05 Cpu, Ram, i/o, etc. £450.00

PDP11/40 Cpu, 124k MMU £1850.00

RT11 ver. 3B documentation kit £70.00

RK05-J 2.5 Mb disk drives £650.00

KLBJA PDP 8 async i/o £175.00

MIBS PDP 8 Bootstrap option £75.00

V750 VDU and Keyboard - current loop £175.00

V752 VDU with RS232 interface £250.00

1000's of EX STOCK spares for DEC PDP8, PDP8A, PDP11 systems & peripherals. Call for details. All types of Computer equipment and spares wanted for PROMPT CASH PAYMENT.

DISPLAY ELECTRONICS

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

32 Biggin Way, Upper Norwood, London SE19 3XF
Telephone 01-679 4414 Telex 894502 Data 01-679 1888



● International Rectifier have brought out a new edition of their power semiconductor product guide and data book. It includes a JEDEC/alpha-numeric index and covers thyristors, rectifiers and Schottky devices of up to 300A rating. Contact International Rectifier, Hurst Green, Oxted, Surrey RH8 9BB, tel 988-3215.


● Yes, Prime have moved to the middle of Nowhere (popularly known as Milton Keynes). The latest in a long line of companies who have decided to set up in the Land of the Concrete Cows, Prime will be spending £6 million on a new research and development centre which will bring 200 jobs to the city when it opens in 1988.

● Marathon Batteries Ltd have produced a small colour brochure describing their range of rechargeable nickel-cadmium cells. The capacities available range from 0.1 to 7 ampere hours and the brochure gives full details of their technical characteristics, construction and charge/discharge performance. For a free copy contact John Rich at Marathon Batteries Ltd, Union Street, Redditch, Worcestershire B98 7BW, tel 0527-62351.

● The Data Protection Registrar has published a 36 page, A5 booklet which provides an introduction and guide to the workings of the 1984 Data Protection Act. The first of a series of guidelines, it is intended to help those covered by the Act to assess its implications. Copies are available from the Office of the Data Protection Registrar, Springfield House, Water Lane, Wilmslow, Cheshire SK9 5AX, tel 0625-535777.

● Citec Ltd have produced a brochure which outlines the potential uses of cermet and polymer thick film technologies. It describes some of the work of the company in applying these technologies to a diverse range of problems, and copies can be obtained from the Product Manager, Special Products Group, BICC-Citetc Ltd, Cheney Manor, Swindon, Wiltshire SN2 2PZ, tel 0793-487301.

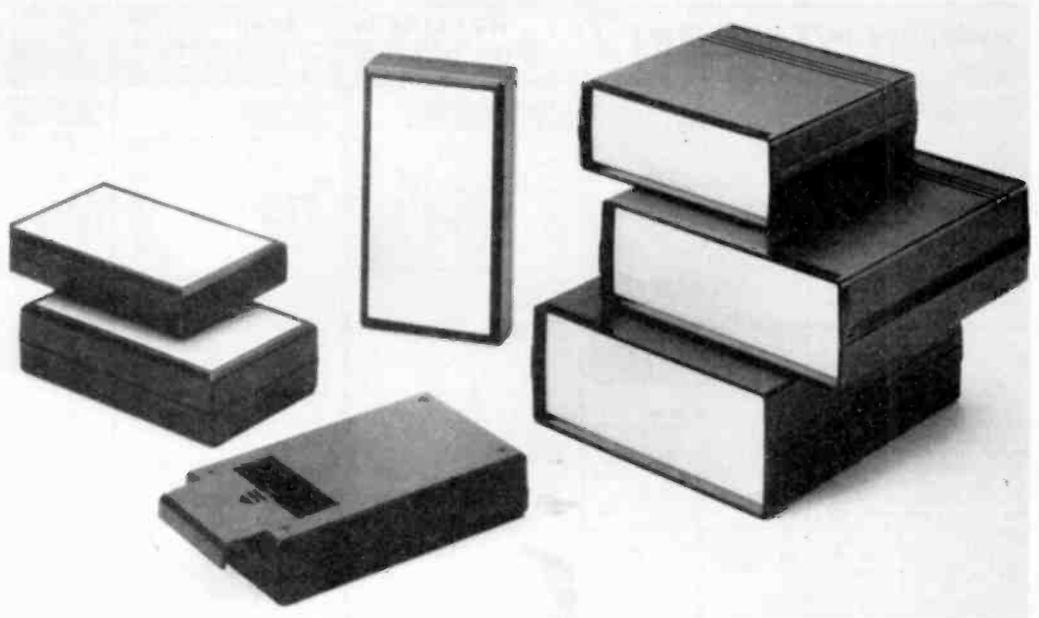● Over half of the workforce of Factron Schlumberger are giving up a day's holiday entitlement in aid of Ethiopia. The company, which makes test equipment and information management systems, employs over 400 staff at its headquarters in Dorset and the £5,000 raised will be used by Oxfam in Ethiopia, Sudan and Mali.



A, A, What's going in 'Ere Then?

West Hyde Developments have added two new designs to their range of small cases, one intended for hand-held application and the other for portable or bench-top equipment. The hand-held case incorporates a compartment for AA or PP3 batteries.

The Novara case comes in three sizes, all designed to fit comfortably into the hand. It is moulded from black ABS in two halves held together with self-tapping screws, and has an

aluminium front panel recessed into the moulding. The two larger sizes are available with an optional battery compartment which accepts either one PP3 battery or two AA cells.

The smallest Novara case measures 145 x 85 x 25mm and costs £5.98, the next size up measures 145 x 85 x 31mm and costs £6.80 or £6.96 with the optional battery compartment, and the largest size measures 145 x 85 x 37 and costs £7.61 or £7.78 with a battery compartment. All prices exclude VAT.

The bench-top case is called the Verona and is available in six sizes. It is moulded from either black or grey ABS in two halves which incorporate bosses to

support a board or chassis as well as slots to support PCBs vertically. The front and back panels are of aluminium and slot into recessed grooves.


The Verona comes in two standard width/depth combinations, each of which is available in three heights. The smaller sizes measure 134 x 129mm and are either 47, 54 or 61mm high, while the larger sizes measure 173 x 154mm and come in the same range of heights. Prices range from £3.60 to £6.22, excluding VAT.

West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Buckinghamshire HP20 1ET, tel 0296-20441.

Fast 8-Bit A/D Converter

Siemens have introduced an eight-bit analogue-to-digital converter which has a conversion time of just 10ns. The new IC will allow full 8-bit conversion at 100MHz, a task which previously required four ICs and used twice as much power.

The SDA 8010 replaces the earlier six-bit SDA 5200 and dissipates just one watt, compared with two watts for four SDA 5200s to achieve the same speed and word length. A complementary digital-to-analogue converter designated the SDA 8005 is also available and is a mirror image of the SDA 8010. The SDA 8005 can operate at up to 150MHz and both devices are compatible with ECL (emitter coupled logic). The SDA 8010 comes in a 24-pin DIL ceramic package.

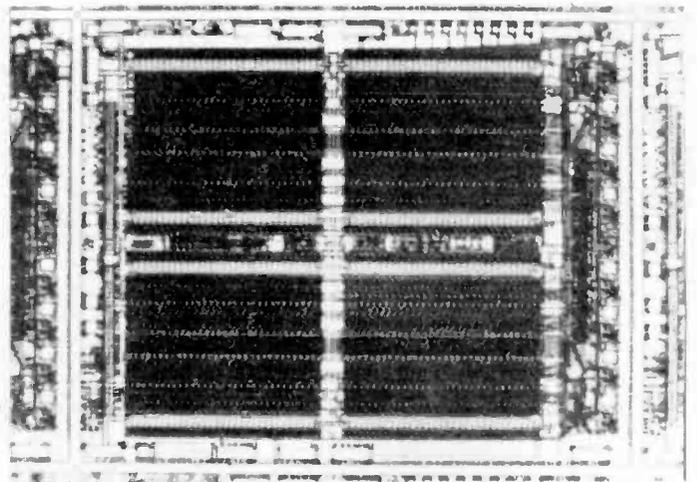

Siemens suggest applications for the new ICs in instrumentation, image processing and medical equipment including digital oscilloscopes, transient recorders, diagnostic equipment,

radar equipment and high resolution graphic systems. Siemens Ltd, Siemens House, Windmill Road, Sunbury-on-Thames, Middlesex TW16 7HS, tel 09327-85691.

Rapid Electronics

MAIL ORDERS:
Unit 1, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
Tel. Orders: Colchester (0206) 36412.
Telex: 987756.

ACCESS AND BARCLAYCARD WELCOME

MIN. D CONNECTORS

Plugs solder lugs	5p	15 wavy	25 way	37 way
Right angle	9p	13p	20p	150p
Sockets solderlug	80p	100p	135p	200p
Right angle	120p	180p	290p	420p
Covers	100p	90p	100p	110p



SOLDERING IRONS

Antex CS 17W Soldering iron	430
2.3 and 4.7mm bits to suit	85
Antex XS 25W soldering iron	530
3.3 and 4.7mm bits to suit	85
Solder pump desoldering tool	480
Spare nozzle for above	70
10 metres 22 swg solder	100
0.5kg 22 swg solder	750

CONNECTORS

DIN Plug Skt Jack Plug Skt	
2 pin 9p 9p 2.5mm 10p 10p	
3 pin 12p 10p 3.5mm 9p 9p	
5 pin 13p 11p Standard 16p 20p	
Phono 10p 12p Stereo 24p 25p	
1mm 12p 13p 4mm 18p 17p	
UHF (CB) Connectors:	
PL259 Plug 40p. Reducer 14p.	
SO239S square chassis skt 38p.	
SO239S round chassis skt 40p.	
IEC 3 pin 250V/6A	
Plug chassis mounting	38p
Socket free hanging	60p
Socket with 2m lead	120p

27128-250 £7.50

Brand new Hitachi product. Ideal for use with the BBC Micro. Please note this price is not a misprint!!

TRANSFORMERS

3VA PCB Mounting	
2x6V@0.25A, 2x9V@0.15A	
2x12V@0.12A, 2x15V@0.1A 180p	
6VA PCB Mounting	
2x6V@0.5A, 2x9V@0.4A	
2x12V@0.3A, 2x15V@0.25A 270p	
Standard Chassis Mounting	
6VA: 2x6V@0.5A, 2x9V@0.4A	
2x12V@0.3A, 2x15V@0.25A 240p	
12VA: 2x6V@1A, 2x9V@0.6A	
2x15V@0.4A, 2x20V@0.3A 350p	

VERO

Verobloc 395	
Veroboard Size 0.1 In matrix	
2.5 x 1	26
2.5 x 3.75	95
3.75 x 5	120
3.75 x 17	350
4.75 x 17	455
VO board	190
Veropins per 100:	
Single sided	55
Double sided	65
Spot face cutter	145
Pin insertion tool	185
Wiring pen	375
Spare spool 75p	Combs 6

SWITCHES

Submit toggle	
SPST 55p, SPDT 60p, DPDT 65p.	
Miniature toggle:	
SPDT 80p, SPDT centre off 90p.	
DPDT 90p, DPDT centre off 100p.	
Standard toggle:	
SPST 35p, DPDT 48p	
Miniature DPDT slide 14p.	
Push to make 15p.	
Push to break 22p.	
Rotary type adjustable stop:	
1P12W, 2P6W, 3P4W all 55p each.	
DIL switches:	
4SPST 80p, 6SPST 80p, 8SPST 100p.	
Min. DPDT slide 14p. Push-make 15p.	

MICRO

2716	310	6800	200	6522	330
2532	380	6118P3	390	6802	280
2732 one time programmable		6264P15	2250	6809	600
2734	280	4116P4	70	6810	140
2762	430	4126-15	480	6821	140
2764-250	430	4126-15 2850	6840	360	80251
2764 88C	430	Z80A CPU 290	6850	165	8253
		Z80A P10 320	6852	240	8255
		Z80A CTC 320	6875	500	8259
		Z80A S10 880	6880	100	MC1488
		Z80A DMA 880	6502	370	MC1489

SOCKETS

8 pin	7p	28p
34 pin	65p	45p
16 pin	10p	55p
18 pin	12p	60p
20 pin	13p	68p
22 pin	15p	75p
24 pin	17p	82p
28 pin	15p	95p
40 pin	25p	135p

Professional ZIF sockets
24 pin 430p 28 pin 480p
40 pin 595p

COMPONENT KITS

0.25W Resistor Kit. Contains 1000 0.25W 5% resistors from 4.7 ohms thru to 10M. Quantities depend upon popularity 1A. 10x10R, 30x407R, 30x10K, 25x470K. Just £7.90
Ceramic capacitor Kit. Total of 250 miniature ceramic capacitors from 22p to 0.1u. Just £6.90
Polyester capacitor Kit. Total of 110 miniature polyester capacitors from 0.01u to 0.47u. Just £6.90
Preset Kit. Total of 110 miniature preset resistors from 100R to 1M. Horizontal mounting type. Just £6.90
Radial Electrolytic Capacitor Kit. A pack containing a total of 93 miniature caps from 1u to 2200u. Just £7.50
Nut and Bolt Kit. Contains 800 assorted items. 100 each 6BA 1/4in, 1/2in, nuts and washers, 4B A 1/4in, 1/2in, nuts and washers. Just £3.20

LINEAR

IC7611	98	LM358	50	LM3916	265	NE567	130	TDA1024	115
555CMOS	80	ICL7622	190	LM370	210	LM13600	110	TL061	40
558CMOS	80	ICL8038	295	LM380	80	MC1310	150	NE871	370
709	36	LM8211A	220	LM392	150	MC1496	70	NE632	160
741	16	ICM7224	785	LM382	130	MC3302	75	NE534	265
748	35	ICM7555	80	LM384	140	MC3340	130	RC4136	65
AY31270	720	ICM7556	150	LM386	90	MF10CN	330	RC4558	40
AY38910	390	LF347	160	LM387	120	ML922	380	TL074	110
AY38912	430	LF351	160	LM390	60	ML924	290	TL082	50
CA3046	65	LF353	75	LM391	48	ML925	290	TL084	105
CA3096E	65	LM856	90	LM392	60	ML926	210	UA224Q	140
CA3098	200	LM100C	325	LM393	60	ML927	210	SN7429	250
CA3090AQ	375	LM301A	30	LM394	60	ML928	210	SP0256AL2425	ULN2003
CA3130E	85	LM311	45	LM395	60	ML929	210	Speech data 50	ULN2004
CA3140E	38	LM318	135	LM396	60	ML929	210	TL074	110
CA3160	95	LM324	45	LM397	60	ML929	210	TL074	110
CA3136	100	LM334	45	LM398	60	ML929	210	TL074	110
CA3180	260	LM335E	125	LM399	60	ML929	210	TL074	110
CA3240E	100	LM339	50	LM399	60	ML929	210	TL074	110
ICL7106	680	LM348	60	LM3914	265	NE566	140	TD1022	490

TRANSISTORS

AC126	35	BC158	11	BC568	10	BF808	23	2N1613	30	2N3906	10
AC126	30	BC158	10	BC569	10	BF808	23	2N218A	45	2N4037	45
AC127	30	BC159	10	BC570	16	BF820	30	2N219A	28	2N4058	10
AC176	25	BC168C	10	BC571	16	BF820	30	2N221A	25	2N4061	10
AC187	25	BC169C	10	BC572	16	BF820	30	2N222A	20	2N4061	10
AC188	25	BC170	8	BC573	16	BF820	30	2N222A	20	2N4061	10
AD142	120	BC171	10	BC574	16	BF820	30	2N222A	20	2N4061	10
AD161	42	BC172	8	BC575	16	BF820	30	2N222A	20	2N4061	10
AD162	42	BC173	16	BC576	16	BF820	30	2N222A	20	2N4061	10
AF124	60	BC178	18	BC577	16	BF820	30	2N222A	20	2N4061	10
AF139	40	BC182	10	BC578	16	BF820	30	2N222A	20	2N4061	10
AF186	70	BC182L	10	BC579	16	BF820	30	2N222A	20	2N4061	10
AF239	55	BC183	10	BC580	16	BF820	30	2N222A	20	2N4061	10
BC107	10	BC183L	10	BC581	16	BF820	30	2N222A	20	2N4061	10
BC107B	12	BC184	10	BC582	16	BF820	30	2N222A	20	2N4061	10
BC108	10	BC184L	10	BC583	16	BF820	30	2N222A	20	2N4061	10
BC108B	12	BC212	10	BC584	16	BF820	30	2N222A	20	2N4061	10
BC109	12	BC212L	10	BC585	16	BF820	30	2N222A	20	2N4061	10
BC109C	10	BC213	10	BC586	16	BF820	30	2N222A	20	2N4061	10
BC109D	12	BC213L	10	BC587	16	BF820	30	2N222A	20	2N4061	10
BC114	22	BC214	10	BC588	16	BF820	30	2N222A	20	2N4061	10
BC115	22	BC214L	10	BC589	16	BF820	30	2N222A	20	2N4061	10
BC117	22	BC237	7	BC590	16	BF820	30	2N222A	20	2N4061	10
BC119	35	BC238	7	BC591	16	BF820	30	2N222A	20	2N4061	10
BC137	40	BC308	10	BC592	16	BF820	30	2N222A	20	2N4061	10
BC139	38	BC327	8	BC593	16	BF820	30	2N222A	20	2N4061	10
BC140	29	BC328	8	BC594	16	BF820	30	2N222A	20	2N4061	10
BC141	30	BC337	8	BC595	16	BF820	30	2N222A	20	2N4061	10
BC142	28	BC338	12	BC596	16	BF820	30	2N222A	20	2N4061	10
BC143	30	BC477	22	BC597	16	BF820	30	2N222A	20	2N4061	10
BC147	10	BC478	22	BC598	16	BF820	30	2N222A	20	2N4061	10
BC148	10	BC479	22	BC599	16	BF820	30	2N222A	20	2N4061	10
BC149	10	BC517	20	BC600	16	BF820	30	2N222A	20	2N4061	10
BC157	11	BC547	5	BC601	16	BF820	30	2N222A	20	2N4061	10

BC548	10	BF804	23	2N1613	30	2N3906	10
BC549	10	BF808	23	2N218A	45	2N4037	45
BC567	10	BF820	30	2N219A	28	2N4058	10
BC568	10	BF820	30	2N221A	25	2N4061	10
BC569	10	BF820	30	2N222A	20	2N4061	10
BC570	16	BF820	30	2N222A	20	2N4061	10
BC571	16	BF820	30	2N222A	20	2N4061	10
BC572	16	BF820	30	2N222A	20	2N4061	10
BC573	16	BF820	30	2N222A	20	2N4061	10
BC574	16	BF820	30	2N222A	20	2N4061	10
BC575	16	BF820	30	2N222A	20	2N4061	10
BC576	16	BF820	30	2N222A	20	2N4061	10
BC577	16	BF820	30	2N222A	20	2N4061	10
BC578	16	BF820	30	2N222A	20	2N4061	10
BC579	16	BF820	30	2N222A	20	2N4061	10
BC580	16	BF820	30	2N222A	20	2N4061	10
BC581	16	BF820	30	2			

Events Diary

Surface Mounting Techniques & Packaging — May 9th

London west Hotel, West Brompton, London. Seminar organised by Hitachi on all aspects of surface mounting techniques and including question and answer session. Begins with lunch at 1.00 pm and runs until 5.15 pm. Cost is £25.00 inclusive. Contact Julie Richardson on 01-861 1414.

Unix Training Course — May 14/15th

Plessey Microsystems Training Centre, Towcester. Training in Unix system III or V, including hands-on experience using a Plessey System 68. Aimed at data managers and software staff interested in multi-user computer techniques. Contact Plessey Microsystems, Sales Office, Water lane, Towcester, Northamptonshire NN12 7JN, tel 0327 50312.

New IEE Wiring Regulations — May 14-16th

Production Engineering Research Association, Melton Mowbray. Three-day non-residential course on the 15th edition of the IEE Regulations. Cost is £300.00 plus VAT with reductions for participants from companies who are members of PERA. Contact the Booking Bureau, PERA Training, Melton Mowbray, Leicestershire LE13 0PB, tel 0664 64133.

Scottish Electronics Production Show — May 14-16th

Anderston Centre, Glasgow. Exhibition of the latest semiconductor and PCB production equipment, assembly equipment, inspection and test systems, interconnection systems, chemicals and laminates. Contact Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham TW1 3SZ, tel 01-891 5051.

Automated Manufacturing Exhibition & Conference — May 14-17th

NEC, Birmingham. Exhibition of industrial robotics and automated manufacturing systems. Contact Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham TW1 3SZ, tel 01-891 5051.

Power '85 — May 21-23rd

Metropole Hotel, Brighton. See February issue for details or phone 01-437 4127.

Gallium Arsenide Integrated Circuits — June 3rd

Royal Lancaster Hotel, London. Seminar covering gallium arsenide technology, circuit design and applications. Cost is £145.00 plus VAT and includes lunch, etc. Contact Miss Louise Marriott, Oyez Scientific and Technical Services Ltd, 3rd Floor, Bath House, 56 Holborn Viaduct, London EC1A 2EX, tel 01-236 4080.

Phone '85 — June 4-6th

Kensington Exhibition Centre, London. See February issue for details or phone 0280 815226.

Unix Training Course — June 11-12th

Plessey Microsystems Training Centre, Towcester. See above for details.

European Unix User Show — June 12-14th

Olympia 2, London. An exhibition designed to focus attention on the Unix system and attended by over 120 leading suppliers of Unix software, hardware, systems, peripherals and services. Contact EMAP International Exhibitions Ltd, Durrant House, 8 Herbal Hill, London EC1R 5JB, tel 01-837 3699.

Computers In Manufacturing Show — June 24-27th

Olympia 2, London. Exhibition and conference which aims to cover the use of computers in design, production engineering and manufacturing. Contact Independent Exhibitions Ltd, 154 Heath Road, Twickenham, Middlesex TW1 4BN, tel 01-891 3426.

Condition Monitoring In Hostile Environments — June 26th

Regent Crest Hotel, London. Seminar organised by ERA Technology and COMRAD which covers equipment monitoring techniques aimed at predicting failure and thus reducing downtime. Contact Terri Eccleston, Seminar Organiser, ERA Technology Ltd, Cleeve Road, Leatherhead, Surrey KT22 7SA, tel 0372 374151.

Leeds Electronics Show — July 3-5th

University of Leeds. The show is in its 22nd year and hopes to have 223 stands on display. Contact Evan Steadman Services Ltd, The Hub, Emson Close, Saffron Walden, Essex CB10 1HL, tel 0799 26699.



Readers' Survey Draw Results

At long last we have finished sifting through the several thousand completed Readers' Survey forms we received. A statistical analysis is being prepared and we plan to spend some time in the near future going through your comments and suggestions. We hope to present some of the results of all this effort in a short article in a forthcoming issue.

Meanwhile there is the matter of the free subscriptions we promised to the authors of the first ten survey forms drawn from a hat. We couldn't find a hat large enough, so with the forms securely placed in a cardboard box we carried out this important ceremony with due pomp and what little dignity we could muster.

Our handsome Classified Sales Executive Caroline Faulkner groped diligently around in the box until she could no longer avoid removing some of its contents while her lovely assistant, ETI Editor Garyherman (38-40-45") shook the box in an unhelpful manner. Assistant Editor Ian Pitt tried vainly to pretend to passers by that all this had nothing whatsoever to do with him while several hangers-on leapt around crying "lights, action," and so forth. The ceremony reached its climax with a brief competition to see who could throw most forms

in the air whilst doing the splits.

Somewhere in the midst of all this, ten forms were separated from the mass and passed to the subscriptions department where, with tears in their eyes, staff signed the necessary cash slips. The ten luck winners are:

A. Armstrong, 12 Grays Walk, Bishopmill, Elgin, Morayshire; L.C. Boothman, 35 Spalding Road, Fens Estate, Hartlepool, Cleveland; E. Habets, Gosperstreet, 47/4700 Eupen, Belgium; G. Hodgson, 2 Marlborough Avenue, High Harrington, Workington, Cumbria; M. Jones, 26 Whitchurch Avenue, Broadstone, Dorset; B.L. Marshall, 3 Blandford Road, Chilwell, Nottingham; A.J. Wills, 28 Cedar Drive, Kingsclere, Newbury, Berkshire; A. Woodroffe, 'Ranworth', The Glebe, Felbridge, East Grinstead, West Sussex; M. Woodward, 75 Nelson Road, Aston, Perry Barr, Birmingham; and J. LePirie, 72, City Way, Rochester, Kent.

These readers will all receive one year's free subscription beginning with this issue. Our commiserations to those who were not lucky enough to be picked but we will leave them with the thought that ETI is almost as enjoyable when paid for as when obtained free-of-charge.

● Rental Electronics have brought out their 1985 catalogue of electronic test equipment available on hire. The range extends from basic items through to the more exotic digital 'scopes, spectrum analysers, etc and even includes CAD/CAM/CAE equipment and 32-bit scientific computers. Rental Electronics Ltd, 7 Arkwright Road, Reading, Berkshire RG2 0LU, tel 0734-876377.

● Barry Porter's audio designs for ETI always prove popular but most constructors have difficulty getting hold of the radial non-polarised electrolytic capacitors he specifies. N.P. Electronics tell us that they stock a full range of Roederstein EKU non-polarised electrolytics and can offer kits of these components for Barry's recent designs at favourable

rates. Contact them at The Mill House, Watlington, Kings Lynn, Norfolk PE38 9DW, tel 0553-810096.

● Voluntary Service Overseas are looking for six people who hold a full City and Guilds, TEC, or other equivalent qualification to work in the Third World for two years. The posts are in Egypt, Sri Lanka, Belize, Kenya and on the Maldiv Islands and mostly involve teaching electronics or training others to maintain electronic equipment. Applicants should be between 23 and 65 and have British or EEC passports, and if posted will receive local rates of pay and free accommodation. Contact the Enquiries Unit, VSO, 9 Belgrave Square, London SW1X 8PW, tel 01-235 5191.

35" Colour Tube And Television

Mitsubishi have developed a colour television tube which measures 35" across the diagonal and is claimed to be the largest in the world. The tube will be used in a new 35" colour television set which will feature audio-visual and RGB inputs.

The tube is said to be the largest direct-view tube ever produced and offers a picture size previously achieved only by projection televisions. Computer simulation was used to optimise the distribution of glass thickness so as to achieve minimum weight and facilitate mass production. A de-

flexion angle of 110 degrees has been used which allows a fairly compact overall size to be achieved, and the complete television is 23" (580mm) deep and 36" (910mm) wide.

The screen area of the new tube is 3.1 times as large as that of a standard 20" television and Mitsubishi claim that the picture remains crisp and clean in spite of the large size. The television includes three sets of audio-visual inputs to permit connection of videocassette and videodisc machines and for the reception of satellite broadcasts and there is also an RGB input for teletext and personal computers.

For details contact the Peripheral Products Group, Mitsubishi Electric (UK) Ltd, Hertford Place, Denham Way, Maple Cross, Rickmansworth, Hertfordshire WD3 2BJ, tel 0923-770 000.



QL Monitor From Microvitec

Microvitec have produced a colour monitor which is designed both technically and visually to suit the Sinclair QL microcomputer and which includes a tilt and swivel stand. The monitor is aimed particularly at business users of the QL and is designed to satisfy the demand for a 'workstation' type display.

Microvitec were the first company to produce a colour monitor which was fully compatible with the QL's 85-column width display and also capable of doing full justice to the machine's colour graphics potential. The new mon-

itor retains the same technical specification, including a 653 pixel-per-line CRT and an 18MHz bandwidth. It has a black finish which matches the external appearance of the QL and the integral stand allows it to be angled to provide the most comfortable working position.

The QL-compatible monitor is expected to sell for just under £300,000. For further information contact the Sales Department, Microvitec PLC, Futures Way, Bolling Road, Bradford, West Yorkshire BD4 7TU, tel 0274-390011.

Passing The Backnumbers

Not before time, we have actually got around to clearing up the ETI office a bit. Amongst the rubble we have found a number of past issues of the magazine, mostly from 1983. Our regular backnumber service does not have the space to handle them, and as some are a bit worse for wear after kicking around in odd corners for so long it seems unfair to expect people to pay the normal £1.50 a time.

Accordingly, we have decided to make them available to readers in return for fifty pence to cover postage, etc. If you want any of the issues listed below, just write to us at the address given on the contents page and enclose a cheque or postal order made out to ASP Ltd. It would also save us time if you would enclose your address either on a gummed label or at least on a piece of ordinary paper

which we can then paste down.

By all means order more than one issue if you wish, but please don't enclose any other requests or enquiries; it would only slow things down. We won't be able to write out explanatory notes or anything, so if your cheque or postal order is returned you should assume that we have run out of copies of the issue you asked for.

The issues we have copies of are:-

NOVEMBER 1982; projects include the first part of the Cortex sixteen-bit computer, a precision pulse generator and a spectrum analyser, and there are features on satellite TV and switched capacitor filters.

JANUARY 1983; projects include the first part of the programmable stage lighting unit, the final Cortex article, a programmable bench power supply, a waveform

multiplier for synthesisers and an ADC for ZX81s or Spectrums, while the features include a review of the movie Tron and an article on operational amplifiers.

MARCH 1983; projects include the second part of the ETI Victory electronic organ, a user-defined graphics board for the ZX81, a 6502 sound board and a logic probe, while the features include a second look at satellite TV in the wake of the Part Report and articles on audio output stage design, broadcast standards and laser diodes.

APRIL 1983; projects include the third parts of both the stage lighting unit and the Victory organ, the first part of a ZX81 music board and a real time clock for 6502-based systems, and there are features on both switched mode power supplies and conventional PSUs and articles on voltage multipliers and the use of nested differentiating feedback loops (NDFLs) in audio amplifier design.

MAY 1983; projects include the


final parts of both the stage lighting unit, the Victory organ and the ZX81 music board, plus an audio compressor/limiter, a stabilised PSU for hi-fi amplifiers and a sixty watt amplifier designed using NDFL principles. The features include an eight-page buyer's guide to hi-fi and an article on four-channel semiconductor devices.

JUNE 1983; projects include the first part of a switched mode power supply design, a numerical keypad for the Acorn Atom and an electronic compass, and there are features on optoelectronics, buying test gear, and the fabrication of mechanical structures on silicon chips.

DECEMBER 1983; projects include the first part of Barry Porter's modular preamplifier, an EPROM controlled light chaser and a sixteen channel A-to-D board, while the features include articles on tone control design and machine code programming.

POWER AMPLIFIER MODULES

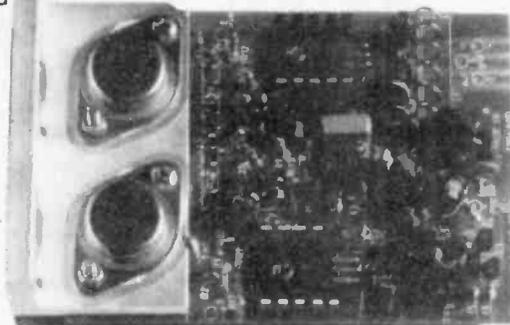After years of extensive tests and empirical research, Crimson have developed the ultimate in Bipolar Power Amplifier Modules, making the most sophisticated and highly protected modules available today.



- All of these modules now incorporate the following:
- HP Protection — Automatic shutdown to prevent damage from unstable signal source.
 - Thermal Protection — A Thermal Sensor which again causes the amplifier to enter the Shutdown Mode before any danger is reached.
 - Power Supply Protection — Diodes have been added to the P.C.B. to prevent reverse polarity damage.


MODULE	POWER/LOAD	V.A.T.	P&P	PRICE INC.
CE608	60	8Ω	£21.00	
CE1004	100	4Ω	£24.50	
CE1008	100	8Ω	£27.50	
CE1704	170	4Ω	£35.00	
CE1708	170	8Ω	£35.00	

Full details of our complete range including Power Supplies, Preamps, Mosfets etc available on large sae or contact our agents:

BRADLEY MARSHALL WILMSLOW AUDIOS
 382-386 EDGWARE RD 35-39 CHURCH ST
 LONDON WILMSLOW
 W2 1EB CHESHIRE

CRIMSON ELEKTRIK STOKE PHOENIX WORKS, 500 KING ST, LONGTON, STOKE-ON-TRENT, STAFFS. PHONE 0782 330520

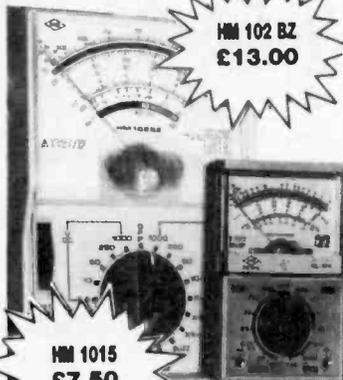AFFORDABLE ACCURACY QUALITY MULTIMETERS FROM ARMON



HM 102 BZ
 £13.00

HM 1015
 £7.50

ANALOGUE

- HM-102BZ 10ADC Range. 20KΩ/VDC, Buzzer, Battery Test Scale. £13.00
- 19 measuring ranges
- HM-102R Low end voltage & current ranges. Jack for Audio o/p Voltages. £11.00
- 20 measuring ranges
- HM-1015 Rugged. Pocket sized meter. for general purpose use. £7.50
- 16 measuring ranges
- Battery, Test Leads and Manual included with each model.

DIGITAL

- HC-6010 0.5% Accuracy. Standard Model £33.50
- HC-5010T 0.25% Accuracy. TR Test Facility £39.50
- All models have full functions and ranges and feature:
- 3 1/2 digit 0.5" LED display
- Low battery indication
- Auto zero & Auto polarity
- ABS Plastic Casing & Tilt Stand
- DC AC 10amp Range
- Overload Protection on all ranges
- Battery, Spare Fuse, Test Leads and Manual



HC 5010
 0.25% accuracy
 £36.50

HC 7030
 0.1% accuracy
 £39.50
 push button

FULL DETAILS ON APPLICATION FROM:- ARMON ELECTRONICS LTD

DEPT K HERON HOUSE, 109 WEMBLEY HILL ROAD, WEMBLEY, MIDDLESEX HA9 6AQ
 TELEPHONE 01-902 4321 TELEX 923965

PLEASE ADD 18% to your order for VAT. P&P Free of charge. Payment by cheque with order
 Offer applicable to mainland UK only


Trade enquiries invited

Please allow 28 days for delivery

1/2 PRICE LCD DMM WITH CARRY CASE

EXCLUSIVE WHILE STOCKS LAST

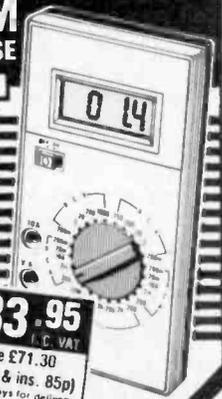
- 3 1/2 DIGIT ■ 26 RANGE
- AUTO ZERO ■ AUTO POLARITY
- AC/DC 10 AMPS ■ TEST LEADS, CARRY CASE, BATTERY & INSTRUCTIONS
- 5 ranges AC/DC volts 5 ranges AC/DC current
- 6 ranges Resistance to 20 meg ohms
- Size: 161 x 87 x 25mm



£33.95
 J.C. VAT
 List price £71.30
 (UK C/P & ins. 85p)
 Allow 10 days for delivery

AUDIO ELECTRONICS
 301 Edgware Road, London,
 W2 1BN 01-724 3564

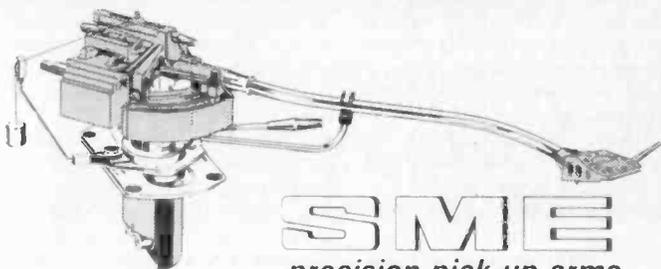ORDER BY POST OR PHONE OR CALL IN OPEN 6 DAYS A WEEK



Please call or write:
 SME Limited, Steyning, Sussex, BN4 3GY
 Telephone: 0903 814321 Telex: 877808 G

READ/WRITE

You Are Not Alone

Dear Sir,

1. In the Feb 1985 issue of ETI you make a lame excuse for not completing the long-delayed JLH article on his THD meter. Yet on pages 3, 26 and 29 you take up invaluable space with idiotic and vulgar rubbishy 'cartoons' unworthy of a reputable journal.

2. Your mix is about 10 to 1 in favour of computer items, some of them quite silly, over audio ideas. You must know that on our bookshop shelves there is a 20 to 1 preponderance of computer magazines both in England and South Africa. Why not yield a little more space for audio, particularly the brilliant JLH?

3. I wrote to you recently about Newrad's failure to supply my order for components for the JLH amplifier. A parcel arrived two weeks ago and I found that at least

25% of the items were missing, including the more expensive polycarbonate capacitors. I wrote again and I believe another package is on the way. Please don't use their 'activities' in ETI in the future.

Yours sincerely,
Dr. A.H. Barzilag
South Africa.

Well, that may be the first time we've been called reputable. We must be slipping. However, to answer your points in turn:

If you saw the March issue, you would realise that the final part of the THD meter project took up four full pages. The cartoons were not an alternative and, in any case, some people actually enjoy such things. Still, we can't please all the people all of the time — as your second point amply demonstrates. ETI's objective is to cover the whole field of electronics.

It's a big field and in any one issue we will not necessarily be able to get the mix precisely correct. Your figures

don't strike me as accurate, but it is undeniable that there is more interest in computer projects right now than in any other part of the electronics field. We reflect that, partly because the proportions apply to our contributors as much as to our readers. If we received more audio projects, we would probably run more audio projects. We do agree with you about John Linsley Hood, though, and we're quite pleased that his contributions to ETI are both frequent and substantial. Perhaps he likes the magazine more than you.

On the final point, we have received a number of complaints about Newrad's delivery of the Linsley Hood MOSFET amp. I've been in touch with the company and they assure me that any problems with the kit are now at an end. The trouble was partly due to necessary alterations in the design and partly to the long lead times for components. Newrad apologise for any inconvenience and ask that you do not phone up with any problems you may have, since this only creates more pressure on time. If you write to them, they will reply — but, they stress, everybody who has ordered a kit will receive a full kit. Delivery times should be acceptable from now on. Naturally, ETI also apologises to any readers who have had trouble with the kit. We can only say that the wait is definitely worth it.

ETI

Please
mention
E.T.I.
when replying
to all
adverts

If an advertisement
is wrong we're here
to put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

The Advertising Standards Authority. ✓

ASA Ltd, Dept 3 Brook House, Torrington Place, London WC1E 7HN

AUDIO ELECTRONICS

ALL ITEMS ON DISPLAY
OPEN 6 DAYS
A WEEK

SCOPES

(UK C/P & Ins. £6.00 or £15.00 secur/cont)

HAMEG All with Component Testers

HM203/5 Dual 20MHZ Bench **£303.60**

HM204/2 With Sweep delay **£419.75**

HM605 Dual 60MHZ **£592.25**

HITACHI (All models available) **£378.35**

V212 Dual 20MHZ

CROTECH All with Component Testers

3030 15MHZ Single Trace Portable **£216.20**

3035 Large Display Bench version **£239.20**

3132 Dual 20MHZ, Component Comparator, DC regulated outputs **£358.80**

PROBES

X1-X10 Scope Probes with adaptors **£11.50**

DIGITAL CAPACITANCE METER

(UK C/P 65p) Large LCD display 8 ranges 10.1pf to 2500 mfd **£69.50**

ANALOGUE MULTIMETERS

(UK C/P 55p)

NH56R 10K/volt 22 Range **£12.95**

102B2 20K/volt 22 Range 10A DC **£14.95**

YN360TR 20K/volt 19 Range plus Hfe test **£15.95**

5001 50K/volt Range doubler 10A DC/20M ohm **£21.95**

830A 30K/volt 26 Range 10A AC/DC 10 meg ohm **£24.95**

DIGITAL MULTIMETERS

(UK C/P 65p) (• With case)

•KD305 (S) 14 Range 10A DC 2M ohm **£29.80**

•KD615 (R) 18 range 10A DC 20 M ohm Hfe tester. **£39.95**

•KD 55C (R) 26 Range 10A AC/DC 20M ohm **£44.50**

3100 Pen type 16 range AC/DC volts, 20M ohm **£45.71**

•3510 (R) Range 10A AC/DC 20M ohm Hfe tester cont, buzzer **£46.52**

MES40 (R) Man/Auto 19 Range 10A AC/DC 20M ohm **£47.73**

LOGIC PROBES

(UK C/P 55p)

10 MHZ DTL/TTL/CMOS, LPI **£24.95.**

TRANSISTOR TESTER

(UK C/P 65p) Direct reading of Hfe and leakage for NPN/PNP transistors & diodes **£27.95**

DC POWER SUPPLIES

220/240 AC input (UK C/P £1.00)

1203 13.8 volt 3 Amp DC output (for all 12 volt DC equipment) **£12.95**

241 Meter indicator Amps/volts 0/30 volt 0/1 Amp **£37.95**

243 3 Amp version **£59.95**

ALSO IN STOCK - range of counters, generators and bench DMMs. Ask for leaflets.

ORDER BY POST OR PHONE OR CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS

301 Edgware Road, London W2 1BN

Tel: 01-724 3564

Complete Equipment Catalogue

Large save (25p UK)

Up to £1000 instant credit Available (Lombard Tricity Finance)

BBC Micro Computer System

ACORN COMPUTER SYSTEMS

BBC Model B Special offer.....	£300 (a)
BBC Model B+Econet.....	£335 (a)
BBC Model B+DFS.....	£346 (a)
BBC Model B+DFS +Econet.....	£399 (a)

UPGRADE KITS

A to B Upgrade Kit.....	£65 (d)
DFS Kit.....	£95 (d)
Econet Kit.....	£55 (d)
Speech Kit.....	£47 (d)

ACORN ADD-ON PRODUCTS

Z80 2nd Processor.....	£348 (a)
6502 2nd Processor.....	£175 (a)
Teltext Adaptor.....	£190 (b)
IEEE Interface.....	£282 (b)
Prestel Adaptor.....	£90 (b)
RH Light pen.....	£39.50 (c)

BBC FIRMWARE

1.2 Operating System.....	£7.50 (d)
Basic II ROM.....	£22.50 (d)
View Word Processor ROM.....	£48.00 (c)
Wordwise.....	£34.00 (d)
BCPL ROM/Disc.....	£52.00 (b)
Disc Doctor/Gremlin Debug ROM.....	£28 (d)
EXMON/TOOL KIT ROM.....	£28 ea (d)
Printmaster (FX80)/Graphics ROM.....	£28 ea (d)
ULTRACALC spreadsheet ROM.....	£89 ea (c)

COMMUNICATION ROM

Termi Emulator.....	£28 (d)
Communicator.....	£59 (d)
Commstar.....	£29 (d)

TORCH UNICON products including the IBM Compatible GRADUATE in stock. For detailed specification on any of the BBC Firmware/Peripherals listed here or information on our complete range please write to us.

PRINTERS

EPSON

RX80FT £225 (a) RX80T £215 (a) FX80 £315 (a) FX100 £435 (a)

KAGA TAXAN

KP 810 (80col) £225 (a) KP910 (156col) £349 (a)
JUKI 6100 £325 (a) BROTHER HR15 £325 (a)

ACCESSORIES

32K Internal Buffer Parallel £99 (b)

EPSON

Serial Interface: 8143 £28 (c); 8148 with 2K £59 (c)
Paper Roll Holder £17 (d); FX80 Tractor Attachment £37 (c)
Ribbons: FX/RX/MX80 £5 (d) FX/RX/MX100 £10 (d)
RX/FX80 Dust Cover £4.50 (d)

KAGA TAXAN

RS232 with 2K Buffer £85 (c) KP810/910 Ribbon £6.00 (d)

JUKI 6100

RS232 with 2K Buffer £65 (c) Ribbon £2.50 (d)
Tractor Attachment £99 (a) Sheet Feeder £180 (a)
BBC Parallel Lead £7 (d) Serial Lead £7 (d)
2000 Sheets Fanfold Paper with extra fine perforation
9.5" x 11" £13 (b) 14.5" x 11" £17.50 (b)
Labels per 1000's; single row 3 1/2" x 17/16" £5.25 (d)
Triple Row 27/16" x 17/16" £5 (d)

MODEMS

— All modems listed below are BT approved

MIRACLE WS2000:

The ultimate world standard modem covers all common BELL and CCITT standards up to 1200 Baud. Allows communication with virtually any computer system in the world. The optional AUTO DIAL and AUTO ANSWER boards enhance the considerable facilities already provided on the modem. Mains powered £129 (b). Auto Dial Board/Auto Answer Board £30 (c) each. (awaiting BT approval) Software lead £4.50.

TELEMOD 2:

Complies with CCITT V23 1200/75 Duplex and 1200/1200 Half Duplex standards that allow communications with VIEWDATA services like PRESTEL, MICRONET etc. as well as user to user communications. Mains powered £64 (b).

BUZZ BOX:

This pocket sized modem complies with V21 300/300 Baud and provides an ideal solution for communications between users, with main frame computers and bulletin boards at a very economic cost. Battery or mains operated, £82 (c). Mains adaptor £8 (d).

BBC to Modem data lead £7.

DISC DRIVES

These are fully cases and wired drives with slim line mechanisms of high quality, Shugart A400 standard interface. Drives supplied with cables manuals and formatting disc suitable for the BBC computer. TEAC 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format.

Single Drives

1 x 100K 40T SS TS55A.....	£85 (b)	1 x 400K 40/80TDS:TS55F.....	£125 (a)
PS100 with psu.....	£123 (b)	PS400 with psu.....	£149 (b)

Dual Drives:

Stacked Version:		Plinth Version:	
2 x 100K 40T SS TD200.....	£175 (a)	2 x 100K 40T SS TD200P.....	£195 (a)
PD200 with psu.....	£200 (a)	PD200P with psu.....	£220 (a)
2 x 400K 80/40T DS: TD800.....	£275 (a)	2 x 400K 80T DS TD800P.....	£295 (a)
PD800 with psu.....	£300 (a)	PD800P with psu.....	£315 (b)

3M 5 1/4" FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box.

40T SS DD £15 (c)	40T DS DD £18 (c)
80T SS DD £22 (c)	80T DS DD £24 (c)

DRIVE ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives.....				£14.50 (c)
Single Disc Cable.....	£6 (d)	10 Disc Library.....	Dual Disc Cable.....	£8.50 (d)
Case.....	£1.80 (c)	30 Disc Case.....		£6 (c)
40 Disc Lockable Box.....	£14 (c)	100 Disc Lockable Box.....		£19 (c)

MONITORS

MICROVITEC 14" RGB:

1431 Standard Resolution.....	£165 (a)
1451 Medium Resolution.....	£240 (a)
1441 Hi Resolution.....	£399 (a)
1431 AP Std Res PAL/AUDIO.....	£210 (a)
1451 AP Med Res PAL/AUDIO.....	£280 (a)
1451 DQ3 Med Res for QL.....	£239 (a)

Above monitors are now available in plastic or metal cases, please specify your requirement.

KAGA Super Hi Res Vision III RGB.....	£325 (a)
Hi Res Vision II.....	£225 (a)

MONOCHROME MONITORS 12":

Kaga Green KX1201 G Hi Res.....	£99 (a)
Kaga Amber KX1201 A Hi Res.....	£105 (a)
Sanyo Green DM8112CX Hi Res.....	£90 (a)
Swivel Stand for Kaga Monochrome.....	£21 (c)

All monitors are supplied with leads suitable for the BBC Computer. Spare leads available.

ATTENTION

All prices in this double page advertisement are subject to change without notice.

ALL PRICES EXCLUDE VAT
Please add carriage 50p unless indicated as follows:
(a) £8 (b) £2.50 (c) £1.50 (d) £1.00

SPECIAL OFFER

2764-25.....	£4
27128-25.....	£8
6264LP-15.....	£9

GANG OF EIGHT INTELLIGENT FAST EPROM COPIER

Copies up to eight eproms at a time and accepts all single rail eproms up to 27256. Can reduce programming time by 80% by using manufacturer's suggested algorithms. Fixed Vpp of 21 & 25 volts and variable Vpp factory set at 12.5 volts. LCD display with alpha moving message. £395 (b).

SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface. Softy II..... £195 (b)
Adaptor for 2764/2564. £25.00 (c)

UV ERASERS

All erasers with built in safety switch and mains indicator.
UV1 B erases up to 6 eproms at a time..... £47 (c)
UV1 T as above but with a timer..... £59 (c)
UV140 erases up to 14 eproms at a time..... £88 (b)
UV141 as above but with a timer..... £71 (b)

CONNECTOR SYSTEMS

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header	Edge	Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

No of Ways				
	9	15	25	37
MALE:				
Ang.Pins	120	180	230	350
Solder	60	85	125	170
IDC	175	275	325	-
FEMALE:				
St.Pin	100	140	210	380
Ang.pins	160	210	275	440
Solder	90	130	195	290
IDC	195	325	375	-
St.Hood	90	95	100	120
Screw	130	150	175	-
Lock	-	-	-	-

TEXTPOOL ZIF

SOCKETS	24-pin £7.50
	28-pin £9.00
	40-pin £12

EDGE CONNECTORS

	0.1"	0.156"
2 x 6-way (commodore)	—	300p
2 x 10-way	150p	—
2 x 12-way (vic 20)	—	350p
2 x 18-way	—	140p
2 x 23-way (ZX81)	175p	220p
2 x 25-way	225p	220p
2 x 28-way (Spectrum)	200p	—
2 x 36-way	250p	—
1 x 43-way	260p	—
2 x 22-way	190p	—
2 x 43-way	395p	—
1 x 77-way	400p	500p
2 x 50-way (S100conn)	600p	—

EURO CONNECTORS

DIN	Plug	Socket
2 x 32 way St Pin	230p	275p
2 x 32 way Ang Pin	275p	320p
3 x 32 way St Pin	260p	300p
3 x 32 way Ang Pin	375p	400p
IDC Skt A + B	—	400p
IDC Skt A + C	—	400p

For 2 x 32 way please specify spacing (A + B, A + C).

AMPHENOL CONNECTORS

	Solder	ZDC
36 way plug	500p	475p
36 way skt	550p	500p
24 way plug	—	—
IEEE	475p	475p
24 way skt	—	—
IEEE	500p	500p
PCB Mtg Skt Ang Pin	—	—
24 way 700p	36way 750p	—

GENDER CHANGERS

25 way D type	
Male to Male.....	£10
Male to Female.....	£10
Female to Female.....	£10

RS 232 JUMPERS

	(25 way D)
24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female Female	£10.00
24" Male Male	£9.50
24" Male Female	£9.50

DIL SWITCHES

4-way	90p	6-way	105p
8-way	120p	10-way	150p

TELEPHONE CONNECTORS

4 way plug	110p
6 way plug	180p
6 way rt.ang skt	160p
Flexible cable	
4 way	50p/m
6 way	72p/m

RIBBON CABLE

(grey/metre)			
10-way	40p	34-way	160p
16-way	60p	40-way	180p
20-way	85p	50-way	200p
26-way	120p	64-way	280p

DIL HEADERS

	Solder	IDC
14 pin	40p	100p
16 pin	50p	110p
18 pin	60p	-
20 pin	75p	-
24 pin	100p	150p
28 pin	160p	200p
40 pin	200p	225p

MISC CONNS

21 pin Scarf Connector	200p
8 pin Video Connector	200p

74 SERIES	
7400	30p
7401	30p
7402	30p
7403	30p
7404	30p
7405	30p
7406	40p
7407	40p
7408	30p
7409	30p
7410	30p
7411	30p
7412	30p
7413	30p
7414	30p
7416	30p
7417	40p
7418	30p
7419	30p
7420	30p
7421	60p
7422	30p
7423	30p
7424	30p
7425	40p
7426	40p
7427	40p
7428	40p
7429	40p
7430	30p
7431	30p
7432	30p
7433	30p
7434	30p
7435	30p
7436	30p
7437	30p
7438	40p
7439	40p
7440	40p
7441	40p
7442	40p
7443	40p
7444	110p
7445	110p
7446	100p
7447	100p
7448	120p
7449	38p
7450	38p
7451	38p
7452	38p
7453	38p
7454	38p
7455	38p
7456	38p
7457	38p
7458	38p
7459	38p
7460	38p
7461	38p
7462	38p
7463	38p
7464	38p
7465	38p
7466	38p
7467	38p
7468	38p
7469	38p
7470	38p
7471	38p
7472	38p
7473	38p
7474	38p
7475	38p
7476	38p
7477	38p
7478	38p
7479	38p
7480	38p
7481	38p
7482	38p
7483	38p
7484	38p
7485	38p
7486	38p
7487	38p
7488	38p
7489	38p
7490	38p
7491	38p
7492	38p
7493	38p
7494	38p
7495	38p
7496	38p
7497	38p
7498	38p
7499	38p
7500	38p

74LS SERIES	
74LS00	24p
74LS01	24p
74LS02	24p
74LS03	24p
74LS04	24p
74LS05	24p
74LS06	24p
74LS07	24p
74LS08	24p
74LS09	24p
74LS10	24p
74LS11	24p
74LS12	24p
74LS99	24p
74LS00	24p

74S SERIES	
74S00	50p
74S01	50p
74S02	50p
74S03	50p
74S04	50p
74S05	50p
74S06	50p
74S07	50p
74S08	50p
74S09	50p
74S10	50p
74S11	50p
74S12	50p
74S99	50p
74S00	50p

4008 SERIES	
4008	60p
4009	45p
4010	60p
4011	24p
4012	25p
4013	36p
4014	60p
4015	70p
4016	36p
4017	36p
4018	60p
4019	60p
4020	60p
4021	60p
4022	70p
4023	30p
4024	48p
4025	24p
4026	90p
4027	40p
4028	60p
4029	50p
4030	35p
4031	125p
4032	100p
4033	250p
4034	250p
4035	30p
4036	70p
4037	110p
4038	100p
4039	250p
4040	60p
4041	55p
4042	50p
4043	60p
4044	100p
4045	100p
4046	60p
4047	60p
4048	55p
4049	30p
4050	35p
4051	65p
4052	60p
4053	60p
4054	80p
4055	80p
4056	80p
4057	400p
4058	400p
4059	400p
4060	400p
4061	400p
4062	400p
4063	400p
4064	400p
4065	400p
4066	400p
4067	400p
4068	400p
4069	400p
4070	400p
4071	24p
4072	24p
4073	24p
4074	24p
4075	24p
4076	24p
4077	24p
4078	24p
4079	24p
4080	24p
4081	24p
4082	24p
4083	24p
4084	24p
4085	24p
4086	24p
4087	24p
4088	24p
4089	24p
4090	24p
4091	24p
4092	24p
4093	24p
4094	24p
4095	24p
4096	24p
4097	24p
4098	24p
4099	24p
4100	24p


VOLTAGE REGULATORS	
7805	50p
7806	50p
7807	50p
7900	50p

OTHER REGULATORS	
LM3090	50p
LM3091	50p
LM3092	50p
LM3093	50p
LM3094	50p
LM3095	50p
LM3096	50p
LM3097	50p
LM3098	50p
LM3099	50p
LM3100	50p
LM3101	50p
LM3102	50p
LM3103	50p
LM3104	50p
LM3105	50p
LM3106	50p
LM3107	50p
LM3108	50p
LM3109	50p
LM3110	50p
LM3111	50p
LM3112	50p
LM3113	50p
LM3114	50p
LM3115	50p
LM3116	50p
LM3117	50p
LM3118	50p
LM3119	50p
LM3120	50p
LM3121	50p
LM3122	50p
LM3123	50p
LM3124	50p
LM3125	50p
LM3126	50p
LM3127	50p
LM3128	50p
LM3129	50p

Interak 1

A METAL Z80A COMPUTER

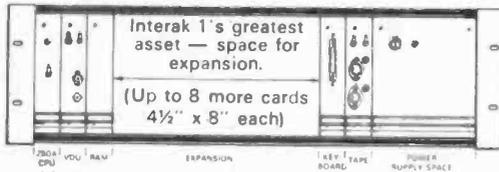Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips — not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from £10.95 to £17.75 + VAT; manuals £1 - £5.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletters etc. No fears about this one going obsolete — now in its fifth successful year! Send us your name and address with a 21p stamp and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work: Interak, Interak, Interak!

Greenbank

Greenbank Electronics (Dept T6E), 92 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391

pantechnic

■ design manufacture and supply

**POWER AMPLIFIERS
HIGH POWER ASSEMBLIES
CONTROL CIRCUITRY**

■ for application in

**INDUSTRY
PUBLIC ADDRESS
HI-FI**

■ available

**OFF THE SHELF
CUSTOMISED
C A D DESIGNED**

tel. 01.361.8715 132 High Road
telex 266 873 New Southgate
PANTEC G LONDON N11 1PG.



Full kit of parts to the above spec **£1699.00**

OR

Build the KBM at your leisure with the following sub assemblies:

(Pack 1) Main 8 slot xt board (tested and fully gtd).....	£490.00	(Pack 7) Keytronics Type keyboard	£139.00
(Pack 2) 130w Power supply complete	£150.00	(Pack 8) Speaker assembly	£10.50
(Pack 3) Multi I/O inc clock calendar, serial port floppy controller, light pen port etc.	£256.00	(Pack 9) Full cable kit.....	£25.00
(Pack 4) Colour graphics card (16 colour).....	£195.00	(Pack A) Hardware Kit (free with case assy).....	£10.00
(Pack 5) Metal case assembly complete	£112.00	(Pack B) 64K dram kit.....	£40.00
(Pack 6) 360k 40t Double sided disk drive (each).....	£145.00	(Pack C) Complete set of manuals	£45.00
		(Pack D) KBM BIOS (only available with main board).....	£55.00

The KBM Canary System Five will run ALL KNOWN IBM-PC-XT SOFTWARE and the system comes with A FULL 1 YEAR GUARANTEE AGAINST FAULTY PARTS. We offer a tele-support service for all our customers and a get you going policy should you have any difficulties.

All prices exclude V.A.T. and carriage as follows: All goods under £100.00 - £5.00. Goods over £100.00 - £10.00.

Education orders are catered for, Telephone for details. Access and Barclaycard are Welcome.

Contact: **KIRKLANDS BUSINESS SYSTEMS LTD, KIRKLAND HOUSE,
27 CITY ROAD, STOKE-ON-TRENT ST4 1DH OR WRITE TO
KIRKLANDS BUSINESS SYSTEMS - FREEPOST - STOKE ON TRENT ST4 1BR
Telephone (0782) 414333 or 415787 now.**

KIRKLANDS BUSINESS MACHINES

Now available for the first time in kit form in the U.K. the fabulous new KBM Canary System Five IBM-Compatible computer

Specifications:

Full IBM-XT Compatibility
8 slot main board dual 360k Teac drives
Colour card
Multi I/O card
128k RAM as standard (upto 1Mb)
8k BIOS — XT compatible
130w Power supply
Metal case assembly
1 Year warranty

Digital & Micro ELECTRONICS


An Argus Specialist Publication

£2.50

Four Channel Power Controller

**Sound To Light
Interface**

**BBC Screen
Handling**

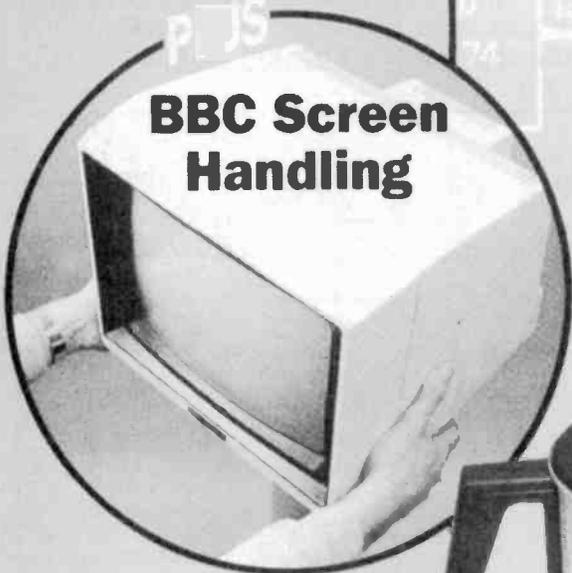


MSX Clock/Diary

Universal A/D

**Data Security
Techniques**

**Assembly
Language**

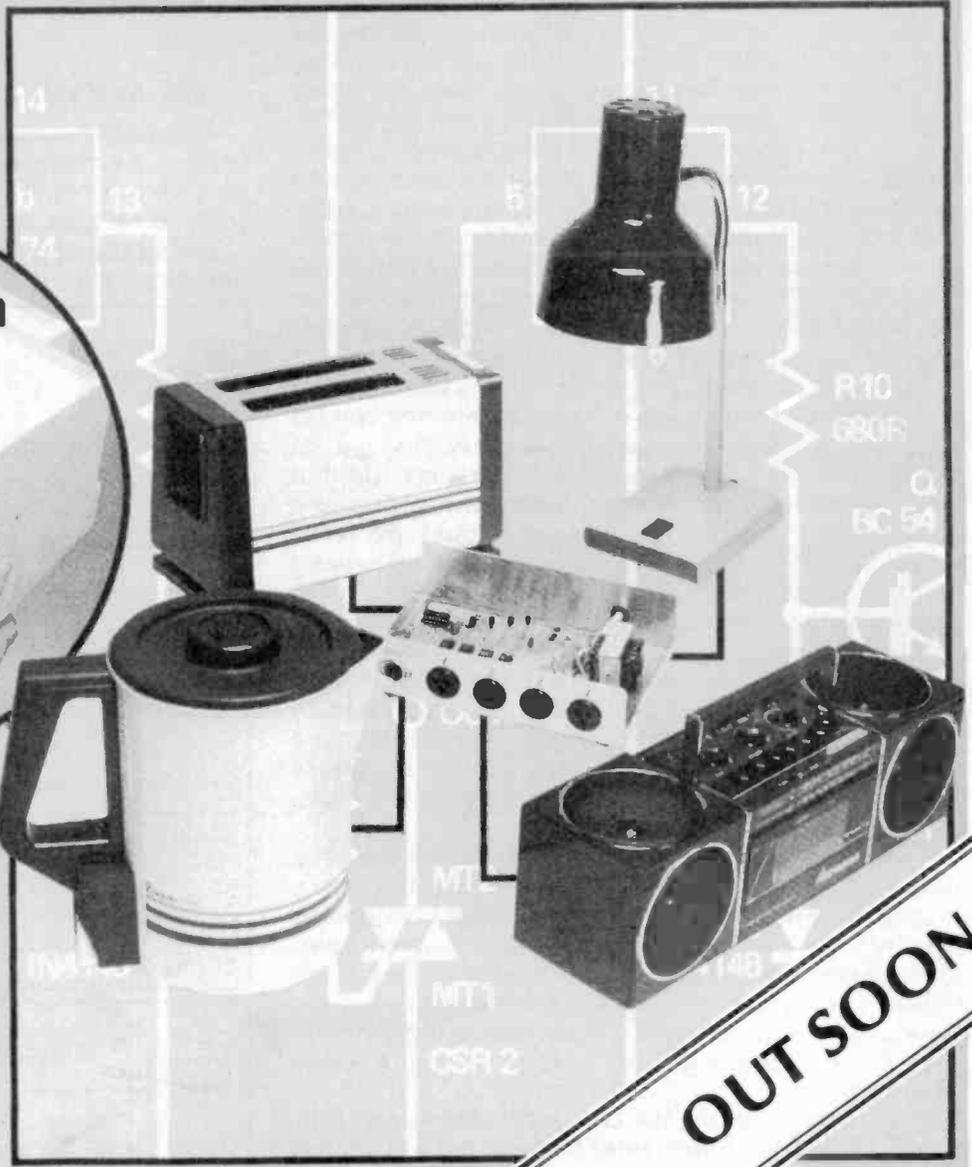

OUT SOON

TIME DOMAIN ANALYSIS

Let your computer do the work after reading Andrew Armstrong's introduction to circuit simulations using BASIC.

There have been complicated and expensive circuit analysis software packages available for some time. Time domain analysis, however, is a simple technique which can be used in BASIC programs on a home computer to analyse circuit performance. The simplicity is due to the fact that analysis is carried out in the time domain rather than the frequency domain.

Frequency domain analysis means calculating the frequency response, and perhaps the phase response, of a linear circuit. The problem is that, even for a very simple-looking circuit, the equations describing the frequency response may be very complicated. Usually, though, the DC behavior of the circuit can be calculated much more easily. What this time domain analysis technique does is to use DC equations for circuit performance, and to apply these equations repetitively at small increments of time. Any required input waveform can be specified as a function, or as a set of data points giving the input voltage at each increment of time.

During each time increment, it is assumed that currents and voltages are constant, while new values for these quantities are calculated. In the first part of the circuit in Fig.1, for example, the charging current of C1 is assumed to be constant during the entire time increment. In reality, the current would decrease steadily as the capacitor charged, so the calculated increase in the charge on the capacitor is greater than the true value. Clearly, the greater the time period, the greater the error. For this reason, a very small time increment is used, and some circuit configurations are analysed using several steps of calculation (ie several time increments) for each point plotted. In effect, time domain analysis involves the integration of equations by numerical approximation. Since they are DC equations, things are relatively simple.

There are a number of circumstances where time domain response is more meaningful than frequency response, of which one obvious example is video. For example, if a low pass filter produces rings and ripples in a square wave signal rather than rounding it off cleanly, those rings will show on the screen - yet the frequency response of the circuit producing the rings may be identical to that of one giving a clean rounding.

Of course, given that the computer time is available, there is no reason not to carry out frequency response analysis by time domain methods. This transfers the


burden of repetitive calculation to the computer rather than the programmer, so that the circuit designer can devote his or her time to thinking about circuit configurations rather than trying to solve equations using complex numbers, which require a piece of paper turned sideways just to write. (And that's only a second order low pass filter!)

DC Analysis

Taking the example of a passive RC low pass filter as in Fig.1, the method of writing the program is, first of all, to write a set of DC equations. These must be chosen so as to be able to be calculated sequentially.

Taking the circuit of Fig.1 as the first example, the equations are:

Fig.1 Low pass filter network.

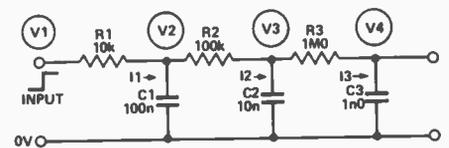


```

10 ' Analogue circuit analysis program - MAIN PROGRAM
20 ' Andrew Armstrong 06 February 1985
30
40 ' MAIN (i.e. CLS) Select and clear graphics screen
50 ' Draw grid for graph
60 ' Draw axes
70 ' Draw axes
80 ' Draw axes
1000 ' Draw axes

```

Listing 1

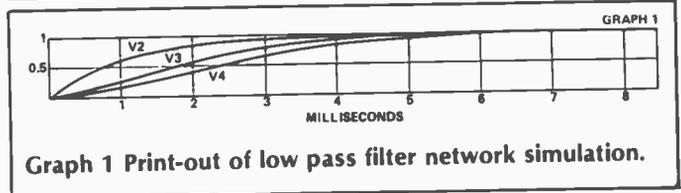

Graph 1 Print-out of low pass filter network simulation.

FEATURE: Time Domain Analysis

$$I1 = (V1 - V2) / R1$$

$$V2 = (I1 - I2) * T / C1$$

and similarly for the second and third parts of the circuit:

$$I2 = (V2 - V3) / R2$$

$$V3 = (I2 - I3) * T / C2$$

$$I4 = (V3 - V4) / R3$$

$$V4 = (I3 - I4) * T / C3$$

The input waveform, V1, is any arbitrary function which is convenient to generate in software. In this case a simple step is used to demonstrate time delay.

A BASIC program to calculate this is shown in Listing 1, and its print out in Graph 1. The number of steps in the loop is set to be suitable given the response time of the circuit in question. Equally, the value used for V1 is set by the Y scale required, though it would be just as simple to use the value 1 and then scale the answer later on in the program.

The only formulae needed to generate these equations are Ohm's law, and the formula for the change in voltage on a capacitor subjected to a steady current for time T: $V = I * T / C$. In each small time increment for computing purposes, the current is assumed to be constant, and the change in voltage is added to the previous total. The initial condition used in this program is that all currents and voltages are 0, which is the default condition of the dialect of BASIC in use here.

The shape of the graph showing the response to the input waveform is of interest in that it shows a distinct difference from the exponential charging characteristic of a single R and C. If many stages are added, the

result will look like Graph 2 in which a single RC time constant is shown for comparison. In this graph, it is assumed that the current drawn from each RC stage by the succeeding one is negligible, or that they are separated by voltage followers, as in Fig. 2. The effect of ten cascaded time constants is plotted. The routine used is shown in Listing 2.


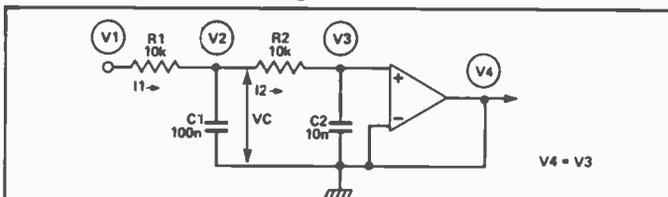


Fig.3 Active low pass filter circuit.

```

10 * Analogue circuit analysis program - MAIN PROGRAM
20 * Andrew Armstrong 06 February 1985
30
40 SCREEN 3,0,0:CLS: Select and clear graphics screen
50 Draw grid for graph
60 FOR N=00 TO 430 STEP 50:LINE (N,0)-(N,63)...:NEXT N:Vertical lines
70 LINE (30,0)-(30,63):LINE (0,63)-(473,63) Draw axes
80 LINE (30,38)-(473,38)...:NEXT N:Horizontal lines
90 GOSUB 170
100 FOR N=1 TO 8:M=(30+(N*50))/79/473:LOCATE M,0:PRINT N:NEXT N:Number scale
110 LOCATE 2,2:PRINT "-1-":LOCATE 2,5:PRINT"0.5" Number scale
120 IF INKEY$ <>" " THEN 120: Do not print "OK" over the graph immediately
130 END
140
150 * Active lowpass filter simulation
160
170 R1=10000:R2=10000:C1=1.2E-07:C2=2.2E-08:DT=.00001:V1=50
180 FOR N=30 TO 474
190 FOR M=1 TO 4
200 I1=(V1-V2)/R1
210 VC=VC+(I1-I2)*DT/C1:V2=VC+V3
220 I2=(V2-V3)/R2:V3=V3+I2*DT/C2
230 NEXT M
240 PSET (N,63-V3)
250 NEXT N:RETURN
    
```

Listing 3

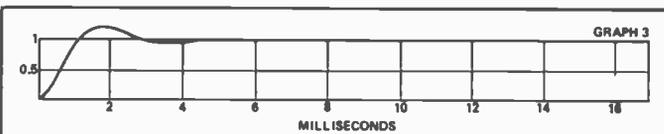

Graph 3 Print-out of active low pass filter simulation.

Overshoot

The technique can easily be applied to active circuits, such as the low pass filter shown in Fig. 3. The component values for this circuit are chosen so that it is underdamped. This results in an overshoot in the response to a step function, as shown in Graph 3.

Conventional wisdom also has it that there will be a peak in the frequency response, but more of this later. Listing 3 shows the equations used - the first part of the program, which draws the scale, is similar in all cases. Note (line 180) that the loop starts at 30 instead of at 0 as in Listing 1. This eliminates the need for the IF statement (Listing 1, line 200), which was only there to illustrate the application of an input step function.

The inner loop of M (Listing 3, line 190 to line 230) allows the calculation of four points for each one plotted on the graph, so that if high rates of change of any variable occur, a reasonable accuracy can be achieved. The size of this loop may be set as large as necessary to achieve good accuracy, but remember that each step of this inner loop is one time increment, so the step size DT should be scaled down appropriately to obtain the benefit from this. Otherwise, the time scale will simply be compressed, and the accuracy the same.


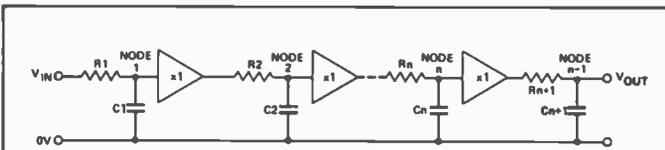


Fig.2 Cascaded time constant circuit.

```

5 DIM V(10) * Array to store node voltages
10 * Analogue circuit analysis program - MAIN PROGRAM
20 * Andrew Armstrong 06 February 1985
30
40 SCREEN 3,0,0:CLS: Select and clear graphics screen
50 Draw grid for graph
60 FOR N=00 TO 430 STEP 50:LINE (N,0)-(N,63)...:NEXT N:Vertical lines
70 LINE (30,0)-(30,63):LINE (0,63)-(473,63) Draw axes
80 LINE (30,38)-(473,38)...:NEXT N:Horizontal lines
90 GOSUB 170
100 FOR N=1 TO 8:M=(30+(N*50))/79/473:LOCATE M,0:PRINT N:NEXT N:Number scale
110 LOCATE 2,2:PRINT "-1-":LOCATE 2,5:PRINT"0.5" Number scale
120 IF INKEY$ <>" " THEN 120: Do not print "OK" over the graph immediately
130 END
140
150 * Cascaded time constant simulation
160
170 R1=10000:C1=.0000001:DT=.00001:V(0)=50
180 FOR N=30 TO 474
190 FOR M=1 TO 4
200 I1=(V(0)-V(L,1))/R1
210 V(L,1)=V(L,1)+I1*DT/C1
220 NEXT M
230 NEXT N
240 PSET (N,63-V(1))
250 NEXT N
260 RETURN
    
```

Listing 2

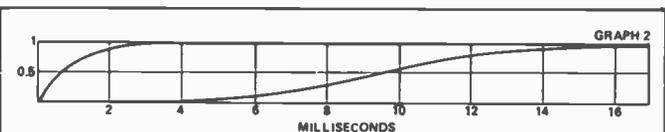

Graph 2 Print-out of cascaded time constant simulation.

COMMENTS ON LISTINGS

The computer for which the programs were written, an Epson PX8, has available a graphics screen, on which the individual LCD points may be set. It is numbered from 0,0 in the top left hand corner to 479,63 in the bottom right hand corner. The screen contents can be copied to a suitable printer using the screen dump mode. Once the purpose of the graph plotting statements is understood, there should be little difficulty in performing the nearest equivalent operations on another machine.

As well as being able to set individual points, lines can be drawn. It is almost as fast to draw a line as to set a single point, so this is employed in lines 60, 70, and 80, as shown on Listing 1, to draw the framework of the graph. The line is drawn to the bit pattern of a repeating 16 bit binary number corresponding to the number specified after the three commas in the line statement, the default being a solid line.

Character positions may be specified in x,y co-ordinates, starting with 1,1 on the top left, and finishing with 80,8 on the bottom right. Only whole character positions can be used, but the statement in line 100 LOCATEs the nearest position to the vertical scale lines, which are every 50 pixels for ease of calculation.

To avoid the message "OK" being printed over the graph, the INKEYS function is used in line 120 to keep the program twiddling its thumbs in a loop and allow time to press the screen dump button.

The calculation part of the programs is quite straightforward, and is detailed earlier on.

The only particular point of interest is that a smaller time increment is used in programs 2, 3 and 4 than in programs 1 and 5, and four steps of calculation are carried out for each point plotted. This reduces an otherwise unacceptable cumulative error in the cascading loop in program 2. In programs 3 and 4 the same technique copes with the high rates of change or voltage in the circuits being simulated.

Listing 4 shows the use of an input waveform other than a step at time=0. A sine wave is used, though any definable function may be used. R1 makes writing the equations convenient.

The only limitations on the size of the loop are how long you care to wait for an answer, and how long your computer is liable to be left undisturbed chonking away in peace while you do something else. In practice, I have found that the time taken to eat lunch is a reasonable limit but really fast machines may never need this long. Compiled Basic (or any compiled language) is to be preferred for complicated simulations.

The only significant difference between the active and the passive filter simulation is that the voltage across C1 is measured relative to the op-amp output instead of relative to 0V.

Lumped Constant

The same idea is applied to the voltage across the source resistor in the lumped constant transmission line simulation (Fig. 4, Listing 4 and Graph 4). The resistors chosen are of the nominal impedance of the line, \sqrt{LC} , so the output rings only a little. It is left to the reader to experiment with other values of R1 and R2. 50R gives some entertaining rings!

In principle, this simulation could be applied to almost any linear circuit. If many similar stages were to be simulated, even though they had different values, it would be better to use a loop as in Listing 2, and to refer to component values stored in arrays.


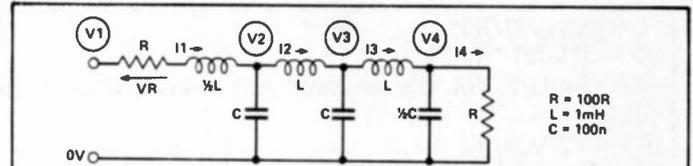


Fig.4 Lumped constant transmission line - equivalent circuit.

```

10 ' Analogue circuit analysis program - MAIN PROGRAM
20 ' Andrew Armstrong 06 February 1985
30 '
40 SCREEN 3,0,0:CLS: Select and clear graphics screen
50 ' Draw grid for graph
60 FOR N=00 TO 400 STEP 50:LINE (N,0)-(N,63)...43690:NEXT N:Vertical lines
70 LINE (30,0)-(30,63):LINE (6,63)-(473,63) Draw axes
80 LINE (30,30)-(473,30)...34952:LINE (30,13)-(473,13)...61600:Horiz lines
90 GOSUB 170
100 FOR N=1 TO 8:N=(30+(N*50))*79/473:LOCATE N,8:PRINT 20*N:NEXT N
110 LOCATE 2,2:PRINT "-|-":LOCATE 2,5:PRINT":.5" Number scale
120 IF INKEYS <"1" THEN 120: Do not print "OK" over the graph immediately
130 END
140 '
150 ' Lumped constant transmission line simulation
160 '
170 L=.001:C=.0000001:R1=100:R2=100:DT=.0000001:V1=100
180 FOR N=30 TO 474
190 FOR M=1 TO 4
200 I1=I1+DT*(V1-V2-VR)*2/L:VR=I1*R1:V2=V2+DT*(I1-I2)/C
210 I2=I2+(V2-V3)*DT/L:V3=V3+DT*(I2-I3)/C
220 I3=I3+(V3-V4)*DT/L:V4=V4+DT*(I3-I4) *2/C:I4=V4/R2
230 NEXT M
240 PSET (N,63-V2):LINE (N,63-V4)-(N,62-V4)'Plot first node and output
250 NEXT N:RETURN
    
```

Listing 4

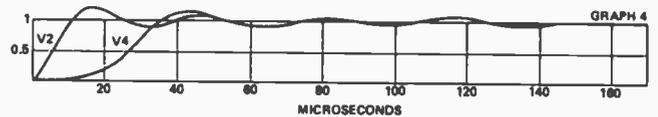

Graph 4 Print-out of lumped constant transmission line simulation.


Frequency Response

All the analysis shown so far gives only the time response of a circuit. There are at least two ways in which it can be adapted to provide a plot of frequency response.

The first and most obvious method is to make the input voltage a sinewave, instead of a step function. A large number of cycles is applied to the circuit to allow the circuit to settle, and then the output signal is plotted, or its amplitude measured and the result stored in an array. The frequency is then incremented and the procedure carried out again. It is clear that such a program would take a long time to run, so the writing of code is left as an exercise for the reader.

There is another method, still under development, which should turn out more elegant and faster to execute. If the output signal from the circuit were to be spectrum analysed, perhaps by a Fourier transform, and compared with the frequency spectrum of the input, then the frequency transfer function of the simulated circuit could be determined. Phase information would be available as well.

Fig.5 A current limited op-amp configuration.

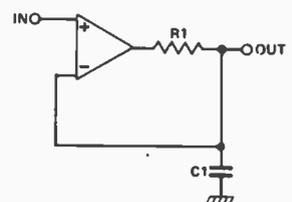


FEATURE: Time Domain Analysis

```

10 ' Analogue circuit analysis program - MAIN PROGRAM
20 ' Andrew Armstrong 06 February 1985
30 '
40 SCREEN 3,0,0:CLS' Select and clear graphics screen
50 ' Draw grid for graph
60 FOR N=00 TO 430 STEP 50:LINE (N,0)-(N,63)...43690:NEXT N:Vertical lines
70 LINE (30,0)-(30,63):LINE (30,31)-(473,31)' Draw axes
80 GOSUB 160
90 FOR N=1 TO 8:M=(30+(N*50))*79/473:LOCATE M,4:PRINT N::NEXT N:Number scale
100 LOCATE 2,4:PRINT "--o--" Number scale
110 IF INKEY <"1" THEN 110' Do not print "OK" over the graph immediately
120 END
130 '
140 ' Current limited op-amp simulation
150 '
160 R1=470:C1=1.8E-07:DT=.00002:ANGLE=ATN(1)/25:GAIN=1000
170 FOR N=30 TO 470
180 V1=30*SIN(ANGLE*(N-30))
190 V0=GAIN*(V1-V2)+V1
200 IF V0>30 THEN V0=30
210 IF V0<-30 THEN V0=-30
220 I1=(V0-V2)/R1:IF I1>.006 THEN I1=.006
230 IF I1<-.006 THEN I1=-.006
240 V2=V2+I1*DT/C1
250 PSET (N,31-V1):PSET (N,31-V2)
260 NEXT N:RETURN

```

Listing 5

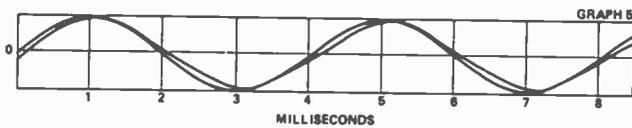

Graph 5 Print-out of current limited op-amp simulation.

This technique should work well, because the frequency spectrum of the input step function is continuous, theoretically from zero to infinity (but only if the simulation is for an infinite period!). Any reasonable range of frequencies is liable to be able to be plotted with little difficulty, once the numerical spectrum analysis is working.


Further Applications

So far, only linear circuits have been considered. It is easy to add the effects of non-linearity anywhere in the circuit by using IF statements. For example, current limiting may be represented by:

IF I>6E-3 THEN I = 6E-3: IF I<-6E-3 THEN I = -6E-3

This limits the current to ± 6 milliamps, typical of the response of some small op-amps. The effect of a current limited opamp connected in the circuit shown in Fig. 5 is simulated by the program in Listing 5, which feeds a sine-wave into the circuit, and gives the output shown in Graph 5.

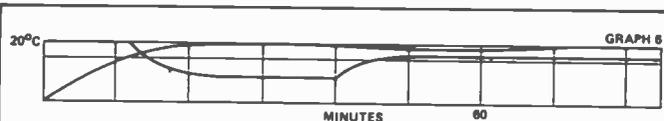This circuit is a first approximation to a model for an op-amp. Equally, a conventional model may be used to simulate a transistor, with sets of values stored in arrays to enable a single transistor simulation subroutine to be used for a multi-transistor circuit.



Graph 6 Print-out of heater control simulation.

The technique can be used for digital and control circuits. For example, Graph 6 shows the effects of PID (proportional, integral, and differential) control using a computer in conjunction with a heating system. In this case, the simulation can be very close to the truth, since the measurements would be sampled and the sampling period of the program can be made identical to that of the system to be used. The thick line on the

THERMAL RESISTANCE TO OUTSIDE = R1 OUTSIDE TEMP = T0

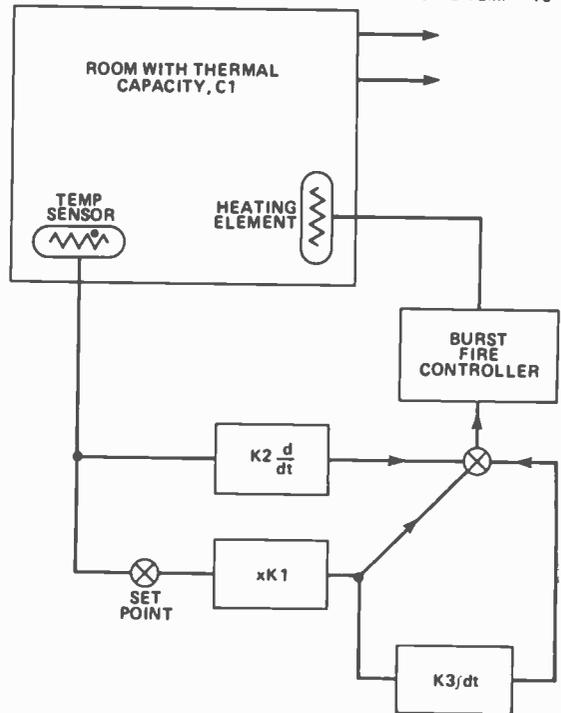


Fig. 6 Block diagram of heater control circuitry.

```

10 'Airconditioning simulation program A. Armstrong 4 Feb. 1985
20 SCREEN 3,0,0:CLS' Select and clear graphics screen
30 '
40 ' Draw grid for graph
50 '
60 FOR N=00 TO 450 STEP 50:LINE (N,0)-(N,63)...43690:NEXT N:Vertical lines
70 LINE (30,0)-(30,63):LINE (30,63)-(473,63)' Draw axes
80 LINE (30,13)-(473,13)...61600' Aiming point
90 GOSUB 130' Call calculation routine
100 LOCATE 55,8:PRINT"60":LOCATE 1,2:PRINT"20°C" Scale number:10
110 IF INKEY <"1" THEN 110'TYPE 1 FOR A PRINTED COPY
120 COPY:END' THE END OF THE MAIN PROGRAM
130 C1=100:R1=20:T0=0:DAT=2:AT=15:PB=5:SP=20:DT=.05:HTC=1'Times in minutes
140 X=DT*.36/HTC:Y=1-X'Heater time constant
150 K3=DT/IAT
160 DT=DT*60' convert to seconds
170 BAND=13+(PB*2.5)
180 LINE (30,BAND)-(473,BAND)...34952' Draw proportional band lower limit
190 K1=1/PB
200 K2=1/(DAT*DT*PB)
210 ONE = DT'One kilowatt of cooling = 1*time increment
220 FOR N=30 TO 470
230 FOR LOOP=1 TO 4
240 HP=(SP-TEMP)*K1:HD=K2*TD
250 H=HP
260 IF HD>1 THEN H=1
270 Y1=Y1+H*K3' INTEGRATE HEATING DEMAND (WITHOUT INTEGRAL TERM)
280 IF Y1<0 THEN Y1=0:IF Y1>1 THEN Y1=1'KEEP INTEGRAL WITHIN LIMITS
290 IF HD>.99 THEN Y1=0'NO INTEGRATION OUTSIDE LINEAR CONTROL REGION
300 H=HP+Y1-HD
310 IF H<0 THEN H=0:IF HD>1 THEN H=1
320 IF HD>1 THEN H=1
330 TPREV=TEMP
340 HEAT=DT*H*2.5*Y+HEAT*X'THERMAL MASS OF HEATER
350 LOSSES=(TEMP-T0)*DT/R1
360 IF N<229 THEN LOSSES = LOSSES*ONE'ADD 1 KW OF COOLING SUDDENLY
370 TEMP=TEMP+(HEAT-LOSSES)/C1
380 TD=.9*TD+.1*(TEMP-TPREV)'SIMPLE DIGITAL FILTERING ALGORITHM
390 NEXT LOOP
400 T1=2.5*TEMP
410 PSET (N,63-T1)
420 PSET (N,63-50*H):PSET (N,62-50*H)
430 NEXT N:RETURN

```

Listing 6

graph represents heater power, the thin line represents temperature. At time 40 minutes, an extra kilowatt of cooling is introduced (to model, say, a window being opened). The graph shows the effect of such a disturbance to the system.

In this example, the maximum heater power is assumed to be 2.5 kW, the room to outside temperature insulation is 20°C per kW, and the outside temperature is 0°C. The thermal capacity of the room is assumed to be 100 kilojoules per degree, and the time constant of the heating element is about one minute.

THE REAL COMPONENTS

In this, the fourth article in his series, John Linsley Hood looks at transistor parameters and design calculations based upon them.

It is a useful thing to be able to calculate how an electronic circuit will behave, and in the case of valves, this was quite straightforward. Transistors are a different and rather more difficult matter, not helped very much by the fact that there are such a wide variety of terms and symbols used by different manufacturers and text books to describe exactly the same thing.

However, it looks more difficult than it is — at least at low frequencies — to do the sums, and I propose to try and prove this. But first, we must specify the meaning of the terms.

Resistance Well, that is straightforward enough, and just defines that quality in the obstruction of current flow which causes a voltage drop (or potential difference). $R=V/I$.

Impedance Basically the same thing as resistance, but allowing for the fact that there is some capacitive or inductive component in the resistance to current flow, so that the actual value will be different at different frequencies. Pure resistance is an uncommon thing in real life because most obstructions to current flow are, in truth, impedances, so this is a word which can be used to describe what one means without much risk of contradiction.

Conductance This is the reciprocal of resistance, and is measured in amps per volt (I/V) instead of volts per amp (V/I).

Admittance This is the reciprocal of impedance, and again is given in terms of amps per volt, but at some specific frequency. Both conductance and admittance are expressed in Siemens ($=S$). $1S=1\text{amp/volt}$, $1\text{mS}=1\text{mA/V}$, and so on.

The symbol R is conventionally used to indicate resistance, and Z to indicate impedance. G is used to indicate conductance, and Y for admittance.

When dealing with transistors it is customary to look at them as small 'black boxes' with four terminals. The input circuit is labelled 1 and the output circuit is labelled 2, as shown in Fig. 1a or in the equivalent circuit shown in Fig. 1b.

Conventionally, again, the currents which flow in circuit 1 as a result of the voltages applied to the input terminals are referred to as i_1 . Those which flow in the

output as a result of voltages in the output are referred to as i_2 and those which flow in the output as a result of currents in the input are described as i_1 and so on.

Originally, the input characteristic was measured as an impedance, Z , giving rise to terms like Z_{11} to define the input impedance, and the output circuit defined as an admittance, so that the output admittance would be specified as Y_{22} . Nowadays, it is much more common for these to be known as h or 'hybrid' parameters, so that Z_{11} becomes h_{11} or h_i , and the output admittance Y_{22} becomes h_{22} or h_o .

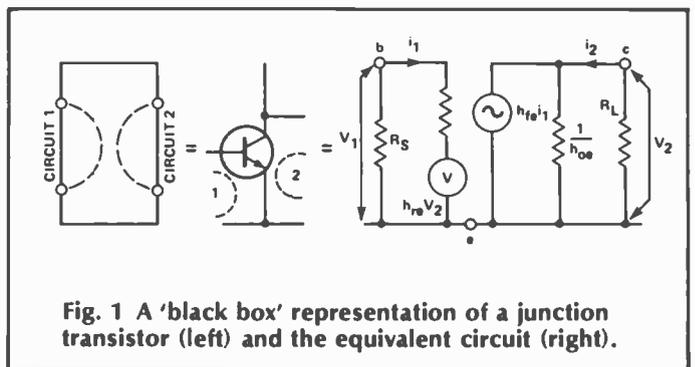


Fig. 1 A 'black box' representation of a junction transistor (left) and the equivalent circuit (right).

However, in addition to these we have the transfer characteristics, such as the forward current transfer ratio. This is written as h_F if we are talking about DC values (usually referred to as static conditions) or h_f if we are referring to dynamic (AC) characteristics. The reverse, or feedback parameter, h_{12} , becomes h_r .

This is complicated a bit by the fact that all of these parameters are affected by the way in which the transistor is used. If it is used in the common emitter configuration with the signal applied to the base, the output taken from the collector, and the emitter tied to the 0V line, these various parameters become h_{FE} or h_{fe} , h_{oe} , h_{re} and so on. Similarly, if one ties the base to a common supply line potential, and applies the signal to the emitter, these parameters would be defined as h_{fb} , h_{ob} , and h_{rb} .

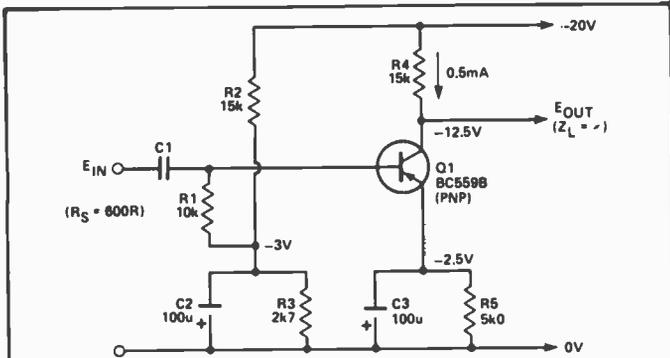


Fig. 2 A practical, common-emitter transistor gain stage which may be used for performance calculations.

Unlike valves and FETs, transistors have a DC conductive path between their three connections, so the output impedance is influenced by the input circuit impedance and vice-versa, and all of these including the current gain, are influenced by the operating current of the device.

A fairly full data sheet for a transistor should include graphs which show the way in which h_{FE} varies as a function of operating current. Ideally it shouldn't vary very much, and in the better modern types it doesn't. The graphs will also show the way in which the input impedance will vary with emitter current, but this will usually be quoted only for the common emitter configuration since this is the most widely used arrangement. If this isn't quoted, a fairly useful rule of thumb is that the input impedance (h_{ie}) is 25x the current gain for a 1mA emitter current, and increases, roughly in proportion, as the operating current is decreased. One should also find values for the output admittance, as μS or $\mu A/V$, and the reverse transfer ratio, h_{re} .

The formula for calculating voltage gain, in the common emitter configuration shown in Fig. 2, is —

$$A_v = - \frac{h_{fe} \times R_L}{h_{ie} + R_s + \Delta h_{e} \times R_L}$$

Δh_e , the common emitter configuration correction factor ($h_{ie} \cdot h_{oe} - h_{fe} \cdot h_{re}$) is often small enough to be ignored, so the gain equation simplifies to —

$$A_v = - \frac{h_{fe} \times R_L}{h_{ie} + R_s}$$

Let's take a genuine example, such as the Mullard BC559, and go through these calculations for an operating current of 0.5mA. The gain of the circuit shown in Fig. 2, at a frequency in the AF range where the impedances of C1, C2 and C3 are small enough to be ignored, can be calculated using the published data:-

$$h_{fe} = 270 \quad h_{ie} = 10k$$

$$h_{oe} = 25 \mu A/V. \quad h_{re} = 0.001.$$

which gives a value of 0.52 for Δh_e .

However, we have to take into consideration the source impedance (R_s), which in this case I have assumed to be a signal generator with a 600 ohm output. This must be added to h_{ie} .

$$A_v = \frac{270 \times R_L}{10k + 600 + 0.52 \times R_L}$$

so the voltage gain becomes —

$$= - \frac{270 \times 15k}{10k6 + 0.52 \times 15k}$$

This is a very favourable condition, since I have also assumed an output impedance which is very high in relation to R4. If, however, the transistors were driven from a similar stage, where the output impedance is $R4 // Z_{oe}$ ($40k // 15k = 10k9$), and it was loaded by the input impedance of a similar transistor, ($Z_{ie} = 10k$), the gain would come down to —

$$A_v = \frac{-270 \times 10k9 // 10k}{20k9 + 0.52 \times 5k2} = 60$$

which is a much more typical figure.

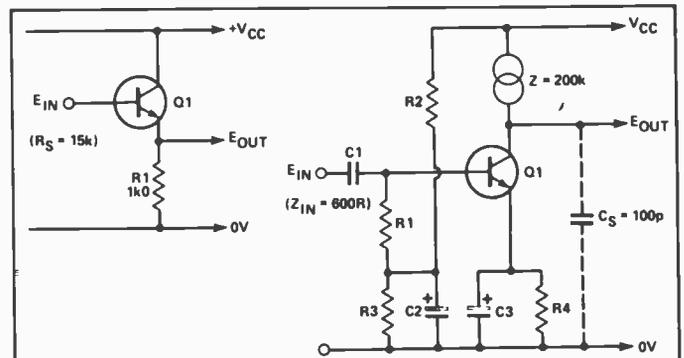


Fig. 3 A transistor arranged as an emitter follower.

Fig. 4 A high gain transistor stage.

Another useful calculation to be able to make is that to discover the input and output impedances of the impedance converting emitter follower circuit of Fig. 3. This is,

$$Z_{in} = (1 + h_{fe}) \times R1, \text{ and} \\ Z_{out} = R3 / (1 + h_{fe}) // R1.$$

For a transistor such as the BC559, driven from a 15k source, the output impedance will be 52 ohms and the effective input impedance will be 271k.

The lesson which can be drawn from this is that, for high stage gains, low source impedances and high output impedances are imperative. However, there are snags. The first of these concerns the effect of output stray capacitance in parallel with the load.

Let us assume, in the case of the circuit shown in Fig. 4, that we have contrived a constant current source as the collector load and this has an effective dynamic impedance of 200k at a collector current of 0.5mA. Using the circuit parameters of Fig. 2, this will give us a gain of 471 at lowish audio frequencies, and if we are driving an emitter follower or similar high impedance load we should not diminish this too much.

However, suppose we have a stray capacitance of 100pF in parallel with the output circuit. The output impedance will then decrease with frequency until, at about 7kHz, the stage gain will have fallen to half its low frequency value.

An aspect of this capacitance load effect which is familiar, and worrying, to audio amplifier designers is the combined effect of a constant current source load and stray capacitance when the amplifier is asked to

FEATURE: Real Components

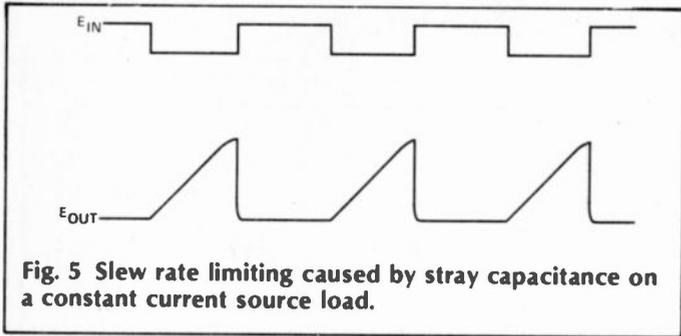


Fig. 5 Slew rate limiting caused by stray capacitance on a constant current source load.

handle a waveform having a rapidly rising voltage transient. I have shown this in Fig 5.

With the circuit shown, the amplifier stage may behave quite well on negative-going transients when the transistor, Q1, can pump current into the load, but on a positive-going waveform, the rate of charge of the capacitor is strictly limited by the constant-current source to 0.5mA, which gives a beautifully linear charging rate to the capacitance. This is lovely in the time base generator of an oscilloscope, but audibly very nasty in an audio amplifier. It gives rise to the defect known as 'slew rate limiting', which is one of the all-too-frequent causes of displeasure in less than high fidelity.

Another related problem inherent in the transistor is that of the Miller effect, due to the capacitance between the base and collector. Since the stage inverts the phase of the signal, at least on non-inductive loads, the side of the internal capacitor electrically connected to the output will rise in potential as the input side falls. If the gain of the stage is M, this has the effect of making the capacitor look like M+1 times its static value, as shown in Fig. 6.

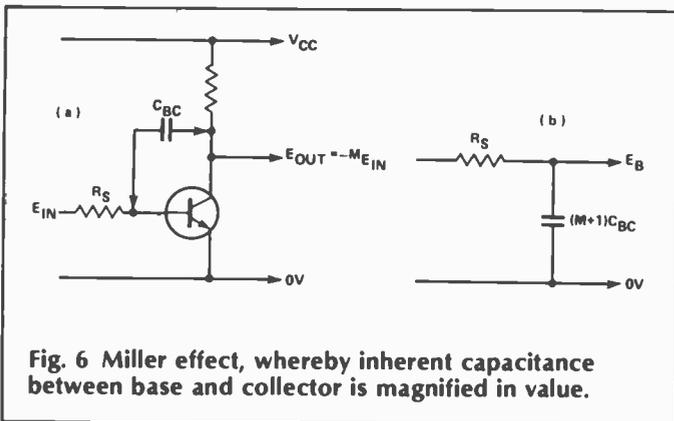


Fig. 6 Miller effect, whereby inherent capacitance between base and collector is magnified in value.

Supposing, therefore, that the stage gain is 150x, and the base-collector capacitance is 5pF, the actual capacitance seen at the transistor end of the source resistor is $5 \times 150\text{pF} = 750\text{pF}$, which will have a considerable effect on the HF response of the circuit.

Other Parameters

Noise figure This is expressed in decibels, and is a measure of the extent to which the transistor input noise (output noise divided by stage gain) is worse than that which would have been due just to the input resistance on its own. All resistors generate noise, the higher the resistance value and the higher the temperature the worse this will be. The formula is —

$$V_n = \sqrt{4 \times K \times T \times \delta f \times R}$$

where K is Boltzmann's constant (1.38×10^{-23}), T is the absolute temperature ($^{\circ}\text{K}$), and δf is the bandwidth.

A typical graph showing the way the noise figure of a transistor varies with collector current and source resistance is shown in Fig. 7. Since the noise will increase at high input resistance values anyway, the best transistor to use if one wants the lowest noise is the one which will give a low noise figure at the lowest useable input resistance.

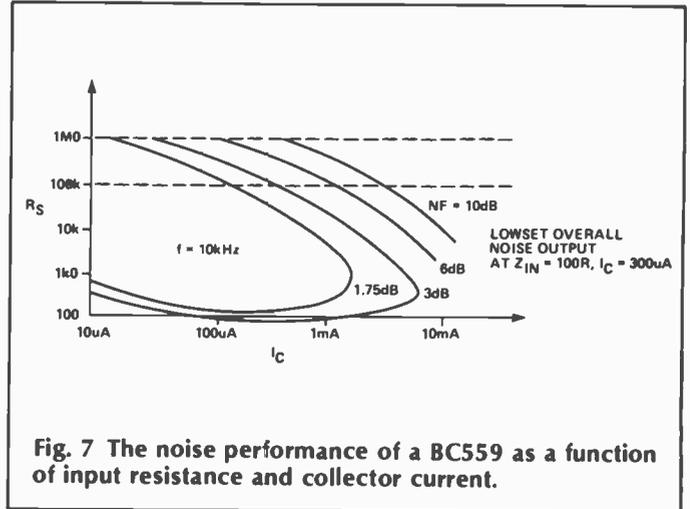


Fig. 7 The noise performance of a BC559 as a function of input resistance and collector current.

Happily, improvements in device manufacture have led to better characteristics, so, if you have a choice, use a device with a high 2N or BC number, rather than a low one. A BC549 is likely to be a better device, at the same cost, than a BC109, since these are both of the same type, only differing in date of design. Surprisingly, PNP small signal devices are better than NPN in this respect because the current flow in the base region — which is of N type — is due to electrons rather than holes.

Transition frequency As the operating frequency increases, so the current gain of a transistor will decrease. NPN devices are normally better than PNP ones in this respect, and since the problem is due to electron/hole mobility in the base and collector regions, devices with thin, highly doped base and collector layers, which will inevitably have a relatively low breakdown voltage, will be best in this application.

The parameter f_t can be thought of as the frequency at which the current gain will have fallen to unity.

Breakdown voltage This can be due to several mechanisms, and is usually destructive unless the current which can flow is limited by some external resistance to a value which does not cause the local thermal dissipation of the device to exceed a safe value.

One of the mechanisms is punch through, which occurs when the depletion layer in the base region resulting from the applied collector voltage extends, as V_c is increased, until it reaches the emitter region. When this happens, the base effectively loses its identity and there is no longer a PN junction to prevent current flow. If the collector region is heavily doped to allow high current flow, the number of minority carriers diffusing into the base will be greater and the depletion layer wider for any given applied voltage, leading to a lower punch through potential.

A second mechanism is the Zener effect. In a highly doped material, a reverse bias will cause the valence band (containing minority carriers) to overlap the conduction band in the semiconductor junction (containing majority carriers, ie, electrons) and current will flow. A small-signal transistor can be used as a cheap

	COMMON EMITTER	COMMON BASE	COMMON COLLECTOR
VOLTAGE GAIN	$\frac{-h_{fe} R_L}{h_{ie} + h_{oe} R_L}$	$\frac{(h_{fe} + \Delta h_e) R_L}{h_{ie} + \Delta h_e R_L}$	$\frac{(1 + h_{fe}) R_L}{h_{ie} + (1 - h_{re} + h_{fe} + \Delta h_e) R_L}$
CURRENT GAIN	$\frac{h_{fe}}{1 + h_{oe} R_L}$	$\frac{-(h_{fe} + \Delta h_e)}{1 - h_{re} + h_{fe} + \Delta h_e + h_{oe} R_L}$	$\frac{-(1 + h_{fe})}{1 + h_{oe} R_L}$
INPUT IMPEDANCE	$\frac{h_{ie} + h_{oe} R_L}{1 + h_{oe} R_L}$	$\frac{h_{ie} + \Delta h_e R_L}{1 - h_{re} + h_{fe} + \Delta h_e + h_{oe} R_L}$	$\frac{h_{ie} + (1 - h_{re} + h_{fe} + \Delta h_e) R_L}{1 + h_{oe} R_L}$
OUTPUT IMPEDANCE	$\frac{h_{ie} + R_S}{h_{ie} + h_{oe} R_S}$	$\frac{h_{ie} + R_S(1 - h_{re} + h_{fe} + \Delta h_e)}{\Delta h_e + h_{oe} R_S}$	$\frac{h_{ie} + R_S}{1 - h_{re} + h_{fe} + \Delta h_e + h_{oe} R_S}$

NOTE: $\Delta h_e = h_{ie} h_{oe} - h_{re} h_{fe}$

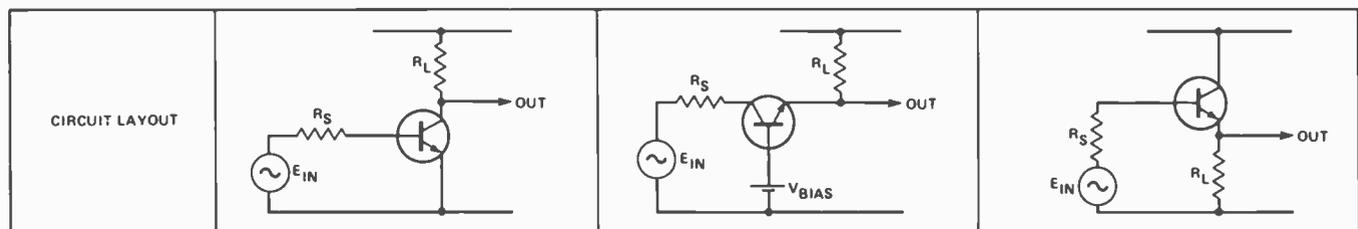


Table 1 Junction transistor performance calculations using h parameters.

zener diode of about 5-6V if it is connected with its emitter reverse biased in relation to its base. This is because the emitter is usually a very heavily doped region. Normally, if the current is held to a sensible level, no damage will occur. The collector should be connected to the base in this application, to keep it from joining in as shown in Fig. 8.

A third mechanism, avalanche breakdown, occurs in lightly doped high voltage transistors if too high a voltage is applied. In this, carriers entering the depletion region are accelerated by the applied potential and, if their velocity is high enough, collisions within the material will generate ion-pairs and further carriers. The result is much like an avalanche, and usually just about as welcome. An exception to this is in avalanche diodes where this mechanism is used to beneficial effect.

In transistors, avalanche effects are greatly influenced by the external base-emitter circuit resistance, and this is the reason why, in general, high voltage and power transistors require conditions of use in which the base circuit resistance is low.

Power Transistors


In principle, one can do all the calculations for power transistors that one can for small signal ones, except that the manufacturers are a lot less forthcoming about the input and output h values. This is because power devices are mainly only used in applications where, as emitter followers or drivers of low impedance loads, the stage gain is a lot less important than the ability of the device to feed current into the load or withstand the voltage swings involved without breakdown.

The parameters one is likely to find published in respect of power transistors, in addition to the ones which are obvious like total power dissipation and safe operating area (which we looked at previously), are those which relate to its operational voltages and switching times.

Of these, the ones which are likely to be of interest,

say, to an audio amplifier designer, are the collector and base saturation voltages. These will be specified at certain base and collector voltages, and relate to the sort of voltage drop which is going to occur across the device when large quantities of current are delivered by it.

A further quality which would be of interest is the variation of current gain with collector current. Ideally, for lower distortion, this curve should be as flat as possible. Also, if one is seeking a high power output, the 'thermal resistance' of the transistor is important. This is usually specified in $^{\circ}\text{C}/\text{watt}$, and infers a perfect stone-cold heat sink, so in practice, the thermal resistance of the heat sink will have to be added to this to

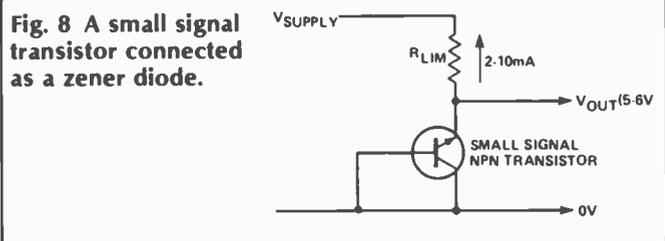

arrive, perhaps, at a figure like $2.5^{\circ}\text{C}/\text{watt}$. The maximum junction temperature which is tolerable will depend on how long you intend the device to last. If you are worried about this, aim to keep your junction temperatures below 150°C , under the worst likely conditions. If one had a total heat-sink + transistor thermal resistance of $2.5^{\circ}\text{C}/\text{W}$, and the ambient temperature was 30°C , this would mean a maximum dissipation of $(150-30)/2.5\text{W}$, or 48 watts.

$V_{ce0\text{ sus.}}$, is the collector voltage at which the transistor will pass a continuous collector current, even when there is no base drive current at all. The manufacturers quote minimum values for this. In practice it means 'keep well below this voltage — unless you are only operating under pulsed voltage conditions'.

The normal maximum operating voltages (usually under relatively low current conditions) are defined as

FEATURE: Real Components

V_{cbo} , which is the maximum voltage permitted between collector and base with the emitter open circuited; V_{ceo} , which is the collector/emitter maximum voltage with the base open circuit, and V_{cer} , which is the permitted maximum collector voltage with some specified value of resistance between emitter and base (see avalanche breakdown above).

V_{ebo} is the reverse biased emitter/base zener voltage, and is usually about 5V for power devices.

Where the power transistor is being used for fast switching applications, the various switching times become important. These are the delay time (t_d), which is the time which elapses after the application of a voltage to the base before any collector current begins to flow; the rise time; the fall time; and the storage times associated with the rise and fall of collector current, and which relate to the length of time it takes for the relatively slow moving holes in the base region to be eliminated.

This is particularly important when the current through the transistor is being turned off. It will not reach a zero value until the stored charge is dissipated, and this is dependent both on the external base-emitter circuit resistance and upon the emitter voltage. If the emitter is reverse biased to some value lower

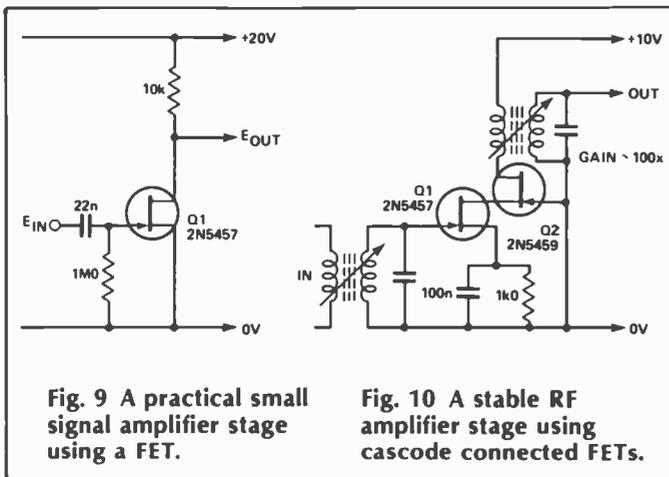


Fig. 9 A practical small signal amplifier stage using a FET.

Fig. 10 A stable RF amplifier stage using cascode connected FETs.

than the zener breakdown level, the stored charge will be removed more rapidly and this may be a critical factor in switching inductive loads.

Because of the larger junction areas all of the capacitance values for power transistors are much larger than for small signal devices, with values in the range 100-1000pF being common.

Junction Field Effect Transistors

Because these are voltage operated devices with a virtually infinite impedance gate electrode, gain calculations are much simpler, at least at low frequencies. As with junction transistors, HF calculations, usually with deliberate or unintentional inductance in the input and output circuits, are a highly complex business, best left to the specialists in this field.

The parameters which are likely to be specified are Y_{fs} , the forward transfer conductance, or forward trans-admittance, which is similar to the G_m , or mutual conductance, figure for a thermionic valve, and is usually expressed in mA/V; and the Y_{os} , or output admittance, of which the reciprocal is similar to the anode resistance of a valve.

Typical values of these parameters, for a 2N5457 FET, are 4-7mA/V at 0V negative gate bias, and 2μS, or 500k. A 2N5459, which has a gate cut-off voltage of about -5V instead of 1.5-2V for the 2N5457 and a zero

gate-bias drain current of 10-15mA instead of 2-5mA, will have a higher zero gate bias Y_{fs} , probably in the range 6-10mA/V. The output impedance is, however, very similar. Junction FETs do have very high drain resistance values, which is why they make such good constant-current sources.

The formula for calculating voltage gain is a simple one:-

$$A_v = - \frac{Y_{fs} \times R_L}{1 + Y_{os} \times R_L}$$

For the common source configuration shown in Fig. 9, and with the component values shown, this becomes:-

$$A_v = - \frac{5 \times 10^{-3} \times 10k}{1 + \frac{10k}{500k}}$$

giving a value for stage gain of 49 at zero gate bias. However, as the negative gate bias is increased the mutual conductance falls, giving proportionately lower stage gains. Once again, I have assumed an infinite impedance load. A load of 10k would halve these stage gain values.

The input capacitance, C_{iss} , is typically 3-6pF, decreasing as the gate becomes more negative. The reverse transfer capacitance (or, more familiarly, the drain-gate capacitance) is typically 1-3pF, becoming less as the drain voltage is increased, and as the gate is made more negative. This is a bit high for stable working as an RF amplifier, but two similar FETs can be connected in cascode as shown in Fig. 10, to make a very stable RF amplifier.

The input noise figure for FETs will be expressed as nV per √Hz, and since this is independent of the source resistance value, the FET will have the least effect in worsening the input noise when the input circuit resistance is very high.

For example, the published figure for a 2N5457 at 25°C is 10nV/√Hz, which for a 20kHz bandwidth is 1.4μV. However, for the same bandwidth, the noise developed across a 1M resistor is 18μV, giving an effective FET noise figure of 0.6dB when used in this circuit. The break-even 6dB noise figure occurs for an input resistance of about 7k.

One of the areas in which junction FETs (and MOSFETs) score heavily in comparison with bipolar transistors is in terms of linearity, with a typical FET amplifier stage offering THD (Total Harmonic Distortion) figures in the absence of negative feedback some 10x lower than for a similar bipolar gain stage. Say, 0.5% THD instead of 5% THD for 5V RMS output. This arises because the FET has a very linear input voltage/output current relationship, especially at near zero gate bias voltages. This compares with bipolar devices which are only linear at very small input signal levels.

Small Signal MOSFETs

The characteristics of these are very similar so far as gain calculations are concerned to those of junction FETs, and the same formulae apply. However, the typical values of drain resistance are more similar to those of a junction transistor than to the junction FET.

Next month I propose to take a look at diodes, in all their various forms.

ETI

**NEXT
MONTH**


AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

Centronics Printer Buffer

Microcomputers are pretty fast devices, far too fast for even the most speedy of printers to match. The result is that your micro often has to sit idle while it waits for the printer to catch up. The solution is to build our printer buffer, a handy store which holds the data destined for the printer while your micro carries on running. For word-processing, listing programs or printing out screen displays, you will find this a most useful piece of equipment next to your computer and printer.

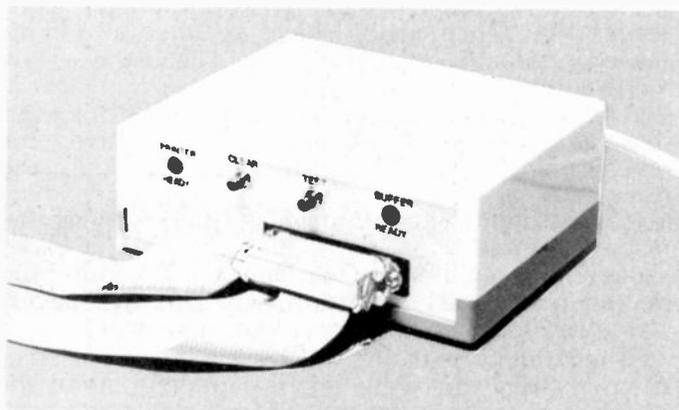

Noise About Noise

A lot has been written recently about the effects of various types of components on the quality of sound an audio system delivers. Not a little of it has been written in ETI. In this provocative article, amplifier designer and manufacturer Neil Munro argues that we should be worrying less about our components and more about our power supplies.

EPROM Emulator

It's not that long since we last described an EPROM emulator, but you can never have too much of a good thing and this design is sufficiently different to be of interest. It is intended to complement the 6802 Evaluation Board featured in the May issue but should work with almost any system.

Second Processor For The Acorn Electron

This valuable accessory has been shown to increase the speed of an Electron to that of a BBC B and its memory capacity to more than twice that of the Beeb. In the second and final part of this project we describe the software necessary to achieve this remarkable improvement.

The Real Components

John Linsley Hood's in-depth series continues with a Look at some semiconductor devices. The topic is diodes and the article will include a look at such exotic items as tunnel diodes and diacs.

Universal EPROM Programmer

In the third and final part of this series, Mike Bedford and Gordon Bennett describe the software and present a complete listing of the programmer source code.

Plus All The Usual Features . . .

Tech Tips, Scratch Pad, Read/Write, Open Channel, News Digest, Trains of Thought, book and equipment reviews, etc, etc. Everything, in fact, that you'd expect from the UK's leading electronics magazine.

**THE JULY ISSUE WILL BE ON SALE
FROM JUNE 7TH. GET IT OR REGRET IT!**

All of the articles mentioned are at an advanced stage of preparation. However, circumstances beyond our control may prevent us including them.

KITS	OPTO	LINEAR ICs
CT1000KB Clock/Timer 17.40	3mm red 9 5mm red 9	555 21 ML926 1.80
CT6000* Programmable Timer 39.00	3mm green 12 5mm green 12	556 40 ML927 1.80
XX114 Relay Kit for above 3.90	3mm yellow 12 5mm yellow 12	741 22 ML928 1.80
XX101 Electronic Lock 11.50	Rectangular square arrow or triangular flat faced	746 30 ML929 1.80
XX102 3 Note Door Chime 5.50	Red 15 Green 10 Yellow 10	A0590 3.30 NM74C911 6.50
XX104 Solid State Switch 2.40	Bicolour 65 Flashing Red 50	AY38910 3.90 NM74C915 96
XX112 Mains Wiring Remote Control 42.00	Tricolour Red 35	CA3080 65 NM74C922 3.90
XX113 MW Radio 5.50	Round 32 Continuous 55	CA3130 85 NM74C926 4.50
XX126 DVM/Thermometer 15.50	Rectangular 45	CA3140 40 NE567 1.25
DL1000K 4-Ch Light Chaser 15.95	11747/1111 55 MOC3070 1.10	ICL7107 9.00 SC668 2.20
DL21000K 4-Ch Light Chaser 18.95	IL074 1.70 MOC3040 1.50	ICL7126 8.00 SS760 2.20
DLA11 Opto Input for above 7.0	ORP12 75 MEL11 35	ICM8566 95 SAB0529 3.50
DL3000K 3-Ch sound to light 12.95	Seven Segment LED Displays	ICM8038 3.10 SAB0600 2.50
TL3000K 300W Touchdimmer 7.75	DL704 3 cc 75 4 Dig 18 cc	LF351 40 SL440 1.35
TS3000K 300W Touchswitch 7.75	FN500 5 ca 85 DIRECT DRIVE	LF356 80 SL486 1.85
LO3000K 300W Lightdimmer 3.95	FN507 5 ca 85 Display 7.00	LM324 40 SL490 2.05
TDR300K IR Remote Controlled Lightdimmer 14.95	400V TRIACS	LM334Z 85 TBA0800 7.0
MK6 IR Transmitter for TOR300K & MK7 4.50	4A 49 8A 58	LM335Z 1.20 TBA10A5 9.0
TDE/1 Touchdimmer Ext. 2.50	8A isolated 65 12A 85	LM339 40 TDA1024 1.20
TSA300K Time Delay Touch Switch (300W) 5.00	8A sensitive 66 25A 2.10	LM348 56 TDA4290 1.98
MK1 Thermostat 4.60		LM358 48 TL061 4.0
MK2 Solid State Relay 2.60		LM380 1.20 TL062 1.30
MK4 Proportional Temperature Controller 6.50		LM381 1.40 TL064 1.30
MK5 Mains Timer 4.50		LM382 1.10 TL071 4.5
MK7 Single channel IR Receiver (240V) 10.50		LM386 88 TL072 7.0
MK9 4-way Keyboard 1.90		LM1035 3.95 TL074 1.30
MK10 16-way Keyboard 5.40		LM1450 34 TL081 3.5
MK11 10-channel 1-3 analogue op IR Receiver 13.50		LM2917 1.90 TL082 4.8
MK12 16-channel IR Receiver 13.50		LM3900 68 TL084 1.00
MK13 11-way Keyboard 4.35		LM3908 80 TL170 5.0
MK14 AC Power Controller 5.20		LM3911 1.75 TL507C 1.20
MK15 Dual Latched SS Relay 4.50		LM3914 2.40 TMS1121 8.50
MK16 Mains powered IR Transmitter 3.50		LM3915 2.40 TMS1601 9.50
MK17 Single channel IR Receiver (12V) 10.50		LM13600 1.10 UA2240 1.45
MK18 Coded IR Transmitter 6.80		LS7210 4.75 UAN2003 7.5
MK19 DC Controlled Audio Amplifier 10.70		LS7220 2.75 UAN2004 7.5
*Includes box. 1 Includes frontpanel. All kits include PCBs, components and assembly instructions. For further details send S.A.E.		LS7225 2.60 ZM414 8.0
		MF10C 2.97 ZM425 3.40
		ML922 3.80 ZM427 5.70
		ML924 2.50 ZM428 4.50
		ML925 2.10 ZM1004E 1.80
		NOW IN STOCK SP0256A12 4.15

SPECIAL OFFERS

2716	3.10	280A PIO	1.99
2732	3.20	280A CPU	1.99
2764	4.20	6821	1.40
27128	7.50	11	

COMPONENT PACKS

1 650 Resistors 47R 10M	4.00
10 per value	
2 40 15W Electrolytics 10 1000µF	3.25
5 per value	
3 60-Polyester Capacitors	5.55
0.01µF 250V 5 values	
4 45 Presets 100R 1M	3.00
5 30 Low Profile IC Sockets	2.40
8 14 & 16 pin	1.75
6 25 Red LEDs 5mm	

We stock: VERD, VELLEMAN KITS, PANTEC KITS, ANTEK IRONS, BOOKS FROM BABANI, T.I. AND ELEKTOR.

For FREE 28 page catalogue send 9x6 SAE today!
Telephone Orders Access & Barclay Card
RING 01-567 8910 (24 Hrs)
Five Six Seven Eight Nine Ten

CRICKLEWOOD ELECTRONICS LTD

FREE! catalogue

It's no secret...

... that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED
40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161
Telex: 91 4977

Intruder Alarms and Accessories

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

contains:
Control Unit
Enclosure & mechanical fittings
Key Switch & 2 keys
LE D's
5 1/2" Horn Speaker
4 high quality surface mounting Magnetic Switches

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95+VAT. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straightforward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today.
Order Code: CS 1370

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 & its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.
Order Code: CS 1480

ALARM CONTROL UNIT CA 1250 Price £19.95+VAT.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system, whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm/tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

TIMER SWITCH & POWER SUPPLY MODULE OP 3570 Price £13.95 + V.A.T.

The OP 3570 consists of an adjustable timer switch and stabilised 12V power supply for use in a wide range of applications including security, lighting control and automatic switching.

The timer section of the module provides switching of loads up to 3A for pre-set times, the duration of which may be set by the user to between 10 secs and 5 mins. The timed period may be triggered by the opening of a loop or the closing of external contacts, with the timed period commencing instantaneously or delayed to provide a form of entrance delay.

The power supply section of the module provides a 12V output of up to 250mA which is sufficient for most applications. The module operates from either 240V a.c. supply or a 12V battery for which trickle charge facilities are included. Connections to the module are by means of screw terminal connectors with no soldering needed.

For mounting the unit an attractive moulded enclosure is available.

ME 357 only £2.85 + V.A.T.

INFRA-RED SYSTEM IR 1470 only £25.61+V.A.T.

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications.
Size 80 x 50 x 35mm

SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063 only £37.00 + V.A.T.

Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - ON, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865 Key Switch 3901, 3" Speaker 3815

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90db of sound or even 110db with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063.

HARDWARE KIT HW 1250 only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label.
Size 200 x 180 x 70mm

DIGITAL ULTRASONIC DETECTOR US 5063 only £13.95 + V.A.T.

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

- 3 levels of discrimination against false alarms
- Crystal control for greater stability
- Adjustable range up to 25ft
- Built-in delays
- 12V operation

ULTRASONIC MODULE ENCLOSURE only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063, for US 4012 order SC 4012.

SIREN & POWER SUPPLY MODULE PSL 1865 only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110db at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

RISCOMP THE SECURITY SPECIALISTS!

Add 15% VAT to all prices
Add 70p post and packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 pm
Closed Wednesday

Saturday 9.00 to 1.00 pm
SAE with all enquiries
Order by telephone or post
using your credit card

FULL RANGE OF ACCESSORIES STOCKED SEND SAE FOR DETAILS

RISCOMP LIMITED
Dept ET1/6
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326

ETI JUNE 1985

ELECTRON SECOND PROCESSOR

Speed-up your Electrons and watch your memory expand with a 6502 second processor, designed by John Wike with Electron owners in mind.

This article describes the addition of a second processor board to an Acorn electron, making 30K bytes of RAM available to BASIC (60k to machine code), and giving an increase in processing speed of up to three times.

The hardware will be described this month and the software next month, together with a complete assembly listing.

What about the others?

Although the term 'second processor' is usually associated with Acorn and their 'Tube' system, multiprocessor designs are found in several microcomputers in the business and scientific markets. Even the Sinclair QL contains two microprocessors, one to handle input/output and the other to do all the computing. So, although the circuit shown here is designed specifically for the Acorn machines, the concept is generally applicable.

It is relatively straightforward to design a circuit board with a processor and some RAM on it, and to interface it with an existing computer system. The real problem is the software, machine code of course, to handle the new hardware.

As the host machine probably has the screen RAM within its memory map, it must be assumed that it will retain the input/output handling functions. This means that the language (usually BASIC) will operate in the second processor.

It is necessary to know how to intercept the input/output routines (PRINT, INPUT, SAVE, LOAD, etc.) so that the data will

be transferred to or from the second processor's memory instead of the host's. Routines can then be written to reside in each processor's memory and allow them to communicate with each other transparently, so that the user will not be aware of any difference in operation from the basic machine.

All this sounds involved, but given a machine that is well supported by reference material and ROM listings, or your own skill at disassembly, it is by no means impossible. So if you are interested have a go!

2P or not 2P?

The owner of an Acorn machine does not need to worry about the foregoing because this article will cover all the ground. He or she will however have to decide whether it is worthwhile adding a second processor to the system. There are several advantages to balance against the effort involved:

Speed

The benchmark system has gained widespread acceptance as a qualitative assessment of the processing speed of a computer. For a full discussion of benchmarks the reader is referred to the

February 1985 edition of Computing Today. Each test consists of 1000 iterations of specific instructions, the times for which are given in Table 1. Also included for interest are the timings for the BBC computer, taken from the Computing Today article. In Mode 6 the unexpanded Electron is approximately 50% slower than the BBC, and in Mode 0 it is 250% slower! With the E2P board fitted it is approximately the same as the BBC in all modes.

Memory

The display memory in the Electron can consume between 8K of RAM in Mode 6 and 20K of RAM in Modes 0, 1 and 2. Add to this the 3.5K used as operating system workspace, up to 1.5K for user-defined characters and an extra 3.75K if the Plus 3 disc drive is fitted, and out of a total of 32K there might only be 3.25K available for programs. The E2P board contains 64K RAM, 30K of which can be used from BASIC whatever the configuration. Machine code programs can use a massive 60K.

Processor

The first requirement of the design was that the hardware and software should react with the Electron operating system in the same way as the official 'Tube'.

Benchmark	Mode 6	Mode 0	E2P	(BBC)
1	0.93	2.11	0.68	0.8
2	4.01	9.35	2.99	3.1
3	11.54	26.97	8.43	8.3
4	12.27	28.86	8.95	8.7
5	12.85	30.15	9.37	9.1
6	19.51	45.72	14.35	13.7
7	30.09	69.88	22.24	21.3

Table 1 Benchmark timings for the Electron with and without E2P.

This is a ULA with eight bi-directional registers, addressed at FCE0 h to FCE7 h, of which seven are used by the support software and only one, at FCE5 h, is accessed directly by the operating system for data transfer during, for example, LOAD and SAVE. So the circuit must detect accesses at FCE5 h and interrupt the second processor to allow it to pass the required data. The other registers can be at any convenient address, since they have their own support software.

The only storage device on the board is the RAM. The top 256 bytes of that are accessible to the Electron, so that several locations can be used as the bi-directional registers. Also, as this is the area where the 6502 goes at Reset, the Electron can control its reset and transfer sufficient code there beforehand to allow it to "boot up". After that the rest of its operating system can be sent via the data byte at FCE5 h.

When deciding where in the Electron memory map to locate

this 256 byte block, it was remembered that sideways ROMs are given the opportunity to initialise themselves at BREAK and to declare themselves during the *HELP command. The block is therefore addressed as a sideways ROM and the first eleven or so bytes are taken up with the necessary data for it to be recognised by the operating system. They also contain a jump instruction so that the 'ROM' software can be in the main program in the Electron RAM.

In order to refresh the dynamic RAM the processor is interrupted every 1 ms and a specific routine scans 128 bytes in 64 μ s. On alternate interrupts it scans another 128 bytes to include all the rows in the RAM. This results in a time overhead of 6% which is considered acceptable by the author. Because the refresh is software controlled there is no facility for a hard reset of the processor. Instead, the 'sideways ROM' routine issues an initialisation request on BREAK.

Interfacing


The board is designed to slot into one of the cartridge sockets on the Plus One interface unit, which provides some of the address decoding. For those people without a Plus One, a circuit is shown allowing connection to the basic Electron.

Current consumption of the board is about half an amp, which the author's machine was able to cope with. If a lot of other devices are drawing power, it may overload the supply. A link (LKI) is provided to disconnect the 5 volt line from the edge connector and an alternative supply can then be connected to the board.

Construction

Construction of this project is straightforward but you are recommended to use a fine tipped soldering iron, and to check the board closely to see that no stray bits of swarf or solder are shorting tracks.

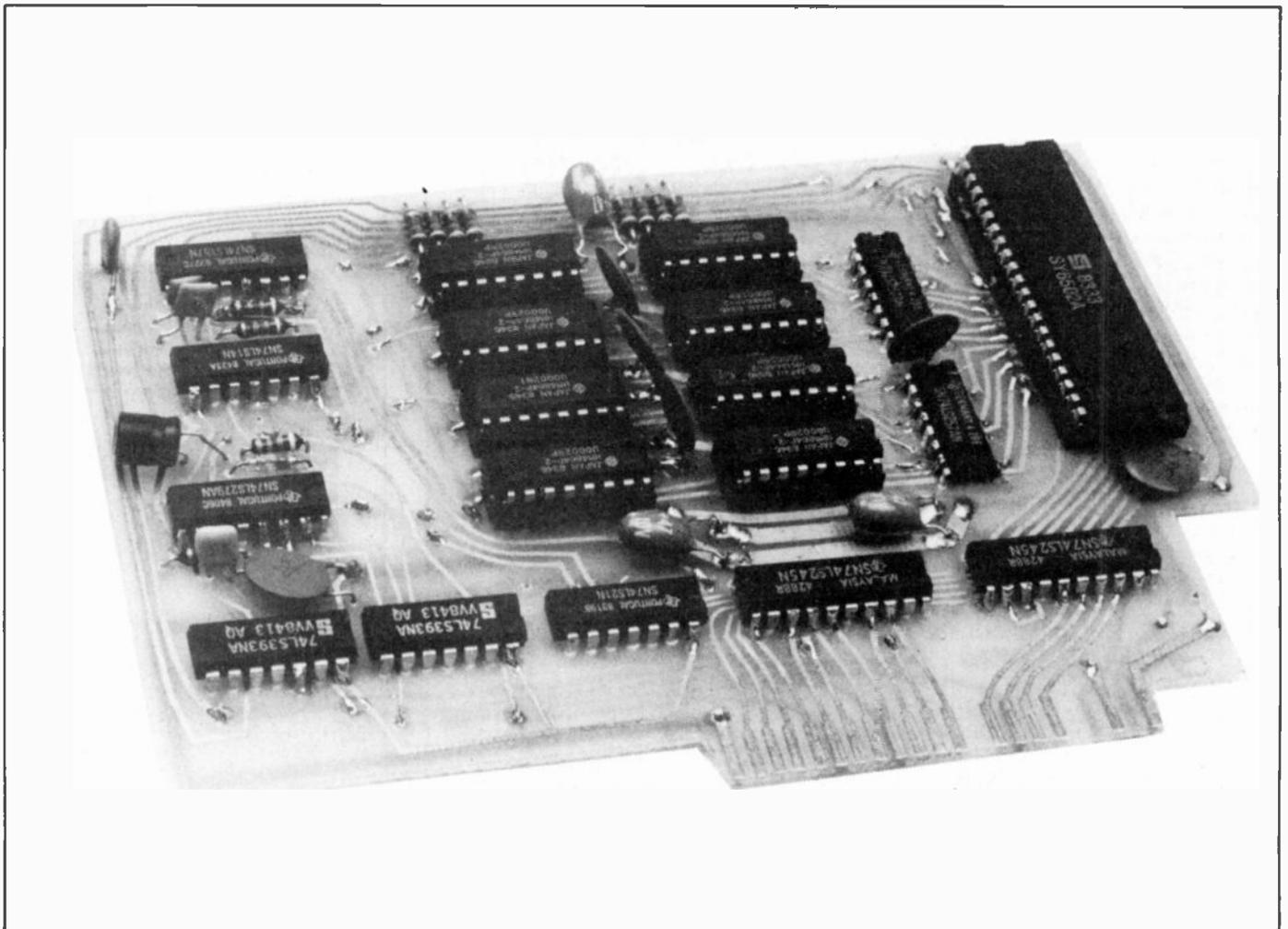As this is a double sided PCB and is not plated through, the first



The author's prototype second processor board (some changes have been made in the final version).

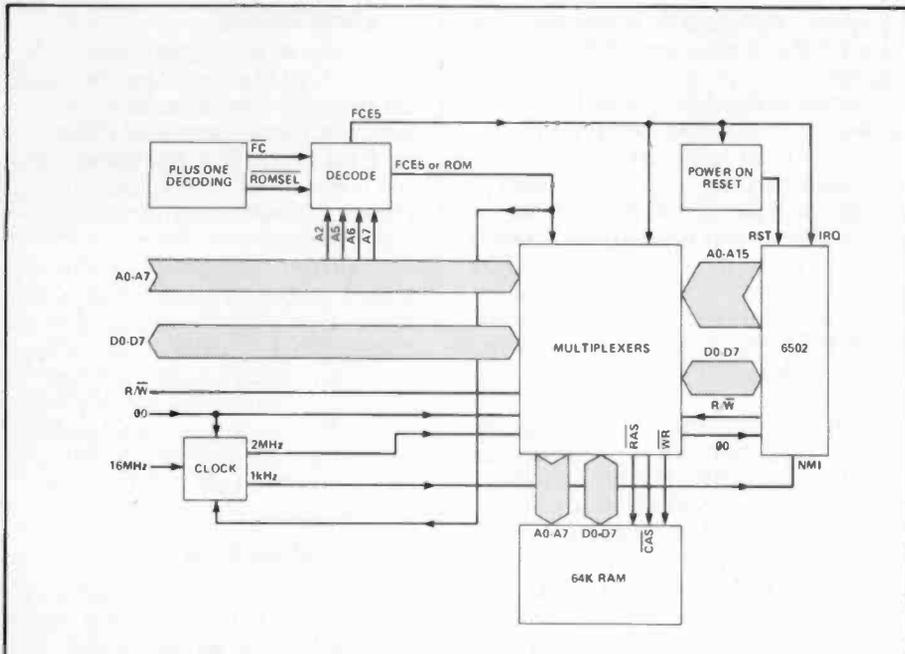


Fig. 1 Block diagram of the second processor board.

thing is to insert all the links and solder them on both sides of the board. Take special care not to miss the ones underneath ICs as these will be impossible to fit afterwards.
Next fit all the ICs except the RAMs and the processor, soldering

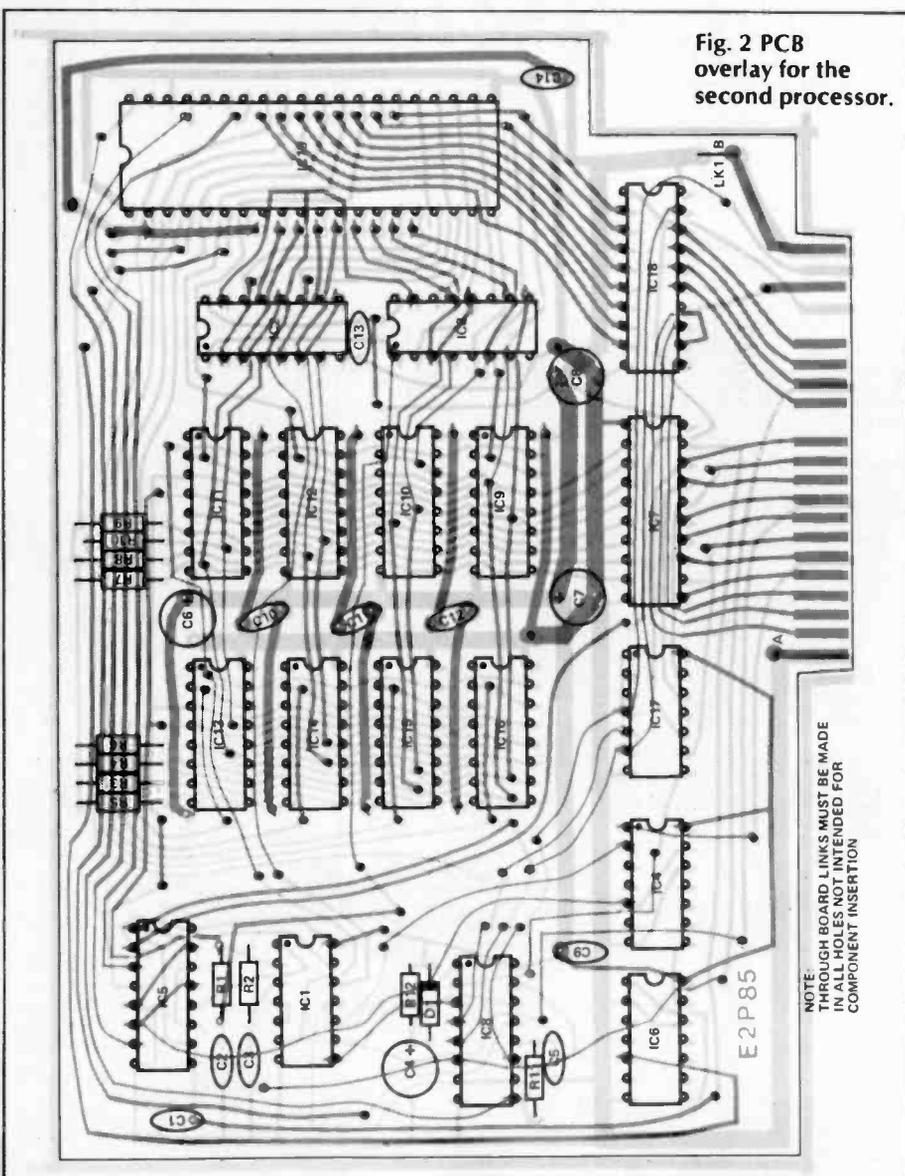


Fig. 2 PCB overlay for the second processor.

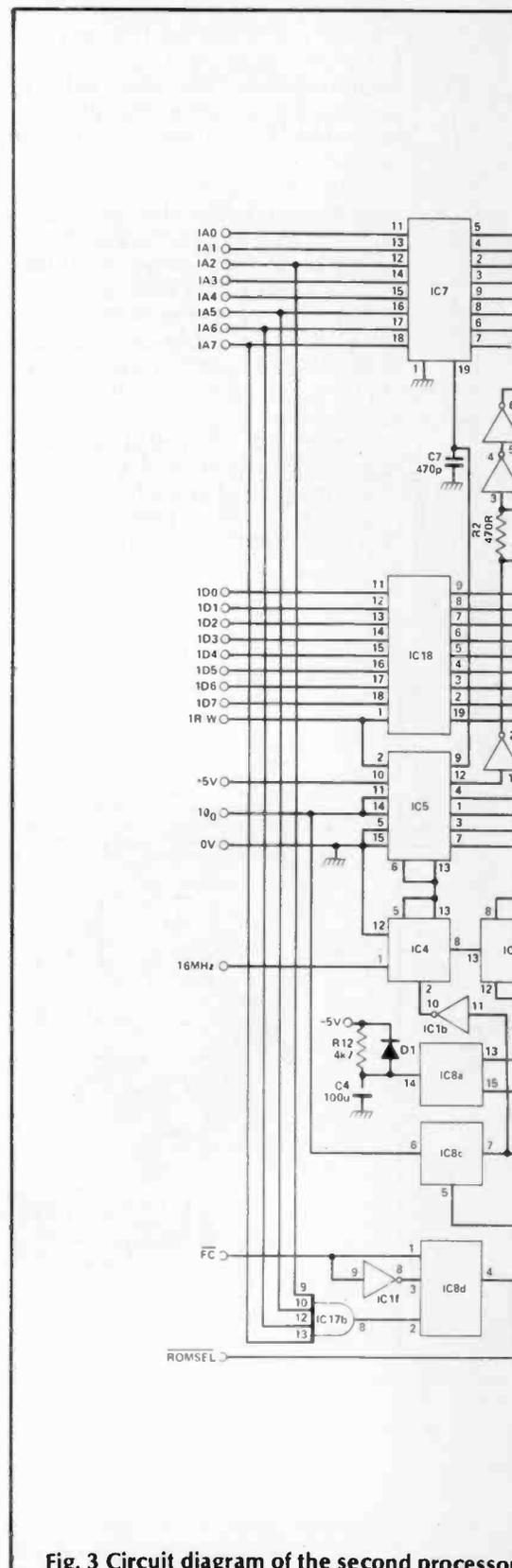


Fig. 3 Circuit diagram of the second processor

PROJECT: Second Processor

their leads on the bottom, top or both, as necessary.

Next fit the resistors, capacitors and diode. Some of these components need to be soldered on both sides of the board.

Now fit the sockets for the RAMs and processor. Use insulat-

ing tape to protect the through-board links before inserting the sockets.

If you intend to power the board from the Electron's 5 volt line fit the link LK1. Otherwise, connect the external supply wires to points A (0 volt) and B (5 volts).

Finally, insert the RAMs and processor into their sockets.

If you do not have the Plus One unit you will now have to construct the interface circuit. This could be done on Veroboard and then connected, along with the second processor board, to the

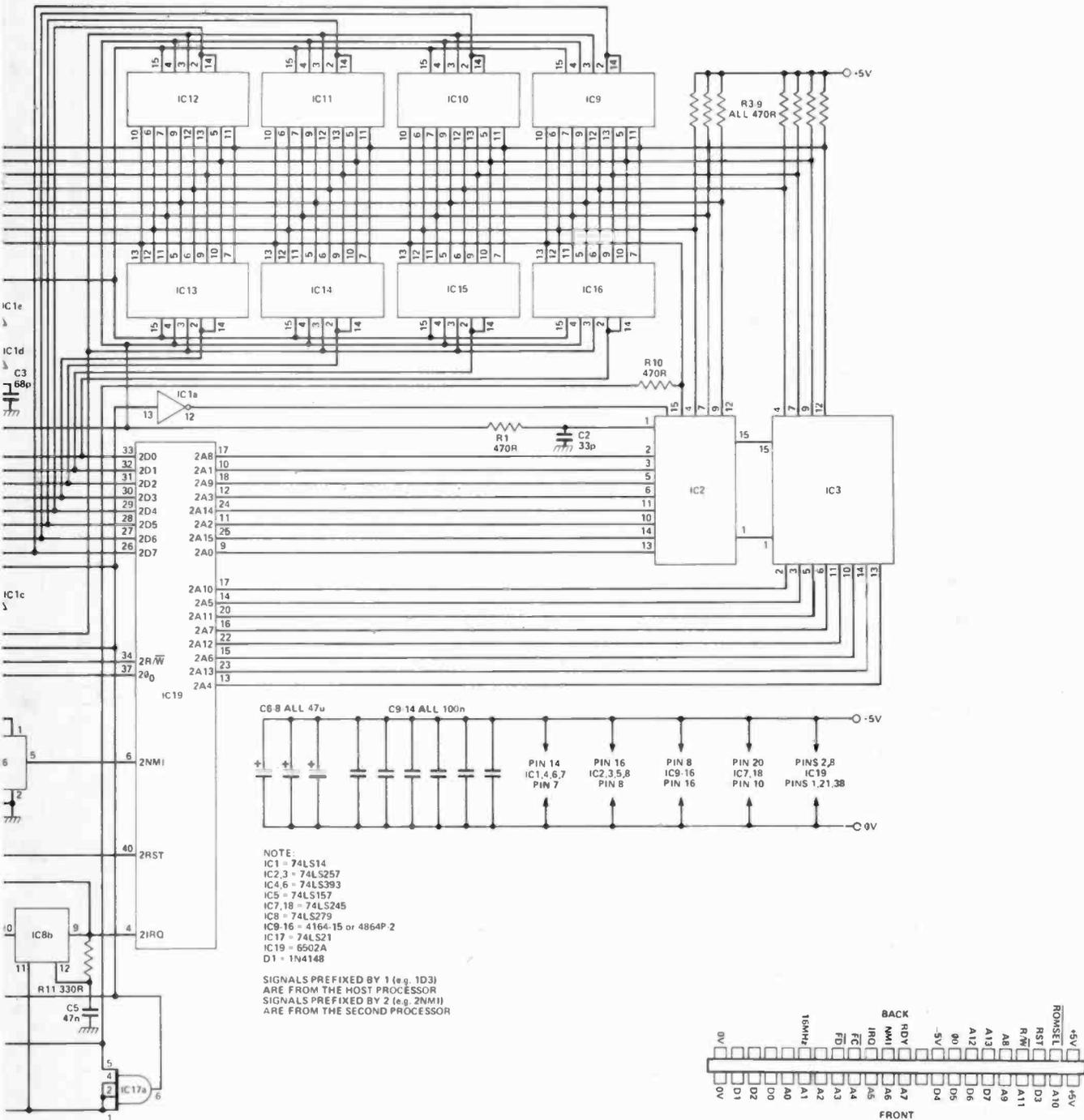


Fig. 4 Plus One cartridge socket edge connector.

PROJECT : Second Processor

PARTS LIST

MAIN BOARD

RESISTORS (all 1/4 watt)

R1,2,3,4,5,6,7,8,	470R
9,10	
R11	390R
R12	4k7

CAPACITORS

(all ceramics unless stated)


C1	470p
C2	33p
C4	100 μ electrolytic
C5	47n
C6, 7, 8	47 μ 10V tantalum
C9,10,11,12,13,14	100n

SEMICONDUCTORS

IC1	74LS14
IC2,3	74LS257
IC4,6	74LS393
IC5	74LS157
IC7,18	74LS245
IC8	74LS279
IC9,10,11,12,13	4164-15/4864P-2
14,15,16	
IC17	74LS21
IC19	6502A (2Mhz)
D1	1N4148

MISCELLANEOUS

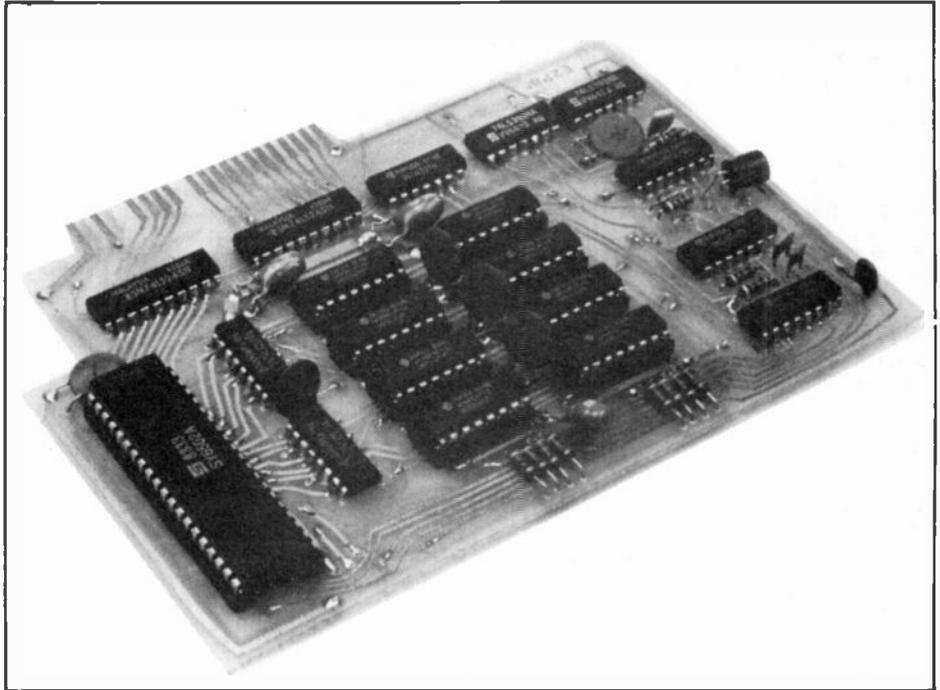40 pin DIL socket, 8x16 pin DIL sockets, wire for links.



BUYLINES

All the components are available readily from advertisers in ETI. The PCB and software are available from the author, John Wike, at 9, Lon-y-Garwa, Caerphilly, Mid-Glamorgan. The price of the PCB is £12, software on tape

is £3.50, and on your disc £2.00, inclusive of postage. If you send a disc please state whether you wish to have the !BOOT file put on it.

ETI

ATTENTION ALL WRITERS . . .

... or just those of you who sometimes think "I could do better than that!"

We want to hear from you!

The magazine you hold in your hand is part of ASP's electronics group of titles. These include *ETI*, *Ham Radio Today*, *Digital and Micro Electronics*, and our new magazine, *Electronics*. All these magazines are looking for new authors, so if you've designed something for yourself that you think may be of interest to others, or if you've a subject you'd like to write a feature article on, then drop us a line with an outline of what you have in mind.

We particularly need:

- Projects for the Commodore Vic 20 and 64, the Amstrad, the BBC A and B, and the Electron computers;
- Simple projects that do something useful, perhaps in a novel or instructive way;
- Radio projects (not necessarily for radio amateurs);
- Features on amateur satellite radio.

If you're interested in writing for us, send an outline of your proposed article to: Dave Bradshaw, Group Editor (Electronics), Argus Specialist Publications, 1 Golden Square, London W1R 3AB.

Please note that while we take ever care, we cannot be held responsible for the loss of unsolicited manuscripts. We advise all authors to keep a photocopy or carbon copy of any article they send us.


LOW COST AUDIO MIXER

This modular mixer from John Linsley Hood is not super-fi, but it is cheap, portable and so versatile you can use any source, except the kitchen sink.

The instrument described here was designed and built for the use of the local 'Talking Newspaper for the Blind', and the circuitry shown was specifically tailored for their needs — which were, basically, for a control console containing the necessary electronics, and fader pots, so that the operator could mix in various voices with programme material from other sources — disc, radio or tape — to produce a final stereo tape cassette. This would then be duplicated for distribution to subscribers.

The general layout is versatile enough for the actual inputs to be modified for other types of input. I will show some of the other input circuits which may be slotted in, in place of, or in addition to, the existing layouts.

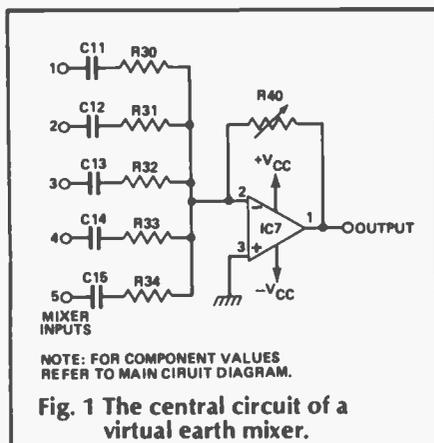One general requirement for all such mixer consoles is the provision of a reasonably quality stereo headphone monitor facility, allowing the control engineer to hear just what he or she is putting on to the tape. The unit has been designed to be operable from a battery DC supply. It could be used as a fully portable 'studio' in conjunction with a suitable battery operated cassette recorder.



No VU metering system has been provided since it is assumed that the recorder used will have this facility.

Basic Layout

The circuitry is organised around the virtual earth mixer layout shown in Fig. 1, which can be hooked up easily around an IC op amp and allows as many inputs as one wishes to be combined together into a common signal (although only five are shown in the diagrams).

This is a very powerful technique for mixing inputs, and has the great benefit that there is no leakage back from one input into another, since the inverting input of IC1 in this layout really does look like an earth point to the incoming signals. This also implies that the input impedance of the circuit is determined by the values chosen for each input resistor, R30, R31

The overall gain of the stage is determined, for any one input channel, by the ratio of R40:Rin (Rin being the input resistor). If R40 is variable (as shown in Fig. 1 but not in the main circuit diagram), the gain of all the input channels may be reduced or increased simultaneously.

The various inputs to this mixer stage are obtained from input stages of the types described below.

Line Input Stage

In the simplest case, where a signal is obtained from a radio or tape recorder having a line output socket — which will give 300-700mV output at a lowish impedance — all that is required is a simple slider pot connected as shown in Fig. 2. On the other hand, if it is known that the unit may be used with signal sources

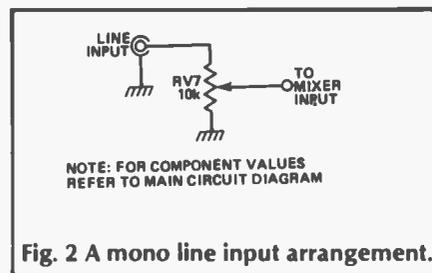


Fig. 2 A mono line input arrangement.

having outputs conforming to the DIN standard — in which the output is arranged to provide 1mV for each 1K of load impedance — the alternative arrangement of Fig. 3 can be used.

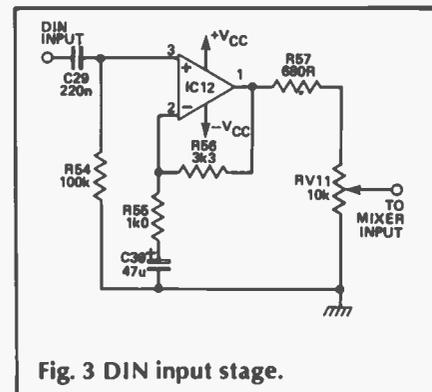


Fig. 3 DIN input stage.

This is quite a versatile system, and can be used with any input source where a flat frequency response is all that is needed, and where the input signal level will not exceed more than about 0.5V RMS.

Microphone Input Stage

This uses an identical circuit layout to that of Fig. 3, but with the values of R55 and R56 changed to R11 and R16 in Fig. 4 to give a higher gain, since the expected output signal level from the mic may be only 2-3mV. The input impedance is also made switchable between 100K and 4K7 (R1 and SW1 in Fig. 4) to suit either crystal or dynamic (moving coil)

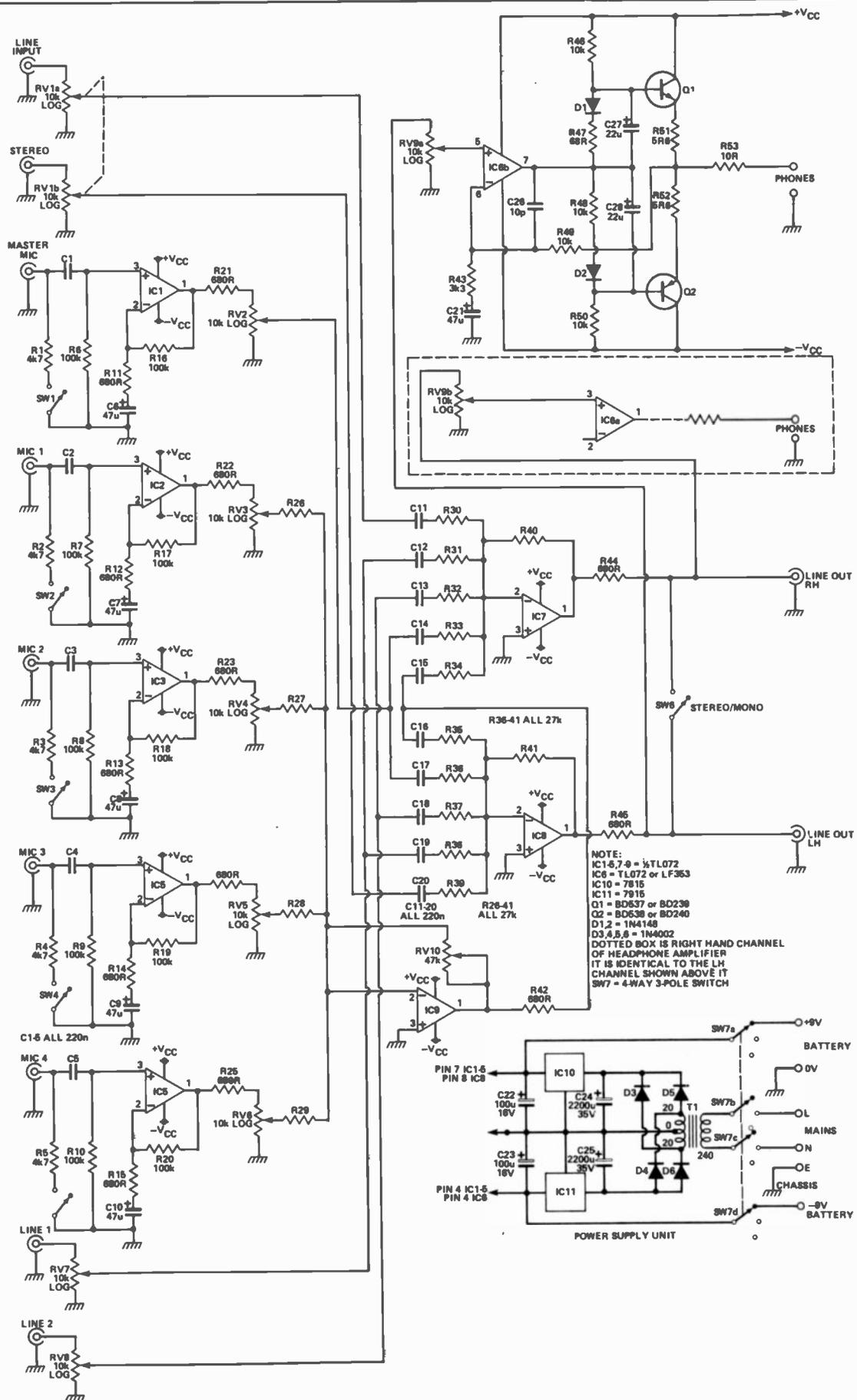


Fig. 10 Circuit diagram of the complete prototype mixer and Fig. 11 (opposite) overlays for the mixer and PSU boards.

Gramophone PU Inputs

This facility was not required for the actual unit which was built, but there is no difficulty in modifying the op amp input stage to provide the required gain and frequency response characteristics. The circuit for this is shown in Fig. 5. Since I am not aiming at the 'ultimate-fi' in this unit, I feel that a conventional series feedback layout, as used in 99.9% of domestic hi-fi amplifiers, will be quite adequate.

The op amp output resistors in the DIN, mic and RIAA stages (R57, R21 and R62, respectively), are included to prevent changes in the loading of the op amp, due to the setting of the output gain controls, which would alter the frequency response characteristics of the gain stage.

Headphone Output Stage

This is fairly conventional, and again uses an op amp as the gain block, to which some muscle power is added by the transistors Q1 and Q2. These are biased into class A by the diode/resistor network R46-R50, D1 and D2. A small capacitor, C26, is connected across the op amp to ensure HF stability. Several pairs of headphones can, if necessary, be connected in parallel, across the output, provided that the isolating resistors (R53) are taken separately to each output jack. This will ensure that there are no problems if phones of dissimilar type of impedance are used. (See Fig. 10).


Mains Power Supply

Although the mixer unit can be used quite satisfactorily on a pair of 9V batteries, batteries are expensive and it is probable that it will be powered from the mains on most occasions. A very simple dual power supply, with a couple of voltage regulator ICs, was used on the prototype, as shown in Fig. 10.

Complete System

The whole unit is shown in Fig. 10 and fitted into a shallow sloping fronted box, 19" long, as shown in the photograph.

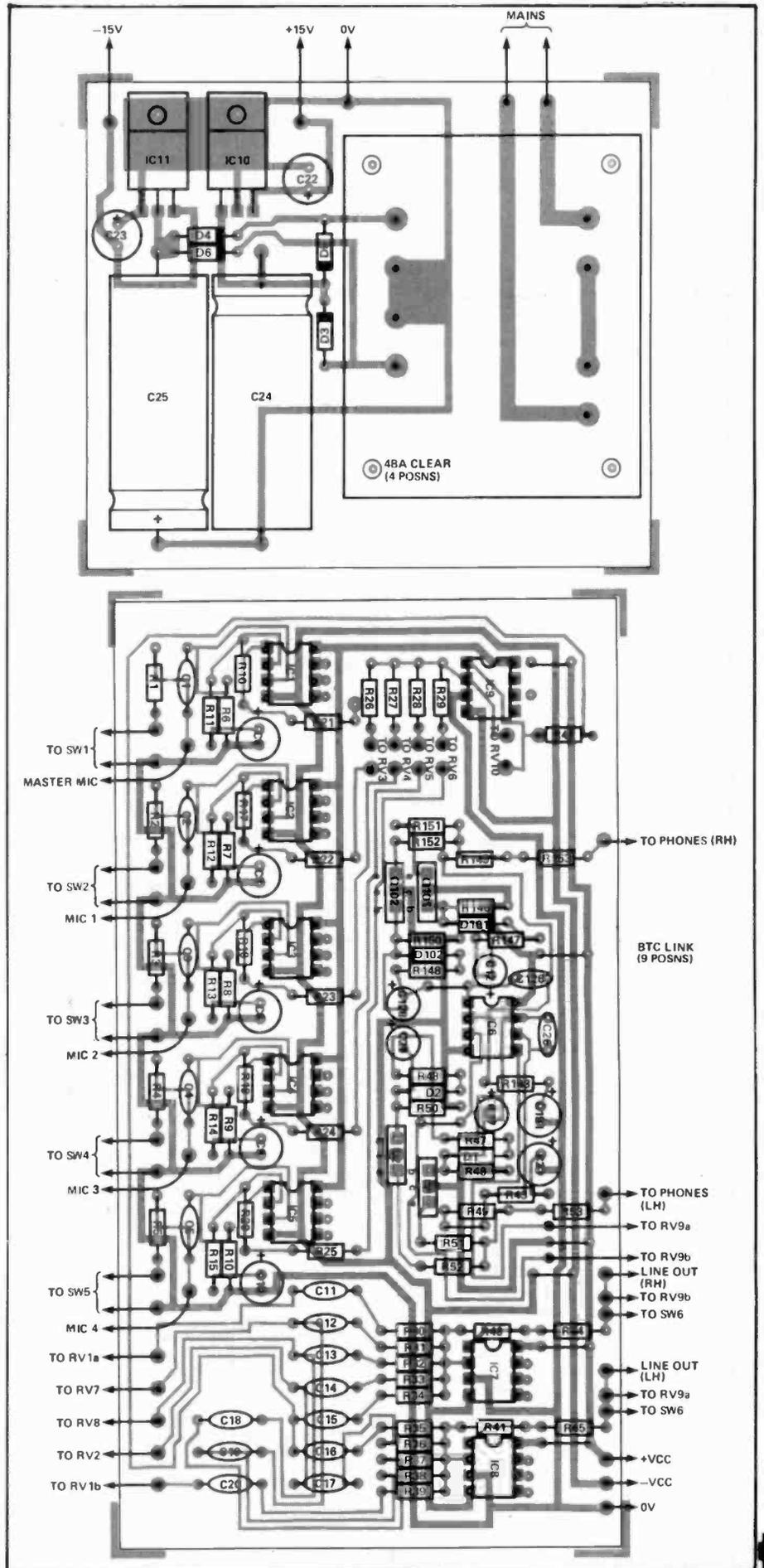Since the specification to which this unit was built called for a stereo line input, as well as a pair of mono line inputs, a ganged 10K slider pot was used for RV1, while single slider units were employed for RV7 and RV8. The four main mic inputs are controlled individually by the slider pots RV3 to



PROJECT: Audio Mixer

RV6, with a master fader, RV10, controlling their overall level so that it can be faded down if, for example, a voice-over commentary is to be superimposed from the master mic.

A dual-gang slider pot, RV9, is used to control the volume level of the headphone outputs. Finally, an overriding stereo/mono control is provided by SW6, which simply parallels the two L and R outputs. In general, however, the unit is used in the stereo mode, with a stereo signal from the line input, over which the (mono) mic input

voices appear on 'centre stage'.

No tone control facilities were required for the unit described in its initial embodiment (shown in the photograph), but subsequently a microphone input treble lift facility was added, to give greater clarity to some of the commentators' voices. This was done as shown in Fig. 7. The unit can completely replace the mic input shown in Fig. 4.

A more formal bass/treble-lift/cut tone control stage could be added, at pin 1 of ICs 7 and 8 in Fig. 10. The tone control circuit is

shown in Fig. 8.

Full stereo system

It is very easy to organise this layout to provide more stereo input channels than the one stereo line input on the prototype.

This is done by taking each pair of inputs, say those from IC2 and IC3 (Fig. 10) and routing them to a pair of master fader stages, IC16a and IC16b, as shown in Fig. 12, and from there to ICs 7 and 8, as before.

The prototype unit was designed round TL071s or their higher specification equivalents, LF351. To enable the addition of extra facilities with relative ease, we have designed the board using TL072s (or LF353s) exclusively. Pads for the unused halves of the op amps can be found on the main PCB.

BUYLINES

There should be no problems with any of the components. Slider pots are widely available, but rotaries would suit. Wirewounds should be available from Watford, Maplin, Electrovalue or any regular ETI advertiser. Watford and Rapid also advertise 3 pole 4 way switches. 19" cases are available from Newrad or through our classifieds. The PCBs are available from the ETI PCB Service

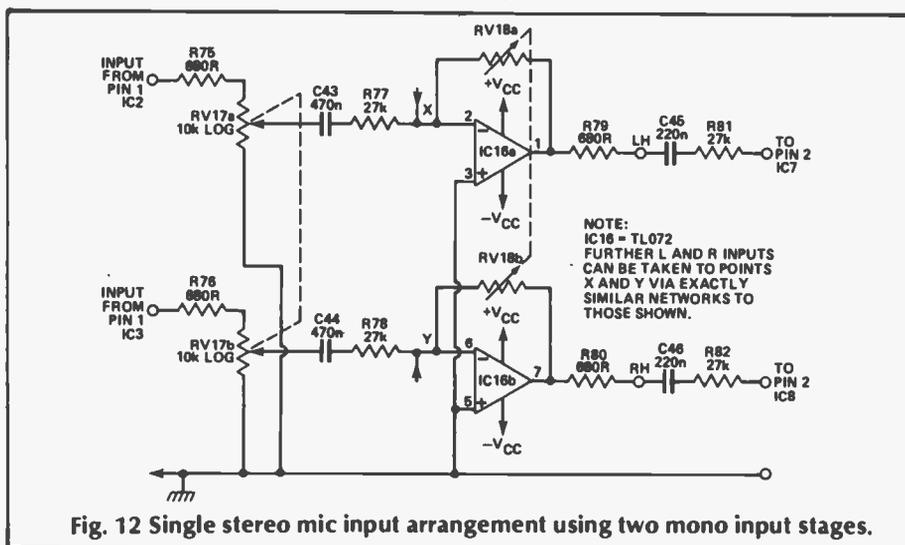


Fig. 12 Single stereo mic input arrangement using two mono input stages.

PARTS LIST

MAIN BOARD

RESISTORS (all 1/2 watt unless stated)

R1,2,3,4,5	4k7
R6,7,8,9,10,16,17	100k
18,29,20	
R11,12,13,14,15	680R
21,22,23,24,25,42,	
44,45	
R26,27,28,29,30	27k
31,32,33,34,35,36,	
37,38,39,40,41	
R43	3k3
R46,49,50	10k
R47,28	68R
R51,52	5R6 W/W
R53	10R W/W
RV1,9	10k log
RV2,3,4,5,6,7,8	10k log
	ganged sliders
RV10	47k
	single sliders
	47k
	single slider

CAPACITORS

C1,2,3,4,5,11,12,	
13,14,15,16,17,18,	
19,20	47µ 16V
C6,7,8,9,10,21	electrolytic
	100µ 16V
C22,23	electrolytic
	2200µ 40V
C24,25	electrolytic
	10p
C26	22µ 16V
C27,28	electrolytic

SEMICONDUCTORS

IC1-6,8,9	TL072/LF353
IC10	7815
IC11	7915
Q1	BD537/BD239
Q2	BD538/BD240
D1,2	IN4148
D3,4,5,6	IN4002

MISCELLANEOUS

SW1,2,3,4,5,6 SPST switches
SW7 3 pole, 4 way switch
Standard jack sockets (13 for main board configuration); PP9 battery clips (x2); 20-0-20 20VA transformer, TR1; 19" shielded cabinet.

(Note: R43-53, C21, 26-28, Q1-2, D1-2 have corresponding components for the right-hand headphone amplifier. They are marked R143-153, C121, 126-128, Q101-102, D101-102 on the overlay diagram).

OPTIONAL BOARDS

RESISTORS (all 1/2 watt)

R54,64,66	100k
R55	1k0
R56	3k3
R57,62,67,74,75,	680R
76,79,80	
R58	47k
R59,68	390R
R61	120k
R63,70	4k7
R65,71,73	2k2

RESISTORS

R69,72	10k
R77,78,81,82	27k
RV11,12,13	10k log sliders
RV13	1k0 slider
RV15,16	100k sliders
RV18	47k ganged slider

CAPACITORS

C29,35,45,46	220n
C30,36	47µ 16V
C31,43,44	electrolytic
	470n
C32	100µ 16V
C33,40,42	electrolytic
	10n
C34	49n (22//27n)
C37	150n
C38	1µ0 ceramic
C39,41	47n

SEMICONDUCTORS

IC12-16	TL072/LF353
---------	-------------

MISCELLANEOUS

Standard jack sockets as required.

(Note: R58-62, RV12 and C31-34 have corresponding components on the second channel of the RIAA equaliser board. They are numbered R158-162. RV112 and C131-134 on the component overlay. Likewise for components R69-74, RV15-16 and C38-42 whose second channel equivalents on the tone control board are marked R169-174, RV115-116 and C138-142).

ETI

UNIVERSAL EPROM PROGRAMMER MKII

Following on from last month's article which covered the theory and described an upgrade modification for existing programmers, Mike Bedford and Gordon Bennett describe an improved EPROM programmer for those building from scratch.

Unlike the Mkl board, the MkII board has been made double sided to cope with the greater component density. In order to keep down the costs, plated through holes have not been used which means that the first task to be carried out in building this project is to insert pins into all the holes marked as such on the component overlay diagram, soldering them on both sides of the board. After having carried out this through pinning, the construction is quite straightforward. One point worth noting is that component leads are sometimes relied upon to make a connection from one side of the board to the other. This means that if a component lead passes through a hole with pads on both sides of the board, the lead should be soldered to them both.

The MKII board will be used in conjunction with a programming console housing a 28 pin ZIF (zero insertion force) socket and 2 LEDs (see photograph). The 2 LEDs on the console connect to the main board via a 3 or 4 core cable connected to SK4, the anodes being connected to A1 and A3, the cathode of the green LED to A2 and the cathode of the red one to A4. The ZIF socket is connected via a length of ribbon cable and a

28-pin DIL header to SK3 on the main board on a pin to pin basis. It should be noted that the DIL socket SK3 is the "wrong way round" with respect to all the DIL ICs on the board and accordingly care should be taken in plugging in the ribbon cable to the console. A 0.1uF capacitor should be connec-

ted between pin 28 and pin 14 on the ZIF socket.

Construction having been completed, it now remains to configure the board to reside at the required address and to set up the various Vcc and Vpp voltages. The addressing is determined by the links, LK1, which are wired into a

OOPS!

Since the appearance of last month's article, a problem has come to light regarding the programming of 27512 EPROMs.

The problem occurs when using the fast programming algorithm with the 27512 and results from the necessary sequence of operation adopted in the software. The \overline{OE} line is held high until dropped to access the EPROM for reading and the \overline{CE} line goes low as soon as the programming voltage is removed from the EPROM.


But on the 27512 the \overline{OE} line is also the Vpp select line and so, although this line is set low by the software at the correct time, the combined line is still held high by the \overline{OE} bit until it is time to read the EPROM. This is because the hardware combines these two lines in an OR gate. The effect is to hold the 27512 in programming mode for an extra 300 micro seconds at a time when, although the address and data busses should not be varying, the programmer itself is changing from program to verifying mode. It is quite possible that this would cause no ill effects, but it is undesirable and should be corrected.

A software solution would require a

separate procedure for the 27512 in an already crowded EPROM, but a far simpler hardware modification is possible. It consists of the removal of two diodes and the substitution of a wire link for one of them. The diodes in question perform an OR function at the input of the active pulldown circuit which operates on pin 22 of the EPROM. They were put there to prevent high dissipation in the 120R resistor by removing the possibility of the software turning on both transistors simultaneously. No problems have been found using the existing software package without these diodes, and their absence has no effect upon the operation of the programmer with other EPROMs.

The modification is:

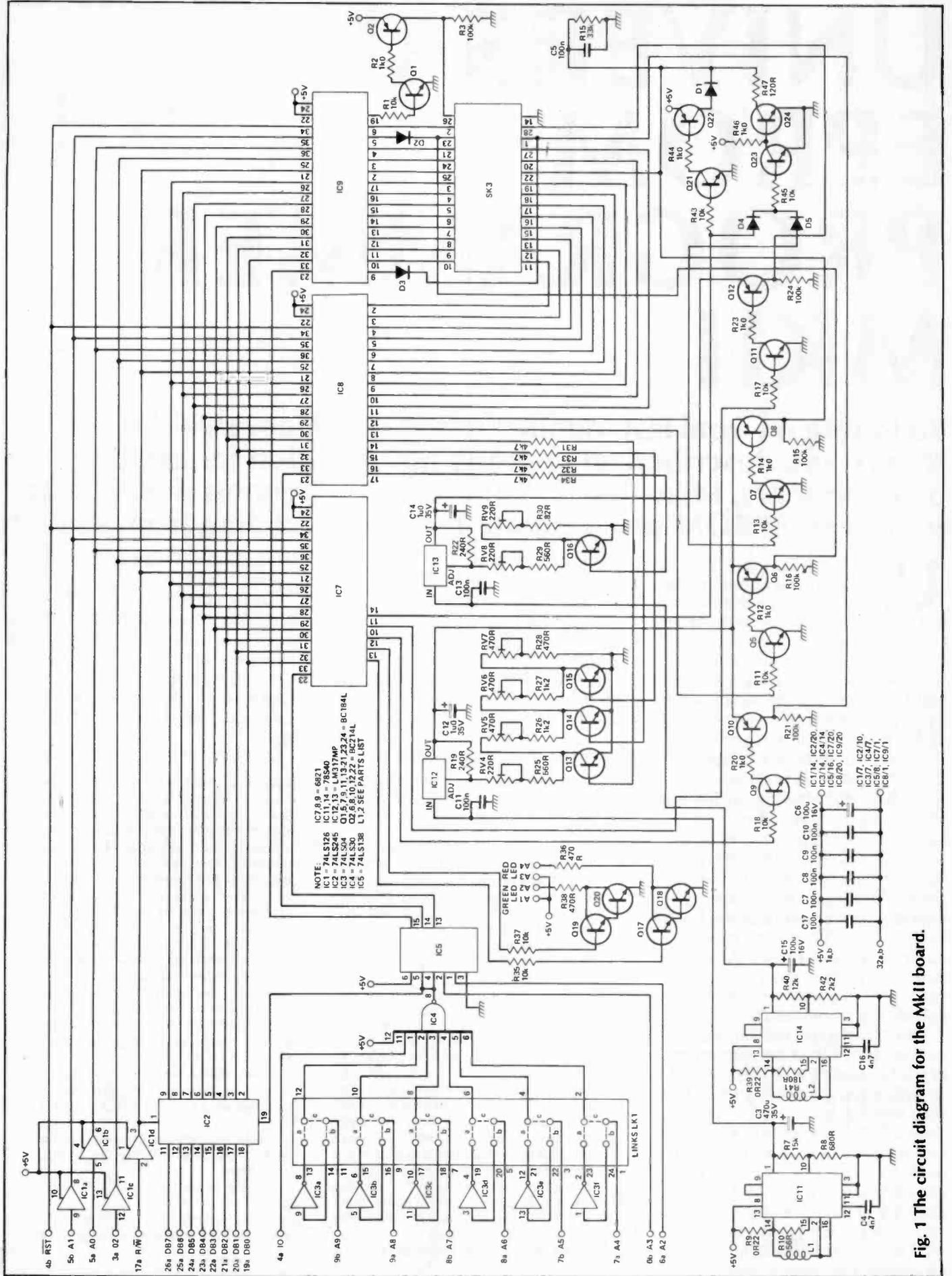- 1) locate and remove the diode in the line from pin 14 of PI0 3 (IC7), the \overline{OE} line;
 - 2) locate and remove the diode in the line from pin 12 of PI0 2 (IC8), the Vpp select line;
 - 3) replace this latter diode with a wire link.
- This will prevent the \overline{OE} line from influencing the pulldown of the Vpp/ \overline{OE} line.



NOTE:
 IC1 - 74LS126
 IC2 - 74LS40
 IC3 - 74LS245
 IC4 - 74LS04
 IC5 - 74LS30
 IC6 - 74LS133
 IC7 - 74LS133
 IC8 - 74LS133
 IC9 - 74LS133
 IC10 - 74LS133
 IC11 - 74LS123
 IC12 - 74LS123
 IC13 - 74LS14
 IC14 - 74LS14
 Q1, 5, 7, 9, 11, 13, 21, 23, 24 - BC184L
 Q2, 6, 8, 10, 12, 22 - BC214L
 IC15 - 74LS138 L.T.2 SEE PARTS LIST

Fig. 1 The circuit diagram for the Mk II board.

PROJECT: EPROM Programmer MkII

HOW IT WORKS

The components in Fig. 1, the circuit diagram of the Mk II board, have been numbered in such a way that they correspond to the component numbers on the Mk I and upgrade boards. Since a few components are removed from the Mk I board when the upgrade board is fitted there will be some gaps in the component numbers on the Mk II programmer. Once this is realised, this arrangement should cause less confusion than if components with the same function were to have different numbers in the two configurations.

The heart of the circuit is three 6821 PIAs which control all the programmer functions. These are interfaced in a standard way to the Tanbus signals on the edge connector. IC1 and IC2 buffer various signals to ensure that only 1 TTL load is applied to a bussed signal and the combination of IC3, IC4, IC5

and the links control the addressing and allow the board to be located within any 16 byte block in the I/O area. The Vpp supply is generated at +30V by the circuitry associated with IC11 which is a step-up circuit and is then regulated to the required level (+25V, +21V, +12.5V or +5V) by a programmable LM317MP regulator, IC12. Since the voltage output of an LM317MP is determined by the value of the resistor between the adjust pin and 0V, the Vpp level is controlled by switching the transistors Q13, Q14 and Q15 from PIA IC8 so cutting out portions of the resistor chain.


A similar approach is used to generate Vcc, IC14 generating +8V and IC13 regulating to +5V or +6V as controlled from IC8. Where a pin on the EPROM (which is connected to SK3) requires a TTL signal level it is

connected directly to an output of one of the PIAs. Where a Vpp or Vcc level is required, however, a NPN/PNP transistor pair is used to carry out the switching under the control of a PIA output. In all such cases the transistor pair must be connected to a PIA 'B' port, these having totem-pole outputs which can supply sufficient current to switch a transistor.

The signal level on some pins may be either TTL or Vpp, depending on the EPROM type. In such cases, both signals are connected to the appropriate pin but the two are isolated from each other by use of a diode on the TTL signal line. When a TTL level is isolated by a diode, this is driven by a PIA 'A' port since these outputs have resistive pull-ups and will give a level that is high enough to be a true TTL high even after allowing for the voltage drop

across a germanium diode.

The data sheets for the 2732 call for a 100uF capacitor (C5) connected between pin 22 and 0V while programming. This will suppress spikes on the Vpp supply which could be detrimental to the EPROM. Unfortunately the provision of such a suppression capacitor will have the result of slowing down logic edges when a TTL level is applied to pin 22. For this reason, the time constant is kept to a minimum by using Q21 and Q22 as a high current OE drive and Q24 to provide a logic low bypassing C5. Transistor Q23 turns on Q24 when neither the OE nor the Vpp signal driving EPROM pin 22 is present. To complete the circuit description, Q17, Q18, Q19 and Q20 form two darlington pairs which are used to drive a pair of LEDs on the programming console.

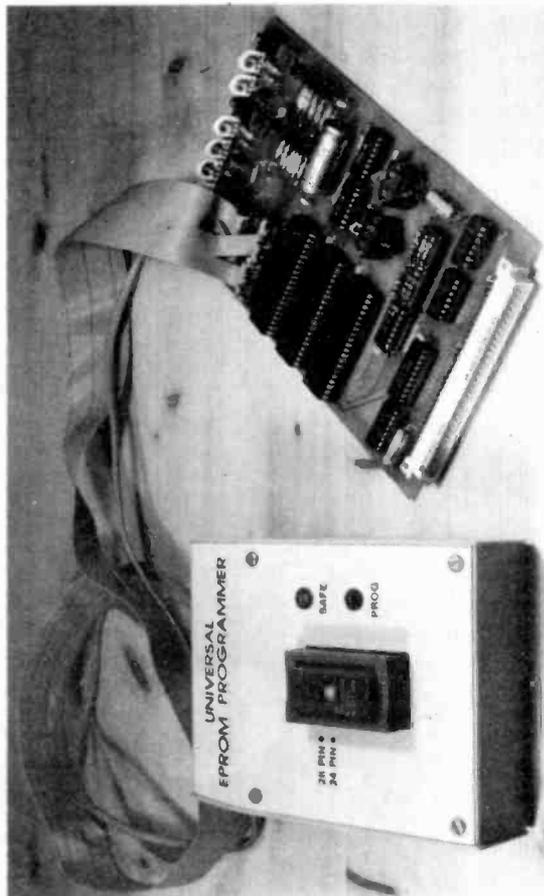

Voltage required	ZIF pin to monitor	Register address offset	Value to write to register (HEX)	Potentiometer to adjust
-	-	0B	00	--
-	-	0A	FF	--
-	-	0B	04	--
-	-	0A	03	--
-	-	07	00	--
-	-	06	FF	--
-	-	07	04	--
+5V	1	06	10	RV4
+12.5V	1	06	40	RV5
+21V	1	06	20	RV6
+25V	1	06	00	RV7
+5V	28	06	80	RV8
+6V	28	06	00	RV9

Table 1 The set-up arrangements for monitoring and adjusting program voltages.

PARTS LIST



Programming Console

- 1 x Instrument case with sloping top
- 1 x 28-pin DIL Zero Insertion Force socket
- 1 x Length of 28-way ribbon cable
- 1 x 28-pin DIL header
- 1 x 100 μ F ceramic capacitor
- 1 x Red LED
- 1 x Green LED
- 1 x Length of 4-way cable

DIL header and plugged into the appropriate DIL socket. The board occupies a 16-byte block within the 1K Tanbus I/O space, the start address relative to the start of this I/O area being 16 times the binary number represented by the block of links. The examples of link selection in Fig. 2 should make it quite clear how to set up any required addresses. The MkII board has been designed with the voltage setting potentiometers placed along the edge of the board so that they may be easily adjusted once the board has been positioned in a card frame. The voltages may now be monitored on the programming console and adjusted, using the potentiometers, by writing values to the programmer registers using the system monitor (or a BASIC program). Table 1 shows the requisite programming voltages, associated pins, registers, data and potentiometers.

MKII UNIVERSAL EPROM PROGRAMMER : HARDWARE SPECIFICATION

- Devices supported** : 2758, 2716, 2516, 2732, 2732A, 2532, 68732, 2764, 2764A, 2564, 68764, 27128, 27128A, 27256, 27512, 27513, 2816, 2864
- Device selection** : Software controlled
- Programming methods** : Intelligent or fixed pulse
- Vpp voltages** : +25V, +21V, +12.5V
- Vcc voltages** : +6V, +5V
- Indicators** : 2 LEDs on console
- PCB format** : 8" x 4½" with indirect connector
- Interface** : Tanbus (6502, 6800, 6809 adaptable)
- Power requirements** : +5V @ 900mA
- Memory space occupied** : 12 bytes selectable to any 16 byte boundary within the I/O area
- System requirements** : RAM — 1K for 2758 to 32K for 27256, 27512* and 27513* plus small amount for support firmware. (*:these EPROMs programmed in 2 segments)
EPROM — 2K utilities package

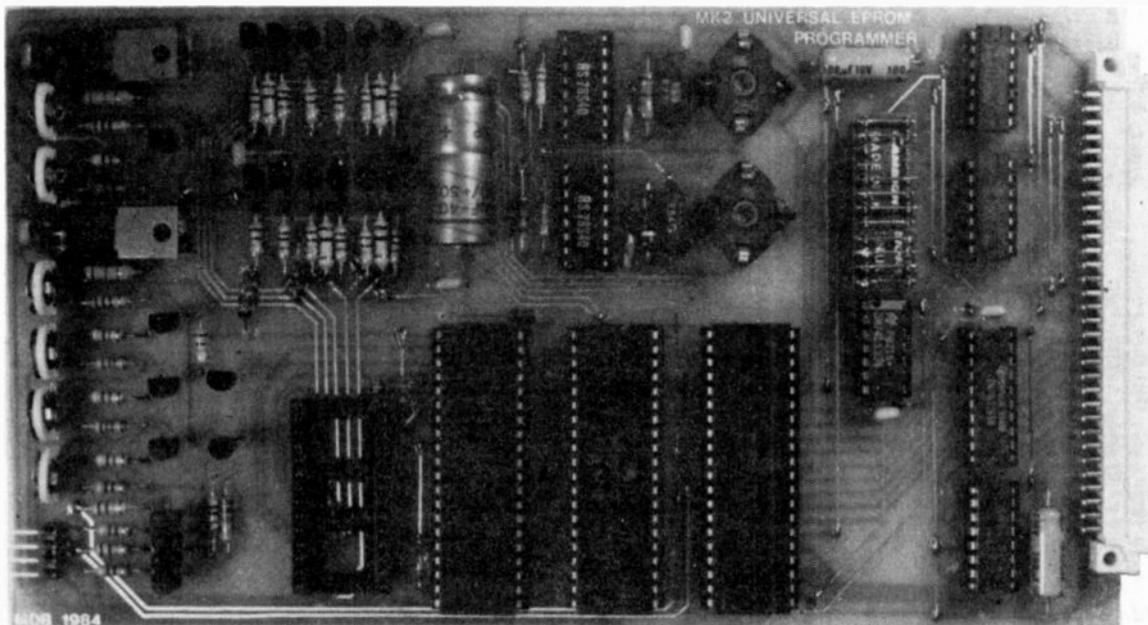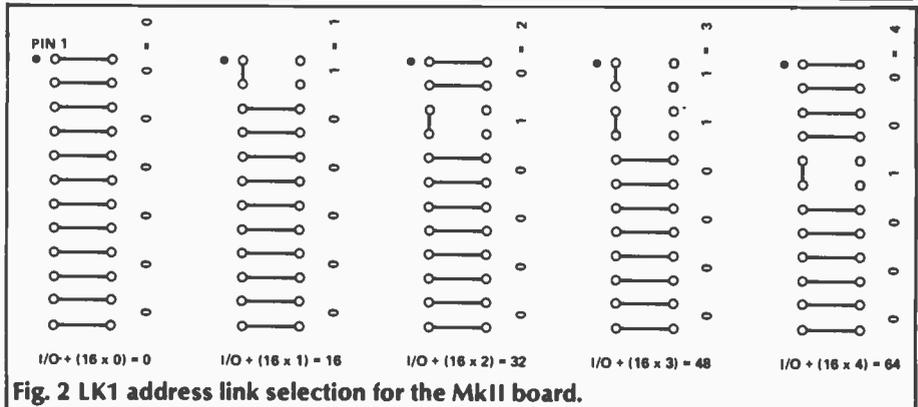

PROJECT : EPROM Programmer MkII

PARTS LIST

RESISTORS (All 1/4W, 5% unless stated)

R1,11,13,17,18,35, 37,43,45	10k
R2,12,14,20,23,44, 46	1k0
R3,15,16,21,24	100k
R7	15k 2%
R8	680R 2%
R9,39	OR22 W/W
R10	56R, 1W
R41	180R, 1W
R41	180R, 1W
R19,22	240R
R25,29	560R
R26,27	1k2
R28,36,38	470R
R30	82R
R31,32,33,34	4k7
R40	12k
R42	2k2
R47	120R 1/2W
RV4,8,9	220R vertical miniature preset
RV5,6,7	470R vertical miniature preset

CAPACITORS

C5,7,8,9,10,11,13, 17	100n Ceramic
C3	470µ 35V axial electrolytic
C4,C16	4n7 ceramic
C6,C15	100µ 16V axial electrolytic
C12,C14	1u0 35V tantalum

SEMICONDUCTORS

IC1	74LS126
IC2	74LS245
IC3	74LS04
IC5	74LS138
IC7,8,9	6821 (or 6520 etc)
IC11,14	78S40
IC12,13	LM317MP
Q1,5,7,9,11,13,14, 15,16,17,18,19, 20,21,23,24	BC184L
Q2,6,8,10,12,22	BC214L
D1,2,3,4,5,	OA91

MISCELLANEOUS

L1	34 turns 24 SWG wire on RM6 pot core (AL=250)
L2	13 turns 22 SWG wire on RM6 pot core (AL=250)
SK3	28 pin DIL socket
Connector A	4 way 0.1" pitch right angled molex connector.
Links	Links wired on 24-way 0.3" width DIL header plugged into DIL socket (use 16-way +8-way)
PCB;	1 x 32-way A+B DIN Euro connec- tor, male angled pins.

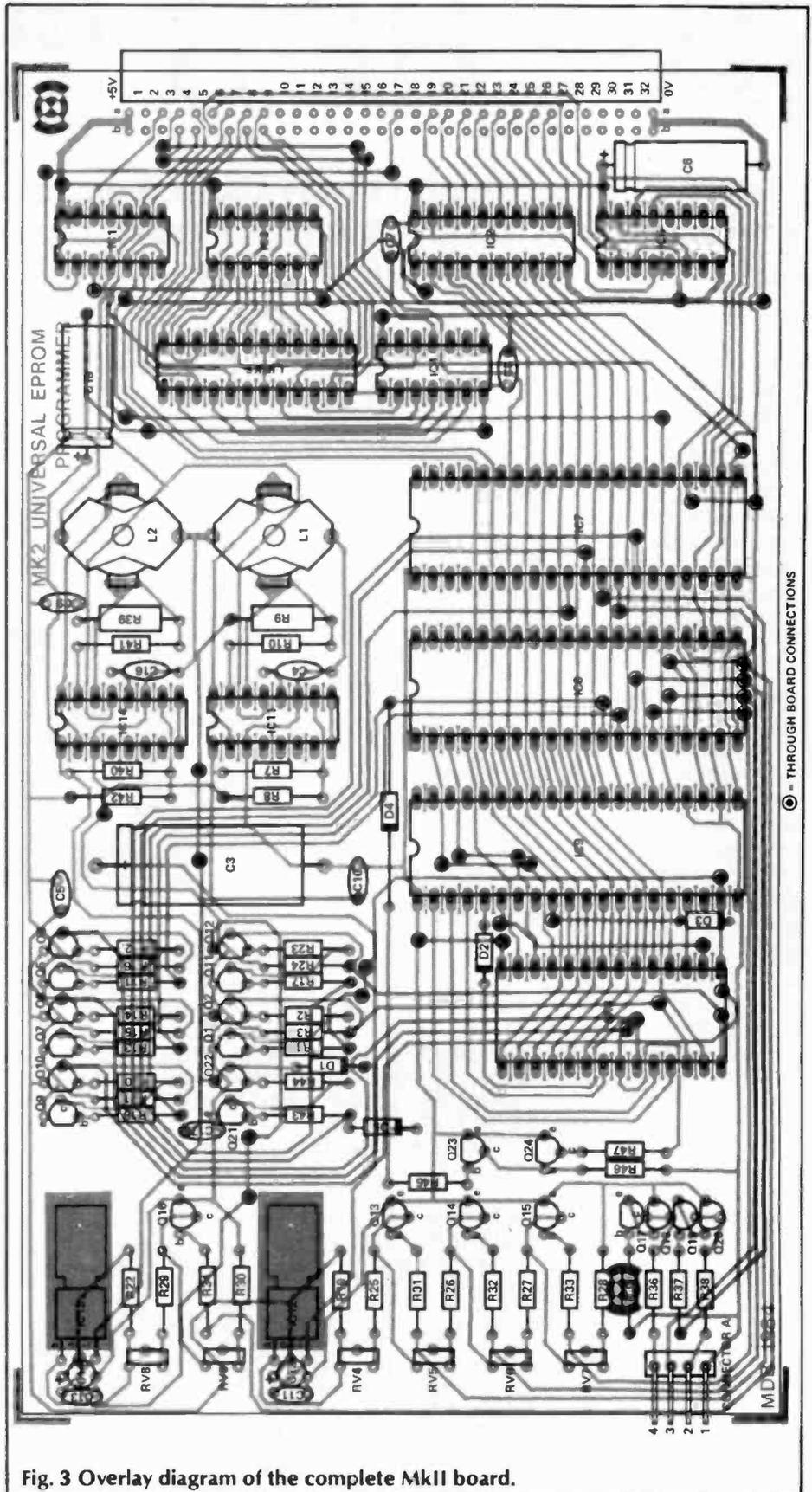


Fig. 3 Overlay diagram of the complete MkII board.

NOTE: Component numbering conforms to original project. R4, R5, R6, C1, C2, IC6, IC10, Q3 and Q4 have not been accidentally omitted. The num-

bers refer to components which have been removed from the original board in the course of producing the MarkII board. *To be continued.*

ETI

THE HEAT PEN


Geoff Phillips' project may make your blood boil or leave you cold — either way you can measure the temperature with this simple digital voltmeter add-on.

The Heat Pen is a low cost temperature probe that transforms a standard DVM into a digital thermometer. Just plug the Heat Pen into any digital voltmeter, place the tip onto a surface, and the DVM shows its temperature directly in °C. Its range is from -50 to +150°C.

Thermocouples are messy: they require cold junction compensation and scale conversion. Stick on labels have their uses but they are expensive and can only be used once. The Heat Pen is an inexpensive solution to your temperature measurement problems.

Temperatures of power transistors can be measured easily. Balance your central heating radiators by measuring inlet and outlet temperatures. Take your own temperature by placing the Heat Pen under your tongue. The uses are endless.

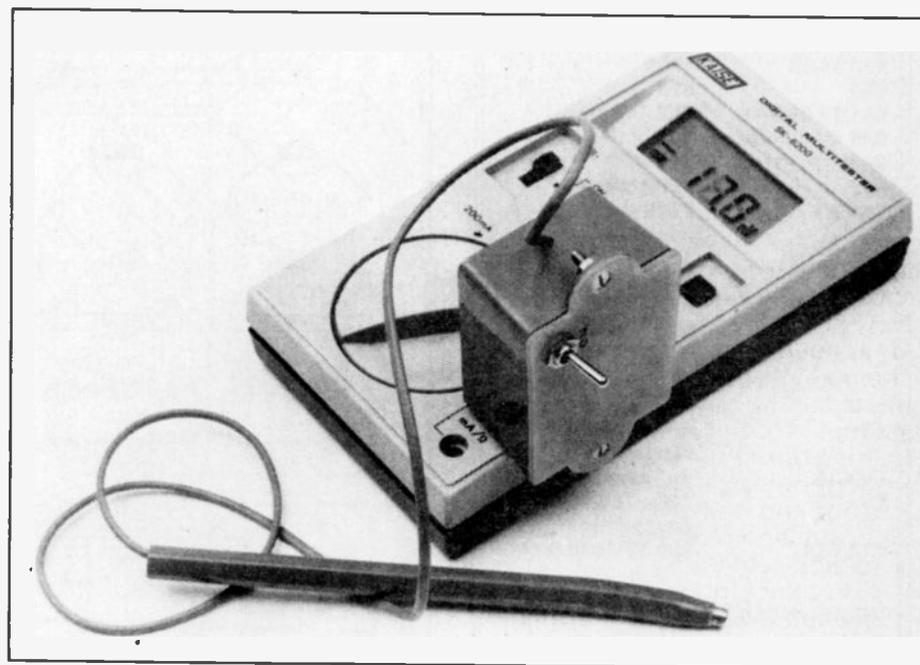A semiconductor temperature sensor is used as the probe tip. It gives a nominal 1µA per Kelvin. This is converted to 10mV per Kelvin. A bandgap voltage reference is amplified to 2.73V. This is subtracted from the voltage signal derived from the probe tip so that the remaining voltage is equivalent



to 10mV per °C. Low power semiconductors are used making the quiescent current drain of the Heat Pen less than 1mA.

Nearly all DVMs are fitted with 4mm input sockets which are pitched 3/4" apart. The Heat Pen's PCB, as well as housing the circuitry, also has two 4mm plugs fir-

mly fitted at the 3/4" pitch. The PCB, along with a PP3 battery fits neatly into a smart plastic potting box. The probe is mounted in a ball point pen casing and is connected to the PCB via a screened cable.

Construction

Fit the resistors, capacitor then IC1 and ZD1 to the PCB. No special precautions are required. Remove the plastic casing from the two 4mm terminals and using a junior hacksaw, cut 11mm off the hexagonal sections of the terminals so that approximately 12mm remains. The terminals already have one hole drilled in the hexagonal section. Ideally a second hole should be drilled 8mm from the first. If you have metric taps, drill these holes for an M3 tap and then tap out the holes. Secure the two 4mm terminals to the PCB with M3x6mm screws. If you cannot lay your hands on metric taps then the terminal may be fixed to the PCB by passing short lengths of heavy gauge copper

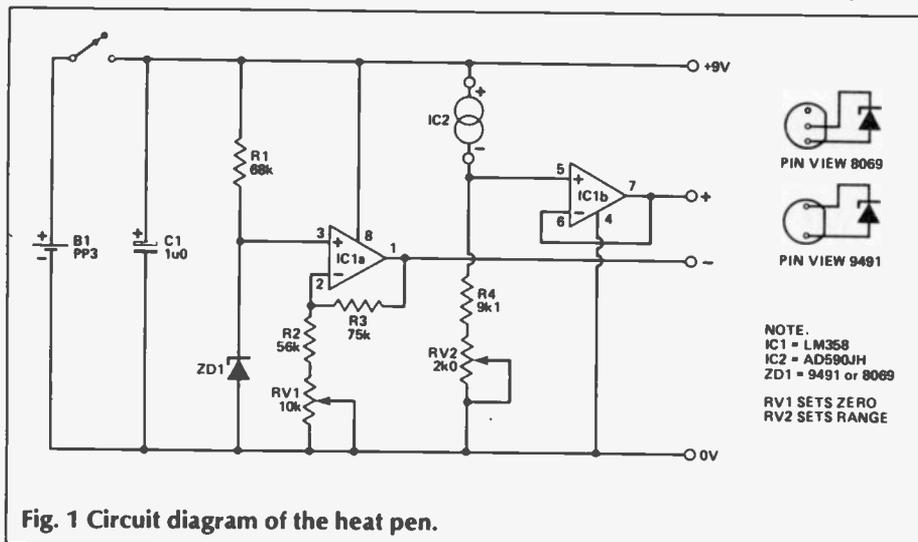


Fig. 1 Circuit diagram of the heat pen.

wire through the holes and soldering the wires in place. The wires are then passed through the holes in the PCB and soldered in place.

Solder the -ve lead of the PP3 battery clip to the 0V terminal of the PCB and solder a 2" lead to the +9V terminal. Solder the core of the screened lead to the PCB and the screen to +9V terminal. The case must now be prepared for the fitting of the PCB.

First of all it is necessary to make a cover for the potting box. This may be made from glass fibre sheet, paxolin, or plastic sheet. Use the potting box as a template and draw around its shape on the plastic sheet with a scribe. Cut out the shape with a hacksaw. After dressing up the cover with a file, temporarily clamp it to the potting box and drill two M4 clear holes through the lugs of the box and cover. Drill and file a hole in the cover for the on/off switch.

The hole will have to be carefully positioned so that the switch does not foul the PP3 battery when the unit is assembled. Fit the switch to the cover. Drill two 4.7mm holes in the side of the potting box (Fig. 2) to allow the 4mm terminals to protrude from the box and one small hole in the opposite end of the box for the screened cable.

Tie a knot in the screened cable about 25mm away from the PCB and then pass the cable through the small hole in the box. Pass the two 4mm terminals on the PCB through the two holes in the box and continue to pull the screened cable through the hole until the PCB is positioned at the bottom of the box.

Pass the screened cable through the empty ball point pen casing and solder it carefully to the tem-

HOW IT WORKS

Fig. 1 shows the circuit diagram of the Heat Pen. IC2 is a semiconductor temperature sensor which gives a nominal 1µA per Kelvin. This is converted to 10mV per Kelvin by R4 in series with RV2. Thus at 0°C RV2 is adjusted for 2.73V at the output of the buffer amplifier IC1b. ZD1 is a bandgap voltage reference which gives a nominal 1.225V. IC1a is a non-inverting amplifier whose gain is adjusted by RV1 to give 2.73V at pin 1. Thus the differential voltage between the two op-amp outputs is equal to 10mV per °C. The heat pen is plugged into a DVM set to the 100mV scale and a reading in °C is given. (The decimal point has to be implied by the user).

PARTS LIST

RESISTORS (All 1% metal film)	
R1	68k
R2	56k
R3	75k
R4	9k1
RV1	10k horizontal lin pre-set
RV2	2k horizontal lin pre-set
CAPACITORS	
C1	1µ0 16V axial electrolytic
SEMICONDUCTORS	
IC1	LM358N
IC2	AD590JH
ZD1	TSC9491BJ or ICL8069DCZR or any 1.225V bandgap voltage reference with tolerance ± 2% and temperature coefficient of 100ppm/degC
MISCELLANEOUS	
PCB; Potting box type GPL2; 4mm terminals; PP3 battery clip; small on/off toggle switch; PP3 battery; ball point pen casing.	

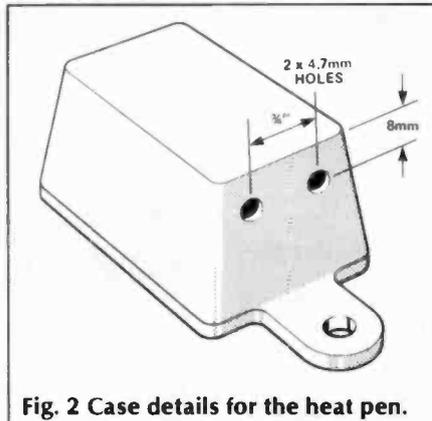


Fig. 2 Case details for the heat pen.

perature sensor AD590JH. Connect the screen to the +ve lead and the case lead of the sensor. Connect the core to the -ve lead of the sensor. Insulate the leads from each other with sleeving then the sensor can be positioned at the tip of the pen casing and secured with adhesive. Solder the +ve lead of the PP3 clip and the +ve lead from the PCB to the two switch terminals. The Heat Pen is now ready for calibration.

Calibration

A crude but effective way of calibrating the Heat Pen is in iced water. Ideally the water should be distilled and free from contaminants which may alter the freezing point temperature. It is important to ensure that water does not penetrate the leads of the temperature sensor as it will cause a leakage current to flow and thus give an erroneous reading. Therefore place the heat pen probe in a

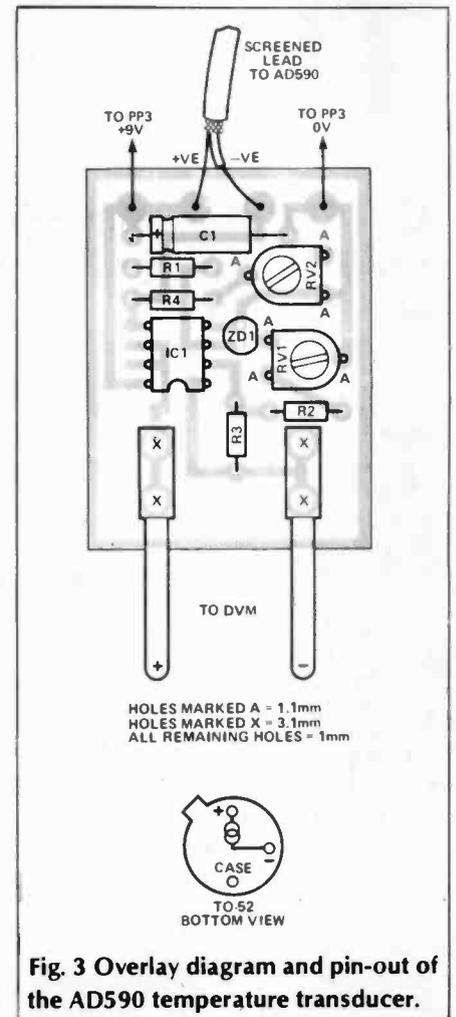


Fig. 3 Overlay diagram and pin-out of the AD590 temperature transducer.


plastic bag and place in a vessel of iced water. Switch on the Heat Pen and with your DVM monitor the voltage at pin 7 of IC1 with respect to 0V. Adjust RV2 for 2.37V.

Now plug the Heat Pen into the DVM. Adjust RV1 until 0.00V is obtained. The unit is now calibrated to 0°C. Cut out a piece of foam rubber to fit on top of the PCB in the box. This is to prevent the battery casing from short circuiting the components, and also to prevent everything from rattling around inside the box. Fit the battery on top of the foam rubber and fit the cover with its switch to the box and secure with two M4 nuts and bolts.

BUYLINES

A complete kit of parts (excluding the PP3 battery) is available from: G.P. Electronic Services, 87 Willowtree Avenue, Durham, DH1 1DZ. The cost is £8.75 inc VAT and postage for the complete kit or £1.75 for the PCB only. Note that the PCB will not be available from our PCB Service.

Introducing...

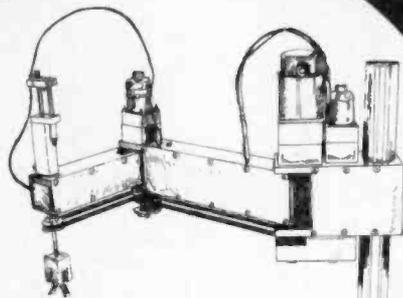

Serpent

under £2000!

Serpent SCARA assembly robot

On show at Automan NEC 14-17th May and at

Training & Development NEC 9-11th July




AND To be featured as a constructional project in Practical Electronics September issue.

<p>OSCILLOSCOPES COSSOR CDU 150. Dual Trace 35MHz Solid State, Portable. 8x10cm display. With manual£200 S.E. LABS SMIII. Dual Trace 18MHz Solid State. Portable AC or External DC Operation. 8 x 10cm display. With manual...£150 TELEQUIPMENT S54A. Single Trace 10 MHz. Solid State. With manual£110 TELEQUIPMENT D43. Dual Trace 25MHZ. With manual£110 TELEQUIPMENT S43. Single Trace 25 MHz With manual£75 EX-MINISTRY CT436. Dual Beam 6MHZ. Size 10 x 10 x 16ins. With manual£75 NEW PROBES AVAILABLE. Switched x1; x 10£11</p>	<p>NEW EQUIPMENT HAMEG OSCILLOSCOPE 605. Dual Trace 60MHZ Delay Sweep. Component Tester£515 HAMEG OSCILLOSCOPE 203.5 Dual Trace 20MHZ Component Tester.....£284 BLACK STAR FREQUENCY COUNTERS. P&P £4 Mete4or 100-100MHZ£99 Meteor 600-600MHZ£128 Meteor 1000-1GHZ£175 BLACK STAR JUPITOR 500 FUNCTION GENERATOR Sine/Square/Triangle 0.1HZ - 500KHZ. p&p £4£110 HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 AMP AC/DC. Complete with batteries & leads. p&p £4£33.50 MULTIMETER type U4324. 33 Ranges. Complete£16 with Batteries & Leads P&P £4.</p>
<p>MULTIMETERS PHILLIPS DMM2517. 4 digit. Auto ranging. Complete with batteries & leads. (Un-used)£95 AVO TEST SET No. 1 (Similar to Avo8 Mk3). Complete with batteries, leads & Carrying Case£80 AVO Model 7X. Complete with Batteries, leads & Carrying Case£40 AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads£25</p>	<p>ADVANCE AM/FM Sig Gen type SG633 7.5 - 230 MHZ£75 AVANCE AM Sig Gen type SG62 150KHZ - 220MHZ£35 PHILIPS WOBBULATOR GM877S. 5-220MHZ & 440-880MHZ£65 LABGEAR COLOUR BAR GENERATOR Type 6037£60. P&P £5 LABGEAR CROSSHATCH GENERATOR CM6004£15. P&P £2</p>
<p>UNBELIEVABLE AVO 8 Mk V. for only£65 Complete with Batteries & Leads</p>	<p>NOW ONLY £12 P&P £3 AVOTRANSISTOR TESTER TT169 Handheld. GO/NOGO for In-situ Testing. Complete with Batteries, leads & instructions</p>
<p>5 1/4" FLOPPY DISK DRIVES TANDOM 1/4 Height. Brand New Single Sided Double Density£70 Double Sided Double Density£100 SHUGART type Sa60. Double Sided. Double Density. 80 Track. Ex-eq£75 P&P all drives £5</p>	<p>MAINS ADAPTOR. New. 240V Input 9V DC 800MA Output. Plugs directly into 13A Socket. P&P £2£5 ea. DELPAK D15-200 POWER SUPPLY MODULE. Encapsulated Ex-eq. 210-250 Input. +/- 15V 200MA Output. P&P £2£7.50 ea.</p>
<p>This is a VERY SMALL SAMPLE OF STOCK, SAE Or Telephone for LISTS Please check availability before ordering. Carriage all units £12 VAT to be added to total of Goods & Carriage.</p>	
<p>STEWART OF READING 110 WYKEHAM ROAD, READING, BERKS RG6 1PL Telephone: 0734 68041</p> <p>Callers welcome 9am to 5.30pm Monday to Saturday Inclusive</p>	

Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

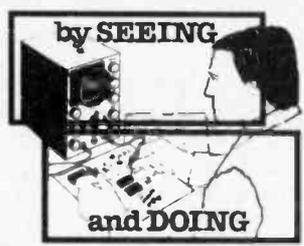

New Job? New Career? New Hobby?
 SEND THIS COUPON NOW.

FREE! COLOUR BROCHURE
 Please send your brochure without any obligation to

OR TELEPHONE US 062 687 2598
 OR TELEX 22758 (24 HR SERVICE)

NAME _____ I am interested in

ADDRESS _____

ELECTRONICS
 MICROPROCESSORS
 RADIO AMATEUR LICENCE
 CITY & GUILDS EXAMS

Other Subjects _____

ET/1/6

British National Radio & Electronics School PO. Box 7, Teignmouth, Devon, TQ14 0HS

ROBOTS For Education, Training and Industry

NEPTUNE I

Kit from £1250

NEPTUNE II

NEPTUNE - for clean hydraulic power - tap water is the hydraulic fluid!

Kit from £1725

MENTOR

Kit from £345

NEPTUNE I 6 axes; 8 bit control system; 2.5Kg capacity; 1120mm reach.

NEPTUNE II 7 axes; 12 bit control system; 2.5Kg capacity; 1120mm reach.

MENTOR DC servo desktop robot; 8 bit control system; 300gm capacity; 420mm reach.

Robots programmed from keyboard or hand-held simulator (model robot). Robots also available ready built.

Robots may also be taught by 'lead by the nose' method.

Extensive software is supplied free with each robot.

Leads available for connection to BBC, ZX Spectrum, Apple IIe, Commodore 64 and VIC 20.

Most other micros are also easily usable with these robots.

Please phone for brochure: 0264 50093.
West Portway Industrial Estate, Andover SP10 3ET.
 A private and independent company giving prompt, personal service.

SERVICE SHEET

Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;
- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);
- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;
- We receive a large number of letters asking if we have published projects for particular items of equipment. Whilst some of these can be answered simply and quickly, others would seem to demand the compiling of a long and detailed list of past projects. To help both you and us, we have made a full index of past ETI projects and features available (see under Backnumbers, below) and we trust that, wherever possible, readers will refer to this before getting in touch with us.
- We will not reply to queries that are not accompanied by a stamped addressed envelope (or international reply coupon). We are not able to answer queries over the telephone. We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.
- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

Subscriptions

The prices of ETI subscriptions are as follows:

UK:	£16.30
Overseas:	£18.30 Surface Mail
	\$24.00 Surface Mail (USA)
	£43.30 Air Mail

Send your order and money to: ETI Subscriptions Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire, HP1 1BB (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

Backnumbers

Backnumbers of ETI are held for one year only from the date of issue. The cost of each is the current cover price of ETI plus 50p, and orders should be sent to: ETI Backnumbers Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire HP1 1BB. Cheques, postal orders, etc should be made payable to ASP Ltd. We suggest that you telephone first to make sure there are still stocks of the issue you require: the number is (0442) 48432. Please allow 28 days for delivery.

We would normally expect to have ample stocks of each of the last twelve issues, but obviously, we cannot guarantee this. Where a backnumber proves to be unavailable, or where the issue you require appeared more than a year ago, photocopies of

individual articles can be ordered instead. These cost £1.50 (UK or overseas surface mail), irrespective of article length, but note that where an article appeared in several parts each part will be charged as one article. Your request should state clearly the title of the article you require and the month and year in which it appeared. Where an article appeared in several parts you should list these individually. An index listing projects only from 1972 to September 1984 was published in the October 1984 issue and can be ordered in the same way as any other photocopy. If you are interested in features as well as projects you will have to order an index covering the period you require only. A full index for the period from 1972 to March 1977 was published in the April 1977 issue, an index for April 1977 through to the end of 1978 was published in the December 1978 issue, the index for 1979 was published in January 1980, the 1980/81 index in January 1982, the 1982 index in December 1982, the 1983 index in January 1984 and the 1984 index in January 1985. Photocopies should be ordered from: ETI Photocopies, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Cheques, postal orders, etc should be made payable to ASP Ltd.

Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details. (Don't forget to give us your telephone number).

Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

OOPS!

Corrections to projects are listed below and normally appear for several months. Large corrections are published just once, after which a note will be inserted to say that a correction exists and that copies can be obtained by sending in an SAE.

CMOS Tester (August 1984)

C3 and C2 are reversed on the overlay; C3 is the electrolytic and C2 the polyester. R33 is 100K not 1M as given in the parts list, and RV1 is a 1M horizontal skeleton preset. R1-16 are two, eight-resistor SIL packages, the component labelled C14 on the overlay is SK1, and the connections to D2 shown in Fig. 3 are reversed. On the circuit diagram, the eight lines connecting SW9-16 to the inverters are shown in reverse sequence. Some of the inverters have been given the wrong designations; the correct sequence, reading down from the top, is:- IC1f, IC2a, IC2b, IC1e, IC1d, IC1c, IC1b, IC1a, IC2c, IC2d, IC2e, IC3d, IC3a, IC3b, IC3c, IC2f. Finally, the pin numbers are missing from ICs 3e and f; the input of IC3e is pin 11 and its output pin 12, and the input of IC3f is pin 14 and its output is pin 15. The PCB is correct in all respects.

AM/FM Radio (November 1984)

In Fig. 2, the oscillator and IF sections should be shown connected to ground; the PCB is correct. In Fig. 4, C31 should be 10n to give the 75us deemphasis shown in Fig. 3, but 4n7 has been found to give a brighter midrange. R38 in Fig. 5 should, of course, be 820k rather than 280k and it and the bottom end of C38, C44 etc should be shown connected to ground. In the construction section on page 25, four pieces of 8mm plywood are mentioned but in fact only three are needed — the fourth side is the front panel. See also the note in December News Digest regarding availability of the inductors.

Digital Control Port (November 1984)

The second sentence in the "Testing" section on page 30 should include the words 'without any ICs in place'. In the second paragraph of that section, the check for +5V should be made on pin 3 of IC101, not IC1. At the bottom of the first column on page 31, the last sentence should finish with B3 = 0.

Video Vandal (November 1984)

In Fig. 8 on page 54, R16 and R17 should be shown connected to the base of Q4, and C12 and SW2 should be in the D output line rather than the OV line. It may also be beneficial to add a diode across R3 with its anode connected to the slider of RV1. In Fig. 10, R52 and LED2 are shown connected across the +12V supply but it is better to place them across the -12V supply so as to even-up the dissipation in the ICs.

Digital Delay Line (December 1984 - January 1985)

In Fig. 6 on page 21 of the December issue, C19 and C20 are both 100uF. In Fig. 8 on page 62 of the January issue, C3 should be marked 33p. On the overlay diagram (Fig. 9, p.64), R37 is missing and should be connected between pin 3 of IC9 and the OV line; R20 is missing and should be located in the holes immediately to the left of R18; R50 is missing and should be connected between pins 1 & 2 of IC14. Some components on the overlay have also been wrongly numbered:- C20 should be marked C19 and C21 should be marked C20; R12 (between ICs 5 & 6) should be marked R22; R48 should be R44, R49 should be R45, R57 should be R46, R51 should be R47, R50 should be R48, and R47 should be R49. The unmarked capacitor directly above what is now C19 is an un-numbered 100n ceramic. C30 does not appear on any diagram or parts list and this is correct.

"Sonneti" Combo (March 1985)

The foil pattern on the overlay diagram has been shown as though from the copper rather than the component side. The foil is correctly shown on the Foil Patterns page from the copper side.

VCDO (March 1985)

RV2 should be 10k (right in parts list, wrong on circuit diagram).

TECH TIPS

Cheap Hour Counter


P. Roch
Luxembourg

It is often useful to be able to measure the period of time for which a piece of mains-powered equipment has been in use, but the elapsed hour counters sold for this purpose are quite expensive. This circuit, which was originally designed for use with a central heating burner, uses a redundant calculator as the display and can be built very cheaply.

The circuit works by taking a 50Hz signal from the piece of equipment being monitored and divides this to drive the '+' key of a calculator. The calculator used must have the facility whereby an entered number, X, is incremented by each push of the '+' key to become 2X, 3X, 4X, etc. Most cheap calculators have this function.

The 50Hz signal is obtained from a small 6V transformer whose primary is connected in parallel with the mains supply to the equipment being monitored. The AC signal is rectified by D1 and then squared-off by the Schmitt trigger, IC1a. The resulting waveform is fed to the twelve stage ripple counter IC2, and the divided output then used to operate the bilateral switch, IC3. The switched output of this IC is connected across the '+' key of the calculator.

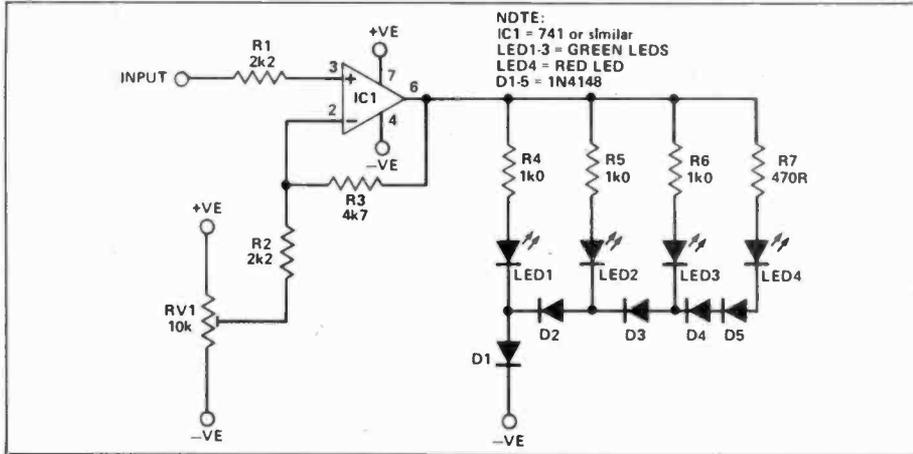In use, the appropriate value of X for the readout required is keyed into the calculator and the 50Hz signal applied to the input. Values of X to give displays in hours, minutes and seconds are given in the table for various divider outputs.



Budget VU Meter


J. Green
London


The circuit uses three or more green LEDs and one red LED to indicate the level of a varying input signal. Each LED is connected to a different point on a chain of diodes and will only light up when the applied voltage exceeds the combined conduction threshold of all the diodes connected between its cathode and the negative rail.

About 5.2V is needed to light all the LEDs in the chain, and this is achieved by using an operational amplifier arranged to give a gain of 3.5. This is sufficient to light the red LED from a standard 0dB signal input. RV1 sets the gain of the op-amp and is adjusted so that the red LED just lights up at the required level.

The circuit works well with a supply of $\pm 5V$, but if you wish to use more LEDs in the chain the supply voltage will have to be increased and the value of R3 raised to increase the gain of the op-amp. An op-amp with a higher current rating may also be required.

Divider Output	hours	X mins	secs
2★★6	0.00036	0.0213	1.28
2★★7	0.00071	0.0427	2.56
2★★8	0.00142	0.0853	5.12
2★★9	0.00284	0.1707	10.24
2★★10	0.00569	0.3413	20.48
2★★11	0.01138	0.6827	40.96
2★★12	0.02276	1.3653	81.92

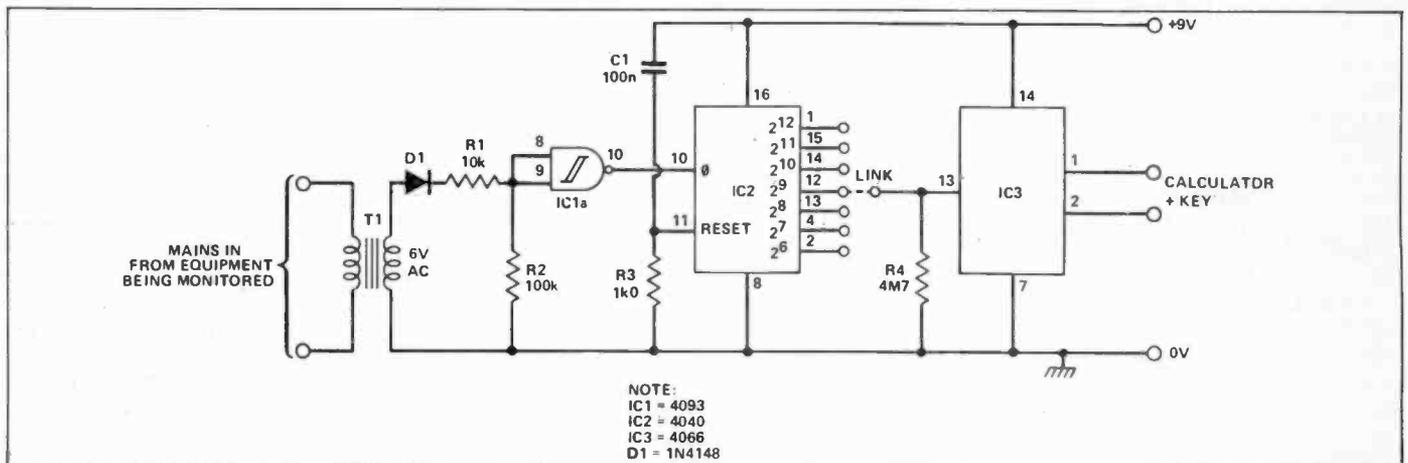

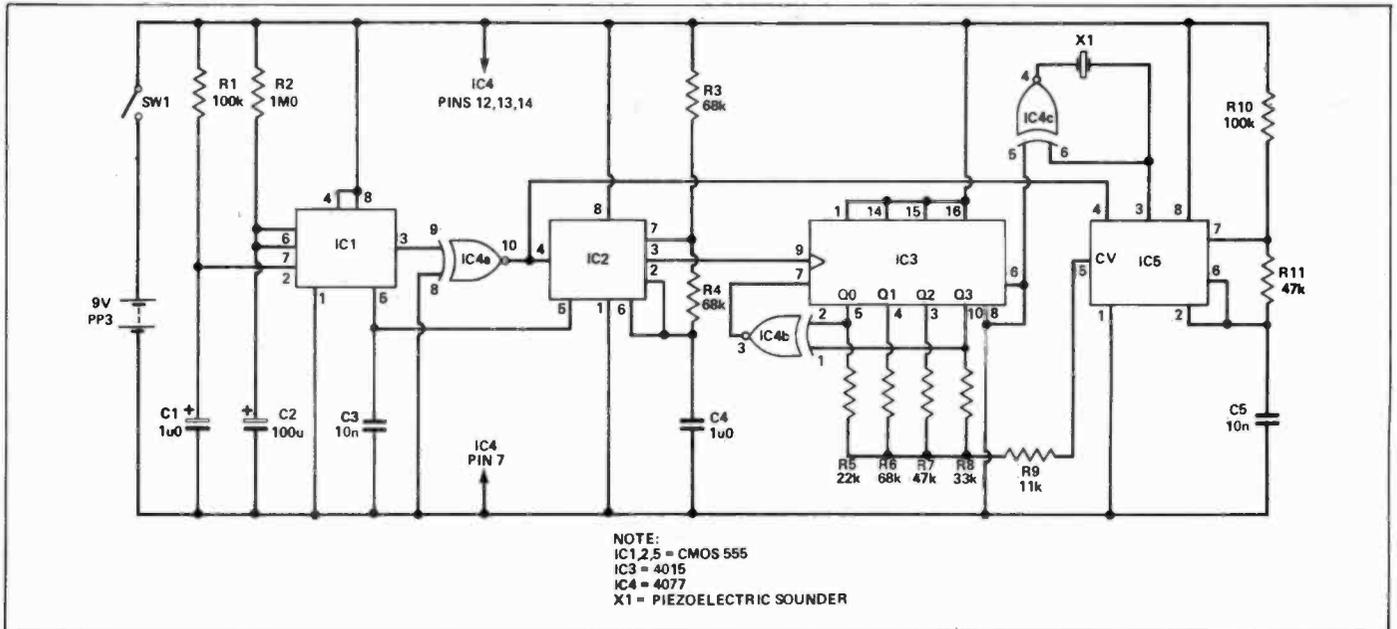

Annoying Alarm

P. Cooper
London

This circuit was designed to drive a computer maniac away from his machine in time for meals and emits an annoying pseudo-random sequence of tones about two minutes

after being switched on. The prototype was arranged to be switched on by the removal of a jack plug so that it could not easily be disabled once activated.

A two minute delay is produced by monostable IC1, which is triggered by C1 when power is applied. IC1's output is inverted to give an active high enable signal which allows astables IC2 and IC5 to run after the delay. IC2 clocks a 4-bit shift register (IC3) at about 5 Hz

while IC5 generates an audio tone whose frequency is modulated by IC3's outputs and R1 to R5. The first and last outputs of the shift register are Exclusive-NOR'ed and the result is fed to the data input to produce the pseudo-random code. The two terminals of the piezoelectric buzzer are driven in antiphase to increase sound output.


The resulting alarm is very annoying, as people present during its development will testify!

Slot Car Brake Lights

M. Kendall
Fleet,
Hampshire

This circuit may be fitted to most small slot-type racing cars and drives two red LEDs mounted at the back of the car. The LEDs are automatically illuminated whenever the slot-car slows down, giving a realistic imitation of the action of car brake lights.

The circuit is based around IC1 which is connected as a differentiator. It monitors the voltage being supplied to the car and turns on Q1 as this falls. D2, ZD1, R1 and C1 provide a regulated supply for IC1. D1 removes any negative going spikes produced by the motor. With a constant voltage across the track the output of IC1 sits at about 2V DC, with a large AC content caused by spikes from the motor. R5 and R6

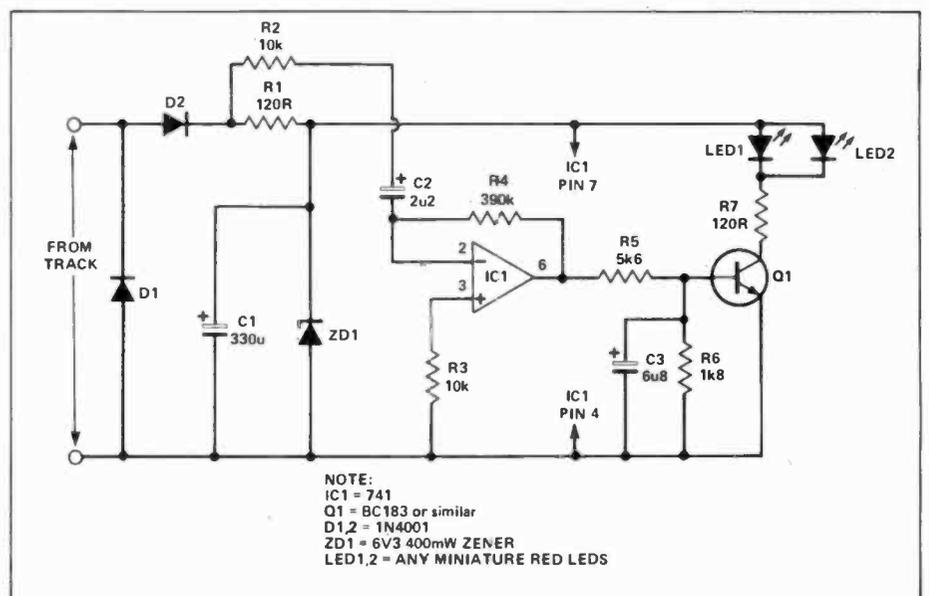


form a potential divider which holds Q1 just off under these conditions and C3 removes most of the AC. When the voltage across the track drops and the car slows down, the output of the IC rises to around 4V increase sound output. and Q1 switches on, lighting the LEDs.


If the LEDs tend to flicker when driving at constant speed C3 can be usefully increased; size is the important consideration here, so use a tantalum capacitor.

The circuit has been fitted in Scalextric rally cars and works well in practice.


FOIL PATTERNS

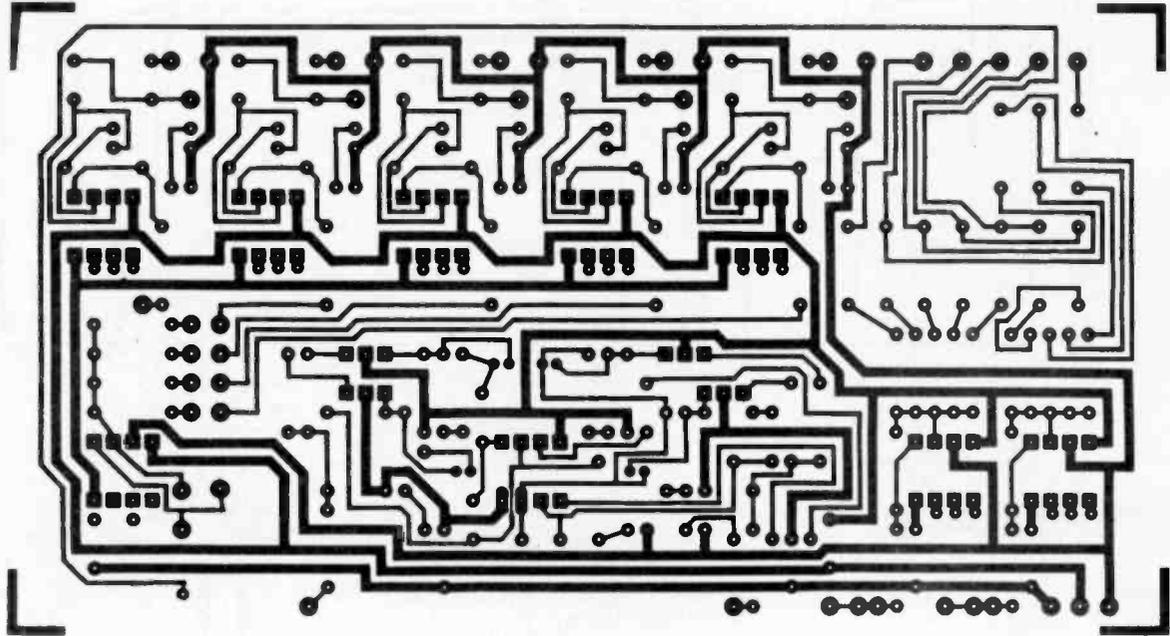

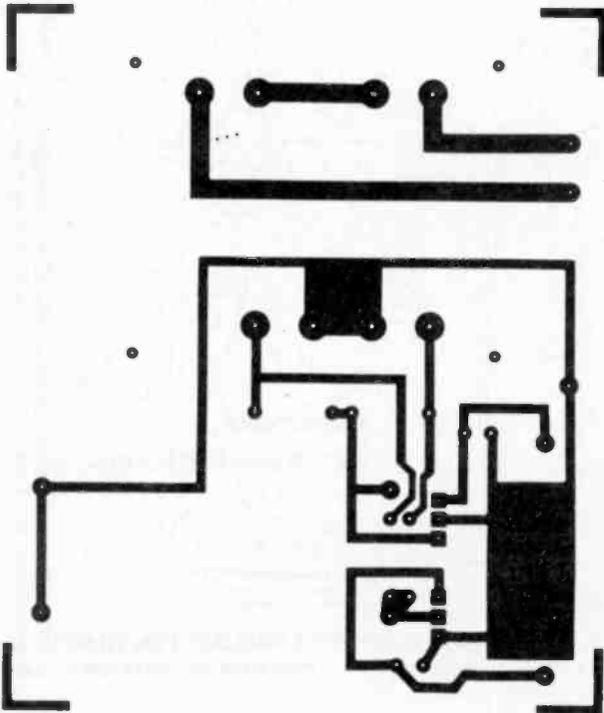
The pattern for the main board of the audio mixer.



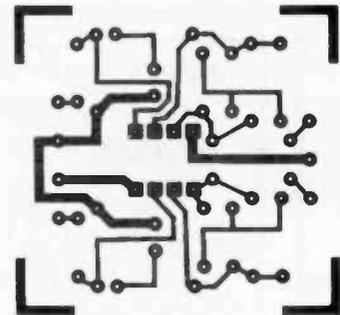
The power supply board for the audio mixer.




The audio mixer RIAA input stage board.

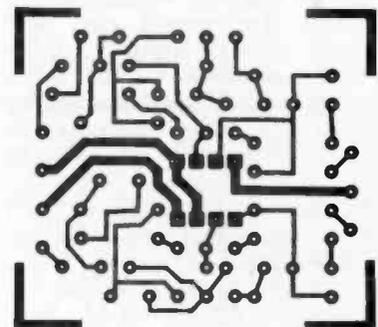


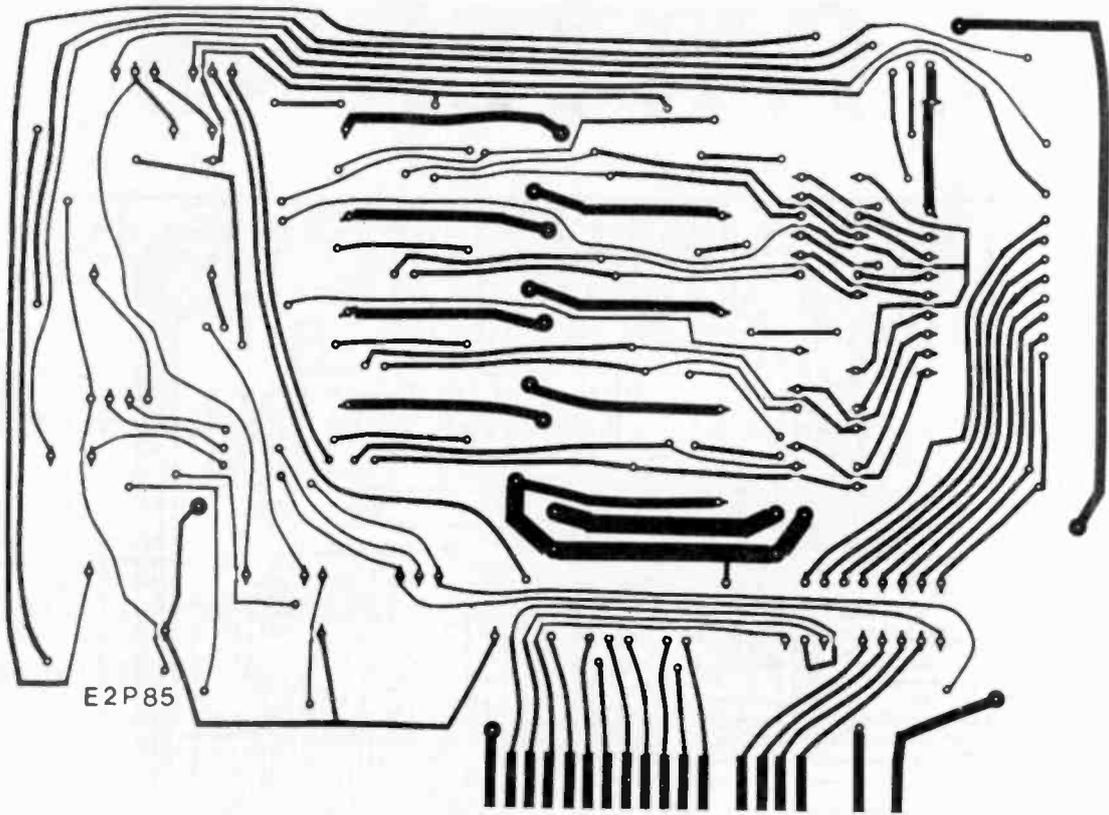
The optional tone control board for the audio mixer.



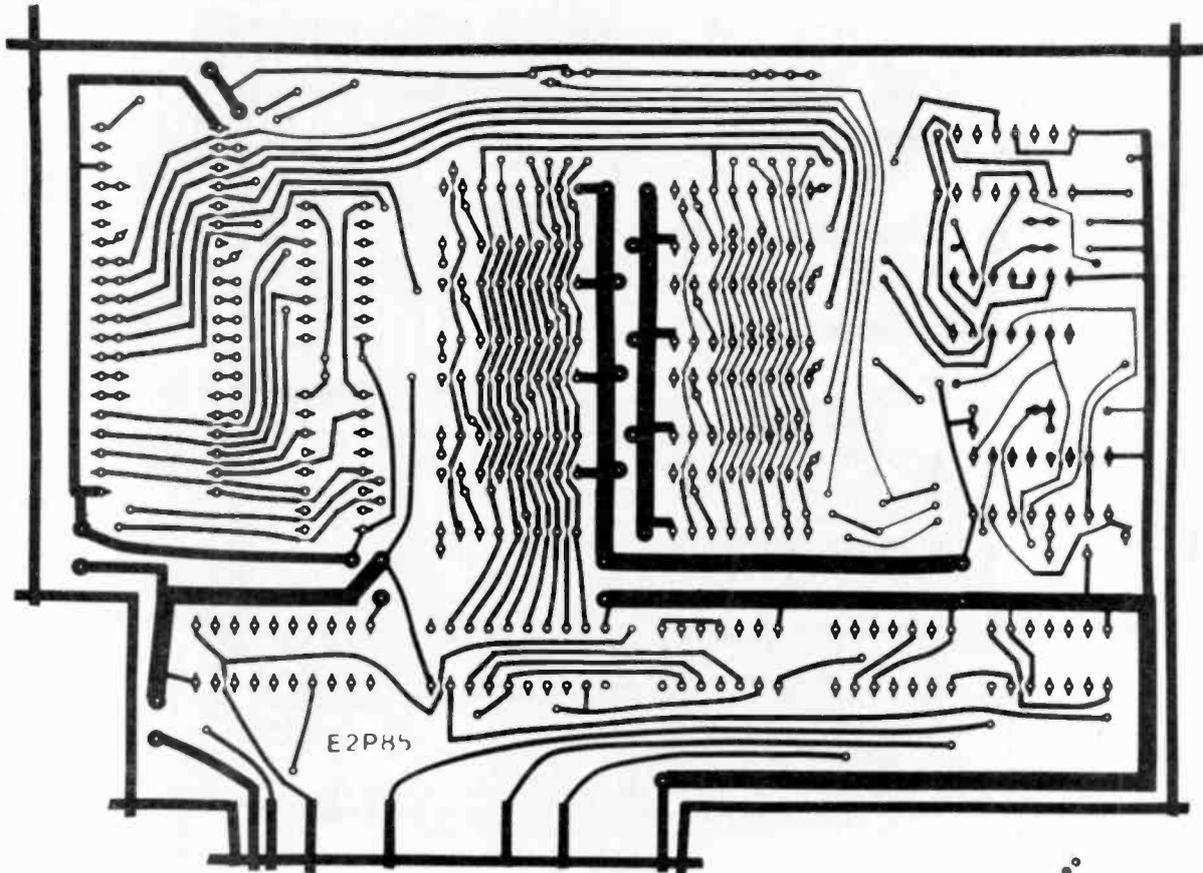The top and bottom foils for the Electron Second Processor board.



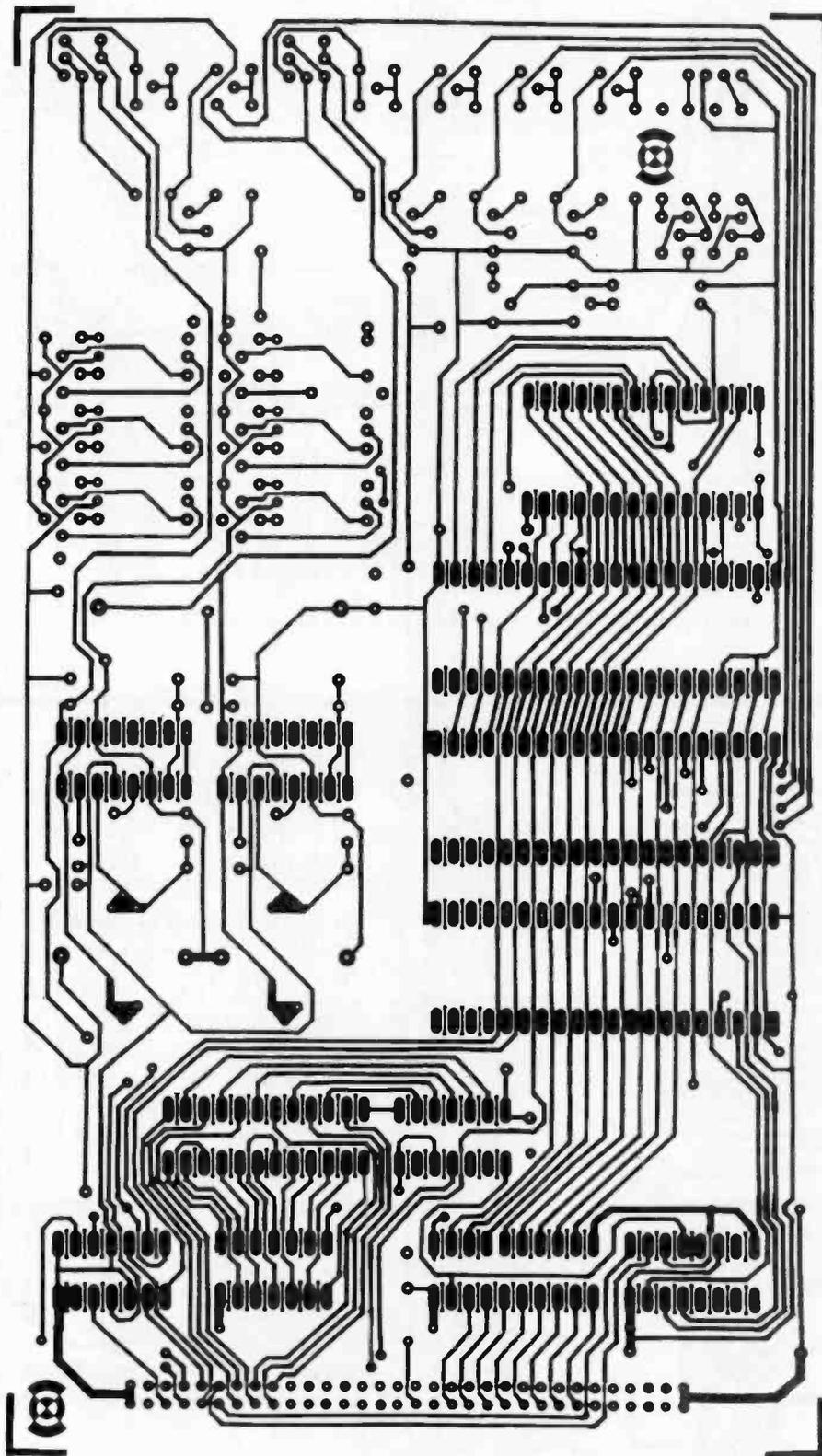

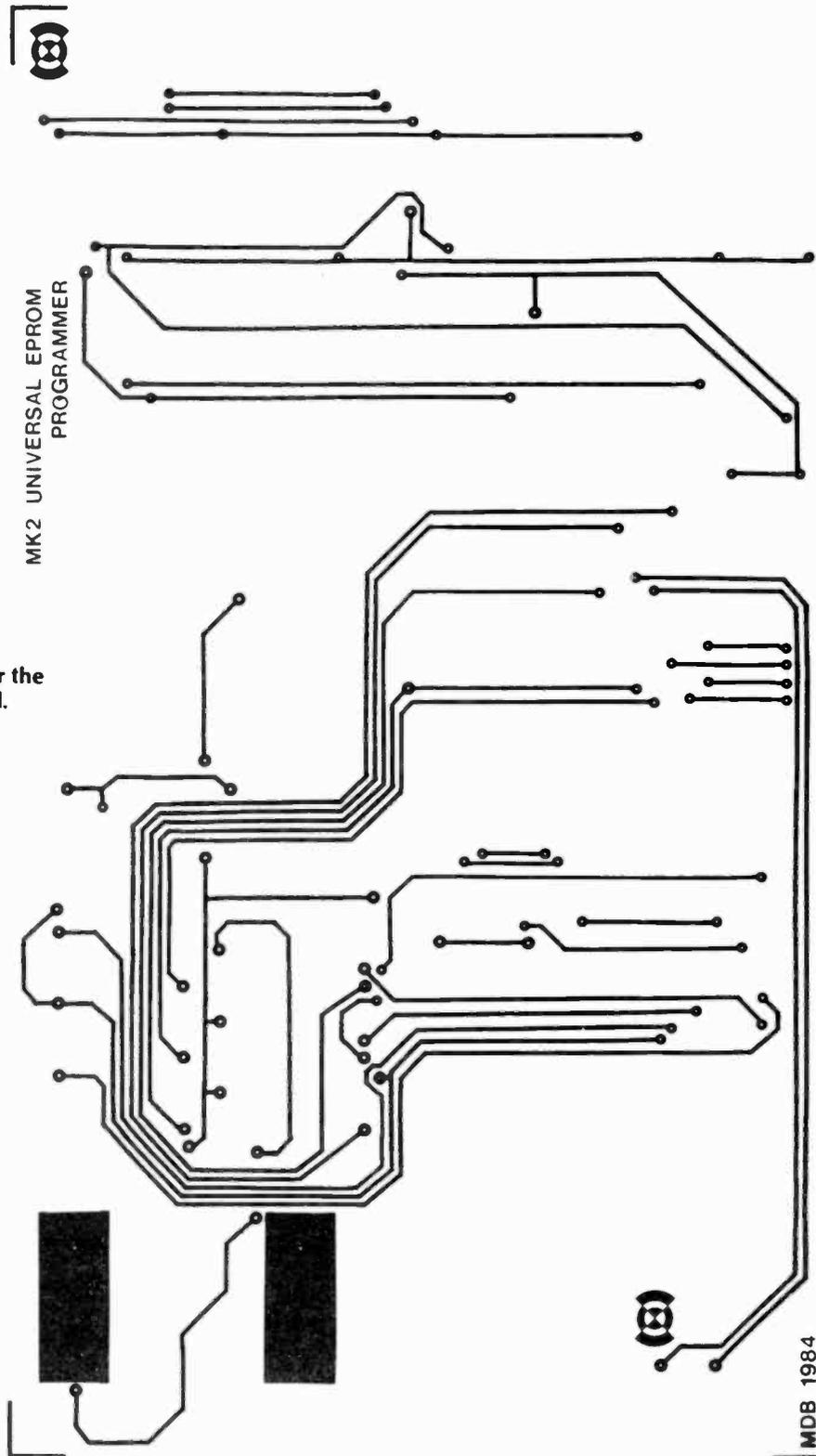

The top and bottom foils for the EPROM Programmer board.

ETI PCB SERVICE

In order to ensure that you get the correct board, you must quote the reference code when ordering. The code can also be used to identify the year and month in which a particular project appeared: the first two numbers are the year, the third and fourth are the month and the number after the hyphen indicates the particular project.

Note that these are all the boards that are available — if it isn't listed, we don't have it.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until after we receive payment.

1981

- E/8106-8 Waa-Phase..... 1.76
- E/8106-9 Alien Attack..... 4.00
- E/8107-1 System A-Input (MM/MC) .. 3.05
- E/8107-2 System A — Preamp 5.95
- E/8107-3 Smart Battery Charger ... 2.27
- E/8108-5 Watchdog Home Security (2 boards) 6.11
- E/8109-1 Mains Audio Link (3 bds) ... 8.45
- E/8109-4 Laboratory PSU 5.21
- E/8110-1 Enlarger Timer..... 3.91
- E/8110-2 Sound Bender..... 3.05
- E/8111-1 Voice Over Unit..... 4.57
- E/8111-3 Phone Bell Shifter..... 3.40
- E/8112-4 Component Tester..... 1.71

1982

- E/8202-2 Allez Cat Pest Repeller ... 1.93
- E/8202-5 Moving Magnet Stage.... 4.01
- E/8202-6 Moving Coil Stage 4.01
- E/8203-4 Capacitance Meter (2bds) 11.66
- E/8205-1 DV Meg 3.13
- E/8206-1 Ion Generator (3 bds) 9.20
- E/8206-4 MOSFET Amp Module ... 7.80
- E/8206-5 Logic Lock 3.52
- E/8206-6 Digital PWM 3.84
- E/8206-7 Optical Sensor 2.00
- E/8206-9 Oscilloscope (4 bds).... 13.34
- E/8212-2 Servo Interface (2 bds) ... 6.75
- E/8212-4 Spectracolumn 5.54

1983

- E/8301-1 Fuel Gauge..... 3.45
- E/8301-2 ZX ADC..... 2.59
- E/8301-3 Programmable PSU..... 3.45
- E/8303-1 SoundBoard 12.83
- E/8303-2 Alarm Module 3.62
- E/8303-3 ZX81 User Graphics 1.07
- E/8303-4 Logic Probe 2.50
- E/8304-1 Real Time Clock..... 8.74
- E/8304-4 Stage Lighting — Main ... 13.73
- E/8304-5 Stage Lighting — Display 3.45
- E/8305-1 Compressor/Limiter 6.19
- E/8305-2 Single PSU..... 3.16
- E/8305-3 Dual PSU..... 4.01
- E/8305-4.2 NDFL Amp 7.88
- E/8305-5 Balance Input Preamp... 3.23
- E/8305-6 Stage Lighting Autofade... 6.19
- E/8305-7 Stage Lighting — Triac bd . 4.74
- E/8306-1 to 3 Pseudo ROM (3bds) . 3.62
- E/8306-5 Atom Keypad..... 5.18
- E/8307-1 Flash Sequencer..... 2.67
- E/8307-2 Trigger Unit Main Board... 2.67

- E/8307-3 Trigger Unit Transmitter 1.66
- E/8307-4 Switched Mode PSU.... 16.10
- E/8308-1 Graphic Equaliser..... 9.10
- E/8308-2 Servo Fail-Safe (4 off) ... 2.93
- E/8308-3 Universal EPROM prog ... 9.64
- E/8309-1 NiCad Charger/Regen ... 3.77
- E/8309-2 Digger..... 3.40
- E/8309-3 64K DRAM 14.08
- E/8311-2 Supply Protector 2.19
- E/8310-2 Car Alarm..... 3.98
- E/8310-3 Typewriter Interface 4.17
- E/8311-1 Mini Drum Synth 3.07
- E/8311-2 Alarm Extender..... 3.21
- E/8311-3 Multiswitch 3.59
- E/8311-4 Multiple Port..... 4.34
- E/8311-5 DAC/ADC Filter 3.22
- E/8311-6 Light Pen 4.60
- E/8311-7 Logic Clip..... 2.51
- E/8311-8 MC Head (JLLH)..... 3.17
- E/8312-1 Lightsaver..... 1.85
- E/8312-2 A-to-D Board..... 12.83
- E/8312-3 Light Chaser (2 bds) 7.54
- E/8312-4 ZX Alarm 6.04

1984

- E/8401-1 Vector Graphics..... 8.27
- E/8402-1 Speech Board (Mini-Mynah) 10.97
- E/8402-2 MP (Modular Preamp) Disc input (mono) 3.73
- E/8402-3 MP Output stage (stereo) 3.73
- E/8402-4 MP Relay/PSU..... 3.73
- E/8402-5 MP Tone, main (mono) ... 3.73
- E/8402-6 MP Tone, filter (stereo) ... 3.73
- E/8402-7 MP Balanced output (st) ... 3.73
- E/8402-8 MP Headphone amp (st) ... 3.73
- E/8402-9 MP Mother board..... 9.01
- E/8403-1 Power Meter 5.81
- E/8403-2 Z80 DRAM..... 9.79
- E/8403-3 Obedient Die 3.76
- E/8404-1 School Timer..... 4.07
- E/8405-1 Auto Light Switch..... 4.01
- E/8405-2 ZX81 EPROM Prog 10.53
- E/8405-3 Mains Borne RC..... 5.07
- E/8405-4 Centronics Interface 4.09
- E/8405-5 Vario 6.62
- E/8405-6 Midi Drum Synth 3.59
- E/8406-1 Oric EPROM Bd..... 19.58
- E/8406-2 Spectrum Joystick 3.30
- E/8407-1 Warlock Alarm 8.19
- E/8408-1 Joystick Interface..... 3.07
- E/8408-2 EPROM Emulator..... 9.11
- E/8408-3 Infrared Transmitter 3.70

- E/8408-4 Infrared Receiver..... 3.98
- E/8408-5 CMOS Tester..... 4.60
- E/8409-1 EX42 Kybd. Interface ... 3.82
- E/8409-2 Banshee Siren..... 3.19
- E/8409-3 Dry Cell Charger..... 2.80
- E/8410-1 Echo Unit..... 3.92
- E/8410-2 Digital Cassette 9.80
- E/8410-3 Disco/Party Strobe 4.80
- E/8411-1 AM/FM Radio (4 bds) ... 13.02
- E/8411-2 Control Port-control bd 12.15
- E/8411-3 Control Port-I/O bd 6.33
- E/8411-4 Capacitance Meter..... 3.55
- E/8411-5 Video Vandal (3 bds) ... 12.10
- E/8411-6 Temperature Controller... 2.88
- E/8411-7 Mains Failure Alarm..... 2.54
- E/8411-8 Knife Light 3.25
- E/8411-9 Stage Lighting Interface... 3.73
- E/8411-10 Perpetual Pendulum ... 3.14
- E/8412-1 Spectrum Centronics ... 3.51
- E/8412-2 Experimenter's DRAM... 14.08
- E/8412-3 Active-8; Motherboard ... 9.37
- E/8412-4 Active-8; Protection Unit 3.67
- E/8412-5 Active-8; Crossover 3.67
- E/8412-6 Active-8; LF EQ..... 3.67
- E/8412-7 Active-8; Equaliser..... 3.67
- E/8412-8 Active-8; Delay Unit..... 3.67

1985

- E/8501-1 Active Bass Speaker..... 2.79
- E/8501-2 DRAM Card Update..... 3.66
- E/8501-3 Digital Delay (2 bds) ... 26.00
- E/8502-1 Digital Delay Expander... 10.79
- E/8502-2 Data Logger 5.17
- E/8503-1 Combo preamplifier..... 4.49
- E/8503-2 THD meter mV & osc. bds 7.02
- E/8503-3 THD meter mains PSU ... 3.49
- E/8503-4 THD meter battery PSU ... 1.36
- E/8503-5 ParaGraph Equaliser IP/MSP & OP/PSU bds..... 9.30
- E/8503-6 ParaGraph Equaliser filter bd 4.51
- E/8504-1 Framestore Memory 11.53
- E/8504-2 Framestore ADC/DAC... 5.23
- E/8504-3 Framestore Control ... 16.51
- E/8504-4 Buzby Meter..... 4.38
- E/8504-5 CCD Delay 3.70
- E/8505-1 6802 board..... 7.87
- E/8505-2 EPROM prog. upgrade ... 4.71
- E/8505-3 Scoreboard controller, PSU and opto-isolator bds..... 11.54
- E/8505-4 Scoreboard digit driver... 4.11
- E/8505-5 Stereo Simulator..... 3.55
- E/8506-1 Audio mixer main bd 5.40
- E/8506-2 Audio mixer PSU bd 3.87
- E/8506-3 Audio mixer RIAA bd.... 2.36
- E/8506-4 Audio mixer tone ctrl. 2.68
- E/8506-5 EPROM Prog/MkII..... 14.25

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £.....
 Add 45p p&p 0.45
 Total enclosed £.....

**PLEASE ALLOW
28 DAYS FOR
DELIVERY**

Signed

Name

Address

REVIEWS

GATE ARRAYS: DESIGN AND APPLICATIONS

Book

John Reed (ed)

*Collins Professional and
Technical Publishers
8 Grafton Street
London W1*

price: £20

This book is divided into nine sections, written by different authors from different companies on (presumably) their specialities. The first section, which lays out the background information and the basic technology, is written by the editor.

Gate Arrays are, typically, ICs with the interconnections between different parts not defined. A customer requiring a specific logic function can specify the interconnection pattern to meet his requirements, and thus can have a "semi custom IC" without having to start from scratch, with all the cost that entails. Even the provision of interconnect masks is not a cheap or simple business, however, so this technology is not for prototyping purposes.


Details of the device technology are provided, both for bipolar and MOS arrays. Analogue/linear arrays are also available (not a lot of people know that) and both bipolar and CMOS versions are discussed. Digital gate arrays are often known as uncommitted logic arrays, or ULAs.

Manufacturing a gate array is a complicated procedure in which a mis-step can be very costly, and computer aided design (CAD) is a big help. About forty pages are devoted to this important topic. Following this is a short section on manufacturing, in which the author comments 'whereas full custom circuits can frequently take up to a full year to implement, gate arrays... can be produced in as little as three weeks from the time a logic diagram is received.' This cannot be cheap!

Once the design has been produced it must be tested. This is not as easy as it sounds, because it is not possible to place a logic probe at any convenient point in a complicated circuit. As the section covering this aspect points out, the design must be carried out so that the functioning of the circuit can be determined by access to the pins, and without having to take the circuit through every conceivable logic state.

After this are three sections on designing with and applying gate arrays. One example shown here is the Acorn Electron, in which most logic not connected with the microprocessor is carried out by a gate array. This includes video handling, sound generation and the cassette interface.

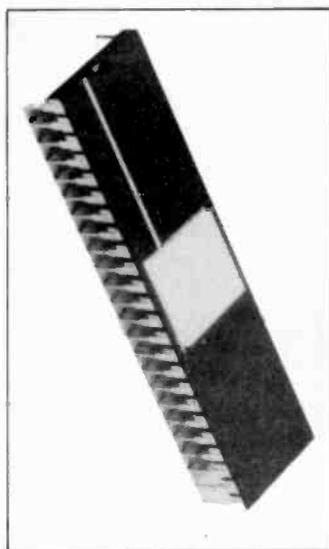The book is primarily addressed to engineers and engineering management who are contem-



DESIGNING MICRO PROCESSOR- BASED CIRCUITRY

Book

*S.J. Cahill
Prentice-Hall International
66 Wood Lane End
Hemel Hempstead
Herts HP2 4RG*

price: £9.95

Titling a book 'Designing Microprocessor-Based Digital Circuitry' is asking for trouble. Especially when the book in question carries a low price tag and is only a couple of hundred pages long. Dangerously so when the blurb claims that the book 'strips away the mystery surrounding microprocessors' and that it requires 'no prior knowledge of digital electronics and can be read by anyone with an appreciation of scientific method.'

The author, S. J. Cahill, works for the Department of Electronic and Electrical Engineering at the University of Ulster — pointedly described as being situated in 'N. Ireland, UK'. His own preface gives the lie to the blurb. The 'objective' of the book, he writes, is 'to strip off the mystery surrounding microprocessors as a digital device.' 'No great prior

knowledge of electronics (is) assumed,' writes Cahill, and 'anyone with an appreciation of scientific method will benefit from the text.' The differences may be small but they are significant. The lesson we can learn is never to trust blurb-writers (or, for that matter, publishers).

That said, the text proper begins with a somewhat doubtful proposition. 'Electronics is defined as the art of processing information by electrical means,' writes the author. One wants to ask him, by whom is it so defined and what does it mean? Cahill has fallen into a trap before taking barely a step.

He has defined the subject of his study in order to fit the book, rather than writing a book which addresses the very real issues of how best to approach and understand microprocessor-based systems. This becomes clear as you move through the book, proceeding from an introduction to logic and digital circuits to a look at microprocessors finishing with the meat of the work — a project to build a 6802 controlled greenhouse thermometer.

This project forms well over half the book and ideas behind it are introduced as early as the first page of the text proper. My first question was, why build this particular project? This is a question that recurs throughout electronics and it's a question which Cahill makes some attempt to answer with, in my opinion, little

array form.

The electronics student is also liable to find this book useful, not least for the background information provided about semiconductor technology and devices. The home constructor will find little of relevance here, but those who are interested for interest's sake should give this informative book a look.

Andrew Armstrong

Received this month:

Microelectronics Systems 1
Checkbook
Microelectronics Systems 2
Checkbook
Microelectronics Systems 3
Checkbook
(*R.E. Vears, Butterworths,
London*).

O-level and CSE Pass-cards,
Electronics
(*P. Clothier BSc, Letts,
London*)

LISP — The Language of Artificial
Intelligence
(*A.A. Berk, Collins, London*)

**These books will be reviewed
next month.**

Also next month, we will be
reviewing the Microprofessor
MPF 1/88 — an 8088-based
development and training
system from Flight Electronics,
Southampton, and the Touchtech
touch screen add-on for Mic-
rovitec monitors from Mic-
rovitec, Bradford.

success. My next question concerned Cahill's tendency to gloss over things that bear too little on the impending project. The book presumes a great deal and treats rather cursorily those aspects of electronics in general — and digital electronics in particular — which don't come within the author's purview.

There can be no doubt that the task Cahill has set himself is difficult. If he doesn't succeed gloriously he can be consoled by the fact that he has made a valiant attempt to take the ground. This is more than most writers on electronics ever do. Given its limitations, the book is well executed, readable and, at times, informative. Naturally, the project itself is handled with unimpeachable comprehensiveness. If you work through the book and construct the project (as suggested, on breadboard) there can be no doubt that you will end up with as good a working knowledge of 6802 MPU as can be had. This would be no small achievement, and no small return on the cost of the book. You would also be in a good position to develop a more general understanding of digital systems and microprocessors than could be guaranteed by any number of introductory texts. In that sense, Cahill's practical approach works — even if it doesn't quite attain his own or the blurb-writer's goal.

Gary Herman

TRAINS OF THOUGHT

Only three years ago if you said 'transistor' to the average railway modeller, he (or, rarely, she) paled visibly. If you said 'integrated circuit' he winced. And if you said 'computer' . . . well, you didn't because before you got that far he would have bolted from the room in blind panic.

A shame really, because the average railway modeller has quite an appreciation of electricity, of logic and of control. It's just that he is what he is because he likes to see things move. He's happy with switches by the bank, relays by the ream and rheostats by the kilowatt. But the thought of electrons doing their thing out of sight inside black plastic cases where he can't get at them, well, that's contrary to all his instincts.

That was three years ago. Since then things have changed — and doubtless there are some who'll say, 'Not for the better'. Many railway modellers now are turning to electronics to solve some of their problems.

LEDs are now extensively used as lamps (known, in the jargon, as aspects) in colour-light signals, an application for which they are far better suited than the traditional 'grain-of-wheat' bulbs. Train detection systems to tell the operator where his trains are — displaying

the status, as like as not, on a mimic diagram — are no longer uncommon. And that's to say nothing of control systems of varying degrees of sophistication, some of which generate simulated sound as well as giving the silkiest ever control of traction power.

Nor has the ubiquitous microcomputer left the railway modelling fraternity unscathed. Besides the miracles of four-bit processing that gave the world such command-control systems as Hornby's Zero-1, no exhibition railway layout is complete without a computerised display to tell the spectators what is supposed to be happening.

Many modellers have found their hands forced, if only because electronics offers the only feasible means to their end, the perfect reproduction in miniature of full-size railway practice. Readers of ETI, in contrast, need no convincing of the value of electronics. But you may perhaps be looking for some new avenue of application to challenge your expertise. If so, I urge you to consider railway modelling with an emphasis on such prototypical operations as multiple-aspect signalling and automatic train stop stems. In future issues I hope to give a selection of circuit ideas to show you some of the things that we modellers get up to in our lofts and attics and which I hope will set your trains of thought on the right lines!

Roger Amos



AND FINALLY, I WISH TO PUBLICLY DENY ANY FINANCIAL INTERESTS IN FIRMS MANUFACTURING MICROPHONES AND STICKY TAPE!

It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code.

Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

BRADLEY MARSHALL LTD.

■ ELECTRONIC COMPONENT ■
■ COMPUTER & SOFTWARE SPECIALIST ■
382-386 EDGWARE ROAD, LONDON W2 1EB
Telephone 01 723-4242

Mullard alfac

THE PRICE IS RIGHT

74LS374	£ 0.65
2147	£ 1.95
6116-3	£ 3.90
4164-15	£ 3.50
6264LP-15	£11.50
2764-25	£ 4.50
27128-250n/s	£ 8.50
27256-250n/s	£21.00
41256-15	£12.50

Please add 70p postage & packing to all orders and add 15% VAT to total
All components brand new/full spec.

TRADE AND EDUCATIONAL ENQUIRIES WELCOME

Bradley Marshall's new premises offer you expert friendly advice

OPEN CHANNEL

British Telecom takes pride of place this month with several items of news, the first being the recent announcement that it intends to provide telephone services to passengers flying on British Airways' 747 Jumbo jets. It makes British Rail's plans for phones on Inter City trains look positively mundane, doesn't it?

In a joint venture with Racal Decca, BT is going to develop a 'flying phone' system in three distinct stages. The first of these will be a technical evaluation exercise which will determine the best aerials, methods, and communications technologies etc, to provide an acceptable service. One of the main determining factors is the requirement that aircraft communications must be within the UHF L-band of frequencies, from about 0.4 GHz to 1.5 GHz with wavelengths from about 77 cm to 19 cm.

The next stage is a marketing evaluation exercise, to find out just who is likely to want to use in-flight telephones. During this stage it is intended that, wait for it, calls will be

free. (Hello operator. What do you mean, I can only make a local call?)

The final stage will be the implementation of a commercial service, which should be available by 1987.

When X Equals Y

On another front — good old-fashioned land based phones — BT appears less sure of itself and its directions. Recently, a spokesman for BT was reported to have confirmed that software problems bugging the development of System X exchanges have been ironed out. The very first BT operated System X exchange at Baynard House in the City of London should, by the time you read this column, be in service. By the end of June, it is planned that 15 such exchanges will be operational in the UK network.

It would appear that all things are hunky dory for the contracted manufacturers of System X exchanges, and that profits must now at least show on their order books. However, the same manufacturers must be feeling somewhat peeved by the even more recent announcements that BT is reported to have asked for tenders for the manufacture of System Y exchanges — to operate alongside their System X counterparts. The System X makers must surely feel that several years' worth of design, development and

manufacture of System X exchanges has been overridden by BT's apparent lack of commitment.

Satellite TV

The direct broadcast by satellite (DBS) debate seems to be reaching a head, with the 'Club of 21' (the consortium which is to operate Britain's DBS television service) baulking at the costs of the proposed satellite rentals.

Unisat, the satellite organisation comprising British Aerospace, GEC and — yes, you've guessed it — British Telecom, whose satellites the DBS organisation are presently bound to use, has priced the use of satellites too highly according to the Club of 21. Britsat, another satellite organisation, has offered satellite rentals to the Club of 21 at a much lower cost, for a longer time, and it promises services sooner.

The debate is compounded by news that foreign manufacturers are soon to produce cheap DBS television receivers. As one of the primary aims of DBS in the UK is to allow British companies to make DBS TVs for our own market, it stands to reason that plans for DBS services must soon be finalised so that they may do just that — before foreign competition does the job for them.

The Club of 21 is now playing a waiting game. They believe they can

force the government's hand to allow a free choice of satellite rental services, thus providing a more economical solution. Unisat is also playing a waiting game — it believes Britsat's service is inferior.


It has not been, however, the government's general policy to wait in the sidelines for arguments to sort themselves out, and there is little likelihood it will do so now, in the light of the foreign competition. So, there really are only two routes it can take. One, it may allow the Club of 21 to choose its own satellite supplier, or two, it may disband the Club of 21 and create an alternative, contractually obliged to accept Unisat's services.

With the government's reputation on negotiating settlements agreeable to all sides (almost non-existent), I would advise the Club of 21 to seriously consider its stance.

Keith Brindley

Trains of Thought and Open Channel welcome letters and information on products and events to do with modelling and telecommunications respectively. Please address correspondence to the relevant column at ETI, ASP Ltd., 1 Golden Square, London W1R 3AB.

FOR QUALITY COMPONENTS BY MAIL ORDER

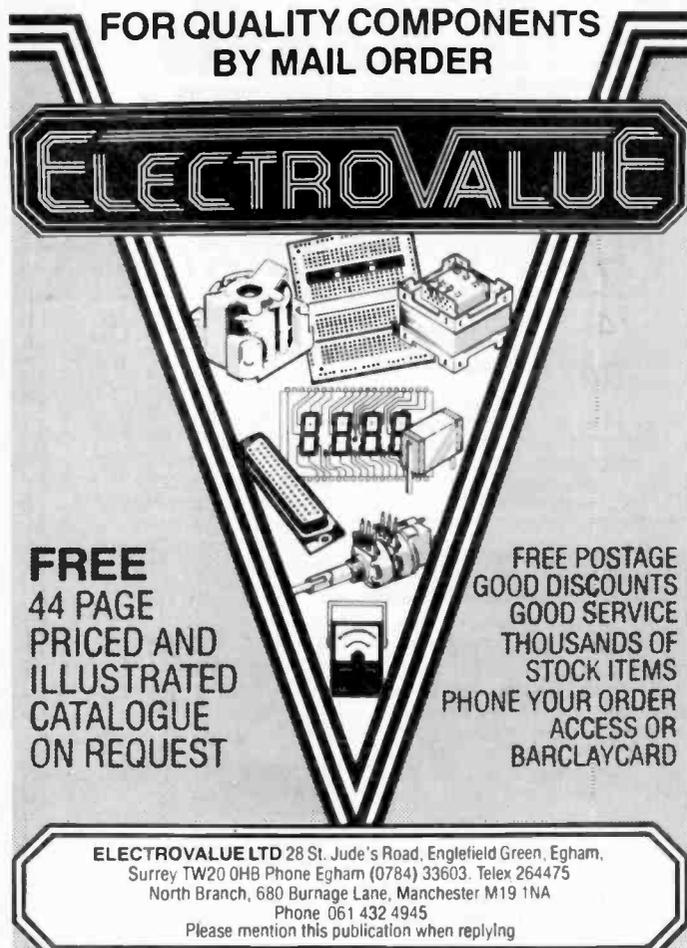

ELECTROVALUE

FREE 44 PAGE PRICED AND ILLUSTRATED CATALOGUE ON REQUEST

FREE POSTAGE GOOD DISCOUNTS GOOD SERVICE THOUSANDS OF STOCK ITEMS PHONE YOUR ORDER ACCESS OR BARCLAYCARD

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475 North Branch, 680 Burnage Lane, Manchester M19 1NA Phone 061 432 4945 Please mention this publication when replying

FREE CAREER BOOKLET

Train for success, for a better job, better pay!

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your **FREE CAREER BOOKLET** today — at no cost or obligation at all.

GCE	Choose from over 40 'O' and 'A' level subjects.	<input type="checkbox"/>
COMPUTER PROGRAMMING	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	INTERIOR DESIGN	<input type="checkbox"/>
POLICE ENTRANCE	HOTEL MANAGEMENT	<input type="checkbox"/>
ELECTRONICS	COMMERCIAL ART	<input type="checkbox"/>

Please send **FREE DETAILS** for the courses ticked above.

Name _____

Address _____

_____ P. Code _____



Dept. EBS65, 312/314 High Street, Sutton, Surrey SM1 1PR. Tel: 01-643 9568/9 or 041-221 2926 (both 24 hours)

ELECTRONICS TODAY INTERNATIONAL CLASSIFIED

Lineage:

40p per word (minimum 15 words)
Semi Display: (minimum 2 cms)
 £11.00 per single column centimetre
 Ring for information on series bookings/discounts
 All advertisements in this section must be prepaid.
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699

Send your requirements to:
 Caroline Faulkner
 ASP Ltd.,
 1 Golden Square,
 London W1.

ALARMS

ALARMS

FREE BOOKLET
 on
BURGLAR ALARMS
 with
LOWEST U.K. DIY PUBLISHED PRICES
 PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
 217 WARBRECK MOOR
 AINTREE, LIVERPOOL L9 0HU

SECURITY Alarm Systems

- FREE COMPREHENSIVE CATALOGUE!
- LOWEST DISCOUNT PRICES
 - HIGHEST QUALITY EQUIPMENT
 - FREE DIY DESIGN GUIDE
 - FULLY ILLUSTRATED
 - MICROCHIP CIRCUITRY
 - QUICK DESPATCH SERVICE
 - FULL INSTRUCTIONS
- SEND SAE OR PHONE
 CTEC SECURITY, Dept E1,
 Stephens Way, Goose Green,
 Wigan WN3 6PH
 Telephone (0942 42444)

LOWEST PRICED TOP QUALITY fire and intruder alarm equipment, etc. S.A.E. for catalogue. Security Services, 162 High St., Hythe, Kent CT21 5JR.

IT'S ALARMING!
 SOME PEOPLE DON'T
 PROTECT THEIR PROPERTY.
 PERSUADE THEM.
**ADVERTISE YOUR ALARM
 SYSTEM HERE.**

KITS

PRINTED CIRCUITS Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

MINIATURE FM TRANSMITTERS. Frequency 60-145 MHz, range ½ mile S.G.F. — P.C.B. All components. Full instructions 9-12v operation, broadcast reception. Super sensitive microphone. Pick-up on FM radio. £6.95 inc; or ready built £8.95: Same day despatch — Zenith Electronics, 21 Station Rd., Industrial Estate, Hailsham, E. Sussex BN27 2EW.

MINIATURE TRANSMITTER, transmits all voices and sounds to any VHF/FM radio up to 5 miles away, size 2in x ½in, tunable 70-150 MHz complete kit, including sensitive microphone, £4.95 send cash/cheque/PO: Tectronics, 22 Lambardes N.A.G., Nr. Dartford, Kent DA3 8HX. Mail order only.

SERVICES

FREE PROTOTYPE of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work Halstead Designs Limited. Tel: halstead (0787) 477408.

ETI. VCDO authentic musical instruments in EPROM £9.95. O. Lucas, 45 Fotherby Ct., Maidenhead, Berks SL6 1SU.

FOR SALE

100W AMPLIFIER — £9.95 built or use the same board for 50W, 150W, 200W into 4 or 8 ohms, etc., by using alternative output transistors and P.S.U. S.A.E. for full details to:- ESS Amplification, 269 Hessle Road, Hull.

BARGAIN!!!

LED 7 SEGMENT DISPLAY, BRAND NEW 14 PIN DIL RED. 43inch, COMMON ANODE DISPLAY 0-9 WITH RIGHT AND LEFT DECIMAL POINT.
 5 pieces £2.00 (40p each)
 10 pieces £3.50 (35p each)
 50 pieces £15.00 (30p each)
 100 pieces £25.00 (25p each)
 1000 pieces £250.00 (20p each)
TELEPHONE YOUR ORDER TO
 0296 613816

BEAT THE BURGLAR

HOME SECURITY AT TRADE PRICES

• MANUFACTURERS OF PROFESSIONAL ALARM EQUIPMENT FOR THE TRADE AND D.I.Y.

• SEND NOW FOR OUR COMPREHENSIVE D.I.Y. GUIDE TO CATALOGUE

S.A.E. OR PHONE

ELECTROGUARD

U.K.
 36 ASHCROFT AVE
 SHAVINGTON
 NR CREW CW2 5HN
 TEL 0270 666311

IRELAND
 134 FINAGHY RD SOUTH
 BELFAST BT10 0DG
 N. IRELAND
 TEL 0232 616962



J. Linsley Hood Designs

Distortion Analyser Kit £25.00 (p&p £1)
 Millivoltmeter Kit £12.25 (p&p 75p)
 Case & Panel £12.00 (p&p £1)
 ETI Mosfet P.Amp. Kit £51.00 (p&p £1.50)
 Audio Signal Gen. (0.02%) £28.50 (p&p £1)
 Audio Signal Gen. (.002%) £36.00 (p&p £2)
 Fixed Freq. Sig. Gen. Kit £11.00 (p&p 50p)
 Send SAE for full information
TELERADIO ELECTRONICS
 325 Fore Street
 London N9 0PE

KIA RETURN AN AD. No 20 . . . quality FET 100 watt fibreglass to 3 poweramp module + relay protection . . . return ad + £10.00 — 8 Cunliffe Rd., Ilkley.

TEKTRONIX OSCILLOSCOPES 556 Dual Beam four trace 50 MHz. Delay Sweep £395, 547 Dual trace 50 MHz Delay Sweep display — switching £250. 581A Dual trace 85 MHz £1.95. 545A dual trace 24 MHz Delay Sweep £135. A.F. Spectrum analyser system £225. Storage oscilloscopes, curve — tracers, manuals, plug-ins, spares. NOVA 3 minicomputa. Other test equipment. Tel: 01-868 4221.

SERVICES

P.C.B.'s manufactured to your specification. Small/Large production. **FAST PROTOTYPE SERVICE.** Photography. Sensitised Laminates Supplied, U.V. Exposure Equipment from manufacturer. **ORBITECHNIC**, 38 Torquay Gardens, Redbridge, Essex. 01-550-3610.

PCB DESIGN & LAYOUT. Taped artworks to your specifications and requirements. **TRAX Limited**, 497 Hitchin Road, Luton, Beds.

ATOMIC CLOCK Z80 based receivers Rugby Time code. LCD Display. Parallel output for Micros £95 Tel: 01-625 6414

WANTED

TURN YOUR SURPLUS transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

BOOKS

PARAPHYSICS JOURNAL (Russian translation); psychotronics, kirlianography, heliophonic music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

KITS

ELECTRONIC ORGAN KEYBOARDS and other parts being cleared out as special offer. Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. 01-986 8455.

SERVICES

QUANTUM TECHNOLOGY PRODUCTS

From

Airwave Communication Ltd.

Manufactures to your design, specification or brief. From bare boards to systems. One offs, prototypes and small batch runs. Projects, Repairs, P.C.B. Service

S.A.E. or Phone for details.

Airwave Communication Ltd.,
 Lisandra House,
 Fore Street, East Loe,
 Cornwall PL13 1AD.
 (05036) 4739 or 3407

NO JOB TOO SMALL

NO PLACE TOO FAR

MICROCOMPUTER REPAIRS

ZXSPECTRUM. Vic20, C64, BBC, QL 15 40/41, Commodore computers, printers and floppy discs. Send faulty machine to: Trident Enterprises Ltd., 37 Linden House, Common Road, Langley, Slough, Berks. Tel: (0753) 48785.

PLANS 'N DESIGN

AMAZING ELECTRONIC plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Old String Works, Bye Street, Ledbury HR8 2AA.

COMPONENTS

RESISTORS, CAPACITORS. 1,000 mixed carbon film 1/4W, 1/2W, 1/2W, 2%, 5%, 10% resistors £2.95. 50 mixed ceramic tube capacitors £1.00. P&P 50p. D.J. Hooker, Romney Marsh Electronics, Pennywood, Clark Road, Greatstone, Romney Marsh, Kent TN28 8PB.

IRISH READERS

MAIL ORDER COMPONENTS

Top quality components
 Great prices
 Return-of-post service

Write or phone for free price list

WAVEFORM ELECTRONICS
 12 Effra Road, Rathmines, Dublin 6.
 Phone(01)0001 If England 987507
 Mail order only please

HUNT ELECTRONICS 1985. COMPONENTS CATALOGUE. send 50p in stamps. Refunded with first order, to P.O. 57, Derby, DE6 6SN. Tel: (0283) 703071.

NI-CAD BATTERIES. AA, 500 MAH £1.00. C 1200 MAH £2.00. D, 1200 MAH £2.20. PP3 110 MAH £4.80. P&P 40p. Free price list! Spectrum Radio & Electronics, 36 Slater St., Liverpool L1 4BX. 051-709-4628.

ETI JUNE 1985

SIT VACANT

ENGINEERS URGENTLY REQUIRED

MUST LIVE LOCALLY

MANCOMP
 Printworks Lane
 Manchester M19 3JP
 Tel: 061-224-1888

ADAPTORS

TELETEXT (Ceefax/Oracle) external adaptors fit any television free cordless remote control. £159.95 inc. VAT and delivery. Access/Visa. Nufax Ltd., Freepost, Bristol BS6 7YZ. Tel: Bristol (0272) 687801-744500.

EQUIPMENT

EPROM COPIER — STAND ALONE
 2716-27128 £175.00
TELEPHONE CONVERSATION RECORDER £75.00
2 LINES INTO 1 ANSWERING MACHINE
 Switching Unit £30.00
 From L.K.F. Systems Ltd
 St. Albans. Tel: 55084

COMPUTER ADD-ONS

EXTERNAL VIDEO BOARD for the CORTEX and other computers using the TMS9929 V.D.P. Fully synchronises the computer to a video fed from camera or V.T.R. Produces a combined picture at the outputs. Unpopulated P.C.B. circuit and details — £30.00. Fully built £100.00. Tim Gray, 1, Larkspur Drive, Featherstone, Wolverhampton, West Mids. WV10 7TN.

EDUCATIONAL

IMPROVE YOUR PROSPECTS

with skills that employers want — learn the easy way with modern home study courses from Ideal Schools.

MODERN ELECTRONICS
 Train for success in the fastest ever growing industrial sector.

COMPUTER PROGRAMMING
 The demand for Programmers is increasing constantly — don't miss out!
 For free booklet write today to



IDEAL SCHOOLS
 (Ref: ETD5)
 60 St. Enoch Sq
 Glasgow G1 UK.
 Tel: 041-248 5200

COMPONENTS

CHEAP CASES

Absolute bargains, rack mounting & free standing. NEW, but manufacturers seconds. No damage.

Send s.a.s. for list.

C. Phillips, 'The Laurels' Tiptoe Road
 Wootton, New Milton, Hants BH25 5SJ
 MAIL ORDER ONLY

ADD-ONS

TANGERINE OWNERS at last 2 **6809** C.P.U. board with expandable monitor in colour. FLEX compatible. Also 14K RAM card to free EPROM space on TANEX S.A.E. For details . . . Ralph Allen Engineering; Forncett-End, Norwich. Tel: (095 389) 420.

BOOKS & PUBS.

THE ART OF MICRO DESIGN

by A. A. Berk £14.95

PRACTICAL DESIGN OF DIGITAL CIRCUITS

by Ian Kempel £11.50

INTERACING TO MICRO'S AND MICROCOMPUTERS

by Owen Bishop £6.75

PRACTICAL ELECTRONICS HANDBOOK

by Ian Sinclair £6.75

FOUNDATIONS OF WIRELESS AND ELECTRONICS 10th Edition

by M. G. Scroggle £9.95

* PRICES INCLUDE P&P *

Many more titles available

SAE for illustrated catalogue and FREE MEMBERSHIP of our EXCHANGE BOOK CLUB

JAMES ELECTRONICS (ETI)

PO Box 2, Rothwell, Leeds LS26 0UY

WHO NEEDS A LOGIC ANALYSER?

Illustrated guide shows you how to decode microprocesses Buff signals using a standard oscilloscope. Price £4.99 + 40p P&P. Crossed cheques/P.O.'s to:- Mr M Rimmer 20, Duddle Lane, Walton-le-Dale, Preston, Lancs PR5 4UD.

ESSEX

R JONES ELECTRONICS

267 Rectory Rd., Grays, Essex
 Tel: (0375) 33158 — 24hr answer phone
 Components, IC's, Full After Sales Services
 Electronic repairs — Industrial & Domestic
 Open 9-5.30pm 6 days a week

LANCASHIRE

ETESON ELECTRONICS

158 Lower Green,
E.E. Poulton-le-Fylde, Blackpool
 Tel: (0263) 885107
 Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.
 Electronic Component Specialists.

MERSEYSIDE

PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982
 47 Whitechapel, Tel 051 236 5489
 Liverpool 2
THE ELECTRONICS SPECIALISTS'
 Open: Tues-Sat 9.30-5.30

ELECTROMART

ELECTROMART

SCRATCH PAD

by Flea-Byte

Now that STC have taken over ICL, poor old Robb Wilmot can't have much to do to fill his time. So, it's hardly surprising that the former ICL technical supremo has accepted a posting with Sir Clive Sinclair, the leading edge of the new technology. Wilmot will be looking after a new division of the Sinclair empire, formed to develop wafer-scale integrated circuits. Wafer-scale integration (WSI) means using a single wafer — or slice of silicon crystal (the biggest of which are 6 inches in diameter) to hold one enormously complicated circuit. The benefits in speed and energy consumption, when compared to circuits which have to wire up several chips, are obvious. So much so that two or three years ago, Gene Amdahl — former IBM whizz-kid and founder of Amdahl Computers — started up his Trilog Corporation with the backing of six or seven of the world's leading computer manufacturers in an attempt to design and build a new computer based on WSI techniques. Some months, and many millions of dollars, later Amdahl gave up. The world, it would appear, was not ready for single circuits on a wafer — although it might be eager for a piece of

cheese on a Ritz cracker. Sir Clive and his new partner Robb 'One Per Desk' Wilmot are not deterred. They have some money and they're going to spend it. Maybe all those customer complaints have finally got through to Sinclair. Since the object of WSI is faster processing time with a lower overhead, perhaps Sir Clive is thinking of a wafer scale circuit with a 28-day clock cycle (or your money back).

★ ★ ★

Another intriguing new hiring came to my attention recently. It seems that Robert Moog is now working for Kurzweil Music. Moog, you will recall, is the man who invented the synthesizer. Or, to be more precise, he realised that silicon components could be used to make flexible and virtually noise-free voltage controlled circuits which could then be patched together to produce complex waveforms generating and wave shaping devices. Moog went on to design many of the now classic VCO, VCA and VCF circuits. He bundled several of them together with a piano-type keyboard and produced one of the very first analogue synthesizers. That was in the mid-sixties and, although he was once on the verge of joining the ranks of Biro, Hoover and Diesel — whose names have entered the language — his career took a nose-dive after reaching this peak. His company was bought out and, in his own words, Moog spent his remaining time there as

'window dressing'. Now he's moved across to join Ray Kurzweil, whose own career has been somewhat checkered. Kurzweil first came to public attention as the man behind optical character readers (OCRs) which can read text aloud, learn new typefaces and scan text for direct entry into databases. The company that produced the OCRs, Kurzweil Computer, was taken over by Xerox in 1980. It is said that Xerox were convinced by the Kurzweil charm that OCRs were about to become as common as photocopiers. It is also said that Xerox have been surprised to discover that this wasn't the case. Kurzweil himself made \$6 million from the deal and went on to set up Kurzweil Music and produce the Kurzweil 250 — an electronic keyboard specifically designed to reproduce the complex tones of a grand piano as accurately as possible. The 250 does more than that, of course. At \$11,000 a machine, it would have to. Kurzweil is very cagey about the technology used, revealing only that the 250 uses a combination of digital sound sampling and ROM-based algorithms. In order to distinguish the 250 from Fairlights, Synclaviers, Emulators and other instruments, Kurzweil describes his technique as 'sound modelling'. The role that Moog played in developing the keyboard seems to have been minimal. According to Kurzweil, his major contribution was 'to settle our endless debates about whether we had got a sound right'. Moog himself says that 'the Kurzweil people understand my capabilities and are using them'. I

don't know whether the Kurzweil 250 sounds like a grand piano or not, but I do know that it sounds like a hype.

★ ★ ★

Good news for those of you who can't afford a Sinclair C5. Designer Felice Campopiano has gone one better than the electric trike and produced an electric bike. The Pedelec's development has been funded by the Greater London Enterprise Board (to the tune of £76,000) and by Campopiano himself (£20,000). It will sell for £325 and have a maximum speed of 16 km/hr. We await with mounting excitement the announcement of an electric pedestrian.

★ ★ ★

Talking of which, more news from the Japanese robot front. The crafty blighters have produced a robot tea-lady which (who?) stops passers-by in their tracks by whispering — seductively, no doubt — 'I'm a vending robot, a tea sales girl. Let's talk.' Readers might like to submit the text of an ensuing conversation. I should point out, however, that ETI is staffed by editing robots and I am a writing robot. We're not noted for our sense of humour, but I'm sure if any of you succeed in making us laugh, I might persuade the subscription robots to send out a free subscription or a binder.

ETI

VISIT OR PHONE

OPEN 6 DAYS A WEEK ALL STOCKS ON DISPLAY

HENRY'S

404 Edgware Road, London, W2 1ED
01-723 1008 : 01-724 0323

VISA

MASTERCARD

ALL PRICES INCLUDE VAT

ASK HENRY'S FIRST

AUDIO ELECTRONICS ORDER BY POST OR PHONE OR CALL IN AND SEE FOR YOURSELF

EQUIPMENT • COMMUNICATIONS • COMPUTERS • COMPONENTS

<p>NEW LOW PRICES</p> <p>MODEM CARDS/COUPLER</p> <p>Brand new. Tested, answer and originate 300 BAUD unceasing acoustic modem card by famous manufacturer. RS232C Input/output, power supply +/- 12V at 180mA. Requires 2 magnetic earpieces. 2 switches. 2 LEDs and connectors to complete. Data supplied. Card only £19.95</p> <p>Card and remainder of small components Telephone Direct Line coupler type LTU 11 MK1L. Suitable for direct coupling PRESTEL adapters and the above acoustic modems. Integral Line select and autodial relays requiring TTL inputs data supply. £9.95</p> <p>1200 BAUD receive 75 BAUD send direct coupled modem for PRESTEL. Requires +5V supply with TTL inputs for data. Line select and autodial. LTU 11 direct coupler required. See above. Data supplied PRESTEL modem card £9.95</p>	<p>ASC 11 KEYBOARD</p> <p>69S DS Compact. 64 key - 5 function keys. Hall effect keyboard with reprogrammable (2716) ASCII output decoder EPROM. Steel key frame for good rigidity. Negative going strobe. Requires +5 volt -12 volt supplies. £24.95</p> <p>COMPACT 58 KEY ASCII KEYBOARD</p> <p>Contactless capacitive high reliability keys. Full 128 ASCII codes. Steel key frame for positive rigidity. 1ms strobe. single +5 volt supply. Repeat key control and caps. lock. £32.50 (UK C/P £1 00 either model)</p>	<p>COMPUTER FANS</p> <p>(UK C/P 600 each. £1.00 per pair)</p> <p>4" 220/230V AC Brand new £7.50 each</p> <p>4" 220/240V AC Ex-units £5.50 each</p> <p>4" 110/115V AC Ex-units £5.00 each</p>	<p>STEREO TUNER/AMPLIFIER 1000's sold</p> <p>4 wave-band stereo tuner amplifier by GEC MW/LW/ SW stereo FM radio 10 - 10 watt stereo amplifier. Inputs for PU tape in/out. Supplied as two assembled units. - easy to connect as illustrated £21.95 (UK C/P £1 50)</p>
<p>THERMAL PRINTER</p> <p>COMPLETE WITH FULL HANDBOOK. 3 ROLLS PAPER</p> <p>£49.95 (UK C/P £1.05)</p> <p>SUITABLE FOR TANDY BBC ORIC NASCOM GEMINI ACORN DRAGON ETC. ETC. (Interface unit with leads £15 - state model) (your enquiries invited)</p>	<p>TOROIDAL TRANSFORMER</p> <p>250 watt isolating trans. Plus 22v 1A, 6.3v 1A, 4 1/2" dia. x 1 1/4".</p> <p>£4.50 (UK C/P 85p)</p>	<p>POCKET RADIATION DETECTORS</p> <p>Desimeter for Gamma and X-Rays. O-5r (UK C/P 56p)</p> <p>£6.95</p>	<p>CASSETTE MECHANISMS</p> <p>Fitted counter. Motor. Stereo record and erase heads. Solenoid, etc. Brand new available 6V DC or 12V DC (state which) £5.95 (UK C/P 65p)</p> <p>ALSO miniature stereo cassette replay mechanism. 12V. 105 x 100 x 40 mm. £5.50 (UK C/P 65p)</p>
<p>ITT 2020 CABINET</p> <p>Professional computer case with keyboard cutout. 18" x 15.5" x 4.5" (front slopes). Ideal for single board computers like the Nascom or Gemini Multiboard (3 cards, etc). Very heavy gauge (25") plastic with metal base. Attractive silver grey finish. £22.95 (UK C/P £2.05)</p>	<p>CHERRY ADD-ON KEYPAD</p> <p>16 button pad non-enclosed £5.95 (UK C/P 50p per 1 to 2)</p>	<p>NICADS</p> <p>EVEREADY 6.4 Volt HEAVY DUTY NICAD approx. 3 1/2" diam x 3 1/2" with magnetic switch £5.95 (UK C/P 55p.1)</p>	<p>MARRIOTT TAPE HEADS</p> <p>(UK C/P 50p per 1 to 4)</p> <p>1/2" TRACK XRPS36 Low Imp. £3.50</p> <p>XRPS18 Med Imp. £2.50</p> <p>XES11 Erase for above £1.25</p> <p>1/2" TRACK 8X RP63 R/P Erase for above £2.25</p> <p>CASSETTE HEADS</p> <p>Stereo £2.95 Mono £1.95 Stereo erase £1.00</p>
<p>STEREO RADIO TUNER</p> <p>Ready built Mw Lw Stereo FM By well known Hi-Fi manufacturer Approx. 6 1/2" x 3 1/2" x 1 1/2" With Data £4.95 (UK C/P 65p)</p>			

ALSO IN STOCK Large range of tools, components, speakers, accessories, peizos, mics, nicads, CB, etc.

cortex

**HARDWARE
SOFTWARE**

MDEX disc O/S + BASIC	£95
MDEX Professional Dev. Sys.	£275
CORTEX POWER-BASIC disc extensions	£43
MDEX Extensions	
Editor	£35
Relocating Assembler/linker	£35
FORTH — screen editor, assembler	£55
— graphics — better than BASIC	£35
PASCAL — by Pre Brinch Hansen	£35
QBASIC — fast BASIC compiler	£150
UCSD Pascal, SPL, META, WINDOW, SPELL	
CORTEX tape software	
Pengo — fast machine code action	£6
Golf — excellent animation	£6
Micropede — rampant caterpillar	£6
Space Bugs, Pontoon, Breakout	each £6
Cassette/CDOS word processor	£13
Add £2 for software on CDOS disc	
Disc Drives	
80 track double-sided double-density	£190
40 track single-sided double density	£120
E-BUS Floppy/Winchester Controller	£135
E-BUS 64/128 Kbytes DRAM card	£145/£245
E-BUS 9995 Processor card	£145
80*24 Character video card	£48

State disc format and add VAT to all prices
!!Brainstem Issue 2 out soon!!



MICRO PROCESSOR ENG LTD
21 HANLEY ROAD SHIRLEY
SOUTHAMPTON
SO1 5AP
TEL: 0703 780084






Newrad

NEWRAD INSTRUMENT CASES LTD

Manufacturers for the Electronics Industry

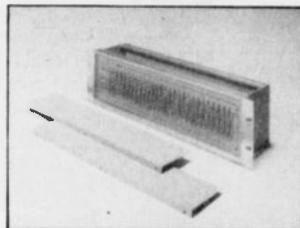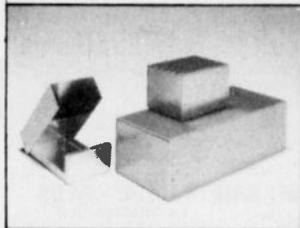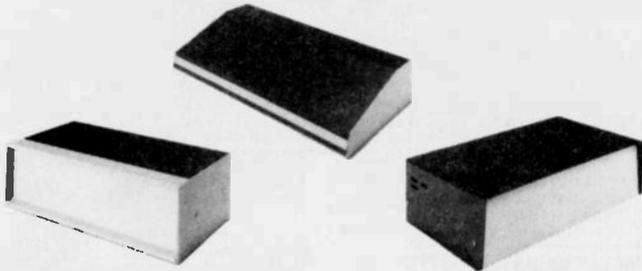UNIT 19 · WICK INDUSTRIAL ESTATE · GORE ROAD
NEW MILTON · HANTS · BH25 6SJ
Telephone: NEW MILTON 621195



WE MANUFACTURE BEAUTIFUL ENCLOSURES

At prices you will find difficult to beat.

Alloy boxes from 80p to rack mounted units from £15 and a host of ranges and sizes in between. Well made - well finished - and all British.

Send large SAE for catalogue which includes £5 in vouchers

MAIL ORDER ADVERTISING

British Code of Advertising Practice

ADVERTISEMENTS IN THIS PUBLICATION ARE REQUIRED TO CONFORM TO THE BRITISH CODE OF ADVERTISING PRACTICE. IN RESPECT OF MAIL ORDER ADVERTISEMENTS WHERE MONEY IS PAID IN ADVANCE, THE CODE REQUIRES ADVERTISERS TO FULFIL ORDERS WITHIN 28 DAYS, UNLESS A LONGER DELIVERY PERIOD IS STATED. WHERE GOODS ARE RETURNED UNDAMAGED WITHIN SEVEN DAYS, THE PURCHASER'S MONEY MUST BE REFUNDED. PLEASE RETAIN PROOF OF POSTAGE/DESPATCH, AS THIS MAY BE NEEDED

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided

1. You have not received the goods or had your money returned; and
2. You write to the Publisher of this publication; summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent (up to a limit of £2,000 per annum for any one Advertiser so affected and up to £6,000 per annum in respect of all insolvent Advertisers. Claims may be paid for higher amounts, or when the above procedure has not been complied with, at the discretion of this publication, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.)

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payment made in response to catalogues etc. received as a result of answering such advertisements). Classified advertisements are excluded.


ETI ADVERTISERS INDEX

Armon	14
Audio Electronics	14/15
BK Electronics	6
BNRES	42
Bradley Marshall	60
Cricklewood	31
Crimson	14
Cybernetic Applications	60/61
Display Electronics	8
Electrovalue	61
Greenbank	18
Henry's	65
ICS	42
Kirkland Business Centre	18
Maplin	OBC
Microprocessor	66
Newrad Instruments	66
Partechnic	18
Powertran	IFC/IBC
Rapid	10
Riscomp	31
SME	14
Stewart of Reading	14
Technical Book Service	66
Technomatic	16 & 17
TK Electronics	31
Watford Electronics	4 & 5

MCS-1

DIGITAL SAMPLER & DELAY LINE

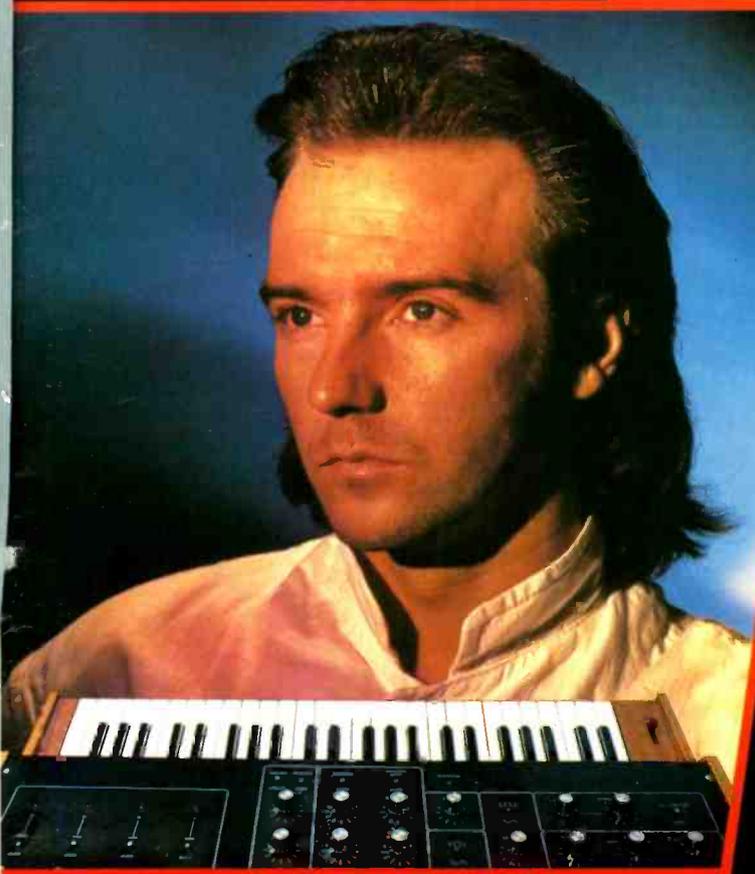Just one of our customers for the MCS/1
- Midge Ure of Ultravox.
Get the professional sound of a
Powertran MCS/1 into your act.



Once again, Powertran and E&MM combine to bring you versatility and top quality from a product out of the realms of fantasy and within the reach of the active musician.

The MCS-1 will take any sound, store it and play it back from a keyboard (either MIDI or ν /octave). Pitch bend or vibrato can be added and infinite sustain is possible thanks to a sophisticated looping system.

All the usual delay line features (Vibrato, Phasing, Flanging, ADT, Echo) are available with delays of up to 32 secs. A special interface enables sampled sounds to be stored digitally on a floppy disc via a BBC microcomputer.



The MCS-1 gives you many of the effects created by top professional units such as the Fairlight or Emulator. But the MCS-1 doesn't come with a 5-figure price tag. And, if you're prepared to invest your time,

it's almost cheap!
MCS-1 complete on ν £849 + VAT
Save even more with the MCS-1 kit:
only £599 + VAT
Demonstration Tape £2.50 + VAT



Powertran kits are complete down to the last nut and bolt, with easy-to-follow assembly instructions.

Specification

Memory Size: Variable from 8 bytes to 64K bytes.
Storage time at 32 KHz sampling rate: 2 seconds.
Storage time at 8 KHz sampling rate: 8 seconds.
Longest replay time (for special effects): 32 seconds.
Converters, ADC & DAC: 8-bit companding.
Dynamic range: 72 dB.
Audio Bandwidth: Variable from 12 KHz to 300 Hz.
Internal 4 pole tracking filters for anti-aliasing and recovery.
Programmable wide range sinewave sweep generator.
MIDI control range: 5 octaves.
+1 V/octave control range: 2 octave with optional transpose of a further 5 octaves

POWERTRAN

CYBERNETICS LIMITED

POWERTRAN CYBERNETICS LIMITED

Portway Industrial Estate, Andover, Hants SP10 3ET, England
Telephone: Andover (0264) 64455

Access/Visa cardholders - save time - order by phone.





BIG CAT

All new in the 1985 Catalogue



From a gentle purr to a mighty roar, the tightly controlled power of the beast is yours to command!

PROFESSIONAL QUALITY HIGH POWER LOUDSPEAKERS

A new range of superb quality loudspeakers.

- ★ Virtually indestructible high temperature voice-coil reinforced with glass-fibre
- ★ 100% heat overload tolerance
- ★ Advanced technology magnet system
- ★ Rigid cast alloy chassis
- ★ Linen or Plastiflex elastomer surrounds
- ★ 5-year guarantee (in addition to statutory rights)



Available in 5, 8, 10, 12, 15 and 18 inch models with 8Ω and some 16Ω impedances and with input powers ranging from 50W to 300W e.g.

- 5in. 50W 95dB 8Ω: XG39N / 16Ω: XG40T £17.95§
- 8in. 100W 98dB 8Ω: XG43W £29.95§
- 10in. 100W 100dB 8Ω: XG46A £29.95§
- 12in. 100W 101dB 8Ω: XG49D £29.95§
- 12in. Twin Cone 100W 100dB 8Ω: XG50E / 16Ω: XG51F £31.95§

Note - the output power doubles for each 3dB increase (ref 1W @ 1m).

PRECISION GOLD MULTIMETERS



A new range of very high quality multimeters offering truly amazing quality at the price.

- Pocket Multimeter. 16 ranges, 2000Ω V DC/AC £6.95§ (YJ06G)
- M-102BZ with Continuity buzzer, battery tester and 10A DC range. 23 ranges. 20,000Ω V DC £14.95§ (YJ07H)
- M-2020S with Transistor, Diode & LED tester and 10A DC range. 27 ranges 20,000Ω V DC £19.95§ (YJ08J)
- M-5050E Electronic Multimeter with very high impedance. FET input. 53 ranges including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95§ (YJ09K)
- M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated PCB for long-term reliability and consistent high accuracy (0.25% +1 digit DCV) £42.50§ (YJ10L)

N.B. All our prices include VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail order (except catalogue).

MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 SHOPS

- BIRMINGHAM Lynton Square, Perry Barr. Tel: 021-356 7292.
 - LONDON 159-161 King Street, Hammersmith. W6. Tel: 01-748 0926.
 - MANCHESTER 8 Oxford Road. Tel: 061-236 0281
 - SOUTHAMPTON 46-48 Bevois Valley Road. Tel: 0703 25831.
 - SOUTHEND 282-284 London Rd. Westcliff-on-Sea. Essex. Tel: 0702-554000
- Shops closed all day Monday.

§ Indicates that a lower price is available in our shops.

Our huge range of top quality electronic components at very competitive prices are all detailed in our catalogue, and with well over 600 new lines in our 1985 edition and many design improvements, it's well worth getting a copy. Here are just a few examples from the catalogue. (The items below are NOT kits).

- ★ Most phono and jack plugs now with integral strain relief sleeve - gold-plated types also available from 14p (gold from 70p)
- ★ Stereo Disco Mixer with cross-fade, talk-over, cue monitoring, aux input, slide controls. Only £58.95 (AF99H)



★ 10-Channel Stereo Graphic Equalisers - 3 models - basic; with peak level meter; and with spectrum analyser - from £77.95



★ Digital Delay Line permits Slap-back, Doubling, Flanging, Chorus and Echo. 11 controls. Only £195.00 (AF98G)

★ Video Enhancer improves picture quality when recording from one VTR to another, and with TV's with monitor input. Only 28.95 (XG59P)

★ Detailed descriptions of the exciting new 74HC range of IC's which combine the advantages of CMOS and TTL. From 46p

★ Keyboards: sloping keys, two-tone grey, mounted in steel frame, very smart cases (extra) available. 61 keys, only £33.95 (YJ12N) 79 keys, only £37.95 (YJ13P)


★ 1% Resistors now 50ppm °C, 0.4W, only 2p each!

★ Auto transformers 120 240V 50VA, £10.75§ (YJ56L). 100VA £14.95§ (YJ57M). 150VA £16.95§ (YJ58N). 250VA £21.95§ (YJ59P).

★ Digital Clinical Thermometer. Only £13.95 (FK51F)



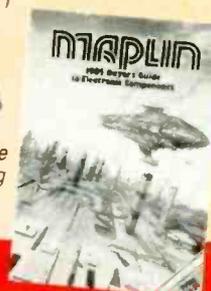Check our 1985 Catalogue for all our other fascinating new lines.



1985 CATALOGUE

Pick up a copy now at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).



☎ Phone before 2pm for same day despatch.

Post this coupon now for your copy of the 1985 catalogue. Price £1.35 + 40p post and packing. If you live outside the U.K. send £2.40 or 11 International Reply Coupons. I enclose £1.75.

Name 355

Address 5/25

All offers subject to availability.

Prices firm until August 10 1985