


electronics today

INTERNATIONAL

DECEMBER 1987 £1.40

TEST GEAR

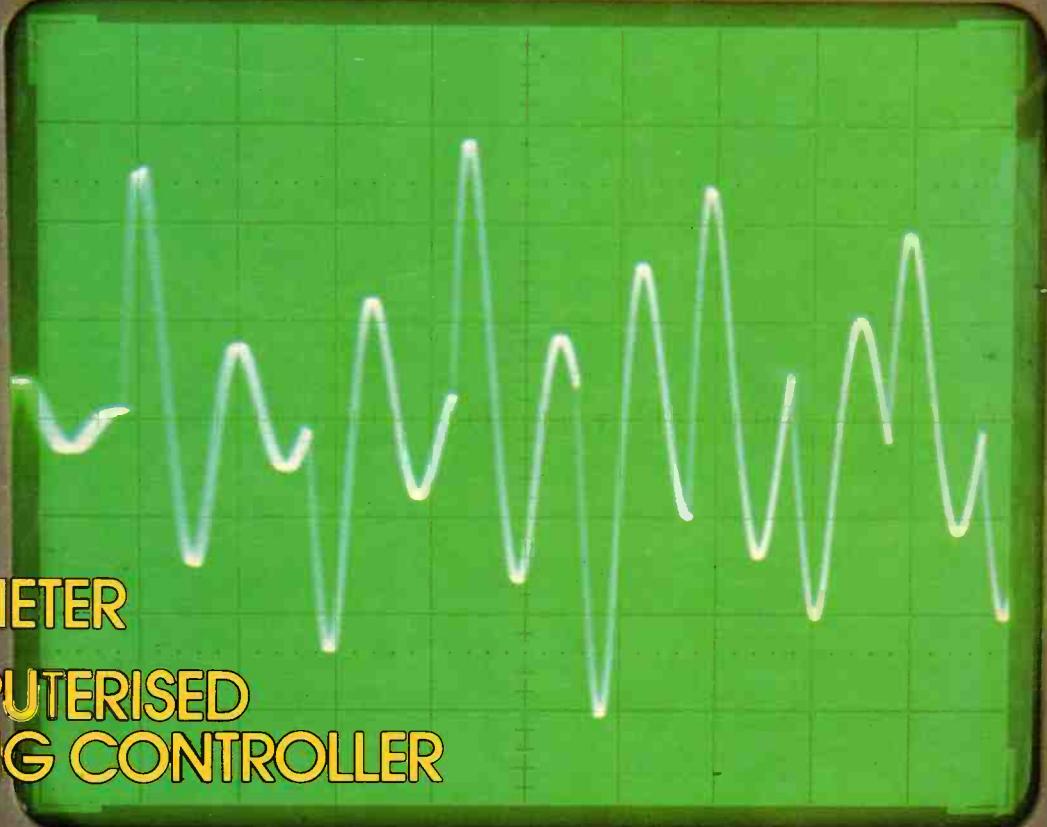WHAT YOU NEED & HOW IT WORKS
BUYING SECOND HAND



SWR METER

COMPUTERISED
HEATING CONTROLLER


INTENS.



FOCUS



ILLUM. OVER

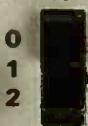

SCAN



1 kHz



CAL.



COMPONENT

TESTER

YOUR FREE COMPONENTS
TO BUILD THE ETI DREAM MACHINE

OMP POWER AMPLIFIER MODULES

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre PCB, and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.



NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV) If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.



LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.



POWER RANGE

8" 50 WATT R.M.S. Hi-Fi/Disco.
20 oz magnet 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea
12" 100 WATT R.M.S. Hi-Fi/Disco.
50 oz magnet 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB PRICE £28.60 - £3.00 P&P ea

MCKENZIE

12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco
2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB PRICE £29.99 + £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone. Res. Freq. 45Hz. Freq. Resp. to 14KHz PRICE £31.49 + £3.00 P&P ea
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz PRICE £57.87 + £4.00 P&P ea
10" 60 WATT R.M.S. 1060GP Gen Purpose/Lead Guitar/Keyboard/Mid/P.A.
2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.99 + £2.00 P&P
10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.
2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB PRICE £44.76 + £3.00 P&P
15" 200 WATT R.M.S. C15200 High Power Bass.
Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £62.41 + £4.00 P&P
15" 400 WATT R.M.S. C15400 High Power Bass.
Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB PRICE £89.52 + £4.00 P&P.

WEM

5" 70 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq. 52Hz. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB PRICE £22.00 + £1.50 P&P ea
8" 150 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB PRICE £32.00 + £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB PRICE £36.00 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1½" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB PRICE £47.00 + £3.00 P&P ea

SOUNDLAB (Full Range Twin Cone)

5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB PRICE £9.99 - £1.00 P&P ea.
6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB PRICE £10.99 - £1.50 P&P ea.
6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1½" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB PRICE £12.99 - £1.50 P&P ea.
10" 60 WATT R.M.S. Hi-Fi/Disco etc.
1½" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB PRICE £16.49 + £2.00 P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt). Price: £8.62 + 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/ RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA / ACCESS/C.O.D. ACCEPTED.

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position key operated facia switch - off - test - armed. 30 second exit and entry delay.

Indoor alarm - Electronic swept freq. siren. 104dB output.

Outdoor Alarm - Electronic swept freq. siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00 Usual Price £228.85

BKE's PRICE £89.99 + £4.00 P&P

? Why buy a collection of self-assembly boards!

IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12". Watts R.M.S. per cabinet. Sensitivity 1W 1mtr dB.

OMP 12-100 Watts 100dB. Price £149.99 per pair.

OMP 12-200 Watts 102dB. Price £199.99 per pair.

Delivery Securicor £8.00 per pair

OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies. XLR connections. MF600 Fan cooled. **Three models** (Ratings: R.M.S. into 4 ohms), Input Sensitivity 775mV.

MF200 (100 + 100)W. £169.00 Securicor

MF400 (200 + 200)W. £228.85 Delivery

MF600 (300 + 300)W. £322.00 £10.00

1 K-WATT SLIDE DIMMER

- * Control loads up to 1kW
- * Compact Size, 43" x 1" x 2 1/2"
- * Easy snap in fixing through panel cabinet cut out
- * Insulated plastic case
- * Full wave control using 8 amp triac
- * Conforms to BS800

* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.

PRICE £13.99 + 75p P&P

BSR P295 ELECTRONIC TURNTABLE

* Electronic speed control 45 & 33 1/3 r.p.m. * Plus Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1/2" cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14v D.C. 65mA Price £36.99 £3.00 P&P



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

- TYPE 'A' (KSN2036A) 3" round with protective wire mesh ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 40p P&P
- TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P
- TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For Quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P
- TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P
- TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment LED Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following — 3 Turntables (Mag.), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot. L. & R. Master Output controls. Output 775mV. Size 360 x 280 x 90mm. Price £134.99 — £3.00 P&P



B. K. ELECTRONICS DEPT ETI


UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR TEL: 0702-527572



electronics today

INTERNATIONAL

AN ARGUS SPECIALIST PUBLICATION

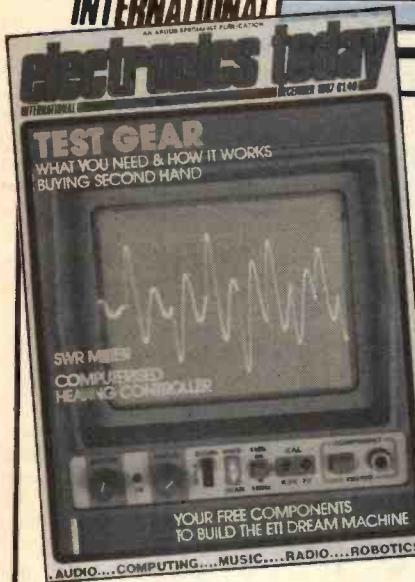

Cover oscilloscope courtesy of Henry's Audio Electronics

Geoff Bains: Editor

Ian Pitt: Deputy Editor

Paul Chappell: Projects Editor

Christopher Harris: Ad Manager

Julie Capstick: Classified Sales

Andrew Selwood: Copy Control

Dave Bradshaw: Group Editor

Published by Argus Specialist Publications Ltd., 1 Golden Square, London W1R 3AB. Tel: 01-437 0626.

UK newtrade distribution by SM Distribution Ltd., 16-18 Trinity Gardens, London SW9 8DX. Tel: 01-274 8611.

Overseas and non-newtrade sales by Magazine Sales Department, 1 Golden Square, London W1R 3AB. Tel: 01-437 0626.

Subscriptions by Infonet Ltd., 5 River Park Estate, Berkhamsted, Herts HP4 1HL. Tel: (04427) 766614.

Typeset by Project Three.

Printed by Adlard & Son, The Garden City Press.

Covers printed by Loxley Brothers Ltd.

ISSN
0142-7229



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1987 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates: UK £16.80 Europe: £21.00 Middle East: £21.20 Far East: £22.80 Rest: £21.50 or US\$32.00.

NOV. 1987

VOL 16 No.11

125

1 Golden Square
London W1R 3AB
Tel: 01-437 0626
Telex: 01-881 1896

ARGUS
PRESS
GROUP

FEATURES

TEST EQUIPMENT.....11

Keith Brindley looks at what test gear is available, what it all does, why you need it and how to use it.

to good use this phasor diagram theory he has been covering recently to good use.

SECOND TIME AROUND.....16

Julian Nolan shows how to save a small fortune by buying test equipment second hand. When you know what to look for, there's a lot of bargains out there waiting.

HARDWARE
DESIGN CONCEPTS.....22
Mike Barwise has filtered out the useful bits from all the technical data on integrated and switched-on capacitor filters.

CIRCUIT THEORY.....20

Paul Chappell shows you how to put

1987 INDEX.....34
Details of all the projects, features, Tech Tips and reviews from the past 12 months of ETI.

PROJECTS

HEATING MANAGEMENT SYSTEM.....25

Harry Bloomfield has everything under control. Keep your home in the tropics but your fuel bills in their place this winter with this sophisticated computerised design.

ELECTRONIC VIOLET.....41
If you thought a row of ivories was the last word on musical instruments then think again. Ronald Alpiar has added to his collection of classical instruments with help from a BBC micro and a lot of ingenuity.

THE DREAM MACHINE.....37

You got the free PCB last month. The free components are on this month's cover. So what's keeping you? Get out the soldering iron, fill the hot water bottle and wait for the Sandman.

SWR METER.....46
Andrew Armstrong uses a simple but cunning sensor to produce an accurate SWR meter for CB or 2m use, and it's a power meter to boot.

REGULARS

NEWS.....4

NEXT MONTH.....6

SATELLITE TV MAG AD.....6

DIARY.....7

READ/WRITE.....9

BACKNUMBERS.....33

PHOTOCOPIES.....33

SPECIAL OFFERS.....19,62

SUBSCRIPTIONS.....15

OPEN CHANNEL.....53

ONCE OVER.....53

THE HI-FI SHOW REPORT.....54

PLAYBACK.....55

PCB SERVICE.....56

OOPS!.....57

PCB FOIL PATTERNS.....58

CLASSIFIED ADS.....63

AD INDEX.....66

If you're still itching to get your hands on the TMS34010 graphics processor described in the April 1987 issue you may be interested to hear about a new design kit from Texas Instruments. It includes all you need to design a bit-mapped graphics system including a TMS34010 processor, a TMS34070 colour palette, an assembler/linker/simulator package and all the necessary data and user guides.


The kit costs £340 plus £2 postage plus VAT from Online Distribution Ltd, Melbourne House, Kingsway, Bedford MK42 9AZ. Tel: (0234) 217 915.

The BBC is to change the frequency of its long-wave Radio 4 transmitters following a recent decision by the World Administrative Radio Conference that all long-wave stations should operate at 9kHz frequency spacings. The new Radio 4 frequency will be 200kHz (1500m) instead of 198kHz (1515m). The long-wave transmitters currently maintain a frequency stability of one part in 1011 or better (using the National Physical Laboratory's caesium standard) and are used by some industries as a reference source. Such companies are advised to check with their equipment suppliers or manufacturers so that modifications can be made to suit the new frequency.

Twits is the slang name for travelling wave tubes and if you're into twits you may be interested in a set of free literature which has just been made available by Ferranti. It includes specifications on travelling wave tubes and tube amplifiers for radar applications and can be obtained from the Professional Components Division, Ferranti Industrial Electronics Ltd, Dunsinane Avenue, Dundee DD2 3PN. Tel: (0382) 89311.

Your mains driven clock or timer can be given a battery back-up with the help of a new 50Hz crystal timebase kit from Electronics and Computer Workshop Ltd. It operates from any DC supply between 5 and 20 volts and uses a 3.2768MHz crystal to ensure a stable output frequency. The kit costs £20.38 inclusive from ECW Ltd, Unit 1, Cromwell Centre, Stepfield, Witham, Essex CM8 3TH. Tel: (0376) 517 413.

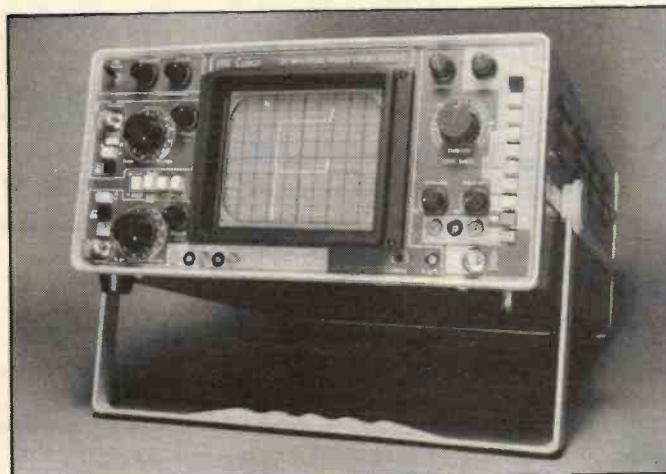Industrial Automation Products is the title of a 200-page catalogue from Analog Devices which describes techniques and devices for data acquisition, signal conditioning, analysis and control. The catalogue includes design hints and a tutorial section on 'real-world IO' and is available free-of-charge. Contact Analog Devices, Station Avenue, Walton-on-Thames, Surrey KT12 1PF. Tel: (0932) 232 222.



Hidden Depths Of 3-in-1 Scope

Crotech Instruments has launched a 25MHz dual-trace oscilloscope which incorporates a bench power supply and a dual component comparator.

The Model 3133 features a timebase range from 40ns/division to 200ms/division, a maximum vertical sensitivity of 2mV/division and a number of trace manipulation facilities including X-Y and addition or subtraction of channels.

Triggering is reliable up to 40MHz and a 10:1 timebase hold-off is provided to ensure reliable triggering on aperiodic and complex waveforms. An active TV

trigger circuit is also included. The rise time is 14ns.

The built-in power supply provides outputs of +5V at 1A and ±12V at 200mA. The dual component comparator allows both active and passive components to be tested and can be used for circuit signature comparison.

The Crotech Model 3133 costs £319 plus VAT and comes with a two-year guarantee.

For further details contact Crotech Instruments Ltd, 2 Stephenson Road, St. Ives, Huntingdon, Cambridgeshire PE17 4WJ. Tel: (0480) 301 818.



Accurate Meter For The Milli-ohms

Startronic claims its latest milli-ohm meter is far more accurate than previous models.

Covering the range from 1 milli-ohm to 200 ohms it is accurate to better than ±0.1% yet uses a test current of only 5mA maximum.

The M210 has three automatically selected ranges and displays the results on a 3½ digit LCD. An over-range indication is provided for resistances above 199.9R. The unit is powered by a 9V PP3/MN1604 battery and includes an automatic shut-off to prevent

the meter being left on for long periods by mistake.

Startronic expects the M210 to be used for checking motor and transformer windings, PCB tracks, switch and connector contacts and soldered connections. It can also be used in earth continuity testing to check for compliance with IEE wiring regulations.

The M210 costs £165 plus VAT complete with test leads and instructions.

Startronic (UK) Ltd, Beeching Road, Bexhill-on-Sea, East Sussex TN39 3LG. Tel: (0424) 214 291.

Testing Times For British Standards

Is your electrical equipment safe to use?

Of course it is, you say, it has a neat little label on it which says This appliance complies with the requirements of British Standard number...!

Unfortunately those reassuring little messages may not be all they appear. Any manufacturer can claim its products reach the required standard and slap on a label to say so.

No doubt companies will go on doing this but if they want their claims to carry real weight they can now turn to a newly-introduced testing service run by the British Standards Institution itself.

The service, called BSI Testing is based in Hemel Hempstead. In return for a suitable fee, manufacturers can have their products inspected in detail and a full report drawn up. Products which pass the tests will be allowed to carry the wording 'a sample of this product has been passed by BSI Testing as complying with the relevant British Standard (BS...). Report number... refers.'

The new service will be run alongside BSI's existing quality assurance programmes such as the well-known Kitemark standard. BSI Testing has been operating this and other programmes for over 25 years and is recognised both nationally and internationally as a leading test centre.

Further details of the new service can be obtained from Robin Dandy, Assistant Director of BSI Testing, on (0442) 230 442.

Microvitec Go For Laser Discs

Microvitec, best known as a manufacturer of colour computer monitors, has recently installed a laser videodisc cutting system which is says is the first of its type in the UK.

The system is manufactured by the Optical Disc Corporation of America and can produce videodisc masters for as little as £395 each compared with £2500 or more using other systems.

The Recordable Laser Video-discs (RLVs) which result from this process are less robust than conventional videodiscs but are fully laservision compatible. They are 12in, single-sided and offer up to 36 minutes playing time or 5400 still frames.

Further details can be obtained from the Microvitec Laser Lab, Futures Way, Bolling Road, Bradford BD4 7TU. Tel: (0274) 734 944.

Manpower Prospects Show Increase

The latest quarterly survey of employment prospects by Manpower PLC shows a slight net increase in the number of electronics companies planning to take on more staff.

Only 4% of employers in the electronics and computer manufacturing industry are planning to lay-off staff compared with 7% in the last quarter and 6% a year ago. At the same time the number planning to increase their staff has risen from 29% to 30%.

If the percentage of companies planning to shed staff is subtracted from the number planning to increase staff, the net figure can be seen to have risen from 22% last quarter to 26% now. The net figure for the last quarter of 1986 was 23%.

Manpower specialises in providing temporary staff for a wide range of industries and carries out regular research on staffing requirements. The latest survey notes that the services sector still offers the best job prospects but that manufacturing (including electronics) is now running a close second. The public sector continues to offer much poorer job prospects by comparison.

Manpower PLC, Manpower House, 270-272 High Street, Slough SL1 1JL. Tel: (0753) 73111.

Data Sockets For BT Phone Lines


The familiar BT master sockets currently used on UK telephone installations will soon be replaced by a new type of multi-purpose connection unit.

As well as providing a socket for plug-in telephones the new wall boxes will include a terminal block for use with personal computers, facsimile machines, Prestel terminals and many other types of data and telecommunications equipment.

The units will be known by the initials NTE (Network Terminating Equipment) and have been designed by Astralux Dynamics to British Telecom's requirements. A detachable wiring module allows connecting leads to be made up at the work bench and simply clipped into the NTE when ready.

Astralux Dynamics has already begun production of the NTE units and expects them to be fitted to all new domestic and single-line business installations in the near future.

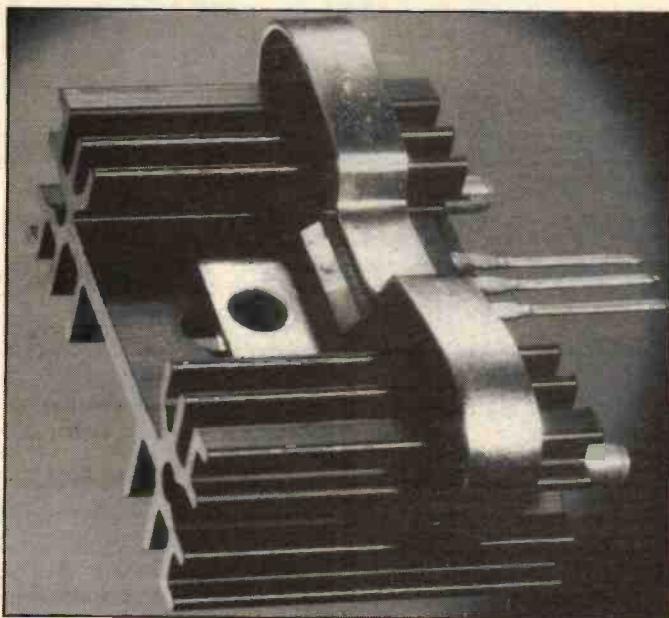Astralux Dynamics Ltd, Red Barn Road, Brightlingsea, Colchester, Essex CO7 0SW. Tel: (0206) 302 571.



Choice Of Heatsinks For The Board


The latest heatsinks from Marston-Palmer can be soldered directly to PCBs and come in a wide range of sizes, profiles and component mounting options.

Known simply as the board-mounted range they offer thermal resistances from 7 to 12°C/W and can be supplied with or without solderable PCB pins. The three extrusion profiles vary in size from 34.5 x 12.5mm to 36.8 x 15mm and all are available in four standard lengths ranging from 25mm to 63mm.

The heatsinks can be supplied ready-drilled in a variety of patterns to suit standard semiconductor packages or undrilled so that components can be attached by means of a spring clip.

Prices range from about 28p to 56p each in quantities of ten or more and a postage charge £2 is payable on small orders. All prices exclude VAT.

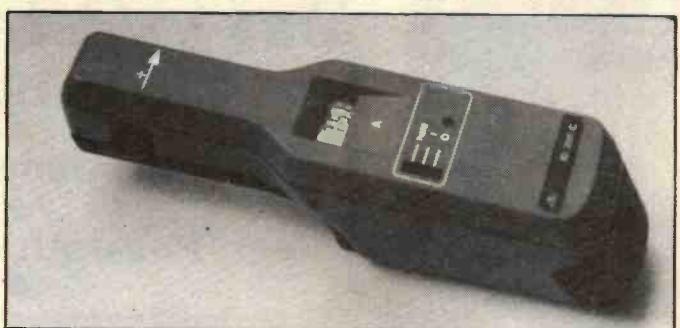Marston Palmer Ltd, Wobaston Road, Fordhouses, Wolverhampton WV10 6QJ. Tel: (0902) 783 361.



Clamps Mean Amps For DC Too

Hartmann and Braun has introduced a clamp-type digital ammeter which measures DC currents.

Like conventional AC clamp meters it works without being directly connected to the circuit under test. The spring-loaded jaws are simply clipped around a conductor and the current is indicated on a 3½ digit liquid crystal display.

The ID 200C uses Hall effect sensors and measures currents up to 199.9A. The accuracy is to within ±0.5A up to 100A and ±1.5A at higher currents. The jaws will accept conductors up to 14mm

diameter and a hold facility is included to allow measurements to be made in awkward places.

The meter will operate for up to 25 hours continuously on one alkaline 9V battery and has been designed to allow comfortable, single-handed operation. It weighs 200g and measures 46 x 51 x 175mm (1.8 x 2.0 x 6.9in).

The ID 200C costs £179.50 plus VAT and comes with a one year guarantee. It can be obtained from Alpha Electronics Ltd, Unit 5, Linstock Trading Estate, Wigan Road, Atherton, Manchester M29 0QA. Tel: (0942) 873 434.

• Axiom Electronics is distributing a data book which gives full technical details on the Sprague range of ICs. Its 750 pages cover linear devices, military CMOS, military driver ICs and a range of high voltage, high current and BiMOS power interface ICs. Applications circuits are included and the book is available free-of-charge from Axiom Electronics Ltd, Turnpike Road, Cressex Industrial Estate, High Wycombe, Buckinghamshire HP12 3NR. Tel: (0494) 461 616.

• Five Star Connectors was set up three years ago as part of STC and aims to supply a wide range of connectors backed up by expert technical advice. The range extends from jack plugs to military-spec multipole connectors and everything is available ex-stock and with no minimum order charge. Full details are contained in a 216-page A4 catalogue which is available from Five Star Connectors, Edinburgh Way, Harlow, Essex CM20 2DF. Tel: (0279) 442 851.

• Fast Fourier Transform (FFT) analysers are rapidly coming down in price and are now used in the assessment of brain waves, wow and flutter, transformer harmonics, horn quality, telephone filter performance and even for gear box analysis. A booklet covering many of these applications has been put together by Hakuto and is now available free on request. Contact Mr. D. Coffey, Hakuto International (UK) Ltd, 33-35 Eleanor Cross Road, Waltham Cross, Hertfordshire EN8 7LF. Tel: (0992) 769 090.

• Texas Instruments has introduced a range of pin-compatible replacements for industry standard comparators offering up to 20 times less power consumption. The TLC339, 393, 3702 and 3704 are fabricated in LinCMOS technology and offer comparable performance to the LM339, 393 and so on, but with input current drains of 20µA per comparator maximum. For further information contact Richard Mann at Texas Instruments Ltd, Manton Lane, Bedford MK41 7PA. Tel: (0234) 63211.

• MathCAD runs on an IBM PC or compatible and allows the user to enter equations, display them with full notation and special symbols, calculate the results and then produce a printout with tables or graphs if required. The package costs £245 plus VAT but you can find out what it's capable of for free using the Mini MathCAD version. It does everything the full system does except that there are some restrictions on storage and printout. Mini MathCAD can be obtained from MathSoft International, FREEPOST, Tamworth, Staffordshire B79 7BR. Tel (0827) 86239.

NEXT
MONTH

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

FAT & FESTIVE, FULL OF FACILITATING FABRICATIONS AND FASCINATING FEATURES

Next month's ETI has 16 extra pages to keep you amused over the festive period. Each and every one is crammed with Christmas goodies of an electronic nature.

MUSIC POTPOURRI

There's a bumper collection of music circuits for all ETI readers intent on adding a little song to the festivities. Where else can you get envelopes, overdrives, cross-pans, Walsh functions and a silk purse, all in the same article?

NEW, IMPROVED...

The ETI mains conditioner from the September 1986 issue has proved to be very popular with the computer and


hi-fi owning populace. Now ETI brings you the improved version which not only does an even better job of cleaning up all the mains-borne grunge but shows you what's going on with lots of pretty lights as well.

MUCH MUCH MORE...

That's not all, of course. The January ETI also features the second parts of the Heating Management System and the Electronic Violet and several new projects to whet the appetite of your soldering iron. And there's the regulars too. Where would Christmas be without your monthly dose of news, reviews, diary, letters and ads from ETI?

The articles listed are all under way but unforeseen circumstances may prevent publication.

JANUARY ETI — OUT DECEMBER 4th

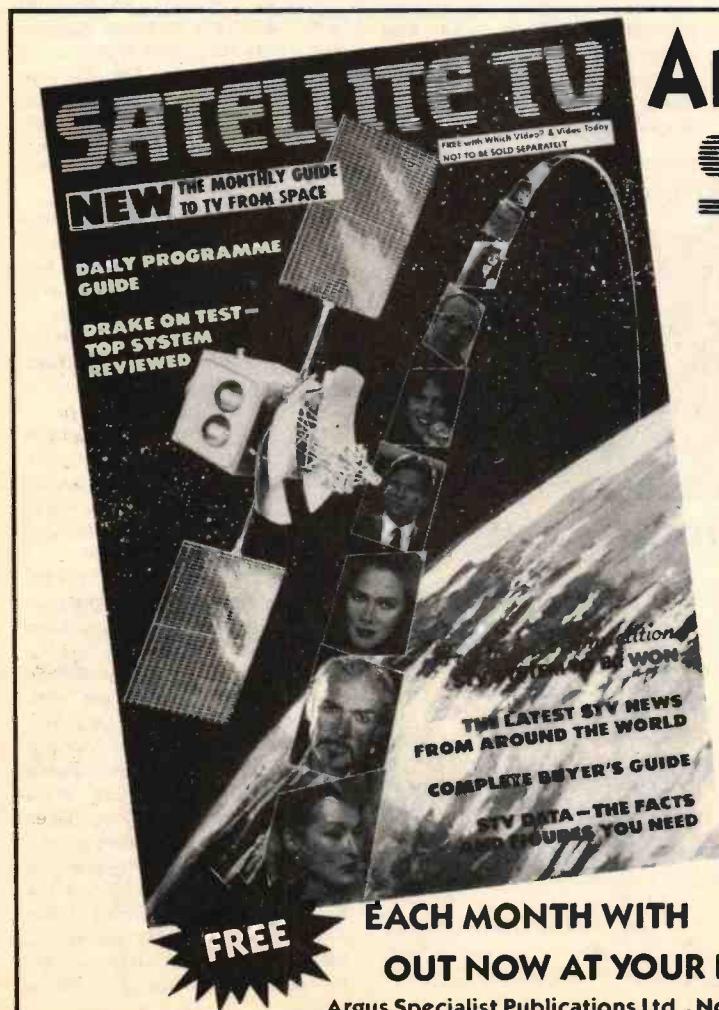

Are you receiving it? SATELLITE TV

- ◆ Easy to understand
- ◆ Full programme details
- ◆ In-depth reviews
- ◆ Interesting features
- ◆ Questions answered
- ◆ and more...

Each month this magazine contains all you need to know about Satellite TV — the latest news, hardware and programme reviews, answers to often-asked readers' questions, interesting features and a comprehensive programme listing for the next month's viewing.

YOU CAN'T AFFORD TO MISS IT!

video
TODAY

**Which
and Video?**

Argus Specialist Publications Ltd., No 1 Golden Square, London W1R 3AB



A Hot Tip From Weller

The Thermolock soldering iron from Weller offers precise control of tip temperature thanks to a novel electronic key.

The temperature is set by plugging one of three temperature keys into a socket on the iron. Each key sets a different temperature (600°C, 700° or 800°C) and is laser trimmed for an accuracy of better than ±6°C.

The iron is rated at 42W and operates from a 24V DC supply. The element is controlled by a thyristor which operates in a zero-voltage switching arrangement,

removing the risk of transients on the tip which might cause damage to static sensitive devices.

The Thermolock is designed for use with the ET series of soldering tips and is supplied with an ETA tip already fitted. A 700° temperature key is also supplied with each iron, the other two keys being sold as optional extras.

The Thermolock costs £42.50 plus VAT and postage and is available from Axiom Electronics, Turnpike Road, Cressex Estate, High Wycombe, Buckinghamshire HP12 3NR. Tel: (0494) 461 616.

Plessey And GEC To Go Halves

Plessey and GEC are to merge their international telecommunications businesses barely a year after a GEC take-over bid for Plessey was ruled out by the Monopolies Commission.

The 50-50 joint venture will produce a company with assets of £600 million and annual sales of more than £1.2 billion. It will take GEC and Plessey from their present positions as 10th and 12th largest companies in the world telecoms market up to 9th place — ahead of the Dutch giant Philips.

The merger was announced on October 1st although it was made clear that agreement still has to be reached on many of the details. However, it is almost certain that job losses will result since both companies are currently producing System X exchange equipment at separate plants. Concentrating this work would bring considerable economies, as was pointed out by the watchdog body Ofcom during last year's takeover bid.

News of the merger came shortly after the publication of a major report on the telecommunications industry by the financial services company Alexander Laing and Cruickshank. The report argues that demand for System X exchanges will wind down after 1990 and that companies involved in the traditional telecoms manufacturing areas of telephones and exchanges will face a fiercely competitive future.

The report also suggests that the future of public switching systems lies with the larger European companies and foresees joint ventures and co-operative agreements as the only means whereby UK companies can remain competitive.

The report is entitled 'Uncrossing the lines? Prospects for Telecommunications Operations & Equipment Manufacturing In The UK'. It is available from Alexander Laing and Cruickshank, Piercy House, 7 Copthall Avenue, London EC2R 7BE. Tel: 01-588 2800.

DIARY: DIARY: DIARY: DIARY: DIARY: DIARY: DIARY: DIARY:

Knowledge Based Systems in Government — November 4-5th

Gatwick Hilton, London. Contact Online at the address below.

Analogue IC Design — November 5th

The IEE, London. Tutorial lecture. Contact the IEE at the address below.

Reproduced Sound Conference — November 5-8th

Hydro Hotel, Windermere. Topics covered include acoustics, digital techniques, measurements and electro-acoustic music. Contact the Institute of Acoustics on 031-225 2143.

The Future Of The Personal/Home Computer — November 10th

The IEE, London. Lecture by Sir Clive Sinclair. Contact the IEE at the address below.

Electronic Message Systems — November 10-12th

Tara Hotel, London. Contact Online at the address below.

Computers in The City — November 17-19th

Barbican Exhibition Centre, London. Contact Online at the address below.

Electronic Displays — November 17-19th

Kensington Exhibition Centre, London. Contact Network Events at the address below.

Interact '87 — November 17-19th

Kensington Exhibition Centre, London. See June '87 ETI or contact Network Events at the address below.

COMPEC — November 17-20

Olympia, London. Contact Cahners at the address below.

Interactive '87 (Interactive video) — December 1-3rd

Metropole Exhibition Centre, Brighton. Contact PLF Communications on (0733) 60535.

System Security — December 1-2nd

Wembley Conference Centre, London. Contact Online at the address below.

Cellular and Mobile Communications — December 2-3rd

Wembley Conference Centre, London. Contact Online at the address below.

Satellite Communications — December 2-3rd

Wembley Conference Centre, London. Contact Online at the address below.

Cross Channel Cable Link — December 3rd

Lecture by G. Struthers (CEGB) at Gonville Hotel, Gonville Place, Cambridge. Contact Eastern Region IEEIE on (0603) 628321.

The UK Space Programme — December 7th

The IEE, London. Lecture by R. Gibson of the British National Space Centre. Contact the IEE at the address below.

British Engineering Supplies & Technology — January 18-21st

Olympia, London. Contact Mack-Brooks Exhibitions on (07072) 75641.

The Which Computer Show — January 19-22nd

NEC, Birmingham. Contact Cahners at the address below.

Electro-Optics And Laser UK — March 22-24th

NEC, Birmingham. Exhibition which runs alongside the Optics-Ecoosa '88 conference at the Birmingham Metropole Hotel. Contact Cahners at the address below.

Computing in the Next Generation — March 25-27th

Annual conference of the British Computer Society's Young Professionals Group. Julia Allen on 01-637 0471 for the venue and other details.

HF Radio Systems And Techniques — April 11-13th

The IEE, London. Conference organised by the IEE and the Institute of Mathematics and its Applications. Contact the IEE at the address below.

ATE 1988 (Automatic Testing and Test Instrumentation) — April 26-28th

Metropole Exhibition Centre, Brighton. Contact Network Events at the address below.

MILTEST 1988 (Military Testing Equipment) — April 26-28th

Olympia, London. Contact Network Events at the address below.

Addresses:

British Kinematograph Sound and Television Society, 547-549 Victoria House, Vernon Place, London WC1B 4DJ. Tel: 01-242 8400.

Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham TW1 3SZ. Tel: 01-891 5051.

Institution of Electrical Engineers, Savoy Place, London WC2R 0BL. Tel: 01-240 1871.

Network Events Ltd, Printers Mews, Market Hill, Buckingham MK18 1JX. Tel: (0280) 815 226.

Online International Ltd., Pinner Green House, Ash Hill Drive, Pinner, HA5 2AE. Tel: 01-868 4466.

For KITS & COMPONENTS - Choose the easy way - with

**Send
50p* & SAE
for CATALOGUE
(AUTUMN 1987)**

*refundable with first order

ORDERS: RING (01) 567 8910 - 24 HRS.

NEW ELECTRONIC GUARD DOG KIT



One of the best deterrents to a burglar is a guard dog and this new kit provides a barking without the biffle! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would-be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need is a mains power, intruder detector and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.

XK125 Complete kit of parts £21.95

DISCO LIGHTING KITS

DL1000K - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. £17.50

DLZ1000K - A lower cost uni-directional version of the above. Zero switching to reduce interference. £9.85

DLA/1 (for DL & DLZ1000K) Optional opto input allowing audio 'beat' light response. 70p

DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel £14.25

The DL8000K is an 8-way sequencer kit with built in opto-isolated sound to light input which comes complete with pre-programmed EPROM containing EIGHTY - YES 80! different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300 W output per channel.

And the best thing about it is the price.

ONLY £28.50



TEN EXCITING PROJECTS FOR BEGINNERS

This Kit has been specially designed for the beginner and contains a SOLDERLESS BREADBOARD, COMPONENTS, and a BOOKLET with instructions to enable the absolute novice to build TEN fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.

ORDER NO XK118 £13.75

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box. 18 time settings.

£42.90

XK114 Relay kit for CT6000, includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts. £4.30

701 115 Additional relays £1.80

VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver suitable for use with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2 cms. The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available - MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used.

MK12 IR Receiver (incl. transformer) £14.85

MK18 Transmitter £7.50

MK9 4-Way Keyboard £2.00

MK10 16-Way Keyboard £5.95

601 133 Box for Transmitter £2.60

HOME LIGHTING KITS

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting.

TDR300K Remote Control Dimmer £16.48

MK8 Transmitter for above £4.95

TD300K Touchdimmer £8.50

TS300K Touchswitch £8.50

TDE/K Extension kit for 2-way switching for TD300K £2.70

LD 300K Light Dimmer £4.35

READ/WRITE

Success On The Brain

Thanks for publishing an EEG monitor circuit which actually looks as though it may work! I haven't finished building it yet so I don't know for sure but I have worked on two designs from other sources in the past which were only good for soldering practice as they were totally useless in operation.

Thanks for a very interesting magazine with a good mix of theory and practice. Even though all is not immediately relevant, I find myself frequently referring to back issues, especially as new developments such as surface mounted devices and PALs become more common.

Keep up the good work.
Hugh Dogherty
Castlewellan, Co. Down.



Alarming Extras

Many thanks for the excellent Car Alarm from Bob Noyes in the August ETI.

To make the alarm simpler to operate (and harder to forget about) how about the following modification to replace key switch SW1 in the original.


With this setup the alarm will be automatically armed when the ignition key is turned to the off position and disabled in any other position. If the override switch SW1 is closed

CORK

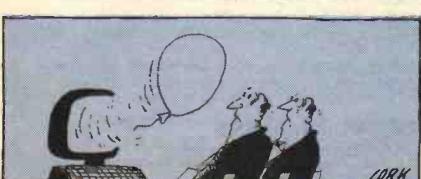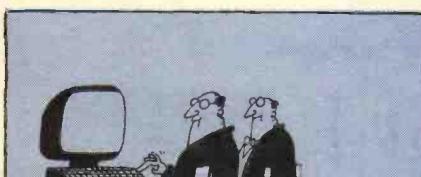

facilities to have large batches of PCBs made for each project to keep the prices low. However, the quality of boards produced is extremely good and the turnaround is now between a week and a fortnight — a far cry from the troubled days of a year ago.

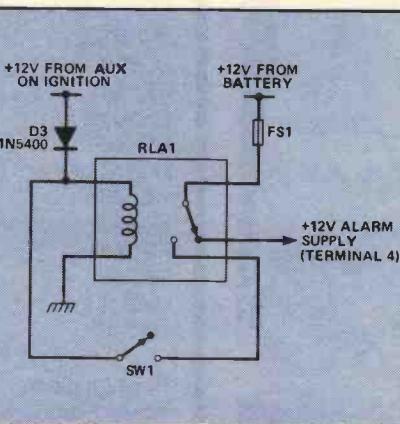The relay only consumes power when the ignition is on. D3 is included to prevent auxiliary circuits from being powered when the alarm is overridden.



when the alarm is off then the alarm will not be activated when the ignition is turned off — useful for stopping at filling stations and so forth.

The relay only consumes power when the ignition is on. D3 is included to prevent auxiliary circuits from being powered when the alarm is overridden.

Adam Hill
Tile Cross, Birmingham.

Thanks for a useful addition to a popular project.

Expensive PCBs?

What an excellent series John Yau's MIDI Master Keyboard was. I have now written to Mr. Yau to order the EPROM and offered a couple of suggestions for possible additions and accessories for the machine.

I enjoy the magazine very much. I think it is the most 'down to earth' of those currently available (no pun intended!).

It's a pity, then, that the PCB Service is relatively expensive compared with some of the opposition. Yes, I know, you did say a few months back that you were having difficulty in getting the PCBs produced economically. But still ...

George Metters
Stoke Gabriel, Devon.

Any constructive criticisms or additions to any project are always welcome. If any reader develops a published project (say, you write some extra code for the MIDI Master Keyboard EPROM) we shall be most interested in hearing of it and may well want to publish the additions in ETI.

The PCBs offered through the ETI PCB Service are a little on the expensive side because they are produced largely on a one-off basis. We do not have the

Cheap PCBs

After years of thrashing out PCB transparent artworks from magazines using rub-down transfers (and filling in the cracks afterwards) I have stumbled across an incredibly simple method of producing near-perfect artworks from the published foil patterns.

Ordinary drafting film is placed in the cartridge paper tray of an ordinary photocopier (not the old 'wet' type, though) and the foil pattern is placed on the glass in the normal way.

The resulting copy is very good. It's a little 'dusty' but the dust doesn't print through onto the board in the UV light box. The copy is fixed using an aerosol clear lacquer (such as RS 556-222) which protects and improves contrast. Et voila! — a positive transparency which is as good as the published foil pattern.

Any blobs on the copy can be corrected by scraping them off with a sharp knife before lacquering.

Rolf Startin
Hammersmith, London.

Mr. Startin sent us samples of each stage of the process and it must be said that the quality of the final PCB is excellent. The drafting film can be bought at any art shop or alternatively you can purchase celluloid film especially for photocopying. Now you've no excuse to avoid making those ETI projects!

This is page nine. You have just read eight pages of information, wit and satire in the form of the preceding cover, contents, news and ads. Surely there was something among that lot which calls out for comment or correction. I'll give you until the end of the magazine and then I expect you to put pen to paper. Write to:

Electronics Today International
1 Golden Square
London W1R 3AB.

TEST EQUIPMENT

Keith Brindley takes a look at the different types of test equipment available and assesses their usefulness to the home constructor.

There are three main areas in which test equipment is used: design and development; manufacture and quality assurance; service and repair. These three areas follow the stages of a product's life, from drawing-board to manufacture to use and ultimately to the scrap heap.

The complexity of the test equipment used at each stage varies enormously. For example, test equipment used at manufacture and quality assurance stages is typically large, complex and pricey — at these stages each appliance is affected by the equipment so the overall cost per appliance is quite small. Also, the better the appliance is made, the less likely it is to break down and require servicing. Size too is usually of little significance here.

Test equipment used for service and repair is a different matter. A service engineer complete with Ford Escort 1.3GL hasn't got a lot of room to spare in his travels, so size is of prime importance. Cost is a high priority, too: the equipment must be sufficient to allow effective service yet be cheap enough for use by all the company's service engineers.

In the development lab test equipment has also to be cost effective, although pure cost is not usually such an important criterion. Of particular concern is that it must be of sufficient complexity to allow the engineer to design and develop the appliance.

For the home constructor, the question of what test equipment to buy is often a knotty one. The home constructor uses test equipment in all three areas, developing, manufacturing and servicing a project from beginning to end. But as the project is not for sale, profit is not a motivating concern, so test equipment can only be financed from the constructor's own pocket. Obviously, the home constructor's test equipment must be as versatile and as cheap as possible.


The Ins And Outs Of Test Equipment

But what does test equipment actually do? In simple terms, it merely allows an observer to see how the appliance is operating. Once the observer has done this, a decision can be made to change appliance operation — but this is a human decision (with all except the most expensive automatic test equipment). Test equipment merely aids the observer.

Test equipment falls into two basic categories:

- equipment which provides a signal of some description to the appliance under test, and
- equipment which monitors and displays the operation of the appliance under test.

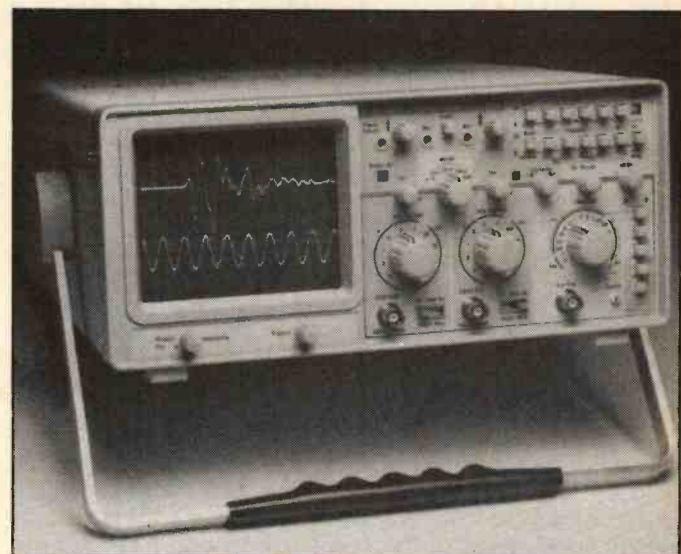The first category includes signal sources, waveform generators and even power supplies. The second category includes meters, oscilloscopes, analysers, etc. There is inevitably overlap between the two categories and some equipment may comprise parts from both, for example logic analysers which feature a digital pattern signal generator together with an oscilloscope-type display.



Before the introduction of the microprocessor, testing an appliance was often as simple as applying a suitable signal at the appliance's input and observing the signals obtained at each stage. Often the only test equipment required was an audio signal source and an AVO meter, maybe an oscilloscope. In many instances today, analogue or digital, this is still the case. When the microprocessor came along it brought with it the requirement to observe many signals simultaneously. An oscilloscope isn't capable of displaying more than a couple of signals at any one time — hence the development of the logic analyser.

The test equipment you need therefore depends almost totally on the projects you build. The more complex they are, the more complex (and costly) the test equipment you are likely to need.

Signal Sources

So what types of test equipment are available, and how do they function? We'll start with the first category we identified: equipment which provides a signal input to the appliance under test.

More by default than by design, signal sources are generally grouped into audio frequency sources (normally called low frequency oscillators) and radio frequency sources (normally called signal generators). There's no logical reason for this and not all manufacturers follow the convention.

This description of signal sources caters only for analogue appliances. Logic pattern generators or word generators are the digital equivalents of the analogue signal source, producing preselected serial or parallel data at a preselected speed.

As far as low frequency oscillators (LFOs) are concerned, most cover the frequency range 1Hz to about 1MHz in a number of switched ranges. Accuracy and stability depend mainly on the method used to produce the signal. Traditionally, harmonic oscillators such as the Wien bridge, the phase shift, or the bridged-T circuit (Fig.1) are used in cheap and cheerful LFOs, and these can produce distortion as low as only 0.001 per cent. The drawback is that stability is not particularly good and some drift of signal frequency can be expected. Another disadvantage is the limited range over which a harmonic oscillator can be tuned (about 3:1), so a lot of capacitor/resistor switching has to be done to produce a large overall output frequency range.

Another fairly cheap method of producing a signal is a relaxation oscillator, for example a stable multivibrator familiar to most home constructors. The most common relaxation design is the function generator shown in Fig.2 which has the advantage that an external voltage can be used to control the generated frequency. This means that a second oscillator can be used to sweep the function generator's output signal frequency over a preselected range — useful when testing some appliances. Frequency ranges of between about 0.01Hz to 2MHz are common, but although the frequency stability can be very precise the distortion is high because any sinewave output is only approximated from the triangular wave of the integrator provided. Typical distortion figures are 1 to 2 per cent. Provided this distortion figure is not a problem, the cheapness and versatility of function generators probably makes them the best type of signal source for the home constructor.

It is also possible to obtain digital LFOs which create an analogue waveform from digital information stored in a ROM. The information is converted to an analogue signal by a DAC. Stability of the signal output is usually pretty good because the stored information is read out on accurate, quartz-locked clock pulses and the distortion depends on the number of quantisation levels (the number of bits in each stored word or information). LFOs like this are usually too expensive for the home constructor but are worth bearing in mind.

RF signal generators can be made with harmonic oscillators in the same way that cheap and reasonable quality LFOs can. The two oscillators commonly used are the Hartley and the Colpitts (Fig.3). Again, limited tuning ranges mean that a lot of switching is needed to get a wide overall range and again, frequency stability is not good.

One way of beating the limited tuning range problem is by mixing the variable frequency oscillator's output with that of a fixed frequency oscillator, as in Fig.4. These heterodyne oscillators are common but the frequency stability is not improved because it still depends on the stability of the variable frequency harmonic oscillator.

Most more expensive signal generators use the phase-locked loop principle, sometimes called the synthesiser method. In this type of signal generator a fixed frequency and highly stable oscillator (usually a crystal reference) is used, so stability is excellent. A detecting circuit (Fig.5) compares the phase of this oscillation with the phase of the signal from a voltage-controlled oscillator after it has passed through a variable divider circuit, while the voltage-controlled oscillator's control voltage is supplied by the phase detector. The feedback loop formed by this phase-locking system stabilises the output signal to a frequency equal to the reference oscillator frequency multiplied by the division ratio of the divider circuit, so an extremely accurate and well defined output signal results.

Whatever your choice of signal source, make sure it is capable of doing whatever you think it will need to do

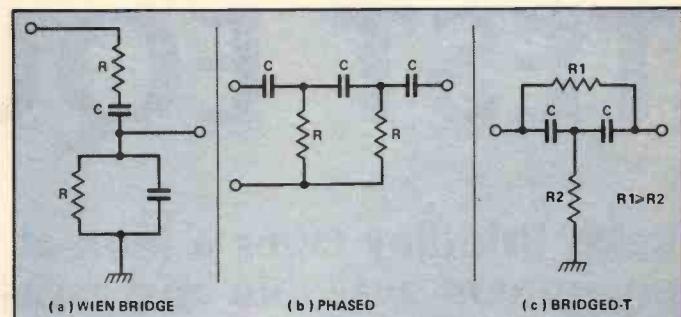


Fig.1 Typical low frequency harmonic oscillators.

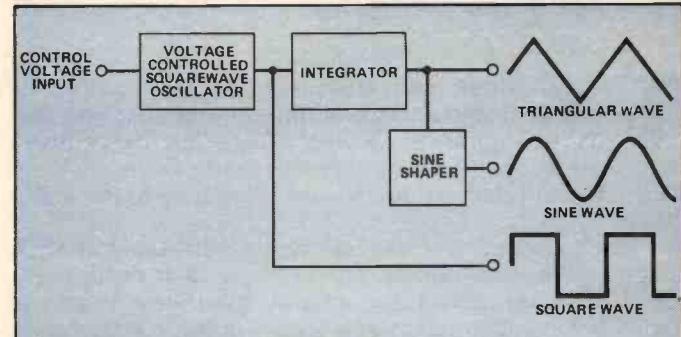


Fig.2 Block diagram of a function generator.

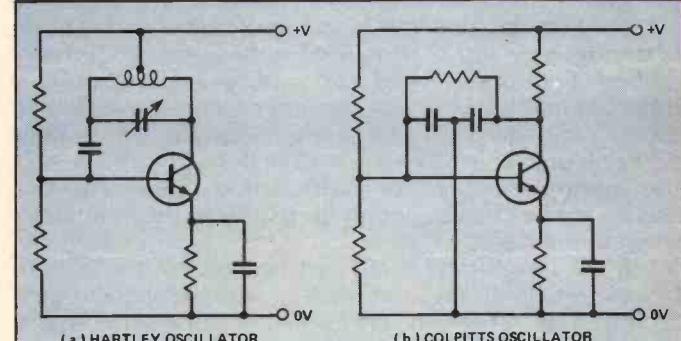


Fig.3 Typical RF harmonic oscillators.

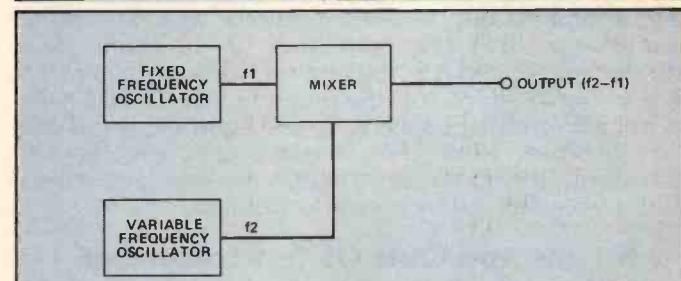


Fig.4 Block diagram of a heterodyne oscillator.

now and in the future. For instance, if you can't afford a source with built-in sweep facilities, buy one with inputs for voltage control of frequency so you can cobble together a simple oscillator to give you the desired sweep.

Meters

Until the last five years or so most meters were analogue with a moving coil or similar display device, but recent developments in segmented LED and LCD displays have allowed fairly cheap digital meters to be made.

The moving-coil movement used in analogue meters is only capable of displaying a value of current or voltage between about $10\mu\text{A}$ to 1mA or $50\mu\text{V}$ to 5V but with parallel and series resistance networks (shunts and multipliers) other voltages and currents may be measured.

FEATURE: Test Equipment

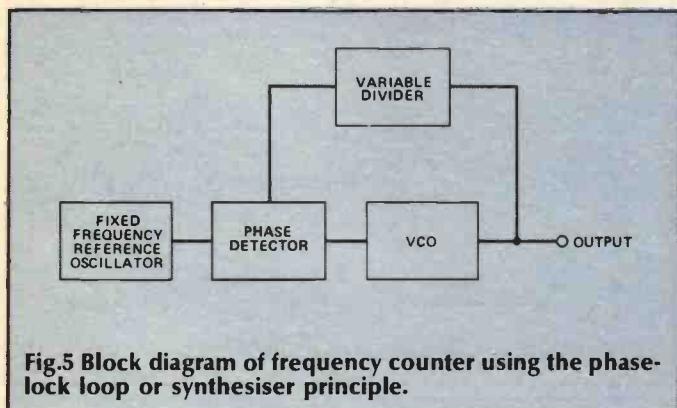


Fig.5 Block diagram of frequency counter using the phase-lock loop or synthesiser principle.

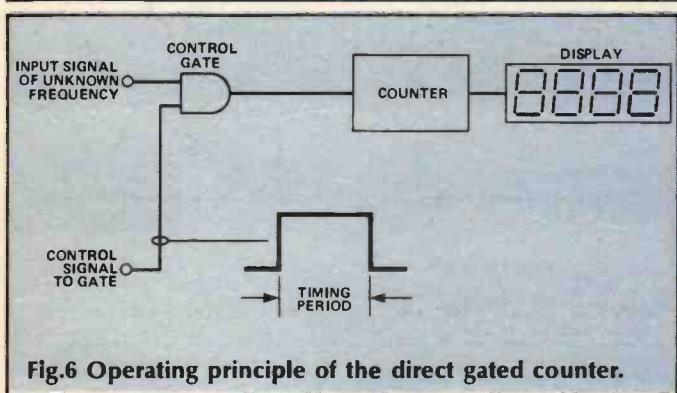


Fig.6 Operating principle of the direct gated counter.

Most moving-coil movements are used in a simple switching arrangement with resistors to give the common-or-garden multimeter capable of measuring a complete range of voltages and currents. A local power source is used to create a current through an external circuit enabling the multimeter to measure resistances as well. The famous Avometer is probably the best known example.

One problem with a basic moving-coil multimeter is its inherent insensitivity. A typical rating is 20,000 ohms per volt, which means that on a 5 volt range the multimeter's resistance to current is 20,000 times 5 which is 100,000 ohms. If the impedance of the circuit being monitored is high the meter's resistance may load the circuit and affect the overall impedance, so producing an inaccurate reading. As a general rule-of-thumb, the meter's resistance should be around ten times the impedance of the monitored circuit to ensure a reasonably accurate reading.

In some instances it will be impossible to ensure this ten times rule and in others you won't know the monitored circuit's impedance, so you won't know if the meter is loading it. Fortunately there is a way round this: take readings of the voltage on two of the meter's voltage ranges. If the monitored circuit's impedance is high enough to cause meter loading, the two readings will differ substantially.

If loading has occurred any reading displayed by the meter is inaccurate but the actual voltage in most instances can be calculated from the expression:

$$V = \frac{E_1 E_2 (R_2 - R_1)}{E_1 R_2 - E_2 R_1}$$

where V =the true voltage, E_1 =the meter reading on the first range setting, E_2 =the meter reading on the second range, R_1 =the input resistance of the meter on the first range setting, and R_2 =the input resistance of the meter on the second range setting.

Another way round the loading problem is to use an amplifier which has an extremely high input impedance as a buffer on the multimeter input. FET amplifiers and op-amps are ideal for this purpose.



Digital multimeters don't usually have this loading problem because their input stages normally include a high impedance input amplifier (around 10 megohm). So, on the face of it, a digital multimeter is the ideal. They are fairly cheap — some versions are much cheaper than analogue multimeters — and extremely accurate (analogue meters at best are only about $\pm 1\%$ accurate due to the limitations of the mechanical movement). However, a digital readout is not always the most convenient since it is quite easy to mis-read and any changes of input voltage (even quite slow changes) can give confusing displays.

For the home constructor, though, a meter is a necessity. If you can only afford one, my advice is to buy as good an analogue meter as possible. If you can afford two, get a digital meter as well.

Counters

Meters operate in only one dimension: they measure and display, say, a voltage, at any one instant in time. The second dimension of time can be incorporated into a measurement in a number of ways, one of which is with test equipment loosely classified as counters, more correctly universal counter timers (UCTs).

UCTs are used to measure occurrences over a specified time, so a UCT could be used to measure the number of cycles arriving each second, which is to say that it can be used to measure frequency. Or it could be used to measure the time between two physically separate events in seconds. Further, it could be used simply to count the number of events occurring. Because of this, UCTs are often lumped together under the title frequency, time and event counters.

Figure 6 shows a signal being gated before it is fed to a standard digital counter and display. The control gate is opened by a pulse of defined period, so the result displayed is simply the number of cycles occurring during that period. If the period is exactly one second, the result will be in Hertz. This is known as the direct gated counter principle. Different gating periods can be used to give different measurement ranges.

It shouldn't take an Einstein to work out that the gating period is critical — if the period is 5% out then the displayed result will be 5% out, too. The gating periods of a UCT are therefore obtained by dividing down the output signal of a stable high frequency, crystal-controlled reference oscillator and the user should always choose the longest gating period possible to ensure highest accuracies. But even crystal oscillators can vary with temperature and ageing, so for highest accuracy some UCTs use temperature compensated crystal oscillators (TCXOs) or even oven controlled crystal oscillators (OCXOs). Most UCTs will have provision for the user to apply a standard reference frequency, too, such as those broadcast by international standards bodies.

For most frequency measurements, the direct gated counter is ideal but for low frequencies the gating period has to be so long that it becomes impracticable.

An alternative is the reciprocating gated counter in which the gate is opened for the period of the input signal itself rather than for a predetermined period. When the gate is open the output of a reference oscillator is passed to the counting circuits. If the input frequency is, say, 1Hz, the gate will open for alternate 0.5s half cycles and with a reference oscillator frequency of 2MHz a total of 1,000,000 pulses will be counted during each gate period. This figure is passed to an arithmetic unit which calculates the reciprocal of 1,000,000 and displays the result. The answer, of course, is 0.000001MHz which is 1Hz.

Some UCTs use the phase-lock loop principle to measure and display a low frequency input, multiplying the frequency of the input signal before gating and then moving the decimal point on the display to restore the original figure.

Most UCTs aren't formed by just one of these principles but are a combination of two or more. Sometimes prescalers may be used to allow the measurement of extremely high frequency signals by first dividing down the signal so that it is within the range measurable by the equipment. Extremely high frequency signals can also be heterodyned down to be measured by the UCT.

Cathode Ray Tube Displays

Most well known of all CRT display test equipment is the oscilloscope and it's probably the most useful piece of test equipment anyone can have. Given some basic limitations it can even be used to measure voltage, frequency and time and so in many applications can be used instead of a multimeter and UCT. But that is not its real power because it is capable of displaying much more than the simpler test equipment can do.

The oscilloscope is a further example of test equipment which measures in two dimensions. However, the 'scope's CRT screen display is a graph of voltage against time, so what you see on the screen is an actual picture of what's happening in the circuit being monitored.

The representation of a signal in graphical form on the CRT screen is called a trace and oscilloscopes usually have one (single-trace) or two (dual-trace) circuits within them capable of doing it. A dual-trace 'scope can display two signals from the circuit under test almost simultaneously — but not quite simultaneously. In a dual-trace 'scope a single electron beam is shared by both traces, so the best the 'scope can do is display one signal, then the other, then return to the first, and so on. This normally occurs so rapidly that eye persistence means you can't tell the switching is happening. Some very expensive oscilloscopes have two separate electron beams but they are normally well out of the home constructor's price range and need no further mention here.

A block diagram of an oscilloscope is shown in Fig.8. Vertical amplifiers raise the input signal level to the voltage required by the vertical deflection plates of the CRT. Similarly a horizontal amplifier amplifies the timebase generator's output to the level required by the horizontal deflection plates. By varying the gains of the vertical amplifiers and by generating varying lengths of timebases, many different amplitudes and frequencies of input signal may be represented on screen.

The basic or real-time oscilloscope can only display repetitive or periodic waveforms. A number of oscilloscopes are non-real-time and can display non-repetitive waveforms. The most well known is the digital storage oscilloscope which captures and stores a single occurrence of an input signal over a given time. The signal

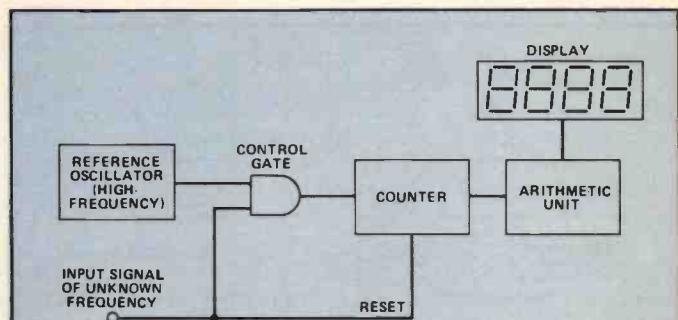


Fig.7 Operating principle of the reciprocating gated counter.

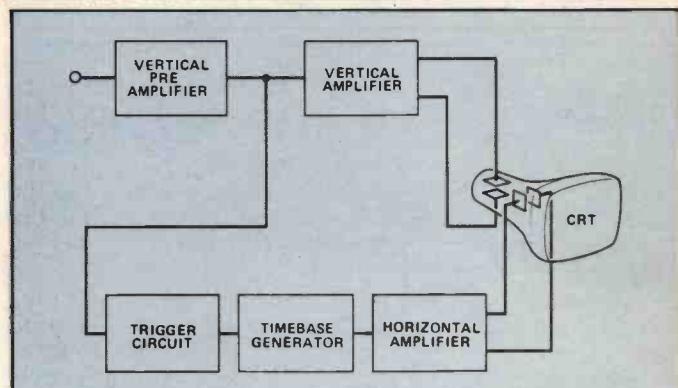


Fig.8 Block diagram of a basic oscilloscope.



is stored as digital information in RAM and then displayed repetitively on the screen. Storage 'scopes are more expensive than basic versions so the user has to decide whether the ability to view non-repetitive waveforms is worth the difference. In more than 99% of oscilloscope applications the viewed waveform will be periodic, so perhaps that helps you to make up your mind.

So what makes a good oscilloscope? First, bandwidth is important. Like any electronic system, the oscilloscope only passes a limited range of frequency components and those outside the bandwidth range are drastically reduced in amplitude. Obviously, the greater the oscilloscope's bandwidth, the greater the range of frequencies which can be represented on screen: common bandwidths are 10 to 20MHz.

Also important is the range of vertical amplifications. The greater the amplification, the smaller the signal that can be represented on screen. Oscilloscope screen displays are marked in a grid of centimetre square divisions known as the graticule. Amplification factors are usually denoted in volts/division or volts/centimetre. Typical amplification factor ranges are from about 10 millivolts/div to 5 volts/div but the better the 'scope, the greater the range.

FEATURE: Test Equipment

So, do you need an oscilloscope for general-purpose, home constructor project building? As long as your project works first time without hiccups, a 'scope is not necessary. But if it doesn't work first time where do you start to fault-find without a 'scope? Ask any engineer what the most important piece of test equipment is — the answer is bound to be an oscilloscope. Buy one if you can afford it.

Logic Analysers

The oscilloscope is ideal for monitoring most analogue and some digital appliances but many digital appliances have buses of 8, 16, or even 32 bits. Only two signals (occasionally four) can be represented on the screen at any one measurement with an oscilloscope, so for this application it's pretty useless. A more specialised test instrument using the oscilloscope principle is the logic analyser.

In simple terms it is a multi-trace digital storage oscilloscope combined with a digital word generator. But it really is much more powerful than that because it's a microprocessor-based device and hence is software-controlled. Whether a logic analyser needs to be in the home constructor's test equipment list is arguable, but it's worth knowing what they're capable of if only for reference.

Logic analysers are usually microprocessor-independent, which means they can be used to monitor systems built around a wide range of microprocessors. To interface between the logic analyser and a particular system you will need interface modules, often nicknamed pods (personality option devices!). A pod is microprocessor-specific so it can be used only to monitor signals within a particular microprocessor's system — a Z80-based pod couldn't be used to interface the logic analyser with an

8085-based system. Sometimes the pods are separate devices, but they can be integral to the logic analyser on, say, a plug-in card. Used with a pod, the general-purpose logic analyser becomes known as a composite logic analyser.

Logic analysers are used in three main operating modes:

- timing analysis — in which the analyser is used very much as an oscilloscope, monitoring signals immediately before and after a particular trigger point. Signals are displayed on the CRT screen but as logic levels against time (unlike the oscilloscope's voltage against time display). So-called glitches in system operation can usually be spotted. The internal word generation functions of the analyser may be used to create the trigger point.

- state analysis — rather than watching logic levels to detect glitches, state analysis presents system operation on-screen as machine code in groups of zeros and ones in binary form. Often, a feature of state analysis is that the machine code is reverse-assembled back into the assembly mnemonics of the system and displayed as such on-screen. This feature is known as disassembly.

- performance analysis — in which the microprocessor system's general software performance is monitored by the analyser. Displays in the form of graphs, histograms, etc may be used to show factors such as system address usage, program statement execution times, etc.

Using a logic analyser is rather like photographing using a zoom lens. First you use the widest angle on the lens (performance analysis) to see how the overall system operates. Then you zoom in closer (state analysis) to see step-by-step program operation. Finally, you zoom right in for a close-up (timing analysis) to look at the actual circuit signals.

ETI

FOR
ALL THE
DETAILS
OF THIS AND
MANY OTHER
ELECTRONICS
PROJECTS, GET
ELECTRONICS TODAY
INTERNATIONAL

SUBSCRIPTION RATES

12 issues UK
12 issues Europe
12 issues Middle East
12 issues Far East
USA
Air Mail Rates on Request

£16.80

£21.00

£22.80

£21.50

\$32.00

£21.20

£21.50

\$32.00

£21.80

£21.50

\$32.00

£21.80

£21.50

\$32.00

£21.80

£21.50

\$32.00

£21.80

£21.50

SECOND TIME AROUND

Julian Nolan shows how to pick up a bargain at the local auctions and equip your workshop without selling your house.

The total world market for test equipment has been estimated at \$5000 million annually, the UK accounting for over £270 million of this. Even when the defence market and indirect sales for export are taken away, the British market for test and measurement equipment is still worth an estimated £40 million per annum. Taking this over nine years and assuming the £40 million to be at least static, this implies there is approximately £350 million worth of test equipment in British industry at the present time.

Estimates show that 15% of this equipment is updated yearly. Currently most manufacturers change their equipment when it is around 7-10 years old but this is gradually being reduced and a replacement period of 3-7 years is expected in the future.

The equipment being disposed of is normally either sold at auction or direct to the appropriate parties. Being only several years old much of it retains a high percentage of its original value and is outside the reach of most amateurs. However, a proportion of the equipment is older or of lower original cost and because of this its secondhand value is lower. This is the range covered by this article.

There are many disadvantages and advantages associated with buying secondhand test equipment. In almost all cases the specification of second user equipment will be higher than that of new equipment of the same price and the quality of construction will usually be higher too. There are some instruments which are of only average constructional quality and these may prove unreliable but with well-constructed instruments of reasonable age and condition there is every chance the reliability will equal that of new equipment manufactured to sell at the same price.

The size and weight of older instruments can be considerably greater than that of comparable instruments manufactured today. This applies particularly to scopes and signal generators but if portability is not essential some relatively old but very good equipment can be obtained quite cheaply.

The obvious points to check are that all the functions work correctly and that the overall physical condition of the instrument is good. Don't be content with checking just the principal ranges and functions — check everything. If a few of the functions don't work correctly it implies that the previous owners weren't too fussy about looking after the instrument. Conversely, an instrument which works correctly in every mode — even those which don't get used too often — is more likely to have been well looked after and regularly serviced.



Marconi signal generators are well worth looking out for. This TF144H 10kHz-70MHz AM RF generator costs about £90

As regards physical condition, pay particular attention to the state of the front panel. If it is scratched and dented the instrument has obviously received a lot of use and this will be reflected in the state of the electrical circuitry. Dents and scratches in the side and top panels are less of a guide because most instruments pick up slight damage here through being stacked.

The innards should be reasonably dust-free and any vents or cooling ducts should be unobstructed. An instrument which has been operated for any period of time with clogged-up cooling vents may well have suffered general or localised overheating with a consequent reduction in reliability. This is particularly true of fan-cooled instruments. Check all the PCBs and components for burn marks and examine all the mechanical components such as switches and connectors. Dirty contacts can be cleaned but excessive wear will mean replacement and some complex switches are very expensive.

Another factor which should be taken into account is the type of active circuitry employed — valve, discrete semiconductor or IC. Many instruments manufactured before 1970 use valves and while these are likely to be less reliable than instruments using semiconductor devices they are still worthy of consideration. The deciding factors will probably be the quality of the particular instrument and your own familiarity with valve circuitry. A well-constructed valve instrument from a reputable manufacturer will be scarcely less reliable than its modern semiconductor counterpart and if you know

enough about valves to be able to service it properly there should be no problems.

Much the same can be said about instruments using discrete semiconductors. Some surprisingly complex instruments were built in the late 1960s using individual transistors throughout and while many of them are highly reliable they need to be checked carefully before purchase. Provided the instrument is made by a reputable company, is in good physical condition and works correctly in all modes of operation you should not go far wrong.

With all second-hand test equipment it is important to check that a service manual is either provided or is readily available. Fault-finding will be more or less impossible on many instruments without one and you will also need it in order to calibrate the instrument correctly. This is important because there is no point in buying high specification second-hand equipment if you are not going to keep it up to scratch. You might just as well spend your money on new equipment with a lower specification.


Oscilloscopes

Many electronics enthusiasts purchase a second-hand oscilloscope because they cannot afford a new one but even if you have a reasonable amount of money to spend you may still find that a used scope is a good buy. For example, a comparatively recent model like the Telequipment D83 (dual-trace, 50MHz bandwidth, delayed sweep, etc) can be purchased second-hand for only a fraction more than you would pay for a modern dual-trace 20MHz oscilloscope with only basic facilities. At the same time it should be borne in mind that oscilloscopes are complex instruments and spares such as CRTs and mains transformers may be difficult to obtain for some older models. The points mentioned in the following paragraphs should be checked carefully before buying any non-guaranteed oscilloscope.

The trace intensity should be such that the trace is clearly visible at the oscilloscope's fastest sweep speed on a triggered waveform of appropriate frequency. The intensity will naturally be better on scopes which use a higher accelerating potential but even on 2kV designs the trace should still be visible under these conditions. A faint or poorly-defined trace indicates either that the oscilloscope is incorrectly set-up or that the tube is reaching the end of its life. An oscilloscope in this condition should be avoided unless you are certain it can be repaired at a reasonable cost. It is also best to ignore any oscilloscope which has suffered screen-burn to such an extent that there are brownish-black points or lines on the tube face.

Digital storage oscilloscopes still command very high prices on the second-hand market but tube storage designs can be obtained for upwards of £100. Unfortunately storage tubes have a comparatively short life and can be very expensive to replace, some costing well over £700. On models such as the Tektronix 564 the tube life can be as little as two years and as these scopes are now around twenty years old they must be checked scrupulously before purchase. A worn tube will usually have a storage capacity which is only a fraction of the intended upper frequency and may also suffer from excessive flooding of the screen and a generally poor and ill-defined trace. All in all, it is best to avoid tube storage oscilloscopes unless they are offered with a comprehensive guarantee.

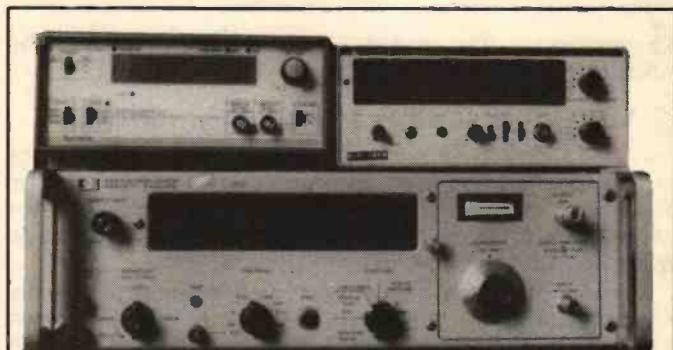Some high-performance oscilloscopes are sold as a mainframe containing only the tube, the power supply and some control circuitry. The timebase and pre-amplifier circuits are supplied as plug-in modules, allowing the specification and functions to be changed as required. These modules may or may not be included



Older digital frequency counters (such as the lower Hewlett-Packard 5245) can be relatively large with a maximum frequency range of about 50MHz but are built to an extremely high specification. The slightly newer Advance TC17 is of comparable size to modern gear

in the price of a second-hand instrument and this should be checked before purchasing because a full set of plug-ins can easily cost more than the mainframe.

Provided size and weight are not a problem some very good oscilloscopes can be purchased for under £200. One example is the Cossor CDU 150, a portable 35MHz dual trace solid-state scope which features delayed sweep and quite a high specification for around £150-£200. The SE Labs SM111 is another portable solid-state oscilloscope with a bandwidth of 18MHz and the useful ability to operate from either mains or external DC supplies. Typical prices are around £120-£160.

The Tektronix 500 Series is a range of mainframe hybrid oscilloscopes which are physically large and weigh around 47kg. The 545A offers dual trace, dual timebase and delayed sweep with bandwidths up to 24MHz depending on the plug-in modules used and represents good value at around £70-£90. The slightly newer 547 offers all the same features with a bandwidth of up to 50MHz and can be thoroughly recommended at around £140-£160. The 585A again offers similar facilities and has a bandwidth of up to 85MHz but its small screen area makes it a poor choice unless the increased bandwidth is particularly important to you. It costs about the same as the 547.

Plug-in modules for the Tektronix 500 Series are widely available and range in price from around £10 up to £500-£600 or so for an IL20 Spectrum Analyser unit. Among the modules available are the Type M which provides 4-traces with a 20MHz bandwidth and the 1A1 which offers two traces at 50MHz bandwidth. Both cost around £60.

A wide range of Telequipment oscilloscopes is also available for under £200 and most represent very good value.

Signal Generators

These offer fewer advantages than oscilloscopes when bought second-hand, the vast majority of synthesised generators being very expensive even when they are no longer new. Standard (non-synthesised) signal generators have greater accuracy, a wider range of features and a better quality of construction when purchased second-hand but some are very large compared to their new rivals. Before buying it is advisable to check the following points:

- is it fully working in all modes and is the sine wave of adequate purity?
- is it accurately calibrated?
- does it have the modulation functions you require?

In the under £100 bracket there is a wide range of instruments — too many to cover fully here. However it should be possible to obtain fairly good but large AF and

FEATURE: Used Test Gear

RF generators for under £130. Examples include the Advance JI (AF) and the Marconi TF801D/8S (RF).

Voltmeters And Frequency Counters

The viability of secondhand units in these areas largely depends on their application. After all what's the advantage of having a 5½ digit second-hand voltmeter when you only require 3½ digit accuracy? You might as well buy a brand new 3½ digit voltmeter.

When buying a used digital voltmeter it is usually advisable to buy from a dealer which offers its own calibration service such as Electronic Brokers or Carston Electronics. Given the low price of DMMs a standard digital voltmeter can be a dubious buy, although the price of most of the older models reflects this: a Solartron A210 6 digit autoranging voltmeter can be bought for typically £30 from some dealers (uncalibrated).

Special-purpose voltmeters such as those with true-RMS or high speed sampling facilities may represent better value for money when bought second-hand but even here the benefit is probably not great. The availability of advanced LSI and VLSI chips has brought us a wide range of new DVMs and DMMs with advanced specifications at comparatively low cost and when the difference in size and weight is taken into account the new instruments will almost invariably represent better value.

Frequency counters on the whole represent better value on the second user market than DVMs but a careful evaluation of both the new and second-hand models available should be carried out before a decision is made. The older frequency counters can have

restrictive bandwidths if they are to be used for RF work, although some such as the Hewlett Packard 5245L (with additional plug-in facility) and the advance TC17 also have timer functions which can be very useful for pulse duration measurement, etc. It is in this sector that the second-hand models are perhaps most cost effective.

The cheapest new counter timer (200MHz) costs around £175 while a second-hand unit with perhaps a bandwidth of 50MHz can be obtained for around £60. For around £200 a recent vintage counter should be available incorporating a fairly substantial number of functions. A number of advantages are to be had by purchasing second-hand frequency counters, such as oven controlled timebases and a more diverse range of functions but a new frequency-only model with perhaps eight times the bandwidth may often be bought for little more.

Conclusion

In most cases second-hand equipment represents a feasible alternative to new equipment in 'light use' or amateur stations but there are certain exceptions to this which have been pointed out. Second-hand test equipment can be purchased from several suppliers, some of whom advertise in this and other publications. A large price difference can sometimes be observed between the various dealers for apparently identical pieces of equipment but this usually reflects the condition of the instrument and the services offered by the dealer such as guarantees, etc. In spite of this it is still worth looking around and checking out the prices, especially in the older equipment.

ETI

Xen-Electronics

I.C.'s	Fixed Voltage Regulators	22 Way	.18	100 μF 50V .19
4001UB	.12	24 Way	.20	1000 μF 10V .23
4011UB	.12	+5 1A	.30	220 μF 10V .06
4011	.12	+1.5A	.68	330 μF 16V .19
4017	.31	+12 1.5A	.30	470 μF 16V .25
4028	.29	+15 1A	.30	Turned Pin Axial Lead
4040	.38	+24 1A	.68	4.7 μF 63V .06
4053	.37	-5 1A	.39	8 Way 16 μF 25V .11
4066	.19	-12 1A	2.10	16 Way 32 μF 25V .18
4031	.12	-15 1A	.39	18 Way 40 μF 10V .22
Z80APU	1.85	-24 1A	.39	20 Way 40 μF 10V .31
Z80API	1.68	+5 0.1A	.28	22 Way 44 μF 10V .31
7217IP1	4.00	+8 0.1A	.28	24 Way 48 μF 10V .31
6402IP1	7.30	+12 0.1A	.28	5/7.5mm Pitch 3.3μF 400V .08
555	.41	+15 0.1A	.36	40 Way 80 μF 100V .80
558	.30	-5 0.1A	.30	Connectors 0 Type 0.022 μF 63V .08
741	.25	-12 0.1A	.30	0.047 μF 100V .08
LM380N	1.87	.51	.30	9 W Skt 4.7 μF 63V .08
TL074CP	.51	Transistors	.30	9 W Plug 0.1 μF 63V .08
SG3526N	3.69	BC107	.16	9 W Cover 0.15 μF 63V .17
SG3526J	4.92	BC108	.21	15 W Skt 0.33 μF 63V .33
SL486DP	2.20	BC109C	.19	15 W Plug 0.47 μF 63V .17
SL490DP	2.13	BC182	.05	15 W Cover 1.07 μF 63V .08
ML9260P	3.04	BC212	.05	25 W Skt 0.25 Watt 5% EACH 0.2
Diodes		BC546B	.04	25 W Plug 0.5 Watt 5% EACH 0.4
1N4001	.05	BC556A	.04	25W Cover 1.16 Watt 5% EACH 0.4
1N4003	.05	BD233	.42	PCB Mount 10 μF 100V .08
1N4005	.05	BFY51	.54	15 W Skt 1.02 GM472W (4.7kV) 1.95
1N4007	.06	BF259	.58	15 W Plug 0.39 Potentiometers PCB Mount
1N5401	.12	BSR50	.49	25 W Plug 2.15 Ceramic Top Adj 0.50
Zener Diodes		IRF520	1.61	Capacitors Radial 100.30
2V7 4W	.05	IRFB40	4.60	Lmdd 1k Ω .30
5V1 4W	.05	J112	.57	2.2 μF 50V .06
7V5 4W	.06	MTP8N10	1.44	2.2 μF 63V .11
9V1 4W	.06	TIP121	.34	4.7 μF 63V .06
10V 4W	.06	TIP126	.34	33 μF 16V .04
11V 4W	.05	TIP31C	.30	47 μF 10V .06
L.E.D.'s		TIP32C	.30	47 μF 25V .06 Project Kits RS232 to Centronics Converter
5mm Dia		2N2646	1.18	47 μF 35V .08
Red	.13	2N3055	.47	47 μF 63V .08 Kit only £18.40
Green	.12	I.C. Sockets Low	.47	47 μF 100V .17 280 Based Controller
Orange	.21	Cost	.10	10 μF 35V .06 Board, 4MHz
Yellow	.15	6 Way	.05	Kit Only £20.45
3mm Dia		8 Way	.07	22 μF 100V .21 Ultrasonic Tapemeasure
Red	.13	14 Way	.11	(Display Module Extra)
Green	.13	16 Way	.13	100 μF 16V .06 Kit Only £23.52
Orange	.21	18 Way	.15	100 μF 25V .07 Four Digit LCD Module for above Kit Only £14.30
Yellow	.13	20 Way	.16	100 μF 35V .08

WHO SAYS WE NEVER GIVE ANYTHING AWAY?

An offer which can only last until stocks are exhausted. The Electronic Industry Telephone Code Book and Diary 1988. Yours absolutely FREE when you next place an order worth £25 or more. Alternatively you can order the diary on its own at a price of £7.25, zero rated, ORDER NOW AND DON'T BE CAUGHT WITHOUT IT!

MAIL OR TELEPHONE ORDERS ONLY PLEASE TO:

Samuel Whites Estate, Bridge Road, Cowes, Isle of Wight, PO31 7LP

Please add £1 for 1st class post and packaging and 15% VAT to total. Stock listing available soon, please send SAE to be put on the mail list.

OMNI ELECTRONICS

for a comprehensive range of components aimed at the enthusiast:

1N4148	4p	1.5A 100V bridge	36p
1N4001	5p	5mm red leds	13p
LM741	25p	5mm green leds	14p
7805	50p	400mW zeners	10p
0A90/0A91	13p	1.3W zeners	17p
Skeleton presets	11p	Red/black phono plugs	14p
UM 1286 modulator	7.95	Quality panel meters	5.98
98mm cable ties	2.00/100	Velleman kits/Babani books	

The above is a sample of our range and includes VAT. P&P 60p. Send for catalogue 20p + 18p or 13p stamp. Shop open: Monday-Friday 9am-6pm, Saturday 9am-5pm.

174 Dalkeith Road
EDINBURGH EH16 5DX
031-667 2611

BINDERS

FOR YOUR VALUABLE COLLECTION
OF ELECTRONICS TODAY
INTERNATIONAL MAGAZINES

• SMART • EASY TO USE • TOP QUALITY
To ASP Readers Services, PO Box 35,
Wolsey House, Wolsey Road, Hemel
Hempstead, Herts HP2 4SS (0442-41221)



Please supply ... Electronics Today International
Binders £5.95 inc. P&P

Total £ (Please make cheques payable to ASP Ltd.)

Years Required — 198..... 198..... 198..... 198.....

Name Address

Please allow 21 days for delivery



This copy of ETI is your magazine —
in more ways than one. You bought
it (and thank you for that!) but it is
ETI readers like you for that! but it is
most of the contents who provide
some ETI pages but we still have a
constant need for good contributors fill
projects and circuits. We'll even pay
you for them!

If, like most ETI readers, you
build electronic devices of your own,
design we want to hear from you.
You may have just finished the hi-fi
amplifier, or a microprocessor-
controlled Selotape dispenser, or
just a great gadget to impress your
friends.

Whatever your project, if it will
appeal to other readers it can earn
you fame and fortune in ETI into
the bargain.

1. C7 1n8 R12 3k3 C9 220n
2. CB 22n
3. C12
4. If you don't
idea to a working
circuits and im-
for ETI proj-
pages. Fr
wa

5. C23 4u7 16V 16s
6. +5V
7. IC6a
8. 15
9. R37 100k
10. IC6b
11. 1V4 10K ANUAL
12. PR3 47K
13. C28 100n

If you don't want to take your idea to a working prototype, novel circuits and improvements to existing ETI projects are always welcome for the ever-popular Tech Tips pages.

From experts in their fields we want features. ETI has a reputation for presenting interesting, informative and wide-ranging features. If you know something the rest of us don't, tell us all through the rest of ETI. Whatever you can contribute to ETI we want to hear from you soon. Write in with a brief description of your idea. Include a circuit diagram or for projects and a brief synopsis of features.

Write to:
The Editor
Electronics Today International,
1 Golden Square,
London, W1R 3AB.

TURBO-WASHER OFFER

FROM SPREADERS SERVICES

**Only
£23.95**



★ NO ELECTRICITY REQUIRED

**★HOSE CONNECTOR & 32oz SOFT SUDS
SUPPLIED**

Connect Turbo Wash to a garden hose and use its unique telescopic jet with 3 interchangeable nozzles for fine spray, power jet and angle spray to cut through the dirt using controlled detergent dispenser facility and clean water rinse in one continuous operation. Its super dirt cutting blade of water cleans cars, caravans, patios, engines, 'too high to reach windows', lawnmowers, gutters, etc. With no parts to rust the Turbo-Wash will last for years and years.

PSST!

Turbo Wash makes a great Christmas gift.

A.S.P. Readers Service, 9, Hall Road,
Maylands Wood Estate, Hemel
Hempstead, Herts. HP2 7BH tel: 0442
41221

To A.S.P. Readers Services, 9, Hall Road, Maylands Wood Estate, Hemel Hempstead
Herts HP2 7BH Please supply Turbo Washers + £23.95
I enclose my cheque/P.O. payable to A.S.P. Ltd., Please debit my Access/Barclaycard
Ac No.

A/C. NO.	<input type="text"/>
----------	----------------------

Signature _____

Name
.....

* * * * *

• • • • • • • • •

Please allow 28

Please allow 28 days for delivery. This offer is available to readers in U.K. only. Overseas enquiries in writing to the above address.

CIRCUIT THEORY

Paul Chappell is still struggling to point his phasors in the right direction.

Continuing with the theme of phasor diagrams, we'll plunge straight in this month with a look at the circuit of Fig.1. Last month we drew phasor diagrams for two components in series but this time we've got parallel connections to consider too. Let's just continue with the same common sense approach and see how far it will take us.

From last month we can immediately draw our phasor diagrams for the two individual branches of the network. These are shown in Figs 2a and b. Not having any component values we don't know the lengths and angles but we do know the general form of the diagrams.

In Fig. 2a, for example, the voltage across the capacitor must lag the voltage across the resistor by 90° because the current through both components is the same. The phasor representing the voltage across the two components will be the sum of the other two voltage phasors.

Similar conditions hold for the resistor and inductor branch of the circuit except that this time the voltage across the inductor leads the voltage across the resistor.

To combine the two separate diagrams into a single diagram representing the whole circuit, we first have to determine the relationship between the phases of the two different branches. Following from last month I have used the current phasor as a reference for each branch and drawn it in the 'cosine' direction. If I immediately combine the two diagrams into one, I will be making the assumption that the currents in the two branches are in phase with each other, which is not necessarily the case.

One thing we do know is that the voltage across the resistor and capacitor must be exactly the same as the voltage across the resistor and inductor, so the phasors representing this voltage on the two diagrams must be one and the same. We can match up the V_{in} phasors by rotating one diagram or the other until they come into line.

Since V_{in} is the input voltage, it would be nice to have it pointing in the reference direction so that all the other voltages can be compared with it. This is done in Figs. 2c,d and the two diagrams are combined in Fig. 2e.

We are still missing a phasor for the total current. This is just the sum of the currents in the two branches, so can easily be added. Note that the fact that it leads the input voltage in Fig. 2e is just an accidental consequence of the way the original diagrams were drawn. When the diagram is scaled to suit real component values it could go either way. We don't know yet.

OK, let's put it to the test. In Fig. 3 I've put in some values for the components. They are not very realistic values but don't worry. In a while I'll show you how to use totally ridiculous values (for real components) and still get the right answers!

Using Fig. 2e as a model, we'll see if we can deduce enough information to draw up a complete phasor diagram for Fig. 3. We'll begin with the easiest phasor of all and draw V_{in} in the cosine direction.

Now we're stuck. All the other phasors seem to involve knowing the value of i_1 or i_2 and we don't know either! Is there any way we can work them out? Looking back at Fig. 2c for a moment, we know that the V_{in} phasor is

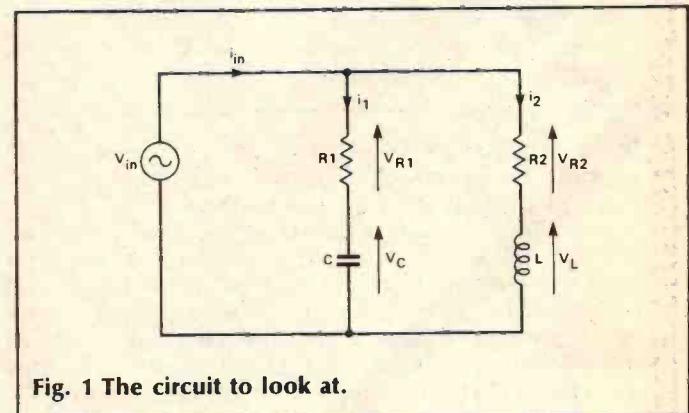


Fig. 1 The circuit to look at.

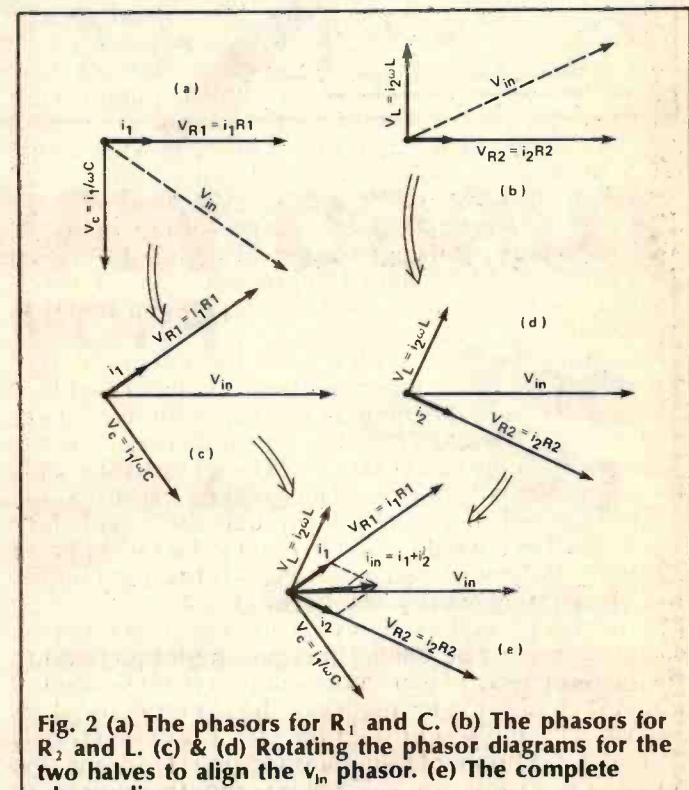


Fig. 2 (a) The phasors for R_1 and C . (b) The phasors for R_2 and L . (c) & (d) Rotating the phasor diagrams for the two halves to align the V_{in} phasor. (e) The complete phasor diagram.

the sum of the other two phasors and can be obtained by placing them nose to tail (Fig. 4a). All we need to calculate the value of i_1 is to apply Pythagoras' theorem to the triangle (since the phasors for V_c and V_{R1} are at right angles).

$$i_1^2 = (2i_1)^2 + \left(\frac{V_{in}}{100}\right)^2 = i_1^2(4 + \frac{1}{100})$$

$$i_1^2 = 2.44$$

$$i_1 = 1.56$$

Now that we have the value of i_1 we can calculate $V_{R1} = 2i_1 = 3.12V$ and $V_c = i_1/100 = 3.9V$. The angles can be

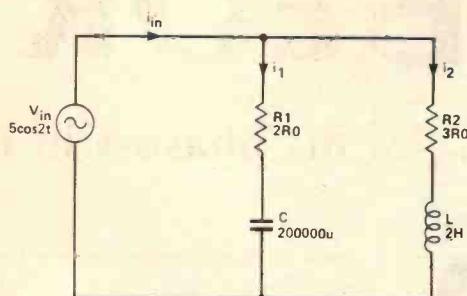


Fig. 3 A circuit with real values.

obtained graphically by plotting the two phasors and using a protractor or simply by making use of the \sin^{-1} and \cos^{-1} buttons on your calculator!

A right-angled triangle based on Fig. 2d will allow i_2 , V_L and V_{R2} to be calculated in a similar manner. The current i_{in} is derived from the triangle formed by i_1 and i_2 as shown in Fig. 4b. Since the triangle does not have a right angle, you'll have to use the 'cosine formula' to calculate the value of i_{in} . Don't worry if your trigonometry isn't up to the job — you can always draw the triangle and measure the side — or wait until next month when we do it the easy way!

The complete phasor diagram showing every single voltage and current in the circuit is shown in Fig. 4c. It shows that we can certainly find out how a circuit responds to a sine wave by using a little common sense and doing a few calculations but even for a circuit this size the simple idea of phasors is being spoiled by the amount of effort involved in working it all out.

What we really need is a procedure that will make things even clearer and can be used with complicated circuits where drawing phasor diagrams from first principles would be almost impossible. That's for next month. For the moment, we haven't quite finished with Fig. 4c yet.

Suppose we had started with the circuit of Fig. 5 instead of Fig. 3. The input frequency is increased by a factor of 1000 and the inductor and capacitor have values reduced by a factor of 1000. The impedance of the inductor will now be $2 \times 1000 \times 2 \div 1000 = 4$. Exactly the same as before! Similarly the impedance of the capacitor would be unchanged. If you check through the calculations you'll see that it would result in exactly the same phasor diagram. The only thing that changes is that the phasors are all spinning round 1000 times as fast.

This result applies to any circuit and to any scaling factor (it needn't be 1000). Note that the frequency and all the inductor and capacitors values must be scaled. If you just change the frequency or the component values individually, the response of the circuit will be entirely different. Component values around one Henry and one Farad are easiest for calculation and the notion of frequency scaling allows one circuit to speak for a whole class of circuits.

For published data the usual choice is to make $\omega=1$, giving 'normalised' component values. To calculate the component values needed for a real circuit, all you do is to divide the published values by the angular frequency you want the circuit to work at!

Have a look at the relationship of the currents in Fig. 1 to the input voltage. The currents in the two individual branches of the network are considerably different in phase from the input voltage but the overall current is only 15° out of phase so the network as a whole looks 'almost' resistive. Is it possible to choose component values to make it appear exactly resistive to the input? If we imagine that R_2 is the resistance of a loudspeaker

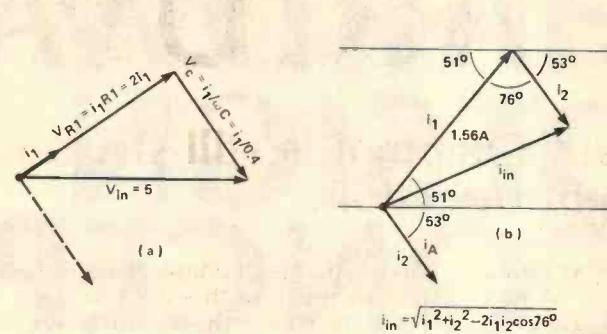


Fig. 4 (a) The phasors for R_1 and C . (b) The phasors for R_2 and L . (c) The complete phasor diagram.

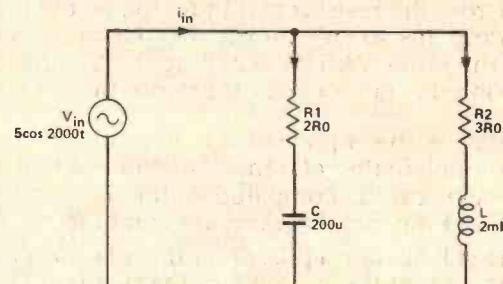


Fig. 5 Scaled values with the same phasor diagram.

coil and L is its inductance, then to a first approximation we have just drawn the phasor diagram for an amplifier driving a loudspeaker and Zobel network. The component values are not quite right but the principle is just the same. The question of just how resistive we can make the load look to the amplifier is quite important.

With circuits working at rather higher frequencies a similar question arises: how can unwanted circuit elements be 'tuned out' or 'neutralised'? If it can be done at all, will it work for all frequencies? If not, how close can we get to a pure resistance over the frequency range of interest? Our common sense approach doesn't seem to be making the answers very clear, so next month we'll start to refine it a little.

HARDWARE DESIGN CONCEPTS

In the last in this series Mike Barwise looks at the integrated continuous and switched capacitor filters.

Filters figure prominently in analogue signal processing. Their uses range from the simple elimination of spurious signals (such as the removal of mains hum in audio amplifiers) to the separation of complex signals into their basic components in instruments like spectrum analysers.

The two fundamental types of filters are passive and active. Passive filters use series/parallel networks of inductances and capacitors, taking advantage of the reciprocal impedance characteristics of these devices with frequency. The problem with the simplest passive filters is the poor 'rolloff' characteristic — the graph of attenuation versus frequency (Fig.1). In order to improve this characteristic, additional elements are added to the network (Fig.2) but the calculation of component values gets increasingly tricky as more 'poles' (series or parallel elements) are added.

The classical solution to this problem is the use of active filters. These again use the impedance versus frequency ($Z:f$) characteristics of capacitors and inductors (or more often, resistors) as the control but in this case they are included in the feedback loop of an operational amplifier (Fig.3).

Such filters are very adaptable, capable of very high orders of rolloff and horribly difficult to design. Another point worthy of mention is the filter 'passband characteristic'. Our simplest passive filter had a rolloff but no flat passband, in that there was a continuous relationship between attenuation and frequency (3dB per octave) throughout its working range.

Once you have a sharp cutoff characteristic (Fig.4) it becomes important how flat the response is in the passband. Various different tradeoffs between cutoff and passband flatness have been adopted as classic models:

BUTTERWORTH maximal flatness in passband, moderate rolloff

CHEBYSHEV maximal rolloff, ripple in passband

To design an active filter with a sharp cutoff at a predictable frequency together with a desired passband flatness characteristic, the maths is quite horrific. The good news is that there is a short cut.

Several semiconductor manufacturers have produced ready made filter building blocks which greatly simplify the design of good filters. A couple of these devices have additional advantages which allow otherwise ferocious problems to be solved quite easily as well, so let's look at a selection.

Integrated Filter Types

There are two device series that I shall discuss, working on different principles. The first is a range of fairly conventional op-amp/R/C filters by Datel. These are 'continuous' signal filters which work on the same

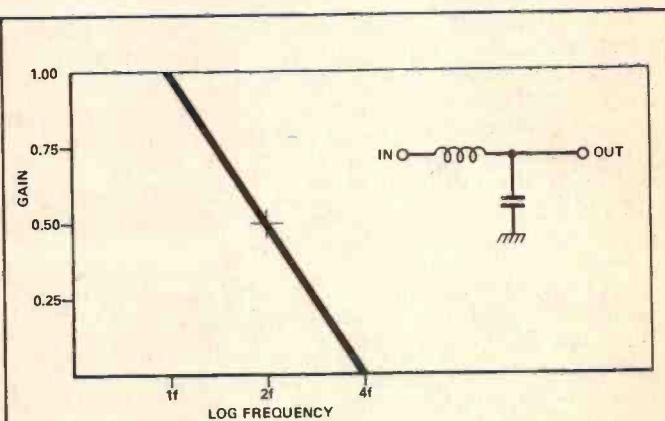


Fig. 1 Rolloff with a simple two pole filter.

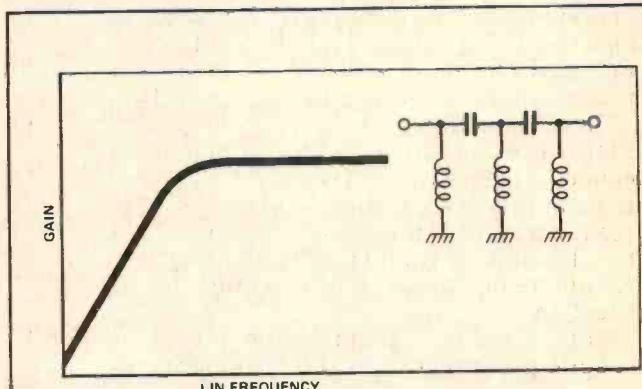


Fig. 2 Better rolloff with a five pole filter.

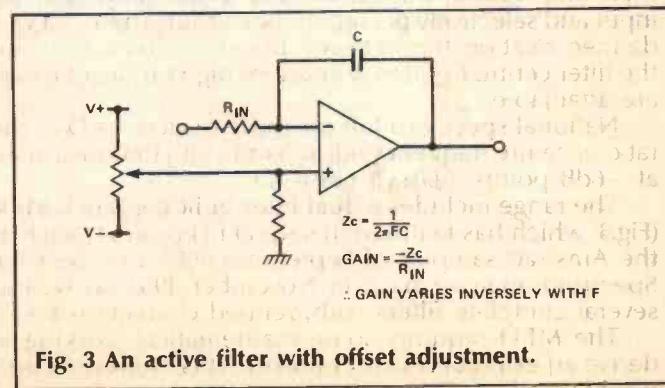


Fig. 3 An active filter with offset adjustment.

principle as the discrete component active filter.

The second type is a range of 'switched capacitor' filters by National Semiconductor. These work on an entirely different principle. They sample the incoming signal at a predetermined rate and pass on to the output only the wanted components. This means that if you look at the filter output waveform on a scope you will see that it consists of many small steps instead of a continuous curve. Occasionally this may cause problems but usually it can be tolerated as a tradeoff against some very powerful advantages which result from this approach.

Datel Tuneable Filters

The Datel range is built around a basic hybrid filter series designated FLJ-UR (Fig.5). These are small single-in-line packages containing various alternative filters. High, low and bandpass are all available in Butterworth characteristic and low and highpass are also available in Chebyshev. There are two frequency bands available: HF 400Hz-5/10/20KHz, and LF 40Hz-1.6KHz. The required frequency (F_c) is set by the addition of up to four external resistors — the only external components for normal use. The response of the LF filters may be extended downwards by the addition of suitable capacitors, when it should be possible to achieve F_c as low as 0.1Hz at the expense of slightly increased noise. The FLJ-UR filters have a fixed rolloff of typically 24dB/octave.

A really crafty addition is the FLJ-ACR1, 2 range of *Logic controlled resistor networks* (Fig.6). These are quite costly, but allow BCD digital control of the filter F_c to within 1% when used with the FLJ-UR filters. Each resistor network contributes one BCD digit of control but they can be cascaded for more resolution.

A spinoff from these basic components is the Datel FLJ-D series of universal programmable filters (Fig.7). These are over-width DIL hybrids containing all components barring a couple of resistors and capacitors which define the gain and rolloff the filter. Low, high and bandpass outputs are available simultaneously from the package and F_c is set by a three-digit BCD input word.

These Datel filters have very good general analogue performance and can be highly recommended anywhere you need a range-switched or fixed-frequency filter. Their one main drawback is their limited F_c setability which is really a feature of the resistor networks rather than the filters. If someone would produce a quad gang precision potentiometer, these filters would be useable to perfection.

More settable, though by no means so good in analogue performance, is the National range.

National Switched Capacitor Filters

The National MF series of filters and filter building blocks are 'switched capacitor' or 'sampling' filters. The incoming waveform is sampled at a rate set by a clock input and selectively passed to the output. There is a well defined relationship between the clock frequency and the filter centre frequency and very high orders of rolloff are attainable.

National specify rolloff for these devices as Q — the ratio of centre frequency (f_0) to bandwidth (bw) measured at -6dB points: $(f_0/bw(-6dB))=Q$.

The range includes a dual filter building block MF10 (Fig.8) which has featured in several ETI projects such as the Amstrad sampler of September 1987 and even the Spectrum analyser back in November 1982, as well as several complete filters with defined characteristics.

The MF10 requires some mathematical working to derive an external resistor network. It is, however a very flexible device, allowing low, high, band, notch and all-

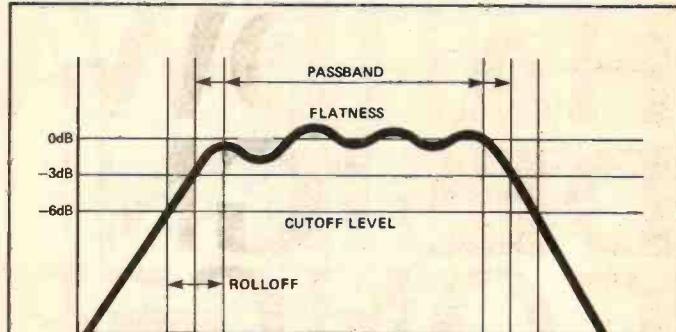


Fig. 4 Passband flatness of a (bad) high order bandpass filter.

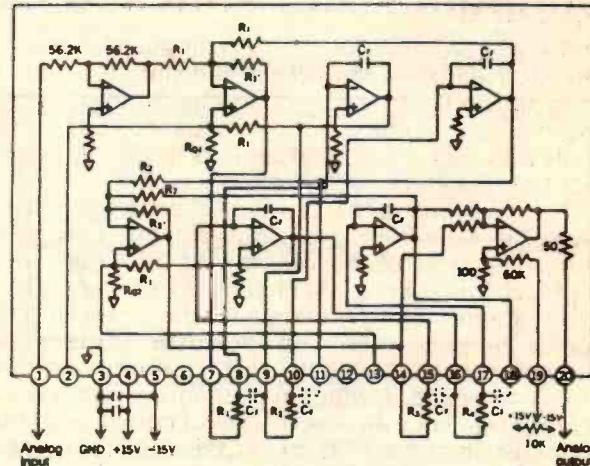


Fig. 5 The FLJ-UR hybrid filter.

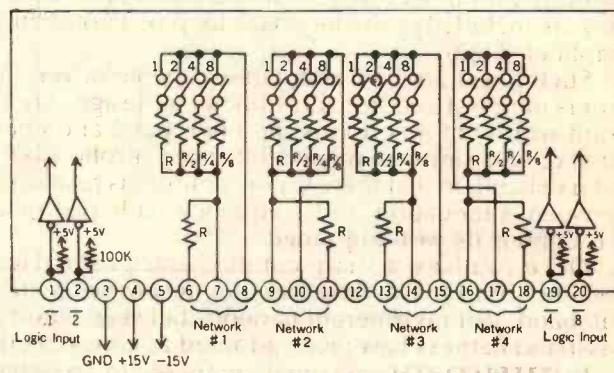


Fig. 6 FLJ-ACR1 logic controlled resistor network.

pass filters of defined Q to be created by variations in the R network.

Of the complete filters, worthy of mention are the MF4 Butterworth low-pass and the most interesting of all, the new MF8 fourth order bandpass filter.

The MF8 (Fig.9) contains two identical bandpass filters which may be cascaded. They are both driven by a common clock and their Q is adjustable by a common 5-bit digital input word. The nominal centre frequency is settable to either clock/50 or clock/100 within a centre frequency range of 0.1Hz to 20KHz (at clock/50) with a maximum clock of 1MHz. The actual f_0 deviates slightly from this nominal according to the Q setting (about 10% worst case) but this is well documented and should pose no problems.

FEATURE: Hardware Design

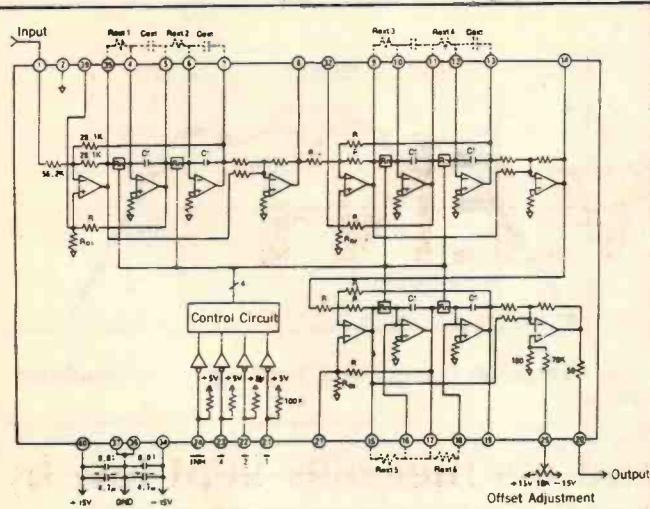


Fig. 7 FLJ-D universal programmable filter.

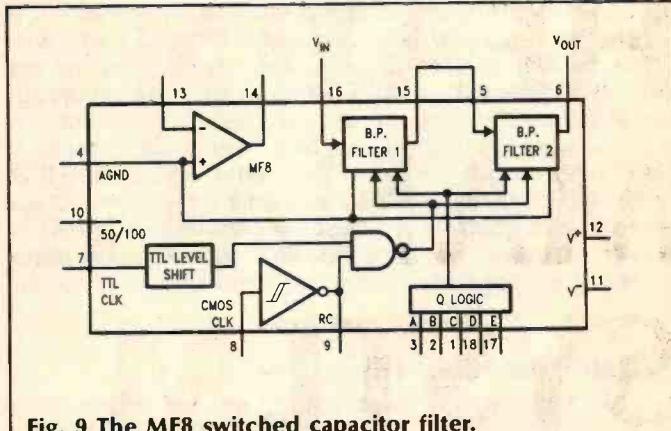


Fig. 9 The MF8 switched capacitor filter.

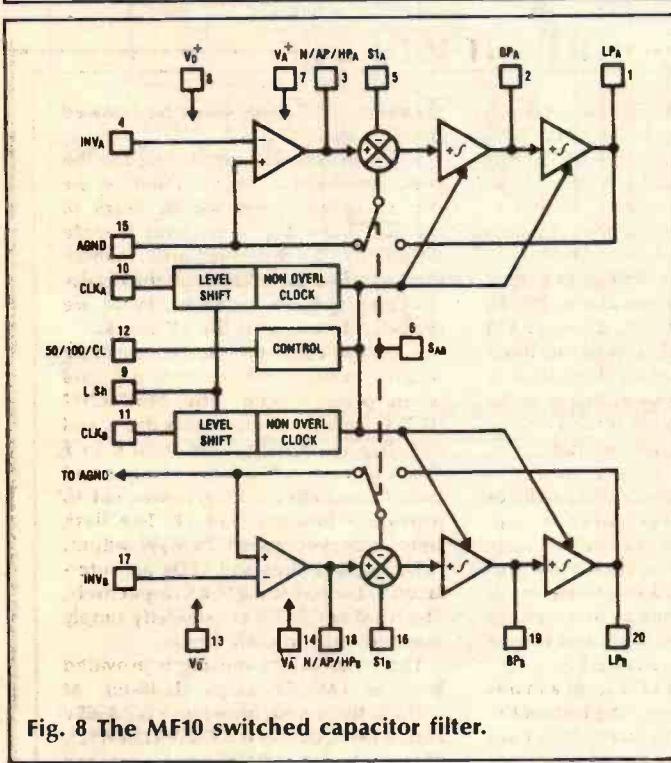


Fig. 8 The MF10 switched capacitor filter.

In conventional fixed frequency applications, well defined passband characteristics can be attained by the use of external feedback resistors in conjunction with an uncommitted op-amp also included in the chip (Fig.10). However, where a less defined passband characteristic can be tolerated, particularly where a very narrow passband is required, the MF8 can be used with no external components to create a single chip bandpass filter capable of variable Q in the range of at least 0.5 (very slow rolloff) to 90 (too much for almost anyone!).

Note that in this configuration there is no *flat passband*. The Q programming simply defines the gradient of the rolloff about f₀. Add to the Q control the direct control of the centre frequency by external adjustment of clock rate and you have a very valuable *tracking bandpass filter* which is entirely digitally controlled.

This highly controllable filter is a valuable data logger front end, where it can perform many jobs from programmable anti-aliasing to simple spectrum analysis of continuous waveforms or, for example, be used at high Q to indicate transient presence of a specified frequency component in a complex waveform.

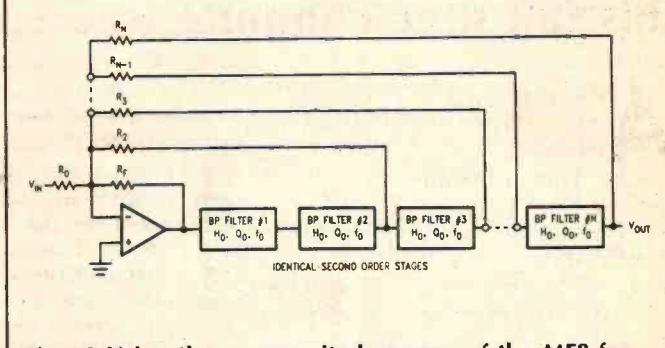


Fig. 10 Using the uncommitted op-amp of the MF8 for well defined passband characteristics.

Being a sampling device, the question of 'aliasing' is sure to be raised in relation to the MF filter itself. The basis of aliasing is the concept that it is impossible to recover by sampling techniques a waveform whose period is equal to or greater than half the sampling rate. Under these conditions, a bogus frequency component is observed with a frequency greater than half the sampling rate by the same amount as the real component is below it. This looks similar to the upper and lower 'sidebands' in radio communications.

In the MF filter range, the maximal bandwidth of the analogue channel is much less than half the clock (sampling) rate under most conditions, so aliasing should not be a problem. In fact the MF10 could form the basis of an ideal digitiser anti-aliasing filter, in low-pass configuration with the f₀ clock driven by the same clock as the ADC conversion trigger.

The final point of caution with these switched capacitor filters is their analogue performance (drift over temperature, absolute device variation and so on). They are potentially not so precise as a continuous filter and they can be quite noisy. There is inevitable clock breakthrough, although this is usually outside the band of interest and their analogue channel noise is likely to be worse than, for example, the Datel continuous filters.

Really, you have to make a choice between the trade-offs. For a fixed filter, I would go for the Datel range every time (subject to cost) but where automatic tracking capability is required, any alternative to the switched capacitor filter with clock control is a really tricky design problem.

I hope these comments have got your fingers itching to get their grip on these devices. Further information on the Datel range can be obtained from Datel (UK). Tel: (0256) 469085. Prices range from the £24 mark. The National MF series are available from many distributors, and the MF8 should be joining the others shortly at a list price around £5 or so.

HEATING MANAGEMENT SYSTEM

Harry Bloomfield is kept warm and his fuel bills kept low by this full spec computerised central heating controller.

A central heating system is nowadays considered an essential for any large flat or house. This controller replaces the usual standard, electro-mechanical clocks and thermostats with a single, versatile and reliable microprocessor based control. This controller is not only an advance over the electro-mechanical systems but also over most commercial electronic add-on controllers.

The main features of the Heating Management System are:

- many fold increase in system reliability
- complex and versatile control programs can be used without reliability suffering
- control of temperature and timing is to a far greater accuracy for greater comfort and economy

The management system offers independent control of two central heating zones — usually upstairs and downstairs — and the water heating.

The temperature of the zones and water can be programmed to vary as the day progresses as well as providing the more normal on/off functions.

Options

With some heating systems it may not be practical to split the home into two heating zones. In this case one relay along with its associated suppression components and temperature sensor can be omitted.

The PCB is designed for a 2732 EPROM (IC5). As the software occupies just 2K a 2716 can be fitted if the track to pin 21 is cut and the pin connected to +5V with an insulated wire link.

The PCB is also designed for a

HOW IT WORKS

The heart of the controller circuit (Fig.1) is the microprocessor. In this case I have used the old faithful 8085 (IC1). This derives its clock signal from the versatile but underused HD146818P real time clock chip (IC2). This provides registers for seconds, minutes, hours, day, month, and year and provides 50 bytes of battery backed RAM and various alarm signals.

Only the minutes, hours, day and RAM are used in this application. The three alarm registers are set up then used as check bytes after a power cut to make sure the clock still contains valid data — that the battery has not run flat.

The clock chip also provides a 1.048576MHz clock (the crystal oscillator clock divided by four) which is supplied to the processor and divided again by two to 0.524288MHz. Such a low processing speed is used to ensure maximum immunity to noise, to create as little as possible noise itself and to give the unit a long and reliable life.

R1,2, C1,2, D6,7 and Q1 form a mains failure detection circuit. The instant the mains supply is lost the base of Q1 goes low and this in turn pulls the processor Reset line low. This stops the processor and switches the clock chip RAM (IC2) to battery backup.

Data corruption of the RAM on switch over to battery power is a common problem with this type of chip. However, this simple mains failure circuit worked perfectly without data corruption with 10,000 artificial mains failures during testing.

The 5V regulator (IC15) has a forward biased diode on its ground terminal to raise the output voltage to about 5.6V. This enables the main supply rail to be separated from the battery rail by diodes D8,9 to provide a charging current for the battery (B1) through R28. However, this

means the regulator must be isolated from its heatsink.

IC3 provides demultiplexing for the processor address bus. Each item on the bus occupies a separate 8K block of memory (see Fig.2) enabling simple decoding of the three high order address lines only by IC4. So although the display occupies only six locations, these are repeated throughout the 8K block.

IC7 provides the time and temperature display during both normal use and when programming. The MM74C917 (IC7) is capable of driving six digits and can display any character from 0 to F (hex). It can also blank the displays and this is used after a long power cut to provide a flashing FFFF FF. The flash signal is derived from IC2's SQW output.

The keyswitches and LEDs are interfaced to the bus using IC8,9 respectively. The RAM and ROM are similarly simply mapped each into 8K blocks.

The temperature sensing is provided by four LM335Z chips (IC16-19). At -27.5°C the output from these is 2.4565V and at 100°C output is 3.7315V (10mV/°C). This works out at 0.5°C per binary step from the ADC chip (IC11) — 256 steps from -27.5 to 100°C.


An accurate and temperature stable reference for the ADC chip is provided by Q8 operating as a constant current source supplying the precision voltage reference, IC20. This is divided by resistor chain R11,RV1,RV12,RV2 and buffered by IC12 to provide the upper and lower reference voltages at IC11.

R29 and C6 decouple IC11 and R7-10, C7-10 provide crude input filtering. Additional smoothing is provided by the software. An average value for each of the four channels is obtained from 256 separate ADC readings.


6116 battery backable RAM chip. Battery backing of the RAM is only necessary if optimising software is to be used (see below) and so a cheaper 4116 RAM can

be used instead if the track to pin 24 is cut and the pin connected to the 5V rail.

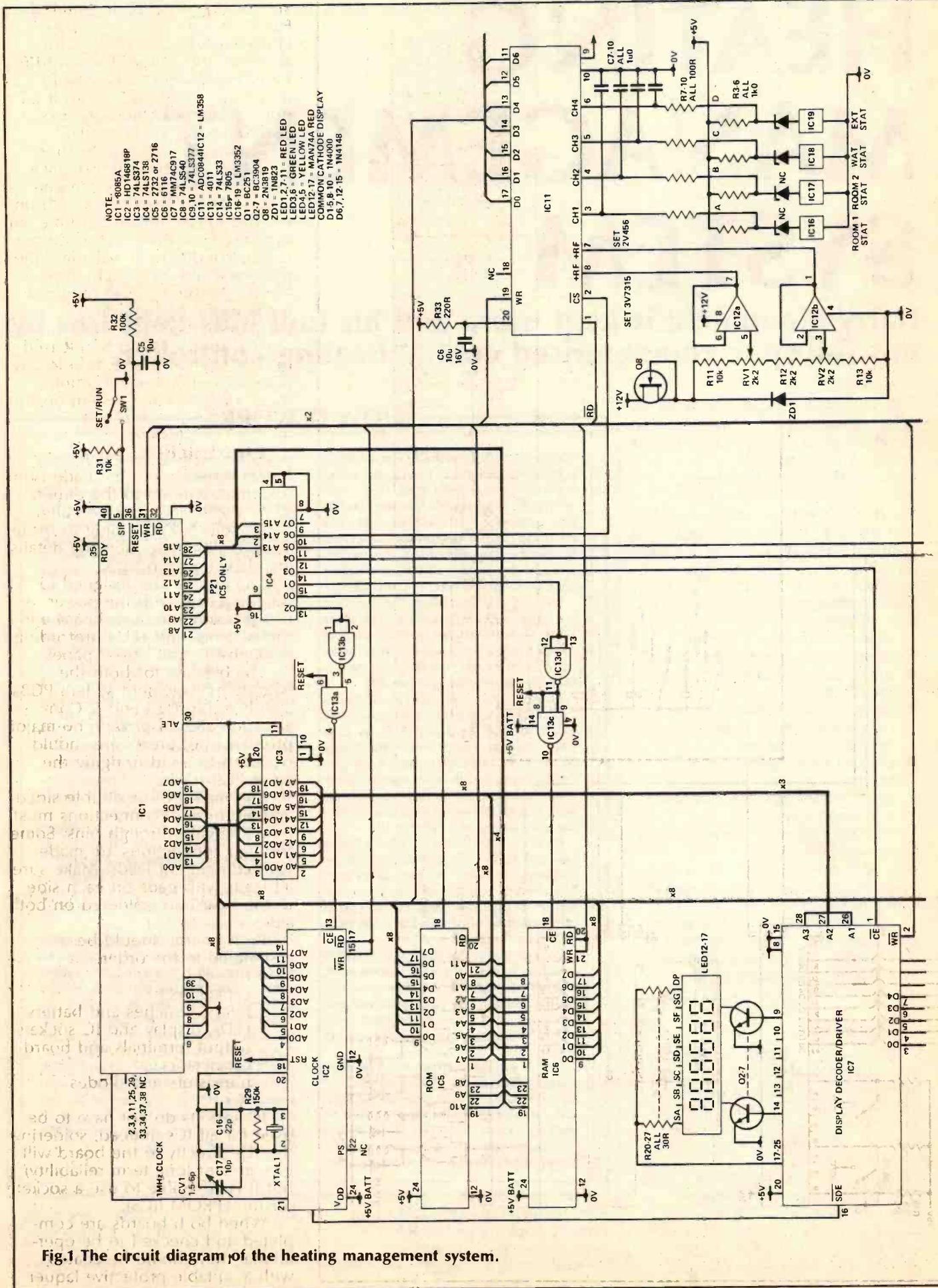Four sensors are provided for. The external sensor is optional



PROJECT: Heating Management

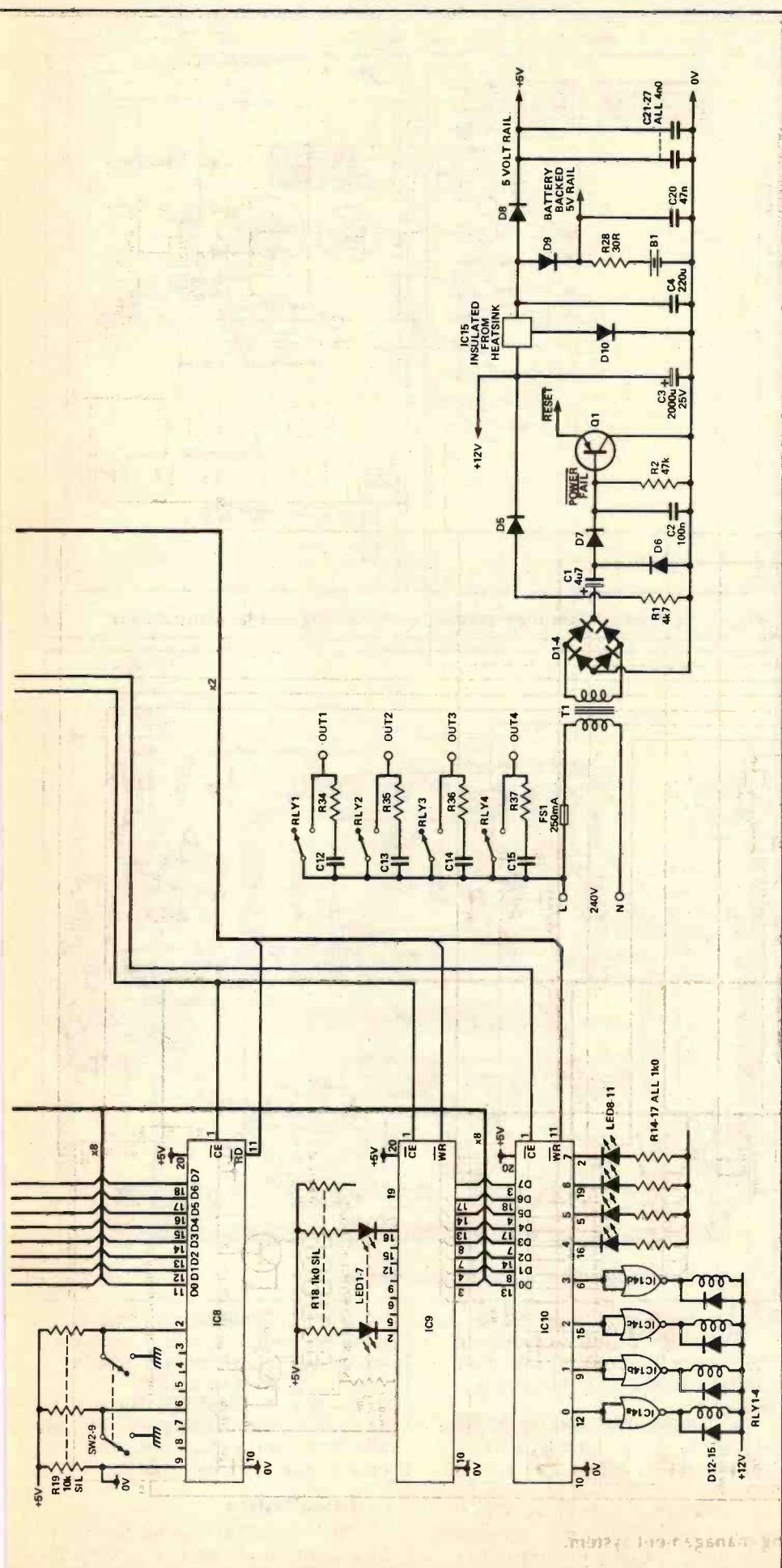

and can be installed if required. However, with the larger size EPROM to contain some extra software, the battery backed 6116 RAM and the external sensor mounted out of the sun on a north facing wall, an optimised controller may be created.

This would make a decision based on previous performance and inside and outside temperatures. Rather than just switch on the heating at the allotted time, an optimised controller uses the prevailing conditions to calculate the time required for switch-on to bring the house to the required temperature by the time programmed.

The author would be pleased to hear from and give help to any reader wishing to try to implement an optimising system on this controller.

Construction

The case should be made from folded aluminium to the dimensions shown in Fig.3 or an alternative selected according to these sizes. Drilling and labelling details are also shown in Fig.3.

The boards are designed to plug together, with the power board below the main board and the switches and LEDs protruding through the unit's front panel.

The overlays for both the heating management system PCBs are shown in Fig.4 and 5. Construction should provide no major problems but great care should be taken to avoid bridging the close PCB tracks.

The main PCB is double sided and all through connections must be made with through pins. Some through connections are made with component leads. Make sure all leads with pads on each side of the board are soldered on both sides.

Both boards should be assembled in the order:

- resistors
- capacitors
- relays, switches and battery
- LEDs, display and IC sockets
- output terminals and board connectors
- transistors and diodes
- ICs

IC sockets do not have to be used for all ICs (indeed, soldering the ICs directly to the board will give greater long term reliability) but it is advisable to use a socket for the EPROM (IC5).

When both boards are completed and checked to be operational they should be coated with a suitable protective lacquer

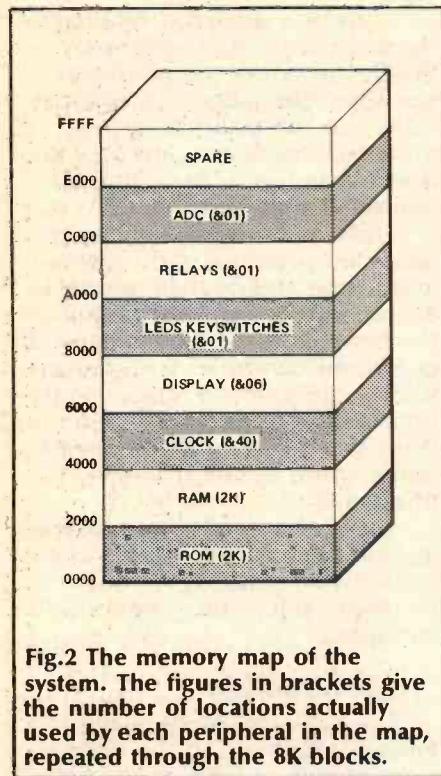


Fig.2 The memory map of the system. The figures in brackets give the number of locations actually used by each peripheral in the map, repeated through the 8K blocks.

to prevent moisture attacking the tracks and to add extra insulation around the main tracks.

The EPROM (IC5) should be programmed with the software given in Listing 1. Ready programmed EPROMs are available from the author (see Buylines).

Testing And Calibration

Connect a temporary mains supply to the power board alone. The relays should click in and the 5V supply rail, 5V battery rail and the 12V relay rail should be checked with a multimeter. Switch off.

H2 Connect two temperature sensors between the *Rm1* input and the screen terminals and between the *Wat* input and screen. The probes themselves should be well insulated and waterproofed with heat shrink sleaving or epoxy resin.

Connect the main board to the power board, switch on again and the display should show a flashing FFFF FF. This confirms that most of the circuitry is working.

Press SET/RUN then HOUR. The display should show 00.00 1d. Press SET/RUN (the display should show 00.00 10) and then ROOM TEMP. The display will now display the temperature of the *Rm1* probe.

Place this in iced water and adjust RV2 so the display shows 00.00.

Now press the WATER TEMP button and with the second probe in boiling distilled water adjust

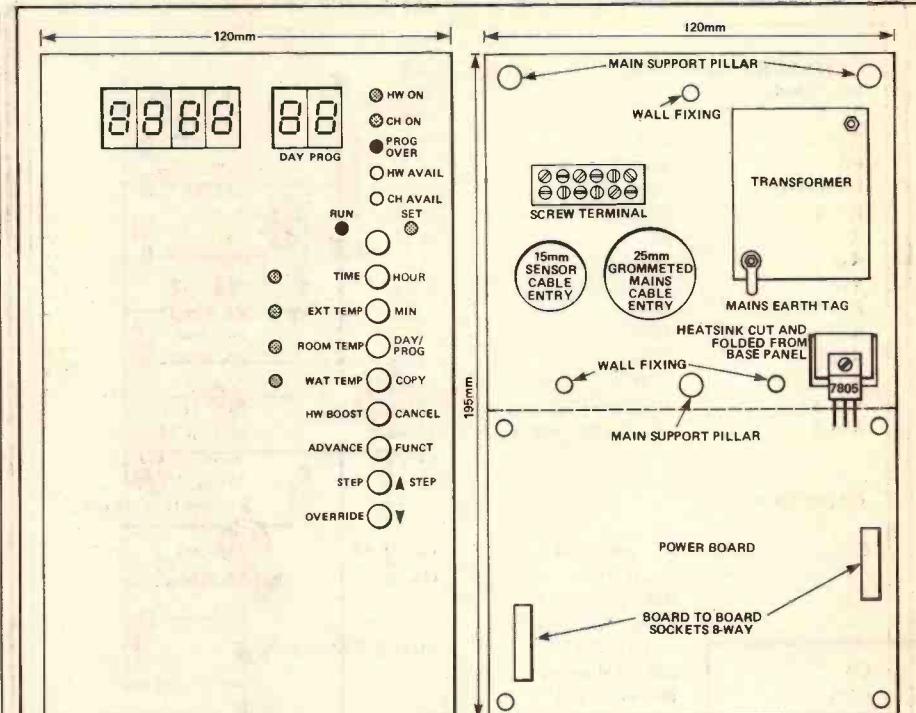


Fig.3 Case construction measurements and drilling and labelling details.

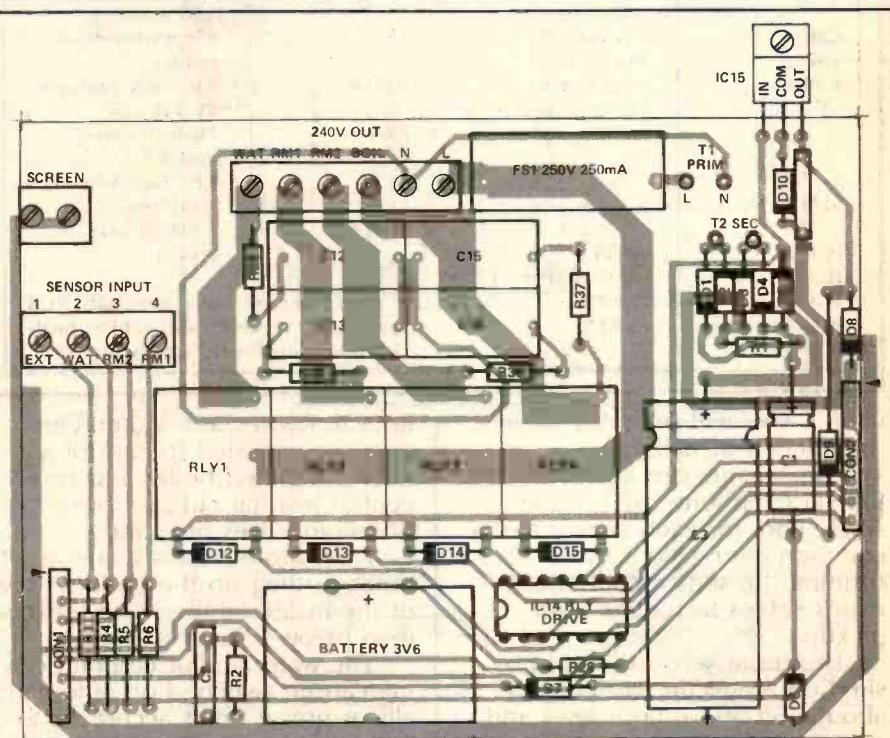


Fig.4 The component overlay of the power board.

RV1 so the display reads 99.50.

RV1 and RV2 interact and so the process should be repeated until no further adjustment is required.

An alternative method of calibration is to use an accurate multimeter to adjust RV1 for a reading of 3.7315V at pin 7 of IC12. Adjust RV2 for 2.4565V at IC12 pin 1. This is much quicker (and less messy!) but does require an accurate meter.

The final calibration required is of the system clock. If an accurate frequency meter is available adjust VC1 to give a clock frequency of 1.048576MHz at pin 21 of IC2. Alternatively VC1 can be adjusted over a few weeks to correct the real time clock.

Installation

The controller should be fixed in a position in the house suitable for both convenient use and tidy

PROJECT: Heating Management

PARTS LIST

RESISTORS (all $\frac{1}{8}$W, 5% unless specified)		IC6	6116
R1		IC7	MM74C917
R2		IC8	74LS540
R3-6,14-17		IC9,10	74LS377
R7-10		IC11	ADC0844
R11,13,31		IC12	LM358
R18		IC13	4011
R19		IC14	74LS33
R20-28,38,39		IC15	7805
R29		IC16-19	LM335Z
R32		Q1	BC251
R33		Q2-7	BC3904
R34-37		Q8	2N3819
RV1,2		ZD1	1N823
		LED1,2,7-11	Red LED
		LED3,6	Green LED
		LED4,5	Yellow LED
		LED12-17	MAN74A red common cathode display
			1N4000
			1N4148
CAPACITORS			
C1	4 μ F 16V axial electrolytic	D1-5,8-10	
C2	100n polyester	D6,7,12-15	
C3	2000 μ 25V axial electrolytic		
C4	220 μ polyester		
C5,6	10 μ 16V axial electrolytic		
C7-10	10 μ 16V tantalum		
C12-15	100n 250VAC suppression		
C16	22p ceramic	B1	3v6 100mA NiCd
C17	10p ceramic	CON1,2	8 way PCB connectors, male and female
C20-27	47n ceramic	FS1	250mA fuse and holder
VC1	1.5-6p miniature preset	RLY1-4	250V 10A contacts 5V TTL coil
SEMICONDUCTORS			
IC1	8085A	SW1-9	Push to make switch
IC2	HD146818P	T1	12V 750mA mains transformer
IC3	74LS374	XTAL1	4.194304MHz crystal
IC4	74LS138		
IC5	2732 or 2716		
PCB; PCB-mount mains terminals; PCB spacers; IC sockets; case; cables; heat-sink mounting for IC15; nuts and bolts.			

wiring. This will probably be in the kitchen or hall.

The sensors can all be connected via telephone cable using a single core for each sensor and a common connection. Avoid running the sensor cable near mains cables to reduce hum pickup.

The room sensors should be sited on an inside partition wall about 5-6ft above floor level and away from local sources of heat. The water sensor should be taped directly onto the copper of the hot water cylinder, about halfway up.

The mains wiring should all be in suitable cable and powered from a 5A fused supply. Special care should be taken to ensure adequate earthing.

Specification And Operation

Four temperature sensing inputs are provided — External,

Room1, Room2 and Water. Outputs are provided to control a mains activated boiler and two central heating radiator zones (solenoid valves or pumps).

Frost protection is active at all times turning on the boiler if any of the inside temperature sensors read below 5°C.

The water and/or central heating can be switched on automatically at preset times according to 24 programs per week — six each for Saturday, Sunday and all the weekdays plus another six for a 'floating' day to replace any weekday (for, say, a shop's early closing day).

Each program allows the central heating or hot water to be switched on, or both on or both off. Program overrides allow for a 'tankful' of water (say, for a bath), a temporary override until the next program and a semi-permanent override for summer or during a holiday (frost protection is still maintained).

Both hot water and central heating automatically turn off at midnight unless the next day's program turns them on again at that time.

Hot water and central heating temperatures can also be controlled. The weekend and weekdays are divided into six periods and the temperature for the hot water and central heating can be set separately for each period.

Program times and temperatures are retained during power failure for over 100 hours.

The LED display gives the time and instantaneous readings of temperature from all sensors in the range -27.5°C to 99.5°C.

The controls can be password locked against tampering.

Start Up

On switch-on the frost protection is in operation and (after setting the time — see below) the following preset programs are operative:

Sunday	(1)	Weekdays	(d)
07.30	HW & CH	06.30	HW & CH
09.30	CH	09.00	
12.00	HW & CH	12.00	HW & CH
14.00	CH	13.30	
17.00	HW & CH	16.30	HW & CH
19.00	CH	19.30	CH

Saturday	(7)	Float day (F) (set to Friday)
07.00	HW & CH	06.30 HW & CH
09.30	CH	09.00
12.00	HW & CH	12.00 HW & CH
14.00	CH	13.30
17.00	HW & CH	15.00 HW & CH
19.00	CH	19.30 CH

Time	CH	HW
Weekends		
00.00-08.00	12°	45°
08.00-10.00	21°	60°
10.00-12.40	18°	50°
12.40-14.00	20°	60°
14.00-17.00	19°	50°
17.00-00.00	22°	60°
Weekdays		
00.00-06.30	12°	45°
06.30-09.00	21°	60°
09.00-11.00	17°	50°
11.00-13.00	20°	60°
13.00-17.00	15°	50°
17.00-00.00	21°	60°

Time	CH	HW
00.00-06.30	12°	45°
06.30-09.00	21°	60°
09.00-11.00	17°	50°
11.00-13.00	20°	60°
13.00-17.00	15°	50°
17.00-00.00	21°	60°

Pressing the SET/RUN button will put the controller into Set or Run mode as indicated by the red and green LEDs on the front panel.

```

0000 31 FF 27 AF BD OB 03 CD 2E 03 21 00 20 0E FF 36
0010 00 23 00 C2 0F 00 3E FF CD DE 03 21 00 20 CD E1
0020 05 21 01 40 CD 27 01 3E 22 8E C2 6B 07 3E 35 B9
0030 C2 6B 07 3E 16 8A C2 6B 07 34 3F 40 FE 8B C2 6B
0040 07 CD 24 01 32 07 20 CD 42 01 CD 59 01 21 10 20
0050 34 3A 04 20 E6 F0 FE 80 C2 62 00 3A 02 20 CD 6F
0060 02 AF FE 40 C2 6E 00 3A 00 20 CD 6F 02 AF FE 20
0070 C2 7A 00 3A 03 20 CD 6F 02 AF FE 10 C2 B2 00 CD
0080 CF 01 CD EO 01 7D D6 27 32 13 20 CD 36 02 A3 47
0090 3A 17 20 BB CA A3 00 7B 32 17 20 34 0F 20 E6 B0
00A0 32 0F 20 7B CD AF 02 CD DC 02 3A 0C 20 6F 3A 26
00B0 40 E6 0F A5 6F 3A 0F 20 E6 08 7D CA C7 00 3A 0F
00C0 20 E6 03 6F 5F 6B 00 07 07 67 3D 20 E6 80
00D0 07 B5 6F 34 09 20 A5 B4 6F 3A 12 20 2F E6 20 B5
00E0 CD FC 02 7D EA 03 6F 7A E6 02 07 B5 6F 3A 09 20
00F0 A5 C9 07 E0 FO B5 6F 3A 06 20 B5 CD OB 03 06
0100 10 0E FF 3A 12 20 FF FE CA 11 01 CD 15 03 CA E7
0110 03 3A 00 80 FE 00 C2 38 03 00 C2 03 01 05 C2 01
0120 01 C3 41 00 21 02 40 3A 04 40 E6 B0 C2 27 01 46
0130 23 23 4E C3 23 56 21 04 20 70 23 71 23 72 CD 32
0140 07 C9 21 00 20 1E 04 E5 CD 40 07 E7 70 80 1F 77
0150 2C 1C FB 0E CB C3 47 01 21 9E 07 11 2D 40 3A
0160 06 20 FE 01 CA 6C 01 FE 07 C2 72 01 21 98 07 11
0170 27 40 23 13 4E 34 07 20 B9 D2 72 01 1B 7E CD
0180 F2 06 32 0E 20 11 0C 00 06 20 FE 01 C2 F1 01 26 0E
0190 00 0E 1E 02 21 FF 1F CD B9 01 1E 04 CD B9 01 1E
01A0 01 3A 00 20 32 0E 20 CD B9 01 79 32 09 20 0E DB
01B0 3A 0F 20 E6 0F 32 0F 20 C9 23 46 34 04 20 A3 3A
01C0 0E 20 CA C7 01 C4 04 D6 02 8B 68 79 B3 AF C9 2E
01D0 01 3A 05 20 CD 98 02 2E 03 3A 04 20 CD 98 02 29
01E0 06 1E FO 26 40 3A 06 20 FE 01 C2 F1 01 26 0E
01F0 C3 15 02 FE 07 C2 FD 01 2E 1A C3 15 02 47 3A 26
0200 40 OF 0F 0F E6 OF BB C2 0E 02 2E 20 AF FE 00
0210 CA 15 02 2E 14 34 07 20 BE 21 02 23 OD C2 15
0220 02 79 FE 06 CA 24 02 1E FF 2B 70 CD 19 5F 7E A3
0230 E6 03 32 OC 20 C9 34 13 20 06 0E FE 05 CA 49 02
0240 DA 49 02 04 D6 C3 3B 02 4F 06 78 FE 03 C2 56
0250 02 3A 26 40 E6 FO E6 FO 02 C2 5D 02 3E 70 FE 01 C2
0260 64 02 3E DO FE 00 C2 6B 02 3E 10 B1 2E 05 C9 FE
0270 3F D2 80 02 47 3E 10 32 11 20 3E 37 90 C3 B2 02
0280 D6 37 1F 47 DA BE 02 AF 32 02 60 C3 93 02 3E 05
0290 32 02 60 3E OC 32 03 60 0E 01 78 06 00 FE 0A DA
02A0 AB 02 04 D6 C3 9D 02 4F 7B 0F 0F OF B1 47
02B0 E6 0F 4F 7D 26 60 FE 01 79 C2 C7 02 5F 3A 10 20
02C0 E6 01 OF OF OF B3 77 2B 7B 1F 1F 1F E6 0F
02D0 5F 3A 11 20 B3 77 32 11 20 79 C1 21 FF 1F 3E
02E0 43 32 0E 20 0E 00 1E 07 16 03 CD B9 01 15 C2 EA
02F0 02 79 A3 CA FB 02 3E OF 32 0B 20 C9 32 0B 20
0300 32 00 B0 AF C9 3A 04 20 E6 OF B0 32 0A 20 EE FO
0310 07 00 00 AF C9 20 E6 80 C0 20 FE 80 C9 19 03 AF
0320 C9 06 3F 0E FF 00 C2 23 03 05 C2 23 03 C9 16 06
0330 CD 21 03 15 C2 30 C9 34 00 00 FE 80 C2 45 03
0340 06 10 CD 05 03 FE 40 C2 4F 03 06 20 CD 05 03 FE
0350 20 C2 59 03 06 40 CD 05 03 FE 10 C2 63 03 06
0360 CD 05 03 47 3A AB 07 BB C2 7D 03 CD 2E 03 3A 00
0370 80 47 3A AB 07 BB C2 7D 03 AF 32 12 20 3A 12 20
0380 FE 00 C2 FF 00 3A 00 B0 FE 01 C2 93 03 21 26 40
0390 CD 88 03 FE 04 C2 96 03 21 0F 20 CD B8 03 FE 08
0400 C2 AB 03 3A 0F 20 FA B0 32 0F 20 FE B1 C2 FF 00
0410 3E FF 32 12 20 C3 FF 00 07 7E E6 03 07 07 57
0420 C9 06 32 18 20 E6 B2 C2 FC 02 CD 21 03 34 00 B0 E6
0430 02 C2 D8 03 C1 C5 85 03 1C 7B E6 03 4F 7E E6 FC
0440 B1 F8 08 77 C3 B9 03 3E 40 CD FC 02 3E 01 32 10
0450 20 AF 32 16 20 3E 10 CD 08 03 CD 15 03 CA 40 04
0460 34 00 80 4F FE 04 C2 23 04 3A 04 20 FE 80 C2 40 04
0470 A2 04 3E 08 07 47 CD 05 03 32 13 20 3E 40 CD FC 02
0480 92 04 3E EE CD 05 21 CE 07 11 0E 04 3E 03 33 C3
0490 E6 07 7E 32 06 40 2D 7E 32 04 40 2D 7E 32 02 40
04A0 AF C9 7E CD A9 07 77 AF C9 BB 08 DA B1 09 79 06 01
04B0 C9 01 C9 7E C9 BB 04 77 AF C9 B9 F2 C1 04 79
04C0 C9 06 01 C9 3A 04 00 40 07 07 07 07 E6 FO F6 0D 02
04D0 05 CD AF 02 AF C9 CD E9 05 E5 CD 18 07 04 00 80
04E0 FE 82 21 05 20 01 01 17 CC A2 04 FE B1 CC B4 04
04F0 E1 E5 7E 07 07 51 01 01 05 3A 00 80 FE 42 C9 04
0500 05 74 CD A9 04 57 C3 13 05 FE 41 C2 13 05 7A CD
0510 BB 04 57 CD 32 07 E6 FB 27 77 3A 00 80 FE 02 C2
0520 32 05 CD E5 7D C2 19 6F 7E 3C E6 03 47 7E E6 FC
0530 BB 77 FE 20 C4 20 05 21 13 20 01 17 CD A2 04
0540 FE 08 C2 56 05 E1 E5 3E CO 77 CD DC 05 21 21 03
0550 3E FF 32 18 20 AF 3E 30 C2 82 05 3A 13 20 FE 12
0560 D8 02 05 3A 26 40 E6 FO C6 10 FE 70 C2 71 05 3E
0570 FO FE 00 C2 78 03 3E 20 47 3A 26 40 E6 OF B0 S2
0580 26 40 E1 E5 3A 02 20 FE 18 CC DC 05 C1 CF 01 CD
0590 34 02 CD AF 02 47 3A 14 20 BB CA B2 05 3F FF 32
05A0 18 20 78 32 16 20 E1 7D C4 19 6F 7E E6 03 07 07
05B0 07 F6 40 CD FC 02 3A 18 20 FE FF C2 BF 05 C9 AF
05C0 32 18 20 21 04 CD F2 05 21 14 40 CD F2 05 21
05D0 1A 40 CD F2 05 21 20 40 CD F2 05 29 3E OC 21 00
05E0 60 77 23 77 23 77 C9 21 0E 40 3A 13 20 B5
05F0 6F C9 7D 5D C6 05 4F 6B 46 23 7E BB DC 07 06 D6
0600 B9 28 06 C3 FB 05 70 28 77 23 E5 7D C6 18 6F
0610 7E 6E 03 47 TE 90 57 23 7E E6 03 B2 28 77 23 7E
0620 E6 FO 20 77 E1 16 01 C9 AF BA CB 16 00 C3 05
0630 21 27 40 FE BO C2 34 06 2E 33 3A 13 20 B5 6F 7E
0640 47 E6 FO OF 32 14 20 3A 00 20 FE 80 C6 74 F2
0650 04 CC F9 06 E5 C6 02 CD 36 02 FE 20 D2 62 06
0660 EE FO CD AF 02 32 18 20 3A 00 80 FE 20 C2 D2 06
0670 21 13 20 01 01 CD A2 04 E1 C3 06 02 21 14 20
0680 01 01 SE FE 02 C2 92 06 CD A2 04 E1 CD 04 06 C3
0690 D2 06 FE 01 C2 A1 06 CD BC 04 E1 CD 04 06 C3 D2
0700 04 FE 10 E1 C2 D2 06 E5 21 13 20 01 01 08 C3 02
0710 05 CD 36 02 FE 22 BB 06 EE FO AF 02 47 3A
0720 18 20 78 E6 07 47 AF E6 08 00 80 DC 22 07 32 04
0730 20 C9 34 04 20 1E 00 FE 04 DA 42 07 1C D6 04 C3
0740 37 07 3A 05 20 07 07 E6 FB B3 C9 21 00 06 C3
0750 00 16 00 78 32 02 C0 3E 03 3D C2 59 07 3A 00 C0
0760 4F 09 15 C2 53 07 44 C9 3E OF 32 04 40 3E 0E 06
0770 08 40 AF CD FC 02 CD 42 01 CD DC 02 3A 06 20 CD
0780 08 03 CD 15 03 C2 6B 07 3A 00 80 FE 00 CA 8B 07
0790 CD EO 04 C3 E7 03 FD FD 40 50 64 70 88 FF 33
07A0 48 5D 6B 8B FF 63 00 01 07 FE 00 CA 80 07 F6 08
07B0 6F 3A 00 20 C9 FF 20 4E 4F 50 26 31 39 38 35
07C0 00 22 00 35 00 16 01 01 01 09 06 00 80 3B 48
07D0 60 70 88 98 33 48 60 6B 78 38 48 60 70 88 98
07E0 33 48 60 6B 78 48 33 7A 63 72 6B 82 33 5B
07F0 70 4B 7A 37 72 4B 72 4B 72 37 70 4B 70 48 72 BB

```

Listing 1 Hex dump of the EPROM software.

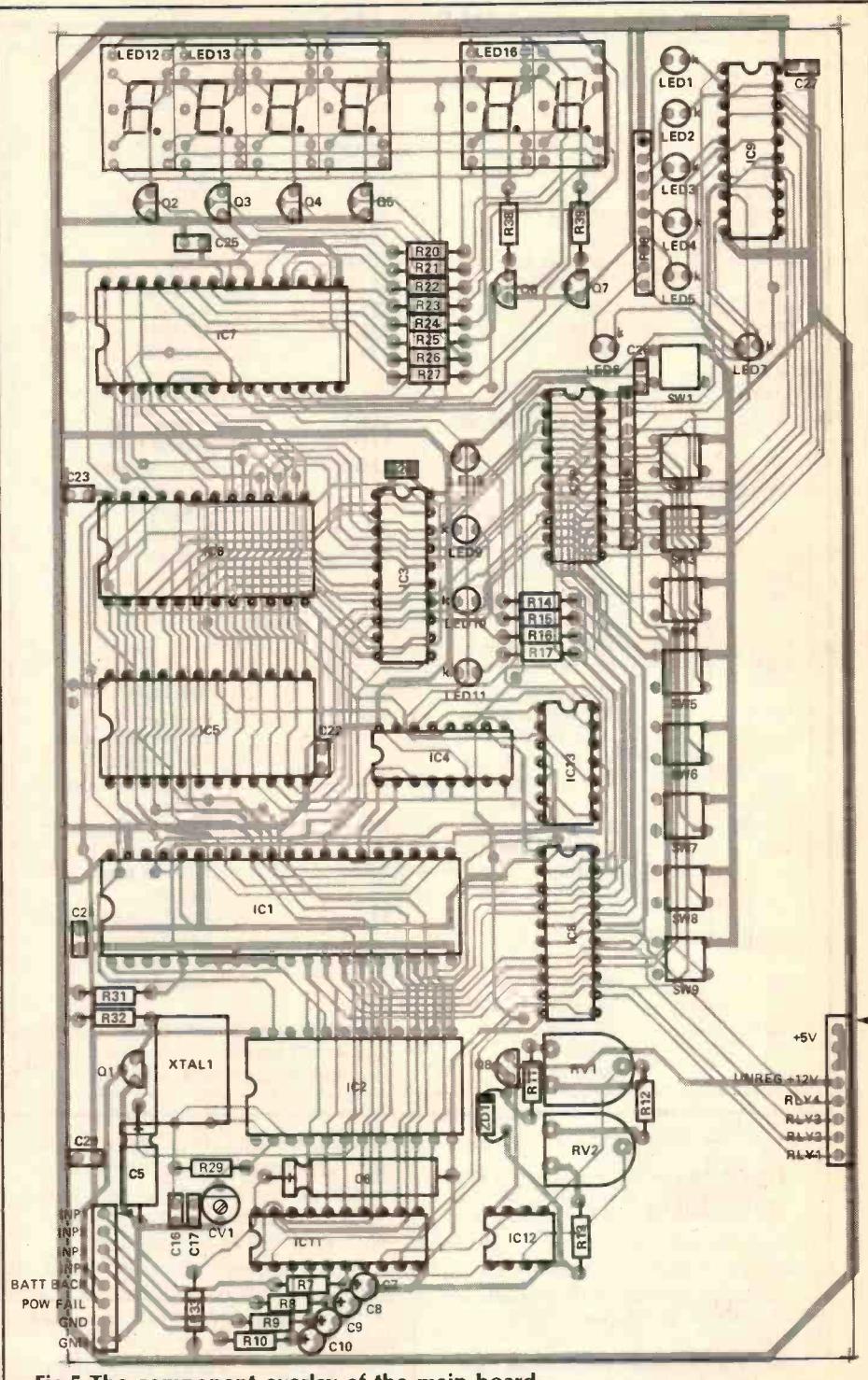


Fig.5 The component overlay of the main board.

The time and temperature measured by the three sensors can be displayed in Run mode by pressing the relevant button.

In Set mode the function being set is indicated by one of the four LEDs to the left of the buttons. You can advance to the next function by pressing the FUNCTION button.

The Time

With the top function LED lit, the time may be set by pressing the HOUR, MIN, and DAY/PROG Buttons in turn and using the Δ buttons to increase and decrease the time displayed.

Pressing the FUNCTION button will enter the time and move on to the program function.

Program Times

The program times for each day are numbered 1 to 6 and the programmable days are labelled 1 for Sunday, d for the weekdays, 7 for Saturday.

Step through each program for each day using the DAY/PROG button. Set the time for each

PROJECT: Heating Management

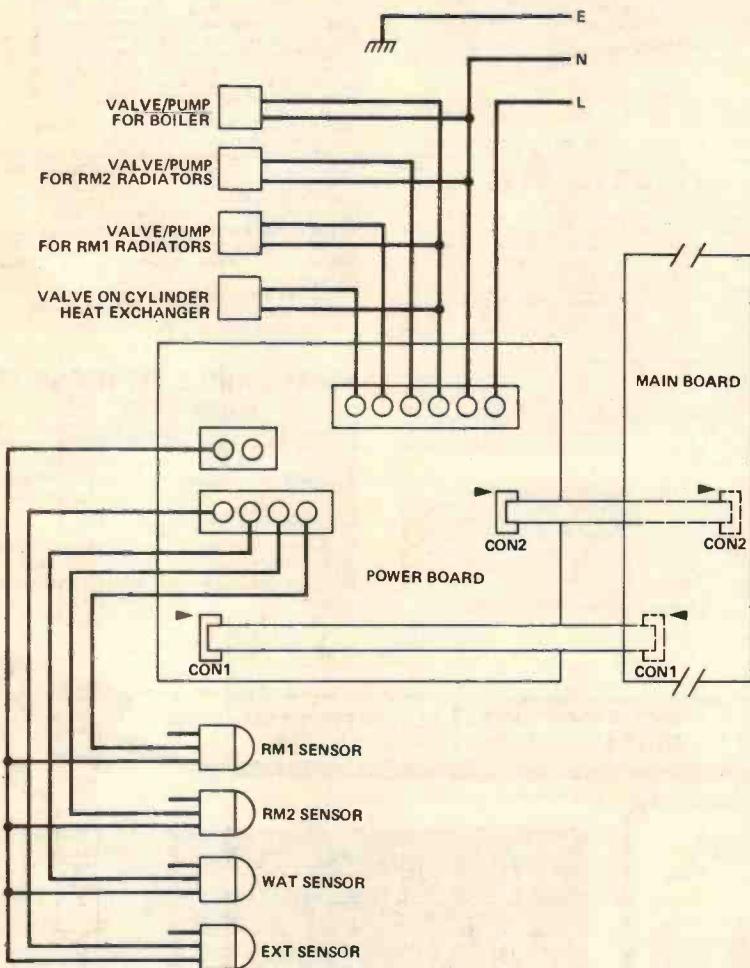


Fig.6 Interconnecting the PCBs and installing the system.

program event in the same way as the time of day is set (note, however, that the minutes is now advanced in ten minute steps). The action at the time set is programmed by pressing the STEP button until the HW AVAIL and CH AVAIL LEDs indicate the desired action.

The program is set when the DAY/PROG button is pressed to move to the next program. The process is repeated for each set of six programs for each programmable day. Programming the floating day is the same except that the day the floating day is to replace is set with the COPY button. Press and hold the COPY button and press the DAY/PROG

button until the day number required is displayed.

If all six programs for any programmable day are not required the unwanted programs can be deleted by pressing the CANCEL button. The display shows CCCC for a short period and the remaining programs are moved down to take up the space. CCCC is displayed for the time of any such cancelled programs.

There is no need to enter program times in chronological order. The software sorts them.

Program Temperatures

The weekend (E) room temperatures are set first. For

each period the set temperature is displayed and can be altered using the Δ and ∇ buttons. The DAY/PROG button sets the temperature and advances to the next period. After all six periods have been programmed the DAY/PROG button moves onto the weekday (d) room temperature periods.

The water temperature is set next and in the same way as the room temperatures.

To save time, the COPY button can be used to copy the current temperature settings to the following periods for that day.

The preset times and temperatures can be set at any time by pressing CANCEL, Δ and ∇ at once in Set mode.

Overrides

Pressing the ADVANCE button allows the control of the central heating and hot water by the timer to be overridden until the next programmed time event. The STEP button and the CH AVAIL and HW AVAIL LEDs are used to set which function(s) remain under the timer control.

The OVERRIDE button is used in the same way but the manual setting remains until cancelled by using the OVERRIDE and STEP buttons to return control of both the hot water and central heating to the pre-programmed sequence.

The HW BOOST button will switch on the hot water (say, for a bath) until the temperature reaches the current period temperature when it shuts off to follow the normal program.

Locking

The controller can be locked by pressing and holding the HOUR and OVERRIDE buttons together for a few seconds. Locking is indicated by the RUN LED going off. To unlock the controller, press the ADVANCE, STEP and OVERRIDE buttons together for five seconds.

ETI


BUYLINES

Most of the components should be available from usual sources. The suppression capacitors (C12-15) are available from Maplin.

The EPROM (IC15) is available ready programmed from the author for £10. Please address all orders and enquiries to Harry Bloomfield, 49 Oak Crescent, Garforth, Leeds LS25 1PW. The PCBs are available from the ETI PCB Service.

**TRADE
LURE**

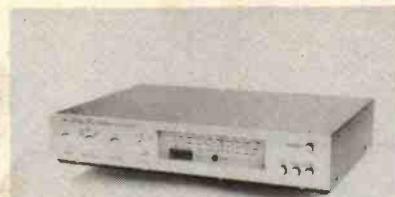LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer.

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit	£33.70
VU Meters to suit	£2.30 each
Reprints of original Articles	75p no VAT
860X Stereo Mic Amplifier	£8.70

LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hood's articles in 'Hi-Fi News'.

Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35. 35 Watt. Discount price for Complete Kit £98.79
K300-45. 45 Watt. Discount price for Complete Kit £102.36
RLH4&5. Reprints of Original Articles from 'Hi-Fi News'
£1.05 no VAT

Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchrodyne AM receiver described in "Wireless World". The complete unit is based to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotics but, thanks to HART engineering, remains easy to build. The Synchrodyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HiFi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of its sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life.
K900W Stereo Kit with Wound Coils and Twin Meter Drive £65.67
RJS1 Reprints of Original Articles £1.30 no VAT

**HIGH QUALITY REPLACEMENT
CASSETTE HEADS**



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks	£7.66
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response	£14.85
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head	£14.60
HX100 Stereo Permalloy R/P head. Special Offer £2.49	
MA481 2/2 Language Lab R/P head	£13.35
SM166 2/2 Erase Head. Standard mounting. AC type	£8.85
SM166 2/2 Erase Head. DC Type	£3.60
HQ751E 4/4 Erase Head for Portastudio etc.	£46.80
Full specifications of these and other special purpose heads in our lists.	

**HART TRIPLE-PURPOSE TEST
CASSETTE TC1**

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback

£4.54

Curved Pole Type for inaccessible heads

£4.85

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

INLAND

Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS

Please send sufficient to cover Surface or Air Post as required.



Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE
(0691) 652894

ALL PRICES EXCLUDE VAT
UNLESS STATED

**TRADE
LURE**
HART ELECTRONIC KITS LTD
4 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

KEF CONSTRUCTOR SERIES SPEAKER KITS

Based on the famous Kef Reference Series, these three DIY designs give the home constructor the opportunity to own an upmarket pair of loudspeakers at a very down-to-earth price!

With a Wilmslow Audio Total Kit it's easy


— no electronic or woodworking skill is necessary. Each kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly), speaker drive units, crossover networks, wadding, grille fabric, terminals, nuts, bolts etc.

Model CS1 is based on the Reference 101, CS3 is equivalent to the Ref. 103.2 and CS9 is based on the Reference 105.2 (but in a conventionally styled encl.).

CS1 £117 pair inc. VAT plus carriage £6
CS3 £143 pair inc. VAT plus carriage £12
CS9 £393 pair inc. VAT plus carriage £18

We also offer a kit (less cabinet) for Elector PL301

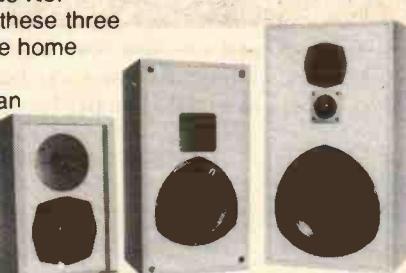Lightning service on telephoned credit card orders!



It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema. Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code. Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.
ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

RACKZ 19" RACK MOUNTING EQUIPMENT CASES

This new range of 19" rack equipment cases have been designed with economy and versatility as their objective. These cases are supplied as a flat pack kit with assembly instructions. The equipment cases feature a black powder coat 1/8" (3mm) aluminium frontpanel with the rest of the case constructed from .7mm or .9mm 'Stelwelt' PVC coated steel. All kits include front panel handles and rubber feet.

They are available in the following popular sizes with all the units having a standard front panel width of 19", and an enclosure width of 17 1/4" (438mm) by a depth of 10" (254mm).

ORDER CODE	HEIGHT	PRICE
U1	19 1/4" (44mm)	16.00
U2	3 1/2" (88mm)	18.00
U3	5 1/4" (133mm)	20.00
U4	7" (178mm)	22.00

All prices Exclude V.A.T.

Please include £2.50 per item for Post & Packing.

Flat pack size = 500 x 260 x 32

Maximum weight = 1.5Kgs.


Blanking Panels and Rack Cabinets also available.

Please send S.A.E. for further details

* TRADE ENQUIRIES WELCOME *

Tel. 0275 823983 for Access/Visa card sales for immediate despatch or send cheque with order to:

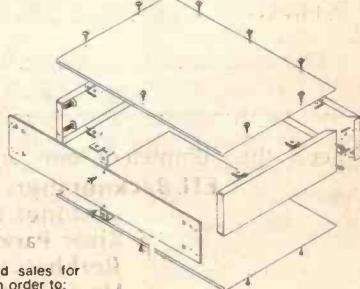RACKZ PRODUCTS PO. BOX NO. 1402, MANGOTSFIELD, BRISTOL,
ENGLAND. BS17 3RY



DIY Speaker catalogue £1.50 post free (export \$6)

BACK NUMBERS

- Missed part one of your favourite project?
- Lost that all-important article on circuit design?
- Desperately need that Tech Tip to get your latest masterpiece going?
- Pining for that one issue to complete your valuable collection?

ETI Backnumbers Department to the rescue!

Please note that backnumbers are only held for 12 months. Articles published previous to this must be obtained through our photocopy service.

PHOTO-COPIES

ETI has been published for over 15 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers are available for only the past 12 months' issues we can supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

PCB foil patterns (where published) and any errata are included with all photocopies as applicable.

Please supply the following backnumbers of ETI.
Note: Backnumbers are held for 12 months only
(complete in block capitals)

Month Year Month Year

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.90 per issue ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:

ETI Backnumbers Department

Infonet Ltd.

**5 River Park Estate
Berkhamsted
Herts HP4 1HL**



Please supply photocopies of the following articles from ETI (complete in block capitals):

Month Year Page (if known)

Title

Month Year Page (if known)

Title

Month Year Page (if known)

Title

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:

ETI Photocopy Service

Argus Specialist Publications

**1 Golden Square
London W1R 3AB**



ETI INDEX 1987

Article

Mth

Pg

Article

Mth

Pg

FEATURES

15 Years (of ETI)		April	12
3D TV		Sept	13
All Above Board (surface mounting)		July	13
Balanced Lines		Feb	14
CMOS Oscillators		Sept	18
Car Electronics		Aug	13
Cellular Radio		Feb	25
Chris Curry Profile		July	26
Circuit Theory (circuit modelling)		April	28
(sine waves)		May	16
(Fourier)		June	21
(Fourier)		July	18
(Thévenin boxes)		Aug	20
(phasor diagrams)		Oct	15
(phasor diagrams)		Nov	22
(phasor diagrams)		Dec	20
Computer Aided Design		Oct	18
Designing For Efficiency (SMPS)	Part I	Nov	27
	Part II	Dec	27
Electronic Car, The		Aug	13
FM From The Beginning		Jan	25
Feedback, Avoiding		Sept	27
Foreign Ports (computer interfacing)		March	13
Forgotten Oscillator, The		Nov	24
Going It Alone (business special)		Jan	40
Graphics Processors		April	15
Hard Times (multiplier ICs)		Aug	28
Hardware Design Concepts		Jan	22
		Feb	21
		March	20
		April	23
		May	12
		June	18
		July	21
		Aug	24
		Sept	20
		Oct	26
		Nov	18
		Dec	22
Hi-fi, The Truth About		May	19
Home CADMAT		Oct	18
Inside Hybrid's Music 5000		Oct	23
Interfacing Standards		March	13
MIDI Interface	Part I	Feb	31
	Part II	Jan	17
Multiplier ICs		Aug	28
Music 5000		Oct	23
Oscillator, The Forgotten		Nov	24
Question Of Balance, A		Feb	14
RIAA Equalisation		June	25
Radio, Cellular		Feb	25
Red Curry (Chris Curry profile)		July	26
Second Time Around (2nd hand test gear)		Dec	16
Snubber Networks		March	26
Stereoscopic Television		Sept	13
Surface Mount Technology		July	13
Switch Mode Power Supplies		Oct	11
Taking Care Of Business		Jan	39
Telephone System, The		June	12
Teletext		Nov	10
Test Gear		Dec	11
Test Gear, Buying second hand		Dec	16
Thinking It Through (business special)		Jan	39
Transputer, The		March	23
Truth About Hi-fi, The		May	19
Useful Addresses (business special)		Jan	46

PROJECTS

24Hr Sundial		April	30
Alarm, Car	errata	Aug	40
Alarm, Flat	errata	Nov	57
Alarm, Rear Wiper	errata	June	43
Alarm, Telephone	errata	Nov	57
Amstrad Sampler		Sept	41
Analyser, LEDline		Feb	50
Audio Selector, Digital		Jan	52
BBC Micro MIDI Interface		April	42
Batlite (battery monitor)		May	24
Big Digits (numeric display)		Oct	30
Boiler Controller		Sept	47
Capacitometer (capacitance meter)	errata	Nov	57
Car Alarm	errata	March	45
Car Lights Reminder	errata	Sept	57
Casino, Credit Card (game)		Aug	40
Concept (mains meter/controller)	errata	Nov	57
Controller, Boiler	errata	Aug	32
Controller, Heating		March	50
Controller, Mains (Computer)	Part I	Oct	37
Controller, Photo Process	Part II	Nov	37
Credit Card Casino (game)	errata	Nov	57
Darkroom Timer		Sept	47
Decoder, Low Distortion Stereo		Dec	25
Digital Audio Selector		Jan	35
Dream Machine		Feb	41
Dwell and Tacho Meter	errata	Aug	57
EEG Monitor		March	50
Electronic Violet	Part I	May	41
ETI Faker	Part II	Feb	46
FM Tuner, PLL	Part III	Jan	52
Flame Simulator	Part I	Nov	32
Flanger, The Better	Part II	Dec	37
Flat Alarm	Part III	Jan	62
Fuzz Box (Hyper-Fuzz)	Part I	Sept	34
Geiger Counter	Part II	Oct	46
Geiger Ratemeter	Part III	Nov	50
Heating Management System	Part I	Dec	41
Hi-fi Power Meter	Part II	April	38
Hyper-Fuzz	Part III	March	34
Kapellmeisters (loudspeakers)	Part I	April	33
Keyboard, MIDI Master	Part II	June	40
	Part III	Jan	47
	Part IV	Aug	57
	errata	June	43
	errata	Nov	57
	errata	Oct	43
	errata	July	33
	errata	Nov	57
	errata	May	27
	Part II	June	33
	Part III	July	40
	Part IV	Aug	32
	errata	Oct	57


ETI INDEX 1987

Article	Mth	Pg	Article	Mth	Pg
Knight Raider (car lights display)			Digital Temperature Readout	Jan	72
LEDline Analyser	errata	Aug 46	Direct-Ion Improvement	Oct	52
LEDscope (LED array oscilloscope)		Nov 57	Electric Guitar De-fleaing	May	46
Lights-on Reminder		Feb 50	Electronic Tuning Fork	May	45
Loudspeakers (Kapellmeisters)		Jan 57	Guitar Lead Checker	May	44
Low Distortion Stereo Decoder	errata	Aug 32	Inductive Track Follower	April	50
MIDI Interface, BBC Micro		July 33	Initials Sender	Aug	50
MIDI Master Keyboard	errata	Nov 57	Metronome	May	44
Low Distortion Stereo Decoder		Feb 46	Missing Pulse Detector, Improved	Jan	68
MIDI Interface, BBC Micro		April 42	Motor Speed Regulator	April	47
MIDI Master Keyboard	errata	Sept 57	Phone Line Monitor	Jan	68
Mains Controller (computer)	Part I	May 27	Priority Selector	Jan	66
Mains Controller/Meter (Concept)	Part II	June 33	Replacement Voltage Regulator	Jan	72
Mains Controller (computer)	Part III	July 40	Shaft Position Indicator	April	48
Mains Controller/Meter (Concept)	Part IV	Aug 32	Simple Audio Limiter	July	52
Mains Controller (computer)	errata	Oct 57	Stereo For Time Delay Effects	Jan	66
Mains Controller/Meter (Concept)	Part I	Jan 35	Trailer Light Controller	Feb	54
Multi-standard Printer Buffer	Part II	Oct 37	Tape Loader For The Spectrum	Oct	52
Nuclear Strategy Simulator	Part II	Nov 18	Thief Staller	Jan	71
Numeric Display (Big Digits)	errata	Nov 57	Two Transistor Latch	Oct	53
PA, Portable		Nov 43	VDU Sync Sorter	Oct	53
PLL FM Tuner		July 28	Valve Distortion Fuzz Box	May	46
Patch Box, RS232 (ETI faker)	errata	Nov 57	Variable Mark-To-Space Generator	Oct	53
Photo Process Controller		Oct 30	Versatile 6502 DRAM Interface	March	54
Portable PA	Part I	Sept 31	Video Clamping Circuit	Jan	69
Power Meter, Hi-fi	Part II	March 34			
Portable PA		April 33			
Power Meter, Hi-fi		April 38			
Power Meter, Hi-fi		Feb 41			
Printer Buffer, Multi-standard	errata	Aug 57			
Quiz Controller		Sept 31			
RGB-Composite Converter	Part I	June 29			
RS232 Patch Box (ETI faker)	Part II	May 33			
Rear Wiper Alarm	errata	Oct 57			
Remindalite		Nov 43			
Rev Counter, Sonic		Nov 40	Allbatteries Solar Cells	Aug	53
Sampler, Amstrad		Jan 32	Amba Multi-function Electronic Tester	Nov	55
Sonic Rev Counter		April 38	BK Electronic Guard Dog	Dec	53
Stereo Decoder, Low Distortion		Aug 44	Circuits On The Small Screen		
Sundial, 24Hr		Aug 32	(CAD Software)	March	28
SWR Meter		Aug 38	Hybrid Music System	Sept	24
Tacho-Dwell Meter		Sept 41	M & A Series Four Mixer Kit	March	32
Telephone Alarm		Aug 47	Riscomp Infra-Red Alarm	Sept	53
Telfax (auto-cue cassette)	errata	Feb 46	Sage Audio Modules	May	47
Tuner, PLL FM	Part I	April 30	Sony D100 CD	Aug	52
Tuner, PLL FM	Part II	March 34	Sony DC2 And D6 Walkman	May	51
Tuner, PLL FM	errata	Dec 46			
Tuner, PLL FM		Jan 62			
Tuner, PLL FM		July 44			
Tuner, PLL FM	errata	Nov 57			
Tuner, PLL FM		May 38			
Tuner, PLL FM	Part I	Nov 57			
Tuner, PLL FM	Part II	March 34			
Tuner, PLL FM	errata	April 33			
Tuner, PLL FM		Nov 57			
TECH TIPS					
3-in-1 Reset		July 52	BOOKS		
50Hz Inverter		Feb 54	62 Home Remote Control And		
Aerial Without Holes	errata	Jan 72	Automation Projects	April	53
Auto Battery Charger		May 57	Build A Better Music Synthesiser	Aug	54
Bargraph Fuel Gauge		March 54	Build A Remote Control Robot		
Brake Light Failure Indicator		Jan 70	For Under £300	April	53
Coherent Optical Proximity Detector		Jan 71	Computer Peripherals That		
Compressed Power Microphone		April 49	You Can Build	July	48
Computer Control Of AC Power		Aug 52	Computer Projects For Railway		
		Jan 66	Modellers	Oct	48
			Electronic Circuits For the Computer		
			Control Of Model Railways	Oct	55
			Electronic Circuits For The		
			Computer Control Of Robots	April	53
			How To Use Special Purpose ICs	Sept	54
			Newnes Computer Engineer's		
			Pocket Book	July	48
			Sinclair And The 'Sunrise' Technology	May	51


Brainwave

Are we about to create a race of Supermen?

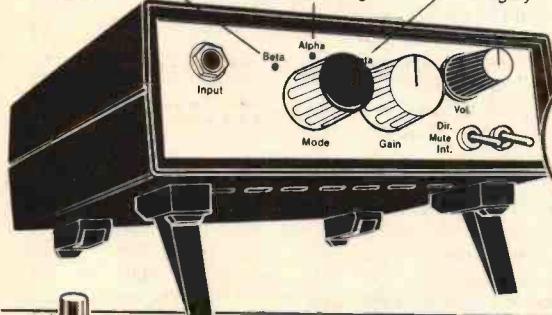- BETA** - Concentration, problem solving, active thought.
- ALPHA** - Relaxation, pleasure, tranquility, positive feelings.
- THETA** - Imagination, creativity, hypnagogic imagery.



monitor

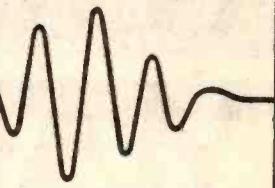

The ETI Brainwave Monitor must be the most astonishing project ever to appear in the pages of an electronics magazine. It will allow you to hear your brainwaves and judge the relative levels of various types. It will also help you to control your mind more effectively, to be at peak performance in all situations.

Doesn't my mind work perfectly well when left to its own devices?

If you've ever been confused, unsure of yourself, shy, unable to pass exams or to impress people at interviews, you know perfectly well that it doesn't. Your mind (and everybody else's) is full of bad habits, inappropriate responses, feelings of inadequacy... all pulling you down. Why should you put up with it?

Mind training sounds like hard work!

It can be. If you want to do it the hard way, go and study under a Zen master for fifty years or so. You'll get there in the end! With the brainwave monitor it takes no effort at all. Just the opposite in fact - trying is the one thing you mustn't do!

How do I start?

At first you use the monitor's internal indicator to exercise your mind. In direct mode you improve the time percentage; in integrate you concentrate on the amplitude. After that, the choice of direction is yours. With the Alpha Plan you can reach the core of your personality to root out the weakness and replace it with inner strength. Otherwise you can just enjoy the feelings of pleasure and clear headedness that alpha training brings, or the creativity and imagery of the theta state.

A friend told me I can use brain power to control lights and things. I can't believe it! As a matter of fact, you can do more than that! The interface sockets on the monitor allow you to turn lights on and off, control toys and electrical gadgets, play computer games... all with your mind! Are we about to create a race of Supermen? Only time will tell.

The Brainwave Monitor is featured in the September, October and November 1987 issues of ETI. The approved parts set contains: two PCBs, all components including three PMI precision amplifiers, shielded box for screening the bio-amplifier, attractive instrument case with tilting feet, controls, switches, knobs, plugs and sockets, leads and materials for electrodes, full instructions for assembly and use.

Parts are available separately. We also have a range of accessories, professional electrodes, books, etc. Please send a stamped, self-addressed envelope if you just want the lists. Otherwise, an SAE + £2 will bring you lists, construction details and further information.

SILVER SOLUTION

This powerful silver plating compound must be the greatest revolution in electronics since the ICI Just wipe on with a cloth to plate PCB tracks, connectors, wire, component leads, etc. with a layer of pure silver!

- * RF circuits.
- * Top flight Hi-Fi.
- * Bio-electronic circuits and electrodes.

LARGE BOTTLE (150ml) SILVER SOLUTION £11.20 + VAT
N.B. The solution will take to brass, copper, etc. but not to steel or pre-plated components.



THE ALPHA PLAN

Can you really train your brain to think more effectively? Can you really achieve peak performance in things you're 'no good at'? Can you really overcome fear, shyness, uncertainty?

... And can you do it all without really trying?


Dr David Lewis's famous Alpha Plan has all the answers. It was recently investigated by a QED television documentary (Alpha - How to Succeed Without Really Trying). And the conclusion? It works!

Dr. Lewis's book 'The Alpha Plan' is yours for only £2.50 (no VAT). Your future is waiting.

Complete Parts Sets for ETI Projects

MAINS CONDITIONER

FEATURED IN ETI,
SEPTEMBER 1986

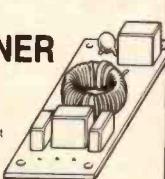

KNIGHT RAIDER

FEATURED IN ETI, JULY 1987

It is astonishing how many people buy or build top-flight hi-fi equipment, and then connect it to a noisy, spiky mains supply. Rather like buying a Ferrari and trying to run it on paraffin, you might think. Expecting crystal clear sound, the poor music enthusiast ends up with a muddy, confused mush, and feels that he has somehow been cheated. 'Is this hi-fi? My music centre sounded just as good!'

The domestic mains supply is riddled with RF interference, noise, transient spikes, and goodness knows what else. Computers crash, radios pop and crackle, tape recordings are spoiled and so on. So why not quite right? Why put up with it when the solution is so simple? The ETI mains conditioner is the low-cost upgrade you will ever buy, and probably the most effective.

Our approved parts set consists of PCB, all components, toroid, enamelled wire, fixing ties, fast response VDR, and full instructions.


ETI MAINS CONDITIONER PARTS SET

ONLY £4.60! + VAT

*Note: the toroid and VDR supplied are superior to the types specified in the article.

MATCHBOX AMPLIFIER

FEATURED IN ETI,
APRIL 1986

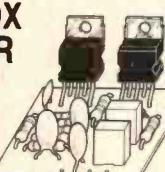

No ordinary amplifiers, these. When our first customers took an interest, it was for the unique size of both modules. At 10mm x 15mm (matchbox), the total disregard for power supplies and speaker impedances, and the impressive power output from these little amplifiers. When they re-ordered, it was for the sound quality.

Two amplifier modules were described, both based on the powerful L165V IC. The single IC version will deliver over 20 Watts into 8 Ohms from a 12V power supply.

The bridge version can provide up to 50W into 4 Ohms.

The specified supply voltage and speaker impedance must be used to achieve maximum power, both modules are quite happy to work from any voltage between 12V and 32V,

and will accommodate any type of speaker. The bridge version is ideal for giving a boost to car Hi-Fi systems, driving two 4 Ohm speakers from a 12V car battery.

Both designer-approved parts sets consist of a roller tinned printed circuit board and all components.

The L165V ICs are also available individually, with a free mini data sheet giving specifications and suggested circuits.

SINGLE IC MATCHBOX BRIDGE AMPLIFIER SET (20W into 4 Ohms) £6.50 + VAT

AMPLIFIER SET (50W into 8 Ohms) £8.90 + VAT

L165V IC, with data, £3.90 + VAT

POWERFUL AIR IONISER

FEATURED IN ETI,
JULY 1986



Ions have been described as 'vitamins of the air' by health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with those on the market, yet was reliable, good to build... and fun! Apart from the serious benefits to health, improving concentration and putting an end to insomnia, the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller tinned printed circuit board, 66 components, case, mains lead, and even the parts for the base! According to one customer, the set costs 'about a third of the cost of the individual components'. What more can we say?

Instructions are included

DIRECT ION PARTS SET £9.50 + VAT

PROJECT BOX

PROJECT CASE
WITH PP3 BATTERY
COMPARTMENT

ONLY £2.60! + VAT



LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

LM2917 Experimenter Set £5.80 + VAT

RUGGED PLASTIC CASE

Suitable for mains conditioner and mains controller.

ONLY £1.65 + VAT



SPECIAL OFFER

Our best selling ioniser kit is now available with an elegant white case.

**WHITE IONISER
PARTS SET ONLY £9.80! + VAT**

Prices shown are exclusive of VAT, so please add 15% to the order total. UK postage is 60p on any order. Carriage and insurance for overseas orders £1.50. Please allow up to 14 days for delivery.

Specialist SEMICONDUCTORS
LIMITED

FOUNDERS HOUSE
REDBROOK
MONMOUTH
GWENT

THE DREAM MACHINE


Paul Chappell puts the free components on this month's cover to good use with a description of the construction of the ETI Dream Machine.

Last month I spoke of dreams in general and described the basic principle of the Dream Machine. You should also have collected your free PCB from the cover. Now that you have the components too, it's time to start on the construction.

You will have to decide before you start whether you want to build the simple version or the complete project because the component layout is slightly different for each.

The simple circuit will give you a taste of the possibilities of the Dream Machine without spending any money! It can be built entirely from the ETI free gifts. The circuit diagram for this version is shown in Fig.1. You will need to feed the output into your hi-fi amplifier to make it audible. Figure 2 shows how to lay out the components on the PCB and how to connect the circuit to your amplifier. The circuit is powered from a PP3 9V battery.

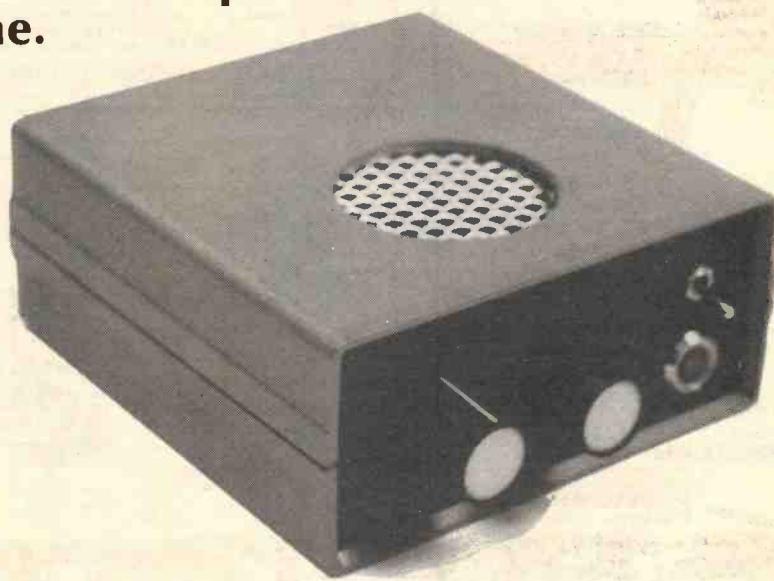The extended Dream Machine circuit is shown in Fig.3. This version is a completely self-contained project with its own mains power supply, amplifier, speaker and controls. Figure 4 shows the component layout for



HOW IT WORKS

The simple version first (Fig.1). This really is simple! The zener produces noise voltages which are buffered by Q1 and amplified by a factor of about 2½. The capacitor gives a gentle roll-off to the higher frequency components and the output is fed to an external audio amplifier.

The complete Dream Machine (Fig.3) is similar in principle but allows variation of the volume and depth of the sound and also allows the circuit to be trimmed for maximum output. RV1 sets the operating conditions for ZD1 to allow it to

produce maximum output. Q1 amplifies the output considerably and RV2 adjusts the steepness of the high frequency cut-off. IC1 amplifies the sound and drives the loudspeaker.

The voltage gain of IC1 is set by R4. C6 cuts the gain of the amplifier at high frequencies to keep it stable. R5 and C9 make the load on the amplifier 'look' more resistive at high frequencies which helps the transient response and the stability. IC2 is a voltage regulator to provide a fixed 12V supply to the circuit.

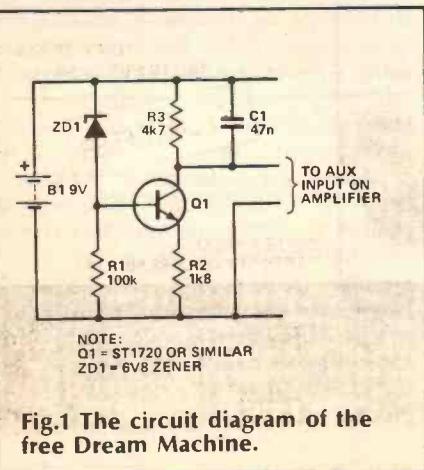


Fig.1 The circuit diagram of the free Dream Machine.

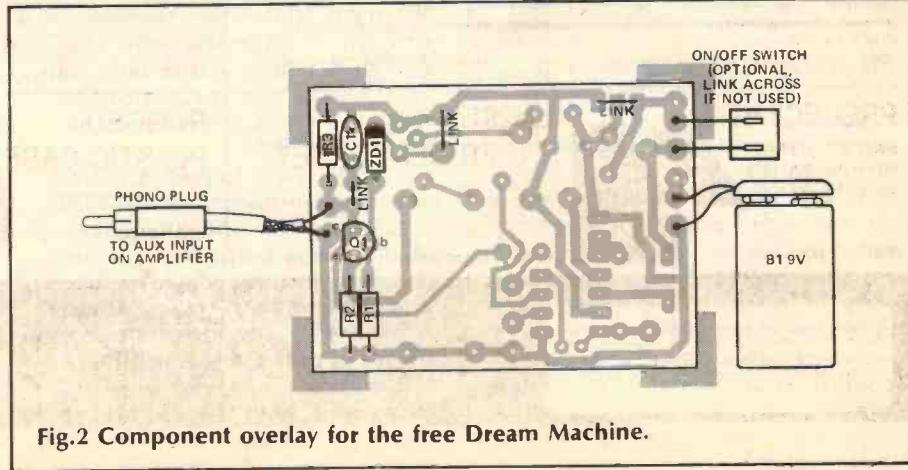


Fig.2 Component overlay for the free Dream Machine.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	100k *
R2	1k8 *
R3	4k7 * (not required for complete project)
R4	47R
R5	1R0
RV1	500k horiz. preset
RV2	4k7 log pot
RV3	10k log pot

CAPACITORS

C1	47n ceramic *
C2	2μ 16V radial electrolytic
C3,5	100μ 16V axial electrolytic
C4	4μ 16V radial electrolytic
C6	220p ceramic
C7	47μ 16V radial electrolytic
C8	220μ 10V axial electrolytic
C9	220n 16V tantalum
C10,11	10μ tantalum 16V
C12	2,200μ 25V electrolytic

SEMICONDUCTORS

IC1	TBA820M
IC2	7812
Q1,2	ST1720 or equivalent
ZD1	6V8 400mW zener*
D1-4	1N4001

MISCELLANEOUS

FS1	500mA fuse and fuse holder
LP1	neon and current limiting resistor
LS1	50R 1/4W 2½in loudspeaker
T1	12V 6VA mains transformer
SW1	SPST mains switch

PCB*; case; knobs; mains flex; cable clamp; screened wire; adhesive pads.

* Components supplied free with this issue

this version and Fig.5 shows a suggested layout for the entire project.

For the prototype we used a case with plastic front and rear panels. It makes the drilling easier and saves the bother of earthing metal panels (which is important in mains powered equipment — even the best made project can go wrong!). The holes for the pots, switches, neon lamp and fuseholder were made by drilling small holes in the correct positions and then widening them out with a reamer.

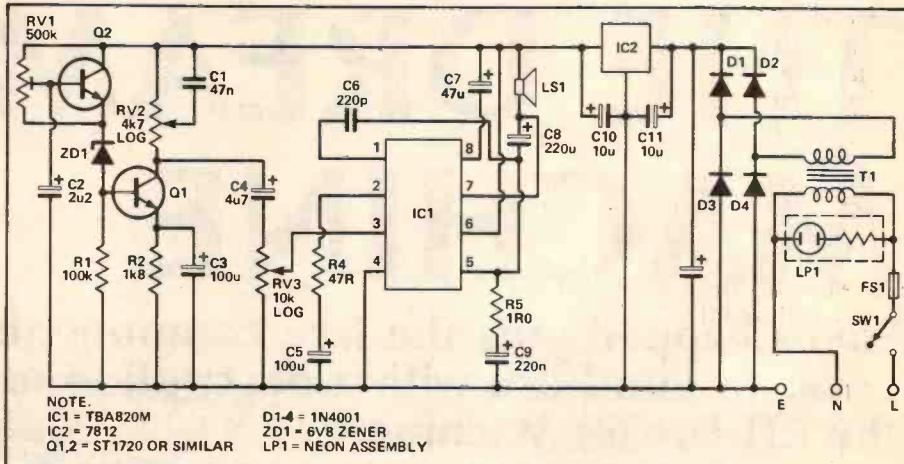


Fig. 3 The circuit diagram of the extended Dream Machine.

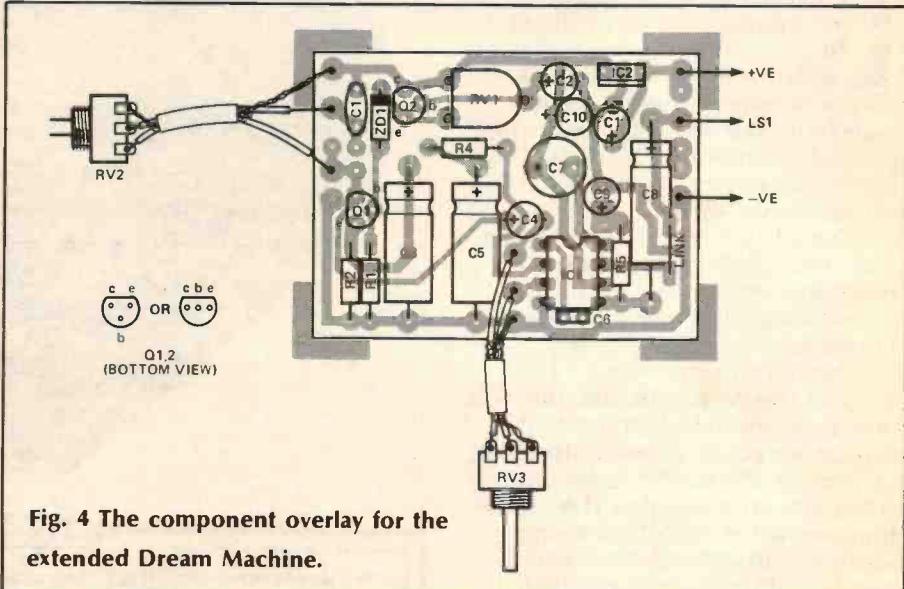


Fig. 4 The component overlay for the extended Dream Machine.

Reams And Reams

The reamer is such a boon and a blessing to mankind that I feel inspired to say a few words about it, just in case there are any beginners amongst you who are still hacking cases about with a kitchen knife.

A reamer is a gently tapered steel cone with sharp fluted protrusions (I don't know what that means but it sounds good!) The theory is that if you haven't got a drill bit of quite the right size, you can drill a hole to the next size smaller, put the reamer in the hole and twist a few times to widen it a little.

What really happens is that you sort through your drill bits, discarding the one that got bent in the tragic carpentry accident, the one that got stuck in the wall and now has a picture hanging from it and the ones that are too blunt to drill cheese until you are left with a single $\frac{3}{16}$ in bit. You drill every hole with this bit and widen them all out with a reamer! Full details can be found in the ETI

workshop manual, to be written as soon as I find my biro!

Reamers come in two types. Some have a handle like a screwdriver, others have a shaft with a hole in it. A bar through the hole gives enough leverage to tackle quite substantial thicknesses of metal.

Either type will munch its way through plastic at high speed but on thick sheets of aluminium the difference in blistering ratios and sore finger index becomes noticeable. Any of the larger electronics catalogues will have reamers in the tool section, so if you haven't already got one — buy one today!

Making a reasonable looking hole for a loudspeaker is always a problem. Some people drill rows of small holes and glue the speaker underneath. It works OK, but looks very home made. This might be a great selling point for Mr Kipper's cakes, but it's definitely to be avoided in electronics projects.

For this project I did the bare minimum of work to make it look

PROJECT: Dream Machine

reasonable. The 1½in hole was made with a hand operated sheet metal punch — the type with two halves that gnash together under the pressure of a nut running along a screw thread and take out a neat circle of plastic in the process. Underneath the hole is a piece of aluminium mesh from the local hardware shop and beneath this the loudspeaker is glued with araldite.

Araldite holds the mesh in place too. On another occasion I tried melting it into the plastic of the case but the mesh was such a good heatsink that the whole case was hot and soft by the time it started sinking in. The result looked something like Dali's liquid watches!

It surprises me that nobody seems to have thought of making a stick-on loudspeaker trim as a standard component. Perhaps they have and I just haven't come across it! Ideally it should stick to the top of the case and have very fine holes. That way you could make a complete pig's breakfast of the drilling without anybody ever knowing!

The transformer should be fixed to the case with suitable nuts and bolts. The smoothing capacitor can be glued to the case or held in place with a double-sided self-adhesive pad. The rectifiers are wired directly between the transformer and capacitor, avoiding the need for veroboard or another PCB for the power supply. Figure 5 shows two ways to do this depending on whether you choose a can type electrolytic or an axial type. Radial electrolytics can be wired in the same way as the can types, with the leads bent into a circle to give a little extra support to the solder joints. The rectifier leads should be insulated — you can use lengths of insulation stripped from the mains wire to do this.

Two double-sided self-adhesive pads will hold the PCB in place firmly — it's not heavy enough to break loose. Screened wire should be used for the connections between the PCB and the pots. The speaker connections can be made with ordinary connecting wire.

Testing

Before switching on, make sure there is a suitable fuse in the fuseholder and check the mains wiring carefully. Set the preset RV1 and both pots to mid position. Switch on the Dream Machine and if all is well you should hear a soft hiss from the loudspeaker.

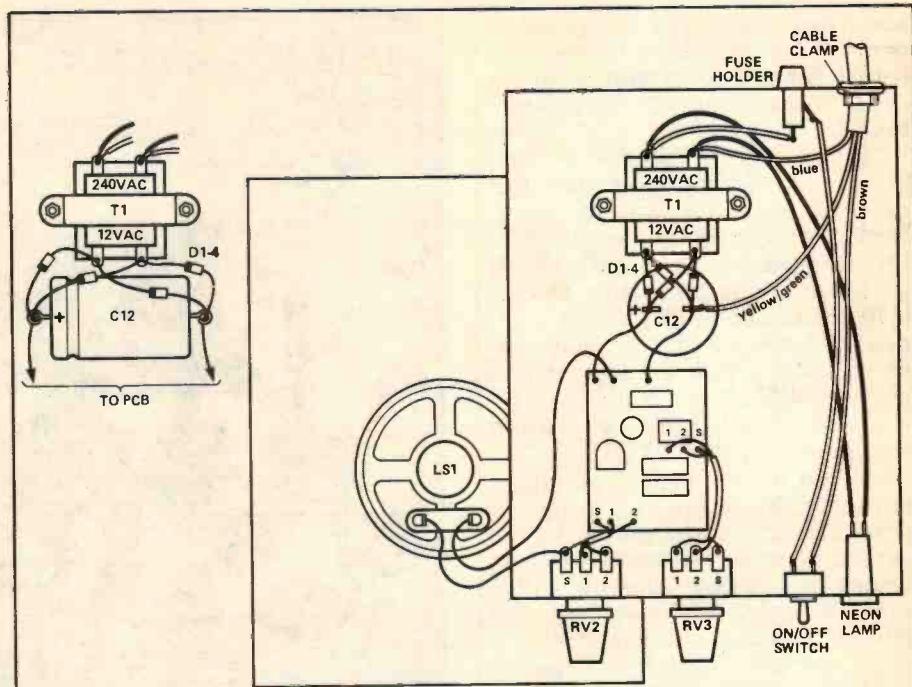


Fig. 5 Wiring up the extended Dream Machine.

If the speaker makes any other kind of sound, switch off immediately.

If there is no sound at all from the loudspeaker, check that the neon lamp is lit. If not, turn off and check the fuse and mains wiring again. If the neon is lit, check with a multimeter that there is about 17V across the smoothing capacitor C12. If not, check the power supply components — in particular, make sure the rectifiers are the right way round.

If all is well so far, check that there is a 12V supply to the PCB, regulated by IC2. The most convenient place to make this check is between the 'screen' connections of the two pots with the negative lead of the meter to the right-hand terminal of RV3 and the positive lead to the left-hand terminal of RV2.

The meter should register a voltage of almost exactly 12V. Too high a reading will almost certainly indicate a damaged regulator or a dry joint on the central pin of the regulator (IC2). Too low a reading and a very hot tab on the regulator will indicate either a solder short somewhere on the board or that IC2 is damaged. In either case, turn off before the circuit catches fire!

If all tests so far are OK, check that the regulator is running cool (the tab should be barely warm to the touch) and see if you can bring on the sound by adjusting RV1. Turn it slowly from one end of its travel to the other. If there is

still no response, touch a damp finger to the central pin of RV3. A loud hum in the loudspeaker will show that IC2 is working!

Any further testing should be carried out with the PCB removed from the case to avoid any possibility of contact with the mains wiring. If the 'finger test' gives no response from the amplifier, remove lead 1 (Fig.5) from RV3 and try again. If it still doesn't work, the amplifier section of the circuit is at fault.

Touch IC1 to see if it is getting hot. If not, you can make some voltage checks to pinpoint the area of the board where the trouble lies. Connect your meter between pins 4 and 6 of IC1 (- to pin 4, + to pin 7) and check that it reads 12V. Check that the voltage at the positive end of C8 is also 12V (if not, check the speaker connections).

Check the voltage at IC2 pin 5. It should be 6V. If not, short pins 3 and 4 of the IC together. If this cures it, check the connections to RV3. If the fault remains, leave the short in place and remove one end of C7 from the PCB. If this brings the voltage on pin 5 to 6V, C7 is faulty and should be replaced. If not, replace the C7 connection and remove one connection of C5. Once again, if this cures the fault, replace C5; if not, put the connection back. Do the same for C6.

If none of this works, you can reasonably conclude that IC1 has been damaged and replace it. If you are not entirely confident

PROJECT: Dream Machine

about your soldering technique, it would be a good idea to use a socket for this IC, which is the most delicate component on the board.

If the amplifier section of the board is working (finger hum, but no hiss), check the voltage between collector and emitter of Q1. This should be at least 1.5V. If it's more, it doesn't matter. If it's less, try adjusting RV1. If this doesn't bring it into line, solder a 4k7 resistor across the terminals of RV2 (between S and 2 in Fig.5). If this doesn't help either, check the voltage across R2 and C3.

When the circuit is working correctly, this should be in the region of 2.5V and should vary according to the setting of RV1. Check this out by adjusting RV1. If there is no change in voltage, check the voltage across ZD1 (if that's not 6.8V, the zener is faulty) then the voltage at the emitter of Q2. If this doesn't change as RV1 is adjusted, suspect RV1 or Q2. If it does, but Q1 emitter voltage doesn't, suspect Q1.

The resistor soldered across RV2 can be left in place if it helps. The short between pins 3 and 4 of IC1 should be removed as soon as the tests on IC1 are completed. When all is working, adjust RV1 carefully for maximum volume, then fasten down the lid of the case and prepare for some dream experiences!

Living With Your Dream Machine

Last month I mentioned several dream experiments but I suspect many people will build this project simply with the intention of helping themselves or their family to have a deep, refreshing sleep. The Dream Machine seems to work particularly well with young children who have troubled nights and this in itself can help the rest of the household to have an unbroken sleep!

With the Dream Machine by your bedside, adjust the volume and depth controls to suit your mood, then lie back and concentrate on the sound. After a while it will start to become almost hypnotic. Constantly changing, yet always the same. (How's that for a Zen paradox?) Very soon you will find yourself being carried away on waves of sound until you have no choice but to drift into a deep, relaxing sleep.

One of the many paradoxes of sleep is that it is not always a time of relaxation. You notice this in yourself by finding it difficult to



get up in the morning — you stumble out of bed still half asleep and feeling as if you've spent the night doing *Circuit Theory* problems or wrestling with alligators. In others it shows itself by restless movements — kicking off the bedclothes, muttering and thrashing about, snoring and grinding teeth.

Morning is the time you really notice having the Dream Machine. When you wake up and actually want to get out of bed, when you feel bright and alert and when you don't fall asleep on the way to work, you know you've slept properly. It can be quite an astonishing experience the first few times it happens!

Once you've got used to having the Dream Machine by your bedside, you can concentrate on some of the dream experiences I mentioned last month. Lucid dreams, where you have complete control over your dream actions, can be very exciting. Just think of all the things you've ever wanted to do... then go ahead and do them! You can't die of dreaming or be arrested for it. Nobody will gossip about it because only you will know!

The only way to bring on a lucid dream is simply to decide to have one. This is easier than it sounds. The chances are that after a few nights you'll find yourself in the middle of a dream and think to yourself 'I'm dreaming. I can do

anything I like!'

Surprisingly enough, this is most unlikely to wake you up. You'll probably find at first that you can keep control for a few minutes at a time before forgetting what you're doing and drifting back into a normal dream. With a bit of practice you'll be able to keep it up for longer and longer. The experience is likely to be on the surreal side — if your ambition is to rob a bank, you may find yourself removing sacks of eels or doughnuts from the vaults. Never mind. Try again tomorrow night!

ETI

BUYLINES

All components for this project are readily available from any component supplier except possibly for IC1. If you have difficulty in obtaining this component it can be supplied by Specialist Semiconductors for £1 inclusive of postage and VAT (see the ad in this issue). A complete parts set including case, transformer, and all fittings and components, to expand the free gift components into the complete Dream Machine will be available from our Readers Services department. Look out for the ad in this issue for full details.

If you missed last month's issue and your free PCB, you can obtain a copy (if you're quick!) by sending £1.90 to Infonet Ltd., Unit 5, River Park Industrial Estate, Billet Lane, Berkhamsted, Herts HP4 1HC. Please be sure to let them know it's ETI you want, and tell them which issue.

ELECTRONIC VIOLET

Ronald Alpiar describes a novel instrument of the violin family you can build yourself.

Now that electronics and computers have so astronomically broadened our musical horizons, it may be time to pause for a moment and consider what we really require of that elusive creature, the ideal musical instrument. Maybe we should ask ourselves whether the almost ubiquitous keyboard is really the only, or even the best answer to a musician's prayer?

This article will introduce readers to a novel breed of musical device which can be constructed by the average handyman at trifling cost — given a BBC micro with the Music 5000 add-on.

A host of desirable qualities might be required of the ideal musical instrument, ranging from beauty of appearance to low cost. Concentrating on purely musical factors I'd narrow it down to three criteria — Ease, Versatility and Intimacy. Let's consider these in turn.


Ease

The instrument should not be so insuperably difficult to perform as to deter all but the most stouthearted. It should be possible to acquire a commendable technique without superhuman effort, and demand no rare inborn gifts of the performer. Portability may also be a consideration — past are the days when every household boasted a piano in its parlour!

At the same time the opposite extreme should also be avoided (an instrument which requires absolutely no training or practice) since these disciplines are needed to develop musicianship as well as technique.

Versatility

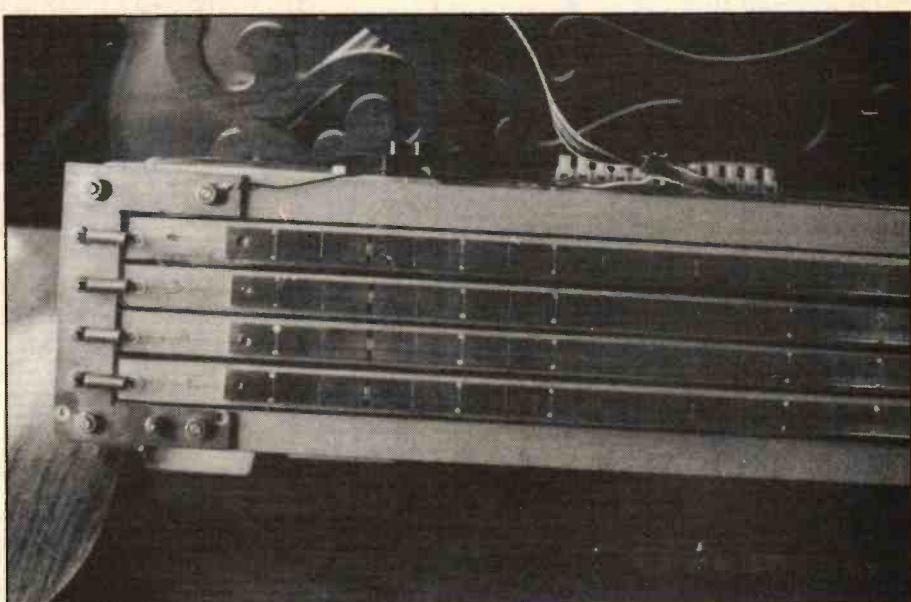Monotony being the enemy of music, the ideal instrument should be capable of producing a wide range of sounds. This



versatility should include everything from sublime beauty to discordant harshness. It should not only cover the full range of audibility but also be capable of dynamically altering the volume and timbre of a note whilst it is sounding — not merely when it commences. The full range of audible frequencies should be available and every variety of waveform and envelope should be at the performer's command.

Intimacy

Anyone who has thrilled to the performance of Tortellier on the cello or of Julian Bream on the guitar will understand what is meant by intimacy — a mystic marriage between the musician and his instrument.

The performer's movements should be appropriate to the sounds produced — just as if he were conducting an orchestra. Control of sound by the breath is perhaps the most intimate medium — reaching its height of expressiveness in the human voice. Next comes the pressure of fingers and the stroke of the arm.

Least intimate of all is the control of sounds by adjustment of knobs, dials, levers and switches. The tendency of more advanced electronic keyboards to incorporate touch sensitivity, despite formidable electronic problems, shows how much importance is attached to the intimacy factor.

So how well do some common instruments measure up to these three criteria? Our comparisons begin with the piano. The instrument is relatively easy to play and the stance comfortable and relaxed. Singlemindedness alone is all that is required to acquire a formidable technique. Touch sensitivity in the keyboard enables individual notes to be accented, rhythms to be established and phrases to be moulded so a fair measure of intimacy is provided, which both organ and harpsichord lack. But this has to be paid for. A pianist must spend many hours of laborious practice to ensure that his audience is not constantly reminded that the thumb is intrinsically more powerful than the little finger!

Many musicians regard the human voice as the most intimate of musical instruments and even a model for other instruments to copy. Unfortunately excellence is within the reach of only those born with exceptional architecture of the vocal cavities and even these favoured few are not excused years of hard training.

If we allow our survey to extend to imaginary instruments, we may turn to the human brain itself. Given careful feedback training some conscious control of the brain's natural EEG rhythms is possible. With the brain's electrical activity interfaced to an audio output device, perhaps one could train oneself to actually *think* music in all its detail without moving a muscle! Presumably this would be the ultimate intimacy. Even if it were possible, control of this instrument would demand mental training at least as intensive as the physical disciplines needed to master any real instrument of music.

Let's come back to earth with the violin family — the violin, viola, cello and bass. Perhaps no other sound can rival the haunting beauty of the violin's G-string played in the upper positions or the voluptuous vibrato of the violoncello. Continuous pitch control provides for vibrato glissando and portamento, all under finger control. The bowing action gives dynamic control of both timbre and volume whilst a note is sounding. Besides this, a number of finger and bowing techniques give added variety: 'pizzicatto', finger harmonics, 'spiccato' (bouncing bow on strings), 'ponticello' (the unearthly sound produced by bowing very close to the bridge), 'col ligno' (playing with the wood surface of the bow rather than with the hair surface) are merely a few special techniques exploited in the instruments' repertoire.

This versatility is bought at a great price. For all its natural appearance under a master's chin, the very stance of violin playing is awkward. Aching arms, sore finger tips, a ricked neck or a locked shoulder can be the first rewards of over-zealous practice. It can take at least a year to learn to produce just one single sustained lovely note!

The very fact that (unlike the piano) the violin is capable of continuous — or analogue — frequency control also makes it all too easy to play out of tune.

INSTRUMENT	EASE	VERSATILITY	INTIMACY
BRASS	♩ ♩ ♩	♩ ♩	♩ ♩
GUITAR	♩ ♩ ♩	♩ ♩	♩ ♩ ♩ ♩
HARP	♩	♩ ♩	♩ ♩ ♩ ♩
HARPISCHORD	♩ ♩ ♩ ♩	♩	♩
ORGAN	♩ ♩ ♩ ♩	♩ ♩ ♩ ♩	♩
PERCUSSION	♩ ♩ ♩ ♩ ♩	♩	♩ ♩
PIANO FORTE	♩ ♩ ♩ ♩	♩ ♩ ♩	♩ ♩ ♩
SYNTHEISER	♩ ♩ ♩ ♩	♩ ♩ ♩	♩
VIOLINS	♩	♩ ♩ ♩ ♩	♩ ♩ ♩ ♩
VOICE	♩ ♩	♩ ♩	♩ ♩ ♩ ♩
WOODWIND	♩ ♩	♩ ♩	♩ ♩

Fig.1 Instrumental league table.

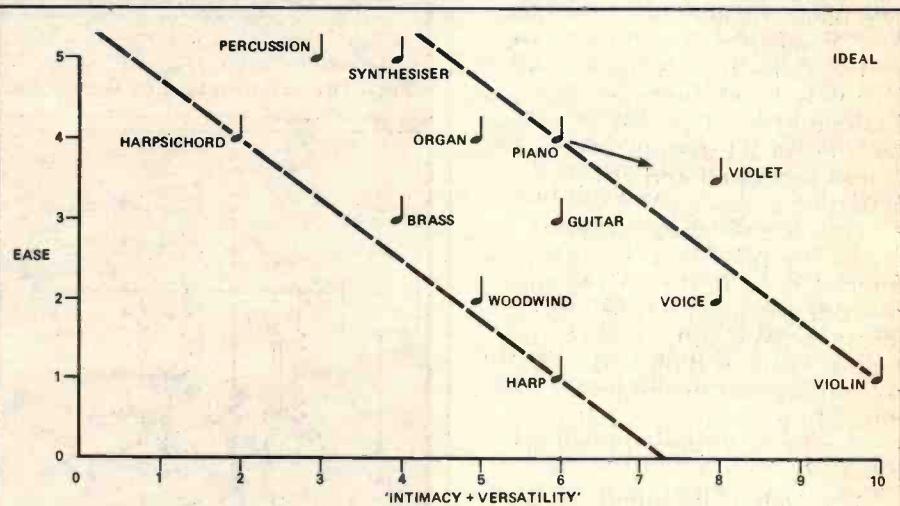


Fig.2 Instrument performance

There are no physical guidelines on the fingerboard. Worse still, the fingerboard's scale is not even linear!

The viola is if anything even more cumbersome than the violin, whilst handling the bass demands some of the qualities of an Olympian athlete. Of the entire family the cello (author's favourite) is the most forgiving and user-friendly. The above mentioned single note can be produced in months rather than years!

By now it is becoming clear that our three cardinal criteria of Ease, Versatility and Intimacy are at odds with each other. An improvement in any one of them appears to bring penalties for the others. The League Table (Fig.1) is of course highly subjective and likely to draw howls of protest. However I believe that the ratings are broadly correct. If we plot Ease against the sum of (Versatility + Intimacy) (Fig.2) existing instruments appear to lie in a diagonal band delimited by the two broken lines, with the ideal instrument well out of bounds.

Maybe we can accept a compromise. I would be willing to consider an instrument which was a *little* harder to play than the piano, provided that it offered continuous pitch and dynamic amplitude under finger control: but only if it were much easier to play than a cello. The arrow in Fig.2 represents the direction we'd like to move.

These were the thoughts back in the pre-home-computer days of the 1970s when the Electronic Violet (now the flower of nearly a decade of design and development) was conceived. Its design requirements can be stated quite simply:

- A horizontal instrument to be played with both hands in a comfortable, seated position.
- Continuous pitch and amplitude under finger control.
- A linear scale.
- The ability to emulate the performance of each member of the violin family and to address its entire repertoire.

Mechanical Design

Figure 3 illustrates the basic design of the Violet. A resistance wire (called the 'string') is stretched taut above, but not quite touching, a horizontal conducting bar (the 'plate'). The left end of the string is earthed, and its right end is maintained at a stabilised, smoothed voltage V_u (upper voltage). Being of uniform section, the voltage at any intermediate point along the string will vary linearly between 0 and V_u . The instrument is played by pressing the string down onto the plate with the fingertip at some point where the string's voltage is say V_p (pitch voltage). The plate voltage then rises from its idle value of 0V to V_p . Both V_u and V_p enter the BBC micro via channels 1 and 2 of the 4-channel analogue port. The ratio V_p/V_u will be used to set the pitch of the sound produced and also to activate gating.

Fine scribed parallel lines across the plate indicate semitone intervals, and further marks may be added to assist the eye to locate octaves, fifths and fourths. Indentations or bumps on the plate (provided they don't interfere with String contact) can be used to aid finger positioning by touch.

The plate is mounted on an insulated wooden lath which floats on a pair of pressure pads at each end. Increasing finger pressure compresses the pads and reduces their electrical resistance. This resistance is converted to a voltage and enters the micro via analogue channel 4 where software converts it to sound amplitude. Both pitch and volume are under dynamic finger control enabling melodies to be played with expression, notes to be accented and finger tremolo to be used.

There are four parallel strings, each with its own independent plate. The four plates are each mounted independently, activating its own pair of pressure pads. In this form the Violet is capable of playing polyphonic music (with up to four voices) opening the door to almost the entire instrumental repertoire.

Interfacing

Before the advent of the home computer, Violet's pitch and amplitude voltages were fed to a bank of four independent exponential-law VCOs and four VCAs. Additional circuitry was used to control gating, to adjust

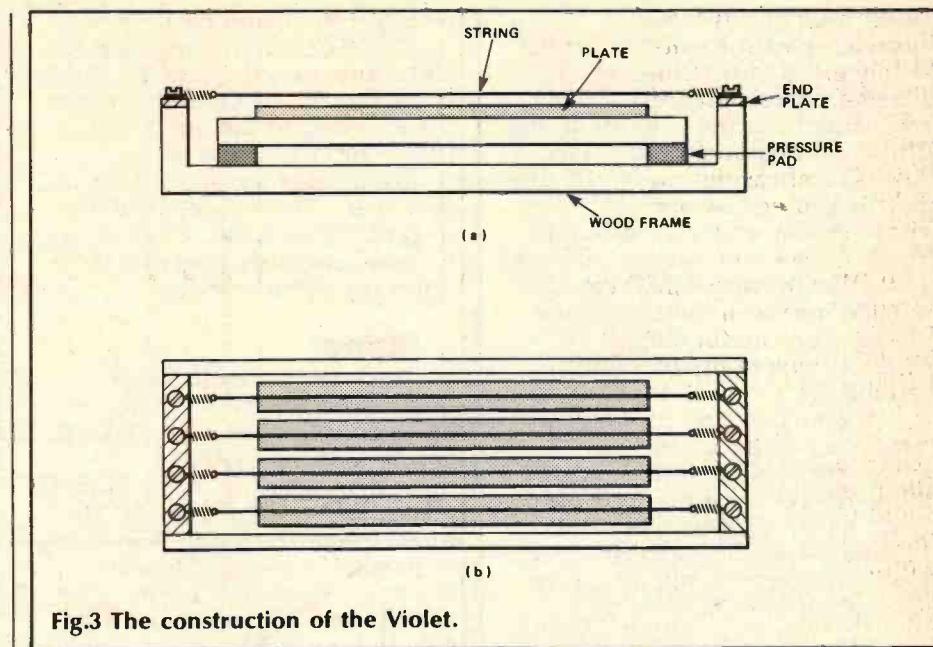


Fig.3 The construction of the Violet.

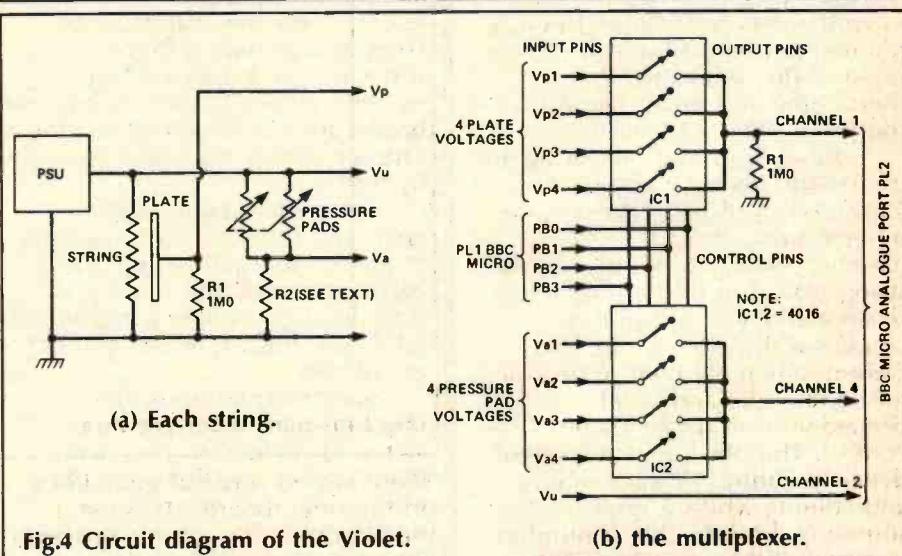


Fig.4 Circuit diagram of the Violet.

PARTS LIST

RESISTORS (1/4W 5%)

R1,11,21,31	1M0
R2,12,22,23	see text

SEMICONDUCTORS

K1,2	4016
PL1	20-way IDC plug
PL2	15-way D connector

MISCELLANEOUS

PCB or stripboard; pressure pads; plates; wooden frame and laths; resistance wire; springs; end plates; ribbon cable; nuts and bolts.

needed to give a voltage somewhere between 1.5-1.75V for V_u (Fig. 4a). The analogue input accepts voltages between 0-1.8V. The actual voltage chosen for V_u is not critical since pitch is determined by voltage ratios V_p/V_u rather than by absolute values. A value of V_u close to (but not exceeding) 1.8V will improve digital-to-analogue conversion accuracy.

Figure 4a shows the connections of power supply, strings and pressure pads diagrammatically. It will be seen that three of the analogue port's four channels are used up with a single string. The multi-string Violet is interfaced by multiplexing channels 1 and 4 as Fig. 4b shows. Each 4016 is simply a bank of four independent single pole switches, each switch activated by its own control pin.

One 4016 multiplexes the V_p from each string to channel 1, the

string voltages (and hence tune the instrument) and provide tone control. However, most of this elaborate circuitry can be replaced by the BBC micro.

A smoothed power supply is

other multiplexes the four pressure pad voltages to channel 4. Since the four strings are in parallel, V_u can proceed straight to channel 2 without multiplexing. The control pins are connected to bits 0-3 of the 8-bit user port. The port is programmed to continuously change the output states of the four lower user port bits so as to repeatedly scan the voltage messages from the four strings in turn. The whole interface can easily be built on stripboard.

Of course, using this system the Violet could simply be extended to eight strings. With some decoding of the user port lines, 64 strings could be used. However, speed of software and dexterity suggest four strings as the optimum number.

Physical Dimensions

An optimum set of physical dimensions has evolved after much trial and error. The distance between semitones on the Plates is fixed at $\frac{3}{4}$ in. This is roughly the maximum distance between centre lines of two adjacent, almost touching fingers of one hand. So adjacent semitones can be played without the fingers getting in each others' way.

The plates are $\frac{1}{2}$ in x $\frac{1}{8}$ in cross section smooth plane aluminium bars, well polished on the upper surface to ensure clean electrical contact. It is important that the upper surface of the plates do not bend under finger pressure. Each is therefore screwed down onto a planed, seasoned wood lath of $\frac{3}{4}$ in cross section. Strips of copper clad, fibreglass backed circuit board can be used as a substitute for aluminium bars. Each plate is 30in long and so encompasses a full three octaves plus an extra full tone at each end.

The strings extend about 3in beyond the plates at each end. This dead space is necessary, otherwise it would be hard to play lowermost and uppermost notes. The lower deadspace also has a useful gating function. The software can be considerably simplified if the electrical length of the strings is precisely 48 semitones = 36in. An inch or two of loose resistance wire above the rightmost end of a stretched 35in String can be used to trim its effective length. Each string is poised about $\frac{1}{8}$ in above its contact plate. Too large a separation would require either a slack string or too much finger

pressure to ensure clean contact.

However if the strings are too close to plates, the precise contact point can be affected by minute irregularities in the string or upper surface of the plate.

The strings are spaced about $\frac{3}{4}$ in apart. This enables the four fingers of one hand, if necessary, to simultaneously play nearby notes on all four strings.

Strings

The strings should be of uniform resistance wire, free of kinks and notches. I use 34SWG Karma wire (Ni-Cr-Al-Mg quaternary alloy). It has a nominal resistance of 9.52ohms/foot. The total resistance of four 36in strings in parallel is about 7.14ohms. Given a potential of up to 1.8V across the String array, the PSU should be capable of delivering at least $\frac{1}{4}$ A for the strings alone. Finer strings have a higher resistance and demand less current. However, they may be harder for the fingertips to locate. Thicker strings are easier to find by touch.

The contact plates are anchored to 0V via 1MΩ resistors to ensure that idle strings are at earth potential. The resistor is large enough to have a negligible effect on linearity when strings are played.

The construction of the pressure pads gives plenty of scope for ingenuity. Pieces of foam rubber moistened in brine work quite well but require regular 'watering' in dry weather and may eventually cause corrosion. Conductive foam used to protect CMOS ICs may also be used. Its slight noisiness under pressure changes can be eliminated by a $1\mu\text{F}$ electrolytic in parallel. At present 1/10in thick pads of a carbon fibre impregnated substance (used in digital weighing machines) are employed. Its resistance varies from about 1000 to 100ohms/cm².

Whatever pressure pad material is chosen, it is important that the amount of actual vertical plate movement be minimal. The material should be pressure rather than compression sensitive. It is much easier for the fingers to play steady plates, than ones which keep on bobbing up and down.

The two pads at the extremities of each plate, mounting bar are wired in parallel. This helps to ensure touch sensitivity is fairly uniform over the length of the plates. The pads are connected between V_u

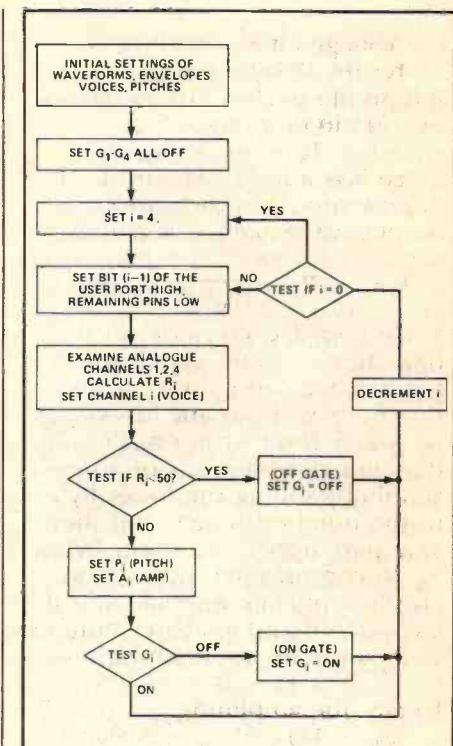


Fig.5 Flow diagram of the Violet software.

and 0V via a loading resistor R_2 . Its value is not critical, something roughly equal to the combined pad resistance at mean pressure will do. The degree of touch sensitivity is in any case under software control, so wide variations in component values can be allowed for.

The PSU should be capable of delivering 1.8V or less at a maximum of 1A giving generous margins to supply strings and pressure pads. It should also provide for a few mA at about 10V (not critical) to power the switching ICs.

Software

The program which operates Violet has to perform a number of tasks:

- Ensure that $\frac{3}{4}$ in movement on the plates = 1 semitone
- Set relative and absolute tuning of the strings
- Set up suitable envelopes and waveforms
- Repeatedly scan plates in turn and convert pitch and pressure pad voltages into sounds and at the same time manipulate appropriate gates when a string is initially played or released.

The author's program was written in the Music 5000 programming language, Ample. The overall flow diagram of the software is shown in Fig.5.

We have already decided that

the voltage change $0V_u$ should represent 48 semitones ($48 \times 16 = 768$ Ample pitch units) so the pitch ratio of a plate:

$$R_i = 768 \times V_{p_i} / V_u$$

Since it is a little awkward to do double precision division in Ample, we actually calculate R_i so:

$$R_i = \frac{(V_{p_i}/8) * 3}{(V_u/8)/256}$$

Since the ADC converter in the BBC micro is only significant to ten bits, we can ignore the last three bits without any loss of accuracy. The division of the denominator by 256 is performed simply by setting the lower byte of the number to zero and then swapping upper and lower bytes.

To convert pitch ratios R_i to absolute pitches we must add the base pitch B and as many multiples of S as we are above string one:

$$P_i = R_i + B + (i-1)*S$$

Finally, the amplitude:

$A_i = 128 + F^*(V_{ai} - M/1000)$ where M is the voltage from the pressure pads corresponding to an amplitude of 128.

However the formula has to be slightly modified to suit Ample's arithmetic. What is actually calculated is:

$128 + (F/10)*(C4/455 - M/100)$ where C4 is the output of analogue channel 4, normalised to an integer in the range 0-8192.

Gating the sounds produced by Violet ensures that notes start and end in a natural way and it is also used to remove any noise caused by uncertain contact when any string is initially depressed and finally released. Gating does not take place when a succession of notes are played on the same string without releasing it.

To perform gating we have to know whether any string is currently active (in contact with its plate) or idle. The plates are anchored to 0V via a 1MΩ resistor when idle and to the left of each plate there is a deadspace of about 3in (four semitones = 64 Ample pitch units).

To test whether a string is active or idle it is sufficient to test whether R_i lies between 0 and 64. Allowing for some margin of error in the ADC conversion, in practise we test for $R_i < 50$.

The complete Ample program is given in Listing 1.

Performance

As with any instrument, the player must practise to perform well on Violet. The first difficulty for newcomers is to learn to locate the strings by touch rather

```

"POW2" [] "USER" [] "QUSER" []
"ALOG" [] "R1" [] "GF1" [] "GF2" []
"GF3" [] "GF4" [] "Base" [] "Sep" []
"MV" [] "Fv" [] "Pi" [] "Ai" []
"Sel" [] "GSOFF" [] "LOOPN" []
"Ns" [] "INIT" [] "PORT" []
"CYCLE" []

"POW2" [1 #12 -1 #+ FOR(2 #*)FOR]
"USER" [256 ## &60 ## &97 &FFF4 CODE #2
#2]
"QUSER" [&FE60 #B!]
"ALOG" [&80 &FFF4 CODE #2 &8000 ## 8 ##
#2 4096 #+]
"R1" [1 ALDG 3 ## 2 ALDG &FF00 AND &B12
# #2]
"GF1" [GVARJ
"GF2" [GVARJ
"GF3" [GVARJ
"GF4" [GVARJ
"Base" [GVARJ
"Sep" [GVARJ
"MV" [GVARJ
"Fv" [GVARJ
"Pi" [1 # Sep #? ## Base #? #+ #+]
"Ai" [4 ALDG 455 #/ #2 MV #? 100 #/ #2
#- Fv #? 10 #/ #2 ## 128 ##]
"Sel" [#11 2 #> IF(3 #)
IF(GF4)ELSE(GF1)IF)ELSE(1 #
IF(GF2)ELSE(GF1)IF)IF]
"GSOFF" [OFF GF1 #! OFF GF2 #! OFF GF3
#! OFF GF4 #!]
"LOOPN" [Ns #?
FOR(INDEX VOICE
INDEX POW2 USER
INDEX SEL
Ri #11 50 #
IF(OFF GATE #2 OFF)ELSE(
INDEX Pi PITCHF
Ai AMP
#11 ON #12 #? OFF #-
IF(ON GATE)IF
)IF
#12 #!
)FORJ
"Ns" [GVARJ
"INIT" [SOUND #11 Ns #! VOICES -400 Base
#! 112 Sep #! 1000 MV #! 200 Fv #! GSOFF
PORT CYCLE]
"PORT" [&62 &2711 #B!]
"CYCLE" [REP(LOOPN)REP]

```

Listing 1 The Ample Violet program.


than by eye but this skill is surprisingly rapidly acquired.

Finger pressure and vibrato and tremolo finger-tip motion must be practiced. The note sounded can depend both on speed of attack and pressure variation whilst it is being sustained.

Perhaps the main difficulty is inherent in Violet's originality. Unlike established instruments, there is absolutely no body of traditional techniques to guide the learner, no virtuosos or teachers for him to emulate by example. Even the simplest decisions have to be made by you the player. Should you use your thumbs or not? Should the instrument be placed with the lowest sounding string nearest or furthest from the body? Should the plate surfaces be horizontal or tilted? What is the best way of deploying the two hands in difficult passages? All this is till virgin territory, in which each explorer must establish his own familiar acre and homestead.

Other Scales

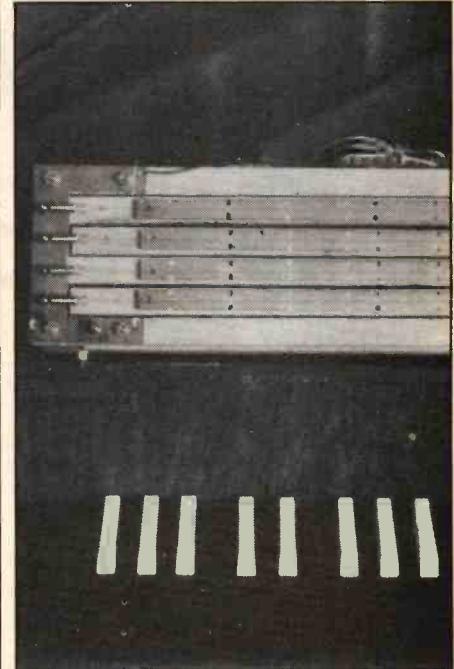Almost all Western music is played on an equally tempered scale of 12 semitones to the



octave. This means the pitch ratio of successive semitones is the irrational number $2^{1/12}$. The equally tempered scale is a compromise, which enables music in all keys to be played equally well (or badly).

Ideally successive notes should have frequency ratios of simple fractions, so that chords sound pleasant to the ear. It is mathematically simple to 'retune' the musical scale to one of the 'perfect' pitches, which prevailed before the equally tempered scale was invented. This enables certain Baroque and Liturgical music to be heard as originally intended.

At the other extreme, the standardisation to a 12 note scale has also been called in question. A very thriving school of music with origins in Holland is based on an equally tempered scale of 31 notes to the octave. Music written in this mode has a strange beauty. Again, it is very simple to retune Violet to this type of scale.

So far we have considered an instrument with different strings tuned to different pitches. However they might be all tuned to the same pitch but differ in sound quality, attack characteristics, or even stereo positioning. The potential is all there.

This version of the Violet relies heavily on the BBC micro, the Music 500 and the Ample language. However, many budding Violet players may not have this equipment. Indeed the original Violet was developed as a stand-alone instrument. Next month I shall describe how that universal instrument can be built.

SWR AND POWER METER

Andrew Armstrong delves into the depths of aerial matching and designs an SWR meter that leaves other waves standing.

Many people swear by their SWR meters, some people swear at them, but few understand what they really do. I am going to try and unravel what SWR represents and what it does, as well as describing the construction of a stylish SWR indicator intended primarily for CB use.

It is also very suitable for use with 2m transceivers of a few watts output, widely used among radio amateurs. Just one component change is needed to give an accurate 2m SWR indicator.

In using a transmitter it is important to transfer as much of the transmitter's output power as possible to the antenna. The SWR indicator can help achieve this by indicating when the aerial is matched to the feeder.

Power Transfer

To understand why correct matching is important, we will first consider the simple case of a DC voltage source with a source resistance feeding into load resistance, as shown in Fig.1.

Under what conditions does the load receive the maximum power? Common sense tells us that if the load resistance is infinite no current flows and no power is transferred. Equally, a zero load resistance would allow plenty of current to flow but all the power would be dissipated in the source resistance. Starting from the formula:

Load power = $I^2 \times R_L$
the following reasoning applies:

$$I = \frac{V}{R_s + R_L}$$

$$\text{Power} = \frac{V^2 R_L}{(R_s + R_L)^2} = \frac{V^2 R_L}{R_s^2 + R_L^2 + 2R_s R_L}$$

$$\text{and if } R_L = R_s \text{ then: Power} = \frac{V^2}{3R_s}$$

If you want to get fancy about it you can differentiate this formula and look for a maximum (at which point the differential



will be zero). Alternatively you can apply intuition and say that by symmetry it seems that the maximum occurs when $R_L = R_s$.

Calculating the power with some sample values corroborates this. Try $R_s = 50$, and calculate $R_L = 49$, $R_L = 50$, and $R_L = 51$.

The same reasoning applies to power transfer using alternating current, even at radio frequencies. The best efficiency occurs, for example, when a transmitter rated at 50ohms output impedance is connected to an antenna matched to 50ohms with a piece of cable having a characteristic impedance of 50ohms.

The analogy with the DC situation is not perfect. The source impedance need not dissipate the same power as the load or indeed any at all. The impedance refers to a relationship between voltage and current given by the ratio of capacitance and inductance.

Line Impedance

In the case of the coaxial cable, the impedance is the same as the apparent electrical resistance which would be experienced momentarily if a voltage source were connected to the end of a long piece of cable. In Fig.2, if the switch is closed the voltage source charges the inner to outer capacitance of the first infinitesimally small part of the inner core, building up a magnetic field and charging the next part of the cable.

The inductance of the inner prevents the whole of the cable capacitance from charging immediately so it is the value of capacitance compared with the inductance per unit length of cable which will determine what current flows per unit applied voltage. The higher the capacitance, the higher the current.

The current flowing into the cable remains constant for a time.

When the cable is charged to the supply voltage all the way to the end, the current continues to flow in at the beginning just as before. The cable charges to double the supply voltage at the far end and continues to charge to this voltage until the charging point reaches the beginning.

Then, and only then, does any equipment connected to the sending end of the cable get to know about what has happened at the receiving end.

Now current flows back into the voltage source and keeps on flowing until the whole cable has discharged to zero voltage, whereupon the whole thing starts again. That is to say that it would if it were not for the resistance of the cable. Instead of setting up a perpetual system of waves bouncing back and forth, the resistance of the copper wire damps the ringing and the cable settles down to being charged to the source voltage.

The important thing is that until the first ring reaches the sending end of the cable, there is a fixed relationship between the applied voltage and the current which flows. This is exactly what resistance is and the figure measured in ohms is referred to as the characteristic impedance of the cable.

It is that value which, if connected as a resistance at the end of the cable, would have just the same relationship between current and voltage as the cable, so that the source current could flow forever without it being possible to determine from the sending end whether there was a resistance at the far end of a short cable, or instead an infinite length of cable.

This is obviously of no consequence when DC is flowing because whatever the load, it will settle down soon enough. If an alternating current is applied, of such a frequency that the cable represents a significant fraction of a quarter wavelength at the speed of propagation of the wave in the cable, then the matching of the load is important. Instead of having a steady voltage which will settle down in time, the voltage at the sending end is constantly changing and waves are constantly being reflected from the end connected to the load. If the load has the wrong resistance, or is partly inductive or capacitive, then reflection from the receiving end will take place.

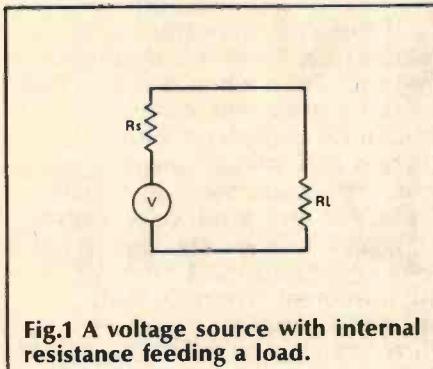


Fig.1 A voltage source with internal resistance feeding a load.

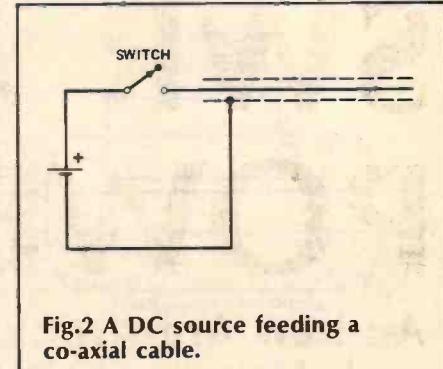


Fig.2 A DC source feeding a co-axial cable.

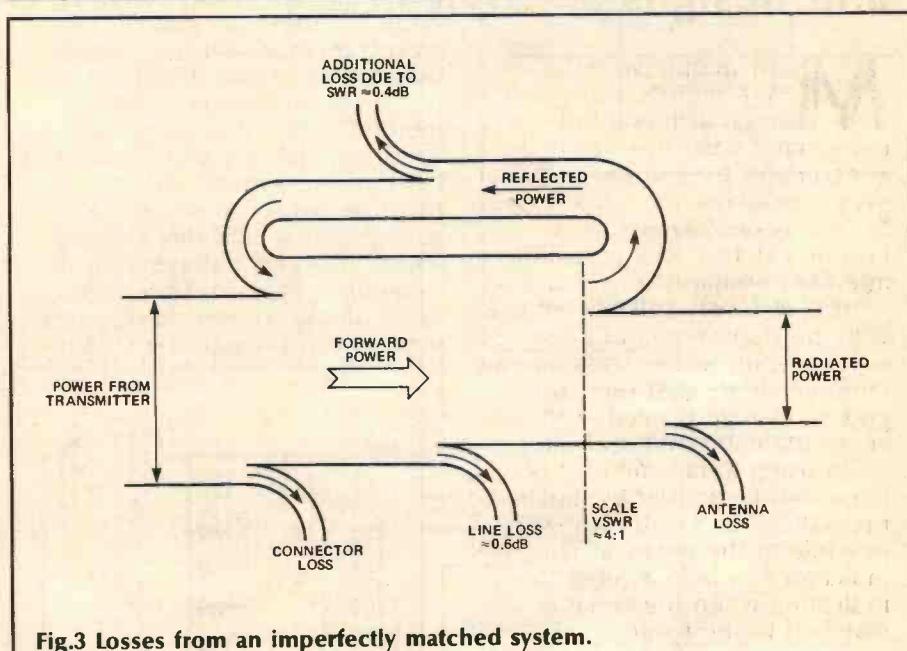


Fig.3 Losses from an imperfectly matched system.

Transmitters

If the signal source includes a resistance equal to the impedance of the cable, the reflected signal will be absorbed in this resistance and wasted. However, most transmitters do not behave like this. Some of the power returned will be absorbed in the output stage but most will be reflected again, back towards the load. The main effect is to increase the peak currents and voltages in the transmitter output stage and risk damaging it.

In this situation, you would expect that in the end most of the transmitter power would reach the load and (if the load was an antenna) be transmitted.

There are two reasons why this is not the case. The first is that there is a loss in the cable as the signal passes through it, both because of the resistance of the copper wire and the dielectric loss. The more passes through the cable made by the signal, the greater the loss. The other reason is that most modern transmitters incorporate circuitry to protect the output stage by turning down

the power if too much reflected power reaches the transmitter output.

A moderate amount of reflected power will not discommodo the transmitter. If the load matching is reasonable but not perfect then the situation will be as illustrated in Fig.3. The extra loss due to imperfect load matching is very small provided the cable loss is not too large. On the other hand, if the loss is significant then the reflected power measured at the transmitter will be less than that measured at the aerial and the system will appear better than it is.

Standing Wave Ratio

If the antenna is perfectly matched, the voltage and current in the coaxial cable are just as they would be in a resistor. That is to say the current is in phase with the voltage. If the matching is poor and reflection is taking place then standing waves are set up in the cable in the manner illustrated in the thought experiment of Fig.2.

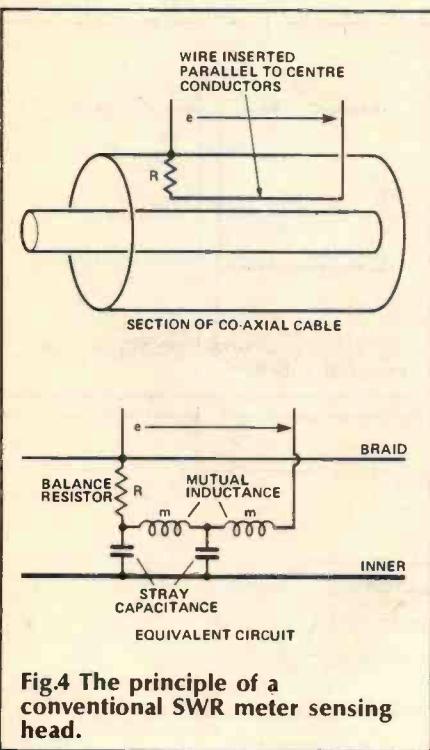


Fig.4 The principle of a conventional SWR meter sensing head.

subtraction will give zero.

If the SWR indicator is calibrated to achieve this double or quits situation when no reflection is taking place, the different amplitude and phase of the current and voltage waveforms when reflection takes place will upset this and produce a reading.

Figure 4 shows the traditional form of pickup used for SWR measurement. There is both inductive coupling to detect current and capacitive coupling to detect voltage. If the resistance value is chosen accurately, this pickup method will only detect power flow in one direction.

The disadvantage of this method is that it is frequency sensitive. The use of a broadband current transformer and a resistive divider to provide a voltage signal provides a system which is largely independent of frequency. This principle is used in the design of the sensing head used in this project, the circuit

By the same token, the voltage across R1 and R2 is not very large and the forward voltage drop of ordinary silicon diodes would prevent any reading from being obtained at moderate power levels.

To enable the unit to work at the power levels encountered in legal CB equipment, low capacitance Schottky diodes are used to rectify the RF output. Even with Schottky diodes to rectify the RF, the efficiency of the detection circuit is lower at power levels under about 0.5W, so that measurement of SWR with the CB transmitter switched to the low power position is not accurate. This should not be a problem, though, because the SWR of an antenna will not change when the power is reduced, so if it is OK on high power it will be OK on low power too.

Capacitive Shield

To prevent the current transformer from picking up a voltage signal capacitively, the toroidal transformer is slipped over a piece of co-axial cable, with the braid still intact. The braid is grounded at one end so that it provides capacitive shielding. The other end is left unconnected. If it were connected it would form a shorted turn and prevent inductive pickup as well.

There is an added bonus from the capacitive shielding. The legal requirement for CB is that radiated harmonics are of extremely low level. Some types of SWR indicator can generate significant harmonic output just as a result of the internal diodes rectifying the RF. This design has a higher impedance display than types with a moving coil meter, so that less current flows in the diodes. Still, some harmonic output will be generated and the capacitive shielding effect of the braid helps to prevent this reaching the aerial.

The components used on the prototype are suitable for power levels up to about 50W. If the sensing head is required to be used at higher power levels, then a higher wattage resistor should be used for R3.

The output from the sensing head is fed to the display via a miniature stereo jack and a three core cable. The prototype used three core miniature mains lead for this purpose.

The display itself uses an LM3914 bargraph IC (IC1). It is

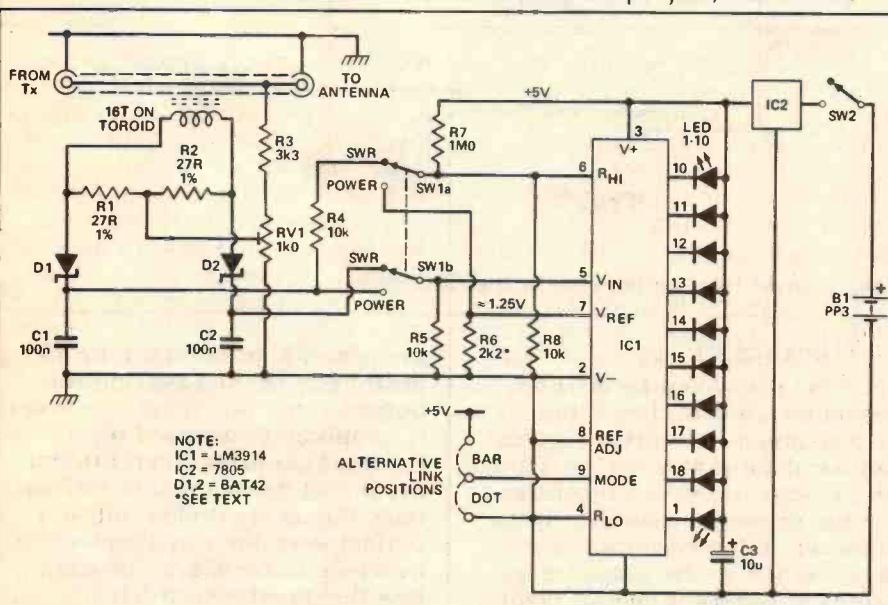


Fig.5 The circuit diagram of the SWR/Power meter.

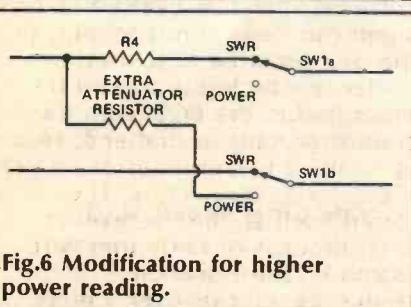


Fig.6 Modification for higher power reading.

The SWR indicator makes use of this by adding or subtracting a signal derived from the cable current to a signal derived from the voltage. If both signals are of the same amplitude then addition will give double the signal while

diagram of which is shown in Fig.5.

In this design, the voltage signal is fed into a resistive centre tap in the current transformer circuit. The load resistors are of a low value to load the current transformer so it is operating accurately in a current mode. The current circulating in the loop comprising the current transformer, R1 and R2 is more or less proportional to the current in the inner of the coaxial cable which passes through the middle of the toroidal transformer. The voltage developed across the resistors is not sufficient to interfere with this.

PROJECT: SWR Meter

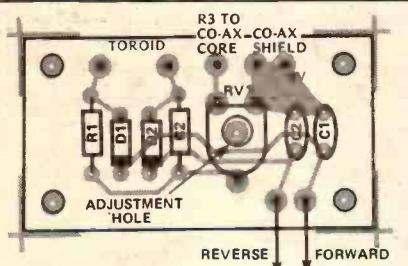


Fig.7 The component overlay for the sensing head board.

PARTS LIST

RESISTORS (all $\frac{1}{4}$ W 5% unless otherwise stated)

R1,2	27R 1%
R3	3k3
R4,5,8	10k
R6	2k2
R7	1M0
RV1	1k0 cermet preset

CAPACITORS

C1,2	220n polyester
C3	10 μ F 16V radial electrolytic

SEMICONDUCTORS

D1,2	BAT42
LED 1-10	Rectangular green LEDs
IC1	LM3914
IC2	7805

MISCELLANEOUS

SK1,2	PL259 connector
SW1	DPDT toggle switch
SW2	SPST toggle switch

PCBs; Diecast box approx 87 x 33 x 27mm and plastic box approx 123 x 63 x 32mm; FX2691 toroidal core; small length of co-axial cable; nuts and bolts.

switched to read power or SWR. In the power mode the internal voltage reference is used to drive the reference chain and if the specified components are used throughout this will give a full scale reading of 5W.

If a higher reading is required, a potential divider resistor should be added as shown in Fig.6.

When the display unit is switched to SWR, the reflected power is displayed as a proportion of the forward power. This gives a measurement of SWR which is largely independent of power. The only power dependence is at very low power when the efficiency of the sensing head is reduced.

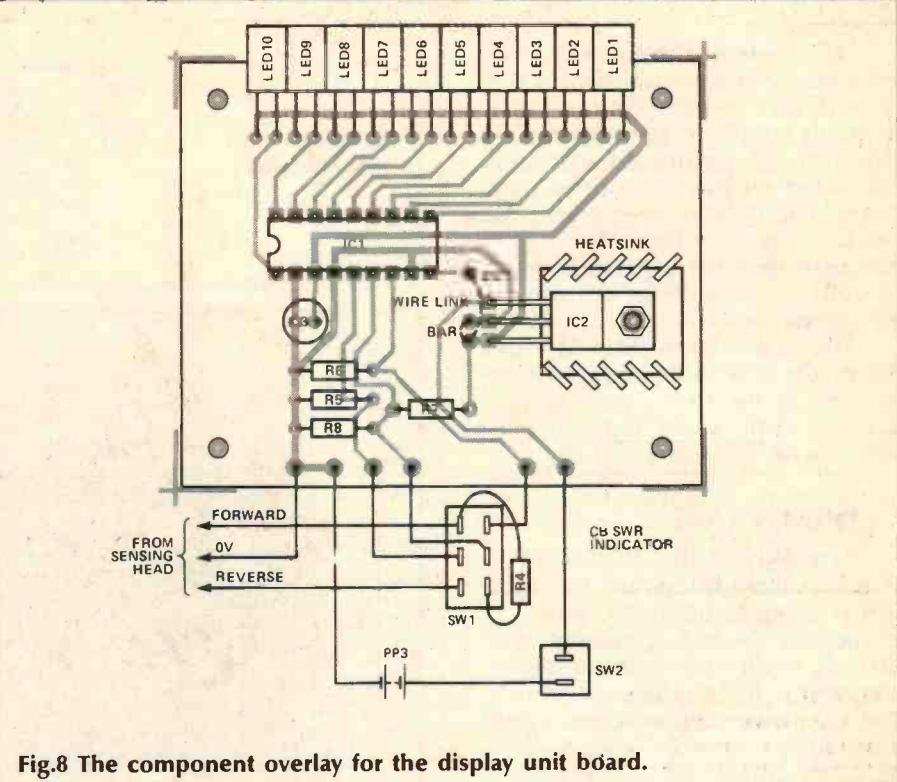


Fig.8 The component overlay for the display unit board.

Very high SWR readings are not of interest in adjusting a (hopefully) fairly efficient antenna, so the forward signal is potted down by R7, R4 and the resistance of the comparator divider chain on the IC which puts approximately 3:1 SWR at the sixth LED along.

The bargraph IC used can provide either a dot or bar display. The bar display looks better but if the unit is powered by a battery, bar mode will run down the battery much faster. It is possible to power the unit from the 12V CB power supply, in which case the bar display is definitely to be preferred. Otherwise a choice must be made between long battery life and the better looking display. A link is provided on the PCB to select the chosen mode.

The brightness of the display is determined by R6, the LED current being approximately ten times the current in R6.

When the CB rig is on receive, there is no forward signal to bias the reference input of the bargraph IC. In this condition, the entire row of LEDs could be switched on instead of being switched off as they should be. To prevent this, R6 provides about 25mV of bias in the absence of signal.

Construction

To achieve reasonable accuracy of measurement, the sensing head should be constructed

neatly with minimum wire lengths (Fig.7). Long wires dangling around inside the equipment can cause stray coupling of the 27MHz RF with a consequent loss of directionality of the detection system. It is recommended that the specified case or a close equivalent is used.

Before any components are mounted on the PCB, the connectors should be mounted on the main body of the case and the board on the lid. When the board is temporarily mounted on the lid, the hole in the board under the preset pot (to permit calibration) should be drilled out to a size large enough to admit a trimming pool with an insulating sleeve slipped over the blade and the hole should be continued through the case. This will ensure accurate lining up of the holes when the time comes to adjust the unit with the lid closed.

The components should be mounted on the PCB, with R3 connected only at one end, ready to connect to the inner of one of the co-axial connectors. The toroid itself should be wound with 16 turns of fairly thin wire (about 0.25mm diameter). It should be slipped over a piece of coaxial cable already cut to length and stripped and tinned.

Remember that only one end of the braid should be grounded, to act as an electrostatic shield. If both ends are grounded the current transformer will pick up

very little.

The leads of the toroidal current transformer and of R3 should be trimmed so there is enough length to permit the board to be connected and then mounted on the lid but not much extra. The output leads to the jack socket may be a little longer because they carry no RF but they should be dressed away from the RF connections.

The earth connections should be made to a solder tag mounted on one of the fixing bolts of the co-axial connectors and should also be as short as practical.

Display Unit

Assembly of the display unit (Fig.8) is straightforward but there are choices to be made. The choice of dot or bar display has already been mentioned and if the unit is to be powered from the CB power supply then a non-reversible connector should be selected and fitted to connect the supply. Just to be on the safe side, it would be a good idea to include a diode in series with the supply to prevent an unfortunate conflagration should it be connected the wrong way round!

If an internal battery is to be used to power the unit, then a cutout must be made in the PCB as shown in the photograph of the display unit.

If only dot display is to be used, then IC2, the 5V regulator need not have a heatsink fitted. Otherwise a small heatsink should be used.



Facia

The difficult part is cutting the slot for the LEDs in the front panel (Fig.9). If the recommended case is used, the mounting holes in the PCB will line up with the bosses inside the case. The way to mark the slot is to mount the LEDs on the board in a straight line, then fit the front panel into the top of the box, and lay the PCB in the top, to which it will eventually be screwed. Line the mounting holes up with the bosses in the side to side axis, and slide the board forward until the LEDs touch the front panel.

After double checking that the board has not moved sideways, mark round the top and both sides of the line of LEDs. Remove the front panel and tidy up the marks with a scriber and rule, and mark the width of the slot as well.

These markings are on the inside of the case, so will not show. The best way to proceed is

Fig.9 The front panel layout.

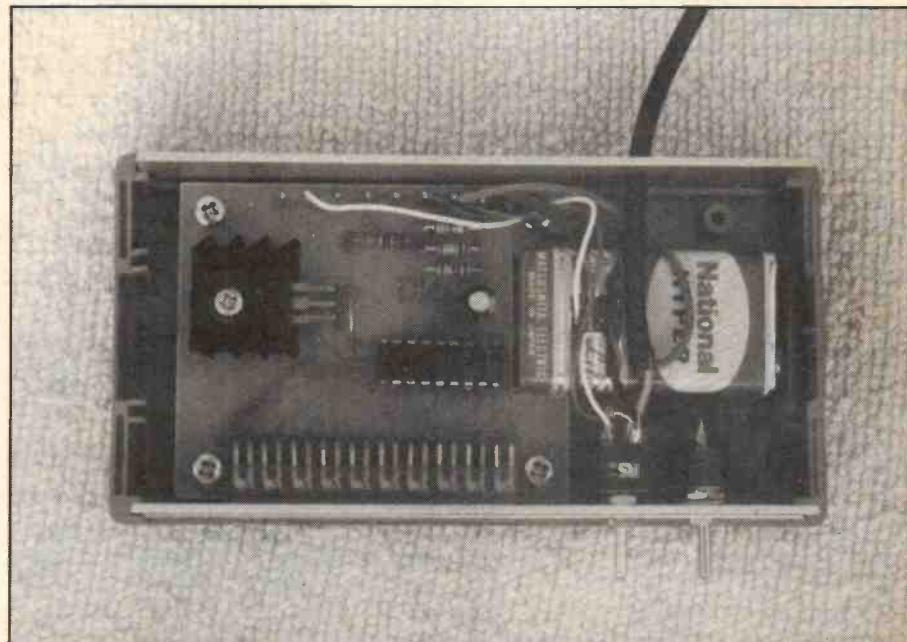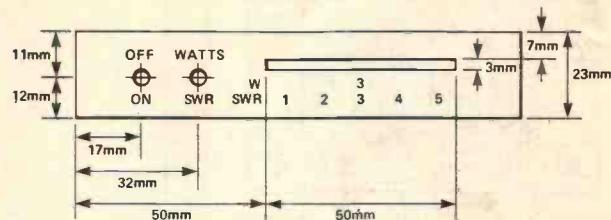

to make a line of centre punchings along the middle of the slot, and then drill a row of small holes. Finally, use a rectangular needle file to join up the holes into a slot. Patience is needed at this point or the finish will be spoilt.

When the slot is accurate and the LEDs fit, holes can be drilled for the two subminiature switches.

One or two holes are required in the back panel as well. If battery power is to be used, the only hole needed is for the lead to the sensing head. If external power is to be used as well, the connector or flying lead also requires a hole.

The wiring up of the PCB to the switches is not difficult. Note that R7 is mounted diagonally across the back of the SWR/Power switch and that the cable to the sensing head is soldered directly to the switch. This should not be connected, however, until the sensing head is adjusted.

Adjustment

To adjust the sensing head as accurately as possible, a good quality 50R load and a DVM are needed. First of all mark one of the co-axial connectors *Transmitter* and the other *Antenna*.

Connect up the transmitter and the dummy load. Plug the connecting lead into the output of the sensing head and connect 10k (or thereabouts) load resistors between the outputs and ground.

Connect the DVM across one or other of the load resistors and switch on the transmitter. Use a trimming tool insulated with a plastic sleeve to adjust RV1 through the hole in the case of the sensing head. If the DVM is connected to the reflected output, there should be a sharp dip in output at some point. If there is not, connect the DVM to the other output and try again. The unit is correctly adjusted when there is very little or no voltage on the reflected output.

Note which wire is the reflected output and connect it to the correct pole of the switch on the display unit. Remember to thread it through the hole in the back of the case first!

Operation

In operation, whether switched to power or SWR measurement, the display will only illuminate while transmitting. The power consumption for the rest of the time is low but is enough to run out a battery overnight if it is left switched on.

It is probably preferable to leave the unit switched to power reading for most of the time and only switch to SWR for the occasional check. If all is well then few or no LEDs will illuminate in the SWR mode so there will be nothing to see. This can be useful, for example, when using CB in a car.

The sensing head can be connected in the antenna lead out of sight while the display unit can be positioned on the dashboard where it can give a reassurance that the transmitter is working normally without the need to take the eyes off the road.

As I said at the start, the unit will work well on 2m with one component change. The toroid has too high an inductance for accurate operation on 2m — the phase shift of the current pickup is too large.

If a lower permeability core suitable for this frequency is used, it will work on 2m but not very well on CB. With the appropriate choice of core, the SWR indicator will work at HF or VHF, the only limitation being that the unit as it stands is designed for about 5W RF output maximum.

ETI



BUYLINES

Most of the components are easily available from usual sources. The toroidal core and co-axial connectors are available from Cirkit.

The PCB is available from the ETI PCB service.

A complete kit of all parts (components, PCB, cases and connectors) for either CB or 2m operation is available for £24.50 including VAT from Cirkit, Park Lane, Broxborne, EN10 7NQ. Tel: (0992) 444111.

BUILD YOUR ETI DREAM MACHINE IN STYLE

Adjust the controls to suit your mood and let the gentle, relaxing sound drift over you. At first you might hear the sound of soft rain, sea surf, or perhaps the wind through distant trees. Almost hypnotic, the sound draws you irresistably into a peaceful, refreshing sleep.

For many, the prospect of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are some strange and mysterious dream experiences waiting. Take lucid dreams, for instance. Imagine being in control of your dreams and able to change them at will to act out your wishes and fantasies. With the Dream Machine it's easy!

The ETI expansion parts set contains all you need to turn the basic Dream Machine into a very special project. The parts set contains:

• PRESTIGE CASE • MAINS POWER SUPPLY COMPONENTS (transformer, rectifiers, capacitors, regulator) • HIGH QUALITY EXPANSION COMPONENTS (TBA820 IC, resistors, capacitors, transistors, preset, loudspeaker) • ALL CONTROLS AND ACCESSORIES (pots, switches, knobs, neon lamp, fuse holder, fuse, mains cable, etc.) • FULL INSTRUCTIONS (Copies of the November and December ETI articles describing construction, testing and all kinds of dream experiments!)

The expansion set costs only £16.95 + postage and VAT
(You will need the free components and PCB from the November and December issues to complete this project)

The complete parts set (including PCB and all components) is yours for only £17.95 + postage and VAT.

To A.S.P. Readers Services, 9, Hall Road, Maylands Wood Estate, Hemel Hempstead, Herts HP2 7BH. Please supply
.....expansion sets ROET 8 @ £16.95
.....complete sets ROET 9 @ £17.95

I enclose my cheque/P.O. payable to A.S.P. Ltd. Please debit my Access/Barclaycard A/c No.

Signature

Name

Address

Please allow 28 days for delivery. This offer is available to readers in U.K. only. Overseas enquiries in writing to the above address.

WITH THIS SPECIAL OFFER PACK OF PARTS
FROM ETI READERS SERVICES.
'EXPANSION' OR 'FULL' KIT.

SECURITY

Modules
Systems
Accessories

MINIATURE PASSIVE INFRA-RED SENSOR RP33

ONLY
£23.95
Plus VAT

Size only 80x60x40mm. Detects intruders up to 12 metres away.



- 12 metre detection range.
- Size only 80x60x40mm.
- 24 Detection zones.
- Wide 85° coverage.
- Switchable LED indicator.

This advanced new intrusion detector operates by detecting the body heat of an intruder moving within the detection field. The use of a pyroelectric sensor means that changes in ambient temperatures are ignored, thus providing a stable and reliable performance. Easily installed in a room or hallway, the unit will provide effective detection of any intrusion.

Operating from a 12V supply and consuming only 15mA, it is ideal for use with the CA 1382, CA 1250 or any equivalent high quality control unit. Supplied with full instructions, its performance compares with detectors costing more than twice the price.

CA 1382 ADVANCED CONTROL UNIT that's simple to install and operate.



- Fully automatic siren re-set.
- Audible entry/exit warning.
- Alarm Sounded memory.
- 2 separate loop inputs + 24hr circuits.
- Built-in electronic siren.
- Easily installed, full instructions supplied.

The latest control panel provides effective and reliable control for all types of security installations. Its advanced circuitry checks the loop circuits every time it is switched on, preventing incorrect operation. Using a simple on/off key switch, it is easily operated by all members of the family. In addition it provides 24 hr. personal attack protection. Housed in a steel case, it is supplied with full operating instructions.

Only £44.95 + VAT Available in kit form with fully built electronics, £39.95 + VAT.

CA 1250 LOW COST ALARM CONTROL MODULE



This tried and tested control unit represents the finest value for money in control systems, providing the following features:

- Built-in electronic siren drives 2 loud speakers.
- Provides exit and entrance delays together with fixed alarm time.
- Battery back-up with trickle charge facility.
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units.
- Anti-tamper and panic facility.
- Stabilised output voltage.
- 2 operating modes full alarm anti tamper and panic facility.
- Screw connections for ease of installation.
- Separate relay contacts for external loads.
- Test loop facility.

Price £19.95 + VAT

HW 1250 - ATTRACTIVE HOUSING plus HARDWARE FOR CA 1250

An attractive steel case designed to house the Control Unit CA 1250 together with the appropriate LED indicators and key switch (available separately). Supplied with the necessary pillars, fixings, and punched front panel, the unit is given a professional appearance by the adhesive silk screened label.

Size: 200x180x70mm. Only £9.50 + VAT

COMPLETE SYSTEM
FROM
£39.95
+ VAT

DP 3570 LIGHTING CONTROLLER

This versatile module provides timed switching of loads up to 3A for pre-set times between 10 secs and 5 mins. the timed period being triggered by the opening or closing of an external loop or switch. The built-in 12V 250mA power supply is available for operating external sensors. Suitable plastic enclosure £2.85 + VAT.



Only £13.95 + VAT

FL 500 QUARTZ HALOGEN FLOOD LIGHT



Whilst intended for security lighting applications, this unit is suitable for lighting patios, pathways and gardens etc. Supplied complete with 500W lamp, priced Protective grill, £1.95 + VAT.

Only £14.95 + VAT

IR 1470 - 50ft. INFRA-RED BEAM SYSTEM

Consists of a separate transmitter & receiver, the system provides an invisible modulated beam which when broken operates the built-in relay. For use with security systems, but also ideal for photographic purposes and industrial applications. Size: 80x50x35mm. Only £25.61 + VAT



US 5063 DIGITAL ULTRASONIC DETECTOR

• 3 levels of discrimination against false alarms • Crystal control for greater stability • Adjustable range up to 25ft • Built-in delays • 12V operation.



ULTRASONIC MODULE ENCLOSURE

Suitable steel enclosure for housing the US 5063 supplied with the necessary mounting pillars and fixings.

Only £2.95 + VAT

RISCOMP LIMITED. The Security Specialist

Dept ETI 12
51 Poppy Road
Princes Risborough
BUCKS
HP17 9DB

ORDER BY MAIL
OR TELEPHONE



Tel: (084 44) 6326



Zenith Electronics.®

Kits - Modules - Hardware

CHRISTMAS SPECIAL

10-Channel variable speed running light kit, drives LED's or Mains lamps - plus 2-FREE LED display boards and LED lamps. An ideal festive project.

- The following are examples of our proven product designs
- ★ High quality touch dimmer 500W R/Built £12.99
- ★ Selectable tone generator 9-12v operation £5.50
- ★ 3 Note Electronic Door Chime unit; 9 volt operation, 3 melodious tones; variable frequency. Kit £9.83
- ★ Miniature FM Transmitter; 60-145MHz. Kit £6.95
- ★ R/Built £8.95
- ★ 3 Watt FM Transmitter, 80-108MHz. Kit £13.99
- ★ R/Built £18.99
- ★ 300 Watt Light Dimmer unit for 240 volt mains lights. Kit £6.95
- ★ 4 Code Digital Code unit plus Key Pad - select own code; 9 volt. Kit £15.95
- ★ 5-100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit £11.11
- ★ VU Meter 10 LED indicator; -5 to +12dB range. Kit. £12.59
- ★ Automatic light controller; automatically turns on and off lights at pre-set times and triggered by darkness. Kit £25.08
- ★ Mains Wiring and Metal Detector. R/Built £11.00
- ★ Zenith Speech Processor P-202 R/Built £25.00
- ★ 18-Watt Car/Home Power Amp. 12-V. Kit £13.23
- ★ Amplifier Power Meter; 10 LED indicator from 0.25-100 Watt Input - 9 volt operation. Kit £9.52
- ★ Light sensitive relay unit; variable sensitivity trigger control; senses light or dark - selectable. Kit £8.45

ALL KITS CONTAIN FULL INSTRUCTIONS: P.C.B.s AND COMPONENTS.

ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.

OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.

PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.

S.A.E. For
—FREE—
Data Pack

DATA SHEET

OSCILLOSCOPES

TELEQUIPMENT D83 Dual Trace 50MHz Delay Sweep. Large Tube	£350
S.E. LABS SM111 Dual Trace 18MHz Solid State, Portable AC or External DC operation 8x10cm display with Manual	£150
TELEQUIPMENT D61 Dual Trace 10MHz With Manual £150	
TELEQUIPMENT D43 Dual Trace 15MHz With Manual £200	
TELEQUIPMENT S54A Single Trace 10MHz. Solid State With Manual	£90
GOULD/ADVANCE DS255 Dual Trace 15MHz £225	
With Manual	
ADVANCE DS250TV. Dual Trace 10MHz £150	
With Manual	
HAMEG 207 Single Trace 8MHz. With Manual £50	

MULTIMETERS

AVO 8 Complete with Batteries & Leads from £45	
AVO 8 MkV Complete with batteries Leads & Case £90	
AVO TEST SET NO 1 (Military version of AVO 8) Complete with Batteries Leads & case £65	
TEST SETS available for AVO METERS Red & Black with 2 croc-cups & 2 prods (P&P £2)	£5
AVO Model 7x Complete with Batteries, Leads & carrying case £40	
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads £10	
AVO - 72 Similar to above but no AC current range. With batteries & leads £10	
ANALOGUE POCKET MULTIMETERS Philips/Taylor etc. With Batteries & Leads from £10	

COMMUNICATION RECEIVERS

RACAL RA17 500KHZ-30MHz with Manual only £150	
Eddystone 730/4 480KHZ-30MHz only £110 each with manual.	

AVO TRANSISTOR TESTER TT169

Handheld GO/NOGO for In-situ Testing. Complete with Batteries Leads & Instructions (P&P £3) unused £12 each	
---	--

ISOLATING TRANSFORMERS 240V INPUT

240V Out 500VA £15(p&p £5) 100VA £8(p&p £4)	
24V Out 500VA £8(p&p £5) 200VA £4(p&p £4)	

STEPPING MOTORS

Type 1 200 Steps per rev. 4 Phase (5 wire) 12V with reduced torque 25oz inch will run on 5V with 15m	
6/12 Steps per rev. 3 Phase, 12/24V will work on 5V £2 as 5 off £7.50	
NORTH AMERICAN PHILLIPS 24 Steps per rev. 4 wire 5V 3.3Amps 0.250pm	£8 m
Type 4 200 Steps per rev. 120V (3 wire) Torque 25 oz inch £4 ea.	
WARNER 24 Steps per rev. 3 Phase (6 wire) 28V. Holding Torque 45 oz. inch £5 ea.	

Used equipment - with 30 days guarantee. Manuals supplied if possible.

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041 Callers welcome 9 am - 5.30 pm Mon.-Fri. (until 8 pm Thurs.)

SAVE ££££'S

BY INSTALLING YOURSELF

DP 3570 LIGHTING CONTROLLER

This versatile module provides timed switching of loads up to 3A for pre-set times between 10 secs and 5 mins. the timed period being triggered by the opening or closing of an external loop or switch. The built-in 12V 250mA power supply is available for operating external sensors. Suitable plastic enclosure £2.85 + VAT.



Only £13.95 + VAT


FL 500 QUARTZ HALOGEN FLOOD LIGHT

Whilst intended for security lighting applications, this unit is suitable for lighting patios, pathways and gardens etc. Supplied complete with 500W lamp, priced Protective grill, £1.95 + VAT.

Only £14.95 + VAT

IR 1470 - 50ft. INFRA-RED BEAM SYSTEM

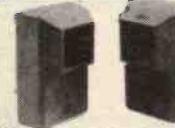Consists of a separate transmitter & receiver, the system provides an invisible modulated beam which when broken operates the built-in relay. For use with security systems, but also ideal for photographic purposes and industrial applications. Size: 80x50x35mm. Only £25.61 + VAT



ULTRASONIC MODULE ENCLOSURE

Suitable steel enclosure for housing the US 5063 supplied with the necessary mounting pillars and fixings.

Only £2.95 + VAT

RISCOMP LIMITED. The Security Specialist

Dept ETI 12
51 Poppy Road
Princes Risborough
BUCKS
HP17 9DB

ORDER BY MAIL
OR TELEPHONE



Tel: (084 44) 6326



Zenith Electronics.®

Kits - Modules - Hardware

CHRISTMAS SPECIAL

10-Channel variable speed running light kit, drives LED's or Mains lamps - plus 2-FREE LED display boards and LED lamps. An ideal festive project.

- The following are examples of our proven product designs
- ★ High quality touch dimmer 500W R/Built £12.99
- ★ Selectable tone generator 9-12v operation £5.50
- ★ 3 Note Electronic Door Chime unit; 9 volt operation, 3 melodious tones; variable frequency. Kit £9.83
- ★ Miniature FM Transmitter; 60-145MHz. Kit £6.95
- ★ R/Built £8.95
- ★ 3 Watt FM Transmitter, 80-108MHz. Kit £13.99
- ★ R/Built £18.99
- ★ 300 Watt Light Dimmer unit for 240 volt mains lights. Kit £6.95
- ★ 4 Code Digital Code unit plus Key Pad - select own code; 9 volt. Kit £15.95
- ★ 5-100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit £11.11
- ★ VU Meter 10 LED indicator; -5 to +12dB range. Kit. £12.59
- ★ Automatic light controller; automatically turns on and off lights at pre-set times and triggered by darkness. Kit £25.08
- ★ Mains Wiring and Metal Detector. R/Built £11.00
- ★ Zenith Speech Processor P-202 R/Built £25.00
- ★ 18-Watt Car/Home Power Amp. 12-V. Kit £13.23
- ★ Amplifier Power Meter; 10 LED indicator from 0.25-100 Watt Input - 9 volt operation. Kit £9.52
- ★ Light sensitive relay unit; variable sensitivity trigger control; senses light or dark - selectable. Kit £8.45

ALL KITS CONTAIN FULL INSTRUCTIONS: P.C.B.s AND COMPONENTS.

ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.

OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.

PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.





S.A.E. For
—FREE—
Data Pack

DATA SHEET

Zenith Electronics, 14 Courtland Business Centre, Hailsham, E. Sussex, U.K. BN27 1AE.

Tel: 0323 847973 Telex: 878334

OPEN CHANNEL

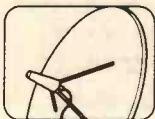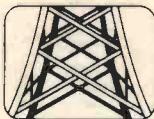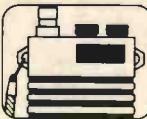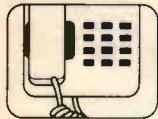

The recent resignation of Sir George Jefferson from the top seat at British Telecom had been more or less expected, for personal reasons. Its timing, on the other hand, was not expected. His resignation came at the end of a long line of public criticisms about BT's operating record and may have appeared to have been brought about by those criticisms.

Analysed in detail, many of the criticisms aimed at BT have been shown as highly subjective and, because of this, unfair. For example, the largest criticism, (the London Business School's recent report on the cost of System X exchanges to the British telephone network and its users) noted that Britain would have been better off with foreign exchange equipment because no development costs would have been incurred.

Other criticisms in that report highlight the use of a procurement policy, a high development cost (\$1.4 billion) and a failure to achieve exchange sales abroad.

The report was taken up by national newspapers in August (the silly season) and reported in terms of cost to the user, as a percentage of current call costs.

These criticisms are all based on factual evidence and of course the facts themselves cannot be disputed. However, the London Business School's interpretation of the facts is open to some criticism itself. First, the use of System X against other digital exchanges from foreign sources.

Buying British

In terms of development cost versus the cost of buying a foreign exchange, London Business School's estimate of \$14 billion for System X may be correct (although it has been disputed) and if so does sound quite a lot compared with the only other two competitive foreign exchanges (the AT&T 5ESS at \$0.75 billion and the Ericsson AXE at \$0.5 billion).

However, what the report omits is that no other comparable exchange sufficiently advanced on a technical basis was available when BT decided upon the development route. So what should BT have done? Wait, in the hope that an acceptable digital exchange happened to arrive at an acceptable price, at an acceptable time?

Also what would be the consequences to the nation? Certainly, our telecommunications industry would be considerably weaker than it is today. Certainly,

there would be a greater number of people on the dole queue. Don't we have enough troubles with the consequences of importing foreign technologies without doing the same with our telephone system?

At least now we have two companies within the UK (Plessey and GEC) with extremely good exchange design, development and manufacturing capabilities, to lead us into the 21st century and the next range of telephone equipment. We also have an exchange system which is at the forefront of current technology.

More Moans

As for the other criticisms in the London Business School's report: A procurement policy is apparently used by every other telecommunications organisation in the world. The high development cost is disputed by the exchange manufacturers and estimated at a lower figure of around \$0.8 billion. Failure to export? It's certainly lower than what might have been expected but some sales have been made abroad. Well, they are subjective and other people may well put a different emphasis on the facts.

Don't get me wrong. I am always one of the first to criticise BT's operation but at least my criticisms are based on current problems, which BT can tackle. Criticisms like those in the London Business School's report are criticisms made in hindsight and I believe are subjective criticisms which can do no good.


BT hopefully has sufficient muscle to shrug them off and tackle the real problems of customer dissatisfaction.

In this respect, most other criticisms are individual ones, which can be remedied by BT on an individual basis. Problems with reaching the directory enquiries service (particularly in London) for example, have to be overcome one way or another directly by BT. Problems with new System X installations, though, are commissioning problems for which the suppliers must be criticised and not BT (the user in these cases).

Our telephone service is a good one. Don't let's forget that. It is also rapidly getting better. The rate at which the service improves can only be hampered by subjective, destructive criticism. Objective, constructive criticism should be our aim.

Keith Brindley

ONCE OVER

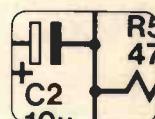

Pressure mats, window foils and passive infra-red detectors are all very well for sophisticated alarm systems but they are a perfect pain to install and only as effective as the control unit and siren or bell they're connected to.

What every good burglar really needs to set him running is the threat of a set of canine gnashers sinking into his backside.

This thought is not an original one and many insurance companies will give discounts on home contents policies if a dog is in residence.

The trouble with dogs, however, is that they are even more of a pain. They require feeding, exercising and to start with they require training and cleaning!

What a blessing for dog haters everywhere is TK's Electronic Guard Dog kit. This clever but remarkably simple circuit provides on command a very reasonable imitation of a dog barking.

Almost all parts required for a complete dog are provided in the £21.95+VAT kit. All that is required is a case and (for the perfectionist) a couple of rotary pots and knobs.

The assembled Electronic Guard Dog is mains powered and triggered by a closing contact. It then gives a few 'barks' spaced at random intervals through the horn speaker. The pitch of the 'barks' can be varied from 'terrier to alsatian'!

The effect is remarkably realistic. In the same room the barks do sound a bit electronic but through a closed door or down a corridor it is genuinely difficult to tell that these barks are not going to be followed by bites!

The PCB is about 2 x 2½in in size and is crammed with three ICs, five transistors, seven diodes, 11 capacitors and 16 resistors, not to mention a terminal block and off-board jack socket, transformer and speaker.

The instructions provided are a little scrappy — they're all on one fading photocopied sheet — but they are clear and correct. The kit I was supplied with had all the parts present and correct (with one extra capacitor, in fact) and it worked perfectly first time.

The barks are formed from a voltage controlled oscillator feeding a simple amplifier which drives the horn speaker. The oscillator is gated by a random sequence generator formed from the usual exclusive-OR-feedback shift register clocked from a simple multivibrator giving a sequence about 15 clocks long. A

monostable gates the multivibrator to provide a set length of the bark sequence.

Almost all the circuit is based on CMOS logic with only the amplifier based around the power transistors. A preset is provided to alter the frequency of the VCO (the pitch of the bark) and information is given on the instruction sheet to change the length of the bark sequence and interval between barks. Being a perfectionist I mounted two pots on the outside of the case for adjusting bark pitch and interval.

A random modulation of the bark frequency and even a low growl in between barks would make the dog imitation more realistic but I guess you can't be too fussy with a simple and cheap kit like this.


The biggest omission is a more versatile triggering mechanism. As it stands, the circuit requires two contacts to be connected to start the barks. However, few alarm triggering devices switch a relay. Most produce a high or low voltage which may well be unsuitable.

The obvious application for the Electronic Guard Dog is to connect it to your doorbell. This is covered in the instructions but will usually require a bridge rectifier and an opto-isolator. It would have been nice to see all this incorporated on the PCB and the components provided in the kit.


However, for £21.95 the Electronic Guard Dog is an entertaining product, the kit is simple and even instructive to build, and it could just prove to be worth its weight in doggy chocs the next time the nice gentleman in the mask and striped jersey comes visiting.

TK Electronics
13 Boston Road,
London,
W7 3SJ.
Tel: 01-579 9794

Martin Tame

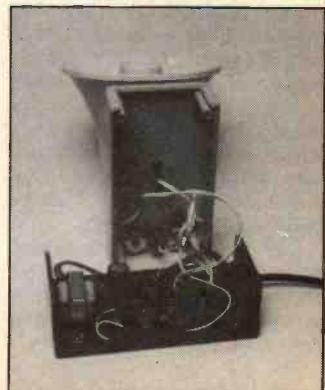

THE HI-FI SHOW

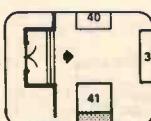

Some psychologists regard hi-fi as a subject with distinct sexual overtones. Grown men lust after it. Some will give almost anything to obtain it and when they do they boast about it at great length to similarly obsessed friends. Glossy magazines print full-colour pictures of the latest models which are then passed around goggle-eyed initiates.

Meanwhile the wife (for it is almost always men who get stuck on hi-fi) stays at home and wonders if the marriage will survive this new passion.

These overtones are rarely as apparent as they were at the 1987 Hi-Fi Show, held on September 17-20th at the Heathrow Penta Hotel, London. While some manufacturers displayed their wares in large halls downstairs, the bulk of the show took place in hotel bedrooms on the first floor.

There, soft music (or in some cases very loud music) poured from discreetly open doors as hi-fi sirens competed to attract the thronging hordes of almost exclusively male visitors.

Carefully-groomed women sat at card tables beside closed doors, encouraging and placating the queues which grew steadily as the time of the next demonstration approached. Then the doors would open and the occupants of the crowded rooms would reel out, sweat soaked and visibly moved, to compare prices and vital statistics in furtive groups before stumbling off in search of further delights.

The Hi-Fi Show lacks some of the surface gloss of other major audio events but the clubby, almost conspiratorial atmosphere more than makes up for it. While the larger companies demonstrated in conditions much like those found at any trade show, some of the smaller outfits settled for cheerfully chaotic presentations in which personality counted for at least as much as the product. One-man companies gave one-man shows and luminaries like Tim de Paravicini of Esoteric Audio Research could be found holding court in tiny hotel rooms, playing favourite records and dispensing advice, opinion and reminiscence.

In this heady atmosphere it was difficult to decide what sounded good and what didn't. Some closed-door demonstrations were very good but most companies chose to audition their equipment in semi-open conditions where concentration was impossible.

This is an inevitable problem at any hi-fi show and the wonder is

that some of the equipment sounded as good as it did. One or two of the smaller companies managed to overcome the limitations but I'm loathe to place too much weight on the subjective impressions gained in such an environment.

The watchwords at this year's show seemed to be vinyl, valve, class A, analogue and (just to be fair) digital. I was intrigued to see how many companies — even quite major ones — were using analogue record decks as a source rather than CD. Linn Sondeks were at least as much in evidence as Cambridge CD1s (the choice, I note, of quite a few of those who preferred CD) while elsewhere Pink Triangles, Revolvers and even more exotic rotating thingummies were to be found feeding top-flight systems.

Thorens was showing the newly reintroduced TD-160 deck, now known as the TD-160S, while Veyd Turntables demonstrated a novel design which uses three electronically-controlled motors to ensure stability. It looks pretty unusual but not as unusual as the Crystal turntable from Oxford Acoustics which resembles a wooden sundial and is billed as the 'ultimate development of the vinyl analogue disc player'.

Record cartridges were on display but it often wasn't made clear which cartridge was being used for a particular demonstration. For this reason they made little impression on me, the only one I recall being the aptly-named design for use with the Revolver turntable. It's called The Bullet.

There was certainly no sign of a decline in the number of valve amplifiers. Beard, EAR and Conrad-Johnson were among those launching new valve products or updates of earlier ones while Luxman continued to push its valve-semiconductor hybrid amps which have a neat little window in the front panel to show off the glowing triodes.

Radford demonstrated the new Renaissance version of the much-lamented STA-25 amplifier but did so through Rogers loudspeakers, a great shame when one remembers that Radford was once better known for its loudspeakers than for amplifiers.

Class A was judged to be a good selling point by several manufacturers and not only for power amplifiers. Luxman was making much of its new class A preamplifier, an idea which might not sound so new to those who recall that most preamplifiers were effec-

tively class A until the arrival of the operational amplifier in IC form. Musical Fidelity was content to employ class A operation only in its power amplifiers but added to the quality/mystique/price of the products by claiming the use of linear crystal oxygen-free copper cable for all internal wiring. Perhaps ordinary wire only operates in class B!



Digital was less heavily hyped than it might have been but there was still a lot of fuss being made about amplifiers with built-in ADC converters. There were also numerous new CD players on show but the most interesting for my money was the CD2 from Cambridge Audio. It boasts 16 bits and 16 times oversampling. Given the way the CD1 has established itself as a near standard the CD2 should be well worth watching.

Digital audio tape was much talked about but little seen. With Sony launching the first domestic DAT machine in the UK shortly after the show, one might have expected a few other manufacturers to take up the challenge and unveil their own models (most of them already have DAT products on sale in Japan or the US). In practice the only machines I saw were from Luxman and Kenwood, while Sansui showed a mock-up of one of its overseas products and admitted it wasn't sure when, if at all, it would be launched in the UK. The Luxman product will sell for around £1500 and is due for launch in November. Kenwood expects its DAT recorder to sell for under £1000 and spoke of launching it next spring.

The question of analogue versus digital in tape machines was also being raised by EAR, Altarus Records and Townshend International who have dubbed themselves the Analogue Allies. Their pamphlet argues that analogue tape bias frequency is directly equivalent to digital sampling rate, giving analogue a rate of around 120kHz compared to the 44.1kHz and 48kHz of CD and DAT. Furthermore they claim the quantisation levels obtained on analogue tape are equivalent to 22 or 23 bits compared with the 14 or 16 bits used in current digital recordings. On this basis they claim analogue is capable of far better results than digital. If you're interested, the pamphlet can be obtained from


Department AA, PO Box 191, Sevenoaks, Kent TN13 3XX.

There were plenty of new loudspeakers but again the problem was deciding which sounded best in such an unhelpful environment. Of immediate visual appeal was the Bose Acoustimass system — a stereo loudspeaker set up which is so small as to be nearly invisible. It consists of a woofer box which lies on the floor and four tiny loudspeakers, each about as big as a couple of cigarette packets, which are supported in pairs on two metal poles. They certainly don't sound bad for the size.




In the automobile department the problems of size and appearance are receiving similar attention. Kef has decided that reasonable bass response cannot be achieved with the usual size of car loudspeakers and has chosen to use larger bass drivers and place them in sealed boxes in the boot. The sound is fed out by means of large diameter flexible hoses to normal size loudspeaker grilles mounted on the rear parcel shelf. The middle and high frequencies are taken care of by separate drive units mounted directly through the parcel shelf in the normal way. I've no idea what they sound like in use and given the prices I'm unlikely to be fitting any in my car in the near future.





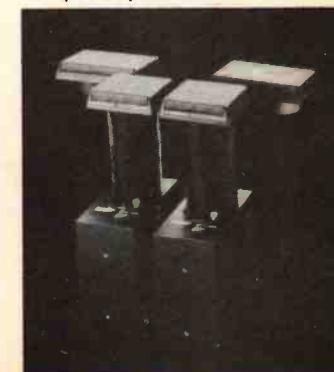
More in the 'why didn't I think of it first' category is a set of active loudspeakers from A&R. They are compact, produce about 15W



PLAYBACK

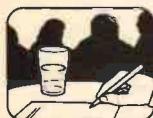

NEXT SHOW
1030

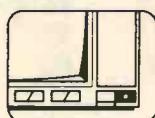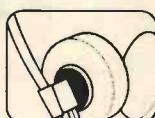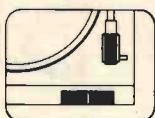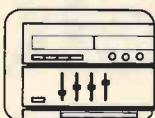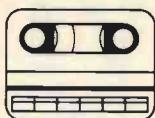

apiece and can operate from car batteries as well as the mains. A&R are marketing them as the ideal accompaniment to a picnic or beach party where they can be fed from a Walkman-style tape player.



Away from the purely hi-fi side of things the most widely trumpeted new product at the show was Philips' CD Video player. Similar machines have already been seen by the press and at trade shows but in theory at least this was the first public showing of the new system. It brings together the existing 8in and 12in laser disc formats and the audio compact disc and adds to them a new format — a 5in gold compact disc which can hold six minutes of video and stereo digital sound plus a further 20 minutes of stereo sound only. The Philips CDV 475 player handles all four types of disc.

I cannot finish without mentioning Yamaha's limited edition Centennial range. Yamaha has been going since 1887 and to celebrate has launched three products destined to strike fear into the stoutest heart and metal fatigue into the stoutest table.

Large, solid and very heavy they feature brushed silvery metal front panels, polished wooden side cheeks and enormous feet in a style I suspect is intended to be timeless but which will almost certainly date very quickly.

The power amplifier has almost all of its front panel area taken up with two huge moving coil meters while the preamplifier is grandly titled a digital control amplifier and features digital signal handling and a digital sound processor designed to add concert hall and other ambience to the music as required. The range is completed by a 16-bit, four times oversampled CD player which, like the preamp, is equipped with full remote control. I'm sure they sound great and are well worth an audition at home but please, please make sure the floorboards are up to it first!

Ian Pitt

I's always nice to receive a little feedback. Earlier this month the offices of ETI received the following letter on September's Playback from Mr. R. Mudhar of Southampton:

I agree wholeheartedly that, were it possible to replicate at my ears in my listening room the sounds I would perceive at my ideal listening position in the case of music which has an 'original sound' then one could go no further. Hi-fi will never achieve that.

This also leaves the question of the large majority of recorded music sold which has no 'original sound' but nevertheless has validity in its own right.

Testing Times

Rather than use instruments to find what is wrong with the signal, let us set ourselves an easier task. Assuming that for a signal to be listenable at all, there is more of what is right with it than what is wrong with it, let us look for some basic things contained in music.

Is there test gear which can:

- print out the words of a song from the sound?
- tell Bach from Beethoven?
- tell from a song if it is sad, hopeful or happy?
- tell if the sax is in tune with the lead guitar?
- tell if anything is in tune at all?

These are no arcane hi-fi subtleties. They are gross aspects vital to the perception of music. I take it as self-evident that to assess something that will pass beautiful music I must be able to perceive beauty and music.

To use test gear as a criterion of sound quality is like going to a concert with earplugs. Why do it?

Specs

If I tell you one amplifier has 0.01% THD and a frequency response flat to 2dB in the 20-20kHz range and another has a THD of 2% and a frequency response flat to 0.01% in the same range, can you honestly tell me which will sound better? To whom? With what music?

If the hi-fi mags printed reams of test statistics would you be able to advise your father-in-law with any chance of getting the best sound for the father-in-law, in his living room? Anybody who has been at any live meeting will have some idea of what perspective or depth might mean — if you can hear that someone is yelling far away and on the left and someone

else is close by on the right you have perspective and depth.

That is a lot better than being a degree course away from knowing what a frequency response of ± 0.01dB 20Hz to 20kHz at 0.01% THD means. Criticism can be levelled at the hi-fi mags for the high price of the gear they typically review but I respect someone who has the courage to say that they like the sound of their kind of music via that piece of kit much more than someone who presents a mass of figures uninterpretable to 95% of their readership.

Those tests that have been undertaken with a decent degree of open-mindedness have used instrumentation of a precision that befits university and research facilities, not maintenance gear. I refer Mr Armstrong to the work by Jean Hiraga on 'Pickup Musicality' and 'Amplifier Musicality' in the April and March 1977 issues of Hi-Fi News & Record Review which attempt to break the usual insanity of averaging out all distortion. I am happy to say that Mr Hiraga took careful measurements and attempted to correlate these with subjective findings rather than hiding behind a barrage of test results.

Boring Worlds

The bottom line is that until we live in a boring world where we all listen to the same music with the same ears in the same way then a person's reaction to music or degradation of the same will inevitably fail the axiomatic requirement for something to be scientifically observable — the same stimulus to appear the same to all observers.

We listen to music in a subjective manner. The diversity of musical tastes shows that. It is clear that the annoyance of interference to the music is entirely subjective. There never will be an objective assessment of the interference to the music as perceived and surely it is this interference as perceived we are trying to reduce. Is not hi-fi there to enhance the quality of life of the human listener, rather than a lab full of test equipment?

Science has given us much of value, but let us not stand so much in awe of it that we fear that side of us that science cannot know.

Well...

Mr. Mudhar has made a number of valid and interesting

points but he does seem to have read a different column from the one I wrote. My severest critic says that (just for once) I then stated my case quite clearly — in the third and fourth paragraphs.

Of course listening pleasure is subjective, as I implied at the time, but we are talking hi-fi here, which means 'high fidelity' — faithful reproduction. The implied purpose of hi-fi is to reproduce the sound of the music played at its source (see that September Playback again).

I happen to enjoy live music and well-played studio recordings. As no hi-fi is perfect, I prefer to have some choice as to what distortion and how much I have to suffer so, yes, THD and frequency response measurements are useful to me in choosing gear for myself and others. They are the least arcane factors quoted by some hi-fi reviewers.

What I object to is the vague confusion of good reproduction and 'musicality'. They are two different things. The use of the term 'musicality' implies that the sound reproduction equipment colours the sound in such a way as to make it more pleasing to the listener. This may be fair enough but it is not the aim of hi-fi. What's more, subjective comments are not useful as an assessment of sound quality because one person's pleasant colouration is another's dreadful noise.

Musical Money

On the other hand, harmonic distortion and frequency response ripple are objective measurements, from which the individual can estimate the suitability of equipment for his own needs. But when instead of this it is implied that a piece of cable, or whatever, is 'musical' and therefore worth triple the price or worse, I smell the presence of bewildered punters who won't trust their ears and are therefore mugs for large sums of money.

Their money would be better spent going to a few concerts to find out what they really do like.

I would like to read Jean Hiraga's work, as he seems to have done exactly what I recommended — carried out measurements to determine the physical basis for a subjective phenomenon. But why are his conclusions 'careful measurements' and mine 'a barrage of test results'?

Another case of woolly words being easier to sell than facts?

Andrew Armstrong

ETI PCB SERVICE

Build your projects in style with a properly designed PCB.

Use the form below (or a photocopy) for your order. Please fill in all parts of the form.

The board reference number tells you when the PCB foil was published. The first two numbers are the year and the next two the month. The number after the dash indicates the particular project in that issue.

The terms are strictly cash with order. Make cheques payable to ASP Ltd. We cannot accept official orders but we can supply a pro-forma invoice if required. Such an order will not be processed until payment is received.

Orders can also be made by telephone on (0442) 41221 for Access and Visa card holders.

Please allow 28 days for delivery.

Price Code	Price (inc VAT) £
C	1.80
D	2.50
E	3.23
F	4.00
G	4.75
H	5.50
J	6.62
K	7.20
L	8.80
M	10.60
N	13.10
O	15.80
P	17.90
Q	21.80
R	23.90
S	25.90
T	29.00
U	32.20
V	35.80
W	37.90
X	40.70

E8107-1	System A Disc Input bd	
	MC-MM.....	F
E8107-2	System A Preamplifier Main	K
E8108-1	System A Power Amp	L
E8109-2	System A PSU	F
E8201-2	Infant Guard	C
E8202-5	MM Stage Disc Preamp (Tilsbrook)	G
E8206-5	Logic Lock	F
E8208-1	Playmate Practice Amp 3bds SA1	K
E8212-1	ELCB	F
E8301-2	Analogue to digital conv (ZX81/ Spectrum)	E
E8305-3	Dual Audio Power Supply, Linsley Hood	G
E8305-5	Balanced Input Preamplifier	F
E8307-2	Flash Trigger-sound or FR	F
E8308-1	Graphic Equaliser 1/8 Oct/Chnl	M
E8308-2	Servo Fail-safe	C
E8309-1	NICAD Charger/Regenerator	F
E8310-3	Typewriter Interface - EX42	F
E8311-1	Mini Drum Synth	F
E8311-8	Moving Coil Pre-Preamp	F
E8312-3	Light Chaser EPROM Controlled (2 Boards)	K
E8402-1	Speech Board	M
E8402-2	Modular Pre-amp Disc Input Mono	F
E8402-3	Modular Pre-amp Stereo Output	F
E8402-4	Modular Pre-amp Relay, PSU	F
E8402-5	Modular Pre-amp Tone Main Mono	F
E8402-6	Modular Pre-amp Tone Filter, Stereo	F
E8402-7	Modular Pre-amp Balanced Output	F
E8402-8	Modular Pre-amp Headphone Amp	F
E8404-2	Mains Remote control Receiver	F
E8405-1	Auto Light Switch	F
E8405-2	ZX81 EPROM Programmer	N
E8405-3	Mains Remote Control Transmitter	H
E8405-4	Centronics Interface	F
E8405-6	Drum Synth	F
E8406-1	Oric EPROM Board	O
E8406-2	Spectrum Joystick	E
E8406-3	Audio Design RIAA Stage	G
E8406-4	AD Buffer/Filter/Tone	H
E8406-5	AD Headphone Amp	F
E8406-6	AD Preamp PSU	K
E8406-7	AD Power Amp	H
E8406-8	AD Power Amp PSU	J
E8406-9	AD Stereo Power Meter	F
E8406-10	AD Input Clamp	C
E8407-1	Warlock Alarm	M
E8408-2	EPROM Emulator	N
E8408-3	Infrared Alarm Transmitter	E
E8408-4	Infrared Alarm Receiver	F
E8409-1	EX42 Keyboard Interface	F
E8409-2	Banshee Siren Unit	F
E8410-1	Echo Unit	F

TO: ETI READERS' SERVICES DEPARTMENT
Argus Specialist Publications Ltd,
9 Hall Road, Hemel Hempstead,
Herts HP2 7BH

Please supply:

No. required per type	Board reference number	Price letter	Price each £	Total for board type £
E	-	£ .	p	£ . p
E	-	£ .	p	£ . p
E	:	£ .	p	£ . p
E	-	£ .	p	£ . p

POSTAGE & PACKING £ 0.75p

TOTAL ENCLOSED £ . p

ORDER TO BE SENT TO: (BLOCK CAPS PLEASE)

Name

Address

.....

Postcode

(Make cheques payable to ASP Ltd)

ACCESS and VISA credit card orders can be taken on (0442) 41221
(office hours only).

E8410-2	Digital Cassette Deck	N
E8410-3	Disco Party Strobe	H
E8411-5	Video Vandal (3boards)	N
E8411-6	Temperature Controller	D
E8411-7	Mains Failure Alarm	D
E8411-8	Knife Light	D
E8411-9	Stage Lighting Interface	F
E8411-10	Perpetual Pendulum	E
E8412-1	Spectrum Centronics Interface	F
E8412-4	Active - 8 Protection Unit	F
E8412-5	Active - 8 Crossover	F
E8412-6	Active - 8 LF EQ	F
E8412-7	Active - 8 Equaliser	F
E8501-3	Digital Delay (2 boards)	T
E8502-1	Digital Delay Expander	N
E8502-2	Data Logger	J
E8503-1	Combo Preamplifier	F
E8503-2	THD Meter mV & oscillator bds (2 boards)	K
E8503-3	THD Meter Mains PSU	F
E8504-1	Framestore Memory	M
E8504-3	Framestore Control	N
E8504-4	Buzby Meter	E
E8504-5	CCD Delay	F
E8505-5	Stereo Simulator	F
E8506-1	Audio Mixer Main	J
E8506-2	Audio Mixer PSU	F
E8506-3	Audio Mixer RIAA	D
E8506-4	Audio Mixer Tone Control	D
E8506-5	EPROM Prog MKII	O
E8508-1	RCL Bridge	N
E8508-2	EX42/BBC Interface	E
E8508-3	EPROM Emulator	L
E8509-1	Spectrum	F
E8509-2	Direct Injection Box	E
E8510-9	Sunrise Light Brightener	K
E8511-1	MTE Waveform Generator	H
E8511-2	Millifaradometer	H
E8511-3	Cymbal Synth	J
E8511-5	Chorus Effect	H
E8511-7	Enlarger Exposure Meter	F
E8511-8	Switching Regulator	E
E8511-9	Second Line of Defence	M
E8512-1	Specdum connector	F
E8512-2	MTE Pulse Generator	H
E8511-3	Specdum	L
E8601-2	Walkmate	L
E8601-3	MTE Counter-timer	M
E8602-1	Digitbaro	O
E8603-2	Programmable Logic Evaluation Board	H
E8603-3	Sound Sampler Analogue Board	R
E8604-1	JLLH PA PSU	H
E8604-2	Matchbox Amplifier	C
E8604-3	Matchbox Amp Bridging Version	C
E8604-4	MTE Analogue/Digital Probe	M
E8605-1	Microlight Intercom	E
E8605-2	Baud Rate Converter	M
E8605-3	Baud Rate Converter PSU Board	G
E8605-4	Portable PA	H
E8606-1	Midi-CV Converter Board	H
E8606-2	Midi-CV Converter PSU	D
E8606-3	Troglograph	F
E8606-4	80m Receiver	H
E8606-5	Sound Sampler	R
E8607-1	Direction	E
E8607-2	Upgradeable Amp, MC stage (Stereo)	G
E8607-3	BBC Motor Controller	F
E8608-1	Digital Panel Meter	G
E8608-2	Upgradeable Amp, MM stage (mono)	H
E8609-1	Mains Conditioner	E
E8609-2	Experimental preamp	F
E8609-3	Upgradeable amp, Tone board (mono)	H

E8609-4	Upgradeable amp, Output board (mono)	F
E8610-1	Audio Analyser Filter Board	L
E8610-2	Audio Analyser Display Driver	K
E8610-3	Audio Analyser Display	H
E8610-4	Audio Analyser Power Supply	F
E8611-1	Audio Switcher (2 bds)	H
E8611-2	PLL Frequency meter (4 bds)	Q
E8611-3	Upgradeable Amp PSU	J
E8611-4	Call meter, main bd.	O
E8611-5	Call meter, interface bd	N
E8612-1	Bongo Box	J
E8612-2	Biofeedback monitor (Free PCB)	E
E8701-1	RGB Converter	F
E8701-2	Mains Controller	D
E8701-3	Flanger	H
E8701-4	Audio Selector main board	M
E8701-5	Audio Selector PSU	H
E8701-6	Tacho-Dwell	F
E8702-1	Ratemeter main board	K
E8702-2	Ratemeter ranging board	F
E8702-3	Photo Process Controller (3bds)	O
E8702-4	LEDline display board (2 off)	K
E8702-5	LEDline PSU and controller (2 bds)	G
E8703-1	Capacitometer	F
E8703-2	Geiger Counter	L
E8703-3	Credit Card Casino	E
E8704-1	BBC micro MIDI interface	L
E8704-2	ETI Faker patch box	H
E8704-3	24Hr. Sundial	E
E8705-3	MIDI Keyboard keyswitch boards (3 boards)	W
E8705-4	Batlite	C
E8705-5	Budget Power Meter	E
E8706-1	Hi-fi Power Meter	N
E8706-2	MIDI Keyboard CPU	U
E8706-3	MIDI Keyboard Front Panel	O
E8706-4	Flame Simulator	G
E8707-1	MIDI Keyboard PSU	H
E8707-2	Telephone Alarm	J
E8707-3	Nuclear Strategy Simulator	J
E8708-1	Remindalite	F
E8708-2	Rear Wiper Alarm	G
E8708-3	Rev Counter	F
E8708-4	Car alarm	F
E8708-5	Knight Raider	J
E8709-1	Boiler Controller	G
E8709-2	Amstrad Sampler (2 bds)	P
E8709-3	Portable PA	G
E8709-4	EEG Monitor (2 bds)	L
E8710-1	Concept CPU board	N
E8710-2	Concept Power board	K
E8710-3	Concept display board	G
E8710-4	Hyper-Fuzz	F
E8710-5	Big Digits digit board	N
E8710-6	Big Digits minute board	F
E8710-7	Big Digits battery board	G
E8711-1	Quiz Controller	E
E8711-2	256K Printer Buffer	N
E8712-1	Heating Management System	O
E8712-2	SWR Meter	H
E8712-3	Dream Machine (free PCB)	D



FM Stereo Tuner (February-April 1987)

In the parts list on page 49 of the February issue, C2 and C3 are listed as 270n types. This line should refer to C2 and C23 and the value should be 470n. In Fig. 7 the un-labelled PCB pad in the top right-hand corner is the +15V input from the power supply. In Fig. 1 in the April issue there is an un-labelled arrow leading from the top of the diagram. It should be marked CONTROL VOLTAGE OUTPUT TO MUTING CIRCUIT. The arrow to the right of the un-labelled one is marked '+5V IN' and should read '+15V IN'. In Fig. 6 in the April issue, C63 and C64 should be shown as 330p, not 3300p. On page 36 of the April issue, in the first paragraph, the reference to R62 should read R64.

Flat Alarm (June 1987)

In the circuit diagram Q2 is shown as an NPN transistor. It should be a PNP device as given in the parts list. IC4 is given in Fig. 2 as a 74LS260 and C5 as 470n. They should be 74LS132 and 4p7 as in the parts list. R13 is incorrectly given as 280R in the parts list instead of 270R.

Nuclear Strategy Simulator (July 1987)

The bridge rectifier (BR1) on the overlay diagram has no polarity markings. It should be positioned with the positive at bottom left, connected to the track which connects to IC8 IN and C4 positive.

Telephone Alarm (July 1987)

In the component overlay (Fig. 2) IC1 and IC2 should be swapped. In addition the capacitor to the right of IC1,2 is C1 and the inductor between them is L1. The unmarked resistor to the left of L1 should be a wire link.

Kappelmeisters (July 1987)

The position of the speaker port in the front panel was omitted from Fig. 2. This should be a 7 1/4x4 1/2in ellipse centred across the panel with its top edge 2 1/2in below the panel top.

Knight Raider (August 1987)

In Fig. 1(a) pins 4 and 5 of IC1 are swapped. IC2-3 show the correct pin-out.

Car Alarm (August 1987)

In Fig. 1 Q7 is not numbered and its emitter is shown unconnected. This connects to earth. The transistors in the parts list went a little awry. Q2-6 are BC237 and Q7 is a TIP31.


Boiler Controller (September 1987)

In Fig. 2 (a) the primary of T2 is shown connected to Earth. This should be neutral. In Fig. 2(b) one of the bridge rectifier diodes, D6-9, is shown the wrong way around. This is correctly shown in Fig. 5.


ETI Concept (October 1987)

The Power Board parts list wrongly lists R6 as 270R. This should be 270k. Also, note that the power board's 0V rail must not be connected to Earth or the 0V rail of the CPU board.


PCB FOIL PATTERNS

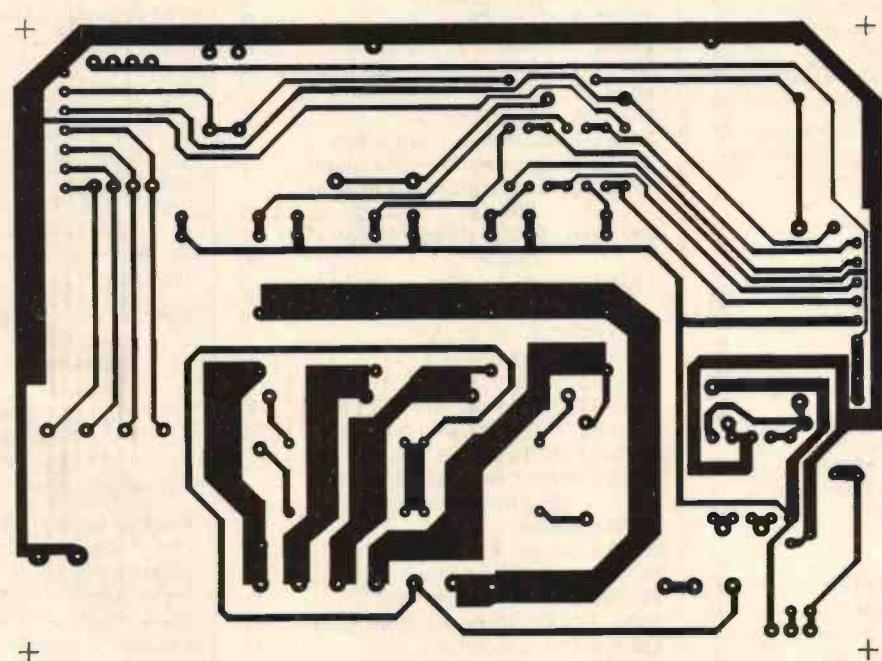


The Heating Management power board foil

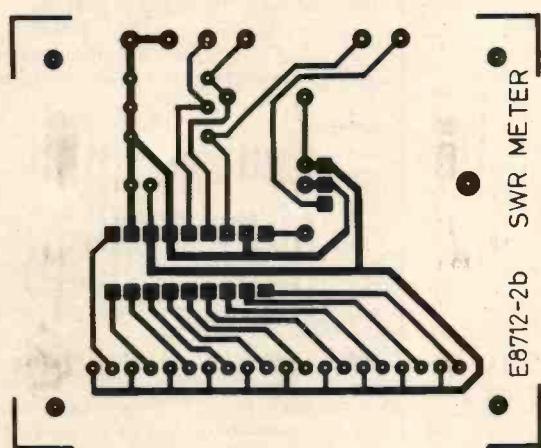

The SWR meter display board

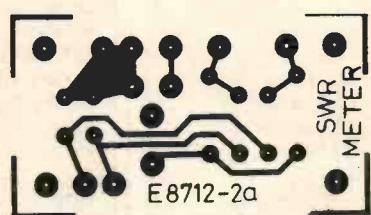


The SWR meter sensor board

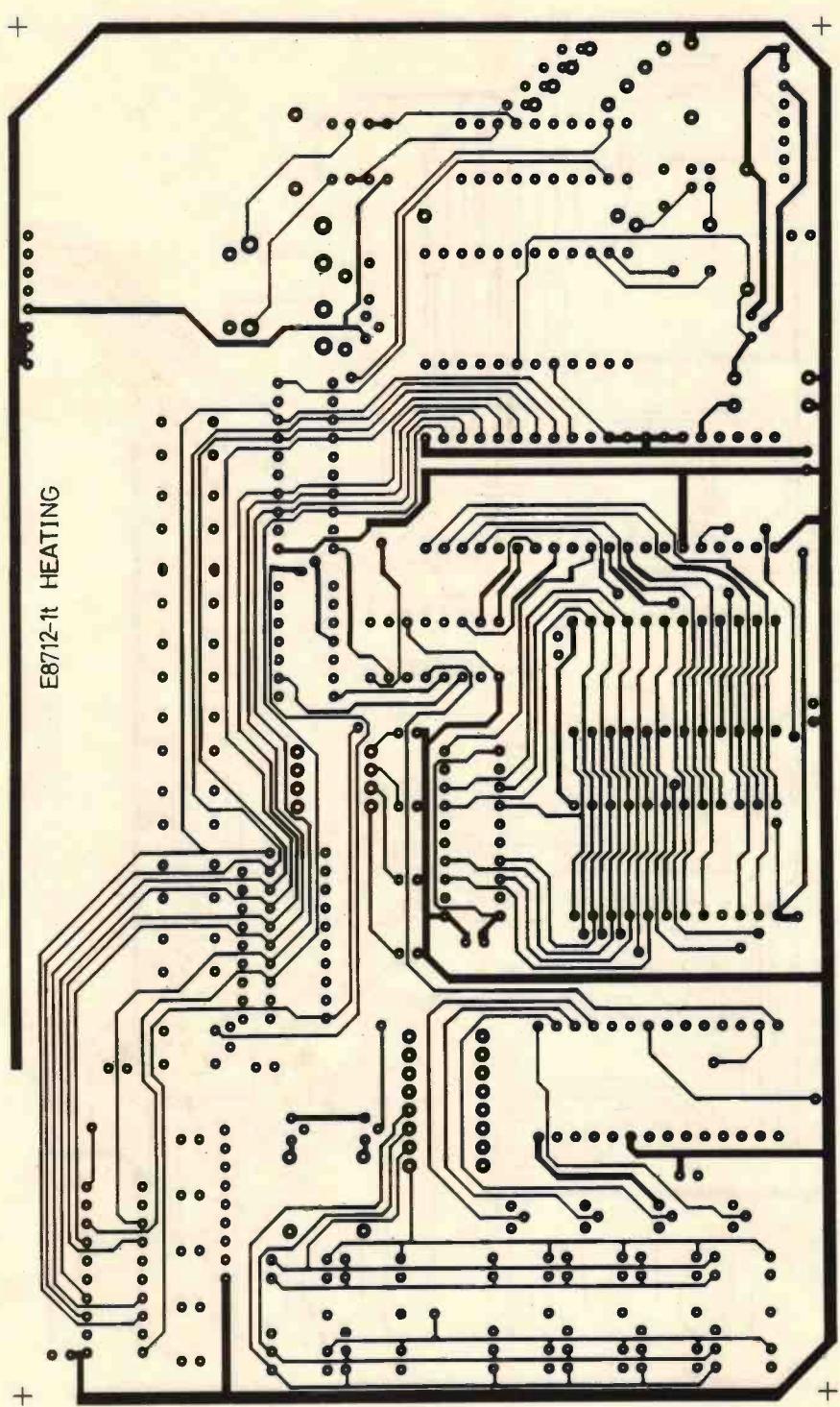

The Heating Management System main board topside foil

PCB FOIL PATTERNS

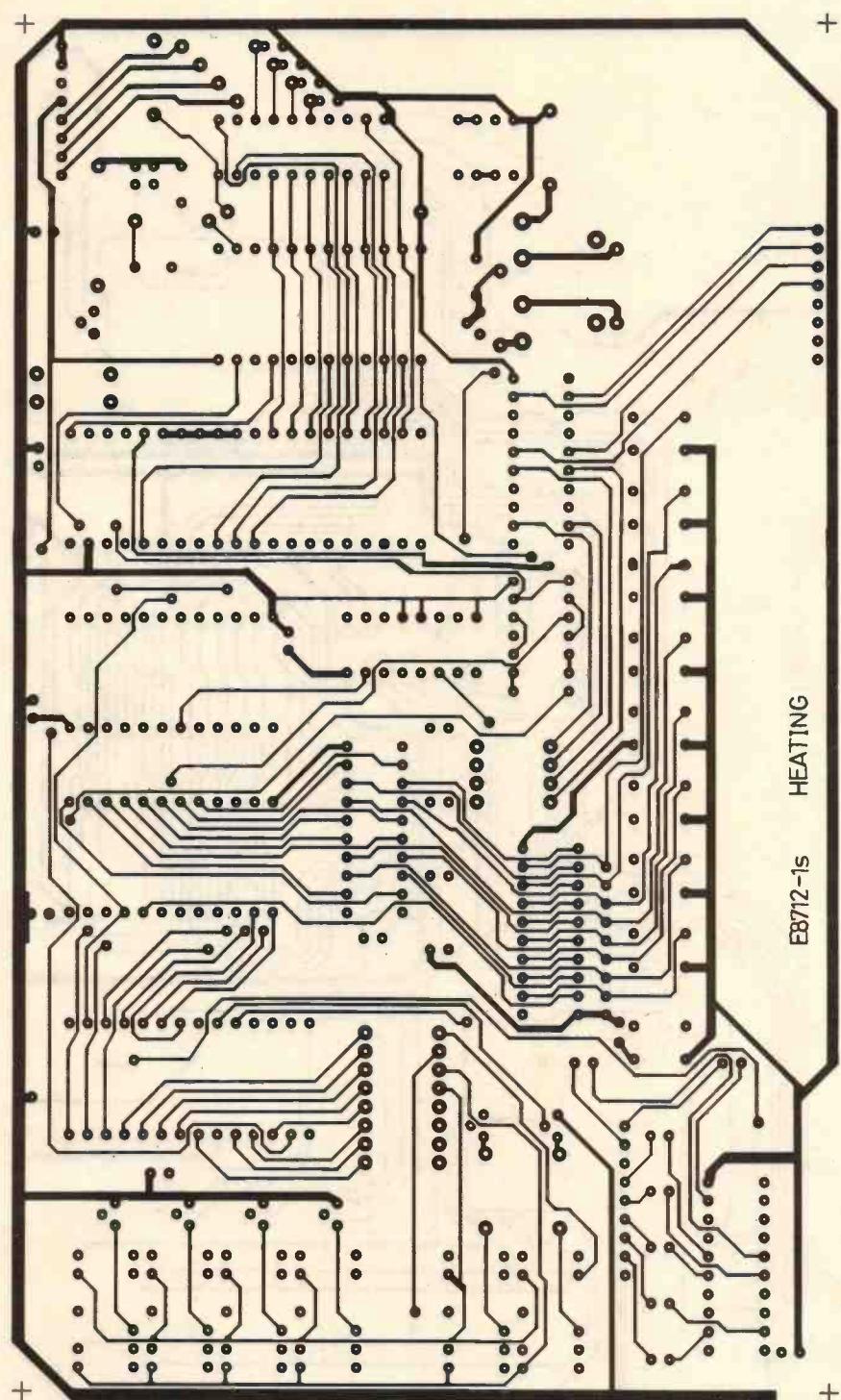

The foil for the solderside of the Heating Management main board

DISK DRIVES • COMPONENTS • CONNECTORS • ELECTRO-MECHANICAL, PCB AND CABLE ASSEMBLIES

Electro Mech Industries Limited

Unit 2, Wessex Industrial Estate, Station Lane, Witney, Oxfordshire. Telephone (0993) 75827 or 76605 Telex: 83147 Attn. ELMEC Fax: 0865-726753 (GRP 2*3)



IBM COMPATIBLES

Superb quality at sensational prices by Beltron Computer Systems Inc.

	EX VAT	P&P
XT COMPATIBLE	£79.00	£0.00
AT COMPATIBLE	£124.50	£0.00
TURBO/AT GEA SYSTEM	£164.00	£0.00
Fully Specified Range of Options/Peripherals available at incredible low prices		
Demonstrations can be arranged by appointment. Write/Phone for brochure & price list.		

MEMOTECH

	60.00	5.00
MTX512 80K RAM	60.00	5.00
MTX612 Series 2 256K RAM	87.00	5.00

	225.00	5.00
MCL 3.5" CP/M Disc Drive Upgrade	225.00	5.00

SPECIAL OFFERS

3.5" CP/M Disc Drive Upgrade, MTX512 Series 2 Computer, 12" HD-Ram, 12" HD-Ram Comprehensive Software Package, Detailed Manuals, 10 x 3.5" Diskettes

All this for £399.95 inc. VAT. Delivery at £10.00 extra

Various Expansions Available

BBC

Master 128

Compact Entry System

Computer Control System

Archimedes Basic 305 System

Archimedes Basic 310 System

Full range of accessories - Send for price list.

£39.00 7.00

£60.00 7.00

£54.00 7.00

£79.00 7.00

£87.00 7.00

£87.00 7.00

EMI DISC DRIVE RANGE

BBC DISC DRIVES

All supplied with Leads, Manual & Utilities Disc

Price (Ex VAT)

5.25" DRIVES, WITHOUT POWER SUPPLY

Single 200K Drive, 40 Track D/S

Single 400K Drive, 40/80 Switchable

Dual 400K Drive, 40 Track D/S

Dual 400K Drive, 40/80 Switchable

£95.00

£112.00

£183.00

£214.00

5.25" DRIVES, WITH POWER SUPPLY

Single 200K Drive, 40 Track D/S

Single 400K Drive, 40/80 Switchable

Dual 400K Drive, 40 Track D/S

Dual 400K Drive, 40/80 Switchable, horizontally mounted monitor stand (Master Version)

£265.00

3.50" DRIVES, WITHOUT POWER SUPPLY

Single 400K Drive, supplied in dual case, with blanking plate, to allow easy upgrade to dual drive.

£95.00

Dual 400K Drive

£165.00

3.50" DRIVES, WITH POWER SUPPLY

Single 400K Drive, as above

£110.00

Dual 400K Drive, as above

£180.00

NB: Please add £3.00 P & P per Single Drive, and £5.00 P & P per Dual Drive

Please add £7.00 delivery on Monitors, £3.00 on Modems

5 1/4" 500K DS/DD MITSUBISHI DISC DRIVE £75.00

5 1/4" IMB DS/DD MITSUBISHI DISC DRIVE £80.00

PHILIPS 8833 COLOUR MONITOR with BBC lead £225.00

SPECIAL OFFER

5 1/4" 500K DS/DD MITSUBISHI DISC DRIVE £75.00

5 1/4" IMB DS/DD MITSUBISHI DISC DRIVE £80.00

PHILIPS 8833 COLOUR MONITOR with BBC lead £225.00

£95.00

£112.00

£183.00

£214.00

£265.00

£95.00

£110.00

£180.00

£225.00

£95.00

£112.00

£183.00

£214.00

£265.00

£95.00

£110.00

£180.00

£225.00

£95.00

£112.00

£183.00

£214.00

£265.00

£95.00

£110.00

£180.00

£225.00

£95.00

£112.00

£183.00

£214.00

£265.00

£95.00

£110.00

£180.00

£225.00

£95.00

£112.00

CRICKLEWOOD

ELECTRONICS LTD

WRITE OR PHONE NOW FOR OUR FREE,
10TH EDITION, MID '87
PINK COMPONENTS CATALOGUE



HUNDREDS OF LOWER PRICES HUNDREDS OF NEW DEVICES

from the U.K.'s number one 100% components shop - no gimmicks, no gadgets, no computers, just millions of components, all easily available by mail order, calling at shop, or credit card telephone orders. Just pick up, or a pen, to get the catalogue (no SAE required) - posted **FREE** to any country on the globe.

CRICKLEWOOD ELECTRONICS LIMITED
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
Tel: 01 450 0995 & 01 452 0161 Telex: 914977



You've finished your project . . .

. . . Now COMPLETE it!

Build an enclosure to fit it exactly


ENCORE has been developed and designed to make any enclosure to the exact dimensions you want. Brand new **ENCORE** is an ingenious but simple extruded strip system that you can shape, bend, file and cut. Incorporated in the section profile is a screw fastening hole. When the plastic sheet is cut to size the drilled holes will register exactly using the jig and drill supplied with each kit.

Our trial kit is just £11.50 which includes delivery and the free jig and drill.

Try **ENCORE** for your current project you'll be surprised what a clean professional finish it gives to any kind of project.

Send for
full details.
FREE
LEAFLET
and price
list

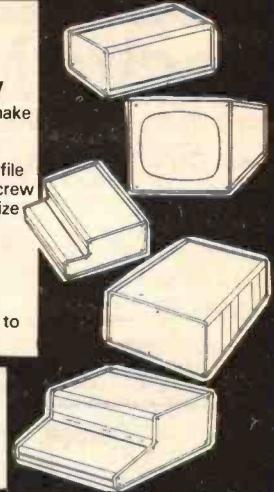ENCORE ENCLOSURES
UNIT 3
WILLAND INDUSTRIAL ESTATE
CULLOMPTON
DEVON EX15 2QW
Phone: (0884) 820955



TRANSFORMERS EX-STOCK

MAINS ISOLATORS		30/15V or 15-0-15V			24/12V or 12-0-12V			80VA	
Prl/Sec	120V X 2 OR	30V	15V	P&P	12V	24V	£ P&P	250	10.49 & 2.56
240 to 415/440V (60-1000VA Tapped Secs)		0.5	1	3.86	1.41	0.3	0.15	500	16.12 & 2.56
20VA	£7.80	P 2.18	2	5.24	1.70	0.5	0.25	1000	28.79 3.25
80	11.50	P 2.31	2	6.00	1.92	1	0.5	1500	34.17 3.68
100	14.43	P 2.31	3	6.82	2.00	1	0.5	2000	51.09 4.62
200	19.03	P 2.10	4	A 8	11.72	2.20	4	3000	86.88 6.30
250	23.01	3.24	5	M 10	14.49	2.31	6 A 3	4000	112.78 OA
500	35.45	3.66	6	P 12	16.40	2.55	8 M 4	5000	190.50 OA
1000	64.28	4.62	8	S 16	21.95	2.60	12 P 6	10KVA	13.20 2.25 239.53 OA
1500	82.92	5.85	10	V 20	24.22	2.84	16 S 8	20	21.17 3.04
3000	99.76	6.76	12	Z 24	28.07	3.95	30	30	240V Cable Input
6000	138.89	OA	15	Y 30	31.66	3.51	30	60	115V USA Socket Outlets
6000	298.89	OA	20	40	43.22	5.95	40	80	20VA £8.34 HV 1.76
50/25V or 25/0-25V		60/30V or 30-0-30V			2X30V Tapped Secs			83	11.33 (4) 1.87
2X25V Tapped Secs		50V	30V	P&P	60V	30V	£ P&P	150	14.57 1P 2.20
50V	25V	0.5	1	5.01	1.76	0.5	1	250	17.87 3.02
1M	5.00	1.50	1	A 2	5.69	1.85	100W TO 4KW	500	29.32 3.19
2P	8.84	2.00	1	M 4	8.87	1.91	CONCATENATED VOLTAGE	1000	41.85 4.34
3S	6	12.54	2.25	P 6	11.15	2.20	TRANSFORMERS FOR	2000	52.30 5.20
4	8	17.16	2.58	S 8	16.12	2.34	Spike-free stable mains	3000	105.26 OA
6	12	21.84	2.79	S 10	23.23	2.78	ALSO VALVE MAINS	110V to 240V Cased	
8	16	30.89	3.15	S 12	26.50	3.02	OUTPUT & MATCHING	Transformers now available	
10	20	36.66	3.60	S 8	37.25	3.62	TRANSFORMERS	Full range AVO's, Meggers	
12	24	47.27	3.80	S 10	43.37	3.99	WINDING SERVICE	TOROIDALS	
				20	49.98	4.65	3VA TO 18KV Stock items by return	Wound to Order	

Unit 211, Stratford Workshops,
Burford Road, London E15 2SP

BARRIE ELECTRONICS LTD
Tel: 01-555 0228 (3 lines)

SPECIAL OFFER FOR SPECTRUM AND BBC MICRO OWNERS

Now your computer can take control for an affordable price. These tried and trusted interfaces from DCP Microdevelopments are offered at £20 off the normal price.

Both units are extremely easy to use from both Basic and assembler/machine code and are supplied ready built and complete with all the documentation you need.

To order by post fill in the form below (or a copy) and send it with your remittance to **ASP READERS' SERVICES (RO ET5/6)**

9 Hall Road, Maylands Wood Estate,
Hemel Hempstead, HP2 7BH

Please make cheques payable to ASP Ltd. Overseas orders add £5 (Interspec) or £10 (Interbeeb) for airpost. Access and Visa card holders can also place their order by phone on (0442) 41221 Allow 28 days for delivery.

Please supply Interspecs (RO ET5) at £29.95 plus £1.95 p&p per order.

Please supply Interbeeb (RO ET6) at £49.95 plus £1.95 p&p per order.

Name


Address

.....

Please debit my ACCESS/VISA card

No to the sum of

£ Signed:

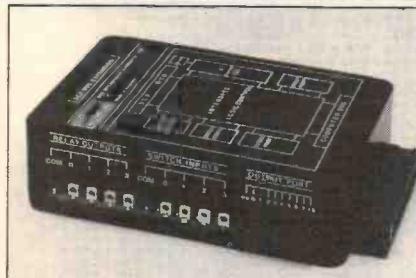

INTERSPEC £29.95

The Interspec unit plugs directly onto the expansion edge connector of the Spectrum to provide a full range of interfacing facilities.

The unit is housed in a plastic case approximately 4½x3x1in which contains the top quality double sided PCB and interface connections.

- 8-bit input port
- 8-bit output port
- four switch sensor inputs
- four relay-switched 12V 1A outputs
- eight channel multiplexed analogue to digital converter
- 15-way expansion bus

All sections of the interface are I/O port mapped and designed for maximum compatibility with existing Spectrum peripherals. Power is supplied through the Spectrum edge connector.

The expansion bus provides all the data and address/control signals for the addition of further DCP modules or home-built devices. Connection is by multi-way PCB connector and all the information required for adding further devices is given.

INTERBEEB

£49.95


The Interbeeb unit connects to the BBC micro's 1MHz bus expansion connector and is supplied complete with its own power supply unit.

The interface unit is housed in a plastic case approx 4½x3x1in which contains the top quality double sided PCB and interface connectors.

- 8-bit input port
- 8-bit output port
- four switch sensor inputs
- four relay-switched 12V 1A outputs
- eight channel multiplexed analogue to digital converter
- precision 2.5V reference
- external power supply
- 15-way expansion bus

All sections of the interface are memory mapped in the 1MHz expansion map for maximum ease of use and compatibility with existing peripherals.

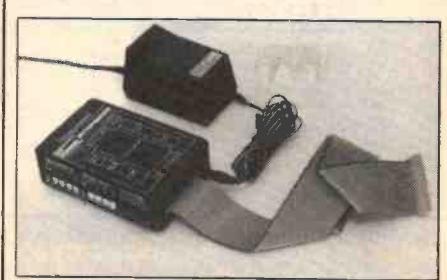The expansion bus provides all the data and address/control signals for the addition of further DCP modules or home-built devices. All the information required for using additional devices is included.



ELECTRONICS TODAY INTERNATIONAL

CLASSIFIED

Lineage:

44p (VAT excl) per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£12.20 per single column centimetre + VAT

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 292



Send your requirements to:
Julie Capstick
ETI Class. Dept.,
ASP Ltd.,
1 Golden Square,
London W1.

FOR SALE

LYTHALL COMMUNICATIONS 49a LINDEN WAY, HADDENHAM, ELY, CAMBS, CB6 3UG. TEL (0353) 740664

CORDLESS TELEPHONE

Range 700 feet, re-dial, call, mute etc. 240v AC power (BABT approved). £89.95p inc P&P.

ANSAFONE

240v AC power, complete, (BABT approved) £99.95p inc P&P

MODEMS(all RS232 to micro)

1. V23 (1200/75 baud) such as used by PRESTEL and XMODEM type protocols. Autoanswer/originate. Duplex. Inc COMSTAR II ROM comms software for BBC micro series. £149.99p inc P&P.
 2. V21 (300/300 baud) + V23(1200/75 baud). Call progress mon speaker, processor controlled, Autodial (pulse/DTMF) with 32 number store, Autoanswer, Duplex, Hayes Compatible so requires no special software. £199.95p inc P&P.
 3. V21 (300/300) + V23(1200/75). Autodial (pulse/DTMF) with 64 number store, Autoanswer (V25 protocols), Duplex, Speed buffering, Hayes command set, Parallel printer port, date and time stamp, BABT approved. £399.00p inc P&P.

COMPUTER SWITCH (patent pending)

Enables your computer to switch external low power circuits (eg Buzzers, Radio's, Alarms, Indicators etc) on and off under software control. Compatible with most computers eg APPLE, ATARI, BBC, EINSTEIN, SINCLAIR. Powered by internal PP3 battery (supplied). Supplied with detailed instructions and example programmes (including morse-trainer+clock/timer) £34.99p inc P&P. Sample programmes available on 5.25" disk for Apple II, add £4.95p

MODEM ELIMINATOR

Enables you to get programmes over wires to another computer of the same type. Internally powered from PP3 battery (supplied). Not suitable for use with other modem. Supplied with detailed instructions. £26.95p inc P&P.

Morse Trainer for Tatung Einstein on disk, (using internal speaker) £5.95p inc P&P. Other software for Einstein SAE.

Send SAE for further details of any item, or send Cheque to O

LYTHALL COMMUNICATIONS, 49 LINDEN

WAY, HADDENHAM, ELY, CAMBS, CB6 3UG.

Accept ACCESS & BARCLAYCARD

MEMORIES + MICROS

2764-25	£2.65	27128-25	£2.85
27256-25	£4.95	27512-25	£8.95
4164-15	£1.10	41256-15	£2.75
6116LP3	£1.95	6264LP-15	£3.30
62256LP-12	£10.95	68008PB	£15.95
68008PB	£19.95	68010PB	£29.95
68681	£9.95	68230	£7.95

Prices include P&P. Please add 15% VAT.
 Discounts for quantity.

Phone 0990 23948

M G COMPUTERS LTD.

4 Victoria Road, South Ascot,
 Berks SL5 9DA.

MISCELLANEOUS

HEATHKIT U.K. Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

WAVETEK, 2MHz function generator - £200 o.n.o. as new. Tel. Redruth 0209 214688.

DEVELOP YOUR ADVERTISING CAMPAIGN WITH ETI— NEW YEAR COPY DEADLINES FEBRUARY ISSUE - 23rd NOV 1987

SPECIAL OFFERS

CONQUER ELECTRONICS OFFERS A WIDE RANGE OF COMPONENTS

(Resistors, Transistors, Capacitors, Diodes, Valves, IC's, Etc.) AT UNBELIEVABLE PRICES!
 DISCOUNTS ON LARGE ORDERS MANUFACTURE, DESIGN & REPAIRS UNDERTAKEN
 For more information or a free catalogue ring: WOKING (04862) 71897 or write to:
 CONQUER ELECTRONICS, 25 Windsor Way, Maybury, Woking, Surrey GU22 8DJ.

CASSETTE MOTORS large and small 2 for £1.00. Mono and stereo cassette tape heads. 2 for £1.00. Microphone small for cass. tel etc. 2 for £1.00 Solar Cells at 35p each. Please add 75p p&p, no VAT. Access card accepted. Golden Orange Supplies, Brockhollands Road, Woodside, Bream, Lydney, Glos. Tel: 0594 563009.

SAGE AUDIO AMPS revealed. Full internal circuits, valves, special components sources. Super Mos/Amp. Detailed operating description for less than cost of module £35. Special offer Supermos £55 brand new from Sage 20 only. Send cheques P.O. to Audio Electronics, 4 John Court, Hoddesdon, Herts.

FREE MEMBERSHIP to a new NATIONAL ELECTRONICS CLUB.
 For details and a free gift of components worth over £10 send only £1.00 p&p to Woodside, Dowsett Lane, Ramsden Heath, Essex CM11 1JL.

WANTED

WANTED urgently required to complete project Editor Assembler for Tandy Colour Computer. Must be in cartridge form. Write Mr. G. Moodie, 44 Seafield Rd., Edinburgh EH6 7LQ Scotland.

IDEAS/INVENTIONS wanted. Call I.S.C. 01 434 1272 or write, Dept ASP 99 Regent St, London W1.

Turn your surplus transistors, IC's etc., into cash. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. Contact:

Coles Harding & Co.
 103 South Brink
 Wisbech, Cambs.

ESTABLISHED OVER 10 YRS
 Tel: 0945 584188

SURVEILLANCE

ESKAN ELECTRONICS

(MANUFACTURERS AND SUPPLIERS OF SURVEILLANCE AND AUDIO EQUIPMENT)

MICRO BUG

SK1 Miniature Transmitter 20mm x 47mm x 20mm, extremely sensitive. Operates from 1.5v battery, elegant metal box included.

Ready built + tested only. £29.50
 Kit Form £24.90

EXTRA MINIATURE TRANSMITTER

EK2 25mm x 30mm x 9mm
 Ready built + tested £49.00

Kit Form £37.95

HIGH POWER FM RADIO TRANSMITTER

EK65, 65W adjustable frequency Mains operated. £650 + £35 p&p (Operation in the UK illegal without licence).

AUTOMATIC TELEPHONE MONITOR

SK19 ready built + tested £34.50
 Kit Form £29.95

Many other surveillance equipment available. Send large S.A.E. for catalogue.

SOUND TO LIGHT UNIT

SK72 separate sensitivity, bass, treble and mid-range frequency controls, designed and manufactured to highest professional standard.

Ready Built..... £39.95 p&p £3.50
 Kit Form £21.95

Casing £11.95

SK70 sound to light control unit

Kit Form £14.95

Send Cheque or P.O. payable to:

ESKAN ELECTRONICS

172 Caledonian Road,

London N1 0SG.

Tel: 01 278 1768

VISA

Trade and Export Enquiries Welcome

SWITCHES

VOICE/SOUND ACTIVATED SWITCHES easy to follow diagrams and uses only £1.00. Components and P.C.B.'s available: Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.

USE 'ELECTRONICS TODAY INTERNATIONAL' TO BUY, SELL & EXCHANGE ALL YOUR PRODUCTS & SERVICES

ELECTRONIC COMPONENTS

BRYANT
ACOUSTIX

5 BELLE VUE TERRACE, GILESGATE, MOOR, DURHAM,
DH 1-2 HR. TEL (091) 3864500.

FREE!

OCT - JAN CATALOGUE NOW AVAILABLE

Please enclose a 4x9" SAE for a copy of our new 1987 catalogue, detailing Accessories, Books, Cable, Caps, Connectors, Semiconductors, Led's etc. Trade list also available.

SPECIAL OFFER LIST SENT OUT WITH ALL CATALOGUES

100's of new items in stock.

8mm LED's NOW IN STOCK

ALARMS

ALARMS

FREE BOOKLET
on
BURGLAR ALARMS
with
LOWEST U.K. DIY PUBLISHED PRICES
PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
217 WARRECK MOOR
AINTREE, LIVERPOOL L9 0HU

AUDIO

HI-FI CLASS A MOSFET POWER AMPLIFIERS

See review
ETI May 87

50W TO 150W, 4-16ohms one unique module

See ETI Oct 87 ad
for more details

Are you still listening to crossover distortion with a class AB amp? Switch to SAGE class A and you'll never switch again.

All CLASS AB amps including MOSFET generate crossover distortion due to storage effects within the O/P devices, this is particularly true of Darlington transistors. The SAGE active bias system is a unique circuit eliminating crossover action completely with far less distortion and an order of magnitude higher speed transient response allowing one to hear far more musical detail than any other class. The specifications speak for themselves.

UNPARALLELED TECHNICAL PERFORMANCE - SUPERIOR 'AUDIO GRADE' COMPONENTS

No other manufacturers amps, kits, or ready built units can match our technical performance, this performance and the use of the very best 'Audio Grade' components inc Filmcaps, (extended foil and propylene). Holco resistors and matched transistors/FET's built exclusively to our spec, make these amplifier modules totally unique and put them soundly in a class of their own. In extremely critical areas such as gain control etc where even BULK FOIL resistors will not do, we use 'exact value' laser trimmed SMD resistors exhibiting totally unmeasurable resistance/voltage change and 5 times less stray inductance.

SPECIFICATION O/P 50W-150W THD 0.0002% Stewrate 250V/us. Frequency response 5Hz to 200kHz, S/N 120dB. Damping factor 800, Sens 0.775V, load Z 4-16.

Full PSU components available in high quality audio electrolytics, 25A & 35A bridge rectifiers, transformers etc. **SPECIAL OFFERS** This issue only Buy two Supermos amps, two 36A bridges and two 15, 000uF 63V grade one Eels (CAPST) and receive two more CAPST free, worth £33. Send £170 plus £5 p&p, limited stocks! Offer closes Nov. 30. Several fully built cased monoblock units are also available at £150 plus £5 p&p.

Send SAE or 4IRC's for more details or £2.50 for Supermos Applications booklet (refunded on purchase) **SUPERMOS Modules £65 total Inc P&P**

SAGE
AUDIO

Construction House, Whitley St, Bingley, Yorks, BD16 4JH
Export Facilities Worldwide. Tel: 0274 568647, TLX 517783, Fax 551065

COMPONENTS

PROMs - EPROMs - PALs ANY PROGRAMMABLE IC SUPPLIED OR BLOWN

Typical prices (excluding VAT)
(Data Entry P&P extra)

2716 £4.20 2732 £3.85
2764 £2.85 2718 £4.40

BIPOLE PROMs from £1.35
e.g. 82S123, 18S030, 74S288

PALs, PLDs etc. from £3.26
e.g. 82S153, 16L8, EP310

Full design and prototyping service.
Any quantity programmed - SAE or phone for details.

P.L.S., 80 Central Road,
Worcester Park, Surrey, KT4 8HU
Phone: 01-330 6540

3" CF2 disks £2.00

3.5" unbranded DS disks £1.20

5.25" unbranded disks, DS 96 £0.38

bulk storage, 5.25"/50 £6.90

bulk storage, 3.5"/80 £8.00

Epson MX/FX80 ribbon £2.60

Epson MX/FX100 ribbon £3.10

Epson LX80/86 ribbon £2.50

M/Tally MT80 ribbon £2.90

printer cable, PC1512/IBM £7.95

All prices Inc. P&P, please add VAT at 15%

T-systems Ltd, The Signal Cabin,
61 High Street, Orpington, Kent.
BR6 0JF.

Carbon Film Resistors 1W E24 series 0.51R to 10MO -1p 100 off per value-75p 1000 off in even hundreds per value-£7 Metal Film 1W 10R to 1MO 5% E12 series-2p 1% E24 series-3p 1/2 Watt metal/carbon film E24 series 1R to 10MO-1p 1 Watt metal/carbon film E12 series 4R7 to 10MO-5p BC107/8/9-12p BC547/8/9-8p BC182L 184L-10p BFY50/51/52-20p 2N3055-50p TIP31A.32A-25p TIP41.42-40p

Tantalum head subminiature electrolytics (Mids/Volts) 0.1/2.2/35, 0.47/35, 3.3/16-14p 4.7/35-15p 2.2/35, 4.7/25, 10/5-15p 4.7/35, 6.8/16-16p 10/16, 22/26-20p 22/16-30p 33/10-30p 47/10-35p 100/6-40p

Aluminum Electrolytics (Mids/Volts) 1/50, 2/25/25, 4.7/25, 4.7/50, 10/16, 10/25, 10/50-5p 22/16, 22/25-5p 22/50, 47/16, 47/25, 47/15-6p 100/16, 100/25-7p 100/50-12p 100/100-14p 220/16-18p 220/25, 220/50-10p 47/16, 47/25, 47/10-25p 1000/25-18p 1000/35, 220/25-22p 4700/25-70p

Minature Polyester Capacitors 250p Wkg. Vertical Mounting .01, .05, .022, .033, .047, .068-4p 0.1-5p 0.15, .22-6p 0.47-8p

Mylar Capacitors 100V Wkg. Vertical Mounting E12 Series. 1000p to 8200p-3p .01 to .068-4p 0.15p 0.15, 0.22-6p

Subminiature Ceramic Plate 100V Wkg. E12 Series Vertical Mounting. 2% 1P8 to 47P-3p 56P to 330P-4p 10% 390P to 4700P-4p Ceramic plate/disc E6 Series 50V 22P to .047-2p

Polystyrene Capacitors 63V Wkg. E12 Series Axial Mounting. 10P to 820P-3p 1000P to 10.000-4p 12.000P-5p 1N4148-2p 1N4002-4p 1N5404-14p W01 bridge-25p OA91-6p AA143-8p W005-20p 1N4006-6p Zener diodes E24 series 3V3 to 33V 400mW-8p 1 watt 1-2p L.E.D.s Red, Green & Yellow 3mm & 5mm-10p 3mm-35p 20mA fuse 0.1A to 5A quick blow-5p Anti Surge-8p High Speed diodes 0.8mm, 1.0mm, 1.3mm, 1.5mm, 2mm-25p Expo Reliant drilling machines 12V d.c. with improved 3 jaw chuck 6.50 Nicads AA-80 HP11-S2 PP3-24.20 Universal Chargers-£6.50 Glass reed switches single pole make contacts-8p Magnets-12p

VAT inclusive. Return postage 20p (free over £5). Lists free.

THE C.R. SUPPLY CO., (DEPT ETI),

127 Chesterfield Road,
Sheffield S8 0RN. Tel. 557771.

CENTRAL REGION

Ex-stock Electronic Components, Test Equipment, Computers, Peripherals, Word Processors.

TECH SUPPLIES

19i Winchester Avenue,
Denny, Stirlingshire,
FK6 6QE.

Phone:
(0324) 825627

NO ORDER TOO SMALL

Open: 9am-4pm and
7.30pm-10pm 7 DAYS.

QUALITY COMPONENTS AND ACCESSORIES

Turntable belts Tape heads Plugs Leads Soldering irons Aerials Crossovers Video copy kits Multimeters Speakers ALTAI SOLDER PUMP £4.50 post free. 3 Volt 300mA REGULATED POWER SUPPLY only £4.80 + 50p p&p.

Send or phone for free lists
STRACHAN ELECTRONICS,
9 Croall Place, Edinburgh EH7 4LT
Tel. 031-556 9549

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0154

47 Whitechapel Tel: 051 236 5489

Liverpool 2

'THE ELECTRONICS SPECIALISTS'

Open: Tues-Sat 9.30-5.30

LONDON

CRICKLEWOOD

ELECTRONICS LTD

FOR COMPONENTS

LOTS OF NEW DEVISES

LOTS OF LOWER PRICES

Phone for our catalogue:

01 452 0161/450 0955 Telex: 914 977

40 Cricklewood Broadway,

London NW2 3ET.

TYNE AND WEAR

ELECTRONIC COMPONENTS AND KITS



STATION ROAD, CULLERCOATS,

NORTH SHEIELDS, TYNE & WEAR NE30 4PO

081 251 4363

MON-SAT 9.30 to 5.30
CLOSED THURS.


ELECTRO MART

Interak 1

AN EXPANDABLE DISK-BASED Z80A DEVELOPMENT SYSTEM YOU CAN BUILD YOURSELF!

Universities, Colleges, Industry, Enthusiasts:

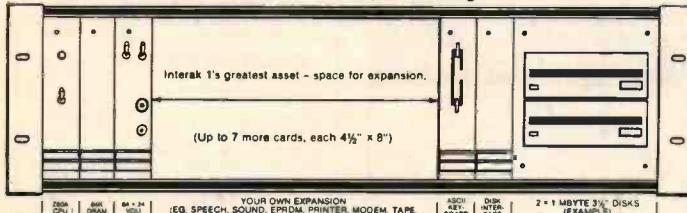Unlike home computers, development systems have entirely "open" architectures, use standard TTL etc. chips (ie no ULA's!), and are built in a proper engineering fashion. Usually these superior products carry a correspondingly superior price tag, but you can build Interak yourself board by board and thus afford a system which would normally be out of your reach and/or understanding.



The initial development system has 64K of RAM, a 4 MHz Z80ACPU, parallel ASCII keyboard interface, VDU Interface (TV set or monitor), and a floppy disk drive interface for up to 4 drives. Any size (including 8" double density) can be used, but our 1 Megabyte 3.5" drives are proving very popular because they can fit into the system rack, (and they only cost £94.00 each + VAT). CP/M Plus is available, giving access to thousands of "public domain" programs.

The system can be described as "future proof" because it uses plug in 4.5" x 8" cards in an industrial quality 19" 3U rack. We have been established since 1970, and this system was first made in 1977 so (unlike almost all other computers) it has stood the test of time.

Send two second class stamps, or telephone for a detailed descriptive leaflet, specification, prices, etc.

Greenbank

Greenbank Electronics (Dept T12E), 460 New Chester Road, Rock Ferry, Birkenhead; Merseyside L42 2AE. Tel: 051-645 3391

ADVERTISERS INDEX

ASP Binders	18
ASP Readers Services	19
Audiokits	66
Barrie Electronics	62
BK Electronics	IFC
Boreland Electronics	66
Cricklewood Electronics	62
Crimson Electrik	10
Display Electronics	IBC
Electromech Industries	61
Encore Enclosures	62
Greenbank Electronics	66
Hart Electronics	32
Henrys Audio Electronics	10
Maplin Electronics	OBC
Microkits	66
Omni Electronics	18
Rackz Mounting Products	32
Riscomp Ltd	52
Specialist Semicon Devices	36
Stewarts of Reading	52
TJA Development	10
TK Electronics	8
Wilmslow Audio	32
XEN Electronics	18
Zenith Electronics	52

Microkit LTD

0536 744664

24 hr 7 days/week

74TTL	LS HC	157	40 55	LM3900	40	TL072	50	MEMORIES DRAM 5V NMOS
00	20 25	158	40 55	OP07CP	65	TL082	45	4164 64K x 1 £0.88
02	20 25	161	55 55	NE555	18	TL084	45	4126 256K x 1 £2.39
04	20 25	163	55 55	TL074	90	ULN2004	70	4416 16K x 1 £3.30
06	20 25	164	55 55					41464 64K x 1 £3.30
10	20 25	165	65 75					
11	20 25	166	65 60					
14	20 28	WD2797	19.00					
20	20 29	WD1797	19.00					
21	20 29	WD9216	14.26					
27	27	7812	30					
42	49	78M12	30					
51	20 25	7515	90					
74	20 39	AD20808	9.90					
85	20 49	LM311	40					
96	20 49	LM324	40					
123	60 55	LM337	1.20					
132	49	LM348	55					
138	40 49	LM358	45					
139	40 49							
153	45 59							

SAVE OVER 40% ON OUR
EQUIPMENT MEMORIES
AND PROMS

1000's of delighted

customers

GUARANTEED UV

ERASSED AND TESTED

4116 16K x 8 £0.75

EPROMS

2114LP 1K x 4 £1.50

2128LP 2K x 8 £2.50

SRAM 5V NMOS

6116LP 2K x 8 £1.10

6264LP 8K x 8 £2.40

62256LP 32K x 8 £14.50

EPROM 5V NMOS

2716 2K x 8 £2.70

2732 4K x 8 £2.65

2764 8K x 8 £1.20

27128 16K x 8 £2.50

All taken from working boards. Try some. You will SAVE POUNDS £££££

2756 32K x 8 £3.75

27512 512K x 8 £14.50

ADD VAT 15% ORDERS UNDER £25 ADD £1 P&P OVER £25 POSTAGE FREE
ORDERS DISPATCHED SAME DAY BEFORE 3.30PM
DEPT (E7) 18 KOLDERMEADOW AV CORBY NN18 9AJ

BORELAND ELECTRONIC ENGINEERS LTD

26, North Road, Edmonton, London N9 7QY.
Tel: 01-805 5494

ELECTRONIC COMPONENT SPECIALISTS

RESISTORS

POTENTIOMETERS

CAPACITORS

SWITCHES

DIODES

BATTERIES

INTERRATED CIRCUITS

CONNECTORS

LEDS

SOCKETS

TRANSFORMERS

CASES

RELAYS

BOOKS

CRYSTALS

ETC.

SEND LARGE S.A.E. FOR PRICE LIST

AUDIOKITS Precision Components

Upgrade your cartridge with Audiokits Cartridge Matching Resistors.

Low cost resistors fitted to almost every amplifier distort the sound.

Get rid of the distortion with Bulk Foil Resistors from Audiokits.

AUDIOKITS RECOMMENDS BULK FOIL RESISTORS FOR LOADING ALL CARTRIDGES COSTING OVER £50

Don't believe us? Read HIFI news sonic tests on resistors June 1987 p33.

Or try a pair of Molco Precision Resistors at 35p each (20R-442K). Whatever improvement they make, Bulk foils will sound even better.

Buy now, or at Penta Show to avoid 1987/8 season price rise. 33R, 100R Bulk Foil for moving coils £4.50 each

47K Bulk Foil for moving magnets £5.50 each.

Send 50p & SAE for Audiokits Component Note ACN07 on Cartridge Loading Resistors & Capacitors.

Also Capacitors for cartridge matching. Highest sonic quality, British made. 200 pF, 470pF (for MMs) 4 & 7nF, 8nF (for MCs) £1 each.

Send SAE (9"X4") (Overseas 3 IRCs) for details of Audiokits Components and Kits.

AUDIOKITS
6, Mill Close, Borrowash, Derby DE7 3GU
Tel: 0332-674929

COMPUTER WAREHOUSE

THE "ALLADINS' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

1000's OF
BARGAINS
FOR CALLERS

HOT LINE DATA BASE

DISTEL®

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell 1000's of stock items, spares and one off bargains. Updated daily.

ON LINE NOW. CCITT, 8 bit word, no parity.

For 300 baud modems call 01-679 1888

For 1200-75 baud modems call 01-679 6183

FREE

Your monitor from its computer! For only £29.95 it becomes a SUPERB HIGH QUALITY * COLOUR * TV SET

The fabulous TELEBOX, an INVALUABLE MUST for the owner of ANY video monitor with a composite input, colour or monochrome. Made by a major UK Co. as a TOP QUALITY, stand alone UHF tuner and costing OVER £75 to manufacture, this opportunity to give your monitor a DUAL FUNCTION must not be missed!! The TELEBOX consists of a compact, stylish two tone charcoal moulded case containing ALL electronics tuner, power supply etc to simply plug in and convert your previously dedicated computer monitor into a HIGH QUALITY COLOUR TV SET, giving a real benefit to ALL the family! Don't worry if your monitor doesn't have sound - THE TELEBOX even has an integral 4 watt audio amplifier for driving an external speaker. PLUS an auxiliary output for superb quality television sound via your headphones or HI FI system etc. Other features include: Compact dimensions of only 15.75" w x 7.5" d x 3.5" h latest technology, BRITISH manufacture, fully tuneable 7 channel pushbutton tuner, Auto AGC circuit, SAW filter, LED status indicator, fully isolated 240V AC power supply for total safety, Mains ON-OFF switch etc. Many other uses.

LIMITED QUANTITY - DON'T MISS THIS OFFER!!!

ONLY £29.95 OR £24.94 if purchased with ANY of our VIDEO MONITORS. Supplied BRAND NEW with full instructions and 2 YEAR warranty. Post and packing £3.50. *When used with colour crt.

COLOUR & MONOCHROME MONITOR SPECIALS

SYSTEM ALPHA 14" COLOUR MULTI INPUT MONITOR

Made by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future requirements. Two video inputs: RGB and PAL Composite Video, allow direct connection to BBC/IBM and most other makes of micro computers or VCR's, including our very own TELEBOX. An internal speaker and audio amp may be connected to computer or VCR for superior sound quality. Many other features: PIL tube, Matching BBC case colour. Major controls on front panel. Separate Contrast and Brightness - even in RGB mode. Separate Colour and audio controls for Composite Video input. BNC plug for composite input, 15 way D' plug for RGB input, modular construction etc etc.

This Must Be ONE OF THE YEAR'S BEST BUYS. PC USER

Supplied BRAND NEW and BOXED complete with DATA and 90 day guarantee. ONLY £159.00 as above OR IBM PC Version £165.00 15 Day D' skt £1.00, BNC skt 75p BBC Interface cable £5.50

DECCA 80 16" COLOUR monitor, RGB Input.

Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the DECCA 80 series TV chassis give 80 column definition and quality found only on monitors costing 3 TIMES OUR PRICE. The quality for the price has to be seen to be believed!! Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, modular construction, auto degaussing circuit, attractive TEAK CASE, compact dimensions only 52cm W x 34 H x 24 D, 90 day guarantee. Although used units are supplied in EXCELLENT condition. ONLY £99.00 + Carriage.

DECCA 80, 16" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL user. ONLY £99.00 + Carr.

REDIFFUSION MARK 3, 20" COLOUR monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for SCHOOLS, SHOPDS, DISCO'S, CLUBS and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 + Carr.

BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors.

All units are fully tested and set for 240v standard working with composite video inputs. Units are pre tested and set up for up to 80 column use. Even when MINOR screen burns exist - normal data displays are unaffected. 30 day guarantee.

12" KGM 320-1 B/W bandwidth input will display up to 132 x 25 lines. £32.95

12" GREEN SCREEN version of KGM 320-1. Only £39.95

9" KGM 324 GREEN SCREEN fully cased very compact unit. Only £49.00

Carriage and insurance on all monitors £10.00

DC POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 5.5a, +12v @ 0.5a, -12v @ 0.1a and +23v @ 0.02a. Dim 18 x 11 x 6 cm, 110 or 240v input. BRAND NEW only £16.95

GOULD G6-40A 5v 40 amp switch mode supply. NEW £130.00

AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.6 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 100 or 240v AC input. Dim 28 x 12.5 x 7 cm NEW £49.94

Carriage on all PSU's £3.00

KEYBOARDS

Manufacturer's BRAND NEW surplus DEC LA34 Un-coded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc. £24.95

AMKEY MPNK-114 Superb word processor chassis keyboard on single PCB with 116 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT! Less than half price

Only £69.00 with data. Carriage on Keyboards £3.50

DISPLAY ELECTRONICS-



DON'T MISS THE CPM Deal

OF the CENTURY

The FABULOUS CPM TATUNG PC2000 Professional Business System

A cancelled export order and months of negotiation enables us to offer this professional PC, CPM system, recently on sale at OVER £1400, at a SCOOOP price just over the cost of the two internal disk drives!! Or less than the price of a dumb terminal!!

Not a toy, the BIG BROTHER of the EINSTEIN computer, the DUAL PROCESSOR PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc, the PC2000 specification, at our prices, CANNOT BE BEATEN!!

The central processor plinth contains the 64K, Z80A processor, DUAL TEAC 55F 5.1" Double sided 40/80 track disk drives (1Mb per drive), PSU, 4K of memory mapped screen RAM, disk controller, RS232, CENTRONICS and system expansion ports, and if that's not enough ready to plug into STANDARDS" DRIVE port up to FOUR 8" disk drives, either in double density or IBM format. The ultra slim 92 key, detachable keyboard features 32 user definable keys, numeric keypad and text editing keys, even its own integral microprocessor which allows the main Z80A to devote ALL its time to USER programs, eliminating "lost character" problems found on other machines. The attractive, detachable 12" monitor combines a green, anti-glare etched screen, with full swivel and tilt movement for maximum user comfort. Supplied BRAND NEW with CPM 2.2, user manuals and full 90 day guarantee. Full data sheet and info on request.

PC2000 System
with CPM Etc.
COST OVER £1400

NOW only £399

NOW only £499
Carriage & Insurance £12.00

PC2000 Wordprocessor System
with CPM and TEC FP25 daisywheel
printer

NOW only £799

MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets

BRAND NEW State of the art products.

DACOM DSL2123 Multi standard 300-300, 1200-75 Auto answer etc.

£268.00

DACOM DSL2123AQ Auto dial, smart modem with multi standard AUTO SPEED detect, and data buffer with flow control etc.

£365.00

DACOM DSL2123GT The CREAM of the intelligent modems, auto dial, auto call, index, buffer etc etc.

£498.00

Stiebeck SB1212 V22 1200 baud FULL DUPLEX sync or async, optional auto dial.

£465.00

TRANSIT 307 A Acoustic coupler 300 baud full duplex, originate only, RS232 interface

£49.00

Ex BRITISH TELECOM full spec, CCITT, ruggedised bargain offers. Sold TESTED with data. Will work on any MICR or system with RS232 interface.

£49.00

MODEM 13A 300 baud unit, only 2" high fits under phone. CALL mode only.

£45.00

MODEM 20-1 75-1200 baud. Compact unit for use as subscriber end to PRESTEL TELECOM GOLD, MICRONET etc.

£39.95 +pp £6.50

MODEM 20-2 1200-75 baud. Same as 20-1 but for computer end.

£65.00 +pp £6.50

DATEL 2412. Made by SE Labs for BT this two part unit is for synchronised data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc.

£199.00 +pp £8.00

DATEL 4800, RACAL MPS4800 baud modem. EX BT good working order. ONLY £295.00 +pp £8.00

SPECIAL OFFER

MODEM TG2393. Ex BT, up to 1200 baud, full duplex 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR +pp £10.00

For more information contact our Sales Office.

MATRIX PRINTERS

SPECIAL BULK PURCHASE of these compact, high speed matrix printers. Built in Japan for the Hazeltine Corporation this unit features quality construction giving 100cps bidirectional, full pin addressable graphics, 6 type fonts, up to 9.5" single sheet or tractor paper handling, RS232 and CENTRONICS parallel interface. Many other features. BRAND NEW and BOXED. COST £420. Our price Only £199.00

RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa.

A300 07191315 12v 3Ah NEW £13.95

A300 07191312 6v 3Ah NEW £9.95

A300 07191202 6-6v 1.8Ah TESTED Ex Equip £5.99

VDU TERMINALS

Standard VDU data entry terminals

at give away prices!!

QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" Green screen, 2 page RAM, TVI 925, Hazeline, ADMSSA emulations, software setup, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE Only £425.00


AJ510 EX RENTAL, Z80 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED with manual only £225.00

ADD5 520 - Dumb terminal, used. 12" b/w screen RS232 interface and printer port. TESTED. ONLY £125.00. Carriage on terminals £10.00

100's of other terminals in stock. CALL for more details.

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONAFIDE account orders from Government Dept's, Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

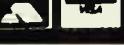32 Biggin Way, Upper Norwood, London SE19 3XF
Telephone 01-679 4414 Telex 894502 Data 01-679 1888



1988 BUYER'S GUIDE TO ELECTRONIC COMPONENTS

Maplin

GET YOUR
CATALOGUE NOW!
NEW MAPLIN STORE 1987

FROM 13th NOVEMBER 1987
Name _____
Address _____
Postcode _____
Town _____
County _____
Postcode _____
Price to receive you send £2.75 or 12 International Reply Coupons.
Send to Maplin Electronic Supplies Ltd P.O. Box 3 Rayleigh, Essex SS6 8LR.
P.S.I. Code _____
E.T.I. 1287

AVAILABLE SOON IN ALL W.H. SMITH'S STORES
Now to receive you send £2.75 or 12 International Reply Coupons.
Send to Maplin Electronic Supplies Ltd P.O. Box 3 Rayleigh, Essex SS6 8LR.
P.S.I. Code _____
E.T.I. 1287

VISIT OUR NEW
SHOP IN BRISTOL
NOW OPEN AT
302 GLOUCESTER ROAD
Tel: (0272) 232014



100% LOW COST CENTRE MODELS
LOW PRICES

£1.60