

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

MARCH 1988

£1.40

GAS ALERT

Protect Your Home

BBC MICRO
OSCILLOSCOPE

SATELLITE TV
Antenna Theory

DRUM FLASH



AUDIO... COMPUTING... MUSIC... RADIO... ROBOTICS...

OMP POWER AMPLIFIER MODULES

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B. and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.



OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms. Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 X 115 X 65mm. PRICE £33.99 + £3.00 P&P.



OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 X 123 X 60mm. PRICE PRICE £39.99 + £3.00 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 X 150 X 100mm. PRICE PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 X 147 X 102mm. PRICE PRICE £79.99 + £4.50 P&P.

NOTE: Mos Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV) If required P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 X 27 X 45mm. PRICE £8.50 - 50p P&P.

LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.



POWER RANGE

8" 50 WATT R.M.S. Hi-Fi/Disco.
20 oz magnet 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq 40Hz Freq Resp to 6KHz Sens. 92dB PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea
12" 100 WATT R.M.S. Hi-Fi/Disco
50 oz magnet 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone Res. Freq 25Hz Freq Resp to 4KHz Sens. 95dB PRICE £28.60 - £3.00 P&P ea

McKENZIE

12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco
12" ally voice coil Ally centre dome Res. Freq 45Hz Freq. Resp. to 6.5KHz Sens. 98dB PRICE £29.99 + £3.00 P&P ea
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
Res. Freq. 45Hz Freq. Resp. to 14KHz PRICE £31.49 + £3.00 P&P ea
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
3" ally voice coil Die-cast chassis Res. Freq. 40Hz Freq. Resp. to 4KHz PRICE £57.87 + £4.00 P&P ea
10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.
2" voice coil. Res. Freq. 75Hz Freq. Resp. to 7.5KHz Sens. 99dB. PRICE £19.99 + £2.00 P&P
10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.
2" voice coil. Res. Freq. 45Hz Freq. Resp. to 7KHz Sens. 101dB PRICE £44.76 + £3.00 P&P
15" 200 WATT R.M.S. C15200 High Power Bass.
Res. Freq. 40Hz Freq. Resp. to 5KHz Sens. 101dB. PRICE £62.41 + £4.00 P&P
15" 400 WATT R.M.S. C15400 High Power Bass.
Res. Freq. 40Hz Freq. Resp. to 4KHz Sens. 102dB PRICE £89.52 + £4.00 P&P.

WEM

5" 70 WATT R.M.S. Multiple Array Disco etc.
1" voice coil Res. Freq. 52Hz Freq. Resp. to 5KHz Sens. 89dB PRICE £22.00 + £1.50 P&P ea
8" 150 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq. 48Hz Freq. Resp. to 5KHz Sens. 92dB PRICE £32.00 + £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1" voice coil Res. Freq. 35Hz Freq. Resp. to 4KHz Sens. 92dB PRICE £36.00 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1 1/2" voice coil Res. Freq. 35Hz Freq. Resp. to 4KHz Sens. 94dB PRICE £47.00 + £3.00 P&P ea

SOUNDLAB (Full Range Twin Cone)

5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil Res. Freq. 63Hz Freq. Resp. to 20KHz Sens. 86dB PRICE £9.99 - £1.00 P&P ea
6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 56Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £10.99 + £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1 1/2" voice coil Res. Freq. 38Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £12.99 + £1.50 P&P ea
10" 60 WATT R.M.S. Hi-Fi/Disco etc.
1 1/2" voice coil. Res. Freq. 35Hz Freq. Resp. to 15KHz Sens. 89dB. PRICE £16.49 + £2.00 P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 X 46 X 14mm (9 volt) Price: £8.62 + 75p P&P.
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 X 84 X 12mm (12 volt) Price: £14.49 + 75p P&P.
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 X 70 X 22mm (9/12 volt). Price: £17.82 Transmitter 80 X 50 X 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.



BURGALAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

Indoor alarm - Electronic swept freq. siren. 104dB output.

Outdoor Alarm - Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00 Usual Price £228.85

BKE's PRICE £89.99 + £4.00 P&P

? Why buy a collection of self assembly boards!

IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS


The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12". Watts R.M.S. per cabinet. Sensitivity 1W 1mtr dB.

OMP 12-100 Watts 100dB. Price £149.99

per pair.

OMP 12-200 Watts 102dB. Price £199.99

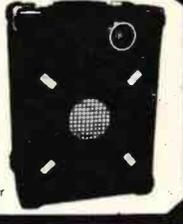per pair. Delivery Securicor £8.00 per pair



OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. Three models (Ratings R.M.S. into 4 ohms). Input Sensitivity 775mV.

MF200 (100 + 100)W. £169.00 Securicor

MF400 (200 + 200)W. £228.85 Delivery

MF600 (300 + 300)W. £322.00 £10.00

1 K-WATT SLIDE DIMMER

- * Control loads up to 1Kw
- * Compact Size 4 1/2" x 1" x 2 1/2"
- * Easy snap-in fixing through panel cabinet cut out
- * Insulated plastic case
- * Full wave control using 8 amp triac
- * Conforms to BS800

* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco, theatres etc.

PRICE £13.99 - 75p P&P

BSR P295 ELECTRONIC TURNTABLE

* Electronic speed control 45 & 33 1/3 r.p.m. * Plus Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1" cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14V D.C. 65mA

Price £36.99 £3.00 P&P




ADC Q4 mag. cartridge for above Price £4.99 ea. P&P 50p

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 Watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each - 40p P&P
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each - 40p P&P
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each - 40p P&P
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each - 40p P&P
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each - 40p P&P
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 X 85 mm Price £3.99 - 40p P&P

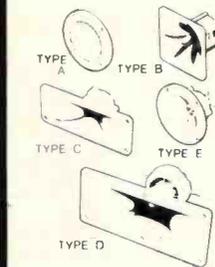

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features. 5 inputs with individual faders, providing a useful combination of the following:-
3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch, Headphone Monitor, Pan Pot, L & R Master Output controls. Output 775mV. Size 360 X 280 X 90mm. Price £134.99 - £3.00 P&P



B. K. ELECTRONICS

DEPT ETI

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA / ACCESS / C.O.D. ACCEPTED.



electronics today

INTERNATIONAL

1 Golden Square
London W1R 3AB
Tel: 01-437 0626
Telex: 01-881 1896

**ARGUS
PRESS
GROUP**

FEATURES

- RECEPTIVE THEORY** 7
Kelth Brindley takes a break from the brand names in this third part of our series on satellite TV to look at the maths behind dish sizing.
- DOMAIN POINTS AGAIN** 16
Paul Chappell narrowly misses some appalling puns with this continued investigation of complex numbers.
- MICRO CIRCUITS** 12
Two programs for PCB design and circuit diagrams running on the Amstrad CPC micros and the BBC micro come under the scrutiny of Malcolm Brown.
- THE LM3524** 18
Arthur Bossard finds there's more to the LM3524 switch mode power supply chip than meets the applications sheet. This IC is good for a number of bizarre uses.

PROJECTS

- GAS ALERT** 21
Greg Thompson has sniffed out a gem of a project. This modular gas detector and alarm is designed to meet the forthcoming British Standard for protection of your home, boat or caravan.
- BEEB-SCOPE** 26
Turn your BBC micro into a low frequency 4-channel oscilloscope with this easy-to-build project from Richard Penney.
- JUMPING JACK FLASH** 34
Paul Chappell has come up with the all-purpose project! Well not quite, but this light flasher device can be used for stage lighting, photography and many other uses.
- SPECTRUM CO-PROCESSOR** 39
Part two of Graeme Durant's twin micro for the Spectrum sees the design of the 256K RAM board with some ingenious design ideas.
- TECH TIPS** 46
Door Chimes
Motorcycle Regulator
Battery Regulator
Printer Switch
Soft Turn-on Dimmer

REGULARS

- NEWS** 5
SUBSCRIPTIONS 38, 50
PLAYBACK 48
OPEN CHANNEL 48
KEYNOTES 49
- PCB FOILS** 51
PCB SERVICE 53
OOPS! 53
CLASSIFIED ADS 55
AD INDEX 58



Cover photo courtesy Health and Safety Executive, Research and Laboratory Division, Explosion and Flame Laboratory, Buxton.

Editor: **Geoff Bains**
Assistant Editor: **Jez Ford**
Projects Editor: **Paul Chappell**
Illustrator: **Jerry Fowler**
Ad Manager: **Christopher Harris**
Classified Sales: **Julie Capstick**
Copy Control: **Andrew Selwood**

- Published by Argus Specialist Publications Ltd., 1 Golden Square, London W1R 3AB. Tel: 01-437 0626.
- UK newstrade distribution by SM Distribution Ltd., 16-18 Trinity Gardens, London SW9 8DX. Tel: 01-274 8611.
- Overseas and non-newstrade sales by Magazine Sales Department, 1 Golden Square, London W1R 3AB. Tel: 01-437 0626.
- Subscriptions by Infonet Ltd., 5 River Park Estate, Berkhamstead, Herts. HP4 1HL. Tel: (04427) 76661.
- Typesetting and origination by Multiform.
- Printed by Adlard & Son, The Garden City Press.
- Covers printed by Loxley Brothers Ltd.

ISSN
0142-7229




Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1988 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisements nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

● Subscription rates: UK £16.80
Europe: £21.00 Middle East: £21.20 Far East: £22.80 Rest: £21.50 or US\$32.00.

For KITS & COMPONENTS - Choose the easy way - with

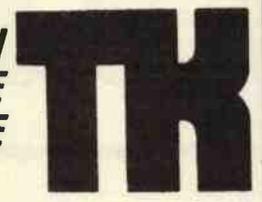Send **50p* & SAE** for **CATALOGUE** (AUTUMN 1987)
*refundable with first order



ORDERS: RING (01) 567 8910 - 24 HRS.

NEW ELECTRONIC GUARD DDG KIT



One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the hassle! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need is a mains supply, intruder detector and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.

XK125 Complete kit of parts £21.95

DISCO LIGHTING KITS

DL1000K - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel.....**£17.60**
DL21000K - A lower cost uni-directional version of the above. Zero switching to reduce interference.....**£9.85**
DLA/1 (for DL & DL21000K) Optional opto input allowing audio 'beat' light response.....**70p**
DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel.**£14.25**

The **DL8000K** is an 8-way sequencer kit with built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES! 80! different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300 V output per channel.

And the best thing about it is the price.

ONLY **£28.50**



TEN EXCITING PROJECTS FOR BEGINNERS

This Kit has been specially designed for the beginner and contains a **SOLDERLESS BREADBOARD, COMPONENTS**, and a **BOOKLET** with instructions to enable the absolute novice to build **TEN** fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.

ORDER NO **XK118** **£13.75**

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box. 18 time settings.

CT6000K.....**£42.90**
XK114 Relay kit for CT6000. Includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts...**£4.30**
701115 Additional relays.....**£1.80**



VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2 cms. The companion transmitter is the **MK18** which operates from a 9V PP3 battery and gives a range of up to 80ft. Two keyboards are available - **MK9** (4-way) and **MK10** (16-way), depending on the number of outputs to be used.

- MK12** IR Receiver (incl. transformer) **£14.85**
- MK18** Transmitter.....**£7.50**
- MK9** 4-Way Keyboard.....**£2.00**
- MK10** 16-Way Keyboard.....**£5.95**
- 601133** Box for Transmitter.....**£2.60**

HOME LIGHTING KITS

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting.

- TR300K** Remote Control Dimmer **£16.45**
- MK6** Transmitter for above **£4.95**
- TD300K** Touchdimmer **£8.50**
- TS300K** Touchswitch **£8.50**
- TDE/K** Extension kit for 2-way switching for TD300K **£2.70**
- LD 300K** Light Dimmer **£4.35**

NEW POWER STROBE KIT

Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high strobe tube and full assembly instructions. Supply: 240V ac. Size: 80 x 50 x 45.

XK124 STROBOSCOPE KIT £12.50

DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches required - details supplied) or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading automatic polarity and overload indication. Typical battery life of 2 years (PP3) **£17.00**

XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS **£6.00**

PROPORTIONAL TEMPERATURE CONTROLLER KIT


Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max. load 3kw (240V ac) Temp. range up to 90°C. Size: 7x4x2.5cms. **MK4 £7.10**



BARGAIN COMPONENT PACKS

Refill those empty component drawers at a fraction of the normal price and don't be caught without that odd resistor or capacitor to complete your project. All components supplied are to full spec. and are not seconds or surplus stock.

- Pack A:** 650 x .25 watt resistor 47R-10M **£4.25**
 - Pack B:** 60 x Radial electrolytics 1uf - 1000uf **£3.25**
 - Pack C:** 30 x Polyester capacitors a or 0.01 uf - 1uf **£4.50**
 - Pack D:** 35 x horizontal presets 1k-1M **£3.00**
 - Pack E:** 30 x IC sockets 8, 14, 16 pin **£2.00**
 - Pack F:** 25 x Red 5mm LEDs **£1.75**
 - Pack G:** 25 x Green 5mm LEDs **£2.00**
 - Pack H:** 30 x 5mm LEDs 10 Red, 10 Green, 10 Yellow **£2.50**
 - Pack J:** 50 x 1n 4148 silicon diodes **£1.00**
 - Pack K:** 40 x npn/pnp transistors BC/182/212 General Purpose **£2.25**
- FREE** Solderless Breadboard (verobloc type). When you buy all ten packs. Prices exclude VAT (15%).

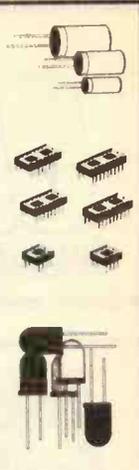

TOOLS ★ TOOLS ★ TOOLS



Good quality tools selected to offer outstanding value for money.

- 650 004** 6in mini. Snipe Nose Pliers. Serrated jaws and return spring. **£2.10**
- 650 005** 6in lap jointed side cutters. Insulated handles and return spring. **£2.10**
- 650 006** Light duty cutters. Cutting capacity 0.22-1.2mm copper wire. **£1.60**

TOOL KIT - Contains: side cutters, snipe nose pliers, wire strippers, flat blade screwdriver, Phillips screwdriver in black textured, reinforced and padded case which when opened out measures 240x205mm **£6.80**



- 650 007** Self-adjustable automatic wire stripper with built-in cable cutter. **£3.95**
 - 650 012** Watchmakers Screwdriver Set. 1.0/1.4/2.0/2.4/3.0/3.8mm **£1.75**
 - 650 019** Set of 4 Stainless Steel Tweezers. Straight nosed, straight hooked-reverse action, bent nosed, flat nosed, 110mm long. **£3.65**
 - 650 602** Reasant 9-12V dc Drill. **£6.90**
 - 650 600** Triam 12V dc Drill. **£10.25**
 - 650 670** Saturn Mains Drill. **£16.50**
- WE ALSO STOCK ANTEX IRONS AND ACCESSORIES**

SECURITY PRODUCTS

Install your own burglar alarm and save pounds. All parts available separately.

- 950 120** Stair Pressure Mat **1.70**
 - 950 125** Floor Mat 29x16 ins. **2.60**
 - 950 130** External bell box - an ideal deterrent on its own! **10.00**
 - 950 130** Xenon Beacon (12v) **10.50**
 - 950 140** Flush door/window contacts **1.22**
 - 950 143** Surface mounting contacts **1.05**
 - 950 160** Alarm Control Unit
 - 950 162** Alarm Control Unit
- This unit incorporates all the features required to form the basis of a complete security system for the home or business. Operating off a 240V AC supply with facility to charge a 12v lead acid standby battery. The unit is housed in a white steel box 225x225x80mm. Full instructions supplied to connect normally open and closed sensors, bells, personal alarms etc. Separate entry and exit alarm delays. 2 zone operation complies with BS 4737 price **£39.95**
- 950170** DOOR PHONE
- An attractively styled 2 station mains powered handset type door phone. Allowing conversation with visitors without opening the door. Free standing or wall mounted, connections to a 9 volt battery for standby. Electric doorlock release button which maybe used with our 701150 lock release mechanism. Ivory and Fawn body 210x100x70mm. **£27.95**

NOT JUST A MULTIMETER

A professional quality 3 1/2 digit multimeter with 34 ranges. As well as the usual current, voltage & resistance this meter features transistor and diode test, continuity AND CAPACITANCE and TEMPERATURE ranges. Basic accuracy is 0.25%. Size: 170x87x42mm. Includes test leads, thermocouple and full instruction & recalibration manual.



- AC Volts 200m-2-20-200-750
- DC Volts 200m-2-20-200-1KV
- AC Current 200u-2m-20m-200m-2A-10A
- DC Current: 200u-2m-20m-200m-2A-10A
- Resistance 200-2K-20K-200K-2M-20M
- Capacitance 2000p-2uF-20uF
- Temperature -10° to 1370°C
- Conductance 200nS
- hFE 0-1000 (NPN & PNP)
- Continuity Buzzer less than 200 ohms (405208) **£55.00**

LOGIC PROBE

A MUST for working with TTL & CMOS devices. Displays logic levels and pulses down to 25nS with LEDs and sound. Comprehensive instruction booklet supplied. Working voltage input impedance Max. i/p frequency


4-16v dc 1M 20MHz **ONLY £9.50**

RECHARGEABLE SOLDERING IRON

Powerful cordless iron complete with table-top/wall-mounting charging bracket. Reaches soldering temperature in 10 seconds. Includes lamp which lights when soldering. Comes with mains charging unit and 12V car battery adaptor. Special Offer **£15.95**

ELECTRONIC WEIGHING SCALES

This kit contains a Single Chip Microprocessor, PCB, displays and all electronics to produce a digital readout of weight in Kgs, or Sts, and Lbs. In normal use a toothed wheel (pattern provided) is made to rotate when a weight is placed onto the scales, interrupting two infra-red beams. The processor counts the number of teeth passing the sensor (up or down, depending on which beam is broken first) and shows the reading on the LED display in Sts. & Lbs., Lbs. or Kgms. A PCB link selects the scale for bathroom or two types of Kitchen Scales. A linear version of the toothed wheel could also be used. Other uses include up/down counters. A low cost digital ruler could be made by using a wheel with the correct tooth to diameter ratio. **ES1 £5.50**

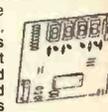

ELECTRONICS
13 BOSTON RD
LONDON W7 3SJ
Tel: 01-567 8910

SEND 9"x6" S.A.E. & 50p FOR CATALOGUE OR CALL AT SHOP MON-FRI 9-5pm SATURDAY 10-4pm

ORDERING INFORMATION: ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere **£6.50**. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.

LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY

● British Telecom is about to embark on the enormous task of digitally mapping the entire UK telephone network — cables, ducts and all.

At present BT basements are overflowing with 450,000 paper maps and diagrams.

After six years these will all be binned and the £19m digital map should be complete, enabling BT to get things wrong even more quickly than they do now!

In the first phase of the operation the principal towns will be mapped using BT's existing processor capacity, supplemented by four VAX computers from Intergraph. The Ordnance Survey will be collaborating with BT since it already has much of the necessary information in digital form.

The shareholders will be pleased.

● The semiconductor suppliers Top Ten of 1987 shows the Japanese companies continuing to gain ground, claiming 48% of the world market last year.

1987	1986	Company	% increase
1	1	NEC	21.0
2	3	Toshiba	29.1
3	2	Hitachi	20.5
4	4	Motorola	21.0
5	5	Texas Inst.	19.3
6	6	Fujitsu	39.1
7	8	Philips/ Signetics	26.9
8	11	Intel	51.4
9	10	Mitsubishi	30.4
10	9	Matsushita	22.6

Figures are taken from Dataquest's 1987 World Survey.

● A selection of seven slimline logic probes are now on the market from OK Industries.

The cheapest is the PRB-20 which has LEDs to indicate HI, Lo and Pulse, capable of 25ns pulse detection with a 20MHz bandwidth. Threshold levels are switchable between TTL and CMOS.

The top model is the PRB-100A with 5ns pulse detection — 100MHz bandwidth.


Prices before VAT range from £21.08 to £39.40.

Full details from OK Industries, Barton Farm Ind. Estate, Chlckenhall Lane, Eastleigh SO5 5RR. Tel: (0703) 619841.

● The Smart Talker Speech Synthesiser (ETI January 1988) can now be obtained as a fully assembled board (including power supply components) for £55 inclusive.

The PCB is still available at £8.00 and the complete parts kit (excluding case) for £40.00.

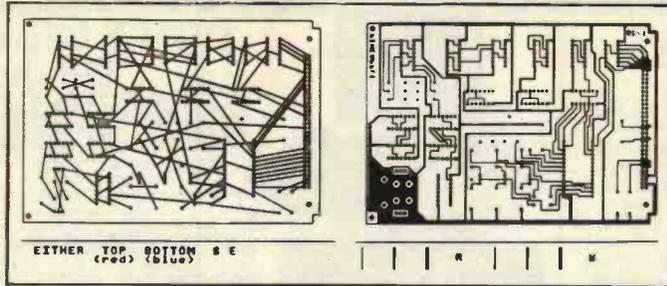Orders to: Russell Vowles, 3 Orchard Way, Uxbridge, Middlesex UB8 2BN. Please add 75p postage.



A Juicy Bit Of Software

Pineapple Software has produced an update for its popular PCB drafting program for BBC micro (reviewed in ETI March 1987).

The update gives the program full auto track routing with up to 190 connections specified by the user then linked by the program. If the result is not quite what you'd hoped for components can be shifted about without

redefining all your connection points, and to help the program in the right direction you can indicate a preferred track direction or even draw a few tracks yourself before the program does the rest.

The update is available to PCB owners for £55 from Pineapple Software, 39 Brownlea Gardens, Seven Kings, Ilford, Essex IG3 9NL. Tel: 01-599 1476.



DAT's The Way It Should Be

At last DAT players are 'officially' on sale in Britain about a year after they first appeared in Japan.

The Sony DTC1000ES is retailing at £1130+VAT and includes the controversial built-in copyguard that stops it recording at the 44.1kHz sampling rate of compact disc.

Since you can't record CD and commercial recordings aren't exactly widely available yet, the only use for this machine will be in the audio industry — and even then only among the less affluent.

Richer studios will be more in-

terested in the PCM2500 which can switch sampling rates (including 44.1kHz) and can match various formats (AES/ EBU, SDIF-2 and Sony/Philips). It cannot however convert signals from one format to another.

Ironically, considering Sony's own stand on copy prohibiting, the PCM2500 can add a copy prohibit code while recording.

HJB is supplying both machines to the UK and should soon have stocks of the even more expensive PCM2000.

For full details contact: HJB, 73-75 Scrubs Lane, London NW10 6QU. Tel: 01-960 1160.

YOUNG ELECTRONIC DESIGNER AWARDS

● The 1988 Young Electronic Designer Awards are up for grabs if you can come up with a commercially viable device with an everyday application.

Last year's winners included a saucepan for the blind, a digital pressure gauge, a speech synthesiser and an animal stress meter (?).

There are three age groups (up to 15, 16-18 and 19-25) and applicants must be in attendance at a

school, college or university in Great Britain.

Apart from the cash on offer, Texas Instruments are offering course sponsorship and a job to the winner of the 19-25 group. (Even more exciting is the possibility of getting on Tomorrow's World.)

Entry forms from: The YEDA Trust, 24 London Road, Horsham, West Sussex RH12 1AY. Tel: (0403) 211048.

● Stereo TV broadcasts have not been shelved indefinitely as recent press reports have been claiming.

Although the BBC Nicam broadcasts will not be off the ground for at least three or four years, the IBA will be introducing a service for London in 1989.

Other IBA transmitters will be updated to broadcast stereo as they become due for routine maintenance, which would put Yorkshire next on the list.

The majority of programmes going out in stereo will be pre-recorded films and music shows because of the lack of facilities for producing stereo in the TV studios.

The IBA are also considering multilingual broadcasting, using the two channels as completely separate soundtracks (dual channel sound).

Meanwhile BBC tests continue and some live programmes are already going out in London in Nicam stereo (Wogan for example) since none of the post-recording problems of stereo sound are encountered.

As for the general belief that the BBC originally scheduled Nicam for introduction in early 1988, the BBC says that this is complete rumour probably started by manufacturers such as Ferguson when they introduced stereo TVs and VCRs.

● Meanwhile you may have noticed some peculiar transmissions going out on BBC2 in the early morning closedown period.

These flickering distorted images of volcanos and skydivers are part of a BBC scrambling experiment with two applications in mind.

The first is the possibility of leasing unused air time to business and medical users to transmit high quality video pictures nationwide on a similar basis to BBC Enterprises' Data-cast service on Ceefax.

The second more disturbing application stems from the Peacock Report's recommendations for Pay-As-You-View television where a scrambling system would be put on BBC broadcasts. The licence-fee would be abolished and consumers pay only for the programmes they watch (it is still unclear if ITV programmes could be watched free under such a system).

Although the BBC opposes this concept as removing any incentive to produce minority programmes, the Government may pass legislation that would give them no choice.

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE "ALLADINS" CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HOT LINE DATA BASE

DISTEL

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell. 1000's of stock items, spares and one off bargains. Updated daily. ON LINE NOW. CCITT, 8 bit word, no parity. For 300 baud modems call 01-679 1888. For 1200-75 baud modems call 01-679 6183

FREE

Your monitor from its computer! For only £29.95 it becomes a SUPERB HIGH QUALITY * COLOUR * TV SET

The fabulous TELEBOX an INVALUABLE MUST for the owner of ANY video monitor with a composite input, colour or monochrome. Made by a major UK Co. as a TOP QUALITY, stand alone UHF tuner and costing OVER £75 to manufacture, this opportunity to give your monitor a DUAL FUNCTION must not be missed! The TELEBOX consists of a compact stylish two tone charcoal moulded case, containing ALL electronic tuner, power supply etc to simply plug in and convert your previously dedicated computer monitor into a HIGH QUALITY COLOUR TV SET, giving a real benefit to ALL the family! Don't worry if your monitor doesn't have sound - THE TELEBOX even has an integral 4 watt audio amplifier for driving an external speaker, PLUS an auxiliary output for superb quality television sound via your headphones or HI FI system etc. Other features include Compact dimensions of only 15.75" w x 7.5" d x 3.5" h latest technology, BRITISH manufacture, fully tuneable 7 channel push button tuner, Auto AGC circuit, SAW filter, LED status indicator, fully isolated 240v AC power supply for total safety, Mains ON-OFF switch etc. Many other uses.

LIMITED QUANTITY - DON'T MISS THIS OFFER!!!

ONLY £29.95 OR £24.94 If purchased with ANY of our VIDEO MONITORS. Supplied BRAND NEW with full instructions and 2 YEAR warranty. Post and packing £3.80 *When used with colour crt.

COLOUR & MONOCHROME MONITOR SPECIALS

'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR

Made by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future requirements. Two video inputs, RGB and PAL. Composite Video, allow direct connection to BBC/IBM and most other makes of micro computers or VCR's. Including our very own TELEBOX. An internal speaker and audio amp may be connected to computer or VCR for superior sound quality. Many other features: PIL tube, Matching BBC case colour, Major controls on front panel. Separate Contrast and Brightness - even in RGB mode. Separate Colour and audio controls for Composite Video Input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc etc.

This Must Be ONE OF THE YEAR'S BEST BUYS. PC USER Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. ONLY £159.00, as above OR IBM PC Version £165.00 15 Day 'D' sct £1.00, BNC sct 75p BNC interface cable £5.90

DECCA 80 16" COLOUR MONITOR, RGB Input.

Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor, as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the DECCA 80 series TV chassis give 80 column definition and quality found only on monitors costing 3 TIMES OUR PRICE. The quality for the price has to be seen to be believed! Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, modular construction, auto degaussing circuit, attractive TEAK CASE, compact dimensions only 52cm W x 34 H x 24 D, 90 day guarantee. Although used, units are supplied in EXCELLENT condition. ONLY £99.00 + Carriage.

DECCA 80, 16" COLOUR monitor, Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.

REDIFFUSION MARK 3, 20" COLOUR monitor. Fitted with standard 75 cm composite video input and sound amp. This large screen colour display is ideal for SCHOOLS, SHOPS, DISCOS, CLUBS and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 + Carr.

BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors. All units are fully cased and set for 240v standard working with composite video inputs. Units are pre tested and set up for up to 80 column use. Even when MINOR screen burns exist - normal data displays are unaffected 30 day guarantee.

12" KGM 320-1 B/W bandwidth input, will display up to 132 x 25 lines. £32.95
12" GREEN SCREEN version of KGM 320-1. Only £39.95
9" KGM 324 GREEN SCREEN fully cased very compact unit. Only £49.00

Carriage and insurance on all monitors £10.00

DC POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 5.5a, -12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £16.95
GOULD G6-40A 5v 40 amp switch mode supply NEW £130.00
AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.6 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 100 or 240v AC input. Dim 28 x 12.5 x 7 cm NEW £49.94
Carriage on all PSUs £3.00

KEYBOARDS

Manufacturer's BRAND NEW surplus

DEC LA34 Uncoded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc £24.95
AMKEY MPNK-114 Superb word processor chassis keyboard on single PCB with 116 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, numeric keypad, cursor pad and 9600 baud SERIAL, TTL, ASCII OUTPUT! Less than half price. ONLY £69.00 with data. Carriage on Keyboards £3.50



DON'T MISS THE CPM Deal OF THE CENTURY

The FABULOUS CPM TATUNG PC2000 Professional Business System

A cancelled export order and months of negotiation enables us to offer this professional PC, CPM system, recently on sale at OVER £1400, at a SCOOPE price just over the cost of the two internal disk drives! Or less than the price of a dumb terminal!!

Not a toy, the BIG BROTHER of the EINSTEIN computer, the DUAL PROCESSOR PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc, the PC2000 specification, at our prices, CANNOT BE BEATEN!!

The central processor plinth contains the 84K, Z80A processor, DUAL TEAC 55F 5 1/4" 1Mb per drive, PSU, 4K of memory backed screen RAM, disk controller, RS232, CENTRONICS and system expansion ports and if that's not enough a ready to plug into STANDARD 'B' DRIVE port for up to FOUR 8" disk drives, either in double density or IBM format. The ultra slim 92 key, detachable keyboard features 32 user definable keys, numeric keypad and text editing keys, even its own integral microprocessor which allows the main Z80A to devote ALL its time to USER programs, eliminating "lost character" problems found on other machines. The attractive, detachable 12" monitor combines a green, anti glare etched screen, with full swivel and tilt movement for maximum user comfort. Supplied BRAND NEW with CPM 2.2, user manuals and full 90 day guarantee. Full data sheet and info on request

PC2000 System with CPM etc. COST OVER £1400

PC2000 Business System with CPM and 'Ready to Run' FAST Sales and Purchase ledger, supports up to 9000 Accounts, VAT etc. COST OVER £1700

PC2000 Wordprocessor System with CPM and TEC FP25 daisywheel printer

NOW only £399

NOW only £499
Carriage & Insurance £12.00

NOW only £799

MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets..... BRAND NEW State of the art products

DACOM DSL2123 Muffl standard 300-300, 1200-75 Auto answer etc £268.00
DACOM DSL2123AQ Auto dial smart modem with multi standard AUTO SPEED detect and data buffer with flow control etc £368.00
DACOM DSL2123GT THE CREAM of the intelligent modems auto dial, auto call, index, buffer etc etc £496.00
Stebeck SB1212 V22 1200 baud FULL DUPLEX, sync or async, optional auto dial £468.00
TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 interface £49.00

Ex BRITISH TELECOM full spec, CCITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICOM or system with RS232 interface.
MODEM 13A 300 baud unit, only 2" high fits under phone CALL mode only £45.00
MODEM 20-1, 75-1200 baud, Compact unit for use as subscriber end to PRESTEL, TELECOM GOLD, MICRONET etc £39.95 +pp £6.50
MODEM 20-2 1200-75 baud Same as 20-1 but for computer end £65.00 +pp £6.50
DATEL 2412. Made by SE Labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc. COST OVER £800. Our price ONLY £199 +pp £8.00
DATEL 4800, RACAL MPS4800 baud modem, EX BT good working order, ONLY £295.00 +pp £8.00

SPECIAL OFFER
MODEM TG2393, EX BT, up to 1200 baud full duplex 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR +pp £10.00

For more information contact our Sales Office.

MATRIX PRINTERS

SPECIAL BULK PURCHASE of these compact, high speed matrix printers. Built in Japan for the Hazeltine Corporation this unit features quality construction giving 100cps, bidirectional, full pin, addressable graphics, 6 type fonts, up to 9.5" single sheet or tractor paper, handling, RS232 and CENTRONICS parallel interface. Many other features. BRAND NEW and BOXED. COST £420. Our price Only £199.00

RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa.
A300 07191315 12v 3Ah NEW £13.95
A300 07191312 6v 3Ah NEW £9.95
A300 07191202 6-0-6v 1.8Ah TESTED Ex Equip £5.99

VDU TERMINALS

Standard VDU data entry terminals at give away prices!!
QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" Green screen, 2 page RAM, TVI 925, Hazeltine, ADMSA emulators, software setup, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE ONLY £425.00
AJ510 - EX Rental, Z80 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00
ADDS 520 - Dumb terminal, used, 12" b/w screen RS232 interface and printer port. TESTED. ONLY £125.00. Carriage on terminals £10.00
100's of other terminals in stock, CALL for more details

SURPLUS SPECIALS ON PRESTEL - VIEWDATA - TELEX

PLESBEY VUTEL, ultra compact unit, slightly larger than a telephone features A STANDARD DTMF TELEPHONE (tone dial) with 5" CRT monitor and integral modem etc. for direct connection to PRESTEL VIEWDATA etc. Designed to sell to the EXECUTIVE at over £600!! Our price BRAND NEW AND BOXED at only £99.00

DECCAFAX VP1 complete Professional PRESTEL system in slimline desk top unit containing Modem, Numeric keypad, CPU, PSU etc. Connects direct to standard RGB colour monitor. Many other features include: Printer output, Full keyboard input, Cassette port etc. BRAND NEW with DATA. A FRACTION OF COST only £55.00

ALPHATANTEL. Very compact unit with integral FULL ALPHA NUMERIC keyboard. Just add a domestic TV receiver and you have a superb PRESTEL system and via PRESTEL the cheapest TELEX service to be found!! Many features: CENTRONICS Printer output, Memory dialling etc. Supplied complete with data and I/O mod for RGB or Composite video outputs AS NEW only £125.00

Post and packing on all PRESTEL units £8.50

EX-STOCK INTEGRATED CIRCUITS

4164 2000 ns D RAMS 9 for £11 4116 ns £1.50 2112 £10.00 2114 £2.50 2102 £2.00 6116 £2.50 EPROMS 2716 £4.50 2732 £3.00 2764 £4.95 27128 £5.50 6800 £2.50 8821 £1.68A09 £8 68B09 £10 8085A £5.50 8088 £15 80A08 £8 NEC765 £8 WD2793 £28 8202A £22 8251 £7 8748 £15 Z80A DART £6.50 Z80A CPU £2.00. Thousands of IC's EX STOCK send SAE for list.

DISK DRIVES

Japanese 5 1/4" half height 80 track double sided disk drives by TEAC, CANON, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £85.00
TEC FB-503 Double sided HH 40 TRK NEW £75.00
SUGART SA400 SS FH 35 TRK £55.00
SIEMENS FDD100 SS FH 40 TRK £85.00
Carriage on 5 1/4" drives £5.50
Brand NEW metal 5 1/4" DISK CASES with internal PSU.
DSKC 2 for 1 HH drive £29.95 +pp £4.00
DRSC 2 for 1 HH drive £22.95 +pp £3.50
DKSC 3 As DSK1 LESS PSU £1.95 +pp £2.50
DKSK 4 As DSK2 LESS PSU £10.95 +pp £2.00
8" IBM format TESTED EX EQUIPMENT.
SHUGART 800/801 SS £175.00 +pp £8.50
SHUGART 851 DS £250.00 +pp £8.50
TWIN SHUGART 851's 2 Mb total capacity in smart case, complete with PSU etc. £595.00
MITSUBISHI M2894-63 8" DS 1 Mb equiv. to SHUGART S850R, BRAND NEW at £275.00
DYVAN 8" Alignment disk £29.00 +pp £1.00
Various disk drive PSUs's Ex Stock SEE PSU section.

HARD DISK DRIVES
DRE/DIABLO Series 30 2.5 Mb total range £525.00
Exchangeable version £295.00, ME3029 PSU £95.00
DIABLO 44/DRE4000A, 8 5+5 Mb from £750.00
CDC HAWK 5+5 Mb £795.00, CDC 9762 80 Mb RM03 etc. £2500.00
PERTEC D3422 5+5 Mb £495.00
RODIME 5 1/4" Winchester ex-stock from £150 CALL
Clearance items - Sold as seen - No guarantee
ICL 231 4 BRAND NEW 14" Mb Removable pack hard disk drive, cost over £2000 with data ONLY £99.00
BASF 6172 8" 23Mb Winchester £199.00
Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

Display Electronics

32 Biggin Way, Upper Norwood, London SE19 3XF
Telephone 01-679 4414 Telex 894502 Data 01-679 1888

RECEPTIVE THEORY

In this third part of his series on satellite television, Keith Brindley considers the mathematical and theoretical side of signal reception and looks at ways of calculating antenna size

Satellite TV systems (or TVRO for the pedantic) are of course examples of communications systems and as such can be looked at mathematically in terms of signal strengths to enable us to define certain minimum standards which are governed by the user's operating requirements.

However these minimum standards are related to television picture quality and as picture quality is largely subjective, some way of relating subjective picture quality to objective signal strengths needs to be devised.

What's more the relation must be made in such a way as to make easy comparisons between similar systems.

The process of calculating a satellite system's quality in this way is known as a *link budget analysis* — so called because it's an analogy with a financial budget, comparing gains and losses in the link between satellite and receiver to give a final result in terms of picture quality.

No Accounting For Taste

The main problem in any communications system (but particularly in TVRO systems) is the level of noise which the receiver output contains. A communications system's noise level is typically quoted in relation to received signal level as a *signal-to-noise ratio* (S/N), where the S/N ratio is given in decibels (dB) by:

$$S/N = 10 \log \left(\frac{\text{signal power}}{\text{noise power}} \right)$$

Most readers will know this and no further time needs to be spent here. However, the S/N ratio depends on a number of other factors within the overall system, particularly regarding satellite television reception. So we need to consider further these related factors.

To do this we must consider some basic transmission calculations. A transmitting satellite rotating in the geo-stationary orbit (GSO) is sufficiently far away from the Earth to be considered an *isotropic* radiating source since it appears from an Earth viewpoint to radiate in all directions (Fig. 1a).

In reality of course this is not the case as all satellites use directional transponders (Fig. 1b) — they are only *effectively* isotropic (remember this term) as far as the earth-bound observer is concerned.

We can calculate an antenna's received signal from an isotropic source if we first calculate the flux density of the source at say a distance D_s because all the radiated signal must pass through an imaginary sphere

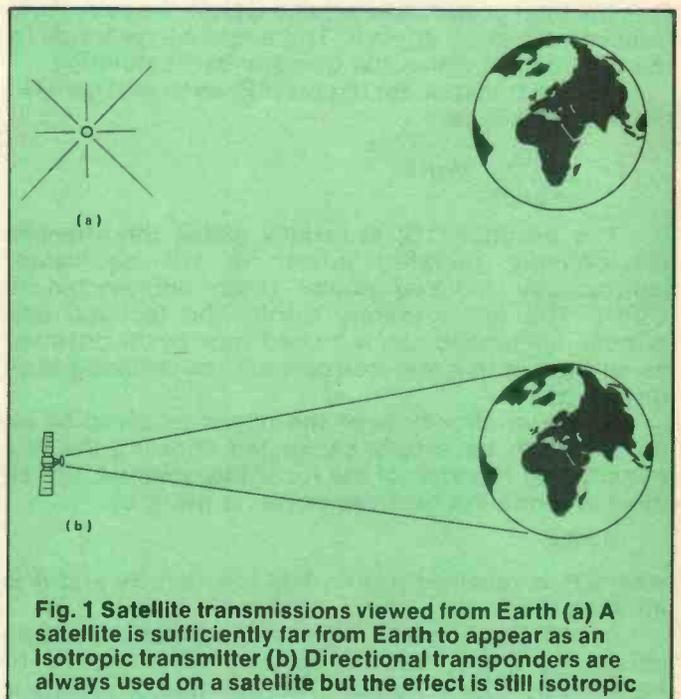


Fig. 1 Satellite transmissions viewed from Earth (a) A satellite is sufficiently far from Earth to appear as an isotropic transmitter (b) Directional transponders are always used on a satellite but the effect is still isotropic

of radius D_s , around the source. The resultant flux density is given by:

$$F = \frac{P_t}{4 \pi D_s^2} \text{ Wm}^{-2}$$

where P_t is the transponder power.

If a receiving antenna is presumed to be positioned on the circumference of the imaginary sphere then two main points are illustrated by this relationship:

- flux density decreases with distances from the source (fairly obvious) as an inverse square
- flux density (in watts) received at the antenna can be simply calculated if the area of the antenna (in m^2) is known.

With a satellite's directional transponder a gain $G(\theta)$ occurs in a direction θ , where gain is defined as the ratio of power per unit solid angle radiated in a given direction to the average power radiated per unit solid angle. That is:

$$G(\theta) = \frac{P(\theta)}{P_o/4\pi}$$

where $P(\theta)$ is the power radiated per unit solid angle,

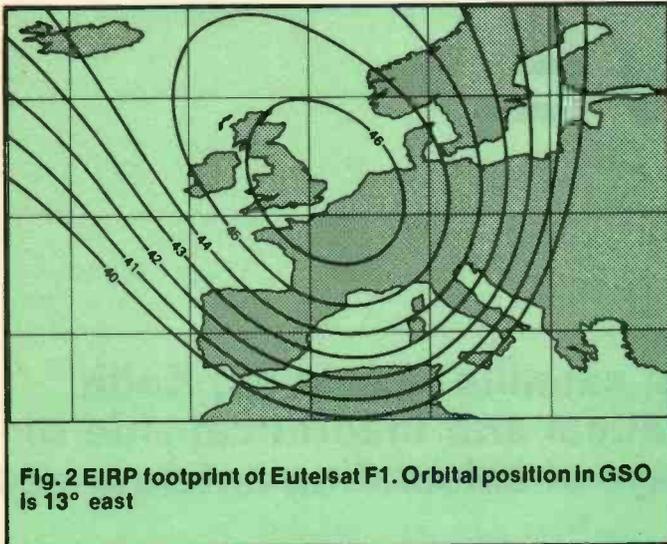


Fig. 2 EIRP footprint of Eutelsat F1. Orbital position in GSO is 13° east

P_0 is the total power radiated and $G(\theta)$ is the gain of the transponder at an angle θ . The angle corresponds to the direction in which the transponder is pointing.

So for a transponder of power P_t watts and gain G_t , the flux density is:

$$F = \frac{P_t G_t}{4 \pi D^2} \text{ Wm}^{-2}$$

The product $P_t G_t$ is usually called the *effective isotropically radiated power* or the *equivalent isotropically radiated power* (both abbreviated to EIRP). The terms merely signify the fact the uni-directional transponder is looked upon by the observer as equivalent to a *real* isotropic source radiating in all directions.

As we've already seen the power received by an antenna can be simply calculated knowing the flux density and the area of the receiving antenna. For an ideal antenna the received power is given by:

$$P_r = FA$$

where P_r is received power, F is flux density and A is antenna area.

In practice however, no antenna is perfect and an efficiency, known as the *aperture efficiency* η , of between 60-75% is normal. This aperture efficiency is said to reduce the area of the antenna's receiving aperture to give an *effective antenna area* A_e where:

$$A_e = \eta A$$

For a practical antenna the received power is therefore:

$$P_r = FA_e$$

So in terms of EIRP received power of a practical antenna is given by:

$$P_r = \frac{P_t G_t A_e}{4 \pi D^2}$$

In other words, received power depends only on the satellite's EIRP, the antenna's effective area, and the distance between the satellite and the antenna.

We can consider this relationship another way, where the term:

$$L_s = \frac{1}{4 \pi D^2}$$

is known as the *spreading loss*, or the *path loss* (in fact it is not a loss in the strict sense at all — it merely accounts for the way energy spreads out as the trans-

mitted wave travels away from the source). The received power can now be calculated as:

$$P_r = \frac{\text{EIRP} \times \text{effective antenna area}}{\text{spreading loss}}$$

and, because all these terms usually are quoted in decibels (that is, logarithmically) then:

$$P_r = \text{EIRP} + A_e - L_s \text{ dB}$$

Again, this represents the ideal situation and in practice other losses such as attenuation due to weather (particularly rainfall) have to be taken into account.

Practical Example

To put things into perspective at this point, we can consider a real antenna site (such as in my back garden) and perform a few calculations to show the idea.

Figure 2 shows the footprint in terms of EIRP of the Eutelsat F1 satellite, positioned at 13° east in the GSO. Each ring of the footprint represents an EIRP 'contour' within which area the EIRP is numerically indicated in units of dBW. Over most of Britain the EIRP is 46dBW.

The units dBW simply means that the power level is referred to 1W. In other words 1W is signified by 0dBW. A positive dBW level means the power is greater than 1W, a negative dBW level means the power is less than 1W. Another common reference power is in units of dBm where the level quoted with those units is referred to 1mW — so that 1mW is signified by 0dBm. Both units are common in communications engineering.

Now in my back garden (in the wilds of the East Midlands) the distance from Eutelsat F1 and the antenna happens to be about 38747km. So the spreading loss in my back garden is:

$$\begin{aligned} L_s &= \frac{1}{4 \pi D^2} = \frac{1}{4 \pi (38747 \times 10^3)^2} \\ &= \frac{1}{1.8866 \times 10^{16}} \\ &= 5.3 \times 10^{-17} \end{aligned}$$

Expressed in decibels, this is: $10 \log (5.3 \times 10^{-17})$ or -162.76dB .

Using a 1.5 metre diameter antenna, the actual area is πr^2 or 1.767m^2 . With an aperture efficiency of, say, 60% (about right for most antennae), the effective antenna area is 1.06m^2 , expressed logarithmically this is 0.25dBm^2 .

It's difficult to define exactly the loss which may occur due to weather conditions but generally 2dB is about right.

Calculating the received power is now just a simple matter:

$$P_r = 46 + 0.25 - 162.76 - 2 = -118.51\text{dBW}$$

which means that only 1.4 picowatts of signal power (work it out for yourselves) is received by the antenna — not a lot!

The received power we've worked out here is normally referred to as the *carrier power* and given the symbol C . In frequency modulation (such as existing satellite television services) and phase modulation systems the two are equal because the carrier level is constant, whether or not a signal is modulated onto the carrier.

Most signal-to-noise calculations for satellite systems use estimates of carrier power rather than signal power and subsequent signal-to-noise ratios normally are quoted as a *carrier-to-noise ratio* (C/N).

Noise

Having calculated the received carrier power, we now have to consider the noise present so that we can compare the two.

Noise in satellite television reception systems follows a classical receiver convention (shown in Fig. 3a) where the receiving antenna is connected to a demodulator through a high-gain amplifier. In a satellite reception system the high-gain amplifier is only one part of the low noise blockdownconverter (LNB). All important parts of the LNB are shown in Fig. 3b.

The noise we want to measure is that noise present at the demodulator input and this is made up of noise which is contributed by various parts of the system including the antenna itself, the waveguide and the high-gain low-noise amplifier (LNA). Although parts following the LNA also contribute noise, their effects are negligible in comparison and so can be ignored.

At the microwave frequencies involved in satellite communications systems, all objects with a temperature above 0K generate noise and so contribute to the total system noise. This *thermal noise* is usually calculated in terms of *noise temperature* by relating temperature to the thermal energy produced by the random movement of electrons, with Boltzmann's constant. Noise is generated by an object at each frequency, so the bandwidth of the receiver also bears directly on the amount of noise present at the demodulator input.

The noise power present at the demodulator input is given by:

$$P_n = kT_s B$$

where k is Boltzmann's constant (1.38×10^{-23}), T_s is the total system noise temperature in degrees Kelvin and B is the receiver bandwidth in Hz.

Total system noise temperature is a combination of the noise temperatures of antenna and LNB. LNB noise temperature may be given by the manufacturer or can be calculated from the LNB's noise figure (NF) which is usually quoted in decibels. LNB noise temperature is:

$$T \left(\text{antilog} \left(\frac{NF}{10} \right) - 1 \right)$$

where T is the temperature in degrees Kelvin (usually taken as $17^\circ\text{C} = 290\text{K}$).

Antenna noise temperature is a bit more difficult to estimate as it varies with antenna, elevation angle and received frequency but manufacturers should supply figures and results are typically in the range 40K to 90K.

In practical terms (my back garden again!) for an antenna with a noise temperature of 60K, an LNB noise figure of 2.5dB and a receiver bandwidth of 30MHz, we can now calculate the noise power present at the demodulator input. The LNB noise temperature is:

$$290 \left(\text{antilog} \left(\frac{2.5}{10} \right) - 1 \right) = 225.7\text{K}$$

so the total system noise temperature is $225.7\text{K} + 60\text{K} = 285.7\text{K}$.

The noise power at the demodulator input can now be calculated as:

$$P_n = 1.38 \times 10^{-23} \times 285.7 \times 30 \times 10^6$$

or, logarithmically in decibels:

$$= -228.6 + 24.6 + 74.8$$

$$= -129.2\text{dBW}$$

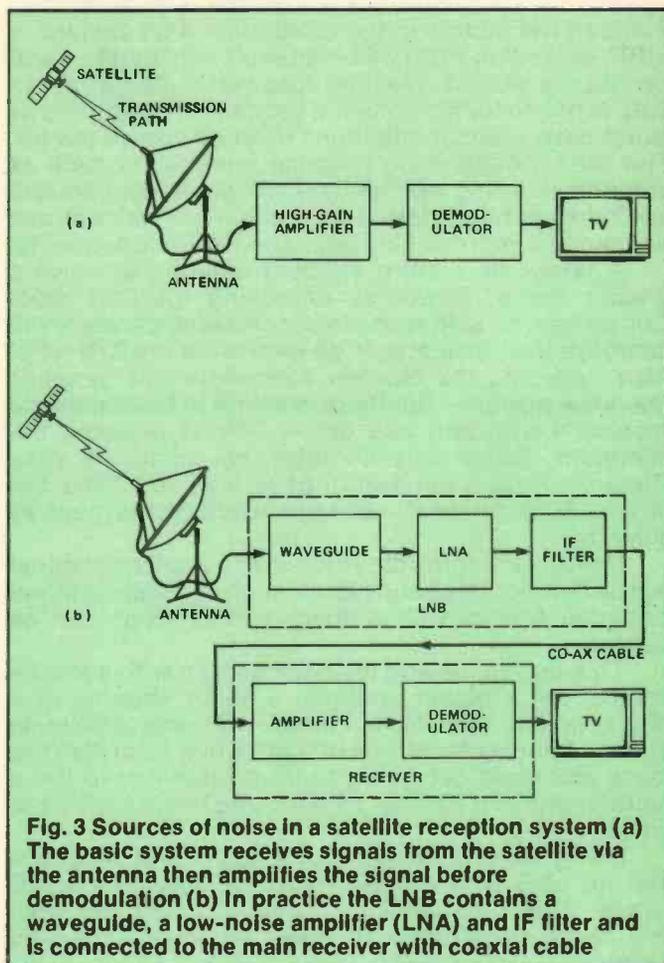


Fig. 3 Sources of noise in a satellite reception system (a) The basic system receives signals from the satellite via the antenna then amplifies the signal before demodulation (b) In practice the LNB contains a waveguide, a low-noise amplifier (LNA) and IF filter and is connected to the main receiver with coaxial cable

Knowing this and using our previous calculation for carrier power the available C/N ratio can be calculated as:

$$\begin{aligned} C/N &= (-118.51) - (-129.2) \\ &= 10.69\text{dB} \end{aligned}$$

Putting Us In The Picture

A simple C/N ratio like this doesn't mean a lot to the uninitiated so we need to look further into what it represents. Measurement of quality of a television picture is a highly subjective area (an adequate picture for one person is no good for another) but the International Radio Consultative Committee (CCIR) has defined a picture quality assessment plan which uses a five-point grading system. This, related to a system's CN ratio, is listed in Table 1 and shown in graphical form in Fig. 4.

From these we can see that a practical C/N ratio of 10.7dB (the system in my back garden) gives a picture which is classed as only just fair. Even more worrying than this, however, is the fact that such a low C/N ratio is probably close to the receiver's FM threshold margin (typically around 8-9dB) and so impulse noise interference showing up as black and white flashes or dots on the screen — the infamous 'sparklies' — could occur.

If this was a real system which I was about to buy, I'd want to know how I could improve the picture quality a bit. Let's go back to the calculations for C/N ratio to find out how. The overall ratio is given (in decibels by:

$$\frac{C}{N} = \frac{P_r}{P_n} = \frac{\text{EIRP} + A_e - L_s - \text{weather loss}}{k + T_s + B}$$

FEATURE: Satellite TV

Some of the factors in the calculation are constant — EIRP, spreading loss L, Boltzmann's constant k — and cannot be altered. Weather loss (estimated at about 2dB, is of course not constant but cannot be ignored as worst-case weather situations must be accounted for. The others depend on physical parameters such as antenna size and efficiency, LNB noise temperature and receiver bandwidth, so a number of measures can be taken to improve C/N ratio and the picture quality.

A larger or a more efficient antenna will give a greater carrier power so improving the C/N ratio. Conversely, an LNB with a lower noise temperature will decrease the noise power, so improving the C/N ratio. Also, reducing the receiver bandwidth will decrease the noise power — but there is a limit to how small the receiver bandwidth can be! — 30MHz is about the minimum. Some satellite television channels (Sky Channel) have a bandwidth of as little as 27MHz but others (Superchannel) have a bandwidth of as much as 36MHz.

If receiver bandwidth is too low, not all the channel will be demodulated and results such as a tearing effect on video scenes with a sharp vertical edge can be caused.

This leaves me and my back garden with a simple choice: get a bigger antenna, a better antenna or a higher quality LNB. Now, the wife's already up in arms about having a monstrous brilliant white 1.5m dish out there and she's not going to let it grow just to get a better picture so a better antenna and better LNB is the answer.

Using an antenna with an efficiency of, say, 65% and an LNB with a noise figure of, say, only 1.5dB (some of the most recently produced LNB's can meet this requirement) we can now re-calculate the C/N ratio.

Effective antenna area is now 65% of 1.767m² (1.15m²) or in decibels: 0.6dB. LNB noise temperature is now:

$$290 \left(\text{antilog} \left(\frac{1.5}{10} \right) - 1 \right) = 119.6\text{K}$$

and total noise temperature is 119.6K+60K=179.6K or in decibels: 22.5dB. Final C/N ratio now becomes:

$$\begin{aligned} \text{C/N} &= 4 + 0.6 - 162.76 - 2 - (-228.6 + 22.5 + 74.8) \\ &= 13.14\text{dB} \end{aligned}$$

This result corresponds to a picture quality which is close to being good on the CCIR five point scale and I'll certainly accept it. Generally, a C/N ratio of about 13dB figure should be aimed for when doing a link budget analysis. This should allow for extremes of weather conditions, minor antenna pointing inaccuracies and the like.

Figure Of Merit

Overall receiver performance is sometimes quoted as a *figure of merit* which is its gain over temperature (G/T). All receiver parameters such as antenna gain, total system noise temperature and so on are catered for in this G/T figure and so the figure of merit is related to the C/N ratio and one can be calculated from the other (approximately) according to the relationship:

$$\text{C/N} = \text{EIRP} + \text{G/T} - 53\text{dB}$$

or inversely:

$$\text{G/T} = \text{C/N} - \text{EIRP} + 53\text{dB}$$


So, the practical example of the system in my back garden (with improved antenna and LNB) has a figure of merit of:

$$\begin{aligned} \text{G/T} &= 13.14 - 46 + 53 \\ &= 20.14\text{dB} \end{aligned}$$

Next month, to round off this series, I shall look at three specific STV systems in detail.

Quality	Grade	Impairment	Approx C/N (dB)
Excellent	5	Imperceptible	20
Good	4	Perceptible but not annoying	15
Fair	3	Slightly annoying	10
Poor	2	Annoying	7
Bad	1	Very annoying	5

Table 1 CCIR picture assessment compared to satellite receiver carrier-to-noise ratio

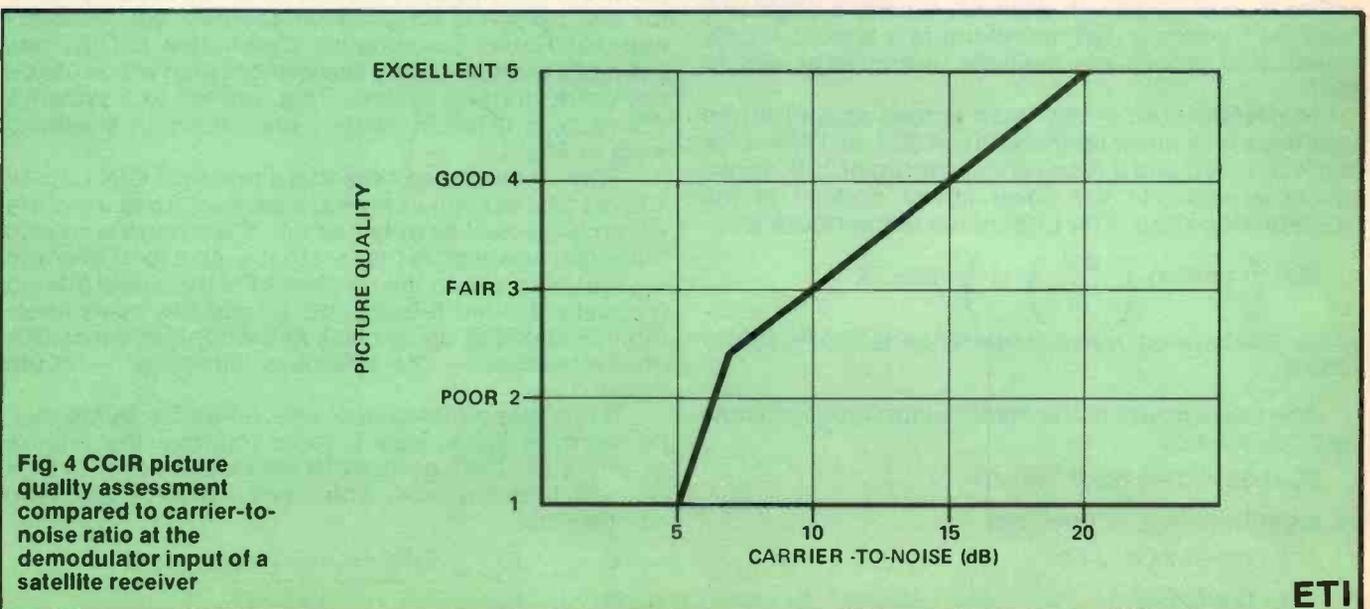



LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchrodyne AM receiver described in "Wireless World". The complete unit is cased to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains easy to build. The Synchrodyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HIFI listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of its sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life. K900W Stereo Kit with Wound Coils and Twin Meter Drive £65.67
RJS1 Reprints of Original Articles £1.30 no VAT

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are fitted:

- HC20 Permalloy Stereo Head. This is the standard head selected as original equipment on most decks £7.85
 - HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £14.86
 - HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £14.60
 - HX100 Stereo Permalloy R/P head. Special Offer £2.49
 - MA481 2/2 Language Lab R/P head £13.35
 - SM166 2/2 Erase Head. Standard mounting, AC type £8.85
 - SM150 2/2 Erase Head. DC Type £3.60
 - HQ751E 4/4 Erase Head for Portastudio etc. ... £46.80
- Full specifications of these and other special purpose heads in our lists.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £4.85
Curved Pole Type for inaccessible heads £4.85


Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

- INLAND**
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50
- OVERSEAS**
Please send sufficient to cover Surface or Air Post as required.

HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer.

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS

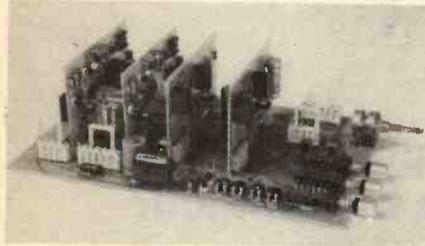

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

- Complete Stereo Record/Play Kit £33.70
- VU Meters to suit £2.30 each
- Reprints of original Articles 75p no VAT
- 860X Stereo Mic Amplifier £8.70

LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hood's articles in "Hi-Fi News". Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

- K300-35. 35 Watt. Discount price for Complete Kit . £98.79
- K300-45. 45 Watt. Discount price for Complete Kit £102.36
- RLH4&5. Reprints of Original Articles from "Hi-Fi News" £1.05 no VAT

Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE
(0691) 652894

ALL PRICES EXCLUDE VAT UNLESS STATED



PINEAPPLE SOFTWARE

Programs for the BBC model 'B', B+, Master and Master Compact with disc drive

DIAGRAM II - now also available for ARCHIMEDES

Diagram II is a completely new version of Pineapples popular 'Diagram' drawing software. The new version has a whole host of additional features which make it into the most powerful and yet quick to use drawing program available for the BBC micro. The new features mean that 'Diagram II' can now be used for all types of drawings, not just circuit diagrams. Scale drawings are possible and the facilities for producing circles and rubber banded lines together with the pixel drawing routines make any type of drawing possible. This advert has been produced completely using Diagram II.

Summary of Diagram II features:-

1. Works on all model BBC computers and makes use of Shadow memory if poss.
2. Rapid line drawing routines with automatic joins for circuit diagrams.
3. Rubber band line and circle drawing modes.
4. Makes use of the Acorn GXR rom to produce ellipses, arcs, sectors, chords and flood filling.
5. Pixel drawing mode allows very fine detail to be added.
6. Defined areas of screen may be moved, copied, deleted or saved to disc.
7. On-screen cursor position indication allows scale drawings to be made.
8. Keyboard keys may be defined to print User Defined Characters allowing new character sets to be used.
9. Wordprocessor files may be loaded and formatted into defined areas.
10. Up to 640 LDCs if shadow memory available, 381 without shadow.
11. Compatible with Marconi Trackerball and most makes of 'mouse'.
12. All 'Diagram Utilities' are included.
13. Completely 'scaleable' print routines allow any area of the diagram to be printed either horizontally or through 90deg. in scales that may be varied in 1/2 steps allowing up to 18 mode 0 screens to be printed on an A4 sheet (still with readable text).
14. Smooth scrolling over the whole area of the diagram.

Diagram II consists of a set of disc files and a 16k Eprom. The disc is formatted 401 sided and 801 sided. Please state if this is unsuitable for your system, or if you require a 3.5" Compact disc

DIAGRAM II - £ 55.00 + vat P & P free


MARCONI TRACKERBALL

- For Model 'B' and B+ (with Icon Artmaster) £ 60.00 + vat
- For Master 128 (with Pointer Rom) £ 60.00 + vat
- Bare Trackerball (no software) £ 49.00 + vat
- Pointer Rom (available separately) £ 12.50 + vat
- Trackerball to mouse adapters £ 8.00 + vat
- Postage and Packing on Trackerballs £ 1.75

PCB

Pineapple's now famous PCB drafting aid produces complex double sided PCB's very rapidly using any model BBC micro and any FX compatible dot-matrix printer. The program is supplied on Eprom and uses a mode 1 screen to display the two sides of the board in red and blue either separately or superimposed. Component layout screens are also produced for a silk screen mask. The print routines allow a separate printout of each side of the board in an expanded definition high contrast 1:1 or 2:1 scale. The print time is typically about 5 mins. for a 1:1 print of a 7" x 5" board. This program has too many superb features to adequately describe here, so please write or 'phone for more details and sample printouts.

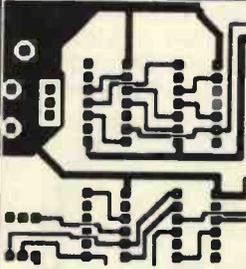£ 85.00 + vat Plotter driver to suit most plotters £ 35.88 +vat



PCB AUTO-ROUTING

This brand new addition to the PCB program greatly increases the power of the software and speeds the design of PCB's even more. A list of up to 150 connections may be entered in the form of a 'rats nest' and then the computer does the rest! You may specify which side of the board you wish a track to be on or you may leave the choice to the computer, and you may also say whether tracks should be allowed to pass between I.C. pins. The program is in the form of a second Eprom, and full features are available on a standard model 'B'. Please write or 'phone for full details.

COMPLETE AUTOROUTE PACKAGE £ 185.00 + VAT
(Including manual Eprom)

ADFS Utilities Rom

ADU is an invaluable utility for all ADFS users. It adds over 22 new commands to the ADFS filing system as well as providing an extensive Menu facility with over 35 sub commands covering areas such as repeated disc connection, saving and loading Rom images, auto booting of files and many more. Copying of DFS discs onto ADFS discs can be made in one pass with automatic creation of the required directories on the ADFS disc. All functions are fully compatible with Winchester drives including BACKUP which allows backing up of Winchesters onto multiple floppies. New commands are as follows:- *ADU, *BACKUP, *CATAL, *CHANGE, *DFSADFS, *DIRALL, *DIRCOPY, *DIRDESTROY, *DIRRENAME, *DISCEDIT, *DRIVE, *FILEIND, *FORMAT, *ILLADU, *LOCK, *MENU, *PURGE, *PURBCK, *UNLOCK, *VERIFY, *UFORMAT, *WIPE

PRICE £ 29.80 + vat

MITEYSPICE - Powerful A.C. & D.C. circuit analyser package - £119.88 +vat
with Graphics output. Send for more details

All orders sent by return

39 Brownlea Gardens, Seven Kings, Ilford, Essex IG3 9NL Tel 01-599 1476



MICRO CIRCUITS

Malcolm Brown takes a look at two programs for the BBC micro and Amstrad CPC machines to help the amateur circuit designer.

In the March 1987 issue of ETI we took a look at several programs for the BBC micro to help you design and draw circuits and PCB foils. One of the winners of that selection was Diagram from Pineapple Software. Now Diagram has been completely rewritten with many additions and improvements as Diagram II. First, however, we'll look at a new contender - a PCB design package for Amstrad CPC micro users.

*PCB Drafting Utility (cassette) £19.99
£21.99 (disk)*

*CADsoft, 18 Ley Crescent,
Astley, Tyldesley,
Manchester M29 7BD.*


The humble Amstrad CPC range of micros provide a lot of computer for not very much money so it is about time they were used to help the struggling electronics enthusiast.

This package is a PCB design tool to produce paper artwork of foils for subsequent photographic transfer to celluloid for UV exposure and etching.

The program is available on cassette for CPC464 users and on 3in disk for those with a CPC664 or CPC6128.

The program is in two parts - the editor and the plotter. Both sections are based on Basic programs with machine code routines.

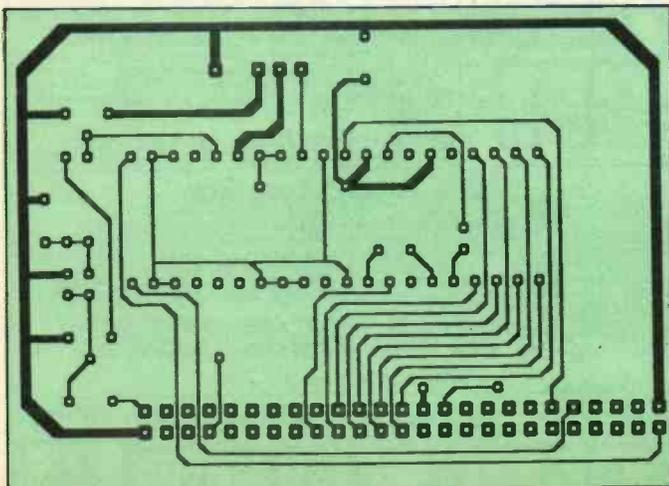The editor is used first to create your PCB design. PCBs up to 25x25in can be designed. The screen display shows a greatly enlarged section - about 4x2½in - at any time. However, the whole PCB can be drawn on at a time if you can manage to do this 'blind'.



This is more useful than it seems at first because it means a track can run for more than the width of the screen and still be drawn in one go.

This is a drawing package which stores the start and end co-ordinates of the lines (tracks) and points (pads) and suffers from the problems associated with this method. Although the whole PCB is much larger than the screen window, you cannot scroll across it. Instead the screen must be entirely redrawn from a new viewpoint each time.

However, that aside, drawing a PCB with this package is easy enough. There are three structures which can be drawn - pads, tracks and DIL packages (which are really just collections of pads - so there's only two structures after all).

Tracks are drawn by rubber banding. The cursor is moved around in discrete 0.05in steps and the Tab key starts and stops line drawing. The lines drawn on the screen in this way do not directly correspond to the tracks on the final PCB. The final width of the tracks is set separately to 0.0125, 0.025, 0.0325 or 0.05in.

Pads are similarly positioned at the current cursor position and they too can be preset in size to 0.05, 0.065, 0.085 or 0.1in.

Both pads and lengths of track can be deleted from the foil by moving the cursor to any part of them and pressing the appropriate key.

Sets of DIL pads are placed on the foil with the function keys and they can be set either horizontally or vertically. The pitch between the rows of pins can be altered to just about any conceivable value but sensible defaults are provided. Setting a row separation of zero provides SIL package pads.

Once on the foil design, the DIL pads are treated as individual pads and must be deleted one at a time.

The program can cope with double-sided boards and both sides are displayed at the same time in different colours. Which side is 'active' - being drawn on at the time - is selected with the U and L keys (upper and lower). All pads are always placed on both sides of the board which can occasionally be a problem.

The completed board can be saved to disk for further editing later or for printout.

The plotter routine uses a standard Epson-compatible dot-matrix printer. Either or both sides of the board can be printed and the printing can be either way around on the paper.

Printouts are made at twice size in four-inch strips which must be joined later for photography and are produced in either a quick draft mode or in the higher quality final mode.

The sections of the foil are drawn out on the screen before dumping to the printer and it is here that the real quality is shown. In this mode the tracks and pads

are expanded to their intended size and the pads take on the normal elongated oval shapes.

CADsoft's PCB Drafting Utility is adequate for most amateur use but it is not to the quality of Pineapple's PCB program (see that March 1987 review) for the BBC micro.

The Amstrad CPC micros have a far greater potential for this kind of work because of their vastly increased memory. However, some silly scrappy Basic programming mistakes (such as overwritten menu prompts and no disabling of the potentially lethal Escape key) means this program cannot be considered a truly professional tool.

Diagram II
£55+VAT (exchange deals
available for Diagram I users).
Pineapple Software, Brownlea
Road, Seven Kings, Ilford, Essex IG3 9NL.
Tel: 01-599 1476.

There are many drawing packages around for the BBC micro but this one uses an entirely new method of storing the picture to make it particularly suited to drawing circuit diagrams.

Many other drawing packages store the start and end co-ordinates of all the lines in the picture along with a code to determine whether a line is drawn or a rectangle or whatever. This can be wasteful of disk space and makes editing the picture slow and difficult.

Other programs (usually the more 'artistic' ones) store the memory mapped screen RAM. This is usually quite economical on storage space but useful editing is nearly impossible.

Diagram II uses neither of these methods. Instead, the picture is stored as an array of character codes (an extended ASCII coding system is used) with the bit map definitions corresponding to each code stored separately.

Of course with a picture (such as an artistic work) with a great deal of variation across it, this is an uneconomical method, to say the least.


However, with a diagram consisting of a great many repeated symbols and sections (as is a circuit diagram) this method is economical and has a few other great advantages.

Most important is the speed in which the diagram can be drawn. This not only means that it can be produced on the screen and edited quickly but also that the section shown on the screen can be just a part of a much greater whole. Diagram II allows smooth scrolling across a complete diagram of up to 30 Beeb mode 0 screens.

This method also allows the complete multi-screen diagram to be easily displayed on one screen with each pixel representing each character of the full sized screen. A complete diagram of up to 8x8 screens can be displayed in this reduced form for checking the 'whole look' of the diagram.

Despite this unique system, when using the program you would not know that Diagram II is any different from other drawing packages. The mechanics of it all are very cleverly hidden. The cursor is used to move around the diagram and a line is left trailing behind. The program automatically lays down the correct line character needed at that point in the diagram. Turn a corner and a right angle turn character is printed, cross another line and a cross character is printed at the intersection.

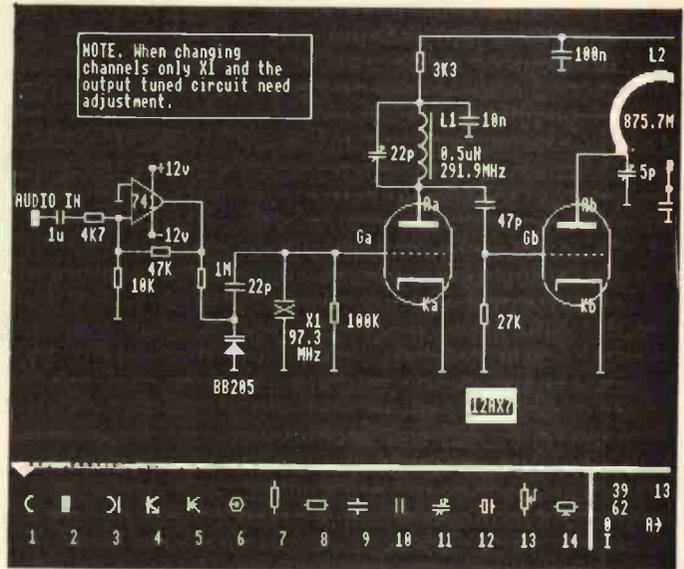A 'blob' can be left at line intersections just by



pressing Ctrl as you pass over the join. Now that just isn't possible with other types of drawing package. They require a precise positioning of a blob symbol after the lines are drawn.

This character system also means diagrams are naturally and easily kept aligned and 'square'. It is genuinely difficult to not draw neat and impressive diagrams using this software.

That's all very well for vertical and horizontal lines but Diagram II can also make use of 'rubber banding' to draw all the diagonal lines in between or for tracing an irregular shape. Amazingly, this still uses predefined characters, automatically selected and positioned to make up all the line sections.

As well as straight lines, Diagram II running on a Master or model B with Acorn's GXR ROM can produce circles, rectangles, ellipses, arcs and triangles, either filled or in outline, to build up large shapes. Without the GXR ROM only circles and filled triangles can be created.

Again, although drawing these shapes is performed with the cursor and is as easy as with any drawing package, the end result is made up of individual predefined characters which go to make up the complex shapes.


Text is positioned on the diagram simply by typing it in when the cursor is at the right position. Text can also be taken from a file created with Wordwise Plus and automatically fitted in a defined section of the diagram.

Diagram II can produce discrete symbols such as transistors, resistors and so forth. These are also made up of characters - up to 12 normal Beeb 8x8-pixel characters.

With a basic model B BBC micro, 335 characters can be defined, shared between the symbols. With a machine using shadow memory (such as the B+ or Master) 880 Beeb characters can be used.

A definite improvement over the old program is the ability to delete unwanted symbols and so free the characters for use with new ones. The complete set of symbols or just a limited subsection from one diagram can be saved to disk to use with another diagram - again a useful addition.

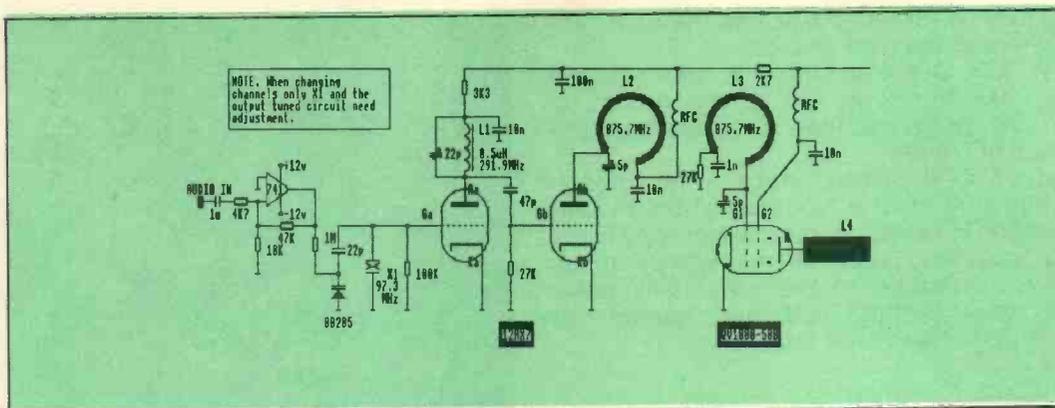To design these symbols a very effective character definer is provided. There have been many such definers produced for the BBC micro but this is one of the best I've seen. It is fast and simple to use. As well as allowing the symbols to be defined one pixel at a time on an enlarged grid, complete symbols can be emptied



or flipped horizontally or vertically.

The character definer can of course be used to define new styles of text characters and these can then be inserted in the diagram just like 'normal' text, from the keyboard.

Each character has a 'direction' defined along with it. This controls the cursor movement after the character is positioned on the diagram. The direction can be defined in any of the four compass directions so that, say, a complete set of upside down characters could be typed right to left straight from the keyboard without fiddling with the cursor between characters.

Any area of the diagram can be defined with the cursor and then deleted, moved, copied to another part of the screen or saved to disk to be inserted into another part of the program or into another diagram altogether.

Borders can also be added in one single movement

and existing diagrams changed in size for additions or shifted across an enlarged diagram.

The completed diagram is stored on disk or printed on a standard Epson compatible dot-matrix printer at just about any size from three screens to just one character across a sheet.

All the parameters entered to control the size, position and codes used for the printout can then be saved to disk to save time for later repeat runs.

The quality of printing is the last factor which makes Diagram II so outstanding. This package really is capable of producing top quality diagrams. It is difficult to see how this package could now really be improved. For anyone looking for ways to edit, store and print out professional circuit diagrams with a bare minimum of equipment, Diagram II is the only answer.

ETI

AUDIOKITS PRECISION COMPONENTS



THE 30+30 INTEGRATED AMPLIFIER

- ★ DESIGNED FOR OUTSTANDING SOUND QUALITY
- ★ VERY HIGH QUALITY COMPONENTS SUPPLIED
- ★ LOW TEMPERATURE GENERATED DISTORTION
- ★ ULTRA LOW NOISE MC STAGE
- ★ STAR EARTHING - MAPPED ON PCB TRACKS
- ★ CLEAN SOUND RIGHT UP TO FULL OUTPUT
- ★ 7 SEPARATELY RECTIFIED POWER SUPPLIES GIVES OUTSTANDING STEREO IMAGERY
- ★ LATEST KITS HAVE IMPROVED HEAT SINKS AND LOWER RESIDUAL NOISE

IMPROVED VERSION ALSO FEATURES

- ★ BULK FOIL RESISTOR (Temp. Coefficient 5ppm/°C) IN CRITICAL PLACES
- ★ HOLCO RESISTORS FOR OUTPUT TRANSISTOR EMITTER RESISTORS
- ★ POLYPROPYLENE AND POLYSTYRENE CAPACITORS
- ★ LONG LIFE ELECTROLYTIC CAPACITORS
- ★ KIMBER CABLE FOR INTERVAL WIRING
- ★ GOLD PLATED PHONO SOCKETS
- ★ EXTRA OUTPUT TRANSISTORS FOR 40 WATT OUTPUT

PRICES Standard 30+30 kit £172 + £6 p&p = £178
Standard with extra o/p transistors £185 + £6 p&p = £191
Improved kit £380 + £6 p&p = £386

Export version to order with 110V or 220V primary transformers. P&P charges by quotation. Delivery 14 to 21 days, but can be longer as lead times for manufacture of case or supply of some top quality parts used in improved version is much greater.

ETI VIRTUOSO PREAMP KITS, PCB'S AND ALL PARTS AVAILABLE.

ETI System A Preamp & Power Amp

ETI Audio Design Preamp & Power Amp

Amazing how many ETI readers are still building system A and Audio Design pre and power amps, many years later. Most are using higher grade parts recommended and supplied by Audio Kits and enjoying much better sound quality than the original design. Special parts list available on request.

For details of Audio Kits components and kits, please send SAE (9" x 4") (overseas 3 IRCs) to:
AUDIOKITS, 6 Mill Close, Borrowwash, Derby DE7 3GU. Tel: 0332 674929

SONY SPEAKERS

MODEL
Z-3000
20 WATT
2-WAY

made in UK

Size 41.5 x
25 x 17cm
approx.

Impedance
6 ohm
nominal.

Finished in
simulated
black teak with
matching grille.



£20.95
per pair + p&p £3.95

JUST OUT
1988
CATALOGUE

Send 50p (cheque or P.O.)
and 230 x 325mm s.a.e.

RTVC


All mail to RTVC, 21 HIGH STREET,
ACTON W3 6NG. Callers to Acton or
323 Edgware Rd, London W2.
Please allow 14 days delivery.

Payments to RTVC Ltd. Order by Access - tel: 01-992 8430.

SURFACE MOUNT

IT'S NEW, IT'S HERE AND ONLY AVAILABLE THROUGH ETI MICRO MINIATURE SURFACE MOUNT PROJECTS

You've heard about them, probably seen and marvelled at them inside your calculator or watch and now you can begin using them with the latest range of surface mounted component kits from SUMA DESIGNS. All the kits are of well proven, in-house design and come complete with all components individually packed for easy identification, high quality fibreglass, surface mount, solder resist P.C.B., full assembly and circuit instructions. All you need is a pair of tweezers, a fine-tipped iron and a steady hand. Using assembly techniques developed to cope with our own prototype and batch manufacture you can be assured of success. To make things even easier we have developed a custom made component jig which although not essential greatly simplifies assembly and is well worth the investment. A full range of SM components are also stocked for your own projects.

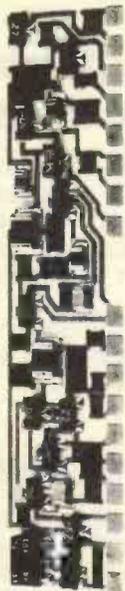

SM20:	SOUND TRIGGERED SWITCH: Triggers from slightest sound, L.E.D. indication, variable sensitivity.	£13.95
SM21:	DIGITAL DICE: Touch control, roll down speed SM L.E.D. readout.	£15.95
SM22:	VHF FM TRANSMITTER: Complete with mic, tuneable over 88-108 band.	£12.95
SM23:	LIVE WIRE DETECTOR: Non-contact indication of live wires, blown fuses etc.	£9.95
SM24:	VHF FM BLEEPER: Transmits constant bleep to nearby FM radio. Tuneable.	£13.95
CHJ22:	Custom designed assembly jig for speedy and accurate assembly.	£6.96

Send 9 x 4 S.A.E. for full details of these and other kits plus all components available.

All prices are inclusive but please add £1.50 per order to cover post & packing.

SUMA DESIGNS The Workshops
95, Main Road, Baxterley,
Near Atherstone,
Warwickshire. CV9 2LE
Telephone: 0827-714476

WIN A 600MHz FREQUENCY COUNTER!

IN THE NEW STYLE WINTER 1987/88

Circuit CATALOGUE

- Oscilloscope Digital Storage Unit
- Temperature Controlled Irons
- 5 and 50W RF Power Heads
- £££s of Discount Vouchers
- Easy to Enter Competition
- Quantity Price Discounts
- PCB Prototyping System
- 2 new HF Receiver kits
- 24 hour order line
- Component Packs
- 12 new books
- Special Offers

ONLY £1.20

PACKED WITH NEW LINES

Available from your local newsagent or direct from Cirkuit at the address shown below

Cirkuit

Access VISA

Cirkuit Distribution Ltd.
Park Lane, Broxbourne, Herts EN10 7NQ
Telephone (0992) 444111 Telex: 22478

TWO GREAT HOBBIES

ONLY
£124.50
INC VAT



... IN ONE GREAT KIT!

The K5000 Metal Detector Kit combines the challenge of DIY Electronics assembly with the reward and excitement of discovering Britain's buried past.

THE KIT - simplified assembly techniques require little technical knowledge and no complex electronic test equipment. All stages of assembly covered in a detailed 36 page manual.

THE DETECTOR - features Analytical Discrimination & Ground Exclusion, backed by the proven pedigree of C-Scope, Europe's leading detector manufacturer.

Ask at your local Hobby/Electronics shop or contact:-



C-Scope International Ltd., Dept. ETI
Wotton Road, Ashford, Kent TN23 2LN.
Telephone: 0233 29181.

DOMAIN POINTS AGAIN

Paul Chappell pulls his phasors together to find a use for mathematics in circuit design

Last month's article was concerned with the mechanics of manipulating complex numbers with hardly a mention of how this might apply to electronics. This month I'll redress the balance and concentrate on applying complex number arithmetic to circuit calculations.

We haven't reached the end of the mathematics by a long way but it's just as well to keep the final objective in sight — to make AC circuit theory as easy as π .

The Story So Far

In an earlier article (November 1987 *Circuit Theory*) I demonstrated that in a capacitor with a sinusoidal voltage applied, the current would also be sinusoidal. The ratio of the voltage and current amplitudes at any given frequency is constant so the capacitor can be thought of as having a 'resistance' to sine waves.

Since the apparent resistance varies with frequency and the voltage and current waves are offset by 90° , it's not quite the same as ordinary resistance. It is given the name *reactance*, the symbol X_c , and for a capacitor C at angular frequency ω it has the value $-1/\omega C$.

For a sinusoidal current of amplitude I , the voltage amplitude will be given by $V=I \times X_c$, just as for an ordinary Ohm's law calculation $V=I \times R$. An inductor has similar properties and a reactance X_L of ωL .

The problem we found with using the straight voltage-to-current amplitude ratio as the 'resistance' of reactive components was that the 'resistances' didn't add for components in series and the usual parallel resistor calculations didn't apply to components in parallel. So the concept of an AC 'resistance' was rather limited in application!

We concluded that this problem arose because the 90° phase difference between voltage and current was not being taken into account. With the aid of complex numbers we are now in a position to correct this flaw and bring out the full power of the ideas.

A Practical Example

Let's take a look at the circuit of Fig. 1(a). To keep our feet firmly on the ground I haven't used normalised values — the frequency and components are those you might find in a real circuit. I haven't specified the input for the moment. All we know is that it's a sine wave of angular frequency 5×10^6 radians per second (roughly 800kHz).

The reactances of the inductor and capacitor at this frequency will be $X_L=500$ ohms and $X_C=400$ ohms. This suggests that the entire circuit has an impedance of $1000R$ and that a 1mA amplitude current should produce a voltage across the circuit of 1V (both at 800kHz).

We already know that this doesn't happen and Fig. 1 shows why. Taking the cosine form of the input

current and freezing the phasors at $t=0$ gives the situation depicted in Fig. 1(b) for the individual voltages across each component and Fig. 1(c) for the combined voltages. The voltage across the entire circuit (V_{in}) has an amplitude of 141mV against a predicted value of 1V. Our estimate was out by a factor of seven!

The diagrams show clearly what has gone wrong. To give the predicted 1V, the voltages would all have to be in phase so their phasors would add in a straight line. They aren't and they don't!

Ordinary numbers can't take into account the direction of the phasors. All they can do is tell you how long they are. Complex numbers can do both!

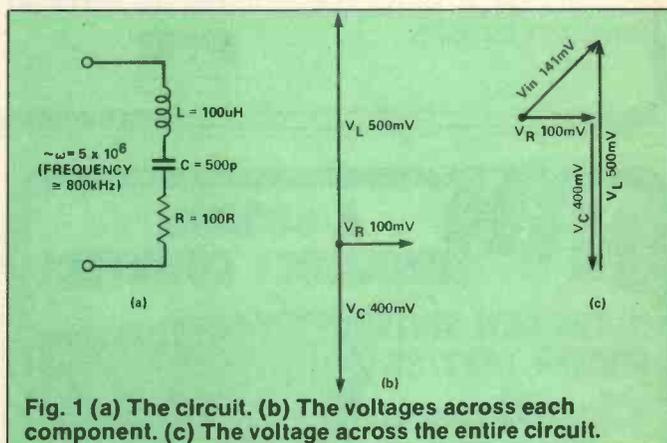


Fig. 1 (a) The circuit. (b) The voltages across each component. (c) The voltage across the entire circuit.

Let's begin again. First of all we'll relabel the circuit as shown in Fig. 2. We have now entered the *frequency domain*! This means every time I mention a current I or a voltage V , they are automatically assumed to be sinusoidal in form (which saves having to state the obvious every two minutes) with amplitudes I and V respectively.

This also means the components are labelled with their complex impedances rather than with their normal component values. We'll see how it works right now.

First of all, we'll set the input frequency to $\omega = 5 \times 10^6$ radians per second. Now we can work out the impedances of each of the components. $Z_L = j500$, $Z_C = -j400$ (note the minus sign — remember that $1/j = -j$) and $Z_R = 100$.

To find the impedance of the entire circuit, just add up the individual impedances. $100 + j500 - j400 = 100 + j100$. If we agree to work in mV and mA, then a 1mA input current (remember: frequency domain so this means a sinusoidal input current of amplitude 1mA and *not* a steady 1mA current) in cosine form will be $I = 1 + j0$ (or just 1 for short!). The voltage will be $I \times Z_{in} = 1 \times (100 + j100) = 100 + j100$ and we're through. Well, almost. My voltmeter doesn't actually register voltages of $100 + j100$!

To express the answer in more familiar terms, we have to translate back to the *time domain*. The voltage $100+j100$ has a modulus (length) of 141 and an argument (angle) of $\tan^{-1}(100/100)=45^\circ=\pi/4$. In full, we've discovered that an input current of $\cos(5 \times 10^6 t)$ at the input will give rise to a voltage $141 \cos(5 \times 10^6 t + \pi/4)$ across the input terminals.

Now let's look at the pictures to see what's going on. First of all, we agree to draw our phasors in the *complex* or *z-plane*. The phasor representing a current of 1mA in cosine form points along the positive real axis and is described in complex number form as $1+j0$ (we're working in units of mA and mV, remember).

This gives rise to a voltage of $(1+j0) \times (j500)$ across the inductor which comes to $j500$ or a phasor of length 500 pointing up the positive imaginary axis. There's no need to draw it again — it's there in Fig. 1(b)!

The voltage across the capacitor comes to $-j400$ — represented by a phasor of length 400 pointing down the negative imaginary axis (as in Fig. 1(b)). The voltage across the resistor you can work out for yourself!

Now we add up the three individual voltages (remember from last month that complex number addition corresponds to addition of phasors in the *z-plane*) giving the result shown in Fig. 1(c). The voltages due to a unit current add correctly so the impedances must also add correctly, since impedance is exactly that — the voltage per unit current.

Time And Frequency Domains

Just about every circuit you've ever seen in the pages of ETI is in the *time domain*. All this means is that if you know how the input behaves as a function of time, you can deduce the output — either by calculation, common sense or by reading the 'How It Works' section!

You might ask yourself what happens when the switch is pressed. What happens just after the pulse reaches IC5? When will the output of IC9 go high? All questions to do with time. First one thing happens, then another, then another ... OK, I won't labour the point any more!

Figure 1(a) is a time domain circuit. You could ask what its response is to a voltage step then draw the output as a graph of voltage against time and so on.

Now, we know that if the input to the circuit of Fig. 1(a) was a sine wave, every single voltage and current would also be a sine wave. So asking how the circuit behaves in time is silly. We know already — it gives sine waves.

If we know the voltages and currents in the circuit at any instant in time, we can deduce what they will be for evermore. So to inspect the circuit we suspend the operation at a single instant in time. All the currents and voltages can be visualised as phasors, immobile as frozen twigs on a February morning.

To help with the calculations, we draw a *frequency domain* circuit as in Fig. 2(a). The input voltage and current are represented by their frozen forms and the components are labelled with their complex impedances which makes it easy to calculate the lengths and angles of all the other frozen twigs.

Having studied the circuit to our hearts' content, we set the phasors spinning again and translate the circuit back into the time domain.

You'll notice that none of the expressions we've used in calculating impedances or whatever has a 't' in it. There is no reference to time. The variable we do have at our disposal is the angular frequency ω . Hence the name frequency domain. So far we haven't made use of the ability to vary ω , but that's about to change.

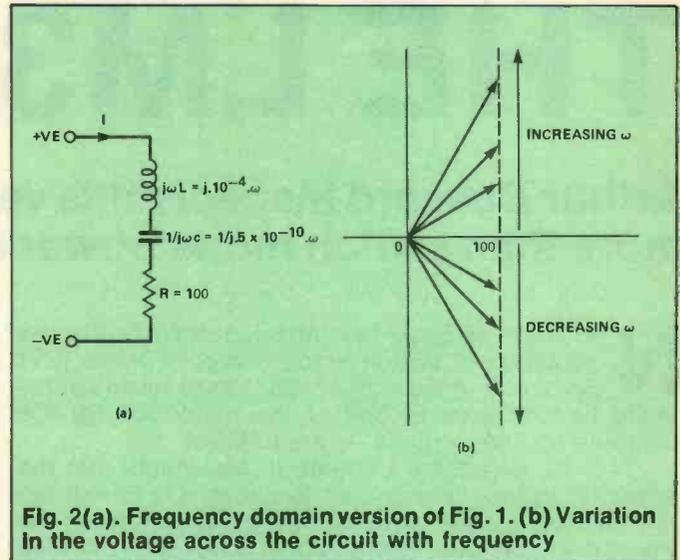


Fig. 2(a). Frequency domain version of Fig. 1. (b) Variation in the voltage across the circuit with frequency

Frequency

Sticking with the circuit of Fig. 1(a), let's see what we can find out about its behaviour at different frequencies. First of all, you'll notice the voltage across L is proportional to frequency. As ω increases, so will the voltage across L. As the frequency decreases, so will the voltage.

For the capacitor, exactly the opposite happens. Up the frequency and the voltage goes down. Reduce the frequency and the voltage rises.

If you think about the effect of this on Fig. 1(c) (assuming an input current of 1mA at various frequencies) as the frequency increases, V_C gets shorter and the V_L phasor gets longer. The resultant voltage across the entire circuit gets larger in magnitude and leads the current by a greater and greater angle.

Reducing the frequency increases V_C and reduces V_L so the overall voltage swings downwards and lags the current by a greater and greater angle. The effect on the voltage across the circuit as a whole is shown in Fig. 2(b) for various frequencies. (It's at times like this I wish I could produce animated graphics with all the phasors altering in length and the voltage phasor gliding along its path. Since we haven't found a way to do it on the pages of ETI, you'll have to use your imagination!)

For some value of ω , the voltage across the circuit will point along the positive real axis. It will be in phase with the input. It will also have its minimum amplitude at this point. (If you can see where this is leading, take the Mrs Beestly prize for supreme cleverness!)

Let's see if we can work out the frequency at which this happens. Looking at Fig. 1(c), it's clear that the condition for the voltage phasor for the whole circuit to point along the positive real axis is that $V_C = -V_L$. If this holds, the voltages across the inductor and capacitor will cancel and the voltage across the entire circuit will be equal to the voltage across R. In mathematical terms we require $1/j\omega C = -j\omega L$. Solving for ω we get $\omega = 1/\sqrt{LC}$.

If you still haven't caught on, perhaps the more familiar $f = 1/2\pi\sqrt{LC}$ will give you a clue!

We've just derived the condition for the circuit to be in resonance. The fact it was obtained so easily is a demonstration of the power of this method of analysis that you'll appreciate if you've ever tried to derive the same result in the time domain with the aid of a page of differential equations!

If you think this is good, you ain't seen nothing yet! Watch this space next month.

ETI

THE LM3524

Arthur Bossard inspects this versatile IC and finds it's good for more than switch mode power supplies

Now that Les Sage has introduced you all to the mysteries of switch mode power supplies (ETI October and November 1987) it seems an appropriate time to look at one of the many control ICs available for the purpose — the LM3524.

This IC is not the ultimate in high-tech, just the opposite, in fact. It is chosen because it is cheap (so you can experiment without heart palpitations at the thought of ten quid going up in smoke!). It is also readily available, doesn't need many external components to make it do its stuff and because it can be used for other control functions (or even as an LED flasher if your imagination deserts you!)

For those not familiar with switching regulators, the LM3524 is a good introduction since the basic functional blocks are not obscured by a mass of control circuitry. There's an over-current sensor, a logic input to shut down the IC in case of faults in other parts of the circuit, and that's your lot.

The functional blocks inside the IC are shown in Fig. 1. The heart of the IC is the oscillator which runs at a frequency set by the resistor and capacitor from pins 6 and 7 respectively. The capacitor is repeatedly charged at a constant current to 3.5V, then quickly discharged back to 1V, resulting in a sawtooth waveform at pin 7.

Forgetting the input amplifier, current limit and all the rest of the paraphernalia for a moment, imagine applying a DC voltage to pin 9 of the IC. (You can actually do it if you want to, as the internal amplifiers are transconductance types and won't be upset by it).

If the voltage at pin 9 is below 1V, the comparator output will always be high since its positive terminal is connected to the sawtooth waveform which is always above 1V. If the voltage at pin 9 is a little above 1V, the comparator output will go low briefly after each discharge of the capacitor. A higher voltage on pin 9 will keep the comparator output low for longer and an input above 3.5V will keep it low all the time.

So the comparator output is a rectangular wave with a duty cycle controlled from zero to 100% by the voltage on pin 9. If this wave were fed directly to a single output transistor, we would already have a very basic voltage controlled pulse-width modulator suitable for use in a switching regulator!

The LM3524 has two output transistors to allow for push-pull operation. Where this is not required, the two transistors are connected in parallel. The flip-flop switches between the two transistors on alternate cycles of the oscillator.

The gate input from the oscillator's output is a 'blanking pulse' to give a short period when both transistors are turned off, preventing cross-conduction at maximum duty cycle.

You can get a 'feel' for the operation of the IC so far by connecting up the circuit of Fig. 2. The LEDs flash alternately as the flip-flop switches from one output transistor to the other. RV2 sets the oscillator frequency and therefore the flashing frequency. RV1 controls the duty cycle of the out pulses.

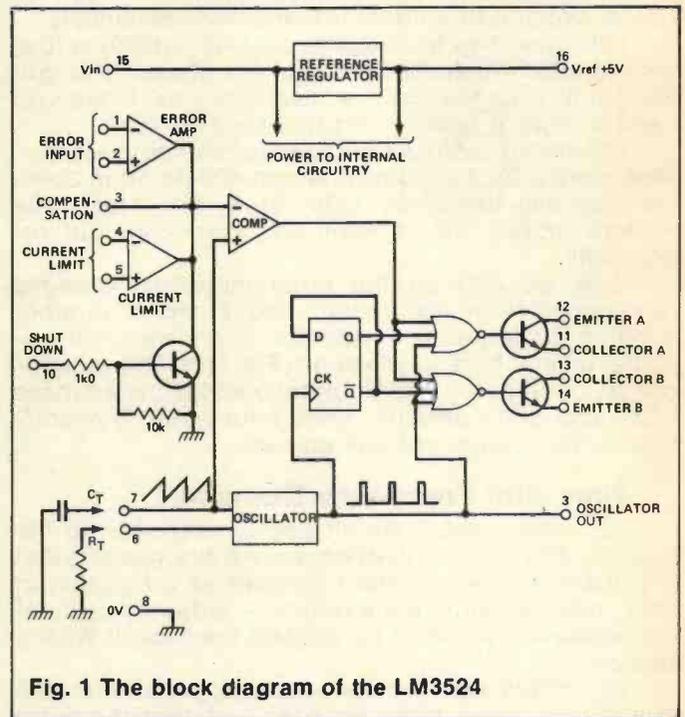


Fig. 1 The block diagram of the LM3524

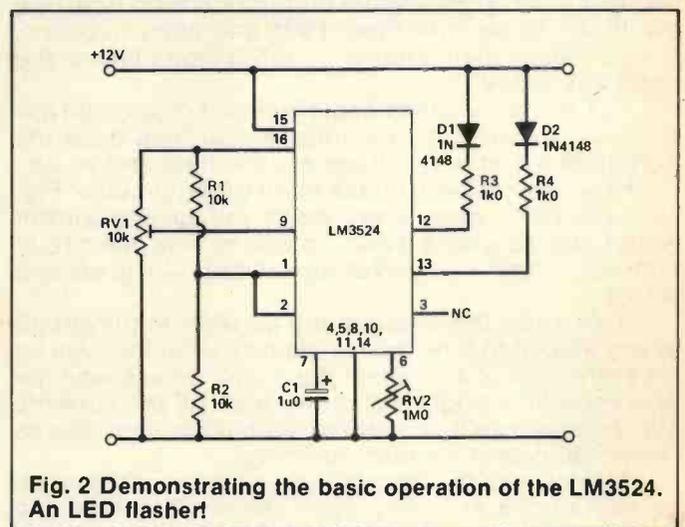


Fig. 2 Demonstrating the basic operation of the LM3524. An LED flasher!

At the ground end of its travel, as soon as one LED turns off, the other turns on (apart from the brief blanking pulse, which won't be visible). As the preset is rotated, the flashing becomes briefer, giving a more 'urgent' look to the display.

This could actually be quite useful for a warning display, or for use with model cars or trains to simulate danger signals.

Strictly speaking, the values of R_T and C_T (RV2 and C1 in Fig. 2) should not be above 100k and 100n respectively for reliable operation. What you'll find is that if you try to reduce the frequency too much the

flip-flop won't switch over, so you'll be left with one flashing LED and another that doesn't light at all.

Switching regulator circuits

The basic step-down regulator configuration is shown in Fig. 3. This is broadly equivalent to a standard series regulator. The input voltage can be anywhere between 8V and an absolute maximum of 40V. The output (for the component values shown) will be 5V. The maximum input current, without an external drive transistor, will be 80mA.

For the small currents involved, L1 will have to be quite high in value to sustain conduction when the transistors are turned off. A value of about 10mH will be needed. D1 can be a 1N4148.

The value of C3 will depend on the amount of ripple that can be tolerated on the output. A value of 1uF is a

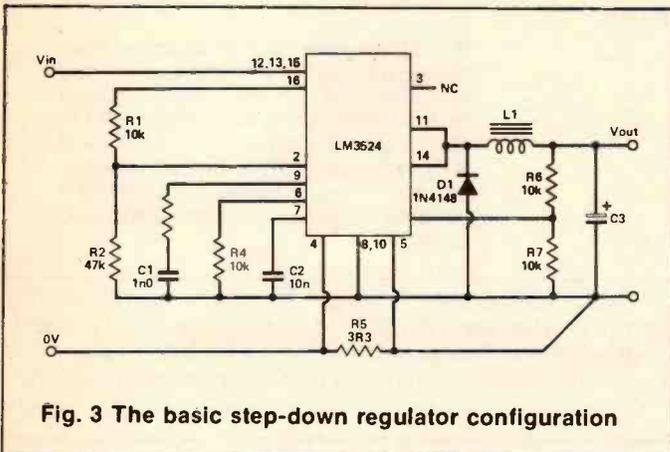


Fig. 3 The basic step-down regulator configuration

reasonable starting point. Increasing the value will improve the smoothing but will make the circuit less able to cope with rapid changes of input or load.

A Step Up

The basic step-up regulator configuration is shown in Fig. 4. Once again, L1 can be about 10mH, C3 1uF and for the low frequency and small currents involved D1 can be a 1N4148. The output voltage will be 27.5V for the component values shown. The input can be anywhere from 8V to about 20V.

The output voltage can be varied by changing the value of R5. If a current limit is needed, it can be connected in the same way as for Fig. 3.

The component values given are intended as a starting point for experiment — this isn't a project! You might like to try finding the limits of each circuit for the values given — particular of the inductor. What is the smallest different in output and input voltage that the circuits will cope with? What is the largest? (Bear in mind that the IC will be damaged by input voltages (Fig. 3) and output voltages (Fig. 4) of over 40V.)

How does it cope with variations of the load? What is the disadvantage of using too large an inductor? Or too small? What happens if you use a 1N4001 in for the rectifiers? Or a schottky diode? What happens if you make the value of the smoothing capacitor 10uF or 1000uF?

My theory about electronics is that an hour spent in intelligent experimentation (where if something goes wrong you ask 'why?' — and make damn sure you come up with an answer!) is worth a week reading a text book. That's not to devalue theory but a touch of practical experience gives meaning to what would otherwise be dry and uninteresting facts.

If your amplifiers oscillate and your regulators

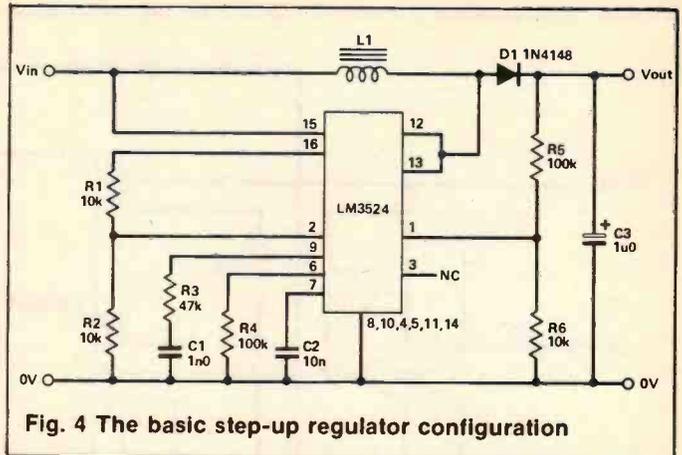


Fig. 4 The basic step-up regulator configuration

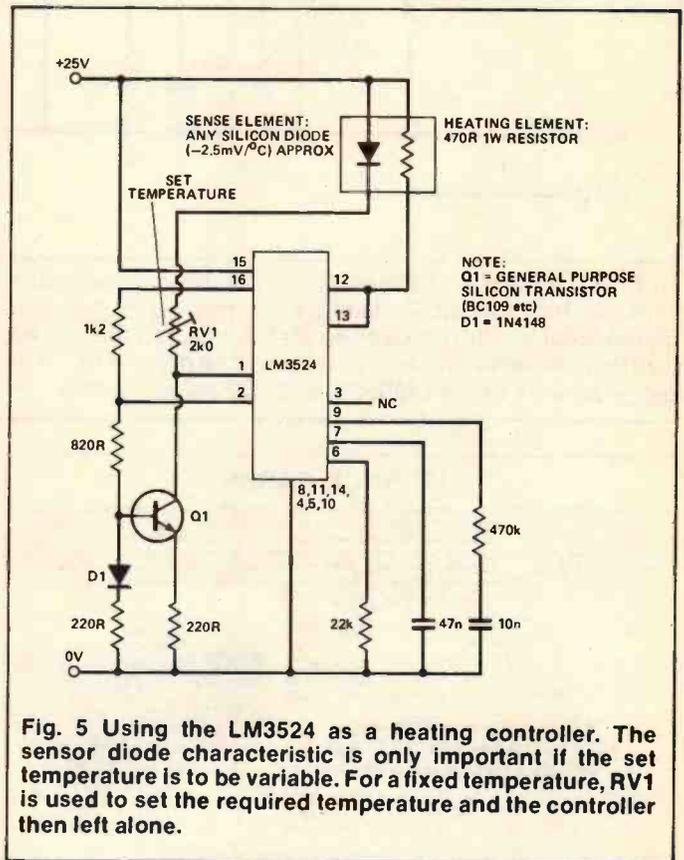


Fig. 5 Using the LM3524 as a heating controller. The sensor diode characteristic is only important if the set temperature is to be variable. For a fixed temperature, RV1 is used to set the required temperature and the controller then left alone.

don't regulate, it gives you the incentive to get to the bottom of what's going on!

Other applications

The LM3524 is quite a versatile little IC and can be used for other purposes besides switching regulators. One thing that occurs to me is that it could be used for temperature regulation of sensitive components — a crystal oven for example.

In its simplest form, the heating element could be a resistor connected to the output transistor collectors (Fig. 5). The temperature sensing element could be a common or garden diode, arranged so that increasing temperature causes a rise in voltage at pin 1 of the IC. The set point would be controlled by varying the DC offset at pin 1 or the voltage at pin 2.

Another possibility is to make optically isolated analogue outputs, such as the ones in the recent ETI EEG Monitor. A different approach would be to vary the mark-to-space ratio of the outputs in sympathy with the analogue signal. The circuit (Fig. 6) is similar

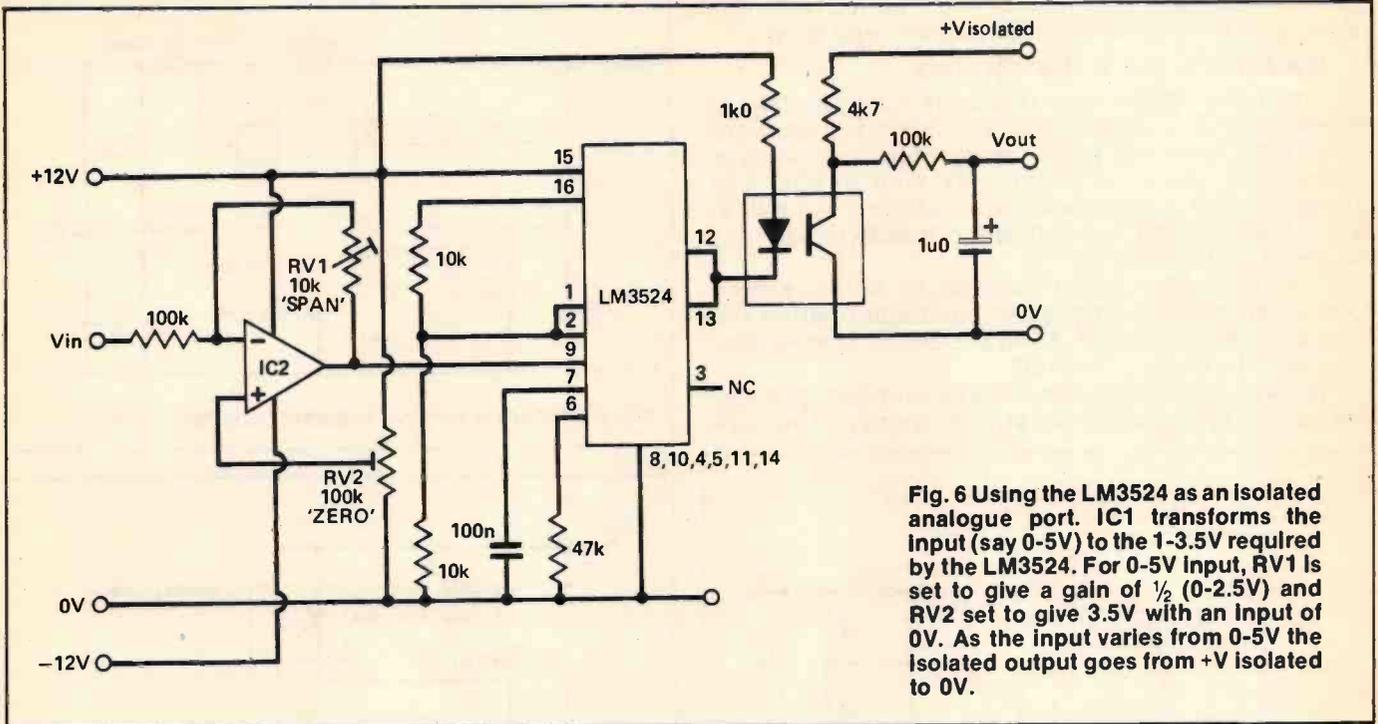


Fig. 6 Using the LM3524 as an isolated analogue port. IC1 transforms the input (say 0-5V) to the 1-3.5V required by the LM3524. For 0-5V input, RV1 is set to give a gain of 1/2 (0-2.5V) and RV2 set to give 3.5V with an input of 0V. As the input varies from 0-5V the isolated output goes from +V isolated to 0V.

to Fig. 2 with the LEDs replaced by the opto-isolator and the two output transistors connected in parallel. Some level shifting is needed on the input to match the available analogue voltage range with the requirements of the LM3524, and IC2 achieves this.

Infra-red remote control? Once you start thinking about it, the possibilities for applying this IC seem endless. Have fun experimenting, and don't forget our Tech Tips page if you come up with something good.

ETI

19" RACK CASES

* Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish * New improved construction and finish * Black anodised aluminium front panels * Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure * Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles * With ventilation slits and plastic feet * Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package spare front panels available.

Order Code	Panel Size W H (inch)	Rear Box W H D	Weight	Price £
1U-10	19 x 1.75	17 x 1.5 x 10	2.4kg	23.50
2U-10	19 x 3.5	17 x 3.0 x 10	2.9kg	24.50
3U-10	19 x 5.25	17 x 5.0 x 10	3.5kg	26.50


**15% discount on
1U-10 2U-10 3U-10
with this advert.**

2U-12	19 x 3.5	17 x 3.0 x 12	3.3kg	25.50
3U-12	19 x 5.25	17 x 5.0 x 12	4.0kg	27.50
4U-12	19 x 7.0	17 x 6.5 x 12	4.6kg	29.95

Please add £3.00 P&P for the first item and £1.50 for each additional item. No VAT to be added to the price.



TEST EQUIPMENTS

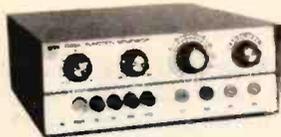

C83A Digital Power Supply/Voltmeter (0/35 Volts 1.5 A)	£44.95
C83B Digital Power Supply (0/30 Volts 1 A)	£38.95
C89A Function Generator (2 Hz to 200 KHz)	£39.95
C86A 60 MHz Counter/Timer	£47.95
C87A Autoranging Capacitance Meter (0.1 pF to 99.9 mF)	£47.95
MV338 Metal-mains detector	£4.99

A new range of quality test equipment at the lowest possible price. The C89A (£34.95) and C86A (£39.95) are also available in kit form with full construction details. Please add £3.00 p/p per item (£1.00 for MV338).

To order send cheque/postal order — please allow up to 7 days despatch for cheque clearance. Quantity discount available. Customers who require further information please send S.A.E. Trade and overseas orders welcome. Mail order only.

T.J.A. DEVELOPMENTS
Dept. ETI, 19 Welbeck Road,
London W3 0JT.

Zenith Electronics. KITS · MODULES · HARDWARE

The following are examples of our proven product designs

- High quality touch dimmer 500W R/Built £12.99
- Selectable tone generator 9-12V operation £5.50
- 3-Note Electronic Door Chime unit, 9 volt operation, three melodious tones; variable frequency. Kit £9.83
- Miniature FM Transmitter; 60-145, MHz. Kit £6.95
- R/Built £8.95
- 3-Watt FM Transmitter, 80-108MHz. Kit £13.99
- R/Built £18.99
- 300-Watt Light Dimmer unit for 240 volt mains lights, Kit £6.95
- 4-Code Digital Code unit plus Key Pad — select own code; 9-volt Kit £15.95
- 5-100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit £11.11

BLACK ICE ALARM

Revolutionary design which will detect black ice for motorists. Kit includes all components, P.C.B. sensor unit, dedicated case and full instructions. Kit £17.53 Ready Built £20.75

- VU Meter 10 LED indicator; -5 to +12dB range. Kit ... £12.99
- Automatic light controller; automatically turns on and off lights at preset times and triggered by darkness. Kit .. £25.08
- Mains Wiring and Metal Detector. R/Built £11.00
- Zenith Speech Processor. P-202. R/Built £25.00
- 18-Watt Car/Home Power Amp. 12-Volt. Kit £13.23
- Amplifier Power Meter; 10-LED indicator from 0.25-100-Watt Input — 9 volt operation. Kit £9.52
- Light-sensitive relay unit; variable sensitivity trigger control; senses light or dark — selectable. Kit £8.45

ALL KITS CONTAIN FULL INSTRUCTIONS, P.C.B.s AND COMPONENTS.

ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.

OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.

PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.

Large SAE
26p stamp for
free catalogue

Zenith Electronics, 14 Cortlandt Business Centre,
Hailsham, E. Sussex, U.K. BN27 1AE.
Tel: 0323 847973 Telex: 878334

GAS ALERT

Greg Thompson promises not to set the world alight with this top-spec gas detector design

Gas explosions in the home, caravans and the like are becoming virtually a daily occurrence. The ET1 modular gas detection system will help to reduce these horrific accidents.

The system will detect and provide early warning of the presence of domestic gas, bottled gas based on methane and explosive vapours such as petrol fumes and other hydrocarbons.

Good Sense

Most inflammable vapour sensors are based on what is known as the 'hot-wire' principle. This involves a small heater element inside the sensor.

The sensor chosen incorporates the usual heater element which is designed to operate at 5V ($\pm 0.2V$). The sensor output is quite simply a varying resistance.

This resistance remains stable whilst the sensor is in clean air but the resistance across the sensor drops when gas or explosive vapour is detected.

The heater element and resistive detector are two ideally independent circuits within the sensor.

HOW IT WORKS

Power enters the circuit via a protective fuse. The specified transformer supplies about 10.5V on the +V rail.

C1, R1 and C2 form a smoothing filter which acts as a safeguard should the unit be powered from an unsmoothed supply. IC1 is a 5V regulator from which the sensor and IC2 are powered. C3 is an additional smoothing capacitor.

LED1 and its series resistor R2 are positioned across the supply rails to provide power-on indication.

The heater element of the sensor is fed directly from the 5V rails. IC2a acts as a voltage comparator biased by resistor R₁ and the sensor itself. R3 and C4 raise the input impedance and also stabilise the op-amp inputs.

When the sensor detects gas its resistance drops below that of R₁ causing the voltage at the inverting input (pin 2) to swing negative which in turn causes the output (pin 1) to go high. The non-inverting input (pin 3) is biased to half the supply potential by R6 and R7 enabling the op-amp to make its comparative decision against the voltage at pin 2.

R10, C5 and R11, D1 form the time delay stage. When gas is detected, pin 1 goes high which will after approxi-

mately 13 seconds take pin 5 high (the non-inverting input of IC2b).

If the gas dissipates within 13 seconds, pin 1 returns low (its normal state). C5 then discharges through R11 and D1. Pin 1 must remain high for the full duration of the 13 seconds before the final alarm is triggered.

Any brief encounter with gas will be shown by the illumination of amber LED2. This is turned on whenever pin 1 goes high via R9 and Q1.

IC2b again serves as a voltage comparator also biased by R6 and R7. If gas is detected for a longer period than 13 seconds the non-inverting input (pin 5) is held high causing the output (pin 7) to also go high. When this happens Q2 and Q3 are also turned on thus switching on the buzzer, red LED3 and reed relay RLA1 via Q3.

The coil of the reed relay also serves as a series resistance for LED3.

Pin 8 and 14 of the relay form a single pole switch. These contacts are normally open and close when the device is triggered.

Push-button SW1 when closed will test the entire circuit. This takes pin 2 low via R4 in the same way that the sensor operates when it has detected a presence of gas.

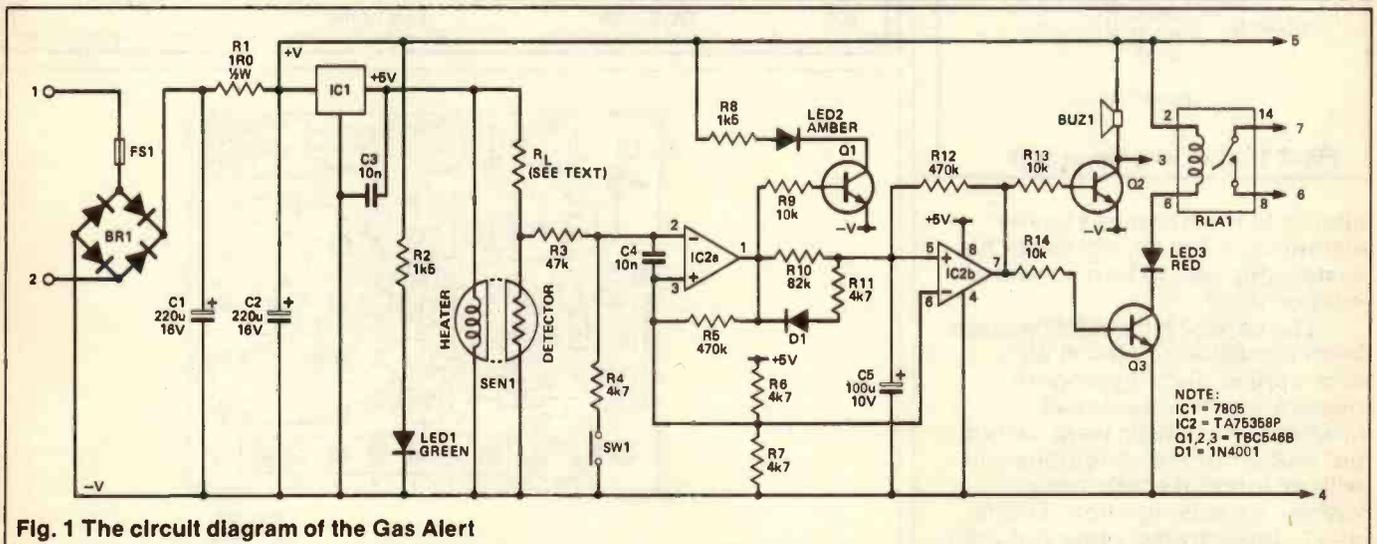


Fig. 1 The circuit diagram of the Gas Alert

As with all hot-wire sensors, respect must be given to current consumption. The heater element in this sensor will draw approximately 170mA when supplied by a 5V regulator. This current drain compares favourably

with other available sensors.

Talking of other devices, use of the 'two dome' sensor/compensator type detector should be avoided. These detectors consume more current and are rendered useless if allowed to

absorb silicone. Gas alarms that are utilised in domestic applications can easily become contaminated with the silicone used in many household spray polishes.

It may seem strange or even

The Sensor

Whilst most of us are more interested in the electrical and environmental characteristics of the sensor, the physical philosophers and philosophically fit will be eager to learn how it works. You will see from Fig. 2 that the heater element passes through a small ceramic tube. This is coated with a layer of tin oxide, SnO_2 .

If tin oxide is heated in a 'clean air' atmosphere, oxygen is absorbed into the surface layer. The rate of absorption remains constant at a given temperature. If, however, a contaminant combustible gas is introduced, this will also be absorbed.

The reaction of a combustible gas with the oxygen causes electrons to be released from the oxygen giving the tin oxide greater electrical conductance. This all takes place between the two electrodes at either end of the ceramic tube. The resultant factor is increased conductivity which is equal to the lowering of its electrical resistance.

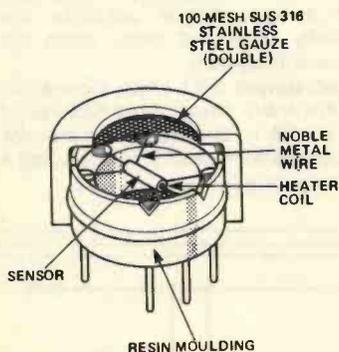


Fig. 2 The hot wire gas sensor

absurd to incorporate a heater element in a gas sensor as such a system appears to be a source of ignition itself.

The sensor type used here has been vigorously tested in an atmosphere of 2:1 hydrogen/oxygen — a very explosive mixture. These tests were carried out under normal conditions and with an internal spark, both without causing ignition. This is due to the extremely fine stainless steel gauze used in the construction of the sensor.

The sensor itself is an internationally proven and accepted device and we stress it cannot itself be a source of ignition. However, careful consideration must be given to the

circuit and system in which it is used.

It's OK for your electric toaster to blow you off the face of the earth but if your gas alarm does the same, it's not on, is it?

It is worth pointing out at this stage that due to relatively high current power consumption it is neither practical nor recommended to operate such a gas detector from dry cell or NiCd batteries.

In our design we have incorporated an independent relay output in the form of a simple single pole make switch. The relay used is of the sealed reed type. This is important as relay contacts create a spark when thrown.

The relay output is included so the detector can be used to trigger existing alarm systems or any external device for that matter.

Some of the more ingenious

readers may decide to develop subtle luxuries such as switching in your extractor fan to help to 'clear the air.'

You may well decide to do this by using the internal reed relay to throw an external mains relay. Mains relays are usually of the open type and will without doubt cause a spark sufficient to ignite a gas filled room. It's recommended that a triac switching circuit be used for switching in any mains powered add-on.

We could also add that the electric motor inside extractor fans will also produce an arc from its commutator brushes but for the moment we'll assume most extractor fans are sufficiently sealed and in any event are normally exposed to clean air on one side.

Having scared the living daylight out of you we will now

PARTS LIST

RESISTORS ($\frac{1}{4}$ W 5% unless specified)

R1	1R0 $\frac{1}{2}$ W
R2, 8	1k5
R3	47k
R4, 6, 7, 11	4k7
R5, 12	470k
R9, 13, 14	10k
R10	82k

CAPACITORS

C1, 2	220 μ 16V radial electrolytic
C3, 4	10n ceramic
C5	100 μ 16V radial electrolytic

SEMICONDUCTORS

IC1	7805
IC2	TA75358P

Q1-3 TBC546B

D1	1N4001
BR1	W02
LED1	Green LED
LED2	Amber LED
LED3	Red LED

MISCELLANEOUS

FS1	500mA, 20mm fuse
RLA1	SPST 12v 1k0 coil DIL reed delay
SEN1	Hot wire gas sensor and matched resistor
SW1	SPST push switch
T1	7V mains transformer
BUZ1	Piezo buzzer
PCB;	7-way terminal block; case; nuts and bolts.

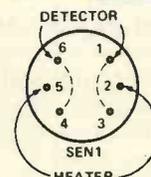
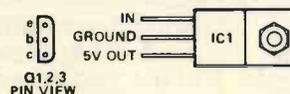
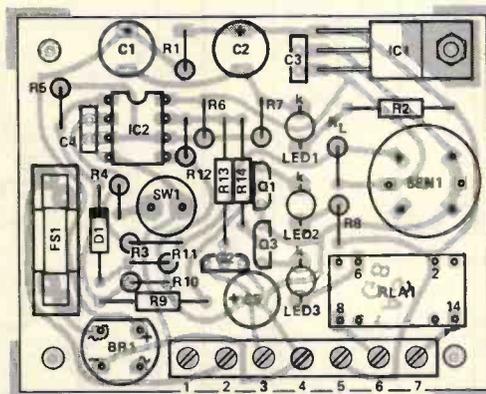


Fig. 3 The component overlay for the Gas Alert

tell you that the alarm will function well before an explosive mixture is allowed to accumulate.

The point at which a mixture of air and explosive vapour or gas will ignite is known as its lower explosive limit (LEL). Such mixtures are defined in parts per million (PPM).

This is the molecular count of explosive mixture per one million molecules of air. The LEL is dependent on the PPM — got it!

Our gas alarm system will trigger when an atmosphere of between 10% and 40% LEL has been reached. This may seem a rather large tolerance window but it includes all explosive atmospheres — methane (natural gas), butane, propane and so on, and other vapours (petrol, methanol, ethanol, propanol Navy Rum, etc).

Alarmingly Falsified

The time honoured expression 'false alarm' is a day-to-day saga in the majority of warning and detection devices of all types. Sophisticated electronic devices incorporating failsafe and fail failsafe are normally so safe that they fail to register anything or they are continually being triggered by just about everything except the gas they were designed for.

It's not a bit of good having a gas detection system triggered off by a quick squirt of hair spray or cooking deposits in the air. It's just switched off when everybody is so fed up of grabbing their wallets and purses and running out into the street and going four or five doors down the road to use someone's phone (next door is too near, they'll go up as well).

Now Hear This

The British Standards Institute is in the process of receiving (this is confidential you understand) a draft proposal from British Gas in respect of domestic gas alarms. Although the document will delve into meticulous detail of test procedures involving gas concentrations, temperature and air pressure, notwithstanding wind velocity, it would appear that some of the more important factors have been overlooked.

The whole purpose of an alarm is to let someone know something is happening. Quite sensibly, the Standard has opted for an audible alarm which it stressed must have a sound level output of 85dB at 3m. Having delved into the depths



of Einstein's archives to create test procedures it omits to specify the frequency of the sound the audible alarm should generate!

Well, British Gas, have you ever heard 85dB at 25kHz? No, that's not surprising because neither has anyone else on this planet. 25kHz is all very well for dogs, they'll be saved!

It may well be that if you buy a gas alarm that has been manufactured to British Standards, your first indication of an imminent explosion is the dog going berserk or your mynah bird flat on its back in the cage pushing up the daisies.

About 400-700Hz would be more suited. However even at a desired frequency, 85dB is certainly not over loud. In an average house you may have an alarm installed in your kitchen. If the kitchen door is closed, your bedroom door is closed, it's the middle of the night and you're asleep, it is open to interpretation as to whether you would hear an alarm operating at this sound pressure level.

The ETI system has an internal buzzer rated at 75dB at 1m but serious provision has been made for external louder audible sounders positioned wherever required. This is of particular importance in larger houses.

Sensors

In the near future British Gas may invite you (at your own cost, of course) to have a gas detection



device fitting in your kitchen. That's fine if you get a gas leak in your kitchen but what about the gas meter under the stairs, the gas fire in the lounge, the central heating boiler in the garage or what have you.

In the light of that, consideration should be given to the installation of more than one sensor in order to provide comprehensive cover.

The ETI gas alert is designed to operate from an AC or DC supply producing 12V. Up to now we have dealt with practical considerations for domestic installations and for this purpose a

240V mains transformer is used.

Boats and (more so) caravans are also prone to gas leaks from faulty low pressure bottled gas (LPG) systems.

This system can be powered from standard 12V lead-acid car batteries — the normal source of power for boats and caravans. The current consumption of around 200mA under normal working conditions, would not be considered a serious drain on such battery systems.

The consumption of the unit rises above 200mA when the alarm is triggered but the last thing you are going to worry about is a flat battery if you're about to spontaneously combust!

The Circuit

As previously mentioned, false alarms are not acceptable in any gas alarm system. The sensor supplied for this project requires no setting-up or calibration. Each individual sensor has been calibrated prior to leaving the manufacturer's factory.

During the manufacture of a complex device such as this component, material tolerances are unavoidable. The inclusion of a resistor (R_L) which is supplied with the sensor enables the device to operate within the prescribed parameters.

If you are assembling more than one detector, care must be taken to ensure each sensor and its companion resistor do not get mixed-up.

As a precaution it is worthwhile measuring the resistance of the resistor supplied and writing its value on the side of the sensor with a fine permanent marker. You will need to use an accurate digital meter if you choose to do this.

IC1 acts as two voltage comparators. As with the rest of the components, a good quality op-amp is chosen — the Toshiba TA75358. In fact this is a dual op-amp in an 8-pin DIL package — an LM358. It features distinct advantages in a circuit of this type.

It is specifically designed to operate on single supply rails, has very low current consumption and its output will swing fully low.

Whilst on the subject of Toshiba, the TBC546B transistors were chosen, again being a quality device and are equivalent to BC546. All right Tosh!

Construction

Assembling the Gas Alert should provide no particular


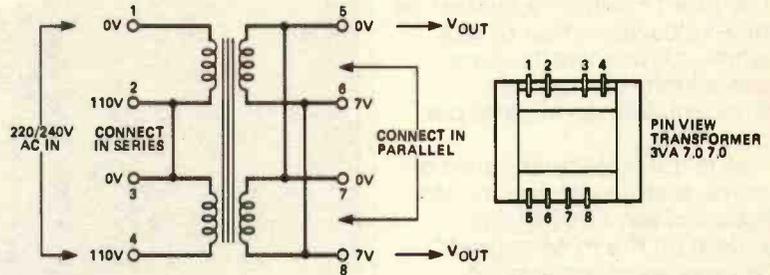


Fig. 4 The 7-0, 7-0 transformer supplied in the Live Audio Systems kit is specifically designed to power the hot wire sensor. For UK mains it must be wired up as shown

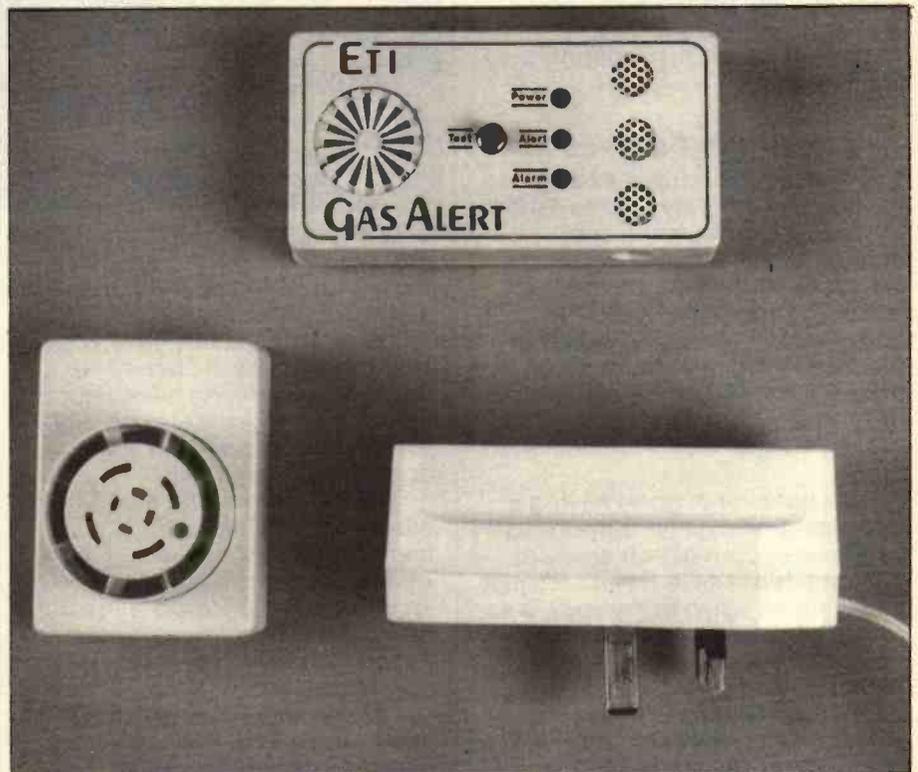

The Live Audio Systems Caravan/Boat Gas Alert along with mains transformer and external siren modules.

problems, particularly if the recommended PCB (Fig. 3) is used.

In the recommended case, the component leads should be trimmed close to the board underside to enable the backpanel to be fitted.

The LEDs should be soldered in first with 8mm sleeves over the leads so that they stand proud of the board at the correct height to protrude through the case top.

The test button should be soldered in next. It must be positioned exactly vertical and with careful comparison to the height of the LEDs, again for correct positioning. Although it is

a little awkward to have this test button protruding throughout construction, it must be fitted at this stage since the amount of heat required might damage more delicate components. The nut on the test button is unused and the pins need trimming off.

The voltage regulator IC1 is bolted flat to the board with its pins at right angles. A small heatsink may be placed on top (held in place by the bolt) but this is not imperative.

The fuseholders should be installed with the fuses in place. Solder in the tags and trim. Fit the bridge rectifier and check its polarity.




The Caravan/Boat Alert.



The mains transformer module.



The External 85dB siren.

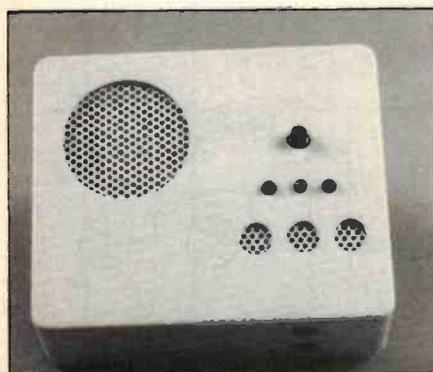

The House Alert.

The transistors and ICs can now be fitted, again with attention to their orientation. Solder the relay into place, treating it like an IC. If the relay is not required, insert a 1K0 resistor between pinholes 2 and 6 to load LED3.

The transformer may be mounted with an additional fuse (500mA) in the mains live input if desired. Rectification and smoothing are performed on the PCB. The transformer can either be mounted in a plug-topped box or in the complete unit with the alarm sounder.

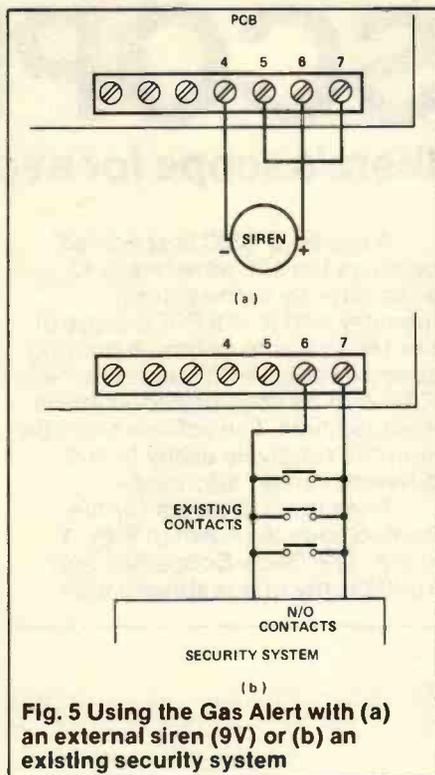


Fig. 5 Using the Gas Alert with (a) an external siren (9V) or (b) an existing security system

Note that the sensor is a rugged 6-pin device which requires no special handling precautions. However, a device such as this should be treated with respect. Neither the heater element nor the internal detector are polarised — they have no positive or negative supply requirement.

The pinout configuration ensures it cannot be inserted into the PCB incorrectly (there are two possible ways and either will do). You will see from the pinout that pins 1 and 3 of the sensor are connected internally, as are 6 and 4. So, pin 1 or 3 and pin 6 or 4 are the sensor's resistive detector. Pin 2 and 5 supply the heater element.

Testing

The unit can be tested by pressing a cigarette lighter over the sensor for about 15 seconds (don't light it unless you want to melt your PCB). The 'Alert' LED (LED 2) should light almost immediately and the alarm should sound after about 20 seconds.

If this doesn't happen (and the supply voltages are known to be operational) then check polarity of components, terminal numbers on the transformer and look for soldering errors.

Installation

Some thought should be given to siting the Gas Alert module or modules. Try to place them near likely sources of leaks — the kitchen, gas meter, gas fires and

so on.

If used for detecting LPG bottle gas, (butane, propane and so on) the sensor should be 6-12in from the floor (LPGs are heavier than air). For domestic or other natural gas, the sensor must be about 12in from the ceiling as these gases are lighter than air.

The placing of the extension siren (if used) will depend on your habits! Don't put it under the stairs with the gas meter — unless you're in the habit of sleeping there.

For use in caravans, I recommend the module with sensor and 75dB sounder in a single box which simply connects to the caravan's 12V DC supply. Similarly for boats, where the unit could be installed in bilges or engine compartments to detect excess fuel vapours.

It is possible to mount the sensor away from the PCB (a case is available to do this — see Buylines). In this case resistor R_L should be wired across the sensor (to maintain the resistive calibration) not into the PCB. This separate unit can then be connected to the PCB using lightweight 3-core cable (do not use screening as one of the cores).

A louder extension siren can also be fitted, powered via the reed relay contacts. A suitable 85dB siren module is available (see Buylines).

ETI

BUYLINES

Although many of the parts used for the Gas Alert are available from usual suppliers, some components are specific to this project. These can be ordered from Live Audio Systems, Unit 52, Tafarnaubach Industrial Estate, Tredegar, Gwent NP2 3AA.

The gas sensor and matching R_L resistor cost £10.95, the mains transformer £2.25 and the PCB £2.25.

A kit of the PCB, sensor and other PCB-mounting components costs £19.95.

A complete kit of the PCB, components, buzzer and screen printed case suitable for 12V caravan or boat use costs £25.75. The small extension sensor case costs £2.95. A box for the transformer incorporating a built-in mains plug is available for £2.75. The extension siren module on its own costs £4.50.

A larger kit including the PCB, components, transformer, siren and a box suitable for mains operation is available for £32.85.

All prices include VAT. Please add 50p per order for postage.

Please address all orders to Live Audio Systems. Enquiries can be answered on (0495) 717462 from 3.00 to 5.00pm.

BEEB-SCOPE

Richard Penney finds there's scope for a scope on his BBC micro

Oscilloscopes are an expensive piece of test gear for the electronics hobbyist. Flashy glowing knob-filled units can have pricetags stretching into the thousands and even the cheapest are well out of birthday present range.

This project is a low-frequency four-channel oscilloscope which is basically a fast analogue to digital converter that adds onto your BBC micro using the 1MHz bus.

A model B BBC is specified because the software needs to poke directly to the screen memory and to the FRED page of the 1MHz bus to optimise running speed. Models with shadow screen RAM can be used provided this is disabled first. The software can be adapted relatively easily to suit different screen addresses.

The circuit diagram for the Beeb-Scope is shown in Figs. 1 and 2. The Beeb-Scope has four inputs (only one is shown) with

input resistance switchable up to 1M Ω on DC coupling. On AC coupling a 1 μ 0 capacitor C1 is placed in series with this (such a large capacitor ensures there is minimal additional attenuation and phase-shift even at low frequencies).

The four inputs have range switches to select one of nine full-scale input voltage ranges — 0.5V, 1V, 2V, 5V, 10V, 20V, 50V, 100V and 'infinite.' On AC coupling these refer to the peak levels not

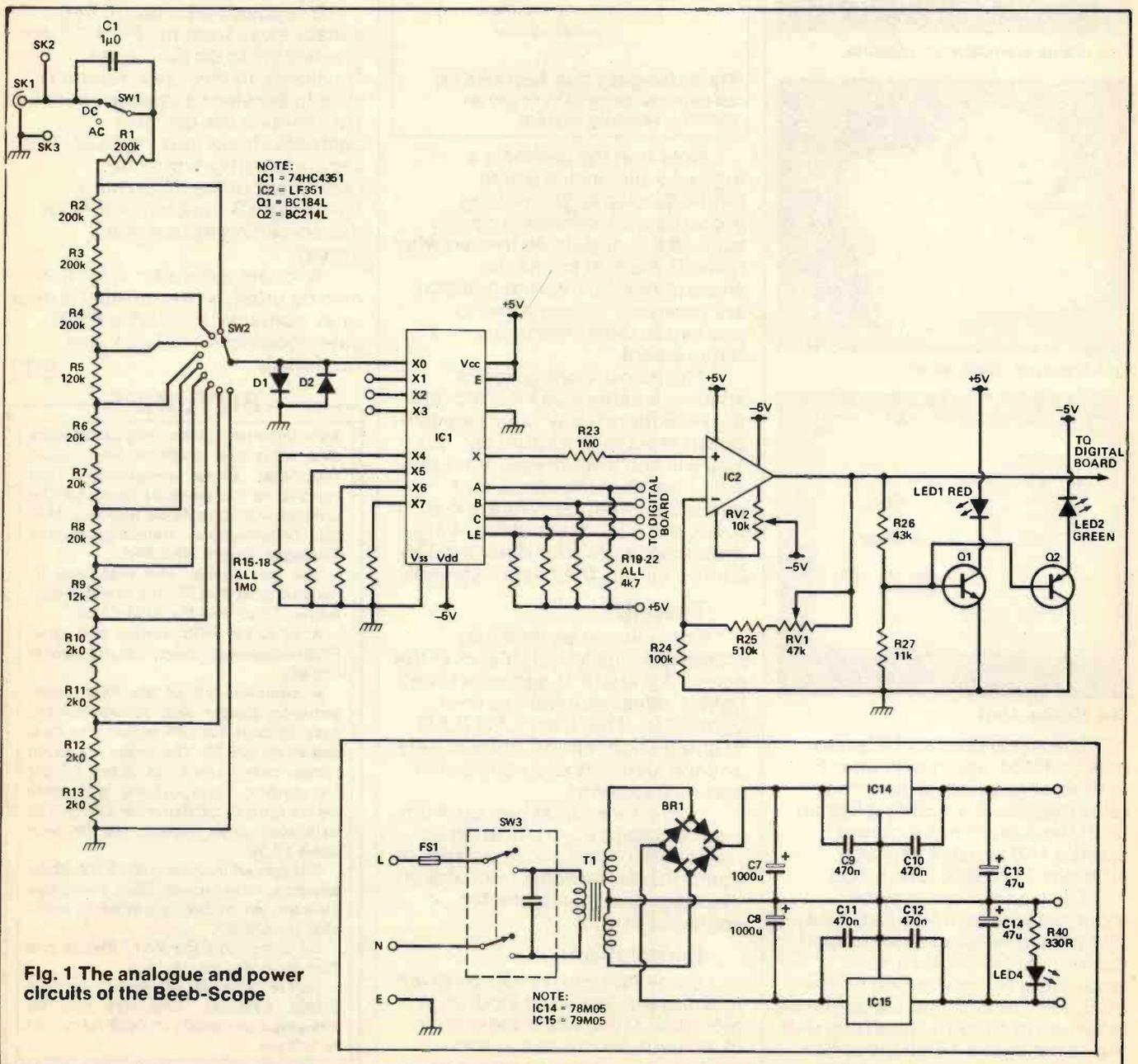


Fig. 1 The analogue and power circuits of the Beeb-Scope

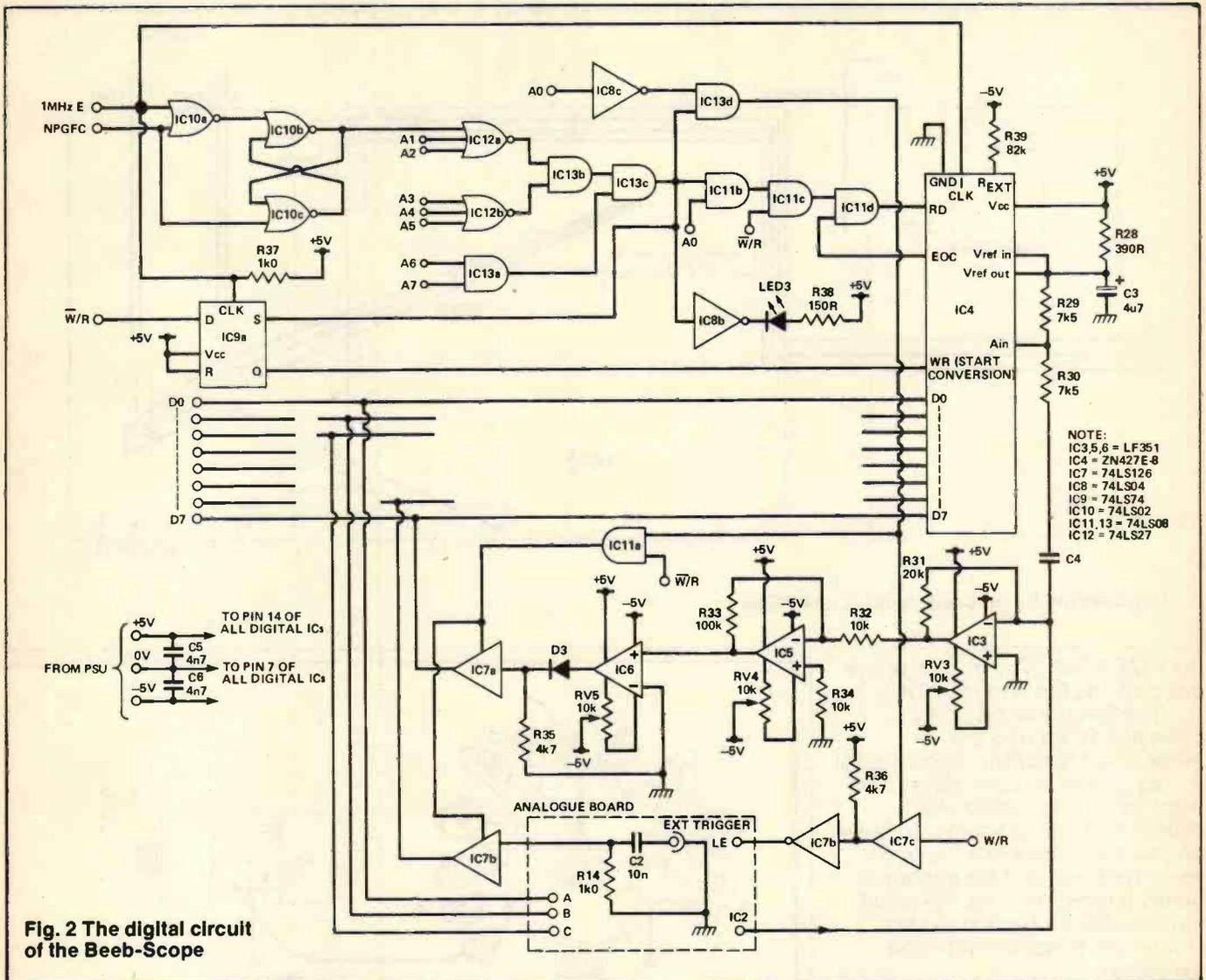


Fig. 2 The digital circuit of the Beeb-Scope

HOW IT WORKS

The circuit diagrams are shown in Figs. 2 and 3. For an explanation of the circuit we shall concentrate on channel one of the unit.

Inputs come (directly or via a capacitor) from BNC socket (SK1) or terminal post (SK2, 3) to an input attenuator consisting of resistor chain R1-R13 tapped at various points by a rotary switch SW2.

This switch determines the input sensitivity and couples the input to analogue switch IC1 which provides channel switching under software control. The selected channel signal is amplified by a factor of 6.375 by IC2, thus boosting the input FSD (from the attenuator) of 400mV to 2.55V (suitable for the ADC chip on the digital board).

The gain is slightly variable (by RV1) to allow maximum accuracy to be obtained. Even uncalibrated. However, the unit is adequately accurate for most uses.

Overload indicators LED1, LED2 are driven from the output via a potential divider and two transistors. The first

starts glowing for inputs above 80% FSD and one each is provided for positive and negative levels in excess of FSD.

The amplified signal now goes to the digital board where it feeds the analogue to digital converter (IC4). An operational differentiator is used to derive a rising-edge pulse.

Most of the ICs on the digital board are concerned with decoding the signals available on the 1MHz bus to ensure access to the device only on receipt of the correct addresses from the computer.

The data-bus is connected directly to IC4, as this has tri-state outputs. A simple potential divider is used to ensure that inputs in the range $\pm 2.55V$ are fed to IC4 as 0 to 2.55V. The data bus is also connected (via various buffers) to the rising-edge and external trigger signals and to the channel-select pins of IC1 on the analogue board.

The external trigger input is simply a TTL input configured in a 'monostable'

arrangement. An 'in-use' indicator is driven by this board, which lights when the board is being accessed by the computer.

The device is memory mapped to the BBC micro's 1MHz bus as shown in Table 1.

The power-supply is a simple unit using a PCB-mounting mains transformer and standard 78M05 and 79M05 voltage regulators to fulfil the $\pm 5V$ power requirements of all the electronics.

&FCC0 Write: Channel selection (0-7) start conversion (9 μ s)

Read: Bit 6=External trigger pulse
 Bit 7=Rising edge pulse (high=rising edge)

&FCC1 Write: start conversion (9 μ s)
 Read: Read digital voltage level

Table 1 Addresses used by the Beeb-Scope

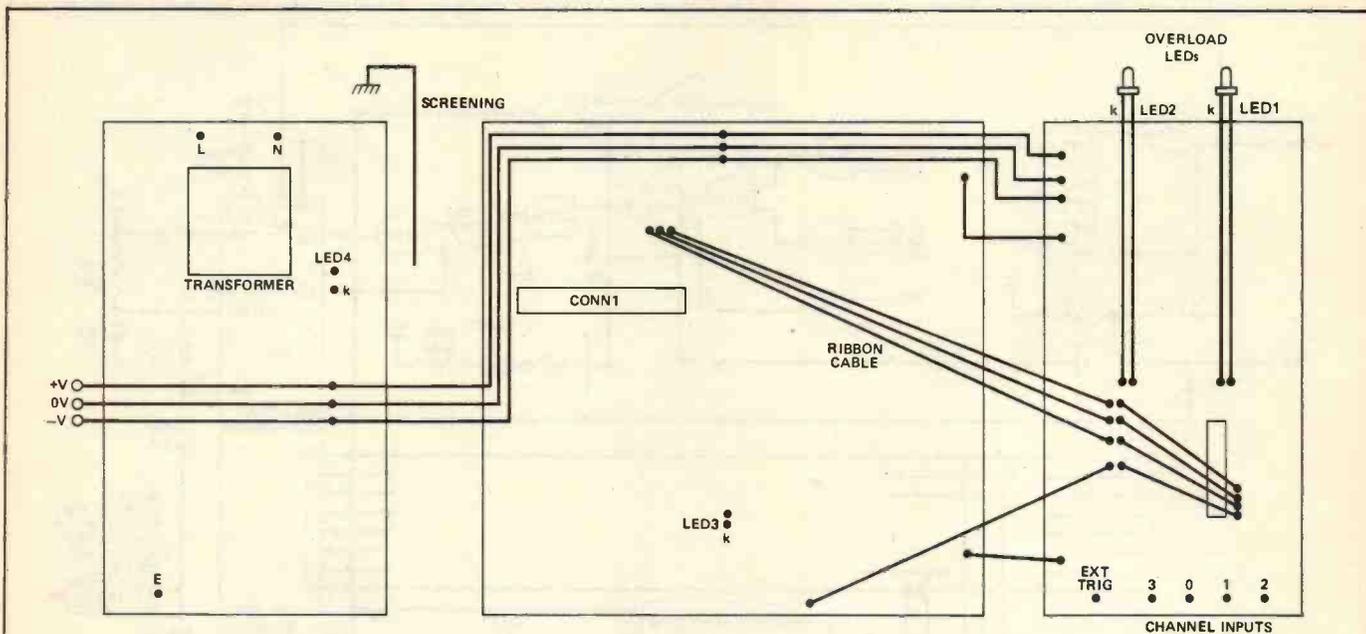


Fig. 3 Wiring for input attenuators and PCBs

the RMS levels. The infinite range grounds the input to the ADC.

The levels can be easily changed by altering the attenuation resistors. If you decide to do so, bear in mind that at FSD the attenuators should yield 400mV and that keeping a suitably large resistor between the most sensitive input and the analogue board is sensible. This will avoid blowing the protection diodes should the maximum input be exceeded.



Calculating the resistor values is simply a matter of applying potential divider theory to the situation. Start with the least sensitive input and work up the resistor ladder.

Each input is protected by two 1N4148 diodes in inverse parallel.

Both the analogue switch (IC1) and ADC (IC4) are fairly tolerant of excessive inputs but the diodes provide a simple and effective way of avoiding damage, keeping inputs to the switch between $\pm 0.65V$. These diodes also protect the analogue switch, which is a CMOS device, against static charges when a particular channel is unused.

The primary purpose of the analogue switch is to alleviate the need for swapping over input leads when monitoring various signals and not to provide a full-blown dual (or rather quadruple) trace display.

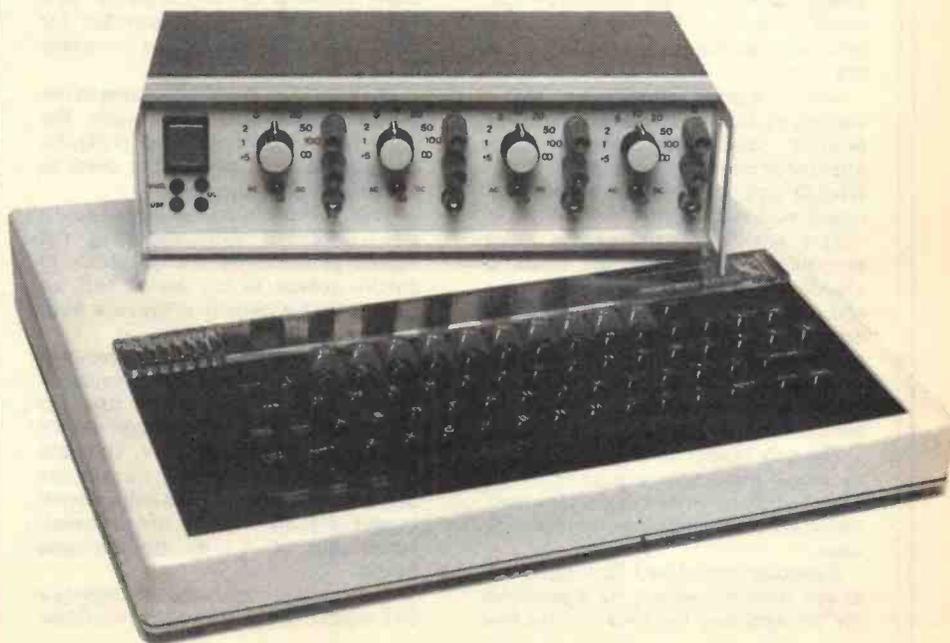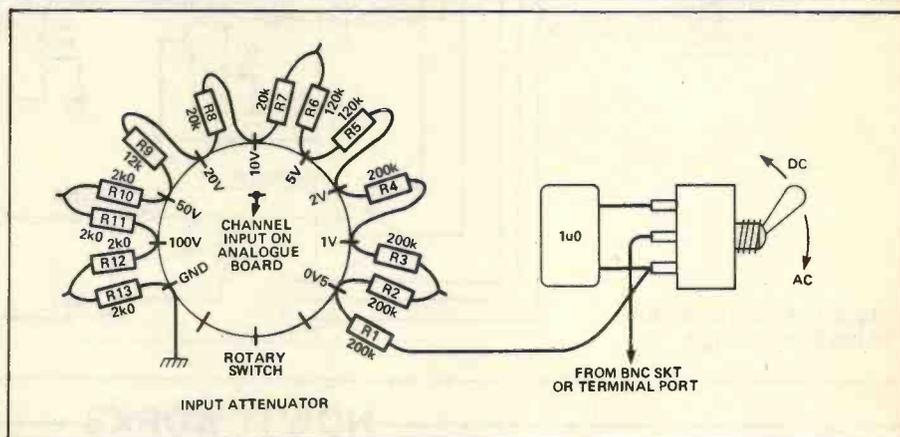
A multi-trace display is only practical for low frequencies (under 500Hz) since if the switch is 'flicked' too rapidly, a meaningless



```

10 MODE4:VDU23;B202;0;0;0;
20 DIM acX 4095
30 var=678;zp=670;par=&B0
40 FOR AX=0 TO 2 STEP2:PX=acX;[OPT AX
50 .scope
60 LDA#255:STA&6BC7
70 LDA#0:STApr+0 \ channel
80 LDA#1:STApr+1 \ sampling speed
90 LDA#0:STApr+2 \ expand
100 LDA#0:STApr+3 \ fast sampling
110 LDA#127:STApr+5 \ trigger level
120 LDA#0:STApr+7 \ param. under c
ursor
130 LDA#4:LDX#1;JBR&FFF4;JBRpcurs:BEI
140 .scplp:LDXpar:LDApar+3;BEQslow;JBR
f&ampamp;JMPslow+3;.slow;JBR&ampamp;:JBR&expa
nd;JBRplot;JBR&par&:JMPscplp
150 .plot
160 LDA#128:STAvr:LDA#0:STAvr+1:STAv
ar+2:LDX#0
170 .pllp:LDAold,X;JBRplotp:LDAdata,X
:CLC:ADCpar+7:STAold,X;JBRplotp
180 INX:LBRvar;BCCpllp:LDA#128:STAvr
LDAvar+1:CLC:ADC#8:STAvr+1:LDAvar+2:ADC
#0:STAvr+2:CPX#0;BNEpllp:RTS
190 .plotp:STApr:LDA#0:STApr+1:ABLzp:R
DLzp+1:LDAzp:CLC:ADC#0:MOD256:STApr:L
DAzp+1:ADC#0:DIV256:STApr+1:LDY#0:LDA
(zp),Y:STApr+2:INX:LDA(zp),Y:STApr+3
200 LDAzp+2:CLC:ADCvar+1:STApr+2:LDAzp
+3:ADCvar+2:STApr+3:DEY:LDAvar:EOR(zp+2)
,Y:RTS
210 .expand:LDApar+2;BNE&xtok:RTS;.ex
ptok:STApr+7;.exptlp2:LDX#127:LDY#254;.e
xptlp:LDAdata,X;STAdata,Y;DEY:DEY:DEX;BN
Exptlp
220 LDX#0;.exptlp:LDAdata,X;CLC:ADCda
ta+2,X;RORA:STAdata+1,X;INX;INX;CPX#254;
BNE&xtlp:DECap+7;BNE&xtlp2:RTS
230 .sample:STX&FCC0;JBRwft:LDY#0
240 .samlp:LDA&FCC1:ST&FCC1:STAdata,Y
:LDXpar+1;.samlp:DEX;BNE&samlp:INX;BNE&
&samlp:RTS
250 .fsamp:STX&FCC0;JBRwft:LDY#0
260 .f&samlp:LDA&FCC1:ST&FCC1:STAdata,Y
:NOP:NOP;INX;BNE&samlp:RTS \ main loop=22
c s =90kHz
270 LDA#FE4D:AND#1;BNE&trig
280 .wft:LDY#0:STY&FCC1
290 .wft:LDA#E4;.wft:LDA&FCC0:NOP:NOP;
BPLwft:NOP:NOP:NOP;DEX;BNE&wft1
300 LDA&FCC1:ST&FCC1;SEC:8BCpar+5;CMP
#2;BCC&trig;CMP#255;BCB&trig;DEY;BNE&wft
310 .&trig:LDA#204:STX&E48:RTS
320 .&trig:LDA#0:STX&E48:RTS
330 .param
340 LDX#198;JBRkey:BPL&trd;JBR&rup
350 .&trd:LDX#214;JBRkey:BPL&tr1;JBR&rdn
360 .&tr1:LDX#230;JBRkey:BPL&trr;JBR&lt
370 .&trr:LDX#134;JBRkey:BPL&trm;JBR&mt
380 .&trm:LDApar+8;BEQ&paramout:LDX#0:LD
Y#80;.del:DEX;BNE&del:DEY;BNE&del;BEQ&par
am;.&paramout:BEI:RTS
390 .key:LDA#129:LDY#255;JBR&FFF4;TYA:
RTS
400 .pcurs:LDAvar+7;EOR#31:STApr:LDA#0
:STApr+1:LDX#4;.pcip:ABLzp:ROLzp+1;DEX;B
NE&pcip
410 LDAzp:CLC:ADC#0:MOD256:STApr:LD
Apr+1:ADC#0:DIV256:STApr+1:LDY#0
420 LDA(zp),Y;CLC:ADC#1:STApr+2:INX;LD
A(zp),Y:ADC#1:STApr+3:DEY
430 LDY#55;.pcip:LDA(zp+2),Y;EOR#255;
STA(zp+2),Y;DEY:BPL&pcip:RTS
440 .mup:LDAvar+7;BNE&upok:RTS;.mupok;
JBR&pcurs;DECvar+7;JMP&pcurs
450 .mdn:LDAvar+7;CMP#3;BNE&dnok:RTS;.
mdnok;JBR&pcurs;INCvar+7;JMP&pcurs
460 .mlt:LDYvar+7:LDApar,Y;CMP#inp,Y;B
NE&mtok:RTS;.mltok;SEC;BCC#1:STApr,Y;JM
PCope
470 .mrt:LDYvar+7:LDApar,Y;CMP#maxp,Y;B
NE&rtok:RTS;.mrtok;CLC:ADC#1:STApr,Y;JM
PCope
480 .pchar;SEC;BCC#32;BPL&chok:RTS;.pc
hok;STApr+4:LDA#0:STApr+5:LDX#3;.pchlp:LA
BLzp+4:ROLzp+5;DEX;BNE&pchlp:LDAzp+5;CLC;
ADC#0:STApr+5
490 LDY#7;.pchlp:LDA(zp+4),Y:STA(zp+2)
,Y;DEY:BPL&pchlp:LDAzp+2:CLC:ADC#8:STAz
p+2:LDAzp+3:ADC#0:STApr+3:RTS
500
510 .cops:LDAvar+7;ABL:CLC:ADCvar+7:A
DC#set MOD256:STApr:LDA#set DIV256:ADC#0
:STApr+1;JMP(zp)!.set
520 JMP&char;JMP&mbas;JMP&xtok;JMP&sta
530 .chan;JBR&stupos:LDApar:CLC:ADC#48
:JBR&pchar;JMP&pcurs
540 .&mbas;JBR&pcurs:LDApar+1;DEX;STXz
p:LDA#0:STApr+1:LDX#2;.tblp:ABLzp:ROLzp+
1;DEX;BNE&tblp:LDApar+1;DEX;TXA;CLC:ADCz
p:STApr:LDAzp+1:ADC#0:STApr+1:LDAzp:CLC:A
DC#25:STApr:LDAzp+1:ADC#0:STApr+1
550 LDA#200:STApr+6;JBR&dec:LDA#20:STAz
p+6;JBR&dec:LDA#2:STApr+6;JBR&dec
560 LDAzp+2:CLC:ADC#8:STApr+2:LDAzp+3;
ADC#0:STApr+3:LDAzp+1:AND#1;BEQ&tbok:LDA#53
:JBR&pchar;JMP&tbok;.tbok:LDA#48;JBR&pchar
;.tbok;JMP&pcurs
570 .expt;JBR&stupos:LDApar+2:CLC:ADC#
48;JBR&pchar;JMP&pcurs
580 .fst;JBR&stupos:LDA#ABC#N;LDXpar
+3;BEQ&fstok:LDA#ABC#Y;.fstok;JBR&pchar;J
MP&pcurs
590 .stupos;JBR&pcurs:LDAzp+2:CLC:ADC#
48:STApr+2:LDAzp+3:ADC#0:STApr+3:RTS
600 .dec:LDX#0;.declp:LDAzp+1;BNE&decok
:LDAzp:CMPzp+6;BCC&decok;.decok:LDAzp;BE
C;BCCzp+6:STApr:LDAzp+1;BCC#0:STApr+1;IN
X;BNE&decip;.decok;1;TXA;CLC:ADC#48;JMP&pc
hok
610 .minp;J;:PX=&00000100;PX=PX+4;[OPT
AX
620 .maxp;J;:PX=&0104FF07;PX=PX+4;[OPT
AX

```

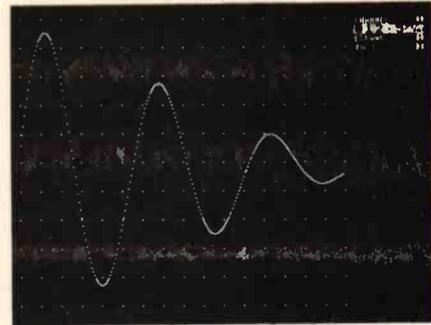

```

630 .data;J;FOR BX=0 TO 252 STEP4:BX:P
X=0;NEXT;PX=PX+256;[OPT AX
640 .old;J;FOR BX=0 TO 252 STEP4:BX:P
X=&B0808080;NEXT;PX=PX+256;[OPT AX
650 .ypos;J;PX=PX+512;[OPT AX
660 J;NEXT
670 REM This calculates the screen add
resses for each possible Y position
680 FOR CX=0 TO 31:AX=&5800+(31-CX)*#1
40;FOR YX=0 TO 7:BX=AX+(7-YX);?;(ypos+(CX
*16)+YX*8)=BX AND 255;?(ypos+(CX*16)+YX*
2+1)*#X DIV256;NEXT;
690 GCOL0,1;FOR YX=0 TO 128 STEP (128/
5);FOR XX=0 TO 256 STEP (256/16);PLOT 69
,XX*4,512+(YX*4);PLOT69,XX*4,512-(YX*4);
NEXT;
700 GCOL3,1;MOVE0,512;PLOT1,1020,0
710 RESTORE740;FOR AX=&5908 TO &5CC8 8
TEP &140;FOR BX=0 TO 52 STEP4;READ !(AX+
BX);NEXT;
720 &maxp=3;REM this should be set to
the highest channel number
730 CALLscope
740 DATA &45552500,&25554547,&57552500
,&55555577,&74545700,&57545476,&40404000
,&70404040,&0,&0,&0,&0,&7E6E663C,&3C6676
\ channel
750 DATA &7E6E663C,&3C6676,&18183818,&
7E1818,&8066663C,&7E3018,&18000000,&18,&6
7C607E,&3C6606,&44&25452,&10181,&2804020
,&29A&BS \ time base
760 DATA &2457500,&754545,&55556200,&
454567,&75555600,&565375,&0,&0,&0,&0,&44
000000,&44281028,&7E6E663C,&3C6676
expand
770 DATA &32223900,&222223,&91A11800,&
B18989,&8800,&0,&0,&0,&0,&0,&0,&0,&0,&7E766
666,&66666E \ fast

```

Listing 1 The BBC Basic/assembly program to operate the Beeb-Scope

output is obtained. The longer the delay between switching and sampling, the more this effect is avoided.

Once locked onto one channel the user is totally oblivious to this effect. The switching effect does not limit the device's use as a low-cost multichannel voltmeter.

The circuit as it stands does not have a sample-and-hold module and the prototype functions perfectly normally without it. The trace is smooth,

even when approaching the highest displayable frequency.

Construction

The prototype was built with four input attenuators although the analogue switch and software can cope with up to eight. To keep costs to a minimum, just one or two could be used.

The components used only in additional inputs (beyond the one illustrated in Fig. 1) have prefixes 100, 200 and 300, so omit some or

all of these if you are using less than four channels.

More inputs can be added by replacing each of the 1M0 pull-down resistors R15-R18 (which represent channels 4, 6, 7 and 5 respectively) with further attenuators and protection diodes.


The Tedious Bit

Construction should be started with the input attenuators, made by soldering resistors directly to the tags of the rotary switches as shown in the wiring diagram (Fig. 3).

This is a tedious task (increasingly so with larger numbers of channels) but care should be taken to avoid errors which can be difficult to correct. Remember to set the stop on the rotary switch to allow nine positions.

Fun Bit

Assembly of the PCBs is quite straightforward. The power supply

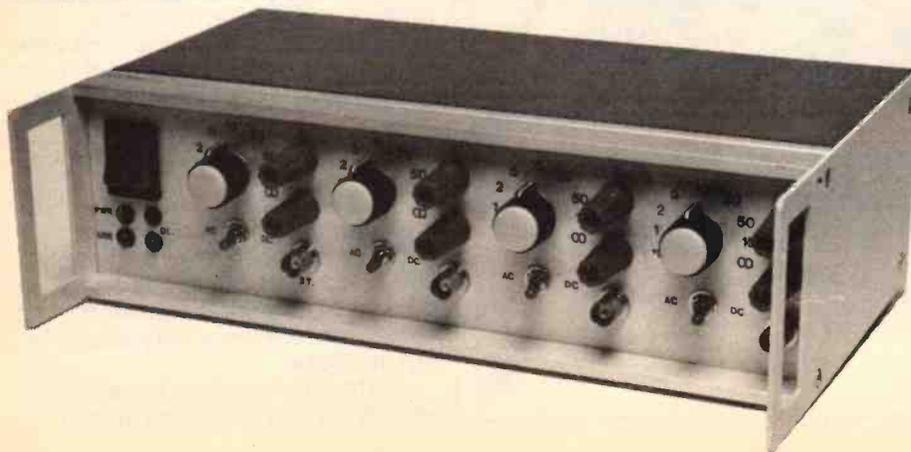


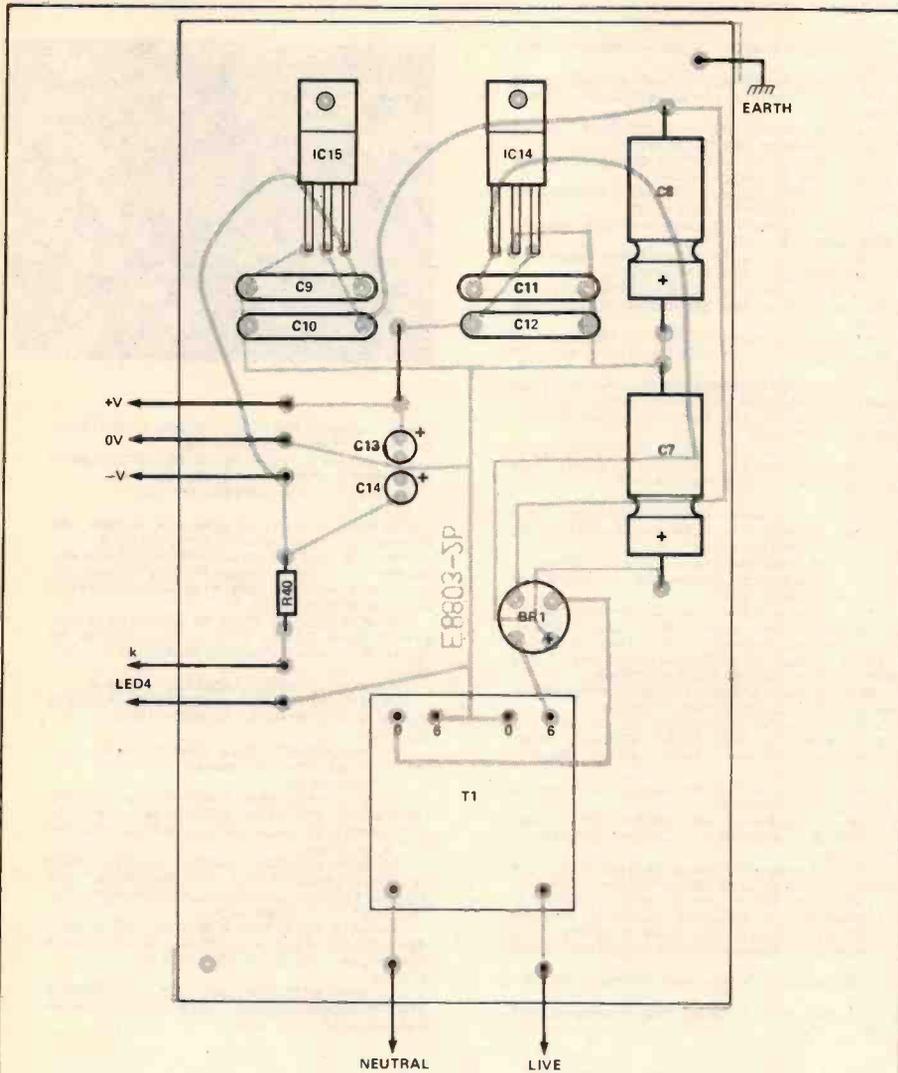


Fig. 4 The component overlay for the power supply board

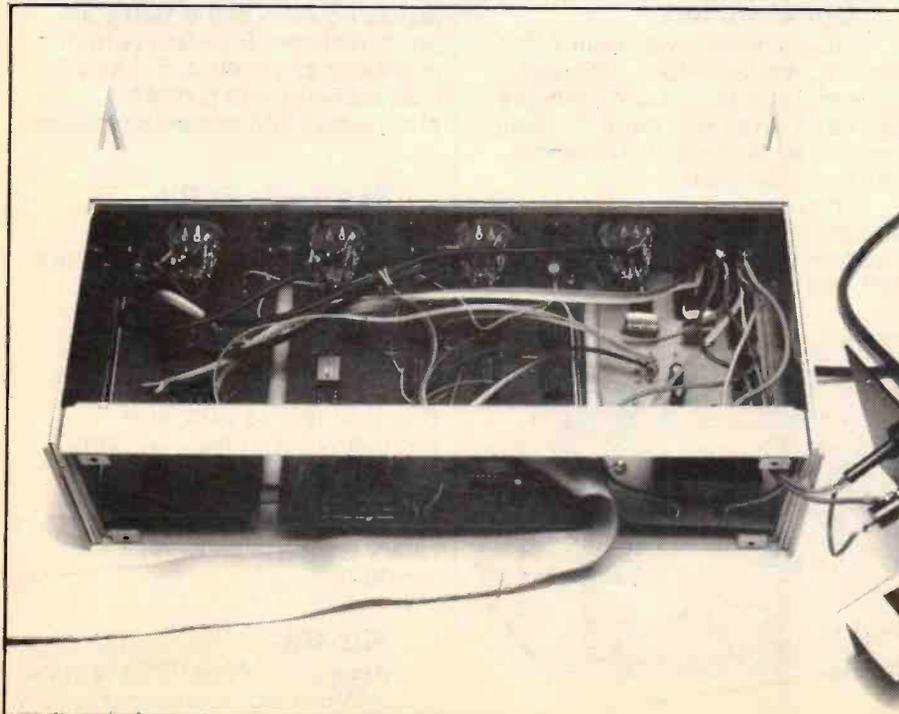

board is probably the best to start on. (Fig. 4).

Assembly order here is not critical. However, it is wise not to insert the transformer until last. Bend the regulators so they lie flat against the board, to make them less vulnerable. This unit should be tested, to ensure the +5V and -5V supply rails are at the correct voltage.

Connect up a temporary (though not slipshod) mains supply. Care should be exercised, as 240V mains will be present on the underside of the transformer.

If all is well, the analogue board should be assembled next (Fig. 5). Again, assembly order is not critical as there is plenty of space on the board. Care should be taken when handling IC1 which is a CMOS device. This should be the last device to be inserted and an IC socket is essential.

The board can be partially tested at this stage by applying power and attaching a suitable signal (a signal-generator is by no means essential — a tape recorder is quite sufficient) to R23 and checking that this appears amplified at the output of the board and that the overload indicators light when they should do.

Lastly the digital board may be tackled (Fig. 6). Start with resistors, capacitors and diode, then insert the IC sockets, presets, links and finally the ICs themselves.

There are a number of links, including some on the underside of the board. There are five pairs of points which must be linked by insulated lengths of wire on the underside of the board. These are shown on the overlay as bracketed numbers. Link (i) to (i), (ii) to (ii) and so forth.

An extensive system of flying links is used above the board to carry power to the IC's. Wires are simply soldered at one end in the holes in the PCB and at the other to the bus-bars formed from tinned copper wire at the top of the board. Use suitably coloured wires to help avoid (possibly expensive) errors.

Testing

It is prudent to make a thorough check of this board before soldering in the IDC cable and to do all possible checking now, as errors are far easier to correct before the whole device is put in a case.

After preliminary checking, link up the power-supply lines to

PROJECT: Beeb-Scope

PARTS LIST

RESISTORS (all 1/4W 5%)

R1-4, 101-104,	
201-204, 301-304	200k
R5, 105, 205, 305	120k
R6-8, 31, 106-108,	
206-208, 306-308	20k
R9, 109, 209, 309	12k
R10-13, 110-113,	
210-213, 310-313	2k Ω
R14, 37	1k Ω
R15-18, 23	1M Ω
R19-22, 35, 36	4k Ω
R24, 33	100k
R25	510k
R26	43k
R27	11k
R28	390R
R29, 30	7k Ω
R32, 34	10k
R38	150R
R39	82k
R40	330R
RV1	47k
RV2-5	10k

CAPACITORS

C1, 101, 201, 301	1 μ 0 polyester
-------------------	---------------------

C2	10n ceramic
C3	4 μ 7 16V radial electrolytic
C4	100p ceramic
C5, 6	4n7 ceramic
C7, 8	1000 μ 16V axial electrolytic
C9, 10, 11, 12	470n polyester
C13, 14	47 μ 25V radial electrolytic

SEMICONDUCTORS

IC1	74HC4351
IC2, 3, 5, 6	LF351
IC4	ZN427E-8
IC7	74LS126
IC8	74LS04
IC9	74LS74
IC10	74LS02
IC11, 13	74LS08
IC12	74LS27
IC14	78M05
IC15	79M05
Q1	BC184L
Q2	BC214L
D1, 2, 3, 101, 102,	
201, 202, 301, 302	1N4148
BR1	WO1

LED1, 4	Red LED
LED2	Green LED
LED3	Yellow LED

MISCELLANEOUS

CON1	34-way IDC PCB header, 34-way IDC socket
	34-way ribbon cable
FS1	80mA anti-surge fuse
SK1 4, 101, 201	BNC 50R socket
SK2, 102, 202, 302	Blue terminal post
SK3, 103, 203, 303	Green terminal post
SW1, 101, 201, 301	SPDT toggle
SW2, 102, 202, 302	Rotary 1P12W (9 positions used)
SW3	Mains neon rocker switch
T1	PCB-mounting mains transformer 6-0-6V 500mA
	PCB; case (300 x 150 x 90mm); wire; fuseholder; nuts and bolts

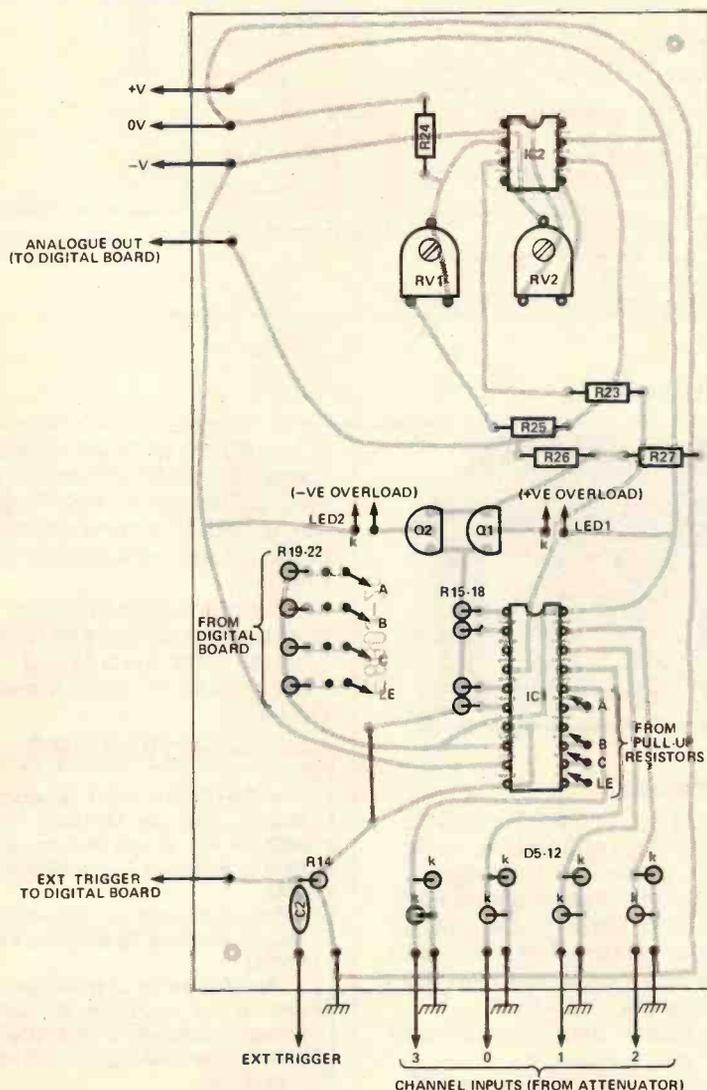


Fig. 5 The component overlay for the analogue board

each board (make sure of the polarity) and hook-up the ribbon cable to the computer. Apply an audio signal to each of the inputs in turn and check that by poking the channel number into &FCC0, you can obtain the signal at the output of the analogue board.

Now ground one input, select that channel (poke the required channel number to &FCC0) and then read &FCC1, which should yield a value between 122 and 134. Interference from nearby TVs and the like may prevent the value from being stable until the unit is properly screened.

With the unit in the case, glue a piece of metal (a scrap piece of aluminium is ideal if you have such a thing — about 50mm square) between the digital and power-supply boards and link this to earth. This will screen the ADC from the transformer and is noticeably beneficial.

Links from the attenuators to the analogue board should be made with screened cable (ordinary audio-frequency type is fine). Most types of wire can be used for the connections to the external trigger input, LEDs and general links between the PCB's.

Tuning

The operational differentiator now needs to be 'tuned.'

For each op-amp on the digital board, short together the two inputs of the op-amp (pins 2 and 3) using a screwdriver and adjust the pre-set until the output voltage


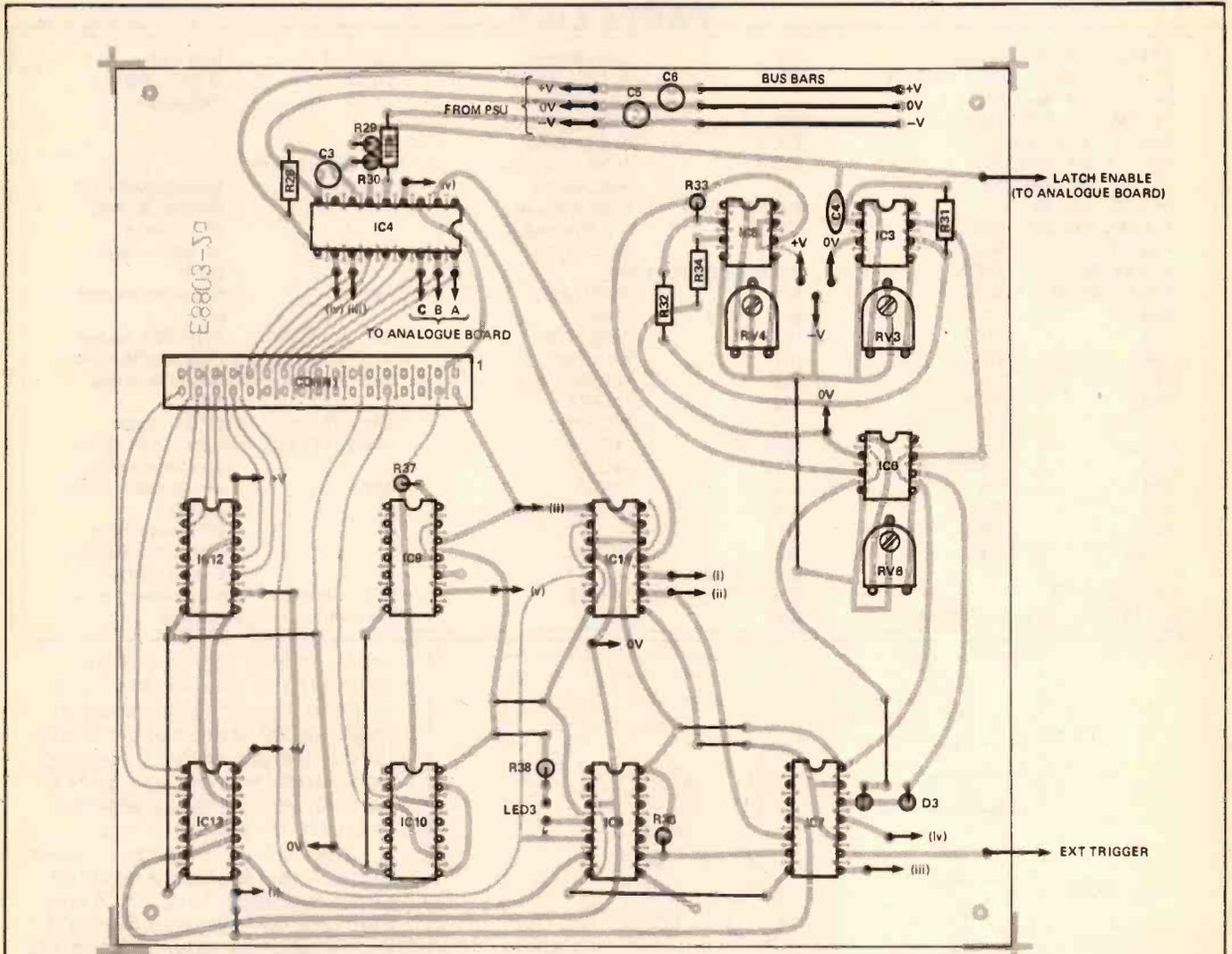


Fig. 6 The component overlay for the digital board

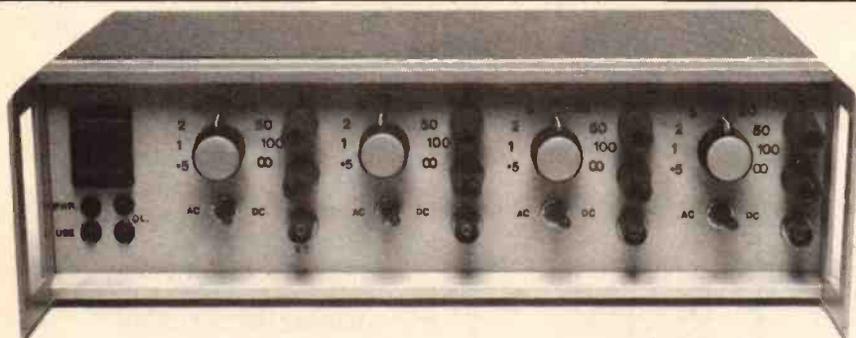

(pin 6 to ground) is as close to zero as possible).

The op-amp on the analogue board can be 'tuned' by linking R23 (either end) to 0V and adjusting the offset-null preset (RV2) until the output is as close to zero as possible. The gain of the op-amp can now be 'tweaked' by applying a known voltage, between 250mV and 350mV, to R23 (again, either end) and adjusting the preset (RV1) so that the input is amplified by a factor of 6.375.

Software

A program in BBC Basic and assembler is given to allow basic operation of the unit (Listing 1).

Those parameters which can be altered are displayed at the top right of the screen. The parameter for alteration is selected with the \uparrow and \downarrow keys and the value incremented or decremented with the \leftarrow and \rightarrow keys.

The time base is given in $\mu\text{s}/\text{point}$, there being 256 points across the trace. The 'Fast' option allow the fastest possible sampling

($11\mu\text{s}/\text{point}$) to be achieved. The 'Expand' option allows the time-base to be halved, quartered and so on, with intermediate points being added between the genuine readings.

Remember to take into account the settings of these three options when calculating frequencies, periodic times and the like.

BUYLINES

ETI

The 74HC4351 (IC1) is stocked by Maplin (part no. UF14Q). Note that both 18 and 20-pin devices exist. The PCB is designed for the 20-pin version only.


The case used for the prototype is also as supplied by Maplin as part no. YM51F.

The IDC cable used to connect the unit to the computer is most easily brought ready assembled. Maplin offer a service for making up such leads, for a small fee.

The PCB is as ever available from the PCB service.

Brainwave monitor

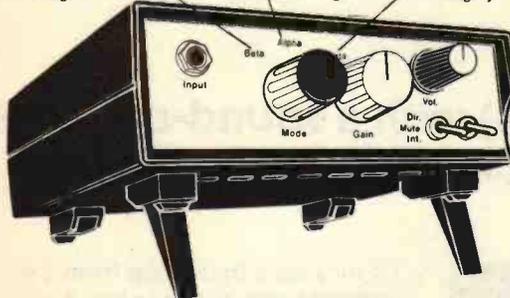- BETA** - Concentration, problem solving, active thought.
- ALPHA** - Relaxation, pleasure, tranquility, positive feelings.
- THETA** - Imagination, creativity, hypnagogic imagery.



BRAINWAVE MONITOR PARTS SET ONLY
£36.90
 + VAT

This unique project will allow you to hear your own brainwaves! Through a simple training program you can learn to control them and achieve peak performance in all situations. It will revolutionise your life!

The approved parts set contains: two PCBs; all components, including three PMI precision amplifiers; shielded box for screening the bio-amplifier; attractive instrument case with tilting feet; controls, switches, knobs, plugs, sockets; leads and brass electrodes, full instructions for assembly and use.

Parts are available separately. We also have a range of accessories, professional electrodes, books, etc. Please send a stamped, self-addressed envelope if you just want the lists. Otherwise, an SAE + £2 will bring you lists, construction details and further information.



THE ALPHA PLAN

Can you really train your mind to think more effectively? Can you really excel at things you're 'no good at'? The Alpha Plan has all the answers!
£2.50 (no VAT)




SILVER SOLUTION

Just wipe on with a cloth to plate PCB tracks, connectors, wire, component leads, coins or household ornaments with a layer of pure silver. It must be magic!
LARGE BOTTLE (150ml) SILVER SOLUTION £11.20 + VAT!

POWER CONDITIONER

As featured in ETI, January 1988. The approved parts set contains PCB, case, toroidal cores, class X and Y capacitors, VDRs, ICs, transistors, LEDs, all components, and full instructions.

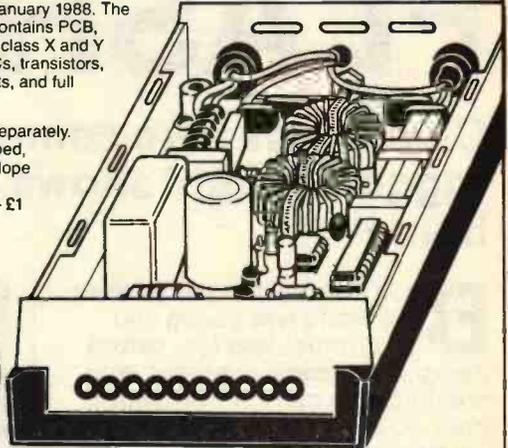Parts are available separately. Please send a stamped, self-addressed envelope if you want the lists. Otherwise, an SAE + £1 will bring you lists, construction details and further information.



POWER CONDITIONER PARTS SET ONLY
£28.50
 + VAT

- For those who will only be satisfied with the best
- Use with Hi-Fi, computers, radios, TV sets to eliminate mains-borne interference
- 10 LED logarithmic display shows the amount of interference removed
- Massive filter section with thirteen capacitors and two current-balanced inductors
- Bank of six VDRs to remove transients and spikes
- Suppresses common mode and differential mode interference

Complete Parts Sets for ETI Projects

FEATURED IN ETI, MARCH 1988

JUMPIN' JACK FLASH

is a

- Lighting wizard - brings any rock band's stage performance to life!
- Sound operated flash - photograph bullets in flight!
- Voice switch and sound to action controller with endless applications.

The parts set consists of a high quality PCB and all components. ICs, opto isolator, triac, heat sink, pots etc. to build the circuit board. What you do next is up to you! The ETI article, supplied free with every set, shows how to make the most of J.F.'s capabilities.

JUMPING JACK FLASH £6.90 + VAT



KNIGHT RAIDER

FEATURED IN ETI, JULY 1987

The ultimate in lighting effects for your Lamborghini, Maserati, Ferrari, BMW (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a bar, bouncing backwards and forwards along the row. Press again and try one of the other six patterns. An LED display on the control box tells you see what the main lights are doing.

The Knight Raider can be fitted to any car (it makes an excellent fog light!) or with low-powered bulbs it can turn any child's pedal car or bicycle into a spectacular TV-age toy!

The control box parts set consists of case, switches, LEDs, PCB, components, hardware and instructions. The sequence board includes PCB, ICs, power FETs, components, hardware and instructions.

KNIGHT RAIDER CONTROL BOX ONLY £6.90 + VAT!
KNIGHT RAIDER SEQUENCE BOARD ONLY £13.90 + VAT!

MATCHBOX AMPLIFIER


FEATURED IN ETI, APRIL 1986

No ordinary amplifiers, these. When our first customers took an interest, it was for the diminutive size (both modules will fit in a matchbox!), the total disregard for power supplies and speaker impedances, and the impressive power output from these little amplifiers. When they re-ordered, it was for the sound quality.

Two amplifier modules were described, both based on the powerful L165V IC. The single IC version will deliver over 20 Watts with a suitable speaker and power supply. The bridge version can provide up to 50W! Although the specified supply voltage and speaker impedance must be used to achieve maximum power, both modules are quite happy to work from any voltage between 12V and 32V, and will accommodate any type of speaker. The bridge version is ideal for giving a boost to car Hi-Fi systems, driving two 4 Ohm speakers in parallel on each channel for best effect.

Both designer-approved parts sets consist of a roller-timed printed circuit board and all components. The L165V ICs are also available individually, with a free mini data sheet giving specifications and suggested circuits.

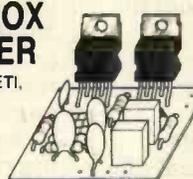SINGLE IC MATCHBOX AMPLIFIER SET (20W into 4 Ohms) £6.50 + VAT
BRIDGE AMPLIFIER SET (50W into 8 Ohms) £8.90 + VAT
L165V IC with data £3.90 + VAT



POWERFUL AIR IONISER

FEATURED IN ETI, JULY 1986

Ions have been described as 'vitamins of the air' by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products, was reliable, good to build... and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller-timed printed circuit board, 66 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs about a third of the price of the individual components! What more can we say?

DIRECT ION PARTS SET WITH BLACK CASE £11.50 + VAT
WITH WHITE CASE £11.80 + VAT
 Instructions are included



SPECIAL OFFERS

- AD7541 Precision 12-bit multiplying DAC £1.20 + VAT
- LM3524 Switch mode regulator IC £0.80 + VAT
- CF585 Calculator IC £1.00 + VAT
- LM339 Quad comparator IC 3 for £1.00 + VAT
- MC1458 Dual op-amp 3 for £1.00 + VAT

All ICs supplied with FREE DATA. Prices apply only while stocks last.

LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

LM2917 Experimenter Set £5.80 + VAT

RUGGED PLASTIC CASE

suitable for mains conditioner and mains controller.

ONLY £1.65 + VAT



LEDs

Green rectangular LEDs for bar-graph displays.

50 for £3.50 500 for £25
 100 for £6 1000 for £45

DIGITAL AND AUDIO EQUIPMENT LEDs

Assorted 3mm LEDs: red, green, yellow and orange. 25 of each (100 LEDs) for £6.80



Prices shown are exclusive of VAT, so please add 15% to the order total. UK postage is 70p on any order. Carriage and insurance for overseas orders £4.50. Please allow up to 14 days for delivery.

Specialist
SEMICONDUCTORS LIMITED

SALES DEPT.
 ROOM 107
 FOUNDERS HOUSE
 REDBROOK
 MONMOUTH
 GWENT

JUMPING JACK FLASH

Clap hands here comes Chappell (Paul) with a sound-activated trigger for light shows on the stage or curtain-drawing in the home

Back in the golden days when the world was young and electronics was fun, before designers became obsessed with creating ever more sophisticated multi IC circuits, a great deal of enjoyment was to be had from the simple pleasure of trying to squeeze the most spectacular performance from the smallest number of components.

If your sensibilities have been jaded by auto-ranging multi functional megachips and rubbed raw from exposure to high-tech gadgetry, just call on J J Flash to bring a breath of fresh air into your life.

Rumour has it that Jack Flash was born when some friends known collectively as Filament started to achieve notoriety around the local pub and club circuit with their special brand of rock music.

For a simple way to give impact to their stage presence, Flash had all the answers. A microphone in the bass drum would pick up the driving beat of the song and relay it to powerful lights which could be trained on any member of the band or even on the audience. For an outrageously OTT effect, a microphone and 100W lamp inside each drum would cause the drum itself to flash each time it was struck!

Of course there are those who would dispute this version of JJ's provenance. Many say that he was called into being as an aid to photography. Capturing a balloon about to burst and a bullet in flight are his finest achievements, they claim. Yet others insist that his main talent is in his versatility as a capable and powerful sound to action controller.

But what of the man himself? What did Flash claim to be? Perhaps we will never know the truth behind the legend but the



story of his life may shed some light on one of the most intriguing mysteries of our time.

Jumping Jack Flash Is A GaAs

One matter which is undisputed is JJF's circuit. It is shown in Fig. 1.

To the left, a microphone picks up sound vibrations and converts them to an electrical signal. This is amplified by an amount set by RV1 and fed to a circuit which responds only when the peaks are above a pre-set level. A timer IC (the good old 555) is triggered by the peaks and gives a pulse of controllable length at its output.

The pulse drives an opto isolated triac, which in its turn drives a lamp. All 500W of it!

The experience of operating the circuit in a small room is not to be missed — it gives a ridiculous sense of power to have every snap of your fingers accompanied by a blinding flash of light. Five hundred Watts in a living room is bright!

The length of the flash is set by RV2 — anything from the briefest supernova to several seconds of atomic blast. For a more restrained effect, you can use lower powered bulbs or coloured lamps.

For use on stage, the sensitivity control RV1 will have to be set very low and the microphone positioned so that it responds to the sound you want.

To pick up a hand clap from the opposite side of the room, it will have to be set somewhere near the maximum.

Construction

The component overlay for the PCB is shown in Fig. 2. There is nothing to cause any difficulties here.

The only point to watch is the mounting of the triac which must make good contact with the heatsink if the circuit is controlling a respectable amount of power.

First lay it on the board with the hole in its tab over the mounting hole in the PCB. You can then judge exactly where to bend the leads. Bend them at right angles to the body of the triac (not too sharply, or you'll weaken them) then insert the triac leads temporarily into their holes to check that the tab hole is aligned with the PCB hole.

Take the triac away from the board, smear the tab with a little heatsink compound then bolt the triac to the heatsink and PCB *before* soldering the leads. A flat washer between the bolt and the triac tab will help to spread the pressure and to prevent the tab from becoming distorted.

Figure 3 shows a suitable power supply for the circuit. Fig. 4 is a suggested layout for the circuit in a small plastic hobby box. There is no need to use a PCB for the power supply unless you are really keen to make a neat job of it. The smoothing capacitors and transformer will support the rectifiers.

The microphone insert can be fixed to the case or can be remote from it at the end of a length of screened cable. If you splash out on a 3.5mm jack plug and socket, you can leave all your options open.

You'll notice the power supply has no regulator ICs. In the days

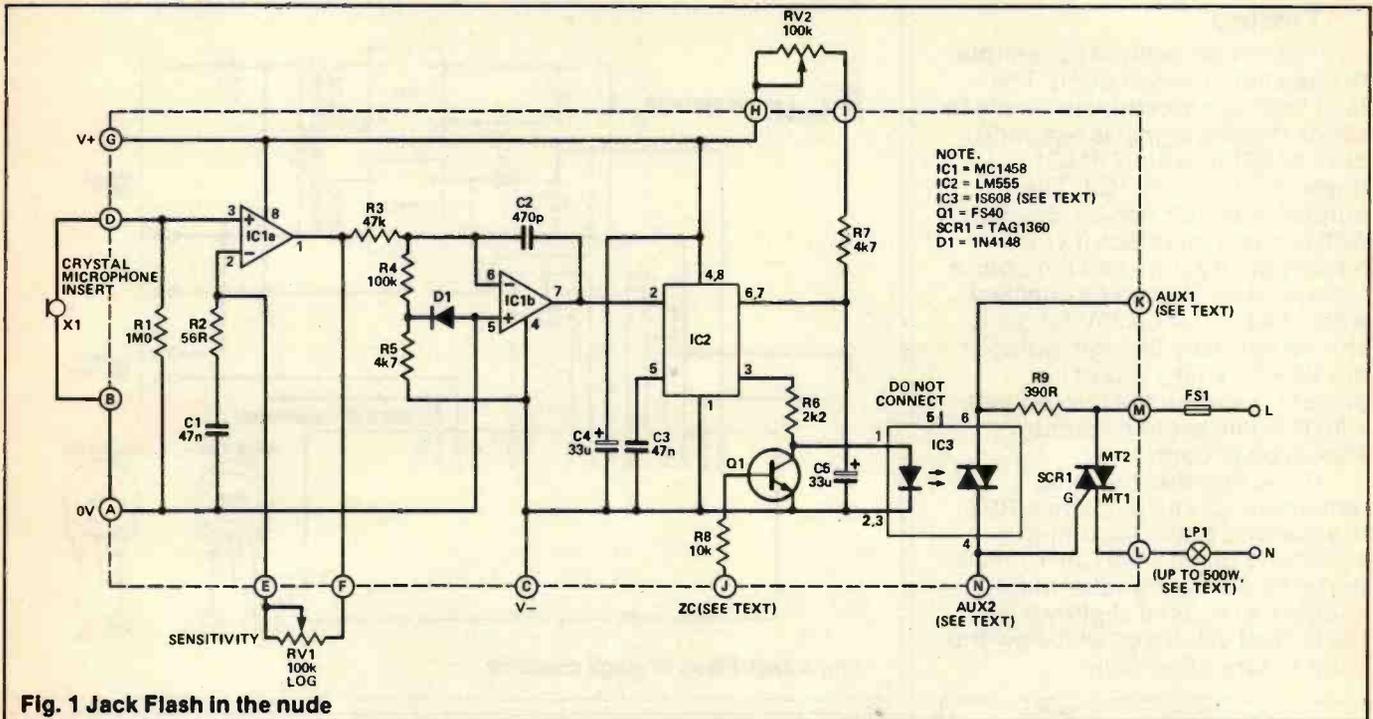


Fig. 1 Jack Flash in the nude

HOW IT WORKS

The signal from the microphone is amplified by IC1a.

Immunity to mains hum is achieved by the crude but effective expedient of giving C1 a low enough value to reduce the gain almost to unity at 50Hz while amplifying the fast spikes of percussive sounds anything up to about 2,000 times.

Components D1, R4, R5 and R3 hold pin 6 of IC1 slightly lower than pin 5 in the absence of a signal, keeping the output high. C2 tames the output of IC1b a little but no attempt is made to rectify or smooth the output since all IC2 requires is a signal which drops briefly below $\frac{1}{3}V+$.

IC2 is the familiar 555 timer connected in monostable mode with time period adjusted by RV2. R6 limits the current to the opto isolator.

When connected as shown in Fig. 3, Q1 diverts the timer's output current from the isolator whenever any appreciable voltage is present across BR2, forming a simple zero crossing detector. The opto triac triggers the main triac via the surge limiting resistor R9. The main triac switches on the load.

when regulators had to be made from discrete components, they would only be used when absolutely necessary. These days they are included in every circuit almost as a reflex action. Just to be different (and since they are not necessary) I've left them out. Saves a quid, doesn't it?

When you come to test the circuit remember that everything beyond the opto coupler (IC3) is live, including the heatsink which

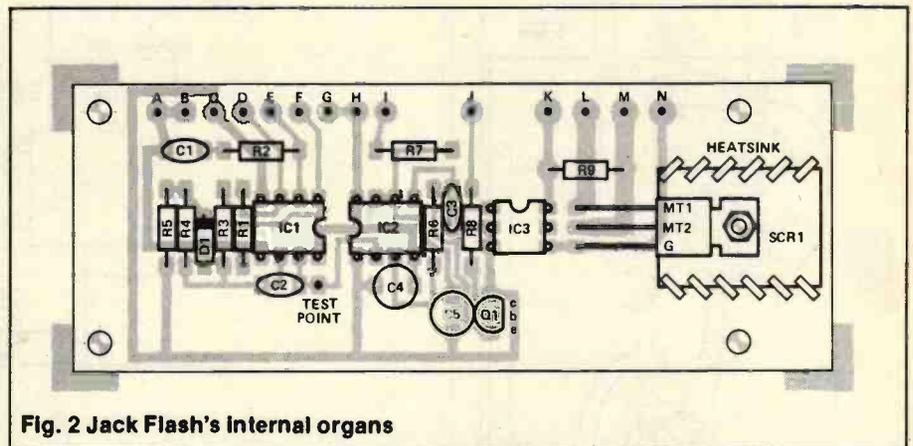


Fig. 2 Jack Flash's internal organs

PARTS LIST

RESISTORS (all $\frac{1}{4}W$ 5%)

R1	1M0
R2	56R
R3	47k
R4	100k
R5	4k7
R6	2k2
R7	4k7
R8	10k
R9	390R
RV1	100k log pot
RV2	100k lin pot

CAPACITORS

C1	47m
C2	470p
C3	47n
C4	33 μ 25V radial electrolytic
C5	33 μ 25V radial electrolytic
C6, 7	1000 μ 25V radial electrolytic

SEMICONDUCTORS

IC1	MC1458
IC2	LM555
IC3	IS608 or similar (MOC3021 etc)
Q1	FS40
SCR1	TAG1360
D1	1N4148
D2	1N4001
BR1, 2	low voltage bridge rectifier, any type

MISCELLANEOUS

X1	Crystal microphone insert (almost any microphone will do as a substitute).
T1	0-6V, 0-6V 6VA.
	Connecting wire; mains wire; plugs; sockets; plastic box. Optional parts for the modified versions are shown in the relevant diagrams.

is connected via the triac tab directly to the mains input. If you think anything may be wrong with the low voltage side of the circuit,

disconnect the mains from the PCB (by removing the connections to points L and N) before checking it out.

Testing

The circuit really is too simple to need much explanation. The fault finding procedure is simply to check that the signal is reaching pin 1 of IC1 and pin 7 of IC1, triggering the timer IC2. The outputs from IC1 can be checked with a crystal earpiece if you haven't got a scope and the output from pin 3 of IC2 can be checked with a test meter on 25V range. It should normally be high, going low when a sharp sound is present. Tapping the microphone with the gain set to maximum should be enough.

If you find that the lamp remains on at all times when RV1 is advanced to the maximum sensitivity (even when the room is perfectly quiet) the value of R4 should be reduced slightly. Use the largest value that will allow the lamp to turn off reliably.

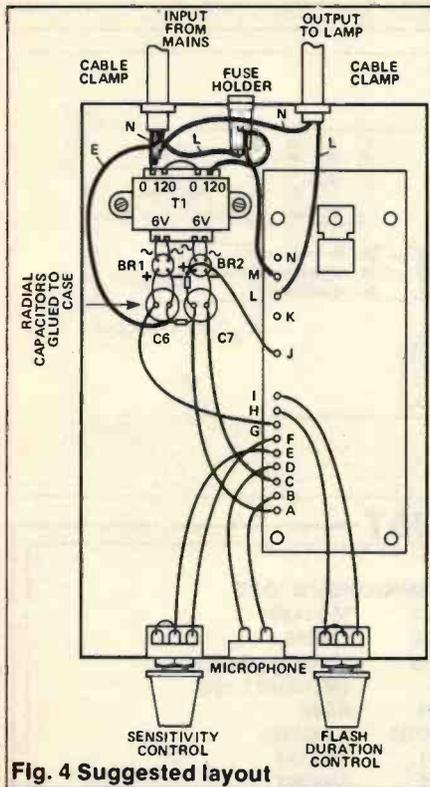


Fig. 4 Suggested layout

Transistor Q1 and the connection to the J terminal form a zero crossing detector to cut down on the interference generated by SCR1. If this feature is not required, D2 and the link to terminal J can both be omitted.

Other Applications

If your pulse doesn't race at the thought of JJF's electric stage performances, perhaps your mind is on photography. Sound triggers for cameras were all the rage a while back, allowing spectacular photographs of such things as

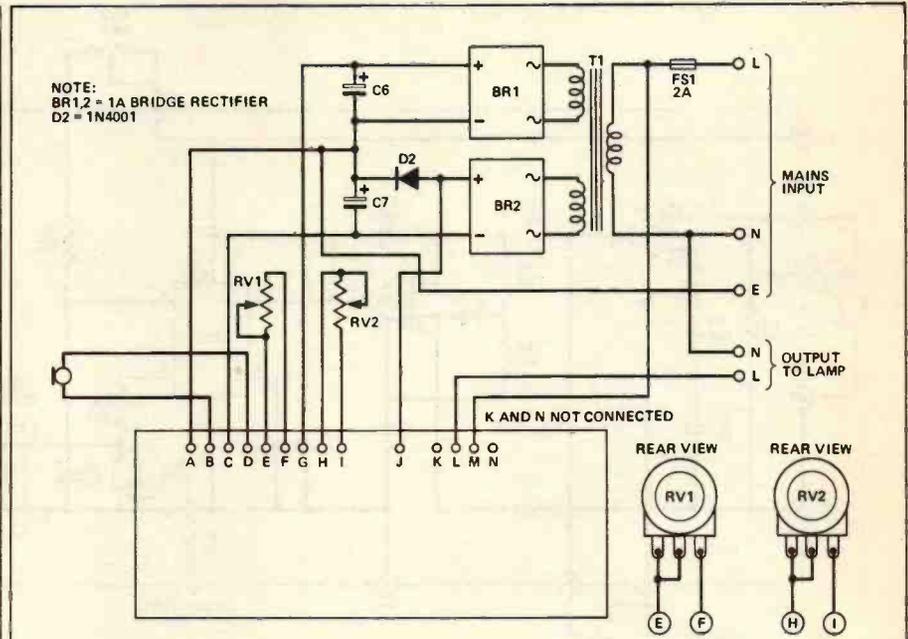


Fig. 3 Jack Flash In stage costume

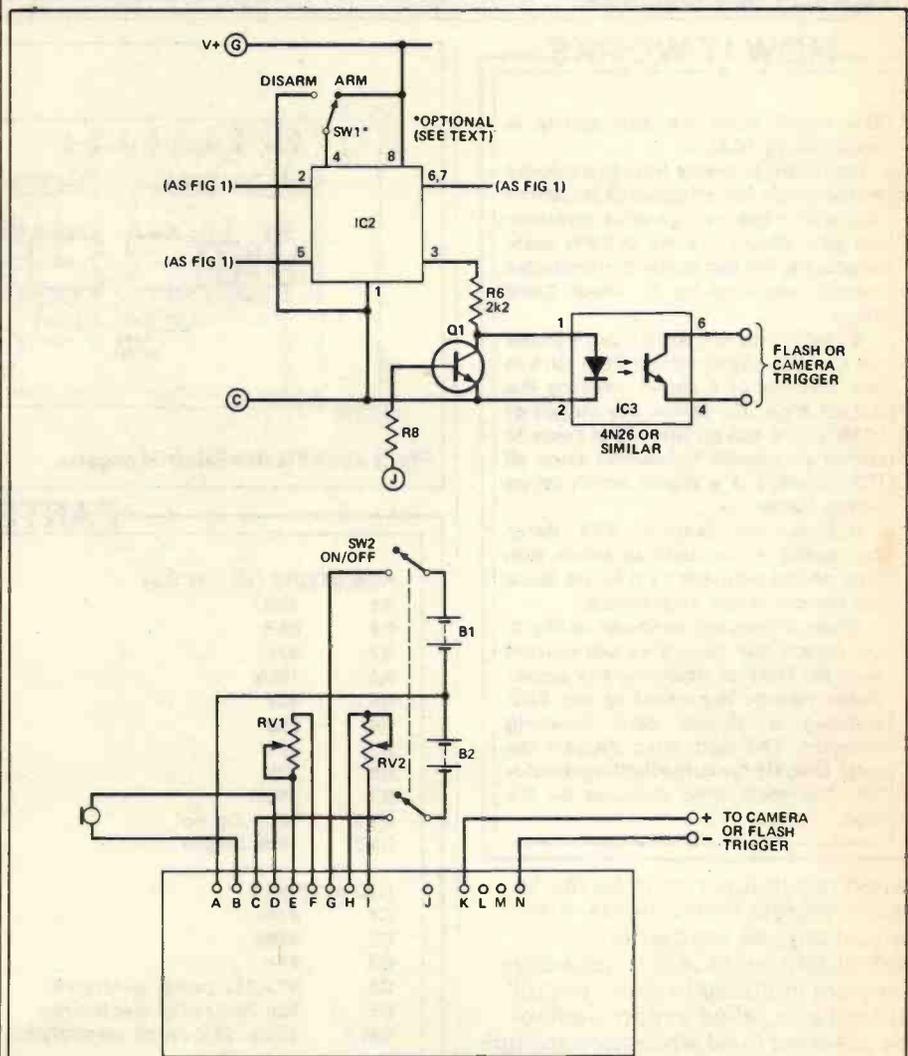


Fig. 5(a) Circuit modifications for the sound trigger. SW1 is optional (see text). Q1 and R8 are not required, but there is no need to remove them. All parts of the circuit not shown are the same as for Fig. 1. (b) Connections to the PCB for photographic sound trigger

PROJECT: Drum Flash


bursting balloons, popping balloons, exploding balloons, balloons going bang and so on.

BUYLINES

Most component suppliers will be able to provide suitable parts for this project. The only awkward device is the opto triac (IC3). If you use a type other than the IS608, it would be wise to increase the value of R9 just in case the surge current rating is lower. Most samples of the more readily available MOC3021 will work without modification to the circuit but if it does not turn on reliably this can be cured by reducing the value of R6 (not less than 1k Ω).

To get you started a parts set for the main circuit including PCB, triac, heat-sink, pots and microphone is available from Specialist Semiconductors (see their ad in this issue). Power supply components are available separately from the same source, although your spares box will probably have suitable components in it.

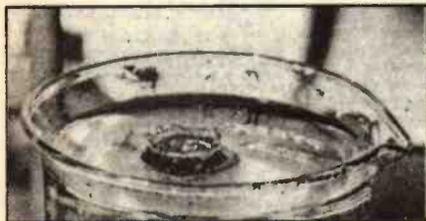The PCB will be available from our Readers Services in due course.



The photographs are made either by using the sound of the exploding balloon to trigger flash lights in a darkened room (the camera shutter would be left open throughout the procedure) or by triggering the camera itself if it was fitted with a solenoid operated shutter.

A touch of the soldering iron will transform JJF into a camera sound trigger. The way to do it is shown in Fig. 5. The power triac and heatsink are removed from the PCB and the opto triac is replaced by an ordinary opto-isolated transistor.

The only other difference is that the circuit is run from a pair of PP3 batteries instead of the mains power supply. You will probably want to put an on-off switch in the power supply as well.

The circuit can be armed by simply turning up the sensitivity. Otherwise, a switch in the 'reset' line of IC2 will give an arm/disarm function. You'll need to cut the PCB track for this.

For general sound switching purposes, the circuit of Fig. 1 can be used for mains applications and the modifications shown in Fig. 5 will make the circuit suitable for low voltage applications. The

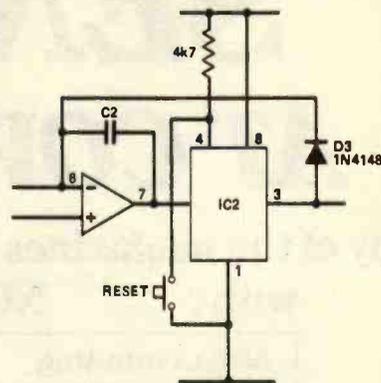


Fig. 6 Making the trigger latch. A diode is added between IC2 pin 3 and IC1 pin 6. The track between pins 4 and 8 of IC2 is cut and pin 4 is taken to V+ via a 4k7 resistor. A reset button is added between pins 1 and 4 of IC2. The remainder of the circuit is as for Fig. 1

other feature you may want to add — latching — is shown in Fig. 6. With this configuration the circuit will latch when a sound triggers the switch and will remain on until the reset button is pressed. So — open your curtains with a whistle or your garage doors with a toot! Or just have fun experimenting.

ETI

It's easy to complain about an advertisement. Once you know how.

One of the ways we keep a check on the advertising that appears in the press, on posters and in the cinema is by responding to consumers' complaints.

Any complaint sent to us is considered carefully and, if there's a case to answer, a full investigation is made.

If you think you've got good reason to complain about an advertisement, send off for a copy of our free leaflet.

It will tell you all you need to know to help us process your complaint as quickly as possible.

The Advertising Standards Authority.  If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 1 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

TRANSFORMERS



3VA to . . . KVA many standard ranges on-the-shelf

Mains Isolators, Autos, Cased Autos, 12/24V, 15/30V, 25/30V, 30/60V, 48/96V. All with intermediate voltage taps. Also Valve, Mains & Output types.

WINDING TO SPEC including Toroidals.

Inverters 12/24V DC to 240V AC constant voltage transformers for spike-free stable mains.

Unit 211, Stratford Workshops, Burford Road, London E15 2SP

BARRIE ELECTRONICS LTD
Tel: 01-555 0228 (3 lines)

BINDERS

FOR YOUR VALUABLE COLLECTION OF ELECTRONICS TODAY INTERNATIONAL MAGAZINES

• SMART • EASY TO USE • TOP QUALITY
To ASP Readers Services, PO Box 35, Wolsley House, Wolsley Road, Hemel Hempstead, Herts HP2 4SS (0442-41221)

£5.95 inc. P&P

Please supply . . . Electronics Today International Binders £5.95 inc. P&P

Total £ (Please make cheques payable to ASP Ltd.)

Years Required — 198 199 198 199

Name
Address

Please allow 21 days for delivery



SUBSCRIPTIONS SENSATIONS!

AT COVER PRICE ONLY!

Any of the magazines from the list below can be delivered to your door
with : **NO handling charge** **NO postage costs**

A&B Computing	£18.00
Aeromodeller	£22.20
Citizens Band	£16.20
Clocks	£27.00
Commodore Disk User	£15.00
Disk User	£17.70
Electronics Digest	£11.00
Electronics Today International	£16.80
Ham Radio Today	£15.60
Military Modelling	£15.60
Model Boats	£15.60
Model Engineer	£26.40
Photography	£15.00
Photoplay	£12.00
Popular Crafts	£16.20
Radio Control Model Cars	£16.20
Radio Control Boat Modeller	£7.50
RCM&E	£14.40
Radio Control Scale Aircraft Quarterly	£9.00
Radio Modeller	£14.40
Sea Classic International	£11.70
Scale Models International	£15.00
Video Today	£15.00
Which Video?	£15.00
Woodworker	£15.60
Your Commodore	£14.40
Model Railways	£13.20
Practical Wargamer	£7.80

The Above Prices Refer to U.K. Subscriptions Only

This offer is also open to existing U.K. subscribers who
may wish to extend their current subscriptions.

Please commence my subscription(s) To..... with the..... Issue
I enclose my cheque/money order for £..... made payable to Argus Specialist Publications Ltd.
or debit £..... from my Access/Barclaycard No.

valid from..... to..... Signature.....

Name.....

Address.....



Send this form with your remittance to:
**INFONET LTD. (N.R.S. 88) 5 River Park Estate,
Berkhamsted, Herts. HP4 1HL.**



SPECTRUM CO-PROCESSOR

Graeme Durant continues to build his add-on computer with this ingenious 256K RAM card

Having covered the design and construction of the Z80 CPU card last month, it is now time to move on and look at the main dynamic RAM cards.

These provide the co-processor with a large area of storage which may be used for program or data. Each DRAM circuit is built on a standard 160 × 100mm eurocard sized double-sided PCB and consists of 256K of store.

Since the Z80 has an address range restricted to 64K, the DRAM card uses a paging mechanism to enable the Z80 to accommodate this increased address range.

Connections to the board are once again made via a DIN41612 connector, the pinout being the same as for the CPU card described last month.


This DRAM card was also designed to be strictly general purpose and it can be used in any Z80 or Z80A based application you like — for example upgrading the available memory in a Z80 based home computer.

DRAM

Dynamic RAM has traditionally been tricky stuff to use. Although DRAM is cheap and can offer large storage capacities on small chips, it has the awkward requirements of periodic refresh and a multitude of carefully timed control signals. These have often been enough to turn the average hobbyist to the alternative expensive and bulky static RAM devices.

Early DRAM devices needed everything doing for them. All refresh strobes and addresses had to be externally generated. As generations of dynamic memory have come and gone, the external hardware overhead has been reduced. Now DRAM has in effect 'grown-up.' It is much more self sufficient and needs a lot less in the way of external prodding to facilitate refresh and data access.

The 'state of the art' DRAM as

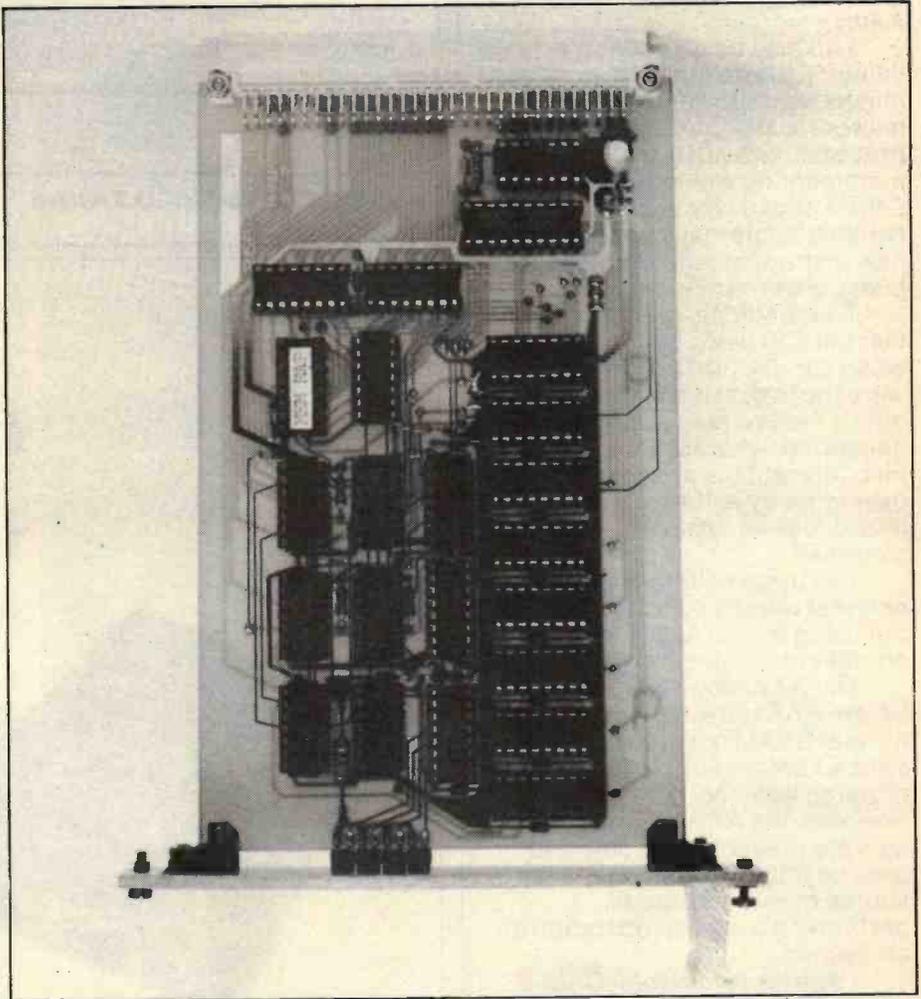

far as performance goes must be the AAA2800 series of CMOS 256Kbit devices, designed by Inmos and produced by NMB in the newest, most advanced CMOS VLSI manufacturing plant in Japan.

These memories combine low-power operation, fast access times and a number of versatile operating modes, making them the world's fastest monolithic 256K DRAM available.

One of the most interesting features included as far as the amateur is concerned is the so called 'CAS before RAS' refresh mode which makes the process of refresh simplicity itself. So the

timing signals required to drive the AAA2800 series are very straightforward. It is for these reasons that the AAA2800 family was chosen for use in this design.

One special feature of this circuit is that all the timing on the board is derived from the main CPU clock using synchronous logic techniques. So it is usable in any Z80 or Z80A based system regardless of the clock frequency.

Also, expensive LSI DRAM controller chips and unreliable RC generated relays are completely avoided. The design is based on ordinary TTL logic and operates reliably under all conditions with no setting up required at all.

Refresh Schemes

The usual method used to achieve the obligatory DRAM refresh process is termed **RAS-only refresh**. This is shown in Fig. 1.

Since the refresh operation only requires that each row within the memory array is accessed, **CAS** is held inactive high and **RAS** is strobed whilst a suitable row refresh address is supplied to the memory chips. To ensure correct operation of the AAA2800, all 256 rows must be refreshed every 4.4ms.

You may be wondering why we cannot just use the built-in refresh mechanism provided by the Z80 microprocessor itself — the processor provides an incrementing row address for the DRAM after every instruction fetch (while it is internally decoding the new instruction and the system buses are otherwise unused).

This would be great but for the fact the Z80 dates back to the days when sub-64K DRAM devices were the best available, and so only a 7-bit refresh address is generated, whereas we need an 8-bit address. This problem can be overcome by software but that introduces an unacceptable time overhead.

The usual solution is an external refresh address generator but using the AAA2800 we have another more elegant option.

The AAA2800 provides a **CAS before RAS refresh mode**. During normal DRAM accesses, **RAS** is strobed before **CAS** to latch-in the required address. If this order is reversed, the AAA2800 ignores the address present on its pins and uses an internal 8-bit counter as a source of row addresses, performing a refresh operation all on its own.

The trick is to strobe **CAS** before **RAS** (Fig. 2) every time the Z80 authorises a refresh cycle and the result is a completely transparent refresh scheme with no wasted time overhead and no external refresh logic required.

Paging

In common with most 8-bit microprocessors, the Z80 is capable of directly addressing only 64K of memory. However, this limited address range can be extended by *paging*. The large block of storage to be addressed is partitioned into areas called pages, each 64K locations or less in size.

The processor addresses the contents of a page directly,

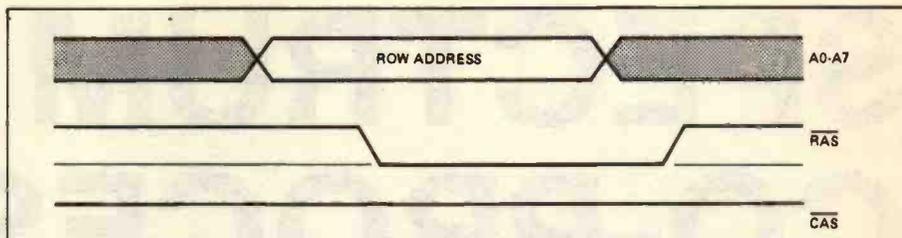


Fig. 1 RAS only refresh


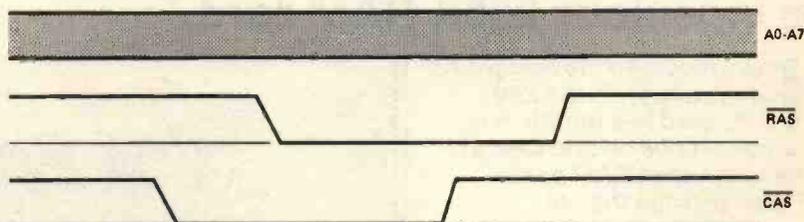


Fig. 2 CAS before RAS refresh

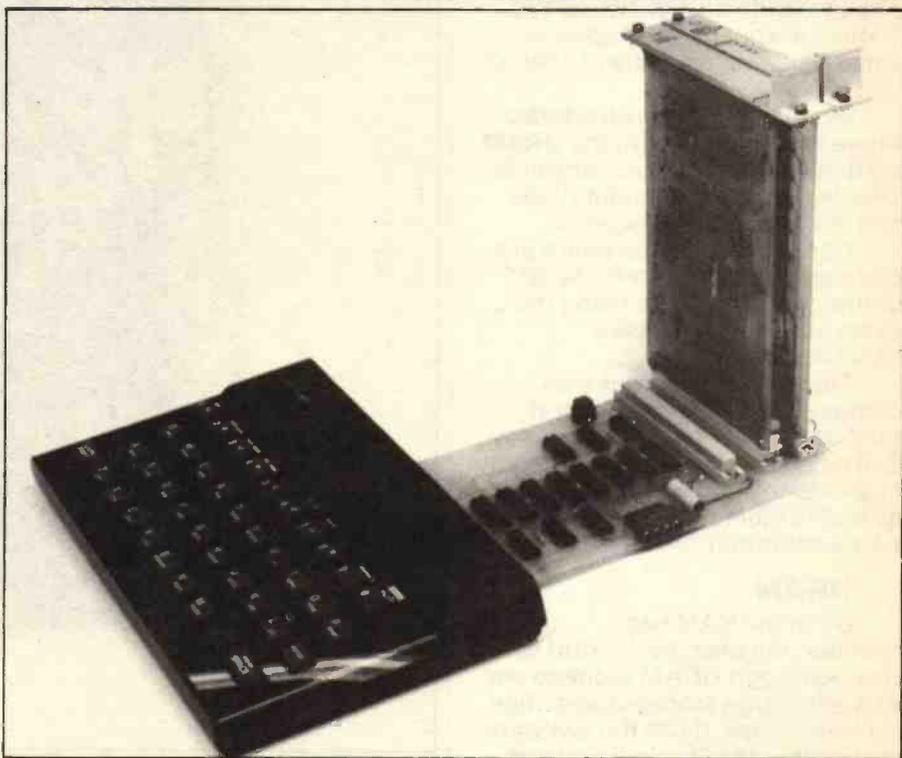

because its address range can handle the entire page in one go. However, the actual page accessed is selected, one at a time, by some other means.

The usual method of page selection is via a *bank select* register. This is a multi-bit latch which holds the currently selected page number and can be updated by the processor to change pages. The memory hardware responds to the contents of the bank register by enabling only the memory page required for access on the Z80 buses.

In a Z80 based system, this register can be addressed as an I/O port so it is conveniently

separate from the memory map — thus avoiding the possibility of being able to page itself out!

The disadvantages of simple paging schemes like this revolve around the fact that the memory space is no longer randomly accessible.

The addressing of a location is now a two stage process, requiring an update of the bank register as well as the memory access itself. This can prove awkward if the program being executed is stored in the paged memory when jumps and subroutine calls may entail page changes.

Unless the machine's operating system has some kind of

monitoring capability to handle such situations, the simplest way round this problem is to provide a small area of permanently enabled memory which is accessible regardless of the current page selected.

When code execution requires a change of page, a routine residing in this unpagged memory is called to change page and then to jump to the required location in the new page. This is the scheme used in this design. A memory map PROM (IC19) is used to permanently disable a section of each page in the paged memory, to allow the unpagged memory to sit undisturbed.

This unpagged memory consists of the operating system EPROM and the scratchpad RAM on the CPU card, described last month. The PROM allows unpagged program areas to be selected in steps of 256 locations so the least possible DRAM space is wasted in any given application.

For this co-processor design, the bottom 5K locations of each 64K page are disabled by the PROM but this can be easily changed for other applications by blowing different map PROM data.

Construction

The construction of the RAM card should not create too many problems, particularly if the suggested PCB layout is used. Like the Z80 CPU card described last month, this board is double sided but for reasons of expense, through-plating is not used to interconnect the two layers.

The through connections are shown in the overlay diagram (Fig. 4) and must be made by either wire links through the board, by the passive component leads, or by means of the IC pins. The various techniques for employing these methods were described last month. Once again 'turned pin' DIL sockets should be used to allow through connections via the IC pins.

As high currents are likely to flow in the memory power and ground lines, multiple through connections are provided to reduce the impedance of these links. These take the form of two or three closely situated through links. All must be made to ensure reliable operation.

This board also includes a large number of supply decoupling capacitors and it is important not to omit any of these. Each RAM chip has its own associated capacitor, connected

close to the power and ground pins. These capacitors must be long leaded axial types to fit the suggested PCB foil and these ensure low supply impedances at high frequencies where noise problems might otherwise exist.

Short M2.5 nuts and bolts should be used to fix the edge connector to the PCB for added strength. Note that two of the connector pins must also be soldered on the top side of the PCB to link through the board.

At this stage you must decide whether to program the card for operation as pages 0-3 or pages 4-7. This determines what you do with the link pads on the PCB.

If you want the card to appear as pages 0-3 then point A should be connected to point C on the circuit diagram by soldering a through link at pad X.

If the card is to appear as pages 4-7, point B on the circuit diagram must be connected to point C with two through connections at pads Y and Z.

The page indication LEDs are fitted next. Since these are closely spaced, light can easily spill from one LED to the next, spoiling the effect. This can be avoided by fitting each LED with a short length of rubber sleeving to trap the light. Note that these LEDs need to be soldered in on the top side of the PC board as well as underneath.

The address mapping PROM IC19 must be fitted to the board before power is applied for the first time. The *How It Works* section explains the PROM programming. See *Buylines* for details of pre-programmed PROMs with the correct specification.

Testing

Testing the completed memory card is not easy at this stage. If you are intending to build up the whole co-processor project, the procedure for testing all the hardware together will be given next month. If, however, the DRAM card is intended for your own particular application then testing must consist of connecting the card into your target system and powering it up, not forgetting to initialise the bank select register.

If data can be reliably stored and retrieved, your DRAM card is fine. If there are problems, first check that you have soldered everything in, particularly on the top side of the board, then ensure all the on-board control signals are active and that addresses and

BUYLINES

Most of the components used on this card should be available from usual component distributors. There are a number of parts which cannot easily be substituted with any old manufacturer's components due to required dimensions or specifications.

The miniature axial ceramic capacitors used throughout this project are available from Verospeed as order code 92-50952H. Verospeed can be contacted at Stansted Road, Boyatt Wood, Eastleigh, Hants SO5 4ZY. Tel. (0703) 644555.

The ultramin 100µ radial electrolytic capacitor was obtained from Maplin as order code RK50E. The DIN41612 backplane connector is also available from Maplin (order code FJ51F). The turned pin IC sockets suitable for use with this PC card are as supplied by most competent stockists but try Maplin's range if uncertain.

The Dynamic RAM chips used in this design are not commonly available due to their relative newness. Since this design makes use of their special CAS before RAS refresh mode, other manufacturer's devices cannot be substituted. The whole range of AAA2800 series RAMs are available from NMB's UK distributor, Mogul Electronics. The circuit was designed to work with any of the range of five AAA2800 series parts (AAA2800, 1, 2, 3 or 4) having access times of 120ns or faster. As the cost of DRAM is continually fluctuating, it is best to choose the cheapest of these parts at the time of ordering. Mogul Electronics can be contacted at Central Court, Knoll Rise, Orpington, Kent BR1 0JA.

Unprogrammed 24S10 PROMs are readily available from many of the regular advertisers in ETI. However, since readers might find it difficult to get these bipolar devices programmed, ready blown PROMs suitable for use in this co-processor project are available from the author for price £6.00 inclusive of postage. Please send cheques or postal orders made payable to the author to 52 Bishops Court, Trumpington, Cambridge CB2 2NN. Allow 28 days for delivery.

Finally, the printed circuit board is available from the PCB service.

data are reaching the DRAM chips.

Like all microprocessor based projects fault finding is extremely difficult without the right gear, and a decent logic analyser will set you back five grand or so. Having said that, a little perseverance with a scope should pay dividends.

Next month we shall look at the final bit of hardware to complete the Spectrum co-processor design — the interface card through which the co-processor can communicate with the Spectrum. We shall also start to examine the software side of things, so don't miss the next exciting episode!

HOW IT WORKS

The heart of the circuit (Fig. 3) is of course the eight dynamic RAM devices, IC22-29. The rest of the circuit can be considered as two distinct areas around this DRAM — the paging/address logic and the circuits which manage the memory chips by generating the required control signals.

Looking first at the paging/address logic, this enables the memory card for access when both a valid page on the card is selected and a valid location within that page is addressed.

The bank select register, consisting of three D-type flip-flops (IC14 and IC33b) is mapped onto the Z80 output port at address 254 by IC20 and IC31a, b, d. The data value sent by the Z80 to this port will determine which page is chosen.

IC18 decodes the port data to see whether one of the four pages on this card is selected. IC33b stores the result, its Q output being low if the current page is on the card. At the same time, IC14 stores the states of the two least significant port data bits.

If the required page does reside on this card then these two bits signify which page from the four is selected and will form two extra address bits to the DRAM devices.

IC21 is used as a two-to-four line binary decoder to light up one of four LEDs to indicate which page is currently selected. This decoder is disabled if the current page is not present on the card so all the LEDs are blanked.

For circuit simplicity inverse logic is used for page selection. Sending 255 to the bank register switches in page zero, 254 switches in page one and so on.


The user has the option of making the card either pages 0-3 or pages 4-7. This is achieved by means of a link on the PCB. If point A is linked to point C, the output of IC18 will be active low when the most significant six bits of data to the bank register port are high. So, pages 0, 1, 2, 3 are decoded onto the card. If point B is linked to point C then port bit D2 is inverted before it gets to IC18 and pages 4, 5, 6, 7 are decoded onto the card.

In this way, up to eight pages of DRAM (two DRAM boards) may be used in the system. The 8-bit port decoding however, allows up to 256 memory pages to be controlled from the processor and if more pages are required then further data bits must be inverted on their way into IC18. This would of course entail modifications to the PCB design itself.

IC19 is an address decode PROM used to disable the memory card when certain addresses occur, allowing other unpagged memory (such as EPROM) to reside in the system.

Its address inputs are connected to the CPU's eight most significant address lines and so the PROM changes its addressed location every 256 Z80 locations.

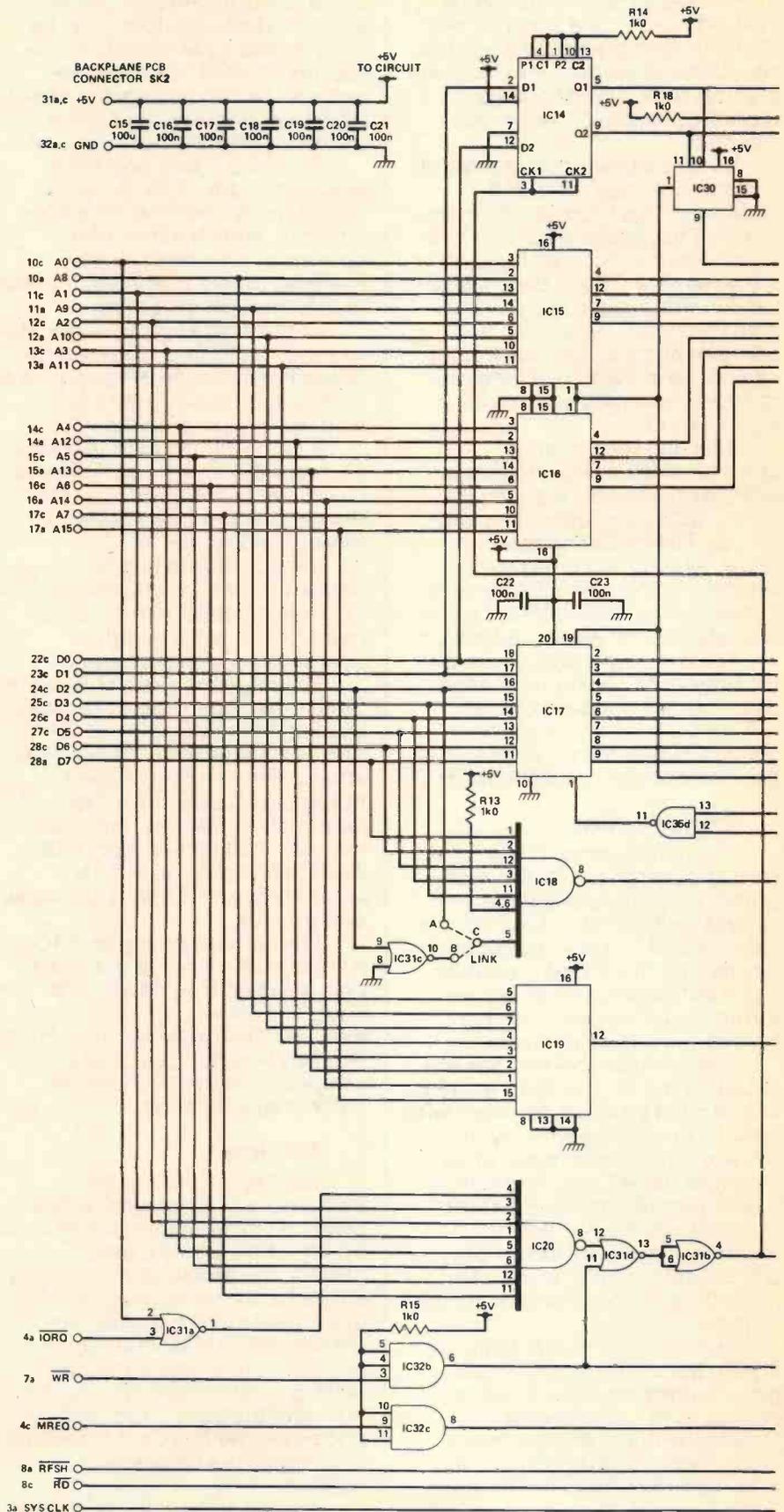The PROM is programmed to produce a logic low at its least significant bit output (pin 12) when the



card is to be disabled. For example, if the first 1K locations are to be reserved for an unpagged EPROM, IC19 should be programmed with the first four locations containing zeros in the LS bit position leaving the rest of the device holding all ones.

For this design, where the first 5K locations must be disabled, IC19 must have its first 20 locations programmed to E(hex) and the following 236 locations programmed to F(hex).

The rest of the circuitry manages the memory devices themselves allowing

PROJECT: Co-processor RAM

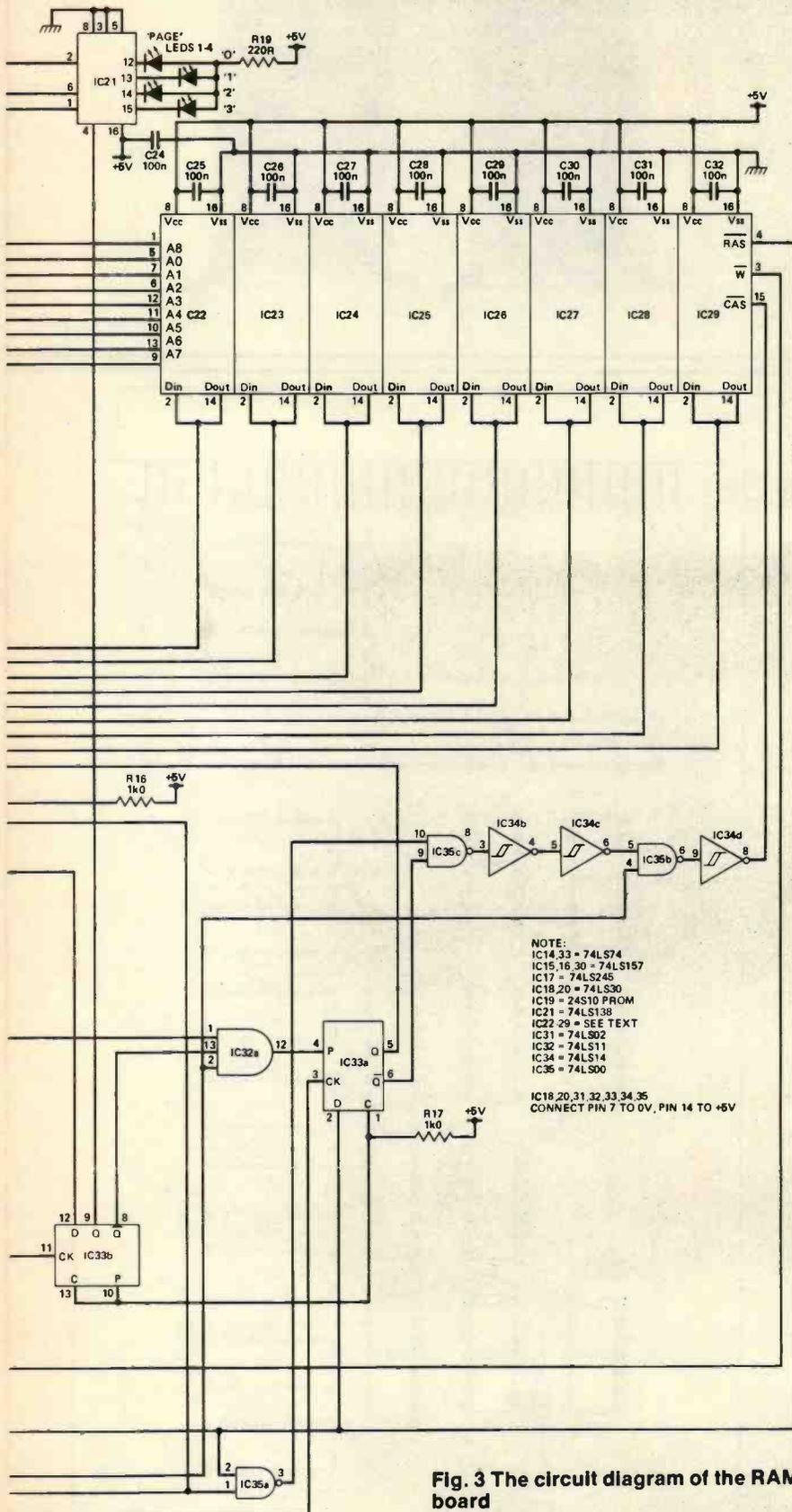


Fig. 3 The circuit diagram of the RAM board

them to be accessed for data storage or retrieval and also handles the refresh requirements.

Dynamic RAM expects to receive its address signals in two halves (the row and column addresses) multiplexed in time onto one set of address pins. The

DRAM devices require three correctly overlapped control signals, $\overline{\text{RAS}}$, $\overline{\text{CAS}}$ and $\overline{\text{W}}$ to make use of this address information. $\overline{\text{RAS}}$ is the strobe which latches in the row address, $\overline{\text{CAS}}$ latches in the column address and $\overline{\text{W}}$ is the write enable control.

A further signal is required to drive the address multiplexers themselves, selecting whether the row or column addresses are being supplied to the DRAM.

In this design the $\overline{\text{RAS}}$ signal is directly obtained by using the Z80 memory access strobe signal $\overline{\text{MREQ}}$ via buffer IC32c. The DRAM write control signal $\overline{\text{W}}$ is the Z80 write strobe $\overline{\text{WR}}$ buffered by IC32b.

The generation of the DRAM $\overline{\text{CAS}}$ and the multiplexer select signal, is a little more complicated. Their precise timing has to tie in with $\overline{\text{RAS}}$ and $\overline{\text{W}}$.

D-type flip-flop IC33a is clocked at high speed by the system clock and on each rising clock edge passes the state of $\overline{\text{MREQ}}$ to its Q output. The relative timing of $\overline{\text{MREQ}}$ with the clock is such that the Q output of IC33a follows $\overline{\text{MREQ}}$ with a delay of about 50ns minimum (assuming a 4MHz clock).

This delayed signal is used to drive the select line of the memory address multiplexer formed by IC15, 16 and 30. The 50ns switchover delay after $\overline{\text{RAS}}$ ensures the row address hold time is not invalidated.

The address multiplexed into the DRAM consists of 16 bits of address from the Z80 and two bits of address from the bank select register, IC14. This results in the required configuration of four 64K pages with each page being directly accessible to the CPU.

The Q output of IC33a goes on to form $\overline{\text{CAS}}$ via IC34b, c, d and IC35b, c. The DRAM chips used in this design (in common with most dynamic memories) require for normal access that $\overline{\text{CAS}}$ goes low after $\overline{\text{RAS}}$ and that the $\overline{\text{W}}$ strobe has settled before $\overline{\text{CAS}}$ goes low.

The delayed $\overline{\text{RAS}}$ signal from IC33a is guaranteed to occur after $\overline{\text{RAS}}$ itself. Similarly IC35a detects when the Z80 $\overline{\text{RD}}$ or $\overline{\text{WR}}$ strobes are active. When this happens it signifies that the DRAM $\overline{\text{W}}$ control is also present. The output of IC35c will go low only when both the delayed $\overline{\text{RAS}}$ and the output of IC35a are active, thus fulfilling the timing requirements for $\overline{\text{CAS}}$ in relation to $\overline{\text{RAS}}$ and $\overline{\text{W}}$.

The output of IC35c is given a little extra delay by IC34b, c to ensure the recently multiplexed column address has had time to settle. This signal then passes via IC35b and IC34d to drive the DRAM $\overline{\text{CAS}}$ line.

IC33a can be disabled via its asynchronous preset input by IC32a, thus holding $\overline{\text{CAS}}$ inactive when a memory access is not required on this card.

This occurs when either the current page is not on this card (IC33b $\overline{\text{Q}}$ is low), when an invalid address has been received (detected by IC19) or when a refresh operation is taking place (Z80 $\overline{\text{RFSH}}$ line low).

When the Z80 authorises a refresh cycle to occur, it drives the $\overline{\text{RFSH}}$ line low before the $\overline{\text{MREQ}}$ ($\overline{\text{RAS}}$) strobe. This $\overline{\text{RFSH}}$ strobe forces $\overline{\text{CAS}}$ low via IC35b to accomplish the automatic $\overline{\text{CAS}}$ before $\overline{\text{RAS}}$ refresh cycle. The result is that refresh occurs trans-

PROJECT: Co-processor RAM

HOW IT WORKS

CONT.

parently to the user during the time the Z80 is internally decoding its next instruction.

Data from the Z80 data bus is buffered onto this card by IC17, an octal transceiver chip. The direction control for this device is simply derived from the Z80 \overline{RD} strobe via IC35d and its enable control is the same signal as the multiplexer select — this being active low during the time that data is moving into or out of the card.

Since each of the AAA2800 devices used is configured as a 256K by one bit memory, each chip handles one bit of the Z80 data word and the address information is fed to all the DRAM chips in parallel.

Numerous supply decoupling capacitors are used throughout the circuit (especially around the RAM chips themselves) to avoid problems with high frequency supply noise. A high value electrolytic capacitor C15 acts as a bulk energy store to reduce problems associated with remotely connected power supplies.

PARTS LIST

RESISTORS (all 0.25W 5% unless otherwise stated)

R13-18 1k0
R19 220R 0.5W 5%

CAPACITORS

C15 100 μ 6V ultramin electrolytic radial
C16-32 100n ceramic

SEMICONDUCTORS

IC14, 33 74LS74
IC15, 16, 30 74LS157
IC17 74LS245
IC18, 20 74LS30
IC19 24S10 PROM
IC21 74LS138
IC22-29 AAA280
IC31 74LS02
IC32 74LS11
IC34 74LS14
IC35 74LS00
LED1-4 green LEDs

MISCELLANEOUS

SK2 DIN41612 type C 64-pin right angle PCB mounting plug
PCB; IC sockets; tinned copper wire for through connections; M2.5 nuts and bolts for DIN connector.


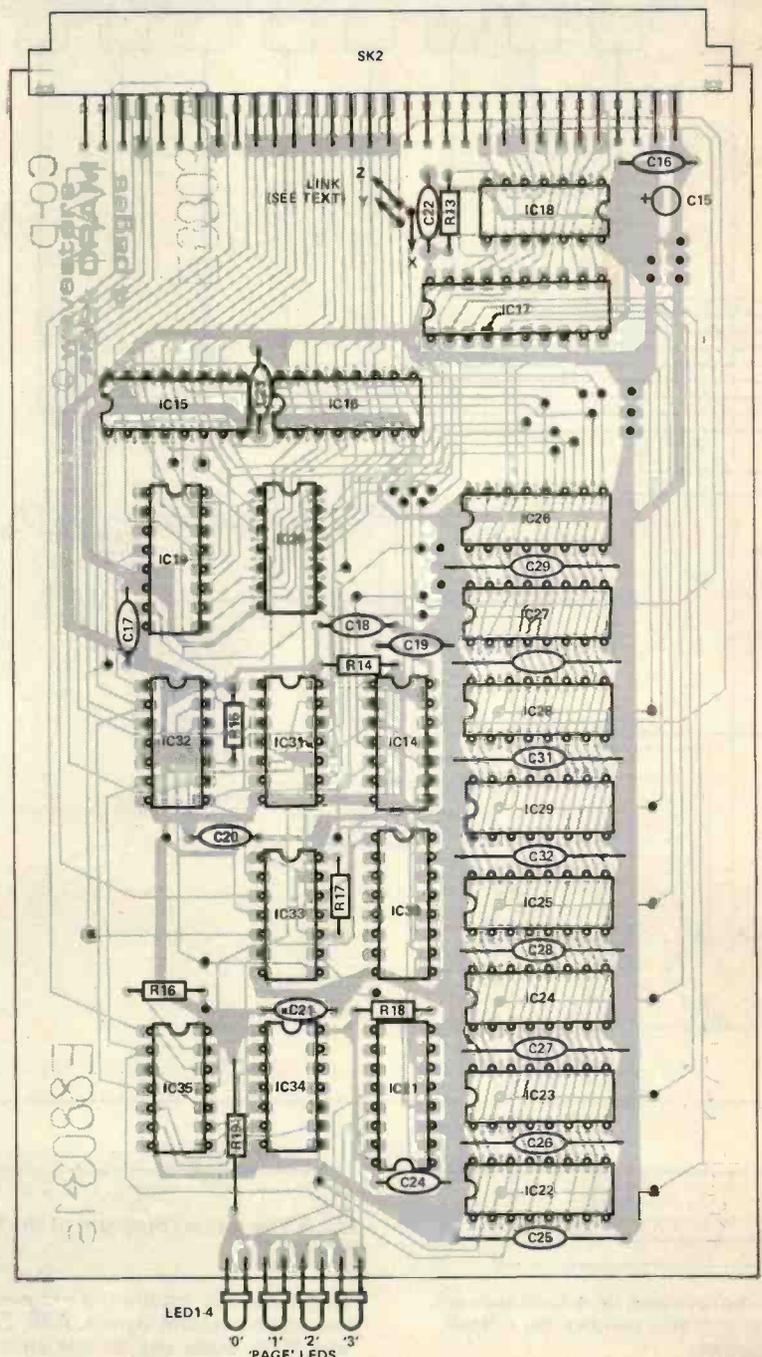


Fig. 4 The component overlay for the RAM board

ETI

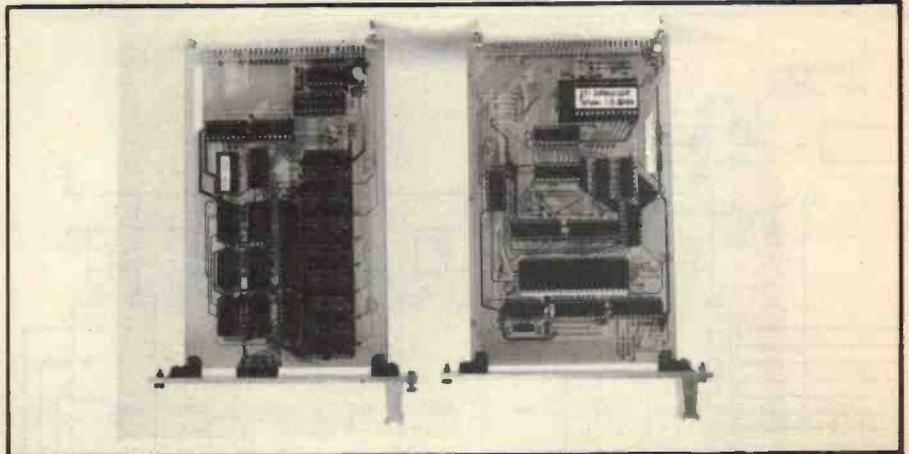

More Transistors, Thyristors, Triacs, Diodes, 74s, Switch Mode PSUs etc. All at competitive prices. Details on request.

Electro Mech Industries Limited

ACCESS or VISA welcome. Just phone your order through, we do the rest. 24hr answerphone. Tel: 0933 75827. Telex: 83147 Att. EL MEC Fax: 0665-726753 (GRP 2-3)

Unit 2, Wessex Industrial Estate, Station Lane, Witney, Oxfordshire. Telephone (0933) 75827 or 76605

IBM COMPATIBLES x VA

Super quality at sensational prices by Berron Computer Systems Inc.

EX VAT P&P	
XT COMPATIBLE	790.00 10.00
AT COMPATIBLE	1245.00 10.00
TURBO/AT EGA SYSTEM	1640.00 10.00

Full technical specs available. Range of options/peripherals available at incredibly low prices. Demonstrations can be arranged by appointment. Write/phone for brochure & price list.

MEMOTECH

MTX512 80K RAM	60.00 5.00
MTX512 Series 2 256K RAM	87.00 5.00
MC3.35" CFM Disc Upgrade	225.00 5.00

SPECIAL OFFERS
3.5" CFM Disc Upgrade. MTX512 Series 2 Computer, 12" Hi-Res Monitor, Comprehensive Software Package, Detailed Manuals. 10 x 3.5" Disquettes. All this for £399.95 inc. VAT. Delivery at £10.00 extra. Various Expansions Available.

BBC

Master 128	395.00 7.00
Compact Entry System	350.00 7.00
Compact Colour System	549.00 7.00
Archimedes Basic 305 System	799.00 7.00
Archimedes Basic 310 System	879.00 7.00

Full range of accessories - See for price list.

EMI DISC DRIVE RANGE

BBC DISC DRIVES
All supplied with Leads, Manual & Utilities Disc

Price (Ex VAT)	
5.25" DRIVES, WITHOUT POWER SUPPLY	
Single 200K drive, 40 Track D/S	£95.00
Single 400K drive, 40/80 Switchable	£112.00
Dual 400K drive, 40 Track D/S	£183.00
Dual 400K drive, 40/80 Switchable	£214.00

5.25" DRIVES, WITH POWER SUPPLY
Single 200K drive, 40 Track D/S £108.00
Single 400K drive, 40/80 Switchable £198.00
Dual 400K drive, 40/80 Switchable £235.00
Dual 400K drive, 40/80 Switchable, horizontally mounted in monitor stand (Master Version) £265.00

3.50" DRIVES, WITHOUT POWER SUPPLY
Single 400K drive, supplied in dual case, with blanking plate, to allow easy upgrade to dual drive. £95.00
Dual 400K drive £165.00

3.50" DRIVES, WITH POWER SUPPLY
Single 400K drive, as above £110.00
Dual 400K drive, as above £180.00

MONO/COLOUR MONITORS
PHILIPS 8833 COLOUR MONITOR with BBC lead £225.00

CASED/UNCASED FLOPPY DISC DRIVES

5.25" FLOPPY DISC DRIVES	Price (Ex VAT)	P and P
500K 48 TPI D/S 40T	£75.00	£2.00
1MB 96 TPI D/S 80T	£80.00	£2.00
• 500K 40 T 48 TPI Cased with PSU & Leads	£105.00	£3.00
• 1MB 80 T 96 TPI Cased with PSU & Leads	£110.00	£3.00

3.50" FLOPPY DISC DRIVES
1MB 135 TPI D/S Slimline £75.00 £1.50
• 1MB 80 T 135 TPI Cased with PSU & Leads £95.00 £3.00
• Twin 1MB 80 T 135 TPI Cased with PSU & Leads £165.00 £5.00

DISC DRIVE ACCESSORIES

DISKETTES
5.25" Double Sided/Double Density £0.90
3.50" Double Sided/Double Density £2.00
3" CF2 £3.99
3" CF2DD £5.00
Regulated PSU (state 5.25" or 3.50") £8.50 £1.50

5.25" Drive Case Takes 1 5.25" H/Height Drive £9.00 £2.00
3.50" Drive Case Takes 2 3.50" Drives £15.00 £2.00
Drive Interface Cable - Single £5.00 £0.50
Drive Interface Cable - Double £7.00 £0.50

5.25" Drive Case and PSU assembled - Takes 1 H/Height Drive £20.00 £3.00
3.50" Drive Case and PSU assembled - Takes 2 Drives £24.00 £3.00

• Available in 110 & 220V Versions

PHILIPS

High-res Green screen monitor. Model No:BM7502 £72.50
High-res Amber screen monitor. Model No:BM7522 £77.50
IBM compatible (Green) with Leads. Model No:BM7513 £95.00
Dark glass, White screen monitor. Model No:BM7542 £77.50

MITSUBISHI - Colour

Med. Res. BBC Compatible Model 1404 £232.00
Med. Res. IBM Compatible Model 1404E £264.00
Med. Res. IBM Compatible + Colour Card Model 1404EC £391.00

HANTAREX

SPECIAL OFFER HX12 HI-RES MONO GREEN £65.00
CT9000 MED RES 14" COLOUR RGB, RGB1 £179.95

MODEMS

Nightingale plus Comstar software £120.00
Answer call mini modem MD101, V21 £73.00
Miracle Technology WS2000 V21, V23 £95.00
Miracle Technology WS3000 V21, V23 AA AD £275.00
Miracle Technology WS3000 V22, V21, V22 AA AD £471.00
Miracle Technology WS3000 V22B1, V22, V21, V23 AA AD £595.00

Price (Ex VAT)
• Available in 110 & 220V Versions

LINEAR ICs

AY-3-1014A	2.75
AY-3-1015D	2.75 1691
AY-3-8470	2.00 1770
AY-3-8475	3.00 1772
AY-3-8710	3.15 1793
AY-3-9725	4.00 2793
CA3011	1.10 2797
CA3018	0.75 5502A
CA3028A	1.00 6521A
CA3030	0.65 6522A
CA3032	1.90 6800
CA3034	1.00 6802
CA3035	2.00 6803
CA3080A	2.00 6808
CA3080E	0.55 8209E
CA3085	1.30 6810
CA3088	1.00 6818
CA3088E	2.00 6820
CA3089Q	2.00 6821
CA3090A	1.10 8065A
CA3100S	2.00 6845
CA3130E	0.75 6847
CA3140T	0.70 6850
CA3181E	1.50 6852
CA3182E	5.00 6854
CA3189E	2.25 6800 P8
CA3193E	1.50 76489
CA3240E	0.90 8035
CA3260E	2.50 8060A
CA3290E	1.10 8065A
HA1366W	1.70 8098
LA3000	1.80 8131
LA4032P	2.45 8155
LA4400	3.50 8156
LA4420	2.25 8212
LA4422	3.20 8214
LA4461	3.50 8216
LC7120	3.00 8224
LC7130	3.00 8226
LC7131	3.00 8228
LM1889N	2.50 8230A
M51513L	2.00 8251A
M51515L	3.00 8253
M51521L	1.80 8255
M51525L	2.80 8256A
MC1330P	1.50 8257-5
MC1349P	1.50 8259
MC1480G	2.80 8271
MC1483R	4.80 8272
MC14897A	1.40 8274
MFC6040	0.90 8283
ML237B	2.80 8284
ML238B	4.50 8288
NE535T	1.10 8286A
NE5301N	0.80 8287
NE5534N	1.00 8288
SAB320P	3.75 8313
SN76008N	2.25 8395
SN76110N	1.20 8397
SN76115AN	1.40 8398
SN76131N	1.25 8749
SN7636N	1.65 9216
SN76600P	1.30 MC1488
SN76660N	0.80 MC1489
SN76707N	2.10 MC3242
SN76708N	3.00 MC3446
TA7204P	1.00 MC3447
TA7205AP	0.90 MC3486
TA7208P	1.30 MC3487
TCA1205	1.80 2732-450N/5P
TA7310P	1.00 2806CPU
CA3020	2.00 280ACTC
HA1387P	2.95 280ADMTA
LM1357P	1.95 280ADMA
LM1358P	1.95 280ADP
LM310N	0.40 280ASIO
LM311N	0.40 280ASIO-1
LM312N	0.35 280ASIO-2
LM313N	0.35 280ASIO-3
LM314N	0.35 280ASIO-4
LM410N	0.35 280ASIO-100

COMPUTER ICs

IN5401	0.10 79L05	0.33
IN5402	0.10 79L08	0.40
IN5403	0.12 79L12	0.33
IN5404	0.14 79L15	0.35
IN5408	0.17 79L24	0.80
CA47	0.14 79L1	0.40
OA90	0.10 7924	0.40
OA91	0.13	
TS941	0.07	

CMOS

74HC & 74HCT	4000	0.18
4001	0.18	0.18
4002	0.18	0.18
4003	0.18	0.18
4004	0.18	0.18
4005	0.18	0.18
4006	0.18	0.18
4007	0.18	0.18
4008	0.18	0.18
4009	0.18	0.18
4010	0.18	0.18
4011	0.18	0.18
4012	0.18	0.18
4013	0.18	0.18
4014	0.18	0.18
4015	0.18	0.18
4016	0.18	0.18
4017	0.18	0.18
4018	0.18	0.18
4019	0.18	0.18
4020	0.18	0.18
4021	0.18	0.18
4022	0.18	0.18
4023	0.18	0.18
4024	0.18	0.18
4025	0.18	0.18
4026	0.18	0.18
4027	0.18	0.18
4028	0.18	0.18
4029	0.18	0.18
4030	0.18	0.18
4031	0.18	0.18
4032	0.18	0.18
4033	0.18	0.18
4034	0.18	0.18
4035	0.18	0.18
4036	0.18	0.18
4037	0.18	0.18
4038	0.18	0.18
4039	0.18	0.18
4040	0.18	0.18
4041	0.18	0.18
4042	0.18	0.18
4043	0.18	0.18
4044	0.18	0.18
4045	0.18	0.18
4046	0.18	0.18
4047	0.18	0.18
4048	0.18	0.18
4049	0.18	0.18</

TECH TIPS


Door Chimes

G Landry
South Africa

This circuit is not just another two tone doorbell but is envelope modulated to give a realistic 'ding-dong' chime sound. It also has the battery saving feature of consuming no power in standby mode.

Pressing SW1 turns on Q1 to power the rest of the circuit. IC1a is a low frequency oscillator providing clock pulses to the decade counter IC2. Q2 is switched on when the counter passes zero and maintains the power for a complete cycle.

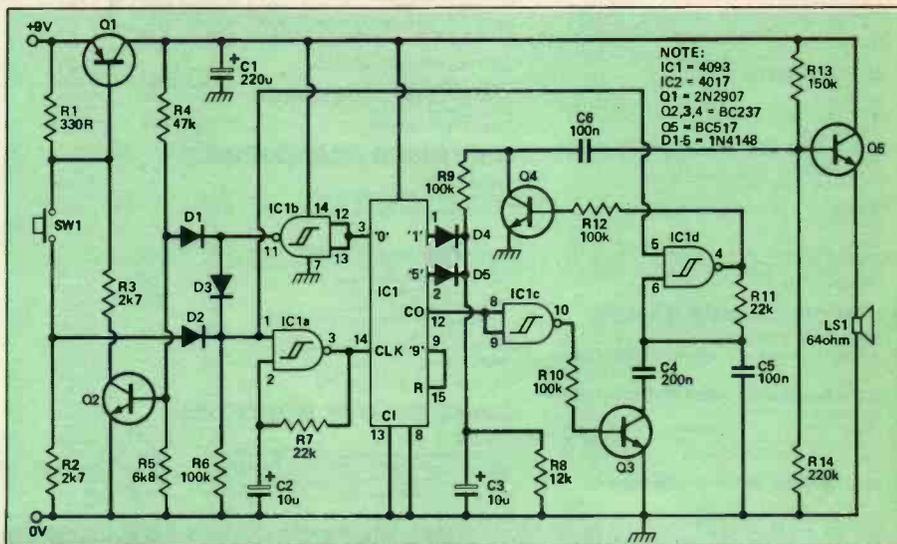The fast attack, slow decay envelope is formed by D4, C3 and R8 at the first count. Q4 modulates the output of audio oscillator IC1d which is fed to amplifier Q5 and the



loudspeaker.

At count 5 from the counter, another envelope is started from D5, C3 and R8. The carry out pin goes low and C4 is introduced in

parallel with C5 to produce the lower 'dong' sound.


At count 9, the counter is reset, Q1,2 are turned off via IC1b and the circuit is ready for another ring.

Motorcycle Regulator

D Noble
Kyle

This circuit was devised to provide regulation for the lighting circuit added to an off-road motorcycle without lights.

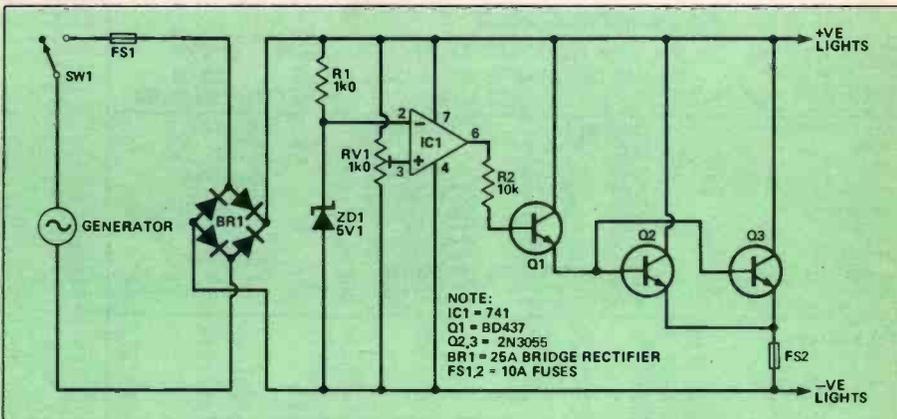The principle is straightforward. Any extra energy from the bike's generator is dumped. The 741 acts as a comparator. The output is low when the supply voltage is less than the desired value. When the supply voltage is greater than the desired output, the output of the 741 goes high and the transistors are switched on, taking




current from the generator and reducing the output voltage.

The switch on voltage is set by RV1. A bridge rectifier was chosen to provide greater power at low

revs (tickover).

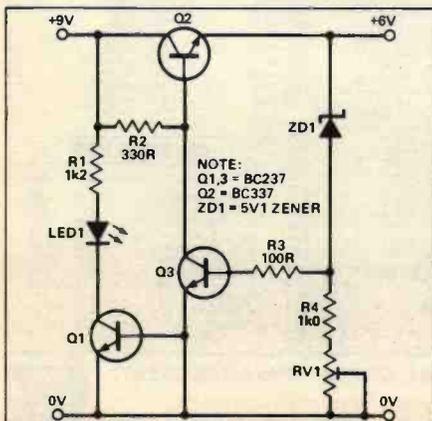The transistors are mounted on a large heatsink and the whole circuit coated with a paint to keep out water.



Battery Regulator

G Landry
South Africa

This voltage regulator circuit provides a 6V output from a 9V battery input and can maintain the output with an input as low as 6.5V. Up to 180mA can be supplied.

On application of power, Q2 switches on via R2. Q3 drives Q2 to ensure the voltage across ZD1 and the base-emitter voltages of Q2 and Q3 are constant with varying

supply voltages and output currents.

The output voltage can be trimmed between 5.7V and 6.7V with RV1 as the zener voltage is dependent on the current through it.

Q1 is switched on and lights LED1 to indicate that regulated output is available. If the supply voltage drops below 6.5V then Q1 and Q3 turn off, the LED goes out and Q2 is driven hard on connecting the output to the supply with minimum power dissipated in the idle regulator.

Printer Switch

M Pill
Nazeling


This design offers a convenient way of enabling two different printers or a printer and a plotter to be used with a computer which has only one parallel printer port. It uses tri-state buffers to switch the signals from the computer to the printer currently required.

Which printer is active at any one time is determined by the toggle switch connected to the 'enable' inputs of the buffers. With the switch in the position shown in the diagram Printer 1 will be active, as the buffer control pin is pulled low by the switch, activating the buffer outputs. The buffers feeding Printer 2 will conversely be open circuit due to the action of R2. The printer control lines are treated in a similar fashion to the data lines.

An added advantage of using buffers in this way is the driving capability they add to the printer port. The printer ports on most computers tend to be unbuffered. This can lead to corruption of data when long cables are used.

The circuit will need a 5V supply which in most instances can be obtained from the computer and fed down an unused wire in the cable.

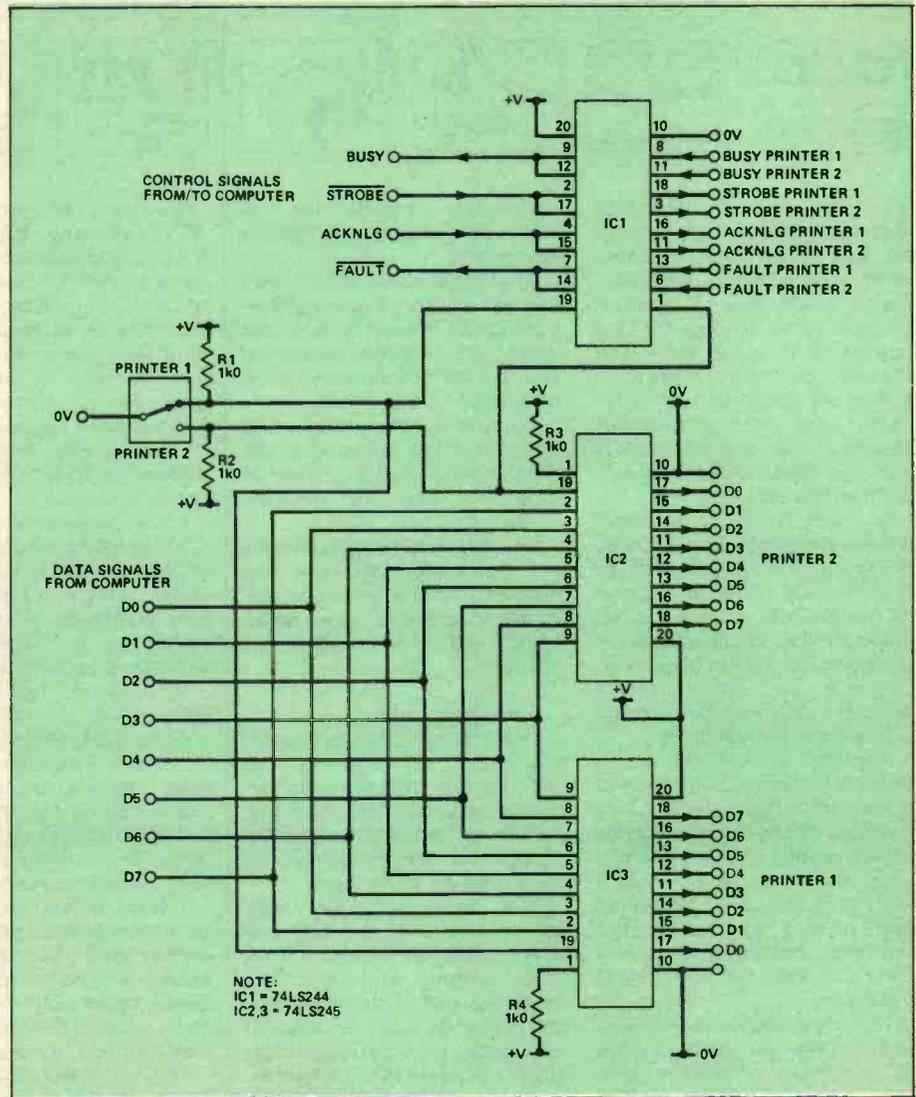The circuit could be expanded to drive more than two printers or even reversed to allow two computers to share one printer.




Soft Turn-On Dimmer

F Choy
Singapore

High current surges through the low resistance of a lamp's cold filament when power is first applied. This can be fatal to the lamp, particularly if switched-on at or near the voltage peaks.

Such a disaster, however, can be avoided by incorporating soft turn-on, that is, to let a lamp be dully lit for a few initial moments, pre-heating its filament. This circuit provides a warm-up period (determined by R7 and C2) of about one second during which analogue switch IC1b opens leaving the wiper of RV1 unconnected. The timing resistance from Q3 is therefore the full resistance of RV1, corresponding to minimum lamp intensity while C2 charges via R7.

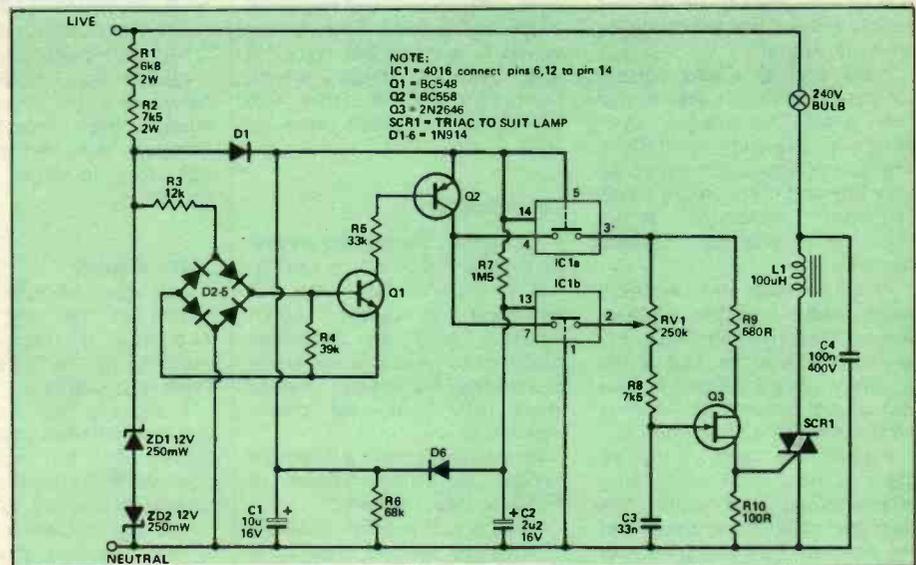After one second, C2 is charged up to the threshold of IC1b




closing it for as long as power remains on. Now the wiper of RV1 is effectively shorted to its upper end resulting in a conventional phase control lamp dimmer. IC1a is switched on by the rectified mains through D1 so the potentials on

each side of switch IC1b are equal. When power is removed, R6 discharges C2 via D6 in preparation for a new warm-up period. The rest of the circuit provides a 12V supply and synchronisation for Q3.

ETI

PLAYBACK

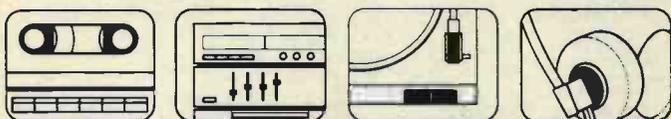

In many areas of electronics good design ideas are thought up and sometimes patented years or decades before they are really practicable. Maybe an effort is made to apply the idea commercially for a while, and the unsuccessful attempt deters further consideration of it for some time after it becomes feasible. The idea of class D audio power amplifiers may well fall into this category.

A class D power amplifier works somewhat like a series pass, switched mode voltage regulator. Of course, the output of the class D amplifier is AC instead of DC and is constantly changing, so it is not possible to optimise the design for a specific output voltage but many of the ideas are the same.

Another application which bears a striking resemblance to a class D audio amplifier is a switched mode uninterruptible power supply. In this system, a variable mark/space ratio switching signal is generated and filtered to remove the switching frequency leaving a 50Hz sine wave on the output of the supply.

The same idea can be applied to audio signals. The problem is more difficult because a wide frequency range must be accommodated. Also, a distortion level acceptable on a power supply would be far too much for an audio signal.

If the problems were solved, the resulting design would have two great advantages over currently available amplifiers. The power dissipation would be very low and there would be no crossover distortion. Why? Because there is no crossover region.

At zero output the switching stage would provide a square-wave at the switching frequency, and the mark/space ratio of this square wave would alter in time with signal excursions. There is no discontinuity at any point.

I admit the same is true of class A amplifiers but for any substantial power rating the heat generated is a problem and the noise of the cooling fan can spoil the music.

Duplication

Recently, over a pint at the local, a friend who works for a consultancy asked my views on high frequency audio amplifier design. Apparently they had been asked to design an audio

distribution amplifier for use with audio cassette duplication equipment.

The draft specification may interest or shock audiophiles, particularly those who advocate amplifier bandwidths exceeding that of a bat, or distortion figures of around 1E-6 per cent.

Apparently the duplication equipment has to work at 128 times normal running speed in order to make the process economic.

The bandwidth specified for the distribution amplifier was 400Hz to 1.6MHz, which corresponds to a single speed audio bandwidth of 3.125Hz to 12500Hz.

Low Response

I do not regard this as impressive at the high frequency end, but the low frequency performance is anomalous. This low frequency response is needed to record the low frequency cue tone used on some tapes.

The basic amplifier was required to drive ten 50R coaxial cables, terminated at both the sending end and the receiving end. This attenuates the signal to half its original amplitude, so a corresponding gain is required in the amplifier.

The normal operating signal level was specified as 4V peak to peak, with an overload margin of 26dB on this level. This corresponds to a maximum signal of 80V peak to peak, which represents 80W into the maximum combined load of 10R.

Specification

This specification may well be partly the result of a specification writer's nightmare but assuming it is realistic I would imagine that an amplifier designed to meet it would use a quasi-complementary output stage with hunky RF power transistors.

How likely is such a device to exhibit distortion figures of 0.01% or less, I wonder?

Here is just another example of how the source material is mistreated before it reaches the punter.

If this type of signal handling is rife in the music publishing industry then it would seem to make that last fractional improvements in hi-fi equipment rather academic.

Andrew Armstrong

OPEN CHANNEL



A couple of months ago (January ETI) *Open Channel* reported on the second generation of cordless telephones, codenamed CT2, currently in development. CT2 cordless phones are digital and will operate at similar frequencies to current cellular radio phones (around 900MHz).

Then I said the first CT2 phones will be similar to existing cordless phones.

I also prophesied that future CT2 cordless phones will be developed as a single base station with a number of portable handsets — rather like existing private branch exchanges without the wires.

It appears, however, that another use for CT2 cordless phones is just around the corner — called *Telepoint* in which base stations are located in public places. Anyone having a portable handset within a short range of the base station can then access the network.

Typical public places would be train stations and shopping centres and the base station areas would be known as *Phone Zones*. Users won't need cash to make a call as they will be billed direct to their home addresses.

This new telephone service (if it gets off the ground) is to be operated by Ferranti and has been developed by a company called Libera, although Libera is in fact part-owned by Ferranti.

Libera has reported that operators in France have already been found and the company is currently recruiting operators in other European countries.

But When?

Operation is hoped for by the middle of the year but this depends on appropriate licensing by the Department of Trade and Industry.

It appears that licensing of systems installed *inside* public places will be more easily obtained than licensing required for system use, say, in the street.

One big problem in the DTI's system licensing procedure is the fact that little or no standards have yet been produced for the proposed system — basically because it's such a new concept. I would hope this should present few problems to the DTI as the system appears to have found market-places both at home and abroad, long before any foreign

competition has even thought of a similar product.

This move by Ferranti into telephone operation services is interesting, particularly when viewed with two other happenings. First, the company's recent merger with American International Signal and Control.

ISC is a large supplier of defence equipment and services, so any experience Ferranti gains from telephone and communications operation will be a big plus in the defence market.

The second notable happening is Plessey's buy-out of Ferranti's semiconductor division. Plessey is reported to have paid £30m for this and will now be by far the largest chip producer in the United Kingdom. As far as Plessey is concerned this can only have advantages in terms of economy and pricing.

Six months ago Ferranti was basically a chip manufacturer and finding life very difficult. Today it is a systems supplier. It will be interesting to watch Ferranti's fortunes in the near future.

No Competition

Plessey, of course, has recently merged its telecommunications division with that of GEC to prevent self-destructive competition.

Rumours abound that Ericsson, too, wants to get in on the act to make a European telecommunications force which will further reduce competition.


If such a merger came off, there would be little to prevent the combined companies from upping prices considerably.

Although this would suit Plessey, GEC and Ericsson, it would not be agreeable to companies (like British Telecom) which as a matter of principle always prefer to foster competition in equipment procurement by inviting tenders from as many individual suppliers as possible.

Given the truth of such rumours Plessey/GEC should take care not to give too much thought to a merger with Ericsson. BT and other customers are not going to change procurement policies just for their benefit. Non-European suppliers will be asked to tender and competition may then be even fiercer.

Keith Brindley

KEYNOTES

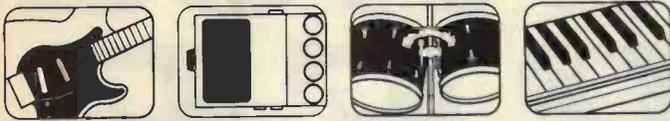

Rubbish! I am referring to the deluge of inaccurate advertising and parrot-fashion media reporting that digital audio technology drags in its turbulent wake.

While not being in quite the same league as relativity or quantum mechanics, the subtleties of analogue/digital conversion have certainly proved sufficiently complex to cause wholesale confusion.

Good CD players sound better than bad CD players, despite having identical 96dB signal to noise (S/N) specifications.

In response, the well-meaning but conditioned equipment reviewer instinctively points the finger of blame at the output sample-and-hold (if present at all) and lowpass filter (often quoted as an anti-aliasing filter, which it isn't — aliasing occurs only at ADC inputs).

In most cases, the accusing finger should instead be directed toward the DACs, which in the case of CD players rarely break 85dB.

Ignore the issue of oversampling, as found in some CD players. Oversampling is simply a technique which allows converter accuracy to be traded off against conversion speed without sacrifice in S/N performance.

Given that precision audio DACs are at best rather suspect, it is worth considering next the other end of the digital chain, the ADC. After all, what comes out cannot be any better than what went in.

In short, audio ADCs are quite definitely not yet firing on all 16 cylinders. Almost all ADCs in current audio use are based on the successive approximation (SA) technique, in which a DAC and voltage comparator placed within a digital feedback loop home in on the input voltage over a number of clock cycles.

A 16-bit SA ADC must perform 16 internal D/A conversions per sample and so cannot be expected to be as accurate as a simple DAC because higher speed generally results in lower precision.

Most 12 and 16-bit ADCs used by the audio industry are Burr-Brown SA types, notably the 16-bit PCM75. This £30 device is quoted as having a dynamic range of 90dB when used in conjunction with a perfect sample-and-hold (which Burr-Brown are unfortunately not able to provide). With a precision

discrete component error-cancelling sample-and-hold and with a lot of care, feeding and loving attention, the PCM75 can reach down as far as 88dB — on a lab bench, when the wind is blowing in the right direction.

In the harsher environment of a commercial production line a figure of 80dB is more typical.

SA is not the only viable approach to A/D conversion but other approaches currently offer little or no advantage. For example, Sony's 16-bit CX20018 dual ADC employs a dual-ramp integration conversion process to achieve a respectable 86dB according to the data sheet but what gives the game away is the fact that Sony use the Burr-Brown converters in their own professional recording products.

Most of the inaccuracies of converters are attributable to resistor ladder tolerances (and thermal drift), settling times, stray capacitance and ground loops. A hidden and easily overlooked source of error in precision converter circuits is actually the stability of the clock. A timing jitter of one part in 65,536 can correspond to the loss of as much as one bit of precision in a 16-bit system.

A well designed crystal oscillator is more stable than this but what about glitches and variable loading effects in the intermediary logic and on the digital supply rails? This source of error applies equally to DACs and ADCs.

Purveyors of 16-bit audio equipment are able to perpetuate their 96dB mythology only by dint of the considerable difficulties involved in accurately measuring S/N beyond about 80dB.

In practice the measured performance depends as much on the measurement configuration as it does on the quality of the converter circuit itself, so it is hard to categorically prove or disprove claims.

Reading a professional audio magazine recently, I happened across an advertisement from TC Electronic of Denmark for a 2U rack-mount delay/effects processor sporting '18-bit resolution, 1MHz sampling rate' at 'a quarter of the price of any truly competitive unit' to boot. Changing the subject, do you see that flock of pigs up there?

Bruno Hewitt

TEST INSTRUMENTS

UK's LARGEST IN-STOCK RANGE

DIGITAL MULTIMETERS

KT305 (*) 26 range plus Hie test 10A AC/DC 20meg buzz 0.5% (R)	£33.00	All 3 1/2 Digit LCD.
KT10 (*) 31 range incl. 5 range CAP 10A AC/DC 20meg buzz 0.5% (R)	£33.00	Case £2.17
KT5005 (S) 4 1/2 digit 26 range plus Hie 10A AC/DC 20meg 0.07% (PB)	£83.00	*4 1/2 Digit.
KD508 (T) 15 range AC/DC volts 0.2A DC 2 meg (S)	£19.50	*With Case.
KD578 (T) 20 range 10A AC/DC auto range display hold 0.8% (R)	£33.50	(R) = Rotary
6010 (T) 28 range 10A AC/DC 20 meg 0.25% (PB)	£39.50	Pb = Push Button
7030 (T) 0.1% version of 6010	£52.13	S = Slide
5010EC (T) 34 range incl. CAP Hie temp etc 0.25% (R)	£53.00	
M3530 (T) 28 range incl. 5 range CAP plus Hie 10A AC/DC 0.5% (R)	£57.00	
M3800 (T) 30 range plus Hie 20A AC/DC 20 meg 0.5% (R)	£35.00	
M3650 (T) 30 range incl. Hie CAP freq. count. 20A AC/DC 0.3% (R)	£77.00	
M3800 (T) 30 range + Hie 20A AC/DC 20meg 0.5% (R)	£36.50	
M4630 (T) 30 Range + CAP + Hie + Databold 20A AC/DC 20meg 0.05% (R)	£41.00	
HC5010 (S) 31 Range 10A AC/DC 20meg 0.25% (R)	£14.95	
HC779 (S) 20 Range 10A AC/DC Auto range + Hie + mem/hold 0.5% (R)	£21.50	
6511 (S) Wallet auto range		
DM205 (S) 14 range 10A DC Hie test display hold 0.5% (R)		

SCOPES (*with probes)

HAMEG - all with component testers	£314.00	GENERAL OST5M	£146.00
*203/6 Dual 20MHz	£698.00	5MHz Bench portable	
*806 Dual 80MHz, 3 chan delay etc	£527.00	HITACHI V212	£330.00
*205/2 Dual 20MHz + digital store	£575.00	Dual 20MHz	
*604 Dual 60MHz + sweep delay	£195.00	+ HUNG CHANG 615 Dual 15MHz	£399.00
THANOR SC110A Batt 10MHz		Batt/ Mains	
Portable			
CROTECH 3031 20MHz Single track + comp.	£199.00		

Also stockists for Hitachi, Hung Chang and Gratech. Scope Add ons. Storage TB201, BCH adaptor DM 358. Logic analysers LA160. Ask for prices and details.

POCKET INSTRUMENTS

*KT905 8 Range Digital Cap Meter	£34.74		
*555 20Hz to 150KHz Audio Generator	£47.50		
2030ET 27 Range multimeter 10A AC/DC + Hie + Cap	£37.90		
5050E-41 Range FET meter 0.1 μA 1000 meg etc	£28.65		
*102BZ 19 Range Meter 20K/V, 10A DC Buzzer	£10.39		
07 20 MHz Logic Probe. TTL, cmos	£9.52		
625 50 MHz Logic Probe + Logic Pulse 0.5/400Hz	£22.95		
X1/X10 Scope/Inst. Probe 250 MHz with access	£11.50		
*PFm 200A 200MHz LED 8 digit Freq counter	£75.00		
KDm6 1.5MHz to 250MHz TR Dipmeter	£43.04		
*ST300 D/300 AMPS AC 5 range 0/600V AC 4 ranges	£32.83	*TC200 Digital LCD	£85.00
10K Ohm clamp meter	£65.00	CAP/RES/IND	
*501 Electronic insulation tester 500V DC 100 meg		625 50 MHz Logic probe	£22.95
*6060 Digital power meter 2KW/4KW true power	£63.04	plus logic pulser	
10A AC/DC volts LCD	£99.50	*519C Digital LCD	£57.00
*TH301 Digital temperature meter with probe LCD	£14.17	CAP/RESIS/Hie	
*HC201 19 range, analogue meter, 12A AC/DC			

MEASURING INSTRUMENTS SECURITY COMMUNICATIONS PUBLIC ADDRESS TOOLS AUDIO/TV/VIDEO/COMPUTER ACCESSORIES - SEE CATALOGUE

BENCH DIGITAL MULTIMETERS

3 1/2 digit LCD 100 μV AC/DC 100mA 100m OHM con buzzer battery operated 20A AC/DC	£89.00
3225 0.25% basic	£119.00
3210 True RMS Version 0.1%	
Tm355 3 1/2 digit LED 10A AC/DC 0.25% (Batt operated)	£85.00
Tm351 LCD 0.1% £115.00: Tm 356 LCD 0.25% £95.00	
8035 LED 20A AC/DC 0.1%	£139.00
8035T LED 20A AC/DC True RMS	£179.00
8145 4 1/2 digit LED 20A AC/DC 0.05%	£169.00



COUNTERS & TIMERS

ALL BENCH MODELS	
FREQUENCY COUNTERS	
MET100 220/240V AC 8 digit	£99.00
MET600 LED 0.1Hz	£126.00
MET1000 RESOLUTION	£175.00
MET1500 5mv min Sensitivity	£199.00
TF200 8 digit LCD batt 200 MHz	£175.00
COUNTER/TIMERS 8 DIGIT LED	
APPOLLO 10 STANDARD MODEL	£219.00
APPOLLO 100 PLUS DISPLAY HOLD RPM STOP WATCH ETC.	£285.00

DC POWER SUPPLIES

240V AC input. Stabilised variable output voltages. Direct meter reading volts and amps.	
243 0/24 volts 0/3 amps DC	£50.39
245 0/24 volts 0/5 amps DC	£64.50
154 5/15 volts 0/4 amps DC	£36.50
0/30V 0/3A DC twin meter	£66.00
THURLEY, GW. THANOR DIGITAL PSU's AVAILABLE	

SIGNAL SOURCES

AC220/240 V operations	
FUNCTION SINE/SQ/TRIANGLE/TTL	£110.00
Jupiter 500 0.1Hz to 500KHz	£110.00
TG101 0.02Hz to 200KHz	£160.00
TG102 0.2Hz to 2MHz	£149.00
Jupiter 2000 0.2Hz to 2MHz	

TV-VIDEO

PAL VHF/UHF 5.5/6/6.5MHz Fm SOUND RGB 2 SYN a/p's Colour - B/W etc.	£199.00
DIGITAL DISPLAY (0.2Hz - 2MHz)	£165.00
20 4 digit 0.2Hz - 2MHz Function	£215.00
8016D 6 digit 0.2Hz - 2MHz Function	£250.00
8019 5 digit AM/FM Function	
SWEEP FUNCTION (0.2Hz - 2MHz)	£190.00
8016S Fm mod 6 types of wave-form	
8019 5 digit 0.2MHz - 2MHz AM/FM Function	£250.00

PLEASE ADD VAT (UK ONLY)

CATALOGUES WITH DISCOUNT VOUCHERS

Send 12 x 19 SAE (E1 Stamp UK) TRADE ■ EDUCATION ■ EXPORT SUPPLIED

ORDER BY POST OR PHONE • OPEN 6 DAYS A WEEK FOR CALLERS

HENRY'S

404 EDGWARE ROAD LONDON W2 1ED Tel: 01-724 0323

Account Enquiries 01-258 1831. Telex 298102 Trans G Also at 301 Edgware Road, W2. Tel: 01-724 3564

2 issues FREE

When you take out a subscription to any of these magazines

	EUROPE	MIDDLE EAST	FAR EAST	REST OF THE WORLD
A&B Computing	£27.30	£27.60	£31.10	£28.30
Aeromodeller	£27.00	£27.20	£29.00	£27.50
Citizens Band	£20.10	£20.30	£21.80	£20.50
Clocks	£32.40	£32.60	£34.70	£33.00
Commodore Disk User	£18.00	£18.20	£19.30	£18.40
Disk User	£21.60	£21.70	£23.20	£22.00
Electronics Digest	£12.90	£13.00	£13.70	£13.10
Electronics Today International	£21.00	£21.20	£22.80	£21.50
Ham Radio Today	£20.10	£20.30	£22.00	£20.60
Military Modelling	£22.40	£22.60	£25.20	£23.10
Model Boats	£20.00	£20.10	£21.80	£20.40
Model Engineer	£35.40	£35.70	£39.00	£36.30
Photography	£22.00	£22.30	£25.00	£22.80
Photoplay	£16.70	£16.90	£18.70	£17.20
Popular Crafts	£21.40	£21.60	£23.60	£22.00
Radio Control Model Cars	£21.10	£21.30	£23.10	£21.60
Radio Control Boat Modeller	£10.00	£10.20	£11.10	£10.30
RCM&E	£20.40	£20.60	£22.90	£21.00
Radio Control Scale Aircraft Quarterly	£11.10	£11.20	£12.00	£11.30
Radio Modeller	£20.00	£20.20	£22.40	£20.60
Sea Classic International	£10.70	£10.80	£12.00	£11.00
Scale Models International	£19.60	£19.80	£21.50	£20.10
Video Today	£20.20	£20.40	£22.30	£20.70
Which Video?	£19.40	£19.50	£21.20	£19.80
Woodworker	£22.80	£23.00	£25.70	£23.50
Your Commodore	£22.00	£22.30	£25.20	£22.80
Model Railways	£19.10	£19.30	£21.50	£19.70
Practical Wargamer	£7.10	£7.20	£8.00	£7.40

The Above Offer Applies to Overseas Subscriptions Only

This offer is also open to existing subscribers who may wish to extend their current subscriptions.

Please commence my subscription(s) To..... with the..... Issue
 I enclose my cheque/ money order for £..... made payable to Argus Specialist Publications Ltd.
 or debit £..... from my Access/Barclaycard No.

valid from..... to..... Signature.....
 Name.....
 Address.....




Send this form with your remittance to:


**INFONET LTD. (S.O. 88) 5 River Park Estate,
 Berkhamsted, Herts. HP4 1HL.**




PCB FOIL PATTERNS

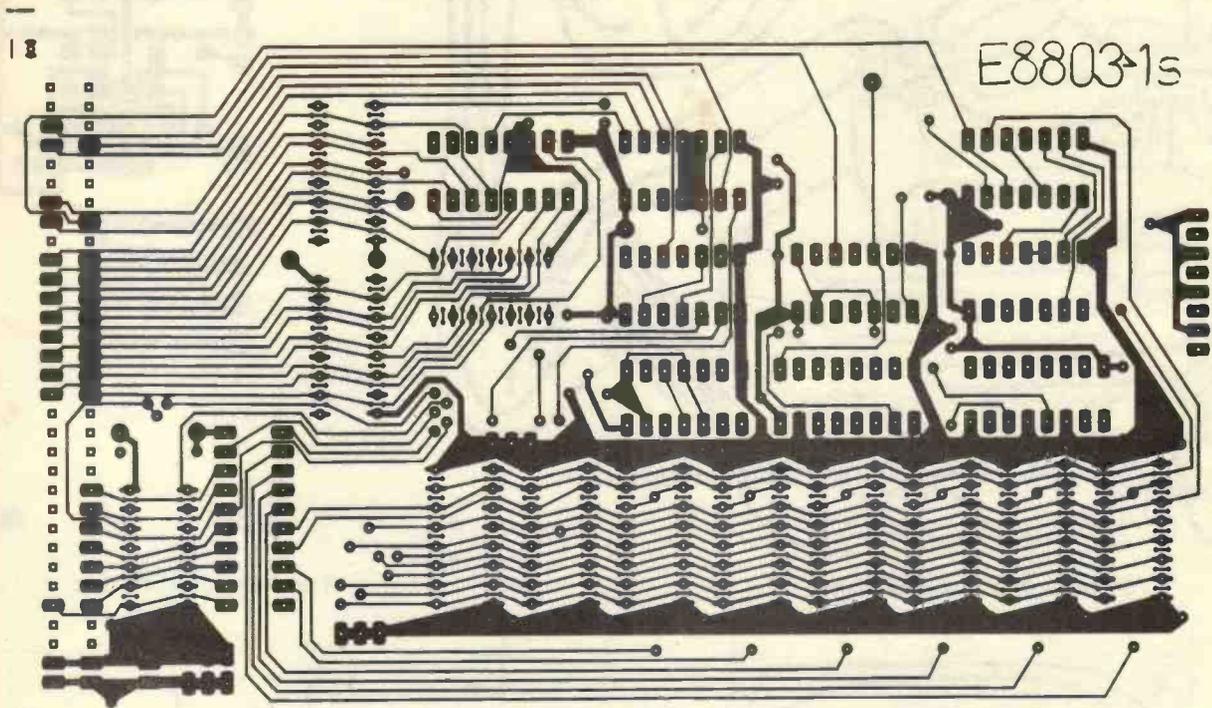

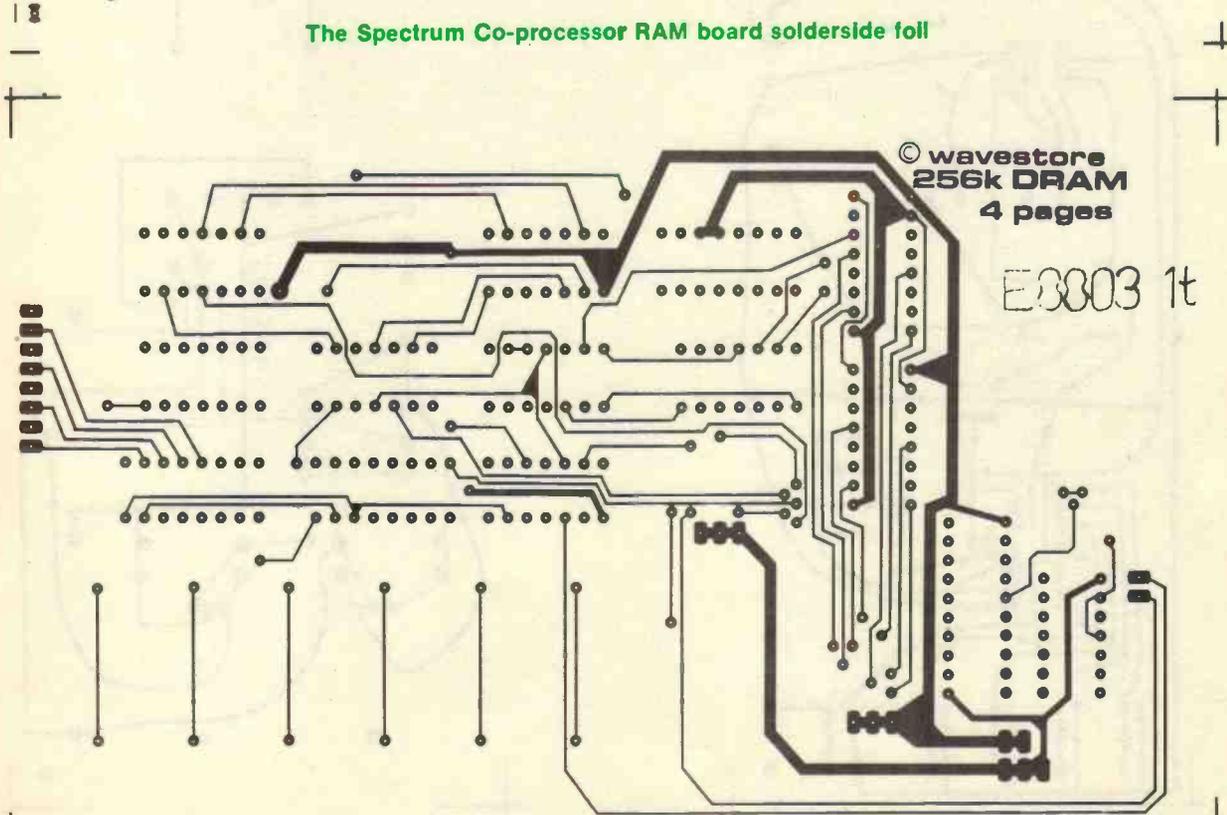
The Spectrum Co-processor RAM board solderside foil



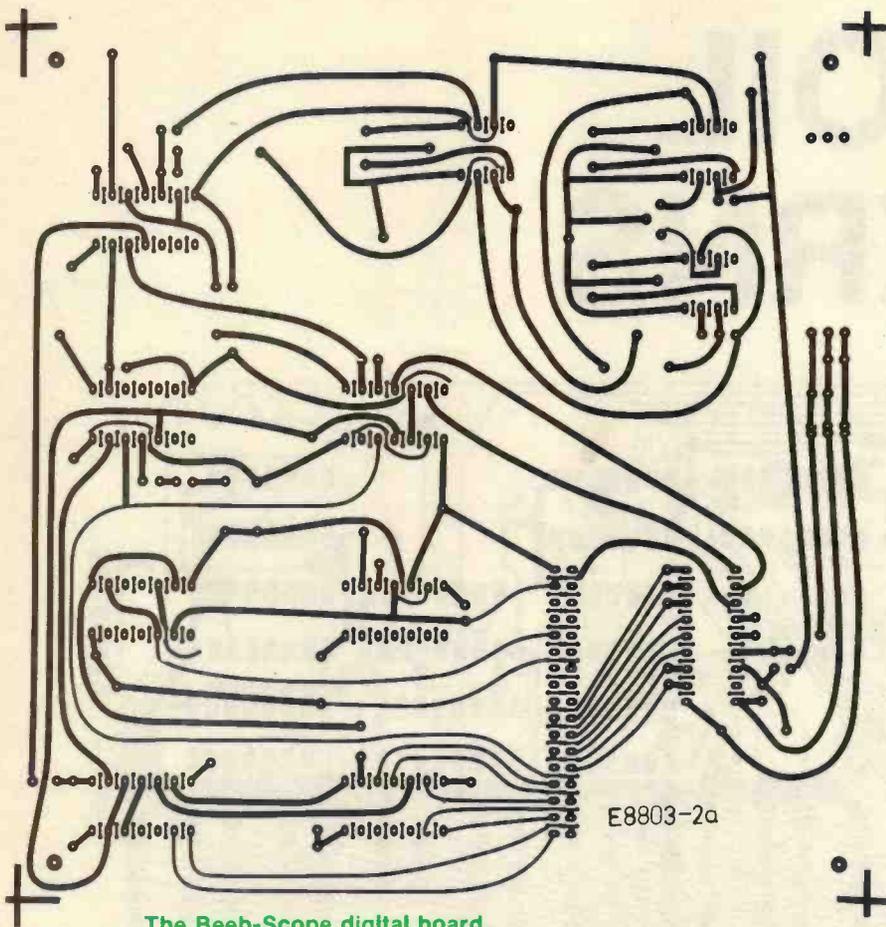
The Spectrum Co-processor RAM board topside foil




The Beeb-Scope digital board

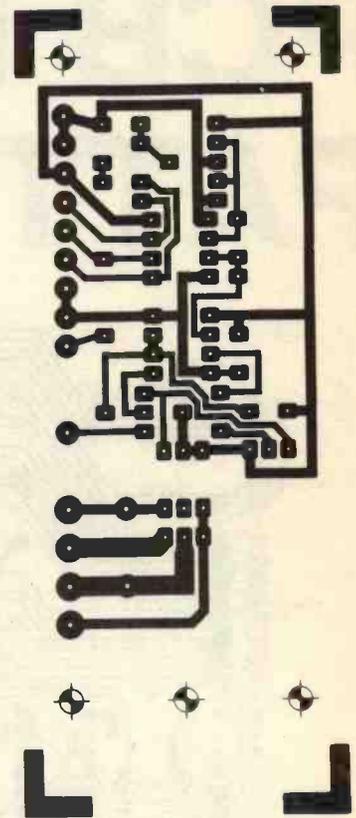


The Jumping Jack Flash foil pattern

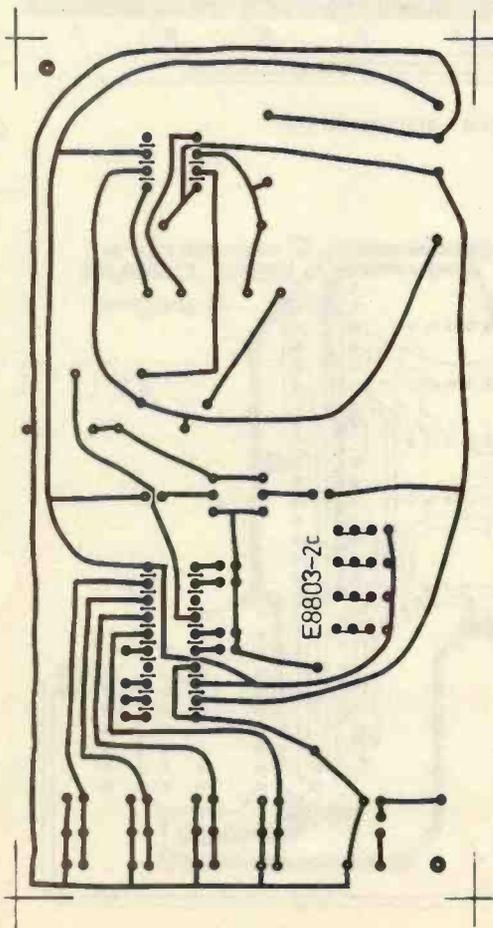

The Beeb-Scope analogue board

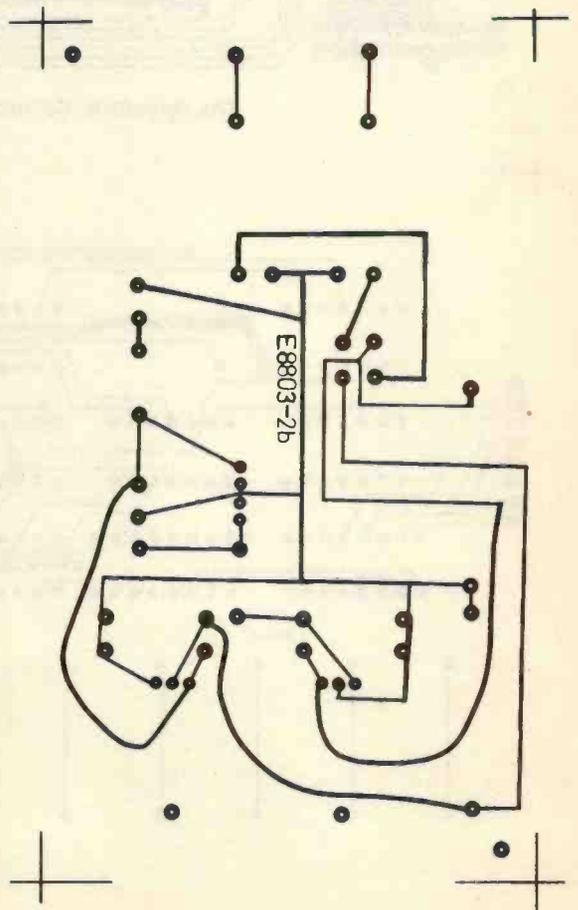

The Beeb-Scope power supply board

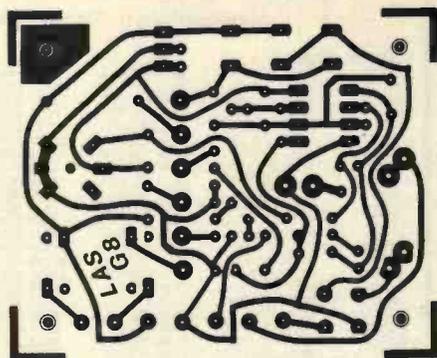

The Gas Alert PCB foil

ETI PCB SERVICE

E8803-1 Co-processor RAM board N	£13.10
E8803-2 Beeb-Scope (3 bds) O	£15.80
E8803-3 Jumping Jack Flash E	£3.23

TO: **ETI READERS' SERVICES DEPARTMENT**
Argus Specialist Publications Ltd,
9 Hall Road, Hemel Hempstead,
Herts HP2 7BH

Please supply:

No. required per type	Board reference number	Price letter	Price each £	Total for board type £
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p

POSTAGE & PACKING £ 0.75p

TOTAL ENCLOSED £ . p

ORDER TO BE SENT TO: (BLOCK CAPS PLEASE)

Name

Address

Postcode

(Make cheques payable to ASP Ltd)
ACCESS and VISA credit card orders can be taken on (0442) 41221
 (office hours only).



Telephone Alarm (July 1987)

In the component overlay (Fig.2) IC1 and IC2 should be swapped. The capacitor to the right of IC1,2 is C1 and the inductor between them is L1. The unmarked resistor to the left of L1 should be a wire link. In the circuit diagram (Fig.1b) IC4a,b should be AND gates. IC5 should be NAND gates. The parts list is correct.

Kappellmeisters (July 1987)

The position of the speaker port in the front panel was omitted from Fig.2. This should be a 7/4x4 1/2 in ellipse centred across the panel with its top edge 2 1/2 in below the panel top.

Knight Raider (August 1987)

In Fig.1(a) pins 4 and 5 of IC1 are swapped. IC2-3 show the correct pin-out.

Car Alarm (August 1987)

In Fig. 1 Q7 is not numbered and its emitter is shown unconnected. This connects to earth. The transistors in the parts list went a little awry. Q2-6 are BC237 and Q7 is a TIP31.

Boiler Controller (September 1987)

In Fig. 2 (a) the primary of T2 is shown connected to Earth. This should be neutral. In Fig. 2(b) one of the bridge rectifier diodes, D6-9, is shown the wrong way around. This is correctly shown in Fig. 5.

EEG Monitor (September 1987)

In Fig.3a the pins of IC1 connected to the power rails are shown swapped around. In Fig.4a R7 is unlabelled and is between C3 and C6. In Fig.5 C20 should be £10 and R18 is unlabelled. It lies between R17 and R19.

ETI Concept (October 1987)

The Power Board parts list wrongly lists R6 as 270R. This should be 270k. Also, note that the power board's 0V rail must *not* be connected to Earth or the 0V rail of the CPU board.

Printer Buffer (November 1987)

The software for the EPROM had three errors listed. The byte at 039A should read 20, at 039B 14 and at 0492 30. All numbers are in Hex.

Dream Machine (December 1987)

The transistors used in this project are ST1702. BC108s can be substituted.

RGB Auto-Dissolve (January 1988)

In Fig. 5 there are marked two D6's. The right hand one should be D5 (they are both 1N4148's anyway). In the text the reference to zener diode D5 should read zener diode ZD1.

PASSIVE INFRA-RED ALARM

(January 1988)
 Fig. 2(a) shows the base of Q1 connected to ground and to R14. It should be connected only to R14.

ELECTRONICS TODAY INTERNATIONAL CLASSIFIED

Lineage:
44p (VAT excl) per word (minimum 15 words)
Semi Display: (minimum 2 cms)
£12.20 per single column centimetre + VAT

Ring for information on series bookings/discounts
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 292

Send your requirements to:
Julie Capstick
ETI Class. Dept.,
ASP Ltd.,
1 Golden Square,
London W1.

ALARMS

ALARMS

FREE BOOKLET

on

BURGLAR ALARMS

with

LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY

051-523 8440

AD ELECTRONICS

217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



KITS



I-TRON'S

TOP SELLING
KITS



- BUG-87** Matchbox sized surveillance transmitter - can be received by any FM/VHS radio..... £4.95
- ROBO-VOX** Instantly transforms your voice into Dalek/Robot type also amazing feedback/sound effects possible. £11.95
- ROBOT CIRCULAR** Unique radio controlled robot - can also be converted to control via computer..... £16.95
- EDU-SCOPE** Build your own oscilloscope with solid state display..... £39.99
- EDU-SCOPE CASEKIT**..... £11.99
- THBRAMIN MUSIC GENERATOR** An electronic device based on an ancient legendary mystical instrument..... £12.75

Please add £0.75 per order for P&P. For FREE Datapack on all our Products /Kits send SAE. Cheques/PO's payable to:-
IMAGINA-TRONICS
Aberdeen House, The Street, Charlwood,
Surrey. RH6 ODS

SURVEILLANCE

ESKAN ELECTRONICS

(MANUFACTURERS AND SUPPLIERS OF SURVEILLANCE AND AUDIO EQUIPMENT)

MICRO BUG

SK1 Miniature Transmitter 20mm x 47mm x 20mm, extremely sensitive. Operates from 1.5v battery, elegant metal box included.

Ready built + tested only. £29.50
Kit Form £24.90

EXTRA MINIATURE TRANSMITTER

EK2 25mm x 30mm x 9mm
Ready built + tested £49.00
Kit Form £37.95

HIGH POWER FM RADIO TRANSMITTER

EK65, 65W adjustable frequency
Mains operated...£650 + £35 p&p
(Operation in the UK illegal without licence).

AUTOMATIC TELEPHONE MONITOR

SK19 ready built + tested £34.50
Kit Form £29.95

Many other surveillance equipment available. Send large S.A.E. for catalogue.

SOUND TO LIGHT UNIT

SK72 separate sensitivity, bass, treble and mid-range frequency controls, designed and manufactured to highest professional standard.

Ready Built.....£39.95 p&p £3.50
Kit Form £21.95

Casing £11.95
SK70 sound to light control unit
Kit Form £14.95

Send Cheque or P.O. payable to:

ESKAN ELECTRONICS

172 Caledonian Road,
London N1 0SG.

Tel: 01 278 1768



Trade and Export Enquiries Welcome

- Components
- Equipment
- Kits
- Surveillance
- PCB's

If you can supply products or services to ETI readers - contact Julie Capstick on 01-437 0626 Ext. 291

COMPONENTS

PROMS - EPROMS - PALS ANY PROGRAMMABLE IC SUPPLIED OR BLOWN

Typical prices (excluding VAT) (Data Entry P&P extra)
2716 £4.20 2732 £3.85
2764 £2.85 27128 £4.40
BIPOLAR PROMS from £1.35
e.g. 82S123, 18S030, 74S288
PALS, PLDs etc. from £3.26
e.g. 82S153, 16L8, EP310
Full design and prototyping service. Any quantity programmed - SAE or phone for details.
P.L.S., 80 Central Road,
Worcester Park, Surrey, KT4 8HU
Phone: 01-330 6540

S.H. COMPONENTS presents 18 pages of very competitively priced semi-conductors, switches, Opto Electronics, etc. Send 50p to: 17 Beeley Road, Grimsby, S. Humberside.

BSR P207 SEMI-AUTO TURNTABLE

Complete with SC12M ceramic cartridge 240V
AC FEW ONLY AT £25 + £2.50 P&P
SP45 3" 40 Watt 8 ohm Baby Boomer
Superb value at only £5.60 + £1.50 P&P
ALTAI SOLDER PUMP £4.50 post free
BAGS OF ASSORTED COMPONENTS
£2.10 each
SEND FOR FREE LISTS.
STRACHAN ELECTRONICS (ET)
9 CROALL PLACE, EDINBURGH EH7 4LT

FREE RESISTORS plus hundreds of low price-manufacturers full spec. components, send £1.50 cheque for samples and lists or 10" x 4" s.a.e. for lists only. Dept. (E), D&M Component Supply Service, 2 Glentworth Avenue, Whitmore Park, Coventry, W. Midlands CV6 2HW.

ELECTRONIC KITS—For those Winter evenings. SAE for details: COVE ELECTRONICS, 7 St. Anne's Avenue, Southbourne, Bournemouth, Dorset BH6 3JR.

MICRO TRANSMITTER KIT, 500m Range, tunable 88-115MHz, sensitive microphone, £3.95. Cheques/PO's to Quantek Ltd., (ETI), 267 Rednal Road, Kings Norton, Birmingham B38 8EB.

FOR SALE

2 TRI-TANKS with chemicals. Hardly used. Must go together to make a complete process for PCB manufacture. Tel: 0327 72994.

TELECOMMUNICATIONS ENGINEERS

Thamesway - one of the fastest growing operating districts within British Telecom, is looking for Telecommunications Engineers in Reading, Basingstoke, Aldershot, Guildford, Slough, Bracknell and surrounding areas.

We are looking for people who, ideally, have electronic/electrical experience or who have an academic background, preferably in maths and science subjects. There are also vacancies for people without qualifications who can demonstrate a practical aptitude as training will be provided.

You must be at least 18 years of age, in good health and hold a current driving licence.

Start salary will range from £5,649-£8,806 depending on age and experience. We offer the first class benefits of a large progressive company, including excellent training, a good pension scheme and every opportunity for advancement.

To apply, just complete the coupon and return it to:

**The Engineering Recruitment Manager
British Telecom DP112
Thamesway District
49 Friar Street
Reading RG1 1BA**

Name _____
 Tel. No. Day _____ Evening _____
 Address _____

 Date of birth _____
 Type of Driving Licence: HGV/CAR/NONE*
 Currently Employed Yes/No*
 When could you start work _____
*Delete which is not applicable
 Qualifications: GCE; City & Guilds; BTEC; HNC etc.)

 Job History (last 4 jobs)
 From: To: Employer: Type of Work: Reason for Leaving:

 Please state why you wish to be considered for a Technical Post:

British Telecommunications plc is an Equal Opportunities Employer. Applications are welcome from Male and Female applicants.

British
TELECOM
It's you we answer to

PCB'S

Labcenter
electronics
PC-B £80

At last, an affordable PCB design tool for your Amstrad PC. Plotting service available. Send SAE for further details, or £2 for demo disk.

Labcenter Electronics
14 Marriner's Drive,
Bradford, BD9 4JT.
Tel: 0274 542868

DESIGN YOUR OWN PCBs

With our powerful drafting utility Available for Amstrad CPC464/664/6128 Double sided boards up to 25 x 25 inch Powerful screen editing facilities Various track widths and pad sizes V1.1 £17.99 Tape £19.99 Disc V2.0 many improvements £29.99 Disc CADsoft System, 18 Lay Crescent, Astley, Tyldesley, Manchester M27 7BD

PRINTED CIRCUIT BOARDS At very competitive rates: 4 pence per square centimetre (less for orders of 10 plus) 1 offs, 100 offs - send artwork (1:1, single sided) or drawings/enquiries. Also artwork carried out. Watling Wires PCB Production, 52 Watling Street, Nuneaton, Warwickshire, CV11 6JL. Telephone (0203) 382296.

PLANS & DESIGNS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage testas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, String Works, Bye St., Ledbury HR8 2AA.

SWITCHES

VOICE/SOUND ACTIVATED SWITCHES easy to follow diagrams and uses only £1.00. Components and P.C.B's available: **Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.**

COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on 06267 79398

REF: ETI/3/88

NAME _____

- City & Guilds Exam 271
- Radio Amateur Licence
- Micro-processor
- Introduction to Television

Radio & Telecommunications Correspondence School, 12, Moor View Drive, Teignmouth, Devon. TQ14 9UN.

ELECTRONICS TECHNICIANS

Updating Courses
London Electronics College, (Dept ETI), 20 Penywern Road, London SW5 9SU. 01-373 8721.

MISCELLANEOUS

HEATHKIT U.K. Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

Copy Deadline for May issue. 1st March.

TMS320 Starter kit incorporating TMS32020, 16K Eprom RS232. Prices from under £300. For further details send S.A.E. to Melek Circuits, 18 Kincardine Drive, Bletchley, Milton Keynes MK3 7PG.

SECURITY

Modules
Systems
Accessories

SAVE £££££'s
BY INSTALLING YOURSELF

MINIATURE PASSIVE INFRARED SENSOR RP33

Size only 80x60x40mm. Detects intruders up to 12 metres away.



- 12 metre detection range.
- Size only 80x60x40mm.
- 24 Detection zones.
- Wide 85° coverage.
- Switchable LED indicator.

This advanced new intrusion detector operates by detecting the body heat of an intruder moving within the detection field. The use of a dual element pyroelectric sensor means that changes in ambient temperature are ignored, thus providing a stable and reliable performance. Easily installed in a room or hallway, the unit will provide effective detection of any intrusion. Operating from a 12V supply and consuming only 15mA, it is ideal for use with the CA 1352, CA 1250 or any equivalent high quality control unit. Supplied with full instructions, its performance compares with detectors costing more than twice the price.

ONLY £23.95
Plus VAT

CA 1250 LOW COST ALARM CONTROL MODULE



This tried and tested control unit represents the finest value for money in control systems, providing the following features:

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm grill lamp and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility.

Price **£19.95 + VAT**

DP 3570 LIGHTING CONTROLLER

This versatile module provides timed switching of loads up to 3A for pre-set times between 10 secs and 5 mins, the timed period being triggered by the opening or closing of an external loop or switch. The built-in 12V 250mA power supply is available for operating external sensors. Suitable plastic enclosure £2.85 + VAT.



Only **£13.95 + VAT**

FL 500 QUARTZ HALOGEN FLOOD LIGHT



Whilst intended for security lighting applications, this unit is suitable for lighting patios, pathways and gardens etc. Supplied complete with 500W lamp, Protective grill, £1.95 + VAT.

Only **£14.95 + VAT**

IR 1470 - 50ft. INFRARED BEAM SYSTEM

Consists of a separate transmitter & receiver, the system provides an invisible modulated beam which when broken operates the built-in relay. For use with security systems, but also ideal for photographic purposes and industrial applications. Size: 80x50x35mm.

Only **£25.81 + VAT**



CA 1352 ADVANCED CONTROL UNIT that's simple to install and operate.



- Fully automatic siren re-set.
- Audible entry/exit warning
- Alarm Sounded memory
- 2 separate loop inputs
- 24hr circuits.
- Built-in electronic siren.
- Easily installed, full instructions supplied.

The latest control panel provides effective and reliable control for all types of security installations. Its advanced circuitry checks the loop circuits every time it is switched on, preventing incorrect operation. Using a simple 'on/off' key switch, it is easily operated by all members of the family. In addition it provides 24 hr. personal attack protection. Housed in a steel case, it is supplied with full operating instructions.

Only **£44.95 + VAT** Available in kit form with fully-built electronics, £39.95 + VAT.

HW 1250 - ATTRACTIVE HOUSING plus HARDWARE FOR CA 1250

An attractive steel case designed to house the Control Unit CA 1250 together with the appropriate LED indicators and key switch (available separately). Supplied with the necessary pillars, fixings, and punched front panel, the unit is given a professional appearance by the adhesive silk screened label. Size: 200x180x70mm.

Only **£9.50 + VAT**



Full Technical Advisory Service

US 5063 DIGITAL ULTRASONIC DETECTOR

• 3 levels of discrimination against false alarms • Crystal control for greater stability • Adjustable range up to 25ft

Only **£13.95 + VAT**



ULTRASONIC MODULE ENCLOSURE

Suitable steel enclosure for housing the US 5063 supplied with the necessary mounting pillars and fixings.

Only **£2.95 + VAT**

RISCOMP LIMITED

Dept ET13
51 Poppy Road
Princes Risborough
BUCKS
HP17 9DB

The Security Specialist

ORDER BY MAIL OR TELEPHONE Tel: (084 44) 6326

Mon to Fri: 9 am - 5 pm
Closed all day Sat & Sun

P&P U.K. orders 75p
Export orders add 10%


Visa

19" RACK MOUNTING EQUIPMENT CASES

This new range of 19" rack equipment cases have been designed with economy and versatility as their objective. These cases are supplied as a flat pack kit with assembly instructions. The equipment cases feature a black powder coat 1/2" (3mm) aluminium front panel with the rest of the case constructed from 7mm or 9mm 'Stelvetite' PVC coated steel. All kits include front panel handles and rubber feet.

ORDER CODE	HEIGHT	PRICE
U1	1 1/4" (44mm)	16.00
U2	3 1/2" (88mm)	18.00
U3	5 1/4" (133mm)	20.00
U4	7" (178mm)	22.00
M&U Sloped mixer console		£25.50

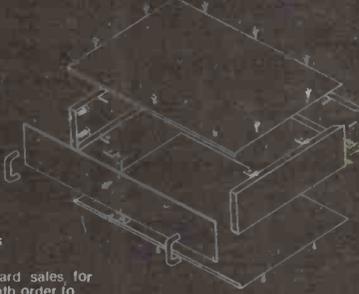All prices Exclude V.A.T.
Please include £2.50 + VAT, Per Item For Post & Packing.
Flat pack size 500 x 260 x 32
Maximum weight - 15Kgs.



Blanking Panels, Racking Consoles and Rack Cabinets also available

Please send S.A.E for further details * TRADE ENQUIRIES WELCOME *


Tel 0275 823983 for Access/Visa card sales for immediate despatch or send cheque with order to

RACKZ PRODUCTS PO. BOX NO. 1402, MANGOTSFIELD, BRISTOL, ENGLAND. BS17 3RY

KEF CONSTRUCTOR SERIES SPEAKER KITS

Based on the famous Kef Reference Series, these three DIY designs give the home constructor the opportunity to own an upmarket pair of loudspeakers at a very down-to-earth price!

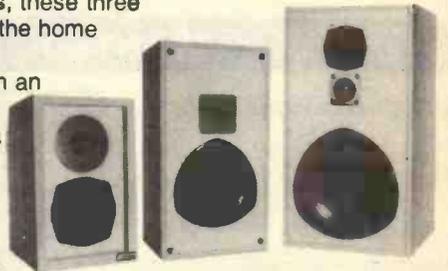With a Wilmslow Audio Total Kit it's easy — no electronic or woodworking skill is necessary. Each kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly), speaker drive units, crossover networks, wadding, grille fabric, terminals, nuts, bolts etc.



Model CS1 is based on the Reference 101, CS3 is equivalent to the Ref. 103.2 and CS9 is based on the Reference 105.2 (but in a conventionally styled encl.).

CS1 £117 pair inc. VAT plus carr/ins £6
CS3 £143 pair inc. VAT plus carr/ins £12
CS9 £393 pair inc. VAT plus carr/ins £18

We also offer a kit (less cabinet) for Elector PL301

Lightning service on telephoned credit card orders!


WILMSLOW AUDIO LTD.
35/39 Church Street, Wilmslow, Cheshire
SK9 1AS Tel: 0625 529599
Call and see us for a great deal on HiFi.
(Closed all day Mondays)

DIY Speaker catalogue £1.50 post free (export \$6)

ADVERTISERS' INDEX

Audiokits	12
Barries Electronics	43
BK Electronics	IFC
Cirkit Distribution	13
Cricklewood Electronics	62
C Scope Electronics	13
Display Electronics	8
Electromech Industries	51
Hart Electronics	18
Henry's Audio Electronics	55
Maplin Electronics	OBC
Pineapple Software	18
Rackz Mounting Products	66
Riscomp Ltd.	66
RTVC	12
SMJ Electronics	62
Specialist Semiconductor Devices	39
Stewarts of Reading	62
Suma Designs	13
TJA Development	26
TK Electronics	6
Wilmslow Audio Electronics	66
XEN Electronics	62
Zenith Electronics	26

WATCH OUT!

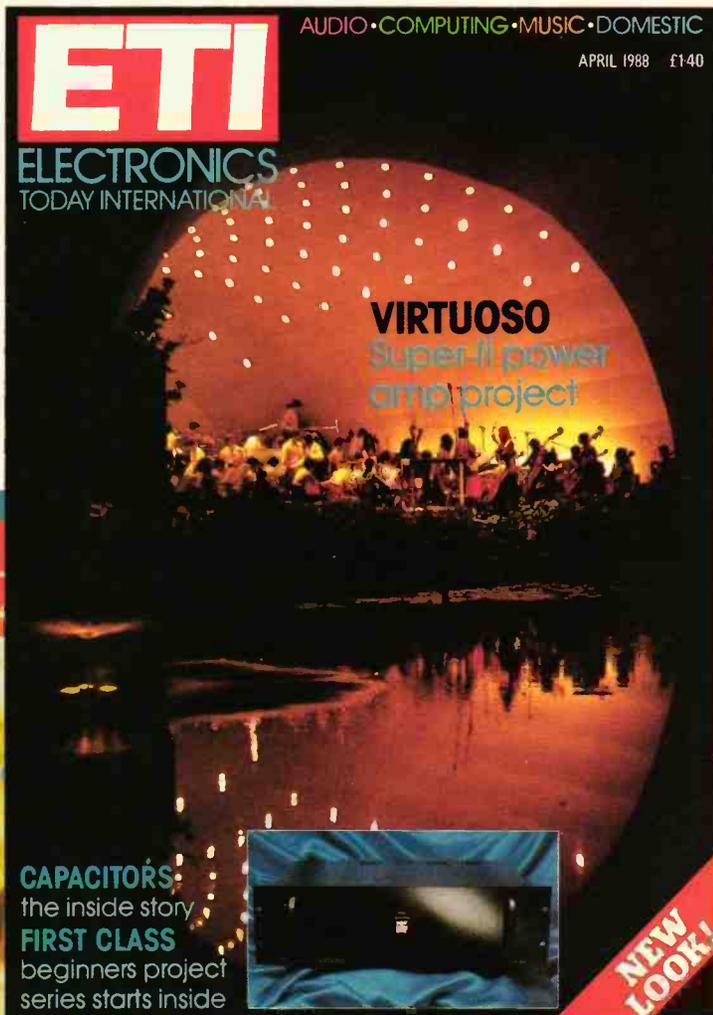

FOR NEXT MONTH'S NEW LOOK ETI

The April issue marks the start of ETI's 17th year of publication and to celebrate the event we have given the whole magazine a facelift.

Next month's ETI has a totally new look, inside and out. Nevertheless it is still crammed to the covers with the usual mixture of features and projects that go to make ETI the best electronics mag around.

The April issue sees the start of the hi-est of fi Virtuoso power amp project to complement the Virtuoso pre-amp of last year. The Spectrum Co-processor is in its third installment and we have the start of a new series of easy projects for the beginner to electronics or the expert short of spare time.

John Linsley Hood gives us the low down on capacitors — what they are, how they're made and how to use them in audio design. Plus there's all the regulars — Circuit Theory, Chip In, Playback, Keynotes, Open Channel, News, letters and much, much more.

Don't be April fooled by the April ETI-Out March 4th

The Dollar has fallen... and so have our Prices!!

PRECISION GOLD MULTIMETERS-OUTSTANDING VALUE FOR MONEY!

BUY NOW, THE TIME IS RIGHT!



Comprehensive

With transistor,
diode and
LED tester.
YJ08J £19.95
£16.95

Professional
Has all the ranges!
YJ09K £34.95
£27.95

Wide Range
With battery tester.
YJ07H £14.95
£11.95

Versatile
Measures temperature
and capacitance.
YP23A
£24.95

Hobby
Ideal for beginners.
YJ76H £8.95
£6.95

Pocket
Rugged, general purpose.
YJ06G £6.95
£5.45

All prices
include VAT.
Please add
50p towards
postage. All
items subject to
availability.



Precision
High sensitivity
on AC
current &
resistance.
YJ10L £41.95
£36.95

Auto Ranging
Top selling
digital.
YJ80B £39.95
£35.95

Practical
Includes
temperature
probe.
YJ79L £64.95
£54.95

Feature Packed
Auto-ranging
with transistor
tester.
YM64U £44.95
£37.95

4 1/2 Digit
Superb
multi-featured
multimeter.
YJ81C £69.95
£59.95

Hobby
Enthusiasts
meter.
YM63T £28.95
£25.95

Push Button
Comprehensive
range of
features.
YJ78K £39.95
£35.95

Low Cost
Push button
digital.
YJ77J £24.95
£21.95

Plus

ORDER NOW AND GET A **FREE** CARRYING CASE WITH YOUR METER (WORTH UP TO £3.95)

Maplin ELECTRONICS

P.O. Box 3, Rayleigh, Essex. Telephone Sales (0702) 554161.

Shops at: Birmingham. Sutton New Road, Erdington. Tel: 021 384 8411.

Bristol. 302 Gloucester Road. Tel: 0272 232014.

London. 159-161 King Street, Hammersmith W6. Tel: 01 748 0926.

Manchester. 8 Oxford Road. Tel: 061 236 0281.

Southampton. 46-48 Bevois Valley Road. Tel: 0703 225831.

Southend-on-Sea. 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000.

Pick up a copy of our 1988 catalogue
from any branch of WHSMITH for just
£1.60. Or to receive your copy by post
send £1.60 + 40p p&p to our P.O. Box
address. If you live outside the U.K.
please send £2.75 or 12 International
Reply Coupons.



We're passing
on our exchange
rate saving
to you!