

ETI**ELECTRONICS
TODAY INTERNATIONAL****THE NORTON DIFFERENCE****Current differencing op-amps explained****CHRONOSCOPE****Test your fire power****BEGINNERS****Battery charger project**

Your free
components to
build the
**BURGLAR
BUSTER**
alarm

BURGLAR BUSTER
The free project to protect
your home



OMP POWER AMPLIFIER MODULES

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre PCB, and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.




OMP100 Mk II Bi-Polar Output power 110 watts R M S into 4 ohms. Frequency Response 15Hz - 30kHz -3dB, T H D. 0.01%, S N R -118dB, Sens. for Max output 500mV at 10K. Size 355 x 115 x 65mm. PRICE £33.99 + £3.00 P&P.

OMP MF100 Mos-Fet Output power 110 watts R M S into 4 ohms. Frequency Response 1Hz - 100kHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T H D. Typical 0.002%, Input Sensitivity 500mV, S N R -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.

OMP/MF200 Mos-Fet Output power 200 watts R M S into 4 ohms. Frequency Response 1Hz - 100kHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T H D. Typical 0.001%, Input Sensitivity 500mV, S N R -130dB, Size 300 x 150 x 100mm. PRICE £62.99 + £3.50 P&P.

OMP/MF300 Mos-Fet Output power 300 watts R M S into 4 ohms. Frequency Response 1Hz - 100kHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T H D. Typical 0.0008%, Input Sensitivity 500mV, S N R -130dB, Size 330 x 147 x 102mm. PRICE £79.99 + £4.50 P&P.

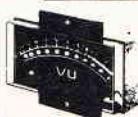NOTE: Mos Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required P.A. version (50KHz bandwidth & Input Sensitivity 75mV) Order - Standard or P.A.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L F D diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case with tinted acrylic front. Size 84 x 27 x 45mm.

PRICE £8.50 - 50p P&P.

LOUDSPEAKERS 5" to 15" up to 400 WATTS R M S Cabinet Fixing in stock. Huge selection of **McKenzie Loudspeakers** available including Cabinet Plans. Large S.A.E. (28p) for free details.



POWER RANGE
8" 50 WATT R.M.S. Hi-Fi/Disco.
 20 oz magnet. 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.
12" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.

MCKENZIE
12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £29.99 + £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £31.49 + £3.00 P&P ea.
15" 150 R.M.S. C15 Bass Guitar/Disco.
 3" ally voice coil. Die cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £57.87 + £4.00 P&P ea.
10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.
 2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.99 + £2.00 P&P.
10" 200 WATT R.M.S. C10200GP Guilar, Keyboard, Disco.
 2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. PRICE £44.76 + £3.00 P&P.
15" 200 WATT R.M.S. C15200 High Power Bass.
 Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £62.41 + £4.00 P&P.
15" 400 WATT R.M.S. C15400 High Power Bass.
 Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £89.52 + £4.00 P&P.

WEIM
5" 70 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 52Hz. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £22.00 + £1.50 P&P ea.
8" 150 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £32.00 + £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £36.00 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £47.00 + £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)
5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 + £1.00 P&P ea.
6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 + £1.50 P&P ea.
10" 60 WATT R.M.S. Hi-Fi/Disco etc.
 1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. PRICE £16.49 + £2.00 P&P.

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles. 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/ RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

BURGLAR ALARM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position key operated facia switch - off - test - armed 30 second exit and entry delay.


Indoor alarm - Electronic swept freq. siren 104dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00 Usual Price £228.85

BKE's PRICE £89.99 + £4.00 P&P
 ? Why buy a collection of sell assembly boards!

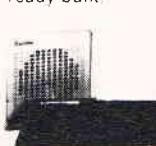IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12". Watts R M S per cabinet. Sensitivity 1W 1mR dB.

OMP 12-100 Watts 100dB. Price £149.99 per pair.

OMP 12-200 Watts 102dB. Price £199.99 per pair.

Delivery Securicor £8.00 per pair.

OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. **Three models** (Ratings R.M.S. into 4 ohms), Input Sensitivity 775mV.

MF200 (100 + 100)W. £169.00 **Securicor**

MF400 (200 + 200)W. £228.85 **Delivery**

MF600 (300 + 300)W. £322.00 **£10.00**

1 K-WATT SLIDE DIMMER

- * Control loads up to 1Kw
- * Compact Size 4 1/2" x 1" x 2"
- * Easy snap fitting through panel cabinet cut out
- * Insulated plastic case
- * Full wave control using 8 amper triac
- * Conforms to BS800
- * Suitable for both resistance and inductive loads in numerous applications in industry, the home, and discos, theatres etc.

PRICE £13.99 - 75p P&P

BSR P295 ELECTRONIC TURNTABLE

* Electronic speed control 45 & 33 1/3 r.p.m. * Plus Minus variable pitch control * Belt driven * All metal platter with strobed ring * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1" cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14v D.C. 65mA
 Price £36.99 - £3.00 P&P

ADC Q4 mag. cartridge for above Price £4.99 ea. P&P 50p



PIEZOELECTRIC TWEETERS MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces improved transient response with a lower distortion level than ordinary dynamic tweeters. As crossover is not required these units can be added to existing speaker systems of up to 100 watts more if 2 put in series. FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER

TYPE 'A' (KSN2036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each - 40p P&P

TYPE 'B' (KSN1005A) 3" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each - 40p P&P

TYPE 'C' (KSN5016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each - 40p P&P

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each - 40p P&P


TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £9.99 each - 40p P&P

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 - 85 mm. Price £3.99 - 40p P&P

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment LED Vu Meters. Many outstanding features: 5 inputs with individual faders providing a useful combination of the following:

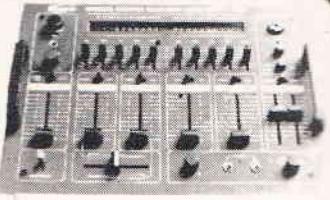3 Turntables (Mag.), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor Pan Pot L & R. Master Output controls. Out put 775mV. Size 360 x 280 x 90mm. Price £134.99 - £3.00 P&P



B. K. ELECTRONICS DEPT ETI

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED



PROFESSIONAL SURVEILLANCE EQUIPMENT KITS

- **MTX**
- **VT500**
- **VOX75**
- **CTX900**
- **DSX900**
- **TLX700**
- **ATR2**
- **XML900**

Micro-miniature VHF transmitter. The smallest kit on the market, measuring an incredible 17mm x 17mm including on-board mic. Super sensitive Fully tuneable over FM band, 9V operation with range up to 1000m. £10.95
 High power version of the MTX with on-board PA stage providing 250mW of RF power. Measures just 20mm x 40mm, power requirements 9-15V. Excellent sensitivity and stability. Fully tuneable over FM band. Ranges over 3000m can be expected. £12.95
 Voice-activated transmitter. Variable sensitivity trigger level switches transmitter on when sounds are detected. Stays on for timer delay variable between 1-20 sec. Fully tuneable output covers all FM band. Very sensitive and low standby current through CMOS circuitry. 9V operation, range up to 1000m. Measures 30mm x 40mm. £15.95
 Sub-carrier scrambled transmitter. Audio is double modulated providing very secure transmissions. Any unauthorised listener will not be able to demodulate signal without DSX900 Decoder unit. Variable modulation on-board. Fully tuneable output covering FM band. 9V operation, range up to 1000m. Measures 30mm x 40mm. £18.95
 Decoder unit for CTX900. Connects to earphone output of receiver to descramble signal from CTX900. Monitor using small speaker or headphones. Variable decode frequency on-board for best resolution. 9-12V operation. Measures 35mm x 50mm. £17.95
 Micro size telephone transmitter. Connects onto line at any point and requires no batteries. Clearly transmits both sides of conversations on both incoming and outgoing calls. Undetectable by phone users. Fully tuneable output covering FM band. Range up to 1000m. Measures just 20mm x 20mm. £9.95
 Micro size telephone recording unit. Connects onto line at any point and connects into ANY normal cassette recorder, standard or micro having MIC and REM sockets. Requires no batteries. Switches recorder on silently when phone is used for incoming or outgoing calls, switches off when phone replaced. Clearly records both sides of conversations. Undetectable by phone users. Measures 10mm x 35mm. £10.95
 RF Bug Detector/Locator. Wide band input circuitry detects presence of RF field and triggers flashing LED and piezo beeper. Variable sensitivity enables source of transmission to be pinpointed to within 6 inches. Max sensitivity will detect MTX or similar transmitter at around 15-20 feet. 9V operation. Measures 55mm x 55mm. £21.95


All kits come fully documented with concise assembly and setting-up instructions, high quality fibreglass PCB and all components necessary to complete the module. All prices are inclusive but please add £1.50 to cover P&P. Orders over £50.00 post free. Please state requirements clearly and enclose cheque or PO to cover.

Phone orders on ACCESS or AMEX accepted. Tel: 0827 714476
 NOTE: It is illegal to operate a transmitter in the UK without a licence
 Send 9x4 SAE for full catalogue of these and other surveillance kits

- SUMA DESIGNS (Dept ETI), THE WORKSHOPS, 95 MAIN ROAD
 BAXTERLEY, NR AATHERSTONE, WARKS CV9 2LE. TEL: 0827 714476



Bare Board
 £17.50
 (plus postage and VAT)

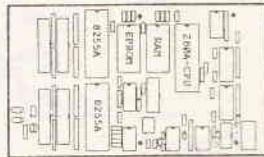

Interak 1

SINGLE BOARD COMPUTER "SBC-1"
 A computer doesn't have to look like you'd expect a computer to look. It doesn't have to have a keyboard and a screen and floppy disks and so on.
 The SBC-1 has the bare minimum of chips a Z80 computer can have and still be a computer: A 4MHz Z80A-CPU chip, an EPROM chip (up to 32K), a static RAM chip (up to 32K) and a pair of 8255A I/O (input output) chips giving 48 individual lines to wattle up and down. There are one or two additional "glue" chips included, but these are simple "74LS" or "HC" parts.

A star feature is that no special or custom chips (ie PALs, ULAs, ASICs etc) are used — and thus there are no secrets. The Z80A is the fastest and best established of all the 8-bit microprocessors — possibly the cheapest too!

Although no serial interface is included, it is easy for a Z80A to wattle one bit up or down at the appropriate rate — the cost is a few pence worth of code in the program: why buy hardware when software will do?

Applications already identified include: Magnetic Card reader, mini printer interface, printer buffer, push button keypad, LCD alphanumeric panel interface, 40-zone security system, modem interface for auto sending of security alarms, code converter (eg IBM PC keyboard codes to regular ASCII), real time clock (with plug in module), automatic horticultural irrigation controller.

By disabling the on-board Z80A-CPU this card will plug into our Interak 1 CP/M Plus disk-based development systems, so if you don't fancy hand-assembling Z80 machine code you don't have to!

The idea is (if you are a manufacturer) you buy just one development system and then turn out the cheap SBC-1 systems by the hundred. If you are really lazy we can write the program for you and assemble the SBC-1 cards so you can get on with manufacturing your product, leaving all your control problems to us.

Greenbank

For more details write or phone us:
Greenbank Electronics, Dept. (T11E), 460 New Chester Road, Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391.

TOP QUALITY AUDIOPHILE COMPONENTS

NEW FROM SAGE AUDIO

HIGHEST POSSIBLE TECHNICAL PERFORMANCE

SUPERMOS 2

(100W to 500W)


±50V to ±75V

THE MOST ADVANCED HI-FI AMP IN THE WORLD

Following the success of the original SUPERMOS we now launch a higher powered version with many new exclusive sound improvements not available on any other amplifier, kit, board, module, or ready made.

FEATURES:-

- Highly efficient distortionless PURE CLASS A throughout (low heat generation)
- Top audiophile components inc. best SMD's.
- Exclusively made matched custom semiconductors.
- Minimal capacitor design (without DC servos).
- PSU sound colouration eliminated
- Advanced PSU feedforward ripple elimination including internally separately regulated voltage AND current to ALL stages using SAGE Super-Supply circuitry.
- Total reactance (difficult speaker) drive capable.

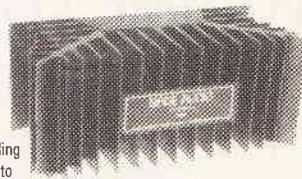

SIZE 240 x 100 x 100mm

THD 0.0001%, Slewrate 685v/us, f-3dB 0.5Hz-350kHz, O/P Current 80amps, Damping factor 940, transient power (2ohms) up to 1800W max.

PLUS By innovative technical design we have eliminated 5 individual sound colouration components found in all other conventional amplifiers.

ELIMINATED - 1) Emitter resistors 2) Zobel networks 3) HF pole compensation 4) Fixed bias Vbe multiplier and temp gen distortions 5) Capacitor sound.

AND THERE'S MORE Sage exclusive CLEAN CLIPPING (not to be confused with soft clipping) eliminates PSU ripple from reaching the output even when severely clipped, this together with individual regulated supplies to all stages (Super-supplies) TOTALLY eliminates PSU component sound colourations, (A World first!)

COMING SOON The SAGE 'ACTIVE PI MODE' CLASS A preamp, THE definitive match to the SUPERMOS power amplifiers.

AND THERE'S MORE . . . We can't possibly describe this amp fully in this ad, to receive a full size 8-page glossy brochure giving full details including active class A information send £1 cheque, PO or coin plus a 26p Large SAE (Overseas send 61RC's). **SUPERMOS 2 modules: £140 (p&p £2).** THE ORIGINAL SUPERMOS MODULES 50-150W £65 plus (£1.50 p&p)

Send to:-

**SAGE
AUDIO**

Wendy (Sales Dept.), Construction House, Whitley Street, Bingley, W. Yorks, BD16 4JH England.

Tel: (0274) 568647, Tlx: 517783, Fax: (0274) 551065

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX • 031 667 2611

The supplier to use if you're looking for

★ A WIDE RANGE of components aimed at the hobbyist ★

★ competitive VAT inclusive prices ★

★ mail order - generally by return of post ★

★ fast, friendly service ★

- by mail order, telephone order or personal call

1988 CATALOGUE NOW READY — SEND 2x18p STAMPS

we do try to keep the goods we list in stock.

Whether you phone, write or call in
 we'll do our best to help you.

Open: Monday-Friday 9.00-6.00


Saturday 9.00-5.00



19" RACK CASES

* Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish * New improved construction and finish * Black anodised aluminium front panels * Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure * Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles * With ventilation slits and plastic feet * Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package spare front panels available

| Order Code | Panel Size | Reel Box | W | H | D | Weight | Price |
|------------|------------|-----------|-------|-------|---|--------|-------|
| 1U-10 | 19x1.75 | 17x1.5x10 | 2.4kg | 23.50 | | | |
| 2U-12 | 19x3.5 | 17x3.0x12 | 3.3kg | 25.50 | | | |
| 3U-12 | 19x5.25 | 17x5.0x12 | 4.0kg | 27.50 | | | |
| 4U-12 | 19x7.0 | 17x6.5x12 | 4.6kg | 29.95 | | | |

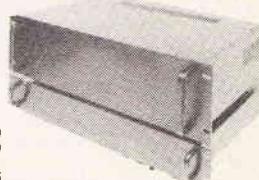

Please add £3.00 P&P for the first item and £1.50 for each additional item.
 No VAT to be added to the price.


A range of low cost, high quality test equipments available, s.a.e. for details. To order send cheque/postal order. Quantity discount available. Customers who require further information please send S.A.E. Trade and overseas orders welcome. Mail order only.

T.J.A. DEVELOPMENTS

Dept. ETI, 19 Welbeck Road,
 Harrow, Middlesex HA2 0RN.


November 1988

VOLUME 17 No 11

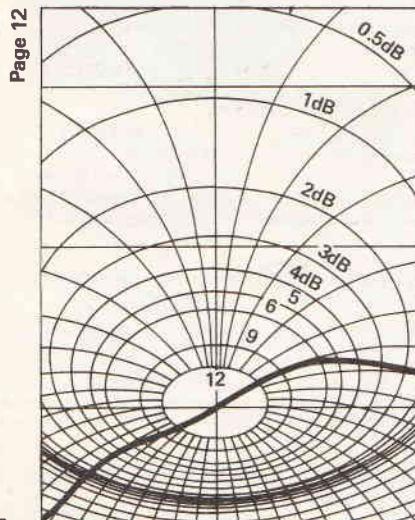

Page 12

Page 35

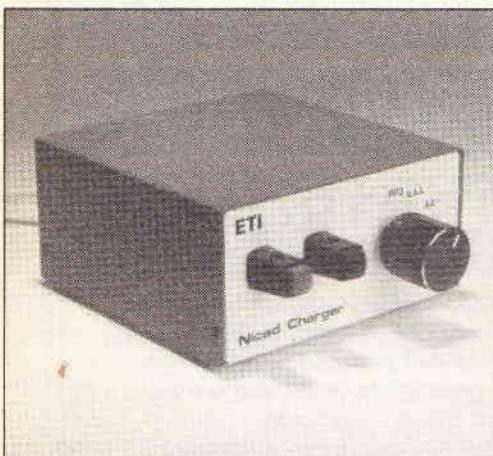

ISSN
0142-7229

ABC

Member of the
Audit Bureau
of Circulation

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1988 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible however, for any variations affecting price or availability which may occur after the publication has closed for press.

• Subscription rates — UK: £18.00. Europe: £22.20.
Middle East: £22.40. Far East: £24.00. Rest: £22.70 or
US\$34.00.

**ARGUS
PRESS
GROUP**

1 Golden Square
London W1R 3AB
Tel: 01-437 0626
Telex: 8811896

Geoff Bains: Editor
Jez Ford: Assistant Editor
Paul Chappell: Projects Editor
Jerry Fowler: Technical Illustrator
Heather Hopkinson: Design

Mark Warford: Photography
Julie Capstick: Ad Manager
Heather Wust: Classified Sales
Andrew Selwood: Copy Control
Mark Webb: Group Editor

REGULARS

| | | | |
|----------------------|-----------|-----------------------|---------------------------|
| News | 6 | 41 | 62 |
| Read/Write | 8 | 52 | 62 |
| Insight | 9 | 54 | 63 |
| Diary | 9 | 56 | 64 |
| Next Month | 11 | 57 | 65 |
| Keep Regular | 20 | Classified Ads | Photocopies |
| Backnumbers | 22 | | Fame & Fortune |
| Subscriptions | 37 | 61 | 66 |
| BMF Report | | | Ad Index |

Published by Argus Specialist Publications Ltd., 1 Golden Square, London W1R 3AB. Tel: 01-437 0626. UK newtrade distribution by SM Distribution Ltd., 6 Leigham Court Road, London SW16 2PG. Tel: 01-677 8111. Overseas and non-newtrade sales by Magazine Sales Department, 1 Golden Square, London W1R 3AB. Tel: 01-437 0626. Subscriptions by Infonet Ltd., 5 River Park Estate, Berkhamsted HP4 1HL. Tel: (04427) 76661. US subscriptions by Wise Owl Publications, 4314 West 238th Street, Torrance, CA90505 USA. Typesetting and origination by Project 3 Filmsetters, Whitstable. Printed and bound by The Chesham Press, Chesham. Covers printed by Loxley Brothers Ltd., Sheffield.



FEATURES/PROJECTS

11

Competition

Win Maplin's stylish calendar clock in our free-to-enter date matching competition

12


Control Strategies

Keith Brindley gets matters firmly under control with an explanation of loops, open and closed, Bode plots and other such tools of the control trade

18

The Norton Difference

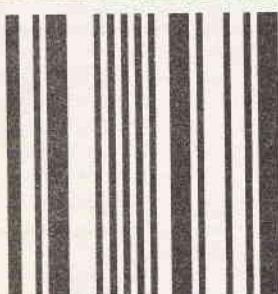Ray Marston launches forth with a short series on this much underused breed of op-amp



21

Behind Bars

Malcolm Brown explains how to read those troublesome baked bean cans with a full explanation of bar codes in general and the July ETI competition in particular

23

Making Sense

Mike Barwise turns the *Chip In* spotlight on sensors and transducers with the first of two looks at this wide field



26

Op-amps


Paul Chappell continues the *Circuit Theory* look at op-amps as differential amplifiers

PROJECT

29

Digital Transistor Tester

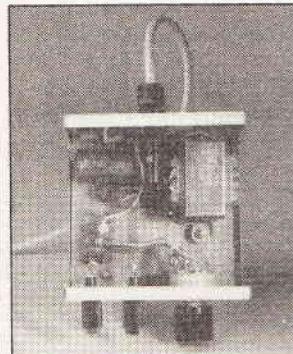Robert Penfold's tester checks for the good, the bad and the leakage



PROJECT

35

NiCd Charger

Keith Brindley charges the batteries other *1st Class* projects cannot reach with this simple-to-build charger for beginners

PROJECT

38

Burglar Buster



Paul Chappell explains how to use the free components on this month's cover to protect your home and valuables

PROJECT


43

Chronoscope


Paul Brow can tell if Superman really is faster than a speeding bullet with this ingenious gun club companion to speed test your pellets

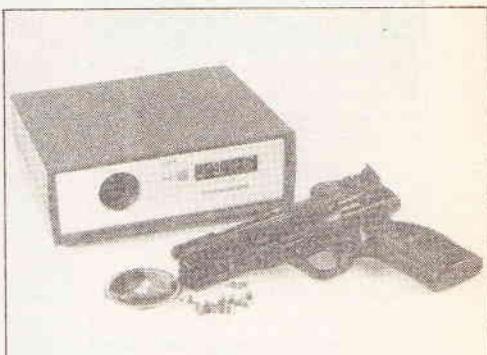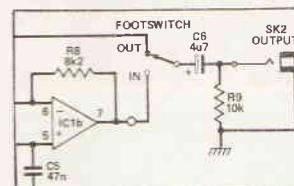

Page 43

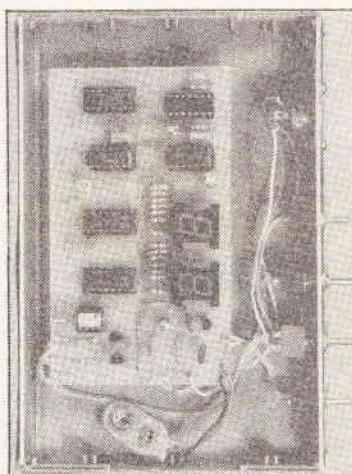

Page 29

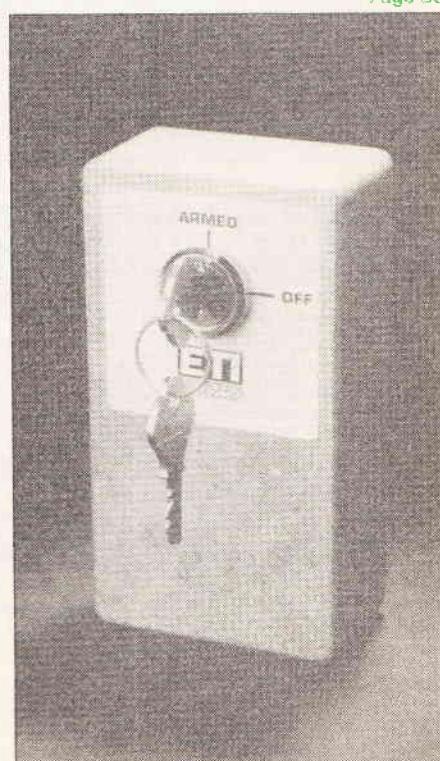

Page 38

49

Tech Tips

More circuits for the needy from the ever ingenious readers of ETI

- 8-way Stereo Selector
- Guitar Preshaper
- Touch-controlled Pre-amp
- Cheap Touch Switch
- Low Current Siren
- Super Woofer
- Spectral Spectrum 128
- Envelope Generator

NEWS


THE PRICE IS UP

It is with great regret that we have to announce a 10p rise in the price of your favourite electronics mag, as of this month.

Despite our continued success since the new-look ETI was launched in April, our man with the desktop calculator and sharpened HB in his mouth tells us that the price of trees has risen something shocking this season.

We deeply apologise and hope that you will consider the extra coin to be money well spent.

SLIMLINE TONIC

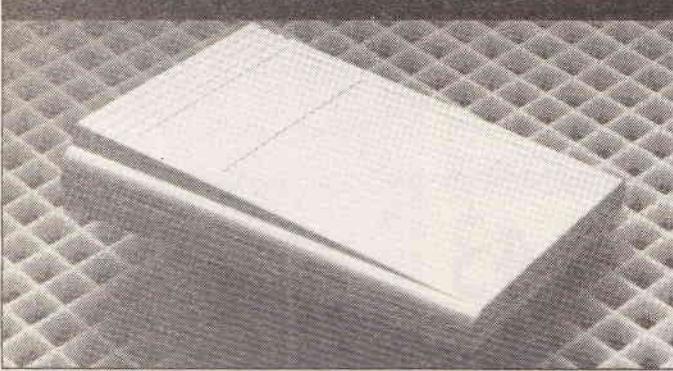

West Hyde has introduced a new slimline case designed for use with membrane keypad switches. The case is sealed to standard IP65 so that with hermetically sealed membrane switches the whole unit can be safely doused with Nescafe.

West Hyde has also announced significant price reductions particularly

DOMESTIC ARGUMENT

Government intentions to allow large industrial electricity users to sign direct contracts with generating companies will lead to increases in domestic charges, warns a new report from economist Dr Dieter Helm.

In order to compete with these direct sales the area distribution boards would have to reduce industrial prices and raise domestic charges to balance the equation.

Dr Helm details the importance of getting the details of regulation (and preferably the regulatory body itself) established quickly and before privatisation, to examine contracts in the period before the splitting of the CEBG and creation of the area boards.

The report *Regulating the Electricity Supply Industry* costs £5 and may be obtained from Blackwells, 108 Cowley Road, Oxford.

FLIP-TOP TV

Panasonic has produced Mini-vision, its new compact portable TC-L3 colour television with a flip-top screen to make use of environmental lighting.

The unit is battery powered though can be powered from the mains or from a car battery (perhaps not the safest place to watch it...).


The 3in screen achieves a sharp clear picture thanks to Panasonic's Active Matrix technology — liquid crystal display with a thin film transistor on each LCD segment to control over 100000 pixels.

The TC-L3 should be available this month at a retail price of £329.95.

For more information contact Panasonic Consumer Electronics, 300-318 Bath Road, Slough SL1 6JB. Tel: (0753) 34522.



ALARM

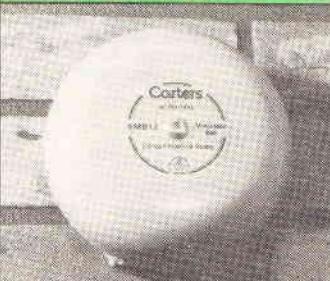

On Teko, Internorm and Combicard 500 products which are benefiting from exchange rates and higher production quantities.

For full details contact West Hyde, 9-10 Park Street Industrial Estate, Aylesbury HP20 1ET. Tel: (0296) 20441.

With burglars to bust this month, Carters has introduced a very reasonable motorised bell which produces a 95dB ringing tone when triggered. The enclosure for the motor is fully weather protected and the bell dome is fitted with anti-tamper clamp screws.

The bells are available for two voltages: 12V at £7.60 + VAT and 24V at £7.90 + VAT.

Contact Carters, A&G Security Electronics, Wrigley Street, Oldham, Greater Manchester OL4 1HW. Tel: 061-633 3033.

CD-INFO

Pergamon's launch of the CD-ROM version of the 10-volume *International Encyclopaedia of Education* includes a free Hitachi CD-ROM drive with every copy. The Hitachi drive is for IBM compatible computers and has been left undedicated so that other CD-ROMs may also be read.

The software for the encyclopaedia attempts to be as simple to use as possible so that casual use in libraries and schools can be encouraged. Search topics are defined in the user's own words rather than being picked from the indexing system. Figures and illustrations are included and all displays may be printed out.

Meanwhile Nimbus is embarking on a series of discs aiming to place the entire World Health Knowledge Base onto CD-ROM. First in the series is an AIDS information and expert system, with a diagnostic aid to examine symptoms and identify diseases that a physician should consider treating. Further details of such treatment can then be accessed.

For details of Pergamon's CD-ROM operation contact PCS, Headway House, 66-73 Shoe Lane, London EC4P 4AB. Tel: 01-377 4918. Nimbus Records is in Wyestone Leys, Monmouth NF5 3SR. Tel: (0600) 890682.



FREEBIES

Avast selection of literature and lists are up for the price of a stamp this month.

Omni's new mail order catalogue of components, tools and accessories is now available for two 18p stamps. Tel: 031-667 2611 or visit the shop at 174 Dalkeith Road, Edinburgh EH16 5DX.

Welwyn has produced a comprehensive guide to its SM resistors (Tel: (0670) 822181) and Multicore has written a trouble-shooting wallchart identifying the problems of SM soldering (Tel: (0442) 233233).

Hitachi has published an excellent 16-page guide to its CMOS and biCMOS gate arrays and also a short brochure on combo codec ICs. Contact Hitachi, 21 Upton Road,

Watford WD1 7TB. Tel: (0923) 224422.

Rittal is giving away a thermal management slide rule to stop your enclosure overheating (Tel: (0909) 567871) and Instrumex has issued the first update to its Instruments for Industry Blue Book. Tel: (0753) 44878.

Handy for Chip In, Hamlin Electronics has a 16-page catalogue of the company's magnetic proximity sensors. Tel: (0379) 644411.

Topax has a full colour brochure of industrial mains conditioners (Tel: 01-977 0055) and lastly Axion Electronics has a free guide to CMOS special functions from Turnpike Road, Cressex Estate, High Wycombe HP12 3NR. Tel: (0494) 461616.

MAIL ORDER

Anew mail order service for components, tools and equipment is being offered by EES from their Southampton address. There is to be no minimum order and all normal credit cards can be used for telephone or written orders.

A catalogue is under production and can be obtained by ringing the number below.

One handy service that EES is offering is one-off customised sheet metal working for enclosures, including hinging, panel cutting and silk screening.

For full details and the catalogue contact ESS, Harrison House, Harrison Road, Swaythling, Southampton SO2 3TL. Tel: (0703) 671166.

MISSION OF SUCCESS

Following up our education special last month, a Lancashire-based company is offering a collection of learning and project packages for schools, colleges and home constructors.


Electronics Success Ltd is an unusual company. It has been set up by a group of Christian electronics and computing engineers to generate capital for a schooling project in the Far East. The vision is to run two schools: one as a fee-charging residential computing school, and the other as a free school for those unable to pay, supported by the fees from the first.

It is an ambitious project and Electronics Success are hoping to generate the initial capital over the next two years.

There are five packages ranging from the £30 *Elementary Learning Package* (containing 125+ components, 2 books and 2 wallcharts) to the £280 *Complete Constructors Package* (with 15 books, 3000 components, test instruments, 20 tools and soldering iron).

For full details contact Electronics Success, PO Box 10, St Annes on Sea, Lancashire FY8 1SA.

GOLDEN OLDIE

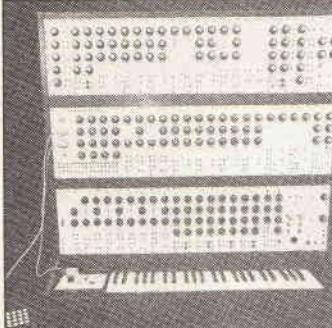


The Digsound Modular Synthesiser projects that appeared in ETI back in 1980 are now available in kit form again.

The original modules are available in improved form together with a range of new units including a keyboard controller and a sound sampler. Also available are analogue and digital VCOs, a profusion of filter modules, processors and effects units.

From these can be constructed a modest monophonic instrument or a TanDram special like the one pictured here.

The variety of components makes price listing a lengthy business but a catalogue with kit information and price lists is available free from Digsound, 16 Lauriston Road, London SW19 4TQ. Tel: 01-946 0467.

MERCURY DESIGNER KIOSKS

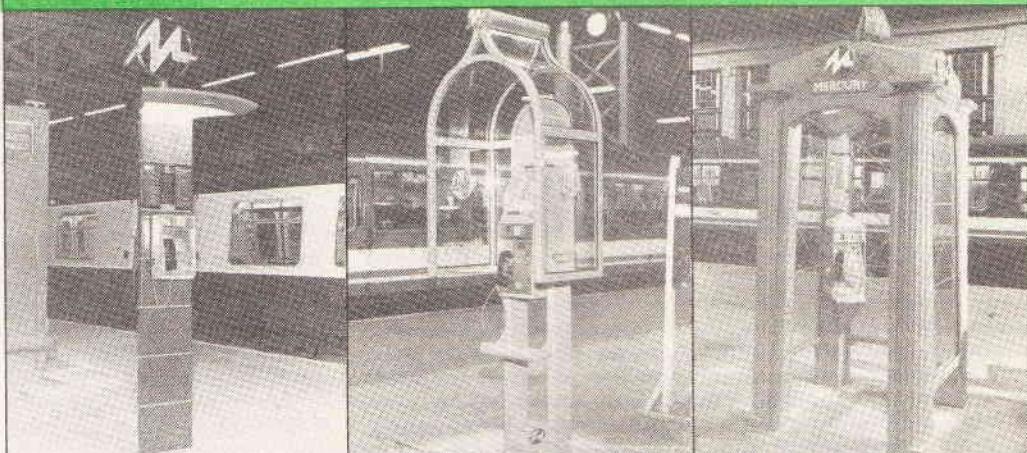

Mercury has opened its offensive on the UK public payphone market with 26 callboxes in London's Waterloo station. The units are cash-free with payment made using Mercury's own phone card, the Mercurycard. Unlike BT's Phonecard boxes, the kiosks can also accept Access, Visa, Amex and Diner's Club cards.

The design of the boxes has been the subject of some criticism. Mercury invited proposals from ten design houses and has selected three final kiosks to be adopted. A range of kiosks provides a 'sympathy with en-

vironment' not available with the single BT kiosk, says Mercury.

The three designs are an art-deco totem, a Gothic glass canopied standing kiosk, and a dreadful classically columned box that is unlikely to be 'sympathetic' anywhere beyond the gates of the British Museum.

However Mercury can be proud of its technology and price structure. Every kiosk is directly connected to Mercury's digital optical fibre network — although this does limit new payphone sites to areas already covered by its own network.

The payphone unit itself, supplied by GPT, is sensibly laid out with simple instructions on LCD display and the useful addition of a volume control. All units will be serviced daily and are self fault reporting.

The charges are also lower than BT callbox rates by an average of 5% (inland) plus the major advantage of phonecard units being 5p rather than BT's 10p, which will halve the cost of brief local calls.

For more details contact Mercury, 90 Long Acre, London WC2E 9NP. Tel: 01-528 2000.

DESIGNER AWARDS

The Young Electronic Designer Awards sponsored by Texas Instruments and Cirkit have grown over the years into quite a major event.

This year's awards ceremony was held in a plush London conference centre with 'personalities' in attendance and Education and Science Minister Kenneth Baker handing out the prizes of cash, certificates, trophies and TI calculators to the winners in the three age groups.

In the under 15 age group the winner was Nicolas Adams (14) who had designed an effective pillow vibrator alarm to alert deaf people that other alarms (clocks, smoke detectors, burglar alarms, etc) were sounding.

The 15-19 group winner, Paul Dagley-Morris (17), also won last year. This year he again concentrated on the disabled market with a radio linked panic button for existing alarm systems in retirement homes and so on.

Hugh Mair (20) won the 19-25 category with a 20MHz digital storage oscilloscope add-on for a PC along with some impressive software.

The cash prizes ranged from £50 for the runner up in the youngest category to £500 for the 19-25 winner along with £600/annum course sponsorship, vacation employment and a guaranteed job with TI after graduation.

MATRIX MANAGEMENT

Professional prototyping using a customised version of a standard board is the service being offered by Matrix Systems.

The initial board uses the Intel 8052AH BASIC together with an on-board EPROM programmer, 8K of EPROM, 8K of static RAM, various ports (for VDU, printer and so on). Further hardware is then built on to the board (plenty of space is available) either by the user or by Matrix who offer production assistance from ASIC

design through to case design.

As an example of the ability of such a system, a CPU card, bus card, I/O card and ADC card can all be replaced by one Matrix board plus three additional ICs to give 16-channel 8-bit data sampling with 24 relay control lines.

For more stuff contact Matrix Systems, 356 Silbury Boulevard, Milton Keynes MK9 2LR. Tel: (0908) 604848.

BENCH METER UPGRADE



Thurlby is marketing a new high accuracy bench digital multimeter, an improved version of the successful 1503.

In addition to normal functions the unit measures frequency up to 4MHz (7MHz with overflow ignored) with 100Hz resolution, and 0.0025% full-

scale accuracy.

Resolution for normal multimeter functions is 10µV, 10mR and 1nA. The unit can be powered from mains or batteries and costs £185.00 + VAT.

Contact Thurlby Electronics, New Road, St Ives, Huntingdon, Cambridgeshire PE17 4BG.

READ|WRITE

PARTICLE ARTICLE

With reference to your article on particle physics in September, may I expound an alternative view?

It is well known that when an electron meets a positron the result is mutual annihilation with formation of two gamma photons, each with energy of 0.51MeV. Conversely a pair of photons at or above this energy can interact to form an electron/positron pair. The logical explanation is that an electron therefore consists of a 0.51MeV photon constrained into a circular path by its own relativistic field. A path length equal to the wavelength gives a circle radius of 3.863×10^{-13} m with toroidal symmetry.

Further, if the photon's plane of polarisation rotates 360° with one wavelength then its field becomes consistent with that of a magnetic dipole (perhaps with a small gyroscopic component). How the dipolar electrical field of a free photon becomes a unipolar field when constrained into a circular path I cannot yet explain.

Neutrinos are similar but have no magnetic dipole or unipolar electric field — my guess is that these are analogous to AC rather than DC, with their fields constantly inverting.

I also propose that quarks are simply leptons (electrons and neutrinos) travelling at such high speeds that almost all their mass is relativistic in nature.

Henry Earle
Nottingham

Yes and no. Yes, $E=mc^2$. Yes, an electromagnetic field can become a matter field and vice versa. But they are not the same thing. The 9.11×10^{-31} kg rest mass of an electron **can** be released as a 0.51MeV photon but the electron is not merely a photon in disguise. Photons only travel at the speed of light because they have zero rest mass — a phrase which should not be interpreted as meaning they might have mass in some other circumstances.

$$m = \frac{m_0}{\sqrt{1 - \frac{v^2}{c^2}}}$$

No matter what circular path you constrain them in, photons are massless. Electrons cannot therefore be made of electromagnetic energy and the points about toroidal symmetry and so on do not follow. You cannot make matter out of photons without changing them into something else — in which case the other arguments don't really work.

RANDOM ERRORS?

I cannot see how the Random Number Display (August 1988) can work. After every ten clock cycles a single digit will be back to its original state with the same interval between it and the next digit. After ten states the 'random' numbers will wrap around.

Adding time delays before a digit is latched simply alters the intervals between the digits.

The only way for the circuit to work is as a single counter from 000 to 999 stopped at random (or with a delay) by the Tripotrimmers Committee.

A Thorne
West Morrs, Dorset

You have assumed that all three counters are locked in phase. In practice even if the oscillators were the same frequency they would drift in phase so that all combinations of 000-999 could be obtained.

EAN MEANS BEANS

I have often wondered about the barcode on my beans and was looking forward to the solution to your puzzle. I am quite at home with binary, hex and checksums but after reading your solution I still have no idea how to decode my beans (I don't even know what EAN stands for). Is this the best your staff writers can do?

While my blood is up, there is another thing. Although an occasional jest is welcome, I find your schoolboy compulsion to squeeze a pun into every other line tiresome. Imagine trying to find Mike Barwise's *Brought to Light* series from the index in two years' time. Any editor that allowed that piece to be published without laser or diode in the title should be tarred, feathered and hung out to dry, head downwards, from the top of Nelson's Column on a thin piece of string.

Niel Mackay
Hastings, East Sussex

OK we give in. The profusion of letters demanding a detailed explanation of barcode encryption are answered on page 21. It took a whole page to explain — the original solution simply did not have enough space to go into detail.

As for the indexing, all articles are cross referenced and appear under both title and subject to avoid just this problem. Please put that thin piece of string away!

SPEAKING FOR OTHERS

I have just read the article by Malcolm Walmsley *Speaking For Yourself* in your September issue and cannot let his remarks pass without comment.


Speaker kits are 'only to be found in obscure electronics dealers and through obscure mail order firms'. We are in our 30th year and with a £1M turnover are hardly obscure.

I have sent you a copy of our DIY speaker catalogue which may help to bring Mr Walmsley up to date. Our 'Total' kits include cabinets in flatback form. These are accurately machined from 18mm MDF with baffle apertures, rebates, etc ready cut. We can supply iron-on veneer for the cosmetic finish of the cabinets. Constructors often send us photographs of the completed speakers — usually beautifully done and the finish is superior to all but the very best of the ready-mades.

Edge glued 3/4in chipboard without battens and then covered with vinylide. Yuk — weak construction and probably not airtight. It's enough to put potential constructors right off the idea.

Dick Stephens
Managing Director,
Wilmslow Audio

Malcolm's obscurity comments in his review of Maplin's speaker kits were directed at the apparent lack of speaker kits in the high street hi-fi dealers today. There was a time when most hi-fi dealers sold speakers in kit form as well as ready made. We accept that Wilmslow Audio has been trading for 30 years and are happy to hear of your excellent turnover, however, the fact remains that to the vast majority of the audio-buying

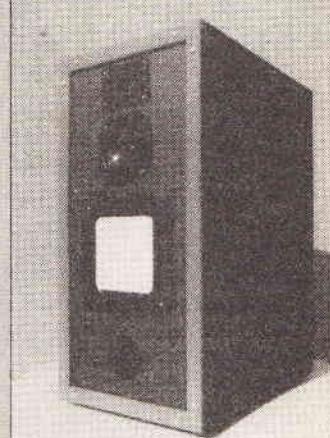

populace speaker kits are nowadays conspicuous by their absence.

Malcolm's chipboard cabinets are certainly airtight and strong. Most commercial speakers are still made of chipboard and even without the ubiquitous battens, the cabinet we had in the ETI office for photography was strong enough to survive a fall down the stairs (sorry Malcolm!) without a scratch. As to the finish, Malcolm could well have purchased some veneer to make his speakers look like everyone else's but the vinyl covering and wood front frame was chosen as a tough and durable finish which looks both attractive and different. The materials chosen are also commensurate with the low price of the Maplin units.

We appreciate the extra ease of construction of your Total kits (although the expense is correspondingly greater) and we (or Malcolm) would be happy to build up a review pair of one of your models in the future.

INFORMATION



CORK

INSIGHT



Japan's electronics industry is presently in a period of painful readjustment to the outside world.

The willingness of major manufacturers to expand and relocate production facilities in Western Europe and America is not simply to facilitate the harmonious global electronics industry — as promoted in the literature of the EIAJ (Electronics Industries Association of Japan).

Japan's exports are suffering badly from the continuing strength of the Yen against the American dollar and the move away from home production is a direct result.

Trade contracts are conducted almost exclusively in dollars so that products made with Yen capital are more expensive on the world market. Manufacturing abroad allows the Japanese companies to compete with foreign firms on equal terms, (although this damages Japan's balance of payments). Many products, particularly consumer electronic equipment, are now being sold back to Japan by Japanese companies but are manufactured in Asia, Europe or America.

The advantages for other countries are obvious — capital investment, employment opportunities since most of the workforce will be local, not to mention a major reduction in Japanese imports. Japan, in the guise of the

EIAJ, carefully takes into account local communities and industries to ensure mutual prosperity and minimising of any initial resentment of the Japanese working practices.

However, the rising yen is not the only problem facing the Japanese economy. There is also the increasing competitiveness of countries in Asia such as Taiwan and South Korea — the NIEs (Newly Industrialising Economies).

Products from Asia are not only gaining global market ground but are beginning to encroach on Japan's home territory. Combined with attractive prices courtesy of the yen, Japanese imports of video equipment for instance rose by almost 300% last year, colour televisions by almost 900%. While they remain as only a fraction of the vast Japanese production, gains of this magnitude need little time to make significant inroads. The climate that is promoting imports to Japan shows no signs of change and the Government can do little in the face of continuing international demand for improved access to Japan's home market.

In 1987 the home market for consumer equipment in Japan exceeded the export market for the first time. This is mainly down to the export market being lost to NIEs and the effect of the strong yen, as well as it being supplied by Japanese manu-

facturers abroad. Export reductions — particularly to the US, now at half their 1985 levels — led to an 11% decline in home production. The reversal in relative importance of imports and exports marks a major change to the structure of the industry.

Home demand has been boosted both by some strong stimulative measures taken by the government and by the introduction of new products — HDTV, digital audio, CD video and DBS receivers. The decreasing likelihood of HDTV being accepted as a global standard will reinforce the domestic market as the major driving force for consumer equipment in the next few years.

In contrast, performance in the field of industrial electronic equipment shows less cause for Japanese concern. Production rose by just under 10% last year with computer peripherals (US markets) and wire communications doing especially well. Domestic demand for the former is also booming and this sector of electronics seems to be relatively trouble-free.

Thirdly comes the component industry. Although exports of all components increased (ironically often through use by those NIE consumer equipment manufacturers), the demand for each area is unstable, with the exceptions of PCBs and LCDs.

There has also been a good deal of trade friction in recent years regarding dumping and subsequent pricing regulations of memory chips between Japan and the US. The semiconductor industry suffers from painful cyclical supply shortages and gluts (we are at present in a DRAM memory famine with prices more than four times their 1986 levels).

Japanese companies lost perhaps \$4 billion in the early eighties by continuing production while US and European companies were moving to other areas. The reward was to massively enlarge the Japanese share of the market and to give them what is now estimated as a two year lead in processing techniques.

With memory demand now booming again only the Japanese have been able to meet demand and large profits have resulted. The Japanese are however well aware that the future is far from assured. Motorola and Siemens are re-starting memory production and NIEs, notably South Korea, are biting increasing large chunks from the market. The future seems to be clouded by political issues to a far greater extent than in the early years of the decade.

For more information contact the EIAJ, 1 Deans Yard, Westminster, London SW1P 3NR. Tel: 01-799 9811.

DIARY



BBC Radio Show — 30th September -9th October

Earls Court, London. 'Spectacular extravaganza' to celebrate 21 years of BBC Radio 1, 2, 3 and 4. Exhibition, live shows, etc. Contact BBC Radio Show, PO Box 100, Chatham, Kent ME5 BLJ

Electronic Displays 88 — October 4-6th

Wembley Conference & Exhibition Centre, London. Contact Blenheim Online on 01-868 4466

Computer Graphics 88 — October 11-13th

Wembley Conference & Exhibition Centre, London. Contact Blenheim Online on 01-868 4466

Digital Signal Processing Seminar — October 13th

Heathrow Penta Hotel, London. Contact ERA Technology on (0372) 374151

Desktop Publishing Show — October 13-15th

Business Design Centre, London. Contact Database Exhibitions on 061-456 8383

ASIC Awareness Seminar — October 17th

London. One of three dates in UK section of tour. Contact organisers and sponsors LSI Logic on (0344) 426544

Satellite Systems For Mobile Communications And Navigation — October 17-19th

IEE, London. Conference organised by IEE. Contact IEE on 01-240 1871

Internecon — October 18-20th

Metropole Exhibition Centre, Brighton. Contact Cahners Exhibitions on 01-891 5051

Southern Electronics Show — October 18-20th

Brighton. Contact Trident International Exhibitions on (0822) 614671

Testmex 1988 (Electronic Testing & Measurement) — October 18-20th

Business Design Centre, London. Contact Network Events on (0280) 815 226

ASIC Awareness Seminar — October 17th

Cambridge. One of three dates in UK section of tour. Contact organisers and sponsors LSI Logic on (0344) 426544

IC Outlook — October 19th

Centre Point Building, London. Market overview seminar. Contact Dataquest on 01-583 9171

ASIC Awareness Seminar — October 17th

Manchester. One of three dates in UK section of tour. Contact organisers and sponsors LSI Logic on (0344) 426544

Commercial Awareness And Business Skills For Young Engineers — October 21-23rd

Strand Palace Hotel, London. Contact IEE on 01-240 1871

SMECTS 88 — October 24-25th

Surface Mount Electronic Components Seminar. Post House Hotel, Heathrow, London. Contact Components Technology Institute on (0425) 73578

INTRON (Irish Electronics Exhibition) — October 26-28th

RDS Main Hall. Contact SDL Exhibitions on Dublin 01-900600

Instrumentation Wembley — October 26-27th

Wembley Conference Centre, London. Contact Trident International Exhibitions on (0822) 614671

ITEX 88 — November 1-3rd

Barbican Centre, London. Information Technology Exchange backed by DTI. Contact Cahners Exhibitions on 01-388 9871

Engineering Products And Technology — November (date to be finalised)

Exhibition and Conference Centre, Doncaster. Contact Trinity Exhibitions on (0895)-58431

Electronic Information Delivery — November 8-9th

Tara Hotel, London. Contact Blenheim Online on 01-868 4466

For KITS & COMPONENTS - Choose the easy way - with

**Send
50p* & SAE
for CATALOGUE
(AUTUMN 1987)**

*refundable with first order

ORDERS: RING (01) 567 8910 - 24 HRS.

ELECTRONIC GUARD DOG KIT



One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would-be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need to obtain supply, instructions and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.

XK125 Complete kit of parts £24.00


DISCO LIGHTING KITS

DL1000K This value-for-money 4-way chaser features bidirectional sequence and dimming 1kW per channel £19.25
DLZ1000K A low-cost uni-directional version of the above. Zero switching to reduce interference £10.80
DLA1 (for DL & DLZ1000K) Optional opto input allowing audio 'beat' light response 77p
DL3000K 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel £15.60

The DLB000K is an 8-way sequencer kit with built-in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80! different sequences including standard flashing and chase routines. The kit includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300 W output per channel.

And the best thing about it is the price.

ONLY £31.50

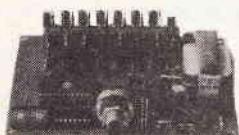

TEN EXCITING PROJECTS FOR BEGINNERS

This Kit has been specially designed for the beginner and contains a SOLDERLESS BREADBOARD, COMPONENTS, and a BOOKLET with instructions to enable the absolute novice to build TEN fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.

ORDER NO XK118 £15.00

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box. 18 time settings.

CT6000K £47.20
XK114 Relay kit for CT6000, includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £4.30
701 115 Additional relays £1.80



VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2 cms. The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 80ft. Two keyboards are available - MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used.

MK12 IR Receiver (incl. transformer)

£16.30
£7.50
£2.20
£6.55
£2.60

HOME LIGHTING KITS

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting.

TDR300K Remote Control Dimmer £18.00
MK8 Transmitter for above £5.10
TD300K Touchdimmer £9.30
TS300K Touchswitch £9.30
TDE/K Extension kit for 2-way switching for TD300K £2.95
LD 300K Light Dimmer £4.75

POWER STROBE KIT

Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality PCB, components, connectors, 5W's strobe tube and full assembly instructions. Supply: 240V ac. Size: 80 x 50 x 45.

XK124 STROBOSCOPE KIT £13.75

DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3' digital liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches required - details supplied) or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading, automatic polarity and overload indication. Typical battery life of 2 years (PP3).



£17.00

XK113 MW RADIO KIT

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms.

Requires PP3 9V battery.

IDEAL FOR BEGINNERS £6.60

PROPORTIONAL TEMPERATURE CONTROLLER KIT

Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max. load 3kw (240V ac). Temp. range up to 90°C. Size: 7x4x2.5cms.

MK4 £7.80

BARGAIN COMPONENT PACKS

Refill those empty component drawers at a fraction of the normal price and don't be caught without that odd resistor or capacitor to complete your project. All components supplied are to full spec, and are not seconds or surplus stock.

Pack A: 650 x 25 watt resistor 47R-10M £4.25

Pack B: 60 x Radial electrolytes 1uf. 1000uf £3.25

Pack C: 30 x Polyester capacitors a or 0.01 uf-1uf £4.50

Pack D: 35 x horizontal presets 1k-1M £3.00

Pack E: 30 x IC sockets 8, 14, 16 pin £2.00

Pack F: 25 x Red 5mm LEDs £1.75

Pack G: 25 x Green LEDs £2.00


Pack H: 30 x 5mm LEDs 10 Red, 10 Green, 10 Yellow £2.50

Pack J: 50 x 1N4148 silicon diodes £1.00

Pack K: 40 x npn/pnp transistors BC182/212 General Purpose £2.25

Solderless Breadboard (verobloc type).

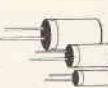When you buy all ten packs, Prices exclude VAT (15%).



GIANT SOLAR CELLS

NOW IN STOCK these giant solar panels 12 x 12ins will deliver over 12 volts 200mA in bright sunlight and 11.5 volts 60mA on a typical British summer day (clouds and overcast). In bright sunshine we measure 17 volts (open circuit) and a short circuit current of over 480mA. HUNDREDS OF USES IN THE CAR OR CARAVAN, E.G.

Charging NiCads, powering low voltage circuits where mains or battery supplies are inconvenient or coupled to a lead acid battery and a simple inverter you could build yourself a self contained mains supply for low power appliances.

£14.50

(+ £1.75 p&p on total order)

Stock No. 303 145

£5.70

(+ £1.75 p&p on total order)

£5.70

(+ £1.7

*Next Month
in*



**ELECTRONICS
TODAY INTERNATIONAL**

**December ETI
— out —
November 4th**

A Touch Of Spring For Winter

The December issue of ETI continues some of the themes in this month. There's the next part of the Burglar Buster free project with the constructional details and the PCB free on the cover. To continue the speed measuring theme (see the Chronoscope in this issue) we have the first DIY radar speed gun. Good for both vehicles and fast moving friends, this portable unit gives direct readout in miles per hour.

For those dark winter nights there's an all-electronic thermostat to drag your central heating system into the eighties. A simple wire-in replacement for most of those yukky mechanical jobs, the ETI thermostat gives you accurate heating control and even tells you the temperature.

Is that all? Of course not. The December ETI is brimming over with goodies to make the winter seem shorter. There's the usual favourites — Chip In and Circuit Theory plus the News stories that matter, the readers' letters that natter and reviews that are really good (well you try and think of a suitable work to rhyme with 'atter'. Answers on a postcard, please . . .)

Winter wouldn't be the same without ETI. Don't miss your copy.

The articles mentioned above are in preparation but circumstances may prevent publication

Make A Date

It's competition time again — and time is the right word (as are date and year) because this month ETI has teamed up with Maplin to give away six of Maplin's 200 year calendar clocks to lucky readers who can solve the cryptic puzzle below.

These clever and stylish clocks feature 12 or 24 hour time display along with date and year and a complete calendar for the current month. There's an alarm built-in too with a four minute snooze.


It's an ideal way to keep track of time and a certain way to be sure you never miss that all important first Friday of the month when ETI is published!

Winning one of these clock/calendars couldn't be simpler. All you have to do is to match up the ten dates below with the ten cryptic descriptions on the entry form. So, if you think that 'Old long since' is referring to 4th November write '4/11' next to the first clue. When you've matched up all ten dates in the list, fill in your name and address and send the coupon, to arrive no later than 7th November, to:

ETI Clock/Calendar competition
1 Golden Square
London W1R 3AB

The first six correct entries out of the editor's deerstalker will win a clock/calendar each.

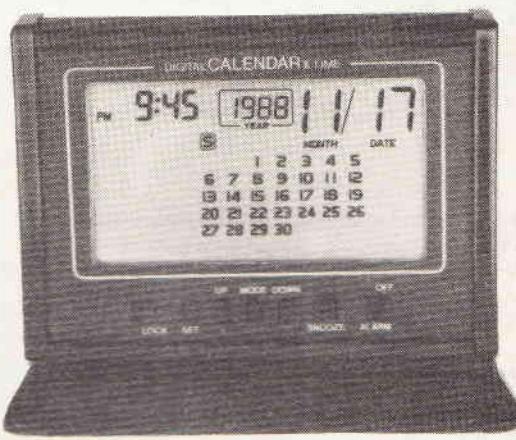1/4 24/12 31/10 14/2 19/6
4/11 31/12 1/5 5/11 11/11



Maplin

| | | | |
|----------------|--------------------------|---------------------|--------------------------|
| Old Long Since | <input type="checkbox"/> | Remember, Remember | <input type="checkbox"/> |
| Massacre | <input type="checkbox"/> | Fools | <input type="checkbox"/> |
| Great Ending | <input type="checkbox"/> | Next ETI | <input type="checkbox"/> |
| Red | <input type="checkbox"/> | Spooky | <input type="checkbox"/> |
| Silent Night | <input type="checkbox"/> | Garfield's Birthday | <input type="checkbox"/> |

Name

Address

CONTROL STRATEGIES

Although micros now seem to rule our lives, they can't do everything. Keith Brindley shows how analogue techniques in systems control will never be overtaken by those nasty little bits

Fortunately for us, most things in the real world are analogue. Digital techniques can only be utilised to good advantage in the approximation of how they function. Analogue techniques still need to be considered, even if a digital representation is to be the final result.

Control

Any electronic system requires control of some sort. Whether it's a simple power supply or a guided missile, some internal part controls the output. In the power supply, voltage regulation and stabilisation ensure

load in the case of the power supply, or wind direction in the case of a guided missile.

Second is known as *feedforward control* shown in Fig.1b where factors which might change are monitored and actions are taken to counteract the effects of the changes. This method is still a 'point and shoot' procedure but the system is adapted according to the factor changes.

Finally, Fig.1c shows *closed-loop control* sometimes called 'feedback control' in which part of the final output is compared with the requirements and a control signal (sometimes called an error signal) adjusts the system.

Of the three strategies, the closed-loop one is arguably the best because it alone measures the effects of the outside factor changes. Feedforward control measures the factor change itself, re-aligning the system to suit. Open-loop control, of course, takes no effects into account at all.

This is not to say that feedback control must be used as the control strategy. Far from it, feedforward control is very effective as long as only a few factor changes occur — and can be a lot cheaper than equivalent feedback control systems. The problem arises when there are too many factor changes (so that measuring and correcting circuits become too involved and expensive) or when unforeseen factors change and no correcting circuits exist, or when gain variations occur. Often, a combination of feedback and feedforward methods is used.

Defining Feedback

Most readers will be aware of feedback (it's how all op-amps function) but a quick definition of terms involved wouldn't go amiss. Fig.2 shows a general block diagram of a feedback system and can represent anything from a single op-amp circuit to a complex stage in a large control system. The amplifier has a gain of G and the feedback has a gain H . The input i is summed with the output of the feedback loop f , such that an error signal e is produced, where:

$$e = i - f$$

Note that the error signal is input minus feedback. This means that the system is a 'negative feedback' system. The minus sign can be thought of as signifying that the output signal has been inverted, or turned through 180° . This is an important point. Positive feedback systems exist of course but are usually only used in oscillators and such like.

We can work out, that:

$$f = oH \text{ and } o = eG$$

so:

$$e = i - eGH$$

which, rearranging, gives the system error:

$$e = \frac{i}{1 + GH}$$

If the quantity GH (known as the 'loop gain') because it is the overall gain of the closed loop) is large then the 1 in the denominator is irrelevant, so $e = i/GH$. Conversely, the input $i = eGH$.

Now, the output $o = Ge$, which means we can generalise the system gain (because gain = output/input) as: Ge/eGH or $1/H$. That is, so long as the loop gain is large, the system gain becomes entirely independent of the amplifier gain. So, the general closed loop feedback system can be represented by a single block, as shown in Fig.3.

The fact that gain variations can be made virtually irrelevant is the real reason why closed loop feedback systems represent the most versatile control strategy.

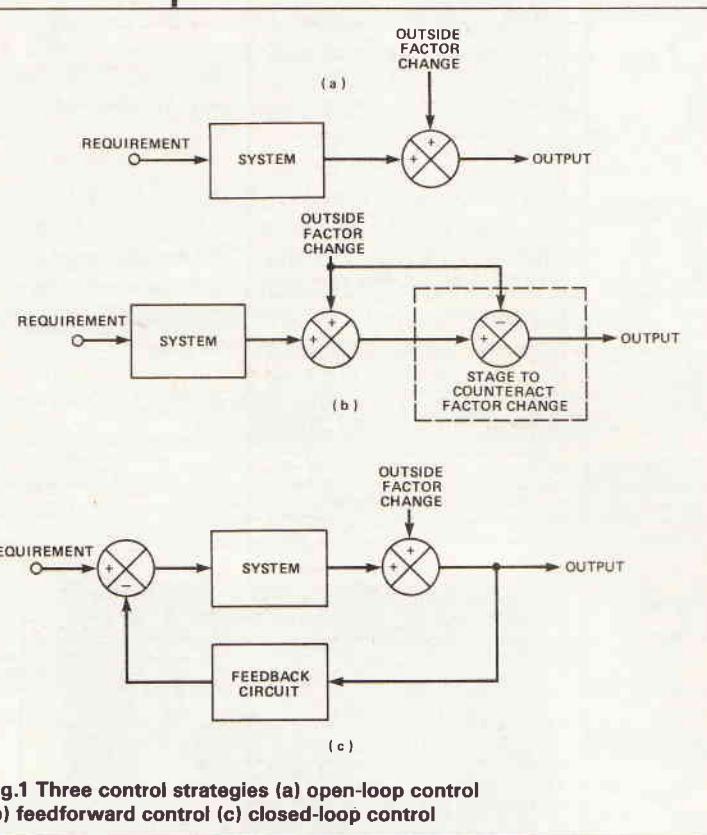


Fig.1 Three control strategies (a) open-loop control
(b) feedforward control (c) closed-loop control

smooth DC voltage output. In the guided missile some technique ensures the missile hits the target.

There are three basic strategies used in any controlled system. Readers will probably be familiar with the strategy names although it's still worth summarising what they are. First is *open-loop control*, shown in Fig.1a. It's a sort of 'point and shoot' method in which the output of the system is specified and the system merely attempts to achieve it. If all things remain equal, open-loop control will produce the required output. However, open-loop control does not take into account factors which may change —


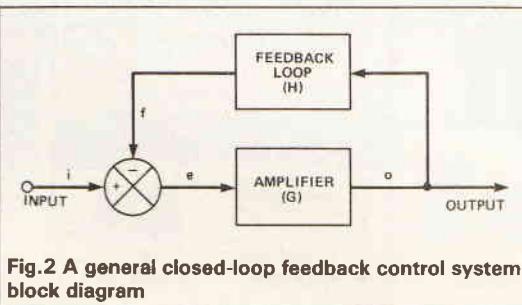


Fig.2 A general closed-loop feedback control system block diagram

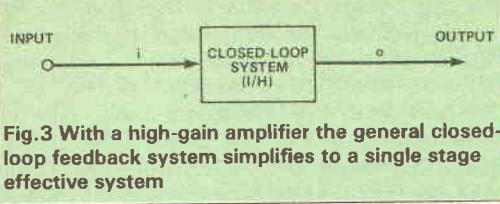

Stability

In a simple system comprising one or even two feedback stages, stability (or rather lack of it) is usually no problem but in more complex control systems, with perhaps three or more stages, a potential exists for instability. The problem is that any closed loop feedback system has a phase shift between input and output. Further, this phase shift is not constant but varies with applied signal frequency.

Generally, instability will occur if at any particular frequency a total phase shift of 360° occurs when overall gain is equal to or greater than unity. At a phase shift of 360° , the negative feedback has, in effect, turned into positive feedback and so the system will tend to instability, oscillating or even locking up at the frequency at which it occurs. If we remember the introduction to negative feedback given previously, we know that negative feedback is the equivalent of a 180° phase shift in the feedback loop, so only a 180° phase shift in the overall system will create a total of 360° phase shift.

How can the designer tell if a system is going to be unstable except by building the thing and turning on? Well, there are complex mathematical methods of modelling system performance but there is an extremely simple graphic approach which will do equally as well. This concerns Bode plot diagrams, which many readers will be familiar with. These show a circuit's performance in two graphs — one of gain variation in decibels with frequency and one of phase shift with frequency. Fig.4 shows an example. It's the fact that any frequency phase shift as well as gain is represented that allow the Bode plots to be of use.

Initially, the whole closed-loop system has to be considered without its feedback loop — as an open-loop system. Fig.5 shows an example of a three-stage control system without its feedback loop. Fig.6 shows Bode plots of all three stages, plotted on one pair of Bode plots. Let's say that the Bode plot of the first stage of Fig.5 is that of a second-order high-pass filter (it has a roll-off of 40dB per decade and phase shift up to 180°). The second stage is a perfect amplifier, with gain of 7.5dB and a bandwidth greater than the limits of our Bode plots, so no phase shift occurs. The final stage is a first-order low-pass filter with a roll-off of 20dB and phase shift up to 90° . None of the individual plots show any tendency to instability because the phase shift in any single plot is never as high as 180° with unity gain (0 dB).

Now, with series coupled gain stages (as these three stages are) the overall gain can be calculated simply by multiplying together the individual gains. However, because the first of the two Bode plots has a vertical axis of gain in dB (it is logarithmic) the overall gain can be plotted linearly simply by adding the three gains together. Similarly, as the vertical axis of the second of the two Bode plots is a linear measurement of phase the overall phase shift can be calculated by adding the three phase shifts.

The final pair of Bode plots becomes that of Fig.7. This shows that a phase shift of 180° occurs at a frequency of 2.2kHz, when the gain is unity. That, plus the 180° phase shift of the negative feedback loop itself when the feedback loop of Fig.5 is closed,

means that a total of 360° of phase shift occurs. So, according to this estimate, when the feedback loop is closed, the system experiences positive feedback at that frequency and will oscillate!

That's all well and good you may say, but this estimate is based on an open-loop. So how do we really know what will happen to the system when the feedback loop is closed? Is our estimate good enough?

Fortunately, control engineers have evolved another graphical method of interpreting theoretical results. It is known as the *Nichols chart*, which is simply a collection of open-loop gain and phase shift data, corresponding to the resultant closed-loop gains and phase shifts. A Nichols chart is shown in Fig.8 where the horizontal axis is of open-loop phase shift, while the vertical axis is of open-loop gain. On top of these perpendicular axes are superimposed a large number of plots of closed-loop phase shifts and gains.

Its use is pretty simple, although tedious. From the results of the final pair of Bode plots from the previous example, plot a line of points corresponding to gain and phase shift at a number of frequencies.


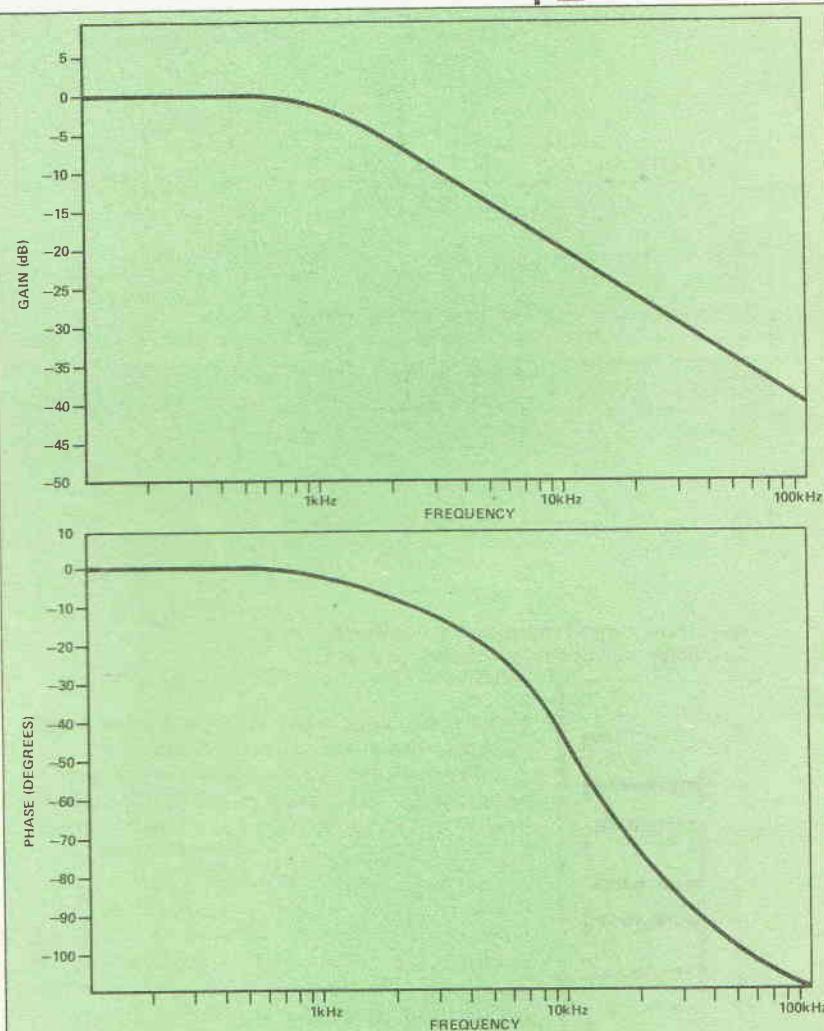


Fig. 4 A possible pair of Bode plots. The upper plot has gain (in dB) as the vertical axis with frequency as the horizontal axis. The lower plot has phase shift (in degrees) as its vertical axis

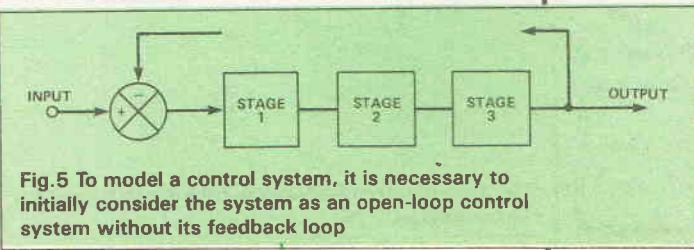

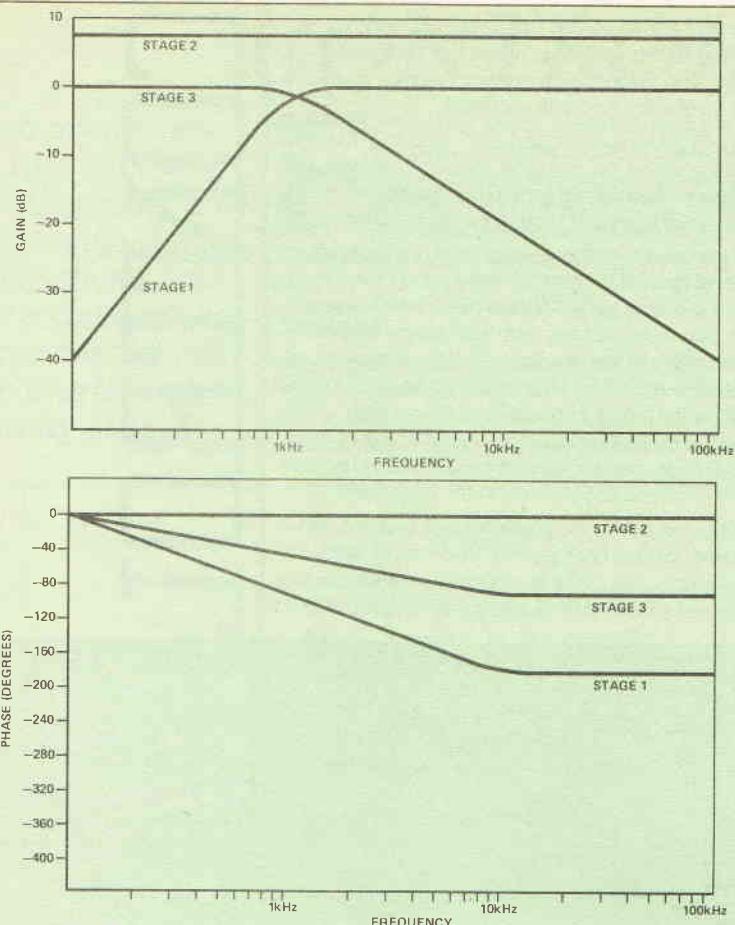


Fig. 6 The Bode plots of the three stages of the system of Fig. 5

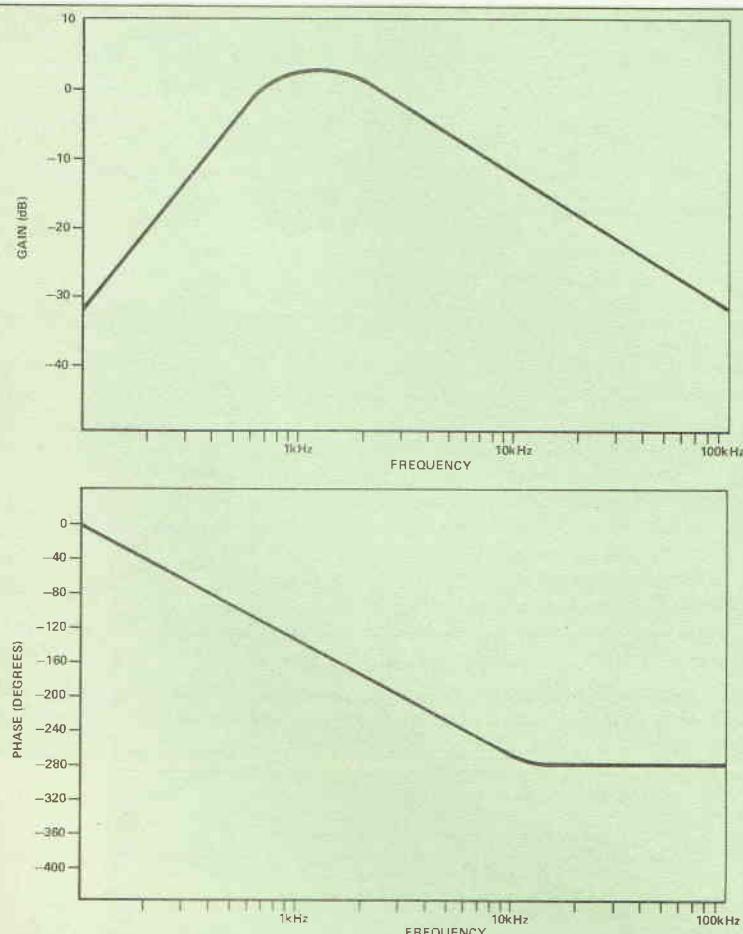


Fig. 7 Estimate of final pair of Bode plots of the system in Fig. 5, found by adding together gains and phase shifts of all three pairs of plots at each frequency

This is shown in Fig. 8. Generally, you should always mark the frequencies on the Nichols chart, too. But as room is limited here, frequencies aren't marked in Fig. 8 but the direction of increasing frequency is — this is important, as we'll see later.

Now from the closed-loop axes, take off measurements of gain and phase shifts at those frequencies and re-plot them onto a new pair of Bode plots, as in Fig. 9, to see what the closed-loop frequency response is really like. As we would expect, the phase shift amounts to 180° at 2.2 kHz, when the gain is a few dBs above unity gain. So, this method proves the system will be unstable too.

Incidentally, control engineers have a rule-of-thumb when using Nichols charts which alleviates the need to re-draw the closed-loop response on a final Bode plot. This is: if the closed-loop frequency response phases to the right of or intersects the $0\text{dB}/-180^\circ$ open-loop intersection when viewed in the direction of increasing frequency, the system is unstable. In the example of Fig. 8, the curve intersects the intersection, so we know the system is unstable. However, if stage 2 of the system had a lower gain then the curve would have passed to the left of the intersection and so the system would have been stable. With experience, control engineers can read information from a Nichols chart as easily as from a Bode plot.

The amount by which a stable system's response passes to the left of the intersection can be referred to as a 'gain margin' — the amount of gain which, if added to the system, would cause the response curve to pass through the intersection. Alternatively, it can be referred to as the 'phase margin' — the amount of extra phase shift which, if added to the system, would cause the curve to pass through the intersection.

Controllers

In the simple systems we have looked at so far, stages have been little more than amplifiers or filters. There are many more types of stages used in control systems. For example, often a stage may follow a mathematical equation of an integrator, in that the output is an integral of the input. The stage could be modelled by the expression:

$$\text{output} = \frac{1}{T_i} \int_0^T \text{input } dt$$

where T_i is the integral time of the controller, generally adjustable with front panel controls or presets.

Other types may be 'proportional' — the output is simply the input multiplied by a constant factor (a simple amplifier is a proportional controller), again adjustable with controls.

Others may be 'derivative' in that the model is one of mathematical differentiation, following the expression:

$$\text{output} = T_d \frac{di}{dt}$$

Some controllers are combinations of more than one type, the most common probably being the 'proportional plus integral' controller, also known as the 'P+I' controller or simply the 'PI' controller and may be modelled by the expression:

$$\text{output} = K(\text{input} + \frac{1}{T_i} \int_0^T \text{input } dt)$$

Similarly, the 'proportional plus integral plus derivative' controller or P+I+D or PID controller is common. In fact, generally speaking, any mathematical model can be used as a control system stage, given that the electronic circuit equivalent can actually be made.

Which controller to use in any given system depends largely on the system, of course, and it's the

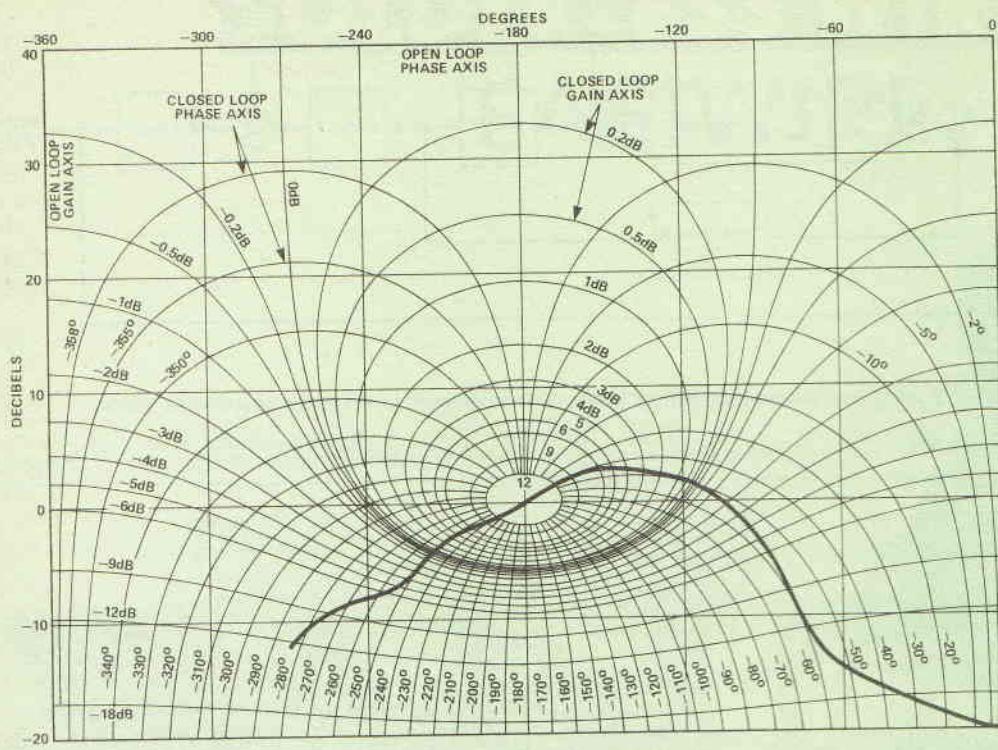


Fig.8 A Nichols chart showing open and closed-loop gain and phase shift axes with a frequency response curve, taken from the results of the Bode plots of Fig.7, transferred onto a Nichols chart

engineer with skill and experience who must design the control system to suit.

Loop De Loop

Single-loop closed-loop control systems, as we've seen, can be complicated enough. Sometimes, the engineer has to resort to a more complicated version of the closed-loop strategy.

The problem arises because the single-loop system is sometimes affected by disturbances within the control loop. Thinking back to the general closed-loop feedback system of Fig.2 and 3, the stage gain is specified as $1/H$ as long as the amplifier gain G is sufficiently high. In reality other factors matter too. The simplified expression relies on applied signals being within a specified bandwidth and disturbances at some places within the loop have a greater effect than at others. Also, it's not always the case that a sufficiently high gain is available or possible within the bounds of the overall system performance.

The answer to the problem is constructing multi-loop closed-loop systems. Such methods are often used where disturbances would otherwise be uncontrollable. Fig.1 shows 'cascade control' in which two control loops exist, one within the other. Two controllers are used, one for the inner loop and one for the outer. Of course, cascade control is only possible if there is some intermediate stage capable of being controlled. Large disturbances within the inner loop can be effectively reduced, particularly as the loop gain of the inner loop may be very much higher than that of the outer loop without affecting overall system performance so the disturbance may then come within the bounds of controllability of the lower gain outer loop.

Often cascade control is used to reduce the time constant of a part of the process, although the inner loop should generally only be placed around the component with the smallest time constant.

Overall benefits of cascade control are a wider bandwidth, with significantly greater reduction of

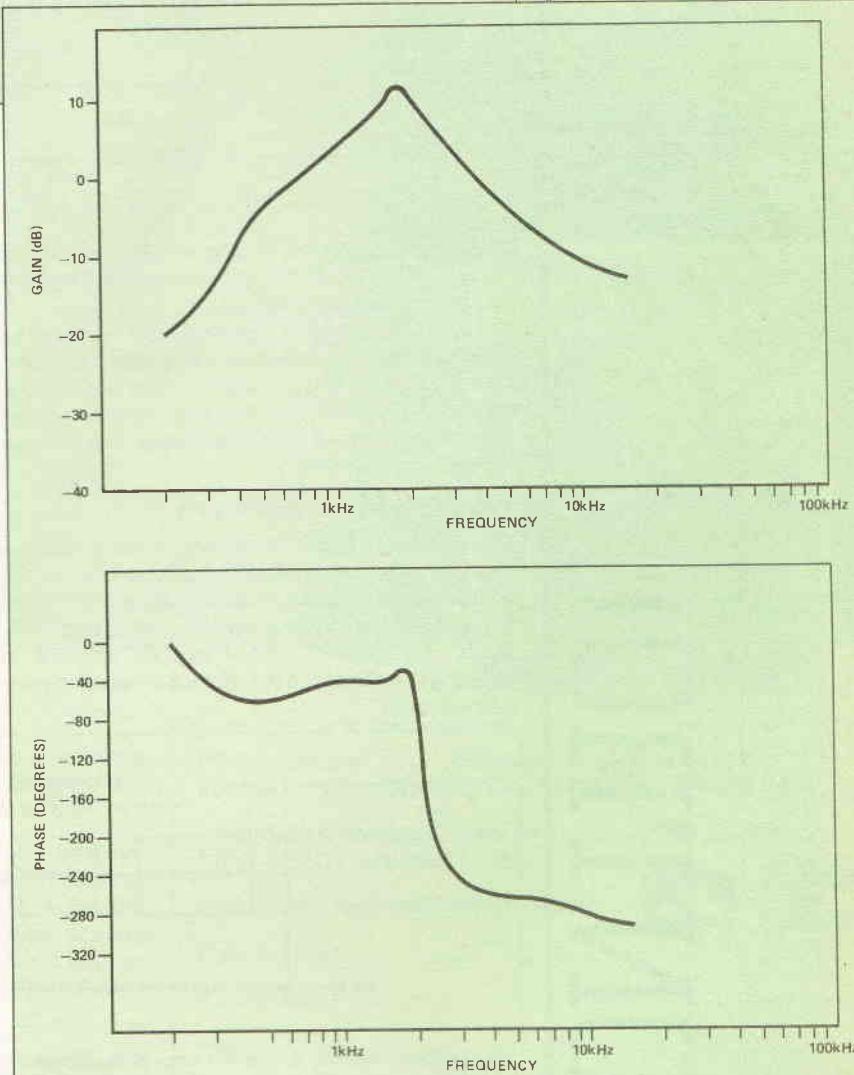


Fig. 9 Final Bode plot estimate of closed-loop frequency response of the system of Fig. 5 when its feedback loop has been closed. Taken from closed-loop response as shown on the Nichols chart of Fig. 8

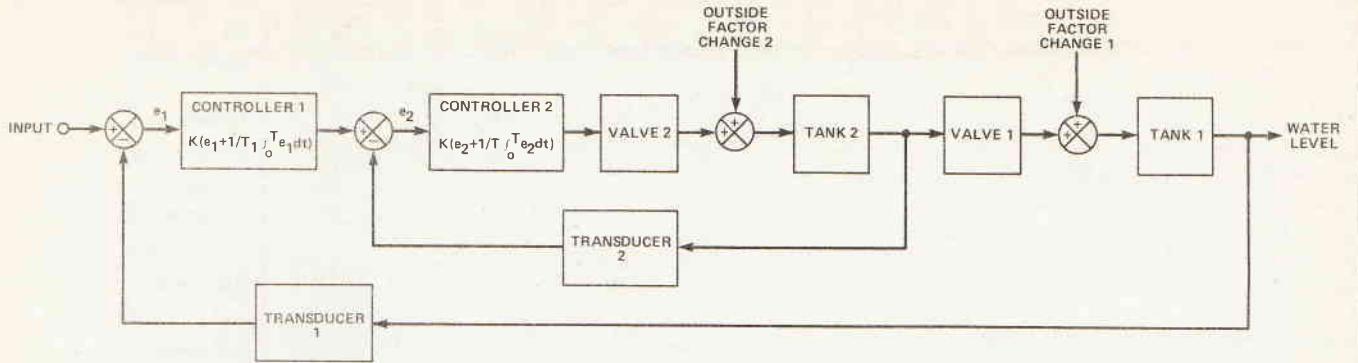


Fig.10 An example of cascade control, a multi-loop closed-loop control strategy. Disturbances in the inner loop may be greatly reduced by cascade control

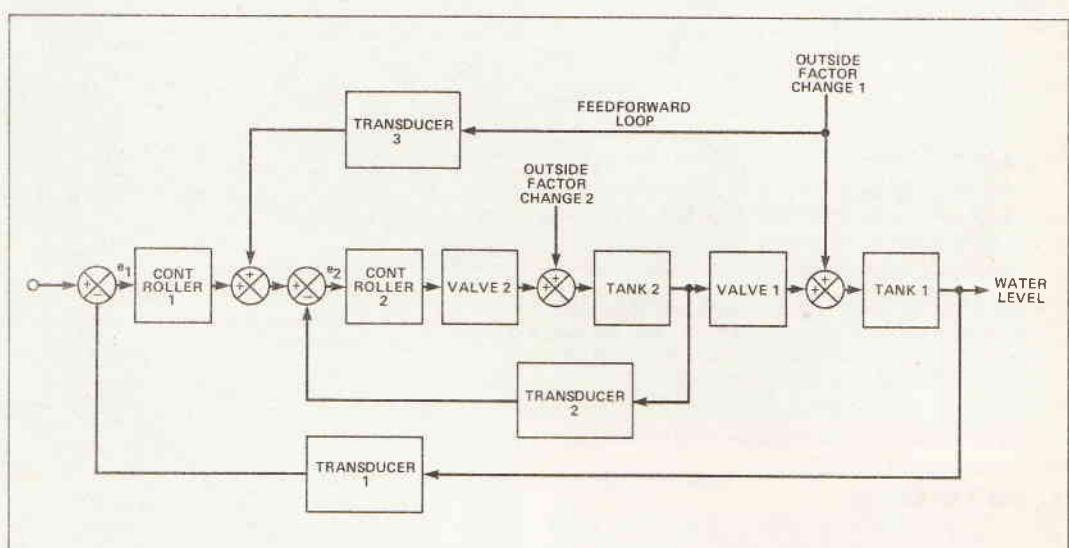


Fig. 11 Feedback control, used with the cascade control example of Fig. 11 to reduce the effects of disturbances which take place outside the inner cascade loop

inner loop disturbances. More and more loops can be used, if enough intermediate stages exist. However, each cascade as you might expect makes the engineer's job more difficult in that modelling of the system and consequent stability forecasting become increasingly complex.

Feeding More Forward

Finally, let's not forget feedforward control, where a disturbance is measured before it has an effect on the control system and counteracting measures are taken. Coupled with a cascade control system such as in Fig. 11, feedforward control can be effective in reducing the effects of a disturbance outside the inner cascade loop.

One specific example of feedforward control is 'ratio control'. Here a control system is used to maintain the ratio of two variables. A possible system might exist in a car's fuel injection system, where the ratio of fuel to air must be strictly maintained so as to ensure the correct mixture is always taken into the engine's combustion chamber. Fig. 12 illustrates such a system. The mass of air being sucked into the engine is measured, the amount of fuel required to give correct fuel-to-air ratio is then calculated by a controller and a valve (the fuel injector) ensures exactly the right amount of fuel is added.


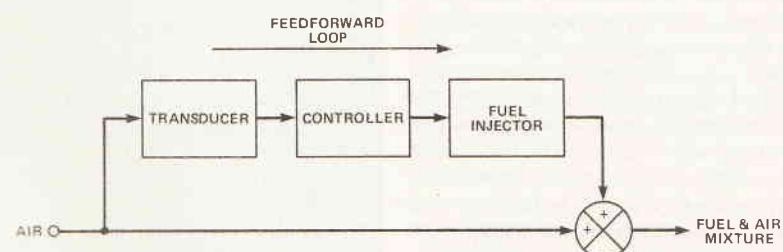


Fig. 12 Ratio control. A specific case of feedback control used to control the ratio of two variables in a control system. The example shown is of an automobile fuel injection system in which the incoming air mass is measured and from this measurement a controller calculates the length of time a fuel injection valve must be opened to present the correct amount of fuel to the combustion cylinder such that exactly the correct ratio of fuel-to-air is sucked into the cylinder

controller calculates the length of time a fuel injection valve must be opened to present the correct amount of fuel to the combustion cylinder such that exactly the correct ratio of fuel-to-air is sucked into the cylinder

SOLDERLESS WIRING

EASIWIRES

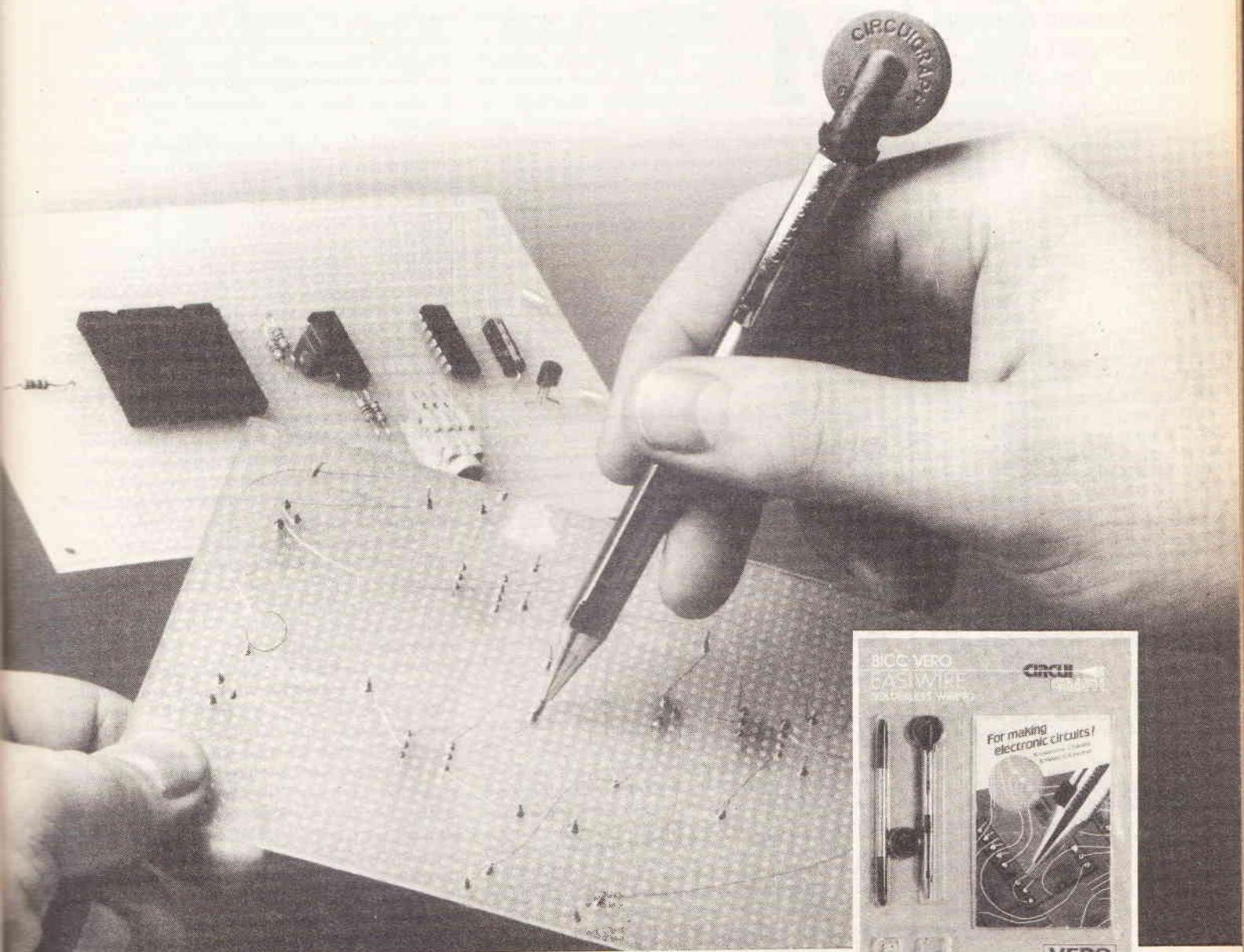

Construct your electronic circuits the new, quick and easy-to-learn way, **WITHOUT** solder: with Circuigraph Easiwire from BICC-VERO

With Easiwire all you do is wind the circuit wire tightly around the component pins. No soldering, no chemicals, no extras, simplicity itself. Circuits can be changed easily, and components re-used.

Easiwire comes in kit form. It contains all you need to construct circuits: a high-quality wiring pen with integral wire cutter, 2 reels of wire, a tool for component positioning and removal, a flexible injection moulded wiring board, double-sided adhesive sheets, spring-loaded terminals and jacks for power connections and an instruction book. Of course, all these components are available separately too.

To take advantage of the special introductory offer, complete the coupon on the right and send it to:

BICC-VERO ELECTRONICS LIMITED,
Flanders Road,
Hedge End,
Southampton, SO3 3LG



Please rush me Easiwire kits, retail price £18.-; **special introductory offer £15.-** (includes p & p and VAT).

I enclose cheque/postal order for made payable to BICC-VERO Electronics Limited

Please debit my credit card as follows:



Card Number

Expiry Date

Name

Address

Signature

or phone 04892 88774 now with your credit card number
(24-hour answering service).

THE NORTON DIFFERENCE

Ray Marston presents the first part of his guide to the current differencing op-amp

Most popular op-amps (Fig. 1a) give an output proportional to the difference between their two input terminal voltages and are thus known as voltage-differencing amplifiers or VDAs. There is however a type of op-amp which gives an output voltage proportional to the difference between the currents applied to its two input pins.

These devices are known as current-differencing amplifiers or CDAs. Figure 1b shows the standard symbol of the CDA, also known as a Norton op-amp.

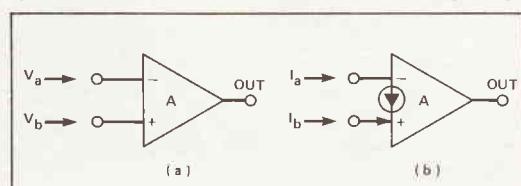


Fig. 1 (a) A conventional op-amp.
(b) A Norton op-amp

The two best known Norton op-amps are the LM3900 and the LM359. The LM3900 is a low-cost medium performance IC that houses four identical op-amps in a 14-pin PIL package (Fig. 2) and can operate from a single-ended 4–36V power supply. Each of its op-amps has a unity-gain bandwidth of 2.5MHz with an open-loop gain of about 70dB, and gives a large output voltage swing. This IC is particularly useful in DC and low frequency applications where several op-amp stages are needed in single-ended supply circuits.

On the other hand, the LM359 is a very fast dual Norton amplifier in which each op-amp has a unity-gain bandwidth of 30MHz with an open-loop gain of about 72dB, and in which most of the op-amp parameters are externally programmable. This IC is particularly useful in video and high frequency amplifier/filter applications.

The LM3900 and LM359 operate in a very different way to conventional op-amps and require the use of special biasing techniques. We will first take a look at the LM3900 and next month we'll move on to the faster LM359.

Inside The Box

The LM3900 incorporates four identical current-differencing op-amps, each having the circuit shown in Fig 3. To aid understanding of the complete circuit, Fig. 4 shows six simple stages in the development of the final design.

Figure 4a shows a basic inverting amplifier circuit. Q1 is a common emitter amplifier with a high-impedance (constant-current) collector load, and gives a high-gain inverting action. Q2 is an emitter load. The high frequency response of the complete amplifier is rolled off by C1, to enhance circuit stability.

Note that the output of this circuit can swing to within a few hundred mV of both zero and the positive supply rail voltage, and that its overall current gain equals the product of the two transistor current gains.

Figure 4b shows how the current gain of the above circuit can be increased with little loss of available output voltage swing, by adding PNP

transistor Q3. The output of this circuit can typically source up to 10mA (via Q2) but can sink only 1.3mA (via Q2's constant-current generator).

Figure 4c increases the sink current by wiring Q4 so that in over-drive conditions it gives class-B operation.

Figure 4d shows transistors Q5 and Q6 used as constant-current generators (biased via a network that is built into the LM3900 IC).

Current Mirrors

The Figure 4d circuit forms the basis of each of the LM3900 amplifier stages, but gives an inverting action. The non-inverting LM3900 requires the assistance of the current mirror circuit of Figure 4e, which is made up of two matched and integrated transistors and simply draws an output current that is almost identical to the input drive current.

The input current is fed to the bases of both Q7 and Q8. Let's say both have current gains of $\times 100$, and both are drawing base currents of $5\mu\text{A}$. In this case both collector currents are $500\mu\text{A}$ plus both base currents. The input and output currents of the circuit are thus almost identical (within a few percent), irrespective of the input current magnitude.

Figure 4f shows the current mirror circuit connected to the basic Fig. 4a circuit to give the current-differencing action of the Norton amplifier. The mirror circuit is driven via the non-inverting input terminal, and the mirror current is drawn from the inverting input terminal, also connected directly to the base of the Q1 amplifier stage. Consequently, the base current of Q1 equals $I^- - I^+$. This is the difference between the two input currents. The complete amplifier (back in Fig. 3) thus gives the current-differencing op-amp action already mentioned.

Note that since both input terminals of the op-amp are connected to transistor base-emitter junctions, both inputs act (in voltage terms) as virtual-ground points. Consequently, these CDA circuits can be made to act like conventional voltage-differencing op-amps by wiring high-value resistors in series with their input terminals, so that the input currents are directly proportional to the input V/R values. When this technique is used, there is no upper limit to the

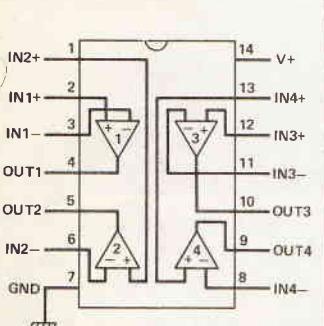


Fig. 2 Connections of the LM3900 quad Norton op-amp

NORTON

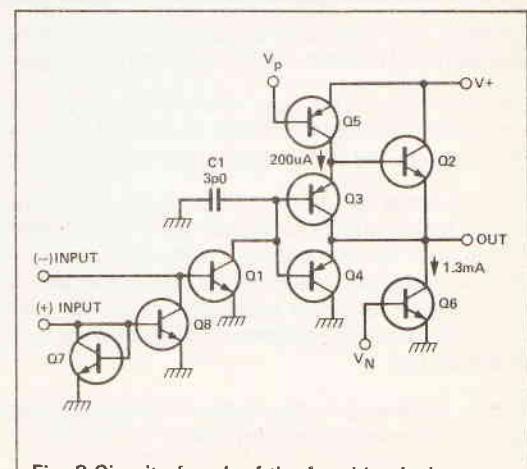


Fig. 3 Circuit of each of the four identical op-amp stages of the LM3900

NORTON

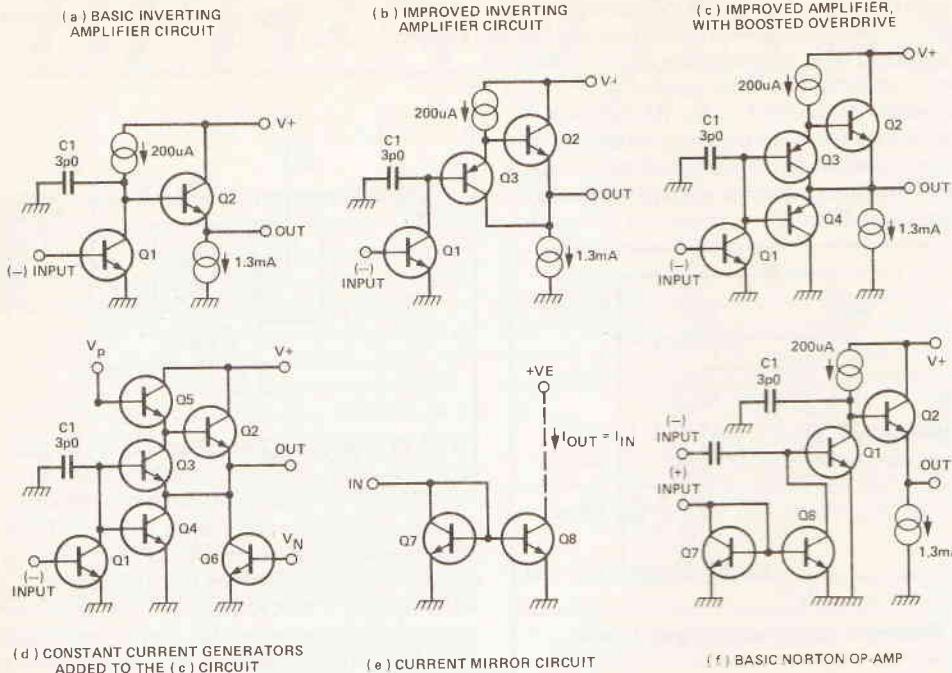


Fig. 4 Development of the LM3900 op-amp circuit

available input common-mode voltage range of the LM3900 op-amp.

Biassing Techniques

The basic amplifier stages of the LM3900 have high current gains, and the output of the amplifier starts to swing down through the half-supply point when the input bias current of Q1 starts to rise above 30nA or so. This input current is normally equal to the difference between the two input terminal currents, which should normally be restricted to the range 0.5 μ A to 500 μ A (ideally about 10 μ A).

In linear applications an op-amp is normally biassed so that its output takes up a quiescent value of half-supply volts to accommodate maximum undistorted signal swings, and Fig. 5a shows how the LM3900 can be biassed to meet this condition.

R1, R2 and C1 generate a decoupled half-supply reference voltage, which applies a reference current to the non-inverting terminal via R3, and a negative feedback current is applied from the op-amp output to the inverting terminal via R4. The basic action is such that the op-amp output automatically adjusts to such a value that the two input currents equalise and hence reduce the internal Q1 base current to near-zero (about 30 μ A) — in Fig. 5a this occurs when V_{out} equals V_{ref} . In practice, the single reference voltage source can be used to apply biassing for several op-amp

stages.

A variation of this biassing system is shown in Fig. 5b. The non-inverting terminal is biassed from the positive supply rail via R1, which has a value approximately double that of R2, causing the output to bias at a quiescent value of half-supply volts. A minor defect of this biassing technique is that it allows supply line ripple to break through to the output, with gain of 0.5.

Note that in Figs 5a and 5b, the input signal is shown connected to the inverting terminal of the amplifier, but in practice the signal can be connected to either input.

Figure 5c shows an alternative biassing technique that can be used when the op-amp is to operate only as an inverting amplifier. In this case the non-inverting terminal is disabled, and feedback potential divider R1, R2 is applied between the output and the inverting terminal. Consequently, since the inverting terminal acts as a transistor base-emitter junction (V_{be} , about 0.55V at 10 μ A bias), the output automatically takes up a quiescent value of $V_{be} \times (1 + R1/R2)$. This is about 6V with the component values shown.

Linear Amplifier Circuits

Six ways of using the LM3900's op-amps as linear amplifiers are shown in Figs 6 to 11. In Figure 6, R2 and R3 bias the output to a quiescent half-supply

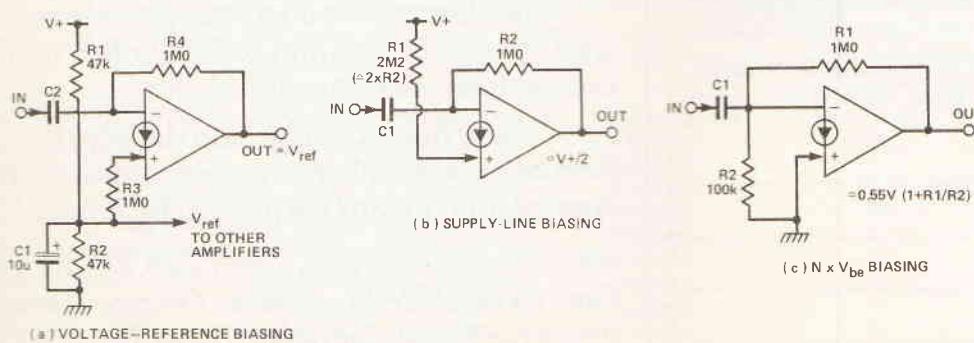


Fig. 5 Methods of biassing LM3900 op-amps for linear operation

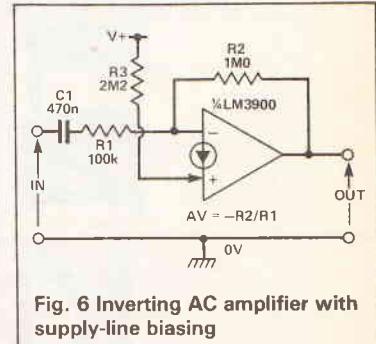


Fig. 6 Inverting AC amplifier with supply-line biassing

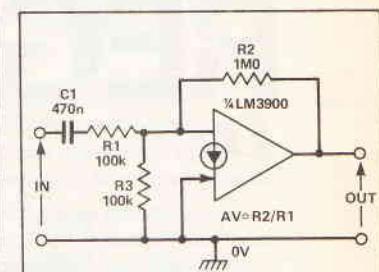


Fig. 7 Inverting AC amplifier with $N \times V_{be}$ biassing

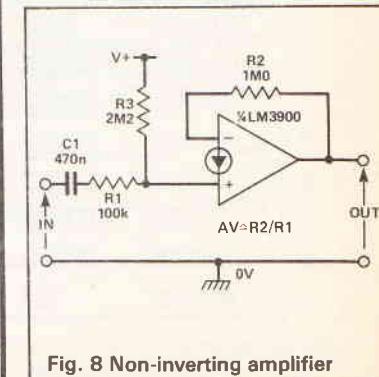


Fig. 8 Non-inverting amplifier

NORTON

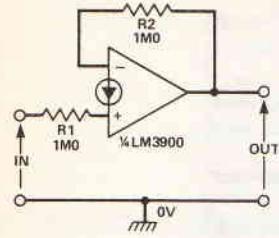


Fig. 11 DC voltage-following buffer

value, and the input signal is fed to the inverting terminal via R1. The voltage gain is determined by the R1, R2 ratio — this acts as a $\times 10$ inverting amplifier.

Figure 7 shows an alternative $\times 10$ inverting amplifier, in which biasing of the type in Fig. 5c is used and the gain is determined by the R1, R2 ratio.

Figure 8 shows a non-inverting amplifier with a gain of approximately ten. Supply-rail biasing is again used, but the input signal is applied to the non-inverting pin via R1.

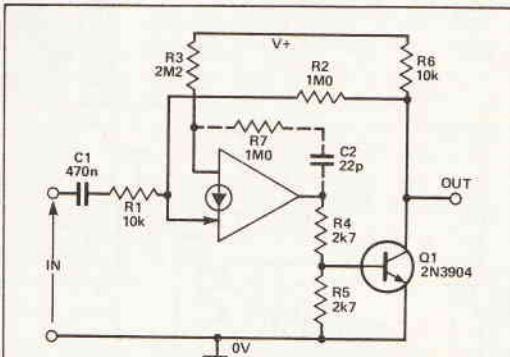


Fig. 9 Wideband (200 kHz) high-gain ($\times 100$) amplifier

The LM3900 op-amps are fairly slow devices with slew rates of only $0.5V/\mu s$, and thus very limited useful bandwidths. Figure 9 increases the useful bandwidth by connecting an external common emitter transistor to the output and transposing the input connections of the standard amplifier. This makes a $\times 100$ 'compound' amplifier with a 200kHz bandwidth.

Because of its very high overall gain, this circuit

may be unstable if care is not taken in layout. R7 and C2 can be used to slightly reduce the bandwidth and enhance stability if required.

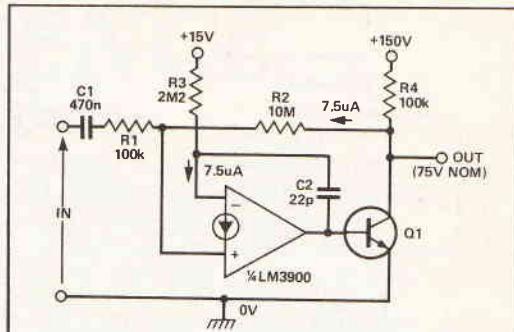


Fig. 10 High-voltage amplifier with $\times 100$ gain

Figure 10 shows the same circuit modified to give a peak-to-peak output voltage swing of 150V (or whatever voltage is used to power Q1). Note that the output voltage of this circuit has a quiescent value of 75V, causing $7.5\mu A$ to be fed to the non-inverting terminal of the op-amp via R2. To give correct biasing, R3 (powered from the 15V supply rail of the op-amp) must also apply $7.5\mu A$ to the inverting pin of the op-amp, as shown.

Finally, Figure 11 shows how to connect an LM3900 op-amp as a unity-gain non-inverting amplifier or voltage following buffer. The input is connected to the non-inverting terminal via R1 (giving the non-inverting action) and R1 and R2 have equal values thus giving unity gain (note that the circuit would give a gain of $\times 2$ if R1 were half the value of R2).

ETI

KEEP REGULAR

Don't miss out on your favourite electronics mag. Why search high and low for a copy? Let your newsagent take the strain and reserve you a copy each month.

Fill in your name and address on the form below and hand it to your local newsagent. It will keep you as regular as All-bran. Alternatively, you can eat the coupon. They you'll need the All-bran.



Dear Mr Newsagent
Please order me a copy of ETI
and reserve/deliver me a copy
every month.



Note this magazine is available to your wholesaler through:
SM Distribution, 6 Leigham Court Road, Streatham, London SW16 2PG. Tel: 01-677 8111.

Name _____

Address _____

Advertisement

PCB Manufacturers – Which to choose?

With scores of PCB manufacturers falling over themselves to make your conventional boards, it can be very difficult to choose the right one.

You could however, choose a PCB manufacturer with more to offer. Such as, assembly, panel printing, final build and design.

Slee Electro Products can provide you with these services and will still offer you competitive prices on your PCB's.

"We're hot on quality and delivery too. And being a member of the Printed Circuit Association, means we have to try harder."

*Slee Electro Products, Tel: 0226 200717,
Fax: 0226 731817, Unit 4, Grange Lane
Industrial Estate, Carrwood Road, Barnsley,
South Yorkshire S71 5AS, England.*

BEHIND BARS

The bar code competition of the July 1988 issue caused quite a response. Not only did many readers enter (and most got somewhere near the truth) but it stirred up an inquisitiveness among many as well.

It seems there is a strong desire to know how to read a can of baked beans and so this short article will describe how the EAN13 bar code system works.

A European Article Numbering (EAN) code is now printed on just about every item you are likely to buy in a high street store. These codes uniquely identify an item for use both by the manufacturer and shipper and by the retail store. The codes do not themselves contain price information but merely identify the item for the retailer's point of sale computer which can then look up the price and description of the article.

There are four EAN code systems in use. The EAN8 system contains just eight digits and is used mainly for in-factory tagging, quality control and the like by manufacturers.

The EAN13 system has 13 digits and it is these codes which are to be found on the proverbial baked bean tin.

Of the 13 digits the first two or three classify the code into broad categories. Codes starting with 978 and 979 for instance are books as these prefixes identify the International Standard Book Numbering (ISBN) system.

Most of the prefixes identify the country of origin of the product. Each country operating the EAN system has its own regulating body to assign the rest of the code. In the UK the body is the Article Numbering Authority (ANA) and the UK prefix is 50. The ANA assigns five digits to the manufacturer and five to the item identifier. You will also see a number of codes starting with numbers between 20 and 29 as this signifies an in-store code.

are also even parity with bar one black, bar seven white and either two or four bars black in total. Set C is in fact the reverse of set A.

The choice of the sequence of set A or set B patterns for the digits of the first field determines the derived first digit. Table 2 gives the set patterns for the derived digits 0-9. The second field is relatively straightforward with all six digits taken from pattern set C.

The final digit of the code is the checksum. This is calculated by the following complex formula:

$$C = (10 - ((3 \times (D2 + D4 + D6 + D8 + D10 + D12)) + D1 + D3 + D5 + D7 + D9 + D11) \bmod 10) \bmod 10$$

The Competition

The July competition barcode (as you will all know by now) represented the digits

45 54 49 65 74 69

which are the ASCII codes in hexadecimal for ETIleti. The derived digit was therefore 4 and from Table 2 it can be quickly seen that this requires a pattern set sequence of ABAABB. The checksum is:

| | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---------------|
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | PATTERN SET A |
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | PATTERN SET B |
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | PATTERN SET C |

Table 1 The three pattern sets used in the EAN system

$$\begin{aligned} C &= (10 - ((3 \times (5+4+9+5+4+9)) + 4+5+4+6 \\ &\quad + 7+6) \bmod 10) \bmod 10 \\ &= (10 - ((3 \times 36 + 32) \bmod 10)) \bmod 10 \\ &= (10 - (140 \bmod 10)) \bmod 10 \\ &= (10 - 0) \bmod 10 \\ &= 0 \end{aligned}$$

Table 1 can now be used to determine the bar patterns required for each digit (as shown in Table 3).

So there you have it. It may seem like an awfully complicated method of labelling your groceries (and so it is) but at least now you can wander around the supermarket impressing the shoppers by picking up a can of beans and announcing proudly 'Aha! This is a can of beans!' — Saturdays will never be dull again.

| Set sequence | Derived digit |
|--------------|---------------|
| AAAAAA | 0 |
| AABABB | 1 |
| AABBAB | 2 |
| AABBBA | 3 |
| ABAABB | 4 |
| ABBAAB | 5 |
| ABBBAA | 6 |
| ABABAB | 7 |
| ABABBA | 8 |
| ABBABA | 9 |

Table 2 The set patterns for the derived digit

EAN13

*By popular demand
Malcolm Brown
reveals the truth
behind the pretty
patterns on your
groceries*

Breaking The Code

So how are the numbers actually encoded? Well — extremely complexly! This system is far more complicated than the simple black/white on/off system used in the Bar Code Lock project in the July issue.

The 13 digits are represented by 12 groups of seven equal width bars (either black or white). It is in effect a 7-bit code. From the first six of the 12 digits this produces a 13th digit is decoded. This is usually written below the bars at the start, outside the bar pattern. The last digit of the 13 is always a checksum.

The two 'fields' (the groups of six digits) are separated and surrounded by a 'guard pattern' of two black bars separated by a white bar (the centre guard itself is surrounded by white bars as well). These do not contribute to the code itself but serve to initialise each read and to determine the speed of movement of the reader over the barcode or vice versa.

The first field is made up of code patterns from either of two sets, set A or set B (see Table 1). Set A patterns are odd parity with bar seven black, bar one white and either three or five black bars in total. Set B patterns are even parity with bar seven black, bar one white and either two or four bars black. The second field is made up of codes from set C. These

| | |
|--------|-------|
| 1 | GUARD |
| 010101 | SET A |
| 101010 | SET B |
| 010101 | SET A |
| 101010 | SET B |
| 010101 | SET B |
| 101010 | GUARD |
| 010101 | SET C |
| 101010 | SET C |
| 010101 | SET C |
| 101010 | SET C |
| 010101 | SET C |
| 101010 | SET C |
| 010101 | GUARD |

Table 3 The competition barcode revealed

BACK NUMBERS

- Missed part one of your favourite project?
- Lost that all-important article on circuit design?
- Desperately need that Tech Tip to get your latest masterpiece going?
- Pining for that one issue to complete your valuable collection?

**ETI Backnumbers Department
to the rescue!**

Please note that backnumbers are only held for 12 months. Articles published previous to this must be obtained through our photocopy service.

Please supply the following backnumbers of ETI. Note: Backnumbers are held for 12 months only (complete in block capitals)

Month Year Month Year

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.90 per issue ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:

ETI Backnumbers Department

Infonet Ltd.

5 River Park Estate

Berkhamsted


Herts HP4 1HL



REDIFFUSION TRANSLATOR

No. 847038

£4.99

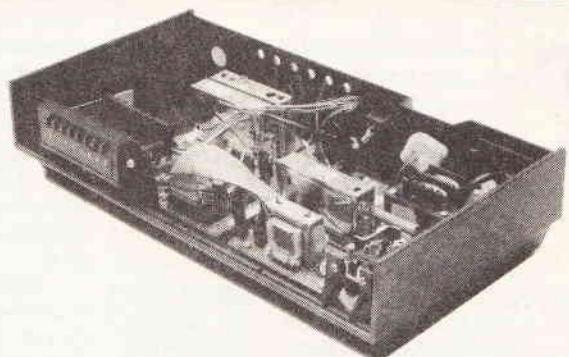


8-way "Preomat" T.V. Tuning of band 1-111 & UHF with AFC, Mains power supply 240V, in cabinet 14 x 7 1/2 x 3 1/2 inches.

The TRANSLATOR may be used directly or modified to convert wired T.V. to normal use with Monitor (IV P-P), T.V. Sound tuner, (HIFI), with any V.C.R. These units are guaranteed in perfect working order and A1 condition

£4.99. P&P £3. Circuit & Modification £1 extra

GRUNDIG INFRA-RED REMOTE CONTROL VIF-K1

£4.99

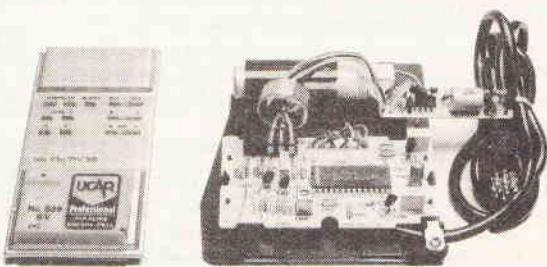

(13 function) consists of transmitter TPV355 & receiver VIF-E1, suitable for use with GRUNDIG VIDEO 2 x 4 Super & Stereo. Brand new & boxed, complete with battery.

£4.99. P&P £2.

VIF-E1 receivers in boxes of 10.

£9.99. P&P £3.50

VIDEO HEAD CLEANERS

VHS or BETA £1.99
with full instructions. P&P £1

V2000 VIDEO TAPES

"MEMOREX". All brand new & boxed.

VCC360 £6.99. VCC480 £7.99. P&P £1

C.B. CONVERTER

40 channel, works in conjunction with standard car radio (A/M). Brand new & boxed.

£2.50. P&P £1

"VIDEOLAB" VIDEO TAPES

Premium quality VHS, which we recommend &

guarantee one for one exchange.

Brand new & boxed.

£1.99. P&P £1

BETA VIDEO RECORDER

"SONY" C5 & C7 "SANYO" etc.
Perfect working order. £39.50

PRICES INCLUDE VAT.

PLEASE NOTE WE ARE INTERESTED IN PURCHASING ALL TYPES OF EQUIPMENT.

STAN WILLETT'S

DEPT. TWS

37 HIGH STREET, WEST BROMWICH,

WEST MIDLANDS B70 6PB

TEL. 021 553 0186

021 559 1437

MAKING SENSE

With increasing automation and computerisation of tasks in all fields of engineering from design, testing and production through to the control of everyday appliances like washing machines and cars, a vast variety of sensors and detectors has come into being. These are the fundamental mechanisms by which computers and controllers observe the outside world and without them no control system could operate.

There are two basic sub-divisions into which all sensors fall — the continuous or static state monitors and the transition or event detectors. The first group (group A) provide an output which indicates the current state of affairs at any given moment and which is able to track with changing input.

The second group (group B) provide no output at all until the monitored state changes. When this happens an output is provided, which indicates that *something* has happened but gives no information about the size or degree of change.

Within each of these two categories there are many alternative sensing techniques and it is in many cases even possible to make the same device operate in either mode. There is also a third category (a rather grey distinction, however) which delivers information about the order of change (group C).

The Great Detectives

We will now look at some real world things we can detect and at a selection of commercially available devices for detecting them. The following is a random list of detectable phenomena:

sound, light, heat, magnetic field, electric current, speed, proximity, motion, acceleration, position, frequency, displacement, pressure. This list is not exhaustive but it shows the variety of stimuli available to the properly designed robot or automation.

Let's look at each in turn, bearing in mind that many overlap in mechanism or purpose. Sound can be detected by means of a microphone within certain frequency limits (say, 20Hz-20kHz). The microphone converts airborne pressure waves into electrical energy by electromagnetic means (moving coil or dynamic microphones and ribbon microphones) or by piezoelectricity (crystal microphones).

The former method delivers a current output and the latter a voltage. The output of either device may be measured continuously via an amplifier (group A) or integrated (averaged) (group C), or it may be used to trigger a comparator set at a critical threshold to provide a group B event detector.

Sound can, however, also be used as a detection medium for other events such as distance and speed and as a communication channel for more complex information transfer. Typical devices are the ultrasonic transducer and detector and the doppler module.

The ultrasonic transducer and detector are a 'loudspeaker' and 'microphone' designed to operate at frequencies above the audible range (30-60kHz), with normally very narrow operational bandwidth. Instead of the 1000:1 frequency range of the conventional microphone and loudspeaker, you can expect a range of say $\pm 10\%$. Working at these frequencies and narrow bandwidth has the advantage of being inaudible, not being affected by normal environmental sounds and being very *directional*. The higher the frequency, the less the sound waves

disperse, which is why 'tweeter' units in hi-fi systems are frequently so complex and expensive (as we don't want high directionality in a hi-fi tweeter).

Distance is measured by emitting a stream of short 'beeps' and measuring the time before the beep is reflected back from the target (the echo time). This is how ASDIC and SONAR work. The directionality of ultrasound is useful here, as it allows comparatively accurate target selection. For this purpose, the frequency of emission is relatively unimportant but the beep length must be short and the echo delay timer has to be very stable. A block diagram is given in Fig. 1.

Speed along the transmission axis can be measured by doppler shift using the same kind of transmitter with a more sophisticated detector which has a wider detection bandwidth. A continuous signal at a very stable frequency is emitted towards the target and the frequency of the reflected signal is measured. If the target is moving towards the sensor, the

CHIP IN

Mike Barwise turns his attention to the enormous range of sensors available

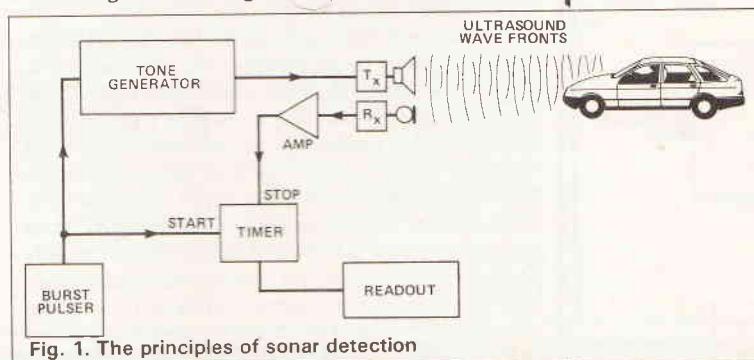


Fig. 1. The principles of sonar detection

wavelength of the return signal is compressed, raising the frequency. If it is moving away, the wavelength is stretched, resulting in a lower frequency. Relative speed between the sensor and target can be very accurately determined in this way (Fig. 2).

As a communication channel, ultrasound has several advantages. It passes through dense, opaque and electrically shielding media (water, concrete, plastics and so on), it is easily detected and coding is simple. Its disadvantages are short link distance and low data rate. The two most common communication techniques are pulsed carrier (the transmitter emits a series of discrete beeps) and frequency modulation or FM (the transmission is continuous but the frequency varies with time). Amplitude modulation is not a recommended method as it is prone to fading (just like AM radio).

Light is another very familiar sensing medium. Some months ago I introduced the optical interrupter

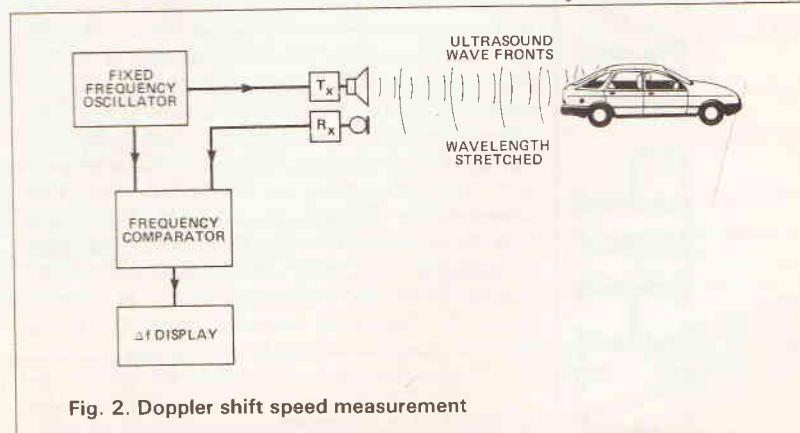


Fig. 2. Doppler shift speed measurement

CHIP IN

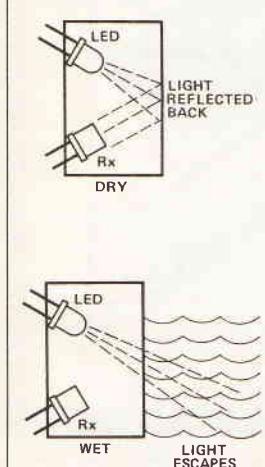


Fig. 3. A refractive fluid level sensor

and we have recently been discussing the esoterics of fibre optic sensors. However, in the real industrial context, there is a plethora of alternatives. The mechanism of the reflectance interrupter can be modified by the inclusion of a lens system to allow operation over distances or 300mm or more, while the transmittance interrupter can be split into two separate boxes and used over distances of several metres in burglar alarms and so on.

However, there are many more subtle and sophisticated optical sensors. A direct spin off from the ordinary interrupter is the optical fluid level sensor. In place of the free path between the emitter and detector there is a piece of glass or plastic which has a refractive index such that the light from the emitter falls on the detector via the reflected path while it is dry. If some other medium (a fluid) covers this material, the resultant change in its refractive properties causes the light to escape without falling on the detector (Fig. 3).

Of course, photocell light meters are well known and used for many light monitoring tasks from photography to health and safety, and in level detectors such as burglar alarms but there are some tricks up our sleeve still to come.

There has been a recent fashion for domestic exterior lighting which switches on when someone approaches, rather than just when it gets dark. These lighting units use a device known as a pyroelectric detector. This consists of an element made of a complex metallic doped ceramic which exhibits a change in conductivity when exposed to changing infra-red flux. Under constant conditions, no output is obtained so this is a group B sensor. It is remarkably sensitive and can detect the change in flux due to body heat as a person moves across its field of view. These devices need quite a lot of care in handling, as they are subject to damage by over-intense illumination and are prone to some unwanted effects such as piezo-electric action (they are vibration sensitive). However they are very useful for the detection of thermally emissive bodies. A typical detection circuit is given in Fig. 4.

One of the more sophisticated applications of the pyroelectric sensor is the sorting of objects of differing temperatures. For this, a 'chopper' is required. Although the sensor only detects changes in intensity, the magnitude of the output change is proportional to the intensity change. A rotating vane set (a 'windmill') between the sensor and the objects to be monitored rotates at a constant speed (Fig. 5) and the sensor monitors the objects and the vane set alternately. A continuous sequence of comparisons is made between the vane temperature and the object temperature. The vanes must of course be maintained at a constant temperature.

The detection of heat is a field where some rapid progress has been made in recent years. The earliest and most common heat sensors with electrical output are thermocouples. These are twisted or welded junctions of dissimilar metals which generate a voltage proportional to the temperature of the junction. They come in various types with differing characteristics and all have the advantages of general robustness, small size and the ability to withstand very high temperatures. However, they are not very linear in their response and their signals require considerable amplification for normal uses. Most common applications are furnace temperature control and the like where the fairly long response times (>0.1 s) and $\pm 0.5^\circ\text{C}$ precision are not limiting factors.

Next to thermocouples, thermistors are the next oldest group A or continuous temperature sensors. These are in effect resistors with a large linear or non-

linear temperature dependency. They are positive or negative working — the resistance increases or decreases with temperature — and can be obtained with a sharp transition temperature between cold and hot resistance, as well as a linear characteristic.

Thermistors have severe limitations on accuracy and tolerance but they serve well in applications such as inrush limiting in high current circuits (high wattage negative linear characteristic), over-temperature protection (low to medium wattage positive rapid transition characteristic) and the like. They can also be made very small and can substitute for thermocouples in many applications.

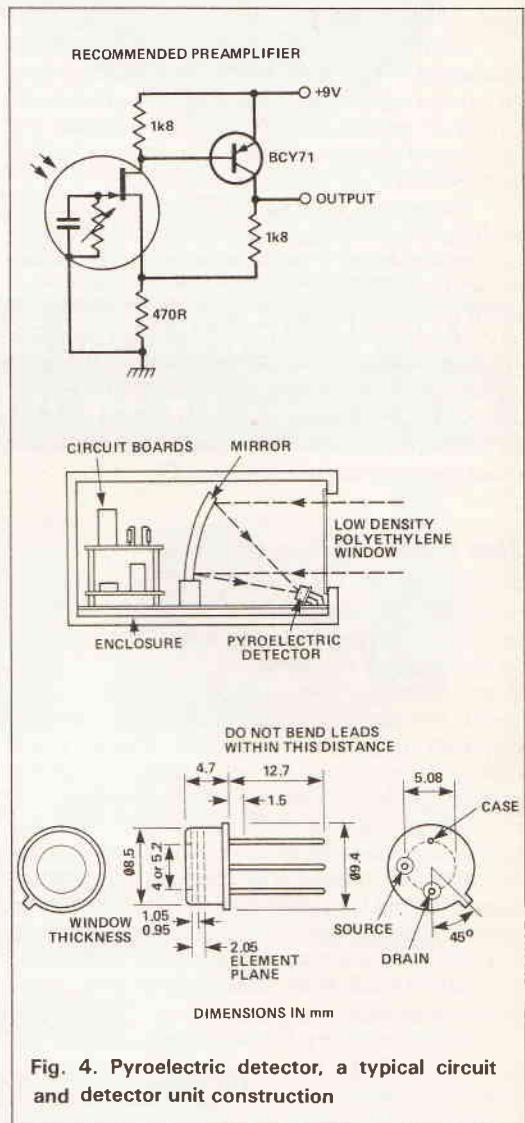


Fig. 4. Pyroelectric detector, a typical circuit and detector unit construction

It is well known (and frequently complained about) that semiconductor reference diodes are temperature dependent. Typically, a two-terminal current reference will have an output current which drifts linearly with temperature. I suppose this characteristic struck some clever person as interesting and they came up with the temperature sensor. The current drift with temperature has been increased and rendered more linear, until we get a device (such as the RS590) which delivers an output current proportional to absolute temperature over the range -55 to $+150^\circ\text{C}$. Thus 0°C is represented by $298.2\mu\text{A}$, as the device is referenced to Absolute temp. Feeding this current through a transimpedance amplifier or measuring the voltage drop across a fixed resistor carrying this current gives us a voltage proportional to temperature.

The capacitive proximity detector works on a similar principle, except that the other component of the tuned circuit is influenced by the detected object, and working distances are generally smaller.

Motion and acceleration are two of the most tricky things to detect and measure. There are so many kinds of motion! Demands range from shaft rotation speed to linear velocity, to displacement versus force, to tracking the erratic path of a randomly moving object. A whole issue of ETI would not be large enough to cover the subject in depth, so next month we will pick a few simple systems.

In the meantime, examples of all the sensors discussed here should be available from decent component stockists.

Even more clever is National's LM35 which is a direct temperature to voltage sensor. This has a power pin, a ground pin and an output pin, the two versions have working ranges of 0 to 100°C and -40 to +110°C respectively. These devices are quite simply foolproof and in addition have no offset.

The final sort of temperature sensor to be mentioned is the assortment of mechanical devices — thermostats and thermal switches. These depend mainly on bimetallic elements, wax filled bellows, gas expansion and so on. They are widely used as emergency limiting devices but they are really too slow and too inaccurate to be considered in the same context as the other sensors mentioned here.

Magnetic field and current sensors have long been based on conventional electromagnetic effects — a current carrying conductor is surrounded by a magnetic field proportional to the current flowing. The commonest technique has been to cause the magnetic field to influence an inductive component in the detection circuit, altering the resonant frequency of

a tuned circuit or directly inducing a current which can be measured.

However, some time ago a gentleman called Hall discovered the Hall effect whereby the behaviour of certain semiconductor devices is influenced by magnetic fields. Small devices (the size of TO220 transistors, for example) are now available, which are influenced by quite small magnetic fields, such as can be induced by a bar magnet about 4mm by 12mm. The Hall effect sensor delivers an output voltage proportional to the magnetic flux or field strength and although the sensitivity of individual devices varies quite a lot, the response is pretty linear and the devices are very robust. One possible use could be for key pressure sensing in keyboards. There are also Hall effect sensors which have inbuilt logic circuits to provide on/off switching.

Having already looked at speed sensing in terms of doppler shift techniques (sound), let us move on to proximity detection.

Industrial proximity detectors are generally based on inductive, capacitive and optical techniques. We have discussed the optical devices, so let's look at the others. The inductive proximity detector works very like the metal detector used by treasure hunters. An LC tuned circuit changes its frequency of oscillation when a conductive material is brought close to its inductive component. These sensors are normally used to detect presence or absence of objects, rather than their distance or position and they have working ranges of 1-20mm depending on the design and the material being sensed. They are generally packaged in boring cylindrical housings and frequently come with dedicated control circuitry.



CHIP IN

**HART
ELECTRONICS**

HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

| | |
|---------------------------------|------------|
| Complete Stereo Record/Play Kit | £33.70 |
| VU Meters to suit | £2.30 each |
| Reprints of original Articles | 75p no VAT |


560X Stereo Mic Amplifier £8.70

LINSLEY HOOD 300 SERIES AMPLIFIER KITS
Superb integrated amplifier kits derived from John Linsley-Hood's articles in Hi-Fi News.

Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35 35 Watt Discount price for Complete Kit £98.79
K300-45 45 Watt Discount price for Complete Kit £102.36
FLH485 Reprints of Original Articles from 'Hi-Fi News' £1.05 no VAT

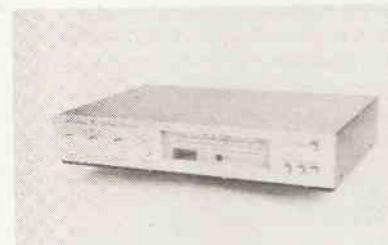LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchrodyne AM receiver described in "Wireless World". The complete unit is cased to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotics but thanks to HART engineering, remains easy to build. The Synchrodyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels as necessary in these days of split programming. If you want the very best in real HiFi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of its sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life.

K900W Stereo Kit with Wound Coils and Twin Meter Drive £65.67
RJS1 Reprints of Original Articles £1.30 no VAT

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £7.65

HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £14.86

HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £14.60

HX100 Stereo Permalloy R/P head. Special Offer £2.49

MA481 2/2 Language Lab R/P head. £13.35

SM168 2/2 Erase Head. Standard mounting AC type £8.85

SM150 2/2 Erase Head, DC Type. £8.85

HQ515E 2/4 Erase Head for Portastudio etc. £46.80

Full specifications of these and other special purpose heads in our lists.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.65 plus VAT and 50p postage!

Tape Head De-magnetiser. Handy size mains operated unit' prevents build up of residual head magnetisation causing noise on playback £4.54

Curved Pole Type for inaccessible heads. £4.85

Send for your free copy of our LISTS Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add post cost of post, packing and insurance as follows:

INLAND
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS
Please send sufficient to cover Surface or Air Post as required.



Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE
(0691) 652894

ALL PRICES EXCLUDE VAT
UNLESS STATED

HART
ELECTRONIC KITS LTD
4 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

Paul Chappell continues to look at op-amps used as differential amplifiers

Carrying on from last month's investigation of a simple differential amplifier, we now have the turbo-charged versions. The first pretender to the title of Ultimate Differential Amplifier is shown in Fig. 1.

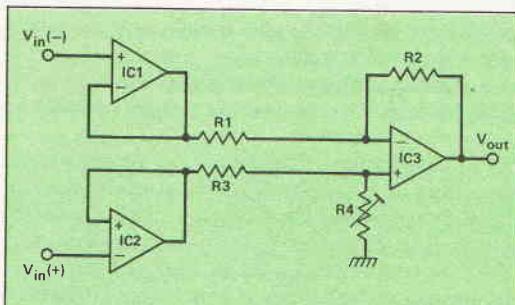


Fig. 1 Last month's circuit with added front ends

This circuit arises from a bull-at-a-gate approach to the problems I mentioned last month. If you remember, the main shortcomings of IC3 and its associated resistors as a differential amplifier were its sensitivity to the output impedances of the drive circuit and the critical dependence for good common mode rejection (CMR) on the matching of R_1/R_2 to R_3/R_4 . Attacking these defects directly, what do you do? Buffer the inputs and trim the resistor match, of course!

It's easy to be unkind about this circuit, but you have to remember that it arose in the early days of op-amp ICs when designers were still much more in tune with discrete component circuits than with plastic packaged amplifiers. If your discrete instrumentation amplifier is affected by source impedances, what more natural than to use a FET or Darlington to buffer the inputs? Figure 1 is the result of applying the same instincts to an op-amp circuit. But if you have three whole op-amps at your disposal, there's a darn sight more effective way to use them than this!

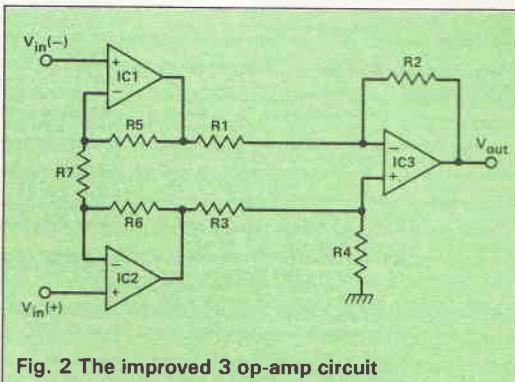


Fig. 2 The improved 3 op-amp circuit

Figure 2 shows the most common high performance configuration. The only difference between this and Fig. 1 is the addition of three resistors, but what a difference they make!

The first thing to notice about the circuit is that because IC1 and IC2 act to maintain their respective input terminals at the same voltage, the voltage at the top of R7 will be $v_{in(-)}$ and at the bottom will be $v_{in(+)}$. The second thing to spot is that any current which flows through R7 must also flow through R5 and R6.

Suppose the circuit is driven by a pure common mode input — that is to say, the inputs $v_{in(-)}$ and $v_{in(+)}$ change in voltage by exactly the same amount. The voltage across R7 will remain constant and so will the current through it. If the current is unchanged, so will be the voltage across R5 and R6. The result is the input voltages, the -input terminals of IC1 and IC2 and the outputs of IC1 and IC2 all move up and down in unison. The signal is passed to the outputs of ICs 1 and 2 without alteration.

Now picture the situation where the two inputs are varying differentially. Since the input voltage appears across R7, by Ohm's law you can easily calculate that any difference in voltage is magnified by $1 + (R_5 + R_6)/R_7$ by the time it appears at the outputs of ICs 1 and 2. The values of R5, 6 and 7 are often chosen to give front end gains of 1000 or more in instrumentation amplifier circuits.

The situation we have, then, is that IC3 and its associated resistors form a differential amplifier which is no better than the one described last month. To be

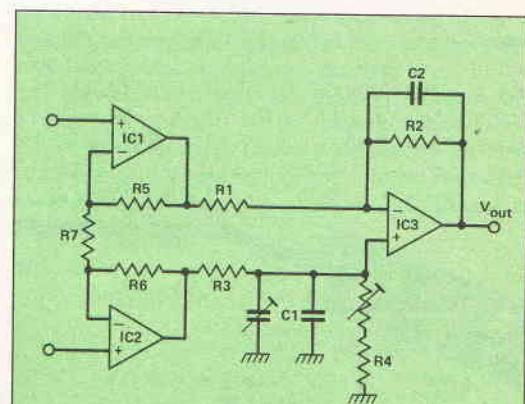


Fig. 3 Additional trimming capacitors for frequency compensation

more accurate — it's exactly the same! The difference is that, with the front-end turbo charger in place, the differential component of the signal is already 1000 times bigger in comparison to the common mode component by the time it hits R1 and R3. This means that, in theory at least (and not so far off in practice), you can add 60dB to the CMR figure that would be achieved by IC3 alone!

If you think I'm about to tell you that the values of R5, 6 and 7 have to be chosen to some absurdly tight tolerance, you're wrong! For reasons which won't be apparent from this simple analysis of the circuit, it's a good idea to make R5 and R6 the same value but matching them to 1% is more than enough. In pre-packaged instrumentation amps (ICs or hybrid cir-

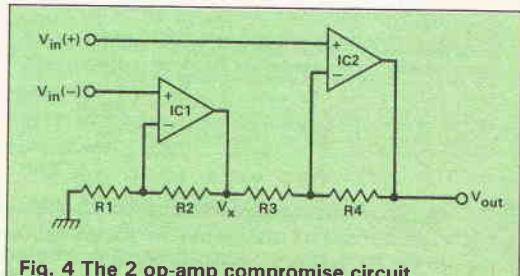


Fig. 4 The 2 op-amp compromise circuit

CIRCUIT THEORY

cuits) R7 is usually an external resistor chosen to set the gain of the circuit and (within reason!) can be any value you like.

The requirement that R1 and R3 should be driven from low resistance sources is settled by the very low output resistances of ICs 1 and 2. In op-amp and resistor versions of the circuit, final tweaking of CMR is usually made by trimming the value of R4.

The circuit still has the requirement that the output resistances of the circuit generating $v_{in(+)}$ and $v_{in(-)}$ should be very low in comparison with the input resistances of the differential amplifier. The input resistances we are dealing with this time though are those of IC1 and 2 which will be several orders of magnitude higher than those resulting from the resistors in last month's circuit. One thing you have to watch is not to spoil this advantage with the bias resistors to the + input terminals of IC1 and 2. In Fig. 2 I haven't shown any bias resistors at all. The ideal situation is that the input op-amps should draw their bias current from the driving circuit. If this is not possible, you've got a bit of juggling to do to make sure that the resistors are large enough to have negligible effect on the CMR but not so big as to cause excessive offset voltage at the output of IC3.

One thing to be aware of with this circuit is that if you aim for huge CMR figures, the calculated values will only be achieved at low frequencies. When I say low, I mean *low!* Try for 110dB, for example, and you will probably find the CMR beginning to fall at frequencies in the 10s of Hz. The main reason is unequal phase shifts of IC1 and 2. This can be compensated for, to some extent by including a pair of capacitors to trim the CMR at higher frequencies (Fig. 3). If you use the circuit for (say) audio rather than instrumentation purposes, the general scheme is to settle for a lower differential gain (otherwise you'll have frequency response problems), to aim for a lower CMR (otherwise you'll be disappointed!) and to trim the low and high frequency CMR individually.

The next circuit (Fig. 4) aims to achieve similar results to Fig. 2 but with only two op-amps. It's not often seen but is an excellent compromise between the cheap 'n' cheerful single op-amp circuit and the full blown instrumentation amplifier.

If last month's circuit was a pair of scissors, this one is a nutcracker! Figure 5a shows the situation where the two inputs are at the same voltage, and it's fairly clear that the condition for the output to remain at 0V under these conditions (and therefore for any common mode component of the input to cancel) is: $R2/R1 = R3/R4$.

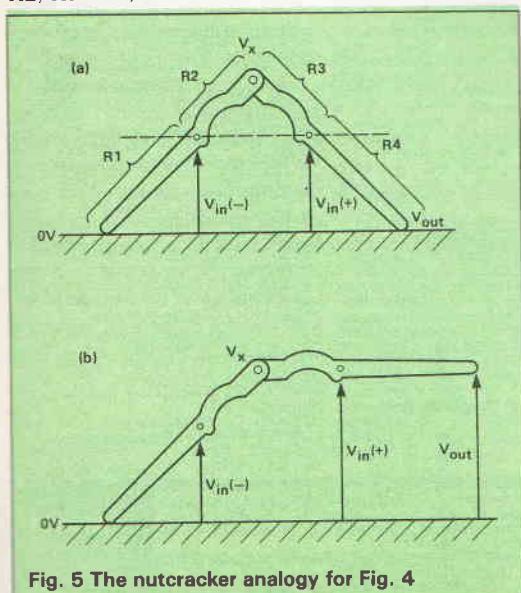


Fig. 5 The nutcracker analogy for Fig. 4

Figure 5b shows how an output is generated when the inputs are at different voltages. As with last month's scissors, you can push the analogy as far as you like if you find it helpful.

The circuit has Fig. 2's advantage of high input resistance but also two of the serious flaws associated with the single op-amp circuit: there's no way to trim the gain and CMR independently and the CMR is critically dependent on the matching of two resistor ratios.

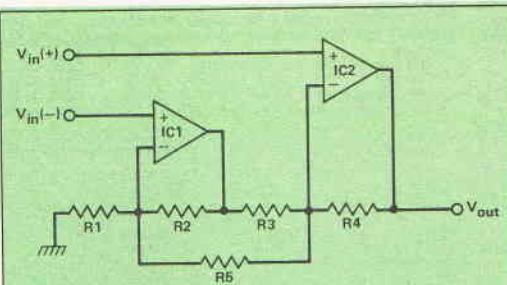


Fig. 6 The improved 2 op-amp circuit

Both of these defects can be overcome by the addition of a single extra resistor, as shown in Fig. 6. The action of R5 is very similar to that of R7 in Fig. 2. The differential input voltage appears across it by the action of IC1 and IC2 maintaining their + and - inputs at the same voltage and it allows you to 'steal' extra differential gain from the circuit without affecting the CMR trim.

That completes our tour of differential amplifiers but before I go I'd like to show you one more circuit. It's not a differential amp but it's another circuit which relies on the matching of two resistor ratios for its performance, which you're probably becoming rather wary of by now! You may also be able to spot some similarities between this circuit (Fig. 7) and last month's subtractor.

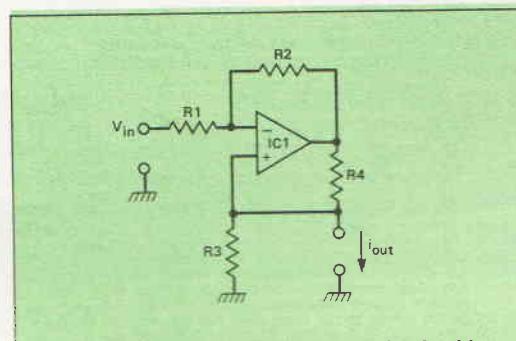


Fig. 7 Not a differential amplifier but a circuit with many faults in common

The idea is that if $R1/R2 = R3/R4$, the output current will be directly proportional to the value of V_{in} and will have a value independent of the resistance of the load. In other words, the circuit is a voltage to current converter.

My reasons for showing it to you are threefold. It's another example of a circuit which works well on paper but not so well in practice (in fact, this one is so bad that I've only once seen it used!). The reason for its shortcomings are the same as those for the differential amps, it's another circuit where the problems are caused by the configuration rather than the quality of the op-amp. It is also (I think, anyway) fairly inscrutable so you might like to exercise your brain cells by trying to come up with an intuitive explanation of why it works! Working out the 'formula' is easy enough but how would you convince someone with no algebra whatsoever that it does (in theory, anyway) do what it's supposed to? You have ten minutes, starting . . . NOW.

RACKS
CABINETS & FANS

SURPLUS BOUGHT & SOLD

ELECTRONIC COMPONENTS & OBSOLETE IC'S

MONITORS VDU'S & PLOTTERS

1000'S OF ITEMS IN STOCK

COMPUTER SYSTEMS & PERIPHERALS

RELAYS MOTORS & STEPPERS

POWER SUPPLIES & INVERTORS

ALL TYPES OF TEST EQUIPMENT

PRINTERS DISK DRIVES & KEYBOARDS

VIDEO EQUIPMENT & CAMERAS

THE 'ALADDINS' CAVE OF ELECTRONIC & COMPUTER EQUIPMENT

COLOUR MONITORS

16" Decca, 80 series budget range, colour monitors. Features include: PIL tube, attractive teak style case, guaranteed 80 column resolution, only seen on monitors costing 3 times our price, ready to connect to a host of computer or video outputs. Manufacturers fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. 1000's sold to date.

DECCA 80 RGB + TTL + SYNC input for BBC type interface etc.

DECCA 80 COMP 75 1/2 composite video input with integral audio amp & speaker ideal for use with video recorder or TELEBOX ST or any other audio visual use.

Only £99.00 (E)

HIGH DEFINITION COLOUR

BRAND NEW CENTRONIC 14" monitors in attractive style moulded case featuring hi res Mitsubishi 0.42 dot pitch tube with 669 x 507 pixels, 28MHz bandwidth. Full 90 day guarantee. Order as 1004-N2 for TTL + sync RGB for BBC etc.

1003-N1 for IBM PC etc fully CGA equiv £159.00 (E)

1005-N2 RGB interface for QL 85 columns £169.00 (E)

20" & 22" AV Specials

Superbly made, UK manufacture, PIL tube, all solid state colour monitors, complete with composite video and sound inputs, attractive teak style case. Ideal for a host of applications including Schools, Shops, Disco's, Clubs etc. Supplied in EXCELLENT little used condition with 90 day guarantee.

20" Monitor £165.00 (F) 22" Monitor £185.00 (F)

MONOCHROME

MOTOROLA M1000-100 5" CRT black & white compact chassis monitor measuring only cm 11.6h, 12w, 22d, ideal for CCTV or computer applications. Accepts standard Composite video or individual H & V syncs. Operates from 12v DC at approx 0.8a. Some units may have minor screen marks, but still in very usable condition. Fully tested with 30 day guarantee & full data.

Only £29.00 (E)

Fully cased as above, with attractive moulded, desk standing swivel and tilt case. Dim cm 12h, 14w, 26d £39.00 (C)

JVC type 751-7 5" ultra compact black & white chassis monitor for 12v 0.7a DC operation. Dim cm 11h, 14w, 18d. Simple DIY circuit data included to convert data and separate sync input to composite video input. Ideal portable equipment etc. Supplied with full data.

Brand New £65.00 (B)

KGM 324 9" Green Screen. Little used fully cased, mains powered high res monitors with standard composite video input. Fully tested and in excellent condition.

£49.00 (E)

20" Black & White monitors by AZTEK, COTRON & NATIONAL. All solid state, fully cased monitors, ideal for all types of AV or CCTV applications. Units have standard composite video inputs with integral audio amp and speaker. Sold in good, used condition, fully tested with 90 day guarantee.

Only £85.00 (F)

FLOPPY DRIVE SCOOP Drives from Only £39.95

A MASSIVE purchase of standard 5.25" disk drives enables us to offer you prime product at all time super low prices. All units unless stated are removed from often BRAND NEW equipment, fully tested and shipped to you with a full 120 day guarantee. All units offered operate from +5 and +12 volts DC, are of standard size and accept the common standard 34 way interface connector.

TANDON TM 100-2A IBM compatible 40 track FH double sided

Only £39.95 (B)

TANDON TM 101-4 FH 80 track double sided

Only £49.95 (B)

JAPANESE Half Height double sided drives by Canon, Tec,

Toshiba etc. Specify 40 or 80 track

Only £75.00 (B)

TEAC FD55-F 40-80 track double sided Half Height

Brand New £115.00 (B)

DISK DRIVE ACCESSORIES

34 Way interface cable and connector single £5.50, Dual £8.50 (A)
5.25" DC power cable £1.75. Fully cased PSU for 2 x 2.5" Drives

£39.95 (B)

£19.50 (A) (C) Chassis PSU for 2 x 8" drives

£39.95 (B)

£175.00 (E)

£260.00 (E)

£175.00 (E)

SUGART 800/801 single sided refurbished

£175.00 (E)

SUGART 851 double sided refurbished

£175.00 (E)

MITSUBISHI M2894-63 Double sided switchable Hard or Soft sector

BRAND NEW £275.00 (E)

SPECIAL OFFER Dual 8" drives with 2mb capacity in smart case with integral PSU

ONLY £499.00 (F)

COMPUTER SYSTEMS

TATUNG PC2000. Big brother of the famous EINSTEIN, the PC2000 professional 3 piece system comprises: Quality high res GREEN 12" monitor, Sculptured 82 key keyboard and plinth unit containing the Z80A CPU and all control electronics. PLUS 2 integral EAC 5.25" 80 track double sided disk drives. Many other features include Dual 8" IBM format disk drive support, Serial and parallel outputs, full expansion port, 64k ram and ready to run software. Supplied complete with CPM, WORDSTAR, BASIC and accounts package.

BRAND NEW

FULL 90 day guarantee.

Original price £1400

Only £299 (E)

QUINOX (IMS) S100 system capable of running either TURBO or standard CPM. Unit features heavy duty box containing a powerful SU, 12 slot S100 backplane, & dual 8" double sided disk drives. Two individual Z80 CPU boards with 192k of RAM allow the use of multi user software with upto 4 RS232 serial interfaces. Many other features include battery backed real time clock, all IC's socketed etc. Units in good condition and tested prior despatch, no documentation at present, hence price of only £245.00 (F)

100 PCB's & IMS A465 64K dynamic RAM. £55.00 (B) IMS A930 FDC controller £85.00 (B), IMS A862 CPU & I/O £65.00 (B)

SAE for full list of other S100 boards and accessories.

Bulk purchase brings you incredible savings on a range of printers to suit all applications. Many other "one off bargains" can be seen at our South London Shop.

HAZELTINE ESPRINT Small desktop 100 cps print speed with both RS232 and CENTRONICS interfaces. Full pin addressable graphics and 6 user selectable type fonts. Up to 9.5" single sheet and tractor paper handling.

Brand New Only £199.00 (E)

CENTRONICS 150 series. A real workhorse for continuous use with tractor feed paper, either in the office, home or factory, desk standing 150 cps 4 type fonts and choice of interfaces. Supplied BRAND NEW Order as:

150-SN up to 9.5" paper handling £185.00 (E)

150-SW up to 14.5" paper handling £225.00 (E)

150-GR up to 14.5" paper plus full graphics £245.00 (E)

When ordering please specify RS232 or CENTRONICS interface.

Ultra Fast 240 cps NEWBURY DATA NDR 8840 High Speed Printers Only £449 !!

A special purchase from a now defunct Government Dept enables us to offer you this amazing British Made quality printer at clearance prices. SAVING YOU OVER £1500 !! The NDR8840 features high speed 240 cps print speed with integral, fully adjustable paper tractor, giving exceptional fast paper handling for multi part forms etc. The unit features 10 selectable type fonts giving up to 226 printable characters on a single line. Many other features include Internal electronic vertical and horizontal tabs, Self test, 9 needle head, Up to 15.5" paper, 15 million character ribbon cartridge life and standard RS232 serial interface. Sold in SUPERB tested condition with 90 day guarantee.

Only £449.00 (F)

EPSON model 512 40 column 3.5" wide paper roll feed, high speed matrix (3 lines per second) printer mechanism for incorporation in point of sale terminals, ticket printers, data loggers etc. Unit features bi directional print head and integral roll paper feed mech with tear bar. Requires DC volts and simple parallel external drive logic. Complete with data, RFE and tested.

Only £49.95 (C)

EPSON model 542 Same spec as above model, but designed to be used as a slip or flatbed printer. Ideal as label, card or ticket printer. Supplied fully cased in attractive, small, desk top metal housing. Complete with data, RFE and tested.

Only £55.00 (D)

FULLY DIABLO, QUME, WORDSTAR compatible. Many features include full width platten - up to 15" paper, host of available daisy wheels, single sheet paper handling, superb quality print. Supplied complete with user manual & 90 day guarantee plus FREE dust cover & daisy

BRAND NEW Only £225.00 (E)

** South London Shop **

Located at 215 Whitehorse Lane, London SE25. The shop is on the main 68 bus route and only a few miles from the main A23 and South Circular roads. Open Monday to Saturday from 9 to 5.30, parking is unlimited and browsers are most welcome. Shop callers also save the cost of carriage.

MODEMS

Modems to suit all applications and budgets. Please contact our technical sales staff if you require more information or assistance.

SPECIAL PURCHASE V22 1200 baud MODEMS ONLY £149 !!

MASTER SYSTEMS type 2/12 microprocessor controlled V22 full duplex 1200 baud. This fully BT approved modem employs all the latest features for error free data comm's at the staggering speed of 120 characters per second, saving you 75% of your BT phone bills and data connect time! If add these facts to our give away price and you have a superb buy!!

Ultra slim unit measures only 45 mm high with many integral features such as Auto answer, FULL LED status indication, RS232 interface, Remote error diagnostics, SYNC or ASYNC use, SPEECH or DATA switching, integral mains PSU, 2 wire connection to BT line etc. Supplied fully tested, EXCELLENT slightly used condition with data and full 120 day guarantee.

BRAND NEW £24.95 (B)

12V 17 Ah Ultra rugged, all weather, virtually indestructible rechargeable NICAD stack by ALCAD. Unit features 10 x individual type XL1.5 cells in wooden case. Supplied to the MOD and made to deliver exceptionally high output currents & withstand long periods of storage in discharged state. Dim cm 51 x 14 x 22. Cost over £250 Supplied unused & tested complete with instructions.

£95.00 (E)

EX EQUIPMENT NICAD cells by GE Removed from equipment and in good, but used condition. "F" size 7Ah 6 for £8 (B) Also "D" size 4Ah 4 for £5 (B)

LIMITED QUANTITY Only £149 (D)

CONCORD V22 1200 baud as new £330.00 (E)

CONCORD V22 1200-2400 BIS £399.00 (E)

RIVON Ex BT Modem 27 V22 1200 £225.00 (E)

DATEL 4800 / RACAL MPS 4800 EX BT

modem for 4800 baud sync use. £295.00 (E)

DATEL 2412 2780/3780 4 wire modem unit. £199.00 (E)

MODEM 20-1 75-1200 BAUD for use with PRESTEL etc EX BT fully tested. £49.00 (E)

TRANSDATA 307A 300 baud acoustic coupler with RS232 I/O. Brand New £49.00 (E)

RS232 DATA CABLES 16 ft long 25D plug to 25 way D socket. Brand New Only £9.95 (A)

As above but 2 metres long £4.99 (A)

BT plug & cable for new type socket £2.95 (A)

RECHARGEABLE BATTERIES

Maintenance free, sealed longlife LEAD ACID

A300 12v 3 Ah £13.95 (A)

A300 6v 3 Ah £9.95 (A)

A300 6-0-6 v 1.8 Ah RFE £5.99 (A)

NICKEL CADMIUM

Quality 12 v 4 Ah cell pack. Originally made for the TECHNICOLOR video company, this unit contains 10 high quality GE Nicad, b type cells, configured in a smart robust moulded case with DC output connector. Dim cm 19.5 x 4.5 x 12.5. Ideal portable equipment etc

BRAND NEW £24.95 (B)

12V 17 Ah Ultra rugged, all weather, virtually indestructible rechargeable NICAD stack by ALCAD. Unit features 10 x individual type XL1.5 cells in wooden case. Supplied to the MOD and made to deliver exceptionally high output currents & withstand long periods of storage in discharged state. Dim cm 51 x 14 x 22. Cost over £250 Supplied unused & tested complete with instructions.

£95.00 (E)

EX EQUIPMENT NICAD cells by GE Removed from equipment and in good, but used condition. "F" size 7Ah 6 for £8 (B) Also "D" size 4Ah 4 for £5 (B)

BRAND NEW 85 Mb Disk Drives ONLY £399

End of line purchase enables this brand new unit to be offered at an all time super low price.

The NEC D2246 80 Mb disk drive features

full CPU control and industry standard SMD

interface. Ultra high speed data transfer and

access times leave the good old ST506 inter-

face standing. Supplied BRAND NEW with

full manual.

Only £399.00 (E)

HP 3270A 8 pen digital A1 drum plotter with IEEE interface.

As New £4750

CHEETAH Telex machine

1.5 kw 115v 60 Hz power source

£950

500 watt INVERTER 24v DC to 240v AC sine

wave 50 Hz output

SOLDER SYSTEMS tin lead roller tinning

machine for PCB manufacture

£350

CALLAN DATA SYSTEMS multi user INTEL

based UNIX system, complete with software

and 40 Mb Winchester disk drive.

£2750

WAYNE KERR RA200 Audio, real time fre-

quency response analyzer

£3000

TEKTRONIX 1411/R PAL TV test signal

standard

£6900

TEKTRONIX R140 NTSC TV test signal

standard

£875

HP 3271A Correlator system

£350

PLESSEY portable Microwave speech / data

link 12v DC, 70 mile range. The pair £275.00

19" Rack cabinets 100's in stock from £15.00

POWER SUPPLIES

All power supplies operate from 220-240 v AC Many other types from 3v to 10kv in stock. Contact sales office for more details.

PLESSEY PL12/2 Fully enclosed 12v DC 2 amp PSU. Regulated and protected. Dim cm 13.5 x 11 x 11

New £16.95 (B)

AC-DC Linear PSU outputs of +5v 5.5a, -5v 0.6a, +24v 5a. Fully regu-

New £49.50 (C)

POWER ONE PHC 24v DC 2 amps Linear PSU fully regulated

New £19.95 (B)

BOSHERT 13088 switch mode supply ideal disk drives or complete

system. +5v 6a, +12 2.5a, -12 0.5a, -5v 0.5a. Dim cm 5.6 x 21 x 10.8

New £29.95 (B)

BOSHERT 13090 same as above spec but outputs of +5v 6a, +24v

New £39.95 (B)

GREENDALE 19ABOE 60 Watt switch mode outputs +5v 6a, +12v

1a, -12v 1a, +15v 1a, D, 12v 10 x 20 x 5.5

RFE Tested £24.95 (B)

CONVER AC130-3001 High grade VDE spec compact 130 watt

switch mode PSU. Outputs +5v 15a, -5v 1a, +8-12v 6a. Dim 6.5 x 27 x 12.5 Current list price £190.

Our price New £59.95 (C)

FARNELL G6/40A Compact 5v 40 amp switch mode fully enclosed

New £14.00 (C)

FARNELL G24 5S Compact 24v 5 amp switch mode fully enclosed

New £95.00 (C)

Special Offer EXPERIMENTORS PSU

ONLY

£16.95 (C)

Made to the highest spec for BT this unit gives several fully protected DC outputs most suited to the Electronics Hobbyist.

+5v 2a, +8-12v 1a, +24v 1a and +5v fully floating at 50ma.

Ideal for school labs etc. Quantity discount available.

Fully tested with data RFE = Removed From Equipment

TV SOUND & VIDEO TUNER ONLY £29.95

TELEBOX ST for monitors with composite video input £29.95

TELEBOX STL as ST, but fitted with integral speaker £34.95

TELEBOX RGB for use with analogue RGB monitors £59.95

Colour when used with colour CRT, RGB version NOT suitable for IBM-CLONE type colour monitors. DATA sheet on request. PAL overseas versions CALL

Keep your hot parts COOL and RUST FREE with our range of BRAND NEW cooling fans.

AC FANS Specify 240 or 110 v

3" Fan dim 80 x 80 x 38 £8.50 (B)


3.5" ETRI slimline 92 x 92 x 25 £9.95 (B)

4" Fan dim 120 x 120 x 38 £12.50 (B)

4" 24v DC 12v 120 x 120 x 25 £14.50 (B)

BUHLER 12v DC 62 mm £12

DIGITAL TRANSISTOR TESTER

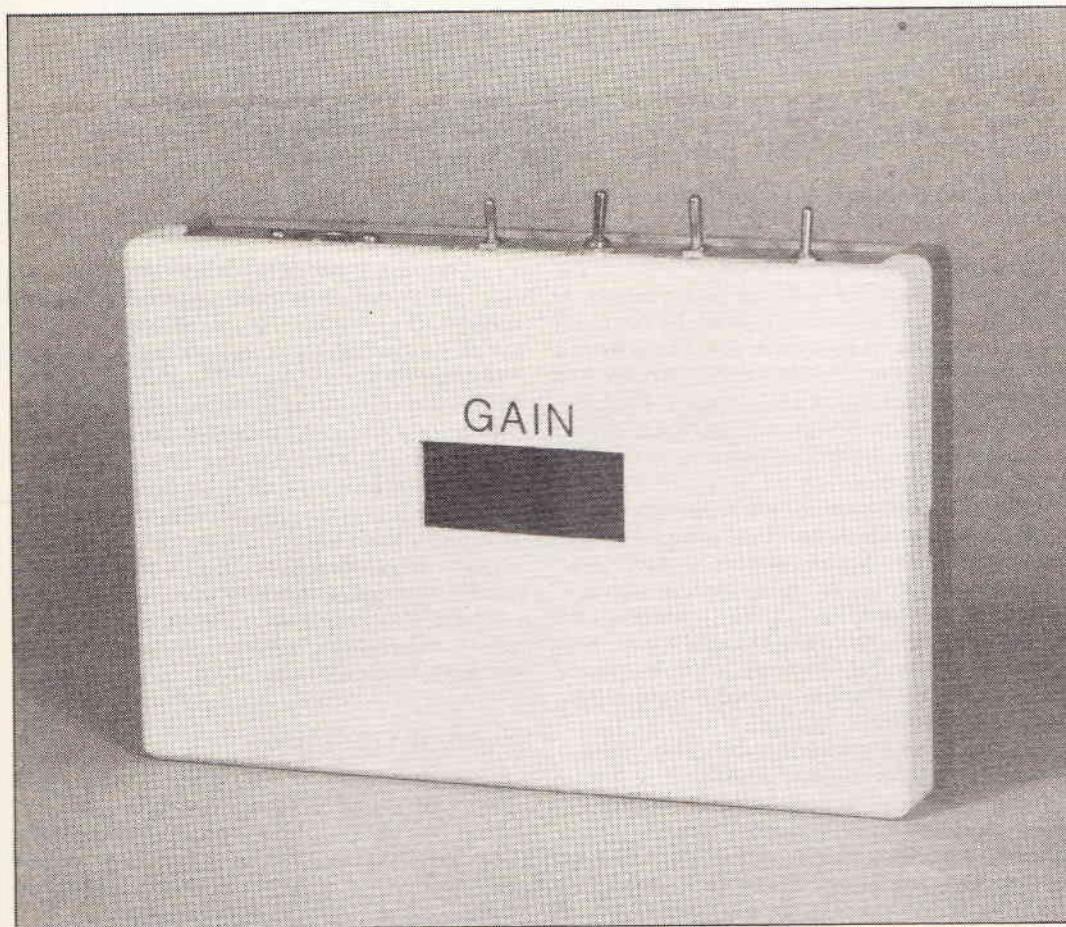

Robert Penfold scorns the analogue and lets his digits do the testing

This transistor tester was developed to fulfil the need for a unit that would provide a quick and convenient means of testing DC current gain (h_{fe}) and leakage. Some other testers are inexpensive to build but provide only basic go/no-go checking or are relatively slow and difficult to use.

There are also some simple but effective circuits based on moving coil meters but the relatively high cost of meters these days makes these designs less

attractive than they once were. On the other hand, an equivalent circuit using a digital readout is substantially more complex but not necessarily much more expensive. A 2-digit display gives better accuracy than most of the moving coil meters currently on sale and certainly more than adequate accuracy for this application.

This design has proved to be quick and easy to use in practice. It can test both NPN and PNP devices and has two gain ranges 0.99 and 0.990. This enables reasonably accurate checks to be made on anything from low gain RF and switching devices through to very high gain audio devices.

An over-range indicator is included on the 2-digit LED display and simple leakage tests can also be made using the unit. Power is obtained from an internal 9V battery.

Testing Theory

Most simple transistor testers operate using the basic test set-up of Fig. 1a. Battery B1 supplies power to the test device with the correct polarity and meter M1


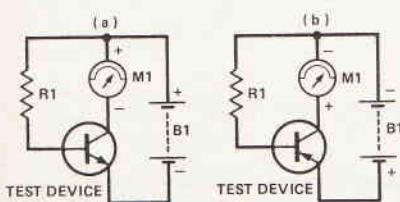


Fig. 1 Basic test circuits for NPN and PNP transistors

PROJECT

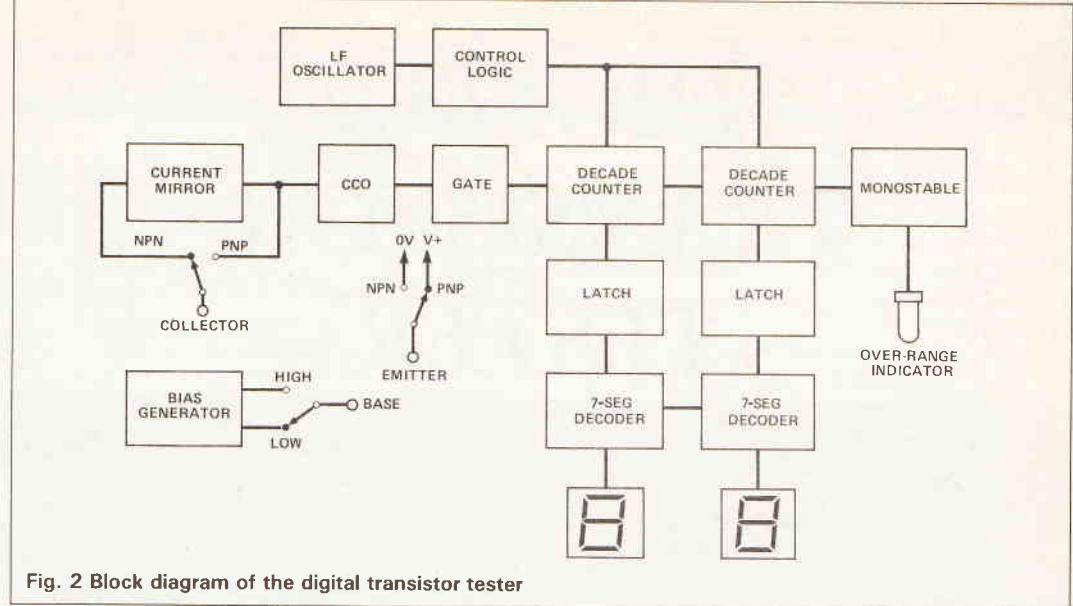

registers the flow of current in the collector circuit. The current flow from the collector to the emitter is normally very low and would typically be about one microamp or less for a silicon device. This is termed the 'leakage' current. Providing a small forward bias current to the base terminal results in a much larger flow of current in the collector circuit. The current gain of the transistor is equal to the collector current divided by the base current.

In this case R1 provides a small reference current to the base of the test device. The higher the gain of the device, the greater the collector current that will be registered on M1. In fact the circuit can be arranged so that M1 provides a readout direct in current gain. For instance with the value of R1 chosen to give a base current of $1\mu\text{A}$ and M1 having a full scale value of 1mA ($1000\mu\text{A}$) M1 would accommodate a current gain range of 0-1000.

This assumes the leakage current is very low and is not inflating the collector current flow but as explained previously, with silicon devices the leakage current is almost invariably insignificant.


Fig. 1a shows the test setup for NPN transistors but the arrangement for PNP testing is essentially the same and is shown in Fig. 1b. It is just a matter of reversing the polarity of the battery and the meter.

This type of testing has a slight flaw in that it is not checking the gain at specific collector currents and voltages. These both vary according to the gain of the test component (high gain giving increased collector current and reduced voltage). The uncertain collector voltage is not of great importance as quite large variations in this factor have a minimal effect on the gain of test components. Variations in collector current have a greater (although still fairly small) influence on current gain. Results are perfectly acceptable in practice provided test components are not tested at very low collector currents. The use of two or more measuring ranges ensures that low gain devices can be checked at an acceptable current and also that they will give a high enough reading to provide reasonable good accuracy.

System Operation

The block diagram of Fig. 2 shows the general arrangement used in this transistor tester. The unit breaks down into two distinct sections, one providing the display and the other converting current gain into a suitable driver signal for the display circuit. The bulk of the circuit is used to provide the display.

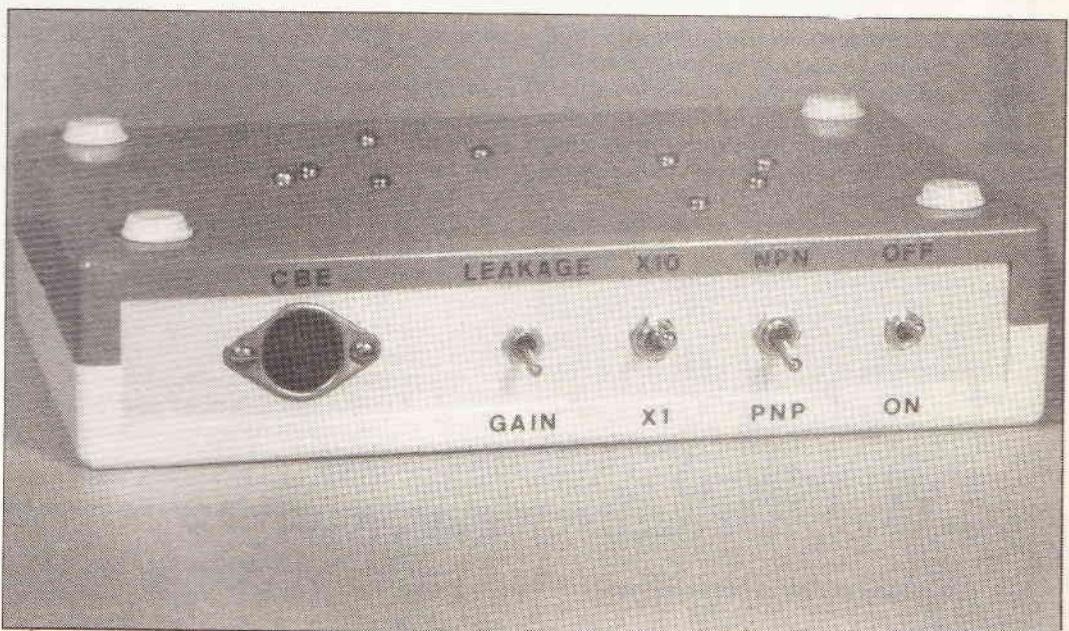The display section is a simple frequency counter



PROJECT

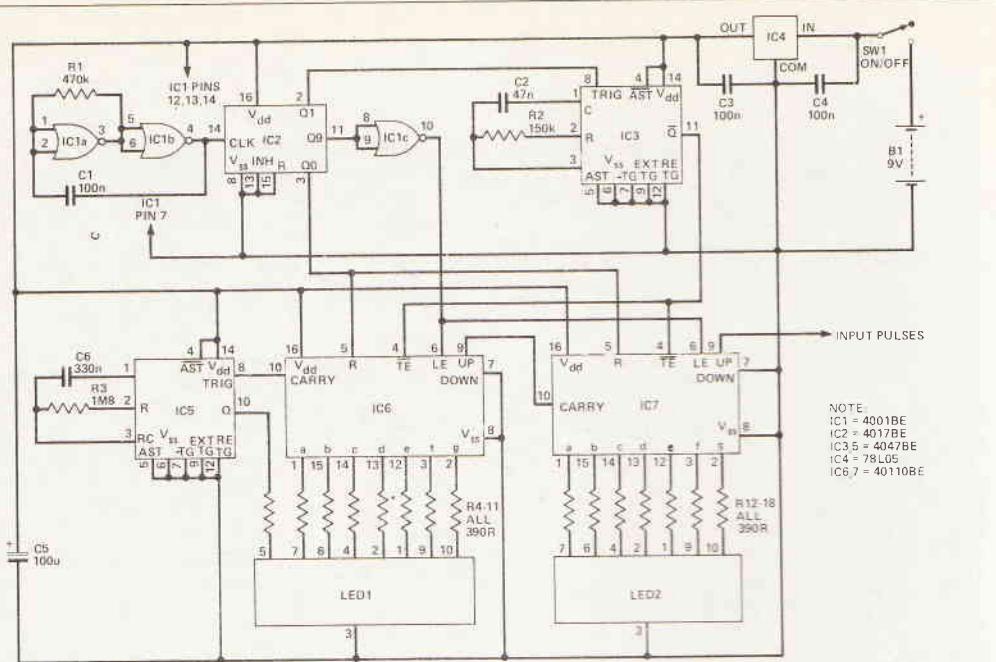


Fig. 3 The circuit diagram of the display section

HOW IT WORKS

The display section (Fig. 3) is built around two CMOS 40110BE integrated circuits which each contain a decade counter, latch and 7-segment decoder/driver. They also have 'toggle enable' inputs that effectively give a built-in gate that avoids the need for an external gate. The 40110BE is actually an up/down counter but in this application it is only used as a straightforward up counter.

Unlike most CMOS devices, these have a high output current capability and they directly drive the common cathode LED displays via current limiting resistors. The carry output of IC6 is used to drive a positive edge triggered monostable based on IC5 and a trigger signal is only provided to IC5 if an overflow occurs. IC5 then activates the overflow indicator LED for just over one second, giving clear warning that the main display reading is erroneous. The overflow indicator is the otherwise unused decimal point segment of the most significant display digit.

The low frequency oscillator uses two gates of IC1 wired as inverters and connected in the standard basic CMOS astable configuration. The oscillator operates at approximately 20Hz but due to a divide by ten action in the control logic circuit this equates to only about two readings per second.

The control logic circuit is built around IC2, which is a CMOS 4017BE one-of-ten decoder. Output 0 (pin 3) going high resets the counters to zero and output 1 (pin 2) going high generates the gate pulse. It does so by triggering monostable multivibrator IC3. This generates a negative gate pulse of about 17ms at its Q output which is used to drive the gate inputs of IC6 and IC7.

With this type of display circuit both gate inputs must be driven and not just the one belonging to the least significant digit. Output 9 drives the latch inputs of the counter chips and latches the new reading prior to a new cycle commencing and the counters being reset. IC1c is used to invert this signal so as to give the negative latching pulse required by IC6 and IC7. Note that outputs 2 to 8 of IC2 as well as its carry output are left unused. Also, one gate of IC1 is left unused but its inputs are tied to the positive supply rail in order to prevent spurious operation.

Power is obtained from a 9V battery but a small 5V regulator provides a well regulated 5V supply for the entire circuit. This ensures the unit provides consistent results as the battery voltage drops.

In the input circuit (Fig. 4) R19 and R20 form a centre-tap on the supply lines and this drives the base terminal of the test device via one of two switched current limiting resistors (R21-R22). These provide the unit with its two measuring ranges and SW2 is used to select the desired base feed resistor. By driving these resistors from the mid-supply voltage there is no need to bother with any NPN/PNP

switching in the base circuit. SW3 can be used to cut off the base current so that leakage checks can be made.

Q1 and Q2 form a conventional current mirror circuit, with R23 and R24 providing current limiting in the event of any accidental short circuits or closed circuit devices being checked.

There is no need to switch out the current mirror in the PNP mode and NPN/PNP switching can therefore be achieved using just a DPDT switch (SW4).

In theory, Q1 and Q2 should be a matched pair to obtain an accurate 1:1 ratio of input to output current. In practice, quite wide differences in their gain did not produce any great discrepancies between the NPN and PNP modes. One way of ensuring really accurate results is to use any two BC559s for Q1 and Q2 initially and to then use the unit to select two reasonably well matched transistors from a batch of (say) half a dozen devices. However, this is by no means essential and unmatched devices should suffice. It is advisable to use transistors from the same gain group (say, two BC559Bs).

The CCO is just a 555 astable circuit. No resistor is used between pins 6 and 7 in order to keep C7's discharge time as short as possible. This makes the period of each cycle almost totally dependent on the charge current and ensures good linearity. A TLC555CP is specified for the IC8 position as this gives a much lower current consumption than the standard 555 and it also seems to be somewhat faster in operation (which again aids good linearity). The collector current at which the devices are tested is dependent on their current gain but is typically around one or two millamps.

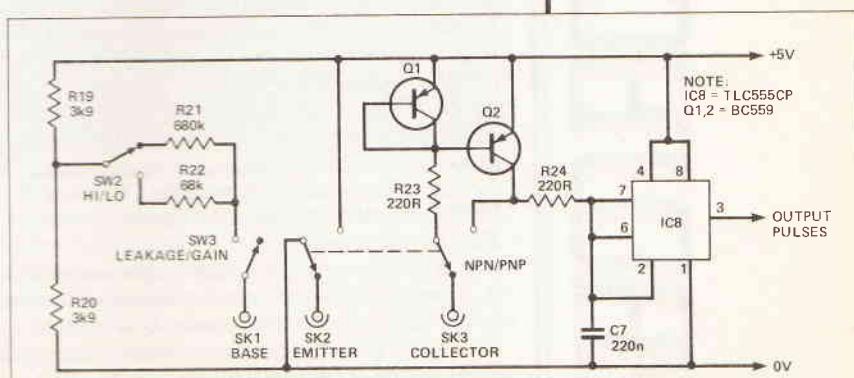


Fig. 4 The circuit diagram of the input section

PROJECT

32

circuit. This is controlled by the low frequency oscillator and a simple logic circuit. First the two decade counters are reset to zero and then a gate at their input is activated. Input pulses then flow into the 2-digit counter circuit until the gate pulse ends. Another pulse from the control logic circuit then activates the two latches, which store the count and feed it through to two 7-segment decoder drivers. The 2-digit display therefore shows the number of pulses received during the gate period.

This cycle is then repeated, with the decade counters being reset again. Note though that resetting the counters does not affect the latches and the old count is displayed until a new one has been taken and has been fed into the latches. The unit accordingly provides a continuous readout which is updated approximately twice per second. If the count goes beyond 99, this is detected by a monostable driven from the second counter, and this activates a warning LED.

The display circuit requires the collector current of the test components to be converted into a proportional frequency. This is not difficult and all that is needed is a CCO (current controlled oscillator) having a reasonably linear control characteristic. This leaves a slight problem in that the CCO operates as a current sink which will operate properly with PNP devices (which act as current sources) but is incompatible with NPN transistors which act as current sinks and must be fed from a current source. The solution to the problem is to drive the CCO direct from PNP transistors but to drive it via a current mirror for NPN transistor testing.

A current mirror is a very simple circuit which provides an output current that is equal but opposite to the input current it receives. One pole of the NPN/PNP switch connects the collector test socket to the input of the current mirror or the CCO, as appropriate. The other pole connects the emitter test socket to the appropriate supply rail. A bias generator

provides two switched base bias currents and these provide the unit with its two measuring ranges.

Construction


Apart from the usual off-board components (controls, sockets, and battery) all the components fit onto the printed circuit board, as detailed in Fig. 5. All the ICs are CMOS types and the usual anti-static handling precautions should be observed when dealing with these. In particular, they should all be fitted in sockets but should not be plugged into the circuit until the unit is complete in all other respects.

It is also advisable to fit the displays in sockets. Apart from eliminating the risk of them sustaining heat damage when they are fitted to the board, this is also advantageous in that it raises them clear of other components on the board. Remember that the displays must be positioned just behind a window cut in the front panel and this will not be possible if other components protrude significantly higher above the board. 0.5 and 0.56in displays are compatible with the PCB layout but the larger type generally seem to offer slightly higher brightness for a given LED current. The displays must be common cathode types.

A dozen link wires are required and these can be made from the leads trimmed from the resistors. Fit single-sided pins at the points where connections to off-board components will be made.

A plastic and metal case having approximate outside dimensions of $180 \times 120 \times 39\text{mm}$ will comfortably accommodate all the components. This assumes a reasonably small battery such as a PP3 is used. The current consumption of the unit is quite high at around $65\mu\text{A}$ and if a small battery is used it must be a 'high power' or nickel-cadmium rechargeable type.

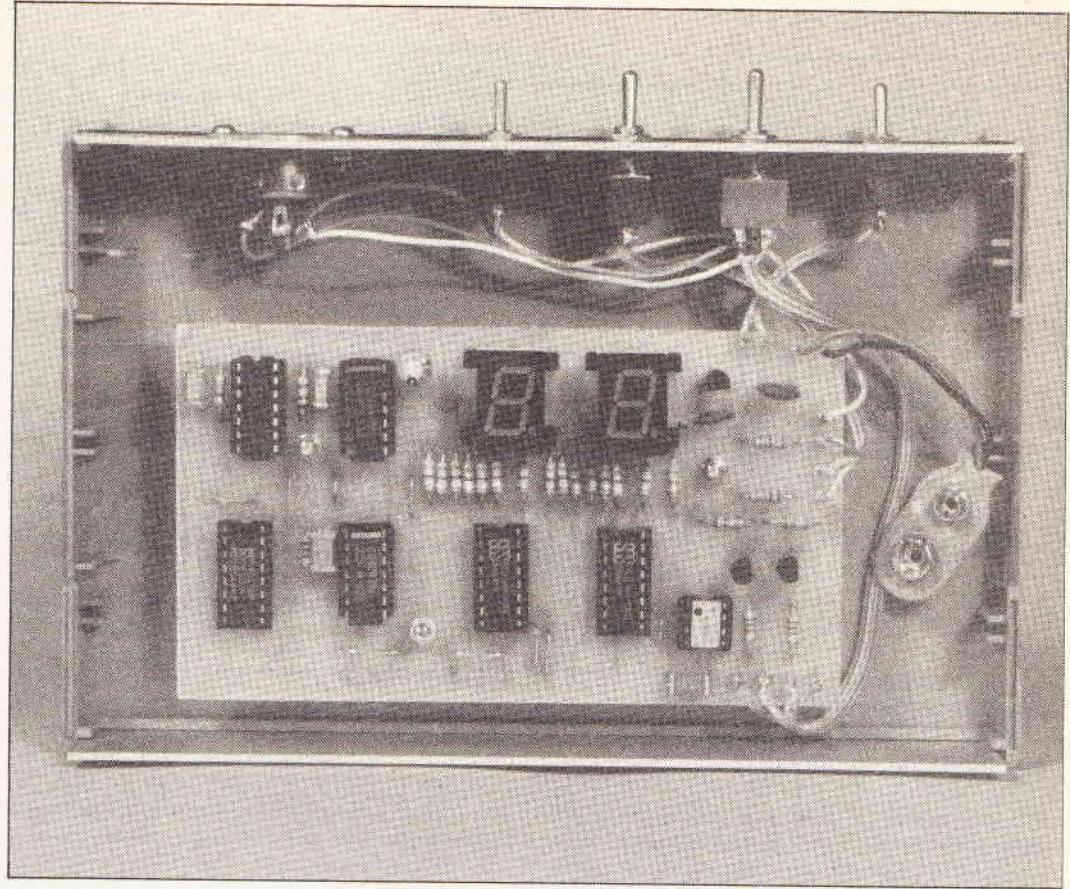The four controls and the test sockets are mounted on the front panel but the case is used vertically so that this effectively becomes the top panel. I used a 3-way DIN socket for SK1-3 and most small



PROJECT

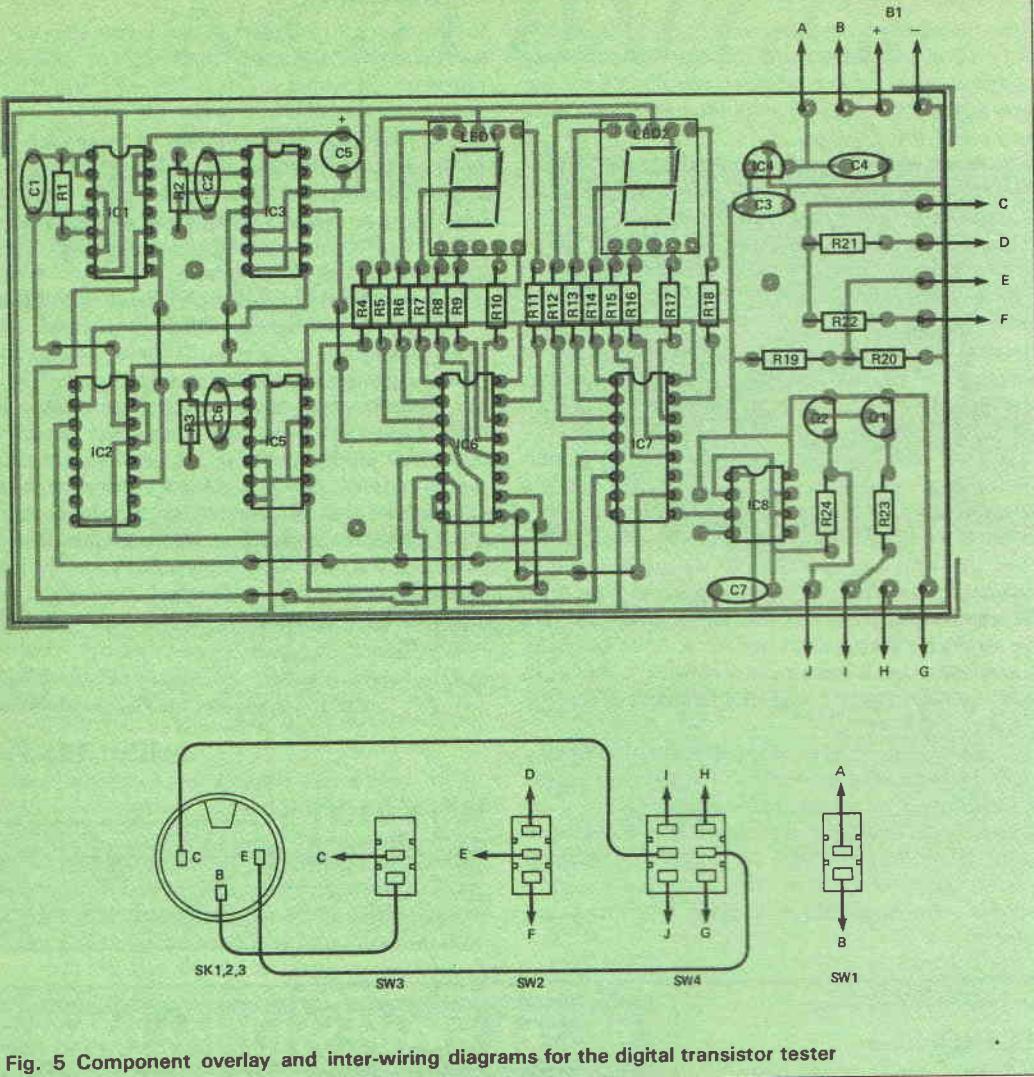


Fig. 5 Component overlay and inter-wiring diagrams for the digital transistor tester

PARTS LIST

| RESISTORS (all 1/4W 5%) | | ICs | |
|-------------------------|------------------------------|--|---|
| R1 | 470k | IC2 | 4017BE |
| R2 | 150k | IC3,5 | 4047BE |
| R3 | 1M8 | IC4 | 78L05 |
| R4-R18 | 390R | IC6,7 | 40110BE |
| R19,20 | 3k9 | IC8 | TLC555P |
| R21 | 680k | Q1,2 | BC559 |
| R22 | 68k | LED 1,2 | 0.5/0.56in common cathode 7-segment display |
| R23,24 | 220R | | |
| CAPACITORS | | MISCELLANEOUS | |
| C1 | 100n polyester | B1 | 9V [PP3] battery |
| C2 | 47n polyester | SK1-3 | 3-pin DIN socket |
| C3,4 | 100n ceramic | SW1,3 | SOST toggle |
| C5 | 100μ 10V radial electrolytic | SW2 | SPDT toggle |
| C6 | 330n polyester | SW4 | DPDT toggle |
| C7 | 220n polyester | | |
| SEMICONDUCTORS | | PCB, Case (180×120×39mm), Battery clip, IC sockets, Connecting wire, Nuts and bolts. | |
| IC1 | 4001BE | | |

transistors will connect satisfactorily with one of these. An alternative would be to use three 1mm sockets mounted in the same triangular pattern. Either way, a set of test leads terminated in small crocodile clips will be needed in order to make connections to uncooperative devices.

The printed circuit board is mounted on the rear panel (base) of the case, using 12mm stand-offs so the fronts of the displays are brought suitably close to

the front panel. A window for the displays must be cut in the front panel. This is not too difficult using a coping saw or fretsaw to make a rough initial cutout and then carefully filing this out to precisely the required size. Some red display window material is then glued in place behind the cutout.

To complete the unit the hard-wiring is added as detailed in Fig. 5. This is all pretty straightforward and should not give any difficulties.

PROJECT

In Use

After giving the wiring the usual final check, switch the unit on and observe the display. This should show an initial random number, followed about half a second later by 00. If this does not happen, switch off at once and recheck the wiring.

Assuming all is well, try connecting a few test devices to the input sockets, remembering to select NPN or PNP, as appropriate. It is unlikely that any damage will occur to silicon devices if the wrong setting is inadvertently tried but greater care should be exercised when dealing with germanium devices. With silicon transistors the leakage currents are generally so low that a 00 display should always be obtained when making leakage tests. Any other reading almost certainly indicates that the device under test is faulty.

The situation is less straightforward with germanium transistors, where quite high leakage currents are not unusual. Leakage readings of up to about 8 are quite normal but anything much higher than this would suggest the device under test is of dubious quality. Remember that gain readings must be adjusted downwards by the appropriate amount if a significant leakage level is detected. For example, if a transistor has a leakage level of 6 and a gain of 45 is measured on the x1 range then the true gain of the component is only 39.

The tester can be used to check diodes. With the cathode terminal connected to the collector socket and the anode connected to the emitter socket, there should be an overflow indication with the unit set to the PNP mode. With SW4 set to the NPN position, the display should read zero for silicon diodes and a very low reading should be obtained with germanium types.

Calibration

In common with many transistor testers, this one has no means of adjusting readings for calibration purposes. Provided C2, C7, R2, R21 and R22 all have tolerances of 5% or better, the unit should give good accuracy. The vagaries of transistor gain parameters are such that there is little point in getting too pedantic about the accuracy of a simple transistor tester. Also, to calibrate the unit it would be necessary to have a reliable transistor tester or reference devices having accurately known gains.

Beware of the transistor checkers built into some multimeters. The accuracy of these ranges often seem to be unspecified and the h_{FE} range of my analogue multimeter seems to under-read by about 50%!

The best calibration source is probably a few transistors which have had their gains accurately checked by feeding them with accurate base currents, measuring the resultant collector currents and then reaching for the calculator to work out the current gains. This is the method used to derive the optimum values for the prototype. If you wish to calibrate the finished unit, despite the difficulties involved, trim the value of R2 to give the unit the correct level of sensitivity.



BUYLINES


None of the components used in this project should cause particular problems. All are available from usual suppliers. The PCB is available from the ETI PCB service as detailed in the back of this issue.

FIELD ELECTRONICS

T.V. VIDEO - ELECTRONIC SPARES - IMPORT & EXPORT
27 CUCKOO HILL ROAD
PINNER, MIDDLESEX HA5 1AS
TEL: 01-868 5650

Super Service
Competitive Prices
Speedy Delivery

Credit Card
Orders Welcome

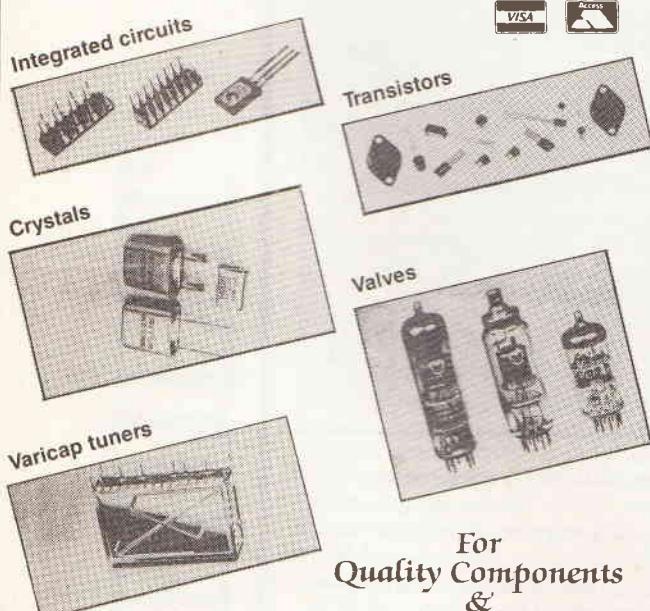

For
Quality Components
&
Fast Service

Please phone or write for catalogue. Mail order only.

METEX PROFESSIONAL DMM'S

EDUCATION AND QUANTITY
PRICES ON REQUEST



3½ and 4½ 12mm LCD Digital multimeters: 5 ranges AC and DC volts:
6 Resistance Ranges to 20M ohm: AC/DC to 20 Amps: h_{FE} Transistor test:
Diode Test: Continuity: Auto polarity and zero: Plus extra features as
below. Size 176 x 90 x 36 mm (3800 172 x 88 x 36):
All with Test Leads:
Fused: Hard carry case and instructions.

**ALL MODELS
WITH FREE
HARD CARRY
CASE**

| MODEL | DIGITS | RANGES | EXTRA FEATURES | BASIC | PRICE |
|-------|--------|--------|--|-------|--------|
| 3800 | 3½ | 32 | Low AC/DC 0/20 micro amp ranges | 0.5% | £35.00 |
| 3610 | 3½ | 30 | LED continuity indicator | 0.3% | £39.09 |
| 3630 | 3½ | 30 | 5-Range Capacitance Test | 0.3% | £45.17 |
| 3650 | 3½ | 30 | 2-Range frequency counter 5-Capacitance | 0.3% | £52.13 |
| 4630 | 4½ | 30 | Data Hold 5-Range Capacitance | 0.05% | £60.83 |
| 4650 | 4½ | 30 | Data Hold, 2-Range Freq. 5-Capacitance | 0.05% | £69.52 |

Add 15% VAT UK only - UK POST/INS etc. FREE (EXPORT EXTRA)

OPEN 6 DAYS A WEEK — CALLERS WELCOME

AUDIO ELECTRONICS

TELEPHONE 01-724 3564

301 EDGWARE ROAD, LONDON W2 1BN

ORDER BY POST OR TELEPHONE

INSTRUMENT
CATALOGUE
Ref TG
UK Send
SAE A4
£1.00

NiCd CHARGER

Most readers will know the benefits of nickel cadmium cells — they are secondary cells and, as such, may be recharged when flat. Their only real disadvantage (the high purchase price when compared with primary cells) is more than outweighed when you consider that they can be recharged over 500 times during useful life.

Naturally users of NiCds need a charger, many of which are available over the counter. The ETI NiCd Charger has one advantage over most of these commercial counterparts in that the cell type is selected with a rotary switch, so that most available types (in fact, all popular types) may be recharged.

This switched selection means those cells and batteries of lower capacity (PP3, AAA, AA) can be recharged at a higher than usual charge rate, thus reducing the time till charged. This can be most useful if you're in a rush — a PP3-sized NiCd battery can be charged from flat in a little under 20 minutes! Details of charging procedures are given later.

Construction

Two methods of construction are offered: PCB or stripboard. Neither method creates any particular problem but the usual procedures and care should be taken, depending on your chosen method.

The PCB component overlay is shown in Fig.3 while the stripboard layout is in Fig.4. There's nothing difficult in either. Solder in the links first (there's only one in the PCB) followed by circuit board pins if you use them (we recommend them!). If you're building your project on stripboard, now is the time to make all the track cuts. Next, solder in passive components, ensuring capacitor C1 is inserted the right way round. Finally, insert and solder bridge rectifier BR1 and integrated circuit IC1, making sure they are both the right way round.

Now, drill the case to mount the circuit board.

HOW IT WORKS

Full-wave rectification of the transformer's 12V AC output is performed by bridge rectifier BR1 (see Fig.1). The resultant DC voltage is smoothed by capacitor C1 to around 17V ($12 \times \sqrt{2}$).

Integrated circuit IC1 is a 7805 voltage regulator which, under normal circumstances, would regulate this to a highly stable and regulated 5V DC output. However, the connection of a resistor between the IC's output and its common connection changes its operation from a voltage regulator to a constant current generator (Fig.2). Output current of the constant current generator is given by:

$$I_{out} = I_R + I_{reg}$$

but,

$$I_R = \frac{V}{R}$$


where V is the regulator nominal voltage. So:

$$I_{out} = \frac{V}{R} + I_{reg}$$

By switching into circuit different values of resistor, different constant currents may be generated. Resistor values are calculated by rearranging the above formula, so that:

$$R = \frac{V}{I_{out} - I_{reg}}$$

Table 1 shows how the denominator is calculated for the required charge currents in the ETI NiCd Charger.

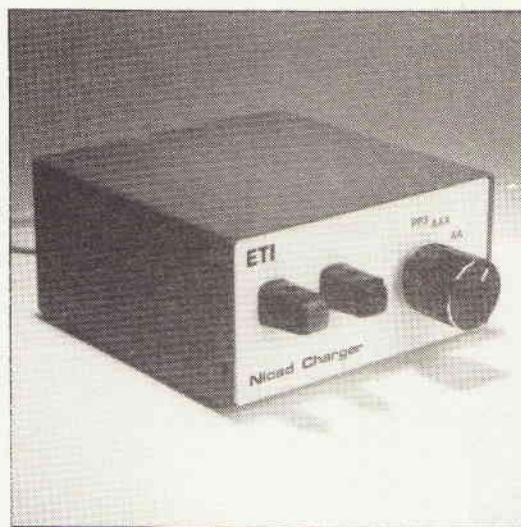

1st
CLASS

Batteries flat? Find out what shape they should be with Keith Brindley's simple charger.

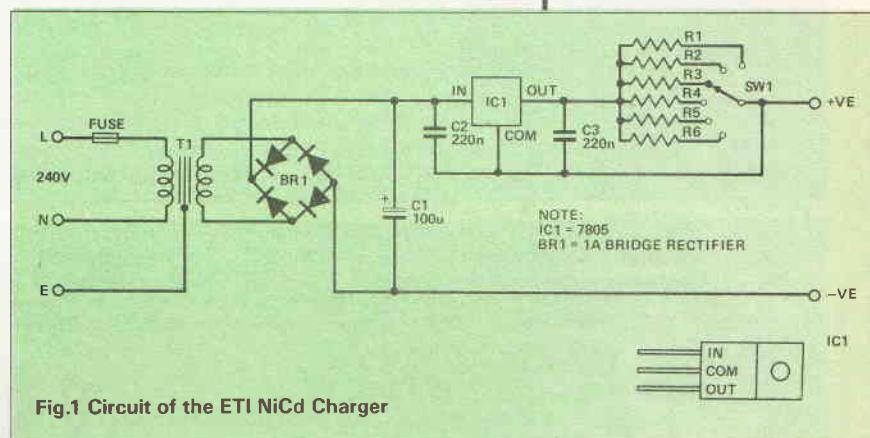


Fig.1 Circuit of the ETI NiCd Charger


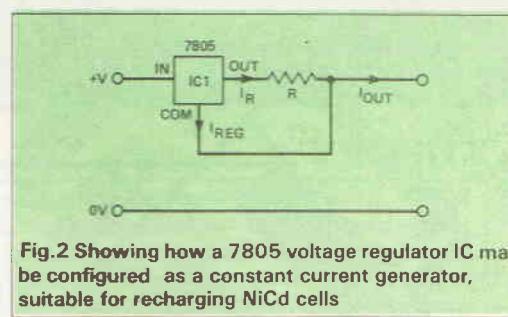


Fig.2 Showing how a 7805 voltage regulator IC may be configured as a constant current generator, suitable for recharging NiCd cells

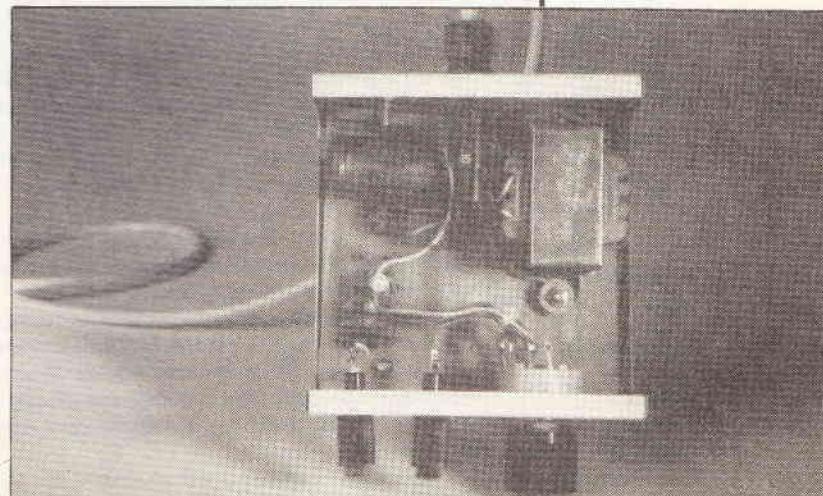

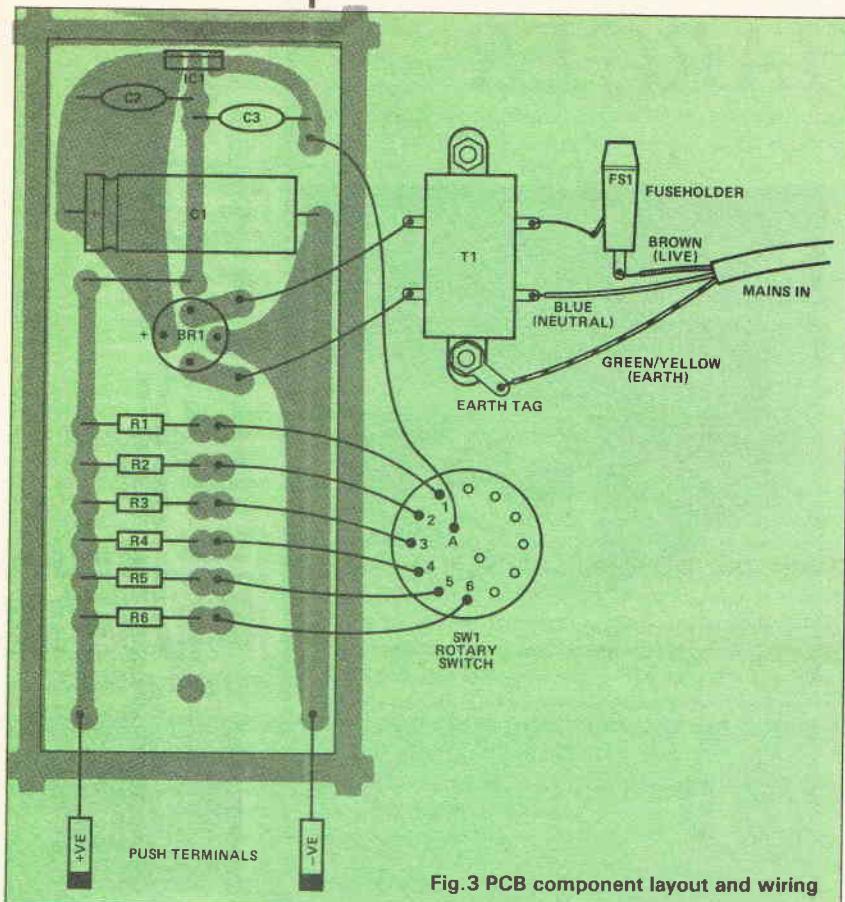


Fig.3 PCB component layout and wiring

| NiCd type | Capacity (mAh) | Current at 10h charge rate (mA) | $I_{out} - I_{reg}$ (mA) | Calculated resistance (R) | NPV (R) | Practical current (mA) |
|-----------|----------------|---------------------------------|--------------------------|---------------------------|---------|------------------------|
| PP3 | 110 | 11 | 6.5 | 770 | 820 | 12 |
| AAA | 180 | 18 | 13.5 | 370 | 390 | 48 |
| AA | 500 | 50 | 45.5 | 100 | 120 | 48 |
| PP9 | 1200 | 120 | 115.5 | 43 | 47 | 115 |
| C | 2200 | 220 | 215.5 | 23 | 27 | 200 |
| D | 4000 | 400 | 395.5 | 12.5 | 15 | 340 |

Table 1 Listing NiCd cell/battery types, capacities, charge rates and calculations for resistances used in the ETI NiCd Charger


switch SW1, terminals, fuseholder, grommet and transformer. Case markings should be applied now.

Mounting the circuit board depends on which constructional method you've chosen. The PCB is best mounted with a fixing bolt and spacer on the bottom of the case. The stripboard can be fixed using self-adhesive pads. Integrated circuit IC1 needs to be bolted to a heatsink or, if you use a metal case like us, to the back panel of the case. As well as eliminating the requirement for a heatsink, bolting IC1 to a metal case provides a second fixing point for your circuit board, too. Mount all the remaining parts.

Following the wiring layout in Fig.3 or Fig.4, wire up your project. This is where circuit board pins come in useful — your circuit board is fixed in position, and it is a relatively simple job to make all interconnections between parts.

No setting up is required but a check can be made on operation if you possess that most useful piece of test equipment, a multimeter. You'll also need at least one NiCd cell (a low resistance resistor — say, 1R0, provides an adequate simulation). Connect the multimeter and the cell(s) or resistor in series and set your multimeter to read at least 350mA FSD. Turn on and check that current values correspond approximately to those given in Table 1 in the *practical current* column. If differences of more than just a couple of percent are found, check all components for polarity and value.

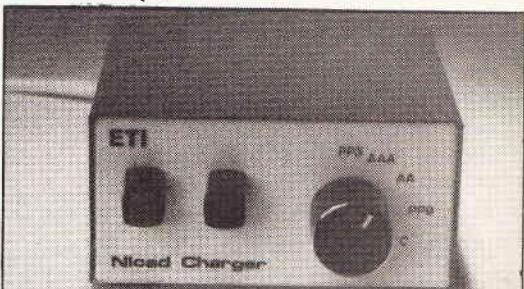In use, you'll need a cell holder of some description, depending on which size of cell, and how many, you want to charge. At the charge rates used (a maximum of 340mA) no problems will be encountered if you want to use cheap plastic cell holders. PP3 and PP9-sized batteries can be connected to the Charger with simple battery connector clips.



THEORY

NiCd cells are rated by capacity — the total amount of electrical energy expressed in Ah or mAh — which can be obtained from them from a fully charged state. In common with other forms of secondary cells, this capacity (given the notation C1) depends on the rate of discharge, so it's best to express C under fixed conditions — usually the rate which brings the cells to an end-point of 1V in five hours — the *five hour rate*.

From this capacity we can calculate rates of charge so that the cells will not be damaged by excessive currents. A couple of rules-of-thumb help here. First, a totally discharged cell can be recharged by a current for a given length of time, calculated from the capacity. Thus a cell with a 1Ah capacity can be recharged from fully discharged by a 1A current for 1h or a 100mA current for 10h or a 10A current for 6 minutes (0.1h) and so on.

Problems can arise, however, because you cannot always be sure a cell is fully discharged, so the cell may become overcharged before the calculated recharge cycle time has elapsed.

Under certain conditions, an overcharge may not cause damage. Many cells (most single cells, such as AAA, AA, C and D-sized cells) are vented so the gases given off when overcharged are released to the atmosphere. Some cells, on the other hand (button cells used in the construction of PP3 and PP9-sized NiCd batteries) are not vented and will explode if overcharged.

This is where the second rule-of-thumb comes in. If a cell or

battery is charged at a rate of C/10, no damage will occur if the charge cycle time is extended by, say, 50%. At a charge rate of C/16, most single cells can remain permanently on charge. Button cells, however, can only remain on charge permanently with a charge current of C/100.

The ETI NiCd Charger is set by resistance values to give a charge rate of C/10 to connected NiCd cells or batteries, thus ensuring an overnight charge is sufficient to give a full recharge. Nearest preferred resistances used in the project, however, mean that a charge of slightly more than 10 hours is required — around 12 to 16 hours, in fact.

Saying all that, it is still perfectly feasible to recharge NiCd cells much more quickly than this, as long as you're sure they are fully discharged! A fully discharged PP3-sized NiCd battery, for example, may be recharged by charging it at the D-cell charge rate (340mA), for a shorter period of time. A quick calculation:

$$\frac{110}{340} \times 60 = 19.4$$

tell us the battery can be recharged in a little over 19 minutes. If you're going to do this, mind you, keep checking the battery temperature, particularly towards the end of the cycle. And for the sake of your living room's decoration, don't forget the battery's on charge!

PARTS LIST

RESISTORS (1/4W 5%, unless stated)

| | |
|----|---------|
| R1 | 820R |
| R2 | 390R |
| R3 | 120R |
| R4 | 47R |
| R5 | 27R, 1W |
| R6 | 15R, 2W |

CAPACITORS

| | |
|------|---|
| C1 | 1000μ, 25V electrolytic (axial for PCB, single-ended for strip). |
| C2,3 | 220n polyester |

SEMICONDUCTORS

| | |
|-----|---------------------------------------|
| BR1 | W005, or similar, 1A bridge rectifier |
| IC1 | 7805 5V voltage regulator |

MISCELLANEOUS

| | |
|---|---------------------------|
| FS1 | 500mA fuse & holder |
| SW1 | 6-way rotary switch |
| T1 | 12V 6VA mains transformer |
| PCB or stripboard, Case, Knob, Terminals, Battery holder, Wire, | |

BUYLINES

None of the components used in the project is difficult to obtain and all should be found at your local outlet or mail order store. The PCB is available from the ETI PCB Service.

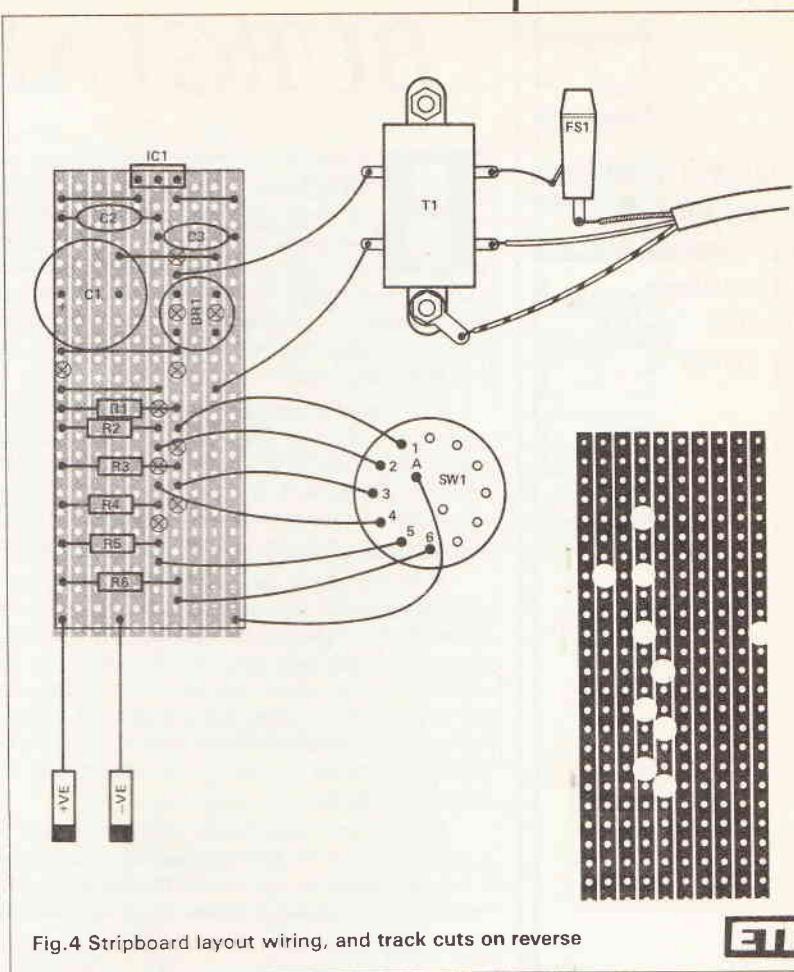


Fig.4 Stripboard layout wiring, and track cuts on reverse



FOR ALL THE DETAILS OF THIS AND MANY OTHER ELECTRONICS PROJECTS, GET

ETI

ELECTRONICS TODAY INTERNATIONAL

SUBSCRIPTION RATES

| | |
|---------------------------|---------|
| 12 issues UK | £18.00 |
| 12 issues Europe | £22.20 |
| 12 issues Middle East | £22.40 |
| USA | £24.00 |
| Air Mail Rates on Request | £22.70 |
| | \$34.00 |

Send this form with your remittance to:

INFONET, 5 River Park Estate, Berkhamsted, Herts, HP4 1HL.

Please begin my subscription(s) to ELECTRONICS TODAY INTERNATIONAL

I enclose my cheque/postal order for £.....

or debit £.....

valid from

NAME (Mr/Mrs/Miss)

ADDRESS

Postcode

Signature

Date

Please use BLOCK CAPITALS and include post codes

BURGLAR BUSTER

Paul Chappell stands by to repel burglars with this simple alarm to use the free components on this month's cover

By this time next year, if statistics are anything to go by, over five hundred ETI readers will have become victims of burglary. I don't mean to imply that there are civil service bureaucrats beavering away somewhere over ETI-related crime figures, I'm just assuming that electronics enthusiasts have about the same chance of being burgled as anybody else, and doing my sums accordingly.

The aim of this project is to make sure that our readers are no longer a representative sample of the population. If most of you build the alarm system (and since the components and PCB are free, there's no excuse not to!) then perhaps only a hundred or maybe only ten or possibly none at all will suffer burglary!

A simple alarm circuit with some of the more popular detection devices is shown in Fig. 1a. The sense circuit consists of a complete loop of wire which visits each of the detection devices in turn. As long as all the switches remain closed, the control box sees the loop as a short circuit. If any single switch opens, the loop is broken and the control box causes the bell to sound. Cutting the wire in the sense loop also sounds the alarm.

For this very basic circuit, all you'd need in the control box would be a relay and a mains transformer. If the relay drew its coil current via the sense loop, breaking the loop would cause its contacts to open.

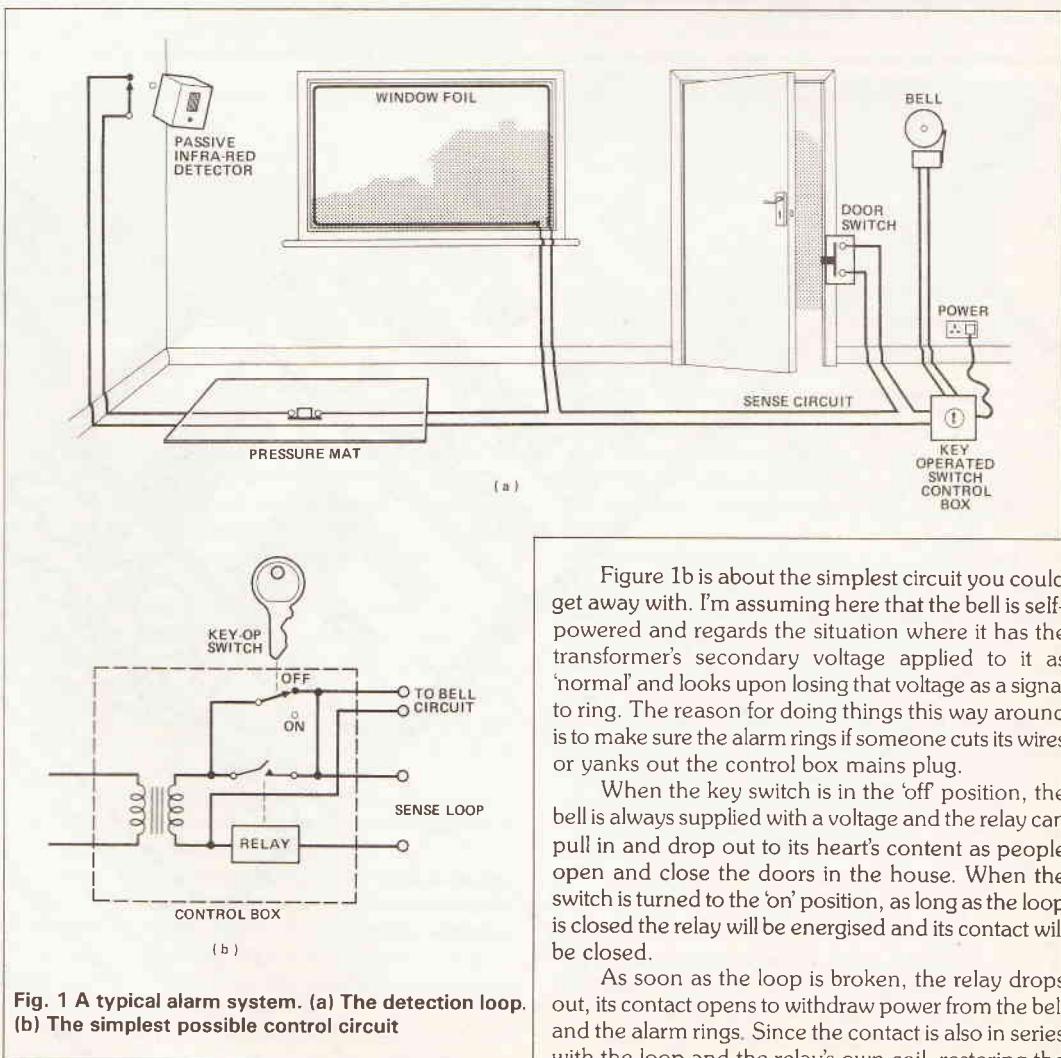
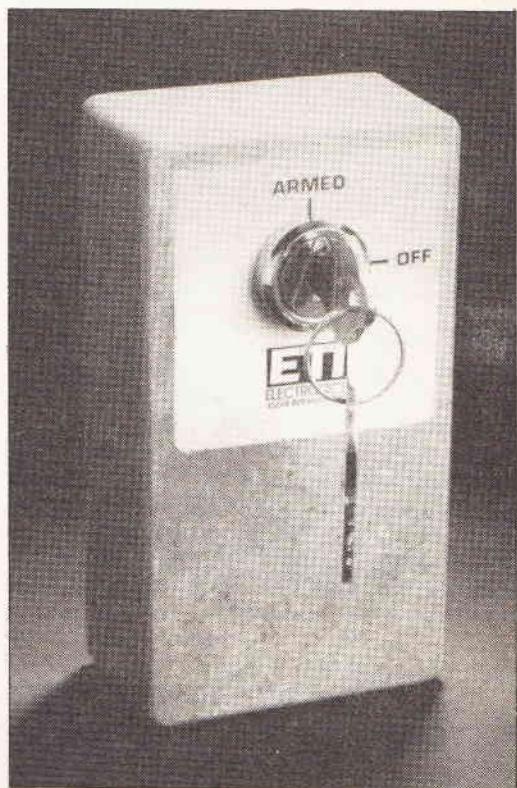


Fig. 1 A typical alarm system. (a) The detection loop. (b) The simplest possible control circuit

Figure 1b is about the simplest circuit you could get away with. I'm assuming here that the bell is self-powered and regards the situation where it has the transformer's secondary voltage applied to it as 'normal' and looks upon losing that voltage as a signal to ring. The reason for doing things this way around is to make sure the alarm rings if someone cuts its wires or yanks out the control box mains plug.

When the key switch is in the 'off' position, the bell is always supplied with a voltage and the relay can pull in and drop out to its heart's content as people open and close the doors in the house. When the switch is turned to the 'on' position, as long as the loop is closed the relay will be energised and its contact will be closed.

As soon as the loop is broken, the relay drops out, its contact opens to withdraw power from the bell and the alarm rings. Since the contact is also in series with the loop and the relay's own coil, restoring the

PROJECT

loop won't stop the alarm from ringing. It must be turned off with the key.

With little more than a relay (and another relay and some batteries for the bell) we already have a working circuit with a certain amount of resistance to being tampered with. What more can be added? The answer is that it depends just how secure you want to be and how much you want to spend on the alarm. Most systems have more sophisticated anti-tamper arrangements (although Fig. 1b won't stand for having its loop wires cut, shorting them together will knock out every switch downstream of the short!) Some have several loops, so that if one is out of action the others will still be on the alert. It's simply a matter of anticipating possible weaknesses and doing all you can to overcome them.

One little problem with Fig. 1b is how do you get out of the house once the alarm is turned on? You have the choice of either leaving the front door without a loop switch or of putting the key switch outside the house. Both put a point of weakness in the system — the first for obvious reasons, the second because any self-respecting burglar could lay his hands on the tools to uproot the switch and could then de-activate the alarm without difficulty.

Most alarms overcome this problem by allowing time for entry or exit through one particular door. Once you turn on the alarm you have maybe thirty seconds to leave the house and close the front door before the switch is armed. When you come back in, you have the same amount of time to dash to the control box and turn the alarm off.

The ETI alarm, using just the free PCB and components, is a two loop system: one sense loop and one anti-tamper loop. There is also space on the PCB for timed entry and exit circuitry which you can add if you wish. The resulting alarm can be used with just about any commercial detection apparatus from pressure mats and window foils to infra-red beams and body heat sensors. Heaven help the poor burglar who comes within range!

The Circuit

The alarm circuit you can build with the free components is shown in Fig. 2. It has two loops — one to sense any attempt to break into your house, the other to detect interference with the wiring or fittings. Both loops must be closed to prevent the alarm from sounding.

In the 'off' position, the key switch supplies 17V to the alarm sounder and allows the relay to pull in whenever both loops happen to be closed. In the 'on' position the relay will only remain energised as long as both loops are intact. As soon as anything is disturbed, the relay drops out, removes the 17V supply to the alarm sounder and also breaks the circuit to its own coil so it can't pull in again even if the loops are restored. The only way to stop the alarm from ringing is to turn it off with the key.

Figure 2b shows a suitable power supply (you can use any 12V mains transformer) and Fig. 2c is a simple alarm sounder. Under normal conditions the sounder's relay will be energised and the battery will charge via D1 and R2. As soon as the control circuit removes the power from the sounder, the relay drops out (D1 prevents the battery from holding it in) and the battery becomes connected across the bell.

In the control circuit, R3 drops the surplus 5V not needed by the 12V relay, R2 and C1 help to avoid accidental triggering of the alarm by interference picked up on the loops, R1 sets a suitable loop current and base drive for Q1 and D1 protects Q1 from the high voltage that would otherwise be generated on removing current from the relay coil.

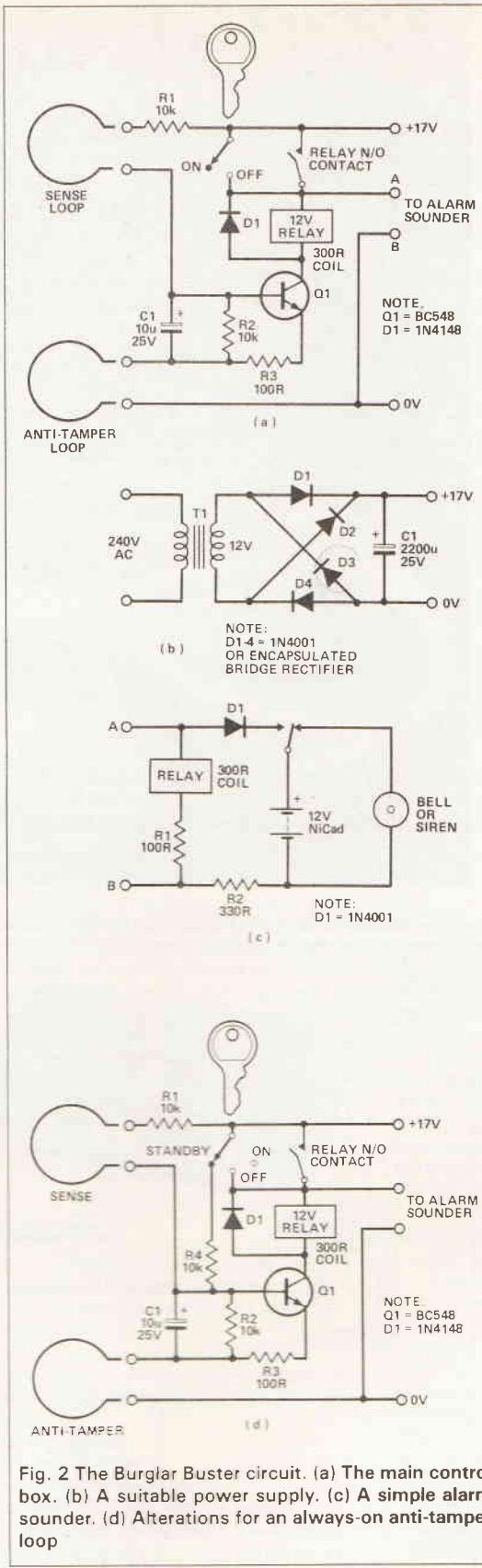


Fig. 2 The Burglar Buster circuit. (a) The main control box. (b) A suitable power supply. (c) A simple alarm sounder. (d) Alterations for an always-on anti-tamper loop

Instead of de-activating the alarm entirely, you might prefer to leave the anti-tamper loop running at all times. Figure 2d shows how this is done: the extra 'standby' position on the key switch disables the sense loop but keeps the anti-tamper circuit in operation.


The Anti-Tamper Loop

The usual way to wire an alarm system is shown in Fig. 3 and since all commercial fittings are intended





PROJECT

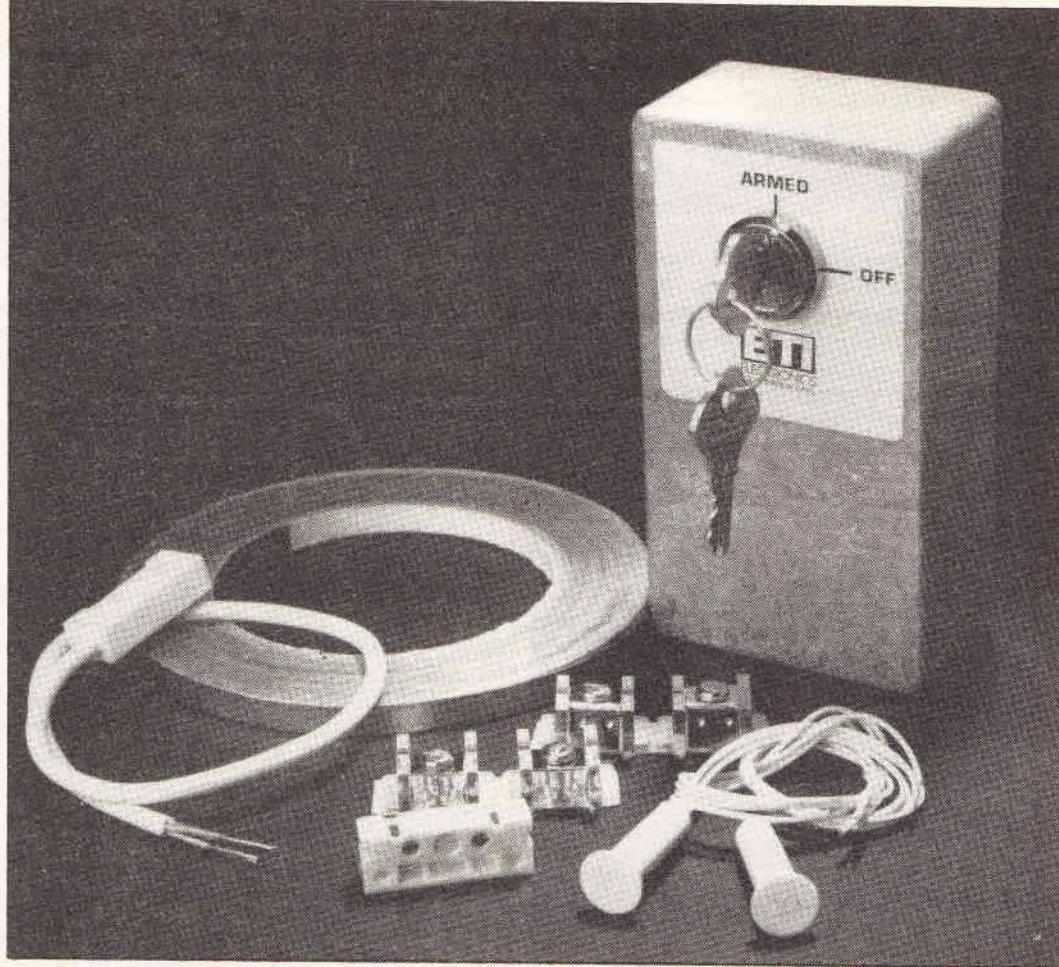

to be used this way, it's as well to stick to it! Both pairs of loop wires travel together along a single four-core cable. Whenever a detection device is to be fitted, the cable enters a junction box. (Some of the more complicated devices such as infra-red sensors and so on will have an internal junction strip but the principle

is exactly the same). The wiring inside the junction box looks complicated but the idea is just to allow the sense loop to be broken by the detection device and the anti-tamper loop to be broken if anybody removes the cover to interfere with the wiring.

If a burglar attempts to interfere with the wiring

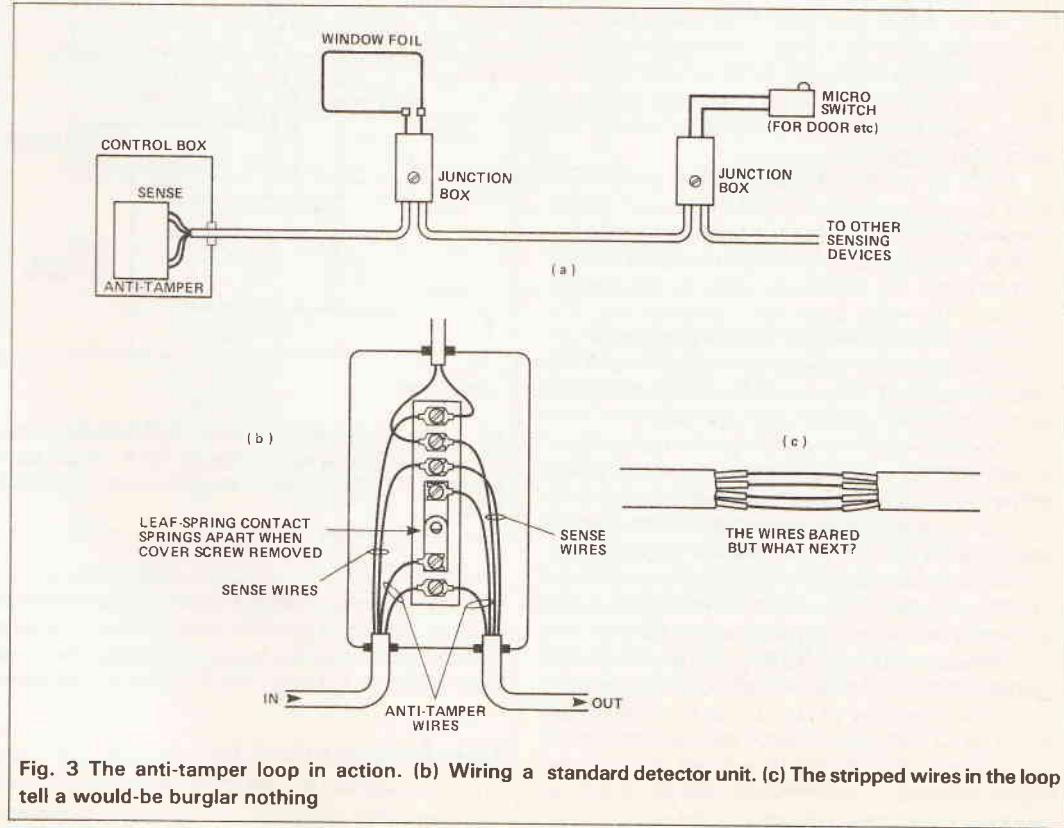


Fig. 3 The anti-tamper loop in action. (b) Wiring a standard detector unit. (c) The stripped wires in the loop tell a would-be burglar nothing

elsewhere, he will be faced with four wires (Fig. 3c). What does he do? Cutting any one of them will sound the alarm, and so will shorting either of the sense wires to either of the anti-tamper wires. Will he risk shorting two wires together to see what happens? Not if he's got any sense!

The control box can protect itself against attack in the same way — a micro switch held closed by the lid can be wired in series with the anti-tamper loop to prevent anybody getting at the insides. Another pair of wires on the same circuit can run up to the bell just to confuse the issue if anybody has a go at the wiring but unless the burglar carries a 17V power supply in his tool kit he's not going to be able to do much harm there.

Parts and Equipment

Just about any electronics catalogue will offer a range of burglar alarm parts: junction boxes, suitable wire, proximity detectors, pressure mats, window foils, and so on. Much of the equipment you can make yourself quite easily. To wire up doors, for instance, you could simply use a micro switch in the door frame (on the hinged side of the door) mounted so that the plunger is held down when the door is closed. It's usual to fix a metal plate to the door to prevent the plunger from digging a hole in the wood.

Proximity detectors (in this case, a posh name for a reed switch and magnet) are considered to be more reliable than micro switches and once again you can fix up a reed in the door frame and magnet on the door without having to go for the commercial versions (which come encapsulated in plastic but apart from that are exactly the same).

The most important thing is to get all the doors and windows wired up. Once you've done that, you

can add more exotic devices at your leisure. I hardly need point out that you'll find all kinds of alarm-related projects if you flick through the pages of your back numbers of ETI.

Key-operated switches are readily available from component suppliers but if you're keen to save money you could nip down to your local car breakers (no, not the type who say 'ten-ten till we do it again' or whatever, I mean the ones who sell odds and ends from old cars) and buy an old ignition switch. As long as they've also got the key, that is!

The relay needn't have a coil resistance of 300R on the dot — a common resistance for small relays seems to be 280R and that's just fine. If the resistance is too far out, you'll have to change the value of R3 to suit. Calculate the current taken by the coil at 12V, then choose R3 to drop 5V at the current you've just calculated. Even easier — make R3 about 5/12 of the coil resistance, to the nearest preferred value, or perhaps one notch below to allow for the voltage drop across Q1 and the supply voltage drop under loaded conditions. Try to avoid coil resistance below about 250R — it increases the dissipation in Q1 and R3 unnecessarily.

Next Month

There's not much point in starting on the construction right now — you haven't got the PCB yet. It will arrive on the cover of next month's mag, so start queueing at your newsagent right away! (Or take out a subscription . . .)

I will also be telling you how to adapt the circuit to give timed exit and entry — there's room on the PCB for this too. There will be a beeper to let you know that you have thirty seconds to escape from the house before the alarm erupts and deafens you . . . and all kinds of things besides. Don't miss it!

PROJECT

ETI

INTERBEEB

£49.95



The Interbeeb unit connects to the BBC micro's 1MHz bus expansion connector and is supplied complete with its own power supply unit.

The interface unit is housed in a plastic case approx 4½x3x1in which contains the top quality double sided PCB and interface connectors.

- 8-bit input port
- 8-bit output port
- four switch sensor inputs
- four relay-switched 12V 1A outputs
- eight channel multiplexed analogue to digital converter
- precision 2.5V reference
- external power supply
- 15-way expansion bus

All sections of the interface are memory mapped in the 1MHz expansion map for maximum ease of use and compatibility with existing peripherals.

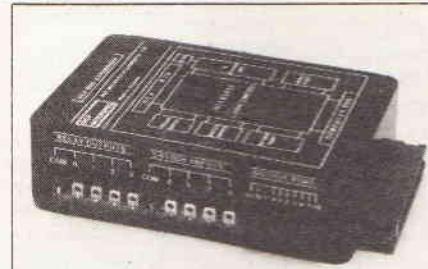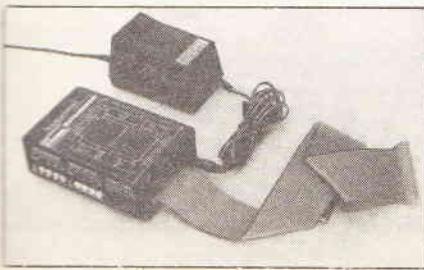The expansion bus provides all the data and address/control signals for the addition of further DCP modules or home-built devices. All the information required for using additional devices is included.



INTERSPEC

£29.95

The Interspec unit plugs directly onto the expansion edge connector of the Spectrum to provide a full range of interfacing facilities.

The unit is housed in a plastic case approximately 4½x3x1in which contains the top quality double sided PCB and interface connections.

- 8-bit input port
- 8-bit output port
- four switch sensor inputs
- four relay-switched 12V 1A outputs
- eight channel multiplexed analogue to digital converter
- 15-way expansion bus

All sections of the interface are I/O port mapped and designed for maximum compatibility with existing Spectrum peripherals. Power is supplied through the Spectrum edge connector.

The expansion bus provides all the data and address/control signals for the addition of further DCP modules or home-built devices. Connection is by multi-way PCB connector and all the information required for adding further devices is given.

SPECIAL OFFER FOR SPECTRUM AND BBC MICRO OWNERS

Now your computer can take control for an affordable price. These tried and trusted interfaces from DCP Microdevelopments are offered at £20 off the normal price.

Both units are extremely easy to use from both Basic and assembler/machine code and are supplied ready built and complete with all the documentation you need.

To order by post fill in the form below (or a copy) and send it with your remittance to **ASP READERS' SERVICES (RO ET5/6)**
9 Hall Road, Maylands Wood Estate,
Hemel Hempstead, HP2 7BH

Please make cheques payable to ASP Ltd. Overseas orders add £5 (Interspec) or £10 (Interbeeb) for airpost.

Access and Visa card holders can also place their order by phone on (0442) 41221 Allow 28 days for delivery.

Please supply Interspecs (RO ET5) at £29.95 plus £1.95 p&p per order.

Please supply Interbeeb (RO ET6) at £49.95 plus £1.95 p&p per order.

Name

Address

.....


Please debit my ACCESS/VISA card

No to the sum of

£ Signed:

POWER CONDITIONER

FEATURED IN ETI
JANUARY 1988

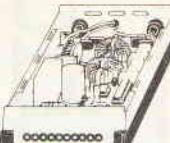

The ultimate mains purifier intended mainly for lowering the noise floor and improving the analytical qualities of top-flight audio equipment.

The massive filter section contains thirteen capacitors and two current balanced inductors, together with a bank of six VDRs. To remove every last trace of interference and RF interference. A ten LED logarithmic display gives a second by second indication of the amount of interference removed. Our approved parts set consists of case, PCB, all components including high permeability toroidal cores, ICs, transistors, class X & Y suppression capacitors, VDRs etc., and full instructions.

PARTS SET £28.50 + VAT

Some parts are available separately. Please send SAE for lists, SAE + £1 for lists, circuit construction details and further information free with parts set.

THE DREAM MACHINE

FEATURED IN ETI
DECEMBER 1987



Adjust the controls to suit your mood and let the gentle relaxing sound drift over you. At first you might hear soft rain, sea surf or the wind through distant trees. Almost hypnotic the sound draws you irresistibly into a peaceful, refreshing sleep.

For many, the thought of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are strange and mysterious dream experiences waiting. Take lucid dreams for instance. Imagine being in control of your dreams and able to change them at will to act out your wishes and fantasies. With the Dream Machine it's easy!


The approved parts set consists of PCB, all components, controls, loudspeaker knobs, lamp, fuseholders, fuse, mains power supply, prestige case and full instructions.

PARTS SET £16.50 + VAT


AVAILABLE WITHOUT CASE FOR ONLY £11.90 + VAT

MAINS CONDITIONER

FEATURED IN ETI
SEPTEMBER 1986

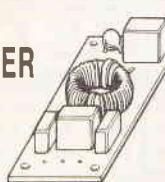

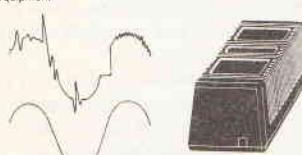Cleans up mains pollution easily and effectively. You'll hardly believe the difference in your Hi-Fi, TV, Video, and all other sensitive equipment.



PARTS SET £4.90 + VAT

RUGGED PLASTIC CASE £1.65 + VAT

POWERFUL AIR IONISERS



Ions, the miraculous vitamins of the air have been created with almost magical powers.

They are said to improve concentration, reduce blood pressure, help you sleep better, and even to raise you IQ! Although some of the claims may be exaggerated, there's no doubt that ionised air is cleaner, purer and more invigorating than dead air. Anyone who has owned an ioniser would never again want to be without one!

The *Mistrail* caused a sensation when it appeared as a project in ETI. Two years later, in October 1988, the *Mistrail* was unveiled. Which will you go for - the compact, powerful valve for money Direct-Ion or the sophisticated, no-compromise *Mistrail*? The choice is yours!

MISTRAIL IONISER PARTS SET £24.80 + VAT

DIRECT-ION PARTS SET (BLACK CASE) £11.50 + VAT

DIRECT-ION PARTS SET (WHITE CASE) £11.80 + VAT



KNIGHT RAIDER

FEATURED IN ETI
JULY 1987

The ultimate in lighting effects for your Lamborghini. Materials: BMX (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves rapidly from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a bit, bouncing backwards and forwards along the row. Press again and try one of the other six patterns. An LED display on the control box lets you see what the main lights are doing.

The Knight Raider can be fitted to any car (it makes an excellent fog light!) or with low powered bulbs it can turn any child's pedal car or bicycle into a spectacular TV-age toy!

The parts set consists of box, PCB and components for control, PCB and components for sequence board, and full instructions.

Lamps not included.

PARTS SET £19.90 + VAT

RAINY DAY PROJECTS



All can be built in an afternoon!

JUMPIN' JACK FLASH (ETI March 1988)

Spectacular rock stage and disco lighting effect!

CREDIT CARD CASINO (ETI March 1987)

The wicked pocket gambling machine

MAINS CONTROLLER (ETI January 1987)

Isolated logic to mains interface

MATCHBOX AMPLIFIERS (ETI April 1986)

Listen, SOW of Hi-Fi power! Iron! an amp small enough to fit in a matchbox

Matchbox Amplifier (20W)

Matchbox Bridge Amplifier

L165V Power Amplifier IC with data and circuits

TACHODWELL METER (ETI January 1987)

Turn your Metro into a Porsche!

HI-FI POWER METER (ETI May 1987)

Measures Hi-Fi output power up to 100W

- includes PCB, components, meters

Mono power meter

Stereo power meter

£6.50 + VAT

£5.90 + VAT

£6.20 + VAT

£6.50 + VAT

£8.90 + VAT

£3.90 + VAT

£16.40 + VAT

£3.90 + VAT

£7.20 + VAT



FEATURED IN ETI
AUGUST 1988

There's nothing quite so encouraging as having a quantifiable result to show for your training efforts. If you are not particularly fit, your resting heart rate will be around 80 beats per minute. As your jogging, aerobics or sport strengthens your heart, the rate will drop dramatically - possibly to 60 bpm or less. With the S101 you can watch your progress day by day.

Breathing is important too. How efficiently do you take up oxygen? How quickly do you recover from oxygen debt after strenuous activity? The S101 will tell you know.

The approved parts set consists of case, 3 printed circuit boards, 36 components (including 17 ICs, quartz crystal, 75 transistors, resistors, diodes and capacitors), LCD switches, plugs, sockets, electrodes, and full instructions for construction and use.

PARTS SET £33.80 + VAT

Some parts are available separately. Please send SAE for lists, SAE + £1 for lists, circuit construction details and training plan (free with parts set).



ARMSTRONG 75W AMPLIFIER

FEATURED IN PE
JULY 1988



A.J. Armstrong's exciting new audio amplifier module is here at last!

Delivering a cool 75W (conservatively rated - you'll get nearer 100W), this MOSFET design embodies the finest minimalist design techniques, resulting in a clean, uncluttered circuit in which every component makes a precisely defined contribution to the overall sound. You can read all about it in the July issue of PE, but why bother with words when your ears will tell you so much more?

Parts set includes top grade PCB and all components.

SPECIAL INTRODUCTORY PRICE FOR FULLY UPGRADED MODULES.


SINGLE PARTS SET £14.90 + VAT

STEREO PAIR £25.90 + VAT

Please send SAE + £1 for data and circuits (free with parts set), including diagrams for matching pre-amp and power supply. This amplifier will not be available from your usual audio supplier - we produce the only designer approved parts set.

BIO-FEEDBACK

FEATURED IN ETI
DECEMBER 1986

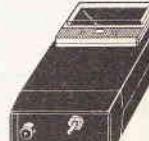

Bio-feedback comes of age with this highly responsive, self-balancing skin response monitor! The powerful circuit has found application in clinical situations as well as on the bio-feedback scene. It will open your eyes to what GSR techniques are really all about.

The complete parts set includes case, PCB, all components, leads, electrodes, conductive gel, and full instructions.

PARTS SET £13.95 + VAT

BIO-FEEDBACK BOOK £3.95 (no VAT)

Please note: the book by Stein and Ray is an authorised guide to the potential of bio-feedback techniques. It is not a hobby book, and will only be of interest to intelligent adults.

BRAINWAVE MONITOR



FEATURED IN ETI
AUGUST 1987

The most astonishing project ever to have appeared in an electronics magazine. Similar in principle to a medical EEG machine, this project allows you to hear the characteristic rhythms of your own mind! The alpha, beta and theta forms can be selected for study and the three articles give masses of information on their interpretation and powers.

In conjunction with Dr. Lewis's Alpha Plan, the monitor can be used to overcome shyness, to help you feel confident in stressful situations, and to train yourself to excel at things you're not good at!

Our approved parts set contains case, two PCBs, screening can for bio-amplifier, all components (including three PMI precision amplifiers), leads, brass electrodes and full instructions.

PARTS SET £36.90 + VAT ALPHA PLAN BOOK £2.50

SILVER SOLUTION (for galvanic electrodes) £3.60 + VAT

Parts set available separately. We also have a range of accessories: professional electrodes, books etc. Please send SAE for lists, SAE + £1 for lists, circuit construction details and further information (free with parts set).

LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the Next Great Little IC feature (ETI, December 1986).

LM2917 EXPERIMENTER SET £5.80 + VAT

LEDs

Green rectangular LEDs for bar-graph displays


50 for £3.50 500 for £25

100 for £6 1000 for £45

DIGITAL AND AUDIO EQUIPMENT LEDs

Assorted 3mm LEDs: red, green, yellow and orange

25 of each (100 LEDs) for £6.80

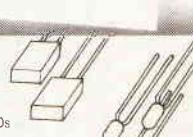

Prices shown are exclusive of VAT so please add 15% to the order total. UK postage is 70p on any order. Carriage and insurance for overseas orders £4.50. Please allow up to 14 days for delivery.

Specialist SEMICONDUCTORS LIMITED

SALES DEPT., ROOM 107, FOUNDERS HOUSE, REDBROOK, MONMOUTH, Gwent.

CHRONOSCOPE



A chronoscope is a device for measuring the velocity of an air gun pellet. Those of the shooting fraternity will realise how useful a chronoscope can be, to check the consistency of the gun, monitor its power output and compare how different pellets perform.

Commercial products are available but as usual they are expensive! This unit can be built for less than half the cost and perform equally as well.

The chronoscope is basically a counter with start and stop sensors. A pellet passes through the start sensor triggers the counter, covers a measured distance and halts the counter by passing the stop sensor. The pellet velocity can then be calculated from the display reading. Pellet velocities cover a wide range but typical values are 500 feet per second (0.22 calibre) or 800 feet per second (0.177 calibre).

Infra-red LEDs and photodiodes are used in two groups of three to detect the moving pellet. Three sensors are used to ensure that the small diameter of the pellet is reliably detected by providing a large detection zone (see Fig. 1). 0.177 calibre pellets are smaller, faster and more difficult to detect but this arrangement works well.

The chronoscope is mains powered, although it can easily be modified for battery operation. The display is a four digit LED type with a separate LED as an overflow indicator (counter exceeded 9999). The display units are 0.5 μ s counts of frequency 2MHz, this value being convenient for the formulae described later.

Construction

The chronoscope has been designed to maximise the use of printed circuit boards to ease construction. Only two components (infra-red emitters) are mounted separately. Following the component overlays (Fig. 3, 4 and 5) assemble each PCB with the smallest components first — wire links, then resistors, IC sockets, capacitors, transistors with regulators and the transformer last.

Double check polarities. Use reasonable caution

when soldering semiconductors. Don't keep the iron on the joint too long. Do not insert the ICs yet. Note the regulators require a substantial heatsink which should be made up as shown in Fig. 6.

The digital display is designed to plug on to the main board using 0.1in pitch PCB connectors. Wire links could be used but are not recommended.

On the subject of wire links, make sure that you solder the three links under the displays before inserting them in place. The display board is secured to the main board with small right angle brackets using the holes marked. The same type of brackets secure the sensor board vertically next to the plastic sensor tube.

The LED on the display board should stand slightly off the board to match the seven segment displays — a transistor mounting pad can be used here. The sensor board needs special attention when mounting the six infra-red photodiodes. These are soldered on the track side of the PCB and must be exactly six inches apart (no metric units around here!) centre to centre. Use the component overlay to align the photodiodes, as shown. Ensure the sensitive face is to the PCB track side when soldering to the board (see Fig. 7 for photodiode details), with the type markings to the component side.

The preset potentiometers are not the usual 0.4in standard type and may be difficult to obtain (see *Buylines*). Solder the 4-way ribbon cable to the sensor

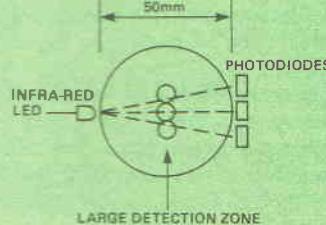


Fig. 1 The enlarged detection zone

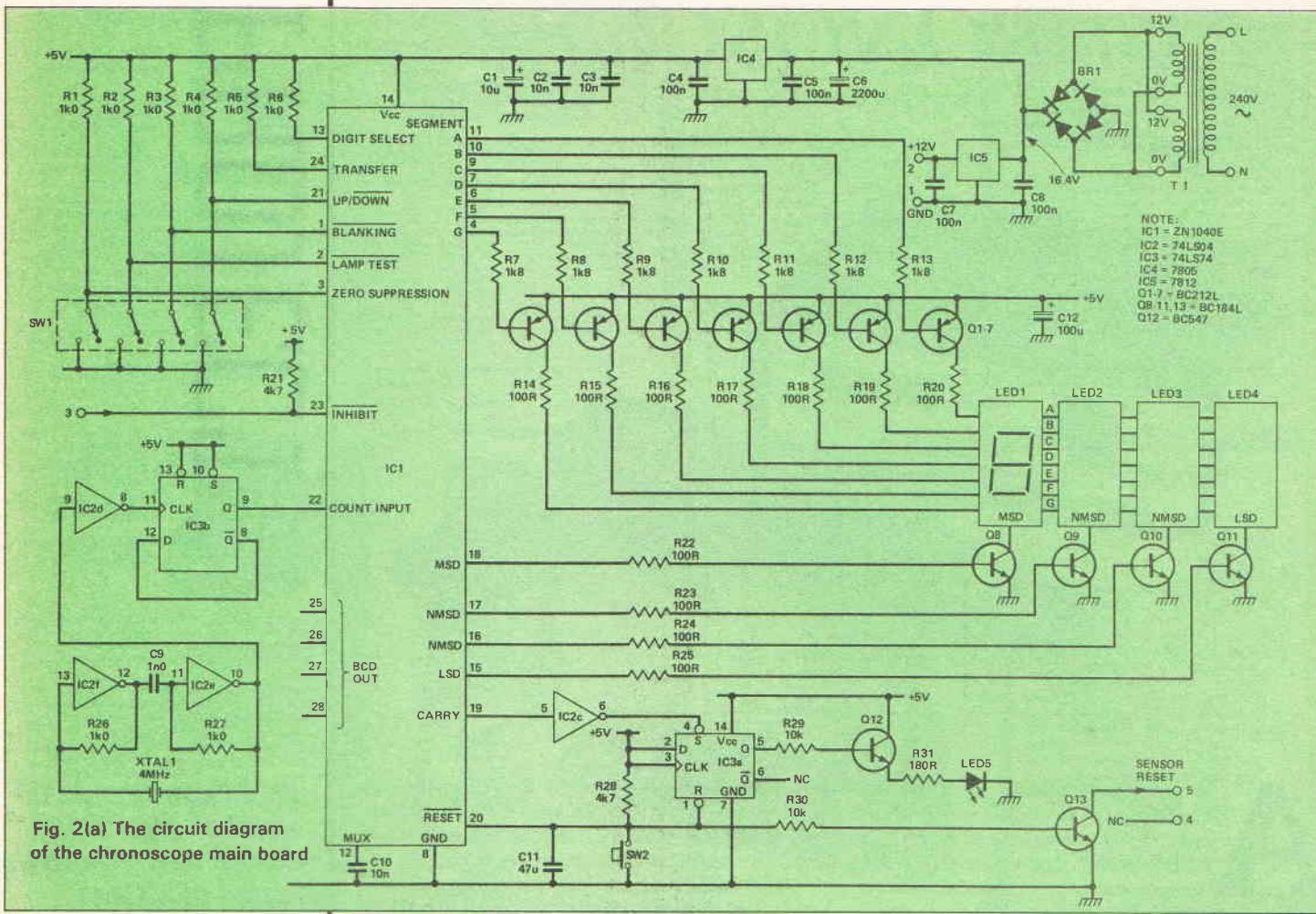


Fig. 2(a) The circuit diagram of the chronoscope main board

HOW IT WORKS

The heart of the chronoscope is the ZN1040E counter. This provides all the counter logic and display multiplexing. Two inverters of IC2 form a simple crystal oscillator with a frequency of 4MHz.

This is divided down to 2MHz by bistable IC3b, which supplies IC1 counter input (pin 22). While IC1 inhibit (pin 23) is held low, IC1 will not count. The inhibit input is toggled by the sensor board whenever a pellet is detected. If the counter overflows, the carry output (IC1 pin 19) is used to set bistable IC3a indicated by LEDs. IC3a is reset by SW5, which also zeros the counter IC1. R28 and C11 provide power on reset. SW1 selects various options on the counter IC1. SW1a ON enables leading zeros. SW1b ON provides a segment test on the display. SW1c ON blanks the display (really useful?). SW1d forces IC1 to count down (well, 4-way DIL switches are easy to obtain!).

Q1-Q7 are the segment drivers. Q8 and Q11 are digit drivers (multiplexing).

The sensor board controls IC1 inhibit. Six very high gain

operational amplifiers together with their associated photodiodes form the detectors. Infra-red light from LED6 causes a current flow in D1-3 holding the non-inverting inputs below the bias voltage set by RV1.

If light to any photodiode is interrupted momentarily, the non-inverting input rises above the bias voltage, causing a high output. The outputs feed an OR gate IC7b. Any one causes bistable IC8a to be set driving IC1 inhibit high via Q15 and starting the counter. An identical arrangement IC9, IC7c, IC7a will reset IC8a and stop the counter. IC7a OR gate allows reset from SW5. Q14, D10 and Q16, D11 monitor the bias setup, both LEDs set just off, for maximum sensitivity.

C15 are power supply decoupling to suppress unwanted spikes and noise.

The power supply is a standard bridge rectifier capacitor arrangement, supplying two voltage regulators IC4 and IC5 for 5V and 12V respectively. C1-8 provides decoupling for the ICs.

board. This then plugs on to the main board with a 0.1in PCB connector (SK4).

Solder twin ribbon cable to the infra-red LEDs and again use PCB connectors to plug on to the sensor board, observing polarity. The LEDs are fitted to the specially made brackets (see Fig. 8) using standard LED clips.

The main counter PCB is fairly straight forward but note the transformer pinout arrangement. I have noticed variations among suppliers. The DIL switch SW1 is optional and can be replaced with links to save costs. Secure the regulators to the heatsink with suitable nuts and bolts.

The boards must be mounted in a case for mains safety and to enclose the photodiodes from external light sources. A suitable tube, 5½ inches long was

used in the prototype to protect the electronics from stray pellets and to give the unit a more professional finish. A piece of plastic gutter downpipe (2in diameter) is ideal. The tube, infra-red emitter brackets and sensor board are secured to a base plate, made from plain SRBP, aluminium or fibreglass.

Secure the tube centrally to the baseplate and then position the sensor PCB and LED brackets to mark the fixing holes. See Fig. 9 for the case layout. Secure the sensor chassis and main board to the case with small self tapping screws. Fig. 10 shows the panel drilling details. The sensor hole in the front and rear panels is large (1½in). I used a Q-Max hole punch for this but if you don't have one, then drill small holes inside a marked circle and file to finish (you'll wish you had bought a Q-Max punch!).

PROJECT

PROJECT

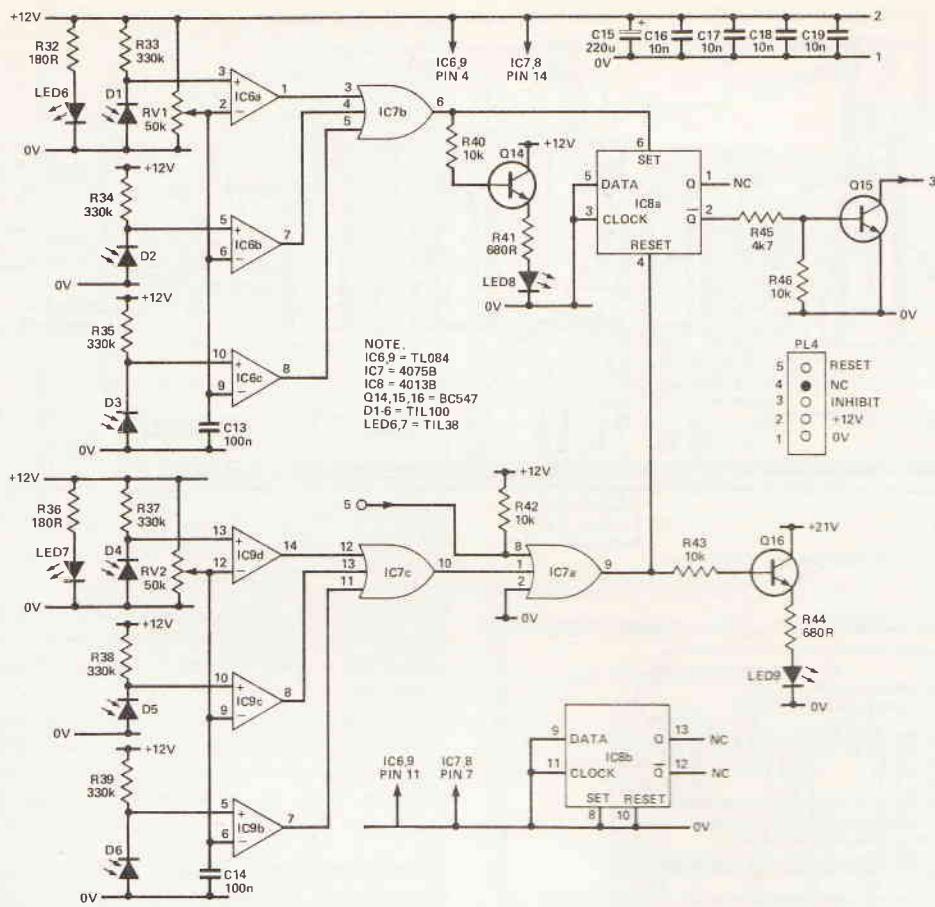


Fig. 2(b) Circuit diagram of the sensor board

Unfortunately, the rectangular hole for the display must be drilled out and filed laboriously, unless you also have a suitable rectangular punch. Paint the inside surface of the front and rear panels near the sensor hole with matt black paint to limit stray light.

Fit a red diffuser (any piece of red transparent plastic film) behind the front panel to enhance the display digits. Slide the panel into the case slots — you will have to 'bow' the panel slightly to clear the reset switch.

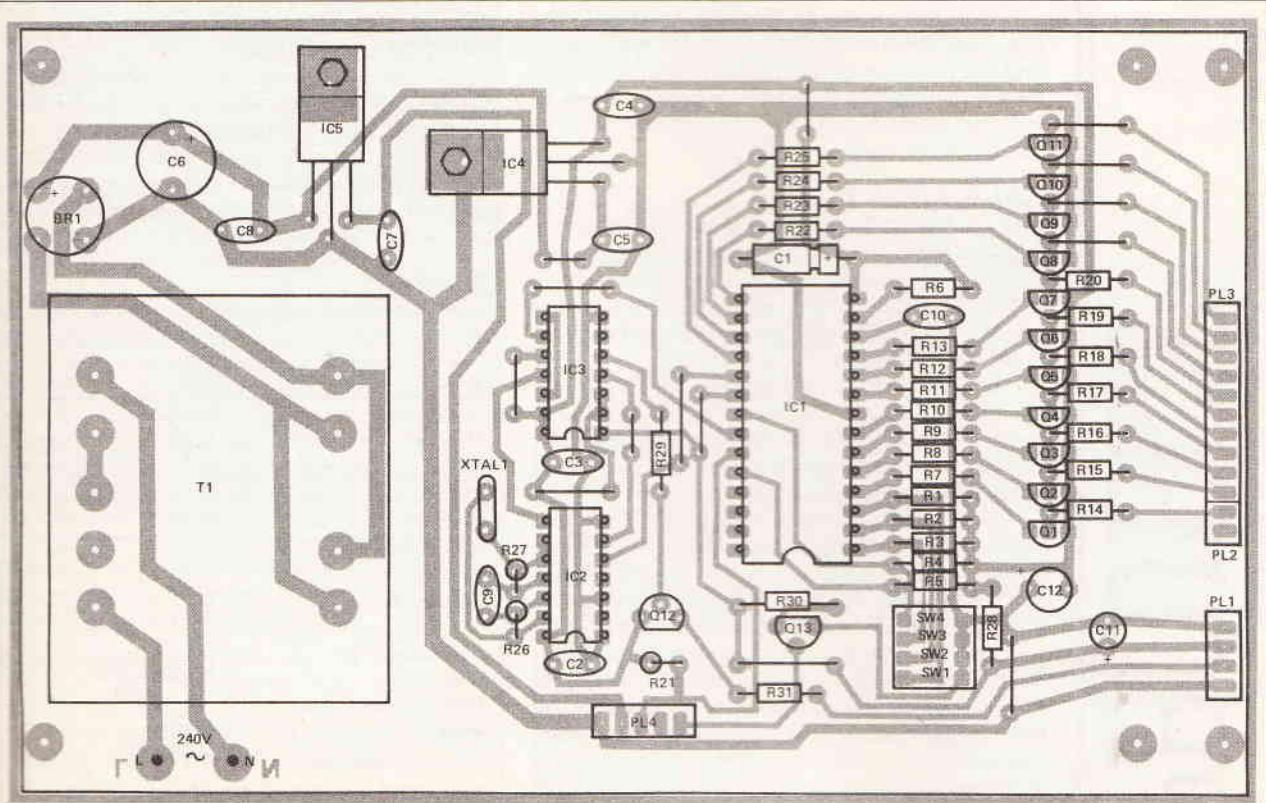


Fig. 3 The component overlay for the counter PCB

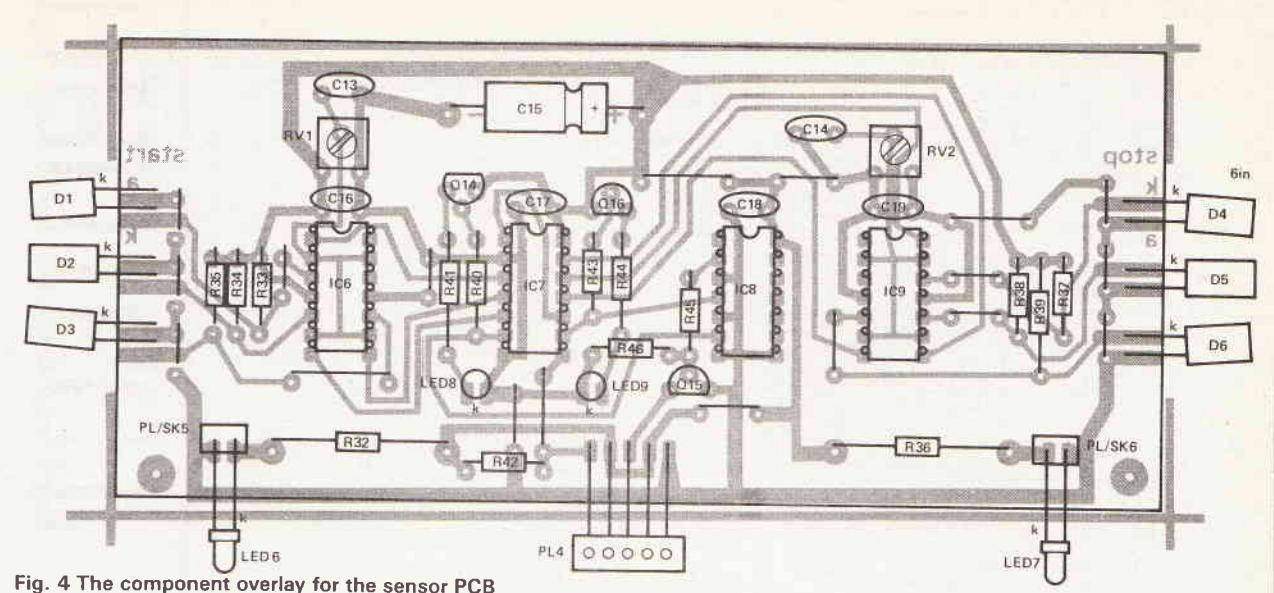


Fig. 4 The component overlay for the sensor PCB

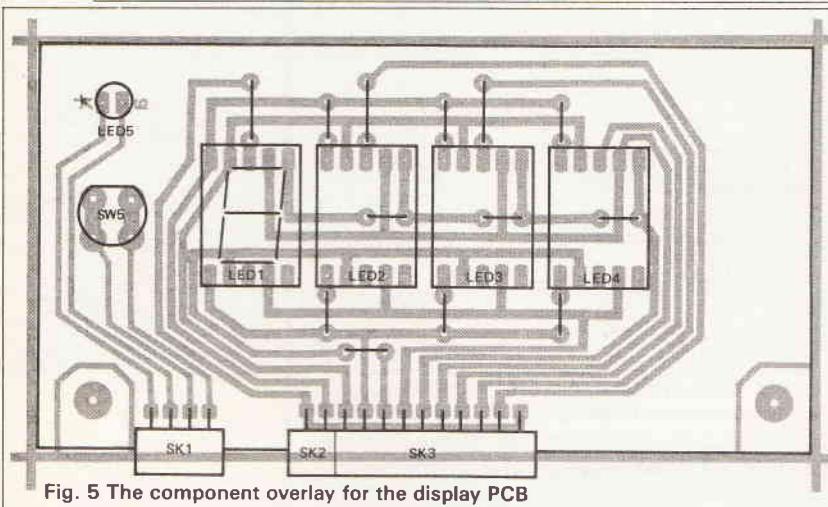


Fig. 5 The component overlay for the display PCB

Note that a mains on/off switch is not used. The Live/Neutral wires are soldered directly to the board and exit via a grommet in the rear panel. Cut a slot for the grommet so that the rear panel can still be removed easily. Finally, a mains plug fuse of 3A or less should be fitted.

Set-up And Testing

Caution! The PCB tracks near the transformer are live! Before inserting the ICs, check all the connectors are made and power up. Check that 5V is present across IC1 pin 14 and IC1 pin 8. Check that 12V is present across C15 on the sensor board. Power off and if all is OK, insert the ICs.

Set the 4-way switch bank all off. Power up and the display should illuminate. If you have an oscilloscope, you could check the clock circuit. There should be a 4MHz square wave (roughly!) at IC2 pin 8 and 2MHz at IC3 pin 9.

Set up the sensors in normal light conditions (with no strong direct sunlight and shield them from artificial lights). Adjust RV1 and RV2 so that LED8 and LED9 just go off. Press RESET and the display should now zero. Interrupt the infra-red beam at D1-3. The counter should clock happily and overflow! Interrupt the beam at D4-6 and the counter should stop. If all is well, fit the cover and prepare for the final testing with an airgun. Be careful! Air weapons are inherently dangerous and should be used with care! If you have a pellet trap, fine — if not, make one! A cardboard box with an opening 4in square, with a thick (1in to 2in) piece of wood (or 1/4 steel) in the end,

stuffed with old rags should be OK. Place this behind the chronoscope pellet 'exit' within a foot or so. This will catch your pellets safely and avoid shooting next door's cat.

Fabricate a mount for the rifle muzzle so that it rests centrally and straight, at the chronoscope 'inlet'. Zero the unit and fire a pellet through the tube, into the trap. You should obtain a reading without overflow.

Trouble Shooting

If the unit does not trigger, check that stray light is not interfering with the sensors and re-adjust RV1 and RV2. If this fails, suspect the IC2,3 clock circuit.

If the clock is started but will not stop, re-adjust RV2. (Check you are shooting straight, too!) No display at all means the 5V supply is missing or that SW1c is on.

A corrupt display shows a fault around Q1-7 or IC1 and a missing digit signifies a fault in Q8-11 or IC1.

Battery Operation

To use the chronoscope with a 12V battery for portable, on-the-range operation, omit Q1, BR1, C7, C8 and IC5 and link the two outer pads of IC5. Connect the battery to the + and - pins of BR1.

A 12V rechargeable battery is recommended due to the fairly high current consumption of the chronoscope (typically 450mA).

Results

The chronoscope display actually shows only the number of clock cycles measured between the pellet

| Type | Cal. | Grains |
|-------------------|-------|--------|
| Eley Wasp | 0.22 | 14.55 |
| Hustler | 0.22 | 12.4 |
| Milbro Caledonian | 0.22 | 13.0 |
| RWS Superpoint | 0.22 | 14.34 |
| RWS Superdome | 0.22 | 14.33 |
| RWS Hobby | 0.22 | 12.2 |
| Bulldog | 0.22 | 13.9 |
| Barracuda | 0.22 | 20.7 |
| Eley Wasp | 0.177 | 7.2 |
| Silhouette | 0.177 | 9.15 |
| Milbro Caledonian | 0.177 | 7.85 |
| RWS Superpoint | 0.177 | 7.9 |
| RWS Superdome | 0.177 | 8.3 |

Table 1 The pellet weight for a selection of types

PROJECT

PARTS LIST

RESISTORS (all 1/4W 5% unless otherwise stated)

| | |
|------------|------------------|
| R1,6,26,27 | 1k0 |
| R7,13 | 1k8 |
| R14-20, | |
| 22-25 | 100R |
| R21,28,45 | 4k7 |
| R29,30,40, | |
| 42,43,46 | 10k |
| R31 | 180R |
| R32,36 | 180R 1W |
| R33-35, | |
| 37-39 | 330k |
| R41,44 | 680R |
| RV1,2 | 50k horiz preset |

CAPACITORS

| | |
|-------------|-------------------------------|
| C1 | 10μ 16V axial electrolytic |
| C2,3,10,16, | |
| 17,18,19 | 10n polyester |
| C4,5,7,8, | |
| 13,14 | 100n polyester |
| C6 | 2200μ 25V radial electrolytic |
| C9 | 1n0 polyester |
| C11 | 47μ 16V radial electrolytic |
| C12 | 100μ 16V radial electrolytic |
| C15 | 220μ 25V axial electrolytic |

SEMICONDUCTORS

| | |
|--------------|--------------------------------|
| IC1 | ZN1040E |
| IC2 | 74LS04 |
| IC3 | 74LS74 |
| IC4 | 7805 |
| IC5 | 7812 |
| IC6,9 | TL084 OR TL074 quad op amp |
| IC7 | 4075B |
| IC8 | 4013B |
| Q1-7 | BC212L |
| Q8-11,13 | BC184L |
| Q12,14,15,16 | BC547 (BC107 or similar) |
| LED 1-4 | FND500 1/2in 7-segment display |
| LED 5,8,9 | Red LED |
| LED 6,7 | TIL38 infra-red LED or similar |
| D1-6 | TIL100 or similar |
| SRI | W005 |

MISCELLANEOUS

| | |
|---------|--|
| PL1 | 4-way PCB connector |
| PL2,5,6 | 2-way PCB connector |
| PL3 | 10-way PCB connector |
| PL4 | 5-way connector |
| SK1 | 4-way angled PCB connector |
| SK2 | 2-way angled PCB connector |
| SK3 | 10-way angled PCB connector |
| SK4 | 5-way PCB connector |
| SK5,6 | 2-way PCB connector |
| SW1 | 4-way DIL switch |
| SW2 | push button SPST |
| T1 | 0.12 O-12V 0.5A PCB mounting mains transformer |
| XTAL1 | 4MHz crystal |
| PCBs | Case, IC sockets, Display filter, 2in drain pipe, Cable, Nuts and bolts. |

passing the front and back sensors. To calculate the speed of the pellet or the power of the gun, some calculations must be performed.

$$\text{Velocity} = \frac{\text{distance}}{\text{time}}$$

$$= \frac{\text{counter frequency} \times \text{measured distance}}{\text{display reading}}$$

The measured distance is 6in (1/2ft) and the clock frequency is 2MHz, so:

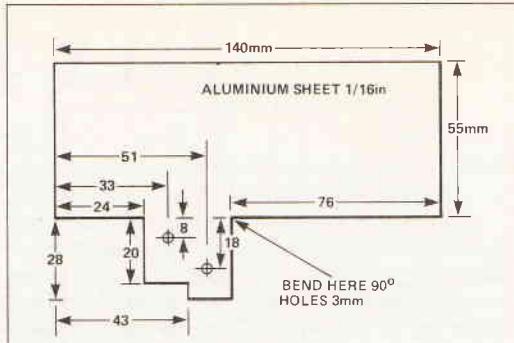


Fig. 6 The heatsink for IC4,5

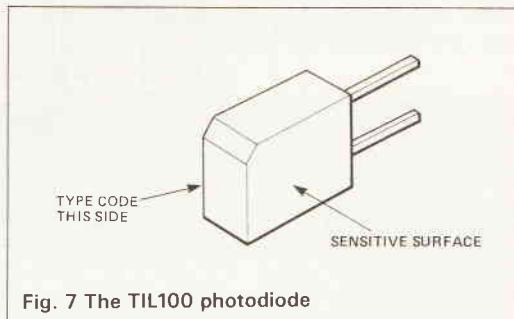


Fig. 7 The TIL100 photodiode

PELLET TYPE: ELEY WASP (7.2 grains)
READINGS: 1188, 1178, 1194, 1180,
 1177,
 1182, 1176, 1209, 1207,
 1163.

AVERAGE OF ABOVE READINGS: 1185

$$\text{VELOCITY} = \frac{1,000,000}{1185} = 843 \text{ ft/s}$$

$$\text{POWER} = \frac{843 \times 843 \times 7.2}{450240} = 11.36$$

Table 2 Typical results obtained by the author

$$\text{velocity (ft/s)} = \frac{2000000 \times \frac{1}{2}}{\text{display}}$$

$$= \frac{1000000}{\text{display}}$$


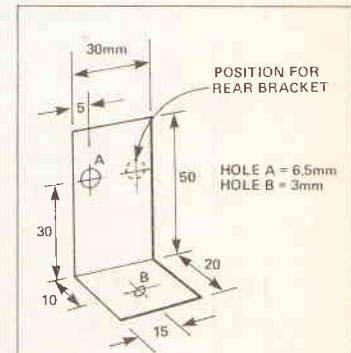


Fig. 8 The bracket to hold the sensor diodes in place (front shown)

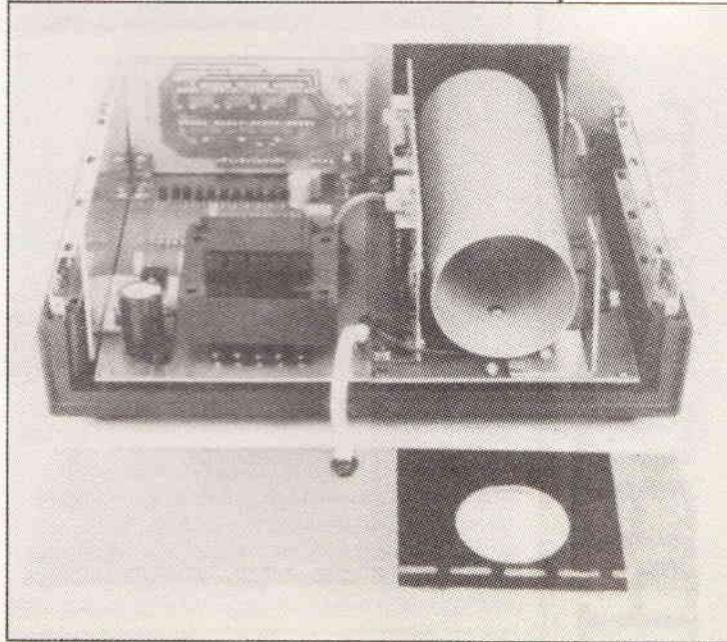

PROJECT

BUYLINES

Most of the components are readily available. Rapid Electronics (Tel: (0206) 272730), Maplin (Tel: (0702) 552911), Electromail (Tel: (0536) 204555) and Farnell (order from Trilogic on (0274) 684289) can supply the more unusual parts.

The transformer is available from Farnell as part 141-481 as are the presets. The 7-segment displays are available from Maplin (FR41U) or Rapid (57-0115). IC1 (the ZN1040E) is available from

Electromail as part 306-285. The case used for the prototype is a Retex RE3 type available from Rapid as part 30-0910.

The author is able to supply any or all parts for the Chronoscope. Send a SAE to ETI Chronoscope, 40 Victoria Avenue, East End Park, Leeds LS9 9DG for a price list. For a list of the weights of pellets, send a SAE to the same address.

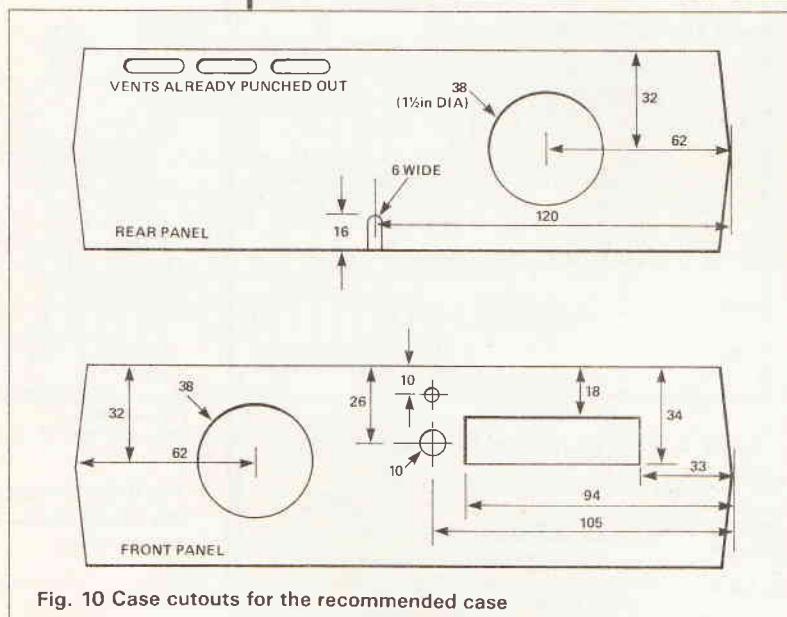
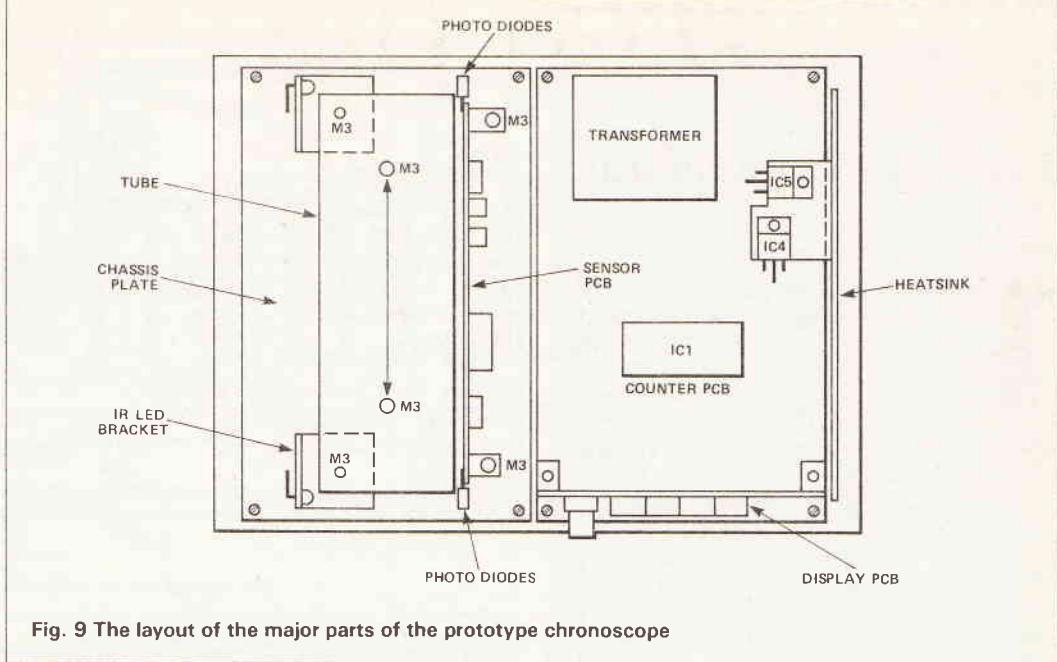


Fig. 10 Case cutouts for the recommended case


The power output of the gun can be calculated with:

$$\text{power (ftlbs)} = \frac{\text{velocity}^2 \times \text{pellet weight}}{450240}$$

The pellet weight is in grains (438 grains = 1 ounce). If you don't know the pellet weight your local airgun stockist should be able to help. Some are given in Table 1. Alternatively, the author can supply a list for common pellets (see *Buylines*).

Typical results are shown in Table 2, obtained using a BSA Mercury S 0.177 calibre air rifle. Note that the legal power limit for an air pistol is 6ftlbs and for a rifle 12ftlbs, above which you need a firearms licence.

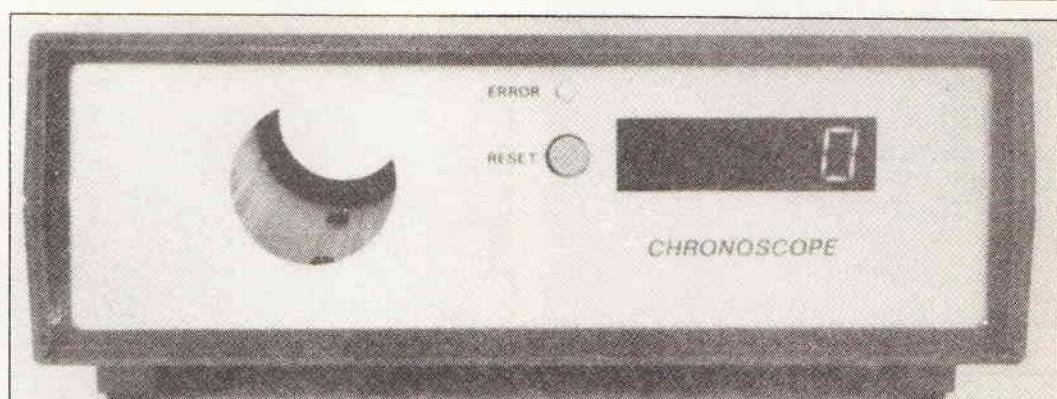To conclude, we should stress again the care that must be exercised when firing guns and rifles through the chronoscope. Always use a pellet trap of some sort.



TECH TIPS

8-way Stereo Selector

D. Ian
East Molesey


This circuit provides noiseless remote selection and routing of eight audio signals, either stereo or balanced pair mono, using simple non-locking push-switches.

The BCD counter IC2 is disabled from counting IC1's 1MHz clock rate by the wired high on pin 1. A momentary closure of SW2, say, is sufficient and the switching action is effectively

debounced. The code 0010 is now present on all the ICs so that LED 2 on IC4 is now lit and inputs A2 and B2 are connected to the outputs of IC5 and IC6.

SW8 selects BCD 1000 inhibiting the 4051s and providing an 'off' facility. ICs 5 and 6 may, of course, be remote from the selection and indicating circuitry — advantageously sited with respect to the audio signal paths.


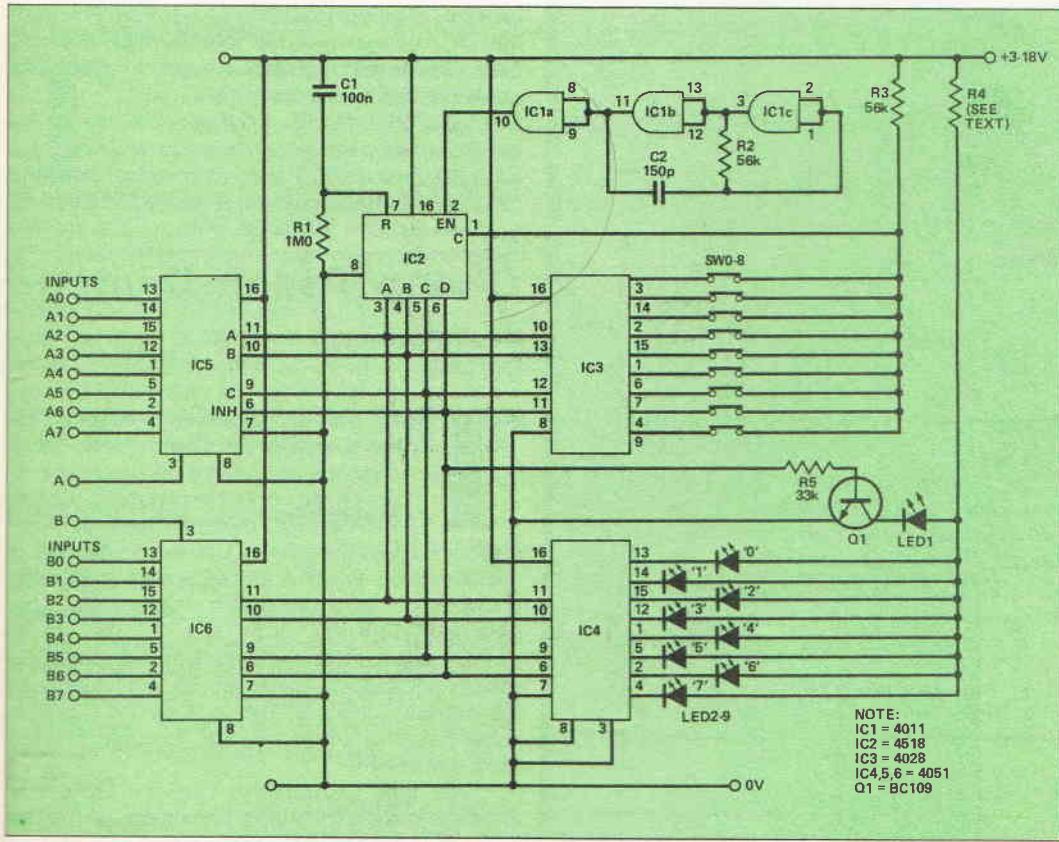
The power requirement is only about 1/2mA above that required by the LEDs. Select R3 to suit the supply voltage assuming 25mA for the LED (so 140R for 6V, 260R for 9V, 380R for 12V, 500R for 15V and so on).



Guitar Preshaper

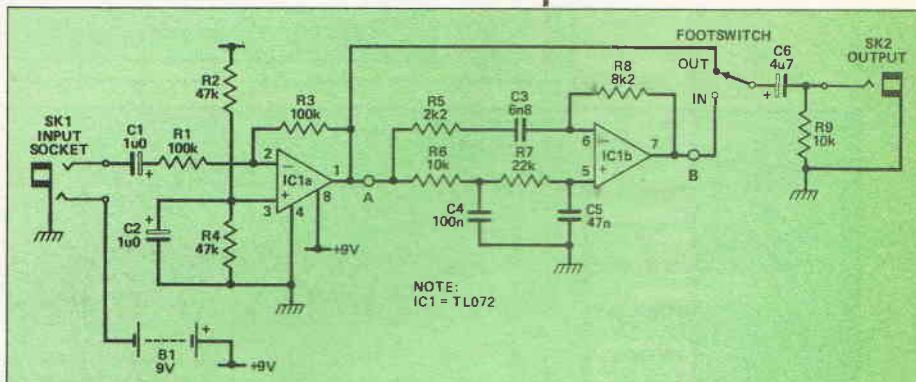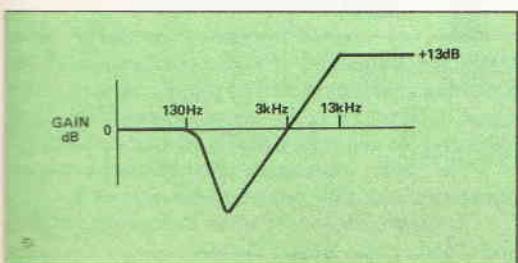I. Harvey
Hastings

Some upmarket bass and guitar amps are fitted with a preset tone circuit to give an instant clean modern sound without the tedious EQ setting. In this circuit IC1b filters high and low frequencies then recombines them to produce a frequency response approximately as shown. This produces a clean bright sound for either 6-string guitar or bass.




The circuit can be built as a footpedal powered from a PP3 (no power LED is included to extend battery life). If fitted in your amplifier between preamp and power amp then the buffering and level shifting circuitry can be omitted leaving just the components between A and B.

READERS CIRCUITS

Touch Controlled Pre-amp

A J Bird
Walsall

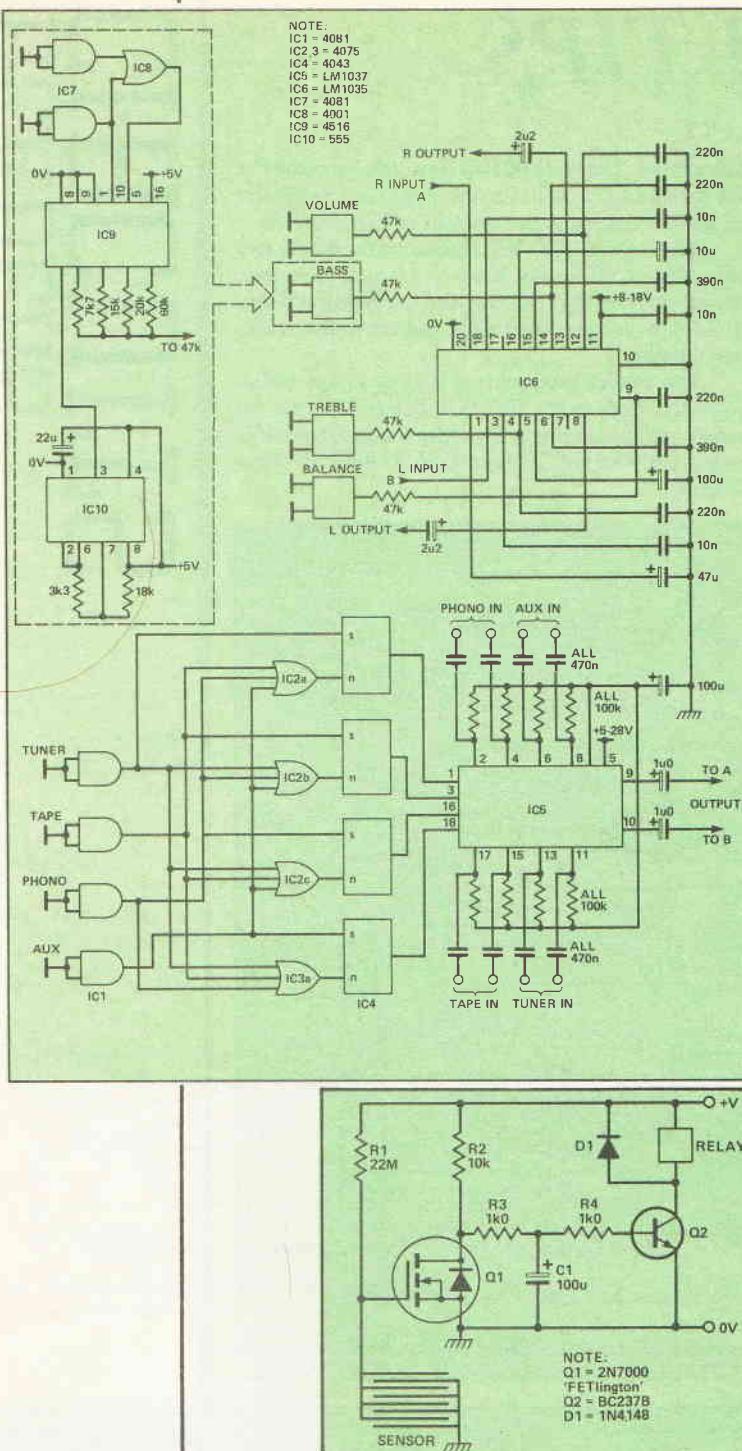

A touch controlled pre-amp with touch plate selection of inputs and volume, bass, treble and balance can be easily constructed with the help of the LM1037 and 1035 audio control ICs.

The touch plate sensors rely on the tied inputs of the AND gates (IC1, 11, 21, 31, 41) floating low and being taken high by a touch on the plate.

IC2, 3 form a latching arrangement so that each touch on an input selector plate will set the relevant flip-flops and reset the others.

The four flip-flop outputs are used to switch on a pair of inputs to IC5 through to IC6. This uses the DC voltage from the four identical volume, bass, treble and balance circuits to filter and attenuate the stereo channels.

The DC control voltage is obtained by weighting the 4-bit output from up/down counter IC13 (23, 33 and 43). The counter is clocked by the 555 timer in astable mode and enabled to count up or down by IC11 and IC12.

Cheap Touch Switch

R J Fletcher
Penzance

This circuit, originally designed as the switch of an alarm system for a disabled person, takes advantage of the high input impedance of the 2N7000 'FETlington.' The high value resistor R1 pulls the gate of Q1 to the positive rail. If the operator's finger is placed across the sensor contacts, the gate voltage falls close to zero. This switches Q1 off.

Q2 acts to invert the signal from Q1 and so the relay is normally de-energised. R3 and R4 provide the correct voltage at the base of Q2. C1 adds some delay to overcome any 'contact' bounce from the sensor.

The type of transistor used for Q2 is not critical and nor is the supply rail voltage. R1 may be reduced to 10M to reduce sensitivity. With a value of 22M it was found the switch could be activated by breathing on the sensor! For the prototype a small piece of stripboard was used for the sensor.

Low Current Siren


G Landry
South Africa

This efficient circuit provides an output of 10V RMS (approx 103dB at 1m) at a current consumption of only 30mA.

Low frequency oscillator IC1a varies the frequency of audio oscillator IC1b by switching in and out C2. The rapidly varying audio signal is gated by IC1c to output amplifier stage Q2,3 and an inverted signal is passed to Q4,5.

The piezo transducer is connected between the stages with 20V peak-to-peak across it.

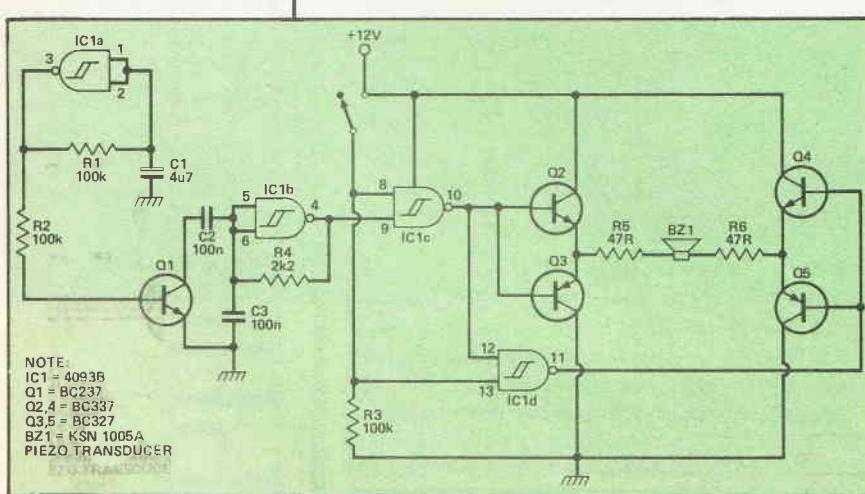Resistors R5 and R6 serve to limit the current and stabilise the output stages.



READERS CIRCUITS

Super Woofer


**Philip Day,
Ponteland, Tyne and Wear.**

This circuit enables a single centrally placed woofer to be added to a stereo system. This gives a cost effective bass enhancer which still preserves the stereo picture via the original speakers.

The right channel is driven in antiphase and the right hand speaker is reverse connected to restore the phase.

C1 and C2 as shown give a crossover at about 800Hz — other values could be tried.

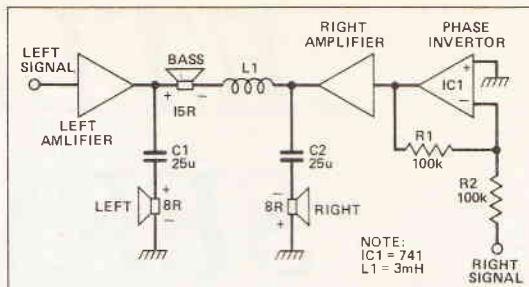The single bass speaker is bridge connected across the antiphase outputs via inductor L1. This has



the incidental advantage of cancelling out in-phase hum and vertical turntable rumble.

Note that for a system playing records only, the inverting IC circuit could be removed by reversing one half of the stereo cartridge.

removed resistors and so to the colour inputs of IC36.


The four components fit on a small piece of stripboard which can sit in the Spectrum case.

Spectral Spectrum 128

**K. D. Hedger,
Gt Yarmouth, Norfolk.**

This circuit modifies the Spectrum 128 to allow selection of any one of eight different palettes, each with eight colours. This makes full use of the 64 colours available from the Spectrum 128's video chip, the TEA2000. The palettes are selected by a simple 'OUT' instruction from either BASIC or machine code.

Inside the Spectrum 128, you will see that the three unused inputs of the TEA2000 (IC36) are tied to ground with R96, R97 and R98. With these resistors carefully removed, this circuit ORs WR, TORQ, A6, A5 and A4 together to detect an 'OUT 31' instruction. The corresponding data is latched from D5,6 and 7 onto the outputs of the enabled IC2. These outputs (R0, G0 and B0) connect to the right hand pads of the

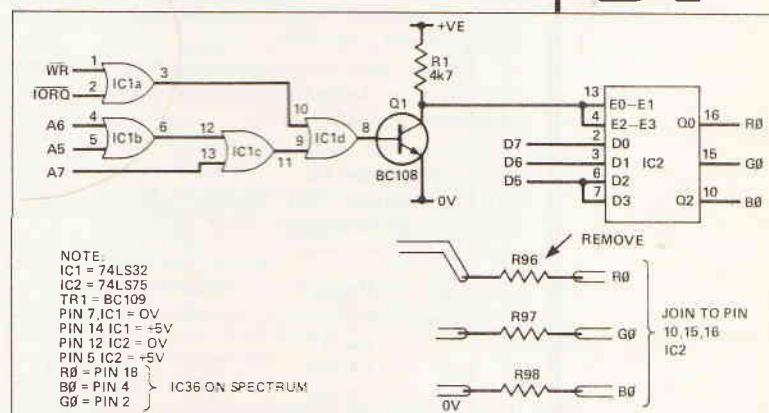

the gate goes high (at the start of a note). At a certain voltage (set by RV2), the flip-flop of IC1a,b resets and C1 discharges at a rate set by the decay pot until it reaches the voltage set by the sustain pot. When the gate is removed (note off) C1 discharges through the release pot.

RV1 sets the maximum sustain level which should be set to match the voltage controlled device. IC4 buffers the voltage across C1 for the output.


I used this circuit with a Moog Rogue with excellent results.

Envelope Generator

**T. Allgood,
Hornchurch, Essex.**

This envelope generator was designed to boost the performance of my ancient monophonic synthesizer which came equipped with only one. This way I can control either the VCA or VCF with each generator. It's a no frills ADSR generator and it's small and cheap.

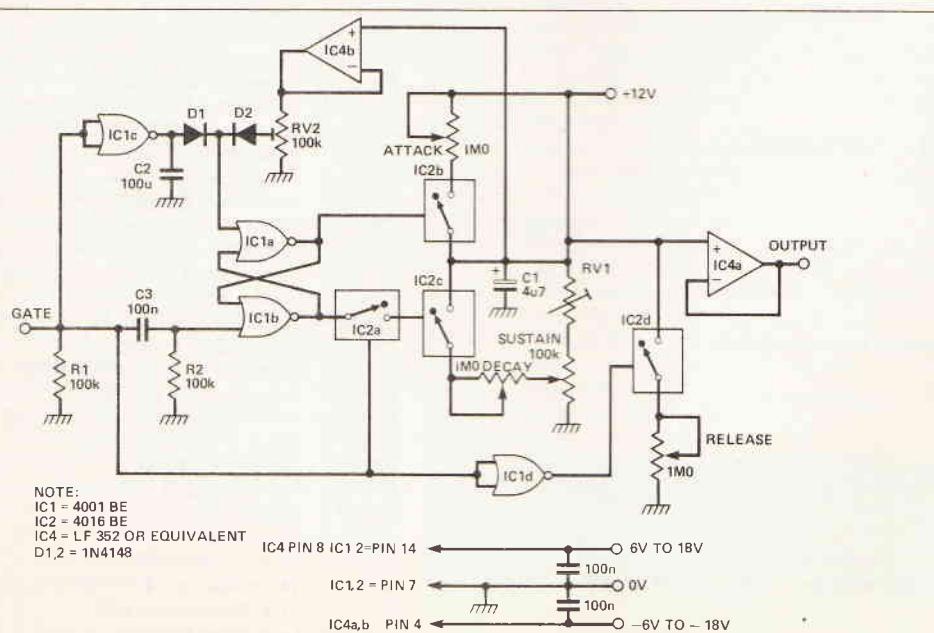C1 charges at a rate set by the attack pot when



ETI PCB SERVICE

**Miss out the mess
with ready-made
pre-drilled PCBs for
ETI projects**

Use the form (or a photocopy) for your order. Please fill out all parts of the form.

Make sure you use the board reference number. This not only identifies the board concerned but also tells you when the project was published. The first two numbers are the year of publication and the next two the month. The number after the dash indicates the particular project in that issue.

Terms are strictly payment with order. We cannot accept official orders but we can supply a pro forma invoice if required. Such orders will not be processed until payment is received.

Please make cheques out to ASP Ltd. Payment can also be made through Access and Visa cards by telephone on (0442) 41221.

Send your order to:

ETI PCB Service, ASP Readers Services, 9 Hall Road, Hemel Hempstead HP2 7BH

| Price code | Price (inc. VAT) | Price code | Price (inc. VAT) |
|------------|------------------|------------|------------------|
| C | £1.80 | N | £13.10 |
| D | £2.50 | O | £15.80 |
| E | £3.25 | P | £17.90 |
| F | £4.00 | Q | £21.80 |
| G | £4.75 | R | £23.90 |
| H | £5.50 | S | £25.90 |
| J | £6.62 | T | £29.00 |
| K | £7.20 | U | £32.20 |
| L | £8.80 | V | £35.80 |
| M | £10.60 | W | £37.90 |
| | | X | £40.70 |

Please supply:

Quantity Ref. no.

Price Code Price Total Price

Post and packing

£0.75

Total enclosed

£

Please send my PCBs to: (BLOCK CAPITALS PLEASE)

Name

Address


Postcode

ACCESS and VISA credit card orders can be taken on (0442) 41221 during office hours.


| | | |
|----------|---|---|
| E8107-1 | System A Disc Input board MC-MM | F |
| E8107-2 | System A pre-amplifier Main | K |
| E8108-1 | System A Power Amp | L |
| E8109-2 | System A PSU | F |
| E8201-2 | Infant Guard | C |
| E8202-5 | MM Stage Disc Pre-amp (Tilsbrook) | G |
| E8206-5 | Logic Lock | F |
| E8208-1 | Playmate Practice Amp (3bds) | K |
| E8212-1 | ELCB | F |
| E8301-2 | Analogue to digital conv ZX81/Spectrum) .. | E |
| E8305-3 | Dual Audio Power Supply, Linsley Hood .. | G |
| E8305-3 | Balanced Input Preamplifier | F |
| E8307-2 | Flash Trigger-sound or FR | F |
| E8308-1 | Graphic Equaliser 1/3 Oct | M |
| E8308-2 | Servo Fail-safe | C |
| E8309-1 | NICAD Charger/Regenerator | F |
| E8310-3 | Typewriter Interface — EX42 | F |
| E8311-1 | Mini Drum Synth | F |
| E8311-8 | Moving Coil Pre-amp | F |
| E8312-3 | Light Chaser EPROM Controlled (2 Bds) .. | K |
| E8402-1 | Speech Board | M |
| E8402-2 | Modular Pre-amp Disc Input Mono | F |
| E8402-3 | Modular Pre-amp Stereo Output | F |
| E8402-4 | Modular Pre-amp Relay, PSU | F |
| E8402-5 | Modular Pre-amp Tone Main Mono | F |
| E8402-6 | Modular Pre-amp Tone Filter, Stereo | F |
| E8402-7 | Modular Pre-amp Balanced Output | F |
| E8402-8 | Modular Pre-amp Headphone Amp | F |
| E8404-2 | Mains Remote control Receiver | F |
| E8405-1 | Auto Light Switch | F |
| E8405-2 | ZX81 EPROM Programmer | N |
| E8405-3 | Mains Remote Control Transmitter | H |
| E8405-4 | Centronics Interface | F |
| E8405-6 | Drum Synth | F |
| E8406-1 | Orius EPROM Board | O |
| E8406-2 | Spectrum Joystick | E |
| E8406-3 | Audio Design RIAA Stage | G |
| E8406-4 | AD Buffer/Filter/Tone | H |
| E8406-5 | AD Headphone Amp | F |
| E8406-6 | AD Preamp PSU | K |
| E8406-7 | AD Power Amp | H |
| E8406-8 | AD Power Amp PSU | J |
| E8406-9 | AD Stereo Power Meter | F |
| E8406-10 | AD Input Clamp | C |
| E8407-1 | Warlock Alarm | M |
| E8408-2 | EPROM Emulator | N |
| E8408-3 | Infra-red Alarm Transmitter | E |
| E8408-4 | Infra-red Alarm Receiver | F |
| E8409-1 | EX42 Keyboard Interface | F |
| E8409-2 | Banshee Siren Unit | F |
| E8410-1 | Echo Unit | F |
| E8410-2 | Digital Cassette Deck | N |
| E8410-3 | Disco Party Strobe | H |
| E8411-5 | Video Vandal (3 boards) | N |
| E8411-6 | Temperature Controller | D |
| E8411-7 | Mains Failure Alarm | D |
| E8411-8 | Knite Light | D |
| E8411-9 | Stage Lighting Interface | F |
| E8411-10 | Perpetual Pendulum | E |
| E8412-1 | Spectrum Centronics Interface | F |
| E8412-4 | Active-8 Protection Unit | F |
| E8412-5 | Active-8 Crossover | F |
| E8412-6 | Active-8 LF EQ | F |
| E8412-7 | Active-8 Equaliser | F |
| E8501-3 | Digital Delay (2 bds) | T |
| E8502-1 | Digital Delay Expander | N |
| E8502-2 | Data Logger | J |
| E8503-1 | Combo Preamplifier | F |
| E8503-2 | THD Meter mV & oscillator boards (2 bds) .. | K |
| E8503-3 | THD Meter Mains PSU | F |
| E8504-1 | Framestore Memory | M |

| | | | | | |
|---------|--|---|---------|---------------------------------------|---|
| E8504-3 | Framestore Control | N | E8705-5 | Budget Power Meter | E |
| E8504-4 | Buzby Meter | E | E8706-1 | Hi-fi Power Meter | N |
| E8504-5 | CCD Delay | F | E8706-2 | MIDI Keyboard CPU | U |
| E8505-5 | Stereo Simulator | F | E8706-3 | MIDI Keyboard Front Panel | O |
| E8506-1 | Audio Mixer Main | J | E8706-4 | Flame Simulator | G |
| E8506-2 | Audio Mixer PSU | F | E8707-1 | MIDI Keyboard PSU | H |
| E8506-3 | Audio Mixer RIAA | D | E8707-2 | Telephone Alarm | J |
| E8506-4 | Audio Mixer Tone Control | D | E8707-3 | Nuclear Strategy Simulator | J |
| E8506-5 | EPROM Prog MKII | O | E8708-1 | Remindalite | F |
| E8507-1 | Noise Gate | H | E8708-2 | Rear Wiper Alarm | G |
| E8508-1 | RCL Bridge | N | E8708-3 | Rev Counter | F |
| E8508-2 | EX42/BBC Interface | E | E8708-4 | Car Alarm | F |
| E8508-3 | EPROM Emulator | L | E8708-5 | Knight Raider | J |
| E8509-1 | Spectrum EPROM card | F | E8709-1 | Boiler Controller | G |
| E8509-2 | Direct Injection Box | E | E8709-2 | Amstrad Sampler (2 bds) | P |
| E8510-9 | Sunrise Light Brightener | K | E8709-3 | Portable PA | G |
| E8511-1 | MTE Waveform Generator | H | E8709-4 | EEG Monitor (2 bds) | L |
| E8511-2 | Millifaradometer | H | E8710-1 | Concept CPU board | N |
| E8511-3 | Cymbal Synth | J | E8710-2 | Concept Power board | K |
| E8511-5 | Chorus Effect | H | E8710-3 | Concept display board | G |
| E8511-7 | Enlarger Exposure Meter | F | E8710-4 | Hyper-Fuzz | F |
| E8511-8 | Switching Regulator | E | E8710-5 | Big Digits digit board | N |
| E8511-9 | Second Line of Defence | M | E8710-6 | Big Digits minute board | F |
| E8512-1 | Specdrum Connector | F | E8710-7 | Big Digits battery board | G |
| E8512-2 | MTE Pulse Generator | H | E8711-1 | Quiz Controller | E |
| E8512-3 | Specdrum | L | E8711-2 | 256K Printer Buffer | N |
| E8601-2 | Walkmate | L | E8712-1 | Heating Management System | O |
| E8601-3 | MTE Counter-timer | M | E8712-2 | SWR Meter | H |
| E8602-1 | Digibaro | O | E8712-3 | Dream Machine (free PCB) | D |
| E8603-2 | Programmable Logic Evaluation Board | H | E8801-2 | Passive IR Alarm | H |
| E8603-3 | Sound Sampler Analogue Board | R | E8801-3 | Deluxe Mains Conditioner | G |
| E8604-1 | JLLH PA PSU | H | E8801-4 | RGB Dissolve | L |
| E8604-2 | Matchbox Amplifier | C | E8802-1 | Electric Fencer | E |
| E8604-3 | Matchbox Amp Bridging Version | C | E8802-2 | Telephone Intercom | L |
| E8604-4 | MTE Analogue/Digital Probe | M | E8802-3 | Transistor Tester (2 bds) | L |
| E8605-1 | Microlight Intercom | E | E8802-4 | Spectrum Co-processor CPU | N |
| E8605-2 | Baud Rate Converter | M | E8803-1 | Co-processor RAM board | N |
| E8605-3 | Baud Rate Converter PSU Board | C | E8803-2 | Beeb-Scope (3 bds) | O |
| E8605-4 | Portable PA | H | E8803-3 | Jumping Jack Flash | E |
| E8606-1 | MIDI-CV Converter Board | H | E8804-1 | Spectrum Co-processor Interface Board | N |
| E8606-2 | MIDI-CV Converter PSU | D | E8804-2 | Combo-lock | E |
| E8606-3 | Trograph | F | E8804-3 | Kitchen Timer | E |
| E8606-4 | 80m Receiver | H | E8805-1 | Virtuoso 2U PSU | M |
| E8606-5 | Sound Sampler | R | E8805-2 | Virtuoso 3U PSU | N |
| E8607-1 | Direction | E | E8805-3 | Bicycle Speedometer | F |
| E8607-2 | Upgradeable Amp, MC stage (Stereo) | G | E8805-4 | Dynamic Noise Reduction | E |
| E8607-3 | BBC Motor Controller | F | E8806-1 | Universal digital panel meter | L |
| E8608-1 | Digital Panel Meter | G | E8806-2 | Universal bar graph panel meter | K |
| E8608-2 | Upgradeable Amp, MM stage (mono) | H | E8806-3 | Virtuoso power amp board | N |
| E8609-1 | Mains Conditioner | E | E8806-4 | Virtuoso AOT board | G |
| E8609-2 | Experimental pre-amp | F | E8806-5 | Metal detector | E |
| E8609-3 | Upgradeable amp, Tone board (mono) | H | E8806-6 | Bicycle dynamo backup | D |
| E8609-4 | Upgradeable amp, Output board (mono) | F | E8807-1 | Bar Code Lock (2 bds) | N |
| E8610-1 | Audio Analyser Filter Board | L | E8807-2 | Analogue Computer Power Board | L |
| E8610-2 | Audio Analyser Display Driver | K | E8807-3 | Bell Boy | F |
| E8610-3 | Audio Analyser Display | H | E8807-4 | Logic Probe | C |
| E8610-4 | Audio Analyser Power Supply | F | E8807-5 | Updated FM stereo decoder | J |
| E8611-1 | Audio Switcher (2 bds) | H | E8807-6 | Breath Rate display board | F |
| E8611-2 | PLL Frequency meter (4 bds) | Q | E8808-1 | Breath rate main board | H |
| E8611-3 | Upgradeable Amp PSU | J | E8808-2 | Breath rate switch board | C |
| E8611-4 | Call meter, main board | O | E8808-3 | Telephone recorder | D |
| E8611-5 | Call meter, interface board | N | E8808-4 | Analogue computer main board (2 bds) | M |
| E8612-1 | Bongo Box | J | E8808-5 | Random number display | O |
| E8612-2 | Biofeedback monitor (Free PCB) | E | E8809-1 | Spectrum EPROM Emulator | M |
| E8701-1 | RGB Converter | F | E8809-2 | Frequency meter (2 bds) | P |
| E8701-2 | Mains Controller | D | E8809-3 | Travellers' Aerial Amp | E |
| E8701-3 | Flanger | H | E8810-1 | Gerrada Marweh Bikebell | E |
| E8701-4 | Audio Selector main board | M | E8810-2 | Peak Programme Meter (2 bds) | N |
| E8701-5 | Audio Selector PSU | H | E8810-3 | Variat-Ion ioniser | K |
| E8701-6 | Tacho-Dwell | F | E8810-4 | TV-to-RGB converter | E |
| E8702-1 | Ratemeter main board | K | E8810-5 | Electron RGB buffer | C |
| E8702-2 | Ratemeter ranging board | F | E8811-1 | NiCd Charger | E |
| E8702-3 | Photo Process Controller (3 bds) | O | E8811-2 | Chronoscope (3 bds) | P |
| E8702-4 | LEDline display board (2 off) | K | E8811-3 | Digital Transistor Tester | G |
| E8702-5 | LEDline PSU and controller (2 bds) | G | | | |
| E8703-1 | Capacitometer | F | | | |
| E8703-2 | Geiger Counter | L | | | |
| E8703-3 | Credit Card Casino | E | | | |
| E8704-1 | BBC micro MIDI interface | L | | | |
| E8704-2 | ETIFaker patch box | H | | | |
| E8704-3 | 24Hr Sundial | E | | | |
| E8705-3 | MIDI Keyboard keyswitch boards (3 bds) | W | | | |
| E8705-4 | Batlite | C | | | |

PCB FOIL PATTERNS

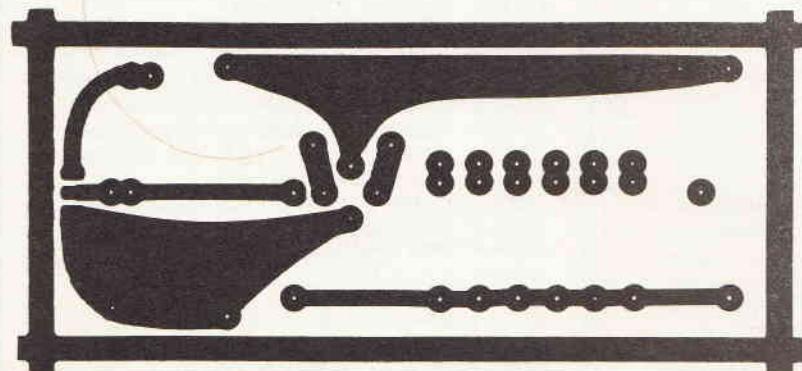


The 1st Class NiCd charger PCB

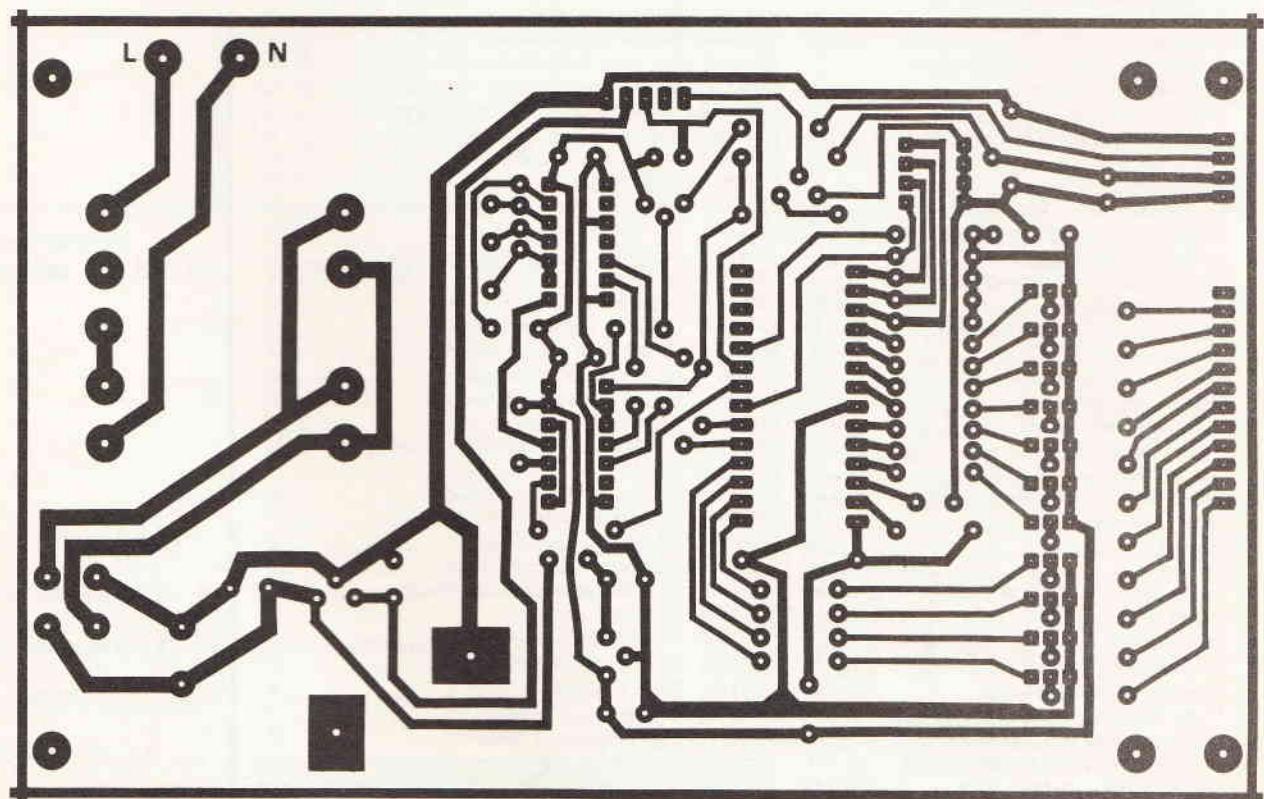



The Chronoscope counter PCB

The Digital Transistor Tester PCB

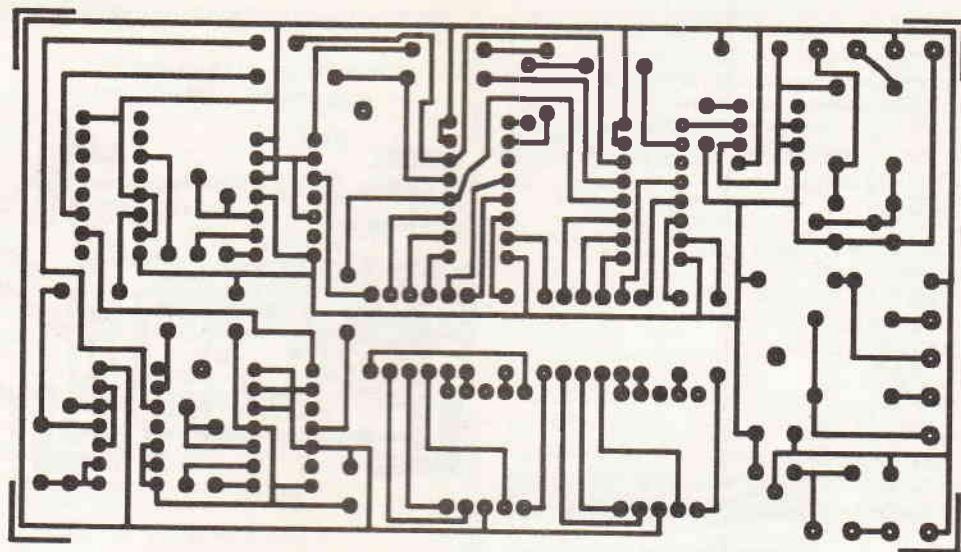


The Chronoscope display PCB

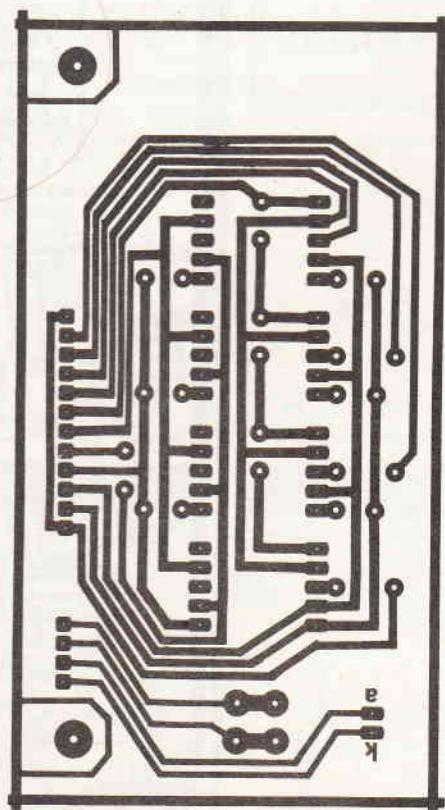

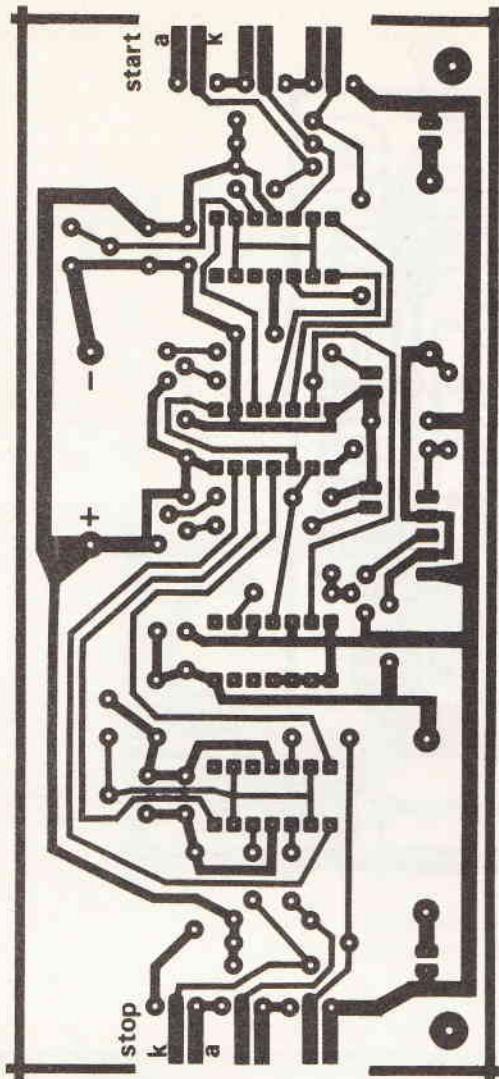

The Chronoscope sensor PCB

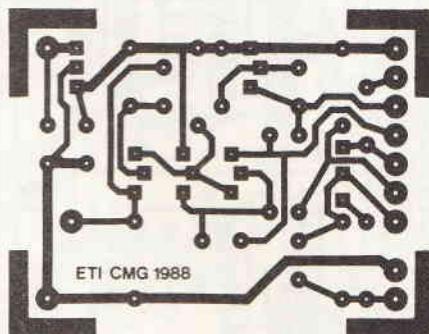

The Burglar Buster PCB --
available free with ETI next month



Dream Machine (December 1987)

The transistors used in this project are ST1702.
BC108s can be substituted.

Heating Management System

(December 1987)

A 4116 is not a suitable alternative to the 6116 specified. A 4016 RAM chip will suffice. In Fig. 1 the junction of R1/D5 should connect to D1-4/C1 and not cross. The zener diodes above the temperature sensor ICs (IC16-19) should be deleted. C4 should be 220n and not 220μ . C7-10 should be 10μ . Q2-7 should be 2N3904 and not BC3904.

RGB Auto-Dissolve (January 1988)

In Fig. 5 there are marked two D6's. The right hand one should be D5 (they are both 1N148's anyway). In the text the reference to zener diode D5 should read ZD1.

Power Conditioner (January 1988)

There is confusion between the values of R7 and R8 in the Parts List and Fig. 1. These should be: R7-27k, R8-10k and not as given in the Parts List. In addition, ZD1 is incorrectly orientated in Fig. 3. The positive terminal should be at the southern end.

Passive Infra-Red Alarm

(January 1988)

Fig. 2(a) shows the base of Q1 connected to ground and to R14. It should be connected only to R14.

Transistor Tester (February 1988)

The foil pattern for the main board was printed reversed left-right on the foil pages.

Spectrum Co-processor (March 1988)

Mogul Electronics, given in the Buylines as suppliers of the RAM chips, have moved to: Unit 11, Vestry Estate, Sevenoaks TN14 5EU. Tel: (0732) 741841.

Dynamic Noise Reduction (May 1988)


The LM1894 is no longer available from the sources listed but it can be obtained from the author. Please address orders to Manu Mehra, 88 Gleneagle Road, Streatham, London SW16 6AF.

QL Output Port (Tech Tips May 1988)

Several problems with the diagram for this one. A5 should read AS — that is, address strobe. Pins 22 and 24 should be connected to +5V and the junction of the (only) resistor and diode connected to VPA on the Q1.

OWL loudspeakers (August 1988)

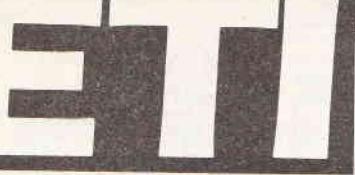Some dimensions were missing from Fig. 7. The bass driver port centre should be $3\frac{3}{4}$ in above the base of the baffle panel. The notches in the side of the tweeter cut-out are $1\frac{1}{2}$ in wide. The top plate is missing from the cutout diagram (Fig. 6). This is $7 \times 15\frac{1}{2}$ in.



ELECTRONICS TODAY INTERNATIONAL



CLASSIFIED

Heather Wust
01-437 0699 Ext 292

Send your requirements to:
Heather Wust, ETI Classified Department, ASP Ltd.,
1 Golden Square, London W1.

Lineage: 54p per word VAT inclusive (minimum 15 words)

Semi Display: (minimum 2 cms)

£12.80 per single column centimetre + VAT

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and

conditions printed on the advertisement rate card (available on request)

COMPONENTS AND EQUIPMENT

PROMs - EPROMs - PALS ANY PROGRAMMABLE IC SUPPLIED OR BLOWN

Typical prices (excluding VAT)
(Data Entry P&P extra)
2716 £4.20 2732 £3.85
2764 £2.85 2712B £4.40
BIPOLAR PROMs from £1.35
e.g. 82S123, 18S030, 74S288
PALS, PLDs etc. from £3.26
e.g. 82S153, 16L8, EP310

Full design and prototyping service.
Any quantity programmed - SAE or
phone for details.

P.L.S., 16 Central Road,
Worcester Park, Surrey, KT4 8HZ.
Phone: 01-330 6540

- Series X Mixer Kits
- up to 1000 inputs
- on-board mic input
- 6 auxiliaries
- versions for recording PA, radio, disco
- From £9.92



Send 19p for catalogue to:

K. Tek, P.O. Box 172A, Surbiton,
Surrey KT6 6HN. Tel: 01-399 3990

FREE ILLUSTRATED CATALOGUE

From Tweeters to Woofers
from Banana Plugs to TV Aerials
Microphones to Multimeters
Fast By-Return Service Visa Card accepted

STRACHAN ELECTRONICS (ETI)
9 Croall Place, Edinburgh EH7 4LT

LIGHTING EQUIPMENT FOR THEATRE, GIGS, DISCO

Professional dimmer modules from 1-50W. Multiway channel desk modules with master fader, A-B dimming & flash, 4-10 way Sequencers - sound to light - rope lights - projectors, Parcans - chasers - floods. Cables - connectors - stands - makes lighting control equipment serviced & repaired. Write or phone for info. 24hr Barlowcard phone orders. Fast return service

CUSTOM CONTROLS, 144 Warwick Road,
Upper Edmonton, London N16 1RT. 01-884 0881

TERMS & CONDITIONS

CLASSIFIED ADVERTISING TERMS & CONDITIONS

Our terms for new advertisers (semi-displays and lineage) are strictly pro-forma payments until satisfactory reference can be taken up excluding recognised advertising agencies. Cheques and PO's should be crossed and made payable to ARGUS SPECIALIST PUBLICATIONS LTD and sent together with the advertisements to:

The Classified Dept.,
No. 1 Golden Square,
London W1R 3AB.

There are no reimbursements for cancellations. Advertisements arriving late for a particular issue will be inserted in the following issue unless accompanied by instructions to the contrary. It is the responsibility of the advertiser to ensure that the first insertion of every series is published correctly, and corrections must be notified in time for the second insertion, otherwise the publishers will not accept liability or offer any reduction in charges. All advertising sales are subject to Government Regulations concerning VAT. Advertisers are responsible for complying with the various legal requirements in force e.g. The Trade Description Act, sex discrimination act & the business advertisements (disclosure) order 1977. Full Terms & Conditions of Advertising available on request.

T-SYSTEMS LTD

COMPUTER SYSTEMS AND COMPONENTS

TN 4146 diodes 3p
TN 4001 diodes 5p
TN 4005 diodes 7p
Min. toggle switch, omni 60p
Min. toggle switch, single pole, changeover 69p
Min. toggle switch, double pole, changeover 79p
Resistor, 0.25 watt, 5% E12 series 10p
LED's, 3 or 5mm, red, green or amber/yellow 20p
Resistors, 0.25 watt, 5% E12 series 25p
DIN plug or socket, 5, 6 or 7 pin 28p
25 way D plug, socket or shell 85p

* Prices include VAT, add 25p P&P if under £2. Cheques payable to T-systems Ltd. * Exclusives for ETI readers, 15% off all prices shown above for the August issue only.
61 High Street, Buntingford,
Kent BR6 0JF

* ACCESS Card series accepted on Tel: 0688 22196 *

Components
are the
biggest
selling item
in ETI so
why not
advertise
yours here?

WANTED

Turn your surplus
transistors, IC's etc., into
cash. Immediate settlement.
We also welcome the
opportunity to quote for
complete factory clearance.
Contact:

COLES HARDING & CO.
103 South Brink
Wisbech, Cambs.
ESTABLISHED OVER 10 YEARS
Tel: 0945 584188
Fax Number: 0945 588844

BOOKS

FULL WORKSHOP SERVICE MANUALS

Any Video Recorder — £10.00 + LSAE
Any Colour/Mono TV, Any Audio, Music
System — £5.00 + LSAE Amateur Radio,
Test, Vintage, Military etc.
State Make/Model/Type with order
FREE Catalogue Unique Repair and Data
Guides with all orders.

MAURITRON TECHNICAL SERVICES (ETI), 8 Cherry Tree Road, Chinnor,
Oxfordshire, OX9 4QY.

KITS

I-TRON'S TOP SELLING KITS



BUG-87 Matchbox sized surveillance transmitter — can be received by any FM/VHS radio £4.95

ROBO-VOX Instantly transforms your voice into Dalek/Robot type — also amazing sound effects possible £11.95

ROBOT CIRCULAR Unique radio controlled robot — can also be converted to control via computer. £18.95

EDU-SCOPE Build your own oscilloscope with solid state display £39.99

EDU-SCOPE CASE KIT £11.99

THERAMIN MUSIC GENERATOR An electronic device based on a legendary mystical instrument. £12.75

RAD-X CONTROL A complete ready built 2 output RADIO CONTROL SYSTEM £19.75

SUPER SOUND-FX MICROCOMPUTER An easy to use and program single chip sound effects Micro completely self contained — Incredible sound routines possible with this unit. **STAR VALUE** .. £9.95

SOUND-FX PRO CONSOLE CASE KIT £3.99

Please add £0.95 per order for P&P. For FREE Datapack on all our Products/Kits send SAE.

Cheques/Po's payable to:-

IMAGINA-TRONICS

Aberdeen House, The Street, Charlwood, Surrey RH6 0DS.

ETI Classified now accepts

ACCESS



and
VISA



Telephone Bookings
01-437 0699

or write to the
Classified Department
1 Golden Sq, W1R 3AB

VHF MICROTHERM KIT.

Tunable 88-115 MHz, 500 metre range, sensitive electret microphone, size 25mm x 20mm. Special offer: complete kit only £3.95 post free. Access orders telephone 021-411 1821 (24 hours), Cheques/POs to Quantek Electronics Ltd (Dept ETI), 45a Station Road, Northfield, Birmingham B31 3TE.

MISCELLANEOUS

HEATHKIT U.K. Spares and service centre, Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

APOINTMENTS

COMPUTER/ELECTRONIC ENGINEERING

MICRO SYSTEM MAINTENANCE LTD

MSM is a national independent third party maintenance company specialising in maintenance of microcomputers and associated peripherals.

Due to expansion we have vacancies for electronic or trainee system service engineers and bench technicians in most areas. We have our own training school to be able to start you in a very interesting career in computer servicing.

Formal qualifications are welcome but not essential. If you feel you have the experience as an amateur in electronics or computing, you could start a rewarding career with MSM.

You will need a good basic knowledge of electronics, a very keen interest in computers and a driving licence.

MSM will provide a company car, tools and an attractive employee package, with any benefits for secure employment.

Please write giving brief details of your qualifications and experience to:

Alan Welbelove (National Service Manager)

Micro System Maintenance Ltd

Unit 15

Westmead Industrial Estate

Westlea

Swindon

Wiltshire

SN5 7YS

Tel: (0793) 616888 or (01) 391 2994

SPECIAL OFFERS

FREE MEMBERSHIP TO THE

NATIONAL COMPONENT CLUB

For details and a free gift of components worth over £10 send only £1 p&p to:

Higher Ansford, Castle Cary,
Somerset BA7 7JG

CASSETTE MOTORS large and small 2 for £1.00. Mono and stereo cassette tape heads. 2 for £1.00. Microphone small for cass. tel. etc. 2 for £1.00. Telephone buzzers at £2.50 each. Please add 75p p&p no VAT. Access card accepted. Golden Orange Supplies, Brockholands Road, Woodside, Bream, Lydney, Glos. Tel: 0594 563009.

J.P.G. ELECTRONICS

Resistors 1/4w 5% carbon E12 1P 1% metal fm E243P Resistor Pack 85 different E12 valves plus ohm link, total content of resistor 1.000 £8.95 LED's Red/Green 3/5mm 6p. each Yellow 11p. each Cable Ties 75mm 1p ea. £5.95/1,000; E49 50/10,000 Power Transistors T/T 3SC, TIP36C, 100V, 25A TOP3, Plastic case £1.56 each 100dB Piezo Buzzer £1.50; Standard Buzzer £0.80 Solar Cells 0.45v 100mA £1.48; 700mA £3.50 Stepping motor 4 phase 12v 5 step 50ohms £8.95 SAA 1027 Stepping motor drive chip £3.95 Miniature FM Transistor kits 100-108MHz high quality sound ideal for cordless microphones or guitars etc £7.48 Metal Latching XLR line plug £1.35 Line Socket £1.45 Ferric Chloride pack for mixing with ½ litre water £1.40 Flux core solder 500g reel £4.95 Automatic Squeeze action wire stripper £3.45 SPECIAL OFFERS Computer grade capacitors with screw terminals 56,000 of 60v £4; 4,700 of 63v £150; 38,000 of 20v £195; 87,000 10v £150 Stereo LW/MW/FM tuner, pre-amp complete with volume/tone control and tuning scale. Brand new in makers box £5.95, Faulty £1.95. Circuit diagram, description and setting up procedure for tuner section described above 50p. LCD display 16 digit 7x5 dots £2.50 Qwerty keyboard 58 key uncased good quality switches £5 CMOS TTL 74HC 74F linear transistor kits, capacitors, resistors, tools etc. always in stock. Please add 75p +p per order VAT inc. J.P.G. ELECTRONICS, 276 Chatsworth Road, Chesterfield S40 2BH. Callers welcome. Access orders (0246) 211202

- Kits
 - Courses
 - Surveillance
 - Switches
 - Plans
 - Designs
- Market your Expertise in ETI by calling 01-437 0699**

BUSINESS OPPORTUNITIES

INVENTOR

with brilliant idea in growth market entertainment field. Needs to meet up with

ELECTRONICS BOFFIN

for further RESEARCH and DEVELOPMENT. PARTNERSHIP envisaged for suitable person with relative experience preferably in the N East area.

Write giving brief cv to
Box ETI 1
1 Golden Square,
London W1R 3AB

FOR SALE

27512 EPROMS £7 each. Toshiba TMM 27512 D-20. Full spec devices, end of production run. Quantity discounts available. Please add £1 p and p. Tel 021-377 6637, 243 Marsh Hill, Erdington, Birmingham.

Eproms ex equip all blank and tested: 2764, £1 each, £9 for 10; 2756, £2 each, £18 for 10; 200 stepper motors, 24/12 volts, £3 each. Add £1 p&p.

EXTECH, THE COMPUTER CENTRE,
53 Queens Street, Morley LS27 8DB
Tel: (0532) 537219

AMAZING GIVEAWAY . . . 40 PCE ASSORTMENT!! + Datapack, 12 full-spec transistors, ZTX500/BC212 (PNP), BC108/9 (NPN) etc, and Mullard CR25 resistor pack. **RETURN ADVERT + 50p coin (p&p)** to KIA-8, Cunliffe Rd, Ilkley LS29.

THE SCIENTIFIC WIRE COMPANY
811 Forest Road, London E17.
Telephone 01-531 1568

ENAMELLED COPPER WIRE

| SWG | 1lb | 8 oz | 4 oz | 2 oz |
|----------|-------|------|------|------|
| 8 to 34 | 3.63 | 2.09 | 1.10 | 0.88 |
| 35 to 39 | 3.82 | 2.31 | 1.27 | 0.93 |
| 40 to 43 | 6.00 | 3.20 | 2.25 | 1.61 |
| 44 to 47 | 8.67 | 5.80 | 3.49 | 2.75 |
| 48 | 15.96 | 9.58 | 6.38 | 3.69 |

SILVER PLATED COPPER WIRE

| | | | | |
|----------|-------|------|------|------|
| 14 to 30 | 10.10 | 5.20 | 2.93 | 1.97 |
| 14 to 30 | 3.97 | 2.41 | 1.39 | 0.94 |

Post Free. Please add V.A.T. at 15%.

Orders under £3.00 add 50p.

SAE for list of copper and resistance wires.

Dealer enquiries welcome.

3 HART CASSETTE Recorder Kits, fully assembled and working, plus 4 sole solenoid operated cassette front loading decks with stereo heads, never been used. Worth £275, sell for £125 ono. — Tel: 0934 513438.

SALE OF SURPLUS COMPONENTS

Top grade Electrolytic Capacitors. 22,000 mFd 80 V 22 A ripple with mounting clip £9.95 ea

Bridge Rectifiers 10A 400V £1.50 ea

25A 200V £2.50 ea

Plastic Mos-FET Power Transistors Hitachi 160V 7A 100W with full data

P-Channel 2SJ 83 £5.00 ea

N-Channel 2SK 227 £5.00 ea

or £9.50 a pair

DIL PCB relays 4K ohm coil 48V 2 C/O contacts rated 2A 99p. ea

THIS MONTH NEVER TO BE MISSED BARGAIN

Heat Sink mounting bar with 6 2SK 227 and 6 2SJ 83 Power Mos-FETs, incorporating 4 PCBs with a wealth of assorted components

£39.95 ea 2 for £69.95

Heat Sink to fit above assembly, suitable for fan cooling £5.95 ea

Ask for list of Power Transistors — S.A.E. with all enquiries please

Please allow £2.00 towards carriage on any quantity of capacitors and this month's bargain assembly. Other items allow £1.00 if goods purchased over £5.00. Otherwise Post Free.

OMICRON (B. J. McNaughton)
33 Acfold Road, Handsworth Wood
Birmingham B20 1ED

PROJECTION

AMAZING PROJECTOR turns any size television into a 7ft TV screen! Easy to assemble! £15 — quantity rates available! Box 2296 ONO.

ALARMS

NEIGHBOURHOOD WATCH BURGLAR ALARM D.I.Y. KIT

will offer a professional system at a DIY price

Ham mini beam 10, 15, 20 metres. Parts integrated circuits, transistors, diodes, valves, resistors, etc.

Service Manual and parts for Spectrum and Amstrad
Send a 8" x 5" SAE for list.

M.J. SEAWARD

(Mail Order)
Dept. (ET), St. Olaf's Road,
Stratton, Nr. Bude, Cornwall.
Telephone: 0288 4892

PLANS AND DESIGNS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue. SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on

REF: ETI/6/88

06267 79398

NAME _____

- Telecomms Tech C&G 271
- Radio Amateur Licence C&G
- Micro-processor
- Introduction to Television

**Radio & Telecommunications Correspondence School,
12, Moor View Drive, Teignmouth, Devon. TQ14 9UN.**

MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

| | |
|---|---|
| Electronics | <input type="checkbox"/> Radio, Audio and TV Servicing |
| Basic Electronic Engineering (City & Guilds) | <input type="checkbox"/> Radio Amateur Licence Exam (City & Guilds) |
| Electrical Engineering | <input type="checkbox"/> Car Mechanics |
| Electrical Contracting/Installation | <input type="checkbox"/> Computer Programming |
| GCE over 40 'O' and 'A' level subjects | |

Name _____
Address _____ P. Code _____
International Correspondence Schools, 312/314 High St., Sutton, Surrey SM1 1PR.
Tel: 01-643 9568 or 041-221 2926 (24 hrs.) Dept EBS58

REFRIGERATION

REFRIGERATION

Fridges, Fridge-freezers and Washing Machines Stocks available, manufacturer guarantees returns (well-known manufacturers).

Please contact Steve on
Rhyl (0745) 343277/343816
Fax: 0745 343038 or write to

C.E.S.

14 Edward Henry Street
Rhyl, Clywdd, N. Wales

CALIBRATION

CALIBRATION

Need not cost a fortune. For a free quote on your D.M.M., oscilloscope or frequency counter. Send type of instrument, make and model details to:

**3 1/2 DIGIT Calibration Service,
D.M.M.
FROM £5 Blarharrow Limited,
(Calibrator Brookside Cottage,
to BS7570) Main Road, Brightstone,
I.O.W. PO30 4DJ**

Send stamped addressed envelope for your free catalogue to:
**172 Caledonian Road,
London N1 0SG.**

Telephone 01-278-1768 VISA
Trade Enquiries Welcome

**TO ADVERTISE IN ETI MAGAZINE
TELPHONE HEATHER WUST ON 01-437 0626**

GOVERNMENT SURPLUS EQUIPMENT

ANCHOR SURPLUS LTD.

The Cattlemarket, Nottingham NG2 3GY Tel 0602 864902
The UK's Largest Genuine Government Surplus Dealer

Always a large stock of Radio, Test, Service and General Equipment in stock. Pye, Racal, Marconi, Tek Redifon, Plessey, Mullard.



Special: Eddystone 730/4 1-30MHz RX £75 - £110. Pye PF2 LB FM from £25. **Phone Rob (G4ROB) For Details.**

Mail Order, Access/Visa Welcome

PCB'S

QUALITY PRINTED CIRCUITS

- ★ Established 15 years ★
- ★ Single or double sided boards ★
- ★ Plated through hole boards ★
- ★ Personal service ★

PAYNE ELECTROPRINT LTD
Marcus Road, Dunkeswell
Nr Honiton, Devon EX14 0RA
Tel: Sales 040 489 646/664

HAVE your electronic ideas become a reality. Let Highland Itec develop and manufacture your circuits at a low cost for prototype and small production runs with comprehensive documentation which includes: Silk screen layouts, photo-artworks, pad-masters, solder-masks, bill of parts. Manufacture includes: Sizes up to 300 x 200mm single or double-sided. Finish: Roller-tinned and drilled. For more details Tel: (0463) 226505 or Fax (0463) 226505

PCB Manufacturers
Which to Choose See Page 15

Labcenter
electronics

PC-B £80

See review in Elektor magazine
At last, an affordable PCB design tool for your Amstrad PC.

Plotting service available.

Send SAE for further details,
or £2 for demo disk.

Labcenter Electronics
**14 Marriner's Drive,
Bradford, BD9 4JT.**
Tel: 0274 542868

SURVEILLANCE

ESKAN ELECTRONICS

LEADING MANUFACTURERS
AND SUPPLIERS OF
SURVEILLANCE AND
SECURITY EQUIPMENT.

MINIATURE TRANSMITTERS,
TELEPHONE MONITORING
EQUIPMENT, AND MANY
OTHERS.

Send stamped addressed
envelope for your free
catalogue to:
**172 Caledonian Road,
London N1 0SG.**

Telephone 01-278-1768 VISA
Trade Enquiries Welcome

Omicron 2

The practical surveillance solution £17.95 inc p&p

- Ideal eavesdropper or baby monitor
- Less than 1/2 matchbox size
- Absolutely shockproof housing
- Built-in sensitive microphone
- Battery life 72 hrs (Alkaline)
- Full 12 month warranty

Simply clip Omicron 2 to battery and hide — no adjustments, no fiddling, no fuss. Hear every sound perfectly on an ordinary FM radio up to 1/4 mile away. This must be the easiest to use, best value surveillance device available.


No quibble 14 day money back guarantee

TRADE MILLEA ELECTRONICS
ENQUIRIES 470-472 LEYMOOR ROAD,
WELCOME HD7 4QF. Tel: (0484) 460003

SWITCHES

VOICE/SOUND ACTIVATED SWITCHES easy to follow diagrams and uses only £1.00. Components and P.C.B.'s available. Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.

BRITISH MUSIC FAIR REPORT

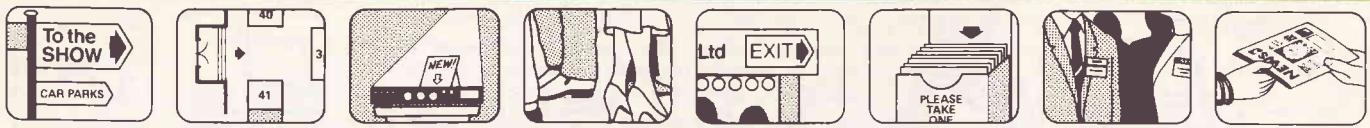

Who played at Wembley this year? Apart from the mega-gigs that have been so prominent in the news over the summer, some 120 exhibitors were also at the Wembley Conference Centre to show off their latest wares in this year's British Music Fair. All the big names in musical instruments were there as well as most of the lesser known companies, although it was not always easy to find who you were looking for, big or small, as the conference centre has a rather confusing layout.

What this venue does have is around 6,700 square feet of air-conditioned exhibition space which allowed a less cluttered layout thus avoiding some of the claustrophobic scenes from last year at Olympia.

Who's Got What?

Let's start with the big boys shall we? Yamaha had a wealth of new products to show from all the divisions. At the pro end of the market we have two new synths designed to make FM synthesis easy for all — the YS200 and the cut-down 8-track sequencer-less YS100. Both are multi-timbral and feature 5-octave touch sensitive keyboard, pitch and modulation wheels and a control panel that looks like a Crazy Golf course. £790 for the 200, £700 for the 100.

From the portable keyboard wing comes the PSS-680 (below) — a 5-octave mini keyboard complete with pitch bend wheel, eight drum pads and MIDI capabilities all for just £250. Also into this category comes five expander boxes to enhance the sound of porta-keyboards that have come in for some stick in the past. The EMQ-1 Sequencer (£299), the EMT-1 and EMT-10 voice expanders (£220 and £300 respectively), the EMR-1 Drumbox (£220) and the EME-1 Reverb unit (£220).

Obviously Yamaha see the portable market as one to get serious about.

I'll Be Blown!

By contrast, Casio seem to be taking the pro market by storm with products like the DH-100 Digital Horn (see photo) which allows wind instru-

mentists access to all the electronic sound he wants for just £99.

Following on from the success of their DG-20 MIDI Guitar Casio have now launched the PG-380 which, if the demos on the stand were anything to go by, gives the most demanding of guitarists an armada of sounds (up to 192) tracked perfectly.

What's nice is that the sounds and ROM cards are compatible with another new product from Casio, this time the keyboardist (just in case you were all feeling left out). The VZ-1 flagship synth certainly leaves a keyboard player with no complaints as far as performance controls and options go. The sounds aren't bad either. Furthermore, for the master keyboard devotee, you can buy the VZ-1 in rack mounted format as the VZ10-M.

Back In LA

Roland's main push on their stand was behind the E-20 and the E-10 keyboards which seem to be straddling two markets. This idea seems to be that these two keyboards will give pro musicians the benefit of all the little tricks that portable keyboard owners have enjoyed all these years. So now you can have the combination of the sounds of a D-20 synth without the programmability but with some rather clever auto accompaniment routines which can be stored in the on-board sequencer and dumped onto RAM card for long-term storage.

I can see what they're getting at because a lot of musicians would like to work out songs and arrangements at home but don't want the hassle of turning a room into a small studio.

Also of interest was the T-110 sampled sound module which won't record sound samples but plays ROM cards of ready-made samples which are available thanks to the S-10 series. As the majority of sampler users just play with presets anyway this would sound like a good investment to a musician at around £600.

What A Combination

This is the first year the UK has seen any evidence of the Yamaha acquisition of Korg. The new catalogue

proves interesting reading with the launch of Korg's Professional Performance series spearheaded by the M1 MIDI Workstation — a full spec master keyboard multi-timbral sampler, digital effects processor and eight track sequencer for around £2000. To add to your sound library, Korg also has two sound modules with specific tasks. The P3 is a sampled piano module with two types of piano onboard (titled Piano 1 and 2!) however it will accept ROM cards as well. Symphony is the other expander from Korg and it has several internal orchestral type sounds and, once again access to that Korg ROM Library.

Street Cred Kawai


It's only in the last two years that Kawai have gained the credibility it needed in the pro market. This year it has done it once again with the K1 synth and the keyboardless K1m expander. Although without the sequencing frills of its rivals it is certainly the most easily programmed and usable as an expander for someone who wants performance control and a bit more than presets.

Akai — Hard To Beat?

Not a whole heap new at the Akai stable. There's the S1000 top of the range sampler which features 16-bit stereo sampling and a 2Mb memory for £2899. For rhythmists the ME35T Drum Pad to MIDI interface was being thrashed by some prospective customers — price nearly £260. To complement this the XE8 drum expander for £500, gives any MIDI instrument a further eight 16-bit sampled drum voices which can be changed via cartridges (wot! No ROM card?).

Akai launched one of the first master keyboards — the MX 73 which is still popular today. However, they have wisely decided not to sit on their laurels and have come up with the MX76 which has an extra three keys on the keyboard, is weighted and has both velocity sensitivity and after-touch along with four programmable sliders which could, for example, be used to control tempo, portamento rate, volume and so on via MIDI.

Akai also had a rather unusual use for low cost sampling technology. Instead of shoving it into a mini keyboard and putting kids off sampling for life, they have put it into the U4 phase trainer. This is a sort of sampler cum pitch shifter which allows you to sample a riff and slow it down without altering the pitch. It could be useful for a musician who needs to practice a riff as he can slow it down to learning speed and keep repeating it, speeding up as he gets better. The audio bandwidth is none too hot, so serious

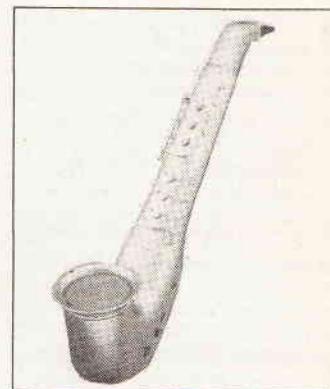

musical applications are out. DJs, Rappers and Housemasters may find them useful for effects.

Typically Tropical

Cheetah gets the prize for the most tropical stand at the show with the sounds of the jungle sound effect record, the astro turf presumably nicked from the local greengrocer and of course the inflatable gorilla. Not a lot new, though — just what's been advertised for the last five months.

Sound Effects

Sound Technology, the UK distributor for Alesis effects and analogue synth masters Oberheim had new things for both at the show.

Alesis had two new additions to its Micro effect series which are the Micro EQ and the Micro Cue Amp, both £125. Planned for the Autumn is the sequel to the excellent Midiverb and the Midiverb 2, the Quadraverb with 100 programmable effects which can be chained together in fours which will get over the problem that most multi-effect units have.


From Oberheim comes the Matrix 1000, a sound expander with 1000 presets on it. The unit is six voice but no mention is given to it being multi-timbral. Nevertheless £450 is still good value for that many options.

Additional Highlights

Having trotted round the big names you may well be forgiven for thinking that that's all that there was of interest. Nothing could be further from the truth.

The Farfisa stand was showing the Midimic — an audio-to-MIDI converter which not only receives a mono sound source from the in-built microphone but also has a line level input for non-MIDI instruments such as guitars, saxophones or even old keyboards. From the demo I received the tracking is excellent and at £200 means anyone who can even whistle a decent tune can now get into professional music.

Darrin Williamson

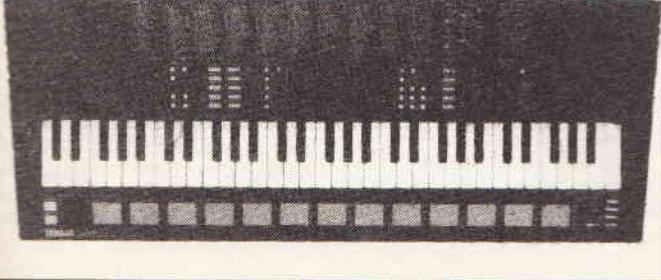


OPEN CHANNEL



The potential UK videotex market is huge. There are, after all, well over 50 million of us living on these fair isles and if even only a tenth of this potential is tapped, there's many a fortune to be made.

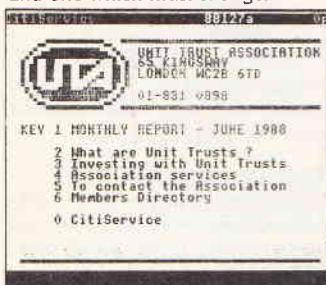Yet the present state-of-the-art here in Britain is ridiculously small. Only a few hundred thousand terminals are in use and the aim of the services appears to be primarily towards the business sector. I would strongly suggest this is a short-sighted attitude and one which must change.



The Prestel service is hardly a service at all. At the risk of being contradicted (I would dearly love to be, if anyone can tell me otherwise) cost is basically prohibitive to all but the keenest of private users and uses of the service are limited such that it is hardly worth the bother, anyway.

This is a preposterous situation. We have, potentially, an extremely good system — on its initiation back in 1979 (yes, nearly ten years ago) it was the best of its kind and should have been constantly developed to remain so through the years. British Telecom, back in the days of the Post Office, thought it would increase telephone revenue and were at that stage reasonably happy to put funds into it.

However, once developed, Prestel was (and still is) allowed to rot and so now falls at about the bottom of the pile compared with other systems. Where Prestel's task was to increase the public's use of the telephone system (it didn't, and still doesn't) other later systems such as France's Minitel have taken videotex to new heights with every year of their use.

The British problem is one of sheer mis-management and poor marketing. Where UK users have to fork out our hard-earned pennies (well, hundreds of pounds, actually) to buy a terminal or buy software to convert a computer into a terminal, the French equivalent of BT (France Telecom) gives the damned terminals away to interested users at the rate of one million terminals a year! France Telecom expects to give everyone a terminal by the end of the century.

Further, whereas we have Prestel and its limited existing uses, France's Minitel is based around an electronic adaptation of the telephone directory.

Instead of looking in a paper directory or phoning Directory Enquiries (that is if you can actually reach Directory Enquiries) French users merely use their free terminals. This electronic directory automatically ensures the terminals will be adequately used and will even pay for themselves given time.


Apart from a few technical details (Minitel is a much easier-to-use system than Prestel — it's menu-based rather than the difficult page-based Prestel) other services remain similar — electronic shopping, travel agencies and so on, although a number of new services have arisen due to Minitel's wider acceptance by the public.

Incidentally, just in case you're a bit suspicious about whether the terminals can pay for themselves, France Telecom estimates each terminal given away pays for itself in the extra revenue generated, *within a year!*

Minitel presently generates some 70 million calls a month, which translates to some 84 million hours connected to the service and that means a lot of money — more even than I get paid by ETI for writing this column! Only around 3.5 million terminals have yet been given away, too. The final figure, when everybody has a terminal, will make BT executives' faces (and, I suspect, those of the Government) go positively green with envy.

Not Cricket

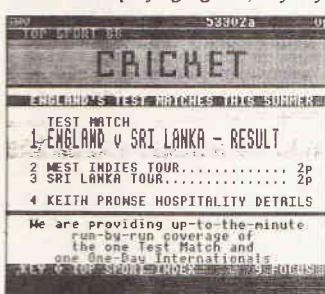Now come on! Can't we take a lesson from all of this? What are we thinking about? I know it's not cricket, but who said we were playing a game, anyway!




We who invented the hovercraft, the jet engine, the computer (there must be others but for the life of me I can't think of any more, offhand) can't even seem to get our act together on this one. Yes, I know the Prestel system doesn't lend itself to the same sort of things that Minitel can do but what the heck!

If Prestel's no good scrap it and let's do it right. We've got ten years experience (give or take a few months) of how our system doesn't work and isn't much good.

Now, let's do it right.

Keith Brindley

PLAYBACK

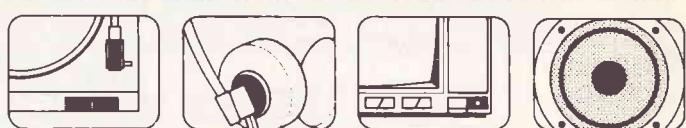

Even in today's hi-tech world there remains plenty of scope for the hi-fi hobbyist to improve his system by paying meticulous attention to detail. Indeed, there is many a way in which systems may be 'tweaked' — all in the name of enhancing the musical experience!

Over the years such techniques as tightening-up cartridge bolts, employing rigid and spiked loudspeaker stands and using good quality interconnection end speaker cables have evolved into a thoroughly logical upgrading process.

However, acting as a foil to these perfectly sensible 'tweaks' there exists a stubborn fringe element insisting on employing quite ludicrous methods to improve audio performance.

One of the silliest ideas to emerge in recent years involves sticking little black squares of metallised polyester over everything in sight. Now, in some cases this process might effect a change in the sound of a system though whether such differences are actually improvements has as much to do with the placebo effect as rational science.

I shall return to this subject at a later date but for now I would like to highlight a particularly illogical and potentially damaging 'tweak' that has surfaced in the hi-fi arena.

This latest concept concerns the use of shorting plugs to load the coaxial digital outputs of the more up-to-date CD players. Apparently by terminating the output in this fashion, the overall sound quality of the CD player is said to be improved. Daft but true.

The tentative rationale for this improvement is thought to be that the plug somehow stops electricity from leaking out the hole!

Most manufacturers employ transistor-transistor logic (TTL) to drive this digital output either via a resistive pad or transformer that isolates the digital and analogue ground lines. Now, whether this digital output is shorted or open circuit there will always be a degree of mistermiation that results in signal reflection, so perhaps these outputs are best loaded with plugs that match the universal output impedance of 75R.

According to the Red Book standard, the peak voltage of a digital output should be set to 0.5V with a master clock frequency of 5.65MHz, a signal that will be injected directly into the earth line if a shorting plug (loaded or unloaded) is employed.

As you might expect from TTL, stages could be permanently damaged by this inappropriate loading. In the case of a shorting plug this peak voltage could realise a current of up to 6.66mA which will

itself set up voltages across common earth lines due to small series inductances.

Of course, this effect will depend very much on the layout of the PCB but with interference set up between digital and analogue earths it is not difficult to imagine jitter effects being exacerbated.

In addition, a greater demand will be placed on the integral power supply as more current is drawn just as fairly significant RF (5.6MHz) magnetic fields may also be developed. The subjective consequences of RF interference are becoming more widely appreciated by the more sane elements of the hi-fi industry and it is likely that this situation will snowball once we enter the 'RF conscious' European Market.




Early research work indicates that down-band products of very high-order difference intermodulation may be responsible for certain grainy and coarse high frequency colourations observed during critical listening tests. Certainly my own experiences of a vast number of CD players point to them sounding worse once the digital output is shorted — a logical conclusion considering the added stress this imposes on the player.

Other enthusiasts, unaware of the electronic consequences of their actions, may expect a change in sound quality and this 'difference' may inadvertently be interpreted as an improvement. I am quite sure that if CD players were manufactured with shorting plugs in place then the fringe element would currently be proposing their removal ...


The ideal situation is presented by those up-market players which enable the user to switch the TTL output on or off when required. Nevertheless, if the presence of localised RF fields is undesirable from the subjective point of view then an unterminated digital output is likely to be preferable to one that is shorted. I now wait with baited breath for someone to suggest we short out any redundant analogue outputs as a way of improving sound quality!

Paul Miller

BLUEPRINT

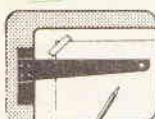

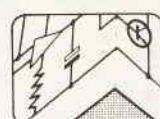This column is a service to readers to provide electronic designs to order. Many a project never gets further than the drawing board because of difficulties with one small part. If you are stuck for a circuit or a technique, let the ETI expert help you out. Send your requirements, with as much detail as possible, to ETI Blueprint, 1 Golden Square, W1R 3AB.



The request for a Blueprint design this month comes from Herbert Jones of Hove, Sussex.

I would like to build an integrating current meter which, linked to a solar cell, would give a reading of average daylight intensity over a period. I have seen a paper describing a device which integrates current by plating metal from one electrode to another. The electrodes have to be weighed to obtain a measurement. A digital readout would be much more useful.

There is a practical way to make a digital integrating meter. The most versatile solution would be to use a microprocessor but this would take far too much time to write the program in machine code. Also, many people do not have EPROM programmers. The circuit in Fig. 1 uses 4000 series CMOS to achieve the aim and uses so little current that a battery can be used to power it.

The system shown here uses a voltage controlled oscillator (VCO) to convert an analogue signal to a frequency. The clock pulses from the VCO are counted and the total is displayed when required.

The Circuit

A solar cell converts light into electricity by means of incident photons giving up their energy to an electron on an individual basis. That is to say, the energy of the electron freed from the atom depends on the energy of the photon which it has absorbed. Silicon solar cells have certain bands of possible energy levels for 'bound' and 'free' electrons and they can only absorb photons having an energy corresponding to a jump between levels in the requisite bands. This means the voltage generated by a solar cell depends on the energy band structure of the cell, rather than on the incident light (assuming the incident light includes photons of the right energy range).

Although the electron energy is not a good indication of the incident light level, the short circuit current is a


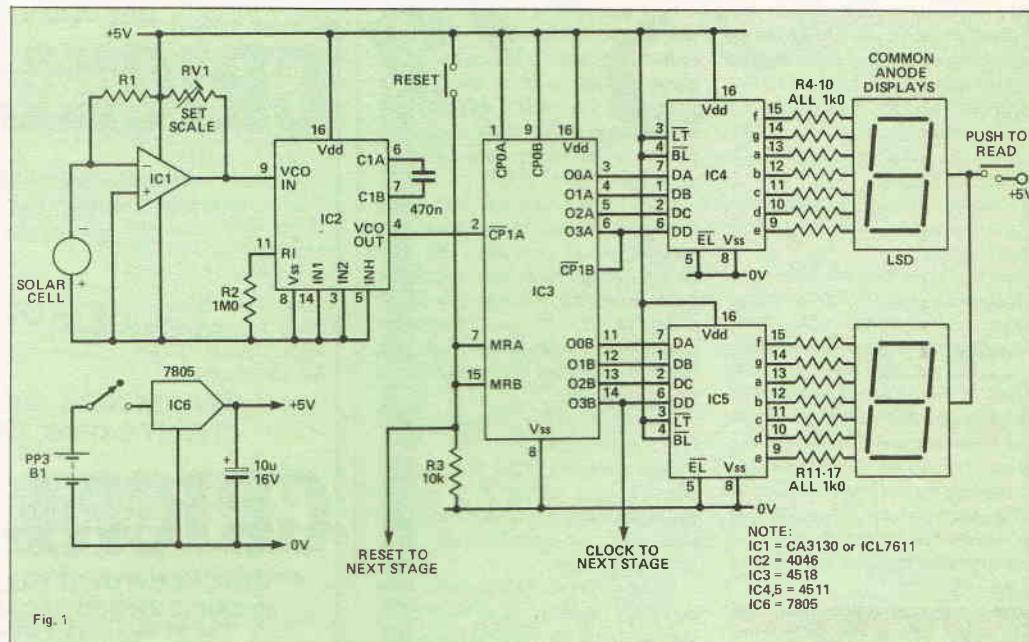


Fig. 1

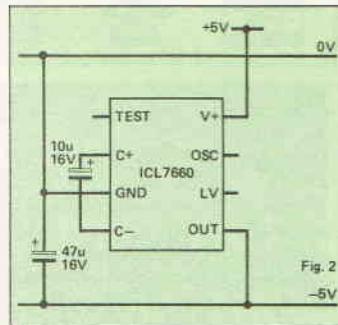

reasonable indication. This is because the number of electrons raised to the conduction band depends on the number of photons in the right energy range which fall on the cell. This correspondence is not perfect because the cell will have defects but it is very good.

In The Right Light

To make use of this characteristic of solar cells, the cell is connected to a current-to-voltage transducer. In this circuit, so long as the op-amp is not overloaded, feedback keeps the voltage across the cell almost at zero. The current from the cell all flows in R1 and RV1, so the voltage output of the current-to-voltage transducer can be calculated by Ohm's Law if you know the current output from the cell.

All this only works if the cell is connected the right way round. If it is not, the output of the op-amp will remain stubbornly at 0V, trying but not succeeding to reach a negative potential.

The output from the current to voltage transducer feeds the VCO control input of a 4046 phase locked loop IC. The frequency of the VCO is proportional to the control voltage. A slight error will be introduced here because the relationship is not perfectly linear but the error is only small.

Out For The Count

The VCO output is fed to a dual decade counter and from the first decade counter to as many cascaded stages of counting as may be required to count the total number of pulses from the VCO.

The counter outputs are fed to BCD-to-seven segment decoder/drivers and thence to 7-segment displays. If a long series of counters is to be used, it may be unnecessary to use displays and drivers on the least significant digits.

For many purposes, adequate resolution would be provided by using displays on the four most significant digits (assuming that measurements in the same range are needed). More displays on less significant digits would, however, display a useful reading with shorter measurement periods. The displays have been shown with a push-to-read switch to minimise battery consumption.

Other Applications

Clearly, the integrating meter part of the circuit can be used to integrate any analogue voltage measurement having a range of approximately 0-4V. With the circuit shown, the limitation on converting some types of signal source to suitable range is the lack of a negative power supply.

Fig. 2 shows a suitable means of generating a negative power supply, and Fig. 3 shows a temperature measuring circuit which uses the negative supply. As an alternative, the more complicated circuit shown in Fig. 4 does not need a negative supply to measure temperature.

Both of these circuits are assumed to be Celsius reading. The temperature sensors provide a Kelvin scaled output but this is unlikely to be of use to determine the difference between a warm day and a cool one.

Andrew Armstrong

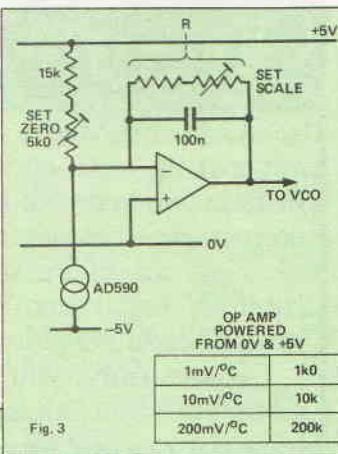


Fig. 3
OP AMP POWERED FROM 0V & +5V

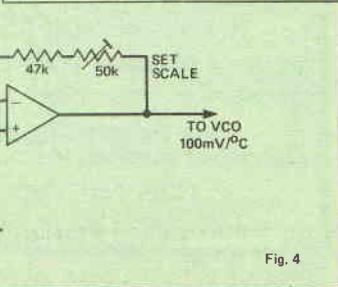


Fig. 4

ONCE OVER



The welcome associated with the glow of a home must be as old as are glowing homes. In the days when the glow was caused by the roaring hearth there was not a lot you could do to automate the glow so it would be there on your return and not wasting fuel all day.

Come the advent of electricity (and more importantly, electronics) and things changed.

Now it is quite possible to have a light at your doorstep which comes on to greet you or visitors only when someone approaches and only when the sun has set. You can't go much further in the way of automated welcomes and there can't be a much more economic solution either.

It is just such a unit that Maplin has been selling for a while now. Called the *Nite Sentry* on the box and simply the *Outdoor PIR* in Maplin's catalogue it has the order number XG96E and a price of £39.95.

The catalogue name gives the game away. This is yet another ingenious application of the passive infra-red detector idea based on a pyro-electric sensor.

The *Nite Sentry* is mains powered and connects up just like any outside light. It is similar in many ways to the passive infra-red alarm project of the ETI January 1988 issue.

Body heat from the visitor is collected by way of a special Fresnel type lens onto a concave mirror where it is focused onto the pyro-electric sensor. The mirror angle can be easily altered to change the height of the detection area over a range of about 15°.

The sensor responds to changes in radiated infra-red heat received. The Fresnel lens creates a pattern of detection zones so as a visitor crosses the area covered by the unit, he will move into and out of the array of sensitive zones, triggering the unit.

So it is much like any passive infrared alarm. In this case, however, rather than connect the unit up to an alarm system (such as the Burglar Buster!) it connects a built-in light socket (up to 100W) to the mains and powers an auxiliary output too for extra lights (up to 600W).

Once triggered, the light stays on for a preset period from about ten seconds to 15 minutes. The *Nite Sentry* even includes a photosensitive cell to disable the unit during the hours of daylight. The photocell is sensibly mounted on the underside of the unit to receive ambient light only and not direct sunlight.


The whole thing — detector and lamp — is encased in a slightly weird cream coloured ABS box with a pearly light cover. It is entirely waterproof and easily mounted on a wall with the mains cable entry through the rear.

Once on the wall it looks rather like a 1960's attempt at bringing the carriage lamp up to date! However, it is not too obtrusive and certainly warrants a position on the wall.

The sensor is rated with a range of a quarter circle 10m in radius. Once up over the front door, the effective range seemed to be nearer 5m but as most front gardens are about this length and passing cars can trigger the detector, this reduction in range is probably a good thing.

Otherwise the unit performed perfectly. It is easy to install. An add-on angled mount is provided if necessary and even a sticker for the photocell is included so the unit can be tested in the daylight. It takes only about 15 minutes to put up, it means you'll never have to leave the light on again and even acts as a mild deterrent to unwelcome visitors. What more can you ask for £40?

Malcolm Brown

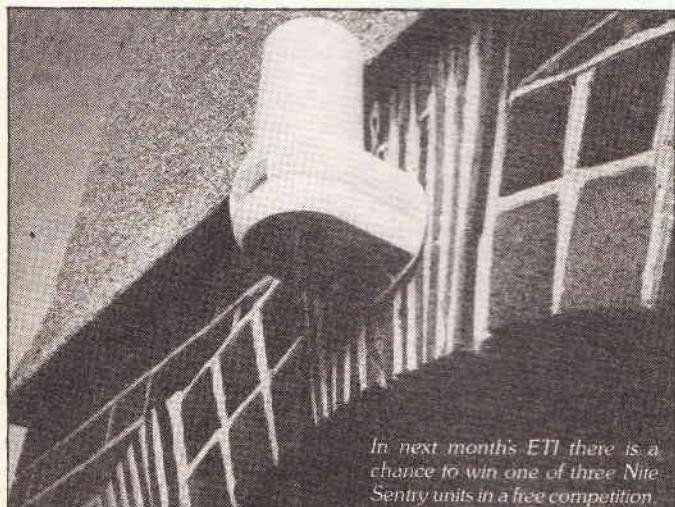

In next month's ETI there is a chance to win one of three *Nite Sentry* units in a free competition.

CRICKLEWOOD ELECTRONICS

SUFFERING FROM COMPONENT DEFICIENCY?

Symptoms: Frustrated, half-built projects, sleepless nights, non-working equipment, out of stock blues.

SEE YOUR SPECIALIST!

CRICKLEWOOD

ELECTRONICS LTD
The components stock centre —
the fast solution to component problems,
old, new, rare and common

SERVICE IS OUR OBSESSION

MAIL ORDERS, TELEPHONE ORDERS,
CREDIT CARDS, CALLERS WELCOME

CRICKLEWOOD

ELECTRONICS LTD
CRICKLEWOOD ELECTRONICS LIMITED
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
Tel: 01 450 0995 & 01 452 0161 Telex: 914977



It's easy
to complain about
an advertisement.
Once you know how.

One of the ways we keep a check on the advertising that appears in the press, on posters and in the cinema is by responding to consumers' complaints.

Any complaint sent to us is considered carefully and, if there's a case to answer, a full investigation is made.

If you think you've got good reason to complain about an advertisement, send off for a copy of our free leaflet.

It will tell you all you need to know to help us process your complaint as quickly as possible.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 1 Brook House,
Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

**Introducing
Digital Audio:
CD, DAT and sampling**

Ian R. Sinclair

112 pages • 216 x 138mm
55 line drawings • £5.95 + 50p p&p
ISBN: 1 870775 05 8

The techniques of digital audio involve methods and circuits that are totally alien to the technician or enthusiast who has previously worked with audio circuits. This book bridges the gap of understanding and explains the principles and methods of digital audio but the mathematics and theory are avoided.

Digital electronics and signals. Analogue to digital conversion. Digital to analogue conversion. Studio digital methods. The CD system. Consumer digital tape systems, S-DAT and R-DAT. Sound synthesis.



**Practical Digital
Electronics
Handbook**

Mike Tooley

January 1988 • 208 pages
216 x 138mm • 100 line drawings
£6.95 + 50p p&p ISBN: 1 870775 00 7

*'A very useful book'
Elektor magazine*

A practical introduction to digital electronics for enthusiasts, technicians and students.

Digital circuits. Logic gates. Bistables and timers. Microprocessors. Memory and input/output devices. RS-232C interface. IEEE-488 and IEEE-1000 microprocessor buses. The oscilloscope.

Full constructional details for nine test gear projects. TTL and CMOS pinouts; binary conversion tables.

Please send me

copy(ies) of **Introducing Digital Audio** (£6.45 each)

cop(ies) of **Practical Digital Electronics Handbook** (£7.45 each)

I enclose my cheque for _____ made payable to PC Publishing.

Name _____

Address _____

Send this coupon to PC Publishing,
139-141 High Street, Edenbridge, Kent TN8 5AX

OSCILLOSCOPES

| | |
|---|------|
| TELEQUIPMENT D83 Dual Trace 50 MHz Delay Sweep. | £350 |
| Large Tube with manual | £350 |
| COSSOR OSCILLOSCOPE CDU150. Dual Trace 35MHz Delay Sweep. Dual State Portable 8x10cm Display. With Manual | £180 |
| NOW ONLY £180 each | |
| Optional Front Protection Cover Containing 2 Probes & Viewing Hood | £10 |
| S.E. LABS SM111 Dual Trace 18MHz Solid State. Portable AC or external DC operation 8x10cm display with Manual | £150 |
| GOULD/ADVANCE OS255 Dual Trace 15MHz with Manual | £225 |
| TELEQUIPMENT D43 Dual Trace 15MHz. With Manual | £100 |
| ADVANCE CS250TV. Dual Trace 10MHz. With Manual | £150 |
| SCOPEX 4D10A Dual Trace 10MHz. With Manual | £150 |
| TELEQUIPMENT S54A Single Trace 10MHz. Solid State with Manual | £90 |

MULTIMETERS

| | |
|---|----------|
| AVO 8 Complete with Batteries & Leads | from £50 |
| AVO 8 Mk V Complete with Batteries & Leads | £90 |
| AVO TEST SET No 1 (Military version of AVO 8. Complete with Batteries & Leads) | £100 |
| TEST LEADS suitable for AVOMETERS. Red & Black with two croc clips & prods (p&p £3) | £5 |
| BLACK EVER READY CASES for AVOS. Unused (p&p £4) | £20 |

| | |
|---|---------------|
| MARCONI AF Power Meter TF893A 20Hz-35kHz. 20W-10W. With Manual (p&p £7) | only £35 |
| MARCONI RF Power Meter TF1152A - DC-500MHz. 0.5 to 25 watts 50ohm. With Manual (p&p £7) | only £45 |
| MARCONI ATTENUATOR TF2162 DC-1MHz 600ohm. 0-11dB on 0.1dB Steps (p&p £7) | £35 |
| HATFIELD ATTENUATOR DC-250MHz. 50ohm 0-100dB (p&p £4) | £60 |
| ADVANCE SG62B AM 150kHz-220MHz | £45 |
| LAGGEAR Colour Bar Generator KG1. 8 Test Patterns (p&p £4) | only £40 each |


STEPPING MOTORS

| | |
|---|---------|
| Type 1 200 Steps per rev. 4 Phase (5 wire) 12 24V Torque 25oz inch will run on 5V with reduced torque | £15.00 |
| Type 2 612 Steps per rev. 3 Phase 12/24V (will work on 5V) | £7.50 |
| Type 3 NORTH AMERICAN PHILIPS 24 Steps per rev. 4 wire 5V 3.3Amps 0.250rmp 0.200 P.P.S | £6 each |
| Type 4 200 Steps per rev. 120V (3 wire) Torque 25oz inch | £4 each |
| Type 7 WARNER 24 Steps per rev. 3 Phase (6 wire) 28V. Holding torque 45oz. inch | £5 each |

Used equipment — with 30 days guarantee. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone or Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.

STEWART OF READING

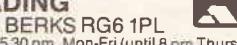110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 0734 68041. Fax: 0734 351696. Callers welcome 9 am-5.30 pm. Mon-Fri (until 8 pm Thurs)



SPECIAL OFFER at ONLY £300 each

TELEQUIPMENT D755 (NATO approved version of D75). Dual Trace. Delay Sweep. 50MHz.

TRIO RF SIGNAL GENERATOR type SG402 100KHz-30MHz. Unused (p&p £7).

COLOUR PAR GENERATOR type PAL MC-101. 8 patterns. Pocket Size. Rechargeable batteries. Complete with Battery Charger/Mains Adaptor. Unused (p&p £4).

COLOUR PAR GENERATOR type PAL MC321. 8 patterns. Video/Sound Output. Unused (p&p £7).

AVO TRANSISTOR ANALYSER MK2 (CT446) Suit case style. Complete with batteries & operating instructions only £25 each (p&p £7)

AVO VALVE TESTER CT160 Suitcase style. 22 Bases only £25 each (p&p £7)

ISOLATING TRANSFORMERS 240V Input

240V Out 500VA ... £15 (p&p £5) 100VA ... £6 (p&p £3)

240V Out 200VA ... £4 (p&p £4)

DISK DRIVE PSU 240V IN 5V 1.6V & 12V 1.5A out Size W125mm H75mm. D180mm. Cased Unused only £10 (p&p £3)

QWERTY KEYBOARD (as in LYNX MICRO) just to make Cased ... £5 each (p&p £3)

FARNELL SWITCHED MODE PSU 5V 40A +/-12.5A £30 each (p&p £4)

OTHER SWITCHED MODE PSU available. Please enquire.

DISKDRIVES 5 1/4" Double Sided. Double Density. 80 track From £50

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 604. Dual Trace 60MHz. Delay Sweep. Component Tester + 2 Probes.

£575

HAMEG OSCILLOSCOPE 2036. Dual Trace 20MHz. Component Tester & 2 Probes

£314

All Other Models Available

BLACK STAR FREQUENCY COUNTERS P&P £4

Meteor 100-100MHz ... £99

Meteor 600-600MHz ... £126

Meteor 1000-1GHz ... £175

BLACK STAR JUPITER 500 FUNCTION GENERATOR

Sine/Square/Triangle 0.1Hz-500KHz £4 ... £110

BLACK STAR ORION. PAL TV/VIDEO COLOUR PATTERN GENERATOR

£199

HUNG CHANG DMM 7030. 3 1/2 digit. Hand held 28 ranges

including 10 Amp AC/DC 0.1%. Complete with batteries & leads. p&p £4

As above DMM 6010. 0.25% ... £39.50

Carrying Case for above ... £33.50

£3

OSCILLOSCOPES PROBES Switched x1:x10 p&p £311

PHOTO-COPIES

ETI has been published for over 15 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers and supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

PCB foil patterns (where published) and any errata are included with all photocopies as applicable.

Please supply photocopies of the following articles from ETI (complete in block capitals):

Month Year Page (if known)

Title

Month Year Page (if known)

Title

Month Year Page (if known)

Title

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:

ETI Photocopy Service

9 Hall Road

Hemel Hempstead

Herts. HP2 7BH




FAME



&

FORTUNE

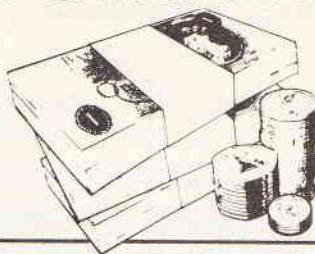

That's what an incredibly small number of people have achieved by contributing articles to ETI. The rest of us have had to make do with total obscurity and enough money for a couple of pints. Nevertheless it's all worthwhile and we need your contributions now!

FEATURES

If you know what you're talking about and it hasn't all been said before, we want you to add to our wide ranging and informative features. If you have a great idea for a feature or two, send in a brief resumé. If you don't have the ideas but you think you have a commanding knowledge of a suitable subject area we want to hear from you too.

Whatever you can contribute to ETI, take the plunge now. We can offer a modicum of fame and a very reasonable fortune.

PROJECTS

ETI has built its reputation on novel, worthwhile projects well designed and accurately presented. If you have recently designed and built a world-beater we want to hear from you. In the first instance send us a brief description of your masterpiece along with a circuit diagram.

Write in to:
The Editor
ETI
1 Golden Square
London W1R 3AB

ADVERTISERS INDEX

| | |
|----------------------------------|-----|
| BICC VERO | 17 |
| BK ELECTRONICS | IFC |
| CRICKLEWOOD ELECTRONICS | 64 |
| DISPLAY ELECTRONICS | 28 |
| FIELD ELECTRONICS | 34 |
| GRATTONS | IBC |
| GREENBANK ELECTRONICS | 3 |
| HART ELECTRONICS | 25 |
| HENRY'S AUDIO ELECTRONICS | 34 |
| MALIN ELECTRONICS | OBC |
| OMNI ELECTRONICS | 3 |
| PC PUBLISHING | 65 |
| SAGE AUDIO | 3 |
| SLEE ELECTRONICS | 20 |
| SPECIALIST SEMICON DEVICES | 42 |
| STEWARTS OF READING | 64 |
| SUMA DESIGNS | 3 |
| TJA DEVELOPMENT | 3 |
| TK ELECTRONICS | 10 |
| STAN WILLETS | 22 |
| WILMSLOW AUDIO ELECTRONICS | 66 |



CONSTRUCTOR SERIES SPEAKER KITS

Based on the famous Kef Reference Series, these three DIY designs give the home constructor the opportunity to own an upmarket pair of loudspeakers at a very down-to-earth price!

With a Wilmslow Audio Total Kit it's easy — no electronic

or woodworking skill is necessary. Each kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly), speaker drive units, crossover networks, wadding, grille fabric, terminals, nuts, bolts etc.

Model CS1 is based on the Reference 101, CS3 is equivalent to the Ref. 103.2 and CS9 is based on the Reference 105.2 (but in a conventionally styled enc.).

CS1 £117 pair inc. VAT plus carriage £6
CS3 £143 pair inc. VAT plus carriage £12
CS9 £393 pair inc. VAT plus carriage £18

We also offer a kit (less cabinet) for Elector PL301


Lightning service on telephoned credit card orders!

WILMSLOW AUDIO LTD.

35/39 Church Street, Wilmslow, Cheshire SK9 1AS Tel: 0625 529599

Call and see us for a great deal on HiFi.
(Closed all day Mondays)

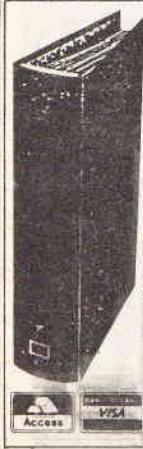DIY Speaker catalogue £1.50 post free (export \$6)



BINDERS

FOR YOUR VALUABLE COLLECTION
OF ELECTRONICS TODAY
INTERNATIONAL MAGAZINES

• SMART • EASY TO USE • TOP QUALITY
To ASP Readers Services, PO Box 35,
Wolsey House, Wolsey Road, Hemel
Hempstead, Herts HP2 4SS (0442-41221)

£5.95
inc.
P&P

Please supply ... Electronics Today International
Binders £5.95 inc. P&P

Total £ (Please make cheques payable to ASP Ltd.)


Years Required — 198.....198.....198.....198.....

Name
Address

Please allow 21 days for delivery



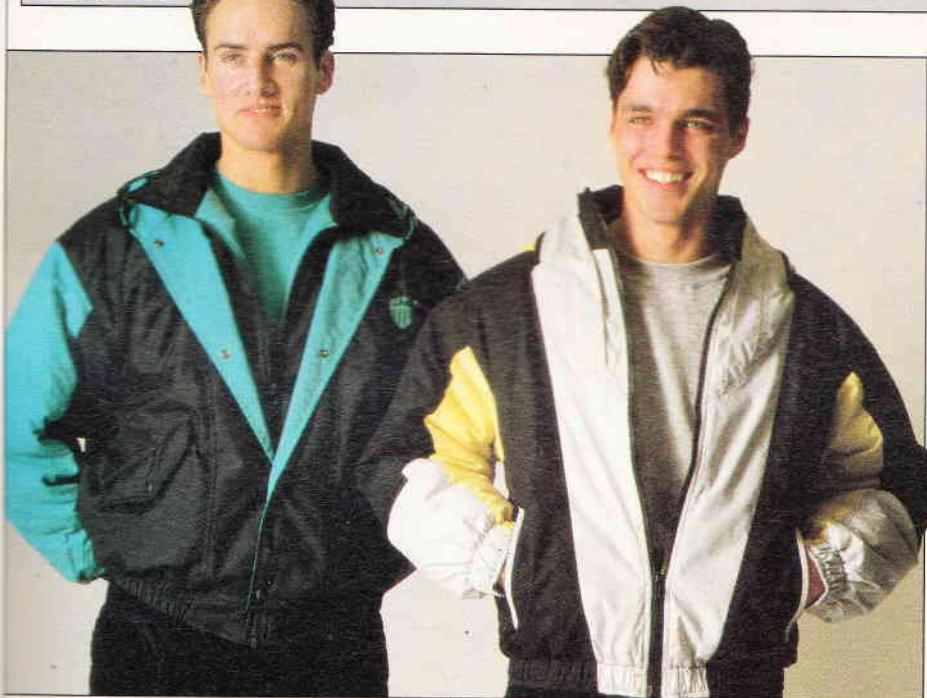A LOT OF STYLE FOR A LOT LESS FROM ARGUS AND GRATAN



Casual Jackets

£32.99 EACH

More than just good-looking, these colourful padded jackets are also very practical.

Both are made from easy-care polyester/cotton fabric and come in a choice of colourways.

Look at the jackets then look at the price and you'll realise that this is one garment you can't afford to be without.



1 Padded jacket with draw string hood, collar and two flap pockets. Front zip and stud fastening.
Polyester 65%, cotton 35%. Available in Blue/Navy and Jade/Black.
Chest sizes: 34/36, 38/40, 42/44 ins.

2 Padded jacket with concealed hood, zip fastening and two slant side pockets.
Polyester 65%, cotton 35%. Available in Grey/Black/Burgundy and Grey/Black/Yellow. Chest sizes: 34/36, 38/40, 42/44 ins.



Telephone orders
direct on 0274 521126
Credit card holders please phone your
order quoting ref: U0015

MOON Phase Watches

£49.99 EACH RECOMMENDED PRICE £99.99

All watches tell the time. Many give the date. But here's one which also tells the phase of the moon.

The Zeon Lunar Moon Phase Watch has a precision quartz movement, three hands, a date display PLUS a fascinating moving skyscape which corresponds to the sky and phase of the moon on any particular night.

These beautiful looking and intriguing watches are water resistant to 100 feet and come in ladies' and gents' styles, complete with a Burgundy leather strap.

The recommended price is £99.99 but we're offering them for an incredible £49.99 each so you can save £50.

Now that's real style.



**HALF
PRICE**

E X C L U S I V E O F F E R H O W T O O R D E R

Send to: Grattan Response,
("Argus Offer"), Admail 79,
Leeds LS1 1XE.

| Please send me | Code | Size | Price | Qty | Total Value of Order |
|--------------------------|------------|------|--------|-----|----------------------|
| Blue/Navy Jacket | 50G273 HB3 | | £32.99 | | |
| Jade/Black Jacket | 50K274 HB3 | | £32.99 | | |
| Grey/Black/Burg. Jacket | 50C105 HB3 | | £32.99 | | |
| Grey/Black/Yellow Jacket | 50H106 HB3 | | £32.99 | | |
| Ladies Moon Phase Watch | 76H902 HB3 | | £49.99 | | |
| Gents Moon Phase Watch | 76T905 HB3 | | £49.99 | | |

Enclose cheque/postal order payable to
GRATTAN RESPONSE ("Argus Offer") or
please debit my Credit Card

p&p £1.50
GRAND TOTAL

Access VISA
Card No.

U0015

Expiry Date Month Year
Signature Date

Name


Address

Postcode

Grattan plc, Anchor House,
Ingleby Road, Bradford BD99 2XG.
Reg. No. 249001 England.
Delivery subject to availability.

THE NEW MAPLIN CATALOGUE IT'S OUT OF THIS WORLD

SEND FOR YOUR COPY TODAY

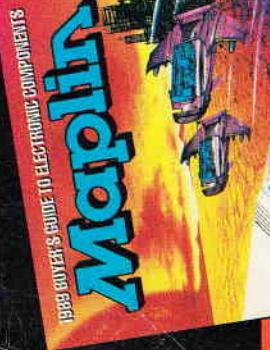

FREE

24 hr
Delivery
Facsimile
Computer
Video
Car Stereo
Mobile
Telecommunications

Thousands of new products at super low prices.
Hundreds of over 500 pages packed with data.

ORDER
OF YOUR COPY
CATALOGUE ON SALE SOON

Pick up a copy from any W.H. Smith for just £1.95 or post this coupon now to receive your copy by post for just £1.95 + 50p p & p. If you live outside the U.K. send £3.40 or 15 International Reply Coupons. Enclose £2.45.

Post Code

ET1 89



Address

AVAILABLE FROM 11th NOVEMBER 1988 IN ALL W.H. SMITH STORES

Send to Maplin Electronics, P.O. Box 3, Rayleigh, Essex SS6 8LR.

11th Nov 88

1988

1988

1988

1988

198