

EI
ELECTRONICS
TODAY INTERNATIONAL

OCTOBER 1989 £1.50

THE ELECTRONICS, SCIENCE & TECHNOLOGY MONTHLY

UNDER SURVEILLANCE

The Inside Story

PROJECT MIDDIMAP
Music Data Manipulation

PROJECT MULTIMETER
Beginners' Test Gear

PROJECT INTRUDERBEAM
Infra-red Alert System

TESTING TEST GEAR
Major New Series

WIN!

John Linsley Hood 80W MOSFET Amplifier Kit

ISSN 0142-7229
9 770142 722009 10

OVP POWER AMPLIFIER MODULES-TURNTABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OVP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OVP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B. and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OVP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. **PRICE £33.99 + £3.00 P&P.**

NEW SERIES II MOS-FET MODULES



OVP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. **PRICE £39.99 + £3.00 P&P.**



OVP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 155 x 100mm. **PRICE £62.99 + £3.50 P&P.**



OVP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 175 x 100mm. **PRICE £79.99 + £4.50 P&P.**

NOTE:— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD — INPUT SENS. 500mV BAND WIDTH 100KHz PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) — INPUT SENS. 775mV BAND WIDTH 50KHz ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 + 50p P&P.**

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE:— INSTRUMENTS, P.A., DISCO, ETC.

ALL MCKENZIE UNITS 8 OHMS IMPEDENCE

- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID., DISCO. RES. FREQ. 80Hz FREQ. RESP. TO 14KHz SENS. 99dB **PRICE £28.59 + £2.00 P&P.**
- 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 70Hz FREQ. RESP. TO 6KHz SENS. 100dB **PRICE £34.70 + £2.50 P&P.**
- 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID. RES. FREQ. 45Hz FREQ. RESP. TO 7KHz SENS. 103dB **PRICE £47.48 + £2.50 P&P.**
- 12" 100 WATT C12100CP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES. FREQ. 45Hz FREQ. RESP. TO 7KHz SENS. 98dB **PRICE £36.66 + £3.50 P&P.**
- 12" 100 WATT C12100TC TWIN CONE) HIGH POWER WIDE RESPONSE, P.A. VOICE, DISCO. RES. FREQ. 45Hz FREQ. RESP. TO 14KHz SENS. 100dB **PRICE £37.63 + £3.50 P&P.**
- 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES. FREQ. 40Hz FREQ. RESP. TO 7KHz SENS. 100dB **PRICE £64.17 + £3.50 P&P.**
- 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES. FREQ. 45Hz FREQ. RESP. TO 5KHz SENS. 100dB **PRICE £85.79 + £3.50 P&P.**
- 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES. FREQ. 40Hz FREQ. RESP. TO 5KHz SENS. 98dB **PRICE £53.70 + £4.00 P&P.**
- 15" 200 WATT C15200BS VERY HIGH POWER BASS RES. FREQ. 40Hz FREQ. RESP. TO 4KHz SENS. 99dB **PRICE £73.26 + £4.00 P&P.**
- 15" 250 WATT C15250BS VERY HIGH POWER BASS RES. FREQ. 40Hz FREQ. RESP. TO 4KHz SENS. 99dB **PRICE £80.53 + £4.50 P&P.**
- 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 40Hz FREQ. RESP. TO 4KHz SENS. 102dB **PRICE £94.12 + £4.50 P&P.**
- 18" 400 WATT C18404BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 27Hz FREQ. RESP. TO 3KHz SENS. 99dB **PRICE £167.85 + £5.00 P&P.**

EARBENDERS:— HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS EXCEPT EB8-50 AND EB10-50 DUAL 4 AND 8 OHM. BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND
- 8" 50 WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz FREQ. RESP. TO 7KHz SENS. 97dB **PRICE £8.90 + £2.00 P&P.**
- 10" 50 WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz FREQ. RESP. TO 5KHz SENS. 99dB **PRICE £12.00 + £2.50 P&P.**
- 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz FREQ. RESP. TO 3KHz SENS. 96dB **PRICE £27.50 + £3.50 P&P.**
- 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. RES. FREQ. 28Hz FREQ. RESP. TO 3KHz SENS. 92dB **PRICE £21.00 + £3.50 P&P.**
- 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz FREQ. RESP. TO 3KHz SENS. 93dB **PRICE £32.00 + £3.50 P&P.**
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 5 1/2" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz FREQ. RESP. TO 20KHz SENS. 92dB **PRICE £9.99 + £1.50 P&P.**
- 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz FREQ. RESP. TO 20KHz SENS. 94dB **PRICE £10.99 + £1.50 P&P.**
- 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz FREQ. RESP. TO 18KHz SENS. 89dB **PRICE £12.99 + £1.50 P&P.**
- 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 35Hz FREQ. RESP. TO 12KHz SENS. 86dB **PRICE £16.49 + £2.00 P&P.**

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm SUPPLY 12V @ 0.5AMP **PRICE £14.49 + £1.00 P&P**

FM MICRO TRANSMITTER (BUG) 100-108MHz, VARICAP TUNED COMPLETE WITH VERY SENSITIVE MIC, RANGE 100-300m, SIZE 56 x 46mm SUPPLY 9V BATTERY **£8.62 + £1.00 P&P**



3 watt FM Transmitter



POSTAL CHARGES PER ORDER £1.00 MINIMUM OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA ACCESS ACCEPTED BY POST. PHONE OR FAX



* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OVP VARISPEED TURNTABLE CHASSIS.



* MANUAL ARM * STEEL CHASSIS * ELECTRONIC SPEED CONTROL 33 & 45 * VARI PITCH CONTROL * HIGH TORQUE SERVO DRIVEN DC MOTOR * TRANSIT SCREWS * 12" DIE CAST PLATTER * NEON STROBE * CALIBRATED BAL. WEIGHT * REMOVABLE HEAD SHELL * 1/2" CARTRIDGE FIXINGS * CUE LEVER * POWER 220 240V 50/60Hz * 390x305mm * SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE.

PRICE £59.99 + £3.50 P&P.

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OVP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:— MXF200 (100w + 100w) MXF400 (200w + 200w) MXF600 (300w + 300w)

All power ratings R.M.S. into 4 ohms.

FEATURES: * Independent power supplies with two Toroidal Transformers * Twin L.E.D. Vu meters * Rotary indexed level controls * Illuminated on/off switch * XLR connectors * Standard 775mV inputs * Open and short circuit proof * Latest Mos-Fets for stress free power delivery into virtually any load * High slew rate * Very low distortion * Aluminium cases * MXF600 Fan Cooled with D.C. Loudspeaker and Thermal Protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:— MXF 200 W19" x H3 1/2" (2U) x D11"
MXF 400 W19" x H5 1/4" (3U) x D12"
MXF 600 W19" x H5 1/4" (3U) x D13"

MXF200 £171.35
MXF400 £228.85
MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH



OVP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS, FINISHED IN HARDWEARING BLACK VYNIDE WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE. INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE 45Hz-20KHz BOTH MODELS 8 OHM, SIZE H18" x W15" x D12"

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OVP 12-100 (100W 100dB) PRICE £159.99 PER PAIR

OVP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

OVP SLIDE DIMMER 1K WATT & 2.5K WATT

CONTROLS LOADS UP TO 1KW & 2.5KW. SUITABLE FOR RESISTIVE AND INDUCTIVE LOADS. BLACK ANODISED CASE. READY TO FLUSH MOUNTED THROUGH PANEL. CABINET CUT-OUTS. ADVANCED FEATURES INCLUDE:—

- * FULL 65mm SLIDE TRAVEL
- * NFON
- * MONITOR INDICATOR
- * FLASH/OVERRIDE BUTTON
- * HIGH & LOW LEVEL PRESETS
- * FULLY SUPPRESSED TO BS 800


SIZES:— 1KW H128xW40xD55mm
2.5KW H128xW76xD79mm

PRICES:— 1K WATT £15.99
2.5K WATT £24.99 + 60p P&P

PIEZO ELECTRIC TWEETERS-MOTOROLA

PIEZO ELECTRIC TWEETERS — MOTOROLA

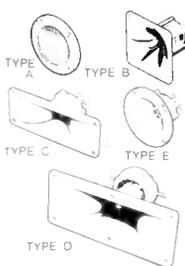Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 50p P&P.

TYPE 'B' (KSN1005a) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.00 each + 50p P&P.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.99 each + 50p P&P.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £9.99 each + 50p P&P.

TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.99 each + 50p P&P.

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £3.99 + 50p P&P.

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following —

3 Turntables (Mag), 3 Mics, 4 Line including CD plus Mic with talk over switch Headphone Monitor, Pan Pot L & R, Master Output controls. Output 775mV. Size 360 x 280 x 90mm. Supply 220-240V

Price £134.99 — £4.00 P&P




B. K. ELECTRONICS Dept ET1

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL: 0702-527572 FAX: 0702-420243

MAKING ELECTRONICS C.A.D. AFFORDABLE

- HAVE YOU BEEN PUTTING OFF BUYING PCB CAD SOFTWARE?
- ARE YOU STILL USING TAPES AND A LIGHT BOX?
- HAVE YOU ACCESS TO AN IBM PC/XT/AT OR CLONE?
- WOULD YOU LIKE TO BE ABLE TO PRODUCE PCB LAYOUTS UP TO 17" SQUARE?
- WITH UP TO 8 TRACK LAYERS AND 2 SILK SCREEN LAYERS?
- PLUS DRILL TEMPLATE AND SOLDER RESIST?
- WITH UP TO 8 DIFFERENT TRACK WIDTHS ANYWHERE IN THE RANGE .002 to .531"?
- WITH UP TO 16 DIFFERENT PAD SIZES FROM THE SAME RANGE?
- WITH PAD SHAPES INCLUDING ROUND, OVAL, SQUARE, WITH OR WITHOUT HOLE, AND EDGE CONNECTOR FINGERS?
- WITH UP TO 1500 IC'S PER BOARD, FROM UP TO 100 DIFFERENT OUTLINES?
- WITH AUTO REPEAT ON TRACKS OR OTHER FEATURES - IDEAL FOR MEMORY PLANES?
- THAT CAN BE USED FOR SURFACE MOUNT COMPONENTS?
- WITH THE ABILITY TO LOCATE COMPONENTS AND PADS ON GRID OR TO .002" RESOLUTION?
- WITH AN OPTIONAL AUTO-VIA FACILITY FOR MULTILAYER BOARDS?
- WITH THE ABILITY TO CREATE AND SAVE YOUR OWN SYMBOLS?
- THAT IS AS GOOD AT CIRCUIT DIAGRAMS AS IT IS AT PCB'S?
- THAT CAN BE USED WITH EITHER CURSOR KEYS OR MOUSE?
- WHERE YOU CAN LEARN HOW TO USE IT IN AROUND HALF AN HOUR?
- WHICH WITH EASY-PLOT AND EASY-GERB CAN OUTPUT TO PEN- PLOTTER OR PHOTO-PLOTTER (VIA BUREAUX)
- **THAT ONLY COSTS FROM £49 INC VAT?**

WRITE OR TELEPHONE FOR FULL INFORMATION

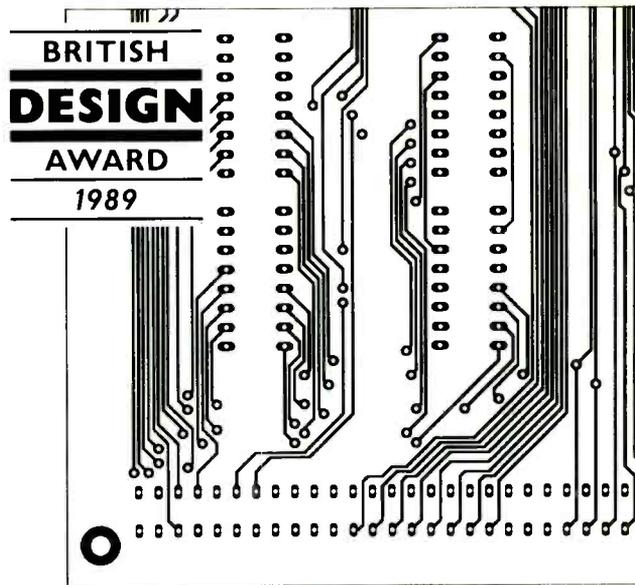

EXCELLENT QUALITY FROM DOT MATRIX PRINTER

TINY-PC, EASY-PC, TINY-PC, EASY-PC, TINY-PC, EASY-PC, TINY-PC, EASY-PC

Number One Systems Ltd



Ref: ETI, HARDING WAY, SOMERSHAM ROAD
ST IVES, HUNTINGDON, CAMBS PE17 4WR

Telephone: 0480 61778 (4 lines)

**NOW FREE
WHILE
STOCKS LAST**

CRICKLEWOOD ELECTRONICS


**1989 100 PAGE COMPONENT
CATALOGUE**

SEND OFF FOR YOUR COPY TODAY...

- WE STOCK AN UNRIVALLED RANGE
- ALL OUR COMPONENTS ARE FIRST CLASS BRANDED ITEMS
- WE OFFER A SAME DAY SERVICE ON ALL STOCK ITEMS
- NO MINIMUM ORDER - IF YOU NEED ONE COMPONENT WE CAN SUPPLY ONE COMPONENT
- WE HAVE ADOPTED A NEW LOWER PRICING POLICY + QUANTITY DISCOUNTS

JUST FILL IN THE COUPON OPPOSITE OR PHONE US ON
01-452 0161 FOR YOUR FREE COPY!

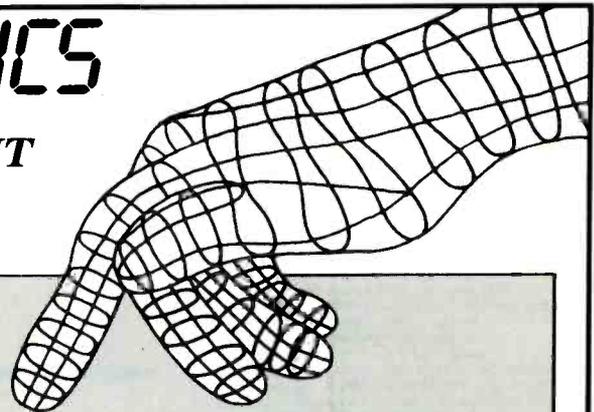CRICKLEWOOD ELECTRONICS LTD
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
TEL: 01-450 0995/452 0161
FAX: 01-208 1441
TELEX: 914977



SEND OFF FOR YOUR FREE CATALOGUE AND VOUCHERS TODAY

I WOULD LIKE TO RECEIVE COPY (COPIES) OF
THE 1989 CRICKLEWOOD ELECTRONICS
COMPONENT CATALOGUE.

NAME

ADDRESS

.....

.....

.....


I WOULD LIKE TO RECEIVE A FREE COPY OF YOUR
1989 CATALOGUE.

October 1989

VOLUME 18 No 10


Jez Ford: Editor
Paul Freeman: Deputy Editor
Paul Chappell: Projects Editor
Mark Webb: Group Editor

Cass Gilroy: Ad Manager
Julie Horsted: Production
Jerry Fowler: Technical Illustration
Mannie Cefai: Photography

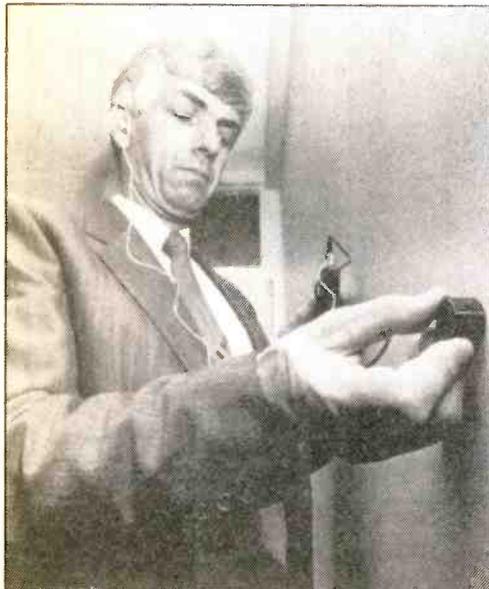

Page 18

Page 44

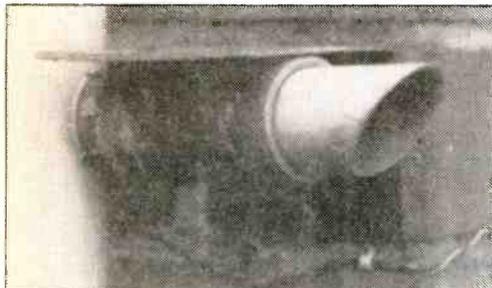

REGULARS

News

6

Book Look


12



Subscriptions


Your chance to win a complete kit for John Linsley Hood's 80W MOSFET Power Amplifier in our spectacular subscriptions offer

8

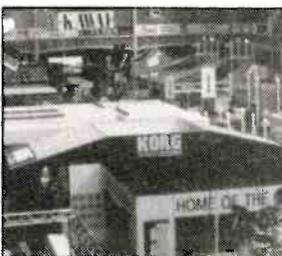

BMF Show News

12

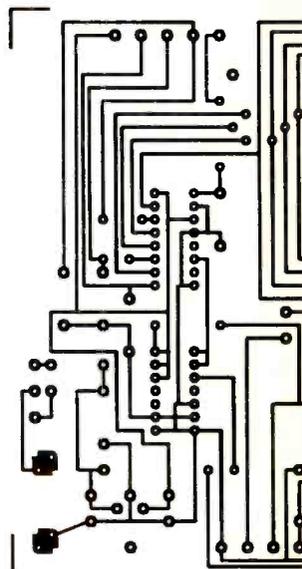

PCB Foil Patterns

62

Playback

9

Photocopies

29

Classified Ads

64

Blueprint

10

PCB Service

35

Next Month

66

Open Channel

11

Oops!

62

Ad Index

66

ISSN 0142-7229

ABC

Member of the Audit Bureau of Circulation

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company © 1989 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

• Subscription rates — UK: £18.00 Europe: £22.20. Middle East: £22.40. Far East: £24.00. Rest: £22.70 or US \$39.00.

ARGUS PRESS GROUP

Argus House
Boundary Way,
Hemel Hempstead
HP2 7ST
Tel: (0442) 66551
Telex: 827797

FEATURES/PROJECTS

Under Surveillance 1: The Circuits


Paul Chappell puts his ear to the wall and picks up some interesting designs for first-time spys

14

Under Surveillance 2: The Inside Story

Helen Armstrong talks to the surveillance experts who supply the industry with concealed equipment for private eye or industrial espionage

18

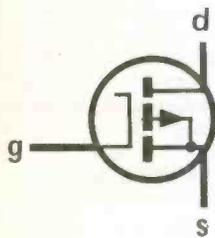

And Then There Were Transistors

John Linsley Hood closes the gate on his two part look at the evolution of the transistor

24

The Good IC Guide

Paul Chappell announces the merits of the L165V power op-amp and puts it through its paces

30

Less Logic

Andy French invites you to join the exclusive OR club as he wades his way through Boolean simplification and finds that there's really very little to be scared about

36

Testing Testing

Mike Barwise returns to the pages of ETI with this first part of a major new series examining the problems associated with basic and advanced test gear and the often simple solutions that can set your results to rights

40

PROJECT Intruderbeam

If there are burglars at the bottom of your garden, you can stop them getting any closer with Geoff Phillips' infra-red warning/deterrent system

44

PROJECT Polybel Tuneware

Trevor Skeggs dumps his digital ditties into last month's polyphonic programmable doorbell with 'Tuneware' and 'PBOS' — the Polybel Operating System

50

PROJECT MIDI Mapper


Robert Penfold crosses the channel in the twinkling of a clock period with this stand-alone unit to filter your musical data stream

53

PROJECT Multimeter

Douglas Kennedy presents a beginners' project for a budget DC meter

59

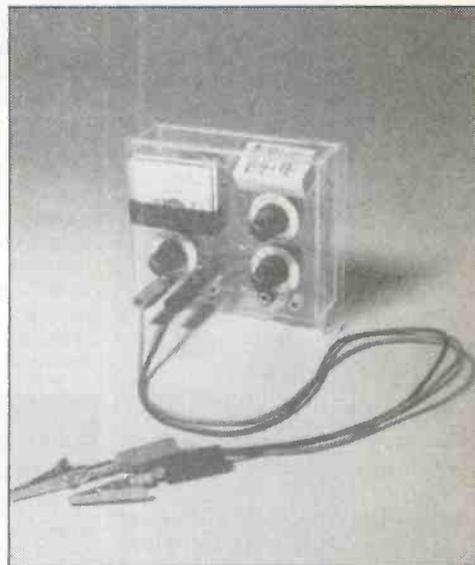


Page 59



Page 50

Page 53

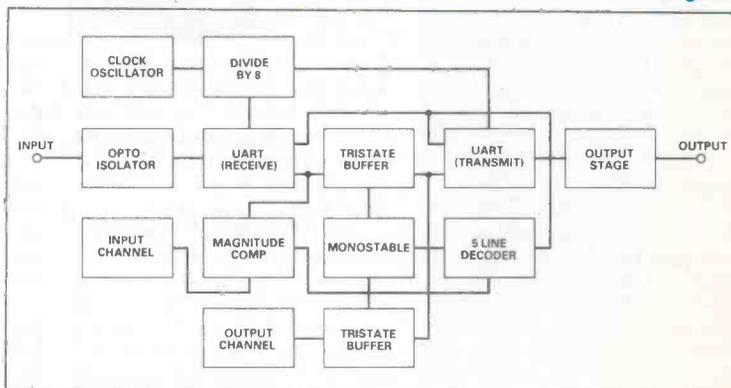

NO SALE

The privatisation of the electricity industry will not include the sale of Britain's Magnox nuclear reactors, because of the huge costs associated with decommissioning.

The announcement came as the bill approached the end of its passage through the House of Lords and forced an embarrassing U-turn on Baroness Hooper, a junior energy minister and representing the Government in the House.

A proposal was made by Labour Energy Spokesman Lord Williams that the entire bill be held until the autumn session, in the hope that the Government might more reliably finalise its plans. "After all" he said, "we are talking nuclear power stations, not tiddly-winks".

The wisdom of including nuclear power in the sell-off equation has always been in doubt. The enormous costs of building nuclear plants and the inconceivable costs of compensation in case of accident would make it unlikely that private enterprise would ever commission new power stations. This would seem to directly contradict the Government's commitment to the nuclear industry.


The Magnox decision only partly solves the problem. As Lord Ezra, former chairman of the National Coal Board, was quick to point out in the House of Lords, there has been no reason given as to why the exemption should not be extended to all nuclear stations.

His questions were later echoed by the Confederation of British Industry, which urged the removal of all nuclear power until the costs are more clearly realised.

There are fears in the industry that troubles with advanced gas-cooled reactors (AGRs) may extend many years beyond the anticipated run-in period. The costs of decommissioning and of reprocessing fuel are also expected to climb rapidly. Unless the Government makes firm guarantees of support, or removes nuclear power from the sell-off altogether, private industry and the free market is likely to spell the end of the British nuclear industry and the general concern will adversely affect the entire privatisation scheme.

It would appear that doubts over the nuclear inclusion are not limited to those in the industry. A recent National Opinion Poll commissioned jointly by Greenpeace and Friends of the Earth indicated that while 17% of interviewees were considering buying electricity shares, only half that number would do so if nuclear power formed part of the offer.

DAT FOR CHRISTMAS

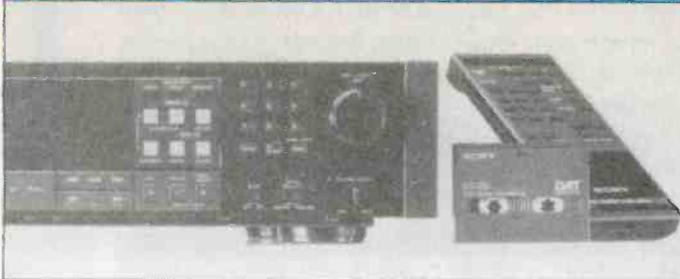

The much awaited Digital Audio Tape machines will be generally available to the public throughout Europe by Christmas.

An agreement comes after argument between the recording and consumer electronics industries over the infringement of copyright issue. It now clears the way for the consumer to make near perfect copies of live or recorded material using DAT, but as a concession the manufacturers agreed that the tape machines will only be able

to copy originals once — a condition the recording companies asked of the manufacturers before the boycott could be lifted. How this is to be achieved is not yet clear.

The recording companies will not receive a royalty for every DAT machine sold as compensation for the infringement of copyright. However, talks will have to start all over again when it comes to discussing the newest technology — the recordable compact disc.

AIR-SEA POWER

If the electricity privatisation bill is passed in its present form, one positive result should be the promotion of renewable energy sources such as wind and sea.

The Government has specified that within ten years of privatisation, some 600MW of the power fed to the grid from nonfossil fuel should come from renewable sources.

As a prelude to this, three experimental wind turbines are to be

built under a £28m scheme announced by the CEBG, and to be funded by PowerGen and National Power (the two generating companies that will be formed from the CEBG) together with the Department of Energy.

The three sites are at Capel Cynon in Dyfed, in North Cornwall and in the northern Pennines. It is hoped that the first of these will be operational by 1991, using 25 turbines to produce between 7.5MW and 12.5MW.

SPEAKER TECHNIC



Latest in the world of outrageous speaker systems are these two units from Technics. They have been designed by Mr Technics himself, Mr Obata, using complex space simulation programs to give the designs shown here.

The SST-1 Sound Space Twin Load Horn appears more like a musical instrument than a speaker system. It uses two different sized horns folded and mounted on the back of the speaker with an acoustic filter for mid-range detail. The price is as spectacular



as the appearance — not yet finalised but expected to be around £1000 a pair.

The SST25Hz and SST35Hz must be approaching the ultimate in subwoofer systems, a horn is folded back at the centre of its length with acoustic coupling in the upper portion. The tentative prices are £1000 for the 35Hz version and £1400 for the 25Hz.

For further details and sales contact Technics, Panasonic House, Willoughby Road, Bracknell, Berkshire RG12 4FP. Tel: (0344) 853205.

TOUCH TECH

A new company has been formed to meet the demands of the hi-tech touch screen industry.

Based at Eastleigh in Hampshire, Touch Screen Technologies Ltd will design and supply touch screens and interfaces, complete with software. It has entered into a joint venture with Gunze Ltd of Japan, to manufacture touch screens for the European market.

The conductive coated film is a metallic oxide coated polyester, manufactured in the US and Japan. With an overall thickness of only 0.75mm, the resistive touch screen is simple to use and has already been applied to the medical, process control and banking industries. They are also considered ideal for airlines, tour operators, hotels and any situation requiring general public access to computers. Touch screens in all shapes and sizes are finding their way onto calculators, personal organisers and into diaries.

For further information, contact Touch Screen Technologies Ltd on (0703) 629545.

FAX CHANGE



Ceefax, the BBC's teletext system, is about to commence a relaunch operation — or perhaps more appropriately a metamorphosis as the changes are taking place slowly.

An estimated six million viewers have teletext sets in this country and the process of finding what you want can be painfully slow at times. This is because data is sent serially through a few lines on the top of the screen of your TV set. Ceefax is now going to use more of these lines to convey the information a little faster. This will be done by increasing the number of pages available and reducing the number of subpages.

It is in the subpage area where access to information can take the time. At present 99 subpages are available, but only eight are used at any one time. You can imagine the eternity it would take to cycle through 99 pages!

Part of the change is that only three subpages will be used, to reduce waiting time. Subject areas of the magazine are to be renumbered as well, each getting its own 'hundred' category. The travel section, for example, is to be expanded and updated more frequently by the new BBC Travel service.

TV GRAPHICS

Conventional television pictures can now be combined with computer graphics on a fully interactive scale, thanks to a breakthrough in image processing from Videologic, a British company based in Hertfordshire.

It is nothing new to overlay computer text onto a full-screen image displayed on a standard television screen. There has also been some success in digitising a continuous TV picture for display on a conventional computer monitor.

But the DVA4000 (Digital Video Adapter) goes further. It allows real-time processing of the signal as a binary array, enabling windowing, fades, layering and so on. An entire image could be reduced to icon size, to be selected when required and 'pulled' to the desired size. This form of video integration requires very fast processing — some 25Mbits per second when used with an IBM PS/2 machine.

The development of the DVA4000 has involved £1.5m research and design using the custom chip CAD facilities of VLSI in the US, and 8-layer PCB manufacturing in the Netherlands.

It supports all 17 VGA modes so needs no extra graphics card and uses a single expansion slot.

For more details contact Videologic, Home Park Ind. Estate, Kings Langley, Herts WD4 8LZ. Tel: (09277) 60511.



CHIP SPEAK

Cogent Technology's modular speech synthesis system can give you a microchip that can add a human voice to your products.

The system interfaces to machine I/O ports producing any number of different speech output combinations. It can give single words or sentences and react to real time situations. A simple system, using 10 to 20 keywords in different combinations will cost a few tens of pounds when produced in quantities of a hundred or more.

The speech is stored on EPROM in the form of digitally recorded and compressed speech. The intonation and inflection of the male or female voice can be changed if required. As the package is miniturised it can be used in anything from a hand held meter to a large machine tool.

Contact Cogent Technology Ltd, Dock Lane, Melton, Suffolk IP12 1PE.

INDUSTRIAL CAMCORDER



A new Video 8 recorder/player is now available from Sony's new range of industrial 8mm audio and video products.

A growing number of Video 8 camcorders are being used in areas such as education, training, travel and research. With the growing acceptance of 8mm format and the ever increasing base of 8mm camcorders, Sony believes the new recorder/player will find a niche in non specialist areas within industry and commerce.

In the industrial sector, Video 8 is now being used for test bed recording, production line monitoring and operational analysis.

Its chief advantage is its small size. The Video 8 tape is no bigger than an audio cassette.

The EVO 520P is a rugged industrial version of its consumer counterpart and being a front loader, it can be rack mounted. The machine has an auto repeat function and in search mode, recognisable colour pictures can be followed with ease, a useful function. The player operates on AC or DC, and the low voltage DC gives the flexibility of usage in field work. The price tag on the EVO 520P is £795.00.

Further information from (0256) 474011 ext 3603.

LASER WORM

Mitsubishi is introducing a new optical disc storage system into the UK.

The MW-5U1 is a laser action WORM drive (Write Once Read Many times) and comes complete with the standard small computer system interface (SCSI) for your PC.

Mitsubishi wants to target the package at places where high volumes of permanent storage are required. These include CAD graphs, database storage and archival systems for legal, financial, scientific and medical organisations. The disc drive can store 300MB on each side of the optical disc cartridge and the software allows standard DOS or MS-DOS read/write access to any PC.

The drive is said to be the fastest available anywhere with random access times of 80ms, track to track times of 1ms and average positioning times of 63ms. Data transfer rate is 5.5Mbits per sec.

The MU-5U1 package comes complete with a 600MB optical disc cartridge and retails at £250.

For further information contact Mitsubishi Electric UK Ltd., Electronics Division, Travellers Lane, Hatfield, Herts AL10 8XB. Tel: (07072) 76100.

AUDIO PARTS

Graham Nalty, the man that gave you the Virtuoso Power amplifier way back in 1988 can supply you with a list of upgraded components for your JLH Audio Design amplifier through Audiokits Precision components.

A list of components is available from Audiokits, 6 Mill Close, Borrowash, Derby DE7 3GU. Tel: (0332) 674929.

CAD CIRCUITS

A machine code utility for designing and printing circuit diagrams for the Sinclair Spectrum (48k, 128k, +2) is now available from BESoft.

The software package offers facilities for drawing, editing, storing and printing of diagrams. The user friendly system includes 50 standard circuit symbols and associated logic gates with 400 more user-definable symbols. The symbols can be rotated or flipped to give the correct orientation and then moved into the correct position.

Labelling of text includes Greek characters and a magnifying facility gives four times the normal size around the area of the cursor. The printer interface options are ZX or Alphacom 32 type. Centronics Interface and Interface 1-RS232 output.

Prices are £17.50 (cassette version) £19.00 (microdrive). Both include postage and packing.

Further information from BESoft, 20 Ashfield Road, Leytonstone, London E11 4DT. Tel: 01-588 3469.

GIANT LEP FOR MANKIND

The Large Electron Positron collider, LEP, built in Geneva, is about ready to shoot its load. The accelerator has a 17-mile circumference and is 11ft wide, burrowing through the border between France and Switzerland — a truly international project funded by the 14 member countries of CERN, the European Centre for Particle Physics.

High on the list of priorities for LEP is a systematic study of the particles that transmit the weak nuclear force, the so-called Z particles.

These have been seen before but not in sufficient quantities to allow analysis.

There is also, as always, the hope of spotting new particles such as the elusive Higgs boson.

ROCKING ROBOTS



ROCK
circus



Rock Circus, a new permanent exhibition of static and animated rock stars, opened in London last month.

The Tussauds Group, famous for its wax figures, decided there was a need for an exhibition of rock music history.

To display such a vibrant part of our culture was a challenge, so they developed and patented the robotics or audio animatronics section of the show. Their movements, lighting,

sound and effects are all controlled by two powerful computers.

Walking around the show, you can hear the full hi-fi sound through cordless infra-red headphones. Many spectacular effects await you on your journey through pop history. A full review of this and the exhibition will be given in next month's ETI.

The show is open daily 10am to 10pm at the London Pavilion, Piccadilly Circus. Prices are £4.20 for adults and £3.15 for children.

YOUR CHANCE TO WIN!

Subscribe to ETI and win a John Linsley Hood 80W MOSFET POWER AMPLIFIER.



What better way is there of making sure you never miss another copy of ETI than by ordering an annual subscription for only £18.00*?

Each issue is delivered direct to your door at no extra cost. For a limited period you now have the chance to win, in our exclusive competition.

To win this complete kit, order your subscription using the coupon provided and study the four pictures below. Each is taken from the cover of ETI in the last six months. Simply write in the correct cover date next to the relevant letter on the coupon and you could be the winner of this spectacular prize.

John Linsley Hoods 80W Audio Design MOSFET Power Amplifier was featured in the May 1989 issue of ETI and the kit is produced by Hart Electronics as the flagship of its pedigree audio range. It combines the excellent performance one expects from a Linsley Hood design, with a versatility unusual in power amplifiers. The passive input stage with gain and balance allows direct input not only from a pre-amp but from CD and tape decks direct.

This offer is also open to current ETI subscribers who wish to renew or extend their current subscription but they must do so using the order form provided. The lucky winner will be the first correct form drawn. A photocopy of the order form will be acceptable if so desired.



These four pictures were each shown on the front covers of:

A C

B D

Please commence my subscription to ETI with the issue. I enclose my Cheque/money order for £18.00 made payable to ARGUS SPECIALIST PUBLICATIONS

Or Debit my Access/Barclaycard number

Valid from to Signature

Name Address

Post Code

New subscriber Subscription renewal/extension (delete as applicable)

Return this order with your remittance to: The Subscription Manager, A.S.P. Argus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST.

ETI/4



*All prices refer to UK subscriptions only

TERMS & CONDITIONS

This offer closes on Friday 29th September and is open to UK residents only. Subscriptions received using the order form provided and showing the correct competition answers will be entered into the DRAW. No cash alternative will be available to the winner. The winner will be announced in a future issue of ETI. The judges decision is final. Full details of the terms and conditions of entry into this promotion are available on request.



PLAYBACK

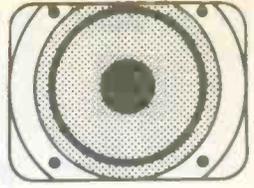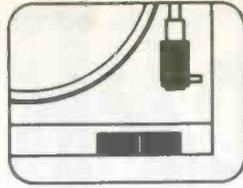

Over the last couple of months I have introduced the concepts of Pulse Density Modulation (Philips) and Pulse Width Modulation (Technics) as applied to D/A reconstruction in modern CD players.

Well the pace of technology has not let up since, for no less than two new D/A converters have been introduced in the last few weeks.

The first of these is a new 16-bit DAC from Philips who, for the time being at least, appears to be covering both multi and single-bit bases! First seen in the sub-200 CD610 CD player, this new 'economy' DAC has been integrated down to an 8-pin DIL package. Imagine, a dual-channel 16-bit converter no larger than an NE5532 op-amp!

Technically the TDA1543, as it is known, falls behind the standards set by their top TDA1541 converters yet some of its specs are quite remarkable. THD and noise typically fall in the -80dB range at peak level (as opposed to the TDA1541's < -100dB) yet in terms of amplitude linearity its -90dB error of just -2.4dB represents tough competition.

Oddly enough if the linearity of the TDA1543 were assessed in terms of s/n, as is the SAA7320 bitstream chip, then a figure of 13 bits would seem most appropriate. However in terms of amplitude its moderate low-level error implies a practical linearity of some 15.6 bits.

Expect to see this new DAC crop up in a number of budget players. Its low 5V supply rating also makes it an ideal candidate for portables and the like.

Of greater surprise this month was NAD's announcement of two new CD players, the 5320 and 5325, which have been designed around a new hybrid DAC from Sanyo. The LC7881 is another low-cost chip yet it combines the virtues of multi-bit operation with the simplicity of a PWM glitchless output.

The LC7881 incorporates two independent D/A converters which latch the incoming 16-bit data stream and sub-divide it into three distinct bit-words. Specifically the first 9 Most Significant Bits (MSBs) are separated to control a series-ladder of 512 resistors ($2^9 = 512$). Acting as a 9-bit

switch this DAC generates two output voltages, V1 and V2, that correspond to levels slightly above and slightly below that described by the 9-bit word.

For truly monotonic conversion the resistance chain of a 9-bit DAC demands an accuracy of less than one part in 512. In a conventional 16-bit DAC the 65536 available quantisation levels require an accuracy 128 times as great for monotonic conversion. This is all well and good but there is little to be gained by truncating the 16-bit code for simplicity of operation if the original 98dB linearity is still desired.

Sanyo has solved this problem by employing the 4 Least Significant Bits (LSBs) to control two variable resistors that are connected in series with the two ends of the 512R chain. These are used to trim the R-string 9-bit converter outputs such that the total voltage across both variable resistors remains constant but that the unit resistance of the main R-string alters in steps of 1/128.

Having accounted for the nine MSBs and the four LSBs the remaining three intermediate bits are employed to generate eight different pulse widths

($2^3 = 8$) within the PWM output DAC. These eight different pulse widths determine the percentage of time occupied by each of the V1 and V2 voltages, necessitating a clock frequency able to accommodate up to 16 different widths.


The maximum data rate is therefore $16 \times 176.4\text{kHz}$ (the latter derived from a 4x oversampling filter) = 2.8224MHz. However, as with previous PWM systems, each 176.4kHz conversion sample must be subdivided into nine equal time slices. This is necessary to accommodate the maximum pulse width (equal to 8x the least pulse width) plus one wait cycle (also equal to a least pulse width). Therefore the clock edge accuracy has to be within $9 \times 7.8224\text{MHz}$ or 25.4016 MHz. Sanyo actually specify 8.4672MHz because they claim a total of 3 clock cycles per PWM conversion cycle.

Either way this is a cost-effective method of avoiding the non-monotonicity, zero-cross distortion and glitches suffered by conventional DACs. Perhaps other hybrid systems are on the horizon. **Paul Miller**

THE VFM TOTAL KIT

Wilmslow Audio's new VFM speaker kit is remarkable **VALUE FOR MONEY!** The design uses an Audax bass unit and a Peerless dome tweeter integrated by a multi-element crossover and gives excellent results for its modest cost.

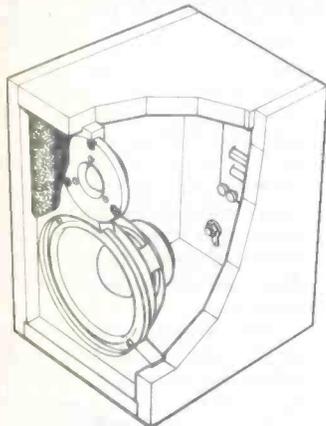The kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly), speaker drive units, assembled crossovers, grille foam, wadding, binding post connectors, screws, assembly instructions, etc.



Dims: 310x206x240mm
Amp. suitability:
10-50 watts.
Impedance: 8 ohms
Response: 70hz-20Khz

PRICE:
£69.95 per pair
plus carr/ins £8

telephone credit card orders

WILMSLOW AUDIO LTD.

35/39 Church Street, Wilmslow, Cheshire
 SK9 1AS Tel: 0625 529599

Call and see us for a great deal on HiFi
 (Closed all day Mondays)

DIY Speaker catalogue £1.50 post free (export \$6)

SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. All units available ready built if required.

- MTX** Micro-miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range. **£12.95**
- VT500** Hi-power audio transmitter. 250mW output. 20mm x 40mm. 9-12V operation. 2-3000m range. **£15.95**
- VOX75** Voice activated transmitter. Variable sensitivity. 30mm x 40mm. 9V operation. 1000m range. **£18.95**
- CTX900** Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm. 9V operation. 1000m range. **£21.95**
- DSX900** Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm. 9-12V operation. **£21.95**
- HVX400** Mains powered audio transmitter. Connects directly to 240v AC supply. 30mm x 35mm. 500m range. **£18.95**
- XT89** Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 28mm. 9V operation. 2-3000m range. **£36.95**
- TKX900** Tracker/Beeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm. 9V operation. 2-3000m range. **£21.95**
- ATR2** Micro size telephone recording interface. Connects between telephone lines (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line. 10mm x 35mm. **£12.95**
- TLX700** Micro miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line. 1000m range. **£12.95**
- XML900** RF bug detector. Variable sensitivity. Triggers LED and beeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation. **£26.95**
- XL7000** Professional bug detector/locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate beeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation. **£54.95**

UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Full catalogue available on receipt of 28p stamp. Trade enquiries welcome.




THE WORKSHOPS
 95 MAIN RD, BAXTERLEY
 NR. ATHERSTONE
 WARCS CV9 2LE



0827 714476

BLUEPRINT

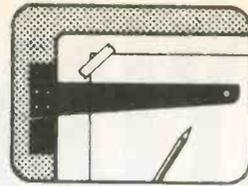

This Blueprint and the one or two following are to be somewhat different from usual. ETI has received an enquiry from the Dyfed Wildlife Trust for help in providing an amplifier to play amplified recordings of bird calls in the hope of attracting migrating birds to re-establish a colony. The project is larger than would be normal for a Blueprint, but it is technically interesting and a *Good Cause* so I decided to see what can be done.

There is limited technical backup at the wildlife trust, so the plan is for ETI to provide the parts and for me to assemble the necessary modules, while explaining in print the rationale behind the design.

Shearwaters

Manx Shearwaters are sea birds which land only to breed, and they seem to do this at night. They nest in burrows, as a result of which the colony on Cardigan Island were exterminated in the 1930s when rats escaped from the wrecked steamer Hereford. Now that the rats have been eradicated from the island the Dyfed Wildlife Trust (sponsored by Cresta Holdings of the Isle of Man) are trying to encourage a new colony of Shearwaters to form.

Previous attempts have involved taking birds too young to fly and transporting them to the island in the hope that once they can fly they will return in the normal migration pattern. This has not worked apparently because the lack of a flourishing colony on the island has meant that the island is quiet and hence not attractive for their return.

The strategy now is to play recordings of the call of the shearwater in the hope of attracting birds to the island. If it works this would eventually

become self sustaining, but some time might be required for the colony to build up to this point.

Power

The island is uninhabited and has difficult access. It is just about possible to land by boat, but impossible armed with tools and electronic equipment. Consequently any electronic equipment installed must be very reliable and able to function without intervention for long periods of time. The use of any power source requiring periodic attention is ruled out, which leaves wind or solar power as the two obvious choices. Power from such sources can vary greatly due to our renowned British weather.

The equipment will initially be delivered by helicopter but maintenance visits could be a problem!

A solar power system by BP Solar is being used. This can be guaranteed to provide 10AH/day at 12V over the period from January to October, with more available in practice over the middle part of the year if the weather is good. The original request was to provide 60W audio output for the whole night, a demand clearly beyond the capability of the power source. In addition it was initially thought that the signal source was to be a highly reliable environmentally sealed automatic tape machine provided by Racal Recorders, consuming 24W. Erk alors!

Subsequently they have provided a CMOS RAM store. The power consumption of this unit is too small to consider, so that what power is available will be able to be fed to the amplifier. Even so, it is quite possible that over 100W will be required to provide an output of 60W. The

average power consumption depends on the waveform of course, and the current consumption will not be as much as if the output were a 60W continuous sine wave.

The exact time for which the unit can run over each period of 24 hours depends on the efficiency, but at least an hour should be possible. The ornithologist confirms that short periods of sound rather than continuous bird calls is likely to be effective, so that the project is now possible within the constraints of the laws of physics.

Now we get to the electronic questions. A pair of 8R horn loudspeakers are available, each rated at 40W. If these were connected in parallel the voltage required to provide a power of 60W would be 15.5V RMS, which translates to 43.8V peak to peak. Any practical amplifier which is to provide 43.8V peak-to-peak will need approximately a 50V supply to do it. As an alternative, one might deliver the required power to the loudspeakers by using a step-up transformer on the output of the amplifier and running the amplifier on the 12V supply.

The disadvantage of running the amplifier on a 12V supply is that, using tried and tested circuit techniques, one is unlikely to swing the output closer to the power supplies than within 2V. The waste of a total of 4V out of a possible output swing of 12V would lower the efficiency of the circuit too much.

Various compromise solutions, using bridge amplifiers for example, were considered and rejected. Some of the solutions considered were technically interesting but the prime requirement is that the equipment shall be reliable. It is simply not practical as an amateur project to design fancy circuits from scratch and be confident of leaving them to run unattended for months on end. For a project of this nature well known and understood technology is needed.

Inversion

The design strategy which I am following is to adapt, with his kind permission, a design done by John Linsley Hood. The April and May 1986 issues of ETI published his design for the 55W power amplifier to run from 12V. This has been carefully designed for the purpose and has probably had more design time applied to it so far than is available before the equipment is to be installed. John Linsley Hood makes the point that the sensible designer will look through his files of other people's designs to see what has been done in a particular area, and perhaps thereby avoid reinventing the wheel or falling foul of

an unobvious snag. This is a case in point.

JLH's amplifier design is in two parts. First of all there is an inverter which increases the battery voltage to 55V, then in a separate module is a simple but sturdy single rail power amplifier. The modules could almost be used as they are designed but certain alterations can improve their applicability to the specific project. At the time of writing this I am hoping to be able to use the PCBs originally designed for the project courtesy of the ETI PCB Service.

One special requirement is that the amplifier system must be capable of being switched on and off automatically, perhaps at intervals of five minutes, without making any sort of power up thump which may startle the birds. It may therefore be necessary to add a slow startup circuit to the 55V inverter. Further, it is preferable if the volume rises over a period of several seconds rather than the sound starting abruptly, again to avoid startling the birds and defeating the object of the exercise.

The frequency range of the bird calls is rather limited, so a full bandwidth is not required from the amplifier. The range is 400Hz to 1.2kHz and for such a narrow range there may be some advantage to be gained by limiting the response of the amplifier. This should become clear on careful examination of the circuit.

As well (if it can be done simply), it might be a good idea to sense the battery voltage and to shut down if it falls too low. Deta/Leda batteries (DJ Batteries in Stoke) donated the solar batteries which are rated for deep discharge, but it would still be possible to damage them if they were utterly flattened and kept that way by too heavy a load. Lead acid batteries, used here for power storage, are vulnerable to the formation of lead sulphate, which is insoluble once formed. This removes lead and active electrolyte from any utility. In severe cases the crystals of lead sulphate can buckle the plates and cause a short circuit. Temperature cycling a partially discharged battery accelerates this process.


Wide temperature swings may be expected, and it is unrealistic to expect the batteries to be fully charged all the time, so they are specially designed to survive this kind of treatment. Nevertheless, their long term utility could be impaired if, due perhaps to a corroded connection to a solar cell, the batteries were flattened and left that way. Hence the consideration of a cutout circuit.

Next month I hope to cover such design adaptations as were necessary, and to report on tests of the modules.

Andrew Armstrong

The Blueprint column is a service to our readers to provide electronic designs to order. Many a project never gets further than the drawing board because of difficulties with one small part. If you're stuck for a circuit or technique, let the ETI expert help you out. The requests that are selected for publication are likely to be of possible general use or interest to other readers. Enquiries such as 'my oscilloscope is broken, how do I fix it?' are not really suitable for Blueprint. If you have an enquiry, send it with as much detail as possible to ETI Blueprint, Argus House, Boundary Way, Hemel Hempstead HP2 7ST.

OPEN CHANNEL

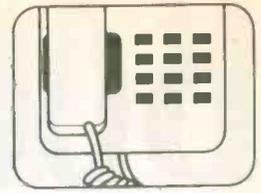

If all accounts are anywhere near true, British Telecom is about to forge ahead with a revised method of applying videotex. BT's own Prestel — the videotex originator designed and developed by BT long before anyone else had even considered videotex — has never even scratched the surface of potential in the UK.

Prestel is ten years old this year and hasn't changed much since it started. When it opened for service, it was the golden goose of the nation — but now it's more a lame duck. But I've argued this before I hear you say. Yes, back in the November 1988 issue of ETI I gave a lengthy sermon, aimed specifically at BT, showing it how to go about revitalising videotex.

In that text I showed how videotex can make good and indeed has in the French videotex system known as *Minitel*. The French equivalent of BT known, would you believe, as France Telecom, has more than four million Minitel terminals in use. Contrasted with Prestel's meagre eighty thousand terminals, this looks fairly impressive.

So what makes Minitel so much

better than Prestel that four million French people want to buy it. Well, for starters, they don't have to buy it! Minitel terminals are given away by France Telecom — the terminals are a loss leader, which presumably can be written off against tax anyway. Terminals earn their real worth by increasing the usage of the French telephone system, bringing in many more times their value in revenue created by the extra telephone calls which are generated. In more monetary terms, France Telecom has estimated that every terminal pays for itself in extra calls within a year. With everyone in the country expected to have a terminal by the end of the century, this means steady growth in telephone traffic (currently growing at over 20 per cent a year) and enormously increased revenue through-out.

Just to contrast with this situation, even BT's boss Iain Vallance has said that he expects the growth of British telephone traffic to slow down to nil over the near future. Something must be done to counteract this.

BT is currently in negotiations with a number of companies, including Alcatel (manufacturer of Minitel terminals) and Tandata (manufacturer of current Prestel terminals), all of which bodes well for UK videotex. Rumours abound that these terminals will be subsidised by BT to be a giveaway or at least very cheap. They'll need to be.

But giving terminals away is not the only thing required if Prestel is to be the figurehead for increased revenue. Even if the terminals are free, who would want to use Prestel? It's not a particularly nice videotex system, for a number of reasons.

First, the videotex services currently provided are virtually irrelevant to the majority of the British public. Minitel has many more services not yet found on Prestel. For example, the computerised French national telephone directory is available via Minitel. BT is always struggling to keep its dialled directory services up to the level of demand — particularly in the cities — so why not put it on Prestel? What about bus, plane and train timetables — local, regional, national and

international? What about home shopping, home banking, business information? True Prestel does supply some of these services but it still hasn't got it right!

Second, technically Prestel is a page-based system which is extremely slow and unwieldy to get around — Minitel, in comparison, is menu-based.

Historically, Prestel has suffered because it was the first videotex system. Everyone else learned from our mistakes. Now it looks as though we're about to get a second chance. Please Mr Vallance, can we learn from everyone else's mistakes and make ours an even better system than theirs.

If we get it right, the public and BT will benefit. But getting it right means having the desired services and the terminals to use those services economically. If the services aren't the ones we need and the terminals are expensive, we'll end up with another useless videotex system. The phoenix arising from the ashes of Prestel may just be another lame duck!

Keith Brindley

Also available

Practical Digital Electronics Handbook

Tooley

1988 · 208 pages · 216 × 138mm
ISBN 1 870775 00 7 · £6.95

- * For enthusiasts, technicians and students
- * Nine test gear projects
- * CMOS and TTL pinouts
- * Tables of reference data

Introduces digital circuits, logic gates, bistables and timers, microprocessors, etc. With nine constructional projects.

'A very useful book' *Elektor*
'A useful low cost guide' *REW*

Electronics — Build and Learn

second edition · RA Penfold

1988 · 128 pages · 216 × 138mm
ISBN 1 870775 15 5 · £5.95

- * For beginner and student
- * Combines theory with practice
- * Practical tests and experiments

Gives full constructional details of a demonstrator unit that is then used to introduce resistors, capacitors, diodes, transistors, etc. Describes how to build these up into useful circuits.

'Recommended' *Prac Elec*

Introducing Digital Audio:

CD, DAT and Sampling · Ian R Sinclair

1988 · 112 pages · 216 × 138mm
ISBN 1 870775 05 8 · £5.95

- * For technicians and students
- * Non mathematical introduction
- * Covers CD and DAT

The principles and methods of digital audio are explained non-mathematically.

Computers and Music

An introduction

RA Penfold

184 pages · 216 × 138mm · ISBN 1 870775 07 4
£7.95

- * Explains the basics of computing
- * No computer knowledge needed
- * Covers music software
- * Set up a MIDI based computer music system
- * Glossary of terms

This book will help you learn the basics of musical computing, running applications programs — like sequencers, notation programs, voice filters etc — wiring up a MIDI system and using it to good effect, in fact just about everything you need to know about hardware and the

programs, with no previous knowledge of computing needed or assumed. It describes the best computers for musical applications, and will help you choose the right components for a system to suit your personal needs, as well as equipping you to fully exploit that system.

Please supply

Quantity

Comps and Music (£7.95) _____

Prac Dig Elec Hbk (£6.95) _____

Elect Bld & Lrn (£5.95) _____

Intro Digi Audio (£5.95) _____

Prac MIDI Hbk (£5.95) _____

Dig Log Gates (£8.95) _____

Short Wave (£4.95) _____

I enclose a cheque/postal order for £ _____ made payable to PC Publishing, at 4 Brook Street, Tonbridge, Kent TN9 2PJ.

Name _____

Address _____

New book

'Readable and informative' *HSR*
'Well worth a read' *Gramophone*

Practical MIDI Handbook

RA Penfold

1988 · reprinted 1989 · 160 pages
216 × 138mm · ISBN 1 870775 10 4 · £5.95

- * For enthusiasts, students, technicians
- * Tables of MIDI codes and reference data

Explains what MIDI can do, how to exploit it to the full, and how to connect up a working system.

'Recommended' *HSR*

'Excellent' *Yamaha XPress*

'Excellent' *Prac Elec*

Digital Logic Gates and Flip-flops

Ian R Sinclair

1989 · 208 pages · 216mm × 138mm
ISBN 1 870775 06 6 · £8.95

- * For technicians and enthusiasts
- * Design and troubleshoot

Treats gates and flip-flops from basics. Boolean algebra and Karnaugh mapping explained and used extensively. Also explains microprocessors as used in digital logic.

Short Wave Frequency List

Cor Both


1987 · Paperback · 96 pages
175 × 120mm · £4.95

- * Pocket sized reference book
- * Lists the world's short wave stations

Enables radio enthusiasts to identify stations from all corners of the globe. Includes stations on 2260 kHz to 21810 kHz at 1kW or more.

Order form

BOOK LOOK

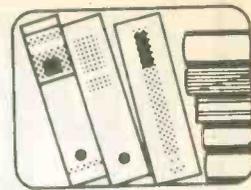

Electronics Engineers Handbook 3rd Edition
Edited by Donald G Fink & Donald Christiansen
Published by McGraw Hill
ISBN 0-07-020982-0
Price £79.95

The Electronic Engineers Handbook, revised in 1989, is a weighty tome covering everything from the basic physics and maths relevant to electronics to applications such as digital audio. It is written in twenty nine sections, grouped in four parts under the general headings: *Principles Employed In Electronics Engineering*, *Materials, Devices, Components and Assemblies*, *Electronic Circuits and Functions*, *Electronic Systems and Applications*.

Each section commences with a detailed contents list, which supplements the brief description at the front

of the book. The book is well indexed and arranged to enable the reader to locate any topic quickly, a necessary point rendered more so as there is more in the book than in several ordinary textbooks.

It is not possible to do full justice to such a work in a short review, so I will examine sections which exemplify the standard of it. Section 1 starts by defining the subject of electronics and carries on to cover relevant aspects of particle physics. It also gives good coverage of electrostatics, magnetism and electromagnetic waves among other items. The derivations of formulae, so beloved of college professors, are not included. If you have some familiarity with a subject area then you will be able to use this book for reference. It will not, however, serve to teach a subject area from scratch.

Clearly some sections have been more thoroughly or more recently updated or rewritten than others. There

are a couple of valve circuits in the subsection covering audio amplifiers. This said, most of the information is either of a fundamental nature and thus becomes out of date slowly (if at all), or is up to date at the time of publication. Examples of the former would be the sections on mathematics or radio wave propagation, while the section on computer software is as up to date as is plausible for a book rather than a magazine. Even in this section, more weight has been placed on general concepts likely to remain valid even after specific programming languages have evolved or fallen out of use.

Who would benefit from this book? The beginner in electronics is unlikely to be able to make enough use of the work to justify its cost. There are no simple designs which the constructor can build or adapt easily. At the other end of the scale, the expert in one narrow field is unlikely to find

the book of any use in his or her field of expertise, because it does not go deeply enough into individual topics to teach the experts.

Serious students of electronics, people who produce subtle and complex project designs, and above all engineers working over a wide range of disciplines are likely to find the book valuable. It is clearly designed as a reference book for the professional who may not be able to remember necessary information about a subject area which is only occasionally necessary to his work. The book has already proved its worth to me in this manner, though it contains some sections to which I shall probably never need to refer. I would recommend this book for committed students or for engineers who want a reference book covering almost everything they need to know and may otherwise have difficulty in finding out.

Andrew Armstrong

Lightwave Technology, An Introduction
Chaimowicz J C A
Butterworths Press
Price £27.50

Seldom, in this age of book after book after book on technology, do I wax even faintly lyrical about any new title. I mostly find them very similar and somewhat lacking. It is most refreshing to discover a new book which breaks the mould.

In this case the mould has been

well and truly smashed. The field of modern optics is generally considered to be abstruse and beyond the average man's comprehension. Here then is the antidote. In little more than 300 pages Mr. Chaimowicz takes us from basic concepts of light rays and lenses, via optical semiconductors, lasers, holography and fibre optics into the as yet uncharted fields of integrated optics. Throughout, he provides a wealth of real-world example, and the mathematics is mostly not even

beyond me.

What makes this book specially exciting however, is the breadth of scholarship the author has brought to bear: not only are we presented with technology (fascinating though it is), but here and there we find derivations of terminology in half-a-dozen languages and notes on photosynthesis, plus historical background and industrial applications, all expressed in a delightfully readable manner which constantly challenges one to look

further. What can one do but read on when presented with the initial proposition that "all light rays are invisible"?

All in all, an excellent book for interested amateurs and students to BSc level. Well worth its price, and guaranteed to stimulate further interest in modern optics. My only reservation is that for a couple of quid more, hardback binding would have stood up better to the use this book is likely to get — on my bookshelf at least.

Mike Barwise



The PSR3500 and PSR4500, top of Yamaha's new home keyboards using the DAS synthesis system. DAS combines AWM (Advanced Wave Memory samples) for the attack and CWM (Customised Wave Modulation — advanced FM) for sustain.

At the 1989 British Music Fair, Olympia was packed to the galleries with exhibitors bringing increasingly complex music technology to the marketplace at decreasingly frightening prices.

Nowhere was this more apparent than the arena of the budget keyboard. This is a market once held almost exclusively by Casio, more recently joined by Yamaha's tumbling-priced FM units. Yamaha now has some well turned-out units at most reasonable prices. The YS100 (£349) and YS200 (£449) have velocity sensitive keyboards and ten on-board digital effects to plump up those 4-operator sounds.

Those who have not yet rushed out to buy Yamaha's remarkable EMT-10 AWM sample expander (£250) might wish to examine the new AVS-10 before they do so. This has been produced to slot into the Electone Home Keyboard and consequently looks dreadful. The samples, however, are close to perfection — piano, choir, strings and timpani ruling the roost. The AVS-10 has 3-channel multitimbral operation

and retails at £399.

But perhaps the most remarkable performances were handed in by Kawai. The technology that brought huge success last year to Kawai's K1 keyboard (and sons) has been blown wholesale into preset sound chips and released in a range of home keyboards.

The PH50 has some 200 of the KI's best sounds and allows you to layer them in the manner of the KI's multi-sounds — at a price of £299. And the technology has even gone into the kid's toys — press the big blue buttons and you can come out with an impressive string sound.

Lastly Roland deserves a mention for its computer-orientated expanders. Designed in 'IBM beige', the CM32L (£369) is similar to the MT32 but bigger, with 128 sounds, 32-voice polyphony and 9-channel multitimbrality. The CM32P (£445) contains 64 PCM sampled sounds and takes U110 ROM cards. It has 31-voice polyphony and 6-channel multitimbral operation. The CM64 (£789) has both in a single rather understated box.

Colin Cat

THE RTC MONITOR II

100 WATT SPEAKER KIT £60.00 +£3.50 P&P (pair)

RESPONSE: 55Hz-20kHz

BASS POLYMER CONE D: 22cm

DOME TWEETER: 14mm

OVERALL SIZE (HWD): 382,252,204mm

RECOMMENDED AMP POWER: 10-100 watts per channel

The performance standard achieved in this compact design is distinctively superior to anything else available at the price. The drive units used are of sophisticated design and have been carefully integrated with a Complex Crossover. Stereo performance is exceptionally good with a well focussed sound stage and sharp resolution of detail. Distortion throughout the frequency range is low even at quite high power input and this gives a great sense of dynamic range and openness especially when used in bi-wired mode.

Supplied with:— 2 READY CUT BAFFLES, ALL CROSSOVER COMPONENTS, 2 BASS MID-RANGE, 2 DOME TWEETERS, HOOK UP WIRE, GRILLE CLOTH, SCREW TERMINALS AND SCREWS.

CROSSOVER KIT. To build 2 sets of crossovers £11+£1.75 post. (Featured in *Everyday Electronics*—May 1989 issue). Reprint Free with Kits



AMPHONIC 125+ 125 POWER AMPLIFIER



125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.

Output power 125W RMS max. per channel
Output impedance 4 to 16 ohms (max. power into 4 ohms)

Sensitivity 450V at 22K ohms


Protection Electronic short-circuit and fuses

Power 220-240V a.c. 50Hz

Chassis dim 435x125x280mm

Weight 10kg approx

£124.99 + £7.00 p&p

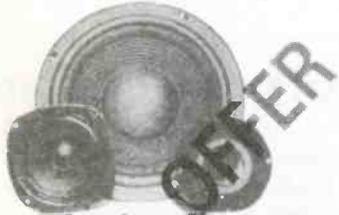

J.B.L. BOLIVAR COMPONENT SPEAKERS
10" HI-FI BASS UNIT WITH 1" VOICE COIL, HIGH COMPLIANT, RE-INFORCED, MOULDED PAPER CONE, ROLLED FOAM EDGE WITH A BIG 4 1/2" MAGNET 6Ω IMPEDANCE £18.73

4 1/2" 100W HI-FI MID RANGE 1" VOICE COIL, PAPER CONED AND DOME TWEETER, MOLDDED PAPER CONE, ROLLED FOAM EDGE FITTED WITH A 3 1/2" MAGNET, 6Ω IMPEDANCE £5.33

4 1/2" HI-FI TWEETER 3/4" VOICE COIL, 1 3/4" CONE WITH FOAM EDGE, 2 1/2" MAGNET, 6Ω IMPEDANCE £6.33

POSTAGE £4.70 PER ORDER

52W 2-WAY COMPONENT SPEAKER SYSTEM £3.95

Comprises 8in rolled surround bass unit and 2 1/4in tweeter for In-Car or Hi-Fi use. 4 ohm. Made by Sanyo.

8 OHM HI-FI COMPONENT SPEAKER £4.95

6 1/2in. Audax 60w. Res freq. 45Hz bass-mid

8in SOUND LAB 60W £12.95

Res freq. 38Hz full range

12in DANTEX 100W £21.75

Res freq. 23Hz bass unit

Postage £3.20 each order

★ SPECIAL PURCHASE

Batteries C size NiCad 2.2 Ah EVERY-READY AN220

£1.98 each

£1 BARGAIN PACKS BUY 10 GET 1 FREE

Please state pack(s) required
No=Order No. Qty=Quantity per-pack

No	Qty	Description
BP010	2	6 1/2" Speaker 8Ω 10 watt
BP012	2	6 1/2" Speaker 4Ω 10 watt
BP013	3	8" x 5" Speaker 4Ω 6 watt made by E.M.I.
BP015A	1	5 1/2" full range 12 watt 4Ω speaker with matching grill. For small p.a. or in car use.
BP015B	1	30 watt, dome tweeter. Size 90x66mm JAPAN made
BP016	6	2200µf can type Electrolytic 25V d.c. computer grade made in UK by PHILIPS
BP017	3	33000µf 16V d.c. electrolytic high quality computer grade UK made
BP018	3	2000µf 50V d.c. electrolytic high quality computer grade made in USA
BP019	20	20 ceramic trimmers
BP020	4	Tuning capacitors, 2 gang dielectric a.m. type
BP021	10	3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA
BP022	5	Push-button switches, push on push off, 2 pole change over. PC mount JAPAN made
BP023	6	2 pole 2 way rotary switch
BP024	2	Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch UK made by LORLIN
BP025	4	3 pole, 3 way miniature rotary switch with one extra position off (open frame YAXLEY type)
BP026	4	4 pole, 2 way rotary switch UK made by LORLIN
BP027	30	Mixed control knobs
BP028	10	Slide potentiometers (popular values)
BP029	6	Stereo rotary potentiometers
BP030	2	100k wire wound double precision potentiometers UK made
BP031	6	Single 100k multitune pots, ideal for varicap tuners UK made by PHILIPS
BP032	4	UHF varicap tuner heads, unboxed and untested UK made by PHILIPS
BP033	2	FM stereo decoder modules with diagram UK made by PHILIPS
BP034	3	AM IF modules with diagram UK made by PHILIPS
BP034A	2	AM-FM tuner head modules. UK made by MULLARD
BP034B	1	Hi-Fi stereo pre-amp module inputs for CD, tuner tape, magnetic cartridge with diagram. UK made by MULLARD
BP035	6	All metal co-axial aerial plugs
BP036	6	Fuse holders, panel mounting 20mm type JAPAN made
BP037	6	In line fuse holders 20mm type UK made by BULGIN
BP038	20	5 pin din, 180° chassis socket
BP039	6	Double phono sockets, Paxolin mounted
BP041	3	2.8m lengths of 3 core 5 amp mains flex
BP042	2	Large VU meters JAPAN made
BP043	30	4V miniature bulbs, wire ended, new untested
BP044	2	Sonotone stereo crystal cartridge with 78 and LP styli JAPAN made
BP045	2	Stereo cassette record and play heads JAPAN made
BP046	4	6-0-6 4VA mains transformers, P.C. mount UK made
BP047	1	24V 750mA mains power supply. Brand new boxed UK made by MULLARD
BP049	10	OC44 transistors. Remove paint from top and it becomes a photo-electric cell (or P12) UK made by MULLARD
BP050	30	Low signal transistors n.p.n., p.n.p. types
BP051	6	14 watt output transistors. 3 complimentary pairs in T066 case (Ideal replacement for AD161 and 162s)
BP052A	1	Tape deck pre-amp IC with record/replay switching No LM1818 with diagram
BP053	5	5 watt audio ICs. No TBA800 (ATEZ)
BP054	10	Motor speed control ICs, as used with most cassette and record player motors
BP055	1	Digital DVM meter I.C. made by PLESSEY as used by THANDAR with diagram
BP056	4	7 segment 0.3 LED display (R.E.D.)
BP057	8	Bridge rectifiers, 1 amp, 24V
BP058	200	Assorted carbon resistors
BP059	1	Power supply PCB with 30V 4VA transformer. MC7818CT IC & bridge rectifier. Size 4" x 2 3/4"
BP060	1	Transcription record player motor 1500rpm 240V a.c.
BP061	5	6.35mm Mono jack plugs
BP063	5	6.35mm stereo switched jack sockets
BP064	12	Coax chassis mount sockets
BP065	1	3mtr Euro-mains lead with a matching chassis socket

MULTIBAND RADIO

VHF 54-176 MHz + AM CB BANDS 1-80

Listen to: AIR TRAFFIC CONTROL,

AIRCRAFT, RADAR

PUBLIC UTILITIES

RADIO AMATEURS AND

MANY MANY MORE

£15.95

POSTAGE £2.85

SQUELCH CONTROL

"RUBBER DUCK AERIAL"

RADIO and TV COMPONENTS ACTON LTD

21 HIGH STREET, ACTON LONDON W3 6NG

MAIL ORDER TERMS. POSTAL ORDERS and or CHEQUES

with orders. Orders under £20 add £3.00 service charge. Nett

monthly accounts to Schools, Colleges and P.L.C. only.

ACCESS + VISA. Phone orders between 9.30 & 12pm please

Phone: 01-723 8432 or 01-992 8430

Callers 323 Edgware Road, London W2

30+30 WATT AMPLIFIER KIT



An easy to build amplifier with a good specification. All the components are mounted on the single P.C.B. which is already punched and backprinted.

■ 30W x 2 (DIN 4 ohm)

■ CD/Aux, tape I, tape II, tuner and phono inputs.

■ Separate treble and bass

■ Headphone jack

Size (H.W.D.) 75x400x195mm

Kit enclosed: case, P.C.B., all components, scale

and knobs £36.80. post £3.50

(Featured project in *Everyday Electronics* April

1989 issue). Reprint Free with kit.

TV SOUND TUNER



In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are quite common and that really is quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder.

£29.50 + £2.50 p&p

As above but with built-in stereo headphone amplifier for the hard of hearing

You can tune into the TV channel you want while still receiving the picture on your TV set. In fact it is rather like a second television, but without the screen. So that the ordinary TV can be placed for everyone to see, and the volume on it can be comfortable for others, while the sound tuner can be placed where you can control it. You will need to plug in one of your own listening aids such as headphones or an induction loop to hear the sound. The tuner is mains operated, has 5 pre-selected tuning controls and can be used in conjunction with a video recorder.

Size: 270x192x65mm. £35.90 + £2.50 p&p

A.M. F.M. STEREO TUNER KIT



SPECIAL OFFER!

£8.95 Plus £2.50 p&p

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics

For ease of construction and alignment it incorporates three Mullard modules and an I.C. I.F. System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM-Ferrite rod, FM-75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to strict P.E. specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

Hi-Fi stereo cassette deck transport mechanism, complete with 3 digit rev counter and tape heads, 12V d.c. operation. Unused manufacturers surplus JAPAN made

£6.20 + £1.50 P&P 2 for £10 + £2.50 P&P

EXTRACTABLE HOUSING FOR YOUR CAR STEREO ★ SIZE DIN E ★ HANDLE INCLUDED ★ SPACE FOR MEMORY BATTERY ★ 4 OR 2 SPEAKER SYSTEM.

ENABLES YOU TO REMOVE YOUR VALUED STEREO FROM YOUR CAR (WITHOUT THE AID OF A HAMMER AND CHISEL, CHAINSAW ETC). £9.95 postage £2.50

UNDER SURVEILLANCE

Paul Chappell lifts the blinds surrounding the problems and solutions in electronic surveillance

SURVEILLANCE



A selection of off-the-shelf surveillance equipment available from Lorraine Electronics Surveillance. 1-3 discreet transmitter housings; 4,8,9,13-15,18 telephone surveillance devices; 5,12 amplifiers; 6,7,10,11,16,17 transmitters.

1: Electronics Bugs: theory and circuits

Before the clamp down on the sale and use of bugging equipment in the USA, there were over sixty companies supporting themselves entirely by the sale of such things. It couldn't happen here, could it? To find the answer you won't need to join some underground organisation — look no further than the pages of the Exchange & Mart, for heaven's sake! There it all is, openly advertised for anyone to buy.

In this and the following articles I'll be looking at some aspects of the surveillance industry and, since this is a practical magazine, giving you some circuits to try out for yourselves. You should be aware that, according to how you use them, you may fall foul of the law. A Paul's eye view of the current legal position follows but although the facts are basically correct, there's no way we can help you if you do something silly and get caught doing it. Let's face it, most people don't take at all kindly to being bugged and if you plant one in your boss's office, he'll give you the boot and have every right to do so. You may end up in court too.

On the other hand, if you use the circuits for a bit of fun, as long as you don't interfere with anyone

else's reception of VHF broadcasts, nobody will bother you — legally they could, but they'll be unlikely to do so (this again is Paul's opinion, you understand). Enough of the lecture. You're all big boys now, so off you go and enjoy the rest of the article.

The Legal Position

Although the planting of bugs and tapping of phones theoretically contravenes all manner of rules and regulations, hauling the 'buggers' through the courts doesn't seem particularly high on anyone's list of priorities. This can be attributed to a very low public awareness of the subject — the general consensus seems to be that you have to be Russian, a member of CND or a brewer to qualify for a bugging. Since most people are none of these, they don't feel particularly threatened by the prospect.

For room bugs, the current situation seems to be this: as long as you enter the premises by some legitimate means (that is, you don't resort to breaking and entering), plant your bug and then retire to a safe distance to listen, the naughtiest thing you have done so far is to contravene the Wireless Telegraphy Act.

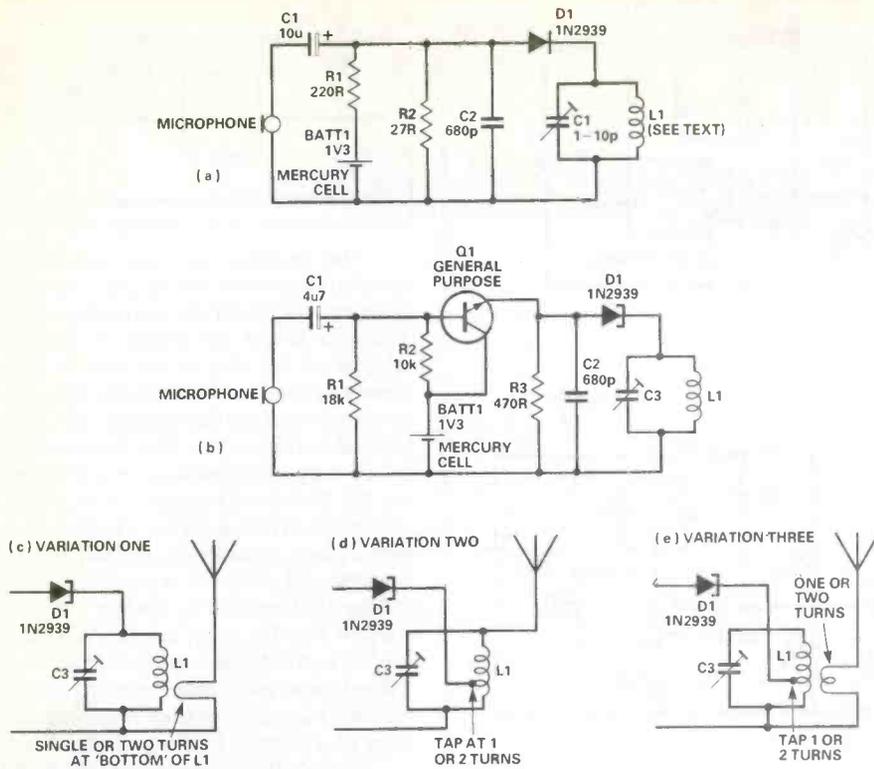


Fig. 1 (a) Tunnel diode microbug (b) Adding a buffer for a microphone (c,d,e) Variations on the circuit

If anyone is insistent enough to have you up in court, it's a slap on the wrist affair. A small fine and you're away.

The thing that is technically illegal is to make use of any information you acquire in this way. This is quite a tricky one because one of the semi-legitimate uses of bugging equipment is for internal investigations. If it is suspected that someone in a company is, let's say, giving away marketing plans to a competitor, the only way to prove it might be to bug his office or his home. The trouble is that if the information is used, even in court, there's the embarrassing question of where it came from. Those who use it are on the wrong side of the law too. The strategy of the good guys will probably be to confront the bad guy with the evidence and persuade him to pack his bags and go. It seems to work.

Tapping phone lines is another matter altogether. This comes under the 1985 Interception of Communications Act which protects letters, telephone calls and various other services licensed by the DTI — Vodaphone, for instance. The very installation of the equipment in the first place is illegal in the case of phone taps.

Having said that, the prospect of suffering the rigour of the law doesn't seem to deter those who make a living from such activities. One or two have even given blow by blow accounts of their activities for the TV cameras. No public outrage, no calls for a tightening of the law or the prosecution of the offenders. Just a mild curiosity at the wacky old things that some people get up to.

A recent development has been the attempt by James Cran to introduce a bill to control electronic surveillance devices. The yawns of his Conservative colleagues have been overwhelming, and although at the time of writing there's still the possibility of a second reading in a few weeks' time, for my money the whole thing will be gone and forgotten by the time you read this.

Room Bugs

These are the devices with the Hollywood superspy image — tiny microtransmitters, totally invisible if planted by the good guys, always leaving some telltale sign if planted by the bad guys. Somehow the Hollywood versions only pick up relevant information too. None of this 'What's for dinner?' or 'Have you seen the new Batman movie yet?' kind of chit chat. Always 'Right, let's talk about the secret plan. You know, the one where we drive into the nuclear widget plant at exactly ten o'clock tomorrow morning disguised as plumbers in the blue van, registration number ETI 1989 . . . You know the kind of stuff.

Real life ain't like that. The first difference, often quite disappointing to those with romantic notions about the business, is that most bugs aren't all that small. The reason is obvious when you think about it. If the bugging operation is going to be worth the aggro, the transmissions have to carry for a reasonable distance. If they only carry to the next room, you might as well just put your ear to the wall or use a simple microphone and tape recorder set-up. If the transmissions are to carry for any worthwhile distance, the bug needs to poke out 10mW or so, which requires a fair sized battery to supply the juice. And if you need a big battery, there's not a lot of point in going all out to miniaturise the electronics.

Tiny bugs do exist — all kinds of ingenious methods have been devised to overcome the power problem and to some extent the deficiencies of the transmitter can be overcome by using a super-sensitive receiver — but they tend to be temperamental, expensive (by which I mean very expensive) and unreliable. Those who earn their beans on toast from planting the things will, for choice, go for the more substantial and reliable ones every time.

Having said all that, Fig.1 shows a circuit that gives scope for being made as small as you could ever want it, simply by virtue of having very few

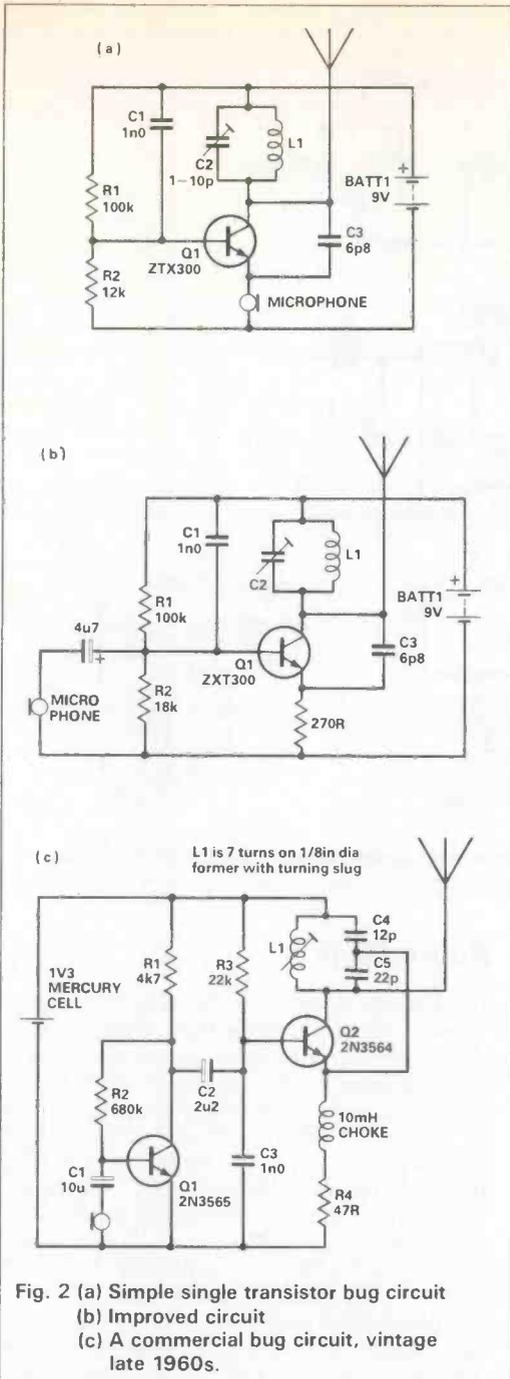


Fig. 2 (a) Simple single transistor bug circuit
 (b) Improved circuit
 (c) A commercial bug circuit, vintage late 1960s.

components. The RF oscillation is sustained by D1 which is a tunnel diode — it won't work with a 1N4148: R1 and R2 serve to bias the diode into the negative resistance region and the microphone modulates the signal by, in effect, shifting the bias point at audio frequency. The whole thing runs from a 1.3V mercury cell.

For the smallest possible size you could try tracking down a hearing aid microphone. These sometimes can be had from surplus component suppliers — if not, you'll have to go to a hearing aid manufacturer and pay the price of a new one. The tuned circuit C3/L1 can be made in a variety of ways. If you're building the thing into a fountain pen, for example, it may be possible to wind L1 around a former that slips into the body of the pen. At 3/8in diameter you'll need about five or six turns to hit the FM broadcast band. The rest of the circuit can be built long and narrow to slip inside L1. Otherwise, you can save a little space by making C1 a fixed ceramic capacitor of about 6p8 and using a small coil with a ferrite tuning slug for L1.

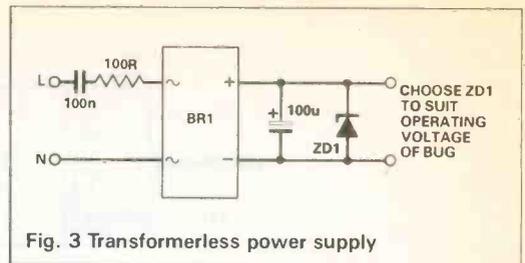


Fig. 3 Transformerless power supply

The antenna may need some experiment. A straight piece of wire will be fine — the output power will vary with the length, generally increasing as the wire gets longer but hitting various maxima and minima on the way as the ratio of wire length to wavelength varies. A few inches will do for a start. If you're going all out for small size, you can't worry too much about the niceties of tuning the antenna — you'll have to rely on any available metal surface to radiate the RF. The metal pen cap, for example.

If you decide to go for a longer antenna, begin with a piece about 2 1/2ft long and snip small pieces from the end until you hit maximum output. Use an ordinary FM receiver for the test — tune it to a clear spot on the dial, then adjust C3 until you hear a feedback whistle. Because the circuit is very crude, it will radiate to some extent at multiples of the C1/L1 resonant frequency, so keep checking for better results even after hearing the first whistle.

When installing the long antenna version, try to keep the antenna straight and vertical if at all possible. If not, don't curl it around. Tape it in a zig-zag. For best range, don't plant it close to the floor — the higher the better. And, if possible, put it near an external wall of the building — the less masonry the signal has to travel through, the stronger it will be. One last thing: bear in mind that anything you can pick up on an FM radio, everyone else in the area can too — including the buggee. It might just give the game away if he tuned across the FM band and heard ... himself! Best modify the receiver a little and use a frequency just outside the broadcast band.

Although the circuit of Fig.1a will work, a lot of improvements can be made without increasing the component count unduly. Buffering the microphone increases the modulation and so the sensitivity — a circuit for this is shown in Fig.1b. There are several ways of attempting to increase the output by tweaking up the matching between diode, tuned circuit and antenna. Figure 1c and onwards show various ways and means. They increase coil winding complexity but needn't increase the size of the bug unduly if you're careful. In each case the basic winding of L1 remains the same. Extra turns are wound over the top of the cold end for the antenna in variations one and three, and L1 is tapped at one to two turns in variations two and three. If you really want to go to town on the output stage, you can even add another variable cap

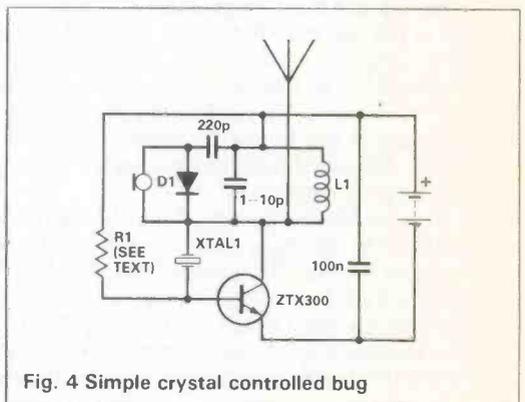


Fig. 4 Simple crystal controlled bug

across the antenna coil. The mods will all give varying degrees of improvement to the basic circuit, but if you're not an experimenter at heart, just stick to 1a or 1b. The circuit can be, and often has been, used in earnest.

Having gone into some detail over the tunnel diode circuit, here are a few transistor ones. For setting up, selecting an antenna and placing the bug, all the same comments apply.

First of all, Fig.2a shows the simplest possible circuit. Almost the simplest anyway — if you are willing to choose R1 by trial and error to suit the particular sample of Q1 you use, R2 can be missed out! The microphone has to be a dynamic of similar type — low impedance and low DC resistance — the latter because all Q1's current passes through the microphone itself. At the cost of an extra resistor and capacitor, Fig.2b is almost as simple.

Figure 2c shows a circuit that was commercially available in the USA until the hoo-hah over Watergate put a stop to such things. Legend has it that the whole thing, including battery, was packed into a volume not much larger than a sugar cube, which just goes to show how small components were in those days. With surface mount components it would just about be possible, although you'd need delicate fingers to wind yourself a tiny 10mH choke. Stick to the tunnel diode, I say.

With the higher voltage transistor circuits, you can do away with the antenna altogether by winding L1 around the edge of the PCB, or even by etching it onto the board. Two square turns about 1/4in on each side will do the trick. The range won't be as good, but you'll avoid the problem of where to put the dangling wires.

Although pretty basic, circuits similar to the ones already described probably account for over 90% of the bugs that are ever used. Most of the time nothing more complex is required. There are those odd occasions, though . . .

For long term monitoring, the power supply problem raises its ugly head again. Every house and office has at least two sources of endless power: the mains wiring and the telephone line. If either of these can be tapped, the bug is there for good. The phone line I'll put aside for the moment. For the mains, Fig.3 shows a convenient way to derive power. A capacitor can be smaller than the smallest mains transformer. The basic bug can be any of the circuits shown so far and the complete circuit can be built into a plug adaptor, a light fitting or whatever. If you have access to the mains, there's no need for radiated RF: the wiring can carry the signal for you. Just use any of the mains intercom circuits that are published from time to time, or get hold of a data sheet on the LM1893 carrier current transceiver (National Semiconductors Linear Databook 3).

For those with sufficient money and resources to develop exotic and impractical devices, all kinds of power sources can and have been tried. As an example, one source of power is the output of commercial radio stations. In most areas you can suck enough power from the air to drive a crystal earpiece, so why not use that very same power to drive a bug? Because it will have a transmission range of about six inches is as good a reason as any not to bother. But suppose you incorporate a very low current standby switch, store up the power when the bug is not in use and turn it on when the sound exceeds a certain threshold. In conjunction with a highly sensitive receiver this might just be on the borderline of feasibility. The next stage is not to rely on the background RF but to generate a strong RF field yourself. Then you have the great holy grail of the


surveillance industry: a completely passive bug. Undetectable because it sits there doing nothing unless activated from outside. No batteries to run down, so it's there for good. Worth the bother? That's not for me to say.

The other problem with long term surveillance is that the simpler bugs will drift off tune — either of their own accord, or because of a change in their environment.

The effects of somebody walking past might be enough to have you reaching for the tuning dial. Unless you have the patience of a saint and a massive coffee budget, you're not going to sit there with the headphones on just in case somebody speaks. Far better to have a tape recorder with voice operated switch and let the thing take care of itself. In this case a crystal controlled bug is called for — about the simplest circuit you can get away with is shown in Fig.4. Modulation is from a variable capacitance diode driven directly by a crystal microphone — not designed according to the highest standards, but it will work! R1 is best chosen on a trial and error basis (or select-on-test as we say in the trade — sounds much better, doesn't it?). Just pop a meter in series with the battery and select for a current of around 5mA. The battery can be any voltage from 1.3V upwards — the only component you'll need to change will be R1.

Beyond this you get to the real high tech stuff. Given access to any device known to man or the facilities and finances to develop bugs as complicated as you choose, there's no end to what might be done. There are very few occasions when anything more sophisticated than a plain radio microphone is really needed — the stakes are only raised when the bugger is aware of the possibility of being bugged and is likely to know how to track and destroy the things, or at least to detect their presence. In this case the battle can raise itself onto ever higher technical planes, with the bugs perhaps encrypting the sound — ideally to make it appear to be noise if picked up on an ordinary receiver — or perhaps lying dormant until activated by one event or another. Maybe it will transmit on a frequency which coincides exactly with that of a broadcast station, so that an RF frequency analyser in unskilled hands will not show anything out of the ordinary. The bug sound could then be recovered by subtracting the broadcast signal picked up by a second receiver from the sum of broadcast and bug picked up by one within range of the bug.

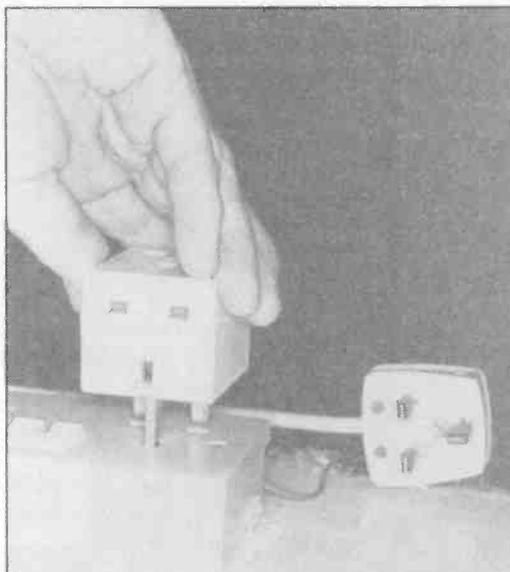Next time around I'll be looking at the other side: how to detect and locate bugs if somebody is unfriendly enough to try bugging you.



UNDER SURVEILLANCE

2: The Inside Story

Helen Armstrong

Mankind has been eavesdropping on its neighbour since long before the eave was invented. A hollowed-out mammoth tusk pressed to the party wall of the cave in 20,000 BC perhaps, or a hand-picked slave planted as a bathroom-suite accessory in ancient Egypt. The first true eavesdropper probably fell out of the rafters onto a far corclove of Hittites, doubtless to face a decisive decommissioning by their counter-surveillance team.

And so to the present day, when several tons of SR-71 screaming at Mach 3 through the troposphere mimics the achievements of stealth and silence — get in, get the guff and get out before they see you coming.

SURVEILLANCE

ETI is grateful to Lorraine Electronics Surveillance and Suma Designs for their help in producing this article. Photographs are courtesy of Lorraine.

For further information contact Lorraine at 716 Lea Bridge Road, London E10 6AW (tel: 01-558 4226) and Suma at The Workshops, 95 Main Road, Baxterley, Warks CV9 2LE (tel: (0827) 714478).

More convenient ways of finding out what foes and relations are up to are available over the counter — available as you have seen in this very ETI indeed. Whether or not you wish to actively partake, covert surveillance devices — ‘bugs’ — have entered legend as surely as the Trojan horse and Watergate.

Where would a spy be without his briefcase of miniature radio transmitters, where foreign policy without its regular expulsions of diplomatic personnel for undiplomatic behaviour?

All this is in the hands of Governments and not for the likes of us, but then the likes of us still have our targets, say those in the business. For the business is in erring spouses and conniving associates.

Lorraine Electronics Surveillance develops and markets both ‘surveillance tools’ plus counter-surveillance tools and services, a combination which director David Benn is quick to rationalise. Not, you would think, that much rationalisation is needed for producing bugs and de-bugs (nobody is surprised when a computer programmer carries out a similar process, after all) but surveillance has an air of heroes and villains about it, and offering both services can look like wearing the black hat and white hat at the same time.

Suffice it to say that any de-bugging consultancy is likely to be looking for rival bugs, as well as its own.

“Contrary to common belief,” says David Benn, “surveillance as such is rarely used for espionage or ‘spying’. Industrial espionage has been going on since the year dot, mostly by bribing someone — say a secretary or a junior manager.” Somebody who is under pressure to live up to a career image but doesn’t earn enough and might weaken in the face of a brown envelope full of used fifties. Sound familiar? — “It’s perhaps more prevalent today, when people in very responsible jobs need more money and where financial information is valuable. Loss of information is more dangerous than money or stock. Stolen information is invisible until your competitors have it.”

Result: managements suspecting that confidential information is going astray need to know where, how, and by whom. In other words, businesses are more likely to bug their own premises than the opposition’s.

Home Guard

“Out of thousands of customers, about 30% are large PLCs checking on the loyalty of their staff,” Benn reckons. “Junior staff are the least of the problem. They may have directors leaving to set up independently and taking company secrets with them, or there may be corrupt buyers taking bribes.”

He breaks operations down into three areas: “recording conversation under difficult conditions” — meaning without being observed; “environmental recording” — or monitoring whole rooms or offices; and telephone monitoring.

The concealed portable tape recorder is a spying staple. Let’s call it a classic case: Lorraine’s is built into a ‘recording briefcase’. Eschewing the obvious false base or sides, the briefcase has most of its electronics, including a microphone and automatic level controlled amplifier, built into the frame. The owner can then choose between a small standard micro-format cassette recorder which tucks out of sight behind the document compartment, invisible to casual observation and standard security checks. Tapes are easy to get hold of that will record for up to three hours, attended or unattended, open or closed, before the tape needs turning. Recording can be started discreetly from outside the case by radio control, or by sound activation.

In other words, the executive to look out for is the one who takes his briefcase to the gents during the second coffee break to turn the tape over. It is a handy alternative to relying on the Minutes to record what was actually said.

Monitoring conversations that you are not supposed to overhear is easy if you can get access to the room in question. Small recorders can be hidden easily but there are maintenance problems, especially for long-term eavesdropping. Tape recorders can click or rumble, tape needs collecting and changing. Radio transmitters have the advantage that once in place they can be left almost indefinitely. Most bugs ‘discovered’ in buildings are long dead and abandoned, found by accident when the place is refurbished.

Lorraine supplies VHF and UHF transmitters built into solid-state desktop calculators, fountain pens, 13A mains sockets and adaptors, indeed any device which does not generate noise of its own (such as a typewriter). If hardware provides its own mains or battery supply, so much the better. The devices use typically around 5mW and, although ‘domestic band’ transmitters are available, these could be picked up on passing car radios.

“We advise clients to go up on the air bands where nobody will hear them,” says Benn. VHF transmitters are available in the range 129.448 to 139.97 MHz and UHF transmitters are available in the range 390 to 450MHz.

Domestic band devices typically use the FM broadcasting band. The advantages are that the transmitter circuit will be very simple and receivers readily available. The disadvantage is that it is easy to check whether this sort of bugging is taking place. Also the transmitted signal occupies a wider bandwidth, making it more susceptible to detection, so it could appear on a local household radio set.

The air band transmitters have the advantage of being narrow band FM, and since the aircraft FM signals are only an echo, you can hear the planes but they can’t hear you.



No Jam Today

One hears about radio stations and other transmissions being jammed by hostile agencies, but jamming is not used by respectable security agents, for good reasons. Besides being highly illegal and very antisocial, it's a dead giveaway.

"If you know what frequency you are jamming on, it is very easy", says Benn, "but if you are being bugged, the chances are you don't know what frequency and can only jam broadband, which will interfere with anything in the area. We would not do it, or allow our customers to do it."

Phone tapping is another area surrounded by myth, some of which is true. If you have a rash of calls which are wrong numbers, or have no apparent caller when you pick up the receiver, or a sudden apparent increase in the number of engineers or telesalespeople on the line, you may be being bugged. It is more likely that the lines are playing up, or the double-glazing world is having a sales push. Crackles or buzzing is unlikely to mean bugging, at least not by the police or government. On the contrary, official bugging is likely to guarantee you the cleanest line in the neighbourhood.

Tapping usually means an interface which switches on a tape recorder whenever the phone is in use. The tape recorder itself can either be triggered by the change in line current or voltage when the receiver is lifted or by vox — the voice itself.

'Bugging' implies a transmitter connected to the line, or mounted in the telephone socket itself. Drawing a significant current from the line to operate the transmitter would interfere with the proper operation of the telephone — doubly so if the current drain continued when the receiver was down. It is for this reason such devices must be very low powered. This, says Lorraine, restricts their range to about 100 feet (worst case). On the plus side, once installed they can be left to get on with it, and only operate when the telephone is in use. No batteries, no tapes.

An *infinity* device can operate over international line distances by holding the line open once the handset has been replaced, allowing the room beyond to be monitored without the occupant's knowledge.

A similar means of holding open the line for telephone lines serving high-sensitivity buildings is mentioned in certain recent 'spy-and-tell' memoirs.

The actual method and site chosen for a bug will depend much on whether the premises belong to the client (giving free access) or to an adversary where bugging must be done by stealth and with a minimum of after-sales service.

There are other ways of getting information. RF emissions from computer monitors, peripherals and cabling has received a lot of publicity recently. A van equipped with a fibre-glass top (or some other structure transparent to radio frequencies) and appropriate receiving equipment parked outside an office block can frequently pick up the exact image displayed on a computer inside the offices. This is a leak which has only come to light with the proliferation of desktop terminals.

'Tempest attack' is a name adopted for this actually non-invasive method. It usually involves picking up harmonics of the line and frame syncs from a monitor on a low frequency receiver, and picking up harmonics of the video on a VHF or UHF receiver. Sync frequencies of 50Hz and 15625Hz do not transmit far, but their harmonics interfere with radio reception, like it or not. Similarly baseband video, covering 50Hz to 5MHz typically, contains high frequency harmonics which transmit over a considerable distance.

Lorraine provides an EMDAR (Electromagnetic Data Analysing Recovery unit) which is not used for stealing information of course. It consists of a scanning receiver covering 25MHz to 2GHz with 100 memories which automatically store the frequencies of the strongest signals. There is also a display on which the strongest received signal can be displayed. In this way the offending computer can be identified. It is handy for demonstrating to customers that data can seep out in ways unthought of. The device costs £15,000.

"This is something that can only be used either for espionage or to prove espionage can be effected," says Benn. "We market it on restricted sale. All the customers who have bought this from us are bona fide security services or public bodies."

The idea is to find RF leaks, trace the source and then provide screening — from individual components to the whole room — to stop them. Companies can also hire the EMDAR and do a check on their own computers, and then call in the security company to carry out screening.

Tempest-proof terminals and PCs are available, according to trade press, but only to Government approved companies. The rest must devise their own security measures or risk data theft. Preventing unwanted radiation from a display is not as simple as it might at first appear. The electronics can be housed in an earthed metal case and all wires in and out of the case screened. The screen for the cathode ray tube is a mesh — about the best protection possible without preventing anyone from seeing the display.

Other obvious means to minimise radiation would include band limiting signals to minimise harmonics and transmitting antiphase signals to cancel such radiation as remains. There must be more to it than this, or the availability of such terminals would not be restricted.

Debugging is an industry in its own right. William Parsons, who runs Lorraine's counter-surveillance service, reckons that there is no easy way to find the hidden ear.

"Counter-surveillance consists of going in with the correct equipment and looking for devices, checking for unusual cables, testing telephone wires and looking for transmitters or hard-wired micro-



phones. The attitude of the person who heads the team — ours and the clients' — is crucial. For instance, we probably carry more equipment than the average counter-surveillance company, and I don't trust in equipment alone, so we do a full physical search as well." Finding electronics devices by electronic means is not straightforward at the professional level.

When high-level meetings are involved, the CS team will do a *sweep* first as described, and then monitor the location for RF signals during the meeting.

Many types of unauthorised device get attached to the telephone system. Lorraine now uses a telephone line analyser which was developed to try to detect or imply the presence of every kind of telephone tapper and bug known to Parsons, in one box.

"Most analysers are not geared to find everything accurately. This one has tests which people say don't find things, such as time domain reflectometry — they don't use them. I know it does: with the 500 metre version, a time domain used in the building will see any series device and 50% of parallel devices connected."

A time domain reflectometer sends a pulse down a line and looks for reflected echoes. A perfectly uniform transmission line which is properly terminated will give only a very low level echo, but if anything is attached to the line its impedance at that point will be changed, and a more obvious reflection will be generated. The time between the sent and received pulses gives an indication of how much cable is between test instrument and tap. This is only an indication, because the rate of propagation of a signal along a transmission line is influenced by the line characteristics, and may be about 70% of the speed of light.

The way to avoid a tap from being detected by a time domain reflectometer is to load the line very lightly with a very high impedance parallel load taking an undetectably small voltage and current, as a pure audio lift-off. Bearing in mind that a telephone line is not a uniform transmission line but has built in irregularities, such a load applied to the line will not be detectable. Of course, a series connected tap will almost certainly disturb the line enough to be detected.

The telephone bug detector also has a function for measuring line capacitance — an increase means that extra cable has been added. It also has a low frequency receiver, an active line test and a line sweep test. The receiver is to detect carrier signals transmitted along the line, and the active line test measures the line voltages with the phone on and off hook. A bug powered from the line may disturb these voltages. The line sweep test applies a voltage to a disconnected line. The voltage is varied from 0-10V and accurate voltage and current meters indicate if any devices start drawing power.

Export

Much of Lorraine's equipment is sold for export only, as most RF surveillance devices are not type approved, putting them beyond the necessary licensing required for RF in the UK. Likewise, attaching listening devices to the telephone system is in breach of various acts covering everything from interception of communications to interfering with BT wiring. It is not illegal to supply the stuff, only to use it. But clearly much is destined for home use. Do Benn and people like him get aggravation from *The Authorities* on this front?

"Authorities are among our customers as well," he emphasises. "We provide an excellent service for industry and commerce and this is recognised by

certain people. There are certain situations in which electronic surveillance is the only option available." He can't be specific, only saying "I think there is a general recognition that we benefit managements rather than harm them."

Why isn't this stuff type approved? The answer will be familiar enough to anyone developing RF or telecomms equipment. "Because it would be horrifically expensive." But there is a simpler, more poetic explanation in the nature of the goods. RF equipment is restricted by law because it can cause catastrophic interference to other services. Bugs, by definition, must be invisible.

"If someone knows you're using it, you're not using it correctly," says Benn. "Surveillance devices, including those for telephones, are typically narrow band, about 5mW — nuisance-free. We sell devices across the board, but customers are strongly advised not to use broadband FM products. We advise customers never to use domestic frequencies."

What about the legality of eavesdropping?

"There are no privacy laws in the UK" — another subject of much public debate in recent months — "although the situation is different in the United States," Benn points out.

So you can eavesdrop to your heart's content, if you can get away without prosecution under the various Wireless Telegraphy and Communications Acts. And if you conceal a wholly legal tape recorder in a rival's premises, there is always *Theft of Electricity* and possibly *Trespass*. In practice, prosecutions rarely happen, for reasons we will shortly see.

Tim Jinks of Suma Designs provides design and consultancy on covert surveillance. He looks on international spying with a practical eye.

"It goes on. Ministries won't admit it, but it goes on in a big way and it's good for national security. It's mostly propaganda — we like to hear that everything's OK."

But the person in the street, he says, feels guilty about using bugs and doesn't like the idea until they have a specific problem which they are desperate to solve.


"It's like contraceptives. They won't come in and say I want to bug my business partner or I think my wife's doing this and that, but they do end up telling you quite a lot." If the company suspects unethical use, he says, they will decline to supply by winding the price up or claiming that their services are unsuitable.

Telephone conversations are best for monitoring, says Jinks. People feel vulnerable in the open and room systems must be voice or remote activated with the risk of noise from the machinery. People say more on the telephone — "most bad deals are done on the phone". Likewise RF transmitters are more trouble-free than local tape recorders, much easier to conceal and can be left for ever.

How easy are bugs to detect? I asked. "When was the last time you looked under your desk?" he countered, adding that I should be looking upwards under the rim, not downwards into the floor filing system.

Touché. This is the low end or cheap and cheerful approach — people are always talking about being bugged, but they rarely suspect it. In that respect, he says, people are gullible.

"The low end is easy to find visually, but the target is unlikely to try and find it. On the other hand, taps can be done in various positions along the line. In theory you don't have to go into the building — up a telegraph pole or into the street junction box." Yes, in theory, the chaps in overalls and hard hats poking about in the street junction box could be tapping your phone. "In that case, you have no chance visually."

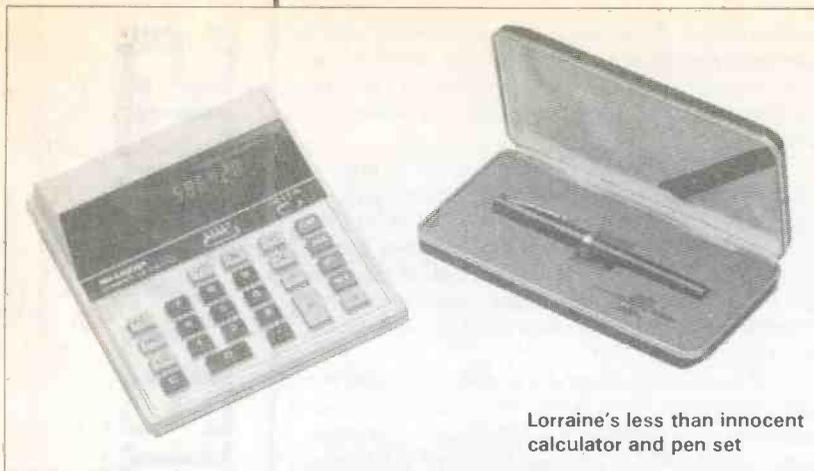

Lorraine's less than innocent calculator and pen set

Open Door

On the other hand, most people at the 'high end' in the professional bugging category are wise to the possibilities. Many companies have their own counter-surveillance officers. Concealing room transmitters from people who are likely to be suspicious must be done with care. Cavity doors are a gift — just knock a piece out of the top rail, weight the aerial wire to that it hangs straight down, fix the thing in and leave it. There's an air gap at the top, acoustics are usually perfect. There is no real need to stop up the hole unless the housekeeper is going to check the top of the doors for dust.

Plasterboard ceilings could be called the modern equivalent of eaves where eavesdropping is concerned. Roll up the carpet, rip up a floorboard, gouge out the plasterboard until about 1/16in is left (something of an art) and leave the device. A transmitter could be on a board the size of a postage stamp, including batteries — it won't drop through the ceiling. Ideal. Coffee tables with false bottoms are good for meaty long-life battery packs, skirting boards are almost purpose-built for concealing extra wiring (especially when tack-down carpet-fixing strip is added), and clock radios provide not only their own mains power but aerials as well. Not so good when the radio is on, but otherwise ideal.

The home and office would seem like an audio paradise for the potential secret-snatcher. Except the bathroom. Running water is pure white noise, the perfect, no-nuisance, all-purpose jammer. Perhaps the most successful bad deals are done in the WC.

Ripping up floorboards is only a reliable option if the customer owns the building — even then, access can be a problem. "I've never been given a disguise other than a corporation name tag," says Jinks. "We say give us free time to install it. We mustn't be seen and we mustn't be working against the clock."

Sometimes the ethics have to be viewed at an angle.

"We were asked to do a house of ill-repute — saunas, solaria, the lot once," he admits. "We thought the client was the vice squad, but it turned out to be the owner checking if the girls were doing a bit of private business."

Recorded information will not be accepted as evidence by courts unless the recording was done on a sealed tape provided and signed for by a solicitor. Clients and targets rarely meet in court.

"Once somebody is confronted with the fact that somebody else knows what he's up to, they usually back down," says Jinks.

"They could probably prosecute the person who bugged them, but people don't know the law inside-out and if they do, there are usually things they want to keep hidden."

He tells of a man who bugged his wife and later confronted her with his findings. "She phoned the DTI and he was done under the Wireless Telegraphy Act. He got a stiff fine but the information he got enabled him to carry out investigations which saved him thousands of pounds in a divorce case."

A Hard Life

De-bugging premises is the real challenge.

"The bugger has it much easier than the debugger," Jinks says, once challenged by a television company to hide some bugs and then have a counter-surveillance company locate them — all on camera. The debugger failed.

Even when devices are activated, the power involved is very low and the frequencies in a sophisticated device are obscure, although 100 to 140MHz FM remains popular — "up to 90%".

A good commercial bug tracer uses a phase locked loop high frequency receiver to sweep across a comparatively narrow band, searching for harmonics of the lower frequency bands. If a signal exceeds the detection threshold, it gives a numerical code which the operator can then enter, locking the device in on the signal. Once locked on, the receiver can analyse the signal and demodulate AM or FM, and check for subcarrier.

Another device tunes slowly through the lower bands searching for the signal rather than its harmonics. It gives a click like a bat, which can be picked up and re-transmitted by a bug. The timing of the return click indicates how near the bug is to the tracer.

But Jinks has higher ambitions than installing his own bugs, "hard, dirty, boring, down-on-the-knees work," and winking out other people's — he wants a better bug.

"Frequency hopping is the real challenge. Every time a transmitter is about to make a frequency jump, it sends a signal to lock its receiver on to a new frequency. You'd have a job catching that."

The real love of his drawing board is 'time slot transmission', where the transmitter monitors for 30 seconds and then compresses the information and transmits it in a millisecond. Properly synchronised, the receiver would hear a smooth conversation. "Nothing on earth can detect that".

What are the chances you are on the right frequency and, if you are, what do you hear?

"You still have to decode it. The idea's still on the bench." He adds that the battery size will have to come down, as well. Of such things is electronic development made.

Like it or not, listening to other people's secrets clearly has a social role. Benn (who may be being optimistic) reckons that about 1% of products sold are mis-applied — used for theft of information that does not rightfully belong or appertain to the client. This provides a useful justification for the counter-surveillance consultancy, if any justification were needed. Company managements are more likely to be searching for outsider bugs than their own — the massed staff of ETI, for instance, have yet to march on Argus Towers searching for management bugs. In an open-plan office you can hear every blessed thing everyone says anyway.

This didn't stop me asking David Benn whether he would sell bugs to people like me. "Fleet Street?", he said (kindly), "they certainly rank among our more interesting customers. What would they do without us?"



Wizard Kit-Packs

THIS MONTH'S WIZARDRY
100 Linotronix 'The Lights Fantastic' RL4850 5mm Red LEDs at **£8.50**

GEC STEREO CASSETTE UNIT
Record/Playback Dolby. Speed 4.75cm (1 1/2 in) per sec. 40-12,500Hz. Twin VU meters. With service manual. Brand new! **Price £12.00 or 2 for £20.00 p&p £3.00**

WIZARD PSU KIT
138volts dc at up to 10amps. Contents of the kit. 1 off main PCB. 1 off 12v dc fan. 1 off 15V Zener. 1 off 25 amp bridge rectifier. 2 off 10,000 µF electrolytic. 1 off 100 ohms w/w resistor. 2 off capacitor clips. 2 off fuse holders. 1 off mains transformer. 1 off mains filter. 1 off mains switch. 1 off heatsink. 1 off set of data sheets **Price £25.76**

IN THE WIZARD'S DEN
We have, from time to time, the following new and s/h stock: Printers, Monitors (Mono/Colour), PSUs Valve Amps, Lots of odds and ends.

MORE DATA — Send a 19p Stamp for Latest List.
Ring the Wizard on 0225 706886 Fax 0225 708594 for more information or a visit to the works.

PAYMENT
Access, Cheque, PO and Cash. Post and packing on components £1.50 or £1.00 for orders over £20.00. Please add VAT to total.

MERLIN SYSTEMS

Merlin Way, Bowerhill Trg Est, Melksham, Wiltshire SN12 6TJ

8031 64180 80188 LOW COST CONTROL MODULES

Module	CPU	RAM	EPROM	I/O	Cost from
uE31	8031	32k	32k	40	£45.95
uE180	64180	32k	32k	48	£69.95
uE188	80188	32k	32k	48	£79.95
uE — BPS 5 volt P/S — Backplane — RS232					£49.95
uE — OPTO 8 channel Optically isolated input					£59.95
uE — RLY 5 Channel Relay board					£39.95
SB51 8031 Cross Assembler — PC Host					£39.95

GNC ELECTRONICS

Tel: 0379 644285

Unit 2B Gilray Road Diss Norfolk IP22 3EU



HOBBYKIT introduces

The smart kit range of over
120 electronic kits

Each smart kit has been tried and tested
having been available in europe for the
last 8 years

SMART KITS ARE EDUCATIONAL

SMART KITS ARE RECREATIONAL

**NO PRIOR ELECTRONIC
KNOWLEDGE IS NECESSARY**

All you need is a soldering iron everything
else is provided in each blister packed
smart kit

Comprehensive catalogue available
including *special* introductory offer

Please send 28p s.a.e. to:

HOBBYKIT LTD

UNIT 19 CAPITOL INDUSTRIAL PARK
CAPITOL WAY LONDON NW9 0EQ
FAX: 01-205 0603

METEX & TEST LAB INSTRUMENTS YOU PAY TRADE PRICES!



3 1/2 AND 4 1/2 DIGIT Dmms

ALL WITH CONTINUITY TEST (★ With Capacitance + With Hfe ○ With Freq.)

PRO SERIES METEX

3 1/2 & 4 1/2 DIGIT

All With Case. 20A AC/DC

17mm Display (3800 12mm)

3800 32 Range 0.5% (+) **£29.40**

3610 30 Range 0.3% (+) **£38.86**

3630 30 Range 0.3% (++) **£46.90**

3650 30 Range 0.3% (+++) **£50.90**

3650B as 3650 with Bargraph **£57.60**

4630B 4 1/2 Digit 30 Range Data **£69.68**

Hold 0.05% (++) **£72.36**

4650 as 4630 Plus Range Freq.

STANDARD SERIES

3 1/2 DIGIT 12 mm DISPLAYS

2315B 17 Range 10 ADC **£19.43**

2318B 23 Range 10ADC (+) **£22.78**

2335 31 Range 10A AC/DC (+) **£26.80**

2325 32 Range 10A AC/DC (++) **£29.40**

2355 32 Range 10A AC/DC (+++) **£33.50**

2365 38 Range 10A AC/DC (+++) **£36.00**

Plus Logic Probe

Also Metex M80 21mm Display


3 1/2 Digit Autorange. Datahold (°) **£59.92**

TEST INSTRUMENTS

3000 LCR AC Bridge	£93.80	TE220 1 MHZ Audio Generator	£87.00
M3002A AC Millivolt Meter 1MHZ	£80.40	3300 Autorange Digital Cap. Meter	£64.00
2020 500 KHZ Function Generator	£85.76	6100 Signal Tracer/Injector	£52.30
4162AD 150 MHZ Fr Gen. Plus 6 Digit Counter	£154.00	5250 150 MHZ 7 Digit Frequency Counter	£64.50
2603AD 1 MHZ Af Gen. plus 6 Digit Counter	£159.00	08T5M 5 MHZ Bench Scope	£144.00
TE200 150 MHZ Rf Gen. (350 MHZ Harmonic)	£80.00	243 0/24V 0/3A Variable PSU	£50.65
		245 0/24V 0/5A Variable PSU	£63.65
		154 4/15V 0/4A Variable PSU	£36.05

"POCKET" TEST INSTRUMENTS

F20 Dual Scale Sound Level Meter 120dB	£33.87	302K LCD Temperature Two 1/P	£34.74
225V VHS Video Head Tester	£30.39	3900TD LCD Dmm With Dwell And Tach Ranges	£49.58
1065 Digital Lux Meter - 3 Ranges	£47.78	KT50 LCD 8 Range Capacitance Meter	£33.50
07 Logic Probe	£6.10	6060 LCD Digital True Power Meter	£64.00
M625 Logic Probe/Pulsar	£14.74	6KW 19	£64.00
300/310 AC Clamp Meter 600A/300V/Resis	£32.83	2070 19 Range Multimeter 10ADC + Buzz	£11.35
M265 Add on AC Clamp Probe for Dmm's	£16.48	2030ET 27 Range 10A AC/DC. Cap. Hfe Temp. Buzz	£35.30
501 Electronic Insulation Tester 500V	£53.00	505DE 41 Range FET mm	£25.33
504 Electronic Insulation Tester 1000V	£65.00	0M5 Wallet Autorange Dmm	£17.95
K0M6 TR Dip Meter 1.5 to 250 MHZ	£45.02	YF120 Pen Type Autorange Dmm	£29.21
1062 LCD Temperature & data hold	£35.50		

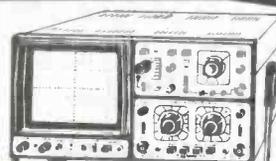

**AUDIO-ELECTRONICS ARE
INSTRUMENT DISTRIBUTORS FOR
HAMEG • FLIGHT • BLACKSTAR
• ALTAI • THURLBY • THANDAR
• CROTECH • LEADER AND HITACHI
PHONE FOR BEST PRICES.**

TELEPHONE YOUR ORDER WITH VISA/ACCESS
OPEN 6 DAYS A WEEK FOR CALLERS

ADD 15% VAT
(UK ONLY)

AUDIO ELECTRONICS


301 Edgware Road, London W2 1BN
Tel: 01-724 3564 Fax: 01-724 0322
Sales office 01-258 1831

TRADE/EDUCATION ORDER ACCEPTED.

EDUCATION AND QUANTITY PRICES AVAILABLE

**INSTRUMENT
CATALOGUE
WITH
DISCOUNT
VOUCHERS
REF TG**
Send A4 SAE
(£1.00) or
£2.00 UK
for full
CATALOGUE

... AND THEN THERE WERE TRANSISTORS

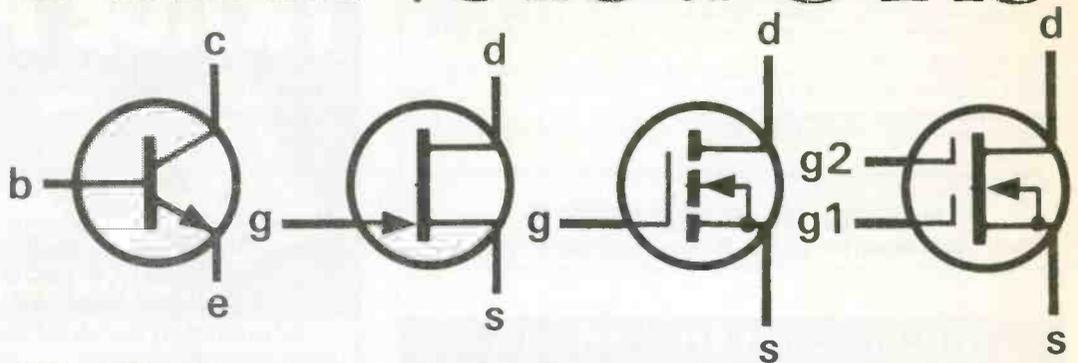

John Linsley Hood continues his semiconductor analysis with the evolution of the transistor

Having dealt with the range of semiconductors and how they are produced, we now move on to the basic p-n junction technology and how this has been extended to provide a whole family of amplifying and switching devices.

Point Contact Diodes And Transistors

The point contact diode is a device of venerable age, dating back to the 'crystal and cat's whisker' types of early radio receivers, and coming into commercial use with the small silicon and germanium diodes used in war-time radar gear.

The physics of its operation had been worked out during the 1930s and it was known that a metallic point in contact with the surface of a semiconductor

would cause a 'depletion zone', especially if reverse biased. This is shown in Fig. 1a.

This led Bardeen, Brattain and Shockley of the Bell Telephone Labs to try the experiment of bringing another sharp edged conductor in contact with the base semiconductor slab, as shown in Fig. 1b, which happened to be next to a reverse biased probe. Lo and behold, the current which was injected by the emitter probe into the depletion region was swept up by the collector.

This has given us both the terms we use for the electrodes (emitter, base and collector) and also the circuit symbol we use. Point contact transistors were never much more than museum pieces, but once the idea had registered, better devices were soon made.

Junction Transistors

Although we use the same names for its electrodes and the same circuit symbol in drawings, the modern bipolar junction transistor is a very different device, and will usually be made as shown in Fig. 2, starting with a very high purity single crystal slice of silicon.

In the case of an npn transistor, the crystal slice will contain a carefully controlled proportion of an n-type impurity, usually either phosphorus or arsenic, and a further dose of n-type impurity will then be diffused into the rear surface to provide an n+ layer for the collector contact.

A thin p-type layer will then be 'epitaxially' (one sided) grown on to the upper surface. By a process of masking, etching and vapour phase diffusion, a series of fairly heavily doped n+ patches will be diffused into this upper face, which after metallising and slicing up into tiny dies (0.5mm square for a typical small signal device), will give individual transistors that look like Fig. 3.

If the collector is biased positively with respect to the p-type base region the depletion region will extend all the way through the base layer and because it is a reverse biased junction, only a very small leakage

TRANSISTORS

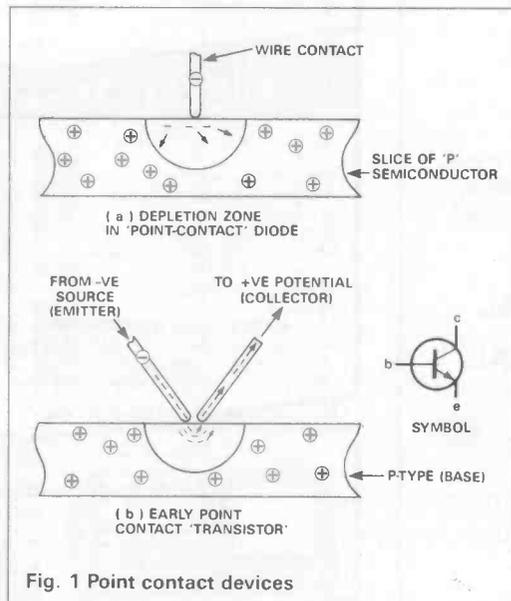


Fig. 1 Point contact devices

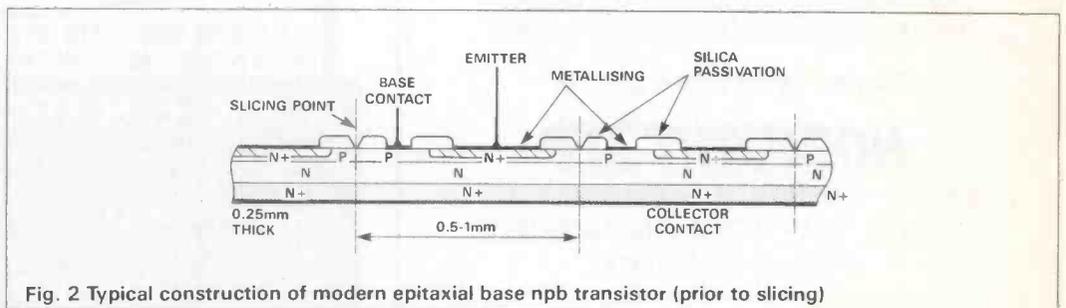


Fig. 2 Typical construction of modern epitaxial base npb transistor (prior to slicing)

current will flow.

However, if the emitter is made negative with respect to the base, or if the base is made positive with respect to the emitter (which amounts to the same thing once the forward voltage exceeds the pn junction potential barrier) electrons will flow from the emitter into the base, and nearly all of them will promptly be swept up by the collector.

With good geometries and careful control of impurity levels, upwards of 99% of the emitted electrons will be captured by the collector. Looking at it another way, less than 1% of the base current will control 99% of the collector flow. If the base is not forward biased with regard to the emitter, neither emitter nor collector current can occur.

The same argument will apply for pnp transistors if one substitutes the concept of 'holes' for electrons.

The way that the collector changes as a function of base voltage and collector voltage, for a typical junction transistor is shown in Fig. 4.

Junction Field Effect Transistors

In principle, this is just about the simplest semiconductor device there is. Its action depends upon the way the depletion zone at a pn junction will grow wider or narrower as the reverse voltage is increased or respectively decreased.

So, if we take a thin slice of n-type silicon, connect a terminal at either end and diffuse a couple of p-type (gate) regions on either side of it, as shown in Fig. 5. The possible channel of non-depleted silicon

(the only kind through which current can flow), can be made either wider or narrower by changing the negative bias applied to the gate.

This allows the current flow through the device to be controlled by the gate voltage, in just the same way as the anode current of a valve can be controlled by the grid voltage. Also like a valve, the gate electrode is normally non-conducting, unless it is biased in a 'forward' direction.

The only minor complication in this device is that the voltage at the 'drain' electrode will increase the reverse bias on the gate with respect to the drain, and make the shape of the depletion zone lop-sided, increasing in thickness at the drain end Fig. 5.

If more than a few volts is applied to the drain, the gate depletion regions will tend to increase so that they 'pinch off' the channel entirely. When this happens, the voltage drop due to current flow at the source end of the channel will disappear leaving only a narrow neck of channel as shown in Fig. 6, and then electrons will tunnel through this.

Because of the way in which the pinch-off becomes tighter as the drain voltage is increased, the drain current remains constant with increasing voltage, as shown in Fig. 7a. A fairly typical drain current vs gate voltage characteristic for an n-channel junction FET is shown in Fig. 7b.

Two final points about junction FETs. Firstly, the gate region is just a pair of quite normal junction diodes, they are *not* prone to damage due to static electricity any more than any other PN junction. Static is a problem only with insulated gate type MOSFETs.

TRANSISTORS

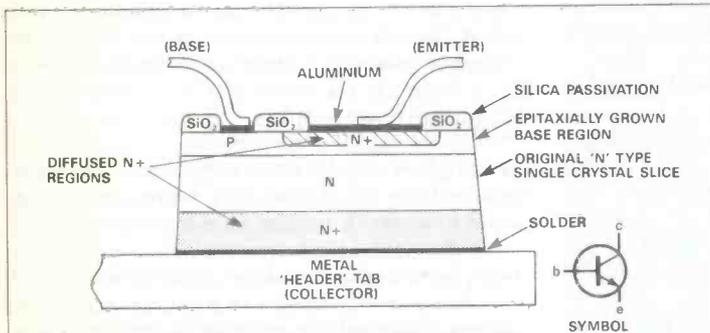


Fig. 3 Section through npn epitaxial base transistor

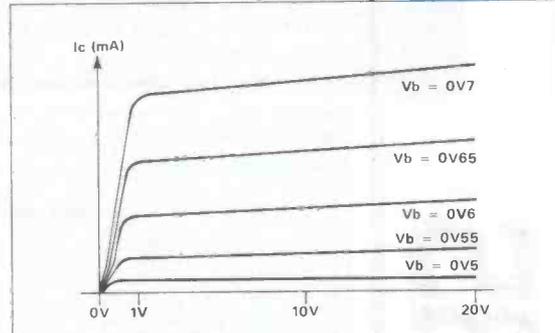


Fig. 4 Junction transistor b/c voltage characteristics

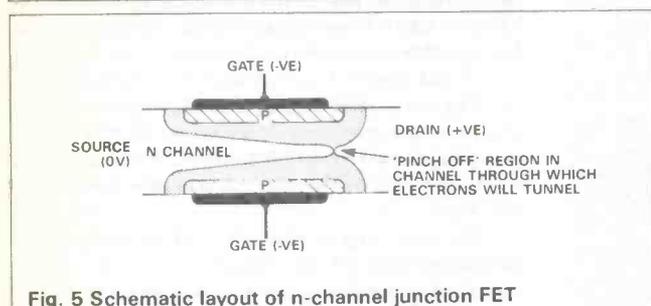


Fig. 5 Schematic layout of n-channel junction FET

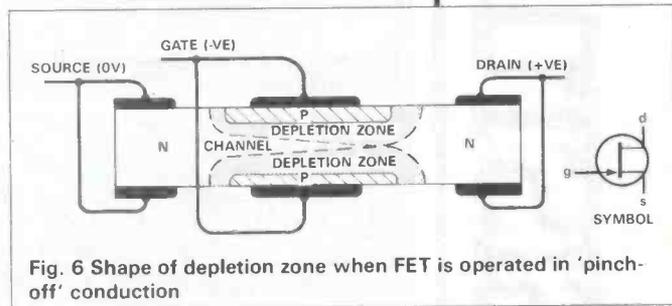


Fig. 6 Shape of depletion zone when FET is operated in 'pinch-off' conduction

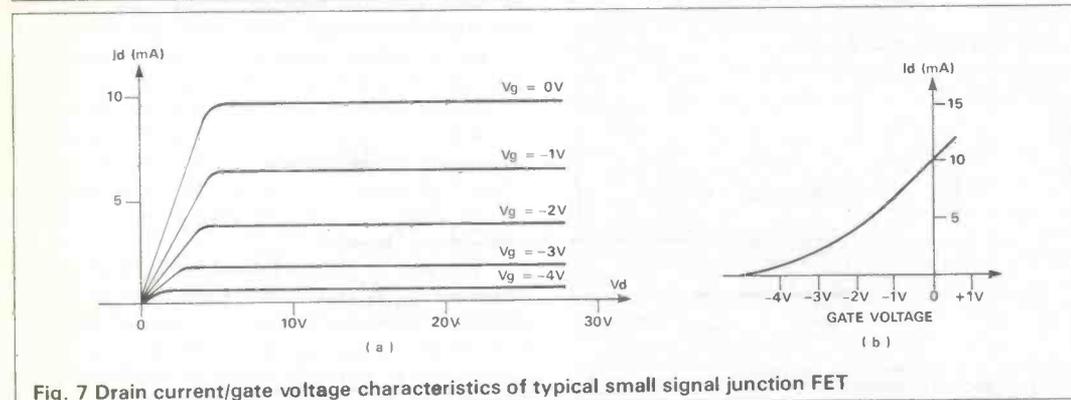


Fig. 7 Drain current/gate voltage characteristics of typical small signal junction FET

TRANSISTORS

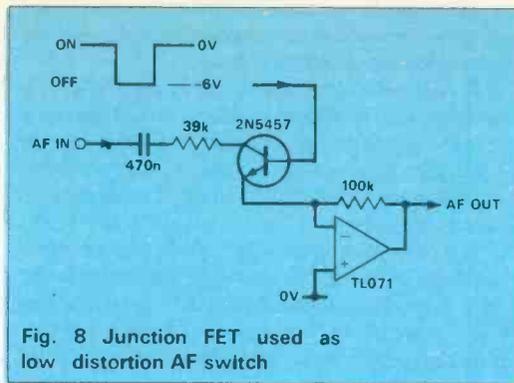


Fig. 8 Junction FET used as low distortion AF switch

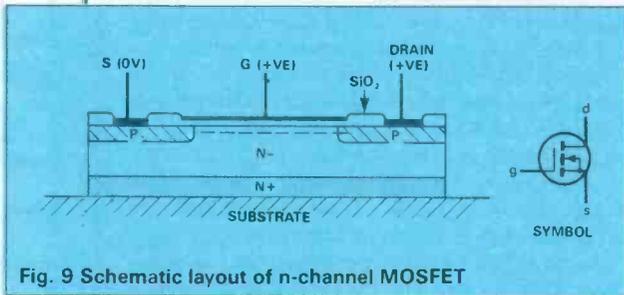


Fig. 9 Schematic layout of n-channel MOSFET

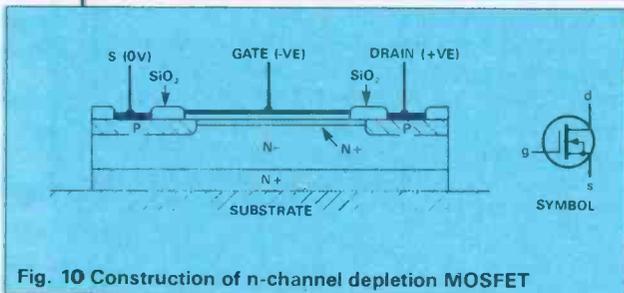


Fig. 10 Construction of n-channel depletion MOSFET

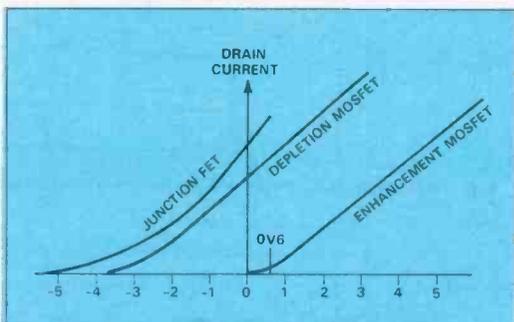


Fig. 11 Comparative characteristics of FETs and MOSFETs

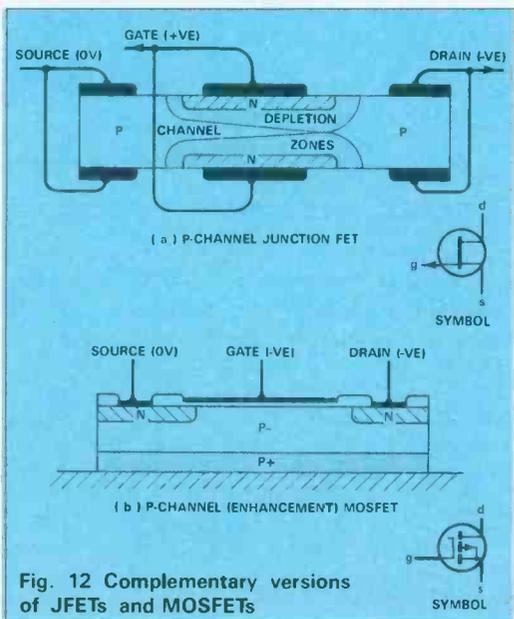


Fig. 12 Complementary versions of JFETs and MOSFETs

Secondly, the capacitance between gate and drain will be a few picofarads, but rather more between gate and source because the depletion zone width is less at this end. Like any other pn junction the depletion zone, which acts like the insulating dielectric layer in a capacitor, will vary with voltage — and so will the capacitance across it. This is a phenomenon which occurs in all reverse biased p-n junctions and is exploited in 'varicap' diodes.

Owing to the relatively long and thin conducting path from source to drain, the conducting resistance of junction FETs is fairly high. This varies from a few hundred ohms typically in the 'on' state, to many megohms when turned 'off'. They can be used as switches in an audio channel but it is prudent to put a 'swamping resistance' in series with the source-drain channel to minimise the possible audio distortion which could be introduced, shown in Fig. 8.

Insulated Gate FETs (MOSFETs)

This is the most recent type of transistor and one which is growing in importance because of its very high input (gate) impedance, its very good linearity, and its high operating speed. Ironically, it was also one of the first types of transistor which the early experimenters tried to make. They were defeated because they were unable to produce semiconductor material of adequate purity, or surfaces adequately free of contamination.

The way these devices are made, in principle, is to take a slice of very lightly doped n-type silicon, and diffuse a couple of p-type zones into it at either end, to serve as 'source' and 'drain' connections, shown in Fig. 9. Normally, the source connector metallising is extended so that it connects to the substrate as well.

A thin layer of a good insulator, usually either silica or silicon nitride, is then formed over the region between the source and the drain. A further metallised region (the gate) is applied on top of this insulator.

If the drain is made positive with respect to the source and substrate, no current will flow, because the drain/substrate connection is a reverse biased p-n junction. However, if a sufficient positive voltage is applied to the gate electrode, it will induce a layer of negative charges (electrons) immediately underneath the gate electrode and these electrons will move, just like any other electrons would, towards the drain. So current will flow.

The very good linearity of this type of device arises because there is a direct relationship between the voltage applied to the gate and the amount of charge induced in the channel between the source and drain.

They are fast in action because the charge under the gate insulator will appear instantly the gate voltage is applied and will disappear again as soon as it is removed. The only practical problems are that if the gate insulation is too thick, it will take a lot of applied voltage to induce electrons in the source-drain channel, whereas if it is too thin it could easily break down if the gate voltage is too high — even briefly.

Also, the conducting path between source and drain is very thin, and consequently its 'on' resistance is very high indeed. The device has to be designed so that there are a lot of drain-source channels connected in parallel.

The sort of gadget shown in Fig. 9 would be described as an n-channel lateral enhancement MOSFET: 'n-channel' because the current flow is due to electrons (n-type carriers), 'lateral' because the current flow is from side to side across the chip, as distinct from downwards through the chip as would

TRANSISTORS

be the case in a junction transistor, and 'enhancement' because the current starts off at zero and increases as the gate is made more positive.

Finally, the 'MOSFET' term, which has now become almost universal as the type name for these devices, is derived from 'metal-oxide-semiconductor FET', because of the way that the early devices were made.

If a thin layer of more highly doped (n+) silicon is formed as a channel before the gate insulating layer is grown, this will conduct electricity from source to drain even without any positive voltage being applied to the gate. The current can then be turned off by a negative gate voltage which will repel the negative charges (free electrons) away from the channel. Such a device is shown in Fig. 10, and this is called an 'n-channel depletion MOSFET'. Comparative drain current vs gate voltage curves for a normal small-signal n-channel junction FET, an n-channel depletion MOSFET, and an n-channel enhancement MOSFET, are shown in Fig. 11. The junction FET will usually have the higher slope.

Both junction FETs and MOSFETs can also be made in 'complementary' p-channel versions by reversing the types of doping, as shown in Figs. 12a and 12b. However, because of the rather slower movement of holes compared with the motion of electrons, they are not quite as fast in operating speed.

Dual Gate MOSFETs

The very good high frequency response of MOSFETs makes their use as RF amplifiers an attractive proposition. Unfortunately, the gate/drain capacitance is much too high, at a few pF, for stability in RF applications.

A dual gate MOSFET with another gate junction interposed between source and drain, shown in Fig. 13, has therefore been introduced. In this, the gate/drain capacitance is only of the order of 0.02pF. These MOSFETs are always of 'depletion' type.

In addition to their usefulness as RF amplifiers, these transistors are very convenient as signal mixers, or signal switches, for both radio and audio applications.

Power MOSFETs

Because of their growing use in high quality audio amplifiers — for which, in my opinion, they beat junction transistors hands down — the actual construction and characteristics of these transistors has received quite a lot of attention in recent years, and I don't propose to add to this.

The only comment I would make here is that with the growing skills of manufacturers in making very precise diffusion and etching masks, the 'T-MOS' type of power MOSFET of the kind shown in Fig. 14, is becoming much more widely used. Here, the channel length is controlled as in the standard 'lateral' MOSFET by the spacings between the surface diffusion regions. The drain region is placed below the gate, so that the current flow is in a 'T' shape. Hence the name 'T-MOS'. The very lightly doped n-region which separates the gate from the drain proper is called the 'drift' region, and it is essential that the bulk of the source-drain voltage drop appears across this, otherwise the gate-drain voltage would exceed the breakdown voltage of the thin gate insulating layer.

This condition may not be met at very high drain current levels, because the drift region may contain secondary carriers due to collisions. So the combination of high drain currents and high drain voltages

may cause gate breakdown, and the circuit designer should take care to avoid this possibility.

The big advantage of the 'T-MOS' design is that it allows both n-channel and p-channel devices to be made, though the higher voltage one are still more commonly of the n-channel type. 'T-MOS' transistors are a bit slower in operating speed than the original 'V-MOS' or 'U-MOS' types because of the time it may take the current carriers to get through the 'drift' region.

However, they are still a great deal faster than the best of the junction power transistors, and this shows in the clarity and transparency of the upper treble region in audio amplifiers in which they are used, in comparison with those based on bipolar junction transistors.

Thyristors And Triacs

All the devices discussed so far have been essentially linear amplifying components, though they can be used as switches. There is a wide range of useful components based on the same semiconductor technology. They are used as fast acting electronic switches in power control applications.

The first of these to come into widespread use was the 'silicon controlled rectifier' or SCR as it is most commonly known. It is also called a 'thyristor' — by analogy with the 'thyatron' valve which operates in a similar manner.

The SCR is basically a pair of transistors, one npn, the other pnp, connected as in Fig. 15. Clearly, if Q1 isn't conducting, no current flows from its collector into Q2 base and so Q2 doesn't conduct either. No current flows from its collector into Q2 base

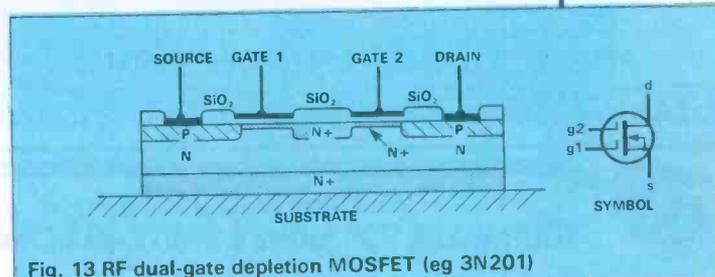


Fig. 13 RF dual-gate depletion MOSFET (eg 3N201)

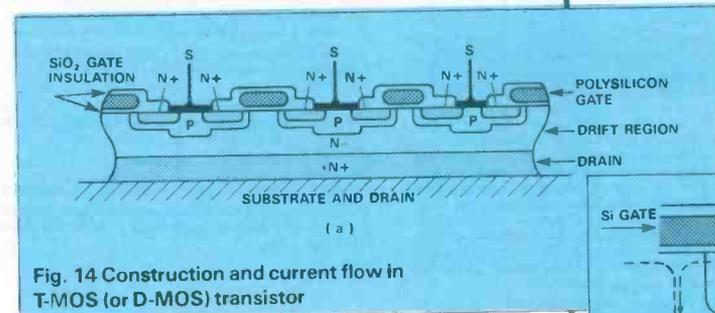


Fig. 14 Construction and current flow in T-MOS (or D-MOS) transistor

and so Q2 doesn't conduct either and no current flows from its collector into Q1 base.

If either transistor should be turned on, however briefly, then each will drive the other into conduction and both will then remain 'on' until either the supply voltage is removed or the base of one or other transistor is connected to its emitter to bypass its input drive.

This little circuit makes a very useful 'trip' mechanism, which can be put together from any available pnp/npn transistor pair. With normal transistors the cumulative loop gain will be so high that it is liable to trip inadvertently, so the resistors R1 and R2 are needed to tame its 'hair trigger' qualities.

Commercial SCRs are effectively two separate low-gain transistors merged together into a four-layer device, in the manner shown in Fig. 16a and 16b. The

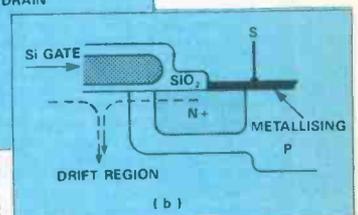


Fig. 15 Simple two-transistor 'thyristor' circuit

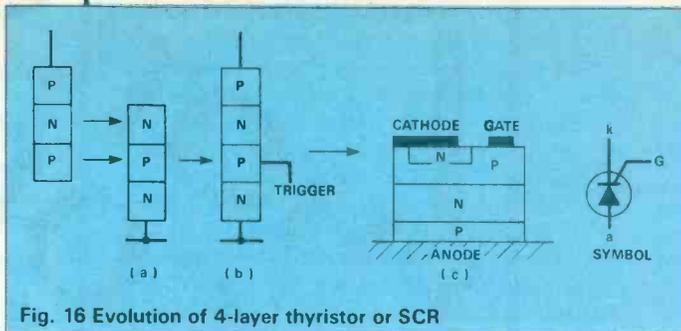


Fig. 16 Evolution of 4-layer thyristor or SCR

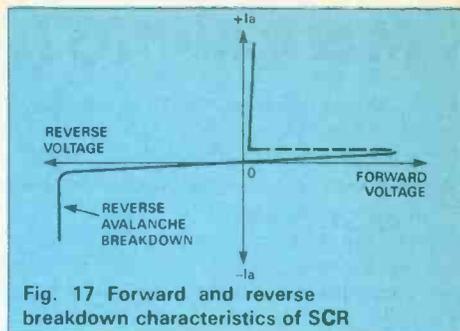


Fig. 17 Forward and reverse breakdown characteristics of SCR

actual construction of the device is more like that shown in Fig. 16c.

This is normally non-conducting in both directions but can be triggered into conduction in its forward mode if a brief pulse of input current is fed into its gate. This results in the kind of conduction curve shown in Fig. 17.

There is an AC version of this, which can be triggered into conduction in both directions, called a 'triac'. This is just a pair of SCRs joined together as shown in Fig. 18a and 18b, which results in the practical structure shown in Fig. 18c, and the type of

conduction curve shown in Fig. 19. Triacs are very useful for light dimming and other forms of AC current control, but they are not available in quite such high power versions as SCRs.

Also, because the component 'transistors' within the triac or SCR are driven hard on, a lot of minority carriers (holes in the n-type region and electrons in the p-type) are produced, and current flow will not stop until all of these have recombined. This means that the high frequency switching performance of both types of these devices isn't very good — perhaps 15-20kHz at the most.

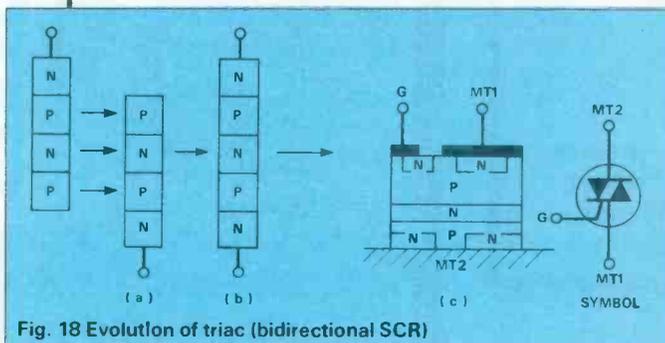


Fig. 18 Evolution of triac (bidirectional SCR)

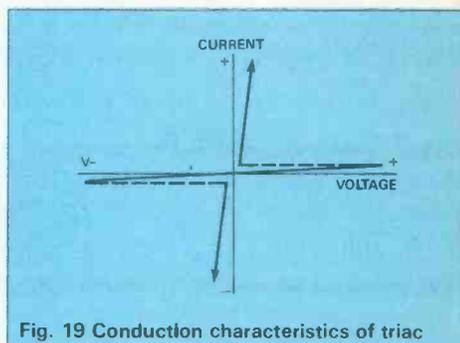


Fig. 19 Conduction characteristics of triac

ETI

HART

HART AUDIO KITS — YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

ALPS PRECISION LOW-NOISE STEREO POTS


Just arrived in stock. Exciting new range of precision audio pots in values to cover most quality amplifier applications. All in 2-gang stereo format. Throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers.

Values available are 10K and 100K Log, 100K Lin and 10K Special Balance (Zero loss in centre position). Our prices are incredibly low for pots of this quality due to large purchases for our quality kits.

2-Gang Lin £6.30
2-Gang Log £7.20
2-Gang Special Balance, zero crosstalk and zero centre loss £7.20

We are so impressed with these new controls that we will include them in our new 80 watt power amplifier kits AT NO EXTRA CHARGE until November 1989.

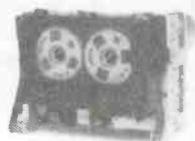SOLENOID CONTROLLED FRONT LOAD CASSETTE DECK TN3600



High quality (0.08%W&F) successor to our very popular SF925F. A very useful high quality cassette mechanism for domestic or industrial use. Offers all standard facilities plus cue and revolve modes all under remote, logic or software control. The power and control requirements are very simple with 12v solenoids and 12v Motor with built in speed control. Deck is supplied as standard fitted with a very nice 10KHz R/P head and a 1.5mH erase head.

TN3600 Deck with stereo head £48.53
INF340 Full manufacturers data £2.90

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard inductances and mounting make fitting easy on nearly all machines and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HS16 Sendust Alloy Stereo Head. High quality head with excellent frequency response and hyperbolic face for good tape to head contact £17.86
HC40 NEW RANGE High Beta Permalloy Stereo head. Modern space save design for easy fitting and low cost. Suitable for chrome metal and ferric tapes, truly a universal replacement head for hi-fi decks to car players and at an incredible price too! £6.65
HX100 Special Offer Stereo Permalloy Head £2.86
HRP373 Downstream Monitor Stereo Combination Head £44.39
HQ551 4-Track Record & Play Permalloy Head for auto-reverse car players or quadraphonic recording £16.79
HS24 Standard Erase Head £2.59
SM166 2/2 AC Erase Head, Standard Mount £12.60
HS9510 2/4 Stereo DC Erase Head £8.70
HQ751E 4/4 AC Erase Head, tracks compatible with HQ551 £57.06
We can supply card reader heads for OEMs at very keen prices.

REEL TO REEL HEADS
999R 2/4 Record/Play 110mH. Suits Stuart Tape Circuits £13.34
998E 2/4 Erase Head 1mH. Universal Mount. Suits Stuart £11.96

TAPE RECORDER CARE PRODUCTS
HART TC1 TEST CASSETTE Our famous triple purpose test cassette. Sets tape azimuth, VU level and tape speed £5.36
DEMI Mains Powered Tape Head Demagnetiser, prevents noise on playback due to residual head magnetisation £4.08
DEMI15 Electronic, Cassette Type, demagnetiser £8.61

Our new SPRING '89 List is FREE. Send for your copy now. Overseas customers welcome, please send 2 IRCs to cover surface post, or 5 for Airmail.
Please add part cost of carriage and insurance as follows:
INLAND: Orders up to £10 — £1; Orders £10 to £49 — £1.50; Orders over £50 — £2.50; Express Courier — £9.
OVERSEAS: Please see the ordering information with our lists.

Yes, you too can afford the very best in real hi-fi equipment by building a HART kit. With a HART kit you can avoid the hilarious prices and magical claims of the 'oxygen free grain oriented copper' brigade and the flashy exterior and mundane interior of the mass market products. With every HART kit you get the benefit of circuit design by world leaders in their field, men of the calibre of John Linsley Hood for instance who has been in the forefront of audio design for many years. This circuit expertise is harnessed to realise its full potential by HART engineering standards which have been famous in the kit field since 1961. The HART approach is simply to give you the best value in hi-fi by combining the best circuit concepts with the latest and best components within a unit carefully designed to bring out your hidden skills as an equipment builder.

Units in the HART audio range are carefully designed to form matched stacks of identically sized cases, in many cases even the control pitches are also lined up from unit to unit for a cohesive look to your customised ensemble.

Flagship of our range, and the ideal powerhouse for your ultimate system is the new AUDIO DESIGN 80 WATT POWER AMPLIFIER, described in the May issue of 'Electronics Today International'. This complete stereo power amplifier has so many features that your really need our list to browse through them all. Glossing over its technical merits, which its pedigree guarantees anyway. It is a power amp with the extra versatility of a built-in passive input stage giving three switched inputs, volume and balance controls. Tape or CD players may therefore be directly connected along with a standard pre-amp output, indeed your system may not need a pre-amp at all with the well balanced output of competent CD players.

Send for our new FREE Spring '89 List. It has full information on this new amplifier as well as details of improvements to other kits in our range.

Our 300 SERIES amplifiers for instance now feature optional phono input sockets and double size LCR power supply capacitors.

The 400 SERIES John Linsley Hood Audiophile Tuner range now incorporates the very latest updated stereo decoder circuit which can also be retro-fitted to existing tuners with our 'Tuner Enhancement Package'.

Also listed are many exciting new products for the serious audiophile such as our Gold plated phono and XLR plugs and sockets and ultimate quality connection leads for CD audio or digital signals.

QUALITY AUDIO KITS

24hr SALES LINE
(0691) 652894

ALL PRICES INCLUDE VAT

HART
HART ELECTRONIC KITS LTD
A PENTLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

M & B RADIO (LEEDS)

DEALERS IN SURPLUS ELECTRONIC EQUIPMENT,
TEST EQUIPMENT AMATEUR RADIO

OSCILLOSCOPE'S

PHILIP'S PM 3232. 10MHZ TRUE DUAL BEAM	£150
COSSOR CDU 150. COMPACT 35MHZ DUAL BEAM SCOPE'S DELAYED SWEEP. LARGE 8CM X 10CM DISPLAY + X1 AND X10 PROBE KIT IN FRONT COVER. SPECIAL PRICE	£165
FULL SERVICE MANUAL £10 EXTRA EQUIPMENT D755. 50MHZ DUAL BEAM SCOPE'S. SOLID STATE DELAYED SWEEP (EX MOD VERSION OF D75)	£275
TELEQUIPMENT D83. 50MHZ AS ABOVE BUT HAS LARGE 8CM X 11CM DISPLAY	£300
TEKTRONIX 466 100MHZ STORAGE SCOPE	£450
TEKTRONIX 475 200MHZ DUAL BEAM SCOPE'S. DELAYED SWEEP. HIGH SPEC. SPECIAL PRICE	£595

SIGNAL GENERATOR'S

MARCONI TF995 "EX MOD" VERSION 1.5MHZ TO 220MHZ AM FM CW WITH (LEAD'S 50Ω + 75Ω PAD'S) SPECIAL PRICE	£65
MARCONI TF 2002 10KHZ TO 72MHZ GENERATOR'S	£95
MARCONI TF 2012 UHF GENERATOR 400MHZ TO 520MHZ	£100
MARCONI TF 2008 AMFM 10KHZ TO 510MHZ WITH BUILT IN SWEEPER HIGH SPEC. WITH RF TEST LEAD KIT	£375
MARCONI TF2015/TF2171 AMFM 10MHZ TO 520MHZ WITH SYNCHRONISER	£500
RACAL RA17 RECEIVER'S 500KCS TO 30MHZ	£150
DATONG FL1 AUDIO FILTER'S	£ 30
RF DUMMY LOAD'S EX MOD. 50Ω NTYPE CONNECTOR 300 WATT'S CONT' 0 - 250 MHZ	ONLY £ 20
BRADLEY ELECTRONIC TESTMETER'S RF TO 1200MHZ	£ 25


ALL PRICES PLUS VAT + CARRIAGE

86 Bishopgate Street
Leeds
LS1 4BB

Tel: (0532) 435649
Fax: (0532) 426881
Mobile: (0836) 288580

Interak 1

Bare Board
£17.50
(plus postage and VAT)

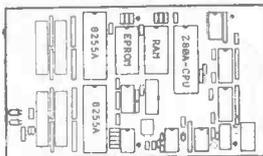

SINGLE BOARD COMPUTER "SBC-1"

A computer doesn't have to look like you'd expect a computer to look. It doesn't have to have a keyboard and a screen and floppy disks and so on.

The SBC-1 has the bare minimum of chips a Z80 computer can have and still be a computer: A 4MHz Z80A-CPU chip, an EPROM chip (up to 32K), a static RAM chip (up to 32K) and a pair of 8255A I/O (input output) chips giving 48 individual lines to waggle up and down. There are one or two additional "glue" chips included, but these are simple "74LS" or "HC" parts.

A star feature is that no special or custom chips (ie PALs, ULAs, ASICs etc) are used — and thus there are no secrets. The Z80A is the fastest and best established of all the 8-bit microprocessors — possibly the cheapest too!

Although no serial interface is included, it is easy for a Z80A to waggle one bit up or down at the appropriate rate — the cost is a few pence worth of code in the program: why buy hardware when software will do?

Applications already identified include: Magnetic Card reader, mini printer interface, printer buffer, push button keypad, LCD alphanumeric panel interface, 40-zone security system, modem interface for auto sending of security alarms, code converter (eg IBM PC keyboard codes to regular ASCII), real time clock (with plug in module), automatic horticultural irrigation controller.

By disabling the on-board Z80A-CPU this card will plug into our Interak I CP/M Plus disk-based development systems, so if you don't fancy hand-assembling Z80 machine code you don't have to!

The idea is (if you are a manufacturer) you buy just one development system and then turn out the cheap SBC-1 systems by the hundred. If you are really lazy we can write the program for you and assemble the SBC-1 cards so you can get on with manufacturing your product, leaving all your control problems to us.

Greenbank

For more details write or phone us:
Greenbank Electronics, Dept. (T10E), 460 New Chester Road,
Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391.

PHOTO -COPIES

ETI has been published for over 15 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers are available for only the past 12 month's issues we can supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

PCB foil patterns (where published) and any errata are included with all photocopies as applicable.

Please supply photocopies of the following articles from ETI (complete in block capitals):

Month Year Page (if known)

Title

Month Year Page (if known)

Title

Month Year Page (if known)

Title

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:


ETI Photocopy Service
Argus House
Boundary Way
Hemel Hempstead
Herts HP2 7ST



THE GOOD IC GUIDE



Paul Chappell announces the ETI Chip Of The Month Award and sees what this power op-amp can do

CIRCUIT THEORY

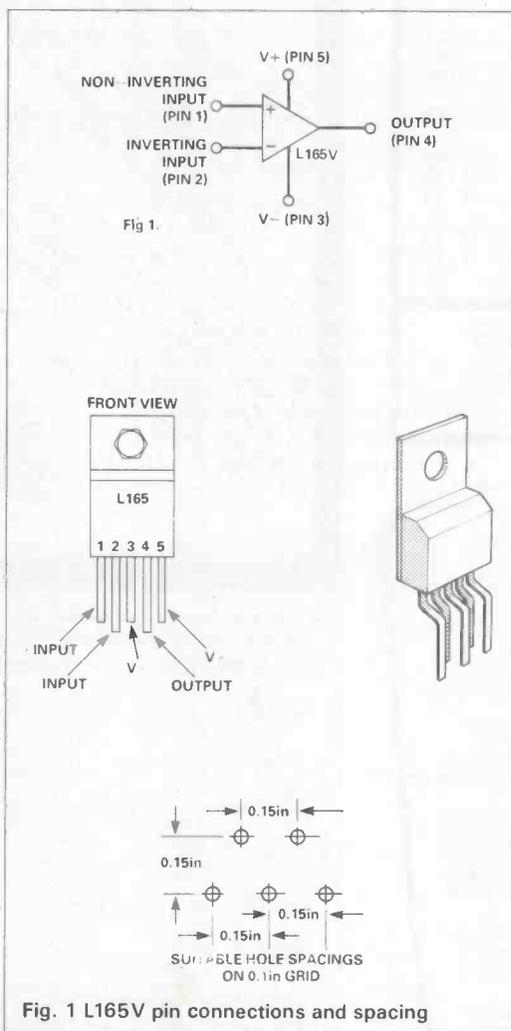

The L165V power op-amp is the IC for this month. Of all the power op-amps currently available, the L165V probably represents the best compromise between price and performance for a general purpose device. Its output current capability of $\pm 3A$ makes it beefy enough to cope with most situations, and the price tag of a few pounds means you won't have to mortgage your house to buy one.

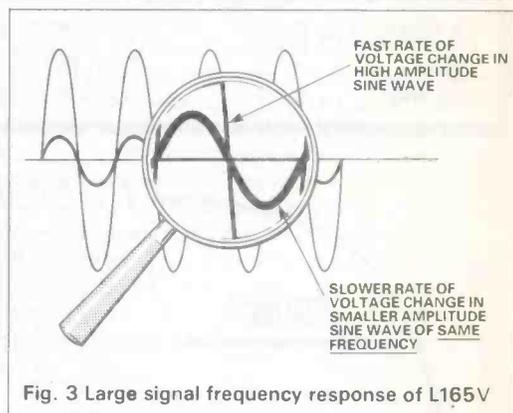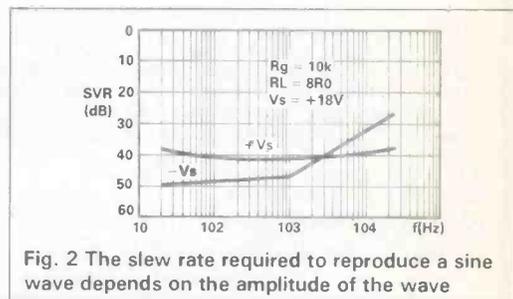First of all, what's the competition? On the cheap 'n' cheerful side there are devices like the Fairchild $\mu A759$ with an output current capability of about $\pm 300mA$, general specifications similar to a 741 and a price tag not much smaller than the L165. On the upmarket side, you could have a National Semicon-




ductors LM12 for around £25. This will give you the means to make an audio amp of hi-fi, though not super-fi, specifications. Downhill with the wind behind it, it might touch 150W RMS. What you have to weigh up is whether you could, by using discrete components, do the same rather cheaper, or do better for the same outlay. At the moment I'm sure you could, but the LM12 is relatively new and if it proves popular in industry the price is bound to fall. Keep an eye on that one!

The Data

An op-amp needs five connections: two for the power supply, two for the inputs and one for the output. The L165 has exactly that, no more and no less. The pin connections are shown in Fig. 1. The pin spacing, which you'll want to know for laying out PCBs, is illustrated in the side view of the IC. Pins 1, 3 and 5 are in a row about 0.15in ahead of pins 2 and 4.

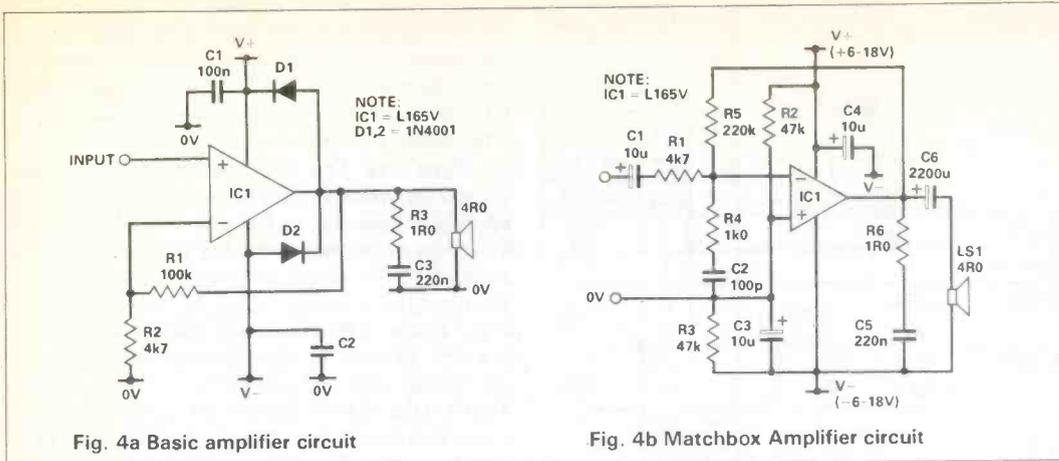The actual spacing between adjacent pins doesn't work out to anything sensible in any scale of measurement that I can discover, but the pins can be bent just a little without stressing the IC and the hole spacings shown will work out fine if you're laying out on a 0.1in grid. The pins are all bent towards the front of the IC so that it can be mounted at the edge of the



board with the tab bolted to a vertical heatsink — possibly the wall of the case if you're using a metal one.

The first thing you'll find on the data sheet, after the obligatory 'Hey! Look what this IC (or some samples of it, anyway) can do!', is a list of absolute maximum ratings as in Table 1. These aren't intended as a guide to operating conditions, they're more by way of warning; exceeding these figures may damage the IC's health.

To some extent the figures are fairly arbitrary. The 36V rating for absolute maximum supply voltage, for instance, doesn't mean that at 35.9V everything is tickety-boo, but at 36.1V the IC smokes. What it does mean is that at anything over 36V the strain on the IC's insides rises very rapidly and is likely to cause an unacceptably high failure rate. Some ICs will fail if you stick exactly to the 36V, some will still fail if you never exceed 30V but it will be a darn sight fewer in the later case. Go up to 40V and you may find that, say, 10% pop immediately, and a large proportion of the rest fail within a fairly short time. Some may soldier on for the usual life of the equipment.

The point is, there isn't really any totally safe level. It's all a matter of statistics and the reliability level you're prepared to accept. Having said all that, exceeding the maximum ratings is asking for trouble and unless you're prepared to replace a lot of ICs, stay well within the quoted figures.

The differential voltage rating is, for most purposes, a technicality. The action of op-amp circuits is normally to maintain the two inputs at the same voltage, so unless you're using the IC as a comparator there's not much chance of the inputs being anything like 30V apart. It's possible to envisage situations where this has a chance of occurring: if you were to feed a very high amplitude signal at a frequency too high for the feedback circuit to deal with properly, the inputs just might end up being 30V apart. But you're not going to do that, are you?

On the next line you see that either input can go as high as V_s (which means to either supply rail) without harming the IC. As long as the other input is within 30V of it, that is.

The next line speaks for itself: if you try to take more than $3\frac{1}{2}A$ from the IC the internal limiting comes into operation and begins to remove drive from the output transistors. The IC has safe operating area protection, which means that it tries not to allow conditions which would lead to overstressing of the IC. Lest this should give you a false sense of security, let me say now that it's a good safety measure but by no means certain to keep the IC from harm no matter what. Under static conditions you can put just about any load on the IC, even a short circuit, and it should be OK. But under dynamic conditions it's possible for a situation to arise that the protection circuit can't cope with — bye bye IC.

The last two lines give an idea of the maximum power and temperature the IC can survive. Note that the 20W figure refers to the dissipation of internally generated heat, not to how much power it will deliver if used as, say, an audio amplifier. The 20W figure could, in fact, be derived from other information: the absolute maximum junction temperature is $150^{\circ}C$, the junction case thermal resistance (from Table 2) is $3^{\circ}C$, so for a case temperature of 90° you would calculate a maximum junction to case temperature difference of $150^{\circ}-90^{\circ}$. The thermal resistance figure tells you that for each 3° temperature difference, 1W will pass from junction to case, so with a 60° temperature difference the dissipation will be $60 \div 3 = 20W$. And there you have it.

Table 2 is a different matter. The figures here are mostly measured at the recommended operating conditions, so you can take them as a guide to how to use the IC comfortably within its limits. The first line is self explanatory: if you use a supply of less than 12V,

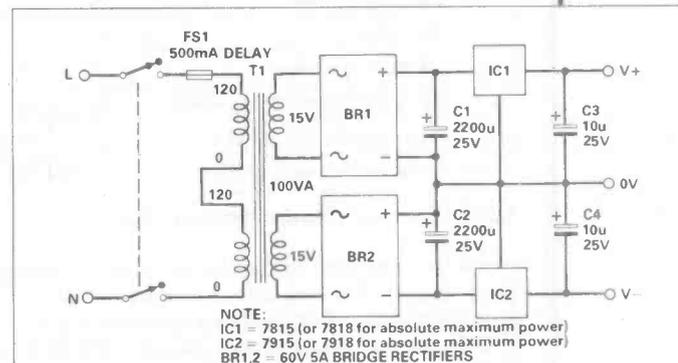


Fig. 5a Power supply for Matchbox amp

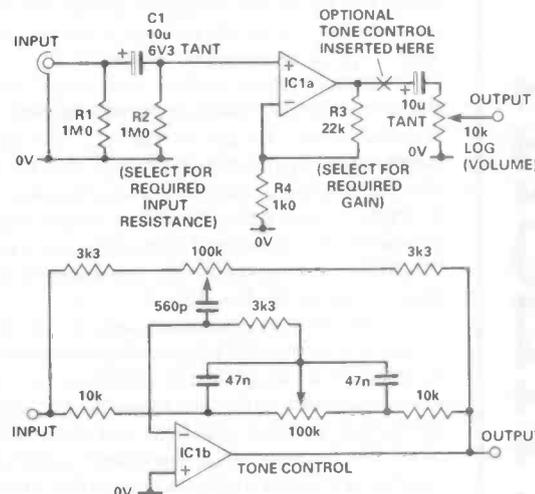


Fig. 5b Pre amplifier and tone control for Matchbox Amp

Parameter	Test conditions	Min	Typ	Max	Unit
V_s Supply voltage		± 6		\pm	V
I_d Quiescent drain current	$V_s = \pm 18V$		40	60	mA
I_b Input bias current			0.2	1	μA
V_{os} Input offset voltage			± 2	± 10	mV
I_{os} Input offset current			± 20	± 200	nA
SR Slew-Rate	$G_v = 10$		8		$V/\mu s$
	$G_v = 1$		6		
V_o Output voltage swing	$f = 1kHz$ $I_p = 0.3A$		27		V_{pp}
	$I_p = 3A$		24		
V_o Output voltage swing	$f = 10kHz$ $I_p = 0.3A$		27		V_{pp}
	$I_p = 3A$		23		
R_i Input resistance (pin 1)	$f = 1kHz$	100	500		$K\Omega$
G_v Voltage gain (open loop)			80		dB
e_n Input noise voltage	$B = 10$ to $10000Hz$		2		μV
i_n Input noise current			100		pA
CMR Common mode rejection	$R_g \leq 10K\Omega$ $G_v = 30dB$		70		dB
SVR Supply voltage rejection	$R_g = 22k\Omega$; $V_{ripple} = 0.5V_{rms}$ $f_{ripple} = 100Hz$	$G_v = 10$	60		dB
		$G_v = 100$	40		dB
η Efficiency	$f = 1kHz$ $I_p = 1.6A$; $P_o = 5W$		70		%
	$R_L = 4\Omega$ $I_p = 3A$; $P_o = 18W$		60		%
T_{sd} Thermal shut-down case temperature	$P_{tot} = 12W$		110		$^{\circ}C$
	$P_{tot} = 6W$		130		

NOTE: $V_s = \pm 15V$; $T_j = 25^{\circ}C$ unless specified.

Table 1 Absolute maximum ratings for L165V

Parameter	Max	Unit
V_s Supply voltage	± 18	V
V_5-V_4 Upper power transistor V_{CE}	36	V
V_4-V_3 Lower power transistor V_{CE}	36	V
V_i Input voltage	V_s	
V_i Differential input voltage	± 15	V
I_o Peak output current (internally limited)	3.5	A
P_{tot} Power dissipation at $T_{case} = 90^{\circ}C$	20	W
T_{sig} , T_j Storage and junction temperature	-40 to 150	$^{\circ}C$

Table 2 Electrical Characteristics of L165V

the IC won't perform too well (it won't stop working altogether — I've had one operating at 9V with tolerable results — but the results won't be too good). Usually, the maximum supply voltage in this table is also the absolute maximum supply voltage. It's more usual to specify a recommended operating voltage range and to put the maximum somewhat less than the *absolute* maximum to leave a safety margin for supply spikes and ripples, and so on.

Quiescent drain current comes next. This is just the current the IC takes to operate its own internal circuitry when it's not doing any amplifying or supplying any current to the load. The typical figure can be ignored: if you reckon up the size of your heatsink or the capacity of the power supply, or whatever, on the basis of typical figures, you'll wish you hadn't when you discover that the devices you've used are all above the 'typical'.

Now the bias and offset section. Once again, unless you belong to the groundless optimism school of design, you can ignore the typical figures. Take the worst case, assume that the actual IC you've got is as bad as they come and all your surprises will be nice ones! The bias current is the current supplied from outside to bias the input circuitry of the op-amp. In this device it actually flows *out* of the terminal. It's useful to know because you can immediately estimate

the voltage drop across the bias resistors: if you're using resistors of the order of 1M Ω for instance, they could drop about 1V each. The significance of the offset voltages and currents I delved into with the op-amps series last year, so go look it up!

Slew rate. This tells you how fast the output voltage can move if it's really in a hurry. Suppose you apply a voltage step to the input. In an ideal world there'd be a corresponding step at the output, but in a real L165 the output will move at a certain speed set mainly by the time it takes the output transistors to get their act together. In the case of a step resulting in a 10V difference in voltage between input terminals, the 'typical' slew rate will be 8V per micro-second. That is, if the output begins by being hard against the lower supply and has to make it all the way to the upper supply voltage, it could take 4 μs to get there. Interestingly there are no minimum slew rate figures specified. I'm not sure whether this is because they are so embarrassingly low, or whether the production spreads are so wide that the manufacturers don't want to commit themselves.

The slew rate has a bearing on the large signal frequency response. Let's suppose we're trying to amplify up a 100kHz signal and really wham it out into the load at maximum voltage. Let's suppose the headroom is 27V (from the next line down in the table it would seem to be a reasonable figure). OK, so we're going to try our darndest to pump out 100kHz at 27V p-p into the load.

Just take a look at Fig. 2 if you've forgotten what a sine wave looks like. Where it crosses the axis it's moving at one helluva rate, and the higher the frequency, the higher that rate will be. It's a simple matter to calculate: for a sine wave of amplitude A and frequency f , the fastest voltage change anywhere on the wave is $2\pi fA$. In this case, bearing in mind that the p-p voltage is *twice* the amplitude, it works out to be about 8.5V per μs . Assuming that the slew rate is indeed 8V per μs , it's not quite going to make it.

Now, look at Fig. 2 again. The second sine wave is at a lower amplitude but still at the same frequency. And it doesn't shift quite so fast in voltage as it crosses the axis. So although the L165 can't quite cope with the 27V 100kHz wave, it may well manage one of the same frequency but slightly smaller amplitude. In fact, we should bet about 25 $\frac{1}{2}$ V maximum at 100kHz, which is in fact in fairly good agreement with the published large signal frequency response graph (Fig. 3), which is quite surprising bearing in mind all the assumptions I've made! You get the general idea, though. The large signal frequency response can be worse than the small signal one, and can vary with the load too.

I hardly need comment on the input resistance and open loop gain. Noise voltages and currents I've had my say about quite recently. Which brings us to the common mode rejection. Ideally an op-amp should amplify *differences* in the voltage between the two inputs. Any voltage common to both should be ignored. The common mode rejection figure gives an indication of how well the IC manages it — there will always be some amplification of common mode signals, but the less the better. The figure of 70dB is quite respectable for an op-amp, although only a typical figure is given (very naughty) and, more worrying still, there's no indication of the frequency at which the measurement was made. A lot of ICs can turn in good figures at low frequency, but they're often pretty dire at any practical audio-type frequency.

Supply voltage rejection is a similar kind of animal: if ripple or noise appears on the power lines, the IC should ignore it. These figures tell you how well it manages it. Once again, a figure for a single

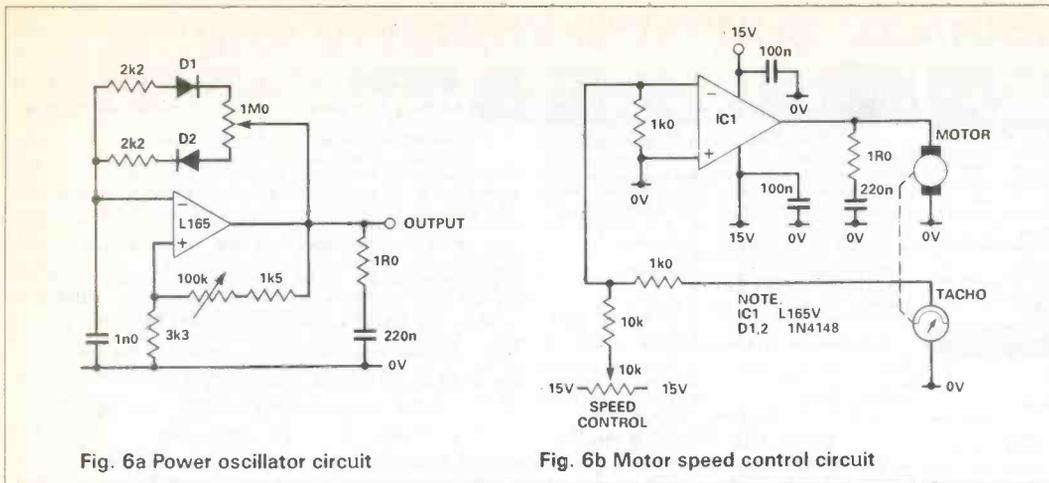


Fig. 6a Power oscillator circuit

Fig. 6b Motor speed control circuit

frequency doesn't tell the whole story: at higher frequencies the rejection can fall off quite dramatically. Always decouple (my boy) no matter what those crafty IC manufacturers may tell you.

The efficiency figure essentially gives you an idea of how much power you can deliver to the load without overheating the IC. If it's popping out 18W at an efficiency of 60%, you can reckon on about two thirds of this figure (12W) for internal heating and arrange your heatsink accordingly. It also tells you how much extra oomph the power supply needs over and above the power delivered to the load. If the IC is going to get warm, somebody has to supply the power to heat it! In the 18W output case, it means you need a minimum of 30VA available from the supply, once you've added the extra 12W of heat.

The thermal shutdown temperature is once again something you need to know for choosing a heatsink. Let's do a rough calculation for an 18W audio amp. The IC has to get rid of 12W of heat and since we'd rather not have the thermal shutdown coming on let's keep the junction temperature to less than 100°C. At a junction to case thermal resistance of 3°C per watt, the case must be kept to 36° below the junction temperature — that is, to not more than 64°. Let's assume quite a high ambient temperature (it's been hot this summer!) of 28°. We need the whole heatsinking assembly to give a temperature difference between the IC cases and the surrounding air of not more than 36°. That is, we want a thermal resistance for the whole works of not more than 3°C/W.

That rules out any of the small PCB fixing heat sinks but, even allowing for a mica washer, should be a doddle for any of the larger heatsinks or a reasonable thickness of case metal. And we're being rather cautious anyway, unless you use your amp to reproduce maximum power sine waves, the heating will be very much less.

Circuits

The basic amplifier circuit, straight from the manufacturer's data, is shown in Fig. 4a. There's not much more to it than an ordinary op-amp non-inverting amplifier. R1 and R2 are the usual feedback resistors, C1 and C2 decouple the supply rails at higher frequencies than the rejection can cope with, D1 and D2 prevent the output from going beyond the supply voltage if an inductive load is connected, R3 and C3 serve to make an inductive load look more resistive and to smooth out impedance changes, and LS is the loudspeaker. That's all there is to it.

Figure 4b shows a practical version of the same circuit — ETI's Matchbox Amplifier from way back in April 1986. With a 32V supply and four ohm speaker, it will pump out about 20W and makes an excellent

bench test amplifier of hi-fi module. And yes, it can be made to fit in a matchbox if the IC is bent parallel to the board!

A suitable power supply for the amplifier module is shown in Fig. 5a. This will allow the full 20W to be used and will power two modules, but if you're not interested in going to maximum power just about any old supply from 12V to 36V (if you want to risk it) will do. If you use an unregulated supply, bear in mind when you do your sums that the smaller transformers will give a substantially higher voltage than you expect — perhaps 15 to 20% higher — under lightly loaded conditions. The output voltage will usually be specified for full load, and the difference between this and the lightly loaded voltage will be much greater for a small transformer than for a large one. Just to complete the picture, a simple flat response pre-amplifier is shown in Fig. 5b. Now you've got a complete audio amplifier. Go for it!

Figures 6a and 6b are both borrowed from the data book, to give an example of some non-amplifier applications. There's an oscillator, not much different from the standard op-amp one that appears again and again. This one does have the added sophistication of a duty cycle control, which works by putting a different resistance in the charge and discharge paths of C1.

Then there's a motor speed controller. The idea is that RV1 provides a voltage to the inverting input of the IC which slams the output against one or other of the supply rails. The motor then accelerates smartly, or shudders to a halt and zips back the other way depending on what it was doing previously and carries on accelerating until the tachometer output cancels out the RV1 voltage and everything settles down to a nice, steady speed. Or so goes the theory. It looks to me like one of those circuits that works fine on the bench and oscillates like crazy if you try to do anything useful with it. Do remember to connect the tachometer the right way around or the motor will go screaming off into ultrasound!

Although the L165 has been around for some time, there still doesn't seem to be that many enthusiast suppliers willing to supply it. To make things easy we've arranged a little deal with Specialist Semiconductors: they will supply the IC, with a data sheet too, at £2.90, which includes postage and VAT. Their normal all-in price for the IC is £5.40, so this sounds like a bargain to me! A complete parts set for the Matchbox Amp module is available from the same source at £8.40 inclusive. Orders to: Colette Marshall, Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent NP5 4LU. Tel: (0600) 3715.

Maplin do the L165 as well at a catalogue price of £3.10. Tel: (0702) 554161.



THE ORIGINAL SURPLUS WONDERLAND!

SPECIAL PURCHASE V22 1200 baud modems

We got a tremendous buy on further stocks of this popular Master Systems 2/12 microprocessor controlled V22 full duplex 1200 baud modem - we can now bring them to you at **half last advertised price!** Fully BT approved unit, provides standard V22 high speed data comm, which at 120 cps, can save your phone bill and connect time by a staggering 75%! Ultra slim 45 mm high. Full featured with LED status indicators and remote error diagnostics. Sync or Async use; speech or data switching; built in 240v mains supply and 2 wire connection to BT. Units are in used but good condition. Fully tested prior despatch, with data and a full 90 day guarantee. What more can you ask for - and at this price!

Only **£69 (D)**

MONITORS

COLOUR MONITORS

Decca 16" 80 series budget range colour monitors. Features include PIL tube, an attractive leak style case and guaranteed 80 column resolution, features which are only normally seen on colour monitors costing 3 times our price! It is absolutely ready to connect to a host of computer or video outputs. Manufacturers fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee.

Decca 80 RGB TTL and sync input for BBC and similar type Interface etc.

Decca 80 COMPO 75 ohm composite video input with integral audio amp & speaker. Ideal for use with video recorder or our Telebox ST, or any other audio visual use.

Any type only **£99.00 (E)**

HI-DEFINITION COLOUR MONITORS

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee.

Only **£149 (E)**

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attract-

**WRITE FOR OUR EIGHT
WEEKLY BARGAIN SHEET &
GET ON OUR MAILING LIST -
FREE!**

Ive leak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.

20"....£155 22"....£170 26"....£185 (F)

MONOCHROME MONITORS

Motorola M1000-100 5" black & white compact chassis measuring only 11.6H x 12W x 2.2D. Ideal for CCTV or computer applications. Accepts standard composite or individual H & V syncs. Needs 12vdc at only 0.8a. Some units may have minor screen blemishes. Fully tested with 30 day guarantee and full data.

£29.00(C)

Fully cased as above in attractive moulded desk standing swivel. Dim 12 x 14.5 x 26cm.

£39.00(C)

JVC 751 ultra compact chassis monitor for 12vdc 0.7a. Dim 11 x 14 x 18cm. Simple DIY data included to convert to composite video input. Full data. **BRAND NEW**

£65.00(B)

20" Black & white monitors by Aztek, Cotron & National. All solid state, fully cased monitors ideal for all types of AV or CCTV applications. Standard composite video inputs with integral audio amp and speaker. Sold in good used condition - fully tested with 90 day guarantee.

£85.00(F)

IBM KEYBOARD DEAL

A replacement or backup keyboard for IBM PC, PC-XT or PC-AT, all in one! It has a switch on the rear to convert between models! LED indicators for Caps, Scroll & Num Locks. Standard 10 function keys plus 56 on the main bank and 19 on the keypad, 85 in all. Made by NCR for the English & US markets. Absolutely standard. Brand new & boxed with manual and key template for user slogans on the function keys. Attractive beige, grey and cream finish, with the usual retractable legs underneath. A generous length of curly cord, terminating in the standard 5 pin DIN plug. A beautiful clean piece of manufacturer's surplus. What a deal! **BRAND NEW AND BOXED ONLY..... £59 (B)**

COMPUTER SYSTEMS

TATUNG PC2000. Big brother of the famous Einstein. The TPC2000 Professional 3 piece system comprises: Quality high resolution Green 12" monitor. Sculptured 92 key keyboard and plinth unit containing Z80A CPU and all control circuits. PLUS 2 integral TEAC 5.25 80 track double sided disk drives. Generous other features include dual 8" IBM format disk drive support. Serial and parallel outputs, full expansion port, 64K ram and ready to run software. Supplied complete with CPM, Wordstar and Basic. Brand new and covered by our famous 90 day guarantee and backup. Normal price of this unit is over £1400!

Our Price ...only..... **£299 (E)**

FLOPPY DISK DRIVES BARGAINS GALORE!

NEW 5 1/4 inch from £29.95!

Massive purchases of standard 5 1/4" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from +5 & +12vdc, are of standard size and accept the standard 34 way connector.

SHUGART SA405. **BRAND NEW** £29.95(B)
TANDON TM100-2A IBM compatible DS £39.95(B)
TANDON TM101-4 80 Track DS £49.95(B)
CANON, TEC etc. DS half height. State 40 or 80T £75.00(B)
TEAC FD-55-F. 40-80 DS half height. **BRAND NEW** £99.00(B)

3 1/2 INCH BRAND NEW AT £19.95!!

Never before seen price for a 3 1/2" drive. Standard size believed to be by Canon. Brand new and packaged - mint condition! 40 track SS, run from +5 & +12vdc with standard power connector.....Only..... **£19.95 or 2 for £34.50(B)**

CHOOSE YOUR 8 INCH!

Shugart 800/801 SS refurbished & tested £125.00(E)
Shugart 851 double sided refurbished & tested £195.00(E)
Mitsubishi M2894-63 double sided switchable hard or soft sectors - **BRAND NEW** £250.00(E)

SPECIAL OFFERS!!

Dual 8" drives with 2 megabyte capacity housed in a smart case with built in power supply! **Only £499.00 (F)**

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only..... **£399(E)**

COOLING FANS

Please specify 110 or 240 volts for AC fans.

THIS MONTH'S SPECIAL!

Very high resolution, fully cased, 14" green or amber screen monitor with non-glare screen & swivel/tilt base. The very latest technology at the very lowest price! Fully compatible PC type input to plug direct to HERCULES card outputs, enabling superb graphics and resolution at give away prices!! The many features include aux +5 & 12v DC output's to power at least 2 disk drives or other equipment. Supplied **BRAND NEW & BOXED. Amber screen version for £79 or Green for.....**

Only **£69.00 EACH (E)**

3 inch	AC 1 1/2" thick	£ 8.50(B)
3 1/2 inch	AC ETRI slimline. Only 1" thick.	£ 9.95(B)
4 inch	AC 110/240v 1 1/2" thick.	£10.95(B)
4 inch	AC 1 1/2" thick	£ 9.95(B)
10 inch	Round. 3 1/2" thick. Rotron 110v	£10.95(B)
62 mm	DC 1" thick. No. 812 for 6/12v. 814 24v.	£15.95(A)
92 mm	DC 12v. 19 mm thick.	£10.95(A)
4 inch	DC 12v. 12w 1 1/2" thick	£12.50(B)
4 inch	DC 24v 8w. 1" thick.	£14.50(B)

RECHARGEABLE BATTERIES

LEAD ACID

Maintenance free sealed long life, all type A300.

12 volts	12 volts 3 amp/hours	£13.95(A)
6 volts	6 volts 3 amp/hours	£ 9.95(A)
6-0-6 volts	Centre tapped 1.8 amp hours	£ 5.95(A)
12 volts	12 volts 24 amp hours. A200. RFE.	£29.00(B)

SPECIAL OFFER!

100 amp/hours at 6 volt! Brand new Chloride Powersafe 3VB11. Leakproof with additional snap-on security lid. Perfect for uninterruptible power supplies, portable power source, caravans etc. Normally costs £80!

£39 (E)

NICKEL CADMIUM

Quality 12v 4ah cell pack. Originally made for the Technicolor video company. Contains 10 GE top quality D nicad cells in a smart robust case with a DC output connector. Ideal for portable equipment. Brandnew.

£19.95(B)

Ex-equipment NICAD cells by GE. Removed from equipment and in good, used condition:

D size 4ah **4 for £5(B)**
F size 7ah **6 for £8(B)**

SPECIAL INTEREST

Recal-Redac real time colour drafting PCB layout system. Includes furniture and huge monitor. Complete ready to go! £3950

DEC VAX11/750 Inc. 2 Meg Ram DZ and full documentation, in brand new condition! **£3900**

Large Calcomp plotter **£ 650**

Tektronix RM529 Waveform Monitor **£ 300**

1.5kw 115v 60hz power source. **£ 950**

Wayne Kerr RA200 audio real time freq.res. analyser. **£3000**

VG Electronics 1033 Teletext Bridge **£3750**

Tektronics R140 NTSC TV test signal standard. **£ 875**

Versatek V80 Printer plotter **£1500**

DEC LS11/02 CPU board **£ 150**

POWER SUPPLIES

All PSU's 220-240vac input and are **BRAND NEW** unless stated. Many types ranging from 3v to 10kv always in stock.

Byte BD301 5vdc @ 1.6a. 12vdc @ 1.5a. Perfect for disk drives; with Molex sockets. Very attractively cased. Illum. sw. **£19.50(B)**
Greendale 19AB0E 60 watts switch mode. +5v @ 6a. ±12v @ 1a. ±15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cm. **£24.95(C)**
Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ±12v @ 6a. 27 x 12.5 x 6.5cm **£49.95(C)**
Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a. +12v @ 2.5a. -12v @ 0.5a. -5v @ 0.5a. **£29.95(B)**
Farnell G6/40A. Switch mode. 5v @ 40a. Encased **£95.00(C)**
Farnell G24/5S. As above but 24v @ 5a. **£65.00(C)**

SPECIAL EXPERIMENTERS PSU'S

Built to BT's rigorous standards. We have no data so units are supplied for experimentation. EPSU1: +5v 2a, -12v 1a, +24v 1a, +5v fully floating 50ma. EPSU2: +5v 6a, +12v 1a, -12v 0.5a & 5 others. 30-70vdc input. Parts alone value!

EPSU1..... **£16.95(C)** EPSU2..... **£9.95(C)**

FLASH!

Lowest ever priced 8 mhz PC-AT 286 clone with 20 mb hard disk and one 5.25" 360k floppy. Complete with a regular type keyboard and very hi-res 14" mono green screen monitor and Hercules graphic card. Guaranteed for 90 days!

Only **£799.00 (E)**

BARGAIN PARTS & BOARDS PACKS

Its stock taking time once more so we have made up a lot of our famous bargain parcels again! These parcels represent the best value for money available and the greatest bargains of the century - a real thrill to open them up when you find that you have bought equipment and components (mostly brand new) for well under a third of our normal low price!!

Mix of general electronic parts & equipment!

5kilo weight for.... **£8.95(B)** 20 kilo weight for.... **£22.50(D)**

Boards Parcels for parts recovery:

Parcels contain almost any type of boards including ICs, memory, logic, passives and vast assortments of parts!

10 board parcel.... **£7.50(B)** 20 board parcel.... **£13.95(C)**

**WRITE FOR ITEMS YOU
DON'T SEE, OUR SHOP AND
WAREHOUSE ARE FULL TO
BURSTING!**

THE AMAZING TELEBOX!

Converts your colour monitor into a
QUALITY COLOUR TV!!



**TV SOUND
& VIDEO
TUNER!**

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and colour video monitor turning same into a fabulous colour TV. Dont worry if your monitor does't have sound, the TELEBOX even has an integral audio amp for driving a speaker! plus an auxiliary output for headphones or Hi Fi system etc. Many other features: LED Status Indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied **BRAND NEW** with full 1 year guarantee.

Telebox ST for composite video input monitors..... **£29.95(B)**
Telebox STL as ST but with integral speaker..... **£34.95(B)**
Telebox RGB for analogue RGB monitors..... **£59.95(B)**

NOT suitable for IBM clone type colour monitors.

BRAND NEW PRINTERS

Epson MX-80 FIT One of the most popular printers around! Bi-directional printing with full logic seeking. 9 x 9 dot matrix for enlarged, bold, condensed etc. Standard parallel interface. Brand label removed from front. Handles tractor, fanfold and individual paper. OK with IBM PC and most others. A tremendous buy!

£129.00 (E)

Hazeltine Esprint small desktop. 100 cps with RS232 and standard parallel. Full pin addressable and 6 user selectable fonts. Up to 9.5" paper. Sheet & tractor feed. **£149.00(E)**

Centronics 150 series. Always known for their reliability in continuous use - real workhorses in any environment. Fast 150 cps with 4 fonts and choice of interfaces.

150-SN up to 9.5" paper..... **£155.00(E)**

150-SW up to 14.5" paper..... **£199.00(E)**

Specify whether serial or parallel required.

CALL FOR THE MANY OTHERS IN STOCK

INCLUDING DAISY WHEELS.

Visit our Shop - Technical help always on hand plus many un-advertised specials. You can buy a colour television for as little as £29! Come and join the gang at 215 Whitehorse Lane!

DISPLAY

-Electronics-

MAIL ORDER/OFFICES

Open Mon-Fri 9.30-5.30
32 Bglgln Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP

100's of bargains for
callalot!
Open Mon-Sat 9-5.30
215 Whitehorse Lane,
South Norwood,

DISTEL © The Original

Free dial-up database
1000's of Items-Info On Line
300bd 01-679-1888, 1200/75
01-679-6183, 1200/1200
01-679-8769

ALL ENQUIRIES

01-679-4414
Fax- 01-679-1927
Telex 894502



Visa
VISA
INTERNATIONAL

All prices for UK Mainland. UK customers ADD 15% VAT to total order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome - minimum account order £25. Carnage charges (A)-£1.50, (B)-£3.50, (C)-£6.50, (D)-£8.50, (E)-£12.50 (F)-£15, (G)-Call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees given on a return to base basis. We reserve the right to change prices & specifications without prior notice. Orders accepted subject to stock. Quotations willingly given for higher quantities than those stated.



PCB SERVICE

October

TELEPHONE
ORDERS
may be made on
**(0442)
66551**
ACCESS or VISA

E8910-1 Multimeter H
E8910-2 MIDI Mapper M

PCBs for the remaining projects are available from the companies listed in Buylines.

Use the form or a photocopy for your order. Please fill out all parts of the form. Make sure you use the board reference numbers. This not only identifies the board but also tells you when the project was published. The first two numbers are the year, the next two are the month.

Terms are strictly payment with order. We cannot accept official orders but we can supply a proforma invoice if required. Such orders will not be processed until payment is received.

Price code	Price (inc. VAT)
C	£1.80
D	£2.50
E	£3.25
F	£4.00
G	£4.75
H	£5.50
J	£6.62
K	£7.20
L	£8.80
M	£10.60
N	£13.10
O	£15.80
P	£17.90
Q	£21.80
R	£23.90
S	£25.90
T	£29.00
U	£32.20
V	£35.80
W	£37.90
X	£40.70

E8807-6	Breath Rate Display Board	F	E8907-1	MIDI Patch Bay	G
E8808-1	Breath Rate Main Board	H	E8907-2	Priority Quiz Switch	E
E8808-2	Breath Rate Switch Board	C	E8907-3	Camera Trigger Infra-reds (2 boards)	G
E8808-3	Telephone Recorder	D	E8907-4	Aerial Amplifier main board	E
E8808-4	Analogue Computer Main Board (2 bds)	M	E8907-5	Aerial Amplifier power supply	E
E8809-1	Spectrum EPROM Emulator	M	E8908-1	Intercom master station	L
E8809-2	Frequency Meter (2 bds)	P	E8908-2	Intercom slave station	F
E8809-3	Travellers' Aerial Amp	E	E8908-3	Intercom power mixer	E
E8810-1	Gerrada Marweh Bikebell	E	E8908-4	Digital joystick-to-mouse conversion	H
E8810-2	Peak Programme Meter (2bds)	N	E8909-1	Twin Loop Metal Locator	H
E8810-4	TV-to-RGB Converter	E	E8909-2	Trembler movement detector	D
E8810-5	Electron RGB Buffer	C	E8909-3	Field power supply (spec 3)	C
E8811-1	NiCd Charger	E	E8909-4	Micro monitors active filter	F
E8811-2	Chronoscope (3 bds)	P	E8909-5	Chronoscope auto-reset	C
E8811-3	Digital Transistor Tester	G			
E8812-1	Doppler Speed Gun (2 bds)	K			
E8812-2	Small Fry Mini Amp	D			
E8812-3	Thermostat	E			
E8812-4	Burglar Buster Free PCB	D			
E8812-5	Burglar Buster Power/relay Board	E			
E8812-6	Burglar Buster Alarm Board	C			
E8812-7	Burglar Buster Bleeper Board	C			
E8901-1	EPROM Programmer mother board	M			
E8901-2	Variat-Ion updated Main Board	H			
E8901-3	Variat-Ion Emitter Board	E			
E8901-4	In-car Power Supply	C			
E8901-5	Granny's Hearing Booster	E			
E8902-1	Compressor/Limiter/Gate	L			
E8902-2	Ultrasonic Horn	D			
E8902-3	Stepper Motor Driver Board	L			
E8902-4	Quest-Ion (2bds)	K			
E8903-1	Intelligent Plotter Solenoid Board	H			
E8903-2	MIDI Programmer	L			
E8903-3	Balanced Disc Input Stage	F			
E8903-4	Digitally Tuned Radio	G			
E8904-1	Camera Trigger	E			
E8904-3	Intelligent Plotter Main Board	O			
E8904-4	Kinetotie Tie Board	N			
E8904-5	Kinetotie Control Board	E			
E8905-1	Guitar Tuner	H			
E8905-2	Camera Trigger Ultrasonics (2 boards)	F			
E8905-3	Bench Power Supply (2 boards)	H			
E8906-1	PC edge connector	F			
E8906-2	MIDI converter CPU	N			
E8906-3	MIDI converter keyboard	N			
E8906-4	MIDI converter control	M			
E8906-5	AF signal generator	G			
E8906-6	Mini bleeper	C			
E8906-7	Caravan heater controller	G			

**TO: ETI PCB SERVICE, READERS' SERVICES,
ARGUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST**

Please supply:

Quantity	Ref. no.	Price Code	Price	Total Price
----------	----------	------------	-------	-------------

Post and packing

£0.75

Total enclosed

£

Please send my PCBs to: (BLOCK CAPITALS PLEASE)

Name

Address

Postcode

CHEQUES SHOULD BE MADE PAYABLE TO ASP Ltd.

LESS LOGIC

Andy French takes his NAND is his hand and NORs his way through to the simplest solutions

Combinational logic is the wonderful world of AND, NAND, OR and NOR where Boolean algebra is king. Whereas sequential logic produces outputs that are a function of time, combinational logic outputs are purely a function of the input values and change immediately the inputs change. If you get up to enormous speeds, things get tougher as gate propagation delays get involved, but otherwise things are eminently easy to handle.

As a result of its relative simplicity, most enthusiasts adopt an 'intuitive' attitude to design, building up gate by gate. The outcome of such cobbling will rarely be the optimum or cheapest solution to a problem. Here we will look at the techniques that can check a circuit's operation and minimise the number of gates used.

Boolean Algebra

Don't worry! Boolean algebra is really no more difficult than ordinary arithmetic, although as with ordinary arithmetic there are a few symbols to be learned first — four of them to be exact.

These symbols are best described in terms of the logic gates that they represent, as shown in Fig. 1. There is nothing magical about the symbols used, they are just a convenient form of logical shorthand.

In a digital logic system there are only two valid states, high or low voltage. We choose to represent these two states with a 1 or a 0 respectively.

Now looking at the truth tables of Fig. 1 you will see that there are columns on either side of a vertical dividing line. Those on the left represent the input information and those on the right the outputs. So for the OR gate you will see that the output is low when both inputs are low, and high when either input A or B is high. The OR function is exactly the same as the ordinary English language or, and is sometimes called 'inclusive' OR.

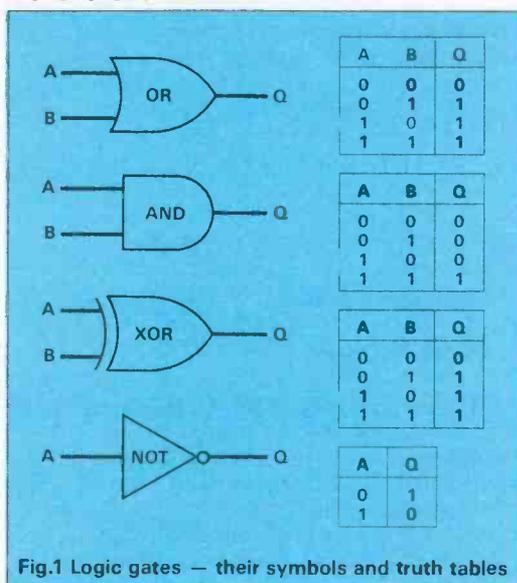


Fig.1 Logic gates — their symbols and truth tables

The other type of OR is the 'exclusive' OR, often abbreviated to XOR. With this, the output is high when either input goes high but you exclude the case where they are both high. Because of this, the XOR gate is

often used as a comparator to test if two inputs are the same.

Boolean expressions can represent only one of two values — *TRUE* or *FALSE* — so don't confuse the symbols with those used in ordinary arithmetic. It is convenient to write the Boolean values as 1 or 0, representing logic high (true) and logic low (false) respectively, giving the familiar truth tables of Fig. 1. Using our Boolean signs with variables A, B and so on, we can write equations to represent digital logic systems.

For example, the circuit of Fig. 2 can be described by the equation:

$$Q = AB + CD$$

Note that it is common to omit the AND dot, just as the multiplication dot is often omitted from ordinary arithmetic. Note also that the Boolean operators have a strict order of priority, so all NOT functions should be interpreted first, followed by AND and finally OR and XOR (equal priority).

So, is $AB + C$ the same as $A.(B + C)$? No it isn't. If in doubt, use brackets — purists may raise their noses but at least your equations will be correct.

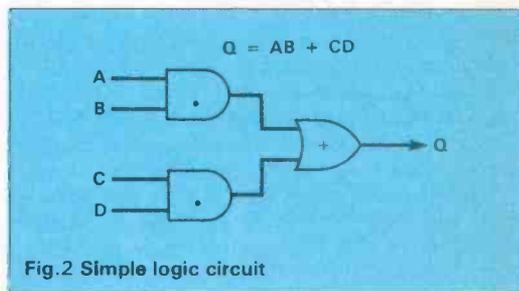


Fig.2 Simple logic circuit

It's The Law

So we can now express logic systems in terms of Boolean equations. This is where the clever bits come in. Using the list of laws in Table 1, equations can be reduced to use less Boolean signs (which implies less gates, less space, lower power consumption, less cost and so on).

It should be noted that the laws are not all independent — some are implied by or may be derived from others. The laws in the right column are said to be the 'duals' of those on the left and may be obtained by replacing 1 with 0, 0 with 1 and + with ..

Communication Law	$A+B=B+A$	$A.B=B.A$
Identity Law	$A+0=A$	$A.1=A$
Idempotency Law	$A+A=A$	$A.A=A$
Inverse Law	$A+\bar{A}=1$	$A.\bar{A}=0$
Universal Bounds	$A+1=1$	$A.0=0$
Associative Law	$A+(B+C)=(A+B)+C$	$A(BC)=(A.B).C$
Absorption Law	$A+(A.B)=A$	$A(A.B)=A$
Distributive Law	$A+(B.C)=(A+B).(A+C)$	$A(B.C)=(A.B).(A.C)$
De Morgan's Law	$\overline{(A+B)}=\bar{A}.\bar{B}$	$\overline{(A.B)}=\bar{A}+\bar{B}$
Involution Law	$A=\bar{\bar{A}}$	
Negation Law	$0=\bar{1}$	$1=\bar{0}$

Table 1 Boolean laws

Most of the laws are quite obvious and easy to prove. De Morgan's law is less so but is a very useful law to know and it is worth working through the truth tables as shown in Fig. 3.

LOGIC

INPUT		\bar{A}	\bar{B}	$\bar{A}\bar{B}$	A+B	$\overline{A+B}$
A	B					
0	0	1	1	1	0	1
0	1	1	0	0	1	0
1	0	0	1	0	1	0
1	1	0	0	0	1	0

INPUT		\bar{A}	\bar{B}	$\bar{A+B}$	A.B	$\overline{A.B}$
A	B					
0	0	1	1	1	0	1
0	1	1	1	1	0	1
1	0	0	1	1	0	1
1	1	0	0	0	1	0

Fig.3 Truth table proof of de Morgan's law

The best way to become familiar with these laws and manipulating Boolean algebra is to practise. A sound understanding here will help you understand what is going on later.

Try following my example simplification in Table 2. If you think you can understand how I obtained the result, then try covering up my working and deriving it for yourself.

As you can see, the end result is far less complex, and is in fact just the exclusive OR function. You can prove it by drawing the truth table.

Getting On The Map

Boolean algebra is fine for proving the validity of a solution system but it is not very practical as a method of reducing logic systems. For a start, as the number of variables (inputs) increases, it becomes more and more likely that that an error will be made. Also, how do we know when we have got the simplest solution and can stop seeking further reductions?

Karnaugh mapping is an ingenious technique which takes the hard work (and algebra!) out of simplification. The Karnaugh map is a pictorial representation of the Boolean equation, similar to a truth table. The empty grids for two, three or four variables are shown in Fig.4.

For each square or 'cell' of the map, the required result with that particular set of inputs is inserted. This is made easier if a truth table is drawn first. (Beware of transposing the inputs when you fill in the map, a common error with disastrous consequences!)

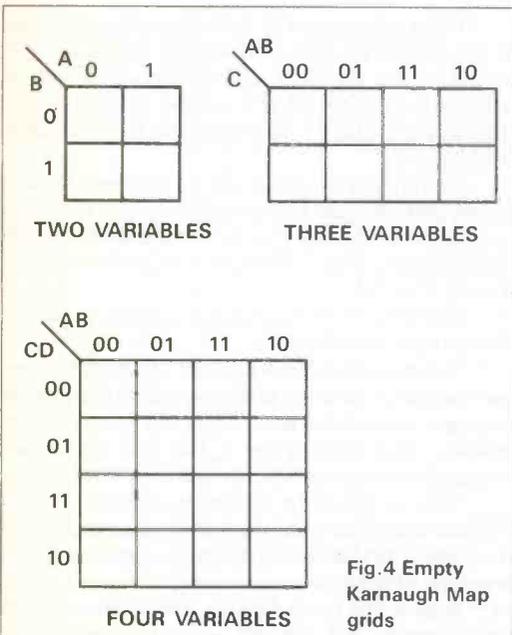


Fig.4 Empty Karnaugh Map grids

Now that you've got your nice two dimensional map, you should think of it as a three dimensional surface! All this really means is that the right most column should be thought of as being next to the left most column. Likewise, the top row is next to the bottom row. This 'edgewise adjacency' is important to remember.

Now groups of cells can begin to be made into clusters. Where ever there is a group of 1s together, they should be circled in groups of one, two, four or eight (powers of two). The idea is to circle all of the ones into the largest groups possible. The example in Fig.5 should clarify this.

The actual minimisation has now been performed and all that remains is to form the resultant Boolean equation for the Karnaugh map. Each of the groups of circled ones can be represented as an AND term, which are ORed together to give the function. In the four variable examples of Fig.5, the circled group in the top row has the variable values B=1, C=0, D=0, and A can be either. The AND term for this group is therefore BCD.

	$Q = \bar{A}\bar{B}.A.\bar{A}\bar{B}.B$
By de Morgan's Law	$Q = \bar{A}\bar{B}.A + \bar{A}\bar{B}.B$
Now expand the brackets	$Q = \bar{A}\bar{A} + \bar{A}\bar{B} + \bar{A}\bar{B} + \bar{B}\bar{B}$
And finally cancelling the redundant terms using the Inverse Law gives	$Q = \bar{A}\bar{B} + \bar{A}\bar{B}$

Table 2 Example of de Morgans calculations.

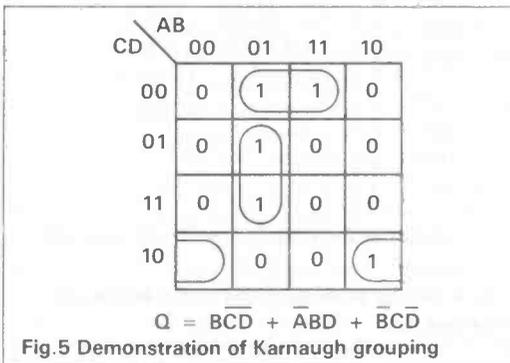


Fig.5 Demonstration of Karnaugh grouping

In some applications, 'don't care' values occur where the circuit specifications dictate that either a particular set of input values cannot occur, or the output state is irrelevant. An example of this is a BCD to 7-segment display decoder. Input values above nine are illegal and so the output is meaningless. When 'don't care' values arise, a 'd' is initially inserted into the appropriate cell of the Karnaugh map. As the 1s are grouped, it will become desirable to change this to either a one or a zero, whichever produces the least number of groups.

Also it sometimes happens that there are many more ones than zeros in a Karnaugh map. If the zeros are then grouped instead of the ones, the resulting function will often be much simpler. Because the zeros are grouped, the resulting function will be the complement of the required function. An inverter will be required at the output to obtain the valid function.

It is advisable, initially at least, to draw a truth table of the simplified function and compare it with the original to check the validity. A few moments longer with pencil and paper can save hours with a logic probe. Finally, note that the Karnaugh mapping technique minimises the number of gates used in a design, but that gates are usually packaged with several others on a single chip. Therefore, unless designing custom chips, the resulting design may leave redundant gates. These gates can be put to good use in reducing the chip count as we will see later.

The Quine-McCluskey Method

The Karnaugh map is a simple and powerful method of reduction which should be adequate for the needs of most hobbyists. However, as the number of input variables increases the size of the Karnaugh map increases rapidly making the chances of errors occurring also increase. For those of you planning to build your own microprocessors from discrete TTL, there is another method.

The Quine-McCluskey method is a tabular technique based upon the inverse laws. It is methodical, but tedious and error prone and so makes ideal computer fodder. Describing the process is, as with many things in life, more difficult than actually performing it, but once understood you will have a very powerful design tool so here we go...

ABCD	Q	
		00000√ 00-0√ -0-0
		10010√ -000 -01-
0000	1	1000√ 001-√ --10
0001	0	
0010	1	20011√ 0-10√
0011	1	0101√ 10-0√ 1--0
0100	0	0110√ 1-00√ 1-1-
0101	1	1010√ -011 11--
0110	1	1100√ 101-√
0111	0	
1000	1	31011√ -101
1001	0	1101√ 110-√
1010	d	41111√ 1-10√
1011	d	11-0√
1100	d	1-11√
1101	d	11-1√
1110	d	111-√
1111	d	

$Q = \overline{B}CD + \overline{B}C\overline{D} + B\overline{C}D + B\overline{C}\overline{D} + \overline{B}D + \overline{B}C + C\overline{D} + A\overline{D} + AC + AB$

Fig.6 Tabular example of the Quine-McClusky method


First of all, draw up a truth table for the function you wish to simplify. Pick out all of the input combinations that result in either a 1 or a *don't care* at the output and sort them into groups according to the number of 1s they contain. Write these in a vertical list such that any combinations with no 1s go into group zero, those with one 1 go into group one and so on. Each group should be labelled and separated from each other by horizontal dividing lines as in Fig.6. Don't worry if any group has no entries — just leave it blank.

Now for every entry in each group compare it with all of the entries in the group immediately below. If any pair of entries differ by just one digit then they are combinable. The terms are combined by replacing the differing digit by a dash, so that 0010 and 0110 would be combined as 0-10.

A new column is made for the combined terms, again in groups according to the number of ones. As the two terms are combined a tick is made next to their entries in the original list. If two identical entries arise in the new column then one of them may be crossed out.

In a similar way the second column entries are now compared with each other, but remember that the dashes must be in the same place if the entries are to be combinable. Make a third column of combined entries and tick those that were combined.

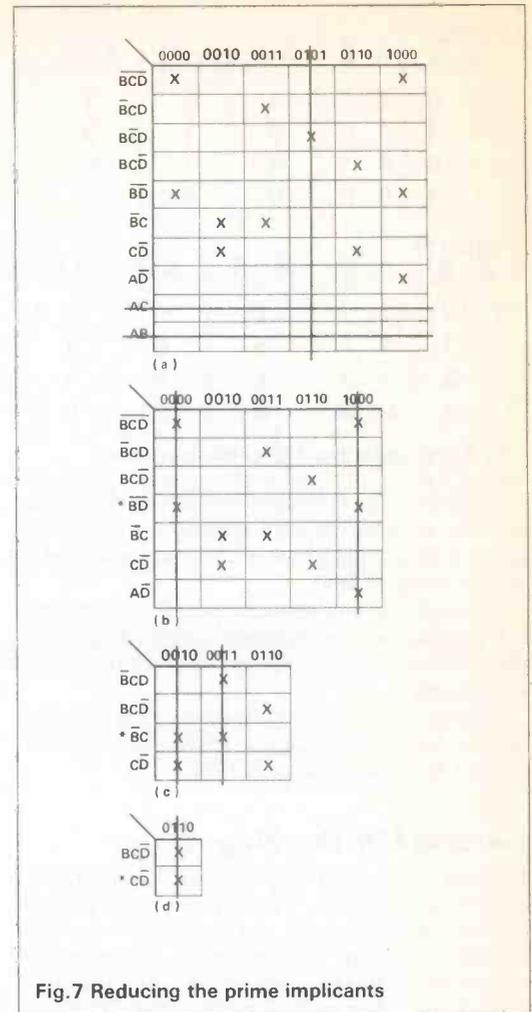Continue this procedure creating new columns



until either only one group exists in a column or none of the terms are combinable. Now for all of the entries that have not been ticked a Boolean term must be formed. This is done in much the same way as it is with the Karnaugh map, but a dash means the term is missing. 01-0 would therefore become $\overline{A}BD$.

The Boolean expressions so obtained are called prime implicants and some may be redundant terms. To obtain the fully minimised 'irredundant polynomial' we use diagrams known as prime implicant tables which enable us to find and eliminate the redundant terms.

These tables (see Fig. 7) are square grids with a horizontal line for each of the prime implicants and a vertical line for each input combination that is required to generate a 1 at the output (taken from the original truth table — do not include the 'don't care' combinations).

Go through the table row by row and at each intersection of a row and column, check if the input combination is covered by the associated horizontal Boolean term. If it is, then mark the intersection with a cross (Fig. 7a).

The bottom two rows have no crosses, so we can delete them as redundant.

Now select a *column* with just one cross (if there aren't any then move on to the next stage). The prime implicant associated with that cross is said to be *essential* and will appear in the final minimised irredundant polynomial, so mark it with an asterisk.

You can delete the column with the cross (Fig. 7b) plus any other columns that have a cross in the row belonging to that essential prime implicant (there are none of these in our example).

Repeat this procedure for any other columns with a single cross. It is not necessary to redraw the

every alteration unless you feel the table is too messy for reliable interpretation.

The next stage is to take the row with the *most* crosses, mark this with an asterisk as an essential, and delete all the columns implicated by the crosses (all these input combinations are covered by this binary expression).


Note in our example we could have picked several rows — it doesn't matter. As a rule pick the simplest Boolean expression first. Note also that picking \overline{BD} leads to the deletion of the left and right columns. This leaves two rows without any crosses — \overline{BCD} and $A\overline{D}$. These rows can also be dumped, leading to Fig. 7c.

Here we repeat the procedure, picking this time \overline{BC} , taking out the left two columns, emptying the top row also, giving Fig. 7d. We choose the simpler term and empty the table, completing the analysis.

Collecting up the prime implicants we have asterisked as essential gives us the simplified result:
 $Q = BCD + BD + \overline{BC} + CD$.

Checking this with a truth table proves that the result is correct.

Having explained the process it is worth mentioning the property of domination, particularly useful if you intend to program a computer with limited memory to perform the process. A row is said to be dominated by another if all of its crosses are duplicated in another single row. Likewise, a column is said to be dominated if all of its crosses are duplicated in another single column. If a row or column is dominated then it may be crossed out immediately. This can reduce computer array sizes, making computation much faster.

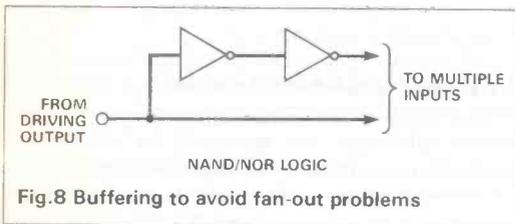

Real Gates

It should be noted that all of the above methods of logic design assume that we are using ideal gates. In practise there is a limited fan out. When a single gate is trying to drive too many other gates, the excessive load pulls the output voltage towards ground and into the illegal range between logic high and logic low. Most logic probes will not be able to diagnose the problem correctly and extensive voltage checks with a high impedance voltmeter, or better still an oscilloscope, will be required.

It is better not to try driving too many more inputs than the manufacturers recommend. Instead use a buffer stage consisting of two inverters to drive half of the inputs, as shown in Fig. 8. Of course, other gates could be used in place of the inverters, depending on what are left over from the main design. Waste not, want not!

Waste Not, Want Not

Using the 'left-over' gates to implement different types of gates to be used in the main circuit can result in a dramatic reduction in the number of packages required for a circuit. Any logic system can be implemented using NAND or NOR gates alone. All of the common combinational logic elements are shown in Fig. 9 and could easily be extended to provide more inputs if required.

To implement a function using NAND logic, first reduce it using either a Karnaugh map or the Quine McCluskey method, then draw a circuit diagram for

the resulting Boolean expression. Next, redraw it replacing all of the AND and OR gates with their NAND equivalents. Wherever two inverters are immediately in series they may be cancelled. Redrawing again omitting the cancelled gates will give the final circuit.

Doing It Discretely

Other tricks can also reduce the number of packages. These days most people leap to ICs when it comes to logic, but discrete component logic gates can also be useful. For instance, inverters generally come in six packs but Sod's law states that the number required for any design is a multiple of six plus one left over. A common emitter stage (Fig. 10a) can be employed to good effect as an inverter, though the savings will probably be in space only since the cost of a 7404 is roughly the same as that of a transistor and the two resistors.

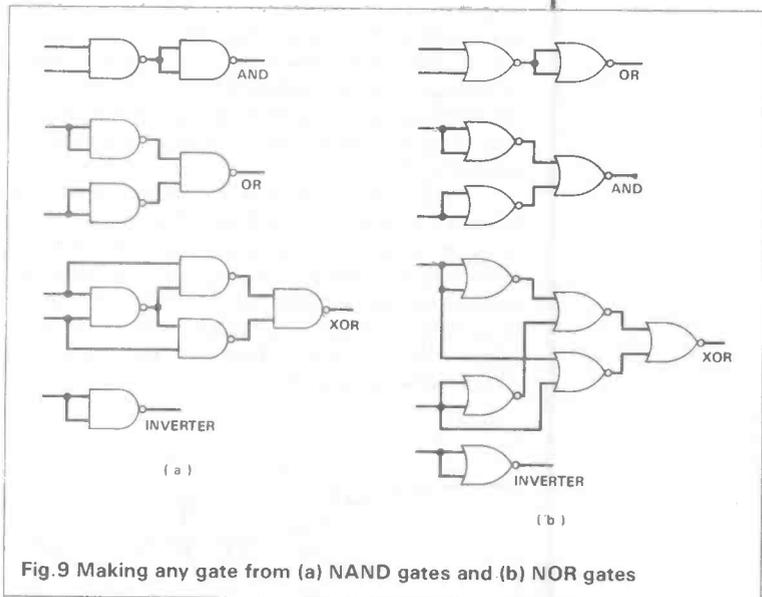


Fig. 9 Making any gate from (a) NAND gates and (b) NOR gates

Need a multiple input AND gate? A fist full of diodes (Fig. 10b) can be cheaper than using many integrated AND gates in cascade and they don't draw any power. OR gates can be constructed in a similar manner (Fig. 10c). One caution though, the passive gates should be used to drive active ones or else the logic levels will sink into the illegal region. Also, use diodes with a fairly low forward voltage drop such as common or garden 1N4148s, definitely not rectifier diodes as these tend to have forward voltage drops in excess of 1V and will almost certainly cause problems. Diode gates were used quite extensively in days gone by when logic ICs were still very expensive, but the two-a-penny cost of TTL and CMOS logic today makes the financial savings less of a consideration except in very high fan-in applications.

An even cheaper AND gate can be constructed if you're using open collector gates. It only requires a single resistor, you just connect all of the inputs together and connect them to the output, using the resistor to pull the output up to the positive supply rail — phantom AND gates (Fig. 10d). Don't try this with ordinary totem pole output gates or else the circuit's life will be short if not spectacular!

So to sum up this article, although standard procedures can help you achieve a correctly working logic circuit, a little extra time spent trying to achieve the best possible utilisation of the available gates can give rise to dramatic savings.

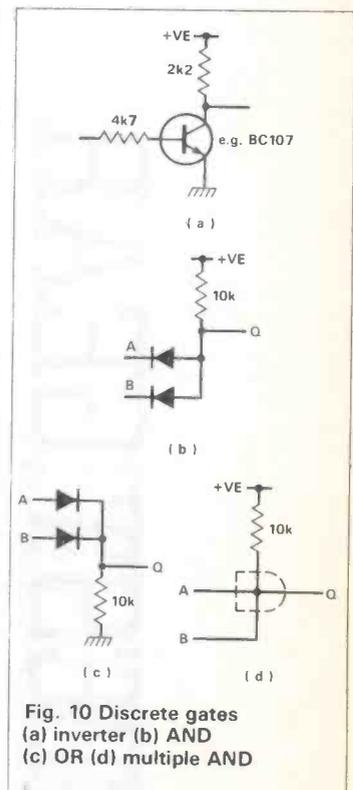


Fig. 10 Discrete gates (a) inverter (b) AND (c) OR (d) multiple AND

TESTING TESTING

1: THE BASICS

Mike Barwise returns with a series explaining the correct way to handle test gear from the humble probe upwards

In this series I will be describing electronics test gear and how it is used, together with any pitfalls or special techniques for getting reliable results. Far too frequently the assumption is made (even by highly trained specialists and research workers) that all their equipment is 100% accurate, reliable and transparent to their experimental data. **WRONG!!!**

The first, second . . . and last point to note is that no test gear is infallible. If there were letters gleaming gold twenty feet high on the front, this could not be emphasised enough. It is not sufficient to be able to take readings when using instruments, you must know how to interpret the readings. Time and time again we will come across situations where the test gear contributes to an error in your results and it is vital to be able either to quantify the error or to find a way of cancelling it out.

The generic name for experiment-induced error is *artefact*. This term will crop up with boring regularity as we proceed to discuss measurement techniques. However I don't mean to put you off — artefact can be cancelled out very successfully using a wide variety of techniques. Most of them are tricks of the trade which you won't find in the majority of textbooks, which are biased towards the theoretical principles. The

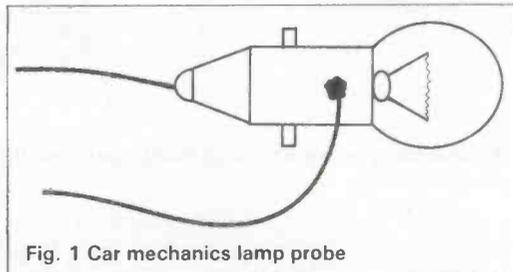


Fig. 1 Car mechanics lamp probe

general assumption in theoretical work (in order to simplify problems) is that components are perfect and test gear transparent. This is right and proper when you are learning background theory for exams and so on, but in the real world things are never quite that neat.

Defining Terms

Before we start, there are two or three terms we must define: *resolution*, *accuracy* and *precision*. These all relate to sources of error inherent in even the very best instruments.

Resolution is the number of divisions on your scale. It is normally expressed as a percentage: 100 marks between zero and maximum equals 1% resolution. Good resolution has nothing inherently to do with high accuracy or high precision.

Accuracy amounts to how much of the resolution you can ignore: if your needle wobbles a total distance equal to two divisions at 1% resolution then it is accurate to 2%, more normally expressed as $\pm 1\%$.

Precision is a measure of how reliably your instrument reading accords with the truth. If your meter reads 99mV when the input voltage is 100mV, its precision is -1% , so long as it always reads 99mV. Precision is the least troublesome of the three sources of error in instrumentation — so long as it is constant and not grossly deficient.

You will commonly find these terms used at random in mail order adverts: the most common being the use of accuracy where resolution should be used. This tends to make very ordinary gear sound more attractive, so watch out!

Common among cheap and bad instruments (not always the same thing!) is variability of any or all of these parameters with age, temperature and other outside influences. You are lost if the variation is significant, as your results will always be unpredictable.

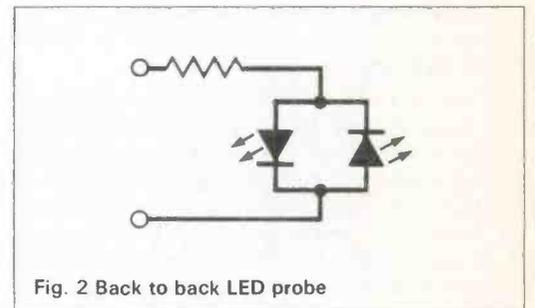


Fig. 2 Back to back LED probe



Maplin's range of multimeters

TEST GEAR

Thus, rule one: never assume new test gear is good. Check it! Neither should you assume that borrowed test gear is good — even if the guy you borrowed it from tells you so, even if he is an incredibly experienced engineer. He is most probably just used to its idiosyncrasies and automatically compensates for them mentally. This is one of the tricks I am going to show you.

Nothing For Nothing

Step two in understanding test gear artefact is the fundamental principle that you get nothing for nothing. Detection of signals is detection of energy, and you can only detect energy by stealing a bit of it. The amount you steal and how you steal it determines whether you significantly alter the signal you are testing or not.

Remember that every time you apply a test probe, even a non-contact probe like a compass needle beside a wire carrying a current, you draw a bit of energy from the thing you are investigating.

Let us take a very crude example (perfectly realistic though!) to demonstrate how things can go wrong. The gear in question is the automotive engineers' test prod. This consists of a 12V lamp (about 2W or 180mA consumption) connected to a pair of flying leads (Fig. 1). It is used to test for open circuits and live terminals among the guts of your car: you connect one lead to either the battery positive or negative and then the lamp lights when the other lead contacts a point of opposite potential. The mechanic is very happy because his test probe is reliable, robust and simple to use.

Now you come home to find that your computer won't talk to your modem and you can't get onto your favourite bulletin board service. OK, whip round to your friendly mechanic and borrow his test probe. After all, you have a hazy memory (head, not micro!) that RS232 works at 12V. You disconnect your modem cable, connect one lead of the test probe to

your hard disk controller in this way, you would have finished up with a bit of smoke and a very big bill indeed.

What does this silly example tell us? Quite simple: when you take your measurements, you must take out much less energy than is in the system. Quite apart from any consideration of damage, a 10% drain into your test gear will produce at best a 10% error in your reading (probably more). It is normally considered reasonable to draw not more than a thousandth (10^{-3}) of the power in the circuit under test. As most affordable general purpose test gear resolves to about 1%, you are always one order less intrusive than you will notice. In special cases this criterion can be tightened. In many modern instruments, tested signal drain (probe current) is vastly less due to advances in technology.

Your next step is to give the lamp back to your mechanic and look for a more suitable test probe. You can cheat a little, because I have just told you that RS232 works at $\pm 12V$ and can deliver about 50mA without problems. Yes — an LED! If you substitute an LED for the lamp, you just might be on the right lines. An LED will light up at a current of 5-25mA depending on the flavour: lime and lemon mostly need more current for a given brightness than cherry. 50mA will blow most of them up, so a series resistor will be needed (say 1k Ω) which will pass about 10mA.

A refinement would be a second LED back to back with the first (Fig.2) as LEDs are diodes (they only conduct one way round). This would indicate whether the RS232 line was high (LED1 on), low (LED2 on) or dead (neither on). This is in fact the basis of the majority of cheap (here I mean overpriced) RS232 testers. Well done! However . . .

The functional RS232 tester we have just developed has a major limitation. It only registers top-notch signals as it is a representative RS232 load. A good output (insufficient voltage swing, low current or a host of other faults) just registers as dead. You can go further: in order to establish what is wrong in more detail, we must think up something a little more sophisticated!

A first line of attack could be to design a monitor which shows at least approximately the voltage swing of the RS232. An obvious solution would be a set of zener diodes (defined reverse breakdown characteristic) and a set of LEDs (Fig.3). This circuit has just one minor problem. It doesn't work.

The zener diodes are fine — not very accurate, but fine. What screws up the performance is the LEDs. An LED has a threshold voltage (minimum for conduction and light output) called V_t of about 1.2 to more than 1.7V, depending again on the type (this is a very variable value from device-to-device). The V_t of each LED would have to be added to the zener voltage, and each pair would need individual testing and tuning. Also, even if you got this right, the higher the RS232 voltage the more LEDs are on, so the higher the current drawn from the circuit under test, the greater the voltage drop at the point under test (the old problem again).

A much better solution (it actually works) is shown in Fig.4. Here, the zener diodes drive transistors which carry the LED current when they are in conduction. Only half the circuit (the positive-going detector) using npn transistors is shown for simplicity but obviously a similar circuit using pnp devices (conducts when base negative) would be included for testing RS232. This test probe will show not only whether the RS232 is functioning but also how good its voltage swing is, with limited precision. Furthermore, the probe draws less than 1/100th of the power from the circuit under test compared with the simple LED of Fig.2.

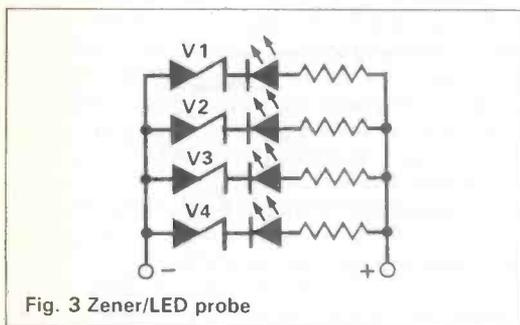


Fig. 3 Zener/LED probe

a good ground point and probe around the RS232 connector with the other. Nothing . . . nothing . . . nothing at all! You are convinced your RS232 port has blown up and you go out and spend lots of hard earned loot on a new one. However . . .

The real problem lay with your choice of test gear. It's perfectly true that RS232 works at 12V ($\pm 12V$ nominal to be precise), but any output can only supply about 50mA and still remain at $\pm 12V$ or $-12V$. Drawing any more current than this causes the output voltage to fall towards 0V. By the time the output is trying to cope with the 12V lamp (about 30R cold thus a little over 300mA) its voltage is very low indeed and the output is just incapable of lighting the lamp.

This does not mean that current is not flowing: just that you can't detect it. Fortunately, although you have not done any good, you have done no harm either (this time). RS232 outputs are designed to withstand continuous short circuit. Now, if you had tested

This is about as far as you can go with simple probes with lights on. Mostly people build probes themselves, but the next step in test gear is the *meter* (multimeter, DVM, DMM and so on). These, you buy. There are two main categories: the *analogue* and the *digital*. It is a common idea that since the invention of the digital meter, the analogue meter is dead and useless. This is not so. Each has its uses, and the experienced electronics engineer usually has a couple of each to hand.

The Analogue Solutions

In the old days, before the advent of cheap A to D converters (the guts of the DVM), people used moving coil and moving iron ammeters and voltmeters and valve voltmeters. Clever engineers still use them sometimes.

They all work on the principle of electro-magnetic attraction and repulsion between a coil of wire and a piece of magnetised iron against the restoring force of a small spring: in some the coil, and in others an iron armature, moves. Over the years, a considerable level of sophistication has been reached

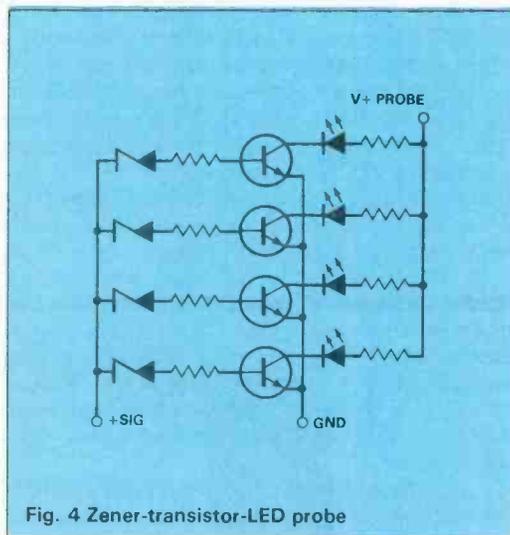


Fig. 4 Zener-transistor-LED probe

in their design and they are remarkably accurate under the right conditions.

Firstly, let us look at the difference between an ammeter (Fig. 5a) and a voltmeter (Fig. 5b). The ammeter measures current passing through it and so does the voltmeter. The only difference is that the voltmeter has a very precise known resistor in series with it, and its scale is calibrated in terms of the voltage required to pass specified currents through it. The resistance of the ammeter has to be negligible in comparison with the circuit it is connected in series with (see Fig. 5c) and the resistance of the voltmeter plus its resistor must be very high compared with the circuit it is connected across (Fig. 5d).

Both these requirements fulfil the rule we have just learned — take as little energy from the system as you can. The ammeter in series with the circuit dissipates energy proportionally to its resistance, and the voltmeter in parallel with the circuit, in inverse proportion, to its resistance.

Moving coil ammeters are sold as 0-5A, 50-0-50mA and so on but in most cases, the actual coil in the meter has quite a high resistance and a significant needle deflection is caused by quite a small current passing through it. The range selection is accomplished by adding a substantial wattage resistor in parallel with the meter coil (Fig. 5e). If the coil resistance is N ohms, and the resistor has a value of $0.11N$ ohms ($N/9$), the current range of the ammeter

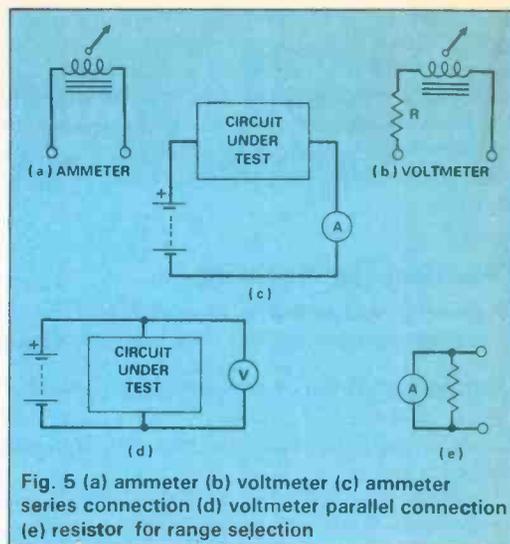


Fig. 5 (a) ammeter (b) voltmeter (c) ammeter series connection (d) voltmeter parallel connection (e) resistor for range selection

will be multiplied by 10. The advantage of this approach is that it is much easier to produce a reliably sensitive delicate mechanism than one chunky enough to carry the whole current you are measuring once you get above about 100mA or so. The best ammeter movements have full scale ranges in the region of 50-100 μ A.

Moving coil volt meters are classified in terms of the current they draw in ohms-per-volt. This is a measure of the total resistance of the meter and its series resistor in terms of the full scale deflection of the meter. Thus a typical value of 20,000 R/V (a good quality general purpose voltmeter) would have a total resistance of 20k for a 1V range, 200k for a 10V range and so on. The current drawn by the meter will vary over its range with the applied (measured) voltage but this specification assures us that the maximum current which can be drawn from the circuit under test is 50 μ A.

Simple moving coil meters have one drawback — you can only use them to obtain sensible readings of DC systems. If you apply AC, the needle will jitter about, changing direction with the AC polarity, and you may shake the movement to pieces. There are solutions using additional external components (more later) but for general purpose chunky AC signals (power supply monitoring and so on) the moving iron movement is most suitable.

This consists of a fixed electromagnet formed of the coil wound on an iron core and an armature made from magnetisable material (carbon-free iron) which does not retain its magnetism well. This, like the keeper on a toy magnet, is attracted to the electromagnet in proportion to the strength of the field, but it does not care about the polarity of the fields the armature has no north or south pole. Even in the presence of an AC magnetic field, the armature will be attracted in proportion to the field strength.

This has an interesting spinoff. In the presence of an AC field, the moving iron voltmeter will tend to display the AC RMS voltage (a measure of the average power capability) rather than the peak-to-peak swing of the AC. For a sine wave, RMS is about 0.7 times the peak voltage and is actually a more useful parameter in many cases. It amounts to the theoretical DC potential you would get if you integrated the AC via a lossless full wave rectifier.

Moving iron meters are, however, rather crude. They are much less linear than moving coil meters, and are remarkably insensitive. In order to improve measurement at low AC signal levels, the valve voltmeter was invented. This is what we shall start by examining next month, in the second part of this series.



PHONE
0474 560521



FAX
0474 333762

P. M. COMPONENTS LTD

SELECTRON HOUSE, SPRINGHEAD ENTERPRISE PARK
SPRINGHEAD ROAD, GRAVESEND, KENT DA11 8HD

TELEX
966371
TOS—PM

VALVES

BRIMAR — COSSOR — FEPAND — GEC
— HIVAC — MAZDA — MULLARDS — RCA —
SIEMANS — SELECTRON — TEONEX — ETC

Over 3 million valves available from stock. Please phone for a competitive quote.

We offer: specially selected pre amp valves; a wide range of matched power valves; high quality CV and ruggedised valves; transmitting, receiving, industrial and rare vintage wireless valves and sockets.

We also offer: Semiconductors; Video Heads and Belts; Integrated Circuits; Diodes; Industrial Cathode Ray Tubes.

How to buy: You may phone our sales desk 0474 560521 (24 hour answering service) and order by credit card or send your order with cheque/postal order and we will despatch all ex stock items the same day.

UK orders p&p £1.00 per order.
Please add 15% VAT to prices shown.
Export orders welcome, carriage at cost.

A selection from our stock of branded valves

2A3	16.50	572B	59.00	7119	9.00	EF804S	19.50
5R4GY	4.95	805	59.00	7247	8.50	EF805S	25.00
5U4G	4.50	811	15.00	7551	8.50	EF806S	25.00
6CA7	3.50	812A	35.00	7581A	11.95	EL34	3.25
6CG7	4.50	813	27.50	7586	15.00	EL84	0.95
6CW4	8.50	845	59.50	7587	19.50	EL86	1.75
6DJ8	1.35	872A	20.00	7591A	8.95	EL519	6.95
6DK6	1.50	5636	5.50	7868	8.50	EY88	0.95
6EJ7	0.85	5642	9.50	8417	8.95	EZ80	0.75
6FQ7	4.50	5751	2.95	E81CC	5.50	GZ32	4.50
6GK6	3.95	5814A	3.25	E82CC	4.50	GZ34	4.50
6JB6A	9.50	5842	11.00	E83CC	4.50	KT66	5.00
6JS6C	9.50	5881	9.95	E88CC	3.50	KT67	9.00
6KD6	10.50	5899	4.50	E88CC01	6.95	KT77	15.00
6L6GC	3.50	5963	1.75	E182CC	9.00	KT88	15.00
6LQ6	9.50	5965	2.15	E188CC	7.50	M8136	7.00
6SN7GT	1.95	6057	3.75	EC8010	12.00	M8137	7.95
6U8A	1.50	6136	2.50	ECC81	1.50	M8162	5.50
6Y6GT	2.50	6146B	9.50	ECC82	0.85	M8195	6.50
6X4	1.50	6189	4.50	ECC83	0.95	PL504	1.25
12AT7	1.50	6201	6.45	ECC83SP	3.50	PL519	4.95
12AT7WA	2.50	6267	5.00	ECC801S	6.95	TT21	45.00
12AU7	0.85	6360	4.50	ECC802S	6.95	QQV03.10	5.50
12AX7	0.95	6550	8.95	ECC803S	6.95	QQV03.20	25.00
12AX7WA	2.50	6550A	13.95	ECF82	1.50	QQV06.40A	27.50
12AY7	3.95	6870	11.50	ECF804	6.50	U19	9.50
12BH7A	4.95	6883B	9.95	ECF805	2.50	UCH41	2.50
12BY7A	3.50	6973	8.95	ECL82	1.00	UL84	1.95
12E1	19.50	7025	2.50	ECL86	1.50	VR150.30	2.50
211	25.00	7027A	10.00	EF86	2.50	Z759	15.00

TOP QUALITY
AUDIOPHILE
COMPONENTS

NEW FROM SAGE AUDIO

HIGHEST POSSIBLE
TECHNICAL
PERFORMANCE


SUPERMOS 2 (100W to 500W ±50V to ±75V)

THE MOST ADVANCED HI-FI AMP IN THE WORLD

Following the success of the original SUPERMOS we now launch a higher powered version with many new exclusive sound improvements not available on any other amplifier, kit, board, module, or ready made.

FEATURES:-

- Highly efficient distortionless PURE CLASS A throughout (low heat generation)
- Top audiophile components inc. best SMD's
- Exclusively made matched custom semiconductors.
- Minimal capacitor design (without DC servos).
- PSU sound colouration eliminated.
- Advanced PSU feedforward ripple elimination including internally separately regulated voltage AND current to ALL stages using SAGE Super-Supply circuitry.
- Total reactance (difficult speaker) drive capable.

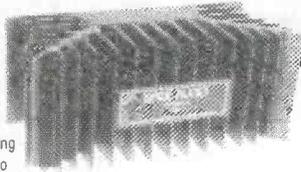

SIZE 240 × 100 × 100mm

THD 0.0001%, Slewrate 685V/us, f-3dB 0.5Hz-350kHz, O/P Current 80amps, Damping factor 940, transient power (2ohms) up to 1800W max.

PLUS By innovative technical design we have eliminated 5 individual sound colouration components found in all other conventional amplifiers.

ELIMINATED - 1) Emitter resistors 2) Zobel networks 3) HF pole compensation 4) Fixed bias Vbe multiplier and temp gen distortions 5) Capacitor sound.

AND THERES MORE ... Sage exclusive CLEAN CLIPPING (not to be confused with soft clipping) eliminates PSU ripple from reaching the output even when severely clipped, this together with individual regulated supplies to all stages (Super-supplies) TOTALLY eliminates PSU component sound colourations. (A World first!)

Supermos £70, Supermos1 £85, Supermos2 £140 each

AND THERE'S MORE ... We can't possibly describe this amp fully in this ad. To receive an 8 page glossy brochure describing these modules inc description of our class A operation and all our products send £1.50 cheque, PO, coins plus a 9" x 12" 28p SAE (note we no longer send information without the above money and SAE or 6IRC's overseas) to:

SAGE AUDIO Sue Wilson, Sales Dept., SAGE AUDIO, Construction House, Whitley Street, Bingley, Yorks. BD16 4JH, England.



BINDERS

FOR YOUR VALUABLE COLLECTION
OF ELECTRONICS TODAY
INTERNATIONAL MAGAZINES
· SMART · EASY TO USE · TOP QUALITY ·
To ASP Readers Services,
Argus House, Boundary Way,
Hemel Hempstead HP2 7ST (0442 66551)

£6.20
inc.
P&P

Please supply Electronic Today International
Binders £6.20 inc. P&P

Total £..... (Please make cheques payable to ASP)

Years Required: 198..... 198..... 198..... 198.....

Name

Address.....

Please allow 21 days for delivery.

BRIAN PRICE — BOHM ORGAN STUDIOS

389 ASPLEY LANE, NOTTINGHAM NG8 5RR Telephone/Fax: 0602-296311

32 years' experience in high quality Organ and Keyboard design behind every BOHM product. Equipment for Home and Professional use.



- ★ Latest from BOHM
- ★ Portable or Spinnet
- ★ 49 note keyboards Touch Sensitive
- ★ 16 Bit Sampled voices
- ★ Stereo Sounds
- ★ 22 Sampled Rhythm Instruments
- ★ 16 Live Rhythms, Fills, Intros, Breaks & Endings
- ★ Tempo Readout
- ★ User Programmable voices, Rhythms & Accompaniments
- ★ Soundcard Programming
- ★ 15000 note Sequencer
- ★ Full MIDI/IN/OUT/THRU
- ★ 160w Stereo HI-FI Amplifier

BOHM MUSICA FUTURA 520 Kit form Price £2230 inc. Stool. Built Price £2563
BOHM DOUBLE KEY 520(P) Kit form Price £2069 inc. Stool. Built Price £2275
Loudspeakers extra for Double Key 2x B100 £474.00 100 watts if required.

Supplied in Kit form or Built by:

THE BOHM SPECIALISTS

Part Exchange welcome. Please write or phone for full illustrated literature and price list.

INTRUDER BEAM

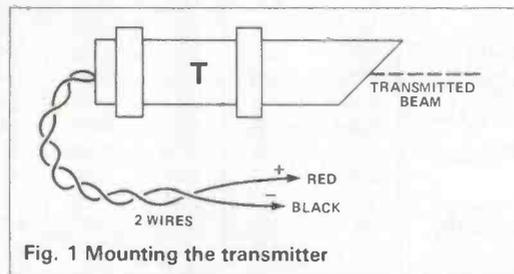


Fig. 1 Mounting the transmitter

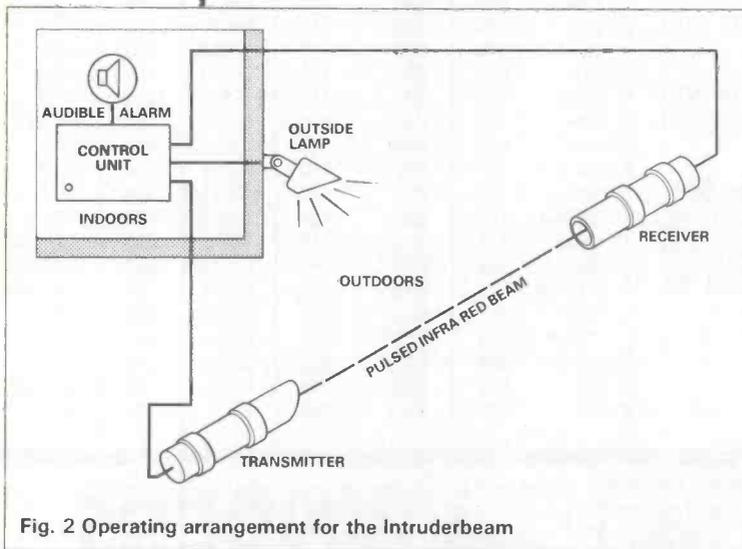


Fig. 2 Operating arrangement for the Intruderbeam

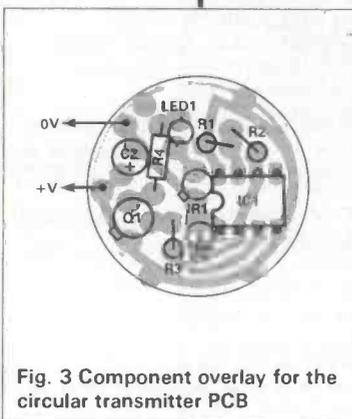


Fig. 3 Component overlay for the circular transmitter PCB


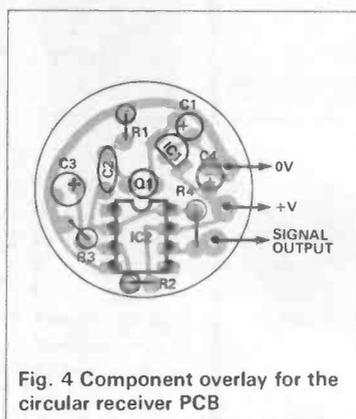


Fig. 4 Component overlay for the circular receiver PCB

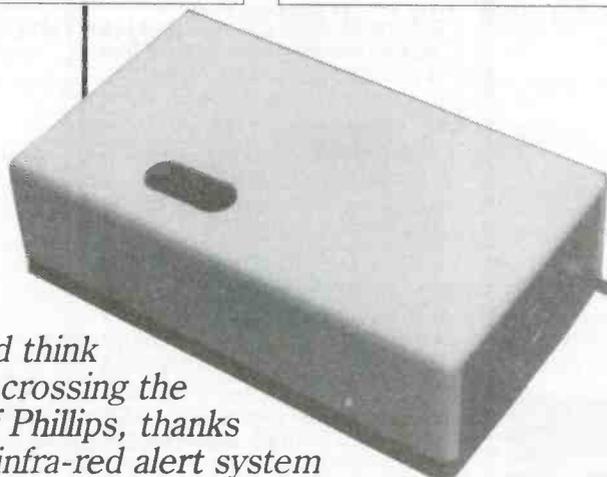

Felons should think twice before crossing the path of Geoff Phillips, thanks to his active infra-red alert system

In these days of high crime figures a burglar alarm for the home is a sound investment. Most alarms however operate on the principle whereby the felon has to actually break into your home before the alarm is triggered. He may be frightened off or a brave burglar may grab something before he runs. Meanwhile costly damage has been done to a window or a door, leading to drawn out insurance claims and the hassle of arranging for the repairs to be carried out. Your property may be in an insecure condition in the meantime.

The intruderbeam system utilises a pulsed active infra-red beam which is installed outdoors to monitor the most vulnerable areas around the doors and windows of your property.

If, during the hours of darkness, the infra-red beam is broken by a prowler the system switches on an internal house light to fool the burglar into thinking he has been spotted and the householder is coming to investigate. In addition, an audible alarm may be sounded to scare the prowler away further. The audible alarm channel is selected manually when required but the internal house light channel is arranged to self-prime at dusk — the householder does not have to remember to switch it on.

It is highly probable that most burglary attempts will be thwarted by the light channel in which case the householder sleeps through the whole event. The system is completely tamper-proof in that any attempts to mask off the transmitter or receiver or to cut any of the wires will trigger the alarm.

Transmitter And Receiver

The system comprises an infra-red transmitter and infra-red receiver and a control unit. Short pulses of infra-red of 900nm wavelength are used for the beam rather than a continuous signal which would be wasteful on energy and difficult to differentiate from the relatively constant infra-red content of daylight. Both the transmitter and receiver are fitted with LEDs to aid alignment.

The control unit is designed to be mounted indoors but as the infra-red beam is outdoors it is essential that the transmitter and receiver are completely waterproof. A perfect solution to the problem was to mount the transmitter and receiver electronics in 1½in plastic waste-water pipe fittings on the principle that if they are designed to keep water in, the pipe fittings will certainly keep water out.

Small circular printed circuit boards are used for the transmitter and receiver circuits which fit into a pipe end blank of the type used where a kitchen sink waste pipe emerges from the outside wall of the house. (The end blank is screwed and allows a plumber to gain access to the section of pipe which leads to the gully grate if a blockage in the pipe occurs.)

The collimating lens for the transmitter or receiver is mounted in a section of pipe which is joined to the end blank section by an in-line pipe join (see Fig. 1). The complete unit can then be mounted to a wall with the operating arrangement as shown in Fig. 2.

PARTS LIST

CONTROL UNIT

RESISTORS (all 1/4W 5% unless stated)

R1	100k
R2	330k
R3	15k
R4	8k2
R5	820R 1/2W
RV1,3	1M0 horizontal skeleton preset
RV2	100k horizontal skeleton preset
LDR1	ORP12

CAPACITORS

C1	4.7μ 35V aluminium electrolytic
C2	2.2μ 35V aluminium electrolytic
C3,4,6	100μ 16V aluminium electrolytic
C5	220μ 25V aluminium electrolytic

SEMICONDUCTORS

IC1	LM324 quad op-amp
IC2	4011 quad NAND gate
IC3	7812 12V regulator
Q1	BCY71
Q2,3	BC107
BR	W01 1A bridge rectifier
D1-4	1N4148
ZD1	BZY88 C5V1
LED1	5mm red LED
LED2	5V flashing LED

MISCELLANEOUS

T1	3VA transformer 12V, 12V
RL1,2	Vertical format 12V DC relay dual changeover contacts
SW1	DP toggle switch
Plastic case. Mains plug and socket. 3-pin 180° DIN plug and chassis socket. Audible alarm.	

TRANSMITTER

RESISTORS (all 1/4W 5%)

R1	100k
----	------

R2,3	100R
R4	10R

CAPACITORS

C1	4μ7 35V aluminium electrolytic
C2	100μ16V aluminium electrolytic

SEMICONDUCTORS

IC1	CMOS 7555 timer
Q1	BC640
LED1	5mm red LED
IR1	TIL31 IR transmitter

MISCELLANEOUS

PCB. 1.5in plastic pipe fittings. Bland end. Pipe (approx 80mm).
Straight coupler. Watchmaker's eyeglass 31mm focal length.

RECEIVER

RESISTORS (all 1/4W 5%)

F1	2k7
F2	1k0
F3	10k
R4	2M7
R5	820R

CAPACITORS

C1,4	22μ 16V aluminium electrolytic
C2	100n polyester 5mm lead pitch
C3	100μ 25V aluminium electrolytic

SEMICONDUCTORS

IC1	78L12 12V 100mA
C2	741
Q1	TIL81 IR receiver
LED1	5mm red LED

MISCELLANEOUS

PCB. 1.5in plastic pipe fittings: blank end, pipe (approx 80mm),
straight coupler. Watchmaker's eyeglass 31mm focal length.

Control Unit

The control unit is designed to supply the necessary DC power to the transmitter and receiver and to process the voltage pulses from the receiver. The unit is powered from 240V AC and must be mounted indoors away from rain and moisture.

The unit constantly monitors the voltage pulses from the receiver and if the pulses disappear (the beam is interrupted) then one or two alarm channels may be activated — the light channel and the audible alarm channel.

The light channel may be used to power an outside floodlamp to really throw light on the scene of the crime or the channel may be used to turn on an internal house light to fool the burglar into thinking someone is coming to investigate.

During the hours of daylight a light dependent resistor senses the ambient light level and inhibits operation of the light channel. This has the advantage that the householder does not have to remember to turn on the alarm at night and off next morning. When 24-hour protection is required, the audible alarm channel may be activated by means of a switch. Either a mains powered alarm may be used or a 12V DC piano sander. (The weirder the alarm sounds the better. If the brain does not recognise a sound it is thrown into confusion and this adds to the deterrent

aspect of any burglar alarm.)

The control unit is fitted with an LED which indicates when the beam is established so that the householder can confirm that there is nothing blocking the beam before he activates the audible alarm channel. A flashing LED is also fitted to remind the owner that the audible alarm channel is set to avoid him accidentally setting off the alarm himself.

Construction — Transmitter

Ensure that the circular PCB (see Fig. 3) will fit into the plastic pipe blank end before fitting the resistors, capacitors and semiconductors. Solder the positive and negative supply leads to the rear of the PCB. The leads should be of a suitable length to run from the required location of the transmitter outdoors to a junction box indoors. Supply cables can then be run from the junction box to the control unit.

Connect the leads to a 12V DC supply to confirm that the circuit operates correctly and the LED is seen to flash at about 3-4Hz. The circuit can then be fitted to the blank end by drilling a hole in the rear of the blank end, passing the leads through the hole and then sealing the whole blank end assembly with silicone rubber or other suitable potting compound.

The PCB may be held in place with adhesive tape while the compound is solidifying. The

PROJECT

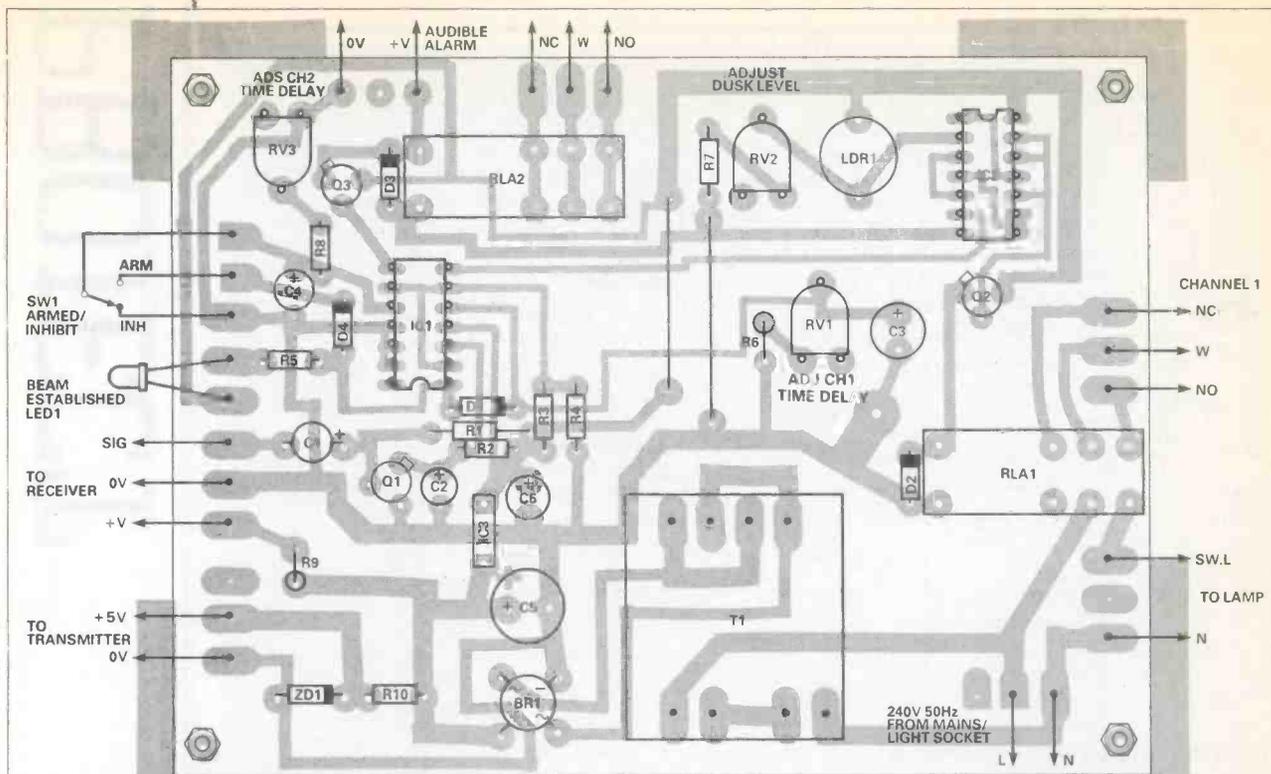


Fig. 5 Component overlay for the control unit PCB

completed assembly can then be screwed into the other section of the blank end which in turn can be inserted into the straight coupler.

A watchmaker's eyeglass of focal length 31mm is used as the collimating lens. Choose an eyeglass which has an outside diameter which is slightly larger than the outside diameter of the plastic pipe (cut according to Fig. 3). The eyeglass is secured to the end of the pipe with sealant or adhesive and when the adhesive is dry, the eyeglass body may be filed until it is flush with the outside diameter of the pipe. The whole assembly can then be inserted in the straight coupler.

HOW IT WORKS

Control unit

Transistor Q1 and associated components (see Fig. 6) are connected as a missing pulse detector. As long as 0V going pulses are being received at C1, C2 is repetitively discharged by Q1. The output of IC1 is normally 0V and thus the 'beam established' LED is illuminated via R5.

If the pulses at C1 cease then C2 charges up to 12V via R2. When the voltage at C2 exceeds that set at pin 2 of IC1a by R3 and R4, the output of IC1 goes high. This causes C3 to be quickly charged up via D1 thereby triggering the 'light channel' alarm circuit.

IC1b, RV1, R6 and C3 function as a monostable circuit which dictates how long the light remains on once the alarm has been triggered.

The light is only turned on during the hours of darkness however and this function is controlled by the quad NAND gate IC2. At dusk, the resistance of the LDR starts to increase. When the voltage at the junction of the LDR and RV2 falls below the switching threshold of IC2a pin 2, then pin 3 goes high and so the two logic 1s at pins 5 and 6 of IC2a cause its output to go low and the light is turned on via IC2c, Q2 and RL1.

IC2d prevents the light from being turned off again when its own light falls on the LDR. The time the light remains on once triggered may be adjusted by RV1.

If the audible alarm channel is required then SW1 must be placed in the *Armed* position. If the infra-red beam is interrupted and IC1a goes high, then the monostable formed by RV3, R8, C4 and IC1c is triggered and the audible alarm is energised via Q3 and RL2. A 12V DC audible alarm may be connected between the emitter of Q3 and

The position of the collimating lens with respect to the infra-red sensor can be adjusted by sliding the pipe/lens assembly in and out of the coupler until the infra-red sensor is at the focal point of the lane. It may be necessary to smear the rubber O-ring in the coupler with Vaseline to make this operation easier. The final position of the lens may be set when the complete system is commissioned.

Construction - Receiver

Construction of the receiver (see Fig. 4) is similar to the transmitter. Only the LED is fitted so as to protrude

0V, but if a mains powered unit is used then the normally open contacts of RL2 may be used.

A second pole of SW1 is used to connect the 5V supply at ZD1 to a flashing LED. This reminds the user that the audible alarm channel has been activated. If the alarm is triggered when the householder is at home, the quick discharge of C4 by SW1a when the switch is operated ensures that the alarm is quickly silenced and does not continue for the time period set by RV3, R8 and C4.

Receiver

The circuit diagram is shown in Fig. 7.

IC1 provides a stabilised 12V supply for the infra-red receiver Q1. Pulses from the receiver are AC coupled by C2 to IC2 which is connected as a comparator. When the amplitude of the pulses exceeds the offset between pins 3 and 2 produced by R2, R3 and R5, the output of IC2 goes from positive to negative saturation. An indication that a pulse of infra-red has been received is given by the LED driven by Q2. This is a very useful facility when attempting to align the receiver to the transmitter.

Transmitter

The circuit is as shown in Fig. 8.

IC1 is connected as an astable multivibrator which produces narrow 0V going pulses at pin 3 of a repetition frequency of a few Hz. Current gain is provided by Q1 so as to drive the infra-red transmitter in series with the LED. The LED gives a brief pulse of light in synchronism with the infra-red pulses and is useful to indicate operation of the transmitter when commissioning the system.


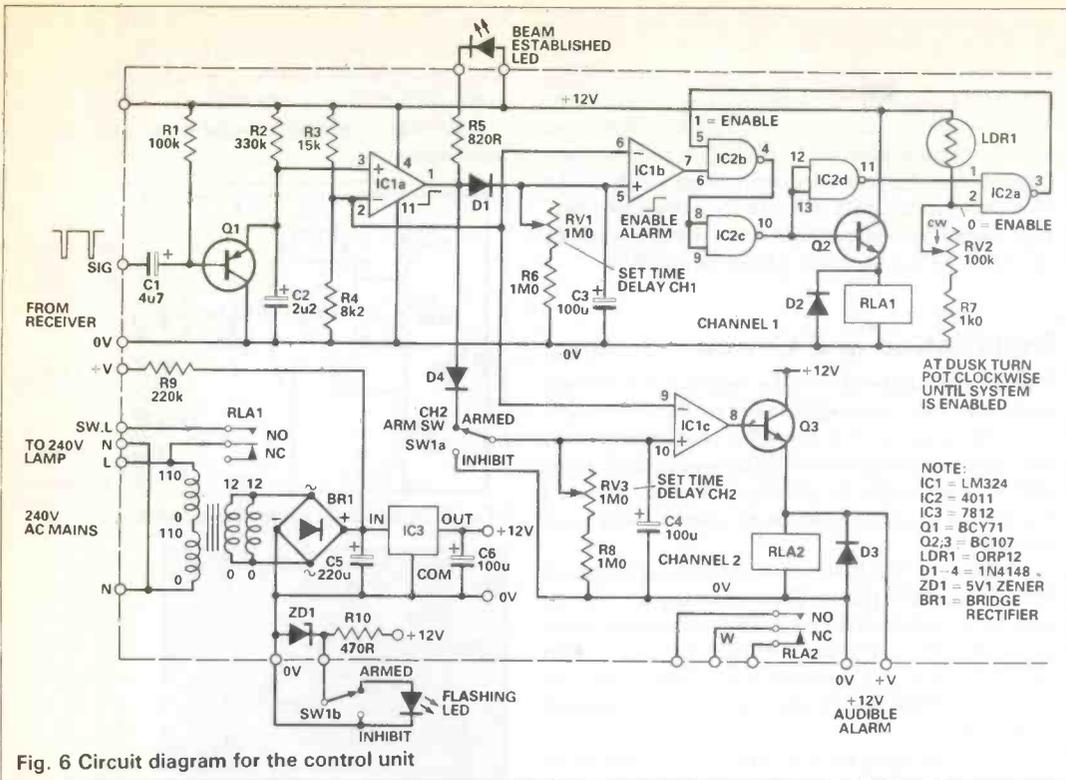


Fig. 6 Circuit diagram for the control unit

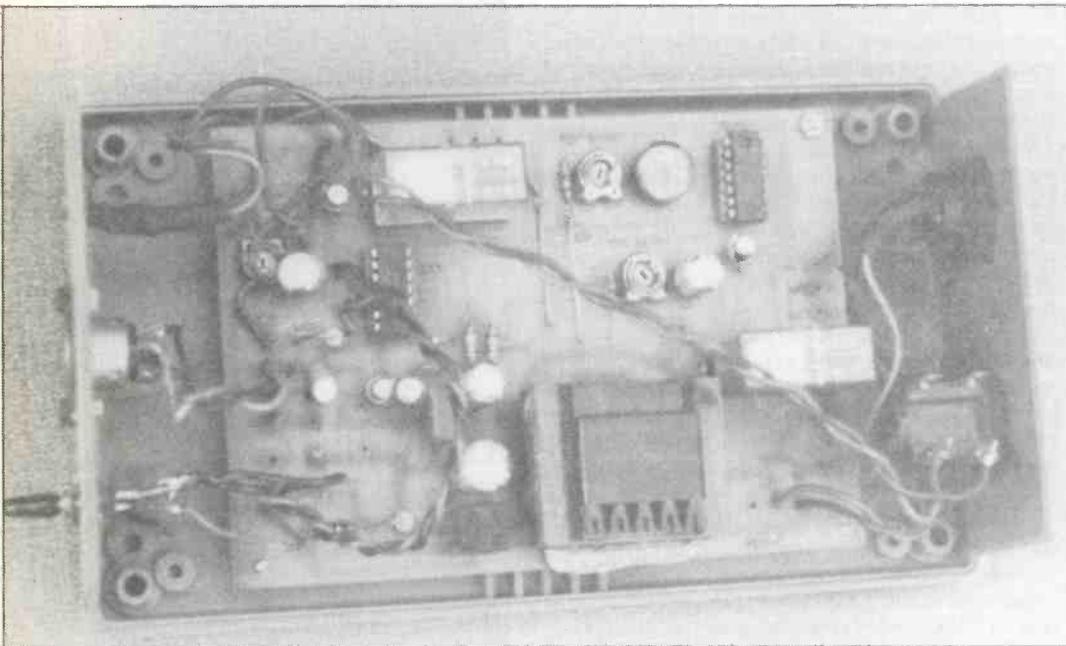

through a second hole in the rear of the blank end. The receiver can only be checked by lining it up to the infra-red pulsed beam produced by the transmitter and checking that the LED on the receiver flashes in sympathy with the transmitter pulses.

Control Unit

The component overlay is shown in Fig. 5.

Fit the power supply components first and test this section before fitting the remainder of the components. It is wise to fit sockets for the integrated circuits so that they may be inserted one at a time.

The control unit PCB should be tested before it is fitted in its case as follows. Temporarily connect the receiver and the transmitter to the control unit and align them so they point directly at each other. Insert IC1 into its socket and check that the "beam established" LED on the control unit is lit. Interrupt the beam and check that the LED extinguishes.

Insert IC2 and simulate darkness by masking off

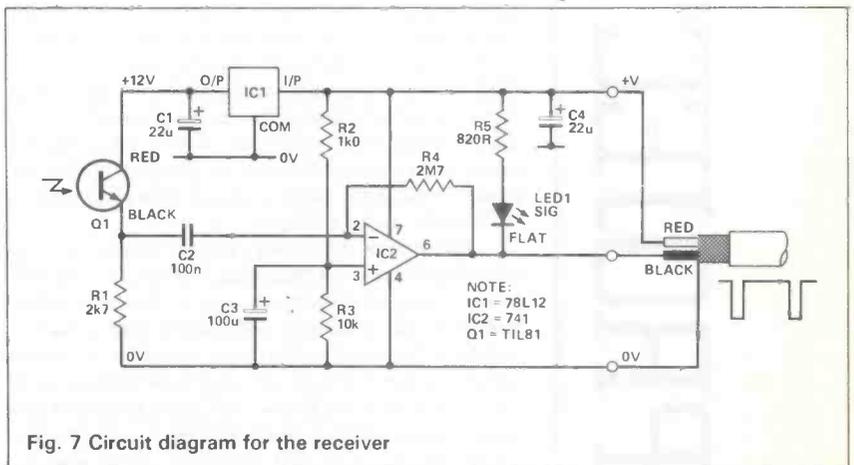


Fig. 7 Circuit diagram for the receiver

The Intruderbeam Active Infra-red Alarm is available in kit form from GP Electronic Services, 87 Willowtree Avenue, Durham City, DH1 1DZ. Tel: 091-384 9707.

Control unit

Full kit including PCB, transformer switch and sockets (but excluding case and audible alarm) £19.50.

PCB only £8.95.

Transmitter

Full kit including PCB (excluding case and lens) £4.50.

PCB only £2.75.

Receiver

Full kit including PCB (excluding case and lens) £4.50.

PCB only £2.75.

the LDR with dark-coloured tape or Plasticene. Check that the relay RL1 operates when the beam is broken and remains energised for a time period adjustable by RV1. The relay should fail to operate if the masking from the LDR is removed and the ambient light level is above the threshold set by RV2. The audible alarm channel may be tested by connecting a link on the PCB to simulate SW1 being in the armed position. RL2 should operate when the beam is broken and stay operated for a time delay adjustable by RV3.

Installation and Commissioning

The installation should only be started when all three units have been thoroughly tested on the workbench.

The transmitter and receiver should be sited so that the beam covers the required area close to doors and windows as the psychological effect is greater if the alarm is triggered when the prowler is close to your property.

The mounting brackets for the transmitter should be adjusted in two planes. This is to enable the receiver and the transmitter to be aligned for maximum signal. The cables should be passed through holes in door or window frames to junction boxes indoors (in case one of the units develops a fault and has to be replaced or repaired).

An ideal siting for the control unit is above an entrance door in the room where the light fitting is to be coupled up to the light alarm channel. The live neutral and switched live will be available at the ceiling rose of the light and these three connections are all that is required to both power the control unit and facilitate the light alarm channel.

Power up the control unit and align the transmitter to the receiver by eye. Confirm that the transmitter is functioning correctly by observing the flashing LED through the collimating lens. Adjust the angle of the receiver for maximum brightness of its flashing LED at the back of the unit. It may then be necessary to adjust the position of the transmitter, although two people may be required for this step — one to watch the receiver LED and the other to adjust the transmitter. If an oscilloscope is available, the amplitude of the pulses at the control unit may be monitored while fine adjustments are made to the positions of both the receiver and transmitter until the pulses are at their maximum amplitude.

Once their positions have been optimised the transmitter and receiver should be securely clamped so that they cannot be easily moved. Check that the 'beam established' LED is lit on the control unit and is seen to extinguish when the beam is interrupted.

The light alarm channel may be tested by temporarily masking off the LDR with tape. After testing, remove the tape, turn RV2 fully anti-clockwise and interrupt the beam with an opaque object. When the ambient light at dusk has reached the level at which operation of the light channel is required, turn RV2 slowly clockwise until the room light being controlled, illuminates. The audible alarm channel is simply tested by throwing the switch to the 'armed' position. By experimentation, set RV1 and RV3 to the desired time delay periods for the light channel and the audible alarm channel.

Remember that any burglar alarm is only effective if someone responds when it is triggered. Many people leave their homes protected by an alarm system while on holiday and assume that someone will act if the alarm is triggered. In reality not many people can be bothered and alarms are heard to ring for hours until a neighbour can't stand the noise any longer and telephones the police. By then the thieves could have made off with the entire contents of the

house. The Intruderbeam resets after the time period set by RV3 so incessant noise from the alarm is less likely, nevertheless it is wise to ask a friendly neighbour to at least have a look over the fence at your property if they hear your alarm sound when you are away from home.


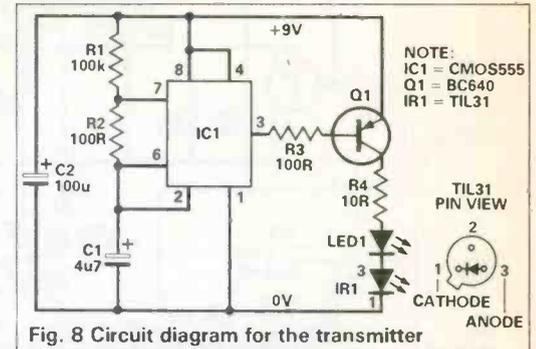


Fig. 8 Circuit diagram for the transmitter

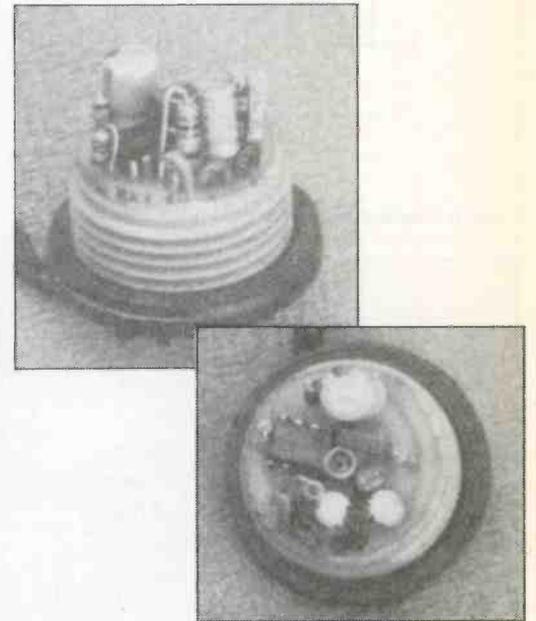

THE TRANSMITTER-RECEIVER

When connected to 5-9V DC the transmitter gives short pulses of infra-red light at about 900nm wavelength, collimated into a narrow beam which is aimed at the receiver.

A light emitting diode gives pulses of visible red light in sympathy with the infra-red. A quick test can thus be made by looking directly into the lens.

The transmitter will operate satisfactorily at any DC voltage between 4V and 10V. Ensure that the correct connections are made otherwise the transmitter may be damaged.

The transmitter should be securely mounted on a wall or similar rigid structure and aimed at the infra red receiver. It is desirable to mount the unit at waist height so that cats and dogs do not interrupt the beam.

The receiver will operate satisfactorily at any DC voltage between 8V and 25V. Ensure that the correct connections are made again. The purple lead gives the output signal of voltage pulses.

The receiver should not be mounted such that strong sunlight can shine directly into the lens aperture.

The angle should be slowly adjusted until the LED at the rear of the casing is seen to flash at regular intervals. Make fine adjustments of the angle in both planes (vertical and horizontal) until the flashes are at their brightest.

The transmitter-receiver combination has been tested and proved to be satisfactory at distances of up to 60 feet. Once the transmitter-receiver combination have been accurately aligned they should be securely clamped so they cannot be accidentally mis-aligned.

PROJECT


No. 1 LIST BAKERS DOZEN PACKS

All packs are £1 each, if your order 12 then you are entitled to another free. Please state which one you want. Note the figure on the extreme left is the pack ref number and the next figures is the quantity of items in the pack, finally a short description.


- BD2 5 13A spurs provide a fused outlet to a ring main where device such as a clock must not be switched off
- BD7 4 in flex switches with neon on/off lights, saves leaving things switched on
- BD9 2 6v. 1A mains transformers upright mounting with fixing clamps
- BD11 1 6 1/2" speaker cabinet ideal for extensions, takes your speaker. Ref BD137 + 50p.
- BD13 12 30 watt reed switches, it's surprising what you can make with these — burglar alarms, secret switches, relay etc. etc
- BD22 2 25 watt loud speaker two unit cross-overs
- BD29 1 B.O.A.C. stereo unit is wonderful breakdown value
- BD30 2 nicad constant current charges adapt to charge almost any nicad battery
- BD32 2 humidity switches, as the air becomes damper the membrane stretches and operates a microswitch
- BD42 5 13A rocker switch three tag so on/off, or change over with centre off
- BD45 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day.
- BD49 5 neon valves, with series resistors, these make good night lights
- BD56 1 mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through on pole
- BD59 2 flat solenoids — you could make your multi-tester read AC amps with this
- BD67 1 suck or blow operated pressure switch, or it can be operated by any low pressure variations such as water level in water tanks
- BD103A 1 6v 750mA power supply, nicely cased with input and output leads
- BD120 2 stripper boards each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers etc
- BD128 10 very fine drills for p.c.b. boards etc. Normal cost about 80p each
- BD132 2 plastic boxes approx. 3" cube with square hole through top so ideal for interrupted beam switch
- BD134 10 motors for model aeroplanes, spin to start so needs no switch
- BD139 6 microphone inserts — magnetic 490 ohm also act as speakers
- BD149 4 reed relay kits you get 16 reed switches and 4 coil sets with notes on making 10 relays and other gadgets
- BD149 6 safety cover for 13A sockets — prevent those inquisitive little fingers getting nasty shocks
- BD180 6 neon indicators in panel mounting holders with lens
- BD193 6 5 amp 3 pin flush mounting sockets makes a low cost disco panel — need cable clips
- BD196 1 in flex simmerstat — keeps your soldering iron etc always at the ready
- BD199 1 mains solenoid very powerful has 1" pull or could push if modified
- BD201 8 keyboard switches — made for computers but have many other applications
- BD211 1 electric clock mains operated put this in a box and you need never be late
- BD221 5 12v alarms make a noise about as loud as a car horn. Slightly solid but OK
- BD242 2 6" X 4" speakers 4 ohm made from Radiomobile so very good quality
- BD252 1 panostat, controls output of boiling ring from simmer to boil leads with push on 1/2" tags — a must for hook ups — mains connections etc
- BD259 50 oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattern
- BD268 1 mini 1 watt amp for record player. Will also change speed of record player motor
- BD283 3 mild steel boxes approximately 3" X 3" X 1" deep — standard electrical
- BD293 50 mixed silicon diodes
- BD305 1 tubular dynamic mic with optional table rest
- BD367 2 4.7uf, non-polarised block capacitors, pcb mounting
- BD400 4 Books. Useful for beginners. Describes amplifiers, test equipment and kit sets
- BD653 2 Miniature driver transformers. Ref LT44. 20k to 1k, centre tapped
- BD553a 2 3.5 volt operated relays, each with two pairs CO contacts
- Most other packs still available and you can choose any as your free one.
- CAMERAS.** Three cameras, all by famous makers. Kodak, etc. One disk, one 35mm and one instamatic. All in first class condition, believed to be in perfect working order, but sold as untested. You can have the three for £10 including VAT, which must be a bargain — if only for the lenses, flash gear, etc. Our ref 10P58.
- 675 VOLT MAINS TRANSFORMER.** PCB mounting. 20va. A very well made (British) transformer. Ideal for laser power supply, etc. Price £4. Our ref 4P38.
- PRETTY CASSETTE PLAYER.** In handy carrying pouch with silk shoulder cord. Ideal present for a young girl. New, tested and in perfect order. Just needs headphones and batteries. Price £4. Our ref 4P35.
- EXTRA SPECIAL CROC CLIPS.** Medium size, just right for most hook-ups. Normally set for around 10p to 15p each. These are insulated and have a length of wire connected to them but this is very easy to snip off if you do not need it. 20 for £1. Our ref BD117A.
- IONISER FOR YOUR CAR.** Experts say that positive ions predominate in a car and can cause you to feel sleepy so we now offer a car ioniser to counteract this. It plugs into the cigarette lighter socket. Price £12 for the complete kit. Our ref 12P8. Our famous transformer operated room ioniser is still available at £12.50. We claim this to have ten times more output than the ETI, the Equaliser and in fact most other popular kits and ready built ionisers.
- COPPER CLAD PANEL.** For making PCB. Size approx 12in long X 8 1/2in wide. Double-sided on fibreglass middle which is quite thick (about 1/8in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref BD683.

POWERFUL IONISER

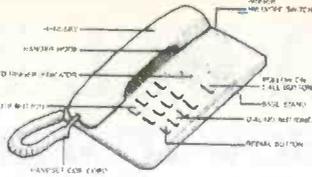Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, shop/workroom etc. Makes you feel better and work harder — complete mains operated kit, case included £12.50 + £2 P&P. Our ref 12P5/1.



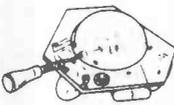MODERN TELEPHONE. Two-piece push-button desk or wall mounting telephone. Fitted with standard BT flat plug for immediate use. Standard model £8. Our ref 8P31. Or similar but with 10 memory feature £10. Our ref 10P68. If not collecting add £2 for special packing.



ELECTRONIC SPACESHIP. Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the components on the pcb. Complete kit £8. Our ref 8P30.

DATA RECORDER FOR COMPUTERS. For playing games or listening to music cassettes. It has a built-in condenser microphone and loud speaker (muted if you use the extension socket). Has the following controls: pause, stop/eject, fast forward, rewind, play and record. Also has built-in tape counter, extension headphone and microphone socket and volume control. Built-in power supply enables it to run from the mains but provision also for battery operation. In 'as new' condition, but customer returns so may have fault. Price only £10 and if you order 4 you get a first one free. Our ref 10P65.

BUSH RADIO MIDI SPEAKERS. Stereo pair. BASS reflex system, using a full range 4in driver of 4 ohms impedance. Mounted in very nicely made black fronted walnut finish cabinets. Cabinet size approx 8 1/2in wide, 14in high and 3 1/2in deep. Fitted with a good length of speaker flex and terminating with a normal audio plug. Price £5 the pair plus £1 post. Our ref 5P141.

3 1/2in FLOPPY DISC DRIVE — DOUBLE SIDED, DOUBLE DENSITY, 80 TRACK. Shugart compatible, has 34 way IDC connector and will interface with almost any computer. Made by the famous Japanese NEC Company. Price £59.50 plus £3 insured post.



ATARI 65XE COMPUTER. At 64k this is most powerful and suitable for home and business. Brand new, complete with PSU, TV lead, owner's manual and six games. Can be yours for only £45 plus £3 insured delivery.

65XE COMPENDIUM. Contains: 65XE Computer, its data recorder XC12 and its joystick, with ten games, for £62.50 plus 14 insured delivery.

AGAIN AVAILABLE: ASTEC PSU. Mains operated switch mode, so very compact. Outputs: +12v 2.5A, +5v 6A, +5v .5A, ±12v .5A. Size: 7 1/2in long X 4 1/2in wide X 2 1/2in high. Cased ready for use. Brand new. Normal price £30+ our price only £10. Our ref 10P34.

VERY POWERFUL 12VOLT MOTOR. 1/2 Horsepower. Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20 plus £2 postage. Our ref 20P22.

PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe so long as you do not look directly into the beam when eye damage could result. Brand new, full spec, £30 plus £3 insured delivery. Mains operated power supply for this tube gives 8kV striking and 1.25kV and 5mA running. Complete kit with case £15. Ditto for 12v battery, also £15. Our ref 15P22.

ORGAN MASTER. Is a three octave musical keyboard. It is beautifully made, has full size (piano size) keys, has gold plated contacts and is complete with ribbon cable and edge connector. Can be used with many computers, request information sheet. Brand new, only £15 plus £3 postage. Our ref 15P15.

FULL RANGE OF COMPONENTS. At very keen prices are available from our associate company SCS COMPONENTS. You may already have their catalogue, if not request one and we will send it FOC with your goods.

HAND-HELD VIDEO LAMP. Mains operated and will enable you to take professional standard videos. Made by the famous Ferguson Company, this uses a 1000W halogen lamp in a fan cooled, hand-held and hand-switched metal housing. Comes complete with optional bar-door assembly and camera bar. Obviously intended to retail at over £60, we offer these at £30 each plus £3 insured delivery. Our ref 30P3.

HIGH RESOLUTION MONITOR. 9in black and white, used Philips tube M24/306W. Made up in a lacquered frame and has open side. Made for use with ODP computer but suitable for most others. Brand new, £16 plus £5 post. Our reference 16P1.

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape 4 1/2in X 4 1/2in X 1 1/2in. The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26.

MONO RADIO CASSETTE RECORDER. AM/FM with all the normal controls. In 'as new' condition but customer returns or shop rejects, so may need attention. Price £10. Order 5 of these and get a sixth one free. Our ref 10P66.

FDD BARGAIN

3 1/2in made by Chinon of Japan. Single sided, 80 track Shugart compatible interface, interchangeable with most other 3 1/2in and 5 1/4in drives. Completely cased with 4 pin power lead and 34 pin computer lead. £40 plus £3 ins del. Our ref 40P1.

MINI MONO AMP. on p.c.b. size 4" X 2" (app). Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each or 13 for £12.00



J & N BULL ELECTRICAL

Dept. E.T.I., 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QT.

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £20 add £1.50 service charge. Monthly account orders accept from schools and public companies. Access & Barclaycard orders are accepted — minimum £5. Phone (0273) 734448 or 203500

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES. 140v 100w pair made by the famous Hitachi Company. Reference 25K413 and its complement 25J118. Only £4 the pair. Our ref 4P42.

HI-VOLT CAPS. Not ceramic but the much more reliable foil type. Good range from 1nf to 35uf at voltages 1kv to 2.5kv. Keen prices, good quantity discounts. Request list.

AGAIN AVAILABLE — THE SOLID STATE RELAY. Will switch up to 10A AC load and can be triggered by very small current from photo cell, computer, etc. £2 each. Our ref 2P183.

BATTERY OPERATED TRAVEL MECHANISM. On a plastic panel measuring approx 9in X 3 1/2in. Is driven by a reversible 12v battery motor, fitted with pulley and belt which rotates a threaded rod and causes a platform to travel backwards and forwards through a distance of approx 5in. Price £5. Our ref 5P140.

MAINS OPERATED WATER VALVE with hose connection for inlet and outlet suitable for low pressure. Auto plant watering, etc. Only £1 each. Our ref BD370.

20 VOLT 4 AMP MAINS TRANSFORMER. Upright mounting with fixing feet. Price £3. Our ref 3P59.

12 VOLT SOLENOID. Has good 1/2in pull or could be made to push if fitted with a rod. Approx 1 1/2in long by 1in square. Price £1. Our ref BD232A.

16 OHM PM SPEAKERS. Approx 7in X 4in. 5 watts. Offered at a very low price so you can use two in parallel to give you 10 watts at 8 ohms. £1 for the two. Our ref BD684.

EHT TRANSFORMER. 4kv 2mA Ex-unused equipment. £5. Our ref 5P139.

4 CORE TINSEL COPPER LEAD. As fitted to telephones, terminating with flat BT plug. 2 for £1. Our ref BD639.

EHT TRANSFORMER. 8kv 3mA £10. Our ref 10P56.

DOUBLE MICRODRIVES. We are pleased to advise you that the Double Microdrives which we were offering at about this time last year as being suitable for the 'QL', 'DPD' and several other computers are again available, same price as before namely £5. Our ref 5P113.

VERY USEFUL MAGNETS. Flat, about 1in long, 1/2in wide and 1/4in thick. Very powerful. 6 for £1. Our ref BD274(a).

ACORN COMPUTER DATA RECORDER. Ref ALF.03. Made for the Electron or BBC computers but suitable for most others. Complete with mains adaptor, leads and handbook. £10.00. Ref 10P44. Add £2 special packing.

SOLAR CELLS. Will give a good current (depending on size) from sunlight or bright daylight. Module A give 100mA. Price £1. Our ref BD631. Model C gives 400mA. Price £2. Our ref 2P199. Model D gives 700mA. Price £3. Our ref 3P42.

SOLAR POWERED NI-CAD CHARGER. 4 NI-CAD batteries AA (HP7) charged in eight hours or two in only 4 hours. It is complete, boxed ready to use unit. Price £6. Our ref 6P3.

METAL PROJECT BOX. Ideal size for battery charger, power supply etc: sprayed grey, size 8" X 4 1/2" X 4 1/2" high, ends are lowered for ventilation other sides are flat and undrilled. Order ref 2P191. Price £2.

4-CORE FLEX CABLE. Cores separately insulated and grey PVC covered overall. Each core covered 7/02mm. Ideal for long telephone runs or similar applications even at mains voltage. 20 metres £2. Our ref 2P196 or 100 metres coil £8. Order ref 8P19.

6-CORE FLEX CABLE. Description same as the 4-core above. Price 15 metres for 12. Our ref 2P197 or 100 metres £9. Order ref 9P1.

13A PLUGS. Good British make complete with fuse, parcel of 5 for £2. Order ref 2P186.

13A ADAPTERS. Takes 2 13A plugs, packet of 3 for £2. Order ref 2P187. 20v - 0 - 20v. Mains transformers 2 1/2 amp (100 watt) loading, tapped primary. 200-245 output mountings £4. Our ref 4P24.

BURGLAR ALARM BELL. 8" gong OK for outside use if protected from rain. 12V battery operated. Price £8. Ref 8P2.

CAPACITOR BARGAIN. Axial ended — 4700uf @ 25v Jap made. Normally 50p each, but you will get 4 for £1. Ref 613.

SINGLE SCREENED FLEX. 7.02 copper conductors, pvc insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m for £1. Our ref BD668.

M.E.S. BULB HOLDERS. Circular base batten type fitting. 4 for £1. Our ref DB127s.

SPRING LOADED TEST PRODS. Heavy duty, made by the famous Bulgin company. Very good quality. Price four for £1. Ref BD597.

3 CORE FLEX BARGAIN No. 1. Core size 5mm so ideal for long extension leads carrying up to 5 amps or short leads up to 10 amps. 15mm for £2. Order ref 2P189.

3 CORE FLEX BARGAIN No. 2. Core size 1.25mm so suitable for long extension leads carrying up to 13 amps — or short leads up to 25A, 10m for £2. Order ref 2P190.

ALPHA-NUMERIC KEYBOARD. This keyboard has 73 keys with contactless capacitance switches giving long trouble free life and no contact bounce. The keys are arranged in two groups, the main area field is a QWERTY array and on the right is a 15 key number pad, board size is approx 13" X 4" — brand new but offered at only a fraction of its cost namely £3, plus £1 post. Ref 3P27.

1/4TH HORSEPOWER 12 VOLT MOTOR. Made by Smiths, the body length of this is approximately 3in, the diameter 3in and the spindle 1/4th of an inch diameter. It has a centre flange for fixing or can be fixed from the end by means of 2 nuts. A very powerful little motor which revs at 3,000 rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price £6. Our ref 6P1, discount for quantities of 10 or more.

3 VOLT MOTOR. Very low current so should be very suitable for working with solar cells. £1 each. Our ref BD681.

MINI SPEAKERS. To use instead of headphones with your personal stereo — simply plug into earphone socket. Excellent sound quality, only £4 per pair. Our ref 4P34.

INNER EAR STEREO HEADPHONES. Ideal for lady listeners as they will not mess up your hair! Come complete in a neat carrying case. Price £3. Our ref 3P56.

STEREO HEADPHONE AMPLIFIER. Very sensitive. A magnetic cartridge or tape head will drive it. Has volume control and socket for stereo headphones. 3v battery operated. £1 each. Our ref BD680.

FET CAPACITOR MICROPHONE EAGLE CI.200. Output equivalent to a high class dynamic microphone while retaining the characteristics of a capacitor microphone. Price £1. Our ref BD646.

SUB-MAN TOGGLE SWITCH. Body size 8mm X 4mm X 7mm SBDT with chrome dolly fixing nuts. 4 for £1.00. Order ref BD649.

SUB-MIN PUSH SWITCH DPDT. Single hole fixing by hexagonal nut. 3 for £1. Our ref BD650.

POLYBEL TUNEWARE

HOW TO SERENADE IN HEX

Trevor Skeggs explains the Polybel Operating System — PBOS — and teaches his polyphonic programmable doorbell to sing a new tune

The September issue of ETI saw (heard?) your Polybel Programmable Music Generator built and tested (I hope) and now you find you're no longer inviting people around on any excuse merely so that they can press your door-push and go gosh. You're bored! Or perhaps the music is too square/hip/sedate/brash? Time to re-program!

There will be three categories of owner amongst you. Firstly those who, as long as it plays a 'toon', couldn't give a damn... these may as well proceed to the next article. Then there is the EPROM owner who wants to 'have-a-go' — you may either skip to the encoding section, or read the next bit jealously. Lastly there is the lucky EEPROM owner, anxious to find out why he's paid extra for it...

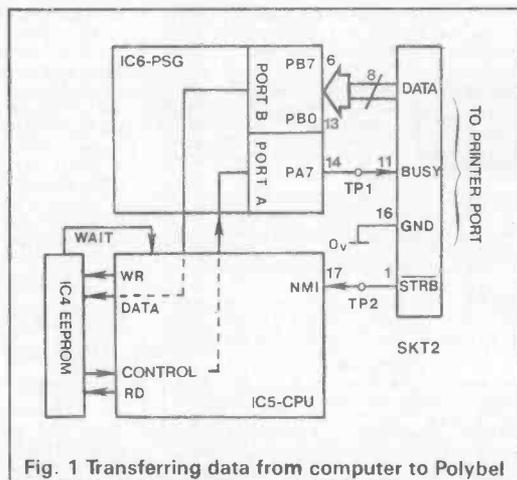
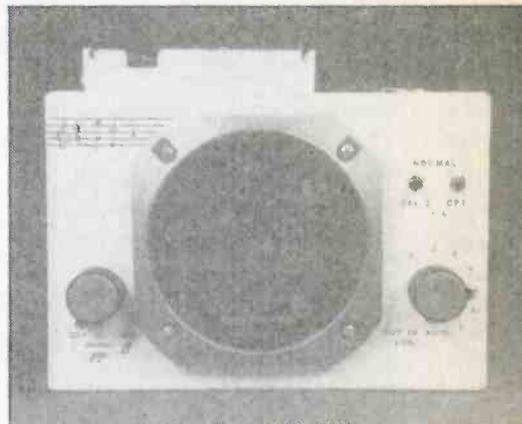


Fig. 1 Transferring data from computer to Polybel

Printing to Polybel!

As stated last month, Polybel accepts data over an 8-bit bus from a home computer. This means that Polybel must try to impersonate a printer. This masquerade is exposed in Fig. 1.

The data from your computer arrives at the Centronics socket over a standard cable (Fig. 2). Here the 8-bit data bus is wired (via the rotary switch — which must be open-circuit — and the DIL header SKT1) to the Programmable Sound Generator (PSG). The active-low *strobe* is taken via a separate wire to the Non-Maskable Interrupt of the Z80 (test-point near C11 on supplied boards or if not fitted then on the lower-end of R12).

The acknowledgement *busy* is taken, via a separate wire, from test-point TP1 near SKT1.

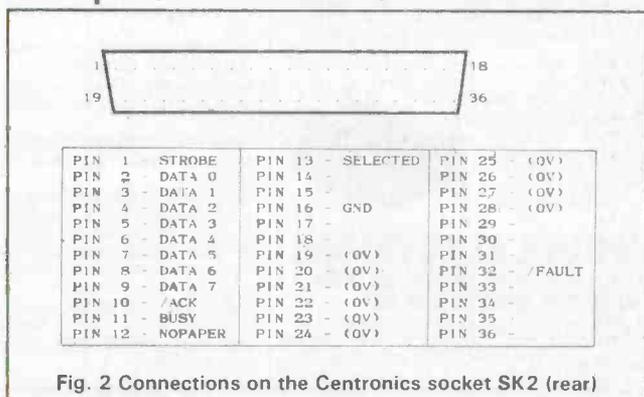


Fig. 2 Connections on the Centronics socket SK2 (rear)

Procedure

How you enter programming mode on the Polybel is dictated by the characteristics of your computer.

Most computers will check *online*, *no paper* and *error* via the *fault* line. Sometimes this will float high (no fault) if not connected whilst others may require sourcing to +5V. This may be checked by attempting to print a character with the printer disconnected. In the event of an error, it may be possible to link this to +5V at the computer socket, else to +6V at SKT2 via a diode and resistor.

Similarly, most computers will check *busy*, and this may or may not require an active current. If it does, then the printer will appear 'ready' when disconnected — when Polybel is off it will accept the first byte. Again, you can test this (having solved the 'fault' problem) by seeing if you can print into free space.

Polybel enters programming mode by either a negative-edge on NMI after having powered-up (that is printing to it when it is active), or by a zero byte on Port B at power-up (that is sending a null byte before it becomes active).

Here then is a possible procedure. Firstly write a data file by any means available to your computer, using the codes detailed in the next section. Preface this file with:

- One or more null bytes.
- Start-code byte, &AA.
- The start address in hex divided by 8 (eg &B0 for &580).
- The length, from 1 to 256 (represented by zero) bytes.

The operating system in pages 0 and 7 must not be overwritten, so keep the address code between &20 (buffer 1) and &C0 for safety.

Connect the printer cable to Polybel, which should be off. Set all switches open-circuit (position C). Send the first (null) byte of the data file, probably with PRINT CHR\$(x). Trigger the unit. Polybel should respond with a 'peep'. Send the data file. Polybel should respond with a 'peep' if the start and address bytes are acceptable, or a raspberry if not.

Tuneware

The operating system interprets buffer codes and manipulates the PSG accordingly. Like a micro-processor instruction set, these codes may be one, two

PROJECT

or three or more bytes in length. Again like a micro, most instructions are single-byte and explicit. The tinted box of instructions lists them all and what they do.

Pitch

The AY-3-8910 PSG chip has one major shortcoming: the clock is pre-scaled by 16 before being divided by the divisor of our choice. In practice this renders the top octaves (smallest divisors) too inaccurate for serious work, especially at 1MHz.

To circumvent this problem, the unusual step of using the 'just scale' has been taken. This means that all notes have a relatively simple numerical ratio to each other and some musicians do not like this because, for example, the note 'G' would contain the same frequency as the 3rd harmonic of 'C'. The look-up table at &0D0-0DF (Listing 1, September) may be replaced by any scale you wish — such tables are often to be found in home-computer BASIC manuals.

Figs. 3 and 4 show the codes for setting the most-used pitches. They are not called 'notes' here because they do not necessarily by themselves create sound (the channel volume or envelope must be enabled).

INSTRUCTIONS

SINGLE-BYTE CODES

&00 and &FF	These do precisely nothing — they are ignored! Strangely enough, this makes them invaluable for EPROM users as the NOP code (&FF) can be liberally sprinkled throughout your code wherever uncertainty exists (tempo or envelope period etc). Then when changes are required, the original code can be rubbed-out (&00) and the blank codes re-programmed without erasing the PROM under UV light. (Do remember, when apparently getting the wrong tune played that the operating system will scan through blank buffers!)
&01-&4F	These codes select various notes for channels A, B or C. See <i>Pitch</i> in the main text.
&70-&7F	Produces one of sixteen tempo-related time-delays. See <i>Timing</i> in the main text.
&50-&5F	A special tremolo (mandolin-like) version of code 7x (only for channels enabled in auto-envelope mode).
&60-&6F	Initiates auto-envelope then behaves as delay-code 7x.
&80-&8F	Manual volume of channel A.
&90-&9F	Manual volume of channel B.
&A0-&AF	Manual volume of channel C.
	Cancels auto-envelope mode for that channel and forces volume from off (&x0) to maximum (&xF).
&C0-&CF	Sets the envelope period for the auto-envelope. Has a restricted range from short clunk (&C1) to medium (piano/guitar). Longer envelopes are obtained by manipulation of register 14.
&D0-&DF	Initiate certain attack/decay envelopes. See AY-3-8910 data manual for full details.
&E0-&E3	Set the bits of Port A which control the filters. For example &E2 sets pin 20 high to turn on the bass filter. Codes &E4 and &E8 are free for you to experiment with (setting spare pins 19 and 18).
&F8-&FA	Put channels A, B or C into auto-envelope mode. The envelope is triggered by delay-code 6x, provided that a suitable envelope period has been set.

DOUBLE-BYTE CODES

&Br dd	Put data byte dd into PSG register r. Direct manipulation of any PSG register serves as a general-purpose fill-in when no shorter code will suffice. The AY-3-8910 handbook is essential for this.
&FO nt	Amplitude decay on channel A.

Sharps, flats, higher and lower octaves are obtained by direct manipulation of the PSG registers.

Channel A is usually reserved for the bass because of its extra filtering. Channel C therefore carries the treble or melody line, and Channel B the alto (stop me if I get too musical for you). Although Channel B can descend into the bass regions (codes &30-&3A), these tend to sound raspy because of insufficient filtering.

Timing

Benefitting from experience of other music programs, where tempo is a matter of trial-and-error and triplets are out of the question, Polybel's Operating System (PBOS) has very precise timing.

The tempo is expressed as beats per quarter-minute (converted to hex) if the meanings of Fig. 5 are to be used (where 1 beat = code &57, &67 or &77). Thus the code for a tempo of 60 beats/minute is $60/4 = 15 = \&0F$ (preceded by &FE, the 'set tempo' byte). One beat will then give a precise delay of one second.

In practice this is too slow even for a death march. A more practical list of tempo codes is given in

&F1 nt	Amplitude decay on channel B.
&F2 nt	Amplitude decay on channel C.
&F4 nt	Frequency sweep on channel C.
&F6 nt	Noise-frequency sweep (flange).

The PSG has only a single auto-envelope, which can control the decay of any or all channels together (for a chord). For polyphonic (non-chordal) music the software must provide additional envelopes. This is done by decrementing the volume register after each minimum time interval ($\frac{1}{2}$ beat) for the duration t specified. Function nt takes any of the forms defined for codes &50-&7F.

&F5 Or This specifies a second register to be simultaneously decremented, allowing any two of the above functions together, such as a rising pitch of decaying amplitude. Cancel with &F5 80.

&F7 aa Next buffer-code to be interpreted is at address aa within the same page. A sort of 'jump' instruction. Stop — all buffers must end with this code if you value your batteries!

&FB 76 Optional 'jump'. If the option switch is open, this command is ignored; else behaves like 'jump' code &F7.

&FC aa Set tempo. See Timing section in main text. Caution: if deleting a tempo, ensure both codes are deleted — a tempo of zero will hang you up forever!

MULTI-BYTE CODES

&F3 aa bb	Define User Function (advanced users only).
&FD aa bb	'Recall'. Repeat the buffer-passage from address aa up to and including address bb within the same page. The passage recalled cannot itself contain a recall, or a 'jump'.

&FB 21 aa p 'Leap' — the next buffer code to be executed is at address aa within page p (&Opaa where $p = 1-7$).

Code &FB actually causes the CPU to quit the Operating System and to start executing Z80 code. Advanced users only! The stop command &FB 76 is in fact the Z80's halt instruction.

The monitor mode uses this technique to break out of the buffer and increment the 'number of callers' location in EEPROM.

Similarly, the tell-tale mode breaks out to check this location before deciding whether to sound a number of peeps or a raspberry!

Fig. 6, where 112 beats/minute is represented in 'normal tempo' as &FE 1C. If the music we were transcribing had an awful lot of 'tails' on the notes we could just as easily use double-tempo (&FE 38) and let code &67 represent one half-beat.

Triplet Timing

A triplet is a group of notes with the number '3' over them. They are to be played at the rate of three notes per two beats. Whereas other music programs give up on this problem, PBOS has three solutions.

1. Use the approximation for a tripleted beat (&66 in Fig. 5).
2. Use the normal codes for a beat or half-beat (&67, &63) to represent the tripleted notes. Use code &6B or &65 for their 'normal' versions (see 'Among Triplets' in Fig. 5).
3. Temporarily up-rate the tempo to one-and-a-half times (Fig. 6).

Method - Making Music

First catch your music!

Legally one should be careful of pinching copyright music, but since The Performing Right Society has, as yet, no special tariff for charging polyphonic programmable doorbells and is on the whole more concerned about rounding up Britain's coach companies and breweries, it is unlikely you'll get a licensing officer appearing on your doorstep!

So, pick your tune. It should ideally have no sharps or flats in the key signature. Else the scale will not sound right (one sharp is acceptable). The music chosen should not be chordal (clumps of notes), but one voice should move with another stationary. The relevance of this was discovered when the original

recipients could hardly tell that Polybel was polyphonic!

A dummy example is shown in Fig. 7. This will be allocated as Tune 5, Bank 2, so at start address &580. Divide the music up into horizontal events — bar-lines are irrelevant.

Event zero starts by setting-up control register 7. Your should always use the code as given, until you can learn *not* to output to the switches! Event zero continues with setting tempo, pitch, channel modes and so on until the first code that produces sound.

The tempo is given here, which we look-up in Fig. 6. If it is not given then you hum the tune whilst counting (in hex) the number of times you tap your foot in 15 seconds!

The 'rest' of event 2 implies sudden quiet, so we kill everything by allocating all channels a manual volume of zero for one beat.

Event 3 shows that we need separate envelopes, since the channels take-on different timings. Here we will arbitrarily allocate channel C to the automatic envelope of the PSG. We will 'assign' register 9 (channel B volume) as the second register for software decay and use the timing-codes that control decay of channel A (& F0 5x or F0 6x).

Event 4 shows a requirement for a note not shown in Fig. 3. This is 'between' codes &4D and &4E. Listing 1 (last month) shows the look-up at &0DD and &0DE to contain &50 and &48; we average these and inject the value directly into register 4 (frequency control for channel C).

At event 7, we end if the 'option' switch is set. Events 7, 8, 9 are the same as events 2, 3, 5 and so we use the 'recall' function before ending.

Best wishes as you encode into the wee hours ... send me your best masterpiece and I'll send you the current library!



Channel C: 40 41 42 43 44 45 46 47 48 49 4A 4B 4C 4D 4E 4F
 Channel B: 20 21 22 23 24 25 26 27 28 29 2A 2B 2C 2D 2E 2F
 Channel A: 01 02 03 04 05 06 07 08 09 0A 0B 0C 0D 0E 0F

Fig. 3 Treble pitch codes

Channel A: 10 11 12 13 14 15 16 17 18 19 1A 1B 1C 1D 1E 1F
 Channel B: 30 31 32 33 34 35 36 37 38 39 3A 3B 3C 3D 3E 3F

Fig. 4 Bass pitch codes

Auto Attack 61 63 67 6B 6F 65 61 62 60 69 66 (Note 1)
 AS Tremolo 51 57 5B 5F 55
 Among Triplets X2 X5 X8 (Note 2) (X = 5.6. or 7) X7 X3
 AS Rest/Delay 71 73 77 7B 7F

Note 1: approximate timing
 Note 2: use multiple codes

Fig. 5 Useful timing codes

Beats Per Minute = 88 92 96 100 104 108 112 116 120 124 128 132 134

↓ = 6F (Double Tempo) 2C 2F 30 32 34 36 38 3A 3C 3E 40 42 44
 ↓ = 67 (Tempo X 1.5) 21 24 27 2A 2D 30 33
 ↓ = 67 (Normal Tempo) 16 17 18 19 1A 1B 1C 1D 1E 1F 20 21 22
 ↓ = 63 (Half-Tempo) 0B 0C 0D 0E 0F 10 11

Fig. 6 Tempos


Event	Addr	Hex Code	Comment	
0	0580	B7 78	Configure ports. Noise off	
	0582	FE 1E	Tempo = 120	
	0584	FF FF	Spare for tempo change	
	0586	F8 F9 FA	All channels on Auto	
1	0589	CF E3	Medium decay. Filters on	
	058B	1E 28 4A	Notes A2,C4,E4	
	058E	67	One beat with attack	
	058F	80 90 A0	Silence	
2	0592	77 for one beat	
	0593	FA	Channel C on Auto again	
	0594	F5 09	Ch. B allocated so	
	0596	1A	Bass E2 for Channel A	
3	0597	2A 4F	E4, B4 for Channels B & C	
	0599	8F 9E	Volumes for Bass & Alto	
	059B	F0 65	Auto attack & Soft decays	
	059D	B4 4C	G-sharp in Channel C	
4	059F	F0 61	Re-start Auto envelope	
	05A1	B2 9A 9E	G3. New soft envelope	
	05A4	4A F0 63	E4. Restart Auto envelope	
	05A7	27 9E	B3. New soft envelope	
5	05A9	F0 73	All 3 decays continue	
	(11)	05AB	FC B2	Optional jump to Event 11
	7	05AD	17 8F	Else new B1 bass, otherwise
	(10)	05AF	FD 97 AA	Repeating 3-6 (\$597-\$5AA)
6	05B2	F8 F9	All Channels auto again.	
	05B4	76 28 4E	Final chord	
	05B7	6F FB 76	2 beats, then shut-down.	
	11	05B7	6F FB 76	

Fig. 7 A worked example of Tuneware

MIDI MAPPER

PROJECT

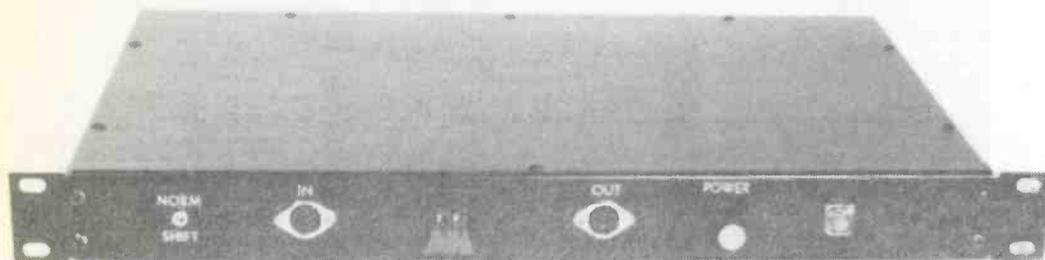Robert Penfold can change channels in mid data stream with his MIDI mapping rack unit



In an ideal MIDI world I suppose there would be no need for add-ons such as a MIDI mapper. In the real world there are plenty of MIDI instruments and other MIDI equipped equipment which have what is only a fairly basic MIDI specification. These days manufacturers of electronic music equipment give most of the current equipment a fairly comprehensive specification — mode 4 operation with multi-timbrality is now the order of the day even on budget synthesisers and samplers. There is usually a great deal of control over which voice of an instrument operates on which MIDI channel.

This contrasts with many instruments of the past, including some of the most popular ones. A common failing of these is the ability to transmit data only on MIDI channel 1, which can be a bit limiting especially if your setup contains more than one instrument of this type. A simple way around this problem is to feed the output of the instrument through a MIDI mapper such as the unit featured in this article. The basic action of this device is to pass most MIDI data unaltered. However, data received on a certain MIDI channel can be retransmitted on a different channel. Both the input and output channels are user selectable via a couple of switches. In our example of a synthesiser restricted to transmission on channel 1, by setting channel 1 on the input selector switch, the data would then be output on any desired channel, as set on the output selector switch.

There are other ways of using the unit, but a certain amount of care needs to be exercised as things might not always work out as you might expect.

The unit can be used in what is effectively the opposite way to the one described above, where it is added at the input of an instrument which can only operate on channel 1, so as to make it respond to data sent on a different channel. Bear in mind though, that this unit only provides channel switching, it does not give MIDI filtering (which is a rather more complex function than one might think). Although it will convert messages on channel to any other desired channel, messages received on channel 1 will be passed straight through to the output, still on channel 1. This might not matter, but it could prevent the desired action from being obtained. If, for instance, you have two mode 3 instruments which are restricted to operation on channel 1, adding this unit ahead of one of these instruments would not permit them to be sequenced separately. However, building a doubled-up version of the unit with two mappers would permit independent operation of the units on any desired channels, except channel 1 which would become a 'no-go area'.

The lack of filtering could be used to good effect with a little ingenuity. With two instruments on

channel 1, and the mapper being added ahead of one of them, both instruments would respond to messages on channel 1. If the mapper was set for channel 2 as the input channel, then messages sent on channel 2 would only be received by this instrument. This would permit solo operation using channel 2 or layering of the instruments by using channel 1. Not fully independent operation but a definite advance on having only layered operation of the instruments.

There are other possible ways of using the unit. As explained in the *How It Works* section, it can be set up to effectively filter out certain types of MIDI data. However, it would be naive to expect a simple device of this type to provide all the functions as a highly sophisticated micro-based design costing hundreds of pounds.

Construction

Refer to Fig. 5 for details of the printed circuit board. Apart from IC4, all the DIL integrated circuits are CMOS types and require the usual anti-static handling precautions. I would recommend the use of a socket for IC4 as well — it is not a static sensitive device but it is not particularly cheap either. 6-pin DIL holders can be a bit difficult to obtain but it is not too difficult to saw an 8-pin type down to size.

When fitting the integrated circuits, note that IC8 has the opposite orientation to the other DIL devices. FS1 is mounted on the board via a pair of fuse-clips. Use plenty of solder when fitting the clips into place so that they are given a very firm mounting. Note that FS1 should be an anti-surge type and not a quick-blow because of the initial surge current as C7 charges up at switch-on.

A number of link-wires are required and for most of these trimmings from resistor leadouts are perfectly adequate. Some 22 swg tinned copper wire will be needed for the longer wires though. The wire must be quite taut on these longer links, or else insulated with PVC sleeving so that there is no risk of them short circuiting together. Crystal XTAL1 must be a miniature wire-ended type (such as an HC-49/U cased crystal) if it is to fit into the layout easily. Printed circuit pins are fitted to the board at the points where connections to off-board components will be made later, so that these connections can easily be made once the board has been installed in the case.

I used an inexpensive 19-inch (one unit high) rackmount case. This is actually somewhat larger than is really necessary and it could easily accommodate two or three boards if necessary. Even if a single board is used, a 19 inch rackmount case is still a good choice as this should make it easy to fit the unit into an existing MIDI system with the minimum of fuss. A light-duty type is perfectly adequate for this application (heavy-duty types can be extremely expensive).

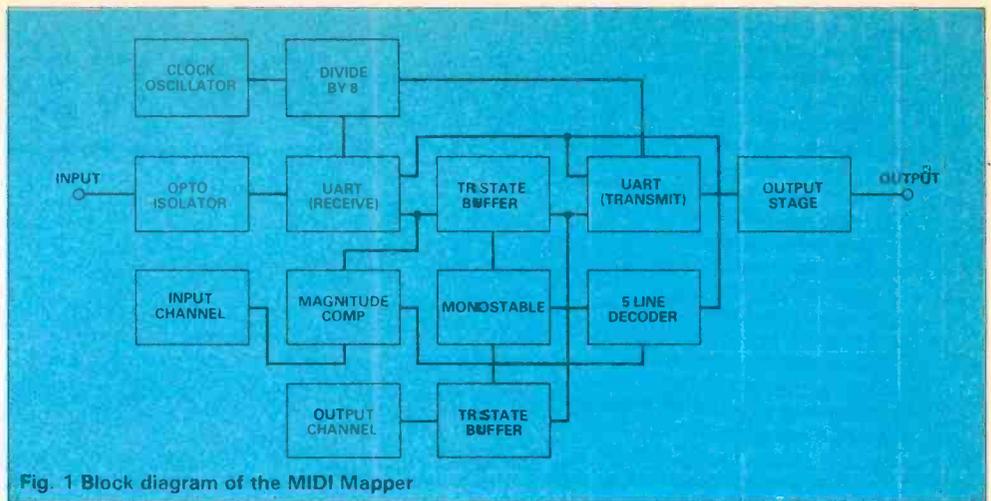


Fig. 1 Block diagram of the MIDI Mapper

HOW IT WORKS

The block diagram of Fig. 1 helps to explain the way in which the unit functions. It is based on a UART (Universal Asynchronous Receiver/Transmitter) which converts the incoming serial MIDI signal into parallel form and then retransmits it in serial form again. However, on appropriate bytes the signal is retransmitted in slightly altered form.

The MIDI standard calls for opto-isolators at all inputs. This is necessary in order to eliminate any problems with high voltages causing damage to equipment, to reduce the risk of hum loops and to prevent digital noise from being coupled into the audio stages of instruments. MIDI outputs are a form of current loop stage and must provide a nominal output current of 5mA.

The MIDI baud rate is 31250, set using a 4MHz crystal oscillator and a divide-by-eight circuit. This gives a clock signal at sixteen times the required baud rate which is what the UART requires. Only one word format is used for MIDI systems — one start bit, eight data bits, one stop bit and no parity. This word format is programmed into the UART by connecting certain of its inputs to the appropriate logic levels. Unlike many serial interface chips, UARTs are perfectly suitable for simple stand alone units and do not have to be programmed via the data bus and suitable software.

In order to understand how the unit provides channel switching you need to understand a few basics about the nature of MIDI signals. Each MIDI message consists of a header byte which contains the code for the type of message concerned (most significant nibble) and the channel number (least significant nibble). These channels messages include such things as note on/off instructions, pitch bend information, and so on. There is another form of MIDI instruction in the form of system messages. With these the most significant nibble has the system message code (1111 in binary) and the least significant nibble contains the code for the particular type of message involved (clock signals, system exclusive, and so on). Many of the header bytes are followed by one or more data bytes.

The unit only needs to process header bytes for channel messages that are on the appropriate channel. System messages must not be altered. Similarly, data bytes for channel messages must not be changed — their channel number is that of the header byte that precedes them and they do not carry any channel information themselves. As the channel number is contained in the least significant nibble, only this nibble is ever processed. The most significant nibble is always passed straight through to the transmitter section of the UART without undergoing any changes.

The least significant nibble is checked for the right channel number using a magnitude comparator which compares the received nibbles with the binary code set using the input channel selector switch. If a match is detected, the comparator sends the appropriate logic level to one input of a 5-line decoder. The other four lines of this circuit are fed with the most significant nibbles. The decoder only provides an output pulse if it detects that the correct logic level is being provided by the magnitude comparator and that the most significant bit is set to 1 (which means that the received byte is a header type and not a data byte) (it will not provide an output pulse if all four bits of the most significant nibble are set to 1, a system message header type).

If a channel message header byte is detected, the decoder

produces an output pulse that triggers a monostable. This controls two tristate buffers, one from its Q output and one from its \bar{Q} output. Normally the upper tristate buffer of Fig. 1 is active and the signal passed through to the output unprocessed. When the monostable is triggered, its outputs momentarily swap states and the other tristate buffer is activated. It then couples through to the transmitter UART the binary code set using the output channel selector switch. This code replaces the channel nibble of the received byte on the transmitted signal.

Figure 2 shows the main circuit diagram for the mapper the comparator, decoder, and monostable circuits are shown separately in Fig. 3 and the mains power supply circuit appears in Fig. 4. Transistor Q2 generates the clock signal to be divided by eight in IC1 (where only three of its seven binary counters are used). Q1 is the output stage.

IC4 and Q3 provide a high speed opto-isolated input. The TL111 specified for IC4 is not a particularly fast device but by using its output transistor in the emitter follower mode together with an external amplifier (Q3) it can handle the relatively high frequencies involved in a MIDI application. Q4 is used to reset the data received flag of UART IC2, and it also produces a pulse to initiate transmission of received bytes.

IC3 and IC5 are the two tristate buffers. These are 8-bit types but in this circuit only four buffers of each one are used. SW1-4 plus R12 to R15 form the output channel selector circuit.

IC6 is the magnitude comparator, a 74HC85 four bit type. SW5-8 plus R16 to R19 are the input channel selector circuit. IC8 is the 5-line decoder, actually a 74HC138 3-line type. The extra two input lines are provided by the positive enable terminal and one of the negative enable inputs. The latter is driven from IC6 via an inverter formed by one gate of IC7.

The positive enable input of IC8 is fed from the most significant data bit. The other three most significant bits of data drive the normal inputs of IC8. Seven of its outputs are ANDed by a simple diode gate circuit and any one of these (active low) outputs going low will trigger the monostable. The latter is based on IC9 which is a 4047BE astable/monostable connected in the negative edge triggered monostable mode. SW9 can be used to disconnect the gate circuit from the monostable so that the channel shifting is disabled.

Output 7 of IC8 is not connected. This is activated when a system message header byte is received. (these must not be altered). A form of MIDI filtering can be obtained by removing some of the diodes in the gate. Some classes of message would then be passed through unaltered while others would be shifted to an unused channel and effectively filtered out. Each output of IC8 represents a different class of message. For example, output 5 (pin 10) is the channel pressure output. By including a diode on this output but not the others, channel pressure messages could effectively be filtered out.

The power supply circuit is unremarkable, just a standard regulated 5V supply using push-pull rectification. As the current consumption of the circuit is only a few milliamps it is quite in order to use battery power if preferred. Omit T1, D8, D9, FS1 and C7, then connect the battery across C8, fitting one pole of the on/off switch in the positive battery lead.

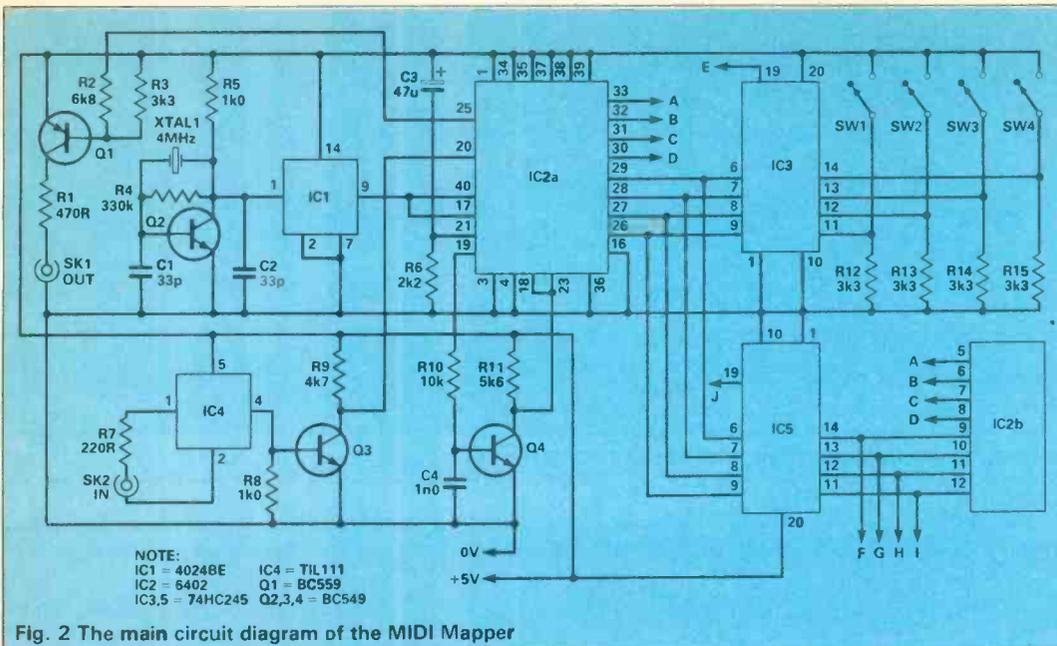


Fig. 2 The main circuit diagram of the MIDI Mapper

The general layout of the unit is not critical but position everything sensibly so that there are a minimum of crossed wires. SK1 and SK2 should be 5-way 180° DIN sockets, the standard type for MIDI equipment. Switches SW1-8 could be two sets of four miniature toggle or slider switches but you would then need to set up the right binary patterns in order to select the desired input and output channels. The extra expense of hexadecimal switches is probably worthwhile, and it is switches of this type that I used on the prototype. A lot of hex switches are printed circuit types which are only intended for preset use. Switches of this type can be wired in if the unit will always be used with the same input and output channels. A few wire links are much easier and cheaper if preset operation is all that

is required.

If selection of the input and output channels via the front panel is required, thumb-wheel style hex switches are probably the best option. I used the miniature RS type. These require one pair of end cheeks if the two switches are to be clipped together to form a single unit, or two pairs of end cheeks if they are to be mounted separately.

The panel cutout can be made using a fretsaw or similar implement. A good way of getting it really accurate is to cut just inside the line marking the boundary of the cutout, and to then carefully file out the hole to precisely the required size. The correct size for the cutout is 31mm x 17mm for a single switch, or 31mm x 24.5mm for a twin switch assembly.

PARTS LIST

RESISTORS (all ½W 5%)

R1	470R
R2	6k8
R3,R12-19	3k3
R4	330k
R5,8	1k0
R6,20	2k2
R7	220R
R9	4k7
R10,21	10k
R11	5k6

CAPACITORS

C1,2	33p ceramic plate
C3	47µ 16V radial elect
C4	1n0 polyester
C5	4n7 polyester
C6	100µ 10V radial elect
C7	1000µ 16V radial elect
C8,9	100n ceramic

SEMICONDUCTORS

IC1	4024BE
IC2	6402
IC3,5	74HC245
IC4	TIL111 opto-isolator
IC6	74HC85
IC7	4001BE
IC8	74HC138
IC9	4047BE
IC10	µA78L05 (+5V 100mA reg.)
D1-7	1N4148

D8,9	1N4002
Q1	BC559
Q2-4	BC549




MISCELLANEOUS

FS1	20mm 100mA anti-surge fuse
NEON1	Mains panel neon
SK1,2	5-way 180° DIN chassis socket
SW18	Hex thumbwheel switch
SW9	SPST miniature toggle
SW10	rotary mains
T1	Mains primary, 9-0-9V 100mA secondary
XTAL1	4MHz (HC-49/U or similar case)
PCB, Case, Knob, IC sockets,	
16 pin DIL holder (2 off)	
20 pin DIL holder (2 off)	
40 pin DIL holder	
Pair of 20mm fuse-clips	
Stand-offs, mains lead and plug, wire, solder, etc.	

BUYLINES

The hex switches used on the prototype are RS components (available from Electromail tel (0536) 204555). The order code for the switches and end cheeks are 337-093 and 338-406 respectively.

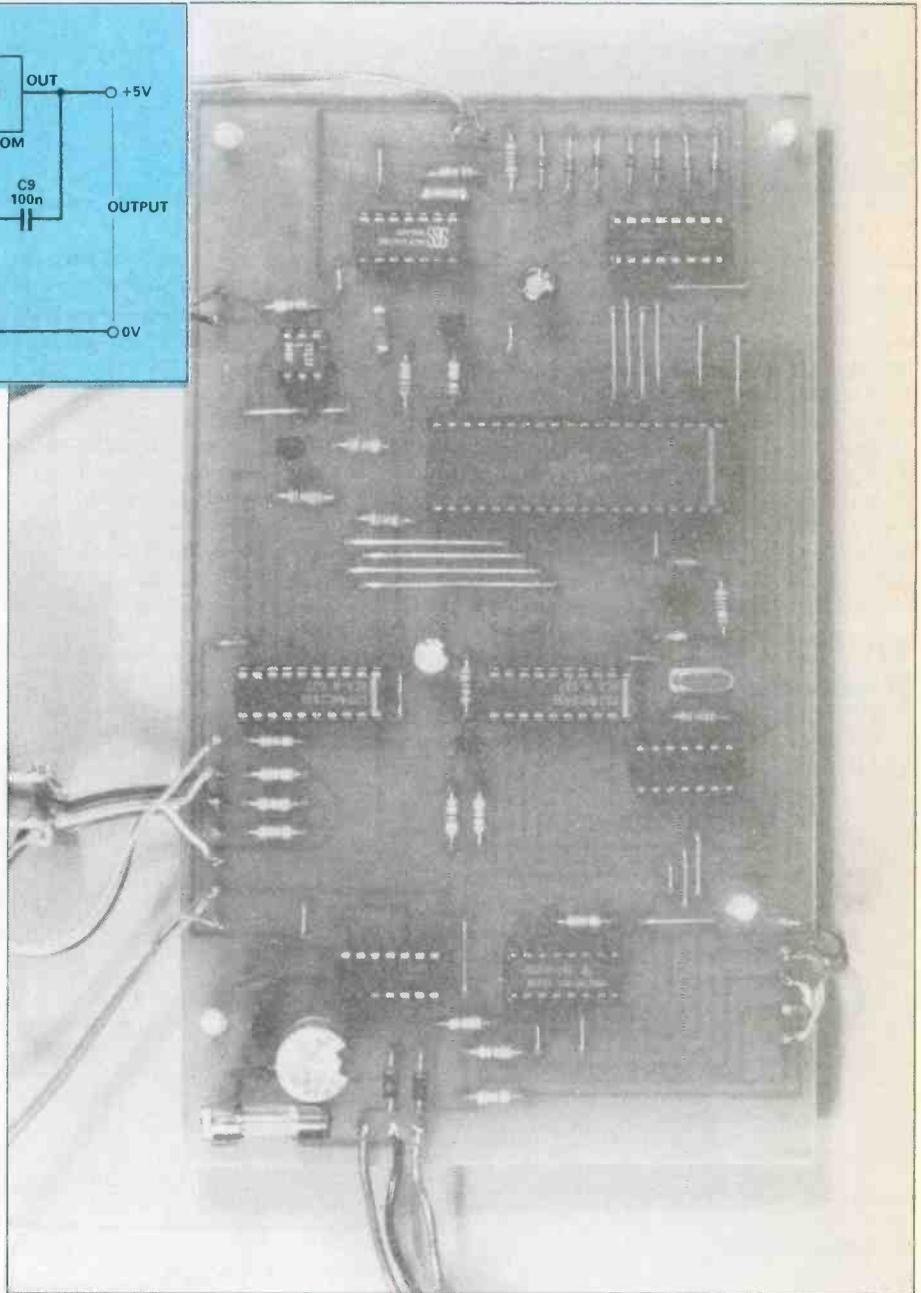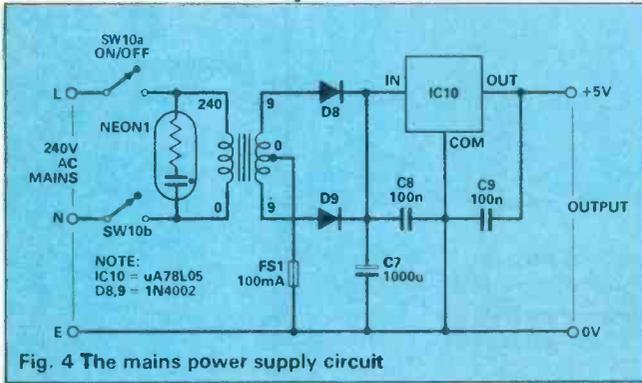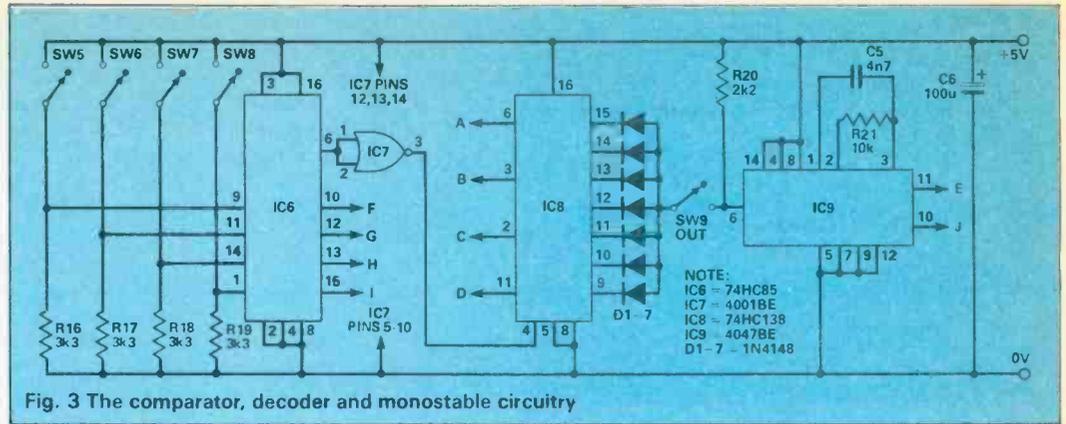The 19-inch rack mount case is a Rackz Products (tel (0275) 823983) type U1, which is an inexpensive light-duty type which is perfectly adequate for this project. Any other one unit high rack-mount case should be suitable but many of the alternatives are prohibitively expensive.



PROJECT

Mount the PCB on the base panel of the case using stand-offs or use long spacers over 6BA mounting bolts. Most of the hard-wiring is straightforward but the wiring to the thumbwheel switches and IN/OUT sockets needs to be completed with care if everything is to work first time. 'Rainbow' ribbon cable is probably the best type to use for the point-to-point wiring.

Note that there is a link wire from pin 2 of SK1 to the chassis tag of this socket but this link must be omitted from SK2 (otherwise the opto-isolator at the input of the unit will be effectively bypassed). Take due care with the mains wiring. The case must be earthed to the mains earth lead and a soldering fitted on one of T1's mounting bolts is an easy way of providing a suitable connection point.

In Use

Assuming you use the specified type of socket connected in the manner shown in Fig. 5, standard MIDI leads can be used to connect the unit to the other items of equipment.

The main point to bear in mind when fitting the unit into a system is that it must not be connected ahead of any item of equipment which must receive the undoctored MIDI signal. For example, if you are using the MIDI THRU method of connection and only one piece of equipment must be fed with the doctored signal, then the processor should be the penultimate unit in the chain of connection, and the equipment to receive the doctored signal connected as the final unit. If the unit is used with a synthesiser that will only

transmit on MIDI channel 1, simply connect the OUT socket of the synthesiser to the IN socket of the mapper. The OUT socket of the mapper is then used to drive the other items of equipment in the system, and the output channel selector of the mapper is used to effectively select the output channel of the synthesiser.

Unfortunately the hex switches are calibrated from 0 to F, whereas MIDI channels are conventionally numbered from 1 to 16. Obviously a little mental arithmetic is all that is needed in order to convert switch settings to their corresponding MIDI channels. SW9 can be used to switch out the channel shifting if desired, (setting the same input and output channel provides the same effect). In either case the unit will only pass the MIDI signal if it is switched on.

PROJECT


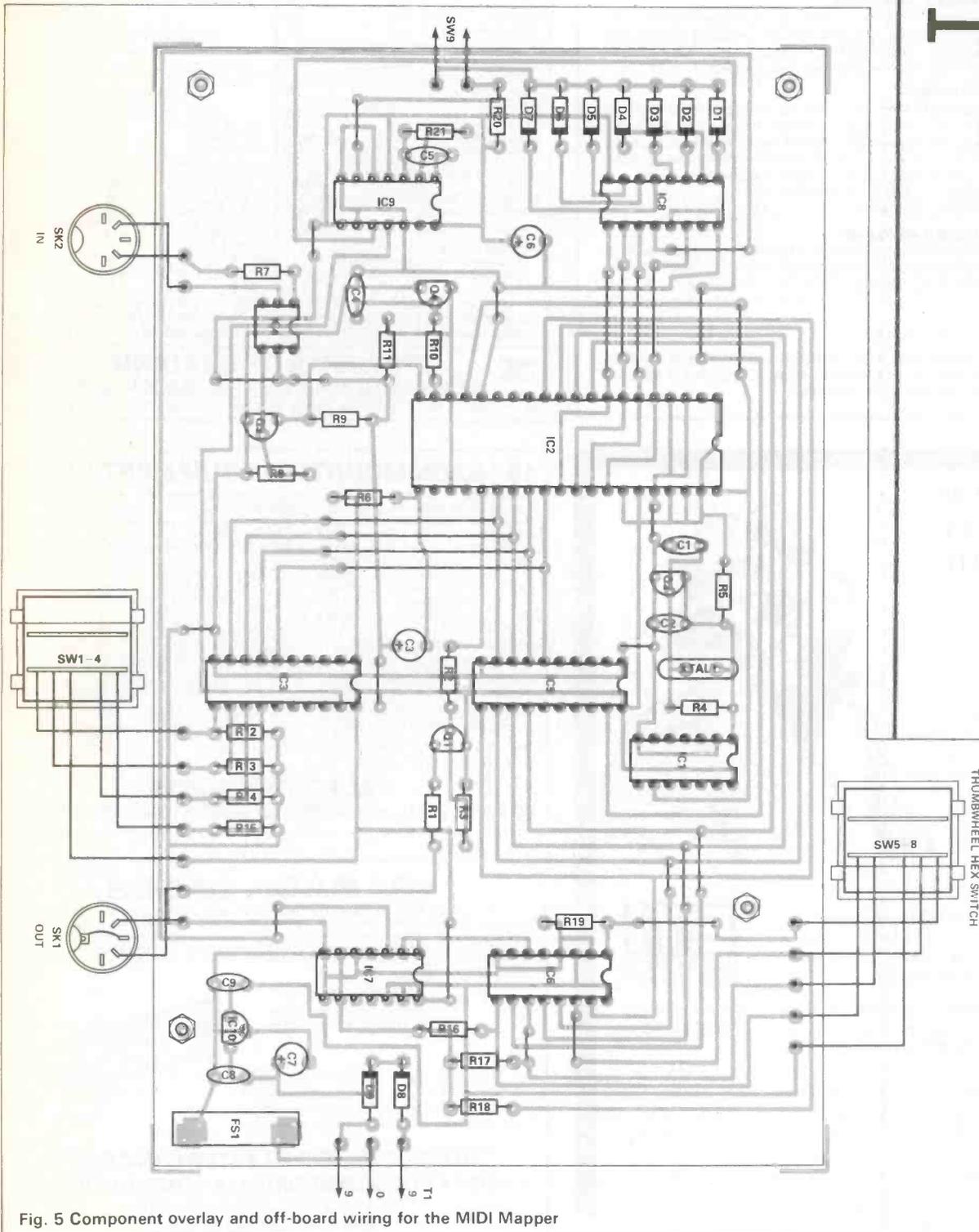


Fig. 5 Component overlay and off-board wiring for the MIDI Mapper

AUDIOKITS Precision Components

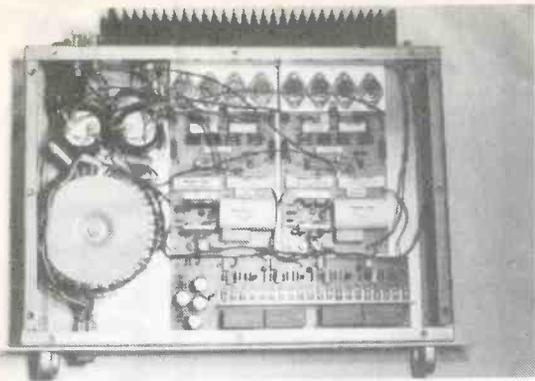

THE VIRTUOSO POWER AMPLIFIER

AUDIOKITS top of the range power amplifier kit and still the number one power amplifier in terms of sound quality and ease of construction and testing. At £325 complete, the standard 100W/Channel version is excellent value for money whilst the 3U upgraded version at £840 offers the kind of sonic performance expected of the world's best power amplifiers.

THE VIRTUOSO PRE-AMP

The ideal constructors preamp. Excellent sonic performance and simple but effective circuitry make it one of the most popular preamp designs published. And its modular construction, including separate power supply regulator board makes it ideal for anyone requiring an MC Stage, Disc Amplifier, Tone Control or Basic Low Level Amplifier on its own. Now even further sonic improvement are possible through better components. For details send now for:

ACN19 VIRTUOSO PREAMP — THE SECOND UPGRADE £5.00
ACN20 REMOTE PREAMP POWER SUPPLY £1.50

AUDIO DESIGN POWER AMPLIFIER


Many ETI readers have substantially improved the sound quality of the original audio design power amplifier by fitting higher grade recommended and supplied by AUDIOKITS. Whether you are building the latest version as published or making your own version in your own case, AUDIOKITS component note and price list offers many useful ideas on improving sound quality at low cost. Send now for:

ACN 22 AUDIO DESIGN POWER AMPLIFIER £2.00

For further details of Audiokits, Audio Amplifier Kits, Electronic Components and Cables, send 9"x4" SAE (overseas 3 IRCs) to Audiokits Precision Components, 6 Mill Close, Borrowash, Derby, DE7 3GU, England. Tel: 0332 674929.

PUT YOUR AGENT ON THE TRAIL

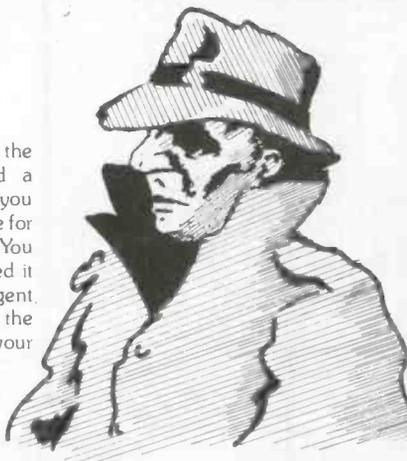You need the facts. just the facts man. You need a steady source to feed you information. Don't settle for a second-rate squealer. You need ETI and you need it good. Put your newsagent on the trail — clip the coupon and hand it to your neighbourhood shop.



Dear Mr Newsagent
Please order me a copy of ETI
and reserve deliver me a copy
every month.



Note this magazine is available to your wholesaler through:
SM Distribution, 6 Leigham Court Road, Sreatham, London
SW16 2PG. Tel: 01-677 8111.

Name _____

Address _____

Oscilloscopes

TEKTRONIX 2213 Dual Trace 60MHz Delay Sweep Dual TB	£400
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£500
TEKTRONIX 454 Dual Trace 150MHz Delay Sweep	£400
GOULD ADVANCE OS3000A Dual Trace 40MHz Delay Sweep	£300
TRIO CS1566A Dual Trace 20MHz Delay Sweep	£250
PHILIPS PM3233 Dual Trace 10MHz	£200
TELEQUIPMENT D75 Dual Trace 50MHz Delay Sweep	£275
KIKUSUI 5530A Dual Trace 35MHz	£250
HP 1220A Dual Trace 15MHz	£200
GOULD ADVANCE OS1100 Dual Trace 30MHz	£210
GOULD ADVANCE OS255 Dual Trace 15MHz	£210
COSSOR CDU150 Dual Trace 35MHz Delay Sweep Solid State	£180
Portable 8x10cm Display	£10
Optional front cover containing 2 probes etc	£10
SE LABS SW111 Dual Trace 18MHz Solid State Portable AC or external DC operation 8x10cm Display	£150
SCOPEX 4010B Dual Trace 10MHz	£150

MARCONI TF2015 AM FM 10-520MHz Sig Gen with Synchroniser TF2171	£550
MARCONI TF2015 without Synchroniser	£425
MARCONI TF2016 AM FM 10MHz-120MHz with Synchroniser TF2173	£400
MARCONI TF2016 without Synchroniser	£300
MARCONI SANDERS SIG SOURCE 6055B 850-2150MHz	£500
DYMAR 1525 AM FM 0.1-18MHz Sig Gen	£200
H P 964 SWEEP OSCILLATOR 712 4GHz	£500
H P 620 Signal Generator 7110Hz	£400
H P 614A Signal Generator 800-2100MHz	£275
FERRISGRAM RT52 Recorder Test Set	£150
WOLKE Wlow & Fluter Meter ME108	£100
LEADER LMV 186A Two channel Millivoltmeter 5Hz-50kHz 100V-300V	£100
LEVELL TG20DM 1Hz-1MHz Sine/Square	£125
MARCONI Automatic Distortion Meter TF2337A 400Hz or 1kHz Measures down to 0.01%	£150
MARCONI TF2700 UNIVERSAL LCR Bridge Battery Operated	From £150
PHILIPS PM6456 FM Stereo Generator	£95
ADVANCE SG62B AM 150kHz-220MHz	£45 (P&P £7)
TEKTRONIX CURVER TRACER type CT71	£325
TRIO SG402 AM Sig Gen 100kHz-30MHz Unused	£75
MARCONI ATTENUATOR TF2162 DC-1MHz 600 Ohm 0-11dB in 0.1dB Steps	£35 (P&P £7)
MARCONI RF POWER METER TF1152A/1 DC-500MHz 0.5-25W 500Ohm with manual	ONLY £45 (P&P £7)

TELEPHONES — YES! REAL DIAL TYPE TELEPHONES — that don't sit around the desk. Type No. 746 supplies with standard BT plug (used). Only £5 each (P&P £3). Quantity discount

Used equipment — with 30 days guarantee. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage



STEWARTS OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Tel: 0734 68041. Fax: 0734 351696. Callers welcome 9am-5.30pm Mon-Fr. (until 8pm Thurs)

SPECIAL OFFER HEWLETT PACKARD OSCILLOSCOPE TYPE 1740A

Dual Trace 100MHz Delay Sweep Trigger View £575

HAMEG MODULAR SYSTEM

HM8001 Main Frame with HM8032 Sine Wave Generator
20Hz-20MHz HM8030 2 Function Generator 0.1-1MHz Sine/Square Triangle and HM8011 2 Digital Multimeter 4 Digit

ONLY £400

RACAL-NORSK Keyboard CASED ASCII Coded + Function keys Unused. Some info £5 each (P&P £3)
FARNELL SWITCHED MODE PSU 5V 40A & +/- 12V 5A £30 each (P&P £4)
OTHER SWITCHED MODE PSUs available. Please enquire
DISK DRIVES 5 1/2 DS/DD 80 track from £50

MULTIMETERS (P&P All AVOs £10)

AVO 8 Complete with Batteries & Leads from £50
AVO 8 MkV Complete with Batteries & Leads £90
AVO TEST SET No 1 (Military version of AVO 8) Complete with Batteries & Leads £65
TEST LEADS suitable for AVOMETERS Red & Black with 2 Croc-Clips & 2 Prods £5 (P&P £3)
Black 'Ever Ready' case for AVOs Unused £15 (P&P £4)

BATTERIES 15 volt £3 each. 10 off £25 (P&P extra)

AVO TRANSISTOR ANALYSIS Mk2 CT446 Suitcase style, complete with batteries and operating instructions (P&P £7) ONLY £25 each

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 604 Dual Trace 60MHz Delay Sweep Component Tester + 2 Probes £575
HAMEG OSCILLOSCOPE 2036 Dual Trace 20MHz Component Tester & 2 Probes £314

All Other Models Available

BLACK STAR FREQUENCY COUNTERS P&P £4
Meter 100-100MHz £99
Meter 500-600MHz £129
Meter 1000-1GHz £178

BLACK STAR JUPITOR 500 FUNCTION GENERATOR
Sine/Square/Triangle 0.1kHz P&P £4 £110
BLACK STAR ORION PALTV/VIDEO COLOUR PATTERN GENERATOR £209

HUNG CHANG DMM 7030 3 1/2 digit Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with batteries & leads P&P £4 £39.50
As above DMM 6010 0.25% £33.50
Carrying Case for above £3

OSCILLOSCOPES PROBES Switched x1 x10 £11 each

19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack equipment cases have been designed with economy and versatility as their objective. These cases are supplied as a flat pack kit with assembly instructions. The ★ NEW IMPROVED DESIGN ★ now features a black powder coat 16SWG (1.5mm) steel front panel with the rear box constructed from 9mm PVC coated steel.

All units are 10" (254mm) deep and are available in the following popular sizes:

TYPE	HEIGHT	PRICE
U1	1" (44mm)	19.55*
U2	3" (88mm)	23.00
U3	5" (133mm)	21.85*
U4	7" (178mm)	24.50*

* Special Offer Price

DELIVERY INCLUDED (UK ONLY)

All prices INCLUDE VAT

Blanking Panels, Racking Consoles and Rack Cabinets are also available.


Please send S.A.E. for details.

★ TRADE ENQUIRIES WELCOME ★

TEL: 0275 823983 FOR ACCESS/VISA SALES
OR CHEQUE WITH ORDER TO:

RACKZ PRODUCTS

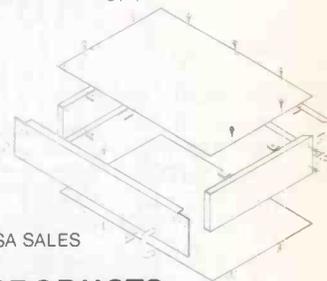PO BOX NO. 1402, MANGOTSFIELD, BRISTOL, ENGLAND BS17 3RY



19" RACK CASES

★ Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish ★ New improved construction and finish ★ Black anodised aluminium front panels ★ Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure ★ Heavy gauge front panel (50) brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet ★ Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package.

Order Code	Panel Size W H (inch)	Rear Box W H D	Weight	Price
U101	19 x 1.75	17 x 1.5 x 10	2.4kg	26.95
U103	19 x 5.25	17 x 5.0 x 10	3.5kg	29.95

U212	19 x 3.5	17 x 3.0 x 12	3.3kg	£29.75
U312	19 x 5.25	17 x 5.0 x 12	4.0kg	£31.95
U412	19 x 7.0	17 x 6.5 x 12	4.6kg	£34.95

Please add £3.00 P&P for the first item and £1.50 for each additional item.
Please add VAT to above prices. Overseas orders welcome.



CRICKLEWOOD ELECTRONICS LTD


40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET

Tel: 01-452 0161 Fax: 01-208 1441

SOLE UK DISTRIBUTORS

THE MULTIMETER

PROJECT

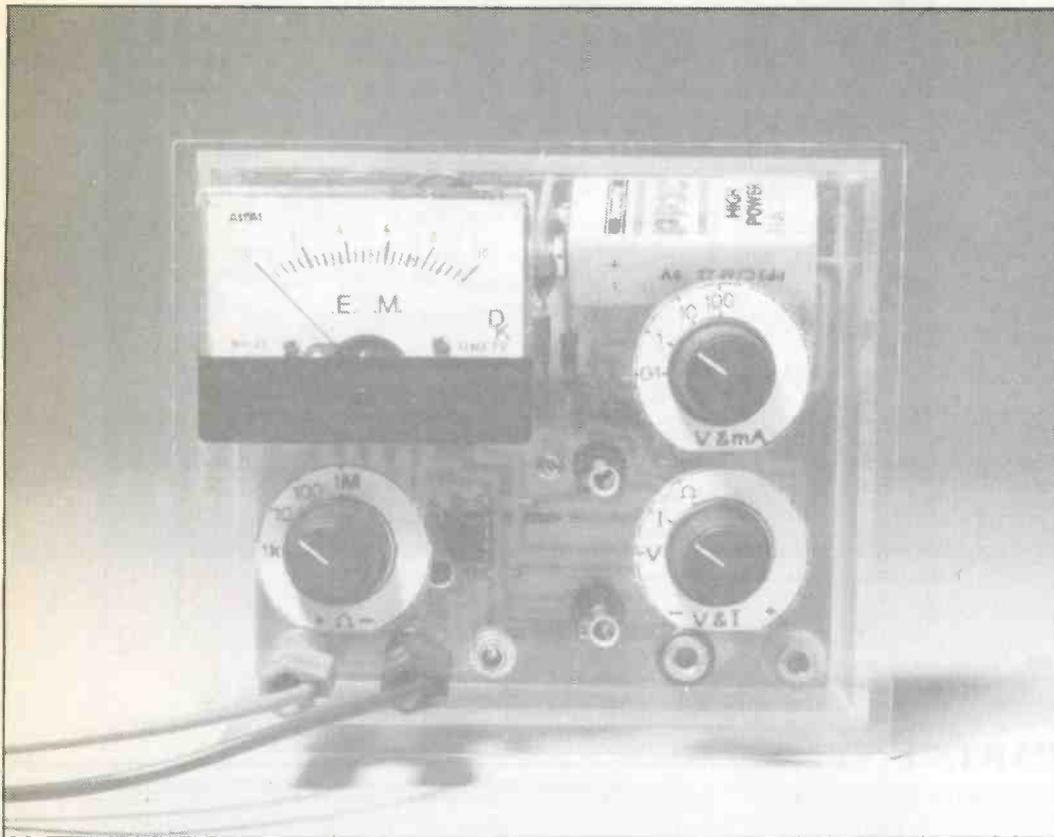

The humble multimeter is the fundamental piece of test gear in every workshop. Without it, most people would not dream of setting out to mend anything, let alone build something. This does present a problem when presenting a project to build such a meter. Dare one build the project without a multimeter to test it? And if you have one, why build one?

You can sort out such arguments for yourself. This simplest answer is to borrow a meter for the weekend. Happily this project is reasonably simple and there isn't too much to go wrong.

It was originally designed as an Industrial Skills class project for BTEC/C&G students. The design criteria were that it should measure a limited range of DC volts, current and resistance with a reasonable degree of accuracy, that it should use low-cost and readily available components. Plus it should be easily put together with a minimum of tools and equipment.

There are four DC voltage ranges with full-scale deflections of 100mV, 1V, 10V and 100V. Four DC current ranges have FSDs of 100mA, 1mA, 10mA and 100mA. There are also four resistance ranges with ranges up to 1k Ω , 10k Ω , 100k Ω and 1M Ω .

Multimeters manufactured with only passive components usually have a non-linear resistance scale. However, this project includes an active device. The friendly LM358 dual op-amp provides the measurement of voltage, current and resistance using a linear scale (ETI March and April 1986 contain more information on the LM358).

The multimeter with its high impedance input has negligible loading effect on the circuit being measured — this is essential when, for example, measuring transistor base voltages.

Zero resistance on most analogue multimeters is on the right-hand side of the meter scale. With this multimeter, voltage, current and resistance have their zero positions on the left-hand side of meter scale.

The multimeter should zero automatically on all ranges once adjusted and calibrated.

The accuracy of the multimeter relies on the close tolerance of resistor values.

Off the shelf 5% tolerance (gold band) are listed, these will give surprisingly good results. However 1% tolerance (brown band) resistors are easily obtainable, except perhaps the 10M value.

Construction

If you are using the PCB from the ETI PCB Service (see centre pages) then construction is very straightforward. Those wishing to etch their own board can find the foil pattern at the back of the magazine.

The component overlay is shown in Fig. 1. Integrated circuits are notoriously fickle things when it comes to soldering and you may prefer to solder in an 8-pin IC socket to take the LM358 rather than fixing it directly to the board.

Solder in the resistors and diodes first. Remember the diodes need to be orientated correctly. Leave enough distance between the red LED and the board so that you can mount it through the case later. The prototype made use of a transparent case made out of something similar to Perspex so that it didn't really matter if the LED protruded from the case or not!

To mount the preset resistors RV1,2 you may need to enlarge the PCB holes slightly — the legs are a bit thicker than those on resistors.

The meter and rotary switches are mounted directly on to the PCB. This improves mechanical and electrical terminal connection. You'll need to cut the eyes from the rotary switch tabs unless you want to make huge holes in your PCB.

The on/off switch and the sockets do not go direct onto the board. They are connected with lengths of 1mm tinned copper wire, although you may

Douglas Kennedy presents some wide-ranging ideas with this simple budget piece of test gear

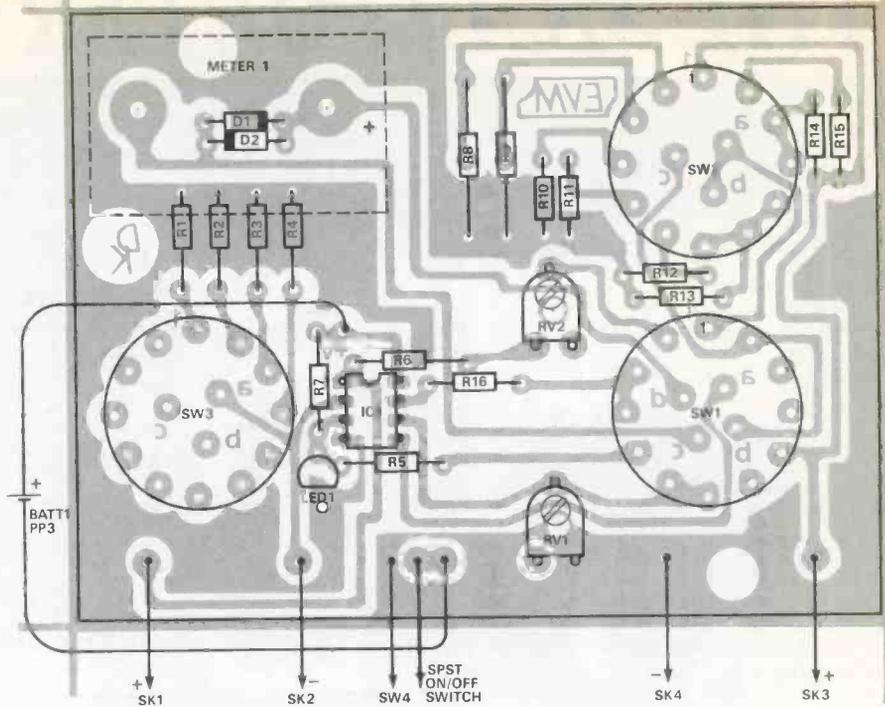


Fig. 1 The component overlay for the multimeter

PARTS LIST

RESISTORS (all 1/4W 5% unless stated)

R1	1M0
R2,13	100k
R3,12	10k
R4-7,11	1k0
R8	1R0 1/2W
R9	10R 1/2W
R10	100R
R14	10M
R15	910k
R16	2k2
RV1	pre-set 10k
RV2	pre-set 220k

SEMICONDUCTORS

IC1	LM358
D1,2	1N4148
LED1	0.2in red LED

MISCELLANEOUS

BATT1	9V PP3 battery
METER1	100µA meter
SK1-4	4mm sockets: 2 red, 2 black
SW1	4-pole 3-way rotary switch
SW2,3	3-pole 4-way rotary switch
SW4	single pole single throw switch
PCB	Knobs (3), IC socket, Battery clip, Case, Test leads.

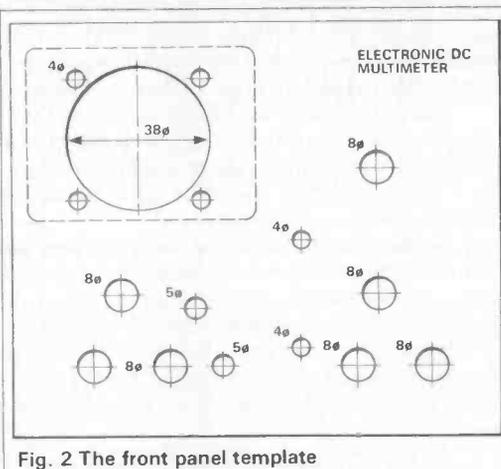


Fig. 2 The front panel template

prefer to wait until you've prepared the front panel and fixed the components on that before you connect them in. It will depend on the case you use and how conveniently things will fit together.

The Front Panel

So that you can get a neatly arranged front panel with the holes and switches in the right place for the PCB,

there is a template for drilling shown in Fig. 2. Place this over your case firmly and scribe the hole positions with a knife or bodger. Then drill all the holes with a 2mm bit and enlarge them to the sizes shown on the template.

The hole for the meter is pretty big and the ideal tool for the job is a 38mm hole-saw. However, panic not if you haven't got one, you can make several small holes around the circumference and then blast your way through with a sharp knife (shortly to become a not so sharp knife). Happily the meter itself covers the edges of the hole so a disastrous botch job will be quite sufficient!

With everything wired in you can finally put the case together. Poke the stems of the switches through the holes you've made and trim them for the knobs. Mark up some dials on the case with the ranges shown in the photograph. Now connect up the PP3 battery (with the on/off switch off), fit that somewhere in the case with tape if necessary, and close the box. Now you're ready to test the meter.

Setting Up And Calibration

Calibrate the voltage and current ranges first. Switch on the multimeter and set the VmA switch (SW2) fully anticlockwise to the 0.1V position. Get a small

HOW IT WORKS

The complete circuit diagram is shown in Fig. 3. Depending on the function selected by the 4-pole selector SW1, the circuit operates as follows.

Voltage Measurement

Figure 4 shows the arrangement for voltage readings. The meter display is proportional to the input voltage which is sampled at the junction of the switched potential divider network and the non-inverting input terminal (pin 5) of IC1a. The op-amp is connected as a unity gain DC amplifier.

Current Measurement

Figure 5 shows the arrangement for current readings. Again IC1a is used in non-inverting mode. The input current is sampled through either R8,9,10 or 11.

Resistance Measurement

A potential difference of 1V6 is produced across the LED which performs a similar function to a zener diode. This reference is used to generate a stable voltage at the non-inverting input of IC1b.

The op-amp gain is set by resistor R1, 2, 3 or 4 switched into the circuit plus the resistor on test, connected to the output terminal and the inverting input terminal of the op-amp.

Therefore a full-scale meter reading on each switch position should equal the value of resistor switched in by SW3.

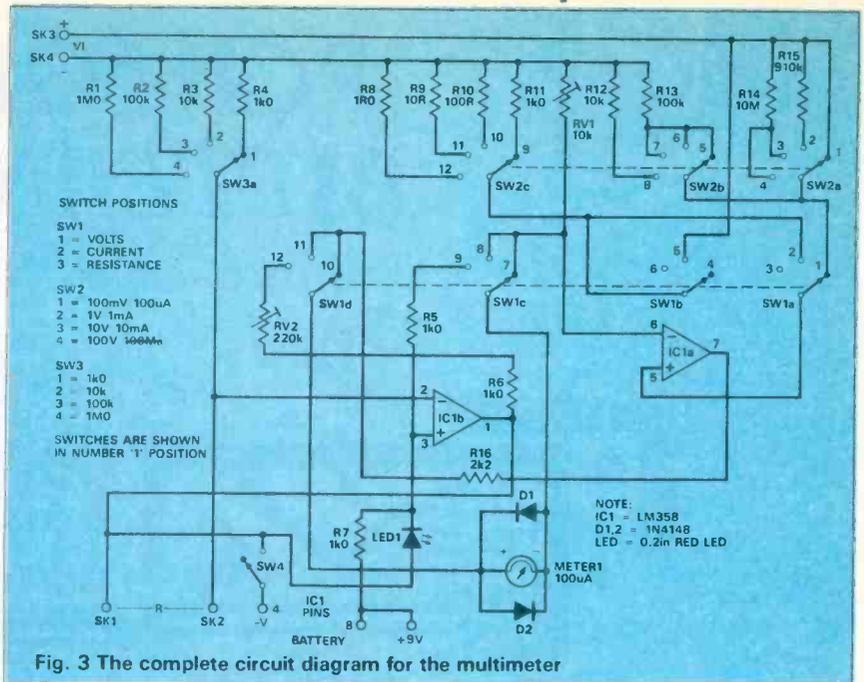


Fig. 3 The complete circuit diagram for the multimeter

screwdriver and tweak the slot adjustment on the meter until it reads exactly zero. Then click SW2 over to the 10V position. Connect a 10V DC supply across the voltage and current input sockets 3 and 4. Adjust RV1 to give a reading of exactly 10V FSD on the meter. And that's it. The multimeter should now give accurate measurements of up to 100V or 100mA in a linear manner.

Resistance Ranges

To calibrate for resistances, set the V&I switch SW1 over to the 'ohms' position. The meter needle should shoot off the scale as you are presenting it with an open circuit — more or less infinite resistance.

Set SW3 to the 10k position and get the closest tolerance 10k resistor you can find and connect across the resistance input sockets SK1,2. Adjust RV2 to give you the full 10k deflection.

No further adjustment should be necessary. Of course calibrating like this does depend on the quality of the supply or components you are using. If you don't have a DC supply (and there's little excuse since ETI published one not so long ago), you could check on the exact voltage of a spare PP3 at a friend's house or at work/school, then rush home and calibrate with that (making sure not to heat it, freeze it or use it in your stereo on the way!). Similarly it might be wise to get a second opinion on the 10k resistor you use to calibrate with, it would be a terrible shame to calibrate with a dud.

Other Things

The multimeter is also useful for basic testing of components. To test a silicon diode simply insert the test leads into the resistance test sockets and put the range on 1k. Connect the positive lead to the anode (no band) and the negative to the cathode (banded). If you get low resistance you're OK, if you get high resistance then the diode is open circuit (which it shouldn't be). Swap the leads over. You should now get a high resistance. If you get a low resistance then your diode is short circuit. Note that germanium diodes normally indicate a small resistance when reversed biased.

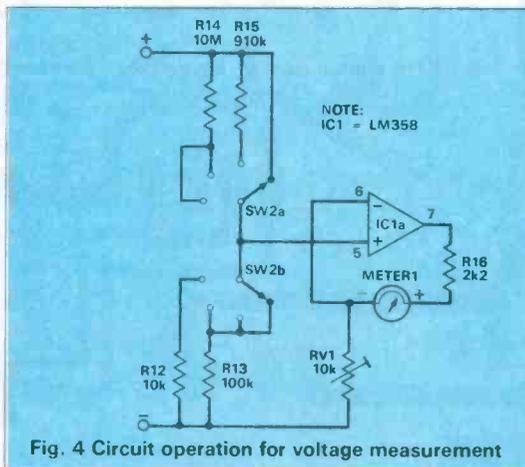


Fig. 4 Circuit operation for voltage measurement

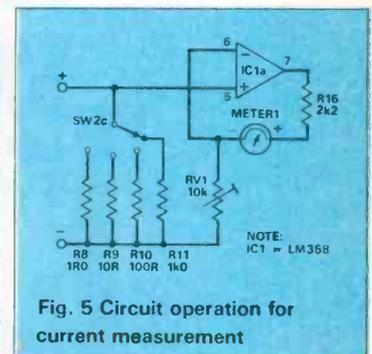


Fig. 5 Circuit operation for current measurement

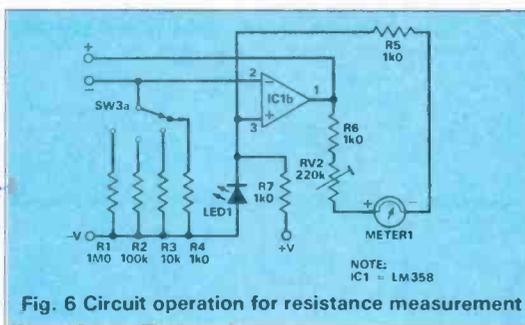


Fig. 6 Circuit operation for resistance measurement

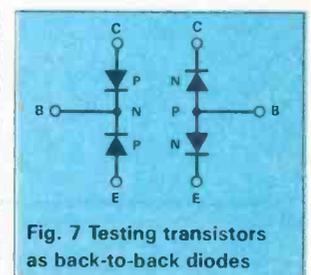


Fig. 7 Testing transistors as back-to-back diodes

You can also check transistors by regarding the silicon sandwich as a pair of diodes and testing accordingly. Figure 7 shows which way the diode equivalents are orientated for NPN and PNP types.

To test a thyristor, connect the positive test lead to the anode and the negative to the cathode. The meter should read high resistance. Momentarily short the anode to the gate and the resistance should go low — even when the gate voltage has been removed.


BUYLINES

All components for the multimeter are easily obtainable from Maplin (tel: (0702) 554161), Rapid Electronics (tel: (0206) 751166), or Electromail (tel: (0536) 204555).

The PCB is available from the ETI PCB Service (see centre pages).



PCB FOIL PATTERNS

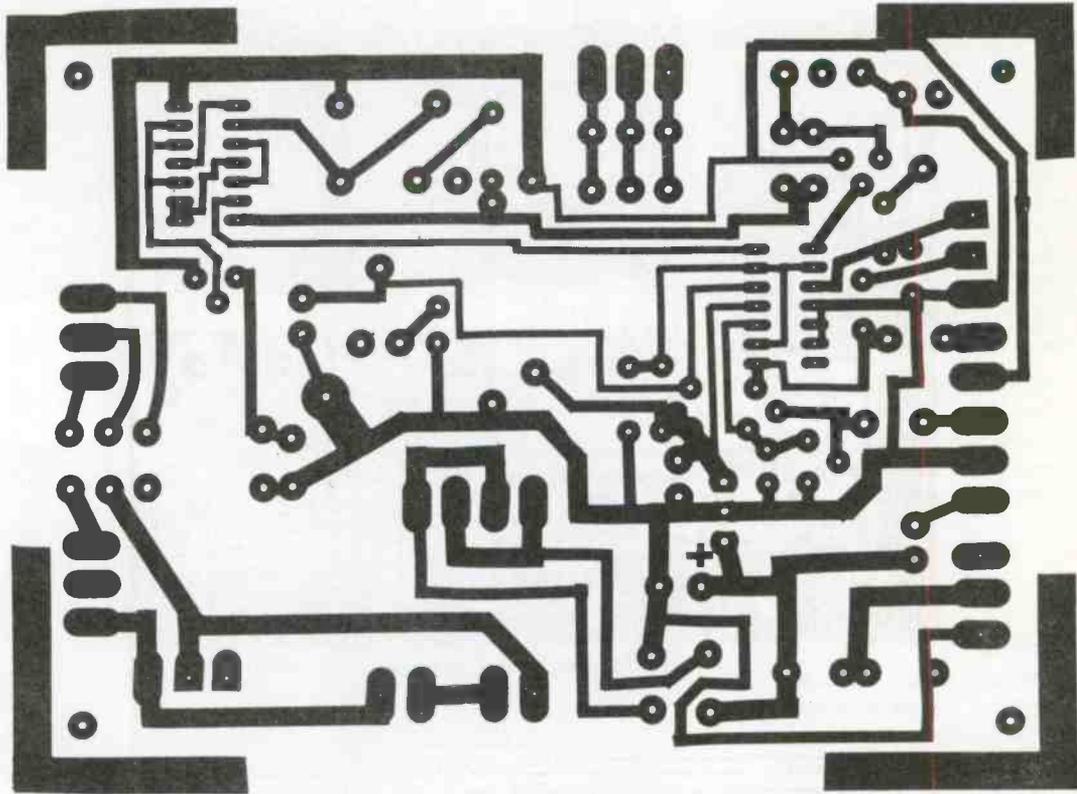


The Intruderbeam Control Unit foil pattern



Field Power Supply for the Spectrum 3 (September 1989)

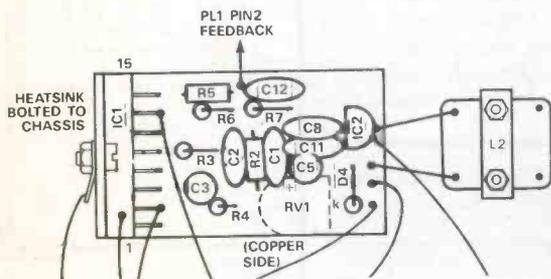
In last month's issue, a design error led to the component overlay being published with the printing densities reversed, rendering it rather difficult to interpret. The board is reproduced here with the error rectified.




Coil Winding Data

Coil	Turns	SWG	Gap in inches	Inductance at I _{DC}
L1	30	18	0.013	200 μ H at 700mA
L2	100	22	0.013	2mH at 50mA
L3	15	18	0.013	40 μ H at 2.5A
T1 _{prim}	30	18	0.013	200 μ H at 2.5A
T2 _{sec}	096	22	—	—

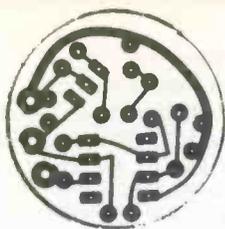
Another omission from the Field Power Supply was the coil winding data, which is shown here.




The Intruderbeam receiver foil

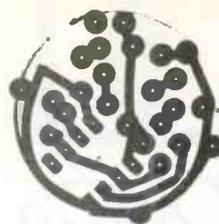

The Intruderbeam transmitter foil

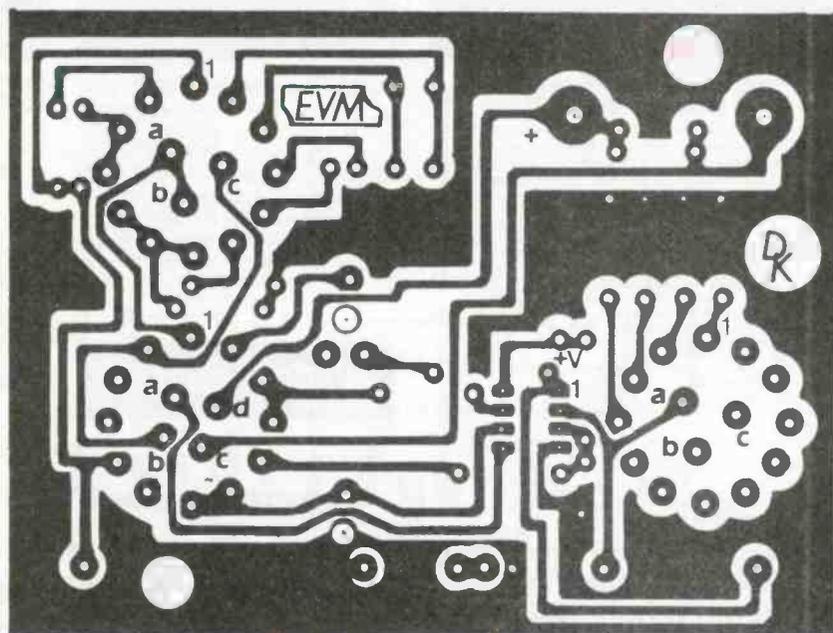

The Multimeter foil pattern

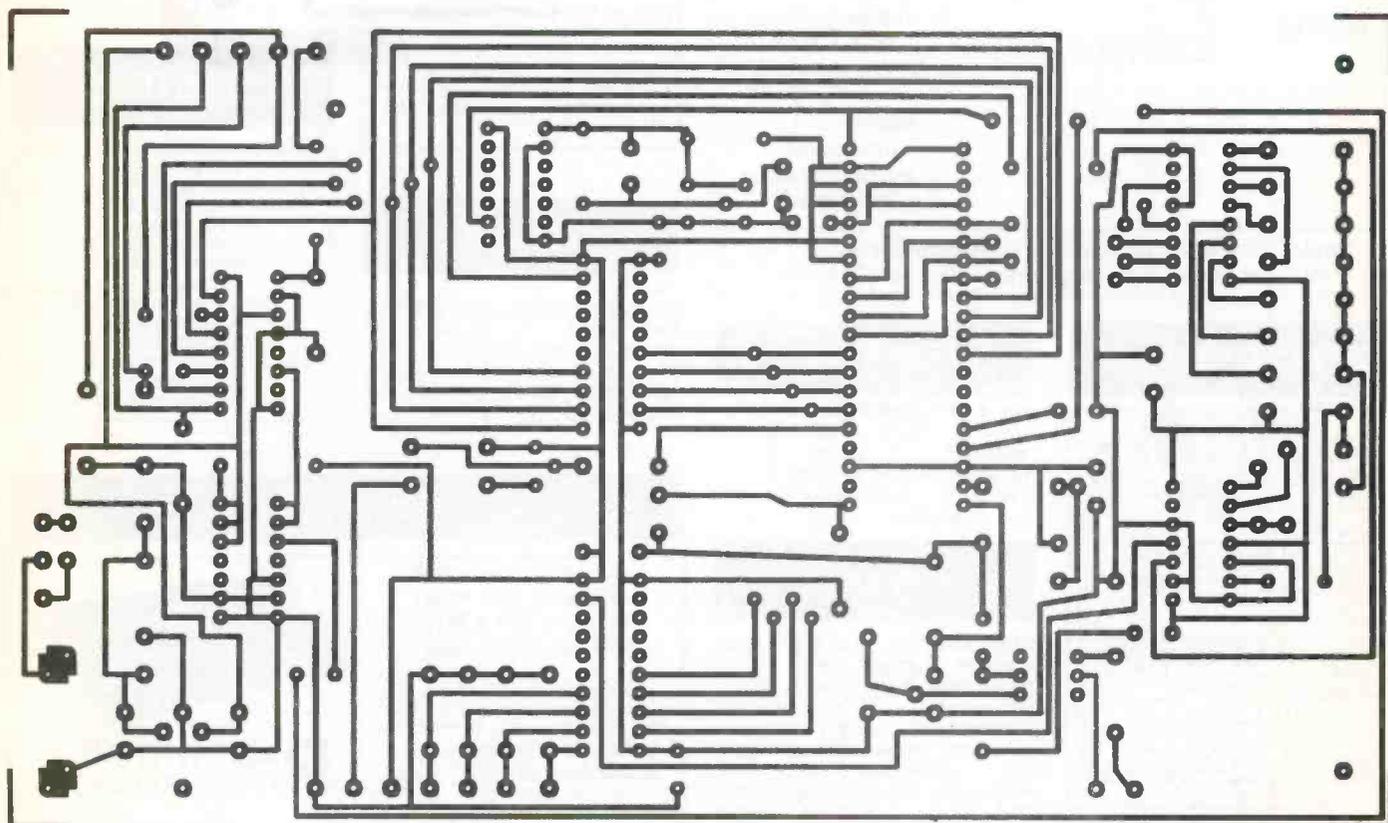

The MIDI Mapper foil pattern

ETI

ELECTRONICS TODAY INTERNATIONAL



CLASSIFIED

CAS GILROY
0442 66551 Ext 314

Send your requirements to:
**ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST.**

Lineage: 50p per word (+ VAT) (minimum 15 words)
Semi Display: (minimum 2 cms)
£13.50 per single column centimetre + VAT

Ring for information on series bookings/discounts
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

COURSES

MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice.
(Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio and TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Electrical Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
GCE over 40 'O' and 'A' level subjects <input type="checkbox"/>	

ICS Name _____ P. Code _____
Address _____ P. Code _____
International Correspondence Schools, 312/314 High St., Sutton, Surrey SM1 1PR.
Tel: 01-643 9566 or 041-221 2926 (24 hrs.) Dept EBS89

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on **0626 779398** (Ref: ETI/9/89)

Name _____	<input type="checkbox"/> Telecomms Tech C&G 271
_____	<input type="checkbox"/> Radio Amateur Licence C&G
_____	<input type="checkbox"/> Micro-processor
_____	<input type="checkbox"/> Introduction to Television

Radio & Telecommunications Correspondence School
12 Moor View Drive, Teignmouth, Devon TQ14 9UN

SPECIAL OFFERS

JPG Electronics

Resistors 1w 5% carbon (E12) 1p, 1% metal film (E24) 3p
Resistor Pack 85 different E12 values + zero ohm link, total content 1,000 resistors £8.95
LED's red or green 3mm or 5mm 6p each, Yellow 11p each
Cable ties 75mm 1p each, £3.95 per 1,000; £49.50 per 10,000
Stepping motor 4 phase 12v 7.5 step 500r/min £8.95
SAA 1027 stepping motor driver chip £3.95
Miniature FM transistor kits £7.94
Computer grade capacitors with screw terminals 5000uf 50v £4, 4700uf 63v £1.50, 33000uf 20v £1.95, 87000uf 10v £1.50, 7 segment C anode LED display 12mm £0.45
LM2931AT50 low drop out 5v regulator TO220 package £0.65
BS250 P channel MOSFET £0.45
BC159 transistor TO92 PNP £3.95 per 100
74LS05 hex inverter £10.00 per 100
AM27502/DC memory £1.50
Sanyo LHMWFM tuner, pre-amp assembly complete with volume knob, cones and tuning scale Brand new in maker's carton £5.95. Faulty £1.95.
Circuit diagram, description and setting up procedure for tuner assembly described above £1.50
Motor star capacitors 15uf 140vac £1.50
40uf 370vac £5.95; 4uf 250vac £1.95
LNE mains suppressor 2x5m+100mf £0.55
5 digit 8v electro. magnetic counter! £1.95
Oval 80mm speakers 136x70mm £0.80
Hour counter (loaded) 7 digit 240vac 50hz £0.95
LCD display 16 digit 7x5 dots dot matrix £2.50
Owerty keyboard 58 key uncasecd good quality switches £5.00
CMOS TTL 74 HC 74F linear transistor kits, capacitors, resistors, tools etc, always in stock.
Please add 75p p&p per order. VAT included

JPG Electronics,
276 Chatsworth Road, Chesterfield S40 2BH
Access orders (0246) 211202 — Callers welcome

FOR SALE

100 WATT POWERAMPS £7 — NEW! Fully assembled + leads, Directions
KIA-8 Cuncliffe Road, Ilkley
Hear it! Free Demo-cassette
£1.50 P&P.

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue. SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

KITS

NEW VHF MICROTRANSMITTER kit, tuneable 80-115MHz, 500 metre range, sensitive electret microphone, high quality PCB. SPECIAL OFFER complete kit ONLY £5 POST FREE. Access orders telephone 021-411 1821, cheques/PO's to: Quantek Electronics Ltd, (Dept ETI), 45a Station Road, Northfield, Birmingham B31 3TE.

MISCELLANEOUS

HEATHKIT U.K. Spares and service centre Cedar Electronics, (HR), Unit 12 Station Drive, Bredon, Tewkesbury, Glos. Tel: 0684-73127.

FOR SALE

A&G ELECTRONICS LTD

If you are buying Electronic Components elsewhere you are almost certainly paying too much! Write to us for a free 1989 catalogue and start saving money.
(Please send two 19p stamps towards postage)
100 Park Avenue, London E6 2SR
Tel: 01-552 2386

SWITCHES

VOICE/SOUND ACTIVATED SWITCHES easy to follow diagrams and uses only £1.00. Components and P.C.B's available: **Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.**

EQUIPMENT

WOULD YOU BUY A CAR WITHOUT A TEST DRIVE? THEN WHY BUY A MIXER WITHOUT A TEST DRIVE?

Thinking about a new project — from a small Mixer to a large studio complex — come and talk over ideas with the people who offer manufacturing and user experience at our new premises:

Unit D, 318 High Road, Benfleet, Essex SS7 5HB

TO TAKE THAT TEST DRIVE —
PHONE 0268-793381
(Weekend Committee visits welcome by prior arrangement)



PARTRIDGE ELECTRONICS

Head Office, 56 Fleet Road, Benfleet, Essex SS7 5JN
Telephone 0268-793256

SURVEILLANCE

SURVEILLANCE & COUNTER SURVEILLANCE EQUIPMENT

WE MANUFACTURE AND SUPPLY TOP QUALITY SURVEILLANCE AND SECURITY EQUIPMENT



including VHF Transmitters
Automatic Telephone Recorders, Recording Briefcases, Bug Detectors, Telephone Counter-Tap Units
We also offer a complete range of accessories.

Including microcassette recorders, microphones, receivers, cassettes and batteries

CCTV AND SECURITY SYSTEMS SPECIALISTS

Write or phone for a detailed catalogue to:

ESKAN ELECTRONICS LTD.
DEPT. ET. 172 CALEDONIAN ROAD, LONDON, N1

1-278 1768

WANTED

Turn your surplus transistors, ICs etc, into cash. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance.

Contact:
COLES HARDING & CO.
103 South Brink
Wisbech, Cambs.
NOW ESTABLISHED OVER 15 YEARS
Tel: 0945 584188
Fax Number: 0945 588844

NEXT MONTH

NOVEMBER ETI — OUT OCTOBER 6th

Inside the November issue he found Paul Chappell's study of counter-surveillance, how to spot the bugs and have you watching them watching you. He found an in-depth explanation of neural networks and their development to the cutting edge of computing. A project to make a serial logic scope for stand-alone data stream monitoring. A smoke-alarm to protect the citizens from harm. The next installment of the *Testing Testing* series. Plus more projects and features than any superhero had a right to expect.

Together with the latest news, reviews and comment on the worlds of audio, computing, music and communications, the November issue of ETI is indeed a superhero among its fellow magazines.

The superhero sat on the ventilation shaft and looked out over the city. He adjusted the elastic of his undies over his latex laggings. Things weren't the same anymore, he thought. Business was bad. Seems no-one wanted a superhero unless he was psychologically disturbed and sinister-looking, rubber bathood and all. Whatever happened to a friendly smile, a cheery quip and that all-important cute hair-curl? The fist-fights and the superpowers? Where were you when the good guys gave you worse wobbles than the bad ones? Standards were definitely slipping in the superhero business.

He sighed and adjusted the volume in his superhero listening device, adapted from one of the surveillance circuits in the October issue of ETI. Just because Batman was mega-rich, it didn't mean he had all the best equipment. For just £1.50, ETI provided all the technical innovation that this superhero required. Why, he had already successfully used October's Intruderbeam to capture the legendary arch-criminals the Pelican, the Jolly Green Giant and Bonnie Langford, as they worked together in a sinister plot to make a new series of The Hot Shoe Show. What a publicity coup that capture should have been — but strangely the city media baron Bruce Wayne had refused to run the story. People wanted more bats, he had said.

Dawn broke through the clouds, filtering down through the smog and lighting the packed skyline with an eerie orange glow. The superhero checked the date — October 6th! Publishing date for the November issue of ETI! He leapt from the parapet into his Superheromobile and headed to the newsagent.



The above articles are in preparation but circumstances (or the Pelican) may prevent publication

ADVERTISERS INDEX

AUDIO ELECTRONICS	23	MAPLIN	OBC
AUDIO KITS	58	MERLIN	23
BK ELECTRONICS	IFC	NUMBER ONE SYSTEMS	3
BRIAN PRICE ELECTRONICS	43	PC PUBLISHING	11
CRICKLEWOOD ELECTRONICS	3	PM COMPONENTS	43
DISPLAY	34	RADIO & TV	13
EMINENCE	58	SAGE AUDIO	43
GREENBANK ELECTRONICS	29	SOLEX	Insert
GNC	23	STEWARTS OF READING	58
HART ELECTRONICS	28	SUMA	9
HOBBYKIT	23	TK ELECTRONICS	IBC
J&N BULL	49	WILMSLOW AUDIO	9
M&B RADIO	29		

KITS & COMPONENTS

ELECTRONIC GUARD DOG



One of the best burglar deterrents is a guard dog and this kit provides the barking. Can be connected to a doorbell, pressure mat or any other intruder detector and produces random threatening barks. All you need is a mains supply, intruder detector and a little time.
XK125 £26.00

DISCO LIGHTING KITS



L100K 8-way sequencer kit will built into opto-isolated sound to light input. Only requires a box and control knob for complete £34.60
DL-000K 4-way chaser features bi-directional sequence and dimming 1kW per channel £21.00
DLZ1000K Uni-directional version of the above. Zero switching to reduce interference £11.80
DLA/1 (for DL & DLZ1000K) Optional opto input allowing audio 'beat'/light response 80p
DL3000K 3-channel sound to light kit, zero voltage switching, automatic level control and built-in mic. 1kW per channel £17.00

POWER STROBE KIT


Produces an intense light pulse at a variable frequency of 1 to 15Hz. Includes high quality PCB, components, connectors, 5Ws strobe tube and assembly instructions. Supply 240V ac. Size 80 x 50 x 45.
XK124 STROBOSCOPE KIT £15.00

SIMPLE KITS FOR BEGINNERS

Kits include all components (inc. speaker where used) and full instructions.
SK1 DDOR CHIME play a tune when activated by a pushbutton. £3.90
SK2 WHISTLE SWITCH switches a relay on and off in response to whistle command. £3.90
SK3 SOUND GENERATOR produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun. £3.90

SPECIAL OFFERS ON KITS FOR SCHOOLS AND TRAINING CENTRES
- contact Sales Office for discounts and samples

VOICE RECORD/PLAYBACK KIT

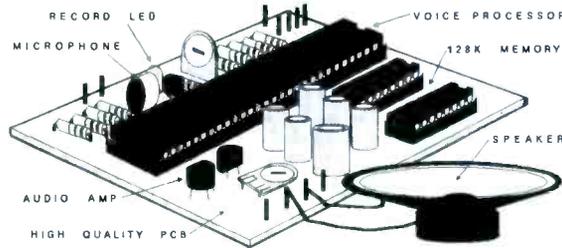

This simple to construct and even simpler to operate kit will record and playback short messages or tunes. It has many uses - seatbelt or lights reminder in the car, welcome messages to visitors at home or at work, warning messages in factories and public places, in fact anywhere where a spoken message is announced and which needs to be changed from time to time. Also suitable for toys - why not convert your daughter's £8 doll to an £80 talking doll!!

Size 78x60x15 mm
Message time 1-5 secs normal speed, 2-10 secs slow speed
XK129 £22.50


TEN EXCITING PROJECTS FOR BEGINNERS

This kit contains a solderless breadboard, components and a booklet with instructions to enable the absolute novice to build ten fascinating projects including a light operated switch, intercom, burglar alarm and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.
XK118 £15.00

MULTIMETER BARGAINS


A high accuracy Autoranging meter with Display Hold, Memory features.
AC volts 0-2-200-750 1.2%
DC volts 0-0.2-2-20-1000 0.8%
AC current 0-2m-200mA 1.2% 0-10A 2%
DC current as for AC
Resistance: 0-200-2K-20K-200K-2M 1%
Continuity Buzzer sounds at /20 ohms
Size 127x69x25mm
405 207 £31.75
A 15 range Autoranging multimeter with 4AC, 5DC and 6 resistance ranges. Only 8x55x108mm. Complete with wallet.
405 206 £19.50
Ask for a leaflet on our range of meters

ELECTRONIC WEIGHING SCALES

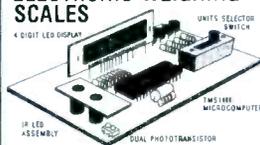

Kit contains a single chip microprocessor, PCB, displays and all electronics to produce a digital LED readout of weight in Kgs or Sts/lbs. A PCB link selects the scale - bathroom/ two types of kitchen scales. A low cost digital ruler could also be made.
ES1 £7.20


ELECTRONIC LOCK KIT

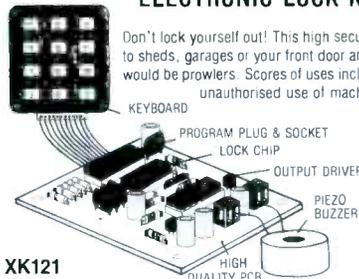

XK121
£15.95

Don't lock yourself out! This high security lock kit will secure doors to sheds, garages or your front door and the built-in alarm will deter would be prowlers. Scores of uses including area access preventing unauthorised use of machinery or even disabling your car. One correct 4 digit code (out of 5000) will open the lock. Incorrect entries sound the alarm and disable the keyboard for up to 3 mins. Kit includes 12-way keypad, and operates from 9 to 15V (50uA) supply. Will drive relay or 701 150 lock mechanism.

SUPER-SENSITIVE MICROBUG KIT

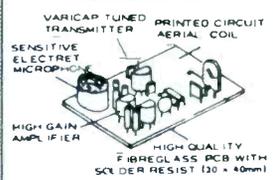

Only 45x25x15mm, including built-in mic. 88-100MHz (standard FM radio). Range approx. 300m depending on terrain. Powered by 9V PP3 (7mA). Ideal for surveillance, baby alarm etc. £5.50

VERSATILE REMOTE CONTROL KIT



Includes all components (+transformer) for a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can switch up to 16 items of equipment on or off remotely. Outputs may be latched to the last received code or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (exc. transformer) 9x4x2 cms. Companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available - MK9 (4-way) and MK10 (16-way).
MK12 IR Receiver £17.00
MK18 Transmitter £7.80
MK9 4-way Keyboard £2.40
MK10 16-way Keyboard £7.00
601133 Box for Transmitter £2.60

MICROPROCESSOR TIME

Kit controls 4 outputs independently switching on/off at 18 preset times over a 7-day cycle. LED display of time/day easily programmed. Includes box.
CT6000K 49.50

XK114 Relay kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £4.75
701115 Additional relays £1.80

TK ELECTRONICS

TK ELECTRONICS
13 Boston Road
London W7 3SJ
Tel: 01-567 8910
Fax: 01-566 1916

ORDERING INFORMATION. All prices exclude VAT. Free p&p on orders over £50 (UK only), otherwise add £1+VAT. Overseas p&p: Europe £3.50, elsewhere £10.00. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002. Local authority and export orders welcome. Goods by return subject to availability.



ORDERS: 01-5678910 24 HOURS

AMAZING LOW PRICE

SOLDERING IRONS

FLAME MASTER HOT GAS SOLDERING TOOL

Superb Pocket Size Portable Gas
Soldering Iron

ONLY
£12.95
FS130



★ Interchangeable Tips ★

- ★ Powered by Butane Gas
- ★ Simple to Refill
- ★ Temperature up to 400°C (750°F)
- ★ Up to 2 Hours Continuous Use

FLAME MASTER 5 IN 1 HOT GAS TOOL KIT

Complete with tough moulded to measure case and including:
MULTI-PURPOSE TOOL

- ★ 4 Interchangeable Soldering Iron Tips
- ★ Soldering Iron
- ★ Hot Cutting Knife
- ★ Wide Area Flame Torch
- ★ High Temperature Flame Torch
- ★ Hot Air Blower

GREAT FOR

- ★ Electrical and Electric Work
- ★ Cutting Plastics and Fibres
- ★ Sealing, Bonding and Shrinking
- ★ Removing Paint and Putty



ONLY
£19.95
FMK30

The Flame Master hot gas tool kit has many uses. It can be a soldering iron, a pencil flame torch, a hot air blower or a wide (flat) flame torch. You can fit the soldering head with a selection of soldering tips and the hot knife, or you can fit the flame head, onto which you can attach the hot blower or the wide flame unit. The choice is yours!

Post Your Order Now...

Order Coupon Send this coupon to P.O. Box 3, Rayleigh, Essex SS6 8LR

Quantity	Description	Code	Price

Name Add Carriage 50p
Address If order below £5 please add 50p
Post Code Total

I authorise you to debit my Credit Card account for the cost of goods despatched.

Credit Card No.


Access Amex Visa Delete as required.

If ordering by Credit Card please sign

Expiry date of Credit Card ETI

Maplin ELECTRONICS

CREDIT CARD HOTLINE

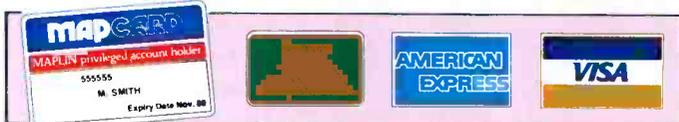

0702 554161

PHONE BEFORE 5PM FOR SAME DAY DESPATCH

ALL PRICES INCLUDE VAT.

All items subject to availability, both items will be on sale in our shops in Birmingham, Bristol, Leeds, Hammersmith, Edgware, Manchester, Nottingham, Southampton and Southend-on-Sea.